
39TH EDITION · 1962

The radio amateur's handbook

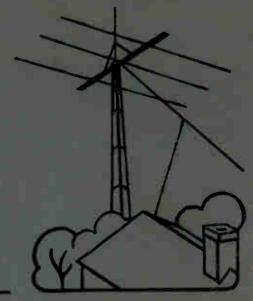THE STANDARD MANUAL OF AMATEUR
RADIO COMMUNICATION




\$3.50 U.S.A. Proper



UBLISHED BY THE AMERICAN RADIO RELAY LEAGUE

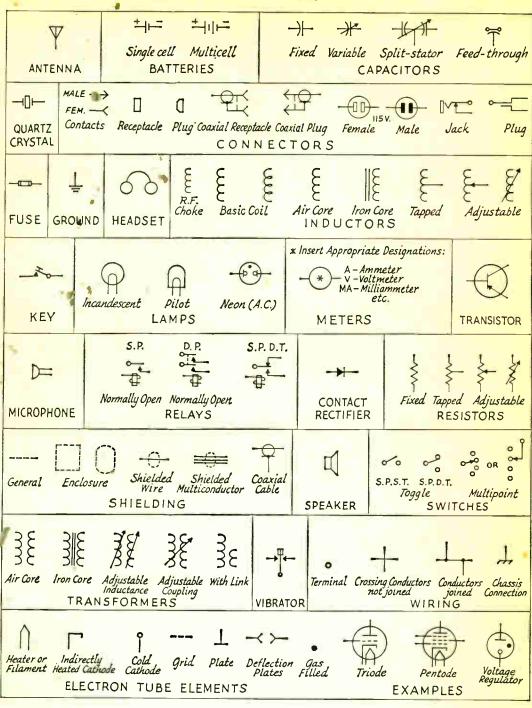SCHEMATIC SYMBOLS USED IN CIRCUIT DIAGRAMS



Where it is necessary or desirable to identify the electrodes or capacitors, the curved element represents the *outside* electrode (marked "outside foil," "ground," etc.) in fixed paperand ceramic-dielectric capacitors, and the *negative* electrode in electrolytic capacitors. In variable or adjustable capacitors (regardless

of dielectric), the curved line indicates the moving element (rotor plates).

In the case of switches, jacks, etc., only the basic combinations are shown. Any combination of these symbols may be assembled as required, following the elementary forms shown.

The new ideas in communications



hallicrafters

For the AM, CW and SSB operator the best for power,

TRANSMITTER. Preferred by the most experienced amateurs for SSB/AM/CW operation because of advanced features . . . beam-switching modulator with unusually high carrier suppression stability—CTO direct reading in kc., and complete 10-meter coverage.

FEATURES: Beam-deflection, high level sideband modulator for low-noise, high-stability signal, Hallicrafters' exclusive 5.0 Mc. quartz crystal filter with sideband rejection of 50 db. or more; CTO direct reading in kilocycles to within 1 kc.; 144 watts plate input (P.E.P. two-tone). Five band output (80, 40, 20, 15, 10 meters). All modes of transmission—CW, AM, SSB. Unwanted sideband down 50 db. or more. Both sidebands transmitted on AM Precision gear driven CTO. Exclusive Hallicrafters patented sideband selection. Logarithmic meter for accurately tuning and carrier level adjustment. Ideal CW keying and break-in operation, push-to-talk and full voice control system built in. Keying circuit brought out for teletype keyer.

FRONT PANEL CONTROLS, FUNCTIONS AND CONNECTIONS: Operation — power off, standby, Mox., Cal., Vox.—P.T.T. Audio level 0-10 R.F. level 0-10. Final tuning 80, 40, 20, 15, 10 meters. Function—upper sideband, lower sideband, DSB, CW. Meter compression. Calibration level 0-10. Driver tuning 0-5. Band selector—80, 40, 20, 15, 10 meters. High stability, gear driven VFO. Microphone, key and headphone monitor jacks.

TUBES AND FUNCTIONS: (2)-6146 Power output amplifiers. 6CB6 variable frequency oscillator. 12BY7 R.F. driver. 6AH6 2nd mixer. 6AH6 3rd mixer. 6AB4 crystal oscillator. 12AX7 voice control. Audio amp. 12AU7 audio amp, and carrier oscillator. 7360 modulator. 12AT7 sideband selecting oscillator. 6AH6 1st mixer. 6AH6 4.95 Mc. amp. 6AU6 9 Mc. amp. 5R4GY HV rectifier. 5V4G LV rectifier. OA2 voltage regulator.

REAR CHASSIS: Co-ax antenna connector, FSK jack, AC accessory outlet. Line fuse. Control connector, ground stud, AC power line cord. Cabinet 20" wide, 10½" high, and 17" deep. Approximate shipping weight 86 lbs. (Conforms to F.C.D.A. specifications.)

CW and SSB reception. Truly a deluxe receiver offering band pass filter front end—equivalent of four tuned circuits preceding first mixer—crystal-controlled, high frequency oscillator—5 step selec-

tivity plus exclusive upper-lower sideband selection—linear CTO, direct reading in kc. A perfect match for Hallicrafters' HT-32B and HT-33B exciters and transmitters.

FREQUENCY COVERAGE: Nine 500 kc segments covering 3.5-4.0 Mc.; 7.0-7.5 Mc.; 14.0-14.5 Mc., 21-21.5 Mc.; 28.0-30.0 Mc.; (4 segments); and WWV.

FEATURES: High order of mechanical and electrical stability; linear tuning; constant tuning rate; separate noise limiters for SSB/CW/AM; amplified dual loop AVC with fast attack-slow release; spurious signal and image rejection better than 60 db. 1 kc calibration marks; transmitter-type VFO with differential TC; 100 kc crystal calibrator; crystal controlled 1st and 3rd conversion oscillators; selectable sidebands; selectivity variable in five steps from 500 to 5000 cycles; product detector for SSB/CW envelope detector for AM; I.F. type noise limiter for SSB/CW automatic threshold series type for AM; band gain equalization: audio inverse feedbacks; "S" meter functions with AVC off.

SENSITIVITY: Less than 1 microvolt on AM-less than ½ microvolt on SSB/CW.

TUNING MECHANISM: Back-lash free gear driven tuning mechanism.

TUBES AND FUNCTIONS: 6DC6 R.F. amplifier – 6BA7 1st mixer – 12AT7 crystal oscillator – 6DC6 1st 1.F. amplifier—6BA7–2nd mixer—6CB6 VFO–6DC6 2nd 1.F. amplifier—6BA6 3rd mixer—12AT7 SSB switching oscillator—6DC6 3rd 1.F. amplifier—6BY6 product detector—6BJ7 2nd AVC, AM detector, ANL—12AX7 BFO 1st audio amplifier—6AQ5 audio output—6AU6 100 kc crystal cal.—6AU6 "S" meter amplifier—6AU6 1st loop AVC amplifier—OA2 voltage regulator-five silicon diodes.

FRONT PANEL CONTROLS: R.F. gain; A.F. gain; tuning; selectivity; function selector (upper-lower SSB; upper-lower AM; on-off switch); cal set lock; receive-standby switch; notch frequency; BFO pitch; AVC/ANL (AVC on-off; SSB/CW ANL; AM/ANL); antenna trimmer; band switch; calibrator on-off; headphone jack.

AUDIO OUTPUT IMPEDANCE: 3.2 and 500 ohms.

POWER REQUIREMENTS: 105/125V, 50/60 cycles AC 85 watts.

PHYSICAL DATA: 16" wide x 10½" high x 16" deep. Shipping weight 47 lbs.







HT-32E

SX-11

HT-33E

whose experience demands clarity and performance

htt-33B LINEAR AMPLIFIER. Famous for effortless power! Heavy duty components leave plenty of reserve even at the maximum legal limit for efficiency and long life (conforms to F.C.D.A. specifications).

FREQUENCY COVERAGE: Complete coverage of amateur bands; 80, 40, 20, 15, 10 meters.

FEATURES: Rated conservatively at the maximum legal input. Third and fifth order distortion products down in excess of 30 db. Built-in R.F. output meter greatly simplifies tune-up. All important circuits metered. Maximum harmonic suppression obtained through pi-network. Variable output loading. Protection of power supply assured by circuit breaker. HT-33B is a perfect match to Hallicrafters' famous HT-32B in size, appearance and drive requirements.

CIRCUIT DETAILS: This power amplifier utilizes a PL-172 high efficiency pentode operating in class AB1. The tube is grid-driven across a non-inductive resistor, thus assuring the maximum stability under all possible conditions. Band switching is accomplished by one knob which selects the proper inductance value for each band. The output circuit is a pi-network with an adjustable output capacitor, accommodating loads from 40 to 80 ohms. 2 panel meters are provided: one is circuit switched to measure grid current, screen current, plate voltage and R.F. output voltage. A second meter continuously monitors cathode current of the PL-172.

TUBES: (1) PL-172 high power pentode; (2) 3B28 rectifiers; (6) OA2 screen regulators.

FRONT PANEL CONTROLS: Meter selector; Filament switch; High Voltage switch; Bias adjustment; Bandswitch; Plate tuning; Plate loading.

PHYSICAL DATA: Gray and black steel cabinet (matches HT-32B) with brushed chrome knob trim. Cabinet: 20" wide x 10½" high x 17" deep. Shipping weight approx. 130 lbs.

REAR CHASSIS: Co-ax input; co-ax output; filament and bias fuse; cutoff bias relay terminals; screen fuse; ground terminal.

HA-4 "T.O. KEYER". The "Stradivarius" of electronic keyers. All-transistorized, compact design, employs digital techniques. Meets all the requirements of the perfectionist in CW operation. Size: 7½" long, 25%" high, 5¾" deep. Weight: 5 lbs.

R-47 SPEAKER. Specifically designed for communications. Compact, lightweight and beautifully styled. Flat response from 300 to 2850 c.p.s. Input impedance: 3.2 ohms. Size $5\frac{1}{2}$ " x $5\frac{1}{4}$ " x $3\frac{1}{4}$ ". Weight $2\frac{1}{4}$ lbs.


SX-101A RECEIVER. Far a d-vanced in technical features and performance. Known throughout the world as the "Heavyweight Champion" for ruggedness and dependability. Provides the sensitivity and selectivity you need.

FEATURES: Complete coverage of 80, 40, 20, 15, 10 meter bands plus a 2 and 6 meter conv. band; Dual scale "S"-meter functions with AVC off. Special 10 Mc. position for WWV. Dual conversion. Exclusive Hallicrafters' upper-lower sideband selection. Tee-notch filter. Full gear drive from tuning knob to gang condensers, 40:1 tuning knob ratio. 100 kc. evacuated marker crystal. Five steps of selectivity from 500 cycles to 5000 cycles. Direct coupled series noise limiter for improved noise reduction. Sensitivity—one microvolt or less on all amateur bands, 52 ohm antenna input. Antenna trimmer. Relay rack panel. Double spaced gang condenser.

FRONT PANEL CONTROLS: Main tuning knob. Crank knob for rapid scan, pointer reset, antenna trimmer, tee-notch frequency, tee-notch depth, sensitivity, band selector, volume, selectivity, BFO, response — (upper-lower sideband AM-CW). AVC on-off, AVC fast-slow, ANL Cal. Rec./standby.

TUBES AND FUNCTIONS: 6DC6, R.F. amplifier—6BY6, 1st converter—12BY7A, high frequency oscillator—6BA6, 1650 kc. 1.F. amplifier—12AT7, dual crystal controlled 2nd conversion oscillator—6BA6, 2nd converter—6DC6 50.75 kc. 1.F. amplifier—6BJ7 AM detector, ANL, AVC—6BY6 SSB/CW detector—6SC7 1st audio amplifier & BFO—6K6, audio power output—6BA6, "S"-meter amplifier—6AU6, 100 kc. crystal oscillator—OA2, voltage regulator—5Y3, rectifier.

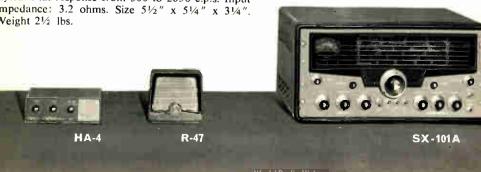PHYSICAL DATA: 20" wide, 10½" high and 16" deep—Panel size 8¾" x 19"—weight approximately 74 lbs. (Conforms to F.C.D.A. specifications.)





SSB equipment with the performance characteristics of the expensive rigs...at a price everyone can afford

the world famous HT-32B and put it in this precisionengineered AM/CW/SSB transmitter—same final amplifier, same rugged VFO construction and same VOX circuitry. The result—you get excellent performance characteristics for smooth, distortion-free speech quality at a very moderate price.

FEATURES: 144 watts plate input (P.E.P. two-tone); five band output (80, 40, 20, 15, 10 meters); all modes of transmission—CW/AM/SSB; unwanted sideband down 40 db. at 1 kc; distortion products down 30 db. or more; carrier suppression down 50 db.; modern styling; instant CW Cal. from any mode; both sidebands transmitted on AM; precision VFO; rugged heavy duty deluxe chassis; 52 ohm pi-network output for harmonic suppression; dual range meter for accurate tuning and carrier level adjustment; ideal CW keying; full voice control system built in.

FRONT PANEL CONTROLS, FUNCTIONS, CONNECTIONS: Operation—(power off, standby, mox, cal, vox); Audio gain; R.F. level; Final tuning: Function—(upper sideband, lower sideband, DSB, CW); carrier balance: Calibration level: Driver tuning; Band selector VFO; Microphone connector; Key jack.

TUBES AND FUNCTIONS: (2)-6146 Power output amplifiers; 6CB6 Variable frequency oscillator; 12BY7 R.F. driver; 6AH6 1st Mixer; 6AH6 2nd Mixer; 6AB4 Crystal oscillator; 12AX7 Voice control; 12AT7 Voice control; 6AL5 Voice control; 12AX7 Audio Amplifier; 12AT7 Audio amp and carrier Oscillator; 12AT7 Audio

Modulator; (2)-12AT7 Balanced Modulators; 5R4GY HV Rectifier; 5V4G LV Rectifier; OA2 Voltage Regulator.

REAR CHASSIS: Co-ax antenna connector; Line fuse; Control connector; AC power line cord.

PHYSICAL DATA: Matching unit for SX-111; cabinet is gray steel with brushed chrome trim and knobs. Size: 9" high x 191/4" wide x 151/2" deep. Shipping wt.; approx., 80 lbs.

essential characteristics of the durable SX-101A—yet in the price range that makes it a wanted unit in any shack. Sensitive is the word for its operation—rugged is the word for its dependability. Beautifully styled and precision built in the true Hallicrafters tradition of excellence in performance.

FREQUENCY COVERAGE: Complete coverage of 80, 40, 20, 15 and 10 meters in five separate bands. Sixth band is tunable to 10 Mc for crystal calibrator calibration with WWV.

FEATURES: AM/CW/SSB reception. Dual conversion, Hallicrafters' exclusive selectable sideband operation. Crystal-controlled 2nd converter. Tee-notch filter. Calibrated "S"-meter. Electrical calibration adjustment. Series noise limiter. Built-in crystal calibrator. Exceptional electrical and mechanical stability. Large slide-rule dial. Envelope detector for AM and product detector for SSB/CW.

SENSITIVITY: One microvolt on all bands. 5 steps of selectivity from 500 to 5000 c.p.s. **TUNING MECHANISM:** New friction-and-gear type with 48:1 tuning ratio. Virtually eliminates backlash.

CONTROLS: Tuning; CAL Reset; Antenna Trimmer; T-notch Frequency; R.F. Gain; A.F. Gain; Band Selector; Function (off-on, standby, upper or lower sideband, calibrate); AVC off-on; BFO off-on; ANL off-on; Selectivity. TUBES: 12 tubes plus voltage regulator and rectifier. 6DC6 R.F. Amplifier; 6BY6 1st converter; 6C4 Oscillator; 6BA6 2nd converter; 12AT7 Dual crystal controlled 2nd conversion oscillator; 6DC6 1650 kc. I.F. amplifier; 6DC6 I.F. amplifier (50 kc.); 6BJ7 AVC-noise limiter AM detector; 12AX7 1st audio and BFO; 6AQ5 Power output; 6BY6 Product detector; 6AU6 Crystal calibrator; 5Y3 Rectifier; OA2 Voltage regulator.

POWER SUPPLY: 105-125 volts, 50-60 cycle AC.

PHYSICAL DATA: Size: 1834" wide x 1014" deep x 834" high. Attractive gray steel cabinet with brushed chrome trim. Shipping weight approximately 40 lbs.

The HT-41 LINEAR AMPLIFIER. NEW and POWERFUL! Here is the low cost linear amplifier you've been looking for—with the capabilities of delivering the "Big" signal on the air! Ideally engineered with conservatively rated components. Ideal companion for the HT-37 in both styling and price.

FEATURES: Complete coverage 80 through 10 meters. Adjustable pi-network output. All important circuits metered. Built in R.F. output meter to simplify tune-up. Built in driver pad. Standby bias supply for complete cutoff during receive.

CIRCUIT DETAILS: This new high power linear amplifier employs two 7094 tetrode-type tubes. These tubes are connected as high Mu grounded grid triodes in Class B. Input circuit designed for 50 to 75 ohm exciters. A completely self-contained power supply uses 866A tubes connected in a full wave rectifier circuit possessing exceptional regulation. Provision also made to control cutoff bias by proper connections to terminal strip on rear of chassis. Overload protection provided by fuse which protects plate, filament, bias and blower circuits.

TUBES: (2) 7094; (2) 866A rectifiers.

FRONT PANEL CONTROLS: Filament switch; high voltage switch; meter switch; band selector; plate tuning; plate loading.

REAR CHASSIS: Co-ax input; co-ax output; AC line cord; plate, filament, bias and blower fuse; terminal strip for bias cutoff relay control and AC control circuits; terminal strip for internal input; grounding bolt and lug.

PHYSICAL DATA: 19¼" wide x 9" high x 15½" deep. Cabinet in gray steel with brushed chrome trim and knobs. Shipping wt.; 97 lbs.

HA-2—HA-6 TRANSVERTERS. A sensible, new approach to VHF operation! Engineered with the usual Hallicrafters precision, these transverters will convert your present 10-meter station to VHF... AM, CW, SSB, RTTY, FM capability. All modes of transmission and reception on your present equipment are useable with these units. A nuvistor front end in the receiver section provides excellent sensitivity and noise figure.

FEATURES: Converts received VHF signals down to 10 meters for reception. Converts 10-meter signal to VHF for transmission. 5894 tube in transmitter final amplifier can be driven up to 120 watts input. Can be driven by exciters with 10 to 100 watt capability. Built-in coaxial antenna relay.

FRONT PANEL CONTROLS AND FUNC-TIONS: Power on-off, range selector; tuning; loading; output indicator; plate current meter. **TUBES:** 12AT7 crystal oscillator; 6AH6 buffer amplifier; 6CW4 R.F. amplifier (REC.); 6AN4 mixer (REC.); 12BY7 mixer (Xmit); 6360 driver (Xmit); 5894 final amplifier.

REAR CHASSIS CONTROLS AND FUNC-TIONS: Receiver co-ax.; antenna co-ax fitting; transmitter co-ax. input hi.; transmitter co-ax. input low; power and control socket; bias adjust, filament and relay fuse; hi-voltage connector.

POWER REQUIRED: 750 volts @ 160 MA; 250 volts @ 70 MA; minus 60 volts @ 10 MA.

PHYSICAL DATA: 8" high x 17" wide x 8%" deep. Gray steel cabinet with silver trim.

MODEL P26—POWER SUPPLY. Hallicrafters power supply for these units supplies all voltages. Only one supply necessary for operation of either the HA-2 or HA-6 when used in stations set up for 6 or 2 meter operation.

R-48 SPEAKER. Modern design eliptical assembly, heavy magnet has fully saturated air gap for exceptional damping, distortion-free response. Switch at rear for selection of music or voice response. Use with SX-100, SX-110, SX-62A or any receiver with 3.2 ohm output. Handsome, gray steel cabinet, 65% high x 131/4" wide x 81/4" deep.



Now!-with Hallikitsbuild an economical high quality amateur band transmitter and receiver



HT-40 TRANSMITTER. Perfectly complements the high performance qualities of the SX-140 receiver. This crystal-controlled 75 watt transmitter has all the Hallicrafters design, quality and engineering features that are equally important to both beginners and old timers.

FEATURES: You get excellent CW performance as well as AM. Full band switching, 80 through 6 meters. Enjoy easy tune-up and crisp, clean styling that has efficient operation as well as appearance in mind. Unit is fully metered, TVI filtered.

SPECIFICATIONS: Maximum D.C. power input: 75 watts. Power output in excess of 35 watts CW, 30 watts peak AM phone. (Slightly less on 6

meters.) Frequency bands: 80, 40, 20, 15, 10 and 6 meters.

TUBES AND FUNCTIONS: 6DQ5 power output; 6CX8 crystal oscillator and driver; 12AX7 speech amplifier; 6DE7 modulator; silicon high voltage rectifiers.

FRONT PANEL: Function (AC off, tune, standby, AM, CW); Band Selector (80, 40, 20, 15, 10, 6); Drive control; Plate tuning, plate loading, Crystal-VFO; Grid Current; Meter; AC indicator light; R.F. output.

REAR CHASSIS: Microphone gain; antenna coax connector; remote control terminals; AC power cord.

SX-140 RECEIVER. It makes good operating sense to team up this quality-engineered receiver with the HT-40. In combination, these two units will give you an excellent performing station for a very modest investment.

FEATURES: You get complete coverage of all amateur bands 80 through 6 meters, with extremely high sensitivity and sharp selectivity. Unit has R.F. stage; S-meter; antenna trimmer; and crystal calibrator. Tuning ratio is 25 to 1.

CONTROLS: Tuning; Antenna Trimmer; Cal Reset; Function (AC off, standby, AM/CW/SSB); Band Selector; Cal on-off; R.F. Gain; Auto. Noise Limiter on-off; Selectivity/BFO; Audio Gain; phone jack; "S"-meter Adj.

TUBES AND FUNCTIONS: 6AZ8 tuned R.F. amplifier and crystal calibrator; 6U8 oscillator and mixer; 6BA6 1650 kc. I.F. amplifier and BFO; 6T8A 2nd detector, AVC, ANL and 1st audio; 6AW8A audio power amplifier and "S"-meter amplifier; (2) silicon high voltage rectifiers.

Both units available fully wired and factory tested.



HA-5 DELUXE VFO. A heterodyne-type VFO for all amateur bands, 80 through 2 meters. A 30 to 1 tuning ratio provides precision tuning.

FEATURES: Illuminated dial. Built-in spotting switch. Self-powered crystals supplied for 80 through 10 meters. (Crystals for 6 and 2 meters available from Hallicrafters.)

OUTPUT FREQUENCY RANGE: 3.5 Mc. to 4.0 Mc., 7.0 Mc. to 7.5 Mc., 8.0 Mc. to 8.222 Mc., and 8.333 Mc. to 8.833 Mc.

POWER SOURCE: 105V AC to 125V AC, 60 cycles.

TUBE COMPLEMENT: VFO and crystal oscillators, 6U8; mixer, 6BA7; output, 6AQ5; voltage regulator, OA2.

PHYSICAL DATA: 7" wide x 5" high x 8½" deep. Shipping weight: 8 lbs.

Time-proven, value-proven general coverage receivers







SX-100

SX-110

S-120 RECEIVER. World's most popular short wave receiver! Provides dependable per-formance in standard broadcast and three short wave bands. New, three-way antenna system for maximum flexibility. Clean, compact "look" of performance on the outside too!

FEATURES: Coverage of 540-1650 kc. plus short wave from 1650 kc. through 31 Mc.; Electrical bandspread; slide-rule dial with imprinted guide to frequencies of foreign, gov't., aviation, etc.; Three-way antenna system - built-in, high-gain ferrite loop for AM, 45" collapsible whip, plus terminals for long wire or doublet antenna, all bands; Front panel BFO/sensitivity control; built-in 5" speaker; front-panel headphone jack automatically disables speaker.

FRONT PANEL CONTROLS: Main Tuning;

Bandspread Tuning; Band Switch; Audio Vol. AC

Off; BFO/Sensitivity

TUBES AND FUNCTIONS: 12BE6 converter; 12BA6 1.F. amplifier/BFO; 12AV6 1st audio, AVC and detector; 50C5 power amplifier. Selenium rectifier. Thermistor heater regulator. Two dial lamps. 105-125V AC/DC at 30 watts. U/L

PHYSICAL DATA: Gray steel cabinet with bright chrome trim, black dial. Size: 13½" wide by 5%" high by 8¾" deep. Shipping wt.: 11¾ lbs.

SX-100 RECEIVER. Most versatile receiver of all! Has everything you need for allaround listening. Beautifully styled. Compactly

built—time-proven.
FREQUENCY COVERAGE: 540 kc.—34 Mc.— Band 1: 538 kc.-1580 kc.-Band 2: 1720 kc.-4.9 Mc.-Band 3: 4.6 Mc.-13 Mc.-Band 4: 12 Mc.-34 Mc. Bandspread dial is calibrated for the 80, 40, 20, 15 and 10 meter amateur bands. Intermediate frequency: 1650 kc. and 51 kc. TYPE OF SIGNALS: AM/CW/SSB.

FEATURES: Selectable side band operation. "Tee-Notch" Filter. Notch depth control. Antenna trimmer. 100 kc. crystal calibrator. Logging dials. Full precision gear drive. Second conversion oscillator crystal controlled - temperature compensation of high frequency oscillator. Phono jack. Socket for D.C. and remote control.

CONTROLS: Pitch control, reception, stand-by, phone jack, response control (upper and lower side band selector), antenna trimmer, notch depth, calibrator on-off, sensitivity, band selector, volume, tuning, AVC on-off, noise limiter on-off, band-spread, selectivity.

AUDIO OUTPUT IMPEDANCE: 3.2/500 ohms: AUDIO POWER OUTPUT: 1.5 watts with 10% or less distortion. POWER SUPPLY: 105/ 125 V., 50/60 cycle AC.

TUBE COMPLEMENT: 6CB6 R.F. amplifier; 6AU6, 1st converter; 6C4, H.F. oscillator; 6BA6, 2nd converter; 12AT7, Dual crystal second oscillators; (2) 6BA6, 50 kc. and 1650 kc. l.F. amplifiers; 6BJ7, AVC-DET-ANL; 6SC7, 1st audio and BFO; 6K6, Power output; 5Y3, Rectifier; OA2, Voltage regulator; 6C4, 1.F. amplifier—(51 kc.); Adul, 100 kc, crystal marker.

PHYSICAL DATA: Gray black steel cabinet

with brushed chrome knob trim, patterned silver back plate and red pointers. Piano hinge top. Size 183/8" wide x 81/2" high x 105/8" deep. Shipping weight approximately 42 lbs. (U.L. approved).

SX-110 RECEIVER. An all-purpose receiver with many of the most wanted features originally designed for the higher priced equipment.

FREQUENCY COVERAGE: Broadcast Band 540-1680 kc plus three short wave bands cover

1680 kc-34 Mc. FEATURES: Slide rule bandspread dial calibrated for 80, 40, 20, 15 and 10 meter amateur bands

and 11 meter citizens' band. Separate bandspread tuning condenser, crystal filter, antenna trimmer,

"S" Meter, one R.F., two I.F. stages.
INTERMEDIATE FREQUENCY: 455 kc.
TUNING ASSEMBLY AND DIAL DRIVE MECHANISM: Ganged, 3 section tuning capacitor assembly with electrical bandspread. Circular main tuning dial is calibrated in megacycles and

has 0-100 logging scale.

AUDIO OUTPUT IMPEDANCE: 3.2 and 500

TUBE COMPLEMENT: Seven tubes plus one rectifier: 6SG7, R.F. amplifier—6SA7, converter—6SG7, 1st 1.F. amplifier—6SK7, 2nd 1.F. amplifier—6SC7, BFO and audio amplifier—6K6GT, Audio output—6H6, ANL-AVC-detector—6Y3GT, rectifier.

AUDIO POWER OUTPUT: 2 watts. POWER SUPPLY: 105/125 V., 50/60 cycle AC. PHYSICAL DATA: Gray steel cabinet with brushed chrome trim. Size 1834" wide x 8" high x 101/4" deep. Shipping weight approximately 32 lhs


S-108 RECEIVER. Features the same basic performance characteristics as the SX-110 (above) without the "S" meter, antenna trimmer and crystal filter. Speaker built in



hallicrafters

communications are born at . . .

"Designed for Performance"®

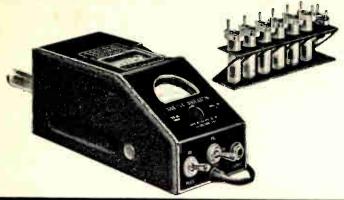

MILLEN NO. 90651 GRID DIP METER

The No. 90651 MILLEN GRID DIP METER is compact and completely self contained. The AC power supply is a the "transformer" type. The drum diat has seven call brated uniform length scales from 1,7 MC to 300 MC with generous over laps plus an arbitrary scale for use will special application inductors. Internal terminal strip per mits battery operation for antenna measurement.

No. 90651, with tube.....

	Addi	tional	Ind	luctors	for	lower	Frequencies	
No.	46702 -	- 925	to	2000	KC.			
No.	46703 -	— 500	to	1050	KC.			
No.	46704 -	-325	to	600	KC .			
No.	46705 -	— 220	to	350	KC.			
















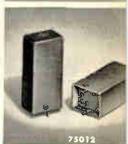

TONE MODULATOR ___ The No. 90751 Tane Modulator is a small IONE MODULATOK. Inc No. 70/31 tane magurator is a small package containing a transistor audio oscillator and its mercury battery, which plugs into the phone tack of a Grid Dip Meter to modulate the signal at approximately 800 cycles for applications requiring a modulated signal. Dimensions: anly 2½ x 1½ x 1½ is.

No. 90751, less bottery

AUDIO CLIPPER ___ The No. 75016 Audio Clipper is a small plug-in symmetrical type clipper with self-contained mercury batteries. It may be used to clip noise for C-W reception as well as for A-M or SSB, or it may be used to clip a sine wave input to form a square wave output. Dimensions: only 2½ x 1½ x 1½ in.

Na. 75016, less batteries

ANTENNA BRIDGE ___ The Millen 90672 Antenna Bridge is an accurate and sensitive bridge for measuring impedances in the range occurate and sensitive origage for measuring impedances in the range of 5 to 500 ohms (ar 20 to 2000 ohms with balun) at radio frequencies up to 140 mc. The variable element is an especially designed differential variable capacitor capable of high accuracy and permanency of calibration. Readily driven by No. 90651 Grid Dipper.

No. 90672

BALUNS -The No. 46672 (1 for each amateur band) wound Balun is an accurate 2 to 1 turns ratio, high Q auto fransformer with the residual reactances tuned out and with very tight caupling between the two halves of the total winding. The points of series and parallel resonance are selected so that each Bolun provides an accurate 4 to 1 impedance ratio over the entire band of frequencies for which it was designed. Suitable for use with the No. 06/27 Actual Paides. designed. Suitable for use with the No. 90672 Antenna Bridge ar medium power transmitters.

No. 46672-80/40/20/15/10

HIGH VOLTAGE POWER SUPPLY -The No. 90281 high voltage power supply has a d.c. output of 700 volts, with maximum current of 235 ma. In addition, a.c. filament power of 6.3 volts a 4 amperes is also available so that this power supply is an ideal uni for use with transmitters, such as the Millen Na. 90801, as well as general laboratory purposes. The power supply uses two No. 816 rectifiers. The panel is standard 834" x 19" rack maunting. No. 90281, less tubes

REGULATED POWER SUPPLY - A compact, uncased, regulated power supply, either for table use in the laboratory or for incorporation as an integral part of larger equipment. 250 v.d.c. unregulated at 115 ma. 105 v.d.c. regulated at 35 ma. Minus 105 v.d.c. regulated bias at 4 ma. 6.3 v. a.c. at 4.2 amps. No. 90201, with tubes.

HIGH FREQUENCY RF AMPLIFIER — A physically small unit capable of a power autput of 70 to 85 watts on Phone or 37 to 110 watts on C-W on 20, 15, 10, 6 or 2 meter amateur bands. Provision is made for quick band shift by means of the Na. 48000 series VHF plug-in cails. The No. 90811 unit uses either an 829-8 ar 3E29. No. 90811 with 10 meter band cails, less tube

PHASE-SHIFT NETWORK —A complete and laboratory aligned pair of phase-shift networks in a single campact $2'' \times 17/6'' \times 4''$ case with characteristics so as to provide a phase shift between the two networks of $90^{\circ} \pm 1.3^{\circ}$ aver a frequency range of 225 cycles to 2750 cycles. Well adapted for use in either single sideband transmitter or receiver. Possible to obtain a 40 db suppression of the unwanted sideband. The No. 75012 precision adjusted phase-shift network eliminates necessity of complicated lab equipment for network adjusted phase-shift network eliminates necessity of complicated lab equipment for network adjusted of the property of nates necessity of complicated lab equipment for network adjustment. No. 75012 ...

JAMES MILLEN

The No. 90923 oscilloscope is an extremely compact $(3\frac{1}{2})_2$ inches high) rock ponel general purpose ascilloscope utilizing the type $3XP-3 \times 1\frac{1}{2}$ inch rectangular face tube. The No. 90923 is complete with vertical and harizontal amplifiers for bolanced deflection and a very linear sweep generator.

Miniature input terminals are on both the front panel and the rear for vertical amplifier input, horizontal amplifier input and synchronizing input, The linear sweep generator covers two cycles per second to 30 kcs. per second in seven overlapping ranges. The trace is unusually sharp and bright due to 2040 valts accelerating palential.

The No. 90923 is ideally suited for many applications, and in particular, for production test, Its small panel uses up very little space in a test rack and the mu-metal shield around the cothode roy tube shields it against magnetic fields so that the oscilloscope may be used accurately in locations with strong stroy magnetic fields. The cothode ray tube is of the mana-occelerator type in which the electron beam is accelerated of the electron gan so that field distortions are minimized and excellent deflection linearity is achieved as well as a very uniform spot size over the entire area which the beam scons.

MILLEN NO. 90923 RACK MOUNTED OSCILLOSCOPE



















FLAT FACE OSCILLOSCOPE ____ 90905-8 5-inch Rock Mounting Bosic Oscilloscope features include: bolonced deflection, front ponel input terminols, rear ponel input terminols, ostigmatism control, blanking input terminols, flat face precision toleronce Dumont SADP1 tube.

BASIC OSCILLOSCOPES — The No. 90902, No. 90903 and No. 90905 Rock Ponel Oscilloscopes, for two, three and five inch tubes, respectively, or en inexpensive basic units comprising power suply, brillioncy and centering controls, sofety features, magnetic shielding, switches, etc. As a transmitter manitar, no additional equipment or accessories are required. By the addition of such units as sweeps, pulse generators, amplifiers, servo sweeps, etc., all of which can be expanded to serve any conceivable industrial or laboratory application.

POWER SUPPLY FOR OSCILLOSCOPE ____ 750 volts d.c. at 3 ma. and 6.3 volts a.c. at 600 ma. 117 volts 50-60 cycle input. Designed especially for use with No. 90901 and No. 90911 ane inch instrumentation ascilloscopes, $4\frac{1}{2}$ 6 in. high \times $1\frac{1}{2}$ 6 \times 2 Vg. Octol plug for input and output. Entire assembly including rectifier is encopsulated. No. 90202, Power Supply (complete)

BEZELS FOR CATHODE RAY TUBES — Standard types are of sotin finish black plastic. 5" size has neaprene support cushion and green lucite filter. 3" and 2" sizes have integral cushioning. No. 80075 (5") ... 80073 (3") 80072 (2") 80071 (1")

WORM DRIVE UNIT — Cost oluminum frome may be ponel or bose mounted. Spring looded split gears to minimize bock losh. Standard ratio 16/1, Also in 48/1 on request.

No. 10000 -- (state ratio)

RIGHT ANGLE DRIVE — Extremely compoct, with provisions for many methods of mounting. Ideal for operating potentiameters, switches, etc., that must be located, for shart leads, in remate parts of chassis. No. 10012

AMATEUR BAND MONITOR OSCILLOSCOPE

A-M or SSB 3.5 to 54 Mc.
Blanks out on Standby
Individual coil for each band

SCOPE — No. 90932 is a complete oscilloscope for monitoring the modulated rf output of a transmitter. Built-in link-coupled tuned circuits cover all amoteur bonds 3.5 to 54 mc. All circuits and accessories are built-in. The monitor will display the r-f envelope and/or the tropezoidal monitoring pattern of single side band transmitters or amplified modulated transmitters. It shows the linearity or non-linearity of Class-8 r-f amplifiers, the parasitic assillation, neutralization, and r-f autput,



2" round tube

- 1









TUBE SOCKETS DESIGNED FOR APPLICATION -TUBE SOCKETS DESIGNED FOR APPLICATION — MODERN SOCKETS for MODERN TUBES! Long Flashover path to chassis permits use with transmitting tubes, 866 rectifiers, etc. Lang leakage path between contacts. Contacts are type praven by hundreds of millions already in government, commercial and broadcast service, to be extremely dependable. Sockets may be mounted either with ar without metal flange. Mounts in standard size chassis hale. All types have barrier between contacts and chassis. All but actal and crystal sockets also have barriers between individual contacts in addition. addition.

Voltage regulator dual contact bayonet sacket, 33991 black phenolic insulation and 33992 with law loss mica filled phenolic insulation.

MILLEN TUBE SOCKETS

No.	Description		No.	Description	ın
			33004-4	Pin Tube :	Socket
		.487" x .095"		Pin Tube	
		1/2" x .125"	330066		
33302-	—Crystal Socket		33008-8		
			33991—S		
			33992-S		
			33207—8		
		Shield, ceromic	33305—A	corn Socke	et
33405-	—5 Pin Socket E	imoc			














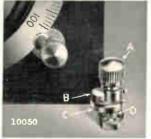



FLEXIBLE COUPLINGS - The No. 39000 series of Millen "De-FLEXIBLE COUPLINGS — The No. 39000 series of Millen "Designed for Application" flexible coupling units include, in addition to improved versions of the conventional types, also such exclusive original designs as the No. 39001 insulated universal joint and the No. 39006 "slide-action" coupling (in both steotite and bakelite insulation). The No. 39006 "slide-action" coupling permits longitudinal shaft motion, eccentric shaft motion and out-of-line aperation, as well as accorded the unitbook healths.

angular drive without backlash.
The No. 39005 and 39005-B (high torque) are similar to the No. 39001. he No. 37005 and 37005-8 (high torque) are similar to the No. 39001, but are not insulated. The steatite insulated No. 39001 has a special anti-backlash pivot and socket grip feature. All of the above illustrated units are for \(\lambda'' \) shaft and are standard production type units. The No. 39016 incorporates features which have long been desired in a flexible coupling. No Backlash — Higher Flexibility — Higher Breakdown Voltage — Smaller Diameter — Shorter Length — Higher Alignment Accuracy — Higher Resistance to Mechanical Shock — Solid Navalating Barcine Diameter — Shorter Length — Higher Alignment Accuracy — Higher Resistance to Mechanical Shock — Solid Navalating Barcine Diameter — Shorter Length — Higher Resistance to Mechanical Shock — Solid Insulating Barrier Diaphragm — Malded as a Single Unit.

CERAMIC PLATE OR GRID CAPS — Soldering lug and contact one-piece. Lug ears annealed and solder dipped to facilitate each combination "mechanical plus soldered" connection of cable.

No. 36001—1/4" No. 36002—1/4" No. 36004—1/4"

SAFETY TERMINAL — Combination high voltage terminal and thru-bushing Tapered contact pin fits firmly into canical socket providing large area, law resistance connection. Pin is swivel mounted in cap to prevent twisting of lead wire.

No. 37001, Black or Red No. 37501, Low loss

STEATITE TERMINAL STRIPS Terminal and lug piece. Lugs are turret type and are free floating so as not to strain L4 ceramic on wide temperature variations. Easy to mount with series of round holes. 1400 volt and 3500 volt series.

POSTS, PLATES, AND PLUGS - The No. 37200 series, in-POSTS, PLATES, AND PLUGS — The No. 37200 series, including both insulated and non-insulated binding pasts with associated plates and plugs, provide various combinations to meet most requirements. The posts have captive heads and keyed maunting. The No. 37291 and No. 37220 are standard in black or red with other colors on special order. No. 37201, No. 37202, and No. 37204 and No. 37222 are available in black, red, ar law loss. The No. 37202 is also available in startite.

also available in steatite.

Description Description No. No. -Single plates, pr. .37212—Dual plug.. 37291—Single plates (tapered), pr.37222—Non-insulated binding post37223—Insulated binding posts......

DIAL LOCK — Compact, easy to mount, positive in action, does not alter dial setting in operation! Rotation of knob "A" depresses finger "B" and "C" without imparting any rotary mation to Dial. Single hole mounted.


No. 10050.....

TUBE CLAMP — No. 33087 is easy to use, easy to install, effective in function. Available in special sizes for all types of tubes. Single hole mounting. Spring steel, cadmium plated.

"Designed for Application"®





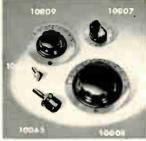



ANEL DIALS — The No. 10035 illuminated panel dial has 12 1 ratio, size, 8 ½" x 6½". Small No. 10039 has 8 to 1 ratio; size, "x 3½". Both are of compact mechanical design, easy to mount have totally self-contained mechanism, thus eliminating back of

nd hove totally self-contained mechanism, thus eliminating back of anel interference. Provision for mounting and morking auxiliary antrols, such as switches, potentiameters, etc., provided on the No. 3035. Standard finish, either size, flat black art metal.

MAFT LOCKS — In addition to the original No. 100%0 and No. 3061. "DESIGNED FOR APPLICATION" shoft locks, we can also interest to a summary of the No. 10062 and No. 10063 for easy numb aperation as illustrated above. The No. 10061 instantly constructed to the No. 10061 instantly constructed in the No. 10062 and No. 10063 for easy number of No. 10062 instantly constructed in the No. oin ''1/4 shoft' volume control, 'shoft locked' type. Eosy to mount.

DIALS AND KNOBS — Just o few of the mony stock types of small dials and knobs are illustrated herewith, 10007 is $1\frac{3}{8}$ " diameter, 10009 is $2\frac{3}{4}$ " and 10008 is $3\frac{1}{2}$ ".

HIGH VOLTAGE INSULATED SHAFT EXTENSION

No. 10061 shoft locks and the No. 39023 insulated high voltage potentiameter extension mountings are available as a single integrated unit — the No. 39024. The proper shoft length is independent of the panel thickness. The standard shoft has provision for screw driver. adjustment. Special shoft arrangements are available for industrial applications. Extension shaft and insulated coupling are molded as a single unit to provide occuracy of alignment and ease of installation. No. 39023, non locking type . No. 39024, locking type

















12000 and 16000 SERIES TRANSMITTING CONDENSERS

Rigid heavy channeled aluminum end plates, isolantite insulation, solished or plain edges. One piece rotor contact spring and connection lug. Compact, easy to mount with connector lugs in convenient

on tig. Comport, easy to mount with connector tugs in convenient occions. Some plate sizes as 11000 series above. he 16000 series has some plate sizes as 0.4000 series. Also has onstant impedance, heavy current, multiple finger rator contactor if new design. Both 12000 and 16000 series available in single and double sections and many capacities and plate spacing.

28000-29000 SERIES VARIABLE AIR CAPACITORS—
'Designed for Application,' double bearings, steatite end plates, admium or silver plated bross plates. Single or double section 022" or .066" oir gap. End plate size: 11/16" x 11/16". Rolar plate adius: 3/4". Shoft lack, reor shoft extension, special mounting prackets, etc., to meet your requirements. The 28000 series has emicircular rotor plate shape. The 29000 series has approximately teach the requirements. troight frequency line rotor plote shope. Prices quoted on request. Aony stock sizes.

NEUTRALIZING, CAPACITOR — Designed originally for use nour amount 9,0881 Power Amplifier, the No. 15011 disc neutraling capocitor has such unique features as rigid channel from, horizontol or vertical mounting, fine thread over-size lead screw with stop to prevent shorting and rotor lock. Heavy rounded-edged oluminum plotes are 2" diameter. Glozed steatite insulation. NEUTRALIZING, CAPACITOR -No. 15011

04000 and 11000 SERIES TRANSMITTING CONDENSERS

Another member of the "Designed for Application" series of trons-Another member of the "Designed for Application" series of transmitting variable air copacitors is the 04000 series with peak voltage ratings of 3000, 6000, and 9000 volts, Right angle drive, 1-1 ratio. Adjustable drive shoft angle for either vertical or sloping panels. Sturdy construction, thick, round-edged, polished aluminum plotes with 13/4" radius. Constant impedance, heavy current, multiple finger rator contactor of new design. Available in all narmal

The 11000 series has 10/1 ratio center drive and fixed angle drive

PERMEABILITY TUNED CERAMIC FORMS — In addition to the popular shielded plug-in permeability tuned forms, 74000 series, the 69040 series of ceramic permeability tuned unshielded forms ore avoilable as standard stock items. Winding diameters avoilable from 34," in 14" and winding space from 19," to 14" or 14".

from 716 to 72 one winding sp	oce from 1/32 to 1/2 .
No. 69041—(Copper Slug)	
No. 69042—(Iron Core)	No. 69054—(Iron Core)
No. 69043—(Copper Slug)	No. 69055(Copper Slug)
No. 69044(Iron Core)	No. 69056-(Iron Core)
No. 69045—(Copper Slug)	No. 69057—(Copper Slug)
No. 69046—(Iron Core)	No. 69058—(Iron Core)
No. 69047—(Copper Slug)	No. 69061—(Copper Slug)
No. 69048-(Iron Core)	No. 69062—(Iron Core)
No. 69051—(Copper Slug)	

"Designed for Application"

MINIATURIZED HIGH RELIABILITY VARIABLE CAPACITORS

MACHINED FROM SOLID BARS OF EXTRUDED BRAS! NO. 25000 SERIES

Modern demands for miniature precision, high Q variable air dielectric capacitors with high reliability require tha all of the stator plates be machined from a solid black a all of the storor plates be machined from a solid block a bross and that all of the rotor plates be machined from (solid black of bross, Staked, saldered, or washer-space; types of construction are adequate for larger capacitar, with wider air gaps but are entirely inadequate for minia

with wider air gaps but are entirely inacequate for minic ture high reliability copacitors for use at high frequencies. The stator terminal is an integral part of the stator. This results from extruding the exact shape required. The rota shaft is an integral part of the rotar, thus alignment a shaft with rator is perfect and there are na pins a press fits.

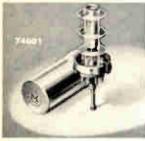
Special copacitors which con be monufactured using all or part of the tooling for standard capocitars are designed and manufactured to arder.

















TRANSMITTING TANK COILS -- A full line - all popular wattages for all bands. Send for special catalog sheet.

Nos. 42000, 43000, 44000, 48000.....

TUNABLE COIL FORM — Stondard octal base of low loss mica-filled bakelite, polystyrene $\frac{1}{2}$ " diometer coil form, heavy oluminum shield, iron tuning slug of high frequency type, suitable for use up to 35 mc. Adjusting screw protrudes through center hale of standard actol socket.

RF CHOKES — Many have copied, few have equalled, and nane have surpossed the genuine original design Millen Designed for Application series of midget RF Chokes. The more popular styles now in constant production ore illustrated herewith. Special styles and variations to meet unusual requirements quickly furnished.

No.	34100	_	2.5	mh.,	250	mo	No.	34105	_	1.0	mh.,	300	ma
No.	34101	_	2.5	mh.,	250	mo	Na.	34106	_	1.0	mh.,	300	ma,
No.	34102	-	2.5	mh.,	250	ma	No.	34107		1.0	mh.,	300	ma
No.	34103	_	2.5	mh.,	250	ma	No.	34108	_	0.1	mh.,	300	ma
No.	34104	_	2.5	mh.,	250	mo	No.	34109	_	1.0	mh.,	300	ma

MILLEN COIL FORMS - Mode of low loss mico filled brown bakelite. Guide funnel makes for easy threading of leads through pins.

Na	4.5000			
D. 1 -	45004			
INO.	43004	 	 	
	4.000			
No.	45005			

SPECIAL RF CHOKES — Figures 1 and 4 illustrate special type of RF chokes available on order. The popular 34300 and 34200 serie are shown in figures 2 and 3 respectively.

OCTAL BASE AND SHIELD — Law loss phenolic base with actol socket plug and oluminum shield can 1%6 x 1%8 x 31%6.

MINIATURE POWDERED IRON CORE RF INDUCTANCES .

The No. J300 — Minioture powdered iron core inductonces, 0.107 in dia. x 3% in. long. Inductances from 3.3 microhenries to 2.5 milli henries ±5%. ElA standord volues plus 25, 50, 150, 250, 350, 500 and 2500 microhenries. Three loyer solenoids from 39 to 350 microhenries. 1% in. wide single pi from 360 to 2500 microhenries. Specio coils on order.

PHENOLIC FORM RF INDUCTANCES - The No. 34300 in-PHENOLIC FORM KF INDUCTANCES — The No. 34300 Inductances — Phenolic coil form with axial leads. Inductances from 0.15 microhenry to 2.5 millihenries \pm 5%. ElA standard values plus 25, 50, 150, 250, 350, 500, and 2500 microhenries. Solenoids from 0.15 to 16 microhenries. Single pi from 18 to 300 microhenries. Multiple pi for higher inductances. Forms γ_{32} " dia. x γ_{16} in. lang, γ_{16} " x γ_{16} ", γ_{14} " x γ_{14} ", and γ_{14} " x 1". Special coils on order.

MINIATURE IF TRANSFORMERS — Extremely high Q — approximately 200 — Variable Coupling — (under, critical, and over) with all adjustments on top. Smoll size $1/l_0^{\prime\prime\prime} \times 1/l_0^{\prime\prime\prime} \times 1/l_0^{\prime\prime\prime} \times 1/l_0^{\prime\prime\prime}$ molded terminal bose. Air capacitor tuned. Coils completely enclosed in cup cores. Tapped primary and secondary. Rugged construction. High electrical stability.

Na.	61455,	55 kc. Universal Trans
No.	61453,	55 kc. BFO
Na.	61160,	600 kc. Universal Trons
No	61163	600 kc REO

LLEN



MINIATURIZED

DESIGNED for APPLICATION miniaturized components developed for use in our own equipment such as the 90901 Oscilloscope, are now available for separate sale. Many of these parts are similar, in most details except size, to their equivalents in our standard component parts group. In certain devices where complete miniaturization is not paramount, a combination of standard and miniature components may possibly be used to advantage. For convenience, we have also listed on this page the extremely small sized coil forms from our standard catalog.

CODE		- 1	DES	CRI	PTI	ON

A001 A006

A007 A008

DESCRIPTION

Bar knab for 'k' ' shaft. 'X' ' high by '%'' long.

Fluted black plastic knab with brass insert for 'k'' shaft.

'K' ' high by '%'' diameter.

'K' ' black plastic dial knab with brass insert for 'k'' shaft.

'K'' diameter dial. '\k'' high.

'M'' black plastic knab. Same as no. A007 except for style.

Right angle drive far '\k'' shafts. Single hale mounting.

1" bar dial far '\k'' shafts. Single hale mounting.

1" bar dial far '\k'' shafts. '\k'' high. 180° or 280° dials far clackwise or counter-clackwise ratation. A012 A014

clockwise or counter-clockwise ratation.

1" fluted knob dial for 1/6" shaft. 1/2" high. Same dial plates A015

as no. A014.

1½'' diameter fluted black plastic knab for ½'' shaft.

Knob, same as no. A007 except with ¾'' diameter

Knob, same as no. A007, but without dial. A017 diameter skirt.

A018 A019 A021

Miniature metal index far miniature dials. A0.50

Miniature dial lock, Shaft lock for 1/2" diameter shaft, 1/4"-32 bushing, Nickel plated brass.

Shaft lock with knurled lacking nut.
Shaft bearing for 1/4" diameter shafts. Nickel plated brass.
Fits 1/44" diameter hole. A062 A066

COMPONENTS

DESCRIPTION CODE

Steatite ceramic standoff or tie-paint, Integral mounting eyelet, 0.205" overall diameter. E001

Black or red plastic binding post plates for Na. E222. F201 Black or red plastic plates for two binding posts spaced 1/2". E202

Black or red plastic plug for two binding pasts spaced 1/2" E212 E222 Metal binding past with jack top.

to E306A Steatite ceramic terminal strips. 36" wide. Terminals spaced 36" an centers. Screw type or salder type E302A thru-terminals.

J300-3.3 to J300-2500 Camplete line of miniature inductances 3.3 to 2500 microhenries. %" long. Diameter 0.115" to 0.297".

Insulated universal joint style flexible caupling far 1/8" dia. M001

M003 M004

M005

shafts.
Salid caupling for ½" dia, shafts, Nickel plated brass.
Universal joint style flexible caupling for ½" diameter shafts, Inverted hubs for shart length. Not insulated.
Universal joint style flexible coupling for ½" diameter shafts.
External hub for maximum flexibility, Not insulated.
Universal joint style flexible caupling for ½" diameter shafts.
Spring finger. Steatite ceramic insulation.
Plastic insulated acupling with nickel plated brass inserts for ½" diameter shafts.
Plastic insulated flexible coupling for ½" diameter shafts. M006

M008

 γ_8 a alumerer snatts. Plastic insulated flexible coupling for V_8''' diameter shafts. $1\gamma_{21}'''$ long by $1\gamma_{31}'''$ diameter. Bronze yoke. Insulated shaft extension for $V_8'''',32$ bushing and V_8''' shaft for mounting sub-miniature potentiometer. M017 M023

M024

ror mounting sub-miniature potentiometer. Lacking insulated shaft extension similar to no. M023. Steatite ceramic coil form. Adjustable core. Winding space 1/3/2 (laimeter by 13/2 (long. Mounting 4-40 hale. Steatite ceramic coil form. Adjustable care. Winding space 0.187" diameter by 3/4" long. No. 10-32 mounting. 69043 69044

15



FOR EVERY APPLICATION

IMMEDIATELY AVAILABLE - FROM STOCK

Over 1,000 items to cover virtually every electronic application. . . . 400 Hermetic items, proved to MIL-T-27A, eliminate costly test delays. . . . Highest reliability in the field. . . . Immediately available from your local distributor. Write for catalog.
















HIGHEST

FIDELITY

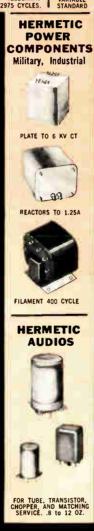PERMALLOY DUST TOROIDS HIGHEST Q, ACCURACY, STABILITY.















REPLACEMENT TYPES



And Special Units to Your Specifications

COMPLETE LINE OF AUDIO & POWER UNITS FOR COMMERCIAL EQUIPMENT

UNITED TRANSFORMER CORPORATION

150 Varick Street, New York 13, N. Y.

PACIFIC MFG. DIVISION: 4008 W. JEFFERSON BLVD., LOS ANGELES 16, CALIF. EXPORT DIVISION: 13 EAST 40th STREET, NEW YORK 16, N. Y. CABLES: "ARLAB"



The finest amateur equipment built...

YOUR PORTABLE HAM SHACK



Collins KWM-2 SSB Transceiver

This versatile single sideband transceiver serves both your fixed station and mobile needs on any fourteen 200-kc bands between 3.4 mc and 29.7 mc (except 5.0—6.5 mc). Crystals are provided for all HF bands except 10 meters where one crystal is supplied with provision for two additional crystals. Now you can move your ham station from the desk to the mobile mount in your car in minutes.

The compact, lightweight KWM-2 provides ample power on 80 through 10 meters with 175 watts PEP input on SSB, or 160 watts on CW. With a two-tone audio keyer and a converter unit, the transceiver may be adapted for RTTY use.

Filter-type SSB generation, Collins permeabilitytuned oscillator, crystal-controlled HF double conversion oscillator, VOX and anti-trip circuits, automatic load control, and RF inverse feedback are top features of the KWM-2.

The Collins 2.1-kc Mechanical Filter, RF amplifier, tuned circuits and several tubes perform the dual role of transmitting and receiving. CW break-in and monitoring sidetone circuits are built in. Four plugs in the mobile mount connect the KWM-2 automatically. A connector provides for antenna selection or loading coil selection for mobile operation.

The KWM-2 is easy to operate. The planetary 20-kc-per-turn knob allows accurate tuning. One-kc divisions on all bands provides ease of tuning and meeting schedules on frequency. Includes 100-kc crystal calibrator.

The KWM-2 weighs 18 lbs. 3 oz. and measures 7¾" H (including legs), 14¾" W, and 13¼" D. Mounts, accessories and power supplies are available for 12-v dc, and 115- and 230-v ac operation.



The finest amateur equipment built...

THE COLLINS S/LINE System Engineered to Give You the Finest in Fixed Station SSB Performance

For the advanced radio operator who wants the only system engineered fixed station available, Collins offers its famous S/Line. Based on a systems concept, each unit of the S/Line augments the others, giving you a complete single sideband station.

With the receiver and transmitter interconnected, the two may be operated as a transceiver. A frequency control switch provides for separation of transmit and receive tuning.

Finished in gray tones, with clean, smooth lines and front panels of dark gray simulated leather, Collins S/Line is equally welcome in your ham shack, den or family room. Each time you go on the air with a complete Collins S/Line, you are assured of the cleanest, clearest signal on the amateur bands.












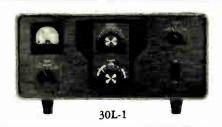

32S-1 Transmitter

The 32S-1 is an SSB or CW transmitter with a nominal output of 100 watts between 3.4 and 29.7 mc (except 5.0 to 6.5 mc). Crystals furnished cover HF amateur bands and 200 kc on 10 meters. Input power is 175 watts PEP on SSB or 160 watts on CW.

Features built into the 32S-1 include Mechanical Filter-type sideband generation; stable, permeability-tuned VFO; crystal-controlled HF oscillator; RF inverse feedback for better linearity; automatic load control for higher average talk power, and protection against flat-topping.

For ac operation, the 516F-2 Power Supply is used with the 32S-1; for 12-v dc operation, the MP-1 Power Supply may be used.

312B-4 Speaker Console

The 312B-4 provides a unitized control for the S/Line or the KWM-2. It houses a speaker, RF directional wattmeter with 200- and 2000watt scales, and switches for station control functions.

75S-3 Receiver

The 75S-3 provides SSB, CW and AM reception between 3.4 and 29.7 mc (except 5.0—6.5 mc) by selection of the appropriate HF heterodyning crystals. Crystals furnished cover HF amateur bands except the 10 meter band, where one crystal is supplied plus provision for two more.

Features incorporated in the 75S-3 include dual conversion with a crystal-controlled first heterodyning oscillator; bandpass first IF; stable, permeability-tuned VFO; RF amplifier designed to minimize cross modulation products; 2.1-kc Mechanical Filter and 200-cycle crystal filter; excellent AVC characteristics; both product and diode detector; rejection notch filter; manual and crystal BFO, and AGC time constant control. The advanced design of the 75S-3 includes the use of only 150 volts on vacuum tube plates, use of silicon diodes in lieu of conventional high vacuum rectifier; and the choice of three degrees of selectivity (also optional Mechanical Filters for AM). Provision for obtaining power from a dc power supply is also made.

With the new Collins 75S-3, you can be assured of the finest amateur receiver available for reception of the CW, SSB, or RTTY modes.

75S-1 Receiver

The 75S-1, designed primarily for SSB, incorporates such features as Collins famous frequency stability; dual conversion; 2.1-kc Mechanical Filter with provision for adding 500-cps Mechanical Filter for CW; AVC system tailored for SSB; silicon rectifiers, and provision for AM reception.

30S-1 and New 30L-1 Linear Amplifiers

The 30S-1 is a completely self-contained, single tube, grounded grid linear amplifier. Requiring 70 to 100 watts driving power (from the 32S-1 or KWM-2), it provides the full legal power input for SSB, CW or RTTY. The tube used is the Eimac 4CX1000A. The 30S-1 may be used on any frequency between 3.4 and 29.7 mc. A special comparator tuning circuit allows tune-up at low power to avoid exceeding the legal dc input of 1 kw. Push button selection of either linear amplifier or exciter output from the front panel. Antenna relay included. Conservatively rated.

The new compact 30L-1 Linear (the same size as the famous KWM-2) provides for 1000 watts PEP input on SSB (500 watts average dc) and 1000 watts average on CW, and has a self-contained power supply. It is designed to be driven by Collins KWM-1, KWM-2 or 32S-1, as well as from most other 70-100 watt CW/SSB exciters. The new unit also features RF inverse feedback; automatic load control; silicon rectifiers and a high/low power switch. Instant warm-up time. Automatic antenna switching from exciter to amplifier included.

Extended Frequency Versions of the S/Line

The 32S-1 and 75S-3 are available in extended frequency versions, designated the 75S-3A and 32S-2. The two differ from the original in that an additional crystal board has been added beneath the chassis. In this board is placed the standard complement of ham band crystals normally received with the equipment. The upper board is available for the placement of whatever additional crystals may be desired up to a total of 14. A front panel switch is added to allow switching between the two crystal boards.



The finest amateur equipment built . . .

COLLINS S/LINE AND KWM-2 ACCESSORIES





302C-3 Directional Wattmeter — Measures forward and reflected power on 200- and 2000-watt scales with accuracy and without calibrating adjustments. Coupler unit mounts separately from indicator-control box. Power loss and mismatch introduced by the instrument are negligible. Fixed or mobile applications.

351E Table Mounts — For mounting the S/Line and KWM-2 and accessories on planes, boats, etc. May be fastened to any flat surface. Front clamps attach to the feet of the units to hold them securely.

351D-2 Mobile Mount — Provides secure mounting for KWM-2 in most automobiles. Cantilever arms fold out of the way when the unit is removed. Mating plugs connect power, receive-transmit antenna, noise blanker antenna, speaker and antenna control as KWM-2 slides into place. Power Supply Cable included.

DL-1 Dummy Load — A 100-watt resistive load for all HF frequencies. Connects permanently in antenna coax line. Front panel or remote switch allows selection of "antenna" or "load." Provides easy comparison of antenna SWR and non-band interference tune-up. Will absorb 30L-1, 30S-1 outputs for short periods. Choice of Type N or RCA antenna connectors.

312B-5 Speaker Console and External PTO—Used with the KWM-2 in fixed station operation to provide separation of receive and transmit frequencies, speaker, directional wattmeter, plus switching for functional control of system. Styled to match KWM-2.

399C-1 Speaker and External PTO — Contains a speaker and a PTO (as in the 312B-5).

136B-2 Noise Blanker—An accessory for the KWM-2 for mobile operation. This noise blanker provides effective reduction of impulse-type noise—particularly ignition noise. Requires separate antenna resonant at 40 mc. Properly installed, this 136B-2 can be the difference between operating and not operating when around other cars.

312B-3 Speaker — Contains a 5" x 7" speaker and connecting cable. Styled to match receiver, transmitter.

516F-2 AC Power Supply — Operates from 115 v ac, 50-60 cps. Provides all voltage for the 32S-1 and KWM-2. Cabinet has provision for mounting a speaker styled to match the KWM-2.

MP-1 Mobile Power Supply — A transistorized inverter powered from a 12-v automobile, aircraft, or boat storage battery to the voltages required for operation of the KWM-1, KWM-2 or KWM-2A. Wiring cable is normally supplied with 351D-2.

440E-1 Cable — For use with MP-1 when the 351D-2 mount is not used. 22' long with plug to match KWM-2 on one end; provision for solder lugs on opposite end.

PM-2 Portable Power Supply — The new PM-2 is compact, lightweight, and provides all voltages needed for the KWM-2. Connects easily and quickly to rear of KWM-2. Operates from either 115 v ac or 220 v ac at 50-400 cps to provide a completely portable SSB and CW station. Contains a small speaker. The PM-2 and KWM-2 may be carried in the CC-2 carrying case, with a combined weight of less than 45 pounds.

MM-1 Mobile Microphone — A dynamic microphone designed to fit comfortably in your hand. A 5' length of coiled cord and attached PJ-068 is supplied with the 22-ounce microphone. For use with the KWM-2 or the S/Line. Push-to-talk switch. Hanger bracket furnished. Brushed aluminum finish. MM-2 Boom Microphone — A high-impedance reluctance microphone/single earphone combination for fixed or mobile operation. PTT not required; operates with VOX control. Sponge-padded headband clasps head firmly but lightly. Microphone boom and ear pipe adjustable for proper fit. Cord and attached plugs furnished.

CC-2 Carrying Case — Specially designed Samsonite Silhouette case for the KWM-2/PM-2 or 30L-1. Attractive molded Royalite interior protects equipment against rough handling. Two spare pockets.

MM-3 Boom Microphone — A high-impedance boom mike which has the same characteristics as the MM-2 except that there is no earphone built into the headset of the MM-3. Ideal for fixed station use where freedom of movement is desired.

SM-1 Desk-Top Microphone — A high-impedance, dynamic mike with styling and output level to match S/Line and KWM-2. Satin aluminum finish. Five-foot coiled cord and attached PJ-068 plug furnished.

351R-1 Rack Adapter — Matching gray rack panel with hardware for mounting 75S-1, 32S-1, KWM-2 or 30L-1. Supporting shelf holds unit securely.

351R-2 Rack Adapter — Matching gray rack panels with hardware for rack mounting S/Line and KWM-2 accessories, 516F-2, 399C-1, 312B-4 and 312B-5. Supporting shelf holds unit securely.


399B-4 Novice Adapter — Plugs into 32S-1 to provide four crystal-controlled channels for novice operation of 32S-1. Crystals not furnished. Removal of one 6146 reduces power of 32S-1 to proper level.

399B-5 Novice Adapter — Plugs into KWM-2 to provide four crystal-controlled channels on transmit. Receiver remains PTO tuned. Crystals not furnished. Removal of one 6146 reduces power of KWM-2 to proper input for novice use.

For further information on the Collins S/Line and accessories, see your nearest authorized Collins distributor or write: Amateur Sales, Collins Radio Company, Cedar Rapids, Iowa.



All that's new in PLASMA research

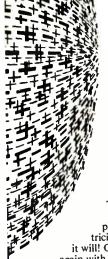

read December

Proceedings

for the facts!

No matter what your field in electronics, having a working knowledge of plasmas is greatly to your advantage. Why? Because plasmas are becoming increasingly important in electronics research and application.

Think of the major new developments in this field. Scientists are using gaseous plasmas to convert heat directly into electricity. Will this affect your work? Of course it will! Others are designing new vacuum pumps, again with gaseous plasmas helping to increase efficiency. Do you see the impact this will have on vacuum tubes, on a whole host of electronics products?

Much specialized research has been done on gaseous plasmas in the last few years. Much more is being planned. To catch up with it, you'd have to read a mass of technical papers. weed through conflicting theories, and often find at the end that the research is not pertinent to your work at all.

Realising this . . .

Proceedings of the IRE devotes its entire December issue to a survey of plasma research and findings to date... More than 15 technical papers, each one written by an authority, will spell out what plasmas are, how they behave, what they can do. Guest editor is Dr. E. W. Herold, Vice President, Research, Varian Associates.

Every special issue of *Proceedings* in the past has remained a definitive reference work for years. Many were sold out almost immediately. If you are not a member of the IRE, make sure of your copy of the December special issue on plasmas by sending in the coupon immediately.

Proceedings of the IRE

The Institute of Radio Engineers
1 East 79th Street, New York 21



more than 15 definitive papers covering the following areas of plasma research and application:

- 1 Fundamental plasma processes
- 2 Applications to communications
- 3 Electric power generation
- 4 Propulsion systems
- 5 Low density plasma explorations
- 6 Generation and amplification of oscillations in plasmas
- 7 Diagnostic procedures

The Institute	of Radio	Engineers
1 East 79th	Street, New	York 21

Please	send	me	the	December	1961	issue	of	Proceedings	of	the	IRE,
contain	ing a	sun	ev c	f the resea	rch c	arried	out	on plasmas.			

Enclosed is \$3.00 (for non-members only).*

Enclosed is company purchase order.

*Extra copies to IRE members, \$1.25 each (limit: 1 extra to a member).

NAME.....

COMPANY.

ADDRESS...



VIKING 1st

NAVIGATOR—40 watts CW input . . . also serves as a flexible VFO exciter. 6146 final amplifier tube—bandswitching 160 through 10 meters. Built-in VFO or crystal control. With tubes, less crystals. Cat. No. 240-126-1 Kit . . . Net \$149.50 Cat. No. 240-126-2 Wired, tested . . . Net \$199.50

adapter.
Cat. No. 242-103 10 Meter "Personal Messenger", 100 milliwatt, with 29,640 crystal, 8 penlight cell battery case... Net \$109.50 Cat. No. 242-104 10 Meter "Personal Messenger", 1 watt, with 29.640 crystal, 8 penlight cell battery case... Net to be Announced Cat. No. 251-806 Leather carrying case and strap... Net \$8.50 Cat. No. 250-804 Rechargeable nickel cadmium battery. Plugs into Cat. No. 250-804 Rechargeable nickel cadmium battery. Plugs into Cat. No. 250-804 Rechargeable nickel cadmium battery. Plugs into Cat. No. 250-804 Rechargeable nickel cadmium battery. Plugs into Cat. No. 250-804 Rechargeable nickel cadmium battery. Plugs into Cat. No. 250-804 Rechargeable nickel cadmium battery. Plugs into Cat. No. 250-804 Rechargeable nickel cadmium battery. Plugs into Cat. No. 250-804 Rechargeable nickel cadmium battery. Plugs into Cat. No. 250-804 Rechargeable nickel cadmium battery. Plugs into Cat. No. 250-804 Rechargeable nickel cadmium battery.

RANGER II—Now—a new version of the popular 75 watt CW or 65 watt AM "Ranger". The "Ranger II" transmitter also serves as an RF/audio exciter for high power equipment. Completely self-contained instant bandswitching 160 through 6 meters! Operates by built-in VFO or crystal control. High gain audio-timed sequence keying. TVI suppressed, Pi-nelwork antenna load matching from 50 to 500 ohms. With tubes, less crystals.

Cat. No. 240-162-1 kit.

Net \$249-50 Cat. No. 240-162-2 Wired, tested

Net \$359,50

VALIANT—275 watts input CW and SSB (P.E.P. with auxiliary SSB exciter) 200 watts phone. Instant bandswitching 160 through 10 meters—built-in VFO or crystal control. Pinetwork output matches antenna loads from 50 to 600 ohms. TVI suppressed—timed sequence keying—built-in low pass, audio filter—self-contained power supplies. With tubes, less crystals.

Cat. No. 240-104-1 Kft . . . Net \$349-50 Cat. No. 240-104-2 Wired, tested . . . Net \$439-50

FIVE HUNDRED—Full 600 watts CW—500 watts phone and SSB (P.E.P. with auxiliary SSB exciter). Compact RF unit designed for desk-top operation. All exciter stages ganged to VFO tuning—may also be operated by crystal control. Instant bandswitching 80 through 10 meters—TVI suppressed—high gain push-to-talk audio system. Wide range pi-network output. With tubes, less crystals. Cat. No. 240-500-1 Kit Net \$749.50 Cat. No. 240-500-2 Wired, tested . . . Net \$749.50



Write for FREE 4-page color brochure describing "Messenger", "Personal Messenger", antennas and accessories!



Choice Among Nation's Amateurs!



The world at your fingertips!

The world at your fingertips!

VIKING "KILOWATT" AMPLIFIER—The only transmitter that provides maximum legal power in all modes—SSB, CW, and plate modulated AM. Class C final amplifier operation provides plate circuit efficiencies in excess of 70% with unequalled broadcastipe high level amplitude modulation. Two 4-440A tubes in Class AB2 easily deliver 2000 watts P.E.P. (Iwice average DC) in SSB mode—provides 1000 watts input AM with two pushpull 810 tubes in Class B modulator service. 1000 watts input Closs B modulator service. 1000 watts input Circuit will match 50 to 500 ohm antenna loads. Pedestal contains complete unit. Excitation requirements: 30 watts RF and 10 watts audio for AM. 10 watts peak for SSB. With tubes.

Cat. No. 251-101-1 Matching accessory desk top, black and three-drawer pedestal . . . Net \$132.00



"COURIER"—Rated a solid 500 watts P.E.P. input with auxiliary SSB exciter as a Class B linear amplifier; 500 watts CW or 200 watts AM linear. Self-contained desk-top package—continuous coverage 3.5 to 30 mcs. Drive requirements: 5 to 35 watts depending on mode and frequency desired. TVI suppressed. With tubes and built-in power supply. Cat. No. 240-352-2 Wired ... Net \$289.50



"THUNDERBOLT"—The hottest linear amplifier on the market—2000 watts P.E.P. (twice average DC) input SSB; 1000 watts CW; 800 watts AM linear, Continuous coverage 3.5 to 30 mcs—instant bandswitching. Drive requirements: approx. 10 watts Class AB2 linear, 20 watts Class Continuous wave. With tubes and built-in power supply. Cat. No. 240-353-1 Kit. . Net \$524.50 Cat. No. 240-353-2 Wired . Net \$589.50



"6N2 THUNDERBOLT"—1200 watts (twice average DC) input SSB and DSB. Class AB1; 1000 watts CW. Class C: and 700 watts input AM inear. Continuous bandswitched coverage on 6 and 2 meters. TVI suppressed. DSI: requirements; approx. 5 watts Class AB1; inear, 6 watts Class C CW. With tubes and built-in- State County Cat. No. 240-362-2 Wired ... Net \$524.50 Cat. No. 240-362-2 Wired ... Net \$589.50

INVADER—More exclusive features than any other Transmitter/Exciter on the market today! Specially developed high frequency symmetrical, multi-section band-pass crystal filter for more than 60 db sidehand suppression—more than 55 db carrier suppression. Instant bandswitching 80 through 10 meters—no extra crystals to buy—no realigning necessary. Delivers solid 200 watts CW and P.E.P. SSB input; 90 watts input AM. Built-in VPC—exclusive RF controlled audio A6C and ALC (limiter type) provide greater average speech power. Wide range pi-network output circuit—extremely smooth. VOX and anti-trip circuits. Fully TVI suppressed. Self-contained heavy-duty power supply. Wired, tested, tubes and crystals. Net \$619.50


HIGH POWER CONVERSION—Take the features and performance of your "Invador"... add the power and flexibility of this unique viking "Hi-Power Conversion" system... and you're "on the air" with the "Invader 2000". Wired, tested, includes everything you need—no soldering necessary—complete conversion in one evening. Cat. No. 240-303-2 Net \$619.50

INVADER 2000—Here are all of the fine features of the "Invader", plus the added power and flexibility of an integral linear amplifier and remote controlled power supply. Rated a solid 2000 watts P.E.P. (twice average DC) input on SSB; 1000 watts CW; and 800 watts input AM! Wide range output circuit (40 to 600 ohms adjustable). Final amplifier provides exceptionally uniform "Q". Exclusive "push-pull" cooling system. Heavy-duty multi-section power supply. Wired, tested, power supply, tubes and crystals.

Cat. No. 240-304-2 Net \$1229.00



WASECA, MINNESOTA

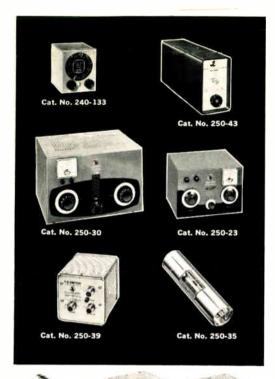



STATION ACCESSORIES

"MATCHBOXES"—Completely integrated antenna matching and switching systems for transmitters. Bandswitching 80 through 10 meters.

Cat. No. 250-23-3 275 watts, with directional coupler and indicator.

Net \$86.50 Cat. No. 250-23 Less directional coupler and indicator.

Net \$54.95 Indicator Net \$54.95 Cat. No. 250-30-3 Kilowatt, with directional coupler and indicator Net \$149.50

LOW PASS FILTER—Wired and pre-tuned.
Cat. No. 250-20 52 ohms impedance Net \$14.95
Cat. No. 250-35 72 ohms impedance Net \$14.95









Cat. No. 250-34

Cat. No. 250-42

Cat. No. 250-25

Cat. No. 250-28

Cat. No. 250-26

Cat. No. 114-310



Cat. No. 250-29









Cat. No.

POWER REDUCER—Up to 20 watts continuous dissipation with 100-150 watt transmitters, used as exciters for Viking "Kilowatt". Net \$13.55

ATTENUATORS—6 db attenuation with power dissipation to serve as exciters for Viking "Thunderbolt".

Cat. No. 250-42-1 for Viking "Ranger" Net \$21.50 Cat. No. 250-42-3 for HT-32 or similar unit . . . Net \$21.50

"SIGNAL SENTRY"—Monitors CW or phone signals up to 50 mc-without tuning. Energized by transmitter RF. With tubes. Cat. No. 250-25 Net \$22.00

CRYSTAL CALIBRATOR—Provide accurate 100 kc check points to 5 mc. with tube, crystal, power cable and extension lead. Cat. No. 250-28 Net \$17.95

DIRECTIONAL COUPLER AND INDICATOR—Provides continuous reading of SWR and relative power in transmission line.
Cat. No. 250-37 Coupler Net \$11.75
Cat. No. 250-38 Indicator Net \$25.00

PRE-TUNED BEAMS—With 3 elements, boom and balun matching

STANDARD KEYS-With Johnson "cushion-contact" design for

STANDARD NETS-WITH STANDARD ST

DELUXE SEMI-AUTOMATIC KEYS—Adjustable from lowest to highcets speeds. Smooth, easy action.

Cat. No. 114-500 % contacts, black wrinkle base . Net \$22.65

Cat. No. 114-501 % contacts, chrome base Net \$22.65

free catalog

Write today for our newest Amateur Catalog! Available nowcontains photos, schematics, and detailed specifications!

FIRST CHOICE AMONG THE NATION'S **AMATEURS**



It pays to insist on

crystals

STANDARD OF EXCELLENCE SINCE 1934

AMATEUR TYPES

Fundamental, PR Type Z-2

Frequency Ranges in Kcs.: 3,500 to 4,000 (80M); 7,000 to 7,425 (40M); 8,000 to 8,222 (2M); 8,334 to 9,000 (6M).

Rugged. Low drift, fundamental oscillators. High activity and power output. Stands up under maximum crystal currents. Stable,

Third Overtone, PR Type Z-9A

6 Meters, PR Type Z-9A

Fifth overtone; for operating directly in 6-meter band; hermetically sealed; calibrated 50 to 54 Mc., ±15 Kc.; .050" pins. \$4.95 Net

CITIZENS BAND CLASS "D" Type Z-9R, Transmitter

FCC assigned frequencies in megacycles: 26.965, 26.975, 26.985, 27.005, 27.015, 27.025, 27.035, 27.055, 27.065, 27.075, 27.085, 27.105, 27.115, 27.125, 27.135, 27.125, 27.125, 27.205, 27.215, 27.225, 27.255 calibrated to .005%. (Be sure to specify manufacturer and model number of equipment) \$2.95 Net CITIZENS BAND CLASS "D"

Type Z-9R, Receiver Specify I.F. frequency, also whether receiver oscillator is above or below transmitter frequency. Calibrated to .005%. (Be sure to specify manufacturer and model number of equipment.)____\$2.95 Net

Type Z-9R, Radio Control FCC assigned frequencies in megacycles: 26.995, 27.045, 27.095, 27.145, 27.195, 27.255; calibrated to .005%. (Be sure to specify manufacturer and model number of equipment.) \$2.95 Net

Type 2XP

2XP

Z-9R

Suitable for converters, experimental, etc. Same holder dimensions as Type Z-2.

1600 to 12000 Kc., (Fund.) ±5 Kc......\$3.45 Net 12001 to 25000 Kc. (3rd Overtone) ±10 Kc......\$4.45 Net

ALL PR CRYSTALS ARE UNCONDITIONALLY GUARANTEED.
ORDER FROM YOUR JOBBER.

COMMERCIAL TYPES

Commercial Crystals available from 100 Kc. to 70 Mc. Prices on request.

Type Z-1, MARS and CAP Official assigned frequencies in the range. Calibrated to .005%. 1600 to 10000 Kc.....\$3.45 Net

Type Z 1, TV Marker Channels 2 thru 13....\$6.45 Net 4.5 Mc. Intercarrier,

.01 % \$2.95 Net 5.0 Mc. Signal Generator,

.01 % \$2.95 Net 10.7 Mc. FM, IF, .01 %\$2.95 Net

Type Z-6A, Frequency Standard

To determine band edge. To keep the VFO and receiver properly calibrated. 100 Kc. . \$6.95



PETERSEN RADIO CO., Inc. 2800 W. Broadway COUNCIL BLUFFS, IOWA

EXPORT SALES: Royal National Corporation, 250 W. 57th Street, New York 19, N.Y., U.S.A.

FOR SALE: MEMBERSCRIPTIONS!

o, it's not a piece of ham gear, but every ham should have one. Nearly all active hams do, and even some nonhams have at least one in the family. It's not edible but it does give you something to chew on. Part of it is intangible, the other part is black and white, but should be read.

That is it? Shucks, OM—a memberscription is a combination membership in the American Radio Relay League and a subscription to QST magazine. It's an investment in goods and services that can't be duplicated anywhere for twice the price. It's an investment that pays dividends right from the first day and increases in value over a period of years.

The fellow who already has a memberscription well knows that his investment helps support an organization that represents his hobby at all international radio conferences, in the Congress, and before domestic regulatory agencies, an organization that publishes over a dozen books and booklets to help the beginner get started and the licensed ham advance himself, an organization that sponsors conventions, contests, and awards such as DXCC, WAS, and the RCC, and an organization that is completely governed and run "By and For the Amateur."

The biggest tangible dividend is QST magazine, pocked with the latest of everything, and delivered 12 times during each memberscription. When saved, back issues of QST make an unsurpassed and invaluable reference library of technical as well as historical data.

emberscribers: Sign up your friends, enemies, good ops, and bad ops (maybe exposure to QST will help them lose their LIDS). Whatever the motive, every ham should get a memberscription and join with nearly 100,000 others in working toward making ham radio a hobby we can all continue to enjoy and be proud of.

Memberscriptions only \$5 a year in the U.S., \$5.25 in Canada, and \$6 elsewhere

THE AMERICAN RADIO
RELAY LEAGUE, INC.

WEST HARTFORD 7, CONNECTICUT

More UHF Power for Mobile Applications



The air-cooled RCA-8121 and RCA-8122 high-perveance "tetrodes" offer more UHF power than ever in compact "low-cost" mobile communications. Featuring a 13.5-volt heater, these beam power tubes give dependable performance with battery operation. The RCA-8072 is a conduction-cooled version of the radiator types. These three unique types employing ceramic-metal construction represent another first from RCA for mobile use.

RCA CERAMIC-METAL TUBES FOR MOBILE USE

Typical CW Operation

Туре	Cooling	Maximum plate Dissipation	Plate Volts	Freq. Mc	Useful Power Output Watts			
8121	Conduction	100*	700	50 175 470	110 105 85			
8122	Forced-Air	150	1500	up to 500	235			
8072	Forced-Air	400	2000	up to 500	300			

*May be higher depending on heat-sink design.



The Most Trusted Name in Electronics

BEAM POWER for All Powers

Whether you're on SSB, AM, or CW—QRP or QRO—there's an RCA beam power tube for every amateur transmitter power level and for frequencies to

450 Mc and beyond.

Beam power tubes make it practical to build compactness into your rig. They do the job with fewer stages, less expensive components, fewer controls. RCA beam power tubes deliver the power with relatively low plate voltages. Thousands of commercial transmitters prove out these facts.

For more useable "transmitter watts" for your dollars, "Socket-up" with RCA beam power tubes. Check the chart at the right for the types you need—and order direct from your RCA Industrial Tube Distributor.

ruj		'Beam'' Po sted accord				Cation
RCA Type	Class of Service	Max. Plate- Input Watts	Max. DC Plate Volts#	Max. Freq. For full Input (Mc)	Max. useful Freq. (Mc)	Heater (H) or Filament (F Volts
5763	CW AM	17 15	350 300	} 50	175	6.0 (H)
6417	Same as	RCA-5763,	except fo	r heater vo	Itage	12.6 (H)
2E26	CW SSB AM	40 37.5 27	600 500 500	125	175	6.3 (H)
2E24	Same as	RCA-2E26	, but has c	uick-heatin	g filamen	6.3 (F)
6893	Same as	RCA-2E26	except fo	r heater vo	Itage	12.6 (H)
832-A*	CW .	50** 36**	750 600	} 200	250	6,3▲(H) 12.6●(H)
807	CW SSB AM	75 90 60	750 750 600	60	125	6.3 (H)
1625	Same as	s RCA-807, of medium	except for 7-pin base	heater vol	tage	12.6 (H)
6524*	SSB AM	85** 85** 55**	600 600 500	}100	470	6.3 (H)
6850*	Same a	s RCA-6524	, except fo	r heater vo	Itage	12.6 (H)
4604	CW	90	750	60	175	6.3 (F) quick-heati
6146	CW SSB AM	90 85 67.5	750 750 600	} 60	175	6.3 (H)
6883	Same a	s RCA-6146	except fo	r heater vo	ltage	12.6 (H)
829-B*	CW SSB AM	120** 120** 90**	750 750 600	} 200	250	6.3 ▲ (H) 12.6 ● (H)
7203/ 4CX250B	CW SSB AM	500 500 300	2000 2000 1500	500		6.0 (H)
7094	CW SSB AM	500 400 335	1500 2000 1200	} 60	175	6.3 (H)
813	CW SSB AM	500 450 400	2250 2500 2000	} 30	120	10 (F)

*Twin-Type **Total for both Units •For series-heater connection ▲For parallel-heater connection ■Max. Ratings for amateur use

For technical data on any of these types write RCA, Commercial Engineering, Section A-11-M, Harrison, N. J.



The Most Trusted Name in electronics

AT IN CONTRACT STREET CO.



A ELECTRON TON TON



M 115 11 11 1

INTRODUCING ...



THE BARKER & WILLIAMSON

Model 6100 TRANSMITTER



All New Design - Frequency Stability Superior to anything offered today -No free-running Oscillators!

- SSB . . . CW . . . AM.
- Frequency coverage: Amateur bands 80 thru 10 and most MARS frequencies.
- Sideband Attenuation better than 50 db.
- Carrier Suppression . . . 50 db or better.
- Distortion products down by 40 db.
- Power Input: CW 180 Watts . . . SSB 140 Watts PEP.

The (BW) 6100 is a NEW transmitter with NEW features — Establishing a NEW standard of performance.

BARKER & WILLIAMSON, Inc.

Radio Communications Equipment Since 1932

BRISTOL, PENNSYLVANIA • STILLWELL 8-5581



Grounded Grid Linear Amplifier

This smartly-styled full kilowatt package of power takes up no more table space than a receiver. Can be driven by commercial and home-built exciters in the 100-watt output class. Includes R.F. section complete with tubes, blower, filament and bias supply and optional input matching unit. Pinetwork output circuit for precise tuning and loading on 80-40-20-15-10 meters.

POWER SUPPLY UNIT LPS-1 Designed as companion to the LPA-1 for side-by-side installation or remote location. Switching panel removable for remote control. Full wave singlephase bridge rectifier with four Type 816 mercury vapor tubes included. Heavy-duty trans-R.F. filtering. former core stacks and superior highvoltage insulation for reliable, continuous operation at 1 KW.

COAXIAL TYPE SWITCHES



These switches are used for switching 52 or 75 ohm coaxial lines. By the twist of a knob test instruments, antennas, transmitters, receivers and many other devices may be switched in or out of a coax line circuit. SO-239 connectors are provided on Models 550A and 551A. Rating is 1KW amplitude modulated. Frequency range to 50Mc. Cross talk is

and 551A. Rating is 1KW amplitude modulated. Frequency range to 50Mc. Cross talk is .45db and .60db between alternate outlets at 30Mc. Size 4" overall x 2¼" depth. One inch shaft length. Shipping weight 2 lbs. Other models are available to order, including single and multiple gang units available to "N" and "phono-type" connectors as specified. specified.



BARKER & WILLIAMSON, Inc. BRISTOL, PENNSYLVANIA

TR SWITCHES — FOR 52-72 OHM COAX LINE

A self-contained unit that provides automatic changeover of antenna from receiver to transmitter or visa from receiver to transmitter or visa versa, with no signal loss. Ideal for break-in operation on CW and SSB or push to talk on AM phone. Model 381 has selectable bandswitching, providing high order of sensitivity and selectivity. Handles full legal limit of power on AM, CW and SSB. Model 380B is for medium power applications. Provides broadband circuitry to eliminate tuning and adjustment.



Model 381-Size 41/x x4"x51/2" Model 380B-Size5"x31/4"x31/2" Shipping wt. 5 lbs.

Shipping wt. 4 lbs.

TRANSISTORIZED POWER CONVERTERS AND INVERTERS

Reliable solid state, shock resistant DC to DC and DC to AC sistant DC to DC and DC to MC power units. They operate from 12 volts DC utilizing power tran-sistors as switching elements. Units eliminate vibrators and Units eliminate vibrators and rotating components, providing higher efficiency in a smaller package. They are ideal for all types of mobile equipment where high voltage DC from a 12 volt DC power source is required.

Max. size 4¼" x 5¼" x 3¼" Ship, wt. not over 1.5 pounds



PI-NETWORK INDUCTORS

Ultra-compact highly efficient and intergrally bandswitched, these pi-network inductor asthese pi-network inductor as-semblies incorporate novel de-sign features. They are designed for single or parallel tube opera-tion from 80 through 10 meters. Windings provide ample current carrying capacity. Maximum''Q'' over the entire operating range. Model 851 for 500 watt finals



FILAMENT CHOKES Grounded Grid Amplifier



Broadband characteristics from 80 Broadband cnaracteristics from over through 10 meters inclusive, requiring no tuning. Used with standard types of filament transformers. Cased the sturdy steel shells with mounting brackets. Two types available.

Model No. FC-15: for use with one or two tubes requiring a total of not more than 15 amps filament current. Dimensions: 1½" x 1½" x 4½".

Model No. FC-30: for one or two tubes requiring a total of not more than 30 amps filament current. Dimensions: $2'' \times 2^{i} 2'' \times 5''$.

600 GRID DIP METER



A highly sensitive, accurately calibrated instrument which can be used as an RF Signal Monitor, Auxiliary Signal Generator, and Absorbtion Wave-meter. The wedge shape makes it easy to handle.

> Plug-in coils are protected Pilg-in coils are protected by colored vinyl plastic sleeves. Sensitivity control permits adjustment for distinctive dips throughout entire 1.75 to 260 mc range. Overall size 3" x 3" x 7". Wt. approx. 2 lbs. Operates from 105-125 v-ac 50-60 cycles.

AUDIO PHASE SHIFT NETWORK



These components are for use in SSB suppressed carrier radio-telephone applications. No larger than a 615 tube, the model 350 consists of an octal base that fits into a standard an octal table socket. It is designed to split any audio signal, from 300 to 3,000 CPS, into two equal amptitude components which are $90^{\circ}\pm1.5^{\circ}$ out of phase with respect to each other. Model 350 Type 2Q4

CYCLOMETER TYPE COUNTER



For units that must be rotated in excess of 360° and reset to the same point. Available for 10 or 100 turns to within one-tenth of a turn. Front plate is 3" x 3". Depth from front of panel is 111/6". Either type available with a positive stop to limit the number of shaft rotations and a positive shaft lock. Price is determined by the shaft lock. Price is determined by the application. Standard finish is black crackle. Other finishes on special

10 Turn Cyclometer-Model No. 3901 100 Turn Cyclometer-Model No. 3902 Numbers decrease with clockwise rotation

Model No. 3902-1 Numbers increase with clockwise rotation.

MODEL 725 BALUN

A universal model handling 1KW on CW and 100% modulated AM phone, 4KW PEP on SSB.



Frequency range 1.5 to 30Mc. For use with any antenna having a 300 ohm feed point. VSWR better than 1.5:1 over entire range. Negligible insertion loss. Coaxial imput fittings. ceramic feed through output. Weather-proof steel case size 3½" x 4½" x 4½". Shipping weight 2½ pounds pounds.

LOW PASS FILTERS



1KW rating. Will reduce serious and unwanted radiation to a minimum of 85 db throughout the TV band and in excess of 100 db on channel "2". No tuning or adjustment required. The waveguide principle employed No tuning or adjustment required. The waveguide principle, employed in design of these units, permits a novel multi-section construction and assembly for greater altenuation in less space, at a lower cost. Units are equipped with SO 239 connector fiftings.

Model 425 for 52 ohm coax lines Model 426 for 75 ohm coax lines Shipping Weight 5 lbs. Size 11" x 2" x 3"

COAX ANTENNA CONNECTORS



Model CC50

These connectors provide a weather proof, mechanically strong connection between a coaxial feed line and proof, metalenance, proof of the center of a dipole antenna. It has an aluminum housing, rust proof eye-bolts and steatite insulation. Provision is made for internal soldered connections. Unit is furnished with rubber bushing for use with small coax cables and includes cement and instructions for installations. Size of both units 6½" x 5¾" x 1½". Shipping weight 2 lbs.

Model CCSI (Military Type)

Model CC51 (Military Type)

RF PLATE CHOKE MODEL 800



This unit is ideal for parallel or series fed high power final amplifier circuits. It is used for operation in the amateur bands—80 through 10 meters inclusive. Winding is on a high quality grooved steatite form, threaded on both ends, for mounting with a ½"—#20 screw. Rating is 2500 VDC at 500 Ma. Size 6" x ½" in diameter. Shipping weight 1 lb.

BALUNS - BIFILAR COIL TYPE



Baluns are impedance matching devices which function to transform a 75 ohm unbalanced RF power source to either a 300 or 75 ohm balance load or visa versa. They are used to feed and match single or folded dipoles, or beam antennas, fed with coax lines. B&W baluns will handle 250 watts AM phone. 500 watt CW and IKW on SSB. Type 3976 kit (illustrated) consists of two Type 3975 coils and a compact 3977 mounting bracket with connector fittings. Baluns are impedance matching de-

MATCHING UNITS MODELS LPA-MU AND LPA-MU-2



A compact pretuned bandswitching A compact pretuned bandswitching turret assembly for correcting mismatch between a fixed driver-exciter unit and the broadbanded input circuitry of the LPA-1. Recommended for driver-exciter units whose output impedance is fixed to a single value. and for cases of whose output impedance is fixed to a single value, and for cases of marginal output inadequate to drive the LPA-1 to a full KW on all bands. Model LPA-MU fits the LPA-1 Linear Amplifier and is coupled with the Pi-Network final tank circuit. Model LPA-MU-2 is similar to the IPA-MII but is designed for Rayker.

PA-MU, but is designed for Barker & Williamson's previous Models L-1000-A and L-1001-A Grounded Grid Linear Amplifiers.






AIR WOUND COILS





All types from 25W thru 1000W

BARKER & WILLIAMSON, Inc. • BRISTOL, PA.

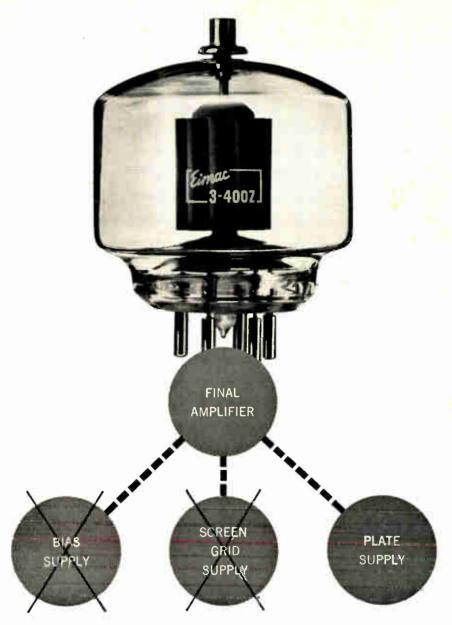

Cross off two power supplies with one of Eimac's new zero-bias triodes!

Another major advance from Eimac: the first high power zero-bias triodes anywhere. Just one of these new tubes will eliminate both screen grid and bias power supplies to simplify your circuit designs. Take your pick of three types: the 3-400Z, shown above, (plate dissipation: 400 watts)... the 3-1000Z (1000 watt plate dissipation)... the ceramic-metal 3CX10,000A7 (10,000 watt plate dissipation). Each offers a power gain of over twenty times in grounded grid service. And their small size accommodates today's lower, more compact equipment. You'll find these zero-bias triodes ideal for class B RF and audio amplifiers. And you'll find them only at Eimac...world leader in transmitting tubes. For ratings, specifications, other details, write: Power Tube Marketing, Eitel-McCullough, Inc., San Carlos, California.




Leading Manufacturer of

TRIBANDERS

NEW DUOBANDER

Both 20 and 40 meter band operation is made possible through a unique Hy-Gain development — the linear decoupling stub, eliminating the use of inductance and capacity traps and decreasing the 40 meter element length by 35%. Beta match for maximum gain and low SWR into a single 52 ohm coax feed. 5KW-PEP; SKW AM. Boom 24 ft; longest element 40 ft. All aluminum with hardware iridite treated. Model DB-24, \$159.50.

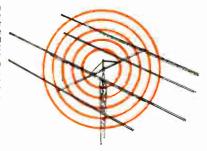




VHF BEAMS

NEW 6 & 2M DUOBANDER

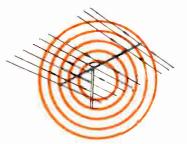A single transmission line system for 6 & 2 meter operation. 52 ohms coax fed, with forward gain of 8.0 db on 6M, 15.0 db on 2M, Flour averages 15-20 db and SWR 1.5 to 1 or less. Rugged construction of 11/4" OD aluminum boom, 7/16" OD elements. Boom 10 ft. longest element 10 ft. Model DB-62, \$32.95.






NEW DOUBLETS

Trapless Hy-Fan doublet takes unlimited power on 40 & 80 Meters, single feed line, 52 ohm coax fed. Copper clad steel stranded wire, cycolac center and end insulators SWR less than 1.5:1 both bands. Length 130 ft. Model 2BDP, \$19.95.

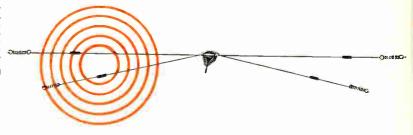New Trap Doublets supplied with solid state "Slim Line" traps for each band for maximum radiation efficiency, center & end insulators, nylon rope for extending lower element, and copper clad stranded steel wire. Take 500 watts AM, 1 kW PEP. Model 3BDT (10-20M), \$17.50 Model 4BDT (10-40M), \$24.50 Model 5BDT (10-80M), \$34.95



Hy-Gain Amateur Antenna Systems feature the finest commercial construction possible in line with proctical beauty. New and efficient concepts improve performance; — the solid state "Slim Traps", the Hy-Gain Beta Match, the Linear Loading Principle, the Capacity Hat and others.

A complete line of accessories is also avail-

able for the listed systems;— stacking and mounting kits, add-on kits for the Verticals, a telescoping mast for the Halos, and mare. For the complete story on the entire Hy-Gain line, ask your local ham dealer — there are more than 500 throughout the world — or write directly to Hy-Gain.

We invite you to compare any Hy-Gain an-

Amateur Communication Antenna Systems



	Boom 6 ft., longest element 26 ft.	69.95
3-Element Thunderbird.	Boom 14 ft., longest element 26 ft.	
4-Element Thunderbird.	Boom 16 ft., longest element 32 ft.	

10-20M Trap Vertical, self-supporting 13.5 ft. high. Model 12AVS	21.95
10-40M Trap Vertical, self-supporting 21 ft. high Model 14AVS	
Hy-Tower, a trapless vertical for 10-80M, 50 ft. overall. Model 18HT	

VERTICALS



2 Meter, 5 Elements. Beta Match, 9.0 db gain. Model 25	\$ 8.95
2 Meter, 10 Element. 12 ft. Boom. 13.4 db gain. Model 210	
11/4 Meter, 11 Elements. Folded ratio dipole. 14.2 db gain. Model 111	\$13.95
3/4 Meter, 13 Elements. 8 ft. Boom. 16.1 db gain. Model 313	

8 Element Beam, 10.1 db gain. Model 5 Element Beam, 9 db gain. Model 65	
6 Meter Halo, mounts 1" mast. Model H 2 Meter Halo, 14" diameter. Model H	
25-50 Mc coverage. Weight 8 lbs. Model GP-1C	\$32.70
50-88 Mc coverage. Weight 5 lbs. Model GP-2C	
100-500 Mc coverage. Weight 3 lbs. Model GP-3C	\$14.97
Discone, 50-500 Mc. Unity gain.	\$29.97

6 METER BEAMS

GROUND PLANES

MONOBANDERS



40	Meter, 2-Element Model 402B	\$99.75
20	Meter, full sized. Model 203B	.\$6 5.95
15	Meter, 8 db gain. Model 153B	\$38.50
10	Meter, 8 db gain. Model 103B	\$32.95

ROTO-BRAKE

Rotator, Brake, Control Unit, 16" Wall Map Indicator, Model RBX-1\$199.95


tenna with any similar competitive system . . . for gain, for construction excellence, for price . . . and for operation, before you choose.

Hy-Gain Antenna Products also manufactures complete lines antenna systems for Citizens Band, FM, the Commercial fields and other special categories.



antenna products

1135 No. 22nd St. Lincoln, Nebr.

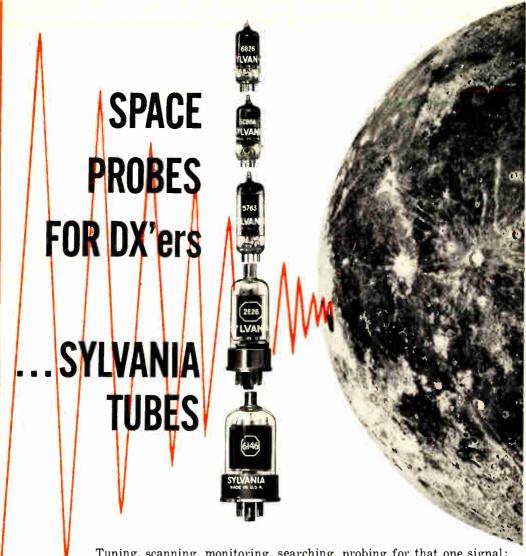

Tuning, scanning, monitoring, searching, probing for that one signal: a new zone, state or country. That demands dependable sigs from the xmtr, high sensitivity with maximum signal-to-noise at the rcvr.

Take a tip from professional "space probers." Industrial, military, broadcast, and aviation communications men have been relying on SYLVANIA POWER TUBES and SYLVANIA RECEIVER TUBES for years for solid copy. They get them from their local franchised SYLVANIA INDUSTRIAL TUBE DISTRIBUTOR. You get them, too, today.

Electronic Tubes Division, Sylvania Electric Products Inc., 1740 Broadway, N.Y. 19, N.Y.







NATIONAL RADIO COMPANY, INC. All Handbook Readers

TO:





Since we have a new catalog on the press this page shows only three of National's receivers. Send for a free copy if you'd like full details on our complete line, including the famous NC-400, the brand new NC-105 and the popular NC-303. Address your letter or postcard to National Radio Co., Dept. RH, Melrose 76, Mass. We'll rush you one of the first copies off the press.





'ATIONAL'S TRIO OF PACE-SETTERS

e are the three new receivers that are already setting the pace for the industry—Each offering more solid performance in its price area than you will believe . . . until you tune one. We invite to try all three—then select the one that best suits your requirements.

Precision double-conversion 80 through 6 meter amateur receiver featuring rock-like stability and unchallenged VHF performance. Five degrees of variable IF selectivity, including selectable SSB with product detector, 1.0 uv sensitivity, 60 db deep T-notch filter, built-in 100 KC calibrator, crystalcontrolled 2nd converter. More features than any other receiver in its price range. \$279.95 am. net.

The 540 KC-30 MC general coverage receiver that tunes like a ham-band-only unit. 1.0 microvolt sensitivity, double conversion with five main tuning ranges, 5.0 KC, 3.0 KC, and 600 cycle variable IF selectivity, full SSB/CW AGC and product detector, 60:1 bandspread vernier drive and National's exclusive dial selector, providing instant choice of calibrated amateur or foreign broadcast bands. \$219.95 am. net.

NC-155 . . . National's newest—A double conversion 80 through 6 meter ham-band-only receiver offering superb performance completely out of proportion with its price. With its basic design derived from the famous NC-270, the NC-155 features 5.0 KC, 3.0 KC and 600 cycle variable IF selectivity, full SSB/CW AGC and product detector, and a velvet 60:1 dial drive that makes SSB signals as easy to tune as AM. 1.0 microvolt sensitivity on 6 meters, too! \$199.95 am. net.

IONAL RADIO COMPANY, INC. MELROSE 76, MASS.

A WHOLLY OWNED SUBSIDIARY OF NATIONAL COMPANY, INC.

The complete line of Gonset Amateur Equipment offers superlative performance at moderate cost

COMMUNICATOR IV-2 METER TRANSCEIVER



Completely new — inside and outl Iransmitter power greater than ever at 24 watts input. High level speech clipping and 10 watts of oudio insure full talk power! Transmitter is crystal controlled, offers choice of six frequencies. Broadbond circuitry in driver eliminates panel controls.

Receiver uses latest frame grid VHF tubes in RF and mixer for low noise figure of 4-6 db, triple conversion with crystal controlled first conversion - . excellent sensitivity, selectivity. Also automatic noise limiter, adjustable squetch, "S" meter, slide rule-type dial, panel speaker. Built-in power supply operates on both 115V AC and 12V DC. DC supply is transistorized, eliminates vibrotor. Power cables are supplied for shift from AC to DC. Size: 5" H, 12½" W, 11" D. Weight, 21.8 pounds.

DC operation is with negative ground only.

Less Microphone

Model #3341 Amateur Net.....369.50

COMMUNICATOR IV-6 METER TRANSCEIVER

Communicator IV for 6 meters is the same size and general appearance as the 2 meter model. Tunable receiver covers 49.9 to 54.1 with the 50-51 mc range spread over one third of the dial range. Receiver is triple conversion type, has sensitivity of 1.0 μv for 10 db (S+N)/N or better. Noise figure is 6-8 db.

Transmitter operates at power input of 24 wotts, has six crystal control positions with socket for external VFO.

Crystals are in the $8.333\ \text{to}\ 9\ \text{mc}$ range. Equipment has push-to-talk provisions.

2-way power supply, 12V DC and 115V AC is built in. DC supply is transistorized, operates negative ground only.

Less Microphone

Model #3342 Amateur Net.....349.50

COMMUNICATOR IV-11/4 METER TRANSCEIVER

The first commerically-produced "pockage" operating on the amateur 220 megacycle band! Operates at an input power of 20 wotts—substantial for VHF—incorporates on excellent superheterodyne receiver.

Triple conversion receiver is continuously tunable over the frequency range of 219.7 to 225.3 mcs. To comply with OCDM requirements, additional provision is made for spot frequency reception on one crystal controlled frequency. Receiver sensitivity is 1.0 μv for 10 db (S+N)/N ratio. Noise figure is 6-8 db, exceptional for equipment of this general type. Adjustable squelch and ANL are included.

Transmitter is crystal controlled, offers choice of 6 frequencies. (Required crystals are within the range of 8.143 to 8.333 mcs.) Provision is made for external VFO. Power input to PA is 20 watts, amplitude modulated by P-P 6BQ5's operating in Class AB1. High level speech clipping and audio shoping are incorporated.

Unit is identical in size and general appearance to the Communicator IV 2 meter model, 2-way power supply for 115V AC and 12V DC (negative ground) is built in.

Less Microphon

Model #3351 Amateur Net.....394.50



VFO FOR 6, 2 AND 11/4 METER COMMUNICATORS

New VFO is designed for use with all Ganset Communicators including Models I, II, III and IV. Dial scale is calibrated for 50,144 and 220 megacycle bands. Microphone connector with FM modulator is provided to allow VFO to be used for Norrow Band FM. Excellent stability.

Model #3357 Amateur Net......69.50



GSB-201 SSB RF LINEAR AMPLIFIER

This entirely new linear amplifier is exceptionally compact—is only $81/2^{\circ}$ high, $129/6^{\circ}$ wide and 17° deep—lends itself readily to table-top mounting. It is finished in blending light colors, presents a handsame clean-cut appearance.

The linear amplifier covers 80, 40, 20, 15 and 10 meter amoteur bands, incorporates full bondswitching, has pin network output. Power input rating is 1500 wats PEP SSB 1000 wats CW, 400 watts AM. This amplifier can be driven by exciters in the 65-150 wat category, GSB-100 and similar units. Stable, grounded-grid circuitry is used.

GSB-201 incorporates a number of desirable operating features which include the use of low cost Type 811A tubes. Older type vacuum tube rectifiers are replaced by modern, long-life silicon types in the high voltage supply. Antenno changeover relay is built-in. A ponel switch permits preliminary tuning to be done at low power. A full vision ponel instrument is switchable to indicate plate current or relative power output.

Amoteur Net

399.50

*PEP input is approximately twice average d.c. input.



GR-212 DUAL CONVERSION RECEIVER

Dual conversion for increase selectivity. Variable BFO. Sensitivity: At least 6 db (5+N)/N at 1 $\mu\nu$ (mad. 30% at 400 cps) input an all H.F. Boads. Two full-vision, illuminated, slide-rule type dials provide instant identification of broadcast and shortwave frequencies. Panel-mounted "S" meter. Band-spread uning knab is inertio fly-wheel weighted for smoothest tuning. Separate band-spread dial for amateur bands. For 115V AC apperation.

Amateur Net 99,50

GR-211 ALL BAND RECEIVER

Similar in appearance to the GR-212. General coverage from standard broadcast through 34 mc band, including WWV, foreign & Voice of America. Printed circuit techniques and advanced design for extro sensitivity, better, quieter reception, even on highest frequency bands. 5 tubes, two solid state rectifiers. TRANSFORMER-POWERED (not ac/dc) for higher over-all gain, better signal-to-noise ratio. Circuit features leading to higher sensitivity include quality, high-Q, permeability-tuned coils. Two full-vision, illuminated, slide-rule type dials provide instant identification of broadcast and short-wave frequencies. Vernier tuning knob counter-weighted for smooth, non-critical short-wave tuning. For 115V AC operation.

Amoteur Net......69.50



SUPER 12 SIX-BAND CONVERTER

Super 12 provides coverage of 6 amateur bonds: 10, 15-20, 40 and 75 meters plus 19 and 49 meters for coverage of international shortwave broadcasts. Calibrated dial scale uses various colors to oid in identification of bonds. Planetary drive provides vernier tuning.

Sensitivity and stability are excellent. Antenna trimmer on ponel maximizes ontenna in use. 8C-HF switch permits instant return to standard BC. Super-12 is ottractive... blends well with instrument ponel of modern cars. Compact size facilitates mounting. Highest quality components and precision workmanship ensure long, trouble-free operation. Installation is simple, non-technical—no alteration or internal connections to existing broadcast receiver. Converter simply patches into antenna input connector af car radio... ottaches to 12 volt accessory post under dost. Install in minutes with ease.

12 volts DC neg, ground only.

Amoteur Net89.50



G-76 ALL BAND TRANSCEIVER FOR FIXED OR MOBILE SERVICE

G-76, on entirely new unit consisting of transmitter and receiver in a single compact housing. Provides AM or CW operation on 80, 40, 20, 15, 10 and 6 meter amoteur bands. The G-76 incorporates proved design features of the famed Ganset G-66/G-77 "Twin sparklers," adds many new advances for top fixed station and mabile operation.

Receiver is duol-conversion with 1st 1-F et 2065 kcs, 2nd 1-F at 202 kcs. Features include BFO for SSB and CW reception—outomatic noise limiter. Unit has excellent selectivity and sensitivity. Transmitter and receiver oscillators are temperature compensated. Transmitter has stoble VFO for all bands except 50 mcs which is crystal control only. Crystal control of other bands is optional. Power input to transmitter is 100 watts AM, phone, 120 watts, CW. Final tube is 60Q5 operating into pi network output. Control is push-to-talk or by T-R switch on panel. Meter facilitates tuning, acts as "S'" meter on receive. Dimensions: 12½" W, 5" H and 10½" deep. Unit has internal sacket for crystal calibrator (optional) also panel switch for colibrator operation.

AC and DC power supplies are available as accessory items at 145.00.

Amoteur Net......399.50

G-50 6 METER FIXED STATION COMMUNICATOR



G-50 is a complete station "package" for 6 meter operation. Receiver is highly sensitive, selective superhet with "S" meter, ANL, adjustable squelch, panel mounted speaker. Transmitter uses 6146 in pi network final at 40-50 watts input. Frequency control is by crystal or built-in highly stable

VFO. Latter gangs with multiplying stages, eliminates excitation controls. Dial is calibrated 50-54 mcs. Modulator uses two 616GB's. Compact housing, 7½," H, 13" W, 12½," D contains receiver, transmitter, power supply. For 115V AC operation.

Amoteur Net......319.50

CD MODEL. Similar in general oppearance to standard amateur model but is certified as meeting applicable specifications under OCDM U-68. Cabinet is same size as amateur model, has appropriate CD markings. Mic. and crystal certificate included.

Model #3300-CD Amoteur Net 349.50

NOISE CLIPPER



Designed for use with either mobile or fixed receivers that utilize the more common types of second detector. Reduces such interference os ignition noise, certain types of power leaks, and other forms of "Pulse" type noise having a low repetition rate and short pulse length. Utilizes a miniature diade in a form of series gate. Easy to install. Complete instructions furnished.

Model #3001 Amateur Net.....11.95

MONITONE



For use as a code proctice oscillatar and as an effective monitor for phane and CW xmtrs. Has audio ascillator controlled by external circuits, provides audible tone on panel speaker or earphones. Separate pitch and volume controls. Uses RF pickup

from xmtr. for operation as effective CW or phone monitor.

Operates from 115 VAC with isolating circuitry so that neither keying nor earphone leads are "hot" ta ground.

Model #3022 Amoteur Net......29.50



GC-105 "GOONEY BIRD" COMMUNICATOR

Silicon diodes to sove current drain...calibrated tunable receiver utilizes low-noise 6828 RF tube sensitive in "Coscode" circuit. AVC is opplied to avoid possibility of blocking by strong local signals. Special gang-tuned circuits give high image rejection. Dual purpose meter automatically switches from relative signal strength to relative autout. Increased modulation copabilities with high level clipping. All tunable circuits controlled from front ponel. Tune-up procedure simplified by use of broad-banded exciter stages. Completely compatible with Ganset's new model 3357 VFO or 6 crystall positions available. Input. 6/12 DC or 115 AC volt operation, power cables supplied. Output: 6 watts nominal. Dimensions: 61/2" high, 151/3" wide, 8" deep.

Amoteur Net......239.50


For further information on Gonset products see your nearest Gonset Distributor or write to —




DIVISION OF YOUNG SPRING & WIRE CORPORATION

801 SOUTH MAIN STREET, BURBANK, CALIFORNIA

The Least Expensive Way to Increase

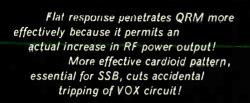

MODEL 664

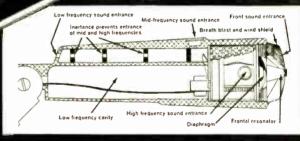

HERE'S HOW IT WORKS

Exclusive E-V Variable-D* (Variable Distance) provides three sound-cancelling entrances at different fixed distances in back of the diaphragm. These entrances, utilizing the proper acoustical impedances, combine to form an effective front-to-back spacing which varies in distance from the diaphragm inversely with frequency. The resulting phase and amplitude conditions provide a uniformly frue cardioid pattern at all frequencies.

Here's What the Top Radio Amateur Operators in the World Say About These E-V Microphones:

CX2CO "My new 664 resulted in better and more consistent QSO's."

W8KML "The 664 surpasses its claims in difficult operational environments."

ZL1HY "During QSO's ... everyone preferred the 951."

W3JNN "I am really sold on the 664."

W8BF "I have had many unsolicited compliments since using the 729."

VQ4ERR "The performance of the 664 matches its thoroughbred appearance."

PY2CK "My 664 microphone vastly Improved my SSB transmission."



World Radio History

Average Peak-Power and Intelligibility!

CHOOSE AN Electro Voice MICROPHONE

Model 664 for Highest Front-to-Back Discrimination Manufactured, Plus Peak-Free Wide-Range Response!

The effective strength of all sounds arriving at the sides of the 664 are reduced by as much as 50%, and arriving directly at the back of the microphone by as much as 90%. This uniquely effective design permits you to work at twice the distance from the microphone . . . a perfect invitation for "arm chair" QSO's—with no VOX tripping problems.

Smooth, peak-free response guarantees maximum P.E.P. Remember, a peak in response in or *out* of the voice range will limit maximum modulation and result in reduction of P.E.P. You do not have to talk with your lips on the mike. For best results, sit back and talk naturally.

Virtually indestructible Acoustalloy® diaphragm withstands high humidity, temperature extremes, corrosive effects of salt air and severe mechanical shock. Extra ruggedness means extra service, year after year.

MORE 664 FEATURES: Output—55 db. On-off switch (can be wired for relay control). 150 ohms or Hi-Z output selected at cable connector. Satin chromium finish. High-pressure die-cast case. Pop-proof filter plus magnetic shield. 90° swivel mounting. 18 ft. cable. 7 16 in. long (less stand coupler) by 1 16 in. diameter. Net Weight 1 lb., 10 oz. Amateur Net, \$51.00. Matching desk stand with DPDT switch. Model 419S, \$9.00. Less switch. Model 419, \$6.00.

The World's Finest Mobile Microphone. Model 600D Dynamic Widely Known As Military Types T-50 And M-105/U!

Designed for high articulation under rugged mobile conditions, the Model 600D provides all the advantages of a dynamic element with peak-free, flat response for maximum P.E.P.

High-impact case soaks up physical abuse, feels comfortable at any temperature, fits hand naturally. Extremely high output of -55 db. is ideal for mobile equipment with severe audio requirements. Available in 50, 250 ohms or Hi-Z. DPDT switch. 6 ft. coiled cord. Panel mounting bracket included. Model 600D Amateur net, \$28.50.



MODEL 729SR

Lowest-Cost Ceramic Cardioid Available ...Includes Every Feature Essential For SSB Operation. Flat, Smooth Response From 300 To 3,000 CPS!

Rugged enough for mobile operation, the slim, small Model 729 fits easily in your hand or slips into the desk stand or floor stand adapter provided, without any hardware adjustments. Hi-Z output -60 db. Two-tone grey, pressure die-cast and plastic construction. Shielded, 8½ ft. cable. 7½ in. long by 1½ in. wide. Net weight 1 lb. Ceramic element unaffected by high heat, humidity. Model 729. Amateur net, \$14.70. Model 729SR with relay-control switch. Amateur net, \$15.90.



MODEL 951

First True Crystal Cardioid With Variable-D Design. Combines High Output With Excellent Noise Rejection At Modest Cost!

Finest crystal microphone available for SSB. Variable-D design of Model 951 cuts room noise, interference from receiver speaker to a minimum. Allows greater working distance to microphone. Peak-free rising response for high intelligibility. Hi-Z output-60 db. High-pressure, die-cast finished in Metalustre grey. On-off switch. Shielded, 18 ft. cable. 5½ in. long (less stand coupler) by 1½ in. diameter. Net weight 1½ lbs. Model 951 Amateur net, \$32.70. Matching desk stand with DPDT switch. Model 418, \$9.00. Less switch. Model 418, \$6.00.





ELECTRO-VOICE, INC., Commercial Products Division
Department 1212HB Buchanan, Michigan



HARVEY



AUTHORIZED DISTRIBUTORS



RCA Tubes and Harvey Service... For Double Dependability!

HARVEY's line of RCA tubes is so complete, that HARVEY can fill virtually any requirement . . . right from stock . . . and deliver at almost a moment's notice.

This is particularly important to AM, FM, and TV Broadcasters, Industrial and Commercial users, Amateurs, and Service-Technicians, all of whom depend on tubes for sustained operation of important electronic equipment.

Write, Wire or Phone for PROMPT HARVEY SERVICE

Visit Harvey's New Ham Radio Center. The latest and best in ham gear is always on display.




ARRL PUBLICATIONS




Storehouses of Information for:

- Novices
- Old Timers
- Students
- Engineers


Supplies for the Active Amateur

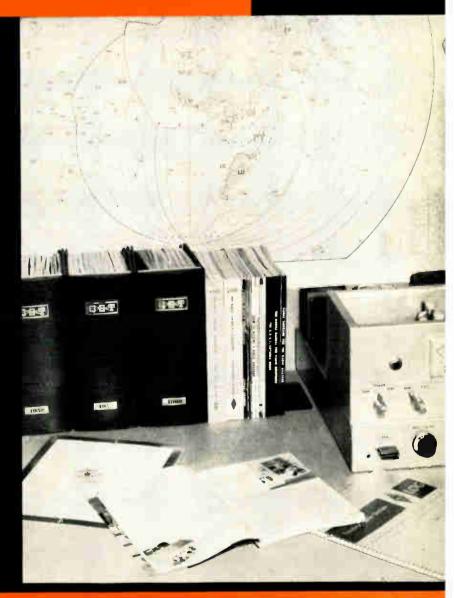

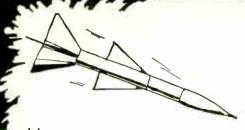THE AMERICAN RADIO RELAY LEAGUE . WEST HARTFORD 7, CONN.



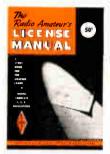the BEST SELLER LIST FOR THE RADIO AMATEUR




MOBILE

MANUAL








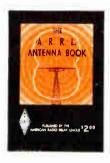




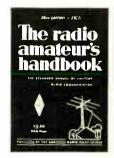






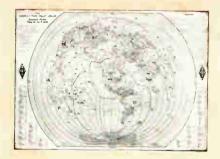

ARRL WORLD MAP

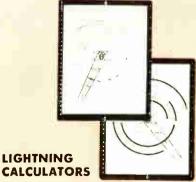Printed in eight colors on heavy map paper with 267 countries clearly outlined. Continental boundaries, time zones, amateur prefixes, plainly marked. Size: 30 x 40 inches. \$2.00.



Quick and accurate answers with ARRL Lightning Calculators! Type A for problems involving frequency inductance, capacity. Type B for resistance, voltage, current and power. \$1.25 each.



- ★ QST Although primarily a ham magazine, QST is found on the desks of engineers, technicians and just about everyone in the electronics field. There is something for everyone in QST, from the Novice to the Old Timer. QST and ARRL membership \$5.00 in U.S.A., \$5.25 in Canada, \$6.00 elsewhere.
- ★ THE RADIO AMATEUR'S HANDBOOK Internationally recognized, universally consulted. Packed with information essential to the amateur and professional alike. Hundreds of photos, diagrams, charts and tables. \$3.50 U.S.A., \$4.00 U.S. Poss. and Canada, \$5.00 elsewhere; Clothbound Edition, \$6.00 in U.S.A. and Possessions and Canada, \$6.50 elsewhere.
- ★ A COURSE IN RADIO FUNDAMENTALS

 A complete course of study for use with the Radio Amateur's Handbook. Applicable to individual home study or class use. \$1 U.S.A. proper, \$1.25 elsewhere.
- ★ HOW TO BECOME A RADIO AMATEUR Tells what amateur radio is and how to get started in this fascinating hobby. Emphasis is given to the needs of the Novice licensee, with three complete simple amateur stations featured. 50 ć.
- ★ THE RADIO AMATEUR'S LICENSE MANUAL Complete with typical questions and answers to all of the FCC amateur exams—Novice, Technician, General and Extra Class. Continually kept up to date. 50 c
- ★ LEARNING THE RADIOTELEGRAPH CODE For those who find it difficult to master the code. Designed to help the beginner. Contains practice material for home study and classroom use. 50 ć.
- ★THE ARRL ANTENNA BOOK Profusely illustrated, the Antenna Book includes information on theory and operation of antennas for all amateur bands; simple doublets, multi-element arrays, rotaries, long wires, rhombics, mobile whips, etc. \$2.00 U.S.A. proper, \$2.25 elsewhere.
- ★ SINGLE SIDEBAND FOR THE RADIO AMATEUR A digest of the best SSB articles from QST. Includes discussions of theory and practical "how-to-build-it" descriptions of equipment. \$1.50 U.S.A. proper, \$1.75 elsewhere.
- ★ THE MOBILE MANUAL FOR RADIO AMATEURS It's a collection of articles on tried and tested equipment that have appeared in QST. A "must" for the bookshelf of anyone interested in the installation, maintenance and operation of mobile stations. \$2.50 U.S.A. proper, \$3.00 elsewhere.
- ★ HINTS AND KINKS If you build equipment and operate an amateur radio station, you'll find this a mighty valuable book in your shack and workshop. More than 300 practical ideas. \$1 U.S.A. proper, \$1.25 elsewhere.



QST BINDERS

No need to let your copies of QST rest in a disordered pile, A QST binder will keep them neat and orderly, Each holds a one-year file. \$3.00 (available in U.S. and Possessions only).



SUPPLIES

Active amateurs need these supplies: ARRL Logbook, 50¢ U.S.A., 60¢ elsewhere. Minilog, 30¢ U.S.A., 35¢ elsewhere. Radiogram blanks, 35¢ per pad postpaid. Message delivery cards, 5¢ each stamped, 2¢ each unstamped. Members' stationery, 100 sheets \$1.00; 250 sheets \$2.00; 500 sheets \$3.00.



Application for Membership



AMERICAN RADIO RELAY LEAGUE

Administrative Headquarters: West Hartford, Connecticut, U. S. A. AMERICAN RADIO RELAY LEAGUE, West Hartford 7, Conn., U.S.A. Being genuinely interested in Amateur Radio, I hereby apply for membership in the American Radio Relay League, and enclose \$5.00* in payment of one year's dues. \$2.50 of which is for a subscription to QST for the same period. [Subscription to QST alone cannot be entered for one year for \$2.50, since membership and subscription are inseparable.] Please begin my subscription with the issue. The call of my station is The class of my operator's license is..... I belong to the following radio societies..... Send my Certificate of Membership

or Membership Card [(Indicate which) to the address below:

A bona fide interest in amateur radio is the only essential requirement, but full voting membership is granted only to licensed radio amateurs of the United States and Canada. Therefore, if you have a license, please be sure to indicate it above.

*\$5.00 in the United States and Possessions. \$5.25, U. S. funds, in Canada. \$6.00, U. S. funds, in all other countries. How Mosley can help choose he antenna for you


n amateur, commercial and military communications systems

How can you select an antenna that you know is right for you? You can know for sure if you investigate before you invest. Asking other hams or other engineers which antenna they have used or recommend is a very effective way to investigate the relative merits of any antenna or antenna system.


Hams who own one of the famous Mosley line of amateur antennas will tell you that they perform as well, or better, than advertised. But after you have talked with other hams, see your distributor. He will be glad to explain the relative merits of such famous Mosley antennas as those shown on the right.

Electronic engineers, too, who have used one of Mosley's new line of commercial antennas will agree that they are built to the same high standards of engineering, material and workmanship as the world famous Mosley amateur antennas.

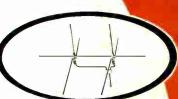
We will gladly supply the names of dozens of leading commercial, military and industrial organizations who have installed Mosley point-to-point antennas in standard configurations which are available "off the shelf" and "customized" antennas in HF and VHF ranges. Write our Government and Industrial Division for our new catalog "Antenna / Systems 1961 /62".



Bi-Directional Vertical Ground Plane

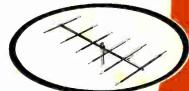

Yagi Six Element

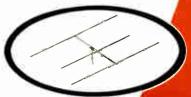

Model TA-20-40



Model 5-402

Look for this black and yellow decal in the windows of nearly 250 amateur and industrial electronic equipment dealers. These signs Identify dealers who carry in stock the Mosley antenna for you.

4610 N. LINDBERGH BLVD. BRIDGETON, MISSOURI



SSB · DSE

GPR-90 (R-825 /URR) . . . a general purpose communications receiver of the double conversion superheterodyne type covering the frequency range of .54 to 31 mcs. Stable — selective — accurate — built-in crystal calibrator.

Bulletin (179) 3005

GPT-750 () 2(AN/URT-17A) . . . is a fully bandswitched, continuously tunable (2-32MC) radio transmitter. The building block concept makes this transmitter versatile, easy to install, operate and maintain. Nineteen models available. SSB, ISB, DSB, AM, CW, FAX, FS. The GPT-750 (.....)2 is ideally suited for fixed station, mobile and shipboard operation.

Bulletin 227 (1007)



SBT-1K

GPR-90

GPR-90RX



GPT-750



World Radio History

HF/LF communications it's TMC

· ISB · CW · MCW · AM · FS

VOX (0-330B/FR)... a direct reading, high stability, Variable Frequency Oscillator providing continuously variable output over the frequency range of 2—64 mcs.

Bulletin (134A) 2010

XFL-2... The TMC Frequency Shift Exciter System, Model XFL-2 is combined low and high frequency shift system. The system combines the TMC Low Frequency Adapter, Model LFA with TMC Frequency Shift Exciter, Model XFK to provide versatile operation over a wide range of frequencies—1 to 6.9 mcs, and 50 to 500 Kcs.


Bulletin (154) 2021

PTE-3 (AN/GRM-33A)... Single Sideband Analyzer designed for the specific purpose of tuning and aligning single sideband exciters and transmitters permitting a visual analysis of intermodulation distortion products, hum and noise The PTE-3 consists of 3 basic TMC units: Spectrum Analyzer Model FSA (AN/URM-116A); A VFO TMC Model VOX (0-330B/FR) and a Two-tone Generator TMC Model TTG (0-579A/URT).

Bulletin (231) 6001



VOX

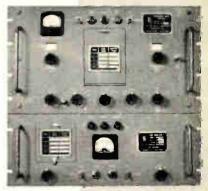

XFI-2

SBT-350 B

The TECHNICAL MATERIEL CORP.


MAMARONECK, NEW YORK

MAMAKONLOK, NEW 10

Ottawa, Ontaria, Canada • Alexandria, Virginia • Garland, Texas

La Mesa, Califarnia • Pampana Beach, Flarida.

and Subsidiaries:

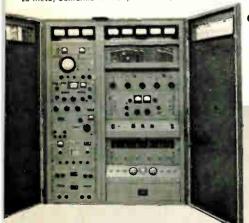

GPT-10K



PTE-3



SPECIALISTS IN PRECISION RADIO CRYSTALS AND QUALITY

ELECTRONIC FOUIPMENT

QUALITY ELECTRONIC **EQUIPMENT FROM INTERNATIONAL**

NUVISTOR



amplifier. Inductive neutralization. Available 26 mc through Kit\$5.95

Wired a	ınd	tested.		\$9.95
Coupling	g s	ection	(each)	.95
Mountin	g C	hassis	(each)	\$2.00

CONVERTERS

TRC Crystal controlled. Three transistors. RF stage. Available all amateur bands 6 through 80 meters.* 600-1600 kc IF or 6 mc IF for use with TRB-1......**\$16.50** * See catalog for other frequencies.

Crystal controlled. Three transistors. Available for any 1 mc band of frequencies between 54 mc and 160 mc. 600-1600 kc IF or 6 mc IF for use with TRB-1.

54	mc	to	100	mc\$20.50	
100	mc	to	160	mc\$20.50	

FM-5000 **FREQUENCY** METER

Beat frequency measuring device. Incorporates a transistor counter circuit, self contained batteries, low RF output for receiver checking, audio

oscillator, transmitter keying circuit, and plug-in oscilla-tors, including heating circuit.

Frequency meter, including batteries, accessories and complete instruction manual. less oscillators and crystals....\$375.00

1 - 4			\$25.00	ea
5 - 24			15.00	ea
25 to 99			9.00	ea
100 or more			8.25	
	"less c	rystal		
Cryst	als for	Óscillato	ors	
100 kc - 1999 kc			\$8.75	ea
2000 kc - 60 mc.			6.25	



CASE Mounting case for TRC-4 or TRC-5. Complete with all items neces-

FO-1L 100 kc OSCILLATOR

\$15.95

\$6 95

Printed circuit oscillator for band edge calibrator and frequency standard. Power: 150 vdc @ 8 ma, 6.3 vac @ 150 ma.

Kit, complete with tube and crystal Wired and Tested



CRYSTAL OSCILLATOR





COMPLETE LINE TRANSIS-TOR SUB-ASSEMBLIES FOR COMPACT RECEIVER / TRANS-MITTER CONSTRUCTION

CONVERTER (TRC-1) Three transistors, crystal controlled 6 mc IF standard. 10 meters. Wired and tested with crystal \$14.50

AUDIO UNIT (TRA-2) Three transistors. Input 100,000 ohms and 50 ohms. Speech input for dynamic microphone. Push-pull power amp. Wired and tested \$14.50

MIXER IF UNIT (TRB-1) Six transistors, 2 diodes. Crystal controlled

local oscillator. Noise limiter and squelch. 6 mc input. Wired and tested with 2 crystals \$32.50

sary for installation in vehicle......\$4.95

TRANSMITTER UNIT (TRT-2) Three transistors. Crystal controlled. Switch for two frequencies. 10 meter range. Transmitter less transistors \$10.00 Transistor Kit \$ 9.00

OSCILLATORS. Three separate transistor units with total of 8 frequency ranges (100 kc to 60 mc). TRO-1 100 kc and 200-2000 kc.

TRO-2 2000 - 20,000 kc. Overtone 15 mc to 60 mc in 5 ranges. Specify frequency (each) \$4.00



VFA-1 CASCODE PRE-AMPLIFIER

For 2 meters or 6 meters. Mounts in standard 3" x 4" x 5" minibox. Power 250 vdc @ 10 to 15 ma, 6.3 vac @ 400 ma. Tube 6BQ7A

(o noo ma. Tabe ob	G(//ti
50 mc	Kit with tube	\$4.95
	Wired with tube	\$8.95
144 mc	Kit with tube	\$4.95
	Wired with tube	\$8.95

World Radio History

FOR DEPENDABILITY IN COMMUNICATIONS...SELECT INTERNATIONAL CRYSTALS

AMATEUR CRYSTALS

Types FA-5, FA-9, FM-9 1000 kc to 137 mc .01% Tolerance Wire mounted plated crystals for the Amateur or Experimenter where tolerance of .01% is permissible and wide range temperatures are not encountered.

Designed to operate into a load capacitance of 32 mmf on the fundamental between 1000 kc and 15 mc. Designed to operate anti-resonance on 3rd overtone modes into grid circuit without additional capacitance load. Fifth overtone crystals and seventh overtone crystals operate at series resonance.

HOLDERS: Metal hermetically sealed. FA-5 and FA-9 are HC/6U pin type. FM-9 is HC/18U pin type. CALIBRATION TOLERANCE: ± .01% of nominal at 30 C

TEMPERATURE RANGE: -40° to 70 C. ± .01% of frequency at 30°C. DRIVE LEVEL: Recommended, maximum 3 milliwatts for overtones; up

to 80 milliwatts for fundamentals, depending on frequency.

FREQUENCY RANGE: FA-5 and FA-9 1000 to 20,000 kc fundamental; 10 mc to 60 mc third overtone; 60 mc to 137 mc fifth and seventh overtone. FM-9 8000 kc to 20,000 kc fundamental; 20,000 kc to 60 mc third overtone; 60 mc to 110 mc fifth overtone; fifth overtone.

COMMERCIAL CRYSTALS 70 kc to 137 mc-Type F-6

Wire mounted, plated crystals for use in commercial equipment where close tolerances must be observed. All units are calibrated for specific load presented by equipment. Crystals are available for all major two-way equipment and in most cases the necessary correlation data is on file. Prices on request.

DE TION AND DATA: Low drift Af-cut blanks are used in these units above 500 kc, and low drift DT and CT-cut blanks are used in units below 500 kc; any crystal can be supplied for operation with or without an oven

TEMPERATURE TOLERONCE: AI - ±.005% from - 55 to +90° C. ±.002% from - 30° to +60° C.

DT-CT-±.01% from -40° to +70° C. CALIPOATION TOLERANCE AT - 0025% of nominal at +30° C. DT-CT - 01% of nominal at +30° C.

LEVELS um, AT Maximum,

aximum, A1— 10 milliwatts 500 kc to 999 kc 4 milliwatts 10,000 kc to 24,000 kc 2 milliwatts 25 mc to 137 mc DT-CT - 2 milliwatts

.765 .238 050 dia F-605 FA-5 750 INT CRYSTAL IN RYCT L .093 dia. F-609 FA-9 .125 dia F-612 FM-9

750



MODEL C-12 ALIGNMENT OSCILLATOR

Crystal controlled for generating standard signals in alignment of IF and RF circults. Accommodates FX-1 crystals from 200 kc to 15,000 kc. Special oscillators for frequencies to 60 mc. Complete with power supply for 115 vac. Oscillator with case, cover and carrying handle (less crystals) crystals)



18 NORTH LEE - OKLA. CITY, OKLA.



CRYSTALS FOR USE IN MILITARY **EQUIPMENT CAN BE SUPPLIED TO MEET** SPECIFICATIONS OF MIL - C - 3098B.

SAVE UP TO 50%

ON THE NEWEST, FINEST AMATEUR RADIO GEAR WITH

HEATHKIT

New Kits

Forty new kits have joined the Heathkit line this fall...choose from over 250 quality kits...the world's most complete line!

New Guarantee

We guarantee you can build any Heathkit and have it perform to factory specifications . . . now you can buy in complete confidence!

New No-Money Down Terms

Now it's even easier to buy from Heath! Any order from \$25 to \$600 can be paid for on Heath's time-pay plan with no down payment!

New 1962 Heathkit Catalog

It's the world's biggest kit catalog ... 100 pages ... complete descriptions, specifications and many schematics. It's yours FREE!



Specially-designed for CW work ... new novice CW TRANSMITTER KIT HX-11

An excellent transmitter for the novice or CW amateur who appreciates a clean, quality signal and real distance getting power! Features 50 watt RF power input on 80 through 10 meters, built-in low pass filter, single-knob bandswitching, switched antenna relay power and pi-network output coupling for complete operating convenience. A "tune-operate" switch allows off-the-air tuning and a large "clear view" meter indicates final grid or plate current. Easy access to crystal socket is provided by a metal pull-out cabinet plug. Power supply is built-in. Careful design and high-quality components used throughout make this kit easy to assemble and assures long, reliable and trouble-free performance for years to come. An outstanding "watts-per-dollar" value in amateur gear. 17 lbs.

Kit HX-11... NO MONEY DOWN, \$5 mo......\$43.50

The DX-60 Surpasses Quality and Performance of Transmitters Costing Far More!

This outstanding phone and cw transmitter offers far more in quality and performance than any other unit in its price and power class! A front panel switch selects any of four crystal positions or external VFO. Controlled carrier modulator and silicon diode power supply are built in. Single knob bandswitching for 80 through 10 meters and pi-network output coupling provide complete operating convenience. Panel meter shows final grid or plate current for easy tuning. Assembly is a marvel of simplicity with clean, rugged construction and thoughtful circuit layout. A precut, cabled wiring harness eliminates tedious wiring and the informative instructions furnished make it an ideal kit for the novice. May be run at reduced power for novice operation. Less crystals. 25 lbs.

Kit DX-60...NO MONEY DOWN, \$9 mo.......\$82.95






New low cost, broad coverage Heathkit VFO HG-10

Covers 80 through 2 meters with each band separately calibrated on a rotating drum-type slide-rule dial. Uses a series tuned Clapp oscillator with regulated plate voltage for stability and a cathode-follower output stage for load isolation. Features 28:1 vernier gear drive, and "spotting" switch for off-the-air tuning. Powered by transmitter. Styled like the Heathkit DX-60 and plugs into it directly. Easy to build. 12 lbs.

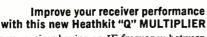Kit HG-10...NO MONEY DOWN, \$5 mo.......\$34.95



May be used with any receiver having an IF frequency between 450 and 460 kc. This "electronic filter," with effective "Q" of approximately 4,000, provides either a sharply-peaked IF curve for CW, a broad peaked IF curve for AM or SSB, or a deep sharp notch for rejecting heterodynes on CW, AM and SSB. Both peak or notch positions are tunable to any point in the receiver's IF bandpass. Ideal for CW reception and heterodyne rejection on receivers or transceivers employing fixed bandwidth mechanical filters such as the Collins 75S-1. Power supply is built-in. 2 lbs.

Kit HD-11.....\$14.9







First of its type! Performs like a "grid-dip" meter but uses a tunnel-diode oscillator and transistors—no tubes! Built-in battery supply for complete portability... use it anywhere for alignment, trouble-shooting, etc. Features color-matched coils and dial scales for easy reading; printed circuit board for easy assembly. Protective cover has storage space for coils. Enclosed vernier-driven drum-type tuning dial prevents accidental change in settings. 3 lbs.

Kit HM-10...NO MONEY DOWN, \$5 mo.......\$34.95





Free Catalog

Send For Your FREE 1962
Heathkit Catalog now! It
details the complete
Heathkit line of quality
kits...over 250...the
world's largest selection.
We'll send your friends
free copies too!

- DR	HEATHKIT'
200	by Daystrom

HEATH COMPANY

Benton Harbor 9, Michigan


Please send the Free Heathkit catalog.

Name.

Address__

City

____State_

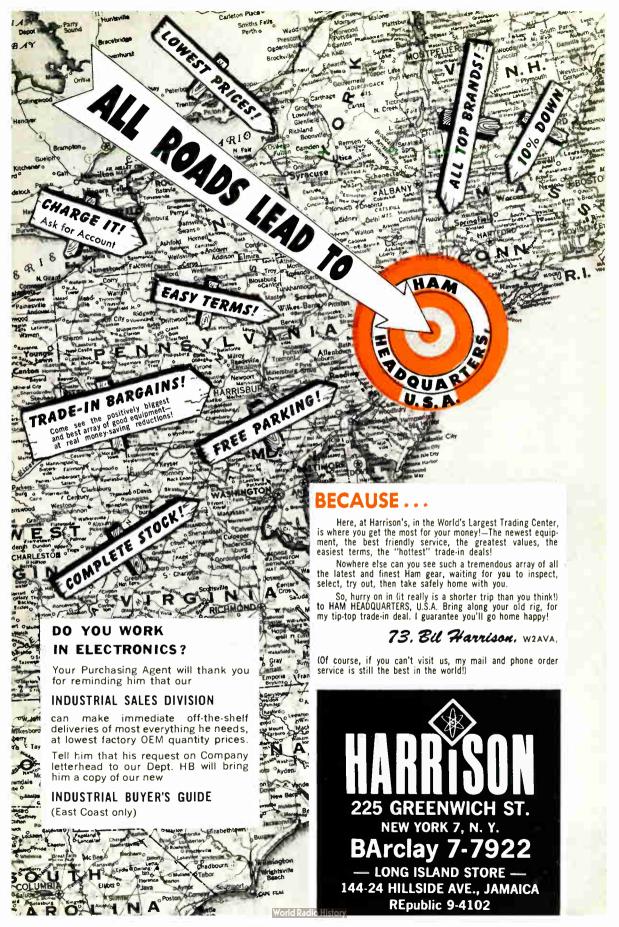



STEP UP TO QUALITY...

RECEIVERS, TRANSMITTERS

In Stock RIGHT NOW at Your HAMMARLUND Distributor

Thrill to the stability and precision of professionally designed, carefully manufactured equipment for amateur use. Scan these pages, and you are sure to find the unit you want.



\$399.50 AMATEUR NET

NEW! HX-50

The first BIG STEP in transmitter history—Hammarlund quality-plus features that literally burst forth in this new, compact filter-type transmitter. Power input 130 watts, P.E.P. Two tone output...50 watts at 10 meters...75 watts or better at 80 meters. Features slide rule dial with band-in-use neon indication.



HQ 100A

Single Conversion

General coverage receiver with extra convenience and performance through independently controlled, continuously variable BFO and Q-Multiplier.

\$189 Amateur Net*



HQ 145X

Dual Conversion Above 10 MC

Pin-point accuracy with single-crystal controlled fixed frequency channel plus top-quality general coverage reception. \$269 Amateur Net

*24 hour clock-timer-\$10 optional

HAMMARLUND QUALITY...

AND ACCESSORIES



MR 30X **MR 50X**

True split channel crystal controlled monitor receiver. Factory tuned to any spe-cific channel within the frequency limits of the instruments. Multiple channels available. MR 30X-25 to 54 MCS. MR 50X-147 to 174 MCS. \$199.50 Amateur Net



HQ 170

Optimum reception of SSB amateur bands. Triple conversion. Razor sharp slot filter with up to 60 db attenuation. The amateur band Specialist.

\$359 Amateur Net



HQ 180

Triple Conversion

The quality standard for the industry. The very finest general coverage receiver available. 18 tube superheterodyne unit for the best in SSB, AM and CW reception. \$429 Amateur Net*



HO 110

For the amateur bands. Optimum selectivity, Dual conversion 12 tube superheterodyne. \$249 Amateur Net



HX 500

100 watt output of the best performance you ever heard. Advanced design SSB transmitter that offers every feature you want—and more. \$695 Amateur Net



HO 105TR

Citizen-Ham band transceiver that incorporates a full-coverage receiver. Now available with built-in speaker in place of 24 hour clock there. of 24 hour clock-timer. \$219.50*†

tHQ 105TRS (Built-in speaker) \$224.50



S-100 S-200 SPEAKERS

Matching speakers for use with HQ 100A, HQ 110, HQ 105TR and HQ 145X, HQ 170 and HQ 180 respectively. Extended coverage. S-100 \$14.95 S-200 \$19.95



NEW ELECTRONIC KEYER EK-1B

contained, battery operated unit with its own built-in speaker. Features ratio control which permits personal "touch" and a full range of speeds for novice or expert operation.
\$39.95 Amateur Net

IMPROVED NOISE SILENCER

Complete, ready to install unit that suppresses impulse noise level in any loca-tion for HQ 170 and HQ 180 receivers. Eliminates ignition or other pulse-type noise that would otherwise obliterate \$33.50 Amateur Net

CRYSTAL CALIBRATOR-XC 100

New plug-in type—provides markers every 100 KCS. HQ 145X, HQ 170, and HQ 180 chassis factory prepared for XC-100 in-\$15.95 Amateur Net stallation.



MANUFACTURING COMPANY, INC., an affiliate of Telechrome

53 West 23rd Street, New York 10, N, Y.

LEO I. MEYERSON, WOGFQ, SAYS:

Now You Pay "NO MONEY DOW

WITH OUR NEW CHARG-A-PLAN CREDIT PROGRAM® (\$20.00 Min.)

- ADD-ON PURCHASES AS YOUR CREDIT GROWS
- SMALL MONTHLY PAYMENTS
- PROMPT SHIPMENT

WRL 's New Comet Kits and

Receives **Transmits** ALL BAND VERTICAL ANTENNA KIT

80-10 Meters

Designed as a space and money saver.
... Ground or roof mounted, self-supmounted, self-sup-porting; handles up to I KW on 10-80M; band change by tap-ping clip. No guys; no radials; 23 feet overall. Heavy wall aluminum tubing, 52 ohm coax fed.

> NO MONEY **DOWN**

Only



TC-6

Handsome, functional desk with sloping top, designed for Amateur or Experimenter use. Durable 34" Nova-Ply. Easily assembled in a few minutes without glue. Holds over 500 lbs. Handy, slide-out leaf. Wood-Mosaic finish. Full size: 49½x-29¾x31". Shpg. wt.: 99 lbs. Shipped truck or xxxxxxxx truck or express.

FIXED OR MOBILE

6M Transceiver

> Kit Only \$3995

New WRL TechCeiver-6 has superhet receiver, built-in noise limiter, is tunable 48-54 MC. Crystal controlled Xmttr. using std. Xtals. (FT 243-8MC). Over 1 watt output. Built-in push-to-talk. 9-tube performance. Smallest talk. 9-tube performance. Smallest Transceiver available: 5x93/4x6". Matching 115VAC supply, Kit \$15.95 Matching 12VDC supply, Kit \$224.95

SS-3



SIGNAL SLICER

Only \$1595

Boosts weak signals by narrow bandpass. For any 455 Kc Receiver IF, with no modification. Self-powered for 115VAC. Ultra high "Q" coils. Step-by-step instructions.

DUO-DOUBLETS WRL

COPPERWELD FOR STRENGTH

Dual band operation, single 52-ohm feed, copperweld wire. Weather proof insulators included. Usable on 15M. Full half wave, each band.

Model 84 (80 & 40 meters) Model 42 (40 & 20 meters)

NO MONEY DOWN

\$7.95

MONEY DOWN

BOX

Easily installed, heavy gauge steel, grey fin-ish. 115 volts. Bulb included. Simply at-tach cord to terminals of 115V antenna relay.

LARGE UNIT (10½x3½x3")

\$495

SMALL UNIT (134x27/x6%")

Antenna Tuner \$1095 MM-100



New Mini-Matcher Kit op-Xmttr. of Oow CW, erates with any Xmttr. of power input 100w CW, 75w Fone or less. Matches to high impedance anten-nas. Unbalanced input and output. High quality ma-terials & assembly manual.

COLINEAR 6-METER

VERTICAL

Self-supporting vertical, 13 ft. high. DX power gain from the ½ electrical wave vertical radiator. Uses ¼-wave radials. Clamps to std. masts up to 1½" O.D. 3 DB gain on 6M. 52 ohm coax fed. ohm coax fed.

Only \$2995



Only

Light weight, spaced for Light weight, spaced for maximum gain (7 db). F/B 18 db. Rugged 4½ ft. boom. Aluminum. May be rotated with TV rotator. Can be shipped parcel post.

Regular 10% down payment plan still available to our customers!

Hallicrafter Equipment

From "the house the hams built" OFFICIAL HALLICRAFTERS WARRANTY SERVICE STATION



for Novice, Technician, General!

MODEL SX140

A high performance, low cost ham band receiver, 80-6 meters. AM/CW/SSB, BFO/Q multiplier, antenna trimmer, ANI, "S" Meter and many other features. Wirel, \$124.95. Kit, \$89.36

MODEL HT40

Carefully designed AM/CW transmitter for 80-6 Meters. Crystal, or external VFO control (with HA5 VFO). 52 ohm pi output with TVI shielding. Dual range metering. Excellent CW keying. 75 watts maximum input power.



MODEL HT32B

IUST \$72500

Amateur Net

A new table top, high efficiency amateur band transmitter, providing SSB/AM/CW/FSK output on 80-10 meters (full 10M coverage). A new dial calibrated directly to 1 KC. New sealed crystal filter for best performance. 144 watts input (PEP). Both sidebands on AM. 52 ohm pi output. Full VOX and break in CW.

Companions for the Most Discriminating Amateur Operation SSB / AM / CW / FSK

Complete ham band coverage 80-10 meters plus tuning range for external 2 and 6 meter converters. Dual conversion, SB selection, built-in calibrator. Every feature carefully designed to result in top performance on reception, be it AM/CW/SSB/FSK.

MODEL

SX101A

JUST \$44500

Amateur Net



You Can Rely On HALLICRAFTERS For Superior Products!

BUY WRL USED GEAR WITH CONFIDENCE

2 WEEK TRIAL AFTER PURCHASE. We guarantee you must be satisfied with performance or you may return the equipment within 2 weeks for refund.

90 DAY PARTS WARRANTY. We guarantee your investment 90 days by our "Same as New" 90 day warranty on all parts.

BONUS FEATURE! Full 90 day return credit: WRL offers a 90 day return privilege whereby you can trade back equipment for full credit (subject to equipment not being damaged) on any of our NEW equipment of being damaged) on any of our NEW higher value. All shipping F.O.B. WRL.



Giant Wall Maps HAM OR CITIZENS BAND

Send for these Call Area maps for your Ham Shack today! 28x36", in multiple colors, showing various call areas for either Amateur Radio or Citizens Band, time zones, monitoring stations, etc. Both now available at 50c each.

	V	₽		
A	`		4	
8		A	7	

WORLD RADIO LABORATORIES

3415 WEST BROADWAY

-	ΩI	IN	CII	RI	UF	FS. I	ΙΟν	VA	HB	63

LEO:	PLEASE	RUSH	ΜE	THE	FOLLOWING	COMET	KITS
HALL	ICRAFTE	RS GEA	\R:_				

SEND

LATEST FREE RECONDITIONED EQUIPMENT LISTS:

FREE FLYER

NAME: CALL: .

ADDRESS: _ _ CITY & STATE:_ RHEOSTATS

when you specify Ohmite components..

you build reliability into your product

RESISTORS

OHMITE®

INDUSTRY-PREFERRED COMPONENTS

RELAYS

TAP SWITCHES

TANTALUM CAPACITORS

VARIABLE TRANSFORMERS

GERMANIUM DIODES



RHEOSTATS—Insure permanently smooth, close control. All-ceramic, vitreous-enameled: 12½, 25, 50, 75, 100, 150, 225, 300, 500, 750, and 1000-watt sizes.

OHMITE RELAYS—Five stock models—DOS, DO, DOSY, CRU, new GR, in 235 different types, three of which are enclosed. At 115 VAC or 32 VDC, noninductive load, Models DOS and DOSY have a contact rating at 15 amp; Model DO, 10 amp; Models GR and CRU, 5 amp. Wide range of coil operating voltages.

TANTALUM CAPACITORS — Units are available in three types: subminiature, insulated, wire-type, in 13 sizes. All 5 MIL sizes of foil-type. Four sizes of slug-type tantalum capacitors. All feature high performance in minimum space and a wide range of capacitance and voltage ratings.

Write for Stock Catalog

POWER RESISTORS—Wire-wound, vitreous-enameled resistors. Stock sizes: 25, 50, 100, 160, 200 watts; values 1 to 250,000 ohms. "Brown Devil" fixed resistors in 5, 10, and 20-watt sizes; values from 0.5 to 100,000 ohms. Adjustable power resistors; quickly adjustable to the value needed. Sizes 10 to 200 watts, to 100,000 ohms. Wire-wound oxial lead resistors in stock sizes of 1, 3, 5, & 10 watts; values, 1 to 50,000 ohms.

R. F. CHOKES — Single-layerwound on low power factor cores with moistureproof coating. Seven stock sizes, 3 to 520 mc. Two units rated 600 ma; others, 1000 ma.

BE RIGHT WITH

OHMITE®

World Radio History

TAP SWITCHES—Compact, highcurrent rotary selectors for a-c use. All-ceramic. Self-cleaning, silver-to-silver contacts. Rated at 10, 15, 25, 50, and 100 amperes.

PRECISION RESISTORS—Four types available: molded silicone-ceramic, vacuum-impregnated, encapsulated, or metal film. Tolerances to ± 0.1% in ½, ¼, ½, ¾, 1, and 2-watt sizes, from 0.1 to 2.000.000 ohms.

VARIABLE TRANSFORMERS—Model YT2, 1½ amp rating, output voltage, 0-120/132V; Model YT4, 3½ amp rating, output voltage 0-120/140V; Model YT8, 7½ amp rating, output voltage 0-120/140V; Model YT20, 20 amp rating, output voltage, 0-120/140V. Also 36-volt units. Input voltage all models, 120V, 60 cycles. Thirty-nine stock models, cased and uncased.

OHMITE MANUFACTURING COMPANY 3608 Howard Street, Skokie, Illinois

MASTER MOBILE-TOPS IN QUALITY & PERFORMANCE

NEW DELUXE HI-"O" COILS



New wide space deluxe antenna coil. Greater efficiency on individ. bands. Easily handles 750 W. P.E.P. Lightest coil of its kind commercially avail-able. Use with 36" base sect. 60" whip.

sect.	•	•	•	٠.	••	۲	٠		
15M								. 5	5.95
20M						,			6.95
40M									7.95
75M		٠							9.95
160M				٠		٠			14.95



FIBRE-GLAS ANTENNA

The Feather-Weight with The Feather meight. Com-Spring-Steel Strength. Com-Fibreglas covering, minimizes electrostatic noises generated by heat, moisture and foreign particles in the air.

FG-80 60" \$4.95 FG-72 72" \$4.95 FG-84 84" \$5.15 FG-96 96" \$5.25 FG-103 103" \$6.95

MASTER-MAGIC TUNABLE WAND

New! band. easy-to-install, single top-loaded, plastic covered fiber-glas antenna. Maximum performance on the desired band.

10 Met.- 5 Ft. L \$8.95 11 Met. - 5 Ft. L. 8.95 15 Met.- 5 Ft. L. 8.95 20 Met. 5 Ft. L. 8.95 9.95 40 Met.- 6 Ft. L. 80 Met. - 6 Ft. L. 9.95



6 or 12 volt madels

Complete \$2495

MASTER MATCHER & FIELD STRENGTH METER. Automatically tunes entire band by remote control.

MULTI-BAND COILS

New plug-in type, operates with std. 3' base, 5' whip. Q of 525. 500 W input. Oper. with 52 ohm cable. Factory pre-tuned.

No. 900-10,15,20,40,75M No. 999-10,15,20M No. SSB-156-40, 75M YOUR

CHOICE \$1495

TWIN 6 - 2 METER BEAM



May be rotated by TV rotor. Complete with baluns, match. harness to 52 ohm. Vertical or horiz. pol. Trem. forward gain. Excell. front to back ratio. Lightweight, sturdy.

With PL-259 COAX \$1695

NEW! SLIM-JIM ALL-RAND BASE LOADING 96" ANTENNA COIL WHIP FOR 10, 11, 15, 20, 40, 80 **METERS** SIZE 1%"x 19" Positive action, just slide whip in or out to loading point and lock nut into position. NO. B-1080 \$1795

MONOPOLE ANTENNA

Folded radiating element for installation requiring a ground plane configuration and a wider useful range.

SR-600-2 2 Met. \$14.95 SR-600-10 10 Met... 24-50 SR-600-11 11 Met... 24-50

SR-600

WRITE FOR FREE CATALOG



UNIVERSAL MOUNTS

Heavy duty comm. ant. mts. Can be attached through opening as small as 3/16". For spring or whip. Pheno insulators. 3/4"-24 th. 530 Double SS. \$21.95

531 Single SS. 11.95 520 Db. S-Cad. Pl. 7.95 519 SI. S-Cad. Pl. 4.95



No.444 \$17.80 No.445 \$7.95 No.446 \$13.45 Adjustable to any bumper. No holes to drill.

MOUNTS











No. I-11 Swivel Mount Fits all antennas 3/4"-24th. \$2.95

140 100WX 232 Series Model 232-C

Base Mount—H.D.—Dble. Tpred. Spring—Swivel Base\$ 9.85
Base Mount—H.D.—Dble. Tpred. Spring—Coax, Conn.
9.85
Base Mount—H.D.—D. Tpd. Sg.—Sp. Sless—Coax Conn. 14.95 232KSS Base Mount—H.D.—Dble. Tpd. Spg.—Spec. Stainless ...
321 or 321C Base Mount—Where no spg. des.—w. sp. rig. type ball jt.

All products are for Universal Use-Mobile, Home, Marine, C.A.P., Civil Defense, Emergency, etc.



Master Mobile Mounts, Inc. 4125 W. JEFFERSON BLVD. . LOS ANGELES 16, CALIF.

232X 232XC 232XSSC

> AT LEADING RADIO JOBBERS **EVERYWHERE**

BELDEN-

Wire and Cable for every Ham Application

Ham Transmission Lines—RG/U Type

Belden 72-ohm RG/U Cables are designed for lowest losses, longer service life, and maximum dependability. Cables are essentially flat with no peaks in attenuation to reduce signal on either high or low frequencies.



8238 Type RG-11/U

Ham Transmission Lines— Parallel Type


Belden transmission line cables are made with brown virgin polyethylene for best weather resistance and lowest losses. Uniform quality control prevents standing waves and mismatches.



8210 72 Ohm—1 KW (RF) Rated

Power Supply Cables

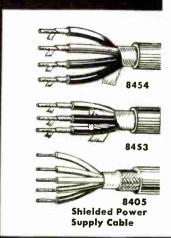Provide dependable service as power supply cords, interconnecting cables on electronic equipment, remote control circuits, special press-to-talk microphone circuits, and other ham applications. Designed for long service life with excellent mechanical and electrical characteristics, and uniform quality. Special jacket offers maximum resistance to abrasion and ozone.




Service Rated-

Quality Controlled-Easy-to-Use-**Packaged Lengths**



High Voltage Lead

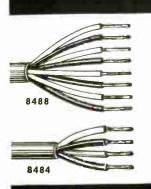New, improved lead offers smaller diameter and greater flexibility and voltage .150" OD, 25,000 V working voltage and 50,000 V breakdown.



Antenna Rotor Cables

Sturdy, flexible, plastic insulated cable for all Ham antenna rotor applications. Cables are color coded for easier hook-up. Chrome, vinyl plastic jacket resists sun and aging.



Coiled Retractile Cables Microphone — Telephone

A variety of types and lengths for most applications. Microphone cables offered with 1, 3, and 4 conductors in vinyl and neoprene—telephone cords with 3 and 4 conductors, vinyl only.

Hook-Up Wire

All colors, types, sizes, insulations, and temperature ranges in stock at your jobber. Available in packaged lengths for easy handling.

8525

Magnet Wire · Lead Wire · Power Supply Cords · Cord Sets and Portable Cord • Electrical Household Cords • Electronic Wires • Welding Cable • Automotive Wire and Cable

orld Radio History

electro

HELPFUL CHARTS & LITERATURE FREE: Write for CONDENSED TUBE CATALOG, information at a glance, rapid tube data reference tables, 25 pages of condensed information arranged for quick reference, Address your distributor or Amperex direct.

COMMUNICATION

RECTIFICATION

SPECIAL PURPOSE

RADIATION DETECTION

AMATEUR

ELECTRO-MEDICAL

SEMICONDUCTORS

Detailed Data Sheets on any of the tubes, and applications engineer service are yours for the aski

RADIATOR CREOIT FOR FORCED AIR-COOLED TUBES

	Allowar
889RA	\$20
891R, 892R	
5604	75
5667	20
6445	
6447	30
6757	75
6801	75

**Price on request. †Price includes 10% Fed. Excise To ALL PRICES SUBJECT TO CHANGE NOTICE

ask Amperex about AMPLIFRAME tube

*AMPLIFRAME, a new concept electron tubes, designed and ma produced exclusively by Ampere incorporates the unique FRAME GR ...the closest approach to the ide "Physicists' grid"—electrical chara teristics but no physical dimension The FRAME GRID results in: . high transconductance per milliampere tighter Gm and plate current toli ance . low transit time . low capatances . lower microphonics . rugg construction



















7093

6977









7459





18515

6688

The prices shown here are suggested list prices. For original equipment manufacturer prices, please write directly to the factory.

6FY5

ELECTRONIC CORP. HICKSVILLE, L. I., N. Y.

IN CANADA: PHILIPS ELECTRONICS INDUSTRIES LTD., TUBE, SEMICONDUCTOR & COMPONENT DEPTS., 116 VANDERHOOF AVENUE, TORDNTO, 17.

Suggested Type No. Resale Price	Suggested Type No. Resale Price	Suggested Type No. Resale Price	Suggested Type No. Resale Price
BEAM POWER TUBES	PENTODES (Con't) *16EJ7 2.90	TETRODES (Con't) 4CX250F 39.35	TRIODES (Con't) 5619 423.00
807 \$3.50 6146 5.90	‡8BQ5 2.60	4X150A 29.35 4X150D 29.35	5658 595.00 5666 280.00
6159 5.90 PE06/40N 5.95	‡45B5 3.50 828 27.60	4X250B 36.50 4X250F 36.50 4X500A 128.50	5667 370.00
DIODE, CLIPPER	5654/6AK5W 3.45 *5847 17.50	4X500A 128.50	5771
COUNTERS, GEIGER	6007 1.50 6008 1.50	6075 250.00	5866 20.00 5867 30.00
75N \$16.50	6083 14.25 6084 3.75	6079 60.00 6155 36.00	5868 55.00 5923 165.00
75NB3 16.50 90NB 27.00 90NB3 27.00	6227 3.75 16267 2.75	6156 46.50 6883 5.90	5924 231.00 5924A 275.00
90NB4 27.00	6375 11.50 6686 5.00	6979 42.50 7527 48.00	6333 290.00 6445 455.00
100C 54.00	6688 8.00 6688A 8.06	7609 29.35 ‡7699 16.00	6446 305.00
100CB 58.00 100HB 54.00	6689 4.50 ‡7189 3.60	TETRODES, BEAM 813 \$21.10	6756 388.00
27.00	*7534 16.50 7693 4.20	7378 45.00	6757 535.00 6758 173.00 6759 206.00
120CB 95.00	7694 4.20 •7737 9.00	TWIN TETRODES 829B \$19.00	6800 350.00 6801 505.00
120NB 95.00	EFP60 8.75 ‡EL37 5.75	832A 15.90 5894 COMM 32.40	6960 150.00 6961 210.00
150NB 66.00	PENTODE, DUO-DIODE	5894 MIL 35.40 5895 18.50	6961 A 230.00 7004 160.00
153C 91.00 200C 67.00	#6DC8 \$3.25 TRIODE-PENTODES	6252 32.40 6360 COMM 6.30	7092 125.00
200CB 71.00 200HB 67.00 200N 56.00	‡6BL8 \$3.80 ‡6BM8 3.20	6360 MIL 6.70 6907 32.40	7459 230.00
200NB 20.20	‡6DX8 3.20 ‡6U8 3.30 ‡50BM8 3.50	6939 14.00 7377 25.00	7805 402.00
230C 43.00 230N 41.00 240C 43.00	‡50BM8 3.50 7643 5.25	THYRATRONS	7807 584.00
2400 43.00 240N 41.00 912NB 53.00	PHOTOMILI TIPLIERS	2D21 \$ 1.85 3C23 11.98	HF300 40.50
COUNTING,	50AVP \$ 62.00 50AVP-SP 78.00	632B 36.00 5632/C3J 15.50	TBL2/500 270.00
INDICATOR TUBES	50AVP	5684/C3JA 19.80 5685/C6JA 27.80	TRIODE, INDICATOR
Z302C \$11.80 Z303C 10.65 Z502S 11.50	53AVP 80.00 53AVP-X 88.00	5727 2.70 AX260 150.00	6977 \$3.50
Z502S 11.50 Z510M 11.00 Z550M 12.00	53UVP . 462.00 54AVP . 158.00 55AVP . 210.00 56AVP . 496.00 56UVP . 696.00	THYRATRONS, HYDROGEN	TWIN TRIODES *14ES8 \$4.55
ET51 61.00	55AVP 210.00 56AVP 496.00	6268 \$32.50 6279 45.00	*14ES8 . \$4.55 6AL5W . 2.10 16AQ8 . 2.60 *16DJ8 . 2.45
ET51 61.00 6370/ET 5.25 6370/EIT 16.50	56UVP 696.00 57AVP 850.00	THYRATRONS, MERCURY 5557/FG17 \$ 9.50	*16ES8 4.33
DIODES, DAMPER	57AVP 850.00 58AVP 850.00 150AVP 62.00 150AVP-SP 76.00	5559 23.00 5560/FG95 33.00	*‡6GM8 4.55 ‡6J6 2.80
6R3/EY81 2.80 16AQ3 2.60	150AVP-SP 76.00 150CVP 84.00	5869 25.00 5870 100.00	19AQ8 3.10 112AT7 3.05
TWIN DIODE	RECTIFIERS	6786 200.00 AX105/FG105 . 53.33	112AU7 2.45 112AX7 2.55
5726/6AL5W \$2.10	11S2A \$ 2.75 15AR4 4.20 15RAGY 1.90	THYRATRONS, XENON	117EW8 2.60 5920 2.95
DIODE, VTVM 6923 \$13.00	‡6CA4 2.10	2050 \$ 3.35 5544 30.50	6085 3.75
IGNITRONS	‡6X4 1.65	5545 29.30 TRIODES	6211 2.35
5551A \$ 65.00 5552A 99.00	575A 22.15 673 22.15 8020AX 24.00	*12ER5 \$ 2.80	*6922 5.50 *6922 MIL 5.50
5553B 245.00 5555 316.00	RECTIFIERS, MERCURY	* † * † 3ER5 2.80	17025 2.90 7062 2.40
5822A 116.00 7585 99.00	857B \$235.00 866AX 3.10	*13FY5 2.80 16AT6 1.90	7119 3.15 *7308 6.00
TUNING INDICATORS 1M3 \$1.95	869B 160.00 869BL 160.00	#16AV6 1.65 #16ER5 2.45 #16FY5 2.80	7316 2.00 E92CC 2.40
6BR5 2.45 6CD7 3.65	872AX 11.65 6508 80.00	*16FY5 2.80 16Q4 6.00 16R4 5.10	TRIGGER TUBES COLD CATHODE
	6693 25.00 7136 25.00	356 660.00 450TH 77.00	7710 \$1.95
6FG6 2.95 DM71 2.00	8008AX 10.65	450TL 77.00 501R 225.00	750T 2.20
KLYSTRON, REFLEX 2K25 \$39.50	RECTIFIERS, XENON	502 210.00 502R 235.00	Z70U/7710 1.35 Z70W/7709 2.10 Z71U/7711 1.95
MAGNETRONS	VOLTAGE REFERENCE	504R 245.00 805 20.10	Z300T 4.95 Z803U 5.50 Z805U/7714 2.35
2J42 \$ ** 5586 417.00	TUBES	810 25.65 811A 8.10	
6972 325.00 7091 **	85A1/OE3 \$2.75 85A2/OG3 2.50 5651 2.50	812A 8.10 833A 53.65	PHOTO CONDUCTIVE CELLS
PENTODES \$ 2.90	VOLTAGE REGULATORS	834 19.30 838 20.00	ORP11 \$ 2.95 ORP30 3.80
*;3EH7 \$ 2.90 *;3EJ7 2.90 *;4EH7 2.90	ΟΔ2 \$1.75	845 20.80 849 185.00	ORP50 3.80 ORP50 1.95 ORP60
*;3EJ7 2.90 *;4EH7 2.90 *;4EJ7 2.90 ;6AU6 2.10	0B2 1.90 90C1 2.50 150B2/6354 3.00	849A 165.00 880 595.00	ORP6075 ORP6175 ORP90 1.95
16BA6 2.00	0334 3.00	889A 235.00 889RA 370.00	61SV 22.00
16BX6 3.15 6CA7 5.60	TETRODES 4-125A \$ 36.00	891 275.00 891R 430.00	PENTAGRID 6687 \$1.55
16CW5 3.50 16DA6 2.85	4-250A 46.50	892 270.00 892R 425.00	BEAM DEFLECTOR TUBE
*16EH7 2.90	4-400A 48.00 4CX250B 39.35	5604 570.00	6218 \$15.00

Surprise!

WALTER ASHE TRADES HIGHER

the always has since 19221

You always save money dealing with Walter Ashe Radio... because we always offer you more for your used transmitters, receiver or other surplus amateur gear*. Find out for yourself... tell us what you have to trade and what you want. We guarantee you'll be genuinely surprised by the Walter Ashe deal! Use the coupon below... mail it today!

DO YOU HAVE OUR NEW 144 PAGE AMATEUR CATALOG?



Check the coupon
...get the amateur's
most complete
catalog of the newest
in equipment, parts
and supplies ...
everything
you need!

Made since 1945

Catalogs mailed only to U.S. and Canada

WALTER ASHE RADIO CO.

Dept. H-62, 1123 Pine St., St. Louis 1, Mo.

WALTER ASHE RADIO	COMPANY
	Street, St. Louis, Missouri
What is the Ashe "Surpr	rise" allowance on
Name	
Address	<u> </u>
City	ZoneState
Send New Catalog	☐ Send Reconditioned Bulletin

9 mportant

AGVERTISING IN THE 1963 HANDBOOK AT NO CHARGE TO QST ADVERTISERS WHO QUALIFY

TO ALL ADVERTISERS IN QST AND THE RADIO AMATEUR'S HANDBOOK AND THEIR AD-VERTISING AGENCIES

- a. An advertiser who uses a total of 6 pages but not as many as 15 pages in QST during the twelve months of November 1961 through October 1962 can run a half-page in the 1963 HAND-BOOK at no charge. The ad can be vertical or horizontal and either black & white or black & white and red.
- b. An advertiser who uses a total of 15 pages or more in QST during the twelve months of November 1961 through October 1962 and who buys one page or more in the 1963 HAND-BOOK can run one additional full page in the HANDBOOK at no charge. The additional page can be either black & white or black & white and red. Or, if the advertiser does not buy a page in the 1963 HANDBOOK he qualifies for a half-page as outlined in the preceding paragraph a.

QST and the Handbook —
The combination covering
the electronic markets:
Amateur, Industrial, Government

Advertising Department

AMERICAN RADIO RELAY

LEAGUE

38 La Salle Rd. West Hartford 7, Conn.



E-Z WAY QUALITY SERVES YOU BEST... ear After Year!



- NO GUYS
- TILTS OVER
- CRANKS UP & DOWN

55,000 PSI HIGH TENSILE STEEL FOR MAXIMUM STRENGTH!

CHALLENGER

Standard duty two section Tower. Cranks up to 40° and down to 24°. Will support 3 el., 15 M Mini-beam or 3 el. tribander at 40' in winds up to 50 mph without guys.

Model RBD 40-P (painted) \$ 99.50 Model with GPK D-40..... 50.00 or BAK-D (building attach kit). 6.75

RBD-40

HOT DIPPED GALVANIZED AFTER FABRICATION.

MEDALIST "40"

Sturdy two section tower. Cranks up to 41 ft. and down to 24 ft. Supports a triband or equivalent at 41° in 70 mph winds or 125 mph when cranked down.

Model GPK-S40 (ground post).... 75.00 Model BAK-S40 (building attach).. 10.50

SATELLITE "60"

A 3 section tower. Cranks up to 58' and down to 25°. Will support a 4 el., 20M full size beam or a 6 el. triband at 60° in wind up to 60mph. . .NO GUYS! 140mph cranked

Model GPK 60-3 (ground post)..... 120.00 Model BAK-X (building attach).... 17.00

RBX-60-3

RBS-40

- Self-supporting to 34 ft.
- Famous E-Z Way Rotor Head.
- Light weight 10 ft. section weighs only 29 lbs.
- Climbable ladder on three sides.

NEW "HP" Economy Series

The HP series is a low cost Ham tower that is built to take it. The famous E-Z Way design has incorporated 55,000 PSI steel into the manufacture of all towers. Light weight and easy to erect. Hot dipped galvanized, electric arc welded and comes complete with base plate and wall bracket.

Model HP-34

Model HP-44......101.90 Model HP-54.....118.85

G-10

G-10. . . FOR HAM, CB, TV or TWO WAY.

E-Z Way's "G-10" is all NEW! Here is the Tower designed to take it, with durability built-in every inch of its superb construction. 55,000 PSI steel ... X-Type bracing ... Light weight, 10 ft. sections weigh only 29 lbs. These are only a few outstanding features that make this tower the strongest of its kind in the field. Fast, easy erection, up to 280 ft. guyed, or 40 ft. self-supporting. Completely electric arc welded and hot dipped galvanized after fabrication.

The NEW "Stack Pole" lets you really get up there! DETAILS TO BE ANNOUNCED

WRITE FOR COMPLETE DETAILS ON ALL E-Z WAY TOWERS.

-Z WAY TOWERS, Inc.

P.O. BOX 5767

TAMPA 5, FLORIDA

your choice of 2 GREAT TIPE RANSM

designed by Hams... for Hams ...



to the highest Ham standards



Kit \$79.95 Wired \$119.95 *U.S. Pat. #D-184,776 "Top quality"—ELECTRONIC KITS GUIDE

Ideal for veteran or novice. "Clean" 90W CW, 65W AMphone with EXT plate modulation. 80 through 10 meters.

60-WATT CW TRANSMITTER #723 Kit \$49.95 Wired \$79.95

"Compact: well-planned layout. Clean-sounding, absolutely hum-free carrier; stable." — ELECTRONICS WORLD

Perfect for novice or advanced ham needing low-power standby rig. "Clean" 60W CW, 50W AM-phone with EXT plate modulation. 80 through 10 meters.



TRANSISTOR CODE PRACTICE OSCILLATOR #706

Complete with battery Select variable tone, flashing light, or both together. Phone jack for private use. Efficient speaker: clean loud signals. Kit \$8.95 Wired \$12,95



New! CITIZENS BAND WALKIE-TALKIE #740

Complete with re-chargeable battery and charger, 9 tran-sistors, 1 diode. Full superhet. U.S. made.

Kit \$54.95 Wired \$79.95



CITIZENS RAND TRANSCEIVERS

Superhet; prealigned xmitter osc; match different antennas network. Single

by variable "pi" & multi-channel models. From Kit \$59.95 Wired \$89.95



HIGH-LEVEL UNIVERSAL MODULATOR-**DRIVER #730**

Kit \$49.95 Wired \$79.95

Delivers 50W undistorted audio for phone operation. Can plate-modulate transmitters having RF inputs up to 100W. Unique over-modula-tion indicator. Cover E-5 \$4.50.



GRID DIP METER

Wired \$49.95 Kit \$29.95 Includes complete set of coils for full band coverage. Continuous coverage 400 kc to 250 mc. 500 ua meter.



Kit \$25.95

PEAK-TO-PEAK EAK•TO•PEAK ¬ VTVM #232 ≌ & exclusive N 0

*UNI-PROBER Kit \$29.95 Wired \$49.95



DC-5MC LAB & TV 5" OSCILLOSCOPE #460 Kit \$79.95 Wired \$129.50

5" PUSH-PULL OSCILLOSCOPE #425 Kit \$44.95 Wired \$79.95



DYNAMIC CONDUCTANCE TURE & TRANSISTOR TESTER #666

City

Kit \$69.95 Wired \$109.95 TUBE TESTER #625 Kit \$34.95 Wired \$49.95



RF SIGNAL GENERATOR #324 (150kc-435mc) Kit \$26.95 Wired \$39.95

TV-FM SWEEP GENERATOR & MARKER #368 Kit \$69.95 Wired \$119.95

EICO

ELECTRONIC INSTRUMENT CO., INC. 3300 NO. BLVD., L.I.C. 1, N. Y.

Export Dept., Roburn Agencies, Inc. 431 Greenwich St., N. Y. 13, N. Y.

EICO, 3300 N. Blvd., L.I.C. 1, N. Y.

☐ Send free Catalog & name of Address.

☐ Send Free Catalog & name of neighborhood distributor.
☐ Send free "Short Course for Novice License." ☐ Send 36-page STEREO HI-FI GUIDE: 25c enclosed for postage & handling.

Zone State Add 5% in the West.

ENGINEERS: Excellent career opportunities in creative electronics design. Write to the Chief Engineer,

A General Electric Two-Way Radio to solve every communication need



General Electric's TPL: Extra-feature performance leader

Ceneral Electric's Transistorized Progress Line offers highest performance...plus standby battery drain so low that you never have to turn off your TPL unit...fix in more places, in more positions, than any other two-way mobile radio you can buy.



The Progress Line: Proven performance leader

Since 1955 General Electric's tubed Progress Line has served customers with economical, high power, high reliability two-way radio. A wide range of models satisfies every mobile communication requirement. For field-proved performance and low maintenance cost even under the most rugged conditions, specify the Progress Line.

The General Electric Pacer: Compact economy leader

The General Electric Pacer gives you every advantage of quality FM communication for limited range applications at the exceptionally low price of \$419.00 . . . and the lowest battery drain of any mobile radio in its class means important additional savings.



Many successful General Electric mobile radio authorized service stations were founded by licensed radio amateurs, and many now utilize the skills of hams on a part-time or full-time basis. Find out how you can become a General Electric service technician. Write National Service Manager, General Electric Company, Communication Products Department, Section 31, Mountain View Road, Lynchburg, Va.





If It's Shown In This Handbook Henry Has It!

HENRY gets the new equipment First YOU get the world's best Terms!

Low Terms

You get the best terms anywhere because Henry finances all the terms with his easy time payment plan. 10% down (or your trade-in accepted as down payment), 20 months to pay.

Long Trades

Henry wants to trade and he trades big. YOU get truly liberal allowances on your equipment. Tell us what you want to trade. We also pay cash for used equipment.

Complete Stocks

Henry has everything in the amateur equipment field, new or used . . . transmitters or receivers, and Henry has the NEW equipment FIRST.

Low Prices

Henry's large purchasing power means low prices to you. You just can't beat our wholesale prices.

100% Satisfaction

Henry gives you a guarantee of "100% satisfaction" or your money back at the end of a 10 day trial.

rite, phone or visit a Henry Store Today!



Henry Radio Stores

Bab Henry WOARA Butler, Mo. ORchord 9-3137

> Ted Henry WALLOU 11240 West Olympic Blvd. Los Angeles 64, Calif. GRanite 7-6701

Walter Henry 931 North Euclid Anaheim, Colif



Norld's Largest Distributors of Short Wave Receivers"

Learn Code the EASY Way

Beginners, Amateurs and Experts alike recommend the INSTRUCTOGRAPH, to learn code and increase speed.

Learning the INSTRUCTOGRAPH way will give you a decided advantage in qualifying for Amateur or Commercial examinations, and to increase your words per minute to the standard of an expert. The Government uses a machine in giving examinations

Motor with adjustable speed and spacing of characters on tapes permit a speed range of from 3 to 40 words per minute. A large variety of tapes are available—elementary, words, messages, plain language and coded groups. Also an "Airways" series for those interested in Aviation.

MAY BE PURCHASED OR RENTED

The INSTRUCTOGRAPH is made in several models to suit your purse and all may be purchased on convenient monthly payments if desired. These machines may also be rented on very reasonable terms and if when renting you should decide to buy the equipment the first three months rental may be applied in full on the purchase price.

ACQUIRING THE CODE

It is a well-known fact that practice and practice alone constitutes ninety per cent of the entire effort necessary to "Acquire the Code," or, in other words, learn telegraphy either wire or wireless. The Instructograph supplies this ninety per cent. It takes the place of an expert operator in teaching the student. It will send slowly at first, and gradually faster and faster, until one is just naturally copying the fastest sending without conscious effort.

BOOK OF INSTRUCTIONS

Other than the practice afforded by the Instructograph, all that is required is well directed practice instruction, and that is just what the Instructograph's "Book of Instructions" does. It supplies the remaining ten per cent necessary to acquire the code. It directs one how to practice to the best advantage, and how to take advantage of the few "short cuts" known to experienced operators, that so materially assists in acquiring the code in the quickest possible time. Therefore, the Instructograph, the tapes, and the book of instructions is everything needed to acquire the code as well as it is possible to acquire it.

MACHINES FOR RENT OR SALE



The Instructograph

ACCOMPLISHES THESE PURPOSES:

FIRST: It teaches you to receive telegraph symbols, words and messages.

SECOND: It teaches you to send perfectly.


THIRD: It increases your speed of sending and receiving after you have learned the code.

With the Instructograph it is not necessary to impose on your friends. It is always ready and waiting for you. You are also free from Q.R.M. experienced in listening through your receiver. This machine is just as valuable to the licensed amateur for increasing his speed as to the beginner who wishes to obtain his amateur license.

Postal Card WILL BRING FULL PARTIC-ULARS IMMEDIATELY

THE INSTRUCTOGRAPH CO.

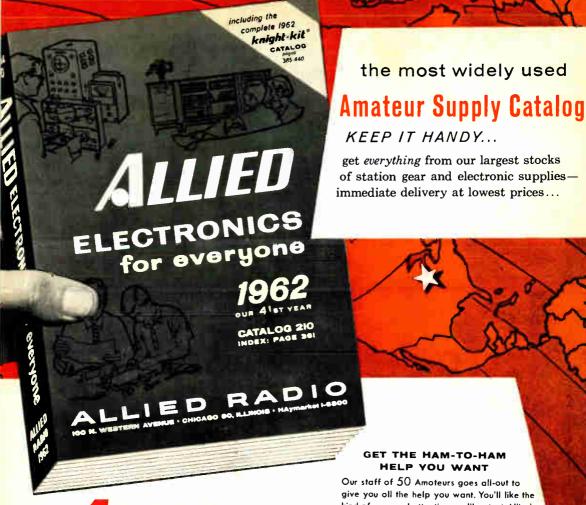4707 SHERIDAN ROAD 4700 S. CRENSHAW BLVD. CHICAGO 40, ILLINOIS
LOS ANGELES 43. CALIFORNIA



IIIFD

gives you every advantage

HIGHEST TRADES: Get the absolute most for your old equipment. Tell us what you've got and what you want—we'll come up fast with the best deal anywhere.

RECONDITIONED GEAR: Large selection, new set guarantee. Ask for latest list of top reconditioned equipment at lowest prices.

NO MONEY DOWN: Easiest terms ever with Allied's new Credit Fund Plan-up to 50% more buying power; up to 24 months to pay. Extra: 15-day trial on all ham gear.

ALLIED RADIO

100 N. WESTERN AVE., CHICAGO 80, ILL.

Serving the amateur for 41 years



Our staff of 50 Amoteurs goes all-out to give you all the help you want. You'll like the kind of personal ottention you'll get ot Allied. You'll get to know helpful Homs like:



W9WHF Jim Sommerville (Ham Division Manager)



WOVH Don Kobiljak (Trades & Tech Help-Mail or Phone)



(Ham Shack)

loe Huffman W9HLA Joe Gizzi



John Chass (Ham Shack)




Tasker Day (Ham Shack)



W9BHD

In Milwaukee W9NGV Lowell Warshawsky

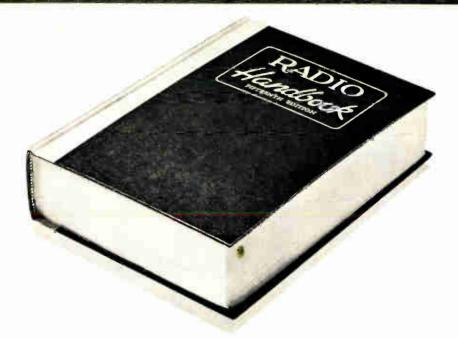

RADIO HANDBOOK

-gives comprehensive, up-to-the-minute data for designing and building radio equipment

Extensive theory—the Radio Handbook covers practically every phase of radio theory, in simplified, easyto-grasp form.

Latest design data - all original material-enables you to design any standard type of transmitting and receiving equipment, from medium to ultra-high frequencies.

Latest construction data-broadest coverage in the field. You get complete original information on how to build and operate advanced high performance equipment. Plans include details on attractive styling. All data clearly indexed. 800 pages all editorial — with hard cover. The largest RADIO HANDBOOK ever published.

at your dealer, plus any tax \$8.50



*Order from your favorite electronic parts distributor If he cannot supply, send us his name and your remittance, and we will supply; foreign, add 10%.

EDITORS and ENGINEERS, Ltd. Summerland 4, California

Dealers: Electronic distributors, order from us. Bookstores, libraries, newsdealers order from Baker & Taylor, Hillside, N.J. Export (exc. Canada), order from H.M. Snyder Co., 440 Park Ave. So., N.Y. 16.

RADIO SHACK

Your Headquarters For Amateur Gear!

HIGHEST TRADES . Correspondent

Call or write W1RY, Art Bates Amateur Radio Correspondent, c/o Radio Shack for a terrific

Use Radio Shack's New Revolving Charge! There's NO MDNEY DDWN and up to 24 months EASIEST TERMS . . There's NO MONET DUTTE and ap-

HAM EXPERTS . .

Everyone you talk to or write to concerning Amateur equipment will be a "Ham" himself, knowledgable, courteous . ready to serve you!



NC-155

NEW! NATIONAL RADIO COMPANY

. . For The Finest In Amateur Performance

NC-270 RECEIVER

\$15 monthly

A true performance pace-setter! Patented ferrite filter and instant sideband selection provide for upper and lower sideband with linear heterodyne detector and separate carrier reinsertion. Dual conversion 80 through 6 meter coverage, crystal calibrator. #44DX750

NC-190 RECEIVER

\$13 monthly

Advanced design general coverage receiver! Instant choice of calibrated amateur or popular foreign broadcast bands. Sensitivity better than 1.0 μv for 10 db S/N ratio. Ferrite filter provides 600 cy., CW, 3 KC SSB, 5 DC AM bandwidths. #450X380

NC-155 RECEIVER


RADIO SHACK CORPORATION, Dept. RA-H

730 Commonwealth Ave., Bastan 17, Mass.

Name Address

City

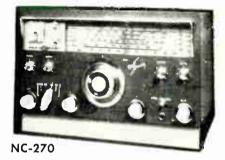Designed exclusively for ham band operation, NC-155 features superb sensitivity (1 μv for 10 db S/N on all bands), top stability and shaped selectivity! Double conversion on 80 through 6 meters. SSB/CW AGC, separate product detector, #45DX739



NC-190

NTS-3 SPEAKERS

For All Of The Above Receivers

Please "QUOTE BIG" on my model I would like to trade in toward 🔲 I would like to purchase State ☐ Check ☐ Money Order ☐ C.O.D.



Modern Design

• Top Performance

Designed from a single sheet of aluminum, the NTS-3 speakers are perfectly damped, low distortion reproducers. 4 cone diameter, 1mp. 3.29. #44DX751

NOW THERE ARE EIGHT RADIO SHACKS TO SERVE YOU

BOSTON, MASS. 730 Commonwealth Ave. **REgent 4-1000**

WEST HARTFORO, CONN. 39 South Main St. ADams 6-5441

BOSTON, MASS. 167 Washington St. REgent 4-1000

STAMFORO, CONN. 29 High Ridge Rd. DAVIs 5-4371

SAUGUS, MASS. E. Shopping Center CEnter 3-5350

NEW HAVEN, CONN, 230-234 Crown St. STate 7-7121


BRAINTREE, MASS. South Shore Plaza Victor 3-9200

PROVIDENCE-CRANSTON, R. I. 1301 Reservoir Ave.

SEND FOR BRAND NEW 1962 RADIO SHACK CATALOG! 336 BARGAIN-FILLED PAGES!

VIBROPLE X

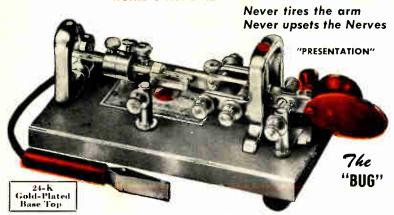THE PIONEER AND ALWAYS THE LEADER WORLD'S NO. 1 KEY SEMI-AUTOMATIC



New Super DeLuxe VIBROPLEX

Presentation

The Super DeLuxe model's JEWEL MOVEMENT completely revolutionizes sending. Makes it easy for every operator.

It has SUPER-SPEED CONTROL mainspring; you go from slowest to highest speed without changing weights.

Vibroplex has TOUCH CONTROL, adjustable to your individual desire.

Vibroplex has FIRM STANCE, a very important item. The rubber feet are so placed the key stays in position.

RICHLY DESIGNED — 24k goldplated base top, polished chromlum machine parts, red trim and jeweled movement. DeLuxe, only \$33.95.

ALL LABOR TAKEN OUT OF SENDING

SEND BETTER — Vibroplex makes uniformly good signals at any speed. They are sharp and easy to read. You will like them.

SEND EASIER—Vibroplex is a perfectly balanced key. You are relieved of all nervous and muscular tension. SEND FASTER — Vibroplex gives you greater speed. More speed than you can ever use. But it's there if you need it.

SEND LONGER — Vibroplex keys last longer. Many keys are still in use after 30 or more years. Nothing to get out of order.



Vibroplex Lightning Bug

Improved design with slotted weights that can't work loose. A bridged damper frame that protects key as all damage, may be removed without disturbing speed weights. Precision machining, trouble proof and adjustable to any speed. Standard, with circuit closer, gray base and chrome top parts, priced at \$21.45. DeLuxe model, priced at \$25.95.*



Vibroplex Original

Praised by its many thousands of satisfied users for ease of operation, sharp, clear signals and all around excellence. They are precision machined and trouble proof. A strong favorite of the elite. Standard, with circuit closer, chrome top parts and gray base, \$19.95. DeLuxe, with red trim, lewel movement and pollshed chrome base, \$23.95.



Vibroplex Blue Racer

A duplicate of the Original Vibroplex except for being only half the size, weight 2 ibs. 8 ozs. Does the same die work as the larger models. Standard, with circuit closer, chrome top parts and gray base, \$22.45. DeLuxe, with chromium base and top parts, red trim and jewel movement, priced at \$26.95.*

Avoid imitations! The "BUG" Trade Mark identifies the Genuine Vibroplex. Accept no substitute Replace your old-fashioned key with all its annoyances with an improved NEW VIBROPLEX. Enjoy sending as never before. Choose yours from those illustrated here.

"VIBRO-KEYER"

Supplies the answer to many years of requests for Vibroplex parts for a keying mechanism in constructing an electronic transmitting unit. Features a beautiful base, size 31-8 by 41-8 and weighing 2 pounds. Red finger and thumb pleces, same large 1 contacts on main frame and trunion lever as used in Vibroplex. A real beauty, adjustable to suit your speed requirements, standard model, priced at \$17.95; Deluxe model, with Chrome Plated Base, priced at only \$22.45.

*Cord and wedge, \$1.75 additional.



NEW SPECIAL ENLARGED Edition of PHILLIPS CODE, \$2.75 Postpoid

Also includes: Radio Code Signals International Morse American Morse Russtan, Greek, Arabic Turkish and Japanese Morse Codes World Time Chart United States Time Chart Commercial "?" Code Aeronautical "Q" Code Miscellaneous Abbreviations. Used international wire, submarine cable and radio telegraph circuits.

Get your copy today!

Prices subject to change without notice

Vibroplex Carrying Case

Keeps key like new. Black simulated morocco. Flexible leather handle. Protects key against dust, dirt and moisture. Insures safe-keeping when not in use. With lock and key, \$6.75.

Every Vibroplex key has 3/16 contacts and is available for left-hand operation. \$2.50 extra.




THE VIBROPLEX CO., Inc., 833 Broadway, New York 3, N. Y.

W. W. ALBRIGHT, President

IF YOU SEND YOU SHOULD USE THE VIBROPLEX

Buy Vibroplex for the easiest sending of your life

Certified Performance

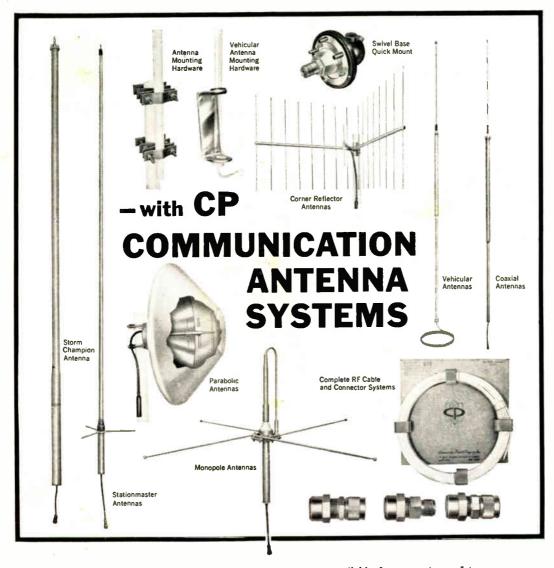

CP "certified performance" components are available for every type of two-way communication installation. Specify CP for base station and vehicular antennas, coaxial cable systems, hardware and accessories. Consult CP for recommendations on your specific requirements.

New catalog available! Contains complete information on CP antennas and accessories plus a handy technical data section. Write on company letterhead for your copy, today!









6th Edition

RADIO OPERATOR'S LICENSE Q & A MANUAL

—by Milton Kaufman—

Completely up-to-date to May 15, 1961 with new supplement. All FCC question revisions and question re-numbering.

More people have earned their commercial radio licenses with this famous book than with any other available today.—It is the best book for FCC license preparation! It is just as indispensable to anyone who desires a commercial 'ticket' as it is to the licensed operator, as a reference volume. Truly, it is a book anyone interested in radio operation can't afford to be without. The Q&A Manual covers elements 1 through 8. It is the only book giving the question—the answer and a detailed follow-through discussion on every vital technical question in the FCC Study Guide. This makes it very easy to answer correctly multiple choice questions!

It is so effective as a teaching aid that it is the standard text in schools teaching commercial radio operating as well as by industrial organizations. All fundamentals required for all kinds of commercial licenses are included. Numerical examples in the follow-through discussion show how problems are solved and answers arrived at. There are many illustrations to make the technical management of the solution o

There are many illustrations to make the technical questions and answers picture-clear. The manual is based on government study guide and supplementary FCC releases. In every regard, there is no equal to this book.

Here is what leading publications in the communications field say about the Q&A Manual, "Thorough treatment"—QST.

up-to-the-minute . . . presentation. Method is clear, logical and easy to read . . ." WIRE AND RABIO COMMUNICATIONS.

Get it at your electronic parts distributor ar backstare, ar arder direct fram:



JOHN F. RIDER PUBLISHER, INC.

116 West 14th Street, New York 11, N. Y.
A division of Mandal Publishing Co. No. 1



Amateur Net \$675.

Have you heard about these new Clegg advances in VHF?

Spectacular advances in the field of electronics in recent years are presenting outstanding opportunities to manufacturers and the serious VHF amateur alike.

Research and development at Clegg Laboratories have played a consistent role in the design and engineering of superior VHF equipment for the serious operators on these bands. From this continuing research have come such products as the Clegg ZEUS transmitter for 6 and 2 meters, the INTERCEP-TOR VHF receiver, the 99'er transceiver for 6 meters, and the 2 x 4 audio oscillator.

Each of these units is outstanding in its field. The ZEUS, for example, provides 185 power-packed watts on both 6 and 2 meters. Automatic feedback control of low level speech clipping permits maximum talk power without splatter. The INTERCEPTOR receiver, using the latest nuvistors in r.f. stages, provides a noise figure of less than 2 db. and sensitivity of better than .25 microvolts.

The 99 er provides a complete VHF station for the ham with a limited budget.

Ask your distributor about these new Clegg VHF units today. Or write for complete information.

Clegg LABORATORIES

502 RT. 53, MT. TABOR, N. J. OAkwood 7-6800



Amateur Net \$139.95.

CLEGG 99'ER 6 METER TRANSCEIVER



FORT ORANGE Radio Distributing Com

904 BROADWAY ALBANY 4 N. Y. U. S.A. AMATEUR HEADQUARTERS

Cable Address "Uncledave"

CALL ALBANY HE 6-8411

NITES GR 7-5891

NOW THAT LONG WINTER EVENINGS ARE COMING, YOU WILL WANT THAT SHACK OF YOURS TO BE IN SHAPE TO HANDLE THE INCREASING ACTIVITY OF THE BANDS WITH THIS HALLICRAFTERS EQUIPMENT



MODEL HT-37. The HT-37 has been carefully engineered to give you the best phasing unit at a moderote price. Complete tabletop high effi-



MODEL HT-41. Truly a ham's dream! The HT-41 linear amplifier is an ideal companion for the HT-37 in price, style, and performance. Complete coverage 80 thru 10 meters; adjustable

pi-network output; all circuits metered; built-in R.F. output meter to aid tune-up; standby bias supply. High efficiency, grounded-grid circuit; new 7094 beam-power. \$395.00



MODEL HA-4 "T. O. Keyer." "The Stradivarius of Electronic Keyers." Hallicrafters offers this equipment for the discriminating e.w. operator who wants perfection. The



MODEL S-120. Another popular Hallicrafters precision-built receiver with many desirable features: Covers broadcast band 550-1600 kc. plus three short-wave bands 1600 kc-30 Mc. Slide



MODEL SX-115. This is a new triple-conversion heterodyne type communication receiver. Combines highest accuracy, stability, sensitivity; linear tuning, constant tuning rate, built-in 100 Kc crystal calibrator, sensitivations.

sitivity less than 1 microvolt, selectable side bands, image rejection better than 60 db. band gain equalization, audio inverse feedback, and many other features. Covers nine 500 Kc segments.

3.5- 4.0 Mc 7.0- 7.5 14.0-14.5

21.0-21.5 28.0-30.0 (4 segments) WWV

\$595.00



MODEL HA-5 DELUXE VFO. High stability heterodyne-type for all bands. Three tubes plus voltage regulator and silicon rectifiers. Extreme stability. Illuminated dial calibrated for all amateur bands, 80 through 2 meters. Output frequency range: 3.5 Mc. to 4.0 Mc., 7.0 Mc. to 7.5 Mc.,

7.8 Mc. to 8.3 Mc., and 8.333 Mc. to 8.833 Mc. Excellent keying; 30 to 1 tuning ratio permits precise tuning....\$79.95

Write Uncledave W2APF with your needs and problems. TRADE-INS ACCEPTED AND FOREIGN TRADE SOLICITED BANK FINANCING

TIME PAYMENTS

18 Months to pay. Life Insurance at no extra cost UNCLE DAVE'S RADIO SHACK A SUBSIDIARY OF FORT ORANGE RADIO

air dux

AIR WOUND COILS



air dux®BALUN

Unbalanced coax lines used on most transmitters can be matched to balanced lines of either 75 or 300 ohms impedance by using the B2009 air dux coils. May be used with transmitters and receivers without adjustment over the frequency range of 80 through 10 meters, and will handle power inputs up to 200 watts.

Two coils required.
Coax connector not included.

B2009 MB2009 Coil with hardware Mounting plate



Standard Air Dux!

A wide selection is available from Jobbers nationally.



2 new pi dux assemblies

The 500 and 1000 watt pi dux assemblies are compact yet conservatively rated. The high frequency coil sections are silver plated for high tank circuit efficiency. A complete technical sheet is included with each assembly.

#195-1 500 watt pi dux Assembly #195-2 1 KW pi dux Assembly



indented pl dux®

Cat. No.	Dia	TPI	Size	of Coll	uh,
816A	1	16	18	33/10	18.0
1014A	11/4	14	18	22532	18.3
1212A	11/2	12	16	23/4	18.3
1411A	13/4	11	14	25/8	18.0
1609A	2	9	14	3	18.1
2007A	21/2	7	12	31/4	18.6
2406A	3	6	10	31/4	18.7



vari-pitch pi dux®

	-	-			
820D10	1	20 & 10	18	31/4	18.0
121206	11/2	12 & 6	14	313/16	18.6
1608D6	2	8 & 6	12	41/8	18.1
2008D5	21/2	8 & 5	12	33/4	18.2
2408D4	3	8 & 4	10	33/4	18.6

Special Designs?

That's our business! We now supply a majority of the air wound coils used by leading equipment manufacturers.



Illumitronic has the most complete line of PLASTIC ROD, TUBING and SHEET.



Also HARNESSING and CABLING materials:



ZIPPERTUBING SPIRAL WRAP SPIRAL COVER VINYL SLEEVING LACING CORD CABLE CLAMPS



illumitronic

sunnyvale,



california

engineering



Amateur Accessories always available at ARROW



TX-86, ONE OF THE MOST VERSATILE HAM XMTRS EVER MADE

90 W. CW, 90 W peak Phone 80 through 6 meters, easily adjusted for notice use
Mobile or fixed use, size: 5" x 7" x 7"
Xtal controlled or can take VFO
Final 6146 runs straight through on Pi-net output ckt, TVI suppressed

\$8495 Complete kit, specify 6 or 12v fil.....

\$10995

MODEL PS-3 AC POW, SUPPLY FOR TX-86 Completely wired and tested \$44.95

AC-1, NOVICE CW XMTR

Xtal controlled for 40 and 80 meters CW Pi-net output ckt, TVI sup-

Includes heavy duty AC Power

Supply 15 w. input; 6V6 osc., 6X5 rect.

Mod. AC-1 complete kit for any 1 band Extra coil kit for other band



\$19⁹⁵



2 & 6 METER CONVERTERS & POWER SUPPLY

Features included on both modele: Crystal Controlled RF Rejection: over 70 db spurious & image Gain: over 30 db

IF Rejection: over 100 db

Noise Figure: better than 4 db Tube Lineup: 2 meter Converter has new, imported 6ES8 high gain, low noise, cascode 1st RF Amp., 6U8A 2nd RF Amp. & Mixer, 6J6 Osc.—Multiplier.

6 meter Converter has 6BSS Cascode RF Amp and 6USA Mixer and Osc. 6 meter 2 meter 6 meter 2 meter Model Model

Converter complete with tubes and stal for 7-11 or 14-18 mc. IF output in Kit form with instructions Wired and tested

CB-6 CB-2 \$19.95 \$23.95 \$27.50 \$33.95 \$1.00 extra

Kit or Wired models for any other output frequencies (30.5-34.5 mc, 28-30 mc, etc.) Power Supply for CB-6 or CB-2

Mod. PS-IK, Kit Mod. PS-IW, Wired and Tested



LEARN CODE & THEORY FAST



TRANSISTORIZED CODE PRACTICE OSCILLATOR AND MONITOR

Serves as code practice osc, and phone-CW monitor without making any changes. Builds into small 2-piece satin finish copper case. Power required: 2 Eveready #912 cells.

\$485 CPS.MTK kit \$575 CPS.MTW wired



CODE PRACTICE OSCILLATOR, KITS

Available in kit or wired form. Produces a pure, steady tone without clicks or chirps. Will handle a large number of headphones or keys. Converts easily to an excellent CW monitor. Variable tone control and volume control. Bullt-in 4 speaker, Operates on 110 volts AC or DC.

Ameco No. CPS-KT-Kit, including tubes. Net Each...\$13.75

AUTHORIZED DISTRIBUTORS OF **ELECTRONIC PARTS & EQUIPMENT**

Arrow's Export Dept. Ships To All Parts Of The World

ARROW ELECTRONICS

65 Cortlandt Street, New York 7, N. Y. • Digby 9-4730 525 Jericho Turneike, Mineola, N. Y. • Ploneer, 6-8686

Trade-ins Welcomed

Your old equipment is worth money at Arrow. Get Arrow's deal before you buy.

With SPRAGUE CAPACITORS and RESISTORS you build Reliability into your equipment!

CAN-TYPE ELECTROLYTICS



Twist-Lok® Capacitors

Hermetically sealed in aluminum cases. Withstand high temperatures (85°C), high surge voltages, high ripple currents.



Screwbase Capacitors

Aluminum cases, Will withstand high a-c ripple. Available with lugs or Insulated wire leads. Common or separate negative terminals.



High µF Capacitors

Molded phenolic cases. Ratings to 10,000 μ F. Designed for low voltage (to 50V) filter circuits.

TUBULAR ELECTROLYTICS



Atom® Capacitors

Tiny, dependable single or multiple section units. Have low leakage, long shelf life. Metal case construction with outer Kraft tube.



Littl-Lytic® Capacitors

Ultra-small, excellent for transistorized circuitry. All-welded construction-no pressure joints to cause 'opens''. Low leakage, extremely long shelf life.

HYPASS® CAPACITORS



Exclusive 3-terminal feed-thru units which effectively by-pass vhf cur-rents. Suppress TVI from transmitters, diathermy, line-conducted radiation, etc.

PAPER-FILM TUBULARS



Black Beauty® Capacitors

Dual dielectric (polyester film and paper) combines best features of both. Solid impregnant, nothing to leak or drip. Molded case. Withstand high temperatures, high humidity.



Orange Drop® Capacitors

Dual dielectric (polyester film and paper), with solid impregnant. Double dipped in epoxy resin. Radial leads. ideal for printed wiring boards.

OIL CAPACITORS



Rectangular Oils

For transmitter power supplies and other high voltage applications. Hermetically sealed in rugged metal cases. Oil-impregnated, oilfilled. High insulation resistance.



Screwbase Oils

Cylindrical screwbase can for easy single hole mounting. Oil-impregnated, oil filled. Small size, will fit tight spaces.

SK-1 SUPPRESSIKIT®



Contains everything needed for effective mobile radio noise suppression of R-F interference beyond 400 mc. For autos with 6 or 12 V gen-

For complete data on these and other Sprague components, get Catalog C-614 from your Sprague Distributor, or write to Sprague Products Company, 505 Marshall St., North Adams, Massachusetts.

CERAMIC CAPACITORS



Cera-mite® Ceramics

Silvered flat-plate design for high by-pass efficiency, high self-resonant frequency. Tough moisture-proof coating. Available in general application, high-K, temperature stable, and temperature-compensating types.



Buttonhead Ceramics

Flat-disc capacitor element sealed in top of hex head for easy screw-mounting. Low self-inductance, high selfresonant frequency. Available for by-pass or feed-thru applications.

MICA CAPACITORS



"Postage-stamp" Micas

Silvered (\pm 5% cap.tol.) or standard $(\pm 20\%$ cap. tol.). Carefully-selected, electrically graded raw mica assures maximum quality



Transmitting Micas

Voltage ratings to 2500 WVDC, 5000 V Test. R-F current tested before and after molding.

WIREWOUND RESISTORS



Koolohm® Resistors

Insulated shell power resistors wound with ceramic-insulated wire. Completely moisture-proof. Ratings to 120 watts in inductive and non-inductive types.



Blue Jacket® Resistors

Vitreous enamel coating guards against humidity and failure from electrolysis. Ratings from 2 to 10 W.

world's largest capacitor manufacturer

EARN ONEY BIG MONEY

MOBILE-RADIO MAINTENANCE

Get into this rapidly growing field with 2nd Class Ticket and LAMPKIN MOBILE-SERVICE METERS



LAMPKIN 105-B MICROMETER FREQUENCY METER

FREQUENCY RANGE on local transmitters 0.1 to 175 MC – to 3000 MC by measuring in multiplier stages. ACCURACY conservatively guaranteed better than 0.0025%—actually 9 out of 10 results come within 0.001%. CALIBRATION table for each meter; charts show percentage off-frequency from FCC assignment. DIAL 4" diameter, 40 turns, totals 8000 divisions spread over 42 feet—resettable better than 5 parts per million. CRYSTAL thermometer on panel automatically indicates dial checkpoint. SIGNAL GENERATOR—a pinpoint CW source for mobile-receiver final alignment.



LAMPKIN 205-A FM MODULATION METER

FREQUENCY RANGE – Continuous 25 MC to 500 MC. No coils to change. Rough and vernier tuning controls. PEAK FM swing shows directly on indicating meter-calibrated 0-12.5 or 0-25.0 peak KC. positive or negative. No charts or tables. ACCURATE—within 10% at full seale. FIELD STRENGTH METER—Reads relative transmitter output. PROTECTED – Panel components recessed behind edges of the case, PORTABLE – Just a 2-finger load.

JUST THESE TWO METERS—WITH NO ADDITIONAL CRYSTALS OR FACTORY ADJUSTMENTS—WILL CHECK FREQUENCY AND FM MODULATION ON HUNDREDS OF TRANSMITTERS. LAMPKIN METERS ARE PREFERRED TEST EQUIPMENT—BY MUNICIPALITIES, 46 OUT OF 50 STATES, BY MOST 2-WAY RADIO MANUFACTURERS, AND BY THOUSANDS OF INDEPENDENT MOBILE-SERVICE ENGINEERS.

NEW . THE PPM METER . . AN ACCESSORY FOR THE TYPE 105-B . . ACCURACY BETTER THAN 0 0001%, AMPLE FOR SPLIT-CHANNEL FREQUENCY CHECKS.

FREE BOOKLET—with facts and figures—send for "HOW TO MAKE MONEY IN MOBILE-RADIO MAINTENANCE".

MAIL COUPON TODAY!

LAMPKIN LABORATORIES, INC.
BRADENTON, FLORIDA

Measurements Section Lampkin Laboratories, Inc. Bradenton, Florida

At no obligation to me, please send

- ☐ "Haw To Make Money in Mobile-Radio Maintenance!"
- Technical data and prices on Lampkin Meters

Name____

City_____

Zone____State__

DIRECTIONAL RF WATTMETERS



Model 43 and Rigid Line Series

Direct reading . . "thru" type measure forward or reflected power in complete systems under operating conditions . . . inserted between transmitter and antenna or load . . . full scale power and frequency range determined by plug-in elements.

50-Ohm nominal



		ELEM	ENTS
Model	Connectors	Frequency (mc)	Power Ranges
		2-30	50, 100, 250, 500 1000 watts
43	QC Type#	25-60; 50-125; 100-250; 200-500; 400-1000	5, 10, 25, 50 100, 250, 500 1000 watts
4712 4715°	1 % " EIA Flanged	2-30; 25-60; 50-125; 100-250; 200-500; 400-1000	.25, .5, 1, 2.5, 5KW
460 4610°	31/8" EIA Flanged	2-30; 25-60; 50-125; 100-250; 200-500; 400-1000	1, 2.5, 5, 10, 25KW
4902	61/8" EIA Flanged	2-30; 25-60; 50-125; 100-250; 200-500; 400-1000	2.5, 5, 10, 25, 50KW
4910	9" Flanged	Per Customer Specifi	cations

*Double Socket Thruline for monitoring of forward and reflected power.

to measure rf power... THRULINE

TERMALINE ... to absorb rf power

Model	Freq. Range	Max. Power	Power Range Scales	Input Connector
6254	30-500 mc	1 w	25, 50, 100, 250, 500 and 1000 milliwatts	Female "BNC"
61	30-500 mc	80 w	Choice of two compatible scales. Lowest .5 watt	Female "N"
611	30-500 mc	60 w	Duat Range 0-15/60 w	Female ''N'
612	30-500 mc	80 w	Dual Range 0-20/80 w	Female "N"
67	30-500 mc	500 w	0-25/100/500 watt	Female ''N''
694	2 · 30 mc	1000 w	0/1000 watt	QC Type*
6835	30-500 mc	1200 w	0-120/600/ 1200 watt	QC Type#
67C*	30-500 mc	2500 w	0-100/500/ 2500 watt	Female "N"

*Water Cooled on High Range

Model	74	718	72R	72-2	
Positions	Six	Eight	Reversing Switch	Two	
Coaxial Circuits	One	One	Two	Two	
Connector	models	to receive L	ectors are stand JG-21/U series r cables and c	plug. Use	

Model	Max. Power	Frequency Range	*Max. VSWR	Input Connector
80 Series	5 w	0-4 KMC	1.25	Male or Female, N; C; BNC
80 A	20 w	0-2 KMC	1.2	Female "N"
81 30	50 w	0-4 KMC	1.2	QC Type∗
818	80 w	0-4 KMC	1.2	Female "N"
8135	150 w	0-4 KMC	1.2	QC Type#
82A	500 w	0-3.3 KMC	1.2	Female "N"
8201	500 w	0-2.5 KMC	1.25	QC Type★
8833	1000 w	0-2.5 KMC	1.25	QC Type#
8813	1000 w	0-2.0 KMC	1.25	1 % EIA Flanged
888	1200 w	0-2.0 KMC	1.25	31/ EIA Flanged
8890	2500 w	0-2.5 KMC	1.25	QC Type∗
82C**	2500 w	0-3.3 KMC	1.2	Female "N"
8950***	5000 w	0-2.5 KMC	1.25	QC Type*

Other water-cooled loads up to 50KW can be supplied.

 $^{\bullet}\text{VSWR}$ is 1.1 or less to 1000 mc on all models — with $^{\prime\prime}\text{N}^{\prime\prime}$ connectors.

Water Cooled *Forced Air

★QC TYPE: Bird Quick-Change Connector, designed for rapid change. Available in following types:

Available in following types:
Female or Male N, C, HN, BNC, LC, LT, UHF, and 7/2" ETA flanged.

Complete Specifications on request.





TERMALINE

RF ABSORPTION WATTMETERS

Portable - Non Radiating

Portable . . . direct reading . . . non-radiating "load" type wattmeter . . . used in field or laboratory to measure and absorb power . . . accuracy ±5% of full scale . . VSWR 1.1 to 1 maximum over operating range.

COAXWITCH

COAXIAL SELECTOR SWITCHES

Dependable, manually operated switches for selecting antennas, receivers, transmitters or other apparatus with coaxial connections. Ideal as a system component in electronic equipment where reliable, repeated channel switching is required; pull knob, rotate, and push in to make contact.

TERMALINE

RF LOAD RESISTORS

Quick-Change Connectors

Reflection-free terminations for 50-ohm coaxial lines . . . low VSWR . . . non-radiating . . . water cooled rating 2500 W to 50 KW . . air cooled rating to 2.5 KW . . forced air to 5 KW. Quick-Change Connectors (*QC Type) available on many models.

COAXIAL RF FILTERS

Our extensive engineering and manufacturing facilities are at your command for the custom design and manufacture of filters to your specifications. Intelligent design, skillfull manufacture assure you of highest performance and reliability. New miniature filters, as light as five ozs., are available and can be produced in quantity.

ELECTRONIC CORPORATION


30303 Aurora Rd., Cleveland 39 (Solon), Ohio CHurchill 8-1200 TWX CGN FS 679

Western Representative: VAN GROOS COMPANY, Woodland Hills, Calif.



COAXIAL RELAYS

4 different models, A.C. or D.C.

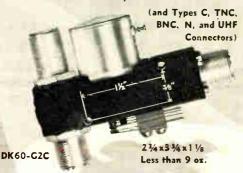

DK60 SERIES RELAYS PRICED FROM . . . \$12.45

See any one of our 700 Dealers and Distributors In U. S. and Canada for catalog sheets or write:

STANDARD RELAYS INCLUDE:

DK60 - SPDT r.f. switch.

DK60-G — SPDT r.f. switch with special "isolation" con-nector in de-energized position.

DK60-2C - SPDT r.f. switch with DPDT auxiliary contacts. DK60-G2C — SPDT r.f. switch with DPDT auxiliary contacts and special "isolation" connector in de-energized position.

- * Relays available in weatherproof boxes for exterior installation.
- Ganged, multiple position switch arrangement available for remote control selection of antennas.
- Unconditional guarantee for period of one year. (We will repair if faulty within one year.)

r.f. SPECIFICATIONS:

r.f. SPECIFICATIONS:
Low YSWR: less than 1.15:1 from 0 to 500 mc. Low
Losses: Pure silver contacts. Parts in crucial positions
plated with fine silver. Low Cross-Talk (greater than 80
db) (in energized position) in DK60-G and DK60-G2C
through use of patented "isolation connector". High Power
Rating: (a) 1 kw through straight connectors (b) to 10w
through "isolation connector"—excellent for video switchlog. SPDT r.f. Contacts: r.f. leakage extremely low, below typical r.f. connectors.

MECHANICAL SPECIFICATIONS:

High Contact Pressures: Long life expectancy greater than 1 million operations. Continuous Duty: Teflon feed-through terminals used on coil to provide connection ease.

ELECTRICAL SPECIFICATIONS:

Wide Variety of Coil Voltages: 6.12.24.32.48.110.220 D.C. volts at 2.0 watts: 6.12.24.110.220 A.C. volts at 6 voltamps, 50.60 cps. (Special voltage or resistance available on request.) Less Than 50°C Temperature Rise Above Amblent: Maximum operating temperature is 100°C except on special order. Auxiliary contacts available for power control—DPDT at 5a. 110 v A.C. on DK60-2C and DK60-G2C.


Manufactured by DOW-KEY COMPANY. Thief River Falls, Minnesota



TRANSISTORIZED TELEPHONE INTERCOM SYSTEM

Model SA-10W

\$23.95 2-unit set

 

Ideal for few feet or up to 9 miles. Each phone has separate red button, which when depressed sends pleasing signal tone; black button for talking. Receiver is transistorized crystal unit; transmitter is carbon unit, Eoch unit has spiral phone cord. Operation requires no switching. Use several units together. Imported.

ALCO R.F. FIELD

STRENGTH METER Single Band I to 250 MC.

\$6.95

Model PSI-1 21/6 x 31/6 x 11/6" Compact! Sensitive! Checks antenna efficiency, Load matching, etc. Requires no battery or other power source. RF measured on accurate meter. Telescoping antenna to 103½", Earphone jack provided for monitoring; case has powerful magnet to grip fender, etc. Imported.

SEND FOR FREE CATALOG Available direct or through

your local distributor

PET-1 FIELD STRENGTH DIDICATES



High sensitivity — 20,000Ω/V New design; wide scale arc Compares with 41/2" meters Measures 31/4" W x 41/2" meters Compact black bakelite case

WITH FREE LEATHER CASE

DC V. ranges: 5-25-250-500-2500 © 20,000? per V.

AC V. ranges: 10-50-100-5001000 @ 10,000Ω per V.

DC current: 50 μα, 2.5 ma. Imported

20,000

ohms per volt

MULTITESTER

GRID DIP METER

WIRED - READY TO USE

Completely calibrated Freq. coverage 1.5 to 300 MC in 6 ranges

\$36.99

Ronges color-coded to motch coils, undomped 1 MA meter. Variable sensitivity control for op-timum grid current adjustment. Calibrated dial, adjustable hairline, allows precise accuracy. Phone jack permits use as modulation monitor. Oscillator tube is 6AFA. 6½ x 3½ x 1½". 6 cails supplied. 117V, 50-60 cps. 2 lbs. Imported.

Model TS-60

\$15.95

ELECTRONIC PRODUCTS, INC.

Dept. 666 — 3 Wolcott Ave., Lawrence, Mass.

PENTA

HIGH-EFFICIENCY

POWER TUBES

Penta power tubes are used by the leading manufacturers of amateur, commercial, and military communications equipment. Follow the example of those who know the wisdom of using only the best. Specify Penta tubes whenever you want long life, reliability, and maximum efficiency.

	Fil. Volts	Fil. Current Amps.	Plate Diss. Max. W.	Plate Voltage Max.	Plate Current Ma. Max.	Screen Voltage Max.	Price
PL-172 BEAM PENTODE	6.0	8.2	1000	3000	1000	600	\$135.00
PL-175A BEAM PENTODE	5.0	14.5	400	4000	350	800	\$ 50.00
PL-177A BEAM PENTODE	6.0	3.2	75	2000	175	600	\$ 29.00
PL-6549 BEAM PENTODE	6.0	3.2	75	2000	175	600	\$ 29.00
PL-4E27A BEAM PENTODE	5.0	7.5	125	4000	200	750	\$ 45.00
PL-4D21 POWER TETRODE	5.0	6.5	125	3000	225	600	\$ 36.00
PL-4D21A POWER TETRODE	5.0	6.5	175	3000	225	600	\$ 37.50
PL-5D22 POWER TETRODE	5.0	14.5	250	4000	350	800	\$ 46.50
PL-4-65A POWER TETRODE	6.0	3.5	65	2000	150	600	\$ 27.00
PL-4-400A POWER TETRODE	5.0	14.5	400	4000	350	800	\$ 48.00
PL-4-1000A POWER TETRODE	7.5	21.0	1000	6000	700	1000	\$132.00
PL-250R RECTIFIER	5.0	10.5		60,000	250	-	\$ 36.00
	Fil. Volts	Fil. Current Amps.	Plate Diss. Max. W.	Plate Voltage Max.	Plate Current Ma. Max.	μ	Price
PL-254W POWER TRIODE	5.0	7.5	100	4000	225	25	\$25.00
PL-6569 POWER TRIODE	5.0	14.5	250	4000	300	45	\$37.50
PL-6580 POWER TRIODE	5.0	14.5	400	4000	350	45	\$45.00



PL-172 Beam Pentode



PL-175A Beam Pentode



PL-177A Beam Pentode



PL-4E27A



PL-4D21A Power Tetrode



PL-5D22 Power Tetrode



PL-4-65A



PL-4-400A Power Tetrode



PL-4-1000A Power Tetrode



PL-6569 Power Triode



PL-6580 Power Triode



PL-184A Socket and Chimney

PENTA LABORATORIES. I

Santa Barbara, California




FIELD ENGINEERING REPRESENTATIVES AND DISTRIBUTORS SERVING MAJOR CITIES.

For further information write for complete Penta catalog.



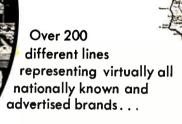for the newest and finest equipment for the radio



Liberal trade-in allowances...

An excellent time-payment plan...

Courteous, friendly service by our staff which includes over fifteen licensed radio amateurs...

A complete, well staffed department to give you excellent service on your mail orders.





great response

Naturally. This smart ham is using a University Model 70. It's dynamic! Now his QSO's are more frequent with better quality. You'd be surprised at the compliments he gets. He's also improved his SSB transmissions... found the perfect budget-minded way to increase peak power and intelligibility. And he doesn't have to swallow this microphone to be heard. All he does is sit back, relax and speak normally. The Model 70 does the rest. Why not let it do the same for you. Comes complete with integral 15-foot 3-conductor shielded cable, Model SA10 slide-on stand adapter and cloth carrying bag. Check the 'specs'. No other dynamic of its type can match the great Model 70! Only \$29.95*

SPECIFICATIONS

Frequency Response: 50-14,000 cps (which extends to a usable limit in the 18,000 cycle region). Impedance: 30/50; 20,000 ohms. Output Level: 30/50 ohms: —50 db/1 mw/10 dynes/cm²; —143 db E1A sensitivity rating; 20,000 ohms into high impedance input; 28 mv/10 dynes/cm². Hum Reference: —120 db/.001 gauss. Dimensions: 1-5/32" maximum diameter, 6" maximum length. Shipping Weight: 21/4 lbs. Finish: Acrylic silver-gray and non-reflecting black.

*Model 71 also available with on-off slide switch \$34.95.

Write for new 12-page catalog with complete details on the entire University Modular Microphone line. Desk 00-11 University Loudspeakers, Inc., 80 South Kensico Ave., White Plains, New York.



Laboratory Standards



A SOUVENIR OF WORLD WAR I

TELEFUNKEN WAVEMETER TYPE K.W. 61g

Frequency Range: 40 kc-2000 kc

Accuracy: 5%

This instrument was calibrated just 23 days before the end of World War I

THE BEST THERE IS TODAY —

MEASUREMENTS' NEW MODEL 760 STANDARD FREQUENCY METER

Frequency Ranges: 25-50 mc

150-175 mc

450-475 mc

Accuracy: at 25 mc

.0004%

at 475 mc .00002% with crystal adjusted

to WWV

Crystal: oven temp. controlled



Price **\$980.00** F.O.B. Boonton

SINCE 1939 — MANUFACTURERS OF FINE PRECISION ELECTRONIC TEST EQUIPMENT

Measurements "FAMOUS FIRSTS" Include:

- First commercial signal generator with built in tuning motor
- First commercially produced electronic peak voltmeter
- · First commercially built pulse generator
- World famous Megacycle Meter, covering 100 kc to 940 mc
- First commercially successful FM testing equipment designed especially for Mobile Communications
- And now a completely new concept of frequency measurements

Write for complete catalog

MEASUREMENTS

A McGraw-Edison Division

BOONTON, NEW JERSEY

National Master Mobile

RME Electro Voice



BIG NAMES
IN AMATEUR EQUIPMENT
IN STOCK AT

*HAMATEUR EADQUARTERS



Everything in electronics...you name it—we have it!
Every known and trusted brand...every type of radio
equipment and parts always in stock to assure you of
prompt service and delivery. We ship around the Globe
...guaranteed complete satisfaction on all orders.

Call or write about your needs. Near new and used equipment. List sent on request.

TRADE IN your old equipment for Liberal Allowance.

CONVENIENT CHARGE PLAN — 10% DOWN



LARGE, FULL SIZE
WORLD WALL MAP
SHOWING RADIO PREFIXES AND

Send 50¢ in coin for your wall map. Enjoy the thrills and fun of contacting more than 2,000,000 licensed stations all over the world. 50¢ will be refunded with your next order.

*Copyright, 1960

RCA)
ELECTION

Antenna products

antenna products





FOR SPEEDY SERVICE call or write

Joe Hotch, KØUFE, Manager
Hamateur Dept.

•	Includes: listening	to S.W.	broadcast.	ship	to	shore.	etc.;	also	more	than	300,000
	amateurs-potenti:	al QSOs fo	r you.								

-USE THIS COUPON TODAY FOR FREE MAP -----Gentlemen: I am enclosing 50c in coin — Please send me map. I understand 50c will be refunded with my first order.

NAME.

ADDRESS.

CITY
I am interested in the following equipment

☐ Send me literature and price list

HB-62

THE Lew & Bonn

LEADERS IN ELECTRONICS FOR MORE THAN 35 YEARS COMPANY

STATE

1211 LaSalle Avenue • Minneapolis 3, Minn. FEDERAL 9-6351



TWO-WAY RADIO

communications equipment

VHF-FM FOR:

MOBILE AIRCRAFT MARINE MOTORCYCLE PORTABLE BASE VHF-AM FOR:

AIRPORT VEHICLES GROUND STATIONS POINTETO=POINT VHF

ANTENNAS REMOTE CONTROLS ĀČČĒSSORIES



NEW! "680 BASECOM"

FOR VHF-FM TWO WAY
MOBILE RADIO

the new 680 series offers

HIGH PERFORMANCE at MODERATE COST with LOW MAINTENANCE!



"680" FEATURES AND OPTIONS:

- ★ PROVEN PERFORMANCE...all the outstanding features of the popular "580" series, plus the following.
- ★ HIGH POWER...100 watts output 25 to 50 mc, 75 watts 144 to 174 mc, both base and mobile.
- ★ TONE SQUELCH... two way tone squelch compatible with other systems to EIA standards.
- ★ Meets all FCC and OCDM requirements.
- ★ SIMULTANEOUS RECEPTION...dual front end receiver for monitoring two frequencies anywhere in the band.
- ★ TRANSMITTER FILAMENT SWITCH . . . reduces battery drain when on "stand-by".
 ★ MONITORS REMOTE CONTROL . . . base
- ★ MONITORS REMOTE CONTROL ... base statian monitors remote transmissions. Intercom provided. All functions available at remote position.

"680 FLEETCOM"

COMBINATION

- MOBILE CONTROL HEAD
- SPEAKER
- TRANSISTOR POWER SUPPLY

ATTENTION DEALERS!
Write for available territories.



RADIO COMMUNICATIONS EQUIPMENT

COMMUNICATIONS COMPANY, Inc.

FOUNDED 1938

CORAL GABLES, MIAMI 34, FLORIDA

BARRY ELECTRONICS

HIGH VOLTAGE PLATE TRANSFORMER:

Input: 115 VAC @ 60 CPS.

Secondary: 3000-2500-0-2500-3000 VAC @ 350 Ma. Insulated for 10 KV. New, factory lopen-frame) construction.

Size: 5"H x 7"W x 6·1/2"D. Wt: 25 lbs.

RCA PRECISION 500 KC CRYSTAL OSCILLATOR:

Accuracy plus or minus 0.0012%. Contains Precision 500 KC crystal, BMS labs Crystal oven, 5840 subminiature tube. Hermetically sealed nickel plated rectangular case. Mounts in standard 7 pin miniature socket. Requires 6.3 VAC or DC, 75 to 100 V.D.C. With schematic, RCA Type A8838300-1. Size: 4-1/2"H x 1-7/16"W x 1-1/8"D. Wtt 1 lb. Cat. #4-500 CRV. (Orig. Govt. Cost: \$172.00)

VERY SPECIAL . . . ONLY \$3.75

HI-VOLTAGE DYNAMOTOR:

Input: 12.6 VDC.

Output: 700 VDC @ 260 Ma.

Brand new. Compact. Mfd. by Sangamo. Looks just like famous Carter compact Dynamotor. With mounting brackets. \$13.95

2.5 KW MODULATION REACTOR TRANSFORMER:

Primary Impedance: 12,000 Ohms. Secondary Impedance: 7500 or 5000 Ohms. Made for use with single power supply for Class B Audio and Class C R.F. For use with separate power supplies; use one 5 to 10 Henry Choke and one 1 Mfd. capacitor. New original boxed. Net wt: 102 lbs. \$42.50

BRAND NEW MODEL 61720 FALLOUT DETECTION METER:

lightweight, hand operated, detects and measures dangerous levels of radioactive fallout. Citizens version of the official fallout detection meter used by Office of Civil Defense. Unit is transistorized and runs on only 2 flashlight batteries. Measures gamma radiation dose rates as high as 500 roentgens per hour. Designed to be used in determining radioactive contamination levels that may result from an \$49.95 enemy attack.

30 WATT MOBILE TRANSMITTER:

Uses 5618 crystal oscillator into CBS 5516 amplifier. Modern design. Only 7 lbs. net weight including built-in 6 V. vibrator power supply. Completely enclosed in aluminum cabinet (5-1/2"H x 7"W x 8"D). Furnished with crystal that doubles near 10 meter band. Will require slight and easy modification for 10 meter operation. A real beauty.

With tubes -\$11.95

VHF TRANSMITTER:

Perfect for 2 meter and/or 1-1/4 meter conversion. late, modern design. Uses two 6201's Into single Amperex 6360 twin Tetrode. Xmtr only 4" x 4" x 11". Only 3-3/4 lbs. Complete with 10-1/2" chrome antenna. Furnished complete with A and B Battery pack, & connection cable and schematic & conversion Info. with case: Buttery weight, 23 lbs.

PRICE: \$15.00 with all tubes.

(We can ship without battery - same price \$15.00).

JENNINGS UCS VACUUM VARIABLE CAPACITOR

Capacity: 10 to 300 Mmf. at 10 KV. Complete, less shaft. Originally sealed Jennings. Government carton. Shpg. Weight: 5 lbs.

Reg. Net Approx.

SALE PRICE:

\$141.00 \$49.00

COAXIAL CABLE

COAXIAL CABLE - FACTORY FRESH STOCK!

Туре	Nominal Impedance	Price Per 100'	Price Per 1000'
RG-8,'U	52 Ohms	\$8.50	\$80.00
RG-8A/U	52 Ohms	12.00	115.00
RG-11/U	72 Ohms	8.00	75.00
RG-11A/U	72 Ohms	9.00	85.00
RG-58/U	52 Ohms	4.50	40.00
RG-58A/U	52 Ohms	5.00	44.00
RG-59/U	72 Ohms	4.50	40.00
RG-59A/U	72 Ohms	5.00	44.00

AUTHORIZED DISTRIBUTOR FOR: NATIONAL, HAMMARLUND, JOHNSON, C-D, WESTINGHOUSE, MOSLEY, B & W, CENTRAL ELECTRONICS, TMC, AND OTHERS.

TUBE HEADQUARTERS OF THE WORLD!!! Complete inventory of Transmitting Special-Purpose, Radio, TV, Foreign, C.R. — 1st Quality Tubes, Name Brands Only. Guaranteed. Sensible Prices. (We carry complete line of Westinghouse tubes).

WRITE FOR THE "GREENSHEET" CATALOG (excellent values on Ham Gear, components, equipment, electron tubes, etc.) A must for every Ham and buyer of electronic parts.

BARRY ELECTRONICS CORP. DEPT. QA	
512 Broadway, New York 12, N. Y.	
Enclosed is money order or check and my order.	
Send copy of the Exciting "Greensheet" Catalog.	
Name	Title
Company	<mark></mark>
Address	
City	

INDUSTRY-PROVED SEMICONDUCTORS FOR YOUR HAM APPLICATIONS



PLUG-IN SILICON RECTIFIER CELLS
Ratings: to 500 ma - 200 to 600 PRV. Diffused junction...high power capability (to 750 ma)...
lets containing standard clipholders and hardware also available ... 5M series.
Battlets 52.218



SD 500 KIT, TV REPLACEMENT

Rating: 500 ma at 130 vac. All-purpose silicon replacement kit offers radio-TV men simple means of replacing all existing silicon rectifier types. Hermetically sealed diode can be wired in or plugged into fuse-clip. To 100 C; needs no heat sink.

Bulletin IR 505



UNISTAC SILICON TY RECTIFIER
Rating: 750 ma at 130 vac. A direct and universal
replacement for all existing selenium stacks up to
500 ma. Eyelet construction. No "special socket,"
conversion kit or drilling required. Especially
suited to the elevated operating temperatures
inherent in most TV sets.





MINIATURE SILICON RECTIFIER CELLS
Ratings: to 750 ma – 200 to 600 PRV. High power
capability (to 750 ma)...peak surge current
capacity (to 50 amps)...ideal for TV diode
replacements...5A series.
Bulletts SR-212



SILICON RECTIFIER TUBE EQUIVALENTS
Ratings: 85 to 1250 ma • 1500 to 10,500 PIV. Highly reliable series of tube replacement rectifiers rated from 1500 to 10,500 PIV, 85 to 1250 ma offer the superior characteristics of silicon on a wide range of high voltage applications.

Bulletin SR-209



SELEMIUM RECTIFIER STACKS
Ratings: From 100 ma to 50 amps. Low forward voltage drop and low leakage characteristics make this series ideal for a wide variety of power applications.

Bulletin SR-170



SUBMINIATURE SELENIUM DIODES
Ratings: to 28 ma - 48 to 384 PRV. High efficiency/
low cost diodes provide stable operation over
-50°C to +100°C range...reverse resistance
to 30 megohms at 30 volts... withstand 1 second
surges to 550 ma... IN1625 series.
Builetis \$1.63A



SILICON ZENER VOLTAGE REGULATORS
Ratings: From 250 milliwatts to 10 watts. A complete series including sub-miniature glass types, miniature single junction types, multiple junction types and double anode units.

250 and 400 mw glass types.* 750 milliwatt and 1 watt types, 3.5 and 10 watt types.*

Bulletins SR-265° and SR-260°°

SOLAR CELLS AND PHOTOCELLS

Wide range of silican and selenium types. Silicon solar cells with conversion efficiencies to 13%...silicon readout photocells with response times to 5 µsec...selenium photocells in wide variety of sizes and shapes.

Bulletins SR-280 (Silicen) and PC-849 (Selenlem)

For complete technical data on these or other IR products, see your local IR distributor. He can supply you with most of these items right off the shelf.

INTERNATIONAL TOR RECTIFIER SYMBOL OF QUALITY IN SEMICORDUCTORS

INTERNATIONAL RECTIFIER CORPORATION: EL SEGUNDO, CALIFORNIA • PHONE OREGON 8-6281 • CABLE RECTUSA

WORLD'S LARGEST SUPPLIER OF INDUSTRIAL SEMICONDUCTORS AND RECTIFIERS



Add an Ameco Nuvistor Preamplifier to your converter or receiver to improve the noise figure and gain. Image and spurious rejection will also be improved as the Model PV has two tuned circuits. Compact, easily connected, low power requirements.

Model PV with tube, wired and tested.

State which band ...

For any band, 80, 40, 20, 15 or 10 meters, the Ameco Modet PH Preamplifier has a better noise figure than most multiband receivers, 23 db. minimum gain, will improve image and spurious rejection with its two tuned circuits. Especially effective on 10 or 15 meters. Model PH with tube, wired and tested.

State which band Write Dept HB 62

AMERICAN ELECTRONICS CO HERRICKS ROAD, MINEOLA, L.I., N.Y.



The new deluxe "Cadillac" line of Ameco VHF Converters uses three RCA Nuvistors—two as RF amplifiers, the third as the mixer. This combination produces an extremely low noise figure, high gain, high image, spurious and IF rejection. These converters do not become obsolete as the output frequency is easily changed when a new receiver is acquired. The CN Converters are built on a compact (2"x2½"x6¾") satin finished copper chassis. A gain control is included. Power requirements: 100 to 300V. at 30 ma. and 6.3V. at 1A. The Ameco PS-1 Power Supply is ideal, available in Kit form (PS-1K) at \$10.50 or Wired and Tested (PS-1W) at \$11.50.

Model CN-50W, CN-144W, CN-220W Nuvistor Converter, wired and tested for any one band (specify IF output). \$44.95

Model CN-50K, CN-144K, CN-220K Nuvistor Converter, in kit form, for any one band (specify IF output)\$31.95 Write Dept. HB-62

AMERICAN ELECTRONICS 178 HERRICKS ROAD, MINEOLA,

OKLA. マロ pay <u>=</u> P&Y Superb construction and unequalled perform-**MODEL TB 1000-4** ance has gained world wide acceptance for ٥ Hornet antennas. ASK THE AMATEUR WHO Satisfied, I Agree to aid Within 10 Days \$99.75 satisfied. OWNS ONE! MODEL TB 1000 Cash Price \$79.75 Budget Terms only \$9.30 per month := := Fully Rated I KW days. Four working elements on all three bands. dget Terms TRIAL. 1f P only \$7.45 per month 2 ö Rated 1 KW AND IT'S SO EASY TO BUY I will pay cash were month for II HEAVY DUTY Agree to Retu. B. FACTORY. MODEL TB 750 · Use the order form below Check the model of your ပ္ပ choice Mail coupon 1000-4. | 1 and \$9.30 per 1000. | | w d \$7.45 per m Tribander for a Satisfied, 1 Ag PRICES F.O.B. 1 Your antenna will be rushed to you for 'try-before you buy evaluation. Thousands of amateurs who have used this plan have found that there is no better way to investigate value in relation to \$59.75 Budget Terms only \$5.50 per month Rated 750 watts cost, before buying. No. If you desire, use time payment plan-low monthly payments. MODEL TB 500 ALL MODELS . . . Rush My d Below. IZ Are Pre-tuned and Easy to Install Have Custom Fittings of Cast Aluminum Cash Price j. Use o Single 52 ohm Coaxiol Trans-\$49.95 Budget Terms : mission Line Have completely weather-sealed Freonly \$4.70 per month Heavy Duty quency-Dividers Have 6061-T6 Aluminum in the Ele-

Prices subject to MAIL YOUR ORDER TODAY - NO MONEY REQUIRED WITH ORDER

*Pat. Pend.

\$4.70

pay



BIRTCHER

Tube / Transistor / Component / Cooling and/or Retention Devices

NOW AVAILABLE FROM AUTHORIZED DISTRIBUTORS FROM COAST TO COAST

KOOL KLAMPS

TOP HOLDING RETAINERS

TUBE CLAMPS

TRANSISTOR CLIPS

TRANSISTOR RADIATORS

DIODE RADIATORS

JAN SHIELD INSERTS

TYPE 2 TUBE CLAMPS

PRINTED CIRCUIT **BOARD RETAINERS**

CALIFORNIA, Gardena **Bell Electronics** FAculty 1-5802

CALIFORNIA, Los Angeles Bell Radio Supply PLeasant 3-4495

CALIFORNIA, Palo Alto Zack Electronics DAvenport 6-5432

CALIFORNIA, San Diego **Bell Electronics** BRowning 8-4350

CALIFORNIA, San Francisco Zack Electronics MArket 1-1422

CONNECTICUT, Hamden 14 Cramer Electronics ATwater 8-3581

D.C., Washington Capitol Radio Wholesalers Inc. HObart 2-0800

FLORIDA, Miami Airwork Corporation TUxedo 7-8253

ILLINOIS, Chicago 50 Merquip Electronics, Inc. AUstin 7-6274

MARYLAND, Baltimore 1 Wholesale Radio Parts Co. Inc. MUIberry 5-2134

MASSACHUSETTS, Newton 64 Cramer Electronics, Inc. WO 9-7700

MICHIGAN, Detroit 35 S. Sterling Company BRoadway 3-2900

MINNESOTA, Minneapolis George Spencer, Inc. LI 5-8811

MISSOURI, St. Louis 32 Interstate Industrial Electronics WYdown 4-7585

NEW JERSEY, Summit R. P. Luce and Company CRestview 3-9250

NEW YORK, Buffalo 2 Summit Distributors TT 4-3100

OHIO, Dayton 4 Srepco, Inc. **BAldwin 4-3871**

OKLAHOMA, Tulsa 19 Radio, Inc. LU 7-9124

TEXAS, Dallas 1 **Adleta Company** Riverside 1-3152

TEXAS. Houston 19 **Busacker Electronics** JA 6-4661

WASHINGTON, Seattle Seattle Radio Supply, Inc. MAin 4-2341

THE BIRTCHER CORPORATION

Monterey Park, California

Call letters of Charles Booher, sales manager of The Birtcher

WEDTO

745 S. Monterey Pass Rd. •

ANgelus 8-8584

You get more for your money from **NEWARK**Check these **HAMMARLUND** values—

(with these Newark extras)

- Top trade-in allowance on your present equipment
- Immediate delivery from Newark's complete stocks
- Complete experienced technical assistance



FOR TOP PERFORMANCE AT MODERATE COST


New HX-50 Transmitter. Brand new, with ultra-modern circuitry, using Compactron and Nuvistor tubes, and all the latest features. A truly versatile unit with up to 75 watts output on SSB-CW, 15 watts AM, covering all bands, 80 thru 10 meters, plus MARS frequencies. Accurate calibration, readable to 500 cycles. With built-in antenna changeover relay. Measures a compact 9½" H x 9½" D x 17½" W.

Newark Catalog No. 97F430 net.......\$39950

HQ-110C Receiver. Dual conversion, 12-tube superheterodyne unit covers all 7 amateur bands, 6 thru 160 meters. Has many features of higher priced receivers ... separate linear detector for SSB and CW, Q-multiplier for continuously variable high selectivity, built-in 100KC crystal calibrator. With 24-hour clock timer, die-cast aluminum front panel.

Newark Catalog No. 97F427 net...... \$25900

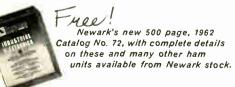HQ-110 (Without clock) No. 97F429 net \$24900



AN AMATEUR STATION OF UNEXCELLED PERFORMANCE

HX-500 Transmitter. Top performance. Filter type sideband transmitter delivers power output of 100 watts PEP on SSB, CW, NBFM, RTTY, on the entire 80 thru-10 meter bands. 25 watts AM output. Stability below 100 cycles. Built-in keying and antenna relays. Automatic level control prevents overloading and increases talk power. Can be rack-mounted. Many other important features.

Newark Catalog No. 97F431 net...... \$69500

HQ-170C Triple Conversion Receiver. This 17-tube receiver provides best possible reception of SSB, CW, and AM signals on the 160 thru 6 meter bands. Bandwidth selectivity is variable from 0.5KC to 3KC; SSB and CW sensitivity 0.5 microvolts for 10:1 signal:noise ratio. Adjustable 445KC slot filter eliminates heterodyne interference. 24-hour clock timer.

Newark Catalog No. 97F433. net \$36900

HQ-170 (Without clock) No. 97F434 net. \$35900



Write Dept. HB-62, Attention Ham Shack for trade-ins. 223 W. Madison St. • Chicago 6, III. • STate 2-2944

In Inglewood, California call: OR 8-0441 • In Grand Rapids, Michigan call: CH 1-5695
In Detroit call: UN 1-6700 • In New York City call: AL 5-4600 • In Denver call: SK 7-3371



proven performers for amateur, laboratory and production use

PANORAMIC

Single Side Band & Communications Systems Analyzers



SSB-3a SINGLE SIDE BAND spectrum analyzer

2 mc-40 mc. 100 cps - 40 mc with Optional REC-1. Set up, adjust, manitar and trauble shoot SSB and AM transmitters and receivers . . . with one convenient, compact and comprehensive package. Uniform sensitivity over entire range.

Quick, accurate measurement and display of

- 2-Tone distortion tests
 - Vestigial carrier amplitude
- Residual hum sidebands
- Dynamic transmission bandwidth
 Out-of-band radiations





MODEL PR-1

PANADAPTOR for amateur use

PR-1, for ham operation, features simultaneous visual observation of many signals on 3-in. CR tube over a band of frequencies up to 200 kc. For spotting replies to your CQ's ... selecting QRM-free spots ... second aural receiver for 3-way QSO's...and a host of other uses.

PANADAPTORS provide continuo us monitoring to find and analyze interference (splatter, harmonics), RF parasitics, irregular transmissions. They are tuning aids for SSB and telemetry signals. Two models (SA-8b and SA-3, in many types. Please specify receiver IF when inquiring or ordering.



MODEL SB-12a

PANALYZORS

Low cost RF spectrum analysis to 1000 mc (higher with external mixers).

- Analyze AM, FM, SSB transmitters
- Investigate pulsed RF signals
- Spot spurious oscillations and modulation

3 models, SB-3, SB-8b, and SB-12a, in many types for narrow and broad band monitoring and analysis

Measurement theary and applications are discussed in THE PANORAMIC ANALYZER. Get an aur mailing list far this free, helpful publication.

Write taday, for detailed specifications and applications of these versatile, economical Panoramic instruments . . . and NEW CATALOG DIGEST Attractive professional career opportunities ovailable.

PANORAMIC ELECTRONICS, INC.

576 So. Fulton Ave., Mt. Vernon, New York • OWens 9-4600 TWX: MT-V-NY-5229 • Cables: Panoramic, Mt. Vernon N. Y. State



Formerly Panoramic Radio Products, Inc.

LearnCode

yourself for your big opportunity

THE Candler WAY IS THE

Champion WAY!



SCIENTIFIC CODE COURSE

Especially designed for the beginner. Teaches the basic principles of code operation scientifically.

Here's your chance to learn quickly and easily...to get maximum speed and proficiency in code...right in your own home. You can save time and money learning the fundamentals of code sending and receiving and the principles of fast, efficient operating with the world-famous CANDLER SYSTEM.

Picture yourself at your own transmitter ... sending out radio code, messages that will be received around the globe. Yes, operators are waiting to communicate with you today, tonight or any time. The knowledge of the world ... intimate friendships you will gain ... may help you in your business, may be a stepping stone to success.

Wouldn't you like to be the invaluable link with the outside world in time of disaster? Or to serve in a national or local emergency? Be ready for service when the opportunity arises! Learn radio and telegraphy now — the Candler way.

For 50 years the CANDLER SYSTEM has trained beginners for all telegraphing requirements, all operator licenses, highest ratings, and FCC specifications, both amateur and commercial. The record of famous amateurs and expert operators who learned the Candler way is proof of what the Candler System offers you. Send for details today!

CANDLER SYSTEM

Dept. 58, 2077 Locust St. Denver 7, Colorado

YOU COULD WORK WONDERS WITH A GOTHAM VERTICAL ANTENNA!

FREE

Send a card for our valuable catalog of 50 different antennas with specifications and characteristics. Gives bands and frequencies covered, element information, size of tubing used, boom length, shipping weight, feed line used, polarization, and other data.

Airmail Order Today — We Ship Tomorrow
GOTHAM Dept. RAH
1805 PURDY AVE., MIAMI BEACH, FLA.
Enclosed find check or money-order for:
V40 VERTICAL ANTENNA FOR 40, 20, 15, 10 AND 6 METER BANDS. ESPECIALLY SUITED FOR THE NOVICE WHO OPERATES 40 AND 15 \$14.95 V80 VERTICAL ANTENNA FOR 80, 40, 20,
15, 10 AND 6 METER BANDS. MOST POPULAR OF THE VERTICALS. USED BY THOUSANDS OF NOVICES, TECHNICIANS, AND GENERAL LICENSE HAMS \$16.95 V160 VERTICAL ANTENNA FOR 160, 80, 40, 20, 15, 10 AND 6 METER BANDS. SAME
AS THE OTHER VERTICAL ANTENNAS, EX- CEPT THAT A LARGER LOADING COIL PERMITS OPERATION ON THE 160 METER BAND ALSO
HOW TO ORDER. Send check or money order directly to Gotham. Immediate shipment by Railway Express, charges collect. Foreign orders accepted.
Name
Address
City Zone State



TV STATION PACKAGE

Ling-Mitter TV Transmitter
Ling Spectator TV Camera
Ling-TV Videa Manitar
1" f 1.9 Lens
Yagaflector Transmitting Antenna
Transmission Line
UHF Converter
Dual Bow Tie Receiving Antenna

OPERATE YOUR OWN TV STATION

LOW COST


AMATEUR'S
TELEVISION STATION
COMPLETELY
PACKAGED
FOR OPERATION IN
THE FCC ASSIGNED
420-450 MC BAND

- Unconditionally Guaranteed
- Amateur Net Package Price \$199500
- Suitable Financing May Be Arranged

ELECTRON CORPORATION

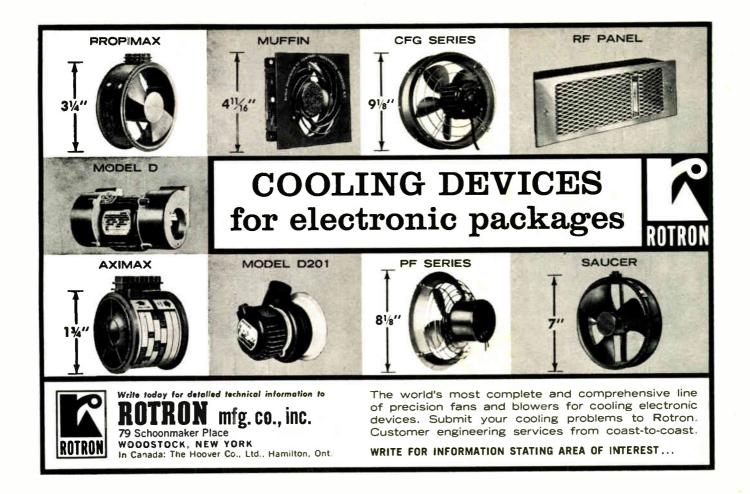Designers And Manufacturers Of Quality Television Systems
P.O. Box 5570 • Dallas, Texas
A SUBSIDIARY OF LING-TEMCO-VOUGHT, INC.





COMPLETE OUTFITTERS

FOR THE

- **H**AM
- **▶** Communications
- ► ELECTRONIC ENGINEERS

EUGENE G. WILE

218-220 South 11th St.

Philadelphia 7, Pa.

WAlnut 3-1343

Distributors of


Nationally Advertised Lines of RADIO, TELEVISION and ELECTRONIC Parts

MODERN EQUIPMENT

FOR LEARNING MORSE CODE

PERFORATORS, TRANSMITTERS, ETC.



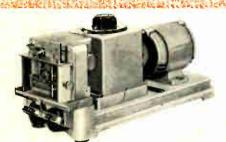

GNT TRANSMITTER MODEL 115

Ideal for learning Morse code, permitting insertion of extended pauses between letters and words.



GNT MORSEINKER MODEL 1532

Operates from tone frequency signals or by Morse Key. Especially designed for training purposes.

"HOW TO LEARN MORSE"



Booklet describing

Morse training

Write for free copy



GNT KEYBOARD PERFORATOR MODEL 50

An instrument for preparing a perforated Morse code slip for use in a transmitter. Maximum speed of operation 750 characters per minute. Provided with a special locking device preventing the simultaneous depression of two keys.

ALSO COMPLETE RANGE OF AUTOMATIC INSTRUMENTS FOR HIGH SPEED MORSE TELEGRAPHY.



TELCOLAB CORPORATION

CHRYSLER BUILDING
NEW YORK 17, N. Y.

U.S., Representatives of:

GNI


GREAT NORTHERN TELEGRAPH WORKS, COPENHAGEN, DENMARK,

Distributors of Canada: TMC Canada Limited, R.R. No. 5, Ottawa, Ontario.


THE HAMS' NO. 1 CHOICE

in clear plastic or metal cases...

Shurite. **METERS**

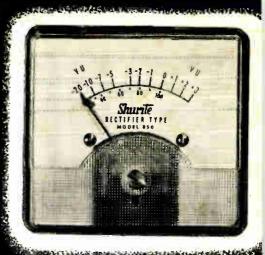

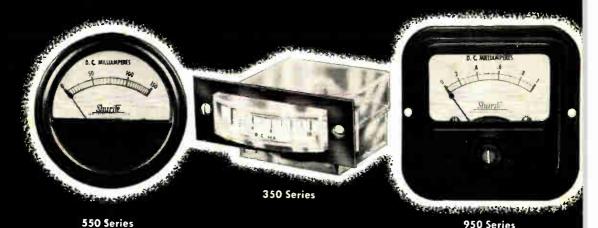850 Sories Shown actual size, zero adjuster optional



Shown approximately three quarter size

CLEAR-PLASTIC CASES: One look will make every ham enthusiastic about the modern, expensive-looking 850 series . . . and you will be pleased to find the meters cost only 20¢ more than the equivalent metal cased meter. Equally good news will be the longer, more visible scale arc...the removable front ... and the availability of zero adjusters on all AC or DC ranges.

ATTRACTIVE METAL CASES: In certain applications—for panel appearance or specialized service conditions, you may prefer to select from the long-time metal favorites, the basic Models 550 or 950 as illustrated. Although all have been modernized in appearance recently, each continues to fit 2 5/32" mounting hole. See Catalog 94 covering all types, including many with zero adjuster.

CHOICE OF MANY TYPES: AC and DC Ammeters, Milliameters, Voltmeters and Resistance Meters. AC meters are double-vane repulsion type with jeweled bearing. DC are polarized-vane solenoid type, or moving magnet construction. Well over 200 ranges and types. Among the most popular are a 0-3 DC Milliammeter with 500 ohms internal resistance and built-in zero adjuster, and a 0-1 DC Milliammeter with 1,000 ohms internal resistance and zero adjuster,

NEW EDGEWISE METER: The 350 series provides an ideal we to dress up a panel. The clear jewel-like plastic frant is ver rich loaking and gathers light for easy reading of its long scal Yet it takes very little panel space and costs much less the you would expect.

DEPENDABLE PERFORMANCE: By far the best torque-ta-weigl ratio in its field gives you a sturdy meter with fast response and ability to duplicate readings. Accuracy well within th standard 5%.


REASONABLE PRICES: Typical of the exceptional values ar the meters illustrated. 0-150 DC Ma, \$2.15 in the 550 or 95 Series, \$2.35 in the 850 Series; 0-10 DC Ma in the 350 Serie \$3.45; 0-1 DC Ma (with zero adjuster), \$3.75 in 550 or 95 Series, \$3,95 in the 850 Series; -20 to 3VU in the 850 Series \$5.85. Other meters are correspondingly low in price. You get th benefit of low costs made possible by large quantity production

GUARANTEED: For one year against defective workmanship and material. Will be repaired or replaced if sent postpaid to the factory with 40¢ handling charge.

WIDELY AVAILABLE: Stocked by leading electronic part distributors for prompt deliveries.

JURITE METERS 130 Wallace Street • New Haven 8, Connectice

P. O. Box 1818

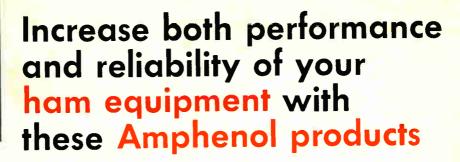

Polyfoam® Coaxial Cable can boost your signal strength as much as 35%. Uses an inert-gas-expanded polyethylene to increase dielectric constant to 1.50 instead of the usual 2.26. Your Amphenol distributor carries RG-8, 11, and 59 in stock.



RF Connectors. The most complete line available anywhere-and your Amphenol distributor has the type and size you need on the shelf available for immediate delivery.



DK Coaxial Switches for antenna switching and similar applications. 14 basic models meet every ham requirement for low cost, high reliability and long life. 100% inspected. Your Amphenol distributor has all commonly used types in stock. Ask for Catalog No. S4.



Do you have this catalog? Amphenol catalog IEC-4 shows virtually every type of connector and coaxial cable you'll ever need, plus technical specs. Your copy is free from your Amphenol distributor, or write us direct at 2803 S. 25th Ave., Broadview, Illinois.



AMPHENDS Distributor Division / Amphenol-Borg Electronics Corporation



DOC AULWURM, W6BBC, maintains contact with other Raytheon field engineers and headquarters staff personnel from his Piedmont, California home.

FIELD ENGINEERING WITH A FUTURE

Doc Aulwurm and his "traveling" ham rig

Arthur (Doc) C. Aulwurm, Senior Field Engineer, and his compact ham rig have traveled the world working on a wide variety of challenging assignments for Raytheon. Doc's story is highly typical of the Raytheon Field Engineer.

Since Doc joined Submarine Signal Company (a predecessor of the present Raytheon organization) in 1945, he has tackled specialized tasks in Karachi, Pakistan; Lakehurst, N. J.; and San Diego, California, among other places.

Doc is now working on sonar equipment at Mare Island Naval Shipyard, California. Future assignments may carry him to other

parts of the world or to headquarters in Massachusetts.

Perhaps you too can qualify for a Raytheon field engineering future. Requirements are previous experience plus an E.E. degree or equivalent in practical know-how in guided missiles, fire control, ground and bombing radar or sonar.


Benefits: attractive salary, insurance, educational programs, relocation assistance, opportunity for advancement. For details, forward your resume to Ronald Guittarr, Electronic Services Division, Raytheon, Northwest Industrial Park, Burlington, Massachusetts.



RAYTHEON COMPANY

ELECTRONIC SERVICES DIVISION



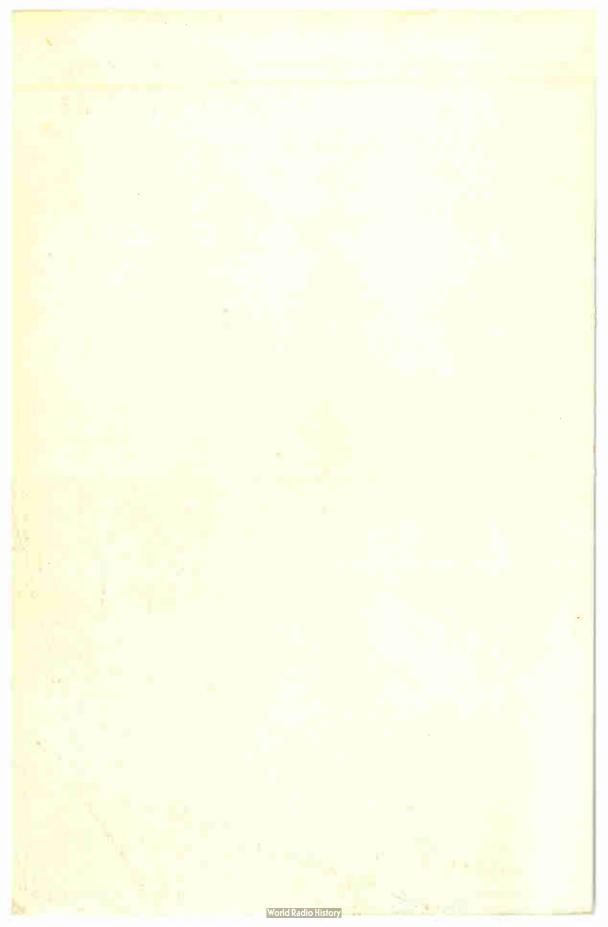

nance curve. For single-signal reception, the audio-frequency image can be reduced by 50 db. or more. Besides practically eliminating the a.f. image, the high selectivity of the crystal filter provides good discrimination against adjacent signals and also reduces the noise.

Two crystal-filter circuits are shown in Fig. 5-25. The circuit at A (or a variation) is found in many of the current communications receivers. The crystal is connected in one side of a bridge circuit, and a phasing capacitor, C_1 is connected in the other. When C_1 is set to balance the crystal-holder capacitance, the resonance curve of the filter is practically symmetrical; the crystal acts as a series-resonant circuit of very high Q and allows signals over a narrow band of frequencies to pass through to the following tube. More or less capacitance at C_1 introduces the "rejection notch" of Fig. 5-24 (at 453.7 kc. as drawn). The Q of the load circuit for the filter is adjusted by the setting of R_1 , which in turn varies the bandwidth of the filter from "sharp" to a bandwidth suitable for phone reception. Some of the components of this filter are special and not generally available to amateurs.

BAND-PASS FILTERS

A single high-Q circuit (e.g., a quartz crystal or regenerative stage) will give adequate single-signal reception under most circumstances. For phone reception, however, either single-sideband or a.m., a band-pass characteristic is more desirable. A band-pass filter is one that passes without unusual attenuation a desired band of frequencies and rejects signals outside this band. A good band-pass filter for single-sideband reception might have a bandwidth of 2500 cycles at -6 db. and 10 kc. at -60 db.; a filter for a.m. would require twice these bandwidths if both sidebands were to be accommodated.

The simplest band-pass crystal filter is one using two crystals, as in Fig. 5-25B. The two crystals are separated slightly in frequency. If the frequencies are only a few hundred cycles apart the characteristic is a good one for c.w. reception. With crystals about 2 kc. apart, a reasonable phone characteristic is obtained. Fig. 5-1 shows a selectivity characteristic of an amplifier with a bandpass (at -6 db.) of 2.4 kc., which is typical of what can be expected from a two-crystal band-pass filter. Compare this with the single-crystal characteristic of Fig. 5-24.

More elaborate crystal filters, using four and six crystals, will give reduced bandwidth at -60 db. without decreasing the bandwidth at -6 db. The resulting increased "skirt selectivity" gives better rejection of adjacent-channel signals. "Crystal-lattice" filters of this type are available commercially for frequencies up to 10 Mc. or so, and they have also been built by amateurs from inexpensive transmitting-type crystals. (See Vester, "Surplus-Crystal High-Frequency Filters," QST, January, 1959; Healey, "High-Frequency Crystal Filters for S.S.B.," QST, October, 1960.)

"Mechanical" filters can be built at frequen-

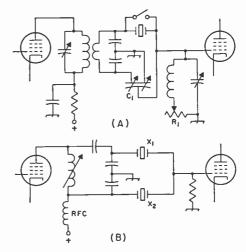


Fig. 5-25—A variable-selectivity crystal filter (A) and a band-pass crystal filter (B).

cies below 1 Mc. These are made up of three sections: an input transducer, a mechanicallyresonant filter section, and an output transducer. The transducers use the principle of magnetostriction to convert the electrical signal to mechanical energy and back again. The mechanically-resonant section consists of carefullymachined metal disks supported and coupled by thin rods. Each disk has a resonant frequency dependent upon the material and its dimensions, and the effective Q of a single disk may be in excess of 2000. Consequently a mechanical filter can be built for either narrow or broad bandpass with a nearly rectangular curve. Mechanical filters are available commercially and are used in both receivers and single-sideband transmitters.

The signal-handling capability of a mechanical filter is limited by the magnetic circuits to from 2 to 15 volts r.m.s., a limitation that is of no practical importance provided it is recognized and provided for. Crystal filters are limited in their signal-handling ability only by the voltage breakdown limits, which normally would not be reached before the preceding amplifier tube was overloaded. A more serious practical consideration in the use of any high-selectivity component is the prevention of coupling "around" the filter (coupling from input to output outside the filter), which can only degrade the action of the filter.

Band-pass filters can also be made by using a number of high-Q inductance-and-capacitance circuits, but their use is generally restricted to frequencies around 100 kc. At higher frequencies it is easier to get desirable selectivity by other means.

Q Multiplier

The "Q Multiplier" is a stable regenerative stage that is connected in parallel with one of the i.f. stages of a receiver. In one condition it narrows the bandwidth and in the other condi-

tion it produces a sharp "null" or rejection notch. A "tuning" adjustment controls the frequency of the peak or null, moving it across the normal pass band of the receiver i.f. amplifier. The shape of the peak or null is always that of a single tuned circuit (Fig. 2-50) but the effective Q is adjustable over a wide range. A Q Multiplier is most effective at an i.f. of 500 kc. or less; at higher frequencies the rejection notch becomes wide enough (measured in cycles per second) to reject a major portion of a phone signal. Within its useful range, however, the Q Multiplier will reject an interfering carrier without degrading the quality of the desired signal

In the "peak" condition the Q Multiplier can be made to oscillate by advancing the "peak" (regeneration) control far enough, and in this condition it can be made to serve as a beat-frequency oscillator. However, it cannot be made to serve as a selective element and as a b.f.o. at the same time. Some inexpensive receivers may combine either a Q Multiplier or some other form of regeneration with the b.f.o. function, and the reader is advised to check carefully any inexpensive receiver he intends to buy that offers a regenerative type of selectivity, in order to make sure that the selectivity is available when the b.f.o. is turned on.

Vacuum-tube versions of the Q Multiplier for 455-kc. i.f. amplifiers are available in kit form; a transistorized version is described later in this chapter. A Q Multiplier will be of no use on c.w. or s.s.b. reception when used with a receiver that employs an oscillating i.f. stage for the b.f.o. Some of the inexpensive "communications" receivers are of this type.

Tee Notch Filter

At low intermediate frequencies (50 – 100 kc.) the T notch filter of Fig. 5-26 will provide a sharp tunable null without an extra vacuum tube.

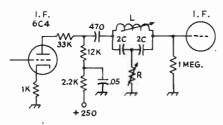


Fig. 5-26—Typicol T-notch filter, to provide o sharp rejection notch ot a low i.f. Adjustment of L chonges the frequency of the notch; odjustment of R controls the depth.

The inductor L resonates with C at the rejection frequency, and when $R=4X_{\rm L}/Q$ the rejection is maximum. ($X_{\rm L}$ is the coil reactance and Q is the coil Q). In a typical 50-kc. circuit, C might be 3900 $\mu\mu\rm f$., making L approximately 2.6 mh. When R is greater than the maximum-

attenuation value, the circuit still provides some rejection, and in use the inductor is detuned or shorted out when the rejection is not desired.

At higher frequencies, the T-notch filter is not sharp enough with available components to reject only a narrow band of frequencies.

Additional I.F. Selectivity

Many commercial communications receivers, and particularly the older ones, do not have sufficient selectivity for amateur use, and their performance can be improved by additional i.f. selectivity. One method is to loosely couple a BC-453 aircraft receiver (war surplus, tuning 190 to 550 kc.) to the front end of the 455-kc. i.f. amplifier in the communications receiver and use the resultant output of the BC-453. The aircraft receiver uses an 85-kc. i.f. amplifier that is sharp for voice work (6.5 kc. wide at -60 db.) and it helps considerably in backing up single-crystal filters for improved c.w. recention.

The BC-453—sometimes called "The Poor Man's Q-Fiver"—uses 12-volt heater tubes and is designed for 24-volt operation. If a 24-volt transformer is available, no wiring changes will be necessary. If a 12-volt transformer is available, the heaters can be rewired. It is usually less expensive to obtain the proper transformer than it is to buy 6.3-volt tubes for the receiver. Any plate-voltage source of 125 to 250 volts at 40 to 80 ma. will be adequate for the B+ supply. A b.f.o. switch and audio and i.f. gain controls should be added to the BC-453 before it is used with the short-wave receiver. Its performance can be checked by tuning in aircraft beacons or low-frequency broadcast stations.

Maximum selectivity will be obtained from the BC-453 when the plungers in the i.f. cans, accessible by unscrewing the caps, are pulled up as far as they will go.

The BC-453 can be coupled to the receiver through a length of shielded wire or small coaxial line. The inner conductor is connected to the antenna post of the BC-453 and the shield is connected to the case. The shield should be connected at the other end to the short-wave receiver chassis, and the inner conductor, suitably insulated, should be wrapped once or twice around the plate pin of the first i.f. amplifier tube in the short-wave receiver. It may require a little experimentation before the proper coupling is obtained; the objective is enough coupling so that the short-wave receiver noise will mask any BC-453 noise, but not so much coupling that the BC-453 is overloaded. Reports of poor performance when using the BC-453 have practically always reduced to overload of the surplus aircraft receiver through too much coupling or coupling at a high-level point in the short-wave receiver.

If a BC-453 is not available, one can still enjoy the benefits of improved selectivity. It is only necessary to heterodyne to a lower frequency the 455-kc. signal existing in the receiver i.f. amplifier and then rectify it after passing it through the sharp low-frequency amplifier. The J. W. Miller Company offers 50-kc. transformers for this application.

RADIO-FREQUENCY AMPLIFIERS

While selectivity to reduce audio-frequency images can be built into the i.f. amplifier, discrimination against radio-frequency images can only be obtained in tuned circuits or other selective elements ahead of the first mixer or converter stage. These tuned circuits are usually used as the coupling networks for one or more vacuum tubes or transistors, and the combinations of circuits and amplifying devices are called radio-frequency amplifiers. The tuned circuits contribute to the r.f. image rejection and the amplifying device(s) determines the noise figure of the receiver.

Knowing the Q of the coil in each tuned circuit between the antenna and the first mixer or converter stage, the image rejection capability can be computed by using the chart in Fig. 2-50. The Q of the input tuned circuit (coupled to the antenna) should be taken as about one-half the unloaded Q of that circuit, and the Q of any other tuned circuit can be assumed to be the unloaded Q to a first approximation (the vacuum tubes will reduce the circuit Q to some extent, especially at 14 Mc. and higher).

In general, receivers with an i.f. of 455 kc. can be expected to have some noticeable image response at 14 Mc. and higher if there are only two tuned circuits (one r.f. stage) ahead of the mixer or converter. Regeneration in the r.f. amplifier will reduce image response, but regeneration usually requires frequent readjustment when tuning across a band. Regeneration is, however, a useful device for improving the selectivity of an r.f. amplifier without requiring a multiplicity of tuned circuits; a practical example will be found later in this chapter.

With three tuned circuits between the antenna and the first mixer, and an i.f. of 455 kc., no images should be encountered up to perhaps 25 Mc. Four tuned circuits or more will eliminate any images at 28 Mc. when an i.f. of 455 kc. is used.


Obviously, a better solution to the r.f. selectivity problem (elimination of image response) is to use an i.f. higher than 455 kc., and most modern receivers use an i.f. of 1600 kc. or higher. The owner of a receiver with a 455-kc i.f. amplifier can enjoy image-free reception on the higher frequencies by using a crystal-controlled converter ahead of the receiver and utilizing the receiver as a "tunable i.f. amplifier" at 3.5 or 7.0 Mc.

For best selectivity r.f. amplifiers should use high-Q circuits and tubes with high input and output resistance. Variable- μ pentodes are practically always used, although triodes (neutralized or otherwise connected so that they won't oscillate) are often used on the higher frequencies because they introduce less noise. However, their lower plate resistance will load the tuned circuits. Pentodes are better where maximum im-

age rejection is desired, because they have less loading effect on the tuned circuits.

Transistor R. F. Amplifier

A typical r.f. amplifier circuit using a 2N370 transistor is shown in Fig. 5-27. Since it is desirable to maintain a reasonable Q in the tuned circuits, to reduce r.f. image response, the base and collector are both tapped down on their tuned circuits. An alternative method, using low-impedance inductive coupling, is shown in Fig. 5-27B; this method is sometimes easier to adjust than the taps illustrated in Fig. 5-27A. The tuned circuits, L_1C_1 and L_2C_2 , should resonate at the operating frequency, and they should be mounted or shielded to eliminate inductive coupling between each other.

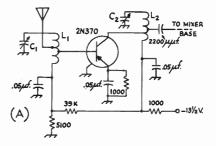

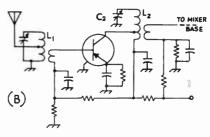


Fig. 5-27—Transistor r.f. amplifier circuit. The low-impedance connections to the base and collector can be
 (A) taps on the inductors or (B) low-impedance coupling links. L₁C₁, L₂C₂—Resonant at signal frequency.

FEEDBACK

Feedback giving rise to regeneration and oscillation can occur in a single stage or it may appear as an over-all feedback through several stages that are on the same frequency. To avoid feedback in a single stage, the output must be isolated from the input in every way possible, with the vacuum tube furnishing the only coupling between the two circuits. An oscillation can be obtained in an r.f. or i.f. stage if there is any undue capacitive or inductive coupling between output and input circuits, if there is too high an impedance between cathode and ground or screen and ground, or if there is any appreciable impedance through which the grid and plate currents can flow in common. This means

110

good shielding of coils and tuning capacitors in r.f. and i.f. circuits, the use of good bypass capacitors (mica or ceramic at r.f., paper or ceramic at i.f.), and returning all bypass capacitors (grid, cathode, plate and screen) for a given stage with short leads to one spot on the chassis. When single-ended tubes are used, the screen or cathode bypass capacitor should be mounted across the socket, to serve as shield between grid and plate pins. Less care is required as the frequency is lowered, but in high-impedance circuits, it is sometimes necessary to shield grid and plate leads and to be careful not to run them close together.

To avoid over-all feedback in a multistage amplifier, attention must be paid to avoid running any part of the output circuit back near the input circuit without first filtering it carefully. Since the signal-carrying parts of the circuit (the "hot" grid and plate leads) can't be filtered, the best design for any multistage amplifier is a straight line, to keep the output as far away from the input as possible. For example, an r.f. amplifier might run along a chassis in a straight line, run into a mixer where the frequency is changed, and then the i.f. amplifier could be run back parallel to the r.f. amplifier, provided there was a very large frequency difference between the r.f. and the i.f. amplifiers. However, to avoid any possible coupling, it would be better to run the i.f. amplifier off at right angles to the r.f.amplifier line, just to be on the safe side. Good shielding is important in preventing over-all oscillation in high-gain-per-stage amplifiers, but it becomes less important when the stage gain drops to a low value. In a high-gain amplifier, the power leads (including the heater circuit) are common to all stages, and they can provide the over-all coupling if they aren't properly filtered. Good bypassing and the use of series isolating resistors will generally eliminate any possibility of coupling through the power leads. R.f. chokes, instead of resistors, are used in the heater leads where necessary.

CROSS-MODULATION

Since a one- or two-stage r.f. amplifier will have a bandwidth measured in hundreds of kc. at 14 Mc. or higher, strong signals will be amplified through the r.f. amplifier even though it is not tuned exactly to them. If these signals are strong enough, their amplified magnitude may be measurable in volts after passing through several r.f. stages. If an undersired signal is strong enough after amplification in the r.f. stages to shift the operating point of a tube (by driving the grid into the positive region), the undesired signal will modulate the desired signal. This effect is called cross-modulation, and is often encountered in receivers with several r.f. stages working at high gain. It shows up as a superimposed modulation on the signal being listened to, and often the effect is that a signal can be tuned in at several points. It can be reduced or eliminated by greater selectivity in the antenna and r.f. stages (difficult to obtain), the

HIGH-FREQUENCY RECEIVERS

use of variable- μ tubes in the r.f. amplifier, reduced gain in the r.f. amplifier, or reduced antenna input to the receiver. The 6BJ6, 6BA6 and 6DC6 are recommended for r.f. amplifiers where cross-modulation may be a problem.

A receiver designed for minimum cross-modulation will use as little gain as possible ahead of the high-selectivity stages, to hold strong unwanted signals below the cross-modulation point. Cross-modulation often takes place in double-conversion superheterodynes at the second converter stage because there is insufficient selectivity up to this point and at this point the signals have quite appreciable amplitudes. Whenever interference drops out quite suddenly with a reduction in the setting of the gain control, cross-modulation should be suspected. Normally, of course, the interference would reduce in amplitude in proportion to the desired signal as the gain setting is reduced.

Gain Control

To avoid cross-modulation and other overload effects in the mixer and r.f. stages, the gain of the r.f. stages is usually made adjustable. This is accomplished by using variable-µ tubes and varying the d.c. grid bias, either in the grid or cathode circuit. If the gain control is automatic, as in the case of a.g.c., the bias is controlled in the grid circuit. Manual control of r.f. gain is generally done in the cathode circuit. A typical r.f. amplifier stage with the two types of gain control is shown in schematic form in Fig. 5-28. The a.g.c. control voltage (negative) is derived from rectified carrier or signal at the detector before the audio amplifier, or in the case of a c.w. or s.s.b. receiver it can be derived from rectified audio. The manual gain control voltage (positive with respect to chassis) is usually derived from a potentiometer across the B+ supply, since the bias can be changed even though little plate current is being drawn.

Tracking

In a receiver with no r.f. stage, it is no incon-

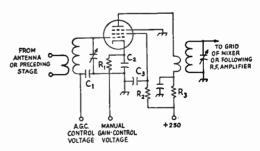


Fig. 5-28—Typical radio-frequency amplifier circuit for a superheterodyne receiver. Representative values for components are as follows:

 C_1 to $C_4-0.01~\mu f.$ below 15 Mc., 0.001 $\mu f.$ at 30 Mc. $R_1,~R_2-See$ Table 5-II. R_3-1800 ohms.

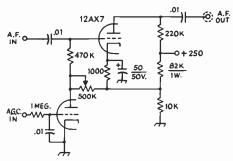


Fig. 5-29—A practical squelch circuit for cutting off the receiver output when no signal is present.

venience to adjust the high-frequency oscillator and the mixer circuit independently, because the mixer tuning is broad and requires little attention over an amateur band. However, when r.f. stages are added ahead of the mixer, the r.f. stages and mixer will require retuning over an entire amateur band. Hence most receivers with one or more r.f. stages gang all of the tuning controls to give a single-tuning-control receiver. Obviously there must exist a constant difference in frequency (the i.f.) between the oscillator and the mixer/r.f. circuits, and when this condition is achieved the circuits are said to track.

In amateur-band receivers, tracking is simplified by choosing a bandspread circuit that gives practically straight-line-frequency tuning (equal frequency change for each dial division), and then adjusting the oscillator and mixer tuned circuits so that both cover the same total number of kilocycles. For example, if the i.f. is 455 kc. and the mixer circuit tunes from 7000 to 7300 kc. between two given points on the dial, then the oscillator must tune from 7455 to 7755 kc. between the same two dial readings. With

the bandspread arrangement of Fig. 5-9A, the tuning will be practically straight-line-frequency if C_2 (bandset) is 4 times or more the maximum capacity of C_1 (bandspread), as is usually the case for strictly amateur-band coverage. C_1 (semicircular plates).

Squelch Circuits

An audio squelch circuit is one that cuts off the receiver output when no signal is coming through the receiver. It is useful in mobile or net work where the no-signal receiver noise may be as loud as the signal, causing undue operator fatigue during no-signal periods.

A practical squelch circuit is shown in Fig. 5-29. A dual triode (12AX7) is used as an amplifier and as a control tube. When the a.g.c. voltage is low or zero, the lower (control) triode draws plate current. The consequent voltage drop across the adjustable resistor in the plate circuit cuts off the upper (amplifier) triode and no signal or noise is passed. When the a.g.c. voltage rises to the cut-off value of the control triode, the tube no longer draws current and the bias on the amplifier triode is now only its normal operating bias, furnished by the 1000-ohm resistor in the cathode circuit. The tube now functions as an ordinary amplifier and passes signals. The relation between the a.g.c. voltage and the signal turn-on point is adjusted by varying the resistance in the plate circuit of the control triode.

Connections to the receiver consist of two a.f. lines (shielded), the a.g.c. lead, and chassis ground. The squelch circuit is normally inserted between detector output and the audio volume control of the receiver. Since the circuit is used in the low-level audio point, its plate supply must be free from a.c. or objectionable hum will be introduced.

IMPROVING RECEIVER SENSITIVITY

The sensitivity (signal-to-noise ratio) of a receiver on the higher frequencies above 20 Mc. is dependent upon the band width of the receiver and the noise contributed by the "front end" of the receiver. Neglecting the fact that image rejection may be poor, a receiver with no r.f. stage is generally satisfactory, from a sensitivity point, in the 3.5- and 7-Mc. bands. However, as the frequency is increased and the atmospheric noise becomes less, the advantage of a good "front end" becomes apparent. Hence at 14 Mc. and higher it is worth while to use at least one stage of r.f. amplification ahead of the first detector for best sensitivity as well as image rejection. The multigrid converter tubes have very poor noise figures, and even the best pentodes and triodes are three or four times noisier when used as mixers than they are when used as amplifiers.

If the purpose of an r.f. amplifier is to improve the receiver noise figure at 14 Mc. and higher, a high- g_m pentode or triode should be used. Among the pentodes, the best tubes are the 6AH6, 6AK5 and the 6BZ6, in the order named. The 6AK5 takes the lead around 30 Mc. The 6J4, 6J6, and triode-connected 6AK5 are the best of the triodes. For best noise figure, the antenna circuit should be coupled a little heavier than optimum. This cannot give best selectivity in the antenna circuit, so it is futile to try to maximize sensitivity and selectivity in this circuit.

When a receiver is satisfactory in every respect (stability and selectivity) except sensitivity on 14 through 30 Mc., the best solution for the amateur is to add a preamplifier, a stage of r.f. amplification designed expressly to improve the sensitivity. If image rejection is lacking in the receiver, some selectivity should be built into the preamplifier (it is then called a preselector). If, however, the receiver operation is poor on the higher frequencies but is satisfactory on the lower ones, a "converter" is the best solution.

Some commercial receivers that appear to lack sensitivity on the higher frequencies can be improved simply by tighter coupling to the antenna. This can be accomplished by changing the antenna feed line to the right value (as determined from the receiver instruction book) or by using a simple matching device as described later in this chapter. Overcoupling the input circuit will often improve sensitivity but it will, of course, always reduce the image-rejection contribution of the antenna circuit.

Regeneration

Regeneration in the r.f. stage of a receiver (where only one stage exists) will often improve the sensitivity because the greater gain it provides serves to mask more completely the first-detector noise, and it also provides a measure of automatic matching to the antenna through tighter coupling. However, accurate ganging becomes a problem, because of the increased selectivity of the regenerative r.f. stage, and the receiver almost invariably becomes a two-handed-tuning device. Regeneration should not be overlooked as an expedient, however, and amateurs have used it with considerable success.

HIGH-FREQUENCY RECEIVERS

High- g_m tubes are the best as regenerative amplifiers, and the feedback should not be controlled by changing the operating voltages (which should be the same as for the tube used in a highgain amplifier) but by changing the loading or the feedback coupling. This is a tricky process and another reason why regeneration is not too widely used.

Gain Control

In a receiver front end designed for best signal-to-noise ratio, it is advantageous in the reception of weak signals to eliminate the gain control from the first r.f. stage and allow it to run "wide open" all of the time. If the first stage is controlled along with the i.f. (and other r.f. stages, if any), the signal-to-noise ratio of the receiver will suffer. As the gain is reduced, the g_m of the first tube is reduced, and its noise figure becomes higher. A good receiver might well have two gain controls, one for the first r.f. stage and another for the i.f. (and any other r.f.) stages. The first r.f. stage gain would be reduced only for extremely strong signals.

TUNING A RECEIVER

C.W. Reception

For making code signals audible, the beat oscillator should be set to a frequency slightly different from the intermediate frequency. To adjust the beat-oscillator frequency, first tune in a moderately weak but steady carrier with the beat oscillator turned off. Adjust the receiver tuning for maximum signal strength, as indicated by maximum hiss. Then turn on the beat oscillator and adjust its frequency (leaving the receiver tuning unchanged) to give a suitable beat note. The beat oscillator need not subsequently be touched, except for occasional checking to make certain the frequency has not drifted from the initial setting. The b.f.o. may be set on either the high- or low-frequency side of zero beat.

The best receiver condition for the reception of code signals will have the first r.f. stage running at maximum gain, the following r.f., mixer and i.f. stages operating with just enough gain to maintain the signal-to-noise ratio, and the audio gain set to give comfortable headphone or speaker volume. The audio volume should be controlled by the audio gain control, not the i.f. gain control. Under the above conditions, the selectivity of the receiver is being used to best advantage, and cross-modulation is minimized. It precludes the use of a receiver in which the gains of the r.f. and i.f. stages are controlled simultaneously.

Tuning with the Crystal Filter

If the receiver is equipped with a crystal filter the tuning instructions in the preceding paragraph still apply, but more care must be used both in the initial adjustment of the beat oscillator and in tuning. The beat oscillator is set as described above, but with the crystal filter set at its sharpest position, if variable selectivity is available. The initial adjustment should be made with the phasing control in an intermediate position. Once adjusted, the beat oscillator should be left set and the receiver tuned to the other side of zero beat (audio-frequency image) on the same signal to give a beat note of the same tone. This beat will be considerably weaker than the first, and may be "phased out" almost completely by careful adjustment of the phasing control. This is the adjustment for normal operation; it will be found that one side of zero beat has practically disappeared, leaving maximum response on the other.

An interfering signal having a beat note differing from that of the a.f. image can be similarly phased out, provided its frequency is not too near the desired signal.

Depending upon the filter design, maximum selectivity may cause the dots and dashes to lengthen out so that they seem to "run together." It must be emphasized that, to realize the benefits of the crystal filter in reducing interference, it is necessary to do all tuning with it in the circuit. Its high selectivity often makes it difficult to find the desired station quickly, if the filter is switched in only when interference is present.

A.M. Phone Reception

In reception of a.m. phone signals, the normal procedure is to set the r.f. and i.f. gain at maximum, switch on the a.g.c., and use the audio gain control for setting the volume. This insures maximum effectiveness of the a.g.c. system in compensating for fading and maintaining constant audio output on either strong or weak signals. On occasion a strong signal close to the

Alignment and Servicing

frequency of a weaker desired station may take control of the a.g.c., in which case the weaker station may disappear because of the reduced gain. In this case better reception may result if the a.g.c. is switched off, using the manual r.f. gain control to set the gain at a point that prevents "blocking" by the stronger signal.

When receiving an a.m. signal on a frequency within 5 to 20 kc. from a single-sideband signal it may also be necessary to switch off the a.g.c. and resort to the use of manual gain control, unless the receiver has excellent skirt selectivity. No ordinary a.g.c. circuit can handle the syllabic bursts of energy from the sideband station, but there are special circuits that will.

A crystal filter will help reduce interference in phone reception. Although the high selectivity cuts sidebands and reduces the audio output at the higher audio frequencies, it is possible to use quite high selectivity without destroying intelligibility. As in code reception, it is advisable to do all tuning with the filter in the circuit. Variable-selectivity filters permit a choice of selectivity to suit interference conditions.

An undesired carrier close in frequency to a desired carrier will heterodyne with it to produce a beat note equal to the frequency difference. Such a heterodyne can be reduced by adjustment of the phasing control in the crystal filter

A tone control often will be of help in reducing the effects of high-pitched heterodynes, sideband splatter and noise, by cutting off the higher audio frequencies. This, like sideband cutting with high selectivity circuits, reduces naturalness.

Spurious Responses

Spurious responses can be recognized without a great deal of difficulty. Often it is possible to identify an image by the nature of the transmitting station, if the frequency assignments applying to the frequency to which the receiver is tuned are known. However, an image also can be recognized by its behavior with tuning. If the signal causes a heterodyne beat note with the desired signal and is actually on the same frequency, the beat note will not change as the receiver is tuned through the signal; but if the interfering signal is an image, the beat will vary in pitch as the receiver is tuned. The beat oscillator in the receiver must be turned off for this test. Using a crystal filter with the beat oscillator on, an image will peak on the side of zero beat opposite that on which desired signals peak.

Harmonic response can be recognized by the "tuning rate," or movement of the tuning dial required to give a specified change in beat note. Signals getting into the i.f. via high-frequency oscillator harmonics tune more rapidly (less dial movement) through a given change in beat note than do signals received by normal means.

Harmonics of the beat oscillator can be recognized by the tuning rate of the beat-oscillator pitch control. A smaller movement of the control will suffice for a given change in beat note than that necessary with legitimate signals. In poorly-designed or inadequately-shielded and -filtered receivers it is often possible to find b.f.o. harmonics below 2 Mc., but they should be very weak or non-existent at higher frequencies.

ALIGNMENT AND SERVICING OF SUPERHETERODYNE RECEIVERS

I.F. Alignment

A calibrated signal generator or test oscillator is a useful device for alignment of an i.f. amplifier. Some means for measuring the output of the receiver is required. If the receiver has a tuning meter, its indications will serve. Lacking an S meter, a high-resistance voltmeter or a vacuum-tube voltmeter can be connected across the second-detector load resistor, if the second detector is a diode. Alternatively, if the signal generator is a modulated type, an a.c. voltmeter can be connected across the primary of the transformer feeding the speaker, or from the plate of the last audio amplifier through a $0.1-\mu f$. blocking capacitor to the receiver chassis. Lacking an a.c. voltmeter, the audio output can be judged by ear, although this method is not as accurate as the others. If the tuning meter is used as an indication, the a.g.c. of the receiver should be turned on, but any other indication requires that it be turned off. Lacking a test oscillator, a steady signal tuned through the input of the receiver (if the job is one of just touching up the i.f. amplifier) will be suitable. However, with no oscillator and tuning an amplifier for the first time, one's only recourse is to try to peak the i.f. transformers on "noise," a difficult task if the transformers are badly off resonance, as they are apt to be. It would be much better to haywire together a simple oscillator for test purposes.

Initial alignment of a new i.f. amplifier is as follows: The test oscillator is set to the correct frequency, and its output is coupled through a capacitor to the grid of the last i.f. amplifier tube. The trimmer capacitors of the transformer feeding the second detector are then adjusted for maximum output, as shown by the indicating device being used. The oscillator output lead is then clipped on to the grid of the next-to-the-last i.f. amplifier tube, and the second-from-the-last transformer trimmer adjustments are peaked for maximum output. This process is continued, working back from the second detector, until all of the i.f. transformers have been aligned. It will be necessary to reduce the output of the test oscillator as more of the i.f. amplifier is brought into use. It is desirable in all cases to use the minimum signal that will give useful output readings. The i.f. transformer in the plate circuit of the mixer is aligned with the signal introduced to the grid of the mixer. Since the tuned circuit feeding the mixer grid may have a very low impedance at the i.f., it may be necessary to boost the test generator output or to disconnect the tuned circuit temporarily from the mixer grid.

If the i.f. amplifier has a crystal filter, the filter should first be switched out and the alignment carried out as above, setting the test oscillator as closely as possible to the crystal frequency. When this is completed, the crystal should be switched in and the oscillator frequency varied back and forth over a small range either side of the crystal frequency to find the exact frequency, as indicated by a sharp rise in output. Leaving the test oscillator set on the crystal peak, the i.f. trimmers should be readigned for maximum output. The necessary readjustment should be small. The oscillator frequency should be checked frequently to make sure it has not drifted from the crystal peak.

A modulated signal is not of much value for aligning a crystal-filter i.f. amplifier, since the high selectivity cuts sidebands and the results may be inaccurate if the audio output is used as the tuning indication. Lacking the a.g.c. tuning meter, the transformers may be conveniently aligned by ear, using a weak unmodulated signal adjusted to the crystal peak. Switch on the beat oscillator, adjust to a suitable tone, and align the i.f. transformers for maximum audio output.

An amplifier that is only slightly out of alignment, as a result of normal drift or aging, can be realigned by using any steady signal, such as a local broadcast station, instead of the test oscillator. One's 100-kc. standard makes an excellent signal source for "touching up" an i.f. amplifier. Allow the receiver to warm up thoroughly, tune in the signal, and trim the i.f. for maximum output.

If you bought your receiver instead of making it, be sure to read the instruction book carefully before attempting to realign the receiver. Most instruction books include alignment details, and any little special tricks that are peculiar to the receiver will also be described in detail.

R.F. Alignment

The objective in aligning the r.f. circuits of a gang-tuned receiver is to secure adequate tracking over each tuning range. The adjustment may be carried out with a test oscillator of suitable frequency range, with harmonics from your 100-kc. standard or other known oscillator, or even on noise or such signals as may be heard. First set the tuning dial at the high-frequency end of the range in use. Then set the test oscillator to the frequency indicated by the receiver dial. The test-oscillator output may be connected to the antenna terminals of the receiver for this test. Adjust the oscillator trimmer capacitor in the receiver to give maximum response on the test-oscillator signal, then reset the receiver

dial to the low-frequency end of the range. Set the test-oscillator frequency near the frequency indicated by the receiver dial and tune the test oscillator until its signal is heard in the receiver. If the frequency of the signal as indicated by the test-oscillator calibration is higher than that indicated by the receiver dial, more inductance (or more capacity in the tracking capacitor) is needed in the receiver oscillator circuit; if the frequency is lower, less inductance (less tracking capacity) is required in the receiver oscillator. Most commericial receivers provide some means for varying the inductance of the coils or the capacity of the tracking capacitor, to permit aligning the receiver tuning with the dial calibration. Set the test oscillator to the frequency indicated by the receiver dial, and then adjust the tracking capacity or inductance of the receiver oscillator coil to obtain maximum response. After making this adjustment, recheck the highfrequency end of the scale as previously described. It may be necessary to go back and forth between the ends of the range several times before the proper combination of inductance and capacity is secured. In many cases, better overall tracking will result if frequencies near but not actually at the ends of the tuning range are selected, instead of taking the extreme dial set-

After the oscillator range is properly adjusted, set the receiver and test oscillator to the high-frequency end of the range. Adjust the mixer trimmer capacitor for maximum hiss or signal, then the r.f. trimmers. Reset the tuning dial and test oscillator to the low-frequency end of the range, and repeat; if the circuits are properly designed, no change in trimmer settings should be necessary. If it is necessary to increase the trimmer capacity in any circuit, more inductance is needed; conversely, if less capacity resonates the circuit, less inductance is required.

Tracking seldom is perfect throughout a tuning range, so that a check of alignment at intermediate points in the range may show it to be slightly off. Normally the gain variation will be small, however, and it will suffice to bring the circuits into line at both ends of the range. If most reception is in a particular part of the range, such as an amateur band, the circuits may be aligned for maximum performance in that region, even though the ends of the frequency range as a whole may be slightly out of alignment.

Oscillation in R.F. or I.F. Amplifiers

Oscillation in high-frequency amplifier and mixer circuits shows up as squeals or "birdies" as the tuning is varied, or by complete lack of audible output if the oscillation is strong enough to cause the a.g.c. system to reduce the receiver gain drastically. Oscillation can be caused by poor connections in the common ground circuits. Inadequate or defective bypass capacitors in cathode, plate and screen-grid circuits also can cause such oscillation. A metal tube with an ungrounded shell may cause trouble. Improper

Improving Performance

screen-grid voltage, resulting from a shorted or too-low screen-grid series resistor, also may be responsible for such instability.

Oscillation in the i.f. circuits is independent of high-frequency tuning, and is indicated by a continuous squeal that appears when the gain is advanced with the c.w. beat oscillator on. It can result from defects in i.f.-amplifier circuits. Inadequate screen or plate bypass capacitance is a common cause of such oscillation.

IMPROVING THE PERFORMANCE OF RECEIVERS

Frequently amateurs unjustly criticize a receiver's performance when actually part of the trouble lies with the operator, in his lack of knowledge about the receiver's operation or in his inability to recognize a readily curable fault. The best example of this is a complaint about "lack of selectivity" when the receiver contains an i.f. crystal filter and the operator hasn't bothered to learn how to use it properly. "Lack of sensitivity" may be nothing more than poor alignment of the r.f. and mixer tuning. The cures for these two complaints are obvious, and the details are treated both in this chapter and in the receiver instruction book.

However, many complaints about selectivity, sensitivity, and other points are justified. Inexpensive, and most second-hand, receivers cannot be expected to measure up to the performance standards of some of the current and top-priced receivers. Nevertheless, many amateurs overlook the possibility of improving the performance of these "bargains" (they may or may not be bargains) by a few simple additions or modifications. From time to time articles in QST describe improvements for specific receivers, and it may repay the owner of a newly-acquired second-hand receiver to examine past issues and see if an applicable article was published. The annual index in each December issue is a help in this respect.

Where no applicable article can be found, a few general principles can be laid down. If the complaint is the inability to separate stations, better i.f. (and occasionally audio) selectivity is indicated. The answer is not to be found in better bandspread tuning of the dial as is sometimes erroneously concluded. For code reception the addition of a "Q Multiplier" to the i.f. amplifier is a simple and effective attack; a Q Multiplier is at its best in the region 100 to 900 kc., and higher than this its effectiveness drops off. The Selectoject is a selective audio device based on similar principles. For phone reception the addition of a Q Multiplier will help to reject an interfering carrier, and the use of a BC-453 as a "Q5-er" will add adjacent-channel selectivity.

With the addition of more i.f. selectivity, it may be found that the receiver's tuning rate (number of kc. tuned per dial revolution) is too high, and consequently the tuning with good i.f. selectivity becomes too critical. If this is the case, a 5-to-1 reduction planetary dial drive mechanism may be added to make the tuning rate more favorable. These drives are sold by the larger supply houses and can usually be added to the receiver if a suitable mounting bracket is

made from sheet metal. If there is already some backlash in the dial mechanism, the addition of the planetary drive will magnify its effect, so it is necessary to minimize the backlash before attempting to improve the tuning rate. While this is not possible in all cases, it should be investigated from every angle before giving up. Replacing a small tuning knob with a larger one will add to ease of tuning; in many cases after doing so it will then be desirable or necessary to raise the receiver higher above the table.

If the receiver appears to lack the ability to bring in the weak signals, particularly on the higher-frequency bands, the performance can often be improved by the addition of an antenna coupler (described elsewhere in this chapter); it will always be improved by the addition of a preselector (also described elsewhere in this chapter).

If the receiver shortcoming is inadequate r.f. selectivity, as indicated by r.f. "images" on the higher-frequency bands, a simple antenna coupler will often add sufficient selectivity to cure the trouble. However, if the images are severe, it is likely that a preselector will be required, preferably of the regenerative type. The preselector will also add to the ability of the receiver to detect weak signals at 14 Mc. and higher.

In many of the inexpensive receivers the frequency calibration of the dial is not very accurate. The receiver's usefulness for determining band limits will be greatly improved by the addition of a 100-kc. crystal-controlled frequency standard. These units can be built or purchased complete at very reasonable prices, and no amateur station worthy of the name should be without one

Some receivers that show a considerable frequency drift as they are warming up can be improved by the simple expedient of furnishing more ventilation, by propping up the lid or by drilling extra ventilation holes. In many cases the warm-up drift can be cut in half. A 7-watt 115-volt lamp mounted under the receiver chassis and wired so that it is turned on when the receiver is turned off will maintain the receiver temperature above the room temperature and will reduce the warm-up drift. The auxiliary heat source is also of help in reducing or eliminating the ill effects of condensation in the receiver, where the receiver is used in a damp location.

Receivers that show frequency changes with line-voltage or gain-control variations can be greatly improved by the addition of regulated voltage on the oscillators (high-frequency and b.f.o.) and the screen of the mixer tube. There is usually room in any receiver for the addition of a VR tube of the right rating.

THE "SimpleX Super Mark II" THREE-TUBE RECEIVER

The name of the receiver shown in Figs. 5-30 and 5-33 derives from "simple," "X" for crystal (filter) and "super" for superheterodyne; hence a "simple crystal-filter superheterodyne." It is an improved version of an earlier model (QST, December, 1958), hence the "Mark II." For less than fifty dollars and a few nights at the workbench, this little receiver will allow you to copy practically any c.w. or s.s.b. signal in the 40- or 80-meter band that a much more expensive receiver might bring in. By the throw of a switch you can tune in WWV on 5.0 Mc. for time signals and standard-frequency transmissions.

Referring to the circuit diagram in Fig. 5-31, the receiver is a superheterodyne with an intermediate frequency of 1700 kc. With the h.f. oscillator tuning 5.2. to 5.7 Mc., the 3.5- or 7-Mc. amateur bands can be tuned nierely by retuning the input circuit. Since C_2 is large enough to hit the two bands without a coil change, the bandchanging process consists of turning C_2 to the low- or high-capacitance end of its range. To copy WWV at 5 Mc., the oscillator must be tuned to 3.3 Mc., and this is done by switching in (via S_{2A}) a preset capacitor, C_5 , across the oscillator circuit.

The advantage of a two-band receiver of this type is that the absence of coil switching makes it easy to build a stable high-frequency oscillator, and the stability of this oscillator then determines the stability of the receiver. Higher-frequency bands (14, 21 and 28 Mc.) can be listened to by adding a crystal-controlled converter; the construction of such a converter is described later in this chapter.

Selectivity at the i.f. is obtained through the use of a single crystal. This, in conjunction with the regeneration provided by the detector, is sharp enough to provide a fair degee of single-signal c.w. reception and yet is broad enough for copy of an s.s.b. phone signal.

In the detector stage, the pentode section of a 6U8A is used as a regenerative detector, and the triode section serves as the b.f.o. Stray coupling at the socket and in the tube provides adequate injection. The regeneration control is not mounted on the panel because, once set below the threshold of oscillation, it is not touched. The

regeneration is not essential to good c.w. or s.s.b. reception, but it helps considerably on a.m. reception. Audio amplification is obtained from the two triode sections of a 6CG7. The primary of a small output transformer, T_1 , serves as the coupling for high-impedance headphone output, and a small loudspeaker or low-impedance headphones can be connected to the secondary.

The power supply uses a small transformer and two selenium rectifiers in a full-wave voltage-doubling circuit. This is about as inexpensive a power supply as can be built, and it also has the advantages of not occupying much space and not generating much heat.

A switch, S_{1A} , at the input of the receiver is included so that the receiver can be used to listen to one's own transmitter without too severe blocking. Another section of the same switch, S_{1B} , shifts the mixer screen voltage from its operating value to zero, to reduce further the sensitivity of the receiver while one is transmitting. If it reduces it so much that the receiver has too little gain, this section of the switch can be omitted from the circuit and the mixer operated at full screen voltage at all times.

An $8 \times 12 \times 3$ -inch aluminum chassis takes all of the parts without crowding, and the location of the components can be seen in the photographs. The receiver is shown with a 7-inch high standard relay-rack panel, which leaves room at one end of the panel for auxiliary equipment or a small transmitter. If desired, a shorter panel of 32-inch aluminum can be used. The panel is held to the chassis by the two switches and the headphones jack. The tuning capacitor, C3, is mounted on a small aluminum bracket, and the capacitor is driven by a Jackson Brothers Planetary Vernier (Arrow Electronics, N.Y.C.) via a Millen 39016 coupling. Before the bracket is finally fastened to the chassis the capacitor and bracket should be used to locate the center for the vernier hole. It pays to take care in mounting the tuning capacitor and its drive, since a smooth tuning drive is essential to any receiver. A National HRT knob is used to turn the vernier, and a paper scale is made as can be seen in one of the photographs.

Tie points are used liberally throughout the

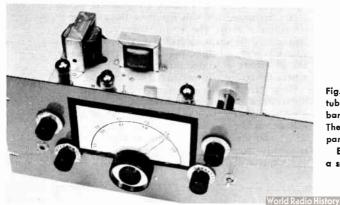


Fig. 5-30—The SimpleX Super receiver uses three dual tubes and a crystal filter to cover the 80- and 40-meter bands, and it can tune to 5 Mc. for copying WWV. The dial scale is made from white paper held to the panel by black tape; the index is clear plastic.

Extra panel space is provided for control circuits or a small transmitter.

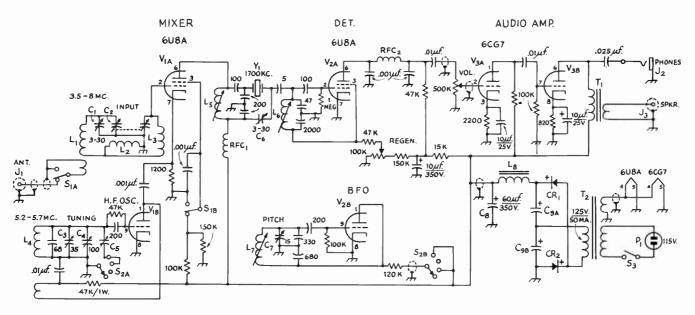


Fig. 5-31—Circuit diagram of the SimpleX Super receiver. Unless otherwise indicated, capacitances are in μμf., resistances are in ohms, resistors are ½ watt. Polarity is shown on electrolytic capacitors, 680 μμf. or less are silver mica or NPO ceramic, 2000-μμf. fixed capacitor is mica. Capacitors specified in decimal-μf, values are ceramic,

 C_1 —3- to 30- $\mu\mu$ f. mica compression trimmer.

C₂-140-140 dual variable (Hammarlund HFD-140).

C₈-35-\(\mu\mu\midget\) raidale (Hammarlund HF-35).

C₄-100-μμf. midget trimmer (Hammarlund MAPC-100).

 C_5 —180- $\mu\mu$ f. silver mica in parallel with 150- $\mu\mu$ f. mica-

compression trimmer (Arco 424).

 C_6 —3- to 30- $\mu\mu$ f, mica compression trimmer with adjustment screw removed.

 C_T -15- $\mu\mu$ f. midget variable (Hammarlund HF-15).

C₈-60-\(mu\)f. 350-v. electrolytic (Mallory TC-68 or equiv.).

C₉-40-40-μf. 150-v. electrolytic, negative not common (Mallory TCS-48 or equiv.).

CR₁, CR₂-50-ma, 130-v, selenium rectifier (Tarzian 50 or equiv.).

J₁, J₃-Phono jack.

J₂-Phone jack.

L1, L3, L4,-See Fig. 5-32.

L₂-18 t. No. 22 enam., closewound on ¼-diam. form (1-watt resistor, 100K or more).

L₅, L₆-105-200 μh. shielded inductor (North Hills SE-120-H).

L₇-36-64 µh. shielded inductor (North Hills SE-120-F).

L₈-16-henry 50-ma. filter choke (Knight 62G137 or equiv.).

P₁—A.c. line plug, preferably fused.

S₁—D.p.d.t. togale.

S2-Two-pole 6-position (4 used) rotary switch (Centralab PA-2003 or equiv.).

S₃-S.p.s.t. toggle

RFC₁, RFC₂—1-mh. r.f. choke (Millen J300-1000).

T₁-Small output transformer, 10K plate to voice coil (Stancor A-3879 or equiv.).

T₂-125-v. 50-ma. and 6.3-v. 2-amp. power transformer (Knight 61G411 or equiv.).

Y₁-1700-kc. crystal (International Crystal FA-5 or equiv.) (All radio stores do not handle all of the above components. For prices and names of dealers, write to North Hills Electronics Inc., Glen Cove, L.I., N.Y.; Knight is handled by Allied Radio, 100 N. Western Ave., Chicago 80, III.)

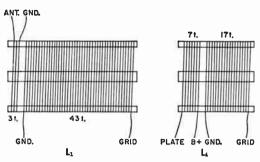


Fig. 5-32—Details of the coil construction. Each one is made from B & W 3012 Miniductor or Illumitronic 632 stock, which is wound 32 t.p.i. and $\frac{3}{4}$ -inch diameter. The separation between coils in L_1 is $1\frac{1}{2}$ turns; the separation between coils in L_4 is 1 turn. L_3 is 43 turns of the same stock.

It is important that the coils be connected as indicated. The coil stock can be cut to the required lengths by pushing in a turn, cutting it inside the coil and then pushing the newly cut ends through to outside the coil. Once outside, the wire can be peeled away with the help of long-nose pliers. When sufficient turns have been removed, the support bars can be cut with a fine saw.

receiver, as junctions for components and interconnecting wires. The coils L₃ and L₄ are mounted on tie points, using short leads, and L_1 is mounted on S_{1A} . If the leads from L_4 are too long, the coil will be "floppy" and the receiver may be unstable. Fig. 5-32 shows how the coils are constructed and connected. The leads from C_2 are brought through the chassis in insulating rubber grommets. The 3- to $30-\mu\mu f$. mica compression trimmer across L_1 is soldered to the associated section of C2. C2 is mounted on top of the chassis and surrounded by a Bud CU-3002-A Minibox, which serves as a dust cover. The partition between the two sections of C2 should be grounded to the chassis, to prevent capacitive coupling between the two sections. The coil L_2 is wound on a high-resistance 1-watt resistor; the ends of the coil are soldered to the leads of the resistor, and the winding will stay in place readily if the resistor is notched at each end before the winding is started.

The receiver is wired with shielded wire for many of the leads, in an effort to minimize hum



HIGH-FREQUENCY RECEIVERS

in the audio and feedthrough around the crystal filter. The shielded leads are marked in Fig. 5-31 where feasible; the simple rule to follow is to shield all B+ leads along with those shown shielded in Fig. 5-31. For ease of wiring, these shielded leads should be installed first or at least early in the construction. As the wiring progresses, a neat-looking unit can be obtained by dressing the leads and components in parallel lines or at right angles. D.c. and a.c. leads can be tucked out of the way along the edges of the chassis, while r.f. leads should be as direct as is reasonable.

If this is a first receiver or construction job, there are several pitfalls to be avoided. When installing a tube socket, orient the socket so the grid and plate leads will be direct and not cross over the socket.

Another thing is to avoid stranded wire for making connections throughout the receiver. Where stranded wire must be used, be careful to avoid wild strands that stray over to an adjacent socket terminal. No. 20 or 22 insulated solid tinned copper wire should be used for connections wherever no shielding is used. Long bare leads from resistors or capacitors should be covered with insulating tubing unless they go to chassis grounds.

The final bugaboo is a poorly-soldered connection. If this is first venture, by all means practice soldering before starting to wire this receiver. Read an article or two on how to solder, or get a friend to demonstrate. A good soldering iron is an essential; there have been instances of a first venture having been "soldered" with an iron that would just barely melt the solder; the iron was incapable of heating the solder and work to where the solder would flow properly.

When the wiring has been completed and checked once more against the circuit diagram, plug in the tubes and the line cord and turn on the receiver through S₈. The tube heaters should light up and nothing should start to smoke or get hot. If you have a voltmeter you should measure about 270 volts on the B+ line.

With headphones plugged in the receiver, you should be able to hear a little hum when the volume control is advanced all the way. If you can't hear any hum, touching a screwdriver to Pin 2 of V_{2A} should produce hum and a loud click. This shows that the detector and audio amplifier are working. The 100K regeneration control should be set at mid range.

The next step is to tune L_5 , L_6 and L_7 to 1700 kc., the crystal frequency. If you have or can

Fig. 5-33—Top view of the SimpleX Super. The tube at the left is the mixer-oscillator 6U8A; the 6CG7 audio amplifier is at the far right. The black knob is on the regeneration control. Toggle switch under the a.c. line cord is the a.c. line switch, S₈. Phono jack at left is the antenna terminal; phono jack at right near volume control is speaker jack, J₈.

World Radio History

borrow a signal generator, put 1700-kc. r.f. in at the grid of the 6U8A mixer and peak L_{5} and L_{6} . Lacking a signal generator, you may be lucky enough to find a strong signal by tuning around with C_3 , but it isn't likely. Your best bet is to tune a broadcast receiver to around 1245 kc.; if the receiver has a 455-kc. i.f. the oscillator will then be on 1700 kc. Don't depend upon the calibration of the broadcast receiver; make your own by checking known stations. The oscillator of the broadcast receiver will furnish a steady carrier that can be picked up by running a wire temporarily from the grid of the 6U8A mixer to a point near the chassis of the b.c. receiver. Adjust L_7 until you get a beat with the 1700-kc. signal, and then peak L_5 and L_6 . If the signal gets too loud, reduce the signal by moving the wire away from the b.c. receiver. Now slowly swing the signal frequency back and forth with the b.f.o. turned off; a spot should be found where the noise rushes up quickly and then drops off. This is the crystal frequency, and L₅ and L₆ should be peaked again on this frequency.

An antenna connected to the receiver should now permit the reception of signals. With C2 nearly unmeshed, the input tuning will be in the region of the 7-Mc. band, and with C2 almost completely meshed, the input circuits will be near 3.5 Mc. Do the tuning with the C_4 in the oscillator circuit, until a known frequency is found (it can be a signal from the station transmitter). Let's say the transmitter has a crystal at 3725 kc. Set C_3 at half capacitance and tune with C_4 until the transmitter is heard. No antenna should be needed on the receiver for this test. Once C₄ is set, put the antenna on the receiver and look around for other known signals. (CHU, the Canadian standard-frequency station at 7335 kc., is a good marker.) With luck the tuning should just be able to cover the 80-meter band; if it covers one end but not the other, a minor readjustment of the trimmer is indicated.

Once the receiver is aligned to receive signals,

switch S₂ so that the b.f.o. is turned off. Advance the regeneration control (turn arm away from grounded end) and a point will be found where the noise increases and a slight "thump" is heard. This is the point where the detector oscil-

Fig. 5-34—Shielded wire, used for most of the d.c. and 60-cycle leads, lends to the clean appearance underneath the chassis. Toggle switch at the left shorts the input of the receiver, and the adjacent rotary switch handles the b.f.o. and the padding capacitor for WWV.

The pitch control, C₇, is at the right, next to the headphone jack. Power supply components (C₈, C₉ and CR₁, CR₂) are mounted on or near rear wall of chassis.

lates; just below this is the most sensitive condition for the reception of a.m. phone signals. Set the regeneration control at this point.


Turn the b.f.o. back on and tune in a c.w. signal. Tuning through the signal with the tuning knob on C_0 , note that the signal is louder on one side of zero beat than on the other. Experiment with the setting of the PITCH control until the maximum single-signal effect (louder one side than the other) is obtained. It may be necessary to pull up the plate of C_0 and to retune L_0 and L_0 before this is accomplished. After a little adjustment, however, the single-signal effect should be quite apparent.

All that remains is to install the dial scale and calibrate it. A 100-kc. oscillator is ideal for this job; lacking one or the ability to borrow one, other signals must be used. If the crystal filter is 1700 kc. exactly, the 80- and 40-meter calibrations will coincide as they do on the scale shown in Fig. 5-30; if not, the calibration marks will be offset on the two bands.

To find WWV at 5 Mc., set S_2 so that C_6 is switched in and the b.f.o. is on and adjust C_6 so that WWV falls on scale.

It may be noticed that tuning C_2 has a slight effect on the tuning of the signal. In other words, tuning C_2 "pulls" the oscillator slightly. To remedy this would have made the receiver more complicated, and the simple solution is merely to first peak C_2 on noise and then tune with C_3 . If two peaks of noise are found in the 80- or 40-meter bands, adjust C_1 until they coincide.

This will be found to be a practical receiver in every way for the c.w. (or s.s.b.) operator. The tuning rate is always the same on 80 or 40, or 15 with a converter, and 21-Mc. s.s.b. signals tune as easily as those on 3.9 Mc. The warm-up drift is negligible, and the oscillator is surprisingly insensitive to voltage changes. Whether or not the oscillator is insensitive to shock and vibration will depend upon the care with which the components are anchored to their respective tie points.

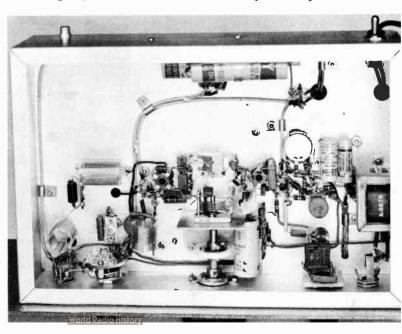

THE 2X4+1 SUPERHETERODYNE

The receiver shown in Figs. 5-35, 5-37 and 5-38 is a two-band four-tube (2X4) receiver with a transistor (+1) 100-kc. frequency standard. Other features include the ability to tune to 5 Mc., for the reception of WWV, and a dual-cystal filter for single-sideband and single-signal c.w. reception. Tuning the 40- and 80-meter amateur bands with good stability and selectivity, the receiver can be used on other bands by the addition of crystal-controlled converters ahead of it.

Referring to the circuit in Fig. 5-36, the pentode section of a 6U8-A is used as a mixer, with the triode portion of the same tube serving as the oscillator. The i.f. is 1700 kc. and the oscillator tunes 5.2 to 5.7 Mc.; tuning the input circuit to the 80-meter band brings in 80-meter signals, and all that is required to hear 40-meter signals is to swing the input tuning, C_1 , to the low-capacitance end of its range. Although, e.g., a 7.05-Mc. (5.35 + 1.7) and a 3.65-Mc. (5.35 -1.7) signal will appear at the same setting of the tuning dial, the two signals cannot be received simultaneously because the double-tuned circuit, C_{1A} , L_1 , and C_{1B} , L_8 , between antenna and mixer grid provides the necessary rejection. Coupling between the two circuits is provided by a small common inductor, L2. To make the two circuits track over the entire range, a 3- to 30-µµf trimmer is provided to compensate for the input capacitance of the mixer. For WWV reception, capacitance Co is added to the oscillator circuit to bring its frequency to 3.3 Mc.

The mixer is followed by the dual crystal filter at 1700 kc. and a stage of i.f. amplification. I.f.

gain is manually controlled by a variable bias control in the cathode circuit of the 6BA6 i.f. amplifier stage. A triode section of a 6CG7, V_{2A} , serves as a grid-leak detector, and the other section is used as the b.f.o. A two-stage audio amplifier follows, providing high-impedance output for headphones or low-impedance output for a loudspeaker. The audio power is sufficient to give more than enough high-impedance headphone volume and quite adequate loudspeaker volume in a quiet room.

The power supply includes a 0C3 to supply regulated 105 volts for the two oscillators and the screen of the mixer.

The transistor 100-kc. calibration oscillator uses for its power source the 8 volts developed across the cathode resistor of $V_{\rm SB}$. Switch S_1 turns the oscillator on and off and also adds the capacitance to the oscillator circuit that permits WWV reception. The four positions of S_1 are off—wwv (only)—CAL (oscillator only)—Both. Although the 100-kc. standard as not essential to the operation of the receiver, its inclusion will be found to be quite valuable.

Construction

The receiver is built on an $8 \times 12 \times 3$ -inch aluminum chassis. A panel can be made from .080-inch thick sheet aluminum or from a standard $8\frac{3}{4}$ -inch rack panel. While the rack panel will be more substantial, it really isn't necessary, and the sheet stock will be adequate. The panel is held to the chassis by the b.f.o. capacitor, C_8 , the line/b.f.o. switch, S_2 , the dial, and an extra pair of 6-32 screws.



Fig. 5-35—The 2X4 + 1 superheterodyne is a four-tube receiver with 7-tube performance. It tunes the 80- and 40meter amateur bands, and provision is included for receiving WWV on 5 Mc. A built-in crystal oscillator provides 100-kc. frequency markers throughout the bands. Black knob on the left-hand side controls the calibration oscillator and the WWV reception.

Fig. 5-36—Circuit diagram of the 2X4 + 1 super-heterodyne. Unless indicated otherwise, decimal capacitances are in μf., other capacitances in μμf., resistors are ½ watt.

- C1-Dual variable, 140 µµf. per section (Hammarlund MCD-140-M).
- C_{2} , C_{3} —480- $\mu\mu$ f. mica compression trimmer (Arco-Elmenco 466).
- C4-4-30 uuf, trimmer (Erie TS2A).
- C₅-100-µµf. midget variable (Hammarlund HF-100).
- $C_6-240 \mu\mu f$. $\pm 5\%$ mica in parallel with $30-\mu\mu f$. mica compression trimmer.
- C_7 —35- $\mu\mu$ f, midget variable (Hammarlund HF-35).
- C_8 -5- $\mu\mu$ f. midget variable (Hammarlund HF-15 with 3 plates removed).
- C₈-3 µµf. approx. Insulated wires twisted together for 3 turns.

- J₁—Phono jack.
- L₁, L₂-43 turns No. 24, 34-inch diam., 32 t.p.i. (B&W 3012 or Illumitronic 632). Coupling coil on L1 is 5 turns, spaced 1 turn from L1.
- La-16 turns No. 20 enam., closewound on 1/4-inch diam. form (100K or higher 1-watt resistor).
- L-7 turns No. 24, part of L5 stock, 1/32 inch from Ls. L-17 turns No. 24, 34-inch diam., 32 t.p.i. (B&W 3012 or Illumitronic 632).
- L_s, L₇—64 to 105 μ h., adjustable (North Hills 120-G in North Hills S-120 shield can).
- L_8 -36 to 64 μ h., adjustable (North Hills 120-F in North Hills S-120 shield can).
- Le-15-henry, 75-ma. filter choke (Stancor C-1002).

- RFC1, RFC2-2.2 mh., self resonant at 1.6 Mc. (Miller 9350-36 or Miller J300-1500).
- RFC_s-10 mh. (National R-50-I).
- S₁-2-pole 6-position (4 used) miniature ceramic switch (Centralab PA-3 with Centralab PA-301 index, 2½ inches used).
- S₂-2-pole 3-position rotary switch (Centralab 1472). T₁-3-watt, 8000 to 3.2 ohms, output transformer (Stancor A-3329).
- T₂-650 v.c.t. at 55 ma., 5 v., 6.3 v. at 2 amp. (Stancor PC-8407).
- Y1. Y2-1700-kc, crystals, FT-243 holders.
- Ys-100-kc. (James Knight H-93 or equiv.)

122

It is worth while to mount the tuning capacitor, C_7 , as accurately as possible with respect to the National ICN dial. For minimum backlash and maximum strength, C_7 is mounted on a three-sided aluminum housing that is securely fastened to the chassis on three sides by $\frac{3}{6}$ -inch lips. A good flexible insulated coupling should be used between dial and capacitor shaft—a Millen 39006 is shown is the photograph.

The location of most of the major components can be determined by reference to the photographs. The inductors L_1 , L_3 and L_4 , L_5 are supported by suitable tie strips, as are the two 480- $\mu\mu$ f. mica compression trimmers, C_2 and C_3 , in the crystal filter circuit and the pair of 330- $\mu\mu$ f. capacitors in the b.f.o. L_1 should be wired so that the outside ends go to antenna and grid, and L_4 , L_5 should be wired with outside ends to plate and grid. L_2 is supported by its leads in a hole in the chassis; a rubber grommet prevents a short to chassis.

Since the rotor of C_1 must not make contact with the panel, a large clearance hole must be provided for the shaft bushing, and a pair of extruded fiber washers used to insulate the bushing from the panel. A brass screw or bayonet lug should be set into the chassis at the shield partition between the two stators of C_1 , and the shield soldered to this chassis connection. The

HIGH-FREQUENCY RECEIVERS

3- to 30- $\mu\mu$ f, compression trimmer across C_{1A} can be soldered between rotor and shield partition.

Many of the connections are made with shielded leads, to minimize hum and chances for feedback or feedthrough. The shielded leads are indicated in Fig. 5-36. The lead from the antenna jack is run in RG-58/U coaxial cable, as is the short lead from C_8 to a 330- $\mu\mu$ f. capacitor. Heater leads to the tubes are made of shielded wire. The shielded leads to the dial lamps are not indicated in Fig. 5-36 but they can be seen in Fig. 5-37

Alignment

The alignment procedure can be simplified if a short-wave receiver or a signal generator can be borrowed. Lacking these, a grid-dip meter can be used to provide a signal source and to check the resonances of the tuned circuits. If the 100-kc. oscillator can be checked on another receiver, it can be used to align the receiver. A broadcast receiver will tell if the 100-kc. oscillator is functioning—it should be possible to identify several of the oscillator's harmonics at 100-kc. intervals in the broadcast band, by the reduction in noise at those points.

The audio amplifier of the receiver can be checked by turning on the receiver and listening

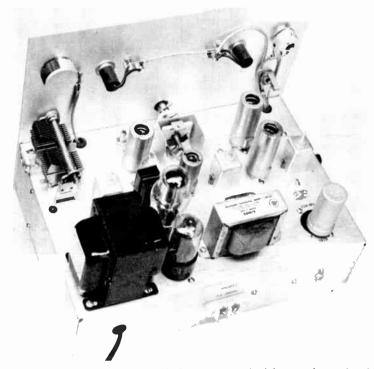


Fig. 5-37—Top view of the 2X4 + 1 receiver. The dual capacitor at the left tunes the receiver input. The main tuning capacitor, rear center, is mounted on a three-sided aluminum bracket for maximum stability. The tube to the left of the bracket is the 6U8-A mixer-oscillator stage, and the 6BA6 i.f. stage is in front of the main tuning capacitor. The remaining tubes in shields are the 6CG7 detector/b.f.o. and the audio 6CG7 (near panel). Metal can plugged in socket above antenna jack houses 100-kc. calibrating crystal.

2X4 + 1 Superhet

to the headphones as the audio gain control is advanced. When it is full clockwise a low-pitched hum should be just audible in the headphones. A further check can be made by bringing a finger near the arm of the audio gain control—the hum should increase.

If a means is available for checking the frequency of the b.f.o., it should be turned on at S_2 and set on or about 1700 kc. by means of the slug in L₈. Do this with C₈ set at half scale. If a broadcast receiver is the only measuring equipment you have, a 1700-kc. signal can be derived from it by tuning the receiver to 1245 kc., which puts its oscillator on 1700 kc. if the standard 455-kc. i.f. is used. A wire from around the receiver to the 2X4 + 1 should provide sufficient signal. Feeding a 1700-kc. signal into the detector by laying the source wire near the grid of the 6BA6 (i.f. gain arm at ground), it should be possible to peak L_7 for maximum signal and, as the signal frequency is changed slightly, a change in pitch of the whistle should be heard. With no incoming signal, a slight rushing noise should be heard in the headphones when the b.f.o. is switched on by S_2 . If this rushing noise is just barely discernible increase the capacitance at Co by adding a few more twists.

If the oscillator $V_{\rm 1R}$ is operating, a voltmeter connected across the 4700-ohm 1-watt resistor in its plate lead should show an increase in voltage

when the stator of C_8 or C_7 is shorted to ground momentarily with a screwdriver or other conductor. Connect the + lead of the voltmeter to the side of the resistor running to + 105 and the —connection to the .001-μf. side. If the oscillator doesn't work, it may be because the outside turns of L_4 and L_5 are not connected to plate and grid respectively. With the b.f.o. on and C1 almost fully meshed, set the tuning capacitor C_7 at about 90 per cent full capacitance. Run C₆ to full capacitance and slowly reduce capacitance. At one point you should hear a loud signal, the second harmonic of the b.f.o. at 3400 kc. If the b.f.o. is reasonably close to frequency, turning on the calibration oscillator should give a weaker signal nearby (on the main tuning dial). Tune C7 to a higher frequency (less capacitance) and you should hear another weaker signal, the 35th harmonic of the oscillator (3500 kc.). Peak C_1 for maximum signal and leave it. Run C₇ back to about 90 per cent full capacitance and then slowly reduce capacitance at C₅ until the 35th harmonic of the oscillator is again heard. If a 3500-kc. signal is available the adjustment can be made in a more straightforward manner.

Once the oscillator trimmer C_{δ} has been set to give the proper tuning range of the oscillator circuit (5.2 to 5.7 Mc.), the next problem is that of adjusting the crystal filter circuit. With a capacitance bridge, or a grid-dip meter and an in-

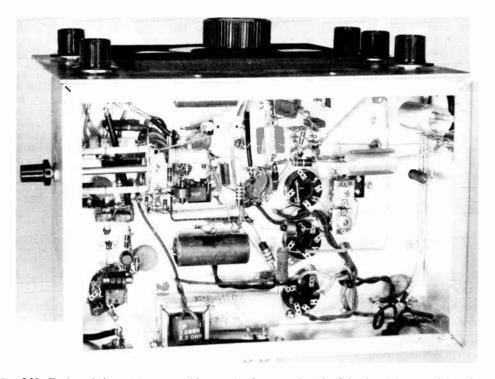


Fig. 5-38—The input inductor L_1 is supported by a terminal strip on the side of the chassis (upper right), and L_3 is supported nearby by a terminal strip mounted on the chassis. The coils are at right angles to minimize inductive coupling. L_2 is supported by the grommet in the chassis. The oscillator inductors, L_1L_5 , are also supported by a terminal strip (top center). A mica compression trimmer to the left of the oscillator inductors is used to center WWV on the tuning dial; the pair of compression trimmers below L_3 are in the crystal filter circuit.

ductance, are set the two capacitors C2 and C8 at the same capacitance (near maximum compression) before soldering them in the receiver. The actual value of capacitance isn't important. Lacking these instruments, tighten the capacitors to full compression and then loosen their screws by 3/4 turn. Tune in a signal—it can be from the 100-kc. oscillator or any other steady source—and peak L₀ for maximum response. Tune off the signal until it disappears and set the pitch control, C₈, to a point where the background noise is reasonably high-pitched. This is easy to determine because at the lowest-pitched point there will be an increase in hum; make the lowest-pitched point the center of the knob scale by adjustment of L₈, and then set the pitch control to one end of its range. Tune back to the signal and "rock" the tuning, C₇, as you change the adjustment of L₆. Look for a condition that gives considerably more response on one side of zero beat than on the other. It is a good idea to buy several extra 1700-kc, crystals and try them in different combinations. Small changes in the setting of C2 or C3 will have an effect on the selectivity characteristic, but bear in mind that a change in C2 or C3 must be compensated for by a readjustment of L₆. With a little patience it should be possible to obtain a marked difference in the output strength on the two sides of zero beat. This will "flip over" to the other side if the pitch control is set at the other end of its range.

The remaining alignment job consists of bringing the input circuits into resonance on both bands. With a signal tuned in at 40 meters, "rock" C_1 back and forth to see if there are two (close-together) points where the signal peaks. If there are, adjust the 3-30- $\mu\mu$ f. trimmer across L_1 until only one peak is found. Check on 80 meters in a similar fashion. If for any reason it is found that the two-peak condition can be eliminated on only one band at a time, it indicates an abnormal amount of antenna reactance, and a compromise adjustment will have to be made. It can also mean that the antenna is not coupled tightly enough to L_1 , which will require increasing the number of turns in the antenna coil.

The antenna coil on L_1 is of necessity a compromise. The 5 turns specified in Fig. 5-36 is

HIGH-FREQUENCY RECEIVERS

correct for an impedance level of about 100 ohms. If the antenna used with the receiver has a 50-or 75-ohm feedline (coaxial line or Twin-Lead), a 3-turn coil is recommended. If the feedline is 300-ohm Twin-Lead, the antenna coil should be 11 turns. With a "random" wire for the receiving antenna, the 5-turn coil is as good a compromise as any.

In operation, the receiver input control, C_1 , should be set for maximum volume on the incoming signal or noise. The i.f. gain should be run at close to minimum on all but the weakest signals, and the audio gain control should be set for comfortable headphone or speaker volume. If an antenna changeover relay is used, it may be possible to monitor your own transmitter by detuning the input circuit to another band; this ability will depend upon the transmitter power and field in the vicinity of the receiver.

Frequency Standard

No trouble should be encountered with the 100-kc. oscillator if care is exercised in handling the transistor. When soldering its leads in place, hold the lead with a pair of pliers; the metal of the pliers will absorb heat and prevent injury to the transistor.


To tune the receiver to WWV, set C1 to mid scale, set S_1 at the WWV position, peak C_1 on noise and slowly tune with C_6 . On a busy day a wide variety of signals will be heard in this region look for one with steady tone modulation and time ticks. If it can't be found within the range of C_6 , set C_7 near one end of its range and try again. An alternate method is to disconnect the antenna, establish the position on the tuning dial (C_1) of several 100-kc. harmonics, connect the antenna and investigate each one of these frequencies. Depending upon one's geographical location, there will be times when WWV cannot be heard on 5 Mc., so don't be discouraged by failure on the first try. Once WWV has been located with good strength, the 50th harmonic of the 100-kc. crystal can be brought to zero beat with WWV by adjustment of C_4 . If the harmonics are too loud and tend to overload the receiver, use a smaller capacitor (10 to 22 $\mu\mu$ f.) than the 47 $\mu\mu$ f. shown in Fig. 5-36.

ADAPTOR PLUG

The sketch below shows an exploded view of an adaptor plug which adapts a conventional u.h.f. series connector for mating with a phono jack. To assemble the plug, solder a 1-inch length of No. 12 copper wire to the center conductor of an SO-239 connector. Next sweat-solder the cap end of a phono plug into the small end of an 83-1H hood. Slip the hood and plug assembly onto the SO-239 connector so that the No. 12 wire inserts in the center conductor of the phono plug. Attach the hood to the connector

with machine screws and solder the wire that is in the tip of the phono plug.

–Robert J. Jarnutowski, K9ITS

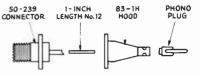

U.h.f. series-to-phono-plug adaptor.

A SELECTIVE CONVERTER FOR 80 AND 40 METERS

Many inexpensive "communications" receivers are lacking in selectivity and bandspread. The 80- and 40-meter performance of such a receiver can be improved considerably by using ahead of it the converter shown in Figs. 5-39 and 5-41. This converter is not intended to be used ahead of a broadcast receiver except for phone reception, because the b.c. set has no b.f.o. or manual gain control, and both of these features are necessary for good c.w. reception. The converter can be built for less than \$20, and that cost can be cut

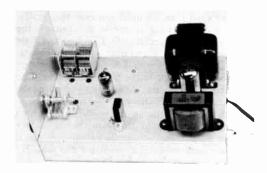


Fig. 5-39—Used ahead of a small receiver that tunes to 1700 kc., this converter will add tuning ease and selectivity on the 80- and 40-meter bands. The input capacitor is the dual section unit at the upper left-hand corner. The crystal and the tuning slug for L₆ are near the center at the foreground edge.

appreciably if the power can be "borrowed" from another source.

The converter uses the tuning principle employed in the two-band superheterodynes described earlier in this chapter. A double-tuned input circuit with large capacitors covers both 80 and 40 meters without switching, and the oscillator tunes from 5.2 to 5.7 Mc. Consequently with an i.f. of 1700 kc. the tuning range of the converter is 3.5 to 4.0 Mc. and 6.9 to 7.4 Mc. Which band is being heard will depend upon the setting of the input circuit tuning (C1 in Fig. 5-40). The converter output is amplified in the receiver, which must of course be set to 1700 kc. To add selectivity, a 1700-kc. quartz crystal is used in series with the output connection. A small power supply is shown with the converter, and some expense can be eliminated if 300 volts d.c. at 15 ma, and 6.3 volts a.c. at 0.45 ampere is available from an existing supply.

Construction

The unit is built on a $7 \times 11 \times 2$ -inch aluminum chassis. The front panel is made from a 6×7 -inch piece of aluminum. The power supply is mounted to the rear of the chassis and the converter components are in the center and front. The layout shown in the bottom view should be followed, at least for the placement of L_1 , L_2 L_3 and L_4 .

The input and oscillator coils are made from a single length of B & W Miniductor stock, No. 3016. Count off 31 turns of the coil stock and

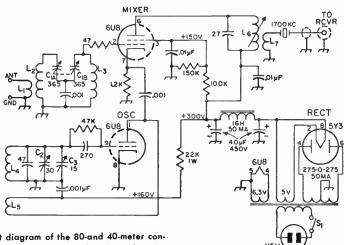


Fig. 5-40—Circuit diagram of the 80-and 40-meter converter. All capacitances given in $\mu\mu f$, unless otherwise noted.

 C_1 —365- $\mu\mu$ f. dual variable, t.r.f. type.

 C_2 —3-30- $\mu\mu$ f. trimmer.

C₈—15-μμf. variable (Bud 1850, Cardwell ZR-15AS, Millen 20015).

 $L_{1s},\ L_{2s},\ L_{4s},\ L_{5}-B$ & W No. 3016 Miniductor, 1-inch diameter, 32 turns per inch, No. 22 wire, cut as below.

 L_1 —8 turns separated from L_2 by one turn (see text). L_2 , L_3 —19 turns.

L₄-21 turns separated from L₅ by one turn.

L₅-8 turns.

 $L_s{=}-105{-}200{\cdot}\mu h.$ slug-tuned coil (North Hills Electric 120H).

L7-See text.

Crystal-1700 kc. (E. B. Lewis Co. Type EL-3).


bend the 32nd turn in toward the axis of the coil. Cut the wire at this point and then unwind the 32nd turn from the support bars. Using a hacksaw blade, carefully cut the polystyrene support bars and separate the 31-turn coil from the original stock. Next, count off 9 turns from the 31-turn coil and cut the wire at the 9th turn. At the cut unwind a half turn from each coil, and also unwind a half turn at the outside ends. This will leave two coils on the same support bars, with half-turn leads at their ends. One coil has 21 turns and the other has 8 turns, and they are separated by the space of one turn. These coils are L_4 and L_5 .

The input coils L_1 and L_2 are made up in the same manner. Standard bakelite tie points are used to mount the coils. Two 4-terminal tie points are needed for L_1L_2 and L_4L_5 , and a one-terminal unit is required for L_5 . The plate load inductance L_6 is a 105-200 μ h. variable-inductance coil (North Hills 120H). The coupling coil L_7 is 45 turns of No. 32 enam. scramble-wound adjacent to L_6 . If the constructor should have difficulty in obtaining No. 32 wire, any size small enough to allow 45 turns on the coil form can be substituted.

The input capacitor, C_1 , is a 2-gang t.r.f. variable, 365 $\mu\mu$ f. per section. As both the stators and rotor must be insulated from the chassis, extruded fiber washers should be used with the screws that hold the unit to the chassis. The panel shaft hole should be made large enough to clear the rotor shaft.

A National type O dial assembly is used to tune C_3 . One word of advice when drilling the holes for the dial assembly: the template furnished with the unit is in error on the 2-inch dimension (it is slightly short) so use a ruler to measure the hole spacing.

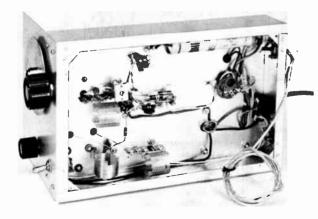It is important that the output lead from the crystal socket be run in shielded wire. A phono jack is mounted on the back of the chassis, and a piece of shielded lead connects from the jack to the crystal socket terminal. The leads from the stators of C_1 and C_2 are insulated from the chassis by means of rubber grommets.



Testing and Adjustment

A length of shielded wire is used to connect the converter to the receiver: the inner conductor of the wire is connected to one antenna terminal; the shield is connected to the other terminal and grounded to the receiver chassis. The use of shielded wire helps to prevent pickup of unwanted 1700-kc. signals. Turn on the converter and receiver and allow them to warm up. Tune the receiver to the 5.2-Mc. region and listen for the oscillator of the converter. The b.f.o. in the receiver should be turned on. Tune around until the oscillator is heard. Once you spot it, tune C₃ to maximum capacitance and the receiver to as close to 5.2 Mc. as you can. Adjust the oscillator trimmer capacitor, C2, until you hear the oscillator signal. Put your receiving antenna on the converter, set the receiver to 1700 kc., and tune the input capacitor, C1, to near maximum capacitance. At one point you'll hear the background noise come up. This is the 80-meter tuning. The point near minimum capacitance - where the noise is loudest - is the 40-meter tuning.

With the input tuning set to 80 meters, turn on your transmitter and tune in the signal. By spotting your crystal-controlled frequency you'll have one sure calibration point for the dial. By listening in the evening when the band is crowded you should be able to find the band edges.

You'll find by experimenting that there is one point at or near 1700 kc. on your receiver where the background noise is the loudest. Set the receiver to this point and adjust the slug on L_6 for maximum noise or signal. When you have the receiver tuned exactly to the frequency of the crystal in the converter, you'll find that you have quite a bit of selectivity. Tune in a c.w. signal and tune slowly through zero beat. You should notice that on one side of zero beat the signal is strong, and on the other side you won't hear the signal or it will be very weak (if it isn't, off-set the b.f.o. a bit). This is single-signal c.w. reception.

When listening to phone signals, it may be found that the use of the quartz crystal destroys some of the naturalness of the voice signal. If

this is the case, the crystal should be unplugged and replaced by a 10- or $20-\mu\mu$ f. capacitor.

Fig. 5-41—Bottom view of the converter showing placement of parts. The coil at the lower left is L_3 , and the input coil, L_1L_2 , is just to the right of L_3 . The oscillator coil L_4L_5 , is at the left near the center. The output coil, L_6 , is near the top center.

A CRYSTAL-CONTROLLED CONVERTER FOR 20, 15 AND 10 METERS

The cure for most of the high-frequency ills of many receivers is the installation of a good crystal-controlled converter between the antenna and the receiver. The converter shown in Figs. 5-42 and 5-44 is intended to be used ahead of a receiver that tunes from 3.5 to 4.0 Mc., although its output range can be modified merely by changing the crystal frequencies. Used with a receiver tuning the 80-meter band only, the 14- and 21-Mc. bands are covered with something left over, but only 500-kc. segments of the 28-Mc. band can be covered without switching crystals. If complete coverage without switching is desired, a wider-range receiver can be used; e.g., the BC-454 surplus receiver, which tunes 3 to 6 Mc.

Referring to Fig. 5-43, the converter consists of an r.f. amplifier, mixer and oscillator stages, and an inexpensive power supply. A cathodebias control (R_1) on the r.f. stage determines the stage gain and prevents overloading on strong signals. The signal circuits, tuned by C_1 and C_2 , cover 14 to 30 Mc. and are peaked by the operator for the band in use. The selector switch, S_2 , is used to switch to the required crystal and output circuit; on 10 meters the same output circuit is used for several crystals. No tuned output from the mixer is included; the tuned circuit (s) of the receiver following the converter being all that is necessary.

The converter is built on a $4 \times 7 \times 2$ -inch chassis and is housed in a $5 \times 9 \times 6$ grey hammertone aluminum utility cabinet. Although the construction is straightforward and should present no particular problems, there are places where caution should be exercised. For example, r.f. leads and bypassing at the 6BZ6 socket should be made as short and direct as possible, to minimize the chance for oscillation of this high-gain stage. Grounding should be done with soldering lugs to the screws that hold the socket to the chassis. Generous use of tie points is advisable, so that both ends of resistors and capacitors will be supported.

Coils L_1 and L_2 are made from a single piece of B&W 3011 Miniductor stock. Start with a 20-turn length of stock. With a pin or knife push in the 6th turn from one end and cut it. Push the cut ends back out and unwind each approximately a half turn to the support bar. Unwind the ends to give the specified turns in each coil (see Fig. 5-43). The coils are supported by standard ticpoint strips; on L_1 the outside ends go to antenna (small coil) and grid, and on L_2 the outside ends go to plate (small coil) and grid. When


Fig. 5-42—A 3-band crystal-controlled converter, to be used ahead of a receiver tuning the 80-meter band. The converter is shown out of its cabinet. Mixer tuning control at right, gain control and line switch at left. The tube in the center is the 6U8A mixer-oscillator.

the coils are mounted, they should be positioned at least $\frac{1}{2}$ inch away from the chassis or panel.

Ceramic or mica capacitors can be used across L_3 , L_4 and L_6 . The 3- $\mu\mu$ f coupling capacitor between pins 1 and 2 of the 6U8A can be a small ceramic or it can be made from two 1-inch lengths of plastic-covered wire twisted together.

When the wiring has been completed and checked, plug the tubes into their sockets and turn the adjustment screws of L3, L4 and L5 until the screws are out of the coil ends as far as they will go. Use a length of coaxial line and suitable plugs to connect the output of the converter to the antenna terminals of the receiver, and connect an antenna to the antenna terminals of the converter. Plug in the line plug (fused with $\frac{1}{2}$ -ampere fuses) and turn on S_1 . The tube heaters should light up. With S₂ switched to the 20-meter position, screw in the slug of L_8 as the knob of C2 is rocked back and forth about the maximum-capacitance end of its range. When an increase in noise is heard as C2 is rocked through a particular point, hold up on the adjustment of L_3 and turn the knob of C_1 . Peak C_1 on noise and tune around with the receiver for any signals. If for any reason the crystal or oscillator is suspected of not operating properly, it can be checked by connecting a voltmeter across the 1000-ohm resistor running to the arm of S_{2A} (+ side of meter to power-supply side). If the oscillator is functioning properly, when Y_1 is removed from its socket the voltage measured across the 1000-ohm resistor should increase.

The slugs in L_4 and L_5 are adjusted in a similar manner, with S_2 in the proper position. After one slug has been adjusted, it may be necessary to touch up the others slightly. A compromise setting will be found for L_5 that allows good operation of either Y_3 or Y_4 .

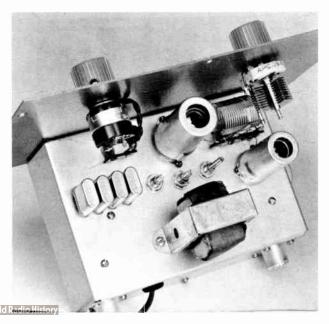

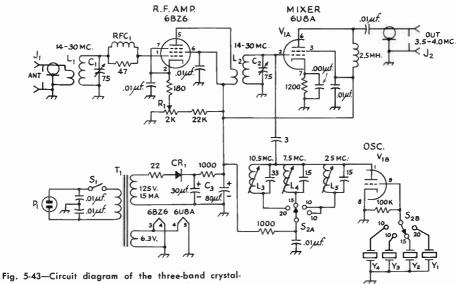


Fig. 5-43—Circuit diagram of the three-band crystalcontrolled converter. Unless indicated otherwise, capacitances are in $\mu\mu f$., resistors are $\frac{1}{2}$ watt.

C₁, C₂—75-μμf. variable (Hammarlund APC-75-B).
C₃—30-80-μf. dual electrolytic, 150-volt, common negative.

CR₁—50-ma. 130-v. selenium rectifier (International Rectifier TO65).

J₁, J₂—Chassis-mounting coaxial connector (SO-239).
 L₁, L₂—12 turns No. 20, 16 t.p.i., ¾-inch diam. (See text). Primary on L₁ is 3 turns, 4 turns on L₂. Separation of 1/16 inch between primary and secondary.

 L_3 -3.1- to 6.8- μ h., slug-tuned (Miller 4405). L_4 , L_5 -1.5- to 3.2- μ h., slug-tuned (Miller 4404). P₁—Fused plug (El Menco).

 R_1 —2000-ohm 1-watt potentiometer, with switch (CTS-IRC Q11-110 with IRC 76-1 switch).

S₁—Part of R₁, see above.

 S_2 —2-pole 5-position (4 used) rotary switch (Centralab PA-2003).

RFC₁—7 turns No. 20 wound on 47-ohm ½-watt resistor. T₁—125 v. at 15 ma., 6.3 v. at 0.6 amp. (Allied Radio's Knight 61 G 410 or equiv.)

Y₁—10.5-Mc. crystal (International Crystal Co., Type FA-9).


Y2-17.5-Mc. crystal.


Y₃—24.5-Mc. crystal.

Y₄-25.0-Mc. crystal.

Fairly sharp tuning of C_1 and C_2 is normal, and it may be found that any given settings will suffice for a receiver tuning range of only a portion of an amateur band. If the gain control cannot be advanced to the maximum-gain position (arm at chassis end of R_1) without oscillation, take a second look at the wiring of the 6BZ6 socket. The grid and plate leads should not be able to "see" each other, and the center post of the socket should be grounded to the chassis by a short length of wire.

With this converter, the 80-meter receiver is serving as a tunable i.f. system. The signal frequency is the indicated receiver frequency plus the crystal frequency; e.g., on 20 meters a 14.1-Mc. signal will appear at 3.6 Mc. (3.6 + 10.5 = 14.1) on the receiver. The over-all system hecomes a double-conversion superheterodyne with a crystal-controlled "front end," a popular arrangement found in many high-priced receivers.

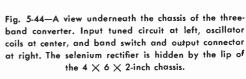

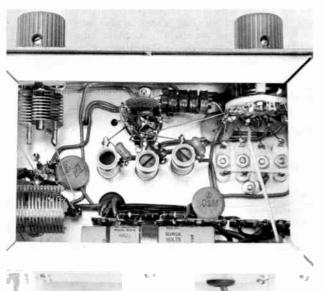

THE "SELECTOJECT"

The Selectoject is a receiver adjunct that can be used as a sharp amplifier or as a single-frequency rejection filter. The frequency of operation may be set to any point in the audio range by turning a single knob. The degree of selectivity (or depth of the null) is continuously adjustable and is independent of tuning. In phone work, the rejection notch can be used to reduce or eliminate a heterodyne. In c.w. reception, interfering signals may be rejected or, alternatively, the desired signal may be picked out and amplified. The Selectoject may also be operated as a low-distortion variable-frequency audio oscillator suitable for amplifier frequency-response measurements, modulation tests, and the like, by advancing the "selectivity" control far enough in the selectiveamplifier condition. The Selectoject is connected in a receiver between the detector and the first audio stage. Its power requirements are 4 ma. at 150 volts and 6.3 volts at 0.6 ampere. For proper operation, the 150 volts should be obtained from across a VR-150 or from a supply with an output capacity of at least 20 μf.

The wiring diagram of the Selectoject is shown in Fig. 5-45. Resistors R_2 and R_3 , and R_4 and R_6 , can be within 10 per cent of the nominal value but

they should be as close to each other as possible. An ohmmeter is quite satisfactory for doing the matching. One-watt resistors are used because the larger ratings are usually more stable over a long period of time.

If the station receiver has an "accessory socket" on it, the cable of the Selectoject can be made up to match the connections to the socket, and the numbers will not necessarily match those shown in Fig. 5-45. The lead between the second detector and the receiver gain control should be broken and run in shielded leads to the two pins of the socket corresponding to those on the plug marked "A.F. Input" and "A.F. Output." If the receiver has a VR-150 included in it for voltage stabilization there will be no problem in getting the plate voltage — otherwise a suitable voltage divider should be incorporated in the receiver, with a 20- to 40-µf. electrolytic capacitor connected from the + 150-volt tap to ground.

In operation, overload of the receiver or the Selectoject should be avoided, or all of the possible selectivity may not be realized.

The Selectoject is useful as a means for obtaining much of the performance for a "Q Mulitplier" from a receiver lacking one.

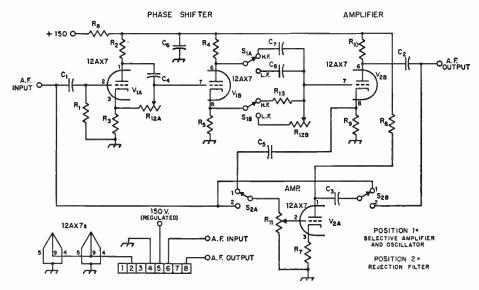


Fig. 5-45—Complete schematic of Selectoject using 12AX7 tubes.

 C_1 —0.01- μ f. mica, 400 volts.

C₂, C₃—0.1-μf. paper, 200 volts.

 C_4 , C_8 --0.002- μf . paper, 400 volts.

C₅-0.05-µf. paper, 400 volts.

C₆-16-µf. 150-volt electrolytic.

 C_7 —0.0002- μ f. mica.

R₁-1 megohm, ½ watt.

R₂, R₃—1000 ohms, 1 watt, matched as closely as possible (see text).

R₄, R₅—2000 ohms, 1 watt, matched as closely as possible (see text). R₆-20,000 ohms, ½ watt.

R₇-2000 ohms, ½ watt.

R₆-10,000 ohms, 1 watt.

R₀-6000 chms, ½ watt.

R₁₀--20,000 ohms, ½ watt.

R₁₁-0.5-megohm ½-watt potentiometer (selectivity).

R₁₂—Ganged 5-megohm potentiometers (tuning control) (IRC PQ11-141 with IRC M11-141.)

R₁₃-0.12 megohm, ½ watt.

S₁, S₈-D.p.d.t. toggle (can be ganged).

ANTENNA COUPLER FOR RECEIVING

In many instances reception can be improved by the addition of an antenna coupler between the antenna feedline and the receiver, and in all cases the r.f. image rejection will be increased. The unit shown on this page consists of one series-tuned circuit and one parallel-tuned circuit; usually its best performance is obtained with the parallel-tuned circuit connected to the receiver input, as indicated in Fig. 5-46. However, the coupler should also be tried with the connections reversed, to see which gives the better results. The desired connection is the one that gives the sharper peak or louder signals when the circuits are resonated.

The coupler is built on one section of a $5 \times 4 \times 3$ -inch Minibox (Bud CU-2105A). Tuning capacitors C_1 and C_2 are mounted directly on the Minibox face, since there is no need to insulate the rotors. The arrangement of the components can be seen in Fig. 5-47.

The coils L_1 and L_2 are made from a single length of B & W 3011 Miniductor. The wire is snipped at the center of the coil and unwound in both directions until there are three empty spaces on three support bars and two empty spaces on the bar from which the snipped ends project. These inner ends run to the connectors J_1 and J_2 . (Fig. 5-46). Unwind turns at the ends of the coils until each coil has a total of 22 turns. When soldering the leads to the 3rd, 6th, 8th and 12th turns from the inside ends of the coils, protect the adjacent turns from solder and flux by placing strips of aluminum cooking foil between the turns. An iron with a sharp point will be required for the soldering.

The "panel" side of the box can be finished off with decals indicating the knob functions and switch positions.

The antenna coupler should be mounted within a few feet of the receiver, to minimize the length of RG-59/U between coupler and receiver. In crowded quarters, the use of M-359A right-angle

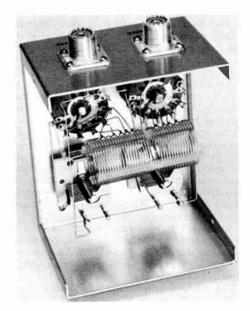


Fig. 5-47—Receiver antenna coupler, with cover removed from case. Unit tunes 6 to 30 Mc. The coil is supported by the leads to the capacitors and switches.

adapters (Amphenol 83-58) and J_1 and J_2 will make it possible to bring out the cables in better lines.

Normally the coupler will be adjusted for optimum coupling or maximum image rejection, but by detuning the coupler it can be used as an auxiliary gain control to reduce the overloading effects of strong local signals. The coupler circuits do not resonate below 6 Mc., but a coupler of this type is seldom if ever used in the 80-meter band; its major usefulness will be found at the higher frequencies.

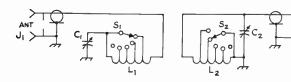


Fig. 5-46—Circuit diagram of the receiver antenna coupler.

 C_1 , C_2 —100- $\mu\mu f$. midget variable (Hammarlund HF-100). J_1 , J_2 —Coaxial cable connector, SO-239.

L₁, L₂—22 turns No. 20, ¾-inch diameter, 16 t.p.i. Tapped 3, 6, 8 and 12 turns from inside end. See text on spacing and tapping.
S1, S2—Single-pole 11-position switch (5 used) rotary switch (Centralab PA-1000).

Preselector 131

A REGENERATIVE PRESELECTOR FOR 7 TO 30 Mc.

The performance of many receivers begins to drop off at 14 Mc. and higher. The signal-tonoise ratio is reduced, and unless double conversion is used in the receiver there is likely to be increased trouble with r.f. images at the higher frequencies. The preselector shown in Figs. 5-48 and 5-49 can be added ahead of any receiver without making any changes within the receiver, and a self-contained power supply eliminates the problem of furnishing heater and plate power. The poorer the receiver is at the higher frequencies, the more it will benefit by the addition of the preselector.

A truly good receiver at 28 Mc. will show little or no improvement when the pre-

selector is added, but a mediocre receiver or one without an r.f. stage will be improved greatly through the use of the preselector.

A 6CG7 dual triode is used in the preselector, one triode as a bandswitched regenerative r.f. stage and the other as a cathode follower. A conventional neutralizing circuit is used in the amplifier; by upsetting this circuit enough the stage can be made to oscillate. Smooth control of regeneration up to this point is obtained by varying one of the capacitances in the neutralizing circuit.

If and when it becomes necessary to reduce gain (to avoid overloading the receiver), the

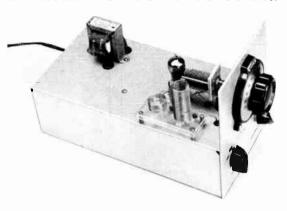


Fig. 5-48—The regenerative preselector covers the range 7 to 30 Mc.; it can be used ahead of any receiver to improve gain, image rejection and, in many cases, sensitivity. A dual triode 6CG7 is used a r.f. amplifier and cathode follower.

regeneration control can be retarded. One position of the bandswitch permits straight-through operation, so the preselector unit can be left connected to the receiver even during low-frequency reception.

The preselector is built on a $5 \times 10 \times 3$ -inch chassis (Bud AC-404). A $5 \times 6\frac{1}{2}$ -inch aluminum panel is held to the chassis by the extension-shaft bushing for the regeneration-control capacitor, C_3 , and the bushing for the rotary switch. The coils, L_1 and L_2 , are supported on a small staging of $1\frac{1}{4} \times 3$ -inch clear plastic. (It can be made from the lid of the box that the Sprague 5GA-S1

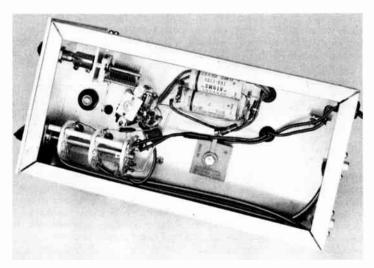


Fig. 5-49—The r.f. components are bunched around the 9-pin miniature tube socket. Power supply components are supported by screws and tie points.

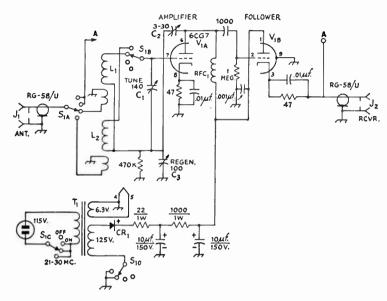


Fig. 5-50—Circuit diagram of the regenerative preselector. Unless otherwise specified, resistors are $\frac{1}{2}$ watt, capacitors are in $\mu\mu$ f., capacitors marked in polarity are electrolytic.

 C_1 —140- $\mu\mu$ f. midget variable (Hammarlund HF-140).

 C_2 —3- to 30- $\mu\mu$ f. mica compression trimmer.

C₃—100-µµf. midget variable (Hammarlund MAPC-100-B).

CR₁—50-ma. selenium rectifier (International Rectifier TO50).

J₁, J₂—Phono jack.

L₁—19 turns, 7-turn primary.

L₂--5 turns, 2-turns primary. Coils are ¾-inch diameter, 16 t.p.i., No. 20 Wire (B & W 3011 Miniductor).

.01-µf. disk ceramic capacitors come in.) All coils can be made from a single length of B&W 3011 Miniductor. They are cemented to the plastic staging with Duco cement.

The rotor of C_1 can be insulated from the chassis by mounting the capacitor bracket on insulating bushings (National XS-6 or Millen 37201); its shaft is extended through the use of an insulated extender shaft (Allied Radio No. 60 H 355). The bandswitch S_1 is made from the specified sections (see Fig. 5-50).

The first section is spaced 3/4 inch from the indexing head, there is 1-inch separation between this and the next section (S_{1B}) , and the next section (S_{1C}, S_{1D}) is spaced 21/2 inches from S_{1B} .

The regeneration control, C_3 , is mounted on a small aluminum bracket. Its shaft does not have to be insulated from the chassis, so either an insulated or a solid shaft connector can be used. The small neutralizing capacitor, C_2 , is supported by soldering one lead of it to a stator bar of C_3 and running a wire from the other lead to pin 6 of the tube socket. The rotor and stator connections from C_1 are brought through the chassis deck through small rubber grommets.

Power supply components, resistors and capacitors are supported by suitable lugs and tie One-turn spacing between coils and primaries. S₁—Three-wafer switch. S_{1A} and S_{1B} are 1-pole 12-position (4 used) miniature ceramic switch sections (Centralab PA-1); S_{1C} and S_{1D} are 2-pole 6-position (4 used) miniature switch (Centralab PA-3). Sections mounted on Centralab PA-301 index assembly.

T₁—125 v. at 15 ma., 6.3 v. at 0.6 amp. (Stancor PS-8415 or Knight 61G410).

RFC1—100-μh. r.f. choke (National R-33).

points. Phono jacks are used for the input and output connectors.

Adjustment

Assuming that the wiring is correct and that the coils have been constructed properly and cover the required ranges, the only preliminary adjustment is the proper setting of C2. Connect an antenna to the input jack and connect the receiver to the output jack through a suitable length of RG-58/U. Turn on the receiver b.f.o. and tune to 28 Mc. with S_1 in the on position. Now turn S₁ to the 21- to 30-Mc, range. Swing the TUNE capacitor, C1, and listen for a loud rough signal which indicates that the preselector is oscillating. If nothing is heard, advance the regeneration control toward the minimum capacitance end and repeat. If no oscillation is heard, it may be necessary to change the setting of C2. Once the oscillating condition has been found, set the regeneration control at minimum capacitance and slowly adjust C2 until the preselector oscillates only when the regeneration control is set at minimum capacitance. You can now swing the receiver to 21 Mc. and peak the preselector tuning capacitor. It will be found that the regeneration capacitance will have to be increased to avoid oscillation.

DCS-500 133

Check the performance on the lower range by tuning in signals at 14 and 7 Mc. and peaking the preselector. It should be possible to set the regeneration control in these two ranges to give both an oscillating and a non-oscillating condition of the preselector.

A little experience will be required before you

can get the best performance out of the preselector. Learn to set the regeneration control so that the preselector is selective, but not so selective that it must be retuned every 10 kc. or so. Changing to another antenna may modify the best regeneration control setting because the loading on the preselector is changed.

DCS-500 DOUBLE-CONVERSION SUPERHETERODYNE

The receiver shown in Fig. 5-51 was designed to meet a need for a better-than-average ham receiver requiring a minimum of mechanical work and using standard and easily obtainable parts. It incorporates such features as a 100-kc. calibrator, provision for reception on all ham bands from 80 through 10 meters, adequate selectivity for today's crowded bands, and stability high enough for copying s.s.b. signals. Dubbed the DCS-500 because of its 500-cycle selectivity in the sharpest i.f. position, it is a double-conversion superheterodyne receiver capable of giving good results on either a.m., c.w. or s.s.b.

The Circuit

Referring to the circuit diagram, Figs. 5-52 and 5-53, a 6BA6 r.f., stage is followed by a 6U8A mixer-oscillator. The 4.5-Mc. mixer output is amplified by a 6BA6 and filtered by a two-stage crystal filter, after which a 6U8A second mixer-oscillator, crystal-controlled, heterodynes the signal to 50 kc.

The combination of i.f. amplifiers may appear rather unusual at first glance, since one might expect that a cascade crystal filter in the highfrequency i.f. would make further selectivity unnecessary. This would be true with highly developed filters, but two filters are needed if the best possible job is to be done on both phone and c.w., and such filters are expensive. With inexpensive surplus crystals such as are used in this receiver it would be difficult, if not impossible, to match the performance of the high-class filters; in addition, special test equipment and extreme care in adjustment would be necessary. The approach used here is to use the surplus crystals without such special adjustment, thereby achieving a good, if not quite optimum, degree of selectivity against strong signals near the desired one, and then to back up the filter by a low-frequency i.f. amplifier that will give the "close-in" straightsided selectivity needed in present-day operation. The over-all result is a high order of protection against strong interfering signals at considerably less cost, for the entire double-i.f. system, than that of two high-performance filters alone. The

Fig. 5-51—The DCS-500 double-conversion superheterodyne. Left bottom, antenna trImmer, 100-kc. calibrator switch; center, left, top to bottom, noise-limiter switch, volume control, sensitivity control; center, right, b.f.o. switch, a.g.c. speed, selectivity; right, headphone jack, b.f.o. pitch control. The dial is a National ICN. Front panel is 8% inches high; the receiver is mounted in a Bud CR-1741 rack cabinet.

choice of 4.5 Mc., approximately, for the first i.f. was based on the availability of surplus crystals around this frequency, with due consideration for minimizing spurious responses. A second i.f. of 50 kc. was chosen because it lent itself nicely to the utilization of low-cost TV horizontal-oscillator coils as i.f. transformers.

The two i.f. amplifiers at 50 kc. contribute the necessary adjacent-channel selectivity. Three degrees of selectivity are available, depending on the degree of capacitive coupling between the two windings of each i.f. transformer. The greater the number of capacitors switched in parallel—that is, the larger the coupling capacitance—the lower the coupling between the windings and thus the greater the selectivity.

A standard diode detector develops the audio output for all reception modes. The output of the detector is simultaneously applied to both the first audio amplifier and the audio a.g.c. circuit. A series-type noise limiter can be used on a.m. to reduce impulse-noise interference, but this type is ineffective on c.w. or s.s.b. because of the large amplitude of the b.f.o. injection voltage.

The b.f.o., a Hartley-type oscillator, can be tuned from 3 kc. above to 3 kc. below its 50-kc. center frequency by the tuning capacitor.

The first audio stage is a normal Class A voltage amplifier with its output either coupled to the grid circuit of the audio output tube or to a phone jack. High-impedance head-phones (20,000 ohns a.c. impedance or higher) are required. Plugging in the phones automatically disconnects the speaker. If low-impedance headphones are used, they can be connected to the speaker terminals. Capacitances shunting the grid resistors restrict the audio response to an upper limit of about 4000 cycles.

The audio output transformer couples to a lowimpedance (3.2-ohm) speaker. The 47-ohm resistor across the secondary protects the transformer in the absence of a speaker load.

The audio output of the detector is also amplified separately in the audio a.g.c. circuit and then



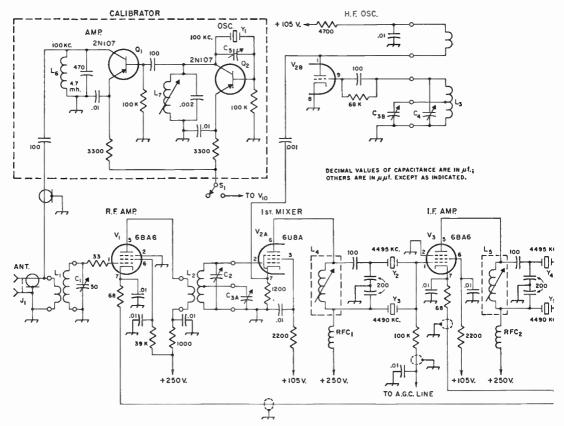


Fig. 5-52—Front-end circuit of the receiver. Unless otherwise specified, resistors are ½ watt; 0.01 and 0.02-μf. capacitors are disk ceramic, 600 volts; 0.5 capacitors are tubular paper or Mylar; capacitors below 0.01 μf. are mica; capacitors marked with polarities are electrolytic.

C₁--50-μμf. variable (Hammarlund HF-50).

C2, C4-See coil table.

 C_3 —2-section variable, 5—28.5 $\mu\mu$ f. per section, double spaced (Hammarlund HFD-30-X).

C5-3-30-µµf. ceramic trimmer.

J₁—Coaxial receptacle, chassis mounting (SO-239).

L1, L2, L3-See coil table.

L₄, L₅—18-36-μh. slug-tuned (North Hills 120E coil mounted in North Hills S-120 shield can).

rectified to develop a negative voltage that can be used for a.g.c. on c.w. and s.s.b. Two different time constants are used in the rectifier filter circuit, for either fast- or slow-decay a.g.c.

The 100-kc. calibrator employs two 2N107 p-n-p transistors, one as the oscillator and the second as a 100-kc. amplifier. Its transistors obtain the necessary operating potential from the cathode resistor of the audio output tube. Output from the 100-kc. unit is capacity-coupled to the antenna winding of the r.f. coil. Calibrating signals at 100-kc. intervals are available on all frequencies covered by the receiver.

The calibrator unit is constructed in a separate Minibox so that it can be plugged into the accessory socket of the receiver or used as an individual unit powered by penlite cells.

The power supply, Fig. 5-54, is a full-wave rec-

L₆-4.7 mh. (Miller 6304).

L7-1-2-mh. slug-tuned (North Hills 120K).

RFC1, RFC2—100-µh. r.f. choke resonant at 4.4 Mc. (Miller 70F104A1).

S₁-Single-pole rotary.

Y₁-100 kc. (James Knights H-93).

Y2, Y4-4495 kc. (surplus).

Ya, Y5-4490 kc. (surplus).

tifier with a choke-input filter. It provides approximately 250 volts d.c. under load. A 0.25- μ f. capacitor is shunted across the 10-henry filter choke to form a parallel-resonant circuit at 120 cycles; this provides an increased impedance to the ripple component and thus reduces hum in the output of the supply.

The power-supply requirements are 250 volts at 110 milliamperes, and 6.3 volts at approximately 5 amperes. Any transformer-choke combination fulfilling the requirements can be used.

Front End

The use of plug-in coils for the front end eliminated the mechanical problems of a bandswitching tuner, and also offered the possibility of realizing higher-Q tuned circuits. Ganged tuning of the r.f. amplifier along with the h.f.

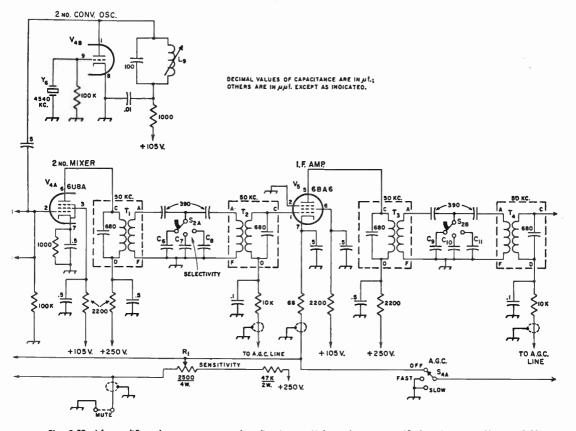


Fig. 5-53—1.f. amplifier, detector, a.g.c. and audio circuits. Unless otherwise specified, resistors are ½ watt; 0.01-and 0.02-μf. capacitors are disk ceramic, 600 volts; 0.5-μf. capacitors are tubular paper or Mylar; capacitors below 0.01 μf. are mica; capacitors marked with polarities are electrolytic.

C₆, C₇, C₈, C₉, C₁₀, C₁₁—0.01 mica (Aerovox CM-30B-103).

C₁₂-9-180-µµf. mica compression trimmer.

 C_{18} —50- $\mu\mu$ f. variable (Hammarlund HF-50).

 C_{14} —0.1- μ f. paper (Sprague 2TM-P1).

J2-Phono jack.

J₈—Closed-circuit phone jack.

L₈-125 mh. (Meissner 19-6848).

L₀-9-18 μh., slug-tuned (North Hills 120D).

M1-0-1 d.c. milliammeter (Triplett 227-PL).

R₁-2500-ohm, 4-watt control, wire-wound.

 R_2 =0.5-megohm control, audio taper with push-pull type switch (S_0) (Mallory No. PP55DT1683).

R₈-1000-ohm, 1-watt control, wire-wound.

RFC_s-10 mh. (National R-50-1).

 S_1 , S_8 —Rotary, 1 section, 1 pole, 2 position.

oscillator and mixer circuits was decided against because of the complexities it would cause in coil construction and the problem of keeping three stages tracking with each other. The r.f. amplifier has to be peaked separately by the antenna trimmer, but separate peaking insures maximum performance at all frequencies.

Construction

The receiver is constructed on a 12 \times 17 \times 2-inch aluminum chassis with an 834×19 -inch aluminum front panel, which permits it to be

S₂—Rotary, 2 section, 1 pole per section, progressively shorting. Switch section Centralab PA-12, index Centralab PA-302.

S₄—Rotary, 1 section, 5 poles per section (4 poles used), 3-position rotary switch (Centralab PA-2015).

 S_{δ} —Rotary, 1 section, 2 poles per section, 2 positions used. (Centralab PA-2003).

T₁-T₅, inc.—50-kc. i.f. transformers made from TV components (Miller 6183); see text.

Te-B.f.o. transformer (Miller 6183); see text.


T₇—Audio interstage transformer, 1:2 ratio (Thordarson 20A16).

T₈—Audio output transformer, 5000 to 4 ohms (Stancor 3856).

Ye-4540 kc. (surplus).

installed in a table-top rack cabinet. The general layout of components can be seen in Figs. 5-55 and 5-57. A good procedure to follow when starting to wire the receiver is first to complete the power supply and heater wiring, and then start wiring from the antenna toward the speaker. This allows proceeding in a logical order so that the work can be picked up readily at any time after an intermission.

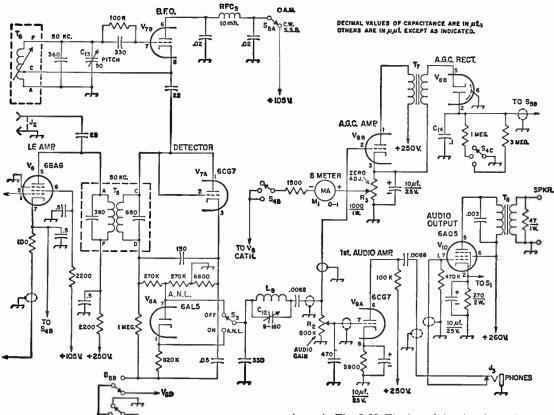In the front end (r.f. amplifier and first mixer), the use of short leads coupled with good quality ceramic tube and coil sockets, is highly



recommended. When mounting the sockets orient them so that the leads to the various points in the circuit will be as short as possible.

A.G.C. LINE


Millen coil shields (80008) are used around the plug-in coils in the front end — i.e., the r.f., mixer and oscillator - and the shield bases are mounted with the same screws that hold the ceramic coil sockets. All plug-in coils are wound with No. 26 enameled wire on Amphenol polystyrene forms, and Hammarlund APC-type airpadder capacitors are mounted in the recesses at the tops of the coil forms. After finishing a coil it is a good idea to fasten the winding and the trimmer capacitor in place with Duco cement. Decal each set of coils for a particular band and mount them on small wooden bases that have holes to take the pins. Then paint or stain each of the coil-set bases. The final result will be a neat and convenient arrangement for holding the coils for each band (Fig. 5-56). Plug-in coil data for each band are given in the coil table.

The tuning capacitor, C_{s} , is mounted on the chassis and reinforced by a bracket to minimize any rocking movement. This bracket is triangular in shape with a right-angle flange at the bottom. It is drilled to take the front bearing sleeve of the tuning capacitor and held firmly to it by the capacitor mounting nut and a lock washer, as

shown in Fig. 5-55. Flexing of the chassis can be minimized by the use of lengths of angle stock bolted to the chassis at strategic points throughout the receiver. Exact alignment of the tuning capacitor with the dial shaft is not always possible, so a flexible coupling (Millen 39016) is used.

When wiring the crystal filter keep leads as short and direct as possible, as this will minimize stray coupling between the input and output ends, which would deteriorate the performance of the crystal-filter circuits.

The 50-kc. i.f. circuits used Miller 6183 TV horizontal-oscillator replacement coils as i.f. transformers. These coils must be altered before they can be used. As they are supplied, the terminal lugs are brought out at the top of the can; these lugs must be reversed before the can is mounted. By applying slight pressure to the phenolic coil form the assembly will slide out of the aluminum shield can and then can be reversed. However, before reassembling the unit a few slight changes must be made. There are actually two separate windings; each one will be tuned and used either as a primary or secondary for the 50-kc. i.f. transformer. The tap on the large winding must be lifted off the soldering lug C, taped, and tucked away, being careful not to break it; this leaves just the lead from the small winding on terminal C. Terminals A and F represent the large winding. The small coil is tuned by connecting a 680-μμf. mica capacitor between terminals C and D; these capacitors should be DCS-500 137

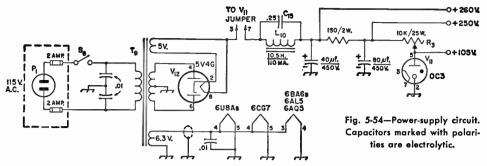

 C_{18} —0.25- μ f. paper, 600 volts. L_{10} —Filter choke, 10.5 henry, 110 ma. (Knight 62 G 139). P_1 —Fuse plug.

S₀—See R₂, Fig. 5-55. T₀—Power transformer, 700 v. c.t., 120 ma.; 5 v., 3 amp.; 6.3 v., 4.7 amp. (Knight 62 G 044).

fastened on the soldering lugs inside the shield can. The can is then slipped back over the coil and capacitor, keeping in mind that the lugs must come out the bottom, and the assembly is ready for mounting on the chassis.

The b.f.o. coil is also a Miller 6183, and the procedure for reversing the assembly before mounting is identical to that followed with the 50-kc. transformers. However, it is not necessary to alter any of the wiring in the b.f.o. transformer, since only the large winding (A - F) and its tap (C) is used.

Point-to-point wiring is recommended, along with generous use of both insulated tie points and ground lugs. Use of shielded wire facilitates routing wires throughout the receiver as the shields can be spot-soldered to ground lugs and to each other in bundles. When wiring, mount components at right angles to the chassis sides wherever possible; this helps give the finished unit a neat appearance. In critical circuits, however, do not sacrifice short and direct leads for the sake of making the unit look pretty.

Placing the receiver in a rack cabinet and

Fig. 5-55—The power supply is built along the back of the chassis; filter capacitor and VR tube are just in back of the filter choke in this view. The crystal calibrator unit at right is cushioned by rubber bumpers mounted on the receiver chassis. C5 is on top of the calibrator unit. Front-end coil shields are at the top right in this photograph, along with the tuning capacitor bracket and flexible coupling. The on-off switch, So, on rear of the audio gain control, is a new push-pull type. Filter crystals are grouped behind the volume control, and the second conversion oscillator crystal is slightly to their left. The 4.5-Mc. i.f. transformers (in the small shield cans) are close to the filter crystals. The b.f.o. coil is at the extreme left in this view; all other large cans contain the 50-kc. i.f. transformers. Connections on the back chassis wall, left to right, are the muting terminals. B-plus output for auxiliary use, speaker terminals, i.f. output (phono jack), and antenna input connector.


marking all controls on the front panel with decals also helps in giving the finished receiver a neat and "commercial" appearance.

The Calibrator

The 100-kc. calibrator is built in a separate $4 \times 4 \times 2$ -inch aluminum box and plugs into the accessory socket at the left rear of the receiver chassis. Fig. 5-58 shows the internal construction. The accessory socket provides the necessary operating voltage for the transistors and offers a convenient means for coupling the 100-kc. harmonics out of the calibrator into the receiver. If the calibrator is to be used as a self-contained unit it must be supplied with 7 to 10 volts.

I.F. Alignment

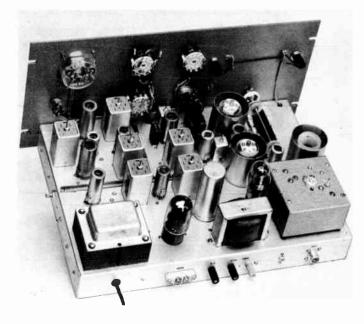Before starting alignment of the receiver, first determine whether the audio stages are functioning correctly. An audio signal should be coupled to the top end of the volume control, and varying the control should change the output level of the audio signal. If an audio signal is not available, the 60-cycle heater voltage will provide a convenient audio signal for checking.



DCS-500 COIL TABLE

All coils wound with No. 26 enameled wire on 1½-inch diameter polystyrene forms. R.f. coil forms are four-prong (Amphenol 24-4P); mixer and oscillator coils are five-prong (Amphenol 24-5P). C₂ and C₄ are Hammarlund APC-50 except on 3.5 Mc., which takes APC-75. Taps are counted from ground end. Primaries and ticklers are close-wound in the same direction as the main coil at bottom of coil form; grid and plate (or antenna) connections at outside ends.

y got and position of the outside cites.		terma, competitions at outside ends.
Band	Secondary	Primary or Tickler
3.5 Mc.	L ₁ , 45¼ turns close-wound. L ₂ , 36¾ turns close-wound, tapped at 26¾ turns. L ₃ , 28¾ turns close-wound, tapped at 19 turns.	1034 turns, 36-inch spacing from secondary. 1134 turns, 34-inch spacing from secondary. 734 turns, 34-inch spacing from secondary.
7 Mc.	Li, 26¼ turns, close-wound. L2, 18¾ turns spaced to 1 inch. Tapped at 9¾ turns. L3, 17¾ turns spaced to ½ inch. Tapped at 4¾ turns.	734 turns, ¼-inch spacing from secondary.
14 Mc.	L ₁ , 13½ turns spaced to ½ inch. L ₂ , 10¾ turns spaced to 1 inch. Tapped at 3 turns. L ₅ , 5¾ turns spaced to ½ inch. Tapped at 1½ turns.	6¼ turns, 5½ inch spacing from secondary. 5¾ turns, 5½ inch spacing from secondary. 3¾ turns, 5½ inch spacing from secondary.
21 Mc.	L_1 , 9½ turns spaced to ½ inch. L_2 , 7¾ turns spaced to $1\frac{1}{2}$ inches. Tapped at 2 turns. L_3 , 6¾ turns spaced to $\frac{15}{16}$ inch. Tapped at 2 turns.	634 turns, 5/16-inch spacing from secondary. 534 turns, 5/6-inch spacing from secondary. 334 turns, 3/6-inch spacing from secondary.
28 Me.	L1, 614 turns spaced to 7/16-inch. L2, 534 turns spaced to 114 inches. Tapped at 2 turns. L3, 434 turns spaced to 34 inch. Tapped at 11/2 turns.	5¼ turns, ¼-inch spacing from secondary. 4¾ turns, ¼-inch spacing from secondary. 2¾ turns, ¼-inch spacing from secondary.

Fig. 5-56—Each set of coils is provided with a wooden base for storage. C₂ and C₄ are mounted in the recesses at the tops of the oscillator and mixer coil forms.


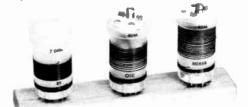


Fig. 5-57—The potentiometer for S-meter adjustment and the audio output transformer are on the right chassis wall in this view. The 50-kc. i.f. trap is located just above the power transformer in the lower right-hand corner. The antenna trimmer is located at extreme life center. The crystal filter sockets are at top center, and to their left on the front wall is the calibrator switch S₁. To the right of the calibrator switch is the sensitivity control, followed to the right by the selectivity switch S₂ and the b.f.o. pitch-control capacitor. The octal accessory socket for the calibrator is at the lower left. As shown, shielded wire spot-soldered together in bundles can be routed conveniently to various points in the receiver. Ceramic sockets are used throughout the front end (center left). Mounting components parallel with the chassis sides helps give the finished unit a neat appearance.

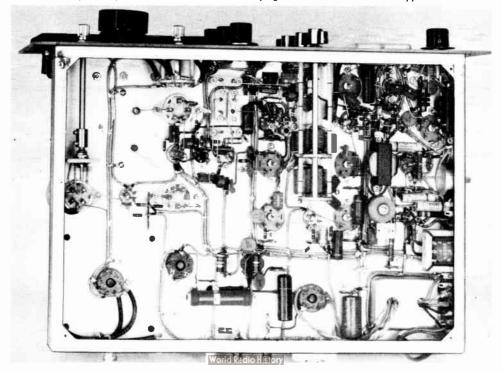


There are various ways to approach the alignment problem. A 50-kc. signal generator can be used; however, these are hard to come by. Some of the better audio oscillators go as high as 50 kc. and can be used for alignment purposes. A second, and possibly superior, method is to use any of the numerous signal generators which will deliver 4.5-Mc. output; fed into the first i.f. amplifier grid, the 4.5-Mc. signal will beat against the second conversion oscillator to produce a 50-kc. i.f. signal which then can be used for alignment. This method also insures that the first i.f. signal will fall within the crystal filter bandpass in case the crystal frequencies are not exact. When aligning, connect a d.c. voltmeter (preferably a v.t.v.m.) across the detector load resistor (point D of T_6 and chassis), set S_2 for high selectivity, (all capacitors in), turn the i.f. gain control about three-quarters open, and tune both the plate circuit of the second conversion oscillator and the 50-kc, i.f. transformers for maximum output, as indicated on the meter. The output of the signal generator should not be modulated, and at the start will most likely be "wide open." However, as alignment progresses the output of the generator will have to be progressively decreased. When aligning the i.f. transformers there should be a definite peak in output as each circuit is brought through resonance. If a particular coil does not peak, that coil and its associated circuits should be checked. After peaking one winding of a transformer, recheck the other; it may need touching up. After alignment of all the 50-kc. coils is completed, go back and "rock" each coil slug to be sure it is peaked for maximum output. This completes the 50-kc. alignment.

Leave the signal generator on, set the b.f.o. pitch control at half capacitance, turn the b.f.o. on, and adjust its coil slug for zero beat with the 50-kc. i.f. signal. Varying the pitch control over its range should produce a tone with a maximum frequency of 3 kc. either side of zero beat.

Next, the 50-kc. trap on the output of the detector should be adjusted. Connect the vertical input terminals of an oscilloscope between the plate of the first audio amplifier and chassis, turn on the b.f.o., and adjust C_{12} for minimum 50-kc. signal on the scope. This trap, made up of C_{12} and L_{8} , attenuates any 50-kc. feed-through.

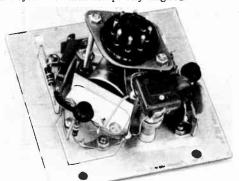The first-i.f. coils at 4.5-Mc. should next be adjusted. Couple the signal generator to the grid of the first mixer and peak L_4 and L_5 for maximum deflection of the v.t.v.m. at the detector. The i.f. system is then completely aligned.



Front-End Alignment

To adjust the front end, plug in a set of coils and check the oscillator frequency range either with a calibrated g.d.o. or on a calibrated general-coverage receiver, the latter being preferable. Keep in mind that the oscillator works 4.5 Mc. above the signal on 80, 40 and 20 meters, and 4.5 Mc. below the signal frequency on the 15- and 10-meter bands. This means that on 15 and 10 meters the oscillator trimmer capacitor, C4, must be at the larger-capacitance setting of the two that bring in signals. After establishing the correct frequency range of the oscillator, inject a signal at the low end of the band into the antenna terminals and peak the mixer capacitor, C_2 , and the antenna trimmer, C_1 , for maximum signal. Then move the test signal to the high end of the band and recheck the mixer trimmer capacitor (the antenna trimmer also will have to be repeaked) for correct tracking. If C2 has to be readjusted, spread the mixer coil turns apart or compress them together until the signal strength is uniform at both ends of the band, without readjustment of C_2 . If the mixer trimmer capacitance had to be increased at the high-frequency end of the band to maintain tracking, the coil tap is too far up the coil and the turns below the tap must be spread apart or the tap itself must be moved down. If the trimmer capacitance has to be decreased the tap is too low. Coil specifications might possibly have to be altered slightly from those given in the table, particularly on the higher frequencies, because of variations in strays from one receiver to another.

General

Adjustment of the calibrator is relatively straightforward, and should present no problems. Turn on the calibrator and you should hear the 100-kc. harmonics on whatever band you happen to be using. Once it is determined that the unit is working correctly, the only adjustment necessary is to set the frequency of the calibrator exactly. The usual reference is WWV or any broadcast station that is on a frequency which is a wholenumber multiple of 100 kc. The frequency tolerance for standard broadcast stations is 20 cycles, thus b.c. stations represent a source for accurate frequency determination.

Using a general-coverage or b.c. receiver, tune in either WWV or a known broadcast station and adjust the calibrator trimmer C_{δ} for zero beat. The calibrator will then provide accurate 100-kc.

Fig. 5-58—Inside view of the calibrator unit. The 100-kc. oscillator coil, L_{16} , is at the right, the oscillator transistor, Q_2 , is in the foreground mounted to the crystal socket, and the amplifier transistor, Q_1 , is mounted at the right on a terminal strip. The 100-kc. crystal is mounted horizontally between the plate and the octal plug. The plug can be mounted on 2-inch screws as shown in the photograph, or on the bottom plate of the Minibox, with flexible leads to the circuit. If the calibrator is to be used as a self-contoined unit (see text) the octal plug is not necessary.

140

signals that can be used for frequency determination and band-edge marking.

The first intermediate frequency can be altered slightly to facilitate the use of particular sets of crystals available. However, if the deviation is more than 20 kc. or so, slight changes may be needed in the h.f. oscillator coil specifications to maintain the proper bandspread.

If the receiver is to be worked in a rack cabinet as shown in Fig. 5-51, or if a cover plate is attached to the bottom of the receiver chassis, minor alignment touch-up may be necessary.

Spraying the receiver chassis with a light coat of clear plastic lacquer before mounting any of

HIGH-FREQUENCY RECEIVERS

the components will prevent fingerprints and oxidation of the chassis.

The audio output stage has adequate power to drive a 5- or 6-inch speaker, which may be mounted in a small open-back metal utility box.

The i.f. output jack at the rear provides a convenient way of attaching accessory devices such as an oscilloscope for modulation checking.

A side-by-side comparison of the finished receiver with some of the better-quality commercial units will show that this receiver can hold its own in sensitivity, selectivity and stability. Needless to say, the more care taken in construction, wiring and alignment the better the results.

A TRANSISTORIZED Q MULTIPLIER

A "Q multiplier" is an electronic device that boosts the Q of a tuned circuit many times beyond its normal value. In this condition the single tuned circuit has much greater selectivity than normal, and it can be utilized to reject or amplify a narrow band of frequencies. There are vacuumtube versions of the Q-multiplier circuit, but the transistorized Q multiplier to be described has the advantage that it eliminates a power-supply problem and is very compact.

Circuit and Theory

Parallel-tuned circuits have been used for years as "suck-out" trap circuits. Properly coupling a parallel-tuned circuit loosely to a vacuum-tube amplifier stage, it will be found that the amplifier stage has no gain at the frequency to which the trap circuit is tuned. The additional tuned circuit puts a "notch" in the response of the amplifier. The principle is used in TV and other amplifiers to minimize response to a narrow band of frequencies. Increasing the Q of the trap circuit reduces the width of the rejection notch.

The transistorized Q multiplier makes use of the above effect for its operation. A tuned circuit is made regenerative to increase its Q and is coupled into the i.f. stage of a receiver. By changing the frequency of the regenerative circuit, the sharp notch can be moved about across the passband of the receiver. The width of the notch is changed by controlling the amount of regeneration.

Fig. 5-59—Circuit diagram of the 455-kc. transistorized Q multiplier. Unless atherwise indicated, capacitances are in μμf., resistances are in ahms, resistors are ½ watt. MIXER W, C.

C₁—15-μμf. variable capacitar (Hammarlund HF-15).
L₁—1000–2000-μh. slug-tuned cail (Narth Hills 120-K.
North Hills Electric Ca., Mineala, N. Y.),
L₂—500–1000-μh. slug-tuned cail (Narth Hills 120-J).
Q₁—CK768 PNP junction transistar.
S₁—Part of R₁.
W₁—Three-faat length of RG-58/U cable.


Although it seems paradoxical, the transistorized Q multiplier with no change in circuitry will also permit "peaking" an incoming signal the way a vacuum-tube Q multiplier does. The mode of operation is selected by adjustment of the regeneration control, and this then usually requires a slight readjustment of the frequency control. The peaking effect is not quite as pronounced as the notch, but it is still adequate to give fairly good single-signal c.w. reception with a receiver of otherwise inadequate selectivity.

The regenerative circuit builds up the signal and feeds it back to the amplifier at a higher level and in the proper phase to add to the original signal. The notch effect described earlier works in a similar manner except that the tuning of the regenerative circuit is such that it feeds back the signal out of phase.

The schematic diagram of the Q multiplier is shown in Fig. 5-59. The inductor L_1 furnishes coupling from the receiver to the Q multiplier, and C_4 is required to prevent short-circuiting the receiver's plate supply. The multiplier proper consists of the tunable circuit $C_1C_3L_2$ connected to a transistor in the collector-tuned commonbase oscillator circuit using capacitive feedback via C_2 . Regeneration is controlled by varying the d.c. operating voltage through dropping resistor R_1 .

Layout

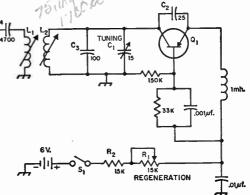The unit and power supply are built in a small



Q Multiplier 141

aluminum "Minibox" measuring $5 \times 2\frac{1}{4} \times 2\frac{1}{4}$ inches (Bud CU-3004) and the operating controls are mounted on a lucite or aluminum subpanel. All parts of the unit are built on one half of the box. This feature not only simplifies construction but makes a battery change a simple job, even if this is required only a couple of times a year.

All major components, such as the two slugtuned coils, tie point, battery holder, regeneration and tuning controls, are mounted directly on the box and subpanel. The remaining resistors, capacitors and the single transistor are supported by their connections to the above parts.

The two slug-tuned coils, L_1 and L_2 , are centered on the box and spaced one inch apart on centers. Operating controls C_1 and R_1 are placed 1½ inches from the ends of the subpanel and centered. The tie point mounts directly behind tuning control C_1 .

Power for the unit is supplied by four penlight cells (type 912) which are mounted in the battery holder (Lafayette Radio Co. Stock No. MS-170) directly behind regeneration control R_1 . Total drain on the battery never exceeds 0.2 ma.

Connection to the receiver is made with a threefoot length of RG-58/U cable brought through the rear wall of the Minibox. A rubber grommet should be placed in the hole to prevent chafing of the cable insulation.

When soldering the transistor in place, be sure to take the usual precautions against heat damage.

Alignment

After completing the wiring (and double-checking it) connect the open end of the three-foot cable to the plate circuit of the receiver mixer tube. This can be done in a permanent fashion by soldering the inner conductor of the cable to the plate pin on the tube socket or any point that is connected directly to this pin, and by soldering the shield to any convenient nearby ground point. If you are one of those people who is afraid to take the bottom plate off his receiver, and you have a receiver with octal tubes, a "chicken connection" can be made by removing the mixer tube and wrapping a short piece of small wire around the plate pin. Reinsert the tube in its socket and solder the center conductor of the coax to the small wire coming from the plate pin. Now ground the coax shield to the receiver chassis. It is important to keep the lead from the tube pin to the coax as short as possible, to prevent stray pickup.

Check the schematic diagram of the receiver for help in locating the above receiver connections.

Turn on the receiver and tune in a signal strong enough to give an S-meter reading. Any decent signal on the broadcast band will do. Next, tune the sing on L_1 until the signal peaks up. You are tuning out the reactance of the connecting cable, and effectively peaking up the i.f. If the receiver has no S meter, use an a.c. voltmeter across the audio output. When this step has been successfully completed the Q multiplier is properly connected to the receiver and when



Fig. 5-60—View of the Q multiplier showing its single connecting cable to the receiver. The box can be placed in any convenient spot on or around the receiver.


switched to "off" (S_1 opened) will not affect normal receiver operation.

The next step is to bring the multiplier into oscillation, and to adjust its frequency to a useful range. Set the tuning control to half capacity and advance the regeneration control to about half open. This latter movement also turns the power on. Tune the receiver to a clear spot and set the receiver b.f.o. to the center of the pass-band. Now adjust the slug of L_2 . The multiplier should be oscillating, and somewhere in the adjustment of L_2 a beat note will be heard from the receiver. This indicates the frequency of oscillation is somewhere on or near the i.f. Swing this into zero beat with the b.f.o.

Final Adjustment

One of the best ways to make final alignment is to simulate an unwanted heterodyne in the receiver and adjust the Q multiplier for maximum

Fig. 5-61—The Q multiplier and its battery supply are combined in one small Minibox. The single transistor is visible near the top right corner.

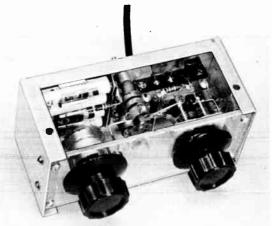

attenuation of the unwanted signal. To do this, tune in a moderately weak signal with the b.f.o. on. A broadcast station received with the antenna disconnected will do. The b.f.o. will beat with the incoming signal, producing an audio tone. Adjust the b.f.o. for a tone of about 1 kc. or so.

Back off on control R_1 until the oscillator becomes regenerative. By alternately adjusting the tuning control, C_1 , and the regeneration control, R_1 , a point can be found where the audio tone disappears, or at least is attenuated. Some slight retouching of L_2 may have to be done in the above alignment, since the movement of any one control tends to "pull" the others. The optimum situation is to have the tuning control C_1 set at

about half capacity when the notch is in the center of the passband.

If you happen to get a super active transistor and the regeneration control does not have the range to stop oscillator action, increase the value of the series resistor R_2 . Conversely, if the unit fails to oscillate, reduce the value of R_2 .

Note that the audio tone can be peaked as well as nulled. If it can not be peaked, a little more practice with the controls should produce this condition. In the unit shown here, the best null was produced with the regeneration control turned only a few degrees. Optimum peak position was obtained with the regeneration control almost at the point of oscillation.

CONELRAD

Effective January 2, 1957, the "Conelrad" rules became part of the amateur regulations. Essentially, compliance with the rules consists of monitoring a broadcast station — standard band, f.m. or TV — either continuously or at intervals not exceeding ten minutes, during periods in which the amateur transmitter is in use. On receipt of a Conelrad Alert all transmitting must cease, except as authorized in 12.193 and 12.194 of the FCC regulations.

The existence of an Alert may be determined as outlined in 12.192(b)(3). Operation during

TO GRID OF 15T 12

ANT 6BE6 5

ANT CIB

CIB

TO GRID OF 15T 12

TO GRI

Fig. 5-62—Converter circuit for monitoring broadcast stations in connection with a communications receiver. Capacitances are in $\mu\mu$ f.

C_{1A}, C_{1B}—Two-gang broadcast capacitor, oscillator section according to i.f. to be used.

L-Loop stick.

T₁—B.c. oscillator transformer (for i.f. to be used).

T₂—1.f. coil and trimmer. This can be taken from an i.f. transformer, or the transformer can be used intact, the output being taken from the secondary.

Note: If only one broadcast station is to be monitored C_{1A} and C_{1B} can be padder-type capacitors (or a combination of padding and fixed capacitance as required) adjusted for the desired station and intermediate frequencies. Other types of tubes may be used. Power can be taken from the receiver.

hours when local broadcast stations are not on the air will require tuning through the standard broadcast band to determine if operation appears to be normal. The presence of any U. S. broadcast stations on frequencies other than 640 and 1240 kc. indicates normal operation.

Perhaps the simplest form of compliance is by means of a simple converter working into the i.f. amplifier of the regular station receiver. A typical circuit is shown in Fig. 5-62. The converter can be built in a small metal case and mounted at a convenient spot on the receiver to that S_1 can be closed at regular intervals for checking the broadcast station. As an alternative, the converter can be mounted out of the way at the rear of the receiver and the switch leads brought out to a convenient spot.


A "FAIL-PROOF" CONELRAD ALARM

The conelrad alarm shown in Fig. 5-63 uses a small b.c. receiver to furnish both audible and visible indications of a Conelrad Alert (the receiver may still be used for normal reception).

With the receiver tuned to a broadcast carrier and the alarm circuit in operation, a green "safe" light indicates that all is well on the broadcast band. When the broadcast carrier goes off, as it will in a Conelrad Radio Alert, the green light goes out, a red "danger" light comes on, a buzzer sounds, and the 115-volt a.c. line to the transmitter is opened up. In other words, the device puts you off the air! The audible and visible warnings also are given in the event of a component failure in either the control receiver or the alarm. Even the disappearance of the 115-volt supply will not go unnoticed, since in that case the green "safe" light will go out, indicating that the alarm is inoperative.

The alarm requires a minimum of 0.7 volts (negative) from the receiver's a.g.c. (automatic gain control) circuit for dependable operation. Receivers having one stage of i.f. amplification will develop at least this much a.g.c. voltage when tuned to a signal of reasonable strength. But watch out for the "superhets" that do not have an i.f. stage; they are of little value as a source of control voltage for the alarm. You

Conelrad 143

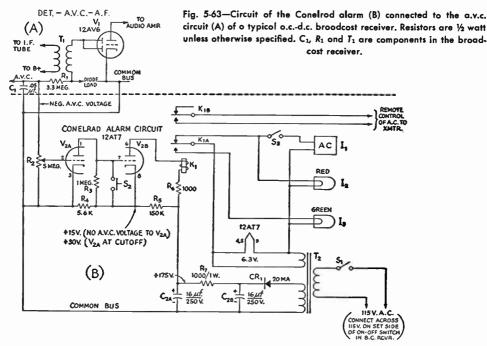

I₁—6-volt a.c. buzzer (Edwords 725).
I₂, I₈—6-volt pilot lomp, No. 47.
K₁—D.p.d.t. sensitive relay, 5000-ohm coil.
R₂—5-megohm potentiometer.

can usually find out if the receiver has an i.f. stage by looking at the tube list pasted on either the chassis or the inside of the cabinet.

The circuit of the alarm is shown in section B, Fig. 5-63. Section A is a typical a.g.c.-detector-first audio stage of an a.c.-d.c. receiver, and shows how the alarm circuit is tied into a receiver.

Although a 12AV6 is shown as the detector, other tubes may be used in some receivers. However, the basic circuit will be much the same.

Finding the a.g.c. (a.v.c.) line in the jumble beneath the chassis of the ordinary a.c.-d.c. receiver is not always easy. Here are a few hints:

Using section A, Fig. 5-63, as a guide, locate the detector tube socket. Trace out the leads going to the secondary of the last i.f. transformer, T_1 . This transformer usually will be adjacent to the detector tube. The lower end of the secondary winding will be connected to several different resistors, one of these being the diode-load filter resistor (approximately 50K in most circuits) and another the a.g.c. filter resistor, R_1 . The value of the latter resistor is ordinarily above one megohm. Trace through R_1 in the direction of the arrow (Fig. 5-63), until you locate the fairly high value (0.05 μ f. or so) a.g.c. filter capacitor, C_1 . Now you have the a.g.c. line clearly identified and the tap for the alarm circuit may be made.

Notice that the cathode of V_1 and the cold side of C_1 are both returned to a common bus or -B line, not directly to the chassis. Also observe that the return for the alarm circuit is made to the common bus in the receiver, not to the chassis of

S₁, S₂—S.p.s.t. rotory switch.
S₂—Momentory-contoct switch (Switchcraft 101).
T₂—Replacement-type power transformer, 150 volts, 25
ma.; 6.3 volts, 0.5 amp. (Merit P-3046).

the set. Do not ground this lead to the chassis or connect it to any exposed metal parts. If there is any difficulty in locating the common bus in the vicinity of the detector stage, check back from the negative side of the power-supply filter capacitors, as this point is always attached to the common bus.

The monitor should be built in an insulated box of some kind and not in a metal case. The box can be made of plywood, or a bakelite instrument case. The bakelite case is ideal for the application, but it must be handled with care during construction to avoid scratching, chipping, or breakage. Be especially careful when drilling large holes such as those used in mounting the pilot-lamp assemblies and switches, because a large drill tends to bind and crack the case.

The chances are pretty good that right after the receiver and the monitor have been turned on the red lamp will light and - if you haven't had the foresight to open S_{\bullet} to prevent the noise the buzzer will sound. Tune the receiver to a broadcast station and see if the red light goes out and the green light comes on. If this happens, close S, and you're all set for conelrad compliance. If the "safe" light does not come on, tune around for a signal strong enough to actuate the alarm. Should the signal of greatest apparent strength fail to trigger the monitor, leave the receiver tuned to this signal and then momentarily press S_3 . The alarm should now lock on "safe," provided the a.g.c. circuit delivers 0.7 volt or more to V_{\perp} .

High-Frequency Transmitters

The principal requirements to be met in c.w. transmitters for the amateur bands between 1.8 and 30 Mc. are that the frequency must be as stable as good practice permits, the output signal must be free from modulation and that harmonics and other spurious emissions must be eliminated or reduced to the point where they do not cause interference to other stations.

The over-all design depends primarily upon the bands in which operation is desired, and the power output. A simple oscillator with satisfactory frequency stability may be used as a transmitter at the lower frequencies, as indicated in Fig. 6-1A, but the power output obtainable is small. As a general rule, the output of the oscillator is fed into one or more amplifiers to bring the power fed to the antenna up to the desired level, as shown in B.

An amplifier whose output frequency is the same as the input frequency is called a straight amplifier. A buffer amplifier is the term sometimes applied to an amplifier stage to indicate that its primary purpose is one of isolation, rather than power gain.

Because it becomes increasingly difficult to maintain oscillator frequency stability as the frequency is increased, it is most usual practice in working at the higher frequencies to operate the oscillator at a low frequency and follow it with one or more frequency multipliers as required to arrive at the desired output frequency. A frequency multiplier is an amplifier that delivers output at a multiple of the exciting frequency. A doubler is a multiplier that gives output at twice the exciting frequency by three, etc. From the viewpoint of any particular stage in a transmitter, the preceding stage is its driver.

As a general rule, frequency multipliers should not be used to feed the antenna system directly, but should feed a straight amplifier which, in turn, feeds the antenna system, as shown in Fig. 1-C, D and E. As the diagrams indicate, it is often possible to operate more than one stage from a single power supply.

Good frequency stability is most easily obtained through the use of a crystal-controlled oscillator, although a different crystal is needed for each frequency desired (or multiples of that frequency). A self-controlled oscillator or v.f.o. (variable-frequency oscillator) may be tuned to any frequency with a dial in the manner of a receiver, but requires great care in

design and construction if its stability is to compare with that of a crystal oscillator.

In all types of transmitter stages, screen-grid tubes have the advantage over triodes that they require less driving power. With a lower-power exciter, the problem of harmonic reduction is made easier. Most satisfactory oscillator circuits use a screen-grid tube.

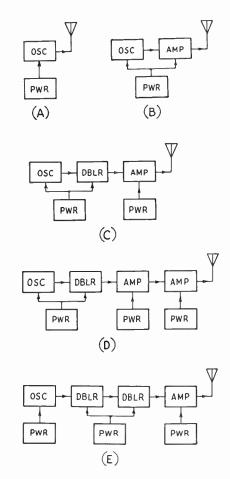


Fig. 6-1—Block diagrams showing typical combinations of oscillator and amplifiers and power-supply arrangements for transmitters. A wide selection is possible, depending upon the number of bands in which operation is desired and the power output.

CRYSTAL OSCILLATORS

The frequency of a crystal-controlled oscillator is held constant to a high degree of accuracy by the use of a quartz crystal. The frequency depends almost entirely on the dimensions of the crystal (essentially its thickness); other circuit values have comparatively negligible effect. However, the power obtainable is limited by the heat the crystal will stand without fracturing. The amount of heating is dependent upon the r.f. crystal current which, in turn, is a function of the amount of feedback required to provide proper excitation. Crystal heating short of the danger point results in frequency drift to an extent depending upon the way the crystal is cut. Excitation should always be adjusted to the minimum necessary for proper operation.

Crystal-Oscillator Circuits

The simplest crystal-oscillator circuit is shown in Fig. 6-2A. An equivalent circuit is shown in Fig. 6-2B, where C_4 represents the grid-cathode capacitance and C_5 indicates the plate-cathode, or output capacitance. The ratio of these capacitors controls the excitation for the oscillator, and good practice generally requires that both of these capacitances be augmented

factorily minimized by proper choice of the oscillator tube.

The circuit of Fig. 6-3A is known as the Tritet. The oscillator circuit is that of Fig. 6-2C. Excitation is controlled by adjustment of the tank L_1C_1 , which should have a low L/C ratio, and be tuned considerably to the high-frequency side of the crystal frequency (approximately 5 Mc. for a 3.5-Mc. crystal) to prevent over-excitation and high crystal current. Once the proper adjustment for average crystals has been found, C_1 may be replaced with a fixed capacitor of equal value.

The oscillator circuit of Fig. 6-3B is that of Fig. 6-2A. Excitation is controlled by C_9 .

The oscillator of the grid-plate circuit of Fig. 6-3C is the same as that of Fig. 6-3B, except that the ground point has been moved from the cathode to the plate of the oscillator (in other words, to the screen of the tube). Excitation is adjusted by proper proportioning of C_6 and C_7 .

When most types of tubes are used in the circuits of Fig. 6-3, oscillation will stop when the output plate circuit is tuned to the crystal frequency, and it is necessary to operate with the plate tank circuit critically detuned for maximum output with stability. However, when the 6AG7, 5763, or the lower-power 6AH6 is used

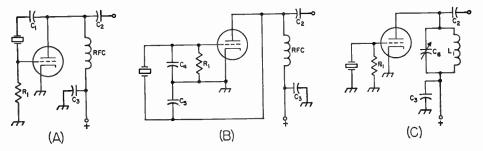


Fig. 6-2—Simple crystal oscillator circuits. A—Pierce. B—Equivalent of circuit A. C—Simple triode oscillator. C_1 is a plate blocking capacitor, C_2 an output coupling capacitor, and C_3 a plate bypass. C_4 and C_5 are discussed in the text. C_6 and L_1 should tune to the crystal fundamental frequency. R_1 is the grid leak.

by external capacitors, to provide better control of the excitation.

The circuit shown in Fig. 6-2C is the equivalent of the tuned-grid tuned-plate circuit discussed in the chapter on vacuum-tube principles, the crystal replacing the tuned grid circuit.

The most commonly used crystal-oscillator circuits are based on one or the other of these two simple types, and are shown in Fig. 6-3. Although these circuits are somewhat more complicated, they combine the functions of oscillator and amplifier or frequency multiplier in a single tube. In all of these circuits, the screen of a tetrode or pentode is used as the plate in a triode oscillator. Power output is taken from a separate tuned tank circuit in the actual plate circuit. Although the oscillator itself is not entirely independent of adjustments made in the plate tank circuit when the latter is tuned near the fundamental frequency of the crystal, the effects can be satis-

with proper adjustment of excitation, it is possible to tune to the crystal frequency without stopping oscillation. The plate tuning characteristic should then be similar to Fig. 6-4. These tubes also operate with less crystal current than most other types for a given power output, and less frequency change occurs when the plate circuit is tuned through the crystal frequency (less than 25 cycles at 3.5 Mc.).

Crystal current may be estimated by observing the relative brilliance of a 60-ma. dial lamp connected in series with the crystal. Current should be held to the minimum for satisfactory output by careful adjustment of excitation. With the operating voltages shown, satisfactory output should be obtained with crystal currents of 40 ma. or less.

In these circuits, output may be obtained at multiples of the crystal frequency by tuning the plate tank circuit to the desired harmonic, the output dropping off, of course, at the higher harmonics. Especially for harmonic operation, a low-C plate tank circuit is desirable.

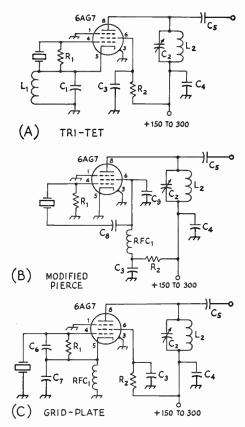


Fig. 6-3—Cammanly used crystal-cantralled ascillatar circuits. Values are thase recommended for a 6AG7 ar 5763 tube. (See reference in text for other tubes.) C₁—Feedback-contral capacitor—3.5-Mc. crystals—apprax. 220-μμt. mica—7-Mc. crystals—approx. 150-μμt. mica.

C₂—Output tank capacitor—100- $\mu\mu$ f, variable for single-band tank; 250- $\mu\mu$ f, variable far two-band tank.

C₃-Screen bypass-0.001-\mu f. disk ceramic.

C4-Plate bypass-0.001-\mu f. disk ceramic.

 C_8 —Output caupling capacitar—50 ta 100 $\mu\mu$ f.

C₆-Excitation-cantrol capacitar-30-μμf. trimmer.

C₇-Excitation capacitor-220- $\mu\mu$ f, mica for 6AG7; 100- $\mu\mu$ f, for 5763.

C₈-D.c. blacking capacitor-0.001-\(mu\)f. mica.

Co-Excitation-control capacitar-220-µµf, mica.

R₁-Grid leak-0.1 megohm, 1/2 watt.

R₂-Screen resistor-47,000 ohms, 1 watt.

L₁—Excitation-control inductance—3.5-Mc. crystals—approx. 4 µh.; 7-Mc. crystals—approx. 2 µh.

L₂-Output-circuit cail-single band:-3.5 Mc.-17 μh.; 7 Mc.-8 μh.; 14 Mc.-2.5 μh.; 28 Mc.-1 μh. Twa-band operation: 3.5 & 7 Mc.-7.5 μh.; 7 & 14 Mc.-2.5 μh.

RFC₁-2.5-mh. 50-ma. r.f. choke.

For best performance with a 6AG7 or 5763, the values given under Fig. 6-3 should be followed closely.

VARIABLE-FREQUENCY OSCILLATORS

The frequency of a v.f.o. depends entirely on the values of inductance and capacitance in the circuit. Therefore, it is necessary to take careful steps to minimize changes in these values not under the control of the operator. As examples, even the minute changes of dimensions with temperature, particularly those of the coil, may result in a slow but noticeable change in frequency called drift. The effective input capacitance of the oscillator tube, which must be connected across the circuit, changes with variations in electrode voltages. This, in turn, causes a change in the frequency of the oscillator. To make use of the power from the oscillator, a load, usually in the form of an amplifier, must be coupled to the oscillator, and variations in the load may reflect on the frequency. Very slight mechanical movement of the components may result in a shift in frequency, and vibration can cause modulation.

V.F.O. Circuits

Fig. 6-5 shows the most commonly used circuits. They are all designed to minimize the effects mentioned above. All are similar to the crystal oscillators of Fig. 6-3 in that the screen of a tetrode or pentode is used as the oscillator plate. The oscillating circuits in Figs. 6-5A and B are the Hartley type; those in C and D are Colpitts circuits. (See chapter on vacuum-tube principles.) In the circuits of A, B and C, all of the above-mentioned effects, except changes in inductance, are minimized by the use of a high-Q tank circuit obtained through the use of large tank capacitances. Any uncontrolled changes in capacitance thus become a very small percentage of the total circuit capacitance.

In the scries-tuned Colpitts circuit of Fig. 6-5D (sometimes called the Clapp circuit), a high-Q circuit is obtained in a different manner. The tube is tapped across only a small portion of the oscillating tank circuit, resulting in very loose coupling between tube and circuit. The taps are provided by a series of three capacitors across the coil. In addition, the tube capacitances are shunted by large capacitors, so the effects of the tube—changes in electrode voltages and loading—are still further reduced. In contrast to the preceding circuits, the resulting tank circuit has a high L/C ratio and therefore the tank current is much lower than in the circuits using high-C tanks. As a result, it will usually

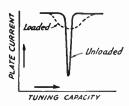


Fig. 6-4—Plate tuning characteristic of circuits of Fig. 6-3 with preferred types (see text). The plate-current dip at resonance braadens and is less pronaunced when the circuit is laaded.

Oscillators 147


be found that, other things being equal, drift will be less with the low-C circuit.

For best stability, the ratio of C_{12} or C_{13} (which are usually equal) to $C_{10} + C_{11}$ should be as high as possible without stopping oscillation. The permissible ratio will be higher the higher the Q of the coil and the mutual conductance of the tube. If the circuit does not oscillate over the desired range, a coil of higher Q must be used or the capacitance of C_{12} and C_{13} reduced.


Load Isolation

In spite of the precautions already discussed, the tuning of the output plate circuit will cause a noticeable change in frequency, particularly in the region around resonance. This effect can be reduced considerably by designing the oscillator for half the desired frequency and doubling frequency in the output circuit.


It is desirable, although not a strict necessity if detuning is recognized and taken into account, to approach as closely as possible the condition where the adjustment of tuning controls in the transmitter, beyond the v.f.o. frequency control, will have negligible effect on the frequency. This can be done by substituting a fixed-tuned circuit in the output of the oscillator, and adding isolating stages whose tuning is fixed between the oscillator and the first tunable amplifier stage in the transmitter. Fig. 6-6 shows such an arrangement that gives good isolation. In the first stage, a 6C4 is connected as a cathode follower. This

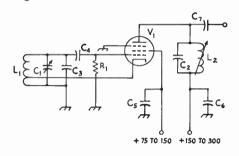


(A) HARTLEY

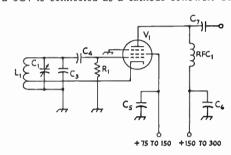

(B) HARTLEY - UNTUNED OUTPUT

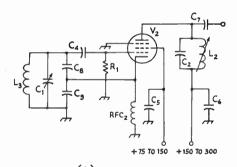

(c)COLPITTS

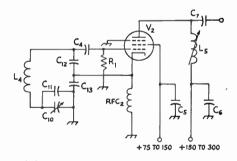

(D) SERIES - TUNED COLPITTS

Fig. 6-5-V.f.o. circuits. Approximate values for 3.5-4.0-Mc. output are given below. Grid circuits are tuned to half frequency (1.75 Mc.).

C₁-Oscillator bandspread tuning capacitor-200-\(mu\mu\mi\)f.

C₂-Output-circuit tank capacitor-47-μμf.

C₃-Oscillator tank capacitor-600-\(\mu\mu\mathbf{f}\), zero-temperature-coefficient mica.

 C_4 —Grid coupling capacitor—100- $\mu\mu f$. zero-temperoture-coefficient mica.

C₅-Screen bypass-0.001-\mu f. disk ceramic.

C₆-Plate bypass-0.001-\mu f. disk ceramic.

 C_7 -Output coupling capacitor-50 to 100- $\mu\mu$ f. mica.

C₈-Oscillator tank capacitor-750-\(mu\mu f\). zero-temperature-coefficient mico.

Co-Oscillator tank capacitor-0.0033-4f. zero-temperature-coefficient mica.

C₁₀-Oscillator bandspread padder-100-\(mu\mu f\), voriable air.

C11-Oscillator bandspread tuning capacitor-50-µµf. variable.

C₁₂, C₁₃—Tube-coupling capacitor—0.002-µf. zero-temperature-coefficient mica.

 $R_1=47,000 \text{ ohms}, \frac{1}{2} \text{ watt.}$

 L_1 -Oscillator tank coil-10 μ h., tapped about onethird-way from grounded end.

L2-Output-circuit tank coil-20-40 µh., adjustable.

L3-Oscillator tank coil-10 µh.

L3-Oscillator tank coil-10 µh.

L-Oscillator tank coil-70 µh.

L5-Output coil-100-140 µh., adjustable.

RFC1-100 µh. r.f. choke.

V1-6AG7, 5763 or 6AH6 preferred; other types

V2-6AG7, 5763 or 6AH6 required for feedback copacitances shown.

drives a 5763 buffer amplifier whose input circuit is fixed-tuned to the approximate band of the v.f.o. output. For best isolation, it is important that the 6C4 does not draw grid current. The output of the v.f.o., or the cathode resistor of the 6C4 should be adjusted until the voltage across the cathode resistor of the 6C4 (as measured with a high-resistance d.c. voltmeter with an r.f. choke in the positive lead) is the same with or without excitation from the v.f.o. L_1 should be adjusted for most constant output from the 5763 over the band.

Chirp

In all of the circuits shown there will be some change of frequency with changes in screen and plate voltages, and the use of regulated voltages for both usually is necessary. One of the most serious results of voltage instability occurs if the oscillator is keyed, as it often is for break-in operation. Although voltage regulation will supply a steady voltage from the power supply and therefore is still desirable, it cannot alter the fact that the voltage on the tube must rise from zero when the key is open, to full voltage when the key is closed, and must fall back again to zero when the key is opened. The result is a chirp each time the key is opened or closed,

unless the time constant in the keving circuit is reduced to the point where chirp takes rapidly place so that the receiving operator's ear cannot detect it. Unfortunately, as explained in the chapter on keying, a certain minimum time constant is necessary if key clicks are to be minimized. Therefore it is evident that the measures necessary for the

reduction of chirp and clicks are in opposition, and a compromise is necessary. For best keying characteristics, the oscillator should be allowed to run continuously while a subsequent amplifier is keyed. However, a keyed amplifier represents a widely variable load and unless sufficient isolation is provided between the oscillator and the keyed amplifier, the keying characteristics may be little better than when the oscillator itself is keyed. (See keying chapter for other methods of break-in keying.)

Frequency Drift

Frequency drift is further reduced most easily by limiting the power input as much as possible and by mounting the components of the tuned circuit in a separate shielded compartment, so that they will be isolated from the direct heat from tubes and resistors. The shielding also will eliminate changes in frequency caused by movement of nearby objects, such as the operator's hand when tuning the v.f.o. The circuit of Fig. 6-5D lends itself well to this arrangement, since relatively long leads between the tube and the tank circuit have negligible effect on frequency because of the large shunting capacitances. The grid, cathode and ground leads to the tube can be bunched in a cable up to several feet long.

Variable capacitors should have ceramic insulation, good bearing contacts and should preferably be of the double-bearing type, and fixed capacitors should have zero temperature coefficient. The tube socket also should have ceramic insulation and special attention should be paid to the selection of the coil in the oscillating section.

Oscillator Coils

The Q of the tank coil used in the oscillating portion of any of the circuits under discussion should be as high as circumstances (usually space) permit, since the losses, and therefore the heating, will be less. With recommended care in regard to other factors mentioned previously, most of the drift will originate in the coil. The coil should be well spaced from shielding and other large metal surfaces, and be of a type that radiates heat well, such as a commercial air-

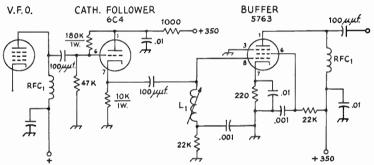


Fig. 6-6—Circuit af an isalating amplifier far use between v.f.a. and first tunable stage. Unless atherwise specified, all capacitances are in μf ., all resistars are $\frac{1}{2}$ watt. L₁, for the 3.5-Mc. band, consists of 100-140 μh . adjustable inductor. RFC₁ is 100 μh . All capacitars are disk ceramic.

wound type, or should be wound tightly on a threaded ceramic form so that the dimensions will not change readily with temperature. The wire with which the coil is wound should be as large as practicable, especially in the high-*C* circuits.

Mechanical Vibration

To eliminate mechanical vibration, components should be mounted securely. Particularly in the circuit of Fig. 6-5D, the capacitor should preferably have small, thick plates and the coil braced, if necessary, to prevent the slightest mechanical movement. Wire connections between tank-circuit components should be as short as possible and flexible wire will have less tendency to vibrate than solid wire. It is advisable to cushion the entire oscillator unit by mounting on sponge rubber or other shock mounting.

Tuning Characteristic

If the circuit is oscillating, touching the grid of the tube or any part of the circuit connected to it will show a change in plate current. In tuning the plate output circuit without load, the plate current will be relatively high until it is tuned near resonance where the plate current will dip to a low value, as illustrated in Fig. 6-4. When the output circuit is loaded, the dip should still be found, but broader and much less pronounced as indicated by the dashed line. The circuit should not be loaded beyond the point where the dip is still recognizable.

Checking V.F.O. Stability

A v.f.o. should be checked thoroughly before it is placed in regular operation on the air. Since succeeding amplifier stages may affect the signal characteristics, final tests should be made with the complete transmitter in operation. Almost any v.f.o. will show signals of good quality and stability when it is running free and not connected to a load. A well-isolated monitor is a necessity. Perhaps the most convenient, as well as one of the most satisfactory, well-shielded monitoring arrangements is a receiver combined with a crystal oscillator, as shown in Fig. 6-7. (See "Crystal Oscillators," this chapter.) The crystal frequency should lie in the band of the lowest frequency to be checked and in the frequency range where its harmonics will fall in the higher-frequency bands. The receiver b.f.o. is turned off and the v.f.o. signal is tuned to beat with the signal from the crystal oscillator instead. In this way any receiver instability caused by overloading of the input circuits, which may result in "pulling" of the h.f. oscillator in the receiver, or by a change in line voltage to the receiver when the transmitter is keyed, will not affect the reliability of the check. Most crystals have a sufficiently low temperature coefficient to give a check on drift as well as on chirp and signal quality if they are not overloaded.

Harmonics of the crystal may be used to beat with the transmitter signal when monitoring at the higher frequencies. Since any chirp at the lower frequencies will be magnified at the higher frequencies, accurate checking can best be done by monitoring at a harmonic.

The distance between the crystal oscillator and receiver should be adjusted to give a good beat between the crystal oscillator and the transmitter signal. When using harmonics of the crystal oscillator, it may be necessary to attach a piece

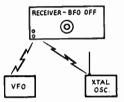


Fig. 6-7—Setup for checking v.f.o. stability. The receiver should be tuned preferably to a harmonic of the v.f.o. frequency. The crystal oscillator may operate somewhere in the band in which the v.f.o. is operating. The receiver b.f.o. should be turned off.

of wire to the oscillator as an antenna to give sufficient signal in the receiver. Checks may show that the stability is sufficiently good to permit oscillator keying at the lower frequencies, where break-in operation is of greater value, but that chirp becomes objectionable at the higher frequencies. If further improvement does not seem possible, it would be logical in this case to use oscillator keying at the lower frequencies and amplified keying at the higher frequencies.

R.F. POWER-AMPLIFIER TANKS AND COUPLING

In the remainder of this chapter the vacuum tubes will be shown, for the most part, with indirectly-heated cathodes. However, many transmitting tubes used directly-heated filaments for the cathodes; when this is done the filament "center-tap" connection will be used, as shown in Fig. 6-8.


PLATE TANK Q

R.f. power amplifiers used in amateur transmitters are operated under Class-C or -AB conditions (see chapter on tube fundamentals). The main objective, of course, is to deliver as much fundamental power as possible into a load, R, without exceeding the tube ratings. The load resistance R may be in the form of a transmission line to an antenna, or the grid circuit of another amplifier. A further objective is to minimize the harmonic energy (always generated by a Class C amplifier) fed into the load circuit. In attaining these objectives, the Q of the tank circuit is of importance. When a load is coupled inductively, as in Fig. 6-10, the Q of the tank circuit

will have an effect on the coefficient of coupling necessary for proper loading of the amplifier. In respect to all of these factors, a tank Q of 10 to 20 is usually considered optimum. A much lower Q will result in less efficient operation of the amplifier tube, greater harmonic output, and greater difficulty in coupling inductively to a load. A much higher Q will result in higher tank current with increased loss in the tank coil.

The Q is determined (see chapter on electrical

Fig. 6-8—Filament center-tap connections to be substituted in place of cathode connections shown in diagrams when filament-type tubes are substituted. T₁ is the filament transformer. Filament bypasses, C₁, should be 0.01-\(mu f\). disk ceramic capacitors. If a self-biasing (cathode) resistor is used, it should be placed between the center tap and ground,

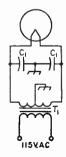

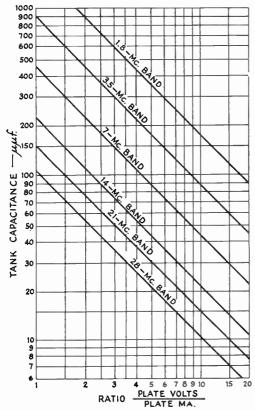


Fig. 6-9—Chart showing plate tank capacitance required for a Q of 10. Divide the tube plate voltage by the plate current in milliamperes. Select the vertical line corresponding to the answer obtained. Follow this vertical line to the diagonal line for the band in question, and thence horizontally to the left to read the capacitance. For a given ratio of plate-voltage/plate current, doubling the capacitance shown doubles the Q, etc. When a split-stator capacitor is used in a bolanced circuit, the capacitance of each section may be one half of the value given by the

laws and circuits) by the L/C ratio and the load resistance at which the tube is operated. The tube load resistance is related, in approximation, to the ratio of the d.c. plate voltage to d.c. plate current at which the tube is operated.

The amount of C that will give a Q of 10 for various ratios is shown in Fig. 6-9. For a given plate-voltage/plate-current ratio, the Q will vary directly as the tank capacitance, twice the capacitance doubles the Q, etc. For the same Q, the capacitance of each section of a split-stator capacitor in a balanced circuit should be half the value shown.

These values of capacitance include the output capacitance of the amplifier tube, the input capacitance of a following amplifier tube if it is coupled capacitively, and all other stray capacitances. At the higher plate-voltage/plate-current ratios, the chart may show values of capacitance,

for the higher frequencies, smaller than those attainable in practice. In such a case, a tank Q higher than 10 is unavoidable.

In low-power exciter stages, where capacitive coupling is used, very low-Q circuits, tuned only by the tube and stray circuit capacitances are sometimes used for the purpose of "broadbanding" to avoid the necessity for retuning a stage across a band. Higher-order harmonics generated in such a stage can usually be attenuated in the tank circuit of the final amplifier.

INDUCTIVE-LINK COUPLING

Coupling to Flat Coaxial Lines

When the load R in Fig. 6-10 is located for convenience at some distance from the amplifier, or when maximum harmonic reduction is desired, it is advisable to feed the power to the load through a low-impedance coaxial cable. The shielded construction of the cable prevents radiation and makes it possible to install the line in any convenient manner without danger of unwanted coupling to other circuits.

If the line is more than a small fraction of a wavelength long, the load resistance at its output end should be adjusted, by a matching circuit if necessary, to match the impedance of the cable. This reduces losses in the cable and makes the coupling adjustments at the transmitter independent of the cable length. Matching circuits for use between the cable and another transmission line are discussed in the chapter on transmission lines, while the matching adjustments when the load is the grid circuit of a following

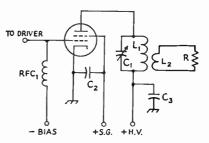


Fig. 6-10—Inductive-link output coupling circuits.

C1—Plate tank capacitor—see text and Fig. 6-9 for capacitance, Fig. 6-33 for voltage rating.

C2—Screen bypass—voltage rating depends on method of screen supply. See paragraphs on screen considerations. Voltage rating same as plate voltage will be safe under any condition.

C₃-Plate bypass-0.001-\(\mu\)f. disk ceramic or mica.

Voltage rating same as C₁, plus safety factor.

L₁-To resonate at operating frequency with C₁. See.

LC chart ond inductance formula in electricallaws chapter, or use ARRL Lightning Calculator.

L2—Reactance equal to line impedance. See reactonce chart and inductance formula in electricollaws chapter, or use ARRL Lightning Colculator

R-Representing lood.

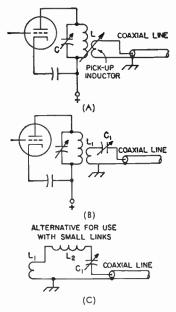


Fig. 6-11—With flat transmission lines, power transfer is obtained with looser coupling if the line input is tuned to resonance. C_1 and L_1 should resonate at the operating frequency. See table for maximum usable value of C_1 . If circuit does not resonate with maximum C_1 or less, inductance of L_1 must be increased, or added in series at L_2 .

amplifier are described elsewhere in this chapter.
Assuming that the cable is properly terminated, proper loading of the amplifier will be assured, using the circuit of Fig. 6-11A, if

1) The plate tank circuit has reasonably high value of Q. A value of 10 is usually sufficient.

2) The inductance of the pick-up or link coil is close to the optimum value for the frequency and type of line used. The optimum coil is one whose self-inductance is such that its reactance at the operating frequency is equal to the characteristic impedance, Z_0 , of the line.

3) It is possible to make the coupling between the tank and pick-up coils very tight.

The second in this list is often hard to meet. Few manufactured link coils have adequate inductance even for coupling to a 50-ohm line at low frequencies.

Capacitance in $\mu\mu$ f. Required for Coupling to Flat Coaxial Lines with Tuned Coupling Circuit

requency	Characteristic Im	pedance of Line
Band	52	75
Mc.	ohms1	ohms1
3.5	450	300
7	230	150
14	115	75
21	80	50
28	60	40

¹ Capacitance values are maximum usable. *Note*: Inductance in circuit must be adjusted to resonate at operating frequency.

If the line is operating with a low s.w.r., the system shown in Fig. 6-11A will require tight coupling between the two coils. Since the secondary (pick-up coil) circuit is not resonant, the leakage reactance of the pick-up coil will cause some detuning of the amplifier tank circuit. This detuning effect increases with increasing coupling, but is usually not serious. However, the amplifier tuning must be adjusted to resonance, as indicated by the plate-current dip, each time the coupling is changed.

Tuned Coupling

The design difficulties of using "untuned" pick-up coils, mentioned above, can be avoided by using a coupling circuit tuned to the operating frequency. This contributes additional selectivity as well, and hence aids in the suppression of spurious radiations.

If the line is flat the input impedance will be essentially resistive and equal to the Z_0 of the line. With coaxial cable, a circuit of reasonable Q can be obtained with practicable values of inductance and capacitance connected in series with the line's input terminals. Suitable circuits are given in Fig. 6-11 at B and C. The Q of the coupling circuit often may be as low as 2, without running into difficulty in getting adequate coupling to a tank circuit of proper design. Larger values of Q can be used and will result in increased ease of coupling, but as the Q is increased the frequency range over which the circuit will operate without readjustment becomes smaller. It is usually good practice, therefore, to use a coupling-circuit Q just low enough to permit operation, over as much of a band as is normally used for a particular type of communication, without requiring retuning.

Capacitance values for a Q of 2 and line impedances of 52 and 75 ohms are given in the accompanying table. These are the maximum values that should be used. The inductance in the circuit should be adjusted to give resonance at the operating frequency. If the link coil used for a particular band does not have enough inductance to resonate, the additional inductance may be connected in series as shown in Fig. 6-11C.

Characteristics

In practice, the amount of inductance in the circuit should be chosen so that, with somewhat loose coupling between L_1 and the amplifier tank coil, the amplifier plate current will increase when the variable capacitor, C_1 is tuned through the value of capacitance given by the table. The coupling between the two coils should then be increased until the amplifier loads normally, without changing the setting of C_1 . If the transmission line is flat over the entire frequency band under consideration, it should not be necessary to readjust C1 when changing frequency, if the values given in the table are used. However, it is unlikely that the line actually will be flat over such a range, so some readjustment of C_1 may be needed to compensate for changes in the input impedance of the line. If the input impedance variations are not large, C_1 may be used as a loading control, no changes in the coupling between L_1 and the tank coil being necessary.

The degree of coupling between L_1 and the amplifier tank coil will depend on the coupling-circuit Q. With a Q of 2, the coupling should be tight—comparable with the coupling that is typical of "fixed-link" manufactured coils. With a swinging link it may be necessary to increase the Q of the coupling circuit in order to get sufficient power transfer. This can be done by increasing the L/C ratio.

PI-SECTION OUTPUT TANK

A pi-section tank circuit may also be used in coupling to an antenna or transmission line, as shown in Fig. 6-12. The optimum values of capacitance for C_1 and C_2 , and inductance for L_1 are dependent upon values of tube power input and output load resistance.

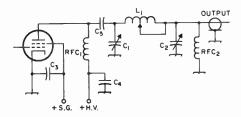


Fig. 6-12—Pi-sectian autput tank circuit.

C1—Input ar plate tuning capacitar. See text or Fig.
6-13 far reactance. Voltage rating equal ta
d.c. plate valtage; twice this far plate modulation.

C₂—Output or laading capacitor. See text ar Fig. 6-15 for reactance. See text for valtage rating.

C₃—Screen bypass, See Fig. 6-10.

C₄—Plate bypass. See Fig. 6-10.

 C_{δ} —Plate blacking capacitor—0.001- μ f, disk ceramic or mica. Valtage rating same as C_{1} .

L₁—See text ar Fig. 6-14 far reactance.

RFC1-See later paragraph an r.f. chakes.

RFC₂=2.5-mh. receiving type (to reduce peak valtage acrass bath C_1 and C_2 and to blow plate power supply fuse if C_5 fails).

Values of reactance for C_1 , L_1 and C_2 may be taken directly from the charts of Figs. 6-13, 6-14 and 6-15 if the output load resistance is the usual 52 or 72 ohms. It should be borne in mind that these values apply only where the output load is resistive, i.e., where the antenna and line have been matched.

Output-Capacitor Ratings

The voltage rating of the output capacitor will depend upon the s.w.r. If the load is resistive, receiving-type air capacitors should be adequate for amplifier input powers up to 1 kw. with plate modulation when feeding 52- or 72-ohm loads. In obtaining the larger capacitances re-

PI-NETWORK DESIGN CHARTS FOR FEEDING 52-OR 72-OHM COAXIAL TRANSMISSION LINES

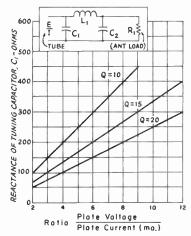


Fig. 6-13—Reactance of input capacitar, C₁, as a function the ratio of plate valtage to plate current.

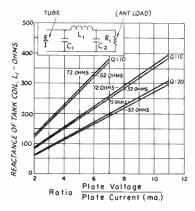


Fig. 6-14—Reactance of tank cail, L₁, as a function of plate valtage and current, for pi networks.

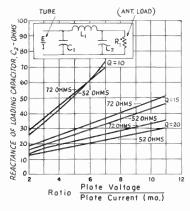


Fig. 6-15—Reactance of laading capacitor, C_2 , as a function of plate voltage and current, for pi networks.

Pi-Section Output Tanks

Fig. 6-16—Multiband tuner circuits. In the unbalanced circuit of A, C₁ and C₂ are sections of a single split-stator capacitor. In the balanced circuit of D, the two split-stator capacitors are ganged to a single control with an insulated shaft coupling between the two. In D, the two sections of L₂ are wound on the same form, with the inner ends connected to C₂. In A, each section of the capacitor should have a voltage rating the same as Fig. 6-33A. In D, C₁ should have a rating the same as Fig. 6-33H (or Fig. 6-33E if the feed system corresponds). C₂ may have the rating of Fig. 6-33E so long as the rotor is not grounded or bypassed to ground.


quired for the lower frequencies, it is common practice to switch fixed capacitors in parallel with the variable air capacitor. While the voltage rating of a mica or ceramic capacitor may not be exceeded in a particular case, capacitors of these types are limited in current-carrying capacity. Postage-stamp silver-mica capacitors should be adequate for amplifier inputs over the range from about 70 watts at 28 Mc. to 400 watts at 14 Mc. and lower. The larger mica capacitors (CM-45 case) having voltage ratings of 1200 and 2500 volts are usually satisfactory for inputs varying from about 350 watts at 28 Mc. to 1 kw. at 14 Mc. and lower. Because of these current limitations, particularly at the higher frequencies, it is advisable to use as large an air capacitor as practicable, using the micas only at the lower frequencies. Broadcast-receiver replacement-type capacitors can be obtained very reasonably. They are available in triple units totaling about 1100 µµf., or dual units totaling about 900 µµf. Their insulation should be sufficient for inputs of 500 watts or more. Air capacitors have the additional advantage that they are seldom permanently damaged by a voltage break-down.

Neutralizing with Pi Network

Screen-grid amplifiers using a pi-network output circuit may be neutralized by the system shown in Figs. 6-23 B and C.

MULTIBAND TANK CIRCUITS

Multiband tank circuits provide a convenient means of covering several bands without the need for changing coils. Tuners of this type consist essentially of two tank circuits, tuned simultaneously with a single control. In a tuner designed to cover 80 through 10 meters, each circuit has a sufficiently large capacitance variation to assure an approximately 2-to-1 frequency range. Thus, one circuit is designed so that it covers 3.5 through 7.3 Mc., while the other covers 14 through 29.7 Mc.

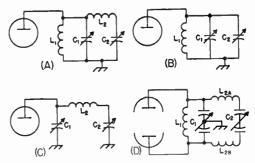

A single-ended, or unbalanced, circuit of this type is shown in Fig. 6-16A. In principle, the reactance of the high-frequency coil, L_2 , is small enough at the lower frequencies so that it can be largely neglected, and C_1 and C_2 are in parallel across L_1 . Then the circuit for low frequencies becomes that shown in Fig. 6-16B. At the high frequencies, the reactance of L_1 is high, so that it may be considered simply as a choke shunting C_1 . The high-frequency circuit is essentially that of Fig. 6-16C, L_2 being tuned by C_1 and C_2 in series.

In practice, the effect of one circuit on the other cannot be neglected entirely. L_2 tends to increase the effective capacitance of C_2 , while L_1 tends to decrease the effective capacitance of C_1 . This effect, however, is relatively small. Each circuit must cover somewhat more than a 2-to-1 frequency range to permit staggering the two ranges sufficiently to avoid simultaneous responses to a frequency in the low-frequency range, and one of its harmonics lying in the range of the high-frequency circuit.

In any circuit covering a frequency range as great as 2 to 1 by capacitance alone, the circuit Q must vary rather widely. If the circuit is designed for a Q of 12 at 80, the Q will be 6 at 40, 24 at 20, 18 at 15, and 12 at 10 meters. The increase in tank current as a result of the increase in Q toward the low-frequency end of the high-frequency range may make it necessary to design the high-frequency coil with care to minimize loss in this portion of the tuning range. It is generally found desirable to provide separate output coupling coils for each circuit.

Fig. 6-16D shows a similar tank for balanced circuits. The same principles apply.

Series or parallel feed may be used with either balanced or unbalanced circuits. In the balanced circuit of Fig. 6-16D, the series feed point would be at the center of L_{10} , with an r.f. choke in series.

(For further discussion see QST, July, 1954.)

R.F. AMPLIFIER-TUBE OPERATING CONDITIONS

In addition to proper tank and output-coupling circuits discussed in the preceding sections, an r.f. amplifier must be provided with suitable electrode voltages and an r.f. driving or excitation voltage (see vacuum-tube chapter).

All r.f. amplifier tubes require a voltage to operate the filament or heater (a.c. is usually permissible), and a positive d.c. voltage between the plate and filament or cathode (plate voltage). Most tubes also require a negative d.c. voltage

(biasing voltage) between control grid (Grid No. 1) and filament or cathode. Screen-grid tubes require in addition a positive voltage (screen voltage or Grid No. 2 voltage) between screen and filament or cathode.

Biasing and plate voltages may be fed to the tube either in series with or in parallel with the associated r.f. tank circuit as discussed in the chapter on electrical laws and circuits.

It is important to remember that true plate, screen or biasing voltage is the voltage between the particular electrode and filament or cathode. Only when the cathode is directly grounded to the chassis may the electrode-to-chassis voltage be taken as the true voltage.

The required r.f. driving voltage is applied between grid and cathode.

Power Input and Plate Dissipation

Plate power input is the d.c. power input to the plate circuit (d.c. plate voltage \times d.c. plate current).—Screen power input likewise is the d.c. screen voltage \times the d.c. screen current.

Plate dissipation is the difference between the r.f. power delivered by the tube to its loaded plate tank circuit and the d.c. plate power input. The screen, on the other hand, does not deliver any output power, and therefore its dissipation is the same as the screen power input.

TRANSMITTING-TUBE RATINGS

Tube manufacturers specify the maximum values that should be applied to the tubes they produce. They also publish sets of typical operating values that should result in good efficiency and normal tube life.

Maximum values for all of the most popular transmitting tubes will be found in the tables of transmitting tubes in the last chapter. Also included are as many sets of typical operating values as space permits. However, it is recommended that the amateur secure a transmitting-tube manual from the manufacturer of the tube or tubes he plans to use.

CCS and ICAS Ratings

The same transmitting tube may have different ratings depending upon the manner in which the tube is to be operated, and the service in which it is to be used. These different ratings are based primarily upon the heat that the tube can safely dissipate. Some types of operation, such as with grid or screen modulation, are less efficient than others, meaning that the tube must dissipate more heat. Other types of operation, such as c.w. or single-sideband phone are intermittent in nature, resulting in less average heating than in other modes where there is a continuous power input to the tube during transmissions. There are also different ratings for tubes used in transmitters that are in almost constant use (CCS-Continuous Commercial Service), and for tubes that are to be used in transmitters that average only a few hours of daily operation (ICAS-Intermittent Commercial and Amateur Service). The latter are the ratings used by amateurs who wish to obtain maximum output with reasonable tube life.

Maximum Ratings

Maximum ratings, where they differ from the values given under typical operating values, are not normally of significance to the amateur except in special applications. No single maximum value should be used unless all other ratings can simultaneously be held within the maximum values. As an example, a tube may have a maximum plate-voltage rating of 2000, a maximum plate-current rating of 300 ma., and a maximum plate-power-input rating of 400 watts. Therefore, if the maximum plate voltage of 2000 is used, the plate current should be limited to 200 ma. (instead of 300 ma.) to stay within the maximum power-input rating of 400 watts.

SOURCES OF ELECTRODE VOLTAGES

Filament or Heater Voltage

The filament voltage for the indirectly heated cathode-type tubes found in low-power classifications may vary 10 per cent above or below rating without seriously reducing the life of the tube. But the voltage of the higher-power filament-type tubes should be held closely between the rated voltage as a minimum and 5 per cent above rating as a maximum. Make sure that the plate power drawn from the power line does not cause a drop in filament voltage below the proper value when plate power is applied.

Thoriated-type filaments lose emission when the tube is overloaded appreciably. If the overload has not been too prolonged, emission sometimes may be restored by operating the filament at rated voltage with all other voltages removed for a period of 10 minutes, or at 20 per cent above rated voltage for a few minutes.

Plate Voltage

D.c. plate voltage for the operation of r.f. amplifiers is most often obtained from a transformer-rectifier-filter system (see power-supply chapter) designed to deliver the required plate voltage at the required current. However, batteries or other d.c.-generating devices are sometimes used in certain types of operation (see portable-mobile chapter).

Bias and Tube Protection

Several methods of obtaining bias are shown in Fig. 6-17. In A, bias is obtained by the voltage drop across a resistor in the grid d.c. return circuit when rectified grid current flows. The proper value of resistance may be determined by dividing the required biasing voltage by the d.c. grid current at which the tube will be operated. Then, so long as the r.f. driving voltage is adjusted so that the d.c. grid current is the recommended value, the biasing voltage will be the proper value. The tube is biased only when excitation is applied, since the voltage drop across the resistor depends upon grid-current flow. When excitation is removed, the bias falls to

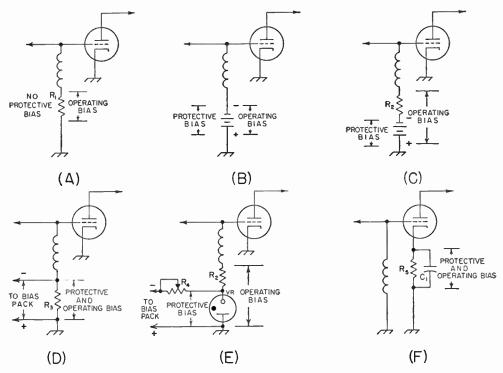


Fig. 6-17—Various systems for obtaining protective and operating bias for r.f. amplifiers. A—Grid-leak. B—Battery. C—Combination battery and grid leak. D—Grid leak and adjusted-voltage bias pack. E—Combination grid leak and voltage-regulated pack. F—Cathode bias.

zero. At zero bias most tubes draw power far in excess of the plate-dissipation rating. So it is advisable to make provision for protecting the tube when excitation fails by accident, or by intent as it does when a preceding stage in a c.w. transmitter is keyed.

If the maximum c.w. ratings shown in the tube tables are to be used, the input should be cut to zero when the key is open. Aside from this, it is not necessary that plate current be cut off completely but only to the point where the rated dissipation is not exceeded. In this case platemodulated phone ratings should be used for c.w. operation, however.

With triodes this protection can be supplied by obtaining all bias from a source of fixed voltage, as shown in Fig. 6-17B. It is preferable, however, to use only sufficient fixed bias to protect the tube and obtain the balance needed for operating bias from a grid leak, as in C. The grid-leak resistance is calculated as above, except that the fixed voltage is subtracted first.

Fixed bias may be obtained from dry batteries or from a power pack (see power-supply chapter). If dry batteries are used, they should be checked periodically, since even though they may show normal voltage, they eventually develop a high internal resistance. Grid-current flow through this battery resistance may increase the bias considerably above that anticipated. The life of batteries in bias service will be approximately the same as though they were subject to a drain equal to the grid current, despite the fact that the

grid-current flow is in such a direction as to charge the battery, rather than to discharge it.

In Fig. 6-17F, bias is obtained from the voltage drop across a resistor in the cathode (or filament center-tap) lead. Protective bias is obtained by the voltage drop across R_5 as a result of plate (and screen) current flow. Since plate current must flow to obtain a voltage drop across the resistor, it is obvious that cut-off protective bias cannot be obtained. When excitation is applied, plate (and screen) current increases and the grid current also contributes to the drop across R5, thereby increasing the bias to the operating value. Since the voltage between plate and cathode is reduced by the amount of the voltage drop across R_5 , the over-all supply voltage must be the sum of the plate and operating-bias voltages. For this reason, the use of cathode bias usually is limited to low-voltage tubes when the extra voltage is not difficult to obtain.

The resistance of the cathode biasing resistor R_5 should be adjusted to the value which will give the correct operating bias voltage with rated grid, plate and screen currents flowing with the amplifier loaded to rated input. When excitation is removed, the input to most types of tubes will fall to a value that will prevent damage to the tube, at least for the period of time required to remove plate voltage. A disadvantage of this biasing system is that the cathode r.f. connection to ground depends upon a bypass capacitor. From the consideration of v.h.f. harmonics and stability with high-perveance tubes, it is preferable

to make the cathode-to-ground impedance as close to zero as possible.

Screen Voltage

For c.w. operation, and under certain conditions of phone operation (see amplitude-modulation chapter), the screen may be operated from a power supply of the same type used for plate supply, except that voltage and current ratings should be appropriate for screen requirements. The screen may also be operated through a series resistor or voltage-divider from a source of higher voltage, such as the plate-voltage supply, thus making a separate supply for the screen unnecessary. Certain precautions are necessary, depending upon the method used.

It should be kept in mind that screen current varies widely with both excitation and loading. If the screen is operated from a fixed-voltage source, the tube should never be operated without plate voltage and load, otherwise the screen may be damaged within a short time. Supplying the screen through a series dropping resistor from a higher-voltage source, such as the plate supply, affords a measure of protection, since the resistor causes the screen voltage to drop as the current increases, thereby limiting the power drawn by the screen. However, with a resistor, the screen voltage may vary considerably with excitation, making it necessary to check the voltage at the screen terminal under actual operating conditions to make sure that the screen voltage is normal. Reducing excitation will cause the screen current to drop, increasing the voltage; increasing excitation will have the opposite effect. These changes are in addition to those caused by changes in bias and plate loading, so if a screen-grid tube is operated from a series resistor or a voltage divider, its voltage should be checked as one of the final adjustments after excitation and loading have been set.

An approximate value for the screen-voltage dropping resistor may be obtained by dividing the voltage *drop* required from the supply voltage (difference between the supply voltage and rated screen voltage) by the rated screen current in decimal parts of an ampere. Some further adjustment may be necessary, as mentioned above, so an adjustable resistor with a total resistance above that calculated should be provided.

Protecting Screen-Grid Tubes

Screen-grid tubes cannot be cut off with bias unless the screen is operated from a fixed-voltage supply. In this case the cut-off bias is approximately the screen voltage divided by the amplification factor of the screen. This figure is not always shown in tube-data sheets, but cut-off voltage may be determined from an inspection of tube curves, or by experiment.

When the screen is supplied from a series dropping resistor, the tube can be protected by the use of a clamper tube, as shown in Fig. 6-18. The grid-leak bias of the amplifier tube with excitation is supplied also to the grid of the clamper tube. This is usually sufficient to cut off

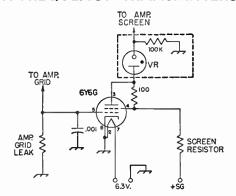


Fig. 6-18—Screen clomper circuit for protecting screen-grid power tubes. The VR tube is needed only for complete cut-off.

the clamper tube. However, when excitation is removed, the clamper-tube bias falls to zero and it draws enough current through the screen dropping resistor usually to limit the input to the amplifier to a safe value. If complete screenvoltage cut-off is desired, a VR tube may be inserted in the screen lead as shown. The VR-tube voltage rating should be high enough so that it will extinguish when excitation is removed.

FEEDING EXCITATION TO THE GRID

The required r.f. driving voltage is supplied by an oscillator generating a voltage at the desired frequency, either directly or through intermediate amplifiers or frequency multipliers.

As explained in the chapter on vacuum-tube fundamentals, the grid of an amplifier operating under Class C conditions must have an exciting voltage whose peak value exceeds the negative biasing voltage over a portion of the excitation cycle. During this portion of the cycle, current will flow in the grid-cathode circuit as it does in a diode circuit when the plate of the diode is positive in respect to the cathode. This requires that the r.f. driver supply power. The power required to develop the required peak driving voltage across the grid-cathode impedance of the amplifier is the r.f. driving power.

The tube tables give approximate figures for the grid driving power required for each tube under various operating conditions. These figures, however, do not include circuit losses. In general, the driver stage for any Class C amplifier should be capable of supplying at least three times the driving power shown for typical operating conditions at frequencies up to 30 Mc., and from three to ten times at higher frequencies.

Since the d.c. grid current relative to the biasing voltage is related to the peak driving voltage, the d.c. grid current is commonly used as a convenient indicator of driving conditions. A driver adjustment that results in rated d.c. grid current when the d.c. bias is at its rated value, indicates proper excitation to the amplifier when it is fully loaded.

In coupling the grid input circuit of an amplifier to the output circuit of a driving stage the

Feeding the Grid

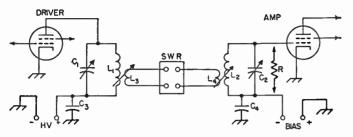


Fig. 6-19—Coupling excitation to the grid of an r.f. power amplifier by means of a low-impedance coaxial line.

C1, C3, L1, L3-See corresponding components in Fig. 6-10.

 C_2 —Amplifier grid tank capacitor—see text and Fig. 6-20 for capacitance, Fig. 6-34 for voltage rating. C_4 —0.001- μ f. disk ceramic.

L₂—To resonate at operating frequency with C₂. See LC chart inductance formula in electrical-laws chapter, or use ARRL Lightning Calculator.

L4—Reactance equal to line impedance—see reactance chart and inductance formula in electrical-laws chapter, or use ARRL Lightning Calculator.

R is used to simulate grid impedance of the amplifier when a low-power s.w.r. indicator, such as a resistance bridge, is used. See formula in text far calculating value. Standing-wave indicator SWR is inserted only while line is made flat.

objective is to load the driver plate circuit so that the desired amplifier grid excitation is obtained without exceeding the plate-input ratings of the driver tube.

Driving Impedance

The grid-current flow that results when the grid is driven positive in respect to the cathode over a portion of the excitation cycle represents an average resistance across which the exciting voltage must be developed by the driver. In other words, this is the load resistance into which the driver plate circuit must be coupled. The approximate grid input resistance is given by:

Input impedance (ohms)
$$= \frac{driving \ power \ (watts)}{d.c. \ grid \ current \ (ma.)^2} \times 620,000$$

For normal operation, the driving power and grid current may be taken from the tube tables.

Since the grid input resistance is a matter of a few thousand ohms, an impedance step-down is necessary if the grid is to be fed from a low-impedance transmission line. This can be done by the use of a tank as an impedance-transforming device in the grid circuit of the amplifier as shown in Fig. 6-19. This coupling system may be considered either as simply a means of obtaining mutual inductance between the two tank coils, or as a low-impedance transmission line. If the line is longer than a small fraction of a wave length, and if a s.w.r. bridge is available, the line is more easily handled by adjusting it as a matched transmission line.

Inductive Link Coupling with Flat Line

In adjusting this type of line, the object is to make the s.w.r. on the line as low as possible over as wide a band of frequencies as possible so that power can be transferred over this range without retuning. It is assumed that the output coupling considerations discussed earlier have been observed in connection with the driver plate

circuit. So far as the amplifier grid circuit is concerned, the controlling factors are the Q of the tuned grid circuit, L_2C_2 , (see Fig. 6-20) the inductance of the coupling coil, L_4 , and the degree of coupling between L_2 and L_4 . Variable coupling between the coils is convenient, but not strictly necessary if one or both of the other factors can be varied. An s.w.r. indicator (shown as "SWR" in the drawing) is essential. An indi-

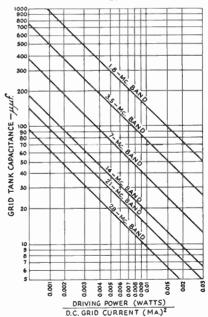


Fig. 6-20—Chart showing required grid tank capacitance for a Q of 12. To use, divide the driving power in watts by the square of the d.c. grid current in milliamperes and proceed as described under Fig-6-9. Driving power and grid current may be taken from the tube tables. When a split-stator capacitor is used in a balanced grid circuit, the capacitance of each section may be half that shown.

cator such as the "Micromatch" (a commercially available instrument) may be connected as shown and the adjustments made under actual operating conditions; that is, with full power applied to the amplifier grid.

Assuming that the coupling is adjustable, start with a trial position of L_4 with respect to L_2 , and adjust C_2 for the lowest s.w.r. Then change the coupling slightly and repeat. Continue until the s.w.r. is as low as possible; if the circuit constants are in the right region is should not be difficult to get the s.w.r. down to 1 to 1. The Q of the tuned grid circuit should be designed to be at least 10, and if it is not possible to get a very low s.w.r. with such a grid circuit the probable reason is that L_4 is too small. Maximum coupling, for a given degree of physical coupling will occur when the inductance of L_4 is such that its reactance at the operating frequency is equal to the characteristic impedance of the link line. The reactance can be calculated as described in the chapter on electrical fundamentals if the inductance is known; the inductance can either be calculated from the formula in the same chapter or measured as described in the chapter on measurements.

Once the s.w.r, has been brought down to 1 to 1, the frequency should be shifted over the band so that the variation in s.w.r. can be observed, without changing C_2 or the coupling between L_2 and L4. If the s.w.r. rises rapidly on either side of the original frequency the circuit can be made "flatter" by reducing the Q of the tuned grid circuit. This may be done by decreasing C2 and correspondingly increasing L2 to maintain resonance, and by tightening the coupling between L_2 and L4, going through the same adjustment process again. It is possible to set up the system so that the s.w.r. will not exceed 1.5 to 1 over, for example, the entire 7-Mc. band and proportionately on other bands. Under these circumstances a single setting will serve for work anywhere in the band, with essentially constant power transfer from the line to the power-amplifier grids.

If the coupling between L_2 and L_4 is not adjustable the same result may be secured by varying the L/C ratio of the tuned grid circuit — that is, by varying its Q. If any difficulty is encountered it can be overcome by changing the number of turns in L_4 until a match is secured. The two coils should be tightly coupled.

When a resistance-bridge type s.w.r. indicator (see measurements chapter) is used it is not possible to put the full power through the line when making adjustments. In such case the operating conditions in the amplified grid circuit can be simulated by using a carbon resistor (½ or 1 watt size) of the same value as the calculated amplifier grid impedance, connected as indicated by the arrows in Fig. 6-19. In this case the amplifier tube must be operated "cold"— without filament or heater power. The adjustment process is the same as described above, but with the driver power reduced to a value suitable for operating the s.w.r. bridge.

When the grid coupling system has been ad-

justed so that the s.w.r. is close to 1 to 1 over the desired frequency range, it is certain that the power put into the link line will be delivered to the grid circuit. Coupling will be facilitated if the line is tuned as described under the earlier section on output coupling systems.

Link Feed with Unmatched Line

When the system is to be treated without regard to transmission-line effects, the link line must not offer appreciable reactance at the operating frequency. Any appreciable reactance will in effect reduce the coupling, making it impossible to transfer sufficient power from the driver to the amplifier grid circuit. Coaxial cables especially have considerable capacitance for even short lengths and it may be more desirable to use a spaced line, such as Twin-Lead, if the radiation can be tolerated.

The reactance of the line can be nullified only by making the link resonant. This may require changing the number of turns in the link coils, the length of the line, or the insertion of a tuning capacitance. Since the s.w.r. on the link line may be quite high, the line losses increase because of the greater current, the voltage increase may be sufficient to cause a breakdown in the insulation of the cable and the added tuned circuit makes adjustment more critical with relatively small changes in frequency.

These troubles may not be encountered if the link line is kept very short for the highest frequency. A length of 5 feet or more may be tolerable at 3.5 Mc., but a length of a foot at 28 Mc. may be enough to cause serious effects on the functioning of the system.

Adjusting the coupling in such a system must necessarily be largely a matter of cut and try. If the line is short enough so as to have negligible reactance, the coupling between the two tank circuits will increase within limits by adding turns to the link coils, or by coupling the link coils more tightly, if possible, to the tank coils. If it is impossible to change either of these, a variable capacitor of 300 µµf. may be connected in series with or in parallel with the link coil at the driver end of the line, depending upon which connection is the most effective.

If coaxial line is used, the capacitor should be connected in series with the inner conductor. If the line is long enough to have appreciable reactance, the variable capacitor is used to resonate the entire link circuit.

The size of the link coils and the length of the line, as well as the size of the capacitor, will affect the resonant frequency, and it may take an adjustment of all three before the capacitor will show a pronounced effect on the coupling.

When the system has been made resonant, coupling may be adjusted by varying the link capacitor.

Simple Capacitive Interstage Coupling

The capacitive system of Fig. 6-21A is the simplest of all coupling systems. In this circuit, the plate tank circuit of the driver, C_1L_1 , serves

Interstage Coupling


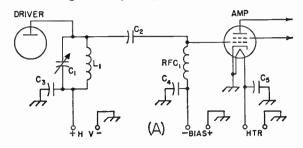


Fig. 6-21—Capacitive-coupled amplifiers.

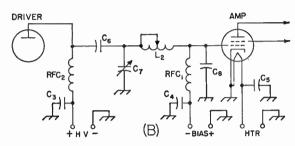A—Simple capacitive coupling. B—Pi-section coupling.



C₁-Driver plate tank capacitor—see text and Fig. 6-9 for capacitance, Fig. 6-33 for voltage rating.

C₂—Coupling capacitor—50 to 150 $\mu\mu$ f. mica, as necessary for desired coupling. Voltage rating sum of driver plate and amplifier biasing voltages, plus safety factor.

C₃-Driver plate bypass capacitar-0.001-\mu f. disk ceramic or mica. Voltage rating same as plate voltage.

C₁-Grid bypass-0.001-\(mu f\), disk ceramic.

C₅-Heater bypass-0.001-\(mu f\), disk ceramic.

C₀-Driver plate blocking capacitor-0.001-µf. disk ceramic or mica. Voltage rating same as C₂.

 C_7 —Pi-section input capacitor—see text referring to Fig. 6-12 for capacitance. Voltage rating—see Fig. 6-33A. C_8 —Pi-section output capacitor—100- $\mu\mu$ f. mica. Voltage rating same as driver plate voltage plus safety factor. I.—To resonate at operating frequency with C_1 . See LC chart and inductance formula in electrical-laws chapter.

L₁—To resonate at operating frequency with C₁. See LC chart and inductance formula in electrical-laws chapter, or use ARRL Lightning Calculator.

L₂—Pi-section inductor—See Fig. 6-12. Approx. same as L₁.

RFC1-Grid r.f. choke-2.5-mh.

RFC2-Driver plate r.f. choke-2.5 mh.

also as the grid tank of the amplifier. Although it is used more frequently than any other system, it is less flexible and has certain limitations that must be taken into consideration.

The two stages cannot be separated physically any appreciable distance without involving loss in transferred power, radiation from the coupling lead and the danger of feedback from this lead. Since both the output capacitance of the driver tube and the input capacitance of the amplifier are across the single circuit, it is sometimes difficult to obtain a tank circuit with a sufficiently low Q to provide an efficient circuit at the higher frequencies. The coupling can be varied by altering the capacitance of the coupling capacitor, C2. The driver load impedance is the sum of the amplifier grid resistance and the reactance of the coupling capacitor in series, the coupling capacitor serving simply as a series reactor. The driver load resistance increases with a decrease in the capacitance of the coupling capacitor.

When the amplifier grid impedance is lower than the optimum load resistance for the driver, a transforming action is possible by tapping the grid down on the tank coil, but this is not recommended because it invariably causes an increase in v.h.f. harmonics and sometimes sets up a parasitic circuit

So far as coupling is concerned, the *Q* of the circuit is of little significance. However, the other considerations discussed earlier in connection with tank-circuit *Q* should be observed.

Pi-Network Interstage Coupling

A pi-section tank circuit, as shown in Fig. 6-21B, may be used as a coupling device between screen-grid amplifier stages. The circuit can also be considered a coupling arrangement with the grid of the amplifier tapped down on the circuit by means of a capacitive divider. In contrast to the tapped-coil method mentioned previously, this system will be very effective in reducing v.h.f. harmonics, because the output capacitor, C_8 , provides a direct capacitive shunt for harmonics across the amplifier grid circuit.

To be most effective in reducing v.h.f. harmonics, C_8 should be a mica capacitor connected directly across the tube-socket terminals. Tapping down on the circuit in this manner also helps to stabilize the amplifier at the operating frequency because of the grid-circuit loading

provided by C_8 . For the purposes both of stability and harmonic reduction, experience has shown that a value of 100 $\mu\mu$ f. for C_8 usually is sufficient. In general, C_7 and L_2 should have values approximating the capacitance and inductance used in a conventional tank circuit. A reduction in the inductance of L_2 results in an increase in coupling because C_7 must be increased to retune the circuit to resonance. This changes the ratio of C_7 to C_8 and has the effect of

moving the grid tap up on the circuit. Since the coupling to the grid is comparatively loose under any condition, it may be found that it is impossible to utilize the full power capability of the driver stage. If sufficient excitation cannot be obtained, it may be necessary to raise the plate voltage of the driver, if this is permissible. Otherwise a larger driver tube may be required. As shown in Fig. 6-21B, parallel driver plate feed and amplifier grid feed are necessary.

R.F. POWER AMPLIFIER CIRCUITRY

STABILIZING AMPLIFIERS

A straight amplifier operates with its input and output circuits tuned to the same frequency. Therefore, unless the coupling between these two circuits is brought to the necessary minimum, the amplifier will oscillate as a tuned-plate tuned-grid circuit. Care should be used in arranging components and wiring of the two circuits so that there will be negligible opportunity for coupling external to the tube itself. Complete shielding between input and output circuits usually is required. All r.f. leads should be kept as short as possible and particular attention should be paid to the r.f. return paths from plate and grid tank circuits to cathode. In general, the best arrangement is one in which the cathode connection to ground, and the plate tank circuit are on the same side of the chassis or other shielding. The "hot" lead from the grid tank (or driver plate tank) should be brought to the socket through a hole in the shielding. Then when the grid tank capacitor or bypass is grounded, a return path through the hole to cathode will be encouraged, since transmission-line characteristics are simulated.

A check on external coupling between input and output circuits can be made with a sensitive indicating device, such as the one diagrammed in Fig. 6-22. The amplifier tube is removed from its socket and if the plate terminal is at the


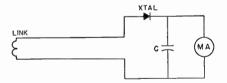



Fig. 6-22—Circuit of sensitive neutralizing indicator. Xtal is a 1N34 crystal detector, MA a 0-1 directcurrent milliammeter and C a 0.001-μf. mica bypass capacitor.

socket, it should be disconnected. With the driver stage running and tuned to resonance, the indicator should be coupled to the output tank coil and the output tank capacitor tuned for any indication of r.f. feedthrough. Experiment with shielding and rearrangement of parts will show whether the isolation can be improved.

Screen-Grid Tube Neutralizing Circuits

The plate-grid capacitance of screen-grid tubes

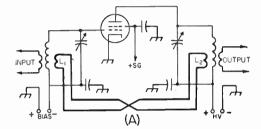

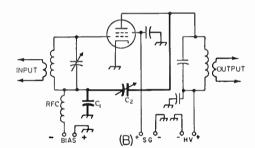

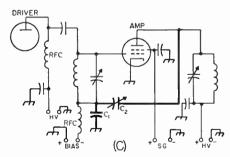


Fig. 6-23—Screen-grid neutralizing circuits. A—Inductive neutralizing. B-C—Capacitive neutralizing.

C₁—Grid bypass capacitor—approx. 0.001-\(\mu t\). mica.

Voltage rating same as biasing voltage in

B, same as driver plate voltage in C.

C₂—Neutralizing capacitor—approx. 2 to 10 $\mu\mu$ f.—see text. Voltage rating same as amplifier plate voltage for c.w., twice this value for plate modulation.

L₁, L₂—Neutralizing link—usually a turn or two will be sufficient.

is reduced to a fraction of a micromicrofarad by the interposed grounded screen. Nevertheless, the power sensitivity of these tubes is so great that only a very small amount of feedback is necessary to start oscillation. To assure a stable amplifier, it is usually necessary to load the grid circuit, or to use a neutralizing circuit.

Fig. 6-23A shows how a screen-grid amplifier may be neutralized by the use of an inductive link line coupling the input and output tank circuits in proper phase. If the initial connection proves to be incorrect, connections to one of the link coils should be reversed. Neutralizing is adjusted by changing the distance between the link coils and the tank coils. In the case of capacitive coupling between stages, one of the link coils will be coupled to the plate tank coil of the driver stage.

A capacitive neutralizing system for screengrid tubes is shown in Fig. 6-23B. C_2 is the neutralizing capacitor. The capacitance should be chosen so that at some adjustment of C_2 ,

$$\frac{C_2}{C_1} = \frac{Tube\ grid-plate\ capacitance\ (or\ C_{gp})}{Tube\ input\ capacitance\ (or\ C_{IN})}$$

The tube interelectrode capacitances $C_{\rm gp}$ and $C_{\rm IN}$ are given in the tube tables in the last chapter. The grid-cathode capacitance must include all strays directly across the tube capacitance, including the capacitance of the tuning-capacitor stator to ground. This may amount to 5 to 20 $\mu\mu$ f. In the case of capacitance coupling, as shown in Fig. 6-23C, the output capacitance of the driver tube must be added to the grid-cathode capacitance of the amplifier in arriving at the value of C_2 . If C_2 works out to an impractically large or small value, C_1 can be changed to compensate by using combinations of fixed mica capacitors in parallel.

Neutralizing Adjustment

The procedure in neutralizing is essentially the same for all types of tubes and circuits. The filament of the amplifier tube should be lighted and excitation from the preceding stage fed to the grid circuit. Both screen and plate voltages should be disconnected at the transmitter terminals.

The immediate objective of the neutralizing process is reducing to a minimum the r.f. driver voltage fed from the input of the amplifier to its output circuit through the grid-plate capacitance of the tube. This is done by adjusting carefully, bit by bit, the neutralizing capacitor or link coils until an r.f. indicator in the output circuit reads minimum.

The device shown in Fig. 6-22 makes a sensitive neutralizing indicator. The link should be coupled to the output tank coil at the low-potential or "ground" point. Care should be taken to make sure that the coupling is loose enough at all times to prevent burning out the meter or the rectifier. The plate tank capacitor should be readjusted for maximum reading after each change in neutralizing.

The grid-current meter may also be used as a neutralizing indicator. With plate and screen voltages removed as described above, there will be a change in grid current as the plate tank circuit is tuned through resonance. The neutralizing capacitor should be adjusted until this deflection is brought to a minimum. As a final adjustment, plate and screen voltages should be applied and the neutralizing capacitance adjusted to the point where minimum plate current, maximum grid current and maximum screen current occur simultaneously. An increase in grid current when the plate tank circuit is tuned slightly on the high-frequency side of resonance indicates that the neutralizing capacitance is too small. If the increase is on the low-frequency side, the neutralizing capacitance is too large. When neutralization is complete, there should be a slight decrease in grid current on either side of resonance.

Grid Loading

The use of a neutralizing circuit may often be avoided by loading the grid circuit if the driving stage has some power capability to spare. Loading by tapping the grid down on the grid tank coil (or the plate tank coil of the driver in the case of capacitive coupling), or by a resistor from grid to cathode is effective in stabilizing an amplifier, but either device may increase v.h.f. harmonics. The best loading system is the use of a pi-section filter, as shown in Fig. 6-21B. This circuit places a capacitance directly between grid and cathode. This not only provides the desirable loading, but also a very effective capacitive short for v.h.f. harmonics. A 100-μμf. mica capacitor for C8, wired directly between tube terminals, will usually provide sufficient loading to stabilize the amplifier.

V.H.F. Parasitic Oscillation

Parasitic oscillation in the v.h.f. range will take place in almost every r.f. power amplifier. To test for v.h.f. parasitic oscillation, the grid tank coil (or driver tank coil in the case of ca-

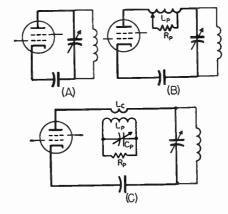


Fig. 6-24—A—Usual parasitic circuit. B—Resistive loading of parasitic circuit. C—Inductive coupling of loading resistance into parasitic circuit.

pacitive coupling) should be short-circuited with a clip lead. This is to prevent any possible t.g.t.p. oscillation at the operating frequency which might lead to confusion in identifying the parasitic. Any fixed bias should be replaced with a grid leak of 10,000 to 20,000 ohms. All load on the output of the amplifier should be disconnected. Plate and screen voltages should be reduced to the point where the rated dissipation is not exceeded. If a Variac is not available, voltage may be reduced by a 115-volt lamp in series with the primary of the plate transformer.

With power applied only to the amplifier under test, a search should be made by adjusting the input capacitor to several settings, including minimum and maximum, and turning the plate capacitor through its range for each of the gridcapacitor settings. Any grid current, or any dip or flicker in plate current at any point, indicates oscillation. This can be confirmed by an indicating absorption wavemeter tuned to the frequency of the parasitic and held close to the plate lead of the tube.

The heavy lines of Fig. 6-24A show the usual parasitic tank circuit, which resonates, in most cases, between 150 and 200 Mc. For each type of tetrode, there is a region, usually below the parasitic frequency, in which the tube will be selfneutralized. By adding the right amount of inductance to the parasitic circuit, its resonant frequency can be brought down to the frequency at which the tube is self-neutralized. However, the resonant frequency should not be brought down so low that it falls close to TV Channel 6 (88 Mc.). From the consideration of TVI, the circuit may be loaded down to a frequency not lower than 100 Mc. If the self-neutralizing frequency is below 100 Mc., the circuit should be loaded down to somewhere between 100 and 120 Mc, with inductance. Then the parasitic can be suppressed by loading with resistance, as shown in Fig. 6-24B. A coil of 4 or 5 turns, 1/4 inch in diameter, is a good starting size. With the tank capacitor turned to maximum capacitance, the circuit should be checked with a g.d.o. to make sure the resonance is above 100 Mc. Then, with the shortest possible leads, a noninductive 100ohm 1-watt resistor should be connected across the entire coil. The amplifier should be tuned up to its highest-frequency band and operated at low voltage. The tap should be moved a little at a time to find the minimum number of turns required to suppress the parasitic. Then voltage should be increased until the resistor begins to feel warm after several minutes of operation, and the power input noted. This input should be compared with the normal input and the power rating of the resistor increased by this proportion; i.e., if the power is half normal, the wattage rating should be doubled. This increase is best made by connecting 1-watt carbon resistors in parallel to give a resultant of about 100 olms. As power input is increased, the parasitic may start up again, so power should be applied only momentarily until it is made certain that the parasitic is still suppressed. If the parasitic starts

up again when voltage is raised, the tap must be moved to include more turns. So long as the parasitic is suppressed, the resistors will heat up only from the operating-frequency current.

Since the resistor can be placed across only that portion of the parasitic circuit represented by $L_{\mathbb{P}}$, the latter should form as large a portion of the circuit as possible. Therefore, the tank and bypass capacitors should have the lowest possible inductance and the leads shown in heavy lines should be as short as possible and of the heaviest practical conductor. This will permit L_p to be of maximum size without tuning the circuit below the 100-Mc. limit.

Another arrangement that has been used successfully is shown in Fig. 6-24C. A small turn or two is inserted in place of L_p and this is coupled to a circuit tuned to the parasitic frequency and loaded with resistance. The heavy-line circuit should first be checked with a g.d.o. Then the loaded circuit should be tuned to the same frequency and coupled in to the point where the parasitic ceases. The two coils can be wound on the same form and the coupling varied by sliding one of them. Slight retuning of the loaded circuit may be required after coupling. Start out with low power as before, until the parasitic is suppressed. Since the loaded circuit in this case carries much less operating-frequency current, a single 100-ohm 1-watt resistor will often be sufficient and a 30-µµf. mica trimmer should serve as the tuning capacitor, C_p .

Low-Frequency Parasitic Oscillation

The screening of most transmitting screen-grid tubes is sufficient to prevent low-frequency parasitic oscillation caused by resonant circuits set up by r.f. chokes in grid and plate circuits. Should this type of oscillation (usually between 200 and 1200 kc.) occur, see paragraph under triode amplifiers.

PARALLEL-TUBE AMPLIFIERS

The circuits for parallel-tube amplifiers are the same as for a single tube, similar terminals of the tubes being connected together. The grid impedance of two tubes in parallel is half that of a single tube. This means that twice the grid tank capacitance shown in Fig. 6-20 should be used for the same Q.

The plate load resistance is halved so that the plate tank capacitance for a single tube (Fig. 6-10) also should be doubled. The total grid current will be doubled, so to maintain the same grid bias, the grid-leak resistance should be half that used for a single tube. The required driving power is doubled. The capacitance of a neutralizing capacitor, if used, should be doubled and the value of the screen dropping resistor should be cut in half.

In treating parasitic oscillation, it is often necessary to use a choke in each plate lead, rather than one in the common lead to avoid building in a push-pull type of v.h.f. circuit, a factor in obtaining efficient operation at higher frequencies.

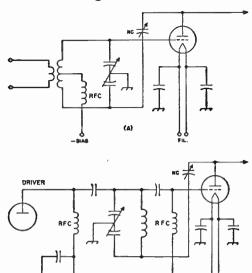


Fig. 6-25—When a pi-network output circuit is used with a triode, a balanced grid circuit must be provided for neutralizing. A—Inductive-link input. B—Capacitive input caupling.

PUSH-PULL AMPLIFIERS

Basic push-pull circuits are shown in Fig. 6-26C and D. Amplifiers using this circuit are cumbersome to bandswitch and consequently are not very popular below 30 Mc. However, since the push-pull configuration places tube input and output capacitances in series, the circuit is widely used at 50 Mc. and higher.

TRIODE AMPLIFIERS

Circuits for triode amplifiers are shown in Fig. 6-26. Neglecting references to the screen, all of the foregoing information applies equally well to triodes. All triode straight amplifiers must be neutralized, as Fig. 6-26 indicates. From the tube tables, it will be seen that triodes require considerably more driving power than screengrid tubes. However, they also have less power sensitivity, so that greater feedback can be tolerated without the danger of instability.

Low-Frequency Parasitic Oscillation

When r.f. chokes are used in both grid and plate circuits of a triode amplifier, the split-stator tank capacitors combine with the r.f. chokes to form a low-frequency parasitic circuit, unless the amplifier circuit is arranged to prevent

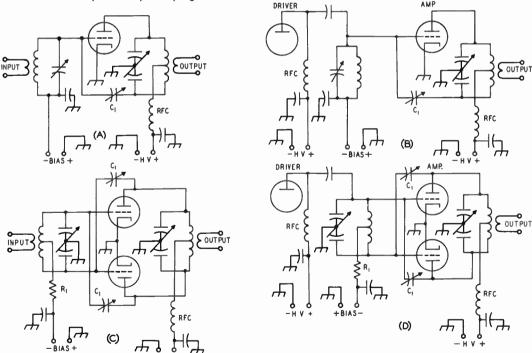


Fig. 6-26—Triade amplifier circuits. A—Link coupling, single tube. B—Capacitive coupling, single tube. C—Link coupling, push-pull. D—Capacitive coupling, push-pull. Aside from the neutralizing circuits, which are mandatory with triodes, the circuits are the same as for screen-grid tubes, and should have the same values throughout. The neutralizing capacitor, C₁, should have a capacitance somewhat greater than the grid-plate capacitance af the tube. Voltage rating should be twice the d.c. plate valtage for c.w., or four times for plate modulation, plus safety factor. The resistance R₁ should be at least 100 ohms and it may consist of part or preferably all of the grid leak. Far other component values, see similar screen-grid diagrams.

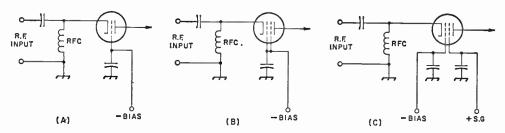


Fig. 6-27—A—Graunded-grid triade input circuit. B—Tetrade input circuit with grid and screen directly in parallel. C—Tetrade circuit with d.c. valtage applied to the screen. Plate circuits are conventional.

it. In the circuit of Fig. 6-26B, the amplifier grid is series fed and the driver plate is parallel fed. For low frequencies, the r.f. choke in the driver plate circuit is shorted to ground through the tank coil. In Figs. 6-26C and D, a resistor is substituted for the grid r.f. choke. This resistance should be at least 100 ohms. If any grid-leak resistance is used for biasing, it should be substituted for the 100-ohm resistor.

Triode Amplifiers with Pi-Network Output

Pi-network output tanks, designed as described earlier for screen-grid tubes, may also be used with triodes. However, in this case, a balanced input circuit must be provided for neutralizing. Fig. 6-25A shows the circuit when inductive-link input coupling is used, while B shows the circuit to be used when the amplifier is coupled capacitively to the driver. Pi-network circuits cannot be used in *both* input and output circuits, since no means is provided for neutralizing.

GROUNDED-GRID AMPLIFIERS

Fig. 6-27A shows the input circuit of a grounded-grid triode amplifier. In configuration it is similar to the conventional grounded-cathode circuit except that the grid, instead of the cathode, is at ground potential. An amplifier of this type is characterized by a comparatively low input impedance and a relatively high driver-power requirement. The additional driver power is not consumed in the amplifier but is "fed through" to the plate circuit where it combines with the normal plate output power. The total r.f. power output is the sum of the driver and amplifier output powers less the power normally required to drive the tube in a grounded-cathode circuit.

Positive feedback is from plate to cathode through the plate-cathode, or plate-filament, capacitance of the tube. Since the grounded grid is interposed between the plate and cathode, this capacitance is very small, and neutralization usually is not necessary.

A disadvantage of the grounded-grid circuit is that the cathode must be isolated for r.f. from ground. This presents a practical difficulty especially in the case of a filament-type tube whose filament current is large. Another disadvantage in plate-modulated phone operation is that the driver power fed through to the output is not modulated.

The chief application for grounded-grid amplifiers in amateur work at frequencies below 30 Mc. is in the case where the available driving power far exceeds the power that can be used in driving a conventional grounded-cathode amplifier.

D.c. electrode voltages and currents in grounded-grid triode-amplifier operation are the same as for grounded-cathode operation. Approximate values of driving power, driving impedance, and total power output in Class C operation can be calculated as follows, using information normally provided in tube data sheets. R.m.s. values are of the fundamental components:

$$E_{p} = r.m.s. \text{ value of r.f. plate voltage}$$

$$= \frac{d.c. \text{ plate volts} + d.c. \text{ bias volts} - \frac{peak \text{ r.f. grid volts}}{1.41}$$

$$I_{p} = r.m.s. \text{ value of r.f. plate current}$$

$$= \frac{rated \text{ power output watts}}{E_{p}}$$

$$E_g = r.m.s.$$
 value of grid driving voltage
= $\frac{peak \ r.f. \ grid \ volts}{1.41}$

$$I_g = r.m.s.$$
 value of r.f. grid current
$$= \frac{rated \ driving \ power \ watts}{F_{rr}}$$

Then,

Driving power (watts) = $E_g (I_p + I_g)$

Driving impedance (ohms) =
$$\frac{E_g}{I_g + I_D}$$

Power fed through from driver stage (watts) = $E_{\rm g}I_{\rm p}$ Total power output (watts) = $I_{\rm p}$ ($E_{\rm g}+E_{\rm p}$)

Screen-grid tubes are also used sometimes in grounded-grid amplifiers. In some cases, the screen is simply connected in parallel with the grid, as in Fig. 6-27B, and the tube operates as a high- μ triode. In other cases, the screen is bypassed to ground and operated at the usual d.c. potential, as shown at C. Since the screen is still in parallel with the grid for r.f., operation is very much like that of a triode except that the positive voltage on the screen reduces driver-power requirements. Since the information usually fur-

Grounded-Grid Amplifiers

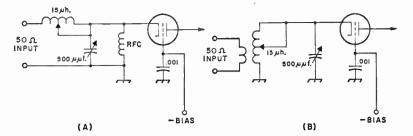


Fig. 6-28—Two
methods of coupling a low-impedance driver to a
grounded-grid input. A—L network.
B — Link - coupled
tank circuit.

nished in tube-data sheets does not apply to triode-type operation, operating conditions are usually determined experimentally. In general, the bias is adjusted to produce maximum output (within the tube's dissipation rating) with the driving power available.

Fig. 6-28 shows two methods of coupling a grounded-grid amplifier to the 50-ohm output of an existing transmitter. At A an L network is used, while a conventional link-coupled tank is shown at B. The values shown will be approximately correct for most triode amplifiers operating at 3.5 Mc. Values should be cut in half each time frequency is doubled, i.e., 250 $\mu\mu$ f. and 7.5 μ h. for 7 Mc., etc.

Filament Isolation

Since the filament or cathode of the grounded-grid amplifier tube operates at some r.f. potential above ground, it is necessary to isolate the filament from the power line. In the case of low-power tubes with indirectly heated cathodes, it is sometimes feasible to depend on the small capacitance existing between the heater and cathode, although it is preferable to provide additional isolation.


In Fig. 6-29A, isolation is provided by a special low-capacitance filament transformer. RFC_1 carries only the cathode current. However, since transformers of this type are not generally available, other means must usually be employed.


In Fig. 6-29B, chokes are used to isolate the filament from the filament transformer. The reactance of the chokes should be several times the input impedance of the amplifier and must be wound with conductor of sufficient size to carry the filament current. It is usually necessary to use a transformer delivering more than the rated filament voltage to compensate the voltage drop across the chokes. In Fig. 6-29C, r.f. chokes are placed in the primary side of the transformer. This reduces the current that the chokes must handle, but the filament transformer must be mounted so that it is spaced from the chassis and other grounded metal to minimize the capacitance of the transformer to ground, RFC1 carries cathode current only.


In the case of the input circuit of Fig. 6-28B, it is sometimes feasible to wind the tank inductor with two conductors in parallel, and feed the filament voltage to the tube through the two conductors, as shown in Fig. 6-29D. This arrangement does not lend itself well to bandchanging, however.


Fig. 6-29—Methods of isolating filament from ground.

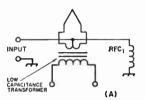A—Special low-capacitance filament transformer. B—
R.f. chokes in filament circuit. C—R.f. chokes in transformer primary. D—Filament fed through input tank inductor.



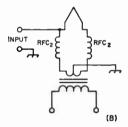

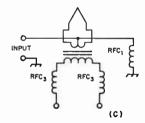

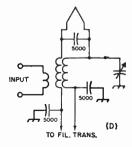

FREQUENCY MULTIPLIERS

Single-Tube Multiplier

Output at a multiple of the frequency at which it is being driven may be obtained from an amplifier stage if the output circuit is tuned to a harmonic of the exciting frequency instead of to the fundamental. Thus, when the frequency at the grid is 3.5 Mc., output at 7 Mc., 10.5 Mc., 14 Mc., etc., may be obtained by tuning the plate tank circuit to one of these frequencies. The circuit otherwise remains the same as that for a straight amplifier, although some of the values and operating conditions may require change for maximum multiplier efficiency.

Efficiency in a single- or parallel-tube multiplier comparable with the efficiency obtainable when operating the same tube as a straight amplifier involves decreasing the operating angle in proportion to the increase in the order of frequency multiplication. Obtaining output comparable with that possible from the same tube as a straight amplifier involves greatly increasing the plate voltage. A practical limit as to efficiency and output within normal tube ratings is reached when the multiplier is operated at maximum permissible plate voltage and maximum permissible grid current. The plate current should be reduced as necessary to limit the dissipation to the rated value by increasing the bias. High efficiency in multipliers is not often required in practice, since the purpose is usually served if the frequency multiplication is obtained without an appreciable gain in power in the stage.

Multiplications of four or five sometimes are used to reach the bands above 28 Mc. from a lower-frequency crystal, but in the majority of lower-frequency transmitters, multiplication in a single stage is limited to a factor of two or three, because of the rapid decline in practicably obtainable efficiency as the multiplication factor is increased. Screen-grid tubes make the best frequency multipliers because their high power-sensitivity makes them easier to drive properly than triodes.

Since the input and output circuits are not tuned close to the same frequency, neutralization usually will not be required. Instances may be encountered with tubes of high trans-conductance, however, when a doubler will oscillate in t.g.t.p. fashion, requiring neutralization. The link neutralizing system of Fig. 6-23A is convenient in such a contingency.

Push-Push Multipliers

A two-tube circuit which works well at even harmonics, but not at the fundamental or odd harmonics, is shown in Fig. 6-30. It is known as the push-push circuit. The grids are connected in push-pull while the plates are connected in parallel. The efficiency of a doubler using this circuit may approach that of a straight amplifier, because there is a plate-current pulse for each cycle of the output frequency.

This arrangement has an advantage in some applications. If the heater of one tube is turned off, its grid-plate capacitance, being the same as that of the remaining tube, serves to neutralize

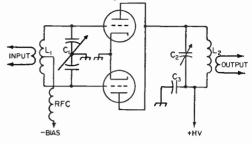


Fig. 6-30—Circuit of a push-push frequency multiplier for even harmonics.

C₁L₁ and C₂L₂—See text.

C₃-Plate bypass-0.001-µf. disk ceramic or mica.

Voltage rating equal to plate voltage plus safety factor.

RFC-2.5-mh. r.f. choke.

the circuit. Thus provision is made for either straight amplification at the fundamental with a single tube, or doubling frequency with two tubes as desired.

The grid tank circuit is tuned to the frequency of the driving stage and should have the same constants as indicated in Fig. 6-20 for balanced grid circuits. The plate tank circuit is tuned to an even multiple of the exciting frequency, and should have the same values as a straight amplifier for the harmonic frequency (see Fig. 6-10), bearing in mind that the total plate current of both tubes determines the \mathcal{C} to be used.

Push-Pull Multiplier

A single- or parallel-tube multiplier will deliver output at either even or odd multiples of the exciting frequency. A push-pull multiplier does not work satisfactorily at even multiples because even harmonics are largely canceled in the output. On the other hand, amplifiers of this type work well as triplers or at other odd harmonics. The operating requirements are similar to those for single-tube multipliers, the plate tank circuit being tuned, of course, to the desired odd harmonic frequency.

METERING

Fig. 6-31 shows how a voltmeter and milliammeter should be connected to read various voltages and currents. Voltmeters are seldom installed permanently, since their principal use is in preliminary checking. Also, milliammeters are not normally installed permanently in all of the positions shown. Those most often used are the ones reading grid current and plate current, or grid current and cathode current.

Milliammeters come in various current ranges. Current values to be expected can be taken from the tube tables and the meter ranges selected accordingly. To take care of normal overloads and pointer swing, a meter having a current

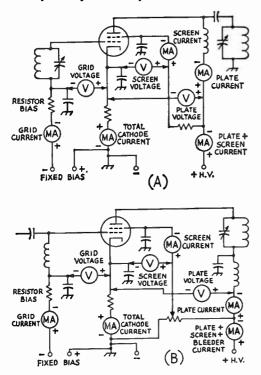


Fig. 6-31—Diagrams showing placement of voltmeter and milliammeter to obtain desired measurements. A—Series grid feed, parallel plate feed and series screen voltage-dropping resistor. B—Parallel grid feed, series plate feed and screen valtage divider.

range of about twice the normal current to be expected should be selected.

Meter Installation

Grid-current meters connected as shown in Fig. 6-31 and meters connected in the cathode circuit need no special precautions in mounting on the transmitter panel so far as safety is concerned. However, milliammeters having zeroadjusting screws on the face of the meter should be recessed behind the panel so that accidental contact with the adjusting screw is not possible, if the meter is connected in any of the other positions shown in Fig. 6-31. The meter can be mounted on a small subpanel attached to the front panel with long screws and spacers. The meter opening should be covered with glass or celluloid. Illuminated meters make reading easier. Reference should also be made to the TVI chapter of this Handbook in regard to wiring and shielding of meters to suppress TVI.

Meter Switching

Milliammeters are expensive items and therefore it is seldom feasible to provide even gridcurrent and plate-current meters for all stages. The exciter stages in a multistage transmitter often do not require metering after initial adjustments. It is common practice to provide a meter-switching system by which a single milliammeter may be switched to read currents in as many circuits as desired. Such a meter-switching circuit is shown in Fig. 6-32. The resistors, R, are connected in the various circuits in place of the milliammeters shown in Fig. 6-31. Since the resistance of R is several times the internal resistance of the milliammeter, it will have no practical effect upon the reading of the meter.

When the meter must read currents of widely differing values, a meter with a range sufficiently low to accommodate the lowest values of current to be measured may be selected. In the circuits in which the current will be above the scale of the meter, the resistance of R can be adjusted to a lower value which will give the meter reading a multiplying factor. (See chapter on Measurements.) Care should be taken to observe proper polarity in making the connections between the resistors and the switch.

A variation of the foregoing method uses the low-current meter as a voltmeter to measure the voltage drop across various low resistances placed in the lines where the currents are to be measured. Both the line resistor and the higher resistance running to the meter (corresponding to a normal voltmeter multiplier) can be varied, to give a wide range for the single meter. Standard values of resistors can usually be found for any desired range.

AMPLIFIER ADJUSTMENT

Earlier sections in this chapter have dealt with the design and adjustment of input (grid) and output (plate) coupling systems, the stabilization of amplifiers, and the methods of obtaining the

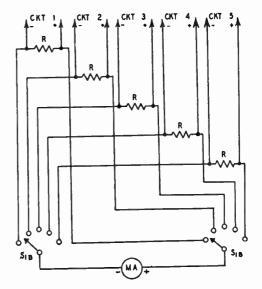


Fig. 6-32—Switching a single milliammeter. The resistors, R, should be 10 to 20 times the internal resistance of the meter; 47 ohms will usually be satisfactary. S_1 is a 2-section rotary switch. Its insulation should be ceramic for high voltages, and an insulating coupling should olways be used between shaft and control.

required electrode voltages. Reference to these sections should be made as necessary in following a procedure of amplifier adjustment.

The objective in the adjustment of an intermediate amplifier stage is to secure adequate excitation to the following stage. In the case of the output or final amplifier, the objective is to obtain maximum power output to the antenna. In both cases, the adjustment must be consistent with the tube ratings as to voltage, current and dissipating ratings.

Adequate drive to a following amplifier is normally indicated when rated grid current in the following stage is obtained with the stage operating at rated bias, the stage loaded to rated plate current, and the driver stage tuned to resonance. In a final amplifier, maximum output is normally indicated when the output coupling is adjusted so that the amplifier tube draws rated plate current when it is tuned to resonance.

Resonance in the plate circuit is normally indicated by the dip in plate-current reading as the plate tank capacitor is tuned through its

range. When the stage is unloaded, or lightly loaded, this dip in plate current will be quite pronounced. As the loading is increased, the dip will become less noticeable. See Fig. 6-4. However, in the base of a screen-grid tube whose screen is fed through a series resistor, maximum output may not be simultaneous with the dip in plate current. The reason for this is that the screen current varies widely as the plate circuit is tuned through resonance. This variation in screen current causes a corresponding variation in the voltage drop across the screen resistor. In this maximum output may occur at an adjustment that results in an optimum combination of screen voltage and nearness to resonance. This effect will seldom be observed when the screen is operated from a fixedvoltage source.


The first step in the adjustment of an amplifier is to stabilize it, both at the operating frequency by neutralizing it if necessary, and at parasitic frequencies by introducing suppression circuits.

If "flat" transmission-line coupling is used, the output end of the line should be matched, as described in the chapter for the case where the amplifier is to feed the grid of a following stage, or in the transmission-line chapter if the amplifier is to feed an antenna system. After proper

match has been obtained, all adjustments in coupling should be made at the *input* end of the line.

Until preliminary adjustments of excitation have been made, the amplifier should be operated with filament voltage on and fixed bias, if it is required, but screen and plate voltages off. With the exciter coupled to the amplifier, the coupling to the driver should be adjusted until the amplifier draws rated grid current, or somewhat above the rated value. Then a load (the antenna grid of the following stage, or a dummy load) should be coupled to the amplifier.

With screen and plate voltages (preferably reduced) applied, the plate tank capacitor should be adjusted to resonance as indicated by a dip in plate current. Then, with full screen and plate voltages applied, the coupling to the load should be adjusted until the amplifier draws rated plate current. Changing the coupling to the load will usually detune the tank circuit, so that it will be necessary to readjust for resonance each time a change in coupling is made. An amplifier should not be operated with its plate circuit off reso-

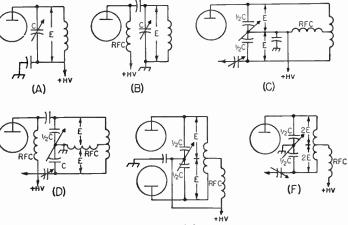

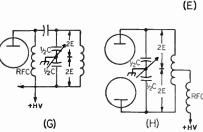


Fig. 6-33—Diagrams showing the peak voltage for which the plate tank capacitor should be rated for c.w. operation with various circuit arrangements. E is equal to the d.c. plate voltage. The values should be doubled for plate modulation. The circuit is assumed to be fully loaded. Circuits A, C and E require that the tank capacitor be insulated from chassis or ground, and from the control.

nance for any except the briefest necessary time, since the plate dissipation increases greatly when the plate circuit is not at resonance. Also, a screen-grid tube should not be operated without normal load for any appreciable length of time, since the screen dissipation increases.

It is normal for the grid current to decrease when the plate voltage is applied, and to decrease again as the amplifier is loaded more heavily. As the grid current falls off, the coupling to the

Component Ratings

driver should be increased to maintain the grid current at its rated value.

COMPONENT RATINGS AND INSTALLATION

Plate Tank-Capacitor Voltage

In selecting a tank capacitor with a spacing between plates sufficient to prevent voltage breakdown, the peak r.f. voltage across a tank circuit under load, but without modulation, may be taken conservatively as equal to the d.c. plate voltage. If the d.c. plate voltage also appears across the tank capacitor, this must be added to the peak r.f. voltage, making the total peak voltage twice the d.c. plate voltage. If the amplifier is to be plate-modulated, this last value must be doubled to make it four times the d.c. plate voltage, because both d.c. and r.f. voltages double with 100-per-cent plate modulation. At the higher plate voltages, it is desirable to choose a tank circuit in which the d.c. and modulation voltages do not appear across the tank capacitor, to permit the use of a smaller capacitor with less plate spacing. Fig. 6-33 shows the peak voltage, in terms of d.c. plate voltage, to be expected across the tank capacitor in various circuit arrangements. These peak-voltage values are given assuming that the amplifier is loaded to rated plate current. Without load, the peak r.f. voltage will run much higher.

The plate spacing to be used for a given peak voltage will depend upon the design of the variable capacitor, influencing factors being the mechanical construction of the unit, the insulation used and its placement in respect to intense fields, and the capacitor plate shape and degree of polish. Capacitor manufacturers usually rate their products in terms of the peak voltage between plates. Typical plate spacings are shown in the following table.

Typical Tank-Capacitor Plate Spacings					
Spacing	Peak	Spacing	Peak	Spacing Peak	
(In.)	Voltage	(In.)	Voltage	(In.) Voltage	
0.015	1000	0.07	3000	0.175 7000	
0.02	1200	0.08	3500	0.25 9000	
0.03	1500	0.125	4500	0.35 11000	
0.05	2000	0.15	6000	0.5 13000	

Plate tank capacitors should be mounted as close to the tube as temperature considerations will permit, to make possible the shortest capacitive path from plate to cathode. Especially at the higher frequencies where minimum circuit capacitance becomes important, the capacitor should be mounted with its stator plates well spaced from the chassis or other shielding. In circuits where the rotor must be insulated from ground, the capacitor should be mounted on ceramic insulators of size commensurate with the plate voltage involved and — most important of all, from the viewpoint of safety to the operator — a well-insulated coupling should be used between the capacitor shaft and the dial. The sec-

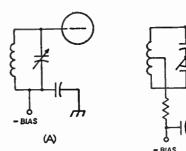


Fig. 6-34—The voltage rating of the grid tank capacitor in A should be equal to the biasing voltage plus about 20 per cent of the plate voltage.

tion of the shaft attached to the dial should be well grounded. This can be done conveniently through the use of panel shaft-bearing units.

Grid Tank Capacitors

In the circuit of Fig. 6-34A, the grid tank capacitor should have a voltage rating approximately equal to the biasing voltage plus 20 per cent of the plate voltage. In the balanced circuit of B, the voltage rating of each section of the capacitor should be this same value.

The grid tank capacitor is preferably mounted with shielding between it and the tube socket for isolation purposes. It should, however, be mounted close to the socket so that a short lead can be passed through a hole to the socket. The rotor ground lead or bypass lead should be run directly to the nearest point on the chassis or other shielding. In the circuit of Fig. 6-34A, the same insulating precautions mentioned in connection with the plate tank capacitor should be used.

Plate Tank Coils

The inductance of a manufactured coil usually is based upon the highest plate-voltage/ plate-current ratio likely to be used at the maximum power level for which the coil is designed. Therefore in the majority of cases, the capacitance shown by Figs. 6-9 and 6-20 will be greater than that for which the coil is designed and turns must be removed if a Q of 10 or more is needed. At 28 Mc., and sometimes 21 Mc., the value of capacitance shown by the chart for a high plate-voltage/plate-current ratio may be lower than that attainable in practice with the components available. The design of manufactured coils usually takes this into consideration also and it may be found that values of capacitance greater than those shown (if stray capacitance is included) are required to tune these coils to the band.

Manufactured coils are rated according to the plate-power input to the tube or tubes when the stage is loaded. Since the circulating tank current is much greater when the amplifier is unloaded, care should be taken to operate the amplifier conservatively when unloaded to prevent damage to the coil as a result of excessive heating.

Tank coils should be mounted at least their diameter away from shielding to prevent a marked loss in Q. Except perhaps at 28 Mc., it is not important that the coil be mounted quite close to the tank capacitor. Leads up to 6 or 8 inches are permissible. It is more important to keep the tank capacitor as well as other components out of the immediate field of the coil. For this reason, it is preferable to mount the coil so that its axis is parallel to the capacitor shaft, either alongside the capacitor or above it.

There are many factors that must be taken into consideration in determining the size of wire that should be used in winding a tank coil. The considerations of form factor and wire size that will produce a coil of minimum loss are often of less importance in practice than the coil size that will fit into available space or that will handle the required power without excessive heating. This is particularly true in the case of screen-grid tubes where the relatively small driving power required can be easily obtained even if the losses in the driver are quite high. It may be considered preferable to take the power loss if the physical size of the exciter can be kept down by making the coils small.

The accompanying table shows typical conductor sizes that are usually found to be adequate for various power levels. For powers under 25 watts, the minimum wire sizes shown are largely a matter of obtaining a coil of reasonable Q. So far as the power is concerned, smaller wire could be used.

Wire Sizes for Transmitting Coils				
Power Input (Watts)	Band (Mc.)	Wire Size		
1000	28-21 14-7 3.5-1.8	6 8 10		
500	28-21 14-7 3.5-1.8	8 12 14		
150	28-21 14-7 3.5-1.8	12 14 18		
75	28-21 14-7 3.5-1.8	14 18 22		
25 or less*	28-21 14-7 3.5-1.8	18 24 28		
*Wire size limited princ	3.5-1.8	28		

Space-winding the turns invariably will result in a coil of higher Q, especially at frequencies above 7 Mc., and a form factor in which the turns spacing results in a coil length between 1 and 2 times the diameter is usually considered satisfactory. Space winding is especially desirable at the higher power levels because the heat developed is dissipated more readily. The power lost in a tank coil that develops appreciable heat

at the higher-power levels does not usually represent a serious loss percentagewise. A more serious consequence, especially at the higher frequencies, is that coils of the popular "air-wound" type supported on plastic strips may deform. In this case, it may be necessary to use wire (or copper tubing) of sufficient size to make the coil self-supporting. Coils wound on tubular forms of ceramic or mica-filled bakelite will also stand higher temperatures.

Plate-Blocking and Bypass Capacitors

Plate-blocking and bypass capacitors should have low inductance. Between 3.5 and 30 Mc. a capacitance of 0.001 μ f. is commonly used. The voltage rating should be 50% above the peak supply voltage.

Disk ceramic capacitors are to be preferred as bypass capacitors, since when they are applied correctly (see TVI chapter), they are series resonant in the TV range and thus very useful in filtering power leads.

R. F. Chokes

The characteristics of any r.f. choke will vary with frequency, from characteristics resembling those of a parallel-resonant circuit, of high impedance, to those of a series-resonant circuit, where the impedance is lowest. In between these extremes, the choke will show varying amounts of inductive or capacitive reactance.

In series-feed circuits, these characteristics are of relatively small importance because the r.f. voltage across the choke is negligible. In a parallel-feed circuit, however, the choke is shunted across the tank circuit, and is subject to the full tank r.f. voltage. If the choke does not present a sufficiently high impedance, enough power will be absorbed by the choke to cause it to burn out.

To avoid this, the choke must have a sufficiently high reactance to be effective at the lowest frequency, and yet have no series resonances near the higher-frequency bands.

Universal pie-wound chokes of the "receiver" type (2.5 mh., 125 ma.) are usually satisfactory if the plate voltage does not exceed 750. For higher voltages, a single-layer solenoid-type choke of correct design has been found satisfactory. The National type R-175A and Raypar RL-100, RL-101 and RL-102 are representative manufactured types.

Since the characteristics of a choke will be affected by any metal in its field, it should be checked when mounted in the position in which it is to be used, or in a temporary set-up simulating the same conditions. The plate end of the choke should not be connected, but the power-supply end should be connected directly, or by-passed, to the chassis. The g.d.o. should be coupled as close to the ground end of the choke as possible. Series resonances, indicating the frequencies of greatest loss, should be checked with the choke short-circuited with a short piece of wire. Parallel resonances, indicating frequencies of least loss, are checked with the short removed.

A THREE-BAND OSCILLATOR TRANSMITTER FOR THE NOVICE

The novice transmitter shown in Figs. 6-35-6-38, inclusive, is easy to build and get working. It is a crystal-controlled, one-tube oscillator capable of running at 30 watts input on the 3.5-, 7-, and 21-Mc. Novice bands. A special feature of the transmitter is a built-in keying monitor which permits the operator to listen to his own sending.

Regulated voltage is used on the screen of the oscillator. This minimizes frequency shift of the oscillator with keying, which is the cause of chirp. In addition, a small amount of cathode bias (R_4) is used on the oscillator. This also tends to improve the keying characteristics in a cathode-keyed simple-oscillator transmitter.

Circuit Details

The oscillator circuit used is the grid-plate type, and the tube is a 6DQ6A pentode. The power output is taken from the plate circuit of the tube. On 80 meters, an 80-meter crystal is needed. On 40, either 80- or 40-meter crystals can be used, although slightly more output will be obtained by using 40-meter crystals. To operate on 15 meters, a 40-meter crystal is used.

The tank circuit is a pi network. The plate tank capacitor is the variable C_6 , and the tank inductance is L_2L_3 . C_8 is a two-section variable, approximately 365 $\mu\mu$ f. per section, with the stators connected together to give a total capacitance of about 730 $\mu\mu$ f. This range of capacitance is adequate for coupling to 50 or 75 ohms on 7 and 21 Mc. When operating on 3.5 Mc., an additional 1000 $\mu\mu$ f. (C_7) is added to furnish the needed range of capacitance. L_1 and R_2 are essential for suppressing v.h.f. parasitic oscillations.

The keying-monitor circuit uses a neon bulb (type NE-2) audio-frequency oscillator connected to the cathode of the 6DQ6A at the key jack, J_1 . The headphones are plugged into J_2 , a jack mounted on the back of the transmitter chassis. Another jack, J_3 , is used as a terminal for the leads that go to the headphone jack on the receiver.

Power Supply

The power supply uses a 5U4G in a full-wave circuit. A capacitor-input filter is used and the output voltage is approximately 370 volts with a cathode current of 90 milliamperes. A 0-150 milliammeter reads cathode current. The screen and grid currents are approximately 4 ma. when the oscillator is loaded.

Construction

All of the components, including the power supply, are mounted on a $2 \times 7 \times 13$ -inch aluminum chassis that is in turn enclosed in a 7 × 9 × 15-inch aluminum box. (Premier AC-1597). One of the removable covers of the box is used as the front panel, as shown in Fig. 6-35. The box has a 1/2-inch lip around both openings, so the bottom edge of the chassis should be placed one inch from the bottom of the panel. The sides of the chassis are also one inch from the sides of the panel. The chassis is held to the panel by S_2 , J_1 , and the mounting screws for the crystal socket, so both the front edge of the chassis and the panel must be drilled alike for these components. S_1 , at the left in the front view, is one inch from the edge of the chassis (that is, two inches from the edge of the panel) and centered vertically on the chasis edge. Thus it is one inch from the bottom of the chassis edge and two inches from the bottom edge of the panel. The hole for J_1 is centered on the chassis edge and the holes for the crystal socket are drilled at the right-hand end of the chassis to correspond with the position of S_1 at the left.

There is nothing critical about the placement of the meter or the shafts for C_6 , C_8 and S_1 . As shown in Fig. 6-38, C_6 is mounted directly above J_1 and approximately two inches from the top of the panel. C_8 similarly is above the crystal socket and on the same horizontal line as C_6 . S_1 is about at the middle of the square formed by these four components.

Fig. 6-35—This 30-watt three-band Novice transmitter is enclosed in a 7 × 9 × 15-inch aluminum box. A group of ¼-inch-diameter holes should be drilled in the top of the box over the oscillator tube, as shown, to provide ventilation. A similar set of holes should be drilled in the back cover behind the oscillator circuit.



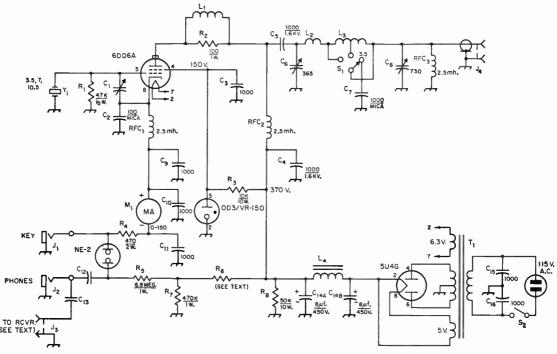


Fig. 6-36—Circuit diagram of the three-band transmitter. Unless otherwise specified, capacitances are in $\mu\mu$ f. Resistances are in ohms (K = 1000).

 C_1 -3-30- $\mu\mu$ f. trimmer.

C2-100-µµf. mica.

C₃, C₉, C₁₀, C₁₁, C₁₅, C₁₆-0.001-\(mu f.\) disk ceramic.

 C_4 , C_5 =0.001- μ f. 1600-volt disk ceramic.

C_α—365-μμf. variable capacitor, single section, broadcast-replacement type.

C7-0.001-µf. 600-volt mica.

C₈—365-μμf. variable capacitor, dual section, broadcast-replacement type.

 C_{12} -500- $\mu\mu$ f. mica or ceramic.

 C_{13} =0.01- μ f. disk ceramic.

 C_{14} -8/8- μ f. 450-volt dual electrolytic capacitor.

J1, J2-Open-circuit phone jack.

J₃-Phono jack, RCA type.

J₄-Coaxial chassis connector, SO-239.

L₁-10 turns No. 18 wire space-wound on R₂.

The holes on the rear edge of the chassis for the coaxial connector J_4 , phone jack J_2 , receiver connector J_3 , and for the a.c. cord are drilled at the same height as those on the front edge. Access holes should be cut in the rear cover of the box at the corresponding positions; these holes may be large enough to clear the components, but not larger than is necessary for this purpose. The cover fits tightly against the rear edge of the chassis and thus maintains the shielding for preventing radiation of harmonics in the television bands. However, it is advisable to fasten the cover to the chassis edge with a few sheet-metal screws, in order to insure good electrical contact.

There are several different types of broadcastreplacement variable capacitors on the market. L_2 —6 turns No. 16 wire, 8 turns per inch, $1\frac{1}{4}$ inches diam. (B & W 3018).

 L_3 -23 turns No. 16 wire, 8 turns per inch, 11/4 inches diam. (B & W 3018). The 7-Mc. tap is 18 turns from the junction of L_2 and L_3 .

L₄-8-h. 150-ma. filter choke (Thordarson 20C54).

M₁-0-150 ma (Shurite 950).

R₁-R₈ inc.-As specified.

RFC₁, RFC₂, RFC₃—2.5-mh. r.f. choke (National R-50 or similar).

S₁-Single-pole 3-position switch (Centralab 1461).

S2-Single-pole single-throw toggle switch.

T₁-Power transformer: 360-0-360 volts, 120 ma.; 6.3 volts, 3.5 amp.; 5 volts, 3 amp. (Stancor PM-8410).

Y₁-Crystal (see text).

Some of these have holes tapped in the front of the frame, and this type can be mounted directly on the panel using machine screws and spacers. Others have mounting holes only in the bottom. In this case, the capacitor can be mounted on a pair of L-shaped brackets made from strips of aluminum.

Both L_2 and L_3 are supported by their leads. One end of L_3 is connected to the stator of C_8 and the other end is connected to a junction on top of a one-inch-long steatite stand-off insulator. L_2 has one end connected to the stator of C_6 and the other end to one of the terminals on S_1 .

The voltage-dividing network consisting of R_6 and R_7 provides the correct voltage for operating the keying monitor, R_6 is 1.65 megohms, a value obtained by using two 3.3-megohm 1-watt



Fig. 6-37—Rear view of the transmitter showing the placement of components above chassis. The loading capacitor, C_8 , is at the left, L_8 is the vertical coil and L_2 the horizontal one. Rubber grommets are used to prevent chafing and to furnish additional insulation on the leads coming from below chassis.

resistors in parallel. These resistors and other small components may be mounted on standard bakelite tie points.

Adjustment and Testing

When the unit is ready for testing, a 15- or 25-watt electric light will serve as a dummy load. One side of the lamp should be connected to the output lead and the other side to chassis ground. A crystal appropriate for the band to be used should be plugged into the crystal socket, and a key connected to the key jack. S_1 should be set to the proper band. S_2 may then be closed and the transmitter allowed to warm up.


Set C_8 at maximum capacitance (plates completely meshed) and close the key. Quickly tune C_6 to resonance, as indicated by a dip in the cathode-current reading. Gradually decrease the capacitance of C_8 , while retouching the tuning of C_6 as the loading increases. Increased loading will be indicated by increasing lamp brightness and by larger values of cathode current. Tune

for maximum lamp brilliance. The cathode current should read between 90 and 100 milliamperes when the oscillator is fully loaded.

 C_1 should be adjusted for the best keying characteristics consistent with reasonably good power output. It is not advisable to attempt to adjust C_1 with a lamp dummy load, since the lamp resistance will change during the heating and cooling that take place during keying, and this will affect the keying characteristic of the oscillator. Use a regular antenna, with or without an antenna coupler or matching network as the antenna system may require, and listen to the keying on the station receiver. Remove the antenna from the receiver to prevent overloading, and adjust the r.f. gain control for a signal level comparable with that at which signals on that band are normally heard. Further details on checking keying will be found in the chapter on keying and break-in.

(Originally described in *QST* December, 1957.)

Fig. 6-38-Below-chassis view. Power-supply components are mounted in the lefthand side and the oscillator section is at the right-hand side. Mounted on the back wall of the chassis is the keying monitor. Although not visible in this view, the monitor companents are mounted on a fourterminal tie point.

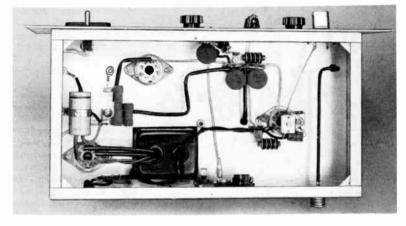

AN INEXPENSIVE 75-WATT FIVE-BAND TRANSMITTER

The transmitter shown in Figs. 6-39 and 6-41 combines the efficiency and flexibility of plug-in coils with good shielding for TVI prevention. It is a two-stage transmitter using a 6AG7 crystal oscillator and an inexpensive 1625 tetrode amplifier. The latter tube is quite inexpensive in surplus and probably represents the least "dollars per watt" of any available tube. Provision is included for crystal-controlled operation, and terminals are provided for connecting v.f.o.

Referring to the circuit diagram of the transmitter, Fig. 6-40, a 6AG7 grid-plate type crystal-controlled oscillator is used. The output can be tuned to the crystal frequency or to multiples of it, depending upon the coil plugged in at L_1 .

Both 80- and 40-meter crystals are used; for 80-meter operation a 3.5-Mc. crystal is used $(L_1$ is not required on this band because RFC₂ serves the purpose.) The same crystal will furnish adequate drive on 40 meters, with the oscillator stage working as a doubler, and it can even be stretched to 20 meters by quadrupling in the oscillator. A 40-meter crystal can be used for 7-Mc. work, and it can be used on 20 by doubling in the oscillator, on 21 Mc. by tripling and on 28 Mc. by quadrupling. With some crystals it will not be possible to get adequate drive by quadrupling to 28 Mc., and in these cases both oscillator and amplifier should be operated as doubler stages. The small trimmer, C1, in the grid circuit is an excitation control, and is set at a position that gives best keying (when the oscillator is keyed) consistent with adequate

The amplifier tank circuit is a pi network designed primarily for working into a low impedance (50 to 75 ohms) load. A 140- $\mu\mu$ f. capacitor, C_s , is used for plate tuning on all bands; on 80 meters it is shunted by an additional 100 $\mu\mu$ f. This is done automatically by a jumper connection in the coil. The loading capacitor is a midget two-section capacitor designed for use in small receivers, but by connecting the two stators in parallel a 500- $\mu\mu$ f. variable is ob-

tained at low cost. On 80 meters it is shunted by a 1000- $\mu\mu$ f. fixed capacitor. RFC_5 and the associated 100-ohm resistor in the plate lead of the 1625 are for suppressing parasitic oscillations.

Two methods of keying are provided. The oscillator and amplifier can be keyed simultaneously, by using the connections of Fig. 6-43A, or the amplifier only can be keyed, with the oscillator running all the time during transmitting, by using the connections of Fig. 6-43C.

The latter keying system should be used if reports of a chirpy signal are obtained. Although it is not shown, it is possible to incorporate a "spotting" switch with the system of Fig. 6-43A; S₁ will serve that purpose in Fig. 6-43C.

A 0-5 milliammeter is used to meter the grid and cathode circuits of the 1625 amplifier stage. When the meter is switched to the grid circuit, it reads directly (0 to 5 ma.), but when it is switched across RFC_3 in the cathode circuit, the 0.1-ohm resistance of the choke serves as a shunt to convert the full-scale reading of the meter to 375 ma.

Construction Details

Before drilling any holes for the components, it would be wise to study the arrangement of parts on the $10\times12\times3$ -inch aluminum chassis. While the location of components is not critical, some initial planning will permit leads to be made direct and as short as possible.

The only unusual construction in the transmitter will be the bracket that holds the 1625 socket and the installation of the shield around the meter. The bracket is made from a piece of aluminum that can be bent in a vise. It is cut in the shape of a symmetrical trapezoid, and a ½-inch wide lip is first bent along the long side. Notches are then cut in the lip to permit the sides to be bent in, to form the bracket as shown in Fig. 6-41. The platform the socket is mounted on measures $2\frac{1}{2} \times 2\frac{3}{4}$ inches, and the sides taper from nothing to 1 inch.

The shield around the meter is a 23/4 ×21/8×15/6-inch "Minibox" (Bud CU-3000A).

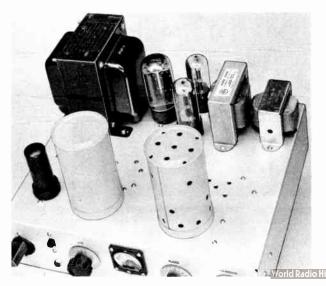


Fig. 6:39—An inexpensive 75-watt transmitter using plug-in coils and an "economy" power supply. The oscillator (left) is a 6AG7; the 1625 output tube is mounted underneath the chassis. Shield cans are baking-powder tins painted gray; the can for the output coil (right) is ventilated for better cooling, as is the chassis behind the can.

Complete transmitter is built on $10\times12\times3$ -inch aluminum chassis. At the rear of the chassis, from left to right: power transformer, 5U4-GB, 6DE4s, 150-ma. choke, 12.6-volt filament transformer.

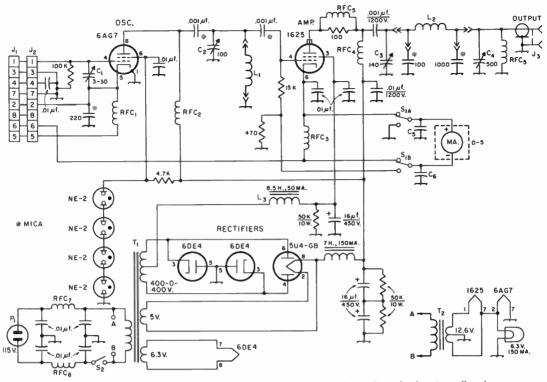


Fig 6-40—Circuit diagram of the inexpensive 75-watt transmitter. Unless indicated otherwise, all resistors are $\frac{1}{2}$ watt, all resistances are in ohms, all capacitances are in $\mu\mu$ f. Electrolytic capacitors are marked with polarity, mica capacitors are marked with *, other fixed capacitors are ceramic.

 C_1 -3- to 30- $\mu\mu$ f. mica compression trimmer.

C2-100-µµf. midget variable (Hammarlund APC-100B).

 C_3 —140- $\mu\mu$ f. midget variable (Hammarlund APC-140B). C_4 —Midget superhet two-gang variable, 365 and 135

C₄—Midget superhet two-gang variable, 305 and 135 μμf., sections connected in parallel (Allied Radio, Chicago, 61 H 008).

 C_5 , C_6 —1500- $\mu\mu f$. feedthrough capacitor (Centralab FT-1500).

J₁, J₂—Octal tube sockets.

J₈-Coaxial receptacle (SO-239).

L1, L2-See coil table.

L_s-8½-h. 50-ma. filter choke (Knight 62 G 136).

L₄—7-h. 150-ma. choke (Stancor C-1710).

MA₁—0-5 milliammeter, 1%-inch square (Micronta).

The section with the lips has a clearance hole for the meter drilled in it, and it is held to the front of the chassis by the meter mounting screws. The other section of the Minibox has two 1500-μμf. feedthrough capacitors mounted in it. At assembly flexible leads from the meter are soldered to the inner ends of the capacitors, and when assembly is completed, the external connections to the meter can be made at the protruding capacitor leads.

No other special construction is required, since all of the components can be mounted with accompanying hardware or by means of 6-32 screws and nuts. Reference to Fig. 6-41 will show how multiple tie points have been provided at every opportunity for the support of

P1-Fused line plug, 11/2-amp. fuses.

RFC₁, RFC₄, RFC₆—2.5-mh. 100-ma. (National R-50).

RFC₂-100 μh. r.f. choke (Millen 34300-100).

RFC₃—0.82- μ h. r.f. choke, 0.1 ohms (Millen 34300-0.82).

RFC₈—8 turns No. 18 enam. wound on 100-ohm (Sprague 5KT1015) resistor.

RFC₇, RFC₈—16 turns No. 18 enam., self-supporting, wound on %-inch diam. form before removing and spacing to occupy % inch length.

S₁-D.p.d.t. toggle.

S2-S.p.s.t. slide or toggle switch.

T₁—800-v.c.t. power transformer, 5 v. at 3 a., 6.3 v. at 5 a. (Thordarson 24RO7-U or Knight 61 G 414).
T₂—12.6 v. at 2.0 amp. (Knight 61 G 420).

resistors, r.f. choke coils, filter capacitors and other components. RFC_7 and RFC_8 are supported between tie points that also serve as terminals for the line cord and associated 0.01- μ f. capacitors. These r.f. choke coils are first wound on a $\frac{1}{2}$ 8-inch diameter form (a drill is excelent) and then removed and stretched slightly. RFC_8 is wound directly over the associated 100-ohm resistor and its ends are soldered to the leads of the resistor.

The two shield cans for L_1 and L_2 are made from baking-powder (Calumet) tins that have clearance holes for the ceramic tube sockets punched in their covers. To dress them up a bit, the cans may be sprayed with gray paint. The can for L_2 was drilled in a few spots to provide ventilation, since the coil may get warm on 80 meters. To provide for the addition of extra capacitors at L_2 in the 80-meter range, a 5-pin socket is used at L_2 and a 4-pin socket at L_1 . A hood (Amphenol 83-765) is used at the back of J_8 to maintain the shielding.

Information on the plug-in coils is given in the coil table. The coils are mounted inside the polystyrene forms. When cutting the coils from the original stock allow a few extra turns for the leads that are run down through the coilform pins. An easy way to cut the coils from the original stock is to heat a razor blade and use it to slice through the polystyrene bars. Ventilation holes are included in the base of the 80-meter coil. Before soldering to the pins of the coil forms, clean the inside of the pins with a drill or Swiss file; it will make soldering a lot easier. When soldering, hold the pin with a pair of pliers, to prevent too much heat from reaching the coil form proper and softening the polystyrene. After the solder has cooled, clean off any rosin with a knife or some alcohol. The coils can be finished off by sliding an identification slip between the coil and the form.

Tune-Up Procedure

For the initial testing, a 60-watt lamp bulb will make a suitable dunmy load. Connect it at J_a through a short length of cable or wires and a plug. Plug in an 80-meter crystal at Pins 1 and 3 or 1 and 7 at J_1 , and connect the telegraph key to Pins 5 and 7 of J_2 . Set C_2 at minimum capacitance, and unscrew the adjustment on C_1 until the plates just begin to separate visibly. Plug in the 80-meter L_2 and the tubes and rectifiers.

With S_2 in the "off" position, plug P_1 (properly fused) into a wall outlet and turn on S_1 . The pilot lamp should light and the cathodes of the rectifiers should warm up. After a half minute or so, close the telegraph key and on a warmed-up receiver tuned to the crystal frequency listen for the oscillator. If you find the oscillator isn't working, check the wiring for errors.

When the oscillator has been checked and is working properly, turn off the transmitter and connect a jumper between Pins 5 and 6 in the plug in J_2 . Now when the key is closed both the oscillator and amplifier will be keyed. Set C_3

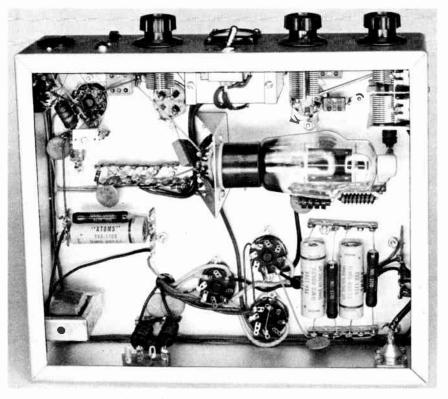


Fig. 6-41—View underneath the chassis of the 75-watt transmitter. The 1625 amplifier tube is mounted horizontally; the tube socket is supported by an aluminum bracket (center). The string of NE-2 neon bulbs, supported by their leads on a multiple tie point, is to the left of the bracket.

At the upper left-hand corner, the panel socket, J_1 , is duplicated by the side socket, J_2 , mounted nearby. The panel socket is used for a crystal socket or for v.f.o. input, and the side socket is for keying and control circuits. Note at the top center that the meter is shielded by the small Minibox.

The a.c. line cord is brought in at the rear of the chassis through a rubber grommet, and the associated 0.01- μ f, capacitors and RFC₈ and RFC₇ are mounted at this point. The r.f. output jack, J_8 , is at the lower right.


Cail Table for 75-Watt Transmitter

All coils except 10-meter L_2 are made from 1-inch diameter 16 t.p.i. No. 20 wire stock (B&W 3015 or Illumitronics 816). L_1 coils are mounted inside 4-pin polystyrene form (Allied Radio 71 H 713) and L_2 coils are mounted inside 5-pin polystyrene (Allied Radio 71 H 714). 10-meter L_2 stock is 34-inch diameter 8 t.p.i. No. 18 wire stock (B&W 3010 or Illumitronics 608).

Band	L_1	L_{2}
80 m.	none	30½ turns *
40 m.	21 turns	20½ turns
20 m.	10½ turns	10½ turns
15 m.	5½ turns	7½ turns
10 m.	Same as 20 m.	7 turns

^{*} With jumpers to connect auxiliary capacitors; see Fig. 6-40. Six 1/4 inch diameter ventilation holes drilled near bottom of coil form.

and C4 at about three-fourths fully meshed and turn on the transmitter again. When the tubes have warmed up, close the telegraph key and tune C_3 between half and fully meshed. A point should be found where the dummy load will show some light. Open the key and switch S_1 to read grid current if it isn't there already. Close the key and observe the grid current; it should be about 3 ma. If it is more it can be reduced by adjustment of C_2 . Switching S_1 to read cathode current, it should read about 1.6 ma. on the meter, corresponding to a cathode current of 120 ma. (The full-scale reading of the meter in this condition is 375 ma.; thus 1.0 = 75 ma., 2.0 = 150 ma., and so on.) If the cathode current at resonance (dip in current as C_3 is tuned) is higher than 1.6 on the meter, the loading can be reduced by turning C_4 in the direction of more capacitance (plates meshed further). Since the

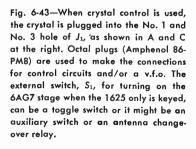


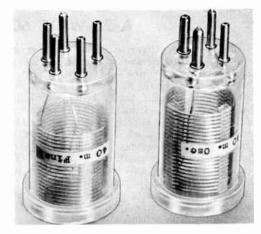


Fig. 6-42—All coils are mounted in (or on) polystyrene plug-in coil forms. The 7-Mc. coils are shown here.

plate voltage runs about 670 volts with this supply, the proper cathode-current reading for 75 watts input is 1.6 (120 ma., allowing 11 ma. for grid and screen-grid currents).

When the transmitter has been checked on 80 meters, the coils for 40 meters can be plugged in and the checking process can be repeated. In this case, and in all others except the 80-meter case, the oscillator tuning C_2 will be relatively sharp. When setting C_2 on the higher ranges (20, 15 and 10 meters), the output should be carefully checked to insure that a wrong harmonic of the crystal is not selected. Use a receiver to check or, better yet, an absorption wavemeter or other selective device.

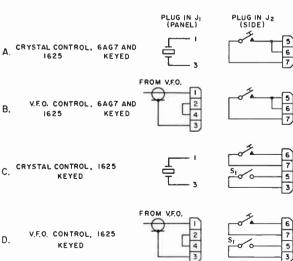When a certain familiarity has been obtained with the operation of the transmitter, plug in a 7-Mc. crystal and tune up the transmitter on 15 meters. Then adjust C_1 so that the amplifier grid current is no more than 3 ma. with C_2 peaked for maximum reading. This adjustment need not be changed after it has been set, with crystals of ordinary activity.



A 75-WATT 6DQ5 TRANSMITTER

The transmitter shown in Fig. 6-44 is designed to satisfy the requirements of either a Novice or General Class licensee. As described here it is capable of running the full 75 watts limit in the 80-, 40- and 15-meter Novice bands, with band switching, crystal switching and other operating features. The General license holder can use the transmitter in any band 80 through 10 meters, and he can add v.f.o. control or amplitude modulation at any time without modifying the 6DQ5 transmitter. Crystal switching is a convenience for rapidly shifting frequency within a band to dodge QRM, and a spot position on the operate switch permits identifying one's frequency relative to others in a band. An accessory socket, X_3 , furnishes a convenient point for borrowing power for a v.f.o. or for controlling the oscillator by an external switch.

Referring to Fig. 6-45, the circuit diagram of the transmitter, the crystal selector switch, S_1 , is used to choose the desired crystal. For crystal-controlled operation crystals would be plugged in pins 1 and 3 and 5 and 7 of socket X_1 . Similar sockets (not shown in the diagram) are used to hold the other crystals. When v.f.o. operation is desired, the v.f.o. output is connected to J_1 , the plug P_1 is inserted in socket X_1 and the former 6AG7 crystal oscillator stage becomes an amplifier or multiplier stage when switch S_1 is turned to position 1.

Since the output of the 6AG7 stage will vary considerably with the bands in use, an excitation control, R_1 , is included to allow for proper adjustment of the drive to the 6DQ5 amplifier. The 6DQ5, a highly sensitive tube, is neutralized to avoid oscillation; the small variable capacitor C_2 and the 390- $\mu\mu$ f. mica capacitor form the neutralizing circuit. Screen or screen and plate modulation power can be introduced at socket X_2 ; for radiotelegraph operation these connections are completed by P_2 . Grid or plate current of the 6DQ5 can be read by proper positioning of S_5 ;

the 0-15 milliammeter reads 0-15 ma, in the gridcurrent position and 0-300 ma, in the platecurrent position.

The transmitter is keyed at J_3 , and a keyclick filter (100-ohm resistor and C_5) is included to give substantially click-free keying. The v.f.o. jack, J_4 , allows a v.f.o. to be keyed along with the transmitter for full break-in operation.

Construction

A $10 \times 17 \times 3$ -inch aluminum chassis is used as the base of the transmitter, with a standard 83/4-inch aluminum relay rack panel held in place by the bushings of the pilot light, excitation control and other components common to the chassis and panel. The panel was cut down to 17 inches in length so that the unit would take a minimum of room on the operating table. A good idea of the relative location of the parts can be obtained from the photographs. The support for the r.f. portion housing is made by fastening strips of 1-inch aluminum angle stock (Reynolds aluminum, available in many hardware stores) to the panel and to a sheet of aluminum 9½ inches long that is held to the rear chassis apron by screws and the key jack, J3. A piece of aluminum angle must also be cut to mount on the chassis and hold the cane-metal (Reynolds aluminum) housing. Fig. 6-47 shows the three clearance holes for the screws that hold this latter angle to the chassis after the cane metal is in place. Build the cane-metal housing as though the holes weren't there and the box has to hold water; this will minimize electrical leakage and the chances for TVI. To insure good electrical contact between panel and angle stock, remove the paint where necessary by heavy applications of varnish remover, with the rest of the panel masked off. The paint will blister and be easy to remove; wash the panel and then drill the holes for the components and screws. (If the holes are drilled first, the remover may leak

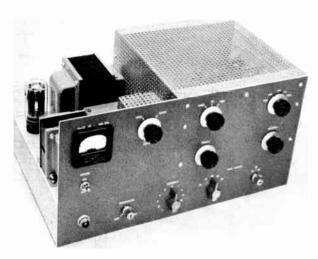


Fig. 6-44—This 75-watt crystal-controlled transmitter has provision for the addition of v.f.o. control. A 6AG7 oscillator drives a 6DQ5 amplifier on 80 through 15 meters.

As a precaution against electrical shock, the meter switch, to the immediate right of the meter, is protected by a cane-metal housing. The switch to the right of the meter switch handles the spot-operate function, and the switch at the far top right is the plate-circuit band switch.

Along the bottom, from left to right: pilot light, excitation control, crystal switch, grid circuit band switch, and grid circuit tuning.

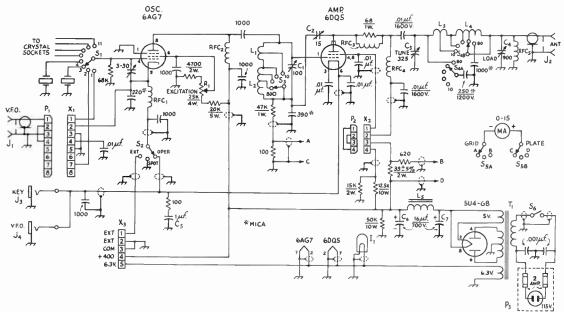


Fig. 6-45—Circuit diagram of the 75-watt 6DQ5 transmitter. Unless specified otherwise, capacitance is in μμf., resistance is in ahms, resistors are ½ watt. C₁—100-μμf. midget variable (Hammarlund HF-100). C₂—15-μμfd. midget variable, .025 inch spacing (Johnson 15J12).

C₃-325-\(\mu\mu\mathre{\text{f}}\), variable (Hammarlund MC-325-M).

C₄—Dual 450-μμf. braadcast replacement variable, two sections cannected in parallel. (Allied Radio 61H059).

C_B-1-\mu f. 400-valt tubular.

 C_6 , C_7 =16- μ f. 700-volt electrolytic (Aerovox PRS).

1,-6-volt pilot lamp.

J₁—Phono jack.

J₂--Coaxial connectar, chassis mounting, type SO-239.

J₃, J₄--Open-circuit phone jack.

L₁-7½ t. No. 18, % inch diam., 8 t.p.i., tapped 5½ turns from grid end (B&W 3006).

L₂-38 t. No. 32, 1 inch diam., 32 t.p.i., tapped 23 and 31 turns up (B&W 3016).

L₃—5 turns Na. 14, 1-inch diam., 4 t.p.i., self-supporting, tapped 3½ turns from plate end.

L₄-15 turns No. 14, 1¾ inch diam., 4 t.p.i., tapped 6¼ and 10¼ from output end (B&W 3021).

L₅-10-henry 200-ma. filter choke (Triad C-16A).

P₁—Octal plug (Amphenol 86-PM8).

P2-4-pin plug (Amphenol 86-PM4).

P₃-Fused line plug.

R₁-25,000-ohm 4-watt potentiameter (Mallory M25MPK).

RFC1, RFC2 $-750-\mu h$. 100-ma. r.f. choke (National R-33).

RFC₃—3 turns No. 14 around 68-ohm 1-watt composition resistor.

RFC₄-1-mh. r.f. choke, 500 ma. (Jahnson 102-752). RFC₈-2.5-mh. r.f. choke (National R-1008).

S₁—1-pole 11-pasition rotary ceramic switch Centralab Y section on P-121 index assembly).
S₂—Single-pole 11-position (3 used) non-shorting rotary switch (Centralab PA-1001).

S₃—Single-pole 12-position (5 used) rotary ceramic switch (Centralab PA-1 on PA-301 index assembly).

S₄—2-pole 5-position rotary ceramic switch (Centralab 2505).

 S_8 =2-pole 6-position (3 used) non-shorting ceramic rotary switch (Centralab PA-2003).

S₆-S.p.s.t. toggle.

T₁-800 v.c.t. 200-ma. power transformer (Triad R-121-A).

X1-Octal tube socket.

X₂-4-pin tube socket.

X₃-5-pin tube socket.

through and spoil the paint on the front of the panel.)

From a suitable piece of cane metal, make the four-sided $2\frac{1}{4} \times 2\frac{1}{4} \times 2\frac{1}{4}$ -inch box that covers S_5 , and fasten it to the utility-box cover with sheet-metal screws. Don't forget J_1 on the side of the box.

The self-supporting coil, L₄, can be wound on the envelope of the 6AG7 and then pulled apart to give the correct winding length.

Installation of the electrical components should present no problems. To insulate it from the chassis, capacitor C_1 is mounted on a small ceramic cone insulator (Johnson 135-500 or National GS-10). The socket for the 6DQ5 is mounted above the chassis on a pair of $\frac{3}{4}$ -inch sleeves, with a large clearance hole under the socket for the several leads running from under the chassis. Cathode and screen bypass capacitors for the 6DQ5 connect to the chassis at soldering lugs under the sleeves.

Taps on L_2 are readily made by first pushing the wire on either side of the desired turn toward the center of the coil.

Note that shielded wire is used for many of the a.c. and d.c. (but not r.f.) power leads; this is done to minimize the chances for stray radiation and it also contributes to the stability of the transmitter.

Adjustment

When the wiring is completed and checked,

disable the amplifier stage by removing P_2 , plug in P_3 and turn on S_5 . The tube heaters and filaments should light up. If a voltmeter is available and connected across C_6 , it should indicate over 500 volts. Later on, with full loading, the plate voltage will run around 400.

With S_1 switched to an 80-meter crystal, S_3 switched to 80 or 40 and S_5 switched to GRID, flip S_2 to spot and tune C_1 through its range. If the crystal is oscillating the meter should give an indication at some setting of C_1 . The grid current reading should vary with the setting of C_1 (maximum at resonance) and with the setting of R_1 (maximum with arm at 20K end). If a key is plugged in at J_3 and S_2 is set to oper, the grid current should appear only when the key is closed. Listen to the signal on a receiver (no antenna); if the signal is chirpy try adjusting the 3-30 $\mu\mu$ f. compression trimmer between grid and cathode of the 6AG7.

With a 40-meter crystal switched in, check for grid current at 14 and 21 Mc., by switching S_3 to the desired band and tuning with C_1 . These settings should be checked with an absorption-type waveneter, since it is possible in some cases to find more than one harmonic in the range of C_1 . The 28-Mc. range can also be checked, but the 4th harmonic of the 7-Mc. crystal will yield only about 1 ma. of grid current.

Next check the neutralization on the 15-meter band. With 21-Mc. grid current indicating, switch S_4 to 15, set C_4 at half scale, and swing C_3

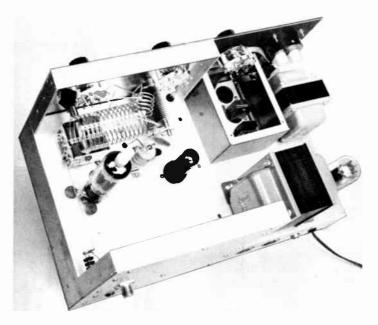


Fig. 6-46—Top view of the 6DQ5 transmitter with cane-metal cover removed. A $3\times4\times5$ -inch utility box (upper right) serves as a shield for the crystals; the cane-metal protection for the meter switch is fastened to the box cover. Phono jack mounted on the meter-side of the box receives v.f.o. output; short length of Twin-Lead from this jack to octol plug brings v.f.o. output to crystal socket. For protection against high voltage, meter terminals are covered by ceramic tube plote caps (Millen 36001).

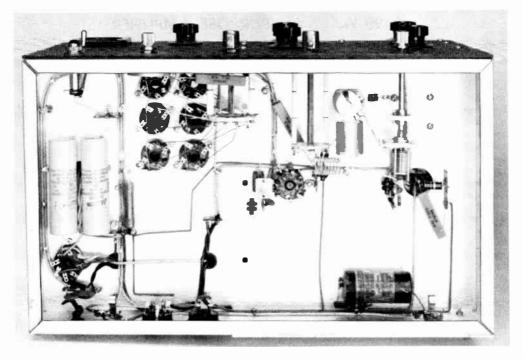


Fig. 6-47—Group of six octal sockets (upper left) serves as crystal sockets. Socket at center of chassis holds 6AG7 oscillator tube; the 3-30- $\mu\mu$ f. mica compression trimmer mounted alongside is excitation control for oscillator stage. Small midget capacitor above coil is neutralizing capacitor adjusted from above chassis; this capacitor and grid tuning capacitor to right must be insulated from chassis.

through its range. Watch closely for a flicker in grid current. If one is observed, try a different setting of C_2 . Work carefully until the flicker is a minimum. A more sensitive indication of neutralization can be obtained by using a germanium diode and a 0-1 milliammeter in the output at J_2 ; adjust C_2 for minimum meter indication. If using this sensitive test, it is wise to start out with R_1 set at half range or less, until it has been determined that the meter will not swing off scale. Under no circumstances use this test with P_2 in place; the 6DQ5 output is quite likely to destroy the crystal diode.

When the amplifier has been neutralized, connect a dunimy load (a 60-watt lamp will do) at J_2 and replace P_2 . Set S_5 to plate and send a few dots as C_3 is tuned through its range. At resonance the lamp should light up and the plate current should dip. The plate current can be made to increase, along with the lamp brilliance, by decreasing the capacitance at C_4 . The 6DQ5 plate current can be run up to 180 ma. (9 ma. on the meter) for Novice work; the grid current should be held at 2 to 4 ma. Crystals in the 3.5-to 4.0-Mc. range should be used for 80- and 40-

meter operation, and 7-Mc. crystals should be used on 40, 20 and 15 meters. For 10-meter operation, it is recommended that a v.f.o. with 20-meter output be used to drive the 6AG7; trying to drive the 6DQ5 with the 4th harmonic of a 7-Mc. crystal is too marginal for all but the most experienced operators. With v.f.o. control, always frequency multiply (double or triple) in the 6AG7 stage to the desired band.

Because the 6DQ5 is capable of drawing high values of plate current when not tuned properly, it will pay to take care in learning how to adjust the transmitter. Once the controls have been "calibrated" and the approximate settings for each band become known, it should no longer be necessary to tune up with the "series-of-dots" technique mentioned above. However, in the early stages of familiarization with the transmitter, the dots, or a fast hand on the key, may save a tube or power supply. The fact that the 6DQ5 can draw such heavy currents at low plate voltages makes it an excellent tube for an effective inexpensive transmitter, but the tube is not as tolerant of careless tuning habits as are some other tubes.

A 90-WATT ALL-PURPOSE AMPLIFIER

The amplifier shown in Figs. 6–48 through 6–51 will serve as a Class- AB_1 linear amplifier or as a Class-C power amplifier with no changes other than the proper adjustment of excitation and loading. To accomplish this, a stabilized bias supply provides proper Class- AB_1 bias; the bias increases to the correct value for Class-C operation when the excitation is brought up to the point that yields normal grid current. A stabilized screen supply is included to insure good linear operation.

Referring to the amplifier circuit in Fig. 6-50, excitation on the desired band is introduced at J_1 . The grid circuit is a commercial assembly, Z_1 , that can be switched to the correct band by S_1 and tuned by C_1 . A pi-network coupler is used in the output, switched by S_2 and tuned by C_3 . Proper loading is obtained by adjustment of C_4 ; to provide sufficient output capacitance in the 80-meter band an additional 680 $\mu\mu f$. is added. A neutralizing circuit, C_2 and a 680- $\mu\mu f$, capacitor, adds to the fundamental stability at the higher frequencies. Parasitic suppressors were found to be necessary in the grid and plate circuits.

Overload protection is provided by a 250-ma, fuse in the cathode circuit. The grid, plate or screen current can be metered by a suitable setting of S_3 ; with the resistances shown the meter provides a full-scale reading 5 ma. on grid current, 25 ma. on screen current, and 250 ma. on plate current.

If it is desired to plate- or screen-modulate the amplifier for a.m. operation, the necessary audio power can be introduced at J_3 .





Fig. 6-48—Front view of the 6146 all-purpose amplifier. The upper panel is part of an $8\times6\times31/2$ -inch Minibox (Bud CU-2109); the ventilated shielding of Reynolds Aluminium cane metal is fastened to the Minibox and base with sheet-metal screws.

Plate-circuit tuning controls and switch are mounted on the Minibox, and the grid-circuit controls, power switches and meter are mounted on the end of the $8\times12\times3$ -inch aluminum chassis that serves as a base.

The power-supply circuit is shown separately (Fig. 6-52) for convenience only, since the amplifier and power supply are all built on the same

 $8 \times 12 \times 3$ -inch chassis. High voltage for the plate of the 6146 is provided by a bridge rectifier using a 5U4-GB and two 6DE4 rectifiers; stabilized screen voltage is obtained from the same supply and two voltage-regulator tubes.

Fig. 6-49—Rear view of the 90-watt allpurpose amplifier with the cane-metal cover removed. One voltage-regulator tube has been removed from its socket (right edge of transformer) to allow the neutralizing capacitor and plate blocking capacitor to be seen. The plate r.f. choke (RFC₃ in Fig. 6-50) is mounted on one side wall, and the load capacitor and safety choke (C₄ and RFC₄ in Fig. 6-50) are mounted on the for side wall.

The rear apron of the chassis (fore-ground) carries the input and output coaxial-connector jacks, the 6146 cathode fuse, and the socket for the a.m. modulator connections. A shorting plug is shown in the socket.

Most

and

construction

collars few components can Construction

RFCz RG-58/U 6146 100 Zį 7250 July GRID 15 1W. 680µµt. X20 X, o 20 1 5% 53 200 0-5 MA -^^^-Y₂ +700

Fig. 6-50—Circuit diagram of the all-purpose amplifier and its bias supply. Unless otherwise indicated, resistors are ½ watt,

C₁-140-\(\mu\mu\mi\), midget variable (Hammarlund APC-140-B).

 C_{g} -10- $\mu\mu$ f, midget variable (Hammarlund HF-15X with one stator plate removed).

C₈-250-µµf. variable (Hammarlund MC-250M).

C4-730-µµf, variable (Broadcast receiver replacement, 365) $\mu\mu$ f, each section, connected in parallel).

CR₁-20-ma, 130-volt selenium rectifier.

J₁, J₂—Coaxial cable connector, SO-239.

J₃-4-pin tube socket.

L₁-3³/₄ turns No. 18 at grid end of L₂, tapped 2 turns from around end.

La-50 turns No. 24, 1% inches long on %-inch diameter threaded ceramic form, Tapped at 5, 8, 13 and 25 turns from grid end.

L_s-4½ turns No. 14, 1¾6 diam., % inch long.

L-18 turns No. 16, 2-inch diameter, 10 t.p.i. Tapped at 11/8, 51/s and 111/s turns from plate end. (B&W 3907-1).

P₁-4-prong plug, with jumper connections as shown.

RFC₁-2.5-mh. 100-ma. r.f. choke (National R-50).

RFC2-5 turns No. 16 wire, wound on 100-ohm 1-watt resistor. RFC₃-1-mh. 500-ma, r.f. choke (Johnson 102-752).

RFC4-2.5-mh. 125-ma. r.f. choke (National R-100S).

S₁-2-pole 6-position (5 used) miniature ceramic switch (Centralab PA-2002).

S₂—1-pole 6-position (5 used) ceramic switch (Centralab 2501). S₂-2-pole 6-position (5 used) non-shorting miniature ceramic switch. (Centralab PA-2003). Alternate contacts used only, to increase voltage rating.

S₄—S.p.s.t. toggle switch.

T₁-6.3-volt filament transformer (Stancor P-6134).

Z₁, comprising C₁, L₂ and S₁, is Harrington Electronics GP-20L unit. Capacitors showing polarity are electrolytic; 680-44f. capacitors are silver mica, .001-4f, are ceramic.

Connection from the chassis washers Ç by mounting soldering made

terminal connected between through place and at the the compartment via

mounting screws

ceramic capacitors

well-insulated

feed-through

of RFC3

ground to

screen and heater

grounded side of the grid-circuit

inside of the cable and not the outside.

available

neutralizing

capacitor,

C2,

hardware stores, and it is an easy matter to bend a piece of it to form the cover. Make the cover with lips on the vertical portion that slip tightly over the sides of the Minibox, and with a bend at the bottom that can be fastened to the chassis. Another piece of cane metal should be cut to serve as a bottom cover; mounting the chassis on rubber feet lifts it above the table and permits good air circulation through the unit.

The self-supported inductor L_3 can be wound on the envelope of one of the 6DE4 rectifiers, removed and pulled apart slightly to give the specified winding length. The taps on L_4 are made by first bending inward the wire on either side of the turn to be tapped, then looping the tap wire around the turn and soldering it securely in place. Both L_3 and L_4 are supported only by their leads.

Testing and Adjustment

With all tubes in their sockets except the 6146, the line cord should be plugged in and the power switch turned on. The bias-supply 0A3 should glow immediately and the rectifier filament and

heaters should light up. The screen-supply regulators should glow. If a voltmeter is available, the high-voltage supply should show first around 400 volts, and then rise slowly to about 950 volts. Switch off the power; the plate supply voltage should decay to less than 100 in under 20 seconds, indicating that the 40,000-ohm resistors are "bleeding" the supply. Note also how long it takes for the voltage to reach a value of only a few volts: this will demonstrate forcefully how long it takes to discharge a high-capacitance filter.

When the power supply has discharged, plug in the 6146, connect the plate cap, and set S_4 to STAND BY. Set the neutralizing capacitor C_2 at half capacitance and the band switches on 80 meters. Turn on the power and set the meter switch, S_3 , to read plate current. The 6146 heater should warm up. Now flip S_4 to operate; the meter should read 10–20 ma. (.2–.4 on the scale). Switching to read screen current, the meter should show under 1 ma. (2 divisions on the meter). There should be no grid current.

Turn off the power and remove the three

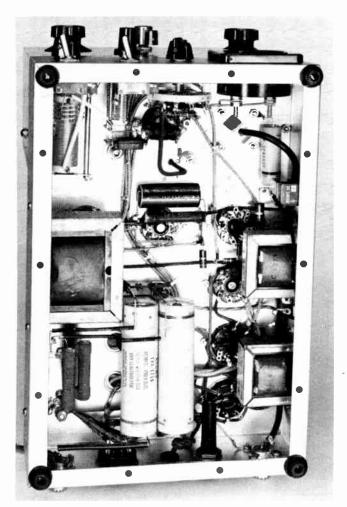


Fig. 6-51-Bottom view of the all-purpose amplifier. The 150-ma, filter choke is mounted on the left-hand wall; the smaller filter choke, the small filament transformer (Ta in Fig. 6-50) and the selenium rectifier are mounted on the righthand wall. The strap of aluminum, visible below the meter at the top right, provides additional support for the length of RG-58/U cable that runs to the output coaxial connector. All power leads except the high voltage to the plate are run in shielded wire.

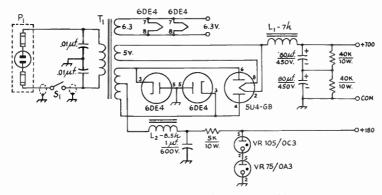


Fig. 6-52—Power supply section of the all-purpose amplifier.

L₁—7-henry 150-ma. choke (Stancor C-1710).

L₂-81/2-henry 50-ma. chake (Stancor C-1279).

P₁-Fused line plug, 3-ampere fuses.

S₁-S.p.s.t. toggle.

T₁-800 v.c.t. at 200 ma., 6.3 v. at 5 amp., 5 v. at 3 amp. (Allied Radio Knight 62 G 033).

rectifier tubes. Connect at J_1 the driver or excitation source to be used - less than a watt is required for linear operation, and only a shade more for Class C. Use the drive at a high frequency, such as 21 or 28 Mc. Turn on the amplifier and switch the band switches to the band corresponding to the excitation-source frequency. Adjust the grid tuning capacitor for a show of grid current; peak the tuning and (if necessary) adjust the excitation for a half-scale reading of grid current. With the loading capacitor C_4 set at half scale, swing the tuning capacitor C₃ through its range. Watch carefully for a slight flicker in grid current. If one is found, adjust the neutralizing capacitor C_2 until the flicker is minimized. The amplifier is now neutralized. Alternatively, a sensitive detector of r.f. can be coupled at the output connector, J_2 , and used instead of the grid-current flicker. Adjust C2 for minimum r.f. in the output when the plate circuit is tuned through resonance. Turn off the power switch and disconnect the excitation source.

Remove the sensitive detector, if used, and replace the rectifier tubes. Turn on the power and switch the meter to read plate current. With the grid and plate circuits switched to the same band (10, 15, 20 or 40) it should be possible to swing the grid and plate tuning to any combination of settings with no change in plate current reading. This indicates that the amplifier is stable and free from oscillation. (The amplifier can be made to oscillate on 80 meters with no grid or plate loading, but in loaded operation it will be stable.)

The antenna and excitation can now be connected and the amplifier used in normal fashion. Used as a linear amplifier, the excitation should be adjusted just below the level that would kick the grid-current indication on signal peaks. Proper loading will be obtained when a steady carrier just under the grid-current level is used for drive and the loading at resonance is set for

about 100 ma. plate current. Under these conditions of loading, a sideband signal will kick the plate current to about 40 or 50 ma. on peaks. Measured p.e.p. input before clipping should be 60 to 70 watts.

When used as a Class-C amplifier, the drive should be increased to where about 2 to 3 ma. grid current is drawn, and the loading to where the 6146 draws about 125 ma. If the amplifier is plate modulated, the plate current should be reduced to 95 ma., to stay within the tube ratings.

Since the amplifier uses a fixed and "stiff" screen supply, it is good practice always to bring up the excitation and loading together, while checking to see that the screen current never exceeds about 15 ma. In normal Class-C operation the screen current will run around 10 ma.

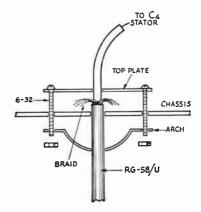


Fig. 6-53—Exploded view of the cable clamp used to hold the coaxial cable running to J_2 . The top plate is a $1\frac{1}{2}$ -inch square of sheet aluminum with holes at the four corners for 6-32 screws. The arch is a $\frac{1}{2}$ 6-inch wire strap that mounts diagonally under the chassis. When tightened, the top plate clamps the cable braid to the chassis; the arch lends support to the cable.

A SELF-CONTAINED 500-WATT TRANSMITTER

Figs. 6-54 through 6-59 show the details of a 500-watt c.w. transmitter, completely self-contained except for the external remote v.f.o. tuning box shown in Figs. 6-58 and 6-59. Provision is made for introducing s.s.b. input at the grid of the driver stage. While plate modulation can be applied to the final amplifier in the usual manner, ratings of the plate power supply limit the safe input to about 250 watts.

The circuit is shown in Fig. 6-57. Switch S_2 permits either v.f.o. or crystal-controlled operation using a 6AH6 oscillator. Either 80- or 40-meter crystals may be used. The v.f.o. circuit is in the 80-meter band and S_1 selects either of two frequency ranges — 3.5 to 4 Mc. for complete coverage of all bands, and 3.5 to 3.6 Mc. for greater bandspread over the low-frequency ends of the wider bands. The plate circuit of the oscillator is on 40 meters for all output bands except 80 meters where it is non-resonant.

A 6CL6 buffer separates the oscillator and the first keyed stage. This stage doubles to 20 meters for 20- and 10-meter output and triples to 15 meters. The driver is a 2E26 which doubles to 10 meters and works straight through on all other bands. This stage is neutralized and a potentiometer in its screen circuit serves as an excitation control.

The final is a 7094, also neutralized, with a pi-network output circuit using a B&W 851 band-switching inductor unit.

A differential break-in keying system using a 12AU7 is included. Both the final amplifier and driver are keyed by the grid-block method. The differential is adjusted by R_1 . Clicks are prevented by envelope-shaping circuits which include C_7 , C_{11} and the grid-leak resistances.

The 100-ohm meter shunts give a full-scale reading of 50 ma., the 51-ohm shunts a full-scale reading of 100 ma., and the 10-ohm resistor in the negative high-voltage lead provides a 500-ma. scale.

Power Supply

The plate transformer in the high-voltage supply uses a transformer designed for a con-

ventional full-wave rectifier circuit with an ICAS d.c. output rating of 300 ma. at 750 volts. A bridge rectifier is used with this transformer so that an output voltage of 1500 is obtained. The short duty cycle of c.w. or s.s.b. operation makes it possible to draw up to the rated maximum of the 7094 (330 ma.) through a choke-input filter without a prohibitive rise in transformer temperature.

The low-voltage supply has two rectifiers. A full-wave rectifier with a capacitive-input filter provides 400 volts for the plate of the driver and the screen of the final amplifier. A tap on a voltage divider across 400 volts provides 300 volts for the plates of the oscillator, buffer and keyer tubes. A half-wave rectifier with a choke-input filter supplies 250 volts of bias for the keyer and fixed bias for the 2E26 and 7094 when they are operating as Class AB₁ linear amplifiers.

Control Circuits

 S_7 is the main power switch. It turns on the low-voltage, filament and bias supplies. Until it has been closed, the high-voltage supply cannot be turned on. In addition to turning on the high-voltage supply, S_8 operates the relay K_1 which applies screen voltage to the final amplifier. Thus, to protect the screen, screen voltage cannot be applied without applying plate voltage simultaneously. J_8 is in parallel with S_8 so that the high-voltage supply can be controlled remotely from an external switch. Also, in parallel with the primary of the high-voltage transformer is another jack, J_7 , which permits control of an antenna relay or other device by S_8 if desired.

The v.f.o.-set switch S_5 turns on the exciter and grounds the screen of the final amplifier.

 S_2 has three positions. One is for crystal control, the second for v.f.o. operation, and the third position is for operating the last two stages of the transmitter as linear amplifiers with an external s.s.b. exciter. In addition to shifting the input of the driver stage from the buffer amplifier to an s.s.b. input connector, fixed bias is provided for AB_1 operation of both stages.

Construction

The transmitter is assembled on a 17 imes 13 imes

Fig. 6-54—A 500-wott transmitter. Power supplies and a differential keyer are included. It operates with the external v.f.o. tuner shown in Fig. 6-59. Controls along the bottom, from left to right, are for low-voltage power, v.f.o./crystals/s.s.b. switch, driver tank switch, driver tank capacitor, final loading, v.f.o. set switch, and high-voltage. Above, from left to right, are controls for excitation, final tank switch, final tank capocitor and meter switch. The band-switch pointer is made by cutting down the metal skirt of a dial similar to the one to the right.

All dials are Johnson.



World Radio History

Fig. 6-55—The only shielding required on top of the chassis is the amplifier enclosure shown. A perforated cover for the enclosure is not shown.

4-inch aluminum chassis with a 19 × 12½-inch panel. The amplifier enclosure measures 8½ inches wide, 8½ inches deep and 7½ inches high. The three permanent sides shown in Fig. 6-55 can be bent up from a single sheet of solid aluminum stock. The top and back (not shown) are made from a sin-


gle piece of Reynolds perforated sheet aluminum. The tube socket is mounted on $\frac{3}{4}$ -inch ceramic cones over a large hole cut in the chassis and covered with a patch of perforated sheet. The tank capacitor C_{15} is mounted on metal spacers to bring its shaft level up to that of the switch on the B&W inductor which is mounted directly on the chassis. The two shafts are spaced 4 inches.

Exciter

A 4 \times 5 \times 6-inch aluminum box is used as the foundation for the exciter. The driver tank capacitor is centered on the chassis with its center approximately 3 inches back from the front edge of the chassis. The capacitor specified has an insulated mounting. If an uninsulated capacitor is substituted, an insulating mounting must be provided. The shafts of S_2 and S_3 are spaced $2\frac{1}{2}$ inches and centered on the front end of the box. On the side of the box toward the tuning capacitor, the oscillator tube, the buffer tube, the low-frequency section (L_6) of the driver tank coil, and the 2E26 are lined up so as to clear the tank capacitor and its shaft. The

latter is fitted with an insulated coupling and a panel-bearing unit. The slug-tuned coils are mounted in holes near the bottom edge of the box. Neutralizing capacitor C_8 is mounted at the rear end of the box, close to the 2E26 socket. The high-frequency section (L_5) of the tank coil is suspended be-

Fig. 6-56—The exciter is assembled using a standard aluminum box as the foundation. The perforated cover has been removed. The bottom of the chassis should also have a perforated metal cover.

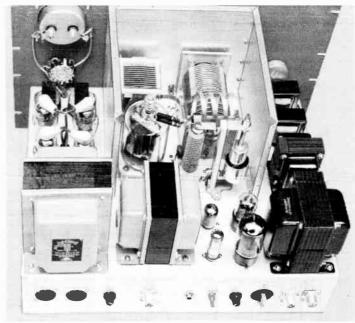


tween the outer end of the low-frequency section and the plate cap of the 2E26. Coil-tap leads run through small feed-through points or grommeted clearance holes in the side of the box.

The loading capacitor C_{16} is placed so that its shaft is symmetrical with the shaft of S_3 , and S_5 is spaced from it to balance S_2 at the other end.


The V.F.O. Tuner

The v.f.o. timer is assembled in a $5 \times 6 \times 9$ -inch aluminum box (Premier AC-596). The dual tuning capacitor C_2 has 7 plates, 4 rotor and 3 stationary, in each section. In the front section, which is used to cover the entire 80-meter band, the two rotor plates nearest the front should be removed. This leaves two rotor plates and two active stator plates, the front stator plate being inactive. In the rear section, the front rotor plate and the last two rotor plates are removed. This leaves one rotor plate riding between two stators.

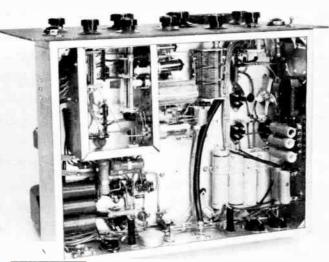The capacitor is mounted on a bracket fastened against the bottom of the box, although it could be mounted from the front cover with spacers to clear the hub of the Millen 10035 dial. The shaft of the capacitor should be central on



World Radio History

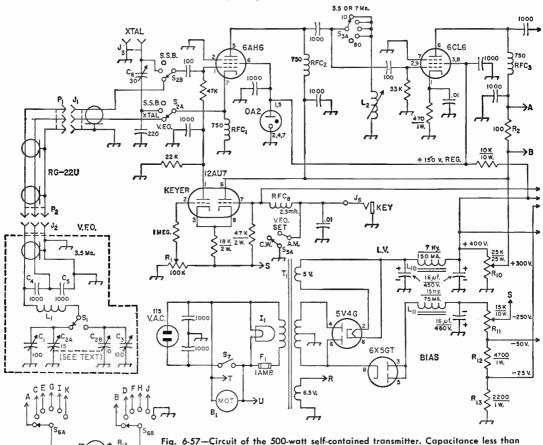

B₁-Blower (Allied 72P715).

C₁, C₃-100- $\mu\mu$ f. air trimmer (Hammarlund APC-100-

C₂—Midget dual variable, 25 μμf. per section (Johnson 167-51 altered as described in the text).
C₄, C₅—0.001-μf. silver mica.

 $C_6 = 30 - \mu \mu f$. mica trimmer (National M-30).

C7, C11-0.1-µf. paper (keyer shaping).

 $C_8-30-\mu\mu f$, miniature variable (Johnson 160-130).

 $C_0-100-\mu\mu f$. midget variable (Johnson 167-11).

 C_{10} = 330- $\mu\mu$ f. mica.

 $C_{12}-10-\mu\mu f$. neutralizing capacitor (Johnson 159-125).

 C_{13} -0.001- μ f. 3000-volt disk ceramic.

 C_{14} =0.001- μ f. 5000-volt ceramic (CRL 858S).

 C_{15} = 250- $\mu\mu$ f. 2000-volt variable (Johnson 154-1).

C₁₆—Triple-gang broadcast variable, 365 μμf, or more per section, sections connected in parallel.

l₁, l₂-One-inch 115-volt panel lamp.

J₁, J₂—Cable connector for RG-22/U (Amphenol 83-22R, UG-103/U).

J₃-Crystal socket (Millen 33102).

J₄, J₅—Coaxial receptacle (SO-239).

J₆—Key jack, open circuit.

J₁, J₈—Chassis-mounting a.c. receptacle (Amphenol 61-F).

K₁—S.p.s.t. 115-volt a.c. relay (Advance GHA/1C/ 115VA or similar).

0.001 μ f. are in $\mu\mu$ f. Fixed capacitors of capacitance greater than 100 $\mu\mu$ f. should be disk ceramic, except as noted below. Fixed capacitors of 100 $\mu\mu$ f. and 220 $\mu\mu$ f. should be mica. Capacitors marked with polarity are electrolytic. Resistors not otherwise marked are ½ watt. R.f. chokes in μ h. unless otherwise marked.

L₁-35 \(\mu\hat{\text{h}}\).-32 turns No. 18, 2 inches diameter, 2 inches long (Airdux 1616).

L₂-Approx. 10 μh.-65 turns No. 26 enam., on %inch iron-slug form (Waters CSA-1011-3).

 L_3 —Approx. 2 μ h.—16 turns No. 26 enam., closewound at center of form similar to L_2 .


L₄—Approx. 1 µh.—13 turns No. 26 enom., ½ inch long at center of form similar to L₂.

L_s—16 turns No. 20, 3/4 inch diameter, 1 inch long, tapped at 10 turns and 13 turns from L_s end (Airdux 616).

L_e—40 turns No. 16, 1½ inches diameter, 2¾ inches long, tapped at mid point and at L_s end (Airdux 1016).

L₇-3 turns No. 14, ½ inch diameter, ¾ inch long.
L₈-4 turns ¾₆ × ½₆-inch copper strip, 1¾ inches diameter, 2½ inches long (part of B&W 851 coil unit).

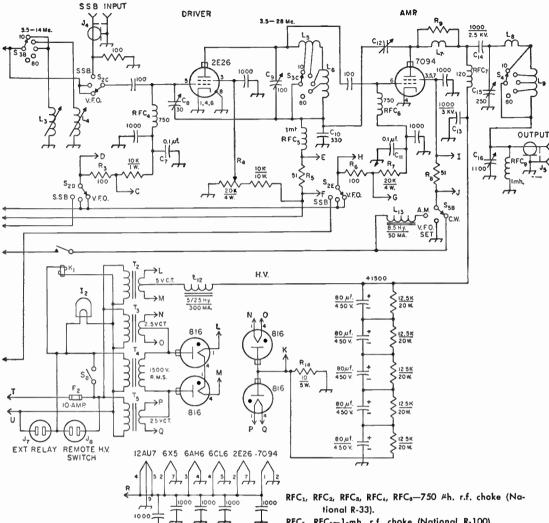 $L_0-4\frac{3}{4}$ turns No. 8, $2\frac{1}{2}$ inches diameter, $1\frac{3}{4}$ inches long, tapped at $1\frac{3}{4}$ turns from L_8 end, plus $9\frac{1}{2}$ turns No. 12, $2\frac{1}{2}$ inches diameter, $1\frac{1}{2}$ inches long, tapped at 6 turns from output end (part of B&W 851 coil unit).



L₁₀-7-hy. 150-ma. filter choke (Stancor C-1710). L₁₁-15-hy. 75-ma. filter choke (Stancor C-1002). L_{12} -5/25-hy. 300-ma. swinging filter choke (Triad C-33A).

M1-Shielded O- 5-ma. d.c. milliammeter, 31/2-inch rectangular (Phaostron).

 P_1 , P_2 —Plug for RG-22/U cable (Amphenol 83-22SP). R₁-100,000-ohm potentiometer.

 R_2 , R_3 , R_6 —100 ohms, 5%.

R₄-20,000-ohm 4-watt potentiometer (Mallory M20-

Rs, Rs-51 ohms, 1 watt, 5%.

R₇-Two 10,000-ohm 2-watt resistors in series.

Ro-Three 100-ohm 1-watt noninductive resistors in parallel.

R₁₀-25,000 ohms, 25 watts with slider.

R₁₁-15,000 ohms, 20 watts, with slider.

R₁₂-4700 ohms, 1 watt.

R₁₃-2200 ohms, 1 watt.

R₁₄-10 ohms (Five 51-ohm 1-watt 5% resistors in parallel).

 $R_{15}-1000$ ohms, $\frac{1}{2}$ watt 5%.

RFC₅, RFC₉-1-mh. r.f. choke (National R-100).

RFC₇-120 μ h. r.f. choke (Raypar RL-101).

RFC₈-2.5-mh. r.f. choke (National R-100).

S₁-Single-pole ceramic rotary switch (Centralab 2000, 2 of 12 positions used).

S₂—Two-wafer ceramic rotary switch (Centralab PA-300 index, PA-4 wafers. S2A and S2B are on one wafer, S_{2C} , S_{2D} nd S_{2E} on second wafer).

S₈-Three-wafer ceramic rotary switch (Centralab PA-301 index, wafers PA-0, 5 positions used). S4-Part of B&W 851 coil unit.

Sz-2-pole 3-position ceramic rotary switch (Centralab 2003, two positions used).

Se-Double-pole ceramic rotary switch (Centralab 2003).

S7, S8-S.p.s.t. toggle switch.

T₁—Power transformer: 750 v.a.c., c.t., 150 ma.; 5 voits 3 amps.; 6.3 voits, 4.7 amps. (Thordarson 22R06).

T₂, T₃—Filament transformer: 2:5 volts, c.t., 3 amps. (Triad F-1X).

T₄-Plate transformer: 1780 volts, c.t., 310 ma., center tap not used (Triad P-14A).

T₅-Filament transformer: 5 volts, c.t., 3 amps. (Triad F-7X).

HIGH-FREQUENCY TRANSMITTERS

the front cover. The coil is suspended between a pair of $2\frac{1}{2}$ -inch ceramic pillars (Millen 31002). It is placed immediately to the rear of the tuning capacitor. The two air trimmers, C_1 and C_3 , are mounted on the top side of the box with their shafts protruding so that they can be adjusted from the top. The bandspread switch is mounted in one end of the box and the cable connector at the other end.

The unit is housed in a standard cabinet (Bud C-1781) having an 8 × 10-inch panel. The dial should be fastened to the panel, making sure that the hub of the dial lines up accurately with the shaft of the tuning capacitor. Then the box is inserted in the cabinet through the front opening. The switch shaft goes out through a hole drilled in the side of the cabinet, and the cable



Fig. 6-58—The remote v.f.o. tuning unit is housed in a stondord metal cobinet. The cable at the right plugs into the main chassis.

goes through a hole in the opposite end to the cable connector. The dial should be set to read zero at maximum capacitance of the tuning capacitor. The box should be supported on spacers.

Adjustment

With all tubes except the rectifiers out of their sockets, the power supplies should be checked first to be sure that they are functioning properly. The voltage output of the low-voltage supply should be in excess of 400 volts, the biasing voltage 300 or more and the high voltage above 1500. The slider on the low-voltage bleeder should be set at approximately three quarters of the way from ground. The slider on the bias-supply bleeder should be set for a reading of -250 volts to ground.

Plug in the oscillator and buffer tubes and an 80-meter crystal if one is available; otherwise connect the v.f.o. tuner. With the low-voltage supply turned on, the 0A2 should glow. When the key is closed, the 0A2 should dim but stay ignited. If it does not, the value of the 10K VR resistor should be reduced.

The v.f.o. can now be adjusted to frequency. Set C_2 at maximum capacitance. Set S_1 to the 80-meter position. Adjust the 80-meter trimmer until a signal is heard at 3500 kc. on a calibrated

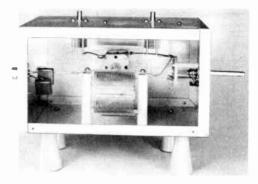


Fig. 6-59—Interior of the v.f.o. tuning box showing the mounting of the coil and other components.

receiver. Then set the receiver to 4000 kc. and tune the v.f.o. until the signal is heard. If the signal is not close to 100 on the dial, carefully bend the rear rotor plate of the 80-meter section of \mathcal{C}_2 outward a little at a time to get the desired bandspread. Each time this adjustment is made, the trimmer should be reset to bring 3500 kc. at zero on the dial.

The same procedure should be followed in adjusting for the other v.f.o. range, aiming for 3600 kc. (or above if desired) at 100 on the dial.

The 2E26 should now be plugged in and the excitation control R_4 set at the ground end (zero screen voltage). S_2 should be set in the v.f.o. position. With low voltage on and the key closed, a 2E26 grid-current reading should be obtained with the band switch in the 80-meter position. With the switch in the 40-meter position, the slug of L_2 should be adjusted for maximum grid current to the 2E26. With the band switch in the 20-meter position, L_3 should be adjusted for maximum grid current, and then the slug of L_4 should be adjusted for maximum grid current with the band switch in the 15-meter position.

Now insert the 7094 in its socket and neutralize the 2E26 as described earlier in this chapter.

Testing of the final amplifier requires a load applied to the output connector. Two 150-watt lamps connected in parallel should serve the purpose. Turning on the high voltage will also apply screen voltage through the relay K_1 . With both band switches set to 10 meters, and C_{16} set at about half capacitance, quickly tune the output circuit to resonance as indicated by the plate-current dip. The load lamp should show an indication of output. Switch the meter to read grid current and neutralize as described earlier in this chapter. After neutralization the amplifier can be loaded to rated plate current. If it is above the rated maximum value, increase C_{16} and retune to resonance, or decrease C_{16} if the plate current is below the rated value.

With the final adjusted and the entire transmitter operating, make a final check on the voltage at the tap on the low-voltage supply, adjusting the slider if necessary to bring the voltage to 300 with the key closed. Be sure to turn off all voltages each time an adjustment is made.

The last adjustment is in the keyer. Adjust the potentiometer R_1 to the point where the oscil-

lator cannot be heard between dots and dashes at normal keying speed.

AN ALL-PURPOSE 813 AMPLIFIER

Figs. 6-60 through 6-63 show the circuit and photographs of an 813 amplifier designed for c.w., a.m., or s.s.b. operation. Provision has been made for convenient changing from one mode to another as well as to any of the bands from 80 through 10 meters.

The circuit is shown in 6-61. A turret-type grid circuit is used and the output circuit is a pi network designed to work into coax cable. The inductor is the rotary-type variable. Provision for neutralizing is included. R_1 is a parasitic

suppressor.

For Class-C c.w. or phone operation, S_4 is open. The 90 volts of fixed bias, furnished by a small bias supply and regulated by the VR90, is augmented by a drop of about 50 volts across the grid-leak resistor R_2 at a normal grid current of 15 ma. This brings the total bias to 140 volts. With S_4 closed, the grid leak is short-circuited and the 90 volts of fixed bias alone remains for AB₂ s.s.b. operation. (An advantage in AB₂ for c.w. operation is that it preserves the keying characteristics of the exciter better than with Class-C operation.) R_3 should be adjusted so that the VR90 just ignites with no excitation.

Screen voltage is regulated at 750 volts by a string of five 0.42s for s.s.b. operation. When the grid drive is increased for Class-C operation, the screen current increases, increasing the drop across the screen resistor R_5 , and the screen voltage falls to 400. The regulators then lose control and the amplifier is ready for plate-screen modulation.

The screen is protected against excessive input, should the load or plate voltage be removed, by the overload relay K_1 . The tripping point is set at 40 ma. by the variable shunt resistor R_4 . If the relay trips, current through R_6 will hold the screen circuit open until plate voltage is removed. One meter, M_1 , measures cathode cur-

rent, while the other meter, M_2 , may be switched to read either grid current or screen current.

Forced-air ventilation is always advisable for a medium- or high-power amplifier if it is buttoned up tight to suppress TVI. A surplus 100 c.f.m. blower does the job more than adequately.

Construction


The amplifier is built on a $13 \times 17 \times 4$ -inch aluminum chassis fastened to a standard 1234×19 -inch rack panel. The r.f. output portion is enclosed in a $12\frac{1}{2} \times 13 \times 8\frac{1}{2}$ -inch box made of aluminum angle and sheet. The VR tubes, relay, blower and meters are mounted external to the box.

The grid tank-circuit components are mounted underneath the chassis and are shielded with a $5 \times 7 \times 3$ -inch aluminum box. A standard chassis of these dimensions might be substituted. The bias and filament transformers are in a second box measuring 6 by 3 by 3 inches. This type of construction, together with the use of shielded wire for all power circuits, was followed to reduce TVI to a minimum. Each wire was bypassed at both ends with 0.001-µf. ceramic disk capacitors. L4 can be adjusted to series resonate with the $600-\mu\mu f$, capacitor at the frequency of the most troublesome channel. A Bud low-pass filter completes the TVI treatment. As a result, the amplifier is completely free of TVI on all channels even in most fringe areas.

Adjustment


In the pi network, the output capacitors are fixed. However, the adjustment of the network is similar to that of the more conventional arrangement using a variable portion of the output capacitance. The only difference is that the "fine" loading adjustment is done with the variable inductor.

Fig. 6-60-W4SUD's all-purpose 813 amplifier. The output-capacitor switch (coarse loading) is above the turns counter for the variable inductor. Dials near the center are for the plate tank capacitor C4 (above) and the grid tank capacitor C1 (below). To the right of the dials are the controls for the plate padder switch S₃ (above) and the grid band switch S₁ (below). The toggle switch below the meters is the mode switch S₄ with the meter switch S₅ to the left. Ventilating holes are drilled in the cover in the area above the tube. The output connector is on the left-hand wall of the shielding box.

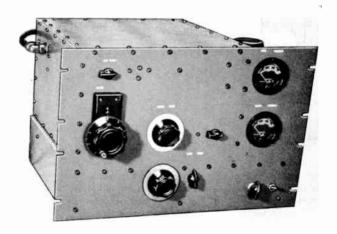

Unless otherwise designated, capacitances are in $\mu\mu$ f.
Capacitors marked with polarity are electrolytic. Other capacitors not listed should be ceramic.

Resistances are in ohms.

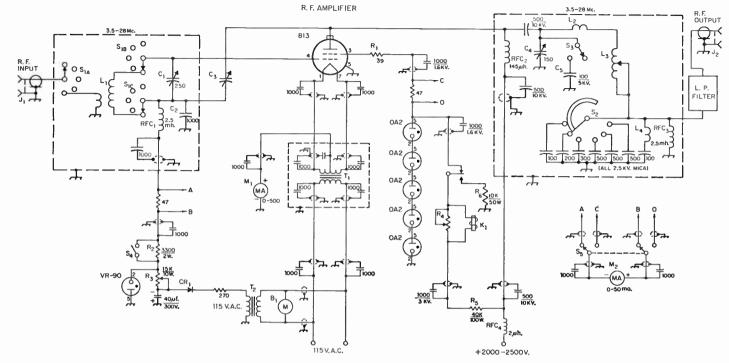

B₁-Ventilating blawer, 100 c.f.m. (surplus).

C1-250-µµf, variable (Hammarlund MC-250-M).

 $C_2 = 1000 - \mu \mu f$. mica.

 C_3 —Neutralizing capacitar, 10 $\mu\mu$ f. maximum (Jahnsan 159-250).

C₄-150-\(mu\)ft. 6000-valt variable (Jahnson 153-12).

C₅—100-μμf, 5000-valt fixed capacitar (surplus vacuum Amperex VC-100, ar twa 200-μμf, 5000valt micas in series).

CR₁-130-valt 50-ma. selenium rectifier.

J₁, J₂—Caaxial receptacle (SO-239).

K₁—Screen averload relay, 2500 ahms, 7 ma. (Patter & Brumfield KCP5).

L₁-3.5 Mc.-32 turns Na. 20, 1-inch diam., 2 inches lang, 5-turn link (B&W 3015 ar Airdux 816).

-7 Mc.-18 turns Na. 20, 3/4-inch diam., 1 1/8 inches lang, 3-turn link (B&W 3011 or Airdux 616).

-14 Mc.-10 turns Na. 18, %-inch diam., 11/4

inches lang, 2-turn link (B&W 3006 ar Airdux 508).

—21 Mc.—7 turns Na. 18, %-inch diam., % inch lang, 1-turn link (B&W 3006 or Airdux 508).

-28 Mc.-5 turns No. 18, %-inch diam., % inch lang, 1-turn link (B&W 3006 ar Airdux 508).

 L_2 —3 turns $\frac{3}{6}$ -inch copper tubing, 1-inch diam., 1 $\frac{3}{4}$ inches lang.

L₁-15-uh, variable inductor (B&W 3852).

Lı-See text.

M₁, M₂-3½-inch d.c. milliammeter.

R₁-39 ahms, ½-watt carban.

R₂-3300 ohms, 2 watts.

R_a-15,000 ahms, 10 watts with slider.

R₄—2000-ahm 4-watt variable resistar (Mallary M2-MPK).

RFC₁ RFC₃—2.5-mh. r.f. chake (National R-50 or similar).

RFC2-Plate r.f. choke (National R-175-A).

RFC4-V.h.f. chake (National R-60).

S₁—Rotary switch: 3 wafers, 3 pales, 11 positions per pole, 5 positions used (Centralab PA-0 wafers, PA-301 index).

S₂—Ratary switch: single pole, 10 pasitions, pragressively shorting, 6 positions used (Centralab PA-2042).

S₃—Rotary switch: s.p.s.t., ceramic (antenna link switch fram BC-375 tuning unit, ar Communications Praducts Model 65).

S₄-S.p.s.t. taggle switch.


S₅-D.p.d.t. rotary switch (Centralab 1405).

T₁—Filament transfarmer: 10 volts, 5 amp. (Thardarsan 21F18).

T₂—Bias transfarmer: 120 valts, 50 ma.; 6.3 valts, 2 amp., filament winding not used; cauld be used for pilat light (Merit P-3045).

813 Amplifier

Fig. 6-62-This view shaws the placement of campanents an the chassis. The 813 sacket is maunted an spacers aver a large clearance hale in the chassis. The several mica autput capacitars are assembled in a stack an a threaded rad fastened ta the left-hand wall of the shielding box. The neutralizing capacitar and the 80meter plate padder are to the right of the tank capacitar. To the right of the bax are the five OA2s (the frant ane hidden), the screen overland relay and the VR90, the blawer and meters.

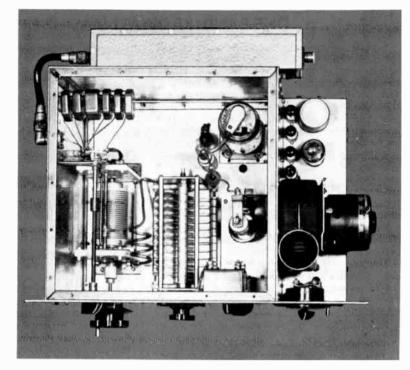


The inductor is fitted with a Groth turns counter, making it easy to return to the proper setting for each band. Until the settings for each band have been found, S_3 should be turned so that all of the output capacitance is in circuit. The inductor should be set near maximum for 80, and approximately half maximum for 40. On the higher-frequency bands, the inductor should be set so that the circuit resonates with the tank capacitor near minimum capacitance. Loading

should increase as the output capacitance is decreased. A change in output capacitance requires a readjustment of C_4 for resonance. When the loading is near the desired point, final adjustment can be made by altering the inductance slightly.

A 20-A or similar exciter is well suited as a driver for this amplifier on all modes. The 813 runs cool at 500 watts input on c.w. and at a little over 500 watts p.e.p. on s.s.b. (Originally described in *QST* for August, 1958.)

Fig. 6-63-Bottom view of the all-purpase 813 amplifier. The grid tank-circuit companents within dashed lines in Fig. 6-62 are enclosed in the bax at lower center. Input links are wound over ground ends of grid coils. Filament and bias transfarmers are in the secand box. The large resistor to the left of the grid box is the screen resistar. The variable resistar in the upper left-hand corner is the relay shunt R4. The selenium bias rectifier is fastened against the left-hand wall of the chassis.

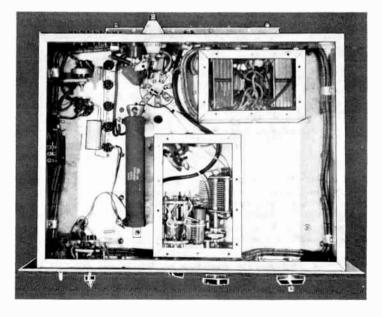

ONE-BAND KILOWATT AMPLIFIERS

Separate kilowatt amplifiers on each of the bands 80 through 10 meters has always been the ne plus ultra of transmitter construction. However, space limitations and cost are the two key factors that have prevented many from realizing this goal. The amplifiers to be described are compact and are constructed economically; the builder may wish to construct one amplifier for his favorite band or the group of five for versatile all-band operation. Advantages of the separate-amplifier philosophy include optimum circuit Q for every band, simplified construction and band switching, less chance for tube failure because each amplifier is pretuned, and fast band changing for the contest-minded. The supply voltages remain on all the amplifiers; only the filament and excitation power are switched to the desired final amplifier.

The availability and proven dependability of the 813 make a pair of them the logical choice for the kilowatt amplifier. A shrewd amateur should have no trouble procuring the tubes through surplus channels or by bartering with local hams.

Referring to the circuit diagram, Fig. 6-65, the

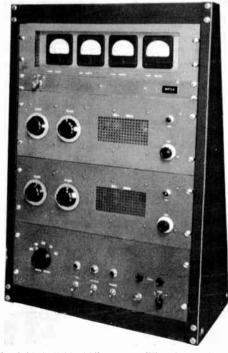


Fig. 6-64—Individual kilawatt amplifiers far twa bands plus camplete metering and all cantral circuits and pawer supplies (except plate) fit handily into a table rack. Amplifiers far five bands plus the plate supply will maunt in flaar rack. Band switch at lawer left (S_B in Fig. 6-65) switches filament supply, excitation and autput cannectians ta all amplifiers in use; screen and plate supplies are cannected to all amplifiers at all times.

amplifier control unit contains the filament, bias and screen supplies. A 3-position mode switch, S_2 , selects the bias for either Class AB_1 or C operation, and in the third position grounds the screen grids, to limit the plate current during initial tuning. Another 3-position switch, S_1 , allows the total or individual screen currents to be read. The latter position is useful in matching tubes. The high-voltage supply should furnish from 1750 to 2250 volts.

Construction

Each amplifier is assembled on a 13×17 -inch aluminum bottom plate. Two $5 \times 13 \times 3$ -inch aluminum chassis are used as the sides of the enclosure. The paint is removed from the back of a 7-inch aluminum rack panel, and a piece of Reynolds cane metal is sandwiched between the panel and the two chassis. A rectangular window in the panel provides additional ventilation and a means for inspecting the color of the tube plates. The top and back of the enclosure are formed from a single piece of cane metal, bent to fit the chassis rear and top. Three lengths of $1 \times 1 \times \frac{1}{16}$ -inch aluminum angle stock are used in the corners of the enclosure, as can be seen in Figs. 6-67 and 6-68.


The variable tank capacitors, C_4 , are mounted on 1-inch stand-off insulators, to bring the shafts to the proper panel height. In the 10-meter amplifier the capacitor shaft must remain above r.f. ground, and a suitable insulated shaft coupling is used. On the other bands, the rotors of the capacitors are grounded to the chassis through metal straps.

On 20, 15 and 10 meters the tank coils are wound self-supporting of ¼-inch diameter soft-drawn copper tubing, and they are supported by their leads. On 80 and 40 the coils are lengths of Air-Dux stock, and they are supported by small ceramic insulators.

The special plate r.f. chokes, RFC₂, are constructed by close-winding No. 24 enameled wire on ¾-inch diameter ceramic insulators. Four-inch long insulators (National GS-4) are used on the 80- and 40-meter bands, and 2-inch long insulators (National GS-3) are used on the other bands. In each case the original base of the insulator is removed and the insulator is mounted on a stand-off (Johnson 135 20). The high-voltage lend and the "cold" end of the choke are connected to a soldering lug mounted between the two insulators.

Bridge neutralization is included in the 20-, 15- and 10-meter amplifiers. The neutralizing capacitors are made from two $\frac{1}{2}$ -inch wide aluminum strips 5 inches long. One strip is connected directly to the plate lead at C_3 and the other is supported by a ceramic feed-through insulator that connects to the rotor of C_1 . The amplifiers are neutralized by adjusting the spacing between the aluminum strips.

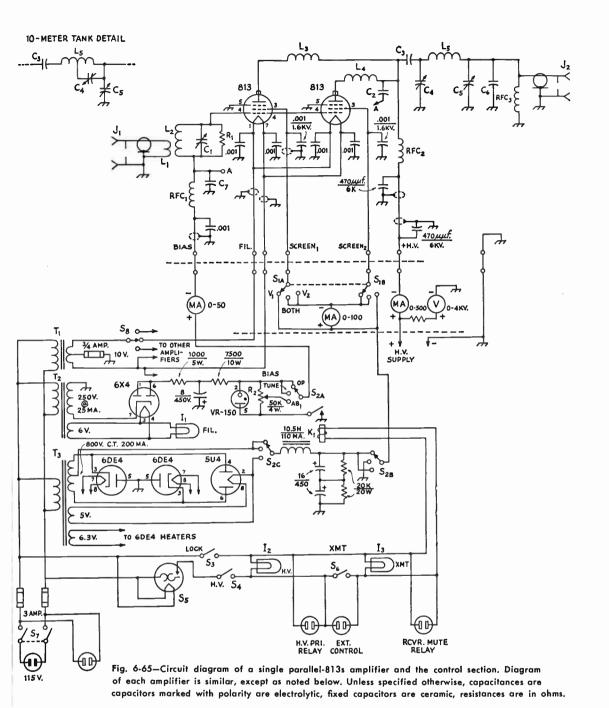The metal ring surrounding the base of the 813



C2-Not used on 80 or 40 meters; see text.

C₃—Two 500-μμf. 20-kv. ceromic (Centralab TV-207) in parallel on 80 m.; single 500-μμf. 20-kv. ceramic on other bands.

 C_1 =0.001- μ f. 1-kv. ceramic on 80 and 40 m.; 240- $\mu\mu$ f. silver mica on other bands.

 l_1 , l_2 , l_3-115 -v. pilot lamp.

J₁, J₂—Coaxial cable receptacle.

K₁-S.p.d.t. relay, 115-v. a.c. coil.

L₃, L₄-Not required on 80 or 40 m.; 6 turns No. 14 on 1/4-inch diam.

 R_1 -10,000 ohms, 2 watts, composition (not wirewound).

R2-50,000 ohms, 4 wotts (Mollory M50MPK).

RFC1-2.5-mh, 75-ma, r.f. choke.

RFC₂—See text.

RFC₃—2.5-mh. 300-ma. r.f. choke.

S₁—Two-pole 3-position rotary switch, shorting type.

S₂—Two-pole 3-position rotary switch, non-shorting type.

S₃-S.p.s.t. lock switch (AHH 81715-L).

 S_s -Time delay relay (Amperite 115N060).

S7-Heavy duty d.p.s.t. toggle.

T₁-10-volt 10-ampere filament transformer (Thordarson 21F19).

T₂-250-volt 25-ma. transformer (Stancor PS-8416). T₈-800-v.c.t. 200-ma., 5- and 6.3-v. heater windings.

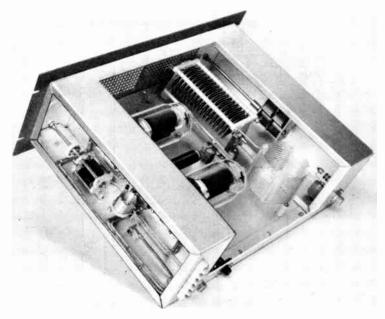


Fig. 6-66—View of the 40-meter amplifier with its cane-metal covering removed. As in each amplifier, the chassis is made from two 5 × 13 × 3-inch chassis and a 13 × 17-inch bose plote. Input and low-voltage leads make up to terminols and jack in center foreground.

should be grounded to the chassis. A piece of Eimac Finger Stock or a homemade contact can be used for the purpose.

All power wiring is done with shielded wire and bypassed as described in Chapter Twenty-Three. The filament leads should be made from No. 14 (or heavier) shielded wire.

The screen and bias supplies plus station control circuits are built on a rack-mounting chassis (Bud CB-1373) behind a 7-inch panel. In the

Class-C position of S_2 , +400 volts is applied to the screens and -150 is connected to the grids. In the Class AB_1 position, the screen voltage is increased to 700 and the grid bias is dropped to a value determined by the setting of R_2 . This latter setting should be one that gives best linearity without exceeding a no-signal plate input of 150 watts for the two 813s; it depends on the plate voltage available. A heavy bleed on the screen supply helps the regulation.

Coil and Capacitor Table					
Band	80	40	20	15	10
C1	100 μμf. (Johnson 100L15)	100 μμf. (Johnson 100L15)	50 μμf. (Johnson 50L15)	50 μμf. (Johnson 50L15)	50 μμf. (Johnson 50L15)
Ca	150 μμf. (Johnson 150E45)	150 μμf. (Johnson 150E45)	35 μμf. (Johnson 35E45)	35 μμf. (Johnson 35E45)	50 μμf. (Hammarlund MC-50-MS)
Съ	710 μμf. (2-gang 365 μμf.)	325 μμf. (Hammarlund MC·325·M)	325 μμf. (Hammarlund MC·325·M)	325 μμf. (Hammarlund MC-325-M)	325 μμf. (Hammarlund MC-325-M)
Св	500 μμf. (Centralab TV-207)	100 μμf. (CRL 850S-100N)			
L ₁	4 t. No. 22*	3 t. No. 22*	2 t. No. 22*	1 t. No. 22*	1 t. No. 22*
L ₂	32 t.p.i. No. 24, 1 inch long, 1 inch diam. (B&W 3016)	16 t.p.i. No. 20 1¼ inch long, 1 inch diam. (B&W 3015)	8 t.p.i No. 18 13/6 inch long, 1 inch diam. (B&W 3014)	8 t.p.i, No. 18 34 inch long 1 inch diam. (B&W 3014)	8 t.p.i. No. 18 ½ inch long, 1 inch diam. (B&W 3014)
Ls	6 t.p.i. No. 12, 3 inch long, 3 inch diam. (Air Dux 2406)	4 t.p.i. No. 12, 3¾ inch long, 2½ inch diam. (Air Dux 2004)	2 t.p.i. ¼-inch copper tubing, 4½ inch long, 2½ i.d.	2 t.p.i. ¼-inch Copper tubing, 3 inch long, 2½ i.d.	2 t.p.i. ½-inch copper tubing, 2 inch long, 2½ i.d. C ₄ tap 2 turns.

^{*} Insulated hookup wire, wound over C_{τ} end of L_{2} .

The unit shown in Fig. 6-65 uses an Ohmite Model 111 switch at S_8 . This is ganged with antenna and excitation switches to permit one-control bandswitching. The relay K_1 is actuated

when the plate supply is turned on; when the relay is open a high bias is applied to the 813s to reduce the plate current to 0 ma. and eliminate receiver noise caused by static plate current.

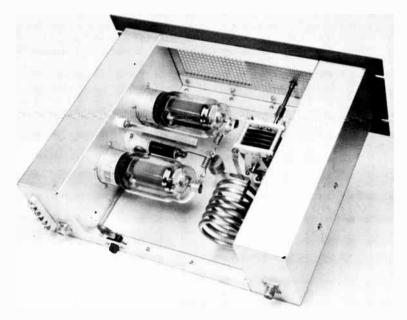


Fig. 6-67—Top view of the 15-meter amplifier. The neutralizing capacitor consists of two strips of aluminum, supported by the plate-blocking capacitor and a feedthrough insulator. It is mounted over the r.f. choke between the two 813 tubes.

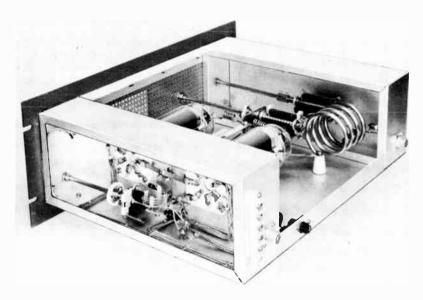


Fig. 6-68—As in the other amplifiers, the 10-meter final uses shielded wires in the filament, screen, and grid-return circuits. For tuning this amplifier uses a small variable capacitor connected across half of the plate coil, to maintain a favorable L/C ratio.

A GROUNDED-GRID HALF KILOWATT

The amplifier shown in Figs. 6-69, 6-71 and 6-72 will run at about 500 watts input on c.w.— or p.e.p. input as an s.s.b. linear — on all bands from 80 through 10 meters. The unit is small enough to sit on the operating table right along with the rest of the station equipment; no need for big racks here.

Using a pair of 811As in parallel in the grounded-grid circuit, this rig is a good one to use following transmitters such as the Viking Ranger, DX-40, Globe Scout, and others of similar power class, for a worth-while increase in power output on c.w. As a linear amplifier following an s.s.b. exciter it requires no swamping because the 811A grids provide a fairly constant load in themselves, and also the fed-through power with grounded-grid presents an additional constant load to the driver. The total driving power needed on any band is less than 20 watts.

An additional useful feature is a built-in directional coupler using a version of the "Mickey Match." Besides its obvious application for checking the s.w.r. on the transmission line to the antenna or for help in tuning up a coaxcoupled antenna coupler, it is practically indispensable as an indicator of relative power output in tuning the amplifier.

The Circuit

A number of tube types could be used in an amplifier of this power class, but the 811As are a good choice because they do not need a bias supply and are not expensive. (Surplus 811s can be used; the ratings are not quite as high but they can be pushed a bit in intermittent service such as c.w. and s.s.b.)

The complete circuit is shown in Fig. 6-70. To save trouble and work, standard components are used throughout — the only special construction is the shielding and a few simple r.f. chokes. The tube filaments are driven directly from coax input from the driver; no tuning is used or is needed in this circuit. The filaments are kept above ground by the B & W type FC15 choke.

The plate tank is the familiar pi network, using a B & W type 851 tapped coil and band-switch assembly. This assembly has been modified slightly in two respects: First, the copper-strip 10-meter coil normally mounted at the top of the rear plate is taken off and moved so that it is supported between the tank assembly and the stator of the tank tuning capacitor as shown in Fig. 6-71. A short length of copper strip is bolted between the free end of the coil and the righthand stator connection of the tuning capacitor, to support the free end. This change is made in order to avoid the long lead that would have to be run from the capacitor to the regular input terminal on the tank assembly, since this terminal is at the right-hand side of the assembly as viewed from the top. The turns of the 10-meter coil are also squeezed together a bit to increase the inductance, because it was found that a rather large amount of capacitance had to be used to tune the circuit to the band with the coil at its original length. The length is now 15% inches between mounting holes.

The second modification is the addition of a pair of switch contacts on the rear switch plate of the tank assembly. There is an extra position on this plate with holes already provided for contacts, and the additional set of contacts is used to switch in fixed output loading capacitance on 80 meters, where a large output capacitance is needed. The variable loading capacitor, C_3 , with the five fixed mica capacitors, C_5 to C_9 inclusive, give continuous variation of capacitance up to 1275 $\mu\mu$ f. on all bands, including the regular switch position for the 80-meter band. However, if the switch is turned to the extra position an additional 1000-µµf. mica capacitor is connected in parallel, so that continuous variation of capacitance to over 2200 µµf. is possible on 80. This takes care of cases where the load resistance happens to be unusually low or reactive.1

¹These contacts can be obtained directly from the manufacturer of the tank assembly. To secure a set of contacts with mounting hardware, send one dollar to

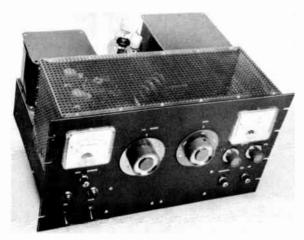


Fig. 6-69—This amplifier operates at a plate input of approximately 500 watts, uses a pair of 811As in grounded-grid, and is complete with power supply on a 13 imes 17 imes 4-inch chassis. The rack panel is 10½ by 19 inches. Front-panel controls include the plate tuning capacitor and band switch in the center, filament and plate power switches with their pilot lights at the lower left, sensitivity control and forward-reflected power switch for the directional coupler at the lower right, variable loading capacitor and auxiliary loadingcapacitor switch underneath the 0-1 milliammeter at the right, and the grid-cathode milliammeter with its switch at the upper left. The filter chake, 866As and plate transformer oc-

cupy the rear section of the chassis.

A 500-ma. d.c. meter is used for reading either total cathode current or grid current alone. The

Barker & Williamson, Beaver Dam and Canal, Bristol, Penna., specifying the type of tank assembly for which they are wanted. The contacts are not catalog items and are not available through dealers. cathode current is read in preference to plate current because of safety considerations. Putting the meter in the hot d.c. plate lead leaves nothing but a little plastic insulation between the high voltage and the meter adjusting screw. It is a bit of a nuisance to have to subtract the grid

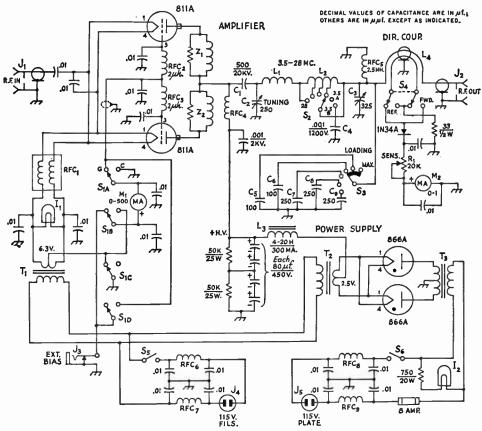


Fig. 6-70—Circuit diagram of the parallel-811A grounded-grid amplifier. Unless otherwise specified, fixed capacitors are disk ceramic, 600-volt rating.

 C_1 =500 $\mu\mu f$., 20,000 volts (TV "doorknob" type). C_2 =250- $\mu\mu f$. variable, 2000 volts (Johnson 250E20). C_3 =325- $\mu\mu f$. variable, receiving type (Hammarlund) MC-325-M).

C4-C0, inc.-1200-volt mica, case style CM-45.

1₁, 1₂-6.3-volt dial lamp, 150-ma. (No. 47).

J₁, J₂-Coax connector, chassis mounting.

J₃-Closed-circuit phone jack.

J₄, J₅—115-volt male connector, chassis mounting (Amphenol 61-M1).

L₁, L₂, S₂—5-band pi-network coil-switch assembly; see text (B & W 851).

L₈—Swinging choke, 4-20 henrys, 300 ma. (UTC S-34).
L₄—Section of coax line with extra conductor inserted; see measurements chapter for construction references.

M₁, M₂—Milliammeter, 3½-inch plastic case (Triplett 327-PL).

R₁—20,000-ohm composition control, linear taper.

RFC₁—Filament-choke assembly, to carry 8 amp. (B & W FC15).

RFC2, RFC3-2 µh. (National R-60).

RFC₄-90 μh.; 4%-inch winding of No. 26, 40 t.p.i., on ¾-inch ceramic form (B & W 800).

RFC₅-2.5 mh., any type.

RFC₆-RFC₉, Incl.—18 turns No. 14 enam., close-wound, 1/2-inch diam., self-supporting.

S₁—4-pole 2-position rotary, nonshorting (Mollory 3242J or Centralab 1450).

S₂-Part of tank assembly; see L₁ L₂.

S₂—Miniature ceramic rotary, 1 section, 1 pole, 6 positions used, progressive shorting (Centralab 2042).

 S_4 —Miniature ceramic rotary, 1 section, 2 poles, 2 positions used, nonshorting (Centralab 2003). S_5 , S_6 —S.p.s.t. toggle.

T₁—Filament transformer, 6.3 volts, 8 amp. min. (UTC S-61).

T₂—Filament transformer, 2.5 volts, 10 amp. (UTC S-57).

T₃—Plate transformer, 3000 volts center-tapped, 300 ma. d.c. (UTC S-47).

Z₁, Z₂-2½ t. No. 16 ½-inch diam., over 100-ohm 2watt carbon resistor. current from the cathode current in order to find the plate current, but it isn't serious. The d.c. grid circuit has a jack, J_3 , for introducing external bias either for blocked-grid keying or for cutting off the plate current during receiving, and a four-pole switch, S_1 , is therefore needed for handling the meter switching while keeping all circuits functioning normally.

The power supply uses 866As with a plate transformer giving 1500 volts each side of the center tap, and working into a single-section choke-input filter. The filter capacitor consists of four 80-µf. electrolytics connected in series to handle the voltage, giving an effective filter capacitance of 20 µf. This supply is running well below its capabilities in the intermittent type of operation represented by c.w. and s.s.b., and the amplifier is somewhat "over-powered" in this respect. A lighter plate transformer can be used since the average current in regular operation is only about half the maximum tube rating of 350 ma. for the pair.

The a.c. inputs to both filaments and plates have TVI filters installed right at the a.c. connectors. The chokes in these filters, RFC_0 to RFC_0 inclusive, are homemade by winding 18 turns of No. 14 enameled wire close-wound on a half-inch dowel or drill,

Construction

The only space available for the filament transformers is below chassis, so these are mounted on the front wall of the chassis as shown in Fig. 6-72. There is plenty of room for all other power-supply parts below chassis, and the photographs make any further comment on this section unnecessary.

The r.f. layout shown in Fig. 6-71 is almost an exact copy of the circuit layout as given in Fig. 6-70. The plate blocking capacitor, C_1 , is mounted on a small right-angle bracket fastened to the left-hand stator connection of the tank capacitor, C_2 . The tube plates are connected to C_1 through individual parasitic-suppressor assemblies, Z_1 and Z_2 . The hot end of the plate

choke, RFC4, also connects to this same point. The tank capacitor is mounted on 34-inch ceramic pillars to bring its shaft to the same height as the switch shaft on the tank-coil assembly. The capacitor is grounded by connecting the bottom of its frame through a half-inch wide strip of aluminum to essentially the same point at which the plate-choke bypass capacitor, a $0.001-\mu f$. 2000-volt disk, is grounded. The ground end of the aluminum strip actually is under the bottom of the plate choke, and the ground lug for the bypass capacitor is just to the left. This strip, plus short leads in the circuit from the tube plates through the tank capacitor to ground, keep the resonant frequency of the loop thus formed well up in the v.h.f. region; this is important because it permits using low-inductance parasitic chokes in shunt with the suppressor resistors, and thus tends to keep the r.f. plate current at the regular operating frequencies out of the resistors. With other tank grounding arrangements originally tried, larger parasitic chokes had to be used and it was impossible to prevent the resistors from burning up when operating on 10, 15 and even 20 meters. Now they do not overheat on any frequency, and v.h.f. parasitics are nonexistent although without the suppressors the parasitics are only too much in evidence.

The output loading capacitors, C_3 through C_9 , are mounted toward the rear so the leads from the tank coil can be kept as short as possible. A length of copper strip is used between the coil and the stator of C_3 ; originally this lead was No. 14 wire but on 10 meters the tank current was enough to heat it to the point of discoloration. The ground lead from the fixed units, made to the rear bearing connection of C_3 , is also copper strip. C_3 and S_3 are operated through extension shafts, using Millen flexible couplings to simplify the alignment problem.

Underneath the chassis, each 811A grid is bypassed directly to the socket-mounting screw nearest the plate choke (right-hand side of the socket in Fig. 6-72). The d.c. leads have small

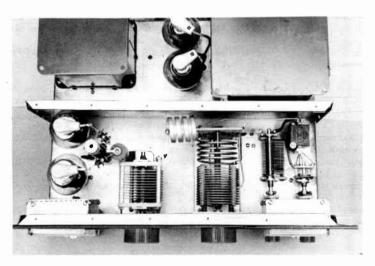


Fig. 6-71—The r.f. section with the shield cover removed. Components here ore readily identifiable by reference to the circuit dioarom. The meters are enclosed in rectongular boxes mode from thin oluminum sheet, formed to be fostened by the meter mounting screws. The bock covers on these boxes ore mode from perforoted oluminum, folded over of the edges ond held on the boxes by sheet-metal screws. The switch for shifting the 0-500 milliommeter (left) from grid to cothode is conceoled by the box which encloses

the meter.

Grounded-Grid Half Kilowatt

chokes, RFC_2 and RFC_3 , with additional bypasses for good r.f. filtering, particularly at v.h.f. since grid rectification generates harmonics in the TV bands. The filament choke, RFC_1 , is mounted so that the filament side is close to the filament terminals on the tube sockets; the other end is bypassed directly to the chassis.

The shielding around the amplifier consists of two pieces of sheet aluminum and a perforated aluminum ("do-it-yourself" type) cover having the shape of an inverted U. Fig. 6-71 shows how the rear wall is made. Its edges are bent to provide flanges for fastening the cover with sheetmetal screws, and there is a similar flange projecting to the rear at the bottom for fastening the wall to the chassis. The front piece extends the full height of the panel and is identically drilled and cut out for meters and controls. It has flanges at the top and extending down the sides from the top to the chassis. The cover itself extends down over the sides of the chassis for about one inch. Numerous screws hold down the cover, to prevent leakage of harmonics.

The shields over the meters are made as described in the caption for the inside top view. Meter leads are bypassed to the shield boxes where they emerge.

Construction of the directional coupler parallels that given for the antenna coupler in Chapter Thirteen.

Operating Conditions and Tuning

The voltage delivered by the power supply is approximately 1500 volts with no drive and with the tubes taking only the no-bias static plate current, which is about 60 ma. At the full load of 350 ma. the voltage is slightly under 1400. Optimum operating conditions for 1400 volts at 350 ma. peak-envelope power input as an s.s.b. linear call for a peak-envelope grid current of 60 ma. The peak-envelope tube power output is close


to 350 watts under these conditions. The same conditions are also about optimum for c.w.

The behavior of the cathode current when tuning a grounded-grid triode amplifier is somewhat confusing, and the meter is principally useful as a check on operating conditions rather than as a tuning indicator. The best indicator of proper tuning of the plate tank capacitor is the forward-power reading of the directional coupler. For any trial setting of the loading controls and driving power, *always* set the plate tank capacitor control at the point which results in a maximum reading on the power-output indicator.

The power indications are only relative, of course, and the sensitivity control should be set to give a reading in the upper half of the scale of the meter.

The objective in adjusting loading and drive is to arrive at maximum power output simultaneously with a plate current of 350 ma. and a grid current of 60 ma. — that is, a total cathode current of 410 ma. when the grid current reading is 60 ma. The loading is critical. If the amplifier is not loaded heavily enough the grid current will be too high and the right value of total cathode current either will not be reached or, if reached, the amplifier will be operating in the "flattening" region as an s.s.b. linear. (It can be operated this way on c.w., however, since linearity is unimportant here.) If the loading is too heavy, the grid current will be low when the cathode current reaches the proper value, but the efficiency will be low. Getting the knack of tuning takes practice, but when done right the tubes will run cool on all bands in regular operation. Running key-down over a period of time may show just a trace of dark red color on the plates since the input and dissipation are somewhat over ratings under these operating conditions, although perfectly satisfactory with keying or s.s.b. voice.

Fig. 6-72-In this below-chassis view, the two filament transformers are at the top, mounted on the chassis wall. The 811A sockets are at the upper left. The rectangular box on the left-hand wall cantains the FC15 filament-choke assembly. The "Mickey Match'' directional caupler is at the upper right. Filter capacitors and the bleeder resistors are in the lawer section. A.c. inlets, fuse halder, bias jack, and the 115volt line TVI filters are an the battom chassis wall.

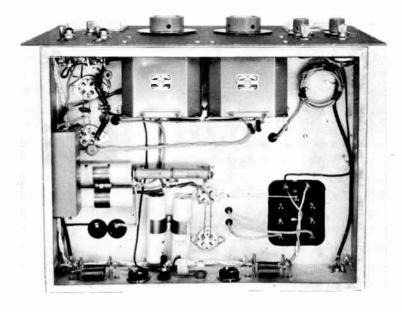

A KILOWATT GROUNDED-GRID AMPLIFIER

The amplifier shown in Figs. 6-73, 6-75 and 6-76 is built around the Penta PL-6580, a high-\$\mu\$ triode designed especially for grounded-grid Class-B r.f. amplifier service. With a plate voltage of from 3000 to 4000, from 700 to 900 watts p.e.p. output can be obtained with about 75 watts driving power. A stabilized bias supply is included that will provide the correct bias for any operating plate voltage between 2500 and 4000.

Referring to the circuit diagram, Fig. 6-74, the cathode (filament) is maintained above ground by the filament chokes RFC_1 and RFC_2 . An L network, tuned by C_1 , provides voltage step-up to the cathode. On 80 meters the capacitor C_1 , together with fixed capacitor C_2 , tunes the filament chokes. On the other bands the fixed capacitor is removed and the proper inductance is shunted across the chokes.

To insure good r.f. grounding of the grid, three 0.001- μ f. disk ceramic capacitors are used between the grid pins and the chassis. The bias supply uses a high-current low- μ 6080 twin triode to stabilize the bias, in conjunction with the 6AU6 control tube and the 0A2 voltage-reference tubes. The bias voltage is set by the position of the arm of R_1 .

The plate circuit of the amplifier departs from more conventional practice in several ways. The output capacitance in the 80-meter condition is relatively small; this is a result of using a low capacitance at C_3 , which in turn lowers the circuit Q and requires a lower output capacitance for proper loading. If a low plate voltage (2500) is to be used, it would be better to increase the capacitance value of C_3 and the capacitance switched across the output on 80 meters. On all of the other frequency ranges the capacitances are more in line with normal Q values. On 15

and 10 meters S_{2B} shorts part of L_4 , to break up a resonance in the unused coil.

Although the PL-6580 requires 5 volts on the filament, a 6.3-volt filament transformer is used. The resistance of RFC_1 and RFC_2 is sufficient to drop the voltage to the correct value. The 6080 regulator and the 6X4 rectifier heaters are also connected to the filament transformer, T_1 .

Construction

Referring to Figs. 6-75 and 6-76, the amplifier is built on a 12 \times 17 \times 3-inch chassis, with a standard 101/2 × 19-inch relay rack panel. Aluminum angle stock is used to form a framework for the perforated-metal sides (not shown in the photographs). To cool the PL-6580, a blower is mounted on the chassis so that the air is pulled in through a perforated-metal side and blown down under the chassis. The chassis, sealed off with an aluminum bottom plate, can only exhaust the air past the tube and, to facilitate this, the tube socket is mounted in a 31/2-inch-diameter hole. The combination of the large hole, the ventilated socket (Johnson 122-275) and the glass chimney (Penta PL-Cl) gives sufficient cooling with any blower of 50 c.f.m. or more.

The plate-circuit band switch, S_2 , is mounted on the chassis and controlled via a right-angle drive. Leads from the switch to L_3 and L_4 are best made with copper tubing or strap. Various 500- $\mu\mu$ f. 5-kv. capacitors in the plate and output circuit are high-voltage ceramic (Centralab 858S-500), mounted on the tuning capacitors or on metal straps.

While meters with integral metal shields (Phaostron Co., Pasadena, Calif.) are shown in Fig. 6-76, an alternative is to use regular meters and small aluminum boxes, as described in Chapter 23.

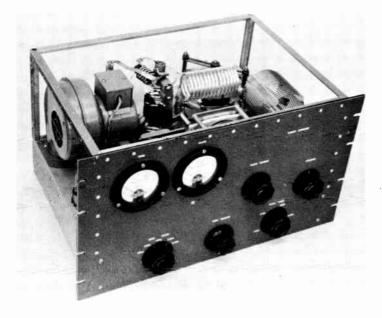


Fig. 6-73-A grounded grid amplifier using the PL-6580 triode. Able to handle a kilowatt p.e.p. input with 3000 volts on the plate, and even more with a higher plate voltage, a chimney surrounds the tube to improve the forced ventilation. In this view the side and top cane-metal panels have been removed.

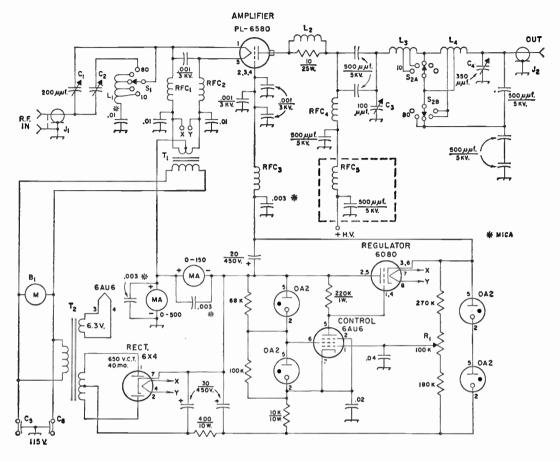


Fig. 6-74—Circuit diagram of the kilowatt grounded-grid linear amplifier. Unless indicated oherwise, capacitances are in μf., resistances are in ohms, resistors are ½ watt. Capacitors marked with polarity are electrolytic, capacitors marked * are mica.

B₁-Ventilating blower, at least 50 c.f.m. (surplus).

 C_1 =200- $\mu\mu$ f. variable (Johnson 200L15).

C₂—200-μμf. variable, locked at full capacitance (Johnson 200L15).

C₃-100-μμf. variable, 0.175-inch spacing (Johnson 100D70).

C₄—350-µµf. variable, 0.075-inch spacing (Johnson 350E30).

 C_6 , C_6 —0.1- μ f. feedthrough, 600 volts (Sprague 80P3). J_1 , J_2 —SO-239 coaxial jack.

 L_1 =20½ turns No. 18, 8 t.p.i., 1-inch diam. Tapped at 2½, 4½ and 9½ turns from ground end (B&W 3014).

L₂-5 turns No. 12, ½ diam., 1½ long, wound around (but not touching) 10-ohm 25-watt resistor, L₂-13¾ turns ¾₆-inch copper tubing, 4½ t.p.i., 1½ inch i.d., silver plated. Tapped at 4¾ and

Adjustment

The bias voltage should be set, with R_1 , to give a no-signal plate input of 150 to 160 watts. The maximum-signal grid current should be about 95 ma. for 2500 volts on the plate to 65 ma. at 4000

7¾ turns from plate end.

L₄-19 ½ turns No. 12, 6 t.p.i., 3 inch diam., 40-meter tap 8 ½ turns from plate end, anti-resonance tap 3 turns from plate end (Illumitronic 2406).

RFC₁, RFC₂-34 turns No. 14 enam., closewound on same 1¼ diam. phenolic tubing.

RFC₃-2-mh. 400-ma. r.f. choke (Miller 4550).

RFC₄-225-\(mu\)h. r.f. choke, 800-ma. (National R-175A).
RFC₅-28 turns No. 20, 16 t.p.i., \(\frac{4}{36}\) diam. (B&W 3007).

S₁—5-position single-pole rotary ceramic, non-shorting (Centralab 2550).

S₂-5-position 2-pole rotary ceramic (two sections Communications Products Model 88).

T₂--6.3 v., 20-amp. filament transformer (Triad F-22A)
T₂--650 v.c.t., 40-ma. power transformer (Stancor PC-8406, 5-v. secondary not used).

plate volts. The input limit is 875 watts at 2500 volts to 1200 watts at 4000 volts.

It is desirable to tune up with an output indicator of some kind. The description of the lowerpowered amplifier earlier in this chapter carries details of the tune-up procedure.

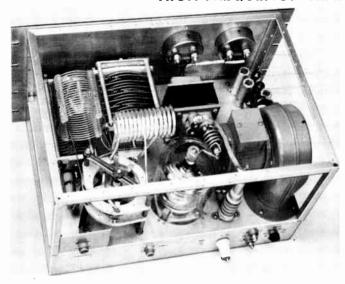


Fig. 6-75—Another view of the grounded-grid amplifier, showing the large switch used in the plate circuit. Tubes visible in the upper right are used in a regulated grid-bios supply. Metal shields on the two panel meters minimize radiation.

High voltage for the plote is brought to the jack on the stand-off insulator at the lower right; the a.c. line is connected to the filter terminals to the right of the insulator.

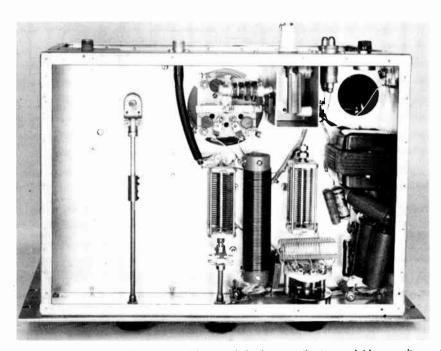


Fig. 6-76—A view under the chassis shows the filament choke between the two voriable capacitors, with the input tuning coil mounted on the input band switch. The small shield compartment at the top surrounds a filter in the B+ lead.

Air from the blower is forced through the hole at the upper right, and it finds its way past the socket and up the chimney as a result of the cut-out area around the socket. The three grid connections on the socket are connected together by a copper strap and bypassed to chassis at three places. An r.f. choke in the grid lead mounts on the socket.

A right-angle drive (National RAD) turns the large band switch mounted above the chassis.

A KILOWATT 4-400A AMPLIFIER

Any transmitter delivering about ten watts will drive the amplifier shown in Figs. 6-77 through 6-82. When used as a Class AB₁ linear for sideband, a peak driving voltage of about 150 is required. The plate tank circuit of the amplifier is homemade from readily available parts.

Referring to Fig. 6-78, the amplifier uses the conventional neutralized grounded-cathode amplifier circuit. Switch S_{1B} shorts out the unused part of grid coil L_2 , and S_{1A} modifies the input link coupling. A Harrington Electronics GP-20L subassembly is shown, but an equivalent circuit can be built from standard parts. The output circuit is a shunt-fed pi network for the amateur bands 3.5 to 30 Mc. The smaller tuning capacitor, C_{10} , is used on 20, 15 and 10 meters, and the larger C_{11} is added for tuning on 40 and 80 meters. Having two tuning capacitors allows the optimum L/C ratio to be maintained on all bands without resorting to an expensive vacuum variable.

A 17-c.f.m. blower supplies adequate forced air cooling for the 4-400A base and plate seals. The blower is connected across the 4-400A filament transformer primary and operates whenever the filament is energized.

All required control and metering circuits are mounted on a separate chassis. Meters are provided for amplifier grid current, screen current, cathode current and plate voltage, to comply with the FCC rule regarding measurement of input powers over 900 watts.

The amplifier is fixed biased at -225 volts for Class C and -150 volts for Class AB₁ operation. The full-wave rectifiers in the bias supply are silicon diodes, with no warm-up time, and full operating bias is applied as soon as the power switch, S_0 , is closed. Time-delay relay K_1 operates K_2 , which is in series with the screen supply primary. Thus there is a 60-second delay before screen potential can be applied to the amplifier tube.

The accessory a.c. socket, J_8 , and the highvoltage filament transformer socket, J_9 , are energized as soon as power switch S_1 is closed. The h.v. plate transformer is turned on by a relay plugged into J_{10} and controlled by the timedelay relay. With this arrangement, it is impossible to apply a.c. to the h.v. rectifier plates before their filaments have had a chance to warm up.

A variable autotransformer in series with the screen-supply primary allows the screen voltage to be adjusted from zero to about 800 volts under load. This makes a convenient arrangement for setting the screen voltage when changing from Class C to Class AB₁ or vice versa, and for adjusting the power input of the amplifier.

A screen overload protection circuit is included. If excessive screen current flows, K_3 is energized and is kept energized by the current

through R_8 . To reset the relay the screen voltage must be momentarily disconnected so that the relay will return to its unenergized condition. This can be done by opening S_7 . The current at which the overload relay throws is set with shunt resistor R_7 ; maximum allowable screen dissipation is 35 watts.

Contruction

The amplifier is built on a 4 × 13 × 17-inch chassis and uses a 14-inch rack panel. All major components are visible in the photographs. The Harrington grid circuit, output loading capacitors and switch, and filament transformer are all below the chassis.

An insulated coupling must be used between the rotor of C_1 and the shaft going to the grid tuning knob. Leads from the grid circuit are brought out through the 3×5 -inch aluminum back plate via a feed-through capacitor and bushings. The input link is connected to the coax receptacle through a length of RG-58/U. The flanged cover of a $5 \times 4 \times 3$ -inch Minibox is slipped over the grid assembly, and this cover is secured to the back plate with four self-tapping screws and to the main chassis with four 6-32 spade bolts.

The ganged loading capacitors (C_{12}) are mounted off the chassis on 1-inch spacers. Connections in the output circuit are made with



Fig. 6-77—The kilowott 4-400A omplifier ond its control unit ore mounted in a 21-inch groy hommertone rack cobinet (Bud CR-1727). Shelf brackets (Bud SA-1350) are mounted on both sides of the cobinet to hold the amplifier chassis. Below the meters, from left to right: filament pilot light, key-type a.c. switch,

Class AB₁/C bios switch, screen autotronsformer, plote switch and plate pilot light.

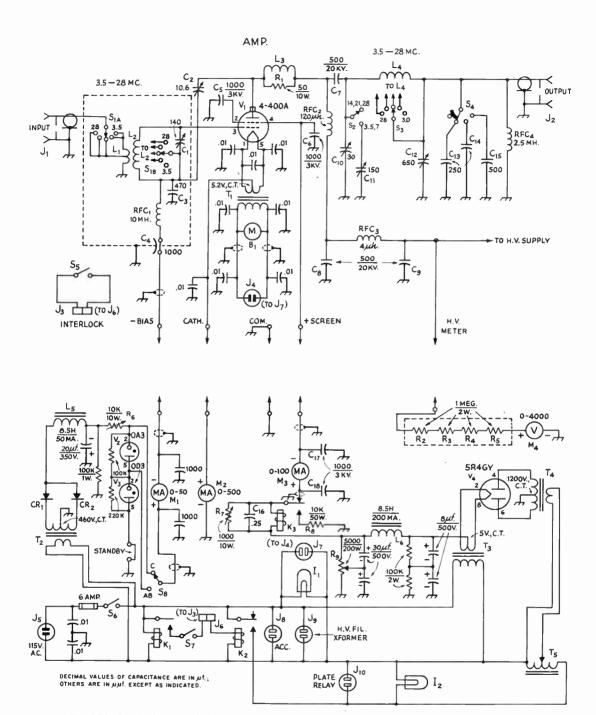


Fig. 6-78—Circuit diagram of the 4-400A amplifier (above the dashed line) and power supply/control unit.

Resistances are in ohms, and resistars are ½-watt unless otherwise indicated. Capacitars not listed are 600-valt disk ceramic except for those marked with polarity, which are electrolytic.

A Kilowatt 4-400A Amplifier

copper or brass strapping to provide low-inductance leads.

The blower is mounted on the rear apron of the chassis by four 6-32 spade lugs attached to the walls of the blower output housing. A 1½ X 1½-inch hole cut in the rear apron of the chassis accommodates the blower; a cork gasket is used between the plastic blower housing and the amplifier chassis.

The chassis should be as airtight as possible to provide maximum air flow to the 4-400A tube, and any small holes should be sealed by covering them with tape.

Plate Tank and Enclosure

The plate tank coil, L_4 , band switch, S_3 , and plate tuning capacitor switch, S_2 , are mounted on two Lucite plates in the center of the chassis. The tank coil comes prewound on one Lucite plate which is positioned $3\frac{1}{2}$ inches above the chassis on ceramic spacers. Hard rubber washers (the type used for packing faucets) are inserted between the ceramic spacers and the Lucite plates to provide a tight fit.

Counting from the blocking capacitor end, the

B₁—Blower-motor assembly, 17 c.f.m. (Ripley, Inc., Middletown, Conn., type 8433).

C₁-140-μμf, midget variable (Hammarlund APC-140-B). Part of Harrington Electronics GP-20L.

C2-10.6-µµf. neutralizing (Johnson N250).

C₃-500-volt mica.

 $C_4-0.001-\mu f$. feed-through (Centralab FT-1000).

 C_8 , C_8 , C_{17} , C_{18} =0.001- μ f., 3000-volt disk ceramic Centralab DD30-120).

C₇, C₈, C₉-500- $\mu\mu$ f., 20,000-volt ceramic (Centralab TV-207).

C₁₀—30-μμf. variable, 0.25-inch spacing (Barker & Williamson CX-45-C butterfly, one section used), or Johnson 50D90 with two stator plates removed).

 C_{11} —150- $\mu\mu$ f. variable, 0.25-inch spacing (Johnson 150D90).

C₁₂-650-µµf. variable (two Hammarlund MC-325M ganged and paralleled).

C13, C14, C15-2500-volt mica (Aerovox 1652L).

C₁₆-200-volt molded paper.

CR₁, CR₂-500-ma. 600-volt peak inverse silicon diode (Sarkes Tarzian F-6).

J₁, J₂-Coaxial receptacle, chassis mounting (SO-239).

Ja, Ja-2-contact socket (Cinch-Jones S-202-B).

J₄, J₅—115-volt plug, chassis mounting (Amphenol 61-M1).

J7-J10, incl.-115-volt socket (Amphenol 61-F1).

K₁-115-volt 60-second time-delay, normally open (Amperite 115N060).

K₂—S.p.d.t. relay, 115-volt a.c. coil (Potter & Brumfield KA5AY).

K₂—S.p.d.t. relay, 2500-ohm 7.2-ma. coil (Advance GHE/1C/2500).

L₁-3¾ turns No. 18 insulated wire on cold end of L_{2i} tapped 2 turns from ground end.

L₂--50 turns No. 24 tinned, 1¾ inches long on ¾inch diam. ceramic form; tapped 5, 8, 13

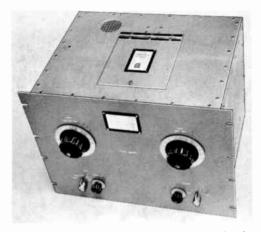


Fig. 6-79—This view of the amplifier shows the bandswitch trap door, air-exhaust port and hole for adjusting neutralization, all in the top of the shielding enclosure. The large knob on the left of the panel is for the 20/15/10-meter plate tuning capacitor, and the matching knob adjusts the capacitor used on 80 and 40. Farther down, from left to right: grid band switch, grid tuning control, variable loading adjustment and loading switch.

and 25 turns from grid end. (Part of Harrington GP-20L).

L₃-3 turns No. 10 tinned, %-inch diam., 1 inch long, mounted on R₃.

L₄—Pi-network coil assembly (Air Dux 195-2 available from Illumitronics Engineering, Sunnydale, Calif.); see text.

P₁-2-contact plug (Cinch-Jones P-202-CCT).

R₁-50-ohm 5-watt noninductive wire-wound (Sprague

 R_6 , R_7 —10-watt adjustable.

R₉-200-watt adjustable; set tap at midpoint.

RFC1-10-mh. r.f. choke (National R-50-I).

RFC₂-120-\(mu\)h. plate r.f. choke (Raypar RL-101).

RFC3-4-\(mu\)h. r.f. choke (National R-60).

RFC₄-2.5 mh. r.f. choke (National R-50).

S₁—Miniature ceramic rotary, 2 poles, 6 positions, 1 section, shorting, 5 positions used (Centralab PA-2002). Part of GP-20L.

 S_2 , S_3 —Homemade, see text and Fig. 6-82.

S₄—Ceramic rotary, 9 positions, 1 section, progressively shorting, 4 positions used (Centralab PISD section and P-270 index assembly).

S₈—S.p.d.t. microswitch (Unimax 2HBW-1).

S₆—S.p.s.t. lock switch (Arrow-Hart & Hegeman 81715-L).

S₇-S.p.s.t. toggle.

T₁—Filament transformer, 5.2 volts, c.t., 24 amp. (Triad F-11U).

T₂—Power transformer, 460 volts, c.t., 50 ma. (Stanco PC-8418).

T₃—Filament transformer, 5 volts c.t., 3 amp. (Thordarson 21F03).

T₄-Power transformer, 1200 volts, c.t., 200 ma. (Thordarson 22R36).

T₆—Variable autotransformer, 0-132 volts, 1.75 amp. (Superior 10B).

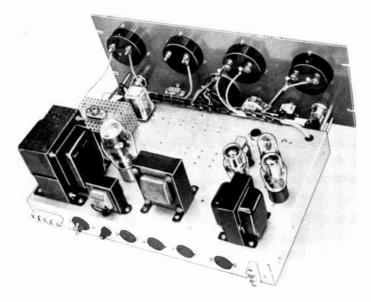


Fig. 6-80—Top view of the control unit. The voltmeter multiplier resistors are housed in a cane-metal protective shield (upper left). Resistors R₈ and R₉ are mounted under the sets of ventilation holes (center near panel).

plate coil is tapped at 4 turns (0.4 μ h.) for 10 meters; 7.5 turns (1 μ h.) for 15 meters; 10.5 turns (2.33 μ h.) for 20 meters, 14 turns (5.2 μ h.) for 40 meters, and 24 turns (16.4 μ h.) for 80 meters. (All the figures include the 4-turn coil made of $\frac{1}{2}$ -inch strap.) The lugs provided with the tank coil assembly should be securely soldered to the coil at these points. Strapping should then be run from these taps to the appropriate band-switch terminals. It should be noted that the

band-switch terminals do not progress in consecutive order, but are arranged to provide the shortest possible lead lengths.

Be sure no iron or steel hardware is used in the band-switch assembly, or for that matter, anywhere in the plate tank circuitry of the amplifier. Each piece of hardware should be checked first with a magnet to insure that it is neither iron nor steel before being used in the plate circuit.

In order to get to the band switch and capacitor


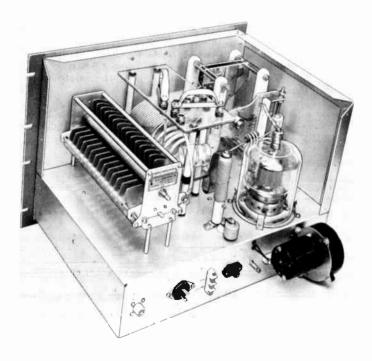


Fig. 6-81-Most of the enclosure has been removed to show the low- and highfrequency plate tuning capacitors, the coil and bandswitch assembly (center) and the 4-400A in its glass chimney (Eimac SK-406). The neutralizing capacitor is behind the tube in this view. A cork gasket is used between chimney and chassis. Across the rear apron: output jack, filament a.c. plua. cathode and ground terminals, high-voltage connector, ground post and blower. The blower hides another terminal strip (for bias and screen connections) and the input jack. The band switch Is made from a $4\frac{1}{8}$ imes 8inch strip of 1/4-inch thick Lucite and Johnson 108-760 jocks and 108-770 plugs. The plugs are mounted an two 31/8-inch utility handles (Bud UH-71A) strengthened by straps of aluminum.

Fig. 6-82—Bottom view of the amplifier. The Minibox shield has been removed from the grid circuit (lower right). Loading capacitors, switch and "safety" choke are at the left. The filament transformer is in the center. Amplifier tube socket is mounted on four tabs spaced evenly around the circular cutout.

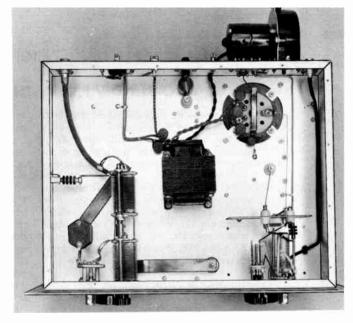

switch, a trap door is provided in the top of the enclosure. Microswitch S_5 is installed so that it is actuated by the trap door. The leads from S_5 are brought out to a jack, J_3 , located on the back wall of the enclosure, and from there to J_6 on the control unit. The trap door measures $6\frac{1}{4}$ by 7 inches and the rectangular cutout in the top of the enclosure is $4\frac{1}{8}$ by $6\frac{1}{4}$ inches. This provides adequate overlap to prevent any leakage of r.f.

Adjustment and Operation

First, determine that the control unit is operating correctly. Apply 115 volts to J_5 , insert the tubes, and turn on the key switch, S_6 . The green filament pilot light should go on immediately. There should also be power at receptacles J_7 , J_8 and J_9 . J_7 and J_9 are for the amplifier and plate supply filament transformers; J_8 , an accessory socket, is provided so that external equipment such as the station receiver can be controlled by S_6 . There should be no power at J_{10} , the plate transformer control socket.

Next, adjust R_6 until the VR tubes just begin to glow. Be sure the standby terminal jumper from Pin 5 of V_3 to ground is in place. Turning S_5 should change the bias from —150 volts in the Class AB₁ position to —225 volts for Class C in the other. With S_5 in the linear position (AB), and leaving a voltmeter on the output of the bias supply, temporarily lift the standby jumper from ground. The output voltage should rise from —150 to approximately —300 volts. The standby terminals provide a convenient way to bias the 4-400A beyond cutoff during standby and receiving periods. This will prevent any annoying diode noise generation.

Open S_6 and again connect an a.c. voltmeter to J_{10} . Put a temporary jumper between the two contacts of J_6 . Close S_6 and S_7 , and after 60 seconds there should be power at J_{10} and the red plate pilot lamp should light. Replace the jumper across J_6 with the leads from the microswitch interlock. Lifting the trap door should

deenergize J_{10} , and the plate pilot bulb should extinguish.

Next, connect a d.c. voltmeter to the output of the screen supply. By adjusting T_5 it should be possible to vary the output from 0 to approximately 850 volts. Finally, adjust R_7 so that K_3 trips when 40 ma. is drawn from the screen supply. This can be checked by connecting a resistor (620 ohms or less, 1 watt) across the supply output and running the voltage up from zero until the drain is 40 ma. This completes the testing of the control unit.

The amplifier must now be neutralized. Set the grid and plate band switches for 28 Mc., and disconnect the screen and plate leads at the amplifier terminals. Couple a sensitive indicating wavemeter to the output end of the plate tank circuit and apply the required -225 volts of bias. Apply drive, resonate the grid circuit and adjust the output of the exciter for rated 4-400A grid current. Neutralizing capacitor C2 should then be adjusted for minimum r.f. in the plate tank circuit. The plate tuning capacitor should be retuned for maximum wavemeter reading after each change of C2. After rated plate and screen voltages have been applied and the amplifier loaded, the neutralizing capacitor should be touched up so that minimum plate current and maximum grid and screen currents occur simultaneously as the plate tank is tuned through resonance.

If the amplifier is to be used for s.s.b., the h.v. power supply should have a minimum output capacitance of $8 \mu f$. For best voltage regulation the plate transformer should have a 220-volt primary. The output of the h.v. power supply should include a $\frac{1}{2}$ -ampere fuse to protect the supply from excessive overloads.

If the amplifier is to be plate modulated, a choke, approximately 10 hy. at 50 or 100 ma., should be inserted in series with the screen lead of the 4-400A. An external switch can be used to short out the choke when using the amplifier for c.w. or s.s.b.

A TWO-BAND V.F.O. WITH DIFFERENTIAL KEYER

The v.f.o shown in Figs 6-83, 6-85 and 6-86 is intended to replace the 3.5- and 7-Mc. crystals used in many transmitters. It will deliver 30 to 50 volts on these two bands, sufficient to drive any normal crystal-oscillator stage as an amplifier or frequency multiplier. To simplify the addition of this v.f.o. to an existing transmitter, the v.f.o. includes a differential keying circuit that can be applied to any subsequent transmitter without modification. When used as a substitute for 80-meter crystals, the output of the v.f.o. unit is 3.5 to 40 Mc. When used as a substitute for 40-meter crystals, the output is 7.0 to 7.43 Mc.

Referring to the circuit diagram, Fig. 6-84, the oscillator uses a 12AT7 triode in the scriestuned Colpitts circuit. Actually two oscillators are included, one operating on 1.8 Mc. and the other on 3.5 Mc. Each triode and its associated tuning circuit is permanently connected, and the one to be used is switched on in the cathode circuit by switch S_{1A} . Another section of the switch, S_{1B} , shifts the differential keying lead to the active triode. The oscillator is followed by a cathode follower, V_{2A} , the triode section of a 6CX8. The cathode follower works with reduced plate voltage (200) obtained from a voltage divider that serves as a bleeder for the power

supply and also drops the screen voltage for the output stage. The output stage is the pentode section of the 6CX8. The bandswitch, S_1 , shorts out part of the output tuning coil for 40-meter operation.

The differential-keying circuit uses a d.p.d.t. relay. One arm of the relay keys the following transmitter in a normal manner, via J_2 and a length of cable. The other arm of the relay, K_{1A} , turns on the oscillator immediately the relay closes, but it doesn't turn off the oscillator immediately when the relay opens because the oscillator blocking bias, developed across a 10K resistor, is not available until the 0A3 conducts. The 0A3 does not conduct until the voltage across the 0.5-\(\mu f\). capacitor has charged to about -100 volts, and it takes an appreciable fraction of a second for the capacitor to charge through the 100K resistor. Negative voltage for the circuit is obtained from a half-wave rectifier circuit using two small silicon rectifiers in series. The plate-voltage supply is conventional and uses a 5V4-GA rectifier and capacitor-input filter to deliver about 425 volts. A d.c. supply for the keying relay is obtained from the heater voltage and a half-wave rectifier. A d.c. relay was used for keying because it was found among the inexpensive relays that were tested, the d.c. relays

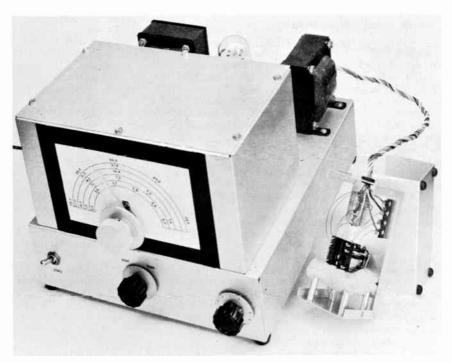


Fig. 6-83—The two-band v.f.o. provides suitable output to drive a former crystal-oscillator stage on 80 or 40 meters. A differential-keying circuit is included that requires no modification of the transmitter following the v.f.o.

The drive is a British planetary drive, with a plastic painter added. The dial is paper, held in place by black electrical Scatch tape. Lawer controls, from left to right, are frequency-spotting switch, band switch, and output peaking.

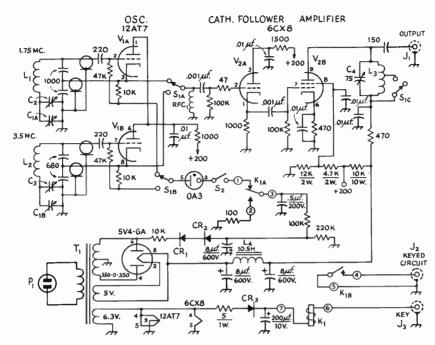


Fig. 6-84—Circuit diagram of the two-band v.f.o. Unless specified otherwise, resistances are in ohms, resistors are $\frac{1}{2}$ watt, capacitances are in $\mu\mu$ f. Fixed capacitors associated with V_1 are silvered mica, all decimal capacitors are ceramic, capacitors marked with polarity are electrolytic.

C₁—Originally 100-μμf, per section dual variable (Johnson 167-53). C_{1A} section modified to have 7 stator and 6 rotor plates; C_{1B} section modified to have 4 stator and 4 rotor plates.

C₂—140-μμf. midget variable (Hammarlund APC-140).
 C₃—100-μμf. midget variable (Hammarlund APC-100).
 C₄—75-μμf. midget variable (Hammarlund APC-75-B).
 CR₁, CR₂—400 p.i.v. 200-ma. silicon rectifier (International Rectifier 2E4 or equiv.).

CR₃—25-v. 250-ma, selenium rectifier (International Rectifier C1H).

J₁, J₂, J₃—Phono jack.

K₁—D.p.d.t. relay, 6-v.d.c. cail (Potter & Brumfield KA-11D). Numbers on the leads correspond to socket (not shown) pin numbers.

keyed faster than the a.c.-actuated ones. The relay is mounted external to the v.f.o. proper, to reduce noise and vibration. No a.c. switch is included because it is assumed that the v.f.o. will obtain its a.c. from a source switched somewhere else. The power supply is fused in the line plug.

Construction

The v.f.o. is built on a $10 \times 12 \times 3$ -inch aluminum chassis. Since the aluminum from which the chassis is built is somewhat flexible, a strengthening rib of 1-inch aluminum angle is bolted across the 10-inch wide front of the chassis (see Fig. 6-85). The chassis is also strengthened by the $6 \times 9 \times 5$ -inch aluminum utility cabinet (Bud AU-1040) that serves as the shield compartment for the tuning capacitor, C_1 , and

L₁-94 turns No. 24, 32 t.p.i., 1-inch diam. (B & W 3016).

L₂-47 turns No. 20, 16 t.p.i., 1-inch diam. (B & W 3015).

L₃—36 turns No. 24, 32 t.p.i., 1-inch diam. (B & W 3016). Tapped 14 turns from plate end.

L₄—10½-henry 110-ma. choke (Knight 62 G 139).

 P_1 —Fused (1½ amp.) line plug.

RFC₁-2.5 mh.

S₁—Two-section rotary switch, each section is 2-pole 6-position (2 used) steatite, total of 3 poles used (Centralab PA-301 index assembly with 2 PA-3 sections).

S2-S.p.s.t. toggle switch.

T₁--700 v.c.t. at 90 ma., 5 v. at 3 a., 6.3 v. at 3.5 a. (Knight 61 G 429).

the associated capacitors and inductors. A spare side of the utility box furnishes aluminum for several small brackets.

Care in construction of the v.f.o. will be rewarded by maximum stability. Of prime importance is the support of the tuning capacitor, C_1 . As can be seen in Fig. 6-86, the capacitor is supported above the chassis at each end by a suitable aluminum bracket. The front bracket is a shallow U-shaped one; one side of the U is the lip fastened to the chassis, and the other side of the U is a lip that supports C_2 and C_3 . The front of the capacitor is held to the bracket by the single-hole mounting provision of the capacitor. The rear bracket for the capacitor is bolted to the capacitor at two points, and a clearance hole is provided for the back bearing of the capacitor. The rotor of the capacitor is electrically con-

nected to the chassis via the front bracket only, and all connections to the chassis from the capacitors and lengths of coaxial cable (see Fig. 6-84) are made to the front rotor terminal of C_1 .

The drive for C_1 is a planetary reduction unit (Jackson Bros. Precision Planetary, available from Arrow Electronics, New York); a short length of $\frac{1}{4}$ -inch diameter rod and an insulated coupling (Millen 39016) connect the drive to the capacitor. Care spent in aligning the capacitor and the drive will be repaid by smooth operation and no backlash. Before installation, check the capacitor and make sure that it turns with reasonable torque. If it binds or is tight, free it by working, loosening the rear bearing slightly, or by oiling (rear bearing only!).

The mica capacitors across each tuned circuit are mounted on multiple tie points that are soldered to the stator supports of C_1 . Coils L_1 and L_2 are supported by sliding strips of sheet polystyrene into the coils and then cementing the strips to the insulating material in the coils. The strips are then supported 1 inch above the chassis by ceramic insulators (Johnson 135-501).

The location of the other components is not too critical, and a little study of Fig. 6-85 will show their location. Switch S_1 is mounted on an aluminum bracket, and the rectifier CR_3 is mounted on a ceramic standoff insulator. The inductor L_3 is mounted in the same manner as L_1 and L_2 , and the tap is made prior to final installation by pushing in two turns each side of the desired turn, thus leaving room for soldering a wire to the turn. Capacitor C_4 is supported by an aluminum bracket; its shaft is at plate d.c. potential and must be insulated from the chassis.

The relay K_1 is mounted on foam rubber in a small "Minibox." The stud of the relay is held to the rubber by a washer and nut, and the rubber is held to the box by screws at the corners. The stud of the relay, or any other part of the relay, must not touch the box. Flexible leads from the relay and its coil run through a rubber grommet to an octal plug (Amphenol 86-CP8 with 3-13 cap), which in turn is plugged into an octal socket at the rear of the v.f.o. In Fig. 6-84, numbers on the leads to the relay correspond to the pin numbers of the plug and socket.

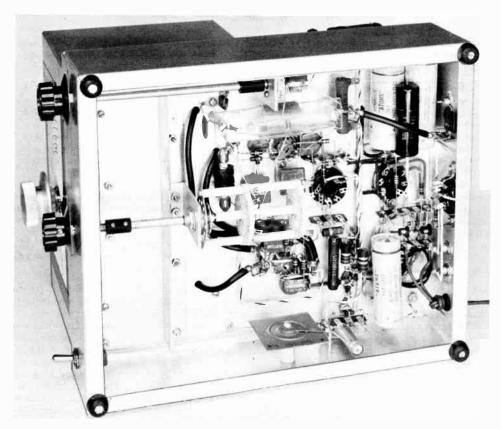


Fig. 6-85—Under the chassis of the two-band v.f.o. Fixed capacitors at the upper right are filter capacitors for the power supply and a 0.5- μ f, capacitor used in the differential keying circuit. The socket for the relay connections mounted on the back wall of the chassis (right in this view), and the filter capacitor for the negative supply is at the bottom right. The lengths of coaxial cable running to the oscillator tube socket (seen below ceramic switch at center) are pieces of RG-58/U coming from the oscillator tuning compartment above the chassis. Their outer conductors are grounded to the chassis near the tube socket.

Adjustment

If the unit is properly wired, the only adjustment necessary will be that of C_2 and C_3 to bring the circuits into proper range. With C_1 fully meshed, set C_2 and C_3 so that the signal falls 5 to 10 kc. lower than 3.5 and 7.0 Mc. respectively. At the high ends (C_1 at minimum capacitance) the signal should be slightly higher than 4.0 and 7.425 Mc. The measurements should be made with the cover in place, although whether the cover is on or off should have very little effect on the frequency. The presence of the cover, securely fastened with sheet metal screws, does contribute to the over-all rigidity of the unit, however.

With nothing connected to J_1 , the output circuit should tune 3.5 and 7.0 Mc. with C_4 almost fully meshed. When a foot or two of coaxial line is used between J_1 and the transmitter to be driven, the setting of C_4 will be changed by the capacitance of the connecting line. If of necessity a long line must be used, it will be necessary to compensate by modification of the inductance of L_8 . RG-59/U has a capacitance of L_9 . RG-59/U has a capacitance of L_9 . PG-59/U has a capacitance of L_9 .

For an example of how the usual crystaloscillator circuit can be modified for use with this v.f.o., see the 75-watt transmitter earlier in this chapter.

Keying

When the v.f.o. is connected to a subsequent amplifier, the keying can be checked by opening S_2 , to allow the v.f.o. to run steadily. The keying can then be monitored and tested by the methods outlined in Chapter Eight. If the keying has strong key clicks, they should be reduced to a satisfactory level by the methods outlined. If a chirp is detected, it is a fault of the v.f.o. unit, and is probably caused by a severe line-voltage change or too much "pulling" through the 6CX8 stage. However, if the v.f.o. has been built carefully, it should be possible to swing C_4 through resonance without changing the frequency of the v.f.o., and this test will show that the buffer effect is adequate.

Once the keyed signal of the subsequent amplifier is satisfactory with S_2 open, the check for good differential keying can be made with S_2 closed. The keying should sound the same with S_2 open or closed, except that when S_2 is open a "back wave" will be heard locally. If the subsequent amplifier has more than one stage and two or more stages are keyed, no back wave should be heard in either position of S_2 .

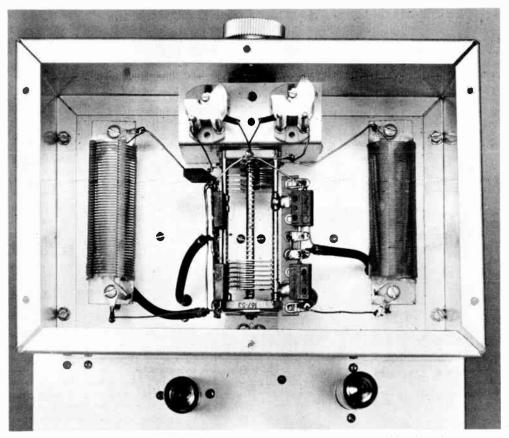


Fig. 6-86—Close-up view of the oscillator tuning compartment. Multiple tie points soldered to the tuning capacitor (center) provide rigid support for the silvered-mica capacitors. All ground (chassis) connections within this compartment are made to the front rotor connection; this includes the outer conductors of the coaxial line.


CONVERTING SURPLUS TRANSMITTERS FOR NOVICE USE

War-surplus radio equipment, available in many radio stores, is a good source of radio parts. Some of the transmitters and receivers can be made to operate in the amateur bands with little or no modification. It would be hard to find a more economical way for a Novice to get started on 40 or 80 meters than by adapting a normally-v.f.o.-controlled surplus "Conimand Set" to crystal control.

The "Command Sets" are parts of the SCR-274N and AN/ARC-5 equipments, transmitters and receivers designed for use in military aircraft. The two series are substantially identical in circuit and construction. Of the transmitters, two are of particular interest to the Novice. These are the BC-696 (part of 274N) or T19 (ARC-5) covering 3 to 4 Mc., and the BC-459 or T22. 7 to 9.1 Mc. The transmitter circuit consists of a 1626 triode variable-frequency oscillator that drives a pair of 1625s in parallel, which for Novice use can be run at 75 watts input. In addition to the 1626 and 1625s the transmitters include a 1629 magic-eye tube, which was used as a resonance indicator with a crystal for checking the dial calibration. The tubes have 12-volt heaters connected in series-parallel for 24-volt battery operation. The BC-696 and 459 are available from surplus dealers at prices ranging from five to fifteen dollars each, depending on condition.

Several methods have been described for converting the transmitters to crystal control for Novice use, but most of them didn't take into consideration the reconversion required to change back to v.f.o. when the Novice became a General-Class license holder.

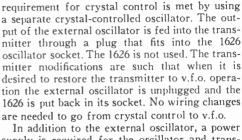In the modification to be described, the Novice



In addition to the external oscillator, a power supply is required for the oscillator and transmitter (Fig. 6-88), and certain wiring changes are needed to make the transmitter itself suitable for aniateur use. These changes consist primarily of removing two relays, changing the tube heater circuit for operation on 12 volts instead of 24 volts, and the addition of a power plug.

Transmitter Modifications

The 80- and 40-meter transmitters are practically identical except for frequency range, and the modifications are the same in both. Remove the top cover and bottom plate. Remove the tubes and crystal from their sockets so there will be no danger of breaking them as you work on the transmitter. If the sockets are not marked by tube types, mark them yourself so you'll know which tube goes where.

The following modifications are required:

- 1) Remove the antenna relay (front panel) and control relay (side of chassis) and unsolder and remove all wires that were connected to the relays with the exception of the wire going to Pin 4 on the oscillator socket.
- 2) Remove the wire-wound resistor mounted on the rear wall of the transmitter.
- 3) Unsolder the wire from Pin 7 of the 1629 socket and move it to Pin 2. Ground Pin 7.
- 4) Unsolder the wires from Pin 1 of the 1625 closest to the drive shaft for the variable capacitors and solder the wires to Pin 7. Run a lead from the same Pin 1 to the nearest chassis ground.
- 5) Unsolder all leads from the power socket at the rear of the chassis and remove the socket. The socket can be pried off with a screwdriver.
- 6) Unsolder the end of the 20-ohm resistor (red-black-black) that is connected to Pin 4 on the oscillator socket and connect it to Pin 6

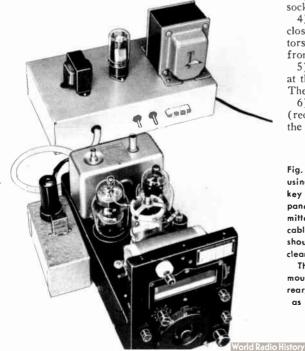


Fig. 6-87—The complete Novice setup, in this case using the 80-meter (BC-696) transmitter. Note the key jack at the lower-left corner of the transmitter panel. The crystal oscillator is connected to the transmitter oscillator-tube socket with o short length of cable terminating in on octal plug. A small notch should be cut in the transmitter cover to provide clearance for the cable when the cover is installed.

The power transformer, rectifier, and choke are mounted on top of the power-supply chassis at the rear, and the control switches are mounted on the wall as shown. Remaining components are underneath.

Converting Surplus

of the calibration crystal socket. There is also a lead on Pin 4 that was connected to the keying relay; connect this lead to the nearest chassis ground point.

 Mount an octal socket (Amphenol 78-RS8) in the hole formerly occupied by the power socket. Install a solder lug under one of the nuts

holding the socket mounting.

8) Wire the octal socket as shown in Fig. 6-88. One of the leads unsoldered from the original power socket is red with a white tracer. This is the B+ lead for the 1625s. The yellow lead is the screen lead for the 1625s and the white lead is the heater lead. Although the manuals covering this equipment specify these colors, it's safer not to take them for granted; check where each lead actually goes before connecting it to the new power socket. The lead from Pin 1 on the power socket to Pin 6 on the calibration-crystal socket is the oscillator plate-voltage lead. The leads from Pins 7 and 8 on the power plug to Pins 1 and 6 on the oscillator socket are new leads to carry power to the external crystal-controlled oscillator. The lead from Pin 4 of the power socket to Pin 2 on the 1629 (resonance indicator) socket is the 12-volt heater lead.

9) Mount a closed-circuit phone jack at the lower left-hand corner of the front panel. Connect a lead from the ungrounded phone jack terminal to Pin 6 (cathode) of either of the 1625 sockets. This completes the modification.

Crystal-Controlled Oscillator Details

The external crystal-controlled oscillator circuit, shown in Fig. 6-89, uses a 6AG7 in the grid-plate oscillator circuit. Either 80- or 40-meter crystals are required, depending on the band in

ma.; 5 volts, 3 amp.; 6.3 volts, 6 amp. (Knight

61G414, Triad R-21A, or equivalent).

use. A tuned plate circuit is not required in the oscillator; it was found that more than adequate grid drive could be obtained with the setup as shown


Output from the oscillator is fed to the transmitter through an 8-inch length of RG-58 coax cable. The cable is terminated in an octal plug, P_2 , which is plugged into the oscillator tube socket in the transmitter. Power for the external oscillator is obtained through this socket.

The crystal-controlled oscillator is built in and on a $4 \times 2 \times 234$ -inch aluminum box. The tube and crystal sockets are mounted on top of the box and the remaining components inside. Layout of parts is not particularly critical but the general arrangement shown in Figs. 6-87 and 6-90 should be followed to insure good results.

In the completed setup, oscillator and amplifier, the cathodes of the 1625s are keyed and the crystal oscillator runs continuously during transmissions. It is thus necessary to turn the oscillator off during standby periods, and this is accomplished by opening the B-plus switch on the power supply. This method is used in preference to keying the oscillator and amplifier simultaneously because keying the oscillator is likely to make the signal chirpy. With amplifier keying the signal is a real T9X.

Power Supply

Fig. 6-88 shows the circuit of the power supply, which uses a 5U4G rectifier and a capacitor-input filter. The power transformer, T_1 , is a type made by several manufacturers. To obtain the necessary 12.6 volts for the heaters, a 6.3-volt filament transformer is connected in series with the 6.3-volt winding on T_1 . This setup also will

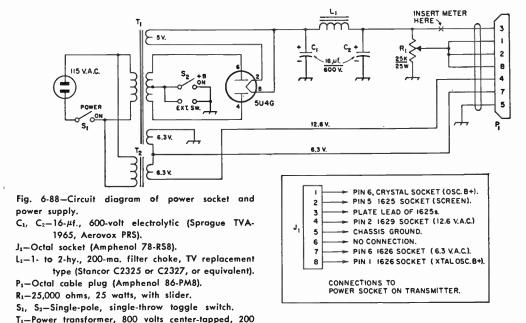

T₂-Filament transformer, 6.3 volts, 3 amp. (Triad F-16X, Knight 62-G-031, or equivalent).

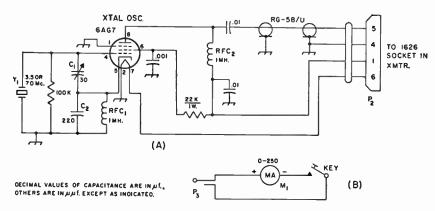


Fig. 6-89—(A) Circuit diagram of external crystal-controlled oscillator. Unless otherwise specified, resistances are in ohms, resistors are $\frac{1}{2}$ watt. The 0.01- and 0.001- μ f. capacitors are disk ceramic. (B) Method of connecting the milliammeter in series with the key.

 $C_1-3-30-\mu\mu f$. trimmer. $C_2-220-\mu\mu f$. fixed mica. $M_1-0-250$ d.c. milliammeter. $P_2-Octal$ plug, male (Amphenol 86-PM8).

provide 6.3 volts for the heater of the 6AG7. Current requirement for the 6AG7 heater is 0.65 amp. and for the 1625s, 0.9 amp. total.

To turn off the plate voltages on the transmitter during stand-by periods, the center tap of T_1 is opened. This can be done in two ways; by S_2 , or by a remotely-mounted switch whose leads are connected in parallel with S_2 . A two-terminal strip is mounted on the power-supply chassis, the terminals being connected to S_2 which is also on the chassis. The remotely-mounted switch can be installed in any convenient location at the operating position. A single-pole, single-throw switch can be used for this purpose or, if desired, a multicontact switch can be used to perform simultaneously this and other functions, such as controlling an antenna-changeover relay.

The high-voltage and heater leads are brought out in a cable to an octal plug, P_1 , that connects to J_1 on the transmitter. The length of the cable will, of course, depend on where you want to install the power supply. Some amateurs prefer to have the supply on the floor under the operating desk rather than have it take up room at the operating position.

The supply shown here was constructed on a $3 \times 6 \times 10$ -inch chassis. The layout is not critical, nor are there any special precautions to take during construction other than to observe polarity in wiring the electrolytic capacitors and to see that the power leads are properly insulated. Never have P_1 unplugged from J_1 when the power supply is turned on; there is danger of electrical shock at several pins of P_1 . Interchanging the inserts of P_1 and J_1 will remove this hazard.

When wiring P_1 don't connect the B-plus lines to Pins 2 or 3, the amplifier plates and screens, at first. It is more convenient to test the oscillator without plate and screen voltages on the amplifier.

When the supply is completed, check between

 P_3 —Phone plug. RFC₁, RFC₂—1-mh. r.f. chokes. Y₁—3.5- or 7-Mc. Novice-band crystal, as required.

chassis ground and the 12.6-volt lead with an a.c. voltmeter to see if the two 6.3-volt windings are connected correctly. If you find that the voltage is zero, reverse one of the windings. If you don't have an a.c. meter you can check by observing the heaters in the 1625s. They will light up if you have the windings connected correctly. Incidentally, leave B plus off, by opening S_2 , for this check.

Next, set the slider on the bleeder resistor, R_1 , at about one-quarter of the total resistor length, measured from the B-plus end of the bleeder. Be sure to turn off the power when making this adjustment. With the tap set about one-quarter of the way from the B-plus end of the bleeder the oscillator plate and amplifier screen voltages will be approximately 250 volts.

Testing the Transmitter

A key and meter connected as shown in Fig. 6-89 are needed for checking the transmitter. When P_3 is plugged into the jack in the transmitter it will measure the cathode current of the 1625s. The cathode current is the sum of the plate, screen and control-grid currents. Some amateurs prefer to install the meter in the plate lead so it reads plate current only. This can be done by opening the B-plus line at the point marked "X" in Fig. 6-88, and inserting the meter in series with the line. However, unless more than one meter is available, don't install it in the power supply setup in this way until after the tests described below have been made.

Insert the external oscillator plug, P_2 , into the 1626 socket and connect P_1 to the transmitter. Plug P_1 into the key jack on the front panel of the transmitter. With S_2 open, turn on the power and allow a minute or two for the tubes to warm up. Next, close the center-tap connection, S_2 , on the power transformer. Set the transmitter dial to the same frequency as that of the crystal in

Converting Surplus

use and close the key. A slight indication of grid current should show on the meter. There is no plate or screen current because there are no screen or plate voltages on the amplifier. If no grid current is obtained, adjust C_1 until grid current shows, or try another crystal.

The next step is to peak the amplifier grid circuit — that is, the 1626 v.f.o tank — for maximum grid-current reading. The v.f.o. trimmer capacitor is in an aluminum box on the top of the chassis at the rear. There is a ½-inch diameter hole in the side of the box; loosen the small screw visible through this hole, thus unlocking the rotor shaft of the trimmer capacitor. Move the rotor-arm shaft in either direction, observing the meter reading, and find the position that gives the highest reading. This should be something more than 10 ma.

Now connect the plate and screen voltage leads to P_1 . Be sure to turn off the power supply before making the connections!

The first test of the rig should be with a dummy load; a 115-volt, 60-watt light bulb can be used for this purpose. The lamp should be connected between the antenna terminal and chassis ground. However, to make the lamp take power it may be necessary to add capacitance in parallel with it. A receiving-type variable capacitor having 250 µµf. or more maximum capacitance will be adequate for the job.

Turn on the power and allow the tubes to warm up, but leave the key open. Set the antenna coupling control on the transmitter to 7 or 8, and set the variable capacitor connected across the dummy load to about maximum capacitance. Next, close the key and adjust the antenna inductance control for an increase in cathode current. Turn the frequency control for a dip in current reading. The indicated frequency will probably differ from that of the crystal in use, but don't worry about it.

Adjust the three transmitter controls, antenna inductance, antenna coupling, and frequency, along with the variable capacitor across the lamp load, until the lamp lights up to apparently full brilliance. The cathode current should be between 150 and 200 ma. With the transmitter fully loaded, adjust C_1 in the crystal oscillator so that the lamp brilliance just starts to decrease. This is the optimum setting for C_1 and no further adjustments are required.

If a d.c. voltmeter is available, check the different voltages in the setup. Using the power supply shown here, the plate voltage on the 1625s is approximately 400 with the amplifier fully loaded. With the plate voltage on the oscillator and screen voltage on the 1625s adjusted to 250 volts (tap on R_1), the oscillator screen voltage is 160 volts. The oscillator takes approximately 30 ma. and the 1625 amplifier screens about 10 ma. when the amplifier is fully loaded.

Getting on the Air

To put the transmitter on the air it is necessary only to connect an antenna to the antenna post and connect a ground lead from the transmitter chassis to a water-pipe ground or to a metal stake driven in the ground. Almost any length of antenna will work, but for best results the minimum length should not be less than about 1/8 wavelength for the band in use. This is approximately 33 feet for 80 meters and 16 feet for 40 meters. It is of course better to make the antenna longer — and to be sure to get the far end as high as possible.

An output indicator will prove to be a handy device for knowing when power is actually going into the antenna. For this purpose use a 6.3-volt, 150-ma. dial lamp. Connect two leads, each about one foot long, to the shell and base of the bulb, respectively. Clip one lead to the antenna post and the other lead on the antenna wire two feet from antenna post. A small amount of power will go through the bulb and this will provide a visual indication of output. Follow the same tuning procedure as outlined above for the dummy antenna. If the bulb gets so bright that it is in danger of burning out, move the leads closer together to reduce the pickup.

It may be found that certain antenna lengths won't work — that is, the amplifier won't load — no matter where the antenna coupling and inductance are set. In such a case, connect a variable capacitor — like the one used with the lamp dummy — between the antenna post and the transmitter chassis. Adjust the capacitor and antenna inductance for maximum brilliance of the output indicator.

A superior antenna system uses a two-wire feeder system and an antenna coupler; examples are given in Chapters 13 and 14. If a coupler is used, the transmitter and coupler should be connected together with coax line. The inner conductor of the coax should be connected to the antenna terminal and the outer braid to the transmitter case, as close to the antenna terminal as possible. If desired, the antenna terminal can be removed and a coax fitting substituted.

When the coveted General Class ticket is obtained, it is only necessary to unplug the crystal oscillator, put the original tube back in the rig, and move out of the Novice band.

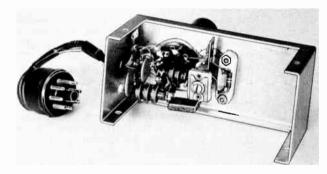


Fig. 6-90—This bottom view of the crystal oscillator shows the arrangement of components. Terminal strips are used for the cable connections and also as a support for C₁, the feedback capacitor.

Power Supplies

Essentially pure direct-current plate supply is required to prevent serious hum in the output of receivers, speech amplifiers, modulators and transmitters. In the case of transmitters, pure d.c. plate supply is also dictated by government regulation


The filaments of tubes in a transmitter or modulator usually may be operated from a.c. However, the filament power for tubes in a receiver (excepting power audio tubes), or those in a speech amplifier may be a.c. only if the tubes are of the indirectly-heated-cathode type, if hum is to be avoided.

Wherever commercial a.c. lines are available, high-voltage d.c. plate supply is most cheaply and conveniently obtained by the use of a transformer-rectifier-filter system. A typical power supply is shown in Fig. 7-1.

In this system, the plate transformer, T_1 , steps up the a.c. line voltage to the required high voltage.

The a.c. is changed to pulsating d.c. by the rectifiers, V_1 and V_2 . Pulsations in the d.c. appearing at the output of the rectifier (points A and B) are smoothed out by the filter composed of L_1 and C_1 . R_1 is a bleeder resistor. Its chief function is to discharge C_1 , as a safety measure, after the supply is turned off. By proper selection of value,

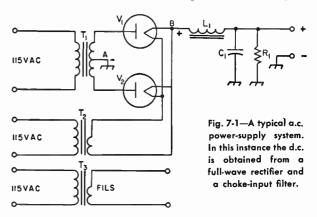 R_1 also helps to minimize changes in output voltage with changes in the amount of current drawn from the supply. T_2 is a step-down transformer to provide filament voltage for the rectifier tubes. It must have sufficient insulation between the filament winding and the core and pri-



mary winding to withstand the peak value of the rectified voltage. T_s is a similar transformer to supply the filaments or heaters of the tubes in the equipment operating from the supply. Frequently these three transformers are combined in a single unit having the 115-volt primary winding and the three secondary windings on one core.

RECTIFIER CIRCUITS

Half-Wave Rectifier

Fig. 7-2 shows three rectifier circuits covering most of the common applications in amateur equipment. Fig. 7-2A is the circuit of a half-wave rectifier. During that half of the a.c. cycle when the rectifier plate is positive with respect to the cathode (or filament), current will flow through the rectifier and load. But during the other half of the cycle, when the plate is negative with respect to the cathode, no current can flow. The shape of the output wave is shown in (A) at the right. It shows that the current always flows in the same direction but that the flow of current is not continuous and is pulsating in amplitude.

The average output voltage—the voltage read by the usual d.c. voltmeter—with this circuit is 0.45 times the r.m.s. value of the a.c. voltage delivered by the transformer secondary. Because the frequency of the pulses in the output wave is relatively low (one pulsation per cycle), consid-

erable filtering is required to provide adequately smooth d.c. output, and for this reason this circuit is usually limited to applications where the current involved is small, such as in supplies for cathode-ray tubes and for protective bias in a transmitter.

Another disadvantage of the half-wave rectifier circuit is that the transformer must have a considerably higher primary volt-ampere rating (approximately 40 per cent greater), for the same d.c. power output, than in other rectifier circuits.

Full-Wave Center-Tap Rectifier

The most universally used rectifier circuit is shown in Fig. 7-2B. Being essentially an arrangement in which the outputs of two half-wave rectifiers are combined, it makes use of both halves of the a.c. cycle. A transformer with a centertapped secondary is required with the circuit. When the plate of V_1 is positive, current flows through the load to the center tap. Current can-

not flow through V_2 because at this instant its cathode (or filament) is positive in respect to its plate. When the polarity reverses, V_2 conducts and current again flows through the load to the center-tap, this time through V_2 .

The average output voltage is 0.45 times the r.m.s. voltage of the entire transformersecondary, or 0.9 times the voltage across half of the transformer secondary. For the same total secondary voltage, the average output voltage is the same as that delivered with a half-wave rectifier. However, as can be seen from the sketches of the output wave form in (B) to the right, the frequency of the output pulses is twice that of the half-wave rectifier. Therefore much less filtering is required. Since the rectifiers work alternately, each handles half of the average load current. Therefore the loadcurrent rating of each rectifier need be only half the total load current drawn from the supply.

Two separate transformers, with their primaries connected in parallel and secondaries connected in series (with the proper polarity) may be used in this circuit. However, if this substitution is made, the primary volt-ampere rating must be reduced to about 40 per cent less than twice the rating of one transformer.

Full-Wave Bridge Rectifier

Another full-wave rectifier circuit is shown in Fig. 7-2C. In this arrangement, two rectifiers operate in series on each half of the cycle, one rectifier being in the lead to the load, the other being in the return lead. Over that portion of the cycle when the upper end of the transformer secondary is positive with respect to the other end, current flows through V_1 , through the load and thence through V_2 . During this period current cannot flow through rectifier V_4 because its plate is negative with respect to its cathode (or filament). Over the other half of the cycle, current flows through V_3 , through the load and

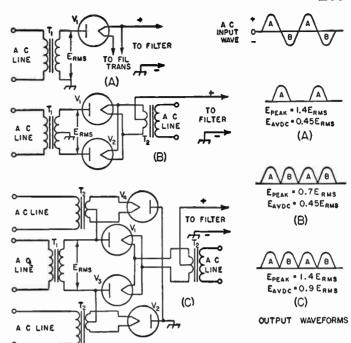


Fig. 7-2—Fundamental vacuum-tube rectifier circuits. A—Half-wave. B—Full-wave. C—Full-wave bridge. A.c.-input and pulsating-d.c. output wave forms are shown at the right. Output-voltage values indicated do not include rectifier drops. Other types of rectifiers may be substituted.

thence through V_4 . Three filament windings are needed-one for V1 and V8 and one each for V_2 and V_4 . The output wave shape (C), to the right, is the same as that from the simple center-tap rectifier circuit. The output voltage obtainable with this circuit is 0.9 times the r.m.s. voltage delivered by the transformer secondary. For the same total transformer-secondary voltage, the average output voltage when using the bridge rectifier will be twice that obtainable with the center-tap rectifier circuit. However, when comparing rectifier circuits for use with the same transformer, it should be remembered that the power which a given transformer will handle remains the same regardless of the rectifier circuit used. If the output voltage is doubled by substituting the bridge circuit for the center-tap rectifier circuit, only half the rated load current can be taken from the transformer without exceeding its normal rating. Each rectifier in a bridge circuit should have a minimum load-current rating of one half the total load current to be drawn from the supply.

Rectifiers

High-Vacuum Rectifiers

High-vacuum rectifiers depend entirely upon the thermionic emission from a heated filament and are characterized by a relatively high internal resistance. For this reason, their application usually is limited to low power, although there are a few types designed for medium and high power in cases where the relatively high internal voltage drop may be tolerated. This high internal resistance make them less susceptible to damage from temporary overload and they are free from the bothersome electrical noise sometimes associated with other types of rectifiers.

Some rectifiers of the high-vacuum full-wave type in the so-called receiver-tube class will handle up to 275 ma. at 400 to 500 volts d.c. output. Those in the higher-power class can be used to handle up to 500 ma. at 2000 volts d.c. in full-wave circuits. Most low-power high-vacuum rectifiers are produced in the full-wave type, while those for greater power are invariably of the half-wave type, two tubes being required for a full-wave rectifier circuit. A few of the lower-voltage types have indirectly heated cathodes, but are limited in heater-to-cathode voltage rating.

Mercury-Vapor Rectifiers

The voltage drop through a mercury-vapor rectifier is practically constant at approximately 15 volts regardless of the load current. For high power they have the advantage of cheapness. Rectifiers of this type, however, have a tendency toward a type of oscillation which produces noise in nearby receivers, sometimes difficult to eliminate. R.f. filtering in the primary circuit and at the rectifier plates as well as shielding may be required. As with high-vacuum rectifiers, full-wave types are available in the lower-power ratings only. For higher power, two tubes are required in a full-wave circuit.

Selenium and Other Semiconductor Rectifiers

Selenium, germanium and silicon rectifiers are finding increasing application in power supplies for amateur equipment. These units have the advantages of compactness, low internal voltage drop (about 5 volts per unit) and low operating temperature. Also, no filament transformers are required.

Individual units of all three types are available with input ratings of 130 volts r.m.s. Selenium units are rated at up to 1000 ma. or more d.c. load current; germanium units have ratings up to 400 ma., and silicon units up to several amperes. In full-wave circuits these load-current figures can be doubled.

The extreme compactness of silicon types makes feasible the stacking of several units in series for higher voltages. Standard stacks are available that will handle up to 2000 volts r.m.s. input at a d.c. load current of 325 ma. Two of these stacks in a full-wave circuit will handle 650 ma., although they are comparatively expensive.

Semiconductor rectifiers may be substituted in any of the basic circuits shown in Fig. 7-2, the terminal marked "+" or "cathode" corresponding to the filament connection. Advantage may be taken of the voltage-multiplying circuits discussed in a later section of this chapter in adapting rectifiers of this type.

Rectifier Ratings

All rectifiers are subject to limitations as to breakdown voltage and current-handling capability. Some tube types are rated in terms of the maximum r.m.s. voltage that should be applied to the rectifier plate. This is sometimes dependent

on whether a choke- or capacitive-input filter is used. Others, particularly mercury-vapor and semiconductor types, are rated according to maximum pcak inverse voltage (p.i.v.)—the peak voltage between anode and cathode while the rectifier is not conducting. In the circuits of Fig. 7-2, the p.i.v. across each rectifier is 1.4 times the r.m.s. value of the voltage delivered by the entire transformer secondary, except that if a capacitive-input filter is used with the half-wave rectifier circuit of Fig. 7-2A, the multiplying factor becomes 2.8.

Rectifiers are rated also as to maximum d.c. load current, and some may carry peak-current ratings in addition. To assure normal life, all ratings should be carefully observed. Staying within their ratings, rectifiers will deliver more current at a given output voltage with a choke-input filter than with capacitor input. However a higher a.c. voltage is required when the choke-input filter is used.


Operation of Rectifiers

In operating rectifiers requiring filament or cathode heating, care should be taken to provide the correct filament voltage at the tube terminals. Low filament voltage can cause excessive voltage drop in high-vacuum rectifiers and a considerable reduction in the inverse peak-voltage rating of a mercury-vapor tube. Filament connections to the rectifier socket should be firmly soldered, particularly in the case of the larger mercuryvapor tubes whose filaments operate at low voltage and high current. The socket should be selected with care, not only as to contact surface but also as to insulation, since the filament usually is at full output voltage to ground. Bakelite sockets will serve at voltages up to 500 or so, but ceramic sockets, well spaced from the chassis, always should be used at the higher voltages. Special filament transformers with high-voltage insulation between primary and secondary are required for rectifiers operating at potentials in excess of 1000 volts inverse peak.

The rectifier tubes should be placed in the equipment with adequate space surrounding them to provide for ventilation. When mercury-vapor tubes are first placed in service, and each time after the mercury has been disturbed, as by removal from the socket to a horizontal position, they should be run with filament voltage only for 30 minutes before applying high voltage. After that, a delay of 30 seconds is recommended each time the filament is turned on.

Rectifiers may be connected in parallel for current higher than the rated current of a single

Fig. 7-3—Connecting mercury-vapor rectifiers in parallel for heavier currents. R₁ and R₂ should have the same value, between 50 and 100 ohms, and corresponding filament terminals should be connected together.

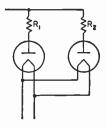

unit. This includes the use of the sections of a double diode for this purpose. With mercury-vapor types, equalizing resistors of 50 to 100 ohms

should be connected in series with each plate, as shown in Fig. 7-3, to help maintain an equal division of current between the two rectifiers.

FILTERS

The pulsating d.c. waves from the rectifiers shown in Fig. 7-2 are not sufficiently constant in amplitude to prevent hum corresponding to the pulsations. Filters consisting of capacitances and inductances are required between the rectifier and the load to smooth out the pulsations to an essentially constant d.c. voltage. Also, upon the design of the filter depends to a large extent the d.c. voltage output, the voltage regulation of the power supply and the maximum load current that can be drawn from the supply without exceeding the peak-current rating of the rectifier.

Power-supply filters fall into two classifications, depending upon whether the first filter element following the rectifier is a capacitor or a choke. Capacitive-input filters are characterized by relatively high output voltage in respect to the transformer voltage, but poor voltage regulation. Choke-input filters result in much better regulation, when properly designed, but the output voltage is less than would be obtained with a capacitive-input filter from the same transformer.

Voltage Regulation

The output voltage of a power supply always decreases as more current is drawn, not only because of increased voltage drops on the transformer, filter chokes and the rectifier (if high-vacuum rectifiers are used) but also because the output voltage at light loads tends to soar to the peak value of the transformer voltage as a result of charging the first capacitor. By proper filter design the latter effect can be eliminated. The change in output voltage with load is called voltage regulation and is expressed as a percentage.

Per cent regulation =
$$\frac{100 (E_1 - E_2)}{E_2}$$

Example: No-load voltage = E_1 = 1550 volts. Full-load voltage = E_2 = 1230 volts. Percentage regulation = $\frac{100 (1550 - 1230)}{1230}$

 $=\frac{32,000}{1230}$ = 26 per cent.

Regulation may be as great as 100% or more with a capacitive-input filter, but by proper design can be held to 20% or less with a choke-input filter.

Good regulation is desirable if the load current varies during operation, as in a keyed stage or a Class B modulator, because a large change in voltage may increase the tendency toward key clicks in the former case or distortion in the latter. On the other hand, a steady load, such as is represented by a receiver, speech amplifier or unkeyed stages in a transmitter, does not require good regulation so long as the proper voltage is obtained under load conditions. Another consideration that makes good voltage regulation desirable is that the filter capacitors must have a voltage rating safe for the highest value to which

the voltage will soar when the external load is removed.

When essentially constant voltage, regardless of current variation is required (for stabilizing an oscillator, for example), special voltage-regulating circuits described elsewhere in this chapter are used.

Load Resistance

In discussing the performance of power-supply filters, it is sometimes convenient to express the load connected to the output terminals of the supply in terms of resistance. The load resistance is equal to the output voltage divided by the total current drawn, including the current drawn by the bleeder resistor.

Input Resistance

The sum of the transformer impedance and the rectifier resistance is called the input resistance. The approximate transformer impedance is given by

$$Z_{\text{TR}} = N^2 R_{\text{PRI}} + R_{\text{SEC}}$$

where N is the transformer turns ratio, primary to secondary (primary to ½ secondary in the case of a full-wave rectifier), and R_{PRI} and R_{SEO} are the primary and secondary resistances respectively. R_{SEO} will be the resistance of half of the secondary in the case of a full-wave circuit.

Bleeder

A bleeder resistor is a resistance connected across the output terminals of the power supply (see Fig. 7-7). Its functions are to discharge the filter capacitors as a safety measure when the power is turned off and to improve voltage regulation by providing a minimum load resistance. When voltage regulation is not of importance, the resistance may be as high as 100 ohms per volt. The resistance value to be used for voltage-regulating purposes is discussed in later sections. From the consideration of safety, the power rating of the resistor should be as conservative as possible, since a burned-out bleeder resistor is more dangerous than none at all!

Ripple Frequency and Voltage

The pulsations in the output of the rectifier can be considered to be the resultant of an alternating current superimposed upon a steady direct current. From this viewpoint, the filter may be considered to consist of shunting capacitors which short-circuit the a.c. component while not interfering with the flow of the d.c. component, and series chokes which pass d.c. readily but which impede the flow of the a.c. component.

The alternating component is called the ripple. The effectiveness of the filter can be expressed in terms of per cent ripple, which is the ratio of the r.m.s. value of the ripple to the d.c. value in terms of percentage. For c.w. transmitters, the output ripple from the power supply should not exceed 5 per cent. The ripple in the ouput of supplies for voice transmitters should not exceed 1 per cent. Class B modulators require a ripple reduction to about 0.25%, while v.f.o.'s, high-gain speech amplifiers, and receivers may require a reduction in ripple to 0.01%.

Ripple frequency is the frequency of the pulsations in the rectifier output wave—the number of pulsations per second. The frequency of the ripple with half-wave rectifiers is the same as the frequency of the line supply—60 cycles with 60-cycle supply. Since the output pulses are doubled with a full-wave rectifier, the ripple frequency is doubled—to 120 cycles with 60-cycle supply.

The amount of filtering (values of inductance and capacitance) required to give adequate smoothing depends upon the ripple frequency, more filtering being required as the ripple frequency is lowered.

CAPACITIVE-INPUT FILTERS

Capacitive-input filter systems are shown in Fig. 7-4. Disregarding voltage drops in the chokes, all have the same characteristics except

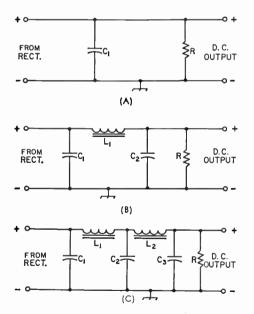


Fig. 7-4—Capacitive-input filter circuits. A—Simple capacitive. B—Single-section. C—Double-section.

in respect to ripple. Better ripple reduction will be obtained when *LC* sections are added, as shown in Figs. 7-4B and C.

Output Voltage

To determine the approximate d.c. voltage output when a capacitive-input filter is used, reference should be made to the graph of Fig. 7-5.

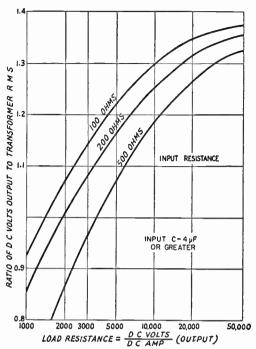


Fig. 7-5—Chart showing approximate ratio of d.c. output voltage across filter input capacitor to transformer r.m.s. secondary voltage for different load and input resistances.

Example:
Transformer r.m.s. voltage — 350
Input resistance — 200 ohms
Maximum load current, including bleeder
current — 175 ma.
Load resistance = 350
0.175 = 2000 ohms approx.

From Fig. 7-5, for a load resistance of 2000 ohms and an input resistance of 200 ohms, the d.c. output voltage is given as slightly over 1 times the transformer r.m.s. voltage, or about 350 volts.

Regulation

If a bleeder resistance of 50,000 ohms is used, the d.c. output voltage, as shown in Fig. 7-5, will rise to about 1.35 times the transformer r.m.s. value, or about 470 volts, when the external load is removed. For greater accuracy, the voltage drops through the input resistance and the resistance of the chokes should be subtracted from the values determined above. For best regulation with a capacitive-input filter, the bleeder resistance should be as low as possible without exceeding the transformer, rectifier or choke ratings when the external load is connected.

Maximum Rectifier Current

The maximum current that can be drawn from a supply with a capacitive-input filter without exceeding the peak-current rating of the rectifier may be estimated from the graph of Fig. 7-6. Using values from the preceding example, the ratio of peak rectifier current to d.c. load current

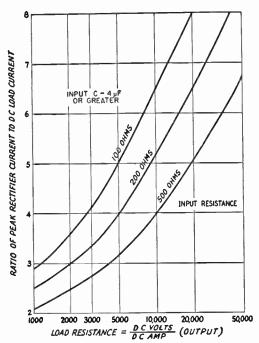


Fig. 7-6—Graph showing the relationship between the d.c. load current and the rectifier peak plate current with capacitive input for various values of load and input resistance.

for 2000 ohms, as shown in Fig. 7-6 is 3. Therefore, the maximum load current that can be drawn without exceeding the rectifier rating is $\frac{1}{3}$ the peak rating of the rectifier. For a load current of 175 ma., as above, the rectifier peak current rating should be at least $3 \times 175 = 525$ ma.

With bleeder current only, Fig. 7-6 shows that the ratio will increase to over 8. But since the bleeder draws less than 10 ma. d.c., the rectifier peak current will be only 90 ma. or less.

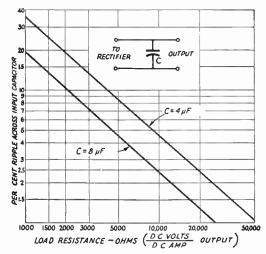


Fig. 7-7—Showing approximate 120-cycle percentage ripple across filter input capacitor for various loads.

Ripple Filtering

The approximate ripple percentage after the simple capacitive filter of Fig. 7-4A may be determined from Fig. 7-7. With a load resistance of 2000 ohms, for instance, the ripple will be approximately 10% with an 8- μ f. capacitor or 20% with a 4- μ f. capacitor. For other capacitances, the ripple will be in inverse proportion to the capacitance, e.g., 5% with 16 μ f., 40% with 2 μ f., and so forth.

The ripple can be reduced further by the addition of LC sections as shown in Figs. 7-4B and C. Fig. 7-8 shows the factor by which the ripple from any preceding section is reduced depending on the product of the capacitance and inductance added. For instance, if a section composed of a choke of 5 h. and a capacitor of 4 μ f. were to be added to the simple capacitor of Fig. 7-4A, the product is $4 \times 5 = 20$. Fig. 7-8 shows that the original ripple (10% as above with 8 μ f. for example) will be reduced by a factor of about 0.09. Therefore the ripple percentage after the new section will be approximately 0.09 \times 10 = 0.9%. If another section is added to the filter, its reduction factor from Fig. 7-8 will be applied to the

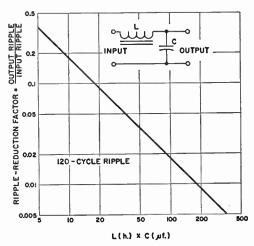


Fig. 7-8—Ripple-reduction factor for various values of L and C in filter section. Output ripple = input ripple × ripple factor.


0.9% from the preceding section; $0.9 \times 0.09 = 0.081\%$ (if the second section has the same *LC* product as the first).

CHOKE-INPUT FILTERS

Much better voltage regulation results when a choke-input filter, as shown in Fig. 7-9, is used. Choke input also permits better utilization of the rectifier, since a higher load current usually can be drawn without exceeding the peak current rating of the rectifier.

Minimum Choke Inductance

A choke-input filter will tend to act as a capacitive-input filter unless the input choke has at

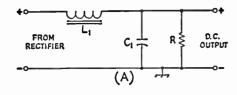

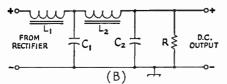


Fig. 7-9—Choke-input filter circuits. A—Single-section.

B—Double-section.

least a certain minimum value of inductance called the **critical** value. This critical value is given by

$$L_{\rm h} = \frac{E_{\rm VOLTS}}{I_{\rm MA.}}$$

where E is the output voltage of the supply, and I is the current being drawn from the supply.

If the choke has at least the critical value, the output voltage will be limited to the average value of the rectified wave at the input to the choke (see Fig. 7-2) when the current drawn from the supply is small. This is in contrast to the capacitive-input filter in which the output voltage tends to soar toward the peak value of the rectified wave at light loads. Also, if the input choke has at least the critical value, the rectifier peak plate current will be limited to about twice the d.c. current drawn from the supply. Most rectifier tubes have peak-current ratings of three to four times their maximum d.c. output-current ratings. Therefore, with an input choke of at least critical inductance, current up to the maximum output-current rating of the rectifier may be drawn from the supply without exceeding the peak-current rating of the rectifier.

Minimum-Load-Bleeder Resistance

From the formula above for critical inductance, it is obvious that if no current is drawn from the supply, the critical inductance will be infinite. So that a practical value of inductance may be used, some current must be drawn from the supply at all times the supply is in use. From the formula we find that this minimum value of current is

$$I_{\text{MA.}} = \frac{E_{\text{VOLTS}}}{L_{\text{h}}}$$

Thus, if the choke has an inductance of 20 h., and the output voltage is 2000, the minimum load current should be 100 ma. This load may be provided, for example, by transmitter stages that draw current continuously (stages that are not keyed). However, in the majority of cases it will be most convenient to adjust the bleeder resistance so that the bleeder will draw the required minimum current. In the above example, the bleeder resistance should be 2000/0.1 = 20,000 ohms.

From the formula for critical inductance, it is seen that when more current is drawn from the supply, the critical inductance becomes less. Thus, as an example, when the total current, including the 100 ma. drawn by the bleeder rises to 400 ma., the choke need have an inductance of only 5 h. to maintain the critical value. This is fortunate, because chokes having the required inductance for the bleeder load only and that will

Swinging Chokes

currents are very expensive.

maintain this value of inductance for much larger

Less costly chokes are available that will maintain at least critical value of inductance over the range of current likely to be drawn from practical supplies. These chokes are called swinging chokes. As an example, a swinging choke may have an inductance rating of 5/25 h, and a current rating of 225 ma. If the supply delivers 1000 volts, the minimum load current should be 1000/25 = 40 ma. When the full load current of 225 ma, is drawn from the supply, the inductance will drop to 5 h. The critical inductance for 225 ma. at 1000 volts is 1000/225 = 4.5 h. Therefore the 5/25-h. choke maintains at least the critical inductance at the full current rating of 225 ma. At all load currents between 40 ma. and 225 ma., the choke will adjust its inductance to at least the approximate critical value.

Table 7-I shows the maximum supply output voltage that can be used with commonly-available swinging chokes to maintain critical inductance at the maximum current rating of the choke. These chokes will also maintain critical inductance for any lower values of voltage, or current down to the required minimum drawn by a proper bleeder as discussed above.

In the case of supplies for higher voltages in particular, the limitation on maximum load re-

TABLE 7-I									
L _h Max. Max. Max. M ma, volts R ¹ m									
3.5/13.5	150	525	13.5K	39					
5/25	175	875	25K	35					
2/12	200	400	12 K	33					
5/25	200	1000	25K.	40					
5/25	225	1125	25 K	45					
2/12	250	500	12K	42					
4/20	300	1200	20 K	60					
5/25	300	1500	25 K	60					
3/17	400	1200	17K	71					
4/20	400	1600	20K	80					
5/25	400	2000	25K	80					
4/16	500	2000	16K	125					
5/25	500	2500	25K	100					
5/25	550	2750	25K	110					

¹ Maximum bleeder resistance for critical in-

² Minimum current (bleeder) for critical inductance.

sistance may result in the wasting of an appreciable portion of the transformer power capacity in the bleeder resistance. Two input chokes in series will permit the use of a bleeder of twice the resistance, cutting the wasted current in half. Another alternative that can be used in a c.w. transmitter is to use a very high-resistance bleeder for protective purposes and only sufficient fixed bias on the tubes operating from the supply to bring the total current drawn from the supply, when the key is open, to the value of current that the required bleeder resistance should draw from the supply. Operating bias is brought back up to normal by increasing the grid-leak resistance. Thus the entire current capacity of the supply (with the exception of the small drain of the protective bleeder) can be used in operating the transmitter stages. With this system, it is advisable to operate the tubes at phone, rather than c.w., rating, since the average dissipation is increased.

Output Voltage

Provided the input-choke inductance is at least the critical value, the output voltage may be calculated quite closely by the following equation:

$$E_0 = 0.9E_t - (I_B + I_L) (R_1 + R_2) - E_r$$

where E_0 is the output voltage; E_t is the r.m.s. voltage applied to the rectifier (r.m.s. voltage between center-tap and one end of the secondary in the case of the center-tap rectifier); I_B and I_L are the bleeder and load currents, respectively, in amperes; R_1 and R_2 are the resistances of the first and second filter chokes; and E_r is the drop between rectifier plate and cathode. The various voltage drops are shown in Fig. 7-12. At no load I_L is zero, hence the no-load voltage may be calculated on the basis of bleeder current only. The voltage regulation may be determined from

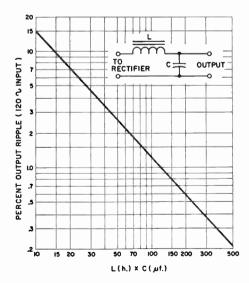


Fig. 7-10—Graph showing combinations of inductance and capacitance that may be used to reduce ripple with a single-section choke-input filter.

the no-load and full-load voltages using the formula previously given.

Ripple with Choke Input

The percentage ripple output from a singlesection filter (Fig. 7-9A) may be determined to a close approximation, for a ripple frequency of 120 cycles, from Fig. 7-10.

> Example: L = 5 h., $C = 4 \mu f.$, LC = 20. From Fig. 7-10, percentage ripple = 7 per cent.

Example: L=5 h. What capacitance is needed to reduce the ripple to 1 per cent? Following the 1-per-cent line to the right to its intersection with the diagonal, thence downward to the LC scale, read LC=120. 120/5 = 24 uf.

In selecting values for the first filter section, the inductance of the choke should be determined by the considerations discussed previously. Then the capacitor should be selected that when combined with the choke inductance (minimum inductance in the case of a swinging choke) will bring the ripple down to the desired value. If it is found impossible to bring the ripple down to the desired figure with practical values in a single section, a second section can be added, as shown in Fig. 7-9B and the reduction factor from Fig. 7-8 applied as discussed under capacitive-input filters. The second choke should not be of the swinging type, but one having a more or less constant inductance with changes in current (smoothing choke).

OUTPUT CAPACITOR

If the supply is intended for use with an audiofrequency amplifier, the reactance of the last filter capacitor should be small (20 per cent or less) compared with the other audio-frequency resistance or impedance in the circuit, usually the tube plate resistance and load resistance. On the basis of a lower a.f. limit of 100 cycles for speech amplification, this condition usually is satisfied when the output capacitance (last filter capacitor) of the filter has a capacitance of 4 to 8 μ f., the higher value of capacitance being used in the case of lower tube and load resistances.

RESONANCE

Resonance effects in the series circuit across the output of the rectifier which is formed by the first choke (L_1) and first filter capacitor (C1) must be avoided, since the ripple voltage would build up to large values. This not only is the opposite action to that for which the filter is intended, but also may cause excessive rectifier peak currents and abnormally high inverse peak voltages. For full-wave rectification the ripple frequency will be 120 cycles for a 60-cycle supply, and resonance will occur when the product of choke inductance in henrys times capacitor capacitance in microfarads is equal to 1.77. The corresponding figure for 50-cycle supply (100-cycle ripple frequency) is 2.53, and for 25cycle supply (50-cycle ripple frequency) 13.5. At least twice these products of inductance and capacitance should be used to ensure against resonance effects. With a swinging choke, the minimum rated inductance of the choke should be used.

RATINGS OF FILTER COMPONENTS

Although filter capacitors in a choke-input filter are subjected to smaller variations in d.c. voltage than in the capacitive-input filter, it is advisable to use capacitors rated for the peak transformer voltage in case the bleeder resistor should burn out when there is no load on the power supply, since the voltage then will rise to the same maximum value as it would with a filter of the capacitive-input type.

In a capacitive-input filter, the capacitors should have a working-voltage rating at least as high, and preferably somewhat higher, than the peak-voltage rating of the transformer. Thus, in the case of a center-tap rectifier having a transformer delivering 550 volts each side of the center-tap, the minimum safe capacitor voltage rating will be 550×1.41 or 775 volts. An 800-volt capacitor should be used, or preferably a 1000-volt unit.

Filter Capacitors in Series

Filter capacitors are made in several different types. Electrolytic capacitors, which are available for peak voltages up to about 800, combine high capacitance with small size, since the dielectric is an extremely thin film of oxide on aluminum foil. Capacitors of this type may be connected in series for higher voltages, although the filtering capacitance will be reduced to the resultant of the two capacitances in series. If this arrangement is used, it is important that each of the capacitors be shunted with a resistor of about 100 ohms per volt of supply voltage, with a power rating adequate for the total resistor current at that voltage. These resistors may serve as all or part of the bleeder resistance (see choke-input filters). Capacitors with higher-voltage ratings usually are made with a dielectric of thin paper impregnated with oil. The working voltage of a capacitor is the voltage that it will withstand continuously.

Filter Chokes

The input choke may be of the swinging type, the required minimum no-load and full-load inductance values being calculated as described above. For the second choke (smoothing choke) values of 4 to 20 henrys ordinarily are used. When filter chokes are placed in the positive leads, the negative being grounded, the windings should be insulated from the core to withstand the full d.c. output voltage of the supply and be capable of handling the required load current.

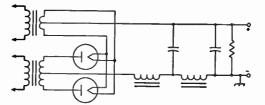


Fig. 7-11—In most applications, the filter chokes may be placed in the negative instead of the positive side of the circuit. This reduces the danger of a voltage breakdown between the choke winding and core.

Filter chokes or inductances are wound on iron cores, with a small gap in the core to prevent magnetic saturation of the iron at high currents. When the iron becomes saturated its permeability decreases, consequently the inductance also decreases. Despite the air gap, the inductance of a choke usualy varies to some extent with the direct current flowing in the winding; hence it is necessary to specify the inductance at the current which the choke is intended to carry. Its inductance with little or no direct current flowing in the winding may be considerably higher than the value when full load current is flowing.

NEGATIVE-LEAD FILTERING

For many years it has been almost universal practice to place filter chokes in the positive leads of plate power supplies. This means that the insulation between the choke winding and its core (which should be grounded to chassis as a safety measure) must be adequate to withstand the output voltage of the supply. This voltage requirement is removed if the chokes are placed in the negative lead as shown in Fig. 7-11. With this connection, the capacitance of the transformer secondary to ground appears in parallel with the filter chokes tending to bypass the chokes. However, this effect will be negligible in practical application except in cases where the output ripple must be reduced to a very low figure. Such applications are usually limited to low-voltage devices such as receivers, speech amplifiers and v.f.o.'s where insulation is no problem and the chokes may be placed in the positive side in the conventional manner. In higher-voltage applications, there is no reason why the filter chokes should not be placed in the negative lead to reduce insulation requirements. Choke terminals, negative capacitor terminals and the transformer center-tap terminal should be well protected against accidental contact, since these will assume full supply voltage to chassis should a choke burn out or the chassis connection fail.

PLATE AND FILAMENT TRANSFORMERS


Output Voltage

The output voltage which the plate transformer must deliver depends upon the required

d.c. load voltage and the type of filter circuit.

With a choke-input filter, the required r.m.s. secondary voltage (each side of center-tap for a

Fig. 7-12—Diagram showing various voltage drops that must be taken into consideration in determining the required transformer voltage to deliver the desired output voltage.

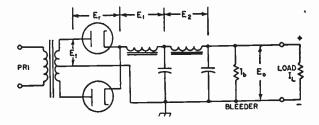

center-tap rectifier) can be calculated by the equation:

$$E_{\rm t} = 1.1 \Big[E_{\rm o} + I(R_1 + R_2) + E \Big]$$

where E_o is the required d.c. output voltage, I is the load current (including bleeder current) in amperes, R_1 and R_2 are the d.c. resistances of the chokes, and E_r is the voltage drop in the rectifier. E_t is the full-load r.m.s. secondary voltage; the open-circuit voltage usually will be 5 to 10 per cent higher than the full-load value.

The approximate transformer output voltage required to give a desired d.c. output voltage with a given load with a capacitive-input filter system can be calculated with Fig. 7-12.

Example:

Required d.c. output volts — 500

Load current to be drawn — 100 ma. (0.1 amp)

Load resistance =
$$\frac{500}{0.1}$$
 = 5000 ohms.

If the rectifier resistance is 200 ohms, Fig. 7-5 shows that the ratio of d.c. volts to the required transformer r.m.s. voltage is approximately 1.15.

The required transformer terminal voltage under load with chokes of 200 and 300 ohms is

$$E_{1} = \frac{E_{0} + I\left(R_{1} + R_{2} + R_{r}\right)}{1.15}$$

$$= \frac{500 + 0.1\left(200 + 300 + 200\right)}{1.15}$$

$$= \frac{570}{1.15} = 495 \text{ volts.}$$

Volt-Ampere Rating

The volt-ampere rating of the transformer depends upon the type of filter (capacitive or choke input). With a capacitive-input filter the heating effect in the secondary is higher because of the high ratio of peak to average current, consequently the volt-amperes handled by the transformer may be several times the watts delivered to the load. With a choke-input filter, provided the input choke has at least the critical inductance, the secondary volt-amperes can be calculated quite closely by the equation:

Sec.
$$V.A. = 0.00075EI$$

where E is the total r.m.s. voltage of the secondary (between the outside ends in the case of a center-tapped winding) and I is the d.c. output current in milliamperes (load current plus bleeder

current). The primary volt-amperes will be 10 to 20 per cent higher because of transformer losses

Broadcast & Television Replacement Transformers in Amateur Transmitter Service

Small power transformers of the type sold for replacement in broadcast and television receivers are usually designed for service in terms of use for several hours continuously with capacitor-input filters. In the usual type of amateur transmitter service, where most of the power is drawn intermittently for periods of several minutes with equivalent intervals in between, the published ratings can be exceeded without excessive transformer heating.

With capacitor input, it should be safe to draw 20 to 30 per cent more current than the rated value. With a choke-input filter, an increase in current of about 50 per cent is permissible. If a bridge rectifier is used (with a choke-input filter) the output voltage will be approximately doubled. In this case, it should be possible in amateur transmitter service to draw the rated current, thus obtaining about twice the rated output power from the transformer.

This does not apply, of course, to amateur transmitter plate transformers which are usually already rated for intermittent service.

Filament Supply

Except for tubes designed for battery operation, the filaments or heaters of vacuum tubes used in both transmitters and receivers are universally operated on alternating current obtained from the power line through a step-down transformer delivering a secondary voltage equal to the rated voltage of the tubes used. The transformer should be designed to carry the current taken by the number of tubes which may be connected in parallel across it. The filament or heater transformer generally is center-tapped, to provide a balanced circuit for eliminating hum.

For medium- and high-power r.f. stages of transmitters, and for high-power audio stages, it is desirable to use a separate filament transformer for each section of the transmitter, installed near the tube sockets. This avoids the necessity for abnormally large wires to carry the total filament current for all stages without appreciable voltage drop. Maintenance of rated filament voltage is highly important, especially with thoriated-filament tubes, since under- or over-voltage may reduce filament life.

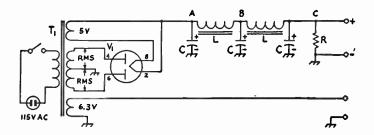


Fig. 7-13—Typical a.c. powersupply circuit for receivers, exciters, or low-power transmitters. Representative values will be found in Table 7-11. The 5-volt winding of 7₁ should have a current rating of at least 2 amp. for types 5Y3-GT and 5V4-GA, and 3 amp. for 5U4-GB.

TYPICAL POWER SUPPLIES

Figs. 7-13 and 7-14 show typical power-supply circuits. Fig. 7-13 is for use with transformers commonly listed as broadcast or television replacement power transformers. In addition to the high-voltage winding for plate supply, these transformers have windings that supply filament voltages for both the rectifier tube and the 6.3-volt tubes in the receiver or low-power transmitter or exciter. Transformers of this type may be obtained in ratings up to 1200 volts r.m.s. centertapped, 200 d.c. ma. output.

Fig. 7-13 shows a two-section filter with capacitor input. However, depending upon the maximum hum level that may be allowable for a particular application, the last capacitor and choke may not be needed. In some low-current applications, the first capacitor alone may provide adequate filtering. Table 7-II shows the

approximate full-load and bleeder-load output voltages and a.c. ripple percentages for several representative sets of components. Voltage and ripple values are given for three points in the circuit—Point A (first capacitor only used), Point B (last capacitor and choke omitted), and Point C (complete two-section filter in use). In each case, the bleeder resistor R should be used across the output.

Table 7-II also shows approximate output voltages and ripple percentages for choke-input filters (first filter capacitor omitted), for Point B (last capacitor and choke omitted), and Point C (complete two-section filter, first capacitor omitted).

Actual full-load output voltages may be somewhat lower than those shown in the table, since the voltage drop through the resistance of the transformer secondary has not been included.

							TA	BLE 7-I	l							
						Capac	itor-Inp	out Pow	er Su	pplie	5					_
T ₁ Rating	V ₁ C L				Ful	Approximate Full-load d.c. Volts at				% A	pprox.	Useful				
Total Volts R.M.S.	Ma. D.C.	Tube Type	μf.	Volts	Н.	Ohms	Ohms	Watts	A	В	С	A	В	B	Volts leeder Load	Outpu Ma.*
650	40	5Y3-GT	8	600	8	400	90K	5	375	360	345	2.5	0.08	0.002	450	36
650	40	5V4-GA	8	600	8	400	90K	5	410	395	375	2.5	0.08	0.002	450	36
700	90	5Y3-GT	8	600	10	225	46K	10	370	350	330	6	0.1	0.002	460	82
700	90	5V4-GA	8	600	10	225	46K	10	410	390	370	6	0.1	0.002	460	82
750	150	5U4-GB	8	700	8	145	25K	10	375	350	330	9	0.2	0.006	500	136
750	150	5V4-GA	8	700	8	145	25K	10	425	400	380	9	0.2	0.006	500	136
800	200	5U4-GB	8	700	8	120	22K	20	375	350	325	12	0.3	0.008	550	184
						Chol	e-Inpu	Power	Sup	plies						
650	40	5Y3-GT	8	450	15	420	18K	10	—	240	225	—	0.8	0.01	265	25
650	40	5V4-GA	8	450	15	420	18K	10	_	255	240	_	0.8	0.01	280	25
700	90	5Y3-GT	8	450	10	225	11K	10	-	240	220	_	1.25	0.02	250	68
700	90	5V4-GA	8	450	10	225	11K	10	_	270	250	_	1.25	0.02	280	68
750	150	5Y3-GT	8	450	12	150	13 K\	20		265	245	_	1	0.015	325	125
750	150	5V4-GA	8	450	12	150	13K	20		280	260	_	1	0.015	340	125
800	200	5U4-GB	8	450	12	140	14K	20		275	250		1	0.015	350	175

Voltage Dropping

Fig. 7-14 shows the conventional circuit of a transmitter plate supply for higher powers. A full-wave rectifier circuit, half-wave rectifier tubes, and separate transformers for high voltage, rectifier filaments and transmitter filaments are

used. The high-voltage transformers used in this circuit are usually rated directly in terms of d.c. output voltage, assuming rectifiers and filters of the type shown in Fig. 7-14. Table 7-III shows typical values for representative supplies, based

Fig. 7-14—Conventional powersupply circuit for higher-power tronsmitters.

C₁, C₂—4 μ f. for approximately 0.5% output ripple; 2 μ f. for approximately 1.5% output ripple. C₂ should be 4 μ f. if supply is for modulator.


R-25,000 ohms.

L₁—Swinging choke: 5/25 h., current rating same as 7₃.

La—Smoothing choke: current rating same as 72.

T₁-2.5 volts, 4 amp., 2500-v. ins. for type 816; 2.5 volts, 10 amp., 10,000-v. ins. for 866A.

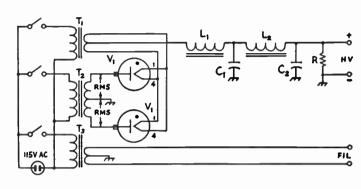T₃—D.c. voltage rating same as output voltage.
T₃—Voltage and current rating to suit transmitter-tube requirements.



V₁—Type 816 for 400/500-volt supply; 866A for athers shown in Table 7-III. See Table 7-III for other values.

on commonly available Transcomponents. former voltages shown are representative for units with dual-voltage secondaries. The bleeder-load voltages shown may be somewhat lower than actually found in practice. Ripple at the output of the first filter section will be approximately 5 per cent with a $4-\mu f$. capacitor, or 10 per cent with a 2-µf. capac-Transformers made for amateur service are designed for choke-input. If a capacitor-input is used rating should be reduced about 30%.

TABLE 7-III										
Approx. Out		T ₁ Rati	La	Voltage	R	Approx. Bleeder-				
Volts	Ma. 1	Approx. V.R.M.S.	Ma.	Н.	Rating C1, C1	Watts	Load Output Volts			
400/500	230	520/615	250	4	700	20	440/540			
600/750	260	750/950	300	8	1000	50	650/800			
1250/1500	240	1500/1750	300	8	2000	150	1300/1600			
1250/1500	440	1500/1750	500	6	2000	150	1315/1615			
2000/2500	200	2400/2900	300 4	8	3000	320 ª	2050/2550			
2000/2500	400	2400/2900	500	6	3000	320 °	2065/2565			
2500/3000	380	2500/3450	500 B	6	4000	500 8	2565/3065			

- ¹ Balance of transformer current rating consumed by bleeder resistor.
- *Use two 160-watt, 12,500-ohm units in series.
- * Use five 100-watt, 5000-ohm units in series.
- 4 Regulation will be somewhat better with a 400- or 500-ma. choke.
- ⁸ Regulation will be somewhat better with a 550-ma. choke.

VOLTAGE DROPPING

Series Voltage-Dropping Resistor

Certain plates and screens of the various tubes in a transmitter or receiver often require a variety of operating voltages differing from the output voltage of an available power supply. In most cases, it is not economically feasible to provide a separate power supply for each of the required voltages. If the current drawn by an electrode, or combination of electrodes operating at the same voltage, is reasonably constant under

normal operating conditions, the required voltage may be obtained from a supply of higher voltage by means of a voltage-dropping resistor in series, as shown in Fig. 7-15A. The value of the series, resistor, R_1 , may be obtained from Ohm's Law, $R = \frac{E_d}{I}$, where E_d is the voltage drop required from the supply voltage to the desired voltage and I is the total rated current of the load.

Example: The plate of the tube in one stage and the screens of the tubes in two other stages

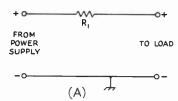


Fig. 7-15—A—A series voltage-dropping resistor. B—Simple voltage divider.

$$R_2 = \frac{E_1}{I_2}$$
; $R_1 = \frac{E - E_1}{I_1 + I_2}$.

I₂ must be assumed.C—Multiple divider circuit.

$$R_3 = \frac{E_2}{I_3}$$
, $R_2 = \frac{E_1 - E_2}{I_2 + I_3}$, $R_1 = \frac{E - E_1}{I_1 + I_2 + I_3}$


require an operating voltage of 250. The nearest available supply voltage is 400 and the total of the rated plate and screen currents is 75 ma. The required resistance is

$$R = \frac{400 - 250}{0.075} = \frac{150}{0.075} = 2000 \text{ ohms.}$$

The power rating of the resistor is obtained from P (watts) = $I^2R = (0.075)^2$ (2000) = 11.2 watts. A 20-watt resistor is the nearest safe rating to be used.

Voltage Dividers

The regulation of the voltage obtained in this manner obviously is poor, since any change in current through the resistor will cause a directly proportional change in the voltage drop across the resistor. The regulation can be improved somewhat by connecting a second resistor from the low-voltage end of the first to the negative power-supply terminal, as shown in Fig. 7-15B. Such an arrangement constitutes a voltage divider. The second resistor, R_2 , acts as a constant load for the first, R1, so that any variation in current from the tap becomes a smaller percentage of the total current through R_1 . The heavier the current drawn by the resistors when they alone are connected across the supply, the better will be the voltage regulation at the tap.

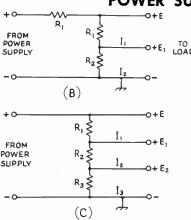

Such a voltage divider may have more than a single tap for the purpose of obtaining more than one value of voltage. A typical arrangement is shown in Fig. 7-15C. The terminal voltage is E, and two taps are provided to give power voltages, E_1 and E_2 , at currents I_1 and I_2 respectively. The smaller the resistance between taps in proportion to the total resistance, the smaller the voltage between the taps. For convenience, the voltage divider in the figure is considered to be made up of separate resistances R_1 , R_2 , R_3 , between taps. R₃ carries only the bleeder current, I₃; R₂ carries I_2 in addition to I_3 ; R_1 carries I_1 , I_2 and I_3 . To calculate the resistances required, a bleeder current, I_3 , must be assumed; generally it is low compared with the total load current (10 per cent or so). Then the required values can be calculated as shown in the caption of Fig. 7-15C, I being in decimal parts of an ampere.

The method may be extended to any desired number of taps, each resistance section being calculated by Ohm's Law using the needed voltage drop across it and the total current through it. The power dissipated by each section may be calculated either by multiplying I and E or I^2 and R,

VOLTAGE STABILIZATION

Gaseous Regulator Tubes

There is frequent need for maintaining the voltage applied to a low-voltage low-current circuit at a practically constant value, regardless of the voltage regulation of the power supply or variations in load current. In such applications,

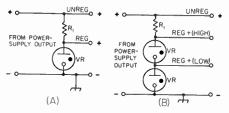


Fig. 7-16—Voltage-stabilizing circuits using VR tubes.

gaseous regulator tubes (0C3/VR105, 0D3/VR150, etc.) can be used to good advantage. The voltage drop across such tubes is constant over a moderately wide current range. Tubes are available for regulated voltages near 150, 105, 90 and 75 volts.

The fundamental circuit for a gaseous regulator is shown in Fig. 7-16A. The tube is connected in series with a limiting resistor, R_1 , across a source of voltage that must be higher than the starting voltage. The starting voltage is about 30 to 40 per cent higher than the operating voltage. The road is connected in parallel with the tube. For stable operation, a minimum tube current of 5 to 10 ma. is required. The maximum permissible current with most types is 40 ma.; consequently, the load current cannot exceed 30 to 35 ma. if the voltage is to be stabi-

Voltage Stabilization

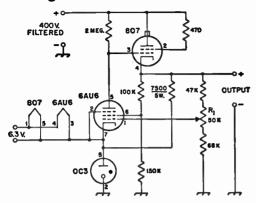


Fig. 7-17—Electronic voltage-regulator circuit. Resistors are ½ watt unless specified otherwise.

lized over a range from zero to maximum load current.

The value of the limiting resistor must lie between that which just permits minimum tube current to flow and that which just passes the maximum permissible tube current when there is no load current. The latter value is generally used. It is given by the equation:

$$R = \frac{(E_{\bullet} - E_{\rm r})}{I}$$


where R is the limiting resistance in ohms, E_8 is the voltage of the source across which the tube and resistor are connected, Er is the rated voltage drop across the regulator tube, and I is the maximum tube current in amperes, (usually 40 ma., or 0.04 amp.).

Fig. 7-16B shows how two tubes may be used

in series to give a higher regulated voltage than is obtainable with one, and also to give two values of regulated voltage. The limiting resistor may be calculated as above, using the sum of the voltage drops across the two tubes for E_r . Since the upper tube must carry more current than the lower, the load connected to the low-voltage tap must take small current. The total current taken by the loads on both the high and low taps should not exceed 30 to 35 milliamperes.

Voltage regulation of the order of 1 per cent can be obtained with these regulator circuits.

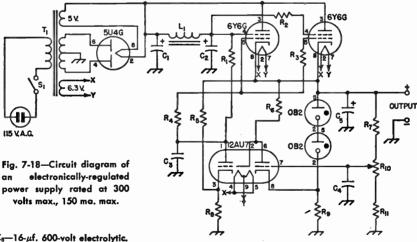A single VR tube may also be used to regulate the voltage to a load current of almost any value so long as the variation in the current does not exceed 30 to 35 ma. If, for example, the average load current is 100 ma., a VR tube may be used to hold the voltage constant provided the cur-



C₁, C₂, C₅-16-\(\mu f\). 600-volt electrolytic.

 C_8 —0.015- μ f. paper.

 C_4 —0.1- μ f. paper.

R₁-0.3 megohm, ½ watt.

R₂, R₃-100 ohms, ½ watt.

R₄-510 ohms, 1/2 watt.

R₅, R₈-30,000 ohms, 2 watts.

Rs-0.24 megohm, 1/2 watt.

R₂-0.15 megohm, ½ watt.

R₉-9100 ohms, 1 watt.

R₁₀-0.1-megohm potentiometer.

R₁₁-43,000 ohms, ½ watt.

L₁-8-hy., 40-ma. filter choke.

\$1-S.p.s.t. toggle.

T₁-Power transformer: 375-375 voltsr.m.s., 160 ma.; 6.3 volts, 3 amps.; 5 volts, 3 amps. (Thor. 22R33).

rent does not fall below 85 ma, or rise above 115 ma. In this case, the resistance should be calculated to drop the voltage to the VR-tube rating at the maximum load current to be expected plus about 5 ma. If the load resistance is constant, the effects of variations in line voltage may be eliminated by basing the resistance on the load current plus 15 ma. Voltage-regulator tubes may also be connected in parallel as described later in this chapter.

Electronic Voltage Regulation

Several circuits have been developed for regulating the voltage output of a power supply electronically. While more complicated than the VRtube circuits, they will handle higher voltages currents and the output voltage may be varied continuously over a wide range. In the circuit of Fig. 7-17, the 0C3 regulator tube supplies a reference of approximately +105 volts for the 6AU6 control tube. When the load connected across the output terminals increases, the output voltage tends to decrease. This makes the voltage on the control grid of the 6AU6 less positive, causing the tube to draw less current through the 2megohm plate resistor. As a consequence the grid voltage on the 807 series regulator becomes more positive and the voltage drop across the 807 decreases, compensating for the reduction in output voltage. With the values shown, adjustment of R₁ will give a regulated output from 150 to 250 volts, at up to 60 or 70 ma. A 6L6-GB can be substituted for the type 807; the available output current can be increased by adding tubes in parallel with the series regulator tube. When this is done, 100-ohm resistors should be wired to

Table of Performance for Circuit of Fig. 7-18									
\overline{I}	II	III	Output voltage - 300						
450 v.	22 ma.	3 mv.	150 ma. 2.3 mv.						
425 v.	45 ma.	4 mv.	125 ma. 2.8 mv.						
400 v.	72 ma.	6 mv.	100 ma. 2.6 mv.						
375 v.	97 ma.	8 mv.	75 ma. 2.5 mv.						
350 v.	122 ma.	9.5 mv.	50 ma. 3.0 mv.						
325 v.	150 ma.	3 my.	25 ma. 3.0 mv.						
300 v.	150 ma.	2.3 mv.	10 ma. 2.5 mv.						

each control grid and plate terminal, to reduce the chances for parasitic oscillations.

Another similar regulator circuit is shown in Fig. 7-18. The principal difference is that screengrid regulator tubes are used. The fact that a screen-grid tube is relatively insensitive to changes in plate voltage makes it possible to obtain a reduction in ripple voltage adequate for many purposes simply by supplying filtered d.c. to the screens with a consequent saving in weight and cost. The accompanying table shows the performance of the circuit of Fig. 7-18. Column I shows various output voltages, while Column II shows the maximum current that can be drawn at that voltage with negligible variation in output voltage. Column III shows the measured ripple at the maximum current. The second part of the table shows the variation in ripple with load current at 300 volts output.

High-Voltage Regulators

Regulated screen voltage is required for screengrid tubes used as linear amplifiers in single-sideband operation. Figs. 7-19 through 7-22 show various different circuits for supplying regulated voltages up to 1200 volts or more.

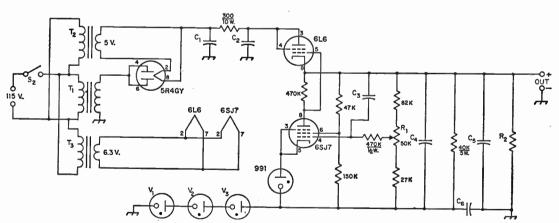


Fig. 7-19—High-voltage regulator circuit by W4PRM. Resistors are 1 watt unless indicated otherwise.

C₁, C₂—4-μf. paper, voltage rating above peak-voltage output of T_1 .

 C_8 -0.1- μf . paper, 600 volts.

C4-12-µf. electroyltic, 450 volts.

 C_5 —40 μ f., voltage rating above d.c. output voltage. Can be made up of a combination of electrolytics in series, with equalizing resistor. (See section on ratings of filter components.)

C₆—4-µt. paper, voltage rating above voltage rating of VR string.

R₁-50,000-ohm, 4-watt potentiometer.

R₂—Bleeder resistor, 50,000 to 100,000 ohms, 25 watts (not needed if equalizing resistors mentioned above are used).

T₁-See text.

T2-Filament transformer; 5 volts, 2 amp.

T₃-Filament transformer; 6.3 volts, 1.2 amp.

V₁, V₂, V₈—See text.

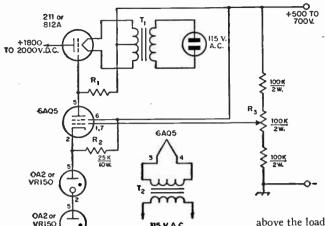


Fig. 7-20—Screen regulator circuit designed by W9OKA. Resistances are in ohms (K = 1000).

R₁--6000 ohms for 211; 2300 ohms for 812A, 20 watts.

R₂-25,000 ohms, 10 watts.

 R_3 —Output voltage control, 0.1-megohm, 2-watt potentiometer.

T₁-Filament transformer: 10 volts, 3.25 amp. for 211; 6.3 volts, 4 amp. for 812A.

T₂—Filament transformer: 6.3 volts, 1 amp.

In the circuit of Fig. 7-19, gas-filled regulator tubes are used to establish a fixed reference voltage to which is added an electronically regulated variable voltage. The design can be modified to give any voltage from 225 volts to 1200 volts, with each design-center voltage variable by plus or minus 60 volts.

The output voltage will depend upon the number and voltage ratings of the VR tubes in the string between the 991 and ground. The total VR-tube voltage rating needed can be determined by subtracting 250 volts from the desired output voltage. As examples, if the desired output voltage is 350, the total VR-tube voltage rating should be 350 - 250 = 100 volts. In this case, a VR-105 would be used. For an output voltage of 1000, the VR-tube voltage rating should be 1000 - 250 = 750 volts. In this case, five VR-150s would be used in series.

The maximum voltage output that can be obtained is approximately equal to 0.7 times the r.m.s. voltage of the transformer T_1 . The current rating of the transformer must be somewhat

above the load current to take care of the voltage dividers and bleeder resistances.

A single 6L6 will handle 90 ma. For larger currents, 6L6s may be added in parallel.

The heater circuit supplying the 6L6 and 6SJ7 should not be grounded. The shaft of R_1 should be grounded. When the output voltage is above 300 or 400, the potentiometer should be provided with an insulating mounting, and should be controlled from the panel by an extension shaft with an insulated coupling and grounded control.

In some cases where the plate transformer has

Fig. 7-21—This regulator circuit used by W1SUN operates from the plate supply and requires no VR string.

A small supply provides screen voltage and reference bias for the control tube.

Unless otherwise marked, resistances are in ohms.

(K = 1000). Capacitors are electrolytic.

R₁-50,000-ohm, 50-watt adjustable resistor.


R₂-0.1-megohm 2-watt potentiometer.

R₃-4.7 megohms, 2 watts.

R₄-0.1 megohm, ½ watt.

T₁—Power transformer: 470 volts center tapped, 40 ma.; 5 volts, 2 amps.; 6.3 volts, 2 amps.

T₃—Filament transformer: 7.5 volts, 3.25 amp. (for V-70D).

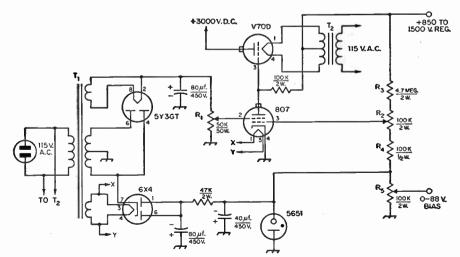

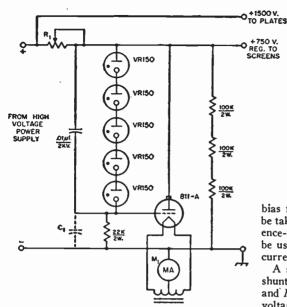


Fig. 7-22—Shunt screen regulator used by W2AZW. Resistances are in ohms (K = 1000).

C1-0.01 \(\psi_1 \), 400 yolts if needed to suppress

C₁-0.01 µf., 400 volts if needed to suppress oscillation.

M1-See text.

R₁---Adjustable wire-wound resistor, resistance and wattage as required.

sufficient current-handling capacity, it may be desirable to operate a screen regulator from the plate supply, rather than from a separate supply. This can be done if a regulator tube is used that can take the required voltage drop. In Fig. 7-20, a type 211 or 812A is used, the control tube being a 6AQ5. With an input voltage of 1800 to 2000, an output voltage of 500 to 700 can be obtained with a regulation better than 1 per cent over a current range of 0 to 100 ma.

In the circuit of Fig. 7-21, a V-70D (or 8005) is used as the regulator, and the control tube is an 807 which can take the full output voltage, making it unnecessary to raise it above ground with VR tubes. If taps are switched on R_1 , the output voltage can be varied over a wide range. Increasing the screen voltage decreases the output voltage. For each position of the tap on R_1 , decreasing the value of R_2 will lower the minimum output voltage as R_2 is varied, and decreasing the value of R_4 will raise the maximum output voltage. However, if these values are made too small, the 807 will lose control.

At 850 volts output, the variation over a current change of 20 to 80 ma. should be negligible. At 1500 volts output with the same current change, the variation in output voltage should be less than three per cent. Up to 88 volts of grid

bias for a Class A or Class AB₁ amplifier may be taken from the potentiometer across the reference-voltage source. This bias cannot, of course, be used for biasing a stage that is drawing grid current.

A somewhat different type of regulator is the shunt regulator shown in Fig. 7-22. The VR tubes and R_a in series are across the output. Since the voltage drop across the VR tubes is constant, any change in output voltage appears across R_a . This causes a change in grid bias on the 811-A grid, causing it to draw more or less current in inverse proportion to the current being drawn by the amplifier screen. This provides a constant load for the series resistor R_a .

The output voltage is equal to the sum of the VR drops plus the grid-to-ground voltage of the 811-A. This varies from 5 to 20 volts between full load and no load. The initial adjustment is made by placing a milliammeter in the filament center-tap lead, as shown, and adjusting R_1 for a reading of 15 to 20 ma, higher than the mormal peak screen current. This adjustment should be made with the amplifier connected but with no excitation, so that the amplifier draws idling current. After the adjustment is complete, the meter may be removed from the circuit and the filament center tap connected directly to ground. Adjustment of the tap on R_1 should, of course, be made with the high voltage turned off.

Any number of VR tubes may be used to provide a regulated voltage near the desired value. The maximum current through the 811-A should be limited to the maximum plate-current rating of the tube. If larger currents are necessary, two 811-As may be connected in parallel. Over a current range of 5 to 60 ma., the regulator holds the output voltage constant within 10 or 15 volts.

BIAS SUPPLIES

As discussed in Chapter 6 on high-frequency transmitters, the chief function of a bias supply for the r.f. stages of a transmitter is that of providing protective bias, although under certain circumstances, a bias supply, or pack, as it is sometimes called, can provide the operating bias if desired.

Simple Bias Packs

Fig. 7-23A shows the diagram of a simple bias supply. R_1 should be the recommended grid leak for the amplifier tube. No grid leak should be used in the transmitter with this type of supply. The output voltage of the supply, when amplifier

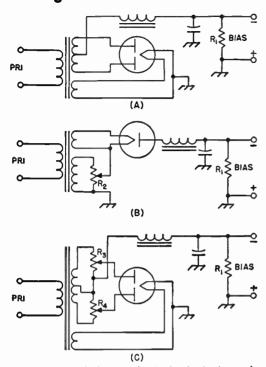


Fig. 7-23—Simple bias-supply circuits. In A, the peak transformer voltage must not exceed the operating value of bias. The circuits of B (half-wave) and C (full-wave) may be used to reduce transformer voltage to the rectifier. R₁ is the recommended grid-leak resistance.

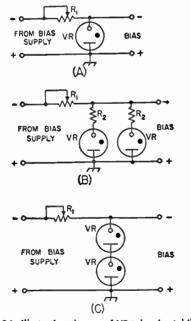


Fig. 7-24—Illustrating the use of VR tubes in stabilizing protective-bias supplies. R_1 is a resistor whose value is adjusted to limit the current through each VR tube to 5 ma. before amplifier excitation is applied. R and R_8 are current-equalizing resistors of 50 to 1000 ohms.


grid current is not flowing, should be some value between the bias required for plate-current cutoff and the recommended operating bias for the amplifier tube. The transformer peak voltage (1.4 times the r.m.s. value) should not exceed the recommended operating-bias value, otherwise the output voltage of the pack will soar above the operating-bias value with rated grid current.

This soaring can be reduced to a considerable extent by the use of a voltage divider across the transformer secondary, as shown at B. Such a system can be used when the transformer voltage is higher than the operating-bias value. The tap on R_2 should be adjusted to give amplifier cut-off bias at the output terminals. The lower the total value of R_2 , the less the soaring will be when grid current flows.

A full-wave circuit is shown in Fig. 7-23C. R_8 and R_4 should have the same total resistance and the taps should be adjusted symmetrically. In all cases, the transformer must be designed to furnish the current drawn by these resistors plus the current drawn by R_1 .

Regulated Bias Supplies

The inconvenience of the circuits shown in Fig. 7-23 and the difficulty of predicting values in practical application can be avoided in most cases by the use of gaseous voltage-regulator tubes across the output of the bias supply, as shown in Fig. 7-24A. A VR tube with a voltage

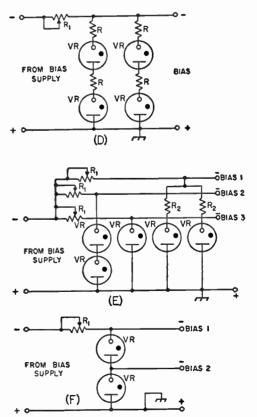

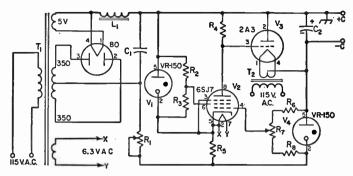


Fig. 7-25—Circuit diagram of an electronically-regulated bias supply.

 C_1 —20- μ f. 450-volt electrolytic. C_2 —20- μ f. 150-volt electrolytic. R_1 —5000 ohms, 25 watts. R_2 —22,000 ohms, $\frac{1}{2}$ watt. R_3 —68,000 ohms, $\frac{1}{2}$ watt. R_4 —0.27 megohm, $\frac{1}{2}$ watt. R_6 —3000 ohms, 5 watts. R_9 —0.12 megohm, $\frac{1}{2}$ watt.

R₀-27,000 ohms, ½ watt.
L₁-20-hy. 50-ma. filter choke.
T₁-Power transformer: 350 volts r.m.s.
each side of center 50 ma.; 5 volts,
2 amp.; 6.3 volts, 3 amp.
T₂-2.5-volt filament transformer
(Thordarson 21F00).

R₇-0.1-megohm potentiometer.

rating anywhere between the biasing-voltage value which will reduce the input to the amplifier to a safe level when excitation is removed, and the operating value of bias, should be chosen. R_1 is adjusted, without amplifier excitation, until the VR tube ignites and draws about 5 ma. Additional voltage to bring the bias up to the operating value when excitation is applied can be obtained from a grid leak resistor, as discussed in the transmitter chapter.

Each VR tube will handle 40 ma. of grid current. If the grid current exceeds this value under any condition, similar VR tubes should be added in parallel, as shown in Fig. 7-24B, for each 40 ma., or less, of additional grid current. The resistors R_2 are for the purpose of helping to maintain equal currents through each VR tube, and should have a value of 50 to 1000 ohms or more.


If the voltage rating of a single VR tube is not sufficiently high for the purpose, other VR tubes may be used in series (or series-parallel if required to satisfy grid-current requirements) as shown in the diagrams of Fig. 7-24C and D.

If a single value of fixed bias will serve for more than one stage, the biasing terminal of each such stage may be connected to a single supply of this type, provided only that the total grid current of all stages so connected does not exceed the current rating of the VR tube or tubes. Alternatively, other separate VR-tube branches may be added in any desired combination to the same supply, as in Fig. 7-24E, to adapt them to the needs of each stage.

Providing the VR-tube current rating is not exceeded, a series arrangement may be tapped for lower voltage, as shown at F.

The circuit diagram of an electronically regulated bias-supply is shown in Fig. 7-25. The output voltage may be adjusted to any value between 40 volts and 80 volts and the unit will handle grid currents up to 35 ma. over the range of 50 to 80 volts, and 25 ma. over the remainder

of the range. If higher current-handling capacity is required, more 2A3s can be connected in parallel with V_s . The regulation will hold to about 0.01 volt per milliampere of grid current. The regulator operates as follows: Since the voltage drop across V_s and V_s is in parallel with the voltage drop across V_s will appear across R_s because the voltage drops across both VR tubes remain constant. R_s is a cathode biasing resistor for V_s , so any voltage change across it appears as a grid-voltage change on V_s . This change in grid voltage is amplified by V_s and appears across R_s which is connected to the plate of V_s and the grids of V_s . This change in voltage swings the grids of V_s . This change in voltage swings the grids of V_s .

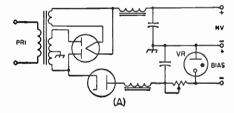

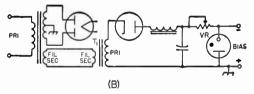


Fig. 7-26—Convenient means of obtaining biasing voltage. A—From a low-voltage plate supply. B—From spare filament winding. I₁ is a filament transformer, of a voltage output similar to that of the spare filament winding, connected in reverse to give 115 volts r.m.s. output. If cold-cathode or selenium rectifiers are used, no additional filament supply is required.

Voltage Multiplying

more positive or negative, and thus varies the internal resistance fo Vs, maintaining the voltage drop across V_s practically constant.

Other Sources of Biasing Voltage

In some cases, it may be convenient to obtain the biasing voltage from a source other than a separate supply. A half-wave rectifier may be connected with reversed polarization to obtain biasing voltage from a low-voltage plate supply, as shown in Fig. 7-26A. In another arrangement, shown at B, a spare filament winding can be used to operate a filament transformer of similar voltage rating in reverse to obtain a voltage of about 130 from the winding that is customarily the primary. This will be sufficient to operate a VR75 or VR90 regulator tube.

A bias supply of any of the types discussed requires relatively little filtering, if the outputterminal peak voltage does not approach the operating-bias value, because the effect of the supply is entirely or largely "washed out" when grid current flows.

VOLTAGE-MULTIPLYING CIRCUITS

Although vacuum-tube rectifiers can be used in voltage-multiplying circuits, the more common application is with selenium, silicon and germanium diodes. The choice of diodes is based on the voltage and current requirements; selenium is

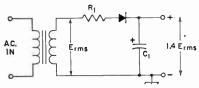


Fig. 7-27—If the current demand is low, a simple halfwave rectifier will deliver a slight voltage increase. Typical values, for Erms = 117 and a load current of 75 ma.:

C1-50-µf., 150-v. electrolytic.

Eoutput-130 volts.

R1-22 ohms.

normally used up to a source voltage of 130, and above that it becomes necessary to use silicon.

A simple half-wave rectifier circuit is shown in Fig. 7-27. Strictly speaking this is not a voltage-multiplying circuit. However, if the current demand is low (a milliampere or so), the d.c. output voltage will be close to the peak voltage of the source, or $1.4E_{\rm rms}$. A typical application of the circuit would be to obtain a low bias voltage from a heater winding; the + side of the output can be grounded by reversing the polarity of the rectifier and capacitor. As with all halfwave rectifiers, the output voltage drops quickly with increased current demand.

The resistor R_1 in Fig. 7-27 is included to limit the current through the rectifier, in accordance with the manufacturer's rating for the diode. If the resistance of the transformer winding is sufficient, R_1 can be omitted.

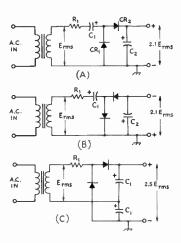



Fig. 7-28—Voltage-doubling circuits. Typical values, for $E_{\rm rms} = 117$ and a load current of 75 ma.: C₁-50-µf. 150-v. electrolytic.


C2-50-µf. 250-v. electrolytic.

Eoutput-245 volts.

R₁-22 ohms.

Voltage-doubling circuits are shown in Fig. 7-28. If the current demand is extremely low, the output voltage will be higher than indicated,

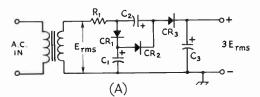

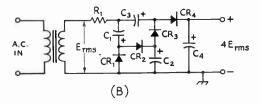

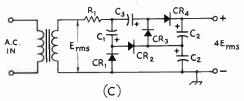


Fig. 7-29—(A) Voltage-tripling and (B, C) voltagequadrupling circuits. Typical values, for $E_{rms} = 117$ and a load current of 75 ma.:

C₁-50-µf. 150-v. electrolytic.

C2-50-µf. 250-v. electrolytic.

C_s, C₄-50-µf. 450-v. electrolytic.

R₁-22 ohms.

but with any reasonable current drain the output voltage will be slightly over twice the a.c. input. In Fig. 7-28A, C_1 charges through CR_1 during one half of the a.c. cycle; CR_2 is nonconductive at this time. During the other half of the cycle CR_2 conducts and C_2 becomes charged; they see as the source the transformer plus the charge in C_1 . By reversing the polarities of the capacitors and diodes, as shown in Fig. 7-28B, the + side of the output can be grounded.

The circuit in Fig. 7-28C is a full-wave voltage-doubling circuit that has several advantages over most other circuits. For a given output voltage, compared to the usual full-wave rectifier circuit (Fig. 7-2B) the full-wave doubler rectifiers require only half the p.i.v. rating. Again for a given output voltage, compared to a full-wave bridge circuit (Fig. 7-2C) only half as many rectifiers (of the same p.i.v. rating) are required.

A voltage-tripling circuit is shown in Fig. 7-29A. On one half of the a.c. cycle CR_1 conducts and C_1 is charged to the source voltage. On the opposite half of the cycle CR_2 conducts and C_3 is charged to twice the source voltage, because it sees the transformer plus the charge in C_1 as the source. At the same time CR_3 conducts and, with the transformer and the charge in C_2 as the

source, C_0 is charged to three times the transformer voltage. The + side of the output can be grounded if the polarities of all of the capacitors and diodes are reversed.

A voltage-quadrupling circuit is shown in Fig. 7-29B. On the negative half of the a.c. cycle, when E_{rms} is negative with respect to ground, C1 charges through CR1. On the positive half of the cycle, C2 charges through CR2 to twice Erma, seeing E_{rms} and C_1 as the source. On the negative half of the cycle, C₈ charges through CR₈ to $3E_{rms}$, seeing E_{rms} and C_2 as the source. On the positive half of the cycle the output capacitance, C_4 , charges to $4E_{rm}$, through CR_4 , seeing E_{rm} , and C_3 as the source. The variation in Fig. 7-29C is similar, except that the output capacitor is made up of the two C_2 in series. The lower C_3 serves the function of C2 in Fig. 7-29B. The polarity of the output can be reversed, to permit grounding of the + terminal, by reversing the polarities of all diodes and capacitors.

The values of capacitance given for the voltage-multiplying circuits are what might be required for $E_{rms} = 115$ and a load of 75 ma.

Larger values will improve the voltage regulation, and smaller values may be used at a sacrifice in regulation.

POWER-LINE CONSIDERATIONS

POWER LINE CONNECTIONS

If the transmitter is rated at much more than 100 watts, special consideration should be given to the a.c. line running into the station. In some residential systems, three wires are brought in from the outside to the distribution board, while in other systems there are only two wires. In the three-wire system, the third wire is the neutral which is grounded. The voltage between the other two wires normally is 230, while half of this voltage (115) appears between each of these wires and neutral, as indicated in Fig. 7-30A. In systems of this type, usually it will be found that the 115-volt household load is divided as evenly as possible between the two sides of the circuit. half of the load being connected between one wire and the neutral, while the other half of the load is connected between the other wire and

neutral. Heavy appliances, such as electric stoves and heaters, normally are designed for 230-volt operation and therefore are connected across the two ungrounded wires. While both ungrounded wires should be fused, a fuse should never be used in the wire to the neutral, nor should a switch be used in this side of the line. The reason for this is that opening the neutral wire does not disconnect the equipment. It simply leaves the equipment on one side of the 230-volt circuit in series with whatever load may be across the other side of the circuit, as shown in Fig. 7-30B. Furthermore, with the neutral open, the voltage will then be divided between the two sides in inverse proportion to the load resistance, the voltage on one side dropping below normal, while it soars on the other side, unless the loads happen to be equal.

The usual line running to baseboard outlets

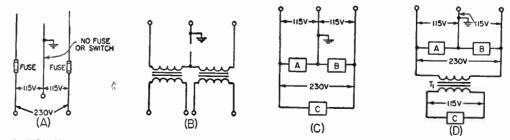


Fig. 7-30—Three-wire power-line circuits. A—Normol 3-wire-line terminotion. No fuse should be used in the gounded (neutrol) line. B—Showing that a switch in the neutral does not remove voltage from either side of the line. C—Connections for both 115- and 230-volt transformers. D—Operating a 115-volt plate transformer from the 230-volt line to avoid light blinking. I₁ is a 2-to-1 step-down transformer.

Power-Line Considerations

is rated at 15 amperes. Considering the power consumed by filaments, lamps, modulator, receiver and other auxiliary equipment, it is not unusual to find this 15-ampere rating exceeded by the requirements of a station of only moderate power. It must also be kept in mind that the same branch may be in use for other household purposes through another outlet. For this reason, and to minimize light blinking when keying or modulating the transmitter, a separate heavier line should be run from the distribution board to the station whenever possible. (A three-volt drop in line voltage will cause noticeable light blinking.)

If the system is of the three-wire type, the three wires should be brought into the station so that the load can be distributed to keep the line balanced. The voltage across a fixed load on one side of the circuit will increase as the load current on the other side is increased. The rate of increase will depend upon the resistance introduced by the neutral wire. If the resistance of the neutral is low, the increase will be correspondingly small. When the currents in the two circuits are balanced, no current flows in the neutral wire and the system is operating at maximum efficiency.

Light blinking can be minimized by using transformers with 230-volt primaries in the power supplies for the keyed or intermittent part of the load, connecting them across the two ungrounded wires with no connection to the neutral, as shown in Fig. 7-30C. The same can be accomplished by the insertion of a step-down transformer whose primary operates at 230 volts and whose secondary delivers 115 volts. Conventional 115-volt transformers may be operated from the secondary of the step-down transformer (see Fig. 7-30D).

When a special heavy-duty line is to be installed, the local power company should be consulted as to local requirements. In some localities it is necessary to have such a job done by a licensed electrician, and there may be special requirements to be met in regard to fittings and the manner of installation. Some amateurs terminate the special line to the station at a switch box, while others may use electric-stove receptacles as the termination. The power is then distributed around the station by means of conventional outets at convenient points. All circuits should be properly fused.

Fusing

All transformer primary circuits should be properly fused. To determine the approximate current rating of the fuse to be used, multiply each current being drawn from the supply in amperes by the voltage at which the current is being drawn. Include the current taken by bleeder resistances and voltage dividers. In the case of series resistors, use the source voltage, not the voltage at the equipment end of the resistor. Include filament power if the transformer is supplying filaments. After multiplying the various voltages and currents, add the individual products. Then divide by the line voltage and

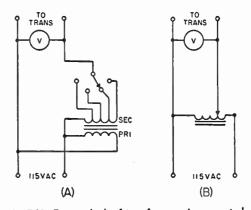


Fig. 7-31—Two methods of transformer primary control. At A is a tapped toy transformer which may be connected so as to boost or buck the line voltage as required. At B is indicated a variable transformer or autotransformer (Variac) which feeds the transformer primaries.

add 10 or 20 per cent. Use a fuse with the nearest larger current rating.

LINE-VOLTAGE ADJUSTMENT

In certain communities trouble is sometimes experienced from fluctuations in line voltage. Usually these fluctuations are caused by a variation in the load on the line and, since most of the variation comes at certain fixed times of the day or night, such as the times when lights are turned on at evening, they may be taken care of by the use of a manually operated compensating device. A simple arrangement is shown in Fig. 7-31A. A toy transformer is used to boost or buck the line voltage as required. The transformer should have a tapped secondary varying between 6 and 20 volts in steps of 2 or 3 volts and its secondary should be capable of carrying the full load current of the entire transmitter, or that portion of it fed by the toy transformer.

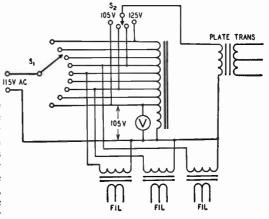


Fig. 7-32—With this circuit, a single adjustment of the tap switch S_1 places the correct primary voltage on all transformers in the transmitter.

The secondary is connected in series with the line voltage and, if the phasing of the windings is correct, the voltage applied to the primaries of the transmitter transformers can be brought up to the rated 115 volts by setting the toy-transformer tap switch on the right tap. If the phasing of the two windings of the toy transformer happens to be reversed, the voltage will be reduced instead of increased. This connection may be used in cases where the line voltage may be above 115 volts. This method is preferable to using a resistor in the primary of a power transformer since it does not affect the voltage regulation as seriously. The circuit of 7-31B illustrates the use of a variable autotransformer (Variac) for adjusting line voltage.

Another scheme by which the primary voltage of each transformer in the transmitter may be adjusted to give a desired secondary voltage, with a master control for compensating for changes in line voltage, is shown in the autotransformer circuit of Fig. 7-32.

This arrangement has the following features: 1) Adjustment of the switch S_1 to make the voltmeter read 105 volts automatically adjusts all transformer primaries to the predetermined correct voltage.

2) The necessity for having all primaries work at the same voltage is eliminated. Thus, 110 volts can be applied to the primary of one transformer, 115 to another, etc., as required to obtain the desired output voltage.

3) Independent control of the plate transformer is afforded by the tap switch S₂. This permits power-input control and does not require an extra autotransformer.

Constant-Voltage Transformers

Although comparatively expensive, special transformers called constant-voltage transformers are available for use in cases where it is necessary to hold line voltage and/or filament voltage constant with fluctuating supply-line voltage. They are rated over a range of 17 v.a. at 6.3 volts output, for small tube-heater demands, up to several thousand volt-amperes at 115 or 230 volts. In average figures, such transformers will hold their output voltages within one per cent under an input-voltage variation of 30 per cent.

CONSTRUCTION OF POWER SUPPLIES

The length of most leads in a power supply is unimportant, so that the arrangement of components from this consideration is not a factor in construction. More important are the points of good high-voltage insulation, adequate conductor size for filament wiring, proper ventilation for rectifier tubes and — most important of all — safety to the operator. Exposed highvoltage terminals or wiring which might be bumped into accidentally should not be permitted to exist. They should be covered with adequate insulation or placed inaccessible to contact during normal operation and adjustment of the transmitter. Power-supply units should be fused individually. All negative terminals of plate supplies and positive terminals of bias sup-

olate supplies and positive terminals of bias sup

Fig. 7-33—A typical low-voltage power supply. The two a.c. connectors permit independent control of filament and high voltage.

plies should be securely grounded to the chassis, and the chassis connected to a waterpipe or radiator ground. All transformer, choke, and capacitor cases should also be grounded to the chassis. A.c. power cords and chassis connectors should be arranged so that exposed contacts are never "live." Starting at the conventional a.c. wall outlet which is female, one end of the cord should be fitted with a male plug. The other end of the cord should have a female receptacle. The input connector of the power supply should have a male receptacle to fit the female receptacle of the cord. The power-output connector on the power supply should be a female socket. A male plug to fit this socket should be connected to the cable going to the equipment. The opposite end of the cable should be fitted with a female connector, and the series should terminate with a male connector on the equipment. If connections are made in this manner, there should be no "live" exposed



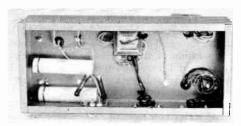


Fig. 7-34. A bottom view of the low-voltage power supply. The separate filament transformer is mounted against the lower wall of the chassis. The electrolytic filter capacitors are mounted on terminal strips. Rubber grommets are used where wires pass through the chassis.

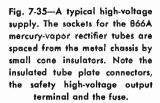

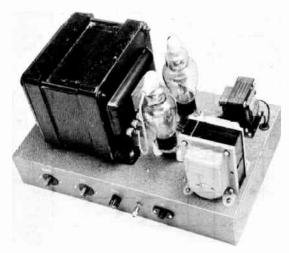

contacts at any point, regardless of where a disconnection may be made.

Rectifier filament leads should be kept short to assure proper voltage at the rectifier socket. Through a metal chassis, grommet-lined clearance holes will serve for voltages up to 500 or 750, but ceramic feed-through insulators should be used for higher voltages. Bleeder and voltage-dropping resistors should be placed where they are open to air circulation. Placing them in confined space reduces the rating.


It is highly preferable from the standpoint of operating convenience to have separate filament transformers for the rectifier tubes, rather than to use combination filament and plate transformers, such as those used in receivers. This permits the transmitter plate voltage to be switched on without the necessity for waiting for rectifier filaments to come up to temperature after each time the high voltage has been turned off. When using a combination power transformer, high voltage may be turned off

without turning the filaments off by using a switch between the transformer center tap and chassis. The switch should be of the rotary type with good insulation between contacts. The shaft of the switch must be grounded.

SAFETY PRECAUTIONS

All power supplies in an installation should be fed through a single main power-line switch so that all power may be cut off quickly, either before working on the equipment, or in case of an accident. Spring-operated switches or relays are not sufficiently reliable for this important service. Foolproof devices for cutting off all power to the transmitter and other equipment are shown in Fig. 7-37. The arrangements shown in Fig. 7-37A and B are similar circuits for two-wire (115-volt) and three-wire (230-volt) systems. S is an enclosed double-throw knife switch of the sort usually used as the entrance switch in house installations. J is a standard a.c. outlet and P a shorted plug to fit the outlet. The switch

Fig. 7-36-Bottom view of the highvoltage supply. The electrolytic capacitors (connected in series) are mounted on an insulating board. Voltageequalizing resistors are connected across each capacitor. Separate input connectors are provided for filament and plate power.

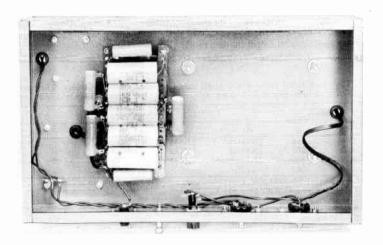

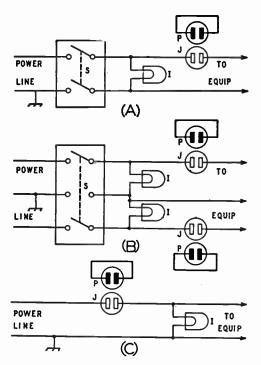


Fig. 7-37—Reliable arrangements for cutting off all power to the transmitter. S is an enclosed double-pole knife-type switch, J a standard a.c. outlet. P a shorted plug to fit the outlet and I a red lamp.

A is for a two-wire 115-volt line, B for a three-wire 230-volt system, and C a simplified arrangement for low-power stations.

should be located prominently in plain sight and members of the household should be instructed in its location and use. I is a red lamp located alongside the switch. Its purpose is not so much to serve as a warning that the power is on as it is to help in identifying and quickly locating the switch should it become necessary for someone else to cut the power off in an emergency.

The outlet J should be placed in some corner out of sight where it will not be a temptation for children or others to play with. The shorting plug can be removed to open the power circuit if there are others around who might inadvertently throw

Selenium-Rectifier Table

All types listed below are rated as follows: Max. input r.m.s. volts — 130, Max. peak inverse volts — 380. Series resistors of 47 ohms are recommended for units rated at less than 65 ma., 22 ohms for 75-and 100-ma. units, 15 ohms for 150-ma. units, and 5 ohms for all higher-current units.

D.C. Ma.	Manufacturer								
Output	Α	В	С	D	E	F			
20	1159		8S20						
30				8Y1					
35			8S35	l	 .	i			
50		RS65Q			50				
65	1002A	RS65	6S65	8J1	65	NA-			
75	1003A	RS75	6S75	5M4	75	NB-5			
100	1004A	RS100	6S100	5M1	100	NC-5			
150	1005A	RS150	6S150	5P1	150	ND.			
200	1006A	RS200	6S200	5R1	200	NE-S			
250	1028A	RS250	6S250	5Q1	250	NF-5			
300	1090A	RS300	6S300	6Q4	300				
350	1023	RS350	6S350	5QS1		NK-			
400	1130	RS400	65400	552	400	NH.			
450		RS450	6S450			NJ-5			
500	1179	RS500	6S500	5S1	500				
600					600				
1000		RS1000							

A — Federal. B — International. C — Mallory D — Radio Receptor. E — Sarkes-Tarzian. F — Sylvania.

the switch while the operator is working on the rig. If the operator takes the plug with him, it will prevent someone from turning on the power in his absence and either injuring themselves or the equipment or perhaps starting a fire. Of utmost importance is the fact that the outlet *I must* be placed in the *ungrounded* side of the line.

Those who are operating low power and feel that the expense or complication of the switch isn't warranted can use the shorted-plug idea as the main power switch. In this case, the outlet should be located prominently and identified by a signal light, as shown in Fig. 7-37C.

The test bench ought to be fed through the main power switch, or a similar arrangement at the bench, if the bench is located remote from the transmitter.

A bleeder resistor with a power rating giving a considerable margin of safety should be used across the output of all transmitter power supplies so that the filter capacitors will be discharged when the high-voltage transformer is turned off.

Silicon Rectifier Table

The types listed below are a small sampling of available rectifiers. They are rated at 750 ma. to a resistive or inductive load, 550 ma. to a capacitive load. VRMs is halved with capacitive-input filter.

P.I.V.	Vrws-		Mar	ufacturer		_
	V BES-	A	В	С	D	E
200	140	1N441B	1N538	1N3193	1N2485/20H	1N 2069
400	280	1N443B	1N540	1N3194	1N2487/40H	1 N 2070
600	420	1N547	1N547	1N3195	1N2489/60H	1N2071
8 0 0	560			1N3196	******	

A - General Electric, 50° C.

B — International Rectifier, 50° C.

C — RCA, 75° C.

D - Sarkes-Tarzian, 100° C.

E — Sylvania.

Keying and Break-In

Section 12.133 of the FCC regulations says "...The frequency of the emitted...wave shall be as constant as the state of the art permits." It also says "... spurious radiation shall not be of sufficient intensity to cause interference in receiving equipment of good engineering design including adequate selectivity characteristics, which is tuned to a frequency or frequencies outside the frequency band of emission normally required for the type of emission being employed by the amateur station."

There are four factors that have to be considered in the keying of a transmitter. They are envelope shape, r.f. clicks, chirp and backwave.

Envelope Shape

The key clicks that go out on the air with the signal are controlled by the shape of the envelope of the signal. The envelope is the outline of the oscilloscope pattern of your transmitter output, but an oscilloscope isn't needed to observe the effects. Fig. 8-1 shows representative scope pat-

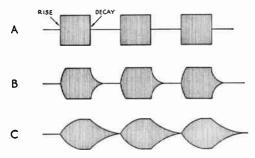


Fig. 8-1—Typical oscilloscope displays of a code transmitter. The rectangular-shaped dots or dashes (A) have serious key clicks extending many kc. either side of the transmitter frequency. Using proper shaping circuits increases the rise and decay times to give signals with the envelope form of B. This signal would have practically no key clicks. Carrying the shaping process too far, as in C, results in a signal that is too "soft" and is not easy to copy.


Oscilloscope displays of this type are obtained by coupling the transmitter r.f. to the vertical plates (Chapter 21) and using a slow sweep speed synchronized to the dot or dash speed of an automatic key.

terns that might be obtained with a given transmitter under various conditions.

It must be emphasized that the on-the-air clicks are determined by the shaping, while the r.f. clicks caused by the spark at the key can only be heard in the station receiver and possibly a broadcast receiver in the same house or apartment.

R.F. Clicks

When any circuit carrying d.c. or a.c. is closed or broken, the small or large spark (depending upon the voltage and current) generates r.f. during the instant of make or break. This r.f. covers a frequency range of many megacycles. When a transmitter is keyed, the spark at the key (and relay, if used) causes a click in the receiver. This click has no effect on the transmitted signal. Since it occurs at the same time that a click (if any) appears on the transmitter output, it must be removed if one is to listen critically to his own signal within the shack. A small r.f. filter is required at the contacts of the key (and relay); typical circuits and values are shown in Fig. 8-2.

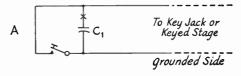



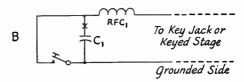


Fig. 8-2—Typical filter circuits to apply at the key (and relay, if used) to minimize r.f. clicks. The simplest circuit (A) is a small capacitor mounted at the key. If this proves insufficient, an r.f. choke can be added to the ungrounded lead (B). The value of C_1 is .001 to .01 μf_{**} , RFC1 can be 0.5 to 2.5 mh., with a current-carrying ability sufficient for the current in the keyed circuit. In difficult cases another small capacitor may be required on the other side of the r.f. choke. In all cases the r.f. filter should be mounted right at the key or relay terminals; sometimes the filter can be concealed under the key. When cathode or center-tap keying is used, the resistance of the r.f. choke or chokes will add cathode bias to the keyed stage, and in this case at highcurrent low-resistance choke may be required, or compensating reduction of the grid-leak bias (if it is used) may be needed. Shielded wire or coaxial cable makes a good keying lead.

A visible spark on "make" can often be reduced by the addition of a small (10 to 100 ohms) resistor in series with C₁ (inserted at point"x"). Too high a value of resistor reduces the arc-suppressing effect on "break."

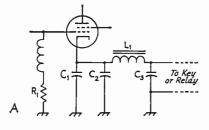To check the effectiveness of the r.f. filter, listen on a lower-frequency band than the transmitter is tuned to, with a short antenna and the receiver gain backed off.



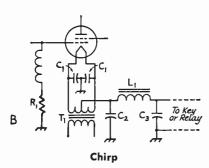

The frequency-stability reference in the opening paragraph refers to the "chirp" observed on many signals. This is caused by a change in frequency of the signal during a single dot or dash.

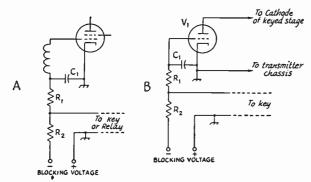


Fig. 8-4—The basic circuit for blocked-grid keying is shown at A. R_1 is the normal grid leak, and the blocking voltage must be at least several times the normal grid bias. The click on make can be reduced by making C_1 larger, and the click on break can be reduced by making R_2 larger. Usually the value of R_2 will be 5 to 20 times the resistance of R_3 . The power supply current requirement depends upon the value of R_2 , since closing the key circuit places R_2 across the blocking voltage supply.

An allied circuit is the vacuum-tube keyer of B. The tube V_1 is connected in the cathode circuit of the stage to be keyed. The values of C_1 , R_1 and R_2 determine the keying envelope in the same way that they do for blocked-grid keying. Values to start with might be 0.47 megohm for R_1 , 4.7 megohm for R_2 and 0.0047 μ f. for C_1 .

The blocking voltage supply must deliver several hundred volts, but the current drain is very low. The 2A3 or other low plateresistance triode is suitable for V_1 . To increase the current-carrying ability of a tube keyer, several tubes can be connected in parallel.

A vacuum-tube keyer adds cathode bias and drops the supply voltages to the keyed stage and will reduce the output of the stage. In oscillator keying it may be impossible to use a v.t. keyer without changing the oscillator d.c. grid return from ground to cathode.

Fig. 8-3—The basic cathode (A) and center-tap (B) keying circuits. In either case C_1 is the r.f. return to ground, shunted by a larger capacitor, C_2 , for shaping. Voltage ratings at least equal to the cut-off voltage of the tube are required. I_1 is the normal filament transformer. C_1 and C_3 can be about 0.01 μ f.

The shaping of the signal is controlled by the values of L_1 and C_2 . Increased capacitance at C_2 will make the signal softer on break; increased inductance at L_1 will make the signal softer on make. In many cases the make will be satisfactory without any inductance.

Values at C_2 will range from 0.5 to 4 μf ., depending upon the tube type and operating conditions. The value of L_1 will also vary with tube type and conditions, and may range from a fraction of a henry to several henrys. When tetrodes or pentodes are keyed in this manner, a smaller value can sometimes be used at C_2 if the screen-voltage supply is fixed and not obtained from the plate supply through a dropping resistor.

Oscillators keyed in the cathode circuit cannot be softened on break indefinitely by increasing the value of C_2 because the grid-circuit time constant enters into the action.

Chirp is an easy thing to detect if you know how to listen for it, although it is amazing how some operators will listen to a signal and say it has no chirp when it actually has. The easiest way to detect chirp is to tune in the code signal at

a low beat note and listen for any change in frequency during a dash. The lower the beat note, the easier it is to detect the frequency change. Listening to a harmonic of the signal will accentuate the frequency change.

The main reason for minimizing chirp, aside from complying with the letter of the regulations, is one of pride, since a properly shaped chirp-free signal is a pleasure to copy and is likely to attract attention by its rarity. Chirps cannot be observed on an oscilloscope pattern of the envelope.

Backwave

The last factor is "backwave," a signal during key-up conditions from some amplifier-keyed transmitters. Some operators listening in the shack to their own signals and hearing a backwave think that the backwave can be heard on the air. It isn't necessarily so, and the best way to check is with an amateur a mile or more away. If he can't hear a backwave on the S9 + signal, you can be sure that it isn't there when the signal is weaker. Backwave is undesirable because it makes a signal harder to copy, even with acceptable shaping and no chirp.

Amplifier Keying

Many two-, three- and even fourstage transmitters are utterly incapable of completely chirp-free amplifier keying because keying the output stage has an effect on the oscillator frequency

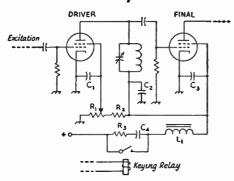


Fig. 8-5—When the driver stage plate voltage is roughly the same as the screen voltage of a tetrode final amplifier, combined screen and driver keying is an excellent system. The envelope shaping is determined by the values of L_1 , C_4 , and R_3 , although the r.f. bypass capacitors C_1 , C_2 and C_3 also have a slight effect. R_1 serves as an excitation control for the final amplifier, by controlling the screen voltage of the driver stage. If a triode driver is used, its plate voltage can be varied for excitation control.

The inductor L_1 will not be too critical, and the secondary of a spare filament transformer can be used if a low-inductance choke is not available. The values of C_4 and R_3 will depend upon the inductance and the voltage and current levels, but good starting values are 0.1 μ f. and 50 ohms.

To minimize the possibility of electrical shock, it is recommended that a keying relay be used in this circuit, since both sides of the circuit are "hot." As in any transmitter, the signal will be chirp-free only if keying the driver stage has no effect on the oscillator frequency.

(The Sigma 41FZ-35-ACS-SIL 6-volt a.c. relay is wellsuited for keying applications.)

and "pulls" through the several stages. This is particularly true when the oscillator stage is on the same frequency as the keyed output stage, but it can also happen when frequency multiplying is involved. Another source of reaction is the variation in oscillator supply voltage under keying conditions, although this can usually be handled by stabilizing the oscillator supply with a VR tube. If the objective is a completely chirp-free transmitter, the first step is to make sure that keying the amplifier stage (or stages) has no effect on the oscillator frequency. This can be checked by listening on the oscillator frequency while the amplifier stage is keyed. Listen for chirp on either side of zero beat to eliminate the possible effect of a chirpy receiver

caused by line-voltage changes or pulling. If no chirp of the steadily running oscillator can be chirp in the stage or stages used for the test. detected, the transmitter can be keyed without This is no assurance that the transmitter can be keyed without chirp in an earlier stage until the same test is passed by the earlier stage.

An amplifier can be keyed by any method that reduces the output to zero. Neutralized stages can be keyed in the cathode circuit, although where powers over 50 or 75 watts are involved it is often desirable to use a keying relay or vacuum tube keyer, to minimize the chances for electrical shock. Tube keying drops the supply voltages and adds cathode bias, points to be considered where maximum output is required. Blocked-grid keying is applicable to many neutralized stages, but it presents problems in high-powered amplifiers and requires a source of negative voltage. Output stages that aren't neutralized such as many of the tetrodes and pentodes in widespread use, will usually leak a little and show some backwave regardless of how they are keyed. In a case like this it may be necessary to key two stages to eliminate backwave. They can be keyed in the cathodes, with blocked-grid keying, or in the screens. When screen keying is used, it is not always sufficient to reduce the screen voltage to zero; it may have to be pulled to some negative value to bring the key-up plate current to zero, unless fixed negative control-grid bias is used. It should be apparent that where two stages are keyed, keying the earlier stage must have no effect on the oscillator frequency if completely chirp-free output is the goal.

Shaping of the keying is obtained in several ways. Blocked-grid and vacuum-tube keyers get suitable shaping with proper choice of resistor and capacitor values, while cathode and screengrid keying can be shaped by using inductors and capacitors. Sample circuits are shown in Figs. 8-3, 8-4 and 8-5, together with instructions for their adjustment. There is no "best" adjustment, since this is a matter of personal preference and what you want your signal to sound like. Most operators seem to like the make to be heavier than the break. All of the circuits shown here are capable of a wide range of adjustment.

If the negative supply in a grid-block keyed stage fails, the tube will draw excessive key-up current. To protect against tube damage in this eventuality, an overload relay can be used or, more simply, a fast-acting fuse can be included in the cathode circuit.

VACUUM-TUBE KEYERS

The practical tube-keyer circuit of Fig. 8-6 can be used for keying any stage of any transmitter. Depending upon the power level of the keyed stage, or more or fewer Type 2A3 tubes can be connected in parallel to handle the necessary current. The voltage drop through a single 2A3 varies from about 70 volts at 50 ma. to 40 volts at 20 ma. Tubes added in parallel will reduce the drop in proportion to the number of tubes used.

When connecting the output terminals of the keyer to the circuit to be keyed, the grounded output terminal of the keyer must be connected to the transmitter ground. Thus the keyer can be used only in negative-lead or cathode keying. When used in cathode keying, it will introduce cathode bias to the stage and reduce the output. This can be compensated for by a reduction in the grid-leak bias of the stage. If an oscillator

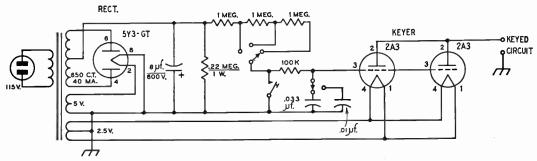


Fig. 8-6—Wiring diagram of a practical vacuum-tube keyer.

stage is keyed, the keyer should be connected in the negative lead, not the cathode.

The negative-voltage supply can be eliminated if a negative voltage is available from some other source, such as a bias supply. A simplified version of this circuit could eliminate the switches and

associated resistors and capacitors, since they are incorporated only to allow the operator to select the combination he prefers. But once the values have been selected, they can be soldered permanently in place. Adjustment of the keying characteristic is the same as with blocked-grid keying.

OSCILLATOR KEYING

One may wonder why oscillator keying hasn't been mentioned earlier, since it is widely used. A sad fact of life is that excellent oscillator keving is infinitely more difficult to obtain than is excellent amplifier keying. If the objective is no detectable chirp, it is probably impossible to obtain with oscillator keying, particularly on the higher frequencies. The reasons are simple. Any keyed-oscillator transmitter requires shaping at the oscillator, which involves changing the operating conditions of the oscillator over a significant period of time. The output of the oscillator doesn't rise to full value immediately so the drive on the following stage is changing, which in turn may reflect a variable load on the oscillator. No oscillator has been devised that has no change in frequency over its entire operating voltage range and with a changing load. Furthermore, the shaping of the keyed-oscillator envelope usually has to be exaggerated, because the following stages will tend to sharpen up the keying and introduce clicks unless they are operated as linear amplifiers.

Acceptable oscillator keying can be obtained on the lower-frequency bands, and the methods used to key amplifiers can be used, but chirpfree clickless oscillator keying is probably not possible at the higher frequencies. Often some additional shaping of the signal will be introduced on "make" through the use of a clamp tube in the output amplifier stage, because the time constant of the screen bypass capacitor plus screen dropping resistor increases the screenvoltage rise time, but it is of no help on the "break" portion of the signal.

Break-In Keying

The usual argument for oscillator keying is that it permits break-in operation, which is true. If break-in operation is not contemplated and as near perfect keying as possible is the objective, then keying an amplifier or two by the methods outlined earlier is the solution. For operating convenience, an automatic transmitter "turner-onner" (see Campbell, QST, Aug., 1956), which will turn on the power supplies and switch antenna relays and receiver muting devices, can be used. The station switches over to the complete "transmit" condition where the first dot is sent, and it holds in for a length of time dependent upon the setting of the delay. It is equivalent to voice-operated phone of the type commonly used by s.s.b. stations. It does not permit hearing the other station whenever the key is up, as does full break-in.

Full break-in with excellent keying is not easy to come by, but it is easier than many amateurs think. Many use oscillator keying and put up with a second-best signal.

Differential Keying

The principle behind "differential" keying is to turn the oscillator on fast before a keyed amplifier stage can pass any signal and turn off the oscillator fast after the keyed amplifier stage has cut off. A number of circuits have been devised for accomplishing the action. One of the simplest can be applied to any grid-block keyed amplifier or tube-keyed stage by the addition of a triode and a VR tube, as in Fig. 8-7. Using this keying system for break-in, the keying will be chirpfree if it is chirp-free with the VR tube removed from its socket, to permit the oscillator to run all of the time. If the transmitter can't pass this test, it indicates that more isolation is required between keyed stage and oscillator.

Another VR-tube differential keying circuit, useful when the screen-grid circuit of an amplifier is keyed, is shown in Fig. 8-8. The normal screen keying circuit is made up of the shaping capacitor C_1 , the keying relay (to remove dangerous voltages from the key), and the resistors R_1 and R_2 .

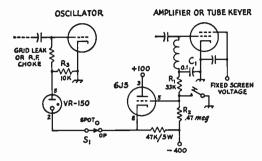


Fig. 8-7—When satisfactory blocked-grid or tube keying of an amplifier stage has been obtained, this VR-tube break-in circuit can be applied to the transmitter to furnish differential keying. The constants shown here are suitable for blocked-grid keying of a 6146 amplifier; with a tube keyer the 6J5 and VR tube circuitry would be the same.

With the key up, sufficient current flows through Rs to give a voltage that will cut off the oscillator tube. When the key is closed, the cathode voltage of the 6J5 becomes close to ground potential, extinguishing the VR tube and permitting the oscillator to operate. Too much shunt capacity on the leads to the VR tube, and too large a value of grid capacitor in the oscillator, may slow down this action, and best performance will be obtained when the oscillator (turned on and off this way) sounds "clicky." The output envelope shaping is obtained in the amplifier, and it can be made softer by increasing the value of C1. If the keyed amplifier is a tetrade or pentade, the screen valtage should be obtained from a fixed voltage source or stiff voltage divider, not from the plate supply through a dropping resistor.

The + supply should be 50 to 100 volts higher than the normal screen voltage, and the - voltage should be sufficient to ignite the VR tube, V_2 , through the drop in R_2 and R_3 . Current through R_3 will be determined by voltage required to cut off oscillator; if 10 volts will do it the current will be 1 ma. For a desirable keying characteristic, R_3 will usually have a higher value than R_3 . Increasing the value of C_3 will soften both "make" and "break."

The tube used at V_2 will depend upon the available negative supply voltage. If it is between 120 and 150, a 0A3/VR75 is recommended. Above this a 0C3/VR105 can be used. The diode, V_1 , can be any diode operated within ratings. A 6AL5 will suffice with screen voltages under 250 and bleeder currents under 5 ma. For maximum life a separate heater transformer should be used for the diode, with the cathode connected to one side of the heater winding.

Clicks in Later Stages

It was mentioned earlier that key clicks can be generated in amplifier stages following the keyed stage or stages. This can be a puzzling problem to an operator who has spent considerable time adjusting the keying in his exciter unit for clickless keying, only to find that the clicks are bad

when the amplifier unit is added. There are two possible causes for the clicks: low-frequency parasitic oscillations and amplifier "clipping."

Under some conditions an amplifier will be momentarily triggered into low-frequency parasitic oscillations, and clicks will be generated when the amplifier is driven by a keyed exciter. If these clicks are the result of low-frequency parasitic oscillations, they will be found in "groups" of clicks occurring at 50- to 150-kc. intervals either side of the transmitter frequency. Of course low-frequency parasitic oscillations can be generated in a keyed stage, and the operator should listen carefully to make sure that the output of the exciter is clean before he blames a later amplifier. Low-frequency parasitic oscillations are usually caused by poor choice in r.f. choke values, and the use of more inductance in the plate choke than in the grid choke for the same stage is recommended.

When the clicks introduced by the addition of an amplifier stage are found only near the transmitter frequency, amplifier "clipping" is indicated. It is quite common when fixed bias is used on the amplifier and the bias is well past the "cut-off" value. The effect can usually be minimized by using a combination of fixed and gridleak bias for the amplifier stage. The fixed bias should be sufficient to hold the key-up plate current only to a low level and not to zero.

A linear amplifier (Class AB₁, AB₂ or B) will amplify the excitation without adding any clicks, and if clicks show up a low-frequency parasitic oscillation is probably the reason.

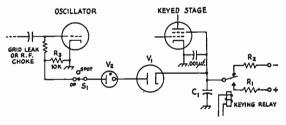


Fig. 8-8—VR-tube differential keying in an amplifier screen circuit.

With key up and current flowing through V1 and V2, the oscillator is cut off by the drop through Rs. The keyed stage draws no current because its screen grid is negative. C1 is charged negatively to the value of the source. When the relay is energized, C1 charges through R_1 to a + value. Before reaching zero (on its way +) there is insufficient voltage to maintain ionization in V2, and the current is broken in R3, turning on the oscillator stage. As the screen voltage goes positive, the VR tube, V2, cannot reignite because the diode, V1, will not conduct in that direction. The oscillator and keyed stage remain on as long as the relay is closed. When the relay opens, the voltage across C1 must be sufficiently negative for V2 to ionize before any bleeder current will pass through Rs. By this time the screen of the keyed stage is so far negative that the tube has stopped conducting. (See Fig. 8-5 for suitable relay.)

TESTING YOUR KEYING

The choice of a keying circuit is not as important as its testing. Any of the circuits shown in this chapter can be made to give satisfactory keying, but must be adjusted properly.

The easiest way to find out what your keyed signal sounds like on the air is to trade stations with a near-by ham friend some evening for a short QSO. If he is a half mile or so away, that's fine, but any distance where the signals are still S9 will be satisfactory.

After you have found out how to work his rig, make contact and then have him send slow dashes, with dash spacing. (The letter "T" at about 5 w.p.m.) With minimum selectivity, cut the r.f. gain back just enough to avoid receiver overloading (the condition where you get crisp signals instead of mushy ones) and tune slowly from out of beat-note range on one side of the signal through to zero and out the other side. Knowing the tempo of the dashes, you can readily identify any clicks in the vicinity as yours or someone else's. A good signal will have a thump on "make" that is perceptible only where you can also hear the beat note, and the click on "break" should be practically negligible at any point. If your signal is like that, it will sound good, provided there are no chirps. Then have him run off a string of fast dots with the bug - if they are easy to copy, your signal has no "tails" worth worrying about and is a good one for any speed up to the limit of manual keying. Make one last check with the selectivity in, to see that the clicks off the signal are negligible even at high signal level.

If you don't have any convenient friends with whom to trade stations, you can still check your keying, although you have to be a little more careful. The first step is to get rid of the r.f. click at the key, as described earlier.

So far you haven't done a thing for your signal on the air and you still don't know what it sounds like, but you may have cleaned up some clicks in the broadcast set. Now disconnect the antenna from your receiver and short the antenna

terminals with a short piece of wire. Tune in your own signal and reduce the r.f. gain to the point where your receiver doesn't overload. Detune any antenna trimmer the receiver may have. If you can't avoid overload within the r.f. gain-control range, pull out the r.f. amplifier tube and try again. If you still can't avoid overload, listen to the second harmonic as a last resort. An overloaded receiver can generate clicks.

Describing the volume level at which you should set your receiver for these "shack" tests is a little difficult. The r.f. filter should be effective with the receiver running wide open and with an antenna connected. When you turn on the transmitter and take the other steps mentioned to reduce the signal in the receiver, run the audio up and the r.f. down to the point where you can just hear a little "rushing" sound with the b.f.o. off and the receiver tuned to the signal. This is with the selectivity in. At this level, a properly adjusted keying circuit will show no clicks off the rushing-sound range. With the b.f.o. on the same gain setting, there should be no clicks outside the beat-note range. When observing clicks, make the slow-dash and fast dot tests outlined previously.

Now you know how your signal sounds on the air, with one possible exception. If keying your transmitter makes the lights blink, you may not be able to tell too accurately about the chirp on your signal. However, if you are satisfied with the absence of chirp when tuning either side of zero beat, it is safe to assume that your receiver isn't chirping with the light flicker and that the observed signal is a true representation. No chirp either side of zero beat is fine. Don't try to make these tests without first getting rid of the r.f. click at the key, because clicks can mask a chirp.

The least satisfactory way to check your keying is to ask another ham on the air how your keying sounds. It is the least satisfactory because most hams are reluctant to be highly critical of another amateur's signal. In a great many cases they don't actually know what to look for or how to describe any aberrations they may observe.

MONITORING OF KEYING

In general, there are two common methods for monitoring one's "fist" and signal. The first, and perhaps less common type, involves the use of an audio oscillator that is keyed simultaneously with the transmitter.

The second method is one that permits receiving the signal through one's receiver, and this generally requires that the receiver be tuned to the transmitter (not always convenient unless working on the same frequency) and that some method be provided for preventing overloading of the receiver, so that a good replica of the transmitted signal will be received. Except where quite low power is used, this usually involves a relay for simultaneously shorting the receiver input terminals and reducing the receiver gain.

BREAK-IN OPERATION

Break-in operation is most easily obtained with a separate receiving antenna, since none of the available antenna change-over relays is fast enough to follow keying. The receiving antenna should be installed as far as possible from the transmitting antenna. It should be mounted at right angles to the transmitting antenna and fed with low pick-up lead-in material such as co-

axial cable or 300-ohm Twin-Lead, to minimize pick-up.

If a low-powered transmitter is used, it is often quite satisfactory to use no special equipment for break-in operation other than the separate receiving antenna, since the transmitter will not block the receiver too seriously. Even if the transmitter keys without clicks, some clicks will be heard when the receiver is tuned to the transmitter frequency because of overload in the receiver. An output limiter, as described in Chapter Five, will wash out these clicks and permit good break-in operation even on your transmitter frequency.

When powers above 25 or 50 watts are used, special treatment is required for quiet break-in on the transmitter frequency. A means should be provided for shorting the input of the receiver when the code characters are sent, and a means for reducing the gain of the receiver at the same time is often necessary. The system shown in Fig. 8-9 permits quiet break-in operation for higher-powered stations. It requires a simple operation on the receiver but otherwise is perfectly straightforward. R_1 is the regular receiver r.f. and i.f. gain control. The ground lead is lifted on this control and run to a rheostat, R_2 , that goes to ground. A wire from the junction runs outside the receiver to the keying relay, K_1 . When the key

is up, the ground side of R_1 is connected to ground through the relay arm, and the receiver is in its normal operating condition. When the key is closed, the relay closes, which breaks the ground connection from R_1 and applies additional bias to the tubes in the receiver. This bias is controlled by R_2 . When the relay closes, it also closes the circuit to the transmitter oscillator. A filter at the key suppresses the clicks caused by the relay current.

The keying relay should be mounted on the receiver as close to the antenna terminals as possible, and the leads shown heavy in the diagram should be kept short, since long leads will allow too much signal to get through into the receiver. Use a good high-speed keying relay.

A few of the recent communications receivers bring the return lead from the r.f. gain control to a normally shorted terminal at the rear of the receiver. The preceding break-in system can be readily applied to a receiver of this type, and it will repay the receiver owner to study the instruction book and determine if his receiver already has this connection made in it. Other receivers have provision for reducing the gain or for blanking the receiver; one popular model has provision for bringing in negative bias from a transmitter grid leak to cut off an audio stage during transmit periods.

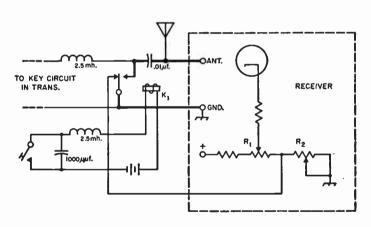


Fig. 8-9—Wiring diagram for smooth break-in operation. The lead shown as a heavy line and the lead from bottom relay contact to ANT post on receiver should be kept as short as possible for minimum pickup of transmitter signal. R₁—Receiver manual gain control.

R₂—5000- or 10,000-ohm wire-wound potentiometer. K₁—S.p.d.t. keying relay. (Sigma 41FZ-35-ACS-SIL or equiv.) Although battery and d.c. relay are shown, any suitable a.c. or d.c. relay and power source can be used.

RECEIVER MUTING AND GRID-BLOCK KEYING

The muting system shown in Fig. 8-10 can be used with any grid-block or tube-keyed transmitter, and it is particularly applicable to the VR-tube differential keying circuit of Fig 8-7. Referring to Fig. 8-10, R_1 , R_2 and C_1 have the same values and functions that the similarly designated components in Figs. 8-4 and 8-7 have. When the key is open, a small current will flow through R_8 , the 0A2 and R_2 , and the voltage drop across R_2 will be sufficient to cut off the 6C4. With the 6C4 cut off, there is no current through R_4 and consequently no voltage appearing across R_4 . The voltage of the receiver a.g.c. bus is zero with respect to ground.

When the key is closed, there is insufficient voltage across the 0A2 to maintain conduction, and consequently there is no current flow through R_3 . With zero voltage between grid and cathode, the 6C4 passes current. The drop across R_4 , and thus the negative voltage applied to the a.g.c. line in the receiver, is determined by the value of R_4 . Thus the key-down gain of the receiver can be adjusted to permit listening to one's own signal, by increasing the value of R_4 until the receiver output level is a comfortable one. To utilize the same antenna for transmitting and receiving, and thus benefit during receiving from any directional properties of the antenna, an electronic transmit-

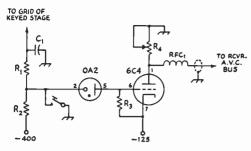


Fig. 8-10—Circuit diagram of a receiver muter for use with grid-block or tube keying.

C₁—Shaping capacitor, see text.

R₁, R₂—Shaping resistors, see text.

R₈-0.1 megohm.

R₄-15,000-ohm 2-watt potentiometer.

RFC₁-1 mh. or less.

receive switch can be used (see later in this chapter).

The receiver a.g.c. bus can be located by reference to the receiver instruction manual, and connection be made to it through a length of shielded wire. The a.g.c. switch in the receiver must be turned to on for the muter to be effective.

If desired, the muting circuit can be built into the transmitter, or it can be mounted on a shelf or small chassis behind the receiver. The two negative voltages can be furnished by one supply and a reasonably heavy voltage divider; the main requirement of the supply is that the nominal -125 volts remain below the normal voltage drop of the 0A2 (150 volts). Installation of the muting circuits should have little or no effect on the keying characteristic of the transmitter; if it does the characteristic can be restored by proper values for R_1 , R_2 and C_1 .

THE "MATCHTONE"

The "Matchtone" is a c.w. tone-generating monitor using a transistor audio oscillator. A diode rectifier in the antenna circuit or the d.c. from a "Monimatch" (see Chap. 13) serves as the keyed source of d.c. power. In addition to the usual function it can be used by the sightless amateur as an audible transmitter-antenna tuning indicator.

While direct monitoring of c.w. transmissions via the receiver is a preferred method because it can reveal much about the keying characteristics, transmissions offset from the receiving frequency call for a separate monitor. The self-powered transistorized monitor fills the bill nicely. The use of the r.f bridge, already connected in the r.f. transmission line, as a source of power for the monitor is a logical choice.

The circuit of the Matchtone and the connections to the Monimatch and the receiver are shown in Fig. 8-11. A small 2- or 3-to-1 push-pull grid-to-plate audio interstage transformer is used for feedback as well as for coupling to the receiver. If a transformer having a p.p. grid winding is not available from the junk box, the audio coupling to the receiver can be obtained by connecting C_2 to the ungrounded end of R_1 . While use of a low value of capacitance for C_2 is necessary to avoid excessive shunting of the high impedance receiver audio circuit, the value shown will provide sufficient coupling for a good audio tone level from the monitor. A third possibility for the audio out-put connection from the monitor is to substitute the headphones for R_1 , together with a singlepole double-throw switch or relay to switch the phones between the monitor and the receiver. The on-off switch, S_1 , can be made a part of R_2 by use of a volume control switch attachment.

The value shown for C_1 gives an audio pitch in the 500-1000 cycle range, depending somewhat on the particular transformer, the setting of R_2 and the transmitter output power. Other values of C_1 can be used to adjust the pitch to the

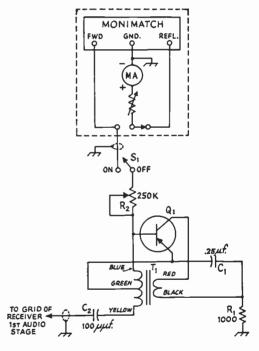


Fig. 8-11—Circuit of the Matchtone. Section enclosed in dashed line is the Monimatch and its indicating circuit; a simple r.f. rectifier will also serve as the d.c. source. Braid of shielded lead to audio grid should connect to receiver chassis.

C₁-Paper.

C₂-Mica or ceramic.

Q1-2N109, CK722 or similar.

R₁-1000 ohms, ½ watt.

R₂-0.25-megohm volume control.

S₁-S.p.s.t. toggle.

T₁—Push-pull interstage audio transformer, 2:1 or 3:1 total grid to plate.

Speed Keys 251

operator's individual preference. R_2 may be adjusted to compensate for the changes in the d.c. current from the rectifier or Monimatch caused by a change in transmitter frequency band or power. Using either a 2N109 or a CK722 transistor, the circuit should oscillate with usable audio level with as little as 0.1 ma. d.c. flowing to ground through the monitor. Other low-cost transistors such as the 2N107 and the 2N170 should work equally well.

Because the pitch of the audio tone is to some degree dependent upon the d.c. voltage obtained from the source, the pitch gives a reasonably accurate indication of correct final amplifier plate circuit tuning (maximum power output) and, if an antenna tuner is used, will also indicate resonance of the tuner to the transmitter output frequency. This characteristic of the Matchtone should be of considerable aid to sightless amateurs. (From QST, January, 1958.)

SPEED KEYS

The average operator finds that a speed of 20 to 25 words per minute is the limit of his ability with a straight hand key. However, he can increase his speed to 30 to 40 w.p.m. by the use of a "speed key." The mechanical speed keys, available in most radio stores, give additional speed by making strings of dots when the key lever is pushed to the right; dashes are made manually by closing the key to the left. After practicing with the speed key, the operator obtains the correct "feel" for the key, which allows him to release the dot lever at exactly the right time to make the required number of dots. A speed key can deliver practically perfect code characters

when used by an operator who knows what good code sounds like; however, one will not compensate for an operator's poor code ability.

An electronic speed key will not compensate for an operator's poor sending ability, either. However, the electronic speed key has the feature that it makes strings of both dots and of dashes, by proper manipulation of the key lever, and in current designs the dashes are self-completing. This means that it is impossible to send anything but the correct length of dash when the key lever is closed on the dash side. It is, of course, possible to send an incorrect number of dashes through poor operator timing.

KEYING SPEEDS

In radio telegraphy the basic code element is the dot, or unit pulse. A dot and space is two unit pulses, and a dash is three unit pulses long. The space between letters is three unit pulses, and the space between words is seven unit pulses. A speed of one baud is one pulse per second.

Assuming that a speed key is adjusted to give

the proper dot, space and dash values mentioned above, the code speed can be found from

Speed (w.p.m.) =
$$\frac{dots/min.}{25}$$

E.g.: A properly adjusted electronic key gives a string of dots that counts to 10 dots per second. Speed = $(60 \times 10) \div 25 = 24$ w.p.m.

AN ELECTRONIC SPEED KEY

The unit shown in Figs. 8-12 and 8-14 represents one of the simpler designs of an electronic key. The total cost of the key, in dollars and construction time, is quite low. The keying lever is made from parts taken from two straight telegraph keys; these are available at less than a dollar each in the war-surplus version (J-38). A more elegant keying lever can be built from a (more-expensive) war-surplus mechanical speed key.

Referring to Fig. 8-13, the timing of the key is provided by the oscillator V_{1A} . When the key is closed, a sawtooth wave is generated by the fast charge and slow discharge of the .25- μ f. capacitor in the cathode circuit. The rate of discharge is set by the total resistance across the capacitor, and the voltage to which the capacitor is charged is determined by the setting of R_1 . The sawtooth wave, applied to the grid of V_{2A} , cannot drive the grid very positive because the 3.3-megohm resistor limits the current; the effect is to "clip the tops" of the sawtooth cycles. The voltage at which V_{2A} passes enough current to close

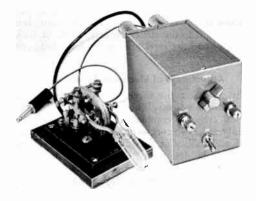


Fig. 8-12—This electronic speed key has a range of approximately 8 to 35 w.p.m., set by the speed control at top center. It has relay output and can be used with any transmitter that can be keyed by a hand key. The key (left) is made from two telegraph keys and a pair of 1/2-inch thick sheet plastic paddles.

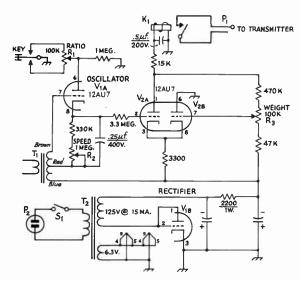


Fig. 8-13—Circuit diagram of the electronic speed key. Unless otherwise specified, resistors are ½ watt. Polarity-marked capacitors are electrolytic, others are tubular paper.

K₁--5000-ohm 3-ma. relay (Sigma 41F-5000S-SIL).

P₁—Phone plug.

P₂—A.c. line plug.

R₁, R₃—100,000-ohm potentiometer, linear taper.

 R_2 —1-megohm potentiometer, linear taper.

S₁—S.p.s.t. toggle.

T₁—5-watt 25,000-to-4-ohm output transformer, secondary not used (Stancor A-3857).

T₂—125-v. 15-ma. and 6.3-v. 0.6-amp. transformer (Stancor PS-8415 or similar).

the relay is set by the position of the arm of R_a .

Except for the tubes, the keyer circuit is housed in a grey Hammertone $6 \times 5 \times 4$ -inch Minibox (Bud CU-2107), as shown in Fig. 8-14. The tube sockets are mounted so that the two tubes project outside at the rear of the unit. The power transformer is mounted on the rear wall, and the toggle switch and the three controls are mounted on the "front" panel. The power line to P_2 , the two-wire cable to P_1 , and the three-wire cable to the key leave the cabinet at the rear through individual rubber grommets. Use multiple tie points generously for the support of the fixed resistors and capacitors.

To make the key, first remove the keys from their bases and strip the bases of their remaining hardware. The four support legs for the key are formed from the original tie strips and shorting switch arms. At the front they bolt to the key frame at the countersunk holes; at the rear they make up to the binding posts. The three-wire cable connects to two binding posts and a supporting leg. A heavy base of ½-inch thich steel adds weight to the structure, and rubber or cork feet glued to the steel prevent its scratching the table.

Adjustment of Electronic Speed Key

In operation, the three controls will serve as their labels indicate. There is a unique (but not highly critical) combination of settings of the weight and ratio controls that will give automatic dots and dashes at the same speed; this setting can only be determined by ear and will be dependent on how well the operator can recognize good code. If the operator taps his foot to count groups of four dots or two dashes, the dots and dashes will have the same speed when the beat is

the same. It is easy to determine whether dots or dashes are too heavy or too light. Connect an ohmmeter to P_1 ; holding the dot lever closed should make the ohmmeter needle hover around half scale, and holding the dash lever closed should make the ohmmeter hover around 75 per cent of the short-circuit reading. Lacking an ohmmeter, the transmitter plate milliammeter can be used; dots and dashes should give 50 per cent and 75 per cent of the key-down value when the keyer controls have been properly adjusted.

QST articles describing other types of electronic speed keys include:

Bartlett, "Compact Automatic Key Design," Dec., 1951. Old "Transistorized Electronic Key and Monitor," May, 1959.

1959.

Kanda, "The 'Ultimatic'——Transistorized," Sept., Oct., 1960.

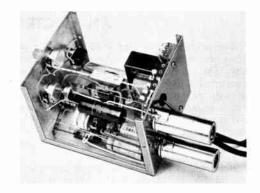


Fig. 8-14—Components for the electronic speed key are mounted on the three walls of a Minibox section, with the tubes projecting out the back. Keep wires away from screw holes, to prevent short circuits when the box is assembled.

ELECTRONIC TRANSMIT-RECEIVE SWITCHES

No antenna relay is fast enough to switch an antenna from transmitter to receiver and back

at normal keying speeds. As a consequence, when it is desired to use the same antenna for trans-

mitting and receiving (a "must" when directional antennas are used) and to operate c.w. break-in or voice-controlled sideband, and electronic switch is used in the antenna. The word "switch" is a misnomer in this case; the transmitter is connected to the antenna at all times and the t.r. "switch" is a device for preventing burn-out of the receiver by the transmitter.

One of the simplest approaches is the circuit shown in Fig. 8-15. The 6C4 cathode follower couples the incoming signal on the line to the receiver input with only a slight reduction in gain. When the transmitter is "on," the grid of the 6C4 is driven positive and the rectified current biases the 6C4 so that it can pass very little power on to the receiver. The factors that limit the r.f voltage the circuit can handle are the voltage break-down rating of the 47- $\mu\mu$ f. capaci-


Fig. 8-15—Schematic diagram of cathode-follower t.r. switch. Resistors are ½-watt. The unit should be assembled in a small chassis or shield con and mounted on or very close to the receiver ontenna terminals. The transmitter transmission line can be connected of the cooxial jack with an M-358 Tee adapter.

The heater and plate power can be "borrowed" from the receiver in most cases.

tor and the voltage that may be safely applied between the grid and cathode of the tube.

To avoid stray pick-up on the lead between the cathode and the antenna terminal of the receiver, this lead should be kept as short as possible. The entire unit should be shielded and mounted on the receiver near the antenna terminals. In wiring the tube socket, input and output circuit components and wiring should be separated to reduce feed-through by stray coupling.

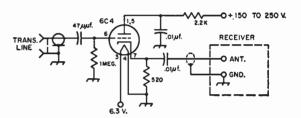The switch should be connected to the transmitter by as short a length of coaxial cable as possible, particularly if the higher-frequency bands (21 and 28 Mc.) are commonly used. If this rule is not observed, there may be conditions where a loss of received signal will be noticed, caused by resonant conditions in the cable and the transmitter output circuit.



SELF-CONTAINED ALL-BAND ELECTRONIC T.R. SWITCH



The t.r. switch shown in Fig. 8-16 differs in several ways from the preceding example. It contains its own power supply and consequently can be used with any transmitter/receiver combination without "borrowing" power. It will add gain and front-end selectivity to the receiver. A commercial switch-coil-capacitor combination is shown in the unit, although the constructor could-build his own if desired.

Referring to the circuit diagram in Fig. 8-17, one triode of a 12AU7 is used as an amplifier stage, followed by the other triode as a cathode-follower stage to couple between the tuned circuit and the receiver. As in the simpler switch, the triodes are biased during transmission periods by rectified grid current, and insufficient power is passed along to the receiver to injure its input circuit.

The t.r. switch is intended to mount behind the transmitter near its output terminal, so that the connecting cable is short. The lead from the t.r. switch to the receiver can be any reasonable length. Components are mounted on the sides and walls of the chassis, although a small bracket will be needed to support the tube socket and another is required to hold the far end of the coil L_1 . The single coil bracket, aided by panel bushings for

Fig. 8-16—The electronic t.r. switch is built in a $5 \times 9 \times 2\frac{1}{2}$ -inch chossis; the bottom plate has been removed to show the placement of parts. Although two receiver outlets are shown on the near foce (a phono jack ond a coaxial receptocle), only one is required, depending upon one's choice of cable terminotion.

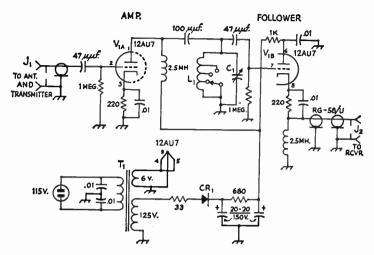


Fig. 8-17—Circuit diagram of the electronic t.r. switch. Unless otherwise specified, resistances are in ohms, resistors are $\frac{1}{2}$ watt, capacitances are in μ f.

C₁—140-μμf. variable (part of Harrington GP-20 tuner). CR₁—200-ma. 360-p.i.v. silicon rectifier (Sarkes Tarzian K-200).

 $J_1\mbox{--}{\mbox{Coaxial}}$ receptacle and tee fitting (SO-239 and M-358).

J₃-Coaxial receptacle or phono jack.

the switch and capacitor C_1 shafts, is sufficient support for the coil-and-capacitor assembly. In wiring the switch, a length of RG-58/U should be used between the cathode-follower load (resistor and r.f. choke) and the output jack J_2 , to minimize "feedthrough" around the tube. A pair of 0.01 μ f. disk ceramic capacitors across the a.c. line where it enters the chassis helps to hold down the r.f. that might otherwise ride in on the a.c. line.

In operation, it is only necessary to switch the unit to the band in use and peak capacitor C_1 for

L₁-52 turns No. 24 on ¾-inch diam. form, 28 t.p.i.
Tapped at 5½, 8½, 13 and 24 turns from
grounded end. (Part of Harrington GP-20 tuner).

T₁—125-v. 15-ma., 6-v. 0.6-amp. transformer (Stancor PS-8415) (GP-20 tuner available from Harrington Electronics, Box 189, Topsfield, Mass.).

maximum signal or background noise. A significant increase in signal or background noise should be observed on any band within the range of the coil/capacitor combination.

TVI and T.R. Switches

The preceding t.r. switches generate harmonics when their grid circuits are driven positive, and these harmonics can cause TVI if steps are not taken to prevent it. Either switch should be well-shielded and used in the antenna transmission line between transmitter and low-pass filter.

Speech Amplifiers and Modulators

The audio amplifiers used in radiotelephone transmitters operate on the principles outlined earlier in this book in the chapter on vacuum tubes. The design requirements are determined principally by the type of modulation system to be used and by the type of microphone to be employed. It is necessary to have a clear understanding of modulation principles before the problem of laying out a speech system can be approached successfully. Those principles are discussed under appropriate chapter headings.

The present chapter deals with the design of audio amplifier systems for communication purposes. In voice communication the primary objective is to obtain the most effective transmission; i.e., to make the message be understood at the receiving point in spite of adverse conditions created by noise and interference. The methods used to accomplish this do not necessarily coincide with the methods used for other purposes,

such as the reproduction of music or other program material. In other words, "naturalness" in reproduction is distinctly secondary to intelligibility.

The fact that satisfactory intelligibility can be maintained in a relatively narrow band of frequencies is particularly fortunate, because the width of the channel occupied by a phone transmitter is directly proportional to the width of the audio-frequency band. If the channel width is reduced, more stations can occupy a given band of frequencies without mutual interference.

In speech transmission, amplitude distortion of the voice wave has very little effect on intelligibility. The importance of such distortion in communication lies almost wholly in the fact that many of the audio-frequency harmonics caused by it lie outside the channel needed for intelligible speech, and thus will create unnecessary interference to other stations.

SPEECH EQUIPMENT

In designing speech equipment it is necessary to know (1) the amount of audio power the modulation system must furnish and (2) the output voltage developed by the microphone when it is spoken into from normal distance (a few inches) with ordinary loudness. It then becomes possible to choose the number and type of amplifier stages needed to generate the required audio power without overloading or undue distortion anywhere in the system.

MICROPHONES

The level of a microphone is its electrical output for a given sound intensity. Level varies greatly with microphones of different types, and depends on the distance of the speaker's lips from the microphone. Only approximate values based on averages of "normal" speaking voices can be given. The values given later are based on close talking; that is, with the microphone about an inch from the speaker's lips.

The frequency response or fidelity of a microphone is its relative ability to convert sounds of different frequencies into alternating current. For understandable speech transmission only a limited frequency range is necessary, and intelligible speech can be obtained if the output of the microphone does not vary more than a few decibels at any frequency within a range of about 200 to 2500 cycles. When the variation expressed in terms of decibels is small between two fre-

quency limits, the microphone is said to be flat between those limits.

Carbon Microphones

The carbon microphone consists of a metal diaphragm placed against an insulating cup containing loosely-packed carbon granules (microphone button). When used with a vacuum-tube amplifier, the microphone is connected in the cathode circuit of a medium- μ triode, as shown in Fig. 9-1A.

Sound waves striking the diaphragm cause it to vibrate in accordance with the sound, and the pressure on the granules alternately increases and decreases, causing a corresponding decrease and increase in the electrical resistance of the microphone. The instantaneous value of this resistance determines the instantaneous value of plate current through the tube, and as a consequent the voltage drop across the plate load resistor increases and decreases with the increases and decreases in granule pressure.

The carbon microphone finds its major amateur application in mobile and portable work; a good microphone in the circuit of Fig. 9-1A will deliver 20 to 30 volts peak output.

Piezo-electric Microphones

The crystal microphone makes use of the piezoelectric properties of Rochelle salts crystals. This type of microphone requires no battery or

transformer and can be connected directly to the grid of an amplifier tube. It is a popular type of microphone among amateurs, for these reasons as well as the fact that it has good frequency response and is available in inexpensive models. The input circuit for the crystal microphone is shown in Fig. 9-1B.

Although the level of crystal microphones varies with different models, an output of 0.03 volt or so is representative for communication types. The level is affected by the length of the cable connecting the microphone to the first amplifier stage; the above figure is for lengths of 6 or 7 feet. The frequency characteristic is unaffected by the cable, but the load resistance (amplifier grid resistor) does affect it; the lower frequencies are attenuated as the value of load resistance is lowered. A grid-resistor value of at least 1 megohm should be used for reasonably flat response, 5 megohms being a customary figure.

The ceramic microphone utilizes the piezoelectric effect in certain types of ceramic materials to achieve performance very similar to that of the crystal microphone. It is less affected by temperature and humidity. Output levels are similar to those of crystal microphones for the same type of frequency response.

Velocity and Dynamic Microphones

In a velocity or "ribbon" microphone, the element acted upon by the sound waves is a thin corrugated metallic ribbon suspended between the poles of a magnet.

Velocity microphones are built in two types, high impedance and low impedance, the former being used in most applications. A high-impedance microphone can be directly connected to the grid of an amplifier tube, shunted by a resistance of 0.5 to 5 megolims (Fig. 9-1C). Low-impedance microphones are used when a long connecting cable (75 feet or more) must be employed. In such a case the output of the microphone is coupled to the first amplifier stage through a suitable step-up transformer, as shown in Fig. 9-1D.

The level of the velocity microphone is about 0.03 to 0.05 volt. This figure applies directly to the high-impedance type, and to the low-impedance type when the voltage is measured across the secondary of the coupling transformer.

The dynamic microphone somewhat resembles a dynamic loud-speaker. A lightweight voice coil is rigidly attached to a diaphragm, the coil being suspended between the poles of a permanent magnet. Sound causes the diaphragm to vibrate, thus moving the coil back and forth between the magnet poles and generating an alternating voltage.

The dynamic microphone usually is built with high-impedance output, suitable for working directly into the grid of an amplifier tube. If the connecting cable must be unusually long, a low-impedance type should be used, with a step-up transformer at the end of the cable.

In general, the dynamic microphones have the

smoothest peak-free response and widest frequency range, and they are also the least susceptible to damage from shock and extremes of temperature and humidity.

THE SPEECH AMPLIFIER

The audio-frequency amplifier stage that causes the r.f. carrier output to be varied is called the modulator, and all the amplifier stages preceding it comprise the speech amplifier. Depending on the modulator used, the speech amplifier may be called upon to deliver a power output ranging from practically zero (only voltage required) to 20 or 30 watts.

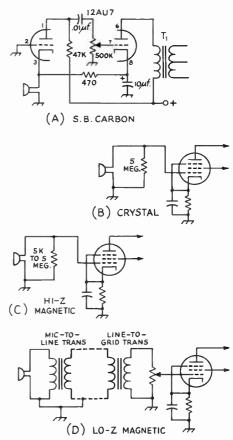


Fig. 9-1—Speech input circuits used with various types of microphones.

Before starting the design of a speech amplifier, therefore, it is necessary to have selected a suitable modulator for the transmitter. This selection must be based on the power required to modulate the transmitter, and this power in turn depends on the type of modulation system selected, as described in Chapter 10. With the modulator picked out, its driving-power requirements (audio power required to excite the modulator to full output) can be determined from the tube tables in a later chapter. Generally speaking, it is advisable to choose a tube or tubes for

Speech Equipment

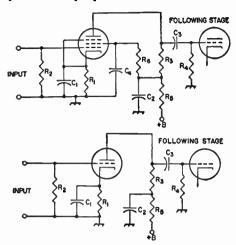


Fig. 9-2—Resistance-coupled voltage-amplifier circuits. A, pentode; B, triode. Designations are as follows:

C₁-Cathode bypass capacitor.

C₂-Plate bypass capacitor.

C3-Output coupling capacitor (blocking capacitor).

C₄-Screen bypass capacitor.

R₁-Cathode resistor.

R2-Grid resistor.

R₃-Plate resistor.

R₄-Next-stage grid resistor.

R₅-Plate decoupling resistor.

R₆-Screen resistor.

Values for suitable tubes are given in Table 9-1. Values in the decoupling circuit, C₂R_s are not critical. R₅ may be about 10% of R₃; an 8- or 10-\mu f. electrolytic capacitor is usually large enough at C₂.

the last stage of the speech amplifier that will be capable of developing at least 50 per cent more power than the rated driving power of the modulator. This will provide a factor of safety so that losses in coupling transformers, etc., will not upset the calculations.

Voltage Amplifiers

If the last stage in the speech amplifier is a Class AB₂ or Class B amplifier, the stage ahead of it must be capable of sufficient power output to drive it. However, if the last stage is a Class AB₁ or Class A amplifier the preceding stage can be simply a voltage amplifier. From there on back to the microphone, all stages are voltage amplifiers.

The important characteristics of a voltage amplifier are its voltage gain, maximum undistorted output voltage, and its frequency response. The voltage gain is the voltage-amplification ratio of the stage. The output voltage is the maximum a.f. voltage that can be secured from the stage without distortion. The amplifier frequency response should be adequate for voice reproduction; this requirement is easily satisfied.

The voltage gain and maximum undistorted output voltage depend on the operating conditions of the amplifier. Data on the popular types of tubes used in speech amplifiers are given in Table 9-I, for resistance-coupled amplification. The output voltage is in terms of *peak* voltage rather than r.m.s.; this makes the rating independent of the waveform. Exceeding the peak value causes the amplifier to distort, so it is more useful to consider only peak values in working with amplifiers.

Resistance Coupling

Resistance coupling generally is used in voltage-amplifier stages. It is relatively inexpensive, good frequency response can be secured, and there is little danger of hum pick-up from stray magnetic fields associated with heater wiring. It is the most satisfactory type of coupling for the output circuits of pentodes and high- μ triodes, because with transformers a sufficiently high load impedance cannot be obtained without considerable frequency distortion. Typical circuits are given in Fig. 9-2 and design data in Table 9-I.

Transformer Coupling

Transformer coupling between stages ordinarily is used only when power is to be transferred (in such a case resistance coupling is very inefficient), or when it is necessary to couple between a single-ended and a push-pull stage. Triodes having an amplification factor of 20 or less are used in transformer-coupled voltage amplifiers. With transformer coupling, tubes should be operated under the Class A conditions given in the tube tables at the end of this book.

Representative circuits for coupling singleended to push-pull stages are shown in Fig. 9-3.

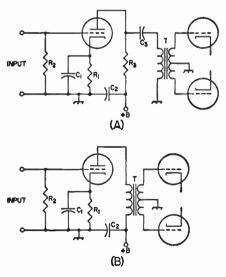


Fig. 9-3—Transformer-coupled amplifier circuits for driving a push-pull amplifier. A is for resistance-transformer coupling; B for transformer coupling. Designations correspond to those in Fig. 9-2. In A, values can be taken from Table 9-1. In B, the cathode resistor is calculated from the rated plate current and grid bias as given in the tube tables for the particular type of tube used.

TABLE 9-I-RESISTANCE-COUPLED VOLTAGE-AMPLIFIER DATA

Data are given for a plate supply of 300 valts. Departures of as much as 50 per cent from this supply voltage will not materially change the operating conditions or the voltage gain, but the output voltage will be in proportion to the ratio of the new voltage to 300 volts. Voltage gain is measured at 400 cycles. Capacitor values given are based on 100-cycle cutoff. For increased low-frequency response, all capacitars may be made larger than specified (cut-off frequency in inverse proportion to capacitor values pravided all are changed in the same proportion). A variation of 10 per cent in the values given has negligible effect on the performance.

	Plate Resistor Megohms	Next-Stage Grid Resistor Megohms	Screen Resistor Megohms	Cathode Resistor Ohms	Screen Bypass µf.	Cathode Bypass µf.	Blocking Capacitor µf.	Output Volts (Peak) ¹	Valtage Gain ²
6\$J7, 12\$J7	0.1	0.1 0.25 0.5	0.35 0.37 0.47	500 530 590	0.10 0.09 0.09	11.6 10.9 9.9	0.019 0.016 0.007	72 96 101	67 98 104
	0.25	0.25 0.5 1.0	0.89 1.10 1.18	850 860 910	0.07 0.06 0.06	8.5 7.4 6.9	0.011 0.004 0.003	79 88 98	139 167 185
	0.5	0.5 1.0 2.0	2.0 2.2 2.5	1300 1410 1530	0.06 0.05 0.04	6.0 5.8 5.2	0.004 0.002 0.0015	64 79 89	200 238 263
6Л, 7СЛ, 12Л-GT	0.1	0.1 0.25 0.5	0.44 0.5 0.53	500 450 600	0.07 0.07 0.06	8.5 8.3 8.0	0.02 0.01 0.006	55 81 96	61 82 94
	0.25	0.25 0.5 1.0	1.18 1.18 1.45	1100 1200 1300	0.04 0.04 0.05	5.5 5.4 5.8	0.008 0.005 0.005	81 104 110	104 140 185
	0.5	0.5 1.0 2.0	2.45 2.9 2.95	1700 2200 2300	0.04 0.04 0.04	4.2 4.1 4.0	0.005 0.003 0.0025	75 97 100	161 200 230
6AU6, 6SH7, 12AU6, 12SH7	0.1	0.1 0.22 0.47	0.2 0.24 0.26	500 600 700	0.13 0.11 0.11	18.0 16.4 15.3	0.019 0.011 0.006	76 103 129	109 145 168
	0.22	0.22 0.47 1.0	0.42 0.5 0.55	1000 1000 1100	0.1 0.098 0.09	12.4 12.0 11.0	0.009 0.007 0.003	92 108 122	164 230 262
	0.47	0.47 1.0 2.2	1.0 1.1 1.2	1800 1900 2100	0.075 0.065 0.06	8.0 7.6 7.3	0.0045 0.0028 0.0018	94 105 122	248 318 371
6AQ6, 6AQ7, 6AT6, 6Q7, 6SL7-GT 6T8-A, 12AT6, 12Q7-GT, 12SL7-GT (one triode)	0.1	0.1 0.22 0.47		1500 1800 2100		4.4 3.6 3.0	0.027 0.014 0.0065	40 54 63	34 38 41
	0.22	0.22 0.47 1.0		2600 3200 3700		2.5 1.9 1.6	0.013 0.0065 0.0035	51 65 77	42 46 48
	0.47	0.47 1.0 2.2		5200 6300 7200	=	1.2 1.0 0.9	0.006 0.0035 0.002	61 74 85	48 50 51
6AV6, 12AV6, 12AX7 {one triade}	0.1	0.1 0.22 0.47	\equiv	1300 1500 1700		4.6 4.0 3.6	0.027 0.013 0.006	43 57 66	45 52 57
	0.22	0.22 0.47 1.0		2200 2800 3100		3.0 2.3 2.1	0.013 0.006 0.003	54 69 79	59 65 68
	0.47	0.47 1.0 2.2	=	4300 5200 5900		1.6 1.3 1.1	0.006 0.003 0.002	62 77 92	69 73 75
6SC7,8 12SC7 8 {one triode}	0.1	0.1 0.25 0.5		750 930 1040		=	0.033 0.014 0.007	35 50 54	29 34 36
	0.25	0.25 0.5 1.0		1400 1680 1840	=	=	0.012 0.006 0.003	45 55 64	39 42 45
	0.5	0.5 1.0 2.0	=	2330 2980 3280		=	0.006 0.003 0.002	50 62 72	45 48 49
6CG7, 6J5, 7A4, 7N7, 6SN7-GTB, 12J5-GT, 12SN7-GT (one triode)	0.047	0.047 0.1 0.22		1300 1580 1800		3.6 3.0 2.5	0.061 0.032 0.015	59 73 83	14 15 16
	0.1	0.1 0.22 0.47		2500 3130 3900	=	1.9 1.4 1.2	0.031 0.014 0.0065	68 82 96	16 16 16
	0.22	0.22 0.47 1.0		4800 6500 7800		0.95 0.69 0.58	0.015 0.0065 0.0035	68 85 96	16 16 16
6C4, 12AU7-A {one triode}	0.047	0.047 0.1 0.22		870 1200 1500		4.1 3.0 2.4	0.065 0.034 0.016	38 52 68	12 12 12
	0.1	0.1 0.22 0.47		1900 3000 4000		1.9 1.3 1.1	0.032 0.016 0.007	44 68 80	12 12 12
	0.22	0.22 0.47 1.0		5300 8800 11000		0.9 0.52 0.46	0.015 0.007 0.0035	57 82 92	12 12 12

¹ Voltage across next-stage grid resistor at grid-current point.

² At 5 volts r.m.s. output.

⁸ Cathode-resistor values are for phase-inverter service.

Designing the Speech Amplifier

The circuit at A combines resistance and transformer coupling, and may be used for exciting the grids of a Class A or AB₁ following stage. The resistance coupling is used to keep the d.c. plate current from flowing through the transformer primary, thereby preventing a reduction in primary inductance below its no-current value; this improves the low-frequency response. With medium- μ triodes (6C5, 6J5, etc.), the gain is equal to that with resistance coupling multiplied by the secondary-to-primary turns ratio of the transformer.

In B the transformer primary is in series with the plate of the tube, and thus must carry the tube plate current. When the following amplifier operates without grid current, the voltage gain of the stage is practically equal to the μ of the tube multiplied by the transformer ratio. This circuit also is suitable for transferring power

Fig. 9-4—Self-balancing phase-inverter circuits. V_1 and V_2 may be a double triode such as the 12AU7 or 12AX7. V_3 may be any of the triodes listed in Table 9-1, or one section of a double triode.

 R_1 —Grid resistor (1 megohm or less).

R₂—Cathode resistor; use one-half value given in Table 9-I for tube and operating conditions chosen.

Rs, R4-Plate resistor; select from Table 9-1.

 $R_{\delta},\ R_{\delta}{\rm -Following\text{-}stage}$ grid resistor (0.22 to 0.47 megohm).

R₇-0.22 megohm.

R₈-Cathode resistor; select from Table 9-1.

R₀, R₁₀—Each one-half of plate load resistor given in Table 9-1.

C₁-10-\mu f. electrolytic.

C₂, C₃-0.01- to 0.1-\(mu f\), paper.

(within the capabilities of the tube) to a following Class AB₂ or Class B stage.

Phase Inversion

Push-pull output may be secured with resistance coupling by using phase-inverter or phasesplitter circuits as shown in Fig. 9-4.

The circuits shown in Fig. 9-4 are of the "selfbalancing" type. In A, the amplified voltage from V_1 appears across R_5 and R_7 in series. The drop across R_7 is applied to the grid of V_2 , and the amplified voltage from V_2 appears across R_6 and R_7 in series. This voltage is 180 degrees out of phase with the voltage from V_1 , thus giving push-pull output. The part that appears across R_7 from V_2 opposes the voltage from V_1 across R_7 , thus reducing the signal applied to the grid of V2. The negative feedback so obtained tends to regulate the voltage applied to the phaseinverter tube so that the output voltages from both tubes are substantially equal. The gain is slightly less than twice the gain of a single-tube amplifier using the same operating conditions.

In the single-tube circuit shown in Fig. 9-4B the plate load resistor is divided into two equal parts, R_9 and R_{10} , one being connected to the plate in the normal way and the other between cathode and ground. Since the voltages at the plate and cathode are 180 degrees out of phase, the grids of the following tubes are fed equal a.f. voltages in push-pull. The grid return of V_3 is made to the junction of R_8 and R_{10} so normal bias will be applied to the grid. This circuit is highly degenerative because of the way R_{10} is connected. The voltage gain is less than 2 even when a high- μ triode is used at V_3 .

Gain Control

A means for varying the over-all gain of the amplifier is necessary for keeping the final output at the proper level for modulating the transmitter. The common method of gain control is to adjust the value of a.c. voltage applied to the grid of one of the amplifiers by means of a voltage divider or potentiometer.

The gain-control potentiometer should be near the input end of the amplifier, at a point where the signal voltage level is so low there is no danger that the stages ahead of the gain control will be overloaded by the full microphone output. With carbon microphones the gain control may be placed directly across the microphone-transformer secondary. With other types of microphones, however, the gain control usually will affect the frequency response of the microphone when connected directly across it. Also, in a high-gain amplifier it is better to operate the first tube at maximum gain, since this gives the best signal-to-hum ratio. The control therefore is usually placed in the grid circuit of the second stage.

DESIGNING THE SPEECH AMPLIFIER

The steps in designing a speech amplifier are as follows:

1) Determine the power needed to modulate

the transmitter and select the modulator. In the case of plate modulation, a Class B amplifier may be required. Select a suitable tube type and determine from the tube tables at the end of this book the grid driving power required, if any.

2) As a safety factor, multiply the required driver power by at least 1.5.

- 3) Select a tube, or pair of tubes, that will deliver the power determined in the second step. This is the last or output stage of the speechamplifier. Receiver-type power tubes can be used (beam tubes such as the 6L6 may be needed in some cases) as determined from the receiving-tube tables. If the speech amplifier is to drive a Class B modulator, use a Class A or AB₁ amplifier.
- 4) If the speech-amplifier output stage is also the modulator and must operate Class AB_2 to develop the required power output, use a low-or medium- μ triode to drive it. If more power is needed than can be obtained from one tube, use two in push-pull, in the driver. In either case transformer coupling will have to be used, and transformer manufacturers' catalogs should be consulted for a suitable type.
- 5) If the speech-amplifier output stage operates Class A or AB₁, it may be driven by a voltage amplifier. If the output stage is push-pull, the driver may be a single tube coupled through a transformer with a balanced secondary, or may be a dual-triode phase inverter. Determine the signal voltage required for full output from the last stage. If the last stage is a single-tube Class A amplifier, the peak signal is equal to the gridbias voltage; if push-pull Class A, the peak-topeak signal voltage is equal to twice the gridbias; if Class AB₁, twice the bias voltage when fixed bias is used; if cathode bias is used, twice the bias figured from the cathode resistance and the maximum-signal cathode current.
- 6) From Table 9-I, select a tube capable of giving the required output voltage and note its rated voltage gain. A double-triode phase inverter (Fig. 9-4A) will have approximately twice the output voltage and twice the gain of one triode operating as an ordinary amplifier. If the driver is to be transformer-coupled to the last stage, select a medium- μ triode and calculate the gain and output voltage as described earlier in this chapter.

7) Divide the voltage required to drive the output stage by the gain of the preceding stage. This gives the peak voltage required at the grid of the next-to-the-last stage.

- 8) Find the output voltage, under ordinary conditions, of the microphone to be used. This information should be obtained from the manufacturer's catalog. If not available, the figures given in the section on microphones in this chapter will serve.
- 9) Divide the voltage found in (7) by the output voltage of the microphone. The result is the over-all gain required from the microphone to the grid of the next-to-the-last stage. To be on the safe side, double or triple this figure.
 - 10) From Table 9-I, select a combination of

tubes whose gains, when multiplied together, give approximately the figure arrived at in (9). These amplifiers will be used in cascade. If high gain is required, a pentode may be used for the first speech-amplifier stage, but it is not advisable to use a second pentode because of the possibility of feedback and self-oscillation. In most cases a triode will give enough gain, as a second stage, to make up the total gain required. If not, a medium-µ triode may be used as a third stage.

A high- μ double triode with the sections in cascade makes a good low-level amplifier, and will give somewhat greater gain than a pentode followed by a medium- μ triode. With resistance-coupled input to the first section the cathode of that section may be grounded (contact potential bias), which is helpful in reducing hum.

SPEECH-AMPLIFIER CONSTRUCTION

Once a suitable circuit has been selected for a speech amplifier, the construction problem resolves itself into avoiding two difficulties—excessive hum, and unwanted feedback. For reasonably humless operation, the hum voltage should not exceed about 1 per cent of the maximum audio output voltage—that is, the hum and noise should be at least 40 db. below the output level.

Unwanted feedback, if negative, will reduce the gain below the calculated value; if positive, is likely to cause self-oscillation or "howls." Feedback can be minimized by isolating each stage with decoupling resistors and capacitors, by avoiding layouts that bring the first and last stages near each other, and by shielding of "hot" points in the circuit, such as grid leads in low-level stages.

Speech-amplifier equipment, especially voltage amplifiers, should be constructed on steel chassis, with all wiring kept below the chassis to take advantage of the shielding afforded. Exposed leads, particularly to the grids of low-level high-gain tubes, are likely to pick up hum from the electric field that usually exists in the vicinity of house wiring. Even with the chassis, additional shielding of the input circuit of the first tube in a highgain amplifier usually is necessary. In addition, such circuits should be separated as much as possible from power-supply transformers and chokes and also from any audio transformers that operate at fairly high power levels; this will minimize magnetic coupling to the grid circuit and thus reduce hum or audio-frequency feedback. It is always safe, although not absolutely necessary, to separate the speech amplifier and its power supply, building them on separate chassis.

If a low-level microphone such as the crystal type is used, the microphone, its connecting cable, and the plug or connector by which it is attached to the speech amplifier, all should be shielded. The microphone and cable usually are constructed with suitable shielding; this should be connected to the speech-amplifier chassis, and it is advisable — as well as necessary — to connect

Modulators and Drivers

the chassis to a ground such as a water pipe. With the top-cap tubes, complete shielding of the grid lead and grid cap is a necessity.

Heater wiring should be kept as far as possible from grid leads, and either the center-tap or one side of the heater-transformer secondary winding should be connected to the chassis. If the center-tap is grounded, the heater leads to each tube should be twisted together to reduce the magnetic field from the heater current. With either type of connection; it is advisable to lay heater leads in the corner formed by a fold in the chassis, bringing them out from the corner to the tube socket by the shortest possible path.

When metal tubes are used, always ground the shell connection to the chassis. Glass tubes used in the low-level stages of high-gain amplifiers must be shielded; tube shields are obtainable for that purpose. It is a good plan to enclose the entire amplifier in a metal box, or at least provide it with a cane-metal cover, to avoid feedback difficulties caused by the r.f. field of the transmitter. R.f. picked up on exposed wiring, leads or tube elements causes overloading, distortion, and self-oscillation of the amplifier.

When using paper capacitors as bypasses, be sure that the terminal marked "outside foil" is connected to ground. This utilizes the outside foil of the capacitor as a shield around the "hot" foil. When paper capacitors are used for coupling between stages, always connect the outside foil terminal to the side of the circuit having the lowest impedance to ground. Usually, this will be the plate side rather than the following-grid side.

MODULATORS AND DRIVERS

CLASS AB AND B MODULATORS

Class AB or B modulator circuits are basically identical no matter what the power output of the modulator. The diagrams of Fig. 9-5 therefore will serve for any modulator of this type that the amateur may elect to build. The triode circuit is given at A and the circuit for tetrodes at B. When small tubes with indirectly heated cath-

DRIVER PLATES

OR LINE

OR LINE

TRANS

MA

HV FOR MOD AMP

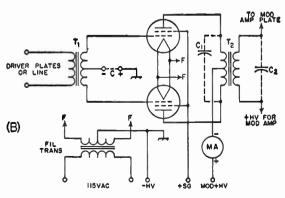


Fig. 9-5—Madulatar circuit diagrams. Tubes and circuit considerations are discussed in the text.

odes are used, the cathodes should be connected to ground.

Modulator Tubes

The audio ratings of various types of transmitting tubes are given in the chapter containing the tube tables. Choose a pair of tubes that is capable of delivering sine-wave audio power equal to somewhat more than half the d.c. input

to the modulated Class C amplifier. It is sometimes convenient to use tubes that will operate at the same plate voltage as that applied to the Class C stage, because one power supply of adequate current capacity may then suffice for both stages.

In estimating the output of the modulator, remember that the figures given in the tables are for the tube output only, and do not include output-transformer losses. To be adequate for modulating the transmitter, the modulator should have a theoretical power capability 15 to 25 per cent greater than the actual power needed for modulation.

Matching to Load

In giving audio ratings on power tubes, manufacturers specify the plate-to-plate load impedance into which the tubes must operate to deliver the rated audio power output. This load impedance seldom is the same as the modulating impedance of the Class C r.f. stage, so a match must be brought about by adjusting the turns ratio of the coupling transformer. The required turns ratio, primary to secondary, is

$$N = \sqrt{\frac{Z_{\rm p}}{Z_{\rm m}}}$$

where N = Turns ratio, primary to secondary

 $Z_{\rm m} = {\rm Modulating\ impedance\ of}$

Class C r.f. amplifier

 Z_p = Plate-to-plate load impedance for Class B tubes

Example: The modulated r.f. amplifier is to operate at 1250 volts and 250 ma. The power input is

$$P = EI = 1250 \times 0.25 = 312$$
 watts

so the modulating power required is 312/2 = 156 watts. Increasing this by 25% to allow for losses and a reasonable operating marging is $156 \times 1.25 = 195$ watts. The modulating impedance of the Class C stage is

$$Z_{\rm m} = \frac{E}{-} = \frac{1250}{0.25} = 5000$$
 ohms.

From the tube tables a pair of Class B tubes is selected that will give 200 watts output when working into a 6900-ohm load, plate-to-plate. The primary-to-secondary turns ratio of the modulation transformer therefore should be

$$N = \sqrt{\frac{Z_p}{Z_m}} = \sqrt{\frac{6900}{5000}} = \sqrt{1.38} = 1.175:1.$$

The required transformer ratios for the ordinary range of impedances are shown graphically in Fig. 9-6.

Many modulation transformers are provided with primary and secondary taps, so that various turns ratios can be obtained to meet the requirements of particular tube combinations. However, it may be that the exact turns ratio required cannot be secured, even with a tapped modulation transformer. Small departures from the proper turns ratio will have no serious effect if the modulator is operating well within its capabilities; if the actual turns ratio is within 10 per cent of the ideal value, the system will operate satisfactorily. Where the discrepancy is larger, it is usually possible to choose a new set of operating conditions for the Class C stage to give a modulating impedance that can be matched by the turns ratio of the available transformer. This may require operating the Class C amplifier at higher voltage and less plate current, if the modulating impedance must be increased, or at lower voltage and higher current if the modulating impedance must be decreased. However, this process cannot be carried very far without exceeding the ratings of the Class C tubes for either plate voltage or plate current, even though the power input is kept at the same figure.

Suppressing Audio Harmonics

Distortion in either the driver or Class B modulator will cause a.f. harmonics that may lie outside the frequency band needed for intelligible speech transmission. While it is almost impossible to avoid some distortion, it is possible to cut down the amplitude of the higher-frequency harmonics.

The purpose of capacitors C_1 and C_2 across the primary and secondary, respectively, of the Class B output transformer in Fig. 9-5 is to reduce the strength of harmonics and unnecessary

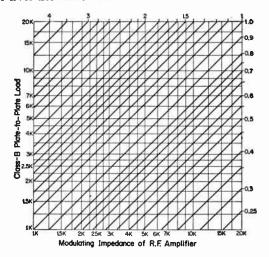


Fig. 9-6—Transformer ratios for matching a Class C modulating impedance to the required plate-to-plate load for the Class B modulator. The ratios given on the curves are from total primary to secondary. Resistance values are in kilohms.

high-frequency components existing in the modulation. The capacitors act with the leakage inductance of the transformer winding to form a rudimentary low-pass filter. The values of capacitance required will depend on the load resistance (modulating impedance of the Class C amplifier) and the leakage inductance of the particular transformer used. In general, capacitances between about 0.001 and 0.01 \(mu f.\) will be required; the larger values are necessary with the lower values of load resistance. The voltage rating of each capacitor should at least be equal to the d.c. voltage at the transformer winding with which it is associated. In the case of C_2 , part of the total capacitance required will be supplied by the plate bypass or blocking capacitor in the modulated amplifier.

A still better arrangement is to use a low-pass filter as shown later, even though clipping is not deliberately employed.

Grid Bias

Certain triodes designed for Class B audio work can be operated without grid bias. Besides eliminating the grid-bias supply, the fact that grid current flows over the whole audio cycle means that the load resistance for the driver is fairly constant. With these tubes the grid-return lead from the center-tap of the input transformer secondary is simply connected to the filament center-tap or cathode.

When the modulator tubes require bias, it should always be supplied from a fixed voltage source. Cathode bias or grid-leak bias cannot be used with a Class-B amplifier. When only a small amount of bias is required it can be obtained conveniently from a few dry cells. The battery is charged by the grid current rather than discharged, but nevertheless it will deteriorate with time. It should be replaced if the voltage meas-

ured across it varies with the signal by more than 10 per cent or so.

As an alternative to batteries, a regulated bias supply may be used. This type of supply is described in the power supply chapter.

Plate Supply

In addition to adequate filtering, the voltage regulation of the plate supply should be as good as it can be made. If the d.c. output voltage of the supply varies with the load current, the voltage at maximum current determines the amount of power that can be taken from the modulator without distortion. A supply whose voltage drops from 1500 at no load to 1250 at the full modulator plate current is a 1250-volt supply, so far as the modulator is concerned, and any estimate of the power output available should be based on the lower figure.

Good dynamic regulation—i.e., with suddenly applied loads—is equally as important as good regulation under steady loads, since an instantaneous drop in voltage on voice peaks also will limit the output and cause distortion. The output ca-

pacitor of the supply should have as much capacitance as conditions permit. A value of at least $10~\mu f$, should be used, and still larger values are desirable. It is better to use all the available capacitance in a single-section filter rather than to distribute it between two sections.

It is particularly important, in the case of a tetrode Class B stage, that the screen-voltage power-supply source have excellent regulation, to prevent distortion. The screen voltage should be set as exactly as possible to the recommended value for the tube. The audio impedance between screen and cathode also must be low.

Overexcitation

When a Class B amplifier is overdriven in an attempt to secure more than the rated power, distortion increases rapidly. The high-frequency harmonies which result from the distortion modulate the transmitter, producing spurious sidebands which can cause serious interference over a band of frequencies several times the channel width required for speech. (This can happen even though the modulation percentage, as defined in the chapter on amplitude modulation, is less than 100 per cent, if the modulator is incapable of delivering the audio power required to modulate the transmitter.)


As shown later, such a condition may be reached by deliberate design, in case the modulator is to be adjusted for peak clipping. But whether it happens by accident or intention, the splatter and spurious sidebands can be eliminated by inserting a low-pass filter (Fig. 9-13) between the modulator and the modulated amplifier, and then taking care to see that the actual modulation of the r.f. amplifier does not exceed 100 per cent.

Operation Without Load

Excitation should never be applied to a Class B modulator until after the Class C amplifier is turned on and is drawing the value of plate current required to present the rated load to the modulator. With no load to absorb the power, the primary impedance of the transformer rises to a high value and excessive audio voltages may be developed in the primary — frequently high enough to break down the transformer insulation.

DRIVERS FOR CLASS-B MODULATORS

Class AB₂ and Class B amplifiers are driven into the grid-current region, so power is con-

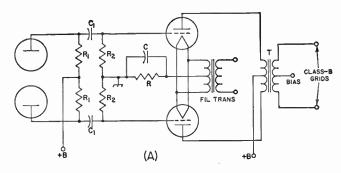

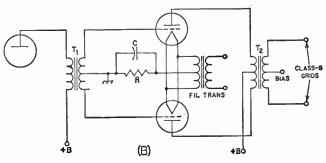


Fig. 9-7—Triode driver circuits far Class B modulators. A, resistance coupling to grids; B, transformer coupling. R_1 in A is the plate resistor for the preceding stage, value determined by the type of tube and aperating canditions as given in Table 9-1. C_1 and R_2 are the coupling capacitor and grid resistor, respectively; values also may be taken from Table 9-1.

In both circuits the output transformer, (T_1T_2) should have the proper turns ratio to couple between the driver tubes and the Class B grids. T_1 in B is usually a 2:1 transformer, secondary to primary. R, the cathode resistor, should be calculated for the particular tubes used. The value of C, the cathode bypass, is determined as described in the text.

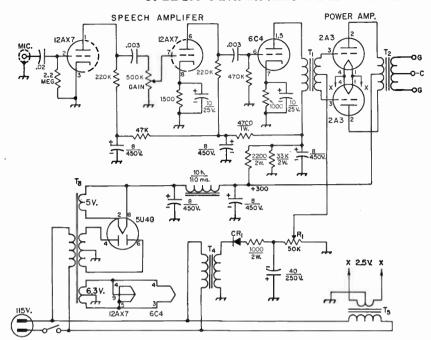


Fig. 9-8—Speech-amplifier driver for 10-15 watts output. Capacitances are in μ f. Resistors are $\frac{1}{2}$ watt unless specified otherwise. Capacitors with polarity indicated are electrolytic; others may be paper or ceramic. CR₁—Selenium rectifier, 20 ma. Class-B tubes used; 15 watt rating.

R₁—50,000-ohm potentiometer, preferably wire wound. T₁—Interstage audio transformer, single plate to pushpull grids, turns ratio 2 to 1 or 3 to 1, total secondary to primary.

T₂—Class-B driver transformer, 3000 ohms plate-toplate; secondary impedance as required by

sumed in the grid circuit. The preceding stage or driver must be capable of supplying this power at the required peak audio-frequency grid-to-grid voltage. Both of these quantities are given in the manufacturer's tube ratings. The grids of the Class B tubes represent a varying load resistance over the audio-frequency cycle, because the grid current does not increase directly with the grid voltage. To prevent distortion, therefore, it is necessary to have a driving source that will maintain the wave form of the signal without distortion even though the load varies. That is, the driver stage must have good regulation. To this end, it should be capable of delivering somewhat more power than is consumed by the Class B grids, as previously described in the discussion on speech amplifiers.

Driver Tubes

To secure good voltage regulation the internal impedance of the driver, as seen by the modulator grids, must be low. The principal component of this impedance is the plate resistance of the driver tube or tubes as reflected through the driver transformer. Hence for low driving-source impedance the effective plate resistance of the driver tubes should be low and the turns ratio of the driver transformer, primary to secondary, should be as large as possible. The maximum

T₃-Power transformer, 700 volts c.t., 110 ma.; 5 volts, 3 amp.; 6.3 volts, 4 amp.

T₄—Power transformer, 125 volts, 20 ma.; 6.3 volts,

T₅-2.5-volt 5-ampere filament transformer (Thordarson 21F00).

turns ratio that can be used is that value which just permits developing the modulator grid-to-grid a.f. voltage required for the desired power output. The rated tube output as shown by the tube tables should be reduced by about 20 per cent to allow for losses in the Class B input transformer.

Low- μ triodes such as the 2A3 have low plate resistance and are therefore good tubes to use as drivers for Class AB2 or Class B modulators. Tetrodes such as the 6V6 and 6L6 make very poor drivers in this respect when used without negative feedback, but with such feedback the effective plate resistance can be reduced to a value comparable with low- μ triodes.

Fig. 9-7 shows representative circuits for a push-pull triode driver using cathode bias. If the amplifier operates Class A the cathode resistor need not be bypassed, because the a.f. currents from each tube flowing in the cathode resistor are out of phase and cancel each other. However, in Class AB operation this is not true; considerable distortion will be generated at high signal levels if the cathode resistor is not bypassed. The bypass capacitance required can be calculated by a simple rule: the cathode resistance in ohms multiplied by the bypass capacitance in microfarads should equal at least 25,000. The voltage rating of the capacitor should be equal

to the maximum bias voltage. This can be found from the maximum-signal plate current and the cathode resistance.

Example: A pair of 2A3s is to be used in Class AB1 self-biased. From the tube tables, the cathode resistance should be 780 ohms and the maximum-signal plate current 100 ma. From Ohm's Law,

$$E = RI = 780 \times 0.10 = 78.6$$
 volts

From the rule mentioned previously, the bypass capacitance required is

 $C = 25,000/R = 25,000/780 = 32 \mu f.$

A 40- or 50-µf. 100-volt electrolytic capacitor would be satisfactory.

Fig. 9-8 is a typical circuit for a speech amplifier suitable for use as a driver for a Class AB2 or Class B modulator. An output of about 13 watts can be realized with the power supply circuit shown (or any similar well-filtered supply delivering 300 volts under load). This is sufficient for driving any of the power triodes commonly used as modulators. The 2A3s in the output stage are operated Class AB1. The circuit provides several times the voltage gain needed for communications-type crystal or ceramic microphones.

The two sections of a 12AX7 tube are used in the first two stages of the amplifier. These are resistance coupled, the gain control being in the grid circuit of the second stage. Although the cathode of the first stage is grounded and there is no separate bias supply for the grid, the grid

Rß

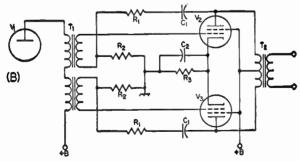


Fig. 9-9—Negative-feedback circuits for drivers for Class B modulators. A-Single-ended beam-tetrode driver. If V1 and V2 are a 615 and 6V6, respectively, or one section of a 6CG7 and a 6AQ5, the following values are suggested: R₁, 47,000 ohms; R₂, 0.47 megohm; R₈, 250 ohms; R₄, R₅, 22,000 ohms; C₁, 0.01 μf.; C2, 50 μf.

B-Push-pull beam-tetrode driver. If V₁ is a 6J5 or 6CG7 and V₂ and V₃ 6L6s, the following values are suggested: R₁, 0.1 megohm; R_2 , 22,000 ohms; R_3 , 250 ohms; C_1 , 0.1 μ f.; C_2 , 100 μ f.

bias actually is about one volt because of "contact potential."

The third stage uses a medium-µ triode which is coupled to the 2A3 grids through a transformer having a push-pull secondary. The ratio may be of the order of 2 to 1 (total secondary to primary) or higher; it is not critical since the gain is sufficient without a high step-up ratio.

The output transformer, T_2 , should be selected to couple between push-pull 2A3s and the grids of the particular modulator tubes used.

The power supply has a capacitor-input filter the output of which is applied to the 2A3 plates through T2. For the lower-level stages, additional filtering is provided by successive RC filters which also serve to prevent audio feedback through the plate supply.

Grid bias for the 2A3s is furnished by a separate supply using a small selenium rectifier and a TV "booster" transformer, T4. The bias may be adjusted by means of R_1 , and should be set to -62 volts or to obtain a total plate current of 80 ma. (as measured in the lead to the primary center tap of T_2) for the 2A3s.

In building an amplifier of this type the constructional precautions outlined earlier should be observed. The Class AB₁ modulators described subsequently in this chapter are representative of good constructional practice.

Negative Feedback

Whenever tetrodes or pentodes are used as drivers for Class B modulators, negative feedback should be used

in the driver stage, for the reason

already discussed.

Suitable circuits for single-ended and push-pull tetrodes are shown in Fig. 9-9. Fig. 9-9A shows resistance coupling between the preceding stage and a single tetrode, such as the 6V6, that operates at the same plate voltage as the preceding stage. Part of the a.f. voltage across the primary of the output transformer is fed back to the grid of the tetrode, V_2 , through the plate resistor of the preceding tube, V_1 . The total resistance of R_4 and R_5 in series should be ten or more times the rated load resistance of V_2 . Instead of the voltage divider, a tap on the transformer primary can be used to supply the feedback voltage, if such a tap is available.

The amount of feedback voltage that appears at the grid of tube V_2 is determined by R_1 , R_2 and the plate resistance of V_1 , as well as by the relationship between R_4 and R_5 . Circuit values for typical tube combinations are given in detail in Fig. 9-9.

The push-pull circuit in Fig. 9-9B requires an audio transformer with a split secondary. The feedback voltage is obtained from the plate of each output tube by means of the voltage divider, R_1 , R_2 . The blocking capacitor, C_1 , prevents the d.c. plate voltage from being applied to R_1 , R_2 ; the reactance of this capacitor should be low, compared with the sum of R_1 and R_2 , at the lowest audio frequency to be amplified. Also, the sum of R_1 and R_2 should be high (ten times or more) compared with the rated load resistance for V_2 and V_3 .

In this circuit the feedback voltage that is developed across R_2 appears at the grid of V_2 (or V_3) through the transformer secondary and grid-cathode circuit of the tube, provided the tubes are not driven to grid current. The per cent feedback is

$$n=\frac{R_2}{R_1+R_2}\times 100$$

where n is the feedback percentage, and R_1 and

 R_2 are connected as shown in the diagram. The higher the feedback percentage, the lower the effective plate resistance. However, if the percentage is made too high the preceding tube, V_1 , may not be able to develop enough voltage, through T_1 , to drive the push-pull stage to maximum output without itself generating harmonic distortion. Distortion in V_1 is not compensated for by the feedback circuit.

If V_2 and V_3 are 6L6s operated self-biased in Class AB_1 with a load resistance of 9000 ohms, V_1 is a 6J5 or similar triode, and T_1 has a turns ratio of 2-to-1, total secondary to primary, it is possible to use over 30 per cent feedback without going beyond the output-voltage capabilities of the triode. Twenty per cent feedback will reduce the effective plate resistance to the point where the output voltage regulation is better than that of 2A3s without feedback. The power output under these conditions is about 20 watts.

INCREASING THE EFFECTIVENESS OF THE PHONE TRANSMITTER

The effectiveness of an amateur phone transmitter can be increased to a considerable extent by taking advantage of speech characteristics. Measures that may be taken to make the modulation more effective include band compression (filtering), volume compression, and speech clipping.

Compressing the Frequency Band

Most of the intelligibility in speech is contained in the medium band of frequencies; that is, between about 500 and 2500 cycles. On the other hand, a large portion of speech power is normally found below 500 cycles. If these low frequencies are attenuated, the frequencies that carry most of the actual communication can be increased in amplitude without exceeding 100-per cent modulation, and the effectiveness of the transmitter is correspondingly increased.

One simple way to reduce low-frequency response is to use small values of coupling capacitance between resistance-coupled stages, as shown in Fig. 9-10A. A time constant of 0.0005 second for the coupling capacitor and following-stage grid resistor will have little effect on the amplification at 500 cycles, but will practically halve it at 100 cycles. In two cascaded stages the gain will be down about 5 db. at 200 cycles and 10 db. at 100 cycles. When the grid resistor is ½ megohm a coupling capacitor of 0.001 µf. will give the required time constant.

The high-frequency response can be reduced by using "tone control" methods, utilizing a capacitor in series with a variable resistor connected across an audio impedance at some point in the speech amplifier. The best spot for the tone control is across the primary of the output transformer of the speech amplifier, as in Fig. 9-10B. The capacitor should have a reactance at 1000 cycles about equal to the load resistance required by the amplifier tube or tubes, while the variable resistor in series may have a value equal to four

or five times the load resistance. The control can be adjusted while listening to the amplifier, the object being to cut the high-frequency response without unduly sacrificing intelligibility.

Restricting the frequency response not only puts more modulation power in the optimum frequency band but also reduces hum, because the low-frequency response is reduced, and helps reduce the width of the channel occupied by the transmission, because of the reduction in the amplitude of the high audio frequencies.

Volume Compression

Although it is obviously desirable to modulate the transmitter as completely as possible, it is

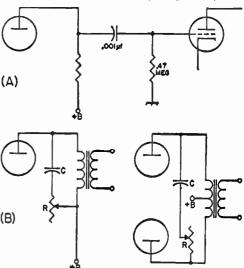


Fig. 9-10—A, use of a small coupling capacitor to reduce low-frequency response; B, tone-control circuits for reducing high-frequency response. Values for C and R are discussed in the text; 0.01 μ f, and 25,000 ohms are typical.

difficult to maintain constant voice intensity when speaking into the microphone. To overcome this variable output level, it is possible to use automatic gain control that follows the average (not instantaneous) variations in speech amplitude. This can be done by rectifying and filtering some of the audio output and applying the rectified and filtered d.c. to a control electrode in an early stage in the amplifier.

A practical circuit for this purpose is shown in Fig. 9-11. V1, a medium-# triode, has its grid connected in parallel with the grid of the last speech amplifier tube (the stage preceding the power stage) through the gain control R_1 . The amplified output is coupled to a full-wave rectifier, V2. The rectified audio output develops a negative d.c. voltage across C1R3, which has a sufficiently long time constant to hold the voltage at a reasonably steady value between syllables and words. The negative d.c. voltage is applied as control bias to the suppressor grid of the first tube in the speech amplifier (this circuit requires a pentode first stage), effecting a reduction in gain. The gain reduction is substantially proportional to the average microphone output and thus tends to hold the amplifier output at a constant level.

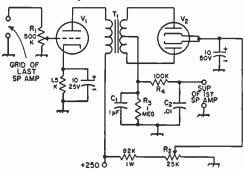


Fig. 9-11—Speech-amplifier output compression circuit.

V₁—6C4, 6C5, 6CG7, 6J5, 12AU7, etc. V₂—6H6, 6AL5, etc.

T₁—Interstage audio, single plate to p.p. grids.

An adjustable bias is applied to the cathodes of V_2 to cut off the tube at low levels and thus prevent rectification until a desired output level is reached. R_2 is the "threshold control" which sets this level. R_1 , the gain control, determines the rate at which the gain is reduced with increasing signal level.

The hold-in time can be increased by increasing the resistance of R_3 . C_2 and R_4 may not be necessary in all cases; their function is to prevent too-rapid gain reduction on a sudden voice peak. The "rise time" of this circuit can be increased by increasing C_2 or R_4 , or both.

The over-all gain of the system must be high enough so that full output can be secured at a moderately low voice level.

Speech Clipping and Filtering

In speech wave forms the average power content is considerably less than in a sine wave of the same peak amplitude. Since modulation per-

centage is based on peak values, the modulation or sideband power in a transmitter modulated 100 per cent by an ordinary voice wave form will be considerably less than the sideband power in the same transmitter modulated 100 per cent by a sine wave. In other words, the modulation percentage with voice wave forms is determined by peaks having relatively low average power content.

If the low-energy peaks are clipped off, the remaining wave form will have a considerably higher ratio of average power to peak amplitude. More sideband power will result, therefore, when such a clipped wave is used to modulate the transmitter 100 per cent. Although clipping distorts the wave form and the result therefore does not sound exactly like the original, it is possible to secure a worth-while increase in modulation power without sacrificing intelligibility. Once the system is properly adjusted it will be impossible to overmodulate the transmitter because the maximum output amplitude is fixed.

By itself, clipping generates the same highorder harmonics that overmodulation does, and therefore will cause splatter. To prevent this, the audio frequencies above those needed for intelligible speech must be filtered out, after clipping and before modulation. The filter required for this purpose should have relatively little attenuation at frequencies below about 2500 cycles, but high attenuation for all frequencies above 3000 cycles.

It is possible to use as much as 25 db. of clipping before intelligibility suffers; that is, if the original peak amplitude is 10 volts, the signal can be clipped to such an extent that the resulting maximum amplitude is less than one volt. If the original 10-volt signal represented the amplitude that caused 100-per-cent modulation on peaks, the clipped and filtered signal can then be amplified up to the same 10-volt peak level for modulating the transmitter.

There is a loss in naturalness with "deep" clipping, even though the voice is highly intelligible. With moderate clipping levels (6 to 12 db.) there is almost no change in "quality" but the voice power is increased considerably.

Before drastic clipping can be used, the speech signal must be amplified several times more than is necessary for normal modulation. Also, the hum and noise must be much lower than the tolerable level in ordinary amplification, because the noise in the output of the amplifier increases in proportion to the gain.

One type of clipper-filter system is shown in Fig. 9-12. The clipper is a peak-limiting rectifier of the same general type that is used in receiver noise limiters. It must clip both positive and negative peaks. The gain or clipping control sets the amplitude at which clipping starts. Following the low-pass filter for eliminating the harmonic distortion frequencies is a second gain control, the "level" or modulation control. This control is set initially so that the amplitude-limited output of the clipper-filter cannot cause more than 100 per cent modulation.

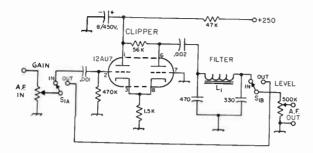


Fig. 9-12—Practical speech clipper circuit with law-pass filter. Capacitances belaw 0.001 μ f. are in $\mu\mu$ f. Resistars are ½ watt. L₁—20 henrys, 900 ahms (Stancar C-1515). S₁—D.p.d.1. taggle ar ratary.

It should be noted that the peak amplitude of the audio wave form actually applied to the modulated stage in the transmitter is not necessarily held at the same relative level as the peak amplitude of the signal coming out of the clipper stage. When the clipped signal goes through the filter, the relative phases of the various frequency components that pass through the filter are shifted, particularly those components near the cut-off frequency. This may cause the peak amplitude out of the filter to exceed the peak amplitude of the clipped signal applied to the filter input terminals. Similar phase shifts can occur in amplifiers following the filter, especially if these amplifiers, including the modulator, do not have good low-frequency response. With poor low-frequency response the more-or-less "square" waves resulting from clipping tend to be changed into triangular waves having higher peak amplitude. Best practice is to cut the lowfrequency response before clipping and to make all amplifiers following the clipper-filter as flat and distortion-free as possible.

The best way to set the modulation control in such a system is to check the actual modulation percentage with an oscilloscope connected as described in the section on modulation. With the gain control set to give a desired clipping level with normal voice intensity, the level control should be adjusted so that the maximum modulation does not exceed 100 per cent no matter how much sound is applied to the microphone.

The practical clipper-filter circuit shown in Fig. 9-12 may be inserted between two speech-amplifier stages (but after the one having the gain control) where the level is normally a few volts. The cathode-coupled clipper circuit gives some over-all voltage gain in addition to performing the clipping function. The filter constants are such as to give a cut-off characteristic that combines reasonably good fidelity with adequate high-frequency suppression.

High-Level Clipping and Filtering

Clipping and filtering also can be done at high level—that is, at the point where the modulation is applied to the r.f. amplifier—instead of in the lowlevel stages of the speech amplifier. In one rather simple but effective arrangement of this type the clipping takes place in the Class-B modulator itself. This is accomplished by carefully adjusting the plate-to-plate load resistance for the

modulator tubes so that they saturate or clip peaks at the amplitude level that represents 100 per cent modulation. The load adjustment can be made by choice of output transformer ratio or by adjusting the plate-voltage/plate-current ratio of the modulated r.f. amplifier. It is best done by examining the output wave form with an oscilloscope.

The filter for such a system consists of a choke coil and capacitors as shown in Fig. 9-13. The values of L and C should be chosen to form a low-pass filter section having a cut-off frequency of about 2500 cycles, using the modulating impedance of the r.f. amplifier as the load resistance. For this cut-off frequency the formulas are

$$L_1 = \frac{R}{7850}$$
 and $C_1 = C_2 = \frac{63.6}{R}$

where R is in ohms, L_1 in henrys, and C_1 and C_2 in microfarads. For example, with a plate-modulated amplifier operating at 1500 volts and 200 ma. (modulating impedance 7500 ohms) L_1 would be 7500/7850 = 0.96 henry and C_1 or C_2 would be 63.6/7500 = 0.0085 μ f. Bypass capacitors in the plate circuit of the r.f. amplifier should be included in C_2 . Voltage ratings for C_1 and C_2 when connected as shown must be the same as for the plate blocking capacitor — i.e., at least twice the d.c. voltage applied to the plate of the modulated amplifier. L and C values can vary 10 per cent or so without seriously affecting the operation of the filter.

Besides simplicity, the high-level system has the advantage that high-frequency components

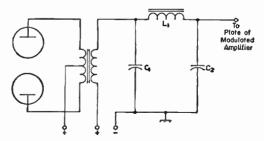


Fig. 9-13—Splatter-suppression filter for use at high level, shown here cannected between a Class B madulatar and plate-madulated r.f. amplifier. Values for L_1 , C_1 and C_2 are determined as described in the text.

A Low-Power Modulator

of the audio signal fed to the modulator grids, whether present legitimately or as a result of amplitude distortion in lower-level stages, are suppressed along with the distortion components that arise in clipping. Also, the undesirable effects of poor low-frequency response following clipping and filtering, mentioned in the preceding

section, are avoided. Phase shifts can still occur in the high-level filter, however, so adjustments preferably should be made by using an oscilloscope to check the actual modulation percentage under all conditions of speech intensity. (For further discussion see Bruene, "High-Level Clipping and Filtering," *QST*, November, 1951.)

A LOW-POWER MODULATOR

A modulator suitable for plate modulation of low-power transmitters or for screen or controlgrid modulation of high-power amplifiers is pictured in Figs. 9-14 and 9-16. As shown in Fig. 9-15, it uses a pair of Class A₁ 6AQ5's in pushpull in the output stage. These are driven by a 6C4 phase inverter. A two-stage preamplifier using a 12AX7 brings the output voltage of a crystal or ceramic microphone up to the proper level for the 6C4 grid. A power supply is included on the same chassis.

The undistorted audio output of the amplifier is 7-8 watts. This is sufficient for modulating the plate of an r.f. amplifier running 10 to 15 watts input, or for modulating the control grids or screens of r.f. amplifiers using tubes having plate-dissipation ratings up to 250 watts. When screen modulation is used the screen power for the modulated amplifier (up to 250 volts) can be taken from the modulator power supply. The wiring shown in Fig. 9-15 provides for this, through an adjustable tap on the 25,000-ohm bleeder resistor, R_5 , in the power supply. If a separate screen supply is used, or if the modulator is used for grid-bias or plate modulation of an r.f. amplifier, the d.c. circuit should be opened at point "X" in Fig. 9-15.

The amplifier uses resistance coupling up to the output-stage grids. The first section, V_{1A} , of the 12AX7 has "contact-potential" bias. The gain control, R_1 , is in the grid circuit of the second section, V_{1B} , of the 12AX7. Negative feedback from the secondary of the output transformer, T_1 , is introduced at the cathode of this tube section. The feedback voltage is dependent on the

ratio of R_2 to R_3 , approximately, and with the constants given is sufficient to result in a considerable reduction in distortion along with improved regulation of the audio output voltage. The latter is important when the unit is used for modulating a screen or control grid, as described in the chapter on amplitude modulation.


The phase inverter is of the split-load type described earlier in this chapter. It drives the push-pull 6AQ5's in the power amplifier. The output transformer used in the power stage is a multitap modulation transformer suitable for any of the types of modulation mentioned above.

Capacitor C_1 across the secondary of the output transformer, T_1 , is used to reduce the high-frequency response of the amplifier. Without it, self-oscillation is likely to occur at a high audio frequency (usually above audibility) because phase shift in the output transformer at the end of its useful frequency range causes the feedback to become positive.

The power supply uses a replacement-type transformer and choke with a capacitor-input filter. Voltage under the modulator and speechamplifier load is 250. The decoupling resistance-capacitance networks in the plate circuits of V_{1A} and V_{1B} contribute additional smoothing of the d.c. for these low-level stages.

The unit includes provision for send-receive switching, S_1 being used for that purpose. S_{1B} can be used to control the r.f. section — for example, by being connected in parallel with the key used for c.w. operation. Simultaneously S_{1A} short-circuits the secondary of T_1 so the transformer will not be damaged by being left without

Fig. 9-14—Speech amplifier and low-power modulator suitable for screen or control-grid modulation of high-power amplifiers, or for plate modulation of an r.f. stage with up to 15 watts plate input. It is assembled on a 7 × 9 × 2-inch steel chossis, with the power supply occupying the left-hand section and the audio circuits the right. The 12AX7 preamplifier is at the lower right-hand corner, the 6C4 phase inverter is to its left, and the 6AQ5 power amplifiers are behind the two. Controls along the chassis edge are, left to right, the power switch, send-receive switch, gain control, and microphone jack.

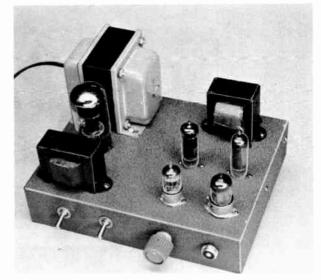

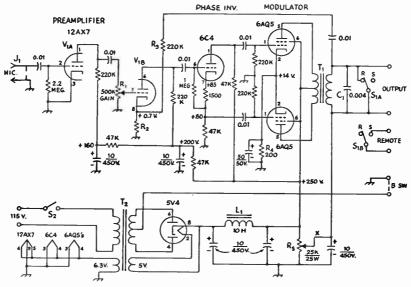


Fig. 9-15—Circuit of the speech amplifier and modulator. All capacitances are in μf .; capacitors with polarities marked are electrolytic, others are ceramic. Resistors are $\frac{1}{2}$ watt except as noted below. Voltages measured to chassis with v.t. voltameter.

J1-Microphone connector (Amphenol 75-PC1M).

L₁-10 henrys, 90 ma. (Triad C-7X).

S₁-D.p.d.t. toggle.

S₂-S.p.s.t. toggle.

T₁-Modulation transformer, tapped secondary, primary 10,000 ohms plate to plate (Thordar-

load. If S_{1B} is connected across the transmitter key, S_1 also can be used as a phone-c.w. switch, being left in the "R" position for c.w. operation.

The terminals marked "B Switch" should be short circuited (indicated by the dashed line) if S_1 is used as a send-receive switch. If a switch on the transmitter is used for send-receive, these terminals may be used for turning the plate voltage in the modulator on and off through an extra pair of contacts on the transmitter send-receive

son 21M68).


T₂—Power transformer, 525 v.c.t., 90 ma.; 6.3 v., 5 amp.; 5 v., 2 amp. (Triad R-10A).

 $R_2{-}1500~\text{ohms,}~1\!\!/_{\!2}~\text{watt.}$

R₄—App. 200 ohms, 2 watts (two 390-ohm 1-watt resistors in parallel).

switch. In that case S_1 should be left in the "send" position for phone operation.

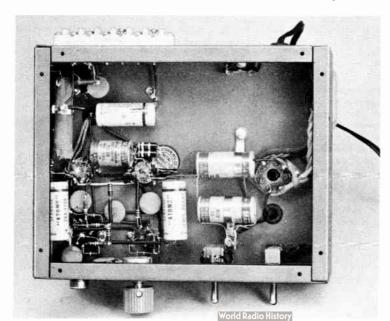The proper secondary taps to use on T_1 will depend on the impedance of the load to which the amplifier is connected. Methods for determining the modulating impedance with various types of modulation are given in the section on amplitude modulation, together with information on connecting the modulator to the r.f. stage.



9-16—Below-chassis Fia. view of the modulator. The rectifier tube socket and electrolytic filter capacitors are at the right in this view. The 12AX7 socket is at the lower left. Bleeder resistor R5 is at the upper left, near the 6-terminal connection strip on the rear edge of the chassis. Placement of components is not critical, but the leads in the first two stages should be kept short and close to the chassis to minimize hum troubles.

A 25-WATT MODULATOR USING PUSH-PULL 6BQ6GTs

The speech amplifier-modulator shown in Figs. 9-17 to 9-19, inclusive, can be used for plate modulation of low-power transmitters running 25 to 50 watts input to the final stage. The circuit as shown is capable of an audio output of 25 watts, but this can be increased to 30 watts by a simple modification. The 6BQ6s in the output stage are operated in Class AB₁. Inexpensive receiver-type replacement components are used throughout, except for the modulation transformer.

The speech amplifier uses a pentode first stage resistance-coupled to a triode second stage. This combination gives sufficient gain for a crystal microphone. The pentode and triode are the two sections of a dual tube, the 6AN8. Transformer coupling is used between the triode and the modulator tubes, in order to get push-pull voltage for the 6BQ6GT grids. Cathode bias is used on the final stage.

The coupling capacitance between the first and second stages is purposely made small to reduce the low-frequency response, and the primary of the output transformer is shunted by C_2 to reduce the amplification at the high-frequency end. C_1 , on the first stage, also tends to reduce high-frequency response in addition to bypassing any r.f. that might be picked up on the microphone cord. These measures confine the frequency response to the most useful portion of the voice range.

 S_2 is the "send-receive" switch. One section opens the power transformer center tap, thus cutting off the plate voltage during receiving periods. The other section can be connected to the key terminals on the transmitter, as indicated in the circuit diagram, to turn the transmitter on and off along with the modulator. If the transmitter is one in which the oscillator is not keyed, S_{2B} may be used to control the trans-

mitter plate voltage, usually by being connected in the 115-volt circuit to the plate-supply transformer.

The "phone-c.w." switch, S_3 , short-circuits the secondary of the modulation transformer, T_3 , when the transmitter is to be keyed, and also opens the center-tap of T_1 so plate voltage cannot be applied to the modulator.

The power supply uses a receiver replacement-type transformer with a capacitor-input filter. Additional filtering for the speech-amplifier stages is provided by the 10-µf. capacitors and the series resistors in the plate circuits. Hum is also reduced by the VR-150 used to regulate the modulator screen voltage. Note that the regulator tube is connected between the screens and cathodes so that the actual screen voltage is 150 and is not reduced by the drop in the cathode bias resistor. Maintaining full screen voltage is important if the rated output is to be secured.


Operating

The 6BQ6GT amplifier requires a plate-to-plate load of 4000 ohms, and the output transformer ratio must be chosen to reflect this load to the plates (see later section on matching a modulator to its load). For most small transmitters running 30 to 50 watts input to the final stage a 1-to-1 transformer ratio will be satisfactory, since the modulating impedance of such transmitters usually is in the neighborhood of 4000 ohms. The secondary of T_3 is connected in series with the d.c. lead to the plate (and screen, if a screen-grid tube) of the Class C amplifier to be modulated. For further details, see the chapter on amplitude modulation.

For checking the modulator operation a milliammeter (0-200 range satisfactory) may be connected in the lead to the center-tap of the primary of T_3 . Without voice input to the microphone the plate current should be approximately

Fig. 9-17—A madulator for transmitters aperating at plate inputs up to 50 watts. The speech amplifier and modulatar are at the left in this view; pawer supply camponents are at the right. The chassis is $7\times11\times2$ inches.



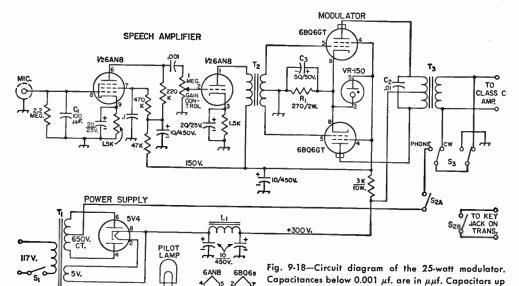

L₁--8 henrys, 150 ma.

S₁-S.p.s.t. toggle.

S2-D.p.d.t. toggle.

S₈-2-pole 2-position rotary (Centralab PA-2003).

 \mathcal{A}

T₁-Power transformer, 650 volts c.t., 150 ma. 5 volts 3 amp.; 6.3 volts, 5 amp.

to 0.01 μf . are ceramic. Resistors are $\frac{1}{2}$ watt unless

otherwise specified.

T₂—Interstage audio, single plate to p.p. grids, pri, to total sec. ratio 1 to 3.

T₈—Modulation transformer, multimatch type (UTC S-19).

50 ma. When modulating the transmitter, the current should "kick" to 60 or 70 ma.; this will usually represent 100 per cent modulation. If the amplifier can be tested with a single-tone signal replacing the microphone, the plate current will be about 165 ma. at full output.

The audio power output can be increased to about 30 watts, sufficient for modulating an 807

at its full phone rating, if the 6BQ6GT cathodes are grounded and bias of about 30 volts from a fixed source such as a small battery is applied to the grids. The battery may be substituted for the cathode resistor if the ground connection is moved from the center tap of the secondary of T_2 to the cathodes of the 6BQ6GTs.

(From QST, December, 1955.)

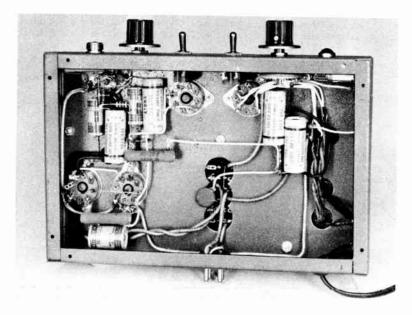


Fig. 9-19-Underchassis view of the 6BQ6GT modulator. The two large capacitors at the right are the filter capacitors in the power supply. The modulator bias resistor and bypass capacitor (R_1C_3) are at lower left. Leads from the modulation transformer go through the three holes in the chassis. Shielded wire is used for heater, microphone input, and gaincontrol leads.

A 50-WATT CLASS AB1 MODULATOR

Four type 1625 tubes were used in the output stage of the modulator shown in Figs. 9-20 and 9-22 for several good reasons. These tubes, 12-volt heater versions of the popular 807, are widely available on the surplus market at attractive prices. With the economical power supply shown here, four 1625s will deliver up to 50 watts of audio, sufficient to modulate a 100-watt transmitter. At higher plate voltages, four 1625s in Class AB₁ will furnish up to 140 watts (at 750 plate volts), sufficient to modulate a 280-watt transmitter.

Referring to the circuit diagram, the speech amplifier consists of a 6AV6 triode and the two triodes of a 6CG7. Transformer coupling between V_{1B} and the modulator tubes gives adequate signal for the 1625s at any rated plate voltage. A built-in bias supply, using a voltage-tripling circuit and selenium rectifiers CR_1 , CR_2 and CR_3 , furnishes operating bias that can be set to the proper value by R_2 . During standby conditions, the modulator is turned off by opening the circuit at J_3 or by adding additional bias through

 J_4 . Since connecting four tetrodes in push-pull parallel can often yield parasitic oscillations, resistors are connected in both control and screen grid circuits of the modulator tubes. With these resistors present, there should be no instabilities of any kind. The low- and high-frequency responses are restricted to good communications levels by proper proportioning of the coupling capacitors and the shunt capacitors. The 0.004- μ f, capacitor across the secondary of T_2 will have a greater effect on restricting high-frequency response if a high-voltage low-current amplifier is being modulated than if a low-voltage high-current r.f. stage is used. The 0.004- μ f, value was selected for use with a 400-volt 200-ma, amplifier.

Provision for connecting an external modulation monitor (see Chapter 10) is included, as well as a power outlet, J_5 , for the monitor or other auxiliary equipment.

Construction

The modulator is built on a $17 \times 10 \times 3$ -inch steel chassis, although an aluminum chassis would



Fig. 9-20—A 50-watt modulator, using four 1625-type tubes in Class AB₁. With higher plate voltage and a larger modulation transformer, the tubes can deliver up to 140 watts of audio power.

Speech amplifier tubes and coupling transformer are at the right, in front of the four 1625s. The two voltage-regulator tubes in the center, in front of the modulation transformer, stabilize the screen voltage on the 1625s.

Power-supply filter choke is at the upper left-hand corner, and the small choke to the immediate right is connected in the screen circuit if a screen-grid r.f. amplifier is used. If desired, a cane-metal housing can be used over the modulator, but the use of high-voltage wire and insulated plate caps practically eliminates the danger of electrical shock when the unit is in its normal position.

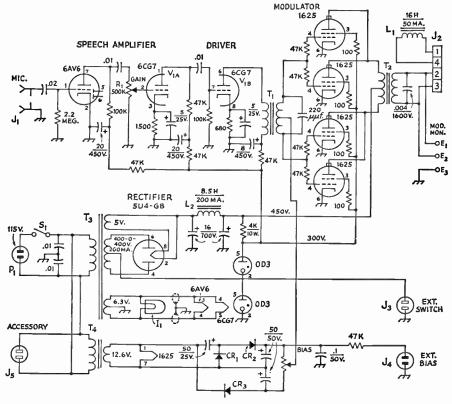


Fig. 9-21—Circuit diagram of the 50-watt modulator. Unless specified otherwise, capacitances are in μf., resistors are ½ watt.

 $C_1-0.004$ μ f., but subject to modification. See text. CR₁, CR₂, CR₃-20-ma. 130-v. selenium rectifier. E₁, E₂, E₃-Nylon tip jacks (Johnson 105-601, 105-602 105-603).

1,-6.3-volt pilot lamp.

 J_1 -Microphone connector (Amphenol 75-PC1M), J_2 -4-prong tube socket.

J₃, J₅—2-pin chassis-mounting a.c. receptacle (Amphenol 61-F1).

J₄—Phono jack.

L₁—Screen choke, used when modulating tetrode amplifier.

probably be almost as strong and would be definitely easier to drill and punch. The components were arranged to keep a.c. leads a reasonable distance away from the speech-amplifier circuits, and the heater leads to the 6AV6 and 6CG7 were run in shielded wire. These shielded leads, and the shielded leads carrying 115 v. a. c., were run along the folded corners of the chassis. Another precaution in wiring the modulator is to keep the leads to and from T_2 away from the speech-amplifier portion of the modulator, to reduce the chances for feedback and consequent audio oscillation. The leads to and from T_2 should be made with well-insulated wire, and wherever they pass through the chassis rubber grommets should be used.

The connections to T_2 will depend upon the voltage-to-current ratio of the d.c. input to the

L₂-8.5-henry 200-ma. filter choke (Knight 61 G 409 or equiv.).

P1-A.c. line plug.

R₁-Volume control, audio taper.

R2-2-watt wire-wound control, linear taper.

S1-S.p.s.t. toggle switch.

 $T_1-1:3$ ratio interstage transformer (Triad A-31X).

 T_2 —60-watt modulation transformer (Stancor A-3893), T_8 —400-0-400 v, at 200 ma., 5 v. at 3 a., 6.3 v. at

5 a (Knight 61 G 414 or equiv.). T₄—12.6 v. at 2 a. (Knight 61 G 420 or equiv.).

modulated stage. With the power supply shown, the modulator is well suited to work with the 75-watt 6DQ5 transmitter and the 90-watt allpurpose amplifier described in Chapter Six. The proper load for the four 1625s, with 450 volts on the plates, is 3800 ohms, rising to 6000 ohms with 750 volts on the plates. An instruction sheet is furnished with the transformer; to determine the transformer taps to be used, first measure the plate voltage and current of the modulated stage. Divide the voltage by the current in amperes, to determine the secondary load, and from the instruction sheet select the connections that come closest to matching the secondary load to 3800 ohms. Although it is not likely that an exact match will be possible, it is of little or no consequence. The ratio of the impedance is the important consideration.

Operation

When the modulator is completed, connect a key or other external switch temporarily at J_3 , and short-circuit J_4 . Plug P_1 into an a.c. outlet, plug in the 5U4-GB and the 0D3s, and turn on S_1 . The filament of the 5U4-GB should glow. Close the key or switch at J_3 ; the 0D3s should light. Open the external switch and plug in the speech amplifier tubes. After allowing time for the 6AV6 and 6CG7 to warm up, as indicated by the heater glow, turn on the external switch and turn off S_1 . Allow a half minute for the filter capacitors to be discharged by the speech amplifier tubes, and then check with a voltmeter that no charge is left in the filter. Open the external switch, plug in the 1625s, and close S_1 . After the heaters warm up, set the arm of R2 to give a voltage of -32 between arm and chassis. Connect the transmitter or a dummy load to the modulator output (never operate the modulator without a load; the modulation transformer insulation may break down). Set the volume control at minimum (arm of R_1 at chassis end) and close J_3 . With a microphone connected at J_1 , speaking into the mike and slowly opening R_1 should deliver audio output from the modulator.

To obtain more power from the four 1625s, it is necessary to use a higher-powered modulation transformer at T_2 and to raise the plate voltage and grid bias. At 750 volts on the plates, the bias should be -35 volts.

The modulator should be turned on and off with the transmitter, so that a load is always furnished for the transformer. The modulator can be placed on standby by opening the circuit at J_3 , or by adding additional negative voltage at J_4 , depending upon the basic station control circuitry.

If a number of 1625s are available, it is desirable to select four that have substantially the same plate current (28 ma.) for the -32 volts bias. The plate currents of the individual tubes can be measured between insulating plate cap and the tube plate cap, connecting the + terminal of the milliammeter to the transformer lead. Turn off the equipment between measurements to avoid the possibility of a dangerous electrical shock.

As with any modulator using an output transformer, the secondary winding should be short-circuited (or the modulator disconnected) when the r.f. amplifier is used for c.w. or as a linear amplifier.

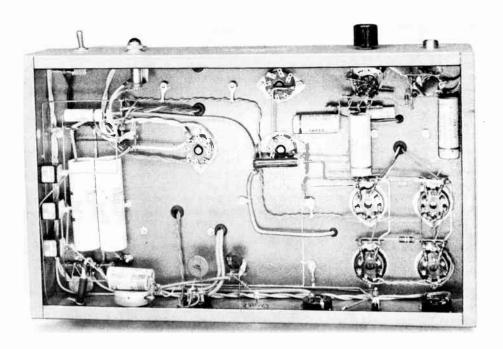


Fig. 9-22—Under the chassis of the 50-watt modulator. Three selenium rectifiers in the bias supply are mounted on the left-hand wall of the chassis. Associated components are grouped around the speech-amplifier sockets (upper right).

Components mounted on the rear apron of the chassis, from left to right, are bias potentiometer, audio power socket J_2 , external bias connection J_4 , external switch connection J_3 , modulation monitor terminals E_1 , E_2 and E_3 , and the accessory socket J_5 .

Shielded wire is used on 60-cycle a.c. leads in the power transformer primaries and secondaries to reduce the possibility of hum pick-up in the speech amplifier section.

A 6146 MODULATOR AND SPEECH AMPLIFIER

The modulator shown in Figs. 9-23 to 9-25, inclusive, uses a pair of 6146s in AB_1 , and is complete with power and bias supplies on a $10 \times 17 \times 3$ -inch chassis. The modulator also is equipped with an audio take-off for scope monitoring.

The audio power that can be obtained (based on measurements) is as follows:

Nominal Plate Voltage	Plate-tp-Plate Load Resistance			
500 volts	75 watts	4200 ohms		
600 volts	95 watts	5200 ohms		
750 volts	120 watts	6700 ohms		

Suitable sets of components for all three of the voltages listed above are readily available, so the power level can be selected to suit the Class C amplifier to be modulated. The modulator shown in the photographs is set up for 750-volt operation, but aside from the power and modulation transformers all components are the same regardless of the voltage level.

Audio Circuits

As shown in the circuit diagram, Fig. 9-24, the audio system consists of a 12AX7 preamplifier with the two tube sections in cascade, followed by a 6C4 voltage amplifier which is transformer-coupled to the grids of the Class AB_1 modulator tubes. The combination provides ample gain for a communications-type crystal, ceramic, or dynamic microphone.

The first stage of the amplifier is "contact-potential" biased, and is resistance-coupled to the second stage. The gain control, R_1 , is in the grid circuit of the second stage. Decoupling resistors and capacitors are included in the plate-supply circuits of these two stages; these decoupling circuits also provide additional plate-supply hum filtering for the two low-level stages.

The secondary of T_1 , the transformer coupling the third speech stage to the modulator grids, is shunted by a 470- $\mu\mu$ f. capacitor to reduce high-

frequency response. The optimum value of capacitance will depend on the particular type of audio transformer selected, as well as on the high-frequency characteristics of the microphone employed. Different values should be tried, to reduce the high-frequency response as much as possible, consistent with intelligibility.


The modulation transformer is of the multimatch type, and the taps should be selected to reflect the proper plate-to-plate load impedance, as given earlier, for the desired power output. The impedance ratio, secondary to primary, will depend on the modulating impedance of the modulated r.f. amplifier, as described earlier in this chapter. The secondary of the modulation transformer is shunted by C_1 to reduce output at the higher audio frequencies, particularly for attenuating high-frequency harmonics that might be generated in the modulator at high output levels. The value suggested (0.005 μ f.) is an average figure and should be modified according to the modulating impedance of the Class-C stage as discussed earlier in this chapter.

Power Supply

Plate power for all tubes in the unit is supplied by a single power transformer. Mercury-vapor rectifiers are used because good voltage regulation is desirable. The filter is a single section with choke input and a large (over 25 \(mu f.\)) output capacitance. The filter capacitor consists of three 80-\(mu f.\) 450-volt electrolytic capacitors in series for 750-volt d.c. output. If the output voltage is 600 or less only two capacitors in series will be needed. These capacitors are shunted by 0.1-megohm resistors to help equalize the d.c. voltages across them.

The 200-volt (approximately) supply for the 6146 screens and the plates of the speech-amplifier tubes is taken from the main supply through a dropping resistor, and is regulated by two 0B2 voltage-regulator tubes in series. A 20-µf. capacitor is connected across the VR tubes to im-

Fig. 9-23—Class-AB₁ modulator using 6146s, complete with speech amplifier and pawer supply. The relay-rack panel is 101/2-inches high. Plate- and filament-supply primary switches, each with its awn pilot lamp, are near the lower edge of the panel. The gain control is at lower center. Along the front of the chassis, just behind the panel, are the plate pawer transformer, filter choke, and modulatian transfarmer, gaing fram left to right. The tubes at the left are the 816 rectifiers, with the 6146s at the right. Along the rear edge are the twa voltageregulatar tubes, the 12AX7 and 6C4 speech amplifier tubes, and the interstage audia transfarmer, T1.

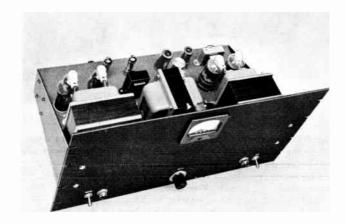

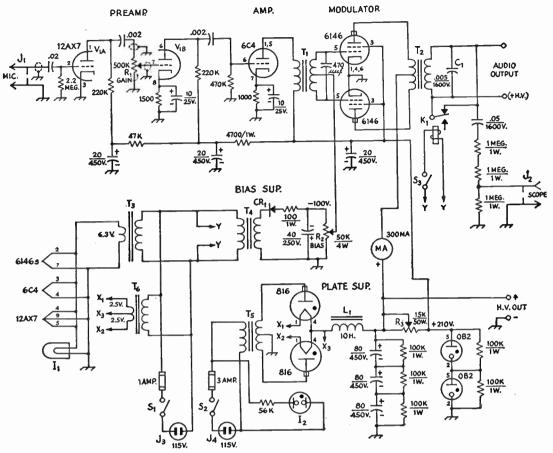


Fig. 9-24—Circuit diagram of the 6146 modulator and power supply. Capacitances are in μ f. unless indicated otherwise; capacitors marked with polarity are electrolytic, others may be paper or ceramic as convenient.

Resistances are in ohms; resistors are $\frac{1}{2}$ watt except as indicated.

C₁-See text.

CR₁-Selenium rectifier, 20 ma. or higher, 130 volts.

1,-6.3-volt pilot lamp.

1₂-Neon lamp, NE-51.

J₁-Microphone connector (Amphenol 75-PC1M).

J₂-Phono jack.

J₅, J₆—115-volt chassis-mounting plug (Amphenol 61-M1).

K₁—Antenna changeover relay, 115-volt coil (Advance AH/2C/115VA; type AM also suitable).

L₁-Filter choke, 10 henrys, 300 ma. (Triad C-19A).

R₁-0.5-megohm control, audio taper.

 R_2 -50,000-ohm wire-wound control, 4 watts.

R₃-15,000-ohm adjustable, 50 watts.

S₁, S₂—S.p.s.t. toggle.

S3-S.p.s.t. mounted on R1.

prove the dynamic regulation in the 6146 screen circuit, since the peak instantaneous screen current exceeds the regulating capacity (30 ma.) of the VR tubes when the modulator is driven to maximum output.

Fixed bias for the 6146 grids is taken from a built-in bias supply using a TV "booster" transformer with a selenium rectifier. This bias is

T₁—Interstage audio, single plate to p.p. grids, 3-to-1 secondary-to-primary ratio (Stancor A-63-C). T₂—Multimatch modulation transformer, 125 watts

(Triad M-12AL). T_s—Filament transformer, 6.3 volts at 4 amp. (Triad

F-53X).

T₄—Power transformer, 117 volts at 20 ma.; 6.3-volt winding unused (Thordarson 26R32).

T₈—Plate transformer. For 500 volts d.c.: 1235 volts c.t., 310 ma. (Triad P-7A); for 600 volts d.c.: 1455 volts c.t., 310 ma (Triad P-11A). Transformer shown is for either 600 or 750 volts d.c. output at 310 ma.; sec. voltage 1780 c.t. for 750 volts (Triad P-14A).

Te-Filament transformer, 5 volts at 3 amp., 2500-volt insulation (Stancor P-4088).

adjustable by means of R_2 . The bias supply and filament transformer are on the same a.c. circuit so that bias is applied to the modulator grids whenever the tube heaters are energized.

Control and Auxiliary Circuits

The modulator includes an oscilloscope takeoff circuit consisting of the 0.05-µf. capacitor and

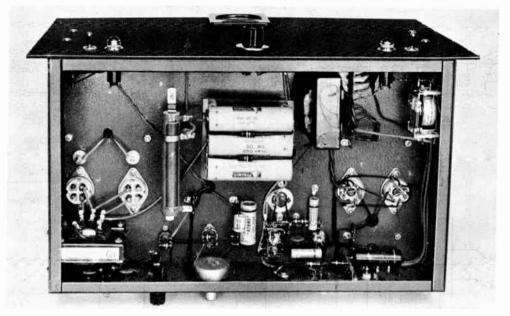


Fig. 9-25—Below-chassis view of the 6146 modulator. The 816 sockets and filament transformer (T_6) are at the lower left. The chassis wall at the bottom has on it, left to right, the 115-volt a.c. plugs, fuse holders, bias control (R_2), microphone input connector (J_1), scope take-off connector (J_2) and a three-terminal strip (Millen 37303) for audio output and positive high voltage connections. The high-voltage filter capacitor bank is in the center, mounted on a plate of plastic insulation which is supported away from the chassis on small pillars. The 6.3-volt transformer (T_2) is to the right of the capacitors. The antenna changeover relay used for shorting the modulation-transformer secondary is on the right-hand chassis wall,

three 1-megohm resistors in series. This can be used for horizontal deflection of a c.r. tube to give the trapezoidal modulation pattern (see chapter on amplitude modulation). Usually, it will be necessary to use an external control for adjusting the amplitude of the sweep voltage so obtained. If desired, a 1-megohm control can be substituted for the fixed resistor at the bottom of the string, thus avoiding the necessity for an external control.

The normally closed contacts of an antennatype relay, K_1 , are used to short-circuit the secondary of the modulation transformer when the transmitter is to be used for c.w. work. The switch, S_3 , that controls the relay is mounted on the gain control, R_1 , so that when the gain is turned all the way off, thus opening the switch, the relay contacts close. This insures that the modulator is inoperative and cannot be driven by accidental voice input (which would result in excessive plate current) when the transformer secondary is short-circuited.

Separate a.c. inputs are provided for the filament-bias and plate power circuits. The plate supply can thus be controlled by an external switch without disturbing the operation of the filament circuits or requiring a modification of the 115-volt wiring.

Terminals are provided for taking out highvoltage d.c. for an external unit. The powersupply equipment has more capacity than is needed by the modulator unit itself (the rating for amateur-type service is somewhat over 300 ma.) and may in some cases be sufficient for operation of the modulated r.f. amplifier as well. At least 200 ma, should be available for this purpose, since the average plate-supply current in the modulator unit alone is less than 100 ma., including the speech-amplifier and VR-tube drain.

Operating Data

The dropping resistor in the screen-supply circuit should be adjusted so that the current through 0B2s is 30 ma. with the bias on the 6146 grids adjusted so that the no-signal plate current is approximately 50 ma. The current through the VR tubes may be measured by opening the lead to the upper 0B2 at pin 5 and inserting a milliammeter of appropriate range.

If a sine-wave signal is used for testing the modulator, full output should be secured with a modulator plate current of approximately 240 ma. This value will be the same for all plate voltages, provided the screen voltage is maintained at approximately 200 volts and the values of plate-to-plate load resistance as specified earlier are used. With voice input the plate current will kick up to about 100 ma. on peaks, depending on the characteristics of the speaker's voice and those of the microphone used. This peak value should be determined under actual operating conditions with an oscilloscope, after which the plate milliammeter can be used as a modulation indicator.

CLASS B MODULATOR WITH FILTER

Representative Class B modulator construction is illustrated by the unit shown in Figs. 9-26 and 9-28. This modulator includes a splatter



Fig. 9-26—A typical Class B modulator arrangement. This unit uses a pair of 811As, capable of an audio power output of 340 watts, and includes a splatter filter. The modulation transformer is at the left and the splatter choke at the right. All high-voltage terminals are covered so they cannot be touched accidentally.

filter, $C_1C_2L_1$ in the circuit diagram, Fig. 9-27, and also has provision for short-circuiting the modulation transformer secondary when c.w. is to be used.

The audio input transformer is not built into

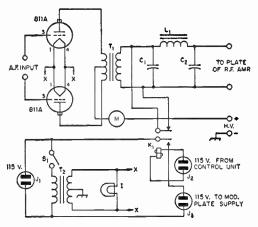


Fig. 9-27—Circuit diagram of the Class B modulator. C₁, C₂, L_1 —See text. (L_1 is Chicago Transformer type SR-300).

K₁—D.p.d.t. relay, high-voltage insulation (Advance type 400).

M-0-500 d.c. milliammeter, bakelite case.
T₁-Variable-ratio modulation transformer (Chicago
Transformer type CMS-1).

T₂-Filament transformer, 6.3 v., 8 omp. 1₁-6.3-volt pilot light.

 X_1 , X_2 —Chassis-type 115-volt plugs, male. X_3 —Chassis-type 115-volt receptacle, female.

S₁-S.p.s.t. toggle.

this unit, it being assumed that this transformer will be included in the driver assembly as is customary. If the modulator and speech amplifier-driver are mounted in the same rack or cabinet, the length of leads from the driver to the modulator grids presents no problem. The bias required by the modulator tubes at their higher plate-voltage ratings should be fed through the center tap on the secondary of the driver transformer. At a plate voltage of 1250 or less no bias is needed and the center-tap connection on the transformer can be grounded.

The values of C_1 , C_2 and L_1 depend on the modulating impedance of the Class C r.f. amplifier. They can be determined from the formulas given in this chapter in the section on high-level clipping and filtering. The splatter filter will be effective regardless of whether the modulator operating conditions are chosen to give high-level clipping, but it is worth while to design the system for clipping at 100 per cent modulation if the tube curves are available for that purpose. The voltage ratings for C_1 and C_2 should at least equal the d.c. voltage applied to the modulated r.f. amplifier.

A relay with high-voltage insulation is used to short-circuit the secondary of T_1 when the

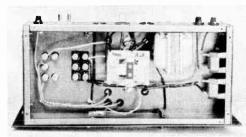


Fig. 9-28—The relay and filament transformer are mounted below the chassis. C₁, C₂ and K₁ are mounted on small stand-off insulators.

relay coil is not energized. A normally closed contact is used for this purpose. The other arm is used to close the primary circuit of the modulator plate supply when the relay is energized. Shorting the transformer secondary is necessary when the r.f. amplifier is keyed, to prevent an inductive discharge from the transformer winding that would put "tails" on the keyed characters and, with cathode keying of the amplifier, would cause excessive sparking at the key contacts. The control circuit should be arranged in such a way that K_1 is not energized during c.w. operation but is energized by the send-receive switch during phone operation.

Careful attention should be paid to insulation since the instantaneous voltages in the secondary circuit of the transformer will be at least twice the d.c. voltage on the r.f. amplifier. If a "hi-fi" amplifier of 10 watts or more output is available, it can be used as the driver for the 811As by coupling as shown in Fig. 9-29.

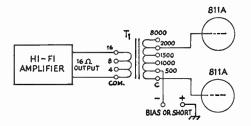


Fig. 9-29—A "hi-fi" audio amplifier will drive a Class-B modulator; a suitable coupling transformer is required. The connections shown here are for a pair of 811As. The amplifier should have an output rating of at least 10 watts.

T₁-10-watt line-to-voice-coil transformer (Stancor A-8104).

CHECKING AMPLIFIER OPERATION

An adequate job of checking speech equipment can be done with equipment that is neither elaborate nor expensive. A typical setup is shown in Fig. 9-30. The construction of a simple audio oscillator is described in the chapter on measurements. The audio-frequency voltmeter can be either a vacuum-tube voltmeter or a multirange volt-ohm-milliammeter that has a rectifier-type a.c. range. The headset is included for aural checking of the amplifier performance.

An audio oscillator usually will have an output control, but if the maximum output voltage is in excess of a volt or so the output setting may be rather critical when a high-gain speech amplifier is being tested. In such cases an attenuator such as is shown in Fig. 9-30 is a convenience.

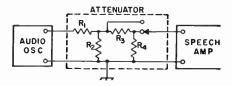


Fig. 9-30—Simple oscillator-attenuator test setup for checking a speech amplifier. It is not necessary that the frequency range of the audio oscillator be continuously variable; one or more "spot frequencies" will be satisfactory. Suitable resistor values are: R₁ and R₃, 10,000 ohms; R₂ and R₄, 1000 ohms.

Each of the two voltage dividers reduces the voltage by a factor of roughly 10 to 1, so that the over-all attenuation is about 100 to 1. The relatively low value of resistance, R_4 , connected across the input terminals also will minimize stray hum pickup on the connecting leads.

The output of a power amplifier such as a modulator or driver for a Class B stage may be checked by using a resistance load of the rated value for the amplifier. A useful circuit arrangement is shown in Fig. 9-31. The load resistance, R_1 , may be a single adjustable unit of appropriate power rating or may be made up of several resistors in series or parallel to give the required resistance. If measurement of the resistance is necessary an ohmmeter will be sufficiently accurate. In the case of a multimatch output transformer the taps should be those that will actually be used with the Class C amplifier with which the modulator is intended to work. R_1 then should have a value equal to the modulating impedance of the r.f. amplifier.

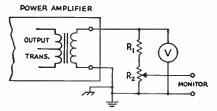


Fig. 9-31—Circuit for measuring power and making qualitative checks of the amplifier output. Values to be used for R_1 and R_2 are discussed in the text. The secondary winding of the output transformer in the amplifier should be disconnected from any d.c. source in the unit and one end connected to chassis as shown. An earth ground should be used on the system.

If an audio oscillator generating a good sine wave is used as the signal source the output power of the amplifier may be measured by an audio-frequency voltmeter as indicated by V. Either a vacuum-tube voltmeter on its a.c. scale or a rectifier-type a.c. voltmeter will be satisfactory, the principal requirements being relatively high impedance (1000 ohms per volt or more) and a reasonably accurate calibration. The power output will be equal to E^2/R_1 , where E is the r.m.s. value of the voltage across the resistor (a.c. instruments usually are calibrated in r.m.s. values). This assumes that the distortion generated in the amplifier is small; if distortion is high, the voltmeter reading will be inaccurate.

If the amplifier is a driver for a Class B modulator, the value of R_1 should be calculated from R/N^2 , where N is the turns ratio, primary to total secondary, of the class B input transformer, and R is the rated plate-to-plate load for the driver tube or tubes. R_1 should of course be connected across the total secondary in this case.

For a qualitative check on distortion, provision is made in Fig. 9-31 for monitoring the output of the amplifier. R_2 should be a wire-wound potentiometer having a resistance of 10 or 20 ohms. A headset may be connected to the "Monitor" terminals. Using the audio oscillator as a signal source, start with the gain control at minimum and then advance it slowly while listening carefully to the tone signal in the headset. When it begins to sound like a musical octave instead of a single tone, or when higher harmonically related tones can be heard along with the desired one, distortion is starting to become ap-

Checking Speech Equipment

preciable. This effect usually will be detectable, but not serious, at full output of the amplifier as indicated by the voltmeter reading. Keep the signal in the headset at a moderate level by adjusting R_2 when necessary. If the amplifier passes the distortion test satisfactorily, reduce the audio input to zero and note whether any hum is audible in the headset. There should be none, if the tone level in the headset at full sine-wave output was no more than moderately high.

After completing these checks with satisfactory results, substitute the microphone for the oscillator input to the amplifier and have someone speak into it at a moderate level. The headset will serve to indicate the speech quality at various output levels. A tape recorder, if available, is useful at this stage since it can be substituted for the headset and will provide a means for comparing the effect of changes and adjustments in the amplifier as well as giving a better over-all

in which it is occurring can be located by working from the last stage toward the front end of the amplifier, applying a signal to each grid in turn from the audio oscillator and adjusting the signal voltage for maximum output. In the case of push-pull stages, the signal may be applied to the primary of the interstage transformer—after disconnecting it from the plate-voltage source and the amplifier tube. Assuming that normal design principles have been followed and that all stages are theoretically working within their capabilities, the probable causes of distortion are wiring errors (such as accidental short-circuit of a cathode resistor), defective components, or use of wrong values of resistance in cathode and plate circuits.

Using the Oscilloscope

Speech-amplifier checking is facilitated considerably if an oscilloscope of the type having

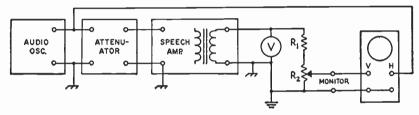


Fig. 9-32—Test setup using the oscilloscope to check for distortion. These connections will result in the type of pattern shown in Fig. 9-33, the horizontal sweep being provided by the audio input signal. For waveform patterns, omit the connection between the audio oscillator and the horizontal amplifier in the scope, and use the horizontal linear sweep.

check on speech quality than the average headset. The effect of measures taken to attenuate high- or low-frequency response in the amplifier is readily observed by comparing recordings made before and after changes. The output quality of the amplifier also can be compared with the original output of the microphone as registered on the recorder. In using a recorder care must be taken to set R_2 so that the first stage in the recorder amplifier is not overloaded. Use the normal gain setting of the recorder and adjust R_2 to give normal level indications.

Amplifier Troubles

If the hum level is too high, the amplifier stage that is causing the trouble can be located by temporarily short-circuiting the grid of each tube to ground, starting with the output amplifier. When shorting a particular grid makes a marked decrease in hum, the hum presumably is coming from a preceding stage, although it is possible that it is getting its start in that particular grid circuit. If shorting a grid does not decrease the hum, the hum is originating either in the plate circuit of that tube or the grid circuit of the next. Aside from wiring errors, a defective tube, or inadequate plate-supply filtering, objectionable hum usually originates in the first stage of the amplifier.

If distortion occurs below the point at which the expected power output is secured the stage amplifiers and a linear sweep circuit is available. A typical setup for using the oscilloscope is shown in Fig. 9-32. With the connections shown, the sweep circuit is not required but horizontal and vertical amplifiers are necessary. Audio voltage from the oscillator is fed directly to one oscilloscope amplifier (horizontal in this case) and the output of the speech amplifier is connected to the other. The scope amplifier gains should be adjusted so that each signal gives the same line length with the other signal shut off.

Under these conditions, when the input and output signals are applied simultaneously they are compared directly. If the speech amplifier is distortion-free and introduces no phase shift, the resulting pattern is simply a straight line, as shown at the upper left in Fig. 9-33, making an angle of about 45 degrees with the horizontal and vertical axes. If there is no distortion but there is phase shift, the pattern will be a smooth ellipse, as shown at the upper right. The greater the phase shift the greater the tendency of the ellipse to grow into a circle. When there is evenharmonic distortion in the amplifier one end of the line or ellipse becomes curved, as shown in the second row in Fig. 9-33. With odd-harmonic distortion such as is characteristic of overdriven push-pull stages, the line or ellipse is curved at

Patterns such as these will be obtained when the input signal is a fairly good sine wave. They will tend to become complicated if the input wave form is complex and the speech amplifier introduces appreciable phase shifts. It is therefore advisable to test for distortion with an input signal that is as nearly as possible a sine wave. Also, it is best to use a frequency in the 500–1000 cycle range, since improper phase shift in the amplifier is usually least in this region. Phase shift in itself is not of great importance in an audio amplifier of ordinary design because it does not change the character of speech so far as the ear is concerned. However, if a complex signal is used for testing, phase shift may make it difficult to detect distortion in the oscilloscope pattern.

Since the oscilloscope amplifiers themselves may introduce phase shift and possibly distortion as well, it is advisable to check the scope before attempting to make checks on the speech amplifier. Apply the signal from the audio oscillator simultaneously to the horizontal and vertical amplifier input terminals. If both amplifiers have the same phase characteristics and negligible distortion the pattern, after suitable adjustment of the gains, will be a straight line as shown at the upper left in Fig. 9-33. If distortion is visible, note whether it changes when the scope gain controls are reduced; if not, the signal voltage from the audio oscillator is too great and should be reduced to the point where the input amplifiers are not overloaded. After finding the proper settings for signal input and scope gains, leave the latter alone in making checks on the speech equipment and adjust the input to the scope by means of R_2 and the output of the audio oscillator. Phase shift in the scope itself is not serious since the presence of distortion in the speech amplifier can be detected by the patterns shown at the right in Fig. 9-33.

In amplifiers having negative feedback, excessive phase shift within the feed-back loop may cause self-oscillation, since the signal fed back may arrive at the grid in phase with the applied signal voltage instead of out of phase with it. Such a phase shift is most likely to be associated with the output transformer. Oscillation usually occurs at some frequency above 10,000 cycles, although occasionally it will occur at a very low frequency. If the pass band in the stage in which the phase shift occurs is deliberately restricted to the optimum voice range, as described earlier, the gain at both very high and very low frequencies will be so low that selfoscillation is unlikely, even with large amounts of feedback.

Generally speaking, it is easier to detect small amounts of distortion with the type of pattern shown in Fig. 9-33 than it is with the wave-form pattern obtained by feeding the output signal to the vertical plates and making use of the linear sweep in the scope. However, the wave-form pattern can be used satisfactorily if the signal from the audio oscillator is a reasonably good sine wave. One simple method is to examine the output of the oscillator alone and trace the pattern on a sheet of transparent paper. The pattern

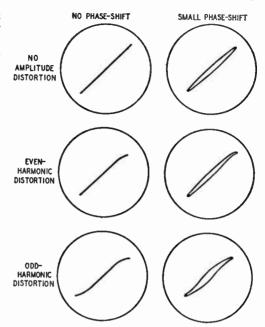


Fig. 9-33—Typical patterns obtained with the connections shown in Fig. 9-32. Depending on the number of stages in the amplifier, the pattern may slope upward to the right, as shown, or upward to the left. Also, depending on where the distortion originates, the curvature in the second row may appear either at the top or bottom of the line or ellipse.

given by the output of the amplifier can then be compared with the "standard" pattern by adjusting the oscilloscope gains to make the two patterns coincide as closely as possible. The pattern discrepancies are a measure of the distortion.

In using the oscilloscope care must be taken to avoid introducing hum voltages that will upset the measurements. Hum pickup on the scope leads or other exposed parts such as the amplifier load resistor or the voltmeter can be detected by shutting off the audio oscillator and speech amplifier and connecting first one and then the other to the vertical plates of the scope, setting the internal horizontal sweep to an appropriate width. The trace should be a straight horizontal line when the vertical gain control is set at the position used in the actual measurements. Waviness in the line indicates hum. If the hum is not in the scope itself (check by disconnecting the leads at the instrument) make sure that there is a good ground connection on all the equipment and, if necessary, shield the hot leads.

The oscilloscope can be used to good advantage in stage-by-stage testing to check wave forms at the grid and plate of each stage and thus to determine rapidly where a source of trouble may be located. When the scope is connected to circuits that are not at ground potential for d.c., a capacitor of about $0.1~\mu f$, should be connected in series with the hot oscilloscope lead. The probe lead should be shielded to prevent hum pickup.

Amplitude Modulation

As described in the chapter on circuit fundamentals, the process of modulation sets up groups of frequencies called **sidebands**, which appear symmetrically above and below the frequency of the unmodulated signal or carrier. If the instantaneous values of the amplitudes of all these separate frequencies are added together, the result is called the modulation envelope. In amplitude modulation (a.m.) the modulation envelope follows the amplitude variations of the audio-frequency signal that is being used to modulate the wave.

For example, modulation by a 1000-cycle tone will result in a modulation envelope that varies in amplitude at a 1000-cycle rate. The actual r.f. signal that produces such an envelope consists of three frequencies - the carrier, a side frequency 1000 cycles higher, and a side frequency 1000 cycles lower than the carrier. These three frequencies easily can be separated by a receiver having high selectivity. In order to reproduce the original modulation the receiver must have enough bandwidth to accept the carrier and the sidebands simultaneously. This is because an a.m. detector responds to the modulation envelope rather than to the individual signal components, and the envelope will be distorted in the receiver unless all the frequency components in the signal go through without change in their relative am-

In the simple case of tone modulation the two side frequencies and the carrier are constant in amplitude—it is only the envelope amplitude that varies at the modulation rate. With more complex modulation such as voice or music the amplitudes and frequencies of the side frequencies vary from instant to instant. The amplitude of the modulation envelope varies from instant to instant in the same way as the complex audio-frequency signal causing the modulation. Nevertheless, even in this case the *carrier* amplitude is constant if the transmitter is properly modulated.

A.M. Sidebands and Channel Width

Speech can be electrically reproduced, with high intelligibility, in a band of frequencies lying between approximate¹y 100 and 3000 cycles. When these frequencies are combined with a radio-frequency carrier, the sidebands occupy the frequency spectrum from about 3000 cycles below the carrier frequency to 3000 cycles above—a total band or channel of about 6 kilocycles.

Actual speech frequencies extend up to 10,000 cycles or more, so it is possible to occupy a 20-kc.

channel if no provision is made for reducing its width. For communication purposes such a channel width represents a waste of valuable spectrum space, since a 6-kc. channel is fully adequate for intelligibility. Occupying more than the minimum channel creates unnecessary interference. Thus speech equipment design and transmitter adjustment and operation should be pointed toward maintaining the channel width at the minimum.

THE MODULATION ENVELOPE

In Fig. 10-1 the drawing at A shows the unmodulated r.f. signal, assumed to be a sine wave of the desired radio frequency. The graph can be taken to represent either voltage or current.

In B, the signal is assumed to be modulated by the audio frequency shown in the small drawing above. This frequency is much lower than the carrier frequency, a necessary condition for good modulation. When the modulating voltage is "positive" (above its axis) the envelope amplitude is increased above its unmodulated amplitude; when the modulating voltage is "negative" the envelope amplitude is decreased. Thus the envelope grows larger and smaller with the polarity and amplitude of the modulating voltage.

The drawings at C shows what happens with stronger modulation. The envelope amplitude is doubled at the instant the modulating voltage reaches its positive peak. On the negative peak of the modulating voltage the envelope amplitude just reaches zero; in other words, the signal is completely modulated.

Percentage of Modulation

When a modulated signal is detected in a receiver, the detector output follows the modulation envelope. The stronger the modulation, therefore, the greater is the useful receiver output. Obviously, it is desirable to make the modulation as strong or "heavy" as possible. A wave modulated as in Fig. 10-1C would produce considerably more useful audio output than the one shown at B.

The "depth" of the modulation is expressed as a percentage of the unmodulated carrier amplitude. In either B or C, Fig. 10-1, X represents the unmodulated carrier amplitude, Y is the maximum envelope amplitude on the modulation uppeak, and Z is the minimum envelope amplitude on the modulation downpeak.

In a properly operating modulation system the modulation envelope is an accurate reproduction of the modulating wave, as can be seen in Fig.

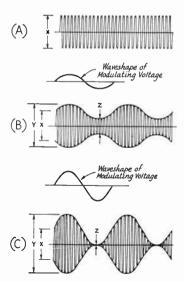


Fig. 10-1—Graphical representation of (A) r.f. output unmodulated, (B) modulated 50%, (C) modulated 100%. The modulation envelope is shown by the thin outline on the modulated wave.

10-1 at B and C by comparing one side of the outline with the shape of the modulating wave. (The lower outline duplicates the upper, but simply appears upside down in the drawing.)

The percentage of modulation is

% Mod. =
$$\frac{Y-X}{X} \times 100$$
 (upward modulation), or % Mod. = $\frac{X-Z}{X} \times 100$ (downward modulation)

If the wave shape of the modulation is such that its peak positive and negative amplitudes are equal, then the modulation percentage will be the same both up and down. If the two percentages differ, the larger of the two is customarily specified.

Power in Modulated Wave

The amplitude values shown in Fig. 10-1 correspond to current or voltage, so the drawings may be taken to represent instantaneous values of either. The power in the wave varies as the square of either the current or voltage, so at the peak of the modulation up-swing the instantaneous power in the envelope of Fig. 10-1C is four times the unmodulated carrier power (because the current and voltage both are doubled). At the peak of the down-swing the power is zero, since the amplitude is zero. These statements are true of 100 per cent modulation no matter what the wave form of the modulation. The instantaneous envelope power in the modulated signal is proportional to the square of its envelope amplitude at every instant. This fact is highly important in the operation of every method of amplitude modulation.

It is convenient, and customary, to describe the operation of modulation systems in terms of sine-wave modulation. Although this wave shape is seldom actually used in practice (voice wave shapes depart very considerably from the sine form) it lends itself to simple calculations and its use as a standard permits comparison between systems on a common basis. With sine-wave modulation the *average* power in the modulated signal over any number of full cycles of the modulation frequency is found to be 1½ times the power in the unmodulated carrier. In other words, the power output increases 50 per cent with 100 per cent modulation by a sine wave.

This relationship is very useful in the design of modulation systems and modulators, because any such system that is capable of increasing the average power output by 50 per cent with sinewave modulation automatically fulfills the requirement that the instantaneous power at the modulation up-peak be four times the carrier power. Consequently, systems in which the additional power is supplied from outside the modulated r.f. stage (e.g., plate modulation) usually are designed on a sine-wave basis as a matter of convenience. Modulation systems in which the additional power is secured from the modulated r.f. amplifier (e.g., grid modulation) usually are more conveniently designed on the basis of peak envelope power rather than average power.

The extra power that is contained in a modulated signal goes entirely into the sidebands, half in the upper sideband and half into the lower. As a numerical example, full modulation of a 100-watt carrier by a sine wave will add 50 watts of sideband power, 25 in the lower and 25 in the upper sideband. Supplying this additional power for the sidebands is the object of all of the various systems devised for amplitude modulation.

No such simple relationship exists with complex wave forms. Complex wave forms such as speech do not, as a rule, contain as much average power as a sine wave. Ordinary speech wave forms have about half as much average power as a sine wave, for the same peak amplitude in both wave forms. Thus for the same modulation percentage, the sideband power with ordinary speech will average only about half the power with sine-wave modulation, since it is the peak envelope amplitude, not the average power, that determines the percentage of modulation.

Unsymmetrical Modulation

In an ordinary electric circuit it is possible to increase the amplitude of current flow indefinitely, up to the limit of the power-handling capability of the components, but it cannot very well be decreased to less than zero. The same thing is true of the amplitude of an r.f. signal; it can be modulated upward to any desired extent, but it cannot be modulated downward more than 100 per cent.

When the modulating wave form is unsymmetrical it is possible for the upward and downward modulation percentages to be different. A simple case is shown in Fig. 10-2. The positive peak of the modulating signal is about 3 times the amplitude of the negative peak. If, as shown

The Modulation Envelope

in the drawing, the modulating amplitude is adjusted so that the peak downward modulation is just 100 per cent (Z=0) the peak upward modulation is 300 per cent (Y=4X). The carrier amplitude is represented by X, as in Fig. 10-1. The modulation envelope reproduces the wave form of the modulating signal accurately, hence there is no distortion. In such a modulated signal the increase in power output with modulation is considerably greater than it is when the modulation is symmetrical and therefore has to be limited to 100 per cent both up and down.

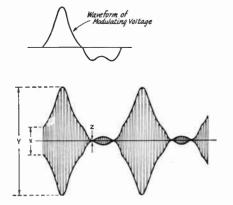


Fig. 10-2—Modulation by an unsymmetrical wave form. This drawing shows 100% downward modulation along with 300% upward modulation. There is no distortion, since the modulation envelope is an accurate reproduction of the wave form of the modulating voltage.

In Fig. 10-2 the peak envelope amplitude, Y, is four times the carrier amplitude, X, so the peakenvelope power is 16 times the carrier power. When the upward modulation is more than 100 per cent the power capacity of the modulating system obviously must be increased sufficiently to take care of the much larger peak amplitudes.

Overmodulation

If the amplitude of the modulation on the

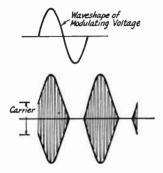


Fig. 10-3—An overmodulated signal. The modulation envelope is not an accurate reproduction of the wave form of the modulating voltage. This or any type of distortion occurring during the modulation process generates spurious sidebands or "splatter."

downward swing becomes too great, there will be a period of time during which the r.f. output is entirely cut off. This is shown in Fig. 10-3. The shape of the downward half of the modulating wave is no longer accurately reproduced by the modulation envelope, consequently the modulation is distorted. Operation of this type is called overmodulation. The distortion of the modulation envelope causes new frequencies (harmonics of the modulating frequency) to be generated. These combine with the carrier to form new side frequencies that widen the channel occupied by the modulated signal. These spurious frequencies are commonly called "splatter."

It is important to realize that the channel occupied by an amplitude-modulated signal is dependent on the shape of the modulation envelope. If this wave shape is complex and can be resolved into a wide band of audio frequencies, then the channel occupied will be correspondingly large. An overmodulated signal splatters and occupies a much wider channel than is necessary because the "clipping" of the modulating wave that occurs at the zero axis changes the envelope wave shape to one that contains highorder harmonics of the original modulating frequency. These harmonics appear as side frequencies separated by, in some cases, many kilocycles from the carrier frequency.

Because of this clipping action at the zero axis, it is important that care be taken to prevent applying too large a modulating signal in the downward direction. Overmodulation downward results in more splatter than is caused by most other types of distortion in a phone transmitter.

GENERAL REQUIREMENTS

For proper operation of an amplitude-modulated transmitter there are a few general requirements that must be met no matter what particular method of modulation may be used. Failure to meet these requirements is accompanied by distortion of the modulation envelope. This in turn increases the channel width as compared with that required by the legitimate frequencies contained in the original modulating wave.

Frequency Stability

For satisfactory amplitude modulation, the carrier frequency must be entirely unaffected by modulation. If the application of modulation causes a change in the carrier frequency, the frequency will wobble back and forth with the modulation. This causes distortion and widens the channel taken by the signal. Thus unnecessary interference is caused to other transmissions.

In practice, this undesirable frequency modulation is prevented by applying the modulation to an r.f. amplifier stage that is isolated from the frequency-controlling oscillator by a buffer amplifier. Amplitude modulation applied directly to an oscillator always is accompanied by frequency modulation. Under existing FCC regulations amplitude modulation of an oscillator is permitted only on frequencies above 144 Mc. Below that frequency the regulations require that

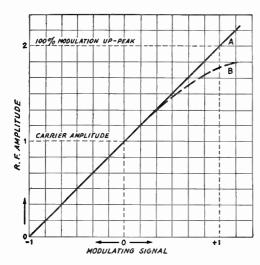


Fig. 10-4—The modulotion chorocteristic shows the relationship between the instantaneous envelope amplitude of the r.f. output (or voltage) and the instantaneous omplitude of the modulating voltage. The ideal charocteristic is a straight line, as shown by curve A.

an amplitude-modulated transmitter be completely free from frequency modulation.

Linearity

At least up to the limit of 100 per cent upward modulation, the amplitude of the r.f. output should be directly proportional to the amplitude of the modulating wave. Fig. 10-4 is a graph of an ideal modulation characteristic, or curve showing the relationship between r.f. output amplitude and instantaneous modulation amplitude. The modulation swings the r.f. amplitude back and forth along the curve A, as the modulating voltage alternately swings positive and negative. Assuming that the negative peak of the modulating wave is just sufficient to reduce the r.f. output to zero (modulating voltage equal to -1 in the drawing), the same modulating voltage peak in the *positive* direction (+1) should cause the r.f. amplitude to reach twice its unmodulated value. The ideal is a straight line, as shown by curve A. Such a modulation characteristic is perfectly linear.

A nonlinear characteristic is shown by curve B. The r.f. amplitude does not reach twice the unmodulated carrier amplitude when the modu-

lating voltage reaches its positive peak. A modulation characteristic of this type gives a modulation envelope that is "flattened" on the uppeak; in other words, the modulation envelope is not an exact reproduction of the modulating wave. It is therefore distorted and harmonics are generated, causing the transmitted signal to occupy a wider channel than is necessary. A nonlinear modulation characteristic can easily result when a transmitter is not properly designed or is misadjusted.

The modulation capability of the transmitter is the maximum percentage of modulation that is possible without objectionable distortion from nonlinearity. The maximum capability can never exceed 100 per cent on the down-peak, but it is possible for it to be higher on the up-peak. The modulation capability should be as close to 100 per cent as possible, so that the most effective signal can be transmitted.

Plate Power Supply

The d.c. power supply for the plate or plates of the modulated amplifier should be well filtered; if it is not, plate-supply ripple will modulate the carrier and cause annoying hum. The ripple voltage should not be more than about 1 per cent of the d.c. output voltage.

In amplitude modulation the plate current of the modulated r.f. amplifier varies at an audiofrequency rate; in other words, an alternating current is superimposed on the d.c. plate current. The output filter capacitor in the plate supply must have low reactance, at the lowest audio frequency in the modulation, if the transmitter is to modulate equally well at all audio frequencies. The capacitance required depends on the ratio of d.c. plate current to plate voltage in the modulated amplifier. The requirements will be met satisfactorily if the capacitance of the output capacitor is at least equal to

$$C = 25 \frac{I}{E}$$

where $C = \text{Capacitance of output capacitor in } \mu_f$.

I = D.c. plate current of modulated amplifier in milliamperes

E = Plate voltage of modulated amplifier

Example: A modulated amplifier operates at 1250 volts and 275 ma. The capacitance of the output capacitor in the plate-supply filter should be at least

$$C = 25 \frac{I}{E} = 25 \times \frac{275}{1250} = 25 \times 0.22 = 5.5 \text{ uf}.$$

AMPLITUDE MODULATION METHODS

MODULATION SYSTEMS

As explained in the preceding section, amplitude modulation of a carrier is accompanied by an increase in power output, the additional power being the "useful" or "talk power" in the sidebands. This additional power may be supplied from an external source in the form of audio-

frequency power. It is then added to the unmodulated power input to the amplifier to be modulated, after which the combined power is converted to r.f. This is the method used in plate modulation. It has the advantage that the r.f. power is generated at the high efficiency characteristic of Class C amplifiers—of the order of 65 to 75 per cent—but has the accom-

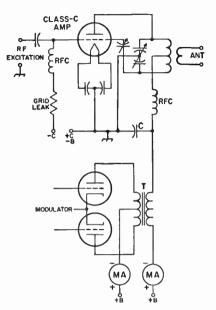


Fig. 10-5—Plate modulation of a Class C r.f. amplifier. The r.f. plate bypass capacitor, C, in the amplifier stage should have reasonably high reactance at audio frequencies. A value of the order of 0.001 μ f. to 0.005 μ f. is satisfactory in practically all cases. (See chapter on modulators.)

panying disadvantage that generating the audiofrequency power is rather expensive.

An alternative that does not require relatively large amounts of audio-frequency power makes use of the fact that the power output of an amplifier can be controlled by varying the potential of a tube element - such as a control grid or a screen grid - that does not, in itself, consume appreciable power. In this case the additional power during modulation is secured by sacrificing carrier power; in other words, a tube is capable of delivering only so much total power within its ratings, and if more must be delivered at full modulation, then less is available for the unmodulated carrier. Systems of this type must of necessity work at rather low efficiency at the unmodulated carrier level. As a practical working rule, the efficiency of the modulated r.f. amplifier is of the order of 30 to 35 per cent, and the unmodulated carrier power output obtainable with such a system is only about one-fourth to one-third that obtainable from the same amplifier with plate modulation.

It is well to appreciate that no simple modulation scheme that purports to get around this limitation of grid modulation ever has actually done so. Methods have been devised that have resulted in modulation at high over-all efficiency, without requiring audio power, by obtaining the necessary additional power from an auxiliary r.f. amplifier. This leads to circuit and operating complexities that make the systems unsuitable for amateur work, where rapid frequency change and simplicity of operation are almost always

The method discussed in this section are the basic ones. Variants that from time to time attain passing popularity can readily be appraised on the basis of the preceding paragraphs. A simple grid modulation system that claims high efficiency should be looked upon with suspicion, since it is almost certain that the high efficiency, if actually achieved, is obtained by sacrificing the linear relationship between modulating signal and modulation envelope that is the first essential of a good modulation method.

PLATE MODULATION

Fig. 10-5 shows the most widely used system of plate modulation, in this case with a triode r.f. tube. A balanced (push-pull Class A, Class AB or Class B) modulator is transformer-coupled to the plate circuit of the modulated r.f. amplifier. The audio-frequency power generated by the modulator is combined with the d.c. power in the modulated-amplifier plate circuit by transfer through the coupling transformer, T. For 100 per cent modulation the audio-frequency power output of the modulator and the turns ratio of the coupling transformer must be such that the voltage at the plate of the modulated amplifier varies between zero and twice the d.c. operating plate voltage, thus causing corresponding variations in the amplitude of the r.f. output.

Audio Power

As stated earlier, the average power output of the modulated stage must increase during modulation. The modulator must be capable of supplying to the modulated r.f. stage sine-wave audio power equal to 50 per cent of the d.c. plate input. For example, if the d.c. plate power input to the r.f. stage is 100 watts, the sine-wave audio power output of the modulator must be 50 watts.

Modulating Impedance; Linearity

The modulating impedance, or load resistance presented to the modulator by the modulated r.f. amplifier, is equal to

$$Z_{\rm m}=rac{E_{
m b}}{I_{
m p}} imes 1000 {
m ohms}$$

where $E_b = D.c.$ plate voltage

 $I_p = D.c.$ plate current (ma.) E_b and I_p are measured without modulation.

The power output of the r.f. amplifier must vary as the square of the instantaneous plate voltage (the r.f. output voltage nust be proportional to the plate voltage) for the modulation to be linear. This will be the case when the amplifier operates under Class C conditions. The linearity depends upon having sufficient grid excitation and proper bias, and upon the adjustment of circuit constants to the proper values.

Adjustment of Plate-Modulated Amplifiers

The general operating conditions for Class C operation are described in the chapter on transmitters. The grid bias and grid current required

Fig. 10-6—Plate and screen modulation of a Class C r.f. amplifier using a screen-grid tube. The plate r.f. bypass capacitor, C_1 , should have reasonably high reactance at oll audio frequencies; a value of 0.001 to 0.005 μ f. is generally satisfactory. The screen bypass, C_2 , should not exceed 0.002 μ f. in the usual case.

When the modulated amplifier is a beam tetrode the suppressor connection shown in this diagram may be ignored. If a base terminal is provided on the tube for the beam-forming plates, it should be connected as recommended by the tube manufacturer.

for plate modulation usually are given in the operating data supplied by the tube manufacturer; in general, the bias should be such as to give an operating angle of about 120 degrees at the d.c. plate voltage used, and the grid excitation should be great enough so that the amplifier's plate efficiency will stay constant when the plate voltage is varied over the range from zero to twice the unmodulated value. For best linearity, the grid bias should be obtained from a fixed-bias source of about the cut-off value, supplemented by enough grid-leak bias to bring the total up to the required operating bias.

The maximum permissible d.c. plate power input for 100 per cent modulation is twice the sine-wave audio-frequency power output available from the modulator. This input is obtained by varying the loading on the amplifier (keeping its tank circuit tuned to resonance) until the product of d.c. plate voltage and plate current is the desired power. The modulating impedance

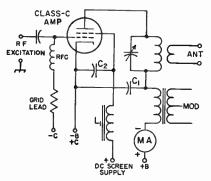


Fig. 10-7—Plate modulation of a beam tetrode, using an audio impedance in the screen circuit. The value of L_1 discussed in the text. See Fig. 10-6 for data on bypass capacitors C_1 and C_2 .

AMPLITUDE MODULATION

under these conditions must be transformed to the proper value for the modulator by using the correct output-transformer turns ratio. This point is considered in detail in the chapter on modulator design.

Neutralization, when triodes are used, should be as nearly perfect as possible, since regeneration may cause nonlinearity. The amplifier also must be completely free from parasitic oscillations.

Although the total power input (d.c. plus audio-frequency a.c.) increases with modulation, the d.c. plate current of a plate-modulated amplifier should not change when the stage is modulated. This is because each increase in plate voltage and plate current is balanced by an equivalent decrease in voltage and current on the next half-cycle of the modulating wave. D.c. instruments cannot follow the a.f. variations, and since the average d.c. plate current and plate voltage of a properly operated amplifier do not change, neither do the meter readings. A change in plate current with modulation indicates nonlinearity. On the other hand, a thermocouple r.f. ammeter connected in the antenna or transmission line will show an increase in r.f. current with modulation, because instruments of this type respond to power rather than to current or voltage.

Screen-Grid Amplifiers

Screen-grid tubes of the pentode or beamtetrode type can be used as Class C plate-modulated amplifiers by applying the modulation to both the plate and screen grid. The usual method of feeding the screen grid with the necessary d.c. and modulation voltages is shown in Fig. 10-6. The dropping resistor, *R*, should be of the proper value to apply normal d.c. voltage to the screen under steady carrier conditions. Its value can be calculated by taking the difference between plate and screen voltages and dividing it by the rated screen current.

The modulating impedance is found by dividing the d.c. plate voltage by the sum of the plate and screen currents. The plate voltage multiplied by the sum of the two currents gives the power input to be used as the basis for determining the audio power required from the modulator.

Modulation of the screen along with the plate is necessary because the screen voltage has a much greater effect on the plate current than the plate voltage does. The modulation characteristic is nonlinear if the plate alone is modulated. However, some beam tetrodes can be modulated satisfactorily by applying the modulating power to the plate circuit alone, provided the screen is connected to its d.c. supply through an audio impedance. Under these conditions the screen becomes self-modulating, because of the variations in screen current that occur when the plate voltage is varied. The circuit is shown in Fig. 10-7. The choke coil L_1 is the audio impedance in the screen circuit; its inductance should be large enough to have a reactance (at the lowest desired audio frequency) that is not less than the impedance of the screen. The screen impedance can be taken to be approximately equal to the d.c. screen voltage divided by the d.c. screen current in amperes.

Choke-Coupled Modulator

The choke-coupled Class A modulator is shown in Fig. 10-8. Because of the relatively low power output and plate efficiency of a Class A amplifier, this method is seldom used except for a few special applications. There is considerably less freedom in adjustment, since no transformer is available for matching impedances.

The modulating impedance of the r.f. amplifier must be adjusted to the value of load impedance required by the particular modulator tube used, and the power input to the r.f. stage should not exceed twice the rated a.f. power output of the modulator for 100 per cent modulation. The plate voltage on the modulator must be higher than the plate voltage on the r.f. amplifier, for

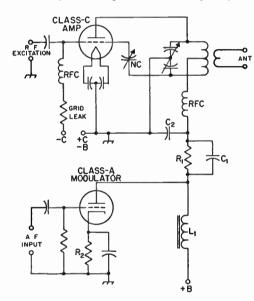


Fig. 10-8—Chake-coupled Class A modulator. The cathode resistor, R_{2r} should have the normal value far aperatian af the madulatar tube as a Class A pawer amplifier. The madulatian chake, L_{1r} , shauld be 5 henrys or mare. A value af 0.001 ta 0.005 μ f. is satisfactory at C_{2r} , the r.f. amplifier plate bypass capacitor. See text for discussion af C_{1r} and R_{1r} .

100 per cent modulation, because the a.f. voltage developed by the modulator cannot swing to zero without a great deal of distortion. R_1 provides the necessary d.c. voltage drop between the modulator and r.f. amplifier. The d.c. voltage drop through R_1 must equal the minimum instantaneous plate voltage on the modulator tube under normal operating conditions. C_1 , an audio-frequency bypass across R_1 , should have a capacitance such that its reactance at 100 cycles is not more than about one-tenth the resistance of R_1 . Without R_1C_1 the percentage of modulation is limited to 70 to 80 per cent in the average case.

GRID MODULATION

The principal disadvantage of plate modulation is that a considerable amount of audio power is necessary. This requirement can be avoided by applying the modulation to a grid element in the modulated amplifier. However, serious disadvantages of grid modulation are the reduction in the carrier power output obtainable from a given r.f. amplifier tube and the more rigorous operating requirements and more complicated adjustment.

The term "grid modulation" as used here applies to all types—control grid, screen, or suppressor—since the operating principles are exactly the same no matter which grid is actually modulated. With grid modulation the plate voltage is constant, and the increase in power output with modulation is obtained by making both the plate current and plate efficiency vary with the modulating signal as shown in Fig. 10-9. For 100 per cent modulation, both plate current and efficiency must, at the peak of the modulation up-swing, be twice their carrier values. Thus at the modulation-envelope peak the power input is doubled, and since the plate efficiency also is doubled at the same instant the peak envelope

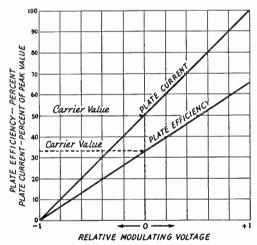


Fig. 10-9—In a perfect grid-madulated amplifier bath plate current and plate efficiency would vary with the instantaneous madulating voltage as shawn. When this is sa the madulatian characteristic is as given by curve A in Fig. 10-4, and the peak envelape output power is faur times the unmodulated carrier power. The variations in plate current with madulation, indicated above, da nat register an a d.c. meter, so the plate meter shows na change when the signal is modulated.

output power will be four times the carrier power. The efficiency obtainable at the envelope peak depends on how carefully the modulated amplifier is adjusted, and sometimes can be as high as 80 per cent. It is generally less when the amplifier is adjusted for good linearity, and under average conditions a round figure of %, or 66

per cent, is representative. The efficiency without modulation is only half the peak efficiency, or about 33 per cent. This low average efficiency reduces the permissible carrier output to about one-fourth the power obtainable from the same tube in c.w. operation, and to about one-third the carrier output obtainable from the tube with plate modulation.

The modulator is required to furnish only the audio power dissipated in the modulated grid under the operating conditions chosen. A speech amplifier capable of delivering 3 to 10 watts is usually sufficient.

Grid modulation does not give quite as linear a modulation characteristic as plate modulation, even under optimum operating conditions. When misadjusted the nonlinearity may be severe, resulting in bad distortion and splatter.

Plate-Circuit Operating Conditions

The d.c. plate power input to the grid-modulated amplifier, assuming a round figure of \(\frac{1}{3} \) (33) per cent) for the plate efficiency, should not exceed 11/2 times the plate dissipation rating of the tube or tubes used in the modulated stage. Use the maximum plate voltage permitted by the manufacturer's ratings, because the optimum operating conditions are more easily achieved with high plate voltage and the linearity also is improved.

Example: Two tubes having plate dissipation ratings of 55 watts each are to be used with grid

The maximum permissible power input, at 33%

efficiency, is $P = 1.5 \times (2 \times 55) = 1.5 \times 110 = 165$ watts The maximum recommended plate voltage for these tubes is 1500 volts. Using this figure, the average plate current for the two tubes will be

$$I = \frac{P}{E} = \frac{165}{1500} = 0.11 \text{ amp.} = 110 \text{ ma},$$

At 33% efficiency, the carrier output to be expected is 55 watts.

The plate-voltage/plate-current ratio at twice carrier plate current is

$$\frac{1500}{220} = 6.8$$

The tank-circuit L/C ratio should be chosen on the basis of twice the average or carrier plate current. If the L/C ratio is based on the plate voltage/plate current ratio under carrier conditions the Q may be too low for good coupling to the output circuit.

Screen Grid Modulation

Screen modulation is probably the simplest form of grid modulation and the least critical of adjustment. The most satisfactory way to apply the modulating voltage to the screen is through a transformer, as shown in Fig. 10-10. With practical tubes it is necessary to drive the screen somewhat negative with respect to the cathode to get complete cut-off of r.f. output. For this reason the peak modulating voltage required for 100 per cent modulation is usually 10 per cent or so greater than the d.c. screen voltage. The latter, in turn, is approximately half the rated screen voltage recommended by the manufacturer under

AMPLITUDE MODULATION

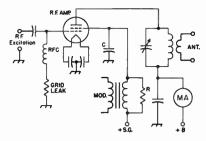


Fig. 10-10—Screen-grid madulation of beam tetrade. Capacitar C is an r.f. bypass capacitar and should have high reactance at audia frequencies. A value af 0.002 μ f, is satisfactory. The grid leak can have the same value that is used far c.w. aperation af the tube.

maximum ratings for radiotelegraph operation.

The audio power required for 100 per cent modulation is approximately one-fourth the d.c. power input to the screen in c.w. operation, but varies somewhat with the operating conditions. A receiving-type audio power amplifier will suffice as the modulator for most transmitting tubes. The relationship between screen voltage and screen current is not linear, which means that the load on the modulator varies over the audiofrequency cycle. It is therefore highly advisable to use negative feedback in the modulator circuit. If excess audio power is available, it is also advisable to load the modulator with a resistance (R in Fig. 10-10) its value being adjusted to dissipate the excess power. There is no simple way to determine the proper resistance except experimentally, by observing its effect on the modulation envelope with the aid of an oscilloscope.

On the assumption that the modulator will be fully loaded by the screen plus the additional load resistor R, the turns ratio required in the coupling transformer may be calculated as follows:

$$N = \frac{E_{\rm d}}{2.5\sqrt{PR_{\rm L}}}$$

where N is the turns ratio, secondary to primary; Ed is the rated screen voltage for c.w. operation; P is the rated audio power output of the modulator; and R_L is the rated load resistance for the modulator.

Adjustment

A screen-modulated amplifier should be adjusted with the aid of an oscilloscope connected to give a trapezoid pattern (see later in chapter). A tone source for modulating the transmitter is a convenience, since a steady tone will give a steady pattern on the oscilloscope. A steady pattern is easier to study than one that flickers with voice modulation.

Having determined the permissible carrier plate current as previously described, apply r.f. excitation and d.c. plate and screen voltages. Without modulation, adjust the plate loading to give the required plate current, keeping the plate tank circuit tuned to resonance. Next, apply modulation and increase the modulating voltage until the modulation characteristic shows curvature (see later in this chapter for use of the oscilloscope). If curvature occurs well below 100 per cent modulation, the plate efficiency is too high at the carrier level. Increase the plate loading slightly and readjust the r.f. grid excitation to maintain the same plate current; then apply modulation and check the characteristic again. Continue until the characteristic is as linear as possible from zero to twice the carrier amplitude.

In general, the amplifier should be heavily loaded. Under proper operating conditions the plate-current dip as the amplifier plate circuit is tuned through resonance will be little more than just discernible. Operate with the grid current as low as possible, since this reduces the screen current and thus reduces the amount of power required from the modulator.

With proper adjustment the linearity is good up to about 90 per cent modulation. When the screen is driven negative for 100 per cent modulation there is a kink in the modulation characteristic at the zero-voltage point. This introduces a small amount of envelope distortion. The kink can be removed and the over-all linearity improved by applying a small amount of modulating voltage to the control grid simultaneously with screen modulation.

In an alternative adjustment method not requiring an oscilloscope the r.f. amplifier is first tuned up for maximum output without modulation and the rated d.c. screen voltage (from a fixed-voltage supply) for c.w. operation applied. Use heavy loading and reduce the grid excitation until the output just starts to fall off, at which point the resonance dip in plate current should be small. Note the plate current and, if possible,

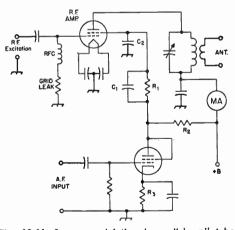


Fig. 10-11—Screen modulation by a "clomp" tube. The grid leak is the normal value for c.w. operation and C_2 should be 0.002 μ f. or less. See text for discussion of C_1 , R_1 , R_2 and R_3 . R_3 should have the proper value for Closs A operation of the modulator tube, but cannot be colculated unless triade curves for the tube are available.

the r.f. output current, and then reduce the d.c. screen voltage until the plate current is one-half its previous value. The r.f. output current should also be one-half its previous value at this screen voltage. The amplifier is then ready for modulation, and the modulating voltage may be increased until the plate current just starts to shift upward, which indicates that the amplifier is modulated 100 per cent. With voice modulation the plate current should remain steady, or show just an occasional small upward kick on intermittent peaks.

"Clamp-Tube" Modulation

A method of screen-grid modulation that is convenient in transmitters provided with a screen protective tube ("clamp" tube) is shown in Fig. 10-11. An audio-frequency signal is applied to the grid of the clamp tube, which then becomes a modulator. The simplicity of the circuit is somewhat deceptive, since it is considerably more difficult from a design standpoint than the transformer-coupled arrangement of Fig. 10-10.

For proper modulation the clamp tube must be operated as a triode Class A amplifier; the method is essentially identical with the chokecoupled Class A plate modulator of Fig. 10-8 except that a resistance, R₂, is substituted for the choke. R₂, in the usual case, is the screen dropping resistor normally used for c.w. operation. Its value should be at least two or three times the load resistance required by the Class A modulator tube for optimum audio-frequency output.

Like the choke-coupled modulator, the clamptube modulator is incapable of modulating the r.f. stage 100 per cent unless the dropping resistor, R_1 , and audio bypass, C_1 , are incorporated in the circuit. The same design considerations hold, with the addition of the fact that the screen must be driven negative, not just to zero voltage, for 100 per cent modulation. The modulator tube must thus be operated at a voltage ranging from 20 to 40 per cent higher than the modulated screen.

Adjustment with this system, once the design voltages have been determined, is carried out in the same way as with transformer-coupled screen modulation, preferably with the oscilloscope. Without the oscilloscope, the amplifier may first be adjusted for c.w. operation as described earlier, but with the modulator tube removed from its socket. The modulator is then replaced, and the cathode resistance, R_3 , adjusted to reduce the amplifier plate current to one-half its c.w. value. The amplifier plate current should remain constant with modulation, or show just a small upward flicker on occasional voice peaks.

Controlled Carrier

As explained earlier, a limit is placed on the output obtainable from a grid-modulation system by the low r.f. amplifier plate efficiency (approximately 33 per cent) under unmodulated carrier conditions. The plate efficiency increases with modulation, since the output increases while the d.c. input remains constant, and reaches a maximum process.

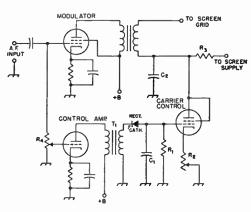


Fig. 10-12—Circuit for carrier control with screen modulation. A small triode such as the 6C4 can be used as the control amplifier and a 6Y6G is suitable as a carrier-control tube. T_1 is an interstage audio transformer having a 1-to-1 or larger turns ratio. R_4 is a 0.5-megohm volume control and also serves as the grid resistor for the modulator. A germanium crystal may be used as the rectifier. Other values are discussed in the text.

mum in the neighborhood of 50 per cent with 100 per cent sine-wave modulation. If the power input to the amplifier can be reduced during periods when there is little or no modulation, thus reducing the plate loss, advantage can be taken of the higher efficiency at full modulation to obtain higher effective output. This can be done by varying the d.c. power input to the modulated stage in accordance with average variations in voice intensity, in such a way as to maintain just sufficient carrier power to keep the modulation high, but not exceeding 100 per cent, under all conditions. Thus the carrier amplitude is controlled by the average voice intensity. Properly utilized, controlled carrier permits increasing the carrier output at maximum level to a value about equal to the rated plate dissipation of the tube, twice the output obtainable with constant carrier.

It is desirable to control the power input just enough so that the plate loss, without modulation, is safely below the tube rating. Excessive control is disadvantageous because the distant receiver's a.v.c. system must continually follow the variations in average signal level. The circuit of Fig. 10-12 permits adjustment of both the maximum and minimum power input, and although somewhat more complicated than some circuits that have been used is actually simpler to operate because it separates the functions of modulation and carrier control. A portion of the audio voltage at the modulator grid is applied to a Class A "control amplifier" which drives a rectifier circuit to produce a d.c. voltage negative with respect to ground. C_1 filters out the audio variations, leaving a d.c. voltage proportional to the average voice level. This voltage is applied to the grid of a "clamp" tube to control the d.c. screen voltage and thus the r.f. carrier level. Maximum output is obtained when the carrier-

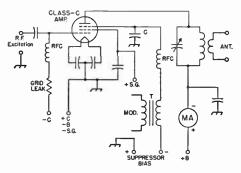


Fig. 10-13—Suppressor-grid modulation of an r.f. amplifier using a pentode-type tube. The suppressor-grid r.f. bypass capacitor, C, should be the same as the grid bypass capacitor in control-grid modulation.

control tube grid is driven to cut-off, the voice level at which this occurs being determined by the setting of R_4 . The input without modulation is set to the desired level (usually about equal to the plate dissipation rating of the modulated stage) by adjusting R_2 . R_3 may be the normal screen-dropping resistor for the modulated beam tetrode, but in case a separate screen supply is used the resistance need be just large enough to give sufficient voltage drop to reduce the normodulation power input to the desired value.

 C_1R_1 and C_2R_3 should have a time constant of about 0.1 second. An oscilloscope is required for proper adjustment.

Suppressor Modulation

Pentode-type tubes do not, in general, modulate well when the modulating voltage is applied to the screen grid. However, a satisfactory modulation characteristic can be obtained by applying the modulation to the suppressor grid. The circuit arrangement for suppressor-grid modulation of a pentode tube is shown in Fig. 10-13.

The method of adjustment closely resembles that used with screen-grid modulation. If an oscilloscope is not available, the amplifier is first adjusted for optimum c.w. output with zero bias on the suppressor grid. Sufficient negative bias is then applied to the suppressor to drop the plate current and r.f. output current to half their original values. The amplifier is then ready for modulation

Since the suppressor is always negatively biased, the modulator is not required to furnish any power and a voltage amplifier can be used. The suppressor bias will vary with the type of pentode and the operating conditions, but usually will be of the order of -100 volts. The peak a.f. voltage required from the modulator is equal to the suppressor bias.

Control-Grid Modulation

Although control-grid modulation may be used with any type of r.f. amplifier tube, it is seldom used with tetrodes and pentodes because screen or suppressor modulation is generally

Types of Modulation

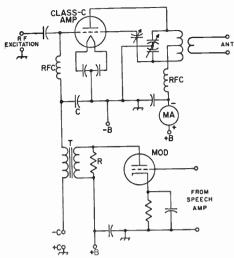


Fig. 10-14—Control-grid modulation af a Class C amplifier. The r.f. grid bypass capacitar, C, shauld have high reactance at audio frequencies (0.005 μ f. ar less).

simpler to adjust. However, control-grid modulation is the only form of grid modulation that is applicable to triode amplifiers. A typical triode circuit is given in Fig. 10-14.

In control-grid modulation the d.c. grid bias is the same as in normal Class C amplifier service, but the r.f. grid excitation is somewhat smaller. The audio voltage superimposed on the d.c. bias changes the instantaneous grid bias at an audio rate, thus varying the operating conditions in the grid circuit and controlling the output and efficiency of the amplifier.

The change in instantaneous bias voltage with modulation causes the rectified grid current of the amplifier to vary, which places a variable load on the modulator. To reduce distortion, resistor R in Fig. 10-14 is connected in the output circuit of the modulator as a constant load, so that the over-all load variations will be minimized. This resistor should be equal to or somewhat higher than the load into which the modulator tube is rated to work at normal audio output. It is also recommended that the modulator circuit incorporate as much negative feedback as possible, as a further aid in reducing the internal resistance of the modulator and thus improving the "regulation"-that is, reducing the effect of load variations on the audio output voltage. The turns ratio of transformer T should be about 1 to 1 in most cases.

The load on the r.f. driving stage also varies with modulation. This in turn will cause the excitation voltage to vary and may cause the modulation characteristic to be nonlinear. To overcome it, the driver should be capable of two or three times the r.f. power output actually required to drive the amplifier. The excess power may be dissipated in a dummy load (such as an incandescent lamp of appropriate power rating) that then performs the same function in the r.f.

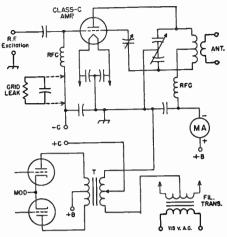


Fig. 10-15—Circuit arrangement for cathode madulation of a Class C r.f. amplifier. Values of bypass capacitors in the r.f. circuits should be the same as far other modulation methads.

circuit that resistor R does in the audio circuit. The d.c. bias source in this system should have low internal resistance. Batteries or a voltageregulated supply are suitable. Grid-leak bias should not be used.

Satisfactory adjustment of a control-grid modulated amplifier requires an oscilloscope. The scope connections are similar to those for screengrid modulation, with audio from the modulator's output transformer secondary applied to the horizontal plates through a blocking capacitor and volume control, and with r.f. from the plate tank circuits coupled to the vertical plates. The adjustment procedure follows that for screen modulation as previously described.

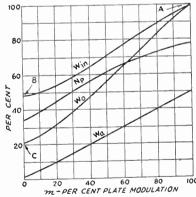


Fig. 10-16—Cathade-modulation performance curves, in terms of percentage of plate madulation plotted against percentage af Class C telephany tube ratings. W_{in}-D.c. plate input watts in terms of percentage of plate-madulation rating.

Wo —Carrier autput watts in per cent af plate-modulatian rating (based an plate efficiency of 77.5%).

Wa —Audio pawer in per cent af d.c. watts input.

N_p —Plate efficiency of the amplifier in percentage.

AMPLITUDE MODULATION

CATHODE MODULATION

The fundamental circuit for cathode modulation is shown in Fig. 10-15. It is a combination of the plate and grid methods, and permits a carrier efficiency midway between the two. Audio power is introduced in the cathode circuit, and both grid bias and plate voltage are modulated.

Because part of the modulation is by the control-grid method, the plate efficiency of the modulated amplifier must vary during modulation. The carrier efficiency therefore must be lower than the efficiency at the modulation peak. The required reduction in efficiency depends upon the proportion of grid modulation to plate modulation; the higher the percentage of plate modulation, the higher the permissible carrier efficiency, and vice versa. The audio power required from the modulator also varies with the percentage of plate modulation, being greater as this percentage is increased.

The way in which the various quantities vary is illustrated by the curves of Fig. 10-16. In these curves the performance of the cathode-modulated r.f. amplifier is plotted in terms of the tube ratings for plate-modulated telephony, with the percentage of plate modulation as a base. As the percentage of plate modulation is decreased, it is assumed that the grid modulation is increased to make the over-all modulation reach 100 per cent. The limiting condition, 100 per cent plate modulation and no grid modulation, is at the right (A); pure grid modulation is represented by the left-hand ordinate (B and C).

Modulating Impedance

The modulating impedance of a cathodemodulated amplifier is approximately equal to

$$m\frac{E_b}{I_b}$$

where m = Percentage of plate modulation (expressed as a decimal)

 $E_b = D.c.$ plate voltage on modulated amplifier

I_b = D.c. plate current of modulated amplifier

The modulating impedance is the load into which the modulator must work, just as in the case of pure plate modulation. This load must be matched to the load required by the modulator tubes by proper choice of the turns ratio of the modulation transformer.

Conditions for Linearity

R.f. excitation requirements for the cathodemodulated amplifier are midway between those for plate modulation and control-grid modulation. More excitation is required as the percentage of plate modulation is increased. Grid bias should be considerably beyond cut-off; fixed bias from a supply having good voltage regulation is preferred, especially when the percentage of plate modulation is small and the amplifier is operating more nearly like a grid-bias modulated stage. At the higher percentages of plate modulation a combination of fixed and grid-leak bias can be used, since the variation in rectified grid current is smaller. The grid leak should be bypassed for audio frequencies. The percentage of grid modulation may be regulated by choice of a suitable tap on the modulation-transformer secondary.

The cathode circuit of the modulated stage must be independent of other stages in the transmitter. When directly heated tubes are modulated their filaments must be supplied from a separate transformer. The filament bypass capacitors should not be larger than about $0.002 \, \mu f$, to avoid bypassing the a.f. modulation.

Adjustment of Cathode-Modulated Amplifiers

In most respects, the adjustment procedure is similar to that for grid-bias modulation. The critical adjustments are antenna loading, grid bias, and excitation.

Adjustments should be made with the aid of an oscilloscope connected in the same way as for grid-bias modulation. With proper antenna loading and excitation, the normal wedge-shaped pattern will be obtained at 100 per cent modulation. As in the case of grid-bias modulation, too light antenna loading will cause flattening of the upward peaks of modulation as also will too high excitation. The cathode current will be practically constant with or without modulation when the proper operating conditions have been established.

LINEAR AMPLIFIERS

If a signal is to be amplified after modulation has taken place, the shape of the modulation envelope must be preserved if distortion is to be avoided. This requires the use of a linear amplifier—that is, one that will reproduce, in its output circuit, the exact form of the signal envelope applied to its grid.

The amplitude-modulated driving signal for a linear amplifier can at no time be permitted to swing below cutoff on the modulation downpeaks. To do so would mean that the part of the modulation envelope near the zero axis (see Fig. 10-1C) would be clipped, since there would be times when the instantaneous signal voltage would be below the minimum value that would cause plate-current flow (see Fig. 10-3).

However, the grid bias may be set at any value less than cutoff. Usually, such amplifiers are operated at or near the Class B condition — that is, with the grid bias at or somewhat less than cutoff. Although Class B operation results in considerable distortion of the individual r.f. cycles applied to the grid, the modulation *cnvelope* is not distorted if the operating conditions are chosen properly. The r.f. distortion produces only r.f. harmonics, and these can be eliminated by the selectivity of the output tank circuit.

A linear amplifier used for a.m. has the same

Oscilloscope Patterns

disadvantages with respect to efficiency that grid modulation does. The reason also is much the same: since the amplifier must handle a peakenvelope power four times as great as the unmodulated carrier power, it cannot be operated at its full capabilities when it is amplifying only the unmodulated carrier. The plate efficiency of the amplifier varies with the instantaneous value of the modulation envelope (Fig. 10-9). The efficiency at the unmodulated carrier level is only of the order of 30-35 per cent.

Because of this low efficiency, linear amplifiers have not had much application in amateur transmitters, especially since equivalent efficiency can be obtained with grid modulation, along with a less critical adjustment procedure. Recently there has been some increase in use of a.m. linears, particularly at v.h.f., as a means of stepping up the modulated power output of very low power transmitters with a minimum of complication in over-all equipment and operation. To obtain a useful increase in power output by this means the linear amplifier must use a tube or tubes capable of relatively large plate dissipation, since about two-thirds of the d.c. power input to the amplifier is consumed in heating the plate and only about one-third is converted to useful carrier output.

CHECKING A.M. PHONE OPERATION

USING THE OSCILLOSCOPE

Proper adjustment of a phone transmitter is aided immeasurably by the oscilloscope. The scope will give more information, more accurately, than almost any collection of other instruments that might be named. Furthermore, an oscilloscope that is entirely satisfactory for the purpose is not necessarily an expensive instrument; the cathode-ray tube and its power supply are about all that are needed. Amplifiers and linear sweep circuits are by no means necessary.

In the simplest scope circuit, radio-frequency voltage from the modulated amplifier is applied to the vertical deflection plates of the tube, usually through blocking capacitors as shown in the oscilloscope circuit in the chapter on measurements, and audio-frequency voltage from the modulator is applied to the horizontal deflection plates. As the instantaneous amplitude of the audio signal varies, the r.f. output of the transmitter likewise varies, and this produces a wedge-shaped pattern or trapezoid on the screen. If the oscilloscope has a built-in horizontal sweep, the r.f. voltage can be applied to the vertical plates as before (never through an amplifier) and the sweep will produce a pattern that follows the modulation envelope of the transmitter output, provided the sweep frequency is lower than the modulation frequency. This produces a wave-envelope modulation pattern.

The Wave-Envelope Pattern

The connections for the wave-envelope pattern are shown in Fig. 10-17A. The vertical deflection plates are coupled to the amplifier tank coil (or an antenna coil) through a low-impedance (coax, twisted pair, etc.) line and pick-up coil. As shown in the alternative drawing, a resonant circuit tuned to the operating frequency may be connected to the vertical plates, using link coupling between it and the transmitter. This will eliminate r.f. harmonics, and the tuning control is a means for adjustment of the pattern height.

If it is inconvenient to couple to the final tank coil, as may be the case if the transmitter is tightly shielded, the pick-up loop may be coupled to the tuned tank of a matching circuit or an-

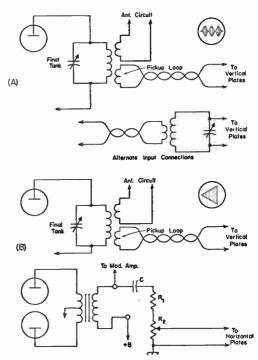


Fig. 10-17—Methods of connecting the oscilloscope for modulation checking. A—connections for wave-envelope pattern with any modulation method; B—connections for trapezoidal pattern with plate or screen modulation.

tenna coupler. Any method (even a short antenna coupled to the tuned circuit shown in the "alternate input connections" of Fig. 10-17A) that will pick up enough r.f. to give a suitable pattern height may be used.

The position of the pick-up coil should be varied until an unmodulated carrier pattern, Fig. 10-18B, of suitable height is obtained. The horizontal sweep voltage should be adjusted to make the width of the pattern somewhat more than half the diameter of the screen. When voice modulation is applied, a rapidly changing pattern of varying height will be obtained. When the

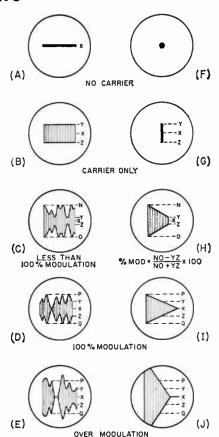


Fig. 10-18—Wave-envelope and trapezoidal patterns representing different conditions of modulation.

maximum height of this pattern is just twice that of the carrier alone, the wave is being modulated 100 per cent. This is illustrated by Fig. 18-18D, where the point X represents the horizontal sweep line (reference line) alone, YZ is the carrier height, and PQ is the maximum height of the modulated wave.

If the height is greater than the distance PQ, as illustrated in E, the wave is overmodulated in the upward direction. Overmodulation in the downward direction is indicated by a gap in the pattern at the reference axis, where a single bright line appears on the screen. Overmodulation in either direction may take place even when the modulation in the other direction is less than 100 per cent.

The Trapezoidal Pattern

Connections for the trapezoid or wedge pattern as used for checking a.m. are shown in Fig. 10-17B. The vertical plates of the c.r. tube are coupled to the transmitter tank through a pick-up loop, preferably using a tuned circuit, as shown in the upper drawing, adjustable to the operating frequency. Audio voltage from the modulator is applied to the horizontal plates through a voltage divider, R_1R_2 . This voltage should be

AMPLITUDE MODULATION

adjustable so a suitable pattern width can be obtained; a 0.25-megohm volume control can be used at R_2 for this purpose.

The resistance required at R_1 will depend on the d.c. voltage on the modulated element. The total resistance of R_1 and R_2 in series should be about 0.25 megohm for each 100 volts. For example, if a plate-modulated amplifier operates at 1500 volts, the total resistance should be 3.75 megohms, 0.25 megohm at R_2 and the remainder, 3.5 megohms, in R_1 . R_1 should be composed of individual resistors not larger than 0.5 megohm each, in which case 1-watt resistors will be satisfactory.

For adequate coupling at 100 cycles the capacitance, in microfarads, of the blocking capacitor, C, should be at least 0.05/R, where R is the total resistance $(R_1 + R_2)$ in megohms. In the example above, where R is 3.75 megohms, the capacitance should be $0.05/3.75 = 0.013 \mu f$, or

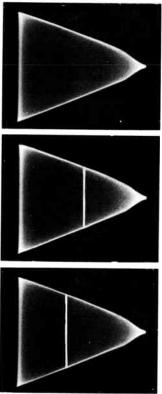


Fig. 10-19—Top—A typical trapezoidal pattern obtained with screen modulation adjusted for optimum conditions. The sudden change in slope near the point of the wedge occurs when the screen voltage passes through zero. Center—If there is no oudio distortion, the unmodulated carrier will have the height and position shown-by the white line superimposed on the sine-wave modulation pattern. Bottom—Even-harmonic distortion in the audio system, when the audio signal applied to the speech amplifier is a sine wave, is indicated by the fact that the modulation pattern does not extend equal horizontal distances on both sides of the unmodulated carrier.

more. The voltage rating of the capacitor should be at least twice the d.c. voltage applied to the modulated element.

Trapezoidal patterns for various conditions of modulation are shown in Fig. 10-18 at F to J, each alongside the corresponding wave-envelope pattern. With no signal, only the cathode-ray spot appears on the screen. When the unmodulated carrier is applied, a vertical line appears; the length of the line should be adjusted, by means of the pick-up coil coupling, to a convenient value. When the carrier is modulated. the wedge-shaped pattern appears; the higher the modulation percentage, the wider and more pointed the wedge becomes. At 100 per cent modulation it just makes a point on the axis, X, at one end, and the height, PQ, at the other end is equal to twice the carrier height, YZ. Overmodulation in the upward direction is indicated by increased height over PQ, and downward by an extension along the axis X at the pointed end.

CHECKING TRANSMITTER PERFORMANCE

The trapezoidal pattern is generally more useful than the wave-envelope pattern for checking the operation of a phone transmitter. However, both types of patterns have their special virtues, and the best test setup is one that makes both available. The trapezoidal pattern is better adapted to showing the performance of a modulated amplifier from the standpoint of inherent linearity, without regard to the wave form of the audio modulating signal, than is the wave-envelope pattern. Distortion in the audio signal also can be detected in the trapezoidal pattern, although experience in analyzing scope patterns is required to recognize it.

If the wave-envelope pattern is used with a

sine-wave audio modulating signal, distortion in the modulation envelope is easily recognizable; however, it is difficult to determine whether the distortion is caused by lack of linearity of the r.f. stage or by a.f. distortion in the modulator. If the trapezoidal pattern shows good linearity in such a case the trouble obviously is in the audio system. It is possible, of course, for both defects to be present simultaneously. If they are, the r.f. amplifier should be made linear first; then any distortion in the modulation envelope will be the result of improper operation in the speech amplifier or modulator, or in coupling the modulator to the modulated r.f. stage.

R. F. Linearity

The trapezoidal pattern is a graph of the modulation characteristic of the modulated amplifier. The sloping sides of the wedge show the r.f. amplitude for every value of instantaneous modulating voltage, exactly the type of curve plotted in Fig. 10-4. If these sides are perfectly straight lines, as drawn in Fig. 10-18 at H and I, the modulation characteristic is linear. If the sides show curvature, the characteristic is nonlinear to an extent shown by the degree to which the sides depart from perfect straightness. This is true regardless of the modulating wave form.

Audio Distortion

If the speech system can be driven by a good audio sine-wave signal instead of a microphone, the trapezoidal pattern also will show the presence of even-harmonic distortion (the most common type, especially when the modulator is overloaded) in the speech amplifier or modulator. If there is no distortion in the audio system, the trapezoid will extend horizontally equal distances on each side of the vertical line representing the

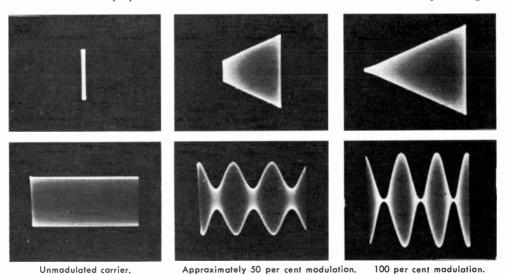


Fig. 10-20—Oscillascope patterns showing proper modulation of a plate-and-screen modulated tetrode r.f. amplifier. Upper row, trapezoidal patterns; lower row, corresponding wave-envelope patterns. In the latter a linear sweep having a frequency one-third that of the sine-wave audio modulating frequency was used, sa that three cycles of the modulation envelope show in the pattern.

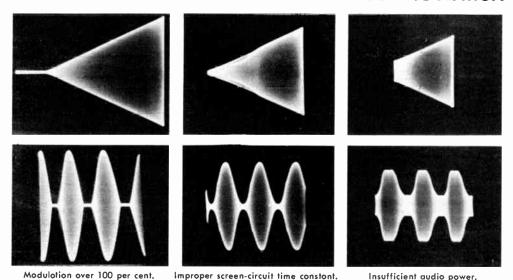


Fig. 10-21—Improper operation or design. These pictures are to the same scale as thase in Fig. 20-20, on the same transmitter and with the same test setup.

unmodulated carrier. If there is even-harmonic distortion the trapezoid will extend farther to one side of the unmodulated-carrier position than to the other. This is shown in Fig. 10-19. The probable cause is inadequate power output from the modulator, or incorrect load on the modulator.

An audio oscillator having reasonably good sine-wave output is highly desirable for testing both speech equipment and the phone transmitter as a whole. With an oscillator and the scope, the pattern is steady and can be studied closely to determine the effects of adjustments.

In the case of the wave-envelope pattern, distortion in the audio system will show up in the modulation envelope (with a sine-wave input signal) as a departure from the sine-wave form, and may be checked by comparing the envelope with a drawing of a sine-wave. Attributing any such distortion to the audio system assumes, of course, that a check has been made on the linearity of the modulated r.f. amplifier, preferably by use of the trapezoidal pattern.

Typical Patterns

Figs. 10-19, 10-20 and 10-21 show some typical scope patterns of modulated signals for different conditions of operation. The screen-modulation patterns, Fig. 10-19, also show how the presence of even-harmonic audio distortion can be detected in the trapezoidal pattern. The pattern to be sought in adjusting the transmitter is the one at the top in Fig. 10-20, where the top and bottom edges of the pattern continue in straight lines up to the point representing 100 per cent modulation. If these edges tend to bend over toward the horizontal at the maximum height of the wedge the amplifier is "flattening" on the modulation up-peaks. This is usually caused by attempting to get too large a carrier output, and can be corrected by tighter coupling to the antenna or by a decrease in the d.c. screen voltage.

Fig. 10-20 shows patterns indicating proper operation of a plate-and-screen modulated tetrode r.f. amplifier. The slight "tailing off" at the modulation down peak (point of the wedge) can be minimized by careful adjustment of excitation and plate loading.

Several types of improper operation are shown in Fig. 10-21. In the photos at the left the linearity of the r.f. stage is good but the amplifier is being modulated over 100 per cent. This is shown by the maximum height of the pattern (compare with the unmodulated carrier of Fig. 10-20) and by the bright line extending from the point of the wedge (or between sections of the envelope).

The patterns in the center, Fig. 10-21, show the effect of a too-long time constant in the screen circuit, in an amplifier getting its screen voltage through a dropping resistor, both plate and screen being modulated. The "double-edged" pattern is the result of audio phase shift in the screen circuit combined with varying screen-tocathode resistance during modulation. The overall effect is to delay the rise in output amplitude during the up-sweep of the modulation cycle, slightly distorting the modulation envelope as shown in the wave-envelope pattern. This effect, which becomes more pronounced as the audio modulating frequency is increased, is usually absent at low modulation percentages but develops rapidly as the modulation approaches 100 per cent. It can be reduced by reducing the screen bypass capacitance, and also by connecting resistance (to be determined experimentally, but of the same order as the screen dropping resistance) between screen and cathode.

The right-hand pictures in Fig. 10-21 show the effect of insufficient audio power. Although the trapezoidal pattern shows good linearity in the r.f. amplifier, the wave-envelope pattern shows

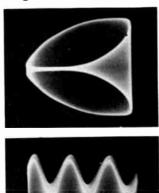


Fig. 10-22—Upper photo—Audio phose shift in coupling circuit between transmitter and horizontal deflection plates. Lower photo—Hum on vertical deflection plates.

flattened peaks (both positive and negative) in the modulation envelope even though the audio signal applied to the amplifier was a sine wave. More speech-amplifier gain merely increases the flattening without increasing the modulation percentage in such a case. The remedy is to use a larger modulator or less input to the modulated r.f. stage. In some cases the trouble may be caused by an incorrect modulation-transformer turns ratio, causing the modulator to be overloaded before its maximum power output capabilities are reached.

Faulty Patterns

The pattern defects shown in Fig. 10-21 are only a few out of many that might be observed in the testing of a phone transmitter, all capable of being interpreted in terms of improper operation in some part of the transmitter. However, it is not always the transmitter that is at fault when the scope shows an unusual pattern. The trouble may be in some defect in the test setup.

Patterns representative of two common faults of this nature are shown in Fig. 10-22. The upper picture shows the trapezoidal pattern when the audio voltage applied to the horizontal plates of the c.r. tube is not exactly in phase with the modulation envelope. The normal straight edges of the wedge are transformed into ellipses which in the case of 100 per cent modulation (shown) touch at the horizontal axis and reach maximum heights equal to the height of the normal wedge at the modulation up-peak. Such a phase shift can occur (and usually will) if the audio voltage applied to the c.r. tube deflection plates is taken from any point in the audio system other than where it is applied to the modulated r.f. stage. The coupling capacitor shown in Fig. 10-17 must have very low reactance compared with the resistance of R_1 and R_2 in series — not larger than a few per cent of the sum of the two resistances.

The wave-envelope pattern in Fig. 10-22 shows the effect of hum on the vertical deflection plates. This may actually be on the carrier or may be introduced in some way from the a.c. line through stray coupling between the scope and the line or because of poor grounding of the scope, transmitter or modulator.

It is important that r.f. from the *modulated stage only* be coupled to the oscilloscope, and then only to the vertical plates. If r.f. is present also on the horizontal plates, the pattern will lean to one side instead of being upright. If the oscilloscope cannot be moved to a position where the unwanted pick-up disappears, a small bypass capacitor (10 $\mu\mu$ f. or more) should be connected across the horizontal plates as close to the eathode-ray tube as possible. An r.f. choke (2.5 mh. or smaller) may also be connected in series with the ungrounded horizontal plate.

MODULATION CHECKING WITH THE PLATE METER

The plate milliammeter of the modulated amplifier provides a simple and fairly reliable means for checking the performance of a phone transmitter, although it does not give nearly as definite information as the oscilloscope does. If the modulated amplifier is perfectly linear, its plate current will not change when modulation is applied if

1) the upward modulation percentage does not exceed the modulation capability of the amplifier,

2) the downward modulation does not exceed 100 per cent, and

3) there is no change in the d.c. operating voltages on the transmitter.

The plate current should be constant, ideally, with any of the methods of modulation discussed in this chapter, with the single exception of the controlled-carrier system. The plate meter cannot give a reliable check on the performance of the latter system because the plate current increases with the intensity of modulation.

Plate Modulation

With plate modulation, a downward shift in plate current may indicate one or more of the following:

- 1) Insufficient excitation.
- 2) Insufficient grid bias.
- 3) R.f. amplifier not loaded properly.
- Insufficient output capacitance in the filter of the modulated-amplifier plate supply.
- Excessive d.c. input to the r.f. amplifier, under carrier conditions. Alternately, the cathode emission of the amplifier tubes may be low.
- 6) In plate-and-screen modulation of tetrodes or pentodes, the screen is not being sufficiently modulated along with the plate. If the d.c. screen voltage is obtained through a dropping resistor, a dip in plate current may occur if the screen bypass capacitance is large enough to bypass audio frequencies.
- 7) Poor voltage regulation of the modulated-

amplifier plate supply. It is readily checked by measuring the voltage with and without modulation. Poor line regulation will be shown by a drop in filament voltage with modulation.

Any of the following may cause an upward shift in plate current:

- Overmodulation (excessive audio power, audio gain too high).
- Incomplete neutralization of the modulated amplifier.
- Parasitic oscillation in the modulated amplifier.

Grid Modulation

With any type of grid modulation, any of the following may cause a downward shift in modulated-amplifier plate current:

- 1) Too much r.f. excitation.
- Insufficient grid bias with control-grid modulation. Grid bias is usually not critical with screen and suppressor modulation.
- 3) With control-grid modulation, excessive resistance in the bias supply.
- Insufficient output capacitance in platesupply filter.
- 5) Amplifier is not loaded heavily enough.

Because grid modulation is not perfectly linear, (always less so than plate modulation) an amplifier that is properly designed and operated may show a small upward plate-current shift with modulation, 10 per cent or less with sinewave modulation and amounting to an occasional upward flicker with voice. An upward plate current shift in excess of this may be caused by

- Overmodulation (excessive modulating voltage).
- 2) Regeneration (incomplete neutralization).
- With control-grid or suppressor modulation, bias too great.
- With screen modulation, d.c. screen voltage too low.
- 5) Audio distortion in modulator.

In grid-modulation systems the modulator is not *necessarily* operating linearly if the plate current stays constant with or without modulation. It is readily possible to arrive at a set of operating conditions in which flattening of the up-peaks is just balanced by overmodulation downward. The oscilloscope provides the only certain check on grid modulation.

COMMON TROUBLES IN THE PHONE TRANSMITTER

Noise and Hum on Carrier

Noise and hum may be detected by listening to the signal on a receiver, provided the receiver is far enough away from the transmitter to avoid overloading. The hum level should be low compared with the voice at 100 per cent modulation. Hum may come either from the speech amplifier and modulator or from the r.f. section of the transmitter. Hum from the r.f. section can be detected by completely shutting off the modulator; if hum remains, the power-supply filters

for one or more of the r.f. stages have insufficient smoothing. With a hum-free carrier, hum introduced by the modulator can be checked by turning on the modulator but leaving the speech amplifier off; power-supply filtering is the likely source of such hum. If carrier and modulator are both clean, connect the speech amplifier and observe the increase in hum level. If the hum disappears with the gain control at minimum, the hum is being introduced in the stage or stages preceding the gain control. The microphone also may pick up hum, a condition that can be checked by removing the microphone from the circuit but leaving the first speech-amplifier grid circuit otherwise unchanged. A good ground (to a cold water pipe, for example) on the microphone and speech system usually is essential to humfree operation.

Spurious Sidebands

A superheterodyne receiver having good selectivity (bandwidth of less than 1 kc.) is needed for checking spurious sidebands outside the normal communication channel. The r.f. input to the receiver must be kept low enough, by removing the antenna or by adequate separation from the transmitter, to avoid overloading and consequent spurious receiver responses. An "S"-meter reading of about half scale is satisfactory. With the selectivity at its sharpest, tune through the region outside the normal channel limits (3 to 4 kilocycles each side of the carrier) while another person talks into the microphone. Spurious sidebands will be observed as intermittent "clicks" or crackles well away from the carrier frequency. Sidebands more than 3 to 4 kc. from the carrier should be of negligible strength, compared with the carrier, in a properly modulated phone transmitter. The causes are overmodulation or nonlinear operation.

With sine-wave modulation the relative intensities of sidebands can be observed if a tone of 1000 cycles or so is used. The "S"-meter will show how the spurious side frequencies (those spaced more than the modulating frequency from the carrier) compare with the carrier itself. Without an "S"-meter, the a.v.c. should be turned off and the b.f.o. turned on; then the r.f. gain should be set to give a moderately strong beat note with the carrier. The intensity of the side frequencies can be estimated from their relative strengths as the receiver is tuned through them.

Receivers having steep-sided band-pass filters for single-sideband reception can be used, but the technique is more difficult. If the band pass is, say, 3 kc., the signal should first be tuned in with the carrier placed at one edge of the pass band. If it is placed at the low edge, for example, the receiver should then be tuned 3 kc. higher so its response will be in the region just outside the normal spectrum space occupied by one sideband. Any "crackles" heard in this region represent the results of nonlinearity of over-modulation. This assumes that the precautions mentioned above with respect to receiver overloading have been carefully observed.

R.F. in Speech Amplifier

A small amount of r.f. current in the speech amplifier — particularly in the first stage, which is most susceptible to such r.f. pickup — will cause overloading and distortion in the low-level stages. Frequently also there is a regenerative effect which causes an audio-frequency oscillation or "howl" to be set up in the audio system. In such cases the gain control cannot be advanced very far before the howl builds up, even though the amplifier may be perfectly stable when the r.f. section of the transmitter is not turned on.

Complete shielding of the microphone, microphone cord, and speech amplifier is necessary to prevent r.f. pickup, and a ground connection separate from that to which the transmitter is connected is advisable.

If the transmitter is "hot" with r.f., the cause usually is to be found in the method of coupling to the antenna. Any form of coupling that involves either a direct or capacitive connection between the transmitter and the transmission line is likely to cause the transmitter chassis to assume an r.f. potential above ground because of "parallel" type currents on the line. An earth connection to the transmitter does not always help in such a case. The best remedy is to use inductive coupling between the transmitter and line

MODULATION MONITORING

It is always desirable to modulate as fully as possible, but 100 per cent modulation should not be exceeded — particularly in the downward direction — because harmonic distortion will be generated and the channel width increased. This causes unnecessary interference to other stations. The oscilloscope is the best instrument for continuously checking the modulation. However, simpler indicators may be used for the purpose, once calibrated.

A convenient indicator, when a Class B modulator is used, is the plate milliammeter in the Class B stage, since the plate current of the modulator fluctuates with the voice intensity. Using the oscilloscope, determine the gain-control setting and voice intensity that give 100 per cent modulation on voice peaks, and simultaneously observe the maximum Class B plate-milliammeter reading on the peaks. When this maximum reading is obtained, it will suffice to adjust the gain so that it is not exceeded.

A high-resistance (1000-ohms-per-volt or more) rectifier-type voltmeter (copper-oxide or germanium type) also can be used for modulation monitoring. It should be connected across the output circuit of an audio driver stage where the power level is a few watts, and similarly calibrated against the oscilloscope to determine the reading that represents 100 per cent modulation.

The plate milliammeter of the modulated r.f. stage also is of value as an indicator of overmodulation, as explained earlier.

A. M. MODULATION MONITOR

The modulation monitor shown in Figs. 10-23 and 10-25 uses two magic-eye tubes and a dual diode. One eye closes whenever the modulation reaches 50 per cent or more, and the second eye closes when the modulation hits 85 per cent or more. In operation, the operator controls his speech to close the "50%" eye much of the time without closing the "85%" eye except on rare occasions. No adjustment of the monitor is required other than the setting of two intensity controls for the ambient light condition. The monitor, with the constants to be described, will work with any plate-modulated amplifier at volt-

ages between 300 and 500; with a slight modification it can be extended to 750 volts.

The circuit diagram is shown in Fig. 10-24. A voltage divider, consisting of R_1 , R_2 plus R_3 , and R_4 , is connected across the plate supply of the modulated stage. The cathodes of two diodes are connected to the modulated voltage applied to the r.f. amplifier, and the anodes of the two diodes are connected through 100K resistors to the junctions on the voltage divider. The voltage divider is proportioned so that the cathode of V_1 is at approximately 50 per cent of the plate supply voltage and the cathode of V_2 is at 15 per cent of the voltage. When the instantaneous voltage is 50 per cent or less of the idling plate voltage, as during the negative portion of a modulation cycle, the upper diode of V_3 will conduct and the voltage drop across the associated 100K resistor will close the eye of V_1 . If during the negative portion of the cycle the instantaneous

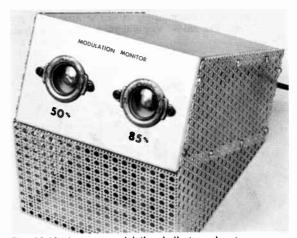


Fig. 10-23—An a.m. modulation indicator using two inexpensive magic eye tubes. It is to be connected to the plate supply and modulation transformer of the plate-modulated transmitter stage. The monitor is built in one half of a Minibox and the entire assembly is supported by a cone-metal housing. Heater transformers hang down from the Minibox, inside the housing.

voltage goes as low as 15 per cent of the supply voltage, the lower diode of V_3 will conduct and the drop across the associated 100K resistor will close the eye of V_2 . Capacitors at the grids of V_1 and V_2 make the edges of the closing eyes readily visible.


Type 1629 magic eye tubes are used because they are common tubes in radio surplus stores and are quite inexpensive. Because they have a limited cathode-to-heater voltage rating, it is necessary to use a separate heater transformer with its center tap connected to a midpoint on the voltage divider. For similar insulation reasons, a separate heater transformer is used for the twin diode, V_3 .

Construction

With the exception of the transformers, all components are mounted inside a $5 \times 7 \times 3$ -inch Minibox. A supporting housing for the chassis is made from a small piece of Reynolds No. 33 aluminum mesh, available in many hardware stores. A 3/8-inch lip bent in on the bottom edge provides greater rigidity for the structure and a surface to which four rubber feet can be attached. The monitor is built within one half of the Minibox and the two transformers are mounted on the other side of this half. Two Amphenol 58-MEA8 assemblies are used to support the magic eye tubes; these include the mounting brackets, the sockets and wires, the light shields and the metal escutcheons. The 6H6 socket is supported off the chassis by two 3/4-inch ceramic insulators.

Operation

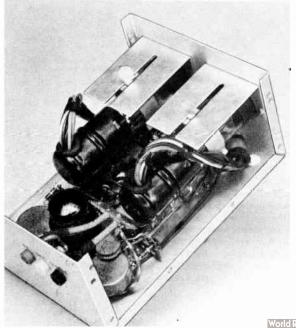When using the monitor with a transmitter, the only adjustment necessary is that of the two 100K intensity controls. The "50%" eye will start to close at about 50 per cent modulation and will be completely closed at around 70 per cent. The "85%" eye will start to close at about



AMPLITUDE MODULATION

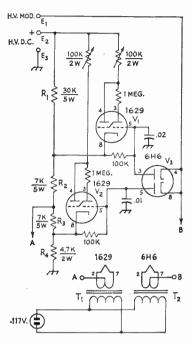


Fig. 10-24—Circuit diagram of the modulation manitar. Unless specified atherwise, resistars are $\frac{1}{2}$ watt, resistances are in ahms, capacitances are in μf .

C₁, C₂-Disk ceramic.

E₁, E₂, E₃—Insulated tip jacks (Jahnson 105—601, —602, —603)

 T_1 -12.6-v. 2-a. transfarmer (Knight 61 G 420) T_2 -6.3-v. 0.6-a. transfarmer (Knight 61 G 416) 85 per cent and be completely closed at 100 per cent modulation.

Higher Voltages

If the monitor is to be used at supply voltages between 500 and 750, several alterations are required. Either the "50%" eye must be eliminated or a second 12.6-volt transformer must be added (so that each 1629 has its own heater supply). At the higher voltage, additional 47K 2-watt resistors should be connected in series with the intensity controls. The voltage divider R_1 through R_4 must be modified for the higher dissipation.

Fig. 10-25—Madulatian manitar with hausing and case remaved. Tie strips and adequately-insulated wire are required. Cable clamps hald the wires fram the magic-eye sackets, ta avaid strain an the tubes. Transfarmers cannat be seen in this view because they are an the ather side of the assembly. Note ventilation hales at right-hand carner.

World Radio History

Suppressed-Carrier and Single-Sideband Techniques

A fully modulated a.m. signal has two-thirds of its power in the carrier and only one-third in the sidebands. The sidebands carry the intelligence to be transmitted; the carrier "goes along for the ride" and serves only to demodulate the signal at the receiver. By eliminating the carrier and transmitting only the sidebands or just one sideband, the available transmitter power is used to greater advantage. The carrier must be reinserted at the receiver, but this is no great problem, as explained later under "Receiving Suppressed-Carrier Signals."

Assuming that the same final-amplifier tube or tubes are used either for normal a.m. or for single sideband, carrier suppressed, it can be shown that the use of s.s.b. can give an effective gain of up to 9 db. over a.m. — equivalent to increasing the transmitter power 8 times. Eliminating the carrier also eliminates the heterodyne interference that so often spoils communication in congested phone bands.

DOUBLE-SIDEBAND GENERATORS

The carrier can be suppressed or nearly eliminated by an extremely sharp filter or by using a balanced modulator. The basic principle in any balanced modulator is to introduce the carrier in such a way that it does not appear in the output but so that the sidebands will. This requirement is satisfied by introducing the audio in push-pull and the r.f. drive in parallel, and connecting the output in push-pull. Balanced modulators can also be connected with the r.f. drive and audio inputs in push-pull and the output in parallel with equal effectiveness. The choice of a balanced modulator circuit is generally determined by constructional considerations and the method of modulation preferred by the builder. Vacuum-tube balanced modulators can be operated at high power levels and the double-sideband output can be used directly into the antenna. A d.s.b. signal can be copied by the same methods that are used for single-sideband signals, provided the receiver has sufficient selectivity to reject one of the sidebands.

In any balanced-modulator circuit there will be no output with no audio signal. When audio is applied, the balance is upset, and one branch will conduct more than the other. Since any modulation process is the same as "mixing" in receivers, sum and difference frequencies (sidebands) will be generated. The modulator is not balanced for the sidebands, and they will appear in the output.

In the rectifier-type balanced modulators

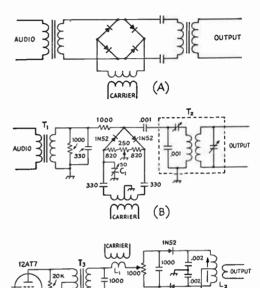


Fig. 11-1—Typical rectifier-type balanced modulators.

The circuit at A is called a "bridge" balanced modulator and has been widely used in commercial work.

(c)

The balanced modulator at B is shown with constants suitable for operation at 450 kc. It is useful for working into a crystal bandpass filter. T₁ is a transformer designed to work from the audio source into a 600-ohm load, and T₂ is an ordinary i.f. transformer with the trimmer reconnected in series with a 0.001-µf. capacitor, for impedance-matching purposes from the modulator. The capacitor C₁ is for carrier balance and may be found unnecessary in some instances—it should be tried connected on either side of the carrier input circuit and used where it is more effective. The 250-ohm potentiometer is normally all that is required for carrier balance. The carrier input should be sufficient to develop several volts across the resistor string.

The circuit at C is shown with constants suitable for operation at 3.9 Mc. T_3 is a step-down output transformer (Stancor A3250, 10,000 to 200 ohms), shunt-fed to eliminate d.c. from the windings. L_1 can be a small coupling coil wound on the "cold" end of the carrier-oscillator tank coil, with sufficient coupling to give two or three valts of r.f. across its output. L_2 is a slug-tuned coil that resonates to the carrier frequency with the effective 0.001 μ f. across it. The 1000-ohm potentio-

meter is for carrier balance.

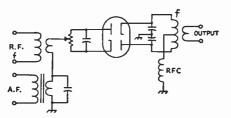


Fig. 11-2—A twin-diode balanced-modulator circuit. This is essentially the same as the circuit in Fig. 11-1C, and differs only in that a twin diode is used instead of dry rectifiers. The heater circuit for the twin diode can be connected in the usual way (one side grounded or center tap grounded).

shown in Fig. 11-1, the diode rectifiers are connected in such a manner that, if they have equal forward resistances, no r.f. can pass from the carrier source to the output circuit via either of the two possible paths. The net effect is that no r.f. energy appears in the output. When audio is applied, it unbalances the circuit by biasing the diode (or diodes) in one path, depending upon the instantaneous polarity of the audio, and hence some r.f. will appear in the output. The r.f. in the output will appear as a double-sideband suppressed-carrier signal. (For a more complete description of diode-modulator operation, see "Diode Modulators," QST, April, 1953, p. 39.)

In any diode modulator, the r.f. voltage should be at least 6 or 8 times the peak audio voltage, for minimum distortion. The usual operation involves a fraction of a volt of audio and several volts of r.f. The diodes should be matched as closely as possible — ohmmeter measurements of their forward resistances is the usual test.

(The circuit of Fig. 11-1B is described more fully in Weaver and Brown, "Crystal Lattice Filters for Transmitting and Receiving," QST, August, 1951. The circuit of Fig. 11-1C is suitable for use in a double-balanced-modulator circuit and is so described in "SSB, Jr.," General Electric Ham News, September, 1950.)

Vacuum-tube diodes can also be used in the two- and four-diode balanced-modulator circuits, and many operators consider them superior to the dry rectifier circuits. A typical balanced modulator circuit using a twin diode (6AL5, 6H6, etc.) is shown in Fig. 11-2. In phasing-type s.s.b. generators (described later) two of these modulators are required, and they are usually worked into a common output circuit. (For a description of a complete s.s.b. exciter using 6AL5 balanced modulators, see Vitale, "Cheap and Easy S.S.B.," QST, March, 1956, and May, 1958.)


Another form of balanced modulator uses the type 7360 "beam-deflection" tube, and it is capable of a high order of carrier suppression (60 db.) with good output (4 volts peak-topeak) and low distortion (45 db.). A typical application is shown in the s.s.b. generators described later in this chapter.

SINGLE-SIDEBAND GENERATORS

Two basic systems for generating s.s.b. signals are shown in Fig. 11-3. One involves the use of a bandpass filter having sufficient selectivity to pass one sideband and reject the other. Filters having such characteristics can only be constructed for relatively low frequencies, and most filters used by amateurs are designed to work somewhere around 500 kc. Good sideband filtering can be done at frequencies as high as 5 Mc. by using multiple-crystal filters. The lowfrequency oscillator output is combined with the audio output of a speech amplifier in a balanced modulator, and only the upper and lower sidebands appear in the output. One of the sidebands is passed by the filter and the other rejected, so that an s.s.b. signal is fed to the mixer. The signal is there mixed with the output of a high-frequency r.f. oscillator to produce the desired output frequency. For additional amplification a linear r.f. amplifier (Class A or Class B) must be used. When the s.s.b. signal is generated around 500 kc. it may be necessary to convert twice to reach the operating frequency, since this simplifies the problem of rejecting the "image" frequencies resulting from the heterodyne process. The problem of image frequencies in the frequency conversions of s.s.b. signals differs from the problem in receivers because the beating-oscillator frequency becomes important. Either balanced modulators or sufficient selectivity must be used to attenuate these frequencies in the output and hence minimize the possibility of unwanted radiations. (Examples of filter-type exciters can be found in QST for June, 1958, and January, 1956.)

The second system is based on the phase relationships between the carrier and sidebands in a modulated signal. As shown in the diagram, the audio signal is split into two components that are identical except for a phase difference of 90 degrees. The output of the r.f. oscillator (which may be at the operating frequency, if desired) is likewise split into two separate components having a 90-degree phase difference. One r.f. and one audio component are combined in each of two separate balanced modulators. The carrier is suppressed in the modulators, and the relative phases of the sidebands are such that one sideband is balanced out and the other is augmented in the combined output. If the output from the balanced modulators is high enough, such an s.s.b. exciter can work directly into the antenna, or the power level can be increased in a following amplifier.

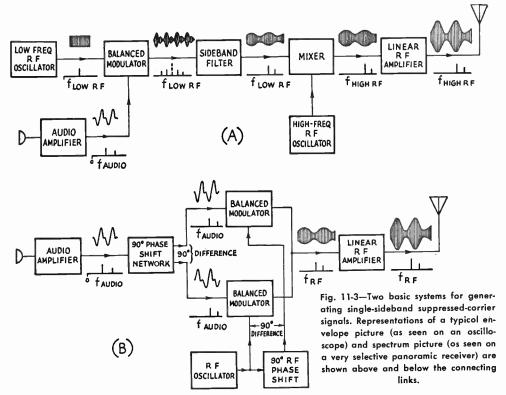Properly adjusted, either system is capable of good results. Arguments in favor of the filter system are that it is somewhat easier to adjust without an oscilloscope, since it requires only a receiver and a v.t.v.m. for alignment, and it is more likely to remain in adjustment over a long period of time. The chief argument against it,



from the amateur viewpoint, is that it requires quite a few stages and at least one frequency conversion after modulation. The phasing system requires fewer stages and can be designed to require no frequency conversion, but its alignment and adjustment are often considered to be a little "trickier" than that of the filter system. This probably stems from lack of familiarity with the system rather than any actual difficulty, and now that commercial preadjusted audio-phasing networks are available,

most of the alignment difficulty has been eliminated. In most cases the phasing system will cost less to apply to an existing transmitter.

Regardless of the method used to generate a s.s.b. signal of 5 or 10 watts, the minimum cost will be found to be higher than for an a.m. transmitter of the same low power. However, as the power level is increased, the s.s.b. transmitter becomes more economical than the a.m. rig, both initially and from an operating standpoint.

FILTER-TYPE S.S.B. EXCITERS

The basic configuration of a filter-type s.s.b. exciter was shown in Fig. 11-3. Suitable filters, sharp enough to reject the unwanted side frequencies a few hundred cycles and above from the carrier frequency, can be built in the range 20 kc. to 10 Mc. The low-frequency filters generally use iron-cored inductors, and the new toroid forms find considerable favor at frequencies up to 50 or 60 kc. These filters are of normal band-pass constant-k and m-derived configuration. In the range 450 to 500 kc., either crystal-lattice or electro-mechanical filters are used. Low-frequency filters are manufactured by Barker & Williamson and by Burnell & Co., and electro-mechanical filters are made by the Collins Radio Co. Crystal filters are available from Hermes Electronics and McCoy Electronics in the megacycles range; homemade filters generally utilize war-surplus crystals. The frequency of the filter determines how many conversions must be made before the operating frequency is reached. If the filter frequency is 30 kc. or so, it is wise to convert first to 500 or 600 kc. and then convert to the 3.9-Mc. band, to avoid the image that would almost surely result if the conversion from 30 to 3900 kc. were made without the intermediate step. When a filter at 500 kc. is used, only one conversion is necessary to operate in the 3.9-Mc. band, but 14-Mc. and higher-frequency operation would require at least two conversions to hold down the images (and local-oscillator signals if balanced mixers aren't used) and make them easy to eliminate.

The choice of converter circuit depends largely on the frequencies involved and the im-

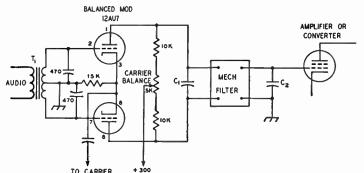


Fig. 11-4—One type of balanced-modulator circuit that can be used with a mechanical filter (Collins F455-31 or F500-31 series) in the i.f. range. The filters are furnished in various types of mountings, and the values of C₁ and C₂ will depend upon the type of filter selected.

T₁-Plate-to-push-pull grids audio transformer.

pedance level. At low frequencies (up to 500 kc.) and low impedances, rectifier-type balanced modulators are often used for mixers, because the balanced modulator does not show the local-oscillator frequency in its output and one source of spurious signal is minimized. At high impedance levels, and at the higher frequencies, vacuum tubes are generally used, in straight converter or balanced-modulator circuits, depending upon the need for minimizing the local-oscillator frequency in the output.

Sideband filters in the 30- to 50-kc. range are usually low-impedance devices, and rectifier-type balanced modulators are common practice. Sideband filters in the i.f. range are higher-impedance circuits and vacuum-tube balanced modulators are the rule in this case. An example of one that can be used with the high-impedance (15,000 ohms) mechanical filter is shown in Fig. 11-4. The filter can be followed by a converter or amplifier tube, depending upon the signal level. Some models of the mechanical filters have a 23-db. insertion loss, while others have only 10.

Crystal-lattice filters are also used to reject the unwanted sideband. These filters can be made from crystals in the i.f. range — many of these are still available from stores selling military surplus. A popular configuration is the "cascaded half lattice" shown in Fig. 11-5. The crystals used in this filter can be obtained at frequencies in the i.f. range, and ones that are within the ranges of the modified i.f. transformers will be satisfactory. Two 100-µµf. capacitors are connected across the secondary winding of two of the transformers to give push-pull output. The crystals should be obtained in pairs 1.8 kc. apart. The i.f. trans-

formers can be either capacitor-tuned as shown, or they can be slug-tuned.

A variable-frequency signal generator of some kind is required for alignment of the filter, but this can be nothing more elaborate than a shielded b.f.o. unit. The signal should be introduced at the balanced modulator, and an output indicator connected to the plate circuit of the vacuum tube following the filter. With the crystals out of the circuit, the transformers can be brought close to frequency by plugging in small capacitors (2 to 5 $\mu\mu$ f.) in one crystal socket in each stage and then tuning the transformers for peak output at one of the two crystal frequencies. The small capacitors can then be removed and the crystals replaced in their sockets.

Tuning the signal source slowly across the pass band of the filter and watching the output indicator will show the selectivity characteristic of the filter. The objective is a fairly flat response for about two kc. and a rapid drop-off outside this range. It will be found that small changes in the tuning of the transformers will change the shape of the selectivity characteristic, so it is wise to make a small adjustment of one trimmer, swing the frequency across the band, and observe the characteristic. After a little experimenting it will be found which way the trimmers must be moved to compensate for the peaks that will rise when the filter is out of adjustment.

The (suppressed) carrier frequency must be adjusted so that it falls properly on the slope of the filter characteristic. If it is too close to the filter mid-frequency the sideband rejection will be poor; if it is too far away there will be a lack of "lows" in the signal.

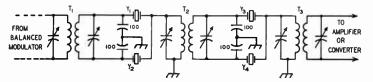


Fig. 11-5—A cascaded half-lattice crystal filter that can be used for sideband selection. The crystals are surplus type of FT-243A holders. Y₁ and Y₃ should be the same frequency and Y₂ and Y₄ should be 1.8 kc. higher. T₁, T₂, T₃—450-kc. i.f.

A HIGH-FREQUENCY CRYSTAL-FILTER SIDEBAND EXCITER

When a sideband signal is generated at 500 kc. or below, several frequency conversions are usually required to move the signal to the 14-Mc. band without danger of "image" signals. By generating the sideband signal at a high frequency, only one frequency conversion is required. The sideband transmitter shown in Figs. 11-6 through 11-9 is built around a commercial 9-Mc. crystal filter and, with a 6DQ5 in the output stage, it will deliver 50 watts p.e.p. on 75, 40 and 20 meters. The crystal filter is furnished with two matching crystals for the oscillator, so that upper or lower sideband can be obtained by shifting the (suppressed) carrier frequency to one side or the other of the crystal-filter pass band.

To facilitate construction and adjustment, the exciter has none of the "frills" to be found in some commercial equipment, although they can of course be added by the experienced amateur. Plug-in coils and crystal control are used, although there is provision for "pulling" the crystal frequency by means of a "VXO" circuit. Voicecontrolled break-in has been omitted in the interests of simplicity (and perhaps a better type of operation), and the transmitter is turned on or off by a foot switch or key. No operating conveniences have been omitted, however, other than the ability to make sudden large frequency changes. A "Calibrate" position of the mode switch permits accurate setting of one's frequency at a level that does not block the receiver, and in the "standby" condition a bias voltage of -100 is available to be applied to any subsequent amplifier that might generate undesirable diode noise without the additional bias.


Referring to the wiring diagram in Fig. 11-7, the two triode sections of a 6CG7 are used in cascade for the speech amplifier, to bring the voice signal up to the desired level of about 1 volt. This is used to modulate the beam of the 7360 balanced-modulator stage. The 7360 is also used as the (suppressed) carrier oscillator, by raising its cathode above r.f. ground and connecting the carrier-frequency crystal between control grid and ground. Two crystals are furnished with the crystal filter; in this case they have nominal frequencies of 8.998500 and 9.001500 Mc. The 12-µµf. adjustable ceramic capacitors (Centralab 827-B) in shunt with the crystals are used to pull the frequencies into correct relationship to the filter pass band. Since the good linearity of the 7360 is destroyed if the grid is driven positive, a 1N34A diode is used to provide bias in addition to that produced by the cathode resistor. Carrier balance is obtained through adjustment of the relative positive biases (about +20 volts) on the deflection plates, and also through the capacitive balance made possible by the range of C_1 . Upsetting the balance by changing the bias on one deflection plate provides a "calibration" signal or, by changing the unbalance still more by closing S2, sufficient carrier for c.w. operation.

The 9-Mc. crystal filter, FL_1 , is a low-impedance device (560 ohms), and the double-sideband signal appearing in L_1 is coupled to FL_1 through a low-impedance winding. A suitable termination for the filter is obtained by the properly-transformed self impedance of the circuit made up of L_2 and the 47- $\mu\mu$ f. capacitor; since the correct


Fig. 11-6—This single-sideband exciter unit uses a 9-Mc. crystal filter and a choice of oscillator frequencies to obtain the upper or lower sideband. The output tube (right) is a 6DQ5. For simplicity, plug-in coils are used, and two of them are shielded by grocery-store products painted gray (center).

One side has been removed for the photograph; the top plate is "plug on" at the four corners through jacks mounted on the four corners of the top plate.

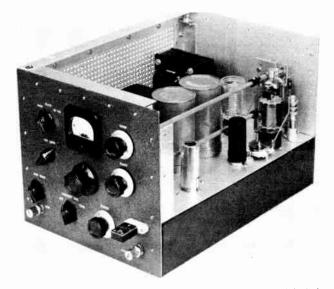The frequency control for the unit is a "VXO," a crystal-controlled oscillator that can be pulled several kc. by a panel control (large knob under meter). The crystal in use is plugged in at the lower right, just



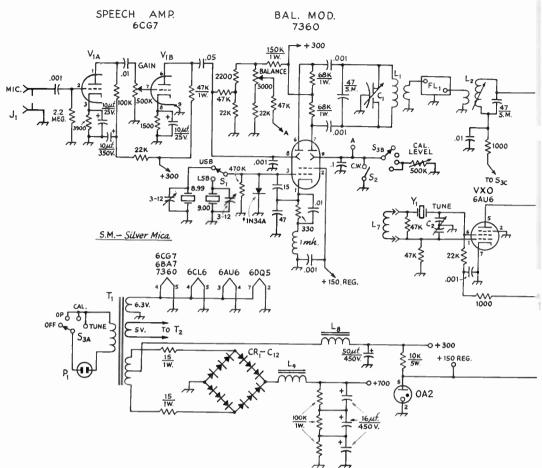above a small CAL control knob that sets the signal level into the receiver when the function switch (left, below VXO control) is on "Calibrate." Small knob at lower left is sideband-selector switch. Switch to left of meter switches meter to grid or cathode of output tube or to r.f. voltmeter on output line; knob just below adjusts sensitivity of r.f. voltmeter.



determination of the coupling is a job for an impedance bridge, it is suggested that the builder use the coil specified for L_2 unless he has facilities for designing his own.

The single-sideband signal from the filter is heterodyned to the operating frequency in a 6BA7 mixer stage operating in the normal maner. The local oscillator (heterodyning) signal is obtained from the 6AU6 VXO* stage in which a variable capacitor is used to pull the crystal frequency lower with an increase in capacitance. Since the value of inductance has some effect on the degree of effectiveness of the pulling, L_7 is made plug-in and is changed with (wide) changes in crystal frequencies. If v.f.o. operation is desired, the circuit can be modified to accept a v.f.o. signal by eliminating C_2 , L_7 , Y_1 and the 47,000-ohm resistor across L₇, and moving the 0.001-µf. capacitor to Pin 6. A 100-ohm cathode resistor would be required, and the v.f.o. signal would be introduced between grid and ground.

The output from the 6BA7 mixer is coupled to the 6CL6 driver through one or two tuned cir-

*Shall, "VXO-A Variable Crystal Oscillator," QST, Jan., 1958.

cuits, depending upon the band. On 3.9 and 7.2 Mc. only one tuned circuit is necessary, and a jumper in the plug-in coil form connects the plate lead of L_3 to the pin connected to the 0.001- μ f. coupling capacitor. On 14 Mc., where the 3rd harmonic from the VXO is fairly close in frequency to the desired signal frequency, two tuned circuits are used, connected as shown in Fig. 11-7. The plate circuit of the 6CL6 driver stage is tuned by C_4 , which is ganged to C_3 to facilitate adjustment and to reduce clutter on the front panel.

The output stage is a 6DQ5 operated in Class AB₁. The stage is neutralized to obtain good stability with high gain, and a pi circuit is used to couple to any low-impedance load. Since the loading capacitor, C_8 , does not have sufficient capacitance for correct loading on some bands, the additional capacitance is mounted in the L_8 plug-in form. As a measure of the output, an r.f. voltmeter is connected across the output, deriving its signal from the 10-10- $\mu\mu$ f. capacitance divider.

Metering is provided for in the output stage grid and cathode, and the r.f. voltmeter just mentioned.

In the power supply, an 800-v. c.t. transformer

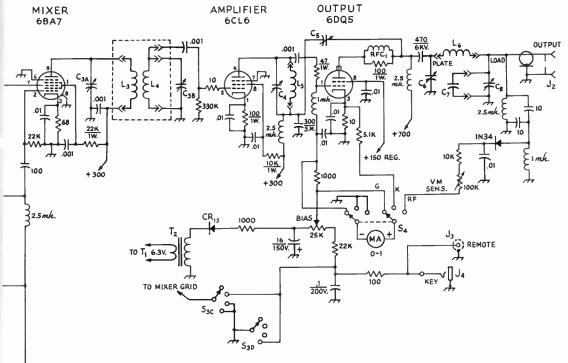


Fig. 11-7—Circuit diagram of the crystal-filter sideband generator. Unless specified otherwise, capacitances are in μμf., decimal capacitances are in μf., resistors are ½ watt, resistances are in ohms. Capacitors marked with polarity are electrolytic.

 C_1 —15- $\mu\mu$ f. differential capacitor (Johnson 160-308).

 C_2 —Dual 50- $\mu\mu$ f. variable (Johnson 167-52).

C₃—Dual 50- $\mu\mu$ f. variable (Hammarlund HFD-50). Each section has 30- $\mu\mu$ f. mica campression trimmer in parallel.

 C_4 —50- $\mu\mu$ f. miniature variable (Hammarlund APC-50B).

 $C_5-11-\mu\mu f$. variable (Johnson 167-1).

C₆-100-μμf. variable (Hammarlund HFA-100A).

C₇—Mounted in L6 form. See coil table.

 C_8 —365- $\mu\mu$ f. midget variable (Allied Radio 61 H 009 or Lafayette Radio MS-261).

CR₁-CR₁₈—400 p.i.v. 500-ma. silicon (Lafayette Radio SP-196).

FL₁—9.0-Mc. crystal filter (McCoy Electronics 32 B1). J₁—Microphane jack (Amphenol 75 PC-1M).

J₂—Caaxial receptacle (SO-239).

J₈—Phona jack.

J₄—Open-circuit phane jack.

provides 700 volts for the output stage, 300 volts for the low-level stages, and regulated 150 volts for the oscillators. Inexpensive silicon rectifiers are used in a combination circuit that provides a basic 700 and 300 volts under load. A small filament transformer, T_a , is connected to the (otherwise) unused 5-volt winding of the power transformer, and the resulting 90 volts at the secondary is rectified to furnish the bias voltage for the output stage.

The mode switch, S_3 , turns on the power supply, and places the transmitter in readiness to be controlled at J_4 . In its third position, S_3 unbal-

L₁, L₂—3.1-6.8-μh. variable inductor (Miller M-4405). Coupling coil is 4 t. No. 22 enam. closewound over "cold" end.

L₃-L₇—See cail table, next page.

L_s-5-henry 100-ma. choke (Stancor C-2305).

L₉-2-henry 200-ma. choke (Stancor C-2325).

P₁—Line plug, preferably fused, 1½ amp.

RFC₁—5 t. No. 22 spacewound on 100-ohm 1-watt resistor.

S₁—2-pale 6-position (2 used) rotary switch (Centralab PA-2003).

S2-S.p.s.t. toggle.

S₃—4-pale 5-position (4 used) 2-section ratary switch (Centralab PA-1013).

T₁—800 v.c.t. 200-ma. power transformer with 6.3- and 5-v. filament windings (Knight 61 G 414).

 T_2 —6.3-v.0.6-amp. fil. transformer (Knight 61 G 416). Y_3 —See coil table, next page.

ances the balanced modulator but keeps the output stage biased off, for calibration purposes, and in the fourth position it unbalances the modulator and turns on the final, for tune-up purposes.

Construction

The transmitter is built on a $10 \times 14 \times 3$ -inch aluminum chassis, with front and rear panels made of sturdy sheet aluminum 9 inches high. The cane-metal sides are bolted to aluminum angle stock that is bolted to the panels; this can be seen in Figs. 11-6 and 11-8. A lip bent inward

310 SIDEBAND

on the bottom of each side plate of cane metal rests on the chassis; see Fig. 11-8. The top plate of cane metal has a banana jack set in each corner, which engages a corresponding banana plug mounted on the angle stock (see Fig. 11-6).

The placement of most of the major components can be seen in the several photographs. The 7360 beam-deflection modulator tube should be mounted well away from transformers or chokes that might be surrounded by an a.c. field, because the tube is sensitive to these a.c. fields and lowfrequency sidebands can be generated by these stray fields. Aluminum brackets made of scrap sheet material will be required to mount Co and C_8 , C_3 and C_4 , and the tie-point strips supporting CR1 through CR12. The bracket supporting C3 has two National TPB feedthrough bushings mounted on the side to shorten the leads between stators and related tube sockets. The neutralizing capacitor, C_5 , must be insulated from the chassis, and another National TPB feedthrough is used from the rotor terminal to the underside of the chassis.

The coil shield cans are made from bakingpowder (Calumet) cans emptied and sprayed on the outside with grey lacquer. A hole is cut in

the cover and the cover is held to the chassis by the same screws that secure the socket. The two black tube shields visible in one of the pictures are ordinary tube shields sprayed with flat black.

Alignment

During the first stages of testing the transmitter, it is suggested that the 10- and 5100-ohm resistors be disconnected from Pin 3 of the 6DO5 socket. This will open the cathode circuit for d.c. and the tube will be inactive in the socket. At the same time, open the lead from L_0 to the rectifiers.

With the tubes in place, and coils and crystals for a band plugged in, the unit should first be tuned as a c.w. transmitter. First checks for output and resonance can be made with S3 in the "calibrate" position, using the 500,000-ohm Calibrate Level control as an excitation control. A useful tool at this point is a pick-up loop and a shielded lead to a receiver (see Fig. 11-14). Checking at L₅ should show r.f. of the desired frequency that is controllable in amplitude by the setting of the Calibrate Level control. With an insulated screwdriver on the padder across C_{3A} , adjust the ganged shafts of C3 and C4 and the screwdriver on the padder for maximum output

			•
Band (Mc.)	3.8-4.0	7.2-7.3	14.2-14.35
Crystal Y1	5.2-5.0	16.2-16.3	5.2-5.35
L_3	46 t.*	22 t.**	10 t.**
Shunt	10,000 ohms	10,000 ohms	None
L_4	None	None	10 t.** ½ inch from L ₃
$L_{\mathfrak{b}}$	46 t.*	22 t.**	10 t.**
Shunt	4700 ohms	4700 ohms	47,000 ohms
L_6	46 t.**	24 t.**	12 t.***
L_7	72 t.*	20 t.**	Same as 3.8 Mc.
C ₇ (μμf.)	1000	330	Availe .

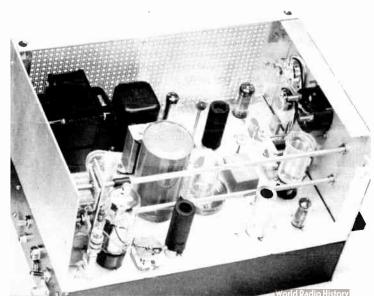


Fig. 11-8-Another view of the top of the filter sideband exciter. The variable capacitor in the VXO circuit is under the meter; the small box to the right of this capacitor is the crystal filter, and the two matched oscillator crystals supplied with the filter are near the panel. The 7360 beam deflection modulator is in the black tube shield near the filter; a grommet on the shaft (next to the 7360) of the balance potentiometer serves as a knob.

Tubes in the foreground, from left to right, are 6AU6 VXO, 6BA7 mixer, 6CL6 (black shield) amplifier and 6DQ5 output stage. The long extension shafts behind the tubes control plate tuning and output loading capacitors.

^{*}No. 24, 32 t.p.i., 1-inch diam. (B&W 3016).

**No. 20, 16 t.p.i., 1-inch diam. (B&W 3015).

***No. 18, 8 t.p.i., 1-inch diam. (B&W 3014).

Coils are mounted in 1½-inch od. polystyrene plug-in coil forms (Allied Radio 24-4P and 24-5P). Shunt resistors are ½-watt except 4700 ohms, which are 1-watt.

A Filter Sideband Exciter

as indicated by the receiver. The object is to set the padder so that its capacitance is equal to the circuit capacitance across L_b , thus enabling the circuits to track. If this alignment is done on 20 meters (preferable), the padder across C_{BB} will also have to be adjusted at the same time.

If S_4 is set to the position for measuring the r.f. output, resonating the output circuit may show a slight amount of r.f. even though the cathode circuit is open. If r.f. is indicated, the stage can be roughly neutralized by setting C_5 for minimum output under these conditions. The receiver, connected at J_2 or coupled to L_6 , is a much more sensitive neutralization indicator, however.

Switching now to "operate", it should be found that there is a setting of the 5000-ohm "balance" control that gives very low output. Test this first with C_1 set at equal capacitances; after finding the minimum setting for the potentiometer try adjusting the capacitor. If the wiring is reasonably symmetrical, it may be found that C_1 has little effect, but this is nothing to worry about. If the tone of the (apparently) suppressed carrier suddenly changes as the potentiometer reaches the null point, it indicates the presence of 60-or 120-cycle residual sidebands, stemming from a.c. at the deflection plates or a magnetic field around the tube.

If the two crystals in the 7360 balanced modulator had exactly the same activity, it might be possible to set their frequencies by adjusting the trimmers across the crystals until, in the testing in the "calibrate" setting of S_3 , exactly the same output was obtained for either setting of S_1 . Since this equal-output condition is not necessarily the case, it becomes necessary to adjust the two trimmers, until, judging by ear, the sideband signal sounds the same for either setting of S_1 (and proper tuning of the receiver). A more sophisticated and accurate approach is to borrow an audio oscillator (if one is lacking) and measure the relative outputs at various audio frequencies for the two settings of S_1 . The output should start to fall off fast below about 400 cycles and above about 3000; the exact figures will be determined by the filter characteristics and by personal preferences of the operator.

When an acceptable sideband signal can be obtained, the transmitter can be turned off long enough to reconnect L₀ and also the resistors in the 6DQ5 cathode circuit. Before turning on the power, a dummy load should be connected at J₂


Fig. 11-9—Underneath the chassis of the sideband exciter. The twelve silicon rectifiers of the power supply are hung between tie points mounted on an aluminum bracket (upper right). The ganged capacitors, C_3 , C_4 that tune the excitation stages are mounted on an aluminum bracket (lower left center); the shaft of C_4 is insulated to keep it above ground potential.

Controls and outlets along the back panel (top) are, left to right: S_2 , output jack, microphone jack, key jack, bias control, remote jack J_3 , and the a.c. line con-

and the 25,000-ohm bias control should be set to give maximum bias (arm closest to capacitor side). Set S_4 to read cathode current (full scale is 200 ma.) and turn on the transmitter. With a key plugged in at I_4 , close the key and turn the bias potentiometer arm until a cathode current of about 30 ma. (reading of 0.15) is obtained. Swinging C_0 around should give no change in cathode current; if the cathode current suddenly kicks up it means the stage is not completely neutralized and needs touching up.

Switching to the "tune" position and using the "calibrate level" control for an excitation control, it should be possible to drive the 6DQ5 into grid current on any of the three bands. With the excitation backed off just below the point of grid current, the output stage should be loaded to draw about 120 ma. cathode current. Switching to "operate" and speaking into the microphone, the gain should be set to where voice peaks kick the cathode current to peaks of 50 ma. (0.25) or so. A much finer adjustment of loading conditions and a better control of speech level before distortion can be obtained by using an oscilloscope to observe the effects of tuning, loading and level.

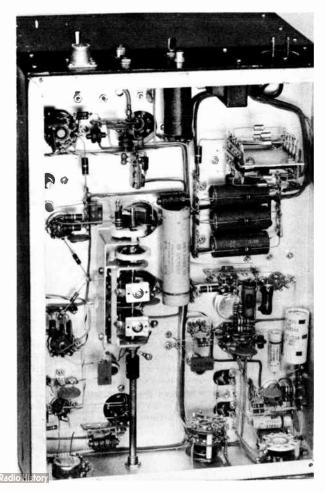No values are given for 10- and 15-meter operation because full output cannot be obtained on these bands without an additional stage of amplification.



312 SIDEBAND

A PHASED SINGLE-SIDEBAND EXCITER

The sideband generator shown in Figs. 11-10 and 11-11 uses the phasing principle outlined earlier (Fig. 11-3B) to produce an upper or lower single-sideband signal. It will also generate a double-sideband signal, with or without carrier. The generator features the new beam-deflection 7360 tube in the balanced modulator portion of the circuit, and it is complete (with power supply) except for the frequency-controlling source. A watt or two of r.f. from a v.f.o. or crystal-controlled oscillator is sufficient for the unit.

Referring to the circuit diagram in Fig. 11-12, a 12AT7 twin triode serves as the speech amplifier. An audio phase-shift network (Barker & Williamson Model 350 2Q4) plugs in the octal socket J2. This preadjusted network has the property of delivering two audio signals differing in phase by 90 degrees ± 1.5 degrees over the range 300 to 3000 cycles. The audio network is protected against low- and high-frequency components outside this range by the couplingcapacitance values and the low-pass filter $C_1C_2L_1L_2$. The two audio signals from the network are equalized by the PHASE control and amplified by V_{2A} and V_{2B} and applied to the deflection plates of the 7360 balanced modulators. The r.f. introduced at J_4 is split and shifted +

and — 45 degrees in the r.f. phase-shift network to give a net difference of 90 degrees.

The output of the balanced modulators is amplified by a Class-A 6CL6, which has sufficient output to drive two or three 6146s in Class AB₁. The tube complement and power supply shown in the circuit diagram are such that the 6Cl.6 can be overdriven on 75, 40 and 20 meters (but Class-A operation demands that the tube never be driven into grid current). On 15 and 10 meters this reserve gain is lacking, and consequently inductor and phase-shift values for these bands are not given.

For ease of adjustment the grid, screen and plate currents of the 6CL6 can be measured, by proper settings of S_4 . Further, the input and output r.f. voltages can be metered, for convenience in setting the excitation and the output tuning.

To simplify the construction and adjustment, plug-in coils and r.f. phase-shift networks are used (Fig. 11-13). The r.f. network is made up of 100-ohm resistors and suitable capacitors (100-ohms reactance at the operating frequency); once adjusted it will hold sufficiently over an amateur band.

The mode switch, S₁, shifts from one sideband output to another by shifting the deflection

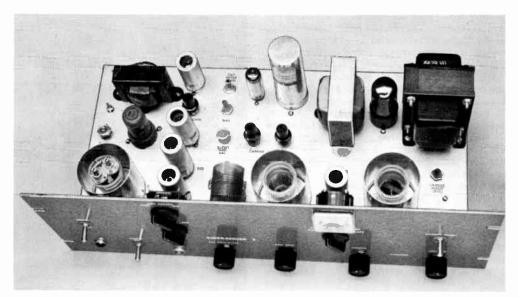


Fig. 11-10—This phosing-type single (ond double) sidebond generator features the 7360 beam-deflection tube in the balanced-modulator section. The 6CL6 output amplifier (behind meter) delivers sufficient output to drive one or more 6146 amplifier tubes in Class AB₁. Plug-in coils are used to simplify construction.

The r.f. phose-shift network (coil form at extreme left, with two capocitor shafts visible) is plug-in for each band. The oudio phase-shift network (B & W Type 2Q4 No. 350) is housed in the tube envelope in front of the audio transformer at rear left. The unshielded tube at reor center is a voltage-regulator tube; two black knobs in front of the VR tube are on the carrier bolonce controls.

Toggle switches on the panel, left to right, are transmit-receive, power and spotting (carrier insert). Iwo knobs at left, obove the microphone jack, turn the mode (lower) and the tune-operate switches. Knob under the meter is on the 5-position meter switch.

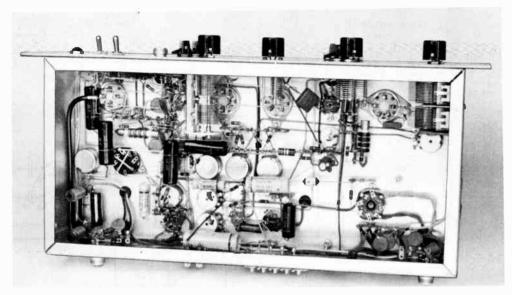


Fig. 11-11—View underneath the chassis of the sideband generator. Tuning capacitors are mounted close under the sockets for the associated plug-in coils. At rear of the chassis (bottom in this view), two terminals are used for bias measurement, and the 4-terminal barrier strip is for making connection to remote control and v.f.o. on-off circuits. Two inductors, part of the low-pass audio filter that protects the audio phase-shift network, are mounted near the r.f. input jack (lower left).

plate to which the audio is applied in one of the balanced modulators. A third position of the switch disables one of the balanced modulators, resulting in double-sideband output from the generator. A spotting switch, S_2 , is used to momentarily unbalance a balanced modulator and allow r.f. to feed through in an amount sufficient to be heard in the receiver. The amount of unbalance is determined by the setting of the SPOT LEVEL resistor. A second circuit of S_2 is available to turn on the external oscillator at the same time. The TUNE-OPERATE switch, S_3 , is used to ground the 6CL6 screen during tune-up procedures.

The power supply includes a bias supply for the 6CL6 amplifier stage. When switch S_6 is closed, normal operating bias is applied to the 6CL6, but when it is opened the bias will rise to the power-supply level and reduce the 6CL6 plate current to zero. This is useful if the 6CL6 generates "diode noise" on standby that is audible in the receiver. REMOTE connections allow the same bias to be applied to a following amplifier during standby, or they can be used to open and close the circuit normally controlled by S_6 .

Construction

The physical arrangement of the major components is shown in Figs. 11-10 and 11-11. The generator is built on an $8 \times 17 \times 3$ -inch aluminum chassis, with a 7-inch high relay rack panel held to it by the components along the bottom front. Millen 80008 2½-inch diameter aluminum shields are used at the sockets for L_4 , L_5 and the r.f. phase-shift network. A minor departure

from convention is the location of the AUDIO GAIN control on the chassis instead of the front panel, but the control is used so seldom that the location is justified.

No special considerations are required in wiring the audio section other than the usual precautions against hum pickup. Before installing L_1 and L_2 they should be set to their correct value of 25 mh. An impedance bridge or Q meter can be used for the purpose, if available. If not, they can be set with an audio oscillator and v.t.v.m. (or oscilloscope). Connect an inductor in parallel with one of the 0.1-\mu f. capacitors, and connect the combination to the audio oscillator output through a high resistance (100K or so). Connect the v.t.v.m. (or 'scope) across the parallel tuned circuit, and adjust the inductor for maximum voltage across the combination when the audio oscillator is set at 3200 cycles. Repeat for the other inductor and capacitor, and do not change the slug settings again. The filter will have a cut-off frequency of 3200 cycles.

R.f. wiring should be made short and direct wherever possible. Input and output are run to jacks J_3 and J_4 in RG-58/U coaxial cable. Try to maintain symmetry of leads in the balanced-modulator portion of the circuit.

Coil and r.f. phase-shift network dimensions are given in the coil table. L_3 is a manufactured product used as is; L_4 and L_5 are made from coil stock and mounted inside the polystyrene plug-in coil forms. The L_5 form also carries padding capacitors for C_7 (these aren't shown in Fig. 11-12). A $39-\mu\mu$ padder for C_6 , used only on 75 meters, can be connected to a spare

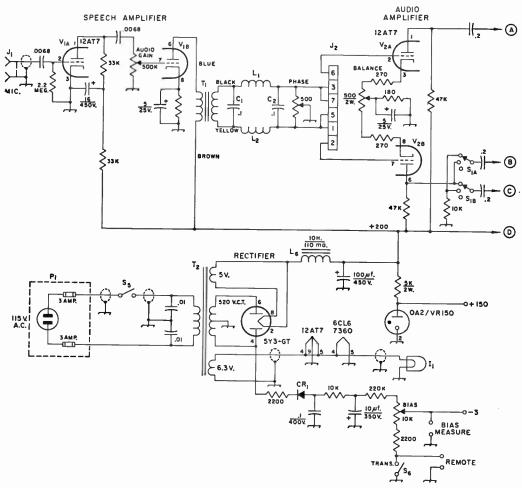


Fig. 11-12—Schematic diagram of the sideband generator. Unless specified otherwise, resistors are ½-watt, .01and .002-µf. capacitors are disk ceramic, 600 volts; .1- and .2-µf. capacitors are tubular paper, 400 volts; capacitors marked with polarities are electrolytic.

C₁, C₂-0.1- μ f. 200-v. paper \pm 10 per cent (Sprague 2TM-P1).

C₃—Dual 100- $\mu\mu$ f. variable (Hammarlund HFD-100).

C₄-15-μμf. variable (Hammarlund MAPC-15).

 C_5 —100- $\mu\mu$ f. variable (Hammarlund APC-100B).

C₀-100-μμf. variable (Hammarlund HFA-100A).

C₇—Dual 365-μμf. variable, stators in parallel (broadcast replacement type).

C₈, C₁₀—See coil table.

 C_0 , C_{11} —32- $\mu\mu$ f. variable (Johnson 30M8 160-130).

CR₁—360 p.i.v. 200-ma. silicon (Sarkes-Tarzian K-200).

l₁-6.3-v. panel light.

J1-Microphone connector (Amphenol 75-PC1M).

J2-Octal tube socket, for phase-shift network.

pin on the socket for L_{δ_1} with the other capacitor terminal connected to the chassis. A jumper in the 75-meter L_{δ} will then connect the padder across C_{δ} .

By cutting a small notch in each side of the coil form, the two trimmer capacitors C_0 and C_{11} can be mounted side by side in the coil form.

J₃, J₄—Coaxial-plug receptacle (SO-239).

L₁, L₂—4–30 mh. slug-tuned coil (Miller 6315) adjusted to 25 mh. See text.

L₃, L₄, L₅—See coil table.

L₀-10-henry 110-ma. filter choke (Knight 62G139).

P₁—Fuse plug.

S₁—3-pole 3-position rotary switch.

S2-D.p.d.t. toggle.

S3-Single-pole 2-position non-shorting rotary switch.

S₄—Two-pole 5-position rotary switch, non-shorting.

S₅, S₆-S.p.s.t. toggle.


T₁—20,000-to-600 ohms tube-to-line transformer (Thordarson 22S91).

T₂—520 v.c.t. at 90 ma., 5 v., 6.3 v. (Knight 61G412).

Since the rotor terminals of C_0 and C_{11} would normally touch each other when the two capacitors are in place, each terminal must be snipped off close to the ceramic. A piece of tinned wire is then soldered to the remaining portion of the terminal and led across the ceramic and up through the hole that will be farther from the

IN 52

OUTPUT

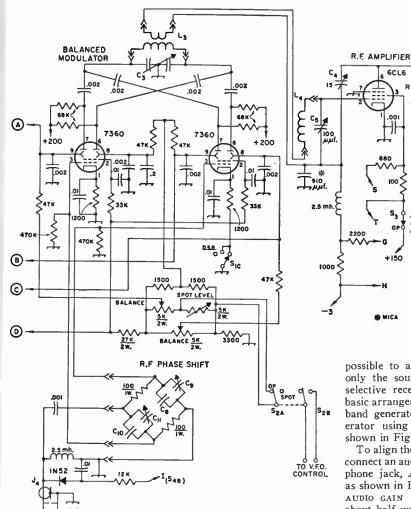

other trimmer capacitor when the two are in place. The connections to C₈, C₁₀ and the two 100-ohm 1-watt (composition, not wirewound) resistors must be made before the wires are snaked through the coil-form pins and soldered. Before soldering to the coil-form pins, the lengths of leads to the stators of C_9 and C_{11} can be measured and soldered. The leads to the rotors from the coil-form pins are long leads that are led up from the pins through the holes in the ceramic end supports. When these long leads have been soldered to the leads from the rotors they will serve to hold C_9 and C_{11} in place. Any surplus length should be snipped off. See Fig. 11-13. When soldering to the pins of the polystyrene coil forms, hold the pin in pliers or a vise, to prevent heat from reaching the polystyrene.

Adjustment

An audio oscillator or other source of lowdistortion single-tone audio is a necessity in the preliminary adjustment of the sideband generator. An oscilloscope is also very useful, but it is

possible to adjust the generator with only the source of single-tone a.f., a selective receiver and a v.t.v.m. The basic arrangement for aligning the sideband generator, or any sideband generator using the phasing method, is shown in Fig. 11-14.

學 .002

6CL6

To align the generator just described, connect an audio oscillator to the microphone jack, J_1 , through an attenuator as shown in Fig. 11-14. Open the 500K AUDIO GAIN control in the generator about half way and apply a 1000-cycle audio tone. Adjust the input level for

approximately 1 volt a.c. at the plates of V_{2A} and V_{2B} , with the 500-ohm balance control set at half resistance. It will be found that the PHASE control will be offset under these conditions; this is perfectly natural since the attenuations through the two channels of the audio phase-shift network are not equal. If a good oscilloscope is available (identical phase shifts through vertical and horizontal amplifiers), the outputs from V_{2A} and V_{2B} should give a circle on the scope face when the vertical and horizontal gains are equalized.

Apply r.f. from the v.f.o. or crystal-controlled oscillator at J_4 , and increase its amplitude until the meter shows full scale with S4 turned full clockwise. A full-scale reading will be close to 10 volts r.m.s. at the No. 3 pins of the 7360 balanced-modulator tubes. With So in the Tune position, and S4 switched to read the grid current of the 6CL6, it should be possible to tune C_3 and C_5 and get an indication of grid current. Turn off the generator by pulling the line plug and temporarily open one side of the 10-ohm



Fig. 11-13—Plug-in coils and r.f. phase-shift networks for the sideband generator. Output tank coils (right) include additional padding capacitor for C₇, as given in the coil table. Polystyrene coil forms are 4-pin (Allied Radio 24-4P) and 5-pin (Allied Radio 24-4P).

resistor in the plate-voltage lead to the 6CL6. The 6CL6 stage can now be neutralized, using for an indicator a receiver connected to the output jack J_a . Use a length of coaxial cable from J_a to the receiver, and install an attenuator network at the receiver antenna terminals, as shown in Fig. 11-14. Adjust the neutralizing capacitor for minimum signal at the receiver, with all circuits resonated, S_a on tune, and the signal backed off below the grid-current level.

Turn off the power, reconnect the 10-ohm resistor, and connect a dummy load to the output of the sideband generator. Couple the scope and/or receiver to the dummy load or L₅, as shown in Fig. 11-14. When connecting to an oscilloscope, a tuned circuit is required, and the r.f. voltage developed across the tuned circuit is applied directly to the vertical deflection plates. The receiver is connected by coupling loosely through a loop and length of shielded cable; when further attenuation is required it is obtained through the use of resistors at the receiver input terminals.

With the oscillator running, tune the balanced

modulator and 6CL6 circuits for maximum output — this resonates these circuits. Next adjust the 5K BALANCE potentiometers for minimum output. Then introduce a single audio tone of around 1000 cycles at the microphone terminal. Here again it may be necessary to use a resistance voltage divider to hold the signal down and prevent overload. Advance the gain control and look at or listen to the output signal from the 6CL6. It is most likely to be a heavily modulated signal. Try various settings of Co and Cu until the modulation is minimized, and experiment as well with slight touches on the BALANCE and PHASE controls. S₂ should be in the OPERATE positions during these adjustments. With the v.t.v.m. check the r.f. voltages at the No. 3 pins of the 7360s - they should be the same within a few per cent. If not, they can be brought into this condition by readjustment of C_9 and C_{11} , consistent with minimum modulation on the output signal.

The s.s.b. signal with single-tone audio input is a steady unmodulated signal. While it may not be possible to eliminate the modulation en-

Band (meters)	La	L ₄	Ls	C7 pad***	C8 C10***
75	47 t. No. 24, 32 t.p.i., 1¼ diam.; 3 turn link (B & W 80 MCL)	41 turns*	27 turns*	910 μμf.	390 μμf.
40	25 t. No. 22, 16 t.p.i., 1¼ diam.; 3 turn link (B & W 40 MCL)	20 turns*	19 turns*	470 μμf.	200 μμf.
20	13 t. No. 18, 8 t.p.i., 1¼ diam.; 2 turn link (B & W 10 MCL)	17 turns**	16 turns**	270 μμf.	91 μμf.

^{*32} t.p.i. No. 24, 1 inch diam. (B & W 3016 Miniductor).

***Silver mica, ± 5 per cent tolerance.

^{**16} t.p.i. No. 20, 34 inch diam. (B & W 3011 Miniductor).

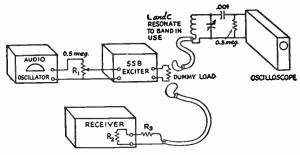


Fig. 11-14—Fundamental arrangement for using an oscilloscope and/or receiver when testing an s.s.b. exciter or transmitter. An audio oscillator is required to furnish the audio signal, and its output is best controlled by the external control R_1 . The audio volume control in the s.s.b. exciter should not be turned on too far, or it should be set at the normal position if you know that position, and all volume controlling should then be done with R_1 and the output attenuator of the audio oscillator. This will reduce the chances of overloading the audio and other amplifier stages in the exciter, a common cause of distortion.

The oscilloscope is coupled to the dummy load through a loop, length of coaxial line, and an L-C circuit tuned to the operating frequency. It is necessary to go directly to the vertical deflection plates of the oscilloscope rather than through the vertical amplifier.

The receiver is coupled to the dummy load through a loop and a length of shielded line. If too much signal is obtained this way, an attenuator, R_2R_3 , can be added to the input terminals of the receiver. Small values of R_2 and large values of R_3 give the most attenuation: in some cases R_2 might be merely a few inches of solid wire.

tirely, it will be possible to get it down to a satisfactorily low level. Conditions that will prevent this are improper r.f. phasing, lack of carrier balance (suppression), distortion in the audio signal (at the source or through overload in the speech amplifier), and lack of audio balance at the 12AT7 audio amplifier. Of these, the r.f. phasing and the audio balance are perhaps the most critical.

A final check on the signal can be made with the receiver in its most selective condition. The spectrum testing described below cannot be done with a broad receiver. Examining the spectrum near the signal, the side signals other than the main one (carrier, unwanted sidebands, and sidebands from audio harmonics) should be at least 30 db. down from the desired signal. This checking can be done with the S-meter

and the a.g.c. on—in the earlier tests the a.g.c. should be off but the r.f. gain reduced low enough to avoid receiver overload.

Examples of the proper and improper scope patterns are shown in Fig. 11-15.

The bias potentiometer for the 6CL6 amplifier should be set initially for a bias of about —3 volts, which should correspond to plate and screen currents of about 30 and 7 ma., respectively. Under maximum-signal conditions, just short of running into grid current, the plate current will kick up slightly. The best indicator of proper modulation level is the output meter.

(For an extensive treatment of the alignment of commercial phasing-type s.s.b. exciters, see Ehrlich, "How to Adjust Phasing-Type S.S.B. Exciters," QST, November, 1956.)

AMPLIFICATION OF S.S.B. SIGNALS

When an s.s.b. signal is generated at some frequency other than the operating frequency, it

is necessary to change frequency by heterodyne methods. These are exactly the same as those

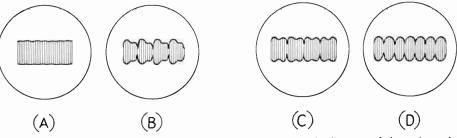


Fig. 11-15—Sketches of the oscilloscope face showing different conditions of adjustment of the exciter unit. (A) shows the substantially clean carrier obtained when all adjustments are at optimum and a sine-wave signal is fed to the audio input. (B) shows improper r.f. phase and unbalance between the outputs of the two balanced modulators. (C) shows improper r.f. phasing but outputs of the two balanced modulators equal. (D) shows proper r.f. phasing but unbalance between outputs of two balanced modulators.

used in receivers, and any of the normal mixer or converter circuits can be used. One exception to this is the case where the heterodyning oscillator frequency is close to the desired output frequency. In this case, a balanced mixer should be used, to eliminate the heterodyning oscillator frequency in the output.

To increase the power level of an s.s.b. signal, a linear amplifier must be used. A linear amplifier is one that operates with low distortion, and the low distortion is obtained by the proper choice of tube and operating conditions. Physically there is little or no difference between a linear amplifier and any other type of r.f. amplifier stage. The circuit diagram of a tetrode r.f. amplifier is shown in Fig. 11-16; it is no different basically than the similar ones in Chapter Six. The practical differences can be found in the supply voltages for the tube and their special requirements. The proper voltages for a number of suitable tubes can be found in Table 11-I; filament-type tubes will require the addition of the filament bypass capacitors C_9 and C_{10} and the completion of the filament circuit by grounding the filament-transformer center tap. The grid bias, E_1 , is furnished through an r.f. choke, although a resistor can be used if the tube is operated in Class AB₁ (no grid current). The screen voltage, E_2 , must be supplied from a "stiff" source (little or no voltage change with current change) which eliminates the use of a dropping resistor from the plate supply unless a voltage-regulator tube is used to stabilize the screen voltage.

Any r.f. amplifier circuit can be adapted to linear operation through the proper choice of operating conditions. For example, the circuit in Fig. 11-16 can be modified by the use of difby the use of another neutralizing scheme, and the resultant amplifier will still be linear if the proper operating conditions are observed. A triode or pentode amplifier circuit will differ in

Fig. 11-16—Circuit diagram of a tetrode linear amplifier using link-coupled input tuning and pi network output coupling. The grid, screen and plate voltages (E_1 E_2 and E_3) are given in Table 11-1 for a number of tubes. Although the circuit is shown for an indirectly-heated cathode tube, the only change required when a filament type tube is used is the addition of the filament bypass capacitors C_0 and

 $$C_{10}$.$ Minimum voltage ratings for the capacitors are given in terms of the power supply voltages.

C₁—Grid tuning capacitor, 3E₁.

C₂—Neutralizing capacitor, 2E₃.

C₃—Grid-circuit bypass capacitor, part of neutralizing circuit, 3E₁.

C4-Plate tuning capacitor, 1.5E3.

C₈—Output loading capacitor. 0.015 spacing for kilowatt peak.

C₆—Plate coupling capacitor, 2E₈.

C7-Screen bypass capacitor, 2E2.

detail; typical circuits can be found in Chapter Six.


The simplest form of linear amplifier is the Class A amplifier, which is used almost without exception throughout receivers and low-level speech equipment. (See Chapter Three for an explanation of the classes of amplifier operation.) While its linearity can be made relatively good, it is inefficient. The theoretical limit of efficiency is 50 per cent, and most practical amplifiers run 25–35 per cent efficient at full output.

At low levels this is not worth worrying about, but when the 2- to 10-watt level is exceeded something else must be done to improve this efficiency and reduce tube, power-supply and operating costs.

Class AB₁ amplifiers make excellent linear amplifiers if suitable tubes are selected. Primary advantages of Class AB₁ amplifiers are that they give much greater output than straight Class A amplifiers using the same tubes, and they do not require any grid driving power (no grid current drawn at any time).

Although triodes can be used for Class AB₁ operation, tetrodes or pentodes are usually to be preferred, since Class AB₁ operation requires high peak plate current without grid current, and this is easier to obtain in tetrodes and pentodes than in most triodes.

To obtain maximum output from tetrodes, pentodes and most triodes, it is necessary to operate them in Class AB_2 . Although this produces maximum peak output, it increases the driving-power requirements and, what is more important, requires that the **driver regulation** (ability to maintain wave form under varying load) be good or excellent. The usual method to improve the driver regulation is to connect a fixed resistor, R_1 , across the grid circuit of the driven stage, to offer a load to the driver that is modified only slightly by the additional load of the tube when

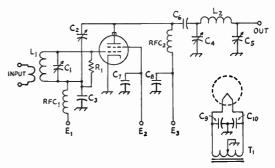

C₈—H.v. bypass capacitor, 2E₈.

C₉, C₁₀—Filament bypass capacitor.

L1-Grid inductor.

L2-Plate inductor.

 R_1 —Grid circuit swamping resistor, required for AB₂. See text.

RFC1-Grid-circuit r.f. choke.

RFC2-Plate r.f. choke.

T₁—Filament transformer.

TABLE 11-I-LINEAR-AMPLIFIER TUBE-OPERATION DATA FOR SINGLE SIDEBAND-GROUNDED-CATHODE CIRCUIT

Unless otherwise noted, rotings are manufacturers' for audio operation. Values given are for one tube. Driving powers represent tube losses only—circuit losses will increase the figures.

Tube	Class	Plate Voltage	Screen Voltage	D.C. Grid Voltage ¹	Zero-Sig, D.C. Plate Current	MaxSig. D.C. Plate Current	Zera-Sig. D.C. Screen Current	MaxSig. D.C. Screen Current	Peak R.F. Grid Voltage	MaxSig. D.C. Grid Current	MaxSig. Driving Power	MaxRated Screen Dissipation	Max,-Rated Grid Dissipation	Avg. Plate Dissipation	MaxSig. Useful Pawer Output
2E26	AB ₁	500	200	- 25	9	45		10	25	0	0	2.5			15
6146 6BB3	AB ₁	600 750	200 195	- 50 - 50	14 12	115 110	.5 .5	14 13	50 50	0	0	3 3	_ =	25 25	47 60
807 1625	AB ₁	600 750	300 300	- 34 - 35	1B 15	70 70	.3 .3	B B	34 35	=	0	3.5 3.5	=	25 30	28 36
811-A	В	1000 1250 1500	Ξ	0 0 4,5	22 27 16	175 175 157	=		93 88 85	13	3.8 3.0 2.2		=	65 65 65	124 155 170
4-65A²	ABı	1500 2000 2500 3000	500 500 400 400	- 90 -105 - 85 - 90	30 20 15 15	83 75 66 60		5 3 3 3	70 80 77 77		=	10 10 10 10	=		60 85 100 120
PL-177A2	AB ₁	1 500 2000	600 600	-110 -115	30 25	175 175	0	B 7	108 112	0	0	10 10	_ =	110 125	140 210
7094	AB ₁	2000	400	_ 50	30	200		35	44	0	42	20			250
	AB ₁	2500	7505	95	25	145		27	90	0	0			I	245
813	AB ₂	2250 2500	750 ⁵ 750 ⁵	- 90 - 95	23 18	158 180	.8 .6	29 28	115 11B		.1	22 22		100 125	258 325
	AB ₁	2000 2500 3000	615 555 510	- 105 100 95	40 35 30	135 (100)4 120 (85)4 105 (75)4	=	14 (4.0) ⁴ 10 (3.0) ⁴ 6.0 (1.5) ⁴	105 100 95	0 0 0	0 0 0	20 20 20	=	=	150 180 200
4-125A	AB ₂	1500 2000 2500	350 350 350	- 41 - 45 - 43	44 36 47	200 150 130	0	17 3 3	141 105 89	9 7 6	1.25 .7 .5	20 20 20	5 5 5	125 125 122	175 175 200
7034/ 4X150A	ABı	1000 1500 1800	300 300 300	- 50 - 50 - 50	50 50 50	225 225 225	0 0	11 11 11	50 50 50	0	0	12 12 12	=	=	115 200 250
	AB ₁	2500 3000 3500 4000	600 600 555 510	-115 -110 -105 -100	65 55 45 40	230 (170) ⁴ 210 (150) ⁴ 185 (130) ⁴ 165 (115) ⁴	=	15 (3.5) ⁴ 12 (2.5) ⁴ 9.5 (2.0) ⁴ 7.5 (1.5) ⁴	115 110 105 100	0 0 0	0 0 0	35 35 35 35	=	=	335 400 425 450
4-250A	AB ₃	1500 2000 2500 3000	300 300 300 300	- 48 - 48 - 51 - 53	50 60 60 63	243 255 250 237	0 0 0	17 13 12 17	96 99 100 99	11 12 11 10	1,1 1,2 1,1 1	35 35 35 35 35	10 10 10 10	150 185 205 190	214 325 420 520
30 4 TL	AB ₁	1500 2000 2500 3000	=	118 170 230 290	135 100 80 65	286 273 242 222	=		118 170 230 290	0000	0 0 0	=	=	=	128 245 305 365
PL-175A3	AB ₁	2500 3000 3500	750 750 750	-143 -150 -160	100 80 75	350 350 350	1 1	35 29 24	143 150 160	0 0 0	0 0 0	25 25 25		265 305 345	570 680 790
PL-172	AB ₁	2000 2500 3000	500 ⁶ 500 ⁶ 500 ⁶	-110 -110 -115	200 220 220	800 800 780	9 9 9	48 43 41	110 110 110	0 0	0 0 0	35 35 35	=		1020 1280 1540
4CX1000A	AB ₁	2000 3000	325 325	- 60 - 60	250 250	1000 900	-2 -2	35 35	60 60	=	0	12 12	0		1020 1680

¹Approximate; adjust to give stated zero-signal plate current, ²Single-sideband suppressed-carrier ratings, voice signal,

360 Mc.
 4Values in parentheses are with two-tone test signal.

⁸0 v. suppressor grid ⁶+75 v. suppressor grid. 320 SIDEBAND

	TABLE 11-II-CLA	I-CLASS-B LINEAR	AMPLIFIER TUBE	OPERATION DATA	OR SINGLE SIDEB	ISS-B LINEAR-AMPLIFIER TUBE OPERATION DATA FOR SINGLE SIDEBAND—GROUNDED-GRID CIRCUIT	RID CIRCUIT	
Tube	Plate Voltoge	D.C. Grid Voltage	Zero-Sig. D.C. Plate Current	MaxSig. D.C. Plate Current	Peak R.F. Grid Voltage	MaxSig. D.C. Grid Current	MaxSig. Driving Power	MaxSig. Useful Power Output
4-125A ¹	2000 2500 3000	000	10 15 20	105 (30) ² 110 (30) ² 115 (30) ²	[]]	555	91 91 91	145 190 240
4-400A1	2000 2500 3000	000	70 80 90	265 (55) ³ 270 (55) ³ 280 (55) ³	F F F	0001	38 39 40	325 435 555
3-400Z	2000 2500 3000	000	62 73 100	400 (265) ³ 400 (274) ³ 333	111	148 (87) ³ 142 (82) ³ 120	32	4454 5605 655
PL-6569	2500 3500 4000	- 60 ⁶ - 90 ⁶ - 10.5 ⁶	30 24	300 270 250	180 220 205	80 68 42	70 ⁷ 75 ⁷ 60 ⁷	550 760 800
PL-6580	2500 3500 4000	- 50 - 85 - 100	60 4 4 5 5 0 4	350 300 300	195 210 230	95 65 65	757 687 727	610 765 910
3-1000Z	3000	00	162 240	800 (550)³ 670	11	254 (147) ⁸ 300	65	10504
¹ Grid and screen connected together. ² Screen current.	nected together.	[§] Two-tone signal. ⁴ Minimum distorti	*Two-tone signal. Minimum distortion products.	8 & A	Vinimum distortion prod pproximate, adjust to cludes bias loss, grid d	Minimum distortion products at 1 k.w. p.e.p. input. Approximate; adjust to give stated zero-signal plate current Includes bias loss, grid dissipation, and feed-through power.	ite current. Ih power.	

it is driven into the grid-current region. This increases the driver's output-power requirements. Further, it is desirable to make the grid circuit of the Class AB₂ stage a high-C circuit, to improve regulation and simplify coupling to the driver. A "stiff" bias source is also required, since it is important that the bias remain constant, whether or not grid current is drawn.

Class B amplifiers are theoretically capable of 78.5 per cent efficiency at full output, and practical amplifiers run at 60-70 per cent efficiency at full output. Triodes normally designed for Class B audio work can be used in r.f. linear amplifiers and will operate at the same power rating and efficiency provided, of course, that the tube is capable of operation at the radio frequency. The operating conditions for r.f. are substantially the same as for audio work — the only difference is that the input and output transformers are replaced by suitable r.f. tank circuits. Further, in r.f. circuits it is readily possible to operate only one tube if only half the power is wanted - pushpull is not a necessity in Class B r.f. work. However, the r.f. harmonics may be higher in the case of the single-ended amplifier, and this should be taken into consideration if TVI is a problem.

For proper operation of Class AB2 and B amplifiers, and to reduce harmonics and facilitate coupling, the input and output circuits should not have a low C-to-L ratio. A good guide to the proper size of tuning capacitor will be found in Chapter Six; use the voltage-to-current ratio existing under p.e.p. conditions. When zero-bias tubes are used, it may not be necessary to add much "swamping" resistance across the grid circuit, because the grids of the tubes load the circuit at all times. However, in AB2 operation, the swamping resistor should be such that it dissipates from five to ten times the power required by the grids of the tubes, insuring an almost constant load on the driver stage and good regulation of the r.f. grid voltage. In turn this means that at least five to ten times more driving power will be required than is indicated in Table 11-I. Where an excess of driving power is available, it is generally better to increase the loading (decrease the resistance of the swamping resistor) to the point where the maximum available driver power is utilized on peaks.

Before going into detail on the adjustment and loading of the linear amplifier, a few general considerations should be kept in mind. If proper operation is expected, it is essential that the amplifier be so constructed, wired and neutralized that no trace of regeneration or parasitic instability remains. Needless to say, this also applies to the stages ahead of it.

The bias supply to the Class AB₂ or B linear amplifier should be quite stiff, such as batteries or some form of voltage regulator. If nonlinearity is noticed when testing the unit, the bias supply may be checked by means of a large electrolytic capacitor. Simply shunt the supply with $100 \ \mu f$, or so of capacity and see if the linearity improves. If so, rebuild the bias supply for better regula-

Amplification of S.S.B. Signals

tion. Do not rely alone on using a large capacitor.

Where tetrodes or pentodes are used, the screen supply should have good regulation and its voltage should remain constant under the varying current demands. If the maximum screen current does not exceed 30 or 35 ma., a string of VR tubes in series can be used to regulate the screen voltage. If the current demand is higher, it may be necessary to use an electronically regulated power supply or a heavily bled power supply with a current capacity of several times the current demand of the screen circuit.

Where VR tubes are used to regulate the screen supply, they should be selected to give a regulated voltage as close as possible to the tube's rated voltage, but it does not have to be exact. Minor differences in idling plate current can be made up by readjusting the grid bias.

The plate voltage applied to the linear amplifier should be held as constant as possible under the varying current-demand conditions. This condition can be met by using low-resistance transformers and inductors and by using a large value of output capacitor in the power-supply filter. An output capacitor value three or four times the minimum required for normal filtering (Chapter Seven) is reasonable. Although some slight improvement can be obtained by using still higher values of capacitance, the problem of turning on the supply without blowing fuses (on the initial surge) starts to become significant.

One should bear in mind that the same amplifier can be operated in several classes of operation by merely changing the operating conditions (bias, loading, drive, screen voltage, etc.). However, when the power sensitivity of an amplifier is increased, as by changing the operation from Class AB₂ to Class AB₁, the stability requirements for the amplifier become stringent.

From the standpoint of ease of adjustment and availability of proper operating voltages, a linear amplifier with Class AB₁ tetrodes or pentodes or one with zero-bias Class B triodes would be first choice. The Class B amplifier would require more driving power. (For examples of Class AB₁ tetrode amplifiers, see Russ, "The 'Little Firecracker' Linear Amplifier," QST, Sept., 1953; Eckhardt, "The Single Side-Saddle Linear," QST, Nov., 1953; Wolfe and Romander, "A 4X-250B Linear," QST, Nov., 1956; Muir, "Grounded-Grid Tetrode Kilowatt," QST, April, 1957; and Rinaudo, "Compact AB₁ Kilowatt," QST, Nov., 1957.)

Tables 11-I and 11-II list a few of the more

popular tubes commonly used for s.s.b. linear-amplifier operation. Except where otherwise noted, these ratings are those given by the manufacturer for audio work and as such are based on a sine-wave signal. These ratings are adequate ones for use in s.s.b. amplifier design, but they are conservative for such work and hence do not necessarily represent the maximum powers that can be obtained from the tubes in voice-signal s.s.b. service. In no case should the average plate dissipation be exceeded for any considerable length of time, but the nature of a s.s.b. signal is such that the average plate dissipation of the tube will run well below the peak plate dissipation.

Getting the most out of a linear amplifier is done by increasing the peak power without exceeding the average plate dissipation over any appreciable length of time. This can be done by raising the plate voltage or the peak current (or both), provided the tube can withstand the increase. However, the manufacturers have not released any data on such operation, and any extrapolation of the audio ratings is at the risk of the amateur. A 35- to 50-per cent increase above plate-voltage ratings should be perfectly safe in most cases. In a tetrode or pentode, the peak plate current can be boosted some by raising the screen voltage.

When running a linear amplifier at considerably higher than the audio ratings, the "two-tone test signal" (described later) should never be applied at full amplitude for more than a few seconds at any one time. The above statements about working tubes above ratings apply only when a voice signal is used — a prolonged whistle or two-tone test signal may damage the tube. (For a method of adjusting amplifiers safely at high input, see Goodman, "Linear Amplifiers and Power Ratings," QST, August, 1957.)

Linear amplifiers are rated in "p.e.p. input" or "p.e.p. output." The "p.e.p." stands for peak envelope power. P.e.p. input is not indicated by the maximum reading the plate milliammeter kicks to (see "Adjustment of Amplifiers" below); it is the input that would be indicated by the plate milliammeter and voltmeter if the amplifier were driven continuously by a single r.f. signal of the peak amplitude the amplifier can handle within its allowable distortion limits. The p.e.p. output is the r.f. output under these same conditions. As implied in the preceding paragraph, it may be impossible to measure the p.e.p. input or output directly without injuring the tube or tubes.

GROUNDED-GRID AMPLIFIERS WITH FILAMENT-TYPE TUBES

It is not necessary to use indirectly heated cathode type tubes in grounded-grid circuits, and filament-type tubes can be used just as effectively. However, it is necessary to raise the filament above r.f. ground, and one way is shown in Fig. 11-17. Here filament chokes are used between the filament transformers and the tube

socket. The inductance of the r.f. chokes does not have to be very high, and 5 to $10 \mu h$, will usually suffice from 80 meters on down. The current-carrying capacities of the r.f. chokes must be adequate for the tube or tubes in use, and if the resistance of the chokes is too high the filament voltage at the tube socket may be too low and the

322 SIDEBAND

tube life will be endangered. In such a case, a higher-voltage filament transformer can be used, with its primary voltage cut down until the voltage at the tube socket is within the proper limits.

Filament chokes can be wound on ceramic or wooden forms, using a wire size large enough to carry the filament current without undue heating. Large cylindrical ceramic antenna insulators can be used for the forms. If enameled wire is used, it should be spaced from half the diameter to the diameter of the wire; heavy string can be used for this purpose. The separate chokes indicated in Fig. 11-17 are not essential; the two windings can be wound in parallel. In this case it is not necessary to space all windings; the two parallel wires can be treated as one wire, winding them together with a single piece of string to space the turns. Enameled wire can be used because the enamel is sufficient insulation to handle the filament voltage.

When considerable power is available for driving the grounded-grid stage, the matching between driver stage and the amplifier is not too important. However, when the driving power is marginal or when the driver and amplifier are to be connected by a long length of coaxial cable, a pi network matching circuit can be used in the input of the grounded-grid amplifier. The input impedance of a grounded-grid amplifier is in the range of 100 to 400 ohms, depending upon the tube or tubes and their operating conditions.

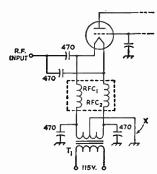


Fig. 11-17—When filament-type tubes are used in a grounded-grid circuit, it is necessary to use filament chokes to keep the filament above r.f. graund. In the portion of a typical circuit shown here, the filament chokes. RFC1 and RFC2, can be a manufactured unit (e.g., B&W FC15 and FC30) or homemade as described in the text. Total plate and grid current can be read on a milliammeter inserted at x.

When data for grounded-grid operation is available (see Table 11-II), the input impedance can be computed from

$$Z_{in} = \frac{(peak \ r.f. \ driving \ voltage)^2}{2 \times driving \ power}$$

From this and the equations for a pi network, a suitable network can be devised.

ADJUSTMENT OF AMPLIFIERS

One of the more important features of the linear amplifier is that the ordinary plate and grid meters are at best only a poor indicator of what is going on. As the meters bounce back and forth, even a person who is thoroughly familiar with this kind of amplifier would be hard put to sense whether the input power registered is attributable to (a) overdrive and underload, which yield distortion, splatter, TVI, etc., or (b) underdrive and too-heavy loading, resulting in inefficiency and loss of output.

The simplest and best way to get the whole story is to make a linearity test; that is, to send through the amplifier a signal whose amplitude varies from zero up to the peak level in a certain known manner and then observe, by means of an oscilloscope, whether this same waveform comes out of the amplifier at maximum ratings.

Test Equipment

Even the simplest type of cathode-ray oscilloscope can be used for linearity tests, so long as it has the regular internal sweep circuit. If this instrument is not already part of the regular station equipment, it might be well to purchase one of the several inexpensive kits now on the market, so that it will be on hand not only to make initial tests but also as a permanent monitor during all operation. Barring a purchase, it is recommended at least that a scope be borrowed to make the line-up checks, whereupon the regular

plate and grid meters can serve thereafter to indicate roughly changes in operating conditions.

All linearity tests require that the vertical plates of the scope be supplied with r.f. from the amplifier output. To avoid interaction within the instrument, it is usually best to connect directly to the cathode-ray tube terminals at the back of the cabinet. A pick-up device and its connections to the oscilloscope are shown in Fig. 11-14. Normally, the pick-up loop should be coupled to the dummy load, antenna tuner, or transmission line; i.e., to a point in the system beyond where any tuning adjustments are to be made.

The only other piece of test equipment will be an audio oscillator. Since only one frequency

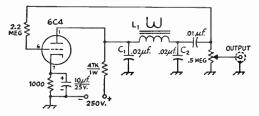


Fig. 11-18—Fixed-frequency audio oscillator having good output waveform. The frequency can be varied by changing the values of C₁ and C₂.

L₁—Small speaker output transformer, secondary not used.

Adjustment of Amplifiers

is needed, the simple circuit of Fig. 11-18 works quite well. Some equipment has a circuit similar to this one built right into the exciter audio system.

Two-Tone Test

The two-tone test involves sending through the amplifier or the system a pair of r.f. signals of equal amplitude and a thousand cycles or so apart in frequency. The combined envelope of two such signals looks like two sine waves folded on one another. If this waveform comes out of the final, well and good; if not, there is work to do.

There are two commonly used ways to generate the two-tone signal, and the choice of which to use depends on the particular type of exciter available.

Method A — for Filter or Phasing Exciters:

- 1) Turn up the carrier insertion until a carrier is obtained at about half the expected output amplitude.
- 2) Connect an audio oscillator to the microphone input and advance audio gain until (when the carrier and the one sideband are equal) the scope pattern takes on the appearance of full modulation; i.e., the cusps just meet at the center line. See Fig. 11-19, photo No. 1.
- 3) To change the drive through the system, increase or decrease the carrier and audio settings together, maintaining equality of the two signals.


Method B — for Phasing Exciters:

- 1) Disable the audio input to *one* balanced modulator, by removing a tube or by temporarily short-circuiting an audio transformer.
- 2) Connect the audio oscillator and advance audio gain to get the desired drive. Note that with one balanced modulator cut out, the resultant signal will be double-sideband with no carrier, hence two equal r.f. signals.


Double-Trapezoid Test

When Method B can be used with phasing exciters, it is possible to derive a somewhat more informative pattern by making a connection from the exciter audio system to the horizontal signal input of the oscilloscope and using this audio signal, instead of the regular internal sweep, to cause the horizontal deflection. Those who are familiar with the regular trapezoid test for a.m. transmitters will recognize this set-up as being the same, except that instead of one trapezoid, this test produces two triangles pointing toward each other.


Each individual triangle is subject to the same analysis as the regular trapezoid pattern; i.e., the sloping sides of the pattern should be straight lines for proper operation. Since it is much easier to tell whether a line is straight or not than to judge the correctness of a sine curve, the double trapezoid has the advantage of being somewhat more positive and sensitive to slight departures from linearity than is the regular two-tone pattern.

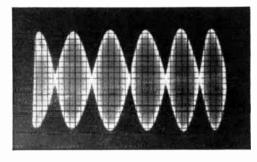

(1)

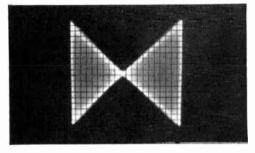

(2)

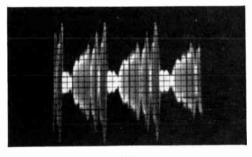

(3)

Fig. 11-19—Correct Patterns. 1—Desired two-tone test pattern. 2—Desired double-trapezoid test pattern. 3—Typical voice pattern in a correctly adjusted amplifier, scope set for 30-cycle sweep. Note that peaks are clean and sharp.

If the audio can be picked off at the plate of the audio modulator tube that is still working, the input signal need not be a pure sine wave; merely whistling or talking into the microphone should produce the appropriate pattern. If, because of the exciter layout, it is necessary to pick up the audio signal ahead of the phase-shift network, it will then be necessary to use a good sine-wave audio oscillator as before. Also, with the latter set-up, the pattern will probably have a loopy appearance at first, and phase correction will be needed to make the figure close up. This can be done either by varying the audio frequency or by putting a phaser in series with the horizontal input to the scope, as shown in Fig. 11-20.

324 SIDEBAND

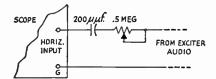


Fig. 11-20—"Phaser" circuit for the oscilloscope.

Ratings

Before proceeding with linearity tests, it is well to have in mind the current and power levels to expect. A suppressed-carrier signal is exactly like an audio signal, except for its frequency, so the audio ratings for any tube are

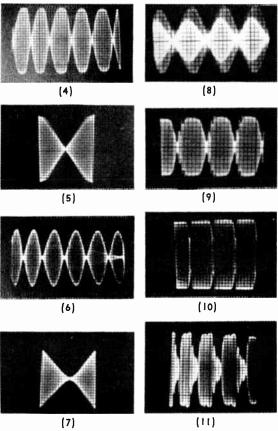


Fig. 11-22—Improper Amplifier Operation. 4—Overdrive, indicated by flattening of peaks. 5—Same as 4, double-trapezoid test. 6—Too much bias, causing crossover to become pinched together rather than cutting straight across center line. 7—Same as 6, double-trapezoid test. 8—Two-tone test with v.h.f. parasitics. Note fuzzy halo or fringe. In milder cases the fuzziness will appear just at the peaks. 9—Two-tone test with fundamental frequency parasitics, accompanied by overdrive. 10—Severe overdrive and parasitics. 11—Voice pattern showing flattening of peaks due to overdrive. When flattening is apparent on the voice pattern, the case is a severe one.

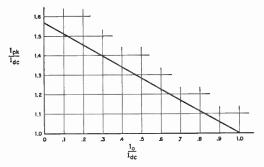


Fig. 11-21—When the two-tone test signal is used for checking the linearity of an amplifier, the peak current is higher than the current indicated by the plate meter. The ratio of these values depends upon the ratio of the idling (no-signal) current to the indicated current.

The graph shows the relationship.

Io = no-signal (idling) current,

 $I_{
m de} =$ meter reading with two-tone test signal,

 $I_{\rm pk} \equiv$ actual peak current.

perfectly applicable for linear r.f. service where no carrier is involved. On the other hand, the ratings sometimes shown for Class B r.f. telephony are *not* what is wanted, because they are for conventional a.m. transmission with carrier.

If audio ratings are not given for the desired tube type, it will be safe to assume that the maximum-signal input for Class B or AB₂ service is about 10 per cent less than the key-down Class C c.w. conditions. The input will have to be held somewhat lower in Class AB₁ operation because the average efficiency is lower and, also, the tube can draw only a limited amount of current at zero grid voltage.

The maximum-signal conditions determined from tube data correspond in s.s.b. work to the very peak of the r.f. envelope; when a two-tone test signal (or voice) is used, the plate milliammeter does not indicate the peak plate current. The relationship between peak current and indicated current is variable with voice signals, but with the two-tone test signal applied there is a definite relationship between indicated (d.c.) current and peak current. This relationship is plotted in Fig. 11-21. Knowing the ratio of the idling current to the plate current with the twotone test signal, I_o/I_{de} , one can find the factor that can be applied to give the peak current. For example, an amplifier draws 50 ma, with no signal and 250 ma. (before flattening) with the two-tone test signal. $I_o/I_{de} = 0.2$, and $I_{pk}/I_{de} =$ 1.45, from Fig. 11-21. Thus $I_{pk} = 1.45 \times 250 =$ 363 ma.

Should the resulting peak input (0.363 × plate voltage) be different than the design value for the particular amplifier tube, the drive and loading adjustments can be changed in the proper directions (always adjusting the loading so that the peaks of the envelope are on the verge of flattening) and the proper value reached.

Using the Linearity Tests

The photos (Figs. 11-19, 11-22 and 11-23) have been taken to show many of the typical patterns that may be encountered with either of the test arrangements described previously. They are classified separately as to those representing correct conditions (Fig. 11-19), faulty operation of the r.f. amplifier (Fig. 11-22), and various other patterns that look irregular but which really represent a peculiarity in the test set-up or the exciter but not in the final (Fig. 11-23).

Aside from the problem of parasitics, which may or may not be a difficult one, it should be possible without much difficulty to achieve the correct linearity pattern by taking action as indicated by the captions accompanying the photos. It can then be assumed that the amplifier is not contributing any distortion to the signal so long as the peak power level indicated by the test is not exceeded. It is entirely possible, however, that good linearity will be obtained only by holding the power down to a level considerably below what is expected, or conversely that there will be signs of excessive plate dissipation at a level that the tubes should handle quite easily. In such cases, some attention should be given to the plate loading, as discussed below.

The several patterns of Fig. 11-24 show how loading affects the output and efficiency of a linear amplifier. In the first two, loading is relatively light and limiting takes place in the final plate circuit. Reserve power is still available in the driver, evidenced by the fact that heavier loading on the final allows the peak output to increase up to the optimum level of the third pattern. With still heavier loading the output ceases to increase but in fact drops somewhat; even though the input power goes up all the time, the efficiency goes down rapidly. In the last two patterns, the driver is the limiting element in the system, and the extra powerhandling capability of the final, due to heavier loading, is wasted by inability of the driver to do it justice.

- 1) For good efficiency, the final itself must be the limiting element in the power-handling capability of the system.
- 2) If the final is not being driven to its limit, it should be loaded less heavily until such is the case.
- 3) If the power level obtained above is less than should be expected, more driving power is needed.

There are several ways to tell whether or not the final is being driven to its limit. One way is to advance the drive until peak limiting is apparent in the output, then move the oscilloscope coupling link over to the driver plate tank and see whether or not the same limiting appears there. Another way is to decrease or increase the final loading slightly and note whether the limiting output level increases or decreases correspondingly. If it does not, the final is not controlling the system. Still another but similar


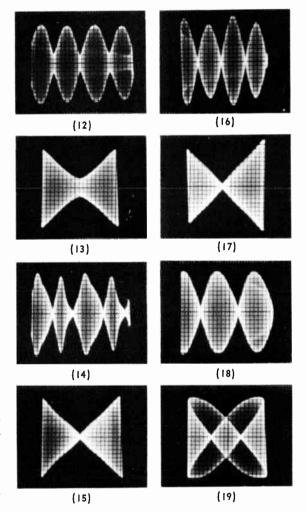


Fig. 11-23—Improper Test Setup. 12—Two r.f. signals unequal. In Method A, caused by improper settings of either carrier or audio control. Method B, either carrier leakage through disabled modulator or unequal sidebands due to selective action of some high-Q circuit off resonance, 13—Same as 12, double-trapezoid test (Method B), 14—Distorted audio, A clue to this defect is that successive waves are not identical, 15-Same distortion as 14, but switched to double trapezoid test pattern. Note that correct pattern prevails regardless of poor audio signal, 16—Carrier leakage through working modulator (Method B only). 17—Same as 16, double trapezoid. 18—(Note tilt to left.) Caused by incomplete suppression of unwanted sideband (Method A) or by r.f. leakage into horizontal circuits of scope. 19—Double trapezoid with audio phase shift in test setup.

method is to detune the final slightly while limiting is apparent, and if proper drive conditions prevail the pattern will improve when the amplifier plate is detuned.

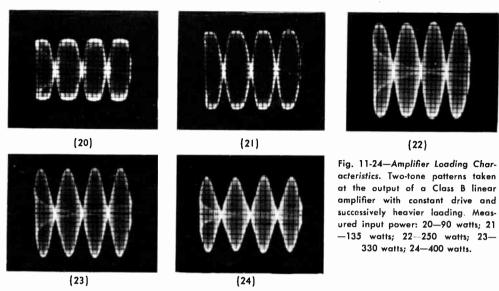The intermediate and driver stages will follow the same laws, except that what is called "load326 SIDEBAND



ing" on a final is often referred to as "impedance matching" when going between tubes. More often than not, an apparent lack of power transfer from a driver to its succeeding stage is due to a poor match. In Class AB_2 or B service, a step-down type of coupling is required between power stages, and a person accustomed to the conventional plate-to-grid coupling capacitor technique will be surprised to find how effective it is to tap the driven stage down on its tank—or otherwise to decouple the system. For example, an 807 driving a pair of 811s requires a voltage step-down of about 3 or 4 to 1 from plate to each grid.

Dummy Load

For the sake of everyone concerned, linearity tests should be kept off the air as much as possible. They make quite a racket and spurious signals are plentiful in earlier stages of misadjustment. Ordinary lamp bulbs make a fine dummy load so long as it is recognized that their impedance is not exactly the same as the antenna and that this impedance changes somewhat as the bulbs light up. These factors can be taken into account by making careful note of plate and grid currents after the transmitter has

been adjusted and is operating with a linearity test signal at maximum linear output into the lamp load. Then, having reconnected the regular antenna, the same loading conditions for the final will be reproduced by adjusting its tuning and loading until the identical combination of plate and grid currents can be obtained. This process will require only a few moments of onthe-air operation.

When the final on-the-air checks are made, it will be convenient to make a few reference marks on the oscilloscope screen to indicate the peak height of the pattern. The scope will then serve as a permanent output monitor for all operations. For best results the sweep should be set for about 30 cycles, in which case the voice patterns will stand out clearly and can easily be kept just within the reference lines. Incidentally, the pattern is really fascinating to watch.

Don't be a "meter bender." Input power isn't everything. If you have to cut your input in half to avoid overload, the fellow at the other end will hardly notice the difference in level. At the same time, your neighbors, both those on the ham band and those next door trying to watch TV, will appreciate the difference right away.

FREQUENCY CONVERSION

The preferred s.s.b. transmitter is probably one that generates the s.s.b. signal at some suitable frequency and then heterodynes the signal into the desired amateur bands, although a few designs exist that generate the s.s.b. signal at the operating frequency and consequently eliminate the need for heterodyning. When the heterodyning is done at low level (involving an s.s.b. signal of not more than a few volts), standard receiving techniques are satisfactory. Normal receiver converter tubes run at manu-

facturer's ratings leave little to be desired. When high-level heterodyning is required, as when an exciter delivering from 5 to 20 watts on a single band is available and multiband operation is desired, a high-level converter is used. Since the efficiency of a converter is only about one-fourth that of the same tube or tubes used in Class AB₂, using a converter stage as the output stage is not very economical, and the high-level converter is generally used to drive the output stage.

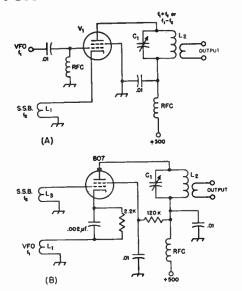


Fig. 11-25—Two examples of "high-level" mixer circuits. The circuit at A has been used with 6V6, 6L6, 6AQ5 and 6Y6 type tubes. With 300 volts on the plate the idling current is about 15 ma., kicking as high as 30 ma. with the s.s.b. signal.

The circuit in B operates with a positive screen voltage and some cathode bias, and is capable of somewhat more output than the circuit shown in A.

In either case the output circuit, C_1L_2 , is tuned to the sum or difference frequency of the oscillator and s.s.b. signal. Coupling coils L_1 and L_3 will usually be three or four turns coupled to their respective driving sources.

Reference to tube manuals will disclose no information of the operation of small transmitting tubes as mixers. However, it has been found that most of the tetrodes in the 15- to 35-watt plate-dissipation class make acceptable mixers, and tubes like the 6V6, 6L6, 807 and 6146 have been used successfully. The usual procedure is to feed one of the signals (oscillator or s.s.b.) to the control grid and the other to the cathode or screen grid. Typical circuits are shown in Fig. 11-25.

(Suggestions for converting to and operating in the 50- and 144-Mc. bands can be found in Tilton, "Single-Sideband Ideas for the V.H.F. Man," QST, May, 1957.)

VOICE-CONTROLLED BREAK-IN

Although it is possible for two s.s.b. stations operating on widely different frequencies to work "duplex" if the carrier suppression is great enough (inadequate carrier suppression would be a violation of the FCC rules), most s.s.b. operators prefer to use voice-controlled break-in and operate on the same frequency. This overcomes any possibility of violating the FCC rules and permits "round table" operation.

Many various systems of voice-controlled break-in are in use, but they are all basically the same. Some of the audio from the speech ampli-

fier is amplified and rectified, and the resultant d.c. signal is used to key an oscillator and one or more stages in the s.s.b. transmitter and "blank" the receiver at the time that the transmitter is on. Thus the transmitter is on at any and all times that the operator is speaking but is off during the intervals between sentences. The voice-control circuit must have a small amount of "hold" built into it, so that it will hold in between words, but it should be made to turn on rapidly at the slightest voice signal coming through the speech amplifier. Both tube and relay keyers have been used with good success. Some voice-control systems require the use of headphones by the operator, but a loudspeaker can be used with the proper circuit. (See Nowak, "Voice-Controlled Break-In . . . and a Loudspeaker," QST, May, 1951, and Hunter, "Simplified Voice Control with a Loudspeaker, *QST*, October, 1953.)

If an antenna relay is used to switch the antenna from the receiver to the transmitter and back again, it is often possible to operate the output linear amplifier stage with some idling current and experience no difficulty with the "diode noise" generated by the amplifier plate current. However, when the receiver, transmitter and antenna are always connected together, as when an electronic transmit-receive switch is used (see Chapter Eight), weak signals will not be heard through the diode noise of the transmitter. To overcome this difficulty, the idling current of the amplifier must be reduced to zero during listening periods. This can be accomplished through the use of the circuit in Fig. 11-26. Here K_1 is a relay controlled by

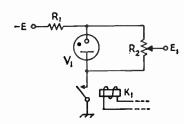


Fig. 11-26—Bias-switching circuit for use with a Class

AB₁ linear amplifier and an electronic t.r. switch.

R₁—4700 ohms, 1 watt.

R₂—100,000 ohms, 2 watts.

K₁—VOX relay or relay controlled by VOX circuit.

V₁—0A2 or 0B2, depending upon amplifier requirements.

the voice-controlled break-in circuit. When the relay is closed, the operating bias E_1 for the linear amplifier is determined by the setting of the arm on R_2 . When the relay is open, the grid bias jumps to the value E, which should be high enough to cut off the amplifier stage. The voltage regulator tube should be one with a nominal voltage drop in excess of the normal bias for the amplifier tube, and the negative supply voltage E should be at least 25 per cent higher than the

328 SIDEBAND

ignition potential of the VR tube. The circuit in Fig. 11-26 is applicable to Class AB₁ amplifiers;

it cannot be used when grid current is drawn during operation.

RECEIVING SUPPRESSED-CARRIER SIGNALS

The reception of suppressed-carrier signals requires that the carrier be accurately reinserted at the receiver. In addition, the reception of a double-sideband suppressed-carrier signal requires that one sideband be filtered off in the receiver before demodulation or that a special type of converter be used. Because little or no carrier is transmitted, the usual a.v.c. in the receiver has nothing that indicates the average signal level, and this fact requires either manual variation of the r.f. gain control or the use of a special a.v.c. system. (As, for example, Luick, "Improved A.V.C. for Sideband and C.W.," QST, October, 1957.)

A suppressed-carrier signal can be identified by the absence of a strong carrier and by the severe variation of the S meter at a syllabic rate. When such a signal is encountered, it should first be peaked with the main tuning dial. (This centers the signal in the i.f. pass band.) After this operation, do not touch the main tuning dial. Then set the r.f. gain control at a very low level and switch off the a.v.c. Increase the audio volume control to maximum, and bring up the r.f. gain control until the signal can be heard weakly. Switch on the beat oscillator, and carefully adjust the frequency of the beat oscillator until proper speech is heard. If there is a slight amount of carrier present, it is only necessary to zero-beat the beat oscillator with this weak carrier. It will be noticed that with incorrect tuning of an s.s.b. signal, the speech will sound high- or low-pitched or even inverted (very garbled), but no trouble will be had in getting the correct setting once a little experience has been obtained. The use of minimum r.f. gain and maximum audio gain will insure that no distortion (overload) occurs in the receiver. It may require a readjustment of your tuning habits to tune the receiver slowly enough during the first few trials.

Once the proper setting of the b.f.o. has been established by the procedure above, all further tuning should be done with the main tuning control. However, it is not unlikely that s.s.b. stations will be encountered that are transmitting the other sideband, and to receive them will require shifting the b.f.o. setting to the other side of the receiver i.f. passband. The initial tuning procedure is exactly the same as outlined above, except that you will end up with a considerably different b.f.o. setting. The two b.f.o. settings should be noted for further reference, and all tuning of s.s.b. signals can then be done

with the main tuning dial. With experience, it becomes a simple matter to determine which way to tune to make the signal sound lower- or higher-pitched if the receiver (or transmitter) drifts off.

When a double sideband suppressed-carrier signal is received, sufficient selectivity will be required in the receiver to eliminate one sideband and convert the signal into a single-sideband signal before detection, where it can be received by the method outlined above. Receiver bandwidths of 3 kc. or less will be required for this purpose, or the use of a "Signal Slicer," a selectivity device that uses the phasing principle. (See GE Ham News, Vol. 6, No. 4, July, 1951.)

Newcomers to single sideband often wonder if there is any device that can be added to a receiver that will make the tuning of sideband signals less critical. At the present time there is no device that will "lock in" automatically. However, if the receiver is lacking in selectivity, an apparent improvement can be obtained by using an adapter that adds selectivity to the receiving system. No improvement in ease of tuning will be noticed on good sideband signals (good suppression of unwanted sideband), but fair or mediocre signals will be easier to tune. The reason is that the adapter makes a better sideband signal out of the incoming signal by removing the vestiges of the unwanted sideband, and a good sideband signal will tune easier than a fair one. The sideband adapters also usually have detectors designed for best detection of sideband signals, a point that was overlooked in some of the older receivers. Good detectors for sideband signals include diodes with sufficient b.f.o. injection (5 to 10 times peak signal) and "product detectors" (see Chapter Five). Either detector is capable of low distortion output if the input is held down.

WHICH SIDEBAND

To identify which sideband the other station is using, remember this simple rule: If tuning the receiver to a *lower* frequency makes the voice sound *lower*-pitched, he is on *lower* sideband.

With any receiver having sufficient selectivity to give a stronger signal on one side than on the other of zero beat, this rule will aid in properly setting the b.f.o.: A selective receiver can be set up for lower-sideband reception by setting the b.f.o. so that there is little or no signal on the low-frequency side of zero beat when tuning through a steady carrier or c.w. signal.

Specialized Communication Systems

FREQUENCY AND PHASE MODULATION

It is possible to convey intelligence by modulating any property of a carrier, including its frequency and phase. When the frequency of the carrier is varied in accordance with the variations in a modulating signal, the result is frequency modulation (f.m.). Similarly, varying the phase of the carrier current is called phase modulation (p.m.).

Frequency and phase modulation are not independent, since the frequency cannot be varied without also varying the phase, and vice versa. The difference is largely a matter of definition.

The effectiveness of f.m. and p.m. for communication purposes depends almost entirely on the receiving methods. If the receiver will respond to frequency and phase changes but is insensitive to amplitude changes, it will discriminate against most forms of noise, particularly impulse noise such as is set up by ignition systems and other sparking devices. Special methods of detection are required to accomplish this result.

Modulation methods for f.m. and p.m. are simple and require practically no audio power. There is also the advantage that, since there is no amplitude variation in the signal, interference to broadcast reception resulting from rectification of the transmitted signal in the audio circuits of the BC receiver is substantially eliminated. These two points represent the principal

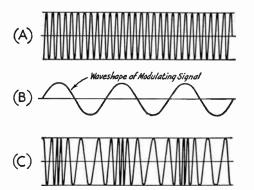


Fig. 12-1—Graphical representation of frequency modulation. In the unmodulated carrier at A, each r.f. cycle occupies the same amount of time. When the modulating signal, B, is applied, the radio frequency is increased and decreased according to the amplitude and polarity of the modulating signal.

reasons for the use of f.m. and p.m. in amateur work.

Frequency Modulation

Fig. 12-1 is a representation of frequency modulation. When a modulating signal is applied, the carrier frequency is increased during one half-cycle of the modulating signal and decreased during the half-cycle of opposite polarity. This is indicated in the drawing by the fact that the r.f. cycles occupy less time (higher frequency) when the modulating signal is positive, and more time (lower frequency) when the modulating signal is negative. The change in the carrier frequency (frequency deviation) is proportional to the instantaneous amplitude of the modulating signal, so the deviation is small when the instantaneous amplitude of the modulating signal is small, and is greatest when the modulating signal reaches its peak, either positive or negative.

As shown by the drawing, the amplitude of the signal does not change during modulation.

Phase Modulation

If the phase of the current in a circuit is changed there is an instantaneous frequency change during the time that the phase is being shifted. The amount of frequency change, or deviation, depends on how rapidly the phase shift is accomplished. It is also dependent upon the total amount of the phase shift. In a properly operating p.m. system the amount of phase shift is proportional to the instantaneous amplitude of the modulating signal. The rapidity of the phase shift is directly proportional to the frequency of the modulating signal. Consequently, the frequency deviation in p.m. is proportional to both the amplitude and frequency of the modulating signal. The latter represents the outstanding difference between f.m. and p.m., since in f.m. the frequency deviation is proportional only to the amplitude of the modulating signal.

Modulation Depth

Percentage of modulation in f.m. and p.m. has to be defined differently than for a.m. Practically, "100 per cent modulation" is reached when the transmitted signal occupies a channel just equal to the bandwidth for which the receiver is designed. If the frequency deviation is greater than the receiver can accept, the receiver distorts the signal, However, on another

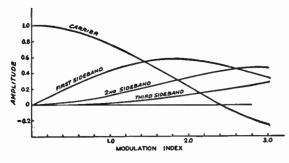


Fig. 12-2—How the amplitude of the pairs of sidebands varies with the modulation index in an f.m. or p.m. signal. If the curves were extended for greater values of modulation index it would be seen that the carrier amplitude goes through zero at several points. The same statement also applies to the sidebands.

receiver designed for a different bandwidth the same signal might be equivalent to only 25 per cent modulation.

In amateur work "narrow-band" f.m. or p.m. (frequently abbreviated n.f.m.) is defined as having the same channel width as a properly modulated a.m. signal. That is, the effective channel width does not exceed twice the highest audio frequency in the modulating signal. N.f.m. transmissions based on an upper audio limit of 3000 cycles therefore should occupy a channel not significantly wider than 6 kc.

F.M. and P.M. Sidebands

The sidebands set up by f.m. and p.m. differ from those resulting from a.m. in that they occur at integral multiples of the modulating frequency on either side of the carrier rather than, as in a.m., consisting of a single set of side frequencies for each modulating frequency. An f.m. or p.m. signal therefore inherently occupies a wider channel than a.m.

The number of "extra" sidebands that occur in f.m. and p.m. depends on the relationship between the modulating frequency and the frequency deviation. The ratio between the frequency deviation, in cycles per second, and the modulating frequency, also in cycles per second, is called the modulation index. That is.

Example: The maximum frequency deviation in an f.m. transmitter is 3000 cycles either side of the carrier frequency. The modulation index when the modulating frequency is 1000 cycles is

Modulation index
$$=\frac{3000}{1000}$$
 = 3

At the same deviation with 3000-cycle modulation the index would be 1; at 100 cycles it would be 30, and so on,

In p.m. the modulation index is constant regardless of the modulating frequency; in f.m. it varies with the modulating frequency, as shown in the above example. In an f.m. system the ratio of the maximum carrier-frequency deviation to the highest modulating frequency used is called the deviation ratio.

Fig. 12-2 shows how the amplitudes of the carrier and the various sidebands vary with the modulation index. This is for single-tone modulation; the first sideband (actually a pair, one above and one below the carrier) is displaced

from the carrier by an amount equal to the modulating frequency, the second is twice the modulating frequency away from the carrier, and so on. For example, if the modulating frequency is 2000 cycles and the carrier frequency is 29,500 kc., the first sideband pair is at 29,498 kc. and 29,502 kc., the second pair is at 29,496 kc. and 29,504 kc., the third at 29,494 kc. and 29,506 kc., etc. The amplitudes of these sidebands depend on the modulation index, not on the frequency deviation.

Note that, as shown by Fig. 12-2, the carrier strength varies with the modulation index. (In amplitude modulation the carrier strength is constant; only the sideband amplitude varies.) At a modulation index of approximately 2.4 the carrier disappears entirely. It then becomes "negative" at a higher index, meaning that its phase is reversed as compared to the phase without modulation. In f.m. and p.m. the energy that goes into the sidebands is taken from the carrier, the total power remaining the same regardless of the modulation index.

Frequency Multiplication

Since there is no change in amplitude with modulation, an f.m. or p.m. signal can be amplified without distortion by an ordinary Class C amplifier. The modulation can take place in a very low-level stage and the signal can then be amplified by either frequency multipliers or straight amplifiers.

If the modulated signal is passed through one or more frequency multipliers, the modulation index is multiplied by the same factor that the carrier frequency is multiplied. For example, if modulation is applied on 3.5 Mc. and the final output is on 28 Mc. the total frequency multiplication is 8 times, so if the frequency deviation is 500 cycles at 3.5 Mc. it will be 4000 cycles at 28 Mc. Frequency multiplication offers a means for obtaining practically any desired amount of frequency deviation, whether or not the modulator itself is capable of giving that much deviation without distortion.

Narrow-Band F.M. and P.M.

"Narrow-band" f.m. or p.m., the only type that is authorized by FCC for use on the lower frequencies where the phone bands are crowded, is defined as f.m. or p.m. that does not occupy a wider channel than an a.m. signal having the same audio modulating frequencies.

If the modulation index (with single-tone modulation) does not exceed 0.6 or 0.7, the most important extra sideband, the second, will be at least 20 db. below the unmodulated carrier level, and this should represent an effective channel width about equivalent to that of an a.m. signal. In the case of speech, a somewhat higher modulation index can be used. This is because the energy distribution in a complex wave is such that the modulation index for any one frequency component is reduced, as compared to the index with a sine wave having the same peak amplitude as the voice wave.

The chief advantage of narrow-band f.m. or p.m. for frequencies below 30 Mc. is that it eliminates or reduces certain types of interference to broadcast reception. Also, the modulating equipment is relatively simple and inexpensive. However, assuming the same unmodulated carrier power in all cases, narrow-band f.m. or p.m. is not as effective as a.m. with the methods of reception used by most amateurs. As shown by Fig. 12-2, at an index of 0.6 the amplitude of the first sideband is about 25 per cent of the unmodulated-carrier amplitude; this compares with a sideband amplitude of 50 per cent in the case of a 100 per cent modulated a.m. transmitter. When copied on an a.m. receiver, a narrow-band f.m. or p.m. transmitter is about equivalent to a 100 per cent modulated a.m. transmitter operating at one-fourth the carrier power. On a suitable (f.m.) receiver, f.m. is as good or better than a.m., watt for watt.

Comparison of F.M. and P.M.

Frequency modulation cannot be applied to an amplifier stage, but phase modulation can; p.m. is therefore readily adaptable to transmitters employing oscillators of high stability such as the crystal-controlled type. The amount of phase shift that can be obtained with good

linearity is such that the maximum practicable modulation index is about 0.5. Because the phase shift is proportional to the modulating frequency, this index can be used only at the highest frequency present in the modulating signal, assuming that all frequencies will at one time or another have equal amplitudes. Taking 3000 cycles as a suitable upper limit for voice work, and setting the modulation index at 0.5 for 3000 cycles, the frequency response of the speechamplifier system above 3000 cycles must be sharply attenuated, to prevent sideband splatter. Also, if the "tinny" quality of p.m. as received on an f.m. receiver is to be avoided, the p.m. must be changed to f.m., in which the modulation index decreases in inverse proportion to the modulating frequency. This requires shaping the speech-amplifier frequency-response curve in such a way that the output voltage is inversely proportional to frequency over most of the voice range. When this is done the maximum modulation index can only be used at some relatively low audio frequency, perhaps 300 to 400 cycles in voice transmission, and must decrease in proportion to the increase in frequency. The result is that the maximum linear frequency deviation is only one or two hundred cycles, when p.m. is changed to f.m. To increase the deviation for n.f.m. requires a frequency multiplication of 8 times or more.

It is relatively easy to secure a fairly large frequency deviation when a self-controlled oscillator is frequency-modulated directly. (True frequency modulation of a crystal-controlled oscillator results in only very small deviations and so requires a great deal of frequency multiplication.) The chief problem is to maintain a satisfactory degree of carrier stability, since the greater the inherent stability of the oscillator the more difficult it is to secure a wide frequency swing with linearity.

METHODS OF FREQUENCY AND PHASE MODULATION


A simple and satisfactory device for producing f.m. in the amateur transmitter is the reactance modulator. This is a vacuum tube connected to the r.f. tank circuit of an oscillator in such a way as to act as a variable inductance or capacitance.

Fig. 12-3 is a representative circuit. The control grid of the modulator tube, V_2 , is connected across the oscillator tank circuit, C_1L_1 , through resistor R_1 and blocking capacitor C_2 . C_8 represents the input capacitance of the modulator tube. The resistance of R_1 is made large compared to the reactance of C_8 , so the r.f. current through R_1C_8 will be practically in phase with the r.f. voltage appearing at the terminals of the tank circuit. However, the voltage across C_8 will lag the current by 90 degrees. The r.f. current in the plate circuit of the modulator will be in phase with the grid voltage, and consequently is 90 degrees behind the current through C_8 , or 90 degrees behind the r.f. tank

voltage. This lagging current is drawn through the oscillator tank, giving the same effect as though an inductance were connected across the tank. The frequency increases in proportion to the amplitude of the lagging plate current of the modulator. The audio voltage, introduced through a radio-frequency choke, RFC₁, varies the transconductance of the tube and thereby varies the r.f. plate current.

The modulated oscillator usually is operated on a relatively low frequency, so that a high order of carrier stability can be secured. Frequency multipliers are used to raise the frequency to the final frequency desired.

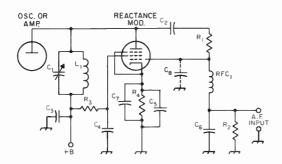A reactance modulator can be connected to a crystal oscillator as well as to the self-controlled type. However, the resulting signal is more phase-modulated than it is frequency-modulated, for the reason that the frequency deviation that can be secured by varying the tuning of a crystal oscillator is quite small.



Design Considerations

The sensitivity of the modulator (frequency change per unit change in grid voltage) depends on the transconductance of the modulator tube. It increases when R_1 is made smaller in comparison with C_8 . It also increases with an increase in L/C ratio in the oscillator tank circuit. However, for highest carrier stability it is desirable to use the largest tank capacitance that will permit the desired deviation to be secured while keeping within the limits of linear operation.

A change in any of the voltages on the modulator tube will cause a change in r.f. plate current, and consequently a frequency change. Therefore it is advisable to use a regulated power supply for both modulator and oscillator. At the low voltage used (250 volts or less) the required stabilization can be secured by means of gaseous regulator tubes.

Speech Amplification

The speech amplifier preceding the modulator follows ordinary design, except that no power is taken from it and the a.f. voltage required by the modulator grid usually is small — not more than 10 or 15 volts, even with large modulator tubes. Because of these modest requirements, only a few speech stages are needed; a two-stage amplifier consisting of a pentode followed by a triode, both resistance-coupled, will more than suffice for crystal microphones.

PHASE MODULATION

The same type of reactance-tube circuit that is used to vary the tuning of the oscillator tank in f.m. can be used to vary the tuning of an amplifier tank and thus vary the phase of the tank current for p.m. Hence the modulator circuit of Fig. 12-3 can be used for p.m. if the reactance tube works on an amplifier tank instead of directly on a self-controlled oscillator.

The phase shift that occurs when a circuit is detuned from resonance depends on the amount of detuning and the Q of the circuit. The higher

Fig. 12-3—Reactance modulator using a high-transconductance pentode (6BA6, 6CL6, etc.).

C₁-R.f. tank capacitance (see text).

C₂, C₈-0.001-µf. mica.

C4, C5, C6-0.0047-µf. mica.

C₇—10-μf. electrolytic.

C₈—Tube input capacitance.

R₁-47,000 ohms.

R₂-0.47 megohm,

R₃—Screen dropping resistor; to give proper screen voltage on modulator tube.

R4—Cathode bias resistor; Class-A operation.

L₁—R.f. tank inductance.

RFC1-2.5-mh. r.f. choke.

the Q, the smaller the amount of detuning needed to secure a given number of degrees of phase shift. If the Q is at least 10, the relationship between phase shift and detuning (in kilocycles either side of the resonant frequency) will be substantially linear over a phase-shift range of about 25 degrees. From the standpoint of modulator sensitivity, the Q of the tuned circuit on which the modulator operates should be as high as possible. On the other hand, the effective Q of the circuit will not be very high if the amplifier is delivering power to a load since the load resistance reduces the Q. There must therefore be a compromise between modulator sensitivity and r.f. power output from the modulated amplifier. An optimum figure for Q appears to be about 20; this allows reasonable loading of the modulated amplifier and the necessary tuning variation can be secured from a reactance modulator without difficulty. It is advisable to modulate at a very low power level - preferably in a stage where receiving-type tubes are used.

Reactance modulation of an amplifier stage usually also results in simultaneous amplitude modulation because the modulated stage is detuned from resonance as the phase is shifted. This must be eliminated by feeding the modulated signal through an amplitude limiter or one or more "saturating" stages — that is, amplifiers that are operated Class C and driven hard enough so that variations in the amplitude of the grid excitation produce no appreciable variations in the final output amplitude.

For the same type of reactance modulator, the speech-amplifier gain required is the same for p.m. as for f.m. However, as pointed out earlier, the fact that the actual frequency deviation increases with the modulating audio frequency in p.m. makes it necessary to cut off the frequencies above about 3000 cycles before modulation takes place. If this is not done, unnecessary sidebands will be generated at frequencies considerably away from the carrier,

CHECKING F.M. AND P.M. TRANSMITTERS

Accurate checking of the operation of an f.m. or p.m. transmitter requires different

methods than the corresponding checks on an a.m. set. This is because the common forms of

measuring devices either indicate amplitude variations only (a d.c. milliammeter, for example), or because their indications are most easily interpreted in terms of amplitude. There is no simple measuring instrument that indicates frequency deviation directly.

However, there is one favorable feature in f.m. or p.m. checking. The modulation takes place at a very low level and the stages following the one that is modulated do not affect the linearity of modulation so long as they are properly tuned. Therefore the modulation may be checked without putting the transmitter on the air, or even on a dummy antenna. The power is simply cut off the amplifiers following the modulated stage. This not only avoids unnecessary interference to other stations during testing periods, but also keeps the signal at such a low level that it may be observed quite easily on the station receiver. A good receiver with a crystal filter is an essential part of the checking equipment of an f.m. or p.m. transmitter, particularly for narrow-band f.m. or p.m.

The quantities to be checked in an f.m. or p.m. transmitter are the linearity and frequency deviation. Because of the essential difference between f.m. and p.m. the methods of checking differ in detail.

Reactance-Tube F.M.

It is possible to calibrate a reactance modulator by applying an adjustable d.c. voltage to the modulator grid and noting the change in oscillator frequency as the voltage is varied. A suitable circuit for applying the adjustable voltage is shown in Fig. 12-4. The battery

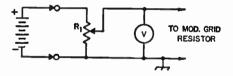


Fig. 12-4—D.c. method of checking frequency deviation of a reactance-tube-modulated ascillator. A 500- or 1000-ohm potentiometer may be used at R₁.

should have a voltage of 3 to 6 volts (two or more dry cells in series). The arrows indicate clip connections so that the battery polarity can be reversed.

The oscillator frequency deviation should be measured by using a receiver in conjunction with an accurately calibrated frequency meter, or by any means that will permit accurate measurement of frequency differences of a few hundred cycles. One simple method is to tune in the oscillator on the receiver (disconnecting the receiving antenna, if necessary, to keep the signal strength well below the overload point) and then set the receiver b.f.o. to zero beat. Then increase the d.c. voltage applied to the modulator grid from zero in steps of about ½ volt and note the beat frequency at each change. Then reverse the battery terminals and repeat. The frequency of the beat note may be

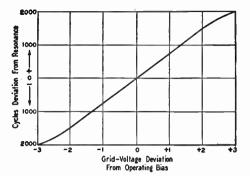


Fig. 12-5—A typical curve of frequency deviation vs. modulator grid voltage.

measured by comparison with a calibrated audio-frequency oscillator. Note that with the battery polarity positive with respect to ground the radio frequency will move in one direction when the voltage is increased, and in the other direction when the battery terminals are reversed. When several readings have been taken a curve may be plotted to demonstrate the relationship between grid voltage and frequency deviation.

A sample curve is shown in Fig. 12-5. The usable portion of the curve is the center part which is essentially a straight line. The bending at the ends indicates that the modulator is no longer linear; this departure from linearity will cause harmonic distortion and will broaden the channel occupied by the signal. In the example, the characteristic is linear 1.5 kc. on either side of the center or carrier frequency.

A good modulation indicator is a "magic-eye" tube such as the 6E5. This should be connected across the grid resistor of the reactance modulator as shown in Fig. 12-6. Note its deflection (using the d.c. voltage method as in Fig. 12-4) at the maximum deviation to be used. For narrow-band f.m. the proper deviation is approximately 2000 cycles (this maximum deviation is based on an upper a.f. limit of 3000 cycles and a deviation ratio of 0.7) at the output frequency. This deflection represents "100 per cent modulation" and with speech input the gain should be kept at the point where it is just reached on voice peaks. If the transmitter is used on more than one band, the gain

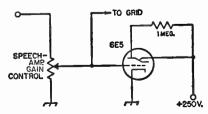


Fig. 12-6—6E5 modulation indicator for f.m. or p.m. modulators. To insure sufficient grid voltage for a good deflection, it may be necessary to connect the gain control in the modulator grid circuit rather than in an earlier speech-amplifier stage.

control should be marked at the proper setting for each band, because the signal amplitude that gives the correct deviation on one band will be either too great or too small on another. For example, if the output frequency is in the 29-Mc. band and the oscillator is on 7 Mc., the deviation at the *oscillator* frequency should not exceed 2000/4, or 500 cycles.

Checking with a Crystal-Filter Receiver

With p.m. the d.c. method of checking just described cannot be used, because the frequency deviation at zero frequency (d.c.) also is zero. For narrow-band p.m. it is necessary to check the actual width of the channel occupied by the transmission. (The same method also can be used to check f.m.) For this purpose it is necessary to have a crystal-filter receiver and an a.f. oscillator that generates a 3000-cycle sine wave.

Keeping the signal intensity in the receiver at a medium level, tune in the carrier at the output frequency. Do not use the a.v.c. Switch on the beat oscillator, and set the crystal filter at its sharpest position. Peak the signal on the crystal and adjust the b.f.o. for any convenient beat note. Then apply the 3000-cycle tone to the speech amplifier (through an attenuator, if necessary, to avoid overloading; see chapter on audio amplifiers) and increase the audio gain until there is a small amount of modulation. Tuning the receiver near the carrier frequency will show the presence of sidebands 3 kc. from the carrier on both sides. With low audio input, these two should be the only sidebands detectable.

Now increase the audio gain and tune the receiver over a range of about 10 kc. on both sides of the carrier. When the gain becomes high enough, a second set of sidebands spaced 6 kc. on either side of the carrier will be detected. The signal amplitude at which these sidebands become detectable is the maximum speech amplitude that should be used. If the 6E5 modulation indicator is incorporated in the modulator, its deflection with the 3000-cycle tone will be the "100 per cent modulation" deflection for speech.

When this method of checking is used with a reactance-tube-modulated f.m. (not p.m.) transmitter, the linearity of the system can be

checked by observing the carrier as the a.f. gain is slowly increased. The beat-note frequency will stay constant so long as the modulator is linear, but nonlinearity will be accompanied by a shift in the average carrier frequency that will cause the beat note to change in frequency. If such a shift occurs at the same time that the 6-kc. sidebands appear, the extra sidebands may be caused by modulator distortion rather than by an excessive modulation index. This means that the modulator is not capable of shifting the frequency over a wide-enough range. The 6-kc. sidebands should appear before there is any shift in the carrier frequency.

R.F. Amplifiers

The r.f. stages in the transmitter that follow the modulated stage may be designed and adjusted as in ordinary operation. In fact, there are no special requirements to be met except that all tank circuits should be carefully tuned to resonance (to prevent unwanted r.f. phase shifts that might interact with the modulation and thereby introduce hum, noise and distortion). In neutralized stages, the neutralization should be as exact as possible, also to minimize unwanted phase shifts. With f.m. and p.m., all r.f. stages in the transmitter can be operated at the manufacturer's maximum c.w.-telegraphy ratings, since the average power input does not vary with modulation as it does in a.m. phone operation.

The output power of the transmitter should be checked for amplitude modulation. It should not change from the unmodulated-carrier value when the transmitter is modulated. If no output indicator is available, a flashlight lamp and loop can be coupled to the final tank coil to serve as a current indicator. If the carrier amplitude is constant, the lamp brilliance will not change with modulation.


Amplitude modulation accompanying f.m. or p.m. is just as much to be avoided as frequency or phase modulation that accompanies a.m. A mixture of a.m. with either of the other two systems results in the generation of spurious sidebands and consequent widening of the channel. If the presence of a.m. is indicated by variation of antenna current with modulation, the cause is almost certain to be nonlinearity in the modulator.

RECEPTION OF F.M. AND P.M. SIGNALS

Receivers for f.m. and p.m. signals differ from those for a.m. and s.s.b. principally in two features — there is no need for linearity in the amplifier stages preceding detection (in fact, it is advantageous if the amplitude variations in the signal and background noise can be "washed out"), and the detector must be capable of converting the frequency variations in the incoming signal into amplitude variations. These amplitude variations, combined with rectification, produce an audio voltage corre-

sponding to the frequency or phase modulation on the signal.

Frequency- or phase-modulated signals can be received after a fashion on any ordinary receiver that has a selectivity curve with sloping sides. As shown in Fig. 12-7A, the receiver is tuned so that the carrier frequency is placed part-way down on one side of the selectivity curve so that the amplitude is less than the maximum that would be possible with normal tuning. When the frequency of the signal varies

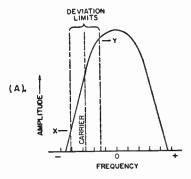

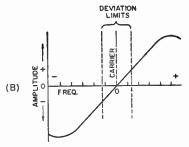


Fig. 12-7—F.m. or p.m. detection characteristics. A—
"Slope detection," using the sloping side of the receiver's selectivity curve to convert f.m. or p.m. to a.m.
for subsequent rectification. B—Typical discriminator
characteristic. The straight portion of this curve between the two peaks is the useful region. The peaks
should always lie outside the pass band of the
receiver's selectivity curve.

with modulation it swings between some such limits as are indicated in Fig. 12-7A, resulting in an amplitude-modulated output varying between X and Y. After this f.m.-to-a.m. conversion the signal goes to a conventional detector (usually a diode) and is rectified in the same way as an a.m. signal.

With most receivers, particularly those hav-

ing steep-sided selectivity curves, the method is not very satisfactory because the distortion is quite severe unless the frequency deviation is small, because the relationship between frequency deviation and output amplitude is linear over only a small part of the selectivity curve.

A detector designed expressly for f.m. or p.m. will have a characteristic similar to that shown in Fig. 12-7B. The output is zero when the unmodulated carrier is tuned to the center, θ , of the characteristic. When the frequency swings higher, the rectified output amplitude increases in the positive direction (as chosen in this example), and when the frequency swings lower the output amplitude increases in the negative direction. Over the range in which the characteristic is a straight line the conversion from f.m. to a.m. is linear and there is no distortion. One type of detector that operates in this way is the frequency discriminator, which combines the f.m.-to-a.m. conversion with rectification to give an audio-frequency output from the frequency-modulated r.f. signal.

Limiter and Discriminator

A practical discriminator circuit is shown in Fig. 12-8. The f.m.-to-a.m. conversion takes place in transformer T1, which operates at the intermediate frequency of a superheterodyne receiver. The voltage induced in the transformer secondary, S, is 90 degrees out of phase with the primary current. The primary voltage is introduced at the center tap on the secondary through C1 and combines with the secondary voltages on each side of the center tap in such a way that the resultant voltage on one side of the secondary leads the primary voltage and the voltage on the other side lags by the same phase angle, when the circuits are resonated to the unmodulated carrier frequency. When rectified, these two voltages are equal and of opposite polarity. If the frequency changes, there is a shift in the relative phase of the voltage components that results in an in-

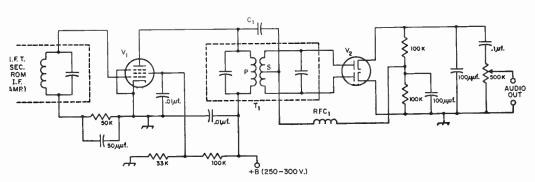


Fig. 12-8—Limiter-discriminator circuit. This type of circuit is frequently used at 455 kc. in the form of an "adapter" for communications receivers, for reception of narrow-band f.m. signals.

C₁—App. 100 $\mu\mu$ f. for 455-kc. i.f.; 50 $\mu\mu$ f. for higher frequencies.

T₁—Discriminator transformer for i.f. used. Push-pull diode transformer may be substituted.

RFC₁—10 mh. r.f. choke for 455-kc. i.f.; 2.5 mh. satisfactory for frequencies above 3 Mc.

V₁—6AU6 or equivalent. V₂—6AL5 or equivalent. crease in output amplitude on one side of the secondary and a corresponding decrease in amplitude on the other side. Thus the voltage applied to one diode of V_2 increases while the voltage applied to the other diode decreases. The difference between these two voltages, after rectification, is the audio-frequency output of the detector.

The ouput amplitude of a simple discriminator depends on the amplitude of the input r.f. signal, which is undesirable because the noise-reducing benefits of f.m. are not secured if the receiving system is sensitive to amplitude variations. A discriminator is always preceded by some form of amplitude limiting, therefore. The conventional type of limiter also is shown in Fig. 12-8. It is simply a pentode i.f. amplifier, V_1 , with its operating conditions chosen so that it "saturates" on a relatively small signal voltage. The limiting action is aided by grid

rectification, with grid-leak bias developed in the 50,000-ohm resistor in the grid circuit. Another contributing factor is low screen voltage, the screen voltage-divider constants being chosen to result in about 50 volts on the screen.

Receiver Tuning with an F.M. Detector

In tuning a signal with a receiver having a discriminator or other type of f.m. detector the tuning controls should be adjusted to center the carrier on the detector characteristic. At this point the noise suppression is most marked, so the proper setting is easily recognized. An amplitude-modulated signal tuned at the same point will have its modulation "washed off" if the signal is completely limited in amplitude and the discriminator alignment is symmetrical. With either f.m. or a.m. signals, there will be a distorted audio-frequency output if the receiver is tuned "off-center."

RADIOTELETYPE

Radioteletype (abbreviated RTTY) is a form of telegraphic communication employing type-writer-like machines for 1) generating a coded set of electrical impulses when a typewriter key corresponding to the desired letter or symbol is pressed, and 2) converting a received set of such impulses into the corresponding printed character. The message to be sent is typed out in much the same way that it would be written on a typewriter, but the printing is done at the distant receiving point. The teletypewriter at the sending point also prints the same material, for checking and reference.

The machines used for RTTY are far too complex mechanically for home construction, and if purchased new would be highly expensive. However, used teletypewriters in good mechanical condition are available at quite reasonable prices. These are machines retired from commercial service but capable of entirely satisfactory operation in amateur work. They may be obtained from a number of sources (latest information on this may be obtained from ARRL, West Hartford, Conn.) on condition that they will be used purely for amateur purposes and will not be resold for commercial use.

Types of Machines

There are two general types of machines, the page printer and the tape printer. The former prints on a paper roll about the same width as a business letterhead. The latter prints on paper tape, usually gummed on the reverse side so it may be cut to letter-size width and pasted on a sheet of paper in a series of lines. The page printer is the more common type in the equipment available to amateurs.

The operating speed of most machines is such that characters are sent at the rate of about 60 words per minute. Ordinary teletypewriters are of the start-stop variety, in which the pulse-forming mechanism (motor driven) is at rest

until a typewriter key is depressed. At this time it begins operating, forms the proper pulse sequence, and then comes to rest again before the next key is depressed to form the following character. The receiving mechanism operates in similar fashion, being set into operation by the first pulse of the sequence from the transmitter. Thus, although the actual transmission speed cannot exceed about 60 w.p.m. it can be considerably slower, depending on the typing speed of the operator.

It is also possible to transmit by using perforated tape. This has the advantage that the complete message may be typed out in advance of actual transmission, at any convenient speed; when transmitted, however, it is sent at the machine's normal maximum speed. A special transmitting head and tape perforator are required for this process. A reperforator is a device that may be connected to the conventional teletypewriter for punching tape when the machine is operated in the regular way. It may thus be used either for an original message or for "taping" an incoming message for retransmission.


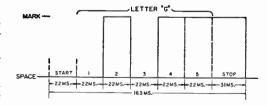


Fig. 12-9—Pulse sequence in the teletype code. Each character begins with a start pulse, always a "space," and ends with a "stop" pulse, always a "mark." The distribution of marks and spaces in the five elements between start and stop determines the particular character transmitted.

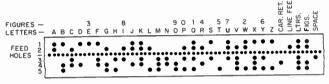

bols are secured by carriage shift.

There are no lower-case letters on a teletypewriter. Where blanks appear in the above chart in the "FIGS" line, characters may differ on different machines.

Teletype Code

In the special code used for teletype every character has five "elements" sent in sequence. Each element has two possible states, either "mark" or "space," which are indicated by different types of electrical impulses (i.e., mark might be indicated by a negative voltage and space by a positive voltage). In customary practice each element occupies a time of 22 milliseconds. In addition, there is an initial "start" element (space), also 22 milliseconds long, to set the sending and receiving mechanisms in operation, and a terminal "stop" element (mark) 31 milliseconds long, to end the operation and ready the machine for the next character.

This sequence is illustrated in Fig. 12-9. which shows the letter G with its start and stop elements. The letter code as it would appear on perforated tape is shown in Fig. 12-10, where the black dots indicate marking pulses. Figures and arbitrary signs — punctuation, etc. — use the same set of code impulses as the alphabet, and are selected by shifting the carriage as in the case of an ordinary typewriter. The carriage shift is accomplished by transmitting either the "LTRS" or "FIGS" code symbol as required. There is also a "carriage return" code character to bring the carriage back to the starting position after the end of the line is reached on a page printer, and a "line feed" character to advance the page to the next line after a line is completed.

Additional System Requirements

To be used in radio communication, the pulses (d.c.) generated by the teletypewriter must be utilized in some way to key a radio transmitter so they may be sent in proper sequence and usable form to a distant point. At the receiving end the incoming signal must be converted into d.c. pulses suitable for operating the printer. These functions, shown in block form in Fig. 12-11, are performed by electronic

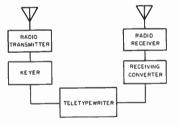


Fig. 12-11—Radioteletype in block form.

units known respectively as the keyer and re-

Fig. 12-10—Teletype letter code as it appears on perforated tape. Start and stop elements do not appear on tape. Elements are numbered from top to bottom, and dots indicate marking pulses. Numerals, punctuation sians, and other arbitrary sym-

The radio transmitter and receiver are quite conventional in design. Practically all the special features needed can be incorporated in the keyer and converter, so that any ordinary amateur equipment is suitable for RTTY with little modification.

Transmission Methods

It is quite possible to transmit teletype signals by ordinary "on-off" or "make-break" keying such as is used in regular hand-keyed c.w. transmission. In practice, however, frequency-shift keying is preferred because it gives definite pulses on both mark and space, which is an advantage in printer operation. Also, since f.s.k. can be received by methods similar to those used for f.m. reception, there is considerable discrimination against noise, both natural and man-made, distributed uniformly across the receiver's pass band, when the received signal is not too weak. Both factors make for increased reliability in printer operation.

Frequency-Shift Keying

General practice with f.s.k. is to use a frequency shift of 850 cycles per second, although FCC regulations permit the use of any value of frequency shift up to 900 cycles. The smaller values of shift have been shown to have a signal-to-noise-ratio advantage in commercial circuits, and are currently being experimented with by amateurs. At present, however, the major part of amateur RTTY work is done with the 850-cycle shift. This figure also is used in much commercial work. The nominal transmitter frequency is the mark condition and the frequency is shifted 850 cycles (or whatever shift may be chosen) lower for space.

On the v.h.f. bands where A2 transmission is permitted audio frequency-shift keying (a.f.s.k.) is generally used. In this case the r.f. carrier is transmitted continuously, the pulses being transmitted by frequency-shifted tone modulation. The audio frequencies used have been more-or-less standardized at 2125 and 2975 cycles per second, the shift being 850 cycles as in the case of straight f.s.k. (These frequencies are the 5th and 7th harmonics, respectively, of 425 cycles, which is half the shift frequency, and thus are convenient for calibration and alignment purposes.) With a.f.s.k. the lower audio frequency is customarily used for mark and the higher for space.

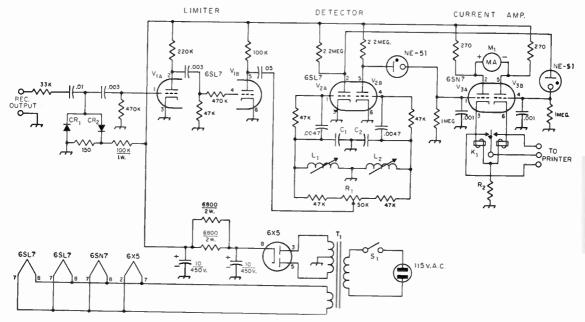


Fig. 12-12—Receiving converter far f.s.k. teletype signals (W2PAT). Unless atherwise indicated, capacitances are in μf. resistances are in ahms, resistars are ½ watt. Capacitors of 0.01 μf. ar less may be mica or ceramic; larger values may be paper. Capacitors with polarities indicated are electrolytic.

C₁—0.15-µf. paper.
C₂—0.1-µf. paper.
C₂—0.1-µf. paper.
CR₁, CR₂—1N34 or equivalent.
K₁—Polar relay, to operate on 20 ma.
L₁—36 mh. (TV width control, GE type RLD-019).
L₂—29 mh. (TV width control, GE type RLD-014).
M₁—Zero-center d.c. milliammeter, 20 ma. or more full scale (may be a 100-0-100 microammeter ap-

propriately shunted).

R₁—50,000-ohm volume control, linear taper.

R₂—1000 ohms, 1 watt.

S₁—S.p.s.t. toggle.

T₁—Power transformer, 500 volts c.t., 30 ma.; 6.3 volts

3 amp.

V₁, V₂—6SL7 (or 12AX7).

V₈—6SN7GT (or 12AU7).

THE RECEIVING CONVERTER

In receiving an f.s.k. teletype signal, the receiver's beat-frequency oscillator is turned on as for ordinary c.w. reception and the receiver tuning is then adjusted so that the mark and space signals produce audio beat tones of 2125 and 2975 cycles. Either frequency can be used for either mark or space, but no matter which may be used at the transmitter, the mark and space frequencies can be reversed at the receiver simply by tuning to the "other side of zero beat." (This cannot be done with a.f.s.k., of course, but the reversal can be accomplished quite simply, if necessary, by interchanging the outputs from the two frequencies as applied to the printer.) The audio-frequency tones are applied to separate rectifiers to convert them into d.c. impulses, which may then be further amplified to the power level required to operate the printer.

The receiving converter which performs these functions generally will include means for clipping or limiting the signals so they are held at constant amplitude, and may also include provision for some shaping of the pulses

to overcome distortion that occurs in transmission. There are many ways by which these results can be accomplished, and the higher the order of performance the more complicated the circuits become. However, satisfactory results under reasonably good receiving conditions can be secured with relatively simple equipment, and the "basic" circuit shown in Fig. 12-12 has proved to be quite successful in practice. It operates as follows:

When audio output from the receiver is applied, the two diodes, CR_1 and CR_2 , which are biased with approximately 0.3 volt, limit the peak voltage at the grid of the limiter tube, $V_{1}A$, to 0.6 volt or less for signal voltages up to 30 volts or more. Additional limiting in $V_{1}A$ further stabilizes the voltage level. $V_{1}B$ is primarily an amplifier, and delivers approximately 15 volts output, constant to within 1 db. for receiver output voltages varying between about 0.5 volt and more than 30 volts.

The two tones, thus limited in amplitude, are applied to two simple filter circuits, L_1C_1 and L_2C_2 , tuned to 2125 and 2975 cycles, respectively.


Fig. 12-13—Modification of converter circuit for use with single-magnet printers. Unless otherwise indicated, capacitances are in μf., resistances in ohms, resistors are ½ watt.
 M1—Zero-center d.c. milliammeter, 100 ma. full scale (may be microammeter with appropriate shunt).
 R1—50,000-ohm volume control.

The two tones are thus separated, one being applied to the grid of V_{2A} and the other to the grid of V_{2B} . V_{2A} and V_{2B} operate as grid-leak detectors, and when a signal is applied to, say, V_{2A} , the flow of grid current

causes the grid to be driven practically to platecurrent cutoff. As a result the plate voltage on V_{2A}, normally 15 volts with no signal, rises to 50 volts. This is sufficient to ignite the neon lamp connected between the plate of V2A and the grid of V₈B, and a positive bias of about 25 volts is applied to the grid of V₃B. V₃B then takes a plate current of about 20 ma. and a bias of 20 volts is developed across the common cathode resistor, R_2 . This is sufficient to cut off the plate current of V_{sA}, hence the left-hand magnet of the polarized relay, K1, is inoperative while the righthand magnet closes the contacts on its side. A similar action takes place when a signal is applied to the grid of V_{2B} but not to V_{2A} ; in this case the relay contacts are pulled to the left. The relay thus keys the mark and space voltages applied to the printer.

Potentiometer R_1 is adjusted so that incoming noise (which will affect both channels equally) is balanced out and does not cause K_1 to operate. The neon lamps improve the operation of the circuit by acting as switches, making for sharp demarcation between mark and

space pulses.

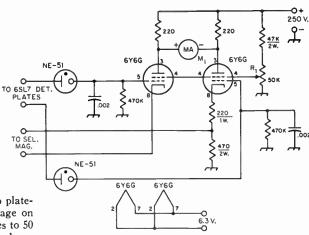

The zero-center meter, M_1 , is not a necessity but is a convenience in making adjustments. R_1 should be adjusted on receiver noise for zero reading. With a 2125-cycle tone the pointer will swing to the left and L_1 should be adjusted for maximum deflection. With a 2975-cycle tone the pointer will swing to the right and L_2 should be adjusted for maximum deflection. Equal deflections should be obtained from both channels.

The keying circuit shown in Fig. 12-12 is for use with the Model 12 machine which requires an external power supply. For machines having a single selector magnet the modification shown in Fig. 12-13 may be used so the printer may be operated directly. These machines usually require a current of 60 ma., which will be furnished by this circuit and may be adjusted to the correct value by means of R₁. Note that a heavier power supply is required than that of Fig. 12-12.

FREQUENCY-SHIFT KEYERS

The keyboard contacts of the teletypewriter actuate a direct-current circuit that operates the printer magnets, and a pair of terminals is provided at which a keyed d.c. signal of the order of 100 volts is available. (Some machines, such as the Model 12, require an external d.c. power supply for this purpose; others have self-contained power supplies.) In the "resting" condition the contacts are closed (mark) and the voltage at the terminals, which are in parallel with the contacts, is zero. In operation, the contacts open for "space" and the full voltage appears across the terminals. As normally connected, the spacing signal has positive polarity.

This keyed d.c. voltage may be used to operate a keyer circuit for the radio transmitter, provided it is not "loaded" to such an extent that it affects the operation of the printer. Alternatively, the keyed current, rather than the voltage, may be used for external keying. This can be done by using an auxiliary keying relay with its coil connected in series with the printer

magnet or relay circuit. A fast-acting relay must be used, and the coil must be one that will operate satisfactorily on the current available in the printer circuit. This will usually be either 20 or 60 milliamperes, depending on the type of machine.

F.S.K. with Variable-Frequency Oscillators

Perhaps the simplest satisfactory circuit for frequency-shift keying a v.f.o. is the one shown in Fig. 12-14A. This operates from the voltage available at the keyboard contact terminals and uses a reactance tube to obtain the required frequency shift.

The frequency shift is obtained by changing the plate resistance of the reactance tube, V_2 , so that in effect the variable capacitor C_2 is alternately disconnected or connected in parallel with the tuning capacitor in the v.f.o. tank circuit. With no voltage applied to the grid, V_2 is biased so that the plate current is low and the effect of C_2 on the oscillator frequency is small.



SPECIALIZED COMMUNICATION SYSTEMS

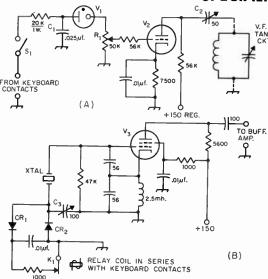


Fig. 12-14—Frequency-shift keyer circuits. Unless otherwise indicated, capacitances are in $\mu\mu$ f., resistances are in ohms, resistors are ½ watt. A—Reactance-tube keyer far use with variable-frequency ascillator (W6OWP). B—Crystal oscillator circuit (W2PAT). It is essential that all leads associated with the crystal portion of the circuit be held to a small fraction of an inch in length if maximum shift is desired.

C₁—Paper (see text).

 C_2 —50- $\mu\mu$ f. midget variable.

C₃-100-µµf. midget variable.

CR1, CR2-1N34 or equivalent.

K₁—Normally closed relay, fast operating, cail current according to printer magnet or relay current.

R1-Volume control.

S₁-S.p.s.t. toggle.

V1-1-watt neon bulb without base resistor.

V₂—6C4 or equivalent.

V₈-6AK5 or equivalent.

When a positive voltage from the keyboard contacts is applied to the grid the plate resistance is low and the oscillator frequency becomes lower because of the greater effect of C_2 . The amount of frequency shift depends on the capacitance of C_2 and the amplitude of the positive voltage applied to the grid of V_2 . The latter can be controlled by R_1 .

 C_1 , the associated 20,000-ohm resistor, and the neon bulb, V_1 , constitute a filter for removing clicks generated at the keyboard contacts. The value of C_1 depends somewhat on the machine, and values up to 0.25 μ f. can be used, if necessary, without objectionable distortion of the keying pulses. The capacitance should be adjusted for clickless keying.

The frequency-shift circuit should be initially adjusted at the lowest radio frequency to be used, since the shift will be smallest in this case. If C_2 is set so a shift of 850 cycles is obtained at this frequency, further adjustment of

the shift may be made by means of R_1 . If the transmitter output is on a higher-frequency band than that on which the v.f.o. operates, the shift at the v.f.o. fundamental frequency must be reduced accordingly.

F.S.K. With Crystal Oscillators

Fig. 12-14B is a circuit which has been found to give a frequency shift of 850 cycles or more with crystals of the type ordinarily used for frequencies of the order of 3.5 Mc. and higher. This is an oscillator of the "grid-plate" type discussed in Chapter 6 on transmitters, with the addition of a variable capacitor, C_8 , in series with the crystal. C_8 reduces the total capacitance across the crystal and thus raises the oscillation frequency. When it is shorted out the capacitance across the crystal is higher and the resulting frequency is lower.

Although relay contacts could be used for shorting the capacitor, the diode arrangement shown in Fig. 12-14B is more reliable in practice. With the contacts of K_1 open there is no d.c. path through CR_2 and it acts simply as a small capacitance (about $1~\mu\mu$ f.) in parallel with C_3 . When the contacts of K_1 are closed there is a d.c. circuit through CR_1 , CR_2 and the 1000-ohm resistor. Thus there is a path for direct current flow as a result of rectification of the r.f. voltage across CR_2 . Because of the d.c. bias the resistance of CR_2 drops to a low value and C_3 is effectively shorted out.

Adjustment of the circuit consists simply of determining the setting of C_s at which the operating frequency is 850 cycles (or the desired shift) higher with the contacts of K_1 open than the frequency when the relay contacts are closed. A normally closed relay is used in order to make the mark frequency lower than the space frequency, in accordance with usual practice.

Frequency Adjustment

The frequency shift, whatever the type of circuit, should be made as nearly exact as available equipment will permit, since the shift must match the frequency difference between the filters in the receiving converter if the signals are to be usable at the receiving end. An accurately calibrated audio oscillator is useful for this purpose. To check, the mark frequency should be tuned in on the station receiver, with the b.f.o. on, and the receiver set to exact zero beat (see Chapter 21 on measurements for identification of exact zero beat). The space frequency should then be adjusted to exactly the desired shift. This may be done by adjusting for an auditory zero beat between the beat tone from the receiver and the tone from the audio oscillator. If an oscilloscope is available, the frequency adjustment may be accomplished by feeding the receiver tone to the vertical plates and the audio-oscillator tone to the horizontal plates, and then adjusting the space frequency for the elliptical pattern that indicates the two frequencies are the same.

Transmission Lines

The place where r.f. power is generated is very frequently not the place where it is to be utilized. A transmitter and its antenna are a good example: The antenna, to radiate well, should be high above the ground and should be kept clear of trees, buildings and other objects that might absorb energy, but the transmitter itself is most conveniently installed indoors where it is readily accessible.

The means by which power is transported from point to point is the r.f. transmission line.

At radio frequencies a transmission line exhibits entirely different characteristics than it does at commercial power frequencies. This is because the speed at which electrical energy travels, while tremendously high as compared with mechanical motion, is not infinite. The peculiarities of r.f. transmission lines result from the fact that a time interval comparable with an r.f. cycle must elapse before energy leaving one point in the circuit can reach another just a short distance away.

OPERATING PRINCIPLES

If a source of e.m.f.—a battery, for example -is connected to the ends of a pair of insulated parallel wires that extend outward for an infinite distance, electric currents will immediately become detectable in the wires near the battery terminals. The electric field of the battery will cause free electrons in the wire connected to the positive terminal to be attracted to the battery, and an equal number of free electrons in the wire connected to the negative terminal will be repelled from the battery. These currents do not flow instantaneously throughout the length of the wires; the electric field that causes the electron movement cannot travel faster than the speed of light, so a measurable interval of time elapses before the currents become evident even a relatively short distance away.

For example, the currents would not become detectable 300 meters (nearly 1000 feet) from the battery until at least a microsecond (one millionth of a second) after the connection was made. By ordinary standards this is a very short length of time, but in terms of radio frequency it represents the time of one

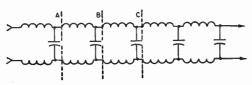


Fig. 13-1—Equivalent of a transmission line in lumped circuit constants.

complete cycle of a 1000-kilocycle current—a frequency considerably lower than those with which amateurs communicate.

The current flows to charge the capacitance

between the two wires. However, the conductors of this "linear" capacitor also have appreciable inductance. The line may be thought of as being composed of a whole series of small inductances and capacitances connected as shown in Fig. 13-1, where each coil is the inductance of a very short section of one wire and each capacitor is the capacitance between two such short sections.

Characteristic Impedance

An infinitely long chain of coils and capacitors connected as in Fig. 13-1, where the small inductances and capacitances all have the same values, respectively, has an important property. To an electrical impulse applied at one end, the combination appears to have an impedance — called the characteristic impedance or surge impedance — approximately equal to $\sqrt{L/C}$ where L and C are the inductance and capacitance per unit length. This impedance is purely resistive.

In defining the characteristic impedance as $\sqrt{L/C}$, it is assumed that the conductors have no inherent resistance - that is, there is no I2R loss in them - and that there is no power loss in the dielectric surrounding the conductors. There is thus no power loss in or from the line no matter how great its length. This may not seem consistent with calling the characteristic impedance a pure resistance, which implies that the power supplied is all dissipated in the line. But in an infinitely long line the effect, so far as the source of power is concerned, is exactly the same as though the power were dissipated in a resistance, because the power leaves the source and travels outward forever along the line.

The characteristic impedance determines the amount of current that can flow when a given voltage is applied to an infinitely long line, in exactly the same way that a definite value of actual resistance limits current flow when a voltage is applied.

The inductance and capacitance per unit length of line depend upon the size of the conductors and the spacing between them. The closer the two conductors and the greater their diameter, the higher the capacitance and the lower the inductance. A line with large conductors closely spaced will have low impedance, while one with small conductors widely spaced will have relatively high impedance.

"Matched" Lines

Actual transmission lines do not extend to infinity but have a definite length and are connected to, or terminate in, a load at the "output" end, or end to which the power is delivered. If the load is a pure resistance of a value equal to the characteristic impedance of the line, the line is said to be matched. To current traveling along the line such a load just looks like still more transmission line of the same characteristic impedance.

In other words, a short line terminated in a purely resistive load equal to the characteristic impedance of the line acts just as though it were infinitely long. In a matched transmission line, power travels outward along the line from the source until it reaches the load, where it is completely absorbed.

R.F. on Lines

The principles discussed above, although based on direct-current flow from a battery. also hold when an r.f. voltage is applied to the line. The difference is that the alternating voltage causes the amplitude of the current at the input terminals of the line to vary with the voltage, and the direction of current flow also periodically reverses when the polarity of the applied voltage reverses. The current at a given instant at any point along the line is the result of a voltage that was applied at some earlier instant at the input terminals. Since the distance traveled by the electromagnetic fields in the time of one cycle is equal to one wavelength (Chapter 2), the instantaneous amplitude of the current is different at all points in a one-wavelength section of line. In fact, the current flows in opposite directions in the same wire in successive half-wavelength sections. However, at any given point along the line the current goes through similar variations with time that the current at the input terminals did.

Thus the current (and voltage) travels along the wire as a series of waves having a length equal to the speed of travel divided by the frequency of the a.c. voltage. On an infinitely long line, or one properly matched by its load, an ammeter inserted anywhere in the line will show the same current, because the ammeter averages out the variations in

current during a cycle. It is only when the line is not properly matched that the wave motion becomes apparent through observations made with ordinary instruments.

STANDING WAVES

In the infinitely long line (or its matched counterpart) the impedance is the same at any point on the line because the ratio of voltage to current is always the same. However, the impedance at the end of the line in Fig. 13-2 is zero --- or at least extremely small --- because the line is short-circuited at the end. The outgoing power, on meeting the short-circuit, reverses its direction of flow and goes back along the transmission line toward the input end. There is a large current in the shortcircuit, but substantially no voltage across the line at this point. We now have a voltage and current representing the power going outward (incident power) toward the shortcircuit, and a second voltage and current representing the reflected power traveling back toward the source.

The reflected current travels at the same speed as the outgoing current, so its instantaneous value will be different at every point along the line, in the distance represented by the time of one cycle. At some points along

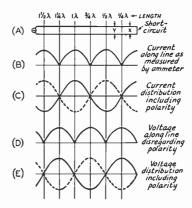


Fig. 13-2—Standing waves of valtage and current along shart-circuited transmission line.

the line the phase of the incident and reflected currents will be such that the currents cancel each other while at others the amplitude will be doubled. At in-between points the amplitude is between these two extremes. The points at which the currents are in and out of phase depend only on the *time* required for them to travel and so depend only on the *distance* along the line from the point of reflection.

In the short-circuit at the end of the line the two current components are in phase and the total current is large. At a distance of one-half wavelength back along the line from the short-circuit the outgoing and reflected components will again be in phase and the re-

Standing Waves

sultant current will again have its maximum value. This is also true at any point that is a multiple of a half wavelength from the short-circuited end of the line.

The outgoing and reflected currents will cancel at a point one-quarter wavelength, along the line, from the short-circuit. At this point, then, the current will be zero. It will also be zero at all points that are an odd multiple of one-quarter wavelength from the short-circuit.

If the current along the line is measured at successive points with an ammeter, it will be found to vary about as shown in Fig. 13-2B. The same result would be obtained by measuring the current in either wire, since the ammeter cannot measure phase. However, if the phase could be checked, it would be found that in each successive half-wavelength section of the line the currents at any given instant are flowing in opposite directions, as indicated by the solid line in Fig. 13-2C. Furthermore, the current in the second wire is flowing in the opposite direction to the current in the adjacent section of the first wire. This is indicated by the broken curve in Fig. 13-2C. The variations in current intensity along the transmission line are referred to as standing waves. The point of maximum line current is called a current loop or current antinode and the point of minimum line current is called a current node.

Voltage Relationships

Since the end of the line is short-circuited, the voltage at that point has to be zero. This can only be so if the voltage in the outgoing wave is met, at the end of the line, by a reflected voltage of equal amplitude and opposite polarity. In other words, the phase of the voltage wave is reversed when reflection takes place from the shortcircuit. This reversal is equivalent to an extra half cycle or half wavelength of travel. As a result, the outgoing and returning voltages are in phase a quarter wavelength from the end of the line, and again out of phase a half wavelength from the end. The standing waves of voltage, shown at D in Fig. 13-2, are therefore displaced by one-quarter wavelength from the standing waves of current. The drawing at E shows the voltages on both wires when phase is taken into account. The polarity of the voltage on each wire reverses in each half wavelength section of transmission line. A voltage maximum is called a voltage loop or antinode and a voltage minimum is called a voltage node.

Open-Circuited Line

If the end of the line is open-circuited instead of short-circuited, there can be no current at the end of the line but a large voltage can exist. Again the incident power is reflected back toward the source. The incident and reflected components of current must be equal and opposite in phase at the open circuit in order for the total current at the end of the line to be zero. The incident and reflected components of voltage are in phase and add together. The result is again that there are standing waves, but the conditions are reversed as compared with a short-circuited line. Fig. 13-3 shows the open-circuited line case.

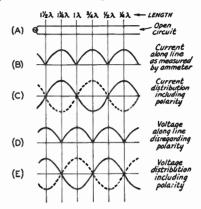


Fig. 13-3—Standing waves of current and voltage along an open-circuited transmission line.

Lines Terminated in Resistive Load

Fig. 13-4 shows a line terminated in a resistive load. In this case at least part of the incident power is absorbed in the load, and so is not available to be reflected back toward the source. Because only part of the power is reflected, the reflected components of voltage and current do not have the same magnitude as the incident components. Therefore neither voltage nor current cancel completely at any point along the line. However, the speed at which the incident and reflected components travel is not affected by their amplitude, so the phase relationships are similar to those in open- or short-circuited lines.

It was pointed out earlier that if the load resistance, $Z_{\rm R}$, is equal to the characteristic impedance, $Z_{\rm 0}$, of the line all the power is absorbed in the load. In such a case there is no reflected power and therefore no standing waves of current and voltage. This is a special case that represents the change-over point

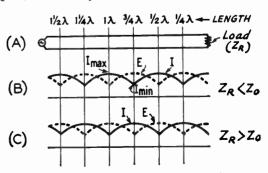


Fig. 13-4—Standing waves on a transmission line terminated in a resistive load.

between "short-circuited" and "open-circuited" lines. If Z_R is less than Z_0 , the current is largest at the load, while if Z_R is greater than Z_0 the voltage is largest at the load. The two conditions are shown at B and C, respectively, in Fig. 13-4.

The resistive termination is an important practical case. The termination is seldom an actual resistor, the most common terminations being resonant circuits or resonant antenna systems, both of which have essentially resistive impedances. If the load is reactive as well as resistive, the operation of the line resembles that shown in Fig. 13-4, but the presence of reactance in the load causes two modifications: The loops and nulls are shifted toward or away from the load; and the amount of power reflected back toward the source is increased, as compared with the amount reflected by a purely resistive load of the same total impedance. Both effects become more pronounced as the ratio of reactance to resistance in the load is made larger.

Standing-Wave Ratio

The ratio of maximum current to minimum current along a line, Fig. 13-5, is called the standing-wave ratio. The same ratio holds for maximum voltage and minimum voltage. It is a measure of the mismatch between the load and the line, and is equal to 1 when the line is perfectly matched. (In that case the "maximum" and "minimum" are the same, since the current and voltage do not vary along the line.) When the line is terminated in a purely resistive load, the standing-wave ratio is

$$S.W.R. = \frac{Z_R}{Z_0} \text{ or } \frac{Z_0}{Z_R}$$
 (13-A)

Where S.W.R. = Standing-wave ratio

 $Z_{\rm R} =$ Impedance of load (must be

pure resistance) $Z_0 = \text{Characteristic impedance of}$

Example: A line having a characteristic impedance of 300 ohms is terminated in a resistive load of 25 ohms. The s.w.r. is

$$S.W.R. = \frac{Z_0}{Z_R} = \frac{300}{25} = 12 \text{ to } 1$$

It is customary to put the larger of the two quantities, Z_B or Z_0 , in the numerator of the

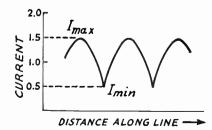


Fig. 13-5—Measurement of standing-wave ratio. In this drawing, I_{max} is 1.5 and I_{min} is 0.5, so the s.w.r. $=I_{\text{max}}I_{\text{min}}=1.5/0.5=3$ to 1.

fraction so that the s.w.r. will be expressed by a number larger than 1.

It is easier to measure the standing-wave ratio than some of the other quantities (such as the impedance of an antenna) that enter into transmission-line computations. Consequently, the s.w.r. is a convenient basis for work with lines. The higher the s.w.r., the greater the mismatch between line and load. In practical lines, the power loss in the line itself increases with the s.w.r., as shown later.

INPUT IMPEDANCE

The input impedance of a transmission line is the impedance seen looking into the sending-end or input terminals; it is the impedance into which the source of power must work when the line is connected. If the load is perfectly matched to the line the line appears to be infinitely long, as stated earlier, and the input impedance is simply the characteristic impedance of the line itself. However, if there are standing waves this is no longer true; the input impedance may have a wide range of values.

This can be understood by referring to Figs. 13-2, 13-3, or 13-4. If the line length is such that standing waves cause the voltage at the input terminals to be high and the current low, then the input impedance is higher than the Zo of the line, since impedance is simply the ratio of voltage to current. Conversely, low voltage and high current at the input terminals mean that the input impedance is lower than the line Zo. Comparison of the three drawings also shows that the range of input impedance values that may be encountered is greater when the far end of the line is open- or short-circuited than it is when the line has a resistive load. In other words, the higher the s.w.r. the greater the range of input impedance values when the line length is varied.

In addition to the variation in the absolute value of the input impedance with line length, the presence of standing waves also causes the input impedance to contain both reactance and resistance, even though the load itself may be a pure resistance. The only exceptions to this occur at the exact current loops or nodes, at which points the input impedance is a pure resistance. These are the only points at which the outgoing and reflected voltages and currents are exactly in phase: At all other distances along the line the current either leads or lags the voltage and the effect is exactly the same as though a capacitance or inductance were part of the input impedance.

The input impedance can be represented either by a resistance and a capacitance or by a resistance and an inductance. Whether the impedance is inductive or capacitive depends on the characteristics of the load and the length of the line. It is possible to represent the input impedance by an equivalent circuit having resistance and reactance either in ser-

ies or parallel, so long as the total impedance and phase angle are the same in either case.

The magnitude and character of the input impedance is quite important, since it determines the method by which the power source must be coupled to the line. The calculation of input impedance is rather complicated and its measurement is not feasible without special equipment. Fortunately, in amateur work it is unnecessary either to calculate or measure it. The proper coupling can be achieved by relatively simple methods described later in this chapter.

Lines Without Load

The input impedance of a short-circuited or open-circuited line not an exact multiple of one-quarter wavelength long is practically a pure reactance. This is because there is very little power lost in the line. Such lines are frequently used as "linear" inductances and capacitances.

If a shorted line is less than a quarter-wave long, as at X in Fig. 13-2, it will have inductive reactance. The reactance increases with the line length up to the quarter-wave point. Beyond that, as at Y, the reactance is capacitive, high near the quarter-wave point and becoming lower as the half-wave point is approached. It then alternates between inductive and capacitive in successive quarter-wave sections. Just the reverse is true of the open-circuited line

At exact multiples of a quarter wavelength the impedance is purely resistive. It is apparent, from examination of B and D in Fig. 13-2, that at points that are a multiple of a half wavelength—i.e., ½, 1, 1½ wavelengths, etc. -from the short-circuited end of the line the current and voltage have the same values that they do at the short circuit. In other words, if the line were an exact multiple of a half wavelength long the generator or source of power would "look into" a short circuit. On the other hand, at points that are an odd multiple of a quarter wavelength—i.e., 1/4, 3/4, 11/4, etc. from the short circuit the voltage is maximum and the current is zero. Since Z = E/I, the impedance at these points is theoretically infinite. (Actually it is very high, but not infinite. This is because the current does not actually go to zero when there are losses in the line. Losses are always present, but usually are small.)

Impedance Transformation

The fact that the input impedance of a line depends on the s.w.r. and line length can be used to advantage when it is necessary to transform a given impedance into another value.

Study of Fig. 13-4 will show that, just as in the open- and short-circuited cases, if the line is one-half wavelength long the voltage and current are exactly the same at the input terminals as they are at the load. This is also true of lengths that are integral multiples of a half wavelength. It is also true for all values of s.w.r. Hence the input impedance of any line, no matter what its Z₀, that is a multiple of a half wavelength long is exactly the same as the load impedance. Such a line can be used to transfer the impedance to a new location without changing its value.

When the line is a quarter wavelength long, or an odd multiple of a quarter wavelength, the load impedance is "inverted." That is, if the current is low and the voltage is high at the load, the input impedance will be such as to require high current and low voltage. The relationship between the load impedance and input impedance is given by

$$Z_{\rm S} = \frac{Z_0^2}{Z_{\rm R}} \tag{13-B}$$

where Zs = Impedance looking into line (line length an odd multiple of one-quarter wavelength)

ZR = Impedence of load (must be pure resistance)

 Z_0 = Characteristic impedance of line

Example: A quarter-wavelength line having a characteristic impedance of 500 ohms is terminated in a resistive load of 75 ohms. The impedance looking into the input or sending end of the line is

$$Z_{\rm S} = \frac{Z_{\rm 0}^2}{Z_{\rm R}} = \frac{(500)^2}{75} = \frac{250,000}{75} = 3333 \text{ ohms}$$

If the formula above is rearranged, we have

$$Z_0 = \sqrt{Z_{\rm S}Z_{\rm R}} \tag{13-C}$$

This means that if we have two values of impedance that we wish to "match," we can do so if we connect them together by a quarter-wave transmission line having a characteristic impedance equal to the square root of their product. A quarter-wave line, in other words, has the characteristics of a transformer.

Resonant and Nonresonant Lines

The input impedance of a line operating with a high s.w.r. is critically dependent on the line length, and resistive only when the length is some integral multiple of one-quarter wavelength. Lines cut to such a length and operated with a high s.w.r. are called "tuned" or "resonant" lines. On the other hand, if the s.w.r. is low the input impedance is close to the Z_0 of the line and does not vary a great deal with the line length. Such lines are called "flat," or "untuned," or "nonresonant."

There is no sharp line of demarcation between tuned and untuned lines. If the s.w.r. is below 1.5 to 1 the line is essentially flat, and the same input coupling method will work with all line lengths. If the s.w.r. is above 3 or 4 to 1 the type of coupling system, and its adjustment, will depend on the line length and such lines fall into the "tuned" category.

It is usually advantageous to make the s.w.r. as low as possible. A resonant line becomes necessary only when a considerable

mismatch between the load and the line has to be tolerated. The most important practical example of this is when a single antenna is operated on several harmonically related frequencies, in which case the antenna impedance will have widely different values on different harmonics.

RADIATION

Whenever a wire carries alternating current the electromagnetic fields travel away into space with the velocity of light. At power-line frequencies the field that "grows" when the current is increasing has plenty of time to return or "collapse" about the conductor when the current is decreasing, because the alternations are so slow. But at radio frequencies fields that travel only a relatively short distance do not have time to get back to the conductor before the next cycle commences. The consequence is that some of the electromagnetic energy is prevented from being restored to the conductor; in other words, energy is radiated into space in the form of electromagnetic waves.

The lines previously considered have consisted of two parallel conductors of the same diameter. Provided there is nothing in the system to destroy symmetry, at every point along the line the current in one conductor has the same intensity as the current in the other conductor at that point, but the currents

flow in opposite directions. This was shown in Figs. 13-2C and 13-3C. It means that the fields set up about the two wires have the same intensity, but opposite directions. The consequence is that the total field set up about such a transmission line is zero; the two fields "cancel out." Hence no energy is radiated.

Practically, the fields do not quite cancel out because for them to do so the two conductors would have to occupy the same space, whereas they are actually slightly separated. However, the cancelation is substantially complete if the distance between the conductors is very small compared to the wavelength. Transmission line radiation will be negligible if the distance between the conductors is 0.01 wavelength or less, provided the currents in the two wires are balanced.

The amount of radiation also is proportional to the current flowing in the line. Because of the way in which the current varies along the line when there are standing waves, the effective current, for purposes of radiation, becomes greater as the s.w.r. is increased. For this reason the radiation is least when the line is flat. However, if the conductor spacing is small and the currents are balanced, the radiation from a line with even a high s.w.r. is inconsequential. A small unbalance in the line currents is far more serious — and is just as serious when the line is flat as when the s.w.r. is high.

PRACTICAL LINE CHARACTERISTICS

The foregoing discussion of transmission lines has been based on a line consisting of two parallel conductors. The parallel-conductor line is but one of two general types, the other being the coaxial or concentric line. The coaxial line consists of a conductor placed in the center of a tube. The inside surface of the tube and the outside surface of the smaller inner conductor form the two conducting surfaces of the line.

In the coaxial line the fields are entirely inside the tube, because the tube acts as a shield to prevent them from appearing outside. This reduces radiation to the vanishing point. So far as the electrical behavior of coaxial lines is concerned, all that has previously been said about the operation of parallel-conductor lines applies. There are, however, practical differences in the construction and use of parallel and coaxial lines.

PARALLEL-CONDUCTOR LINES

A type of parallel-conductor line sometimes used in amateur installations is one in which two wires (ordinarily No. 12 or No. 14) are supported a fixed distance apart by means of insulating rods called "spacers." The spacings used vary from two to six inches, the smaller spacings being necessary at frequencies of the order of 28 Mc. and higher so that radiation

will be minimized. The construction is shown in Fig. 13-6. Such a line is said to be airinsulated. Typical spacers are shown in Fig. 13-7. The characteristic impedance of such "open-wire" lines is between 400 and 600 ohms, depending on the wire size and spacing.

Parallel-conductor lines also are occasionally constructed of metal tubing of a diameter of ½ to ½ inch. This reduces the characteristic impedance of the line. Such lines are mostly used as quarter-wave transformers, when different values of impedance are to be matched.

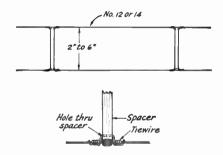


Fig. 13-6—Typical construction of open-wire line. The line conductor fits in a groove in the end of the spacer, and is held in place by a tie-wire anchored in a hole near the groove.

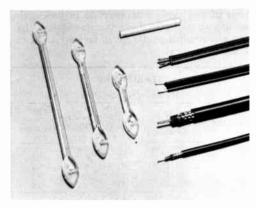


Fig. 13-7—Typical manufactured tronsmission lines and spacers.

Prefabricated parallel-conductor line with air insulation, developed for television reception, can be used in transmitting applications. This line consists of two conductors separated one-half to one inch by molded-on spacers. The characteristic impedance is 300 to 450 ohms, depending on the wire size and spacing.

A convenient type of manufactured line is one in which the parallel conductors are imbedded in low-loss insulating material (polyethylene). It is commonly used as a TV leadin and has a characteristic impedance of about 300 ohms. It is sold under various names, the most common of which is "Twin-Lead." This type of line has the advantages of light weight, close and uniform conductor spacing, flexibility and neat appearance. However, the losses in the solid dielectric are higher than in air, and dirt or moisture on the line tends to change the characteristic impedance. Moisture effects can be reduced by coating the line with silicone grease. A special form of 300-ohm Twin-Lead for transmitting uses a polyethylene tube with the conductors molded diametrically opposite; the longer dielectric path in such line reduces moisture troubles.

In addition to 300-ohm line, Twin-Lead is obtainable with a characteristic impedance of 75 ohms for transmitting purposes. Lightweight 75-and 150-ohm Twin-Lead also is available.

Characteristic Impedance

The characteristic impedance of an air-insulated parallel-conductor line is given by:

$$Z_0 = 276 \log \frac{b}{a} \tag{13-D}$$

where Z_0 = Characteristic impedance

b = Center-to-center distance between conductors

a =Radius of conductor (in same units as b)

It does not matter what units are used for a and b so long as they are the same units. Both quantities may be measured in centimeters, inches, etc. Since it is necessary to have a

table of common logarithms to solve practical problems, the solution is given in graphical form in Fig. 13-8 for a number of common conductor sizes.

In solid-dielectric parallel-conductor lines such as Twin-Lead the characteristic impedance cannot be calculated readily, because part of the electric field is in air as well as in the dielectric.

Unbalance in Parallel-Conductor Lines

When installing parallel-conductor lines care should be taken to avoid introducing electrical unbalance into the system. If for some reason the current in one conductor is higher than in the other, or if the currents in the two wires are not exactly out of phase with each other, the electromagnetic fields will not cancel completely and a considerable amount of power may be radiated by the line.

Maintaining good line balance requires, first of all, a balanced load at its end. For this reason the antenna should be fed, whenever possible, at a point where each conductor "sees" exactly the same thing. Usually this means that the antenna system should be fed at its electrical center. However, even though the antenna appears to be symmetrical, physically, it can be unbalanced electrically if the part connected to one of the line conductors is coupled to something (such as house wiring or a metal pole or roof) that is not duplicated on the other part of the antenna. Every effort should be made to keep the antenna as far as possible from other wiring or sizable metallic objects. The transmission line itself will cause some unbalance if it is not brought away from the antenna at right angles to it for a distance of at least a quarter wavelength.

In installing the line conductors take care to see that they are kept away from metal. The minimum separation between either con-

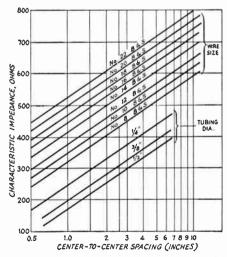


Fig. 13-8—Chart showing the characteristic impedance of spaced-conductor parallel tronsmission lines with air dielectric. Tubing sizes given ore for outside diameters.

ductor and all other wiring should be at least four or five times the conductor spacing. The shunt capacitance introduced by close proximity to metallic objects can drain off enough current (to ground) to unbalance the line currents, resulting in increased radiation. A shunt capacitance of this sort also constitutes a reactive load on the line, causing an impedance "bump" that will prevent making the line actually flat.

COAXIAL LINES

The most common form of coaxial line consists of either a solid or stranded-wire inner conductor surrounded by polyethylene dielectric. Copper braid is woven over the dielectric to form the outer conductor, and a waterproof vinyl covering is placed on top of the braid. This cable is made in a number of different diameters. It is moderately flexible, and so is convenient to install. Some different types are shown in Fig. 13-7. This solid coaxial cable is commonly available in impedances approximating 50 and 70 ohms.

Air-insulated coaxial lines have lower losses than the solid-dielectric type, but are rarely used in amateur work because they are expensive and difficult to install as compared with the flexible cable. The common type of air-insulated coaxial line uses a solid-wire conductor inside a copper tube, with the wire held in the center of the tube by means of insulating "beads" placed at regular intervals.

Characteristic Impedance

The characteristic impedance of an airinsulated coaxial line is given by the formula

$$Z_0 = 138 \log \frac{b}{a} \tag{13-E}$$

where Z_0 = Characteristic impedance

b = Inside diameter of outer conductora = Outside diameter of inner con-

ductor (in same units as b)

The formula for coaxial lines is approximately correct for lines in which bead spacers are used, provided the beads are not too closely spaced. When the line is filled with a solid dielectric, the characteristic impedance as given by the formula should be multiplied by $1/\sqrt{K}$, where K is the dielectric constant of the material.

ELECTRICAL LENGTH

In the discussion of line operation earlier in this chapter it was assumed that currents traveled along the conductors at the speed of light. Actually, the velocity is somewhat less, the reason being that electromagnetic fields travel more slowly in material dielectrics than they do in free space. In air the velocity is practically the same as in empty space, but a practical line always has to be supported in some fashion by solid insulating materials. The result is that the fields are slowed down; the currents travel a shorter distance in the time of one cycle than they do in space, and so the wavelength along the line is less than the wavelength would be in free space at the same frequency.

TABLE 13-I					
Transmission-Line Data					
Туре	Description or Type Number	Charac- teristic Imped- ance	Velocity Factor	Capaci- tance per foot; µµf.	
Coaxial	Air·insulated	50-100	0.851		
	RG-8/U	53	0.66	29.5	
	RG-58/U	53	0.66	28.5	
	RG-11/U	75	0.66	20.5	
	RG-59/U	73	0.66	21.0	
Parallel-	Air-insulated	200-600	0.9752		
Conduc-	214-0808	75	0.68	19.0	
tor	214-0238	75	0.71	20.0	
	214-0798	150	0.77	10.0	
	214-0568	300	0.82	5.8	
	214-076 ⁸	300	0.84	3.9	
	214-0228	300	0.85	3.0	

¹Average figure for small-diameter lines with ceramic beads.

²Average figure for lines insulated with ceramic spacers at intervals of a few feet.

8Amphenol type numbers and data. Line similar to 214-056 is made by several manufacturers, but rated loss may differ from that given in Fig. 13-11. Types 214-023, 214-076, and 214-022 are made for transmitting applications.

Whenever reference is made to a line as being so many wavelengths (such as a "half wavelength" or "quarter wavelength") long, it is to be understood that the electrical length of the line is meant. Its actual physical length as measured by a tape always will be somewhat less. The physical length corresponding to an electrical wavelength is given by

Length in feet =
$$\frac{984V}{f}$$
 (13-F)

where f = Frequency in megacycles V = Velocity factor

The velocity factor is the ratio of the actual velocity along the line to the velocity in free space. Values of V for several common types of lines are given in Table 13-I.

Example: A 75-foot length of 300-ohm Twin-Lead is used to carry power to an antenna at a frequency of 7150 kc. From Table 13-I, V is 0.82. At this frequency (7.15 Mc.) a wave-

Length (feet) =
$$\frac{984V}{f} = \frac{984}{7.15} \times 0.82$$

= 137.6 × 0.82 = 112.8 ft.

The line length is therefore 75/112.8 = 0.665wavelength.

Because a quarter-wavelength line is frequently used as a linear transformer, it is convenient to calculate the length of a quarter-wave line directly. The formula is

Length (feet) =
$$\frac{246V}{f}$$
 (13-G)

where the symbols have the same meaning as above.

Baluns 349

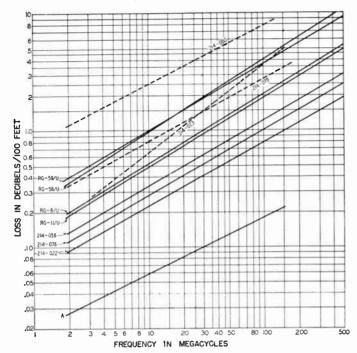


Fig. 13-9 — Attenuation data for common types of transmission lines. Curve A is the nominal attenuation of 600-ohm open-wire line with No. 12 conductors, not including dielectric loss in spacers nor possible radiation losses. Additional line data are given in Table 13-1.

LOSSES IN TRANSMISSION LINES

There are three ways by which power may be lost in a transmission line: by radiation, by heating of the conductors (I^2R loss), and by heating of the dielectric, if any. Radiation losses are in general the result of "antenna currents" on the line, resulting from undesired coupling to the radiating antenna. They cannot readily be estimated or measured, so the following discussion is based only on conductor and dielectric losses.

Heat losses in both the conductor and the dielectric increase with frequency. Conductor losses also are greater the lower the characteristic impedance of the line, because a higher current flows in a low-impedance line for a given power input. The converse is true of dielectric losses because these increase with the voltage, which is greater on high-impedance lines. The dielectric loss in air-insulated lines is negligible (the only loss is in the insulating spacers) and such lines operate at high efficiency when radiation losses are low.

It is convenient to express the loss in a transmission line in decibels per unit length, since the loss in db. is directly proportional to the line length. Losses in various types of lines operated without standing waves (that is, terminated in a resistive load equal to the characteristic impedance of the line) are given in graphical form in Fig. 13-9. In these curves the radiation loss is assumed to be negligible.

When there are standing waves on the line the power loss increases as shown in Fig. 13-10. Whether or not the increase in loss is serious depends on what the original loss would have been if the line were perfectly matched. If the loss with perfect matching is very low, a large s.w.r. will not greatly affect the efficiency of the line—i.e., the ratio of the power delivered to the load to the power put into the line.

Example: A 150-foot length of RG-11/U cable is operating at 7 Mc. with a 5-to-1 s.w.r. If perfectly matched, the loss from Fig. 13-9

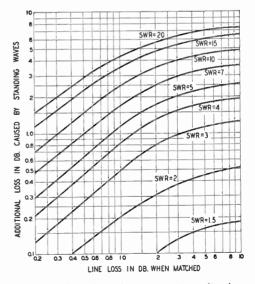


Fig. 13-10—Effect of standing-wave ratio on line loss. The ordinates give the additional loss in decibels for the loss, under perfectly matched conditions, shown on horizontal scale.

would be $1.5 \times 0.4 = 0.6$ db. From Fig. 13-10 the additional loss because of the s.w.r. is 0.73 db. The total loss is therefore 0.6 + 0.73 = 1.33 db.

An appreciable s.w.r. on a solid-dielectric line may result in excessive loss of power at the higher frequencies. Such lines, whether of the parallel-conductor or coaxial type, should be operated as nearly flat as possible, particularly when the line length is more than 50 feet or so.

LOADS AND BALANCING DEVICES

The most important practical load for a transmission line is an antenna which, in most cases, will be "balanced"—that is, symmetrically constructed with respect to the feed point. Aside from considerations of matching the actual impedance of the antenna at the feed point to the characteristic impedance of the line (if such matching is attempted) a balanced antenna should be fed through a balanced transmission line in order to preserve symmetry with respect to ground and thus avoid difficulties with unbalanced currents on the line. Such currents, as pointed out earlier in this chapter, will result in undesirable radiation from the transmission line itself.

If, as is often the case, the antenna is to be fed through coaxial line (which is inherently unbalanced) some method should be used for connecting the line to the antenna without upsetting the symmetry of the antenna itself. This requires a circuit that will isolate the balanced load from the unbalanced line while providing efficient power transfer. Devices for doing this are called baluns. The types used between the antenna and transmission line are generally "linear," consisting of transmission-line sections as described in Chapter 14.

The need for baluns also arises in coupling a transmitter to a balanced transmission line, since the output circuits of most transmitters have one side grounded. (This type of output circuit is desirable for a number of reasons, including TVI reduction.) The most flexible type of balun for this purpose is the inductively coupled matching network described in a subsequent section in this chapter. This combines impedance matching with balanced-tounbalanced operation, but has the disadvantage that it uses resonant circuits and thus can work over only a limited band of frequencies without readjustment. However, if a fixed impedance ratio in the balun can be tolerated, the coil balun described below can be used without adjustment over a frequency range of about 10 to 1 - 3 to 30 Mc., for example. Alternatively, a similarly wide band can be covered by a properly designed transformer (with the same impedance limitation) but the design principles and materials used in such transformers are quite specialized. Their construction is beyond the scope of this Handbook.

Coil Baluns

The type of balun known as the "coil balun" is based on the principles of a linear transmission-line balun as shown in the upper drawing

of Fig. 13-11. Two transmission lines of equal length having a characteristic impedance Z_0 are connected in series at one end and in parallel at the other. At the series-connected end the lines are balanced to ground and will match an impedance equal to $2Z_0$. At the parallel-connected end the lines will be matched by an impedance equal to $Z_0/2$. One side may be connected to ground at the parallel-connected end, provided the two lines have a length such that, considering each line as a single wire, the balanced end is effectively decoupled from the parallel-connected end. This requires a length that is an odd multiple of 1/4 wavelength. The impedance transformation from the series-connected end to the parallel-connected end is 4 to 1.

A definite line length is required only for decoupling purposes, and so long as there is adequate decoupling the system will act as a 4-to-1 impedance transformer regardless of line length. If each line is wound into a coil, as in the lower drawing, the inductances so formed will act as choke coils and will tend to isolate the series-connected end from any ground connection that may be placed on the parallel-connected end. Balun coils made in this way will operate over a wide frequency range, since the choke inductance is not critical. The lower frequency limit is where the coils are no longer effective in isolating one end from the other; the length of line in each coil should be about equal to a quarter wavelength at the lowest frequency to be used.

The principal application of such coils is in going from a 300-ohm balanced line to a 75-ohm coaxial line. This requires that the Z_0 of the lines forming the coils be 150 ohms. Design data for winding the coils is not available; however, Equation 13-D can be used for determining the approximate wire spacing.

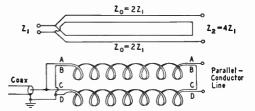


Fig. 13-11—Baluns for matching between push-pull and single-ended circuits. The impedance ratio is 4 to 1 from the push-pull side to the unbalanced side. Coiling the lines as shown in the lower drawing increases the frequency range over which satisfactory operation is obtained.

Impedance Matching

Allowance should be made for the fact that the effective dielectric constant will be somewhat greater than 1 if the coil is wound on a form. The proximity effect between turns can be reduced by making the turn spacing somewhat larger than the conductor spacing. For operation at 3.5 Mc. and higher frequencies the length of each conductor should be about 60 feet. The conductor spacing can be adjusted to the proper value by terminating each line in a noninductive 150-ohm resistor and adjusting the spacing until an impedance bridge at the input end shows the line to be matched to 150 ohms.

A balun of this type is simply a fixed-ratio transformer, when matched. It cannot compensate for inaccurate matching elsewhere in the system. With a "300-ohm" line on the balanced end, for example, a 75-ohm coax cable will not be matched unless the 300-ohm line actually is terminated in a 300-ohm load.

NONRADIATING LOADS

Typical examples of nonradiating loads for a transmission line are the grid circuit of a power amplifier (considered in the chapter on transmitters), the input circuit of a receiver, and another transmission line. This last case includes the "antenna tuner"—a misnomer because it is actually a device for coupling a transmission line to the transmitter. Because of its importance in amateur installations, the antenna coupler is considered separately in a later part of this chapter.

Coupling to a Receiver

A good match between an antenna and its transmission line does not guarantee a low standing-wave ratio on the line when the antenna system is used for receiving. The s.w.r. is determined wholly by what the line "sees" at the receiver's antenna-input terminals. For minimum s.w.r. the receiver input circuit must be matched to the line. The rated input impedance of a receiver is a nominal value that varies over a considerable range with frequency. Methods for bringing about a proper match are discussed in the chapter on receivers.

The most desirable condition is that in which the receiver is matched to the line Z_0 and the line in turn is matched to the antenna. This transfers maximum power from the antenna to the receiver with the least loss in the transmission line.

COUPLING THE TRANSMITTER TO THE LINE

The type of coupling system that will be needed to transfer power adequately from the final r.f. amplifier to the transmission line depends almost entirely on the input impedance of the line. As shown earlier in this chapter, the input impedance is determined by the standing-wave ratio and the line length. The simplest case is that where the line is terminated in its characteristic impedance so that the s.w.r. is 1 to 1 and the input impedance is equal to the Z_0 of the line, regardless of line length.

Coupling systems that will deliver power into a flat line are readily designed. For all practical purposes the line can be considered to be flat if the s.w.r. is no greater than about 1.5 to 1. That is, a coupling system designed to work into a pure resistance equal to the line Z_0 will have enough leeway to take care of the small variations in input impedance that will occur when the line length is changed, if the s.w.r. is higher than 1 to 1 but no greater than 1.5 to 1.

Current practice in transmitter design is to provide an output circuit that will work into such a line, usually a coaxial line of 50 to 75 ohms characteristic impedance. The design of such output circuits is discussed in the chapter on high-frequency transmitters. If the input impedance of the transmission line that is to be connected to the transmitter differs appreciably from the value of impedance into which the transmitter output circuit is designed to operate, an impedance-matching network must be inserted between

the transmitter and the line input terminals.

IMPEDANCE-MATCHING CIRCUITS FOR PARALLEL CONDUCTOR LINES

As shown earlier in this chapter, the input impedance of a line that is operating with a high standing-wave ratio can vary over quite wide limits. The simplest type of circuit that will match such a range of impedances to 50 to 75 ohms is a parallel-tuned circuit approximately resonant at the operating frequency. In its ordinary form, such a circuit will be connected to a short length of coaxial line or

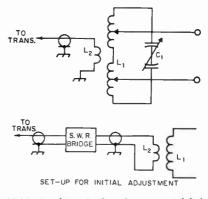


Fig. 13-12—Matching circuits using a coaxial link, for use with parallel-conductor transmission lines. Adjustment setup using an s.w.r. bridge is shown in the lower drawing. Design considerations and method of adjustment are discussed in the text.

"link" by inductive coupling as shown in Fig. 13-12, the other end of the cable being attached to the output terminals of the transmitter. The cable may be any convenient length if the impedance that it "sees" at the matching circuit is equal to its own characteristic impedance. This method has the further advantage that the coaxial link offers an ideal spot for the insertion of a low-pass filter for preventing harmonic interference to television and f.m. reception.

The constants of the tuned circuit C_1L_1 are not particularly critical; the principal requirement is that the circuit must be capable of being tuned to the operating frequency. Constants similar to those used in the plate tank circuit will be satisfactory. The construction of L_1 must be such that it can be tapped at least every turn. L_2 must be tightly coupled to L_1 , and the inductance of L_2 should be approximately the value that gives a reactance equal to the Z_0 of the connecting line at the frequency in use. An average reactance of about 60 ohms will suffice for either 52- or 75-ohm coaxial line.

The most satisfactory way to set up the system initially is to connect a coaxial s.w.r. bridge in the link as shown in Fig. 13-12. The "Monimatch" type of bridge, which can handle the full transmitter power and may be left in the line for continuous monitoring, is excellent for this purpose. However, a simple resistance bridge such as is described in the chapter on measurements is perfectly adequate, requiring only that the transmitter output be reduced to a very low value so that the bridge will not be overloaded. To adjust the circuit, take a trial position of the line taps on L_1 , keeping them equidistant from the center of the coil, and adjust C_1 for minimum s.w.r. as indicated by the bridge. If the s.w.r. is not close to 1 to 1, try new tap positions and adjust C1 again, continuing this procedure until the s.w.r. is practically 1 to 1. The setting of C_1 and the tap positions may then be logged for future reference. At this point, check the link s.w.r. over the frequency range normally used in that band, without changing the setting of C1. No readjustment will be required if the s.w.r. does not exceed 1.5 to 1 over the range, but if it goes higher it is advisable to note as many settings of C_1 as may be necessary to keep the s.w.r. below 1.5 to 1 at any part of the band. Changes in the link s.w.r. are caused chiefly by changes in the s.w.r. on the main transmission line with frequency, and relatively little by the coupling circuit itself. A single setting of C₁ at mid-frequency will suffice if the antenna itself is broadtuning.

If it is impossible to get a 1-to-1 s.w.r. at any settings of the taps or C_1 the s.w.r. on the main transmission line is high and the line length is probably unfavorable. Ordinarily there should be no difficulty if the transmission-line s.w.r. is not more than about 3 to 1,

but if the line s.w.r. is higher it may not be possible to bring the link s.w.r. down except by using the methods for reactance compensation described in a subsequent section of this chapter.

The matching adjustment can be considerably facilitated by using a variable capacitor in series with the matching-circuit coupling coil as shown in Fig. 13-13. The additional adjustment thus provided makes the tap settings on L_1 much less critical since varying C_2

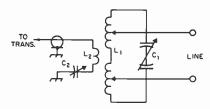


Fig. 13-13—Using a series capacitor for control of coupling between the link and line circuits with the coax-coupled matching circuit.

has the effect of varying the coupling between the two circuits. For optimum control of coupling, L2 should be somewhat larger than when C2 is not used - perhaps twice the reactance recommended above - and the reactance of C2 at maximum capacitance should be the same as that of L_2 at the operating frequency. L_1 and C_1 are the same as before. The method of adjustment is the same, except that for each trial tap position C_1 and C_2 are alternately adjusted, a little at a time, until the s.w.r. is brought to its lowest possible value. In general, the adjustment sought should be the one that keeps C2 at the largest possible capacitance, since this broadens the frequency response. Also, the taps on L_1 should be kept as far apart as possible, while still permitting a match, since this also broadens the frequency response of the circuit.

Once the matching circuit is properly adjusted, the s.w.r. bridge may be removed, if necessary, and full power applied to the transmitter. The power input should be adjusted by the coupling or loading control built into the transmitter, not by making any changes in the matching-circuit adjustments. If an amplifier having a parallel-tuned tank circuit will not load properly, tuned coupling should be used into the coax link.

It is possible to use a circuit of this type without initially setting it up with the s.w.r. bridge. In such a case it is a matter of cut-and-try until adequate power transfer between the amplifier and main transmission line is secured. However, this method frequently results in a high s.w.r. in the link, with consequent power loss, "hot spots" in the coaxial cable, and tuning that is critical with frequency. The bridge method is simple and gives the optimum operating conditions quickly and with certainty.

Impedance Matching

Untuned Coupling

A simple coil can be used for coupling to a line having a high standing-wave ratio providing the line length is adjusted so there is a current loop near the point where it connects to the pick-up coil. The coupling will be maximum, for a given degree of separation between the pick-up coil and the amplifier tank coil, if the line is pruned to a length such that the input impedance is just sufficiently capacitive to cancel the inductive reactance of the pick-up coil. This can be done by cut-andtry. The higher the s.w.r. on the line the easier it becomes to load the amplifier with loose coupling between the two coils. The sharper the antenna and the higher the line s.w.r. the more difficult it becomes to operate with this system over a band without progressively changing the line length.

Series and Parallel Tuning

Lines classified as "tuned" or "resonant"—
i.e., cut to lengths approximately equal to
integral multiples of one-quarter wavelength,
and operating with a high standing-wave ratio
— are characterized by having either very high
or very low input impedances. Also, the input
impedances of such lines are essentially
resistive.

Under these conditions the circuit arrangements shown in Fig. 13-14 will work satisfactorily. Their advantage over the circuit of Fig. 13-12 is that it is not necessary to provide for taps on the matching-circuit coil, L_1 . "Series" tuning is used when a current loop occurs at or near the input end of the line; i.e., when the input impedance is low. "Parallel" tuning is used when there is a voltage loop at or near the input end; i.e., when the input end; i.e., when the input impedance is high.

In the series case, the circuit formed by L_1 , C_1 and C_2 with the line terminals short-circuited should tune to the operating frequency. C_1 and C_2 should be maintained at equal capacitance. In the parallel case, the circuit formed by L_1 and C_1 should tune to resonance with the line disconnected.

The L/C ratio in either circuit depends on the transmission line Zo and the standingwave ratio. With series tuning, a high L/Cratio must be used if the s.w.r. is relatively low and the line Zo is high. With parallel tuning, a low L/C ratio must be used if the s.w.r. is relatively low and the transmission-line Z_0 also is low. With either series or parallel tuning the L/C ratio becomes less critical when the s.w.r. is high. As a first approximation, coil and capacitor values of the same order as those used in the plate tank circuit may be tried. The coupling coil, L2, should have a reactance about equal to the Zo of the coaxial line, just as in the case of the circuit of Fig. 13-14. The coupling between L_1 and L_2 should be continuously adjustable.

A balanced capacitor is used in the parallel

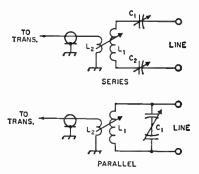


Fig. 13-14—Link-coupled series and parallel tuning.

circuit, in preference to a single unit. An alternative scheme to maintain balance is to use two single-ended capacitors in parallel, but with the frame of one connected to one side of the line and the frame of the other connected to the other side of the line. The same two capacitors may be switched in series when series tuning is to be used.

As an alternative to adjustable coupling between L_1 and L_2 , fixed coupling may be used and a variable capacitor connected in series with L_2 as shown in Fig. 13-13.

These circuits should be set up and adjusted in the same way as the tapped matching circuit, Fig. 13-12. That is, an s.w.r. bridge should be used to indicate the impedance match, which is brought about by alternately adjusting C_1 and the coupling between L_1 and L_2 until the bridge shows a null.

In the event that there is difficulty in bringing the s.w.r. down to 1 to 1 in the coaxial link, the probable cause is that the input impedance of the transmission line is neither very high nor very low. In such a case, if series tuning does not work it may pay to try parallel tuning, and vice versa. If a match cannot be secured with either, the circuit should be changed to that of Fig. 13-14.

Adjustment Without the S.W.R. Bridge

Use of the s.w.r. bridge with the circuits described above is the only certain way of arriving at optimum adjustments. However, if a bridge is not available, the transmitter usually can be made to take the proper load by a cut-and-try method of adjustment. In the case of Fig. 13-12, take a trial position of the taps fairly close to the center of L₁. With loose coupling between L1 and L2 (this may be controlled either by adjustment of the ·mutual inductance or by means of the series capacitor C2) and with the amplifier plate tank circuit tuned to resonance as indicated by the plate-current dip, vary C1 until a setting is found that causes the plate current to rise to a peak. This peak should be less than the expected normal loaded plate current. Then increase the coupling between L_1 and L_2 , readjust C_1 for maximum plate current, and readjust the amplifier tank for the platecurrent dip. Continue until the amplifier is fully loaded at the plate-current dip, increasing the coupling between the transmitter tank and the coax line if necessary to obtain full loading. Then spread the taps on L_1 a little farther apart and go through the same procedure. The object is to use the widest spread between taps that will permit proper loading of the transmitter.

The procedure with series or parallel tuning is similar except that there are no taps to adjust. If full loading cannot be secured with either, the circuit should be changed to Fig. 13-12.

Although this cut-and-try method generally will lead to adequate transmitter loading, the adjustments seldom are optimum from the standpoint of low s.w.r. in the coax link. This may lead to excessive power dissipation in the link, with overheating the result. Also, the loading may change more rapidly with small frequency changes than would be the case with a matching circuit adjusted for optimum performance with the aid of the s.w.r. bridge.

Lines of Random Length

Series or parallel tuning will always work satisfactorily with lines having a high standing-wave ratio so long as either a current loop or node occurs at the input end of the transmission line. This will be the case if the antenna is resonant and the line length is a multiple of one-quarter wavelength. However, it is not always possible to couple satisfactorily when intermediate line lengths are used. This is because at some lengths the input impedance of the line has a considerable reactive component, and because the resistive component is too large to be connected in series with a tuned circuit and too small to be connected in parallel.

The coupling system shown in Fig. 13-12 is capable of handling the resistive component of the input impedance of the transmission lines used in most amateur installations, regardless of the standing-wave ratio on the line. Consequently, it can generally be used wherever either series or parallel tuning would normally be called for, simply by setting the taps properly on the coil. (A possible exception is where the s.w.r. is considerably higher than 10 to 1 and the line length is such as to bring a current loop at the input end. In such a case the resistance may be only a few ohms, which is difficult to match by means of taps on a coil.)

Within limits, the same circuit is capable of being adjusted to compensate for the reactive component of the input impedance; this merely means that a 1-to-1 s.w.r. in the link will be obtained at a different setting of C_1 than would be the case if the line "looked like" a pure resistance. Sometimes, however, C_1 does not have enough range available to give complete compensation, particularly when (as is

the case with some line lengths when the s.w.r. is high) the input impedance is principally reactive.

Under such conditions it is necessary, if the line length cannot be changed to a more satisfactory value, to provide additional means for compensating for or "canceling out" the reactive component of the input impedance. As described earlier in this chapter, the input impedance can be considered to be equivalent to a circuit consisting either of resistance and inductance or resistance and capacitance. It is generally more convenient to consider these elements as a parallel combination. If the line appears inductive, a suitable capacitance in parallel will resonate the circuit. The resistive impedance that remains can easily be matched to the coax link by means of the circuit of Fig. 13-12.

The practical application of this principle is shown in Fig. 13-15, where L and C are the

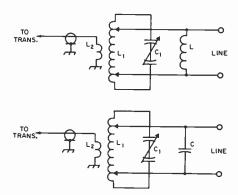


Fig. 13-15—Reactance cancellation on random-length lines having a high standing-wave ratio.

reactances required to cancel out the line reactance, L for cases where the line is capacitive, C for lines having inductive reactance. The amount of either inductance or capacitance required is easily determined by trial, using the s.w.r. bridge in the coax link. First disconnect the main transmission line from L1 and connect a noninductive resistor in its place. A 1-watt carbon resistor of about the same resistance as the line Z_0 will do, if a low-power bridge of the resistance type is used. With the "Monimatch" bridge, a suitable load may be made by connecting carbon resistors in parallel; for example, five 1500ohm 2-watt resistors in parallel will make a 300-ohm load capable of handling 10 watts of r.f. Adjust the coil taps and C_1 for a 1-to-1 standing-wave ratio in the link, as described earlier. This determines the proper setting of C_1 for a purely resistive load. Then take off the resistor and connect the line, again adjusting the taps and C_1 to make the s.w.r. as low as possible, and compare the new setting of C_1 with the original setting. If the capacitance has increased, the line reactance is inductive

Matching To Coaxial Lines

and a capacitor must be connected at C in Fig. 13-15. The amount of capacitance needed to bring the proper setting of C_1 near the original setting can be determined by trial. On the other hand, if the capacitance of C_1 is less than the original, an inductance must be connected at L. Trial values will show when the proper tuning conditions have been reached.

It is not necessary that C_1 be at exactly the original setting after the compensating reactance has been adjusted; it is sufficient that it be in the same vicinity.

Using this procedure practically any length of line can be coupled properly to the transmitter, even when the line s.w.r. is quite high. Unfortunately, no specific values can be suggested for L and C, since they vary widely with Z_0 , line length and s.w.r. Their values usually are comparable with the values used in the regular coupling circuits at the same frequency.

MATCHING TO COAXIAL LINES

Coaxial transmission lines usually are (or at least should be) operated at a low-enough standing-wave ratio so that no special matching circuits are needed; the line simply may be connected to the transmitter output terminals. A properly designed transmitter output circuit (see chapter on high-frequency transmitters) will be capable of handling variations in s.w.r. that are acceptable from the standpoint of line losses.

However, there are cases where it becomes necessary to provide some frequency selectivity between the transmitter and antenna system in order to prevent undesirable radiation of harmonics. A matching circuit of the same general type as those discussed above can provide a considerable degree of selectivity in addition to matching the input impedance of the transmission line to the Z_0 of the coaxial link. The difference in the circuit arrangement is simply that the secondary or output side need not be balanced with respect to ground.

Fig. 13-16 shows a typical circuit. Except for the fact that there is only one coil tap, the design considerations and adjustment procedure are the same as described for Fig. 13-12. Also, the series capacitor, C_2 , shown in Fig. 13-13 may be used with this circuit for fine variation of the effective coupling between

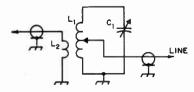


Fig. 13-16—Inductively coupled matching circuit for coupling between coaxial lines. The principles are the same as in Fig. 13-12; the secondary circuit is simply made single-ended for use with a coaxial transmission line.

 L_1 and L_2 . Constants for the circuit L_1C_1 are not critical; any convenient values that will tune to the operating frequency may be used. The Q of this circuit, and hence the selectivity, is controlled principally by the position of the line tap. As the tap is moved farther up the coil the Q and selectivity decrease.

The practical matching circuits described in the following section may be used with coaxial line simply by connecting the outer conductor of the line to the center of the coil and tapping the inner conductor along one side. The balanced circuit may still be used, although if the coupler is to be used only with coaxial line the circuit may be made single-ended as shown in Fig. 13-16.

"Half-wave" Filters for Harmonic Suppression

If impedance matching is not a consideration—i.e., the transmission line to the antenna is operating at a low s.w.r.—but harmonic suppression is desirable, the circuit of Fig. 13-17 may be used as an alternative to Fig. 13-16. This is a "half-wave" filter circuit, so called because it has similar properties to a half-wave transmission line. When inserted in a line, the impedance at the input terminals of the filter is the same impedance that the filter "sees" at its output terminals. Thus if the line input impedance is a pure resistance of 50 ohms, the impedance at the filter input terminals also will be 50 ohms.

Just as in the half-wave line case, the characteristic impedance of the filter can be any value without altering its performance with respect to input and output impedance. However, it is desirable in the interests of broad-band operation

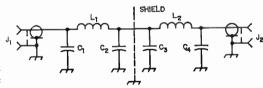


Fig. 13-17—Half-wave filter for harmonic suppression. The two sections of the filter should be shielded from each other as indicated by the dashed line, and the whole filter should be constructed in a shield enclosure to insure effective operation. A separate filter is required for each amateur band. All capacitors have the same value, as do all inductors, for a given band. Suggested constants are as follows:

2.2 <i>μ</i> h.
1.3 µh.
0.57 <i>μ</i> h.
0.375 <i>µ</i> h.
0.3 <i>μ</i> h.

Design is based on standard values of fixed mica capacitors. Larger capacitances may be made up by using smaller-capacitance units in parallel, if necessary. See text for voltage ratings. Inductances may be adjusted to proper value by resonating to center of band with the capacitance value given in the above table.

to make the filter characteristic impedance approximately the same as the Z_0 of the line. The constants given in Fig. 13-17 will serve for either 50- or 75-ohm line. The filter can be used without adjustment at any frequency within the amateur band for which it is designed.

The capacitance values required are fairly large, but under the assumed conditions (low s.w.r. on the line, filter Z_0 approximately equal to line Z_0) the voltages across the capacitors are low. Mica capacitors having a voltage rating suitable for the power level are satisfactory. The peak rating required is equal to $\sqrt{2PZ_0}$.

where P is the r.f. power and Z_0 is the characteristic impedance of the line. This value should be doubled for 100 per cent amplitude modulation, and it is advisable to allow a safety factor in addition. A rating of 1500 volts d.c. will be sufficient for a kilowatt a.m. transmitter if the line is well matched by the antenna.

The attenuation of a filter of this type is about 30 db. at the second harmonic and greater at higher harmonics, until limited by self-resonances at high frequencies that occur in the inductors. These usually are not important at harmonics below the fourth.

COUPLER OR MATCHING-CIRCUIT CONSTRUCTION

The design of matching or "antenna coupler" circuits has been covered in the preceding section, and the adjustment procedure also has been outlined. When circuits of this type are used for transferring power from the transmitter to a parallel-conductor transmission line, a principal point requiring attention is that of maintaining good balance to ground. If the coupler circuit is appreciably unbalanced the currents in the two wires of the transmission line will also be unbalanced, resulting in radiation from the line.

In most cases the matching circuit will be built on a metal chassis, following common practice in the construction of transmitting units. The chassis, because of its relatively large area, will tend to establish a "ground"— even though not actually grounded — particularly if it is assembled with other units of the transmitter in a rack or cabinet. The components used in the coupler, therefore, should be placed so that they are electrically symmetrical with respect to the chassis and to each other if a parallel-conductor transmission line is to be used.

Fig. 13-18—Circuit diagram of an antenna coupler for "random" antennas. All contacts of S_2 are not shown.

C₁, C₂—150 μμf. See text for spacing.
 J₁, J₂—Coaxial receptacles (SO-239).
 L₁—20 turns No. 12 bare, 2½ inch diam., 6 t.p.i. (B&W 3905-1). Tapped every other turn.
 S₁—Three-pole 5-position ceramic rotary switch.

 S_1 —Three-pole 3-position ceramic rotary switch. S_2 —Single-pole 11-position ceramic rotary switch.

In general, the construction of a coupler circuit for parallel lines should physically resemble the tank layouts used with push-pull amplifiers. In parallel-tuned circuits a split-stator capacitor should be used. The capacitor frame should be insulated from the chassis because, depending on line length and other factors, harmonic reduction and line balance may be improved in some cases by grounding and in others by not grounding. It is therefore advisable to adopt construction that permits either. Provision also should be made for grounding the center of the coil, for the same reason. The coil in a parallel-tuned circuit should be mounted so that its hot ends are symmetrically placed with respect to the chassis and other components. This equalizes stray capacitances and helps maintain good balance.

When the coupler is of the type that can be shifted to series or parallel tuning as required, two separate single-ended capacitors will be satisfactory. As described earlier, they should be connected so that both frames go to corresponding parts of the circuit — i.e., either to the coil or to the line — for series tuning, and when used in parallel for parallel tuning should be connected frame-to-stator.

A coupler designed and adjusted so that the connecting link acts as a matched transmission line may be placed in any convenient location. Some amateurs prefer to install the coupler at the point where the main transmission line enters the station. This helps maintain a tidy station layout when an air-insulated parallel-conductor transmission line is used. With solid-dielectric lines, which lend themselves well to neat installation indoors, it is probably more desirable to install the coupler where it can be reached easily for adjustment and band-changing.

MATCHING TO "RANDOM" ANTENNAS

In many cases it is impractical or impossible to install a conventional antenna complete with transmission line. Under these conditions, the only solution may be to string a wire to an existing support or between two supports and run one end to the transmitter. Such a "random" antenna will not couple conveniently to the low-impedance output of most transmitters unless its length

Coupler Construction

happens to be an odd multiple of a quarter wavelength. In cases where a random antenna must be used, the antenna-coupler circuit of Fig. 13-18 provides a simple solution. Although specific values are given for C_1 , C_2 and L_1 , they are not critical. C_1 and C_2 should be at least 150 $\mu\mu f$. The spacing of C_1 and C_2 should be 0.025 inch for transmitter inputs of 100 watts or less. L_1 may be a convenient length of any of the twoto three-inch diameter air inductors, or it can be a homemade coil on a ceramic form. It should be tapped every two or three turns. The tuner may be built in an open "breadboard" style, or it can be enclosed in a metal cabinet or chassis. If it is built breadboard, it may be more convenient to use a small clip instead of S_2 to vary the inductance of L_1 . An elaborate version can be made with a built-in Monimatch and output indicator.

The several configurations that can be obtained from the coupler are shown in Fig. 13-20. The letters correspond to those on the switch S_1 .

When first using this tuner with an antenna, try various positions of C_1 , C_2 , S_1 and S_2 in order to find the point at which maximum output is obtained (maintaining a constant transmitter input). When the correct settings have been found for each frequency band, and these settings have been noted for future reference, it is an easy matter to hop from band to band. With certain settings and configurations it will be possible to dissipate a large part of the transmitter output in the tuner itself, and for this reason an output indicator is highly desirable, at least for the initial tune-up. Either an r.f. ammeter in the output lead or an r.f. voltmeter from it to chassis will be satisfactory. Under some conditions a neon bulb will serve as an r.f. voltmeter.

If TVI is a problem, the low-pass filter should be installed in the line between coupler and transmitter.

A WIDE-RANGE COUPLER FOR ANY ANTENNA

The coupler shown in Figs. 13-21, 13-23 and 13-24 will match a transmitter's 50- or 70-ohm

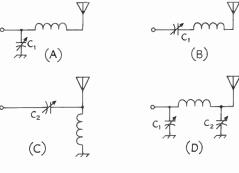


Fig. 13-19—The variaus configurations that can be obtained from the "randam-wire" antenna caupler.

(E)

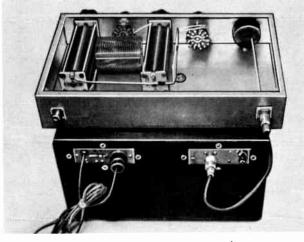


Fig. 13-20—An example of how the antenna caupler can be built. In this case the companents are installed in a 10 × 17 × 3-inch aluminum chassis that serves as the support for the transmitter. An r.f. ammeter (right) is used as an output indicator. (W4UWA/DL4, QST, Navember, 1958).

output to antenna loads as low as 10 ohms and as high as 4000, balanced or unbalanced. In principle it resembles the couplers of Figs. 13-13 and 13-16, but instead of using a tapped coil (and its necessary complexity) for load changes it uses a capacitive voltage divider. Referring to Fig. 13-22, the capacitors C_2 , C_3 and C_4 , connected in series across the inductance L_1 form the divider.

To simplify construction and duplication, a single length of coil stock is used for the inductance. The link, L_2L_3 , is actually two coils. For 80 and 40 meters, the two coils are connected in series to provide an 8-turn link. On 20, 15 and 10 the coils are connected in parallel, resulting in the equivalent of a two-turn link. Using the two coils in this fashion provides tighter coupling to L_1 than would be obtained if a single link were tapped, and it maintains symmetry with respect to the large coil.

A Monimatch is included as a tuning indicator. Some form of indicator is required to show when the unit is correctly adjusted. If a Monimatch or similar indicator is already available, this part of Fig. 13-22 can be eliminated.

As designed and shown, this unit will handle about 500 watts on c.w. or s.s.b. and about half that power on a.m. phone. For amateurs using less power (in the 50- to 100-watt level), the capacitor spacings can be reduced at a saving in cost, and suitable capacitors are specified in Fig. 13-22. The coil remains the same for either power level—there isn't enough difference in coil cost to warrant using a different coil unless space is at a premium.

If substitutions for the specified capacitors are contemplated, no harm will be done if higher-capacitance units are substituted. However, if lower capacitance values are used they will limit the range over which a match can be obtained.

The complete coupler, including the Monimatch, is built on a $3\times10\times14$ -inch aluminum chassis. The front panel is made from a 10×10 -inch piece of aluminum sheet stock. The link

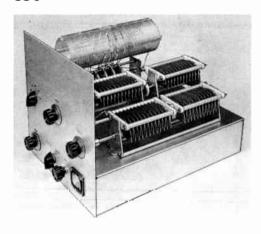


Fig. 13-21—This wide-range antenna coupler can be used with parallel-line or coaxial transmission lines, as well as with a wire af randam length. The capacitors at the center of the chassis are insulated from the chassis and from each other; the near capacitor is o normal split-statar copacitar and is mounted an the chassis. The coil of the far side is supported by its leads above the band switch.

Controls along the bottom, fram left to right, ore the link capacitor, the Monimatch farward-reflected switch and the Monimatch sensitivity control. capacitor, C_1 , is mounted under the chassis, as is the Monimatch. The loading capacitor, C_3 , is mounted directly on the chassis top along the right-hand side; the ganged capacitors, C2 and C_4 are supported off the chassis by one-inch ceramic stand-off insulators and their shafts are connected together and to the panel shaft by suitable insulated shaft couplings. The two output leads that go to J_3 and J_5 are taken off the rotor mounting points between the two capacitors. These leads run down below chassis to the connectors through two rubber grommets. If suitable feed-through insulators are available they can be used to mount C_2 and C_4 and the under-chassis leads taken from them.

Fig. 13-24 shows how to make L_1 , L_2 and L_3 . Cut a total of 66 turns from a length of coil stock, making sure to leave enough lead length at each end of the coil for connections to the switch. At 281/2 turns from each end of the coil cut the wire and unwind 1/2 turn from the support bars. This will give two coils of 28 turns and another of 9 turns. Cut the 9-turn coil at the center and unwind the half turns, leaving two coils of 4 turns each. The two 28-turn coils are connected together at the center by soldering the two inside leads together.

The coil assembly is supported by its own leads, and it is mounted over S_2 . The switch is made from a Centralab P-122 index and four single-pole five-position rotary ceramic switch sections (Centralab T or X). Two switch mounting brackets of sheet aluminum are used to support the switch assembly.

The Monimatch is mounted in a $2\frac{1}{4} \times 2\frac{1}{4} \times$

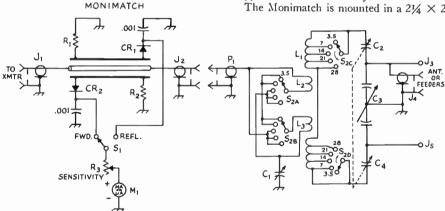


Fig. 13-22—Circuit diagram of the antenna coupler and Monimatch.

C₁-250-\mu f. variable, 0.045-inch spacing for high pawer (Johnson 250E20); 0.025-inch spocing far low power (Hammarlund MC-250-M).

C₂, C₄-100-µµf. variable, 0.125-inch spacing for high power (Johnson 100E45); 0.025-inch spacing for low power (Hommarlund MC-100-M).

 C_3 —100- $\mu\mu$ f.-per-section, dual voriable, 0.125-inch spacing for high power (Johnson 100ED45); 0.025-inch spacing for low power (Hammarlund MCD-100-M).

CR1, CR2-1N34A germanium diodes.

J1, J2, J4-Chassis-type coax receptacles, type SO-239.

J₃, J₅-Feedthraugh insulators.

L1, L2, L3-See Fig. 13-24 and text.

M₁-0-1 ma. or less; see text.

P₁—Coax plug, type PL-259.

 R_1 , R_2 —Far 50-ohm bridge, 100 ahms, $\frac{1}{2}$ -watt composition; for 70-ohm bridge, 150 ohms, 1/2watt composition.

R₃-20,000-ohm control, linear taper.

S₁-Rotory, 1 pole, 2 positions (Centralab type 1460). S2-Ceramic rotary, 4 poles, 5 positions, 1 pole per

> section, 4 sections (Centralob index type P-122 with type "T" or "X" sections).

Coupler Construction

5-inch aluminum box (Bud Minibox CU-3004A). Chassis-type coax fittings (SO-239) are mounted in the center of each end of the box. A piece of ¼-inch o.d. copper tubing, 45% inches long, is connected between the two inner pins of the coax fittings. The two pick-up leads for the bridge are made from No. 14 solid wire held in the proper position by two insulating spacers. Details of the spacers are shown in Fig. 13-25. The spacers can be made from ½- to ¼-inch thick polystyrene or bakelite.

Two flat strips of copper, 5% inch wide by 47% inches long, are installed as shown in Fig. 13-23. The method of mounting the strips is quite simple. Solder a lug to each end of each strip, allowing the end of the lug with the screw hole to project beyond the edge. Bend this part of the lug up at right angles to the strip. The strips are then mounted by using the top and bottom screws and nuts of the coax fittings.

When soldering the germanium diodes to the pickup wires, hold the lead of the diode with a pair of pliers between the point of soldering and the body of the diode. This will keep excess heat from reaching the diodes and ruining them.

For a 50-ohm bridge R_1 and R_2 should be 150-ohm, $\frac{1}{2}$ -watt resistors. For 70-ohm bridge use 100 ohms, $\frac{1}{2}$ watt. The resistors used should be composition or carbon, not wire-wound.

The leads to S_1 are brought out of the Monimatch box through two feedthrough insulators and run from there to the switch in shielded wire. M_1 as shown is a 500- μ a. meter, but a 0-1 milliammeter can be used.

Adjustment Procedure

The coupler can be used with practically any antenna system. With a balanced line (open-wire or Twin-Lead), the conductors should be connected to terminals J_3 and J_5 . A coax line from the antenna should be connected to J_4 . For singlewire feed, such as a wire fed at the end, the wire

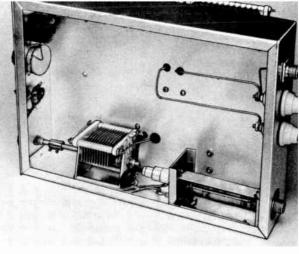


Fig. 13-23—The link capacitor and the Monimatch are mounted underneath the chassis.

should be connected to J_3 and the coupler chassis grounded to an earth ground.

Connect a length of coax between the transmitter and the coupler, using either 50- or 70ohm coax, depending on which value the Monimatch was built to handle. Feed some power through the system and set S_1 to read forward power. Adjust R₃ for a full-scale meter deflection. Next, set S1 to read reflected power and tune C_1 and C_2C_4 for minimum reading. If it is impossible to get the reading down to zero (the object of the adjustment), try a different setting of C₃ and again adjust the other two controls. Once the zero reading is obtained, the coupler is correctly adjusted for that particular frequency. Make a note of the settings and proceed to the next band. If an accurate record is kept it will be simple to change bands quickly.

If an antenna system is encountered that cannot be matched, although this is unlikely, the simplest thing to do is to increase or decrease the length of the feed line. A little experimentation will quickly set up a "matched" condition.

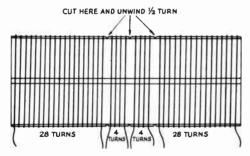


Fig. 13-24—Details of the coil assembly. Not shown are the taps needed for changing bands. The tap points listed below all are counted from the outside ends of the coil.

7 Mc.—12 turns.
14 Mc.—23 turns.
14 Mc.—23 turns.
The coil stock in 3 inches in diam., No. 14, 8 turns per inch (Illumitronic, Air Dux 2408T).

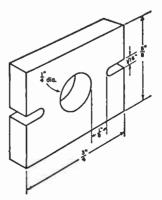


Fig. 13-25—Dimensions of the insulating spacers used to hold the pick-up wires in place in the Monimatch.

Antennas

An antenna system can be considered to include the antenna proper (the portion that radiates the r.f. energy), the feed line, and any coupling devices used for transferring power from the transmitter to the line and from the line to the antenna. Some simple systems may omit the transmission line or one or both of the coupling devices. This chapter will describe the antenna proper, and in many cases will show popular types of lines, as well as line-to-antenna couplings where they are required. However, it should be kept in mind that any antenna proper can be used with any type of feedline if a suitable coupling is used between the antenna and the line. Changing the line does not change the type of antenna.

Selecting an Antenna

In selecting the type of antenna to use, the majority of amateurs are somewhat limited through space and structural limitations to simple antenna systems, except for v.h.f. operation where the small space requirements make the use of multielement beams readily possible. This chapter will consider antennas for frequencies as high as 30 Mc.-a later chapter will describe the popular types of v.h.f. antennas. However, even though the available space may be limited, it is well to consider the propagation characteristics of the frequency band or bands to be used, to insure that best possible use is made of the available facilities. The propagation characteristics of the amateur-band frequencies are described in Chapter Fifteen. In general, antenna construction and location become more critical and important on the higher frequencies. On the lower frequencies (3.5 and 7 Mc.) the vertical angle of radiation and the plane of polarization may be of relatively little importance; at 28 Mc. they may be all-important.

Definitions

The polarization of a straight-wire antenna is determined by its position with respect to the earth. Thus a vertical antenna radiates vertically polarized waves, while a horizontal antenna radiates horizontally polarized waves in a direction broadside to the wire and vertically polarized waves at high vertical angles off the ends of the wire. The wave from an antenna in a slanting position, or from the horizontal antenna in directions other than mentioned above, contains components of both horizontal and vertical polarization.

The vertical angle of maximum radiation of an antenna is determined by the free-space

pattern of the antenna, its height above ground, and the nature of the ground. The angle is measured in a vertical plane with respect to a tangent to the earth at that point, and it will usually vary with the horizontal angle, except in the case of a simple vertical antenna. The horizontal angle of maximum radiation of an antenna is determined by the free-space pattern of the antenna.

The impedance of the antenna at any point is the ratio of the voltage to the current at that point. It is important in connection with feeding power to the antenna, since it constitutes the load to the line offered by the antenna. It can be either resistive or complex, depending upon whether or not the antenna is resonant.

The field strength produced by an antenna is proportional to the current flowing in it. When there are standing waves on an antenna, the parts of the wire carrying the higher current have the greater radiating effect. All resonant antennas have standing waves—only terminated types, like the terminated rhombic and terminated "V," have substantially uniform current along their lengths.

The ratio of power required to produce a given field strength with a "comparison" antenna to the power required to produce the same field strength with a specified type of antenna is called the **power gain** of the latter antenna. The field is measured in the optimum direction of the antenna under test. The comparison antenna is generally a half-wave antenna at the same height and having the same polarization as the antenna under consideration. Gain usually is expressed in decibels.

In unidirectional beams (antennas with most of the radiation in only one direction) the **front-to-back** ratio is the ratio of power radiated in the maximum direction to power radiated in the opposite direction. It is also a measure of the reduction in received signal when the beam direction is changed from that for maximum response to the opposite direction. Front-to-back ratio is usually expressed in decibels.

The bandwidth of an antenna refers to the frequency range over which a property falls within acceptable limits. The gain bandwidth, the front-to-back-ratio bandwidth and the standing-wave-ratio bandwidth are of prime interest in amateur work. The gain bandwidth is of interest because, generally, the higher the antenna gain is the narrower the gain bandwidth will be. The s.w.r. bandwidth is of interest because it is an indication of the transmission-line efficiency over the useful frequency range of the antenna.

GROUND EFFECTS

The radiation pattern of any antenna that is many wavelengths distant from the ground and all others objects is called the free-space pattern of that antenna. The free-space pattern of an antenna is almost impossible to obtain in practice, except in the v.h.f. and u.h.f. ranges. Below 30 Mc., the height of the antenna above ground is a major factor in determining the radiation pattern of the antenna.

When any antenna is near the ground the free-space pattern is modified by reflection of radiated waves from the ground, so that the actual pattern is the resultant of the free-space pattern and ground reflections. This resultant is dependent upon the height of the antenna, its position or orientation with respect to the surface of the ground, and the electrical characteristics of the ground. The effect of a perfectly reflecting

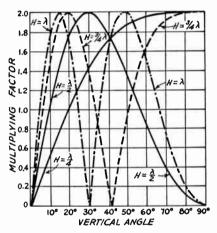


Fig. 14-1—Effect of ground on radiation of horizontal antennas at vertical angles for four antenna heights.

This chart is based on perfectly conducting ground.

ground is such that the original free-space field strength may be multiplied by a factor which has a maximum value of 2, for complete reinforcement, and having all intermediate values to zero, for complete cancellation. These reflections only affect the radiation pattern in the vertical plane—that is, in directions upward from the earth's surface—and not in the horizontal plane, or the usual geographical directions.

Fig. 14-1 shows how the multiplying factor varies with the vertical angle for several representative heights for horizontal antennas. As the height is increased the angle at which complete reinforcement takes place is lowered, until for a height equal to one wavelength it occurs at a vertical angle of 15 degrees. At still greater heights, not shown on the chart, the first maximum will occur at still smaller angles.

Radiation Angle

The vertical angle of maximum radiation is of primary importance, expecially at the higher frequencies. It is advantageous, therefore, to erect the antenna at a height that will take advantage of ground reflection in such a way as to reinforce the space radiation at the most desirable angle. Since low angles usually are most effective, this generally means that the antenna should be high-at least one-half wavelength at 14 Mc., and preferably three-quarters or one wavelength, and at least one wavelength, and preferably higher, at 28 Mc. The physical height required for a given height in wavelengths decreases as the frequency in increased, so that good heights are not impracticable; a half wavelength at 14 Mc. is only 35 feet, approximately, while the same height represents a full wavelength at 28 Mc. At 7 Mc. and lower frequencies the higher radiation angles are effective, so that again a useful antenna height in not difficult of attainment. Heights between 35 and 70 feet are suitable for all bands, the higher figures being preferable.

Imperfect Ground

Fig. 14-1 is based on ground having perfect conductivity, whereas the actual earth is not a perfect conductor. The principal effect of actual ground is to make the curves inaccurate at the lowest angles; appreciable high-frequency radiation at angles smaller than a few degrees is practically impossible to obtain over horizontal ground. Above 15 degrees, however, the curves are accurate enough for all practical purposes, and may be taken as indicative of the result to be expected at angles between 5 and 15 degrees.

The effective ground plane—that is, the plane from which ground reflections can be considered to take place—seldom is the actual surface of the ground but is a few feet below it, depending upon the character of the soil.

Impedance

Waves that are reflected directly upward from the ground induce a current in the antenna in

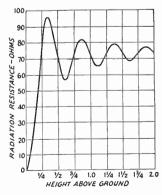


Fig. 14-2—Theoretical curve of variation of radiation resistance for a very thin half-wave horizontal antenna as a function of height in wavelength above perfectly reflecting ground.

passing, and, depending on the antenna height, the phase relationship of this induced current to the original current may be such as either to increase or decrease the total current in the antenna. For the same power input to the antenna, an increase in current is equivalent to a decrease in impedance, and vice versa. Hence, the impedance of the antenna varies with height. The theoretical curve of variation of radiation resistance for a very thin half-wave antenna above perfectly reflecting ground is shown in Fig. 14-2. The impedance approaches the free-space value as the height becomes large, but at low heights may differ considerably from it.

Choice of Polarization

Polarization of the transmitting antenna is generally unimportant on frequencies between 3.5 and 30 Mc. However, the question of whether the antenna should be installed in a horizontal or vertical position deserves consideration for other reasons. A vertical half-wave or quarterwave antenna will radiate equally well in all horizontal directions, so that it is substantially nondirectional, in the usual sense of the word. If installed horizontally, however, the antenna will tend to show directional effects, and will radiate best in the direction at right angles, or broadside, to the wire. The radiation in such a case will be least in the direction toward which the wire points.

The vertical angle of radiation also will be affected by the position of the antenna. If it were not for ground losses at high frequencies, the vertical half-wave antenna would be preferred because it would concentrate the radiation horizontally, and this low-angle radiation is preferable for practically all work.

THE HALF-WAVE ANTENNA

A fundamental form of antenna is a single wire whose length is approximately equal to half the transmitting wavelength. It is the unit from which many more-complex forms of antennas are constructed. It is known as a dipole antenna.

The length of a half-wave in space is:

Length (feet) =
$$\frac{492}{Freq. (Mc.)}$$
 (14-A)

The actual length of a half-wave antenna will not be exactly equal to the half-wave in space, but depends upon the thickness of the conductor in relation to the wavelength as shown in Fig. 14-3, where K is a factor that must be multiplied by the half wavelength in free space to obtain the resonant antenna length. An additional shortening effect occurs with wire antennas supported by insulators at the ends because of the capacitance added to the system by the insulators (end effect). The following formula is sufficiently accurate for wire antennas at frequencies up to 30 Mc.:

Length of half-wave antenna (feet) =

$$\frac{492 \times 0.95}{Freq. (Mc.)} = \frac{468}{Freq. (Mc.)}$$
 (14-B)

Example: A half-wave antenna for 7150 kc. (7.15 Mc.) is $\frac{468}{7.15} = 65.45$ feet, or 65 feet 5

Above 30 Mc. the following formulas should be used, particularly for antennas constructed from rod or tubing. K is taken from Fig. 14-3.

Length of half-wave antenna (feet) =

$$\frac{492 \times K}{Freq. (Mc.)}$$
 (14-C)

$$\frac{492 \times K}{Freq. \text{ (Mc.)}}$$
 (14-C)
$$or \ length \text{ (inches)} = \frac{5905 \times K}{Freq. \text{ (Mc.)}}$$
 (14-D)

Example: Find the length of a half wavelength antenna at 29 Mc., if the antenna is made of 2-inch diameter tubing. At 29 Mc., a half wavelength in space is $\frac{492}{29} = 16.97$ feet, from Eq. 14-A. Ratio of half wavelength to conductor diameter (changing wavelength to inches) is $\frac{16.97 \times 12}{10.97 \times 12} = 101.8$. From Fig. 14-3, K = 0.963 for this ratio. The length of the antenna, from Eq. 14-C, is $\frac{492 \times 0.963}{1}$ 16.34 feet, or 16 feet 4 inches. The answer is obtained directly in inches by substitution in Eq. 14-D: $\frac{5905 \times 0.963}{20} = 196$ inches.

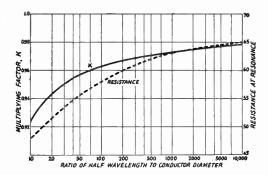


Fig. 14-3-Effect of antenna diameter on length for half-wave resonance, shown as a multiplying factor, K, to be applied to the free-space half wavelength (Equation 14-A). The effect of conductor diameter on the center impedance also is shown.

Current and Voltage Distribution

When power is fed to an antenna, the current and voltage vary along its length. The current is maximum (loop) at the center and nearly zero (node) at the ends, while the opposite is true of the r.f. voltage. The current does not actually reach zero at the current nodes, because of the end effect; similarly, the voltage is not

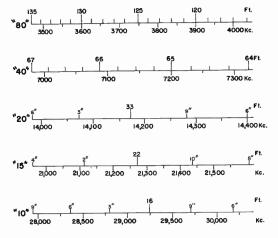


Fig. 14-4—The above scales, based on Eq. 14-B, can be used to determine the length of a half-wave antenna of wire.

zero at its node because of the resistance of the antenna, which consists of both the r.f. resistance of the wire (ohmic resistance) and the radiation resistance. The radiation resistance is an equivalent resistance, a convenient conception to indicate the radiation properties of an antenna. The radiation resistance is the equivalent resistance that would dissipate the power the antenna radiates, with a current flowing in it equal to the antenna current at a current loop (maximum). The ohmic resistance of a half wavelength antenna is ordinarily small enough, compared with the radiation resistance, to be neglected for all practical purposes.

Impedance

The radiation resistance of an infinitely-thin half-wave antenna in free space is about 73 ohms. The value under practical conditions is commonly taken to be in the neighborhood of 60 to 70 ohms, although it varies with height in the manner of Fig. 14-2. It increases toward the ends. The actual value at the ends will depend on a number of factors, such as the height, the physical construction, the insulators at the ends, and the position with respect to ground.

Conductor Size

The impedance of the antenna also depends upon the diameter of the conductor in relation to the wavelength, as indicated in Fig. 14-3. If the diameter of the conductor is increased the capacitance per unit length increases and the inductance per unit length decreases. Since the radiation resistance is affected relatively little, the decreased L/C ratio causes the Q of the antenna to decrease, so that the resonance curve becomes less sharp. Hence, the antenna is capable of working over a wide frequency range. This effect is greater as the diameter is increased, and is a property of some importance at the very-high frequencies where the wavelength is small.

Radiation Characteristics

The radiation from a dipole antenna is not uniform in all directions but varies with the angle with respect to the axis of the wire. It is most intense in directions perpendicular to the wire and zero along the direction of the wire,

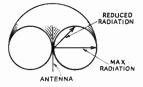


Fig. 14-5—The free-space radiation pattern of a half-wave antenna. The antenna is shown in the vertical position, and the actual "doughnut" pattern is cut in half to show how the line from the center of the antenna to the surface of the pattern varies. In practice this pattern is modified by the height above ground and if the antenna is vertical or horizontal. Fig. 14-1 shows some of the effects of height on the vertical angle of radiation.

with intermediate values at intermediate angles. This is shown by the sketch of Fig. 14-5, which represents the radiation pattern in free space. The relative intensity of radiation is proportional to the length of a line drawn from the center of the figure to the perimeter. If the antenna is vertical, as shown, then the field strength will be uniform in all horizontal directions; if the antenna is hori-



Fig. 14-6—Illustrating the importance of vertical angle of radiation in determining antenna directional effects. Off the end, the radiation is greater at higher angles. Ground reflection is neglected in this drawing of the freespace pattern of a horizontal antenna.

zontal, the relative field strength will depend upon the direction of the receiving point with respect to the direction of the antenna wire. The variation in radiation at various vertical angles from a half wavelength horizontal antenna is indicated in Figs. 14-6 and 14-7.

FEEDING A DIPOLE ANTENNA

Direct Feed

If possible, it is advisable to locate the antenna at least a half wavelength from the transmitter and use a transmission line to carry the power from the transmitter to the antenna. However, in many cases this is impossible, particularly on the lower frequencies, and direct feed must be used. Three examples of direct feed are shown in Fig. 14-8. In the method shown at A, C_1 and C_2 should be about 150 $\mu\mu$ f. each for the 3.5-Mc. band, 75 $\mu\mu$ f. each at 7 Mc., and proportionately smaller at the higher frequencies. The antenna coil connected between them should resonate to 3.5 Mc. with about 60 or 70 $\mu\mu$ f. for the 80-meter

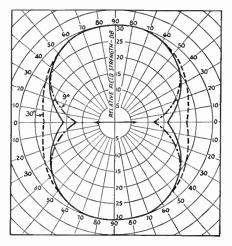


Fig. 14-7—Horizontal pattern of a horizontal half-wave antenna at three vertical radiation angles. The solid line is relative radiation at 15 degrees. Dotted lines show deviation from the 15-degree pattern for angles of 9 and 30 degrees. The patterns are useful for shape only, since the amplitude will depend upon the height of the antenna above ground and the vertical angle considered. The patterns for all three angles have been proportioned to the same scale, but this does not mean that the maximum amplitudes necessarily will be the same. The arrow indicates the direction of the horizantal antenna wire.

band, for 40 meters it should resonate with 30 or 35 $\mu\mu$ f., and so on. The circuit is adjusted by using loose coupling between the antenna coil and the transmitter tank coil and adjusting C_1 and C_2 until resonance is indicated by an increase in plate current. The coupling between the coils should then be increased until proper plate cur-

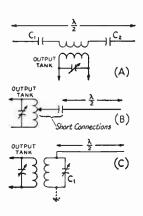


Fig. 14-8—Methods of directly exciting the half-wave antenna. A, current feed, series tuning; B, voltage feed, capacitive coupling; C, voltage feed, with inductively coupled antenna tank. In A, the coupling circuit is not included in the effective electrical length of the antenna system proper. Link coupling can be used in A and C.

rent is drawn. It may be necessary to re-resonate the transmitter tank circuit as the coupling is increased, but the change should be small.

The circuits in Fig. 14-8B and C are used when only one end of the antenna is accessible. In B, the coupling is adjusted by moving the tap toward the "hot" or plate end of the tank coil—the series capacitor may be of any convenient

value that will stand the voltage, and it doesn't have to be variable. In the circuit at C, the antenna tuned circuit (C_1 and the antenna coil) should be similar to the transmitter tank circuit. The antenna tuned circuit is adjusted to resonance with the antenna connected but with loose coupling to the transmitter. Heavier loading of the tube is then obtained by tightening the coupling between the antenna coil and the transmitter tank coil.

Of the three systems, that at A is preferable because it is a symmetrical system and generally results in less r.f. power "floating" around the shack. The system of B is undesirable because it provides practically no protection against the radiation of harmonics, and it should only be used in emergencies.

Transmission-Line Feed for Dipoles

Since the impedance at the center of a dipole is in the vicinity of 70 ohms, it offers a good match for 75-ohm two-wire transmission lines. Several types are available on the market, with different power-handling capabilities. They can be connected in the center of the antenna, across a small strain insulator to provide a convenient connection point. Coaxial line of 75 ohms impedance can also be used, but it is heavier and thus

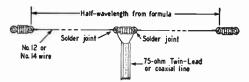


Fig. 14-9—Construction of a dipole fed with 75-ohm line. The length of the antenna is calculated from Equation 14-B or Fig. 14-4.

not as convenient. In either case, the transmission line should be run away at right angles to the antenna for at least one-quarter wavelength, if possible, to avoid current unbalance in the line caused by pick-up from the antenna. The antenna length is calculated from Equation 14-B, for a half wavelength antenna. When No. 12 or No. 14 enameled wire is used for the antenna, as is generally the case, the length of the wire is the overall length measured from the loop through the insulator at each end. This is illustrated in Fig. 14-9.

The use of 75-ohm line results in a "flat" line

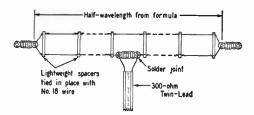


Fig. 14-10—The construction of an open-wire folded dipole fed with 300-ohm line. The length of the antenna is calculated from Equation 14-B or Fig. 14-4.

Feeding Dipoles

over most of any amateur band. However, by making the half-wave antenna in a special manner, called the **two-wire** or **folded dipole**, a good match is offered for a 300-ohm line. Such an antenna is shown in Fig. 14-10. The open-wire line shown in Fig. 14-10 is made of No. 12 or No. 14 enameled wire, separated by lightweight spacers of Lucite or other material (it doesn't have to be a *low-loss* insulating material), and the spacing can be on the order of from 4 to 8 inches, depending upon what is convenient and what the operating frequency is. At 14 Mc., 4-inch separation is satisfactory, and 8-inch spacing can be used at 3.5 Mc.

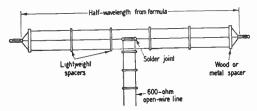


Fig. 14-11—The construction of a 3-wire folded dipole is similar to that of the 2-wire folded dipole. The end spacers may have to be slightly stronger than the others because of the greater compression force on them. The length of the antenna is obtained from Equation 14-B or Fig. 14-4. A suitable line can be made from No. 14 wire spaced 5 inches, or from No. 12 wire spaced 6

The half wavelength antenna can also be made from the proper length of 300-ohm line, opened on one side in the center and connected to the feedline. After the wires have been soldered together, the joint can be strengthened by molding some of the excess insulating material (polyethylene) around the joint with a hot iron, or a suitable lightweight clamp of two pieces of Lucite can be devised.

Similar in some respects to the two-wire folded dipole, the three-wire folded dipole of Fig. 14-11 offers a good match for a 600-ohm line. It is favored by amateurs who prefer to use an open-wire line instead of the 300-ohm insulated line.

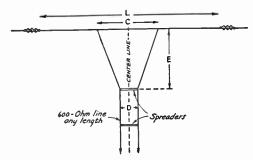


Fig. 14-12—Delta-matched antenna systems. The dimensions C, D, and E are found by formulas given in the text. It is important that the matching section, E, come straight away from the antenna without any bends.

The three wires of the antenna proper should all be of the same diameter.

Another method for offering a match to a 600-ohm open-wire line with a half wavelength antenna is shown in Fig. 14-12. The system is called a **delta match**. The line is "fanned" as it approaches the antenna, to have a gradually increasing impedance that equals the antenna impedance at the point of connection. The dimensions are fairly critical, but careful measurement before installing the antenna and matching section is generally all that is necessary. The length of the antenna, *L*, is calculated from Equation 14-B or Fig. 14-4. The length of section *C* is computed from:

$$C ext{ (feet)} = \frac{118}{Freq. ext{ (Mc.)}}$$
 (14-E)

The feeder clearance, E, is found from

$$E ext{ (feet)} = \frac{148}{Freq. (Mc.)}$$
 (14-F)

Example: For a frequency of 7.1 Mc., the length

$$L = \frac{468}{7.1} = 65.91$$
 feet, or 65 feet 11 inches

$$C = \frac{118}{7.1} = 16.62$$
 feet, or 16 feet 7 inches.

$$E = \frac{148}{7.1} = 20.84$$
 feet, or 20 feet 10 inches.

Since the equations hold only for 600-ohm line, it is important that the line be close to this value. This requires 5-inch spaced No. 14 wire, 6-inch spaced No. 12 wire, or 3¾-inch spaced No. 16 wire.

If a half wavelength antenna is fed at the center with other than 75-ohm line, or if a two-wire dipole is fed with other than 300-ohm line, standing waves will appear on the line and coupling to the transmitter may become awkward for some line lengths, as described in Chapter 13. How-

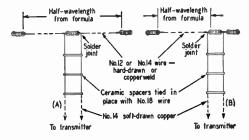


Fig. 14-13—The half-wave antenna can be fed at the center or at the end with an open-wire line. The antenna length is obtained from Equation 14-B or Fig. 14-4.

ever, in many cases it is not convenient to feed the half-wave antenna with the correct line (as is the case where multiband operation of the same antenna is desired), and sometimes it is not convenient to feed the antenna at the center. Where multiband operation is desired (to be discussed later) or when the antenna must be fed at one end by a transmission line, an open-wire line of from 450 to 600 ohms impedance is generally used. The impedance at the end of a half

wavelength antenna is in the vicinity of several thousand ohms, and hence a standing-wave ratio of 4 or 5 is not unusual when the line is connected to the end of the antenna. It is advisable, therefore, to keep the losses in the line as low as possible. This requires the use of ceramic or Micalex feeder spacers, if any appreciable power

is used. For low-power installations in dry climates, dry wood spacers boiled in paraffin are satisfactory. Mechanical details of half wavelength antennas fed with open-wire lines are given in Fig. 14-13. Regardless of the power level, solid-dielectric Twin-Lead is not recommended for this use.

LONG-WIRE ANTENNAS

An antenna will be resonant so long as an integral number of standing waves of current and voltage can exist along its length; in other words, so long as its length is some integral multiple of a half wavelength. When the antenna is more than a half-wave long it usually is called a long-wire antenna, or a harmonic antenna

Current and Voltage Distribution

Fig. 14-14 shows the current and voltage distribution along a wire operating at its fundamental frequency (where its length is equal to a

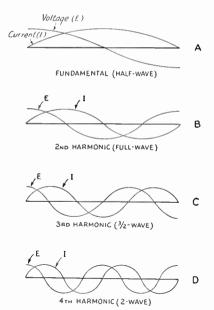


Fig. 14-14—Standing-wave current and voltage distribution along an antenna when it is operated at various harmonics of its fundamental resonant frequency.

half wavelength) and at its second, third and fourth harmonics. For example, if the fundamental frequency of the antenna is 7 Mc., the current and voltage distribution will be as shown at A. The same antenna excited at 14 Mc. would have current and voltage distribution as shown at B. At 21 Mc., the third harmonic of 7 Mc., the current and voltage distribution would be as in C; and at 28 Mc., the fourth harmonic, as in D. The number of the harmonic is the number of half waves contained in the antenna at the particular operating frequency.

The polarity of current or voltage in each

standing wave is opposite to that in the adjacent standing waves. This is shown in the figure by drawing the current and voltage curves successively above and below the antenna (taken as a zero reference line), to indicate that the polarity reverses when the current or voltage goes through zero. Currents flowing in the same direction are in phase; in opposite directions, out of phase.

It is evident that one antenna may be used for harmonically-related frequencies, such as the various amateur bands. The long-wire or harmonic antenna is the basis of multiband operation with one antenna.

Physical Lengths

The length of a long-wire antenna is not an exact multiple of that of a half-wave antenna because the end effects operate only on the end sections of the antenna; in other parts of the wire these effects are absent, and the wire length is approximately that of an equivalent portion of the wave in space. The formula for the length of a long-wire antenna, therefore, is

Length (feet) =
$$\frac{492 (N - 0.05)}{Freq. (Mc.)}$$
 (14-G)

where N is the number of half-waves on the antenna.

Example: An antenna 4 half-waves long at 14.2 Mc. would be
$$\frac{492 (4 - 0.05)}{14.2} = \frac{492 \times 3.95}{14.2}$$

= 136.7 feet, or 136 feet 8 inches.

It is apparent that an antenna cut as a half-wave for a given frequency will be slightly off resonance at exactly twice that frequency (the second harmonic), because of the decreased influence of the end effects when the antenna is more than one-half wavelength long. The effect is not very important, except for a possible unbalance in the feeder system and consequent radiation from the feedline. If the antenna is fed in the exact center, no unbalance will occur at any frequency, but end-fed systems will show an unbalance on all but one frequency in each harmonic range.

Impedance and Power Gain

The radiation resistance as measured at a current loop becomes higher as the antenna length is increased. Also, a long-wire antenna radiates more power in its most favorable direction than does a half-wave antenna in its most favorable

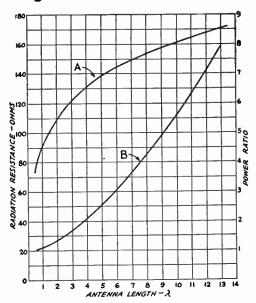


Fig. 14-15—Curve A shows variation in radiation resistance with antenna length. Curve B shows power in lobes of maximum radiation for long-wire antennas as a ratio to the maximum radiation for a half-wave an-

direction. This power gain is secured at the expense of radiation in other directions. Fig. 14-15 shows how the radiation resistance and the power in the lobe of maximum radiation vary with the antenna length.

Directional Characteristics

As the wire is made longer in terms of the number of half wavelengths, the directional ef-

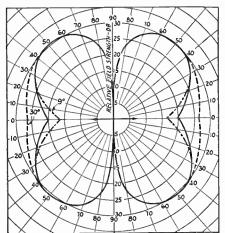


Fig. 14-16—Horizontal patterns of radiation from a full-wave antenna. The solid line shows the pattern for a vertical angle of 15 degrees; dotted lines show deviation from the 15-degree pattern at 9 and 30 degrees. All three patterns are drawn to the same relative scale; actual amplitudes will depend upon the height of the antenna.

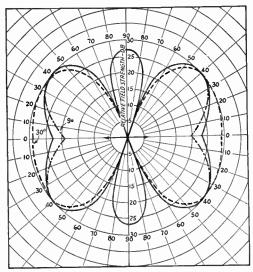


Fig. 14-17—Horizontal patterns of radiation from an antenna three half-waves long. The solid line shows the pattern for a vertical angle of 15 degrees; dotted lines show deviation from the 15-degree pattern at 9 and 30 degrees. Minor lobes coincide for all three angles.

fects change. Instead of the "doughnut" pattern of the half-wave antenna, the directional characteristic splits up into "lobes" which make various angles with the wire. In general, as the length of the wire is increased the direction in which maximum radiation occurs tends to approach the line of the antenna itself.

Directional characteristics for antennas one wavelength, three half-wavelengths, and two wavelengths long are given in Figs. 14-16,

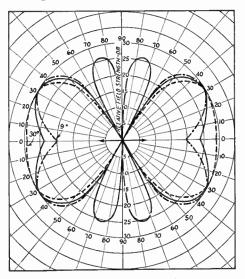


Fig. 14-18—Horizontal patterns of radiation from an antenna two wavelengths long. The solid line shows the pattern for a vertical angle of 15 degrees; dotted lines show deviation from the 15-degree pattern at 9 and 30 degrees. The minor lobes coincide for all three angles.

14-17 and 14-18, for three vertical angles of radiation. Note that, as the wire length increases, the radiation along the line of the antenna becomes more pronounced. Still longer antennas can be considered to have practically "end-on" directional characteristics, even at the lower radiation angles.

Methods of Feeding

In a long-wire antenna, the currents in adja-

cent half-wave sections must be out of phase, as shown in Fig. 14-14. The feeder system must not upset this phase relationship. This is satisfied by feeding the antenna at either end or at any current loop. A two-wire feeder cannot be inserted at a current node, however, because this invariably brings the currents in two adjacent half-wave sections in phase. A long wire antenna is usually made a half wavelength at the lowest frequency and fed at the end.

MULTIBAND ANTENNAS

As suggested in the preceding section, the same antenna may be used for several bands by operating it on harmonics. When this is done it is necessary to use tuned feeders, since the impedance matching for nonresonant feeder operation can be accomplished only at one frequency unless means are provided for changing the length of a matching section and shifting the point at which the feeder is attached to it.

A dipole antenna that is center-fed by a soliddielectric line is useless for even harmonic operation; on all even harmonics there is a voltage maximum occurring right at the feed point, and the resultant impedance mismatch causes a large standing-wave ratio and consequently high losses arise in the solid dielectric. It is wise not to attempt to use on its even harmonics a halfwave antenna center-fed with coaxial cable. On odd harmonics, as between 7 and 21 Mc., a current loop will appear in the center of the antenna and a fair match can be obtained. High-impedance solid-dielectric lines such as 300-ohm Twin-Lead may be used in an emergency, provided the power does not exceed a few hundred watts, but it is an inefficient feed method.

When the same antenna is used for work in several bands, the directional characteristics will vary with the band in use.

Simple Systems

The most practical simple multiband antenna is one that is a half wavelength long at the lowest frequency and is fed either at the center or one end with an open-wire line. Although the standing wave ratio on the feedline will not approach 1.0 on any band, if the losses in the line are low the system will be efficient. From the standpoint of reduced feedline radiation, a centerfed system is superior to one that is end-fed, but the end-fed arrangement is often more convenient and should not be ignored as a possibility. The center-fed antenna will not have the same radiation pattern as an end-fed one of the same length, except on frequencies where the length of the antenna is a half wavelength. The end-fed antenna acts like a long-wire antenna on all bands (for which it is longer than a half wavelength), but the center-fed one acts like two antennas of half that length fed in phase. For example, if a full-wavelength antenna is fed at one end, it will have a radiation pattern as shown in Fig. 14-16, but if it is fed in the center the pattern will be somewhat similar to Fig. 14-7, with the maximum radiation broadside to the wire. Either antenna is a good radiator, but if the radiation pattern is a factor, the point of feed must be considered.

Since multiband operation of an antenna does not permit matching of the feedline, some attention should be paid to the length of the feedline if convenient transmitter-coupling arrangements are to be obtained. Table 14-1 gives some suggested antenna and feeder length for multiband operation. In general, the length of the feedline can be other than that indicated, but the type of coupling circuit may change.

Open-wire line feed is recommended for an antenna of this type, since the losses will run too high in solid-dielectric line. For low-power applications up to a few hundred watts, open-wire TV line is convenient and satisfactory to use. However, for high-power installations up to the kilowatt limit, an open-wire line with No. 14 or No.

TABLE 14-1 Multiband Tuned-Line-Fed Antennas

Antenna Length (Ft.)	Feeder Length (Ft.)	Band	Type of Coupling Circuit
With end feed:			
135	45	3.5 - 21 28	Series Parallel
67	45	7 – 21 28	Series Parallel
With center feed	i:		
		1 2 2 2	
135	42	3.5 - 21	Parallel Series
135	771/2		
		28	Series

Antenna lengths for end-fed antennas are approximate and should be cut to formula length at favorite operating frequency.

Where parallel tuning is specified, it will be necessary in some cases to tap in from the ends of the coil for proper loading—see Chapter 13 for examples of antenna couplers.

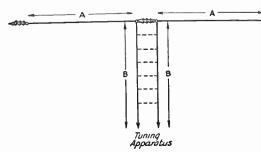


Fig. 14-19—Practical arrangement of a shortened antenna. When the total length, A+B+B+A, is the same as the antenna length plus twice the feeder length of the center-fed antennas of Table 14-I, the same type of coupling circuit will be used. When the feeder length or antenna length, or both, makes the sum different, the type of coupling circuit may be different but the effectiveness of the antenna is not changed, unless A+A is less than a quarter wavelength.

12 conductors should be used. This can be built from soft-drawn wire and ceramic or other suitable spacers, or it can be bought ready-made.

Antennas for Restricted Space

If the space available for the antenna is not large enough to accommodate the length necessary for a half wave at the lowest frequency to be used, quite satisfactory operation can be secured by using a short antenna and making up the missing length in the feeder system. The antenna itself may be as short as a quarter wavelength and will radiate fairly well, although of course it will not be as effective as one a half wave long. Nevertheless such a system is useful where operation on the desired band otherwise would be impossible.

Tuned feeders are a practical necessity with such an antenna system, and a center-fed antenna will give best all-around performance. With end feed the feeder currents become badly unbalanced.

With center feed, practically any convenient length of antenna can be used. If the total length of antenna plus twice feedline is the same as in Table 14-I, the type of tuning will be the same as stated. This is illustrated in Fig. 14-19. If the total length is not the same, different tuning conditions can be expected on some bands. This should not be interpreted as a fault in the antenna, and any tuning system (series or parallel) that works well without any trace of heating is quite satisfactory. Heating may result when the taps with parallel tuning are made too close to the center of the coil—it can often be corrected by using less total inductance and more capacitance.

Bent Antennas

Since the field strength at a distance is proportional to the current in the antenna, the high-current part of a dipole antenna (the center quarter wave, approximately) does most of the radiating. Advantage can be taken of this

fact when the space available does not permit building an antenna a half-wave long. In this case the ends may be bent,

either horizontally or vertically, so that the total length equals a half wave, even though the straightaway horizontal length may be as short as a quarter wave. The operation is illustrated

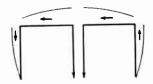


Fig. 14-20—Folded arrangement for shortened antennas. The total length is a half-wave, not including the feeders. The horizontal part is made as long as convenient and the ends dropped down to make up the required length. The ends may be bent back on themselves like feeders to cancel radiation partially. The horizontal section should be at least a quarter wave long.

in Fig. 14-20. Such an antenna will be a somewhat better radiator than a quarter wavelength antenna on the lowest frequency, but is not so desirable for multiband operation because the ends play an increasingly important part as the frequency is raised. The performance of the system in such a case is difficult to predict, especially if the ends are vertical (the most convenient arrangement) because of the complex combination of horizontal and vertical polarization which results as well as the dissimilar directional characteristics. However, the fact that the radiation pattern is incapable of prediction does not detract from the general usefulness of the antenna. For one-band operation with a "flat" line, end-loading with coils (5 feet or so in from each end) is practical and efficient.

"Windom" or Off-Center-Fed Antenna

A multiband antenna that enjoyed considerable popularity in the 1930s is the "off-center feed" of "Windom," named after the amateur who wrote a comprehensive article about it. Shown in Fig. 14-21A, it consists of a half wavelength antenna on the lowest-frequency band to be used, with a single-wire feeder connected 14% off center. The antenna will operate satisfactorily on the even-harmonic frequencies, and thus a single antenna can be made to serve on the 80-, 40-, 20-, and 10-meter bands. The single-wire feeder shows an impedance of approximately 600 ohms to ground, and consequently the antenna coupling system must be capable of matching this value to the transmitter, A tapped parallel-tuned circuit or a properly-proportioned pi-network coupler is generally used. Where TVI is a problem, the antenna coupler is required, so that a low-pass filter can be used in the connecting link of coaxial line.

Although theoretically the feed line can be of any length, some lengths will tend to give trouble with "too much r.f. in the shack," with the consequence that r.f. sparks can be drawn from

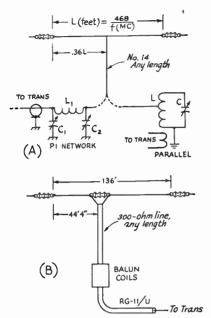


Fig. 14-21—Two versions of the off-center-fed antenna. (A) Single-wire feed shows approximately 600 ohms impedance to ground and is most conveniently coupled to the transmitter as shown. The pi-network coupling will require more capacity at C_1 than at C_2 . L_1 is best found by experiment—an inductance of about the same size as that used in the output stage is a good starting point. The parallel-tuned circuit will be a tuned circuit that resonates at the operating frequency with L and C close to those used in the output stage. The tap is found by experiment, and it should be as near the top of L as it can and still give good loading of the transmitter.

(B) Two-wire off-center feed uses 300-ohm TV line. Although the 300-ohm line can be coupled directly to some transmitters, it is common practice to step down the impedance level to 75 ohms through a pair of "balun" coils.

the transmitter's metal cabinet and/or v.f.o. notes will develop serious modulation. If such is found to be the case, the feeder length should be changed.

A newer version of the off-center-feed antenna uses 300-ohm TV Twin-Lead to feed the antenna, as shown in Fig. 14-21B. It is claimed that the antenna offers a good match for the 300-ohm line on four bands and, although this is more wishful thinking than actual truth, the system is widely used and does work satisfactorily. It is subject to the same feed line length and "r.f.in-the-shack" troubles that the single-wire version enjoys. However, in this case a pair of "balun" coils can be used to step down the impedance level to 75 ohms and at the same time alleviate some of the feedline troubles. This antenna system is popular among amateurs using multiband transmitters with pi-network-tuned output stages.

With either of the off-center-fed antenna systems, the feedline should run away from the an-

tenna at right angles for as great a distance as possible before bending. No sharp bends should be allowed anywhere in the line.

Multiband Operation with Coaxial Line Feed

The proper use of coaxial line requires that the standing-wave ratio be held to a low value, preferably below 2:1. Since the impedance of an ordinary antenna changes widely from band to band, it is not possible to feed a simple antenna with coaxial line and use it on a number of bands without tricks of some kind. The single exception to this is the use of 75-ohm coaxial line to feed a 7-Mc. half-wave antenna, as in Fig. 14-19; this antenna can also be used on 21 Mc. and the s.w.r. in the line will not run too high.

One multiband antenna system that can be used by anyone without much trouble is shown in Fig. 14-22. Here separate dipoles are connected to one feedline. The 7-Mc. dipole also serves on 21 Mc. A low s.w.r. will appear on the feedline in each band if the dipoles are of the proper length. The antenna system can be built by suspending one set of elements from the one above, using insulator-terminated wood spreaders about one foot long. An alternative is to let one antenna droop several feet under the other, bring ropes attached to the insulators back to a common support point. It has been found that a separation of only an inch or two between dipoles is satisfactory. By using a length of the Twin-Lead used for folded dipoles (one Copperweld conductor and one soft-drawn), the strong wire can be used for the low-frequency dipole. The soft-drawn wire is then used on a higher band, supported by the solid dielectric.

A vertical antenna can be operated on several bands and fed with a single length of coaxial line provided the antenna is no longer than 0.6 wavelength at the highest frequency and that a suitable matching network for each band is used at the base. A good radial or ground system is required. The matching sections can be housed in a

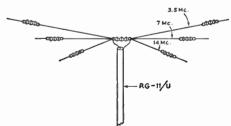


Fig. 14-22—An effective "all-band" antenna fed with a single length of coaxial line can be constructed by joining several half wavelength antennas at their centers and feeding them at the common point. In the example above, a low s.w.r. will be obtained on 80, 40, 20 and 15 meters. (The 7-Mc. antenna also works at 21 Mc.) If a 28-Mc. antenna were added, 10-meter operation could also be included.

The antenna lengths can be computed from formula 14-B. The shorter antennas can be suspended a foot or two below the longest one.

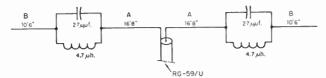


Fig. 14-23—Sketch showing dimensions of a trap dipole covering the 40-, 20- and 10-meter bands. The total span is less than 60 feet.

weatherproof box and changed manually or by stepping relays; their form will vary from parallel-tuned circuits to L sections. (See McCoy, QST, December, 1955, for description of L-section coupler.)

Multiband "Trap" Antennas

Another approach to the problem of multiband operation with a single untuned feedline is the use of parallel-tuned circuits installed in the antenna at the right points to "divorce" the remainder of the antenna from the center section (part fed by coaxial line) as the transmitter is changed to a higher-frequency band. This principle of the divorcing circuits is utilized in a commercial "all-band" vertical antenna, and a 5-band kit for horizontal antennas is also available commercially. The divorcing circuits are also used in several commercial multiband beams for the 14-, 21- and 28-Mc. bands.

The multiband antenna system shown in Fig. 14-23 may be of interest to the ham who wishes to work on several bands but doesn't have sufficient space for an 80-meter antenna and consequently is limited to 40 meters and below. (A five-band antenna requires more than a 100-foot span; see Greenberg, QST, October, 1956.)

On 40 meters the traps serve as inductors to load the system to 7 Mc. On 20, the traps (resonant to 14.1 Mc.) divorce the B sections from the antenna proper. On 28 Mc. the entire antenna becomes approximately a 5/2-wavelength radiator.

As shown in Fig. 14-24, each trap is literally built around an "egg" or "strain" insulator. In this type of insulator, the hole at one end is at right angles to the hole at the other end, and the wires are fastened as in Fig. 14-25. These insulators have greater compressive strength than ten-

sile strength and will not permit the antenna to fall should the insulator break, since the two interlooped wires prevent it. There is ample space within the inductor for both the insulator and capacitor. The plastic covers are not essential but are considered desirable because they provide mechanical pro-

Fig. 14-24—The 14-Mc. trap is enclosed in a weatherproof cover made of plastic sheet. The ceramic capacitor and strain insulator are inside the coil.

tection and prevent the accumulation of ice or soot and tars which may not wash off the traps when it rains.

Electrically, each trap consists of a 25- $\mu\mu$ f. capacitor shunted by 4.7 μ h, of inductance. A Centralab ceramic transmitting capacitor 857-25Z, rated at 15,000 volts d.c., is shown and will safely handle a kilowatt. Other ceramic capacitors rated at approximately 6000 volts would be satisfactory, as well as cheaper. The inductors are made of No. 12 wire, $2\frac{1}{2}$ inches in diameter, 6 turns per inch (B & W 3905-1 coil stock).

One may wish to choose a different frequency in the 20-meter band for which optimum results are desired; for example, 14.05 Mc. for c.w. operation, 14.25 Mc. for phone operation, or perhaps 14.175 Mc. for general coverage. In any case, the number of inductor turns is adjusted accordingly.

Trap Adjustment

As a preliminary step, loops of No. 12 wire are fitted to one of the egg insulators in the normal manner (see Fig. 14-25), except that after the wraps are made, the end leads are snipped off close to the wraps. A capacitor is then placed in position and bridged with short leads across the insulator and soldered sufficiently to provide temporary support. The combination is then slipped inside about 10 turns of the inductor, one end of which should be soldered to an insulator-capacitor lead.

Adjustment to the resonant frequency can now proceed, using a grid-dip meter.

Coupling between the g.d.o. and the trap should be very loose. To insure accuracy, the station receiver should be used to check the g.d.o. frequency. The inductance should be reduced 1/4 turn at a time. If one is careful, the resonant fre-

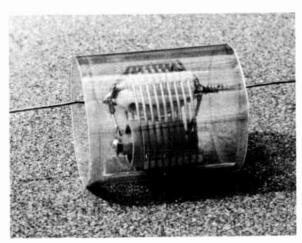


Fig. 14-25—Method of connecting the antenna wire to the strain insulator. The antenna wire is cut off close to the wrap before checking the resonant frequency of the trap.

quency can easily be set to within a few kilocycles of the chosen figure.


The reason for snipping the end leads close to the wraps and the inclusion of the loops through the egg insulator soon becomes apparent. The resonant frequency of the capacitor and inductor alone is reduced about 20 kc. per inch of end lead length and about 350 kc. by the insulator loops. The latter add approximately $2 \mu \mu f$. to the fixed capacitor value and account for the total of 27 $\mu \mu f$. shown in Fig. 14-23.

Assembly

Having determined the exact number of inductor turns, the trap is taken apart and reassembled with leads of any convenient length. One may, of course, connect the entire lengths of sections \mathcal{A} and \mathcal{B} to the trap at this time, if desired. But, if more convenient, a foot or two of wire can be fastened and the remaining lengths soldered on just before the antenna is raised.

The protective covers are most readily formed by wrapping two turns (plus an overlap of ½ inch) of 0.020-inch polystyrene or lucite sheeting around a 3-inch plastic disk held at the center of the cylinder so formed. The length of the cover should be about 4 inches. A very small amount of plastic solvent (a cohesive cement that actually softens the plastic surfaces) should then be applied under the edge of the overlap and the joint held firmly for about two minutes to insure a strong, tight seal. The disk is pushed out and the inner seam of the sheeting sealed.

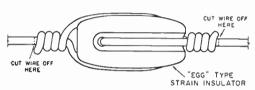The trap is then placed in the plastic cylinder and the end disks marked where the antenna



wires are to pass through. After drilling these holes, the disks are slipped over the leads, pressed into the ends of the cylinder and a small amount of solvent applied to the periphery to obtain a good seal. Some air can flow in and out of the trap through the antenna-wire holes, and this will prevent the accumulation of condensation.

Length Adjustment

Standing-wave ratios are not uniform throughout the band or bands for which an antenna is designed. In a trap antenna, the choice of frequencies for best performance is a compromise. After making the traps resonant at 14.1 Mc., sections A are adjusted for resonance. Sections B are then adjusted for resonance at approximately 7.2 Mc. For the dimensions shown, with the antenna about 250 ft, above street level and 35 ft. above electrical ground, an s.w.r. of virtually 1 to 1 was obtained at 7.2 Mc., with maximums of 1.3 and 1.1 at 7.0 and 7.3 Mc., respectively. In the 20-meter band, the s.w.r. was also 1 to 1 at 14.1 Mc., 1.1 at 14.0 Mc. and 1.3 at 14.3 Mc. In the 10-meter band, the s.w.r. was 1.3 to 1 at 28.0 Mc., 1.1 at 28.4 Mc., 1.5 at 29 Mc., and only 2.4 at the upper extreme of the band. The s.w.r. on 21 Mc, will be high because the antenna is not resonant in that band.

RG-59/U cable forms the transmission line and is connected to the antenna through a Continental Electronic & Sound Co. "Dipole Dri-Fit Connector." After connecting the cable and antenna wires, the connector should be coated with several layers of insulating varnish to make certain that the junction is watertight.

VERTICAL ANTENNAS

A vertical quarter-wavelength antenna is often used in the low-frequency amateur bands to obtain low-angle radiation. It is also used when there isn't enough room for the supports for a horizontal antenna. For maximum effectiveness is should be located free of nearby objects and it should be operated in conjunction with a good ground system, but it is still worth trying where these ideal conditions cannot be obtained.

Four typical examples and suggested methods for feeding a vertical antenna are shown in Fig. 14-26. The antenna may be wire or tubing supported by wood or insulated guy wires. When tubing is used for the antenna, or when guy wires (broken up by insulators) are used to reinforce the structure, the length given by the formula is likely to be long by a few per cent. A check of the standing-wave ratio on the line will indicate the frequency at which the s.w.r. is minimum.

and the antenna length can be adjusted accordingly.

A good ground connection is necessary for the most effective operation of a vertical antenna (other than the ground-plane type). In some cases a short connection to the cold-water system of the house will be adequate. But maximum performance usually demands a separate ground system. A single 4- to 6-foot ground rod driven into the earth at the base of the antenna is usually not sufficient, unless the soil has exceptional conductivity. A minimum ground system that can be depended upon is 6 to 12 quarter wavelength radials laid out as the spokes of a wheel from the base of the antenna. These radials can be made of heavy aluminum wire, of the type used for grounding TV antennas, buried at least 6 inches in the ground. This is normally done by slitting the earth with a spade and pushing the Verticals 373

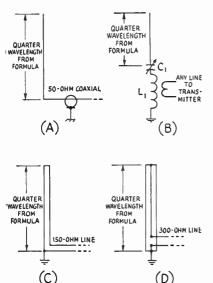


Fig. 14-26—A quarter-wavelength antenna can be fed directly with 50-ohm coaxial line (A) with a low standing-wave ratio, or a coupling network can be used (B) that will permit a line of any impedance to be used. In (B), L_1 and C_2 should resonate to the operating frequency, and L_1 should be larger than is normally used in a plate tank circuit at the same frequency. By using multiwire antennas, the quarter-wave vertical can be fed with (C) 150-or (D) 300-ohm line.

wire into the slot, after which the earth can be tamped down.

The examples shown in Fig. 14-26 all require an antenna insulated from the ground, to provide for the feed point. A grounded tower or pipe can be used as a radiator by employing "shunt feed," which consists of tapping the inner conductor of the coaxial-line feed up on the tower until the best match is obtained, in much the same manner as the "gamma match" (described later) is used on a horizontal element. If the antenna is not an electrical quarter wavelength long, it is necessary to tune out the reactance by adding capacity or inductance between the coaxial line and the shunting conductor. A metal tower supporting a TV antenna or rotary beam can be shunt-fed only if all of the wires and leads from the supported antenna run down the center of the tower and underground away from the tower.

THE GROUND-PLANE ANTENNA

A ground-plane antenna is a vertical quarter-wavelength antenna using an artificial metallic ground, usually consisting of four rods or wires perpendicular to the antenna and extending radially from its base. Unlike the quarter-wavelength vertical antennas without an artificial ground, the ground-plane antenna will give low-angle radiation regardless of the height above actual ground. However, to be a true ground-plane antenna, the plane of the radials should be at least

a quarter wavelength above ground. Despite this on limitation, the antenna is useful for DX work in any band below 30 Mc.

The vertical portion of the ground-plane antenna can be made of self-supported aluminum tubing, or a top-supported wire depending upon the necessary length and the available supports. The radials are also made of tubing or heavy wire depending upon the available supports and necessary lengths. They need not be exactly symmetrical about the base of the vertical portion.

The radiation resistance of a ground-plane antenna varies with the diameter of the vertical element. Since the radiation resistance is usually in the vicinity of 30 to 32 ohms the antenna can be fed with 75-ohm coaxial line if a quarter wavelength matching section of 50-ohm coaxial line is used between the line and the antenna. (See "Quarter-Wave Transformers" in this chapter.)

For multiband operation, a ground-plane antenna can be fed with tuned open-wire line.

Three-Band Ground-Plane Antenna

A three-band ground-plane antenna using wire elements and fed with coaxial line is shown in Fig. 14-27. The builder (K5AYJ) elected to mount it on top of a 34-foot length of galvanized iron pipe, since a ground-plane antenna close to the ground is not a ground-plane antenna at all. Four 17-foot "drooping radials" form the ground plane and double as guy wires. These four wires are fastened to a pipe flange at the top of the mast. At one point on the mast the pipe sections are joined by a T fitting, which provides a con-

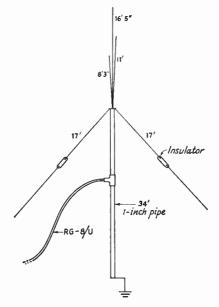


Fig. 14-27—The 14-, 21- and 28-Mc. ground-plane antenna uses wire elements. Vertical elements are taped to a cane pole; the four radials also serve as guy wires. The radials "droop" a little, making a 40-degree angle with the supporting 1-inch pipe.

venient point for bringing out the RG-8/U feed line. If it is more convenient to bring out the coax at the base of the mast, one can eliminate the T fitting and use an ordinary coupling.

A cane fishing pole supports the three separate vertical elements. These elements, made of No. 12 wire, are taped to the pole every three inches with Scotch electrical tape. The bottom end of the pole is jammed tight into the upper end of the

support pipe and the coaxial line is brought out of the pipe through a small hole just below the bottom of the flange. The inner conductor of the coaxial line is soldered to the junction of the three vertical elements and the braid of the coaxial line is connected to the pipe flange. Anyone worrying about the insulating ability of a cane pole can forget it; it is being used at a low-impedance point.

ANTENNAS FOR 160 METERS

Results on 1.8 Mc. will depend to a large extent on the antenna system and the time of day or night. Almost any random long wire that can be tuned to resonance will work during the night but it will generally be found very ineffective during the day. A vertical antenna—or rather an antenna from which the radiation is predominantly vertically polarized—is probably the best for 1.8-Mc. operation. A horizontal antenna (horizontally-polarized radiation) will give better results during the night than the day. The vertically-polarized radiator gives a strong ground wave that is effective day or night, and it is to be preferred on 1.8 Mc.

The low-angle radaition from a horizontal antenna ½ or ¼ wavelength above ground is almost insignificant. Any reasonable height is small in terms of wavelength, so that a horizontal antenna on 160 meters is a poor radiator at angles useful for long distances ("long," that is, for this band). Its chief usefulness is over relatively short distances at night.

Bent Antennas

Since ideal vertical antennas are generally out of the question for practical amateur work, the best compromise is to bend the antenna in such a way that the high-current portions of the antenna run vertically. It is advisable to place the antenna so that the highest currents in the antenna occur at the highest points above actual ground. Two antenna systems designed along these lines are shown in Fig. 14-28. The antenna of Fig. 14-28B uses a full half wavelength of wire but is bent so that the high-current portion runs vertically. The horizontal portion running to L_1C_1 should run 8 or 10 feet above ground.

Grounds

A good ground connection is generally important on 160 meters. The ideal system is a number of wire radials buried a foot or two underground and extending 50 to 100 feet from the central connection point. The use of any less than six or eight radials is inadvisable.

If the soil is good (not rocky or sandy) and generally moist, a low-resistance connection to the cold-water pipe system in the house will often serve as an adequate ground system. The connection should be made close to where the pipe enters the ground, and the surface of the pipe should be scraped shiny before tightening the

clean ground clamp around the cold-water pipe. A 6- or 8-foot length of 1-inch water pipe, driven into the soil at a point where there is considerable natural moisture, can be used for the ground connection. Three or four pipes driven into the ground 8 or 10 feet apart and all joined

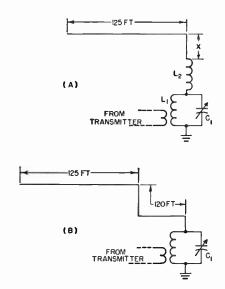


Fig. 14-28—Bent antenna for the 160-meter band. In the system at A, the vertical portion (length X) should be made as long as possible. In either antenna system, L₁C₁ should resonate at 1900 kc., roughly. To adjust L₂ in antenna A, resonate L₁C₁ alone to the operating frequency, then connect it to the antenna system and adjust L₂ for maximum loading. Furthur loading can be obtained by increasing the coupling between L₁ and the link.

together at the top with heavy wire are more effective than the single pipe.

The use of a counterpoise is recommended where a buried system is not practicable or where a pipe ground cannot be made to have low resistance because of poor soil conditions. A counterpoise consists of a number of wires supported from 6 to 10 feet above the surface of the ground. Generally the wires are spaced 10 to 15 feet apart and located to form a square or polygonal configuration under the vertical portion of the antenna.

LONG-WIRE DIRECTIVE ARRAYS

As the length (in wavelengths) of an antenna is increased, the lobes of maximum radiation make a more acute angle with the wire. Two long wires can be combined in the form of a horizontal "V", in the form of a horizontal rhombus, or in parallel, to provide a long-wire directive array. In the "V" and rhombic antennas the main lobes reinforce along a line bisecting the acute angle between the wires; in the parallel antenna the reinforcement is along the line of the lobe. This reinforcement provides both gain and directivity along the line, since the lobes in other directions tend to cancel. When the proper configuration for a given length and height above ground is used, the power gain depends upon the length (in wavelengths) of the wires.

Rhombic and "V" antennas are normally bi-

directional along the bisector line mentioned above. They can be made unidirectional by terminating the ends of the wires away from the feed point in the proper value of resistance. When properly terminated, "V" and rhombic antennas of sufficient length work well over a three-to-one or four-to-one frequency range and hence are useful for multiband operation.

Antenna gains of the order of 10 to 15 db. can be obtained with properly-constructed long-wire arrays. However, the pattern is rather sharp with gains of this order, and rhombic and "V" beams are not used by amateurs as commonly as they were, having been displaced by the rotatable multi-element Yagi beam. Further information on these antennas can be found in *The ARRL Antenna Book*.

BEAMS WITH DRIVEN ELEMENTS

By combining individual half-wave antennas into an array with suitable spacing between the antennas (called elements) and feeding power to them simultaneously, it is possible to make the radiation from the elements add up along a single direction and form a beam. In other directions the radiation tends to cancel, so a power gain is obtained in one direction at the expense of radiation in other directions. There are several methods of arranging the elements. If they are strung end to end, so that all lie on the same straight line, the elements are said to be collinear. If they are parallel and all lying in the same plane, the elements are said to be broadside when the phase of the current is the same in all, and end-fire when the currents are not in phase.

Collinear Arrays

Simple forms of collinear arrays, with the current distribution, are shown in Fig. 14-29. The

shown will result in an "X"-shaped pattern that no longer has the maximum radiation at right angles to the wire.

Collinear arrays may be mounted either horizontally or vertically. Horizontal mounting gives increased horizontal directivity, while the vertical directivity remains the same as for a single element at the same height. Vertical mounting gives the same horizontal pattern as a single eleangles.

Broadside Arrays

Parallel antenna elements with currents in phase may be combined as shown in Fig. 14-30 to form a broadside array, so named because the direction of maximum radiation is broadside to the plane containing the antennas. Again the gain and directivity depend upon the spacing of the elements.

Broadside arrays may be suspended either with the elements all vertical or with them horizontal

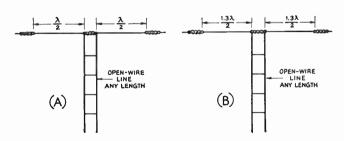



Fig. 14-29—Callinear antennas in phase. The system at A is knawn as "twa half waves in phase" and has a gain af 1.8 db. aver a half-wave antenna. By lengthening the antenna slightly, as in 8, the gain can be increased to 3 db. Maximum radiation is at right angles to the antenna. The antenna at A is sametimes called a "dauble Zepp" antenna, and that at B is knawn as an "extended dauble Zepp."


two-element array at A is popularly known as "two half-waves in phase" or a double Zepp antenna. It will be recognized as simply a center-fed dipole operated at its second harmonic.

By extending the antenna, as at B, the additional gain of an extended double Zepp antenna can be obtained. Carrying the length beyond that

and one above the other (stacked). In the former case the horizontal pattern becomes quite sharp, while the vertical pattern is the same as that of one element alone. If the array is suspended horizontally, the horizontal pattern is equivalent to that of one element while the vertical pattern is sharpened, giving low-angle radiation.

Fig. 14-30—Simple broadside array using horizontal elements. By making the spacing S equal to % wavelength, the antenna at A can be used at the corresponding frequency and up to twice that frequency. Thus when designed for 14 Mc. it can also be used on 21 and 28 Mc. The antenna at B can be used on only the design band. This array is bidirectional, with maximum radiation "broadside" or perpendicular to the antenna plane (perpendicularly through this page). Gain varies with the spacing S, running from 21/2 to almost 5 db. (See Fig. 14.32).

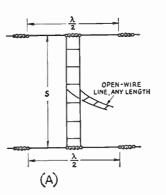

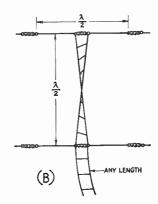

Broadside arrays may be fed either by tuned open-wire lines or through quarter-wave matching sections and flat lines. In Fig. 14-30B, note the "crossing over" of the phasing section, which is necessary to bring the elements into proper phase relationship.

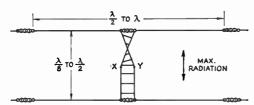


Fig. 14-31—Top view of a horizontal end-fire array. The system is fed with an open-wire line at x and y; the line can be of any length. Feed points x and y are equidistant from the two insulators, and the feed line should drop down vertically from the antenna. The gain of the system will vary with the spacing, as shown in Fig. 14-32, and is a maximum at ½ wavelength. By using a length of 33 feet and a spacing of 8 feet, the antenna will work on 20, 15 and 10 meters.

End-Fire Arrays

Fig. 14-31 shows a pair of parallel half-wave elements with currents out of phase. This is

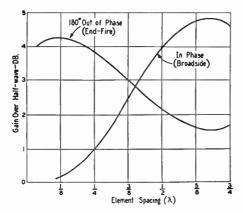


Fig. 14-32—Gain vs. spacing for two parallel half-wave elements combined as either broadside or end-fire arrays.

known as an end-fire array because it radiates best along the plane of the antennas, as shown.

The end-fire array may be used either vertically or horizontally (elements at the same height), and is well adapted to amateur work because it gives maximum gain with relatively close element spacing. Fig. 14-32 shows how the gain varies with spacing. End-fire elements may be combined with additional collinear and broadside elements to give a further increase in gain and directivity.

Either tuned or untuned lines may be used with this type of array. Untuned lines preferably are matched to the antenna through a quarter-wave matching section or phasing stub.

Combined Arrays

Broadside, collinear and end-fire arrays may be combined to give both horizontal and vertical directivity, as well as additional gain. The lower angle of radiation resulting from stacking elements in the vertical plane is desirable at the higher frequencies. In general, doubling the number of elements in an array by stacking will raise the gain from 2 to 4 db.

Although arrays can be fed at one end as in Fig. 14-30B, it is not especially desirable in the case of large arrays. Better distribution of energy between elements, and hence better overall performance will result when the feeders are attached as nearly as possible to the center of the array.

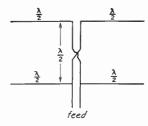


Fig. 14-33—A four-element combination broadsidecollinear array, popularly known as the "lazy-H" antenna. A closed quarter-wave stub may be used at the feed point to match into an untuned transmission line, or tuned feeders may be attached at the point indicated. The gain over a half-wave antenna is 5 to 6 db.

Parasitic Elements

A four-element array, known as the "lazy-H" antenna, has been quite frequently used. This arrangement is shown, with the feed point indicated, in Fig. 14-33. (Compare with Fig. 14-30B). For best results, the bottom section should be at least a half wavelength above ground.

It will usually suffice to make the length of each element that given by Equations 14-B or 14-C. The phasing line between the parallel elements should be of open-wire construction, and its length can be calculated from:

Length of half-wave line (feet) =

$$\frac{480}{Freq. (Mc.)}$$
 (14-H)

Example: A half-wavelength phasing line for 28.8 Mc. would be $\frac{480}{28.8} = 16.66$ feet = 16 feet 8 inches.

The spacing between elements can be made equal to the length of the phasing line. No special adjustments of line or element length or spacing are needed, provided the formulas are followed closely.

DIRECTIVE ARRAYS WITH PARASITIC ELEMENTS

Parasitic Excitation

The antenna arrays previously described are bidirectional; that is, they will radiate in directions both to the "front" and to the "back" of the antenna system. If radiation is wanted in only one direction, it is necessary to use different element arrangements. In most of these arrangements the additional elements receive power by induction or radiation from the driven element generally called the "antenna," and reradiate it in the proper phase relationship to achieve the desired effect. These elements are called parasitic elements, as contrasted to the driven elements which receive power directly from the transmitter through the transmission line.

The parasitic element is called a director when

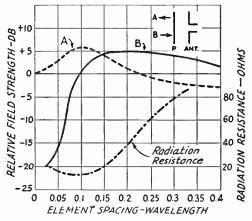


Fig. 14-34—Gain vs. element spacing for an antenna and one parasitic element. The reference point, 0 db., is the field strength from a half-wave antenna alone. The greatest gain is in direction A at spacings of less than 0.14 wavelength, and in direction B at greater spacings. The front-to-back ratio is the difference in db. between curves A and B. Variation in radiation resistance of the driven element also is shown. These curves are for a self-resonant parasitic element. At most spacings the gain as a reflector can be increased by slight lengthening of the parasitic element: the gain as a director can be increased by shortening. This also improves the front-to-back ratio.

it reinforces radiation on a line pointing to it from the antenna, and a reflector when the reverse is the case. Whether the parasitic element is a director or reflector depends upon the parasitic-element tuning, which usually is adjusted by changing its length.

Gain vs. Spacing

The gain of an antenna with parasitic elements varies with the spacing and tuning of the elements and thus for any given spacing there is a tuning condition that will give maximum gain at this spacing. The maximum front-to-back ratio seldom if ever, occurs at the same condition that gives maximum forward gain. The impedance of the driven element also varies with the tuning and spacing, and thus the antenna system must be tuned to its final condition before the match between the line and the antenna can be completed. However, the tuning and matching may interlock to some extent, and it is usually necessary to run through the adjustments several times to insure that the best possible tuning has been obtained.


Two-Element Beams

A 2-element beam is useful where space or other considerations prevent the use of the larger structure required for a 3-element beam. The general practice is to tune the parasitic element as a reflector and space it about 0.15 wavelength from the driven element, although some successful antennas have been built with 0.1-wavelength spacing and director tuning. Gain 115. element spacing for a 2-element antenna is given in Fig. 14-34, for the special case where the parasitic element is resonant. It is indicative of the performance to be expected under maximumgain tuning conditions.

Three-Element Beams

A theoretical investigation of the 3-element case (director, driven element and reflector) has indicated a maximum gain of slightly more than 7 db. A number of experimental investigations have shown that the optimum spacing between the driven element and reflector is in the region of 0.15 to 0.25 wavelength, with 0.2 wavelength representing probably the best over-all choice.

Fig. 14-35—Gain of 3-element Yagi versus director spacing, the reflector spacing being fixed at 0.2 wavelength.

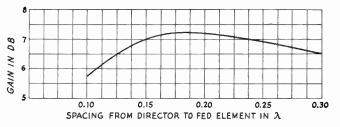

With 0.2 wavelength reflector spacing, Fig. 14-35 shows the gain variation with director spacing. It is obvious that the director spacing is not especially critical, and that the over-all length of the array (boom length in the case of a rotatable antenna) can be anywhere between 0.35 and 0.45 wavelength with no appreciable difference in gain.

Wide spacing of both elements is desirable not only because it results in high gain but also because adjustment of tuning or element length is less critical and the input resistance of the driven element is higher than with close spacing. The latter feature improves the efficiency of the antenna and makes a greater band width possible. However, a total antenna length, director to reflector, of more than 0.3 wavelength at fre-

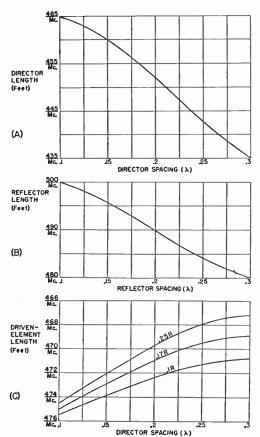


Fig. 14-36—Element lengths for a 3-element beam. These lengths will hald closely for tubing elements supported at an near the center.

quencies of the order of 14 Mc. introduces considerable difficulty from a constructional standpoint, so lengths of 0.25 to 0.3 wavelength are frequently used for this band, even though they are less than optimum.


In general, the gain of the antenna drops off less rapidly when the reflector length is increased beyond the optimum value than it does for a corresponding decrease below the optimum value. The opposite is true of a director. It is therefore advisable to err, if necessary, on the long side for a reflector and on the short side for a director. This also tends to make the antenna performance less dependent on the exact frequency at which it is operated, because an increase above the design frequency has the same effect as increasing the length of both parasitic elements, while a decrease in frequency has the same effect as shortening both elements. By making the director slightly short and the reflector slightly long, there will be a greater spread between the upper and lower frequencies at which the gain starts to show a rapid decrease.

When the over-all length has been decided upon, the element lengths can be found by referring to Fig. 14-36. The lengths determined by these charts will vary slightly in actual practice with the element diameter and the method of supporting the elements, and the tuning of a beam should always be checked after installation. However, the lengths obtained by the use of the charts will be close to correct in practically all cases, and they can be used without checking if the beam is difficult of access.

The preferable method for checking the beam is by means of a field-strength meter or the S-meter of a communications receiver, used in conjunction with a dipole antenna located at least 10 wavelengths away and as high as or higher than the beam that is being checked. A few watts of power fed into the antenna will give a useful signal at the observation point, and the power input to the transmitter (and hence the antenna) should be held constant for all of the readings. Beams tuned on the ground and then lifted into place are subject to tuning errors and cannot be depended upon. The impedance of the driven element will vary with the height above ground, and good practice dictates that all final matching between antenna and line be done with the antenna in place at its normal height above ground.

Simple Systems: the Rotary Beam

Two- and 3-element systems are popular for rotary-beam antennas, where the entire antenna

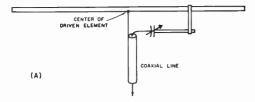

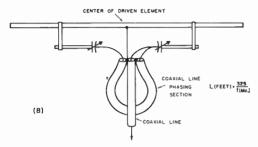


Fig. 14-37—The most popular methods of feeding the driven element of a beam antenna are (A) the gamma match and (B) the T match. The aluminum tubing or rod used for the matching section is usually of smaller diameter than the antenna element; its length will vary somewhat with the spacing and number of elements in the beam. The coaxial line in the phasing section can be coiled in a 2- or 3-foot diameter coil instead of hanging as shown.

system is rotated, to permit its gain and directivity to be utilized for any compass direction. They may be mounted either horizontally (with the plane containing the elements parallel to the earth) or vertically.

A 4-element beam will give still more gain than a 3-element one, provided the support is sufficient for about 0.2 wavelength spacing between elements. The tuning for maximum gain involves many variables, and complete gain and tuning data are not available.

The elements in close-spaced (less than onequarter wavelength element spacing) arrays preferably should be made of tubing of one-half to one-inch diameter. A conductor of large diameter not only has less ohmic resistance but also has lower Q; both these factors are important in close-spaced arrays because the impedance of the driven element usually is quite low compared to that of a simple dipole antenna. With 3- and 4-element close-spaced arrays the radiation resistance of the driven element may be so low that ohmic losses in the conductor can consume an appreciable fraction of the power.

Feeding the Rotary Beam

Any of the usual methods of feed (described later under "Matching the Antenna to the Line") can be applied to the driven element of a rotary beam. Tuned feeders are not recommended for lengths greater than a half wavelength unless open lines of copper-tubing conductors are used. The popular choices for feeding a beam are the gamma match with series capacitor and the T match with series capacitors and a half-wavelength phasing section, as shown in Fig. 14-37. These methods are preferred over any others because they permit adjustment of the matching and the use of coaxial line feed. The variable capacitors can be housed in small plastic cups for weatherproofing; receiving types with close spacing can be used at powers up to a few hundred watts. Maximum capacity required is usually 140 $\mu\mu$ f. at 14 Mc. and proportionately less at the higher frequencies.

If physically possible, it is better to adjust the matching device after the antenna has been installed at its ultimate height, since a match made with the antenna near the ground may not hold for the same antenna in the air.

Sharpness of Resonance

Peak performance of a multielement parasitic array depends upon proper phasing or tuning of the elements, which can be exact for one frequency only. In the case of close-spaced arrays, which because of the low radiation resistance usually are quite sharp-tuning, the frequency range over which optimum results can be secured is only of the order of 1 or 2 per cent of the resonant frequency, or up to about 500 kc. at 28 Mc. However, the antenna can be made to work satisfactorily over a wider frequency range by

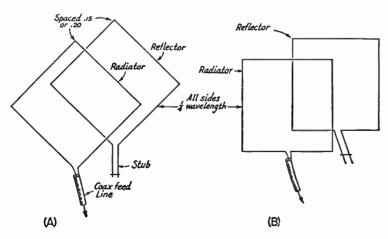


Fig. 14-38—The cubical quad antenna, consisting of two square loops one of which is driven and the other is used as a parasitic reflector. The planes of the loops are parallel, and the loops are coaxial although shown offset in these drawings for clarity. Note the difference in feed points in A and B; the shift in feed point is necessary if both loop orientations are to transmit signals of the same polarization (horizontal in both cases shown here).

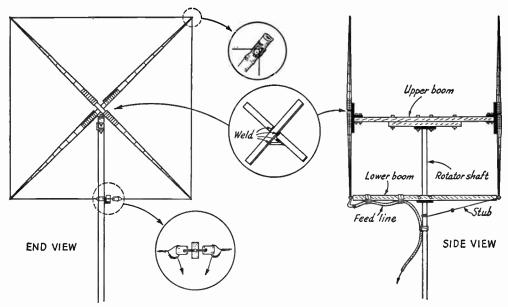


Fig. 14-39—End and side views of a quad. Upper insert shows method of fastening antenna wire to support arms. Center insert shows construction of support-arm mounting bracket. Lower insert shows method of attaching feed line and stub to the center insulators. Two small egg insulators are used, fastened to end of lower boom as shown with a small nail.


The length of one side is found from L (feet)
$$=$$
 $\frac{251}{f(\text{Mc.})}$

adjusting the director or directors to give maximum gain at the *highest* frequency to be covered, and by adjusting the reflector to give optimum gain at the *lowest* frequency. This sacrifices some gain at all frequencies, but maintains more uniform gain over a wider frequency range.

The use of large-diameter conductors will broaden the response curve of an array because the larger diameter lowers the Q. This causes the reactances of the elements to change rather slowly with frequency, with the result that the tuning stays near the optimum over a considerably wider frequency range than is the case with wire conductors.

Combination Arrays

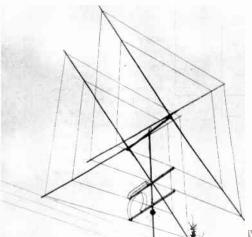It is possible to combine parasitic elements with driven elements to form arrays composed



of collinear driven and parasitic elements and combination broadside-collinear-parasitic elements. Thus two or more collinear elements might be provided with a collinear reflector or director set, one parasitic element to each driven element. Or both directors and reflectors might be used. A broadside-collinear array can be treated in the same fashion.

THE "QUAD" ANTENNA

The "cubical quad" or, simply, "quad" antenna consists of a pair of square loops, one-quarter wavelength on a side or one-wavelength around the periphery, one loop being driven and the other used as a parasitic reflector. The separation between the two is usually of the order of 0.15 to 0.2 wavelength, with the planes of the loops parallel.

Fig. 14-38 shows typical quad arrangements, that at B being the more frequently used. The reflector is tuned by means of a stub to a lower frequency than the one at which the fed loop is driven, just as is done with the conventional straight elements in a driven element-reflector array of the parasitic type. With the reflector in place and properly tuned the impedance of the driven element at the feed point is of the same order as the characteristic impedance of coaxial cable, so ordinarily the standing-wave ratio on

Fig. 14-40—A 15/10-meter quad. Tuning stubs for the reflectors are looped back along the tie bars. Total weight of this assembly, not including the mast, is 13 pounds.

World Radio History

the transmission line will be low enough so that no special means need be included for matching.

A few measurements on the quad have indicated that its gain is roughly comparable with that of a three-element Yagi of ordinary design. A number of attempts have been made to use the parasitic element as a director instead of as a reflector, and to use both a reflector and director in a three-element arrangement, these have not generally been successful; hence the driven-element-reflector combination is the one universally used.

The quad is a more cumbersome structure than an ordinary parasitic beam, but is light in weight and relatively inexpensive. Diagonal spreaders, usually of bamboo, are used to support the corners of the loop, the loop itself being made of ordinary antenna wire. The spreaders usually are mounted on a boom which in general is similar to the booms used with Yagi antennas and is also similarly mounted on the mast or tower and rotated. The light weight permits rotation by a TV rotator. Constructional details of a typical quad are given in Fig. 14-39.

If the fishing poles are well treated with a weatherproofing compound they will last several years. Weatherproofing compounds are available at all lumber dealers. Get straight poles with no splits in them. No insulators are necessary, the poles themselves acting as long insulators. The easiest way to mount the antenna wire on the arms is to lay a long length of wire on the ground

and mark it at the approximate quarter-wave intervals, and use these marks to indicate where the wire fastens to the pole.

Dual and triple quads can be built for the bands 20 through 10 meters. One such antenna is shown in Fig. 14-40, a dual quad for 15 and 10 meters. The same supporting structure is used for the two antennas, making the boom length equal to 0.15 to 0.2 wavelengths at the lower-frequency band. Separate coaxial cable feed lines are brought down from the two driven elements. In a two-band quad (20/15 or 15/10) the length of one side is obtained from

 $L ext{ (feet)} = 250 \div ext{ (Mc.)}$

In the case of any quad or combination of quads, each quad should be tuned up separately for maximum forward gain by adjusting the stub length on the reflector element and checking the field strength with a nearby ham. If accessible, the reflector element can be resonated with a grid-dip meter to a frequency just below the lowest to be used; this is a good starting place for further adjustment. The resonance of the antenna system can be checked by finding the frequency that gives the lowest s.w.r. on the feed line; this lowest s.w.r is not necessarily 1.0. If the resonant frequency is higher than the desired frequency, lengthen the driven element; shorten the element if the resonant frequency is too low. In the dual antennas that have been constructed. there has been little or no evidence of interaction of tuning.

MATCHING THE ANTENNA TO THE LINE

The load for a transmission line may be any device capable of dissipating r.f. power. When lines are used for transmitting applications the most common type of load is an antenna. When a transmission line is connected between an antenna and a receiver, the receiver input circuit (not the antenna) is the load, because the power taken from a passing wave is delivered to the receiver.

Whatever the application, the conditions existing at the load, and only the load, determine the standing-wave ratio on the line. If the load is purely resistive and equal in value to the characteristic impedance of the line, there will be no standing waves. If the load is not purely resistive, and/or is not equal to the line Z_0 , there will be standing waves. No adjustments that can be made at the input end of the line can change the s.w.r., nor is it affected by changing the line length.

Only in a few special cases is the load inherently of the proper value to match a practicable transmission line. In all other cases it is necessary either to operate with a mismatch and accept the s.w.r. that results, or else to take steps to bring about a proper match between the line and load by means of transformers or similar devices. Impedance-matching transformers may take a variety of physical forms, depending on the circumstances.

Note that it is essential, if the s.w.r. is to be made as low as possible, that the load at the point of connection to the transmission line be purely resistive. In general, this requires that the load be tuned to resonance. If the load itself is not resonant at the operating frequency the tuning sometimes can be accomplished in the matching system.

THE ANTENNA AS A LOAD

Every antenna system, no matter what its physical form, will have a definite value of impedance at the point where the line is to be connected. The problem is to transform this anenna input impedance to the proper value to match the line. In this respect there is no one "best" type of line for a particular antenna system, because it is possible to transform impedances in any desired ratio. Consequently, any type of line may be used with any type of antenna. There are frequently reasons other than impedance matching that dictate the use of one type of line in preference to another, such as ease of installation, inherent loss in the line, and so on, but these are not considered in this section.

Although the input impedance of an antenna system is seldom known very accurately, it is often possible to make a reasonably close estimate of its value. The information earlier in this chapter can be used as a guide.

Matching circuits may be constructed using ordinary coils and capacitors, but are not used very extensively because they must be supported at the antenna and must be weatherproofed. The systems to be described use linear transfomers.

The Quarter-Wave Transformer or "Q" Section

As mentioned previously (Chapter 13), a quarter-wave transmission line may be used as an impedance transformer. Knowing the antenna impedance and the characteristic impedance of the

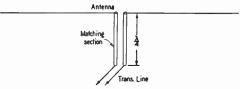


Fig. 14-41—"Q" matching section, a quarter-wave impedance transformer.

transmission line to be matched, the required characteristic impedance of a matching section such as is shown in Fig. 14-41 is

$$Z = \sqrt{Z_1 Z_0}$$
 (14-I)

where Z_1 is the antenna impedance and Z_0 is the characteristic impedance of the line to which it is to be matched.

Example: To match a 600-ohm line to an antenna presenting a 72-ohm load, the quarterwave matching section would require a characteristic impedance of $\sqrt{72 \times 600} = \sqrt{43,200} = 208$ ohms.

The spacings between conductors of various sizes of tubing and wire for different surge impedances are given in graphical form in the chapter on "Transmission Lines." (With ½-inch tubing, the spacing in the example above should be 1.5 inches for an impedance of 208 ohms.)

The length of the quarter-wave matching section may be calculated from

Length (feet) =
$$\frac{246 V}{f}$$
 (14-J)

where V = Velocity factorf = Frequency in Mc.

Example: A quarter-wave transformer of RG-11/U is to be used at 28.7 Mc. From the table in Chapter Thirteen, V=0.66.

Length
$$=\frac{246 \times 0.66}{28.7} = 5.67$$
 feet
= 5 feet 8 inches

The antenna must be resonant at the operating frequency. Setting the antenna length by formula is amply accurate with single-wire antennas, but in other systems, particularly close-spaced arrays, the antenna should be adjusted to resonance before the matching section is connected.

When the antenna input impedance is not known accurately, it is advisable to construct the matching section so that the spacing between conductors can be changed. The spacing then may be adjusted to give the lowest possible s.w.r. on the transmission line.

Folded Dipoles

A half-wave antenna element can be made to match various line impedances if it is split into two or more parallel conductors with the transmission line attached at the center of only one of them. Various forms of such "folded dipoles" are shown in Fig. 14-42. Currents in all conductors are in phase in a folded dipole, and since the conductor spacing is small the folded dipole is equivalent in radiating properties to an ordinary single-conductor dipole. However, the current flowing into the input terminals of the antenna from the line is the current in one conductor only, and the entire power from the line is delivered at this value of current. This is equivalent to saying that the input impedance of the antenna has been raised by splitting it up into two or more conductors.

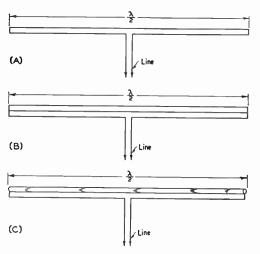


Fig. 14-42—The folded dipole, a method for using the antenna element itself to provide an impedance transformation.

The ratio by which the input impedance of the antenna is stepped up depends not only on the number of conductors in the folded dipole but also on their relative diameters, since the distribution of current between conductors is a function of their diameters. (When one conductor is larger than the other, as in Fig. 14-42C, the larger one carries the greater current.) The ratio also depends, in general, on the spacing between the conductors, as shown by the graphs of Figs. 14-43 and 14-44. An important special case is the 2-conductor dipole with conductors of equal diameter; as a simple antenna, not a part of a directive array, it has an input resistance close enough to 300 ohms to afford a good match to 300-ohm Twin-Lead.

The required ratio of conductor diameters to give a desired impedance ratio using two conductors may be obtained from Fig. 14-43. Similar information for a 3-conductor dipole is given

Folded Dipoles

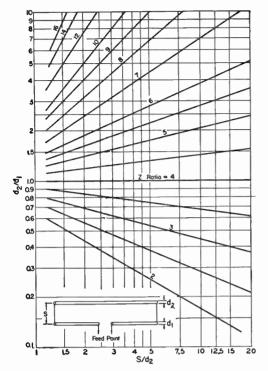


Fig. 14-43—Impedance transformation ratio, two-conductor folded dipole. The dimensions d_1 , d_2 and s are shown on the inset drawing. Curves show the ratio of the impedance (resistive) seen by the transmission line to the radiation resistance of the resonant antenna system.

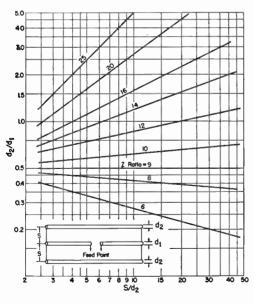


Fig. 14-44—Impedance transformation ratio, three-conductor folded dipole. The dimensions d_1 , d_2 and s are shown on the inset drawing. Curves show the ratio of the impedance (resistive) seen by the transmission line to the radiation resistance of the resonant antenna system.

in Fig. 14-44. This graph applies where all three conductors are in the same plane. The two conductors not connected to the transmission line must be equally spaced from the fed conductor, and must have equal diameters. The fed conductor may have a different diameter, however. The unequal-conductor method has been found particularly useful in matching to low-impedance antennas such as directive arrays using close-spaced parasitic elements.

The length of the antenna element should be such as to be approximately self-resonant at the median operating frequency. The length is usually not highly critical, because a folded dipole tends to have the characteristics of a "thick" antenna and thus has a relatively broad frequency-response curve.

"T" and "Gamma" Matching Sections

The method of matching shown in Fig. 14-45A is based on the fact that the impedance between any two points along a resonant antenna is resistive, and has a value which depends on the spacing between the two points. It is therefore possible to choose a pair of points between which the impedance will have the right value to match a transmission line. In practice, the line cannot be connected directly at these points because the distance between them is much greater than the conductor spacing of a practicable transmission line. The "T" arrangement in Fig. 14-45A overcomes this difficulty by using a second conductor paralleling the antenna to form a matching section to which the line may be connected.

The "T" is particularly suited to use with a parallel-conductor line, in which case the two points along the antenna should be equidistant from the center so that electrical balance is maintained.

The operation of this system is somewhat complex. Each "T" conductor (y in the drawing) forms with the antenna conductor opposite it a short section of transmission line. Each of these transmission-line sections can be considered to be terminated in the impedance that exists at the point of connection to the antenna. Thus the part of the antenna between the two points carries a transmission-line current in addition to the normal antenna current. The two transmission-line

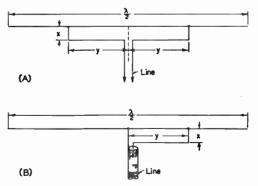


Fig. 14-45—The "T" match and "gamma" match.

matching sections are in series, as seen by the main transmission line.

If the antenna by itself is resonant at the operating frequency its impedance will be purely resistive, and in such case the matching-section lines are terminated in a resistive load. However, since these sections are shorter than a quarter wavelength their input impedance—i.e., the impedance seen by the main transmission line looking into the matching-section terminals—will be reactive as well as resistive. This prevents a perfect match to the main transmission line, since its load must be a pure resistance for perfect matching. The reactive component of the input impedance must be tuned out before a proper match can be secured.

One way to do this is to detune the antenna just enough, by changing its length, to cause reactance of the opposite kind to be reflected to the input terminals of the matching section, thus cancelling the reactance introduced by the latter. Another method, which is considerably easier to adjust, is to insert a variable capacitor in series with the matching section where it connects to the transmission line, as shown in Fig. 14-37. The capacitor must be protected from the weather.

The method of adjustment commonly used is to cut the antenna for approximate resonance and then make the spacing x some value that is convenient constructionally. The distance y is then adjusted, while maintaining symmetry with respect to the center, until the s.w.r. on the transmission line is as low as possible. If the s.w.r. is not below 2 to 1 after this adjustment, the antenna length should be changed slightly and the matching-section taps adjusted again. This process may be continued until the s.w.r. is as close to 1 to 1 as possible.

When the series-capacitor method of reactance compensation is used (Fig. 14-37), the antenna should be the proper length to be resonant at the operating frequency. Trial positions of the matching-section taps are taken, each time adjusting the capacitor for minimum s.w.r., until the standing waves on the transmission line are brought down to the lowest possible value.

The unbalanced ("gamma") arrangement in Fig. 14-45B is similar in principle to the "T," but is adapted for use with single coax line. The method of adjustment is the same.

BALANCING DEVICES

An antenna with open ends, of which the half-wave type is an example, is inherently a balanced radiator. When opened at the center and fed with a parallel-conductor line this balance is maintained throughout the system, so long as the causes of unbalance discussed in the transmission-line chapter are avoided.

If the antenna is fed at the center through a coaxial line, as indicated in Fig. 14-46A, this balance is upset because one side of the radiator is connected to the shield while the other is connected to the inner conductor. On the side connected to the shield, a current can flow down

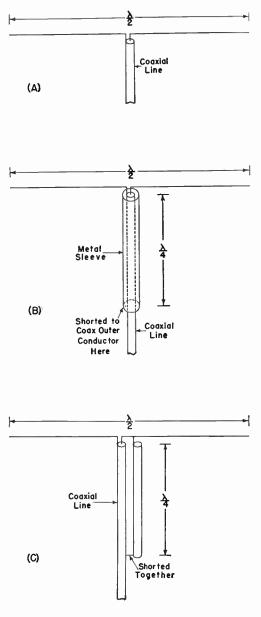




Fig. 14-46—Radiator with coaxial feed (A) and methods of preventing unbalance currents from flowing on the outside of the transmission line (B and C). The half-wave phasing section shown at D is used for coupling between an unbalanced and a balanced circuit when a 4-to-1 impedance ratio is desired or can be accepted.

Baluns

over the *outside* of the coaxial line, and the fields thus set up cannot be canceled by the fields from the inner conductor because the fields *inside* the line cannot escape through the shielding afforded by the outer conductor. Hence these "antenna" currents flowing on the outside of the line will be responsible for radiation.

Linear Baluns


Line radiation can be prevented by a number of devices whose purpose is to detune or decouple the line for "antenna" currents and thus greatly reduce their amplitude. Such devices generally are known as baluns (a contraction for "balanced to unbalanced"). Fig. 14-46B shows one such arrangement, known as a bazooka, which uses a sleeve over the transmission line to form, with the outside of the outer line conductor, a shorted quarter-wave line section. As described earlier in this chapter, the impedance looking into the open end of such a section is very high, so that the end of the outer conductor of the coaxial line is effectively insulated from the part of the line below the sleeve. The length is an electrical quarter wave, and may be physically shorter if the insulation between the sleeve and the line is other than air. The bazooka has no effect on the impedance relationships between the antenna and the coaxial line.

Another method that gives an equivalent effect is shown at C. Since the voltages at the antenna terminals are equal and opposite (with reference to ground), equal and opposite currents flow on the surfaces of the line and second conductor. Beyond the shorting point, in the direction of the transmitter, these currents combine to cancel out. The balancing section "looks like" an open circuit to the antenna, since it is a quarter-wave parallel-conductor line shorted at the far end, and thus has no effect on the normal antenna operation. However, this is not essential to the line-balancing function of the device, and baluns of this type are sometimes made shorter than a quarter wavelength in order to provide the shunt inductive reactance required in certain types of matching systems.

Fig. 14-46D shows a third balun, in which equal and opposite voltages, balanced to ground, are taken from the inner conductors of the main transmission line and half-wave phasing section. Since the voltages at the balanced end are in series while the voltages at the unbalanced end are in parallel, there is a 4-to-1 step-down in impedance from the balanced to the unbalanced side. This arrangement is useful for coupling between a balanced 300-ohm line and a 75-ohm coaxial line, for example.

RECEIVING ANTENNAS

Nearly all of the properties possessed by an antenna as a radiator also apply when it is used for reception. Current and voltage distribution, impedance, resistance and directional characteristics are the same in a receiving antenna as if it were used as a transmitting antenna. This reciprocal behavior makes possible the design of a

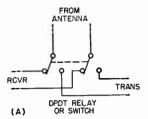

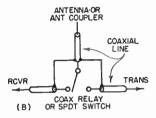


Fig. 14-47—Antenna changeover for receiving and transmitting in two-wire (A) and coaxial line (B). The lowpass filter for TVI reduction should be connected between switch or relay and the transmitter.

receiving antenna of optimum performance based on the same considerations that have been discussed for transmitting antennas.

The simplest receiving antenna is a wire of random length. The longer and higher the wire, the more energy it abstracts from the wave. Because of the high sensitivity of modern receivers, sometimes only a short length of wire strung around the room is used for a receiving antenna, but such an antenna cannot be expected to give good performance, although it is adequate for loud signals on the 3.5- and 7-Mc. bands. It will serve in emergencies, but a longer wire outdoors is always better.

The use of a tuned antenna improves the operation of the receiver, because the signal strength is greater than with a wire of random length. Where local electrical noise is a problem, as from an electrical appliance, a measure of relief can often be obtained by locating the antenna as high above and as far as possible from the noise source and power lines. The lead-in wire, from the center of the antenna, should be a coaxial line or shielded twin-conductor cable (RG-62/U). If the twin-conductor cable is used, the conductors connect to the antenna binding posts and the shield to the ground binding post of the receiver.

Antenna Switching

Switching of the antenna from receiver to transmitter is commonly done with a change-over relay, connected in the antenna leads or the coupling link from the antenna tuner. If the relay is one with a 115-volt a.c. coil, the switch or relay that controls the transmitter plate power will also control the antenna relay. If the convenience of a relay is not desired, porcelain knife switches can be used and thrown by hand.

Typical arrangements are shown in Fig. 14-47. If coaxial line is used, a coaxial relay is recom-

mended, although on the lower-frequency bands a regular switch or change-over relay will work almost as well. The relay or switch contacts should be rated to handle at least the maximum power of the transmitter. An additional refinement is the use of an electronic transmit-receive switch, which permits full break-in operation even when using the transmitting antenna for receiving. For details and circuitry on t.r. switches, see Chapter Eight.

ANTENNA CONSTRUCTION

The use of good materials in the antenna system is important, since the antenna is exposed to wind and weather. To keep electrical losses low, the wires in the antenna and feeder system must have good conductivity and the insulators must have low dielectric loss and surface leakage, particularly when wet.

For short antennas, No. 14 gauge hard-drawn enameled copper wire is a satisfactory conductor. For long antennas and directive arrays, No. 14 or No. 12 enameled copper-clad steel wire should be used. It is best to make feeders and matching stubs of ordinary soft-drawn No. 14 or No. 12 enameled copper wire, since hard-drawn or copper-clad steel wire is difficult to handle unless is under considerable tension at all times. The wires should be all in one piece; where a joint cannot be avoided, it should be carefully soldered. Open-wire TV line is excellent up to several hundred watts.

In building a two-wire open line, the spacer insulation should be of as good quality as in the antenna insulators proper. For this reason, good ceramic spacers are advisable. Wooden dowels boiled in paraffin may be used with untuned lines, but their use is not recommended for tuned lines. The wooden dowels can be attached to the feeder wires by drilling small holes and binding them to the feeders.

At points of maximum voltage, insulation is most important, and Pyrex glass or ceramic insulators with long leakage paths are recommended for the antenna. Insulators should be cleaned once or twice a year, especially if they are subjected to much smoke and soot.

In most cases poles or masts are desirable to lift the antenna clear of surrounding buildings, although in some locations the antenna will be sufficiently in the clear when strung from one chimney to another or from a housetop to a tree. Small trees usually are not satisfactory as points of suspension for the antenna because of their movement in windy weather. If the antenna is strung from a point near the center of the trunk of a large tree, this difficulty is not so serious. Where the antenna wire must be strung from one of the smaller branches, it is best to tie a pulley firmly to the branch and run a rope through the pulley to the antenna, with the other end of the rope attached to a counterweight near the ground. The counterweight will keep the tension on the antenna wire reasonably constant even when the branches sway or the rope tightens and stretches with varying climatic conditions.

Telephone poles, if they can be purchased and installed economically, make excellent supports because they do not ordinarily require guying

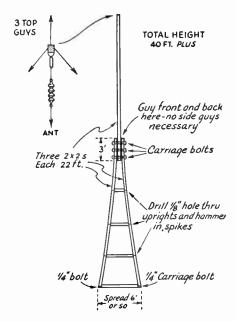


Fig. 14-48—Details of a simple 40-foot "A"-frame mast suitable for erection in locations where space is limited.


in heights up to 40 feet or so. Many low-cost television-antenna supports are now available, and they should not be overlooked as possible antenna aids.

"A"-FRAME MAST

The simple and inexpensive mast shown in Fig. 14-48 is satisfactory for heights up to 35 or 40 feet. Clear, sound lumber should be selected. The completed mast may be protected by two or three coats of house paint.

If the mast is to be erected on the ground, a couple of stakes should be driven to keep the bottom from slipping and it may then be "walked up" by a pair of helpers. If it is to go on a roof, first stand it up against the side of the building and then hoist it from the roof, keeping it vertical. The whole assembly is light enough for two men to perform the complete operation—lifting the mast, carrying it to its permanent berth, and fastening the guys—with the mast vertical all the while. It is entirely practicable, therefore, to erect this type of mast on any small, flat area of roof.

By using $2 \times 3s$ or $2 \times 4s$, the height may be extended up to about 50 feet. The 2×2 is too flexible to be satisfactory at such heights.

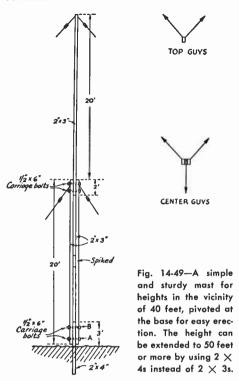

SIMPLE 40-FOOT MAST

The mast shown in Fig. 14-49 is relatively strong, easy to construct, readily dismantled, and costs very little. Like the "A"-frame, it is suitable for heights of the order of 40 feet.

The top section is a single 2×3 , bolted at the bottom between a pair of 2×3 s with an overlap of about two feet. The lower section thus has two legs spaced the width of the narrow side of a 2×3 . At the bottom the two legs are bolted to a length of 2×4 which is set in the ground. A short length of 2×3 is placed between the two legs about halfway up the bottom section, to maintain the spacing.

The two back guys at the top pull against the antenna, while the three lower guys prevent buckling at the center of the pole.

The 2×4 section should be set in the ground so that it faces the proper direction, and then made vertical by lining it up with a plumb bob. The holes for the bolts should be drilled beforehand. With the lower section laid on the ground, bolt A should be slipped in place through the three pieces of wood and tightened just enough so that the section can turn freely on the bolt. Then the top section may be bolted in place and the mast pushed up, using a ladder or another 20-foot 2×3 for the job. As the mast goes up, the slack in the guys can be taken up so that the whole structure is in some measure continually supported. When the mast is vertical, bolt B should be slipped in place and both A and Btightened. The lower guys can then be given a final tightening, leaving those at the top a little slack until the antenna is pulled up, when they

should be adjusted to pull the top section into line.

GUYS AND GUY ANCHORS

For masts or poles up to about 50 feet, No. 12 iron wire is a satisfactory guy-wire material. Heavier wire or stranded cable may be used for taller poles or poles installed in locations where the wind velocity is likely to be high.

More than three guy wires in any one set usually are unnecessary. If a horizontal antenna is to be supported, two guy wires in the top set will be sufficient in most cases. These should run to the rear of the mast about 100 degrees apart to offset the pull of the antenna. Intermediate guys should be used in sets of three, one running in a direction opposite to that of the antenna, while the other two are spaced 120 degrees either side. This leaves a clear space under the antenna. The guy wires should be adjusted to pull the pole slightly back from vertical before the antenna is hoisted so that when the antenna is pulled up tight the mast will be straight.

When raising a mast that is big enough to tax the available facilities, it is some advantage to know nearly exactly the length of the guys. Those on the side on which the pole is lying can then be fastened temporarily to the anchors beforehand, which assures that when the pole is raised, those holding opposite guys will be able to pull it into nearly vertical position with no danger of its getting out of control. The guy lengths can be figured by the right-angled-triangle rule that "the sum of the squares of the two sides is equal to the square of the hypotenuse." In other words, the distance from the base of the pole to the anchor should be measured and squared. To this should be added the square of the pole length to the point where the guy is fastened. The square root of this sum will be the length of the guy.

Guy wires should be broken up by strain insulators, to avoid the possibility of resonance at the transmitting frequency. Common practice is to insert an insulator near the top of each guy, within a few feet of the pole, and then cut each section of wire between the insulators to a length which will not be resonant either on the fundamental or harmonics. An insulator every 25 feet will be satisfactory for frequencies up to 30 Mc. The insulators should be of the "egg" type with the insulating material under compression, so that the guy will not part if the insulator breaks.

Twisting guy wires onto "egg" insulators may be a tedious job if the guy wires are long and of large gauge. A simple time- and fingersaving device (piece of heavy iron or steel) can be made by drilling a hole about twice the diameter of the guy wire about a half inch from one end of the piece. The wire is passed through the insulator, given a single turn by hand, and then held with a pair of pliers at the point shown in Fig. 14-50. By passing the wire through the hole in the iron and rotating the iron as shown, the wire may be quickly and neatly twisted.

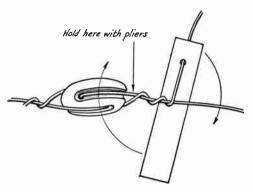


Fig. 14-50-Using a lever for twisting heavy guy wires.

Guy wires may be anchored to a tree or building when they happen to be in convenient spots. For small poles, a 6-foot length of 1-inch pipe driven into the ground at an angle will suffice.

HALYARDS AND PULLEYS

Halyards or ropes and pulleys are important items in the antenna-supporting system. Particular attention should be directed toward the choice of a pulley and halyards for a high mast since replacement, once the mast is in position, may be a major undertaking if not entirely impossible.

Galvanized-rion pulleys will have a life of only a year or so. Especially for coastal-area installations, marine-type pulleys with hardwood blocks and bronze wheels and bearings should be used.

For short antennas and temporary installations, heavy clothesline or window-sash cord may be used. However, for more permanent jobs, \(\frac{1}{3}\)eninch or \(\frac{1}{2}\)-inch waterproof hemp rope should be used. Even this should be replaced about once a year to insure against breakage.

It is advisable to carry the pulley rope back up to the top in "endless" fashion in the manner of a flag hoist so that if the antenna breaks close to the pole, there will be a means for pulling the hoisting rope back down.

BRINGING THE ANTENNA OR FEED LINE INTO THE STATION

The antenna or transmission line should be anchored to the outside wall of the building, as shown in Fig. 14-52, to remove strain from the

lead-in insulators. Holes cut through the walls of the building and fitted with feed-through insulators are undoubtedly the best means of bringing the line into the station. The holes should have plenty of air clearance about the conducting rod, especially when using tuned lines that develop high voltages. Probably the best place to go through the walls is the trimming board at the top or bottom of a window frame which provides flat surfaces for lead-in insulators. Cement or rubber gaskets may be used to waterproof the exposed joints.

Where such a procedure is not permissible,


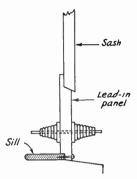


Fig. 14-51—An antenna lead-in panel may be placed over the top sash or under the lower sash of a window. Substituting a smaller height sash in half the window will simplify the weatherproofing problem where the sash

the window itself usually offers the best opportunity. One satisfactory method is to drill holes in the glass near the top of the upper sash. If the glass is replaced by plate glass, a stronger job will result. Plate glass may be obtained from automobile junk yards and drilled before placing in the frame. The glass itself provides insulation and the transmission line may be fastened to bolts fitting the holes. Rubber gaskets will render the holes waterproof. The lower sash should be provided with stops to prevent damage when it is raised. If the window has a full-length screen, the scheme shown in Fig. 14-52B may be used.

As a less permanent method, the window may be raised from the bottom or lowered from the top to permit insertion of a board which carries the feed-through insulators. This lead-in arrangement can be made weatherproof by making an overlapping joint between the board and win-

Fig. 14-52—A—Anchoring feeders takes the strain from feed-through insulators or window glass. B—Going through a full-length screen, a cleat is fastened to the frame of the screen on the inside. Clearance holes are cut in the cleat and also in the screen.

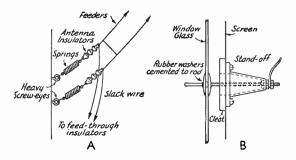

dow sash, as shown in Fig. 14-51, or by using weatherstrip material where necessary.

Coaxial line can be brought through clearance holes without additional insulation.

ROTARY-BEAM CONSTRUCTION

It is a distinct advantage to be able to shift the direction of a beam antenna at will, thus securing the benefits of power gain and directivity in any desired compass direction. A favorite method of doing this is to construct the antenna so that it can be rotated in the horizontal plane. The use of such rotatable antennas is usually limited to the higher frequencies-14 Mc. and above—and to the simpler antenna-element combinations if the structure size is to be kept within practicable bounds. For the 14-, 21and 28-Mc. bands such antennas usually consist of two to four elements and are of the parasiticarray type described earlier in this chapter. At 50 Mc. and higher it becomes possible to use more elaborate arrays because of the shorter wavelength and thus obtain still higher gain. Antennas for these bands are described in another chapter.

The problems in rotary-beam construction are those of providing a suitable mechanical support for the antenna elements, furnishing a means of rotation, and attaching the transmission line so that it does not interfere with the rotation of the system.

Elements

The antenna elements usually are made of metal tubing so that they will be at least partially self-supporting, thus simplifying the sup-

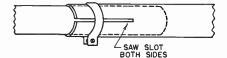


Fig. 14-53—Details of telescoping tubing for beam elements.

porting structure. The large diameter of the conductor is beneficial also in reducing resistance,

which becomes an important consideration when close-spaced elements are used.

Aluminum alloy tubes are generally used for the elements. The elements frequently are constructed of sections of telecsoping tubing making length adjustments for tuning quite easy. Electrician's thin-walled conduit also is suitable for rotary-beam elements. Regardless of the tubing used, the ends should be plugged up with corks sealed with glyptal varnish.

The element lengths are made adjustable by sawing a 6- to 12-inch slot in the ends of the larger-diameter tubing and clamping the smaller tubing inside. Homemade clamps of aluminum can be built, or hose clamps of suitable size can be used. An example of this construction is shown in Fig. 14-53. If steel clamps are used, they should be cadmium- or zinc-plated before installation.

Supports

Metal is commonly used to support the elements of the rotary beam. For 28 Mc., a piece of 2-inch diameter duraluminum tubing makes a good "boom" for supporting the elements. The elements can be made to slide through suitable holes in the boom, or special clamps and brackets can be fashioned to support the elements. Fittings for TV antennas can often be used on 21- and 28-Mc. beams. "Irrigation pipe" is a good source of aluminum tubing up to diameters of 6 inches and lengths of 20 feet. Muffler clamps can be used to hold beam elements to a boom.

Most of the TV antenna rotators are satisfactory for turning the smaller beams.

With all-metal construction, delta, "gamma" or "T"-match are the only practical matching methods to use to the line, since anything else requires opening the driven element at the center, and this complicates the support problem for that element.

"PLUMBER'S-DELIGHT" CONSTRUCTION

The lightest beam to build is the so-called "plumber's delight", an array constructed entirely of metal, with no insulating members between the elements and the supporting structure. Some suggestions for the constructional details are given in Figs. 14-54, 14-55 and 14-56. These show portions of a 4-element 10-meter beam, but the same principles hold for 15- and 20-meter beams.

Boom material can be the irrigation pipe suggested earlier (available from Sears Roebuck). Muffler clamps and homemade brackets (aluminum or cadmium-plated steel) can be used to hold the parasitic elements to the boom, as shown in Fig. 14-54. The muffler clamps and all hard-

ware should be cadmium-plated to forestall corrosion; the plating can be done at a plating shop and will not be very expensive if it is all done at the same time.

Muffler clamps and a steel plate can be used to hold the boom to the supporting mast, as shown in Fig. 14-55. For maximum strength, the mast section should be a length of galvanized iron pipe. The plate thickness should run from \(^{1}\)16 inch for a 10-meter beam to \(^{1}\)2 inch or more for a 20-meter beam. Steel plates of this thickness are best cut in a welding shop, where it can be done quickly for a nominal fee. After the plate has been cut and the muffler-clamp holes drilled, the plate, clamps and hardware should be plated.


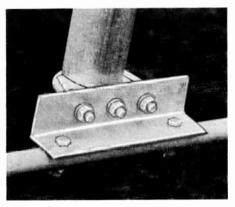


Fig. 14-54—Muffler clamps can be used to hold beam elements to the boom. The angle can be aluminum angle or angle iron; if iron is used it should be cadmium plated. This example shows a 3/4-inch-diameter element held to a 2-inch diameter boom.

The photograph in Fig. 14-56 shows one way a T-matched driven element can be assembled with its half-wave balun. Three coaxial chassis receptacles are fastened to a 1/4-inch thick sheet

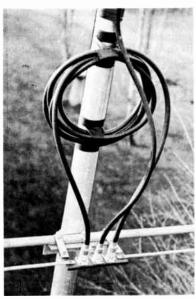

Fig. 14-55—The boom can be tied to the mast with muffler clamps and a steel plate. The coaxial line from the driven element is taped to the boom and mast.



of phenolic that is supported below the driven element by three aluminum straps. The two T rods are also supported by the phenolic sheet at the inner ends and by suitable straps at the outer ends where they make up to the driven element.

Rotation

It is convenient but not essential to use a motor to rotate the beam. If a rope-and-pulley arrangement can be brought into the operating room or if the pole can be mounted near a window in the operating room, hand rotation will work.

If the use of a rope and pulleys is impracticable, motor drive is about the only alternative. There are several complete motor driven rotators on the market, and they are easy to mount, convenient to use, and require little or no maintenance. Generally speaking, light-weight units are better because they reduce the tower load.

The speed of rotation should not be too great—one or 1½ r.p.m. is about right. This requires a considerable gear reduction from the usual 1750-r.p.m. speed of small induction motors; a large reduction is advantageous because the gear train will prevent the beam from turning in weather-vane fashion in a wind. The usual beam does not require a great deal of power for rotation at slow speed, and a ½-hp. motor will be ample. A reversible motor should be used. War-surplus "prop pitch" motors have found wide application for rotating 14-Mc. beams, while TV rotators can be used with many 28-Mc. lightweight beams.

Driving motors and gear housings will stand the weather better if given a coat of aluminum paint followed by two coats of enamel and a coat of glyptal varnish. Even commercial units will last longer if treated with glyptal varnish. Be sure that the surfaces are clean and free from grease before painting. Grease can be removed by brushing with kerosene and then squirting the surface with a solid stream of water. The work can then be wiped dry with a rag.

The power and control leads to the rotator should be run in electrical conduit or in lead covering, and the metal should be grounded.

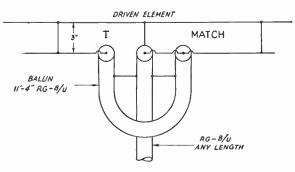


Fig. 14-56—Details of a coaxial-line termination board and T-match support for a 10-meter beam. The balun of a half-wavelength of coaxial line is coiled and then fastened to the boom with tape.

A COMPACT 14-Mc. 3-ELEMENT BEAM

A 20-meter beam no larger than the usual 10-meter beam can be made by using center-loaded elements and close spacing. Such an antenna will show good directivity and can be rotated with a TV-antenna rotator.

Constructional details of the elements are shown in Figs. 14-57 and 14-58. The loading coils are space-wound by interwinding plumb line (sometimes known as chalk line) with the No. 12 wire coils. The coil ends are secured by drilling small holes through the polystyrene bar, as shown in Fig. 14-60. The coils should be sprayed or painted with Krylon before installing the protective Lucite tubes.

The beam will require 4-foot lengths of the

clamps can be used for this purpose. The boom is a 12-foot length of 1½-inch o.d. 61ST aluminum tubing, with 0.125-inch wall.

The line is coupled and matched at the center of the driven element through adjustment of the link wound on the outside of the Lucite tubing. To check the adjustment of the elements, first resonate the driven element to the desired frequency in the 14-Mc. band with a grid-dip oscillator. Then resonate the director to approximately 14.8 Mc., and the reflector to approximately 13.6 Mc. This is not critical and only serves as rough point for the final tuning, which is done by use of a conventional field-strength indicator. Check the transmitter load-


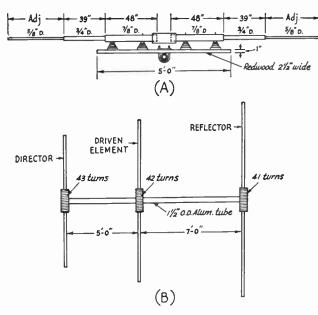


Fig. 14-57—Dimensions of a compact 14-Mc. beam. A—Side view of a typical element. TV-antenna "U" clamps hold the support arms to the boom. Birnbach 4176 insulators support the elements. B—Top plan of the beam showing element spacing and loading-coil dimensions. Elements are made of aluminum tubing. Construction of the loading coils and adjustment of the elements are discussed in the text. End-section lengths of 41 inches for the reflector, 40 inches for the director will be close to optimum.

tubings indicated in Fig. 14-57A. For good telescoping, element wall thickness of 0.058 inch is recommended. The ends of the tubing sections should be slotted to permit adjustment, and secured with clamps, so that the joints will not work loose in the wind. Perforated ground

ing and readjust if necessary. Adjust the director for maximum forward gain, and then adjust the reflector for maximum forward gain. At this point, check the driven element for resonance and readjust if necessary. Turn the reflector toward the field-strength indicator and adjust for

Fig. 14-58—Detailed sketch of the loading and coupling coils at the center of the driven element, and its mounting. Similar loading coils (see text) are used at the centers of the director and reflector.

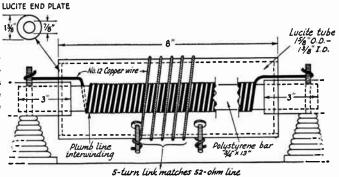

back cut-off. This must be done in small steps. Do not expect the attenuation off the sides of a short beam to be as high as that obtained with full-length elements. The s.w.r. of the line feeding the antenna can be checked with a bridge, and after the elements have been tuned, a final


adjustment of the s.w.r. can be made by adjusting the coupling at the antenna loading coil turns and spacing. As in any beam, the s.w.r. will depend upon this adjustment and not on any that can be made at the transmitter. Transmitter coupling is the usual for any coaxial line.

A "ONE-ELEMENT ROTARY" FOR 21 Mc.

The directional properties of a simple half-wavelength antenna become more apparent at higher frequencies, and it is possible to take advantage of this fact to build a "one-element rotary" for 21 or 28 Mc. To take advantage of the directional properties of the antenna, it is only

vise or by laying the end of the tubing on a hard surface and then hammering it flat. This will provide enough space to accommodate the coax fitting (Amphenol type 83-1R). A 5%-inch hole will be needed in the flat section to clear the shell of the coax fitting.

Fig. 14-59—(A) Diagram of the 21-Mc. antenna and mounting. The U-bolts that hold the 2 by 2 to the floor flange are standard 2-inch TV mast type bolts. (B) A more detailed drawing of the coil and coax-fitting mountings. The ¼-inch spacing between turns is not critical, and they can vary as much as 1/16 inch without any apparent harm to the match.

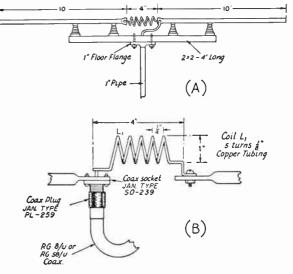

necessary to rotate it 180 degrees. It can be rotated by hand, as will be described, or by a small TV antenna rotator. A 28-Mc. antenna should be made full size (14-C) and fed at the center with RG-11/U.


The 21-Mc. antenna is made from two pieces of 1/2-inch diameter electrical thin-wall steel tubing or conduit. This tubing is readily available at any electric supply shop. It comes in 10-foot lengths and, while 20 feet is short for a halfwave antenna at 21-Mc., with loading the length is just about right for 52-ohm line feed. (A halfwavelength antenna would normally be fed with 72-ohm cable, since the antenna offers a good match for this impedance value. In this antenna system, the shorter elements, plus the small coil, offer a good match for 52-ohm cable.) If aluminum tubing is available, it can be used in place of the conduit, and the antenna will be lighter in weight. As shown in Figs. 14-59 and 14-60, the two pieces of tubing are supported by four stand-off insulators on a four-foot-long 2 by 2. The coax fitting for the feed line is mounted on the end of one of the lengths of tubing. A mounting point is made by flattening the end of the tubing for a length of about $1\frac{1}{2}$ inches. The tubing can be flattened by squeezing it in a


The coil, L_1 , is made from $\frac{1}{18}$ -inch diameter copper tubing. It consists of 5 turns spaced $\frac{1}{18}$ 4 inch apart and is 1 inch inside diameter. The coil is connected in series with the inner conductor pin on the coax fitting and the other half of the antenna. To secure a good connection at the coax fitting, the coil lead should be wound around the inner-conductor pin and soldered. The other end of the coil can be connected with a screw and nut.

Mounting

The antenna can be mounted on a 1-inch floor flange and held in place by two 2-inch bolts, as shown in Fig. 14-61. The floor flange can be connected to a 12-foot length of 1-inch pipe which will serve as a mast. Television antenna wall mounts can be used to support the mast.

In the installation shown in Fig. 14-61, 19-inch wall mounts were used in order to clear the eaves of the house. A 2-inch long piece of 1¼-inch pipe was used as a sleeve, and it was clamped in the U bolt on the bottom wall mount. A ¼-inch hole was drilled through the mast pipe approximately 6 inches from the bottom. Then a 1½-inch bolt was slipped through the hole and the mast was then mounted in the sleeve on the bottom wall mount. The bolt acted as a

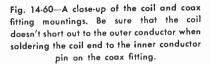

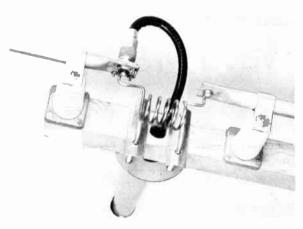

bearing point against the top of the sleeve. Another ¼-inch hole was drilled through the mast about three feet above the bottom wall mount. A piece of ¼-inch metal rod, six inches long, was forced through the hole so that the rod projected on each side of the mast. To turn the mast, a piece of rope was attached to each end

Fig. 14-61—Over-all view of the antenna and mounting.
The feedline comes out of the bottom of the mast and
through the wall into the shack.

of the rod and the rope was brought into the shack, so that the antenna could be rotated by the "arm-strong" method. Obviously, one could spend more money for a "de luxe" version and use a TV antenna rotator and mast.

RG-8/U 52-ohm coax cable is recommended to feed the antenna. For power inputs up to 100 watts, the smaller and less expensive RG-58/U can be used. However, when you buy RG-58/U, be sure that the line is made by a reputable manufacturer (such as Amphenol or Belden). Some of the line made for TV installations is of inferior quality and is likely to have higher losses. The feedline was fed up through the mast pipe and through a ¾-inch hole in the 2 by 2. An Amphenol 83-1SP fitting on the end of the coax line connects to the female fitting on the antenna.

Coupling to the Transmitter

It may be found that, when the feed line is coupled to the transmitter, the antenna won't take power. Since the line is terminated at the antenna in its characteristic impedance of 52 ohms, the output of the final r.f. amplifier must be adjusted to couple into a 52-ohm load. Where the output coupling device is a variable link, all that may be needed is the correct setting of the link. If the link is fixed, one end of the link can be grounded to the transmitter chassis and the other end of the link connected in series with a small variable capacitor to the inner conductor of the feed line. The outer conductor of the coax is grounded to the transmitter chassis. The capacitor is tuned to the point where the final amplifier is properly loaded. For transmitters having a pi-network output circuit, it is merely a matter of adjusting the network to the point where the amplifier is properly loaded.

Wave Propagation

Much of the appeal of amateur communication lies in the fact that the results are not always predictable. Transmission conditions on the same frequency vary with the year, season and with the time of day. Although these variations usually follow certain established patterns, many peculiar effects can be observed from time to time. Every radio amateur should have some understanding of the known facts about radio wave propagation so that he will stand some chance of interpreting the unusual conditions

when they occur. The observant amateur is in an excellent position to make worthwhile contributions to the science, provided he has sufficient background to understand his results. He may discover new facts about propagation at the very-high frequencies or in the microwave region, as amateurs have in the past. In fact, it is through amateur efforts that most of the extended-range possibilities of various radio frequencies have been discovered, both by accident and by long and careful investigation.

CHARACTERISTICS OF RADIO WAVES

Radio waves, like other forms of electromagnetic radiation such as light, travel at a speed of 300,000,000 meters per second in free space, and can be reflected, refracted, and diffracted.

An electromagnetic wave is composed of moving fields of electric and magnetic force. The lines of force in the electric and magnetic fields are at right angles, and are mutually per-

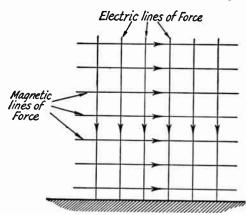


Fig. 15-1—Representation of electric and magnetic lines of force in a radio wave. Arrows indicate instantaneous directions of the fields for a wave traveling toward the reader. Reversing the direction of one set of lines would reverse the direction of travel.

pendicular to the direction of travel. A simple representation of a wave is shown in Fig. 15-1. In this drawing the electric lines are perpendicular to the earth and the magnetic lines are horizontal. They could, however, have any position with respect to earth so long as they remain perpendicular to each other.

The plane containing the continuous lines of electric and magnetic force shown by the grid-

or mesh-like drawing in Fig. 15-1 is called the wave front.

The medium in which electromagnetic waves travel has a marked influence on the speed with which they move. When the medium is empty space the speed, as stated above, is 300,000,000 meters per second. It is almost, but not quite, that great in air, and is much less in some other substances. In dielectrics, for example, the speed is inversely proportional to the square root of the dielectric constant of the material.

When a wave meets a good conductor it cannot penetrate it to any extent (although it will travel through a dielectric with ease) because the electric lines of force are practically shortcircuited.

Polarization

The polarization of a radio wave is taken as the direction of the lines of force in the electric field. If the electric lines are perpendicular to the earth, the wave is said to be vertically polarized; if parallel with the earth, the wave is horizontally polarized. The longer waves, when traveling along the ground, usually maintain their polarization in the same plane as was generated at the antenna. The polarization of shorter waves may be altered during travel, however, and sometimes will vary quite rapidly.

Spreading

The field intensity of a wave is inversely proportional to the distance from the source. Thus if in a uniform medium one receiving point is twice as far from the transmitter as another, the field strength at the more distant point will be just half the field strength at the nearer point. This results from the fact that the energy in the wave front must be distributed over a greater area as the wave moves away from the source. This inverse-distance law is based on the assumption that there is nothing in the

The lonosphere

medium to absorb energy from the wave as it travels. This is not the case in practical communication along the ground and through the atmosphere.

Types of Propagation

According to the altitudes of the paths along which they are propagated, radio waves may be classified as ionospheric waves, tropospheric waves or ground waves.

The ionospheric or **sky wave** is that part of the total radiation that is directed toward the ionosphere. Depending upon variable conditions in that region, as well as upon transmitting wave length, the ionospheric wave may or may not be returned to earth by the effects of refraction and reflection.

The tropospheric wave is that part of the total radiation that undergoes refraction and reflection in regions of abrupt change of dielectric constant in the troposphere, such as may

occur at the boundaries between air masses of differing temperature and moisture content.

The ground wave is that part of the total ra-



Fig. 15-2—Showing how both direct and reflected waves may be received simultaneously.

diation that is directly affected by the presence of the earth and its surface features. The ground wave has two components. One is the surface wave, which is an earth-guided wave, and the other is the space wave (not to be confused with the ionospheric or sky wave). The space wave is itself the resultant of two components—the direct wave and the ground-reflected wave, as shown in Fig. 15-2.

IONOSPHERIC PROPAGATION

PROPERTIES OF THE IONOSPHERE

Except for distances of a few miles, nearly all amateur communication on frequencies below 30 Mc. is by means of the sky wave. Upon leaving the transmitting antenna, this wave travels upward from the earth's surface at such an angle that it would continue out into space were its path not bent sufficiently to bring it back to earth. The medium that causes such bending is the ionosphere, a region in the upper atmosphere, above a height of about 60 miles, where free ions and electrons exist in sufficient quantity to have an appreciable effect on wave travel.

The ionization in the upper atmosphere is believed to be caused by ultraviolet radiation from the sun. The ionosphere is not a single region but is composed of a series of layers of varying densities of ionization occurring at different heights. Each layer consists of a central region of relatively dense ionization that tapers off in intensity both above and below.

Refraction

The greater the intensity of ionization in a layer, the more the path of the wave is bent. The bending, or refraction (often also called reflection), also depends on the wavelength; the longer the wave, the more the path is bent for a given degree of ionization. Thus low-frequency wayes are more readily bent than those of high frequency. For this reason the lower frequencies—3.5 and 7 Mc.—are more "reliable" than the higher frequencies—14 to 28 Mc.; there are times when the ionization is of such low value that waves of the latter frequency range are not bent enough to return to earth.

Absorption

In traveling through the ionosphere the wave gives up some of its energy by setting the ionized particles into motion. When the moving ionized particles collide with others this energy is lost. The absorption from this cause is greater at lower frequencies. It also increases with the intensity of ionization, and with the density of the atmosphere in the ionized region.

Virtual Height

Although an ionospheric layer is a region of considerable depth it is convenient to assign to it a definite height, called the virtual height. This is the height from which a simple reflection would give the same effect as the gradual

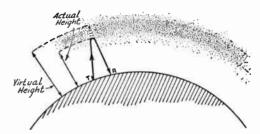


Fig. 15-3—Bending in the ionosphere, and the echo or reflection method of determining virtual height.

bending that actually takes place, as illustrated in Fig. 15-3. The wave traveling upward is bent back over a path having an appreciable radius of turning, and a measurable interval of time is consumed in the turning process. The virtual height is the height of a triangle having equal sides of a total length proportional to the time taken for the wave to travel from T to R.

Normal Structure of the lonosphere

The lowest useful ionized layer is called the *E* layer. The average height of the region of maximum ionization is about 70 miles. The air at this height is sufficiently dense so that the ions and electrons set free by the sun's radiation

do not travel far before they meet and recombine to form neutral particles, so the layer can maintain its normal intensity of ionization only in the presence of continuing radiation from the sun. Hence the ionization is greatest around local noon and practically disappears after sundown.

In the daytime there is a still lower ionized area, the *D* region. *D*-region ionization is proportional to the height of the sun and is greatest at noon. The lower amateur-band frequencies (1.8 and 3.5 Mc.) are almost completely absorbed by this layer, and only the high-angle radiation is reflected by the *E* layer. (Lower-angle radiation travels farther through the *D* region and is absorbed.)

The second principal layer is the F layer, which has a height of about 175 miles at night. At this altitude the air is so thin that recombination of ions and electrons takes place very slowly. The ionization decreases after sundown, reaching a minimum just before sunrise. In the daytime the F layer splits into two parts, the F_1 and F_2 layers, with average virtual heights of, respectively, 140 miles and 200 miles. These layers are most highly ionized at about local noon, and merge again at sunset into the F layer.

SKY-WAVE PROPAGATION

Wave Angle

The smaller the angle at which a wave leaves the earth, the less the bending required in the ionosphere to bring it back. Also, the smaller the angle the greater the distance between the point where the wave leaves the earth and that at which it returns. This is shown in Fig. 15-4. The vertical angle that the wave makes with a tangent to the earth is called the wave angle or angle of radiation.

Skip Distance

More bending is required to return the wave to earth when the wave angle is high, and at times the bending will not be sufficient unless the wave angle is smaller than some critical value. This is illustrated in Fig. 15-4, where A

and smaller angles give useful signals while waves sent at higher angles penetrate the layer and are not returned. The distance between T and R_1 is, therefore, the shortest possible distance, at that particular frequency, over which communication by ionospheric refraction can be accomplished.

The area between the end of the useful ground wave and the beginning of ionospheric-wave reception is called the **skip zone**, and the distance from the transmitter to the nearest point where the sky wave returns to earth is called the **skip distance**. The extent of the skip zone depends upon the frequency and the state of the ionosphere, and also upon the height of the layer in which the refraction takes place. The

higher layers give longer skip distances for the same wave angle. Wave angles at the transmitting and receiving points are usually, although not always, approximately the same for any given wave path.

Critical and Maximum Usable Frequencies

If the frequency is low enough, a wave sent vertically to the ionosphere will be reflected back down to the transmitting point. If the frequency is then gradually increased, eventually a frequency will be reached where this vertical reflection just fails to occur. This is the critical frequency for the layer under consideration. When the operating frequency is below the critical value there is no skip zone.

The critical frequency is a useful index to the highest frequency that can be used to transmit over a specified distance—the maximum usable frequency (m.u.f.). If the wave leaving the transmitting point at angle A in Fig. 15-4 is, for example, at a frequency of 14 Mc., and if a higher frequency would skip over the receiving point R₁, then 14 Mc. is the m.u.f. for the distance from T to R₁.

The greatest possible distance is covered when the wave leaves along the tangent to the earth; that is, at zero wave angle. Under average conditions this distance is about 4000 kilometers or 2500 miles for the F_2 layer, and 2000 km. or 1250 miles for the E layer. The distances vary with the layer height. Frequencies above these limiting m.u.f.'s will not be returned to earth at any distance. The 4000-km. m.u.f. for the F_2 layer is approximately 3 times the critical frequency for that layer, and for the E layer the 2000-km. m.u.f. is about 5 times the critical frequency.

Absorption in the ionosphere is least at the maximum usable frequency, and increases very rapidly as the frequency is lowered below the m.u.f. Consequently, best results with low power always are secured when the frequency is as close to the m.u.f. as possible.

It is readily possible for the ionospheric wave to pass through the E layer and be refracted back to earth from the F, F_1 or F_2 layers. This

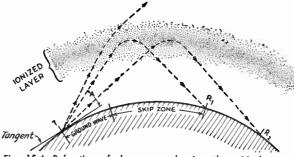


Fig. 15-4—Refraction of sky waves, showing the critical wave angle and the skip zone. Waves leaving the transmitter at angles above the critical (greater than A) are not bent enough to be returned to earth. As the angle is decreased, the waves return to earth at increasingly greater distances.

is because the critical frequencies are higher in the latter layers, so that a signal too high in frequency to be returned by the E layer can still come back from one of the others, depending upon the time of day and the existing conditions.

Multihop Transmission

On returning to the earth the wave can be reflected upward and travel again to the ionosphere. There it may once more be refracted, and again bent back to earth. This process may be repeated several times. Multihop propagation of this nature is necessary for transmission over great distances because of the limited heights of the layers and the curvature of the earth, which restrict the maximum one-hop distance to the values mentioned in the preceding section. However, ground losses absorb some of the energy from the wave on each reflection (the amount of the loss varying with the type of ground and being least for reflection from sea water), and there is also absorption in the ionosphere at each reflection. Hence the smaller the number of hops the greater the signal strength at the receiver, other things being **Fading**

Two or more parts of the wave may follow slightly different paths in traveling to the receiving point, in which case the difference in path lengths will cause a phase difference to exist between the wave components at the receiving antenna. The total field strength will be the sum of the components and may be larger or smaller than one component alone, since the phases may be such as either to aid or oppose. Since the paths change from time to time, this causes a variation in signal strength called fading. Fading can also result from the combination of single-hop and multihop waves, or the combination of a ground wave with an ionospheric or tropospheric wave.

Fading may be either rapid or slow, the former type usually resulting from rapidly-changing conditions in the ionosphere, the latter occurring when transmission conditions are relatively stable. Severe changes in signal strength of 10 to 20 db. or more are called "deep" fades, in contrast to the more normal "shallow" fades of a few db.

It frequently happens that transmission conditions are different for waves of slightly different frequencies, so that in the case of voicemodulated transmission, involving sidebands differing slightly from the carrier in frequency, the carrier and various sideband components may not be propagated in the same relative amplitudes and phases they had at the transmitter. This effect, known as selective fading, causes severe distortion of the signal. The distortion is most marked on amplitude-modulated signals and at high percentages of modulation; it is possible to reduce the effects considerably by using "exalted-carrier reception" and "singlesideband" techniques that, in effect, reduce the modulation percentage at the receiver.

Back Scatter

Even though the operating frequency is above the m.u.f. for a given distance, it is usually possible to hear signals from within the skip zone. This phenomenon, called back scatter, is caused by reflections from distances beyond the skip zone. Such reflections can occur when the transmitted energy strikes the earth at a distance and some of it is reflected back into the skip zone to the receiver. Such scatter signals are weaker than those normally propagated, and also have a rapid fade or "flutter" that makes them easily recognizable.

A certain amount of scattering of the wave also takes place in the ionosphere because the ionized region is not completely uniform. Scattering in the normal propagation direction is called forward scatter, and is responsible for extending the range of transmission beyond the distance of a regular hop, and for making communication possible on frequencies greater than the actual m.u.f.

OTHER FEATURES OF IONOSPHERIC PROPAGATION

Cyclic Variations in the lonosphere

Since ionization depends upon ultraviolet radiation, conditions in the ionosphere vary with changes in the sun's radiation. In addition to the daily variation, seasonal changes result in higher critical frequencies in the E layer in summer, averaging about 4 Mc. as against a winter average of 3 Mc. The F layer critical frequency is of the order of 4 to 5 Mc. in the evening. The F_1 layer, which has a critical frequency near 5 Mc. in summer, usually disappears entirely in winer. The daytime maximum critical frequencies for the F_2 are highest in winter (10) to 12 Mc.) and lowest in summer (around 7 Mc.). The virtual height of the F_2 layer, which is about 185 miles in winter, averages 250 miles in summer. These values are representative of latitude 40 deg. North in the Western hemisphere, and are subject to considerable variation in other parts of the world.

Very marked changes in ionization also occur in step with the 11-year sunspot cycle. Although there is no apparent direct correlation between sunspot activity and critical frequencies on a given day, there is a definite correlation between average sunspot activity and critical frequencies. The critical frequencies are highest during sunspot maxima and lowest during sunspot minima. During the period of minimum sunspot activity the lower frequencies—7 and 3.5 Mc.—frequently are the only usable bands at night. At such times the 28-Mc. band is seldom useful for long-distance work, while the 14-Mc. band performs well in the daytime but is not ordinarily useful at night.

Ionosphere Storms

Certain types of sunspot activity cause considerable disturbances in the ionosphere (iono-

sphere storms) and are accompanied by disturbances in the earth's magnetic field (magnetic storms). Ionosphere storms are characterized by a marked increase in absorption, so that radio conditions become poor. The critical frequencies also drop to relatively low values during a storm, so that only the lower frequencies are useful for communication. Ionosphere storms may last from a few hours to several days. Since the sun rotates on its axis once every 28 days, disturbances tend to recur at such intervals, if the sunspots responsible do not become inactive in the meantime. Absorption is usually low, and radio conditions good, just preceding a storm.

Sporadic-E Ionization

Scattered patches or clouds of relatively dense ionization occasionally appear at heights approximately the same as that of the *E* layer, for reasons not yet known. This **sporadic-***E* ionization is most prevalent in the equatorial regions, where it is substantially continuous. In northern latitudes it is most frequent in the spring and early summer, but is present in some degree a fair percentage of the time the year 'round. It accounts for much of the night-time short distance work on the lower frequencies (3.5 and 7 Mc.) and, when more intense, for similar work on 14 to 28 Mc. Exceptionally intense sporadic-*E* ionization permits work over distances exceeding 400 or 500 miles on the 50-Mc. band.

There are indications of a relationship between sporadic-E ionization and average sunspot activity, but it does not appear to be directly related to daylight and darkness since it may occur at any time of the day. However, there is an apparent tendency for the ionization to peak at mid-morning and in the early evening.

Tropospheric Propagation

Changes in temperature and humidity of air masses in the lower atmosphere often permit work over greater than normal ground-wave distances on 28 Mc. and higher frequencies. The effect can be observed on 28 Mc., but it is generally more marked on 50 and 144 Mc. The subject is treated in detail later.

PREDICTION CHARTS

The Central Radio Propagation Laboratory of National Bureau of Standards offers prediction charts three months in advance, by means of which it is possible to predict with considerable accuracy the maximum usable frequency that will hold over any path on the earth during a monthly period. The charts can be obtained from the Superintendent of Documents, U. S. Government Printing Office, Washington 25, D. C. for 10 cents a copy or \$1.50 per year. They are called "CRPL-D Basic Radio Propagation Predictions." The use of the charts is explained in Circular 462, "Ionospheric Radio Propagation," available for \$1.25 from the same address. This publication also contains much information of value to those who wish to pursue the subject of ionospheric propagation in more detail.

PROPAGATION IN THE BANDS BELOW 30 MC.

The 1.8-Mc., or "160-meter," band offers reliable working over ranges up to 25 miles or so during daylight. On winter nights, ranges up to several thousand miles are not impossible. Only small sections of the band are currently available to amateurs, because of the loran (navigation) service in that part of the spectrum.

The 3.5-Mc., or "80-meter," band is a more useful band during the night than during the daylight hours. In the daytime, one can seldom hear signals from a distance of greater than 200 miles or so, but during the darkness hours distances up to several thousand miles are not unusual, and transoceanic contacts are regularly made during the winter months. During the summer, the static level is high.

The 7-Mc., or "40-meter," band has many of the same characteristics as 3.5, except that the distances that can be covered during the day and night hours are increased. During daylight, distances up to a thousand miles can be covered under good conditions, and during the dawn and dusk periods in winter it is possible to work stations as far as the other side of the world, the signals following the darkness path. The winter months are somewhat better than the summer ones. In general, summer static is much less of a problem than on 80 meters, although it can be serious in the semitropical zones.

The 14-Mc., or "20-meter," band is probably the best one for long-distance work. During the high portion of the sunspot cycle it is open to some part of the world during practically all of the 24 hours, while during a sunspot minimum it is generally useful only during daylight hours and the dawn and dusk periods. There is practically always a skip zone on this band.

The 21-Mc., or "15-meter," band shows highly variable characteristics depending on the sunspot cycle. During sunspot maxima it is useful for long-distance work during a large part of the 24 hours, but in years of low sunspot activity it is almost wholly a daytime band, and sometimes unusable even in daytime. However, it is often possible to maintain communication over distances up to 1500 miles or more by sporadic-E ionization which may occur either day or night at any time in the sunspot cycle.

The 28-Mc. ("10-meter) band is generally considered to be a DX band during the daylight hours (except in summer) and good for local work during the hours of darkness, for about half the sunspot cycle. At the very peak of the sunspot cycle, it may be "open" into the late evening hours for DX communication. At the sunspot minimum the band is usually "dead" for long-distance communication, by means of the F_2 layer, in the northern latitudes. Nevertheless, sporadic-E propagation is likely to occur at any time, just as in the case of the 21-Mc. band.

There will often be exceptions to the general conditions described above, and their observation is a very interesting facet of amateur radio.

PROPAGATION ABOVE 50 MC.

The importance to the amateur of having some knowledge of wave propagation was stressed at the beginning of this chapter. An understanding of the means by which his signals reach their destination is an even greater aid to the v.h.f. worker. Each of his bands shows different characteristics, and knowledge of their peculiarities is as yet far from complete. The observant user of the amateur v.h.f. assignments has a good opportunity to contribute to that knowledge, and his enjoyment of his work will be greatly enhanced if he knows when to expect unusual propagation conditions.

CHARACTERISTICS OF THE V.H.F. BANDS

An outstanding feature of our bands from 50 Mc. up is their ability to provide consistent and interference-free communication within a limited range. All lower frequencies are subject to varying conditions that impair their effectiveness for work over distances of 100 miles or less at least part of the time, and the heavy occupancy they support results in severe interference problems in areas of dense population. The v.h.f. bands, being much wider, can handle many times the amateur population without crowding, and their characteristics for local work are more stable. It is thus to the advantage of amateur radio as a whole to make use of 50 Mc. and higher bands for short-range communication wherever possible.

In addition to reliable local coverage, the v.h.f. bands also exhibit several forms of long-distance propagation at times, and use of 50 and 144 Mc. has been taken up in recent years by many isolated amateurs who must depend on these propagation peculiarities for all or most of their contacts. It is particularly important to these operators that they understand common propagation phenomena. The material to follow supplements information presented earlier in this chapter, but deals with wave propagation only as it affects the occupants of the world above 50 Mc. First let us consider each band.

50 to 54 Mc.: This band is borderline territory between the DX frequencies and those normally employed for local work. Thus just about every form of wave propagation found throughout the radio spectrum appears, on occasion, in the 50-Mc. region. This has contributed greatly to the popularity of the 50-Mc. band.

During the peak years of a sunspot cycle it is occasionally possible to work 50-Mc. DX of world-wide proportions, by reflection of signals from the F_2 layer. Sporadic-E skip provides contacts over distances from 400 to 2500 miles or so during the early summer months, regardless of the solar cycle. Reflection from the aurora regions allows 100- to 1000-mile work during pronounced ionospheric disturbances. The everchanging weather pattern offers extension of the normal coverage to as much as 300 to 500 miles.

This develops most often during the warmer months, but may occur at any season. In the absence of any favorable propagation, the average well-equipped 50-Mc. station should be able to work regularly over a radius of 75 to 100 miles or more, depending on local terrain.

144 to 148 Mc.: Ionospheric effects are greatly reduced at 144 Mc. F_2 -layer reflection is unlikely, and sporadic-E skip is rare. Aurora DX is fairly common, but signals are generally weaker than on 50 Mc. Tropospheric effects are more pronounced than on 50 Mc., and distances covered during favorable weather conditions are greater than on lower bands. Air-mass boundary bending has been responsible for communication on 144 Mc. over distances in excess of 2500 miles, and 500-mile work is fairly common in the warmer months. The reliable range under normal conditions is slightly less than on 50 Mc., with comparable equipment.

220 Mc. and Higher: Ionospheric propagation is unlikely at 220 Mc. and up, but tropospheric bending is more prevalent than on lower bands. Amateur experience on 220 and 420 Mc. is showing that they can be as useful as 144 Mc., when comparable equipment is used. Under minimum conditions the range may be slightly shorter, but when signals are good on 144 Mc., they may be better on 220 or 420. Even above 1000 Mc. there is evidence of tropospheric DX.

PROPAGATION PHENOMENA

The various known means by which v.h.f. signals may be propagated over unusual distances are discussed below.

 F_2 -Layer Reflection: Most contacts made on 28 Mc. and lower frequencies are the result of reflection of the wave by the F_2 layer, the ionization density of which varies with solar activity, the highest frequencies being reflected at the peak of the 11-year solar cycle. The maximum usable frequency (m.u.f.) for F_2 reflection also follows other well-defined cycles, daily, monthly, and seasonal, all related to conditions on the sun and its position with respect to the earth.

At the low point of the 11-year cycle, such as in the early '50s, the m.u.f. may reach 28 Mc. only during a short period each spring and fall, whereas it may go to 60 Mc. or higher at the peak of the cycle. The fall of 1946 saw the first authentic instances of long-distance work on 50 Mc. by F_2 -layer reflection, and as late as 1950 contacts were made in the more favorable areas of the world by this medium. The rising curve of the current solar cycle again made F_2 DX on 50 Mc. possible in the low latitudes in the winter of 1955-6. DX was worked over much of the earth in the years 1956 through 1959, falling off in 1960. Loss of the 50-Mc. band to television in some countries will limit the scope of 50-Mc. DX in years to come.

The F_2 m.u.f. is readily determined by observation, and it may be estimated quite accur-

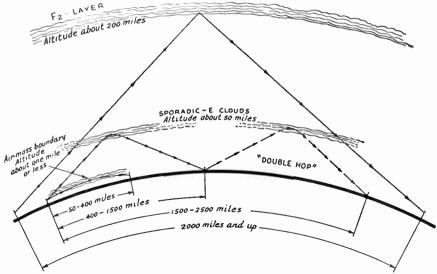


Fig. 15-5—The principal means by which v.h.f. signals may be returned to earth, showing the approximate distances over which they are effective. The F_2 layer, highest of the reflecting layers, may provide 50-Mc. DX at the peak of the 11-year sunspot cycle. Such communication may be world-wide in scope. Sporadic ionization of the E region produces the familiar "short skip" on 28 and 50 Mc. It is most common in early summer and in late December, but may occur at any time, regardless of the sunspot cycle. Refraction of v.h.f. waves also takes place at air-mass boundaries, making possible communication over distances of several hundred miles on all v.h.f. bands. Normally it exhibits no skip zone.

ately for any path at any time. It is predictable for months in advance, enabling the v.h.f. worker to arrange test schedules with distant stations at propitious times. As there are numerous commercial signals, both harmonics and fundamental transmissions, on the air in the range between 28 and 50 Mc., it is possible to determine the approximate m.u.f. by careful listening in this range. Daily observations will show if the m.u.f. is rising or falling, and once the peak for a given month is determined it can be assumed that another will occur about 27 days later, this cycle coinciding with the turning of the sun on its axis. The working range, via F2 skip, is roughly comparable to that on 28 Mc., though the minimum distance is somewhat longer. Two-way work on 50 Mc. by reflection from the F_2 layer has been accomplished over distances from 2200 to 12,000 miles. The maximum frequency for F_2 reflection is believed to be about 70 Mc.

Sporadic-E Skip: Patchy concentrations of ionization in the E-layer region are often responsible for reflection of signals on 28 and 50 Mc. This is the popular "short skip" that provides fine contacts on both bands in the range between 400 and 1300 miles. It is most common in May, June and July, during morning and early evening hours, but it may occur at any time or season. Multiple-hop effects may appear, making possible work over more than 2500 miles.

The upper limit of frequency for sporadic-E skip is not positively known, but scattered instances of 144-Mc. propagation over distances in excess of 1000 miles indicate that E-layer reflection, possibly aided by tropospheric effects, may be responsible.

Aurora Effect: Low-frequency communication is occasionally wiped out by absorption in the ionosphere, when ionospheric storms, associated with variations in the earth's magnetic field, occur. During such disturbances, however, v.h.f. signals may be reflected back to earth, making communication possible over distances not normally workable in the v.h.f. range. Magnetic storms may be accompanied by an aurora-borealis display, if the disturbance occurs at night and visibility is good. Aiming a beam at the auroral curtain will bring in signals strongest, regardless of the direction to the transmitter.

Aurora-reflected signals are characterized by a rapid flutter, which lends a "dribbling" sound to 28-Mc. carriers and may render modulation on 50- and 144-Mc, signals completely unreadable. The only satisfactory means of communication then becomes straight c.w. The effect may be noticeable on signals from any distance other than purely local, and stations up to about 1000 miles in any direction may be worked at the peak of the disturbance. Unlike the two methods of propagation previously described, aurora effect exhibits no skip zone. It is observed frequently on 50 and 144 Mc. in northeastern U. S. A., usually in the early evening hours or after midnight. The highest frequency for auroral reflection is not yet known, but pronounced disturbances have permitted work by this medium in the 220-Mc. band.

Tropospheric Bending: The most common form of v.h.f. DX is the extension of the normal operating range associated with easily observed weather phenomena. It is the result of the change in refractive index of the atmosphere at the boundary between air masses of differing


temperature and humidity characteristics. Such boundaries usually lie along the western or southern edges of a stable slow-moving area of high barometric pressure (fair, calm weather) in the period prior to the arrival of a storm.

A typical upper-air sounding showing temperature and water-vapor gradients favorable to v.h.f. DX is shown in Fig. 15-6. An increase in temperature and a sharp drop in water-vapor gradient are seen at about 4000 feet.

Such a favorable condition develops most often in the late summer or early fall, along the junction between air masses that may have come together from such widely separated points as the Gulf of Mexico and Northern Canada. Under

the 144-Mc. band may show strong signals from far beyond visual distances when lower frequencies are relatively inactive. It is probable that this tendency continues on up through the microwave range, and there is good evidence to indicate that our assignments in the u.h.f. and s.h.f. portions of the frequency spectrum may someday support communication over distances far in excess of the optical range.

Scatter: Forward scatter, both ionospheric and tropospheric, may be used for marginal communication in the v.h.f. bands. Both provide very weak but consistent signals over distances that were once thought inpossible on frequencies higher than about 30 Mc.

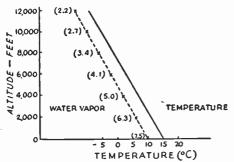

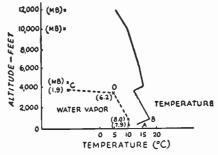


Fig. 15-6—Upper-air conditions that produce extended-range communication on the v.h.f. bands. At the left is shown the U. S. Standard Atmosphere temperature curve. The humidity curve (dotted) is that which would result if the relative humidity were 70 per cent from the ground level to 12,000 feet elevation. There is only slight refraction under this standard condition. At the right is shown a sounding that is typical of marked refraction of v.h.f. waves. Figures in parentheses are the "mixing ratio"—grams of water vapor per kilogram of dry air. Note the sharp break in bath curves at about 4000 feet. (From Collier, "Upper-Air Conditions for 2-Meter DX," QST, September, 1955.)

stable weather conditions the two air masses may retain their original character for several days at a time, usually moving slowly eastward across the country. When the path between two v.h.f. stations separated by fifty to several hundred miles lies along such a boundary, signal levels run far above the average value.

Many factors other than air-mass movement of a continental character provide increased v.h.f. operating range. The convection along coastal areas in warm weather is a good example. The rapid cooling of the earth after a hot day in summer, with the air aloft cooling more slowly, is another, producing a rise in signal strength in the period around sundown. The early morning hours, when the sun heats the air aloft, before the temperature of the earth's surface begins to rise, may be the best of the day for extended v.h.f. range, particularly in clear, calm weather.

The v.h.f. enthusiast soon learns to correlate various weather manifestations with radio-propagation phenomena. By watching temperature, barometric pressure, changing cloud formations, wind direction, visibility, and other easily-observed weather signs, he can tell with a reasonable degree of accuracy what is in prospect on the v.h.f. bands.

The responsiveness of radio waves to varying weather conditions increases with frequency. The 50-Mc. band is more sensitive to weather variations than is the 28-Mc. band, and

Tropospheric scatter is prevalent all through the v.h.f. and microwave regions, and is usable over distances up to about 400 miles. Ionospheric scatter, augmented by meteor bursts, brings in signals over 600 to 1300 miles, on frequencies up to about 100 Mc. Either form of scatter requires high power, large antennas and c.w. technique to provide useful communication.

Back scatter, of the type heard on lower bands, is also heard occasionally on 50 Mc., when F_2 or sporadic-E skip is present.

Reflections from Meteor Trails: Probably the least-known means of v.h.f. wave propagation is that resulting from the passage of meteors across the signal path. Reflections from the ionized meteor trails may be noted as a Doppler-effect whistle on the carrier of a signal already being received, or they may cause bursts of reception from stations not normally receivable. Ordinarily such reflections are of little value in communication, since the increases in signal strength are of short duration, but meteor showers of considerable magnitude and duration may provide fluttery signals from distances up to 1500 miles on both 50 and 144 Mc.

As meteor-burst signals are relatively weak, their detection is greatly aided if high power and high-gain antennas are used. Two-way communication of sorts has been carried on by this medium on 50 and 144 Mc. over distances of 600 to 1300 miles.

V.H.F. Receivers

Good receiving facilities are all-important in v.h.f. work. High sensitivity, adequate stability and good signal-to-noise ratio, necessary attributes in a receiving system for 50 Mc. and higher frequencies, are most readily attained through the use of a converter working into a communications receiver designed for lower frequencies. Though receivers and converters for the v.h.f. bands are available on the amateur market, the amateur worker can build his own with fully as good results, usually at a considerable saving in cost.

Basically, modern v.h.f. receiving equipment is little different from that employed on lower frequencies. The same order of selectivity may be used on all amateur frequencies up to at least 450 Mc. The greatest practical selectivity should be employed in v.h.f. reception, as it not only allows more stations to operate in a given band, but is an important factor in improving the signal-to-noise ratio. The effective sensitivity of a receiver having "communication" selectivity can be made much better than is possible with broadband systems.

This rules out converted radar-type receivers and others using high intermediate frequencies. The superregenerative receiver, a simple but broadband device that was popular in the early days of v.h.f. work, is now used principally for portable operation, or for other applications where high sensitivity and selectivity are not of prime importance. It is capable of surprising performance, for a given number of tubes and components, but its lack of selectivity, its poor signal-to-noise ratio, and its tendency to radiate a strong interfering signal have eliminated the superregenerator as a fixed-station receiver in areas where there is appreciable v.h.f. activity.

R. F. AMPLIFIER DESIGN

The noise generated within the receiver itself is an important factor in the effectiveness of v.h.f. receiving gear. At lower frequencies, and to a considerable extent on 50 Mc., external noise is a limiting factor. At 144 Mc. and higher the receiver noise figure, gain and selectivity determine the ability of the system to respond to weak signals. Proper selection of r.f. amplifier tubes and appropriate circuit design aimed at low noise figure are more important in the v.h.f. receiver "front end" than mere gain.

Triode or Pentode?

Certain triode tubes have been developed with this end in view. Their superiority over

pentode types is more pronounced as we go higher in frequency. Because of the limitation on sensitivity imposed by external noise at that frequency, triode or pentode r.f. amplifiers give about the same results at 50 Mc. Thus the pentode types, which offer the advantages of better selectivity and simpler circuitry, are often used for 50-Mc. work. But at 144 Mc., the newer triodes designed for r.f. amplifier service give fully as much gain as the pentodes, and with lower internal noise. With the exception of the simplest unit, the equipment described in the following pages incorporates low-noise r.f. amplifier techniques.

Neutralizing Methods

When triodes are used as r.f. amplifiers some form of neutralization of the grid-plate capacitance is required. This can be capacitive, as is commonly used in transmitting applications, or inductive. The alternative to neutralization is the use of grounded-grid technique. Circuits for v.h.f. triode r.f. amplifier stages are given in Figs. 16-1 through 16-4.

A dual triode operated as a neutralized pushpull amplifier is shown at 16-1. This arrange-

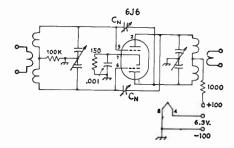


Fig. 16-1—Schematic diagram of a push-pull r.f. amplifier for v.h.f. applications. This circuit is well-suited to use with antenna systems having balanced lines. Coil and capacitor values not given depend on the frequency at which the amplifier is to be used. Neutralizing capacitance, Cx, may be built up by twisting ends of insulated leads together.

ment is well adapted to v.h.f. preamplifier applications, or as the first stage in a converter, particularly when a balanced transmission line such as the popular 300-ohm Twin-Lead is used. It is relatively selective and may require resistive loading of the plate circuit, when used as a preamplifier. The loading effect of the following circuit may be sufficient to give the required

R. F. Amplifier Design

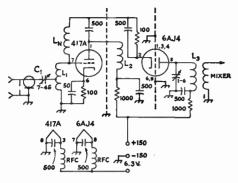


Fig. 16-2—Circuit af the cascade r.f. amplifier. Caupling capacitar, C_1 , may be amitted if spuriaus receiver responses are not a problem. Neutralizing winding, $L_{\rm N}$ should resonate at the signal frequency with the gridplate capacitance of the first tube. Base cannections are far 417A and 6AJ4, but ather small triades may be used.

band width, when the push-pull stage is inductively coupled to the mixer.

A triode amplifier having excellent noise figure and broadband characteristics is shown in Fig. 16-2. Commonly called the cascode, it uses a triode or triode-connected pentode followed by a triode grounded-grid stage. This circuit is extremely stable and uncritical in adjustment. At 50 Mc. and higher its over-all gain is at least equal to the best single-stage pentode amplifier and its noise figure is far lower.

Neutralization is accomplished by the coil LN, whose value is such that it resonates at the signal frequency with the grid-plate capacitance of the tube. Its inductance is not critical; it may be omitted from the circuit without the stage going into oscillation, but neutralization results in a lower noise figure than is possible without it. Any of several v.h.f. tubes may be used in the cascode circuit. The example shown in Fig. 16-2 uses the 417A, followed by a 6AJ4. Two 6AJ4s would work almost equally well, as would the 6AM4, 6AN4 and 6BC4. Pin connections in Fig. 16-2 should be changed to suit the tubes selected.

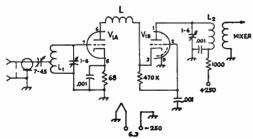


Fig. 16-3—Simplified cascade circuit far use with dual triades having separate cathodes. Cail and capacitance values nat given depend an frequency. Bifilar r.f. chakes are accasianally used in heater leads. L matches impedances between tubes and impraves averall naise figure.

A simplified version of the cascode, using a dual triode tube designed especially for this application, is shown in Fig. 16-3. By reducing stray capacitance, through direct coupling between the two triode sections, this circuit makes for improved performance at the frequencies above 100 Mc. The two sections of the tube are in series, as far as plate voltage is concerned, so it requires higher voltage than the other circuits shown.

The neutralization process for the cascode and neutralized-triode amplifiers is somewhat similar. With the circuit operating normally the neutralizing adjustments (capacitance of CN in Fig. 16-1; inductance of LN in Fig. 16-2) can be set for best signal-to-noise ratio. The best results are obtained using a noise generator, adjusting for lowest noise figure, but careful adjustment on a weak signal provides a fair approximation. Noise generators and their use in v.h.f. receiver adjustment are treated in July, 1953, QST, p. 10, and in this Handbook, Chapter 21.

Grounded-grid r.f. amplifier technique is illustrated in Figs. 16-4 and 16-25. Here the input is in the cathode lead, with the grid of the tube grounded, to act as a shield between cathode and plate. The grounded-grid circuit is stable and easily adjusted, and is well adapted to broadband applications. The gain per stage is low, so that two or more stages may be required.

Tubes well-suited to grounded-grid amplifier service include the 6J4, 6AN4, 6AJ4, 6AM4, 6BC4, 417A and 416B. Disk-seal tubes such as the "lighthouse" and "pencil tube" types are often used as r.f. amplifiers above 500 Mc., and the new ceramic tubes show great possibilities for r.f. amplifier service in the u.h.f. range.

Great care should be used in adjusting the r.f. portion of a v.h.f. receiver, whatever circuit is used. If it is working properly it will control the noise figure of the entire system.

Reducing Spurious Responses

In areas where there is a high level of v.h.f. activity or extensive use of other frequencies in the v.h.f. range, the ability of the receiver to operate properly in the presence of strong signals may be an important consideration. Special tube types, otherwise similar to older numbers, have been developed for low overload and cross-modulation susceptibility. The 6BC8, which may be used as a replacement for the 6BQ7A or 6BZ7, is one of these.

Modification of the converter design can also improve performance in these respects. In general, the gain ahead of the mixer stage should be made no more than is necessary to achieve good noise figure characteristics. The plate voltage on the r.f. amplifier should be kept as high as practical, to prevent easy overloading.

Rejection of signals outside the desired frequency range can be improved by the use of high-Q tuned circuits ahead of the first r.f. amplifier stage. Television transmitters are particularly troublesome in this respect, and one or

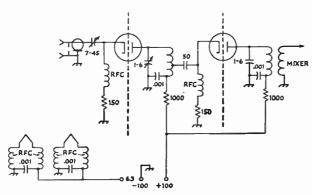


Fig. 16-4—Grounded-grid amplifier. Position of tap on plate coil should be adjusted for lowest noise figure. Low gain with this circuit makes two stages necessary for most applications. R.f. choke and coil values depend on frequency.

more coaxial-type circuits inserted in the lead from the antenna to the converter may be necessary to keep such signals from interfering with normal reception.

A common cause of unwanted signals appearing in the tuning range is the presence of oscillator harmonics in the energy being fed to the mixer of a crystal-controlled converter. This may be prevented by using a high oscillator frequency, to keep down the number of multiplications, and by shielding the oscillator and multiplier stages from the rest of the converter.

Signals at the intermediate frequency may ride through a converter. This can be prevented by keeping down capacitive interstage coupling in the r.f. circuitry, and by shielding the converter and the receiver antenna terminals. The problem of receiver responses is dealt with in QST for April, 1955, p. 56, and February, 1958, p. 27.

MIXER CIRCUITS

The mixer in a v.h.f. converter may be either a pentode or a triode tube. Pentodes give generally higher output, and may require less injection. When used without a preceding r.f. amplifier stage, the triode mixer may provide a better noise figure. With either tube, the grid circuit is tuned to the signal frequency, and the plate circuit to the intermediate frequency.

A simple triode mixer is shown in Fig. 16-5A, with a pentode mixer at B. A dual-triode version (push-push mixer) is shown at C. The push-push mixer is well adapted to use at 420 Mc., and may, of course, be used at any lower frequency. Dual tubes may be used as both mixer and oscillator, combining the circuits of Figs. 16-5 and 16-6. A 6U8 could use its pentode as a mixer (16-5B) and the oscillator portion (16-6A) would be a triode. Dual-triode tubes (6]6, 12AT7 and many others) would combine 16-5A and 16-6A. In dual triodes having separate cathodes some external coupling may be required, but the common cathode of the 6J6 will provide sufficient injection in most cases. If the injection is more than necessary it can be reduced by dropV.H.F. Receivers

ping the oscillator plate voltage, either directly or by increasing the value of the dropping resistor.

A pentode mixer is less subject to oscillator pulling than a triode, and it will probably require less injection voltage. In a pentode mixer with no r.f. amplifier, plate current should be held to the lowest usable value, to reduce tube noise. This may be controlled by varying the mixer screen voltage. When a good r.f. amplifier is used the mixer plate current may be run higher, for better operation with strong signals.

Occasionally oscillation near the signal frequency may be encountered in v.h.f. mixers. This usually results from stray lead inductance in the mixer plate circuit, and is

most common with triode mixers. It may be corrected by connecting a small capacitatice from plate to cathode, *directly* at the tube socket. Ten to 25 $\mu\mu$ f. will be sufficient, depending on the signal frequency.

OSCILLATOR STABILITY

When a high-selectivity i.f. system is employed in v.h.f. reception, the stability of the oscillator is extremely important. Slight variations in oscillator frequency that would not be noticed when a broadband i.f. amplifier is used become intolerable when the passband is reduced to crystal-filter proportions.

One satisfactory solution to this problem is the use of a crystal-controlled oscillator, with frequency multipliers if needed, to supply the



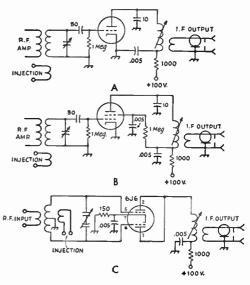


Fig. 16-5—Typical v.h.f. mixer circuits for triode (A), pentode (B) and push-push triode (C). Circuits A and B may be used with one portion of various dual-purpose tubes. Plate current of pentode (B) should be held at lowest usable value if no r.f. stage is used.

Fig. 16-6 — Recammended ascillator circuits for tunable v.h.f. converters. Dual-triode-version (B) is recommended far 220 or 420 Mc. R.f. choke coil and capacitor values not given depend on frequency.

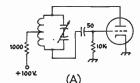

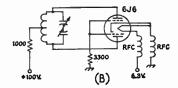

injection voltage. Such a converter usually employs one or more broadband r.f. amplifier stages, and tuning is done by tuning the receiver with which the converter is used to cover the desired intermediate frequency range.

When a tunable oscillator and a fixed intermediate frequency are used, special attention must be paid to the oscillator design, to be sure that it is mechanically and electrically stable. The tuning capacitor should be solidly built, preferably of the double-bearing type. Split-stator capacitors specifically designed for v.h.f., service, usually having ball-bearing end plates and special construction to insure short leads, are well worth their extra cost. Leads should be made with stiff wire, to reduce vibration effects. Mechanical stability of air-wound coils can be improved by tying the turns together with narrow strips of household cement at several points.

Recommended oscillator circuits for v.h.f. work are shown in Fig. 16-6. The single-ended oscillator may be used for 50 or 144 Mc. with good results. The push-pull version is recommended for higher frequencies and may also be used on the two lower bands, as well. Circuit A works well with almost any small triode, or one half of a 6J6 or 12AT7. The 6J6 is well suited to push-pull applications, as shown in circuit 16-6B.

THE I.F. AMPLIFIER

Superheterodyne receivers for 50 Mc. and up should have fairly high intermediate frequencies, to reduce both oscillator pulling and image response. Approximately 10 per cent of the signal frequency is commonly used, with 10.7 Mc. being set up as the standard i.f. for commercially-built f.m. receivers. This particular frequency has a disadvantage for 50-Mc. work, in that it makes the receiver subject to image response from 28-Mc. signals, if the oscillator is on the low side of the signal frequency. A spot around 7 Mc. is favored for amateur converter service, as practically all communications receivers are capable of tuning this range.

For selectivity with a reasonable number of i.f. stages, double conversion is usually employed in complete receivers for the v.h.f. range. A 7-Mc. intermediate frequency, for instance, is changed to 455 kc., by the addition of a second mixer-oscillator. This procedure is, of course, inherent in the use of a v.h.f. converter ahead of a communications receiver.

If the receiver so used is lacking in sensitivity, the over-all gain of the converter-receiver combination may be inadequate. This can be corrected by building an i.f. amplifier stage into the converter itself. Such a stage is useful even when the gain of the system is adequate without it, as the gain control can be used to permit operation of the converter with receivers of widely different performance. If the receiver has an S-meter, its adjustment may be left in the position used for lower frequencies, and the converter gain set so as to make the meter read normally on v.h.f. signals.


Where reception of wide-band f.m. or unstable signals of modulated oscillators is desired, a converter may be used ahead of an f.m. broadcast receiver. A superregenerative detector operating at the intermediate frequency, with or without additional i.f. amplifier stages, also may serve as an i.f. and detector system for reception of wide-band signals. By using a high i.f. (10 to 30 Mc. or so) and by resistive loading of the i.f. transformers, almost any desired degree of bandwidth can be secured, providing good voice quality on all but the most unstable signals. Any of these methods may be used for reception in the microwave region, where stabilized transmission is extremely difficult at the current state of the art.

THE SUPERREGENERATIVE RECEIVER

The simplest type of v.h.f. receiver is the superregenerator. It affords fair sensitivity with few tubes and elementary circuits, but its weaknesses, listed earlier, have relegated it to applications where small size and low power consumption are important considerations.

Its sensitivity results from the use of an alternating quenching voltage, usually in the range between 20 and 200 kc., to interrupt the normal oscillation of a regenerative detector. The regeneration can thus be increased far beyond the amount usable in a straight regenerative circuit. The detector itself can be made to furnish the quenching voltage, or a separate oscillator tube can be used. Regeneration is usually controlled by varying the plate voltage in triode detectors, or the screen voltage in the case of pentodes. A typical circuit is shown in Fig. 16-7.

Fig. 16-7—Superregenerative detector circuit for self-quenched detector. Pentode tube may be used, varying screen voltage by means of the potentiometer to control regeneration.

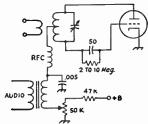

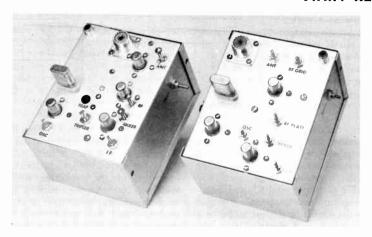


Fig: 16-8—The 50- and 144-Mc. crystal-controlled converters are built in 3 \times 4 \times 5-inch Miniboxes and are designed to work into a receiver that tunes 14 to 18 Mc. Plate voltage required is +150, and use of a 0D3-stabilized supply is suggested.

CRYSTAL-CONTROLLED CONVERTERS FOR 50, 144 AND 220 Mc.

The three converters shown in Figs. 16-8 through 16-15 are designed to be used with a receiver that tunes 14 to 18 Mc. (14 to 19 Mc. for the 220-Mc. converter.). Designed around

the "Nuvistor" miniature triode and a crystalcontrolled local-oscillator signal, they offer low noise figures and high stability on the three bands. The power-supply requirement is 150

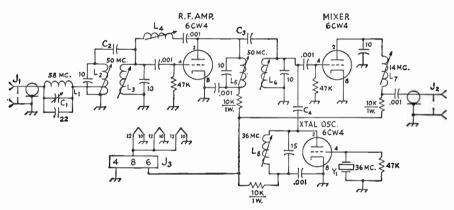


Fig. 16-9—Schematic diagram and parts information for the 50-Mc. converter. Resistors ½ watt unless specified. Fixed copacitors are ceramic; decimal values in μf., others in μμf.

 C_1 -3-30- $\mu\mu$ f, mica trimmer.

C₂, C₃—No. 22 insulated hookup wires 2 inches long, twisted together for approximately 1½ inches.

C4-Same, but 1-inch wires twisted for 1/2 inch.

J₁—Coaxial connector, SO-239.

J₂—Phono jack.

J₃-8-pin plug (Amphenol 86-RCP8).

L₁-5 turns No. 18, ½-inch diom., 8 t.p.i. (B & W No. 3002).

 L_2 —10 turns No. 28 enam., close-wound on V_4 -inch ironslug phenolic form, tapped ot 3 turns; 0.65 to 1.3 μ h. (Miller form No. 20A000RBI).

Ls, La, La—8 turns No. 28 enam., close-wound on ¼-inch iron-slug phenolic form. Range 0.43 to 0.85 $\mu h.$ L_{8} set for 0.64 $\mu h.$, L_{5} for 0.66, L_{6} for 0.73 $\mu h.$ (Miller coils No. 20A687RBI). L_{2} and L_{8} are % inch opart c. to c. L_{5} to L_{6} is % inch; L to L_{8} is % inch.

L₄—No. 32 enam., close-wound ½ inch on ¼-inch ironslug phenolic form; 3.8 to 8.5 μh., set for 6.9 μh. (Miller coil No. 20A686RBI).

L₇—Universal-wound coil, 4.7 to 10 μh., set for 7.9 μh. (Miller coil No. 20A826RBI).

L₈—8 turns No. 32 enam., close-wound on ¼ inch ironslug phenolic form; 0.67 to 1.25 μh., set for 0.94 μh. (Miller coil No. 20A106RBI).

Y1-36-Mc. crystal (International Crystal Mfg. Co. FA-5).

volts for the plate-power source (preferably stabilized, by a 0D3) and 6.3 volts for the heaters. A suitable power-supply circuit is given in Fig. 16-16.

At 50 Mc. noise coming in on the antenna is a limiting factor, even in the quietest location. This antenna noise is much lower on 144 and 220 Mc. At 50 Mc. one r.f. stage gives all the sensitivity that can be used, but at 144 and 220 Mc. a "cascode" stage using two tubes is needed to approach the point where antenna noise is the limiting factor.

The 50-Mc. Converter

The 50-Mc. converter is shown at the right in Fig. 16-8, and the circuit is given in Fig. 16-9. Referring to Fig. 16-8 (right), the oscillator

tube and crystal are at the left, and the r.f. stage is at the top, near the input connector. Turning to the circuit diagram, Fig. 16-9, it will be seen that two tuned circuits are used between antenna and r.f. grid, and two more tuned circuits are used to couple the r.f. stage to the mixer. The trap circuit, L_1C_1 is optional. Its purpose is to reject Channel-2 video signals that might cause interference to 50-Mc. reception, as the result of the second harmonic of the oscillator (72 Mc.) beating with a Channel-2 TV signal. There is no need for the trap if there is no Channel-2 TV station in the vicinity, and the lead from J_1 should then be run directly to the tap on L_2 .

An overtone crystal of the type that needs no special circuit is used in the oscillator, and the oscillator signal is coupled to the mixer through

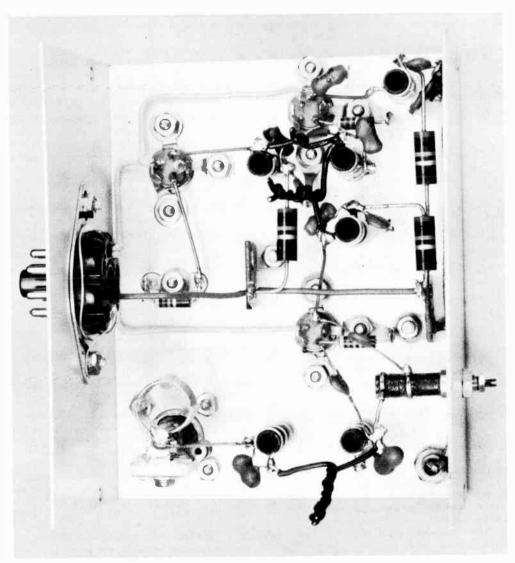


Fig. 16-10—Bottom view of the 50-Mc. converter. The antenna connector and trap circuit are in the lawer left corner. The neutralizing cail, L_4 , is mounted horizontally, at lower right.

a small capacitor made by twisting two insulated wires.

A good idea of the parts arrangement can be obtained from the bottom view, Fig. 16-10. The input coils, L_2 and L_3 , are to the right of the antenna connector, and the output jack, J_2 , is to the right of L_3 . The output coil, L_7 , is at the top right of the picture, and a shielded wire is run from the coil (actually from the 0.001- μ f. capacitor) to the output jack.

Nuvistor sockets have two small tabs on them that are bent against the underside of the chassis after they have been installed. The tabs require that clearance slots be filed for them after the ½-inch hole for the socket has been drilled or punched. Note in Fig. 16-10 that these tabs are clamped to the chassis by washers held to the chassis by 4-40 hardware.

When the converter is completed, the tubes should be plugged in and a power supply (any 150-volt d.c. and 6.3-volt a.c. source; see Fig. 16-16) connected at J_s through a mating cable plug (Amphenol 78-PF8). With all the tubes in place, and the crystal, the oscillator should be checked first. A voltmeter connected between chassis and the junction of L_8 and the 10,000-

ohm resistor will indicate about 70 to 90 volts with the oscillator oscillating, and it should drop back to about 50 volts when there is no oscillation. Start with the core in L_8 unscrewed (closest to chassis) and slowly run it in while watching the voltmeter. The voltage should rise to about 90 volts and then drop suddenly. Set the core for the highest voltmeter reading (lowest oscillator plate current) at which the oscillator will start each time power is applied. If a wavemeter is available, check the frequency of oscillation to see that it is 36 Mc.

The 50-Mc. converter is now ready to receive strong signals, as soon as it is connected to the receiver. Make up a cable of any small coax, putting a phono-pin plug on one end. The other end connects to the receiver antenna terminals. This may require a coax fitting for some receivers, but most have screw terminals. Connect the inner conductor to the antenna terminal and the outer sheath to the ground terminal or the receiver chassis. Do this with the shortest possible leads, to keep down pickup of signals at 14 Mc.

Now a 50-Mc. signal is needed. This can be from a grid-dip oscillator, a nearby 50-Mc. station, the harmonic of a transmitter, or ideally, a

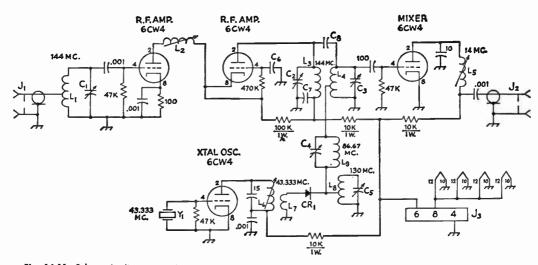


Fig. 16-11—Schematic diagram and parts information for the 144-Mc. converter. Resistors $\frac{1}{2}$ watt unless specified. Fixed capacitors are ceramic unless specified. Decimal values in μ f., others in μ μ f.

 C_1 , C_2 , $C_3-1-7.5-\mu\mu$ f. ceramic trimmer (Centralab 829-7).

C₄-4-30-μμf. ceramic trimmer (Mallory ST-554-N).

C₅–20- $\mu\mu$ f. miniature variable (Hammarlund MAC-20). C₆, C₇ – 0.001- μ f. button-type bypass (Centralab

Ce, C₇ — 0.001-\(\mu\)f. button-type bypass (Centralab ZA-102). Do not use disk-ceramic or other wire-lead capacitors for these points.

C₈—No. 22 insulated hookup wires 11/4 inches long, twisted together for approximately 1 inch.

CR1—Crystal-diode rectifier; 1N82.

J₁—Coaxial connector, SO-239.

J_Phono jack.

J₈-8-pin plug (Amphenol 86-RCP8).

L₁, L₈-6 turns No. 18, ¼-inch diam. ½ inch long. Tap at 2½ turns.

L₂—5 turns No. 28 ename!, close-wound on ¼-inch ironslug form. Range 0.24 to 0.41 μh., set for 0.33 μh. (Miller coil No. 20A337RBI).

L₃-6½ turns No. 18, ¼-inch diam., % inch long.

L₄—5 turns like L₃, ½ inch long, tapped at 2 turns. L₈ and L₄ are parallel, ¾ inch apart, c. to c.

Ls—Universal-wound coil, 4.7 to 10 μh., set for 7.9 μh. (Miller coil No. 20A826RBI).

L₆—9 turns No. 28 enamel, close-wound on ¼-inch iron-slug form. Range 0.58 to 1 μh., set for 0.82 μh. (Miller coil No. 20A827RBI).

 $L_7-1\frac{1}{2}$ turns insulated hookup wire around L_6 .

Lo-8 turns No. 18, 14-inch diam., % inch long.

Y₁—43.333-Mc. crystal (International Crystal Mfg. Co. FA-5).

good signal generator. For any except the last, connect some kind of antenna to J_1 . A short piece of wire will do at first, and the length can be varied to suit the strength of the signal. Set the stud in L_4 at about the middle of its range. Next, peak the screws in L_2 , L_3 , L_5 , L_6 and L_7 for maximum signal strength. Now disable the r.f. amplifier stage by disconnecting the 10,000-ohm resistor from L_5 , or by removing the heater lead from Pin 12 of the socket. Adjust L_4 for minimum signal. Replace the heater or plate voltage and readjust all coils except L_4 for maximum signal again.

The converter should be close to optimum performance if everything has been done properly to this point. If the Channel 2 trap is used, adjust it so that no interference is heard from the local TV station. If the station is very near by,

it may still be heard as long as the cover is off the converter case. It should disappear when the case is assembled. Recheck the adjustment of $L_{\rm a}$ and $L_{\rm a}$ after final adjustment of the trap.

Further work to improve weak-signal reception should be done with a noise generator, though satisfactory results can be obtained on weak signals if the work is done with care. The aim should be better signal-to-noise ratio, rather than merely greater signal strength. Using the receiver S meter, or the audio sound of a weak signal, tune for maximum signal with respect to noise.

As a final check, put a 50-ohm resistor across J_1 . Observe the noise level. Now remove the resistor and put on an antenna system with 50-ohm feed. If the noise rises appreciably, this external noise is the limiting factor in v.h.f. recep-

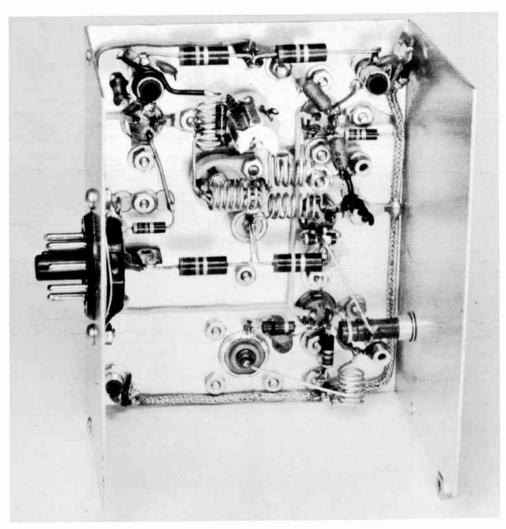


Fig. 16-12—Interior of the 144-Mc. converter. Details of parts arrangement are given in the text. The i.f. output from the mixer plate coil, L₅, (upper right) is brought through a shielded lead down the side and across the bottom to the output connector, J₂, at the lower left.

tion, and the only improvement one can make from here on is to put up a bigger or higher antenna, or move to a quieter location.

The 144-Mc. Converter

The 144-Mc. converter, Figs. 16-8 and 16-12. uses a two-tube "cascode" r.f. amplifier ahead of the mixer, and a frequency-multiplying system is required to provide the desired 130-Mc. local-oscillator signal. Handwound coils are used in the r.f. circuits, instead of slug-tuned coils, with the exception of the matching reactance (L2 in Fig. 16-11) which must be adjusted for best noise figure. The crystal oscillator works on 43.333 Mc. and drives a crystal-diode frequency tripler to 130 Mc. A trap circuit tuned to the second harmonic rejects the second harmonic and another circuit accentuates the third harmonic and provides a "clean" local-oscillator signal at 130 Mc. As with the 50-Mc. converter, the second-harmonic trap circuit (L_9C_4) can be omitted if no local interference problem exists. In the case of the converter pictured, a local f.m. station at 100.8 Mc. gave an output signal at 14.2 Mc. by beating against the 86.6-Mc. second harmonic of the oscillator. A trap in the antenna circuit was not as effective, since it caused some deterioration of the 144-Mc. noise figure.

Referring to Fig. 16-12, the construction is similar to that of the 50-Mc. converter, with a few exceptions. The coils can be wound to speci-

fication on a \mathcal{U}_4 -inch diameter drill and then mounted on associated tuning capacitors, tie points or ground lugs. In the photograph, the r.f. amplifier input circuit is in the lower right-hand corner. The coil above it is L_2 , the matching reactance, mounted on the side of the box. The two air-wound coils side by side and just to the right of center are for the amplifier plate and the mixer grid $(L_8$ and $L_4)$. The second-harmonic trap circuit is to their left, just below the third harmonic tank circuit, L_8C_8 . The oscillator plate coil and the output coil are in the upper left and right corners, respectively.

Adjustment of the 144-Mc. converter is similar, except that the multiplier tank circuit, L_8C_5 , should be adjusted for maximum signal. External noise may not be discernible in quiet locations on 144 Mc., and the antenna check outlined for 50 Mc. may be inconclusive. Adjustment of all r.f. circuits should be made carefully for greatest margin of signal over noise, using weak signals. The minimum-signal method of adjusting coil L2 may be followed initially, but readjustment for optimum signal-to-noise ratio (or lowest noise figure, using a noise generator) should produce a worthwhile improvement. Do not use the second-harmonic trap, L₀C₄, unless it is necessary to eliminate f.m. interference, as this circuit introduces one more variable to complicate the adjustment procedure.

In most areas 2-meter activity is spread over

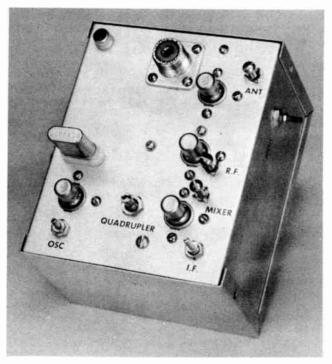


Fig. 16-13—The 220-Mc. converter uses four 6CW4 tubes and a semi-conductor frequency quadrupler.

Screw on the side is neutralization adjustment.

more of the band than is the case with 50 Mc. The converter response can be made uniform across most or all of the band by tuning the i.f. output coil, L_5 , for maximum response near the high end or middle of the band. This coil affects only the gain of the converter; detuning it does not reduce the signal-to-noise ratio. The r.f. amplifier plate and mixer grid circuits, C_2 - L_3 and C_3 - L_4 have only a minor effect on noise figure, so they can also be "stagger-tuned" to some extent to achieve uniform response.

A fair final check on the 144-Mc. converter performance is to detune the diode multiplier circuit, L_0C_0 , and note its effect on the signal-tonoise ratio. If the r.f. amplifier is working properly it should be possible to detune this circuit so that the gain drops an S unit or two, before there is any effect on the signal-to-noise ratio observable on weak signals.

The 220-Mc. Converter

The 220-Mc. converter, Figs. 16-13 and 16-15, is similar to the 144-Mc. converter in both construction and circuitry. A cascode r.f. stage is used ahead of the mixer, and a diode frequency quadrupler is used to furnish a 206-Mc. local-oscillator signal from a 51.5-Mc. crystal oscillator. Two tuned circuits are used between r.f. stage and mixer, coupled by a small capacitance. Because the 220-Mc. band is 5 Mc. wide, the receiver following this converter must tune from 14 to 19 Mc.

As can be seen in Fig. 16-15, the construction is quite similar to that of the 144-Mc. converter. The inductors L_1 , L_4 , L_4 and L_8 are first wound

on a 1/4-inch diameter rod or drill and then spaced to meet the specifications. They are supported by soldering the ends directly to tube pins, ground lugs or capacitor terminals. The Nuvistor sockets are set in 1/2-inch diameter holes in which two notches have been filed to accept the tabs; the tabs are then bent over and held to the chassis by washers and 4-40 hardware. The two 0.001- μ f. capacitors bypassing the grid of the second 6CW4 and the bottom end of L_8 are mica "button" capacitors (Centralab ZA-102). When mounting the tubular trimmer capacitors that are used to tune the signal circuits, it will be necessary to notch the holes slightly to clear the mounting.

The adjustment of the converter is quite similar to that of the 144-Mc. converter, and the instructions given earlier apply equally as well to the 220-Mc. band. Depending upon the local operating habits, it may be desirable to peak the circuits for a particular portion of the band. In areas where TV sets are tuned to Channel 7, there may be substantial TV-receiver local-oscillator radiation that will mess up the first megacycle or two of the band, and consequently the amateur activity will peak around 222 or 223 Mc. Both a grid-dip oscillator or signal generator, and a noise generator will be found to be very useful in getting best results from the converter.

Power Supply

The circuit for a suitable power supply is given in Fig. 16-16. Any power supply of 180 volts or more (enough to fire a 0D3) will be

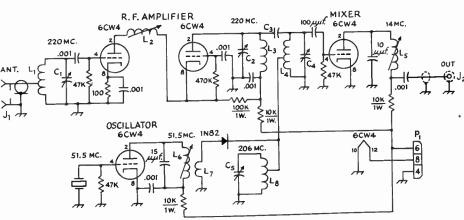


Fig. 16-14—Circuit diagram of the 220-Mc. crystal-controlled converter. Unless specified otherwise, resistors are $\frac{1}{2}$ watt, resistances are in ohms, capacitances in μ f.

C₁, C₂, C₄=1-6 $\mu\mu$ f, tubular trimmer (Centralab. 829-6). C₈=2 $\mu\mu$ f, made by twisting two insulated wires 1 inch.

 C_b —15- $\mu\mu$ f. variable (Hammarlund MAC-15). J₁—Chassis-mounting coaxial receptacle (SO-239).

J₂—Phono jack.

L₁-2¼ t. No. 18 spaced wire diam., ¼ inch i.d., tapped ¾ t. from ground end.

L₃-0.12 - 0.19 μh. adjustable inductor (Miller 20A157R8I).

Ls-2¾ t. No. 18 spaced twice wire diam., ¼ inch i.d.

L₆—4.t. as L₅, tapped 1 turn from ground end. L₆—4.7 - 10.0 µh. adjustable inductor (Miller 20A826R8I).

 L_0 =0.43 - 0.85 μ h. adjustable inductor (Miller 20A687R81).

L_r—1½ t. insulated wire wound on ground end of L_e.
 L_e—4 t. No. 18 spaced three times wire diam., ¼ inch i.d., tapped 1¼ t. from ground end.

P1-Chassis-mounting octal plug (Amphenol 86-CP8).

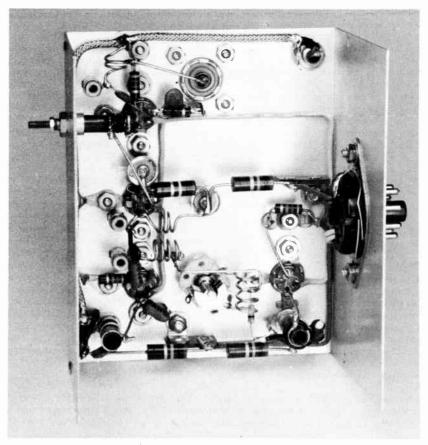


Fig. 16-15—View underneath the chassis of the 220-Mc. converter. The long shielded wire runs from $L_{\rm b}$ at the lower left to the output jack. Silver-button mica capacitors (Centralab ZA-102) that bypass the plate coil and the control grid of the second 6CW4 (center left) are also used to support several resistors. Coil $L_{\rm b}$ is supported by the terminals of $C_{\rm b}$ (bottom center). Chassis is part of $3\times4\times5$ -inch Minibox.

suitable; depending upon the voltage available the value of R_1 may have to be changed. R_1 should have a value such that with no current being taken from terminal 6 the current through the 0D3 is between 30 and 40 ma.

Using Other Intermediate Frequencies

The i.f. tuning range beginning at 14 Mc. was selected as the most desirable for most receivers. Other ranges may be preferred, and the i.f. can be altered easily enough. The injection frequency is lower than the signal frequency by whatever i.f. you intend to use. For example, a 50-Mc. converter with a 7-Mc. i.f. would have a crystal and injection frequency of 50-7, or 43 Mc. The 144-Mc. converter would have a 137-Mc. injection frequency, and the crystal would be one-third of this, or 45.667 Mc.

Generally speaking, single-conversion communications receivers (most inexpensive types, and all older receivers) work best with low intermediate frequencies, such as 7 Mc. or lower. Double-conversion receivers will be satisfactory in the 14-Mc. range in almost every case, and

some are stable enough to do well around 30 Mc. At least one communications receiver, the NC-300, has a range designed especially for v.h.f. converter use, starting at 30.5 Mc.

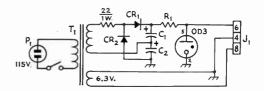


Fig. 16-16--Typical power supply for the 50-, 144- or 220-Mc. converter.

 C_1 , C_2 —40- μ f. separate section dual capacitor (Sprague TCS-48).

 CR_1 , CR_2 —400 p.i.v. silicon rectifier (1N1763 or equiv.) J_1 —Octal socket.

P₁—Line plug, preferably fused.

R₁-3000 ohms, 5-watt wirewound.

S₁—S.p.s.t. toggle.

T₁-250 v.c.t. at 50 ma., 6.3 v. at 2 amp. (Knight 62 G 008 or equiv.).

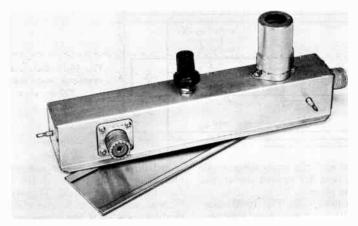


Fig. 16-17—220-Mc. trough-line preamplifier. Unit connects by cable to a remote receiver or converter.

PREAMPLIFIER FOR 220 Mc.

The amplifier shown in Figs. 16-17 to 16-20 will improve the gain and noise figure of a 220-Mc. converter that is not operating at maximum effectiveness. It also provides some additional selectivity, which may be helpful in areas where signals from outside the band are trouble-some. The plate circuit has high Q, so it must be retuned in covering the band.

The schematic diagram given in Fig. 16-18. The signal is fed into the cathode of the grounded-grid amplifier. The plate circuit is a trough line. Any of the small u.h.f. triodes may

be used, though a 6AM4 is shown. Check pin connections and cathode resistor values for other types.

Construction

The outer conductor of the line, which also serves as the chassis, is made of flashing copper. If the details of Fig. 16-19 are followed, it may be made from a single piece. A small copper shield is placed across the tube socket to isolate the input and plate circuits. Just where this shield is located depends on the tube used, as various

Fig. 16-18—Wiring diagram for the 220-Mc. preamplifier. Capacitance is in $\mu\mu$ f., resistance is in ahms.

 C_1 —5- $\mu\mu$ f. miniature variable (Hammarlund MAC-5).

 C_2 —3-30- $\mu\mu$ f. mica trimmer. See text.

C_s, C₄—500- $\mu\mu$ f. feed-through bypass (Centralab MFT-500).

J₁, J₂—Coaxial chassis receptacle (SO-239).

L₁—Inner conductor of trough line—¼-inch copper tubing, 6¼ inches long. C₁ connects 1¾ inches from plate end. See Fig. 16-19 and text. L₂—Coupling laop—insulated hookup wire 3 inches long. Laop portion lays close to cold end of L₁ far 2 inches. Hot end comes through chassis an feed-through bushing (National TPB).

RFC₁, RFC₂, RFC₃—18 t. No. 24 enam., closewound, 1/8 inch diam.

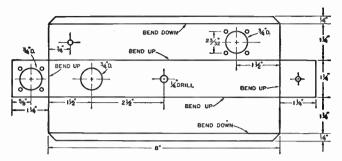


Fig. 16-19—Details of the outer conductor and chassis for the 220-Mc. preamplifier.

tubes have different grid pin arrangements. All grid terminals are bent flat against the copper case, and soldered in place.

The left end (bottom view, Fig. 16-20) contains the coaxial fitting for the antenna connection, the r.f. chokes and other components of the input circuit. The plate line, tuning capacitor, output coupling loop and coax fitting, and the B-plus feed-through capacitor mount in the large portion. A bottom cover for the line can be made of copper 8 inches long and 2½ inches wide. Bend over a quarter inch on each side, and slip the cover over the edges of the case.

The inner conductor is ½-inch copper tubing. Start with a piece 6½ inches long. Saw the ends lengthwise to depths of ½ and ½ inch. Cut off one half at each end. The remaining portions are used to make connections. The half-inch end is bent down to solder to the plate lugs of the socket. The quarter-inch end solders to the feedthrough capacitor.

The tuning capacitor, C_1 , is mounted with its stator bars toward the tube end of the line. The inner conductor will rest between these bars and they can be soldered to it readily. Plate voltage


is fed through C_6 , heater voltage through C_6 . Output is taken off through the coupling loop, L_2 , visible in Fig. 16-20. The series capacitor, C_2 , was omitted from the preamplifier, though it might be useful if the amplifier works into a converter with an untuned input circuit.

Adjustment

The preamplifier may be connected to the converter through a coaxial line of any convenient length, but the converter input should be a coaxial fitting. To put the preamplifier into service, adjust the plate line for maximum signal strength. Then check the position of the coupling loop, adjusting for maximum response. Readjust the tuning of the line as the coupling is changed.

The tuning range of C_1 is not wide, so be sure that it actually tunes the line at both ends of the band. Some adjustment of tuning range can be had by rotating the mounting of the capacitor 180 degrees. If this does not bring the tuning within range, the mounting hole can be elongated and the position of the trimmer adjusted as required.

Fig. 16-20 — Bottom view of the preamplifier

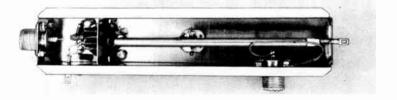

RECEIVERS FOR 420 Mc.

For best signal-to-noise ratio, receivers for any frequency should have the highest degree of selectivity that can be used successfully at the frequency in question. With crystal control or its equivalent in stability accepted as standard practice on all bands up through 148 Mc., there is little point in using more bandwidth in receivers for these frequencies than is necessary for satisfactory voice reception, a maximum of about 10 kc. Such communication selectivity is now being used successfully by most workers on 220 and

420 Mc., too, but it imposes several problems not encountered on lower bands.

First is the matter of oscillator instability in the converter. Even the best tunable oscillator at 420 Mc. suffers from vibration and hand-capacity effects sufficiently to make it difficult to hold the signal in a 10-kc. i.f. band width.

Then, there are still some unstable transmitters being used in work on 220 and 420 Mc. It is out of the question to copy these on a selective receiver. Last, searching a band 30 megacycles wide is excessively time-consuming when communications-receiver selectivity is used in the i.f.

There is no single solution to these problems, but the best approach appears to be that of breaking up of the band into segments for different types of operation. This is being done by mutual agreement among 420-Mc. operators at present, as follows: 420 to 432 Mc. — modulated oscillators and wide-band f.m., 432 to 436 Mc. — crystal-controlled c.w., a.m. and narrow-band f.m.; 436 to 450 — television.

The first segment can be covered with a superregenerative receiver, a superheterodyne having a wideband i.f. system, or a converter used ahead of an f.m. broadcast receiver. The high selectivity required for best use of the middle portion makes a crystal-controlled or otherwise highly stable converter and communications receiver combination almost mandatory. Amateur TV is usually received with a converter ahead of a standard TV receiver, tuned to some channel that is not in use locally.

Many of the tubes used on the v.h.f. bands are useless at 420 Mc., and the performance of even the best u.h.f. tubes is down compared to lower bands. Only the lighthouse or pencil-triode tubes and a few of the miniatures are usable, and these require modifications of conventional circuit technique to produce satisfactory results.

Crystal diodes are often used as mixers in 420-Mc. receivers, as in this frequency range they work nearly as well as vacuum tubes. The over-all gain of a converter having a crystal mixer is about 10 db. lower than one using a tube, so this difference must be made up in the i.f. amplifier. The noise figure of a receiver having a crystal mixer and no r.f. stage includes the noise figure of the i.f. amplifier following the mixer, so best results require that the i.f. amplifier employ low-noise techniques discussed earlier in this chapter. If the i.f. is 50 Mc. or higher it is particularly important that a low-noise triode be used for the first i.f. stage.

Crystal diodes of the type used in radar mixers, such as the 1N21 series, are well suited to 420-Mc. mixer service, though care must be taken to avoid damage from transmitter r.f. energy. Other types of crystal diodes such as the 1N72 and CK710 will stand higher values of crystal current, and their use is recommended.

Few conventional vacuum tubes work well as mixers at 420 Mc. and higher. The 6J6 is useful where a balanced input circuit is desired, as in Fig. 16-5C. For single-ended circuitry the 6AM4, 6AN4 and 6CW4 are recommended. They may be used in grounded-grid or grounded-cathode circuits.

Fig. 16-21—A highly effective r.f. amplifier for 420 Mc, The tank circuit is a half-wave line made of flashing copper. Coaxial fittings are for input and output connections. Heater and plate voltages are brought in on feed-through bypass capacitors just visible on either side of the 6AJ4 tube.

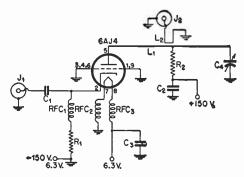


Fig. 16-22—Schematic diagram of the 420-Mc. r.f. amplifier.

 C_1 -500- $\mu\mu$ f. ceramic.

C₂, C₃—1000-μμf, ceramic feedthrough (Erie style 2404).
 C₄—Copper tabs, %-inch diam.; see text and photographs.

R₁-150 ohms, ½ watt.

R₂-470 ohms, 1/2 watt.

L₁—¼-inch copper tubing, 7% inches long, tapped 2% inches from plate end.

 L_2 —Loop of insulated wire adjacent to L_1 for $\frac{3}{4}$ inch.

J₁, J₂—Coaxial fitting.


RFC1, RFC2, RFC3—9 turns No. 22, %-inch diam., spaced one diam.

For high-selectivity coverage of the 432- to 436-Mc. segment of the band, a common practice is to use a crystal-controlled converter working into another converter for either the 50- or 144-Mc. band, tuning the latter for the four-megacycle tuning range.

A 420-MC. R.F. AMPLIFIER

The r.f. amplifier shown in Figs. 16-21 through 16-23 is capable of a gain of more than 15 db. and its noise figure can be as low as 6 db. with careful adjustment. It will make a large improvement in the sensitivity of any converter or receiver that has no r.f. stage, or one that is working poorly.

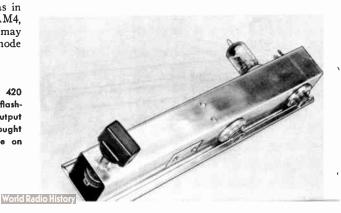The design shown is for either the 6AJ4 or 6AM4, but with suitable socket and pin-connection changes the 417A, 6BC4 or 6AN4 will work equally well. It is a grounded-grid amplifier with a half-wave line in the plate circuit. The antenna is connected to the cathode of the tube through a coupling capacitor. As the input impedance of the grounded-grid stage is low, nothing is gained



by the use of a tuned circuit in the cathode lead. Output is taken off through a coupling loop at the point of lowest r.f. voltage along the line.

The amplifier is built in a frame of flashing copper that serves as the outer conductor of the tank circuit. The whole assembly is 10 inches long and 1½ inches square, except for the bottom, which is about 1¾ inches wide. Edges are folded over with lips ¼ inch wide which slide into a bottom cover made from copper sheet 2¼ by 10 inches in size, with its edges bent up ¼ inch wide on each side.

The plate circuit is made of ¼-inch copper tubing tuned by a copper-tab capacitor at the far end from the tube. Plate voltage is fed in at the point of minimum r.f. voltage, which in this instance is about 5 inches from the open end. The antenna is connected to the cathode through a coupling capacitor. The input impedance of the grounded-grid amplifier is so low that nothing is gained by using a tuned circuit at this point. The cathode and heater are maintained above ground potential by small air-wound r.f. chokes.

The tube socket is two inches in from the end of the trough, and is so oriented that its plate connection, Pin 5, is in the proper position to connect to the line with the shortest possible lead. A copper shielding fin is mounted across the interior of the trough 2½ inches from the end, dividing the socket so that Pins 3, 4, 5 and 6 are on the plate side of the partition.

Minimum grid-lead inductance is important. This was insured by bending all the grid prongs down against the ceramic body of the socket, and then making the mounting hole just big enough to pass this part of the socket and the prongs. They were soldered to the wall of the trough.

Input and output connections are coaxial fittings mounted on the side wall of the trough. B-plus and heater voltage are brought into the assembly on feed-through capacitors mounted on the same side of the trough as the tube. Connection to the inner conductor of the line is made with a grid clip, so that the point of connection can be adjusted for optimum results.

The copper tubing is slotted at the plate end with a hack saw to a depth of about ¼ inch, and a strip of flashing copper soldered into this slot to make the plate connection. A copper tab about

the size of a one-cent piece is soldered to the other end of the tubing to provide the stationary plate of C_{\bullet} . The line is supported near the low-voltage point by a ¼-inch-thick block of polystyrene. This is centered at a point 5¼ inches in from the tube end of the trough assembly. The hole for the B-plus feedthrough is $4\frac{1}{2}$ inches from the same end.

The movable plate of C_4 is soldered to a screw running through a nut soldered to the upper surface of the trough at a point $\frac{3}{2}$ inch in from the open end. If a fine-thread screw is available for this purpose it will make for easier tuning, though a 6-32 thread was used in this model. This made a wobbly contact, so a coil spring was installed between the top of the trough and the knob to keep some tension on the adjusting screw.

Adjustment of the 420-Mc. amplifier is made easier if a noise generator is used, though it is not as important as in the case amplifiers with tuned input circuits. If the amplifier is working properly there will be an appreciable rise in noise as the plate circuit is tuned through resonance, and it may break into oscillation if operated without load. When connected to a following stage, with a reasonably matched antenna plugged into J_1 , the amplifier should not oscillate unless the coupling loop, L_2 , is much too far from the inner conductor.

When the amplifier is operating stably and tuned to a test signal (or to a peak of response to a noise generator), the next step is to locate the optimum position for feeding the plate voltage into the line. This may be done by running a pencil lead slowly up and down the inner conductor, until a spot is found where touching the lead to the line has little or no effect on the operation of the amplifier. The plate voltage clip should be placed at this point and the process repeated, moving the clip slightly until it is at the minimum-voltage point precisely. This adjustment should be made at the midpoint of the tuning range over which the amplifier is to be used.

The position of the coupling loop should then be adjusted for best signal-to-noise ratio. This will probably turn out to be with the insulated wire lying against the inner conductor for a distance of about ¾ to 1 inch, starting at the minimum-voltage point just located.


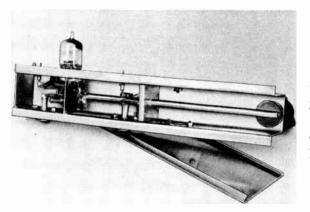


Fig. 16-23—Bottom view of the 420-Mc. r.f. amplifier, with the slip-on cover removed. The inner conductor of the tank circuit is held in place by a block of polystyrene, mounted near the low-voltage point on the line. The plate-voltage feedthrough and output coupling loop may be seen at the left of this support. Heater, cathode and antenna-circuit companents are in a separate compartment at the tube end of the assembly. The line is tuned at the opposite end by a handmade copper-tab capacitor.

A CRYSTAL-CONTROLLED CONVERTER FOR 432 Mc.

The crystal-controlled converter shown in Figs. 16-24 and 16-26 uses two grounded-grid r.f. stages and a grounded-grid mixer. This proved to be a more stable arrangement and easier to duplicate than one with grounded-cathode stages. A major source of over-all feedback is the heater connections, and more elaborate heater-line filtering will be found in this unit than is usually the case. The local-oscillator signal at 418 Mc. is obtained by tripling twice from a 46.44-Mc. crystal oscillator, once in a triode section of a 6J6 and one through a 1N82 diode.

Fig. 16-24—The 430-Mc. converter is built in a 5 × 7 × 3-inch Minibox. At the top in this view, from left to right: input jack, r.f. amplifier, r.f. amplifier, mixer, output jack. The tube (shielded) is a 616, used as crystal oscillator and frequency multiplier.

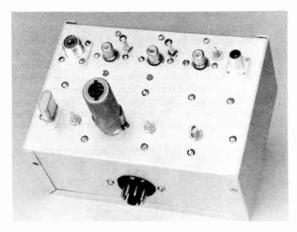

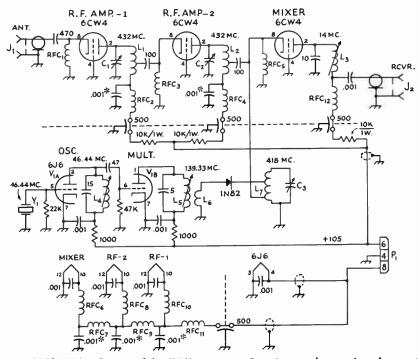


Fig. 16-25—Wiring diagram of the 430-Mc. converter. Capacitance values are in $\mu\mu f$., except decimal values which are in μf . Resistors are ½ watt unless specified otherwise. All 0.001- μf . capacitors marked * are button-type (Centralab ZA-102); other 0.001- μf . capacitors are disk ceramic. All 500- $\mu\mu f$. feedthrough capacitors are Centralab FT-500.

C₁, C₂-6-\(\mu\mu\mu\)f. ceramic variable (Centralab 829-6)

C_s-15-\(\mu\mu\mathre{\psi}\) variable (Hammarlund MAC-15)

L₁, L₂, L₇—See Fig. 16-27.

L₈—4.7–10.0-µh. adjustable inductor (Miller 20A826RBI).

L₄--0.43-0.85-\(mu\)h..adjustable inductor (Miller 20A687RBI).

L₀--0.119-0.187-μh. adjustable inductor (Miller 20A157RBI).

 L_6 —2 t. No. 20 insulated wound around ground end of L_6 .

RFC₁-RFC₁₁—8 inches No. 22 enam. cleaned ½ inche each end and wound on 10K or higher ½-watt resistor.

RFC₁₂-50-µh. r.f. choke (Millen 34300-50).

J₁—Coaxial chassis receptacle (SO-239).

J₂—Coaxial chassis receptacle (UG-290A/U).

P₁—Octal plug (Amphenol 86-CP8).

Y₁-46.44-Mc. crystal (International Crystal FA-9).

418 V.H.F. RECEIVERS

Referring to the circuit diagram in Fig. 16-25, the circuitry through the oscillator-multiplier chain is similar to that shown for the lower-frequency converters described earlier in this chapter. Adjustable inductors tune the circuits on the lower frequencies, and at 418 Mc. a variable capacitor, C_3 , tunes a half-turn coil, L_7 (see Figs. 16-26 and 16-27). In the signal channel, 6CW4s are used as grounded-grid amplifiers and mixer, and the coupling circuits are ceramic trimmers and half-turn inductors. The B+ leads are filtered heavily as are the heater leads. For over-all good stability, numerous ceramic feed-

through and button bypass capacitors are used. Study of Figs. 16-24 and 16-26 will give a good idea of the location of the various components. The shield partition is built from a 3½-inch wide strip of aluminum, and a ¾-inch lip is bent on one edge for mounting on the chassis. The line of screws holding the chassis bisects the chassis.

Practically all of the components will be supported by tube-socket pins, button or feed-through capacitors, ground lugs or tie points. The exception is the diode multiplier, which is supported at one end by the point on L_7 to which

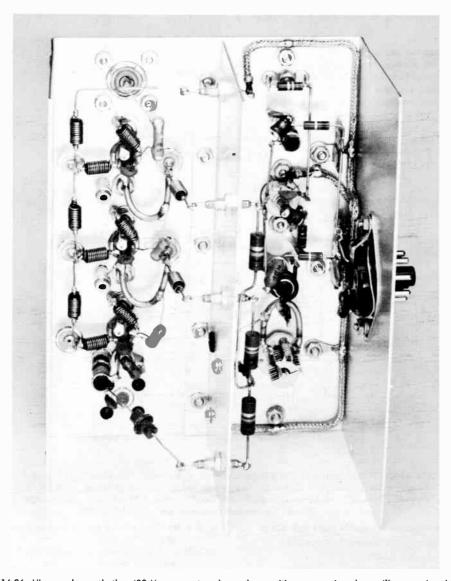


Fig. 16-26—View underneath the 430-Mc. converter shows the partition separating the oscillator and multiplier (right) from the r.f. and mixer. R.f. chokes mounted on button bypass capacitors (left) provide filtering for heater wiring. Feedthrough bypass capacitors in partition are 2 inches from chassis, except heater feedthrough (top) which is ½ inch from chassis. Oscillator injection lead from L₇ to the cathode of the mixer runs through rubber grommet in partition.

it is soldered and at the other by an end of L_{\bullet} . A regulated 105-volt power supply is recommended for use with the converter. The crystal oscillator should be checked first, by measuring the voltage drop across the 1000-ohm resistor to L₄. The drop across this resistor will be greater when the stage is not oscillating than when it is, and the slug of L_4 should be set at a lowerinductance value than that which gives minimum voltage drop across the resistor, to insure proper starting and operation. If a wavemeter is available, the frequency of output should be checked. The slug of L_{δ} should be set for minimum voltage drop across the 1000-ohm resistor connected to L_5 , and again the frequency should be checked with a wavemeter if one is available. The third harmonic of a 144-Mc. signal source can be used to align the r.f. stages, after which C_8 and L_6 should be peaked for maximum signal.

If any instability is experienced in the signal circuits, as evidenced by regeneration or oscillations at some setting of C_1 and C_2 , look for

poor connections or poor grounds. In some cases the instability may also be caused by having the mixer tap too high above ground on L_7 .

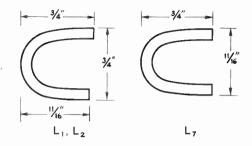


Fig. 16-27—Details of "coils" L₁, L₂ and L₇. Material is No. 10 tinned copper wire. Taps on L₁ and L₂ are ½ up from ground end; taps on L₇ are ½ and ½ up from ground end.

A CRYSTAL-CONTROLLED CONVERTER FOR 1296 Mc.

The converter described is the result of an effort to simplify circuits and construction of a converter for 1296 Mc. to a point where it could be duplicated with a minimum of effort, and a limited amount of equipment.

Only five tubes are used, and one of these is a

voltage regulator for the crystal oscillator. One half of a 12AT7, V_{1A} , is an overtone oscillator at approximately 53.4 Mc. The second half, V_{1B} , doubles to 106.8 Mc. A 6CY5, V_{2} , doubles to 213.6 Mc. and drives a 6AK5 doubler to 427 Mc. The output of V_{8} drives a DR303 diode multiplier

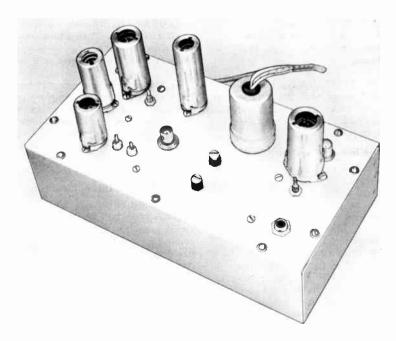


Fig. 16-28—From the top, the 1296-Mc. converter looks much like conventional designs for the v.h.f. bands. Across the lower portion of the chassis are the cascode i.f. amplifier stage and its output jack, left, the power connections shielded by means of an aluminum film can, the voltage regulator tube, and the 12AT7 crystal oscillator. In the upper right are the 6CY5 and 6AK5 frequency multipliers. The black nuts, left center, are used for tension on the adjusting screws for the u.h.f. circuits.

420 V.H.F. Receivers

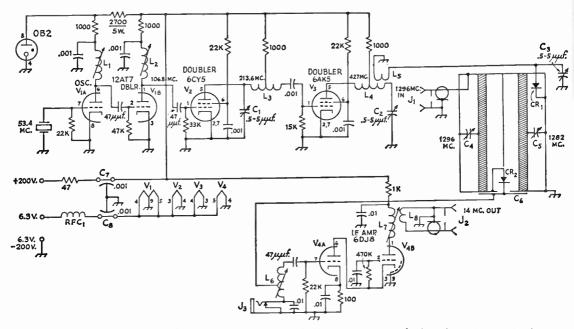


Fig. 16-29—Circuit diagram and parts information for the 1296-Mc. converter. Decimal values of capacitors are in μ f.

 C_1 , C_2 , C_3 -0.5- to 5- $\mu\mu$ f. trimmer (Erie 532-08-OR5).

C4, Cc-Cavity tuning screws; see text.

C_e-U.h.f. bypass: 1¾ × ¾-inch brass plate, insulated from end of r.f. assembly with .005-inch plastic film. See Figs. 16-30 and 16-32.

C₇, C₈—0.001-µf. feed-through bypass (Centralab FT-

CR₁-Multiplier diode, DR 303 or 1N82.

CR₂—Mixer diode, 1N21B, C, D, E, or MA 421B.

J₁, J₂—Coaxial fitting, BNC type.

J3-Closed-circuit jack.

to 1282 Mc. The 1282-Mc. energy is coupled to the mixer crystal along with the input signal, and the 14-Mc. difference frequency is amplified by a 6DJ8 cascode i.f. stage and coupled with a link to the output jack.

The Injection System

The crystal oscillator is operated at low voltage and with a regulated plate supply to improve stability, a critical factor in operation at 1296 Mc. Variations in oscillator frequency that would go unnoticed at lower frequencies become disturbing at 1296 Mc., for even though the oscillator frequency is high to start with, it is being multiplied twenty-four times. Oscillator stability is improved if the crystal is not subjected to large and sudden changes in temperature. It was found that mounting the crystal inside the chassis, where it is protected from drafts, resulted in much better stability than mounting above the chassis. The three multiplier stages are quite conventional and need very little comment, with one possible exception: Pins 2 and 7 of the 6AK5 should be grounded as directly as possible. Any stray inductance in the cathode lead seems to have a large effect on the output power of this stage. L_1 —11 turns No. 22 enam. close-wound on ¼-inch slugtuned form (CTC PLS-6 or LSM).

L2-4 turns like L1.

L₃—6 turns No. 22 tinned, ¼-inch diam., ¾ inch long, center-tapped.

 L_4 -3 turns like L_3 , $\frac{5}{16}$ inch long.

 L_5 —1 turn insulated hookup wire at center of L_4 .

 L_0 , L_7 —25 turns No. 28 enam. closewound on form like L_1 . Tap on L_0 3½ turns from cold end.

 L_3-4 turns insulated hookup wire around B+ end of L_7 . RFC1-11 t. No. 22 spacewound on 1-watt resistor.

Crystal diode multipliers may be new to some, but they provide a very simple way to get small amounts of r.f. at this frequency. Several types of crystal diodes may be used. When the converter was first constructed, various types were tried, and 1N82 diodes gave the best performance. Later, a DR303 was tried, and it gave about twice the output.

U.H.F. Circuitry

The tuned circuits at 1282 and 1296 Mc. are halfwave coaxial lines, shorted at each end and tuned capacitively at their centers. The outer conductors are formed of thin brass sheet, soldered at the joints. Dimensions are not critical, except for length, and the circuit will probably work if the length is within plus or minus 1/8 inch. The center conductors are 1/4-inch brass rod, drilled and tapped at each end. The lines are tuned by 8-32 screws which provide a small variable capacitance to ground at the center of each line. A nut is soldered on the inside of each trough to provide threads, and a nylon nut (or short length of nylon rod tapped 8-32) is used on top of the chassis as a jam nut. This provides tension on the screw to give smooth tuning. The mixer crystal holder is made by

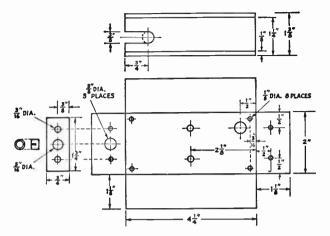


Fig. 16-30—Details of the sheet-metal parts of the trough-line tank circuits. The small plate at the left is insulated from the end of the trough assembly with thin sheet teflon. Slot in the partition, upper portion of drawing, provides space for the mixer crystal, as shown in Figs. 16-31 and 16-32.

soldering a ¼-inch length of ¼-inch i.d., ¼6-inch o.d. brass tubing in the ¼6-inch hole in the mixer bypass plate, then making two saw cuts across the end of the tubing at 90-degree angles to form fingers. These are bent in until they grip the large end of the crystal firmly. The mixer bypass plate is insulated by covering the side away from the crystal holder with cellophane tape, and is mounted on the end of the trough lines with 4-40 screws and insulating shoulder washers. The holder for the small end of the crystal is a contact removed from an octal tube socket.

The antenna input connector is a UG 1094/U BNC fitting. It must be spaced up with a few 3/8-inch i.d. washers so that the threads will just reach through the chassis and the trough line with enough length for the nut. The center con-

nection of the fitting should be cut down so that it clears the ¼-inch rod that is the trough line center conductor. If desired, a type N fitting could be used by drilling out the hole for the larger fitting. The input loop is soldered to the end of the trough line about ¾6 inch up from the bottom, and run straight over to the input fitting. The coupling loop to the mixer crystal is soldered to the end of the trough line between the mixer crystal and the center conductor. The entire u.h.f. portion of the converter can be silver plated, if means are available, but this is not mandatory.

Filtering

The power to the converter should be filtered to prevent signals in the i.f. range from getting into the converter and back into the receiver.

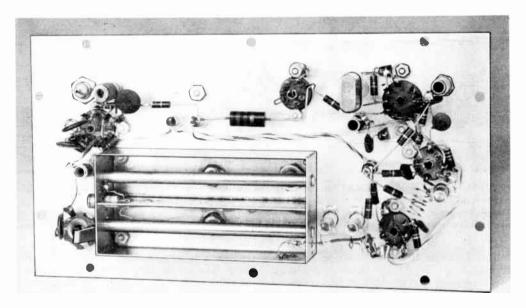


Fig. 16-31—Bottom view of the 1296-Mc. converter. Oscillator multiplier components are at the right. Note the diode multiplier in the lower right corner of the 1282-Mc. tank circuit. The mixer crystal is at the left end of the tank circuits.

422 V.H.F. Receivers

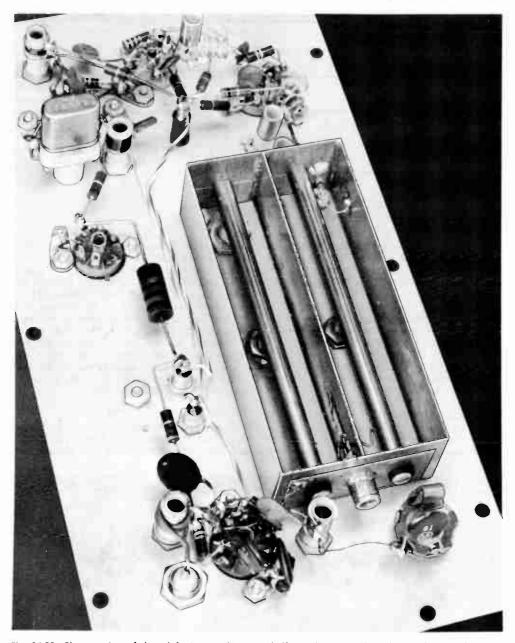


Fig. 16-32—Close-up view of the u.h.f. circuits. These are halfwave lines, tuned at their midpoints. The mixer crystal is held in place by a slotted brass sleeve, soldered to a capacitor plate on the outside of the trough. Though it is not visible in the picture, the capacitor plate is insulated from the trough end with a thin film of plastic. Screws that hold the inner conductors in position are insulated from the capacitor plate by fiber washers.

This is accomplished by bringing in B + through a 47-ohm resistor and a feed-through bypass capacitor. The filament power comes through a choke wound on a 1-watt resistor and through a feed-through bypass. To cover the exposed terminals on top of the converter, an aluminum can that 35-mm. film is packaged in was used. The top was flattened by placing the

top over a large dowel and hammering out the bulge. The top is then drilled for the feed-through capacitors and the terminal strip mounting screw. The top is held in place on the top of the chassis with these components. The power cable is brought in through a grommet in the bottom of the film can. The paint can be removed from the film can with lacquer thinner.

Adjustment

The oscillator and multiplier stages can be checked out as in any converter, using a grid-dip meter to tune circuits, up to the 213-Mc. stage. The output of the 427-Mc, stage can be checked by temporarily disconnecting the multiplier diode where it connects to the side of the trough line and putting a meter in series with the diode to ground. Current here should be 6 ma. or more. The diode should then be reconnected and a 0-1-ma, meter connected to the mixer current jack. The tuning screw in the 1282-Mc. trough line should be adjusted until crystal current is obtained. If the crystal current is less than 0.2 ma., solder a 1/2-inch long piece of wire to the contact at the small end of the mixer crystal and bend the other end near the center conductor of 1282-Mc. line, and readjust the tuning.

Next, adjust the tuning of the 1296-Mc. line until the crystal current dips. This indicates that the input circuit is tuned to 1282 Mc. Back the screw out slightly, and you will be near 1296 Mc. Connect the converter to a receiver tuned to 14 Mc. and adjust the i.f. amplifier coils for maximum noise in the receiver. At this point you can listen for the harmonic of a 144- or 432-Mc. transmitter and peak up the input on that signal. For further improvement a crystal diode noise generator will be required.

With a noise generator, experiment with size and shape of input coupling and mixer coupling loops, and local oscillator injection. It may be worthwhile, also, to try different taps on the i.f. input coil. When changing mixer crystals, do not decide which is best until you have optimized these adjustments for the particular crystal in question. A 1N21E may seem no better than the 1N21B you started with, until things are peaked up for the new crystal. Then there is a difference.

It is important that the shortest possible feedline be used at this frequency. RG-8/U is commonly used, but has about 9-db. loss per 100 feet. The converter has a BNC input connector as RG-55/U cable is used between the converter and the antenna relay, a distance of three feet. From the relay to the antenna, RG-8/U is used. Double-shielded cables such as RG-71/U 93ohm or RG-55/U 53-ohm cable should be used between converters and the receiver to keep signals at the intermediate frequency from leaking to the receiver.

(From March, 1961, QST.)

K6AXN provided a drawing of the converter top plate which can be used as a template for drilling. Copies of this template will be sent free of charge upon receipt of a stamped self-addressed envelope. Address ARRL Technical Dept., West Hartford 7, Conn.

1296 Mc. and higher

The September, 1960, issue of QST carried an article on the conversion of the war-surplus APX-6 transponder to a 1215-Mc. transmitter receiver. Anyone interested in this frequency will do well to consider the unit, since it is an inexpensive way to get started on the band.

The August, 1960, issue of QST described an

experimental transceiver for 5650 Mc. based on using the 2K26 reflex klystron as transmitter and receiver local oscillator. Elementary waveguide techniques are used with a horn antenna.

An account of experimental two-way communication above 20 kMc. was carried in the May, 1959, issue of OST.

V.H.F. Transmitters

Transmitter stability regulations for the 50-Mc. band are the same as for lower bands, and proper design may make it possible to use the same rig for 50, 28, 21, and even 14 Mc., but incorporation of 144 Mc. and higher in the usual multiband transmitter is generally not feasible. Rather, it is usually more satisfactory to combine 50 and 144 Mc., since the two bands are close to a third-harmonic relationship. At least the exciter portion of the transmitter may be made to cover both bands very readily.

Though no stability restrictions are imposed by law on amateur operation at 144 Mc. and higher, the use of stabilized narrow-band systems pays off in improved effectiveness in both transmitter and receiver. It is this factor, more than the interference potentialities of the wideband systems, which makes it desirable to employ advanced techniques at 144, 220 and 420 Mc.

The low-power stages of a transmitter for the v.h.f. bands need not be greatly different in design from those used for lower bands, and the techniques of Chapter Six can be used. The constructor has the choice of starting at some lower frequency, usually around 6, 8 or 12 Mc., multiplying to the operating frequency in one or more additional stages, or he can use a high initial frequency and thus reduce the number of multiplier stages. The first approach has the virtue of using low-cost crystals, but h.f. crystals may effect an economy in power consumption, an important factor in portable or emergency-powered gear.

CRYSTAL OSCILLATORS

Crystal oscillator stages for v.h.f. transmitters may make use of any of the circuits shown in Chapter Six when crystals up to 12 Mc. are used. but certain variations are helpful for higher frequencies. Crystals for 12 Mc. or higher are usually of the overtone variety. Their frequency of oscillation is an approximate odd multiple of some lower frequency, for which the crystal is actually ground. Thus 24-Mc. crystals commonly used in 144-Mc. work are 8-Mc. cuts, specially treated for overtone characteristics. The overtone crystals currently being supplied are nearly as stable as those designed for fundamental operation, and they are easy to handle in properly designed circuits.

Best results are usually obtained with overtone crystals if some regeneration is added. This makes for easy starting under load and greater output than would be obtainable in a simple tri-

ode or tetrode circuit. Regenerative circuits, with constants for 8- or 24-Mc. crystals, are shown in Figs. 17-20 and 17-24. Triodes are shown, but the same arrangement may be used with tetrode or pentolde tubes. The important point in either case is the amount of regeneration, controlled by the number of turns below the tap in L_1 of Fig. 17-20 or 17-24. There should be only enough feedback to assure easy crystal starting and satisfactory operation under load; too much will result in oscillation not under the control of the crystal.

Overtone operation is possible with standard fundamental-type crystals, using these circuits. Practically all will oscillate on their third overtones, and fifth and higher odd overtones may be possible. Adjustment of regeneration is more critical, however, if the crystals are not ground for overtone characteristics. The frequency may not be an exact multiple of that marked on the crystal holder, so care should be used in working with crystals that are near a band edge.

Crystals ground for overtone service can be made to oscillate on other overtones than the one marked on the holder. For more discussion of overtone oscillator techniques, see QST for April, 1951, page 56, and March, 1955, page 16.

Crystals are now available for frequencies up to around 100 Mc. They are somewhat more expensive and more critical in operation than those for 30 Mc. and lower, however. Use of 50-Mc. crystals is made occasionally as a means of preventing radiation of the harmonics from lower frequency crystals that might cause TVI.

FREQUENCY MULTIPLIERS

Frequency multiplying stages in a v.h.f. transmitter follow standard practice, the principal precaution being arrangement of components for short lead length and minimum stray capacitance. This is particularly important at 144 Mc. and higher. To reduce the possibility of radiation of oscillator harmonics on frequencies that might interfere with television or other services, the lowest satisfactory power level should be used. Low-powered stages are easier to shield or filter, in case such steps become necessary.

Common practice in v.h.f. exciter design is to make the tuned circuits capable of operation over the whole range from 48 to 54 Mc., so that the output stage can drive either an amplifier at 50 to 54 Mc. or a tripler from 48 to 144 Mc. Tripling is often done with push-pull stages, particularly when the output frequency is to be

144 Mc. or higher.

AMPLIFIERS

Most transmitting tubes now used by amateurs will work on 50 Mc., but for 144 Mc. and higher the tube types are limited to those having low input and output capacitances and compact physical structure. Leads must be as short as possible, and soldered connections should be avoided in high-powered circuits, where heating may be great enough to melt the solder.

Plug-in coils and their associated sockets or jack bars are generally unsatisfactory for use at 144 Mc. and higher because of the stray inductance and capacitance they introduce. One way around this trouble is the use of a dual tank circuit in which the inductor for 144 Mc. is a conventional tuned line, with its shorting bar made as a removable plug. When the stage is to be used on another band the short is removed and a coil is plugged into the jack, the line then serving as a pair of plate leads. Such an arrangement will operate as efficiently on 144 Mc. as if it were designed for that band alone.

At 220 Mc. and higher it may be necessary to employ half-wave lines as tuned circuits, as shown in Fig. 17-28 (P_1 in place).

Neutralization of triode amplifiers for 50 and 144 Mc. can follow standard practice, but the stray inductance and capacitance introduced by the neutralizing circuits may be excessive for 220 Mc. and higher. In such instances groundedgrid amplifiers may be used. Driving power is applied to the cathode circuit, with the grid acting as a shield. Some of the drive appears in the output, so both the driver and amplifier must be modulated when a.m. is used. For this reason the grounded-grid amplifier is used mainly for f.m.

Instability shows up frequently in tetrode amplifiers as the result of ineffective screen bypassing. The solution lies in series-resonating the screen circuits to ground, as shown in Figs. 17-13 and 17-24. The r.f. choke and capacitor values vary with frequency, so screen neutralization is essentially a one-band device.

FREQUENCY MODULATION

Though f.m. has not enjoyed great popularity in v.h.f. operation, probably because of lack of suitable receivers in most v.h.f. stations, its possibilities should not be overlooked, particularly for the higher bands. At 420 Mc., for instance, the efficiency of most amplifiers is so low that it is often difficult to develop sufficient grid drive for proper a.m. service. With f.m. any amount of grid drive may be used without affecting the audio quality of the signal, and the modulation process adds nothing to the plate dissipation. Thus considerably higher power can be run with f.m. than with a.m. before damage to the tubes develops or the signal is of poor quality.

Frequency modulation also simplifies transmitter design. The principal obstacle to greater use of f.m. in v.h.f. work is the wide variation in selectivity of v.h.f. receivers, making it difficult for the operator to set up his deviation so that it will be satisfactory for all listeners.

V.H.F. TVI PREVENTION AND CURE

The principal causes of TVI from v.h.f. transmitters are as follows:

- 1) Adjacent-channel interference in Channel 2 from 50 Mc.
- 2) Fourth harmonic of 50 Mc. in Channels 11, 12 or 13, depending on the operating frequency.
- 3) Radiation of unused harmonics of the oscillator or multiplier stages. Examples are 9th harmonic of 6 Mc., and 7th harmonic of 8 Mc. in Channel 2; 10th harmonic of 8 Mc. in Channel 6; 7th harmonic of 25-Mc. stages in Channel 7; 4th harmonic of 48-Mc. stages in Channel 9 or 10; and many other combinations. This may include i.f. pickup, as in the cases of 24-Mc. interference in receivers having 21-Mc. i.f. systems, and 48-Mc. trouble in 45-Mc. i.f.'s.
- 4) Fundamental blocking effects, including modulation bars, usually found only in the lower channels, from 50-Mc. equipment.
- 5) Image interference in Channel 2 from 144 Mc., in receivers having a 45-Mc. i.f.
- 6) Sound interference (picture clear in some cases) resulting from r.f. pickup by the audio circuits of the TV receiver.

There are many other possibilities, and u.h.f. TV in general use will add to the list, but nearly all can be corrected completely, and the rest can be substantially reduced.

Items 1, 4 and 5 are receiver faults, and nothing can be done at the transmitter to reduce them, except to lower the power or increase separation between the transmitting and TV antenna systems. Item 6 is also a receiver fault, but it can be alleviated at the transmitter by using f.m. or c.w. instead of a.m. phone.

Treatment of the various harmonic troubles, Items 2 and 3, follows the standard methods detailed elsewhere in this *Handbook*. It is suggested that the prospective builder of new v.h.f. equipment familiarize himself with TVI prevention techniques, and incorporate them in new construction projects.

Use as high a starting frequency as possible, to reduce the number of harmonics that might cause trouble. Select crystal frequencies that do not have harmonics in TV channels in use locally. Example: The 10th harmonic of 8-Mc. crystals used for operation in the low part of the 50-Mc. band falls in Channel 6, but 6-Mc. crystals for the same band have no harmonic in that channel.

If TVI is a serious problem, use the lowest transmitter power that will do the job at hand. Much interesting work can be done on the v.h.f. bands with but a few watts output, particularly if a good antenna system is used.

Keep the power in the multiplier and driver stages at the lowest practical level, and use link coupling in preference to capacitive coupling.

Plan for complete shielding and filtering of the r.f. sections of the transmitter, should these steps become necessary.

Use coaxial line to feed the antenna system, and locate the radiating portion as far as possible

from TV receivers and their antenna systems. Some v.h.f. TV tuners have removable strips that can be replaced with double-conversion inserts for u.h.f. reception. For a number of channels the first conversion frequency may then fall in or near the 144-Mc. band. Where this method

is employed for u.h.f. reception the receiver is very sensitive to 144-Mc. interference. The cure is to replace the strips with others having a different conversion frequency, or use a conventional u.h.f. converter for reception of the channels from 14 up.

HIGH-POWER TRANSMITTER FOR 50 AND 144 Mc.

The gear described in the next several pages shows how transmitting equipment for two v.h.f. bands can be coordinated in design so as to work from a single exciter. If the builder so desires, the station may be operated from one set of power supplies and speech equipment, with a single set of meters measuring the important currents in both transmitters. Each item can be used by itself, or they combine readily to cover both 50 and 144 Mc., at a power level approaching the legal limit.

In order of their description they are an exciter capable of delivering up to 40 watts output at 48 to 54 Mc., a companion amplifier for the 50-Mc. band, a tripler-driver-amplifier for 144 Mc., and a dual antenna coupler for feeding 50- and 144-Mc. antennas having balanced lines. Their physical appearance is such that they combine neatly for rack mounting, as seen in Fig. 17-1.



THE EXCITER

Though it is shown mounted on the same panel as the 50-Mc. amplifier in Fig. 17-2, the exciter unit might well be used alone, as a versatile 50-Mc. transmitter capable of running up to about 65 watts input. Provision is made for taking off 48-Mc. output at two power levels, through J_8 or J_2 , the latter being used for driving the 144-Mc. tripler to be described later.

The exciter is completely shielded, and its power leads are filtered to prevent radiation of harmonics by the power cable. In addition, there are built-in traps to absorb unwanted oscillator harmonics that might otherwise be passed on to the amplifier, or to the antenna. Harmonics of this kind are particularly troublesome when they fall in Channel 2, which is so close to the operating frequency that a filter in the antenna line is


relatively ineffective against them.

The interstage coupling circuits are of band-pass design. Once they are properly adjusted they require no further tuning, when the frequency is changed over a 4-Mc. range. Thus only the crystal switch and the output plate circuit need be adjusted when changing frequency.

Circuit Details

The oscillator is a 5763, using crystals above 6, 8, 12, or 24 Mc. for 144-Mc. operation, or 6.25, 8.34, 12.5 or 25 Mc. for 50 Mc. Its plate circuit tunes 24 to 27 Mc., quadrupling, tripling or doubling the crystal frequency. (Crystals at 24 to 27 Mc. are overtone cuts that oscillate at one-third the marked fre-

Fig. 17-1—A high-power r.f. section for a 50- and 144-Mc. station. Equipment includes a band-pass exciter for both bands, a 50-Mc. r.f. amplifier built on the same panel, a tripler-driver-amplifier for 144 Mc., and a dual antenna coupler for both frequencies. Units can be operated with a single set of power supplies, and with common speech equipment and meters.

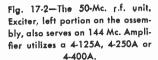



quency in this circuit.) A series-tuned trap, L_1C_1 , in the oscillator plate circuit absorbs the third harmonic of 6-Mc. crystals. This 18-Mc. energy otherwise would pass on to the next stage, where it would be tripled to a frequency in Channel 2. This harmonic has been found to be a common cause of 50-Mc. TVI in Channel 2 areas.

The doubler is also a 5763. A second trap, C.L., in the grid circuit, is tuned to the 7th harmonic of 8-Mc. crystals. The two traps thus prevent radiation of energy in Channel 2, the most critical transmitter problem a 6-meter man is likely to encounter in correcting TVI. They can be modified for other frequencies to suit local problems. An example is the 10th harmonic of 8-Mc. crystals, that falls in Channel 6. A trap for the 5th harmonic of the crystal frequency should take care of this.

The 6146 amplifier stage has a shunt-fed pinetwork plate circuit. For best stability over the entire operating range the stage is neutralized. The choke, RFC_4 , is provided to short out the d.c. voltage that would appear on the output circuit if C_9 , should break down. The choke in the plate lead, RFC_6 , is for parasitic oscillation suppression. Note that each of the three cathode leads is bypassed separately at the socket. The exciter may be keyed in the 6146 cathode jack, J_4 .

Double-tuned band-pass circuits between the oscillator and doubler, and between the doubler and final, provide essentially flat response from 48 to 52 Mc., or 50 to 54 Mc. A potentiometer in the doubler screen circuit provides excitation control for the 6146, and may be used to compensate for variations in drive that may appear at some spots in the band.

The link winding on the doubler plate circuit, L_6 , is for the purpose of taking off low-level 48-Mc. output to drive the tripler in the 144-Mc. r.f. unit. Note that the keying jack in the 6146 cathode circuit is the open-circuit type. Removing the key thus disables the 6146 stage, when the first two stages are being used in this way. Separate heater and filament switches on all units

allow them to be operated separately. Highvoltage supplies may be left connected to all r.f. units, energizing only the filaments and heaters in the ones being used.

Construction

The exciter is built on a 5 \times 10 \times 3-inch aluminum chassis, with a bottom plate and a perforated aluminum cage to complete the shielding. The small knobs at the lower left of the front view are for the crystal switch and the excitation control. The crystal switch has 12 positions. Ten are for the crystals on the multiple crystal socket (Johnson No. 126-120-1). One more crystal position is provided on the front panel (a convenience if you want to use a frequency not covered by the 10 crystals in the multiple socket), and the 12th switch position is for an external v.f.o. It connects the 5763 grid to the coaxial v.f.o. input fitting, and shorts out RFC1, and its parallel capacitor. The stage then functions as a frequency multiplier. The output frequency of the v.f.o. could thus be in the 6-, 8or 12-Mc. range. Above the excitation control may be seen the knobs for the 6146 plate and output coupling capacitors.

Three coaxial connectors are on the rear wall of the exciter. The one at the outside edge is for v.f.o. input. The others are the doubler and 6146 output fittings. Two 4-terminal steatite strips handle the various power and metering leads. Adjacent to each terminal except the ground connection is a feed-through bypass capacitor to take the power lead through the chassis.

TVI that might result from radiation of harmonics by the power leads is prevented by filtering of each lead. The feed-through bypasses are connected to the exciter circuits through r.f. chokes, the inner ends of which are again bypassed with small disk ceramic capacitors. All power leads are made with shielded wire, bonded at intervals to the chassis.

The side view shows the multiple crystal socket at the front of the chassis. Separate crystal sockets may be used if desired. The oscillator and

doubler tubes are in the foreground. The trap capacitors, C_1 and C_4 , are adjacent to these tubes, while C_2 and C_3 , are between them, a bit off their center line. To the rear of the 5763 doubler are C_5 and C_7 . The grid tuning capacitor for the 6146, C_6 , is just visible inside the amplifier compartment.

A separate lead is provided for each power circuit. Fixed bias for the 6146 is brought in from the bias supply that is part of the high-power amplifier assembly. This bias is desirable to prevent the plate current from rising too high when the excitation is backed off. If the exciter is used alone, fixed bias is unnecessary. External meters can be connected in any of the circuits at the terminal strips.

The sides, back and top of the amplifier cage are Reynolds "Do-It-Yourself" perforated aluminum sheet, now available in many hardware stores. The pieces are joined together at the corners with lengths of 3/8-inch aluminum angle which can be bought or bent up from sheet stock. The tuning and loading capacitors are mounted on the front of the cage, so this part should be a piece of solid sheet stock rather than the perforated material. The dimensions of the cage are not critical. The original is 53/4 inches deep, 25/8 inches across, and 41/4 inches high. Make provision for removing the top and outside sheets of perforated stock for convenience in servicing, when the exciter is mounted against the amplifier unit. Extension shafts and couplings bring out the amplifier controls to the panel.

Inside the cage, the 6146 can be seen with its socket mounted above the chassis on ½-inch metal sleeves. The cathode and screen bypasses should connect to separate ground lugs on the

top of the chassis, with the shortest possible leads. This wiring can be done conveniently before the socket is mounted on the chassis if nuts are used temporarily to hold the ground lugs in place over the socket mounting screws. The neutralizing adjustment, C₈, is mounted on the rear wall of the cage, and wired to the 6146 plate clip and the feed-through bushing with 3/8-inch wide strips of thin copper. A ceramic insulator mounted on the wall near the 6146 plate cap supports the junction of RFCs, RFC3, and C9. An ordinary tie point supports the other end of RFC3 and the shielded power lead. The plate coil, Lo, can be seen in back of the 5763 doubler tube, wired between the stators of C_{10} and C_{11} . C_{12} and RFC_4 are mounted near C11, and hooked between its stator bar and a ground lug. A short length of RG-58/U coax runs down through a hole in the chassis from C_{11} over to J_3 .

Most of the parts visible in the chassis view can be identified from our description of the panel, rear, and topside layouts. The oscillator cathode choke, RFC₁, can be seen mounted upright near the oscillator tube and crystal sockets. Both 5763 sockets should be oriented so that Pins 4 and 5 are adjacent to the outside chassis wall. L_1 is visible between C_1 and the oscillator tube socket. L_2 and L_3 run between this socket and that of the doubler. These coils are made from a single length of Miniductor stock with the specified number of turns removed to provide spacing between them. The same applies to L_6 and L_7 . These are to the left of the 6146 socket. L_4 is between the doubler socket and C_4 . The trap coils are mounted with their axes vertical, to minimize coupling to the band-pass coils. Lo is wound around and cemented to the bypassed end of L₅.

The power lead r.f. chokes are mounted between single-terminal tie points on the rear lip of the chassis and the feed-through capacitors. The disk ceramic bypasses are then applied to the tie points. A single-terminal tie point mounted under RFC_1 holds one end of the 3300-ohm doubler screen resistor and the lead over to the terminal strip at the rear. A double tie point is mounted between the two 5763 sockets to support the bypassed ends of L_2 and L_3 . Another over nearer the rear of the chassis supports the cold end of L_5 and the bottom of the doubler grid resistor.

Wiring will be simplified by the following procedure. Before mounting the crystal switch, ground one terminal of each crystal socket through a bus wire. Connect short lengths of tinned wire to the other terminal of each socket that

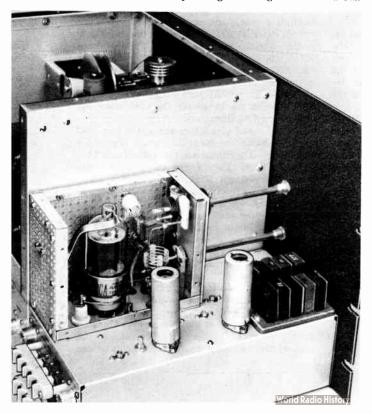


Fig. 17-3—Side view of the exciter, with cover removed. Band-pass coupling circuits eliminate front-panel tuning controls except for crystal switch and output stage tuning.

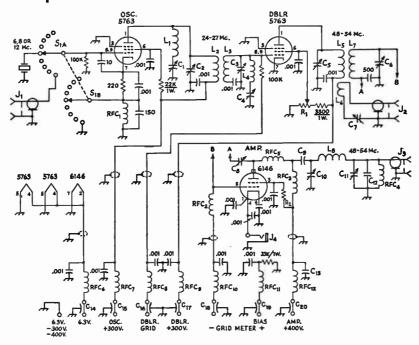


Fig. 17-4—Schematic diagram of 48–54-Mc. exciter. All capacitances less than .001 μ f. are in $\mu\mu$ f. All .001- μ f. capacitors are disk ceramic. All resistors are $\frac{1}{2}$ 2 watt unless otherwise specified.

C₁, C₂, C₃—35- $\mu\mu$ f. miniature trimmer (Hammarlund MAPC-35).

 C_4 —10- $\mu\mu f$. miniature variable (Hammarlund MAC-10). C_5 , C_6 —20- $\mu\mu f$. miniature variable (Hammarlund MAC-20)

 C_7 —50- $\mu\mu$ f, miniature trimmer (Hammarlund MAPC-50). C_8 —15- $\mu\mu$ f, miniature trimmer (Hammarlund MAPC-15).

C₉, C₁₃—.001-µf. 3000-volt disk ceramic.

C₁₀—35-μμf. miniature variable (Hammarlund HF-35).
C₁₁—100-μμf. miniature variable (Hammarlund MAPC-100B).

 C_{12} —100- $\mu\mu$ f. 1000-volt mica.

 C_{14} – C_{20} –.001- $\mu\mu$ f. feedthrough-type ceramic (Centralab FT-1000).

L₁-16 turns No. 24, %-inch diam., 32 t.p.i. (B & W Miniductor No. 3008).

L₂, L₃—12 turns each No. 20, %-inch diam., 16 t.p.i. (B & W Miniductor No. 3007). Make from one piece of Miniductor with 5 turns removed between coils. Cold ends are adjacent.

L4-10 turns No. 20, ½-inch diam., 16 t.p.i. (B & W Miniductor No. 3003).

will be under the switch. Then when the latter is installed, the wires can be run to the proper contacts and soldered in place. Note that the front wafer of the switch is used for shorting out RFC1, while the crystal socket connections are made to the rear wafer, which is more accessible. The v.f.o. input socket is connected to the proper switch contact with a length of RG-58/U coax.

In assembling the power lead filtering components at the rear of the chassis, the disk ceramic bypasses can most easily be mounted on the tie points before the latter are fastened inside the

L₅, L₇—6 turns No. 20, ½-inch diam., 16 t.p.i. (B & W Miniductor No. 3003). Make from one piece of Miniductor with 3 turns removed between coils.

L₆—2 turns hookup wire wound around cold end of L₅ and cemented in place.

Ls-4 turns No. 18, %-inch diam., 8 t.p.i. (B & W Miniductor No. 3010).

 J_1 , J_2 , J_3 —Coaxial chassis fitting (Amphenol 83-1R).

J₄-Open-circuit phone jack.

R₁-25,000-ohm 4-watt pot.

 R_2 -33,000-ohm 3-watt (3 100,000-ohm 1-watt in parallel).

RFC₁-2.5-mh. r.f. choke (National R-100S).

RFC₂, RFC₄—7-μh. solenoid v.h.f. choke (Ohmite Z-50).

RFC₅—6 turns No. 22 tinned wire, ¼-inch diam., spaced one-wire diam.

RFC₆-RFC₁₂-15 turns No. 24 enam. close-wound on high value 1-watt resistor.

\$1-2-pole 12-position miniature ceramic rotary (Centralab PA-2005).

chassis. Wiring up the power leads should be done before the r.f. chokes are mounted in place.

THE 50-MC. AMPLIFIER

Though the exciter and amplifier are pictured on a single panel, the possibility of using either by itself should not be overlooked. The exciter will make a fine low-powered transmitter, and the final amplifier may be used with any exciter delivering 15 watts or more.

It will take up to the legal limit of power with a 4-400A tube, 750 watts with a 4-250A, or 400 watts with a 4-125A.

The plate circuit is a larger version of the one used in the 6146 stage of the exciter, a shunt-fed pi-network. Operation is completely stable without neutralization, probably because the natural neutralized frequency of the tubes is close to 50 Mc. Provision was originally made for neutralization, but it was found to be unnecessary. Parasitic suppression devices were not required, but if the layout is varied appreciably from that shown, the builder should check for both types of instability with great care.

The jack in the filament center-tap lead is for keying, or for insertion of a grid-bias modulator. A bias supply that delivers about 50 volts negative for the 6146 and 150 for the final amplifier is included in the final stage assembly. Filament transformers for the exciter and final are also part of this unit. Separate filament switches are included; one for the exciter and the other for the final tube and the blower motor. Power leads, except the high voltage, are brought in on an 8-pin plug.

Building the Amplifier

A $12 \times 10 \times 3$ -inch aluminum chassis is used for the amplifier unit. Thus, it may be combined with the exciter on a $10\frac{1}{2}$ -inch rack panel, if desired. The amplifier controls mounted near the panel bottom are, left to right, the input link reactance capacitor, C_1 ; the grid tuning capacitor, C_2 ; and S_1 and S_2 . S_1 applies a.c. to the transformer for the exciter heaters and to the bias

supplies. S_2 applies a.c. to the filament transformer of the amplifier and starts the cooling fan. Above the switches on the panel are the amplifier plate tuning and loading controls.

On the rear of the chassis, coaxial connectors for r.f. input and output are mounted at either end. Between them are the high-voltage connector for the plate supply, the cathode circuit jack, and a fitting for the remaining power and meter leads.

Above the chassis, the 4-250A tube is seen near the front of the chassis. Note that its socket is mounted on $\frac{1}{2}$ -inch sleeves. Holes $\frac{3}{6}$ -inch in diameter are drilled in the chassis directly underneath those provided in the socket for the passage of cooling air. Holes are also drilled adjacent to the cathode, grid, and screen pins to pass their leads. Bypassing of cathode and screen is done above the chassis. The heat radiating plate connector for the 4-250A was cut down to four fins to reduce the over-all height requirement. The filament transformer, T_{s} , and the screen modulation choke, L_{s} , are also topside.

The amplifier plate circuit components are to the left of the tube. The tuning capacitor, C_{7} , originally a neutralizing capacitor, is mounted on the side wall of the shielding assembly. Two modifications should be made to the neutralizing unit before mounting. The circular plates supplied should be replaced with larger ones, 3 inches in diameter, to increase the available tuning range. The bearing assembly of the rotor

disk must be temporarily removed, and a strap of copper run between the screw holding the bearing in place and the opposite (grounded) end of the square ceramic insulating pillar, grounding the capacitor rotor. Two copper straps must be inserted between the stator disk and its insulator, to connect the stator with the blocking capacitor, C_6 , and with L_3 .

The blocking capacitor, the shunt-feed r.f. choke, RFC_2 , and the high-voltage bypass, C_6 , are assembled into one unit before mounting in the amplifier. This is done with the aid of the hardware supplied with the TV-type high-voltage capacitors. The bypass capacitor, on the bottom of the stack, is equipped with one terminal threaded and one tapped. The latter is on the bottom end, for fastening the assembly to the chassis. The threaded terminal screws into the $2\frac{1}{2}$ -inch ceramic insulator upon which RFC_2 is wound.

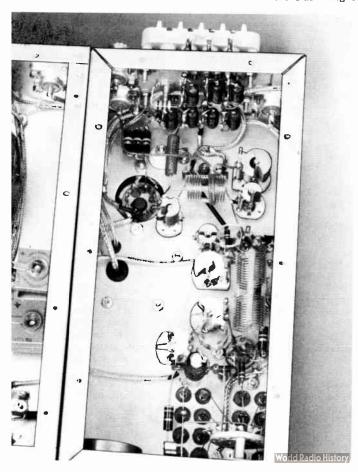


Fig. 17-5—Bottom view of the 50-Mc. exciter, showing band-pass circuits and TVI protective measures.

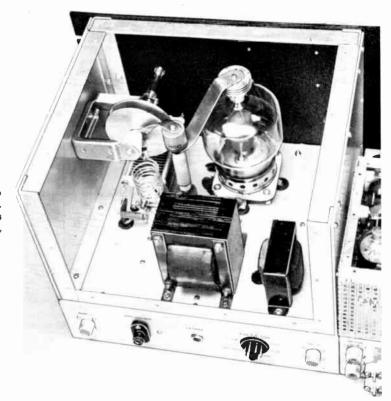


Fig. 17-6—Interior of the 50-Mc. final amplifier. Plate tuning capacitor is modified neutralizing unit, left.

The ends of the choke winding are secured by lugs at each end of the insulator. Cs should be fitted with a threaded terminal at the lower end for screwing into the top of the insulator. This also serves to fasten the 3/4-inch wide strip of copper which runs up to the 4-250A plate cap. Finally, the longer of the two copper strips coming from the stator of C_7 is screwed to the top of C₅. A 1/2-inch feedthrough bushing brings the high-voltage up to the hot side of C_6 . The loading capacitor, C8, is mounted on the chassis directly underneath C7. The plate coil, L₃, gets rather warm when the rig is operated at high power level, so both of its ends must be bolted in place rather than soldered. One end is bent around and fastened under a nut provided on the stator of C8. The other is bolted to the short length of copper strap previously fastened to the stator of C7. A length of RG-8/U coaxial cable is run between C₈ and J₂. At the capacitor end, this cable is connected to lugs under the stator and frame mounting screws.

Solid sheet aluminum is used for the enclosure of this unit, as it must be reasonably airtight except for holes directly above the tube itself. The side that supports C_7 must of fairly heavy stock for rigidity. Home-bent ¾-inch angle stock was used to hold the assembly together. If the over-all height of the unit is kept to just about that of the $10\frac{1}{4}$ -inch rack panel, there will be enough clearance above the tube plate connector.

Most of the under-chassis components are visible in the bottom view. The grid circuit is near the front edge of the chassis. Copper strap connects the tube socket grid pin with the stator of C_2 . L_2 then is soldered between this strap and a tie point. L_1 is slid inside the cold end of L_2 , and cemented lightly in place.

The cooling fan sucks air in from the side of the amplifier near the back corner. The motor is mounted on an aluminum bracket. The fan as supplied will blow, rather than suck, so the blades must be bent back to reverse their pitch. A small piece of aluminum window screening shields the hole cut in the chassis side for the fan.

Bias supply components occupy the lower left quarter of the bottom view. Layout and wiring of this portion of the rig is anything but critical. Shielded wire was used for all power leads. Bypassing at the power connector should be done with very short leads, and C₁₄ should be mounted as close as possible to the high-voltage connector.

Adjustment and Operation

An initial setting of the exciter controls can be made before power is applied, if a grid-dip meter is available. The series traps, L_1C_1 and L_4C_4 , introduce varying amounts of reactance across the tuned circuits when they are adjusted, so some further adjustment will be needed after these are set up finally, but the following

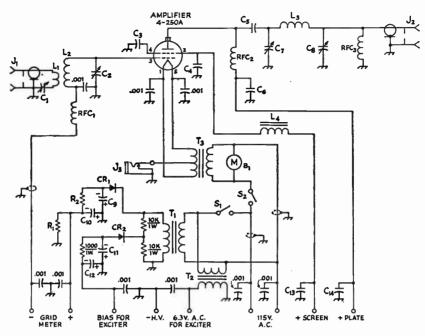


Fig. 17-7—Schematic diagram and parts list for the 4-250A amplifier. All capacitors marked ,001 μ f. are 600-volt disk ceramic.

 C_1 —50- $\mu\mu$ f. miniature variable (Hammarlund HF-50).

C₂-15- μ H, miniature variable, double-spaced (Hammarlund HF-15X).

Ca, C4, C13-.001-µf. 1000-volt disk ceramic.

 C_{5} , C_{6} , C_{14} ,—500- $\mu\mu f$. 20,000-volt ceramic (Cornell-Dubilier MM120T5).

C₇—Disk-type capacitor with 3-inch diam. plates (made from Millen 15011).

 C_s —250- $\mu\mu$ f. variable, double-spaced (Johnson 250-F20).

C₉, C₁₀, C₁₁, C₁₂—12-µf. 250-volt electrolytic.

J₁, J₂—Coaxial chassis fitting (Amphenol 83-1R).

J₈-Closed-circuit phone jack.

CR₁-65-ma. selenium rectifier (Federal 1002A).

CR₂-20-ma. selenium rectifier (Federal 1159).

L₁--5 turns No. 24, ½-inch diam., 32 t.p.i. (B & W Miniductor No. 3004).

L₂—4 turns No. 18, %-inch diam., 8 t.p.i. (B & W Miniductor No. 3010).

procedure will result in a close approximation.

Disconnect one end of L. Fig. 17-4 Couple

Disconnect one end of L_8 , Fig. 17-4. Couple the grid-dip meter to L_2 and tune it with C_2 to about 24.5 Mc. Leaving the setting of C_2 at that position, lift one end of L_2 . Reconnect L_8 and resonate C_8L_8 to about 25.5 Mc. Reconnect L_2 , and the circuits should be set for operation on 48 to 52 Mc. For 50 to 54 Mc., the frequencies should be 25.5 and 26.5 Mc.

Procedure for the second band-pass circuit is similar except for the frequencies involved. For 48 to 52 Mc., disconnect L_7 and tune C_8L_6 to 49 Mc. Reconnect L_7 and disconnect L_6 , tuning L_7C_6 to 51 Mc. Reconnect L_8 . For the 50- to 54-Mc. range these frequencies would be about 51 and 53 Mc.

L_s—6 turns No. 12 tinned wire, 1-inch diam., spaced twice wire diam.

L4-Filter choke, about 10-hy. 100-ma. (Triad C-10X).

B₁—Blower motor and fan (Allied cat. No. 72P715).

R1-20,000 ohms 10 watts.

R₂--500 ohms 2 watts (2 1000-ohm 1-watt resistors in parallel).

RFC1, RFC3-7-µh. solenoid choke (Ohmite Z-50).

RFC₂—Solenoid choke, 42 turns No. 24 d.c.c. closewound on ½-inch diam., 2½-inch long insulator (National GS-2).

S1, S3-Single-pole single-throw toggle switch.

T₁—Power transformer, 135 volts at 50 ma. (Triad R-30X).

T₂—Filament transformer, 6.3 volts at 3 amp. (Triad

T₈—Filament transformer, 5.2 volts c.t. at 15 am. (Triad F-11U).

Connect a source of 6.3 volts a.c. at 2.5 amperes or more between the ground and heater terminals, and a low-range meter from the doubler grid return terminal to ground. Insert crystals for the desired frequency range. Apply about 200 volts d.c. to the oscillator plate-screen terminal through a 50- or 100-ma. meter. Current should be 20 to 30 ma., and grid current in the following stage should be about 0.5 ma., when the voltage is increased to the normal 300 volts. Touch up the tuning of the band-pass circuit, if necessary, to get uniform response across the desired range.

The trap circuits can be adjusted at this point, tuning for minimum signal at the frequency to be attenuated in each case. A receiver tuning to the harmonic frequencies is helpful. These will be

50-Mc. Amplifiers

about 18 to 20.25 Mc. for the first trap and 56 to 60 Mc. for the second, if they are for Channel 2. A TV receiver on the channels to be protected may also be used, merely tuning the traps for minimum TVI. Some slight readjustment of the band-pass circuit may be needed after the final trap tuning is done.

Now remove the grid current meter and ground the metering terminal in the doubler grid circuit. Connect a meter (0 to 5 ma. or more) between the terminals provided for measuring the 6146 grid current. Set the screen potentiometer, R_1 , to about the middle of its range and apply about 200 volts to the doubler plate-screen input terminal. Adjust the band-pass circuit, $L_{\rm b}C_{\rm b}$, $L_{\rm T}C_{\rm o}$ for nearly uniform response across the desired range, using the 6146 grid current as the output indication. There should be at least 2 ma. across a 4-Mc. range when the doubler plate voltage is raised to 300. Note that the screen potentiometer controls the input to the doubler, and through it the excitation to the 6146.

The 48-Mc. output coupling adjustment, L_6C_7 , may be checked at this time. The line to a 144-Mc. tripler stage should be connected to I_2 , and the series capacitor, C_7 , adjusted for maximum grid current in the driven stage. Recheck the adjustment of the band-pass circuit after this is done.

The 6146 amplifier stage had to be neutralized for stable operation. Its adjustment was not critical, however, and C_8 could be set anywhere near minimum capacitance with good results. Start out with its plates meshed about $\frac{1}{6}$ -inch. With grid drive applied but no plate or screen voltage, tune the 6146 plate circuit through resonance, trying various settings of C_8 until there is no grid current dip at resonance.

A load for the 6146 output circuit is now required. This can be a 40- or 60-watt lamp, with a 50- $\mu\mu$ f. capacitor in series to tune out its reactance. Adjust it for minimum reflected power, as indicated on an s.w.r. bridge. With the load connected and grid drive on, apply 300 to 400 volts to the amplifier plate and screen terminal. Tune C_{10} for maximum indicated output. Loading can

be adjusted by varying C_{11} , returning C_{10} after each movement of C_{11} .


Recheck for neutralization at this point, working for a setting of C_8 at which minimum plate current, maximum grid current, and maximum output all occur at the same setting of the plate tuning capacitor, C_{10} . The input can be run up to about 65 watts with plate modulation and 35-40 watts output should be obtained. Higher input can be run on c.w. Plate voltage should not exceed about 400 with plate modulation, though it can be somewhat more for c.w.

Now make a final check on the trap circuits, if necessary. In case TVI is experienced, adjust the traps while someone watches the TV screen, and see whether any improvement is possible. Remember that the traps shown were designed primarily to reduce Channel 2 interference. Where the trouble is with other channels, the traps can be modified to reduce the offending harmonic as required. A low-pass filter or a 4th harmonic trap will be needed if there is harmonic interference in Channels 11-13.

The amplifier as shown furnishes heater voltage and protective bias for the exciter. Hook together the 6.3-volt and ground terminals of the two units, and connect the bias output pin on the amplifier to the 6146 grid return in the exciter. Apply 115 volts a.c. to the appropriate pins on the amplifier power plug. When S_1 , Fig. 17-7, is closed, the exciter heaters and the bias supplies are energized. The bias voltages are about 50 and 150 negative for the driver and amplifier, respectively. Closing S_2 lights the amplifier filament and starts the fan motor.

For the initial testing of the amplifier disconnect its fixed bias supply, by lifting the connection between R_1 and R_2 , so that instability will be more evident. Connect the output of the exciter through a length of coaxial cable to J_1 . IIook a 0-25- or 0-50-ma. meter to the terminals provided for measuring grid current. Turn on the exciter and adjust the driver output and amplifier input for maximum grid current. Set this current between 10 and 15 ma. with the excitation control, R_1 , in the exciter. To insure proper

Fig. 17-8—Bottom view of 50-Mc. exciter and amplifier. Note that the two units are built separately, though they mount together on a single panel. Amplifier unit includes bias and filament supplies for both.

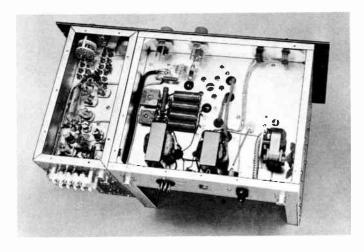

adjustment of the amplifier grid circuit, insert an s.w.r. bridge unit such as a Micromatch in the coax connecting the driver and amplifier, and tune C_1 and C_2 in the amplifier alternately for minimum reflected power. Adjust the driver tuning for maximum forward power.

Never apply screen voltage without having the plate voltage on also, and do not operate the amplifier without load. Either will result in excessive screen dissipation, and almost certain tube failure if continued for any length of time. A usable dummy load for testing can be made by connecting two or more 100-watt lamps in parallel. A variable series capacitor, $50~\mu\mu f$. or more, will be helpful in making the lamp load something like 50 ohms, resistive, at this frequency.

It is well to start with something less than maximum voltages in testing. If the plate voltage is under 1000 and the screen voltage about 200 to 300 volts, little harm can result if something is not quite right. With the dummy load connected, apply plate and screen voltages. Set C_8 near the middle of its range and tune C_7 for maximum output. If this occurs at or close to the end of the tuning range of C_7 , adjust the spacing of the turns in the plate coil accordingly. Adjust C_8 for maximum output, returning C_7 as required. If the grid current dropped below 10 ma. under load, increase the drive with the doubler screen potentiometer in the exciter.

Check now for stability. Briefly cut off the drive and see if the amplifier grid current drops to zero. If it doesn't, the amplifier either needs neutralization, or it has a parasitic oscillation. If no grid current shows with drive removed, note whether, when drive is applied and the amplifier is tuned properly, maximum output, minimum plate current and maximum grid current all occur at the same plate tuning. If they do, the amplifier is operating satisfactorily.

If oscillation does show up, check its frequency. If it is much higher than the operating frequency (probably over 150 Mc.) v.h.f. parasitic suppres-

sion measures are in order. If it is in the 50-Mc. region, neutralization will be required. These troubles are most common in multiband designs, and unlikely in a layout of this sort. Neutralization of the capacity-bridge type, like that in the exciter, can be incorporated readily, and parasitic suppression is covered in detail elsewhere in this Handbook. Neutralization may require additional grid-plate capacitance in some layouts. Provision was made for neutralization in the original layout (explaining the plugged hole in the front panel), but it was found to be unnecessary.

When the amplifier is operating stably, the plate and screen voltages may be increased in accordance with the tube manufacturer's ratings, for the type of operation intended. Operating conditions are different for the three tubes which can be used and they should follow the manufacturer's recommendations. This is not to say that variations from the published data are unsafe or undesirable. Any of the values can be varied over quite a range if the maximum rating for each tube element concerned is not exceeded. In this connection, it is highly desirable to provide continuous metering for the grid, screen, and plate currents. This, with a knowledge of the applied voltages, will help insure proper operation and make correct adjustment a simple matter.

A 144-MC. DRIVER-AMPLIFIER

The unit shown in Figs. 17-9 through 17-14 is a three-stage tripler-driver-amplifier that may be used with the exciter just described. Driving power at 48 Mc. may be taken from the doubler stage (by connecting to J_2 in Fig. 17-4) or from the output stage, running at low power. Almost any 50-Mc. transmitter of 3 to 5 watts output could be used by substituting a suitable crystal and retuning the stages for operation at 48 to 49.3 Mc. If a small 144-Mc. transmitter is available, the tripler stage may be dispensed with, in which case about 5 watts drive on 144 Mc. is required.

This section of the station is built in two parts. The tripler and driver stages are in the small portion at the right of Fig. 17-9, with the final stage at the left. All are push-pull stages, the tripler and driver using dual tetrodes. The tripler is an Amperex 6360, followed by an RCA 6524 straight-through amplifier. This drives a pair of 4-125As in the final stage.



Fig. 17-9—The high-power 2-meter rig, with shielding enclosures in place. The small unit at the right houses the tripler and driver stages.

144-Mc. Driver Amplifier

Input to the 4-125As can be up to 600 watts on a.m. phone, or 800 watts on c.w. or f.m. By suitable adjustment of screen and plate voltages the power can be dropped as low as 150 watts input and still maintain good efficiency. Some means of reducing power is highly desirable, as most operation on 144 Mc. can be carried on satisfactorily with low power.

The Driver Portion

The tripler and driver stages, Figs. 17-11 and 17-12, both operate well below their maximum ratings. Self-tuned grid circuits are used in each stage. This simplifies construction, and in the case of the driver stage, reduces the possibility of self-oscillation. With a surplus of drive available, the grid circuit of the 6524 may be resonated as low as 130 Mc. There is little tendency to tuned-plate tuned-grid oscillation, therefore, and neutralization is not required.

Tripler and driver are built on a standard $5 \times 10 \times 3$ -inch aluminum chassis, with the tripler at the back. Its plate circuit is tuned from the front panel by an extension shaft. Omission of the screen bypass on the tripler is intentional as the stage works satisfactorily without screen bypassing.

The 6524 is easily over-driven. This may be corrected by squeezing the driver grid coil turns closer together, lowering the resonant frequency until the desired 2.5 to 3.5 ma. is obtained across the band. The farther it can be resonated below 144 Mc. the less likelihood there is of self-oscillation in the driver stage.

The 6524 is mounted horizontally, and holes are drilled in the chassis under the tube to allow for air circulation. Plate leads are made of thin phosphor bronze or copper, bent into a semicircle, connecting the butterfly capacitor and the heat-dissipating connectors. This allows the latter to be removed for changing tubes, without putting undue strain on the plate pins. The connectors have to be sawed or filed down on the insides to fit on the 6524 pins. The coupling link at the driver plate circuit is tuned, to provide efficient transfer of energy to the amplifier grids.

Small feedthrough bypasses are used in the

driver screen circuit. C_6 is mounted in the aluminum plate that supports the 6524 socket, and C_6 is in the chassis surface.

Amplifier Features

Design of the 4-125A grid circuit is important in achieving

Fig. 17-10—Rear view of the 4-125A final stage. The split-stator capacitor near the middle of the picture is the screen neutralizing adjustment. The plate line is tuned with a capacitor made from parts of a neutralizing unit, mounted on ceramic stand-offs.

efficient transfer of energy from the driver stage. The input capacitance of the large tetrodes is so high that a tuned grid circuit of conventional design cannot be used at 144 Mc., so a half-wave line is substituted, as shown in Figs. 17-13 and 17-14. The input coupling link is series tuned, permitting adjustment for minimum standing wave ratio on the coaxial line connecting it to the driver stage output link. The grid line, L_1L_2 , is made of $\frac{1}{4}$ -inch copper tubing, to reduce heat losses.

Maintaining the 4-125A screens and filament leads at ground potential for r.f. is necessary for stability. To this end, the tube sockets are mounted above the chassis, rather than below. They are elevated only enough to allow the socket contacts to clear the chassis, and are mounted corner to corner, with the inner corners almost touching. The grid line is brought up through ½-inch chassis holes and soldered directly to the grid contacts. This determines the line spacing, about 1½-inches center to center.

The inner filament terminals on each socket are grounded to the chassis. The others connect to feedthrough bypasses with the shortest posible leads. These are joined under the chassis with a shielded wire and tied to the filament transformer. The r.f. chokes in the screen leads are under the chassis, their wire leads coming up through Millen type 32150 feedthrough bushings inserted in chassis holes under the screen terminals. The two screen terminals on each socket are strapped together with a 3/8-inch wide strip of flashing copper. The screen neutralizing capacitor is mounted as close to the sockets as possible and still leave room for the shaft coupling on its rotor. Leads to its stators are about one half inch long.

More compact and symmetrical design is possible if a modified single-section capacitor is used for C_6 . It should be the type having supports at both ends of the rotor shaft. The Millen 19140 and Hammarlund MC-140 are suitable units for the purpose. The stator bars are sawed at each side of the center stator plate. The front rotor plate is removed, making a split-stator variable with 4 plates on each stator and 8 on the



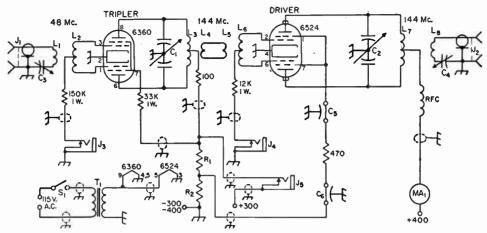


Fig. 17-11—Schematic diagram of the tripler and driver stages of the high-powered 2-meter transmitter.

C₁, C₂—10.5 $\mu\mu$ f.-per-section butterfly variable (Johnson 10LB15).

C₈—25- $\mu\mu$ f. screwdriver-adjustment variable (Hammarlund APC-25).

C₄-25-μμf. miniature variable (Bud LC-1642).

 $C_{\delta r}$, C_{δ} —500- $\mu\mu f$. feed-through bypass (Centralab FT-500).

R₁—11,000 ohms 2 watts (two 22,000-ohm 1-watt resistors in parallel).

 R_2 —50,000 ohms 2 watts (two 100,000-ohm 1-watt resistors in parallel).

 L_1 —2 turn insulated wire around center of L_2 . Twist leads to J_1 and C_3 .

L₂—13 turns No. 20, %-inch diam., %-inch long, center tapped (B & W Miniductor No. 3007).

rotor. This procedure may not be applicable to all 140- $\mu\mu$ f. capacitors, but any method that results in a balanced unit having about 50 $\mu\mu$ f. per section should do.

Construction of the final plate circuit should be clear from Fig. 17-10. Tuning is done with parts of a disk-type neutralizing capacitor (Millen 15011) mounted on ceramic stand-offs $3\frac{1}{2}$ -inches high. These are made of one 1-inch and one $2\frac{1}{2}$ -inch stand off each, fastened together with a threaded insert. Connection to the lines is made with copper or silver strap, $4\frac{1}{2}$ inches from

L_s—3 turns No. 14 enamel, ¾-inch diam., spaced ¼6 inch center-tapped.

 L_4-2 turns No. 18 enamel, same as L_3 , inserted at center. L_5-2 turns No. 18 enamel, same as L_6 , inserted at center.

L₀—4 turns No. 14 enamel, ½-inch diam., turns spaced wire diameter.

 L_7 —2 turns No. 14 enamel, 1-inch diam., spaced ¼-inch.

L₈—1 turn No. 14 enamel between turns of L₇.

J₁, J₂—Coaxial fitting, female (Amphenol 83-1R).

J₃, J₄, J₅—Closed-circuit jack. Insulate J₅ from panel and chassis.

MA1-External meter not shown in photo, 200 ma.

S₁-Toggle switch.

T₁—Filament transformer, 6.3 volts, 3 amp. (UTC S-55).

the plate end. Silver plating of all tank circuit parts is a worth-while investment, though it should not be considered a necessity. A shaft coupling designed for high-voltage service is attached to the threaded shaft of the movable plate, and this is rotated with a shaft of insulating material brought out to the front panel.

A word about the extension shafts is in order at this point. If they are of metal they may have a serious detuning effect in some circuits, even though they are connected through insulating couplings. Bakelite rod is fine, but since the in-

sulating qualities are of no importance, ¼-inch wooden doweling will do the job just as well. Lucite or polystyrene rod will not stand the heat and should not be used.

World Radio H.ssory

Fig. 17-12—Side view of the tripler and driver stages. Coil adjacent to the 6360 tripler tube is the grid coil for the 6524 driver. Plate leads for the driver tube are flexible copper straps, to permit removal of the tube from its socket. Screwdriver adjustment at the lower right is the reactance tuning capacitor for the tripler input link.

144-Mc. Driver Amplifier

The final chassis is aluminum, 10 by 12 by 3 inches, matching up with the driver chassis to fit into a standard 10½-inch rack panel. Complete enclosure is a must for TVI prevention, and it pays dividends in improved stability by providing effective isolation of circuits that tend to give trouble in open layouts.

The enclosures were made by mounting 1/2-inch aluminum angle stock around the edges of the chassis of both units and cutting the sides and covers to fit. It was not intended to cool the driver unit originally, so the enclosure was made of perforated aluminum. The blower for the final provided plenty of air, however, so three holes are made in the walls of the two chassis to allow some of the air flow to go through the driver enclosure as well. The chassis are bolted together where the vent holes are drilled. The main flow is up through the amplifier chassis, around the 4-125As, and out through the 1/4-inch holes drilled in the top cover above the tubes. Holes in the amplifier chassis are drilled to line up with the ventilating holes in the 4-125A sockets. All other holes and cracks are sealed with household cement to confine the air to the desired paths, and bottom covers are fitted tightly to both

The somewhat random appearance of the front panel is the result of the development of the unit in experimental form. A slight rearrangement of some of the noncritical components could be made to achieve a symmetrical panel layout readily enough.

Operation

The two units have their own filament transformers. Plate supply requirements are 300 volts at 50 ma. for the tripler, 400 volts at 100 ma. for the driver, 300 to 400 volts at 75 ma. for the final screens and 1000 to 2500 volts at 400 ma. for the final plates. The driver plates and final screens may be run from the same supply, but more flexibility is possible if they are supplied separately. A variable-voltage supply for final screens is a fine way to control the power level.

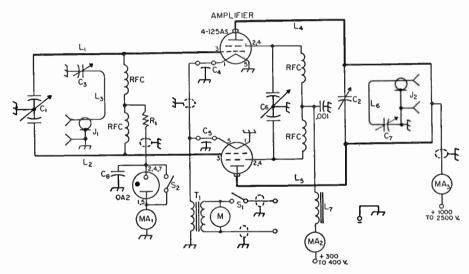


Fig. 17-13—Schematic diagram of the 4-125A amplifier for 144 Mc.

 C_1 —30- $\mu\mu$ f.-per-section split-stator variable (Hammarlund HFD-30X).

C₂—Plate tuning capacitor made from Millen 15011 neutralizing unit; see text and photo.

 C_8 —25- $\mu\mu$ f. miniature variable (Bud LC-1642).

C₄, C₅—500- $\mu\mu$ f. feedthrough bypass (Centralab FT-500).

C_e—Approx. 50-μμf.-per-section split-stator variable. Make from Millen 19140 or Hammarlund MC-140; see text.

 C_7 -25- $\mu\mu$ f. variable (Johnson 25L15).

Ca-0.25-µf. tubular.

R₁-5000 ohms, 10 watts.

L₁, L₂—¼-inch copper tubing, 12 inches long, spaced 1½ inches center to center. Bend around 1½-inch radius, 1 inch from grid end.

Ls—Loop made from 5 inches No. 14 enamel. Portion coupled to line is 1 inch long each side, about % inch from line.

L₄, L₆—½-inch copper tubing 12 inches long, spaced 1½ inches center to center. Bend around 2-inch radius to make line 4 inches high. Attach C₂ 4½ inches from plate end.

Le—Loop made from 7 inches No. 14 enamel. Sides spaced 1½ inches.

L₇-5-h. (min.) 100-ma. rating filter choke.

 J_1 , J_2 —Coaxial fitting, female (Amphenol 83-1R).

MA₁, MA₂, MA₃—External meters, not shown; 100, 200 and 500 ma.

M—Motor-blower assembly, 17 c.f.m. (Ripley Inc., Middletown, Conn., Type 8433).

RFC-V.h.f. solenoid choke (Ohmite Z-144). Four required.

S1-Toggle Switch.

S2-Rotary jack-type switch (Mallory 720).

T₁—Filament transformer, 5-volt 13-amp. (Chicaga FO-513).

In putting the rig on the air the stages are fired up separately, beginning with the tripler. A jack (J_a , in Fig. 17-11) is provided on the front panel for measuring the 6360 grid current. About 1 ma. through the 150,000-ohm grid resistor is plenty of drive. The series capacitor, C_a , in the link can be used as a drive adjustment, if more than necessary is available.

Next plug the grid meter into the 6524 grid current jack, J_4 , and tune the 6360 plate circuit for maximum grid current. If it is higher than 3 to 4 ma. increase the inductance of the grid coil, L_6 , by squeezing its turns closer together. Now apply plate and screen voltage to the 6524, and check for signs of self-oscillation. If the plate circuit is tuned down to the same frequency as that at which the grid coil resonates with the tube capacitance, the stage may oscillate, but if it is stable across the intended tuning range there should be no operating difficulty resulting from a tendency to oscillate lower in frequency, and no neutralization should be needed.

Connect a coaxial line between the driver output and the final grid input preferably with a standing-wave bridge connected to indicate the standing-wave ratio on this line. Tune the driver plate circuit and its series-tuned link for maximum grid current in the final amplifier. Adjust the final grid tuning, C_1 , for maximum grid current, and the series capacitor, C_3 , in the link for minimum reflected power on the s.w.r. bridge. Adjust the coupling loop position for maximum transfer of power, using the least coupling that will achieve this end.

Adjust the screen neutralizing capacitor, C_6 , for maximum final grid current, with the plate and screen voltages off. Do not attempt to run the final stage without load. With a fixed screen supply the screen dissipation goes very high when the plate load is removed or made too light. It is important to meter the screen current at all times. With 4-125As danger to the plates can be detected by their color, but the screen current is the only indication of possible damage to that element.

There is no suitable inexpensive dummy load

for testing a v.h.f. rig of this power level. The best load is probably an antenna. This can be an indoor gamma-matched dipole, fed with coax. Its series capacitor should be adjusted for a standing-wave ratio close to 1:1. The Micromatch can be used in this operation, but adjustments should be made at less than full power. Watch for any sign of heating in the bridge unit.

The position of the coupling loop, L_0 , should be adjusted for maximum transfer of energy to the antenna, keeping the coupling as loose as possible. The series capacitor, C_1 , can be used as a loading adjustment thereafter. If the screen voltage is continuously variable it will be found that there is an optimum value around 325 to 350 volts.

Below are some conditions under which the rig has been operated experimentally:

Stage	$E_{\mathfrak{p}}$	$I_{\mathfrak{p}}$	E_{*e}	Ise	$I_{\mathbf{g}}$
Tripler	300 v.	35 ma.	_	_	1.5 ma.
Driver	400 v.	92 ma.	_	8 ma.	3-4 ma.
Final	1000 v.	300 ma.	400 v.	60 ma.	22 ma.
Final	2000 v.	350 ma.	350 v.	45 ma.	20 ma.
Final	2500 v.	400 ma.	320 v.	40 ma.	18 ma.

The first and third conditions given for the final stage represent extremes, both exceeding the tubes' ratings in some way, so they are not recommended. At low plate voltages the screen has to be run above recommended ratings to make the tubes draw their full rated plate current and operate efficiently. At high plate voltages the screen dissipation drops markedly. The use of 4-125As at a full kilowatt input exceeds the manufacturer's maximum ratings, and is done at the user's risk. To operate safely, the maximum plate voltage for voice work at 144 Mc. should probably not go over 2000. At this level the tubes will handle 600 watts input on voice, and 750 watts on c.w. easily.

Modulation and Keying

Keying is done in the screen circuit of the driver stage, and in the screen and plate circuits of the tripler. Cathode keying of the driver was attempted, but it caused instability troubles, so was abandoned. The screen method makes the

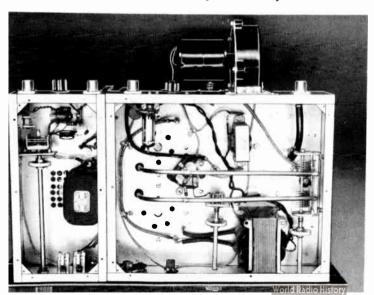


Fig. 17-14—Under-chassis view of the 2-meter transmitter. Tripler grid and plate circuits are at the upper left. Only two of the three jacks on the front panel show in the lower left. The half-wave line used in the 4-125A grid circuit is the main item of interest in the amplifier section. Both units are fitted with bottom covers, to provide shielding and confine the flow of cooling air to the desired areas.

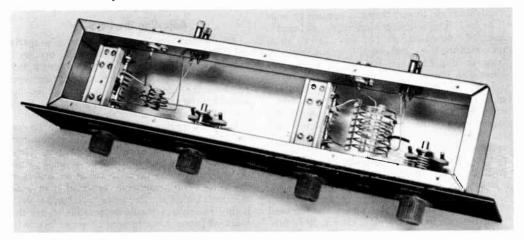


Fig. 17-15—Antenna couplers for 50 and 144 Mc. designed for use with the high-power transmitters on the previous pages.

key hot, so an insulated key or a keying relay must be used in the interest of safety. The keying jack must be insulated from the panel.

Fixed bias for the final amplifier is provided by the VR-tube method. When the tube ignites at the application of drive, the capacitor C_8 charges. Removing excitation stops the flow through the VR tube and leaves the negative charge in the capacitor applied to the amplifier grids. The effectiveness of this system requires a low-leakage capacitor for C_8 .

Modulation is applied to the plates only. A choke of about 10 henrys is connected in the screen lead, or the modulation can be supplied through a screen winding on the modulation transformer. The bypass value in the screen circuit should be low enough to avoid affecting the higher audio frequencies. Occasionally audio resonance in the screen choke may cause a singing effect on the modulation. If this develops, the choke may be shunted with a resistor. Use the highest value that will stop the singing.

In neutralizing the 4-125As it may be found that what appears to be the best setting of the screen capacitor will result in a very large drop in grid current when plate voltage is applied. The setting may be altered slightly, raising the full-load grid current, without adversely affecting the stability of the amplifier. The final check for neutralization is twofold. There should be no oscillation when drive is removed; and maximum grid current, minimum plate current and maximum output should all show at one setting of the plate tuning capacitor. The latter condition may be observed only when the amplifier is operated without fixed bias.

ANTENNA COUPLERS FOR 50 AND 144 MC.

The antenna couplers shown in Figs. 17-15, and at the top of Fig. 17-1, can be used with 52-ohm or 75-ohm coaxial line, and with balanced lines of any impedance from 200 to 600 ohms or

more. They were designed for use with the highpower transmitters described previously, but may be used at any power level.

Construction

The two couplers are identical circuitwise. They are built inside a standard 3 by 4 by 17-inch aluminum chassis, with a bottom plate to complete the shielding. The panel is 3½ inches high. If only one coupler is required, a 3 by 4 by 6-inch utility box can be used. Terminals on the back of the chassis include a coaxial input fitting and a two-post output fitting for each coupler. The circuit diagram, Fig. 17-16, serves for both.

The 50-Mc. coils are cut from commercially

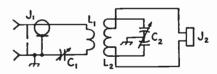


Fig. 17-16—Circuit and parts information for the v.h.f. antenna couplers.

 C_1 —100- $\mu\mu$ f. variable for 50 Mc., 50- $\mu\mu$ f. for 144 Mc. (Hammarlund MC-100 and MC-50).

C₂—35-μμf. per-section split-stator variable, 0.07-inch spacing (Hammarlund MCD-35SX). Reduce to 4 stator and 4 rotor plates in each section in 144-Mc. coupler for easier tuning; see text.

J₁--Coaxial fitting, female.

J2-Two-post terminal assembly (National FWH).

L₁—50 Mc.: 4 turns No. 18 tinned, 1 inch diameter, 1/6inch spacing (Air-Dux No. 808T).

114 Mc.: 2 turns No. 14 enam., 1 inch diameter, 1/6-inch spacing. Slip over L₂ before mounting.

L₃—50 Mc.: 7 turns No. 14 tinned, 1½ inch diameter, ¼ inch spacing (Air Dux No. 1204). Tap 1½ turns from each end.

144 Mc.: 5 turns No. 12 tinned, ½ inch diameter, % inch long. Tap 1½ turns from each end.

available stock, though they can be made by hand if desired. The coupling winding, L_1 , is inserted inside the tuned circuit. The polyethylene strips on which the coils are wound keep the two coils from making electrical contact, so no support other than the wire leads in needed.

Leads to L_1 are brought out between the turns of L_2 , and are insulated from them by two sleeves of spaghetti, one inside the other. Do not use the soft vinyl type of sleeving, as it will melt too readily if, through an accident to the antenna system, the coil should run hot. In the 144-Mc. coupler the positions of the coils are reversed, with the tuned circuit, L_2 , at the center, and the coupling coil outside it.

Similar tuning capacitors are used in both couplers, but some of the plates are removed from the one in the 144-Mc. circuit. This provides easier tuning, though it has little effect on the minimum capacitance, and therefore on the size of the coil.

Adjusting the Couplers

An antenna coupler can be adjusted properly only if some form of standing-wave bridge is connected in the line between the transmitter and the coupler. If it is a power-indicating type, so much the better, as it then can be used for adjusting the transmitter loading, and the work can be done at normal transmitter power.

With the bridge set to read forward power, adjust the coupler capacitors and the transmitter tuning roughly for maximum indication. Now set the bridge to read reflected power, and adjust the antenna coupler capacitors, first one and then the other, until minimum reflected power is achieved. Unless the line input impedance is very highly reactive, it should be possible to get the reflected power down to zero, or very close to it. Adjustment of the coupler is now complete. Tuning for maximum transfer of power from the transmitter is done entirely at the transmitter.

SIMPLE TRANSMITTERS FOR 50 AND 144 Mc.

The two transmitters shown in Fig. 17-17 are designed to fill several needs. They can be used as complete r.f. sections for 50 and 144 Mc., or they serve well as exciters for higher-powered amplifiers. Depending on the final amplifier tubes chosen, the power level can be anything from under 10 to as much as 50 watts input. At low power they are well suited to mobile and portable applications. Provision is included for c.w. operation. Modulation equipment for the transmitters can be found elsewhere in this Handbook.

The designs are as similar as possible, mechanically and electrically, the tubes and many of the parts being interchangeable. They are built on standard 5 by 10 by 3-inch aluminum chassis, with shield covers of perforated aluminum over their output stages. These shields are an aid to TVI prevention, and they provide protection for the tuned circuits mounted topside.

Circuitry

Both transmitters employ third-overtone crystal oscillators of simple design. Crystals should be in the range between 8.34 and 9 Mc. or 25 and 27 Mc. for 50-Mc. operation. For 144-Mc. work the crystals are 8 to 8.22 Mc. or 24- to 24.66 Mc. If the feedback in the oscillator circuit is adjusted to make conventional 8-Mc. crystals oscillate on their third overtone, crystals in the 24-to 27-Mc. range will also work. If only the latter (third overtone) type crystals are used, the feedback can be set at a lower level. This is controlled by the position of the tap on the coil, L_1 . Crystals in the 8-Mc. range that multiply out close to a band edge should be checked carefully under actual operating conditions in the equipment, as the oscillation frequency may not be exactly three times that marked on the holder.

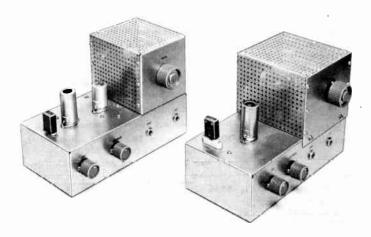


Fig. 17-17—Transmitters far 50 (right) and 144 Mc. Designs are similar and many parts are interchangeable. Pawer ratings may be varied fram under 10 ta mare than 50 watts input, depending an tube used in the autput stage.

The oscillator is the triode portion of a 6U8 triode-pentode. The pentode section is a frequency multiplier, doubling to 50 Mc. in the 6-meter transmitter and tripling to 72 Mc. in the 144-Mc. one. The doubler section drives the output stage in the 50-Mc. rig. An extra stage is required to reach 144 Mc. This is a 6BC4 triode used as a doubler from 72 to 144 Mc. The output stage is a 2E26, where the input power is to be under 25 watts. A 6146 may be used at higher power levels. There is substantially no difference in the driving power required by these tubes, and they can be interchanged with only slight readiustment of the tuned circuits.

When the exciters are to drive an amplifier using an 829B or a 5894, the output tube should be a 2E26. The plate supply voltage need be no more than 300 volts, and as little as 200 may suffice. When the units are used alone the final plate voltage should be 300 for a 2E26, or 400 to 500 for the 6146. If the latter tube is used in exciter service the output will be sufficient to drive tetrode amplifiers of up to 1 kilowatt input.

Construction

Arrangement of parts is not particularly critical, though it would be well for the inexperienced constructor to follow the layouts shown closely in all principal details. Layout drawings, Figs. 17-21 and 17-25 are provided for those who may wish to make exact duplicates. The dimensions given apply only when identical parts to those of the original are purchased. Check sockets, particularly, for mounting dimensions before following the layouts in complete detail.

The shield covers of the two transmitters were made in slightly different ways, to illustrate differing techniques. The method used in the 50-Mc. unit may be the easier of the two for amateurs not well equipped with metal working tools. The front and back plates are 5 inches wide and 4½ inches high. The bottom half inch of each plate overlaps the main chassis, and is fastened to it with self-tapping screws. The cover is made of perforated aluminum, available in many hardware stores. This can be cut and bent with simple tools. The box thus made is 4 inches high, 5 inches wide and 5 inches deep.

The perforated cover is made larger than these dimensions by about 3% inch on all sides. The extra material is bent over so that the front and back plates can be fastened to it with self-tapping screws.

In the 144-Mc. transmitter the edges of the front and back plates are bent over, so that the cover need be only a plate bent into an inverted U. The enclosure is 4 by 4 by 5 inches in size. The bent-over edges of the front and back walls show plainly in the top view, Fig. 17-22.


Building the 50-Mc. Transmitter

Looking at the bottom view of the 50-Mc. transmitter, Fig. 17-19, we see the oscillator tuning capacitor, C_1 , and the plate coil, L_1 , at the right. Next to the left is the 6U8 socket. The doubler plate coil, L_2 , and the amplifier grid coil, L_3 , are between the tube sockets. Note that these coils are mounted side by side, with their axes vertical. Their position with respect to each other is adjusted for maximum grid drive, with the optimum spacing being about one coil diameter. The amplifier screen-dropping resistor (4 1-watt resistors in parallel) is just above the 2E26 socket. Jacks for cathode keying and grid-current measurement occupy the left side of the front wall, as seen in Fig. 17-19.

Arrangement of parts inside the shield compartment can be seen in Fig. 17-18. The amplifier tube, a 6146 in this instance, is at the left side of the box. The plate tuning capacitor, C_4 , is near the middle of the front wall. The antenna loading capacitor, C_5 , and the coaxial output fitting, J_1 , are on the rear wall. The power connector strip in centered on the rear wall of the chassis. Note the parasitic choke, L_4 , between the tube and the plate coil. This is wound on the resistor in parallel with it. The plate coil, L_5 , is mounted with its axis vertical. The output coupling coil, L_6 , is close against the bottom of L_6 , and insulated from it by spaghetti sleeving.

The type of socket used for the amplifier tube is important. Do not use the common moulded socket with an elevated grounding ring having 4 lugs spaced around its circumference. These lugs may introduce coupling between the circuits grounded or bypassed thereto, causing instability

Fig. 17-18—Laaking dawn inside the amplifier shield. The plate tuning capacitar, C4, is an the frant wall, with the laading adjustment, C5, an the rear wall. Parasitic suppressar and plate cail cannect ta tap statar bar af C4. Black lead, lawer left, runs thraugh a rubber grammet ta the neutralizing capacitar, belaw the chassis.

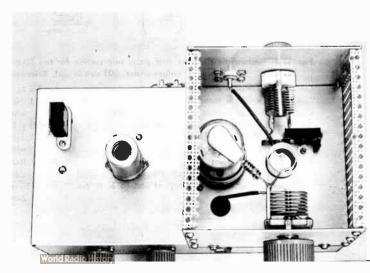

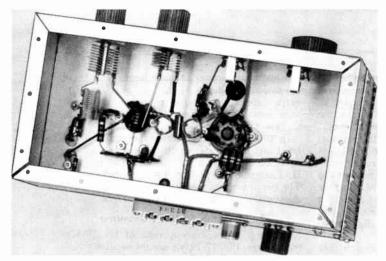


Fig. 17-19—Bottom view of the 50-Mc. transmitter. Note positions of the various coils, particularly those in the doubler plate and amplifier grid circuits, near the middle of the assembly.

that cannot be neutralized out. A Millen ceramic socket was used in the original, but any type that does not have the separate grounding lugs and ring is suitable. Grounding should be done to lugs under the nuts used for mounting the socket. It is imperative that bypass capacitor connections be made with virtually no leads at all, particularly in the amplifier circuits. Note that each cathode lead is bypassed separately. This is important where the cathode is keyed, as in this instance.

The neutralizing capacitor, C_8 , is a type intended for mounting with one side grounded, so another mounting method must be provided in this application. A small tab of copper about $\frac{3}{8}$ by 1 inch in size supports the capacitor, the end of the tab being soldered to a lug on the 3-lug tie-point strip nearest the socket. The $150-\mu\mu f$. bypass at the low end of L_8 connects

from that point to the ground lug at the middle of the terminal strip. The lead from the sleeve of C_s is a stiff wire that passes up through a $\frac{1}{2}$ -inch hole in the chassis to the lower stator terminal of the plate tuning capacitor, C_4 . The latter is mounted with its stator terminals one above the other.

Adjustment and Operation

For initial tests a power supply capable of delivering 200 to 300 volts d.c. at about 100 ma., and 6.3 volts a.c. or d.c. at 1.7 amperes may be used. (Only 1.25 amp. will be needed if a 2E26 is used.) The negative side of the plate supply and one side of the heater supply are connected together. The oscillator is tested first. This is done by feeding plate power to the 4700-ohm resistor in the oscillator plate lead only, disconnecting the doubler plate-screen lead temporarily.

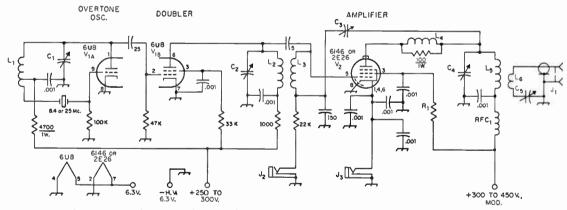


Fig. 17-20—Schematic diagram and parts information for the 50-Mc. transmitter. Capacitors are ceramic unless specified. Values under .001 are in μμf. Resistors ½ watt unless specified.

 C_1 -50- $\mu\mu$ f. variable (Johnson 157-4).

 C_2 -25- $\mu\mu$ f. variable (Johnson 157-3).

 C_{a} —0.5 to 3 $\mu\mu$ f. ceramic trimmer (Erie 3139D).

 C_4 —25- $\mu\mu$ f. variable (Jahnson 167-2).

 $C_6-75 \mu\mu f$. (Jahnson 157-5).

L₆-75 μμτ. (Jannson 157-5) J₁-Coaxial chassis fitting.

J₂, J₃—Closed-circuit jack.

L₁-14 t. No. 20 tinned, ½-inch diam., % inch long, tapped at 4½ t. from crystal end (B & W No. 3003).

L2-61/2 t., 7/16 inch long, similar to L1.

La-71/4 t., 1/2-inch long, similar to L2.

L4—5 t. No. 20 waund on and spaced to fill 100-ohm 1watt resistor.

L=31/2 t. No. 14 tinned, 34-inch i.d., 1/2-inch long.

L_e—2 t. No. 14, similar to and at cold end of L₅. Cover with spaghetti sleeving.

R₁—37,500 ohms, 4 watts (4 150,000-ohm 1-watt resistors in parallel).

RFC₁—Single-layer v.h.f. choke, 2 to 7 μh. (Ohmite Z-50 or National R-60).

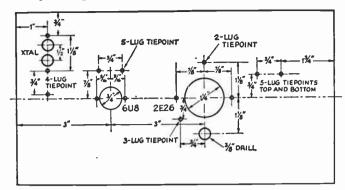


Fig. 17-21—Layout drawing of the 50-Mc. chassis top. Precise duplication is not important, though the general parts layout should be followed. Hole sizes may vary with different types of sockets.

Apply heater voltage only, and allow the tubes to warm up for 30 seconds or more. Connect a 100-milliampere meter in the lead to the plate supply, and apply power. Swing the oscillator tuning capacitor, C_1 , through its range. There will be a sharp dip in current to about 10 ma. as the crystal starts oscillating.

Check the frequency of oscillator with a griddip meter or wavemeter. If you have a receiver that tunes the 25- or 50-Mc. region, listen for the oscillator to determine if it is crystal controlled. The frequency will change only slightly, if at all, when the circuit is tuned through resonance. Listen to the note with the receiver beat oscillator on, and place a screwdriver or other metal object near the tuned circuit. There should be very little change in frequency. Should the frequency change more than a few hundred cycles under these tests the oscillator may not be controlled by the crystal.

Self-oscillation is the result of too much feed-back. This can be corrected by moving the tap lower on the coil. Too little feedback may prevent the oscillator from working at all, or it may drop out of oscillation when loaded appreciably by the following stage. The cure is to raise the tap position on the coil.

When the oscillator is working correctly, remove the milliammeter from its power lead and connect it between the high-voltage source and the junction of the screen resistor and 1000-ohm resistor at the low end of the plate coil. Plug a low-range milliammeter, preferably 5 or 10 ma., into the grid current jack, J_s , of the amplifier. Apply plate voltage to the first two stages and tune the double plate circuit for maximum grid current, as read on the meter in J_s . This should be at least 2 ma., with a 250-volt plate supply. Try varying the separation between L_s and L_s , leaving spacing at the point that yields greatest grid current. Retune the doubler plate circuit as the spacing is changed.

Next comes neutralization of the amplifier. With drive on, but no plate or screen voltage, tune the amplifier plate circuit through its range, watching the grid current meter. There may be a downward dip in grid current when the plate circuit is resonated. Adjust the neutralizing capacitor, C_3 , a turn or two and check the grid current dip again. If there is less change than before, the

adjustment was in the right direction. Continue in this way until no downward movement can be seen in the grid current as the plate circuit is tuned through resonance.

If neutralization cannot be achieved, a different value of bypass will be required at the low end of $L_{\rm a}$. If the neutralizing capacitor is at minimum setting when neutralization is approached, a larger value of bypass will be needed. Try 220 $\mu\mu\rm f$. as a next step.

Power may now be applied to the final amplifier. This can be from the same source as has been used for the earlier tests, for the time being. The meter may be removed from the doubler power lead and connected between the junction of the r.f. choke, RFC₁, and screen resistor and the terminal on the back of the transmitter. This will measure the combined plate and screen current drawn by the amplifier. The meter may also be plugged into the cathode jack, where it will read combined plate, screen and grid current.

A light bulb of about 25 watts or more can be connected to a coaxial fitting and used as a dummy load in place of an antenna. This will not represent a 50-ohm load, so the tuning of the stage will not be the same as when a matched antenna system is used, but it will do for initial tests, and it will give a rough indication of power output.

Apply plate-screen power to all stages, and tune the plate circuit of the amplifier to the point where plate current dips the lowest. Now adjust the series capacitor, retuning the plate capacitor, until maximum brilliance is seen in the load lamp. Check carefully for any sign of oscillation in the amplifier. Remove the crystal from its socket briefly, while watching the amplifier grid current. This current and the amplifier output should drop to zero, and remain there regardless of the tuning of any of the transmitter circuits. Should grid current appear with the oscillator inoperative, recheck neutralization. The grid-current dip may be only an approximate indication of neutralization, so the adjustment may have to be touched up after power is applied to the amplifier. Turn off power as a safety measure when this is done. With perfect neutralization, maximum grid current, minimum plate current and maximum output will all occur at the same setting of the amplifier

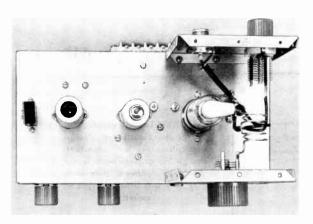


Fig. 17-22—Top view of the 144-Mc. transmitter with shield cover removed. A 2E26 is shown in the amplifier socket.

plate circuit tuning. Perfection in this respect may not be possible, but there should be no sign of oscillation (grid current in the amplifier when the drive is removed) at any setting of the tuning controls.

When the rig is operated with a properly designed antenna the settings of the amplifier plate and antenna loading adjustments may be somewhat different from those obtained with a lamp load. Both should be adjusted for maximum power delivered to the antenna. This can be recorded on a field-strength meter, giving a relative indication of the power radiated by the antenna. Better than this is a power-indicating standing-wave bridge, which may be left connected in the line to the antenna at all times, thus giving a constant indication of transmitter operation.

Final operating conditions for the transmitter

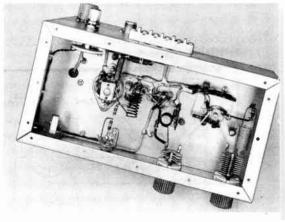


Fig. 17-23—Bottom of the 144-Mc. transmitter, with oscillator-tripler at the right. Doubler stage is near the middle of the chassis and amplifier at the left.

will depend on the supply voltage and final tube used. With a 300-volt supply the oscillator plate current will run about 10 ma. with the oscillator operating properly, and 17 ma. with the crystal out of oscillation. The double plate-screen current is about 12 ma. Amplifier grid current will be at least 3 ma. without plate and screen voltage, and around 2.5 ma. with the amplifier operating under load. These values will be slightly lower with a 250-volt supply. Platescreen current to the amplifier will depend on the power level and tube. With a 2E26 at 300 volts the current will be about 20 ma. at resonance, with no load, and 95 ma. off resonance. Loaded for maximum efficiency the 2E26 plate and screen current will be about 60 ma. With a 6146 at 450 volts the loaded plate and screen current will be about 120 ma.

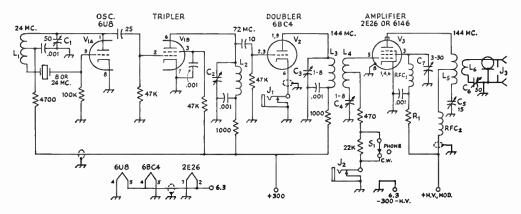


Fig. 17-24—Schematic diagram and parts information for the 144-Mc. transmitter.

 C_1 , C_6 —50- $\mu\mu$ f. variable (Johnson 157-4).

 C_2 , C_5 —15- $\mu\mu$ f. variable (Johnson 157-2).

C₈, C₄—1-8- $\mu\mu$ f. plastic trimmer (Erie 532-10).

J1, J2-Closed-circuit jack.

J₈—Coaxial chassis fitting.

L₁—14 turns No. 20 tinned, ½-inch diam., ½ inch long tapped at 4 turns from crystal end (B & W No. 3003).

L₂--5¾ turns No. 18 enam., 7/16-inch diam., ¾ inch lona.

Le-2¾ turns No.18 enam., 7/16-inch diam., ¼ inch long.

L₄—6 turns No. 18 enam., 7/16-inch diam., % inch long, center tapped.


L₆—4 turns No. 14 tinned, ¾-inch diam., turns spaced 2 diameters. Make extra space at center for L₆; see Fig. 17-22.

L₆—1 turn No. 14 enamel, 34-inch diam. Cover with insulating sleeving and insert at center of L₅. R₁—33,000 ohms, 3 watts (3 100,000-ohm 1-watt resistors in parallel).

RFC1-7-µh, solenoid choke (Ohmite Z-50).

RFC₂-1.8-µh. solenoid choke (Ohmite Z-144).

S₁—S.p.s.t. switch, any type.

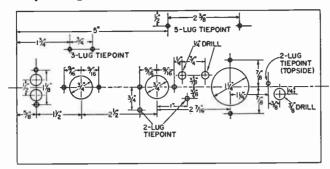

The 50-Mc. transmitter was described originally in QST for October, 1958.

The 144-Mc. Transmitter

Layout and testing of the 144-Mc. unit are very similar to the 50-Mc. model already described, so only the points of difference will be covered in this part of the text. Looking at the bottom view, Fig. 17-23, the oscillator tuned circuit is at the far right. The tripler plate capacitor, C_2 , is next on the front wall. The 6U8 socket is between these two capacitors, on the center line of the chassis. The 6BC4 doubler socket is approximately in the middle of the chassis. The coil mounted vertically at the right and slightly below the 6BC4 socket is the tripler plate coil, L_2 .

The doubler plate coil, L_s , and the amplifier grid coil, L_4 , are mounted on a common center line and close together, making them appear as one coil in the photograph. The top end of L_s , as seen in the schematic diagram, Fig. 17-24, is toward the back of the chassis. The grid end of L_a is toward the front. Capacitors C_s and C_4 are cylindrical plastic trimmers. They are at either side of and just above the upper end of L_s .

The amplifier socket is at the left. The screen tuning capacitor, C_7 , is mounted across the socket. Screen voltage is fed through the r.f. choke just above the socket. The switch for shorting out the grid leak when c.w. is used is in the upper left corner of the photograph. The two jacks on the front wall are for keying (far left) and grid current measurement.

Circuit differences between the two units, aside from the inclusion of the extra multiplier stage in the 144-Mc. model, arise mainly from the effects of tube and circuit capacitances at the higher frequency. Tube capacitances load the tuned circuits heavily, so series-tuned circuits are used in the amplifier stage. It will be seen that the keying jack is connected in the cathode of the doubler stage instead of in the amplifier cathode lead. It is difficult to bypass the amplifier cathode completely at 144 Mc., and the insertion of the keying jack in that position would cause oscillation. Screen bypassing is a similar problem, as conventional bypassing methods are ineffective at this and higher frequencies. Bringing the screen to ground potential requires a critical value of capacitance, so a trimmer (C_7) is connected from screen to ground.

Fig. 17-25—Layout drawing of the 144-Mc. chassis.

Adjustment Procedure

The power supply for testing the 144-Mc. transmitter should deliver 6.3 volts at 1.6 amperes if a 2E26 amplifier tube is used. With a 6146 it should be capa-

ble of supplying 2 amperes. Initially 250 to 300 volts at 150 ma, will do for the plate supply. Final plate voltage for a 6146 may be as high as 500 volts.

Testing the first two stages is similar to that outlined for the 50-Mc. transmitter, except for the frequencies involved. Make sure that the oscillator is between 24 and 24.66 Mc., and that the pentode section of the 6U8 multiplies this frequency by 3. Tune the tripler plate circuit, L_2 - C_2 , for maximum output, as indicated by a 2-volt 60-ma. pilot lamp coupled to the cold end of L_2 with a single-turn loop of insulated wire about the diameter of the coil.

Next apply plate voltage to the 6BC4 doubler, and tune it for maximum amplifier grid current. Adjustment of C_3 and C_4 will interlock to some extent, but be sure that each is tuned for maximum grid current, as read in I_2 . The switch S_1 can be in either position for this adjustment, though the grid current will be much higher if it is in the closed position.

Neutralization is done similarly to the manner outlined for the 50-Mc. transmitter, except that the setting of the screen capacitor, C_7 , is the means by which it is achieved. If stability is approached as C_7 reaches maximum capacitance, a larger trimmer will be needed. Experimentation with the value of the r.f. choke in the screen lead may also be helpful. A variation of the neutralization system shown is the use of a critical value of inductance in the screen lead, and the elimination of C_7 . Grid current, when neutralization is completed, should be at least 1.5 mawith S_1 in the open position. Go over all adjustments carefully, and experiment with the spacing between L_8 and L_4 if the grid drive is low.

The balance of the testing is similar to the 50-Mc. procedure. Plate current for the 6BC4 doubler will be about 25 ma. Amplifier grid current should be all that can be obtained, but preferably not below 1.5 ma. under full load. Should it be less than 1.5 ma., running the amplifier at slightly less than full loading may make it possible to get satisfactory output and still retain good modulation characteristics.

Amplifier plate current at resonance with no load will be higher than on 50 Mc., and the output will be lower. Efficiency will be lower with a 6146 than with a 2E26, but the higher plate dissipation rating of the 6146 may make its use desirable if more output is needed than can be

obtained with the 2E26. Either transmitter can be used in mobile service. For 6-volt cars the tubes can be as shown. Twelve-volt equivalents of all the tube types are now available for cars with 12-volt systems.

Modulation and Keying

For voice work a modulator is required. This should have a power output of approximately half the input to the final amplifier. Several suitable modulators are shown in other chapters of this Handbook. The plate and screen current of the amplifier are run through the secondary of the modulator output transformer. If the transmitter is to run at low power, a single 300-volt supply can be used for all stages, including the modulator, if it has a sufficiently high current rating.

Keying methods differ for the two r.f. units. The 50-Mc. transmitter is keyed for c.w. by breaking the cathode lead. This would cause instability if applied to the 144-Mc. transmitter, so the latter is keyed in the cathode of the doubler

stage. Fixed bias must be applied to the final amplifier grid, to keep the plate current to a safe value. The voltage required will depend on the plate voltage applied to the final. The plate current need not be cut completely off, but merely held to less than the plate dissipation rating for the tube used. A 22½ volt battery is sufficient for plate voltages up to 400. The simplest way to apply bias, for occasional c.w. use, is to plug it into the grid current jack. The positive terminal of the bias battery should connect to the ground side of the plug.

The switch S_1 cuts out the 27,000-ohm grid resistor, so that the grid bias will not be excessive when fixed bias is applied. The rig can be operated in this manner (fixed bias plus the smaller of the two grid resistors) on voice, if it is desirable or convenient to do this. The grid current is so low that the bias battery will last almost indefinitely, and a small hearing aid size is suitable. It can be mounted inside the chassis and wired into the circuit permanently, where more frequent c.w. operation is expected.

SIMPLE TRANSMITTER FOR 220 AND 420 Mc.

The transmitter in Figs. 17-26-17-29 is for the newcomer who wants to start with simple gear, going on to something better when he has gained construction and operating experience. It is built in two units, with the idea that the modulator can be retained when the r.f. portion is discarded.

The r.f. section is a simple oscillator with two 6AF4 or 6AT4 tubes in push-pull. Its plate circuit is changed from a quarter-wave line at 220 Mc. to a half-wave line at 420 Mc. by plugging in suitable terminations at the end of the tuned circuit

Because the oscillator is modulated directly it will have considerable frequency modulation, and the signal will not be readable on selective receivers unless the modulation is kept at a very low level. Where a broader receiver is in use at the other end of the path a higher modulation level can be employed.



Fig. 17-26—The simple transmitter for 220 and 420 Mc. is made in two parts. The modulator, left, may be retained for use with more advanced r.f. sections than the simple oscillator shown at the right. The two units may be plugged together or connected by a cable.

Construction

The two units are built on identical 5 by 7 by 2-inch aluminum chassis, connecting by means of a plug on the oscillator and a socket on the modulator. Power is fed through a similar plug on the back of the modulator. Arrangement of parts in the modulator is not critical, but the oscillator should be exactly as shown.

Fig. 17-27—Bottom view of the oscillator unit, showing the two-band tank circuit. The line terminations, with their protecting caps removed, are in the foreground. At the left is the 220-Mc. plug, with the 420-Mc. one at the right.

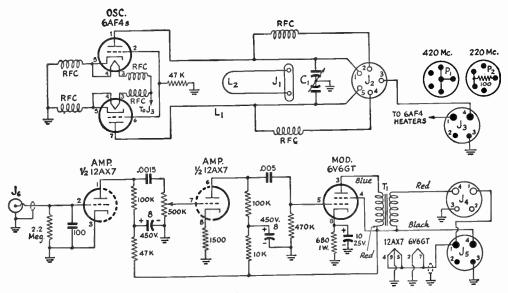


Fig. 17-28—Schematic diagram and parts information for the two-band oscillator and modulator.

- C₁—10.5-μμf.-per-section butterfly variable (Johnson 10LB15).
- L₁—2 3½ inch pieces No. 12 tinned, spaced ½ inch.

 Bend down ¾ inch at tube end and ½ inch at
 socket end. R.f. chokes connect ¾ inch from
 bend at tube end. Connect C₁ at 1 inch from
 bend at socket end.
- L₂—Hairpin loop 2¼ inches long and ½ inch wide, No. 16, covered with insulating sleeving.
- J₁—Crystal socket used for antenna terminal.
- J₂-5-contact ceramic socket (Amphenol 49-RSS5).

The modulator is designed for a crystal microphone. It delivers 3 to 10 watts output, depending on the plate voltage and whether a 6V6 or 6L6 tube is used. It may be considered as a long-term investment that will be suitable for use with any r.f. section of up to 20 watts input that may be constructed at a later date.

Sockets for the tubes are one inch apart center to center, $2\frac{3}{16}$ inch in from the end of the chassis. C_1 is at the exact center of the chassis,

with J_2 1½ inches to its left, as seen in Fig. 17-27. At the far left is a crystal socket, used for the antenna terminal, J_1 . One-inch ceramic standoffs are mounted on the screws that hold J_2 in place. These support the antenna coupling loop, L_2 .

J₃, J₅—4-contact male fitting (Amphenol 86–RCP4).
J₄—4 contact female chassis fitting (Amphenol 78–S4 or RS4).

- Je-Microphone connector (Amphenol 75-PC1M).
- P₁—5-contact male cable connector (Amphenol 86-PM5) with Pins 2, 3 and 4 joined together.
- P₂—Same as P₁, but with Pins 1 and 5 joined. Connect 100-ohm resistor between these and Pin 3.
- RFC (6 required)—12 turns No. 28 enamel close-wound on high-value 1-watt resistor.
- T₁-10-watt modulation trans. (Merit A-3008).

Testing and Use

A power supply delivering about 200 volts d.c. at 50 ma. or more and 6.3 volts at 1 amp. or more is needed. Plug the units together or connect them by a cable. With a cable, a milliammeter may be connected between the No. 4 pins to measure the oscillator plate current. Otherwise the meter should be connected temporarily between Pin 4 of J_8 and Pin 3 of J_2 , in place of the wire shown in Fig. 17-28.

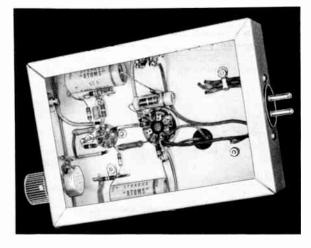


Fig. 17-29—Looking at the underside of the modulator.

Plate current should be about 25 to 30 ma. If the stage is oscillating there will be a fluctuation in current as the plate line is touched with an insulated metal object. Do not hold the metal in the hands for this test! The frequency is best checked by means of Lecher wires, a technique that is covered in the chapter on measurements.

With the dimensions given the range with P_1 plugged in should be about 405 to 450 Mc. With P_2 plugged in the frequency should fall within

the 220-Mc. band with C_1 set in the same position as it was for the middle of the 420-Mc. band. Some alteration of the connection point for C on L_1 may be necessary to achieve this.

In using the transmitter it is well to stay between 221 and 224 Mc. to avoid out-of band operation. On 420, keep the transmitter below 432 Mc. to avoid interference with the high-selectivity work that is done between 432 and 436 Mc. (More details on this rig in Dec., 1954, QST.)

A 40-WATT TRANSMITTER FOR 220 Mc.

The crystal-controlled transmitter shown in Figs. 17-30 and 17-32 will run 30 to 40 watts at 220 Mc. Referring to Fig. 17-31, a simple overtone oscillator circuit uses one half of a 12AT7 dual triode. The crystal may be between 8.15 and 8.33 Mc. or 24.45 and 25 Mc. In either case, the frequency of oscillation is in the latter range, as the crystal works on its third overtone. The second half of the 12AT7 is a tripler to 73 to 75 Mc. This stage has a balanced plate circuit, so that its output may be capacitively coupled to the grids of a second 12AT7, working as a push-pull tripler to 220 Mc. The low side of the first tripler plate circuit has a balancing capacitor, C3, so that a capacitance equal to the output capacitance of the 12AT7 can be added to that side of the circuit. Without this the two halves of the pushpull tripler may receive unequal drive, and one half of the tube will run hotter than the other.

The plate circuit of the push-pull tripler is inductively coupled to the grid circuit of an Amperex 6360 dual tetrode amplifier that runs straight through on 220 Mc. Similar inductive coupling transfers the drive to the grid circuit of the final amplifier stage, an Amperex 6252 dual tetrode. This tube is a somewhat more efficient outgrowth of the 832A, which may also be used, though with lower efficiency and output. Base connections are the same for both tubes.

The grid return of the 6252 is brought out to the terminal strip on the back of the unit, to allow for connection of a grid meter. Both this point and the tip jack in the 6360 grid return have 1000-ohm resistors completing the grid returns to ground, so that operation of the stages is unaffected if the meters are removed.

Instability in tetrode amplifiers for v.h.f. service may develop as a result of the ineffective bypassing of the screen. In the case of the 6360 stage stable operation was obtained with no by-

passing at all, while on the 6252 a small mica trimmer was connected directly from the screen terminal to ground. It is operated near the minimum setting.

Construction

The transmitter is built on an aluminum plate 6 by 17 inches in size. This screws to a standard chassis of the same dimensions, which serves as both shield and case. Cut-outs about three inches square are made in the chassis and base plate, above and below the tube, to allow for ventilation. These openings are fitted with perforated aluminum or screening to preserve shielding. The case should be equipped with rubber feet, to avoid marring the surface it rests on, and to allow air circulation around the tube.

The tube sockets and all the controls except the tuning capacitor of the oscillator are mounted along the center line of the cover plate. The 220-Mc. stages are inductively coupled, using hairpin loop tank circuits the dimensions of which are given in Fig. 17-33. The tuning range of these circuits is affected by the widths of the loops as well as their length, so some variation can be had by squeezing the sides together or spreading them apart.

It is important that the method of mounting the 6252 socket be followed closely. An aluminum bracket about 2% inches high and 4 inches wide supports the socket. Note that the socket and tube are on the same side of the plate. Holes are drilled in the plate in line with the control grid terminals to pass the grid leads. These holes are 3%-inch diameter, and are equipped with rubber grommets to prevent accidental shorting of the grid leads to ground. The shape of the grid inductance should be such that its leads pass through the centers of the holes. The socket is supported on 5%-inch metal pillars.

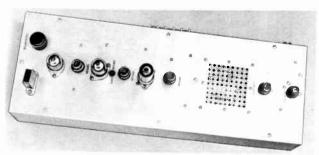


Fig. 17-30—Top view of the 220-Mc. transmitter. Final amplifier tube is inside the chassis, below the screened ventilation hole. Power connections, keying jack and output terminal are on the back of the chassis.

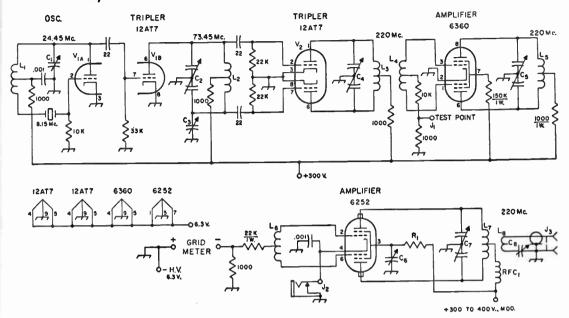


Fig. 17-31—Schematic diagram and parts information for the 220-Mc. transmitter. Capacitor values below 0.001 μ f. are in μ uf. Resistors $\frac{1}{2}$ watt unless specified.

 C_1 —50- $\mu\mu$ f. miniature variable (Hammarlund MAPC-50-B).

C₂, C₅, C₅—8- $\mu\mu$ f. miniature butterfly variable (Johnson 160-208).

Ca. Ca-3-30-uuf, mica trimmer.

C₇—Butterfly variable, 1 stator and 1 rotor (Johnson 167–21, with plates removed).

 C_8 —15- $\mu\mu$ f. miniature variable (Hammarlund MAPC-15-B).

J₁—Tip jack, insulated.

J₂-Closed-circuit phone jack.

Ja-Coaxial chassis fitting, SO-239.

L1-15 t. No. 20 tinned, 1/2-inch diam., 1 inch long (B &

It may be necessary to bend the socket lugs slightly to keep them from shorting to the mounting plate. The heater lead comes to the top of the plate, and the cathode lead bends around the bottom of it.

Power leads are made with shielded wire, and are brought out to a terminal strip on the back of the chassis. These leads and the coax to the output connector should be long enough so that the plate on which the transmitter is built can be lifted off the chassis and inverted as shown in the photograph.

Adjustment

Initial tests should be made with a power supply that delivers no more than 250 volts, and as little as 150 to 200 volts can be used. If the voltage is more than 250, insert a 5000-ohm 10-watt resistor in series with the power lead temporarily. Plate voltage should be applied to the various stages separately, starting with the oscillator, making sure that each stage is working correctly before proceeding to the next.

W Miniductor No. 3003). Tap at 4 turns from crystal end; see text.

L₂—12 t. No. 18 tinned, ½-inch diam., 1 inch long, center-tapped.

L_s, L_s, L_s, L_s—U-shaped loops No. 18 enam., centertapped. Dimensions given in Fig. 17-33.

L₇-2 t. No. 14 enam., 1-inch, 1-inch diam., leads % inch long. Center-tapped, space turns ½ inch apart.

L_e—1 t. No. 18 enam., inserted between turns of L₇. Cover with insulating sleeving.

R₁—23,500 ohms, 2 watts. (Two 47,000-ohm 1-watt resistors in parallel.)

RFC₁-25 t. No. 28 enam. on 1-watt high-value resistor.

A milliammeter of 50- to 100-ma, range should be connected temporarily in series with the 1000-ohm resistor in the oscillator plate lead. When power is applied the current should be not more than about 10 ma. Rotate C1 and note if an upward kick occurs, probably near the middle of the range of C1. At this point the stage is oscillating. Lack of oscillation indicates too low feedback, or a defective crystal. Listen for the note on a communications receiver tuned near 24 Mc., if one is available. There should be no more than a slight change in frequency when a metallic tool is held near the tuned circuit, or when the circuit is tuned through its range. The note should be of pure crystal quality. If there is a rough sound, or if the frequency changes with mechanical vibration, the oscillator is not controlled by the crystal. This indicates too much feedback, and the tap on the coil, L_1 , should be moved near the crystal end.

The proper amount of feedback is the lowest tap position that allows the oscillator to start readily under load. If 24-Mc. crystals are used,

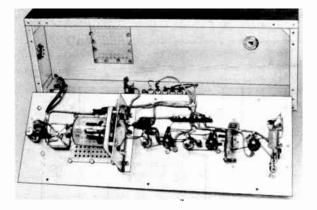


Fig. 17-32—Interior view of the 220-Mc. transmitter. All r.f. components are mounted on an aluminum plate, which is screwed to the top of a standard 6 × 17-inch chassis. Screen trimmer capacitor C₀ mounts on the tube socket mounting plate.

The crystal socket and the oscillator coil and capacitor are at the far right. Next is the first 12AT7 socket. Next to the left is the first tripler plate coil, mounted over its trimmer, with the mica balancing padder, C_8 , above. The 12AT7 tripler, the test point, J_1 , the tuning capacitor C_4 , the tripler plate and amplifier grid loops, L_8 and L_4 , the 6360 socket, the 6360 plate and amplifier grid loops, the 6252, and its tuned circuits follow in that order. The series capacitor, C_8 , and the coaxial lead to the output connector, J_8 , are at the far left.

the tap can be lower on the coil than with 8-Mc. crystals. When 8-Mc. crystals are operated on the third overtone, as in this case, the frequency of oscillation may not be exactly three times that marked on the crystal holder.

Now apply plate voltage to the second half of the 12AT7, again using a temporary plate meter connected in series with the 100-ohm decoupling resistor that feeds plate power to L_2 . Current will be about 10 ma., as with the oscillator. Tune C_2 for maximum output. This can be determined by brilliance indication in a 2-volt 60-ma. pilot lamp connected to a 1-turn loop of insulated wire coupled to L_2 . Check the frequency of this stage with a wavemeter.

Now connect a low-range milliammeter (not more than 10 ma.) between the test point. J_1 , and ground. Apply power to the push-pull tripler, again using a temporary milliammeter connected in the lead to the plate coil, L₃. Tune the plate circuit for maximum indication on the grid meter. Plate current will be about 20 ma. Adjust the position of L_8 with respect to L_4 for maximum grid current. Now go back over all previous adjustments and set them carefully for maximum grid current. Adjust the balancing padder, Cs, retuning Cs each time this is done, until the combination of C_2 and C_3 that gives the highest grid current is found. Check the frequency to be sure that the stage is tripling to 220 Mc.

Now apply power to the 6360 plate circuit, again using the temporary meter to check the current. Connect the low-range milliammeter between the grid-metering terminal on the connector strip and ground. Set the screen trimmer,

 C_{6_1} near minimum, and tune the 6360 plate circuit for maximum grid current. With 300 volts on the preceding stages, it should be possible to get at least 4 ma. Adjust the spacing between L_{5} and L_{6} carefully for maximum grid current, returning C_{5} each time this is done. Plate current should not exceed 55 ma.

Check for neutralization of the final amplifier by tuning C_7 through resonance while watching the grid-current meter. If there is no change, or only a slight rise as the circuit goes through resonance, the stage is near enough to neutralization to apply plate power. The 6252 has built-in cross-over capacitance, intended to provide neutralization in the v.h.f. range, so it is likely to be stable at this frequency. If there is a downward kick in the grid current at resonance, adjust the screen trimmer until it disappears. If best neutralization shows at minimum setting of the screen trimmer it may be desirable to eliminate the trimmer.

With an antenna or dunimy load connected at J_{\bullet} , final plate voltage can be applied. Tune the final plate circuit for maximum output, with a meter of 100 ma. or higher range connected to read the combined plate and screen current. This meter may be connected in the power lead, or it can be plugged into the cathode jack. In the latter position it will read the combined plate, screen and grid currents. Tune for maximum output and note the plate current. If it is much over 100 ma., loosen the coupling between L_{7} and L_{8} . The input should not be over 50 watts at this frequency.

A final check for neutralization should now be made. Pull out the crystal or otherwise disable the early stages of the transmitter. The grid current and output should drop to zero. If they do not, adjust the screen trimmer until they do. Make this test only very briefly, as the tubes will draw excessive current when drive is removed. When perfect neutralization is achieved, maximum output will be found at a setting of C_7 at which plate current is at a minimum and grid current at maximum.

Operation

All stages should be run as lightly as possible, for stable operation and long tube life. No more than 300 volts should be run on the exciter stages, and if sufficient grid drive can be obtained, lower voltage is desirable. The 6360 stage

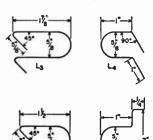


Fig. 17-33—Details of the hairpin loops used in the 220-Mc. transmitter.

runs with rather low drive, and its efficiency is consequently poor, but it delivers enough power to drive the 6252, even when run at as low as 250 volts, if all stages are operating as they should.

Observe the plates of the tubes when the transmitter is operated in a darkened room. There should be no reddening of the plates. If one side of any of the last three stages shows red and the other does not it is evidence of unbalance. This can usually be corrected by adjustment of the balancing trimmer, C_a , in the first tripler plate

circuit. Lack of symmetry in lead lengths or unbalanced capacitance to ground in any of the r.f. circuits may also lead to lopsided operation.

Though the 6252 is rated for up to 600 volts on the plates, it is recommended that no more than 400 be used in this application, particularly if the stage is to be modulated for voice work.

For voice work the plate-screen current of the 6252 is run through the secondary of the output transformer on the modulator. The latter should have an output of 20 watts or so.

A TRIPLER-AMPLIFIER FOR 432 Mc.

Only tubes designed especially for u.h.f. service will work satisfactorily at 420 Mc. and higher. The various small receiving triodes made for u.h.f. TV use will work well in low-powered frequency multipliers and r.f. amplifiers for transmitting, but the trend is to tetrodes. Several of the latter are now available.

The tripler-amplifier shown in Figs. 17-34 to 17-37 delivers up to 20 watts output on 432 Mc. when driven on 144 Mc. by any 2-meter unit delivering 10 watts output or more. In plate-modulated service the output is 12 watts. Tubes are RCA 6524 dual tetrodes, but with slight modification Amperex 6252s or 5894s may be used. With 6252s the output will be about the same as with the 6524. The 5894 will deliver up to 40 watts with higher plate voltages. The 832A may also be used, but the output will be no more than 4 or 5 watts. Forced-air cooling and shielding are recommended.

The tripler tube is mounted vertically, at the left, with its socket 1½ inches below the chassis. There is just room under the socket for the selfresonant input circuit, L2. The amplifier is horizontal, with its socket mounted in back of a plate that is 8 inches from the left edge of the $3 \times 4 \times$ 17-inch aluminum chassis. The shielding enclosure is 31/4 inches wide by 31/2 inches high. A cooling fan is mounted on the rear wall of the chassis. Air circulates around the tripler tube through its 2-inch hole, flowing out through holes in the top cover. Holes are drilled in the chassis under the amplifier tube, and in the cover over it. With a bottom plate fitted to the chassis there should be enough air flowing through both top vents to lift a paper briskly when the fan is started.



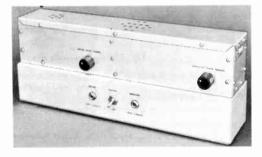


Fig. 17-34—A tripler-amplifier for 432 Mc. using dual tetrodes. Shielded construction and forced-air cooling are employed.

Half-wave lines are used in all 432-Mc. circuits. The grid circuit of the amplifier is capacitively coupled to the tripler plate line, the two overlapping about 1¼ inches. The spacing between them must be adjusted carefully for maximum grid drive. Plate voltage is fed to the lines through small resistors. These should be connected at the point of lowest r.f. voltage on the lines. The amplifier grid r.f. chokes are connected at the tube socket.

Note that the plate line capacitors, C_1 and C_2 , have their rotors floating. This is important. Grounding the rotors, or use of capacitors having metal end plates, may introduce multiple r.f. paths and circuit unbalance. The capacitors have small metal mounting brackets that are not connected directly to the rotors, but even so it was necessary to resort to polystyrene mounting plates for best circuit balance and efficiency. Holes $\frac{34}{2}$ inch in diameter are punched in the front wall to pass the rotor shafts.

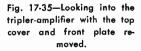

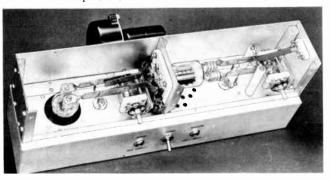

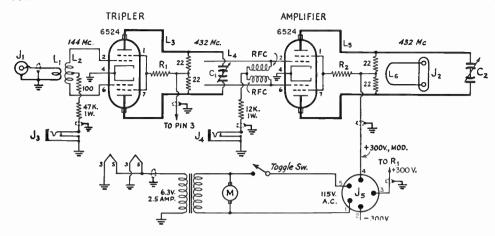


Fig. 17-36—Schematic diagram for the 432-Mc. tripler-amplifier.

C₁, C₂—10-μμf.-per-section split stator, double spaced (Bud LC-1664). Do not use metal end-plate or grounded-rotor types.

R₁, R₂—23,500 ohms, 2 watts (two 47,000-ohm 1-watt resistors in parallel).

 L_1 —2 turns No. 20 enam., $\frac{1}{2}$ -inch diam. Insert between turns of L_2 .

L₂—4 turns No. 16 enam., ½-inch diam., ½-inch long, center tapped.

Ls—Copper strap on heat-dissipating connectors, 3½ inches long. Twist 90 degrees ½ inch from plate end. Space ¾ inch.

L4-Copper strap 2% inches long, soldered to grid termi-

Testing

The tripler-amplifier is designed to operate in conjunction with a 144-Mc. transmitter such as the 2E26 rig shown in Fig. 17-17. A plate supply of 300 volts at 200 ma. is needed (400 volts may be used with 5894s). Apply power to the 144-Mc. driver stage and adjust the spacing of the turns in L_2 and the degree of coupling between L_1 and L_2 for maximum tripler grid current. This should be about 3 ma.

Next apply plate and screen voltage to the tripler and tune C_1 for maximum grid current in the amplifier, with no plate or screen voltage to the latter. Adjust the position of the grid lines with respect to the plate circuit, readjusting C_1 whenever a change is made, until at least 4 ma. grid current is obtained.

Now connect a lamp load across the output

nals. Space about ½ inch.

L₈—Copper strap 3% inches long, fastened to heatdissipating connectors. Space ¾ inch. All tank circuits of flashing copper ½ inch wide.

Le—Coupling loop, No. 20 enam. U-shaped portion is 1 inch long and % inch wide. Mount on 3-inch ceramic stand-offs.

J₁—Coaxial input fitting (Amphenol 83-1R).

J₂—Crystal socket used for antenna terminal.

Ja, Ja-Closed-circuit jack.

J₈—5-pin male chassis connector (Amphenol 86-RCP5).
M—Motor-blower assembly, 17 c.f.m. (Ripley Inc., Middletown, Conn., Type 8433).

terminal, J_2 . Ordinary house lamps are not suitable. A fair load can be made by connecting 6 or more blue-bead pilot lamps in parallel. This can be done by wrapping a $\frac{1}{4}$ -inch copper strap around the brass bases and soldering them all together. Then another strap should be soldered to the lead terminals. Apply plate and screen voltage and tune C_2 for maximum lamp brilliance. It should be possible to develop a very bright glow in the 6-lamp load with a plate current of about 100 ma, at 300 volts.

Cut drive very briefly to check for oscillation in the final stage. Grid current should drop to zero. The screen and grid resistors shown are for operation with plate modulation. More input can be run if the screen or grid resistance is decreased, but this should be done only when the rig is to be used for f.m. or c.w. service.

Operating conditions are about as follows: tripler grid current—2 to 3 ma.; amplifier grid current—3 to 4 ma.; tripler plate and screen current—90 ma.; amplifier plate and screen current—110 ma.; output—12 watts.

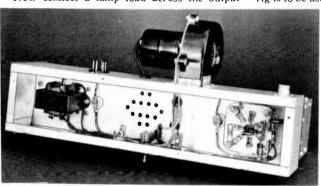


Fig. 17-37—Bottom view of the 432-Mc. transmitter.

V.H.F. Antennas

While the basic principles of antenna design remain the same at all frequencies where conventional elements and transmission lines are used, certain aspects of v.h.f. work call for changes in antenna techniques above 50 Mc. Here the physical size of arrays is reduced to the point where some form of antenna having gain over a simple halfwave dipole can be used in almost any location, and the rotatable highgain directional array has become a standard feature of all well-equipped v.h.f. stations. The importance of antenna gain in v.h.f. work cannot be over-emphasized. By no other means can so large a return be obtained from a small investment as results from the erection of a good directional array.

DESIGN CONSIDERATIONS

At 50 Mc, and higher it is usually important to have the antenna work well over all or most of the band in question, and as the bands are wider than at lower frequencies the attention of the designer must be focused on broad frequency response. This may be attained in some instances through sacrificing other qualities such as high front-to-back ratio.

The loss in a given length of transmission line rises with frequency. V.h.f. feedlines should be kept as short as possible, therefore. Matching of the impedances of the antenna and transmission line should be done with care, and in open locations a high-gain antenna at relatively low height may be preferable to a low-gain system at great height. Wherever possible, however, the

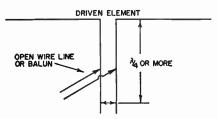


Fig. 18-1—Combination tuning and matching stub for v.h.f. arrays. Sliding short is used to tune out reactance of the driven element or phasing system. Transmission line, either balanced or coax, is connected at the point of lowest standing-wave ratio. Adjustment procedure is outlined in text.

v.h.f. array should be well above heavy foliage, buildings, power lines or other obstructions.

The physical size of a v.h.f. array is usually more important than the number of elements. A 4-element array for 432 Mc. may have as much

gain over a dipole as a similarly designed array for 144 Mc., but it will intercept only one-third as much energy in receiving. Thus to be equal in communication, the 432-Mc. array must equal the 144-Mc. antenna in *capture area*, requiring three times as many elements, if similar element configurations are used in both.

Polarization

Early v.h.f. work was done with simple antennas, and since the vertical dipole gave as good results in all directions as its horizontal counterpart offered in only two directions, vertical polarization became the accepted standard. Later when high-gain antennas came into use it was only natural that these, too, were put up vertical in areas where v.h.f. activity was already well established.

When the discovery of various forms of longdistance propagation stirred interest in v.h.f. operation in areas where there was no previous experience, many newcomers started in with horizontal arrays, these having been more or less standard practice on frequencies with which these operators were familiar. As use of the same polarization at both ends of the path is necessary for best results, this lack of standardization resulted in a conflict that, even now, has not been completely resolved.

Tests have shown no large difference in results over long paths though evidence points to a slight superiority for horizontal in certain kinds of terrain, but vertical has other factors in its favor. Horizontal arrays are generally easier to build and rotate. Where ignition noise and other forms of man-made interference are present, horizontal systems usually provide better signal-to-noise ratio. Simple 3- or 4-element arrays are more effective horizontal than vertical, as their radiation patterns are broad in the plane of the elements and sharp in a plane perpendicular to them.

Vertical systems can provide uniform coverage in all directions, a feature that is possible only with fairly complex horizontal arrays. Gain can be built up without introducing directivity, an important feature in net operation, or in locations where the installation of rotatable systems is not possible. Mobile operation is simpler with vertical antennas. Fear of increased TVI has kept v.h.f. men in some densely populated areas from adopting horizontal as a standard.

The factors favoring horizontal have been predominant on 50 Mc., and today we find it the standard for that band, except for emergency net operation involving mobile units. The slight

advantage it offers in DX work has accelerated the trend to horizontal on 144 Mc. and higher bands, though vertical polarization is still widely used. The picture on 144, 220 and 420 Mc. is still confused, the tendency being to follow the local trend. The newcomer should check with local amateurs to see which polarization is in general use in the area he expects to cover. Eventual standardization should be a major objective, and to this end it is recommended that horizontal polarization be established in areas where activity is developing for the first time.

IMPEDANCE MATCHING

Because line losses increase with frequency it is important that v.h.f. antenna systems be matched to their transmission lines carefully. Lines commonly used in v.h.f. work include open-wire, usually 300 to 500 ohms impedance, spaced ½ to two inches; polyethylene-insulated flexible lines, available in 300, 150 and 72 ohms impedance; and coaxial lines of 50 to 90 ohms impedance.

The various methods of matching antenna and line impedance are described in detail in Chapter 14. Matching devices commonly used in v.h.f. arrays fed with balanced lines include the folded dipole in its various forms, Fig. 14-42, the "T" Match, Fig. 14-45, the "Q" section, Fig. 14-41. and the adjustable stub, Fig. 18-1. The gamma match, useful for feeding the driven element of a parasitic array with coaxial line, is shown in schematic form in Fig. 14-45. Balanced loads such as a split dipole or a folded dipole can be fed with coax through a balun, as shown in Fig. 14-46. Practical examples of the use of these devices are shown in the following pages. The principles upon which their operation depends are explained in Chapter 14, with the exception of the adjustable stub of Fig. 18-1.

The Corrective Stub

The adjustable stub shown in Fig. 18-1 provides a means of matching the antenna to the transmission line and also tuning out reactance in the driven element. It is, in effect, a tuning device to which the transmission line may be connected at the point where impedances match. Both the shorting stub and the point of connection are made adjustable, though once the proper points are found the connections may be made permanent.

For antenna experiments the stub may be made of tubing, and the connections made with sliding clips. In a permanent installation a stub of open-wire line, with all connections soldered, may be more satisfactory mechanically. The transmission line may be open-wire or Twin-Lead, connected directly to the stub, or coaxial line of any impedance, which should be connected through a balun.

To adjust the stub start with the short at a point about a half wavelength below the antenna, moving the point of connection of the transmission line up and down the stub until the lowest standing-wave ratio is achieved. Then move the shorting stub a small amount and readjust the line connection for lowest s.w.r. again. If the minimum s.w.r. is lower than at the first point checked the short was moved in the right direction. Continue in that direction, readjusting the line connection each time, until the s.w.r. is as close to 1:1 as possible. When adjustments are completed the portion of the stub below the short can be cut off, if this is desirable mechanically.

TYPES OF V.H.F. ARRAYS

Directional antenna systems commonly used in amateur v.h.f. work are of three general types, the collinear, the Yagi, and the plane reflector

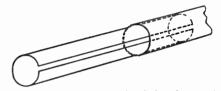


Fig. 18-2—Inserts for the ends of the elements in o v.h.f. array provide a means of adjustment of length for optimum performance. Short pieces of the element material are sawed lengthwise and compressed to fit inside the element ends.

array. Collinear systems have two or more driven elements end to end, fed in phase, usually backed up by parasitic reflectors. The Yagi has a single driven element, with one or more parasitic elements in front and in back of the driven element, all in the same plane. The plane-reflector array has a large reflecting surface in back of its driven element or elements. This may be a sheet of metal, a metal screen, or closely spaced rods or wires. The reflector may be a flat plane, or it can be bent into several forms, such as the corner and the parabola.

Examples of all three types are described, and each has points in its favor. The collinear systems such as the 12- and 16-element arrays of Figs. 18-14 and 18-15 require little or no adjustment and they present few feed problems. They work well over a wide band of frequencies. Yagi, or parasitic, arrays, Figs. 18-5 to 18-10, depend on fairly precise tuning of their elements for gain, and thus work over a narrower frequency range. They are simple mechanically, however, and usually offer more gain for a given number of elements than do the collinear systems. Plane- and corner-reflector arrays are broadband devices, having broad forward lobes and high front-to-back ratio. They are easily adjusted, but somewhat cumbersome mechani-

ELEMENT LENGTHS AND SPACINGS

Designing a v.h.f. array presents both mechanical and electrical problems. The electrical problems are basic, and their solution involves choosing the type of performance most desired. Mechanical design, on the other hand, can be subject to almost endless variations, and the form that the array will take can usually be

TABLE 18-I								
Dimensions	for V.H.F.	Arrays in	Inches					

Freq. (Mc.)	52*	146*	222.5*	435*
Driven Element	106.5	38	24 7/8	1234
Change per Mc.*	2	0.25	0.12	0.03
Reflector	1111/2	40	261/8	133/8
1st Director	1011/2	36	235%	121/8
2nd Director	991/2	35 3/4	233/8	12
3rd Director	971/2	35	23	113/8
1.0 Wavelength	234	81	53	27
0.625 Wavelength	147	501/2	331/8	1634
0.5 Wavelength	117	401/2	261/2	13.5
0.25 Wavelength	581/2	201/4	131/4	63/4
0.2 Wavelength	47	16	105%	53/8
0.15 Wavelength	35	12	8	4
Balun loop (coax)	76	26.5	171/4	83/4

^{*}Dimensions given for element lengths are for the middle of each band. For other frequencies adjust lengths as shown in the third line of table. Example: A dipole for 50.0 Mc. would be 106.5 + 4 = 110.5 inches.

Apply change figure to parasitic elements as well. For phasing lines or maching sections, and for spacing between elements, the midband figures are sufficiently accurate. They apply only to openwire lines.

Parasitic-element lengths are optimum for 0.2 wavelength spacing.

decided by the materials and tools available. One common source of materials for amateur arrays is commercially built TV antennas. They can often be revamped for the amateur v.h.f. bands with a minimum of effort and expense.

Dimensions for Yagi or collinear arrays and their matching devices can be taken from Table 18-I. The driven element is usually cut to the formula:

Length (in inches) =
$$\frac{5540}{Freq. (Mc.)}$$

This is the basis of the lengths in Table 18-I, which are suitable for the tubing or rod sizes commonly used. Arrays for 50 Mc. usually have ½ to 1-inch elements. For 144 Mc. ¼ to ½-inch stock is common. Rod or tubing ½ to ¾ inch in diameter is suitable for 220 and 420 Mc. Note that the element lengths in the table are for the middle of the band concerned. For peaked performance at other frequencies the element

lengths should be altered according to the figures in the third line of the table.

Reflector elements are usually about 5 per cent longer than the driven element. The director nearest the driven element is 5 per cent shorter, and others are progressively shorter, as shown in the table. Parasitic elements should also be adjusted according to Line 3 of the table, if peak performance is desired at some frequency other than midband.

Parasitic element lengths of Table 18-I are based on element spacings of 0.2 wavelength. This is most often used in v.h.f. arrays, and is suitable for up to 4 or 5 elements. Other spacings can be used, however. If the element lengths are adjusted properly there is little difference in gain with reflector spacings of 0.15 to 0.25 wavelength. The closer the reflector is to the driven

Fig. 18-3—Omnidirectional vertical array for 144 Mc. Elements of aluminum clothesline wire are mounted on ceramic standoff insulators screwed to a wooden pole. Feedline shown is 52-ohm coax, with a balun at the feedpoint, Twin-Lead or other 300-ohm balanced line may also be used, but it should be brought away horizontally from the supporting pole and elements for at least a quarter wavelength. Coax may be taped to the support.



element, the shorter it must be for optimum forward gain, and the greater will be its effect on the driven element impedance.

Directors may also be spaced over a similar range. Closer spacing than 0.2 wavelength for arrays of two or three elements will require a longer director than shown in Table 18-I. Thus it can be seen that close-spaced arrays tend to work over a narrower frequency range than wide-spaced ones, when they are tuned for best performance. They also result in lower driven-element impedance, making them more difficult to feed properly. Spacings less than 0.15 wavelength are not commonly used in v.h.f. arrays for these reasons.

PRACTICAL DESIGNS FOR V.H.F. ARRAYS

The antenna systems pictured and described herewith are examples of ways in which the information in Table 18-I can be used in arrays of proven performance. Dimensions can be taken from the table, except where otherwise noted. If the builder wishes to experiment with element adjustment, a simple method is shown in Fig. 18-2. With elements ½-inch or larger diameter a piece of the element material can be used. It is sawed lengthwise and then compressed to make a tight fit inside the end of the element.

A readily available material often used for

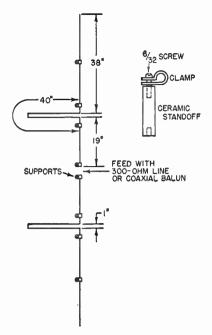


Fig. 18-4—Dimensions and supporting method for the 144-Mc. vertical array.

elements in arrays for 144 Mc. and higher is aluminum clothesline wire. This is a stiff hard-drawn wire about ½ inch in diameter. It should be used in preference to a similar-appearing wire commonly sold for TV grounding purposes. The latter is too soft to make satisfactory elements if the length is more than about two feet.

A Collinear Array for 144 Mc.

Where a vertically-polarized array having some gain over a dipole is needed, yet directivity is undesirable, collinear half-wave elements may be mounted vertically and fed in phase, as shown in Figs. 18-3 and 18-4. Such an array may have 3 elements, as shown, or 5. The impedance at the center is approximately 300 ohms, permitting it to be fed directly with TV-type line, or through a coaxial balun, as in the model shown. Either 52- or 72-ohm line may be employed without serious mismatch.

The array is made from two pieces of aluminum clothesline wire about 97 inches long overall. These are bent to provide a 38-inch top section, a folded-back 40-inch phasing loop, and a 19-inch center section. These elements are mounted on ceramic pillars, which are fastened to a round wooden pole. Small clamps of sheet aluminum are wrapped around the elements and screwed to the stand-offs. A cheaper but somewhat less desirable method of mounting is to use TV screw-eye insulators to hold the elements in place.

Feeding the array at the center with a coaxial balun makes a neat arrangement. The balun loop may be taped to the vertical support, and the coaxial line likewise taped at intervals down the mast. The same type of construction can be ap-

plied to a 220-Mc. vertical collinear array, using the lengths for that band given in Table 18-I.

PARASITIC ARRAYS

Single-bay arrays of 2 to 5 elements are widely used in 50-Mc. work. These may be built in many different ways, using the dimensions given in the table. Probably the strongest and lightest structure results from use of aluminum or dural tubing (usually 1¼ to 1½ inches in diameter) for the boom, though wood is also usable. If the elements are mounted at their midpoints there is no need to use insulating supports. Usually the elements are run through the boom and clamped in place in a manner similar to that shown in Fig. 18-12. Where a metal boom is used the joints between it and the elements must be tight, as any movement at this point will result in noisy reception.

2-Element 50-Mc. Array

The 2-element antenna of Fig. 18-5 was designed for portable use, but it is also suitable for fixed-station work with minor modification. The 2-meter array above it is described later. The elements are made in three sections, for portability, using inserts similar to that shown in Fig. 18-2. The driven element is gamma matched for coax feed, and the parasitic element is a 0.15-wavelength spaced director. Details of the gamma section, the boom and its supporting clamp are shown in Fig. 18-6. The arm is about 12 inches long, and the capacitor is a $50-\mu\mu f$.



Fig. 18-5—Two-element 50-Mc. and four-element 144-Mc. arrays designed for portable use. Support is sectional TV masting clamped to car door handle. Elements of 50-Mc. array are made in three sections, for stowing in back of car. Antenna for 144 Mc. is cutdown TV array. Both use gamma match, as shown in Fig. 18-6.



Fig. 18-6—Details of the gamma match for the 50-Mc. portable array. In a permanent installation the variable capacitor should be mounted in an inverted plastic cup or other device to protect it from the weather. The gamma arm is about 12 inches long for 50 Mc., 5 inches for 144 Mc.

variable. Clean, tight connections between the arm and element are important. Where the array is to be mounted permanently outdoors the capacitor may be protected from the weather by mounting it in an inverted plastic cup. More details on this array are given in August, 1955, QST.

3-Element Lightweight Array

The 3-element 50-Mc. array of Fig. 18-7 weighs only 5 pounds. It uses the closest spacing that is practical for v.h.f. applications, in order to make an antenna that could be used individually or stacked in pairs without requiring a cumbersome support. The elements are half-inch aluminum tubing of 1/16-inch wall thickness, attached to the 1½-inch dural boom with aluminum castings made for the purpose. (Dick's, 62 Cherry Ave., Tiffin, Ohio, Type HASL.) By limiting the element spacing to 0.15 wavelength the boom is only 6 feet long. Two booms for a stacked array (Fig. 18-11) can thus be cut from a single 12-foot length of tubing.

The folded-dipole driven element has No. 12 wire for the fed portions. These are mounted on 3/4-inch cone standoff insulators and joined to the outer ends of the main portion by means of metal pillars and 6-32 screws and nuts. When the wires are pulled up tightly and wrapped around the screw, solder should be sweated over the nuts and screw ends to seal the whole against weather corrosion. The same treatment should be used at each standoff. Mount a soldering lug on the ceramic cone and wrap the end of the lug around the wire and solder the whole assembly together. These joints and other portions of the array may be sprayed with clear lacquer as an additional protection.

The inner ends of the folded dipole are 1½ inches apart. Slip the dipole into its aluminum casting, and then

drill through both element and casting with a No. 36 drill, and tap with 6-32 thread. Suitable inserts for mounting the stand-offs can be made by cutting the heads off 6-32 screws. Taper the cut end of the screw slightly with a file and it will screw into the standoff readily.

Cut the dipole length according to Table 18-I, for the middle of the frequency range you expect to use most. The reflector and director will be approximately 4 per cent longer and shorter, respectively. The closer spacing of the parasitic elements (0.15 wavelength) makes this deviation from the dimensions of the table desirable.

The single 3-element array has a feed impedance of about 200 ohms at its resonant frequency. Thus it may be fed with 52-ohm coax and a balun. A gamma-matched dipole may also be used, as in the 2-element array. If the gamma match and 72-ohm coax are used, a balun will convert to 300-ohm balanced feed, if Twin-Lead or 300-ohm open-wire TV line feed is desired. If the dimensions are selected for optimum performance at 50.5 Mc. the array will show good performance and fairly low standing-wave ratio over the range from 50 to 51.5 Mc.

A closeup of a mounting method for this or any other array using a round boom is shown in Fig. 18-8. Four TV-type U bolts clamp the horizontal and vertical members together. The metal plate is about 6 inches square. If ¼-inch sheet aluminum is available it may be used alone, though the photograph shows a sheet of 1/16-inch stock backed up by a piece of wood of the same size for stiffening.

High-Performance 4-Element Array

The 4-element array of Fig. 18-9 was designed for maximum forward gain, and for direct feed with 300-ohm balanced transmission line. The parasitic elements may be any diameter from ½ to 1 inch, but the driven element should be made as shown in the sketch. The same general arrangement may be used for a 3-element array, except that the solid portion of the dipole should

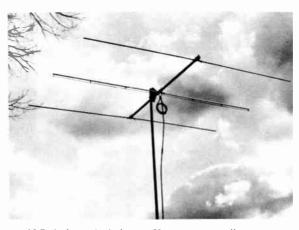


Fig. 18-7—Lightweight 3-element 50-Mc. array. Feedline is 52-ohm coax, with a balun for connection to the folded-dipole driven element. Balun may be coiled as shown or taped to supporting pipe.


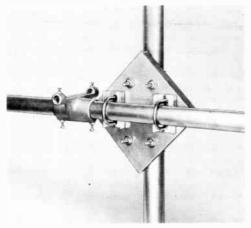


Fig. 18-8—Closeup photograph of the boom mounting for the 50-Mc. array. A sheet of aluminum 6 inches square is backed up by a piece of wood of the same size. TV-type U clamps hold the boom and vertical support together at right angles. At the left of the mounting assembly is one of the aluminum castings for holding the beam elements.

be 3/4-inch tubing instead of 1-inch. With the element lengths given the array will give nearly uniform response from 50 to 51.5 Mc., and usable gain to above 52 Mc. It may be peaked for any portion of the band by using the information in Table 18-I.

If a shorter boom is desired, the reflector spacing can be reduced to 0.15 wavelength and both

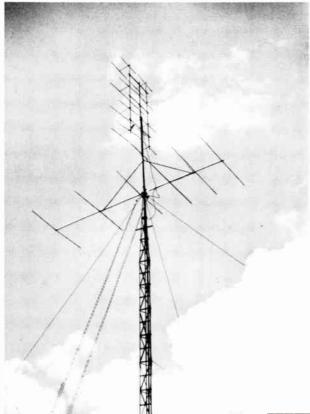

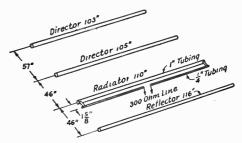


Fig. 18-9—Details of a 4-element 50-Mc. array designed for 300-ohm balanced feed. Element lengths and spacings were derived experimentally for optimum performance over the first 1.5 megacycles of the band.

directors spaced 0.2 or even 0.15 wavelength, with only a slight reduction in forward gain and bandwidth.

5-Element 50-Mc. Array

As aluminum or dural tubing is usually sold in 12-foot lengths this dimension imposes a practical limitation on the construction of a 50-Mc. beam. A 5-element array that makes optimum use of a 12-foot boom may be built according to Table 18-I. If the aluminum casting method of mounting elements shown for the 3-element array is employed the weight of a 5-element beam can be held to under 10 pounds. The gamma match and coaxial line are recommended for feeding such an array, though a balun and 72-ohm coax can be used for the rotating portion of the line, converting to balanced feed at the anchor point.

Elements should be spaced 0.15 wavelength, or about 36 inches. With 5 or more elements, good bandwidth can be secured by tapering the element lengths properly. A dipole 110 inches long, with a 116-inch reflector, and directors of 105, 103 and 101 inches respectively will work well over the first two megacycles of the band, provided that the s.w.r. is adjusted for optimum at 51 Mc.

Long Yagis for 50 Mc.

With boom lengths greater than about 12 feet and with more elements than 4, somewhat better performance can be obtained by using gradually increasing spacing between the directors. The 6-element array in Fig. 18-10 is an example of this approach. It also employs a variation of the gamma match that has mechanical advantages. The long boom and wide-spaced elements give a sharpness of horizontal pattern that is not obtainable with the same number of elements in a stacked array.

The long Yagi is not a broadband device. This one works well over the first megacycle of the band with the following dimensions. Sub-

Fig. 18-10—A 6-element long Yagi for 50 Mc. and a 16-element collinear array for 144 Mc. Both are allmetal construction. Each has its own vertical member, which is clamped to the rotating vertical pipe that runs down through the tower bearing.

Parasitic Arrays

tract 2 inches from each element for each megacycle higher. Reflector — 116 inches. Driven element — 110.5. First director — 105.5. Second director — 104. Third director — 102.75. Fourth director — 101.5. Spacings are, from back forward: 36, 36, 42, 59 and 70 inches. If a longer array is to be built each additional director should be 70 inches from the last.

Construction

The long Yagi is built similar to the 3-element array of Fig. 18-7 and 18-8, using those same castings for mounting the elements. The gusset plate for fastening the boom to the vertical support is made larger, and four U bolts are used on each member instead of two. The array is mounted at its center of gravity, rather than at its physical center. The boom is braced to prevent drooping, at points about 5 feet out from the mounting point. Braces are aluminum tubing, flattened at the ends, and clamped to the boom and the vertical member. Suspension bracing, as shown in Fig. 18-10, provides strength with lightweight supports.

The dimensions given require a boom slightly more than 20 feet long. This was made up by splicing, but if a 20-foot length is available in one piece the spacings of the two forward directors can be made slightly less, in order to avoid splicing. Element spacing is not particularly critical, but lengths are fairly so.

The Gamma Match

The gamma match is ideal for matching arrays fed with coax. The arrangement shown in Fig. 18-11 combines the adjustable arm with the series capacitor, and provides a rugged assembly that can be weather-proofed readily. The main arm is cut from the same material as the elements, 15 inches long. It is supported parallel to the driven element by means of two 1-inch ceramic standoffs and sheet-aluminum clips. Its inner end is connected to the inner conductor of a coaxial fitting, mounted on a small bracket screwed to the boom.

The series capacitor, for tuning out the reactance of the matching arm and making connection to the driven element, is ¼-inch rod or tubing 14 inches long. It is maintained coaxial with the main arm by two polystyrene bushings. One is force-fitted to the end of the rod and the

other is fitted tightly inside the main arm to act as a bearing. These can be made from pieces of 3/4-inch diameter polystyrene rod stock, drilled to pass the 1/4-inch rod. A clip of sheet aluminum connects the rod and the driven element. Be sure that a clean tight contact is made at this point.

Adjustment

Matching requires an s.w.r. bridge. It can be done properly in no other way. Mount the beam at least a half wavelength above ground and clear of trees and wires by at least the same distance. Set the transmitter at a frequency in the middle of the range you want to work (50.3 is a good spot for low-end operation) and adjust the position of the clip and the length of the rod outside the main arm for minimum s.w.r. Move first one variable and then the other until zero reflected power is indicated. Tighten the clip solidly, tape over the junction between the arm and the rod with waterproof tape, and the array is ready for use.


144-MC. PARASITIC ARRAYS

The main features of the arrays described above can be adapted to 144-Mc. antennas, but the small physical size of arrays for this frequency makes it possible to use larger numbers of elements with ease. Few 2-meter antennas have less than 4 or 5 elements, and most stations use more, either in a single bay or in stacked systems.

Parasitic arrays for 144 Mc. can be made readily from TV antennas for Channels 4, 5 or 6. The relatively close spacing normally used in TV arrays makes it possible to approximate the recommended 0.2 wavelength at 144 Mc., though the element spacing is not a critical factor. A 4-element array for 144 Mc. made from a Channel 6 TV Yagi is shown in Fig. 18-5. It is fed with a gamma match and 52-ohm coax, and was designed primarily for portable work. As most TV antennas are designed for 300-ohm feed the same feed system can be employed for the 2-meter array that is made from them.

If one wishes to build his own Yagi antennas from available tubing sizes, the boom of a 2-meter antenna should be 3/4 to 1 inch aluminum or dural. Elements can be 1/4 to 1/2-inch stock, fastened to the boom as shown in Fig. 18-12.

Fig. 18-11 — Details of the gamma match used on the 6-element 50-Mc. array. Series capacitor is formed by sliding a rod or tube inside the main arm.

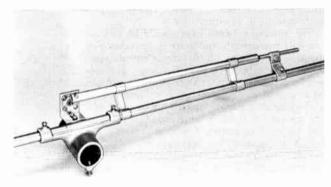

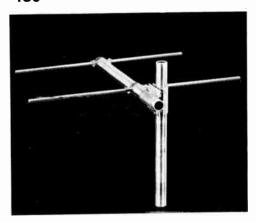


Fig. 18-12—Model showing method of assembling allmetal arrays for 144 Mc. and higher frequencies. Dimensions of clamps are given in Fig. 18-16.

Recommended spacing for up to 6 elements is 0.2 wavelength, though this is not too critical. Gamma match feed is recommended for coax, or a folded dipole and balun may be used. If balanced line is to be used the folded dipole is recommended, the 4 to 1 ratio of conductor sizes being about right for most designs.

Very high gain can be obtained with long Yagi-type arrays for 144 Mc. and higher frequencies, though the bandwidth of such antennas is considerably narrower than for those having up to 4 or 5 elements. The first two directors in long Yagis are usually spaced about 0.1 wavelength. The third is spaced about 0.2, increasing to 0.4 wavelength or so for the forward directors. Highest gain is obtained when all directors are made the same length, but better front-to-back ratio and lower side lobe content results if the director lengths are tapered 1/8 to 1/4 inch per director. Tapering the element lengths also widens the effective bandwidth. There is more on long Yagis in QST for January and September, 1956,

STACKED YAGI ARRAYS

The gain (in power) obtainable from a single Yagi array can be more than doubled by stacking two or more of them vertically and feeding them in phase. This refers to horizontal systems, of course. Vertically-polarized bays are usually stacked side by side. The principles to follow apply in either case.

The spacing between bays should be at least one-half wavelength, and more is desirable. For dipoles or Yagis of up to three elements optimum spacing between bays is about 5% wavelength, but with longer Yagis the spacing can be increased to one wavelength or more. Bays of 5 elements or more, spaced one wavelength, are commonly used in antennas for 144 Mc. and higher frequencies. Optimum spacing for long Yagis is about two wavelengths.

Where half-wave stacking is to be employed, the phasing line between bays can be treated as a double "Q" section. If two bays, each designed for 300-ohm feed, are to be stacked a half wavelength apart and fed at the midpoint between them, the phasing line should have an impedance of about 380 ohms. No. 12 wire spaced one inch will do for this purpose. The midpoint then can be fed either with 300-ohm line, or with 72-ohm coax and a balun.

When a spacing of 5% wavelength between bays is employed, the phasing lines can be coax. (The velocity factor of coax makes a full wavelength of line actually about 5% wavelength physically.) The impedance at the midpoint between two bays is slightly less than half the impedance of either bay alone, due to the coupling between bays. This effect decreases with increased spacing.

When two bays are spaced a full wavelength the coupling is relatively slight. The phasing line can be any open-wire line, and the impedance at the midpoint will be approximately half that of the individual bays. Predicting what it will be with a given set of dimensions is difficult, as many factors come into play. It will usually be of a value that can be fed through the combination of a "Q" section and a transmission line of 300 to 450 ohms impedance. An adjustable "Q" section, or an adjustable stub like the one shown in Fig. 18-1, may be used when the antenna impedance is not known.

The stacked 3-over-3 for 50 Mc., Fig. 18-13, uses a coaxial phasing line and an additional section of coax to provide for the flexible por-

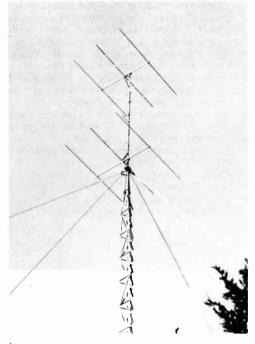


Fig. 18-13—Stacked array for 50 Mc. using two of the 3-element bays of Fig. 18-7. Phasing system and flexible section for rotation are of coaxial line. A "Q" section matches this to 450-ohm apen-wire line far run to the station.

Collinear Arrays

tion of the feedline. Each bay is fed with a balun and halfwave section of RG-8/U cable. These are joined at the center between bays with a Tee fitting. As each bay has an impedance of 200 ohms, two 50-ohm leads are paralleled at the center, resulting in an impedance of about 20 ohms, when the coupling effect between bays is included. A flexible section of 50-ohm coax one wavelength long, with a balun at the end, steps this up to about 80 ohms. A "Q" section of ¼-inch tubing ¾ inch center to center steps this up to the point where it can be fed with 450-ohm open-wire TV line.

The "Twin-Five" for 144 Mc.

A popular stacked array for 144-Mc. work is the Twin-Five, originally developed by W2PAU.1 In this design two 5-element arrays of standard design are stacked a full wavelength apart. If the folded-dipole driven elements are constructed so that the individual bays have a feed impedance of about 400 ohms the midpoint of the open-wire phasing line can be fed with 52-ohm coax and a balun. Where open-wire line is desired, the impedances can be matched through a "O" section of about 300 ohms impedance. If the constructor is in doubt as to the actual feed impedance to be matched, the stub arrangement of Fig. 18-1 will take care of a wide range of impedances and lines to be matched. Dimensions can be taken from Table 18-I.

An effective 20-element array can be made by using two of these arrays side by side, with full-wave spacing horizontally also. The impedance at the midpoint of the horizontal phasing line will then be about 100 ohms, which is still well within the range of "Q" sections of practical dimensions.

LARGE COLLINEAR ARRAYS FOR 144 MC. AND HIGHER

High gain and very broad frequency response are desirable characteristics found in curtains of half-wave elements fed in phase and backed up by reflectors. The reflector can be made up of parasitic elements, or it can be a screen extending approximately a quarter wavelength beyond the ends of the driven elements. There is not a large difference between the two types of reflectors, except that higher front-to-back ratio and somewhat broader frequency response are achieved with the plane reflector.

12- and 16-Element Arrays

Two collinear systems that may be used on 144, 220 or 420 Mc. are shown in Figs. 18-14 and 18-15. Either may be fed directly with 300-ohm transmission line, or through coaxial line and a balun. In the 12-element array, Fig. 18-14, the reflectors are spaced 0.15 wavelength in back of the driven elements, while the 16-element array, Figs. 18-15 and 18-10, uses 0.2 wave-

length spacing. Dimensions may be taken from Table 18-I, and figures for the middle of the band will give good performance across either band

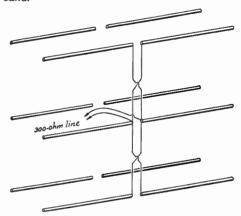


Fig. 18-14—Element arrangement and feed system of the 12-element array. Reflectors are spaced 0.15 wavelength behind the driven elements.

The supporting frame for either array may be made of wood or metal. Details of a metal support for the 12-element array are shown in Figs. 18-16 and 18-17. Note that all elements are mounted at their midpoints, and that no insulators are used. The elements are mounted in front of the supporting frame, to keep metal out of the field of the array. This method is preferable to that wherein mechanical balance is maintained through mounting the driven ele-

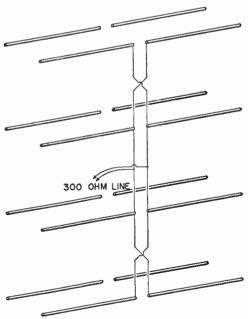


Fig. 18-15—Schematic drawing of a 16-element array.

A variable "Q" section may be inserted at the feed point if accurate matching is desired. Reflector spacing is 0.2 wavelength.

¹ Brown—"The Wide-Spread Twin-Five" CQ, March, 1950.

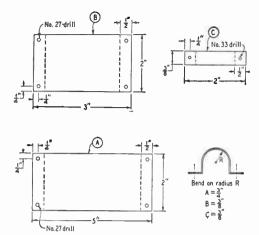


Fig. 18-16—Detail drawings of the clamps used to assemble the all-metal 2-meter array. A, B and C are before bending into "U" shape. The right-angle bends should be made first, along the dotted lines as shown, then the plates may be bent around a piece of pipe af the proper diameter. Sheet stock should be \(\frac{1}{6} \)-inch or heavier aluminum.

ments in front and the reflectors in back of the supporting structure.

Two 12-element arrays may be mounted one above the other and fed in phase, to form a 24-

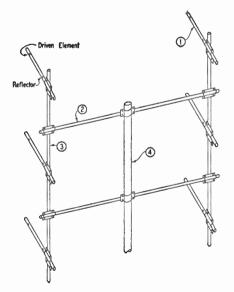


Fig. 18-17—Supporting framework for a 12-element 144-Mc. array of all-metal design. Dimensions are as follows: element supports (1) ¾ by 16 inches; horizontal members (2) ¾ by 46 inches; vertical members (3) ¾ by 86 inches; vertical support (4) 1½-inch diameter, length as required; reflector-to-driven-element spacing 12 inches. Parts not shown in sketch: driven elements ¼ by 38 inches; reflectors ¼ by 40 inches; phasing lines No. 18 spaced 1 inch, 80 inches long, fanned out to 3½ inches at driven elements (transpose each half-wave section).

element array. This is done in the 420-Mc. array of Fig. 18-18. The two midpoints are connected through a phasing line one wavelength long, and the center of this phasing line fed through a "Q" section. The impedance at the midpoint is about 150 ohms, requiring a 255-ohm "Q" section for feeding with 450-ohm open-wire line.

Combination of collinear arrays may be carried further. Pairs of 16-element systems fed in phase are common, and even 64-element arrays (4 16-element beams fed in phase) are used in some leading stations on 144 Mc. Configurations of 32 to 64 elements are not difficult to build and support at 220 or 420 Mc. Examples of 16-and 24-element arrays for 220 and 420 Mc. are shown mounted back to back in Fig. 18-18.

ARRAYS FOR 220 AND 420 MC.

The use of high-gain antenna systems is almost a necessity if work is to be done over any great distance on 220 and 420 Mc. Experimentation with antenna arrays for these frequencies is fascinating indeed, as their size is so small as to permit trying various element arrangements

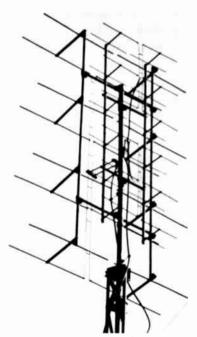


Fig. 18-18—A 24-element array for 420 Mc. and a 16element for 220 mounted back-to-back on a single support.

and feed systems with ease. Arrays for 420 Mc., particularly, are convenient for study and demonstration of antenna principles, as even highgain systems may be of table-top proportions.

Any of the arrays described previously may be used on these bands, but those having large numbers of driven elements in phase are more readily adjusted for maximum effectiveness.

Miscellaneous Systems

A 16-element array for 220 Mc. and a 24-element array for 420 Mc. are shown mounted back-to-back in Fig. 18-18. The 220-Mc. portion follows the 16-element design already described. It is fed at the center of the system with 300-ohm tubular Twin-Lead, matched to the center impedance of the array through a "Q" section of 1%-inch tubing, spaced about 1½ inches center to center. This spacing was adjusted for minimum standing-wave ratio on the line.

Elements in the array shown are of r_{0} -inch aluminum fuel-line tubing, which is very light in weight and easily worked. The supporting structure is dural tubing, using the clamp assembly methods of Fig. 18-16.

The 420-Mc. array uses two 12-element assemblies similar to Fig. 18-14, mounted one above the other, about one half wavelength separating the bottom of one from the top of the other. The two sets of phasing lines are joined by one-wavelength sections of Twin-Lead at the middle of the array. This junction, which has an impedance of around 150 ohms, is fed with 300-ohm tubular Twin-Lead through an adjustable "Q" section.

Elements in the 420-Mc. array are cut from thin-walled ½-inch tubing. Their supports are the ½-inch stock used for the 220-Mc. elements. Slots were cut in the ends of these supports to take the elements, and a 4-40 screw was run through both pieces and drawn up tightly with a nut. The horizontal supports were fastened in holes drilled in the vertical members, and were also held in place with a 6-32 screw and nut. The small size and light weight of the 420-Mc. array require no clamps to make a strong assembly.

The two one-wavelength sections of 300-ohm line are 21¾ inches long, taking the propagation factor into account. The "Q" section may be any convenient size tubing, ¼ to ½ inch diameter. It should be made adjustable, as matching is important at this frequency. Dimensions can be taken from Table 18-I.

(For an example of stacking several commercial 220-Mc. beams, see Tilton, "A 66-Element Stacked-Yagi Array for 220 Mc.," *QST*, January, 1959.)

MISCELLANEOUS ANTENNA SYSTEMS

Coaxial Antennas

At v.h.f. the lowest possible radiation angle is essential, and the coaxial antenna shown in Fig. 18-19 was developed to eliminate feeder radiation. The center conductor of a 70-ohm concentric (coaxial) line is extended one-quarter wave beyond the end of the line, to act as the upper half of a half-wave antenna. The lower half is provided by the quarter-wave sleeve, the upper end of which is connected to the outer conductor of the concentric line. The sleeve acts as a shield about the transmission line and very little current is induced on the outside of the line by the antenna field. The line is non-resonant, since its characteristic imped-

ance is the same as the center impedance of the half-wave antenna. The sleeve may be made of copper or brass tubing of suitable diameter to clear the transmission line. The coaxial antenna is somewhat difficult to construct, but is superior to simpler systems in its performance at low radiation angles.

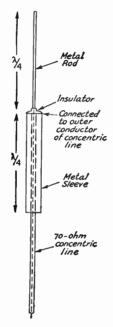


Fig. 18-19—Coaxial antenna. The insulated inner conductor of the 70-ohm concentric line is connected to the quarter-wave metal rod which forms the upper half of the antenna.

Broadband Antennas

Certain types of antennas used in television are of interest because they work across a wide band of frequencies with relatively uniform response. At very-high frequencies an antenna made of small wire is purely resistive only over a very small frequency range. Its Q, and therefore its selectivity, is sufficient to limit its optimum performance to a narrow frequency range, and readjustment of the length or tuning is required for each narrow slice of the spectrum. With tuned transmission lines, the effective length of the antenna can be shifted by retuning the whole system. However, in the case of antennas fed by matched-impedance lines, any appreciable frequency change requires an actual mechanical adjustment of the system. Otherwise, the resulting mismatch with the line will be sufficient to cause significant reduction in power input to the antenna.

A properly designed and constructed wideband antenna, on the other hand, will exhibit very nearly constant input impedance over several megacycles.

The simplest method of obtaining a broadband characteristic is the use of what is termed a "cylindrical" antenna. This is no more than a conventional doublet in which large-diameter tubing is used for the elements. The use of a relatively large diameter-to-length ratio lowers the Q of the antenna.

As the diameter-to-length ratio is increased,

end effects also increase, with the result that the antenna must be made shorter than thinwire antenna resonating at the same frequency. The reduction factor may be as much as 20 per cent with the tubing sizes commonly used for amateur antennas at v.h.f.

Plane-Reflector Arrays

At 220 Mc. and higher, where their dimensions become practicable, plane-reflector arrays are widely used. Except as it affects the impedance of the system, as shown in Fig. 18-20, the spacing between the driven elements and the reflecting plane is not particularly critical. Maximum gain occurs around 0.1 to 0.15 wavelength, which is also the region of lowest impedance. Highest impedance appears at about 0.3 wavelength. A plane reflector spaced 0.22 wavelength in back of the driven elements has no effect on their feed impedance. As the gain of a plane-reflector array is nearly constant at spacings from 0.1 to 0.25 wavelength, it may be seen that the spacing may be varied to achieve an impedance match.

An advantage of the plane reflector is that it may be used with two driven element systems, one on each side of the plane, providing for two-band operation, or the incorporation of horizontal and vertical polarization in a single structure. The gain of a plane-reflector array is slightly higher than that of a similar number of driven elements backed up by parasitic reflectors. It also has a broader frequency response and higher front-to-back ratio. To achieve these ends, the reflecting plane must be larger than the area of the driven elements, extending at least a quarter wavelength on all sides. Chicken wire on a wood or metal frame makes a good plane reflector. Closely spaced wires or rods may be substituted, with the spacing between them running up to 0.1 wavelength without reduction in effectiveness.

Cone Antennas

From the cylindrical antenna various specialized forms of broadly resonant radiators have been evolved, including the ellipsoid, spheroid, cone, diamond and double diamond. Of these, the conical antenna is perhaps the most interesting. With large angles of revolution, the variation in the characteristic impedance with changes in frequency can be reduced to a very low value, making such an antenna suitable for extremely wide-band operation. The cone may be made up either of sheet metal or of multiple wire spines. A variation of this form of antenna is widely used in TV reception.

Corner Reflectors

In the corner reflector two plane surfaces are set at an angle, usually between 45 and 90 degrees, with the antenna on a line bisecting this angle. Maximum gain is obtained with the antenna 0.5 wavelength from the vertex, but compromise designs can be built with closer spacings. There is no focal point, as would be the

case for a parabolic reflector. Corner angles greater than 90 degrees can be used at some sacrifice in gain. At less than 90 degrees the gain increases, but the size of the reflecting sheets must be increased to realize this gain.

At a spacing of 0.5 wavelength from the vertex, the impedance of the driven element is approximately twice that of the same dipole in free space. The impedance decreases with smaller spacings and corner angles, as shown in Fig. 18-20. The gain of a corner-reflector array with a 90-degree angle, 0.5 wavelength spacing and sides one wavelength long is approximately 10 db. Principal advantages of the corner reflector are broad frequency response and high front-to-back ratio.

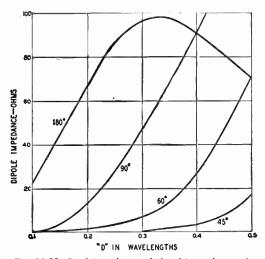


Fig. 18-20—Feed impedance of the driven element in a corner-reflector array for corner angles of 180 (flat sheet), 90, 60 and 45 degrees. "D" is the dipole-to-vertex spacing.

Parabolic Reflectors

A plane sheet may be formed into the shape of a parabolic curve and used with a driven radiator situated at its focus, to provide a highly directive antenna system. If the parabolic reflector is sufficiently large so that the distance to the focal point is a number of wavelengths, optical conditions are approached and the wave across the mouth of the reflector is a plane wave. However, if the reflector is of the same order of dimensions as the operating wavelength, or less, the driven radiator is appreciably coupled to the reflecting sheet and minor lobes occur in the pattern. With an aperture of 10 to 20 wavelengths, a practical size for microwave work, a beam width of approximately 5 degrees may be achieved.

A reflecting paraboloid must be carefully designed and constructed to obtain ideal performance. The antenna must be located at the focal point. The most desirable focal length of the parabola is that which places the radiator along the plane of the mouth; this length is equal to one-half the mouth radius.

Mobile and Portable-Emergency Equipment

The amateur who goes in for mobile operation will find plenty of room for exercising his individuality and developing original ideas in equipment. Each installation has its special problems to be solved.

Most mobile receiving systems are designed around the use of a h.f. converter working into a standard car broadcast receiver tuned to 1500 kc. which serves as the i.f. and audio amplifiers. The car receiver is modified to take a noise limiter and provide power for the

While a few mobile transmitters may run an input to the final amplifier as high as 100 watts or more, an input of about 30 watts normally is considered the practical limit unless the car is equipped with a special battery-charging system. The majority of mobile operators use phone.

In contemplating a mobile installation, the car should be studied carefully to determine the most suitable spots for mounting the equipment. Then the various units should be built in a form that will make best use of that space. The location of the converter should have first consideration. It should be placed where the controls can be operated conveniently without distracting attention from the wheel. The following list suggests spots that may be found suitable, depending upon the individual car.

On top of the instrument panel
Attached to the steering post
Under the instrument panel
In a unit made to fit between the lower lip
of the instrument panel and the floor at
the center of the car

The transmitter power control can be placed close to the receiver position, or included in the converter unit. This control normally operates relays, rather than to switch the power circuit directly. This permits a minimum length of heavy-current battery circuit. Frequency within any of the phone bands sometimes is changed remotely by means of a stepping-switch system that switches crystals. In most cases, however, it is necessary to stop the car to make the several changes required in changing bands.

Depending upon the size of the transmitter unit, one of the following places may be found convenient for mounting the transmitter.

In the glove compartment Under the instrument panel

In a unit in combination with or without the converter, built to fit between the lower edge of the instrument panel and the floor at the center

On the ledge above the rear seat In the trunk

Most mobile antennas consist of a vertical whip with some system of adjustable loading for the lower frequencies. Power supplies are of the vibrator, motor-generator, or transistor type operating from the car storage battery.

Units intended for use in mobile installations should be assembled with greater than ordinary care, since they will be subject to considerable vibration. Soldered joints should be well made and wire wrap-arounds should be used to avoid dependence upon the solder for mechanical strength. Self-tapping screws should be used wherever feasible, otherwise lock-washers should be provided. Any shafts that are normally operated at a permanent or semi-permanent setting should be provided with shaft locks so they cannot jar out of adjustment. Where wires pass through metal, the holes should be fitted with rubber grommets to prevent chafing. Any cabling or wiring between units should be securely clamped in place where it cannot work loose to interfere with the operation of the car.

NOISE ELIMINATION

Electrical-noise interference to reception in a car may arise from several different sources. As examples, trouble may be experienced with ignition noise, generator and voltage-regulator hash, or wheel and tire static.

A noise limiter added to the car broadcast receiver will go far in reducing some types, especially ignition noise from passing cars as well as your own. But for the satisfactory reception of weaker signals, some investigation and treatment of the car's electrical system will be necessary.

Ignition Interference

Fig. 19-1 indicates the measures that may be taken to suppress ignition interference. The capacitor at the primary of the ignition coil should be of the coaxial type; ordinary types are not effective. It should be placed as close to the coil terminal as possible. In stubborn cases,

two of these capacitors with an r.f. choke between them may provide additional suppression. The size of the choke must be determined experimentally. The winding should be made with wire heavy enough to carry the coil primary current. A 10,000-ohm suppressor resistor should be inserted at the center tower of the distributor, a 5000-ohm suppressor at each spark-plug tower on the distributor, and a 10,000 ohm suppressor at each spark plug. The latter may be built-in or external. A good suppressor element should be molded of material having low capacitance. Several concerns manufacture satisfactory suppressors. In extreme cases, it may be necessary to use shielded ignition wire. Suppressor ignition wire kits having the resistance distributed throughout the length of the wire are available from some automobile supply dealers. Distributed resistance of this type is somewhat superior to lumped resistance and may be used if the lead lengths are right to fit your car. They should not be cut, but used as they are sold.

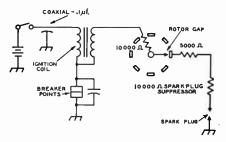


Fig. 19-1—Ignition system with recommended suppression methods.

Generator Noise

Generator hash is caused by sparking at the commutator. The pitch of the noise varies with the speed of the motor. This type of noise may be eliminated by using a 0.1- to 0.25 μ f. coaxial capacitor in the generator armature circuit. This capacitor should be mounted as near the armature terminal as possible and directly on the frame of the generator.

To reduce the noise at 28 Mc., it may be necessary to insert a parallel trap, tuned to the middle of the band, in series with the generator output lead. The coil should have about 8 turns of No. 10 wire, space-wound on a 1-inch diameter and should be shunted with a $30-\mu\mu$ f. mica trimmer. It can be pretuned by putting it in the antenna lead to the home-station receiver tuned to the middle of the band, and adjusting the trap to the point of minimum noise. The tuning may need to be peaked up after installing in the car, since it is fairly critical.

Voltage-Regulator Interference

In eliminating voltage-regulator noise, the use of two coaxial capacitors, and a resistor-mica-capacitor combination, as shown in Fig. 19-2, are effective. A 0.1- to 0.25-µf. coaxial capacitor

should be placed between the battery terminal of the regulator and the battery, with its case well grounded. Another capacitor of the same size and type should be placed between the generator terminal of the regulator and the generator. A 0.002-µf. mica capacitor with a 4-ohm carbon resistor in series should be connected between the field terminal of the regulator and ground. Never use a capacitor across the field contacts or between field and ground without the resistor in series, since this greatly reduces

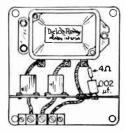




Fig. 19-2—The right way to install bypasses to reduce interference from the regulator. A capacitor should never be connected across the generator field lead without the small series resistor indicated.

the life of the regulator. In some cases, it may be necessary to pull double-braid shielding over the leads between the generator and regulator. It will be advisable to run new wires, grounding the shielding well at both ends. If regulator noise persists, it may be necessary to insulate the regulator from the car body. The wire shielding is then connected to the regulator case at one end and the generator frame at the other.

Wheel Static

Wheel static shows up as a steady popping in the receiver at speeds over about 15 m.p.h. on smooth dry streets. Front-wheel static collectors are available on the market to eliminate this variety of interference. They fit inside the dust cap and bear on the end of the axle, effectively grounding the wheel at all times. Those designated particularly for your car are preferable, since the universal type does not always fit well. They are designed to operate without lubrication and the end of the axle and dust cap should be cleaned of grease before the installation is made. These collectors require replacement about every 10,000 miles.

Rear-wheel collectors have a brush that bears against the inside of the brake drum. It may be necessary to order these from the factory through your dealer.

Tire Static

This sometimes sounds like a leaky power line and can be very troublesome even on the broadcast band. It can be remedied by injecting an antistatic powder into the inner tubes through the valve stem. The powder is marketed by General Cement and possibly others.

General Cement dealers can also supply a convenient injector for inserting the powder.

Tracing Noise

To determine if the receiving antenna is picking up all of the noise, the shielded lead-in should be disconnected at the point where it connects to the antenna. The motor should be started with the receiver gain control wide open. If no noise is heard, all noise is being picked up via the antenna. If the noise is still heard with the antenna disconnected, even though it may be reduced in strength, it indicates that some signal from the ignition system is being picked up by the antenna transmission line. The

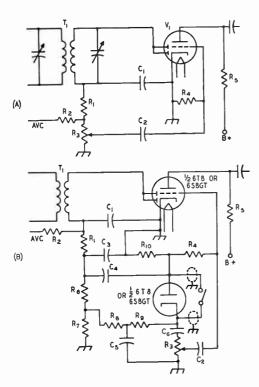


Fig. 19-3—Diagrams showing addition of noise limiter to car receiver. A—Usual circuit. B—Modification.

lead-in may not be sufficiently-well shielded, or the shield not properly grounded. Noise may also be picked up through the battery circuit, although this does not normally happen if the receiver is provided with the usual r.f.-chokeand-bypass capacitor filter.

In case of noise from this source, a direct wire from the "hot" battery terminal to the receiver is recommended. Ignition noise varies in repetition rate with engine speed and usually can be recognized by that characteristic in the early stages. Later, however, it may resolve itself into a popping noise that does not always correspond with engine speed. In such a case, it is a good idea to remove all leads from the generator so that the only source left is the ignition system.

Regulator and generator noise may be detected by racing the engine and cutting the ignition switch. This eliminates the ignition noise. Generator noise is characterized by its musical whine contrasted with the ragged raspy irregular noise from the regulator.

With the motor running at idling speed, or slightly faster, checks should be made to try to determine what is bringing the noise into the field of the antenna. It should be assumed that any control rod, metal tube, steering post, etc., passing from the motor compartment through an insulated bushing in the firewall will carry noise to a point where it can be radiated to the antenna. All of these should be bonded to the firewall with heavy wire or braid. Insulated wires can be stripped of r.f. by bypassing them to ground with 0.5-\mu f. metal-case capacitors. The following should not be overlooked: battery lead at the ammeter, gasoline gauge, ignition switch, headlight, backup and taillight leads and the wiring of any accessories running from the motor compartment to the instrument panel or outside the car.

The firewall should be bonded to the frame of the car and also to the motor block with heavy braid. If the exhaust pipe and muffler are insulated from the frame by rubber mountings, they should likewise be grounded to the frame with flexible copper braid.

Noise Limiting

Fig. 19-3 shows the alterations that may be made in the existing car-receiver circuit to provide for a noise limiter. The usual diodetriode second detector is replaced with a type having an extra independent diode. If the car receiver uses octal-base tubes, a 6S8GT may be substituted. The 7X7 is a suitable replacement in receivers using loktal-type tubes, while the 6T8 may be used with miniatures.

The switch that cuts the limiter in and out of the circuit may be located for convenience on or near the converter panel. Regardless of its placement, however, the leads to the switch should be shielded to prevent hum pick-up.

Several other noise limiter circuits are described in ARRL's publication, *The Mobile Manual For Radio Amateurs*. The *Mobile Manual* also describes a combination noise limiter and audio squelch circuit. Squelch circuits are designed to suppress receiver background noise in the absence of signals (see Chapter 5); their chief use is in fixed-frequency (net) operation.

At least one manufacturer (Gonset) produces a complete noise limiter unit. The unit is mounted external to the main chassis and takes operating voltages from the receiver.

A MOBILE CONVERTER FOR 3.5 THROUGH 28 MC.

Figures 19-4 through 19-7 show a crystal-controlled converter covering 3.5 through 28 Mc. without complex band switching or gangtuned circuits. Plug-in coil assemblies provide rapid band changing and allow construction for either single-band or multiband operation. The converter uses the car broadcast receiver as a tunable i.f. amplifier.

Plate power requirements for the converter are approximately 20 milliamperes at 200 to 250 volts. This means that the unit can be supplied from the car-receiver power pack without overloading it.

The Circuit

The circuit diagram of the converter is shown in Fig. 19-5. A 6BZ6 is used in the r.f. amplifier, and a 12AT7 operates as a mixer-oscillator. The oscillator is crystal-controlled and works on the low-frequency side of the signal frequency. J_1 , J_2 , and J_3 are the antenna-input, mixer-output and power jacks, respectively. S_1 performs the switching in changing over from ham-band to broadcast input. S_{1A} and S_{1B} shift the antenna from the converter input circuit to the car receiver, and S_{1C} is the heater on-off switch.

Since the tuning of the converter is fixed, the circuits of the r.f. amplifier and the mixer must be broadbanded to pass all frequencies in any ham band. A slug-tuned coil, L_3 , is used in the amplifier plate circuit, and RFC_1 provides a broad-band plate load for the mixer tube V_{2A} . The grid circuit of the amplifier also uses a slug-tuned coil and includes a trimmer capacitor, C_1 , that permits peaking the input for the antenna in use, or in tuning completely across a band. A slug-cored coil is used at L_4 to facilitate resonating the circuit near the crystal frequency.

The frequency of the oscillator must differ from the frequency of the received signal by the frequency of the tunable i.f. amplifier. With the car broadcast receiver following the converter, the i.f. range will be from approximately 550 to 1550 kc. Since the tunable i.f. range is thus limited to a band 100 kc. wide, the tuning range of the system with any single crystal will be restricted to 1 Mc. This is sufficient for all except the 28-Mc. band. Two crystals are required to cover the entire 10-meter band. The first of these gives a tuning range of 28 to 28.9 Mc. and the second permits tuning 28.8 to 29.7 Mc. An accompanying frequency chart lists the crystal frequencies and the ranges over which the broadcast receiver must be tuned to cover the amateur bands.

Construction

The input-tuning capacitor, C_1 , the pilot lamp and the switch are in line across the panel of the converter as shown in Fig. 19-4. Each of these components is centered $\frac{3}{4}$ inch down from the top of the case and each is separated from the other in horizontal plane by $\frac{1}{4}$ inches. The male jacks for the grid, plate and oscillator coils are below C_1 , I_1 and S_1 in that order. Each jack is centered $\frac{1}{8}$ inches up from the bottom of the cabinet.

The chassis, shown in Fig. 19-7, may be made of thin aluminum sheet and should be fastened to the side walls of the cabinet with homemade brackets, or angle stock. The sockets for V_1 (at the right as seen in the rear view) and V_2 are centered 15% inches in from the right and left edges of the chassis, respectively. J_3 is centered on the rear wall of the chassis with J_1 and J_2 to the right and left.

A bottom view of the converter clearly shows the components mounted below deck.

The exterior and the interior of the coil box are shown in Figs. 19-4 and 19-7. Wind the antenna coupling coils, L_1 in Fig. 19-5, around the ground ends of the grid coils before the latter are soldered in place. Wind the coupling coils rather snugly but not so tightly as to prevent adjustment of the coupling to L_2 during testing of the converter.

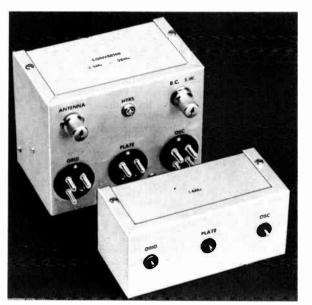


Fig. 19-4—The aluminum case for the converter measures $3\times4\times5$ inches (Bud CU-3005 or Premier AMC-1005). Amphenol type 86-CP4 male jacks mounted on the front of the box mate with MIP 4-prong sockets mounted on the rear of the coil compartment shown in the foreground. Knobs for C_1 and S_1 are to the left and right, respectively, of the pilot lamp. The coil box measures $2^1\!\!\!/ \times 2^1\!\!\!/ \times 2^1\!\!\!/ \times 5$ inches (Bud CU-3004 or Premier AMC-1004). Slug-adjustment screws for L_2 , L_3 and L_4 protrude through rubber grommets mounted on the

front wall of the plug-in coil assembly.

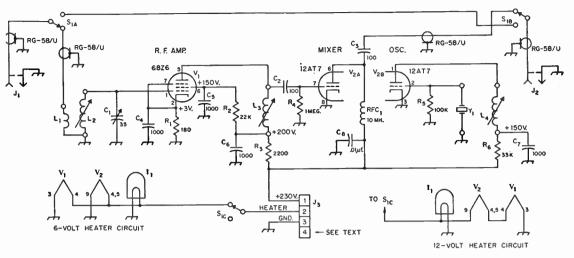


Fig. 19-5—Circuit diagram of the crystal-controlled mobile converter. Unless otherwise indicated, capacitances are in $\mu\mu f$., resistances are in ohms, resistors are $\frac{1}{2}$ watt.

 C_1 —35- $\mu\mu f$, midget variable (Mammarlund MAPC-35-B).

 C_2 , C_3 —100- $\mu\mu$ f. ceramic tubular.

C₄, C₅, C₆, C₇—1000-\(\mu\mu\)f. disk ceramic.

C₈-0.01-µf. disk ceramic.

l₁—Pilot-light assembly [Johnson 147-503 with No. 44 (6-volt) or No. 1815 (12-volt) lamp].

J₁, J₂—Motorola-type shielded jack (ICA 2378).

J₃—4-prong male chassis connector (Cinch-Jones P-304-AB).

L1, L2, L3, L1—See coil chart.

An a.c. transformer may be used for the filaments while testing the converter. The plate supply should deliver 20 milliamperes at 200 to 250 volts. A modulated-signal generator covering the bands for which the converter has been constructed is extremely helpful. To be most effective, the generator should have a 50-ohm output termination. A grid-dip meter for preliminary adjustment of the slug-tuned coils is useful, but not essential to alignment. If at all possible, the car receiver that is to be used as the tunable i.f. should be used during the testing.

Using coaxial-cable leads, connect the signal generator and the broadcast receiver to J_1 and J_2 , respectively. Switch S_1 to the ham-band position, and apply heater power. The receiver need not be turned on at this time, and plate

Fig. 19-6—A bottom view of the mobile converter. The amplifier tube socket at the right is mounted with Pin 7 facing toward the rear wall of the chassis. R_1 and R_2 are to the right and left of the socket, respectively. The socket for V_2 is mounted with Pins 4 and 5 facing toward the rear of the unit. C_2 is to the lower left of R_2 , and RFC_1 is mounted on the front wall of the housing. C_7 and R_6 are to the left of the base of the choke. C_6 , C_8 and R_5 are to the right of RFC_1 . The output coupling capacitor C_3 is supported between Terminal 4 of J_3 and Pin 6 of the socket for V_2 , R_1 and R_5 are partially visible to the right and left, respectively,

of the V2 socket.

R₁—180 ohms, ½ watt.

R₂-22,000 ohms, ½ watt.

 $R_3{-2200}$ ohms, $1\!\!/_{\!2}$ watt.

 R_1 —1 megohm, $\frac{1}{2}$ watt. R_5 —0.1 megohm, $\frac{1}{2}$ watt.

R₆-33,000 ohms, ½ watt.


RFC₁-10-mh. r.f. choke (National R-100S).

S₁—3-pole 3-position (used as 3 p.d.t.) selector switch (Centralab PA-1007).

Y₁—See text and frequency chart (International Crystals type FA-9).

power for the converter does not have to be applied. Now, rotate C_1 to approximately half capacitance and then adjust L_2 to resonance (use the grid-dip meter as the indicator) at the low end of the band. Move the grid-dipper over to the plate circuit of the amplifier and peak L_3 at the center of the band. Next, couple the meter to L_4 of the oscillator and tune the coil to the frequency of the crystal in use.

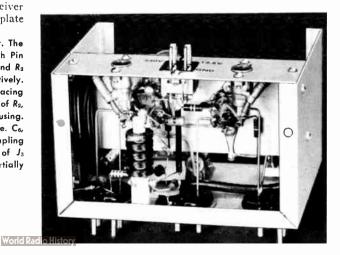After these initial adjustments, plate power may be applied to the converter and a frequency-indicating device used to detect oscillation of V_{2B} . If the grid-dip meter is the self-rectifying type it may be used for the check. An absorption-type wavemeter with indicator or a



Coil Chart for the Mobile Converter							
Band	Turns	Ind. Ronge, μh.		Type No.			
Mc.	$L_{\mathtt{i}}$	L_{2}	$L_{\rm a}$	L_4	$L_{\mathbf{a}}$	L_3	L_4
3.5-4	14	3664	64–105	105-200	120-F	120-G	120-H
7-7.3	7	9-18	18-36	36-64	120-D	120-E	120-F
14-14.35	• 4	3-5	5–9	9-18	120-B	120-C	120-D
21-21.45	3	2-3	3-5	3-5	120-A	120-B	120-B
28-28.9	3	1-1.6	1.6-2.7	2.7-4.5	1000-A	1000-B	1000-C
28.8-29.7	3	1-1.6	1.6-2.7	2.7-4.5	1000-A	1000-B	1000-C

Note: L_1 is wound with No. 28 d.c.c. wire at grounded end of L_2 . L_2 , L_3 and L_4 are slug-tuned coils manufactured by North Hills Electric Co., Inc. (Mineola, L.I.)

receiver tuned to the crystal frequency (with the b.f.o. on) may also be used for the purpose. L_4 should be tuned through resonance to the *high*-frequency side of the crystal frequency until the crystal oscillates reliably as indicated by rapid starting when plate power is turned on.

With the converter and the i.f. amplifier both turned on, and with the signal generator tuned to the center of the band, tune the receiver until the test signal is heard. Peak L_3 and L_4 for best response and then peak L_2 with C_1 set at half capacitance. The coupling between L_1 and L_2 may now be adjusted for optimum performance.

If the aforementioned test equipment is not available, the converter may be aligned while using a strong local of known frequency as the signal source. Of course, the signal frequency must be in the band for which the converter is to be aligned. In using this system, first set the broadcast receiver as closely as possible to the proper i.f. frequency (see the frequency chart) and then tune L₄ until the crystal oscillates. It is advisable to tune the receiver through a narrow

range as the oscillator coil is being adjusted to assure that the test signal will be heard as soon as the crystal breaks into oscillation. After the signal is detected, the grid, plate and oscillator circuits may be adjusted for maximum gain.

The mobile antenna should be resonant and tightly coupled to the converter. Traps for suppressing interference caused by strong local broadcast signals that feed in through the converter to the tunable i.f. have not been included in the converter because the need for them will be entirely dependent on local broadcast-station power and frequency assignments.

(Originally described in QST, Nov. 1957). (For a description of a bandswitching crystal-controlled converter, see QST, January, 1955, or The Mobile Manual for Radio Amateurs.)

Frequency Chart for the Mobile Converter Band Crystal I.F. Range Mc. Freq., Mc. Kc.3.5 - 42.9 650-1100 7 - 7.36.4 600-900 14-14.35 13.4 600-950 21-21.45 20.4 600-1050 28-28.9 27.4 600-1500 28.8-29.7 28.2 600-1500

Note: I.f. range indicates broadcast receiver tuning range necessary for covering the associated amateur frequencies.



Fig. 19-7—Homemade L-shaped chassis, mounted on small brackets fastened to the side walls of the converter housing, is $4^{1}\%_{6}$ inches long, 2 inches wide and $1^{1}\%_{2}$ inches deep. V_{1} is mounted on the chassis to the right of V_{2} as seen in this rear view. J_{1} , J_{3} and J_{2} are in line in that order from right to left across the rear wall of the chassis. An interior view of a coil compartment is shown in the foreground. Terminals of the coils are soldered directly to the socket terminals. Notice that the crystal for the oscillator is mounted adjacent to L_{4} .

"HYBRID" CRYSTAL-CONTROLLED CONVERTER

The converter shown in Figs. 19-8 and 19-9 combines a 12-volt r.f. pentode and two transistors in a circuit that requires only a 12-volt d.c. source for all power requirements. As a result, it is admirably suited for use with any of the newer hybrid receivers. ("Hybrid" receivers combine tubes and transistors; the tubes are special in that they operate with only 12 volts on plate and screen.) The oscillator is crystal-controlled, and stations are tuned in by adjustment of the b.c. receiver used as a tunable i.f. amplifier.

Referring to the circuit diagram, Fig. 19-8, the r.f. stage uses a 12EK6 pentode with a fixed-tune input circuit, L_1L_2 , and a plate circuit tuned from the panel through C_1 . Mixer and oscillator stages both use the 2N274 transistor; the mixer input is "tapped down" on the coupling circuit to provide a good match and to maintain selectivity. In the oscillator section, crystals and plate coil are switched. It will be noted that, for simplicity in presenting the diagram, all of the coils at L_1 and L_2 and all of the taps on L_3 are not shown. Further, all of the crystals are not shown. However, after a little study it should be apparent to anyone contemplating construction of the unit where the missing coils, taps and crystals are connected.

All of the components fit comfortably in and on a $3 \times 4 \times 5$ -inch Minibox. Referring to Fig. 19-9, the components are mounted on the U-shaped half of the Minibox. It is intended that

the other half of the Minibox, the portion with the guide lips, be mounted under the dashboard of the car. It is then a simple matter to remove or replace the "working" portion of the converter. The crystals plug in at the back of the box and are covered by a small aluminum box that prevents their accidental damage and eliminates a source of broadcast feedthrough.

Two 3-pole 5-position ceramic rotary switch sections provide all of the necessary switching. The poles S_{1A} , S_{1B} and S_{1B} make up the rear section. The r.f. chokes used at L_6 and L_7 mount directly on the front section (S_{1F} and the others).

Range	Crystal	B.C. Receive	er L ₁	L_2
3.5· 4.0	2.5 Mc.	1000- 1500	3 t. No. 28	68-130 μh. (Miller 4409)
7.0- 7.5	6.0 Mc.	1000- 1500	2 t. No. 28	14.8-31 μh. (Miller 4407)
14.0- 14.5	13.0 Mc.	1000- 1500	1½ t. No. 18	6.7-15 µh. (Miller 4406)
21.0· 21.5	20.0 Mc.	1000- 1500	1 t. No. 18	3.1-6.8 µh. (Miller 4405)
28.54 29.5	28.0 Mc.	540- 1500	1 t. No. 18	1.5-3.2 μh. (Miller 4404)

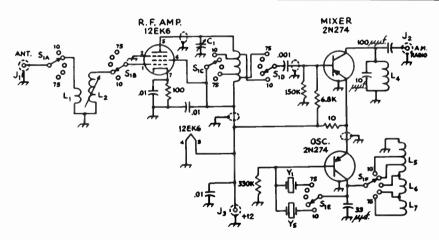


Fig. 19-8—Circuit diagram of the hybrid crystal-controlled converter. Unless specified otherwise, capacitances are in μf., resistances are in ohms, resistors are ½ watt.

 C_1 —100- $\mu\mu$ f. midget variable (Hammarlund HF-100).

J1, J2, J3-Phono jacks.

L₁, L₂-See table.

L₃—47 turns No. 20, 16 t.p.i., 1-inch diam. (B&W 3015 Miniductor). S_{1C} taps 5, 7, 12 and 25 turns from plate end; S_{1D} taps 4, 6, 11, 19 and 30 turns from plate end.

L₄-1-mh. r.f. choke (Millen J300-1000).

Lo-31 turns No. 20, 16 t.p.i., %-inch diam. (B&W 3007

Miniductor). S_{1P} taps 9½ and 16½ turns from grounded end.

L₀-25 μh. r.f. choke (Millen J300-25)

L₇-100-μh. r.f. choke. (Millen 34300-100)

S₁—Six-pole 5-position rotary ceramic switch, 3 poles per section. (Centralab PA-5 sections on PA-301 index assembly. Sections spaced ½ inch and 2½ inch from index.)

Y1-Y5-See crystal table.

All of the input coils, L_1L_5 , are mounted on the rear apron, just above the tube socket. To minimize coupling from the coils to L_3 , L_3 is mounted parallel to the front panel, supported at one end by a tie point and at the other by a 1-inch ceramic insulator. Further to isolate the coils, an aluminum shield is placed between L_3 and the set of input coils. The remaining coil, L_6 , is mounted alongside the switch.

Tie points are used generously throughout the converter, to support components that might otherwise vibrate loose. The transistor leads are all soldered to tie points. While soldering, hold the wire in pliers or other form of "heat sink," to minimize the heat that reaches the transistor.

Note in Fig. 19-8 that some of the leads use shielded wire. These include the plate lead of the r.f. stage, the lead from S_{1D} to the base of the mixer transistor and the collector lead to the oscillator transistor. In wiring the converter, it is advisable to plan the wiring in advance, since

of necessity some wires will eventually interfere with others. If the switched leads to L_t and L_2 are wired before the shield and L_3 are installed, the construction will be easier than if the leads to L_1 and L_2 were left to the last.

With the 12EK6 removed from its socket, the converter should not draw more than 3 ma. or so, The oscillator can be checked for oscillation by listening for it on a communications receiver. If the oscillator should fail to work on 15 or 10 meters, the taps on L_5 may have to be moved.

Replace the tube in its socket and adjust the input coils, L_2 , to resonance with a grid-dip meter. With the ear radio tuned to the middle of its range, touch up L_2 on each band for maximum noise. Peak C_1 for maximum gain while listening to a weak signal, and once more check the tuning of L_2 . On the higher frequencies it will be possible to hear "image" signals on occasion. This is an inescapable result of using a low i.f. (the b.c. receiver) and not an indication that the converter isn't working properly.

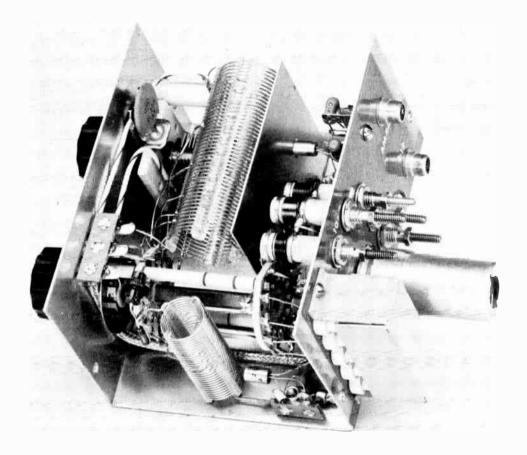


Fig. 19-9—The 12-volt hybrid crystal-controlled converter with the hausing removed. The large cail (center) is the interstage coupling coil between r.f. tube and mixer transistor. The tube and crystals plug in at the rear, and the input tuning slugs project out the rear. The antenna jack cannot be seen; it is below the tube socket.

The only panel controls are interstage tuning and band switch.

Converters 473

CRYSTAL-CONTROLLED CONVERTERS FOR 50 AND 144 MC.

The mobile converters shown in Figs. 19-10 through 19-13 combine simplicity with good v.h.f. design practice. Although only two tubes are used in each, the converters include a stage of r.f. amplification plus crystal-controlled oscillators. Ten meters was chosen as the i.f. because when the broadcast receiver is used as the tunable i.f. for v.h.f. converters images are a problem, and only 1 Mc. at a time could be tuned. The converters described here, therefore, are designed to work into a 10-meter converter or receiver. This can be a tunable converter which in turn works into the broadcast receiver, or a complete self-contained 10-meter receiver.

The 50-Mc. Unit

The circuit diagram for the 50-Mc. unit is shown in Fig. 19-11. A 6AK5 is used as an r.f. amplifier. The same gain with lower noise can be obtained with a cascode-type dual-triode amplifier, but the performance of this pentode stage is satisfactory and its design is considerably simpler than the triode amplifier.

The crystal oscillator makes use of a 22-Mc. overtone crystal. A crystal on the required injection frequency eliminates the need for multiplier stages, and makes possible the use of a simple oscillator circuit. The 10-meter receiver or converter is tuned from 28 to 30 Mc. in covering 50 to 52 Mc. If a general coverage receiver covering 26 to 30 Mc. is used, a 24-Mc. crystal in the oscillator will allow tuning 50 to 54 Mc. However, any injection frequency may be used to cover a desired portion of the band.

The pentode half of the 6U8 tube is used as a mixer. The oscillator and mixer sections are in the same tube envelope so there is enough stray coupling between the two for adequate oscillator injection.

The diagram shows the heaters connected for 12 volts. If 6-volt operation is desired, the heaters are connected in parallel and R_1 is disregarded.

The converters are built in a $5\frac{1}{4} \times 3 \times 2\frac{1}{8}$ -

inch Minibox. All of the parts are mounted on the bottom half of the box while the upper half (the one with lips) is fastened under the car dash. The bottom half containing all the components can be slid in and out for easy servicing.

Fig. 19-10 shows the placement of most of the components. The output peaking control C_1 and switch S_1 are mounted on one side of the chassis to form the front panel. The tubes, slug-tuned inductances, crystal socket and antenna connectors are mounted directly opposite on the back wall. Two tie-points are bolted to the base of the box for connecting and supporting leads and components. When wiring, make the r.f. leads as short and direct as possible.


The 144-Mc. Unit

The circuit diagram for the 144-Mc. converter is shown in Fig. 19-13. Two 6U8 tubes are used with the pentode section of one tube acting as the r.f. amplifier followed by the triode-section mixer. The other 6U8 is used as an overtone crystal oscillator and pentode frequency multiplier. By combining all the features of a 4-tube crystal-controlled converter in a two-tube model space-saving simplicity is achieved.

The same basic circuit used in the 50-Mc. model is followed in the 144-Mc. unit except for the addition of a multiplier stage following the crystal oscillator. The oscillator operates at 38.666 Mc. and is multiplied to 116 Mc. in the tripler stage. As in the 50-Mc. converter, this unit is designed to work into a 10-meter receiver or converter. If the i.f. tunes from 27 to 30 Mc., the converter will tune from 144 to 147 Mc. However, any segment of the band may be tuned by choosing the proper crystal frequency.

Unlike the 50-Mc. converter, the oscillator-multiplier stages of the 144-Mc. converter are physically separated from the mixer stage. It is necessary, therefore, to couple the 116-Mc. energy from the multiplier stage to the grid of the mixer. Capacitor C_2 is used for this purpose. It consists of a pair of twisted hook-up wires with one end of one lead connected to the mixer

Fig. 19-10—View of the 50-Mc. converter. The Inductances are from left to right: (bottom) L₇, (top) L₅L₆, L₂L₄, L₁L₂. The top af crystal Y₁ can be seen between the tubes. The 22-ahm 2-watt resistor in the center of the chassis is the heater current compensating resistar, used for 12-volt aperation. Input and output antenna connectors are maunted on opposite ends of the back wall. Power is fed to the unit through the twisted power cable running in from the left side of the photograph.

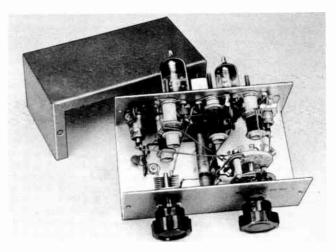

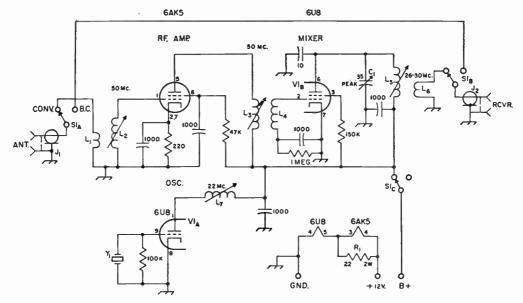


Fig. 19-11—Schematic diagram for the 50-Mc. mobile converter. All resistors ½ watt unless otherwise specified. Capacitor values below 0.001 μf. are in μμf. All 0.001 μf. capacitors are disk ceramic. Other fixed capacitors are tubular ceramic.

 C_1 —35- $\mu\mu$ f. midget variable capacitor (Hammarlund MAPC-35-B).

J1, J2-Automobile type antenna connectors.

 L_1 —3 turns No. 20 insulated wire, close-wound over cold end of L_2 .

L₂--9 turns No. 20 enam. wire, close-wound on $\frac{1}{2}$ inch slug tuned coil.

L_a—16 turns No. 20 enam. wire, close-wound on ½ inch stug tuned coil form.

L₄—6 turns No. 20 insulated wire, close-wound over cold end of L₃

L₅-14 turns No. 20 enam. wire, close-wound on ½ inch

slug tuned coil form.

L₆—2 turns No. 20 insulated wire, close-wound over cold end of L₂.

L₇—28 turns No. 30 enam. wire, close-wound on ½ inch slug tuned coil.

R₁—22-ohm 2-watt resistor (used for 12-volt heater operation only).

S₁—Three-pole two-position rotary switch (Centralab PA-2007).

Y₁—22 Mc. overtone crystal. (International Crystal type FA-5 for miniature socket, FA-9 for standard socket).

grid and the end of the other lead connected to the multiplier plate.

The circuit diagram shows the heaters connected for 12-volt operation. For 6 volts, the heaters should be connected in parallel.

The same basic outline of construction used in the 50-Mc. converter is followed in the 144-Mc. unit. Fig. 19-12 shows how output peaking

control C_1 and the control switch S_1 are mounted on the front wall of the chassis while most of the remaining parts are secured to the rear surface. A single tie point is mounted on the bottom of the chassis for connecting and supporting various leads. The input and output antenna connectors are mounted at opposite ends of the back wall of the chassis.

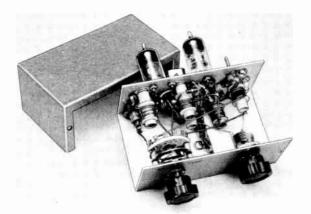


Fig. 19-12—View of the 144-Mc. converter. The inductances from left to right are: (top) L_1L_2 , L_2L_4 , L_2L_6 , (bottom) L_7 and L_8 . All components except S_1 and C_1 are mounted on the back wall of the chassis. A single tie point in the bottom of the channel supports various leads and provides junctions for sundry connections. The input and output antenna connectors are placed near the bottom right and left of the back panel. The crystal Y_1 is between the two tubes. Converter power is fed through the twisted cable which passes through a hole and grommet in the back wall of the chassis.

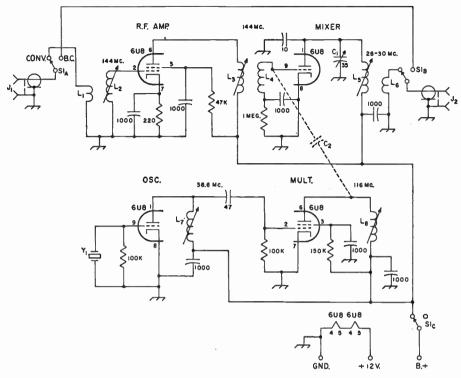


Fig. 19-13—Schematic diagram for the 144-Mc. converter. All resistors $\frac{1}{2}$ watt unless otherwise specified. Capacitor values below 0.001 μ f. are in $\mu\mu$ f. All 1000- $\mu\mu$ f. capacitors are disk ceramic. Other fixed capacitars are tubular ceramic.

- C₁—35- $\mu\mu$ f. midget variable capacitor (Hammarlund MAPC-35-B).
- C2-Oscillator injection capacitor (see text).
- J₁, J₂—Automobile type antenna connectors.
- L₁-2 turns No. 18 enam., % inches long, on ½ inch slug tuned coil form.
- L₂—2 turns No. 20 insulated wire, close wound over cald end of L₁.
- L_s—2 turns Na. 18 enam., ¾ inches lang, on ½ inch slug tuned coil form.

Testing the Converters

The 50-Mc. converter requires 0.625 ampere at 6 volts (or 0.45 ampere at 12 volts) for the heaters, and around 15 to 20 at 150 volts for the plate supply. If the car radio delivers in excess of 180 volts, the plate voltage on the converter should be dropped by a series resistor.

The 144-Mc. converter requires 0.9 ampere at 6 volts (or 0.45 ampere at 12 volts) for the heaters. A plate voltage of 150 volts is required at about 30 ma.

All tuned circuits should be checked for resonance with a grid-dipper. The proper frequency for each circuit is given in Figs. 19-11 and 19-13. Apply power to the converter under test, and adjust the oscillator circuit until it goes into oscillation. This can be confirmed by tuning the home receiver to the oscillator frequency. Tune

- L₄—2 turns No. 20 insulated wire, close waund aver cold end of L₃.
- L₆—9 turns No. 24 enam., clase wound on ½ inch slug tuned coil form.
- L_e—2 turns Na. 20 insulated wire, clase wound over cold end of L_s.
- L₇—10 turns No. 24 enam., close wound on ½ inch slug tuned coil form.
- L_e-5 turns No. 18 enam., ½ inches long, on ½ inch slug tuned coil form.
- S_1 —Three-pole two-position rotary switch (Centralab PA-2007).
- Y₁—38.666 Mc. overtone crystal (International Crystal Ca. type FA-5 far miniature sacket, FA-9 far standard sacket).

the oscillator inductance until the maximum oscillator signal is obtained. Now feed a 50 or 144-Mc. signal into the converter under test. This signal may come from a signal generator or a grid-dip meter, it may be a harmonic from a low-frequency transmitter stage, or it may be an actual signal from the antenna. Go through the converter stage by stage, adjusting the inductances for peak output.

After the first run the converter should be spot-checked through the entire band to make sure that the over-all response is fairly uniform.

The output capacitor C_1 is used to peak the output circuit during normal operation, and during the preliminary tune-up it must be peaked at each frequency on which the converter is checked. L_{δ} is adjusted so that C_1 peaks at mid-capacitance in the center of the i.f. tuning range.

A 65-WATT MOBILE TRANSMITTER

The transmitter shown in Figs. 19-14 through 19-20 is a compact (14 inches wide, 1134 deep and 3½ inches high) self-contained unit featuring a transistorized modulator and power supply. The output stage is a plate-modulated 6883 (12.6-volt heater version of the 6146). When the transmitter is being used the front section drops down, as shown in Fig. 19-14, to reveal the panel controls. Latches on either side secure the hinged section and prevent its rattling.

Referring to the circuit diagram, Fig. 19-19, a Nuvistor v.f.o. in the 160-meter band is followed by a 12BA6 stage driven at 80 meters. This in turn is followed by a 12AU6 frequency



Fig. 19-14—The 65-watt mobile transmitter has a Nuvistor v.f.o., a 6146 output stage and transistors in the modulator and power supply. In this view the sheet-metal top and sides have been removed to show the arrangement of parts. The panel carrying the meter and switches (see Fig. 19-18) is recessed in a $3\frac{1}{2}$ high \times $2\frac{3}{4}$ deep by 14-inch box; the box is hinged and folds up when the transmitter is not in use. Major chassis is built from $\frac{3}{4}$ -inch wide by $\frac{1}{6}$ -inch thick aluminum angle and a $\frac{9}{2}$ \times 14-inch sheet of aluminum. A ventilation hole covered with cane metal is partially visible below the 6146 (center).

The 6883 socket is mounted on a $2\times4\frac{1}{2}\times3\frac{1}{4}$ -inch miniature chassis (Bud CB-1625) that houses the multiplier and driver plate coils; see Fig. 19-16. Controls (upper panel) from left to right are v.f.o. tuning, bandswitch (upper) and driver tune, output loading switch, loading, plate tuning and plate bandswitch. Toggle switch just visible under the plate tuning control is the on-off switch in the 12-volt line.

Controls on the bottom panel, from left to right, are gain (above the microphone jack, tune switch, zero switch, and meter switch above the key jack.

multiplier that works "straight through" when the output frequency is 80 or 40 meters; it doubles to 40 meters when the output frequency is 20 or 15 meters, and it quadruples to 20 when the output band is 10 meters. A 6417 driver works "straight through" on all bands except 10 meters, when it is operated as a doubler. The output stage uses a Harrington Electronics GP-50 tank circuit for coupling to the antenna; this prefabricated unit is intended for use with link coupling, but in this application a pinetwork circuit is used and the coupling link is put to work with a germanium diode in an output-indication circuit. The loading control drives a dual capacitor, and a loading switch, S_3 , allows one or two sections of the variable to be used or for additional fixed capacitors to be connected.

In the modulator circuit, a two-stage speech amplifier is used ahead of the 2N242 driver to bring the carbon-microphone signal to a useful level. The driver transformer, T_3 , is actually a transistor output transformer, but it has the right ratio to give proper push-pull drive for the 2N441 modulators. The microphone jack has provision for a push-to-talk switch on the microphone; the push-to-talk circuit is used to control a relay, K_1 , that doubles as antenna changeover relay and power switch.

The power supply has two transistors that oscillate at several hundred c.p.s.; this a.c. is

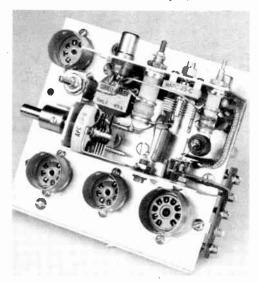


Fig. 19-15—The v.f.o. section is built in the U-shaped portion of a $3\frac{1}{4} \times 2\frac{1}{6} \times 1\frac{3}{6}$ -inch Minibox (Bud CU-2101-A) mounted on a sheet of aluminum; the other half of the Minibox serves as the cover. The Nuvistor socket and the oscillator coils are mounted on one side of the Minibox. Jack J_1 is mounted on the other side of the Minibox and is visible between the two right-hand tube sockets.

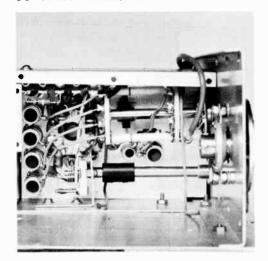


Fig. 19-16—View into the 6883 socket housing; the v.f.o. section has been removed. The short length of coaxial cable running from the front section of the switch is terminated in P_1 . Coils L_4 , L_5 and L_6 are visible between the two switch wafers; the other coils are the driver plate-circuit inductors. The driver plate tuning capacitor is mounted an a small bracket.

Planetary drive for the v.f.o. capacitor (right) is English and distributed in the U.S. (Arrow Electronics).

stepped up through T_a and rectified in a dual circuit that provides 600- and 300-volt outputs.

To eliminate mechanical linkages, two bandswitches are used. One, S_1 , switches a padding capacitor across the v.f.o. on all bands but 80 meters (to restrict the tuning range) and also selects the proper coils for the multiplier and driver plate circuits. The other band switch, S_2 , is part of the pre-fabricated tank circuit. Remembering to turn two band switches when changing bands is no great trick.

The meter switch, S_8 , allows the 0-1 milliammeter to be used as a 0-10 milliammeter for measuring grid current and as a 0-200 milliammeter for measuring cathode current. The resistance of R_1 was beyond the limits of measurement of the lab equipment, but it was adjusted to give a 0-10 ampere range to the meter when switched to the MoD position. If the builder does not have access to an ammeter in this range, he can guess at the value of R_1 and use

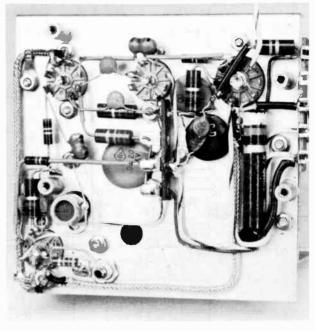


Fig. 19-17—View underneath the v.f.o./multiplier section. The plate is supported by four tapped pillars.


anything that holds the meter on scale during modulation peaks.

When a transistor power supply is overloaded it stops working. This means that under normal conditions a transistor power supply would not continue to function if the final amplifier were off resonance, and tuning the transmitter would be a touchy cut-and-try process. To facilitate tune-up, a 500-ohm resistor is cut into the 6883 cathode circuit when S_4 is opened. This limits the off-resonance plate current to a low value.

The cabinet for the transmitter is special and made from 34-inch-wide aluminum angle and 18-gauge (0.040) sheet stock. The cover and sides are not shown in any of the illustrations; they are made from one piece of sheet stock bent in the shape of a shallow U. The transmitter is hung under the instrument panel of the car by two brackets that make up to the sides of the transmitter. Whether or not a ventilation

Fig. 19-18—Rear view of the meter panel. Leads from this unit terminate in the 11-pin socket, which is mounted on the back of the housing opposite this panel. A jumper cable plugs into this socket and into a similar socket in the bottom of the major unit.

The first three stages of the speech-amplifier section are mounted on a plastic plate (lower left) next to the gain control. Transformer \mathcal{I}_1 can be seen at the center of the panel.

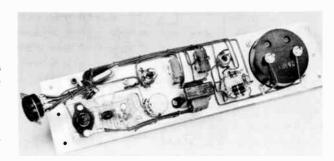

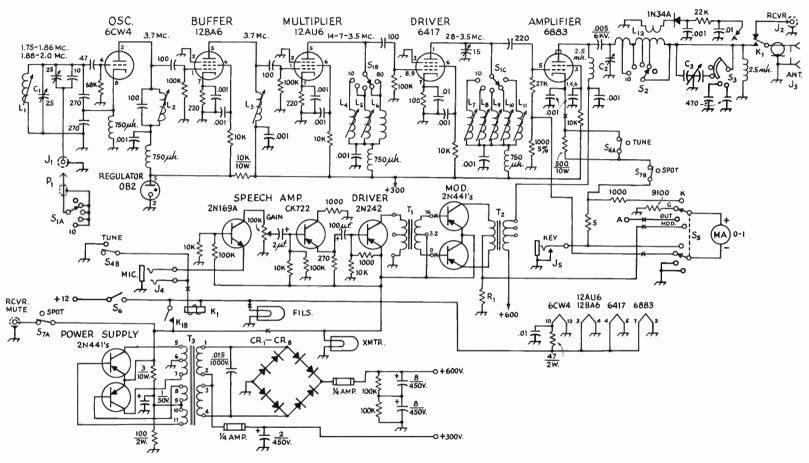


Fig. 19-19—Circuit diagram of the mobile transmitter. Unless specified otherwise, capacitances are in $\mu\mu$ f., decimal values are in μ f., resistances are in ohms, resistors are ½ watt.

65-Watt Transmitter

 C_1 —25- $\mu\mu$ f. variable (Hammarlund APC-25-B).

 C_2 =200- $\mu\mu$ f. variable (Part of Harrington Electronics GP-50 tank assembly).

C_s—Dual variable capacitor, 365 $\mu\mu$ f. per section (Miller 2112).

CR₁, CR₈—600 p.i.v. 750·ma, silicon rectifier (Sarkes Tarzian 1N2484).

J₁, J₂-Phono jack.

J_s—Coaxial chassis receptacle (SO-239).

J₄—Three-conductor phone jack.

J₅-Closed-circuit phone jack.

 K_1 —D.p.d.t. antenna relay, 12-volt coil (Advance AH/C2/12VD).

 L_1 —40 μ h. (Miller 4408, 30 to 69 μ h.).

L₂—16–24-μh. adjustable inductor (Miller 4507).

L₃--68-130-\(mu\), adjustable inductor (Miller 4409).

L₄-9-16-µh, adjustable inductor (Miller 4506).

L₅-24-35µh, adjustable inductor (Miller 4508).

 L_8 —100- μ h. r.f. choke (Millen 34300-100).

 L_7 —0.9—1.6- μ h. adjustable inductor (Miller 4403).

L₃-1.5-3.2-µh. adjustable inductor (Miller 4404).

 L_0 =3.1-6.8- μ h. adjustable inductor (Miller 4405).

 L_{10} —15–31- μ h. adjustable inductor (Miller 4407).

 L_{11} —68–130- μ h. adjustable inductor (Miller 4409).

L₁₂—Part of Harrington Electronics GP-50 tank assembly. P₁—Phono plug.

R₁—One to two feet of heavy (No. 12 or so) wire, adjusted to give 10-ampere full-scale reading. See text.

S₁—3-pole 5-position rotary switch, two sections. (Made from two Centralab PA-3 sections and one PA-301 index assembly).

S₂—Part of Harrington Electronics GP-50 tank assembly.
S₈—10-position single pole, progressively unshorting
(Centralab PA-13 section and PA-301 index assembly).

S₄-S.p.s.t. toggle switch.

S₅—Two-pole 6-position (4 used) rotary ceramic, nonshorting (Centralab PA-2003).

S₈—15-ampere 125-volt toggle switch (Cutler-Hammer 7361K5).

T₁.-48-ohm c.t. to 3.2/8/16-ohm secondary. 3.2-ohm tap used as center tap for secondary. (Thordarson TR-61).

T₂—40-watt output transformer, 6-ohm c.t. primary to 6000-ohm secondary (Triad Ty-66A).

T₃—Toroidal power transformer, 12.6 v. input, 300/600 v. at 200 ma. output (Triad TY-84).

hole (covered with cane metal) is placed in the cover will depend upon whether the car leaks.


The front compartment that drops down is also made of sheet stock and angle stock. The panel of this section makes up to angle stock on the sides; Fig. 19-14 suggests the location of these strips by the visible heads of screws on the right-hand end past the meter.

Also not visible in any of the pictures is the socket that picks up the leads from the dropped panel (see Fig. 19-18). This socket is located under the two horizontally-mounted power transistors at the rear center of the transmitter; the socket is an Amphenol 77MIP11 and the mating cable plug is an Amphenol 86-PM11. A small "x" is shown in Fig. 19-19 in each lead that is run through these plugs and sockets. The 11th lead is a ground lead, not necessary when everything is bolted together but useful during the testing stage.

Many of the sections of the transmitter can be tested before their final placement in the unit, and this will make the initial testing easier. The power supply can be tested as a unit before installation, as can the speech amplifier and driver and modulator. The oscillator can be tested out of the transmitter, but its final adjustment must be made in the transmitter because P_1 and J_1 must be connected. The high-frequency range is adjusted first by setting S_1 to the 80meter position and setting C_1 at minimum capacitance. The slug in L1 is then set for a frequency of 2.005 Mc. (4.010 Mc. if the receiver is tuned to 75 meters). S₁ is then switched to another band and C1 is turned to maximum capacitance. The 25-µµf. trimmer capacitance should then be set to give an oscillator frequency of 1.745 Mc. (3.490 Mc.).

The cores of the various inductors are adjusted for maximum drive in the various bands; in some cases it may be found advantageous to "stagger tune" two stages. In operation, the 6883 is run with a grid current of 3 to 4 ma. and a cathode current of 120 ma.

Fig. 19-20—Power supply and modulator of the mobile transmitter. The bridge-rectifier diodes, CR1 through CR8, are mounted on a plastic sheet above the power transformer T3 (left). Modulator transistors are mounted on vertical plate (insulated by mica washers). The entire section, including the modulation transformer (right), is supported by tapped pillars.

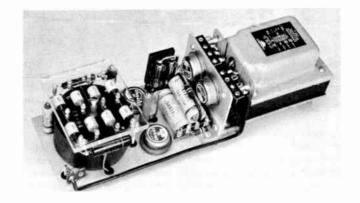

MOBILE TRANSMITTERS FOR 50 AND 144 MC.

Figs. 19-21 through 19-26 show circuits and constructional details of compact transmitters covering the 6- and 2-meter bands. The units are only 3 inches deep and therefore are suitable for under-the-dash mounting.

Output on 50-Mc. is obtained by using crystals in the 50-Mc. range. This eliminates any necessity for multiplier stages and greatly simplifies the circuit. In the two-meter unit, a 48-Mc. crystal is used which is multiplied to 144 Mc. by a tripler stage.

Although the r.f. amplifier used in the transmitters will operate at higher voltages, the units are designed primarily to work from a 300-volt, 100-ma. supply. A transistor modulator can be used with the units with a saving in total current drain.

The 50-Mc. Unit

The circuit of the 50-Mc. transmitter is shown in Fig. 19-23. A 5763 (6417 when using 12-volt heaters) is triode-connected in an overtone-type crystal oscillator. Feedback winding L_2 helps to sustain 3rd-overtone oscillation and may require some slight adjustment for optimum output in its placement with respect to L_1 . The 50-Mc. signal from the oscillator is capacitively coupled to the grid of the 2E26 (6893 when using 12-volt heaters) amplifier. A jack J_1 on the rear of the transmitter allows the grid



Fig. 19-21—View of the 50-Mc. transmitter showing the r.f. amplifier tank circuits and output loading control. C_3 is on the top right of the panel with C_2 just below it. Output indicator I_1 is below C_2 . This view also shows the two antenna connectors, power plug and grid current jack which are mounted on the rear surface.



Fig. 19-22—The 50-Mc. mobile transmitter is built into a $7\times5\times3$ -inch aluminum Minibox (Bud CU-3008). Oscillator coil L_1L_2 is near the top left. The jack on the right rear panel is the grid-current meter jack. One-inch holes are punched in both halves of the Minibox for ventilation. Perforated hole plugs can be used for neater appearance. In actual use, the transmitter would sit with the tubes horizontal. The half of the box at left is mounted under the car dash so that the transmitter half can be easily pulled in and out of position for servicing or adjustment.

current to be measured whenever it is necessary. The amplifier plate tank circuit, C_2L_3 , is tuned to resonance by variable capacitor C_2 , and antenna coupling is adjusted by C_8 .

The 144-Mc. Unit

The 144-Mc. circuit is shown in Fig. 19-25. The oscillator is similar to the one used in the 50-Mc. transmitter. The 48-Mc. signal from the oscillator is capacitively coupled to the pentode multiplier which is operated as a frequency tripler. From the tripler, the signal is inductively coupled to the grid of the r.f. amplifier. Since this stage contains a fixed capacitor, it is tuned by "pinching" or "spreading" the turns of L_{\bullet} . As in the 50-Mc. unit, provision is made for measuring grid current (jack J_1).

The amplifier tank circuit in the 144-Mc. model is series tuned. Output coupling is through a single-turn link, L_6 . Neutralization is required in this unit; the neutralizing capacitor consists of a $2\frac{1}{2}$ -inch length of No. 12 wire with one end connected to pin 5 (control grid) of the amplifier tube, and with the other end run up beside the amplifier tube after passing through the chassis (see the photograph in Fig. 19-21). A piece of spaghetti is used to insulate the neutralizing wire from the chassis.

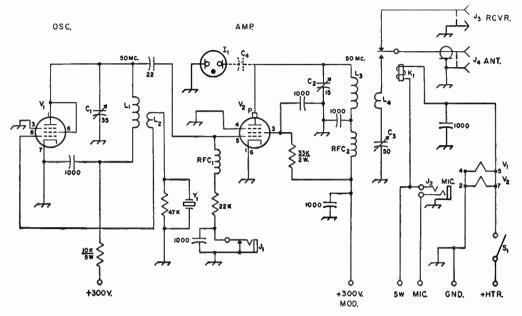


Fig. 19-23—Schematic diagram of the 50-Mc. mobile transmitter. Unless otherwise indicated, capacitances are in $\mu\mu f$., resistances are in ohms, resistors are ½ watt unless specified otherwise.

C₁--35- $\mu\mu$ f, midget variable capacitor (Hammarlund MAPC-35-B).

C₂—15- $\mu\mu$ f, midget variable capacitor (Hammarlund HF-15).

 C_8 —50- $\mu\mu$ f. midget variable capacitor (Hammarlund MAPC-50-B).

C₄—Coupling capacitor for output indicator (see text).
K₁—Midget antenna relay s.p.d.t. (Advance AM/2C/-12VD. Note: the last four figures in the number indicate the coil voltage. For 6 volts d.c. it should read /6VD).

L₁--3. turns No. 20, %-inch dia., % inches long (B & W 3006).

Ls—2 turn link No. 20 insulated wire, close wound over cold end of L₁.

Ls-4 turns No. 16, 1-inch dia., 1-inch long (B & W 3013).

L₄—2 turn link No. 20 insulated wire, close-wound over cold end of L₈.

I-Neon bulb (NE-2).

J1-Circuit-closing jack.

J₈—3-conductor mike jack.

Ja, J4-Automobile type antenna connectors.

RFC₁, RFC₂—Single-layer v.h.f. choke, 2 to 7 μh. (Ohmite Z-50 or National R-60).

\$1-S.p.s.t. slide switch.

V₁-5763 for 6 volts, 6417 for 12 volts.

V2-2E26 for 6 volts, 6893 for 12 volts.

Y₁-50-Mc. 3rd overtone crystal (International Crystal Co. type FA-9).


Construction


A $7 \times 5 \times 3$ -inch Minibox is used as the chassis for the transmitters. A single bracket supports the tubes and associated parts. The bracket has a single bend and is fastened to the Minibox with machine screws.

The 6- and 2-meter transmitters are almost identical mechanically. The only real difference between the two is that the 2-meter model has an additional multiplier tube, mounted in line with the oscillator tube on the bracket.

All parts should be mounted before wiring is begun. Since both ends of the chassis are open, wiring and mounting of parts is a simple job. The photographs show the relative position of

Fig. 19-24—The 144-Mc. transmitter with the r.f. amplifier tube removed to show the neutralizing lead $C_{\rm N}$. Except for the 6BJ6 multiplier tube in the foreground, the same basic layout is used here as in the 50-Mc. unit.

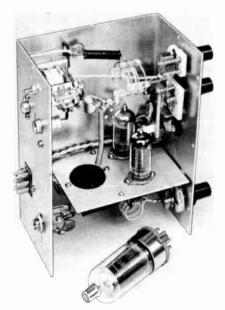

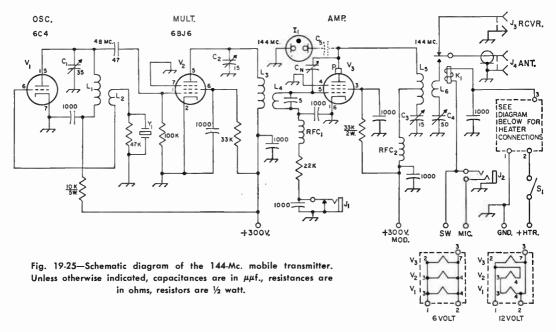

C₁—35-μμf. midget variable capacitor (Hammarlund MAPC-35-B).

C₂, C₃—15-μμf. midget variable capacitor (Hammarlund HF-15).

C₄—50-μμf, midget variable capacitor (Hammarlund MAPC-50-B).

 C_5 —Coupling capacitor for output indicator (see text). C_n —Neutralizing capacitor (see text).

K₁—Midget antenna relay s.p.d.t. (Advance AM/2C/-12VD. Note: the last four figures in the number indicate the coil voltage. For 6 volts it should read 6VD.)

L₁-4 turns No. 20, % inch diam., $\frac{1}{16}$ inches long (B & W 3006).

L₂-2 turn link No. 20 insulated wire, close wound over cold end of L₁.

L₈-2 turns No. 20 insulated wire 1/2-inch diam.

L₄—1 turn No. 20 insulated wire ½-inch diam.

most of the components. Try to keep r.f. leads as short as possible. The relay, antenna connectors, power plug and grid current jack are all mounted on the rear panel.

The output indicator I_1 is coupled to the output circuit through a small capacitor. This capacitor is actually a few turns of hook-up wire wound over a piece of insulated wire that is connected to the final tank circuit. If the lamp fails to ignite, a few more turns may be needed.

Testing Notes

An a.c. power supply delivering 300 volts at 100 ma. can be used during testing of the transmitter. Heater-current requirements for the 50-Mc. unit are 1.55 ampere for 6-volt operation and 0.775 ampere for 12 volts. The 144-Mc. unit requires 1.1 ampere at 6 volts and 0.55 ampere at 12 volts. Do not connect the plate supply to the r.f. amplifier power terminal

L₆—3 turns No. 16, 1-inch diam., ¾ inches long, center tapped (B & W 3013).

 L_6-1 turn link No. 20 insulated wire wound in the center of L_5 .

I₁-Neon bulb (NE·2).

J₁-Circuit closing jack.

J₂—3 conductor mike jack.

 J_3 , J_4 —Automobile type antenna connector.

RFC₁, RFC₂—Single-layer v.h.f. choke, 2 to 7 μh. (Ohmite Z-50 or National R-60).

S₁-S.p.s.t. slide switch.

V1-6C4.

V2-6BJ6.

V₃-2E26 for 6 volts, 6893 for 12 volts.

Y₁—48 Mc. 3rd overtone crystal. Crystal frequency found by dividing desired output frequency by 3 (International Crystal Co. type FA-9).

(marked "300 mod." in the circuit diagram) at this time. The correct crystal and a dummy load should be kept on hand for the test.

To test the driver stage, plug a grid-current meter (0.5 ma.) in J_1 , and apply heater voltage. Plug in the proper crystal and turn on the plate voltage (exciter stages only). As quickly as possible adjust capacitor C_1 until the oscillator goes into oscillation. This will be indicated by a downward kick in the plate current. Grid current should begin to show when oscillation occurs. In the 144-Mc. unit, adjust for maximum grid current by "pinch-tuning" L3, L4 once oscillation has begun. Adjust C_1 for maximum grid current. If there is difficulty in obtaining grid drive, try adjusting the position of L_2 with respect to L₁. In the 2-meter model, some rearrangement of L₈ and L₄ may be needed in order to achieve maximum grid drive.


Before testing the 144-Mc. amplifier it will be

Mobile Modulators

Fig. 19-26—View of the 144-Mc. transmitter. The coil and link near the top left rear are L₁L₂. In the foreground are coils L₃L₄.

necessary to neutralize it. With power applied to the exciter portion, slowly rotate the output tuning control C_3 through its full range. If the amplifier is neutralized, there will be no fluctuation in the grid current. If there is such a fluctuation, adjust the neutralizing wire to a new position with respect to the amplifier tube and swing the plate-tuning control again. Repeat until the grid current remains steady, showing that the amplifier is neutralized.

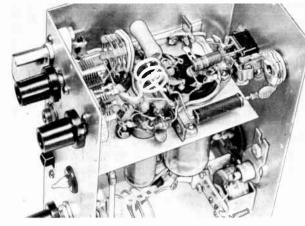Connect a dummy load to the output antenna connector, close the antenna relay and apply plate power to the entire transmitter. As quickly as possible, tune C_3 for minimum plate current. It is necessary to perform this operation rapidly because the amplifier may draw excessive plate current when not tuned to resonance. When tuned to resonance, the output indicator bulb



 I_1 will light. This r.f. indicator is not only a tuning aid in the car but also acts as a continuous monitor to show that the transmitter is in operation. Capacitor C_4 is the loading control and should be adjusted for maximum plate current after the amplifier is resonated.


A microphone jack J_2 is included on the transmitter chassis to simplify the control circuits. Leads from the microphone (marked "sw" and "mic" in the diagram) go to the power connector at the rear of the transmitter.

MOBILE MODULATORS

Vacuum-tube modulators for mobile operation are in general similar to those used in fixedstation installations. Equipment shown in the section on modulators may be modified for use with almost any mobile transmitter. As in fixed

SPEECH AMPLIFIER

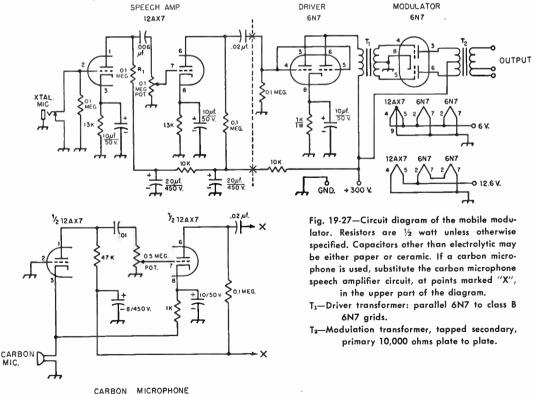station work, the mobile modulator must be capable of supplying to the plate modulated r.f. stage sine-wave audio power equal to 50 per cent of the d.c. plate input for 100 percent modulation.



A 10-WATT MOBILE MODULATOR

Fig. 19-27 shows a modulator that can be used with any mobile a.m. transmitter whose input does not exceed 20 to 25 watts. A resistance-coupled speech amplifier using a single 12AX7 drives a Class A 6N7 which in turn drives a Class B 6N7. The 6N7 uses the two triode sections in parallel, to obtain sufficient driving power.

Also shown in Fig. 19-27 are the changes in the speech-amplifier circuit necessary to adapt it for use with a carbon microphone. D.c. voltage for the carbon microphone is obtained by connecting the microphone in series with the speech-amplifier cathodes.

The modulator requires 300 volts at about 90 ma. for plate power, and 6 volts at 1.9 amperes or 12 volts at .95 amperes for the heaters. Heater connections are given for both voltages.

The plate supply should use a large capacitance (100 μ f. or more) in the output, to serve as a reservoir for the heavy current demands on voice peaks

The main constructional precaution to be observed when building the modulator is that the output transformer T_2 should not be mounted too close to the speech amplifier circuits. Separation will reduce the chance of feedback through stray coupling. A tube shield over the 12AX7 will serve to hold it in the socket over bumpy roads; good octal sockets will normally need no tube clamps to retain the 6N7s.

In any mobile installation, the modulator may be separated from the r.f. assembly by any convenient distance. The cable connecting the modulator to the r.f. section should be made with individually shielded leads.

A 25-WATT TRANSISTOR MODULATOR

The circuit shown in Fig. 19-28 is that of a complete transistor modulator; it is a 12-volt 25-watt Class B modulator. The advantages of a transistor modulator of this type are the compactness (25 watts of audio from a unit readily housed in a $3 \times 4 \times 5$ -inch utility cabinet), high over-all efficiency, no warm-up time and low idling current. Further, by requiring only the 12 volts from the battery, it allows full use of the high-voltage supply by the r.f. section. The modulator will modulate an r.f. stage input of between 45 and 50 watts, at an impedance level of 4000 ohms with the output transformer listed (about 450 volts and 110 ma.). Suitable 12-volt heater tubes for the modulated output stage include the 1625 (similar to 807) and the 6883 (similar to the 6146). The exciter portion of the transmitter can be made up of 6417s (similar to the 5763) or of 12V6-GTs or 12L6-GTs. Maximum economy will be obtained with a transistorized power supply.

For a modulation transformer the unit uses a 6,3-volt filament transformer, T_a . To obtain a true center tap for the driver transformer, a transformer having taps at 4 and 16 ohms is used. Since the impedance varies as the square of the turns ratio, the 4-ohm tap provides a center tap.

It may be found necessary to add an input filter on the 12-volt line to prevent hash from getting into the microphone circuit and adding noise.

Transistor Mounting

Because the collector connection is common with the case of the transistor, mica spacers must be used between the transistor cases and ground. (Insulator package No. 1221264). These can be obtained in a special mounting kit from Delco distributors.

Be careful to apply as little heat as possible when soldering any transistor connections.

Either G.E. 2N190 or RCA 2N109 can be used for the input transistors. Although several other types could be used for the output transistors, the specified 2N278 (Delco DS-501) should be easier to obtain than some since it is sold as a replacement in car-radio service.

It is not likely that a 0.1-ohm 1-watt resistor (see Fig. 19-28) can be purchased at any radio store. A satisfactory substitute is to wind a suitable length of resistance wire over a 2-watt resistor used as a form, or three 0.33-ohm ½-watt resistors can be wired in parallel to obtain a value sufficiently close.

Testing

After wiring and construction of the unit is completed, testing for proper operation can be done in several ways. One method is simply to connect a 4000-ohm 10-watt resistor across the modulation transformer output connections and then place a d.c. animeter in series with the 12-volt line, and watch the current variation while talking into the microphone. The idling current should be around 700 ma., kicking up to above 2 amperes on peaks. Do not, under any circumstances, try to operate the unit without a load of some sort on the output terminals as this may damage the output transistors.

Another method of testing is to place another 6.3-volt filament transformer back-to-back with the modulation transformer, to bring the impedance down to a low level, and then connect a p.m. speaker to the 6.3-volt winding.

A scope test can be made after the unit is connected to the transmitter. The Class C load level can be adjusted for impedance matching.

An F1 carbon microphone is suitable for use with this unit. Although not shown in Fig. 19-28, the unit should be connected so that it is turned on only while the transmit-receive switch is in the transmit position. An inexpensive 12-volt automobile-horn relay (e.g., Echlin HR

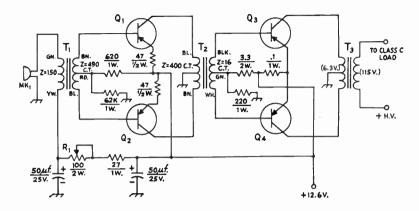


Fig. 19-28—Circuit of the 25-watt transistor modulator. Resistances are in ohms. Capacitors are electrolytic.

MK₁—Single-button carbon microphone.

Q1, Q2-2N190 (GE) or 2N109 (RCA).

Q₃, Q₁-2N278 (Delco DS-501).

R₁-100-ohm 2-watt potentiometer.

T₁—150 ohms c.t. (c.t. not used) to 490 ohms c.t. (Thordarson TR-5).

 T_2 —400 ohms c.t. to 16 ohms, c.t. (see text), Stancor TA-41).

T₃—6.3-volt c.t., 3-amp, filoment transformer used as modulation transformer (see text) (Stancor P-5014).

101), available at most filling stations or automobile parts distributors, should be used to close and open the circuit. The relay arm and contact should be connected in the +12.6-volt lead from the battery and fuse. If excessive sparking is noted at the relay contacts it may be reduced by moving the 50-\(\mu \)f. 25-volt capacitor to the fuse side of the relay contacting circuit.

Concerning placement of the unit in the car: Try to find a location away from high-temperature spots and in a well-ventilated area. The trunk is not recommended since there is little ventilation; this area can become quite hot in the summertime and damage to the transistors could result. The engine compartment makes a

convenient place to mount the unit but this space is not adequately ventilated except possibly while the car is in motion. The most favorable spot is on the fire wall in the passenger compartment, or under the front seat. These areas are usually well ventilated, or at least cooler than any other enclosed section of the car. As in any mobile installation where the modulator is some distance from the r.f. section, good practice demands that the audio leads from the secondary of the modulation transformer to the modulated r.f. stage should be made with individually-shielded leads.


(Original description appeared in QST for November, 1959.)

THE MOBILE ANTENNA

For mobile operation in the range between 1.8 and 30 Mc., the vertical whip antenna is almost universally used. Since longer whips present mechanical difficulties, the length is usually limited to a dimension that will resonate as a quarter-wave antenna in the 10-meter band. The car body serves as the ground connection. This antenna length is approximately 8 feet.

With the whip length adjusted to resonance in the 10-meter band, the impedance at the feed point, X, Fig. 19-29, will appear as a pure resistance at the resonant frequency. This resistance will be composed almost entirely of radiation resistance (see index), and the efficiency will be high. However, at frequencies lower than the resonant frequency, the antenna will show an increasingly large capacitive reactance and a decreasingly small radiation resistance.

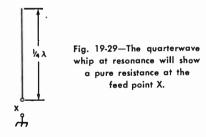The equivalent circuit is shown in Fig. 19-30. For the average 8-ft. whip, the reactance of the



capacitance, C_A , may range from about 150 ohms at 21 Mc. to as high as 8000 ohms at 1.8 Mc., while the radiation resistance, R_B , varies from about 15 ohms at 21 Mc. to as low as 0.1 ohm at 1.8 Mc. Since the resistance is low, considerable current must flow in the circuit if any appreciable power is to be dissipated as radiation in the resistance. Yet it is apparent that little current

can be made to flow in the circuit so long as the comparatively high series reactance remains.



Fig. 19-30—At frequencies below the resonant frequency, the whip antenna will show capacitive reactance as well as resistance. RR is the radiation resistance, and CA represents the capacitive reactance.

Eliminating Reactance

The capacitive reactance can be canceled out by connecting an equivalent inductive reactance, $L_{\rm L}$, in series, as shown in Fig. 19-31, thus tuning the system to resonance.



Fig. 19-31 - The capacitive reactance at frequencies lower than the resonant frequency of the whip can be canceled out by adding an equivalent inductive reactance in the form of a loading coil in series with the antenna.

Unfortunately, all coils have resistance, and this resistance will be added in series, as indicated at Ro in Fig. 19-32. While a large coil may

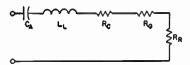


Fig. 19-32—Equivalent circuit of a loaded whip antenna. CA represents the capacitive reactance of the antenna, LL an equivalent inductive reactance. Ro is the loading-coil resistance, RG the ground-loss resistance, and RB the radiation resistance.

radiate some energy, thus adding to the radiation resistance, the latter will usually be negligible compared to the loss resistance introduced. However, adding the coil makes it possible to feed power to the circuit.

Ground Loss

Another element in the circuit dissipating power is the ground-loss resistance. Fundamentally, this is related to the nature of the soil in the area under the antenna. Little information is available on the values of resistance to be expected in practice, but some measurements have shown that it may amount to as much as 10 or 12 ohms at 4 Mc. At the lower frequencies, it may constitute the major resistance in the circuit.

MOBILE EQUIPMENT

Fig. 19-32 shows the circuit including all of the elements mentioned above. Assuming CA lossless and the loss resistance of the coil to be represented by Rc, it is seen that the power output of the transmitter is divided among three resistances— R_c , the coil resistance; R_g , the ground-loss resistance; and $R_{\rm R}$, the radiation resistance. Only the power dissipated in R_R is radiated. The power developed in R_c and R_o is dissipated in heat. Therefore, it is important that the latter two resistances be minimized.

MINIMIZING LOSSES

There is little that can be done about the nature of the soil. However, poor electrical contact between large surfaces of the car body, and especially between the point where the feed line is grounded and the rest of the body, can add materially to the ground-loss resistance. For example, the feed line, which should be grounded as close to the base of the antenna as possible, may be connected to the bumper, while the bumper may have poor contact with the rest of the body because of rust or paint.

Loading Coils

The accompanying tables show the approximate loading-coil inductance required for the

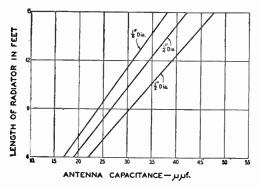


Fig. 19-33-Graph showing the approximate capacitance of short vertical antennas for various diameters and lengths, at 3.9 Mc. These values should be approximately halved for a center-loaded antenna.

various bands. The graph of Fig. 19-33 shows the approximate capacitance of whip antennas of various average diameters and lengths. For 1.8. 4 and 7 Mc., the loading-coil inductance required (when the loading coil is at the base) will be approximately the inductance required to resonate in the desired band with the whip capacitance taken from the graph. For 14 and 21 Mc., this rough calculation will give more than the required inductance, but it will serve as a starting point for final experimental adjustment that must always be made.

Also shown in table 19-I are approximate values of radiation resistance to be expected with an 8-ft, whip, and the resistances of loading coils — one group having a Q of 50, the other a Q of 300. A comparison of radiation and coil

TABLE 19-I

	Approximate Values for 8-ft. Mobile Whip							
	Base Loading							
fkc.	Loading Lµh.	R _C (Q50) Ohms	R _C (Q300) Ohms	R _R Ohms	Feed R* Ohms	Matching Lµh *		
1800	345	77	13	0.1	23	3		
3800	77	37	6.1	0.35	16	1.2		
7200	20	18	3	1.35	15	0.6		
14,200	4.5	7.7	1.3	5.7	12	0.28		
21,250	1.25	3.4	0.5	14.8	16	0.28		
29,000	••••	••••			36	0.23		
	Center Loading							
1800	700	158	23	0.2	34	3.7		
3800	150	72	12	0.8	22	1.4		
7200	40	36	6	3	19	0.7		
14,200	8.6	15	2.5	11	19	0.35		
21,250	2.5	6.6	1.1	27	29	0.29		

Rc = Loading-coil resistance; RR = Radiation resistance.

* Assuming loading coil Q=300, and including estimated ground-loss resistance.

Suggested coil dimensions for the required loading inductances are shown in a following table.

resistances will show the importance of reducing the coil resistance to a minimum, especially on the three lower-frequency bands.

To minimize loading-coil loss, the coil should have a high ratio of reactance to resistance, i.e., high Q. A 4-Mc. loading coil wound with small wire on a small-diameter solid form of poor quality, and enclosed in a metal protector, may have a Q as low as 50, with a resistance of 50 ohms or more. High-Q coils require a large conductor, "air-wound" construction, turns spaced, the best insulating material available, a diameter not less than half the length of the coil (not always mechanically feasible), and a minimum of metal in the field. Such a coil for 4 Mc. may show a Q of 300 or more, with a resistance of 12 ohms or less. This reduction in loading-coil resistance may be equivalent to increasing the transmitter power by 3 times or more. Most low-loss transmitter plug-in coils of the 100watt size or larger, commercially produced, show a Q of this order. Where larger inductance values are required, lengths of low-loss spacewound coils are available.

Center Loading

The radiation resistance of the whip can be approximately doubled by placing the loading coil at the center of the whip, rather than at the base, as shown in Fig. 19-34. (The optimum position varies with ground resistance. The center is optimum for average ground resist-

ance.) However, the inductance of the loading coil must be approximately doubled over the value required at the base to tune the system to resonance. For a coil of the same Q, the coil resistance will also be doubled. But, even if this

TABLE 19-II

S	Suggested Loading-Coil Dimensions						
Req'd	Turns	Wire	Diam.	Length	Form or		
Lμh.		Size	In.	In.	B & W Type		
700	190	22	3	10	Polystyrene		
345	135	18	3	10	Polystyrene		
150	100	16	21/2	10	Polystyrene		
77	75	14	2½	10	Polystyrene		
77	29	12	5	4¾	160T		
40	28	16	2½	2	80B less 7 t.		
40	34	12	2½	4¾	80T		
20	17	16	2½	1¾	80B less 18 t.		
20	22	12	2½	2¾	80T less 12 t.		
8.6	16	14	2	2 3	40B less 4 t.		
8.6	15	12	2½		40T less 5 t.		
4.5	10	14	2	1¼	40B less 10 t.		
4.5	12	12	2½	4	40T		
2.5	8	12	2	2	15 B		
2.5		6	2 3/8	4½	15 T		
1.25	6	12	1 3/4	2	10B		
1.25	6	6	2 3/8	43/2	10T		


 


Fig. 19-34—Placing the loading coil at the center of the whip antenna, instead of at the base, increases the radiation resistance, although a larger coil must be used.

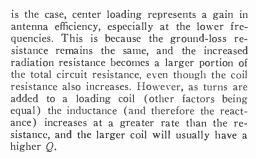

Top Loading Capacitance

Since the coil resistance varies with the inductance of the loading coil, the coil resistance can be reduced by reducing the number of turns. This can be done, while still maintaining resonance, by adding capacitance to the portion of the antenna above the coil. This capacitance can be provided by attaching a capacitive surface as high up on the antenna as is mechanically feasible. Capacitive "hats," as they are usually called, may consist of a light-weight metal ball,

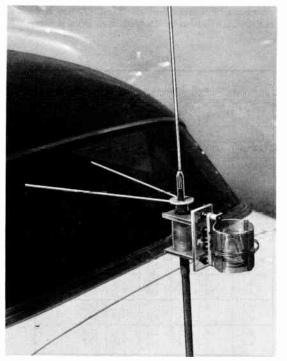




Fig. 19-35—The top-loaded 4-Mc, antenna designed by W6SCX. The loading coil is a B & W transmitting coil. The coil can be tuned by the variable link which is connected in series with the two halves of the coil.

cylinder, disk, or wheel structure as shown in Fig. 19-35. This should be added to the capacitance of the whip above the loading coil (from Fig. 19-33) in determining the approximate inductance of the loading coil.

When center loading is used, the amount of capacitance to be added to permit the use of the same loading inductance required for base loading is not great, and should be seriously considered, since the total gain made by moving the coil to the center of the antenna may be quite marked.

Tuning the Band

Especially at the lower frequencies, where the resistance in the circuit is low compared to the coil reactance, the antenna will represent a very high-Q circuit, making it necessary to retune for relatively small changes in frequency. While many methods have been devised for tuning the whip over a band, one of the simplest is shown in Fig. 19-36. In this case, a standard B & W plug-in coil is used as the loading coil. A length of large-diameter polystyrene rod is drilled and tapped to fit between the upper and lower sections of the antenna. The assembly also serves to clamp a pair of metal brackets on each side

Fg. 19-36—W8AUN's adjustable capacity hat for tuning the whip antenna over a band. The coil is a B & W type B 160-meter coil, with a turn or two removed. Spreading the rods apart increases the capacitance. This simple top loader has sufficient capacitance to permit the use of approximately the same loading-coil inductance at the center of the antenna as would normally be required for base loading.

of the polystyrene block that serve both as support and connections to the loading-coil jack bar.

A 1/6-inch steel rod, about 15 inches long, is brazed to each of two large-diameter washers with holes to pass the threaded end of the upper section. The rods form a loading capacitance that varies as the upper rod is swung away from the lower one, the latter being stationary. Enough variation in tuning can be obtained to cover the 80-meter band. (Original description appeared in QST, September, 1953.)

REMOTE ANTENNA RESONATING

Fig. 19-37 shows circuits of two remote-control resonating systems for mobile antennas. As shown, they make use of surplus d.c. motors driving a loading coil removed from a surplus ARC-5 transmitter. A standard coil and motor may be used in either installation at increased expense.

The control circuit shown in Fig. 19-37A is a three-wire system (the car frame is the fourth conductor) with a double-pole double-throw switch and a momentary (normally off) single-pole single-throw switch. S_2 is the motor reversing switch. The motor runs so long as S_1 is closed.

The circuit shown in Fig. 19-37B uses a latching relay, in conjunction with microswitches, to automatically reverse the motor when the roller reaches the end of the coil. S_3 and S_6 operate

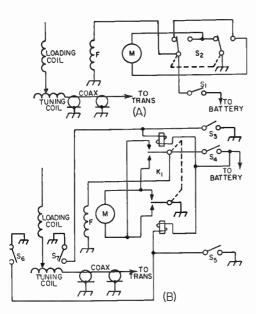


Fig. 19-37—Circuit of the remote mobile-whip tuning systems.

K₁-D.p.d.t. latching relay.

S₁, S₃, S₄, S₈—Momentary-contact s.p.s.t., normally open.

S2-D.p.d.t. toggle.

So, S₇—S.p.s.t, momentary-contact microswitch, normally open.

the relay, K_1 , which reverses the motor. S_4 is the motor on-off switch. When the tuning coil roller reaches one end or the other of the coil, it closes S_0 or S_7 , as the case may be, operating the relay and reversing the motor.

The procedure in setting up the system is to prune the center loading coil to resonate the antenna on the highest frequency used without the base loading coil. Then, the base loading coil is used to resonate at the lower frequencies. When the circuit shown in Fig. 19-37A is used for control, S_1 is used to start and stop the motor, and S_2 , set at the "up" or "down" position, will determine whether the resonant frequency is raised or lowered. In the circuit shown in Fig. 19-37B, S_4 is used to control the motor. S_2 or S_3 is momentarily closed (to activate the latching relay) for raising or lowering the resonant frequency. The broadcast antenna is used with a wavemeter to indicate resonance.

(Originally described in QST, Dec., 1953.)

Several companies offer motor tuning for getting optimum performance over a low-frequency band. (For a complete description of the commercially available remotely-tuned systems, see Goodman, "Frequency Changing and Mobile Antennas," *QST*, Dec., 1957.)

Automatic Mobile Antenna Tuning

A somewhat more complex antenna tuning system for 75 and 40 meters is one that automatically tunes the antenna as the transmitter frequency is shifted. After initial adjustments, the radiator is kept in resonance without attention from the operator. (For a description of the automatic system, see Hargrave, "Automatic Mobile Antenna Tuning, QST, May, 1955.)

FEEDING THE ANTENNA

It is usually found most convenient to feed the whip antenna with coax line. Unless very low-Q loading coils are used, the feed-point impedance will always be appreciably lower than 52 ohms — the characteristic impedance of the commonly-used coax line, RG-8/U or RG-58/U. Since the length of the transmission line will seldom exceed 10 ft., the losses involved will be negligible, even at 29 Mc., with a fairly-high s.w.r. However, unless a line of this length is made reasonably flat, difficulty may be encountered in obtaining sufficient coupling with a link to load the transmitter output stage.

One method of obtaining a match is shown in Fig. 19-38. A small inductance, $L_{\rm M}$, is inserted at the base of the antenna, the loading-coil inductance being reduced correspondingly to maintain resonance. The line is then tapped on the coil at a point where the desired loading is obtained. Table 19-I shows the approximate inductance to be used between the line tap and ground. It is advisable to make the experimental matching coil larger than the value shown, so that there will be provision for varying either side of the proper position. The matching coil can also be of the plug-in type for changing bands.

Fig. 19-38 — A method of matching the loaded whip to 52-ohm coax cable. $L_{\rm L}$ is the loading coil and $L_{\rm M}$ the matching coil.



Adjustment

For operation in the bands from 29 to 1.8 Mc., the whip should first be resonated at 29 Mc. with the matching coil inserted, but the line disconnected, using a grid-dip oscillator coupled to the matching coil. Then the line should be attached, and the tap varied to give proper loading, using a link at the transmitter end of the line whose reactance is approximately 52 ohms at the operating frequency, tightly coupled to the output tank circuit. After the proper position for the tap has been found, it may be necessary to readjust the antenna length slightly for resonance. This can be checked on a field-strength meter several feet away from the car.

The same procedure should be followed for each of the other bands, first resonating, with the g.d.o. coupled to the matching coil, by adjusting the loading coil.

After the position of the matching tap has been found, the size of the matching coil can be reduced to only that portion between the tap and ground, if desired. If turns are removed here, it will be necessary to reresonate with the loading coil.

If an entirely flat line is desired, a s.w.r. indicator should be used while adjusting the line tap. With a good match, it should not be necessary to readjust for resonance after the line tap has been set.


It should be emphasized that the figures shown in the table are only approximate and may be altered considerably depending on the type of car on which the antenna is mounted and the spot at which the antenna is placed.

ANTENNAS FOR 50 AND 144 MC.

A Simple Vertical Antenna

The most convenient type of antenna for mobile v.h.f. work is the quarter-wave vertical radiator, fed with 50-ohm coaxial line. The antenna, which may be a flexible telescoping "fish pole," can be mounted in any of several places on the car. An ideal mounting spot is on top of the car, though rear-deck mounting presents a better spot for esthetic reasons. Tests have shown that with the car in motion there is no observable difference in average performance of the antennas, regardless of their mounting positions. There may be more in the way of directional effects with the rear-deck mount, but the over-all advantage of the roof mount is slight.

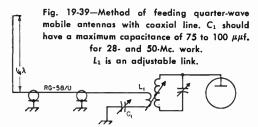A good match may be obtained by feeding the simple vertical with 50-ohm line. However, it is well to provide some means for tuning the system, so that all variables can be taken care of. The simplest tuning arrangement consists of a variable capacitor connected between the low side of the transmitter coupling coil and ground, as shown in Fig. 19-39. This capacitor should



have a maximum capacitance of 75 to $100 \mu\mu f$. for 50 Mc., and should be adjusted for maximum loading with the least coupling to the transmitter. Some method of varying the coupling to the transmitter should be provided.

Horizontal Polarization

Horizontally polarized antennas have a considerable advantage over the vertical whip under usual conditions of mobile operation. This is particularly true when horizontal polarization is used at both ends of a line-of-sight circuit, or on a longer circuit over reasonably flat terrain. An additional advantage, especially on 6 meters, is a marked reduction in ignition noise from neighboring cars as well as from the station car.

A Horizontally Polarized Two-Band Antenna for V.H.F.

One type of horizontally-polarized antenna, called the "halo," is shown in Fig. 19-40. It is a dipole bent into a circle, with the ends capacitively loaded to reduce the circumference. Since the 50- and 144-Mc. bands are almost in third harmonic relationship, it is possible to build a single halo that will work on both bands. The antenna is changed from one band to another by changing the spacing between the end loading plates and adjusting the matching mechanism.

Mechanical Details

The halo is made of $\frac{7}{16}$ -inch aluminum fuelline tubing. This material is both strong and very light, but any tubing of about $\frac{7}{2}$ -inch diameter could be used equally well. The loop is 67 inches in circumference and the capacitor plates are $\frac{21}{4}$ inches square, with the corners rounded off.

To fasten the capacitor plates to the ends of the tubing, aluminum rod stock is turned down on a lathe to make a tight fit into the ends. This is tapped for 6-32 thread, and then forced into the tubing ends. Holes are drilled through tubing and inserts, at each end of the halo, and a screw run through each to keep the inserts from turning around or slipping out. The binding-

head screws that hold the plates to the inserts are equipped with lock washers. The holes for mounting the ceramic cone spacer are drilled directly below the center, midway between the center and the edge of the capacitor plates.

The halo is set into a slot cut in the vertical support. This slot should be just big enough to permit the halo to be forced into it. The halo has to be stiffened, so cut it at the center and insert about 2 inches of aluminum rod, again turned down on a lathe to fit tightly inside the tubing. The two pieces of tubing are then pushed together, over the insert, and drilled each side of center to pass 6–32 screws. The halo and insert are also drilled at the midpoint, to pass the mounting screw. This is an 8–32 screw, 1½ inches long. If lathe facilities are not available, the mounting of the capacitor plates and the securing of the halo to the vertical support can be handled with angle brackets.

Mechanical stability is important so straps of aluminum ½ inch wide are wrapped around the halo either side of the mounting post. These are bent at right angles and the ends pulled together with a bolt.

The matching arm is 141/2 inches long, of the same material as the halo itself. It is mounted below the halo on two 3/4-inch cone standoffs. For convenience in detaching the feed line a coaxial fitting is mounted on an L bracket bolted to the vertical support. The stator bar of the $25-\mu\mu$ f. variable capacitor (Johnson 167-2) is soldered directly to the coaxial fitting. The rotor of the capacitor is connected to the gamma arm through a piece of stiff wire. For further stiffening an aluminum angle bracket is screwed to the lower mounting stud of the capacitor and the other end mounted under the screw that holds the first cone standoff in place. Contact between the arm and the halo proper is made through a strap of 1/2-inch wide aluminum bent to form a sliding clip. Be sure that a clean tight contact is made between the tubing and the clip, as high current flows at this point. A poor or varying contact will ruin the effectiveness of the antenna.

Adjustment

The capacity-loaded halo is a high-Q device so

it must be tuned on-the-nose, or it will not work properly. The only reliable method for adjusting a halo is to use a standing-wave bridge, making tuning and matching adjustments for minimum reflected power. Using a field-strength meter and attempting to adjust for maximum radiated power can give confusing indications, and is almost certain to result in something less than maximum effectiveness.


The adjustment process with this design can be simplified if the halo is first resonated approximately to the desired frequency ranges with the aid of a grid-dip meter. Set the clip at about one inch in from the end of the arm, and the series capacitor at the middle of its range. Check the resonant frequency of the loop with the grid-dip meter, with the ¾-inch spacer between the capacitor plates. It should be close to 50 Mc. If the frequency is too low, trimming the corners of the plates or putting shims under the ceramic spacer will raise it somewhat. If the frequency is too high already, make new and slightly larger capacitor plates.

Next, insert an s.w.r. bridge between the antenna and the transmission line. Apply power and swing the capacitor through its range, noting whether there is a dip in reflected power at any point. If the reflected power will not drop to zero, slide the clip along the gamma arm and retune the capacitor, until the lowest reading possible is obtained. If this is still not zero, the halo is not resonant. If the halo capacitance is on the low side, moving the hands near the plates will cause the reflected power to drop. Closer spacing of the plates, larger plates or a longer halo loop are possible solutions.

These adjustments should be made on a frequency near the middle of the range you expect to use. Adjusting for optimum at 50.25 Mc., for example, will result in usable operation over the first 500 kc. of the band, and a good match (below 1.5 to 1) from 50.1 to 50.4. The s.w.r. will rise rapidly either side of this range.

To tune up on 144 Mc., insert the ½-inch cone between the capacitor plates. Slide the clip back on the gamma arm about 3 to 4 inches and repeat the adjustment for minimum reflected power, using a frequency at the middle of a 2-Mc. range.

Fig. 19-40—The 2-band halo as it appears when set up for 50-Mc. operation. Changing to 144 Mc. involves decreasing the plate spacing by swapping cone insulators, and resetting the gamma matching clip and series capacitor.

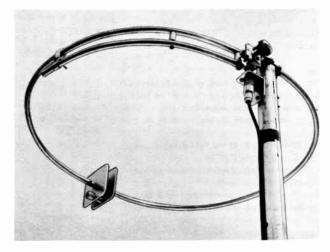

Tuning up at 145 Mc., for example, will give quite satisfactory operation from the low end to 146 Mc., the halo being much broader in frequency response when it is operated on its third harmonic. In this model the series capacitor in the gamma arm was at about the middle of its range for 50 Mc., and near minimum for 144 Mc. Slight differences in mechanical construction may change the value of capacitance required, so these settings should not be taken as important.

The photograph, Fig. 19-40, shows a method used to avoid running the chance that the second ceramic cone would be missing when a band change was to be made. The head was cut from a 6-32 screw, leaving a threaded stud about 1/2 inch long. This is screwed into one of the ceramic cones. The other cone then serves as a nut, to tighten down the capacitor plate. In changing bands merely swap cones. (Original description appeared in QST, Sept., 1958.)

Commercial versions of the one- and two-band halo antennas are available.

Bibliography

Swafford, "Improved Coax Feed for Low-Frequency Mobile Antennas," QST, December, 1951.
Roberge McConnell, "Let's Go High Hat!," QST, Janu-

ary, 1952

Belrose, "Short Antennas for Mobile Operation," QST, September, 1953,

Dinsmore, "The 'Hot-Rod' Mobile Antenna," QST, September, 1953.

tember, 1953.

Picken & Wambsganss, "Remote Mobile-Antenna Resonating," QST, December, 1953.

Webster, "Mobile Loop Antennas," QST, June, 1954.

Tilton, "Have you Tried V.H.F. Mobile?" QST, September 1954. tember, 1954.

Hargrave, "Automatic Mobile Antenna Tuning," QST, May, 1955.

Morgan, "Tuning the Mobile Antenna from the Driver's Seat," QST, October, 1955, Braschwitz, "Directional Antenna for the Transmitter Hunter," QST, April, 1956.

Tilton, "Polarization Effects in V.H.F. Mobile," QST, December, 1956

Breetz, "A Simple Halo for 2-Meter Mobile Use," QST, August, 1957.

Harris, "Continuously Loaded Whip Antennas," OST. May, 1958.

Mellen and Milner, "Big Wheel on Two," QST, Sept., 1961. Also "Big Wheel Performance Tests," QST, Oct., 1961.

A FIELD-STRENGTH METER FOR PORTABLE-MOBILE USE

The field-strength meter of Figs. 19-41 through 19-43 can be used in a mobile station as an antenna-resonance indicator or as a continuous output indicator showing that the transmitting system is actually radiating. It is designed to be inserted between the automobile broadcast receiving antenna, which acts as the r.f. pick-up, and the broadcast receiver. Small magnets or



Fig. 19-41-A front view of the field-strength meter. Sensitivity control R₁ is to the right of the 0-1 indicating meter. Antenna input and ouput connectors are mounted on the right end of the box.

Fig. 19-42—Circuit of the field-strength meter. CR1-Crystal diode (1N34A).

 J_{1} , J_2 —Automobile type antenna connectors. RFC₁-2.5 mh, r.f. choke.

R₁-500 ohm potentiometer (Mallory U-2).

S1-S.p.d.t. switch for above potentiometer.


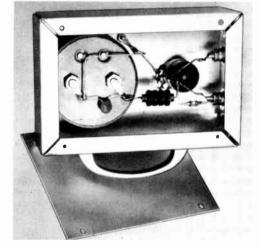


Fig. 19-43—Inside view of the meter. The back plate shown in the photograph is used as a cover for the box.

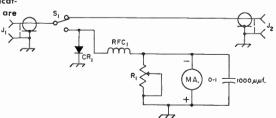rubber suction cups on the back plate will hold the meter securely on top of the car dash, Although in this position the meter will be face up in most cases, it can nevertheless usually be read from the driver position.



A handle can be mounted on the meter box so that the meter can easily be carried about for portable measurements. The same basic layout less the handle can be used if the box is to be mounted under the dash or in the glove compartment.

The circuit for the field-strength meter is shown in Fig. 19-42. The values shown are not critical. Nearly any type of crystal detector can be used and the meter movement can be anything from $100~\mu a$. to 2 ma. or more, depending upon the size and placement of the antenna and the power output of the transmitter. All components, including the 3-inch indicating meter, are housed in a $2~\times~6~\times~4$ -inch aluminum

chassis. If a smaller meter-is used, the box could be reduced in size accordingly. However, in mobile operation a large meter is more convenient to read while in motion. An illuminated meter could be substituted for the one shown in the photograph for use at night. A switch, S_1 , is used in the circuit to switch the antenna to the field-strength meter position or straight through to the broadcast set. For portable or temporary mobile operation, a short pick-up wire can be used instead of the automobile receiving antenna. The pick-up antenna lead comes into a connector mounted on one end of the box. There is a second connector for attaching the lead to the broadcast receiver.

CONELRAD MONITORING

The conelrad rules discussed in the chapters on high-frequency receivers and operating a station must be observed by amateurs who operate mobile. One convenient form of compliance is by means of a separate tunable converter covering the broadcast band, and converting to the same i.f. as the i.f. used by the ham-band converter. This type of converter may also be used when the car radio is used as the tunable i.f. for a broad-band converter, providing that the receiver is tuned to the converter i.f. at tenminute intervals. This can be accomplished most conveniently by setting one of the push buttons to tune the receiver to the monitor output frequency.

The circuit of a broadcast-band converter is shown in Fig. 19-44. The input circuit $C_{1A}L_2$ covers the broadcast band. The oscillator circuit $C_{1B}L_3$ tunes the range of 2050 to 3000 kc. to produce an i.f. of 1500 kc. A type 6SA7 may be used in the circuit and, of course, either a 12BE6 or a 12SA7 should be used for 12-volt operation.

Plates must be removed from C_{1B} to provide the required tuning range. The oscillator section of the dual unit is the one having the smaller number of plates. Starting at the rear, all rotor plates except five should be removed. It isn't necessary to remove the unused stators. Be very careful to make sure that there are no shorted plates after the modification is complete.

 L_2 is a ferrite-core loopstick. This coil usually comes with a length of wire attached to the ungrounded end and wound around the loopstick. When unwound, the short length of wire is intended to provide additional pickup if needed. Disconnect this wire from L_2 and, without unwinding it, use it for L_1 .

 L_3 is close-wound with 60 turns No. 30 enameled, and either tapped at about one third of the way up from the ground end, or with a separate cathode coil consisting of about one third the number of turns on L_3 , wound over the ground end of L_3 , and wound in the same direction. The bottom end of this winding should be grounded.

Power for the converter may be taken from the car radio supply since the current requirement is negligible. With 150 volts at the positive B terminal of the converter, the converter draws approximately 4 ma. and the drop across R_2 : is about 100 volts. The converter will work well at supply voltages up to 350 or more without change in the resistance value of R_2 . The current drain will, of course, be higher at the higher supply voltages, and the wattage rating of the resistor may have to be increased. If current drain is an important consideration, the resistance value of R_2 can be increased in proportion to the increase in supply voltage.

ANT. 1500-550 kc. 7 1500 kc. 1

Fig. 19-44—Circuit of the conelrad converter for mobile use.

C₁—Dual variable capacitor, broadcastreplacement type for superhet receivers, C_{1B} altered as described in the text (approx. 90 μμf.).

 C_2 -47- $\mu\mu$ f. mica.

C₃-0,1-\(mu f\), 400-volt paper.

 C_4 —180- $\mu\mu$ f. mica trimmer (Arco type 463). L_1 —See text.

 L_2 —BC ferrite core loopstick (approx. 230 μ h.).

 L_3 —See text (approx. 65 μ h.).

L₄—National XR-50 iron-slug form wound full with No. 32 enam. wire (approx. 85 μh.).

L₅--15 turns No. 28 wound over cold end of L₄.

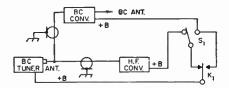


Fig. 19-45—Block diagram showing a switching system for the conelrad converter. K_1 represents a spare set of contacts on the change-over relay. S_1 is a s.p.d.t. toggle. With K_1 in the receiving position as shown, power from the broadcast receiver may be applied to either the b.c. converter or the ham-band converter. With K_1 in the transmitting position, power is applied to the broadcast converter for conelrad monitoring during transmitting periods.

The oscillator can be checked for proper frequency range by the use of a grid-dip meter before power is applied or, after power has been turned on, by listening on a communications receiver covering the 2-to-3 Mc. range.

Now connect an antenna to the input of the converter and connect the converter to the broadcast receiver. Set the broadcast receiver at 1500 kc. (or to the frequency normally used with the ham-band converter). Turn on the power and adjust C_4 and the slug of L_4 for a peak in noise (if you can't find a signal). Then adjust the slug of L_2 for maximum response.

Fig. 19-45 shows how the converter can be connected into a convenient switch system. (Originally described in *QST*, June, 1957).

MOBILE POWER SUPPLY

By far the majority of amateur mobile installations depend upon the car storage battery as the source of power. The tube types used in equipment are chosen so that the filaments or heaters may be operated directly from the battery. High voltage may be obtained from a supply of the vibrator-transformer-rectifier type, a small motor generator or a transistor-transformer-rectifier system operating from the car battery.

Filaments

Because tubes with directly heated cathodes (filament-type tubes) have the advantage that they can be turned off during receiving periods and thereby reduce the average load on the battery, they are preferred by some for transmitter applications. However, the choice of types with direct heating is limited and the saving may not always be as great as anticipated, because directly heated tubes may require greater filament power than those of equivalent rating with indirectly heated cathodes. In most cases, the power required for transmitter filaments will be quite small compared to the total power consumed.

Plate Power

Under steady running conditions, the vibrator-transformer-rectifier system and the motor-generator-type plate supply operate with approximately the same efficiency. However, for the same power, the motor-generator's over-all efficiency may be somewhat lower because it draws a heavier starting current. On the other hand, the output of the generator requires less filtering and sometimes trouble is experienced in eliminating interference from the vibrator.

Transistor-transformer-rectifier plate supplies currently available operate with an efficiency of approximately 80 per cent. These compact, lightweight supplies use no moving parts (vibrator or armature) or vacuum tubes, and draw no starting surge current. Most transistorized supplies are designed to operate at 12 volts d.c. and some units deliver 125 watts or more.

Converter units, both in the vibrator and rotating types, are also available. These operate at 6 or 12 volts d.c. and deliver 115 volts a.c. This permits operating standard a.c.-powered equipment in the car. Although these systems have the advantage of flexibility, they are less efficient than the previously mentioned systems because of the additional losses introduced by the transformers used in the equipment.

Mobile Power Considerations

Since the car storage battery is a low-voltage source, this means that the current drawn from the battery for even a moderate amount of power will be large. Therefore, it is important that the resistance of the battery circuit be held to a minimum by the use of heavy conductors and good solid connections. A heavyduty relay should be used in the line between the battery and the plate-power unit. An ordinary toggle switch, located in any convenient position. may then be used for the power control. A second relay may sometimes be advisable for switching the filaments. If the power unit must be located at some distance from the battery (in the trunk, for instance) the 6- or 12-volt cable should be of the heavy military type.

A complete mobile installation may draw 30 to 40 amperes or more from the 6-volt battery or better than 20 amperes from a 12-volt battery. This requires a considerably increased demand from the car's battery-charging generator. The voltage-regulator systems on cars of recent years will take care of a moderate increase in demand if the car is driven fair distances regularly at a speed great enough to insure maximum charging rate. However, if much of the driving is in urban areas at slow speed, or at night, it may be necessary to modify the charging system. Special communications-type generators, such as those used in police-car installations, are designed to charge at a high rate at slow engine speeds. The charging rate of the standard system can be increased within limits by tightening up

Mobile Power Supply

slightly on the voltage-regulator and currentregulator springs. This should be done with caution, however, checking for excessive generator temperature or abnormal sparking at the commutator. The average 6-volt car generator has a rating of 35 amperes, but it may be possible to adjust the regulator so that the generator will at least hold even with the transmitter, receiver, lights, etc., all operating at the same time.

If higher transmitter power is used, it may be necessary to install an a.c. charging system. In this system, the generator delivers a.c. and works into a rectifier. A charging rate of 75 amperes is easily obtained. Commutator trouble often experienced with d.c. generators at high

current is avoided, but the cost of such a system is rather high.

Some mobile operators prefer to use a separate battery for the radio equipment. Such a system can be arranged with a switch that cuts the auxiliary battery in parallel with the car battery for charging at times when the car battery is lightly loaded. The auxiliary battery can also be charged at home when not in use.

A tip: many mobile operators make a habit of carrying a pair of heavy cables five or six feet long, fitted with clips to make a connection to the battery of another car in case the operator's battery has been allowed to run too far down for starting.

THE AUTOMOBILE STORAGE BATTERY

The success of any mobile installation depends to a large extent upon intelligent use and maintenance of the car's battery.

The storage battery is made up of units consisting of a pair of coated lead plates immersed in a solution of sulphuric acid and water. Cells, each of which delivers about 2 volts, can be connected in series to obtain the desired battery voltage. A 6-volt battery therefore has three cells, and a 12-volt battery has 6 cells. The average stock car battery has a rated capacity of 600 to 800 watt-hours, regardless of whether it is a 6-volt or 12-volt battery.

Specific Gravity and the Hydrometer

As power is drawn from the battery, the acid content of the electrolyte is reduced. The acid content is restored to the electrolyte (meaning that the battery is recharged) by passing a current through the battery in a direction opposite to the direction of the discharge current.

Since the acid content of the electrolyte varies with the charge and discharge of the battery, it is possible to determine the state of charge by measuring the *specific gravity* of the electrolyte.

An inexpensive device for checking the s.g. is the hydrometer which can be obtained at any automobile supply store. In checking the s.g., enough electrolyte is drawn out of the cell and into the hydrometer so that the calibrated bulb floats freely without leaning against the wall of the glass tube.

While the readings will vary slightly with batteries of different manufacture, a reading of 1.275 should indicate full charge or nearly full charge, while a reading below 1.150 should indicate a battery that is close to the discharge point. More specific values can be obtained from the car or battery dealer.

Readings taken immediately after adding water, or shortly after a heavy discharge period will not be reliable, because the electrolyte will not be uniform throughout the cell. Charging will speed up the equalizing, and some mixing can be done by using the hydrometer to withdraw and return some of the electrolyte to the cell several times.

A battery should not be left in a discharged condition for any appreciable length of time. This is especially important in low temperatures when there is danger of the electrolyte freezing and ruining the battery. A battery discharged to an s.g. of 1.100 will start to freeze at about 20 degrees F., at about 5 degrees when the s.g. is 1.150 and at 16 below when the s.g. is 1.200.

If a battery has been run down to the point where it is nearly discharged, it can usually be fast-charged at a battery station. Fast-charging rates may be as high as 80 to 100 amperes for a 6-volt battery. Any 6-volt battery that will accept a charge of 75 amperes at 7.75 volts during the first 3 minutes of charging, or any 12-volt battery that will accept a charge of 40 to 45 amperes at 15.5 volts, may be safely fast-charged up to the point where the gassing becomes so excessive that electrolyte is lost or the temperature rises above 125 degrees.

A normal battery showing an s.g. of 1.150 or less may be fast-charged for 1 hour. One showing an s.g. of 1.150 to 1.175 may be fast-charged for 45 minutes. If the s.g. is 1.175 to 1.200, fast-charging should be limited to 30 minutes.

Care of the Battery

The battery terminals and mounting frame should be kept free from corrosion. Any corrosive accumulation may be removed by the use of water to which some household ammonia or baking soda has been added, and a stiff-bristle brush. Care should be taken to prevent any of the corrosive material from falling into the cells. Cell caps should be rinsed out in the same solution to keep the vent holes free from obstructing dirt. Battery terminals and their cable clamps should be polished bright with a wire brush, and coated with mineral grease.

The hold-down clamps and the battery holder should be checked occasionally to make sure that they are tight so the battery will not be damaged by pounding when the car is in motion.

Voltage Checks

Although the readings of s.g. are quite reliable as a measure of the state of charge of a normal

battery, the necessity for frequent use of the hydrometer is an inconvenience and will not always serve as a conclusive check on a defective battery. Cells may show normal or almost normal s.g. and yet have high internal resistance that ruins the usefulness of the battery under load.

When all cells show satisfactory s.g. readings and yet the battery output is low, service stations check each cell by an instrument that measures the voltage of each cell under a heavy load. Under a heavy load the cell voltages should not differ by more than 0.15 volt.

A load-voltage test can also be made by measuring the voltage of each cell while closing the starter switch with the ignition turned off. In many cars it is necessary to pull the central dis-

tributor wire out to prevent the motor starting.

Electrolyte Level

Water is evaporated from the electrolyte, but the acid is not. Therefore water must be added to each cell from time to time so that the plates are always completely covered. The level should be checked at least once per week, especially during hot weather and constant operation.

Distilled water is preferred for replenishing, but clear drinking water is an acceptable substitute. Too much water should not be added, since the gassing that accompanies charging may force electrolyte out through the vent holes in the caps of the cells. The electrolyte expands with temperature. (From *QST*, August, 1955.)

EMERGENCY AND INDEPENDENT POWER SOURCES

Emergency power supply which operates independently of a.c. lines is available, or can be built in a number of different forms, depending upon the requirements of the service for which it is intended.

The most practical supply for the average individual amateur is one that operates from a car storage battery. Such a supply may take the form of a small motor generator (often called a dynamotor), a rotary converter, a vibrator-transformer-rectifier combination, or transistor supply.

Dynamotors

A dynamotor differs from a motor generator in that it is a single unit having a double armature winding. One winding serves for the driving motor, while the output voltage is taken from the other. Dynamotors usually are operated from 6-, 12-, 28- or 32-volt storage batteries and deliver from 300 to 1000 volts or more at various current ratings.

Successful operation of dynamotors requires heavy direct leads, mechanical isolation to reduce vibration, and thorough r.f. and ripple filtration. The shafts and bearings should be thoroughly "run in" before regular operation is attempted, and thereafter the tension of the bearings should be checked occasionally to make certain that no looseness has developed.

In mounting the dynamotor, the support should be in the form of rubber mounting blocks, or equivalent, to prevent the transmission of vibration mechanically. The frame of the dynamotor should be grounded through a heavy flexible connector. The brushes on the high-voltage end of the shaft should be bypassed with $0.002~\mu f$, mica capacitors to a common point on the dynamotor frame, preferably to a point inside the end cover close to the brush holders. Short leads are essential. It may prove desirable to shield the entire unit, or even to remove the unit to a distance of three or four feet from the receiver and antenna lead.

When the dynamotor is used for receiving, a filter should be used similar to that described

for vibrator supplies. A 0.01- μ f. 600-volt (d.c.) paper capacitor should be connected in shunt across the output of the dynamotor, followed by a 2.5-mh. r.f. choke in the positive high-voltage lead. From this point the output should be run to the receiver power terminals through a smoothing filter using 4- to 8- μ f. capacitors and a 15- or 30-henry choke having low d.c. resistance.

Vibrator Power Supplies

The vibrator type of power supply consists of a special step-up transformer combined with a vibrating interrupter (vibrator). When the unit is connected to a storage battery, plate power is obtained by passing current from the battery through the primary of the transformer. The circuit is made and reversed rapidly by the vibrator contacts, interrupting the current at regular intervals to give a changing magnetic field which induces a voltage in the secondary. The resulting square-wave d.c. pulses in the primary of the transformer cause an alternating voltage to be developed in the secondary. This high-voltage a.c. in turn is rectified, either by a vacuum-tube rectifier or by an additional synchronized pair of vibrator contacts. The rectified output is pulsating d.c., which may be filtered by ordinary means. The smoothing filter can be a single-section affair, but the output capacitance should be fairly large --- 16 to 32 μ f.

Fig. 19-46 shows the two types of circuits. At A is shown the nonsynchronous type of vibrator. When the battery is disconnected the reed is midway between the two contacts, touching neither. On closing the battery circuit the magnet coil pulls the reed into contact with one contact point, causing current to flow through the lower half of the transformer primary winding. Simultaneously, the magnet coil is short-circuited, deënergizing it, and the reed swings back. Inertia carries the reed into contact with the upper point, causing current to flow through the upper half of the transformer primary. The magnet coil again is energized, and the cycle repeats itself.

The synchronous circuit of Fig. 19-46B is provided with an extra pair of contacts which

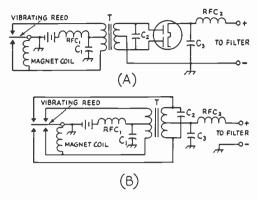


Fig. 19-46—Basic types of vibrator power-supply circuits.

A—Nonsynchronous. B—Synchronous.

rectifies the secondary output of the transformer, thus eliminating the need for a separate rectifier tube. The secondary center-tap furnishes the positive output terminal when the relative polarities of primary and secondary windings are correct. The proper connections may be determined by experiment.

The buffer capacitor, C2, across the transformer secondary, absorbs the surges that occur on breaking the current, when the magnetic field collapses practically instantaneously and hence causes very high voltages to be induced in the secondary. Without this capacitor excessive sparking occurs at the vibrator contacts, shortening the vibrator life. Correct values usually lie between 0.005 and 0.03 μ f., and for 250-300-volt supplies the capacitor should be rated at 1500 to 2000 volts d.c. The exact capacitance is critical, and should be determined experimentally. The optimum value is that which results in least battery current for a given rectified d.c. output from the supply. In practice the value can be determined by observing the degree of vibrator sparking as the capacitance is changed. When the system is operating properly there should be practically no sparking at the vibrator contacts. A 5000-ohm resistor in series with C2 will limit the secondary current to a safe value should the capacitor fail.

Vibrator-transformer units are available in a variety of power and voltage ratings. Representative units vary from one delivering 125 to 200 volts at 100 ma. to others that have a 400volt output rating at 150 ma. Most units come supplied with "hash" filters, but not all of them have built-in ripple filters. The requirements for ripple filters are similar to those for a.c. supplies. The usual efficiency of vibrator packs is in the vicinity of 70 per cent, so a 300-volt 200-ma. unit will draw approximately 15 amperes from a 6volt storage battery. Special vibrator transformers are also available from transformer manufacturers so that the amateur may build his own supply if he so desires. These have d.c. output ratings varying from 150 volts at 40 ma. to 330 volts at 135 ma.

Vibrator-type supplies are also available for

operating standard a.c. equipment from a 6- or 12-volt storage battery in power ratings up to 100 watts continuous or 125 watts intermittent.

"Hash" Elimination

Sparking at the vibrator contacts causes r.f. interference ("hash," which can be distinguished from hum by its harsh, sharper pitch) when used with a receiver. To minimize this, r.f. filters are incorporated, consisting of RFC_1 and C_1 in the battery circuit, and RFC_2 with C_3 in the d.c. output circuit.

Equally as important as the hash filter is thorough shielding of the power supply and its connecting leads, since even a small piece of wire or metal will radiate enough r.f. to cause interference in a sensitive amateur receiver.

The power supply should be built on a metal chassis, with all unshielded parts underneath. A bottom plate to complete the shielding is advisable. The transformer case, vibrator cover and the metal shell of the tube all should be grounded to the chassis. If a glass tube is used it should be enclosed in a tube shield. The battery leads should be evenly twisted, since these leads are more likely to radiate hash than any other part of a well-shielded supply. Experimenting with different values in the hash filters should come after radiation from the battery leads has been reduced to a minimum. Shielding the leads is not often found to be particularly helpful.

UNIVERSAL POWER SUPPLY

A vibrator-type power supply may be designed to operate from a storage battery only, or from either a battery or 115 volts a.c. Most late-model cars use 12-volt batteries, but there are still many cars with 6-volt systems in operation — a point to consider where emergency operation is an objective.

The circuit of a universal power supply for emergency, mobile, or home-station use is shown in Fig. 19-47. The unit furnishes a d.c. output of 300 volts at 160 ma. and can be operated from any of the above-mentioned sources. Shifting from one power source to another is accomplished by plugging P_1 or P_2 , connected to the selected source, into one of the two chassis connectors J_1 or J_2 . The vibrator-primary current is 11.6 amperes with 6-volt input under loaded conditions, and 6.8 amperes with 12-volt input.

To adapt equipment for optional 6- or 12-volt operation, 6-volt tubes must be used with their heaters in series-parallel. Fig. 19-48 shows a typical example of connections.

Battery input connections are made through P_5 which plugs into a cigar-lighter socket in mobile service.

For 6-volt operation P_1 is plugged into J_1 . For 12-volt operation P_1 is plugged into J_2 . For 115-volt a.c. operation P_2 is plugged into J_2 .

Positive high-voltage output from the supply is fed to Pins 3 on output connectors J_3 and J_4 . The three heater connections are made through Pins 1, 2 and 6. The cable for transmitter plug P_3 has provision for connecting to a transmit-

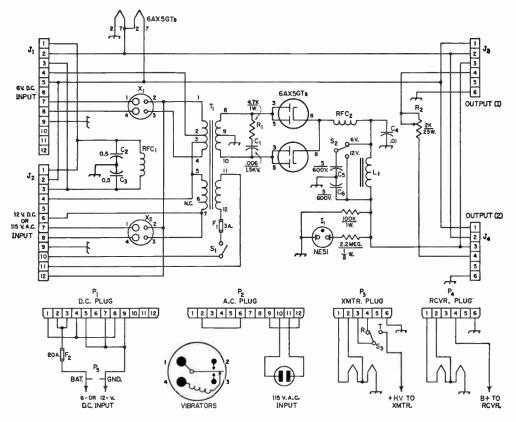


Fig. 19-47—Circuit of the universal power supply. All capacitances are in μf .

F₁-3-amp. cartridge fuse.

F2-20-amp, cartridge fuse.

 J_{1} , J_2 —12-contact male chassis connector (Cinch-Jones P-312-AB).


J₈, J₄—6-contact female chassis connector (Cinch-Jones S-306-AB).

L₁--5-h. 200-ma. 80-ohm filter choke (Merit C-1396, Stancor C-1411).

P₁, P₂—12-contact female cable connector (Cinch-Jones S-312-CCT).

P₃, P₄—6-contact male cable connector (Cinch-Jones P-306-CCT).

Fig. 19-48 — Circuit showing typical seriesparallel heater connections for 6-volt and 6/12-volt tubes. Resistor R_1 is used when necessary to balance the currents in the two branches. The dashed line shows how the switching system connects all tubes in parallel for 6-volt operation by grounding.

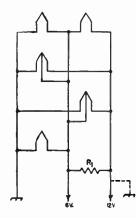

P₅-Cigar-Lighting plug (Mallory R-675).

RFC1-30 turns No. 14 enam., ½-inch diam., close-wound.
RFC2-1-mh. r.f. choke (National R-300-U, Millen 34106).
1-Combination power transformer: 6-volt d.c. vibrator or 115 v a.c. input; 300 volts, 160 ma.; 6.3 volts 3 amp.; 6.3-volt 4.5-amp. tap on vibrator primary (Merit P-3176).

X₁—4-prong tube socket for 6-volt vibrator (Mallory 4501 vibrator).

X₂—4-prong tube socket for 12-volt vibrator (Mallory G4501 vibrator).

receive switch (S_8) at the transmitter. In the transmit position the plate voltage is fed to the transmitter. In the receive position the switch feeds the plate voltage, via Pin 4, through series voltage-dropping resistor R_2 to Pin 4 on the other output jack and thence to the receiver. It will be noticed that the same circuit results with P_8 and P_4 in either output jack.

(Originally described in QST, Oct., 1957.)

TRANSISTOR POWER SUPPLIES

A mobile or portable power supply using transistors has high over-all efficiency at its rated power output. Since there are no moving parts there are few maintenance problems. Capacitors and resistors may occasionally need

Transistor Supply

220/10W

3/10W

replacement, but if the transistors are operated within their electrical and thermal ratings, their life expectancy is in terms of years rather than hours

In a transistor power supply, the transistors operate as electronic switches to interrupt the d.c. through the primary of the power transformer much like the mechanical vibrator does in a vibrator supply.

When voltage is applied to the power supply circuit, current will flow through the transistors; however, since no two transistors are precisely alike electrically, initially one will conduct a little more current than the other. This difference current or "starting" current will cause a small voltage to be induced in the transformer winding connected to the bases of the transistors. The polarity is such that the con-

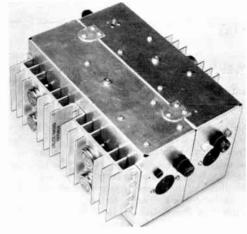


Fig. 19-49—Triple transistar pawer supply delivers +600, +250 and -300 valts. Ribbed aluminum heat sinks are standard item, were painted black after picture was taken. Tube sackets are used as jacks for autput and cantral circuits, tip jacks are valtage test paints. Twa chassis are hinged an underside, lacked tagether an tap by twa tabs af aluminum and sheetments.

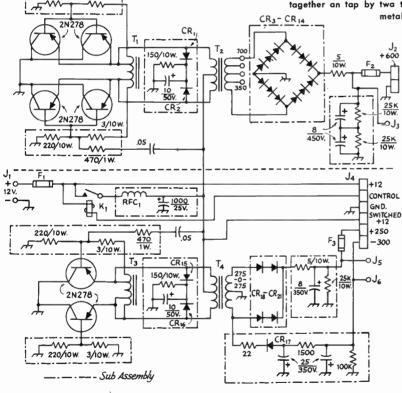


Fig. 19-50—Circuit diagram of the triple transistarized power supply. Capacitances are in μf., resistars are ½ watt unless specified atherwise. Capacitars marked with palarity are electralytic; athers are paper.

CR₁—CR₁₇—400 p.i.v. 350-ma. silican rectifier (International Rectifier 5E4).

CR₁₈—CR₂₁—400 p.i.v. 600-ma. silican rectifier (G. E. 1N1695).

F₁-30-ampere fuse.

Fg-14-ampere fuse.

F_s—½-ampere fuse.

J₁-Insulated terminal (Millen 37001).

J₂, J₃—Tube sacket.

Ja, Ja, Ja-Insulated tip jack.

K₁—S.p.s.t. relay, 60-amp. cantacts, 12-valt cail (Patter & Brumfield MB3D).

RFC₁—20 turns Na. 10 ename! clase-waund an ½-inch diameter.

T₁—Taraid feedback transfarmer (Osbarne 2709).

T_s—Pawer transfarmer with Hypersil care, 295 v.a. Secandary tapped far 700, 650, 550 ar 350 valts. (Osbarne 16553-12).

T_s—Taraid feedback transfarmer (Osbarne 716).

T₄—Pawer transfarmer with Hypersil care, 120 v.a.

Secandary 550 v.c.t. (Qsbarne 14572A-12).


(T₁ - T₄ available fram Osbarne Transfarmer
Ca., 3834 Mitchell, Detrait 7, Mich.)

ducting transistor is biased to conduct even more heavily while the base of the other transistor is biased to cutoff. This process continues until the increasing current causes magnetic saturation of the transformer core, at which time the induced voltage drops to zero and there is no longer enough base bias to maintain the collector current. When this happens the current decreases, causing an induced voltage of opposite polarity. The process then reverses so that the previously nonconducting transistor starts to conduct and the previously conducing transistor becomes cut off. The result is an alternating current of square-wave form through the transformer primary. This in turn induces a steppedup voltage in the h.v. secondary of the transformer.

The transistor supply is self-protecting against overload because if a short circuit or heavy overload occurs oscillations cease and the input current drops to a low value. The output voltage regulation is extremely good making the transistor supply especially useful as a source of plate or screen power for a single-sideband mobile or portable rig.

In a transistor power supply that has not been properly designed, small spikes may appear on the leading edges of the square wave generated in the transistor power oscillator. Even though the spikes are of short duration they can cause punch-through of the transistor junction if the total voltage exceeds the transistor collec-

Fig. 19-51—Only electrical connections between the two chassis are through fastenings and the +12-volt lead (top center). Construction of the units is simplified by generous use of sub-assemblies (outlined in dot-and-dash lines in Fig. 19-50). The sub-assemblies are made up on multiple tie-point strips, wired and put in place. Bridge rectifier section, CR3 through CR14, is made on four tie-point strips arranged in a square (lower left). The insulated terminal on the low-voltage supply (upper right) receives the +12 volts from the battery.

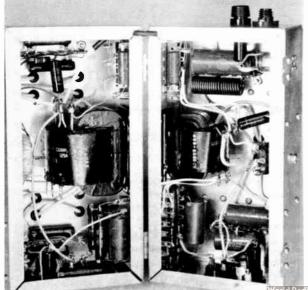

tor-to-emitter rating. The amplitudes of these spikes can be held to a safe value if the primary and secondary coils on the power transformer are tightly coupled and a large capacitor is connected across the low-voltage supply.

Transistor power transformers are available in both conventional and toroidal construction, with outputs ranging up to 150 watts. The supply shown in Figs. 19-49 and 19-51 has three outputs: 590 volts at 120 ma. (dropping to 570 volts at 225-ma. peaks), 250 volts at 125 ma., and a 300-volt negative supply for bias purposes. The high-voltage section uses silicon diodes in series in a bridge rectifier circuit, and the low-voltage section uses a center-tapped transformer and silicon diodes in series in a full-wave rectifier circuit. The transistors are mounted on ribbed aluminum heat sinks (Delco 7270606).

The wiring diagram, Fig. 19-50, is drawn with a horizontal dashed line that separates the high-voltage supply from the other two. This dashed line also represents the distribution of the components between the two $5 \times 9\frac{1}{2} \times 3$ -inch aluminum chassis that make up the cabinet. A single heavy wire carries the +12 volts from one chassis to the other. Provision is included for remote control of the power (and +12 volts) through the heavy-duty relay.

It is very important to provide good heat transfer from the mounting bases of the transistors to the heat sinks, and a small amount of silicone lubricant should be spread on the transistor when it is bolted to the sink.

Matched pairs of 2N278 transistors were used in the high-voltage supply. If matched pairs were not used in parallel, it would be necessary to include 0.1-ohm current-equalizing resistors in series with each emitter.

Since heat is the prime limiting factor in transistor power supply operation, placement of the unit in the car should have some special consideration. Try to find a location away from high-temperature spots and in a well-ventilated area.

GASOLINE-ENGINE DRIVEN GENERATORS

For higher-power installations, such as for communications control centers during emergencies, the most practical form of independent power supply is the gasoline-engine driven generator which provides standard 115-volt 60-cycle supply.

Such generators are ordinarily rated at a minimum of 250 or 300 watts. They are available up to ten kilowafts, or big enough to handle the highest-power amateur rig. Most are arranged to charge automatically an auxiliary 6-or 12-volt battery used in starting. Fitted with self-starters and adequate mufflers and filters, they represent a high order of performance and efficiency. Many of the larger models are liquid-cooled, and they will operate continuously at full load.

World Radio History

Mobile Power

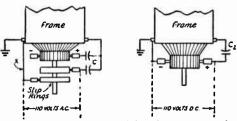


Fig. 19-52—Connections used for eliminating interference from gas-driven generator plants. C should be 1 μ f., 300 volts, paper, while C₂ may be 1 μ f. with a voltage rating of twice the d.c. output voltage delivered by the generator. X indicates an added cannection between the slip ring on the grounded side of the line and the generator frame.

The output frequency of an engine-driven generator must fall between the relatively narrow limits of 50 to 60 cycles if standard 60-cycle transformers are to operate efficiently from this source. A 60-cycle electric clock provides a means of checking the output frequency with a fair degree of accuracy. The clock is connected across the output of the generator and the second hand is checked closely against the second hand of a watch. The speed of the engine is adjusted until the two second hands are in synchronism.

Output voltage should be checked with a voltmeter since a standard 115-volt lamp bulb, which is sometimes used for this purpose, is very inaccurate.

Noise Elimination

Electrical noise which may interfere with receivers operating from engine-driven a.c. generators may be reduced or eliminated by taking proper precautions. The most important point is that of grounding the frame of the generator and one side of the output. The ground lead should be short to be effective, otherwise grounding may actually increase the noise. A water pipe may be used if a short connection can be made near the point where the pipe enters the ground, otherwise a good separate ground should be provided.

The next step is to loosen the brush-holder locks and slowly shift the position of the brushes while checking for noise with the re-

ceiver. Usually a point will be found (almost always different from the factory setting) where there is a marked decrease in noise.

From this point on, if necessary, bypass capacitors from various brush holders to the frame, as shown in Fig. 19-52, will bring the hash down to within 10 to 15 per cent of its original intensity, if not entirely eliminating it. Most of the remaining noise will be reduced still further if the high-power audio stages are cut out and a pair of headphones is connected into the second detector.

POWER FOR PORTABLES

Dry Cell Batteries

Dry-cell batteries are a practical source of power for supplying portables or equipment which must be transported on foot. However, they are costly and have limited current capability. The zinc-carbon cells lose their power even when not in use, if allowed to stand idle for periods of a year or more. This makes them uneconomical if not used more or less continuously.

The mercury cell has a much higher ratio of ampere-hour capacity to volume at higher current densities than are obtainable from the conventional dry cell. Mercury batteries are well suited for emergency portable operation even after many months of storage.

Typical service life data for several types of zinc-carbon cells and batteries is given in Table 19-III. The figures show length of service time before the cell terminal voltage drops to 1.0 volt (in B-batteries, when individual cells reach 1.0 volt).

Mercury batteries and cells are available in several sizes and shapes. Some may be operated at current drains up in the ampere range and others are available in potentials in the hundreds of volts. A typical 1.35-volt mercury cell measuring only $2\frac{1}{4} \times 2\frac{1}{4} \times 2\frac{3}{4}$ inches, has a capacity of 43 ampere hours (maximum current 3 amperes). Cells of this type would be useful for filament or heater applications. A representative mercury B-battery has a voltage of 67.5 volts and a capacity of 3.6 ampere hours (maximum current 250 ma.). It measures about $3\frac{1}{16} \times 1\frac{1}{2} \times 10\frac{1}{6}$ inches.

Service life of	TABLE 19-III some typical zinc-carbon cells an	d batteries			
Cell or Battery	ASA Cell Size		nuous vice		ırs per service
		ma.	hrs.	ma.	hrs.
1.5 v. penlite cell 1.5 v. flashlight cell 1.5 v. ignition cell	AA D #6	30 160 500	14 9 43	20 130 500	33 21 80
45 v., 67.5 v., 90 v. B-battery	F30 F40 F70	18 19 20	9 15 35	16 17 24	1· 2· 4

Construction Practices

TOOLS AND MATERIALS

While an easier, and perhaps a better, job can be done with a greater variety of tools available, by taking a little thought and care it is possible to turn out a fine piece of equipment with only a few of the common hand tools. A list of tools which will be indispensable in the contruction of radio equipment will be found on this page. With these tools it should be possible to perform any of the required operations in preparing panels and metal chassis for assembly and wiring.

INDISPENSABLE TOOLS

Long-nose pliers, 6-inch. Diagonal cutting pliers, 6-inch. Wire stripper. Screwdriver, 6- to 7-inch, 1/4-inch blade. Screwdriver, 4- to 5-inch, 1/4-inch blade. Scratch awl or scriber for marking lines. Combination square, 12-inch, for laying out work. Hand drill, 1/4-inch chuck or larger, 2-speed type preferable. Electric soldering iron, 100 watts, 1/4-in. tip. Hack saw, 12-inch blades. Center punch for marking hole centers. Hammer, ball-peen, 1-lb. head. Heavy knife. Yardstick or other straightedge. Carpenter's brace with adjustable hole cutter or socket-hole punches (see text). Large, coarse, flat file. Large round or rat-tail file, 1/2-inch diameter. Three or four small and medium files-flat, round, half-round, triangular. Drills, particularly 1/4-inch and Nos. 18, 28, 33, 42 and 50. Combination oil stone for sharpening tools.

ADDITIONAL TOOLS

Solder and soldering paste (noncorroding).

Medium-weight machine oil.

Bench vise, 4-inch jaws. Tin shears, 10-inch, for cutting thin sheet metal. Taper reamer, 1/2-inch, for enlarging small holes. Taper reamer, 1-inch, for enlarging holes. Countersink for brace. Carpenter's plane, 8- to 12-inch, for woodworking. Carpenter's saw, crosscut. Motor-driven emery wheel for grinding. Long-shank screwdriver with screw-holding clip for tight places. Set of "Spintite" socket wrenches for hex nuts. Set of small, flat, open-end wrenches for hex nuts. Wood chisel, 1/2-inch. Cold chisel, 1/2-inch. Wing dividers, 8-inch, for scribing circles. Set of machine-screw taps and dies. Dusting brush.

Socket punches, esp. 5/8", 3/4", 11/8" and 11/4".

It is an excellent idea for the amateur who does constructional work to add to his supply of tools from time to time as finances permit.

Several of the pieces of light woodworking machinery, often sold in hardware stores and mail-order retail stores, are ideal for amateur radio work, especially the drill press, grinding head, band and circular saws, and jointer. Although not essential, they are desirable should you be in a position to acquire them.

Twist Drills

Twist drills are made of either high-speed steel or carbon steel. The latter type is more common and will usually be supplied unless specific request is made for high-speed drills. The carbon drill will suffice for most ordinary equipment construction work and costs less than the high-speed type.

While twist drills are available in a number of sizes, those listed in bold-faced type in Table 20-I will be most commonly used in construction of amateur equipment. It is usually desirable to purchase several of each of the commonly used sizes rather than a standard set, most of which will be used infrequently if at all.

Care of Tools

The proper care of tools is not alone a matter of pride to a good workman. He also realizes the energy which may be saved and the annoyance which may be avoided by the possession of a full kit of well-kept sharpedged tools.

Drills should be sharpened at frequent intervals so that grinding is kept at a minimum each time. This makes it easier to maintain the rather critical surface angles required for best cutting with least wear. Occasional oilstoning of the cutting edges of a drill or reamer will extend the time between grindings.

The soldering iron can be kept in good condition by keeping the tip well tinned with solder and not allowing it to run at full voltage for long periods when it is not being used. After each period of use, the tip should be removed and cleaned of any scale which may have accumulated. An oxidized tip may be cleaned by dipping it in sal ammoniac while hot and then wiping it clean with a rag. If the tip becomes pitted it should be filed until smooth and bright, and then tinned immediately by dipping it in solder.

Tools 503

Useful Materials

Small stocks of various miscellaneous materials will be required in constructing radio apparatus, most of which are available from hardware or radio-supply stores. A representative list follows:

Sheet aluminum, solid and perforated, 16 or 18 gauge, for brackets and shielding. ½ × ½-inch aluminum angle stock.

14-inch diameter round brass or aluminum rod for shaft extensions.

Machine screws: Round-head and flat-head, with nuts to fit. Most useful sizes: 4-36, 6-32 and 8-32, in lengths from ¼ inch to 1½ inches. (Nickel-plated iron will be found satisfactory except in strong r.f. fields, where brass should be used.)

Bakelite, lucite and polystyrene scraps.

Soldering lugs, panel bearings, rubber grommets, terminal-lug wiring strips, varnished-cambric insulating tubing.

Shielded and unshielded wire. Tinned bare wire, Nos. 22, 14 and 12.

Machine screws, nuts, washers, soldering lugs, etc., are most reasonably purchased in quantities of a gross.

CHASSIS WORKING

With a few essential tools and proper procedure, it will be found that building radio gear on a metal chassis is no more of a chore than building with wood, and a more satisfactory job results. Aluminum is to be preferred to steel, not only because it is a superior shielding material, but because it is much easier to work and to provide good chassis contacts.

The placing of components on the chassis is shown quite clearly in the photographs in this *Handbook*. Aside from certain essential dimensions, which usually are given in the text, exact duplication is not necessary.

Much trouble and energy can be saved by spending sufficient time in planning the job. When all details are worked out beforehand the actual construction is greatly simplified.

Cover the top of the chassis with a piece of wrapping paper or, preferably, cross-section

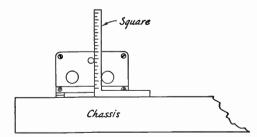


Fig. 20-1—Method of measuring the heights of capacitor shafts, etc. If the square is adjustable, the end of the scale should be set flush with the face of the head.

TABLE	20-1	
Maraharad	Deill	S:

			Drilled for
	Diameter	Will Clear	Tapping Iron,
Number	(mils)	Screw	Steel or Brass*
1	228.0		
2	228.0	12-24	
3	213.0	12-24	14–24 –
4	209.0	12-20	-
5	205.0		_
6	204.0	_	
7	201.0		
8	199.0	-	 12-24
9	196.0	-	
10	193.5	10-32	_
11	191.0	10-24	
12	189.0	_	
13	185.0	-	-
14	182.0	-	
15	180.0	_	_
16	177.0		12-24
17	173.0		
18	169.5	8-32	_
19	166.0	_	12-20
20	161.0	_	-
21	159.0		10-32
22	157.0		_
23	154.0		_
24	152.0		
25	149.5	_	10-24
26 27	147.0 144.0	-	
28	140.0	6-32	-
29	136.0	0-32	9_22
30	128.5	_	8–32
31	120.0	_	_
32	116.0	_	
33	113.0	4-36, 4-40	-
34	111.0		 6-32
35	110.0		6-32
36	106.5		_
37	104.0		
38	101.5	_	_
39	099.5	3-48	
40	098.0	_	_
41	096.0	-	
42	093.5	-	4-36, 4-40
43	089.0	2-56	_
44	086.0	_	_
45	082.0		3-48
46	081.0	_	_
47	078.5	_	_
48	076.0	- - - -	
49	073.0	_	2-56
50	070.0	_	_
51 52	067.0 063.5	_	_
52 53	063.5 059.5	_	-
54	055.0	_	_
34	033.0	_	_

*Use one size larger for tapping bakelite and hard rubber.

paper, folding the edges down over the sides of the chassis and fastening with adhesive tape. Then assemble the parts to be mounted on top of the chassis and move them about until a satisfactory arrangement has been found, keeping in mind any parts which are to be mounted underneath, so that interferences in mounting may be avoided. Place capacitors and other parts with shafts extending through the panel first, and arrange them so that the controls will form the desired pattern on the panel. Be sure to line up the shafts

squarely with the chassis front. Locate any partition shields and panel brackets next, and then the tube sockets and any other parts, marking the mounting-hole centers of each accurately on the paper. Watch out for capacitors whose shafts are off center and do not line up with the mounting holes. Do not forget to mark the centers of socket holes and holes for leads under i.f. transformers, etc., as well as holes for wiring leads. The small holes for socket-mounting screws are best located and center-punched, using the socket itself as a template, after the main center hole has been cut.

By means of the square, lines indicating accurately the centers of shafts should be extended to the front of the chassis and marked on the panel at the chassis line, the panel being fastened on temporarily. The hole centers may then be punched in the chassis with the center punch. After drilling, the parts which require mounting underneath may be located and the mounting holes drilled, making sure by trial that no interferences exist with parts mounted on top. Mounting holes

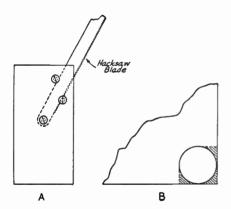


Fig. 20-2—To cut rectangular hales in a chassis corner, holes may be filed out as shown in the shaded portion of B, making it possible ta start the hack-saw blade along the cutting line. A shows how a single-ended handle may be canstructed for a hack-saw blade.

along the front edge of the chassis should be transferred to the panel, by once again fastening the panel to the chassis and marking it from the rear.

Next, mount on the chassis the capacitors and any other parts with shafts extending to the panel, and measure accurately the height of the center of each shaft above the chassis, as illustrated in Fig. 20-1. The horizontal displacement of shafts having already been marked on the chassis line on the panel, the vertical displacement can be measured from this line. The shaft centers may now be marked on the back of the panel, and the holes drilled. Holes for any other panel equipment coming above the chassis line may then be marked and drilled, and the remainder of

the apparatus mounted. Holes for terminals etc., in the rear edge of the chassis should be marked and drilled at the same time that they are done for the top.

Drilling and Cutting Holes

When drilling holes in metal with a hand drill it is important that the centers first be located with a center punch, so that the drill point will not "walk" away from the center when starting the hole. When the drill starts to break through, special care must be used. Often it is an advantage to shift a two-speed drill to low gear at this point. Holes more than ½ inch in diameter may be started with a smaller drill and reamed out with the larger drill.

The chuck on the usual type of hand drill is limited to 1/4-inch drills. Although it is rather tedious, the 1/4-inch hole may be filed out to larger diameters with round files. Another method possible with limited tools is to drill a series of small holes with the hand drill along the inside of the diameter of the large hole, placing the holes as close together as possible. The center may then be knocked out with a cold chisel and the edges smoothed up with a file. Taper reamers which fit into the carpenter's brace will make the job easier. A large rat-tail file clamped in the brace makes a very good reamer for holes up to the diameter of the file, if the file is revolved counterclockwise

For socket holes and other large round holes, an adjustable cutter designed for the purpose may be used in the brace. Occasional application of machine oil in the cutting groove will help. The cutter first should be tried out on a block of wood, to make sure that it is set for the correct diameter. The most convenient device for cutting socket holes is the socket-hole punch. The best type is that which works by turning a take-up screw with a wrench.

The burrs or rough edges which usually result after drilling or cutting holes may be removed with a file, or sometimes more conveniently with a sharp knife or chisel. It is a good idea to keep an old wood chisel sharpened and available for this purpose.

Rectangular Holes

Square or rectangular holes may be cut out by making a row of small holes as previously described, but is more easily done by drilling a ½-inch hole inside each corner, as illustrated in Fig. 20-2, and using these holes for starting and turning the hack saw. The socket-hole punch and the square punches which are now available also may be of considerable assistance in cutting out large rectangular openings.

CONSTRUCTION NOTES

If a control shaft must be extended or insulated, a flexible shaft coupling with ad-

equate insulation should be used. Satisfactory support for the shaft extension, as well as electrical contact for safety, can be provided by means of a metal panel bearing made for the purpose. These can be obtained singly for use with existing shafts, or they can be bought with a captive extension shaft included. In either case the panel bearing gives a "solid" feel to the control.

The use of fiber washers between ceramic insulation and metal brackets, screws or nuts will prevent the ceramic parts from breaking.

Gauge	American	U.S.	Birmingham
No.	or B. & S.	Standard ²	or Stubs ³
-	2007	.28125	.300
1	.2893	.265625	.284
2	.2376	.263623	.259
3			.239
4	.2043	.234375	
5	.1819	.21875	.220 .203
6	.1620	.203125	
7	.1443	.1875	.180
8	.1285	.171875	.165
9	.1144	.15625	.148
10	.1019	.140625	.134
11	.09074	.125	.120
12	.08081	.109375	.109
13	.07196	.09375	.095
14	.06408	.078125	.083
15	.05707	.0703125	.072
16	.05082	.0625	.065
17	.04526	.05625	.058
18	.04030	.05	.049
19	.03589	.04375	.042
20	.03196	.0375	.035
21	.02846	.034375	.032
22	.02535	.03125	.028
23	.02257	.028125	.025
24	.02010	.025	.022
25	.01790	.021875	.020
26	.01594	.01875	.018
27	.01394	.0171875	.016
28	.01264	.0171873	.014
28 29	.01264	.0140625	.014
			.013
30	.01003	.0125	
31	.008928	.0109375	.010
32	.007950	.01015625	.009
. 33	.007080	.009375	.008
34	.006350	.00859375	.007
35	.005615	.0078125	.005
36	.005000	.00703125	.004
37	.004453	.006640626	
38	.003965	.00625	
39	.003531		
40	.003145		

[!] Used for aluminum, copper, brass and non-ferrous alloy sheets, wire and rods.

Cutting and Bending Sheet Metal

If a sheet of metal is too large to be cut conveniently with a hack saw, it may be marked with scratches as deep as possible along the line of the cut on both sides of the sheet and then clamped in a vise and worked back and forth until the sheet breaks at the line. Do not carry the bending too far until the break begins to weaken; otherwise the

edge of the sheet may become bent. A pair of iron bars or pieces of heavy angle stock, as long or longer than the width of the sheet, to hold it in the vise will make the job easier. "C"-clamps may be used to keep the bars from spreading at the ends. The rough edges may be smoothed up with a file or by placing a large piece of emery cloth or sandpaper on a flat surface and running the edge of the metal back and forth over the sheet.

Bends may be made similarly. The sheet should be scratched on both sides, but not so deeply as to cause it to break.

Finishing Aluminum

Aluminum chassis, panels and parts may be given a sheen finish by treating them in a caustic bath. An enamelled container, such as a dishpan or infant's bathtub, should be used for the solution. Dissolve ordinary household lye in cold water in a proportion of 1/4 to 1/2 can of lye per gallon of water. The stronger solution will do the job more rapidly. Stir the solution with a stick of wood until the lye crystals are completely dissolved. Be very careful to avoid any skin contact with the solution. It is also harmful to clothing. Sufficient solution should be prepared to cover the piece completely. When the aluminum is immersed, a very pronounced bubbling takes place and ventilation should be provided to disperse the escaping gas. A half hour to two hours in the solution should be sufficient, depending upon the strength of the solution and the desired surface.

Remove the aluminum from the solution with sticks and rinse thoroughly in cold water while swabbing with a rag to remove the black deposit. Then wipe off with a rag soaked in vinegar to remove any stubborn stains or fingerprints.

Soldering

The secret of good soldering is in allowing time for the *joint*, as well as the solder, to attain sufficient temperature. Enough heat should be applied so that the solder will melt when it comes in contact with the wires being joined, without touching the solder to the

DECIMAL E	QUIVALE	NTS OF PRACT	IONS
1/32	.03125	17/32	.53125
1/16	.0625	9/16	.5625
3/32	.09375	19/32	.59375
1/8	.125	5/8	.625
5/32	.15625	21/32	.65625
3/16	.1875	11/16	.6875
7/32	.21875	23/32	.71875
1/4	.25	3/4	.75
9/32	.28125	25/32	.78125
5/16	.3125	13/16	.8125
11/32	.34375	27/32	.84375
3/8	.375	7/8	.875
13/32:	.40625	29/32	.90625
7/16	.4375	15/16	.9375
15/32	.46875	31/32	.96875
1/2	.5	1	1.0

² Used for iron, steel, nickel and ferrous alloy sheets, wire and rods.

³ Used for seamless tubes; also by some manufacturers for copper and brass.

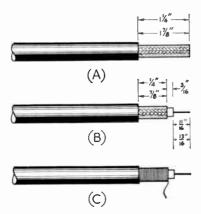


Fig. 20-3—Cable-stripping dimensions for Jones Type P-101 plugs. Smaller dimensions are for ¼-inch plugs, the larger dimensions for ½-inch plugs. As indicated in C, the remaining copper braid is wound with bare or tinned wire and then tinned, to make a snug fit in the sleeve of the plug. Hold a hot iron to the sleeve after the cable is inserted to solder

the sleeve to the braid.

iron. Always use rosin-core solder, never acidcore. Except where absolutely necessary, solder should never be depended upon for the mechanical strength of the joint; the wire should be wrapped around the terminals or clamped with soldering terminals.

When soldering crystal diodes or carbon resistors in place, especially if the leads have been cut short and the resistor is of the small ½-watt size, the resistor lead should be gripped with a pair of pliers up close to the resistor so that the heat will be conducted away from the resistor. Overheating of the resistor while soldering can cause a permanent resistance change of as much as 20 per cent. Also, mechanical stress will have a similar effect, so that a small resistor should be mounted so that there is no appreciable mechanical strain on the leads.

Trouble is sometimes experienced in soldering to the pins of coil-forms or male cable

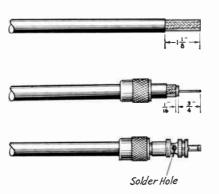


Fig. 20-4—Dimensions for stripping ½-inch cable to fit Amphenol Type 83-1SP (PL-259) plug.

CONSTRUCTION PRACTICES

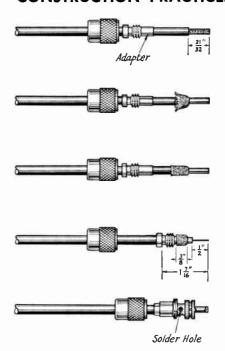


Fig. 20-5—Method of assembling ¼-inch cable, Amphenol Type 83-1SP (PL-259) plug and adapter.

plugs. It helps first to tin the inside of the pins by applying soldering paste to the hole, and then flowing solder into the pin. Then immediately clear the solder from the hot pin by a whipping motion or by blowing through the pin from the inside of the form or plug. Before inserting the wire in the pin, file the nickel plate from the tip. After soldering, round the solder tip off with a file.

When soldering to the pins of polystyrene coil forms, first clean the inside of each pin with a suitable twist drill. Then hold the pin to be soldered with a pair of heavy pliers, to form a "heat sink" and insure that the pin does not heat enough in the coil form to loosen and become misaligned.

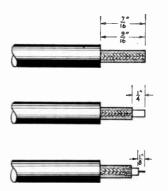


Fig. 20-6—Stripping dimensions for Amphenol 82-830 and 82-832 plug-in connectors. The longer exposed braid is for the first type.

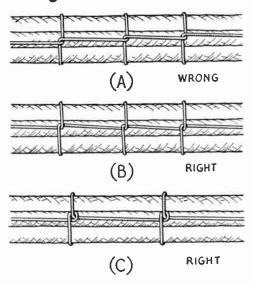


Fig. 20-7—Methods of lacing cables. The method shown at C is more secure, but takes more time than the method of B. The latter is usually adequate for most amateur requirements.

Wiring

The wire used in connecting up amateur equipment should be selected considering both the maximum current it will be called upon to handle and the voltage its insulation must stand without breakdown. Also, from the consideration of TVI, the power wiring of all transmitters should be done with wire that has a braided shielding cover. Receiver and audio circuits may also require the use of shielded wire at some points for stability, or the elimination of hum.

No. 20 stranded wire is commonly used for most receiver wiring (except for the high-frequency circuits) where the current does not exceed 2 or 3 amperes. For higher-current heater circuits, No. 18 is available. Wire with cellulose acetate insulation is good for voltages up to about 500. For higher voltages, thermoplastic-insulated wire should be used. Inexpensive wire strippers that make the removal of insulation from hook-up wire an easy job are available on the market.

In cases where power leads have several branches in the chassis, it is convenient to use fiber-insulated tie points or "lug strips" as anchorages or junction points. Strips of this type are also useful as insulated supports for resistors, r.f. chokes and capacitors. High-voltage wiring should have exposed points held to a minimum, and those which cannot be avoided should be rendered as inaccessible as possible to accidental contact or short-circuit.

Where shielded wire is called for and capacitance to ground is not a factor, Belden type 8885 shielded grid wire may be used. If

capacitance must be minimized, it may be necessary to use a piece of car-radio lowcapacitance lead-in wire, or coaxial cable.

For wiring high-frequency circuits, rigid wire is often used. Bare soft-drawn tinned wire, sizes 22 to 12 (depending on mechanical requirements), is suitable. Kinks can be removed by stretching a piece 10 or 15 feet long and then cutting into short lengths that can be handled conveniently. R.f. wiring should be run directly from point to point with a minimum of sharp bends and the wire kept well spaced from the chassis or other grounded metal surfaces. Where the wiring must pass through the chassis or a partition, a clearance hole should be cut and lined with a rubber grommet. In case insulation becomes necessary, varnished cambric tubing (spaghetti) can be slipped over the wire.

In transmitters where the peak voltage does not exceed 2500 volts, the shielded grid wire mentioned above should be satisfactory for power circuits. For higher voltages, Belden type 8656, Birnbach type 1820, or shielded ignition cable can be used. In the case of filament circuits carrying heavy current, it may be necessary to use No. 10 or 12 bare or enameled wire, slipped through spaghetti, and then covered with copper braid pulled tightly over the spaghetti. The chapter on TVI shows the manner in which shielded wire should be applied. If the shielding is simply slid back over the insulation and solder flowed into the end of the braid, the braid usually will stay in place without the necessity for cutting it back or binding it in place. The braid should be burnished with sandpaper or a knife so that solder will take with a minimum of heat.

R.f. wiring in transmitters usually follows the method described above for receivers with due respect to the voltages involved.

Where power or control leads run together for more than a few inches, they will present a better appearance when bound together in a single cable. The correct technique is illustrated in Fig. 20-7; both plastic and waxed-linen lacing cords are available for the purpose.

To give a "commercial look" to the wiring of any unit, run any cabled leads along the edge of the chassis. If this isn't possible, the cabled leads should then run parallel to an edge of the chassis. Further, the generous use of bakelite tie points (mounted parallel to an edge of the chassis), for the support of one or both ends of a resistor or fixed capacitor, will add to the appearance of the finished unit. In a similar manner, "dress" the small components so that they are parallel to the panel or sides of the chassis.

Winding Coils

Close-wound coils are readily wound on the specified form by anchoring one end of a length of wire (in a vise or to a doorknob)

	TABLE 20-II							
Standard Component Values								
20%	10%	5%						
Tolerance	Tolerance	Tolerance						
10	10	10						
		11						
	12	12						
		13						
15	15	15						
		16						
ľ	18	18						
		20						
22	22	22						
	0.7	24						
	27	27 30						
33	33	33						
, ,,	33	36						
	39	39						
	37	43						
47	47	47						
"	••	51						
	56	56						
		62						
68	68	68						
		75						
	82	82						
		91						
100	100	100						

and the other end to the coil form. Straighten any kinks in the wire and then pull to keep the wire under slight tension. Wind the coil to the required number of turns while walking toward the anchor, always maintaining a slight tension on the wire.

To space-wind the coil, wind the coil simultaneously with a suitable spacing medium (heavy thread, string or wire) in the manner described above. When the winding is complete, secure the end of the coil to the coilform terminal and then carefully unwind the spacing material. If the coil is wound under suitable tension, the spacing material can be easily removed without disturbing the winding. Finish the space-wound coil by judicious applications of Duco cement, to hold the turns in place.

COMPONENT VALUES

Values of composition resistors and small capacitors (mica and ceramic) are specified throughout this Handbook in terms of "preferred values." In the preferred-number system, all values represent (approximately) a constant-percentage increase over the next lower value. The base of the system is the number 10. Only two significant figures are used. Table 20-II shows the preferred values based on tolerance steps 20, 10 and 5 per cent. All other values are expressed by multiplying or dividing the base figures given in the table by the appropriate power of 10. (For example, resistor values of 33,000 ohms, 6800 ohms, and 150 ohms are obtained by multiplying the base figures by 1000, 100, and 10, respectively.)

"Tolerance" means that a variation of plus or minus the percentage given is considered


satisfactory. For example, the actual resistance of a "4700-ohm" 20-per-cent resistor can lie anywhere between 3700 and 5600 ohms, approximately. The permissible variation in the same resistance value with 5-per-cent tolerance would be in the range from 4500 to


4900 ohms, approximately.


Only those values shown in the first column of Table 20-II are available in 20-per-cent tolerance. Additional values, as shown in the second column, are available in 10-per-cent tolerance; still more values can be obtained in 5-per-cent tolerance.

In the component specifications in this *Handbook*, it is to be understood that when no tolerance is specified the *largest* tolerance available in that value will be satisfactory.

Values that do not fit into the preferrednumber system (such as 500, 25,000, etc.)

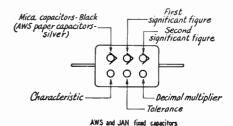

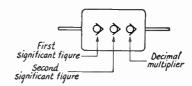

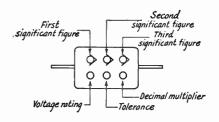

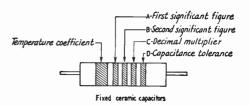


Fig. 20-8—Color coding of fixed mica, molded paper and tubular ceramic capacitors. The color code for mica and molded paper capacitors is given in Table 20-III.

Table 20-IV gives the color code for tubular ceramic capacitars.

easily can be substituted. It is obvious, for example, that a 5000-ohm resistor falls well within the tolerance range of the 4700-ohm 20-per-cent resistor used in the example above. It would not, however, be usable if the tolerance were specified as 5 per cent.

COLOR CODES

Standardized color codes are used to mark values on small components such as composition resistors and mica capacitors, and to identify leads from transformers, etc. The resistor-capacitor number color code is given in Table 20-III.


Fixed Capacitors

The methods of marking "postage-stamp" mica capacitors, molded paper capacitors, and tubular ceramic capacitors are shown in Fig. 20-8. Capacitors made to American War Standards or Joint Army-Navy specifications are marked with the 6-dot code shown at the top. Practically all surplus capacitors are in this category. The 3-dot EIA code is used for capacitors having a rating of 500 volts and ±20% tolerance only; other ratings and tolerances are covered by the 6-dot EIA code.

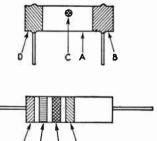Examples: A capacitor with a 6-dot code has the following markings: Top row, left to right, black, yellow, violet; bottom row, right to left, brown, silver, red. Since the first color in the top row is black (significant figure zero) this is the AWS code and the capacitor has mica dielectric. The significant figures are 4 and 7, the decimal multiplier 10 (brown, at right of second row), so the capacitance is 470 $\mu\mu$ f. The tolerance is \pm 10%. The final color, the characteristic, deals with temperature coefficients and methods of testing (see Table 20-V on page 510).

A capacitor with a 3-dot code has the following colors, left to right: brown, black, red. The significant figures are 1, 0 (10) and the multiplier is 100. The capacitance is therefore $1000~\mu\mu\text{f}$.

A capacitor with a 6-dot code has the following markings: Top row, left to right, brown, black, black; bottom row, right to left, black, gold, blue. Since the first color in the top row



Fixed composition resistors

Fig. 20-9—Color coding of fixed composition resistors, The color code is given in Table 20-III. The colored areas have the following significance:

A-First significant figure of resistance in ohms.

B—Second significant figure.

C-Decimal multiplier.

D-Resistance tolerance in per cent. If no color is shown the tolerance is ±20%.

is neither black nor silver, this is the EIA code. The significant figures are 1, 0, 0 (100) and the decimal multiplier is 1 (black). The capacitance is therefore 100 $\mu\mu$ f. The gold dot shows that the tolerance is \pm 5% and the blue dot indicates 600-volt rating.

Ceramic Capacitors

Conventional markings for ceramic capacitors are shown in the lower drawing of Fig. 20-8. The colors have the meanings indicated in Table 20-IV. In practice, dots may be used instead of the *narrow* bands indicated in Fig. 20-8.

Example: A ceramic capacitor has the following markings: Broad band, violet; narrow bands or dots, green, brown, black, green. The significant figures are 5, 1 (51) and the decimal multiplier is 1, so the capacitance is 51 $\mu\mu$ f. The temperature coefficient is -750 parts per million per degree C., as given by the broad band, and the capacitance tolerance is $\pm 5\%$.

TABLE 20-III	
Resistor-Capacitor Color Code	

Color	ignificant Figure	Decimal Multiplier	Tolerance (%)	Voltage Rating*
Black	0	1	_	
Brown	1	10	1*	100
Red	2	100	2*	200
Orange	3	1,000	3*	300
Yellow	4	10,000	4*	400
Green	5	100,000	5*	500
Blue	6	1,000,000	6*	600
Violet	7	10,000,000	7*	700
Gray	8	100,000,000	8*	800
White	9	1,000,000,000	9*	900
Gold	_	0.1	5	1000
Silver	-	0.01	10	2000
No color	-	-	20	500
	* Appl	ies to capacito	ors only.	

TABLE 20-IV Color Code for Ceramic Capacitors								
Capacitance Tolerance More Less Temp.								
Color	Signi- ficant Figure	imal Multi- plier	than 10 μμf.	than 10 μμf. (in μμf.)	Coeff. p.p.m. /deg. C.			
Black	0	1	± 20	2.0	0			
Brown	1	10	± 1		-30			
Red	2	100	± 2		80			
Orange	3	1000			-150			
Yellow	4 5				-220			
Green			± 5	0.5	-330			
Blue	6				-470			
Violet	7				-750			
Gray	8	0.01		0.25	30			
White	9	0.1	± 10	1.0	500			

CONSTRUCTION PRACTICES

		PILOT-LAMP	DATA		
Lamp	Bead	Base	Bulb	RAT	ING
No.	Color	(Miniature)	Type	Volts	Amb.
40	Brown	Screw	T-31/4	6-8	0.15
40A1	Brown	Bayonet	T-31/4	6-8	0.15
41	White	Screw	T-31/4	2.5	0.5
42	Green	Screw	T-31/4	3.2	**
43	White	Bayonet	T-31/4	2.5	0.5
44	Blue	Bayonet	T-31/4	6-8	0.25
45	*	Bayonet	T-31/4	3.2	**
46 ²	Blue	Screw	T-31/4	6-8	0.25
471	Brown	Bayonet	T-31/4	6-9	0.15
48	Pink	Screw	T-31/4	2.0	0.06
498	Pink	Bayonet	T-31/4	2.0	0.06
49A8	White	Bayonet	T-31/4	2.1	0.12
50	White	Screw	G-31/2	6-8	0.2
512	White	Bayonet	G-31/2	6-8	0.2
53		Bayonet	G-31/2	14.4	0.12
55	White	Bayonet	G-41/2	6-8	0.4
2925	White	Screw	T-31/4	2.9	0.17
292A5	White	Bayonet	T-31/4	2.9	0.17
1455	Brown	Screw	G-5	18.0	0.25
1455A	Brown	Bayonet	G-5	18.0	0.25
1487	_	Screw	T-31/4	12-16	0.20
1488	_	Bayonet	T-31/4	14	0.15
1813	_	Bayonet	T-31/4	14.4	0.10
1815	_	Bayonet	T-31/4	12-16	0.20

- ¹ 40A and 47 are interchangeable.
- ² Have frosted bulb.
- 8 49 and 49A are interchangeable.
- 4 Replace with No. 48.
- ⁵ Use in 2.5-volt sets where regular bulb burns out too frequently.
- * White in G.E. and Sylvania; green in National Union, Raytheon and Tung-Sol.
- ** 0.35 in G.E. and Sylvania; 0.5 in National Union, Raytheon and Tung-Sol.

Fixed Composition Resistors

Composition resistors (including small wirewound units molded in cases identical with the composition type) are color-coded as shown in Fig. 20-9. Colored bands are used on resistors having axial leads; on radial-lead resistors the colors are placed as shown in the drawing. When bands are used for color

TABLE 20-V Capacitor Characteristic Code						
Color Sixth Dot	Temperature Coefficient p.p.m./deg. C.	Capacitance Drift				
Black Brown Red Orange Yellow Green	± 1000 ± 500 + 200 + 100 - 20 to + 100 0 to + 70	$\begin{array}{c} \pm \ 5\% \ +1 \ \mu\mu\text{i}. \\ \pm \ 3\% \ +1 \ \mu\mu\text{i}. \\ \pm \ 0.5\% \\ \pm \ 0.3\% \\ \pm \ 0.1\% \ +0.1 \ \mu\mu\text{i}. \\ \pm \ 0.05\% \ +0.1 \ \mu\mu\text{i}. \end{array}$				

coding the body color has no significance.

Examples: A resistor of the type shown in the lower drawing of Fig. 20-9 has the following color bands: A, red; B, red; C, orange; D, no color. The significant figures are 2, 2 (22) and the decimal multiplier is 1000. The value of resistance is therefore 22,000 ohms and the tolerance is $\pm 20\%$.

A resistor of the type shown in the upper drawing has the following colors: body (A), blue; end (B), gray; dot, red; end (D), gold. The significant figures are 6, 8 (68) and the decimal multiplier is 100, so the resistance is 6800 ohms. The tolerance is ± 5%.

1.F. Transformers

Blue — plate lead. Red — "B" + lead.

Green - grid (or diode) lead. Black — grid (or diode) return.

Note: If the secondary of the i.f.t. is centertapped, the second diode plate lead is green-

and-black striped, and black is used for the center-tap lead.

A.F. Transformers

Blue — plate (finish) lead of primary.

Red — "B" + lead (this applies whether the primary is plain or center-tapped).

Brown - plate (start) lead on center-tapped primaries. (Blue may be used for this lead if polarity is not important.)

Green - grid (finish) lead to secondary.

Black - grid return (this applies whether the secondary is plain or center-tapped).

Yellow - grid (start) lead on center-tapped secondaries. (Green may be used for this lead if polarity is not important.)

Note: These markings apply also to line-togrid and tube-to-line transformers.

Power Transformers

1)	Primary LeadsBlack
	If tapped:
	CommonBlack
	TapBlack and Yellow Striped
	FinishBlack and Red Striped
2)	High-Voltage Plate WindingRed
	Center-TapRed and Yellow Striped
3)	Rectifier Filament WindingYellow

- Center-Tap......Yellow and Blue Striped
- 4) Filament Winding No. 1......Green Center-Tap.....Green and Yellow Striped
- 5) Filament Winding No. 2.....Brown Center-Tap....Brown and Yellow Striped
- 6) Filament Winding No. 3.....Slate Center-Tap......Slate and Yellow Striped

	TABLE 20-VI							
Brea	Breaking Load (Pounds) For Antenna Wire							
	Hard Drawn	Soft Drawn	Copperweld (40% conduct)					
No. 18	85		150					
16	135		250					
14	215	125	400					
12	335	200	710					
10	530	315	1130					

COPPER-WIRE TABLE

			T	urns per L	inear Inch	12	Turns	per Square	Inch2	Feel pe	r Lb.		Current		
Wire Size A.W.G. (B&S)	Diam. in Mils¹	Circular Mil Area	Enamel	S.S.C.4	D.S.C.	D.C.C.	s.c.c.	Enamel S.C.C.	D.C.C.	Bare	D.C.C.	Ohms per 1000 ft. 25° C.	Carrying Capacitys at 700 C.M. per Amp.	Diam. in mm.	Nearest British S.W.G. No.
1 2 3 4 5 6 7 8 9 10 11 12 13 14 15 16 17 18 19 20 21 22 23 24 25 26 27 28 29 30 31 33 33 33 33 36 36 37 38 38 39 40 30 30 30 30 30 30 30 30 30 30 30 30 30	289 .3 257 .6 229 .4 204 .3 181 .9 162 .0 144 .3 128 .5 114 .4 101 .9 90 .74 80 .81 71 .96 64 .08 57 .07 245 .26 40 .30 35 .89 31 .96 22 .57 20 .10 17 .90 15 .94 14 .20 15 .94 14 .20 15 .94 16 .20 17 .90 18 .928 7 .950 7 .080 6 .305 6 .305 6 .305 6 .305 6 .305 6 .305 7 .000 8 .928 7 .950 7 .080 6 .305 6 .305 6 .305 6 .305 6 .305 7 .000 8 .928 7 .950 7 .080 8 .928 7 .950 7 .080 8 .928 7 .950 7 .080 8 .928 8 .928 7 .050 8 .955 8 .9	83690 66370 52640 41740 33100 26250 20820 16510 13090 10380 8234 6530 5178 4107 3257 22583 2048 1624 1288 1022 810 1 642 4 1288 1022 810 1 5178 404 0 254 1 259 5 404 0 30 5 159 8 126 7 159 8 159 8 159 7 159 8 159 7 159 8 159 8 1								3.947 4.977 6.276 7.914 9.980 12.58 15.87 20.01 25.23 31.82 40.12 50.59 63.80 80.44 101.4 127.9 161.3 203.4 256.5 323.4 407.8 514.2 648.4 817.7 1031 1300 1639 2067 2607 3287 4145 6591 8310 10480 13210 106660 21010 20500 33410		.1264 .1593 .2009 .2533 .3195 .4028 .5080 .64028 .5080 .6402 .8077 1.018 1.284 1.619 2.042 2.575 3.247 4.094 5.163 6.510 8.210 10.35 13.05 16.46 20.76 26.17 33.00 41.62 52.48 66.17 83.44 1052 1026 1026 1026 1026 1026 1026 1026 102	119 . 6 94 . 8 75 . 2 59 . 6 47 . 3 37 . 5 29 . 7 14 . 8 11 . 8 9 . 33 7 . 40 5 . 87 4 . 65 3 . 69 2 . 93 2 . 32 1 . 84 1 . 46 1 . 16 9 . 18 2 . 36 3 . 36 9 . 33 2 . 32 2 . 32 1 . 84 1 . 46 1 . 16 9 . 18 9 . 33 2 . 32 2 . 32 2 . 32 1 . 84 1 . 46 1 . 146 1 . 144 1 . 146 1 . 144 1 . 144	7 .348 6 .544 5 .827 6 .621 4 .115 3 .665 3 .264 2 .588 2 .053 1 .828 1 .450 1 .150 1 .024 .9116 .8118 .7230 .6438 .5733 .5106 .4409 .3606 .4409 .3606 .2586 .2019 .2696 .2706 .2696 .2706	1 3 4 5 7 8 8 9 10 11 12 13 14 15 16 17 18 18 18 19 20 21 22 23 24 25 26 27 29 30 31 33 34 36 37 38 39 40 41 42 43 44

¹ A mil is 1/1000 (one-thousandth) of an inch. ² The figures given are approximate only, since the thickness of the insulation varies with different manufacturers. ³ 700 circular mils per ampere is a satisfactory design figure for small transformers, but values from 500 to 1000 C.M. are commonly used. For 1000 C.M./amp, divide the circular mil area (third column) by 1000; for 500 C.M./amp, divide circular mil area by 500, ⁴ Single silk-covered. ⁵ Double silk-covered. ⁷ Double cotton-covered.

Measurements

It is practically impossible to operate an amateur station without making measurements at one time or another. Although quite crude measurements often will suffice, more refined equipment and methods will yield more and better information. With adequate information at hand it becomes possible to adjust a piece of equipment for optimum performance quickly and surely, and to design circuits along established principles rather than depending on cut-and-try.

Measuring and test equipment is valuable during construction, for testing components before installation. It is practically indispensable in the initial adjustment of radio gear, not only for establishing operating values but also for tracing possible errors in wiring. It is likewise needed for locating breakdowns and defective components in existing equipment.

The basic measurements are those of current, voltage, and frequency. Determination of the values of circuit elements—resistance, inductance and capacitance — are almost equally important. The inspection of waveform in audio-frequency circuits is highly

useful. For these purposes there is available a wide assortment of instruments, both complete and in kit form; the latter, particularly, compare very favorably in cost with strictly home-built instruments and are frequently more satisfactory both in appearance and calibration. The home-built instruments described in this chapter are ones having features of particular usefulness in amateur applications, and not ordinarily available commercially.

In using any instrument it should always be kept in mind that the accuracy depends not only on the inherent accuracy of the instrument itself (which, in the case of commercially built units is usually within a few per cent, and in any event should be specified by the manufacturer) but also the conditions under which the measurement is made. Large errors can be introduced by failing to recognize the existence of conditions that affect the instrument readings. This is particularly true in certain types of r.f. measurements, where stray effects are hard to eliminate, and in the measurement of d.c. and a.c. voltages across extremely high-impedance circuits.

VOLTAGE, CURRENT, AND RESISTANCE

D.C. MEASUREMENTS

A direct-current instrument — voltmeter, ammeter, milliammeter or microammeter — is a device using electromagnetic means to deflect a pointer over a calibrated scale in proportion to the current flowing. In the D'Arsonval type a coil of wire, to which the pointer is attached, is pivoted between the poles of a permanent magnet, and when current flows through the coil it causes a magnetic field that interacts with that of the magnet to cause the coil to turn. The design of the instrument is usually such as to make the pointer deflection directly proportional to the current.

A less expensive type of instrument is the moving-vane type, in which a pivoted softiron vane is pulled into a coil of wire by the magnetic field set up when current flows through the coil. The farther the vane extends into the coil the greater the magnetic pull on it, for a given change in current, so this type of instrument does not have "linear" deflection—the intervals of equal current are crowded together at the low-current end and

spread out at the high-current end of the scale. The same basic instrument is used for measuring either current or voltage. Goodquality instruments are made with fairly high sensitivity — that is, they give full-scale pointer deflection with very small currents — when intended to be used as voltmeters. The sensitivity of instruments intended for measuring large currents can be lower, but a highly sensitive instrument can be, and frequently is, used for measurement of currents much greater than needed for full-scale deflection.

Panel-mounting instruments of the D'Arsonval type will give a smaller deflection when mounted on iron or steel panels than when mounted on nonmagnetic material. Readings may be as much as ten per cent low. Specially calibrated meters should be obtained for mounting on such panels.

VOLTMETERS

Only a fraction of a volt is required for full-scale deflection of a sensitive instrument (1 milliampere or less full scale) so for meas-

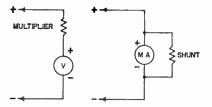


Fig. 21-1—How voltmeter multipliers and milliammeter shunts are connected to extend the range of a d.c.

uring voltage a high resistance is connected in series with it, Fig. 21-1. Knowing the current and the resistance, the voltage can easily be calculated from Ohm's Law. The meter is calibrated in terms of the voltage drop across the series resistor or multiplier. Practically any desired full-scale voltage range can be obtained by proper choice of multiplier resistance, and voltmeters frequently have several ranges selected by a switch.

The sensitivity of the voltmeter is usually expressed in "ohms per volt." A sensitivity of 1000 ohms per volt means that the resistance

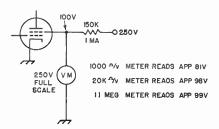


Fig. 21-2—Effect of voltmeter resistance on accuracy of readings. It is assumed that the d.c. resistance of the screen circuit is constant at 100 kilohms. The actual current and voltage without the voltmeter connected are 1 ma. and 100 volts. The voltmeter readings will differ because the different types of meters draw different amounts of current through the 150-kilohm resistor,

of the voltmeter is 1000 times the full-scale voltage, and by Ohm's Law the current required for full-scale deflection is 1 milliampere. A sensitivity of 20,000 ohms per volt, another commonly used value, means that the instrument is a 50-microampere meter. The higher the resistance of the voltmeter the more accurate the measurements in high-resistance circuits. This is because the current flowing through the voltmeter will cause a change in the voltage between the points across which the meter is connected, compared with the voltage with the meter absent, as shown in Fig. 21-2.

Multipliers

The required multiplier resistance is found by dividing the desired full-scale voltage by the current, in amperes, required for fullscale deflection of the meter alone. Strictly, the internal resistance of the meter should be subtracted from the value so found, but this is seldom necessary (except perhaps for very low ranges) because the meter resistance will be negligibly small compared with the multiplier resistance. An exception is when the instrument is already provided with an internal multiplier, in which case the multiplier resistance required to extend the range is

$$R = R_{\rm m}(n-1)$$

where R is the multiplier resistance, $R_{\rm m}$ is the total resistance of the instrument itself, and n is the factor by which the scale is to be multiplied. For example, if a 1000-ohms-per-volt voltmeter having a calibrated range of 0-10 volts is to be extended to 1000 volts, $R_{\rm m}$ is $1000 \times 10 = 10,000$ ohms, n is 1000/10 = 100, and R = 10,000(100 - 1) = 990,000 ohms.

If a milliammeter is to be used as a voltmeter, the value of series resistance can be found by Ohm's Law:

$$R = \frac{1000E}{I}$$

where E is the desired full-scale voltage and I the full-scale reading of the instrument in milliamperes.

Accuracy

The accuracy of a voltmeter depends on the calibration accuracy of the instrument itself and the accuracy of the multiplier resistors. Good-quality instruments are generally rated for an accuracy within plus or minus 2 per cent. This is also the usual accuracy rating of the basic meter movement.

When extending the range of a voltmeter or converting a low-range milliammeter into a voltmeter the rated accuracy of the instrument is retained only when the multiplier resistance is precise. Precision wire-wound resistors are used in the multipliers of high-quality instruments. These are relatively expensive, but the home constructor can do quite well with 1% tolerance composition resistors. They should be "derated" when used for this purpose — that is, the actual power dissipated in the resistor should not be more than 1/4 to 1/2 the rated dissipation and care should be used to avoid overheating the body of the resistor when soldering to the leads. These precautions will help prevent permanent change in the resistance of the unit.

Ordinary composition resistors are generally furnished in 10% or 5% tolerance ratings. If possible errors of this order can be accepted, resistors of this type may be used as multipliers. They should be operated below the rated power dissipation figure, in the interests of long-time stability.

MILLIAMMETERS AND AMMETERS

A microammeter or milliammeter can be used to measure currents larger than its full-scale reading by connecting a resistance

shunt across its terminals as shown in Fig. 21-1. Part of the current flows through the shunt and part through the meter. Knowing the meter resistance and the shunt resistance. the relative currents can easily be calculated.

The value of shunt resistance required for a given full-scale current range is given by

$$R = \frac{R_{\rm m}}{n-1}$$

where R is the shunt, R_m is the internal resistance of the meter, and n is the factor by which the original meter scale is to be multiplied. The internal resistance of a milliammeter is preferably determined from the manufacturer's catalog, but if this information is not available it can be measured by the method shown in Fig. 21-3. Do not attempt to use an ohmmeter to measure the internal

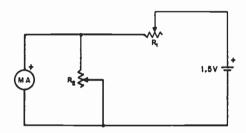


Fig. 21-3—Determining the internal resistance of a milliammeter or microammeter, R₁ is an adjustable resistor having a maximum value about twice that necessary for limiting the current to full scale with R2 disconnected; adjust it for exactly full-scale reading. Then connect R2 and adjust it for exactly half-scale reading. The resistance of R2 is then equal to the internal resistance of the meter, and the resistor may be removed from the circuit and measured separately. Internal resistances vary from a few ohms to several hundred ohms, depending on the sensitivity of the instrument.

resistance of a milliammeter; the instrument may be ruined by doing so.

Homemade milliammeter shunts can be constructed from any of the various special kinds of resistance wire, or from ordinary copper wire if no resistance wire is available. The Copper Wire Table in this Handbook gives the resistance per 1000 feet for various sizes of copper wire. After computing the resistance required, determine the smallest wire size that will carry the full-scale current (250 circular mils per ampere is a satisfactory figure for this purpose). Measure off enough wire to provide the required resistance. Accuracy can be checked by causing enough current to flow through the meter to make it read full scale without the shunt; connecting the shunt should then give the correct reading on the new range.

Current Measurement with a Voltmeter

A current-measuring instrument should have very low resistance compared with the resistance of the circuit being measured;

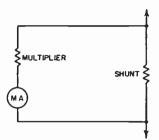


Fig. 21-4—Voltmeter method of measuring current. This method permits using relatively large values of resistance in the shunt, standard values of fixed resistors frequently being usable. If the multiplier resistance is 20 (or more) times the shunt resistance, the error in assuming that all the current flows through the shunt will not

be of consequence in most practical applications.

otherwise, inserting the instrument will cause the current to differ from its value with the instrument out of the circuit. (This may not matter if the instrument is left permanently in the circuit.) However, the resistance of many circuits in radio equipment is quite high and the circuit operation is affected little, if at all, by adding as much as a few hundred ohms in series. In such cases the voltmeter method of measuring current, shown in Fig. 21-4, is frequently convenient. A voltmeter - or lowrange milliammeter provided with a multiplier and operating as a voltmeter — having a full-scale voltage range of a few volts, is used to measure the voltage drop across a comparatively high resistance acting as a shunt. The formula previously given is used for finding the proper value of shunt resistance for a given scale-multiplying factor, R_m in this case being the multiplier resistance.

D.C. Power

Power in direct-current circuits is determined by measuring the current and voltage. When these are known, the power is equal to the voltage in volts multiplied by the cur-

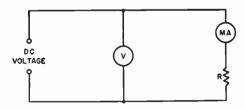


Fig. 21-5—Measuring resistance with a voltmeter and milliammeter. If the approximate resistance is known the voltage can be selected to cause the milliammeter, MA, to read about half scale. If not, additional resistance should be first connected in series with R to limit the current to a safe value for the milliammeter. The set-up then measures the total resistance, and the value of R can be found by subtracting the known additional resistance from the total.

rent in amperes. If the current is measured with a milliammeter, the reading of the instrument must be divided by 1000 to convert it to amperes.

RESISTANCE MEASUREMENTS

Measurement of d.c. resistance is based on measuring the current through the resistance when a known voltage is applied, then using Ohm's Law. A simple circuit is shown in Fig. 21-5. The internal resistance of the ammeter or milliammeter, MA, should be low compared with the resistance, R, being measured, since the voltage read by the voltmeter, V, is the voltage across MA and R in series. The instruments and the d.c. voltage should be chosen so that the readings are in the upper half of the scale, if possible, since the percentage error is less in this region.

An ohmmeter is an instrument consisting fundamentally of a voltmeter (or milliammeter, depending on the circuit used) and a small dry battery as a source of d.c. voltage, calibrated so the value of an unknown resistance can be read directly from the scale. Typical ohmmeter circuits are shown in Fig. 21-6. In the simplest type, shown in Fig. 21-6A, the meter and battery are connected in series with the unknown resistance. If a given deflection is obtained with terminals A-B shorted, inserting the resistance to be measured will cause the meter reading to decrease. When the resistance of the voltmeter is known, the following formula can be applied:

$$R = \frac{eR_m}{E} - R_m$$

where R is the resistance under measurement,
e is the voltage applied (A-B shorted),
E is the voltmeter reading with R connected, and

 $R_{\rm m}$ is the resistance of the voltmeter.

The circuit of Fig. 21-6A is not suited to measuring low values of resistance (below a hundred ohms or so) with a high-resistance voltmeter. For such measurements the circuit of Fig. 21-6B can be used. The milliammeter should be a 0-1 ma. instrument, and R_1 should be equal to the battery voltage, e, multiplied by 1000. The unknown resistance is

$$R = \frac{I_2 R_m}{I_1 - I_2}$$

where R is the unknown,


R_m is the internal resistance of the milliammeter,


I₁ is the current in ma. with R disconnected from terminals A-B, and

I₂ is the current in ma. with R connected.

The formula is approximate, but the error will be negligible if e is at least 3 volts so that R_1 is at least 3000 ohms.

A third circuit for measuring resistance is shown in Fig. 21-6C. In this case a highresistance voltmeter is used to measure the

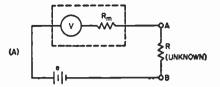

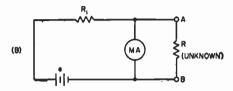

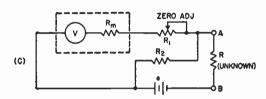


Fig. 21-6—Ohmmeter circuits. Values are discussed in the text.

voltage drop across a reference resistor, R2. when the unknown resistor is connected so that current flows through it, R2 and the battery in series. By suitable choice of R₂ (low values for low resistance, high values for high-resistance unknowns) this circuit will give equally good results on all resistance values in the range from one ohm to several megohms, provided that the voltmeter resistance, $R_{\rm m}$, is always very high (50 times or more) compared with the resistance of R_2 . A 20,000-ohms-per-volt instrument (50-μamp. movement) is generally used. Assuming that the current through the voltmeter is negligible compared with the current through R. the formula for the unknown is

$$R = \frac{eR_2}{E} - R_2$$

where R and R₂ are as shown in Fig. 21-6C, e is the voltmeter reading with A-B shorted, and

E is the voltmeter reading with R connected.

The "zero adjuster," R₁, is used to set the voltmeter reading exactly to full scale when the meter is calibrated in ohms. A 10,000-ohm variable resistor is suitable with a 20,000-ohms-per-volt meter. The battery voltage is usually 3 volts for ranges up to 100,000 ohms or so and 6 volts for higher ranges.

A. C. Measurements

Several types of instruments are available for measurement of low-frequency alternating currents and voltages. The better-grade panel 516 MEASUREMENTS

instruments for power-line frequencies are of the dynamometer type. This compares with the D'Arsonval movement used for d.c. measurements, but instead of a permanent magnet the dynamometer movement has a field coil which, together with the moving coil, is connected to the a.c. source. Thus the moving coil is urged to turn in the same direction on both halves of the a.c. cycle.

Moving-vane type instruments, described earlier, also are used for a.c. measurements. This is possible because the pull exerted on the vane is in the same direction regardless of the direction of current through the coil. The calibration of a moving-vane instrument on a.c. will, in general, differ from its d.c. calibration.

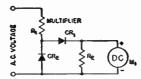


Fig. 21-7—Rectifier-type a.c. voltmeter circuit, with "linearizing" resistor and diode for back-current correction.

For measurements in the audio-frequency range, and in applications where high impedance is required, the rectifier-type a.c. instrument is generally used. This is essentially a sensitive d.c. meter, of the type previously described, provided with a rectifier for converting the a.c. to d.c. A typical rectifier-type voltmeter circuit is shown in Fig. 21-7. The half-wave meter rectifier, CR_1 , is frequently of the copper-oxide type, but crystal diodes can be used. Such a rectifier is not "perfect"

— that is, the application of a voltage of reversed polarity will result in a small current flow — and so CR_2 is used for eliminating the effect of reverse current in the meter circuit. It does this by providing a low-resistance path across CR_1 and the meter during the a.c. alternations when CR_1 is not conducting.

Resistor R_2 shunted across M_1 is used for improving the linearity of the circuit. The effective resistance of the rectifier decreases with increasing current, leading to a calibration scale with nonuniform divisions. This is overcome to a considerable extent by "bleeding" several times as much current through R_2 as flows through M_1 so the rectifier is always carrying a fairly large current.

Because of these expedients and the fact that with half-wave rectification the average current is only 0.45 times the r.m.s. value of a sine wave producing it, the impedance of a rectifier-type voltmeter is rather low compared with the resistance of a d.c. voltmeter using the same meter. Values of 1000 ohms per volt are representative, when the d.c. instrument is a 0-200 microammeter.

The d.c. instrument responds to the average value of the rectified alternating current. This average current will vary with the shape of the a.c. wave applied to the rectifier, and so the meter reading will not be the same for different wave forms having the same maximum values or the same r.m.s. values. Hence a "wave-form error" is always present unless the a.c. wave is very closely sinusoidal. The actual calibration of the instrument usually is in terms of the r.m.s. value of a sine wave.

Modern rectifier-type a.c. voltmeters are capable of good accuracy, within the waveform limitations mentioned above, throughout the audio-frequency range.

Fig. 21-8—Vacuum-tube voltmeter circuit.

 C_{1r} , C_{3} =0.002- to 0.005- μ f. mica. C_{2} =0.01 μ f., 1000 to 2000 volts, paper or mica.

C₄-16 μf. electrolytic, 150 volts.

CR₁-400 p.i.v. rectifier.

R₁—1 megohm, ½ watt.

 R_2 to R_6 , inc.—To give desired voltage ranges, totaling 10 megohms.

 R_6 , R_7 —2 to 3 megohms.


R_s-10,000-ohm variable.

R₉, R₁₀-2000 to 3000 ohms.

R11-5000- to 10,000-ohm control.

 R_{12} —10,000 to 50,000 ohms.

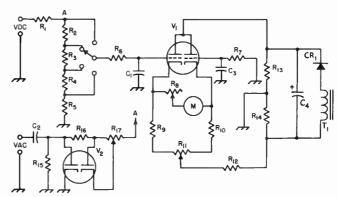R₁₈, R₁₄—App. 25,000 ohms. A 50,000-ohm slider-type wire-wound can be used.



R₁₅-10 megohms.

R₁₆-3 megohms.

R₁₇—10-megohm variable.

T₁-130-volt 15-ma. transformer (only secondary shown).

M-0-200 μ amp. to 0-1 ma. range.

V₁—Dual triode, 12AU7.

V2-Dual diode, 6AL5.

COMBINATION INSTRUMENTS— THE V.O.M.

Since the same basic instrument is used for measuring current, voltage and resistance, the three functions can readily be combined in one unit using a single meter. Various models of the "v.o.m." (volt-ohm-milliammeter) are available commercially, both completely assembled and in kit form. The less expensive ones use a 0-1 milliammeter as the basic instrument, providing voltmeter ranges at 1000 ohms per volt. The more elaborate meters of this type use a microammeter-0-50 microamperes, frequently-with voltmeter resistances of 20,000 ohms per volt. With the more sensitive instruments it is possible to make resistance measurements in the megohms range. A.c. voltmeter scales also are frequently included.

The v.o.m., even a very simple one, is among the most useful instruments for the amateur. Besides current and voltage measurements, it can be used for checking continuity in circuits, for finding defective components before installation — shorted capacitors, open or otherwise defective resistors, etc. — shorts or opens in wiring, and many other checks that, if applied during the construction of a piece of equipment, save much time and trouble. It is equally useful for servicing, when a component fails during operation.

THE VACUUM-TUBE VOLTMETER

The usefulness of the vacuum-tube voltmeter (v.t.v.m.) is based on the fact that a vacuum tube can amplify without taking power from the source of voltage applied to its grid. It is therefore possible to have a voltmeter of extremely high resistance, and thus take negligible current from the circuit under measurement, without using a d.c. instrument of exceptional sensitivity.

The v.t.v.m. has the disadvantage that it requires a source of power for its operation, as compared with a regular d.c. instrument. Also, it is susceptible to r.f. pick-up when working around an operating transmitter, unless well shielded and filtered. The fact that one of its terminals is grounded is also disadvantageous in some cases, since a.c. readings in particular may be inaccurate if an attempt is made to measure a circuit having both sides "hot" with respect to ground. Nevertheless, the high resistance of the v.t.v.m. more than compensates for these disadvantages, especially since in the majority of measurements they do not apply.

While there are several possible circuits, the one commonly used is shown in Fig. 21-8. A dual triode, $V_{i,j}$ is arranged so that, with no voltage applied to the left-hand grid, equal currents flow through both sections. Under this condition the two cathodes are at the same potential and no current flows through M. The currents can be adjusted to balance

by potentiometer R_{11} , which takes care of variations in the tube sections and in the values of cathode resistors R_0 and R_{70} . When a positive d.c. voltage is applied to the left-hand grid the current through that tube section increases, so the current balance is upset and the meter indicates. The sensitivity of the meter is regulated by R_0 , which serves to adjust the calibration. R_{12} , common to the cathodes of both tube sections, is a feed back resistor that stabilizes the system and makes the readings linear. R_0 and C_1 form a filter for any a.c. component that may be present, and R_0 is balanced by R_7 connected to the grid of the second tube section.

To stay well within the linear range of operation the scale is limited to 3 volts or less in the average commercial instrument. Higher ranges are obtained by means of the voltage divider formed by R_1 to R_5 , inclusive. As many ranges as desired can be used. Common practice is to use 1 megohm at R_1 , and to make the sum of R_2 to R_5 , inclusive, 10 megohms, thus giving a total resistance of 11 megohms, constant for all voltage ranges. R_1 should be at the probe end of the d.c. lead to minimize capacitive loading effects when measuring d.c. voltages in r.f. circuits.

Values to be used in the circuit depend considerably on the supply voltage and the sensitivity of the meter, M. R_{19} , and R_{15} — R_{16} , should be adjusted by trial so that the voltmeter circuit can be brought to balance, and to give full-scale deflection on M with about 3 volts applied to the left-hand grid. The meter connections can be reversed to read voltages that are negative with respect to ground.

A.C. Voltage

For measuring a.c. voltages up to 4 Mc., the rectifier circuit in the lower left of Fig. 21-8 is used. One diode of V_2 is a half-wave rectifier and the other acts as a balancing device, adjustable by R_{17} , against contact potential effects that would cause a residual d.c. voltage to appear at the v.t.v.m. grid.

The rectifier output voltage is proportional to the peak amplitude of the a.c. wave, rather than to the average or r.m.s. values. Since the positive and negative peaks of a complex wave may not have equal amplitudes, a different reading may be obtained on such wave forms when the voltmeter probe terminals are reversed. This "turnover" effect is inherent in any peak-indicating device, but is not necessarily a disadvantage. The fact that the readings are not the same when the voltmeter connections are reversed is an indication that the wave form under measurement is unsymmetrical. In some measurements, as in audio amplifiers, a peak measurement is more useful than an r.m.s. or average-value measurement because amplifier capabilities are based on the peak amplitudes.

The scale calibration usually is based on the r.m.s. value of a sine wave, R_8 being set so

518 MEASUREMENTS

that the same scale can be used either for a.c. or d.c. The r.m.s. reading can easily be converted to a peak reading by multiplying by 1.41.

INSTRUMENT CALIBRATION

When extending the range of a d.c. instrument, calibration usually is necessary - although resistors for voltmeter multipliers often can be purchased to close-enough tolerances so that the new range will be accurately known. However, in calibrating an instrument such as a v.t.v.m. a known voltage must be available to provide a starting point. Fresh dry cells have an open-circuit terminal voltage of approximately 1.6 volts, and one or more of them may be connected in series to provide several calibration points on the low range. Gas regulator tubes in a power supply, such as the 0C3, 0D3, etc., also provide a stable source of voltage whose value is known within a few per cent. Once a few such points are determined the voltmeter ranges may be extended readily by adding multipliers or a voltage divider as appropriate.

Shunts for a milliammeter may be adjusted by first using the meter alone in series with a source of voltage and a resistor selected to limit the current to full scale. For example, a 0-1 milliammeter may be connected in series with a dry cell and a 2000-ohm variable resistor, the latter being adjusted to allow exactly 1 milliampere to flow. Then the shunt is added across the meter and its resistance adjusted to reduce the meter reading by exactly the scale factor, n. If n is 5, the shunt would be adjusted to make the meter read 0.2 milliampere, so the full-scale current will be 5 ma. Using the new scale, the second shunt is added to give the next range, the same procedure being followed. This can be carried on for several ranges, but it is advisable to check the meter on the highest range against a separate meter used as a standard, since the errors in this process tend to be cumulative.

MEASUREMENT OF FREQUENCY

ABSORPTION FREQUENCY METERS

The simplest possible frequency-measuring device is a resonant circuit, tunable over the desired frequency range and having its tuning dial calibrated in terms of frequency. It operates by extracting a small amount of energy from the oscillating circuit to be measured, the frequency being determined by the tuning setting at which the energy absorption is maximum (Fig. 21-9).

Such an instrument is not capable of very

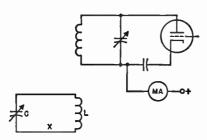


Fig. 21-9—Absorption frequency meter and a typical application. The meter consists simply of a calibrated resonant circuit LC. When coupled to an amplifier or oscillator the tube plate current will rise when the frequency meter is tuned to resonance. A flashlight lamp may be connected in series at X to give a visual indication, but it decreases the selectivity of the instrument and makes it necessary to use rather close coupling to the circuit being measured.

high accuracy, because the Q of the tuned circuit cannot be high enough to avoid uncertainty as to the exact dial setting and because any two coupled circuits interact to some ex-

tent and change each others' tuning. Nevertheless, the absorption frequency meter or "wavemeter" is a highly useful instrument. It is compact, inexpensive, and requires no power supply. There is no ambiguity in its indications, as is frequently the case with the heterodyne-type instruments.

When an absorption meter is used for checking a transmitter, the plate current of the tube connected to the circuit being checked can provide the necessary resonance indication. When the frequency meter is loosely coupled to the tank circuit the plate current will give a slight upward flicker as the meter is tuned through resonance. The accuracy is greatest when the loosest possible coupling is used.

A receiver oscillator may be checked by tuning in a steady signal and heterodyning it to give a beat note as in ordinary c.w. reception. When the frequency meter is coupled to the oscillator coil and tuned through resonance the beat note will change. Again, the coupling should be made loose enough so that a just-perceptible change in beat note is observed.

An approximate calibration for the meter, adequate for most purposes, may be obtained by comparison with a calibrated receiver. The usual receiver dial calibration is sufficiently accurate. A simple oscillator circuit covering the same range as the frequency meter will be useful in calibration. Set the receiver to a given frequency, tune the oscillator to zero beat at the same frequency, and adjust the frequency meter to resonance with the oscillator as described above. This gives one calibration point. When a sufficient number of such points has been obtained a graph may be

Frequency 519

drawn to show frequency vs. dial settings on the frequency meter.

INDICATING FREQUENCY METERS

The plain absorption meter requires fairly close coupling to the oscillating circuit in order to affect the plate current of a tube sufficiently to give a visual indication. However, by adding a rectifier and d.c. microammeter or milliammeter, the sensitivity of the instrument can be increased to the point where very loose coupling will suffice for a good reading. A typical circuit for this purpose is given in Fig. 21-10, and Figs. 21-11 and 21-12 show how such an instrument can be constructed.

The rectifier, a crystal diode, is coupled to the tuned circuit L_1C_1 through a coupling coil, L₂, having a relatively small number of turns. The step-down transformer action from L_1 to L₂ provides for efficient energy transfer from the high-impedance tuned circuit to the lowimpedance rectifier circuit. The number of turns on L₂ can be adjusted for maximum reading on the d.c. milliammeter; when doing this, use a fixed value of coupling between L_1 and the source of energy. The proper number of turns for this purpose will depend on the sensitivity of M_1 . The coil dimensions given in Fig. 21-10 are for a 0-500 microammeter but will also be satisfactory for a 0-1 milliammeter. Less than optimum coupling is preferable, in most cases, since heavy loading lowers the Q of the tuned circuit L_1C_1 and makes it less selective. The coupling is reduced by reducing the number of turns on L₂.

The meter can be used with a pick-up loop and coaxial line connected to J_1 . Energy picked up by the loop is fed through the cable to L_2 and thence coupled to L_1C_1 . This is a convenient method of coupling to circuits where it would be physically difficult to secure inductive coupling to L_1 . The pick-up cable should not be self-resonant, as a transmission-line section, at any frequency within the range in which it is to be used, so two cable lengths are provided. The longer one is

Fig. 21-11—The indicating frequency meter, plug-in coils, and pick-up cables. The meter is built in a bakelite meter case measuring 6½ × 3½ × 2 inches. The 3-inch dial is cut from a piece of aluminum and has a paper hand-calibrated scale cemented on. Hairline indicators are clear plastic mounted on small metal pillars. A 2-inch d.c. instrument is used. Pick-up loops are one turn of No. 14, spaghetti covered, soldered to the ends of the cables. The longer cable (5 feet) is useful to 30 Mc.; the shorter (13 inches) can be used for the full frequency range.

Both are RG-58/U.

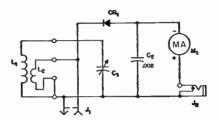


Fig. 21-10—Circuit diagram of indicating frequency meter.

 C_1 -50- $\mu\mu$ f. variable (Johnson 50R12).

C₂-0.002-\mu f. disk ceramic.

CR₁—General purpose germanium diode (1N34, etc.)

J₁--Phono jack.

J2-Closed-circuit phone jack.

M₁-D.c. microammeter or 0-1 milliammeter.

	Coil [Coil Data				
Freq. Range	Turns, Lı	Turns, La	Length, In.			
3-6 Mc.	60	5	close-wound			
6-12 Mc.	29	5	11/4			
12-25 Mc.	13	2	1			
23-50 Mc.	51/4	1	1/2			
50-100 Mc.	11/2	1/2	1/4			
90-225 Mc.	See below					

All except 90–225-Mc. coil wound with No. 24 enam. wire on 1-inch diameter 4-prong forms (Millen 45004). L_2 interwound at bottom of L_1 , using smaller wire where necessary. The 90–225-Mc. coil consists of a hairpin loop of No. 14 tinned wire just clearing the bottom of the coil form, which is cut to $\frac{1}{2}$ -inch length. L_2 is a similar harpin of No. 16 wire bent over so it almost touches L_2 .

useful up to 30 Mc. and the shorter at all frequencies up to the maximum useful frequency of the instrument (225 Mc.).

By plugging a headset into the output jack (phones having 2000 ohms or greater resistance should be used for greatest sensitivity) the frequency meter can be used as a monitor for modulated transmissions.

The bakelite case is a desirable feature since the instrument can be brought close to circuits being checked without the danger of



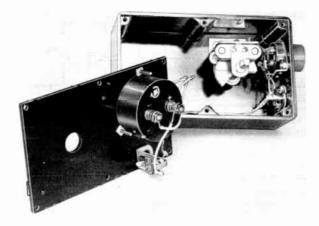


Fig. 21-12—Inside the wavemeter. Only the milliammeter and phone jack are mounted on the removable panel. The tuning capacitor is mounted vertically on an aluminum bracket fastened to the bottom of the case. The crystal diode is mounted between a coil-socket prong and a tie point. The phono lack for the pick-up cables is of the lower right.

short-circuiting any of their wiring. This could occur with a metal-cased unit.

In addition to the uses mentioned earlier, a meter of this type may be used for final adjustment of neutralization in r.f. amplifiers. For this purpose the pick-up loop may be loosely coupled to the plate tank coil. In this case L_1 may be removed from its socket and the meter used as an untuned rectifier. This reduces the sensitivity and insures that the r.f. pickup is only from the tank coil to which the loop is closely coupled.

THE SECONDARY FREQUENCY STANDARD

The secondary frequency standard is a highly stable low-power oscillator generating a fixed frequency, usually 100 kc. It is nearly always crystal-controlled, and inexpensive 100-kc. crystals are available for the purpose. Since the harmonics are multiples of 100 kc. throughout the spectrum, some of them can be compared directly with the standard frequencies transmitted by WWV.

The edges of most amateur bands also are exact multiples of 100 kc., so it becomes possible to determine the band edges very accurately. This is an important consideration in amateur frequency measurement, since the only regulatory requirement is that an amateur transmission be inside the assigned band, not on a specific frequency.

Frequency Standard with Harmonic Amplifier

The frequency standard circuit shown in Fig. 21-13 includes a tuned amplifier to increase the strength of the higher harmonics, and incorporates a crystal-diode sawtooth generator to make the harmonic strength reasonably uniform throughout the usable frequency spectrum of the instrument. It will produce useful calibration signals at 100-kc. intervals up to about 60 Mc. The strength of a particular harmonic may be peaked up by selecting the proper amplifier tuning range with S_2 and adjusting C_4 .

The 100-kc. oscillator uses the triode section of a 6AN8, while the amplifier uses the pentode section of the same tube. Power required for the unit is 150 volts at 10 ma. and 6.3 volts at 0.45 amp. This may be taken from the accessory socket of a receiver, or a special supply easily can be made using a TV "booster" transformer (such as the Merit P-3046 or equivalent).

The standard is built in a $4 \times 5 \times 6$ inch chassis-type box (Fig. 21-14). R_2 and S_2 are mounted on the panel, with the amplifier plate coils mounted on S_2 . The remaining components are mounted on the chassis, C_4 being insulated from it because its plates are above ground for d.c. For the same reason, an insulated shaft extension is used for front-panel control of C_4 .

Connection between the standard and the receiver can be made through a wire from the hot terminal of J_1 to the antenna input post on the receiver. Depending on how well the receiver is shielded, such a wire may not be needed at the lower-frequency end of the range.

Adjusting to Frequency

The frequency can be adjusted exactly to 100 kc. by making use of the WWV transmissions tabulated later in this chapter. Select the WWV frequency that gives a good signal at your location at the time of day most convenient. Tune it in with the receiver b.f.o. off and wait for the period during which the modulation is absent. Then switch on the 100kc. oscillator and adjust its frequency, by means of C_1 , until its harmonic is in zero beat with WWV. The exact setting is easily found by observing the slow pulsation in background noise as the harmonic comes close to zero beat, and adjusting to where the pulsation disappears or occurs at a very slow rate. The pulsation can be observed even more readily by switching on the receiver's b.f.o., after approximate zero beat has been secured. and observing the rise and fall in intensity (not frequency) of the beat tone. For best

results the WWV signal and the signal from the 100-kc. oscillator should be about the same strength. It is advisable not to try to set the 100-kc. oscillator during the periods when the WWV signal is tone-modulated, since it is difficult to tell whether the harmonic is being adjusted to zero beat with the carrier or with a sideband.

Using the Standard

Basically, the 100-kc. standard provides a means for indicating the exact receiver dial settings at which frequencies that are multiples of 100 kc. are to be found. The harmonics of the standard can thus be used to check the dial calibration of a receiver, and many of the better-grade communications receivers either include a 100-kc. oscillator for this purpose or have provision for installing one as an accessory. The actual frequency of at least one 100-kc. point in a given amateur band must be known, of course, but this is generally an easy matter since the activity in amateur bands usually makes identification of the band-edge "marker signal" quite simple. After one frequency is known, the consecutive 100-kc. harmonic signals are simply counted off from it.

Although the 100-kc. standard does not make possible the exact measurement of a frequency, it is readily possible to determine whether or not the signal is in a particular 100-kc. segment. If the unknown signal tunes in between, say, 21,200 and 21,300 kc., as indicated by the marker signals in the receiver, its frequency obviously lies between those two figures. For purposes of complying with the amateur regulations it is usually sufficient to know that the signal is above, or below,

some specified 100-kc. point, since the edges of the amateur bands or sub-bands usually are at such points. If a closer measurement is desired a fairly good estimate usually can be made by counting the number of dial divisions between two 100-kc. points and dividing the number into 100 to find how many kilocycles there are per dial division.

In using the receiver to check one's own transmitting frequency it is necessary to take special precautions to reduce the strength of the signal from the transmitter to the point where it does not overload the receiver nor create spurious responses that could be taken for the actual signal. This invariably means that the receiving antenna must be disconnected from the receiver, and it may be necessary, in addition, to short-circuit the receiver's antenna input terminals. Try to reduce stray pickup to such an extent that the transmitter's signal is no stronger than normal incoming signals at the regular gain-control settings. With some receivers this may require additional shielding around the signalfrequency circuits, and perhaps filtering of the a.c. and speaker leads where they leave the chassis, to prevent energy picked up on these leads from getting into the front end of the receiver.

More Precise Methods

The methods described above are quite adequate for the primary purpose of amateur frequency measurements — that is, determining whether or not a transmitter is operating inside the limits of an amateur band, and the approximate frequency inside the band. For measurement of an unknown frequency to a high degree of accuracy more advanced meth-

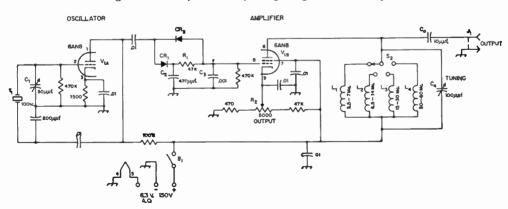


Fig. 21-13—Circuit of the 100-kc. crystal calibrator. Unless otherwise indicated, capacitances are in μf., resistances are in ohms, resistors are ½ watt.

C₁—50- $\mu\mu$ f. midget variable (Hammarlund MAPC-50), C₄—100- $\mu\mu$ f. variable (Hammarlund HF-100).

CR1, CR2-1N34A.

J₁—Phono jack.

L₁-3.5-7 Mc., 10 μh. (National R-33 r.f. choke). L₂-6.5-14 Mc., 4.7 μh. (IRC type CL-1 r.f. choke). L₈-15-30 Mc., 1.0 μh. (IRC type CL-1 r.f. choke). L₄—30–60 Mc., 0.22 µh.; 4 turns No. 20 plastic-insulated wire, %-inch diam.


R₂-5000-ohm potentiometer (Mallory U-14).

S₁—S.p.s.t., mounted on R₂ (Mallory US-26).

S₂—1-section, 1-pole, 4-position miniature phenolic rotary switch (Centralab PA-1000),


Y1-100-kc. crystal.

STANDARD FREQUENCIES AND TIME SIGNALS

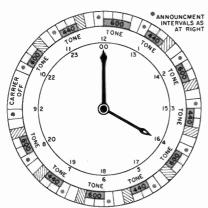

The Central Radio Propagation Laboratory of the National Bureau of Standards maintains two radio transmitting stations, WWV near Washington, D.C., and WWVH at Puunene, T.H., for broadcasting standard radio frequencies of high accuracy. WWV broadcasts are on 2.5, 5, 10, 15, 20 and 25 megacycles per second, and those from WWVH are on 5, 10, and 15 Mc. The radio-frequency signals are modulated by pulses at 1 cycle per second, and also by standard audio frequencies alternating between 440 and 600 c.p.s.

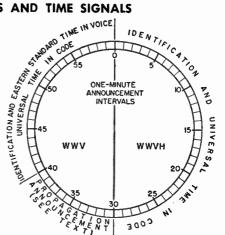Transmissions are continuous, with the following exceptions: The WWV transmissions are interrupted for a 4-minute period beginning at approximately 45 minutes after the hour, as indicated above; the



WWVH transmissions are interrupted for a 3-minute period beginning approximately 10 seconds after the hour and each 15 minute interval thereafter. WWVH is also silent each day for a 34-minute period beginning at 1900 Universal Time.

Accuracy

Transmitted frequencies are accurate within 1 part in 100 million. The WWV transmissions are generally stable to 1 part in a billion in any given day, although this is not guaranteed. Frequencies are based on an atomic standard, and daily corrections to the transmitted frequencies are subsequently published each month in the Proceedings of the IRE.

Time Signals

The 1-c.p.s. modulation is a 5-millisecond pulse at intervals of precisely one second, and is heard as a tick. The pulse transmitted by WWV consists of 5 cycles of 1000 cycle tone; that transmitted by WWVH consists of 6 cycles of 1200-cycle tone. On the WWV transmissions, the 440- or 600-cycle tone is blanked out beginning 10 milliseconds before and ending 25 milliseconds after the pulse. On the WWVH transmissions, the pulse is superimposed on the tone. The pulse on the 59th second is omitted, and for additional identification the zero-second pulse is followed by another 100 milliseconds later. On WWV during the minutes identified by coarse cross-hatching (above) a high-speed pulse code is transmitted, giving the time of day and the accuracy of the time. It sounds like an erratic "buzz."

Propagation Notices

During the announcement intervals at 19½ and 49½ minutes after the hour, propagation notices applying to transmission paths over the North Atlantic are transmitted from WWV on 2.5, 5, 10, 15, 20, and 25 Mc. Similar forecasts for the North Pacific are transmitted from WWVH during the announcement intervals at 9 and 39 minutes after the hour.

These notices, in telegraphic code, consist of the letter N, W, or U followed by a number. The letter designations apply to propagation conditions as of the time of the broadcast, and have the following significance:

W — Ionospheric disturbance in progress or expected. U - Unstable conditions, but communication possible with high power.

N - No warning.

The number designations apply to expected propagation conditions during the subsequent 12 hours and have the following significance:

1—impossible; 2—very poor; 3—poor; 4—fair to poor; 5—fair; 6—fair to good; 7—good; 8—very good; 9—excellent.

Special IGY Transmissions

The special broadcasts instituted during the International Geophysical Year may be continued through part or all of 1962. These broadcasts include information on IGY "Alerts" and "Special World Intervals." The broadcasts from WWV are at 4½ and 34½ minutes past the hour and those from WWVH are at 14 and 44 minutes past the hour. Each such transmission is preceded by the letters "AGI" in International Morse Code. The code used for the information is as follows:

5 A's — State of alert. 5 E's — No state of alert.

5 S's — Special World Interval begins at 0001 Z the following day.


5 T's — Special World Interval terminates at 2359Z. 3 long dashes — Special World Interval in progress.

CHU

CHU, the Canadian time-signal station, transmits on 3330.0, 7335.0 and 14,670.0 kc. Voice announcement of the minute is made each minute; the 29th second time tick is omitted.

Fig. 21-14—A 100-kc, frequency standard and harmonic amplifier. The crystal in this unit is in the metal-tube type envelope. Power and r.f. output connections are taken through the rear chassis lip.

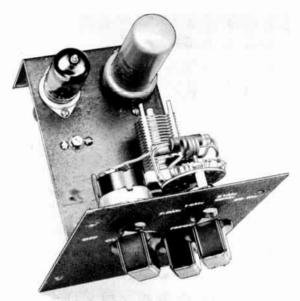The crystal diodes, CR_1 and CR_2 , are mounted on a tie-point strip underneath the chassis. The shaft of C_1 can be seen in front of the vacuum tube.



ods can be used. Accurate signals at closer intervals can be obtained by using a multivibrator in conjunction with the 100-kc. standard, and thus obtaining signals at intervals of, say, 10 kc. or some other integral divisor of 100. Temperature control is frequently used on the 100-kc. oscillator to give a high order of stability (Collier, "What Price Precision?", *QST*, September and October, 1952). Also, the secondary standard can be

used in conjunction with a variable-frequency interpolation oscillator to fill in the standard intervals (Woodward, "A Linear Beat-Frequency Oscillator for Frequency Measurement," QST, May, 1951). An interpolation oscillator and standard can be combined in one instrument to give signals throughout the spectrum. One application of this type was described in QST for May, 1949 (Grammer, "The Additive Frequency Meter").

TEST OSCILLATORS AND SIGNAL GENERATORS

THE GRID-DIP METER

The grid-dip meter is a simple vacuum-tube oscillator to which a microammeter or lowrange milliammeter has been added for reading the oscillator grid current. A 0-1 milliammeter is sensitive enough in most cases. The grid-dip meter is so called because if the oscillator is coupled to a tuned circuit the grid current will show a decrease or "dip" when the oscillator is tuned through resonance with the unknown circuit. The reason for this is that the external circuit will absorb energy from the oscillator when both are tuned to the same frequency; the loss of energy from the oscillator circuit causes the feed-back to decrease and this in turn is accompanied by a decrease in grid current. The dip in grid current is quite sharp when the circuit to which the oscillator is coupled has reasonably high Q.

The grid-dip meter is most useful when it covers a wide frequency range and is compactly constructed so that it can be coupled to circuits in hard-to-reach places such as in a transmitter or receiver chassis. It can thus be used to check tuning ranges and to find unwanted resonances

of the type described in the chapter on TVI. Since it is its own source of r.f. energy it does not require the circuit being checked to be energized. In addition to resonance checks, the grid-dip meter also can be used as a signal source for receiver alignment and, as described later in this chapter, is useful in measurement of inductance and capacitance in the range of values used in r.f. circuits.

The grid-dip meter shown in Fig. 21-15 is representative, although this particular unit has a higher frequency limit than similar inexpensive units. It uses the 6CW4 (Nuvistor) triode for the oscillator, and it can be used with the power supply and metering circuit shown in Fig. 21-18.

Referring to the circuit in Fig. 21-16, a resistor, R_2 , is plugged in with each coil (the resistor is mounted in the coil form). It forms a voltage divider with the normal grid leak, R_1 , and brings the metering circuit into the best range for the transistor booster.

The construction of the meter is straightforward; a small aluminum bracket supports the

524 MEASUREMENTS

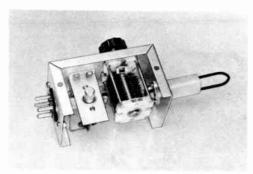


Fig. 21-15-Grid-dip meter covering the range 1.7 to 275 Mc., with the 90-165 Mc. coil in place. The power supply and transistor meter booster are a separate unit (see Fig. 21-17). The split-stator tuning capacitor is made from a single-stator variable. The Nuvistor tube socket is mounted on a small bracket, and a tie point under the bracket supports associated capacitors and resistors that aren't supported by socket and tuningcapacitor terminals.

Nuvistor socket within the $2\frac{1}{4} \times 2\frac{1}{4} \times 4$ -inch Minibox that is used as a housing. A 5-pin socket (Amphenol 78-S5S) is mounted at one end of the Minibox, and the variable capacitor stator leads are soldered directly to two of the pins. Coils in the low-frequency ranges are wound with enameled wire on 34-inch diameter forms. In the intermediate ranges coil stock (B&W Miniductor) is mounted inside the coil forms, with one end of the coil close to the open end of the form, for ease in coupling. The two highest-range coils are hairpin loops of No. 14 wire, covered with insulation as a safety precaution. In every case the associated Ra is mounted in the coil form. The highest range requires that only the base of the coil form be used, since the loop is shorter than the form.

The power supply for the grid-dip meter may be included with the oscillator, but since this increases the bulk and weight a separate supply is often desirable. The power supply shown in Fig. 21-18 uses a miniature power transformer with a silicon rectifier and a simple filter to give approximately 120 volts for the oscillator plate. It also uses a transistor booster for the meter because it was designed for use with a u.h.f. grid-dip meter. A supply to be used with only the unit of Fig. 21-15 could eliminate the transistor by using a 0-1 milliammeter between lead 3 of P_1 and chassis ground. In this case R_2 could also be eliminated, and the B+ for pin 4 of P1 should be derived from the arm of a 0.1-megohm potentiometer connected across the power supply. The adjustable plate voltage source is necessary to bring the grid current into the range of the meter.

The instrument may be calibrated by listening to its output with a calibrated receiver. The calibration should be as accurate as possible, although "frequency-meter accuracy" is not required in the applications for which a grid-dip meter is useful.

The grid-dip meter may be used as an indicating-type absorption wavemeter by shutting off the plate voltage and using the grid and cathode of the tube as a diode. However, this type of circuit is not as sensitive as the crystaldetector type shown earlier in this chapter, because of the high-resistance grid leak in series with the meter.

In using the grid-dip meter for checking the resonant frequency of a circuit the coupling should be set to the point where the dip in grid current is just perceptible. This reduces interaction between the two circuits to a minimum and gives the highest accuracy. With too-close coupling the oscillator frequency may be "pulled" by the circuit being checked, in which case different readings will be obtained when resonance is approached from the high-frequency side as compared with approaching from the low side.

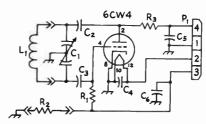


Fig. 21-16—Circuit diagram of the grid-dip meter. C_1 -50 $\mu\mu$ f. per section (Johnson 167-11 with stator bars sawed between 6th and 7th plates).

 C_2 , C_3 —100- $\mu\mu$ f, ceramic.

 C_4 , C_5 , C_6 —0.001- μ f. disk ceramic.

P₁-4-pin chassis plug (Amphenol 86-CP4).

R₁-47,000 ohms, ½ watt.

R₂—See table below.

R₃-1.000 ohms.

Range	L ₁	Ra
1.7-3.2 Mc.	195 turns No. 34 enam.*	680
2.7-5.0	110 turns No. 30 enam.*	470
4.4-7.8	51½ turns No. 30 enam.*	470
7.5-13.2	24½ turns No. 30 enam.*	470
12-22	31 t. No. 24 (B&W 3004)**	1000
20-36	14 t. No. 24 (B&W 3004)**	680
33-60	8½ t. No. 20 (B&W 3003)***	680
54-99	3% t. No. 20 (B&W 3003)***	1000
90-165	3%-inch loop No. 14, ½-inch separation	1500
150-275	1¼-inch loop No. 14, ¼-inch separation	3300

*Wound on 34-inch diameter polystyrene form (Allied *Wound 6..., Radio 71 H 723). ***16 t.p.i.

U.H.F. Grid-Dip Oscillator

The range of the grid-dip meter shown in Fig. 21-17 is from 275 to 725 Mc., a higher range than any of the inexpensive meters now available. It is able to cover these high frequencies by virtue of the 6CW4 (Nuvistor) tube and the series-tuned circuit. Unfortunately the series-tuned circuit becomes impractical with

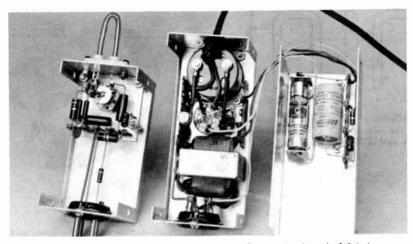


Fig. 21-17—Grid-dip meter for the 300- to 700-Mc. range. The oscillator section is at the left in its own case, and the power supply plus transistorized indicator is at the center and right. In the oscillator section, the 6CW4 (Nuvistor) socket is to the left of the tuning capacitor.


this tube at lower frequencies, and to cover the lower frequencies the circuit of Fig. 21-16 must be used. The u.h.f. grid-dip oscillator uses a transistor amplifier to amplify the changes across the unusually-low value of grid resistor. The low value of grid resistor is required because higher values will cause the oscillator to "squegg."


The grid-dip meter is built in a $2\frac{1}{4} \times 2\frac{1}{4} \times 4$ -inch Minibox, and the power supply and meter circuit is built in a similar enclosure. In use the two Miniboxes are connected by a short length of four-conductor cable.

The "heart" of the meter is the oscillator section, which is built on a 1¾ × 1%-inch piece of %-inch thick polystyrene. The Nuvistor

socket is mounted in one corner and the tuning capacitor is mounted a little above center. The coil socket, a National CS-6, is mounted on the end of the Minibox. The polystyrene sheet is supported by four 1-inch 6-32 screws, and the sockets and variable capacitor are positioned so that direct connections can be made between plate pin and coil socket, capacitor rotor and coil socket, and capacitor stator and grid pin. The various resistors and r.f. chokes are supported at one end by a multiple-terminal tie strip mounted on the polystyrene sheet and at the other end by the socket pins and other terminals.

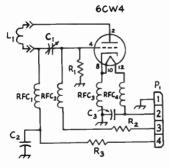The coils are made from No. 10 tinned-copper wire; as a safety precaution they are covered



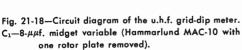

 C_2 —150- $\mu\mu$ f. ceramic.

 C_8 —0.001- μ f. ceramic.

C4-20-4f., 250-volt electrolytic.


CR₁-400 p.i.v. rectifier (Sarkes Tarzian 2F4).

J₁-4-pin tube socket.

M₁-0-500 microammeter.

P₁-4-pin plug (Amphenol 86-CP4).

Q₁-2N1264 transistor.

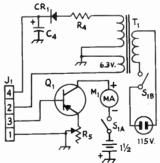

R₁—330 ohms, 1 watt.
R₂—47,000 ohms, ½ watt.
R₃—1,000 ohms.
R₄—22 ohms, ½ watt.
R₅—10,000-ohm potentiometer.
RFC₁, RFC₂—22-μh. r.f. choke (Millen 34300-22).
RFC₃, RFC₄—0.82-μh. r.f. choke (Millen 34300-82).
S_{1A}, S_{1B}—D.p.s.t., part of R₄. Switches should be open when R₄ at maximum resistance.

T₁--6.3- and 125-v. transformer (Knight 61 G 410).

526 MEASUREMENTS

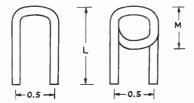


Fig. 21-19—Details of the coils used in the u.h.f. griddip meter. The material is No. 10 tinned-copper wire. One turn in end of low-frequency coil.

Range	Dimension "L"	"M"
271-324 Mc.	2¾	11/4
312-378	31/6	_
372-463	2	_
413-519	1%	_
446-565	1¼	_
544-730	1/2*	_

^{*}Shape closed end to be nearly square.

except at the tips by clear plastic insulation. Details are given in Fig. 21-19.

Frequency calibration of the meter can be started by reference to u.h.f. TV stations in the area, if any, or by reference to 420-Mc. amateur gear.

AUDIO-FREQUENCY OSCILLATORS

A useful accessory for testing audio-frequency amplifiers and modulators is an audio-frequency signal generator or oscillator. Checks for distortion, gain, and the troubles that occur in such amplifiers do not require elaborate equipment; the principal requirement is a source of one or more audio tones having a good sine wave form, at a voltage level adjustable from a few volts down to a few millivolts so the oscillator can be substituted for the type of microphone to be used.

An easily constructed oscillator of this type is shown in Figs. 21-20 to 21-22, inclusive.

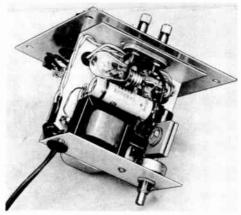



Fig. 21-20—Bottom view of the audio oscillator, showing the power-supply components and amplitude-control lamp, I1. The lamp is mounted by wires soldered to its base. The selenium rectifier is supported by a tie-point strip. Placement of resistors, which are hidden by the other components, is not critical. The unit fits in a $4 \times 5 \times 6$ inch box.

Three audio frequencies are available, approximately 200, 900 and 2500 cycles. These three frequencies are sufficient for testing the frequency response of an amplifier over the range needed for voice communication.

The circuit uses a double triode as a cathodecoupled oscillator, the second section of the tube providing the feedback necessary for oscillation through the common cathode connection. The 3-watt lamp in this feedback loop acts as a variable resistance to control the oscillation amplitude and thus maintain the operating conditions at the point where the best wave form is generated. This operating point is set by the 'oscillation control," R1. The frequency is determined by the resistance and capacitance in

33 K Jyt CR₁-20-ma, selenium rectifier /212AU7 1-3-watt, 115-volt lamp (G.E. 356). L₁-8 henrys, 40 ma. (Thordarson 20C-52). 2.28 R1, R2-Volume controis. S₁-2-pole 5-position (3 used) rotary switch. S2-S.p.d.t. toggle. Sa-S.p.s.t. toggle (mounted on R1). T₁-Power transformer, 150 volts, 25 ma.; 6.3 voits 0.5 amp. (Merit P-

3046).

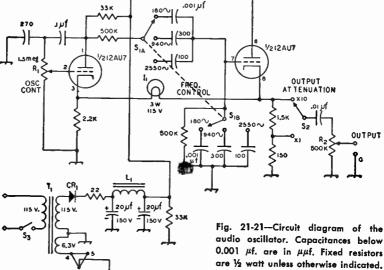

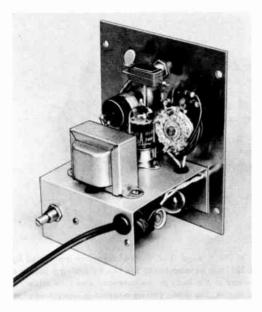


Fig. 21-22—Inside view of the audio oscillator. The a.c. switch, S_3 , is mounted on the output control at the left on the panel. The ceramic capacitors in the frequency-determining circuits are mounted on the rotary switch, S_1 , at the right. S_2 is above the tube, and T_1 is on the near edge of the chassis, which is a U-shaped piece of aluminum $3\frac{1}{2}$ inches deep with $1\frac{1}{2}$ inch lips. R_1 is mounted on the near lip at the left,

the coupling circuit between the first-section plate and second-section grid. Various values of capacitance can be selected by means of S_1 to set the frequency. The actual frequencies measured in the unit shown in the photographs are given on the diagram. They may be either increased or decreased by using smaller or larger capacitances, respectively.

Output is taken from the cathode of the second triode section. Either the full output, 1.5 volts, or approximately one-tenth of it, can be selected by S_2 . On either of these two ranges smooth control of output is provided by R_2 .

The built-in power supply uses a small transformer and a selenium rectifier to develop approximately 150 volts. Hum is reduced to a negligible level by the filter consisting of the 8-henry choke and $20-\mu f$. capacitors.

An oscilloscope is useful for preliminary checking of the oscillator since it will show wave form. R_1 should be set at the point that will ensure oscillation on all three frequencies when switching from one to the other.

NOISE GENERATORS

A noise generator is a device for creating a controllable amount of radio-frequency noise ("hiss"-type noise) evenly distributed throughout the frequency spectrum of interest. The simplest type of noise generator is a diode, either vacuum-tube or crystal, with direct current flowing through it. The current is also made to flow through a load resistance which in general is chosen to equal the characteristic impedance of the transmission line to be connected to the receiver's input terminals. The resistance then substitutes for the line, and the amount of r.f. noise fed to the input terminals of the receiver is controlled by controlling the d.c. through the diode.

The usefulness of the noise generator in amateur work lies in the fact that it provides a means for adjusting the "front-end" circuits of a receiver for optimum signal-to-noise ratio (see sections on receiver design). Although it can be built at little expense, it is actually more effective for this purpose than costly laboratory-type signal generators. A simple circuit using a crystal diode is shown in Fig. 21-23. Fig. 21-24 illustrates the construction,

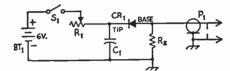


Fig. 21-23—Circuit of a simple crystal-diode noise generator.

BT₁—Dry-cell battery, any convenient type.

 C_1 -500- $\mu\mu$ f. ceramic, disk or tubular.

CR₁—Silicon diode, 1N21 or 1N23. Diodes with "R" suffix have reversed polarity. (Do not use ordinary germanium diodes).

P₁—Coaxial fitting, cable type.

R₁—50,000-ohm control, counterclockwise logarithmic taper.

 R_2 —51 or 75 ohms, $\frac{1}{2}$ -watt composition. S_1 —S.p.s.t. toggle (may be mounted on R_1).

the principal requirement being that R_2 should be mounted right on the terminals of the coaxial fitting and that lead lengths should be as short as possible in the circuit formed by C_1 , CR_1 and R_2 . If these lead lengths are negligible the instrument should give uniform performance up to at least 150 Mc. R_2 should match the particular line and input impedance for which the receiver is designed.

To use the generator, screw the coaxial fitting on the receiver's input fitting, open S_1 , and measure the noise output of the receiver using an a.c. vacuum-tube voltmeter or similar a.f. voltage indicator. Make sure that the receiver's r.f. and audio gain controls are set well within the linear range, and do not use a.g.c. Then turn on the noise generator and set R₁ for an appreciable increase in output, say twice the original noise voltage, and note the dial setting. Receiver front-end adjustments may then be made with the object of attaining the same noise increase with the lowest possible direct current through the diode - that is, with the largest possible resistance at R1.

528 MEASUREMENTS

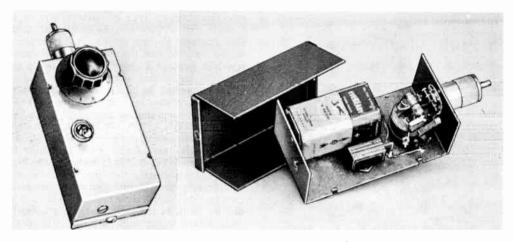


Fig. 21-24—Crystal-diade naise generatar maunted in a 1 % × 2 % × 4-inch bax. Mast af the space is accupied by the miniature 6-valt dry-cell battery. The caaxial fitting (PL-259) can be maunted to the bax by cutting a hale in a small square sheet-capper plate to make a snug fit over the end of the bady of the cannector and then saldering it in place. Hales can be drilled in the plate for mounting screws. The diade can be mounted in improvised clips, the larger being a small-size grid-grip and the smaller a miniature socket cantact.

The instrument may be used for comparing different receivers or different front-end arrangements, since this type of measurement is independent of receiver bandwidth (which has a marked effect on the actual signal-to-noise ratio). For consistent measurements the

battery voltage should be checked to make sure that it does not change with the setting of R_1 .

(Further information on noise generators, with additional references, may be found in QST for July, 1953.)

R.F. MEASUREMENTS

R.F. CURRENT

R.f. current-measuring devices use a thermocouple in conjunction with an ordinary d.c. instrument. The thermocouple is made of two dissimilar metals which, when heated, generate a small d.c. voltage. The thermocouple is heated by a resistance wire through which the r.f. current flows, and since the d.c. voltage developed is proportional to the heating, which in turn is proportional to the power used by the heating element, the deflections of the d.c. instrument are proportional to power rather than to current. This causes the calibrated scale to be compressed at the low-current end and spread out at the high-current end. The useful range of such an instrument is about 3 or 4 to 1; that is, an r.f. ammeter having a full-scale reading of 1 ampere can be read with satisfactory accuracy down to about 0.3 ampere, one having a full scale of 5 amperes can be read down to about 1.5 amperes, and so on. No single instrument can be made to handle a wide range of currents. Neither can the r.f. ammeter be shunted satisfactorily, as can be done with d.c. instruments, because even a very small amount of reactance in the shunt will cause the readings to be highly dependent on frequency.

Fig. 21-25 shows a convenient way of using



Fig. 21-25—R.f. ammeter maunted far cannecting inta a caaxial line far measuring pawer. A "2-inch" instrument will fit inta a 2 × 4 × 4 metal bax.

an r.f. ammeter for measuring current in a coaxial line. The instrument is simply mounted in a metal box with a short lead from each terminal to a coaxial fitting. The shunt capacitance of an ammeter mounted in this way has only a negligible effect on accuracy at frequencies as high as 30 Mc. if the instrument has a bakelite case. Metal-cased meters should be mounted on a bakelite panel which in turn can be mounted behind a cut-out that clears the meter case by ½ inch or so.

R.F. VOLTAGE

An r.f. voltmeter is a rectifier-type instrument in which the r.f. is converted to d.c., which is then measured with a d.c. instrument. The best type of rectifier for most ap-

R.F. Measurements

plications is a crystal diode, such as the 1N34 and similar types, because its capacitance is so low as to have little effect on the behavior of the r.f. circuit to which it is connected. The principal limitation of these rectifiers is their rather low value of safe inverse peak voltage. Vacuum-tube diodes are considerably better in this respect, but their size, shunt capacitance, and the fact that power is required for heating the cathode constitute serious disadvantages in many applications.

One of the principal uses for such voltmeters is as null indicators in r.f. bridges, as described later in this chapter. Another useful application is in measurement of the voltage between the conductors of a coaxial line, to show when a transmitter is adjusted for optimum output. In either case the voltmeter impedance should be high compared with that of the circuit under measurement, to avoid taking appreciable power, and the relationship between r.f. voltage and the reading of the d.c. instrument should be as linear as possible—that is, the d.c. indication should be directly proportional to the r.f. voltage at all points of the scale.

All rectifiers show a variation in resistance with applied voltage, the resistance being highest when the applied voltage is small. These variations can be fairly well "swamped out" by using a high value of resistance in the d.c. circuit of the rectifier. A resistance of at least 10,000 ohms is necessary for reasonably good linearity with a 0-1 milliammeter. High resistance in the d.c. circuit also raises the impedance of the r.f. voltmeter and reduces its power consumption.

The basic voltmeter circuit is shown in Fig. 21-26. It is simply a half-wave rectifier with a meter and a resistor, R_1 , for improving the linearity. The time constant of C_1R_1 should be large compared with the period of the lowest radio frequency to be measured — a condition that can easily be met if R_1 is at least 10,000 ohms and C_1 is 0.001 μ f. or more — so C_1 will stay charged near the peak value of the r.f. voltage. The radio-frequency choke may be omitted if there is a low-resistance d.c. path through the circuit being measured. C_2 provides additional r.f. filtering for the d.c. circuit.

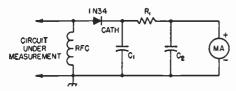


Fig. 21-26—R.f. voltmeter circuit using a crystal rectifier and d.c. microammeter ar 0-1 milliammeter.

The simple circuit of Fig. 21-26 is useful for voltages up to about 20 volts, a limitation imposed by the inverse-peak voltage ratings of crystal diodes. A dual range voltmeter circuit, 0-20 and 0-100 volts, is shown in Fig. 21-27.

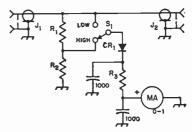


Fig. 21-27—Dual-range r.f. voltmeter circuit. Capactances are in $\mu\mu$ f.; capacitors are disk ceramic.

CR₁—1N34 or equivalent.

J₁, J₂—Coaxial connectors, chassis-mounting type.

R₁-1000 ohms, 1 watt.

R₂-3300 ohms, 2 watts.

 R_s —App. 22,000 ohms (see text), $\frac{1}{2}$ watt.

S₁—S.p.d.t. rotary switch (Centralab 1460).

A voltage divider, R_1R_2 , is used for the higher range. An instrument using this circuit is shown in Fig. 21-28. It is designed for connection into a coaxial line. The principal constructional precautions are to keep leads short, and to mount the components in such a way as to minimize stray coupling between them and to keep them fairly well separated from metal surfaces.

For accurate calibration (the power method described below may be used) R₃ should be adjusted, by selection of resistors or using two in series to obtain the desired value, so that the meter reads full scale, with S_1 set for the low range, with 20 volts r.m.s. on the line. A frequency in the vicinity of 14 Mc. should be used. Then, with S_1 set for the high range, various resistors should be tried at R₁ or R₂ until with the same voltage the meter reads 20 per cent of full scale. The resistance variations usually will be within the range of 10 per cent tolerance resistors of the values specified. The readings at various other voltages should be observed in order to check the linearity of the scale.

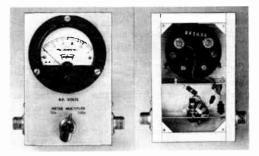


Fig. 21-28—Dual-range r.f. voltmeter for use in coaxial line, using a 0-1 d.c. milliammeter. The voltage-divider resistors, R_1 and R_2 (Fig. 21-27) are at the center in the lower compartment. The bypass capacitors and R_3 are mounted on a tie-point strip at the right. The unit is built in a $4\times 6\times 2$ inch aluminum chassis, with an aluminum partition connecting the two sides of the box to form a shielded space. A bottom plate, not shawn, is used to complete the shielding.

530 MEASUREMENTS

to the shield.

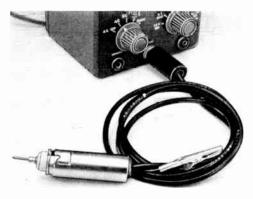


Fig. 21-29—The r.f. probe is used in conjunction with a vacuum-tube voltmeter. The case of the probe is constructed from a 7-pin ceramic tube socket and a 2½-inch tube shield. A half-inch grommet at the top of the tube shield prevents the output lead of the probe from chafing. The flexible copper-braid grounding lead and alligator clip provide a low-inductance return path from the test circuit. The d.c. output of the probe goes to the phone plug, which plugs into the d.c. input jack of the v.t.v.m.

Calibration

Calibration is not necessary for purely comparative measurements. A calibration in actual voltage requires a known resistive load and an r.f. ammeter. The setup is the same as for r.f. power measurement as described later.

V.T.V.M. R.F. PROBE

R.f. up to about 30 volts peak and a frequency of 200 Mc. is most conveniently measured with a v.t.v.m. (Fig. 21-8) and an r.f. probe. An r.f. probe is merely a rectifier that uses a v.t.v.m. to indicate the magnitude of the rectified voltage. The resultant d.c. voltage is very nearly equal to the peak value of the r.f. voltage.

The unit shown in Figs. 21-29 and 21-31 and schematically in Fig. 21-30 is similar in circuitry to most of the conventional peak-indicating, shunt-type commercial r.f. probes. However, it can be constructed for considerably less than the cost of a commercial unit. If all parts, including the shielded wire, alligator clip, tie point, resistor, phone plug, tube socket, tube shield, capacitor, and diode are purchased new, the total cost of the unit is approximately \$2.25.

The isolation capacitor, crystal diode, and resistor are mounted on a bakelite 5-lug ter-

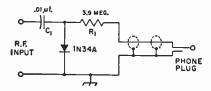


Fig. 21-30—The r.f. probe circuit.

minal strip, as shown in Fig. 21-32. One end lug should be rotated 90 degrees so that it extends off the end of the strip. All other lugs should be cut off flush with the edge of the strip. Where the inner conductor connects to the terminal lug, unravel the shield three-quarters of an inch, slip a piece of spaghetti over it, and then solder the braid to the ground lug on the terminal strip. Remove the spring from the tube shield, slide it over the cable, and crimp it to the remaining quarter inch of shield braid. Solder both the spring and a 12-inch length of flexible copper braid

Next, cut off the pins on a seven-pin miniature ceramic or mica shield-base tube socket. Use a socket with a cylindrical center post, such as the Johnson 120-277. Crimp the terminal lug previously bent out at the end of the strip and insert it into the center post of the tube socket from the top. Insert the end of a phone tip or a pointed piece of heavy wire into the bottom of the tube socket center post, and solder the lug and tip to the center post. Insert a half-inch grommet at the top of the tube shield, and slide the shield over the cable and flexible braid down onto the tube socket. The spring should make good contact with the tube shield to insure that the tube shield (probe case) is grounded. Solder an alligator clip to the other end of the flexible braid and mount a phone plug on the free end of the shielded wire.

Mount components close to the terminal strip, to keep lead lengths as short as possible and minimize stray capacitance. Use spaghetti over all wires to prevent accidental shorts. When soldering the crystal diode, hold the end to be soldered with a pair of long-nose pliers, to conduct damaging heat away from the diode.



Fig. 21-31—Close-up of the inside of the probe. The 1N34A crystal diode rectifier, calibrating resistor, and input capacitor are mounted tight to the terminal strip with shortest leads possible. Spaghetti tubing is placed on the diode leads to prevent accidental short circuits. The tube-shield spring and Rexible-copper grounding lead are soldered to the cable braid (the cable is RG-58/U coax). The tip can be either a phone tip or a short pointed piece of heavy wire.

Using the Probe

The a.c. input voltage that the probe can handle safely is limited to about 21 volts r.m.s. or 30 volts peak, as a result of the 60-volt peak-inverse rating of the 1N34A crystal diode. The phone plug on the probe cable plugs into the d.c. input jack of the v.t.v.m., and r.m.s. voltages are read on the vacuum-tube voltmeter's negative d.c. scale. When using the probe be sure that any d.c. voltage on the circuit being checked does not exceed the d.c. voltage rating of C_1 .

The accuracy of the probe is approximately

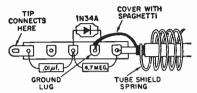


Fig. 21-32—Component mounting details.

 \pm 10 per cent from 50 kc. to 250 Mc. For example, if the error of the v.t.v.m. used with the probe is \pm 5 per cent, then the over-all error of the measuring system is \pm 15 per cent. At low values of input voltage, below a volt or so, the accuracy of the probe is somewhat poorer because of the nonlinearity of the 1N34A crystal diode. At these lower input voltages the output of the probe more closely approaches a square-law relationship than a linear one.

The approximate input impedance of a probe of this type is 6000 ohms shunted by 1.75 $\mu\mu$ f. (at 200 Mc.), and the amount of error introduced because of circuit loading by the probe is dependent on the impedance of the source of the a.c. voltage being measured. If peak values are desired rather than r.m.s., the r.m.s. values can be multiplied by 1.41 or the peak scales on the v.t.v.m. can be read directly if so calibrated.

R.F. POWER

Measurement of r.f. power requires a resistive load of known value and either an r.f. ammeter or a calibrated r.f. voltmeter. The power is then either I^2R or E^2/R , where R is the load resistance in ohms.

The simplest method of obtaining a load of known resistance is to use an antenna system with coax-coupled matching circuit of the type described in the chapter on transmission lines. When the circuit is adjusted, by means of an s.w.r. bridge, to bring the s.w.r. down to 1 to 1 the load is resistive and of the value for which the bridge was designed (52 or 75 ohms).

The r.f. ammeter should be inserted in the line in place of the s.w.r. bridge after the matching has been completed, and the transmitter then adjusted — without touching the matching circuit — for maximum current. A 0-1 ammeter is useful for measuring the approximate range 5-50 watts in 52-ohm line, or 7.5-75 watts in 75-ohm line; a 0-3 instrument can be used for 13-450 watts in 52-ohm line and 20-675 watts in 75-ohm line. The accuracy is usually greatest in the upper half of the scale.

An r.f. voltmeter of the type described in the preceding section also can be used for power measurement in a similar setup. It has the advantage that, because its scale is substantially linear, a much wider range of powers can be measured with a single instrument.

INDUCTANCE AND CAPACITANCE

The ability to measure inductance and capacitance saves time that might otherwise be spent in cut-and-try. A convenient instrument for this purpose is the grid-dip oscillator, described earlier in this chapter.

For measuring inductance, use is made of a capacitance of known value as shown at A in Fig. 21-33. With the unknown coil connected to the standard capacitor, couple the grid-dip meter to the coil and adjust the oscillator frequency for the grid-current dip, using the loosest coupling that gives a detectable indication. The inductance is then given by the formula

$$L_{\mu h.} = \frac{25,330}{C_{\mu\mu f.} f^2_{Mo.}}$$

The reverse procedure is used for measuring capacitance—that is, a coil of known inductance is used as a standard as shown at B. The unknown capacitance is

$$C_{\mu\mu}t. = \frac{25,330}{L_{\mu h}.f^2_{Mo.}}$$

The accuracy of this method depends on the accuracy of the grid-dip meter calibration and the accuracy with which the standard values of L and C are known. Postage-stamp

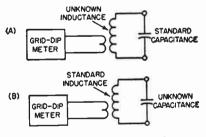


Fig. 21-33—Setups for measuring inductance and capacitance with the grid-dip meter.

silver-mica capacitors make satisfactory capacitance standards, since their rated tolerance is ±5 per cent. Equally good inductance standards can be made from commercial machine-wound coil material.

A single pair of standards will serve for measuring the L and C values commonly used

in amateur equipment. A good choice is 100 $\mu\mu$ f. for the capacitor and 5 μ h. for the coil. Based on these values the chart of Fig. 21-35 will give the unknown directly in terms of the resonant frequency registered by the griddip meter. In measuring the frequency the coupling between the griddip meter and resonant circuit should be kept at the smallest value that gives a definite indication.

A correction should be applied to measurements of very small values of L and C to include the effects of the shunt capacitance of the mounting for the coil, and for the inductance of the leads to the capacitor. These amount to approximately 1 $\mu\mu$ f. and 0.03

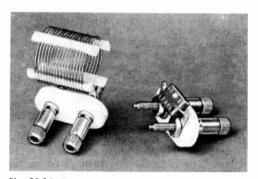


Fig. 21-34—A convenient mounting, using binding-post plates, for L and C standards made from commercially-available parts. The capacitor is a 100- $\mu\mu$ f. silver mica unit, mounted so the lead length is as nearly zero as possible. The inductance standard, 5 μ h., is 17 turns of No. 3015 B & W Miniductor, 1-inch diameter, 16 turns per inch.

μh., respectively, with the method of mounting shown in Fig. 21-34.

Coefficient of Coupling

The same equipment can be used for measurement of the coefficient of coupling between two coils. This simply requires two measurements of inductance (of one of the coils) with the coupled coil first open-circuited and then short-circuited. Connect the 100-µµf. standard capacitor to one coil and measure the inductance with the terminals of the second coil open. Then short the terminals of the second coil and again measure the inductance of the first. The coefficient of coupling is given by

$$k = \sqrt{1 - \frac{L_2}{L_1}}$$

where k = coefficient of coupling

I₁ = inductance of first coil with terminals of second coil open

L₂ = inductance of first coil with terminals of second coil shorted.

R.F. RESISTANCE

Aside from the bridge methods used in transmission-line work, described later, there is relatively little need for measurement of r.f. resistance in amateur practice. Also, measurement of resistance by fundamental methods is not practicable with simple equipment. Where such measurements are made, they are usually based on known characteristics of available resistors used as standards.

Most types of resistors have so much inherent reactance and skin effect that they do

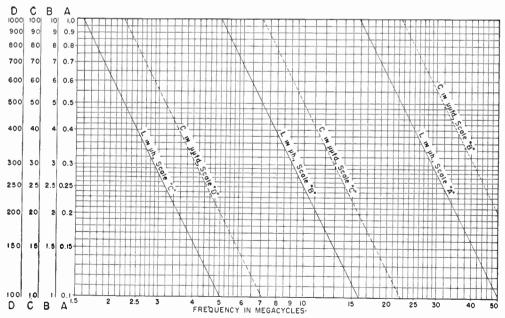


Fig. 21-35—Chart for determining unknown values of L and C in the range 0.1 to 100 μ h. and 2 to 1000 $\mu\mu$ f., using standards of 100 $\mu\mu$ f. and 5 μ h.

not act like "pure" resistance at radio frequencies, but instead their effective resistance and impedance vary with frequency. This is especially true of wire-wound resistors. Composition (carbon) resistors of 25 ohms or more as a rule have negligible inductance for frequencies up to 100 Mc. or so. The skin effect also is small, but the shunt capacitance cannot be neglected in the higher values of these resistors, since it reduces their impedance and makes it reactive. However, for most purposes the capacitive effects can be

considered to be negligible in composition resistors of values up to 1000 ohms, for frequencies up to 50 to 100 Mc., and the r.f. resistance of such units is practically the same as their d.c. resistance. Hence they can be considered to be practically pure resistance in such applications as r.f. bridges, etc., provided they are mounted in such a way as to avoid magnetic coupling to other circuit components, and are not so close to grounded metal parts as to give an appreciable increase in shunt capacitance.

ANTENNA AND TRANSMISSION-LINE MEASUREMENTS

Two principal types of measurements are made on antenna systems: (1) the standing-wave ratio on the transmission line, as a means for determining whether or not the antenna is properly matched to the line (alternatively, the input resistance of the line or antenna may be measured); (2) the comparative radiation field strength in the vicinity of the antenna, as a means for checking the directivity of a beam antenna and as an aid in adjustment of element tuning and phasing. Both types of measurements can be made with rather simple equipment.

FIELD-STRENGTH MEASUREMENTS

The radiation intensity from an antenna is measured with a device that is essentially a very simple receiver equipped with an indicator to give a visual representation of the comparative signal strength. Such a field-strength meter is used with a "pick-up antenna" which should always have the same polarization as the antenna being checked—e.g., the pick-up antenna should be horizontal if the transmitting antenna is horizontal. Care should be taken to prevent stray pickup by the field-strength meter itself or by any transmission line that may connect it to the pick-up antenna.

Field-strength measurements preferably should be made at a distance of several wavelengths from the transmitting antenna being tested. Measurements made within a wavelength of the antenna may be misleading, because of the possibility that the measuring equipment may be responding to the combined induction and radiation fields of the antenna, rather than to the radiation field alone. Also, if the pick-up antenna has dimensions comparable with those of the antenna under test it is likely that the coupling between the two antennas will be great enough to cause the pick-up antenna to tend to become part of the radiating system and thus result in misleading field-strength readings.

A desirable form of pick-up antenna is a dipole installed at the same height as the antenna being tested, with low-impedance line such as 75-ohm Twin-Lead connected at the center to transfer the r.f. signal to the

field-strength meter. The length of the dipole need only be great enough to give adequate meter readings. A half-wave dipole will give high sensitivity, but such length will not be needed unless the distance is several wavelengths and a relatively insensitive meter is used.

Field-Strength Meters

The crystal-detector wavemeter described earlier in this chapter may be used as a field-strength meter. It may be coupled to the transmission line from the pick-up antenna through the coaxial-cable jack, J_1 .

The indications with a crystal wavemeter connected as shown in Fig. 21-10 will tend to be "square law"—that is, the meter reading will be proportional to the square of the r.f.

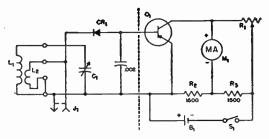


Fig. 21-36—Transistor d.c. amplifier applied to the wavemeter of Fig. 21-10 to increase sensitivity. Components not listed below are the same as in Fig. 21-10. B₁—Small flashlight cell.

M₁-0-1 d.c. milliammeter (see text).

Q1-2N107, CK722, etc.

R₁-10,000-ohm control.

voltage. This exaggerates the effect of relatively small adjustments to the antenna system and gives a false impression of the improvement secured. The meter reading can be made more linear by connecting a fairly large resistance in series with the milliammeter (or microammeter). About 10,000 ohms is required for good linearity. This considerably reduces the sensitivity of the meter, but the lower sensitivity can be compensated for by making the pick-up antenna sufficiently large.

Transistorized Wavemeter and Field-Strength Meter

A sensitive field-strength meter can be made by using a transistor as a d.c. amplifier following the crystal rectifier of a wavemeter. A circuit of this type is shown in Fig. 21-34. Depending on the characteristics of the particular transistor used, the amplification of current may be 10 or more times, so that a 0-1 milliampere d.c. instrument becomes the equivalent of a sensitive microammeter.

The circuit to the left of the dashed line in Fig. 21-36 is the same as the wavemeter circuit of Fig. 21-10, and the transistor amplifier can easily be accommodated in the case shown in Figs. 21-11 and 21-12.

The transistor is connected in the commonemitter circuit with the rectified d.c. from the crystal diode flowing in the base-emitter circuit. Since there is a small residual current in the collector circuit with no current flowing in the base-emitter circuit, the d.c. meter is connected in a bridge arrangement so the residual current can be balanced out. This is accomplished, in the absence of any signal input to the transistor base, by adjusting R_1 so that the voltage drop across it is equal to the voltage drop from collector to emitter in the transistor. R_2 and R_3 , being of the same reistance, have equal voltage drops across them and so there is no difference of potential across the meter terminals until the collector current increases because of current flow in the base-emitter circuit.


The collector current in a circuit of this type is not strictly proportional to the base current, particularly for low values of base current. The meter readings are not directly proportional to the field strength, therefore, but tend toward "square law" response just as in the case of a simple diode with little or no resistance in its d.c. circuit. For this reason the d.c. meter, M_1 , should not have too-high sensitivity if reasonably linear response is desired. A 0-1 milliammeter will be satisfactory.

The zero balance should be checked at intervals while the instrument is in use, since the residual current of the transistor is sensitive to temperature changes.

IMPEDANCE AND STANDING-WAVE RATIO

Adjustment of antenna matching systems requires some means either of measuring the input impedance of the antenna or transmission line, or measuring the standing-wave ratio. "Bridge" methods are suitable for either measurement.

There are many varieties of bridge circuits, the two shown in Fig. 21-37 being among the most popular for amateur purposes. The simple resistance bridge of Fig. 21-37A consists essentially of two voltage dividers in parallel across a source of voltage. When the voltage

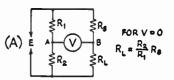

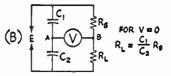


Fig. 21-37—Basic bridge circuits. (A) Resistance bridge;
(B) resistance-capacitance bridge. The latter circuit is used in the "Micromatch," with R_s a very low resistance (1 ohm or less) and the ratio C₁/C₂ adjusted accordingly for a desired line impedance.

drop across R_1 equals that across R_n the drops across R_2 and R_L are likewise equal and there is no difference of potential between points A and B. Hence the voltmeter reading is zero and the bridge is said to be "balanced." If the drops across R_1 and R_n are not equal, points A and B are at different potentials and the voltmeter will read the difference. The operation of the circuit of Fig. 21-37B is similar, except that one of the voltage dividers is capacitive instead of resistive.

Because of the characteristics of practical components at radio frequencies, the circuit of Fig. 21-37A is best suited to applications where the ratio R_1/R_2 is fixed; this type of bridge is particularly well suited to measurement of standing-wave ratio. The circuit of Fig. 21-37B is well adapted to applications where a variable voltage divider is essential (since C_1 and C_2 may readily be made variable) as in measurement of unknown values of $R_{\rm L}$.

S.W.R. Bridge

In the circuit of Fig. 21-37A, if R₁ and R₂ are made equal, the bridge will be balanced when $R_L = R_s$. This is true whether R_L is an actual resistor or the input resistance of a perfectly matched transmission line, provided R_{\bullet} is chosen to equal the characteristic impedance of the line. Even if the line is not properly matched, the bridge will still be balanced for power traveling outward on the line, since outward-going power sees only the Z_{\bullet} of the line until it reaches the load. However, power reflected back from the load does not "see" a bridge circuit and the reflected voltage registers on the voltmeter. From the known relationship between the outgoing or "forward" voltage and the reflected voltage, the s.w.r. is easily calculated:

S.W.R. =
$$\frac{V_o + V_r}{V_o - V_r}$$

where V_{\circ} is the forward voltage and V_{r} is the reflected voltage. The forward voltage is

equal to E/2 since R_{\bullet} and R_{L} (the Z_{\bullet} of the line) are equal. It may be measured either by disconnecting R_{L} or shorting it.

Measuring Voltages

For the s.w.r. formula above to apply with reasonable accuracy (particularly at high standing-wave ratios) the current taken by the voltmeter must be inappreciable compared with the currents through the bridge "arms." The voltmeter used in bridge circuits employs a crystal diode rectifier (see discussion earlier in this chapter) and in order to meet the above requirement — as well as to have linear response, which is equally necessary for calibration purposes — should use a resistance of at least 10,000 ohms in series with the milliammeter or microammeter.

Since the voltage applied to the line is measured by shorting or disconnecting R_L (that is, the line input terminals), while the reflected voltage is measured with R_L connected, the load on the source of voltage E is different in the two measurements. If the regulation of the voltage source is not perfect, the voltage E will not remain the same under these two conditions. This can lead to large errors. Such errors can be avoided by using a second voltmeter to maintain a check on the voltage applied to the bridge, readjusting the coupling to the voltage source to maintain constant applied voltage during the two measurements. Since the "input" voltmeter is

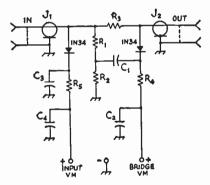


Fig. 21-38—Bridge circuit for s.w.r. measurements. This circuit is intended for use with a d.c. voltmeter, range 5 to 10 volts, having a resistance of 10,000 ohms per volt or greater.

 C_1 , C_2 , C_3 , C_4 —0.005- or 0.01- μ f. disk ceramic. R_1 , R_2 —47-ohm composition, $\frac{1}{2}$ or 1 watt.

Rs-52- or 75-ohm (depending on line impedance) composition, ½ or 1 watt; precision type preferred.

R₄, R₅-10,000 ohms, ½ watt.

J₁, J₂—Coaxial connectors.

Meter connects to either "input" or "bridge" position as required.

simply used as a reference, its linearity is not important, nor does its reading have to bear any definite relationship to that of the

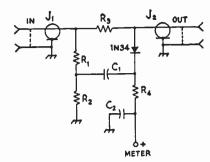


Fig. 21-39—A simple bridge circuit useful for Impedance-matching in coaxial lines.

C₁, C₂-0.005- or 0.01-µf. disk ceramic.

R₁, R₂-47-ohm composition, ½ watt.

Rs-52- or 75-ohm (depending on line impedance) composition, ½ watt; precision type preferred.

R₄-1000-ohm composition, ½ watt.

J₁, J₂-Coaxial connector.

The meter may be a 0-1 milliammeter or d.c. voltmeter of any type having a sensitivity of 1000 ohm per volt or greater, and a full-scale range of 5 to 10 volts.

Negative side of meter connects to ground.

"bridge" voltmeter, except that its range has to be at least twice that of the latter.

A practical circuit incorporating these features is given in Fig. 21-38.

If the bridge is to be used merely for antenna adjustment, where the object is to secure the lowest possible s.w.r. rather than to measure the s.w.r. accurately, the voltmeter requirements are not stringent. In this case the object is to get as close to a "null" or balance (that is, zero reading) as possible. At or near exact balance the voltmeter impedance is not important. Neither is it necessary to maintain constant input voltage to the bridge. This simplifies the bridge circuit considerably, Fig. 21-39 being a practical example. The construction of a bridge of this type suitable for antenna and transmission line adjustments is shown in Fig. 21-40.

Bridge Construction

A principal point in the construction of an s.w.r. bridge is to avoid coupling between the resistors forming the bridge arms, and between the arms and the voltmeter circuit. This can be done by keeping the resistance arms separated and at right angles to each other, and by placing the crystal and its connecting leads so that the loop so formed is not in inductive relationship with any loops formed by the bridge arms. Shielding between the bridge arms and the crystal circuit is helpful in reducing such couplings, although it is not always necessary. The two resistors forming the "ratio arms," R₁ and R₂, should have identical relationships with metal parts, to keep the shunt capacitances equal, and also should have the same lead lengths so the inductances will balance. Leads should be kept as short as possible.

Testing and Calibration

In a bridge intended for s.w.r. measurement (Fig. 21-38) rather than simple matching, the first check is to apply just enough r.f. voltage, at the highest frequency to be used, so that the bridge voltmeter reads full scale with the load terminals open. Observe the input voltage, then short-circuit the load terminals and readjust the input to the same voltage. The bridge voltmeter should again register full scale. If it does not, the ratio arms, R_1 and R_2 , probably are not exactly equal. These two resistors should be carefully matched, although their actual value is not critical. If a similar test at a low frequency shows better balance, the probable cause is stray inductance or capacitance in one arm not balanced by equal strays in the other.

After the "short" and "open" readings have been equalized, the bridge should be checked for null balance with a "dummy" resistance, equal to the line impedance, connected to the load terminals. It is convenient to mount a half- or 1-watt resistor of the proper value in a coax connector, keeping it centered in the connector and using the minimum lead length. The bridge voltmeter should read zero at all frequencies. A reading above zero that remains constant at all frequencies indicates that the "dummy" resistor is not matched to R_3 , while readings that vary with frequency

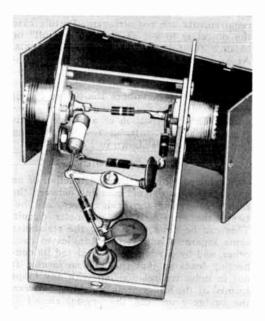


Fig. 21-40—An inexpensive bridge for matching adjustments using the circuit of Fig. 21-39. It is built in a $1\% \times 2\% \times 4$ -inch "Channel-lock" box. The standard resistor, R_3 , bridges the two coax connectors. A pin jack is provided for connection to the d.c. meter, 0-1 ma. or 0-500 μ a.; the meter negative can be connected to the case or to one of the coax fittings.

indicate stray reactive effects or stray coupling between parts of the bridge.

When the operation is satisfactory on the two points just described, the null should be checked with the dummy resistor connected to the bridge through several different lengths of transmission line, to ensure that Rs actually matches the line impedance. If the null is not complete in this test both the dummy resistor and R₃ will have to be adjusted until a good match is obtained. With care, composition resistors can be filed down to raise the resistance, so it is best to start with resistors somewhat low in value. With each change in R3. adjust the dummy resistor to give a good null when connected directly to the bridge, then try it at the end of several different lengths of line, continuing until the null is satisfactory under all conditions of line length and frequency.

With a high-impedance voltmeter, the s.w.r. readings will closely approximate the theoretical curve of Fig. 21-41. The calibration can

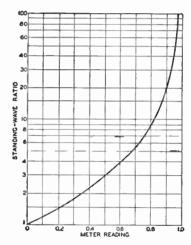


Fig. 21-41—Standing-wave ratio in terms of meter reading (relative to full scale) after setting forward voltage to full scale.

be checked by using composition resistors as loads. Adjust the transmitter coupling so that the bridge voltmeter reads full scale with the output terminals open, and then check the input voltage. Connect various values of resistance across the output terminals, making sure that the input voltage is readjusted to be the same in each case, and note the reading with the meter in the bridge position. This check should be made at a low frequency such as 3.5 Mc. in order to minimize the effect of reactance in the resistors. The s.w.r. is given by

$$S.W.R. = \frac{R_L}{R_0} \text{ or } \frac{R_0}{R_L}$$

where R_0 is the line impedance for which the bridge has been adjusted to null, and R_L is the resistance used as a load. Use the formula

that places the larger of the two resistances in the numerator. If the readings do not correspond exactly for the same s.w.r. when appropriate resistors above and below the line impedance for which the bridge is designed are used, a possible reason is that the current taken by the voltmeter is affecting the measurements.

Using the Bridge

The operating procedure is the same whether the bridge is used for matching or for s.w.r. measurement. Apply power with the load terminals either open or shorted, and adjust the input until the bridge voltmeter reads full scale. Because the bridge operates a very low power level it may be necessary to couple it to a low-power driver stage rather than to the final amplifier. Alternatively, the plate voltage and excitation for the final amplifier may be reduced to the point where the power output is of the order of a few watts. Then connect the load and observe the voltmeter reading. For matching, adjust the matching network until the best possible null is obtained. For s.w.r. measurement, note the r.f. input voltage to the bridge after adjusting for full-scale with the load terminals open or shorted, then connect the load and readjust the transmitter for the same input voltage. The bridge voltmeter then indicates the standing-wave ratio as given by Fig. 21-41.

Antenna systems are in general resonant systems and thus exhibit a purely-resistive impedance at only one frequency or over a small band of frequencies. In making bridge measurements, this will cause errors if the r.f. energy used to operate the bridge is not free from harmonics and other spurious components, such as frequencies lower than the desired operating frequency that may be fed through the final amplifier from a frequencydoubler stage. When a good null cannot be secured in, for example, the course of adjusting a matching section for 1-to-1 s.w.r., a check should be made to ensure that only the desired measurement frequency is present. An indicating-type absorption frequency meter coupled to the load usually will show whether energy on undesired frequencies is present in significant amounts. If so, additional selectivity must be used between the source of power and the measuring circuit.

Bridge for Monitoring S.W.R.

The low power level at which resistance-type bridges must operate is a disadvantage when the bridge is used as an operating adjunct — e.g., for the adjustment of matching circuits when changing bands, or for readjustment of such circuits within a band. For this purpose a bridge is needed that will carry the full power output of the transmitter without absorbing an appreciable fraction of it.

The "Monimatch" shown in Figs. 21-42 to

21-44, inclusive, is such a device. It makes use of the combined effects of inductive and capacitive coupling between the center conductor of a coaxial line and a length of wire parallel to it. When the coupled wire is properly terminated in a resistance, the voltage induced in it by power travelling along the line in one direction will be balanced out in

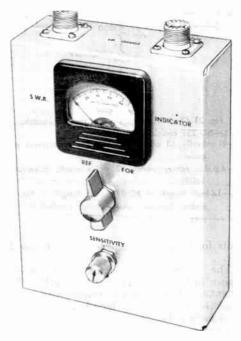


Fig. 21-42—The Monimatch, an s.w.r. monitor that can be left in the line at all times. The unitshawn here will handle a kilowatt.

the crystal-rectifier r.f. voltmeter circuit, but power travelling along the line in the opposite direction will cause a voltmeter indication. If the bridge is adjusted to match the Z_{\circ} of the coaxial line being used, the voltmeter will respond only to the reflected voltage, just as in the case of the resistance-type bridges. The power consumed in the bridge is below one watt, even at the maximum power permitted amateur transmitters.

The circuit of Fig. 21-43 uses a d.p.d.t. switch to exchange the voltmeter and the terminating resistance, so that either the forward or reflected voltage can be measured. The sensitivity of this type of bridge is proportional to frequency, so higher power is required for a given voltmeter deflection at low than at high frequencies. The sensitivity also increases with an increase in pickup length, but this should not be longer than about 1/20 wavelength, to avoid standingwave effects in the pick-up circuit. For higher frequencies the length should be decreased in proportion to the wavelength. This reduces the sensitivity considerably at the lower frequencies, so it is advisable to make separate

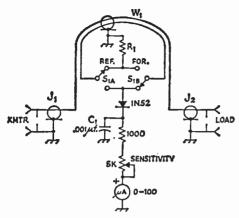


Fig. 21-43—Wiring diagram of the Monimatch. J₁, J₂—SO-239 coaxial receptacle.

R₁—Nominally 33 ohms. See text for adjustment procedure.

S₁-4.p.d.t. rotary switch (2 poles used). (Centralab 1409)

W1--14-inch length of RG-8/U with length of No. 20 enam. inserted under outer conductor. See text.

units for v.h.f. and the frequencies below 30 Mc.

The additional conductor in the bridge shown in the photographs is a length of No. 20 enameled wire running under 8 inches of the RG-8/U shield. The length of the RG-8/U is 14 inches. To insert the No. 20 wire under the cable shield, first loosen the braid by bunching it from the ends toward the center. Punch the two small holes for the wire and then snake the wire through one hole, under the braid, and out the other hole. Next, smooth out the braid to its original length, being careful not to apply so much pressure that the enamel on the wire is scratched. Check with an ohmmeter to make sure the wire and braid are not short circuited. There are several types of enameled wire (e.g., Formvar, Nylclad) that have an extremely tough covering, and the use of one of these is recommended. The covering is somewhat difficult to remove for soldering, but the use of the wire will insure against an inadvertent short-circuit to the outer conductor of the coaxial line.

It is important when assembling and wiring the Monimatch that good symmetry be maintained. Each end of the length of RG-8/U should be connected in the same way, with at least two connections made between the outer conductor and the coaxial connectors (see Fig. 21-44). The ground connection for R_1 and for the 0.001- μ f. capacitor should be the midpoint on the outer conductor of the RG-8/U. The outer conductor is connected to the chassis only at J_1 and J_2 ; the cable is stiff enough to be self-supporting and can be dressed away from the chassis at other points.

A dummy antenna of the same resistance as the Z_{\bullet} of the line should be used to adjust R_1 (Fig. 21-43). Make the connecting leads as short as possible. Only 30 or 40 watts will be required at 21 and 28 Mc. to give close to fullscale deflection, and a dummy load capable of handling this power for a short time can be made from 13 680-ohm 1-watt resistors in parallel. (See "V.H.F. Dummy Loads," QST, March, 1960.) Try several different 33-ohm resistors (with slightly different d.c. resistances) at R1, and use the one that gives a minimum reading with S1 at "REF" when nearly a full-scale reading can be obtained with S₁ at FOR. A final test on the Monimatch is to reverse the transmitter and load connections; a good minimum should be obtained with S_1 at For.

It is possible to generate harmonics in the voltmeter of sufficient intensity to cause TVI. If TVI is a problem, a low-pass filter should be connected in the line between the Monimatch and the antenna coupler or antenna. In many cases an antenna coupler will have sufficient selectivity to reject the harmonics.

. Impedance Bridge

The bridge shown in Figs. 21-45 to 21-47, inclusive, uses the basic circuit of Fig. 21-37B and incorporates a "differential" capacitor to obtain an adjustable ratio. When a resistive load of unknown value is connected in place of R_L , the C_1/C_2 ratio may be varied to attain a balance, as indicated by a null reading. The capacitor settings can be calibrated in terms of resistance at R_L , so the unknown value can be read off the calibration.

The differential capacitor consists of two identical capacitors on the same shaft, arranged so that when the shaft is rotated to increase the capacitance of one unit, the capacitance of the other decreases. The practical circuit of the bridge is given in Fig. 21-46. Satisfactory operation hinges on observing the same constructional precautions as in the case of the s.w.r. bridge. Although a high-impedance voltmeter is not essential, since the bridge is always adjusted for a null, the use of such a voltmeter is advisable because its better linearity makes the actual null settings more accurately observable.

With the circuit arrangement and capacitor shown, the useful range of the bridge is from about 5 ohms to 400 ohms. The calibration is such that the percentage accuracy of reading is approximately constant at all parts of the scale. The midscale value is in the range 50-75 ohms, to correspond to the Z_0 of coaxial cable. The reliable frequency range of the bridge includes all amateur bands from 3.5 to 54 Mc.

Checking and Calibration

A bridge constructed as shown in the photographs should show a complete null at all frequencies within the range mentioned above when a 50-ohm "dummy" load of the type

Impedance Bridge

Fig. 21-44—Rear view of Monimatch with cane-metal cover removed. To maintain symmetry, the terminating resistor R_1 and the crystal diode are connected to the midpoints of the leads between S_{1A} and S_{1B} , and R_1 and C_1 are grounded to the center of the coaxial-line outer conductor via the heavy wire running across the variable resistor. The outer conductor of the coaxial line is connected to the chassis only at J_1 and J_2 , and two connections are made in each case.

described earlier in connection with the s.w.r. bridge is connected to the load terminals. The bridge may be calibrated by using a number of $\frac{1}{12}$ -walt 5% tolerance composition resistors of different values in the 5-400 ohm range as loads, in each case balancing the bridge by adjusting C_1 for a null reading on the meter. The leads between the test resistor and J_2 should be as short as possible, and the calibration preferably should be done in the 3.5-Mc. band where stray inductance and capacitance will have the least effect.

Using the Bridge

Strictly speaking, a simple bridge can measure only purely resistive impedances. When the load is a pure resistance, the bridge can be balanced to a good null (meter reading zero). If the load has a reactance component the null will not be complete; the higher the ratio of reactance to resistance in the load the

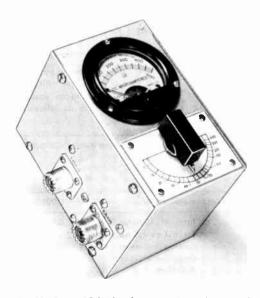


Fig. 21-45—An RC bridge for measuring unknown values of impedance. The bridge operates at an r.f. input voltage level of about 5 volts. The aluminum box is 3 by 4 by 5 inches.



poorer the null reading. The operation of the bridge is such that when an exact null cannot be secured, the readings approximate the resistive component of the load for very low values of impedance, and approximate the total impedance at very high values of impedance. In the mid-range the approximation to either is poor, for loads having considerable reactance.

In using the bridge for adjustment of matching networks C_1 is set to the desired value (usually the Z_0 of the coaxial line) and the matching network is then adjusted for the best possible null.

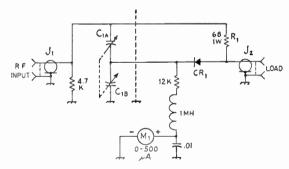


Fig. 21-46—Circuit of the impedance bridge. Resistors are composition, ½ watt except as noted. Fixed capacitors are ceramic.

C₁—Differential capacitor, 11-161 $\mu\mu$ f. per section (Millen 28801).

 CR_1 —Germanium diode (1N34, 1N48, etc.). J_1 , J_2 —Coaxial connectors, chassis type. M_1 —0-500 microammeter. 540 MEASUREMENTS

PARALLEL-CONDUCTOR LINES

Bridge measurements made directly on parallel-conductor lines are frequently subject to considerable error because of "antenna" currents flowing on such lines. These currents, which are either induced on the line by the field around the antenna or coupled into the line from the transmitter by stray capacitance, are in the same phase in both line wires and hence do not balance out like the true transmission-line currents. They will nevertheless actuate the bridge voltmeter, causing an indication that has no relationship to the standing-wave ratio.

S.W.R. Measurements

The effect of "antenna" currents on s.w.r. measurements can be largely overcome by using a coaxial bridge and coupling it to the parallel-conductor line through a properly designed impedance-matching circuit. A suitable circuit is given in Fig. 21-48. An antenna coupler can be used for the purpose. In the balanced tank circuit the "antenna" or parallel components on the line tend to balance out and so are not passed on to the s.w.r. bridge. It is essential that L_1 be coupled to a "cold" point on L_2 to minimize capacitive coupling,

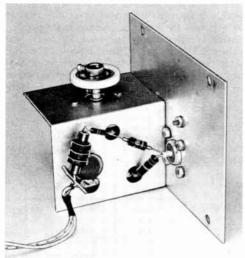


Fig. 21-47 — All components except the meter are mounted on one of the removable sides of the box. The variable capacitor is mounted on an L-shaped piece of aluminum (with half-inch lips on the inner edge for bolting to the box side) 2 inches wide, 2½ inches high and 2¾ inches deep, to shield the capacitor from the other components. The terminals project through holes as shown, with associated components mounted directly on them and the load connector, J_z . Since the rotor of C_1 must not be grounded, the capacitor is operated by an extension shaft and insulated coupling.

The lead from J_1 to C_{1A} should go directly from the input connector to the capacitor terminal (lower right) to which the 68-ohm resistor is attached. The 4700-ohm resistor is soldered across J_1 .

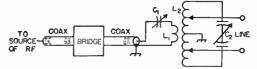


Fig. 21-48—Circuit for using coaxial s.w.r. bridge for measurements on parallel-conductor lines. Values of circuit components are identical with those used for the similar "antenna-coupler" circuit dscussed in the chapter on transmission lines.

and also desirable that the center of L_2 be grounded to the chassis on which the circuit is mounted. Values should be such that L_2C_2 can be tuned to the operating frequency and that L_1 provides sufficient coupling, as described in the transmission-line chapter. The measurement procedure is as follows:

Connect a noninductive ($\frac{1}{2}$ - or 1-watt carbon) resistor, having the same value as the characteristic impedance of the parallel-conductor line, to the "line" terminals. Apply r.f. to the bridge, adjust the taps on L_2 (keeping them equidistant from the center), while varying the capacitance of C_1 and C_2 , until the bridge shows a null. After the null is obtained, do not touch any of the circuit adjustments. Next, short-circuit the "line" terminals and adjust the r.f. input until the bridge voltmeter reads full scale. Remove the short-circuit and test resistor, and connect the regular transmission line. The bridge will then indicate the standing-wave ratio on the line.

The circuit requires rematching, with the test resistor, whenever the frequency is

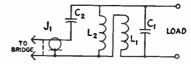



Fig. 21-49—Tuned balun for coupling between balanced and unbalanced lines. L_1 and L_2 should be built as a bifilar winding to get as tight coupling as possible between them. Typical constants are as follows:

4 μμf.	420 μμf.
39 μμf.	0.0015 μf.
None	0.001 μf.
62 μμf.	0.0045 #f.
	62 μμf.

Capacitors in unit shown in Fig. 21-50 are NPO disk ceramic. Units may be paralleled to obtain proper capacitance.

Fig. 21-50 — Balun construction (W2ZE). 150-ohm Twin-lead may be used for the bifilar winding in place of the ordinary wire shown. Symmetrical construction with tight coupling between the two coils is essential to good performance.



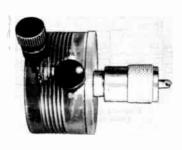

changed appreciably. It can, however, be used over a portion of an amateur band without readjustment, with negligible error.

Impedance Measurements

Measurements on parallel-conductor lines and other balanced loads can be made with the impedance bridge previously described by using a balun of the type shown schematically in Fig. 21-49. This is an autotransformer having a 2-to-1 turns ratio and thus provides a 4-to-1 step-down in impedance from a balanced load to the output circuit of the bridge, one side of which is grounded. L₁ and L₂ must be as tightly coupled as possible, and so should be constructed as a bifilar winding. The circuit is resonated to the operating frequency by C_1 , and C_2 serves to tune out any residual reactance that may be present because the coupling between the two coils is not quite perfect.

Fig. 21-50 shows one method of construct-

ing such a balun. The two interwound coils are made as nearly identical as possible, the "finish" end of the first being connected to the "start" end of the second through a short lead running under the winding inside the form. The center of this lead is tapped to give the connection to the shell side of the coax connector. C_1 should be chosen to resonate the circuit at the center of the band for which the balun is designed with J_1 open, and C_2 should resonate the circuit to the same frequency with both J_1 and the "load" terminals shorted. The frequency checks may be made with a grid-dip meter. (For further details, see QST for August, 1955.)

With the balun in use the bridge is operated in the same way as previously described, except that all impedance readings must be multiplied by 4. The balun also may be used for s.w.r. measurements on 300-ohm line in conjunction with a resistance bridge designed for 75-ohm coaxial line.

THE OSCILLOSCOPE

The cathode-ray oscilloscope gives a visual representation of signals at both audio and radio frequencies and can therefore be used for many types of measurements that are not possible with instruments of the types discussed earlier in this chapter. In amateur work, one of the principal uses of the scope is for displaying an amplitude-modulated signal so a phone transmitter can be adjusted for proper modulation and continuously monitored to keep the modulation precentage within proper limits. For this purpose a very simple circuit will suffice, and a typical circuit is described later in this section.

The versatility of the scope can be greatly increased by adding amplifiers and linear deflection circuits, but the design and adjustment of such circuits tends to be complicated if optimum performance is to be secured, and is somewhat outside the field of this section. Special components are generally required. Oscilloscope kits for home assembly are available from a number of suppliers, and since their cost compares very favorably with that of a home-built instrument of comparable design, they are recommended for se-

rious consideration by those who have need for or are interested in the wide range of measurements that is possible with a fullyequipped scope.

CATHODE-RAY TUBES

The heart of the oscilloscope is the cathoderay tube, a vacuum tube in which the electrons emitted from a hot cathode are first accelerated to give them considerable velocity, then formed into a beam, and finally allowed to strike a special translucent screen which fluoresces, or gives off light at the point where the beam strikes. A beam of moving electrons can be moved laterally, or deflected, by electric or magnetic fields, and since its weight and interia are negligibly small, it can be made to follow instantly the variations in periodically-changing fields at both audio and radio frequencies.

The electrode arrangement that forms the electrons into a beam is called the electron gun. In the simple tube structure shown in Fig. 21-51, the gun consists of the cathode, grid, and anodes Nos. 1 and 2. The intensity

542 MEASUREMENTS

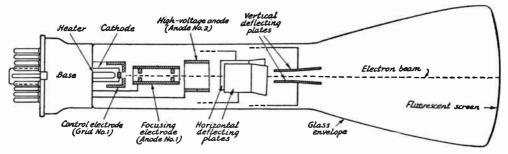


Fig. 21-51—Typical construction for a cathode-ray tube of the electrostatic-deflection type.

of the electron beam is regulated by the grid in the same way as in an ordinary tube. Anode No. 1 is operated at a positive potential with respect to the cathode, thus accelerating the electrons that pass through the grid, and is provided with small apertures through which the electron stream passes. On emerging from the apertures the electrons are traveling in practically parallel straight-line paths. The electrostatic fields set up by the potentials on anode No. 1 and anode No. 2 form an electron lens system which makes the electron paths converge or focus to a point at the fluorescent screen. The potential on anode No. 2 is usually fixed, while that on anode No. 1 is varied to bring the beam into focus. Anode No. 1 is, therefore, called the focusing electrode.

Electrostatic deflection, the type generally used in the smaller tubes, is produced by deflecting plates. Two sets of plates are placed at right angles to each other, as indicated in Fig. 21-51. The fields are created by applying suitable voltages between the two plates of each pair. Usually one plate of each pair is connected to anode No. 2, to establish the polarities of the vertical and horizontal fields with respect to the beam and to each other.

Formation of Patterns


When periodically-varying voltages are applied to the two sets of deflecting plates, the path traced by the fluorescent spot forms a pattern that is stationary so long as the amplitude and phase relationships of the voltages remain unchanged. Fig. 21-52 shows how one such pattern is formed. The horizontal sweep voltage is assumed to have the "sawtooth" waveshape indicated. With no voltage applied to the vertical plates the trace simply sweeps from left to right across the screen along the horizontal axis X-X' until the instant H is reached, when it reverses direction and snaps back to the starting point. The sine-wave voltage applied to the vertical plates similarly would trace a line along the axis Y-Y' in the absence of any deflecting voltage on the horizontal plates. However, when both voltages are present the position of the spot at any instant depends upon the voltages on both sets of plates at that instant. Thus at time

B the horizontal voltage has moved the spot a short distance to the right and the vertical voltage has similarly moved it upward, so that it reaches the actual position B' on the screen. The resulting trace is easily followed from the other indicated positions, which are taken at equal time intervals.

Types of Sweeps

A sawtooth sweep-voltage wave shape, such as is shown in Fig. 21-52, is called a linear sweep, because the deflection in the horizontal direction is directly proportional to time. If the sweep were perfect the fly-back time, or time taken for the spot to return from the end (H) to the beginning (I or A) of the horizontal trace, would be zero, so that the line HI would be perpendicular to the axis Y-Y'. Although the fly-back time cannot be made zero in practicable sweep-voltage generators it can be made quite small in comparison to the time of the desired trace AH, at least at most frequencies within the audio range. The line H'I' is called the return trace; with a linear sweep it is less brilliant than the pattern, because the spot is moving much more rapidly during the fly-back time than during the time of the main trace.

The linear sweep shows the shape of the

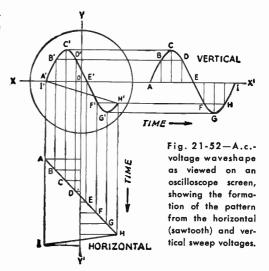

wave in the same way that it is usually represented graphically. If the period of the a.c. voltage applied to the vertical plates is considerably less than the time taken to sweep horizontally across the screen, several cycles of the vertical or "signal" voltage will appear in the pattern.

For many amateur purposes a satisfactory horizontal sweep is simply a 60-cycle voltage of adjustable amplitude. In modulation monitoring (described in the chapter on amplitude modulation) audio-frequency voltage can be taken from the modulator to supply the horizontal sweep. For examination of audio-frequency wave forms, the linear sweep is essential. Its frequency should be adjustable over the entire range of audio frequencies to be inspected on the oscilloscope.

Lissajous Figures

When sinusoidal a.c. voltages are applied to the two sets of deflecting plates in the oscilloscope the resultant pattern depends on the relative amplitudes, frequencies and phase of the two voltages. If the ratio between the two frequencies is constant and can be expressed in integers a stationary pattern will be produced. This makes it possible to use the oscilloscope for determining an unknown frequency, provided a variable frequency standard is available, or for determining calibration points for a variable-frequency oscillator if a few known frequencies are available for comparison.

The stationary patterns obtained in this way are called Lissajous figures. Examples of some of the simpler Lissajous figures are given in Fig. 21-53. The frequency ratio is found by counting the number of loops along two adjacent edges. Thus in the third figure from the top there are three loops along a horizontal edge and only one along the vertical, so the ratio of the vertical frequency to the horizontal frequency is 3 to 1. Similarly, in the fifth figure from the top there are four loops along the horizontal edge and three along the vertical edge, giving a ratio of 4 to 3. Assuming that the known frequency is applied to the horizontal plates, the unknown frequency is

$$f_2 = \frac{n_2}{n_1} f_1$$


where $f_1 = \text{known frequency applied to horizontal plates}$,

f₂ = unknown frequency applied to vertical plates,

 $n_1 =$ number of loops along a vertical edge, and

n₂ = number of loops along a horizontal edge.

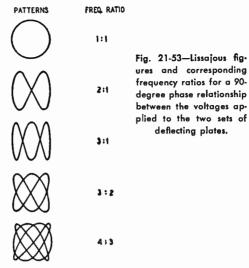An important application of Lissajous figures is in the calibration of audio-frequency signal generators. For very low frequencies the 60-cycle power-line frequency is held accurately enough to be used as a standard in



most localities. The medium audio-frequency range can be covered by comparison with the 440- and 600-cycle modulation on the WWV transmissions. An oscilloscope having both horizontal and vertical amplifiers is desirable, since it is convenient to have a means for adjusting the voltages applied to the deflection plates to secure a suitable pattern size. It is possible to calibrate over a 10-to-1 range, both upwards and downwards, from each of the latter frequencies and thus cover the audio range useful for voice communication.

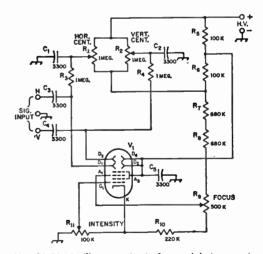


Fig. 21-54—Oscilloscope circuit for modulation monitoring. Constants are for 1500- to 2500-volt h.v. supply. For 1000-1500 volts, omit R₈ and connect the bottom end of R₇ to the top end of R₉.

C₁-C₅, inc.—3000-volt disk ceramic.

R₁, R₂, R₉, R₁₁-Volume-control type, linear taper.

R₉, R₄, R₅, R₆, R₁₀—½ watt.

R₇, R₈-1 watt.

V₁—Electrostatic-deflection cathode-ray tube, 2- to 5inch. See tube tables for base connections and heater ratings of type chosen.

Basic Oscilloscope Circuit

The essential oscilloscope circuit is shown in Fig. 21-54. The minimum requirements are supplying the various electrode potentials, plus controls for focusing and centering the spot on the face of the tube and adjusting the spot intensity. The circuit of Fig. 21-54 can be used with electrostatic-deflection tubes from two to five inches in face diameter, with voltages up to 2500. This includes practically all the types popular for small oscilloscopes.

The circuit has provision for introducing signal voltages to the two sets of deflecting plates. Either set of deflecting electrodes $(D_1D_2$, or D_3D_4) may be used for either horizontal or vertical deflection, depending on how the tube is mounted.

The high voltage may be taken from a transmitter power supply if desired. The current is only a milliampere or so. The voltage preferably should be constant, such as is obtained from a supply having a constant load—e.g., the supply for the Class C amplifier in an a.m. transmitter.


In the circuit of Fig. 21-54 the centering controls are at the full supply voltage above ground and therefore should be carefully insulated by being mounted on bakelite or similar material rather than directly on a metal panel or chassis. Insulated couplings or extension shafts should be used. The focusing control is also several hundred volts above ground and should be similarly insulated.

The tube should be protected from stray magnetic fields, either by enclosing it in an iron or steel box or by using one of the special c.r. tube shields available. If the heater transformer (or other transformer) is mounted in the same cabinet, care must be used to place it so the stray field around it does not deflect the spot. The spot cannot be focussed to a fine point when influenced by a transformer field.

Modulation Monitoring

The addition of Fig. 21-55 to the basic circuit of Fig. 21-54 provides all that is necessary for modulation checking. The r.f. from the transmitter is applied to the vertical plates through a tuned circuit L_1C_1 and link L_2 . When adjusted to the transmitter operating frequency the tuned circuit furnishes ample deflection voltage even from a low-power transmitter, and C_1 can be used to control the pattern height.

Deflection voltage for the horizontal plates can be taken from the modulation transformer secondary of an a.m. transmitter, or 60-cycle deflection can be used to give a wave-envelope type pattern. In either case a maximum of about 200 volts r.m.s. will give full-width deflection. This voltage is almost independent of the size of c.r. tube used. Methods of using such a scope for modulation checking are described in the chapter on amplitude modulation.

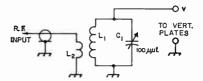

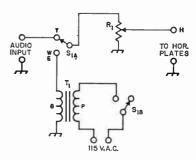


Fig. 21-55—Circuits for supplying r.f., audio, and a.c. voltages to oscilloscope deflection plates for modulation monitoring.

C₁-100-µµf. variable, receiving type.

L₁--1.75 Mc.: 30 enam. close-wound on 1-inch form, coil length ¾ inch.

3.5-8 Mc.: 30 turns No. 22 enam., close-wound on 1-inch form.

13-30 Mc.; 7 turns No. 22, spread to ¾ inch length on 1-inch form.

Ls—2 or more turns, as required for sufficient coupling, at cold end of L₁.

R₁-Volume control, 0.25 megohm or more.

S1-D.p.d.t. switch.

T₁—Interstage audio transformer, any type. Use secondary-to-primary turns ratio of 1-to-1 to 2-to-1.

Frequency Limitations of Oscilloscopes

Most commercial or kitted oscilloscopes include vacuum-tube amplifiers between the input terminals and the deflection plates, to increase the sensitivity and usefulness of the instrument. Depending upon the construction of the amplifiers, their useful frequency range may be only as high as several hundred kc., although more expensive instruments will include amplifiers that work in the megacycle range. The operator should acquaint himself with the frequency limitations of the 'scope through study of the specifications, since attempts to pass, e.g., a 450-kc. i.f. signal through an amplifier that cuts off at 100 kc. are doomed to failure. No such frequency limits apply when the connection is made directly to the deflection plates, and consequently r.f. at 20 to 30 Mc. can be applied by the method shown in Fig. 21-55. A practical limitation will be found when r.f. from the vertical plates is (stray) capacitively coupled to the horizontal-deflection plates; this will show as a thickening of the trace. In some instances it can be reduced by r.f. bypassing of the horizontal deflection plates.

Assembling a Station

The actual location inside the house of the "shack"—the room where the transmitter and receiver are located—depends, of course, on the free space available for amateur activities. Fortunate indeed is the amateur with a separate room that he can reserve for his hobby, or the few who can have a special small building separate from the main house. However, most amateurs must share a room with other domestic activities, and amateur stations will be found tucked away in a corner of the living room, a bedroom, a large closet, or even under the kitchen stove! A spot in the cellar or the attic can almost be classed as a separate room, although it may lack the "finish" of a normal room.

Regardless of the location of the station, however, it should be designed for maximum operating convenience and safety. It is foolish to have the station arranged so that the throwing of several switches is required to go from "receive" to "transmit," just as it is silly to have the equipment arranged so that the operator is in an uncomfortable and cramped position during his operating hours. The reason for building the station as safe as possible is obvious, if you are interested in spending a number of years with your hobby!

CONVENIENCE


The first consideration in any amateur station is the operating position, which includes the operator's table and chair and the pieces of equipment that are in constant use (the receiver, send-receive switch, and key or microphone). The table should be as large as possible, to allow sufficient room for the receiver or receivers, frequency-measuring equipment, monitoring equipment, control switches, and keys and microphones, with enough space left over for the log-

book, a pad and pencil, and perhaps a large ash tray. Suitable space should be included for radiogram blanks and a call book, if these accessories are in frequent use. If the table is small, or the number of pieces of equipment is large, it is often necessary to build a shelf or rack for the auxiliary equipment, or to mount it in some less convenient location in or under the table. If one has the facilities, a semicircular "console" can be built of wood, or a simpler solution is to use two small wooden cabinets to support a table top of wood or Masonite. A flush-type door will make an excellent table top. Homebuilt tables or consoles can be finished in any of the available oil stains, varnishes, paints or lacquers. Many operators use a large piece of plate glass over part of their table, since it furnishes a good writing surface and can cover miscellaneous charts and tables, prefix lists, operating aids, calendar, and similar accessories.

If the major interests never require frequent band changing, or frequency changing within a band, the transmitter can be located some distance from the operator, in a location where the meters can be observed from time to time (and the color of the tube plates noted!). If frequent band or frequency changes are a part of the usual operating procedure, the transmitter should be mounted close to the operator, either along one side or above the receiver, so that the controls are easily accessible without the need for leaving the operating position.

A compromise arrangement would place the v.f.o. or crystal-switched oscillator at the operating position and the transmitter in some convenient location not adjacent to the operator. Since it is usually possible to operate over a portion of a band without retuning the trans-

Here is a station that is completely homebuilt. At the left is a linear amplifier and power supply in a floor-mounted rack. On the console, at the left, are an antenna patch box and t.r. switch and the station control panel. In center of the console is a threetiered rack containing a ham-bands only receiver at the bottom, a sideband exciter in the middle, and above that a converter for frequencies outside the ham bands. At the far right is a frequency meter and monitor. The console is also home-built, in a shape that provides good operating convenience. (W2TBZ/4, Springfield, Va.)

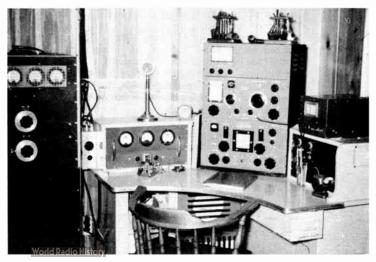

mitter stages, an operating position of this type is an advantage over one in which the operator must leave his position to change frequency.

Controls

The operator has an excellent chance to exercise his ingenuity in the location of the operating controls. The most important controls in the station are the receiver tuning dial and the send-receive switch. The receiver tuning dial should be located four to eight inches above the operating table, and if this requires mounting the receiver off the table, a small shelf or bracket will do the trick. With the single exception of the amateur whose work is almost entirely in traffic or rag-chew nets, which require little or no attention to the receiver, it will be found that the operator's hand is on the receiver tuning dial most of the time. If the tuning knob is too high or too low, the hand gets cramped after an extended period of operating, hence the importance of a properly located receiver. The majority of c.w. operators tune with the left hand, preferring to leave the right hand free for copying messages and handling the key, and so the receiver should be mounted where the knob can be reached by the left hand. Phone operators aren't tied down this way, and tune the communications receiver with the hand that is more convenient.

The hand key should be fastened securely to the table, in a line just outside the right shoulder and far enough back from the front edge of the table so that the elbow can rest on the table. A good location for the semiautomatic or "bug" key is right next to the hand-key, although some operators prefer to mount the automatic key in front of them on the left, so that the right forearm rests on the table parallel to the front edge.

The best location for the microphone is directly in front of the operator, so that he doesn't have to shout across the table into it, or run up the speech-amplifier gain so high that all manner of external sounds are picked up. If the microphone is supported by a boom or by a flexible "goose neck," it can be placed in front of the operator without its base taking up valuable table space.

In any amateur station worthy of the name, it should be necessary to throw no more than one switch to go from the "receive" to the "transmit" condition. In phone stations, this switch should be located where it can be easily reached by the hand that isn't on the receiver. In the case of c.w. operation, this switch is most conveniently located to the right or left of the key, although some operators prefer to have it mounted on the left-hand side of the operating position and work it with the left hand while the right hand is on the key. Either location is satisfactory, of course, and the choice depends upon personal preference. Some operators use a foot-controlled switch, which is a convenience but doesn't allow too much freedom of position during long operating periods.

If the microphone is hand-held during phone

operation, a "push-to-talk" switch on the microphone is convenient, but hand-held microphones tie up the use of one hand and are not too desirable, although they are widely used in mobile and portable work.

The location of other switches, such as those used to control power supplies, filaments, phone/c.w. change-over and the like, is of no particular importance, and they can be located on the unit with which they are associated. This is not strictly true in the case of the phone/c.w. DX man, who sometimes has need to change in a hurry from c.w. to phone. In this case, the change-over switch should be at the operating table, although the actual change-over should be done by a relay controlled by the switch.

If a rotary beam is used the control of the beam should be convenient to the operator. The direction indicator, however, can be located anywhere within sight of the operator, and does not have to be located on the operating table unless it is included with the control.

Frequency Spotting

In a station where a v.f.o. is used, or where a number of crystals are available, the operator should be able to turn on only the oscillator of his transmitter, so that he can spot accurately his location in the band with respect to other stations. This allows him to see if he has anything like a clear channel, or to see what his frequency is with respect to another station. Such a provision can be part of the "send-receive" switch. Switches are available with a center "off" position, a "hold" position on one side, for turning on the oscillator only, and a "lock" position on the other side for turning on the transmitter and antenna relay. If oscillator keying is used, the key serves the same purpose, provided a "send-receive" switch is available to turn off the high-voltage supplies and prevent a signal going out on the air during adjustment of the oscillator frequency.

For phone operation, the telegraph key or an auxiliary switch can control the transmitter oscillator, and the "send-receive" switch can then be wired into the control system so as to control the oscillator as well as the other circuits.

Comfort

Of prime importance is the comfort of the operator. If you find yourself getting tired after a short period of operating, examine your station to find what causes the fatigue. It may be that the chair is too soft or hasn't a straight back or is the wrong height for you. The key or receiver may be located so that you assume an uncomfortable position while using them. If you get sleepy fast, the ventilation may be at fault. (Or you may need sleep!)

POWER CONNECTIONS AND CONTROL

Following a few simple rules in wiring your power supplies and control circuits will make it an easy job to change units in the station. If

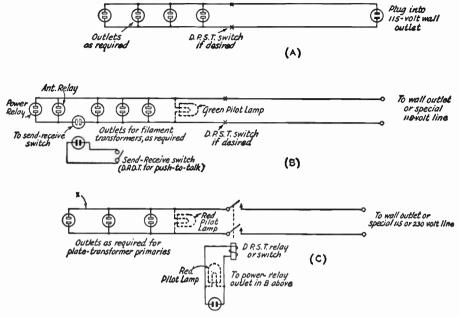


Fig. 22-1—Power circuits for a high-power station. A shows the outlets for the receiver, monitoring equipment, speech amplifier and the like. The outlets should be mounted inconspicuously on the operating table. B shows the transmitter filament circuits and control-relay circuits, if the latter are used. C shows the plate-transformer primary circuits, controlled by the power relay. Where 230- and 115-volt primaries are controlled simultaneously, point "X" should connect to the "neutral" or common. A heavy-duty switch can be used instead of the relay, in which case the antenna relay would be connected in circuit C. If 115-volt pilot lamps are used, they can be connected as shown. Lower-voltage lamps must be connected across suitable windings on transformers. With "push-to-talk" operation, the "send-receive" switch can be a d.p.d.t. affair, with the second pole controlling the "on-off" circuit of the receiver.

the station is planned in this way from the start, or if the rules are recalled when you are rebuilding, you will find it a simple matter to revise your station from time to time without a major rewiring job

It is neater and safer to run a single pair of wires from the outlet over to the operating table or some central point, rather than to use a number of adapters at the wall outlet.

Interconnections

The wiring of any station will entail two or three common circuits, as shown in Fig. 22-1. The circuit for the receiver, monitoring equipment and the like, assuming it to be taken from a wall outlet, should be run from the wall to an inconspicuous point on the operating table, where it terminates in a multiple outlet large enough to handle the required number of plugs. A single switch between the wall outlet and the receptacle will then turn on all of this equipment at one time.

The second common circuit in the station is that supplying voltage to rectifier- and transmitter-tube filaments, bias supplies, and anything else that is not switched on and off during transmit and receive periods. The coil power for control relays should also be obtained from this circuit. The power for this circuit can come from a wall outlet or from the transmitter line, if a

special one has been installed for the station.

The third circuit is the one that furnishes power to the plate-supply transformers for the r.f. stages and for the modulator. (See chapter on Power Supplies for high-power considerations.) When it is opened, the transmitter is disabled except for the filaments, and the transmitter should be safe to work on. However, one always feels safer when working on the transmitter if he has turned off every power source.

With these three circuits established, it becomes a simple matter to arrange the station for different conditions and with new units. Anything on the operating table that runs all the time ties into the first circuit. Any new power supply or r.f. unit gets its filament power from the second circuit. Since the third circuit is controlled by the send-receive switch (or relay), any power-supply primary that is to be switched on and off for send and receive connects to circuit C.

Break-In and Push-To-Talk

In c.w. operation, "break-in" is any system that allows the transmitting operator to hear the other station's signal during the "key-up" periods between characters and letters. This allows the sending station to be "broken" by the receiving station at any time, to shorten calls, ask for "fills" in messages, and speed up opera-

tion in general. With present techniques, it requires the use of a separate receiving antenna or a "t.r. box" and, with high power, some means for protecting the receiver from the transmitter when the key is "down." Several methods, applicable to high-power stations, are described in Chapter Eight. If the transmitter is low-powered (50 watts or so), no special equipment is required except the separate receiving antenna and a receiver that "recovers" fast. Where break-in operation is used, there should be a switch on the operating table to turn off the plate supplies when adjusting the oscillator to a new frequency, although during all break-in work this switch will be closed.

"Push-to-talk" is an expression derived from the "push" switch on some microphones, and it means a phone station with a single control for all change-over functions. Strictly speaking, it should apply only to a station where this single send-receive switch must be held in place during transmission periods, but any fast-acting switch will give practically the same effect. A control switch with a center "off" position, and one "hold" and one "lock" position, will give more flexibility than a straight "push" switch. The one switch must control the transmitter power supplies, the receiver "on-off" circuit and, if one is used, the antenna change-over relay. The receiver control is necessary to disable its output during transmit periods, to avoid acoustic feedback.

Switches and Relays

It is dangerous to use an overloaded switch in the power circuits. After it has been used for some time, it may fail, leaving the power on the circuit even after the switch is thrown to the "off" position. For this reason, large switches, or relays with adequate ratings, should be used to control the plate power. Relays are rated by coil voltages (for their control circuits) and by their contact current and voltage ratings. Any switch or relay for the power-control circuits of an amateur station should be conservatively rated; overloading a switch or relay is very poor



economy. Switches rated at 20 amperes at 125 volts will handle the switching of circuits at the kilowatt level, but the small toggle switches rated 3 amperes at 125 volts should be used only in circuits up to about 150 watts.

When relays are used, the send-receive switch closes the circuits to their coils. The energized relays close the heavy-duty relay contacts. Since the relay contacts are in the power circuit being controlled, the switch handles only the relay-coil current. As a consequence, this switch can have a low current rating.

SAFETY

Of prime importance in the layout of the station is the personal safety of the operator and of visitors, invited or otherwise, during normal operating practice. If there are small children in the house, every step must be taken to prevent their accidental contact with power leads of any voltage. A locked room is a fine idea, if it is possible, otherwise housing the transmitter and power supplies in metal cabinets is an excellent, although expensive, solution. Lacking a metal cabinet, a wooden cabinet or a wooden framework covered with wire screen is the nextbest solution. Many stations have the power supplies housed in metal cabinets in the operating room or in a closet or basement, and this cabinet or entry is kept locked - with the key out of reach of everyone but the operator. The power leads are run through conduit to the transmitter, using ignition cable for the high-voltage leads. If the power supplies and transmitter are in the same cabinet, a lock-type main switch for the incoming line power is a good precaution.

A simple substitute for a lock-type main switch is an ordinary line plug with a short connecting wire between the two pins. By wiring a female receptacle in series with the main power line in the transmitter, the shorting plug will act as the main safety lock. When the plug is removed and hidden, it will be impossible to energize the transmitter, and a stranger or child isn't likely to spot or suspect the open receptacle.

An essential adjunct to any station is a **short**ing stick for discharging any high voltage to ground before any work is done in the transmitter. Even if interlocks and power-supply bleeders are used, the failure of one or more of these

This neat "built-in" installation features separate finals and exciters for each band, along with room for receiver, frequency meter, oscilloscope, Q multiplier and v.h.f. converter. All units are mounted on the three large panels; the panels are hinged at the bottom sa that they can be lowered for service work on the individual units. A common power supply is used, and band-changing consists of turning on the filaments in the desired r.f. section.

(W9OVO, Sturgeon Bay, Wisc.)

components may leave the transmitter in a dangerous condition. The shorting stick is made by mounting a small metal hook, of wire or rod, on one end of a dry stick or bakelite rod. A piece of ignition cable or other well-insulated wire is then run from the hook on the stick to the chassis or common ground of the transmitter, and the stick is hung alongside the transmitter. Whenever the power is turned off in the transmitter to permit work on the rig, the shorting stick is first used to touch the several high-voltage leads (plate r.f. choke, filter capacitor, tube plate connection, etc.) to insure that there is no high voltage at any of these points. This simple device has saved many a life. Use it!

Fusing

A minor hazard in the amateur station is the possibility of fire through the failure of a component. If the failure is complete and the component is large, the house fuses will generally blow. However, it is unwise and inconvenient to depend upon the house fuses to protect the lines running to the radio equipment, and every power supply should have its primary circuit individually fused, at about 150 to 200 per cent of the maximum rating of the supply. Circuit breakers can be used instead of fuses if desired.

Wiring

Control-circuit wires running between the operating position and a transmitter in another part of the room should be hidden, if possible. This can be done by running the wires under the floor or behind the base molding, bringing the wires out to terminal boxes or regular wall fixtures. Such construction, however, is generally only possible in elaborate installations, and the average amateur must content himself with trying to make the wires as inconspicuous as possible. If several pairs of leads must be run from the op-

erating table to the transmitter, as is generally the case, a single piece of rubber- or vinylcovered multiconductor cable will always look neater than several pieces of rubber-covered lamp cord, and it is much easier to sweep around or dust.

The antenna wires always present a problem, unless coaxial-line feed is used. Open-wire line from the point of entry of the antenna line should always be arranged neatly, and it is generally best to support it at several points. Many operators prefer to mount any antenna-tuning assemblies right at the point of entry of the feedline, together with an antenna changeover relay (if one is used), and then the link from the tuning assembly to the transmitter can be made of inconspicuous coaxial line. If the transmitter is mounted near the point of entry of the line, it simplifies the problem of "What to do with the feeders?"

Lightning and Fire Protection

The National Electrical Code (NFPA No. 70) adopted by the National Fire Protection Association, although purely advisory as far as the NFPA is concerned, is of interest because it is widely used in law and for legal regulatory purposes. Article 810 deals with radio and television equipment, and Section C treats specifically amateur transmitting and receiving stations. Pertinent paragraphs are reprinted below:

810-11. Material. Antenna and lead-in conductors shall be of hard-drawn copper, bronze, aluminum alloy, copper-clad steel or other high-strength, corrosion-resistant material. Soft-drawn or medium-drawn copper may be used for lead-in conductors where the maximum span between points of support is less than 35 feet.

810-12. Supports. Outdoor antenna and lead-in conductors shall be securely supported. They shall not be attached to poles or similar structures carrying electric light or power wires or trolley wires of more than 250 volts between conductors. Insulators supporting the antenna conductors shall have sufficient

A neat operating bench can be built from wood and covered with linoleum. There is enough room on the table shown here to house the transmitter, receiver, and numerous adjuncts and accessories. Interconnecting wiring is run behind the units or underneath the table. (W3AQN, York, Pa.)



mechanical strength to safely support the conductors. Lead-in conductors shall be securely attached to the antenna.

810-13. Avoidance of Contacts with Conductors of Other Systems. Outdoor antenna and lead-in conductors from an antenna to a building shall not cross over electric light or power circuits and shall be kept well away from all such circuits so as to avoid the possibility of accidental contact. Where proximity to electric light and power service conductors of less than 250 volts between conductors cannot be avoided, the installation shall be such as to provide a clearance of at least two feet. It is recommended that antenna conductors be so installed as not to cross under electric light or power conductors.

810-14. Splices. Splices and joints in antenna span shall be made with approved splicing devices or by such other means as will not appreciably weaken the conductors.

Soldering may ordinarily be expected to weaken the conductor. Therefore, the joint should be mechanically secure before soldering.

810-15. Grounding. Masts and metal structures supporting antennas shall be permanently and effectively grounded, without intervening splice or connection. 810-52. Size of Antenna. Antennas for amateur

transmitting and receiving stations shall be of a size not less than given in Table 810-52.

Table 8	310-52	
Size of Amateur-Sta	tion Outdoor A	Intenna
	Minimum Condu	
	When Maxin Span Lei	
	Less than	Over
Material	150 feet	150 feet
Hard-drawn copper Copper-clad steel, bronze or other high-strength	14	10
material	14	12

810-53. Size of Lead-In Conductors. Lead-in conductors for transmitting stations shall, for various maximum span lengths, be of a size at least as great as that of conductors for antenna specified in 810-52.

810-54. Clearance on Building. Antenna conductors for transmitting stations, attached to buildings, shall be firmly mounted at least 3 inches clear of the surface of the building on nonabsorptive insulating supports, such as treated pins or brackets, equipped with insulators having not less than 3-inch creepage and airgap distances. Lead-in conductors attached to buildings shall also conform to these requirements, except when they are enclosed in a continuous metal shield which is permanently and effectively grounded. In this latter case the metallic shield may also be used as a conductor.

810-55. Entrance to Building. Except where protected with a continuous metal shield which is permenently and effectively grounded, lead-in conductors for transmitting stations shall enter building by one of the following methods:

(a) Through a rigid, noncombustible, nonabsorptive insulating tube or bushing.

(b) Through an opening provided for the purpose in which the entrance conductors are firmly secured so as to provide a clearance of at least 2 inches.
(c) Through a drilled window pane.

810-56. Protection Against Accidental Contact. Lead-in conductors to radio transmitters shall be so located or installed as to make accidental contact with them difficult.

810-57. Lightning Arrestors-Transmitting Stations. Each conductor of a lead-in for outdoor antenna shall be provided with a lightning arrestor or other suitable means which will drain static charges from the antenna system.

Exception No. 1. When protected by a continuous metallic shield which is permanently and effectively grounded

Exception No. 2. Where the antenna is permanently and effectively grounded.

810-21. Grounding Material. The grounding conductor shall, unless otherwise specified, be of copper, aluminum, copper-clad steel, bronze, or other corrosion-resistant material.

810-22. Insulation. The grounding conductors may be uninsulated.

810-23. Supports. The grounding conductors shall be securely fastened in place and may be directly attached to the surface wired over without the use of insulating supports. Where proper support cannot be provided the size of the grounding conductor shall be increased proportionately.

810-24. Mechanical Protection. The grounding conductor shall be protected where exposed to physical damage or the size of the grounding conductor shall be increased proportionately to compensate for the lack of protection.

810-25. Run in Straight Line. The grounding conductor shall be run in as straight a line as practicable from the antenna mast and/or lightning arrestor to the grounding electrode.

810-26. Grounding Electrode. The grounding conductor shall be connected to a metallic underground water piping system. Where the building is not supplied with a (suitable) water system (one buried deeper than ten feet) the connection shall be made to the metal frame of the building when effectively grounded or to a grounding electrode. At a penthouse or similar location the ground conductor may be connected to a water pipe or rigid conduit. 810-27. Grounding Conductor. The grounding con-

ductor may be run either inside or outside the build-

ing.

810-59. Size of Protective Ground. The protective ground conductor for transmitting stations shall be as large as the lead-in, but not smaller than No. 10 copper, bronze or copper-clad steel.

810-60. Size of Operating Grounding Conductor. The operating grounding conductor for transmitting stations shall be not less than No. 14 copper or its equivalent.

810-70. Clearance from Other Conductors. All conductors inside the building shall be separated at least 4 inches from the conductors of other light or signal circuit unless separated therefrom by conduit or some firmly fixed non-conductor such as porcelain tubes or flexible tubing.

810-71. General. Transmitters shall comply with the following:

(a) Enclosing. The transmitter shall be enclosed in a metal frame or grille, or separated from the operating space by a barrier or other equivalent means, all metallic parts of which are effectually connected to ground.

(b) Grounding of Controls. All external metallic handles and controls accessible to the operating personnel shall be effectually grounded.

No circuit in excess of 150 volts between conductors should have any parts exposed to direct contact. A complete dead-front type of switchboard is pre-

ferred. (c) Interlocks on Doors. All access doors shall be provided with interlocks which will disconnect all voltages in excess of 350 volts between conductors

when any access door is opened. (d) Audio Amplifiers. Audio amplifiers which are located outside the transmitter housing shall be suitably housed and shall be so located as to be readily accessible and adequately ventilated.

If coaxial line is used, compliance with 810-57 above is readily achieved by grounding the shield of the coax at the point where it is nearest to the ground outside the house. Use a heavy wire the aluminum wire sold for grounding TV antennas is good. If the cable can be run underground, one or more grounding stakes should be located at the point where the cable enters the ground, at the antenna end. A grounding stake, to be effective in soils of average conductivity, should

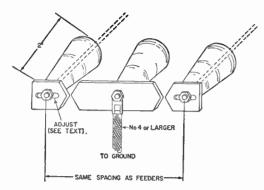


Fig. 22-2—A simple lightning arrester made from three stand-off or feed-through insulators and sections of brass or copper strap. It should be installed in the open-wire or Twin-Lead line at the point where it is nearest the ground outside the house. The heavy ground lead should be as short and direct as possible.

be not less than 8 feet long. Galvanized ¾-inch iron pipe is acceptable, as is ⅓-inch steel rod or ½-inch non-ferrous rod. Making connection to the outside of the outer conductor of the coaxial line will normally have no effect on the s.w.r. in the line, and consequently it can be done at any point or points. A commercial model of a lightning arrester for coaxial line is available.


Open-wire or Twin-Lead transmission lines can comply with 810-57 above through the use of a spark gap such as the one sketched in Fig. 22-2. The center contact should be grounded with a No. 4 or larger wire. The gaps can be made from

1/8 × 1/2-inch flat brass rod shaped as shown, and the gaps should be set sufficiently far apart to prevent flash-over during normal operation of the transmitter. Depending upon the power of the transmitter and the s.w.r. pattern on the line, the gap may run anything from 1/32 to 3/16 inch. It may spark intermittently when a thunderstorm is building up or is in the general area.

Rotary beams using a T or gamma match and with each element connected to the boom will usually be grounded through the supporting metal tower. If the antenna is mounted on a wooden pole or on the top of the house, a No. 4 or larger wire should be connected from the beam to the ground by the shortest and most direct route possible, using insulators where the wire comes close to the building. From a lightning-protection standpoint, it is desirable to run the coaxial and control lines from a beam down a metal tower and underground to the shack. If the tower is well grounded and the antenna is higher than any surrounding objects, the combination will serve well as a lightning rod.

The sole purpose of lightning rods or grounded roofs is to protect a building in case a lightning stroke occurs; there is no accepted evidence that any form of protection can prevent a stroke.*

Experiments have indicated that a high vertical conductor will generally divert to itself direct hits that might otherwise fall within a coneshaped space of which the apex is the top of the conductor and the base a circle of radius approximately two times the height of the conductor. Thus a radio mast may afford some protection to low adjacent structures, but only when low-impedance grounds are provided.

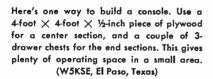



^{*} See "Code for Protection Against Lightning," National Bureau of Standards Handbook 46, for sale by the Superintendent of Documents, Washington 25, D.C.

BCI and **TVI**

Every amateur has the obligation to make sure that the operation of his station does not, because of any shortcomings in equipment, cause interference with other radio services. It is unfortunately true that much of the interference that amateurs cause to broadcast and television reception is directly the fault of b.c. and TV receiver construction. Nevertheless, the amateur can and should help to alleviate interference even though the responsibility for it does not lie with him.

Successful handling of interference cases requires winning the listener's cooperation. Here are a few pointers on how to go about it.

Clean House First

The first step obviously is to make sure that the transmitter has no radiations outside the bands assigned for amateur use. The best check on this is your own a.m. or TV receiver. It is always convincing if you can demonstrate that you do not interfere with reception in your own home.

Don't Hide Your Identity

Whenever you make equipment changes — or shift to a hitherto unused band or type of emission — that might be expected to change the interference situation, check with your neighbors. If no one is experiencing interference, so much the better; it does no harm to keep the neighborhood aware of the fact that you are operating without bothering anyone.

Should you change location, announce your presence and conduct occasional tests on the air, requesting anyone whose reception is being spoiled to let you know about it so steps may be taken to eliminate the trouble.

Act Promptly

The average person will tolerate a limited amount of interference, but the sooner you take steps to eliminate it, the more agreeable the listener will be; the longer he has to wait for you, the less willing he will be to cooperate.

Present Your Story Tactfully

When you interfere, it is natural for the complainant to assume that your transmitter is at fault. If you are certain that the trouble is not in your transmitter, explain to the listener that the reason lies in the receiver design, and that some modifications may have to be made in the receiver if he is to expect interference-free reception.

Arrange for Tests

Most listeners are not very competent observers of the various aspects of interference. If at all possible, enlist the help of another amateur and have him operate your transmitter while you see for yourself what happens at the affected receiver.

In General

In this "public relations" phase of the problem a great deal depends on your own attitude. Most people will be willing to meet you half way, particularly when the interference is not of long standing, if you as a person make a good impression. Your personal appearance is important. So is what you say about the receiver — no one takes kindly to hearing his possessions derided. If you discuss your interference problems on the air, do it in a constructive way — one calculated to increase listener cooperation, not destroy it.

INTERFERENCE WITH STANDARD BROADCASTING

Interference with a.m. broadcasting usually falls into one or more rather well-defined categories. An understanding of the general types of interference will avoid much cut-and-try in finding a cure.

Transmitter Defects

Out-of-band radiation is something that must be cured at the transmitter. Parasitic oscillations are a frequently unsuspected source of such radiations, and no transmitter can be considered satisfactory until it has been thoroughly checked for both low- and high-frequency parasitics. Very often parasitics show up only as transients, causing key clicks in c.w. transmitters and "splashes" or "burps" on modulation peaks in a.m. transmitters. Methods for detecting and eliminating parasitics are discussed in the transmitter chapter.

In c.w. transmitters the sharp make and break that occurs with unfiltered keying causes transients that, in theory, contain frequency components through the entire radio spectrum. Practically, they are often strong enough in the immediate vicinity of the transmitter to cause serious interference to broadcast reception. Key clicks can be eliminated by the methods detailed in the chapter on keying.

A distinction must be made between clicks generated in the transmitter itself and those set up by the mere opening and closing of the key contacts when current is flowing. The latter are of the same nature as the clicks heard in a receiver when a wall switch is thrown to turn a light on or off, and may be more troublesome nearby than the clicks that actually go out on the signal. A filter for eliminating them usually has to be installed as close as possible to the key contacts.

Overmodulation in a.m. phone transmitters generates transients similar to key clicks. It can be prevented either by using automatic systems for limiting the modulation to 100 per cent, or by continuously monitoring the modulation. Methods for both are described in the chapter on amplitude modulation.

BCI is frequently made worse by radiation from the power wiring or the r.f. transmission line. This is because the signal causing the interference, in such cases, is radiated from wiring that is nearer the broadcast receiver than the antenna itself. Much depends on the method used to couple the transmitter to the antenna, a subject that is discussed in the chapters on transmission lines and antennas. If it is at all possible the antenna itself should be placed so that it is not in close proximity to house wiring, telephone and power lines, and similar conductors.

Image and Oscillator-Harmonic Responses

Most present-day broadcast receivers use a built-in loop antenna as the grid circuit for the mixer stage. The selectivity is not especially high at the signal frequency. Furthermore, an appreciable amount of signal pick-up usually occurs on the a.c. line to which the receiver is connected, the signal so picked up being fed to the mixer grid by stray means.

As a result, strong signals from nearby transmitters, even though the transmitting frequency is far removed from the broadcast band, can force themselves to the mixer grid. They will normally be eliminated by the i.f. selectivity, except in cases where the transmitter frequency is the image of the broadcast signal to which the receiver is tuned, or when the transmitter frequency is so related to a harmonic of the broadcast receiver's local oscillator as to produce a beat at the intermediate frequency.

These image and oscillator-harmonic responses tune in and out on the broadcast receiver dial just like a broadcast signal, except that in the case of harmonic response the tuning rate is more rapid. Since most receivers use an intermediate frequency in the neighborhood of 455 kc., the interference is a true image only when the amateur transmitting frequency is in the 1800-kc. band. Oscillator-harmonic responses occur from 3.5- and 7-Mc. transmissions, and sometimes even from higher frequencies

Since images and harmonic responses occur

at definite frequencies on the receiver dial, it is possible to choose operating frequencies that will avoid putting such a response on top of the broadcast stations that are favored in the vicinity. While your signal may still be heard when the receiver is tuned off the local stations, it will at least not interfere with program reception.

There is little that can be done to most receivers to cure interference of this type except to reduce the amount of signal getting into the set through the a.c. line. A line filter such as is shown in Fig. 23-1 often will help accomplish this. The values used for the coils and capacitors are in general not critical. The effectiveness of the filter may depend considerably on the ground connection used, and it is advisable to use a short ground lead to a cold-water pipe if at all possible. The line cord from the set should be bunched up, to minimize the possibility of pick-up on the cord. It may be necessary to install the filter inside the receiver, so that the filter is connected between the line cord and the set wiring, in order to get satisfactory operation.

Cross-Modulation

With phone transmitters, there are occasionally cases where the voice is heard whenever the broadcast receiver is tuned to a b.c. station, but there is no interference when tuning between stations. This is cross-modulation, a result of rectification in one of the early stages of the receiver. Receivers that are susceptible to this trouble usually also get a similar type of interference from regular broadcasting if there is a strong local b.c. station and the receiver is tuned to some *other* station.

The remedy for cross-modulation in the receiver is the same as for images and oscillator-harmonic response — reduce the strength of the amateur signal at the receiver by means of a line filter.

The trouble is not always in the receiver, since cross modulation can occur in any nearby rectifying circuit — such as a poor contact in water or steam piping, gutter pipes, and other conductors in the strong field of the transmitting antenna — external to both receiver and transmitter. Locating the cause may be difficult, and is best attempted with a battery-operated portable broadcast receiver used as a "probe" to find the spot where the interference is most intense. When such a spot is located, inspection of the metal structures in the vicinity should indicate the cause. The remedy is to make a good electrical bond between the two conductors having the poor contact.

Audio-Circuit Rectification

The most frequent cause of interference from operation at 21 Mc. and higher frequencies is rectification of a signal that by some means gets into the audio system of the receiver. In the milder cases an amplitude-modulated signal will be heard with reasonably good quality, but is not tunable—that is, it is present no matter what the frequency to which the receiver dial

554 BCI AND TVI

is set. An unmodulated carrier may have no observable effect in such cases beyond causing a little hum. However, if the signal is very strong there will be a reduction of the audio output level of the receiver whenever the carrier is thrown on. This causes an annoying "jumping" of the program when the interfering signal is keyed. With phone transmission the change in audio level is not so objectionable because it occurs at less frequent intervals. Rectification ordinarily gives no audio output from a frequency-modulated signal, so the interference can be made almost unnoticeable if f.m. or p.m. is used instead of a.m.

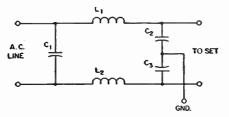


Fig. 23-1—"Brute-force" a.c. line filter for receivers. The values of C_{1} , C_{2} and C_{3} are not generally critical; capacitances from 0.001 to 0.01 μf . can be used. L_{1} and L_{2} can be a 2-inch winding of No. 18 enameled wire on a half-inch diameter form. In making up such a unit for use external to the receiver, make sure that there are no exposed conductors to offer a shack hazard.

Interference of this type usually results from a signal on the power line being coupled by some means into the audio circuits, although the pickup also may occur on the set wiring itself. A "brute-force" line filter as described above may or may not be completely effective, but in any event is the simplest thing to try. If it does not do the job, some modification of the receiver will be necessary. This usually takes the form of a simple filter connected in the grid circuit of the tube in which the rectification is occurring. Usually it will be the first audio amplifier, which in most receivers is a diode-triode type tube.

Filter circuits that have proved to be effective are shown in Fig. 23-2. In A, the value of the grid leak in the combined detector/first audio tube is reduced to 2 to 3 megohms and the grid is bypassed to chassis by a 250- $\mu\mu$ f. mica or ceramic capacitor. A somewhat similar method that does not require changing the grid resistor

is shown at B. In C, a 75,000-ohm (value not critical) resistor is connected between the grid pin on the tube socket and all other grid connections. In combination with the input capacitance of the tube this forms a low-pass filter to prevent r.f. from reaching the grid. In some cases, simply bypassing the heater of the detector/first audio tube to chassis with a 0.001-µf. or larger capacitor will suffice. In all cases, check to see that the a.c. line is bypassed to chassis; if it is not, install bypass capacitors (0.001 to 0.01 µf.).

Handling BCI Cases


Assuming that your transmitter has been checked and found to be free from spurious radiations, get another amateur to operate your station, if possible, while you make the actual check on the interference yourself. The following procedure should be used.


Tune the receiver through the broadcast band, to see whether the interference tunes like a regular b.c. station. If so, image or oscillator-harmonic response is the cause. If there is interference only when a b.c. station is tuned in, but not between stations, the cause is cross modulation. If the interference is heard at all settings of the tuning dial, the trouble is pickup in the audio circuits. In the latter case, the receiver's volume control may or may not affect the strength of the interference, depending on the means by which your signal is being rectified.

Having identified the cause, explain it to the set owner. It is a good idea to have a line filter with you, equipped with enough cord to replace the set's line cord, so it can be tried then and there. If it does not eliminate the interference. explain to the set owner that there is nothing further that can be done without modifying the receiver. Recommend that the work be done by a competent service technician, and offer to advise the service man on the cause and remedy. Don't offer to work on the set yourself, but it you are asked to do so use your own judgment about complying; set owners sometimes complain about the over-all performance of the receiver afterward, often without justification. If you work on it, take it to your station so the effect of the changes you make can be observed. and return the receiver promptly when you have finished.

MISCELLANEOUS TYPES OF INTERFERENCE

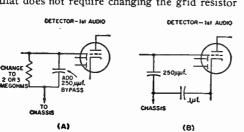The operation of amateur phone transmitters occasionally results in interference on telephone



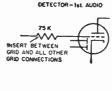

(C)

Fig. 23-2—Methods of eliminating r.f. from the grid of a combined detector/first-audio stage. At A, the value of the grid leak is reduced to 2 or 3 megohms, and a bypass capacitor is added. At B, bath grid and cathade are bypassed.

lines and in audio amplifiers used in public-address work and for home music reproduction. The cause is rectification of the signal in an audio circuit.

Telephone Interference

Telephone interference can be cured by connecting a bypass capacitor (about 0.001 μ f.) across the microphone unit in the telephone handset. The telephone companies have capacitors for this purpose. When such a case occurs, get in touch with the repair department of the phone company, giving all the particulars. Do not attempt to work on the telephone yourself.

Hi-Fi and P. A. Systems

In interference to public-address and "hi-fi" installations the principal sources of signal pick-

up are the a.c. line or a line from the power amplifier to a speaker. All amplifier units should be bonded together and connected to a good ground such as a cold-water pipe. Make sure that the a.c. line is bypassed to chassis in each unit with capacitors of about $0.01~\mu f$. at the point where the line enters the chassis. The speaker line similarly should be bypassed to the amplifier chassis with about $0.001~\mu f$.

If these measures do not suffice, the shielding on the amplifiers may be inadequate. A shield cover and bottom pan should be installed in such cases.

The spot in the system where the rectification is occurring often can be localized by seeing if the interference is affected by the volume control setting; if not, the cause is in a stage following the volume control.

TELEVISION INTERFERENCE (See also Chap. 17)

Interference with the reception of television signals usually presents a more difficult problem than interference with a.m. broadcasting. In BCI cases the interference almost always can be attributed to deficient selectivity or spurious responses in the b.c. receiver. While similar deficiencies exist in many television receivers, it is also true that amateur transmitters generate harmonics that fall inside many or all tele-

vision channels. These spurious radiations cause interference that ordinarily cannot be eliminated by anything that may be done at the receiver, so must be prevented at the transmitter itself.

The over-all situation is further complicated by the fact that television broadcasting is in three distinct bands, two in the v.h.f. region and one in the u.h.f.

V.H.F. TELEVISION

For the amateur who does most of his transmitting on frequencies below 30 Mc. the TV band of principal interest is the low v.h.f. band between 54 and 88 Mc. If harmonic radiation can be reduced to the point where no inter-

ference is caused to Channels 2 to 6, inclusive, it is almost certain that any harmonic troubles with channels above 174 Mc. will dis-

appear also.

The relationship between the v.h.f. television channels and harmonics of amateur bands from 14 through 28 Mc. is shown in Fig. 23-3. Harmonics of the 7- and 3.5-Mc, hands are not shown because they fall in every television channel. However, the harmonics above 54 Mc. from these bands are of such high order that they are usually rather low in amplitude, although they may be strong enough to interfere if the television receiver is quite close to the amateur transmitter. Loworder harmonics - up to about the sixth — are usually the most difficult to eliminate.

Of the amateur v.h.f. bands, only 50 Mc. will have harmonics falling in a v.h.f. television chan-

nel (channels 11, 12 and 13). However, a transmitter for any amateur v.h.f. band may cause interference if it has multiplier stages either operating in or having harmonics in one or more of the v.h.f. TV channels. The r.f. energy on such


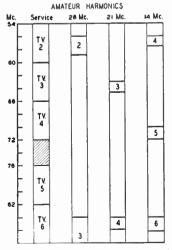


Fig. 23-3—Relationship of amateur-band harmonics to v.h.f. TV channels, Harmonic interference from transmitters operating below 30 Mc. is most likely to be serious in the low-channel group (54 to 88 Mc.).

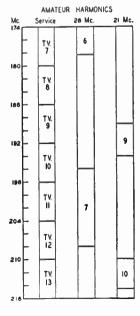

556 BCI AND TVI

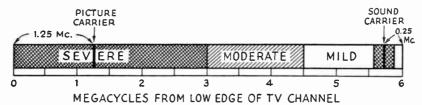


Fig. 23-4—Location of picture and sound carriers in a monochrame television channel, and relative intensity of interference as the location of the interfering signal within the channel is varied without changing its strength. The three regions are not actually sharply defined as shawn in this drawing, but merge into one another gradually.

frequencies can be radiated directly from the transmitting circuits or coupled by stray means to the transmitting antenna.

Frequency Effects

The degree to which transmitter harmonics or other undesired radiation actually in the TV channel must be suppressed depends principally on two factors, the strength of the TV signal on the channel or channels affected, and the relationship between the frequency of the spurious radiation and the frequencies of the TV picture and sound carriers within the channel. If the TV signal is very strong, interference can be eliminated by comparatively simple methods. However, if the TV signal is very weak, as in "fringe" areas where the received picture is visibly degraded by the appearance of set noise or "snow" on the screen, it may be necessary to go to extreme measures.

In either case the intensity of the interference depends very greatly on the exact frequency of the interfering signal. Fig. 23-4 shows the placement of the picture and sound carriers in the standard TV channel. In Channel 2, for example, the picture carrier frequency is 54 + 1.25 = 55.25 Mc. and the sound carrier frequency is 60 - 0.25 = 59.75 Mc. The second harmonic of 20.25 = 59.75 Mc. The second harmonic of 20.25 = 2.02 Mc. above the low edge of the channel and is in the region marked "Severe" in Fig. 23-4. On the other hand, the second harmonic of 29.500 kc. (59.000 kc. or 59 Mc.) is 59 - 54 = 5 Mc. from the low edge of the channel and falls in the region marked "Mild." Interference at



Fig. 23-5—"Cross-hatching," caused by the beat between the picture carrier and an interfering signal inside the TV channel,

this frequency has to be about 100 times as strong as at 56,020 kc. to cause effects of equal intensity. Thus an operating frequency that puts a harmonic near the picture carrier requires about 40 db. more harmonic suppression in order to avoid interference, as compared with an operating frequency that puts the harmonic near the upper edge of the channel.

For a region of 100 kc. or so either side of the sound carrier there is another "Severe" region where a spurious radiation will interfere with reception of the sound program, and this region also should be avoided. In general, a signal of intensity equal to that of the picture carrier will not cause noticeable interference if its frequency is in the "Mild" region shown in Fig. 23-4, but the same intensity in the "Severe" region will utterly destroy the picture.

Interference Patterns

The visible effects of interference vary with the type and intensity of the interference. Complete "blackout," where the picture and sound disappear completely, leaving the screen dark, occurs only when the transmitter and receiver are quite close together. Strong interference ordinarily causes the picture to be broken up, leaving a jumble of light and dark lines, or turns the picture "negative" - the normally white parts of the picture turn black and the normally black parts turn white. "Cross-hatching" - diagonal bars or lines in the picture accompanies the latter, usually, and also represents the most common type of less-severe interference. The bars are the result of the beat between the harmonic frequency and the picture carrier frequency. They are broad and relatively few in number if the beat frequency is comparatively low - near the picture carrier - and are numerous and very fine if the beat frequency is very high -- toward the upper end of the channel. Typical cross-hatching is shown in Fig. 23-5. If the frequency falls in the "Mild" region in Fig. 23-4 the cross-hatching may be so fine as to be visible only on close inspection of the picture, in which case it may simply cause the apparent brightness of the screen to change when the transmitter carrier is thrown on and

Whether or not cross-hatching is visible, an amplitude-modulated transmitter may cause "sound bars" in the picture. These look about

Reducing Harmonic Generation

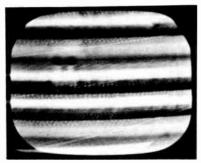


Fig. 23-6—"Saund bars" ar "madulatian bars" accampanying amplitude madulatian af an interfering signal. In this case the interfering carrier is strang enough ta destray the picture, but in mild cases the picture is visible thraugh the harizantal bars. Saund bars may accampany madulatian even thaugh the unmadulated carrier gives no visible crass-hatching.

as shown in Fig. 23-6. They result from the variations in the intensity of the interfering signal when modulated. Under most circumstances modulation bars will not occur if the amateur transmitter is frequency- or phase-modulated. With these types of modulation the cross-hatching will "wiggle" from side to side with the modulation.

Except in the more severe cases, there is seldom any effect on the sound reception when interference shows in the picture, unless the frequency is quite close to the sound carrier. In the latter event the sound may be interfered with even though the picture is clean.

Reference to Fig. 23-3 will show whether or not harmonics of the frequency in use will fall in any television channels that can be received in the locality. It should be kept in mind that not only harmonics of the final frequency may interfere, but also harmonics of any frequencies that may be present in buffer or frequency-multiplier stages. In the case of 144-Mc. transmitters, frequency-multiplying combinations that require a doubler or tripler stage to operate on a frequency actually in a low-band v.h.f. channel in use in the locality should be avoided.

Harmonic Suppression

Effective harmonic suppression has three separate phases:

- 1) Reducing the amplitude of harmonics generated in the transmitter. This is a matter of circuit design and operating conditions.
- 2) Preventing stray radiation from the transmitter and from associated wiring. This requires adequate shielding and filtering of all circuits and leads from which radiation can take place.
- 3) Preventing harmonics from being fed into the antenna.

It is impossible to build a transmitter that will not generate *some* harmonics, but it is obviously advantageous to reduce their strength, by circuit design and choice of operating conditions, by as large a factor as possible before attempt-

ing to prevent them from being radiated. Harmonic radiation from the transmitter itself or from its associated wiring obviously will cause interference just as readily as radiation from the antenna, so measures taken to prevent harmonics from reaching the antenna will not reduce TVI if the transmitter itself is radiating harmonics. But once it has been found that the transmitter itself is free from harmonic radiation, devices for preventing harmonics from reaching the antenna can be expected to produce results.

REDUCING HARMONIC GENERATION

Since reasonably efficient operation of r.f. power amplifiers always is accompanied by harmonic generation, good judgment calls for operating all frequency-multiplier stages at a very low power level — plate voltages not exceeding 250 or 300. When the final output frequency is reached, it is desirable to use as few stages as possible in building up to the final output power level, and to use tubes that require a minimum of driving power.

Circuit Design and Layout

Harmonic currents of considerable amplitude flow in both the grid and plate circuits of r.f. power amplifiers, but they will do relatively little harm if they can be effectively bypassed to the cathode of the tube. Fig. 23-7 shows the paths followed by harmonic currents in an amplifier circuit; because of the high reactance of the tank coil there is little harmonic current in it, so the harmonic currents simply flow through the tank capacitor, the plate (or grid) blocking capacitor, and the tube capacitances. The lengths of the leads forming these paths is of great importance, since the inductance in this circuit will resonate with the tube capacitance at some frequency in the v.h.f. range (the tank and blocking capacitances usually are so large compared with the tube capacitance that they have little effect on the resonant frequency). If such a resonance happens to occur at or near the same frequency as one of the transmitter harmonics, the effect is just the same as though a harmonic tank circuit had been deliberately introduced; the harmonic at that frequency will be tremendously increased in amplitude.

Such resonances are unavoidable, but by keeping the path from plate to cathode and from

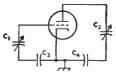


Fig. 23-7—A v.h.f. resanant circuit is farmed by the tube capacitance and the leads through the tank and blacking capacitars. Regular tank cails are not shawn, since they have little effect an such resanances. C₁ is the grid tuning capacitar and C₂ is the plate tuning capacitar. C₃ and C₄ are the grid and plate blacking ar bypass capacitars, respectively.

558 BCI AND TVI

grid to cathode as short as is physically possible, the resonant frequency usually can be raised above 100 Mc. in amplifiers of medium power. This puts it between the two groups of television channels.

It is easier to place grid-circuit v.h.f. resonances where they will do no harm when the amplifier is link-coupled to the driver stage, since this generally permits shorter leads and more favorable conditions for bypassing the harmonics than is the case with capacitive coupling. Link coupling also reduces the coupling between the driver and amplifier at harmonic frequencies, thus preventing driver harmonics from being amplified.

The inductance of leads from the tube to the tank capacitor can be reduced not only by shortening but by using flat strip instead of wire conductors. It is also better to use the chassis as the return from the blocking capacitor or tuned circuit to cathode, since a chassis path will have less inductance than almost any other form of connection.

The v.h.f. resonance points in amplifier tank circuits can be found by coupling a grid-dip meter covering the 50-250 Mc. range to the grid and plate leads. If a'resonance is found in or near a TV channel, methods such as those described above should be used to move it well out of the TV range. The grid-dip meter also should be used to check for v.h.f. resonances in the tank coils, because coils made for 14 Mc. and below usually will show such resonances. In making the check, disconnect the coil entirely from the transmitter and move the grid-dip meter coil along it while exploring for a dip in the 54-88 Mc. band. If a resonance falls in a TV channel that is in use in the locality, changing the number of turns will move it to a lesstroublesome frequency.

Operating Conditions

Grid bias and grid current have an important effect on the harmonic content of the r.f. currents in both the grid and plate circuits. In general, harmonic output increases as the grid bias and grid current are increased, but this is not necessarily true of a particular harmonic. The third and higher harmonics, especially, will go through fluctuations in amplitude as the grid current is increased, and sometimes a rather high value of grid current will minimize one harmonic as compared with a low value. This characteristic can be used to advantage where a particular harmonic is causing interference, remembering that the operating conditions that minimize one harmonic may greatly increase another.

For equal operating conditions, there is little or no difference between single-ended and pushpull amplifiers in respect to harmonic generation. Push-pull amplifiers are frequently trouble-makers on even harmonics because with such amplifiers the even-harmonic voltages are in phase at the ends of the tank circuit and hence appear with equal amplitude across the whole

tank coil, if the center of the coil is not grounded. Under such circumstances the even harmonics can be coupled to the output circuit through stray capacitance between the tank and coupling coils. This does not occur in a single-ended amplifier having an inductively coupled tank, if the coupling coil is placed at the cold end, or with a pi-network tank.

Harmonic Traps

If a harmonic in only one TV channel is particularly bothersome—frequently the case when the transmitter operates on 28 Mc.—a trap tuned to the harmonic frequency may be installed in the plate lead as shown in Fig. 23-8. At the harmonic frequency the trap represents a very high impedance and hence reduces the amplitude of the harmonic current flowing through the tank circuit. In the push-pull circuit both traps have the same constants. The L/C ratio is not critical but a high-C circuit usually will have least effect on the performance of the plate circuit at the normal operating frequency.

Since there is a considerable harmonic voltage across the trap, radiation may occur from the trap unless the transmitter is well shielded. Traps should be placed so that there is no coupling between them and the amplifier tank circuit.

A trap is a highly selective device and so is useful only over a small range of frequencies.

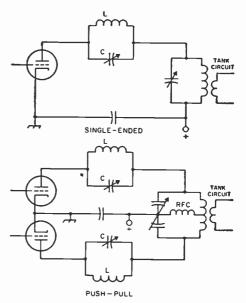


Fig. 23-8—Harmonic traps in an amplifier plate circuit. L and C should resonate at the frequency of the harmonic to be suppressed. C may be a 25- to 50-μμf, midget, and L usually consists of 3 to 6 turns about ½2 inch in diameter for Channels 2 through 6. The inductance should be adjusted so that the trap resonates at about half capacitance of C before being installed in the transmitter. The frequency may be checked with a grid-dip meter. When in place, the trap should be adjusted for minimum interference to the TV picture.

Preventing Radiation

A second- or third-harmonic trap on a 28-Mc. tank circuit usually will not be effective over more than 50 kc. or so at the fundamental frequency, depending on how serious the interference is without the trap. Because they are critical of adjustment, is is better to prevent TVI by other means, if possible, and use traps only as a last resort.

PREVENTING RADIATION FROM THE TRANSMITTER

The extent to which interference will be caused by direct radiation of spurious signals depends on the operating frequency, the transmitter power level, the strength of the television signal, and the distance between the transmitter and TV receiver. Transmitter radiation can be a very serious problem if the TV signal is weak, if the TV receiver and amateur transmitter are close together, and if the transmitter is operated with high power.

Shielding

Direct radiation from the transmitter circuits and components can be prevented by proper shielding. To be effective, a shield must completely enclose the circuits and parts and must have no openings that will permit r.f. energy to escape. Unfortunately, ordinary metal boxes and cabinets do not provide good shielding, since such openings as louvers, lids, and holes for running in connections allow far too much leakage.

A primary requisite for good shielding is that all joints must make a good electrical connection along their entire length. A small slit or crack will let out a surprising amount of r.f. energy; so will ventilating louvers and large holes such as those used for mounting meters. On the other hand, small holes do not impair the shielding very greatly, and a limited number of ventilating holes may be used if they are small - not over 1/4 inch in diameter. Also, wire screen makes quite effective shielding if the wires make good electrical connection at each crossover. Perforated aluminum such as the "do-it-yourself" sold at hardware stores also is good, although not very strong mechanically. If perforated material is used, choose the variety with the smallest openings. The leakage through large openings can be very much reduced by covering such openings with screening or perforated aluminum, well bonded to all edges of the opening.

The intensity of r.f. fields about coils, capacitors, tubes and wiring decreases very rapidly with distance, so shielding is more effective, from a practical standpoint, if the components and wiring are not too close to it. It is advisable to have a separation of several inches, if possible, between "hot" points in the circuit and the nearest shielding.

For a given thickness of metal, the greater the conductivity the better the shielding. Copper is best, with aluminum, brass and steel following in that order. However, if the thickness is adequate for structural purposes (over 0.02 inch) and the shield and a "hot" point in the circuit are not in close proximity, any of these metals will be satisfactory. Greater separation should be used with steel shielding than with the other materials not only because it is considerably poorer as a shield but also because it will cause greater losses in near-by circuits than would copper or aluminum at the same distance. Wire screen or perforated metal used as a shield should also be kept at some distance from high-voltage or high-current r.f. points, since there is considerably more leakage through the mesh than through solid metal.

Where two pieces of metal join, as in forming a corner, they should overlap at least a half inch and be fastened together firmly with screws or bolts spaced at close-enough intervals to maintain firm contact all along the joint. The contact surfaces should be clean before joining, and should be checked occasionally—especially steel, which is almost certain to rust after a period of time.

The leakage through a given size of aperture in shielding increases with frequency, so such points as good continuous contact, screening of large holes, and so on, become even more important when the radiation to be suppressed is in the high band — 174-216 Mc. Hence 50- and 144-Mc. transmitters, which in general will have frequency-multiplier harmonics of relatively high intensity in this region, require special attention in this respect if the possibility of interfering with a channel received locally exists.

Lead Treatment

Even very good shielding can be made completely useless when connections are run to external power supplies and other equipment from the circuits inside the shield. Every such conductor leaving the shielding forms a path for the escape of r.f., which is then radiated by the connecting wires. Hence a step that is essential

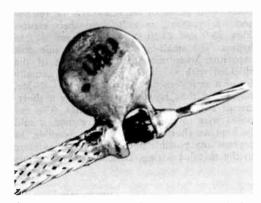


Fig. 23-9—Proper method of bypassing the end of a shielded lead using disk ceramic capacitor. The 0.001μf, size should be used for 1600 volts or less; 500 μμf, at higher voltages. The leads are wrapped around the inner and outer conductors and soldered, so that the lead length is negligible. This photograph is about four times actual size.

560 BCI AND TVI



Fig. 23-10—Bypassing with a mica capacitor the end of a high-voltage lead. The end of the shield braid is soldered to a lug fastened to the chassis directly underneath. The other terminal of the capacitor is similarly bolted directly to the chassis. When the bypass is used at a terminal connection block the "hot" lead should be soldered directly to the terminal, if possible, but in any event connected to it by a very short lead.

in every case is to prevent harmonic currents from flowing on the leads leaving the shielded enclosure.

Harmonic currents always flow on the d.c. or a.c. leads connecting to the tube circuits. A very effective means of preventing such currents from being coupled into other wiring, and one that provides desirable bypassing as well, is to use shielded wire for all such leads, maintaining the shielding from the point where the lead connects to the tube or r.f. circuit right through to the point where it leaves the chassis. The shield braid should be grounded to the chassis at both ends and at frequent intervals along the path.

Good bypassing of shielded leads also is essential. Bearing in mind that the shield braid about the conductor confines the harmonic currents to the inside of the shielded wire, the object of bypassing is to prevent their escape. Figs. 23-9 and 23-10 show the proper way to bypass. The small-type 0.001-µf. ceramic disk capacitor, when mounted on the end of the shielded wire as shown in Fig. 23-9, actually forms a series-resonant circuit in the 54-88-Mc. range and thus represents practically a shortcircuit for low-band TV harmonics. The exposed wire to the connection terminal should be kept as short as is physically possible, to prevent any possible harmonic pickup exterior to the shielded wiring. Disk capacitors of this

capacitance are available in several voltage ratings up to 3000 volts. For higher voltages, the maximum capacitance available is approximately 500 $\mu\mu$ f., which is large enough for good bypassing of harmonics. Alternatively, mica capacitors may be used as shown in Fig. 23-10, mounting the capacitor flat against the chassis and grounding the end of the shield braid directly to chassis, keeping the exposed part as short as possible. Either 0.001- μ f. or 470- $\mu\mu$ f. (500 $\mu\mu$ f.) capacitors should be used. The larger capacitance is series-resonant in Channel 2 and the smaller in Channel 6.

These bypasses are essential at the connection-block terminals, and desirable at the tube ends of the leads also. Installed as shown with shielded wiring, they have been found to be so effective that there is usually no need for further harmonic filtering. However, if a test shows that additional filtering is required, the arrangement shown in Fig. 23-11 may be used. Such an r.f. filter should be installed at the tube end of the shielded lead, and if more than one circuit is filtered care should be taken to keep the r.f. chokes separated from each other and so oriented as to minimize coupling between them. This is necessary for preventing harmonics present in one circuit from being coupled into another

In difficult cases involving Channels 7 to 13i.e., close proximity between the transmitter and receiver, and a weak TV signal - additional lead-filtering measures may be needed to prevent radiation of interfering signals by 50- and 144-Mc. transmitters. A recommended method is shown in Fig. 23-12. It uses a shielded lead bypassed with a ceramic disk as described above, with the addition of a low-inductance feedthrough type capacitor and a small r.f. choke, the capacitor being used as a terminal for the external connection. For voltages above 400, a capacitor of compact construction (as indicated in the caption) should be used, mounted so that there is a very minimum of exposed lead, inside the chassis, from the capacitor to the connection terminal.

As an alternative to the series-resonant bypassing described above, feed-through type capacitors such as the Sprague "Hypass" type may be used as terminals for external connections. The ideal method of installation is to mount them so they protrude through the chassis, with thorough bonding to the chassis all around the hole in which the capacitor is mounted. The principle is illustrated in Fig. 23-13.

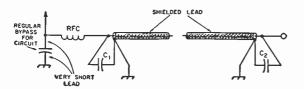


Fig. 23-11—Additional r.f. filtering of supply leads may be required in regions where the TV signal is very weak. The r.f. choke should be physically small, and may consist of a 1-inch winding of No. 26 enameled wire on a ¼-inch form, close-wound. Manufactured single-layer chokes having an inductance of a few microhenrys also may be used.

Preventing Radiation

Meters that are mounted in an r.f. unit should be enclosed in shielding covers, the connections being made with shielded wire with each lead bypassed as described above. The shield braid should be grounded to the panel or chassis immediately outside the meter shield, as indicated in Fig. 23-14. A bypass may also be connected across the meter terminals, principally to prevent any fundamental current that may be present from flowing through the meter itself. As an alternative to individual meter shielding the meters may be mounted entirely behind the panel, and the panel holes needed for observation may be covered with wire screen that is carefully bonded to the panel all around the hole.

Care should be used in the selection of shielded wire for transmitter use. Not only should the insulation be conservatively rated for the d.c.

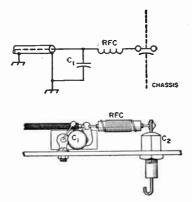


Fig. 23-12—Additional lead filtering for harmonics or ather spurious frequencies in the high v.h.f. TV band (174-216 Mc.)

C1-0.001-µf. disk ceramic.

C₂-0.001-µf. feed-thraugh bypass (Erie Style 326). (Far 500-2000-valt lead, substitute Plastican Glass mike, LSG-251, far C₂.)

RFC—14 inches Na. 26 enamel clase-waund an ¾6-inch diam. farm ar resistar.

voltage in use, but the insulation should be of material that will not easily deteriorate in soldering. The r.f. characteristics of the wire are not especially important, except that the attenuation of harmonics in the wire itself will be greater if the insulating material has high losses at radio frequencies; in other words, wire intended for use at d.c. and low frequencies is preferable to cables designed expressly for carrying r.f. The attenuation also will increase with the length of the wire; in general, it is better to make the leads as long as circumstances permit rather than to follow the more usual practice of using no more lead than is actually necessary. Where wires cross or run parallel, the shields should be spot-soldered together and connected to the chassis. For high voltages, automobile ignition cable covered with shielding braid is recommended.

Proper shielding of the transmitter requires that the r.f. circuits be shielded entirely from

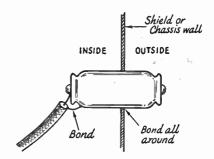


Fig. 23-13—The best method of using the "Hypass" type feed-through capacitar. Capacitances of 0.01 to 0.1 \(\mu \). Capacitars of this type are useful for high-current circuits, such as filament and 115-valt leads, as a substitute for the r.f. chake shown in Fig. 23-11, in cases where additional lead filtering is needed.

the external connecting leads. A situation such as is shown in Fig. 23-15, where the leads in the r.f. chassis have been shielded and properly filtered but the chassis is mounted in a large shield, simply invites the harmonic currents to travel over the chassis and on out over the leads outside the chassis. The shielding about the r.f. circuits should make complete contact with the chassis on which the parts are mounted.

Checking Transmitter Radiation

A check for transmitter radiation always should be made before attempting to use low-pass filters or other devices for preventing harmonics from reaching the antenna system. The only really satisfactory indicating instrument is a television receiver. In regions where the TV signal is strong an indicating wavemeter such as one having a crystal or tube detector may be useful; if it is possible to get any indication at all from harmonics either on supply leads or

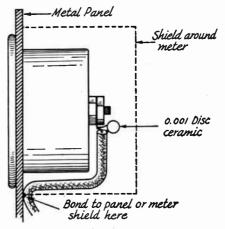


Fig. 23-14—Meter shielding and bypassing. It is essential to shield the meter mounting hale since the meter will carry r.f. through it to be radiated. Suitable shields can be made from 2½- or 3-inch diameter metal cans ar small metal chassis baxes.

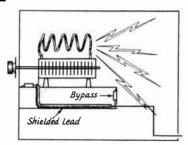


Fig. 23-15—A metal cabinet can be an adequate shield, but there will still be radiation if the leads inside can pick up r.f. from the transmitting circuits.

around the transmitter itself, the harmonics are probably strong enough to cause interference. However, the absence of any such indication does not mean that harmonic interference will not be caused. If the techniques of shielding and lead filtering described in the preceding section are followed, the harmonic intensity on any external leads should be far below what any such instruments can detect.

Radiation checks should be made with the transmitter delivering full power into a dummy antenna, such as an incandescent lamp of suitable power rating, preferably installed inside the shielded enclosure. If the dummy must be external, it is desirable to connect it through a coaxmatching circuit such as is shown in Fig. 23-16. Shielding the dummy antenna circuit is also desirable, although it is not always necessary.

Make the radiation test on all frequencies that are to be used in transmitting, and note whether or not interference patterns show in the received picture. (These tests must be made while a TV signal is being received, since the beat patterns will not be formed if the TV picture carrier is not present.) If interference exists, its source can be detected by grasping the various external leads (by the insulation, not the live wire!) or bringing the hand near meter faces, louvers, and other possible points where harmonic energy might escape from the transmitter. If any of these tests cause a change—

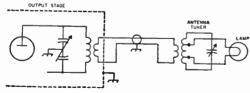


Fig. 23-16—Dummy-antenna circuit for checking harmonic radiation from the transmitter and leads. The matching circuit helps prevent harmonics in the output of the transmitter from flowing back over the transmitter itself, which may occur if the lamp load is simply connected to the output coil of the final amplifier. See transmission-line chapter for details of the matching circuit. Tuning must be adjusted by cut-and-try, as the bridge method described in the transmission-line chapter will not work with lamp loads because of the change in resistance when the lamps are hot.

not necessarily an *increase* — in the intensity of the interference, the presence of harmonics at that point is indicated. The location of such "hot" spots usually will point the way to the remedy. If the TV receiver and the transmitter can be operated side-by-side, a length of wire connected to one antenna terminal on the receiver can be used as a probe to go over the transmitter enclosure and external leads. This device will very quickly expose the spots from which serious leakage is taking place.

As a final test, connect the transmitting antenna or its transmission line terminals to the outside of the transmitter shielding. Interference created when this test is applied indicates that weak currents are on the outside of the shield and can be conducted to the antenna when the normal antenna connections are used. Currents of this nature represent interference that is conducted *over* low-pass filters, and hence cannot be eliminated by such filters.

PREVENTING HARMONICS FROM REACHING THE ANTENNA

The third and last step in reducing harmonic TVI is to keep the spurious energy generated in or passed through the final stage from traveling over the transmission line to the antenna. It is seldom worthwhile even to attempt this until the radiation from the transmitter and its connecting leads has been reduced to the point where, with the transmitter delivering full power into a dummy antenna, it has been determined by actual testing with a television receiver that the radiation is below the level that can cause interference. If the dummy antenna test shows enough radiation to be seen in a TV picture, it is a practical certainty that harmonics will be coupled to the antenna system no matter what preventive measures are taken.

In inductively coupled output systems, some harmonic energy will be transferred from the final amplifier through the mutual inductance between the tank coil and the output coupling coil. Harmonics of the output frequency transferred in this way can be greatly reduced by providing sufficient selectivity between the final tank and the transmission line. A good deal of selectivity, amounting to 20 to 30 db. reduction of the second harmonic and much higher reduction of higher-order harmonics, is furnished by a matching circuit of the type shown in Fig. 23-16 and described in the chapter on transmission lines. An "antenna coupler" is therefore a worthwhile addition to the transmitter.

In 50- and 144-Mc. transmitters, particularly, harmonics not directly associated with the output frequency—such as those generated in low-frequency early stages of the transmitter—may get coupled to the antenna by stray means. For example, a 144-Mc. transmitter might have an oscillator or frequency multiplier at 48 Mc., followed by a tripler to 144 Mc. Some of the 48-Mc. energy will appear in the plate circuit of the tripler, and if passed on to the grid of the final amplifier will appear as a 48-Mc. modula-

Keeping Harmonics From the Antenna

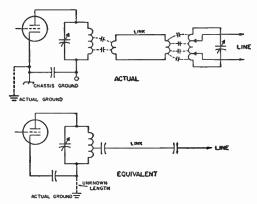


Fig. 23-17—The stray capacitive coupling between coils in the upper circuit leads to the equivalent circuit shown below, for v.h.f. harmonics.

tion on the 144-Mc. signal. This will cause a spurious signal at 192 Mc., which is in the high TV band, and the selectivity of the tank circuits may not be sufficient to prevent its being coupled to the antenna. Spurious signals of this type can be reduced by using link coupling between the driver stage and final amplifier (and between earlier stages as well) in addition to the suppression afforded by using an antenna coupler.

Capacitive Coupling

The upper drawing in Fig. 23-17 shows a parallel-conductor link as it might be used to couple into a parallel-conductor line through a matching circuit. Inasmuch as a coil is a sizable metallic object, there is capacitance between the final tank coil and its associated link coil, and between the matching-circuit coil and its link. Energy coupled through these capacitances travels over the link circuit and the transmission line as though these were merely single conductors. The tuned circuits simply act as masses of metal and offer no selectivity at all for capacitively-coupled energy. Although the actual capacitances are small, they offer a good coupling medium for frequencies in the v.h.f. range.

Capacitive coupling can be reduced by coupling to a "cold" point on the tank coil — the end connected to ground or cathode in a single-ended stage. In push-pull circuits having a split-stator capacitor with the rotor grounded for r.f., all parts of the tank coil are "hot" at even har-

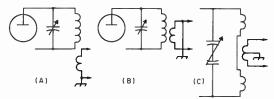


Fig. 23-18—Methods of coupling and grounding link circuits to reduce capacitive coupling between the tank and link coils. Where the link is wound over one end of the tank coil the side toward the hot end of the tank should be grounded, as shown at B.

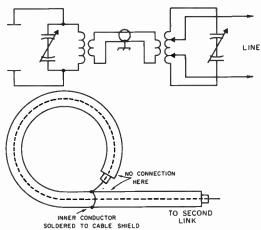


Fig. 23-19—Shielded coupling coil constructed from coaxial cable. The smaller sizes of cable such as RG-59/U are most convenient when the coil diameter is 3 inches or less, because of greater flexibility. For larger coils RG-8/U or RG-11/U can be used.

monics, but the center of the coil is "cold" at the fundamental and odd harmonics. If the center of the tank coil, rather than the rotor of the tank capacitor, is grounded through a bypass capacitor the center of the coil is "cold" at all frequencies, but this arrangement is not very desirable because it causes the harmonic currents to flow through the coil rather than the tank capacitor and this increases the harmonic transfer by pure inductive coupling.

With either single-ended or balanced tank circuits the coupling coil should be grounded to the chassis by a short, direct connection as shown in Fig. 23-18. If the coil feeds a balanced line or link, it is preferable to ground its center, but if it feeds a coax line or link one side may be grounded. Coaxial output is much preferable to balanced output, because the harmonics have to stay inside a properly installed coax system and tend to be attenuated by the cable before reaching the antenna coupler.

At high frequencies — and possibly as low as 14 Mc. — capacitive coupling can be greatly reduced by using a shielded coupling coil as shown in Fig. 23-19. The inner conductor of a length of coaxial cable is used to form a oneturn coupling coil. The outer conductor serves as an open-circuited shield around the turn, the shield being grounded to the chassis. The shielding has no effect on the inductive coupling. Because this construction is suitable only for one turn, the coil is not well adapted for use on the lower frequencies where many turns are required for good coupling. Shielded coupling coils having a larger number of turns are available commercially. A shielded coil is particularly useful with push-pull amplifiers when the suppression of even harmonics is important.

A shielded coupling coil or coaxial output will not prevent stray capacitive coupling to the an564 BCI AND TVI

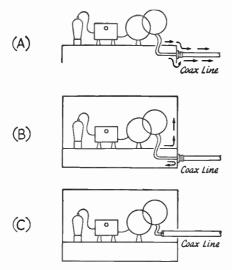


Fig. 23-20—Right (B) and wrong (A and C) ways to connect o coaxial line to the transmitter. In A or C, harmonic energy coupled by stray copacitance to the outside of the cable will flow without hindronce to the antenna system. In B the energy cannot leave the shield and can flow out only through, not over, the cable.

tenna if harmonic currents can flow over the outside of the coax line. In Fig. 23-20, the arrangement at either A or C will allow r.f. to flow over the outside of the cable to the antenna system. The proper way to use coaxial cable is to shield the transmitter completely, as shown at B, and make sure that the outer conductor of the cable is a continuation of the transmitter shielding. This prevents r.f. inside the transmitter from getting out by any path except the inside of the cable. Harmonics flowing through a coax line can be stopped by an antenna coupler or low-pass filter installed in the line.

Low-Pass Filters

A low-pass filter properly installed in a coaxial line, feeding either a matching circuit (antenna coupler) or feeding the antenna directly, will provide very great attenuation of harmonics. When the main transmission line is of the parallel-conductor type, the coax-coupled matching-circuit arrangement is highly recommended as a means for using a coax low-pass filter.

A low-pass filter will transmit power at the fundamental frequency without appreciable loss if the line in which it is inserted is properly terminated (has a low s.w.r.). At the same time it has large attenuation for all frequencies above the "cut-off" frequency.

Low-pass filters of simple and inexpensive construction for use with transmitters operating below 30 Mc. are shown in Figs. 23-21 and 23-23. The former is designed to use mica capacitors of readily available capacitance values, for compactness and low cost. Both use the same circuit, Fig. 23-22, the only difference being in the

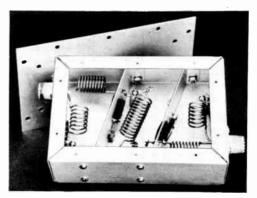


Fig. 23-21—An inexpensive low-pass filter using silvermica postage-stamp capacitors. The box is a 2 by 4 by
6 aluminum chassis. Aluminum shields, bent and folded
at the sides and bottom for fastening to the chassis,
form shields between the filter sections. The diagonal
arrangement of the shields provides extra room for
the coils and makes it easier to fit the shields in the
box, since bending to exact dimensions is not essential.
The bottom plate, made from sheet aluminum, extends
a half inch beyond the ends of the chassis and is provided with mounting holes in the extensions. It is held
on the chassis with sheet-metal screws.

L and C values. Technically, they are three-section filters having two full constant-k sections and two m-derived terminating half-sections, and their attenuation in the 54-88-Mc. range varies from over 50 to nearly 70 db., depending on the frequency and the particular set of values used. At high frequencies the ultimate attenuation will depend somewhat on internal resonant conditions associated with component lead lengths. These leads should be kept as short as possible.

The power that filters using mica capacitors can handle safely is determined by the voltage and current limitations of the capacitors. The power capacity is least at the highest frequency. The unit using postage-stamp silver mica capacitors is capable of handling approximately 50 watts in the 28-Mc. band, when working into a properly-matched line, but is good for about 150 watts at 21 Mc. and 300 watts at 14 Mc. and lower frequencies. A filter with larger mica capacitors (case type CM-45) will carry about 250 watts safely at 21 Mc., this rating increasing to 500 watts at 21 Mc. and a kilowatt at 14 Mc. and lower. If there is an appreciable mismatch between the filter and the line into which it works, these ratings will be considerably decreased, so in order to avoid capacitor failure it is highly essential that the line on the output side of the filter be carefully matched.

The power capacity of these filters can be increased considerably by substituting r.f. type fixed capacitors (such as the Centralab 850 series) or variable air capacitors, in which event the power capability will be such as to handle the maximum amateur power on any band. The construction can be modified to accommodate vari-

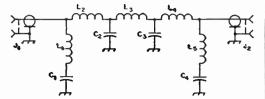


Fig. 23-22—Low-pass filter circuit, J_1 and J_2 are chassistype coaxial connectors. In the table below the letters refer to the following:

- A-Using 100- and 70-µµf. 500-volt silver mica capacitors in parallel for C₂ and C₃.
- B—Using 70- and 50- $\mu\mu$ f, silver mica capacitors in parallel for C₂ and C₃.
- C—Using 100- and 50- $\mu\mu$ f. mica capacitors, 1200-volt (case-style CM-45) in parallel for C₂ and C₃.
- D and E-Using variable air capacitors, 500- to 1000volt rating, adjusted to values given.

	A	В	С	D	E	_
Z _o	52	75	52	52	75	ohms
f_0	36	35.5	41	40	40	Mc.
f ₀₀	44.4	47	54	50	50	Mc.
f_1	25.5	25.2	29	28.3	28.3	Mc.
	32.5	31.8	37.5	36.1	36.1	Mc.
C_1, C_4	50	40	50	46	32	μμf.
C_2, C_3	170	120	150	154	106	$\mu\mu$ f.
L_1, L_5	5 1/2	6	4	5	61/2	turns*
L_2, L_4	8	11	7	7	91/2	turns*
L_{a}	9	13	8	8 1/2	111/2	turns*

*No. 12 or No. 14 wire, ½-inch inside diameter, 8 turns per inch.

able air capacitors as shown in Fig. 23-23.

Using fixed capacitors of standard tolerances, there should be little difficulty in getting proper filter operation. A grid-dip meter with an accurate calibration should be used for adjustment of the coils. First, wire up the filter without L_2 and L_4 . Short-circuit J_1 at its inside end with a screwdriver or similar conductor, couple the grid-dip meter to L_1 and adjust the inductance of L_1 , by varying the turn spacing, until the circuit resonates at f_{∞} as given in the table. Do the same thing at the other end of the filter with L_5 . Then couple the meter to the circuit formed by L_5 , C_2 and C_5 .

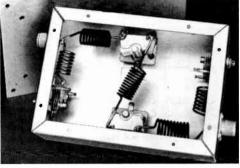


Fig. 23-23—Low-pass filter using variable air capacitors. The box is a 2 by 5 by 7 aluminum chassis, fitted with a bottom plate of similar construction to the one used in Fig. 23-21.

and adjust L_3 to resonate at the frequency f_1 as given by the table. Then remove L_3 , install L_2 and L_4 and adjust L_2 to make the circuit formed by L_1 , L_2 , C_1 and C_2 (without the short across J_1) resonate at f_2 as given in the table. Do the same with L_4 for the circuit formed by L_4 , L_5 , C_3 and C_4 . Then replace L_3 and check with the grid-dip meter at any coil in the filter; a distinct resonance should be found at or very close to the cut-off frequency, f_c .

The filter constants suggested at D and E in Fig. 23-22 are based on the optimum design for good impedance characteristics—that is, with m=0.6 in the end sections—and a cut-off frequency below the standard i.f. for television receivers (sound carrier at 41.25 Mc.; picture carrier at 45.75 Mc.). This is to avoid possible harmonic interference from 21 Mc. and below to the receiver's intermediate amplifier. The other designs similarly cut off at 41 Mc. or below, but m in these cases is necessarily based on the capacitances available in standard fixed capacitors.

Filters for 50- and 144-Mc. Transmitters

Since a low-pass filter must have a cut-off frequency above the frequency on which the transmitter operates, a filter for a v.h.f. transmitter cannot be designed for attenuation in all television channels. This is no handicap for v.h.f. work but means that the filter will not be effective when used with lower-frequency transmit-

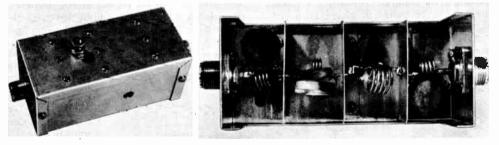


Fig. 23-24—Low-pass filter for use with 50-Mc. transmitters at powers up to about 300 watts. The housing is a 21/4-inches square by 5-inches long Minibox. Connections between the various sections of the filter are made through 5/16-inch clearance holes cut in the centers of the shielding partitions.

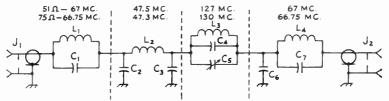


Fig. 23-25—Circuit of the 6-meter low-pass filter. See table for capacitance and inductance values.

C₁, C₂, C₃, C₄, C₆, C₇—6000-volt disk ceramic (Centralab DD60, Sprague 60GA, Erie HD6 or similar). C₅—45-μμf. ceramic trimmer (Centralab 822BN). J₁, J₂—Chassis-mounting coax receptacle (SO-239). Resonant frequencies refer to the following independent combinations: L₁C₁, L₂C₂C₃, L₃C₃C₆ and L₄C₇.

Capacitance (μμf.) and Inductance (μh.) Values for the 6-Meter Low-Pass Filter						
C1, C3, C2 C4 C5 C6 L1, L4 L2 L3	C ₇	50 ohms 68 82 100 7-45 39 0.0825 0.3 0.0622	75 ohms 47 56 68 7-45 25 0.121 0.441 0.0915			
Coi	Coil Dimensions (All No. 16 Wire)					
L(μh.)	Turns	I.D. Tur	ns Spacing			
0.441 0.3 0.121 0.0915 0.0825 0.622		½ inch ½ inch ½ inch ½ inch ½ inch 1	inch turn inch			

ters, unless it happens that no local TV channels fall inside the pass band of the filter.

Fig. 23-24 shows a filter for 50- or 75-ohm coax suitable for a 50-Mc. transmitter of any power up to about 300 watts. The circuit diagram is given in Fig. 23-25. If the values of inductance and capacitance can be measured, the components can be preset and assembled without further adjustment. Alternatively, the grid-dip meter method described earlier may be used. The resonant frequencies are checked for the following combinations (see Fig. 23-25): L_1C_1 , $L_2C_2C_8$ (L_8 and associated capacitors lifted), L₃C₃C₆ (L₂ lifted at C_8 and L_4C_7 lifted at C_6), and L_4C_7 . Coil turns are spread apart or squeezed together in adjusting to the resonant frequencies. When sections have been resonated, the filter is reconnected and, with a suitable termination, Co is adjusted for minimum response at 55.25 Mc.

In constructing the filter, the coils are supported by the coax connectors and by the short capacitor leads, one of which is soldered to a ground lug. The only stand-off insulators are the two supporting L_{3} , C_{4} and C_{5} . Leads should be centered in the middle of the holes through the shields, and excess solder resin cleaned from capacitor bodies and stand-off insulators.

The filter will have about 0.3 db. attentuation up to 51 Mc. and about 3 to 4 db. at 53 Mc. At 55.25 and above the attenuation should never be less than 25 or 30 db.

A filter for low-power 144-Mc. transmitters is shown in Fig. 23-26. It is designed for maximum attenuation in the 190-215 Mc. region to suppress the spurious radiations in that range that frequently occur with 144-Mc. transmitters, but also has good attenuation for all frequencies above 170 Mc. Optimum capacitance values are given in Fig. 23-27. If possible, several units of the nearest standard values available should be measured and those having values closest to the optimum used. Adjust the filter as follows:

First, mount L_1 and C_1 , short J_1 temporarily at its inner terminals, and adjust L_1 until the combination resonates at 200 Mc. as shown by a griddip meter. Next, remove the short from J_1 and connect L_2 and C_2 , adjusting L_2 until the circuit formed by $L_1L_2C_1C_2$ resonates at 144 Mc. Then disconnect L_2 and mount L_3 between C_2 and C_3 . Adjust L_3 until the circuit $L_3C_2C_3$ resonates at 112 Mc. Next, disconnect L_3 and follow a similar procedure starting from the other end with L_3 and C_4 . Finally, reconnect all coils; a check at any point in the filter should show resonance at 160 Mc.

Filter Installation

To be effective, a low-pass filter must be installed so that all the output of the transmitter flows through it. If harmonic currents are permitted to flow on the outside of the connecting coaxial cables, they will simply flow over the filter and on up to the antenna, and the filter does not have an opportunity to stop them.

Fig. 23-28 shows the proper way to install a filter between a shielded transmitter and a matching circuit. The coax, together with the

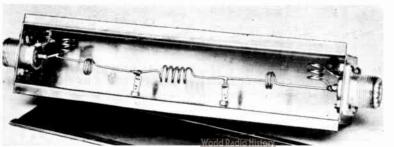


Fig. 23-26—A 52-ohm low-pass filter for 144-Mc. Transmitters. Case is made from flashing copper and is 1½ inches square by 7½ inches long. Cover slips on flanges folded out at the bottom; ends are folded down and soldered.

Fig. 23-27—Low-pass filter for 144-Mc. operation through 50-ohm coaxial line.

C₁, C₄—10- $\mu\mu$ f. ceramic (Sprague 10TS-Q10). C₂, C₃—39- $\mu\mu$ f. ceramic (Sprague 10TS-Q39).

J1, J2-Coaxial fitting (SO-239).

L₁, L₅—3 turns, ¼-inch long, leads ¼-inch long each end. L₂, L₄—2 turns ½-inch long, leads 1 inch long each end. L₈—5 turns ¾-inch long, leads %-inch long each end. All coils of No. 18 tinned copper, ¼-inch diam.

shields about the transmitter and filter, forms a continuous shield to keep all the r.f. inside. The r.f. forced to flow through the filter and the harmonics are attenuated. If there is no harmonic energy left after passing through the filter, shielding from that point on is not necessary. However, the antenna-coupler chassis arrangement shown in Fig. 23-28 is desirable because it will tend to prevent fundamental-frequency energy from flowing from the matching circuit back over the transmitter; this helps eliminate feed-back troubles in audio systems.

When a filter does not seem to give the harmonic attenuation of which it should be capable, the probable reason is that harmonics are bypassing it because of improper installation and inadequate transmitter shielding, including lead filtering. However, occasionally there are cases where the circuits formed by the cables and the apparatus to which they connect become reso-

nant at a harmonic frequency. This greatly increases the harmonic output at that frequency. Such troubles can be completely overcome by substituting a slightly different cable length. The most critical length is that connecting the transmitter to the filter. Checking with a grid-dip meter at the final amplifier output coil usually will show whether an unfavorable resonance of this type exists.

SUMMARY

The methods of harmonic elimination outlined in this chapter have been proved beyond doubt to be effective even under highly unfavorable conditions. It must be emphasized once more, however, that the problem must be solved one step at a time, and the procedure must be in logical order. It cannot be done properly without two items of simple equipment: a griddip meter and wavemeter covering the TV bands, and a dummy antenna.

To summarize:

1) Take a critical look at the transmitter on

the basis of the design considerations outlined under "Reducing Harmonic Generation".

2) Check all circuits, particularly those connected with the final amplifier, with the grid-dip meter to determine whether there are any resonances in the TV bands. If so, rearrange the circuits so the resonances are moved out of the critical frequency region.

3) Connect the transmitter to the dummy antenna and check with the wavemeter for the presence of harmonics on leads and around the transmitter enclosure. Seal off the weak spots in the shielding and filter the leads until the wavemeter shows no indication at any harmonic frequency.

4) At this stage, check for interference with a TV receiver. If there is interference, determine the cause by the methods described previously and apply the recommended remedics until the interference disappears.

5) When the transmitter is completely clean on the dummy antenna, connect it to the regular antenna and check for interference on the TV receiver. If the interference is not bad, an antenna coupler or matching circuit installed as previously described should clear it up. Alternatively, a low-pass filter may be used. If neither the antenna coupler nor filter makes any difference in the interference, the evidence is strong that the interference, at least in part, is being caused by receiver overloading because of the strong fundamental-frequency field about the TV antenna and receiver. (See later section for identification of fundamental-frequency interference.) A coupler and/or filter, installed as described above, will invariably make a difference in the intensity of the interference if the interference is caused by transmitter harmonics alone.

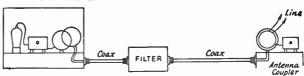


Fig. 23-28—The proper method of installing a low-pass filter between the transmitter and antenna coupler or matching circuit. If the antenna is fed through coax the antenna coupler may be omitted but the same construction should be used between the transmitter and filter. The filter should be thoroughly shielded.

6) If there is still interference after installing the coupler and/or filter, and the evidence shows that it is probably caused by a harmonic, more attenuation is needed. A more elaborate filter may be necessary. However, it is well at this stage to assume that part of the interference may be caused by receiver overloading, and take steps to alleviate such a condition before trying highly-elaborate filters, traps, etc., on the transmitter.

HARMONICS BY RECTIFICATION

Even though the transmitter is completely free from harmonic output it is still possible for interference to occur because of harmonics 568 BCI AND TVI

generated outside the transmitter. These result from rectification of fundamental-frequency currents induced in conductors in the vicinity of the transmitting antenna. Rectification can take place at any point where two conductors are in poor electrical contact, a condition that frequently exists in plumbing, downspouting, BX cables crossing each other, and numerous other places in the ordinary residence. It also can occur in any exposed vacuum tubes in the station, in power supplies, speech equipment, etc., that may not be enclosed in the shielding about the r.f. circuits. Poor joints anywhere in the antenna system are especially bad, and rectification also may take place in the contacts of antenna changeover relays. Another common cause is overloading the front end of the communications receiver when it is used with a separate antenna (which will radiate the harmonics generated in the first tube) for break-in.

Rectification of this sort will not only cause harmonic interference but also is frequently responsible for cross-modulation effects. It can be detected in greater or less degree in most locations, but fortunately the harmonics thus generated are not usually of high amplitude. However, they can cause considerable interference in the immediate vicinity in fringe areas, especially when operation is in the 28-Mc. band. The amplitude decreases rapidly with the order of the harmonic, the second and third being the worst. It is ordinarily found that even in cases where destructive interference results from 28-Mc. operation the interference is comparatively mild from 14 Mc., and is negligible at still lower frequencies.

Nothing can be done at either the transmitter or receiver when rectification occurs. The remedy is to find the source and eliminate the poor contact either by separating the conductors or bonding them together. A crystal wavemeter (tuned to the fundamental frequency) is useful for hunting the source, by showing which conductors are carrying r.f. and, comparatively, how much.

Interference of this kind is frequently intermittent since the rectification efficiency will vary with vibration, the weather, and so on. The possibility of corroded contacts in the TV receiving antenna should not be overlooked, especially if it has been up a year or more.

TV RECEIVER DEFICIENCIES

Front-End Overloading

When a television receiver is quite close to the transmitter, the intense r.f. signal from the transmitter's fundamental may overload one or more of the receiver circuits to produce spurious responses that cause interference.

If the overload is moderate, the interference is of the same nature as harmonic interference; it is caused by harmonics generated in the early stages of the receiver and, since it occurs only on channels harmonically related to the transmitting frequency, is difficult to distinguish

from harmonics actually radiated by the transmitter. In such cases additional harmonic suppression at the transmitter will do no good, but any means taken at the receiver to reduce the strength of the amateur signal reaching the first tube will effect an improvement. With very severe overloading, interference also will occur on channels not harmonically related to the transmitting frequency, so such cases are easily identified.

Cross-Modulation

Upon some circumstances overloading will result in cross-modulation or mixing of the amateur signal with that from a local f.m. or TV station. For example, a 14-Mc. signal can mix with a 92-Mc. f.m. station to produce a beat at 78 Mc. and cause interference in Channel 5, or with a TV station on Channel 5 to cause interference in Channel 3. Neither of the channels interfered with is in harmonic relationship to 14 Mc. Both signals have to be on the air for the interference to occur, and eliminating either at the TV receiver will eliminate the interference.

There are many combinations of this type, depending on the band in use and the local frequency assignments to f.m. and TV stations. The interfering frequency is equal to the amateur fundamental frequency either added to or subtracted from the frequency of some local station, and when interference occurs in a TV channel that is not harmonically related to the amateur transmitting frequency the possibilities in such frequency combinations should be investigated.

I. F. Interference

Some TV receivers do not have sufficient selectivity to prevent strong signals in the intermediate-frequency range from forcing their way through the front end and getting into the i.f. amplifier. The once-standard intermediate frequency of, roughly, 21 to 27 Mc., is subject to interference from the fundamental-frequency output of transmitters operating in the 21-Mc. band. Transmitters on 28 Mc. sometimes will cause this type of interference as well.

A form of i.f. interference peculiar to 50-Mc. operation near the low edge of the band occurs with some receivers having the standard "41-Mc." i.f., which has the sound carrier at 41.25 Mc. and the picture carrier at 45.75 Mc. Sol-Mc. signal that forces its way into the i.f. system of the receiver will beat with the i.f. picture carrier to give a spurious signal on or near the i.f. sound carrier, even though the interfering signal is not actually in the nominal passband of the i.f. amplifier.

There is a type of i.f. interference unique to the 144-Mc. band in localities where certain u.h.f. TV channels are in operation, affecting only those TV receivers in which double-conversion type plug-in u.h.f. tuning strips are used. The design of these strips involves a first intermediate frequency that varies with the TV channel to be received and, depending on the particular strip design, this first i.f. may be in

or close to the 144-Mc. amateur band. Since there is comparatively little selectivity in the TV signal-frequency circuits ahead of the first i.f., a signal from a 144-Mc. transmitter will "ride into" the i.f., even when the receiver is at a considerable distance from the transmitter. The channels that can be affected by this type of i.f. interference are:

Receivers with 21-Mc. second i.f.	Receivers with 41-Mc. second i.f.*		
Channels 14–18, inc.	Channels 20-25, inc.		
Channels 41–48, inc.	Channels 51-58, inc.		
Channels 69–77, inc.	Channels 82 and 83.		

If the receiver is not close to the transmitter, a trap of the type shown in Fig. 23-31 will be effective. However, if the separation is small the 144-Mc. signal will be picked up directly on the receiver circuits and the best solution is to readjust the strip oscillator so that the first i.f. is moved to a frequency not in the vicinity of the 144-Mc. band. This has to be done by a competent technician.

I.f. interference is easily identified since it occurs on all channels—although sometimes the intensity varies from channel to channel—and the cross-hatch pattern it causes will rotate when the receiver's fine-tuning control is varied. When the interference is caused by a harmonic, overloading, or cross modulation, the structure of the interference pattern does not change (its intensity may change) as the fine-tuning control is varied.

High-Poss Filters

In all of the above cases the interference can be eliminated if the fundamental signal strength can be reduced to a level that the receiver can handle. To accomplish this with signals on bands below 30 Mc., the most satisfactory device is a high-pass filter having a cut-off frequency between 30 and 54 Mc., installed at the tuner input terminals of the receiver. Circuits

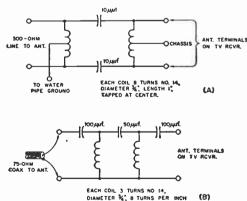


Fig. 23-29—High-pass filters for installation at the TV receiver antenna terminals. A—balanced filter for 300-ohm line, B—for 75-ohm coaxial line. Important: Do not use a direct ground on the chassis of a transformerless receiver. Ground through a 0.001-μf. mica capacitor.

that have proved effective are shown in Figs. 23-29 and 23-30. Fig. 23-30 has one more section than the filters of Fig. 23-29 and as a consequence has somewhat better cut-off characteristics. All the circuits given are designed to have little or no effect on the TV signals but will attenuate all signals lower in frequency than about 40 Mc. These filters preferably should be constructed in some sort of shielding container, although shielding is not always necessary. The dashed lines in Fig. 23-30 show how individual filter coils can be shielded from each other. The capacitors can be tubular ceramic units centered in holes in the partitions that separate the coils.

Simple high-pass filters cannot always be applied successfully in the case of 50-Mc. transmissions, because they do not have sufficiently-sharp cut-off characteristics to give both good attenuation at 50-54 Mc. and no attenuation above 54 Mc. A more elaborate design capable of giving the required sharp cut-off has been described (Ladd, "50-Mc. TVI—Its Causes and Cures," QST, June and July, 1954). This article

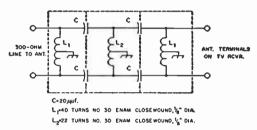


Fig. 23-30—Another type of high-pass filter for 300ohm line. The coils may be wound on ½-inch diameter plastic knitting needles. *Important:* Do not use a direct ground on the chassis of a transformerless receiver. Ground through a 0.001-μf. mica capacitor.

also contains other information useful in coping with the TVI problems peculiar to 50-Mc. operation. As an alternative to such a filter, a high-O wave trap tuned to the transmitting frequency may be used, suffering only the disadvantage that it is quite selective and therefore will protect a receiver from overloading over only a small range of transmitting frequencies in the 50-Mc. band. A trap of this type using quarter-wave sections of Twin-Lead is shown in Fig. 23-31. These "suck-out" traps, while absorbing energy at the frequency to which they are tuned, do not affect the receiver operation otherwise. The assembly should be slid along the TV antenna lead-in until the most effective position is found, and then fastened securely in place with Scotch Tape. An insulated tuning tool should be used for adjustment of the trimmer capacitor, since it is at a "hot" point and will show considerable body-capacitance effect.

High-pass filters are available commercially at moderate prices. In this connection, it should be understood by all parties concerned that while an amateur is responsible for *harmonic* radiation from his transmitter, it is no part of his

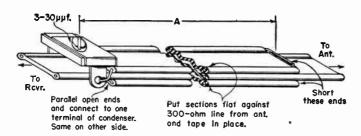


Fig. 23-31—Absorption-type wave trap using sections of 300-ohm line tuned to have an electrical length of ¼ wavelength at the transmitter frequency. Approximate physical lengths (dimension A) are 40 inches for 50 Mc. and 11 inches for 144 Mc., allowing for the loading effect of the capacitance at the open end. Two traps are used in parallel, one on each side of the line to the receiver.

responsibility to pay for or install filters, wave traps, etc. that may be required at the receiver to prevent interference caused by his fundamental frequency. The set owner should be advised to get in touch with the organization from which he purchased the receiver or which services it, to make arrangements for proper installation. Proper installation usually requires that the filter be installed right at the input terminals of the r.f. tuner of the TV set and not merely at the external antenna terminals, which may be at a considerable distance from the tuner. The question of cost is one to be settled between the set owner and the organization with which he deals.

Some of the larger manufacturers of TV receivers have instituted arrangements for cooperating with the set dealer in installing highpass filters at no cost to the receiver owner. FCC-sponsored TVI Committees, now operating in many cities, have all the information necessary for effectuating such arrangements. To find out whether such a committee is functioning in your community, write to the FCC field office having jurisdiction over your location. A list of the field offices is contained in The Radio Amateur's License Manual, published by ARRL.

If the fundamental signal is getting into the receiver by way of the line cord a line filter such as that shown in Fig. 23-1 may help. To be most effective it should be installed inside the receiver chassis at the point where the cord enters, making the ground connections directly to chassis at this point. It may not be so helpful if placed between the line plug and the wall socket unless the r.f. is actually picked up on the house wiring rather than on the line cord itself.

Antenna Installation

Usually, the transmission line between the TV receiver and the actual TV antenna will pick up a great deal more energy from a nearby transmitter than the television receiving antenna itself. The currents induced on the TV transmission line in this case are of the "parallel" type, where the phase of the current is the same in both conductors. The line simply acts like two wires connected together to operate as one. If the receiver's antenna input circuit were perfectly balanced it would reject these "parallel" or "unbalance" signals and respond only to the

true transmission-line ("push-pull") currents; that is, only signals picked up on the actual antenna would cause a receiver response. However, no receiver is perfect in this respect, and many TV receivers will respond strongly to such parallel currents. The result is that the signals from a nearby amateur transmitter are much more intense at the first stage in the TV receiver than they would be if the receiver response were confined entirely to energy picked up on the TV antenna alone. This situation can be improved by using shielded transmission line -coax or, in the balanced form, "twinax"for the receiving installation. For best results the line should terminate in a coax fitting on the receiver chassis, but if this is not possible the shield should be grounded to the chassis right at the antenna terminals.

The use of shielded transmission line for the receiver also will be helpful in reducing response to harmonics actually being radiated from the transmitter or transmitting antenna. In most receiving installations the transmission line is very much longer than the antenna itself, and is consequently far more exposed to the harmonic fields from the transmitter. Much of the harmonic pickup, therefore, is on the receiving transmission line when the transmitter and receiver are quite close together. Shielded line, plus relocation of either the transmitting or receiving antenna to take advantage of directive effects, often will result in reducing overloading, as well as harmonic pickup, to a level that does not interfere with reception.

U.H.F. TELEVISION

Harmonic TVI in the u.h.f. TV band is far less troublesome than in the v.h.f. band. Harmonics from transmitters operating below 30 Mc. are of such high order that they would normally be expected to be quite weak; in addition, the components, circuit conditions and construction of low-frequency transmitters are such as to tend to prevent very strong harmonics from being generated in this region. However, this is not true of amateur v.h.f. transmitters, particularly those working in the 144-Mc. and higher bands. Here the problem is quite similar to that of the low v.h.f. TV band with respect to transmitters operating below 30 Mc.

There is one highly favorable factor in u.h.f.

		TA	BLE 23-I			
Ha	rmonic Relations	hip—Amateur	V.H.F. Bands	and U.H.F. 1	V Channels	
Amateur Band Harmonic	Fundamental Freq. Range	Affected	Amateur Band	Harmonic	Fundamental Freq. Range	Affected
144 Mc. 4th	144.0-144.5 144.5-146.0	31 32	220 Mc.	3rd	220–220.67 220.67–222.67	45 46
.	146.0–147.5 147.5–148.0	33 34			222.67-224.67 224.67-225	47 48
5th	144.0–144.4 144.4–145.6	55 56		4th	220–221 221–222.5	82 83
	145.6–146.8 146.8–148	57 58	420 Mc.	2nd	420–421 421–424	75 76
6th	144–144.33 144.33–145.33	79 80			424-427 427-430	77 78
	145.33–147.33 147.33–148	81 82			430-433 433-436	79 80

TV that does not exist in the most of the v.h.f. TV band: If harmonics are radiated, it is possible to move the transmitter frequency sufficiently (within the amateur band being used) to avoid interfering with a channel that may be in use in the locality. By restricting operation to a portion of the amateur band that will not result in harmonic interference, it is possible to avoid the necessity for taking extraordinary precautions to prevent harmonic radiation.

The frequency assignment for u.h.f. television consists of seventy 6-megacycle channels (Nos. 14 to 83, inclusive) beginning at 470 Mc. and ending at 890 Mc. The harmonics from amateur bands above 50 Mc. span the u.h.f. channels as shown in Table 23-I. Since the assignment plan calls for a minimum separation of six channels between any two stations in one locality, there is ample opportunity to choose a fundamental frequency that will move a harmonic out of range of a local TV frequency.

COLOR TELEVISION

The color TV signal includes a subcarrier spaced 3.58 megacycles from the regular picture carrier (or 4.83 Mc. from the low edge of the channel) for transmitting the color information. Harmonics which fall in the color subcarrier region can be expected to cause break-up of color in the received picture. This modifies the chart of Fig. 23-3 to introduce another "severe" region centering around 4.8 Mc. measured from the low-frequency edge of the channel. Hence with color television reception there is less opportunity to avoid harmonic interference by choice of operating frequency. In other respects the problem of eliminating interference is the same as with black-and-white television.

INTERFERENCE FROM TV RECEIVERS

The TV picture tube is swept horizontally by the electron beam 15,750 times per second, using a wave shape that has very high harmonic content. The harmonics are of appreciable amplitude even at frequencies as high as 30 Mc., and when radiated from the receiver can cause considerable interference to reception in the amateur bands. While measures to suppress radiation of this nature are required by FCC in current receivers, many older sets have had

no such treatment. The interference takes the form of rather unstable, a.c.-modulated signals spaced at intervals of 15.75 kc.

Studies have shown that the radiation takes place principally in three ways, in order of their importance: (1) from the a.c. line, through stray coupling to the sweep circuits; (2) from the antenna system, through similar coupling; (3) directly from the picture tube and sweepcircuit wiring. Line radiation often can be reduced by bypassing the a.c. line cord to the chassis at the point of entry, although this is not completely effective in all cases since the coupling may take place outside the chassis beyond the point where the bypassing is done. Radiation from the antenna is usually suppressed by installing a high-pass filter on the receiver. The direct radiation requires shielding of high-potential leads and, in some receivers, additional bypassing in the sweep circuit; in severe cases, it may be necessary to line the cabinet with screening or similar shielding ma-

Incidental radiation of this type from TV and broadcast receivers, when of sufficient intensity to cause serious interference to other radio services (such as amateur), is covered by Part 15 of the FCC rules. When such interference is caused, the user of the receiver is obligated to take steps to eliminate it. The owner of an offending receiver should be advised to contact the source from which the receiver was purchased for appropriate modification of the receiving installation. TV receiver dealers can obtain the necessary information from the set manufacturer.

It is usually possible to reduce interference very considerably, without modifying the TV receiver, simply by having a good amateur-band receiving installation. The principles are the same as those used in reducing "hash" and other noise — use a good antenna, such as the transmitting antenna, for reception; install it as far as possible from a.c. circuits; use a good feeder system such as a properly balanced two-wire line or coax with the outer conductor grounded; use coax input to the receiver, with a matching circuit if necessary; and check the receiver to make sure that it does not pick up signals or noise with the antenna disconnected.

Operating a Station

The enjoyment of our hobby comes mostly from the operation of our station once we have finished its construction. Upon the station and its operation depend the communication records that are made. The standing of individuals as amateurs and respect for the capabilities of the whole institution of amateur radio depend to a considerable extent on the practical communications established by amateurs, the aggregate of all our station efforts.

An operator with a slow, steady, clean-cut method of sending has a big advantage over the poor operator. The technique of speaking in connected thoughts and phrases is equally important for the voice operator. Good sending is partly a matter of practice but patience and judgment are just as important qualities of an operator as a good "fist."

Operating knowledge embracing standard procedures, development of skill in employing c.w. to expand the station range and operating effectiveness at minimum power levels and some net know-how are all essentials in achieving a triumphant amateur experience with top station records, personal results, and demonstrations of what our stations can do in practical communications.

OPERATING COURTESY AND TOLERANCE

Normal operating interests in amateur radio vary considerably. Some prefer to rag-chew, others handle traffic, others work DX, others concentrate on working certain areas, countries or states and still others get on for an occasional contact only to check a new transmitter or antenna.

Interference is one of the things we amateurs have to live with. However, we can conduct our operating in a way designed to alleviate it as much as possible. Before putting the transmitter on the air, listen on your own frequency. If you



hear stations engaged in communication on that frequency, stand by until you are sure no interference will be caused by your operations, or shift to another frequency. No amateur or any group of amateurs has any exclusive claim to any frequency in any band. We must work together, each respecting the rights of others. Remember, those other chaps can cause you as much interference as you cause them, sometimes more!

In this chapter we'll recount some fundamentals of operating success, cover major procedures for successful general work and include proper forms to use in message handling and other fields. Note also the sections on special activities, awards and organization. These permit us all to develop through our organization more success together than we could ever attain by separate uncoordinated efforts that overlook the precepts established through operating experience.

C.W. PROCEDURE

The best operators, both those using voice and c.w., observe certain operating procedures regarded as "standard practice."

1) Calls. Calling stations may call efficiently by transmitting the call signal of the station called three times, the letters DE, followed by one's own station call sent three times. (Short calls with frequent "breaks" to listen have proved to be the best method.) Repeating the call of the station called four or five times and signing not more than two or three times has proved excelent practice, thus: WØBY WØBY WØBY WØBY WØBY WØBY WØBY DE W1AW W1AW W1AW AR.

CQ. The general-inquiry call (CQ) should be sent not more than five times without interspersing one's station identification. The length of repeated calls is carefully limited in intelligent amateur operating. (CQ is not to be used when testing or when the sender is not expecting or looking for an answer. Never send a CQ "blind." Listen on the transmitting frequency first.)

The directional CQ: To avoid useless answers and lessen QRM, every CQ call should be made informative when possible. Respect, do not answer, such calls not applicable to you.

Examples: A United States station looking for any Hawaiian amateur calls: CQ KH6 CQ KH6 DE W41A W41A W41A K. A Western station with traffic for the East Coast when looking for an intermediate relay station calls: CQ EAST CQ EAST CQ EAST DE W51GW W51GW W51GW K. A station with messages for points in Massachusetts calls: CQ MASS CQ MASS DE W7CZY W7CZY W7CZY K.

Hams who do not raise stations readily may find that their sending is poor, their calls ill-timed or their judgment in error. When conditions are right to bring in signals from the desired locality, you can call them. Short calls, at about the same frequency, with breaks to listen, will raise stations with minimum time and trouble.

2) Answering a Call: Call three times (or less); send DE; sign three times (or less); after contact is established decrease the use of the call signals of both stations to once or twice. When a station receives a call but does not receive the call letters of the station calling, QRZ? may be used. It means "By whom am I being called?" QRZ should not be used in place of CQ.

3) Ending Signals and Sign-Off: The proper use of \overline{AR} , \overline{KN} , \overline{SK} and \overline{CL} ending signals is as follows:

AR—End of transmission. Recommended after call to a specific station before contact has been established.

Example: W6ABC W6ABC W6ABC W6ABC W6ABC DE W9LMN W9LMN AR. Also at the end of transmission of a radiogram, immediately following the signature, preceding identification.

K—Go ahead (any station). Recommended after CQ and at the end of each transmission during QSO when there is no objection to others breaking in.

Example: CQ CQ CQ DE W1ABC W1ABC K or W9XYZ DE W1ABC K.

KN—Go ahead (specific station), all others keep out. Recommended at the end of each transmission during a QSO, or after a call, when calls from other stations are not desired and will not be answered.

Example: W4FGH DE EL4A KN.

SK—End of QSO. Recommended before signing last transmission at end of a QSO.

Example: SK W8LMN DE W5BCD.

CL—I am closing station. Recommended when a station is going off the air, to indicate that it will not listen for any further calls.

Example: SK W7HIJ DE W2JKL

- 4) Testing. When it is necessary for a station to make test signals they must not continue for more than 10 seconds and must be composed of a series of VVV followed by the call sign of the station emitting the test signals. Always listen first to find a clear spot if possible, to avoid causing unwarranted QRM of a QSO in progress.
- 5) Receipting for conversation or traffic: Never receipt for a transmission until it has been entirely received. "R" means "transmission received as sent." Use R only when all is received correctly.
- 6) Repeats. When most of a transmission is lost, a call should be followed by correct abbreviations to ask for repeats. When a few words on the end of a transmission are lost, the last word received correctly is given after? AA, meaning

"all after." When a few words at the beginning of a transmission are lost, ?AB for "all before" a stated word should be used. The quickest way to ask for a fill in the middle of a transmission is to send the last word received correctly, a question mark, then the next word received correctly. Another way is to send "?BN [word] and [word]."

Do not send words twice (QSZ) unless it is requested. Send single. Do not fall into the bad habit of sending double without a request from fellows you work. Don't say "QRM" or "QRN" when you mean "QRS." Don't CQ unless there is definite reason for so doing. When sending CQ, use judgment.

General Practices

When a station has receiving trouble, the operator asks the transmitting station to "QSV." The letter "R" is often used in place of a decimal point (e.g., "3R5 Mc.") or the colon in time designation (e.g., "2R30 PM"). A long dash is sometimes sent for "zero."

The law concerning superfluous signals should be noted. If you *must* test, disconnect the antenna system and use an equivalent "dummy" antenna. Send your call frequently when operating. Pick a time for adjusting the station apparatus when few stations will be bothered.

The up-to-date amateur station uses "breakin." For best results send at a medium speed. Send evenly with proper spacing. The standardtype telegraph key is best for all-round use. Regular daily practice periods, two or three periods a day, are best to acquire real familiarity and proficiency with code.

No excuse can be made for "garbled" copy. Operators should copy what is sent and refuse to acknowledge a whole transmission until every word has been received correctly. Good operators do not guess. "Swing" in a fist is not the mark of a good operator. Unusual words are sent twice, the word repeated following the transmission of "?". If not sure, a good operator systematically asks for a fill or repeat. Sign your call frequently, interspersed with calls, and at the end of all transmissions.

On Good Sending

Assuming that an operator has learned sending properly, and comes up with a precision "fist"— not fast, but clean, steady, making well-formed rhythmical characters and spacing beautiful to listen to— he then becomes subject to outside pressures to his own possible detriment in everyday operating. He will want to "speed it up" because the operator at the other end is going faster, and so he begins, unconsciously, to run his words together or develops a "swing."

Perhaps one of the easiest ways to get into bad habits is to do too much playing around with special keys. Too many operators spend only enough time with a straight key to acquire "passable" sending, then subject their newly-developed "fists" to the entirely different movements of bugs, side-swipers, electronic keys, or

what-have-you. All too often, this results in the ruination of what might have become a very good "fist."

Think about your sending a little. Are you satisfied with it? You should not be—ever. Nobody's sending is perfect, and therefore every operator should continually strive for improvement. Do you ever run letters together — like Q for MA, or P for AN — especially when you are in a hurry? Practically everybody does at one time or another. Do you have a "swing"? Any recognizable "swing" is a deviation from perfection. Strive to send like tape sending; copy a W1AW Bulletin and try to send it with the same spacing using a local oscillator on a subsequent transmission.

Check your spacing in characters, between characters and between words occasionally by making a recording of your fist on an inked tape recorder. This will show up your faults as nothing else will. Practice the correction of faults.

USING A BREAK-IN SYSTEM

Break-in avoids unnecessarily long calls, prevents QRM, gives more communication per hour of operating. Brief calls with frequent short pauses for reply can approach (but not equal) break-in efficiency.

A separate receiving antenna facilitates breakin operation. It is only necessary with breakin to pause just a moment with the key up (or to cut the carrier momentarily and pause in a phone conversation) to listen for the other station. The click when the carrier is cut off is as effective as the word "break."

C.w. telegraphy break-in is usually simple to arrange. With break-in, ideas and messages to be transmitted can be pulled right through the holes in the QRM. Snappy, efficient amateur work with break-in usually requires a separate receiving antenna and arrangement of the transmitter and receiver to eliminate the necessity for throwing switches between transmissions.

In calling, the transmitting operator sends the letters "BK" at intervals during his call so that stations hearing the call may know that break-in is in use and take advantage of the fact. He pauses at intervals during his call, to listen for a moment for a reply. If the station being called does not answer, the call can be continued.

With a tap of the key, the man on the receiving end can interrupt (if a word is missed). The other operator is constantly monitoring, awaiting just such directions. It is not necessary that you have perfect facilities to take advantage of break-in when the stations you work are break-in-equipped. After an invitation to break is given (and at each pause) press your key—and contact can start immediately.

VOICE OPERATING

The use of proper procedure to get best results is just as important as in using code. In telegraphy words must be spelled out letter by letter. It is therfore but natural that abbreviations and shortcuts should have come into widespread use.

Voice-Operating Hints

1) Listen before calling.

2) Make short calls with breaks to listen. Avoid long CQs; do not answer over-long CQs.

Use push-to-talk or voice control. Give essential data concisely in first transmission.

- 4) Make reports honest. Use definitions of strength and readability for reference. Make your reports informative and useful. Honest reports and full word description of signals save amateur operators from FCC trouble.
- 5) Limit transmission length. Two minutes or less will convey much information. When three or more stations converse in round tables, brevity is essential.
- 6) Display sportsmanship and courtesy. Bands are congested . . . make transmissions meaningful . . . give others a break.
- 7) Check transmitter adjustment . . . avoid a.m. overmodulation and splatter. On s.s.b. check carrier balance carefully. Do not radiate when moving v.f.o. frequency or checking n.f.m. swing. Use receiver b.f.o. to check stability of signal. Complete testing before busy hours!

In voice work, however, abbreviations are not necessary, and should have less importance in our operating procedure.

The letter "K" has been agreed to in telegraphic practice so that the operator will not have to pound out the separate letters that spell the words "go ahead." The voice operator can say the words "go ahead" or "over," or "come in please."

One laughs on c.w. by spelling out HI. On phone *use* a laugh when one is called for. Be natural as you would with your family and friends.

The matter of reporting readability and strength is as important to phone operators as to those using code. With telegraph nomenclature, it is necessary to spell out words to describe signals or use abbreviated signal reports. But on voice, we have the ability to "say it with words." "Readability four, Strength eight" is the best way to give a quantitative report. Reporting can be done so much more meaningfully with ordinary words: "You are weak but you are in the clear and I can understand you, so go ahead," or "Your signal is strong but you buried under local interference." Why not say it with words?

Voice Equivalents to Code Procedure

Voice	Code	Meaning
Go ahead; over	K	Self-explanatory
Wait; stand by Received	ĀS R	Self-explanatory Receipt for a correctly- transcribed message or for "solid" transmis- sion with no missing portions

Phone-Operating Practice

Efficient voice communication, like good c.w. communication, demands good operating. Adherence to certain points "on getting results" will go a long way toward improving our phoneband operating conditions.

Use push-to-talk technique. Where possible arrange on-off switches, controls or voice-con-

trolled break-in for fast back-and-forth exchanges that emulate the practicality of the wire telephone. This will help reduce the length of transmissions and keep brother amateurs from calling you a "monologuist" — a guy who likes to hear himself talk!

Listen with care. Keep noise and "backgrounds" out of your operating room to facilitate good listening. It is natural to answer the strongest signal, but take time to listen and give some consideration to the best signals, regardless of strength. Every amateur cannot run a kilowatt, but there is no reason why every amateur cannot have a signal of good quality, and utilize uniform operating practices to aid in the understandability and ease of his own communications.

Interpose your call regularly and at frequent intervals. Three short calls are better than one long one. In calling CQ, one's call should certainly appear at least once for every five or six CQs. Calls with frequent breaks to listen will save time and be most productive of results. In identifying, always transmit your own call last. Don't say "This is W1ABC standing by for W2DEF"; say "W2DEF, this is W1ABC, over." FCC regulations show the call of the transmitting station sent last.

Include country prefix before call. It is not correct to say "9RRX, this is 1BDI." Correct and legal use is "W9RRX, this is W1BDI." FCC regulations require proper use of calls; stations have been cited for failure to comply with this requirement.

Monitor your own frequency. This helps in timing calls and transmissions. Transmit when there is a chance of being copied successfully—not when you are merely "more QRM." Timing transmissions is an art to cultivate.

Keep modulation constant. By turning the gain "wide open" you are subjecting anyone listening to the diversion of whatever noises are present in or near your operating room, to say nothing of the possibility of feedback, echo due to poor acoustics, and modulation excesses due to sudden loud noises. Speak near the microphone, and don't let your gaze wander all over the station causing sharply-varying input to your speech amplifier; at the same time, keep far enough from the microphone so your signal is not modulated by your breathing. Change distance or gain only as necessary to insure uniform transmitter performance without overmodulation, splatter or distortion.

Make connected thoughts and phrases. Don't mix disconnected subjects. Ask questions consistently. Pause and get answers.

Have a pad of paper handy. It is convenient and desirable to jot down questions as they come in the course of discussion in order not to miss any. It will help you to make intelligent to-the-point replies.

Steer clear of inanities and soap-opera stuff.
Our amateur radio and also our personal reputation as serious communications workers depend on us.

Avoid repetition. Don't repeat back what the

other fellow has just said. Too often we hear a conversation like this: "Okay on your new antenna there, okay on the trouble you're having with your receiver, okay on the company who just came in with some ice cream, okay . . . [etc.]." Just say you received everything O.K. Don't try to prove it.

Use phonetics only as required. When clarifying genuinely doubtful expessions and in getting your call identified positively we suggest use of the ARRL Phonetic List. Limit such use to really-necessary clarification.

The speed of radiotelephone transmission (with perfect accuracy) depends almost entirely upon the skill of the two operators involved. One must learn to speak at a rate allowing perfect understanding as well as permitting the receiving operator to copy down the message text, if that is necessary. Because of the similarity of many English speech sounds, the use of alphabetical word lists has been found necessary. All voice-operated stations should use a standard list as needed to identify call signals or unfamiliar expressions.

ARRL Word List for Radiotelephony

ADAM	JOHN	SUSAN
BAKER	KING	THOMAS
CHARLIE	LEWIS	UNION
DAVID	MARY	VICTOR
EDWARD	NANCY	WILLIAM
FRANK	ОТТО	X-RAY
GEORGE	PETER	YOUNG
HENRY	QUEEN	ZEBRA
IDA	ROBERT	

Example: W1AW . . . W 1 ADAM WILLIAM . . . W1AW

Round Tables. The round table has many advantages if run properly. It clears frequencies of interference, especially if all stations involved are on the same frequency, while the enjoyment value remains the same, if not greater. By use of push-to-talk, the conversation can be kept lively and interesting, giving each station operator ample opportunity to participate without waiting overlong for his turn.

Round tables can become very unpopular if they are not conducted properly. The monologuist, off on a long spiel about nothing in particular, cannot be interrupted; make your transmissions short and to the point. "Butting in" is discourteous and unsportsmanlike; don't enter a round table, or any contact between two other amateurs, unless you are invited. It is bad enough trying to copy through prevailing interference without the added difficulty of poor voice quality; check your transmitter adjustments frequently. In general, follow the precepts as hereinbefore outlined for the most enjoyment in round tables as well as any other form of radiotelephone communication.

WORKING DX

Most amateurs at one time or another make "working DX" a major aim. As in every other phase of amateur work, there are right and wrong ways to go about getting best results in

working foreign stations, and it is the intention of this section to outline a few of them.

The ham who has trouble raising DX stations readily may find that poor transmitter efficiency is not the reason. He may find that his sending is poor, or his calls ill-timed, or his judgment in error. When conditions are right to bring in the DX, and the receiver sensitive enough to bring in several stations from the desired locality, the way to work DX is to use the appropriate frequency and timing and call these stations, as against the common practice of calling "CQ DX."

The call CQ DX means slightly different things to amateurs in different bands:

a) On v.h.f., CQ DX is a general call ordinarily used only when the band is open, under favorable "skip" conditions. For v.h.f. work, such a call is used for looking for new states and countries, also for distances beyond the customary "line-of-sight" range on most v.h.f. bands.

b) CQ DX on our 7-, 14-, 21- and 28-Mc. bands may be taken to mean "General call to any foreign station." The term "foreign station" usually refers to any station in a foreign continent. (Experienced amateurs in the U. S. A. and Can-

DX OPERATING CODE

(For W/VE Amateurs)

Some amateurs interested in DX work have caused considerable confusion and QRM in their efforts to work DX stations. The points below, if observed by all W/VE amateurs, will go a long way toward making DX more enjoyable for everybody.

- 1. Call DX only after he calls CQ, QRZ?, signs SK, or phone equivalents thereof
 - 2. Do not call a DX station:
 - a. On the frequency of the station he is working until you are sure the QSO is over. This is indicated by the ending signal \overline{SK} on c.w. and any indication that the operator is listening, on phone
 - b. Because you hear someone else calling
 - c. When he signs KN, AR, CL, or phone
 - d. Exactly on his frequency
 - e. After he calls a directional CQ, unless of course you are in the right direction or area.
- 3. Keep within frequency-band limits. Some DX stations operate outside. Perhaps they can get away with it, but you cannot
- 4. Observe calling instructions of DX stations. "10U" means call ten kc. up from his frequency, "15D" means 15 kc. down. etc.
- "15D" means 15 kc. down, etc.

 5. Give honest reports. Many foreign stations depend on W and VE reports for adjustment of station and equipment
- 6. Keep your signal clean. Key clicks, chirps, hum or splatter give you a bad reputation and may get you a citation from FCC.
- 7. Listen for and call the station you want. Calling CQ DX is not the best assurance that the rare DX will reply
- 8. When there are several W or VE stations waiting to work a DX station, avoid asking him to "listen for a friend." Let your friend take his chances with the rest. Also avoid engaging DX stations in rag-chews against their wishes.

ada do not use this call, but answer such calls made by foreign stations.)

c) CQ DX used on 3.5 Mc. under winter-night conditions may be used in this same manner. At other times, under average 3.5-Mc. propagation conditions, the call may be used in domestic work when looking for new states or countries in one's own continent, usually applying to stations located over 1000 miles distant from you.

The way to work DX is not to use a CQ call at all (in our continent). Instead, use your best tuning skill — and listen — and listen — and listen. You have to hear them before you can work them. Hear the desired stations first; time your calls well. Use your utmost skill. A sensitive receiver is often more important than the power input in working foreign stations. If you can hear stations in a particular country or area, chances are that you will be able to work someone there.



"---DO A LOT OF SHOOPING"

One of the most effective ways to work DX is to know the operating habits of the DX stations sought. Doing too much transmitting on the DX bands is not the way to do this. Again, *listening* is effective. Once you know the operating habits of the DX station you are after you will know when and where to call, and when to remain silent waiting your chance.

Some DX stations indicate where they will tune for replies by use of "10U" or "15D." (See point 4 of the DX Operating Code.) In voice work the overseas operator may say "listening on 14,225 kc." or "tuning upward from 28,500 kc." Many a DX station will not reply to a call on his exact frequency.

ARRL has recommended some operating procedures to DX stations aimed at controlling some of the thoughtless operating practices sometimes used by W/VE amateurs. A copy of these recommendations (Operating Aid No. 5) can be obtained free of charge from ARRL Headquarters.

In any band, particularly at line-of-sight frequencies, when directional antennas are used, the directional CQ such as CQ W5, CQ north, etc., is the preferable type of call. Mature amateurs agree that CQ DX is a wishful rather than a practical type of call for most stations in the North Americas looking for foreign contacts. Ordinarily, it is a cause of unnecessary QRM.

Conditions in the transmission medium often make it possible for the signals from low-powered transmitters to be received at great distances. In general, the higher the frequency band the less important power considerations become, for occasional DX work. This accounts in part

1-16-53			DIAL	SIGNALS AST	SIGNALS RET	FREQ. MC.	TYPE	WATTS	ENDING GSO	OTHER DATA
1815 V	MOTOD	×	3.65	589	569X	3.5	A1	250	1843	Tfc-rec'd 6, sent 10
1920	CQ	X				7				
1921	X	W4TWI	7.16	369	579				1932	Vy heavy QRM on me
21 25 V	W8UKS	×	3.83	59	47	3.9	Α3	100	2205	Sam '
1-18-53			-							
)705 \	VK4EL	×	14.03			14	A1	250		Answered a W6
2709 7	ZL2ACV	X	14.07	339	559X				0720	
0721	X	KA2KW	14.07	469X	349				0733	First KA
0736	CQ	X								
0737	X	W6TI	14.01	589	589C				0812	

KEEP AN ACCURATE AND COMPLETE STATION LOG AT ALL TIMESI F.C.C. REQUIRES IT.

A page from the official ARRL log is shown above, answering every Government requirement in respect to station records. Bound logs made up in accord with the above form can be obtained from Headquarters for a nominal sum or you can prepare your own, in which case we offer this form as a suggestion. The ARRL log has a special wire binding and lies perfectly flat on the table.

for the relative popularity of the 14-, 21- and 28-Mc. bands amoung amateurs who like to work DX.

KEEPING AN AMATEUR STATION LOG

The FCC requires every amateur to keep a complete station operating record. It may also contain records of experimental tests and ajustment data. A stenographer's notebook can be ruled with vertical lines in any form to suit the user. The Federal Communications Commission requirements are that a log be maintained that shows (1) the date and time of each transmission, (2) all calls and transmissions made (whether

two-way contacts resulted or not), (3) the input power to the last stage of the transmitter, (4) the frequency band used, (5) the time of ending each QSO and the operator's identifying signature for responsibility for each session of operating. Messages may be witten in the log or separate records kept—but record must be retained for one year as required by the FCC. For the convenience of amateur station operators ARRL stocks both logbooks and message blanks, and if one uses the official log he is sure to comply fully with the Government requirements if the precautions and suggestions included in the log are followed.

MESSAGE HANDLING

Amateur operators in the United States and a few other countries enjoy a privilege not available to amateurs in most countries—that of handling third-party message traffic. In the early history of amateur radio in this country, some amateurs who were among the first to take advantage of this privilege formed an extensive relay organization which became known as the American Radio Relay League.

Thus, amateur message-handling has had a long and honorable history and, like most services, has gone through many periods of development anc change. Those amateurs who handled traffic in 1914 would hardly recognize it the way some of us do it today, just as equipment in those days was far different from that in use now. Progress has been made and new methods have been developed in step with advancement in communication techniques of all kinds. Amateurs who handled a lot of traffic found that organized operating schedules were more effective than random relays, and as techniques advanced and messages increased in number, trunk lines were organized, spot frequencies began to be used, and there sprang into existence a number of traffic nets in which many stations operated on

the same frequency to effect wider coverage in less time with fewer relays; but the old methods are still available to the amateur who handles only an occasional message.

Although message handling is as old an art as is amateur radio itself, there are many amateurs who do not know how to handle a message and have never done so. As each amateur grows older and gains experience in the amateur service, there is bound to come a time when he will be called upon to handle a written message, during a communications emergency, in casual contact with one of his many acquaintances on the air, or as a result of a request from a nonamateur friend. Regardless of the occasion, if it comes to you, you will want to rise to it! Considerable embarrassment is likely to be experienced by the amateur who finds he not only does not know the form in which the message should be prepared, but does not know what to do with his station.

Traffic work need not be a complicated or time-consuming activity for the casual or occasional message-handler. Amateurs may participate in traffic work to whatever extent they wish, from an occasional message now and then to becoming a part of organized traffic systems. This chapter explains some principles so the reader may know where to find out more about the subject and may exercise the message-handling privilege to best effect as the spirit and opportunity arise.

Responsibility

Amateurs who originate messages for transmission or who receive messages for relay or delivery should first consider that in doing so they are accepting the responsibility of clearing the message from their station on its way to its destination in the shortest possible time. Fortyeight hours after filing or receipt is the generally-accepted rule among traffic-handling amateurs, but it is obvious that if every amateur who relayed the message allowed it to remain in his station this long it might be a long time reaching its destination. Traffic should be relayed or delivered as quickly as possible.

Message Form

Once this responsibility is realized and accepted, handling the message becomes a matter of following generally-accepted standards of form and transmission. For this purpose, each message is divided into four parts: the preamble, the address, the text and the signature. Some of these parts themselves are subdivided. It is necessary in preparing the message for transmission and in actually transmitting it to know not only what each part is and what it is for, but to know in what order it should be transmitted, and to know the various procedure signals used with it when sent by c.w. If you are going to send a message, you may as well send it right.

Standardization is important! There is a great deal of room for expressing originality and individuality in amateur radio, but there are also times and places where such expression can only cause confusion and inefficiency. Recognizing the need for standardization in message form and message transmitting procedures, ARRL has long since recommended such standards, and most traffic-interested amateurs have followed them. In general, these recommendations, and the various changes they have undergone from



Here is an example af a plain-language message in carrect ARRL farm. The preamble is always sent as shawn: number, statian af arigin, check, place af arigin, time filed, date.

The state of the self-dependent of the same of the order of the control of the self-dependent and the self-depende

year to year, have been at the request of amateurs participating in this activity, and they are completely outlined and explained in *Operating an Amateur Radio Station*, a copy of which is available upon request or by use of the coupon at the end of this chapter.

Clearing a Message

The best way to clear a message is to put it into one of the many organized traffic networks, or to give it to a station who can do so. There are many amateurs who make the handling of traffic their principal operating activity, and many more still who participate in this activity to a greater or lesser extent. The result is a system of traffic nets which spreads to all corners of the United States and covers most U. S. possessions and Canada. Once a message gets into one of these nets, regardless of the net's size or coverage, it is systematically routed toward its destination in the shortest possible time.

Amateurs not experienced in message handling should depend on the experienced message-handler to get a message through, if it is important; but the average amateur can enjoy operating with a message to be handled either through a local traffic net or by free-lancing. The latter may be accomplished by careful listening for an amateur station at desired points, directional CQs, use of the National Calling and Emergency frequencies, or by making and keeping a schedule with another amateur for regular work between specified points. He may well aim at learning and enjoying through doing. The joy and accomplishment in thus developing one's operating skill to top perfection has a reward all its own.

If you decide to "take the bull by the horns" and put the message into a traffic net yourself (and more power to you if you do!), you will need to know something about how traffic nets operate, and the special Q signals and procedure they use to dispatch all traffic with a maximum of efficiency. Reference to net lists in QST (usually in the November and January issues) will give you the frequency and operating time of the net in your section, or of other nets into which your message can go. Listening for a few minutes at the time and frequency indicated should acquaint you with enough fundamentals to enable you to report into the net and indicate your traffic. From that time on you follow the instructions of the net control station, who will tell you when and to whom (and on what frequency, if different from the net frequency) to send your message. Since most nets use the special "QN" signals, it is usually very helpful to have a list of these before you (list available from ARRL Hq., Operating Aid No. 9).

Network Operation

About this time, you may find that you are enjoying this type of operating activity and want to know more about it and increase your proficiency. Many amateurs are happily "addicted" to traffic handling after only one or two brief exposures to it. Much traffic is at present being

Emergency Communication

conducted by c.w., since this mode of communication seems to be popular for record purposes—but this does not mean that high code speed is a necessary prerequisite to working in traffic networks. There are many nets organized specifically for the slow-speed amateur, and most of the so-called "fast" nets are usually glad to slow down to accommodate slower operators, especially those nets at state or section level.

It is a significant operating fact that code speed or word speed alone does not make for efficiency-sometimes the contrary! A highspeed operator who does not know procedure can "foul up" a net much more completely and more quickly than can a slow operator. It is a proven fact that a bunch of high-speed operators who are not "savvy" in net operation cannot accomplish as much during a specified period as an equal number of slow operators who know net procedure. Don't let low code speed deter you from getting into traffic work. Given a little time, your speed will reach the point where you can compete with the best of them. Concentrate first on learning net procedure, for most traffic nowadays is handled on nets.

Much traffic is also handled on phone. This mode is exceptionally well suited to short-range traffic work and requires knowledge of phonetics and procedure peculiar to voice operation. Procedure is of paramount importance on phone, since the public may be listening. The major

problem, of course, is QRM.

Teamwork is the theme of net operation. The net which functions most efficiently is the net in which all participants are thoroughly familiar with the procedure used, and in which operators refrain from transmitting except at the direction of the net control station, and do not occupy time with extraneous comments, even the exchange of pleasantries. There is a time and place for everything. When a net is in session it should concentrate on handling traffic until all traffic is cleared. Before or after the net is the time for rag-chewing and discussion. Some details of net operation are included in Operating an Amateur Radio Station, mentioned earlier, but the whole story cannot be told. There is no substitute for actual participation.

The National Traffic System

To facilitate and speed the movement of message traffic, there is in existence an integrated national system by means of which originated traffic can normally reach its destination area the same day the message is originated. This system uses the local section net as a basis. Each section net sends a representative to a "regional" net (normally covering a call area) and each "regional" net sends a representative to an "area" net (normally covering a time zone). After the area net has cleared all its traffic, its members then go back to their respective regional nets, where they clear traffic to the various section net representatives. By means of connecting schedules between the area nets, traffic can flow both ways so that traffic originated on the West Coast reaches the East Coast with a maximum of dispatch, and vice versa. In general local section nets function at 1900, regional nets at 1945, area nets at 2030 and the same or different regional personnel again at 2130. Some section nets conduct a late session at 2200 to effect traffic delivery the same night. Local standard time is referred to in each case.

The NTS plan somewhat spreads traffic opportunity so that casual traffic may be reported into nets for efficient handling one or two nights per week, early or late; or the ardent traffic man can operate in both early and late groups and in between to roll up impressive totals and speed traffic reliably to its destination. Old-time traffic men who prefer a high degree of organization and teamwork have returned to the traffic game as a result of the new system. Beginners have shown more interest in becoming part of a system nationwide in scope, in which anyone can participate. The National Traffic System has vast and intriguing possibilities as an amateur service. It is open to any amateur who wishes to participate.

The above is but the briefest résumé of what is of necessity a rather complicated arrangement of nets and schedules. Complete details of the System and its operation are available to anyone interested. Just drop a line to ARRL Headquarters.

EMERGENCY COMMUNICATION

One of the most important ways in which the amateur serves the public, thus making his existence a national asset, is by his preparation for and his participation in communications emergencies. Every amateur, regardless of the extent of his normal operating activities, should give some thought to the possibility of his being the only means of communication should his community be cut off from the outside world. It has happened many times, often in the most unlikely places; it has happened without warning, finding some amateurs totally unprepared; it can happen to you. Are you ready?

There are two principal ways in which any



amateur can prepare himself for such an eventuality. One is to provide himself with equipment capable of operating on any type of emergency power (i.e., either a.c. or d.c.), and equipment which can readily be transported to the scene of disaster. Mobile equipment is especially desirable in most emergency situations.

Such equipment, regardless of how elaborate or how modern, is of little use, however, if it is not used properly and at the right times; and so another way for an amateur to prepare himself for emergencies, by no means less important than the first, is to learn to operate efficiently. There are many amateurs who feel that they know how to operate efficiently but who find themselves considerably handicapped at the crucial time by not knowing proper procedure, by being unable, due to years of casual amateur operation, to adapt themselves to snappy, abbreviated transmissions, and by being unfamiliar with message form and procedures. It is dangerous to overrate your ability in this; it is better to assume you have things to learn . . . and it makes you a respected communicator to know them.

In general it can be said that there is more emergency equipment available than there are operators who know properly how to operate during emergency conditions, for such conditions require clipped, terse procedure with complete break-in on c.w. and fast push-to-talk on phone. The casual rag-chewing aspect of amateur radio, however enjoyable and worth-while in its place, must be forgotten at such times in favor of the business at hand. There is only one way to gain experience in this type of operation, and that is by practicing it. During an emergency is no time for practice; it should be done be-

forehand, as often as possible, on a regular basis.

This leads up to the necessity for emergency organization and preparedness. ARRL has long recognized this necessity and has provided for it. The Section Communications Manager (whose address appears on page 6 of every issue of QST) is empowered to appoint certain qualified amateurs in his section for the purpose of coordinating emergency communication organization and preparedness in specified areas or communities. This appointee is known as an Emergency Coordinator for the city or town. One is specified for each community. For coordination and promotion at section level a Section Emergency Coordinator arranges for and recommends the appointments of various Emergency Coordinators at activity points throughout the section. Emergency Coordinators organize amateurs in their communities according to local needs for emergency communication facilities.

The community amateurs taking part in the local organization are members of the Amateur Radio Emergency Corps (AREC). All amateurs are invited to register in the AREC, whether they are able to play an active part in their local organization or only a supporting role. Application blanks are available from your EC, SEC, SCM or direct from ARRL Headquarters. In the event that inquiry reveals no Emergency Coordinator appointed for your community, your SCM would welcome a recommendation either from yourself or from a radio club of which you are a member. By holding an amateur operator license, you have the responsibility both to your community and to amateur radio to uphold the traditions of the service.

Among the League's publications is a booklet

Before Emergency

PREPARE yourself by providing a transmitter-receiver setup together with an emergency power source upon which you can depend.

TEST both the dependability of your emergency equipment and your own operating ability in the annual ARRL Simulated Emergency Test and the several annual on the air contests, especially Field Day.

REGISTER your facilities and your availability with your local ARRL Emergency Coordinator. If your community has no EC, contact your local civic and relief agencies and explain to them what the Amateur Service offers the community in time of disaster.

In Emergency

LISTEN before you transmit. Never violate this principle.

latest developments.

REPORT at once to your Emergency Coordinator so that he will have up-to-the-minute data on the facilities available to him. Work with local civic and relief agencies as the EC suggests, offer these agencies your services directly in the absence of an EC.

RESTRICT all on-the-air work in accordance with FCC regulations, Sec. 12.156, whenever FCC "declares" a state of communications emergency.

QRRR is the official ARRL "land SOS," a distress call for emergency only. It is for use only by a station seeking assistance.

RESPECT the fact that the success of the amateur effort in emergency depends largely on circuit discipline. The established Net Control Station should be the supreme authority for priority and traffic routing.

COOPERATE with those we serve. Be ready to help, but stay off the air unless there is a specific job to be done that you can handle more efficiently than any other station.

COPY all bulletins from W1AW. During time of emergency special bulletins will keep you posted on the

After Emergency

REPORT to ARRL Headquarters as soon as possible and as fully as possible so that the Amateur Service can receive full credit. Amateur Radio has won glowing public tribute in many major disasters since 1919. Maintain this record.

ARRL Operating Organization

entitled *Emergency Communications*. This booklet, while small in size, contains a wealth of information on AREC organization and functions and is invaluable to any amateur participating in emergency or civil defense work. It is free to AREC members and should be in every amateur's shack. Drop a line to the ARRL Communications Department if you want a copy, or use the coupon at the end of this chapter.

The Radio Amateur Civil Emergency Service

In order to be prepared for any eventuality, FCC and the Office of Civil and Defense Mobilization (OCDM), in collaboration with ARRL, have promulgated the Radio Amateur Civil Emergency Service. RACES is a temporary amateur service, intended primarily to serve civil defense and to continue operation during any extreme national emergency, such as war. It shares certain segments of frequencies with the regular Amateur Service on a nonexclusive basis. Its regulations have been made a sub-part of the familiar amateur regulations; that is, the original regulations have become sub-part A, the RACES regulations being added as sub-part B. Copies of both parts are included in the latest edition of the ARRL License Manual.

If every amateur participated, we would still be far short of the total operating personnel required properly to implement RACES. As the service which bears the responsibility for the successful implementation of this important function, we face not only the task of installing

(and in some cases building) the necessary equipment, but also of the training of thousands of additional people. This can and should be a function of the local unit of the Amateur Radio Emergency Corps under its EC and his assistants, working in close collaboration with the local civil defense organization.

The first step in organizing RACES locally is the appointment of a Radio Officer by the local civil defense director, possibly on the recommendation of his communications officer. A complete and detailed communications plan must be approved successively by local, state and OCDM regional directors, by the OCDM National office, and by FCC. Once this has been accomplished, applications for station authorizations under this plan can be submitted direct to FCC. QST carries further information from time to time, and ARRL will keep its field officials fully informed by bulletins as the situation requires. A complete bibliography of QST articles dealing with the subject of civil defense and RACES is available upon request from the ARRL Communications Department.

In the event of war, civil defense will place great reliance on RACES for radio communications. RACES is an Amateur Service. Its implementation is logically a function of the Amateur Radio Emergency Corps—an additional function in peacetime, but probably an exclusive function in wartime. Therefore, your best opportunity to be of service will be to register with your local EC, and to participate actively in the local AREC/RACES program.

ARRL OPERATING ORGANIZATION

Amateur operation must have point and constructive purpose to win public respect. Each individual amateur is the ambassador of the entire fraternity in his public relations and attitude toward his hobby. ARRL field organization adds point and purpose to amateur operating.

The Communications Department of the League is concerned with the practical operation of stations in all branches of amateur activity. Appointments or awards are available for ragchewer, traffic enthusiast, phone operator, DX man and experimenter.

There are seventy-three ARRL Sections in the League's field organization, which embraces the United States, Canada and certain other territory. Operating affairs in each Section are supervised by a Section Communications Manager elected by members in that section for a twoyear term of office. Organization appointments are made by the section managers, elected as provided in the Rules and Regulations of the Communications Department, which accompany the League's By-Laws and Articles of Association. Section Communications Managers' addresses for all sections are given in full in each issue of QST. SCMs welcome monthly activity reports from all amateur stations in their jurisdiction.

Whether your activity embraces phone or telegraphy, or both, there is a place for you in the League organization.

LEADERSHIP POSTS

To advance each type of station work and group interest in amateur radio, and to develop practical communications plans with the greatest success, appointments of leaders and organizers in particular single-interest fields are made by SCMs. Each leadership post is important. Each provides activities and assistance for appointee groups and individual members along the lines of natural interest. Some posts further the general ability of amateurs to communicate efficiently at all times, by pointing activity toward networks and round tables, others are aimed specifically at establishment of provisions for organizing the amateur service as a standby communications group to serve the public in disaster, civil defense need or emergency of any sort. The SCM appoints the following in accordance with section needs and individual qualifications:

PAM Phone Activities Manager. Organizes activities for OPSs and voice operators in his section. Promotes phone nets and recruits OPSs.

RM Route Manager. Organizes and coordinates c.w.

traffic activities. Supervises and promotes nets and recruits ORSs.

SEC Section Emergency Coordinator. Promotes and administers section emergency radio organization.

EC Emergency Coordinator. Organizes amateurs of a community or other local area for emergency radio service; maintains liaison with officials and agencies served, also with other local communication facilities. Sponsors tests, recruits for AREC and encourages alignment with RACES.

STATION APPOINTMENTS

ARRL's field organization has a place for every active amateur who has a station. The Communications Department organization exists to increase individual enjoyment and station effectiveness in amateur radio work, and we extend a cordial invitation to every amateur to participate fully in the activities, to report results monthly, and to apply to the SCM for one of the following station appointments. ARRL membership and the General Class license or VE equivalent is prerequisite to appointments, except OES is available to Novice/Technician grades,



OPS Official Phone Station. Sets high voice operating standards and procedures, furthers phone nets and traffic.

ORS Official Relay Station. Traffic service, operates c.w. nets; noted for 15 w.p.m. and procedure ability.

OBS Official Bulletin Station, Transmits ARRL and FCC bulletin information to amateurs.

OES Official Experimental Station. Collects and reports v.h.f.-u.h.f.-s.h.f. propagation data, may engage in facsimile, TT, TV, work on 50 Mc. and/or above. Takes part as feasible in v.h.f. traffic work, reports same, supports v.h.f. nets, observes procedure standards.

OO Official Observer. Sends cooperative notices to amateurs to assist in frequency observance, insures high-quality signals, and prevents FCC trouble.

Embiem Colors

Members wear the ARRL emblem with blackenamel background. A red background for an emblem will indicate that the wearer is SCM, SECs, ECs, RMs, and PAMs may wear the emblem with green background. Observers and all station appointees are entitled to wear blue emblems.

SECTION NETS

Amateurs gain experience and pleasure and add much accomplishment to the credit of all of

amateur radio, when organized into effective nets interconnecting cities and towns.

The successful operation of a net depends a lot on the Net Control Station. This station should be chosen carefully and be one that will not hesitate to enforce each and every net rule and set the example in his own operation.

A progressive net grows, obtaining new members both directly and through other net members. Bulletins may be issued at intervals to keep in direct contact with the members regarding general net activity, to keep tab on net procedure, make suggestions for improvement, keep track of active members and weed out inactive ones.

A National Traffic System is sponsored by ARRL to facilitate the over-all expeditious relay and delivery of message traffic. The system recognizes the need for handling traffic beyond the section-level networks that have the popular support of both phone and c.w. groups (OPS and ORS) throughout the League's field organization. Area and regional provisions for NTS are furthered by Headquarters correspondence. The ARRL Net Directory, revised in December each year, includes the frequencies and times of operation of the hundreds of different nets operating on amateur band frequencies.

Radio Club Affiliation

ARRL is pleased to grant affiliation to any amateur society having (1) at least 51% of the voting club membership as full members of the League, and (2) at least 51% of members government-licensed radio amateurs. In high school radio clubs bearing the school name, the first above requirement is modified to require one full member of ARRL in the club. Where a society has common aims and wishes to add strength to that of other club groups and strengthen amateur radio by affiliation with the national amateur organization, a request addressed to the Communications Manager will bring the necessary forms and information to initiate the application for affiliation. Such clubs receive fieldorganization bulletins and special information at intervals for posting on club bulletin boards or for relay to their memberships. A travel plan providing communications, technical and secretarial contact from the Headquarters is worked out seasonally to give maximum benefits to as many as possible of the twelve hundred active affiliated radio clubs. Papers on club work, suggestions for organizing, for constitutions, for radio courses of study, etc., are available on request.

Club Training Aids

One section of the ARRL Communications Department handles the Training Aids Program. This program is a service to ARRL affiliated clubs. Material is aimed at education, training and entertainment of club members. Interesting quiz material is available.

Training Aids include such items as motionpicture films, film strips, slides, audio tapes and lecture outlines. Bookings are limited to ARRL-

Operating Activities and Awards

affiliated clubs, since the visual aids listings are not sufficiently extensive to permit such services to other groups.

All Training Aids materials are loaned free (except for shipping charges) to ARRL affiliated clubs. Numerous groups use this ARRL service to good advantage. If your club is affiliated but has not yet taken advantage of this service, you are missing a good chance to add the available features to your meeting programs and general club activities. Watch club bulletins and QST or write the ARRL Communications Department for TA-21 and TA-32.

WIAW

The Maxim Memorial Station, W1AW, is dedicated to fraternity and service. Operated by the League headquarters, W1AW is located about four miles south of the Headquarters offices on a seven-acre site. The station is on the air daily, except holidays, and available time is divided between different bands and modes. Telegraph and



phone transmitters are provided for all bands from 1.8 to 144 Mc. The normal frequencies in each band for c.w. and voice transmissions are

as follows: 1820, 3555, 3945, 7080, 7255, 14,100, 14,280, 21,075, 21,330, 28,080, 29,000, 50,900 and 145,800 kc. Operating-visiting hours and the station schedule are listed every other month in *QST*.

Operation is roughly proportional to amateur interest in different bands and modes, with one kw. except on 160 and v.h.f. bands. W1AW's daily bulletins and code practice aim to give operational help to the largest number.

All amateurs are invited to visit W1AW, as well as to work the station from their own shacks. The station was established to be a living memorial to Hiram Percy Maxim, to carry on the work and traditions of amateur radio.

OPERATING ACTIVITIES

Within the ARRL field organization there are several special activities. During six months of the year, the first week end is an occasion for ARRL officials, officers, and directors to get together over the air. This activity is known to the gang as the LO (League officials) party. For all appointees, quarterly CD parties are scheduled additionally to develop operating ability and a spirit of fraternalism.

In addition to those for appointees and officials, ARRL sponsors various other activities open to all amateurs. The DX-minded amateur may participate in the Annual ARRL International DX competition during February and March. This popular contest may bring you the thrill of work-

ing new countries and building up your DXCC totals; certificate awards are offered to top scorers in each country and ARRL section (see page 6 of any QST) and to club leaders. Then there is the ever-popular Sweepstakes in November. Of domestic scope, the SS affords the opportunity to work new states for that WAS award. A Novice activity is planned annually. The interests of v.h.f. enthusiasts are also provided for in contests held in January, June and September of each year. Where enough logs (three) are received to constitute minimum "competition" a certificate in spot activities, such as the "SS" and v.h.f. party, is awarded the leading newcomer for his work considered only in competition with other newcomers.

As in all our operating, the idea of having a good time is combined in the Annual Field Day with the more serious thought of preparing ourselves to render public service in times of emergency. A premium is placed on the use of equipment without connection to commercial power sources. Clubs and individual groups always enjoy themselves in the "FD," and learn much about the requirements for operating under knockabout conditions afield.

ARRL contest activities are diversified to appeal to all operating interests, and will be found announced in detail in issues of QST preceding the different events.

AWARDS

The League-sponsored operating activities heretofore mentioned have useful objectives and provide much enjoyment for members of the fraternity. Achievement in amateur radio is recognized by various certificates offered through the League and detailed below.

WAS Award

WAS means "Worked All States." This award is available regardless of affiliation or nonaffiliation with any organization. Here are the simple rules to follow in going after your WAS:



 Two-way communication must be established on the amateur bands with each of the states; any and all amateur bands may be used. A card from the District of Columbia may be submitted in lieu of one from Maryland.

2) Contacts with all states must be made from the same location. Within a given community one location may be defined as from places no two of which are more than 25 miles apart.

3) Contacts may be made over any period of years, provided only that all contacts are from the same location, and except that only contacts with Alaska dated

January 3, 1959, or later count, and only contacts with Hawaii dated August 21, 1959, or later count.

 QSL cards, or other written communications from stations worked confirming the necessary two-way contacts, must be submitted by the applicant to ARRL headquarters.

5) Sufficient postage must be sent with the confirmations to finance their return. No correspondence will be returned unless sufficient postage is furnished.

6) The WAS award is available to all amateurs. It is required that the confirmations submitted be placed alphabetically in order by states.

7) Address all applications and confirmations to the Communications Department, ARRL, 38 La Salle Road, West Hartford, Conn.

DX Century Club Award

Here are the rules under which the DX Century Club Award will be issued to amateurs who have worked and confirmed contact with 100 countries in the postwar period.

1) The DX Century Club Award Certificate for confirmed contracts with 100 or more countries is available to all amateurs everywhere in the world.

2) Confirmations must be submitted direct to ARRL headquarters for all countries claimed. Claims for a total of 100 countries must be included with first application. Confirmation from foreign contest logs may be requested in the case of the ARRL International DX Competition only, subject to the following conditions:

a) Sufficient confirmations of other types must be submitted so that these, plus the DX Contest confirmations, will total 100. In every case, Contest confirmations must not be requested for any countries from which the applicant has regular confirmations. That is, contest confirmations will be granted only in the case of countries from which applicants have no regular confirmations.

b) Look up the contest results as published in QST to see if your man is listed in the foreign scores. If he isn't, he did not send in a log and no confirmation is possible.

c) Give year of contest, date and time of QSO.

d) In future DX Contests, do not request confirmations until after the final results have been published, usually in one of the early fall issues. Requests before this time must be ignored.

3) The ARRL Countries List, printed periodically in QST, will be used in determining what constitutes a "country." This chapter contains the Postwar Countries List.

4) Confirmations must be accompanied by a list of claimed countries and stations to aid in checking and for future reference.

5) Confirmations from additional countries may be submitted for credit each time ten additional confirmations are available. Endorsements for affixing to certificates and showing the new confirmed total (110, 120, 130, etc.) will be awarded as additional credits are granted. ARRL DX Competition logs from foreign stations may be utilized for these endorsements, subject to conditions stated under (2).

6) All contacts must be made with amateur stations working in the authorized amateur bands or with other stations licensed to work amateurs.

7) In cases of countries where amateurs are licensed in the normal manner, credit may be claimed only for stations using regular government-assigned call letters. No credit may be claimed for contacts with stations in any countries in which amateurs have been temporarily closed down by special government edict where amateur licenses were formerly issued in the normal manner.

8) All stations contacted must be "land stations" . . . contacts with ships, anchored or otherwise, and aircraft, cannot be counted.

9) All stations must be contacted from the same call area, where such areas exist, or from the same country in cases where there are no call areas. One exception is allowed to this rule: where a station is moved from one call area to another, or from one country to another, all contacts must be made from within a radius of 150 miles of the initial location.

10) Contacts may be made over any period of years from November 15, 1945, provided only that all contacts

be made under the provisions of Rule 9, and by the same station licensee; contacts may have been made under different call letters in the same area (or country), if the licensee for all was the same.

11) Any altered or forged confirmations submitted for CC credit will result in disqualification of the applicant. The eligibility of any DXCC applicant who was ever barred from DXCC to reapply, and the conditions for such application, shall be determined by the Awards Committee. Any holder of the Century Club Award submitting forged or altered confirmations must forfeit his right to be considered for further endorsements.

12) Operating ethics: Fair play and good sportsmanship in operating are required of all amateurs working toward the DX Century Club Award. In the event of specific objections relative to continued poor operating ethics an individual may be disqualified from the DXCC by action of the ARRL Awards Committee.

13) Sufficient postage for the return of confirmations must be forwarded with the application. In order to insure the safe return of large batches of confirmations, it is suggested that enough postage be sent to make possible their return by first-class mail, registered.

14) Decisions of the ARRL Awards Committee regarding interpretation of the rules as here printed or later

amended shall be final.

15) Address all applications and confirmations to the Communications Department, ARRL, 38 La Salle Road, West Hartford 7, Conn.

WAC Award

The WAC award, Worked All Continents, is issued by the International Amateur Radio Union (IARU) upon proof of contact with each of the six continents. Amateurs in the U.S.A., Possessions and Canada should apply for the award through ARRL, headquarters society of the IARU. Those elsewhere must submit direct to their own IARU member-society. Residents of countries not represented in the Union may apply directly to ARRL for the award. Two basic types of WAC certificates are issued. One contains no endorsements and is awarded for c.w, or a combination of c.w. and phone contacts; the other is awarded when all work is done on phone. There is a special endorsement to the phone WAC when all of the confirmations submitted clearly indicate that the work was done on two-way s.s.b. The only special band endorsements are for 3.5 and 50 Mc.

Code Proficiency Award

Many hams can follow the general idea of a contact "by ear" but when pressed to "write it down" they "muff" the copy. The Code Proficiency Award permits each amateur to prove himself as a proficient operator, and sets up a



system of awards for step-by-step gains in copying proficiency. It enables every amateur to check his code proficiency, to better that proficiency, and to receive a certification of his re-

ceiving speed.

This program is a whale of a lot of fun. The League will give a certificate to any licensed radio amateur who demonstrates that he can copy perfectly, for at least one minute, plainlanguage Continental code at 10, 15, 20, 25, 30 or 35 words per minute, as transmitted during special monthly transmissions from W1AW and W6OWP.

As part of the ARRL Code Proficiency program W1AW transmits plain-language practice material each evening at speeds from 5 to 35 w.p.m. All amateurs are invited to use these transmissions to increase their code-copying ability. Non-amateurs are invited to utilize the lower speeds, 5, 7½ and 10 w.p.m., which are transmitted for the benefit of persons studying the code in preparation for the amateur license examination. Refer to any issue of QST for details of the practice schedule.

Rag Chewers Club

The Rag Chewers Club is designed to encourage friendly contacts and discourage the "hello-good-by" type of QSO. It furthers fraternalism through amateur radio. Membership certificates are awarded.

How To Get in: (1) Chew the rag with a member of the club for at least a solid half hour. This does not mean a half hour spent in trying to get a message over through bad QRM or QRN, but a solid half hour of conversation or message handling. (2) Report the conversation by card to The Rag Chewers Club, ARRL, Communications Department, West Hartford, Conn., and ask the member station you talk with to do the same. When both reports are received you will be sent a membership certificate entitling you to all the privileges of a Rag Chewer.

How To Stay in: (1) Be a conversationalist on the air instead of one of those tongue-tied infants who don't know any words except "cuagn" or "cul," or "QRU" or "nil." Talk to the fellows you work with and get to know them. (2) Operate your station in accordance with the radio laws and ARRL practice. (3) Observe rules of courtesy on the air. (4) Sign "RCC" after each call so that others

may know you can talk as well as call.

A-1 Operator Club

The A-1 Operator Club should include in its ranks every good operator. To become a member, one must be nominated by at least two operators who already belong. General keying or voice technique, procedure, copying ability,

judgment and courtesy all count in rating candidates under the club rules detailed at length in Operating an Amateur Radio Station. Aim to make yourself a fine operator, and one of these days you may be pleasantly surprised by an invitation to belong to the A-1 Operator Club, which carries a worth-while certificate in its own

Brass Pounders League

Every individual reporting more than a specified minimum in official monthly traffic totals is given an honor place in the QST listing known as the Brass Pounders League and a certificate to recognize his performance is furnished by the SCM. In addition, a BPL Traffic Award (medallion) is given to individual amateurs working at their own stations after the third time they "make BPL" provided it is duly reported to the SCM and recorded in QST.

The value to amateurs in operator training, and the utility of amateur message handling to the members of the fraternity itself as well as to the general public, make message-handling work of prime importance to the fraternity. Fun, enjoyment, and the feeling of having done something really worth while for one's fellows is accentuated by pride in message files, records, and letters from those served.

Old Timers Club

The Old Timers Club is open to anyone who holds an amateur call at the present time, and who held an amateur license (operator or station) 20-or-more years ago. Lapses in activity during the intervening years are permitted.

If you can qualify as an "Old Timer," send an outline of your ham career. Indicate the date of your first amateur license and your present call. If eligible for the OTC, you will be added to the roster and will receive a membership certificate.

INVITATION

Amateur radio is capable of giving enjoyment, self-training, social and organization benefits in proportion to what the individual amateur puts into his hobby. All amateurs are invited to become ARRL members, to work toward awards, and to accept the challenge and invitation of fered in field-organization appointments. Drop a line to ARRL Headquarters for the booklet Operating an Amateur Radio Station, which has

CONELRAD COMPLIANCE

The FCC rules for the Amateur Service concerned with requirements in the event of enemy attack are contained in the ARRL License Manual as part of the amateur regulations, Sections 12.190 through 12.196. These are the rules for control of electromagnetic radiation, conelrad, to minimize radio navigational aids to an enemy. Read and follow these rules. They concern you.

Amateurs are required to shut down when a Conelrad Radio Alert is indicated. FCC requires monitoring, by some means, of a broadcast station while you operate. By use of proper equipment, each amateur can make his conelrad compliance routine and almost automatic. You will find descriptions of such devices, most of them quite simple, in this Handbook and in QST.

detailed information on the field-organization appointments and awards. Accept today the invi-

tation to take full part in all League activities and organization work.

OPERATING ABBREVIATIONS AND PREFIXES

Q SIGNALS

Given below are a number of Q signals whose meanings most often need to be expressed with brevity and clearness in amateur work. (Q abbreviations take the form of questions only when each is sent followed by a question mark.)

- QRG Will you tell me my exact frequency (or that of.....)? Your exact frequency (or that of.....)is.....kc.
- QRH Does my frequency vary? Your frequency varies.
- QRI How is the tone of my transmission? The tone of your transmission is.....(1. Good; 2. Variable; 3. Bad).
- QRK What is the readability of my signals (or those of.....)? The readability of your signals (or those of.....) is.....(1. Unreadable; 2. Readable now and then; 3. Readable but with difficulty; 4. Readable; 5. Perfectly readable).
- QRL Are you busy? I am busy (or I am busy with). Please do not interfere.
- QRM Are you being interfered with? I am interfered with.
- QRN Are you troubled by static? I am being troubled by static.
- QRO Must I increase power? Increase power.
- QRP Must I decrease power? Decrease power.
- QRQ Shall I send faster? Send faster (.....words
- QRS Shall I send more slowly? Send more slowly
- QRT Shall I stop sending? Stop sending.
- QRU Have you anything for me? I have nothing for you.
- QRV Are you ready? I am ready.
- QRW Shall I tell.....that you are calling him onkc.? Please inform.....that I am calling on.....kc.
- QRX When will you call me again? I will call you again at.....hours (on.....kc.).
- QRZ Who is calling me? You are being called by.....
- QSA What is the strength of my signals (or those of)? The strength of your signals (or those of.....) is......(1. Scarcely perceptible; 2. Weak; 3. Fairly good; 4. Good; 5. Very good).
- QSB Are my signals fading? Your signals are fading. QSD Is my keying defective? Your keying is defec-
- tive.

 QSG Shall I send....messages at a time? Send.....
 messages at a time.
- QSL Can you acknowledge receipt? I am acknowledging receipt,
- QSM Shall I repeat the last message which I sent you, or some previous message? Repeat the last message which you sent me [or message(s) number(s)....].
- QSO Can you communicate with....direct or by relay? I can communicate with.....direct (or by relay through.....).
- QSP Will you relay to....? I will relay to....
- QSV Shall I send a series of Vs on this frequency (orkc.)? Send a series of Vs on this frequency (or....kc.).
- QSW Will you send on this frequency (or on...kc.)?

- I am going to send on this frequency (or onkc.).
- QSX Will you listen to.....on....kc.? I am listening to.....on....kc.
- QSY Shall I change to transmission on another frequency? Change to transmission on another frequency (or on...kc.).
- QSZ Shall I send each word or group more than once? Send each word or group twice (or...times).
- QTA Shall I cancel message number....as if it had not been sent? Cancel message number..... as if it had not been sent.
- QTB Do you agree with my counting of words? I do not agree with your counting of words; I will repeat the first letter or digit of each word or group.
- QTC How many messages have you to send? I havemessages for you (or for....).
- QTH What is your location? My location is.....
- QTR What is the exact time? The time is.....

Special abbreviations adopted by ARRL:

- QST General call preceding a message addressed to all amateurs and ARRL members. This is in effect "CQ ARRL."
- QRRR Official ARRL "land SOS." A distress call for emergency use only by a station in an emergency situation.

The R-S-T System

READABILITY

- 1 Unreadable.
- 2 Barely readable, occasional words distinguishable.
- 3 Readable with considerable difficulty.
- 4 Readable with practically no difficulty.
- 5 Perfectly readable.

SIGNAL STRENGTH

- 1 Faint signals, barely perceptible.
- 2 Very weak signals.
- 3 Weak signals.
- 4 Fair signals.
- 5 Fairly good signals.
- 6 Good signals.
- 7 Moderately strong signals.
- 8 Strong signals.
- 9 Extremely strong signals.

TONE

- 1 Extremely rough hissing note.
- 2 Very rough a.c. note, no trace of musicality.
- 3 Rough low-pitched a.c. note, slightly musical,
- 4 Rather rough a.c. note, moderately musical.
- 5 Musically-modulated note.
- 6 Modulated note, slight trace of whistle.
- 7 Near d.c. note, smooth ripple.
- 8 Good d.c. note, just a trace of ripple.
- 9 Purest d.c. note.

If the signal has the characteristic steadiness of crystal control, add the letter X to the RST report. If there is a chirp, the letter C may be added to so indicate. Similarly for a click, add K. The above reporting system is used on both c.w. and voice, leaving out the "tone" report on voice.

AC3Sikkim	KC6Eastern Caroline Islands	VKLord Howe Island
AC4Tibet	KC6 Western Caroline Islands	VKWillis Islands
	KG1(See OX)	VK9Christmas Island
APEast Pakistan	KG4 Guantanamo Bay	VK9Cocos Islands
APWest Pakistan	KG6 Marcus Island	VK9Nauru Island
BV, (C3)Formosa	KG6 Mariana Islands	VK9Norfolk Island
BY, (C)China	KG61—(See KA0)	VK9Papua Territory
C9 Manchuria	KH6Hawaiian Islands	VK9 Territory of New Guinea
CEChile	KH6Kure Island	VK0 (See CE9)
CE9, KC4, LU-Z, VKØ,	KJ6Johnston Island	VKØHeard Island
ACS	KL7	VKØ Heard Island VKØ Macquarie Island
CE9(See VP8)	KM6Midway Islands	VO(See VE)
CE9 (See VP8) CE9A Easter Island CE9Z. Juan Fernandez Archipelago CM. CO Cuba	KP4Puerto Kico	VP1 British Honduras
CEOZ. Juan Fernandez Archipelago	KP6 . Palmyra Group, Jarvis Island KR6	VP2Anguilla
CM, COCuba	KK6 Kyukyu Islands	VP2 Antigua, Barbuda
CD Delici-	KS4B Serrana Bank &	VP2British Virgin Islands
CN2, 8, 9	Roncador Cay KS4Swan Islands	VP2
	KS4Swan Islands KS6American Samoa	VP2Granada & Dependencies VP2Montserrat VP2St. Kitts, Nevis
CR5 Portuguese clinica CR5 Principe, Sao Thome CR6 Angola CR7 Mozambique CR8 Damao, Diu CR8 Goa	WVA Viegin Islanda	VP2 St Kitte Navie
CD6 Angola	KV4 Virgin Islands KW6 Wake Island KX6 Marshall Islands	VP2St. Lucia
CR7 Mozambique	KX6 Marshall Islands	VP2 St. Vincent & Dependencies
CR8 Damao Diu	KZ5	VP2St. Vincent & Dependencies VP3British Guiana
CR8 Goa	LAJan Mayen	VP4 Trinidad & Tohago
CR9 Macao	LANorway	VP5Cayman Islands
CR9	LASvalbard	VP5 Jamaica
("I'I Portugal	LUArgentina	VP5Turks & Caicos Islands
CT2Azores	LU-Z(See CE9, VP8)	VP6 Barbados
CT2	LXLuxembourg	VP4 Trinidad & Tobago VP5 Cayman Islands VP5 Jamaica VP5 Jamaica VP5 Turks & Caicos Islands VP6 Barbados VP7 Bahama Islands VP0 (See CFO)
[X	LZBulgaria	VP8(See CE9)
DJ, DL, DMGermany	LZ Bulgaria M1 San Marino	VP8Falkland Islands
DJ, DL, DMGermany DUPhilippine Islands	MP4Bahrein	VP8
EASpain EA6Balearic Islands	MP4	VP8, LU-Z. South Orkney Islands
EA6Balearic Islands	MP4Trucial Oman	VP8, LU-Z. South Sandwich Islands
EA8Canary Islands	OAPeru	VP8, LU-Z, CE9 South Shetland Islands
EA9Ifni	OD5Lebanon	South Shetland Islands
EA9Rio de Oro	OEAustria	VP9 Bermuda Islands
EA9Spanish Morocco	OHFinland	VQ1Zanzibar
EAUSpanish Guinea	OHØAland Islands	VO2Northern Rhodesia VO3Tanganyika Territory
EAØ Spanish Guinea EI Republic of Ireland EL Liberia EP, EQ Iran	OKCzechoslovakia	VQ4Kenya
ED EO I	ON4Belgium OX, KG1Greenland	VOT
Er, EQ—iran	OV Factors	VO5
ET2 Eritrea	OYFaeroes OZDenmark	VQ8Chagos Islands
ET3 Ethiopia F France	PAG PI1 Netherlands	VQ8
FAAlgeria	PAØ, PI1Netherlands PJNetherlands West Indies	VQ8Rodriguez Island
FB8 . Amsterdam & St. Paul Islands	PJ2M— Sint Maarten PK Indonesia PX Andorra	VQ9Seychelles
FB8Comoro Islands	PKIndonesia	VR1 British Phoenix Islands
FD9 Varguelan Islanda	PXAndorra	VR1Gilbert & Ellice Islands
FB8Tromelin Island FC (unofficial)Corsica FG7Guadeloupe FK8New Caledonia	PYBrazil PYØFernando de Noronha	& Ocean Island
FC (unofficial) Corsica	PYØFernando de Noronha	VR2Fiji Islands
FG7	PYØTrindade & Martim Vaz Islands	VR2Fiji Islands VR3 .Fanning & Christmas Islands
FK8 New Caledonia	Martim Vaz Islands	VR4Solomon Islands
FL8French Somaliland	PZINetherlands Guiana	VR5Tonga Islands VR6Pitcairn Island
FM7Martinique	SL, SMSweden	VR6 Pitcairn Island
FO8Clipperton Island	SPPoland ST2Sudan	VSISingapore
FO8 French Oceania	ST2Sudan	VS4
FP8 .St. Pierre & Miquelon Islands	SUEgypt	VS5 Bruner
FK7 Kennion Island	SV Crete SV Dodecanese SV Greece	VS6
FS7 Saint Martin FU8, YJ1 New Hebrides FW8 Wallis & Futuna Islands	SVDodecanese	VS0 Kamaran Islanda
FWO Walls & France Islands	TA Turkey	VS9 Maldive Islands
FW8 Wallis & Futuna Islanus	TF	VS9Maldive Islands VS9Sultanate of Oman VU .Andaman and Nicobar Islands
FY7French Guiana & Inini GEngland GCChannel Islands	TGGuatemala	VU . Andaman and Nicobar Islands
GC Channel Islands	TICosta Rica	VULaccadive Islands
GC Channel Islands GD Isle of Man GI Northern Ireland	T19 Cocos Island	VULaccadive Islands
GINorthern Ireland	TJ Cameroons Republic	W(See K)
GM Scotland	TJ Cameroons Republic TL Central African Republic	\(\text{V} \) \(\text{Csec K} \) \(\text{XE} \) \(\text{XF} \) \(\text{Mexico} \) \(\text{XE4} \) \(\text{Revilla Gigedo} \) \(\text{XT} \) \(\text{Voltaci Rep.} \) \(\text{XW8} \) \(\text{Laos} \) \(\text{XZ2} \) \(\text{Burma} \) \(\text{VA Figurists} \)
GW Wales HA Hungary HB Switzerland	TN Congo Republic TR Gabon Republic TS Tunisia	AL4 Revilla Gigedo
HAHungary	TK	Yuvo Ten
HBSwitzerland	TSTunisia	XW8Laos
HUEcuador	TTChad Republic	VA Afahaniata
HC8Galapagos Islands HELiechtenstein	TV Dehaman Bandhia	
HELiechtenstein	TU	VI (See FUS)
	IIA1 6 IIN1 Furanean Pussian	YI Iraq YJ (See FU8) YK Syria
HI Dominican Republic HKØ Bajo Nuevo HKØ Malpelo Island HKØ San Andres and Providencia	TZ Mali Republic UA1, 6, UN1 European Russian Socialist Federated Soviet	YN, YNØNicaragua
HKG Malnelo Island	Republic	YORumania
HKØ San Andres and Providencia	UA1 Franz Josef Land	YSSalvador
HLKorea	UA2	YUYugoslavia
HPPanama	UA9. Ø Asiatic Russian S.F.S.R.	YVVenezuela
HP Panama HR Honduras	UB5Ukraine	YVØAves Island
HS Thailand HV Vatican HZ Saudi Arabia	UB5	ZAAlbania
HVVatican	UD6 Azerbaijan UF6 Georgia UG6 Armenia UH8 Turkoman UH0 Turkoman	ZB1Malta
HZ Saudi Arabia	UF6Georgia	ZB2Gibraltar
II. ITIItaly	UG6Armenia	7C5 Delaish Neath Desert
IS1Sardinia	UnoTurkoman	7C4 Drittish North Borneo
JA, KAJapan	U18Uzbek	7Dt Signer I come
JilMongolia	Ujo ladznik	7D3 Combin
17a Notherland New Cultura	TIM9 Kinghia	ZC4
JAPAN Japan JT1 Mongolia JY Jordan JZØ Netherlands New Guinea K, W United States of America	U18 Uzbek UJ8 Tadzhik UL7 Kazakh UM8 Kirghiz UO5 Moldavia UW8 Lithania	
KAØ, KG61Bonin &	UP2 Lithuania	ZD8Ascension Island
Volcano Islands	UO2Latvia	ZD8Ascension Island ZD9Tristan da Cunha &
KB6 Baker, Howland & American	UP2 Lithuania UQ2 Latvia UR2 Estonia	Gough Islands
Phoenix Islands	VE, VOCanada	ZESouthern Rhodesia
KC4(See CE9)	VKAustralia	ZK1Cook Islands
KC4(See CE9) KC4Navassa Island	VK	ZK1Cook Islands ZK1Manihiki Islands

INTERNATIONAL PREFIXES

AAA-ALZ	United States of America	044077	(Sarvice obbrowletions)
AMA-AOZ	Spain	QAA QZZ RAA RZZ	(Service abbreviations) Union of Soviet Socialist Republics
APA-ASZ	Pakistan India	$SAA \cdot SMZ$	Sweden
AXA-AXZ	Commonwealth of Australia	SNA-SRZ SSA-SSM	People's Republic of Poland Egypt
ATA-AWZ AXA-AXZ AYA-AZZ	Argentine Republic China	SSN-STZ	Sudan
BAA-BZZ	China	SSA-SSM SSN-STZ SUA-SUZ SVA-SZZ TAA-TCZ	Egypt
CAA-CEZ CFA-CKZ	Chile Canada	SVA-SZZ TAA-TC7	Greece . Turkey
CLA-CMZ	Cuba	TDA-TDZ	Guatemala
CNA-CNZ	Morocco	TEA-TEZ	Costa Rica
COA-COZ CPA-CPZ	Cuba Bolivia	TFA-TFZ TGA-TGZ	Iceland Guatemala
COA-CRZ CSA-CUZ CVA-CXZ CYA-CZZ	Portuguese Overseas Provinces	TITL CITY	France and French Community
CŠA-CUZ	Portugal	TIA-TIZ	Costa Rica
CVA-CXZ	Uruguay Canada	TJA-TJZ TKA TK7	Republic of Cameron
DAA-DIZ	Germany	THA-THZ TIA-TIZ TIA-TIZ TKA-TKZ TKA-TKZ TMA-TMZ TNA-TNZ TNA-TNZ TOA-TOZ TRA-TRZ TSA-TSZ	France, and Community Central African Republic France, French Community
DUA-DZZ	Republic of the Philippines	TMA-TMZ	France, French Community
EAA-EHZ EIA-EJZ	Spain Ireland	TNA-TNZ	Republic of the Congo (Brazzaville) France, French Community Republic of Gabon
EVAČV	Union of Soviet Socialist Republics	TRA-TRZ	Republic of Gabon
ELA-ELZ	Liberia	TSA-TSZ TTA-TTZ	Tunisia
EMA-EOZ EPA-EQZ	Union of Soviet Socialist Republics Iran	TTA-TTZ	Republic of Chad
FRA-FRZ	Union of Soviet Socialist Republics	TUA-TUZ TVA-TVZ	Republic of the Ivory Coast France, French Community
ESA-ESZ	Estonia	TVA-TVZ TYA-TYZ TZA-TZZ	Republic of Dahomey
ETA-ETZ	Ethiopia	TZA-TZZ	Republic of Mali
ESA-ESZ ETA-ETZ EUA-EWZ EXA-EZZ	Bielorussian Soviet Socialist Republic Union of Soviet Socialist Republics	URA-UUZ URA-UTZ	Union of Soviet Socialist Republics Ukrainian Soviet Socialist Republic
FAA-FZZ	France and French Community	UAA-UOZ URA-UTZ UUA-UZZ	Union of Soviet Socialist Republics
GAA-GZZ	Great Britain	VAA-VGZ	Canada Commonwealth of Australia
HAA-HAZ HBA-HBZ	Hungarian People's Republic Switzerland	VHA-VNZ VOA-VOZ	Commonwealth of Australia Canada
HVA-HDZ	Ecuador	VPA-VSZ	British Overseas Territories
HEA-HEZ	Switzerland	377C A 3731777	India
HFA-HFZ HGA-HGZ	People's Republic of Poland Hungarian People's Republic	VIA-VWZ VXA-VYZ VZA-VZZ WAA-WZZ XAA-XIZ XJA-XOZ VAA-VPZ	Canada
HHA-HHZ	Republic of Haiti	WAA-WZZ	Commonwealth of Australia United States of America
HHA-HHZ HIA-HIZ	Dominican Republic Republic of Colombia	XAA XIZ	Mexico
HJA-HKZ HLA-HMZ	Republic of Colombia	XJA-XOZ XPA-XPZ	Canada
HNA-HNZ	Korea Iraq	XOA-XPZ	Denmark Chile
HOA-HPZ	Republic of Panama	XŠA-XSZ	China
HOA-HRZ HSA-HSZ	Republic of Honduras Thailand	XTA-XTZ	France and French Community Republic of the Upper Volta
HTAHTZ	Nicaragua	XUA-XUZ	Cambodia
HUA-HUZ	Republic of El Salvador	XPA-XPZ XQA-XRZ XSA-XSZ XTA-XTZ XTA-XTZ XUA-XUZ XVA-XVZ XWA-XWZ XYA-XZZ YAA-YAZ YBA-YHZ YIA-YIZ YIA-YIZ	Viet-Nam
HVA-HVZ HWA-HYZ	Vatican City State France and French Community	XWA-XWZ	Laos
HZA-HZZ	Saudi Arabia	XYA-XZZ	Portuguese Overseas Provinces Burma
IAA-IZZ	Italy and Mandated Territories	YAA-YAZ	Afghanistan
JAA-JSZ	Japan Mongolian People's Republic	YBA-YHZ	Republic of Indonesia
JTA-JVZ JWA-JXZ	Norway	YIA-YIZ YIA-YIZ	Iraq New Hebri des
JWA-JXZ JYA-JYZ JZA-JZZ	Jordan	YJA-YJZ YKA-YKZ YLA-YLZ	Syria
JZA-JZZ	Netherlands New Guinea United States of America	YLA-YLZ	Latvia
KAA-KZZ LAA-LNZ	Norway Norway	YMA-YMZ	Turkey
LUA-LWZ	Argentine Republic	YNA-YNZ YOA-YRZ	Nicaragua Roumanian People's Republic
LXA-LXZ LYA-LYZ	Luxembourg	YSA-YSZ	Republic of El Salvador
LZA-LZZ	Lithuania People's Republic of Bulgaria	YTA-YUZ	Yugoslavia
MAA-MZZ	People's Republic of Bulgaria Great Britain	YYA-YUZ YYA-YYZ YZA-YZZ ZAA-ZAZ ZBA-ZJZ ZKA-ZMZ ZNA-ZOZ ZPA-ZPZ ZPA-ZPZ	Venezuela Yugoslavia
NAA-NZZ	United States of America	ZAA-ZAZ	Albania
OAA-OCZ ODA-ODZ	Peru Lebanon	ZBA ZIZ	British Overseas Territories
OEA-OEZ	Austria	ZXA-ZMZ ZXA-ZOZ	New Zealand British Overseas Territories
OFA-OJZ	Finland	ZPA-ZPZ	Paraguav
OKA-OMZ	Czechoslovakia		British Overseas Territories
ONA-OTZ OUA-OZZ	Belgium Denmark	ZŘA-ZŨZ ZVA-ZZZ	Union of South Africa Brazil
PAA-PIZ	Netherlands	2AA-2ZZ	Great Britain
PJA-PJZ PKA-POZ	Netherlands Antilles Republic of Indonesia	3AA-3AZ	Monaco
PPA-PYZ	Brazil	3BA-3FZ 3GA-3GZ	Canada Chile
PZA-PZZ	Surinam	3HA-3UZ	China


Abbreviations

3VA-3VZ	Tunisia	5UA-5UZ	Republic of the Niger
3WA-3WZ	Viet-Nam	5VA-5VZ	Togolese Republic
3XA-3XZ	Guinea	6AA-6BZ	Egypt
3YA-3YZ	Norway	6CA-6CZ	Syria
3ZA-3ZZ	People's Republic of Poland	6DA-6JZ	Mexico
4AA-4CZ	Mexico	6KA-6NZ	Korea
4DA-4IZ	Republic of the Philippines	60A-60Z	Somalia
4JA-4LZ	Union of Soviet Socialist Republics	6PA-6SZ	Pakistan
4MA-4MZ	Venezuela	6TA-6UZ	Sudan
4NA-4OZ	Yugoslavia	6VA-6WZ	Republic of the Senegal
4PA-4SZ	Ceylon	7AA-7IZ	Indonesia
4TA-4TZ	Peru	7JA-7NZ	Japan
4UA-4UZ	United Nations	7SA-7SZ	Sweden
4VA-4VZ	Republic of Haiti	7ZA-7ZZ	Saudi Arabia
4WA-4WZ	Yemen	8AA-8IZ	Indonesia
4XA-4XZ	State of Israel	8JA-8NZ	Japan
4YA-4YZ	International Civil Aviation Organization	8SA-8SZ	Sweden
4ZA-4ZZ	State of Israel	8TA-8YZ	India
5AA-5AZ	Libya	8ZA-8ZZ	Saudi Arabia
5BA-5BZ	Republic of Cyprus	9AA-9AZ	San Marino
5CA-5GZ	Morocco	9BA-9DZ	Iran
5JA-5KZ	Colombia	9EA-9FZ	Ethiopia
5LA-5MZ	Liberia	9GA-9GZ	Ghana
5NA-5OZ	Nigeria	9KA-9KZ	Kuwait
5PA-5QZ	Denmark	9MA-9MZ	Malaya
5RA-5SZ	Madagascan Republic	9NA-9NZ	Nepal
5TA-5TZ	Islamic Republic of Mauretania	90A-9TZ	Republic of the Congo (Leopoldville)
	•	9UA-9UZ	Territory of Ruanda-Urundi

ABBREVIATIONS FOR C.W. WORK

Abbreviations help to cut down unnecessary transmission. However, make it a rule not to abbreviate unnecessarily when working an operator of unknown experience,

when working	an operator of unknown experience.		
AA	All after	OB	Old boy
AB	All before .	ŎM	Old man
ABT	About	OP-OPR	Operator
ADR	Address	OSC	Oscillator
		OSC	
AGN	Again	OT	Old timer; old top
ANT	Antenna	PBL	Preamble
BCI	Broadcast interference	PSE	Please
BCL	Broadcast listener	PWR	Power
BK	Break; break me; break in	PX	Press
BN	All between; been	R	Received as transmitted; are
B4	Before	RAC	Rectified alternating current
č	Yes	RCD	Received
ČFM	Confirm; I confirm	REF	Refer to; referring to; reference
	Check	RIG	
CK			Station equipment
CL	I am closing my station; call	RPT	Repeat; I repeat
CLD-CLG	Called; calling	RX, RCVR	Receiver
CUD	Could	SED	Said
CUL	See you later	SEZ	Says
CUM	Come	SIG	Signature; signal
ĊW	Continuous wave	SINE	Operator's personal initials or nickname
DLD-DLVD	Delivered	SKED	Schedule
DX	Distance, foreign countries	SRI	Sorry
ECO	Electron-coupled oscillator	SVC	Service; prefix to service message
ES	And, &	ŤFČ	Traffic
FB	Fine business; excellent	TMW	Tomorrow
GA		T MI W	
	Go ahead (or resume sending)	TNX-TKS	Thanks
GB.	Good-by	TT	That .
GBA	Give better address	TU	Thank you
GE	Good evening	TT TU TVI	Television interference
GG	Going	TVL	Television listener
GM	Good morning	TX	Transmitter
GN	Good night	TXT	Text
GND	Ground	UR-URS	Your; you're; yours
GP	Ground plane	VFO	Variable-frequency oscillator
ĞŪD	Good	Ϋ́Υ	Very
HI	The telegraphic laugh; high	WA	Word after
HR	Here; hear	WB	Word before
HV	Have	wd-wds	Word; words
iiw	How		
		WKD-WKG	Worked; working
LID	A poor operator	WL_	Well; will
MA, MILS	Milliamperes	WUD	Would
MSG	Message; prefix to radiogram	WX	Weather
N_	No	XMTR	Transmitter
ND	Nothing doing	XTAL	Crystal
NIL	Nothing; I have nothing for you	YF (XYL)	Wife
NM	No more	YL '	Young lady
NR	Number	73	Best regards
NW	Now; I resume transmission	88	Love and kisses
	•		

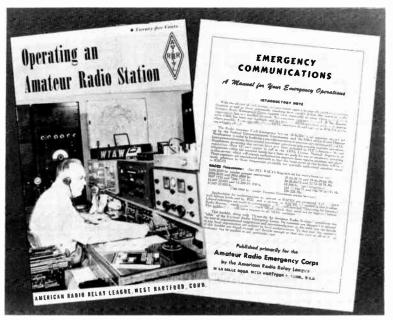

▶ Operating an Amateur Radio Station covers the details of practical amateur operating. In it you will find information on Operating Practices, Emergency Communication, ARRI Operating Activities and Awards, the ARRI Field Organization, Handling Messages, Network Organization, "Q" Signals and Abbreviations used in amateur operating, important extracts from the FCC Regulations, and other helpful material. It's a handy reference that will serve to answer many of the questions concerning operating that arise during your activities on the air.

▶ Emergency Communications is the "bible" of the Amateur Radio Emergency Corps. Within its eight pages are contained the fundamentals of emergency communication which every amateur interested in public service work should know, including a complete diagrammatical plan adaptable for use in any community, explanation of the role of the American Red Cross and FCC's regulations concerning amateur operation in emergencies. The Radio Amateur Civil Emergency Service (RACES) comes in for special consideration, including a table of RACES frequencies on the front cover.

The two publications described above may be obtained without charge by any Handbook reader. Either or both will be sent upon request.

AMERICAN RADIO RELAY LEAGUE
38 La Salle Road
West Hartford 7, Connecticut, U. S. A.
Please send me, without charge, the following:
☐ OPERATING AN AMATEUR RADIO STATION ☐ EMERGENCY COMMUNICATIONS
Name(Please Print)
Address
•

Vacuum Tubes and Semiconductors

For the convenience of the designer, the receiving-type tubes listed in this chapter are grouped by filament voltages and construction types (glass, metal, miniature, etc.). For example, all miniature tubes are listed in Table I, all metal tubes are in Table II, and so on.

Transmitting tubes are divided into triodes and tetrodes-pentodes, then listed according to rated plate dissipation. This permits direct comparison of ratings of tubes in the same power classification.

For quick reference, all tubes are listed in numerical-alphabetical order in the index. Types having no table reference are either obsolete or of little use in amateur equipment. Base diagrams for these tubes are listed.

Tube Ratings

Vacuum tubes are designed to be operated within definite maximum (and minimum) ratings. These ratings are the maximum safe operating voltages and currents for the electrodes, based on inherent limiting factors such as permissible cathode temperature, emission, and power dissipation in electrodes.

In the transmitting-tube tables, maximum ratings for electrode voltage, current and dissipation are given separately from the typical operating conditions for the recommended classes of operation. In the receiving-tube tables, ratings and operating data are combined. Where only one set of operating conditions appears, the positive electrode voltages shown (plate, screen, etc.) are, in general, also the maximum rated voltages.

For certain air-cooled transmitting tubes, there are two sets of maximum values, one designated as CCS (Continuous Commercial Service) ratings, the other ICAS (Intermittent Commercial and Amateur Service) ratings. Continuous Commercial Service is defined as that type of service in which long tube life and reliability of performance under continuous operating conditions are the prime

consideration. Intermittent Commercial and Amateur Service is defined to include the many applications where the transmitter design factors of minimum size, light weight, and maximum power output are more important than long tube life. ICAS ratings are considerably higher than CCS ratings. They permit the handling of greater power, and although such use involves some sacrifice in tube life, the period over which tubes give satisfactory performance in intermittent service can be extremely long.

The plate dissipation values given for transmitting tubes should not be exceeded during normal operation. In plate modulated amplifier applications, the maximum allowable carrier-condition plate dissipation is approximately 66 per cent of the value listed and will rise to the maximum value under 100 per cent sinusoidal modulation.

Typical Operating Conditions

The typical operating conditions given for transmitting tubes represent, in general, maximum ICAS ratings where such ratings have been given by the manufacturer. They do not represent the *only* possible method of operation of a particular tube type. Other values of plate voltage, plate current, etc., may be used so long as the maximum ratings for a particular voltage or current are not exceeded.

Equivalent Tubes

The equivalent tubes listed in Table VIII are used occasionally in amateur service. In addition to the types listed, other equivalents are available for special purposes such as series-heater string operation in TV receivers. These types require unusual values of heater voltage (3.15, 4.2, etc.), and have controlled warm-up time characteristics to minimize voltage unbalance during starting. Except for heater design, these types correspond electrically and mechanically to 6-volt prototypes.

INDEX TO TUBE TABLES

I - Miniature Receiving Tubes	V16	IX - Control and Regulator Tubes	V25
		X — Rectifiers	
III - 6.3-Volt Glass Tubes with Octal		XI - Triode Transmitting Tubes	
Bases			
IV - 6.3-Volt Lock-In Base Tubes	V22	mitting Tubes	V30
V — 1.5-Volt Battery Tubes	V22	XIII — Electrostatic Cathode-Ray	
VI - High-Voltage Heater Tubes	V23	Tubes	V32
		XIV — Transistors	
VIII - Equivalent Tubes	V23	XV — Crystal Diodes	V34

INDEX TO VACUUM-TUBE TYPES

Base-diagram section

7. ype Page Base Base Base Base Base Base Base Bas	4 - 4
*** *** *** *** *** *** *** *** *** *** *** *** ** *** *** *** *** *** *** *** *** *** *** *** *** ** *** *** *** *** *** *** *** *** *** *** *** *** ** *** *** *** *** *** *** *** *** *** *** *** *** ** *** *** *** *** *** *** *** *** *** *** *** *** ** *** *** *** *** *** *** *** *** *** *** *** *** ** *** *** *** *** *** *** *** *** *** *** *** *** ** *** *** *** *** *** *** *** *** *** *** *** *** ** *** *** *** *** *** *** *** *** *** *** *** *** ** *** *** *** *** *** *** *** *** *** *** *** *** ** *** *** *** *** *** *** *** *** *** *** *** *** ** *** *** *** *** *** *** *** *** *** *** *** *** ** *** *** *** *** *** *** *** *** *** *** *** *** ** *** *** *** *** *** *** *** *** *** *** *** *** ** *** *** *** *** *** *** *** *** *** *** *** *** ** *** *** *** *** *** *** *** *** *** *** *** *** ** *** *** *** *** *** *** *** *** *** *** *** *** ** *** *** **	
Page	V24 V24 V27
7 ye	2422222
Type Page Bar	\\\\\\\\\\\\\\\\\\\\\\\\\\\\\\\\\\\\\\

Fuge Type Page T			Type 10211 B 1021 B 1023 C 10334 A 10334 A 10338 B	
Page Type	VV34 V34 V34	VVV4 V34 V34	2	
Type				
SEMICONDUCTORS Progr. Type Progr	~~~~~ ~~~~~~~~~~~~~~~~~~~~~~~~~~~~~~~~	\$	V <vvvvvvv 2="" 2<="" th=""><th></th></vvvvvvv>	
EMICONDUCTORS Type Page Type Page Type Page Type 10034 V34 2N100 V33 2N371 V33 SE54 10036 V34 2N100 V33 2N372 V33 SE54 10036 V34 2N100 V33 2N374 V33 SE54 100370 342 2N160 V33 2N374 V33 SE54 100370 342 2N160 V33 2N374 V33 CK728 100370 342 2N160 V33 2N374 V33 CK728 100370 342 2N160 V33 2N344 V33 HB1 100470 342 2N150 V33 2N41 V33 HB1 10048 2N247 V33 2N44 V33 HB1 10049 2N247 V33 2N44 V33 HB1 10049 2N34 V33 2N34 V33	1N443B 1N448 1N548 1N540	IN198A IN279 IN283 IN295	17.76 1.011.68 1.011.68 1.011.68 1.011.68 1.011.68 1.011.68 1.011.68 1.011.68	
yp Page Type Page Type Vage SEA SE	222424 22242 22242	2 V V V V V V V V V V V V V V V V V V V	V V V V V V V V V V V V V V V V V V V	æ
yp Page Type Page Type Vage SEA SE			Type IN634. IN636. IN2069 IN2070 IN2071 IN2485/200 IN2485/200 IN2487/200 IN2487/600 IN2487/600 IN31943	MICONDI
yp Page Type Page Type Vage SEA SE	VVV 3333333333333333333333333333333333	24422 34422 34422	11 22 22 22 22 22 22 22 22 22 22 22 22 2	בַ
Type Page Type 2015 201372			XXXXXXXXXXXXXXXXXXXXXXXXXXXXXXXXXXXXXX)RS
7'qq				
Type 5854 5856 5856 5856 5856 5856 5856 5856	@N055C			
	V2777			

1810 V20 787, 74 1820 V21 778 1822 V21 778 1822 V22 778 1822 V24 788 1824 V25 788 1824 V26 788 1825 V27 788 1826 V27 788 1	
5000 2 2 2 A G 6000 2 A G 6000 2 2 A G 6000 2 A G	
70555 70555	
HRC2531. 4AC HRC2531. 4AC HRC2531. 4AC HRC2575. V31 7BM HRC2575. V31 7BM HRC3544. 3BM HRC3544. 3BM HRC3546. 3BM HRC364. 3BM HRC364. 3BM HRC364. 3BM HRC366. 3	
RK522 RK523 RK524 RK525 RK526 RK	\$\\\\\\\\\\\\\\\\\\\\\\\\\\\\\\\\\\\\\

VACUUM-TUBE BASE DIAGRAMS


Socket connections correspond to the base designations given in the column headed "Base" in the classified tube-data tables. Bottom views are shown throughout. Terminal designations are as follows:

RC = Ray-Control Eelectrode
Ref = Reflector
S = Shell
TA = Target IS = Internal Shield K = Cathode = Anode D = Deflecting Plate F = Filament
FE = Focus Elect.
G = Grid
H = Heater = Beam NC = No Connection
P = Plate (Anode)
P₁ = Starter-Anode BP = Bayonet Pin BS = Base Sleeve U = Unit ■ Gas-Type Tube C = Ext. Coating
CL = Collector H = Heater IC = Internal Con. Par = Beam Plates

Alphabetical subscripts D, P, T and HX indicate, respectively, diode unit, pentode unit, triode unit or hexode unit in multi-unit types. Subscript CT indicates filament or heater tap.


Generally when the No. 1 pin of a metal-type tube in Table II, with the exception of all triodes, is shown connected to the shell, the No. 1 pin in the glass (G or GT) equivalent is connected to an internal shield.


E.I.A. TUBE BASE DIAGRAMS

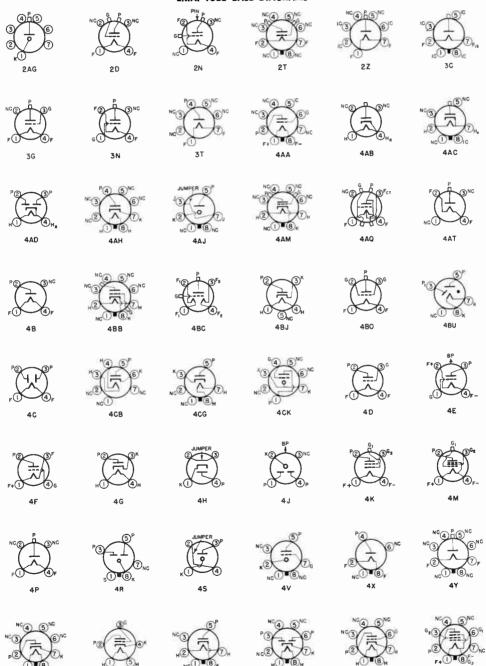

5AB


5AC

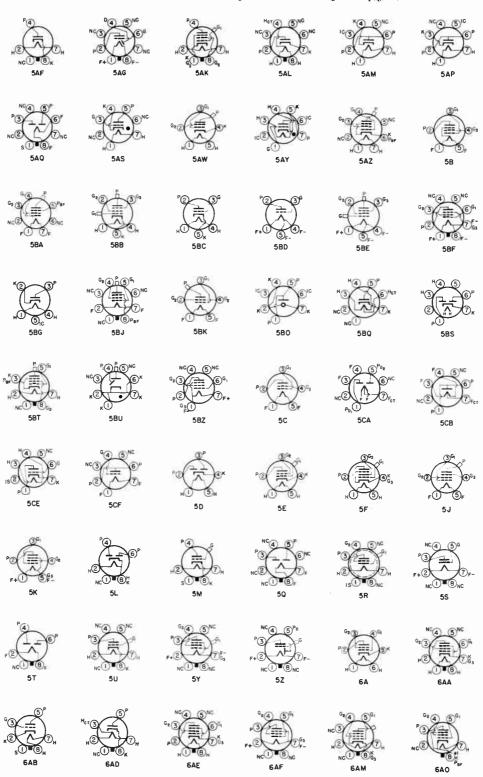


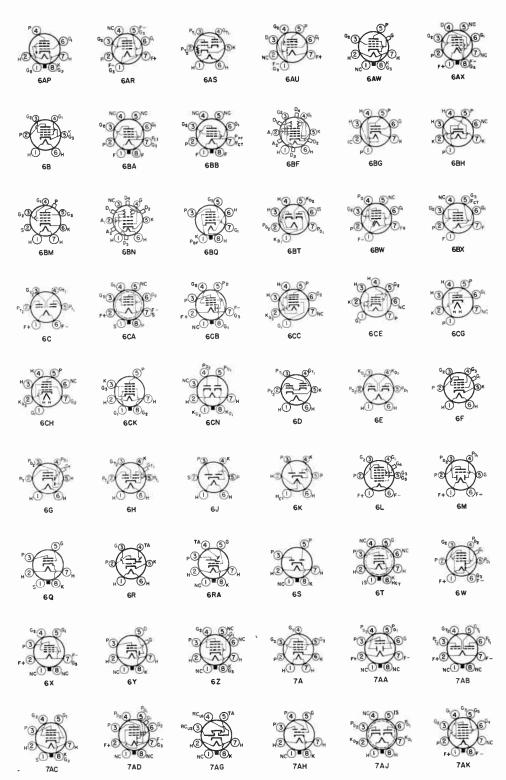

V8 Chapter 25


TUBE BASE DIAGRAMS

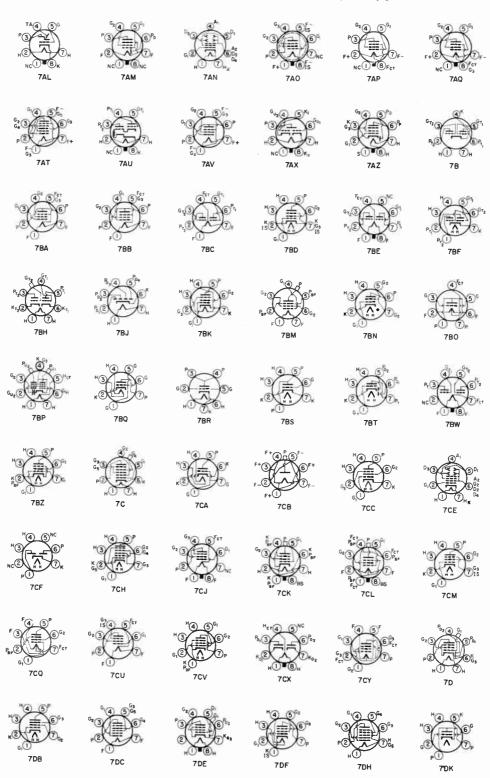


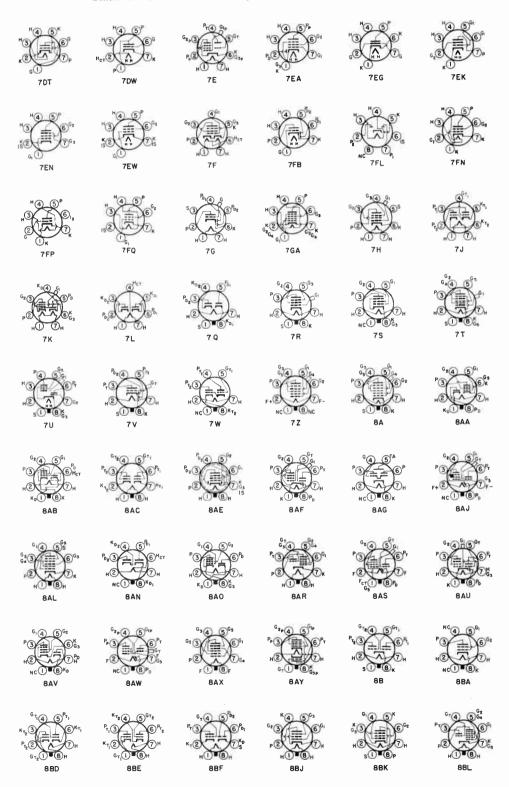

V10 Chapter 25


TUBE BASE DIAGRAMS

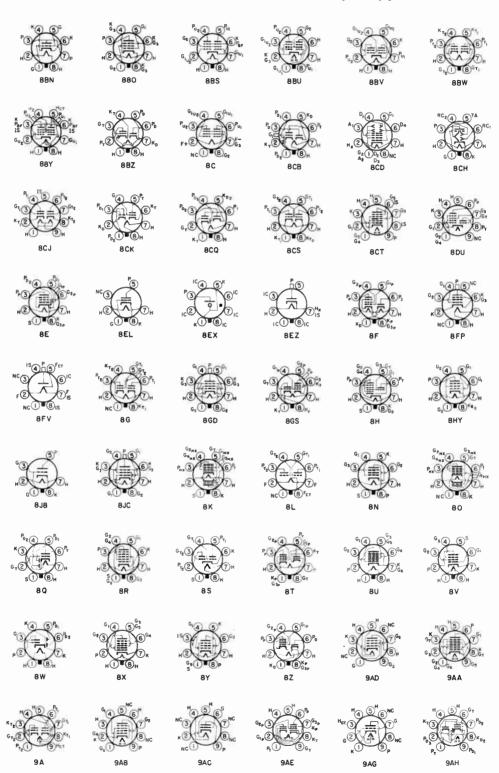


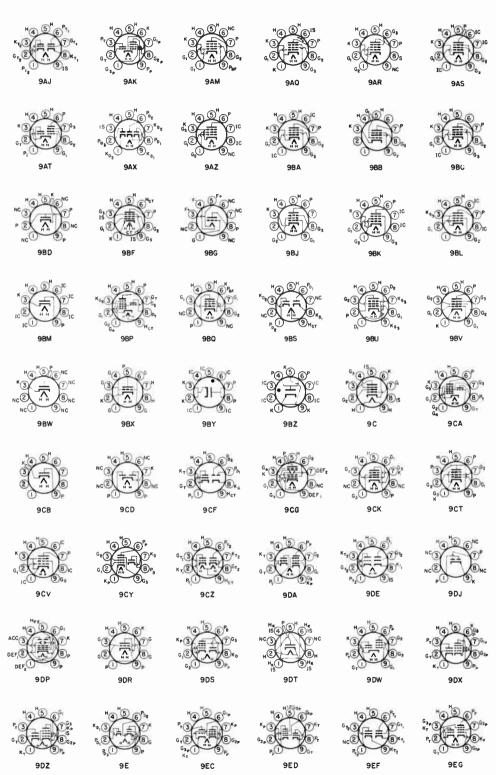



V12 Chapter 25

TUBE BASE DIAGRAMS

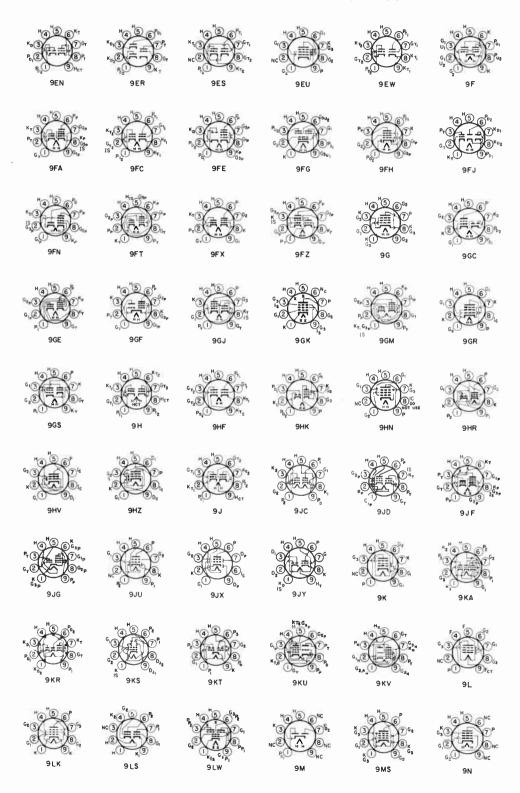

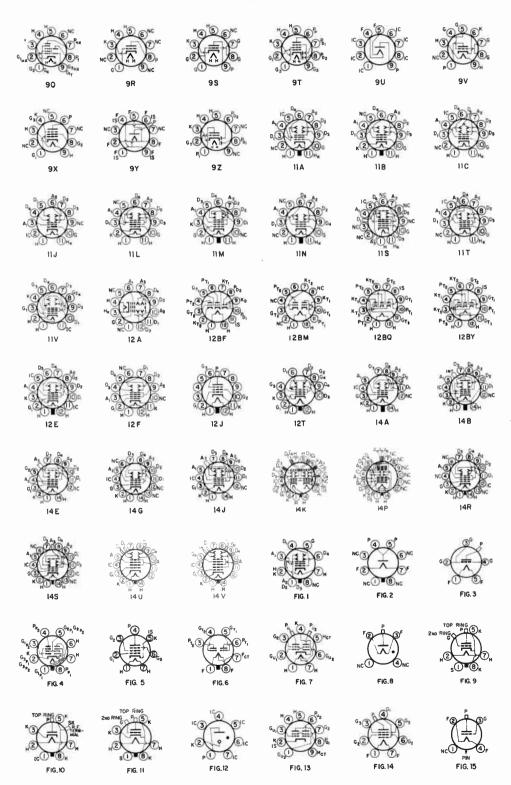

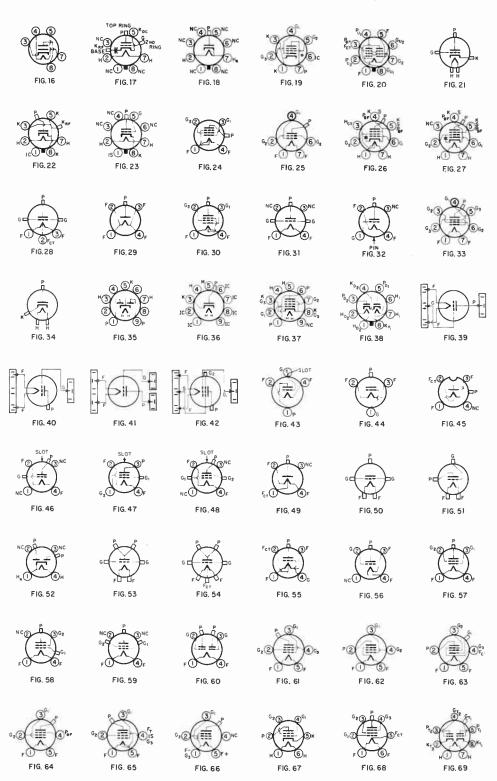

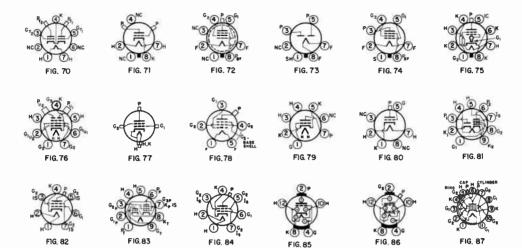



Туре	Name	Base		. or ater	Ca	pacitar μμf.	nces	ار د.		E	5		Ohms.	CON-	L	Load Res. Ohms	
			v.	Amp.	Cin	Cout	Cgp	Plate Supply	Grid	Screen	Screen Ma.	Plate Ma.	Plate Res. (Transcon- ductance	Amp. Factur	Load Res. (Watts
1A3	H.f. Diode	5AP	1.4	0.15	_	_	_		Ma	ix. a.c. vo	Itage per	plate - 1	17. Max. c	output curr	ent -0.	5 ma.	
1AF4	Sharp Cut-off Pent.	SAR	1.4	0.025	3.8	7.6	0.009	90	0	90	0.55	1.8	1.8 meg.	1050	-	T -	T -
1L4	Sharp Cut-off Pent.	6AR	1.4	0.05	3.6	7.5	0.008	90	0	90	2.0	4.5	350K	1025	-	_	+-
1L6	Pentagrid Conv.	7DC	1.4	0.05	7.5	12.0	0.3	90	0	45	0.6	0.5	650K	300	-	_	_
1R5	Pentagrid Conv.	7AT	1.4	0.05	7.0	12.0	0.3	90	0	67.5	3.5	1.5	400K	280	G	rid No. 1	100K
1\$4	Pentagrid Pwr. Amp.	7AV	1.4	0.1	_	_	T -	90	-7.0	67.5	1.4	7.4	100K	1575	-	8K	0.27
1\$5	Diode — Pentode A ₁ Amp.	- GAU	1.4	0.05				67.5	0	67.5	0.4	1.6	600K	625	-	-	_
	K.T. Amp.			1	<u> </u>	_	_	90	0	90	Scre	en Resis	tor 3 meg.	, grid 10 m	eg.	1 meg.	0.05
1174	Variable-µ Pent,	6AR	1.4	0.05	3.6	7.5	0.01	90	0	67.5		3.5	500K	900	T -	-	_
104	Sharp Cut-off Pent.	SAR	1.4	0.05	3.6	7.5	0.01	90	0	90	0.5	1.6	1 meg.	900	_	_	_
105	Diode Pentode	6BW	1.4	0.05	_	_		67.5	0	67.5	0.4	1.6	600K	625	_	_	T -
2E30	Beam Pwr. A ₁ Amp. Pent. A ₁ Amp. A ₁ Amp. A ₁ Amp. A ₁ Amp. A ₂ Amp. A ₃ Amp. A ₄ Amp.	7CQ	6.0	0.65	9.5	6.6	0.2	250 250 250 250	450° 225° -25 -30	250 250 250 250	3.3/7.4 6.6/14.8 3/13.5 4/20	88 ² 82 ² 120 ²	63K	3700 — —	40 ⁵ 80 ⁵ 48 ⁵ 40 ⁵	4.5K 9K ⁶ 8K ⁶ 3.8 ⁶	9 12.5
2EA51	Sharp Cut-off Pent.	7EW	2.4	0.60	3.8	2.3	0.06	250	-1	150	4/20	10	150K	8000	40"	3.5	17
2EN5:	Dual Diode	7FL	2.1	0.45	-	-	0.00	2.50			Itage per			utput curr	nnt 5/	7	
			1.4	0.2			1	135	-7.5	90	2.6	14,92	90K	T Curr	- 3,1	Jilla.	100
3A4	Pwr. Amp. Pent.	7BB	2.8	0.1	4.8	4.2	0.34	150	-8.4	90	2.2	14.12	100K	1900	-	8K	0.6
3A5 3DK61	H.f. Dual Triode ¹⁰	7BC	2.8	0.11	0.9	1.0	3.2	90	-2.5	-	-	3.7	8.3K	1800	15		_
	Sharp Cut-off Pent.	7CM	3.15	0.6	6.3	1.9	0.02	300	-6,5	150	3.8	12	1000	9800	<u> </u>		-
3Q4	Pwr. Amp. Pent.	7BA -	2.8	0.1	5.5	3.8	0.2	90	-4.5	90	2.1	9.5	100K	2150	_	10K	0.27
			1.4	0.05		 	-	-	-	+	1.7	7.7	120K	2000	-	_10K	0.24
354	Pwr. Amp. Pent.	7BA	2.8	0.05	_	_	_	90	-7	67.5	1.4	6.1	100K	1575	-	8K	0.27
4EW6:	Sharp Cut-off Pent.	7CM	4,2	0.03	10.0	2.4	0.04	300	-3.5	180	3.2	11		1425	-		0.235
6AB4	U.h.f. Triode	5CE	6.3	0.15	2.2	0.5	1.5	250	200°	100	3.2	10	10.9K	1400 5500	60		-
6AD8	Duat Diode — Pent.	91	6.3	0.3	4.0	4.6	0.002	250	-2	85	2.3	6,7		1100	00		
	A. Amn							80	150°	- 03	2.3	16	1 meg. 2.27K	6600	15		-
6AF4A	U.h.f. — Triode Osc. 950 Mc.	7DK	6.3	0.225	2.2	0.45	1.9	100	10KΩ	-	0.49	22	- Z.Z/K	0000	- 13		+=
								250	180*	150	2.0	6.5	800K	5000	-		+=
6AG5	Sharp Cut-off Pent.	7BD	6.3	0.3	6.5	1.8	0.03	100	180°	100	1.4	4.5	600K	4500	-		+=
CAUC	Sharp Cut-off Pent. Amp.	784		0.45				300	160*	150	2.5	10	500K	9600	=		-
6AH6	Pent. Triode Amp.	7BK	6.3	0.45	10.0	2.0	0.03	150	160*	-		12.5	3.6K	11K	40		$\vdash =$
6AJ4	U.h.f. Triode	9BX	6.3	0.225	4.4	0.18	2.4	125	68*	_	_	16	4,2K	10K	42		-
						-		180	200°	120	2.4	7.7	690K	5100	- "-		_
6AK5	Sharp Cut-off Pent.	7BD	6.3	0.175	4.0	2.8	0.02	150	330°	140	2.2	7	420K	4300	-		
								120	200°	120	2.5	7.5	340K	5000	_		
6AK6	Pwr. Amp. Pent.	7BK	6.3	0.15	3.6	4.2	0.12	180	-9	180	2.5	15	200K	2300	_	10K	1.1
6AL5	Dual Diode ¹⁰	6BT	6.3	0.3	_	_	-		M	ax. r.m.s	. voitage	-117. M	ax. d.c. ou	tput currer	nt - 9 m		
6AM4	U.h.f. Triode	9B X	6.3	0.225	4.4	0.16	2.4	150	100°		_	7.5	10K	9000	90	_	_
6AM8A:	Diode — Sharp Cut-off Pent.	9C Y	6.3	0.45	6.0	2.6	0.015	200	120*	150	2.7	11.5	600K	7000	_	_	-
6AN4	U.h.f. Triode	7DK	6.3	0.225	2.8	0.28	1.7	200	100°	_	_	13	_	10K	70	_	_
6AN5	Beam Pwr. Pent.	7BD	6.3	0.45	9.0	4.8	0.075	120	120*	120	12.0	35	12.5K	8000	_	2.5K	1.3
GANSA:	Medium-µ Triode	9DA	6.3	0.45	2.0	2.7	1.5	200	-6	_	-	13	5.75K		_	_	-
	Sharp Cut-off Pent.	JUA	0.3	0.43	7.0	2.3	0.04	200	180°	150	2.8	9.5	30K	6200	_	_	_
6AQ5A‡	Beam Pwr, Pent,	7BZ	6.3	0.45	8,3	8.2	0.35	180	-8.5	180	3/4	30z	58K	3700	295	5.5K	2.0
					-14		0.00	250	-12.5	250	4.5/7	472	52K	4100	455	5K	4.5
6AQ6	Dual Diode —	7BT	6.3	0.15	1.7	1.5	1.8	100	-1	_		0.8	61 K	1150	70	_	
	High-µ Triode						-11	250	-3		-	1	58K	1200	70		
6AR5	Pwr. Amp. Pent.	6CC	6.3	0.4	_	_	_	250	-16.5	250	5.7/10	35 ²	65K	2400	345	7K	3.2
6AR8	Sheet Beam	9DP						250	- 18	250	5.5/10	33 ²	68K	2300	325	7.6K	3.4
6AS5	Beam Pwr. Amp.	7CV	6.3	0.3	12	- 6.2	-	150 1	0.5	TV Cold			nous Dete	ctor — Bur			
6AS6	Sharp Cut-off Pent,	7CM	6.3	0.8	12	6.2	0.6	150	-8.5	110	2/6.5	36²	110"	5600	355	4.5K	2.2
6AS8	Diode — Sharp Cut-off Pent.	9DS	6.3	0.175	7	2,2	0.2	120 200	-2	120	3.5	5.2	110K	3200	-		
6AT6	Duplex Diode — High-µ Triode	7BT	6.3	0.45	2.3	1.1	2.1	250	180* -3	150	3	9.5	300K	6200	- 70	_	_
	Medium·µ Triode				2.3	0.5	1.5	100		_		8.5	58K	1200	70	_	
GATSA;	Sharp Cut-off Pent.	9DW	6.3	0.45	4.5	0.9	0.025	250	100° 200°	150	1.6	8.5	6.9K	4600	40		
GAUGA:	Sharp Cut-off Pent.	7BK	6.3	0.3	5.5	5	0.023	250	68*	150		7.7	750K	4600	_		
	Medium-µ Triode				2.6	0.34	2.2	150	150+	150	4.3	9	1 meg.	5200	40	_	
6AU8A:	Sharp Cut-off Pent.	9D X	6.3	0.6	7.5	3.4	0.06	200	82*	125	3.4	15	8.2K 150K	4900	40		
6AV6	Dual Diode — High-µ Triode	7BT	6.3	0.3	2.2	0.8	2.0	250	-2	125	3,4	1.2	62.5K	7000 1600	100		
	High-µ Triode				3.2	0.32	2.2	200	-2	_		4	17.5K	4000	70	_	
GAW8A:	Sharp Cut-off Pent.	9DX	6.3	0.6	11	2.8	0.036	200	180*	150	3.5	13	400K	9000	-/0		<u> </u>
CAVO	Medium-µ Triode	41.5			2.5	1	1.8	150	56*	130	5.5	18	400K	8500	40		
6A X8	Sharp Cut-off Pent.	9AE	6.3	0.45	5	3.5	0.006	250	120*	110	3.5	10	400K	4800	40	_	
CA 70	Medium-µ Triode	055		0::	2	1.7	1.7	200	-6	- 110		13	5,75K	3300	19		
6AZ8	Semiremote Cut-off Pent.	9ED	6.3	0.45	6.5	2.2	0.02	200	180°	150	3	9.5	300K	6000	- 19	_	
6BA6	Remote Cut-off Pent.	7BK	6.3	0.3	5.5	5	0.0035	250	68°	100	4.2	11	1 meg.	4400	-	_	
6BA7	Pentagrid Conv.	8CT	6.3	0.3		sc. 20Ks		250	-1	100	10	3.8	1 meg.	950	-	_	
	Medium-µ Triode				2.5	0.7	2.2	200	-8		- 10	8	6.7K	2700	18		
BA8A;	Sharp Cut-off Pent,	9DX	6.3	0.6	11	2.8	0.036	200	180+	150	3.5	13	400K	9000	16	_	
6BC4	U.h.f. Medium·µ Triode	9DR	6.3	0.225	2.9	0.26	1.6	150	100*	150	3.3	14.5	400K	10K	48	-	
BBC5	Sharp Cut-off Pent.	7BD	6.3	0.3	6.5	1.8	0.03	250	180+	150	2.1	7.5	800K	5700	46	-	
6BC7	Triple Diode	9AX	6.3	0.45	0.0	1.0							rcath. vo				
					2.5	1.3	1.4	150	220°		= 12 Ma.	10	rcath, vo	6200			
BC8	Medium-µ Dual Triode10	9AJ	6.3	0.4						- 1					35	- 1	_

Tues	Nr	Base		, or ater	Ca	pacitano μμf.	ces	, ×		_			Ohms	ron-	7	Ohms	
Туре	Name	Dase	٧.	Amp.	Cin	Cout	Cap	Plate Supply	Grid	Screen	Screen Ma.	Plate	Plate Res. 0	Transcon- ductance ¹¹	Amp. Factor	Res. C	Watts
6BD6	Remote Cut-off Pent.	7BK	6.3	0.3	4.3	5.0	0.005	100 250	-1 -3	100	5	13	150K 800K	2500 2000		_	=
6BE6	Pentagrid Conv.	7CH	6.3	0.3	0	sc. 20K	12	250	-1.5	100	6.8	2.9	1 meg.	475	=	_	-
6BE8A:	Medium·µ Triode	9EG	6.3	0.45	2.8	1.5	1.8	150	56*	_	_	18	5K	8500	40	_	
	Sharp Cut-off Pent.				4.4	2.6	0.04	250	68*	110	3.5	10	400 K	5200	-	254	1.9
6BF5 6BF6	Beam Pwr. Amp.	7BZ 7BT	6.3	0.3	1.8	0.8	0.65	110 250	-7.5 -9	110	4/10.5	39 ² 9.5	12K 8.5K	7500 1900	36 ⁵	2.5K	0.3
6BH5	Dual Diode — Medium·µ Triode Remote Cut·off Pent.	9AZ	6.3	0.2	4.9	5.5	0.002	250	-2.5	100	1.7	6.0	1.1 meg.	2200	-	-	-
6BH6	Sharp Cut-off Pent.	7CM	6.3	0,15	5.4	4.4	0.0035	250	-1	150	2.9	7.4	1.4 meg.	4600 -	_		_
6BH8:	Medium-µ Triode	9D X	6.3	0.6	2.6	0.38	2.4	150	-5		_	9.5	5.15K	3300	17	_	
	Sharp Cut-off Pent.			0.15	4.5	5.5	0.046	200 250	82*	125 100	3.4	15 9.2	150K	7000 3800	_		
6BJ6A 6BJ7	Remote Cut-off Pent. Triple Diode	7CM 9AX	6.3	0.15	4.3								1.3 meg. current ea		_ 1.0 M	a.	
18189	Dual Diode — Medium-µ Triode	9ER	6.3	0.6	2.8	0,38	2.6	250	_9	_	_	8	7.15K	2800	20		
6BK5	Beam Pwr. Pent.	9BQ	6.3	1.2	13	5	0.6	250	-5	250	3.5/10	372	100K	8500	355	6.5K	3.5
6BK6	Dual Diode — High-μ Triode	78T	6.3	0.3	3	ļ <u> </u>	-	250	-2 56*			1.2	62.5K 4.6K	1600 9300	100	_	-
6BK7B	Medium-µ Dual Triode ¹⁰ Triode	9AJ	6.3	0.4	2.5	1.8	1.8	150 250	-1.3			14	4.0K	5000	20	_	_
6BL8	Pentode	Fig. 83	6.3	0.43	5.2	3.4	0.025	250	-1.3	175	2.8	10	400K	6200	47	-	_
6BN4A	Medium-µ Triode	7EG	6.3	0.2	3.2	1.4	1.2	150	220*	_	_	9	6.3K	6800	43	-	_
6BN6	Gated-Beam Pent.	7DF	6.3	0.3	4.2	3.3	0.004	80	-1.3	60	5	0.23		2500	- 20	68K	_
6BN8; 6BQ5	Dual Diode — High-µ Triode Pwr. Amp. Pent.	9ER 9CV	6.3	0.6	3.6 10.8	0.25 6.5	2.5 0.5	250 300	-3 -7.3	200	10.8	1.6 49.5 ²	28K 38K	2500	70	5.2K	173
6BQ7A	Medium-µ Dual Triode10	9AJ	6.3	0.76	2.85	1.35	1.15	150	220*	_	10.0	9	6.1K	6400	39	J.2R	-
GBRSAI	Medium-µ Triode	9FA	6.3	0.45	2.5	0.4	1.8	150	56*	_	_	18	5K	8500	40	_	_
	Sharp Cut-off Pent.				5	2.6	0.015	250	68*	110	3.5	10	400K	5200	-	-	_
6BS8 6BT6	Low-Noise Dual Triode ¹⁰	9AJ 7BT	6.3	0.4	2.6	1.35	1.15	150 250	220° -3	_		10	5K 58K	7200 1200	36 70	_	 -
6BT8	Dual Diode — High-µ Triode Dual Diode — Pent.	9FE	6.3	0.45	7	2.3	0.04	200	180*	150	2.8	9.5	300K	6200	-		-
6BU6	Dual Diode — Low-µ Triode	7BT	6.3	0.3	_	-	-	250	-9	-	_	9.5	8.5K	1900	16	10K	0.3
6BU8	Dual Pent.10	9FG	6.3	0.3	6	31	_	1001	_	67.5	3.3	2.2	-	_	_	_	\equiv
6B A8‡	Dual Diode — Medium-µ Triode	9FJ	6.3	0.6	3.6	0.4	2	200 250	330* 68*	110	2.5	10	5,9K 250K	5600 5200	33		
6B X8	Dual Diode — Pent. Dual Triode ¹⁰	9HK	6.3	0.45	4.8	2.6	0.02	65	-1	110	3.5	9	250K	6700	25	_	-
6BY6	Pentagrid Amp.	7CH	6.3	0.3	5.4	7.6	0.08	250	-2.5	100	9	6.5	E _{c3} = -	-2.5 V.	1900	_	_
6B Y8‡	Diode — Sharp Cut-off Pent.	9FM	6.3	0.6	5.5	5	0.0035	250	68*	150	4.3	10.6	1 meg.	5200		_	_
6BZ6	Semiremote Cut-off Pent.	7CM	6.3	0.3	7.5	1.8	0.02	200	180*	150	2.6	11	600K	6100		_	<u> </u>
6BZ7 6BZ8	Medium-µ Dual Triode10 Dual Triode10	9AJ 9AJ	6.3	0.4	2.5	1.35	1.15	150 125	220° 100°	_	_	10 101	5.6K 5.6K	6800 8000	38 45	_	$\vdash =$
6C4	Medium-µ Triode	6BG	6.3	0.15	1.8	1.3	1.6	250	-8.5	_		10.5	7.7K	2200	17	_	 -
6CA5	Beam Pent.	7C V	6.3	1.2	15	9	0.5	125	-4.5	125	4/11	36²	15K	9200	375	4.5K	1.5
6CB6A‡	Sharp Cut-off Pent.	7C M	6.3	0.3	6.5	1.9	0.02	200	180*	150	2.8	9.5	600 K	6200	_	_	_
6CE5‡	R.f. Pent.	7BD 7CM	6.3	0.3	6.5	1.9	0.03	200	180*	150 150	2.8	9.5	600 K	6200 6200	<u> </u>	_	 -
6CF6 6CG6	Sharp Cut-off Pent. Semiremote Cut-off Pent.	7BK	6.3	0.3	5	5	0.008	250	-8	150	2.3	9	720K	2000	 -	_	+=
6C G7t	Medium-µ Dual Triode10	LAR	6.3	0.6	2.3	2.2	4	250	-8	_	_	9	7.7K	2600	20	_	_
6CG8A:	Medium-µ Triode	9GF	6.3	0.45	2.6	0.05	1.5	100	100*	_	_	8.5	6.9K	5800	40	_	_
	Sharp Cut-off Pent.		<u> </u>		4.8	0.9	0.03	250 200	200* -6	150	1.6	7.7	750K 5,75K	4600 3300	19	_	-
6C H8	Medium-µ Triode Sharp Cut-off Pent.	9FT	6.3	0.45	1.9	2.25	0.025	200	180°	150	2.8	9.5	300K	6200	19	-	-
6CL6	Pwr. Amp. Pent.	98 V	6.3	0.65	11	5.5.	0.12	250	-3	150	7/1.2	312	150K	11K	30s	7500	2.8
6CL8A1	Medium-µ Triode	9FX	6.3	0.45	2.7	0.4	1.8	300		_	_	15	5K	8000	40	_	
	Sharp Cut-off Tetrode	9CK			5	0.02	0.02	300 315	-1 -13	300 225	22/6	12 35²	100K 80K	6400 3750	345	8.5K	5.5
6C M6	Beam Pwr. Amp. Medium- Triode No. 1		6.3	0.45	8	8.5 0.5	3.8	200	-13	- 223	2.2/6	5	11K	2000	20	0.JK	- 3.3
6C M7‡	Dual Triode No. 2	9ES	6.3	0.6	3.5	0.4	3	250	-8	_	_	10	4.1K	4400	18	_	_
6C M81	High-µ Triode	9FZ	6.3	0.45	1.6	0.22	1.9	250	-2	_	_	1.8	50K	2000	100	-	_
an wet	Sharp Cut-off Pent.	J. 2			6	2.6	0.02	200	180*	150	2.8	9.5	300 K	6200	70	_	_
6C N7;	Dual Diode — High-µ Triode	9EN	6.3 3.15	0.3	1.5	0.5	1.8	250	-1	_		0.8	54K 58K	1300 1200	70	_	 -
	Medium-u Triode	45-		_	2.7	0.4	1.8	125	56*		-	15	5K	8000	40	_	_
ec ds‡	Sharp Cut-off Tetrode	9GE	6.3	0.45	5	2.5	0.019	125	-1	125	4.2	12	140K	5800	_	_	_
6CR6	Diode — Remote Cut-off Pent.	7EA	6.3	0.3	-	-	_	250	-2	100	3	9.5	200K	1950	- 22	_	=
6C R8‡	Triode	9GJ	6,3	0.45	6	2.8	0.018	125 125	-2 56*	125	3	12	5.5 K	7700	22		+=
6CS5	Pentode Bearn Pwr. Pent.	9CK	6.3	1.2	15	9	0.018	200	180*	125	2.2	472	28K	8000	=	4K	3.8
6CS6	Pentagrid Amp.	7CH	6.3	0.3	5.5	7.5	0.05	100	-1	30	1.1	0.75	1 meg.	950	E _{c3} =	0 V.	-
6CS7‡	Medium-µ Triode No. 1	9EF	6.3	0.6	1.8	0.5	2.6	250	-8.5	-	_	10.5	7,7K	2200	17	_	_
-	Dual Triode Triode No. 2				3.0	0.5	2.6	250	- 10.5	-	4/9.5	19	3.45K	4500 7500	15.5		- 22
6CU5 6CW4	Bearn Pwr. Pent. Triode	7CV Fig. 85	6.3	0.13	13.2	8.6	0.7	120 70	-8 0	110	4/8,5	50 ²	10K 5.44K	12.5K	68	2.5K	2,3
6CW5	Pentode	9C V	6.3	0.76	12	6	0.52	170	-12.5	170	5	70	-	-	-	2,4 K	5.6
	Medium-µ Triode	9DX	6.3	0.75	2.2	0.38	4.4	150	150*		_	9.2	8.7K	4600	40	_	-
6C X8	Sharp Cut-off Pent.				9	4.4	0.06	200	68*	125	5.2	24	70K	10K	-		
6CY5	Sharp Cut-off Tetrode	7EW	6.3	0.2	4.5	3	0.03	125	-7	80	1.5	10	100K	8000	_		├ ─
	Dissimilar —	9EF	6.3	0.75	1.57	0.37	1.87	2507	-37		_	1.27	52K7	13007	687		I —

Туре	Name	Base	Fil. Hea	or ater	Ca	pacitan μμf.	ces	۷ .		_	_		Ohms	-CON-	1	Ohms	_
1346	Name		٧.	Amp.	Cin	Cout	Свр	Plate Supply	Grid Bias	Screen	Screen Ma.	Plate Ma.	Plate Res.	Transcon- ductance ¹¹	Amp. Factor	Res.	Watts
6CZ5‡	Beam Pwr. Amp. A ₁ Amp. AB ₁ Amp ³	9HN	6.3	0.45	8	8.5	0.7	250 350	-14 -23.5	250 280	4.6/8 3/13	48 ² 103 ²	73K	4800	465 465	5K 7.5K ⁶	5.4 1.5
6DB5	Beam Pwr. Amp.	9GR	6.3	1.2	15	9	0,5	200	180*	125	2.2/8.5	46/47	28K	8000	-	4K	3.8
6DB6	Sharp Cut-off Pent.	7CM	6.3	0.3	6	5	0.0035	150	-1	150	6.6	5.8	50K	2050	Ec	-3 V.	-
6DC6	Semiremote Cut-off Pent.	7CM	6.3	0.3	6.5	2	0.02	200	180*	150	3	9	500K	5500	_	_	_
6DE6	Sharp Cut-off Pent.	7CM	6.3	0.3	6.3	1.9 0.52 ⁷	0.02	200 250 ⁷	180° -11'	150	2.8	9.5	600K	6200 2000 ⁷	17,57	_	-
6DE7	Dissimilar — Dual Triode	9HF	6.3	0.9	5.50	10.52	8,5*	1504	-17.5*	-	+ -	5.5 ⁷ 35 ⁸	8.75K ⁷ 925 ⁸	6500*	68		-
6D18	Twin Triode	9AJ	6.3	0.365	3.3	1.8	1.4	90	-1.3	-	-	15	-	12.5K	33	_	
6D K6	Sharp Cut-off Pent.	7CM	6.3	0.3	6.3	1.9	0.02	300	-6.5	150	3.8	12		9800	_	_	_
6DR7	Dissimilar — Dual Triode	9HF	6.3	0.9	2.2	0.34	4.5	330	3			1.4	_	1600	687		-
6DS4	High-µ Triode	Fig. 85	6.3	0.135	5.5 4.1	1.0	8.5 .92	275 70	- 17.5 0	_	-	35 8	5.44 K	6500 12.5K	68 68		
								250	-8.5	200	3/10	32 ²	28K	5800	325	8K	3.8
6DS5	Beam Pwr. Amp.	7BZ	6.3	0.8	9.5	6.3	0.19	250	270°	200	3/9	25 ²	28K	5800	275	8K	3.6
6DT5	Pwr. Amp. Pent.	9HN	6.3	0.76	10.8	6.5	0.5	300	-7.3	200	10.8	49.5²	38K	_	_	5.2K	17
6DT6 6DT8	Sharp Cut-off Pent. High-µ Dual Triode ¹⁰	7EN 9DE	6.3	0.3	5.8 2.7	1.6	0.02	150 250	560°	100	2.1	1.1	150K 10.9K	615 5500	60	_	
6D W5	Beam Pwr. Amp.	9CK	6.3	1,2	14	1.6	1.6 0.5	200	-22.5	150	2	10 55	15K	5500	60	_	
6EA5	Sharp Cut-off Tet.	7EW	6.3	0.2	3.8	2.3	.06	250	-1	140	0,95	10	150K	8000	_	_	
6EA81	Triode	9AE	6.3	0.45	3	0.3	1.7	330	-12	_	_	18	5K	8500	40	_	
,	Sharp Cut-off Pent.				5	2.6	0.02	330	_9	330	4	12	80K	6400	_	_	
6EB5	Dual Diode High-µ Triode	6BT	6.3	0.3	2.4	.36	4,4	330					rent 5.5 ma	2700	100	_	
6EB8	Sharp Cut-off Pent.	9D X	6.3	0.75	11	4.2	0.1	330	_5 _9	_	7	2 25	37 K	12,5K	100	_	
6EH5	Power Pentode	7C V	6.3	1.2	17	9	0.65	135	0	117	14.5	42	11K	14.6K	_	3K	1.4
6EH8	Triode	9JG	6.3	0.45	2.8	1.7	1.8	125	-1	_	_	13.5	_	7500	40	_	
	Pentagrid Conv.	1 1			4.8	2.4	0.02	125	-1	125	4	12	170K	6000	_	_	
6ER5 6ES5	Tetrode	7FN 7FP	6.3	0.18	4.4 3.2	3.0	0.38	200	-1.2	0	0	10	8K	10.5K	80	_	
6ES8	Triode Dual Triode	9DE	6.3	0.20	3,4	3.2 1.7	1.9	200 130	-1.2	_	_	10 15	8K	9000 12.5K	75 34		
6EU7	Twin Triode	9LS	6.3	0.3	1.6	0.2	1.5	100	-1.2	_	-	0.5	80 K	1250	100	_	
6EU8	Triode	9JF	6.3	0.45	5.0	2.6	0.02	150	_	_	_	18	5K	8500	40	_	_
	Pentode	Į į			3.0	1.6	1.7	125	-1	125	4	12	80 K	6400	_	_	
GE V5	Sharp Cut-off Tet. Triple Tripde No. 1	7EW	6.3	0.2	4.5	2.9	0.035	250	-1	80	0.9	11.5	150K	8800	-		
6EZ8	Triple Triode No. 1 Triode No. 2 & 3	9KA	6.3	0.45	2.6	1.2	1.5	330	-4	_	-	4.2	13.6K	4200	57	_	_
6FG5	Pentode	7GA	6.3	0.2	4.2	2.8	0.02	250	-0.2	250	.42	9	250K	9500	-	_	_
6FG7	Triode	9GF	6.3	0,45	3.0	1.3	1.8	125	-1	_	_	13	5700	7500	43	_	
	Pentode				5.0	2.4	0.2	125	-1	125	4	11	180K	6000	-	_	
6FH5	Triode Duplex	7FP	6,3	0.2	3.2 2.4	3.2	0.6	135	-1			11	5600	9000	50	_	
6FM8	Diode	9KR	6.3	0.45	2.2	=			ħ	Aax. a.c.	voltage =	200, Ma	x. d.c. out	put curren	t = 5 m	a.	
	Triode		***		1.5	0.16	1.8	300	-3	_	_	1	58K	1200	70	_	
6FQ5	Triode	7FP	6.3	0.18	4.8	4.0	0.4	135	-1.2	_	_	11.5	5500	11K	60	_	_
6FV6	Sharp Cut-off Tetrode	7FQ	6.3	0.2	4.5	3	0.03	125	-1	80	1.5	10	100K	8000	-		
6FV8	Triode Pentode	9FA	6.3	0.45	2.8 5	1.5	0.02	330 330	-1 -1	125	4	14	5K 200K	8000 6500	40	_	
6FW8	Medium-µ Twin Triode	9AJ	6.3	0.4	3.4	2.4	1,9	100	-1.2	-	_	15	2500	13K	33		
6FY5	Tetrode	7FN	6.3	0.2	4.75	3,3	0,50	135	-1	_	-	11	-	13K	70		
6GJ8	Triode	9AE	6.3	0.6	3.4	1.6	2.6	125	-1			13.5	5K	8500	40	_	_
	Pentode				8	2.4	0.36	125	-1	125	4.5	12	150K	7500	-	_	
6GK5	High-µ Triode Power Pentode	7FP 9GK	6.3	0.18	5 10	3.5 7.0	0.52	135 250	-1 -7.3	250	5,5	11.5	5400 38K	15K 11,3K	78 —	 5.2 K	5.7
6GM6	Pentode	7CM	6.3	0.4	10	2.4	0.036	125	-7.5	125	3.4	14	200K	13K	=	- J.Z.N	-
6GM8	Twin Triode	9DE	6.3	0.33	3	1,8	1,3	6.3	0	_		0,9	5K	2600	14	_	
90m0		302	0.0	0.33				12.6	0	_	_	2.5	3.4K	4600	100	_	
6GN8	High-µ Triode Sharp Cut-off Pent.	9DX	6.3	0.75	2.4	0.36 4.2	0.1	250	-2	 150	5.5	2 25	37K 60K	2700	100	_	
6GS8	Twin Pentode	9LW	6.3	0.30	6.0	3.2	- 0.1	100	-10	67.5	3.6	2.0	- OUN	11,5K		_	
6GY8	Triple Triode	9MB	6.3	0.45		-		125	-1	-	-	4.5	14K	4500	63	_	
6HF8	High-µ Triode	9D X	6.3	0.78	2.8	2.6	3.5	200	-2	_	_	4	17.5K	4000	70	_	
	Sharp Cut-off Pent.				10	4.2	0.1	200	68*	125	7 .	25	75K	12.5K	-	-	
614	Grounded-Grid Triode Medium-u A ₁ Amp. 10	7BQ	6.3	0.4	7.5	3.9	0.12	150	100° 50°		_	15 8.5	4.5K 7.1K	12K 5300	55 38	_	
elev:	Medium-µ A ₁ Amp. ¹⁰ Dual Triode Mixer	78F	6.3	0.45	2.2	0.4	1.6	150	810*	_	_	4,8	10,2K	1900		k voltage	
6R8	Triple Diode-Triode	9E	6.3	0.45	1.5	1.1	2.4	250	-9	_	_	9.5	8.5K	1900	16	10K	0.3
6S4A	Medium-µ Triode	9AC	6.3	0.6	4.2	0.9	2,6	250	8	_	_	26	3.6K	4500	16	_	_
6T4	U.h.f. Triode	7DK	6.3	0.225	2.6	0.25	1.7	80	150*	_	_	18	1.86K	7000	13	-	
GT8A:	Triple Diode-High-µ Triode	9E	6.3	0.45	1.6	1	2.2	100 250	-1 -3	_	_	0.8	54K 58K	1300 1200	70 70		_
	Medium-µ Triode				2.5	0,4	1.8	150	-3 56*		_	18	5K	8500	40	-	
6U8A‡	Sharp Cut-off Pent.	9AE	6.3	0.45	5	2.6	0.01	250	68*	110	3,5	10	400K	5200	-	_	
6V8	Triple Diode — Triode	9AH	6.3	0.45		_	_	100	-1	_	_	0.8	54K	1300	70	-	_
1		JA11	0.3	0.43	2.0		1,	250	-3 100e	-	-	1	58K	1200	70	-	
6X8A;	Medium-µ Triode Sharp Cut-off Pent.	9AK	6.3	0.45	2.0 4.3	0.5	0.09	100 250	100° 200°	150	1.6	8.5 7.7	6.9K 750K		40	_	
	Sharp Cut-on Fent.			-	4.3	0,7	0.03	200	200	150	1.0	1.1	750K				_

Type	Name	Base		or ater	Ca	pacitan μμf.	Ces	4 v.		£	5		Ohms	Transcon- ductance ¹¹	. L	Load Res. Ohms	" ts
.,,,,			٧.	Amp.	Cin	Cout	Cap	Plate Supply	Grid	Scree	Screen Ma.	Plate Ma.	Piate Res.		Amp. Factor	_	Watts
1284	Medium-µ Triode	9AG	12.6	0.3	4.9	0.9	5.6	250 250	−9 −12.5	=	-	23 4.4	2.5K	8000	20	-	-
12AB5	Beam Pwr. Amp. Ann.	9EU	12,6	0.2	8	8.5	0.7	250	-12.5	250	4.5/7	472	50K	4100	455	5K	4.5
	AB ₁ Amp.	1			_			250	-15	250	5/13	792	60K1	3750	705	10Ke	10
12AB6	Pentode Pentode	7CC 7BK	12.6	0.15	5.5 4.3	5	0.004	250 12.6	0	100	4.2 0.2	0.55	1 meg. 500K	730	-	-	-
12AC6 12AD6	Remote Cut-off Pent. Pentagrid Conv.	7CH	12.6	0.15	8	8	0.003	12.6	0	12.6	1.5	0.45	1 meg.	260	Grid	No. 1 Re	s. 33 K
			12.6	0.225	1.67	0.57	1.87		-2	12.7	- 110		1	1600	_		T
12AD7	Dual High-µ Triode10	9A	6.3	0.45	1.6*	0.45*	1.8*	250			_	1.25	62.5K		100		
12AE6A	Dual Diode — Medium-µ Triode	7BT	12.6	0.15	1.8	1.1	2	12.6	0	_	_	0.75	15K	1000	15	_	<u> </u>
12AE7	Low-µ Dissimilar	9A	12.6	0.45	4.7	0.75	3.9	16		<u> </u>	-	7.5	31.5K 985	4000 6500	13 6.4	_	 -
12AF6	Double Triode R.f. Pent.	7BK	12.6	0.15	4.2 5.5	0.85	0.006	12.6	0	12.6	0.35	0.75	300 K	1150	- 0.4	-	+=
12AJ6	Dual Diode — High-µ Triode	7BT	12.6	0.15	2.2	0.8	2	12.6	0	-	-	0.75	45K	1200	55	-	<u> </u>
	Medium-µ Triode	965	12.6	0.45	1.5	0.3	12	12.6	0.9	<u> </u>	_	0.25	27K	550	15		-
12AL8	Tetrode	363	12.0	0.43	8	1.1	0.7	12.6	-0.8	12.6**	50**	25	1K	8000	-	-	-
12AQ5	Beam Pwr. Amp. A ₁ Amp. AB ₁ Amp. ³	7BZ	12.6	0.225	8.3	8.2	0.35	250 250	-12.5 -15	250 250	4.5/7 5/13	472 792	52K 60K ¹	4100 37501	45 ⁵	5K 10K ⁶	4.5
			12.6	0.15	2.27	0.57	1.57	100	270*	-	-	3.7	15K	4000	60	-	-
12AT7	High-µ Dual Triode10	9A	6.3	0.3	2.28	0.48	1.58	250	200*	-	_	10	10.9K	5500	60	_	
12AU7A	Medium-µ Dual Triode10	9A	12.6	0.15	1.67	0.57	1.57	100	0	_	_	11.8	6.25K	3100	19.5	_	_
	modeling bags tillogs		6.3	0.3	1.68	0.35*	1.58	250	-8.5 120*	=	_	10.5	7.7K	2200 6100	17	-	<u> </u>
12AV7	Medium-µ Dual Triode10	9A	6.3	0.225	3.17	0.57	1.9*	100	56*	-		18	6.1 K	8500	37	-	+=
12AW6	Sharp Cut-off Pent.	7C M	12.6	0.45	6.5	1.5	0.025	250	200*	150	2	7	800K	5000	42	-	+=
	High-µ A ₁ Amp. ¹⁰		12.6	0.15	1.67	0.467	1.7'	250	-2	-	-	1.2	62.5K	1600	100	_	 -
12AX7A	Dual Triode Class B	9A	6.3	0.3	1.68	0.34*	1.78	300	0		_	40 ²	_	_	145	16K6	7.5
12AY7	Medium-μ A ₁ Amp.	9A	12.6	0.15	1.3	0.6	1.3	250	-4			3	<u> </u>	1750	40	<u> </u>	
	Dual Triode ¹⁰ Low-Level Amp.		6.3	0.3	3.17	0.57	1.97	150	2700° 270°	-	Plate resi	3.7	OK. Grid re	4000	0.1 meg. 60	V. G. =	12.5
12AZ7A;	High-µ Dual Triode10	9A	12.6 6.3	0.225	3.18	0.5	1.98	250	200*	+=-	_	10	10.9K	5500	60	-	+=
1284A;	Low-µ Triode	9AG	12.6	0.3	5	1.5	4.8	150	-17.5	_	_	34	1.03K	6300	6.5	-	_
12BH7A:	Medium-µ Dual Triode10	9A	12.6	0.3	3.27	0.57	2.67	250	-10.5	_	_	11.5	5.3K	3100	16.5	_	_
		7BK	6.3	0.6	3.2 ⁸ 5.5	0.4*	2.6 ^a	12.6	-0.65	12.6	0.0005	1.35	500K	1350		_	+
12BL6	Sharp Cut-off Pent.		12.6	0.15		1		100	270*	-	- 0.0003	3.7	15K	4000	60	-	+=
12BR7A;	Dual Diode — Medium-µ Triode	9CF	6.3	0.45	2.8	1	1.9	250	200*	-	_	10	10.9K	5500	60	-	_
12B V7	Sharp Cut-off Pent.	9BF	12.6	0.3	11	3	0.055	250	68*	150	6	25	90K	12K	1100	_	_
	·		6.3	0.6	7.5	3.3	0.007	200	-2.5	200	2.6	10	550K	7100	-	_	+_
12B X6	Pentode	9AQ	12.6	0.15										1			+-
12BY7A;	Sharp Cut-off Pent.	9BF	6.3	0.6	6.57	0.77	0.055 2.5 ⁷	250	68*	150	6	25	90K 31.8K	12K 3200	1200	_	-
12BZ7	High-µ Dual Triode10	9A	6.3	0.6	6.5*	0.55*	2.58	250	-2	_	_				100	_	
12CN5	Pentode	7C V	12.6	0.45	-	-	0.25	12.6	0	12.6	0.35	4.5	40K	3800	-	_	<u> </u>
12CT8	Medium-µ Triode Sharp Cut-off Pent.	9DA	12.6	0.3	7.5	0.19	0.044	150 200	-6.5 -8	125	3.4	9 15	8.2K 150K	7000	40	_	+=
12C X6	Sharp Cut-off Pent.	7BK	12.6	0.15	7.6	6.2	0.05	12.6	0	12.6	1.4	3	40K	3100	 	_	-
12DE8	Diode — Remote Cut-off Pent.	Fig. 81	12.6	0.2	5.5	5.7	0.006	12.6	0.8	12.6	0.5	1.3	300K	1500	-	_	
12D K7	Dual Diode — Tetrode	9HZ	12.6	0.5	_	_		12.6	0	12.6	1	6	4K	5000	-	3.5K	0.01
12DL8	Dual Diode — Tetrode	9HR	12.6	0.55	12	1.3	_	12.6	-0.5	12.6**	75**	40	480	15K	7.2	_	-
12DM7	Twin Triode	9A	6.3 12.6 12.6	0.26	1.6	0.39	1.7	100	-1.0	-	-	0.5	80 K	1250	100	_	_
12DQ7	Beam Pwr. Pent.	9BF	6.3	0.6	10	3.8	0.1	330	_	180	5.6	26	53K	10.5K	_	_	_
12DS7A	Dual Diode	9JU	12.6	0.4				Max.	a.c. volta	ge = 16.	Max. d.c 75	. output (urrent = 5	5 ma. 15K	7.2	800	.04
12DT6	Pwr. Tetrode Pentode	7EN	12.6	0.15	-	<u> </u>	_	150	-4.5	100	2.1	1.1	150K	- 13K	7.2	-	.04
	High-µ		12.6	0.15	1.6	0.46	1.7			.50				1600	100		
12 0 T7	Dual Triode	9A	6.3	0.3	1.6	0.34	1.7	300	-2			1.2	62.5K	1000	100	_	_
12DU7	Dual Diode	9J X	12.6	0,275	11	120	0.0	10			diode cur			6200	Ι —	9.31/	Dat
	Tetrode Dual Diode	-	-	-	11	3.6	0.6	16	— Max	16 average	1.5 diode cur	12 rent = 1	0 ma.	6200		2.7K	.025
12DV7	Dual Diode	9JY	12.6	0.15	1.3	0.38	1.6	16		average		0.4	19K	750	14		Τ-
12D V8	Dual Diode — Tetrode	9HR	12.6	0.375	9.0	1.0	12	12.6	18*		_	6.82	_	_	7.6	1250	.005
12DW7	Double Triode	9A	12.6	0.15	1.6	0.44	1.7	250	-2	=	_	1.2	62.5K	1600	100	_	-
120 11		Jn.	6.3	0.30	1.7	0.4	1.5	250	-8.5	_	_	10.5	7,7K	2200	17		-
12DW8	Diode Diode Trieds	anc	12.6	0.45	1.6 ⁷	0.7	1.8	16	0	_	-	7.58	_	2700 6500	9.5 6.4		1-
	Dissimilar Dual Triode		-	-	2	0.78	3.2	16	0	-	_	1.2	10K	2000	20	_	+=
12D Y8	Sharp Cut-off Triode Tetrode	อาก	12.6	0.35	11	3	0.74	16	_	12.6	2	14	5K	6000	_	_	+=
12DZ6	Pwr. Amp. Pent.	78 K	12.6	0.175	12.5	8.5	0.25	12.6	_	12.6	2.2	4.52	25K	3800	_	_	<u> </u>
12EA6	R.F. Pent.	7BK	12.6	0.175	11	4	0.04	12.6	- 3.4	12.6	1.4	3.22	32K	3800	_	_	-
12EC8	Medium-µ Triode	9FA	12.6	0.225	2.6	0.4	1.7	16	-2.2	=	-	2.4	6K	4700	25	_	_
					4.6	2.6	.02	16	-1.6	12.6	_	0.66	750K	2000	_	l —	_

Type	Name	Base		l. or ater	Ca	pacitar $\mu \mu f$.	ices	٧ .		_	_		Ohms.	COD-	ī	Ohms	_
.,,,,			٧.	Amp.	Cin	Cout	Cap	Plate Supply	Grid Bias	Screen	Screen Ma.	Plate Ma.	Plate Res. (Transcon- ductance ¹¹	Amp. Factor	Res. C	Watts
12ED5;	Pwr. Amp. Pent.	7C V ·	12.6	0.45	14	8.5	0.26	150	-4.5	150	11	36²	14K	8500	-	-	1.5
12EG6	Dual Control Heptode	7CH	12.6	0.15	_	_	_	30	I —	12.6	2.4	0.4	150K	800	-	I -	I -
12EK6	R.f. Pent.	7BK	12.6	0.2	10	5.5	0.032	12.6	-4.0	12.6	2	4.4	40K	4200	_	-	_
12EL6	Dual Diode — High-µ Triode	7FB	12.6	0.15	2.2	1	1.8	12.6	0	I -	_	0.75	45K	1200	55	I -	T -
12EM6	Diode — Tetrode	9HV	12.6	0.5	_	_	_	12.6	0	12.6	1	6	4K	5000	_	-	_
12F8	Duat Diode — Remote Cut-off Pent.	9FH	12.6	0.15	4.5	3	0.06	12.6	0	12.6	0.38	1	333K	1000	_	_	_
12FK6	Dual Diode — Low-µ Triode	7BT	12.6	0.15	1.8	0.7	1.6	16	0	1 -	_	1.3	6.2K	1200	7.4	_	_
12FM6	Dual Diode — Medµ Triode	78T	12.6	0.15	2.7	1.7	1.7	30	0	_	_	1.8	5.6K	2400	13.5	_	_
12FQ8	Twin Double Plate Triode	9KT	12.6	0.15	1.7	0.27	0.9	250	-1.5	_	_	1.5	76K	1250	95	_	
12FR8	Pentode Triode — Diode	9KU	12.6	0.32	8.5 2.6	5.5 2.0	0.15	12.6	-0.8	12.6	0.7	1.9	400K	2700 1200	_ 10		=
12FT6	Dual Diode — Triode	7BT	12.6	0.15	1.8	1.1	2.0	30	0	-	_	2	7.6K	1900	15	-	-
12FX8	Triode Heptode	9KV	12.6	0.27	2.2	0.25	1.3	12.6 12.6	1.6	=	_	0.29	500K	1400	10	_	_
12GA6	Heptode	7CH	12.6	0.15	5.0	13	0.05	12.6	0	12.6	0.80	0.30	1 meg.	140	_	-	+=
12H4	General Purpose Triode	7DW	12.6	0.15	2.4	0.9	3.4	90	0.	-	-	10		3000	20		
12J8	Dual Diode — Tetrode	9GC	12.6	0.325	10,5	4.4	0.7	12.6	-0	12.6	1.5	125	6K	5500	-	2.7K	0.02
12K5	Tetrode (Pwr. Amp. Driver)	7EK	12.6	0.45	-	-	-	12.6	-2	12.6**	85**	8	800	7000	5,6	800	0.02
12R5±	Beam Pwr. Pent.	7CV	12.6	0.45	13	9	0.55	110	-8.5	110	3.3	40	13K	7000	- 0.0	500	0.033
1207	Dual Medium-u Triode10	9A	12.6	0.15	1.67.8	0.47	1.57.8	12.6	0	-		1	12.5K	1600	20		+=
18FW6	Remote Cut-off Pent.	7CC	18	0.15	5.5	5	0.0035	150		100	4.4	11	250K	4400	_		-
18FX6	Dual Control Heptode	7CH	18	0.1	-	_		150		-		2.3	400K	7100	-	-	_
18F Y6	High-u Triode — Diode	78T	18	0.1	2.4	0.22	1.8	150	-1	-		0.6	77K	1300	100		_
25F5	Beam Pwr. Pent.	7CV	25	0.15	12	6	0.57	110	-7.5	110	3/7	36, 37	16K	5800	-	2.5K	1.2
32ET5	Beam Pwr. Pent.	7CV	32	0.1	12	6	0.6	150	-7.5	130		-	21.5K	5500	_	2.8K	1.2
3585	Beam Pwr. Amp.	7BZ	35	0.15	11	6.5	0.4	110	-7.5	110	3/7	412	_	5800	405	2.5K	1.5
50B5	Beam Pwr, Amp.	7BZ	50	0.15	13	6.5	0.5	110	-7.5	110	4/8.5	50²	14K	7500	495	2.5K	1.9
5686	Beam Pwr. Pent.	9G	6.3	0.35	6.4	8.5	0.11	250	-12.5	250	35	275	45K	3100	_	9K	2.7
5687	Medium-µ Dual Triode10	9H	12.6	0.45	47	0.6 ⁷	47 48	120 250	-2 -12.5		_	36 12.5	1.7K 3K	11K 5500	18.5 16.5	=	_
5722	Noise Generating Diode	5C8	6.3	1.5	_	2.2	_	200	_	_	_	35	_	_	_	_	_
5842/ 417A	High-µ Triode	97	6.3	0.3	9.0	1.8	0.55	150	62*	-	_	26	1.8K	24 K	43	_	_
5879	Sharp Cut-off Pent.	SAD	6.3	0.15	2.7	2.4	0.15	250	-3	100	0.4	1.8	2 meg.	1000	_	_	
6386	Medium-u Dual Triode10	8CJ	6.3	0.35	2	1.1	1.2	100	200°	-	_	9.6	4.25K	4000	17	_	_
6887	Dual Diode	6BT	6.3	0.2			x. peak in			e = 360 V	. Max. o		current ear				
6973	Pwr. Pentode	9EU	6.3	0.45	6	6	0.4	440	-15	300	-	_	73K	4800	_	_	_
7189	Pwr. Pentode	9CV	6.3	0.76	10.8	6.5	0.5	250	-7.3	250	5.5	48	40K	11.3K	_	_	_
7258	Sharp Cut-off Medium-µ Triode	9DA	12.6	0.195	7 2	2.4	0.4	330 330	-3	125	3.8	12 15	170K 4.7K	7800 4500	 21	_	_
7586	Medium-µ Triode	Fig. 85	6.3	0.135	4.2	1.6	2.2	75	0	_	_	10.5	3000	11.5K	35	_	_
7587	Sharp Cut-off Tet.	Fig. 89	6.3	0.15	6.5	1.4	.01	125	68*	50	2.7	10	200K	10.5K	_	_	_
7895	High-u Triode	Fig. 85	6.3	0.135	4.2	1.7	0.9	110	0	-		7	6800	9400	64	_	_
9001	Sharp Cut-off Pent.	78D	6.3	0.15	3.6	3	0.01	250	-3	100	0.7	2	1 meg.	1400	_	_	_
9002	U.h.f. Triode	7BS	6.3	0.15	1.2	1.1	1.4	250	-7	-	-	6.3	11.4K	2200	25	_	_
9003	Remote Cut-off Pent.	7BD	6.3	0.15	3.4	3	0.1	250	-3	100	2.7	6.7	700K	1800	_	_	_
9006	U.h.f. Diode	6BH	6.3	0.15				Max.	a.c. volta	ge = 270.	Max. d.	c. output	current =	5 ma.			

- † Controlled heater warm-up characteristic. Ω Oscillator gridleak or screen-dropping resistor ohms.

 ** Space-charge grid.

- Per Plate.
 Maximum-signal current for full-power output.
 Values are for two tubes in push-pull.
 Unless otherwise noted.
- 5 No signal plate ma.
 6 Effective plate-to-plate.
 7 Triode No. 1.
 2 Triode No. 2.
- 9 Oscillator grid current ma. 10 Values for each section. 11 Micromhos. 12 Through 33K.

TABLE II - METAL RECEIVING TUBES

Characteristics given in this table apply to all tubes having type numbers shown, including metal tubes, glass tubes with "G" suffix, and bantam tubes with "GT" suffix.

For "G" and "GT"-tubes not listed (not having metal counterparts), see Tables III, V, VI and VIII.

Туре	Name	Base		l. or ater	Ca	pacitan μμf.	ces	, ×		_	_		Ohms	COD- COD-	- F	Ohms	<u> </u>
,,,,,			٧.	Amp.	Cin	Cout	Cep	Plate Supply	Grid	Scree	Scree Ma.	Plate Ma.	Plate Res. (Trans	Amp. Facto	Res.	Watts
6A8	Pentagrid Conv.	8A	6.3	0.3				250	-3	100	2,7	3.5	360K	550	_	_	
940	rentagrio conv.	98	0.3	0.3	_	_	_		bb (Osc.)	250 V. tl	arough 20	K. Grid r	esistor (Os	c.) 50K. lb	, = 4 ma.	$I_{g1} = 0.4 \text{ r}$	na.
6AC7	Sharp Cut-off Pent.	8N	6.3	0.45	11	5	0.15	300	160°	150	2.5	10	1 meg.	9000	_		_
1852	Snarp Cut-on Pent.	914	0.3	0.45	11	3	0.13	300	160*	60Ks	2.5	10	1 meg.	9000	_	_	_
6AG7	Pwr. Amp. Pent.	8 Y	6.3	0.65	13	7.5	0.06	300	-3	150	7/9	30/31	130K	11K	_	10K	3
6B8	Dual-Diode — Pent.	8E	6.3	0.3	6	9	0.005	250	-3	125	2.3	10	600K	1325	_	_	_
6C5	Medium-u A ₁ Amp.	**	6.3	0.3	2	11	2	250	-8	_	_	8	10K	2000	20	— .	_
	Triode Biased Detector	6Q	0.3	0.3	3	11	2	250	-17		PI	ate currer	nt adjusted	to 0.2 ma	. with no	signal.	
6F5	High-µ Triode	5M	6.3	0.3	5.5	4	2.4	250	-2	_	_	0.9	66K	1500	100	_	_

TABLE II - METAL RECEIVING TUBES - Continued

Characteristics given in this table apply to all tubes having type numbers shown, including metal tubes, glass tubes with "G" suffix, and bantam tubes with "GT" suffix.

For "G" and "GT"tubes not listed (not having metal counterports), see Tables III, V, VI and VIII.

Туре	Name	Base		, or ater	Ca	pacitan μμf.	Ces	, v.		2	E		Plate Res. Ohms	Transcon- ductance ¹²	19	Ohms	. 3
			٧.	Amp.	Cin	Cout	Cap	Plate Supply	Grid	Screen Voits	Screen Ma.	Plate Ma.	Plate Res.	Trans	Amp. Factor ¹³	Load Res.	Watts Output
	A ₁ Amp. ^{1, 5}							250	-20	2010	_	31/34	2.6K	2600	6.8	4K	0.85
	AB ₂ Amp. ^{1, 6}]						350	730*	13211	-	50, 60	_	_		10K7	9
6F6		7\$	6.3	0.7	6.5	13	0.2	350 250	-38 -16.5	250	6/11	48, 92 34, 36	80K	2500	_	6K ⁷ 7K	13 3.2
oro	Pwr. Amp. Pent. A ₁ Amp.5	13	0.3	0.7	0.3	13	0,2	285	-20	285	7/13	38/40	78K	2500	-	7K	4,8
		1						375	-26	250	5/20	34/82	-	-	8211	10K ⁷	18.5
	AB ₂ Amp. ⁶							375	340°	250	8/18	54/77	_	_	9411	10K ⁷	19
6H6	Dual Diode	70	6.3	0.3	_		_			a.c. volta	ge per pl		r.m.s. Ma			ma. d.c.	,
615	Medium-µ Triode	6Q	6.3	0.3	3.4	3.6	3.4	250	-8 -3	100	0.5	9	7.7K	2600 1225	20		
6J7	Sharp Cut- A ₁ Amp. off Pent. Biased Detector	7R	6.3	0.3	7	12	0.005	250	-3 10K*	100	0.5		1 meg. al cathode		0.43 ma	0.5 me	
	Variable-µ R.f. Amp.		-	0.0	Ι,	10	0.005	250	-3	125	2.6	10.5	600K	1650	990	-	
6K7	Pent. Mixer	7R	6.3	0.3	7	12	0.005	250	-10	100			Osc.	peak vol	ts = 7		
6K8	Triode — Hexode	- 8K	6.3	0.3	_	_	_	250	-3	100	6	2.5	600K	350			
	Hexode Conv. Triode	- T	0.0	0.0				100	50K®	2010		3.8	1 70)sc.) = 0.1		1 14
	A ₁ Amp. ^{1, 5} A ₁ Amp. ⁵	-						250 250	-20 167*	250	5.4/7.2	40/44 75/78	1.7K	4700	1410	5K 2.5K	6.5
	Self Bias		-			1		300	218*	200	3/4.6	51/55	_		12.710	4.5K	6.5
	A ₁ Amp, ⁵	1				ļ		250	-14	250	5/7.3	72/79	22.5K	6000	1410	2.5K	6.5
	Fixed Bias							350	-18	250	2.5/7	54, 66	33K	5200	1810	4.2K	10.8
	A ₁ Amp.s	1						250	125*	250	10/15	120/130	_		35.611	5K7	13.8
6L6-GB2	Beam Self Bias	7AC	6.3	0.9	11.5	0.5	0.9	270 250	125* -16	270 250	11/17	134 145 120/140	24.55	5500s	28.211	5K ⁷	18,5
	Pwr. Amp. A ₁ Amp. ⁶ Fixed Bias							270	-17,5	270	11/17	134/155	23.55	57005	3511	5K ⁷	14.5
	AB, Amp. Self Bias	1				1		360	270°	270	5/17	88/100	-	3700	40.611	9K7	24.5
	AB ₁ Amp.6	1						360	-22.5	270	5/11	88 140		-	4511	3.8K7	18
	Fixed Bias							360	-22.5	270	5/15	88/132	_	_	4511	6.6K ⁷	26,5
	AB ₂ Amp.6			İ		1		360	-18	225	3.5/11	78 142	_	_	5211	6K3	31
	Fixed Bias	-	-	-	_	-		360 250	-22.5 -3	270 100	5/16 6.5	88/205 5.3	600K	1100	7211	3.8K ⁷	47
GL7	Pentagrid — A ₁ Amp. Mixer Amp. Mixer	71	6.3	0.3	_	-		250	-6	150	9.2	3.3	1 meg.	350	-1514	_	-
6N7GT	Class-B B Amp.9 Twin Triode A, Amp.15	8B	6.3	0.8	_	_	_	300 250	0 -5		_	35 70 6	11.3K	3100	8211	8K ⁷	10
607	Twin Triode A ₁ Amp. 15 Dual Diode — High-µ Triode	7 V 2	6.3	0.3	5	3.8	1.4	250	-3	_		1	58K	1200	70	 -	-
6R7	Dual Diode — Triode	7 V2	6.3	0.3	4.8	3.8	2.4	250	-9			9.5	8,5K	1900	16	10K	0,28
6SA7GT	Pentagrid Conv.	8R2	6.3	0.3	9.5	12	0.13	250	03	100	8	3.4	800K		Grid No. 1	resistor 20	K.
								100	-1	100	10.2	3.6	50 K	900	_	_	_
6SB7Y	Pentagrid Conv.	8R	6.3	0.3	9.6	9.2	0.13	250 250	-1 22K ⁸	100 12Ks	10	3.8 6.8/6.5	1 meg.	950 Spotion	in 88—108		<u> </u>
6SC7	High-µ Dual Triode5	85	6.3	0,3	2	3	2	250	-2 -2	1210	12/13	0.8/0.3	53K	1325	70	MIC. Selv	ICe.
6SF5	High-µ Triode	GAB ²	6.3	0.3	4	3,6	2.4	250	-2	_	-	0.9	66K	1500	100	_	_
6SF7	Diode — Variable-µ Pent.	7AZ	6.3	0,3	5.5	6	0.004	250	-1	100	3.3	12.4	700K	2050	-	_	_
6SG7	H.f. Amp. Pent.	8BK	6.3	0.3	8.5	7	0.003	250	-2.5	150	3.4	9.2	1 meg.	4000	_		_
6SH7	H.f. Amp. Pent.	8BK	6.3	0.3	8.5	7	0.003	250	-1	150	4.1	10.8	900K	4900	-		_
6SJ74 6SK7	Sharp Cut-off Pent. Variable-µ Pent.	8N 8N	6.3	0.3	6	7	0.005	250 250	-3 -3	100	0.8 2.6	9.2	1 meg. 800K	1650 2000	-		_
6SQ7GT	Variable-µ Pent. Dual Diode — High-µ Triode	80	6.3	0.3	3.2	3	1.6	250	-3	-		0.9	91 K	1100	100		-
6SR7	Dual Diode — Triode	80	6.3	0.3	3.6	2.8	2.4	250	-9	-	_	9.5	8.5K	1900	16	_	-
								180	-8.5	180	3/4	29 30	50K	3700	8,510	5.5K	2
	A ₁ Amp.s			0.15				250	-12.5	250	4.5 / 7	45/47	50K	4100	12.510	5K	4.5
6V6GTA	Beam Pwr. Amp.	7AC	6.3	0.45	10	11	0.3	315 250	13 15	225 250	2.2 6 5/13	34, 35 70/79	80K	3750 3750	3011	8.5K 10K ⁷	5.5
	AB ₁ Amp.s							285	-15 -19	285	4/13.5	70, 92	70K	3600	3811	8K7	14
1620	Sharp Cut-off Pent,	7R	6.3	0.3	7	12	0,005	250	-13	100	0.5	2	1 meg.	1225	-		
5693	Sharp Cut-off Pent.	8N	6.3	0.3	5.3	6.2	0.005	250	-3	100	0.85	3	1 meg.	1650	_	_	_
* Cath	node resistor-ohms.				4 Alen	type 6SJ	7¥			10	ec prid l	eak — So	rn ret	12 Min	cromhos.		

^{*} Cathode resistor-ohms.

TABLE III - 6.3-VOLT GLASS TUBES WITH OCTAL BASES

(For "G" and "GT"-type tubes not listed here, see equivalent type in Tables 11 and VIII; characteristics and connections will be similar)

Туре	Name	ate Dissi- stion Watts	Base		l. or eater	Ca	pacitan μμf.	ces	ا _۲ ۲.		£	£		Ohms	scon-	. =	Ohms	" Ħ
		Plate		٧.	Amp.	Cin	Cout	Cab	Plate Supp	Grid Bias	Scree	Scree Ma.	Plate Ma.	Plate Res.	Transco	Amp. Facto	Load Res.	Watts
6AL7GT	Electron-Ray Indicator	-	8CH	6.3	0.15	_	_	_									, outward v vith —6 vo	
6AQ7GT	Duat Diode — High-µ Triode	-	8CK	6.3	0.3	2.8	3.2	3	250	-2	_	_	2.3	44K	1600	70	_	-

Cardiobe resistor offinis.

Screen tied to plate.

No connection to Pin No. 1 for 6L6G, 6Q7G, 6RGT/G, 6S7G, 6S7GT/G and 6SF5-GT.

Grid bias — 2 wolts if separate oscillator excitation is used.

<sup>Also type 6SJ7Y,
Values are for single tube or section.
Values are for two tubes in push-pull.
Plate-to-plate value.</sup>

⁸ Osc. grid leak — Scrn. res. ⁹ Values for two units. ¹⁰ Peak a.f. grid voltage. ¹¹ Peak a.f. G-G voltage.

¹² Micromhos, 13 Unless otherwise noted. 14 G₃ voltage. 15 Units connected in parallel.

TABLE III - 6.3-VOLT GLASS TUBES WITH OCTAL BASES - Continued

(For "G" and "GT"-type tubes not listed here, see equivalent type in Tables II and VIII; characteristics and connections will be similar)

Туре	Name	Plate Dissi- pation Watts	Base		l. or eater	Ca	pacitan μμf:	ces	ly V.		5	5		Ohms	Transcon- ductance*		Ohms	. 5
		Plate		V.	Amp.	Cin	Cout	Cap	Plate Supply	Grid	Screen	Screen Ma.	Plate Ma.	Plate Res. (Tran	Amp. Factor	Load Res.	Watts
6AR6	Beam Pent.	-	6BQ	6.3	1.2	11	7	0.55	250	-22.5	250	5	77	21K	5400			-
6AR7GT	Duat Diode — Remote Pent.	-	7DE	6.3	0.3	5.5	7.5	0.003	250	-2	100	1,8	7	1.2 meg.	2500	_	_	_
6AS7GA	Low-µ Twin Triode — D.C. Amp. ¹	-	8 B D	6.3	2.5	6.5	2.2	7.5	135	250*	-	_	125	0.28K	7000	2		-
6AU5GT	Beam Pwr. Amp.3	10	6CK	6.3	1.25	11.3	7	0.5	115	-20	175	6.8	60	6K	5600			_
6AV5GA	Beam Pwr. Amp.3	11	6CK	6.3	1.2	14	7	0.5	250	-22.5	150	2.1	55	20K	5500		-	-
6BD5GT	Beam Pwr. Amp.3	-	6CK	6.3	0.9	-	-		310	- 200	310	_	90	_	-	-	-	-
6BG6GA	Beam Pwr, Amp.3	20	5BT	6.3	0.9	11	6	0.8	250	-15	250	4	75	25K	6000		-	_
6BL7GTA	Medium-µ Dual Triode1	-	88D	6.3	1.5	4,4	0.9	6	250	-9	-	-	40	2.15K	7000	15	_	
6BQ6GTB 6CU6	Beam Pwr. Amp. ³	11	6AM	6.3	1.2	15	7	0.6	250	-22.5	150	2.1	57	14.5K	5900	-	-	-
6BX7GT	Dual Triode ¹	l –	8BD	6.3	1.5	5	3.4	4.2	250	390*	_	_	42	1.3K	7600	10	_	_
6CB5A	Beam Pwr. Amp.3	26	8GD	6.3	2.5	22	10	0.4	175	-30	175	- 6	90	5K	8800	-	_	_
6CD6GA	Beam Pwr. Amp. ³	20	58T	6.3	2.5	24	9.5	0.8	175	-30	175	5.5	75	7.2K	7700	-	_	1 -
6C K4	Low-u Triode		8JB	6.3	1.25	8	1.8	6.5	550	- 26	-	-	55	1.0K	6500	6.7	_	-
6CL5	Beam Pwr, Amp.3	25	8GD	6.3	2.5	20	11.5	0.7	175	-40	175	7	90	6K	6500	_	_	_
6CU6	Beam Pwr, Amp.3	11	6AM	6.3	1.2	15	7	0.55	250	-22.5	150	2.1	55	20K	5500	_	_	_
6DG6GT	Beam Pwr. Amp.	-	75	6.3	1.2		-	_	200	180°	125	8.5	47	28K	8000	_	4K	3.8
6DN6	Beam Pwr. Pent. ³	15	5BT	6.3	2.5	22	11.5	0.8	125	18	125	6.3	70	4K	9000	-	_	-
	Dissimilar					2.2	0.7	4	350	-8	-		8	9K	2500	22	_	1 -
6DN7	Dual Triode	-	8BD	6.3	0.9	4.6		5.5	550	-9.5	-		68	2K	7700	15	_	_
6DQ5	Beam Pwr, Amp.3	24	8JC	6.3	2.5	23	11	0.5	175	- 25	125	5	110	5.5K	10.5K	_	-	-
6DQ6B	Beam Pwr. Amp. ³	18	6AM	63	1.2	15	7.	0.55	250	-22.5	150	2.4	75	20K	6600	_	_	_
6E5	Electron Ray - Triode	-	6R	6.3	0.3			_	250	-	-	_	-		3-	_	_	-
6EA7	Dissimilar — Dual Triode	-	8BD	6.3	1.05	2.2	0.6	4 8	350 550	-3 -25	=	-	1.5 95	34K 770	1900 6500	65 5	-	1
6EF6	Beam Pwr, Amp,5		75	6.3	0.9	11.5	9	0.8	250	- 18	250	2	50	-	5000	-	_	
6EY6	Beam Pwr. Pent.	-	7AC	6.3	0.68	8.5	7	0.7	350	- 17.5	300	3	44	60K	4400	_		_
6EZ5	Beam Pwr. Pent.	-	7AC	6.3	0.8	9	7	0.6	350	- 20	300	3.5	43	50K	4100	-		-
6FH6	Beam Pwr. Pent.	-	6AM	6.3	1.2	33	8	0.4	770	-22.5	220	1.7	75	12K	6000			_
6GW6	Beam Power Amp.3	17.5	GAM	6.3	1.2	17	7	0.5	250	-22.5	150	2.1	70	15K	7100			+ -
6K6GT	Pwr. Amp. Pent.		75	6.3	0.4	5.5	6	0.5	315	-21	250	4/9	25 28	110K	2100	_	9K	4.5
6S8GT	Triple-Diode — Triode	_	8CB	6.3	0.3	1.2	5	2	250	-2	-	-	-	91K	1100	100	-	- 1,0
6SD7GT	Semi-Remote Pent.	-	8N	6.3	0.3	9	7.5	0.0035	250	-2	125	3	9.5	700K	4250	-	_	+ -
6SL7GT	High-µ Dual Triode1	-	8BD	6.3	0.3	3.4	3.8	2.8	250	-2	-	_	2.3	44K	1600	70		-
6SN7GTB	Medium-µ Dual Triode1	-	8BD	6.3	0.6	3	1.2	4	250	-8		_	9	7.7K	2600	20		+ =
6W6GT	Beam Pwr. Amp.	_	75	6.3	1.2	15	9	0.5	200	180°	125	2/8.5	46/47	28K	8000	20	4K	3.8
6Y6GA	Beam Pwr. Amp.	_	75	6.3	1.25	15	1	0.7	200	-14	135	2.2 9	61/66	18.3K	7100		2.6K	6
1635	High-µ Dual Triode		8B	6.3	0.6	10	-	0.7	300	0	130		6.6 54	10.31	7100		12K²	10.4
6550	Power Pentode	35	7\$	6.3	1.6	14	12	0.85	400	- 16.5	225	18	105	27 K	9000		3K	20
7027	Beam Pwr. Amp,	30	8HY	6.3	0.9	10	7.5	1.5	450	- 30	350	19.2	194	6715	6000		6K2	50

^{*} Cathode resistor-ohms.

Per section.

TABLE IV - 6.3-VOLT LOCK-IN-BASE TUBES

For other lock-in-base types see Tables V, VI, and VII

Туре	Name	Base		l. or ater	Ca	pacitar μμ1.	ices	<u>, v</u>		<u> </u>	<u> </u>		Ohms	con-		Ohms	
1,700	, , , , , , , , , , , , , , , , , , ,		٧.	Amp.	Cin	Cout	Свр	Plate Supply	Grid Bias	Screen Volts	Scree Ma.	Plate Ma.	Plate Res.	Trans	Amp. Facto	Load Res.	Watts
7A8	Octode Conv.	80	6.3	0.15	7.5	9	0.15	250	-3	100	3.2	3	50K	And	de grid 2	50 Volts ma	X,1
7AH7	Remote Cut-off Pent.	8 V	6.3	0.15	7	6.5	0.005	250	250°	250	1.9	6.8	1 meg.	3300	_	_	
7AK7	Sharp Cut-off Pent.	8 V	6.3	0.8	12	9.5	0.7	150	0	90	21	41	11.5K	5500	_	_	
7B7	Remote Cut-off Pent.	8 V	6.3	0.15	5	6	0.007	250	-3	100	1.7	8.5	750K	1750	_	_	
707	Sharp Cut-off Pent.	8 V	6.3	0.15	5.5	6.5	0.007	250	-3	100	0.5	2	2 meg.	1300	_	_	_
7E7	Dual Diode — Pent.	8AE	6.3	0.3	4.6	5.5	0.005	250	330*	100	1.6	7.5	700K	1300	_	_	_
7F8	Medium-µ Dual Triode ²	8BW	6.3	0.3	2.8	1.4	1.2	250	500*	_	_	6	14,5K	3300	48	_	_
7 K 7	Dual Diode - High- Triode	8BF	6.3	0.3	2.4	2	1.7	250	-2	_		2.3	44K	1600	70	_	_

^{*} Cathode resistor-ohms.

TABLE V-1.S-VOLT FILAMENT BATTERY TUBES

Туре	Name	Base		l. or ater	Ca	pacitan μμf.	ces	ا۲ ۷.		5	5		Ohms	scon-		Ohms	. 5
,,,,,	, , , , , , , , , , , , , , , , , , ,		٧.	Amp.	Cin	Cout	Csp	Plate	Grid	Scree	Scree Ma.	Plate	Plate Res.	Tran	Amp. Facto	Load Res.	Watts
1A7GT	Pentagrid Cony.	72	1.4	0.05	7	10	0.5	90	0	45	0.7	0.6	600 K	Eы	Anode · g	rid = 90 Vo	its.
1H5GT	Diode High-µ Triode	5Z	1.4	0.05	1.1	4.6	1	90	0	I -	_	0.15	240K	275	65	_	$\overline{}$
1LN5	Sharp Cut-off Pent.	7AD	1.4	0.05	3	8	0.007	90	0	90	0.35	1.6	1.1 meg.	800		_	
1N5GT	R.f. Pentode	5 Y	1.4	0.05	3	10	0.007	90	0	90	0.3	1.2	1.5 meg.		_	_	_
3E6	Sharp Cut-off Pent.	7CJ	2.81	0.05	5.5	8	0.007	90	0	90	1.2	2.9	325K	1700	_	_	_

¹ Center-tap filament permits 1.4 volt operation.

² Plate-to-plate value.

³ Horz, Deflection Amp.

⁴ Micromhos. 5 Vert. Deflection Amp.

¹ Through 20K resistor.

² Each section.

³ Micromhos.

² Micromhos.

TABLE VI-HIGH-VOLTAGE HEATER TUBES

See also Table VIII.

Туре	Name	Base		. or ater	Ca	pacitar μμf.	ices	<u>, 7</u>		5	£		Ohms	scon- ance ²	_	Ohms	. 5
.,,,,	***************************************		٧.	Amp.	Cin	Cout	Cap	Plate Supply	Grid	Screen Voits	Scree Ma.	Plate Ma.	Plate Res.	Trans	Amp. Facto	Load Res.	Watts Output
12A6	Beam Pwr. Amp.	75	12.6	0.15	8	9	0,3	250	-12.5	250	3.5 5.5	30 32	70K	3000	_	7.5K	3.4
12EN6:	Beam Pwr. Amp.	75	12,6	0.6	14	8	0.65	200	-9.5	110	2.2	50	28K	8000	-	_	_
12L6GT:	Beam Pwr. Pent.	7\$	12.6	0.6	15	10	0.6	200	-7.5 180*	110 125	4, 10 2.2, 8.5	49 50 46/47	13K 28K	8000 8000		2K 4K	2.1 3.8
21E X6	Beam Pwr. Pent.	58 T	21.5	0.6	22	8.5	1.1	_	- 30	195	.3	67	8.5K	7700	_	_	_
50C6GA	Beam Pwr. Amp.	7\$	50	0.15	_		_	200	- 14	135	2.2/9	61/66	18.3K	7100	_	2.6K	6
117N7GT	Rect. — Beam Pwr. Amp.	VA8	117	0.09	_	_	-	100	-6	100	5	51	16K	7000	_	3K	1.2
5824	Beam Pwr. Pent.	7\$	25	0.3	_	_	_	135	-22	135	2.5/14.5	61,69	15K	5000	_	1.7K	4,3
6082	Low∙µ Dual Triode¹	88 D	26.5	0.6	6	2.2	8	135	250*	_	_	125	0.28K	7000	2	_	

TABLE VII - SPECIAL RECEIVING TUBES

Туре	Name	Base		l. or ater	Ca	pacitar μμf.	nces	٧.		5	ç		Ohms	con-		Load Res. Ohms	
туре	ivame		٧.	Amp.	Cin	Cout	Cep	Plate Supply	Grid	Screen	Screen Ma.	Plate Ma.	Plate Res. (Transcon- ductance ²	Amp. Factor	Load Res.	Watts Output
3Q5GT	Beam Pwr. Amp.	7AP	2.81	0.05	8	6.5	0.6	90	-4.5	90	1.3	9.5	90K	2200	_	8K	0.27
6810	Dual Triode Dual Diode	12BF	6.3	0.6			_	250	-8 Diode c	urrent for	continuo	10 ous opera	7.2K tion = 5 m	2500 a.	18		<u> </u>
6C10	Triple Triode	12BQ	6.3	0.6	1.6	0.3	1.7	250	-2	_	_	1.2	62.5K	1600	100	_	Γ-
6D10	Triple Triode	12BQ	6.3	0.45	2.2	0.5	1.5	125	-1	_	_	4.2	13.6K	4200	57	_	_
6F4	Acorn Triode	78 R	6.3	0.225	2	0.6	1.9	80	150°	_	-	13	2.9K	5800	17		T -
6FJ7	Dissimilar	12BM	6.3	0.9	2.2	0.48	3.8	250	-8	_	_	8	9K	2500	22.5		T -
6FJ/	Dual Triode	IZDM	0.3	0.5	4.0	0.54	5.0	250	- 9.5	_	_	41	2K	7700	15.4	_	_
	7-1-1-				1.9	1.8	1.3	250	-8.5	_		10.5	7.7K	2200	17	_	_
6K11	Triple Triode	12BY	6.3	0.6	1.8	0.7	1.3	250	-2.0		_	1.2	62.5K	1600	100	_	_
	Triode				1.8	1.8	1.3	250	-2.0	_	_	1.2	62.5K	1600	100		_
6L4	Acorn Triode	78R	6.3	0.225	1.8	0.5	1.6	80	150*	_		9.5	4.4K	6400	28	_	_
	Triple				1.9	1.7	1.8	150	0	_	_	22	7K	2500	18		_
6Q11	Triode	128 Y	6.3	0.6	1.8	0.6	2.0	250	-2			1.2	62.5K	1600	100		_
					1.8	1.7	2.0	250	-2		_	1.2	62.5K	1600	100	_	
7E5/1201	H.f. Triode	8BN	6.3	0.15	3,6	2.8	1.5	180	-3	_	_	5.5	12K	3000	36	_	_
954	Detector Amp. — A ₁ Amp.	588	6.3	0.15	3.4	3	0.007	250	-3	100	0,7	2	1 meg.	1400		_	<u> </u>
337	Pentode (Acorn) Detector	455	0.0	00				250	-6	100			to 0.1 ma.			250K	
955	Medium· Triode (Acorn)	5BC	6.3	0.15	1	0.6	1.4	250	-7	_		6.3	11.4K	2200	25		
			0.0		Ľ.	ļ.,,	-	90	-2.5	-	_	2.5	14.7K	1700	25	_	
956	Remote Cut-off A ₁ Amp.	588	6.3	0.15	3.4	3	0.007	250	-3	100	2.7	6.7	700K	1800			
	Pent. (Acorn) Mixer					-		250	-10	100			r peak volt			_	
958A	Medium-µ Triode (Acorn)	58D	1.25	0.1	0.6	0.8	2.6	135	-7.5	- 67.5	-	3	10K	1200	12	_	
959	Sharp Cut-off Pent. (Acorn)	5BE	1.25	0.05	1.8	2.5	0.015	135	-3	67.5	0.4	1.7	800K	725	-	_	
1609	Amplifier Pentode	58	1.1	0.25	7	7	1	135	-1.5	67.5	0.65	2.5	400K		-	_	-
6173	U.h.f. "Pencil" Diode	Fig. 34	6.3	0.135		late to K		050		verse =3			-50 Ma. I		utput - 5.	.5 ma.	
7077	Ceramic U.h.f. Triode		6.3	0.24	1.9	0.01	1.0	250	-5			6.4	8.9K	9000			_
7360	Beam Deflection	9KS	6.3	0.35	_	L -		-					a See Chap				
9004	U.h.f. Diode (Acorn)	4BJ	6.3	0.15		te to K							Max. d.c. o				
9005	U.h.f. Diode (Acorn)	5BG	3.6	0.165	į Pla	te to K -	= 0.8			Max, a	.c. voitag	e - 11/.	Max. d.c. o	output curi	rent – I m	ia.	

^{*} Cathode resistor-ohms

TABLE VIII-EQUIVALENT TUBES

The equivalent tubes listed in this table are, in general, designed for industrial, military and other special-purpose applications. These tubes are generally not directly interchangeable because of mechanical and/or electrical differences involving basing, heater characteristics, moximum ratings, interelectrode capacitances, etc.

Туре	Equivalent a	nd Table	Base	E†1	li²	Туре	Equivalent a	nd Table	Base	E _f 1	112
1K3	113	X	3C	1.25	0.2	6A6	6N7	- 11	78	6.3	0.8
1LH4	1H5GT	V	5AG	1.4	0.05	6A7	6A8	II I	7 C	6.3	0.3
3EA5	2EA5		7EW	2.9	0.45	6AE8	6K8	II I	8DU	6.3	0.3
3LF43	305GT	VII	688	2.8	0.05	6AU7;	12AU7A	l l	9A	3.15	0.6
3V43	304	1	6B X	2.8	0.05	6AX7;3	12AX7	1	9A	6.3	0.3
4DK6	3DK6	1	7CM	4.2	0.45	606	637	11	6F	6.3	0.3
5DJ4	5U4GB	X	8KS	5.0	3.0	6C S8;	6CR8	1	9FZ	6.3	0.45
5EA8	6EA8		9ÁE	4.7	0.6	6C U8	6AN8	1	9G M	6.3	0.45
5FV8	6FV8		9FA	4.7	0.6	6EW6	4EW6	1	7C M	6.3	0.4

^{*} Cathode resistor-ohms. ‡ Controlled heater warm-up characteristic.

¹ Each section.

² Micromhos.

¹ Center-tap filament permits 1.4-volt operation.

² Micromhos.

Type	Equivalent as	nd Table	Base	E _f 1	1,2	Туре	Equivalent an	d Table	Base	E _f 1	112
6SU7GTY	6SL7GT	III	8BD	6.3	0.3	19CL8A	6CL8A	1	9FX	18.9	0.15
6Y6GT	6Y6GA	- III	7\$	6,3	1.25	25BQ6GA	6BQ6GTB	III	6AM	25	0.3
7A4	6J5	TI	5AC	6,3	0.3	258Q6GT	6BO6GTB	III	6AM	25	0.3
A6	6H6	11	7AJ	6.3	0.15	25BQ6GTB:	6BQ6GTB	III	6AM	25	0.3
IA7	6SK7	H	87	6.3	0.3	25C5	50C5	VIII	7C V	25	0.3
184	6SF5	11	5AC	6.3	0.3	25C6GA	50C6GA	VIII	75	25	0.3
B5	6K6GT	101	GAE	6.3	0.4	25C A5	6CA5	1	7CV	25	0.3
7B6	6SQ7	- 11	8W	6.3	0.3	25CD6G	6CD6GA	in	5BT	25	0.6
788	6A8	11	8 X	6,3	0.3	25CD6GA:	6CD6GA	III	5BT	25	0.6
7C5	6V6	II	GAA	6.3	0.45	25CD6GB:	6CD6GA	111	5BT	25	0.6
E Y61	6EY6	III	7AC	7.2	0,6	25CU6	6CU6	III	6AM	25	0.3
IF7	6SL7GT	111	8AC	6.3	0,3	25DN6;	6DN6	111	5BT	25	0.6
1H7	6SG7	- II	87	6.3	0.3	25E C6:	25CD6GB	AIII	5BT	25	0.6
N7	6SN7GT	HI	8AC	6,3	0.6	25EH5	6EH5	1	7CV	25	0.3
107	6SA7	II	8AL	6.3	0.3	25L6GT	12L6GT	VI.	75	25	0.3
0EB8±	6EB8	1	9DX	10.5	0.45	25SA7GT	6SA7GT	ii ii	8AD	-	- 0.3
2A8GT	6A8	il	8A	12.6	0.15	25W6GT	6W6GT	- iii	75	25	0.3
2AL5	6AL5	T	6BT	12.6	0.15	35C5	35B5	- iii	7C V	35	0.15
2AT6	6AT6		7BT	12.6	0.15	35L6GT	35B5	-i	75	35	0.15
2AUG	6AU6A	Ť	7BK	12.6	0,15	41	6K6GT	ill	6B	6.3	0.4
2AV5GA:	6AV5GT	111	6C K	12.6	0.6	42	6F6	ii ii	68	6.3	0.7
2AV6	6AV6	- iii	7BT	12.6	0.15	50A5	12L6GT	VI	GAA	50	0.15
284	12B4A±3	i	9AG	12.6	0.3	50BK5	6BK5		980	50	0.15
2BA6	6BA6		78 K	12.6	0.15	50C5	50B5		7C V	50	0.15
28A7	6BA7	-i	8CT	12.6	0.15	50C6G	50C6GA	VI	75	50	0.15
28D6	6BD6	-i	78 K	12.6	0.15	50L6GT	12L6GT	VI	7AC	50	
BEG	6BE6	-	7CH	12.6	0.15	75	6SQ7	NI NI	6G	6,3	0.15
BF6	6BF6	1	78T	12.6	0.15	78	65Q7 6K7	- 11	6F		0.3
18K51	6BK5	<u>'</u>	9BQ	12.6	0.15	1221	617	- 11	6F	6.3	0.3
BK6	6BK6	- 	7BT	12.6	0.0	1223	637	11	7Ř	6.3	0.3
BN6	6BN6	- 	7DE	12.6	0.15	1631	6L6GB	11	7AC	6.3 12.6	0.3
BOGGAT	6B06GTB	111	6AM	12.6	0.13	1632	12L6GT				
BOSTI	6B06GTB	in	6AM	12.6	0.6	1634	6SC7	VI II	7S 8S	12.6 12.6	0.6
BOGTBI	6BQ6GTB	111	6AM	12,6	0.6	5591	6AK5				0.15
BT6	6BT6		7BT	12,6	0.15	5654	6AK5	1	78D	6.3	0.15
BUG	6BU6	- i -	78T	12.6	0.15	5670	2C51		8CJ	6.3	0.175
BW4	6BW4	X	9DJ	12.6	0.45	5679	6H6	11	7CX		
BY7	12BY7At3	î	9BF	12.6	0.43	5691	6SL7GT	111	8BD	6.3	0.15
BZ6t	6BZ6	- 	7CM	12.6	0.15	5692	6SN7GT	111	88D	6.3	0.6
C5t	50B5	i	7CV	12.6	0.13	5725	6AS6	111	7C M		0.6
C8	6B8	ii	8E	12,6	0.15	5726	6AL5		6BT	6.3	0.175
CA51	6CA5	- "	7CV	12.6	0.13	5749	6BA6	+	78K	6.3	0.3
CM6	6CM6	- i - 	9CK	12.6	0.225	5750	6BE6		76H	6.3	0.3
CR6	6CR6	-	7EA	12.6	0.223	57513	12AX7			6.3	0.3
CS5t	6CS5	i	9CK	12.6	0.13	5814A3	12SN7GT	VIII	9A	12.6	0.175
CS6	6CS6	- i - 	7CH	12.6	0.0	5871	6V6GTA		9A 7AC	12.6	0.175
CU5±	6CU5	- i	7CV	12.6	0.13	5881	6L6GB	11	7AC	6.3	0.9
CUG	6CU6	111	6A M	12.6	0.6	5910	104	1		6.3	0.9
DB5t	6DB5	1111	962	12.6	0.6	5915	6BY6	-	GAR 7CH	6.3	0.05
DF73	12AX7 ·	i	9A	12.6	0.15	59633	12AU7A		9A		0.3
DQ6AI	6DQ6B	in	6AM	12.6	0.13	5964	6J6A	- !		12.6	0.15
DT5	6DT5	-;;;	9HN	12.6	0.6	5965 ³	12AV7		7BF	6.3	0.45
DT8	6DT8	i	9DE	12.6	0.15	6046	12L6GT	VI VI	9A 7AC	12.6	0.225
DW51	6DW5	- 	9CK	12.6	0.13	60573		A1		25	0.3
EF61	6EF6	ill	7S	12.6	0.6	6057	12AX7 6AL5	+	9A 6BT	12.6	0.15
G4	6,15	111	6BG	12.6	0.45	6059	6J7	11	9BC	6.3	0.3
H6	6H6	11	70	12.6	0.15	60603	12AT7	-		6.3	0.15
ISGT	6,15	11	6Q	12.6	0.15	6060°	6V6GTA	 	9A	12.6	0.15
17GT	637	- 11	7R	12.6	0.15	6064	6AM6	-	9AM 7DB	6.3	0.45
K7GT	6K7	11	7R	12.6	0.15	6065	6BH6	1	7DB	6.3	
K8	6K8	11	8 K	12,6	0.15	6068	6AT6			6.3	0.2
SEGT	6S8GT	111	8CB	12.6	0.15	50673	12AU7A		7BT	6.3	0.3
	6SA7	111	8R					111	9A	12.6	0.15
SA7 SC7	6SC7	11	85	12.6	0.15	6080 6101	6AS7G 6J6A	111	8BD	6.3	2.5
SF5	6SF5	11	6AB	12.6	0.15	6132		1	7BF	6.3	0.45
5F7	6SF7	- "	7AZ	12.6	0.15	6136	6CH6 6AU6A	1	9BA	6,3	0.75
SG7	6SG7	11	8BK	12.6	0.15	6186	6AG5	- ! - !	7BK	6.3	0.3
H7	6SH7	11	8BK	12.6	0.15			1	7BD	6.3	0.3
517	6SJ7	11	8N	12.6	0.15	6201 ³ 6265	12AT7 6BH6	1	9A	12,6	0.15
S K7	6SK7	H	BN	12.6	0.15	6350 ³	12BH7A	1	7CM	6.3	0.175
L7GT	6SL7GT	111	8BD	12.6				-	9CZ	12.6	0.3
N7GT	6SN7GTB	101	88D	12.6	0.15	6485	6AH6	<u> </u>	7BK	6.3	0.45
	6SN/GTB				0.3	6627	DB2	IX	5B0		-
N7GTA		111	8BD	12.6	0.3	6660	6BA6	1	7CC	6.3	0.3
07	6SQ7	11	8Q	12.6	0.15	6661	6BH6	1	7C M	6.3	0.15
R7	6SR7	II T	8Q	12.6	0.15	6662	6BJ6A	1	7CM	6.3	0.15
WEGT:	6W6GT	111 ,	7\$	12.6	0.6	6663	6AL5	1	6BT	6.3	0.3
17	6SK7	11	87	12.6	0.15	6664	6AB4	1	5CE	6.3	0.15
NF7	7AF7	IV	BAC	12.6	0.15	6669	AQ5A	1	7BZ	6.3	0.45
B6	6SQ7	II	8W	12.6	0.15	6676	6CB6A	1	7CM	6.3	0.3
F7	6SL7GT	111	8AC	12.6	0.15	6677	CL6	T	9B V	6.3	0.65
N7 Q7	6SN7GTB	111	8AC	12,6	0.6	6678	6U8A‡	1	9AE	6.3	0.45
	6SA7	H I	BAL	12.6	0.15	66793	12AT7	1	9 A	12.6	0.15

TABLE VIII - EQUIVALENT TUBES - Continued

Туре	Equivalent a	nd Table	Base	Er1	le ²	Туре	Equivalent as	nd Table	Base	Er1	l _f 2
6680³	12AU7A		9A	12.6	0.15	7060	6AU8	1	9D X	13.5	0.280
66813	12AX7	i	9A	12,6	0.15	7061	12AB5	1	9EU	13.5	0.210
6829³	5965	VIII	9A	12.6	0,225	7137	6J4	T	78Q	6.3	0.4
6897	2C39	XI	_	6.3	1.05	7167	6CV5	1	7EW	13.5	0.09
7000	617	- 11	7R	6.3	0.3	7408	6V6-GTA	181	7AC	6.3	0.45
70253	12AX7	VII	9A	12.6	0,15	7543	6AU6	1	7BK	6.3	0.3
7054	12BY7	T	9BF	13.5	0.275	7700	6J7	- II	6F	6.3	0.3
7055	6AL5		6BT	13.5	0.155	EEC813	12AT7		9A	12.6	0.15
7056	6CB6		7CM	13.5	0.150	EEC823	12AU7A	1	9A	12.6	0.15
7057	6BZ7	1	9AJ	13.5	0.180	EEC833	12AX7	- 1	9A	12.6	0.15
7058	12AX7	1	9A	1.35	0.155	KT-664	6L6GB	- 11	7AC	6.3	1.27
7059	6U8		9AE	13.5	0.195	XXD	7AF7	IV	8AC	12.6	0.15

[†] Controlled heater warm-up characteristics.

Filament or heater voltage.

Filament or heater current.

TABLE IX-CONTROL AND REGULATOR TUBES

•	Name	Base	Cathode	Fil. or	Heater	Peak Anode	Max. Anode	Minimum Supply	Oper- ating	Oper- ating	Grid	Tube Voltage
Туре	Name	Dase	Cathode	Voits	Amp.	Voltage	Ma.	Voltage	Voltage	Ma.	Resistor	Drop
0A2 6073	Voltage Regulator	580	Cold	_	_	-	-	185	150	5–30	_	_
0A3/VR75	Voltage Regulator	4AJ	Cold	_	_	_	_	105	75	5-40		_
0A4G 1267	Gas Triode Starter-Anode Type	4V 4V	Cold	_	-	1	With 105-120 peak r.f. vol)-volt a.c. and age 55. Peak	de suppiy, p	eak starter-and 100. Average d.o	de a.c. voltage : . ma = 25.	is 70
0A5	Gas Pentode	Fig. 19	Cold	_	_		Plat	e -750 V., Se	creen -90 V	., Grid +3 V., P	ulse85 V.	
0B2 6074	Voltage Regulator	580	Cold	_	-	_	_	133	108	5–30	_	_
0B3/VR90	Voltage Regulator	4AJ	Cold	_	_	_	_	125	90	5-40	_	_
0C2	Voltage Regulator	580	Cold	_	_	_	_	105	75	5-30		_
0C3/VR105	Voltage Regulator	4AJ	Cold	_	_	_	_	135	105	5-40	_	_
0D3/VR150	Voltage Regulator	4AJ	Cold	_			_	185	150	5-40		_
2D21	Grid-Controlled Rectifier Relay Tube	7BN	Htr.	6.3	0.6	650 400	500	_	650	100	0.1-10 ⁴ 1.0 ⁴	8
			194	6.3	0.25	100	Ep = 3	350; Grid volt	s = -50; A	vg. Ma. = 25;		0;
6D4	Control Tube	5AY	Htr.	6.3	0.25				Voltage dr	op = 16.		
90C1	Voltage Regulator	580	Cold	_	_	_	_	125	90	1-40	_	_
B84	Gas Triode Grid Type	60	Htr.	6.3	0.6	300	300	_	_	2	25000	_
						350	300	_	_	75	25000	
967	Grid-Controlled Rectifier	3G	Fil.	2.5	5.0	2500	500	-52	_	_	_	10-24
1265	Voltage Regulator	4AJ	Cold	_		_		130	90	5–30		_
1266	Voltage Regulator	4AJ	Cold	_	_	_			70	5-40		_
1267	Relay Tube	47	Cold	-				Cha	racteristics	same as OA4G		
2050	Grid-Controlled Rectifier	8BA	Htr.	6.3	0.6	650	500			100	0.1-104	8
5651	Voltage Regulator	5BO	Cold	_	_	115		115	87	1.5-3.5		_
5662	Thyratron — Fuse	Fig. 79	Htr.	6.3	1.5	2003				mp., 60 cycle, h		50 V.
5696	Relay Service	7BN	Htr.	6.3	0.15	500 ³		10	00 ma. peak	current; 25-ma.	average.	
5727	Gas Thyratron	7BN	Htr.	6.3	0.6	650			_	_		
5823	Relay or Trigger	4CK	Cold	_	_		Max.			ak Ma. 🗕 100; A	lvg. Ma. – 25.	
5962	Voltage Regulator	2AG	Cold	_	_	_		730	700	5/555	_	_
5998	Series Regulator	8BD	Htr.	6.3	2.4	250	125	_	110	100	3504	_
6308	Voltage Regulator	8EX	Cold	_			3.5	115	87	_	_	_
6354	Voltage Regulator	Fig. 12	Cold	_	_		_	180	150	5–15	_	_
K Y21	Grid-Controlled Rectifier	_	Fil.	2.5	10.0	_	_	_	3000	500	_	_
RK61	Radio-Controlled Relay		Fil.	1.4	0.05	45	1.5	30	_	0.5-1.5	34	30

¹ No base. Tinned wire leads. 2 At 1000 anode volts.

TABLE X-RECTIFIERS-RECEIVING AND TRANSMITTING See Also Table IX -- Controls and Regulator Tubes

_		P	Cathode	Fil. or	Heater	Max. A.C.	O.C. Output	Max. Inverse	Peak Plate	Туре
Туре	Name	Base	Cathode	Volts	Amp.	Voltage Per Plate	Current Ma.	Peak Voltage	Current Ma.	Type
0Z4-G	Full-Wave Rectifier	4R	Cold	_	-	300	75	1000	200	GAS
1G3-GT/ 1B3-GT	Half-Wave Rectifier	3C	Fil.	1.25	0.2	_	1.0	33000	30	HV
1 K3/1J3	Half-Wave Rectifier	3C	Fil,	1.25	0.2	_	0.5	26000	50	HV
1 V2	Half-Wave Rectifier	90	Fil.	0.625	0.3	_	0.5	7500	10	HV
2B25	Half-Wave Rectifier	3 T	Fil.	1.4	0.11	1000	1.5	_	9	HV
2 X2 · A	Half-Wave Rectifier	4AB	Htr.	2.5	1.75	4500	7.5		_	HV
2 Y2	Half-Wave Rectifier	4AB	Fil.	2.5	1,75	4400	5.0	_	_	HV
2Z2/G84	Half-Wave Rectifier	4B	Fil.	2.5	1.5	350	50	_	_	HV
3B24	Half-Wave Rectifier	F1- 40	Fa	5.0	3.0	_	60	20000	300	HV
3024	maii-wave Rectifier	Fig. 49	Fil.	2.55	3.0		30	20000	150	nv

³ Heater center-tapped for operation at half voltage shown.
4 British version of 6L6.

³ Peak inverse voltage. ⁴ Megohms.

⁵ Values in μ amperes. ⁶ Cathode resistor-ohms.

TABLE X - RECTIFIERS - RECEIVING AND TRANSMITTING - Continued See Also Table IX - Controls and Regulator Tubes

_				Fil. or	Heater	Max. A.C.	D.C. Output	Max. Inverse	Peak Plate	
Туре	Name	Base	Cathode	Volts	Amp.	Voltage Per Plate	Current Ma.	Peak Voltage	Current Ma.	Туре
B28	Half-Wave Rectifier	4P	Fil.	2.5	5.0	_	250	10000	1000	GA
AT4	Full-Wave Rectifier	5L	Htr.	5.0	2.25	550	800	1550	-	HV
						300³	350 ³			
5AU4	Full-Wave Rectifier	5T	Fil.	5.0	4.5	4003	3253	1400	1075	HV
						5004	3254	1	1	
5AW4	Full-Wave Rectifier	5T	Fil.	5.0	4.0	4503	2503	1550	750	HV
	T GIT-WAYE RECEIPED		111.	5.0	4.0	5504	2504	1550	750	п
5R4GY	Full-Wave Rectifier	5T	Fil.	5.0	2.0	9003	1503	2800	650	HV
5RGYA						9504	1754		950	
5046	Full-Wave Rectifier	5T	Fil.	5.0	3.0	2003		me as Type 5Z3		HV
5U4GA	Full-Wave Rectifier	5T	Fil.	5.0	3.0	300 ³ 450 ³	275 ³ 250 ³	1550		l
7U46A	ruii-wave rectifier	31	rii,	5.0	3.0	5504	2504	1550	900	HV
		_	-	-	-	3003	3003	-	-	-
5U4GB	Full-Wave Rectifier	5T	Fil.	5.0	3.0	4503	2753	1550	1000	HV
5AS4A	I UII-MAYE NECUNEI	, ,,	""	3.0	3.0	5504	2754	1330	1000	l nv
		+	-	-	+	425 ³				-
5 V 3	Full-Wave Rectifier	5T	Htr.	5.0	3.8	5004	350	1400	1200	HV
5V4GA	Full-Wave Rectifier	5L	Htr.	5.0	2.0	3753	175	1400	525	HV
5X4G	Full-Wave Rectifier	50	Fil.	5.0	3.0	1		me as Type 5Z3	020	HV
5Y3-G-GT	Full-Wave Rectifier	5T	Fil.	5.0	2.0			me as Type 80		HV
5Y4-G-GT	Full-Wave Rectifier	5Q	Fil.	5.0	2.0			ame as Type 80		HV
5Z3	Full-Wave Rectifier	4C	Fil.	5.0	3,0	500	250	1400	_	HV
5Z4	Full-Wave Rectifier	5L	Htr.	5.0	2.0	400	125	1100		HV
BAF3	Half-Wave Rectifier	9CB	Htr.	6.3	1.2	_	185	4500	750	HV
SAV4	Full-Wave Rectifier	5BS	Htr.	6.3	0.95	_	90	1250	250	HV
BAX5GT	Full-Wave Rectifier	65	Htr.	6.3	1.2	450	125	1250	375	HV
BBW4	Full-Wave Rectifier	9DJ	Htr.	6.3	0.9	450	100	1275	350	HV
6B X4	Full-Wave Rectifier	5BS	Htr.	6.3	0.6	_	90	1350	270	HV
6B Y5G	Full-Wave Rectifier	6C N	Htr.	6.3	1.6	3753	175	1400	525	HV
BCA4	Full-Wave Rectifier	9M	Htr.	6.3	1.0	3503	150	1000	450	HV
SDA4A	Half-Wave Diode	406	Htr.	6.3	1.2	_	155	4400	900	HV
BDE4	Half-Wave Rectifier	4C G	Fil.	6.3	1.6	_	175	5000	1100	HV
BU4GT	Half-Wave Rectifier	406	Htr.	6.3	1.2	_	138	1375	660	HV
8 V 4	Full-Wave Rectifier	9 M	Htr.	63.	0.6	350	90	_		HV
6 X4/6063	Full-Wave Rectifier	7CF	Htr.	6.3	0.3	3253	70	1250	210	HV
8X5GT		65			ļ	4504	1	1230	210	Π¥
BZ3	Half-Wave Rectifier	4G	Fil.	6.3	0.3	350	50	_	_	HV
12DF5	Full-Wave Rectifier	985	Htr.	6.3	0.9	450	100	1275	350	HV
12013	rull-wave necunel	353	mu.	12.6	0.45	1				пу
12 X4	Full-Wave Rectifier	5BS	Htr.	12.6	0.3	6503	70	1250	210	HV
						9004	70	1250	210	
25Z5	Rectifier-Doubler	6E	Htr.	25	0.3	125	100	_	500	HV
35W4	Half-Wave Rectifier	5BQ	Htr.	351	0.15	125	60	330	600	HV
15Z4GT	Half-Wave Rectifier	5AA	Htr.	35	0.15	250	100	700	600	HV
35Z5G	Half-Wave Rectifier	6AD	Htr.	351	0.15	125	60	-		HV
6AM3	Half-Wave Rectifier	5BQ	Htr.	36	0.1	117	75	365	530	HV
ODC4	Half-Wave Rectifier	5BQ	Htr.	50 50	0.15	117	100	330	720	HV
TDBYOG	Full-Wave Rectifier	70	Htr.	50	0.15	125	85			HV
10	Full-Wave Rectifier	4C	Fil.	5.0	2.0	350 ³ 500 ⁴	125 125	1400	375	HV
3	Full-Wave Rectifier	4C	Fil.	5.0	3.0	500	250	1400	800	MV
3-V	Full-Wave Rectifier	4AD	Htr.	5.0	2.0	400	200	1100		HV
17N7GT	Rectifier-Tetrode	8AV	Htr.	117	0.09	117	75	350	450	HV
1723	Half-Wave Rectifier	4CB	Htr.	117	0.04	117	90	300		HV
16	Half-Wave Rectifier	4P	Fil.	2.5	2.0	2200	125	7500	500	MV
36	Half-Wave Rectifier	4P	Htr.	2.5	5.0	_	_	5000	1000	HV
86-A-AX	Half-Wave Rectifier	4P	Fil.	2.5	5.0	3500	250	10000	1000	MV
68 B	Half-Wave Rectifier	4P	Fit.	5.0	5.0	_	_	8500	1000	MV
66 Jr.	Half-Wave Rectifier	4B	Fil.	2.5	2.5	1250	250²			MV
72A/872	Half-Wave Rectifier	4AT	Fil.	5.0	7.5	_	1250	10000	5000	MV

¹ Tapped for pilot lamps.
2 Per pair with choke input.

TABLE XI-TRIODE TRANSMITTING TUBES

		Ma	ximum	Rating	•		Cati	node	Caj	pacitar	ices					Typical	Operatio	n		
Туре	Plate Dissi- pation Watts	Plate Voltage	Plate Current Ma.	D.C. Grid Current Ma.	Freq. Mc. Full Ratings	Amplification Factor	Voits	Amperes	Cin μμf.	C _{sp} μμί.	Cout μμf.	Base	Class of Service ¹	Plate Voltage	Grid Voltage	Plate Current Ma.	D.C. Grid Current Ma.	Approx. Driving Power Watts	P-to-P Load Ohms	Approx. Output Power Watts
958-A	0.6	135	7	1.0	500	12	1.25	0.1	0.6	2.6	0.8	5BD	C-T-O	135	-20	7	1.0	0.035		0.6
BJ6A12	1.5	300	30	16	250	32	6.3	0.45	2.2	1.6	0.4	7BF	C-T	150	- 10	30	1.6	0.035		3.5

³ Capacitor input, 4 Choke input,

⁵ Using only one-half of filament.

		Max	imum l	Ratine		Ť	Cath	ode	Cap	acitan	ces				1	Typical (Operatio	n		
Туре	Plate Dissipation Watts	Plate Voltage	Plate Current Ma.	D.C. Grid Current Ma.	Freq. Mc. Full Ratings	Amplification Factor	Volts	Amperes	Cin µµf.	C _s , μμ1.	Cout μμf.	Base	Class of Service ¹	Plate Voltage	Grid	Plate Current Ma.	D.C. Grid Current Ma.	Approx. Driving Power Watts	P-to-P Load Ohms	Approx, Output Power Watts
9002	1.6	250	8	2.0	250	25	6.3	0.15	1.2	1.4	1.1	7BS	C-T-O	180	- 35	7	1.5			0.5
955	1.6	180	- 8	2.0	250	25	6.3	0.15	1.0	1.4	0.6	5BC	C-T-0	180 180	-35 -30	12	1.5 2.0	0.2		1.43
HY114B	1.8	180	12	3.0	300	13	1.4	0.155	1.0	1.3	1.0	2T	C-P	180	-35 -15	12	2.5	0.3		1,43
6F4	2.0	150	20	8.0	500	17	6.3	0.225	2.0	1.9	0.6	7BR	C-T-O	150	550* 20004	20	7.5	0.2	_	1.8
12AU7A ²	2.766	350	126	3.56	54	18	6.3	0.3	1.5	1.5	0.5	9A	C-T-O	350	-100	24	7		_	6.0 1.25
6026	3.0	150	30	10	400	24	6.3	0.2	2.2	1.3	0.38	Fig. 16	C·T·O	135 300	1300 ⁴ 35	20	9.5 2.0	0.4		4.03
H Y615 H Y-E1148	3.5	300	20	4.0	300	20	6.3	0.175	1.4	1.6	1.2	Fig. 71	C-P-	300	-35	20	3.0	0.4		3,53
6C4	5.0	350	25	8.0	54	18	6.3	0.15	1.8	1.6	1.3	6BG	C-T-O	300	-27	25	7.0	0.35	_	5.5
2C36	5.0	15003		-	1200	25	6.3	0.4	1.4	2.4	0.36	Fig. 21	C-T-016	1000s	0	9005	·-	_		2005
2C37	5	350	_	_	3300	25	6.3	0.4	1.4	1.85	0.02	Fig. 21	C-T-012	150	30004	15	3.6		-	0.5
5764	5	1500s	11.5	_	3300	25	6.3	0.4	1.4	1.85	0.02	Fig. 21	C-T-016	10005	0	1300s	-			2005
5675	5	165	30	8	3000	20	6.3	0.135	2.3	1.3	0.09	Fig. 21	G-G-O	120 350	-8 -100	25 60	10			0.05
6N7GT2	5.54	350	306	5.06	10 500	35	6.3	0.8	2.1	1.3	0.05	6B Fig. 11	C-T-011	250	-100	20	0.3	- -		0.075
2C40	6.5	500	25	-		36	6.3					1	C-T	350	-33	35	13	2.4	_	6.5
5893	8.0	400	40	13	1000	27	6.0	0.33	2.5	1.75	0.07	Fig. 21	C-P	300	-45	30	12	2.0	_	6.5
	-					4-				2.2	0.02		C-T	350	-50	35	15	_	_	_
GL-6442 2C34/	8.0	350	35	15	2500	47	6.3	0.9	5.0	2.3	0.03	-	C-P	275	-50	35	15 20		_	16
RK342	10	300	80	20	250	13	6.3	0.8	3.4	2.4	0.5	Fig. 70	C·T·O	300	-36	80		1.8	_	l _
2C43	12	500	40	-	1250	48	6.3	0.9	2.9	1.7	0.05	Fig. 11	C·T·O	470		387	-		_	97
6263	13	400	55	25	500	27	6.3	0.28	2.9	1.7	0.08	_	C-T	350	-58	40	15 12	3 2.4		10
									2.95	1.75	0.07		C-P C-T	320 350	-52 45	40	15	3	-	8
6264	13	400	50	25	500	40	6.3	0.28	2.90				C-T	450	-140	90	20	5.2	_	26
HY75A	15	450	90	25	175	9.6	6.3	2.6	1.8	2.6	1.0	2T	C-P	400	-140	90	20	5.2	_	21
			_	-						_			C-T	600	-150	65	15	4.0	_	25
801-A/801	20	600	70	15	60	8.0	7.5	1.25	4.5	6.0	1.5	4D	C-P	500	-190	55	15	4.5	_	18
		1											B ⁷	600	-75	130	320°	3.08	10K	45
T20	20	750	85	25	60	20	7.5	1.75	4.9	5.1	0.7	36	C-T	750 750	-85 -140	85 70	18 15	3.6		38
	20	7.50						-	-	-			C-P C-T	750	-140	85	28	3.75	-	44
-700	20	750	95	30	60	62	7.5	1.75	5.3	5.0	0.6	36	C-P	750	-100	70	23	4.8	_	38
TZ20	20	/50	85	30	00	02	7.5	1.75	0.0	0.0	0.0	"-	B ⁷	800	0	40/136	160°	1.88	12K	70
15E18	20	_	_	-	600	25	5.5	4.2	1.4	1.15		Fig. 51		2000	-130	63	18	4.0		100
											0.3		C·T·O	1500	-95	67	13	2.2		75
25T 3-25A3	25	2000	75	25	60	24	6.3	3.0	2.7	1.5	0.0	3G	B ⁷	2000	_70 _80	72 16/80	9 270°	1.3 0.7 ⁸	55.5K	110
	-			-	100			-	2.1	1.8	0.1	Fig. 31	D.	2000	-170	63	17	4.5	-	100
3 C 2 8 1 8					60	1			2.5	1.7	0.4	3G	C-T-O	1500	-110	67	15	3.1		75
3C3418 3-25D3	25	2000	75	25		23	6.3	3.0	2.0	1.6	0.2			1000	-80	72	15	2.6		47
24G					150				1.7	1.5	0.3	2D		2000	-85	16/80	290°	1.18	55.5K	110
	25	2000	75								Τ		C-T	2000	-130	63	18	4	_	100
3C24	17	1600	60	713	60	24	6.3	3.0	1.7	1.6	0.2	2D	C-P	1600	-170 -42	53 24/130	2709	3.1	21.4K	68 112
	25	2000	75							-	-	-	AB ₂ ⁷ C-T	1250	-140	56	18	4.0	21.4K	90
H K24	25	2000	75	30	60	25	6.3	3.0	2.5	1.7	0.4	36	C-P	1500	-145	50	25	5.5	_	60
	30		65	-	-		-			_	_		G-M-A	1000	-135	50	4	3.5	_	20
8025	20	1000	65	20	500	18	6.3	1.92	2.7	2.8	0.35	4AQ	C-P	800	-105	40	10.5	1.4		22
	30	1	80	20									C-T	1000	-90	50	14	1.6		35
HY31Z²	30	500	150	30	60	45	6.3	3.5	5.0	5.5	1.9	Fig. 60	C-T	500	-45 -100	150 150	25 30	2.5 3.5	-	56 45
HY1231Z2	30	300	150				12.6	1.7	-		-	<u> </u>	C-P C-T	400 450	-100	80	12	3.3		7.5
316A VT-191	30	450	80	12	500	6.5	2.0	3.65	1.2	1.6	0.8	-	C-P	400	+=	80	12	_	_	6.5
	+			1	_								C-T	1000	-75	100	25	3.8	_	75
809	30	1000	125	-	60	50	6.3	2.5	5.7	6.7	0.9	36	C-P B ⁷	750	-60	100 40/200	32 1559	4.3 2.7*	11.6K	55 145
		-	-	+		1							C-T-O	1000	90	100	20	3.1		75
1623	30	1000	100	25	60	20	6.3	2.5	5.7	6.7	0.9	36	C-P	750	-125	100	20	4.0	-	55
										1	-	-	B7	1000	-40 -140	30/200 150	230°	9.0	12K	145
T40	40	1500	150	40	60	25	7.5	2.5	4.5	4.8	0.8	36	C-T-O	1250	-115	115	20	5.25	+=	104
	<u> </u>	-	-	-	-	-		-	-	+	+	 	C·T·O	1500	-90	150	38	10	_	165
			150	45	60	62	7.5	2.5	4.8	5.0	0.8	36	C-P	1250	-100	125	30	7.5		116
	40		1 130	43	00	32	7.3	2.0	1.0	3.0			B7	1500	-9	250ª	285°	6.0a	12K	250
TZ40	40	1500						+			1			2000	-135	105	45	1,2		200
TZ40	40	1500		-	-				4.5		0.2	3.0						1.13	-	
				50	100	20	5.0	4.0	4.1	1 2	0.3	3 G	C-T	l	1	125		13	_	
TZ40 3-50A4 35T 3-50D4	- 50	2000	150	50	100	39	5.0	4.0	2.5	1.8	0.3	3G 2D	C-P	1500	-150	90	40	11	=	105
TZ40 3-50A4 35T				50	100	39	5.0	4.0	-	1.8	-	-	C·P	1500 2000	-150 -40	90 4/167	40 255°	11 4.0°		105 235
7Z40 3-50A4 35T 3-50D4 35TG	- 50	2000	150	_	-	-		-	2.5	-	0.4	2D	C-P B ⁷ C-T	1500 2000 3000	-150 -40 -290	90 4/167 100	40	11	 27.5K	105
TZ40 3-50A4 35T 3-50D4				50	100	39	5.0	4.0	-	1.8	-	-	C·P	1500 2000	-150 -40	90 4/167	40 255° 25	11 4.0° 10	27.5K	105 235 250

¹ See page V29 for Key to Class-of-Service abbreviations.

		M	eximum	Ratin	gs		Ca	thode	Ca	pacita	nces					Typical	Operati	ion		
Туре	Plate Dissi- pation Watts	Plate Voltage	Plate Current Ma.	D.C. Grid Current Ma.	Freq. Mc. Full Ratings	Amplification Factor	Voits	Amperes	Cin µµ1.	С _{ер} µµ1.	Cout µµ1.	Base	Class of Service	Plate Voltage	Grid	Plate Current Ma.	D.C. Grid Current Ma.	Approx. Driving Power Watts	P-to-P Load Ohms	Approx. Output Power Watts
T55	55	1500	150	40	60	20	7.5	3.0	5.0	3.9	1.2	36	C-T C-P	1500 1500	-170 -195	150 125	18	6.0 5.0	=	170 145
826	55	1000	140	40	250	31	7.5	4.0	3.0	2.9	1.1	780	C-T-O C-P G-M-A	1000 1000 1000	-70 -160 -125	95 65	35 40 9.5	5.8 11.5 8.2	=	90 70
830B 930B	60	1000	150	30	15	25	10	2.0	5.0	11	1.8	3G	C-T-O C-P	1000 800	-110 -150	140 95	30 20	7.0 5.0	=	90 50
811-A19	65	1500	175	50	60	160	6.3	4.0	5.9	5.6	0.7	3G	C·T C·P	1000 1500 1250	-35 -70 -120	20/280 173 140	270° 40 45	7.1 10.0	7.6K	175 200 135
B12-A	65	1500	175	35	60	29	6.3	4.0	5.4	5.5	0.77	3G	C·T C·P	1500 1500 1250	-4.5 -120 -115	32/313 173 140	170° 30 35	6.5 7.6	12.4K	340 190 130
5514	65	1500	175	60	60	145	7.5	3.0	7.8	7.9	1.0	480	C·T C·P	1500 1500 1250	-48 -106 -84	28 310 175 142	270° 60 60	5.0 12 10	13.2K	340 200 135
3-75A3 75TH	75	3000	225	40	40	20	5.0	6.25	2.7	2.3	0.3	20	C·T C·P	2000 2000	-4.5 -200 -300	350* 150 110	88* 32 15	6.5* 10 6	10.5K	400 225 170
3-75A2 75TL	75	3000	225	35	40	12	5.0	6.25	2.6	2.4	0,4	2D	B ⁷ C⋅T C⋅P	2000 2000 2000	-90 -300 -500	50, 225 150 130	350° 21 20	38 8 14	19.3K	300 225 210
3005	85	1500	200	45	60	20	10	3.25	6,4	5.0	1.0	3G	AB ₂ ⁷ C·T C·P	2000 1500 1250	-190 -130 -195	50/250 200 190	600° 32 28	58 7.5 9.0	18K	350 220 170
V-70-D	85	1750	200	45	30	-	7.5	3.25	4,5	4.5	1.7	3G	B ⁷ C·T	1500 1750 1500	-70 -100 -90	40 310 170 165	310° 19 19	4.0 3.9 3.9	10K	300 225 195
I-100A4	100	3000	225	60	40	40	5.0	6.2	20	20	0.4	•••	C-P C-T	1500 1250 - 3000	-90 -72 -200	165 127 165	19 16 51	3.7 2.6	=	185 122 400
00TH	100	3000	223	00	40	40	5.0	6.3	2.9	2.0	0.4	2D	C-P B ⁷ C-T	3000	-65 -400	40 215	3359	5.08	31K	650
-100A2 00TL	100	3000	225	50	40	14	5.0	6.3	2.3	2.0	0.4	20	C·P G·M·A B ⁷	3000	560 185	60 40/215	2.0 640°	7.0 6.0*	30K	90 450
/T127A	100	3000	_	_	150	15.5	5.0	10.4	2.7	2.3	0.35	Fig. 53	C-T B ⁷	2000 1500	-340 -125	210	67 44	7.3	3K	315 200
11	100	1250	175	50	15	12	10	3.25	6.0	14.5 9.25	5.5	4E	C·T C·P B ⁷	1250 1000 1250	-225 -260 -100	150 150 20/320	18 35 410°	7.0 14 8.08		130 100 260
54	100	4000	225	60	_	25	5.0	7.5	2.5	2.7	0.4	2N	C·T C·P B ⁷	3000 2500 2500	-245 -360 -80	165 168 40/240	40 40 460°	18 23 25		400 335 420
C X100A515	100 70	1000	12514	50	2500	100	6.0	1.05	7.0	2.15	0.035	_	G-G-A C-P	800	-20 -15	80 75	30	6	-	27
X100A11 C39	100	1000	60	40	500	100	6.3	1.1	6.5	1.95	0.03	_	G-I-C	600	-35	60	40	5.0	_	20
L2C39A15 L2C39B15	100 70	1000	12514	50	500	100	6.3	1.0	6.5 7.0	1.9 1.9	0.035 0.035	_	C-T-O C-P	900	-40 -150	90	30 50	_	-	40
i L146	125	1500	200	60	15	75	10	3.25	7.2	9.2	3.9	Fig. 56	C·T·O C·P B ⁷	1250 1000 1250	-150 -200	180 160 34/320	30 40	=	 8.4K	150 100 250
L152	125	1500	200	60	15	25	10	3.25	7.0	8.8	4.0	Fig. 56	C·T·O C·P	1250 1000 1250	-150 -200 -40	180 160 16/320	30 30		- 8.4K	150 100 250
05	125	1500	210	70	30	40/60	10	3.25	8.5	6.5	10.5	3N	C-T C-P B ⁷	1500 1250 1500	-105 -160 -16	200 160 84/400	40 60 280°	8.5 16 7.0*	 	215 140 370
X9900/ 866 ¹⁵	135	2500	200	40	150	25	6.3	5.4	5.8	5.5	0.1	Fig. 3	C·T C·P B'	2500 2000 2500	-200 -225 -90	200 127 80/330	40 40 350°	16 16 14 ⁸	 	390 204 560
150A3 52TH	150	3000	450	85	40	20	5.0 10	12.5 6.25	5.7	4.8	0.4	4BC	C·T C·P	3000 2500 2500	-300 -350 -125	250 200 40/340	70 30 390°	27 15 16*	— — 17K	600 400 600
150A2 52TL	150	3000	450	75	40	12	5 10	12.5 6.25	4.5	4.4	0.7	4BC	C-T B ⁷	3000 3000	-400 -260	250 65/335	40 6759	20		600 700
F201A	150	2500	200	50	30	18	10-11	4.0	8.8	7.0	1.2	Fig. 15	C·T C·P B'	2500 2000 2500	-300 350 -130	200 160 60/360	18 20 4609	8 9 8*	 	380 250 600
72	150	2500	200	-	_	170	6.3	4.0	-	_	_	3G	В'	1500 2000	0	60/350 80/360		5.5	12.5K 16.5K	380 530
10	175	2500	300	75	30	36	10	4.5	8.7	4.8	12	2N	C·T C·P G·M·A	2500 2000 2250	-180 -350 -140	300 250 100	60 70 2.0	19 35 4	_ 	575 380 75
16	V20 5a-	Kau to O	ass-of-Se	nula- :	here de la co								B ₁	2250	-60	70/450	380°	138	11.6K	725

		44. 1		hadia	T		Cath	ode	Can	acitan	ces					Typical (peratio	n		
Туре	Plate Dissi- pation Watts		Plate Current Ma. W	Current Ma.	Freq. Mc. Full Ratings	Amplification Factor	Volts	Amperes	Cin μμ1.	C _{gp} μμ1.	Cout μμf.	Base	Class of Service ¹	Plate Voltage	Grid Voltage	Plate Current Ma.	D.C. Grid Current Ma.	Approx. Driving Power Watts	P-to-P Load Ohms	Approx. Output Power Watts
000	175	2500	300	45	30	16.5	10	4.5	5.0	6.4	3.3	2N	C·T·O C·P G·M·A B ⁷	2500 2000 2250 2250	-240 -370 -265 -130	300 250 100 65/450	40 37 0 560*	20 2.5 7.9*		575 380 75 725
200	200	2500	350	80	30	16	10	5.75	9.5	7.9	1.6	2 N	C-T C-P	2500 2000	-280 -260	350 300	54 54	25 23	=	685 460
92/ ¹⁵ -200A3	200 130	3500 2600	250 200	25 ¹³	150	25	10	5.0	3.6	3.3	0.29	Fig. 28	C·T C·P B ⁷	3500 2500 2000	-270 -300 -50	228 200 120/500	30 35 520°	15 19 20*	 	375 600
C34	200	3500	250	2513	60	23	11-12	4.0	6.0	6.5	1.4	2 N	C-T C-P	3000 2000	-400 -300	250 250	28 36 450°	16 17 13*		600 385 780
·300	200	3000	300			23	11	6,0	6.0	7.0	1.4	_	B ⁷ C⋅T C⋅P	3000 3000 2000	-115 -400 -300	60/360 250 250	28	20 17		600 385
				50	30	12.6	5.0	10	6.1	4.2	1.1	2N	B ⁷ C⋅T C⋅P	3300 3000	-100 -600 -670	300 195	40	7.5* 34 24	=	750 780 460
06	225	3300	300	50	30	12.0	3.0	10	0.1	7.2	1	-	B ⁷ C-T•0	3300 2000 3000	-240 -100 -150	80/475 357 333	930° 94 90	358 29 32	16K	1120 464 750
-250A4 50TH	250	4000	350	4013	40	37	5.0	10.5	4.6	2.9	0.5	2N	C-P	2000 2500 3000	-160 180 200	250 225 200	60 45 38	22 17 14	=	335 400 435
	-	_					-	_	-	-	-		AB ₂ ⁷ C·T·O	1500 2000 3000	-200 -350	350 335	460° 45 45	22 29	4.2K	455 750
-250A2 50TL	250	4000	350	3513	40	14	5.0	10.5	3.7	3.0	0.7	2 N	C-P	2000 2500 3000	-520 -520 -520	250 225 200	29 20 14	24 16 11	=	335 400 435
5867	250	3000	400	80	100	25	5.0	14.1	7.7	5.9	0.18	Fig. 3	C-T C-P	1500 3000 2500	-40 -250 -300	200/700 363 250	69 70	38* 27 28	3.8K	580 840 482 1280
AX-9901 PL-656919	250	4000	300	120	30	45	5.0	14.5	7.6	3.7	0.1	Fig. 3	G-G-A	3000 2500 3000 3500 4000	-110 -70 -95 -110 -120	570° 300 300 285 250	465° 85 110 90 50	32 7520 8520 8520 7020	14.2K	555 710 805 820
3-300A3				6013	40	20	5.0	25	13.5	10.2	0.7	4BC	C-T-O	1500 2000 1500	-125 -200 -200	665 600 420	115 125 55	25 39 18	=	700 900 500
304TH	300	3000	900	6013	40	20	10	12.5	13.3	10.2	0.7	150	C-P AB ₂ ⁷	2000 2500 1500	-300 -350 -65	400 1065	60 60 330°	26 29 25*	2.84	
3-300A2	300	3000	900	5013	40	12	5.0	25	12.1	8.6	0.8	4BC	C-T-O	2000 2000 2000 2000 2500	- 250 - 300 - 500 - 500 - 525	500 500 200	90 85 30 75 18	33 36 18 52 11	- - - -	700 900 410 810 425
304TL ¹⁹	300	3000					10	12.5					AB ₁ ⁷	2500 1500 2500 1500	-550 -118 -230 -118	270/57 160/48	3 460°	36 0 0 39*	2.54F 8.5K 2.75F	610
833A	350	3300	500	100	30	35	10	10	12.3	6.3	8.5	Fig. 41	C-T-O	2250 3000 2500 3000	-160 -300	335	85 70 75 70	23 20 30 26		78 80 63 80
	45015	400015			2015		1	1	1	1.	0.03	Fi. A	B7	3000 3000	-7		0 4009	20*	9.5K	165
3-400Z	400	3000	400	120	110	200	5.0	14.5	7.4		_	Fig. 3	G-G-B	4000	-110	350	92	10520	-	108
PL-658019	400	400015	350	120		45	5.0	21.3	7.0	3.3	0.1	301	a-u-n	2500 3000		350	95	85 65	 -	1360

G-I-C = Grid-isolation circuit.
G-M-A = Grid-modulated amp.
2 Twin triode. Values, except interelectrode capacitances, are for both sections in push-pull.
3 Output at 112 Mc.
4 Grid leak resistor in ohms.
5 Peak values.

6 Per section.

7 Values are for two tubes in push-pull.

Max. signal value.
Peak a.f. grid-to-grid volts.
Plate-pulsed 1000-Mc. osc.

11 Class-B data in Table II.
12 1000-Mc. c.w. osc.
13 Max. grid dissipation in watts.
14 Max. cathode current in ma.
15 Forced-air cooling required.
19 Plate-pulsed 3300-Mc. osc.
19 1900-Mc. c.w. osc.
18 No Class-B data available.
19 Linear-amplifier tube-operation data for single sideband in Table 11-1.
29 Includes bias loss, grid dissipation, and feed-through power.

through power.

		Maxir	num f	Rating	s	Cati	node	Ca	apacita	nces				,	,	Typica	I Operation	on			,	
Туре	Plate Dissi- pation Watts	Plate Voltage	Screen Dissi- pation Watts	Screen Voitage	Freq. Mc. Futl Ratings	Voits	Amperes	Cin μμf.	C _{gp} μμf.	Cout μμf.	Base	Class of Service ¹⁴	Plate Voltage	Screen Voltage	Suppressor Voltage	Grid	Plate Current Ma.	Screen Current Ma.	Grid Current Ma.	Approx. Driving Power Watts	P-to-P Load Ohms	Approx. Output Power Watts
7717	2	180	0.5	180	Ι-	6.3	0.2	4.5	0.03	3	7EW	C-P	125	80	-	-1	10	1.4	-	-	-	=
69393	7.5	275	3	200	500	6.3	0.75	6.6	0.15	1.55	Fig. 13	C-P	200	200	<u> </u>	20	55	13	1.7	1.0	-	7.
	7.0	1	,	200	300	12.6	0.375	0.5	0.10	1.00	119.10	C-M	200	190	+=	68K1	46	10	2.2	0.9	\vdash	-
7701	9	350	3.5	300	175	13.6	0.16	7	0.15	3.6	9MS	C-P	250	250	_	- 12.5	28	3.1	-		_	_
2E30	10	250	2.5	250	160	6	0.7	10	0.5	4.5	7CQ	C·T AB ₂ ⁶	250 250	200	-	-50 -30	50 40 120	10	2.5	0.2	2 0V	17
***	1.0			200		10.0	0.7	1,5	0.0	10	0014	C-T	500	200	40	- 70	80	15	4	0.2	3.8K	28
837	12	500	8	300	20	12.6	0.7	16	0.2	10	6B M	C-P	400	140	40	-40	45	20	5	0.3	-	11
7551 7558	12	300	2	250	175	6.3	0.38	10	0.15	5.5	9LK	C-T	300 250	250 250	_	- 55 - 75	80 70	5.1	1.6	1.5	-	10
1330	-			-		0.3	0.0				-	C-T	350	250	+=	-28.5	48.5	6.2	2.3	0.1	<u> </u>	12
5763	13.5	350	2	250	50	6.3	0.75	9.5	0.3	4.5	9K	C-P	300	250	_	-42.5	50	6	2.4	0.15	† <u>-</u>	10
6417	13.3	330		250	- ×	12.6	0.375	3.5	0.5	4.5	311	C-M2	300	250	-	75	40	4	1	0.6		2.
	-	-	-	-	-	+		-		-	-	C-M ⁴	300 500	235 180	-	100 45	35 54	5 8	2.5	0.6	-	18
2E24	13.5	600	2.5	200	125	6.35	0.65	8.5	0.11	6.5	7CL	C-T	600	195	_	-50	66	10	3	0.21	+=	27
2E2613						6.3	0,8				1	C-T	600	185	_	-45	66	10	3	0,17	_	27
6893	13.5	600	2.5	200	125	12.6	0.4	12.5	0.2	7	7CK	C-P AB ₂ 6	500	180	_	50 15	54 22, 150	327	2.5	0.15	- OV	18 54
			-	-		-	-				-	C-T	300	200	-	-45	100	32'	3	0.36	8K	18.
63603	14	300	2	200	200	6.3	0.82	6.2	0.1	2.6	Fig. 13	C-P	200	100	_	15K1	86	3.1	3.3	0.2	_	9.
9300-	14	300		200	200	12.6	0.41	0.2	0.1	2.0	rig. 13	C-M11	300	150	-	-100	65	3.5	3.8	0.45	_	4.
	-	-	-	-	-	-					-	AB ₂	300 450	200	-	-21.5 -45	30, 100 75	1/11.4	648	0.04	6.5K	17.
2E25	15	450	4	250	125	6	0.8	8.5	0.15	6.7	5BJ	C-P	400	200		-45	60	12	3	0.4	_	16
				<u> </u>								AB ₂ 6	450	250		- 30	44 150	10 40	3	0.97	6K	40
B32 A3	15	750	5	250	200	6.3 12.6	0.8	8	0.07	3.8	7BP	C-T	750 600	200	-	-65 -65	48 36	15	2.8	0.19	-	26
	-	-				12.0	0,0				-	C·F	400	300	-	55	75	16	2.6	0.16		17
1619	15	400	3.5	300	45	2.5	2	10.5	0.35	12.5	Fig. 74	C-P	325	285	-	- 50	62	7.5	2.8	0.18	-	13.
												AB ₂ 6	400	300	0	- 16.5	75 150	6.5, 11.5	_	0.47	6K	36
5516	15	600	5	250	80	6	0.7	8.5	0.12	6.5	7CL	C·P	600 475	250 250	-	-60 -90	75 63	15	5	0.5		32
3316	13	000	,	230	00	0	0.7	0.3	0.12	0.5	762	AB ₂ 6	600	250	-	-25	36/140	1/24	47	0.16	10.5K	67
6252/						6.3	1.3					C-T	600	250	_	-60	140	14	4	2.0	-	+ =
A X99103	20	750	4	300	300	12.6	0.65	6.5	-	2.5	Fig. 7	C-P	500	250		-80	100	12	3	4.0	-	_
	-						\vdash					B C·T	500 450	250 250	_	-26 -45	25, 73 100	0.7/16	5211	0.15	20 K	23.5
1614	25	450	3.5	300	80	6.3	0,9	10	0.4	12,5	7AC	C-P	375	250	_	-50	93	7	2	0.15		24.
												AB ₁ 6	530	340	_	-36	60, 160	207	=	=	7.2K	50
B15 ³	25	500	4	200	125	6.3	1.6	13.3	0.2	8.5	8B Y	C-T-O C-P	500 400	200 175	_	-45 -45	150 150	17	2.5	0.13		56 45
,,,	23	300		200	123	12.6	0.8	13.3	0.2	0.5		AB ₂	500	125		- 15	22, 150	327	-	0.16	8K	54
												C-T	600	300	_	- 60	90	10	5	0.43	_	35
1624	25	600	3.5	300	60	2.5	2	11	0,25	7.5	Fig. 66	C-P AB,6	500 600	275 300		-50 -25	75 42 180	5 15	3.3 106 ⁸	0.25	7.54	24
4604	25	750	3	250	60	6.3	0.65	11	0.24	8.5	7CL	C-T	400	190		- 60	150	11	2	4.5	7.5K	72
			Ť						0.2			C-T	500	170	_	-66	135	9	2.5	0.2		48
514613						6.3	1.25					1	750	160	_	- 62	120	11	3.1	0.2	_	70
						\vdash	-					C-T12	400 400	190 150	_	-54 -87	150	7.8	3.4	3.0 0.4		35 32
5883	25	750	3	250	60	12.6	0.625	13.5	0.22	8.5	7C K	C-P	600	150	_	-87	112	7.8	3.4	0.4	_	52
												AB ₂ 6	600	190	_	- 48	28 270	1.2 20	27	0.03	5K	113
159						26.5	0.3					AB ₁ 6	750 750	165 195	_	- 46 - 50	22/240 23/220	0.3 20	2.6 ⁷	0.04	7.4K	131
			\vdash				3.05	-				C.T	600	200	_	-44	120	8	3.7	0.2	8K	56
5524 ³ 5850	25	600	-	300	100	6.3	1.25 0.625	7	0.11	3,4	Fig. 76	C-P	500	200	_	-61	100	7	2.5	0.2	_	40
						12.0	0.023					AB ₂	500	200 250		-26 -45	20 116	0.1 10	2.6	0.1	11.1K	40
107 ¹³ 107W						6.3	0.9			_	5AW	C-P	750 600	275	_	-45	100	6.5	3.5	0.22		50 42.5
933	30	750	3.5	300	60			12	0.2	7		AB ₂ ⁶	750	300	_	- 32	60 240	5/10	928	0.27	6.95K	120
62513	20	700		000		12.6	0.45	12	0.0		5AZ	B10	750	-	- 20.5	0	15, 240	-	5558	5.37	6.65K	120
E22	30	750	10	250	_	6.3	1.5	13	0,2	8	53	C-T-O	750	250	22.5	-60	100	16	6	0.55	_	53
9033	40	600	7	250	250	6.3	0.9	6.7	0.08	2.1	Fig. 7	C-P	600	250 250	-	-80 -100	200	16 24	8	1.2		80 85
894A	1		\vdash			14.0	0.5		-	-		C-F	500	200	_	-45	240	32			_	
29B3	40	750	7	240	200	6.3	2.25	14.5	0.12	7	7BP	C-P	425	200	-	-45	212	35	12	0.7	_	83 63
E293			_			12.6	1.125					В	500	200	_	– 18	27 230	_	568	0.39	4.8K	76
ID24	45	2000	10	400	125	6.3	3	6.5	0.2	2.4	Fig. 75	C·T·O	2000	375	_	-300	90	20	10	4.0		140
	.,,							510				-	1500 750	375 300	_	-300 -100	90 240	22	10	4.0 1,5	_	105
						12.6	1.6				Fig. 26	C-T	600	300	_	-100	215	30	10	1,25		135
ID22						25.2	0.8	- [000	300								
ID22 ID32	50	750	14	350	60	6.3	3.75	28	0.27	13	Fig. 27	C-P	600	-	=	-100 -100	220 175	28 17	10	1.25	=	100

¹⁴ See page V32 for Key to Class-of-Service abbreviations.

		Maxim	um R	atings		Catho	de	Cap	acita	1005						Typical	Operation	1		-		-
Туре	Plate Dissi- pation Watts	Piate Voltage	Screen Dissi- pation Watts	Screen Voltage	Freq. Mc. Full Ratings	Voits	Amperes	Cin µµf.	C _{ap} μμf.	Cout μμf.	Base	Class of Service ¹⁴	Plate Voltage	Screen	Suppressor Voltage	Grid Voltage	Plate Current Ma.	Screen Current Ma.	Grid Current Ma.	Approx. Driving Power Watts	P-to-P Load Ohms	Approx. Output
14	65	1500	10	300	30	10	3.25	13.5	0.1	13.5	Fig. 64	C-P	1500 1250	300 300	_	-90 -150	150 145	24	10	3.2		1
		-		-			-					C·T·O	1500	250	-	-85	150	40	18	3.2	_	1
								_			40	0.1.0	3000	250	_	-100	115	22 40	10	3.5	_	1
-65A13	65	3000	10	600	150	6	3.5	8	80,0	2.1	Fig. 25	C-P	1500 2500	250 250	=	-125 -135	110	25	12	2.6	=	2
			1									AB ₂ 6	1800	250	_	-50	50, 250	307	180s	2.67	20K	2
E27/	75	4000	30	750	75	5	7.5	12	0.06	6.5	7B M	C-T C-P	2000 1800	500 400	60	-200 -130	150	11	8	1.4	-	1
1K257	75	4000	25	750	7516	5	7.5	13.8	0.04	6.7	78 M	C-T	2000	500	60	200	150	11	6	1.4	_	2
IK257B	75	4000	23	730	73	,	7.5	10.0	0.01			C-P	1800 2000	400	60	-130 -125	135 150	11	5	0.8	=	1
L-177A ¹³	75	2000	10	600	-	6	3.2	7.5	0.06	4.2	Fig. 14	C-T-C-P	1000	400	0	-105	150	16	5	0.7	_	1
					175		2.6	3.5	0.00	2.4	Fig. 14	C·T C·P	2000	400	70	-125 -140	150 125	12	5	0.8	-	2
L-6549	75	2000	10	600	175	6	3.5	7.5	0.09	3.4	rig. 14	AB ₂ 6	2000	400	70	-85	30/225	0.1/10	180s	0.053	19K	1
			1	1	1							C·T	1500	400	75 75	-100 -140	180	28 28	12	2.2	-	H
28	80	2000	23	750	30	10	3,25	13.5	0.05	14.5	5J	C-P AB ₁ 6	1250 2000	400 750	60	- 140	50/270	2/60	240	0	18.5K	1
270	90	1260	_	425	175	6.3	3.1	8	0,4	0.14	Fig. 84	C-T	850	400	-	-100	275	15	8	10		F
271	80	1350			500	13.5	1.25	16	0.13	0.011	Fig. 87	AB ₁	665 700	400 200	-	-119 -30	300	15	20	10	-	H
072	100	2200	8	400	300	13.5		10	0.13	0.011	11g. 07	C·T·O	900	300	-	30	170	1	10	3	=	t
816°	115	1000	4.5	300	400	6.3	2.1	14	0.085	0.015	Fig. 77	C-P AB.6	700 850	250 300	-	-50 -15	130 80/200	0/20	10 30s	3	7K	H
884	110	1000				26.5	0.52					AB ₂ 6	850	300	+-	-15	80/335	0/25	468	0.3	3.96K	t
	-	_	_		\vdash	_						C·T·O	1250	300	0	-75	180	35 40	12	1.7	-	F
													2250 1250	400 300	0	-155 -160	220 150	35	15	2.9	-	t
1313	125	2500	20	800	30	10	5	16.3	0.25	14	5BA	C-P	2000	350	0	-175	200	40	16	4.3	_	1
												AB ₂ 6	2000 2500	750 750	0	-90 -95	40/315 35/360	1.5/58	230 ⁸	0.17	16K	+
	-	- -	+	+-	-	-			-			C·T·O	2000	350	-	-100	200	50	12	2.8	-	İ
					1							0.1.0	3000 2000	350 350	-	-150 -220	167 150	30	9	2,5	-	+
I-125A ¹³ ID21	125	3000	20	600	120	5	6.5	10.8	0.07	3.1	5BK	C-P	2500	350	+=	-210	152	30	9	3.3	+=	+
155	123	3000	20		120		0.0					AB ₂ 6	2500	350	=	-43	93/260	0/6	1788	1.07	22 K	I
												AB ₁ 6 GG	2500 2000	600	=	-96 0	50/232 10/10517	0.3/8.5	1924	1617	20.3K	Ŧ
4E27A/	105	4000	20	750	75	5	7.5	10.5	0.08	4.7	78M	C·T	3000	500	60	-200	167	5	6	1.6	=	1
5-125B	125	4000	20	750	//3	1	7.5	10.5	0.00	1		C·T	1000 2000	750 500	40	-170 -90	160	21 45	12	0.6	-	+
303	125	2000	30	600	20	10	5	17.5	0.15	29	5J	C-P	1600	400	100	-80	150	45	25	5	-	İ
	†	1	1	1	1				2.5	1.0	Fig. 02	C·T C·P	1500 1200	400	=	-100 -130	330 275	20	5	5	 -	Ŧ
7094	125	2000	20	400	60	6.3	3.2	9.0	0,5	1.8	Fig. 82	ABI	2000	400	+=	-65	60/400	-	1208	0	12K	İ
1X150A		\vdash		+-	1	6	2.6	15.5	0.03	4.5	Flg. 75	C·T·O	1250	250	_	-90	200	20	10	0.8	ļ —	Ŧ
X150G15	150*	1250	12	400	500	2.5	6.25	27	0.035		-	C·P AB ₂ 6	1000	250 300	+-	-105 -44	4757	0/65	100*	0.15	5.6K	+
3122	150	2200	8	400	500	13.5	1.3	16	0.13	0.011	Fig. 87	C·T·O	1000	200	三	-30	300	10	30	5		Ŧ
												C·T·O	2500 3000	500	-	-150 -180	300	60	9	2.6	-	+
4-250A13	2004	4000	25	600	110	5	14.5	12.7	0.12	4.5	5BK	C-P	2500	400	=	-200	200	30	9	2.2	-	1
5D22 6156	250*	4000	35	600	110	,	14.5	12.7	0.12	4.5	0011	AB ₂ s	3000 2000	300	=	-310 -48	225 5107	30 0/26	198*	3.2 5.5 ⁷	8K	+
					1							AB ₁ 6	2500	600	1=	-110	4307	0.3/13	1804	0	11.4K	İ
			1	1		1.				4.3	Fin 16	C·T·O	2000	250	E	-90	250	25 25	27	2.8	+=	+
1X250B	250*	2000	12	400	175	6	2.1	18.5	0,04	4.7	Fig. 75	C-P AB ₁ 6	1500 2000	250 350	+=	-100 -50	500²	307	100*	0	8.26K	1
7034/9	250	2000	12	300		6	2.6					C-T-0	2000	250	=	-88	250	24	8	2.5	-	1
4X150A	250	+	+-	+-	150	-	+	16	0.03	4.4	Fig. 75	C-P AB,6	2000	300	+=	-118	200	0/36	1068	0.2	8.1K	+
7035/13 4 X150D	250	2000	12	400		26.5	0.58					AB ₁ 6	2000	300	E	-50	100/470	0/36	100s	0	8.76K	1
4C X-		0000		10.0	500	_	2 35	20.5	0.04	, 0		C·T C·P	2000 1500	250 250	=	-90 -100	250	25 25	27	2.8	+-	+
300A	3009	2000	12	400	500	6	2.75	29.5	0.04	4,8	_	AB ₁ 6	2000		+=	-50	5007	307	100¢	0	8.26K	1
PL-175A1	3 400	4000	25	600	1-	5	14.5	15.1	0.06	9.8	Fig. 86	C-T-C-P	4000	600	0	-200	350	29	6 7	1.4	=	I
	+	+	+	-	+	+-	-	+-	+	+	<u> </u>	C-T-C-P	2500 4000	300	0	-180 -170	350 270	22.5	10	1.6	+-	+
4-400A	400°	4000	35	600	110	5	14.5	12.5		1	5BK	GG	2500	0	1-	0	80/27017	5517	10017	3817	4.0K	1
		2200	8	400	500	13.5	1.3	16	0.13		Fig. 88	C·T·O	2000	200	Τ —	-30	300	5	30	5	_	- 1

¹⁴ See page V32 for Key to Class-of-Service abbreviations.

		Maxin	ıum F	ating	s	Cath	ode	Ca	pacita	nces						Typica	l Operation	n				
Туре	Plate Dissi- pation Watts	Plate Voltage	Screen Dissi- pation Watts	Screen Voltage	Freq. Mc. Full Ratings	Volts	Amperes	Cin µµf.	Cgp μμί.	Cout µµf.	Base	Class of Service 14	Plate Voltage	Screen Voltage	Suppressor Voltage	Grid Voltage	Plate Current Ma.	Screen Current Ma.	Grid Current Ma.	Approx. Driving Power Watts	P-to-P Load Ohms	Approx. Output Power Watts
												C-T	3000	500	_	-150	700	146	38	11	-	1430
4-1800A	1000	6000	75	1000	_	7.5	21	27.2	.24	7.6	_	C-P	3000	500	_	-200	600	145	36	12	_	1390
4-1000M	1000	0000	,,,	1000	_	7.5		21.2	.64	7.0	_	AB ₂	4000	500	_	-60	300/1200	0, 95	-	11	7K	3000
												GG	3000	0	_	0	100, 70017	10517	17017	13017	2.5K	1475
													2000	325	_	-55	500, 2000	-4, 60	-	_	2.8K	2160
4C X1000A	1000	3000	12	400	400	6	12.5	35	.005	12		AB ₁	2500	325	_	-55	500, 2000	-4/60	-	_	3.1K	2920
													3000	325	_	- 55	500, 1800	-4 60	-	_	3.85K	3360
													2000	400	75	- 150	725	44	22	4.1	_	1110
												C-T	2500	500	75	-175	960	64	31	6.8	_	1870
PL-172	1000	3000	35	600	_	6	7.8	38	.09	18			3000	500	75	-175	900	56	24	4.8	_	2170
	. 300	2200	30	550		,	7.0	30	.00		_		2000	500	75	-110	400/1600	20 90	2108	_	2.65K	1820
												ABı	2500	500	75	-110	440 1600	20 85	210*	_	3.5K	310
													3000	500	75	-115	440 1500	10 / 75	2008	_	4.6K	2680

Grid-resistor.
Doubler to 175 Mc.
Dual tube. Values for both sections, in push-pull, Interelectrode capacitances, however, are for each section.
Tripler to 175 Mc.
Filament limited to intermittent operation.

6 Values are for two tubes in push-pull 7 Max.-signal value.

Max.-signal value.

9 Feak grid-lo-grid af. volts.

9 Forced-air cooling required.

10 Two tubes triode connected, G₂ to G₁ through 20K Ω. Input to G₂.

11 Tripler to 200 Mc

12 Typical Operation at 175 Mc.

13 Linear-amplifier tube-operation data for single-sideband in Chap. 11.

14 KEY TO CLASS-OF-SERVICE ABBREVIATIONS

AB₁ = Class-AB₁ push-pull a.f. modulator.

AB₂ = AB₂ push-pull a.f. modulator.

B = Class-B push-pull a.f. modulator.

C-M = Frequency multiplier.

C-P = Class-C plate-modulated telephone.

C-T = Class-C plate-modulated telephone.

C-T = Class-C amplifier-osc.

GG = Grounded-grid (grid and screen connected together).

15 No Class B data available.

16 HK257B 120 Mc. full rating.

17 Single tone.

17 Single tone.

TABLE XIII - ELECTROSTATIC CATHODE-RAY TUBES

Type ⁶	He	ater	Base	Anode No. 2	Anode No. 1	Anode	Cut-off	Deflection Avg. Volts DC/Inch			
Type	Volts	Amp.	Dase	Voltage	Voltage:	No. 3 Voltage	Grid Voltage ²	D ₁ D ₂	D ₃ D ₄		
1EP1-2-11	6.3	0.6	11 7	1000	100, 300		-14/-42	210/310	240/350		
2BP1-11	6.3	0.6	12E	2000	300 560	_	-135	270	174		
3AQP1	6.3	0.6	12E	2750	1100	_	-83/ - 193	73 99	26/35		
3BP1A	6.3	0.6	14G	2000	575		-30/-90	200	148		
3FP7A	6.3	0.6	14J	2000	575	4000	-3090	250	180		
3GP1A-3GP4A	6.3	0.6	11 N	1500	245/437	_	-25, -75	96 144	84/126		
3JP1A-7A-11A	6.3	0.6	14J	2000	400, 690	4000	-45/ -75	180 220	133/163		
3KP1-4-11	6.3	0.6	11 M	2000	320/600	_	-0, -90	100, 136	76/104		
3RP1-4-3RP1A	6.3	0.6	12E	2000	330, 620	_	-135	146/198	104/140		
3SP1-4-7	6.3	0.6	12E	2000	330/620	_	-28/ -135	146/198	104/140		
3UP1	6.3	0.6	12F	2000	320, 620		- 126	240, 310	232/296		
3WP1-2-11	6.3	0.6	12T	2000	330 620	_	-60/-100	83 101	57/70		
5ABP1-7-11	6.3	0.6	14J	2000	400, 690	4000	-52/-87	26/34	18/24		
5ADP1-7-11	6.3	0.6	143	1500	300 515	3000	-34/-56	40/50	30.5/37.5		
5AMP1	6.3	0.6	140	2500	0/300	_	-34/-56	40 50 -	20/25		
5AQP1	6.3	0.6	14G	2500	0/300		-34/ -56	40/50	31,5/38,5		
5ATP1-2-7-11	6.3	0.6	147	6000	0 700	_	-34 -56	94, 116	34/42		
5BPIA	6.3	0.6	11 N	2000	450	_	-20/-60	84	76		
5BP7A	6.3	0.6	11 N	2000	375, 560	_	-20/-60	70/98	63/89		
5CP1A	6.3	0.6	14J	2000	575	4000	-30/-90	92	78		
5CP1B-2B-7B-11B	6.3	0.6	14J	2000	400/690	4000	-45/-75	83/101	70 /86		
5CP7A-11A-12	6.3	0.6	14J	2000	575	4000	-30/ -90	92	74		
5GP1	6.3	0.6	11A	2000	425	_	-24/-56	36	72		
5HP1A	6.3	0.6	11 N	2000	450	_	-20/-60	84	76		
5JP1A—4A	6.3	0.6	11\$	2000	333, 630	. 4000	-45/-105	77, 115	77/115		
5LP1A—4A	6.3	0.6	117	2000	376, 633	4000	-30 -90	83.124	72/108		
5MP1-4-5-11	2.5	2.1	7AN	1500	375	_	-15 -45	66	60		
5NP1-4	6.3	0.6	11A	2000	450	_	-20/-60	84	76		
5RP1A-4A	6.3	0.6	14P	2000	362, 695	20000	-30 -90	140 210	131/197		
5\$P1-4	6.3	0.6	14K	2000	363 695	4000	-30 -90	74 110	62 /94		
5UP1-7-11	6.3	0.6	12E	2000	340, 360	_	-90	56/77	46/62		
5VP7	6.3	0.6	11 N	2000	315 562	_	-20 -60	70 98	63/89		
5XP1A-2A-11A	6.3	0.6	14P	2000	362 / 695	12000	-45 -75	130 159	42/52		
902-A	6.3	0.6	8CD	600	150		-30 -90	139	117		
908-A	2.5	2.1	7CE	1500	430	_	-25/ -75	114	109		
2002	6.3	0.6	Fig. 1	600	120	_		0.165	0.175		
2005	2.5	0.6	Fig. 14	2000	1000	200	- 35	0.55	0.565		

1 Bogey value for focus. Voltage should be adjustable about value shown.

² Bias for visual extinction of undeflected spot. Voltage should be adjustable from 0 to the higher value shown.

3 Discontinued.

⁴ Cathode connected to Pin 7.

5 In mm./volt d.c.

⁶ Phosphor characteristics (see next column).

Designation P1 P2 P4

Color and persistance Green medium Blue-green medium

Special recording Special recording of high speed traces.

Blue very short Slue white short — Yellow long Blue whort — Special recording of high speed traces. Radar indicators.

Scilloscope. P5 P7 PII

P12 Orange long Application Oscilloscope.

Special oscilloscopes and radar. Television.


Radar indicators.

			Maximum	Ratings			Chara	cteristics		Typical (Operation	Common	Emitter C	ircuit
N.	Tuna		Collector		Emitter	Noise	Input	Freq.	41	Collec	tor	Power Gain	Output Load R.	Power Output
No.	Туре	Diss. Mw.	Ma.	Volts	Ma.	Figure Db.	Res. Onms ¹	Cutorf Mc.	Use	Ma.	Voits	Ob.	Ohms	Mw.
N34	PNP	50	50	-25	10	18	1000	0.6	Audio ²	-1.0	-6	40	30K	125
N35	NPN	50	100	25	-10	16	1000	0.8	Audio ²	1.0	6	40	30K	125
N 43	PNP	155	-50	- 45	50	6	_	1.3	Audio	-1.0	5	39		_
N44	PNP	155	-50	-45	50	6		1.0	Audio	-1.0	-5	43		
N78	NPN	75	20	15	-20	12	_	6.0	I.FR.F.	_	-	30	_	
N94	NPN	50	50	20	_	_		2.0	I.F.	0.5	6	24	100K	_
N94A	NPN	50	50	20	_	15	_	5.0	I.FR.F.	0.5	6	30	100K	_
N107	PNP	50	-10	-12	10	22	700	0.6	_	-1.0	5	38	30K	
N109	PNP	50	-35	-12	35	_	750	_	Audio ²	-35.0	-4.5	30	200	75
N139	PNP	35	-15	-16	15	4.5	500		LF.	-1.0	-9	30	30K	_
N140	PNP	35	-15	-16	15	T -	700	7.0	I.FR.F.	-0.4	9	27	75K	
N155	PNP	8500	-3000	-30	_	_	20	0.3	Audio ²	-360.0	-14	30	_	93
N167	NPN	65	75	30	_	-	_	8.0	I.FR.F.	_	_	_	_	_
N169A	NPN	55	20	25	-20	_	500	5.0	I.FR.F.	1.0	5	27	15K	
N175	PNP	20	-2	-10	2	6	3570	_	Audio	-0.5	-4	43	_	_
N233	NPN	50	100	10		-	-	2.0	1.F.	_	_	21		_
N247	PNP	35	-10	-35	10	8		30.0	R.F.	-1.0	-9	24	_	_
N255	PNP	1500	-3000	-15	-	<u> </u>	_	0.2	Audio ²	- 500.0	-6	27	T-	53
N256	PNP	1500	-3000	-30	_	_	_	0.2	Audio ²	-500.0	-12	27	_	10 ³
N270	PNP	150	-75	-12	-75	_		_	Audio ²	_	-12	32	_	500
N274	PNP	35	-10	-35	10	8		30.0	R.F.	-1.0	-9	45	_	T -
N278	PNP		-13000	-50	13000		_	.004	Audio ²	_	-12	24	_	_
N292	NPN	65	20	15		—	_	6.0	I.FR.F.	_	_	25	_	
N301	PNP	7500	-1000	-20	1000	<u> </u>	_	_	Audio ²		-14.4	30	_	123
N301 A	PNP	7500	-1000	-30	1000	-		_	Audio ²	_	-14.4	30		123
N307	PNP	10000	- 1000	35	_	_	-	0.3	Audio		_	30	_	
2N331	PNP	200	-200	-30	200	9	-	1.0	Audio	-1.0	6	44	_	-
N351	PNP	10000	-3000	-40	3000		_	_	Audio ²	-3000	-40	_	_	
N370	PNP	80	-10	-20	10		1750	30.0	R.F.	-1.0	-12	12.5	_	_
2N371	PNP	80	-10	-20	10	-	_	30.0	R.F.	-1.0	-12	-	_	_
2 N372	PNP	80	-10	-20	10	_	100	30.0	Mixer	-1.0	-12	17	11K	_
2N372	PNP	80	-10	-25	10	 	2200	30.0	I.F.	-1.0	-12	40	_	_
2N374	PNP	80	-10	-25	10	-	2600	30.0	Conv.	-1.0	-12	40	_	-
2N376	PNP	10000	-3000	-30	3000	+	_	_	Audio ²	-3000	-40	_	_	_
2N384	PNP	120	-10	-30	10	_	30	100.0	R.F.	-1.5	-12	15	_	_
2 N 407	PNP	150	-70	-20	70	 	_	_	Audio ²	-40	_9	33	800	160
2N411	PNP	80	-15	-13	15	+	700	10.0	I.FR.F.	-0.6	-9	32	_	_
2N441	PNP	- 00	13000	-40	13000	_		.005	Audio ²		-12	23	-	_
2 N 442	PNP	-	13000	-50	13000	_		.005	Audio ²	_	-12	23		_
2N544	PNP	80	-10	-18	10	 	2100	30.0	R.F.	1.0	-12	30		T -
2 N 5 5 4	PNP		-3000	-30	3000	_	_	_	Audio	_	_	_	_	_
2 N 588	PNP	80	-50	-18	50	<u> </u>		200.0	R.F.	_	-	_	_	_
2N677	PNP	50000	-15000	- 50		_		_	Switching	_		60	_	
2N1102	NPN	180	100	40	-100	+	500	_	Audio	_	_	-	-	_
2N1225	PNP	120	-10	-30	10	_	30	100.0	R.F.	-1.5	- 12	15	_	T-
2 N1266	PNP	80	-10	-10		+-			I.F.	_	_	22	_	-
2 N 1396	PNP	120	-10	-30	10	_	30	100.0	R.F.	-1.5	-12	15	_	_
2N1742	PNP	60	-10	-15	-	+		1000.0	v.h.f. amp.	_	_	-	_	_
2N1742 2N1743	PNP	60	-	-15	+=	+		1000.0	v.h.f. mix.	_	_	<u> </u>	<u> </u>	T -
2N1743 3N37	TET	30	20	7		+ -	-	90.0	R,F,		_	_	-	-
SN37 CK722	PNP	180	-10	-22	10	25	800	-	-	-1.0	6	39	20 K	T -
CK722	PNP	180	-10	-10	- 10	- 23	-	3.5	I.FR.F.	-1.0	-6	_	_	T -
	SB	10	-5	-4.5	+	+=		30.0	R,F,	-0.5	-3	-	25K	T -
SB100	DND 28	30	-3	-15	+=	+		600.0	v.h.f. osc.	-		_	_	-
T-1859	PNP	30		-13	_	Two transis				3 Power output				-

¹ Common emitter circuit

² Two transistors in Class B

³ Power output watts

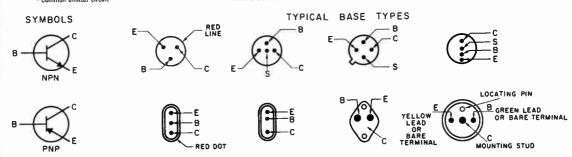

Code for identifying typical junction transistors. The leads are marked C-collector, 8-base, E-emitter and S-interlead shield and metal case.

Туре	Use	Max. Inverse Voits	Max. Average Ma.	Min. Forward Ma, ²	Max. Reverse μ-Amp.
1 N21B4	Mixer		— 3060 Mc.	10.3 db.	Overall Noise Figure
1N21C4	Mixer		— 3060 Mc.	8.3 db.	Overall Noise Figure
1 N23C4 1 N254	Mixer		— 9375 Mc.		Overall Noise Figure
1N34	Mixer General Purpose		— 1000 Mc.		verall Noise Figure
1 N34A	General Purpose	60 75	50	5.0	800 @ −50 V.
1 N 3 5	General Purpose	50	22.5	5.0 7.5	500 @ −50 V.
1 N38	General Purpose	100	50	3.0	100 @ -10 V.
1N38A	General Purpose	100	50	4.0	625 @ -100 V.
1 N39A	General Purpose	225	40	4.0	500 @ −100 V. 600 @ −200 V.
1N48	General Purpose	85	50	4.0	833 @ -50 V.
1N52A	General Purpose	85	50	5.0	100 @ -50 V.
1 N54A	Hi-Back Resistance	75	50	5.0	100 @ -50 V.
1N55A	General Purpose	170	50	4.0	500 @ −150 V.
1 N 56 A 1 N 58 A	Hi-Conduction	50	60	15.0	300 @ −30 V.
1N60	General Purpose Vid. Detector	115	50	4.0	600 @ −100 V.
1 N63	Hi-Back Resistance	25 125	50 50	5.0	40 @ −20 V.
1 N64	Vid. Detector	20	50	4.0 0.1	50 @ -50 V.
1N65	General Purpose	85	50	2.5	25 @ -1.3 V.
1 N66A	General Purpose	60	50	5.0	200 @ -50 V. 800 @ -50 V -
1 N67	Hi-Back Resistance	80	35	4.0	50 @ -50 V.
1N67A	Hi-Back Resistance	100	50	4.0	50 @ -50 V.
1N68	Hi-Back Resistance	100	35	3.0	625 @ -100 V.
1 N68A	General Purpose	100	50	3.0	625 @ −100 V.
1 N69A	General Purpose	75	40	5.0	500 @ −50 V.
1N70A 1N77A	General Purpose	125	30	3.0	300 @ −50 V.
1 N81	Photo Diode General Purpose	50 V.,			
1N82	Mixer	Max. Freq.	30	3.0	10 @ −10 V.
1 N82A	Mixer	Max. Freq.			veralt Noise Figure
1 N89	Restorer	80	30	3.5	veralf Noise Figure
1N90	General Purpose	75	30	5.0	100 @ −50 V. 750 @ −50 V.
1 M91 ·	Pwr. Rectifier	100	150	470 @ 0.5 V.	2700 @ -100 V.
1 N95	General Purpose	60	250	10.0	500 @ -50 V.
1N96	General Purpose	60	250	20.0	500 @ -50 V.
1 N97 1 N98	General Purpose	80	250	10.0	100 @ −50 V.
1N99	Hi-Back Resistance General Purpose	100	250	20.0	100 @ −50 V.
1N100	General Purpose	80	300 300	10.0	50 @ -50 V.
1N116	General Purpose	60	30	20.0 5.0	50 @ −50 V.
1N117	General Purpose	60	30	10.0	100 @50 V. 100 @ -50 V.
1N118	General Purpose	60	30	20.0	100 @ -50 V.
1 N126A	General Purpose	75	30	5.0	850 @ -50 V.
1N127A	General Purpose	125	30	3.0	300 (a −50 V,
1 N128	General Purpose	50	30	3.0	10 @ −10 V.
1N151 1N152	General Purpose General Purpose	100	500	1570 @ 0.7 V.	2400 @ -100 V.
1N153	General Purpose	200 300	500	1570 @ 0.7 V.	1900 @ −200 V.
1 N158	Pwr. Rectifier	380	500 500	1570 @ 0.7 V.	1200 @ −300 V.
1N191	Computer	90	30	5.0	-
1N192	Computer	70	30	5.0	25 @ -10 V. 50 @ -10 V.
1N198A	Hi-Temperature	100	30	4.0	250 @ -50 V. (75°C)
1N279	Hi-Conduction	35	_	100,0	200 @ -20 V.
1 N283	Hi-Conduction	25	_	200.0	80 @ -10 V.
1 N294	Switching	70	60	5.0	800 @ 50 V.
1 N 295 1 N 448	Vid. Detector	40		_	
1 N634	100-Volt Computer 60-Volt Very Low Z	120		25.0	100 @ −100 V.
1N636	General Purpose	120 75		50.0	115 @ −100 V.
2E4	Silicon Power Rectifier	400	200	2.5	20 @. −20 V.
5E4	Silicon Power Rectifier	400	350	-	
5E5	Silicon Power Rectifier	500	350		-
5E6	Silicon Power Rectifier	600	350		
HBI	Zener Diode (Zener Volts-7.5)	6.8	85	17.0	5 @ -3.5 V.
HB2	Zener Diode (Zener Volts-20)	18	50	5.0	5 (a, -10 V.
HB3	Zener Diode (Zener Volts-40)	36	30	2.7	10 (a −20 V.
HB4 HB5	Zener Diode (Zener Volts-75)	75	17	0.9	20 (a −39 V.
HB6	Zener Diode (Zener Volts-170) Zener Diode (Zener Volts-300)	150	12	3.03	40 (a -82 V.
M150	Silicon Power Rectifier	270	9	1.53	70 @ -150 V.
M500	Silicon Power Rectifier		Max.	Rms. Input: 130 V., Peak Inv	erse: 360 V., D.C. Current: 150 Ma.
			ingx.	mins, imput: 130 V., Peak Inv	erse: 400 V., D.C. Current: 500 Ma.

 ¹ A bar, plus sign, or color dot denote the cathode end of crystal diodes. Diode color code rings are grouped toward the cathode end.
 2 At +4 Volts.
 3 At +4 Volts.
 4 Polarity is such that the base is the anode and the tip is the cathode, R-types have opposite polarity.

Index

Text A	Antenna Gain
PAGE	Antenna Length
"A" Battery	Antenna Masts
"A"-Frame Mast	Antenna Matching381–385
A-1 Operator Club	Antenna, Wire Breaking Load 510
A.C	Antennas:
A.C. Line Filters554	Beams
A.G.C. 101	Bent
A.M. (see "Amplitude Modulation") 58	Construction
ARRL Emblem Colors 582	Trumber b Bongment to the trumber of the
ARRL Operating Organization581-585	Compact 11 1120 C Later and Later an
Abbreviations for C.W. Work	Rotary Beams
Absorption Frequency Meters	Supports
Affiliation, Club	Dipole
Air-Insulated Lines	Folded Dipole
Alignment, Receiver	Ground-Plane
"All-Band" Antennas	Half-Wave
Alternating Current	Halo 490
Alternations	Long-Wire
Aluminum Finishing 505	Mobile485–492
Amateur Bands 14	Multiband
Amateur Radio Emergency Corps578-580	Off-Center Fed
Amateur Radio History 9-13	Quad379–381
Amateur Operator and Station Licenses 13	Receiving 385 Resonating Remote 489
Amateur Regulations	
Amateur's Code, The	Restricted Space
American Radio Relay League:	Switching 385
Headquarters	"Trap"
Joining the League	V-Beam
Ampere	Vertical
Amplification 61–67, 81	V.H.F453-464
Amplification Factor 62	"Windom"
Amplification Factor, Current	160-Meter
Amplification Factor, Voltage62-63	Antinode
Amplifier Adjustment	Antistatic Powder
Amplifier, Cathode Follower	
Amplifier Classifications	Appointments, Station
Amplifier, Grounded-Grid70-71, 164-165 Amplifier Keying244	Arrays in Combination
Amplifier Keying	Assembling a Station
Amplifier, Speech	Atmospheric Bending
	Atoms
Amplifiers (see basic classifications, e.g., "Receivers," "Transmitters," "Radiotelephony," and "V.H.F.")	Audio-Amplifier Classifications65-67
telephony," and "V.H.F.")	Audio-Circuit Rectification 553
Amplifiers, Class A, B, C	Audio Converters
Amplifiers, Resistance Coupled 257	Audio Frequencies
Amplifiers, Transistors83-84, 109	Audio Frequency Shift Keying
Amplitude, Current	Audio Harmonics, Suppression of 262 Audio Image 106
Amplitude Modulation	Audio Image 106 Audio Limiting 102
Angle of Radiation	Audio Oscillators
Anode	Audio Oscinators
Antenna Couplers	Audio Range Restriction
Antenna Diameter vs. Length	Audio Squelch
	-

## Comparison of Capacitance Capacitance	Auroral Reflection PAGE 400 Autodyne Reception 86, 91 Automatic Gain Control 101, 102 Automobile Storage Battery 495 Autotransformer 40 Average-Current Value 17 Awards 582-584	Buncher
Baud 251 CHU 522 BCI 552 CL Computation 531 B.F.O. 101 CR and L/R Time Constants 30-31 BPL 585 Cable Lacing 507 Back Current 80 Cable Stripping 506 Back-E.M.F. 26, 31, 32 Calibrator Crystal 137, 520 Back Resistance 80 Capacitance and Capacitors 23-25 Back Scatter 397, 401 Distributed 54 Back Scatter 397, 401 Distributed 54 Balanced Circuit 54 Feedback 69 Balanced Modulator 303-304 Feedback 69 Band-Pass Filters 92-93 Interelectrode 68-79, 161 Band-Pass Filters 50-51 Parallel 25 Bands, Amateur 14 Plate Tank 150 Bandwidth, Antenna 360 Series 25 Base, Transistor 81 Tube Output 69 Bazooka 384 Ca		C (Capacitance)
SCI	Baud 251	
BPL 585 Cable Lacing 507 Back Current 80 Cable Stripping 506 Back Resistance 80 Capacitance and Capacitors 23-25 Back Resistance 397, 401 Capacitance and Capacitors 23-25 Back Wave 244 Baffle Shields 54 Baffle Shields 54 Feedback 69 Balanced Circuit 54 Feedback 69 Balun 303-304 Fromula 24 Band-Changing Receivers 92-93 Hand-Pass Filters 48 Inductance, and Frequency Charts 45 Band-Pass Filters 50-51 Parallel 25 Bandspreading 92 Bandwidth, Antenna 360 Measurement 531 Bander Radio Propagation Predictions 398 Series 25 Bastery, Service Life 501 Series 25 Battery 16, 59-62, 495, 501 Capacitance-Resistance Time Constant 30-31 Capacitors-Input Filter 222 Capacitors-Input Filter		CL Computation
Back Current 80 Cable Stripping 506 Back-E.M.F. 26, 31, 32 Calibrator Crystal 137, 520 Back Resistance 80 Capacitance and Capacitors 23-25 Back Scatter 397, 401 Capacitance and Capacitors 23-25 Bash Shields 54 Feedback 69 Balanced Circuit 54 Feedback 69 Balanced Modulator 303-304 Feedback 69 Band-Changing Receivers 92-93 Feedback 69 Band-Pass Coupling 48 Measurement 157 Bands, Amateur 14 Place Tank 150 Bandspreading 92 Parallel 25 Bandwidth, Antenna 360 Specific Inductive 23 Bandwidth, I.F. 87 Tube Output 68-69 Basic Radio Propagation Predictions 398 Reactence 33, 45 Bazock Radio Propagation Predictions 398 Reactence 33, 45 Beam Element Lengths 378, 455 Band-Setting	BPL	
Back Resistance 80 Capacitance and Capacitors 23-25 Back Scatter 397, 401 Sapacitance: Backwave 244 Distributed 54 Baffle Shields 54 Feedback 69 Balanced Circuit 54 Feedback 69 Balun 303-304 Grid Tank 157 Balun 350, 384, 541 Inductance, and Frequency Land Band-Changing Receivers 92-93 Inductance, and Frequency Land Band-Changing Receivers 92-93 Measurement 45 Band-Pass Filters 50-51 Measurement 531 Bands, Amateur 14 Plate Tank 150 Bandspreading 92 Series 25 Bandwidth, Antenna 360 Specific Inductive 23 Bastery 16, 59-62, 495, 501 Capacitance Resistance Time Constant 30-31 Battery 16, 59-62, 495, 501 Reactance 33, 45 Beam Element Lengths 375-381, 455 Band-Setting Band-Setting </td <td>Back Current 80</td> <td>Cable Stripping 506</td>	Back Current 80	Cable Stripping 506
Back Scatter 397, 401 Capacitance: 54 Baffle Shields 54 Feedback 69 Balanced Circuit 54 Feedback 69 Balanced Modulator 303–304 Grid Tank 157 Balun 350, 384, 541 Inductance, and Frequency Charts 45 Band-Changing Receivers 92–93 Measurement 531 Band-Pass Filters 50–51 Parallel 25 Bands, Amateur 14 Plate Tank 150 Bandwidth, Antenna 360 Series 25 Bandwidth, I.F. 87 Tube Input 68–69 Bastery 16, 59–62, 495, 501 Tube Output 69 Bazooka 384 Reactance 33, 45 Baeam Element Lengths 375–381, 456 Reactance 33, 45 Beam Tetrodes 70 Bandspread 92 Beat Frequencies 58 Buffer 497 Beat Oscillator 86, 100–101 Capacitors 53, 170, 560	Back Resistance 80	
Baffle Shields 54 Feedback 69 Balanced Circuit 54 Formula 24 Balanced Modulator 303-304 Grid Tank 157 Balun 350, 384, 541 Inductance, and Frequency Charts 45 Band-Pass Coupling 48 Measurement 531 Band-Pass Filters 50-51 Parallel 25 Bandspreading 92 Series 25 Bandwidth, Antenna 360 Series 25 Bandwidth, I.F 87 Tube Input 68-69 Basic Radio Propagation Predictions 398 Tube Output 69 Battery 16, 59-62, 495, 501 Capacitive Coupling 46, 158, 563 Battery 16, 59-62, 495, 501 Reactance 33, 45 Bazooka 384 Reactance 33, 45 Beam Element Lengths 375-381, 456 Band-Setting 92 Beat Frequencies 58 Band-Setting 92 Beat Note 86, 100-101 Bypas 53, 170, 560	Back Scatter	Capacitance:
Balanced Circuit 54 Formula 24 Balanced Modulator 303–304 Grid Tank 157 Balun 350, 384, 541 Inductance, and Frequency Charts 45 Band-Pass Coupling 48 Inductance, and Frequency Charts 45 Band-Pass Filters 50–51 Measurement 531 Bands Amateur 14 Plate Tank 150 Bandspreading 92 Series 25 Bandwidth, Antenna 360 Series 25 Base, Transistor 81 Tube Input 68–69 Bastery 16, 59–62, 495, 501 Tube Output 69 Bazooka 384 Reactance 33, 45 Beam Element Lengths 375–381, 456 Reactance 33, 45 Beam Tetrodes 70 Band-Setting 92 Beat Frequencies 58 Band-Setting 92 Band-Setting 92 Band-Setting 92 Band-Setting 92 Band-Setting 92	Baffle Shields 54	
Balun	Balanced Circuit	Formula 24
Band-Changing Receivers 92-93 Interelectrode 68-79, 161 Band-Pass Coupling 48 Measurement 531 Band-Pass Filters 50-51 Parallel 25 Bands, Amateur 14 Plate Tank 150 Bandspreading 92 Series 25 Bandwidth, Antenna 360 Specific Inductive 23 Bandwidth, I.F. 87 Tube Input 68-69 Basic Radio Propagation Predictions 398 Tube Output 69 Battery 16, 59-62, 495, 501 Capacitive Coupling 46, 158, 563 Battery 501 Reactance 33, 45 Bazooka 384 Capacitive Coupling 46, 158, 563 Reactance 33, 45 Capacitor-Input Filter 222 Capacitors: Band-Setting 92 Bean Tetrodes 70 Bandspread 92 Beat Frequencies 58 Buffer 497 Beat Oscillator 86, 100-101 Ceramic 509	Balun	
Band-Pass Filters 50-51 Parallel 25 Bands, Amateur 14 Plate Tank 150 Bandspreading 92 Series 25 Bandwidth, Antenna 360 Specific Inductive 23 Bandwidth, I.F. 87 Tube Input 68-69 Basse, Transistor 81 Tube Output 69 Bastery 16, 59-62, 495, 501 Capacitive Coupling 46, 158, 563 Battery 501 Reactance 33, 45 Bazooka 384 Reactance 33, 45 Beam Element Lengths 375-381, 456 Band-Setting 92 Beat Frequencies 58 Buffer 497 Beat Note 86 Bypass 53, 170, 560 Beat Oscillator 86, 100-101 Ceramic 509	Band-Changing Receivers92–93	Interelectrode
Bands, Amateur 14 Plate Tank 150 Bandspreading 92 Series 25 Bandwidth, Antenna 360 Specific Inductive 23 Bandwidth, I.F. 87 Tube Input 68-69 Base, Transistor 81 Tube Output 69 Bastery 16, 59-62, 495, 501 Capacitance-Resistance Time Constant 30-31 Battery, Service Life 501 Reactance 33, 45 Bazooka 384 Reactance 33, 45 Beam Antennas 375-381, 456 Capacitor-Input Filter 222 Capacitors: Band-Setting 92 Beat Frequencies 58 Buffer 497 Beat Oscillator 86, 100-101 Ceramic 509	Band-Pass Filters 50-51	
Bandwidth, Antenna 360 Specific Inductive 23 Bandwidth, I.F. 87 Tube Input 68-69 Base, Transistor 81 Tube Output 69 Baster Radio Propagation Predictions 398 Capacitance-Resistance Time Constant 30-31 Battery 16, 59-62, 495, 501 Capacitive Coupling 46, 158, 563 Bazooka 384 Reactance 33, 45 Beam Antennas 375-381, 456 Capacitors: Capacitors: Beam Element Lengths 378, 455 Band-Setting 92 Beat Frequencies 58 Buffer 497 Beat Oscillator 86, 100-101 Egypas 53, 170, 560	Bands, Amateur	Plate Tank 150
Bandwidth, I.F. 87 Tube Input. 68-69 Base, Transistor 81 Tube Output. 69 Bastic Radio Propagation Predictions 398 Capacitance-Resistance Time Constant 30 31 Battery, Service Life 501 React Coupling 46, 158, 563 Bazooka 384 Reactance 33, 45 Beam Antennas 375-381, 456 Capacitor-Input Filter 222 Beam Tetrodes 70 Band-Setting 92 Beat Frequencies 58 Buffer 497 Beat Note 86, 100-101 Sepans 53, 170, 560 Geramic 509 Ceramic 509	Bandwidth, Antenna 360	
Basic Radio Propagation Predictions 398 Capacitance-Resistance Time Constant 30-31 Battery 16, 59-62, 495, 501 Capacitive Coupling 46, 158, 563 Battery, Service Life 501 Reactance 33, 45 Bazooka 384 Capacitor-Input Filter 222 Beam Antennas 375-381, 456 Capacitor-Input Filter 222 Beam Element Lengths 378, 455 Band-Setting 92 Beat Frequencies 58 Buffer 497 Beat Note 86 Bypass 53, 170, 560 Beat Oscillator 86, 100-101 Ceramic 509	Bandwidth, I.F	Tube Input
Battery. 16, 59-62, 495, 501 Capacitive Coupling 46, 158, 563 Battery, Service Life 501 Reactance 33, 45 Bazooka 384 Capacitor-Input Filter 222 Beam Antennas 375-381, 456 Capacitors: Band-Setting 92 Beam Tetrodes 70 Band-Setting 92 Beat Frequencies 58 Buffer 497 Beat Note 86 Bypass 53, 170, 560 Beat Oscillator 86, 100-101 Ceramic 509	Basic Radio Propagation Predictions 398	Tube Output
Bazooka 384 Beam Antennas Capacitor-Input Filter 222 Beam Antennas 375–381, 456 Capacitors: 92 Beam Element Lengths 378, 455 Band-Setting 92 Beam Tetrodes 70 Bandspread 92 Beat Frequencies 58 Buffer 497 Beat Note 86 Bypass 53, 170, 560 Beat Oscillator 86, 100–101 Ceramic 509	Battery16, 59-62, 495, 501	Capacitive Coupling 46, 158, 563
Beam Antennas .375–381, 456 Capacitors: Beam Element Lengths .378, 455 Band-Setting 92 Beam Tetrodes .70 Bandspread 92 Beat Frequencies .58 Buffer .497 Beat Note .86 Bypass .53, 170, 560 Beat Oscillator .86, 100–101 Ceramic .509	Bazooka	
Beam Tetrodes 70 Bandspread 92 Beat Frequencies 58 Buffer 497 Beat Note 86 Bypass 53, 170, 560 Beat Oscillator 86, 100-101 Ceramic 509	Beam Antennas	Capacitors:
Beat Frequencies 58 Buffer 497 Beat Note 86 Bypass 53, 170, 560 Beat Oscillator 86, 100–101 Ceramic 509	Beam Tetrodes 70	
Beat Oscillator	Beat Frequencies	Buffer
	Beat Oscillator 86, 100–101	Bypass
	Bending, Tropospheric	Color Code
Bias	Bias	
Bias, Cathode 72 Fixed 24	Bias, Cathode	Fixed 24
Bias, Fixed	Bias, Fixed 155	
Bias, Operating 154-156 Neutralizing 160	Bias, Operating	Neutralizing
Bias Stabilization	Bias Stabilization	
Bias Supplies 234–237 Plate Blocking 170 "Birdies" 94, 114 Plate Spacing 169	Bias Supplies	Plate Blocking
Bleeder	Bleeder	Plate Tank Voltage 169
Blocked-Grid Keying. 246, 249 Ratings. 152 Blocking Capacitor. 53 Semiconductor, Voltage-Variable 81, V34	Blocked-Grid Keying	Ratings
Booms, Rotary Beam	Booms, Rotary Beam	Trimmer
Brass Pounders League 585 Variable 24–25 Breakdown Voltage 23, 24, 25, 169 Carbon Microphone 255	Breakdown Voltage 23 24 25 160	Variable24-25
Break-In	Break-In	Carrier
Bridge Rectifiers 219 Carrier Suppression 303 Bridge-Type Standing-Wave Indicators 534-538 Carriers, Semiconductor 79	Bridge-Type Standing-Wave Indicators 534_538	Carrier Suppression
Bridge, Impedance 538 Cascade Amplifiers 66	Bridge, Impedance	Cascade Amplifiers
Broadband Antennas, V.H.F	Broadcast Interference Elimination of 559	Cascode R.F. Amplifiers 403
Broadside Arrays	Broadside Arrays	Cathode
Buffer Amplifier	Buffer Capacitors 144, 285 Buffer Capacitors 497	Cathode-Bias
204, 203	101	201, 200 Capations

PAGE	PAGE
Cathode-Coupled Clipper	Color Codes, EIA
Cathode, Directly Heated 60	Color Television
Cathode Follower	Colpitts Circuit
Cathode, Indirectly Heated 60	Combination Arrays
Cathode Injection 95	Compact Antennas
Cathode Keying. 244	Compact 14-Mc. 3-Element Beam 390
Cathode Modulation	Complex Waves
Cathode Modulation Performance Curves. 293	Component Ratings and Installation
Cathode Ray Oscilloscopes	100 151 005
	Component Values
Cathode Pagistar V32	Component values
Cathode Resistor	Compression, Speech Amplifier
Catwhisker	Concentric-Line Matching Section 381
Cavity Resonators	Concentric Transmission Line 348
Cell	Condenser (see Capacitor)
Center Loading, Mobile Antenna 487	Conductance 19
Center-Tap, Filament 71	Conductance, Mutual 62
Center-Tap Full-Wave Rectifier	Conductivity
Center-Tap Keying	Conductor Size, Antennas
Ceramic Microphone	Conductors
Channel Width	Cone Antennas, V.H.F
Characteristic Curves61-62, 80, 82, 83	Conelrad142, 493, 585
Characteristic, Impedance341, 347	Constant, Time
Characteristics, Dynamic	Constants, LC
Characteristics of Radio Waves394–395	Constant-Voltage Transformers 240
Charges, Electrical	Construction, Antenna385–393
Charging, Capacitor	Construction, Coupler
Chassis Layout	Construction Practices
Chirp, Keying	Construction Tools
Choke:	Contact-Potential Bias72-73
Coil	Continental Code
Filter	Control Circuits, Station546-547
Radio-Frequency	Control Grid 61
Swinging	Controlled Carrier
Choke-Coupled Modulation 288	Conversion Efficiency 94
Choke-Input Filter	Conversion, Frequency
Circuit Symbols	Conversion of Fractional and Multiple
Circuit Tracking	Units
Circuits, Balanced and Single-Ended 54	Converter Tube Operating Values 95
Clamp Tubes	Converters, Audio
Clamp Tube Modulation	Converters, Frequency
Clapp Oscillator	Converters, Teletype
Class A Amplifiers	Converters, V.H.F
Class AB Amplifiers	Converters, U.H.F
Class B Amplifiers	Copper-Wire Table
Class B Modulators	Cores
Class C Amplifiers 67	Corner Reflector Antenna, V.H.F 461
Clicks, Keying	Corrective Stub
Clipping Circuits	Counterpoise
Clipping-Filter Circuit	Countries List, ARRL
Clipping, Speech	Coupled Circuits
Club Affiliation	Couplers, Antenna
Coax-Coupled Matching Circuit 351	Construction
Coaxial Antennas, V.H.F	Coupling 29
Coaxial-Line Circuits	Coupling:
Coaxial Line Data	Antenna to Receiver
Coaxial-Line Matching Section	Amplifier-Output
Coaxial Plug Connections 507	Antenna to Line
Coaxial Transmission Lines	Band-Pass
Code (Continental) and Code Practice13-14	Capacitive
Code Proficiency Award 584	Capacitor64
Code, Underwriters550-551	Choke
Coefficient of Coupling	Circuits46, 64
Coefficient, Temperature	Close
Coil (see "Inductance")	Coefficient of
Coils, Dimensions of	Critical
Coils, Winding	Feedline
Coils, Wire Sizes for Transmitting 170	Impedance 64
Collector	Inductive
Collinear Arrays 375, 455, 456, 461	Interstage

PAGE	PAGE
Link48, 150, 157	D.C
Loose	D.C. Instruments512-515
Pi-Section	D.C. Measurements
Resistance 64	Decay, Voltage
Tight	Decibel
To Flat Coaxial Lines	Decimal Equivalents of Fractions 505
To Wave Guides and Cavity Resonators 57	Deflection Plates
Transformer 46, 64, 257 Transmitter to Line 351	Degeneration
Tuned	Degree, Phase
Critical:	Demodulation
Angle	Density, Flux
Coupling. 47	Design of Speech Amplifiers
Frequency	Detection
Inductance	Detector Blocking and Pull-In 91
Cross-Modulation	Detectors
Cross-Talk (Telephone)	Deviation Ratio
Crystal:	Diagrams, Schematic Symbols for 2
Diodes	Dielectric
Filters	Dielectric Constants
Microphones	Dielectric Puncture Voltage 23
Oscillators144, 145–146, 424	Difference of Potential
Rectifiers	Differential Keying
Resonator	Diode Clippers
Crystal Calibrator	Diode Detectors
Crystal-Controlled Converters	Diodes
417-423, 468, 471, 473 Crystal-Controlled Oscillators 144, 145-146, 424	Diodes, Crystal
Crystal Detector	Diodes, Voltage-Variable Capacitor 81 Diodes, Zener 80–81, V34
Crystal-Filter Phasing 106–107	Dipole
Crystal Filter, Tuning with	Dipole, Folded
Crystal, Germanium	Direct Current 16–17
Crystal-Lattice Filter	Direct Feed for Antennas
Crystals, Overtone	Directive Antennas
Crystals, Piezoelectric	Directivity, Antenna
Current:	Director, Antenna
Alternating	Directors, ARRL
Amplification Factor	Discharging, Capacitor
Antenna	Discriminator
Direct	Disk-Seal Tubes 76
Distribution, Antenna	Dissipation, Plate and Screen 156
Eddy	Distortion, Audio
Electric	Distortion, Harmonic
Gain 82	Dividers, Voltage
Lag and Lead	Divisions, ARRL 12
Loop343, 362	Doubler, Frequency 144
Magnetizing	Double-Humped Resonance Curve 48
Measurement	Double Sideband
Node343, 362	Double Superheterodyne
Plate 60	Downward Modulation 284
Pulsating	Drift, Frequency
Ratio, Decibel	Drift Transistor 82
Values	Drill Sizes (Table) 503
Curve Resonance	Driven-Element Directive Antennas 375
Curves, Tube-Characteristic	Driver
Cut-Off Frequency 82	Dummy Load
Cut-Off, Plate-Current 61-62. 70	DXCC
C.W. Abbreviations 589	DX Century Club Award 583-584
C.W. Procedure	DX Operating Code
C.W. Reception	Dynamic:
Cycle	Characteristics 62
Cyclic Variations in Ionosphere	Instability 74
D	
-	Dynamometer Movement
D'Arsonval Movement	Dynamotors
D Region	Dynatron-Type Oscillator

PAGE	PAGE
E	Feedback
	Feedback Percentage 266
E (Voltage)	Feed, Series and Parallel
<i>E</i> Layer	Feeder Length
E.M.F., Back	Feeders and Feed Systems 341-359, 363-365
E.M.F., Induced 26	Feeding Dipole Antennas
Eddy Current Value	Feeding Long-Wire Antennas
Effective Current Value	Feeding Mobile Antennas
Efficiency	Feeding Rotary Beams
Conversion	Fidelity
Power	Field Direction
Transformer	Field, Electromagnetic
Electric Current	Field, Electrostatic
Electrical Charge	Field Intensity
Electrical Laws and Circuits15-58	Field Meanstactatic
Electrical Quantities Combala for	Field, Magnetostatic
Electrical Quantities, Symbols for	Field Strength
Electrical Safety Code, National550-551	Field-Strength Meter492, 533
Electrode	Filament
Electrode Voltages, Sources	Filament Center-Tap
Electrolytic Capacitor	Filament Hum
Electromagnetic:	Filament Isolation
Deflection	
Field	Filament Voltage
Waves	Filter Capacitors in Series
Electromotive Force (E.M.F.)	Filter Component Ratings 225
Electron:	Filter, Crystal
Gun 542	Filter Resonance
Lens	Filters50-51
Transit Time. 76	Audio
Electronic:	Band-Pass
Conduction	Basic Sections
Speed Key	Crystal-Lattice
Voltage Regulation	Cut-Off Frequency
Transmit-Receive Switch	Design Formulas
Electrons	Harmonic Suppression
Electrostatic:	High-Pass
Deflection 543	Keying
Field	Line
Element Spacing, Antenna378, 379, 455, 458	Lead
Elements, Vacuum Tube	Low-Pass
Emergency Communication	
	Mechanical
Emergency Communications580, 590	M-Derived
Emergency Coordinator	Pass-Band 51
Emergency Points	Pi-Section
Emergency Power Supply 496	Power-Supply
Emission:	R.F. Click
Electron	Stop Band
Secondary 69	Terminating Impedance
Thermionic 59	Filtering, Audio
Emitter, Transistor	Filtering, Negative-Lead. 226
End Effect	Filtering, TVI554, 558, 560, 564–566, 569
End-Fire Arrays 376	Filter-Type S.S.B. Exciters
Energy	
	Finishing Aluminum
Envelope, Modulation	First Detector
Equivalent Noise Resistance	Fixed Bias
Equivalent Series and Parallel Circuits	Fixed Capacitor
_ (A.C.)	Flat Lines 345
Excitation	Flux Density, Magnetic
Exciter Units (see "Transmitters")	Flux, Leakage
Exciting Voltage	Flux Lines
Extended Double-Zepp Antenna 375	Fly-Back 543
	Focusing Electrode 543
F	Folded Dipole
Z.	Folded Dipole Nomogram
EM (UD	Force, Electromotive
F.M. (see "Frequency Modulation")	Force, Lines of
F Layer	Form, Log 577
<u>Fading</u>	Form, Message 578
Farad	Fractions, Decimal Equivalents 505
·	,

DAGE	PAGE
Free-Space Pattern	Grid-Leak Detectors
Frequency	Grid Modulation
Frequency Bands, Amateur	Grid-Plate Capacitance
Frequency Conversion	Grid-Plate Crystal Oscillator
Frequency Convertors (Receiver)94–96	Grid-Plate Transconductance
Frequency Measurement:	Grid-Separation Circuit
Absorption Frequency Meters 518	Grid-Tank Capacitance
Frequency Standards	Ground
Heterodyne Frequency Meters	Ground Effects
Interpolation-Type Frequency Meter. 521	Ground-Plane Antenna
Precise Measurements	Ground Point, R.F
WWV and WWVH Schedules	Ground Potential
Frequency and Phase Modulation 329, 330	Ground Waves
Narrow-Band Reactance-Modulator	Grounded Antennas
Unit	Grounded-Base Circuit83
Deviation Ratio	Grounded-Collector Circuit84
Discriminator	Grounded-Emitter Circuit
Index, Modulation	Grounded-Grid Amplifier . 70–71, 163–165, 328,
Methods	402–403
On V.H.F. 425	Grounded-Grid Amplifier, Driving Power. 164
Principles 329	Grounded-Grid Amplifier-Power Output. 164
R.F. Amplifiers 334	Guys, Antenna
Reactance Modulator 332	Guys, Antenna
Reception	
Transmitter Checking 332	
Frequency Multiplication 330	H
Frequency Multipliers	
Frequency Response, Microphone 255	Half-Lattice Crystal Filter
Frequency Shift Keying	Half-Wave Antenna
Frequency Spectrum Nomenclature	Half-Wave Antenna Lengths
	Half-Wave Phasing Section
Frequency Spotting 547 Frequency Stability 285	Half-Wave Rectifiers
Frequency-Wavelength Conversion	Halo Antenna
Front End Overloading, TV	Halvards, Antenna. 387
Front-to-Back Ratio	Hang A.G.C. System 102
	Harmonic
Full-Wave Bridge Rectifiers 219 Full-Wave Center-Tap Rectifiers 218	Amateur Bands/TV 549, 555, 565, 571
Fundamental Frequency 17	Antenna
Fusing	Distortion
rusing200, 540	Generation. 557
	Reduction
_	Suppression
G	Suppression Filters
	Traps
Gain, Directive Antennas	Hartley Circuit
Gain Control	Hash Elimination 497
"Gamma" Match	Headphones 105
Ganged Tuning92–93	Heater
Gaseous Regulator Tubes	Heater Connections for 6-Volt and 6/12-
Gasoline-Engine-Driven Generators 500	Volt Tubes
Gauges, Standard Metal	Heater Voltage
Generator	Henry
Generator Noise	Heterodyne Frequency Meters 521
Germanium Crystal Diodes79-80, V34	Heterodyne Reception
Grid	Heterodyning
Bias	Hi-Fi Interference
Capacitor	High-C45, 74
Current	High Frequencies
Excitation	High-Frequency Oscillator 96
Impedance	High-Frequency Receivers
Injection, Mixer 95	High-Frequency Transmitters144-217
Keying	High-Pass Filters 50-51, 569
Leak	High-Q Circuit
Resistor	High-Vacuum Rectifiers
Suppressor	High- μ Tubes
Voltage	Hiram Percy Maxim Memorial Station12, 583
Grid-Cathode Capacitance 68-69	History of Amateur Radio 9-12
Grid-Dip Meters	Hole Conduction
Grid-Input Impedance	Hole Cutting 504

PAGE	PAGE
Holes 79	Inductive Coupling
Horizontal Angle of Radiation 360	Inductive Neutralization
Horizontal Polarization of Radio Waves 394,	Inductive Reactance
453, 490	Inductor
Hum	Inductors, Dimensions of
Hysteresis	Infinite-Impedance Detector89-90
	Input Choke
	Input Impedance
-	Input, Plate Power
I	Instability, Receiver
	Instrument Calibration
I (Current)	Instantaneous Current Value
ICAS	Insulators
I.F. 93	Interelectrode Capacitances
ITV	Interference, Television and Broadcast 552–571
Ignition Interference	Intermediate Frequency
Image	Intermediate Frequency Amplifier 97, 405
Image, Audio-Frequency	Intermediate Frequency Amplifier, Tran-
Image Ratio. 93	sistor
Image Response	Intermediate Frequency Bandwidths,
Impedance	Table99
Antenna	Intermediate Frequency Interference, TV. 568
Bridge	Intermediate Frequency Transformers 99
Characteristic	Intermediate Frequency Transformer Color
Complex	Code
Grid Input. 157	Intermittent Direct Current
Grounded-Grid Amplifier Input. 164, 321–322	International Amateur Prefixes
Folded Dipole	International Prefixes
Input70, 83, 156–157, 344	International Morse Code
Matching	Interpolation-Type Frequency Meter 521
Measurements	Interstage Coupling, Capacitive
Modulating	Interstage Coupling, Pi-Network
Output	Interstage Transformer 99
Parallel Circuits	Inverse-Distance Law of Propagation 394
Ratio	Inverse Peak Voltage, Rectifier
Resistive	
Series Circuits	Inversion, Temperature
	Ionosphere 395–400
Surge	Ionosphere Storms 397
Transformer 221	Ionospheric Propagation 395–400
Transformer Quarter-Wave 381	Ions
Transformer Ratio	Iron-Core Coils 27, 37
Transmission-Line	Hon-Core Cons
Impedance-Coupled Amplifiers	
Imperfect Ground	J
Improving Receiver Performance 115	•
Impulse Noise	Junction Diodes 80
Incident Power 349	0411011011
Incident Power	Junction Transistors 82
Index, Modulation	0411011011
Index, Modulation	Junction Transistors 82
Index, Modulation330Indicating Wavemeters519Indicators, Signal-Strength104-105	0411011011
Index, Modulation 330 Indicating Wavemeters 519 Indicators, Signal-Strength 104-105 Indicators, Tuning 104-105	Junction Transistors 82
Index, Modulation 330 Indicating Wavemeters 519 Indicators, Signal-Strength 104-105 Indicators, Tuning 104-105 Induced E.M.F. 26	Junction Transistors 82 K Keeping a Log. 577
Index, Modulation 330 Indicating Wavemeters 519 Indicators, Signal-Strength 104-105 Indicators, Tuning 104-105 Induced E.M.F. 26 Inductance 26-30	Name
Index, Modulation 330 Indicating Wavemeters 519 Indicators, Signal-Strength 104-105 Indicators, Tuning 104-105 Induced E.M.F. 26 Inductance 26-30 Calculation 26, 27	K Keeping a Log. 577 Key Chirps 148, 243 Key Clicks 243, 247
Index, Modulation 330 Indicating Wavemeters 519 Indicators, Signal-Strength 104-105 Indicators, Tuning 104-105 Induced E.M.F. 26 Inductance 26-30 Calculation 26, 27 Capacitance and Frequency Charts 45	K Keeping a Log. 577 Key Chirps 148, 243 Key Clicks 243, 247 Keyer Tubes 245
Index, Modulation 330 Indicating Wavemeters 519 Indicators, Signal-Strength 104-105 Indicators, Tuning 104-105 Induced E.M.F. 26 Inductance 26-30 Calculation 26, 27 Capacitance and Frequency Charts 45 Critical 223	K Keeping a Log. 577 Key Chirps 148, 243 Key Clicks 243, 247 Keyer Tubes 245 Keyers, Vacuum-Tube 245
Index, Modulation 330 Indicating Wavemeters 519 Indicators, Signal-Strength 104-105 Indicators, Tuning 104-105 Induced E.M.F. 26 Inductance 26-30 Calculation 26, 27 Capacitance and Frequency Charts 45 Critical 223 Distributed 54	K Keeping a Log. 577 Key Chirps 148, 243 Key Clicks 243, 247 Keyer Tubes 245 Keyers, Vacuum-Tube 245 Keying:
Index, Modulation 330 Indicating Wavemeters 519 Indicators, Signal-Strength 104-105 Indicators, Tuning 104-105 Induced E.M.F. 26 Inductance 26-30 Calculation 26, 27 Capacitance and Frequency Charts 45 Critical 223 Distributed 54 Leakage 39	K Keeping a Log. 577 Key Chirps 148, 243 Key Clicks 243, 247 Keyer Tubes 245 Keying: Amplifier 244
Index, Modulation 330 Indicating Wavemeters 519 Indicators, Signal-Strength 104-105 Indicators, Tuning 104-105 Induced E.M.F. 26 Inductance 26-30 Calculation 26, 27 Capacitance and Frequency Charts 45 Critical 223 Distributed 54 Leakage 39 Measurement 531	K K Keeping a Log. 577 Key Chirps 148, 243 Key Clicks 243, 247 Keyer Tubes 245 Keyers, Vacuum-Tube 245 Keying: 244 Amplifier 244 Audio Frequency Shift 337
Index, Modulation 330 Indicating Wavemeters 519 Indicators, Signal-Strength 104-105 Indicators, Tuning 104-105 Induced E.M.F. 26 Inductance 26-30 Calculation 26, 27 Capacitance and Frequency Charts 45 Critical 223 Distributed 54 Leakage 39 Measurement 531 Mutual 29-30	K Keeping a Log. 577 Key Chirps 148, 243 Key Clicks 243, 247 Keyer Tubes 245 Keyens, Vacuum-Tube 245 Keying: Amplifier 244 Audio Frequency Shift 337 Back Wave 244
Index, Modulation 330 Indicating Wavemeters 519 Indicators, Signal-Strength 104-105 Indicators, Tuning 104-105 Induced E.M.F. 26 Inductance 26-30 Calculation 26, 27 Capacitance and Frequency Charts 45 Critical 223 Distributed 54 Leakage 39 Measurement 531 Mutual 29-30 Parallel 29	K Keeping a Log. 577 Key Chirps 148, 243 Key Clicks 243, 247 Keyer Tubes 245 Keyers, Vacuum-Tube 245 Keying: Amplifier 244 Audio Frequency Shift 337 Back Wave 246, 248 Break-In 246, 248
Index, Modulation 330 Indicating Wavemeters 519 Indicators, Signal-Strength 104-105 Indicators, Tuning 104-105 Induced E.M.F. 26 Inductance 26-30 Calculation 26, 27 Capacitance and Frequency Charts 45 Critical 223 Distributed 54 Leakage 39 Measurement 531 Mutual 29-30 Parallel 29 Plate Tank 169	K Keeping a Log. 577 Key Chirps 148, 243 Key Clicks 243, 247 Keyer Tubes 245 Keyers, Vacuum-Tube 245 Keying: Amplifier 244 Audio Frequency Shift 337 Back Wave 244 Break-In 246, 248 Differential 246 246
Index, Modulation 330 Indicating Wavemeters 519 Indicators, Signal-Strength 104-105 Indicators, Tuning 104-105 Induced E.M.F. 26 Inductance 26-30 Calculation 26, 27 Capacitance and Frequency Charts 45 Critical 223 Distributed 54 Leakage 39 Measurement 531 Mutual 29-30 Parallel 29 Plate Tank 169 Series 29	K Keeping a Log. 577 Key Chirps 148, 243 Key Clicks 243, 247 Keyer Tubes 245 Keyers, Vacuum-Tube 245 Keying: Amplifier 244 Audio Frequency Shift 337 Back Wave 244 Break-In 246, 248 Differential 246 Frequency Shift 337, 339
Index, Modulation 330 Indicating Wavemeters 519 Indicators, Signal-Strength 104-105 Indicators, Tuning 104-105 Induced E.M.F. 26 Inductance 26-30 Calculation 26, 27 Capacitance and Frequency Charts 45 Critical 223 Distributed 54 Leakage 39 Measurement 531 Mutual 29-30 Parallel 29 Plate Tank 169 Series 29 Slug-Tuned 93	K Keeping a Log. 577 Key Chirps 148, 243 Key Clicks 243, 247 Keyer Tubes 245 Keying: Amplifier 244 Audio Frequency Shift 337 Back Wave 244 Break-In 246, 248 Differential 246 Frequency Shift 337, 339 Grid-Block 245, 249 Septimental 246 248 Septimental 246 248 Septimental 246 246 Septimental Septimental Septi
Index, Modulation 330 Indicating Wavemeters 519 Indicators, Signal-Strength 104-105 Indicators, Tuning 104-105 Induced E.M.F. 26 Inductance 26-30 Calculation 26, 27 Capacitance and Frequency Charts 45 Critical 223 Distributed 54 Leakage 39 Measurement 531 Mutual 29-30 Parallel 29 Plate Tank 169 Series 29 Slug-Tuned 93	K Keeping a Log. 577 Key Chirps 148, 243 Key Clicks 243, 247 Keyer Tubes 245 Keyers, Vacuum-Tube 245 Keying: Amplifier 244 Audio Frequency Shift 337 Back Wave 246 248 Differential 246 248 Differential 246 Frequency Shift 337, 339 Grid-Block 245 249 Key-Click Reduction 243, 247 246 248 Chey-Click Reduction 243, 247 246 248 Chey-Click Reduction 243, 247 247 248 Chey-Click Reduction 243, 247 248 Chey-Click Reduction 244 Ch
Index, Modulation 330 Indicating Wavemeters 519 Indicators, Signal-Strength 104-105 Indicators, Tuning 104-105 Induced E.M.F. 26 Inductance 26-30 Calculation 26, 27 Capacitance and Frequency Charts 45 Critical 223 Distributed 54 Leakage 39 Measurement 531 Mutual 29-30 Parallel 29 Plate Tank 169 Series 29 Slug-Tuned 93 Small Coil 27, 28 Inductance-Resistance Time Constant 30-31	K K Keeping a Log. 577 Key Chirps. 148, 243 Key Clicks. 243, 247 Keyer Tubes. 245 Keyers, Vacuum-Tube. 245 Keying: 244 Amplifier. 244 Audio Frequency Shift. 337 Back Wave. 244 Break-In. 246, 248 Differential. 246 Frequency Shift. 337, 339 Grid-Block 245, 249 Key-Click Reduction 243, 247 Methods. 244-248
Index, Modulation 330 Indicating Wavemeters 519 Indicators, Signal-Strength 104-105 Indicators, Tuning 104-105 Induced E.M.F. 26 Inductance 26-30 Calculation 26, 27 Capacitance and Frequency Charts 45 Critical 223 Distributed 54 Leakage 39 Measurement 531 Mutual 29-30 Parallel 29 Plate Tank 169 Series 29 Slug-Tuned 93 Small Coil 27, 28 Inductance-Resistance Time Constant 30-31 Inductance in Series and Parallel 29	K Keeping a Log. 577 Key Chirps 148, 243 Key Clicks 243, 247 Keyers, Vacuum-Tube 245 Keying: Amplifier 244 Audio Frequency Shift 337 Back Wave 244 Break-In 246, 248 Differential 246 Frequency Shift 337, 339 Grid-Block 245, 249 Key-Click Reduction 243, 247 Methods 244-248 Monitoring 248, 250
Index, Modulation 330 Indicating Wavemeters 519 Indicators, Signal-Strength 104-105 Indicators, Tuning 104-105 Induced E.M.F. 26 Inductance 26-30 Calculation 26, 27 Capacitance and Frequency Charts 45 Critical 223 Distributed 54 Leakage 39 Measurement 531 Mutual 29-30 Parallel 29 Plate Tank 169 Series 29 Slug-Tuned 93 Small Coil 27, 28 Inductance-Resistance Time Constant 30-31	K Keeping a Log. 577 Key Chirps. 148, 243 Key Clicks. 243, 247 Keyer Tubes. 245 Keyers, Vacuum-Tube. 245 Keying: 244 Audio Frequency Shift. 337 Back Wave. 244 Break-In. 246, 248 Differential. 246 Frequency Shift. 337, 339 Grid-Block 245, 249 Key-Click Reduction 243, 247 Methods. 244-248 Monitoring. 248, 250

PAGE	PAGE
Speeds	Load Resistor
	Loaded Circuit Q
Keys, Speed	Boarding Coll Barrett College
Keys, Electronic	Local Oscillator93
Keys, Electronic, Speed Adjustment of 251	Log, Station 577
Kilocycle	Long-Wire Antennas366-367
Kilowatt	Long Wire Antenna Lengths 366
Kilowatt Hour	Long-Wire Directive Arrays
Klystrons	Loops, Current and Voltage 362
	Losses, Hysteresis
	Losses in Transmission Lines
L	Loudspeaker Coil Color Code
-	Loudspeakers
L (Inductance)	Low-C
	Low-Frequencies
LC Computation	
LC Constants	Low-Pass Filters50-51, 569
L/C Ratios45-46, 151-152, 290	Low-Q
L Network	Low- μ Tubes
L/R Time Constant	
Lacing Cable	
Lag Circuits 244	M
Lag, Current or Voltage32–37	
Laminations	M.U.F. (see "Maximum Usable Fre-
Laws Concerning Amateur Operations 13	quency")396, 399
Laws, Electrical15–58	Magnetic Storms
Lazy-H Antenna	Magnetizing Current
Lead, Current or Voltage	Magnetrons
Lead-In, Antenna	Majority Carriers
Leakage Current	Marker Frequencies
Leakage Flux	Masts
Leakage Inductance. 39	Matched Lines
	Matching, Antenna
	Matching-Circuit Construction
Learning the Radiotelegraph Code	
Level, Microphone	Maximum Average Rectified Current 80
License Manual, The Radio Amateur's 13	Maximum Safe Inverse Voltage 80
Licenses, Amateur	Maximum Usable Frequency396, 399
Light, Speed of	Measurements:
"Lighthouse" Tubes	Antenna
Lightning Arrester	Capacitance
Lightning Protection	Current513, 528
Limiter Circuits	Field Strength
Limiters, Noise	Frequency
Limiting Resistor	Impedance
Line Filters	Inductance
Line, Open-Circuited	Keying
Line Radiation	Modulation
Line-Voltage Adjustment 239	Phase 32
Linear Amplifier Tube Operation,	Power
Grounded Cathode	Radio Frequency 528
Linear Amplifier Tube Operation,	Resistance
Grounded Grid	Standing-Wave Ratio
Linear Amplifiers	Transmission Line
Linear Baluns	Voltage
Linear Sweep	Measuring Instruments
Linear Transformers	Mechanical Filter 107
Linearity	Medium of Propagation
Lines, Coaxial	Medium- μ Tubes 62
Lines, Matched	Megacycle
Lines of Force	Megohm
Lines, Nonresonant and Resonant 345	Mercury-Vapor Rectifiers
Lines, Parallel Conductor	Message Form
Lines, Transmission	Message Handling
Lines, Unterminated	Metal Gauges, Standard 505
Link Coupling	Metal, Resistivity of
Link Neutralization	Meteor Trails 401
Lissajous Figures 544	Metering
Load, Antenna	Meters, Volt-Ohm-Milliampere 517
Load Impedance	Meter Accuracy 513
Load Isolation, V.F.O. 147–148	Meter Installation

PAGE	PAGE
Meter Multiplier	Modulators (see "Radiotelephony") 261 "Monimatch"
Meter Switching	"Monimetch" 357 537
Mho	M'4
7	Monitors248, 250, 301, 544
Microampere	Motorboating 114
Microfarad and Micromicrofarad 24	Moving-Vane Instrument
Microhenry	
Micronetity	$\operatorname{Mu}\left(\mu\right)$
Micromho	Mu, Variable 70
Microphones	Multiband Antennas
	Multiband Tonk Circuits
Microvolt	Multiband Tank Circuits
Microwaves	Multihop Transmission396–397, 400
Miller Effect	Multimeters
Milliammeters	
3.6:11:	Multipliers, Frequency
Milliampere	Multipliers, Voltage
Millihenry 26	Multipliers, Voltmeter
Millivolt	Multirange Meters
7.6:11:	
Milliwatt	Muting, Receiver
Minority Carriers	Mutual Conductance
Mixers	Mutual Inductance 29
Mirrore Transistor	Without Inductance
Mixers, Transistor	
Mobile:	
Antennas	N
36 141 36 111	••
Power Supply	N-Type Material
Receivers:	N.F.M. Reception
Mobile Converter for 3.5-28 Mc 468	Narrow-Band Frequency Modulation329, 330
Control Converses for 3.5-26 Mc 406	Narrow-Dand Frequency Modulation329, 330
Crystal-Controlled Converters for 50	National Electrical Safety Code 550-551
and 144 Mc 473	National Traffic System 579
"Hybrid" Crystal-Controlled Conver-	
ter	Negative Feedback
Transmitters:	Negative-Lead Filtering
6- and 2-Meter Mobile Transmitters. 480	Negative-Resistance Oscillators 77
A CEA Makila There will 470	
A 65-watt Mobile Transmitter 476	Network Operation
10-Watt Modulator	Neutralization
25-Watt Transistor Modulator 484	Neutralizing Capacitor 160
Signal Field-Strength Meter 492	Neutral Wire 238
Modes of Propagation	Nodes343, 362
Modulation, Heterodyning and Beats 58	Noise Figures 87
Modulation:	Noise Generators 527
Amplitude Modulation 58, 283	Noise-Limiter Circuits
Capability	Noise, Receiver86–87, 102
	NT-1 Till1 NT-1-1- ACE ACE
	Noise Elimination, Mobile
Characteristic	Noise Reduction
Characteristic Chart286, 289, 293	Noise Silencer, I.F
Checking A.M. Phone Operation 280, 295	
Chala Canalal Madalat	
Choke-Coupled Modulation 288	Nomenclature, Frequency-Spectrum17-18
Clamp-tube	Nonconductors
Controlled-Carrier Systems	Nonlinearity
Driving Power 050 000	
Driving Power	Nonradiating Loads
Envelope	Nonresonant Lines
Frequency Modulation	Nonsynchronous Vibrators
Grid Modulation 289	Nucleus
	11 ucicus 19
Impedance	
Index 330	
Linearity	0
	V
Methods	
Monitoring	Off-Center Fed Antenna
Narrow-Band Frequency329, 330	Official Bulletin Station 582
Percentage of	Official Experimental Station
Phase Modulation	Official Observer
Plate Modulation	Official Phone Station 582
	Official Relay Station 582
Power	Ohm
Screen-Grid Amplifiers	Ohm's Law
Screen-Grid Modulation 290	Ohm's Law for A.C
Suppressor-Grid Modulation 292	Ohmmeters 515
Test Equipment280, 295, 526, 542	Old Timers Club 585
Velocity Modulation	One-Element Rotary for 21 Mc
Waya Forms 900 904 905 900 900	
Wave Forms282, 284, 285, 296-299	Open-Circuited Line
Modulator Tubes	Open-Wire Line 346
	- · · · · · · · · · · · · · · · · · · ·

PAGE	PAGE
Operating an Amateur Radio Station . 578, 579, 590	Pentode Amplifiers69–70
	Pentode Crystal Oscillators
Operating Angle, Amplifier	
Operating a Station	Pentodes
Operating Bias	Percentage of Modulation
Operating Conditions, R.F. Amplifier-Tube 153	Per Cent Ripple
Operating Courtesy	Permeability
Operating Point	Phase32–33
Operator License, Amateur	Phase Inversion
Oscillation	Phase Modulation (see also "Frequency
	and Phase Modulation")
Oscillations, Parasitic	
Oscillator Keying	Phase Modulation Reception
Oscillators73–75, 85	Phase Relations, Amplifiers
Audio 526	Phase-Splitter Circuit
Beat-Frequency	Phased Antennas
Crystal144, 145–146, 424	Phasing-Type S.S.B. Exciters304, 312
Grid-Dip	Phone Activities Manager 581
Overtone	Phone Reception
Transistor	Phonetic Alphabet 575
V.F.O	Pi Network
Oscilloscope Patterns: 282, 284, 285, 296–299,	Pi Network Design
317, 323–326	Pi-Section Coupling
317, 323–326 Oscilloscopes	Pi-Section Filters49–50
Output Capacitor, Filter	Pi-Section Tank Circuit
Output Limiting	Pierce Oscillator
Output Power. 65	Piezoelectric Crystals
Output Voltage, Power Supply225, 226	Piezoelectric Effect
Overexcitation, Class B Amplifier	
Overloading, TV Receiver 568	Pilot-Lamp Data
Overmodulation	Plane-Reflector Antennas, V.H.F 464
Overmodulation Indicators 301	Plate-Cathode Capacitance
Overtone Oscillators	Plate-Current Shift
Oxide-Coated Cathode	Plate-Grid Capacitance
	Plate
	Blocking Capacitor
_	Current
P	
•	Detectors
	Detectors 89 Dissipation 154
P (Power)	Detectors 89 Dissipation 154 Efficiency 67
P (Power)	Detectors 89 Dissipation 154 Efficiency 67 Modulation 287, 299
P (Power) 22 P.E.P. 321 P-Type Material 79	Detectors 89 Dissipation 154 Efficiency 67 Modulation 287, 299 Resistance 62
P (Power) 22 P.E.P. 321 P-Type Material 79 P.M. (see "Phase Modulation") 329, 330	Detectors 89 Dissipation 154 Efficiency 67 Modulation 287, 299 Resistance 62 Resistor 64
P (Power) 22 P.E.P. 321 P-Type Material 79	Detectors 89 Dissipation 154 Efficiency 67 Modulation 287, 299 Resistance 62 Resistor 64 Supply, Audio 263, 286
P (Power) 22 P.E.P. 321 P-Type Material 79 P.M. (see "Phase Modulation") 329, 330	Detectors 89 Dissipation 154 Efficiency 67 Modulation 287, 299 Resistance 62 Resistor 64 Supply, Audio 263, 286
P (Power) 22 P.E.P. 321 P-Type Material 79 P.M. (see "Phase Modulation") 329, 330 Padding Capacitor 92 Page Printer 336	Detectors 89 Dissipation 154 Efficiency 67 Modulation 287, 299 Resistance 62 Resistor 64 Supply, Audio 263, 286 Plate Tank Capacitance 150
P (Power) 22 P.E.P. 321 P-Type Material 79 P.M. (see "Phase Modulation") 329, 330 Padding Capacitor 92 Page Printer 336 Parabolic Reflectors 464	Detectors 89 Dissipation 154 Efficiency 67 Modulation 287, 299 Resistance 62 Resistor 64 Supply, Audio 263, 286 Plate Tank Capacitance 150 Plate Tank Q 149-150
P (Power) 22 P.E.P. 321 P-Type Material 79 P.M. (see "Phase Modulation") 329, 330 Padding Capacitor 92 Page Printer 336 Parabolic Reflectors 464 Parallel Amplifiers 65-66, 162	Detectors 89 Dissipation 154 Efficiency 67 Modulation 287, 299 Resistance 62 Resistor 64 Supply, Audio 263, 286 Plate Tank Capacitance 150 Plate Tank Q 149-150 Plate Tank Voltage 154
P (Power) 22 P.E.P. 321 P-Type Material 79 P.M. (see "Phase Modulation") 329, 330 Padding Capacitor 92 Page Printer 336 Parabolic Reflectors 464 Parallel Amplifiers 65-66, 162 Parallel Antenna Tuning 353	Detectors 89 Dissipation 154 Efficiency 67 Modulation 287, 299 Resistance 62 Resistor 64 Supply, Audio 263, 286 Plate Tank Capacitance 150 Plate Tank Q 149-150 Plate Tank Voltage 149-150 Plate Transformer 226
P (Power) 22 P.E.P. 321 P-Type Material 79 P.M. (see "Phase Modulation") 329, 330 Padding Capacitor 92 Page Printer 336 Parabolic Reflectors 464 Parallel Amplifiers 65-66, 162 Parallel Antenna Tuning 353 Parallel Capacitances 25	Detectors 89 Dissipation 154 Efficiency 67 Modulation 287, 299 Resistance 62 Resistor 64 Supply, Audio 263, 286 Plate Tank Capacitance 150 Plate Tank Q 149-150 Plate Tank Voltage 154 Plate Transformer 226 Plate Tuning, Power-Amplifier 167
P (Power) 22 P.E.P. 321 P-Type Material 79 P.M. (see "Phase Modulation") 329, 330 Padding Capacitor 92 Page Printer 336 Parabolic Reflectors 464 Parallel Amplifiers 65-66, 162 Parallel Antenna Tuning 353 Parallel Capacitances 25 Parallel Circuits 20-22, 25, 29, 34, 36	Detectors 89 Dissipation 154 Efficiency 67 Modulation 287, 299 Resistance 62 Resistor 64 Supply, Audio 263, 286 Plate Tank Capacitance 150 Plate Tank Q 149-150 Plate Tank Voltage 154 Plate Transformer 226 Plate Tuning, Power-Amplifier 167
P (Power) 22 P.E.P. 321 P-Type Material 79 P.M. (see "Phase Modulation") 329, 330 Padding Capacitor 92 Page Printer 336 Parabolic Reflectors 464 Parallel Amplifiers 65-66, 162 Parallel Antenna Tuning 353 Parallel Capacitances 25 Parallel Circuits 20-22, 25, 29, 34, 36 Parallel-Conductor Line 346	Detectors
P (Power) 22 P.E.P. 321 P-Type Material 79 P.M. (see "Phase Modulation") 329, 330 Padding Capacitor 92 Page Printer 336 Parabolic Reflectors 464 Parallel Amplifiers 65-66, 162 Parallel Antenna Tuning 353 Parallel Capacitances 25 Parallel Circuits 20-22, 25, 29, 34, 36 Parallel-Conductor Line 346 Parallel-Conductor Line Measurements 540	Detectors 89 Dissipation 154 Efficiency 67 Modulation 287, 299 Resistance 62 Resistor 64 Supply, Audio 263, 286 Plate Tank Capacitance 150 Plate Tank Q 149-150 Plate Tank Voltage 154 Plate Transformer 226 Plate Tuning, Power-Amplifier 167 Plates, Deflection 543 "Plumber's Delight" Antenna 389 Point-Contact Diode 79-80
P (Power) 22 P.E.P. 321 P-Type Material 79 P.M. (see "Phase Modulation") 329, 330 Padding Capacitor 92 Page Printer 336 Parabolic Reflectors 464 Parallel Amplifiers 65-66, 162 Parallel Antenna Tuning 353 Parallel Capacitances 25 Parallel Circuits 20-22, 25, 29, 34, 36 Parallel-Conductor Line 346 Parallel-Conductor Line Measurements 540 Parallel Feed 53	Detectors
P (Power) 22 P.E.P. 321 P-Type Material 79 P.M. (see "Phase Modulation") 329, 330 Padding Capacitor 92 Page Printer 336 Parabolic Reflectors 464 Parallel Amplifiers 65-66, 162 Parallel Antenna Tuning 353 Parallel Capacitances 25 Parallel Circuits 20-22, 25, 29, 34, 36 Parallel-Conductor Line 346 Parallel-Conductor Line Measurements 540 Parallel Feed 53 Parallel Impedance 36, 44	Detectors 89 Dissipation 154 Efficiency 67 Modulation 287, 299 Resistance 62 Resistor 64 Supply, Audio 263, 286 Plate Tank Capacitance 150 Plate Tank Voltage 154 Plate Tank Voltage 154 Plate Transformer 226 Plate Tuning, Power-Amplifier 167 Plates, Deflection 543 "Plumber's Delight" Antenna 389 Point-Contact Diode 79-80 Point-Contact Transistor 81 Polarization 360, 362, 453, 490
P (Power) 22 P.E.P. 321 P-Type Material 79 P.M. (see "Phase Modulation") 329, 330 Padding Capacitor 92 Page Printer 336 Parabolic Reflectors 464 Parallel Amplifiers 65-66, 162 Parallel Amtenna Tuning 353 Parallel Capacitances 25 Parallel Circuits 20-22, 25, 29, 34, 36 Parallel-Conductor Line 346 Parallel Feed 53 Parallel Impedance 36, 44 Parallel Inductances 29	Detectors
P (Power) 22 P.E.P. 321 P-Type Material 79 P.M. (see "Phase Modulation") 329, 330 Padding Capacitor 92 Page Printer 336 Parabolic Reflectors 464 Parallel Amplifiers 65-66, 162 Parallel Amtenna Tuning 353 Parallel Capacitances 25 Parallel Circuits 20-22, 25, 29, 34, 36 Parallel-Conductor Line 346 Parallel Feed 53 Parallel Impedance 36, 44 Parallel Inductances 29	Detectors
P (Power) 22 P.E.P. 321 P-Type Material 79 P.M. (see "Phase Modulation") 329, 330 Padding Capacitor 92 Page Printer 336 Parabolic Reflectors 464 Parallel Amplifiers 65-66, 162 Parallel Antenna Tuning 353 Parallel Capacitances 25 Parallel Circuits 20-22, 25, 29, 34, 36 Parallel-Conductor Line 346 Parallel-Conductor Line Measurements 540 Parallel Feed 53 Parallel Impedance 36, 44 Parallel Inductances 29 Parallel Reactances 34-35	Detectors
P (Power) 22 P.E.P. 321 P-Type Material 79 P.M. (see "Phase Modulation") 329, 330 Padding Capacitor 92 Page Printer 336 Parabolic Reflectors 464 Parallel Amplifiers 65-66, 162 Parallel Antenna Tuning 353 Parallel Capacitances 25 Parallel Circuits 20-22, 25, 29, 34, 36 Parallel-Conductor Line 346 Parallel-Conductor Line Measurements 540 Parallel Feed 53 Parallel Impedance 36, 44 Parallel Inductances 29 Parallel Reactances 34-35 Parallel Resistances 20-21	Detectors
P (Power) 22 P.E.P. 321 P-Type Material 79 P.M. (see "Phase Modulation") 329, 330 Padding Capacitor 92 Page Printer 336 Parabolic Reflectors 464 Parallel Amplifiers 65-66, 162 Parallel Antenna Tuning 353 Parallel Capacitances 25 Parallel Circuits 20-22, 25, 29, 34, 36 Parallel-Conductor Line 346 Parallel-Conductor Line Measurements 540 Parallel Feed 53 Parallel Impedance 36, 44 Parallel Reactances 29 Parallel Resistances 34-35 Parallel Resistances 20-21 Parallel Resonanace 43-46	Detectors
P (Power) 22 P.E.P. 321 P-Type Material 79 P.M. (see "Phase Modulation") 329, 330 Padding Capacitor 92 Page Printer 336 Parabolic Reflectors 464 Parallel Amplifiers 65-66, 162 Parallel Capacitances 25 Parallel Circuits 20-22, 25, 29, 34, 36 Parallel-Conductor Line 346 Parallel-Conductor Line Measurements 540 Parallel Feed 53 Parallel Impedance 36, 44 Parallel Reactances 34-35 Parallel Resistances 20-21 Parallel Resonanace 43-46 Parasitic Elements, Antenna Arrays with	Detectors
P (Power) 22 P.E.P. 321 P-Type Material 79 P.M. (see "Phase Modulation") 329, 330 Padding Capacitor 92 Page Printer 336 Parabolic Reflectors 464 Parallel Amplifiers 65-66, 162 Parallel Capacitances 25 Parallel Circuits 20-22, 25, 29, 34, 36 Parallel-Conductor Line 346 Parallel-Conductor Line Measurements 540 Parallel Feed 53 Parallel Impedance 36, 44 Parallel Reactances 29 Parallel Resistances 20-21 Parallel Resonanace 43-46 Parasitic Elements, Antenna Arrays with 376, 456	Detectors
P (Power) 22 P.E.P. 321 P-Type Material 79 P.M. (see "Phase Modulation") 329, 330 Padding Capacitor 92 Page Printer 336 Parabolic Reflectors 464 Parallel Amplifiers 65-66, 162 Parallel Antenna Tuning 353 Parallel Capacitances 25 Parallel Circuits 20-22, 25, 29, 34, 36 Parallel-Conductor Line 346 Parallel-Conductor Line Measurements 540 Parallel Impedance 36, 44 Parallel Impedance 29 Parallel Reactances 34-35 Parallel Resistances 20-21 Parallel Resonanace 43-46 Parasitic Elements, Antenna Arrays with 376, 456 Parasitic Excitation 376	Detectors
P (Power) 22 P.E.P. 321 P-Type Material 79 P.M. (see "Phase Modulation") 329, 330 Padding Capacitor 92 Page Printer 336 Parabolic Reflectors 464 Parallel Amplifiers 65-66, 162 Parallel Antenna Tuning 353 Parallel Capacitances 25 Parallel Circuits 20-22, 25, 29, 34, 36 Parallel-Conductor Line 346 Parallel-Feed 53 Parallel Feed 53 Parallel Impedance 36, 44 Parallel Reactances 29 Parallel Resistances 20-21 Parallel Resonanace 43-46 Parasitic Elements, Antenna Arrays with 376, 456 Parasitic Excitation 376, 456 Parasitic Oscillations 161-162	Detectors
P (Power) 22 P.E.P. 321 P-Type Material 79 P.M. (see "Phase Modulation") 329, 330 Padding Capacitor 92 Page Printer 336 Parabolic Reflectors 464 Parallel Amplifiers 65-66, 162 Parallel Antenna Tuning 353 Parallel Capacitances 25 Parallel Circuits 20-22, 25, 29, 34, 36 Parallel-Conductor Line 346 Parallel-Conductor Line Measurements 540 Parallel Feed 53 Parallel Impedance 36, 44 Parallel Reactances 34-35 Parallel Resistances 20-21 Parallel Resonanace 43-46 Parasitic Elements, Antenna Arrays with 376, 456 Parasitic Excitation 376, 456 Parasitic Excitations 161-162 Patterns, Oscilloscope 282, 284, 285, 296-299,	Detectors 89 Dissipation 154 Efficiency 67 Modulation 287, 299 Resistance 62 Resistor 64 Supply, Audio 263, 286 Plate Tank Capacitance 150 Plate Tank Voltage 149-150 Plate Tank Voltage 125 Plate Transformer 226 Plate Tuning, Power-Amplifier 167 Plates, Deflection 543 "Plumber's Delight" Antenna 389 Point-Contact Diode 79-80 Point-Contact Transistor 81 Polarization 360, 362, 453, 490 Positive Feedback 68 Potential Difference 15, 16 Potential, Ground 54 Power, Antistatic 466 Power 22-23 Power Amplification Ratio 65-67 Power Amplification sand Control 547-549
P (Power) 22 P.E.P. 321 P-Type Material 79 P.M. (see "Phase Modulation") 329, 330 Padding Capacitor 92 Page Printer 336 Parabolic Reflectors 464 Parallel Amplifiers 65-66, 162 Parallel Capacitances 25 Parallel Circuits 20-22, 25, 29, 34, 36 Parallel Circuits 20-22, 25, 29, 34, 36 Parallel-Conductor Line 346 Parallel Feed 53 Parallel Feed 53 Parallel Impedance 36, 44 Parallel Resistances 29 Parallel Resistances 20-21 Parallel Resonanace 43-45 Parasitic Elements, Antenna Arrays with 376, 456 Parasitic Excitation 376 Parasitic Oscillations 161-162 Patterns, Oscilloscope 282, 284, 285, 296-299, 317, 323-326	Detectors
P (Power) 22 P.E.P. 321 P-Type Material 79 P.M. (see "Phase Modulation") 329, 330 Padding Capacitor 92 Page Printer 336 Parabolic Reflectors 464 Parallel Amplifiers 65-66, 162 Parallel Antenna Tuning 353 Parallel Capacitances 25 Parallel Circuits 20-22, 25, 29, 34, 36 Parallel-Conductor Line 346 Parallel-Conductor Line Measurements 540 Parallel Feed 53 Parallel Impedance 36, 44 Parallel Reactances 34-35 Parallel Resistances 20-21 Parallel Resonanace 43-46 Parasitic Elements, Antenna Arrays with 376, 456 Parasitic Excitation 376, 456 Parasitic Excitations 161-162 Patterns, Oscilloscope 282, 284, 285, 296-299,	Detectors 89 Dissipation 154 Efficiency 67 Modulation 287, 299 Resistance 62 Resistor 64 Supply, Audio 263, 286 Plate Tank Capacitance 150 Plate Tank Voltage 149-150 Plate Tank Voltage 125 Plate Transformer 226 Plate Tuning, Power-Amplifier 167 Plates, Deflection 543 "Plumber's Delight" Antenna 389 Point-Contact Diode 79-80 Point-Contact Transistor 81 Polarization 360, 362, 453, 490 Positive Feedback 68 Potential Difference 15, 16 Potential, Ground 54 Power, Antistatic 466 Power 22-23 Power Amplification Ratio 65-67 Power Amplification sand Control 547-549
P (Power) 22 P.E.P. 321 P-Type Material 79 P.M. (see "Phase Modulation") 329, 330 Padding Capacitor 92 Page Printer 336 Parabolic Reflectors 464 Parallel Amplifiers 65-66, 162 Parallel Capacitances 25 Parallel Circuits 20-22, 25, 29, 34, 36 Parallel Circuits 20-22, 25, 29, 34, 36 Parallel-Conductor Line 346 Parallel Feed 53 Parallel Feed 53 Parallel Impedance 36, 44 Parallel Resistances 29 Parallel Resistances 20-21 Parallel Resonanace 43-45 Parasitic Elements, Antenna Arrays with 376, 456 Parasitic Excitation 376 Parasitic Oscillations 161-162 Patterns, Oscilloscope 282, 284, 285, 296-299, 317, 323-326	Detectors 89 Dissipation 154 Efficiency 67 Modulation 287, 299 Resistance 62 Resistor 64 Supply, Audio 263, 286 Plate Tank Capacitance 150 Plate Tank Voltage 149-150 Plate Tank Voltage 154 Plate Transformer 226 Plate Tuning, Power-Amplifier 167 Plates, Deflection 543 "Plumber's Delight" Antenna 389 Point-Contact Diode 79-80 Point-Contact Transistor 81 Polarization 360, 362, 453, 490 Positive Feedback 68 Potential Difference 15, 16 Potential, Ground 54 Power 22-23 Power Amplification 65-67 Power Amplification Ratio 65 Power Amplificency 65 Power Connections and Control 547-549 Power Efficiency 22, 23 Power Factor 37
P (Power) 22 P.E.P. 321 P-Type Material 79 P.M. (see "Phase Modulation") 329, 330 Padding Capacitor 92 Page Printer 336 Parabolic Reflectors 464 Parallel Amplifiers 65-66, 162 Parallel Antenna Tuning 353 Parallel Capacitances 25 Parallel Circuits 20-22, 25, 29, 34, 36 Parallel-Conductor Line 346 Parallel Feed 53 Parallel Impedance 36, 44 Parallel Inductances 29 Parallel Resistances 20-21 Parallel Resonanace 43-45 Parasitic Elements, Antenna Arrays with 376, 456 Parasitic Excitation 376 Parasitic Oscillations 161-162 Patterns, Oscilloscope 282, 284, 285, 296-299, 317, 323-326 24 Patterns, Radiation 364, 367 Patterns, TVI 556-557	Detectors 89 Dissipation 154 Efficiency 67 Modulation 287, 299 Resistance 62 Resistor 64 Supply, Audio 263, 286 Plate Tank Capacitance 150 Plate Tank Voltage 149-150 Plate Tank Voltage 154 Plate Transformer 226 Plate Tuning, Power-Amplifier 167 Plates, Deflection 543 "Plumber's Delight" Antenna 389 Point-Contact Diode 79-80 Point-Contact Transistor 81 Polarization 360, 362, 453, 490 Positive Feedback 68 Potential Difference 15, 16 Potential, Ground 54 Power, Antistatic 466 Power 22-23 Power Amplification 65 Power Amplification Ratio 65 Power Amplifice 547-549 Power Connections and Control 547-549 Power Efficiency 22, 23<
P (Power) 22 P.E.P. 321 P-Type Material 79 P.M. (see "Phase Modulation") 329, 330 Padding Capacitor 92 Page Printer 336 Parabolic Reflectors 464 Parallel Amplifiers 65-66, 162 Parallel Antenna Tuning 353 Parallel Capacitances 25 Parallel Circuits 20-22, 25, 29, 34, 36 Parallel-Conductor Line 346 Parallel-Feed 53 Parallel Feed 53 Parallel Impedance 36, 44 Parallel Reactances 29 Parallel Resonanace 43-45 Parallel Resonanace 43-46 Parasitic Elements, Antenna Arrays with 376, 456 Parasitic Excitation 376, 456 Parasitic Excitations 161-162 Patterns, Oscilloscope 282, 284, 285, 296-299, 317, 323-326 Patterns, Radiation 364, 367 Patterns, TVI 556-557 Peak-Current Value 17	Detectors 89 Dissipation 154 Efficiency 67 Modulation 287, 299 Resistance 62 Resistor 64 Supply, Audio 263, 286 Plate Tank Capacitance 150 Plate Tank Voltage 149-150 Plate Tank Voltage 154 Plate Transformer 226 Plate Tuning, Power-Amplifier 167 Plates, Deflection 543 "Plumber's Delight" Antenna 389 Point-Contact Diode 79-80 Point-Contact Transistor 81 Polarization 360, 362, 453, 490 Positive Feedback 68 Potential Difference 15, 16 Power, Antistatic 466 Power 22-23 Power Amplification 65-67 Power Amplification Ratio 65 Power Amplification 547-549 Power Efficiency 22, 23 Power Gain, Antenna 360, 367 Power, Incident 342
P (Power) 22 P.E.P. 321 P-Type Material 79 P.M. (see "Phase Modulation") 329, 330 Padding Capacitor 92 Page Printer 336 Parabolic Reflectors 464 Parallel Amplifiers 65-66, 162 Parallel Amtenna Tuning 353 Parallel Circuits 20-22, 25, 29, 34, 36 Parallel-Conductor Line 346 Parallel-Conductor Line Measurements 540 Parallel Feed 53 Parallel Impedance 36, 44 Parallel Restances 29 Parallel Restances 20-21 Parallel Resonanace 43-45 Parasitic Excitation 376, 456 Parasitic Excitation 376, 456 Parasitic Excitation 376, 456 Parterns, Oscilloscope 282, 284, 285, 296-299, 317, 323-326 284 Patterns, Radiation 364, 367 Patterns, TVI 556-557 Peak Envelope Power 321	Detectors 89 Dissipation 154 Efficiency 67 Modulation 287, 299 Resistance 62 Resistor 64 Supply, Audio 263, 286 Plate Tank Capacitance 150 Plate Tank Voltage 149-150 Plate Tank Voltage 154 Plate Tuning, Power-Amplifier 167 Plates, Deflection 543 "Plumber's Delight" Antenna 389 Point-Contact Diode 79-80 Point-Contact Transistor 81 Polarization 360, 362, 453, 490 Positive Feedback 68 Potential Difference 15, 16 Powertial, Ground 54 Power Amplification 65-67 Power Amplification Ratio 65 65 65-67 Power Amplifier 65 65 65 Power Connections and Control 547-549 Power Efficiency 22, 23 Power Factor 37
P (Power) 22 P.E.P. 321 P-Type Material 79 P.M. (see "Phase Modulation") 329, 330 Padding Capacitor 92 Page Printer 336 Parabolic Reflectors 464 Parallel Amplifiers 65-66, 162 Parallel Capacitances 25 Parallel Circuits 20-22, 25, 29, 34, 36 Parallel Circuits 20-22, 25, 29, 34, 36 Parallel Conductor Line 346 Parallel Feed 53 Parallel Impedance 36, 44 Parallel Restances 29 Parallel Restances 34-35 Parallel Resonanace 43-46 Parasitic Excitation 376, 456 Parasitic Excitation 376, 456 Parterns, Oscilloscope 282, 284, 285, 296-299, 317, 323-326 Patterns, Radiation 364, 367 Patterns, TVI 556-557 Peak-Current Value 17 Peak-Current Value 17 Peak-Voltage Rating (Rectifier) 220	Detectors 89 Dissipation 154 Efficiency 67 Modulation 287, 299 Resistance 62 Resistor 64 Supply, Audio 263, 286 Plate Tank Capacitance 150 Plate Tank Voltage 149-150 Plate Tank Voltage 154 Plate Tuning, Power-Amplifier 167 Plates, Deflection 543 "Plumber's Delight" Antenna 389 Point-Contact Diode 79-80 Point-Contact Transistor 81 Polarization 360, 362, 453, 490 Positive Feedback 68 Potential Difference 15, 16 Power, Antistatic 466 Power 22-23 Power Amplification 65-67 Power Amplifier 65 Fower Connections and Control 547-549 Power Efficiency 22, 23 Power Factor 37 Power, Incident 342 Power, Incident 342
P (Power) 22 P.E.P. 321 P-Type Material 79 P.M. (see "Phase Modulation") 329, 330 Padding Capacitor 92 Page Printer 336 Parabolic Reflectors 464 Parallel Amplifiers 65-66, 162 Parallel Antenna Tuning 353 Parallel Capacitances 25 Parallel Croutits 20-22, 25, 29, 34, 36 Parallel-Conductor Line 346 Parallel Feed 53 Parallel Impedance 36, 44 Parallel Resistances 29 Parallel Resistances 34-35 Parallel Resistances 20-21 Parallel Resonanace 43-46 Parasitic Elements, Antenna Arrays with 376, 456 Parasitic Excitation 376 Parterns, Oscilloscope 282, 284, 285, 296-299, 317, 323-326 29 Patterns, Radiation 364, 367 Patterns, TVI 556-557 Peak-Current Value 17 Peak Envelope Power 321 <td> Detectors</td>	Detectors
P (Power) 22 P.E.P. 321 P-Type Material 79 P.M. (see "Phase Modulation") 329, 330 Padding Capacitor 92 Page Printer 336 Parabolic Reflectors 464 Parallel Amplifiers 65-66, 162 Parallel Capacitances 25 Parallel Circuits 20-22, 25, 29, 34, 36 Parallel Circuits 20-22, 25, 29, 34, 36 Parallel Conductor Line 346 Parallel Feed 53 Parallel Impedance 36, 44 Parallel Restances 29 Parallel Restances 34-35 Parallel Resonanace 43-46 Parasitic Excitation 376, 456 Parasitic Excitation 376, 456 Parterns, Oscilloscope 282, 284, 285, 296-299, 317, 323-326 Patterns, Radiation 364, 367 Patterns, TVI 556-557 Peak-Current Value 17 Peak-Current Value 17 Peak-Voltage Rating (Rectifier) 220	Detectors

PAGE	PAGE
Power Output	Q Signals
Power Ratio, Decibel	QST
Damon Danding	
Power, Reactive	Quad Antenna
Power, Reflected	Quad Antenna Length
Power Sensitivity 65	Quarter-Wave Transformer
Power-Supply Construction Data227-242	•
Power Supplies:	
Detterr Corrier Life 501	•
Battery Service Life	R
Bias Supplies	
Combination A.CStorage Battery Sup-	R (Resistance)
plies	RACES 581
Construction	RC Circuits 30–31
Comptending 1 (and Classical Discussion 1	
Constructional (see Chapters Five and	RC Time Constant30-31
Six)	RCC Certificate
Dry Batteries 501	R.F
Dynamotors	R.F. Probe
Emergency Power Supply	
Ellerent Comple	
Filament Supply	<u>RST</u> System
Heavy-Duty Regulated Power Supply 232	RTTY 336
Input Resistance	Radials 372
Load Resistance	Radiation, Transmission Line 346
Mercury Batteries	
	Radiation Angle
Noise Elimination 501	Radiation Characteristics 363
Output Capacity	Radiation from Transmitter 559
Output Voltage	Radiation Patterns
Plate Supply	Radiation Resistance
Principles	Radio Amateur Civil Emergency Service. 581
Safety Precautions	Radio Frequency17-18
Selenium Rectifiers	Radio Frequency Choke
Transformer Voltage	Radio Frequency Circuits41-52
Transistor	Radiotelegraph Operating Procedure572-574,
Typical	589
Vibrators	Radiotelephone Operating Procedure 574-575
Vibrator Supplies 497	Radiotelephony:
Preamplifier, Receiver	Adjustments and Testing280, 295, 322, 332
Prediction Charts	Audio-Harmonic Suppression 262
Droformed Values Common and	
Preferred Values, Component 508	Checking A.M. Transmitters
Prefixes	Checking F.M. and P.M. Transmitters. 331
Primary Coil	Constructional:
Probe, R.F 530	Class B Modulator
Procedure, C. W	Low-Power Modulator (8 Watts) 269
Procedure, Voice	
Product Detector90, 96	Phasing-Type S.S.B. Exciters304, 312
Propagation, Ionospheric395–396, 397–398,	Speech Amplifier Circuit with Nega-
399-400	tive Feedback
Propagation Modes 56	Speech-Amplifier with Push-Pull
Propagation Phenomena	Triodes
Propagation Predictions	25-watt Modulator using Push-Pull
Propagation, Tropospheric 398, 400-401	6BQ6GTs
Propagation, V.H.F	50-watt AB ₁ Modulator
Protective Bias	6146 Modulator and Speech Amplifier
Public Relations, BCI-TVI	(120 Watts)
Dublic Commissions, DOI-1 VI	
Public Service	Driver Stages
Pulleys, Antenna	Measurements
Pulsating Current	Microphones
Puncture Voltage	Modulation 283
Duch Dull Amplification of CC 162	
Push-Pull Amplifier	Modulators and Drivers
Push-Pull Multiplier	Monitors
Push-Push Multiplier	Output Limiting
·	Overmodulation Indicators 301
	Principles
^	
Q	Reception
·- ·- ·-	Resistance-Coupled Speech-Amplifier
Q43, 47, 55, 149–150 'Q-Fiver''108	Data
'Q-Fiver''	Single-Sideband Transmission 303
Q, Loaded Circuit	Speech Amplifiers
Q, Mobile Antenna	
O Multiplion 107 440	
<i>Q</i> Multiplier	Kadioteletype 336_340
	Radioteletype
'Q''-Section Transformer	Radioteletype F.S.K. Converter

PAGE	n. a.
Radio Waves, Characteristics of 394–395	PAGE
	Reflection, Ground
Radio Waves, Propagation of 398-401	Reflector, Antenna
Rag Chewers Club 585	Refraction of Radio Waves395, 400, 401
Range, V.H.F	Regeneration
Ratio, Deviation	Regenerative Detectors
Ratio, Image	Regenerative I.F
	Degenerative 1.F
Ratio, Impedance	Regulation, Voltage
Ratio, Short-Circuit Current Transfer 83	Regulations, Amateur
Ratio, Turns	Regulations, Conelrad142, 493, 585
Ratio, Power-Amplification	Regulator, High Voltage 239
Ratio, Power Voltage, and Current 41	Regulator, High Voltage 232 Regulator Tubes 230
Datio Standing Warra 244 524	Deviler Velter Con Vot
Ratio, Standing Wave	Regulator, Voltage230, V25
Ratio, Transformer	Relays 548
Ratio, Voltage-Amplification	Reperforator
Ratio, L/C	Resistance
Reactance, Capacitive	Resistance, Back
	Desistance Personal Of
Reactance Charts	Resistance, Forward
Reactance, Inductive	Resistance-Bridge Standing-Wave Indica-
Reactance, Leakage	tor 534
Reactance Modulator	Resistance-Capacitance Time Constant30-31
Reactance, Transmission-Line 341	Resistance-Coupled Amplifier Data (Chart) 258
Denetive Device	Desistance to Control of Desistant (Chart) 200
Reactive Power	Resistance in Series and Parallel
Readability Scale	Resistive Impedance 44
Receiver Alignment113-115	Resistivity of Metals
Receiver, Communications 86	Resistor
Receiver, Coupling to	Resistor Color Code. 509
Receiver Muting 249	Resistor Wattage
Receiver Servicing	Resonance
Receivers, High-Frequency (See also	Resonance Curve
"V.H.F.")	Resonance, Filter 225
Antennas for	Resonance, Sharpness of
Constructional:	December Cincile Country
	Resonant Circuits, Coupled 47
Antenna Coupler for Receiving 130	Resonant Frequency 42
Crystal-Controlled Converter for 20, 15	Resonant-Line Circuits
and 10 Meters	Resonant Transmission Lines 345
DCS-500 Double-Conversion Superhet. 133	Resonator, Cavity
"Fail-Proof" Conelrad Alarm 142	Demands Plat
	Response, Flat48, 68
Regenerative Preselector for 7 to 30 Mc. 131	Response, Frequency48, 68, 255
Selective Converter for 80 and 40 125	Restricted-Space Antennas
"Selectoject"	Restriction of Frequency Response266, 328
Simple-X Super	Return Trace
Transistanized O Multiplian 140	
Transistorized Q Multiplier	Rhombic Antenna
$2 \times 4 + 1$ Superhet	"Ribbon" Microphone
Converters94–96	Ripple Frequency and Voltage 221, 223, 225
Detectors87-91	RMS Voltage 17
High-Frequency Oscillator 96–97	Rochelle Salts Crystals
Improving Performance of	
Timproving refrormance of	Rotary Antennas
Noise Reduction 102	Rotary Antennas, Feedlines for 378
Radio-Frequency Amplifier 109	Rotary-Beam Construction
Regenerative Detectors90-91	Route Manager
Selectivity	
Sensitivity	
Cuporbatanduma	
Superheterodyne93	S
Superregenerative	
Tuning 92-93 112-113 336	S-Meters
Reception, A.M. and C.W	S Scale
Reception, N.F.M., F.M. and P.M. 334	S.S.B. Exciters 305
Reception, Single-Sideband	Safety
Rectification	Safety Code, National Electric 550-551
In Non-Linear Conductors 567	Saturation
Rectified A.C. 60	Saturation Point. 60
Rectifiers	Sawtooth Sweep
Postifica Maraum Vanor 000, 272, 120, 104	
Rectifiers, Mercury-Vapor220, V25	Schematic Symbols
Rectifiers, Ratings	Screen Bypass Capacitor
Rectifiers, Selenium	Screen Circuits, Tuned
Rectifier-Type Voltmeter	Screen Dissipation
Reflected Power	Screen Dropping Resistor
Reflection of Radio Waves342, 399-401	Screen-Grid Keying 245
Reflection from Meteor Trails 401	Screen-Grid Modulation 290

Screen-Grid Neutralization 160	Generators
Screen-Grid Tube Protection	Identification 328
Screen-Grid Tubes	Mixers 326
Screen Voltage	Signal Reception
Screen-Voltage Supply	Transmission
Second Detector	Two-Tone Test
Secondary Coil	Single-Signal Reception
Secondary Emission 69	Skin Effect
Secondary Frequency Standard 520	Skip Distance
Section Communications Manager580, 581	Skip Zone
Section Emergency Coordinator580, 581	Skirt Selectivity
Section Nets	Sky Wave
Selective Fading 397 Selectivity 42, 47–48, 86, 87	Slug-Tuned Inductance
Selectivity, I.F	Smoothing Choke
Selectivity, Receiver	Soldering
Selenium Rectifiers	Space Charge
Self-Bias	Space Wave
Self-Controlled Oscillators 144, 146–149	Spark Plug Suppressors
Self-Inductance	Specific Gravity
Self-Oscillation	Specific Inductive Capacity
Semiconductors79–85	Spectrum, Frequency
Sending	Speech Amplifiers
Sensitivity, Receiver	Speech-Amplifier Construction 260
Series Antenna Tuning	Speech Amplifier Design
Series Capacitances	Speech Clipping and Filtering
Series Circuits	Speech Compression
Series Feed	Speech Equipment
Series-Parallel Resistances 20–22	Speed Key 250 Splatter 285
Series Reactances	Splatter-Suppression Filter 268
Series Resistances. 20–21	Sporadic-E Layer Ionization
Series Resonance41-43	Sporadic-E Skip
Series Voltage-Dropping Resistor 229	Spotting, Frequency 547
Servicing Superhet Receivers	Spreading of Radio Waves
Sharp Cut-Off Tubes 70	Spurious Responses94, 113, 403, 568
Sheet Metal Cutting and Bending 505	Spurious Sidebands
Shielding	Squegging97
Shields	Squelch Circuits
Short-Circuiting 23	Stability, Amplifier
Short Skip	Stability, Frequency
Shot-Effect Noise	Stabilization, Voltage
Shot Noise	Stacked Arrays
Shunt Capacitance 92	Stagger-Tuning
Shunt Matching, Ground-Plane Antenna. 372	Standard Component Values 508
Shunt, Meter	Standards, Frequency
Sideband Cutting 98	Standard Metal Gauges
Sideband Interference	Standing Waves
Sidebands	Standing-Wave Ratio
Sidebands, F.M. and P.M. 330	Standing-Wave Calibration
Side Programatics 303	Starting Voltage (Regulator Tubes) 230
Side Frequencies58, 283Signal Envelope Shape243	Static Collectors
Signal Generators. 523	
Signal-to-Image Ratio 93	Station Assembling
Signal Monitoring. 248	Station Log
Signal-Strength Indicators 104–105	Storage Battery, Automobile
Signal-Strength Scale	Straight Amplifier
Signal Voltage	Stray Receiver Rectification 557
Silencer, Noise 104	Stubs, Antenna-Matching 454
Silicon Diodes	Sunspot Cycle
Sine Wave	Superheterodyne
Single-Ended Circuits	Superheterodyne, Alignment and Servicing
Single Sideband (see also	113-115
"Radiotelephony"):	Superhigh Frequencies (see Ultra High Fre-
Adjustment 322 Amplification 317	quencies and Very High Frequencies) Superimposed A.C. on D.C
Exciters	Superregeneration 405
	TOO

T.	CITE	D	AGE
	GE		
	303	Transformer Efficiency	38
Suppressor Grid	69	Transformer, Gamma379,	383
Suppressor-Grid Modulation 2	292		221
	82		381
Surface Barrier Transistor			
Surface Wave 3	395	Transformer Power Relationships	38
Surge Impedance	347	Transformer, "Q"-Section	381
Surplus Transmitters for Novices, Convert-			261
	214	Transformer, T-Match379,	
			900
	543		238
Swinging Choke 2	224	Transformers:	-40
Switch	19	Air-Tuned	99
	241	Auto	40
Switches, Power548-5		2	240
Switching, Antenna	253	Diode	99
Switching, Meter	67	Filament	227
Symbols for Electrical Quantities	2	Ī.F	99
	$\tilde{2}$		99
Symbols, Schematic	_	Permeability-Tuned	
Symbols, Transistors	33		226
Synchronous Vibrators	196	Triple-Tuned	99
		Variable-Selectivity	99
		Transistors	
			V33
T			
		Transistor Current Transfer Ratio83,	
"T"-Match to Antennas379, 3	383		523
"T"-Section Filters	50	Transistor I.F. Amplifier	100
T.R. Switch		Transistor Mixers	96
Tank Circuit Capacitance150, 152, 1			499
Tank-Circuit $Q.\ldots43$, 1	151		109
Tank Circuits, Multiband	153	Transistor Symbols82,	V33
Tank Constants		Transit Time	-77
	503		341
	336	Transmission Lines as Circuit Elements55	
	555		349
Teletype Code 3	336	Transmission-Line Construction	346
Television Interference, Eliminating 552-5			150
Temperature Effects on Resistance		Transmission-Line Data	
	19		000
	100	Transmission-Line Feed for Half-Wave An-	
Termination, Line 3	341	tennas	364
Tertiary Winding	99	Transmission Line Length	348
	523		349
	573	Transmission Lines, Spacing346,	
		Transmission Lines, Spacing	971
Tetrode	69	Transmission, Multihop396-397,	
Tetrode Neutralization	160	Transmit-Receive Switch	253
Tetrodes, Beam	70	Transmitters: (see also "Very High Fre-	
Thermal-Agitation Noise	86	quencies", "Ultrahigh Frequencies"	
Thermionic Emission	59	and "Mobile")	
	528	Constructional:	
Thoriated-Tungsten Cathodes	60	An Inexpensive 75-Watt Five-Band	
Tickler Coil	91	Transmitter	174
	543	Converting Surplus Transmitters for	
Time Constant			214
	522	Grounded-Grid Amplifier (500 Watts)	198
	166	Kilowatt Amplifier, One Band	194
Tone Control	266	Kilowatt Grounded-Grid Amplifier	202
Tone Scale	586	Kilowatt 4-400A Amplifier	205
Tools		Phased Single-Sideband Exciter	312
	487	Remote-Tuned V.F.O	190
'	543	Self-Contained 500-Watt Transmitter	186
	467	Single Sideband Exciter	307
Tracking92-93, 1	110	Single 813 Amplifier	191
	582	V.F.O. With Differential Keyer	210
	10	3-Band Transmitter for the Novice	
Transatlantics			171
Transconductance, Grid-Plate	62	(30 Watts)	171
Transformation, Impedance	45	75 Watt 6DQ5 Transmitter	
Transformer Color Codes 509-5	510	(Five Bands)	178
Transformer Construction	40	90 Watt All-Purpose Amplifier	182
Transformer Coupling		Metering	167
Transformer Current	38	Principles and Design	
Transformer, Delta-Matching	365	Transverse-Electric and Magnetic Mode	56

"Tron" Antonna	PA	
"Trap" Antennas		36
Traveling-Wave Tube		247
Trimmer Capacitor	VR Tubes	230
Triodes		V1
Triode Amplifiers		68
Triode Clippers		245
Triode-Hexode Converter 96	Vacuum Tube Plate Power Input, Plate	
Tripler, Frequency	Dissipation 1	54
Tri-Tet Oscillator 146	Vacuum Tube Principles59-	.78
Trophosphere Propagation		17
Tropospheric Bending		30
Tropospheric Waves		24
Trouble Shooting (Receivers)	Variable-Frequency Oscillators146-148, 2	70
Trouble Shooting (Speech Equipment)280, 300		48
Tube Elements	Velocity Microphone	256
Tube Kever		77
Tube Noise	Velocity Modulation76-	.77
Tube Operating Conditions, R.F. Amplifier 153	Velocity of Radio Waves 18, 3	94
Tube Ratings, Transmitting		43
Tubes, Modulator		60
Tuned Coupling	Vertical Antennas	
Tuned Screen Circuits 425	Vertical Antennas, Capacitance of 4 Vertical Polarization of Radio Waves 394, 4	86
Tuned-Grid Tuned-Plate Circuit. 74	Very High Frequencies (V.H.F.):	.00
Tuned-Line Tank Circuit		55
Tuned Transmission Lines		39
Tuners, Antenna, Construction of 130, 356-359	Antenna Systems	
Tuning Indicators	Propagation	.01
Tuning R.F. Amplifiers 167 Tuning Receivers 92–93	Receivers	23
Tuning Slug. 93	Construction: Crystal-Controlled Converter for	
Tunnel Diode		17
Turns Ratio	Crystal-Controlled Converter for 50	
TVI425, 552		73
TV Receiver Deficiencies 568	Crystal-Controlled Converters for 50.	
"Twin-Five" Array 461		06
Twin-Lead	Crystal-Controlled Converter for	
1 wo-10ne 1est		$\frac{19}{13}$
		14
97		15
Ü		05
	V.H.F. Receiver Design 4	02
Ultra-High Frequencies:	Transmitters424-4	.52
Cavity Resonators 57 Circuits 55–57		39
Grid-dip Meter	Construction: High-Power Transmitter for 50 and	
Klystrons. 77		26
"Lighthouse" Tubes		29
Magnetrons	144-Mc. Driver-Amplifier 4	34
Pencil Tubes	Simple Transmitters for 50 and 144	
Tank Circuits .55–57 Transmission-Line Tanks .55–56		40
Traveling-Wave Tubes 78	Simple Transmitter for 220 and 420	40
Tubes		146 151
Velocity Modulation	Mobile Transmitters for 50 and 144	.01
Waveguides56-57		80
Unbalance in Transmission Lines 347	40-Watt Transmitter for 220 Mc 4	48
Underwriters' Code	Design	
Unsymmetrical Modulation 284	** ** 0	210
	V.F.O	
Untuned Transmission Lines	V.F.O	72
	V.F.O. 146-148, 2 VVV Signals 5 Vibrator Power Supplies 4	72 96
Untuned Transmission Lines 345 Upward Modulation 284	V.F.O. 146-148, 2 VVV Signals 5 Vibrator Power Supplies 4 Virtual Height 3	72 96 95
Untuned Transmission Lines	V.F.O. 146–148, 2 VVV Signals 5 Vibrator Power Supplies 4 Virtual Height 3 Voice-Controlled Break-In 3	72 96
Untuned Transmission Lines	V.F.O. 146–148, 2 VVV Signals 5 Vibrator Power Supplies 4 Virtual Height 3 Voice-Controlled Break-In 3	72 96 95 27 74
Untuned Transmission Lines 345 Upward Modulation 284	V.F.O. 146–148, 2 VVV Signals 5 Vibrator Power Supplies 4 Virtual Height 3 Voice-Controlled Break-In 3 Voice Equivalents to Code Procedure 5 Voice Operating 574–5	72 96 95 27 74

Volt-Ampere-Reactive 36 Volt-Ampere Rating 227 Voltage Amplification 62-63, 257 Voltage Amplifier 65 Voltage Breakdown 23, 24, 25 Voltage Decay 30, 31 Voltage Distribution, Antenna 366 Voltage Distribution, Antenna 366 Voltage Gain 64, 257 Voltage Loop 343, 362 Voltage-Amplification Ratio 63 Voltage Multiplier Circuits 238 Voltage Node 343, 362 Voltage Regulation 221, 222, 230 Voltage-Regulator Interference 466 Voltage Rise 43 Voltage-Stabilized Power Supplies 230 Voltmeters 512, 517, 528 Volume Compression 266	Wave, Sky 395 Wave Form 17 Wavelength 17-18 Wavelength-Frequency Conversion 18 Wavelengths, Amateur 14 Waves, Complex 17, 37 Waves, Distorted 63 Waves, Electromagnetic 15 Wave Traps 569 Wheel Static 466 Wide-Band Antennas, V.H.F. 463 "Windom" Antenna 369 Wire, Breaking Load for Antenna 510 Wiring Diagrams, Symbols for 2 Wiring, Station 549-550 Wiring, Transmitter 506-50 Word Lists for Accurate Transmission 575 Working DX 575-576 Working Voltage, Capacitor 225 Workshop Practice 502-511 WWV and WWVH Schedules 522
w	x
W1AW	X (Reactance)
WAS Award 583 Watt 22 Watt-Hour 23 Watt-Second 23 Wave Angle 360, 361, 363, 396 Wave-Envelope Pattern 285, 296-299 Wave Front 394	Y "Yagi" Antennas
Wave, Ground 395 Wave Guide Dimensions 56–57 Wave Guides 56 Wavemeters 518 Wave Propagation 394–401 Wave, Sine 17, 32	Z (Impedance) 36 Zener Diodes 80-81, V34 Zener Knee 80 Zero Beat 91 Zero-Bias Tubes 66

Jhe Catalog Section



In the following pages is a catalog file of products of certain principal manufacturers and distributors who serve the radio field: industrial, commercial, amateur. All firms whose advertising has been accepted for this section have met The American Radio Relay League's rigid standards for established integrity; their products and engineering methods have received the League's approval.

 \star

*

 \star

★ 39th EDITION 1962 ★

INDEX OF ADVERTISERS

CATALOG SECTION

The Radio Amateur's Handbook

Pa	ge	Pag	е
Alco Electronic Products, Inc	84	Illumitronic Engineering	8
	71	Institute of Radio Engineers	1
American Electronics Co	93	Instructograph Co	0
American Radio Relay League26, 41-44, 6	64	International Crystal Mfg. Co., Inc48, 4	9
Amperex Electronics Corp62, (63	International Rectifier Corp	
	03		_
	79	Johnson Co., E. F	A
	64	Johnson Co., E. 1,1,1,1,1,1,1,1,1,1,1,1,1,22-2	7
•		Informatio Positio	۰
Barker & Williamson, Inc28-3	30	Lampkin Laboratories, Inc	
	91	Lampkin Laboratories, Inc	'
Belden Mfg. Co			_
	82	Master Mobile Mounts	
	94	Measurements Div	_
	89	Millen Mfg. Co., Inc., James10-1	
	83	Mosley Electronics, Inc 4	5
	-		
Candler System Co	97	National Radio Co., Inc	5
	76	Newark Electronics Corp 9	5
Collins Radio Co	-		
	75	Ohmite Mfg. Co	8
	90	_	
commence con man con man con man con man con con con con con con con con con co	, ,	Panoramic Radio Products, Inc	6
Dow-Key Co., Inc	84	Penta Laboratories	_
bow-key con, man in in in in in in in in in in in in in	-	Petersen Radio Co	
Editors & Engineers, Ltd	72	2	_
• • • • • • • • • • • • • • • • • • • •	31	Radio Shack Corp 7	2
	98	Raytheon Mfg. Co	_
	67	RCA Electron Tube Div	
Electro-Voice, Inc		Rider Publisher, John F	
			_
	86	Rotron Mfg. Co., Inc	y
E-Z Way Towers	36	Shurite Meters	^
EA Common Davidio Distr	77		_
Ft. Orange Radio Distr	77	Sprague Products Co	_
Consert Floring Co	40	Sylvania Electric Products, Inc 3	4
	68 .~	* . 1	~
Gonset Division36,		Technical Materiel Corp46, 4	
Gotham	97	Telcolab Corp	ı
11 III 6 C TI	^	11 72 177 / 6	,
	-9	United Transformer Corp	
Hammarlund Mfg. Co., Inc		University Loudspeakers, Inc	/
Harrison Radio52, 5		VIII 1 6 1	
	40	Vibroplex Co., Inc	4
Heath Co., The			_
	69	Webster Mfg. Co	_
	93	Wile, Eugene G	
Hy-Gain Antenna Products Co32, 3	33	World Radio Labs	7

The new ideas in communications



hallicrafters

For the AM, CW and SSB operator the best for power,

most experienced amateurs for SSB/AM/CW operation because of advanced features . . . beam-switching modulator with unusually high carrier suppression stability—CTO direct reading in kc., and complete 10-meter coverage.

FEATURES: Beam-deflection, high level sideband modulator for low-noise, high-stability signal, Hallicrafters' exclusive 5.0 Mc. quartz crystal filter with sideband rejection of 50 db. or more; CTO direct reading in kilocycles to within 1 kc.; 144 watts plate input (P.E.P. two-tone). Five band output (80, 40, 20, 15, 10 meters). All modes of transmission—CW, AM, SSB. Unwanted sideband down 50 db. or more. Both sidebands transmitted on AM Precision gear driven CTO. Exclusive Hallicrafters patented sideband selection. Logarithmic meter for accurately tuning and carrier level adjustment. Ideal CW keying and break-in operation, push-to-talk and full voice control system built in. Keying circuit brought out for teletype keyer.

FRONT PANEL CONTROLS, FUNCTIONS AND CONNECTIONS: Operation – power off, standby, Mox., Cal., Vox.—P.T.T. Audio level 0-10 R.F. level 0-10. Final tuning 80, 40, 20, 15, 10 meters. Function—upper sideband, lower sideband, DSB, CW. Meter compression. Calibration level 0-10. Driver tuning 0-5. Band selector—80, 40, 20, 15, 10 meters. High stability, gear driven VFO. Microphone, key and headphone monitor jacks.

TUBES AND FUNCTIONS: (2)-6146 Power output amplifiers. 6CB6 variable frequency oscillator. 12BY7 R.F. driver. 6AH6 2nd mixer. 6AH6 3rd mixer. 6AB4 crystal oscillator. 12AX7 voice control. Audio amp. 12AU7 audio amp, and carrier oscillator. 7360 modulator. 12AT7 sideband selecting oscillator. 6AH6 1st mixer. 6AH6 4.95 Mc. amp. 6AU6 9 Mc. amp. 5R4GY HV rectifier. 5V4G LV rectifier. OA2 voltage regulator.

REAR CHASSIS: Co-ax antenna connector, FSK jack, AC accessory outlet. Line fuse. Control connector, ground stud, AC power line cord. Cabinet 20" wide, 10½" high, and 17" deep. Approximate shipping weight 86 lbs. (Conforms to F.C.D.A. specifications.)

SX-115 RECEIVER. First in its class for AM, CW and SSB reception. Truly a deluxe receiver offering band pass filter front end-equivalent of four tuned circuits preceding first mixer-crystal-controlled, high frequency oscillator-5 step selec-

tivity plus exclusive upper-lower sideband selection—linear CTO, direct reading in kc. A perfect match for Hallicrafters' HT-32B and HT-33B exciters and transmitters.

FREQUENCY COVERAGE: Nine 500 kc segments covering 3.5-4.0 Mc.; 7.0-7.5 Mc.; 14.0-14.5 Mc., 21-21.5 Mc.; 28.0-30.0 Mc.; (4 segments); and WWV.

FEATURES: High order of mechanical and electrical stability; linear tuning; constant tuning rate; separate noise limiters for SSB/CW/AM; amplified dual loop AVC with fast attack-slow release; spurious signal and image rejection better than 60 db. 1 kc calibration marks; transmitter-type VFO with differential TC; 100 kc crystal calibrator; crystal controlled 1st and 3rd conversion oscillators; selectable sidebands; selectivity variable in five steps from 500 to 5000 cycles; product detector for SSB/CW envelope detector for AM; I.F. type noise limiter for SSB/CW automatic threshold series type for AM; band gain equalization; audio inverse feedbacks; "S" meter functions with AVC off.

SENSITIVITY: Less than 1 microvolt on AM-less than ½ microvolt on SSB/CW.

TUNING MECHANISM: Back-lash free gear driven tuning mechanism.

TUBES AND FUNCTIONS: 6DC6 R.F. amplifier – 6BA7 1st mixer – 12AT7 crystal oscillator – 6DC6 1st 1.F. amplifier—6BA7–2nd mixer—6CB6 VFO–6DC6 2nd 1.F. amplifier—6BA6 3rd mixer—12AT7 SSB switching oscillator—6DC6 3rd 1.F. amplifier—6BY6 product detector—6BJ7 2nd AVC, AM detector, ANL—12AX7 BFO 1st audio amplifier—6AQ5 audio output—6AU6 100 kc crystal cal.—6AU6 "S" meter amplifier—6AU6 1st loop AVC amplifier—OA2 voltage regulator-five silicon diodes.

FRONT PANEL CONTROLS: R.F. gain; A.F. gain; tuning; selectivity; function selector (upper-lower SSB; upper-lower AM; on-off switch); cal set lock; receive-standby switch; notch frequency; BFO pitch; AVC/ANL (AVC on-off; SSB/CW ANL; AM/ANL); antenna trimmer; band switch; calibrator on-off; headphone jack.

AUDIO OUTPUT IMPEDANCE: 3.2 and 500 ohms.

POWER REQUIREMENTS: 105/125V, 50/60 cycles AC 85 watts.

PHYSICAL DATA: 16" wide x 101/2" high x 16" deep. Shipping weight 47 lbs.







HT-32E

SX-11

HT-33E

whose experience demands clarity and performance

HT-33B LINEAR AMPLIFIER. Famous for effortless power! Heavy duty components leave plenty of reserve even at the maximum legal limit for efficiency and long life (conforms to F.C.D.A. specifications).

FREQUENCY COVERAGE: Complete coverage of amateur bands; 80, 40, 20, 15, 10 meters.

FEATURES: Rated conservatively at the maximum legal input. Third and fifth order distortion products down in excess of 30 db. Built-in R.F. output meter greatly simplifies tune-up. All important circuits metered. Maximum harmonic suppression obtained through pi-network. Variable output loading. Protection of power supply assured by circuit breaker. HT-33B is a perfect match to Hallicrafters' famous HT-32B in size, appearance and drive requirements.

CIRCUIT DETAILS: This power amplifier utilizes a PL-172 high efficiency pentode operating in class AB1. The tube is grid-driven across a non-inductive resistor, thus assuring the maximum stability under all possible conditions. Band switching is accomplished by one knob which selects the proper inductance value for each band. The output circuit is a pi-network with an adjustable output capacitor. accommodating loads from 40 to 80 ohms. 2 panel meters are provided: one is circuit switched to measure grid current, screen current, plate voltage and R.F. output voltage. A second meter continuously monitors cathode current of the PL-172.

TUBES: (1) PL-172 high power pentode; (2) 3B28 rectifiers; (6) OA2 screen regulators.

FRONT PANEL CONTROLS: Meter selector; Filament switch; High Voltage switch; Bias adjustment; Bandswitch; Plate tuning; Plate loading.

PHYSICAL DATA: Gray and black steel cabinet (matches HT-32B) with brushed chrome knob trim. Cabinet: 20" wide x 101/2" high x 17" deep. Shipping weight approx. 130 lbs.

REAR CHASSIS: Co-ax input; co-ax output; filament and bias fuse; cutoff bias relay terminals; screen fuse; ground terminal.

HA-4"T.O. KEYER". The "Stradivarius" of electronic keyers. All-transistorized, compact design, employs digital techniques. Meets all the requirements of the perfectionist in CW operation. Size: 71/2" long, 25/8" high, 53/4" deep. Weight: 5 lbs.

R-47 SPEAKER. Specifically designed for communications. Compact, lightweight and beautifully styled. Flat response from 300 to 2850 c.p.s. Input impedance: 3.2 ohms. Size 5½" x 5¼" x 3¼". Weight 21/2 lbs.


SX-101A RECEIVER. Far advanced in technical features and performance. Known throughout the world as the "Heavyweight Champion" for ruggedness and dependability. Provides the sensitivity and selectivity you need.

FEATURES: Complete coverage of 80, 40, 20, 15, 10 meter bands plus a 2 and 6 meter conv. band; Dual scale "S"-meter functions with AVC off. Special 10 Mc. position for WWV. Dual conversion. Exclusive Hallicrafters' upper-lower sideband selection. Tee-notch filter. Full gear drive from tuning knob to gang condensers, 40:1 tuning knob ratio. 100 kc. evacuated marker crystal. Five steps of selectivity from 500 cycles to 5000 cycles. Direct coupled series noise limiter for improved noise reduction. Sensitivity-one microvolt or less on all amateur bands, 52 ohm antenna input. Antenna trimmer. Relay rack panel. Double spaced gang condenser.

FRONT PANEL CONTROLS: Main tuning knob. Crank knob for rapid scan, pointer reset, antenna trimmer, tee-notch frequency, tee-notch depth, sensitivity, band selector, volume, selectivity, BFO, response – (upper-lower sideband AM-CW). AVC on-off, AVC fast-slow, ANL Cal. Rec./standby.

TUBES AND FUNCTIONS: 6DC6. R.F. amplifier-6BY6. 1st converter-12BY7A, high frequency oscillator -6BA6, 1650 kc. I.F. amplifier-12AT7, dual crystal controlled 2nd conversion oscillator—6BA6, 2nd converter—6DC6 50.75 kc. I.F. amplifier-6BJ7 AM detector, ANL, AVC - 6BY6 SSB/CW detector-6SC7 1st audio amplifier & BFO-6K6, audio power output-6BA6, "S"-meter amplifier-6AU6, 100 kc. crystal oscillator-OA2, voltage regulator-5Y3, rectifier.

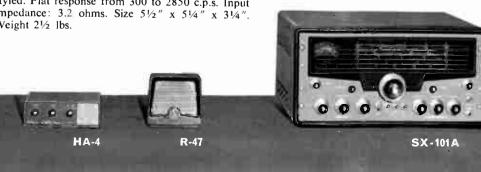PHYSICAL DATA: 20" wide, 101/2" high and 16" deep-Panel size 834" x 19"-weight approximately 74 lbs. (Conforms to F.C.D.A. specifications.)





SSB equipment with the performance characteristics of the expensive rigs...at a price everyone can afford

HT-37 TRANSMITTER. We took the "heart" of the world famous HT-32B and put it in this precision-engineered AM/CW/SSB transmitter—same final amplifier, same rugged VFO construction and same VOX circuitry. The result—you get excellent performance characteristics for smooth, distortion-free speech quality at a very moderate price.

FEATURES: 144 watts plate input (P.E.P. two-tone); five band output (80, 40, 20, 15, 10 meters); all modes of transmission—CW/AM/SSB; unwanted sideband down 40 db. at 1 ke; distortion products down 30 db. or more; carrier suppression down 50 db.; modern styling; instant CW Cal. from any mode; both sidebands transmitted on AM; precision VFO: rugged heavy duty deluxe chassis; 52 ohm pi-network output for harmonic suppression; dual range meter for accurate tuning and carrier level adjustment; ideal CW keying; full voice control system built in.

FRONT PANEL CONTROLS, FUNCTIONS, CONNECTIONS: Operation—(power off, standby, mox, cal, vox): Audio gain; R.F. level; Final tuning; Function—(upper sideband, lower sideband, DSB, CW); carrier balance; Calibration level; Driver tuning; Band selector VFO; Microphone connector; Key jack.

TUBES AND FUNCTIONS: (2)-6146 Power output amplifiers; 6CB6 Variable frequency oscillator; 12BY7 R.F. driver; 6AH6 1st Mixer; 6AH6 2nd Mixer; 6AB4 Crystal oscillator; 12AX7 Voice control; 12AT7 Voice control; 6AL5 Voice control; 12AX7 Audio Amplifier; 12AT7 Audio amp and carrier Oscillator; 12AT7 Audio

Modulator; (2)-12AT7 Balanced Modulators; 5R4GY HV Rectifier; 5V4G LV Rectifier; OA2 Voltage Regulator.

REAR CHASSIS: Co-ax antenna connector; Line fuse; Control connector; AC power line cord.

PHYSICAL DATA: Matching unit for SX-111; cabinet is gray steel with brushed chrome trim and knobs. Size: 9" high x 191/4" wide x 151/2" deep. Shipping wt.; approx., 80 lbs.

essential characteristics of the durable SX-101A—yet in the price range that makes it a wanted unit in any shack. Sensitive is the word for its operation—rugged is the word for its dependability. Beautifully styled and precision built in the true Hallicrafters tradition of excellence in performance.

FREQUENCY COVERAGE: Complete coverage of 80, 40, 20, 15 and 10 meters in five separate bands. Sixth band is tunable to 10 Mc for crystal calibrator calibration with WWV.

FEATURES: AM/CW/SSB reception. Dual conversion, Hallicrafters' exclusive selectable sideband operation. Crystal-controlled 2nd converter. Tee-notch filter. Calibrated "S"-meter. Electrical calibration adjustment. Series noise limiter. Built-in crystal calibrator. Exceptional electrical and mechanical stability. Large slide-rule dial. Envelope detector for AM and product detector for SSB/CW.

SENSITIVITY: One microvolt on all bands. 5 steps of selectivity from 500 to 5000 c.p.s. **TUNING MECHANISM:** New friction-and-gear type with 48:1 tuning ratio. Virtually eliminates backlash.

CONTROLS: Tuning; CAL Reset; Antenna Trimmer; T-notch Frequency; R.F. Gain; A.F. Gain; Band Selector; Function (off-on, standby, upper or lower sideband, calibrate); AVC off-on; BFO off-on; ANL off-on; Selectivity. TUBES: 12 tubes plus voltage regulator and rectifier. 6DC6 R.F. Amplifier; 6BY6 1st converter; 6C4 Oscillator; 6BA6 2nd converter; 12AT7 Dual crystal controlled 2nd conversion oscillator; 6DC6 1650 kc. I.F. amplifier; 6DC6 I.F. amplifier (50 kc.); 6BJ7 AVC-noise limiter AM detector; 12AX7 1st audio and BFO; 6AQ5 Power output; 6BY6 Product detector; 6AU6 Crystal calibrator; 5Y3 Rectifier; OA2 Voltage regulator.

POWER SUPPLY: 105-125 volts, 50-60 cycle AC.

PHYSICAL DATA: Size: 1834" wide x 1014" deep x 834" high. Attractive gray steel cabinet with brushed chrome trim. Shipping weight approximately 40 lbs.

and POWERFUL! Here is the low cost linear amplifier you've been looking for—with the capabilities of delivering the "Big" signal on the air! Ideally engineered with conservatively rated components. Ideal companion for the HT-37 in both styling and price.

FEATURES: Complete coverage 80 through 10 meters. Adjustable pi-network output. All important circuits metered. Built in R.F. output meter to simplify tune-up. Built in driver pad. Standby bias supply for complete cutoff during receive.

circuit Details: This new high power linear amplifier employs two 7094 tetrode-type tubes. These tubes are connected as high Mu grounded grid triodes in Class B. Input circuit designed for 50 to 75 ohm exciters. A completely self-contained power supply uses 866A tubes connected in a full wave rectifier circuit possessing exceptional regulation. Provision also made to control cutoff bias by proper connections to terminal strip on rear of chassis. Overload protection provided by fuse which protects plate, filament, bias and blower circuits.

TUBES: (2) 7094; (2) 866A rectifiers.

FRONT PANEL CONTROLS: Filament switch; high voltage switch; meter switch; band selector; plate tuning; plate loading.

REAR CHASSIS: Co-ax input; co-ax output; AC line cord; plate, filament, bias and blower fuse; terminal strip for bias cutoff relay control and AC control circuits; terminal strip for internal input; grounding bolt and lug.

PHYSICAL DATA: 19¼" wide x 9" high x 15½" deep. Cabinet in gray steel with brushed chrome trim and knobs. Shipping wt.; 97 lbs.

HA-2—HA-6 TRANSVERTERS. A sensible, new approach to VHF operation! Engineered with the usual Hallicrafters precision, these transverters will convert your present 10-meter station to VHF... AM, CW, SSB, RTTY, FM capability. All modes of transmission and reception on your present equipment are useable with these units. A nuvistor front end in the receiver section provides excellent sensitivity and noise figure.

FEATURES: Converts received VHF signals down to 10 meters for reception. Converts 10-meter signal to VHF for transmission. 5894 tube in transmitter final amplifier can be driven up to 120 watts input. Can be driven by exciters with 10 to 100 watt capability. Built-in coaxial antenna relay.

FRONT PANEL CONTROLS AND FUNC-TIONS: Power on-off, range selector; tuning; loading; output indicator; plate current meter. **TUBES:** 12AT7 crystal oscillator; 6AH6 buffer amplifier; 6CW4 R.F. amplifier (REC.); 6AN4 mixer (REC.); 12BY7 mixer (Xmit); 6360 driver (Xmit); 5894 final amplifier.

REAR CHASSIS CONTROLS AND FUNC-TIONS: Receiver co-ax.; antenna co-ax fitting; transmitter co-ax. input hi.; transmitter co-ax. input low; power and control socket; bias adjust, filament and relay fuse; hi-voltage connector.

POWER REQUIRED: 750 volts @ 160 MA; 250 volts @ 70 MA; minus 60 volts @ 10 MA.

PHYSICAL DATA: 8" high x 17" wide x 8%" deep. Gray steel cabinet with silver trim.

MODEL P26—POWER SUPPLY. Hallicrafters power supply for these units supplies all voltages. Only one supply necessary for operation of either the HA-2 or HA-6 when used in stations set up for 6 or 2 meter operation.

R-48 SPEAKER. Modern design eliptical assembly, heavy magnet has fully saturated air gap for exceptional damping, distortion-free response. Switch at rear for selection of music or voice response. Use with SX-100, SX-110, SX-62A or any receiver with 3.2 ohm output. Handsome, gray steel cabinet, 65% high x 1314 wide x 814 deep.



Now!-with Hallikitsbuild an economical high quality amateur band transmitter and receiver



HT-40 TRANSMITTER. Perfectly complements the high performance qualities of the SX-140 receiver. This crystal-controlled 75 watt transmitter has all the Hallicrafters design, quality and engineering features that are equally important to both beginners and old timers.

FEATURES: You get excellent CW performance as well as AM. Full band switching, 80 through 6 meters. Enjoy easy tune-up and crisp, clean styling that has efficient operation as well as appearance in mind. Unit is fully metered, TV1 filtered.

SPECIFICATIONS: Maximum D.C. power input: 75 watts. Power output in excess of 35 watts CW, 30 watts peak AM phone. (Slightly less on 6

meters.) Frequency bands: 80, 40, 20, 15, 10 and 6 meters.

TUBES AND FUNCTIONS: 6DQ5 power output; 6CX8 crystal oscillator and driver; 12AX7 speech amplifier; 6DE7 modulator; silicon high voltage rectifiers.

FRONT PANEL: Function (AC off, tune, standby, AM, CW); Band Selector (80, 40, 20, 15, 10, 6); Drive control; Plate tuning, plate loading, Crystal-VFO; Grid Current; Meter; AC indicator light; R.F. output.

REAR CHASSIS: Microphone gain; antenna coax connector; remote control terminals; AC power cord.

SX-140 RECEIVER. It makes good operating sense to team up this quality-engineered receiver with the HT-40. In combination, these two units will give you an excellent performing station for a very modest investment.

FEATURES: You get complete coverage of all amateur bands 80 through 6 meters, with extremely high sensitivity and sharp selectivity. Unit has R.F. stage; S-meter; antenna trimmer; and crystal calibrator. Tuning ratio is 25 to 1.

CONTROLS: Tuning; Antenna Trimmer; Cal Reset; Function (AC off, standby, AM/CW/SSB); Band Selector; Cal on-off; R.F. Gain; Auto. Noise Limiter on-off; Selectivity/BFO; Audio Gain; phone jack; "S"-meter Adj.

TUBES AND FUNCTIONS: 6AZ8 tuned R.F. amplifier and crystal calibrator; 6U8 oscillator and mixer; 6BA6 1650 kc. I.F. amplifier and BFO; 6T8A 2nd detector, AVC, ANL and 1st audio; 6AW8A audio power amplifier and "S"-meter amplifier; (2) silicon high voltage rectifiers.

Both units available fully wired and factory tested.



HA-5 DELUXE VFO. A heterodyne-type VFO for all amateur bands, 80 through 2 meters. A 30 to 1 tuning ratio provides precision tuning.

FEATURES: Illuminated dial. Built-in spotting switch. Self-powered crystals supplied for 80 through 10 meters. (Crystals for 6 and 2 meters available from Hallicrafters.)

OUTPUT FREQUENCY RANGE: 3.5 Mc. to 4.0 Mc., 7.0 Mc. to 7.5 Mc., 8.0 Mc. to 8.222 Mc., and 8.333 Mc. to 8.833 Mc.

POWER SOURCE: 105V AC to 125V AC, 60 cycles.

TUBE COMPLEMENT: VFO and crystal oscillators, 6U8; mixer, 6BA7; output, 6AQ5; voltage regulator, OA2.

PHYSICAL DATA: 7" wide x 5" high x 8½" deep. Shipping weight: 8 lbs.

Time-proven, value-proven general coverage receivers







SX-100

SX-110

S-120 RECEIVER. World's most popular short wave receiver! Provides dependable per-formance in standard broadcast and three short wave bands. New, three-way antenna system for maximum flexibility. Clean, compact "look" of performance on the outside too!

FEATURES: Coverage of 540-1650 kc. plus short wave from 1650 kc. through 31 Mc.; Electrical bandspread; slide-rule dial with imprinted guide to frequencies of foreign, gov't., aviation, etc.; Three-way antenna system - built-in, high-gain ferrite loop for AM, 45" collapsible whip, plus terminals for long wire or doublet antenna, all bands; Front panel BFO/sensitivity control; built-in 5" speaker; front-panel headphone jack

automatically disables speaker.

FRONT PANEL CONTROLS: Main Tuning;
Bandspread Tuning; Band Switch; Audio Vol. AC

Off; BFO/Sensitivity

TUBES AND FUNCTIONS: 12BE6 converter; 12BA6 1.F. amplifier/BFO; 12AV6 1st audio, AVC and detector; 50C5 power amplifier. Selenium rectifier. Thermistor heater regulator. Two dial lamps. 105-125V AC/DC at 30 watts. U/L listed

PHYSICAL DATA: Gray steel cabinet with bright chrome trim, black dial. Size: 13½" wide by 57%" high by 8¾" deep. Shipping wt.: 11¾ lbs.

SX-100 RECEIVER. Most versatile receiver of all! Has everything you need for allaround listening. Beautifully styled. Compactly

built-time-proven.

FREQUENCY COVERAGE: 540 kc.-34 Mc.-Band 1: 538 kc.-1580 kc.-Band 2: 1720 kc.-4.9 Mc.-Band 3: 4.6 Mc.-13 Mc.-Band 4: 12 Mc.-34 Mc. Bandspread dial is calibrated for the 80, 40, 20, 15 and 10 meter amateur bands. Intermediate frequency: 1650 kc. and 51 kc. TYPE OF SIGNALS: AM/CW/SSB.

FEATURES: Selectable side band operation. "Tee-Notch" Filter. Notch depth control. Antenna trimmer. 100 kc. crystal calibrator. Logging dials. Full precision gear drive. Second conversion oscillator crystal controlled - temperature compensation of high frequency oscillator. Phono jack. Socket for D.C. and remote control.

CONTROLS: Pitch control, reception, stand-by, phone jack, response control (upper and lower side band selector), antenna trimmer, notch depth, calibrator on-off, sensitivity, band selector, volume, tuning, AVC on-off, noise limiter on-off, band-spread, selectivity.

AUDIO OUTPUT IMPEDANCE: 3.2/500 ohms: AUDIO POWER OUTPUT: 1.5 watts with 10% or less distortion. POWER SUPPLY: 105/

125 V., 50/60 cycle AC.

TUBE COMPLEMENT: 6CB6 R.F. amplifier; 6AU6, 1st converter; 6C4, H.F. oscillator; 6BA6, 2nd converter; 12AT7, Dual crystal second oscillators; (2) 6BA6, 50 kc. and 1650 kc. l.F. amplifiers; 6BJ7, AVC-DET-ANL; 6SC7, 1st audio and BFO; 6K6, Power output; 5Y3, Rectifier; OA2, Voltage regulator; 6C4, 1.F. amplifier-(51 kc.);

OAUG, 100 kc, crystal marker.

PHYSICAL DATA: Gray black steel cabinet with brushed chrome knob trim, patterned silver back plate and red pointers. Piano hinge top. Size 183's" wide x 81/2" high x 105's" deep. Shipping weight approximately 42 lbs. (U.L. approved).

SX-110 RECEIVER. An all-purpose receiver with many of the most wanted features originally designed for the higher priced equipment.

FREQUENCY COVERAGE: Broadcast Band 540-1680 kc plus three short wave bands cover 1680 kc-34 Mc.

FEATURES: Slide rule bandspread dial calibrated for 80, 40, 20, 15 and 10 meter amateur bands and 11 meter citizens' band. Separate bandspread tuning condenser, crystal filter, antenna trimmer,

"S" Meter, one R.F., two I.F. stages.
INTERMEDIATE FREQUENCY: 455 kc.
TUNING ASSEMBLY AND DIAL DRIVE MECHANISM: Ganged, 3 section tuning capacitor assembly with electrical bandspread. Circular main tuning dial is calibrated in megacycles and

has 0-100 logging scale.

AUDIO OUTPUT IMPEDANCE: 3.2 and 500

TUBE COMPLEMENT: Seven tubes plus one rectifier: 6SG7, R.F. amplifier-6SA7, converter -6SG7, 1st 1.F. amplifier-6SK7, 2nd 1.F. amplifier-6SC7, BFO and audio amplifier-6K6GT, Audio output-6H6, ANL-AVC-detector-6Y3GT, rectifier.

AUDIO POWER OUTPUT: 2 watts. POWER SUPPLY: 105/125 V., 50/60 cycle AC.

PHYSICAL DATA: Gray steel cabinet with brushed chrome trim. Size 1834" wide x 8" high x 1014" deep. Shipping weight approximately 32 lhs


S-108 RECEIVER. Features the same basic performance characteristics as the SX-110 (above) without the "S" meter, antenna trimmer and crystal filter. Speaker built in



hallicraftere

ommunications are born at . . .

"Designed for Performance"®

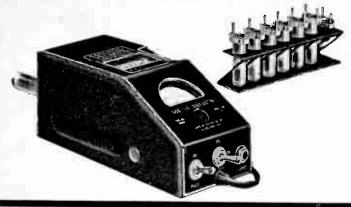

MILLEN NO. 90651 GRID DIP METER

The No. 90651 MILLEN GRID DIP METER is compoct one completely self contained. The AC power supply is a the "transformer" type. The drum diat has seven call broted uniform length scales from 1,7 MC to 300 MC with generous over lops plus on orbitrory scale for use will special application inductors. Internal terminal strip per mits bottery operation for ontenno measurement.

No. 90651, with tube.....

	Add	itio	nol	Ind	luctors	for	Lower	Frequencies
No.	46702	_	925	to	2000	KC		
No.	46703	_	500	to	1050	кC		
No.	46704	_	325	to	600	KC		
No.	46705	_	220	to	350	KC		

















TONE MODULATOR — The No. 90751 Tone Modulator is a small package containing a transistor audio ascillator and its mercury battery, which plugs into the phane jack of a Grid Dip Meter to modulate the signal at approximately 800 cycles for applications requiring a modulated signal. Dimensions: only $2\frac{34}{4} \times 1\frac{36}{16} \times 1\frac{36}{16}$ in.

No. 90751, less bottery

AUDIO CLIPPER ___ The No. 75016 Audio Clipper is a small plug-in symmetrical type clipper with self-contained mercury batteries. It may be used to clip noise for C-W reception os well os for A-M or SSB, or it may be used to clip a sine wove input to form a squore wove output. Dimensions: only 2½ x 1½ x 1½ in.

No. 75016, less botteries

ANTENNA BRIDGE ___ The Millen 90672 Antenna Bridge is an occurate and sensitive bridge for measuring impedances in the range occurrie and sensitive bridge for measuring impedances in the range of 5 to 500 ohms (or 20 to 2000 ohms with bolum) at radio frequencies up to 140 mc. The variable element is an especially designed differen-tial variable capacitor capable of high occuracy and permanency of colibration. Readily driven by No. 90651 Grid Dipper.

No., 90672 ..

The No. 46672 (1 for each amateur band) wound BOLUNS — The No. 400/2 (I for each amateur band) wound bolun is an occurate 2 to 1 turns ratio, high Q outs transformer with the residual reactances tuned out and with very tight coupling between the two holves of the total winding. The points of series and porollel resonance are selected so that each Bolun provides an occurate 4 to 1 impedance ratio over the entire band of frequencies for which it was designed. Suitable for use with the No. 00/272 Autona Buildon. designed. Suitable for use with the No. 90672 Antenno Bridge as medium power tronsmitters.

Na. 46672-80/40/20/15/10

HIGH VOLTAGE POWER SUPPLY -The No. 90281 high voltage power supply has a d.c. author of 700 volts, with maximum current of 235 ma. In addition, a.c. filoment power of 6.3 volts a 4 amperes is also available so that this power supply is an ideal unifor use with transmitters, such as the Millen No. 90801, as well as general laboratory purposes. The power supply uses two No. 816 rectifiers. The panel is standard 834" x 19" rock mounting.

No. 90281, less tubes ...

REGULATED POWER SUPPLY - A compoct, uncosed, regulated power supply, either for table use in the laboratory or for incorporation os on integral port of larger equipment, 250 v.d.c. unregulated at 115 ma. 105 v.d.c. regulated at 35 mo. Minus 105 v.d.c. regulated bias at 4 ma. 6.3 v. a.c. at 4.2 amps. No. 90201, with tubes.

HIGH FREQUENCY RF AMPLIFIER — A physically small unit capable of a power output of 70 to 85 watts on Phone or 87 to 110 wotts on C-W on 20, 15, 10, 6 or 2 meter amoteur bands. Provision is mode for quick band shift by means of the No. 48000 series VHF plug-in cails. The No. 90811 unit uses either on 829-8 or 3E29. No. 90811 with 10 meter bond coils, less tube

PHASE-SHIFT NETWORK —A complete and laboratory oligned pair of phase-shift networks in a single compact $2'' \times 17/h$, $2'' \times 4''$ case with characteristics so as to provide a phase shift between the two networks of $90^{\circ} \pm 1.3^{\circ}$ over a frequency range of 225 cycles to 2750 cycles. Well adopted for use in either single sidebond transmitter or receiver. Possible to obtain a 40 db suppression of the unwanted sidebond. The No. 75012 precision adjusted phase-shift network eliminates necessity of complicated lab equipment for network eliminates necessity of complicated lab equipment for network eliminates necessity of complicated lab equipment for network eliminates necessity of complicated lab equipment for network eliminates. nates necessity of camplicated lab equipment for network adjustment. No. 75012 ...

JAMES MILLEN

The No. 90923 oscilloscope is an extremely compact ($3V_2$ inches high) rock ponel general purpose ascilloscope utilizing the type $3V_2-3$ x $1V_2$ inch rectangular face tube. The No. 90923 is complete with vertical and harizontal amplifiers for bolanced deflection and a very linear sweep generalar.

Miniature input terminals are an both the front panel and the rear for vertical amplifier input, horizontal amplifier input and synchronizing input. The linear sweep generator covers two cycles per second to 30 kcs. per second in seven averlapping ranges. The trace is unusually sharp and bright due to 2040 volts accelerating potential.

The No. 90923 is ideally suited for mony applications, and in particular, for production test, its small panel uses up very little space in a test rack and the mu-metal shield around the cothode ray tube shields it against magnetic fields so that the oscilloscope may be used actuately in lacotions with strong stroy magnetic fields. The cothode ray tube is of the mono-accelerator type in which the electron beam is accelerated or the electron gan so that field distortions are minimized and excellent deflection linearity is achieved as well as a very uniform spat size over the entire area which the beam scans.

MILLEN NO. 90923 RACK MOUNTED OSCILLOSCOPE


















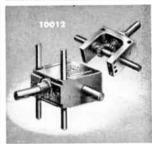

MILLEN ONE INCH MODULE OSCILLOSCOPES — Minioturized, packaged panel mounting cathode ray oscilloscope designed for use in instrumentation in place of the conventional "pointer type" moving coil meters uses the 1" tube. Panel bezel matches in size and type the standard 2" square meters. Magnitude, phose displacement, wave shope, etc. are constantly visible on scope.

No. 90901, 1CP1, less tube No. 90911, 1EP1, less tube .

FLAT FACE OSCILLOSCOPE — 90905-8 5-inch Rack Mounting Basic Oscilloscope features include: balanced deflection, front panel input terminals, rear ponel input terminals, astigmatism control, blanking input terminals, flat face precision tolerance Dumant SADP1 tube.

BASIC OSCILLOSCOPES — The No. 90902, No. 90903 and No. 90905 Rack Panel Oscilloscopes, for two, three and five inch rubes, respectively, are inexpensive basic units comprising power supply, brilliancy and centering controls, safety features, magnetic shielding, switches, etc. As a transmitter monitar, no additional equipment or accessories are required. By the addition of such units as sweeps, pulse generators, amplifiers, serva sweeps, etc., all of which can be expanded to serve any conceivable industrial or laboratory application.

POWER SUPPLY FOR OSCILLOSCOPE ____ 750 volts d.c. at 3 ma. and 6.3 volts a.c. at 600 ma. 117 volts 50-60 cycle input. Designed especially for use with No. 90901 and No. 90911 one inch instrumentation oscilloscopes. $4\frac{1}{2}$ 6 in. high \times $1\frac{1}{2}$ 6 \times 2 \frac{1}{6}8. Octol plug for input and output. Entire assembly including rectifier is encapsulated. No. 90202, Power Supply (complete)

BEZELS FOR CATHODE RAY TUBES — Standard types are af sotin finish black plastic. 5" size has neaprene support cushion and green lucite filter. 3" and 2" sizes have integral cushioning. No. 80075 (5") ... 80073 (3") 80072 (2") 80071 (1")

WORM DRIVE UNIT — Cast aluminum frame may be panel or base mounted. Spring loaded split geors to minimize back lash. Standard ratio 16/1, Alsa in 48/1 on request.

No. 10000 -- (state ratio)

RIGHT ANGLE DRIVE — Extremely compact, with provisions for many methods of mounting. Ideal for operating potentiameters, switches, etc., that must be located, for short leads, in remate parts of chassis. No. 10012

AMATEUR BAND MONITOR OSCILLOSCOPE

A-M or SSB 3.5 to 54 Mc.
Blanks out on Standby
Individual coil for each band

SCOPE — Na. 90932 is a complete oscilloscope for monitoring the modulated rf output of a transmitter. Built-in link-coupled tuned circuits cover all amateur bonds 3.5 to 54 mc. All circuits and accessories are built-in. The monitor will display the r-f envelope and/or the tropezoidal monitoring pattern of single side band transmitters or amplified modulated transmitters. It shows the linearity or non-linearity of Class-8 r-f amplifiers, the parasitic oscillation, neutralization, and r-f output,



2" round tube

ILLEN









TUBE SOCKETS DESIGNED FOR APPLICATION -TUBE SOCKETS DESIGNED FOR APPLICATION — MODERN SOCKETS for MODERN TUBES! Long Flashover path to chassis permits use with transmitting tubes, 866 rectifiers, etc. Long leakage path between contacts. Contacts are type praven by hundreds of millions already in government, commercial and broadcast service, to be extremely dependable. Sockets may be mounted either with or without metal flange. Mounts in standard size chassis hale. All types have barrier between contacts and chassis. All but actal and crystal sockets also have barriers between individual contacts in addition. addition.

Voltage regulator dual contact bayonet socket, 33991 black phenalic insulation and 33992 with low loss mica filled phenalic insulation.

MILLEN TUBE SOCKETS

No.	Description		No.	Description
33102Cry	stal Socket	3/4" x .125"	33005-5	Pin Tube Socket Pin Tube Socket Pin Tube Socket
33302—Cry 33407—Mir	rstal Socket Siature Sock	.487" x .050"et only, ceramic	33008-8	Pin Tube Socket ocket for 991
33307-Mir	niature Sock	et, Shield, ceramic	33207-82	ocket for 991 9 Socket
33309—No 33405—5 P	val Socket, 'in Socket E	Shield, ceromicimoc	33305—A	corn Socket














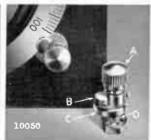



FLEXIBLE COUPLINGS - The No. 39000 series of Millen "De-FLEXIBLE COUPLINGS — The No. 39000 series of Millen "Designed for Application" flexible coupling units include, in addition to impraved versions of the conventional types, also such exclusive original designs as the No. 39001 insulated universal joint and the No. 39006 "slide-action" coupling (in bath steatite and backlete insulation). The No. 39006 "slide-action" coupling permits longitudinal shaft motion, eccentric shoft motion and out-of-line aperation, as well as angular drive without backlosh.

The No. 39005 and 39005-8 (high torque) are similar to the No. 39001, but are a limitated. The steatic insulated No. 20001 has a series of the similar to the No. 39001, but are a limitated.

Inter No. 37003 and 37003-18 (high torque) are similar to the No. 39001, but are not insulated. The steatite insulated No. 39001 has a special anti-backlash pivot and socket grip feature. All of the above illustrated units are for \(V_4 \) shaft and are standard production type units. The No. 39016 incorporates features which have long been desired in a flexible caupling. No Backlash — Higher Flexibility — Higher Breakdown Voltage — Smaller Diameter — Sharter Length — Higher Alignment Accuracy — Higher Resistance to Mechanical Shock — Salid Insulating Barries Diameter — Sharter Length — Higher Resistance to Mechanical Shock — Salid Insulating Barries Diameter — Melded — Salid Natural States — Salid Nat Insulating Barrier Diaphragm — Malded as a Single Unit.

CERAMIC PLATE OR GRID CAPS - Soldering lug and contact one-piece. Lug ears onnealed and solder dipped to facilitate each combination "mechanical plus soldered" connection of cable.

No. 36001—%6" No. 36002—1/6" No. 36004—1/4"

SAFETY TERMINAL — Combination high voltage terminal and thru-bushing Tapered contact pin fits firmly into canical socket providing large area, low resistance connection. Pin is swivel maunted in cap to prevent twisting of lead wire.

No. 37001, Black or Red No. 37501, Low lass

STEATITE TERMINAL STRIPS Terminal and lug piece. Lugs are turret type and are free floating so as not to strain L4 ceramic on wide temperature variations. Easy to mount with series of round holes. 1400 volt and 3500 volt series.

POSTS, PLATES, AND PLUGS - The No. 37200 series, in-POSIS, PLAIES, AND PLUGS — The No. 37200 series, in-cluding both insulated and non-insulated binding posts with associated plates and plugs, provide various combinations to meet most require-ments. The posts have captive heads and keyed mounting. The No. 37291 and No. 37223 are standard in black or red with other colors on special order. No. 37201, No. 37202, and No. 37204 and No. 37222 are available in black, red, or low loss. The No. 37202 is

also available in steatite.

Description No. Description -Single plates, pr. .37212—Dual plug.. 37291—Single plates (tapered), pr.37222—Non-insulated binding post37223—Insulated binding posts......

DIAL LOCK — Compact, easy to mount, positive in action, does not alter dial setting in operation! Rotation of knob "A" depresses finger "B" and "C" without imparting any rotary motion to Dial. Single hole mounted.

No. 10050.....

TUBE CLAMP — No. 33087 is easy to use, easy to install, effective in function. Available in special sizes for all types of tubes. Single hole mounting. Spring steel, cadmium plated.

"Designed for Application"®










ANEL DIALS — The No. 10035 illuminated panel dial has 12 $^{\circ}$ 1 ratio; size, $^{\circ}$ 8 $^{\circ}$ 9 $^{\circ}$ 7 x $^{\circ}$ 9 $^{\circ}$ 7. Small No. 10039 has 8 to 1 ratio; size, $^{\circ}$ 7 x 3 $^{\circ}$ 4 $^{\circ}$ 7. Both are of compact mechanical design, easy to mount nd have totally self-contained mechanism, thus eliminating back of anel interference. Provision for mounting and marking auxiliary antrols, such as switches, potentiometers, etc., provided on the No. 1035. Standard finish, either size, flat black art metal.

JO35. Stondard trisin, etinet size, tid block of method.

MAFT LOCKS — In addition to the original No. 10060 and No. 2061 "DESIGNED FOR APPLICATION" shaft locks, we can also trinish such variations as the No. 10062 and No. 10063 for easy numb operation as illustrated above. The No. 10061 instantly control, any plain "V_A shaft" valume control, condenser, etc. from plain" to "shaft locked" type. Easy to mount.

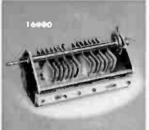DIALS AND KNOBS — Just a few of the many stock types of small dials and knobs are illustrated herewith, 10007 is $1\frac{5}{8}$ " diameter, 10009 is $2\frac{3}{4}$ " and 10008 is $3\frac{1}{2}$ ".

















12000 and 16000 SERIES TRANSMITTING CONDENSERS

— Rigid heavy channeled aluminum end plates, Isolantile insulation, solished or plain edges. One piece rator contact spring and connection lug. Compact, easy to mount with connector lugs in convenient agations. Same plate sizes as \$1000 series above.

ron lug. Compact, easy to mount with connector lugs in convenient acations. Same plate sizes as 10000 series above. The 16000 series has same plate sizes as 0.4000 series. Also has anstant impedance, heavy current, multiple finger rotor contactor if new design. Both 12000 and 16000 series available in single and double sections and many capacities and plate spacing.

28000-29000 SERIES VARIABLE AIR CAPACITORS—
'Designed for Application,' double bearings, stealite end plates, admium or silver plated brass plates. Single or double section 022" or .066" air gap. End plate size: 1%6" x 1½6". Rotor plate adius: 3½". Shaft lock, reor shoft extension, special mounting prackets, etc., to meet your requirements. The 28000 series has emi-circular rotor plate shape. The 29000 series has approximately traight frequency line rotor plate shape. Prices quoted on request. Anny stock sizes.

NEUTRALIZING, CAPACITOR — Designed originally for use n aur awn No. 90881 Power Amplifier, the No. 15011 disc neutralizing capacitor has such unique features as rigid channel frome, horizontal or vertical mounting, fine thread over-size lead screw with stap to prevent shortling and rotar lock. Heavy rounded-edged polished aluminum plates are 2" diameter. Glozed steatite insulation. No. 15011......

04000 and 11000 SERIES TRANSMITTING CONDENSERS

Another member of the "Designed for Application" series of transmitting variable air capacitars is the 04000 series with peak voltage ratings of 3000, 6000, and 9000 volts. Right angle drive, 1-1 ratio. Adjustable drive shaft angle for either vertical ar sloping panels. Sturdy construction, thick, round-edged, polished aluminum plates with 134," radius. Constant impedance, heavy current, multiple finger rotar contactor of new design. Available in all normal capacities.

The 11000 series has 10/1 ratio center drive and fixed angle drive shaft

PERMEABILITY TUNED CERAMIC FORMS — In addition to the popular shielded plug-in permeability tuned forms, 74000 series, the 69040 series of ceromic permeability tuned unshielded forms are available as standard stock items. Winding diameters available from 1/6" to 1/2" and winding space from 1/5" to 1/2".

from 716 to 72 one winding sp	oce from '732 to 1 72 .
No. 69041—(Capper Slug)	No. 69052—(Iron Core)
Na. 69042—(Iron Core)	No. 69054—(Iron Core)
No. 69043—(Copper Slug)	No. 69055(Copper Slug)
No. 69044(Iron Core)	No. 69056—(Iron Core)
No. 69045—(Copper Slug)	Na. 69057—(Copper Slug)
No. 69046(Iron Care)	No. 69058—(Iron Care)
No. 69047—(Copper Slug)	No. 69061(Copper Slug)
Na. 69048—(Iron Core)	No. 69062—(Iron Care)
No. 69051—(Copper Slug)	

"Designed for Application"

MINIATURIZED HIGH RELIABILITY VARIABLE CAPACITORS



Modern demands for miniature precision, high Q variable air dielectric capocitors with high reliability require tha all of the statar plates be machined from a solid block o

all of the stater plates be machined from a solid block ob brass and that all of the rotor plates be machined from c solid block of brass. Staked, soldered, or washer-space, types of construction are adequate for larger capacitor with wider air gaps but are entirely inadequate for minia with wider air gaps but are entirely inacequate for minia ture high reliability capocitors far use at high frequencies. The stator terminal is an integral port of the stator. This results from extruding the exact shape required. The roto shaft is an integral port of the rotor, thus alignment a shaft with rotar is perfect and there are no pins of press fits.

Special capocitors which can be manufactured using all or part of the tooling for standard capacitors are designed and manufactured to order.

















TRANSMITTING TANK COILS — A full line wattages for all bands. Send for special catalog sheet. - A full line - all popular

Nos. 42000, 43000, 44000, 48000.....

TUNABLE COIL FORM $\frac{1}{V_2}$ Standard octal base of low loss micafilled bakelite, polystyrene $\frac{1}{V_2}$ diameter coil form, heavy aluminum shield, iron tuning slug of high frequency type, suitable for use up to 35 mc. Adjusting screw protrudes through center hole of standard octal socket.

No. 74001, with iron core...... No. 74002, less iron core......

RF CHOKES — Many have copied, few have equalled, and nane have surpassed the genuine original design Millen Designed for Application series of midget RF Chokes. The more popular styles now in constant production are illustrated herewith. Special styles and variations to meet unusual requirements quickly furnished.

No. 34100												
No. 34101	_	2.5	mh.,	250	ma	Na.	34106	_	1.0	mh.,	300	ma
No. 34102		2.5	mh.,	250	ma	No.	34107	_	1.0	mħ.,	300	ma
No. 34103	_	2.5	mh.,	250	ma	No.	34108	_	1.0	m h.,	300	ma
No. 34104	$\overline{}$	2.5	mh.,	250	ma	No.	34109	_	1.0	mh.,	300	ma

MILLEN COIL FORMS - Made of low loss mica filled brown bokelite. Guide funnel makes for easy threading of leads through pins.

No. 45000...... No. 45004..... No. 45005.

SPECIAL RF CHOKES — Figures 1 and 4 illustrate special type of RF chokes available on order. The popular 34300 and 34200 serie are shown in figures 2 and 3 respectively.

OCTAL BASE AND SHIELD — Low loss phenolic base with actal socket plug and aluminum shield can $1\%_6 \times 1\%_8 \times 3^1\%_6$.

MINIATURE POWDERED IRON CORE RF INDUCTANCES -

The No. 3300 — Miniature powdered iron core inductances, 0.107 is dia. x 3% in. long. Inductances from 3.3 microhenries to 2.5 milli henries ± 5%. ElA standord values plus 25, 50, 150, 250, 350, 500 and 2500 microhenries. Three layer solenoids from 39 to 350 micra henries. 1/4 in. wide single pi from 360 to 2500 microhenries. Specia coils on order.

PHENOLIC FORM RF INDUCTANCES - The No. 34300 in-THENOLIC FORM RF INDUCTANCES — The No. 34300 Inductances — Phenolic coil form with axial leads. Inductances from 0.15 microhenry to 2.5 millihenries $\pm 5\%$. ElA standard values plus 25, 50, 150, 250, 350, 500, and 2500 microhenries. Solenoids from 0.15 to 16 microhenries. Single pi from 18 to 300 microhenries. Multiple pi for higher inductances. Forms γ_{32} " dia. x γ_{16} in. long, γ_{16} " x γ_{16} ", γ_{16} ", γ_{16} ", and γ_{16} " x γ_{16} ". Special coils on order.

MINIATURE IF TRANSFORMERS — Extremely high Q — approximately 200 — Variable Coupling — (under, critical, and over) with alt adjustments on top. Small size $1/l_0^{\prime\prime\prime}$ x $1/l_0^{\prime\prime\prime}$ Molded terminal base. Air capacitor tuned. Coils completely enclosed in cup cores. Tapped primary and secondary. Rugged construction. High electrical stability.

No. 61455,	455 kc. Universal Trans.
No. 61453,	455 kc. BFO
No. 61160,	1600 kc. Universal Trans
No. 61163	1600 kc REO

LLEN



MINIATURIZED

DESIGNED for APPLICATION miniaturized components developed for use in our own equipment such as the 90901 Oscillo-scope, are now available for separate sale. Many of these parts are similar, in most details except size, to their equivalents in our standard component parts group. In certain devices where complete miniaturization is not paramount, a combination of standard and miniature components may possibly be used to advantage. For convenience, we have also listed on this page the extremely small sized coil forms from our standard catalog.

	DESCRIPTION
CODE	DESCRIPTION

A001 A006

A007 A008

DESCRIPTION

Bar knab for ½" shaft. ½" high by ¾" long.
Fluted black plastic knab with brass insert for ½" shaft.
½" high by ¾" diameter.
¾" black plastic dial knab with brass insert far ¾" shaft.
¾" black plastic wild knab with brass insert far ¾" shaft.
¾" black plastic knab. Same os no. A007 except far style.
Right angle drive far ¾" shafts. Single hale mounting.
1" bar dial far ¼" shafts. Single hale mounting.
1" bar dial far ½" shafts. Single hale mounting.
1 bar dial far ½" scale. A012 A014

clockwise or counter-clackwise ratation.
I'' fluted knob dial for 1/8" shaft, 1/2" high. Same dial plates A015

as no. A014.

1½'' diameter fluted black plastic knab far ½'' shaft.

Knob, same as no. A007 except with ¾'' diameter

Knob, same as no. A007, but without dial. A017

diameter skirt. A018 A019 A021

Miniature metal index for miniature dials. A0.50

Miniature dial lack, Shaft lack for 1/8" diameter shaft, 1/4"-32 bushing, Nickel plated brass. A062

Shaft lock with knurled locking nut.
Shaft bearing for ½" diameter shafts. Nickel plated brass,
Fits ½"diameter hole. A066

COMPONENTS

CODE DESCRIPTION

Steatite ceramic standoff or tie-paint, Integral mounting eyelet, 0.205" overall diameter. E001

Block or red plastic binding post plates for Na. E222. F201 Black or red plastic plates for two binding posts spaced 1/2". E202

Black or red plastic plug for two binding pasts spaced 1/2" E212 E222 Metal binding past with jack top.

to E306A Steatite ceramic terminol strips. 1/6" wide. Terminals spaced 3/4" an centers. Screw type or salder type E302A thru-terminals.

J300-3.3 to J300-2500 Camplete line of miniature inductances 3.3 to 2500 microhenries. %" long. Diameter 0.115" to 0.297".

Insulated universal joint style flexible caupling far 1/8" dio. M001

M003 M004

M005

shafts.
Salid caupling for ½" dio. shafts. Nickel plated brass.
Universal joint style flexible coupling for ½" diometer shafts.
Inverted hubs for shart length. Not insulated.
Universal joint style flexible coupling for ½" diameter shafts.
External hub for moximum flexibility. Not insulated.
Universal joint style flexible caupling for ½" diameter shafts.
Spring finger. Steatite ceramic insulation.
Ye" diameter shafts.
Plastic insulated acupling with nickel plated brass inserts for Ye" diameter shafts. M006

M008

 γ_8 a animeter snatts. Plastic insulated flexible coupling for V_8''' diameter shafts. $1\gamma_8'''$ long by $1\gamma_8'''$ diameter. Bronze yake. Insulated shaft extension for V_8''' 32 bushing and V_8''' shaft for mounting sub-miniature potentiameter. M017 M023

M024

69043 69044

15



FOR EVERY APPLICATION

IMMEDIATELY AVAILABLE - FROM STOCK

Over 1,000 items to cover virtually every electronic application. . . . 400 Hermetic items, proved to MIL-T-27A, eliminate costly test delays. . . Highest reliability in the field. . . . Immediately available from your local distributor. Write for catalog.





FILTERS

TELEMETERING 400 to 70000 CYCLES.





LOW PASS HIGH PASS BAND PASS 60 to 12000 CYCLES.

TELEGRAPH 425 to 2975 CYCLES.

VARIABLE

DECADE

PERMALLOY DUST TOROIDS HIGHEST Q, ACCURACY, STABILITY.





MINIATURE HERMETIC

TRANSISTOR POWER



INVERTERS TO 550V

TRANSISTOR SUPPLY

COMPACT WIDE RANGE



ULTRA COMPACT





VOLTAGE ADJUSTORS . . . STEPDOWN . . . ISOLATION UNITS TO 2500 W.

COMMERCIAL GRADE



HERMETIC POWER COMPONENTS



PLATE TO 6 KV CT



REACTORS TO 1.25A



FILAMENT 400 CYCLE

HERMETIC **AUDIOS**



PULSE



MINIATURE WOUND CORE.





HIGHEST FIDELITY





LINEAR STANDARD

BROADCAST AND HI-FI FAVORITES





FOR SERVO MOTORS 2 TO 18 WATTS.

REPLACEMENT TYPES



AUOIO, POWER, FILAMENT AND REACTORS TO 200 MA.

And Special Units to Your Specifications

UNITED TRANSFORMER CORPORATION

150 Varick Street, New York 13, N. Y.

PACIFIC MFG. DIVISION: 4008 W. JEFFERSON BLVD., LOS ANGELES 16, CALIF. EXPORT DIVISION: 13 EAST 40th STREET, NEW YORK 16, N. Y. CABLES: "ARLAB"



The finest amateur equipment built...

YOUR PORTABLE HAM SHACK



Collins KWM-2 SSB Transceiver

This versatile single sideband transceiver serves both your fixed station and mobile needs on any fourteen 200-kc bands between 3.4 mc and 29.7 mc (except 5.0—6.5 mc). Crystals are provided for all HF bands except 10 meters where one crystal is supplied with provision for two additional crystals. Now you can move your ham station from the desk to the mobile mount in your car in minutes.

The compact, lightweight KWM-2 provides ample power on 80 through 10 meters with 175 watts PEP input on SSB, or 160 watts on CW. With a two-tone audio keyer and a converter unit, the transceiver may be adapted for RTTY use.

Filter-type SSB generation, Collins permeabilitytuned oscillator, crystal-controlled HF double conversion oscillator, VOX and anti-trip circuits, automatic load control, and RF inverse feedback are top features of the KWM-2.

The Collins 2.1-kc Mechanical Filter, RF amplifier, tuned circuits and several tubes perform the dual role of transmitting and receiving. CW break-in and monitoring sidetone circuits are built in. Four plugs in the mobile mount connect the KWM-2 automatically. A connector provides for antenna selection or loading coil selection for mobile operation.

The KWM-2 is easy to operate. The planetary 20-kc-per-turn knob allows accurate tuning. One-kc divisions on all bands provides ease of tuning and meeting schedules on frequency. Includes 100-kc crystal calibrator.

The KWM-2 weighs 18 lbs. 3 oz. and measures 7¾" H (including legs), 14¾" W, and 13¼" D. Mounts, accessories and power supplies are available for 12-v dc, and 115- and 230-v ac operation.




The finest amateur equipment built...

THE COLLINS S/LINE System Engineered to Give You the Finest in Fixed Station SSB Performance

For the advanced radio operator who wants the only system engineered fixed station available, Collins offers its famous S/Line. Based on a systems concept, each unit of the S/Line augments the others, giving you a complete single sideband station.


With the receiver and transmitter interconnected, the two may be operated as a transceiver. A frequency control switch provides for separation of transmit and receive tuning.

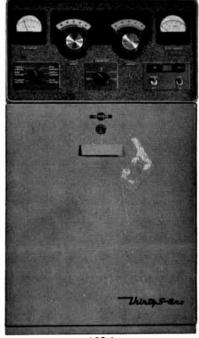
Finished in gray tones, with clean, smooth lines and front panels of dark gray simulated leather, Collins S/Line is equally welcome in your ham shack, den or family room. Each time you go on the air with a complete Collins S/Line, you are assured of the cleanest, clearest signal on the amateur bands.




30S-1



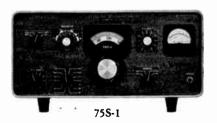

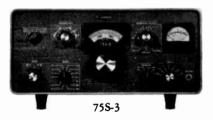

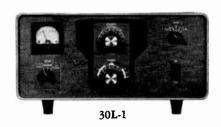

32S-1 Transmitter

The 32S-1 is an SSB or CW transmitter with a nominal output of 100 watts between 3.4 and 29.7 mc (except 5.0 to 6.5 mc). Crystals furnished cover HF amateur bands and 200 kc on 10 meters. Input power is 175 watts PEP on SSB or 160 watts on CW.

Features built into the 32S-1 include Mechanical Filter-type sideband generation; stable, permeability-tuned VFO; crystal-controlled HF oscillator; RF inverse feedback for better linearity; automatic load control for higher average talk power, and protection against flat-topping.

For ac operation, the 516F-2 Power Supply is used with the 32S-1; for 12-v dc operation, the MP-1 Power Supply may be used.

312B-4 Speaker Console

The 312B-4 provides a unitized control for the S/Line or the KWM-2. It houses a speaker, RF directional wattmeter with 200- and 2000-watt scales, and switches for station control functions.

75S-3 Receiver

The 75S-3 provides SSB, CW and AM reception between 3.4 and 29.7 mc (except 5.0—6.5 mc) by selection of the appropriate HF heterodyning crystals. Crystals furnished cover HF amateur bands except the 10 meter band, where one crystal is supplied plus provision for two more.

Features incorporated in the 75S-3 include dual conversion with a crystal-controlled first heterodyning oscillator; bandpass first IF; stable, permeability-tuned VFO; RF amplifier designed to minimize cross modulation products; 2.1-kc Mechanical Filter and 200-cycle crystal filter; excellent AVC characteristics; both product and diode detector; rejection notch filter; manual and crystal BFO, and AGC time constant control. The advanced design of the 75S-3 includes the use of only 150 volts on vacuum tube plates, use of silicon diodes in lieu of conventional high vacuum rectifier; and the choice of three degrees of selectivity (also optional Mechanical Filters for AM). Provision for obtaining power from a dc power supply is also made.

With the new Collins 75S-3, you can be assured of the finest amateur receiver available for reception of the CW, SSB, or RTTY modes.

75S-1 Receiver

The 75S-1, designed primarily for SSB, incorporates such features as Collins famous frequency stability; dual conversion; 2.1-kc Mechanical Filter with provision for adding 500-cps Mechanical Filter for CW; AVC system tailored for SSB; silicon rectifiers, and provision for AM reception.

30S-1 and New 30L-1 Linear Amplifiers

The 30S-1 is a completely self-contained, single tube, grounded grid linear amplifier. Requiring 70 to 100 watts driving power (from the 32S-1 or KWM-2), it provides the full legal power input for SSB, CW or RTTY. The tube used is the Eimac 4CX1000A. The 30S-1 may be used on any frequency between 3.4 and 29.7 mc. A special comparator tuning circuit allows tune-up at low power to avoid exceeding the legal dc input of 1 kw. Push button selection of either linear amplifier or exciter output from the front panel. Antenna relay included. Conservatively rated.

The new compact 30L-1 Linear (the same size as the famous KWM-2) provides for 1000 watts PEP input on SSB (500 watts average dc) and 1000 watts average on CW, and has a self-contained power supply. It is designed to be driven by Collins KWM-1, KWM-2 or 32S-1, as well as from most other 70-100 watt CW/SSB exciters. The new unit also features RF inverse feedback; automatic load control; silicon rectifiers and a high/low power switch. Instant warm-up time. Automatic antenna switching from exciter to amplifier included.

Extended Frequency Versions of the S/Line

The 32S-1 and 75S-3 are available in extended frequency versions, designated the 75S-3A and 32S-2. The two differ from the original in that an additional crystal board has been added beneath the chassis. In this board is placed the standard complement of ham band crystals normally received with the equipment. The upper board is available for the placement of whatever additional crystals may be desired up to a total of 14. A front panel switch is added to allow switching between the two crystal boards.



The finest amateur equipment built . . .

COLLINS S/LINE AND KWM-2 ACCESSORIES





302C-3 Directional Wattmeter — Measures forward and reflected power on 200- and 2000-watt scales with accuracy and without calibrating adjustments. Coupler unit mounts separately from indicator-control box. Power loss and mismatch introduced by the instrument are negligible. Fixed or mobile applications.

351E Table Mounts — For mounting the S/Line and KWM-2 and accessories on planes, boats, etc. May be fastened to any flat surface. Front clamps attach to the feet of the units to hold them securely.

351D-2 Mobile Mount — Provides secure mounting for KWM-2 in most automobiles. Cantilever arms fold out of the way when the unit is removed. Mating plugs connect power, receive-transmit antenna, noise blanker antenna, speaker and antenna control as KWM-2 slides into place. Power Supply Cable included.

DL-1 Dummy Load — A 100-watt resistive load for all HF frequencies. Connects permanently in antenna coax line. Front panel or remote switch allows selection of "antenna" or "load." Provides easy comparison of antenna SWR and non-band interference tune-up. Will absorb 30L-1, 30S-1 outputs for short periods. Choice of Type N or RCA antenna connectors.

312B-5 Speaker Console and External PTO—Used with the KWM-2 in fixed station operation to provide separation of receive and transmit frequencies, speaker, directional wattmeter, plus switching for functional control of system. Styled to match KWM-2.

399C-1 Speaker and External PTO — Contains a speaker and a PTO (as in the 312B-5).

136B-2 Noise Blanker—An accessory for the KWM-2 for mobile operation. This noise blanker provides effective reduction of impulse-type noise—particularly ignition noise. Requires separate antenna resonant at 40 mc. Properly installed, this 136B-2 can be the difference between operating and not operating when around other cars.

312B-3 Speaker — Contains a 5" x 7" speaker and connecting cable. Styled to match receiver, transmitter.

516F-2 AC Power Supply — Operates from 115 v ac, 50-60 cps. Provides all voltage for the 32S-1 and KWM-2. Cabinet has provision for mounting a speaker styled to match the KWM-2.

MP-1 Mobile Power Supply — A transistorized inverter powered from a 12-v automobile, aircraft, or boat storage battery to the voltages required for operation of the KWM-1, KWM-2 or KWM-2A. Wiring cable is normally supplied with 351D-2.

440E-1 Cable — For use with MP-1 when the 351D-2 mount is not used. 22' long with plug to match KWM-2 on one end; provision for solder lugs on opposite end.

PM-2 Portable Power Supply — The new PM-2 is compact, lightweight, and provides all voltages needed for the KWM-2. Connects easily and quickly to rear of KWM-2. Operates from either 115 v ac or 220 v ac at 50-400 cps to provide a completely portable SSB and CW station. Contains a small speaker. The PM-2 and KWM-2 may be carried in the CC-2 carrying case, with a combined weight of less than 45 pounds.

MM-1 Mobile Microphone — A dynamic microphone designed to fit comfortably in your hand. A 5' length of coiled cord and attached PJ-068 is supplied with the 22-ounce microphone. For use with the KWM-2 or the S/Line. Push-to-talk switch. Hanger bracket furnished. Brushed aluminum finish. MM-2 Boom Microphone — A high-impedance reluctance microphone/single earphone combination for fixed or mobile operation. PTT not required; operates with VOX control. Sponge-padded headband clasps head firmly but lightly. Microphone boom and ear pipe adjustable for proper fit. Cord and attached plugs furnished.

CC-2 Carrying Case — Specially designed Samsonite Silhouette case for the KWM-2/PM-2 or 30L-1. Attractive molded Royalite interior protects equipment against rough handling. Two spare pockets.

MM-3 Boom Microphone — A high-impedance boom mike which has the same characteristics as the MM-2 except that there is no earphone built into the headset of the MM-3. Ideal for fixed station use where freedom of movement is desired.

SM-1 Desk-Top Microphone — A high-impedance, dynamic mike with styling and output level to match S/Line and KWM-2. Satin aluminum finish. Five-foot coiled cord and attached PJ-068 plug furnished.

351R-1 Rack Adapter — Matching gray rack panel with hardware for mounting 75S-1, 32S-1, KWM-2 or 30L-1. Supporting shelf holds unit securely.

351R-2 Rack Adapter — Matching gray rack panels with hardware for rack mounting S/Line and KWM-2 accessories, 516F-2, 399C-1, 312B-4 and 312B-5. Supporting shelf holds unit securely.

399B-4 Novice Adapter — Plugs into 32S-1 to provide four crystal-controlled channels for novice operation of 32S-1. Crystals not furnished. Removal of one 6146 reduces power of 32S-1 to proper level.

399B-5 Novice Adapter — Plugs into KWM-2 to provide four crystal-controlled channels on transmit. Receiver remains PTO tuned. Crystals not furnished. Removal of one 6146 reduces power of KWM-2 to proper input for novice use.

For further information on the Collins S/Line and accessories, see your nearest authorized Collins distributor or write: Amateur Sales, Collins Radio Company, Cedar Rapids, Iowa.



All that's new in PLASMA research



read December

Proceedings

for the facts!

No matter what your field in electronics, having a working knowledge of plasmas is greatly to your advantage. Why? Because plasmas are becoming increasingly important in electronics research and application.

Think of the major new developments in this field. Scientists are using gaseous plasmas to convert heat directly into electricity. Will this affect your work? Of course it will! Others are designing new vacuum pumps, again with gaseous plasmas helping to increase efficiency. Do you see the impact this will have on vacuum tubes, on a whole host of electronics products?

Much specialized research has been done on gaseous plasmas in the last few years. Much more is being planned. To catch up with it, you'd have to read a mass of technical papers. weed through conflicting theories, and often find at the end that the research is not pertinent to your work at all.

Realising this . . .

Proceedings of the IRE devotes its entire December issue to a survey of plasma research and findings to date... More than 15 technical papers, each one written by an authority, will spell out what plasmas are, how they behave, what they can do. Guest editor is Dr. E. W. Herold, Vice President, Research, Varian Associates.

Every special issue of *Proceedings* in the past has remained a definitive reference work for years. Many were sold out almost immediately. If you are not a member of the IRE, make sure of your copy of the December special issue on plasmas by sending in the coupon immediately.

Proceedings of the IRE

The Institute of Radio Engineers
1 East 79th Street, New York 21



more than 15 definitive papers covering the following areas of plasma research and application:

- 1 Fundamental plasma processes
- 2 Applications to communications
- 3 Electric power generation
- 4 Propulsion systems
- 5 Low density plasma explorations
- 6 Generation and amplification of oscillations in plasmas
- 7 Diagnostic procedures

The Institute	of Radio	Engineers
1 East 79th	Street, New	York 21

Please send	me	the	December	1961	issue	of	Proceedings	of	the	IRE,
containing a	ELIPV	ev c	f the resea	irch c	arried	out	on plasmas			

Enclosed is \$3.00 (for non-members only).*


Enclosed is company purchase order.

*Extra copies to IRE members, \$1.25 each (limit: 1 extra to a member).

NAME....

COMPANY...

ADDRESS...

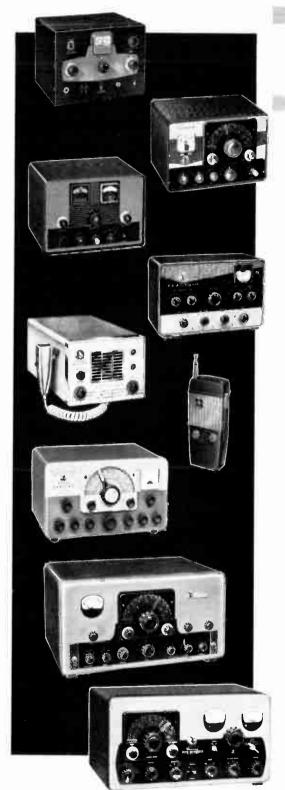

CB Equipment

Write for FREE 4-page color brochure describing "Messenger", "Personal Messenger", antennas and accessories!

VIKING 1st

ADVENTURER—Self-contained50 watts CW inputrugged 807 transmitting tubeinstant bandswitching 80 through 10 meters. Crystal or external VFO control—wide range pi-network output—timed sequence keying. With tubes, less crystals. Cat. No. 240-181-1 Kit
Cat. No. 240-181-1 Kit Net \$ 54.95
NAVIGATOR—40 watts CW input also serves as a flexible VFO exciter. 6146 final amplifier tube—bandswitching 160 through 10 meters. Built-in VFO or crystal control. With tubes, less crystals, Cat. No. 240-126-1 Kit Net \$149.50 Cat. No. 240-126-2 Wired, tested Net \$199.50
CHALLENGER—70 watts phone input 80 through 6; 120 watts CW input 80 through 10 85 watts CW on 6 meters. Two 6DQ6A final amplifier tubes. Crystal or external VFO control—TVI suppressed—wide range pi-network output. With tubes, less crystals. Cat. No. 240-182-1 Kit
Cat. No. 240-182-2 Wired, tested Net \$154.75
6N2—Rated 150 watts CW and 100 watts phone—instant bandswitching coverage 6 and 2 meters. Fully TVI suppressed—use with "Viking I, II", "Ranger I, II", "Valiant" or similar power supply/medulators. Uperates by crystal control or external VFO with 8-9 mc. output. With ubes, less crystals. Kit
Cat, No. 240-201-2 Wired, tested , Net \$169.50
10 METER "MESSENGER"—A compact, superbly-engineered transceiver. Ideal for fixed location or mobile operation. Completely crystal controlled, the 10-Meter "Messenger" contains 10 tubes (including rectifier). Instant selection of five frequencies in the range of 29.4 to 29.7 mcs., within a 300 kc. segment of the 10-meter band. Superheterodyne receiver has excellent sensitivity and selectivity. ANL, AVC—positive action (request). Wide range pi-L network output, push-to-talk ceramic microphone! Transmitter section uses a 7054 crystal scillator coupled to a high gain 7061 final amplifier—deliver scillation crisp, well modulated signal! Unit is light weight, easy to install. With power cords, tubes, microphone and 29,640 kc. crystals for Vacional Calling and Emergency Frequency. Cat. No. 242.201 15V AC only Cat. No. 242.203 115V AC/EV DC. Net \$139.75 Cat. No. 242.203 115V AC/EV DC. Net \$139.75 Cat. No. 242.203 115V AC/EV DC. Net \$139.75 Cat. No. 242.203 115V AC/EV DC. Net \$139.75 Cat. No. 242.203 115V AC/EV DC. Net \$139.75 Cat. No. 242.203 115V AC/EV DC. Net \$139.75
10 METER "PERSONAL MESSENGER" Compact, hand-hald crustal
controlled transceiver. Available in 100 milliwatt or 1 wait output models. Gosteins eleven transistors and four diodes. Unit is fleshle and easy to operate. Superheterodyne receiver with exclusive tuned RF amplifier gives twice the sensitivity and more than 40% increase in range over similar type units with conventional circuitry. Both transmitter and receiver sections have staggered tuned circuits for frequency coverage from 29.450 nic. to 29.700 nic, williput returning any portion of ellher section. Powerful two-stage transmitter punches signal home even at extreme ranges—delivers higher power output than similar units with same rated input! Shaped high output "pushpull" audio provides unmatched intelligibility and razor-sharp voice reproduction for 100% copy! For operation with penlight cells or ecchargeable nickel cadmium batteries. Accessories, in addition to
those listed below, include earphone and plug, car cigarette lighter dadapter. Cat. No. 242-103 10 Meter "Personal Messenger", 100 milliwatt, with 29.640 crystal, 8 penlight cell battery case Net \$109.50 Cat. No. 242-104 10 Meter "Personal Messenger", 1 watt, with 29.640 crystal, 8 penlight cell battery case Net to be Announced Cat. No. 251-806 Leather carrying case and strap, Net \$8.50 Cat. No. 230-804 Rechargeable nickel cadmium battery. Plugs into 115 V AC outlet to recharge Net \$19.95
RANGER II—Now—a new version of the popular 75 watt CW or 65 watt AM "Ranger". The "Ranger II" transmitter also serves as an RF/audio exciter for high power equipment. Completely self-contained instant bandswitching 160 through 6 meters! Operates by built-in VFO or crystal control. High gain audio-timed sequence keying. TVI suppressed, Pi-nelwork antenna load matching from 50 to 500 ohms. With tubes, less crystals.
Cat. No. 240-162-2 Wired, tested Net \$359,50
VALIANT—275 watts input CW and SSB (P.E.P. with auxiliary SSB exciter) 200 watts phone. Instant bandswitching 160 through 10 meters—built-in VFO or crystal control. Pi-network output matches antenna loads from 50 to 600 ohms. TVI suppressed—timed sequence keying—built-in low pass, audio filter—self-contained power supplies. With tubes, less crystals. Cat. No. 240-104-1 Kit
Lat. No. 240-104-2 wirea, testea Net \$439.50
FIVE HUNDRED—Full 600 watts CW—500 watts phone and SSB (P.E.P. with auxiliary SSB exciter). Compact RF unit designed for desk-top operation. All exciter stages ganged to VFO tuning—may also be operated by crystal control. Instant bandswitching 80 through 10 meters—TVI suppressed—high gain push-to-talk audio system. Wide range pi-network output. With tubes, less crystals. Cat. No. 240-500-1 Kit
Car. 110. 240-300-2 Miled, tested



Choice Among Nation's Amateurs!



The world at your fingertips!

The world at your fingertips!

VIKING "KILOWATT" AMPLIFIER—The only transmitter that provides maximum legal power in all modes—SSB. CW, and plate modulated AM. Class C final amplifier operation provides plate circuit efficiencies in excess of 70% with unequalled broadcast-type high level amplitude modulation. Two 4-440A tubes in Class AB2 easily deliver 2000 watts P.E.P. (twice average DC) in SSB mode—provides 1000 watts input AM with two push-pull 810 tubes in Class B modulator service. 1000 watts input Class B modulator service. 1000 watts input Class B modulator service. 1000 watts input Class B modulator service. 1000 watts input Class B modulator service. 1000 watts put circuit will match 50 to 500 ohm antenna loads. Pedestal contains complete unit. Excitation requirements: 30 watts RF and 10 watts audio for AM. 10 watts peak for SSB. with tubes.

Cat. No. 240-1000 Wired Net \$1595.00 Cat. No. 251-101-1 Matching accessory desk top, black and three-drawer pedestal ... Net \$132.00



"COURIER"—Rated a solid 500 watts P.E.P. input with auxiliary SSB exciter as a Class B linear amplifier; 500 watts CW or 200 watts AM linear. Self-contained desk-top package—continuous coverage 3.5 to 30 mcs. Drive requirements: 5 to 35 watts depending on mode and frequency desired. TVI suppressed. With tubes and built-in power supply. Cat. No. 240-352-2 Wired ... Net \$289.50

"THUNDERBOLT"—The hottest linear amplifier on the market—2000 watts P.E.P. (twice average DC) input SSB; 1000 watts CW; 800 watts AM linear. Continuous coverage 3.5 to 30 mcs—instant bandswitching. Drive requirements: approx. 10 watts Class AB2 linear, 20 watts Class C continuous wave. With tubes and built-in power supply. Cat. No. 240-353-1 Kit. . Net \$524.50 Cat. No. 240-353-2 Wired . Net \$589.50



"6N2 THUNDERBOLT"—1200 watts (twice average DC) input SSB and DSB. Class ABI: 1000 watts CW, Class C, and 700 watts input AM linear. Continuous bandswitched coverage on 6 and 2 meters. TVI suppressed, Drive requirements; approx. 5 watts Class ABI linear, 6 watts Class C CW. With tubes and builtin power supply

and built-in power supply. Cat. No. 240-362-1 Kit . . Cat. No. 240-362-2 Wired

INVADER—More exclusive features than any other Transmitter/Exciter on the market today! Specially developed high frequency symmetrical, multi-section band-pass crystal filter for more than 60 db sidehand suppression—more than 55 db carrier suppression! Instant bandswitching 80 through 10 meters—no extra crystals to buy—no realigning necessary. Delivers solid 200 watts CW and P.E.P. SSB input; 90 watts input AM. Built-in VFD—exclusive RF controlled audio A6C and ALC (limiter type) provide greater average speech power. Wide range pi-network output circuit—extremely smooth. VDX and anti-trip circuits. Fully TVI suppressed. Self-contained heavy-duty power supply. Wired, tested, tubes and crystals.


HIGH POWER CONVERSION—Take the features and performance of your "Invador"... add the power and flexibility of this unique viking "Hi-Power Conversion" system... and you're "on the air" with the "Invader 2000". Wired, tested, includes everything you need—no soldering necessary—complete conversion in one evening. Cat. No. 240-303-2 Net \$619.50

INVADER 2000—Here are all of the fine features of the "Invader", plus the added power and flexibility of an integral linear amplifier and remote controlled power supply. Rated a solid 2000 watts P.E.P. (twice average DC) input on SSB; 1000 watts CW; and 800 watts input AM! Wide range output circuit (40 to 600 ohms adjustable). Final amplifier provides exceptionally uniform "Q". Exclusive "push-pull" cooling system, Heavy-duty multi-section power supply, Wired, tested, power supply, tubes and crystals.

Cat. No. 240-304-2 Net \$1229.00



WASECA, MINNESOTA

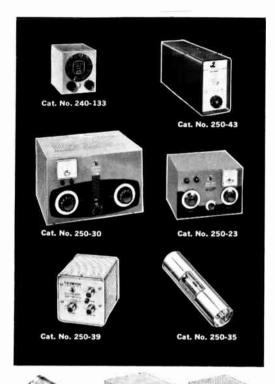



STATION ACCESSORIES

. Net \$54.95 Cat. No. 250-30-3 Kilowatt, with directional coupler and indicator Net \$149.50

LOW PASS FILTER—Wired and pre-tuned.
Cat. No. 250-20 52 ohms impedance Net \$14.95
Cat. No. 250-35 72 ohms impedance Net \$14.95







Cat. No.

Cat. No. 250-25

Cat. No. 250-28



Cat. No. 250-29









114-310 Cat. No.

POWER REDUCER—Up to 20 watts continuous dissipation with 100-150 watt transmitters, used as exciters for Viking "Kilowatt". Net \$13.95

Cat. No. 250-34

POWER DIVIDER—Up to 35 watts continuous dissipation with 50-75 watt output transmitters, when driving 'iking 'ikilowatt'. Cat. No. 250-34 Net \$25.5

ATTENUATOR5—6 db attenuation with power dissipation to serve as exciters for Viking "Thunderbolt".

Cat. No. 250-42-1 for Viking "Ranger" Net \$21.50 Cat. No. 250-42-3 for HT-32 or similar unit . . . Net \$21.50

"SIGNAL SENTRY"—Monitors CW or phone signals up to 50 mc-without tuning. Energized by transmitter RF. With tubes. Cat. No. 250-25 Net \$22.00

CRYSTAL CALIBRATOR—Provide accurate 100 kc check points to 5 mc. with tube, crystal, power cable and extension lead. Cat. No. 250-28 Net \$17.95

DIRECTIONAL COUPLER AND INDICATOR—Provides continuous reading of SWR and relative power in transmission line.
Cat. No. 250-37 Coupler Net \$11.75
Cat. No. 250-38 Indicator Net \$25.00

PRE-TUNED BEAM5—With 3 elements, boom and balun matching

STANDARD KEYS-With Johnson "cushion-contact" design for STANDARD NETS-WITH STANDARD STANDARD STANDARD NETS-WITH STANDARD NETS-

DELUXE SEMI-AUTOMATIC KEYS-Adjustable from lowest to high-

cets speeds. Smooth, easy action.

Cat. No. 114-500 % contacts, black wrinkle base . Net \$20.65

Cat. No. 114-501 % contacts, chrome base Net \$20.65

free catalog

Write today for our newest Amateur Catalog! Available nowcontains photos, schematics, and detailed specifications!

FIRST CHOICE AMONG THE NATION'S **AMATEURS**





It pays to insist on

crystals

STANDARD OF EXCELLENCE SINCE 1934

AMATEUR TYPES

Fundamental, PR Type Z-2

Frequency Ranges in Kcs.: 3,500 to 4,000 (80M); 7,000 to 7,425 (40M); 8,000 to 8,222 (2M); 8,334 to 9,000 (6M).

Rugged. Low drift, fundamental oscillators. High activity and power output. Stands up under maximum crystal currents. Stable,

Third Overtone, PR Type Z-9A

6 Meters, PR Type Z-9A

Fifth overtone; for operating directly in 6-meter band; hermetically sealed; calibrated 50 to 54 Mc., ±15 Kc.; .050" pins. \$4.95 Net

CITIZENS BAND CLASS "D" Type Z-9R, Transmitter

FCC assigned frequencies in megacycles: 26.965, 26.975, 26.985, 27.005, 27.015, 27.025, 27.035, 27.055, 27.065, 27.075, 27.085, 27.105, 27.115, 27.125, 27.135, 27.105, 27.205 calibrated to .005%. (Be sure to specify manufacturer and model number of equipment) \$2.95 Net CITIZENS BAND CLASS "D"

Type Z-9R, Receiver Specify I.F. frequency, also whether receiver oscillator is above or below transmitter frequency. Calibrated to .005%. (Be sure to specify manufacturer and model number \$2.95 Net of equipment.)

Type Z-9R, Radio Control FCC assigned frequencies in megacycles: 26.995, 27.045, 27.095, 27.145, 27.195, 27.255; calibrated to .005%. (Be sure to specify manufacturer and model number of equipment.) \$2.95 Net

Type 2XP

2XP

Z-9R

Suitable for converters, experimental, etc. Same holder dimensions as Type Z-2.

1600 to 12000 Kc., (Fund.) ±5 Kc......\$3.45 Net 12001 to 25000 Kc. (3rd Overtone) ±10 Kc......\$4.45 Net

ALL PR CRYSTALS ARE UNCONDITIONALLY GUARANTEED.
ORDER FROM YOUR JOBBER.

COMMERCIAL TYPES

Commercial Crystals available from 100 Kc. ta 70 Mc. Prices on request.

Type Z-1, MARS and CAP Official assigned frequencies in the range. Calibrated to .005%. 1600 to 10000 Kc.....\$3.45 Net

Type Z 1, TV Marker Channels 2 thru 13....\$6.45 Net

4.5 Mc. Intercarrier, .01 % \$2.95 Net 5.0 Mc. Signal Generator,

.01 % \$2.95 Net 10.7 Mc. FM, IF, .01 %\$2.95 Net

Type Z-6A, Frequency Standard

To determine band edge. To keep the VFO and receiver properly calibrated. 100 Kc. .. \$6.95



PETERSEN RADIO CO., Inc. 2800 W. Broadway COUNCIL BLUFFS, IOWA

EXPORT SALES: Royal National Corporation, 250 W. 57th Street, New York 19, N.Y., U.S.A.

FOR SALE: MEMBERSCRIPTIONS!

o, it's not a piece of ham gear, but every ham should have one. Nearly all active hams do, and even some nonhams have at least one in the family. It's not edible but it does give you something to chew on. Part of it is intangible, the other part is black and white, but should be read.

That is it? Shucks, OM—a memberscription is a combination membership in the American Radio Relay League and a subscription to QST magazine. It's an investment in goods and services that can't be duplicated anywhere for twice the price. It's an investment that pays dividends right from the first day and increases in value over a period of years.

The fellow who already has a memberscription well knows that his investment helps support an organization that represents his hobby at all international radio conferences, in the Congress, and before domestic regulatory agencies, an organization that publishes over a dozen books and booklets to help the beginner get started and the licensed ham advance himself, an organization that sponsors conventions, contests, and awards such as DXCC, WAS, and the RCC, and an organization that is completely governed and run "By and For the Amateur."

The biggest tangible dividend is QST magazine, packed with the latest of everything, and delivered 12 times during each memberscription. When saved, back issues of QST make an unsurpassed and invaluable reference library of technical as well as historical data.

good ops, and bad ops (maybe exposure to QST will help them lose their LIDS). Whatever the motive, every ham should get a memberscription and join with nearly 100,000 others in working toward making ham radio a hobby we can all continue to enjoy and be proud of.

Memberscriptions only \$5 a year in the U.S., \$5.25 in Canada, and \$6 elsewhere

THE AMERICAN RADIO RELAY LEAGUE, INC.

WEST HARTFORD 7, CONNECTICUT

.........

More UHF Power for Mobile Applications



The air-cooled RCA-8121 and RCA-8122 high-perveance "tetrodes" offer more UHF power than ever in compact "low-cost" mobile communications. Featuring a 13.5-volt heater, these beam power tubes give dependable performance with battery operation. The RCA-8072 is a conduction-cooled version of the radiator types. These three unique types employing ceramic-metal construction represent another first from RCA for mobile use.

RCA CERAMIC-METAL TUBES FOR MOBILE USE

Typical CW Operation

Туре	Cooling	Maximum plate Dissipation	Plate Volts	Freq. Mc	Useful Power Output Watts		
8121	Conduction	100*	700	50 175 470	110 105 85		
8122	Forced-Air	150	1500	up to 500	235		
8072	Forced-Air	400	2000	up to 500	300		

*May be higher depending on heat-sink design.



The Most Trusted Name in Electronics

BEAM POWER for All Powers

Whether you're on SSB, AM, or CW-QRP or QRO-there's an RCA beam power tube for every amateur transmitter power level and for frequencies to 450 Mc and beyond.

Beam power tubes make it practical to build compactness into your rig. They do the job with fewer stages, less expensive components, fewer controls. RCA beam power tubes deliver the power with relatively low plate voltages. Thousands of commercial transmitters prove out these facts.

For more useable "transmitter watts" for your dollars, "Socket-up" with RCA beam power tubes. Check the chart at the right for the types you need-and order direct from your RCA Industrial Tube Distributor.

RCA Type	Class of Service	Max. Plate- Input Watts	Max. DC Plate Volts#	Max. Freq. For full Input (Mc)	Max. useful Freq. (Mc)	Heater (H) or Filament (F Volts
5763	CW	17 15	350 300	} 50	175	6.0 (H)
6417	Same as	RCA-5763	except fo	r heater vo	Itage	12.6 (H)
2E26	CW SSB AM	40 37.5 27	600 500 500	} 125	175	6.3 (H)
2E24	Same as	RCA-2E26	, but has c	uick-heatin	g filamen	t 6.3 (F)
6893	Same as	RCA-2E26	except fo	r heater vo	Itage	12.6 (H)
832-A*	CW AM	50** 36**	750 600	} 200	250	6.3▲(H) 12.6●(H)
807	CW SSB AM	75 90 60	750 750 600	60	125	6.3 (H)
1625	Same as	RCA-807, of medium	except for 7-pin base	heater vol	tage	12.6 (H)
6524*	CW SSB AM	85** 85** 55**	600 600 500	} 100	470	6.3 (H)
6850*	Same as	RCA-6524	, except fo	r heater vo	Itage	12.6 (H)
4604	cw	90	750	60	175	6.3 (F) quick-heatin
6146	CW SSB AM	90 85 67.5	750 750 600	} 60	175	6.3 (H)
6883	Same a	RCA-6146	except fo	r heater vo	ltage	12.6 (H)
829-B*	CW SSB AM	120** 120** 90**	750 750 600	} 200	250	6.3▲(H) 12,6●(H)
7203/ 4CX250B	CW SSB AM	500 500 300	2000 2000 1500	} 500		6.0 (H)
7094	CW SSB AM	500 400 335	1500 2000 1200	} 60	175	6.3 (H)
813	CW SSB	500 450	2250 2500	30	120	10 (F)

*Twin-Type **Total for both Units •For series-heater connection

▲For parallel-heater connection ■Max. Ratings for amateur use

For technical data on any of these types write RCA, Commercial Engineering, Section A-11-M, Harrison, N. J.



in Electronics



AFLECTRON (



INTRODUCING ...



Model 6100
TRANSMITTER



All New Design - Frequency Stability Superior to anything offered today -No free-running Oscillators!

- SSB . . . CW . . . AM.
- Frequency coverage: Amateur bands 80 thru 10 and most MARS frequencies.
- Sideband Attenuation better than 50 db.
- Carrier Suppression . . . 50 db or better.
- Distortion products down by 40 db.
- Power Input: CW 180 Watts . . . SSB 140 Watts PEP.

The (BW) 6100 is a NEW transmitter with NEW features — Establishing a NEW standard of performance.

BARKER & WILLIAMSON, Inc.

Radio Communications Equipment Since 1932

BRISTOL, PENNSYLVANIA • STILLWELL 8-5581



Grounded Grid Linear Amplifier

This smartly-styled full kilowatt package of power takes up no more table space than a receiver. Can be driven by commercial and home-built exciters in the 100-watt output class. Includes R.F. section complete with tubes, blower, filament and bias supply and optional input matching unit. Pinetwork output circuit for precise tuning and loading on 80-40-20-15-10 meters.

POWER SUPPLY UNIT LPS-1 — Designed as companion to the LPA-1 for side-by-side installation or remote location. Switching panel removable for remote control. Full wave single-phase bridge rectifier with four Type 816 mercury vapor tubes included. R.F. filtering. Heavy-duty transformer core stacks and superior high-voltage insulation for reliable, continuous operation at 1 KW.

COAXIAL TYPE SWITCHES



These switches are used for switching 52 or 75 ohm coaxial lines. By the twist of a knob test instruments, antennas, transmitters, receivers and many other devices may be switched in or out of a coax line circuit. SO-239 connectors are provided on Models 550A and 551A. Rating is 1 kW amplitude modulated. Frequency range to 50Mc. Cross talk is

and 551A. Rating is 1KW amplitude modulated. Frequency range to 50Mc. Cross talk is .45db and .60db between alternate outlets at 30Mc. Size 4" overall x 2¼" depth. One inch shaft length. Shipping weight 2 lbs. Other models are available to order, including single and multiple gang units available to "N" and "phono-type" connectors as specified.



BARKER & WILLIAMSON, Inc. BRISTOL. PENNSYLVANIA

TR SWITCHES — FOR 52-72 OHM COAX LINE


A self-contained unit that provides automatic changeover of antenna from receiver to transmitter or visa versa, with no signal loss. Ideal for break-in operation on CW and SSB or push to talk on AM phone. Model 381 has selectable bandswitching, providing high order of sensitivity and selectivity. Handles full legal limit of power on AM, CW and SSB. Model 380B is for medium power applications. Provides broadband circuitry to eliminate tuning and adjustment.



Model 381—Size 4½ x4"x5½" Model 380B—Size5"x3½"x3½" Shipping wt. 5 lbs.

TRANSISTORIZED POWER CONVERTERS AND INVERTERS

 Reliable solid state, shock resistant DC to DC and DC to AC power units. They operate from 12 volts DC utilizing power transistors as switching elements. Units eliminate vibrators and rotating components, providing higher efficiency in a smaller package. They are ideal for all types of mobile equipment where high voltage DC from a 12 volt DC power source is required.





PI-NETWORK INDUCTORS

Ultra-compact highly efficient and intergrally bandswitched, these pi-network inductor assemblies incorporate novel design features. They are designed for single or parallel tube operation from 80 through 10 meters. Windings provide ample current carrying capacity. Maximum "Q" over the entire operating range. Model 851 for 500 watt finals



FILAMENT CHOKES Grounded Grid Amplifier



Broadband characteristics from 80 through 10 meters inclusive, requiring no tuning. Used with standard types of filament transformers. Cased in sturdy steel shells with mounting brackets. Two types available.

Model No. FC-15: for use with one or two tubes requiring a total of not more than 15 amps filament current. Dimensions: 1½" x 1½" x 4½".

Model No. FC-30: for one or two tubes requiring a total of not more than 30 amps filament current. Dimensions: 2" x 2½" x 5".

600 GRID DIP METER



A highly sensitive, accurately calibrated instrument which can be used as an RF Signal Monitor, Auxiliary Signal Generator, and Absorbtion Wave-meter. The wedge shape makes it easy to handle.

Plug-in coils are protected by colored vinyl plastic sleeves. Sensitivity control permits adjustment for distinctive dips throughout entire 1.75 to 260 mc range. Overall size 3" x 3" x 7" Wt. approx. 2 lbs. Operates from 105-125 v-ac 50-60 cycles.

AUDIO PHASE SHIFT NETWORK



These components are for use in SSB suppressed carrier radio-telephone applications. No larger than a 615 tube, the model 350 consists of an octal base that fits into a standard an octal table from the first into scandard octal tube socket. It is designed to split any audio signal, from 300 to 3,000 CPS, into two equal amptitude components which are $90^{\circ}\pm1.5^{\circ}$ out of phase with respect to each other. Model 350 Type 2Q4

CYCLOMETER TYPE COUNTER




For units that must be rotated in excess of 360° and reset to the same point. Available for 10 or 100 turns to within one-tenth of a turn. Front plate is 3" x 3". Depth from front of panel is 111/6". Either type available with a positive stop to limit the number of shaft rotations and a positive shaft lock. Price is determined by the shaft lock. Price is determined by the application. Standard finish is black crackle. Other finishes on special

10 Turn Cyclometer-Model No. 3901 100 Turn Cyclometer-Model No. 3902 Numbers decrease with clockwise rotation

Model No. 3902-1 Numbers increase with clockwise rotation.

MODEL 725 BALUN

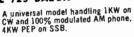



Frequency range 1.5 to 30Mc. For use with any antenna having a 300 ohm feed point. VSWR better than 1.5:1 over entire range. Negligible insertion loss. Coaxial imput fittings, ceramic feed through output. Weather-proof steel case size 3%" x 4%" x 47/16". Shipping weight 2½ pounds.

LOW PASS FILTERS



1KW rating. Will reduce serious and unwanted radiation to a minimum of 40 throughout the TV band and in excess of 100 db on channel "2". No tuning or adjustment required. The waveguide principle, employed in design of these units, permits a novel multi-section construction and accombly for greater attenuation in assembly for greater attenuation in less space, at a lower cost. Units are equipped with SO 239 connector fittings.

Model 425 for 52 ohm coax lines Model 426 for 75 ohm coax lines Size 11" x 2" x 3"

COAX ANTENNA CONNECTORS



Model CC50

These connectors provide a weather Inese connectors provide a weather proof, mechanically strong connection between a coaxial feed line and the center of a dipole antenna. It an aluminum housing, rust proof eye-bolts and steatite insulaproof eye-bolts and steatite insulation. Provision is made for internal soldered connections. Unit is furnished with rubber bushing for usith small coax cables and includes cement and instructions for installations. Size of both units 6½" x 5½" x 1½". Shipping weight 2 lbs.

Model CC51 (Military Type)

RF PLATE CHOKE MODEL 800



This unit is ideal for parallel or series fed high power final amplifier circuits. It is used for operation in the amateur bands—80 through 10 meters inclusive. Winding is on a high quality grooved steatite form, threaded on both ends, for mounting with a ¼"—#20 screw. Rating is 2500 VDC at 500 Ma. Size 6" x ½" in diameter. Shipping weight 1 lb.

BALUNS - BIFILAR COIL TYPE



Baluns are impedance matching devices which function to transform a 75 ohm unbalanced RF power source to either a 300 or 75 ohm balance load or visa versa. They are used to feed and match single or folded dipoles, or beam antennas, fed with coax lines. B&W baluns will handle 250 watts AM phone. 500 watt CW and IKW on SSB. Type 3976 kit (illustrated) consists of two Type 3975 coils and a compact 3977 mounting bracket with connector fittings. Baluns are impedance matching de-

MATCHING UNITS MODELS LPA-MU AND LPA-MU-2



A compact pretuned bandswitching turret assembly for correcting mis-match between a fixed driver-exciter unit and the broadbanded input circuitry of the LPA-1. Recom-mended for driver-exciter units whose output impedance is fixed to whose output impedance is fixed to a single value, and for cases of marginal output inadequate to drive the LPA-1 to a full KW on all bands. Model LPA-MU fits the LPA-I tinear Amplifier and is coupled with the Pi-Network final tank circuit. Model LPA-MU-2 is similar to the IPA-MII but is designed for Rayker.

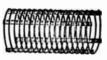
Model LPA-MU-Z is similar to the LPA-MU, but is designed for Barker & Williamson's previous Models L-1000-A and L-1001-A Grounded Grid Linear Amplifiers.














All types from 25W thru 1000W

BARKER & WILLIAMSON, Inc. • BRISTOL, PA.

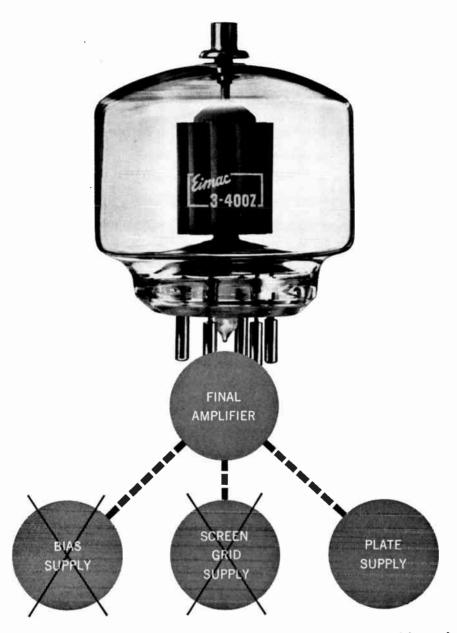

Cross off two power supplies with one of Eimac's new zero-bias triodes!

Another major advance from Eimac: the first high power zero-bias triodes anywhere. Just one of these new tubes will eliminate both screen grid and bias power supplies to simplify your circuit designs. Take your pick of three types: the 3-400Z, shown above, (plate dissipation: 400 watts)...the 3-1000Z (1000 watt plate dissipation)...the ceramic-metal 3CX10,000A7 (10,000 watt plate dissipation). Each offers a power gain of over twenty times in grounded grid service. And their small size accommodates today's lower, more compact equipment. You'll find these zero-bias triodes ideal for class B RF and audio amplifiers. And you'll find them only at Eimac...world leader in transmitting tubes. For ratings, specifications,

other details, write: Power Tube Marketing, Eitel-McCullough, Inc., San Carlos, California.





Leading Manufacturer of

TRIBANDERS

NEW DUOBANDER

Both 20 and 40 meter band operation is made possible through a unique Hy-Gain development — the linear decoupling stub, eliminating the use of inductance and capacity traps and decreasing the 40 meter element length by 35%. Beta match for maximum gain and low SWR into a single 52 ohm coax feed. 5kW, PEP; 3KW AM. Boom 24 ft. longest element 40 ft. All aluminum with hardware iridite treated. Model DB-24, 519.50.

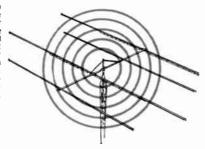


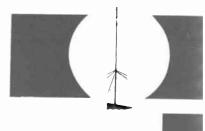


VHF BEAMS

NEW 6 & 2M DUOBANDER

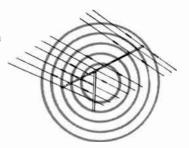A single transmission line system for 6 & 2 meter operation. 52 ohms coax fed, with forward gain of 8.0 db on 6M. 15.0 db on 2M. Fj. averages 15-20 db and SWR 1.5 to 1 or less. Rugged construction of 11/4" OD aluminum boom, 7/16" OD elements. Boom 10 ft., longest element 10 ft. Model DB-62, \$32.95.




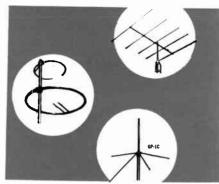

NEW DOUBLETS

Trapless Hy-Fan doublet takes unlimited power on 40 & 80 Meters, single feed line, 52 ohm coax fed. Copper clad steel stranded wire, cycolac center and end insulators. SWR less than 1.5:1 both bands. Length 130 ft. Model 2BDP, \$19.95.

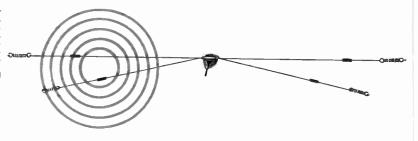New Trap Doublets supplied with solid state "Slim Line" traps for each band for maximum radiation efficiency, center & end insulators, nylon rope for extending lower element, and copper clad stranded steel wire. Take 500 watts AM, 1 kW PEP. Model 3BDT (10-20M), \$71.50 Model 4BDT (10-40M), \$24.50 Model 5BDT (10-80M), \$34.35




Hy-Gain Amateur Antenna Systems feature the finest commercial construction possible in line with practical beauty. New and efficient concepts improve performance; — the solid state "Slim Traps", the Hy-Gain Beta Match, the Linear Loading Principle, the Capacity Hat and others.

A complete line of accessories is also avail-

able for the listed systems;— stacking and mounting kits, add-on kits for the Verticals, a telescoping mast for the Halos, and more. For the complete story on the entire Hy-Gain line, ask your local ham dealer — there are more than 500 throughout the world — or write directly to Hy-Gain.

We invite you to compare any Hy-Gain an-


Amateur Communication Antenna Systems

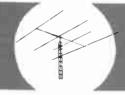

2-Element Thunderbird.	Boom 6 ft., longest element 26 ft.
Model TH-2	\$ 69.95
3-Element Thunderbird.	Boom 14 ft., longest element 26 ft. \$ 99.75
4-Element Thunderbird.	Boom 16 ft., longest element 32 ft.

10-20M Trap Vertical, self-supporting 13.5 ft. high.	
Model 12AVS	\$ 21.95
10-40M Trap Vertical, self-supporting 21 ft. high	
Model 14AVS	\$ 29.95
Hy-Tower, a trapless vertical for 10-80M, 50 ft. overall.	
Model 18HT	£120 50

VERTICALS

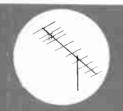


2 Meter, 5 Elements. Beta Match, 9.0 db gain. Model 25
2 Meter, 10 Element. 12 ft. Boom. 13.4 db gain.
Model 210\$14.95
11/4 Meter, 11 Elements. Folded ratio dipole.
14.2 db gain. Model 111\$13.95
3/4 Meter, 13 Elements. 8 ft. Boom. 16.1 db gain.
Model 313\$12.95

6 METER BEAMS HALOS

GROUND PLANES

MONOBANDERS

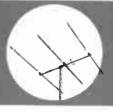

40 Meter, 2-Element "Hy-Seven". Model 402B	\$99.75
20 Meter, full sized. 8 db gain. Model 203B	\$6 5.95
15 Meter, 8 db gain. 25 db F/B. Model 153B	\$38.50
10 Meter, 8 db gain. 25 db F/B. Model 103B	\$32.95

ROTO-BRAKE

Rotator, Brake, Control Unit, 16" Wall Map Indicator, Model RBX-1\$199.95

tenna with any similar competitive system . . . for gain, for construction excellence, for price . . . and for operation, before you choose.


Hy-Gain Antenna Products also manufactures complete lines antenna systems for Citizens Band, FM, the Commercial fields and other special categories.



antenna products

1135 No. 22nd St. Lincoln, Nebr.

World Radio History

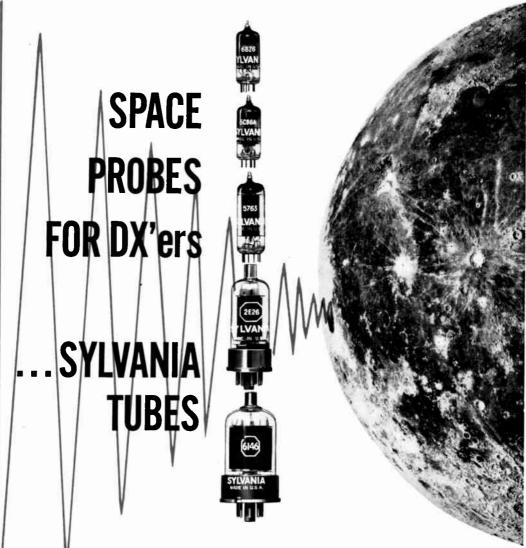


Tuning, scanning, monitoring, searching, probing for that one signal: a new zone, state or country. That demands dependable sigs from the xmtr, high sensitivity with maximum signal-to-noise at the revr.

Take a tip from professional "space probers." Industrial, military, broadcast, and aviation communications men have been relying on SYLVANIA POWER TUBES and SYLVANIA RECEIVER TUBES for years for solid copy. They get them from their local franchised SYLVANIA INDUSTRIAL TUBE DISTRIBUTOR. You get them, too, today.

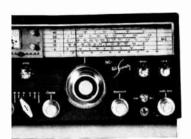Electronic Tubes Division, Sylvania Electric Products Inc., 1740 Broadway, N.Y. 19, N.Y.











2

3

NATIONAL RADIO COMPANY, INC.

TO: All Handbook Readers

Since we have a new catalog on the press this page shows only three of National's receivers. Send for a free copy if you'd like full details on our complete line, including the famous NC-400, the brand new NC-105 and the popular NC-303. Address your letter or postcard to National Radio Co., Dept. RH, Melrose 76, Mass. We'll rush you one of the first copies off the press.

'ATIONAL'S TRIO OF PACE-SETTERS

e are the three new receivers that are already setting the pace for the industry—Each offering more solid performance in its price area than you will believe . . . until you tune one. We invite to try all three—then select the one that best suits your requirements.

Precision double-conversion 80 through 6 meter amateur receiver featuring rock-like stability and unchallenged VHF performance. Five degrees of variable IF selectivity, including selectable SSB with product detector, 1.0 uv sensitivity, 60 db deep T-notch filter, built-in 100 KC calibrator, crystal-controlled 2nd converter. More features than any other receiver in its price range. \$279.95 am. net.

The 540 KC—30 MC general coverage receiver that tunes like a ham-band-only unit. 1.0 microvolt sensitivity, double conversion with five main tuning ranges, 5.0 KC, 3.0 KC, and 600 cycle variable IF selectivity, full SSB/CW AGC and product detector, 60:1 bandspread vernier drive and National's exclusive dial selector, providing instant choice of calibrated amateur or foreign broadcast bands. \$219.95 am. net.

NC-155...
National's newest—A double conversion 80 through 6 meter ham-band-only receiver offering superb performance completely out of proportion with its price. With its basic design derived from the famous NC-270, the NC-155 features 5.0 KC, 3.0 KC and 600 cycle variable IF selectivity, full SSB/CW AGC and product detector, and a velvet 60:1 dial drive that makes SSB signals as easy to tune as AM. 1.0 microvolt sensitivity on 6 meters, too! \$199.95 am. net.



The complete line of Gonset Amateur Equipment offers superlative performance at moderate cost

COMMUNICATOR IV-2 METER TRANSCEIVER



Completely new — inside and outl transmitter power greater than ever at 24 watts input. High level speech clipping and 10 watts of audio insure full talk power! Transmitter is crystal controlled, offers choice of six frequencies. Broadbond circuitry in driver eliminates panel controls.

Receiver uses latest frame grid VHF tubes in RF and mixer for low noise figure of 4-6 db, triple conversion with crystal controlled first conversion . . excellent sensitivity, selectivity. Also outomatic noise limiter, adjustable squetch, "S" meter, slide rule-type dial, panel speaker. Built-in power supply operates an both 115V AC and 12V DC. DC supply is transistorized, eliminotes vibrator. Power cobles are supplied for shift from AC to DC. Size: 5" H, 12½" W, 11" D. Weight, 21.8 pounds.

DC operation is with negative ground only.

Less Micraphone Madel #3341 Amateur Net.....369.50

COMMUNICATOR IV-6 METER TRANSCEIVER

Cammunicator IV for 6 meters is the some size and general appearance as the 2 meter madel. Tunoble receiver covers 49.9 to 54.1 with the 50-51 mc range spread aver ane third of the dial range. Receiver is triple conversion type, has sensitivity of 1.0 μ v for 10 db (S+N)/N or better. Noise figure is 6-8 db.

Transmitter operates at power input of 24 watts, has six crystal control positions with socket for external VFO.

Crystals are in the $8.333\ \text{to}\ 9\ \text{mc}$ range. Equipment has pushta-talk pravisions.

2-way power supply, 12V DC and 115V AC is built in. DC supply is transistorized, aperates negative graund only.

Less Microphone Madel #3342 Amateur Net.....349.50

COMMUNICATOR IV-11/4 METER TRANSCEIVER

The first commerically-produced "package" aperating on the amateur 220 megacycle band! Operates at an input power of 20 watts—substantial for VHF—incorparates an excellent superheteradyne receiver.

Triple canversian receiver is continuously tunable over the frequency ronge at 219.7 to 225.3 ms. To camply with OCDM requirements, additional pravision is made for spot frequency receptian on one crystal controlled frequency. Receiver sensitivity is 1.0 μv for 10 db (S+N)/N ratia. Noise figure is 6-8 db, exceptional far equipment af this general type. Adjustable squelch and ANL are included.

Transmitter is crystal controlled, offers choice of 6 frequencies. (Required crystols are within the range of 8.143 to 8.333 mcs.) Provision is mode for external VFO. Pawer input to PA is 20 watts, amplitude modulated by P-P 6BQ5's aperating in Class AB1. High level speech clipping and audio shaping are incarporated.

Unit is identical in size and general appearance to the Communicator IV 2 meter model. 2-way power supply for 115V AC and 12V DC (negative ground) is built in.

Less Microphone Madel #3351 Amateur Net..... 394.50



VFO FOR 6, 2 AND 11/4 METER COMMUNICATORS

New VFO is designed for use with all Ganset Communicators including Models I, II, III and IV. Dial scale is calibrated for 50,144 and 220 megacycle bands. Microphone connector with FM modulator is provided to allaw VFO to be used for Narraw Band FM. Excellent stability.

Model #3357 Amateur Net......69.50



GSB-201 SSB RF LINEAR AMPLIFIER

This entirely new linear amplifier is exceptionally compoct—is only 8½" high, 12½" wide and 17" deep—lends itself readily to table-top mounting. It is finished in blending light colors, presents o handsome clean-cut appearance.


The linear omplifier covers 80, 40, 20, 15 and 10 meter omoteur bands, incorporates full bandswitching, hos pin netwark-output. Power input roting is 1500 wats PEP SSB, 1000 wats CW, 400 watts AM. This amplifier can be driven by exciters in the 65-150 wat category, GSB-100 and similar units. Stable, grounded-grid circuitry is used.

GSB-201 incorporates a number of desirable operating features which include the use of low cost Type 811A tubes. Older type vacuum tube rectifiers are replaced by madern, long-life silicon types in the high voltage supply. Antenna changeover relay is built-in. A panel switch permits preliminary tuning to be done at low pawer. A full vision ponel instrument is switchoble to indicote plate current ar relative power output.

Amateur Net.

..399.50

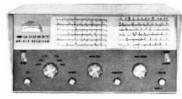*PEP input is approximately twice average d.c. input.



GR-212 DUAL CONVERSION RECEIVER

Dual conversion for increase selectivity. Variable BFO. Sensitivity: At least 6 db (5+N)/N at 1 $\mu\nu$ (mod. 30% at 400 cps) input on all H.F. Bands. Two full-vision, illuminated, slide-rule type dials provide instant identification of broadcast and shortwave frequencies. Panel-mounted "S" meter. Band-spread tuning knab is inertia fly-wheel weighted for smoothest tuning. Separate bond-spread dial for amoteur bands. Far 115V AC apperation.

Amateur Net 99,50

GR-211 ALL BAND RECEIVER

Similar in appearance to the GR-212. General coverage from standard broadcast through 34 mc band, including WWV, foreign & Voice of America. Printed circuit techniques and advanced design for extra sensitivity, better, quieter reception, even an highest frequency bands. 5 tubes, twa solid state rectifiers. TRANSFORMER-POWERED (not ac/dc) for higher aver-all goin, better signal-to-noise ratia. Circuit features leading to higher sensitivity include quality, high-Q, permeability-tuned cails. Two full-visian, illuminated, slide-rule type dials provide instant identification of broadcast and short-wave frequencies. Vernier tuning knob counter-weighted for smooth, non-critical short-wave tuning. For 115V AC operation.

Amateur Net......69.50



SUPER 12 SIX-BAND CONVERTER

Super 12 provides coverage of 6 amateur bands: 10, 15-20, 40 and 75 meters plus 19 and 49 meters far coverage of international shortwave broadcasts. Calibrated dial scale uses various colors to aid in identification of bands. Planetary drive provides vernier tuning.

Sensitivity and stability are excellent. Antenna trimmer on ponel maximizes antenna in use. 8C-HF switch permits instant return to standard BC. Super-12 is attractive... blends well with instrument ponel of modern cors. Campact size facilitates mounting. Highest quality components and precision workmanship ensure long, trouble-free operation. Installation is simple, non-technical—no alteration or internal connections to existing broadcast receiver. Converter simply patches into antenna input connector af cor radio...ottaches to 12 volt occessory post under dosh. Install in minutes with ease.

12 valts DC neg, ground only.



G-76 ALL BAND TRANSCEIVER FOR FIXED OR MOBILE SERVICE

G-76, on entirely new unit consisting of tronsmitter and receiver in a single compact housing. Provides AM or CW operation on 80, 40, 20, 15, 10 and 6 meter amoteur bands. The G-76 incorporates proved design features of the famed Ganset G-66/G-77 "Twin sparklers," adds many new advances for top fixed station and mabile operation.

Receiver is duol-conversion with 1st 1-F at 2065 kcs, 2nd 1-F at 262 kcs. Features include BFO for SSB and CW reception—outsomatic noise limiter. Unit has excellent selectivity and sensitivity. Transmitter and receiver oscillators are temperature compensated. Transmitter has stable VFO for all bands except 50 mcs which is crystal control only. Crystal control of other bands is optional. Power input to transmitter is 100 watts AM, phane, 120 watts, CW. Final tube is 60QS operating into pi network output. Control is push-to-tolk or by T-R switch on panel. Meter facilitates tuning, acts as "S" meter on receive. Dimensions: 12½" W, 5" H and 10½" deep. Unit has internal sacket for crystal calibrator (aptional) also ponel switch for colibrator apperation.

AC and DC power supplies ore available as accessory items at 145.00.

Amateur Net......399.50

G-50 6 METER FIXED STATION COMMUNICATOR



G-50 is a complete station "package" for 6 meter aperation. Receiver is highly sensitive, selective superhet with "S" meter, ANL, adjustable squelch, ponel mounted speaker. Transmitter uses 6146 in pi network final at 40-50 walts input. Frequency control is by crystol or built-in highly stable

VFO. Latter gangs with multiplying stages, eliminates excitation controls. Dial is calibrated 50-54 mcs. Modulatar uses two 616GB's. Campact housing, 7½," H, 13" W, 12½," D contains receiver, transmitter, pawer supply. For 115V AC operation.

Amateur Net......319.50

CD MODEL. Similar in general appearance to standard amateur model but is certified as meeting applicable specifications under OCDM U-68. Cabinet is same size as amateur model, has appropriate CD markings. Mic. and crystal certificate included.

Model #3300-CD Amoteur Net 349.50

NOISE CLIPPER



Designed for use with either mabile or fixed receivers that utilize the more common types of second detector. Reduces such interference as ignition noise, certain types of power leaks, and other forms of "Pulse" type noise having a low repetition rate and short pulse length. Utilizes a miniature diode in a form of series gate. Easy to install. Complete instructions furnished.

Model #3001 Amateur Net.....11.95

MONITONE



For use as a code proctice oscillatar and as on effective manitor for phane and CW xmtrs. Has audio ascillatar controlled by external circuits, provides audible tone on panel speaker ar earphones. Separate pitch and volume controls. Uses RF pickup

from xmtr. for operation as effective CW or phone monitor.

Operates from 115 VAC with isolating circuitry so that neither keying nor earphone leads are "hot" ta ground.

Model #3022 Amateur Net.....29.50



GC-105 "GOONEY BIRD" COMMUNICATOR

Silican diodes to sove current drain...colibrated tunoble receiver utilizes low-noise 6828 RF tube sensitive in "Coscode" circuit. AVC is opplied to avoid possibility of blacking by strong local signals. Special gong-tuned circuits give high image rejection. Dual purpose meter automatically switches from relative signal strength to relative output. Increased modulation copobilities with high level clipping. All tunoble circuits controlled from front ponel. Tune-up procedure simplified by use of broad-bonded exciter stages. Completely compotible with Ganset's new model 3357 VFO or 6 crystal positions available. Input: 6/12 DC or 115 AC volt operation, power cables supplied. Output: 6 wotts nominal. Dimensions: 6½, high, 15½ wide, 8" deep.

Amoteur Net......239.50


For further information on Gonset products see your nearest Gonset Distributor or write to —




DIVISION OF YOUNG SPRING & WIRE CORPORATION

801 SOUTH MAIN STREET, BURBANK, CALIFORNIA

The Least Expensive Way to Increase

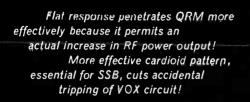

MODEL 664

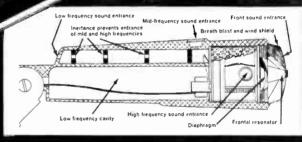

HERE'S HOW IT WORKS

Exclusive E-V Variable-D* (Variable Distance) provides three sound-cancelling entrances at different fixed distances in back of the diaphragm. These entrances, utilizing the proper acoustical impedances, combine to form an effective front-to-back spacing which varies in distance from the diaphragm inversely with frequency. The resulting phase and amplitude conditions provide a uniformly true cardioid pattern at all frequencies.

Here's What the Top Radio Amateur Operators in the World Say About These E-V Microphones:

CX2CO "My new 664 resulted in better and more consistent QSO's."

W8KML "The 664 surpasses its claims in difficult operational environments."

ZL1HY "During QSO's ... everyone preferred the 951."

W3JNN "I am really sold on the 664."

W8BF "I have had many unsolicited compliments since using the 729."

VQ4ERR "The performance of the 664 matches its thoroughbred appearance."

PY2CK "My 664 microphone vastly Improved my SSB transmission."



Average Peak-Power and Intelligibility!

CHOOSE AN Electro Voice MICROPHONE

Model 664 for Highest Front-to-Back Discrimination Manufactured, Plus Peak-Free Wide-Range Response!

The effective strength of all sounds arriving at the sides of the 664 are reduced by as much as 50%, and arriving directly at the back of the microphone by as much as 90%. This uniquely effective design permits you to work at twice the distance from the microphone . . . a perfect invitation for "arm chair" QSO's—with no VOX tripping problems.

Smooth, peak-free response guarantees maximum P.E.P. Remember, a peak in response in or *out* of the voice range will limit maximum modulation and result in reduction of P.E.P. You do not have to talk with your lips on the mike. For best results, sit back and talk naturally.

Virtually indestructible Acoustalloy® diaphragm withstands high humidity, temperature extremes, corrosive effects of salt air and severe mechanical shock. Extra ruggedness means extra service, year after year.

MORE 664 FEATURES: Output—55 db. On-off switch (can be wired for relay control). 150 ohms or Hi-Z output selected at cable connector. Satin chromium finish. High-pressure die-cast case. Pop-proof filter plus magnetic shield. 90° swivel mounting. 18 ft. cable. 7 16 in. long (less stand coupler) by 11/2 in. diameter. Net Weight 1 lb., 10 oz. Amateur Net, \$51.00. Matching desk stand with DPDT switch. Model 419S, \$9.00. Less switch. Model 419, \$6.00.

The World's Finest Mobile Microphone. Model 600D Dynamic Widely Known As Military Types T-50 And M-105/UI

Designed for high articulation under rugged mobile conditions, the Model 600D provides all the advantages of a dynamic element with peak-free, flat response for maximum P.E.P.

High-impact case soaks up physical abuse, feels comfortable at any temperature, fits hand naturally. Extremely high output of -55 db. is ideal for mobile equipment with severe audio requirements. Available in 50, 250 ohms or Hi-Z. DPDT switch. 6 ft. coiled cord. Panel mounting bracket included. Model 600D Amateur net, \$28.50.



MODEL 729SR

Lowest-Cost Ceramic Cardioid Available ...Includes Every Feature Essential For SSB Operation. Flat, Smooth Response From 300 To 3,000 CPS!

Rugged enough for mobile operation, the slim, small Model 729 fits easily in your hand or slips into the desk stand or floor stand adapter provided, without any hardware adjustments. Hi-Z output -60 db. Two-tone grey, pressure die-cast and plastic construction. Shielded, 8½ ft. cable. 7½ in. long by 1½ in. wide. Net weight 1 lb. Ceramic element unaffected by high heat, humidity. Model 729. Amateur net, \$14.70. Model 729SR with relay-control switch. Amateur net, \$15.90.



MODEL 951

First True Crystal Cardioid With Variable-D Design. Combines High Output With Excellent Noise Rejection At Modest Cost!

Finest crystal microphone available for SSB. Variable-D design of Model 951 cuts room noise, interference from receiver speaker to a minimum. Allows greater working distance to microphone. Peak-free rising response for high intelligibility. Hi-Z output-60 db. High-pressure, die-cast finished in Metalustre grey. On-off switch. Shielded, 18 ft. cable. 5½ in. long (less stand coupler) by 1½ in. diameter. Net weight 1½ lbs. Model 951 Amateur net, \$32.70. Matching desk stand with DPDT switch. Model 418S, \$9.00. Less switch. Model 418, \$6.00.

See your Electro-Voice distributor and choose an Electro-Voice Microphone . . . For the fastest, easiest and least expensive way to boost the efficiency and quality of your rig! Satisfaction is guaranteed or your money refunded!



ELECTRO-VOICE, INC., Commercial **Products** Division

Department 1212HB Buchanan, Michigan



HARVEY



AUTHORIZED DISTRIBUTORS



RCA Tubes and Harvey Service... For Double Dependability!

HARVEY's line of RCA tubes is so complete, that HARVEY can fill virtually any requirement . . . right from stock . . . and deliver at almost a moment's notice.

This is particularly important to AM, FM, and TV Broadcasters, Industrial and Commercial users, Amateurs, and Service-Technicians, all of whom depend on tubes for sustained operation of important electronic equipment.

Write, Wire or Phone for PROMPT HARVEY SERVICE

Visit Harvey's New Ham Radio Center. The latest and best in ham gear is always on display.




ARRL PUBLICATIONS




Storehouses of Information for:

- Novices
- Old Timers
- Students
- Engineers

Supplies for the Active Amateur

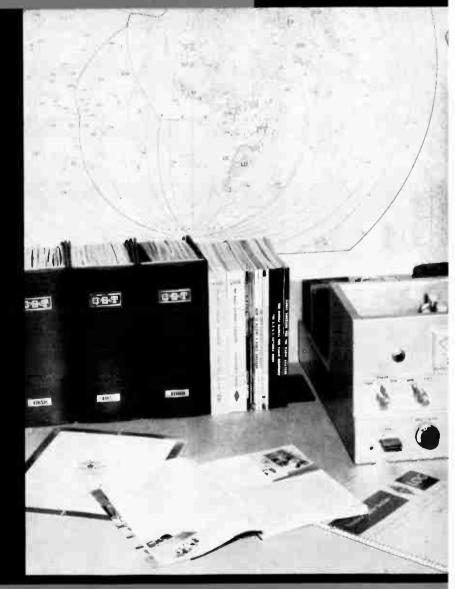

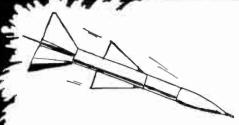THE AMERICAN RADIO RELAY LEAGUE . WEST HARTFORD 7, CONN.



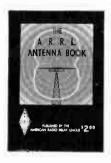
the BEST SELLER LIST FOR THE RADIO AMATEUR!























ARRL WORLD MAP

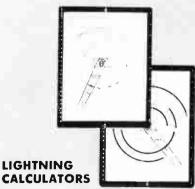Printed in eight colors on heavy map paper with 267 countries clearly outlined. Continental boundaries, time zones, amateur prefixes, plainly marked. Size: 30 x 40 inches. \$2.00.



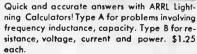



- ★ QST Although primarily a ham magazine, QST is found on the desks of engineers, technicians and just about everyone in the electronics field. There is something for everyone in QST, from the Novice to the Old Timer. QST and ARRL membership \$5.00 in U.S.A., \$5.25 in Canada, \$6.00 elsewhere.
- ★ THE RADIO AMATEUR'S HANDBOOK Internationally recognized, universally consulted. Packed with information essential to the amateur and professional alike. Hundreds of photos, diagrams, charts and tables. \$3.50 U.S.A., \$4.00 U.S. Poss. and Canada, \$5.00 elsewhere; Clothbound Edition, \$6.00 in U.S.A. and Possessions and Canada, \$6.50 elsewhere.
- ★ A COURSE IN RADIO FUNDAMENTALS A complete course of study for use with the Radio Amateur's Handbook. Applicable to individual home study or class use. \$1 U.S.A. proper, \$1.25 elsewhere.
- ★ HOW TO BECOME A RADIO AMATEUR Tells what amateur radio is and how to get started in this fascinating hobby. Emphasis is given to the needs of the Novice licensee, with three complete simple amateur stations featured. 50 ć.
- ★ THE RADIO AMATEUR'S LICENSE MANUAL Complete with typical questions and answers to all of the FCC amateur exams—Novice, Technician, General and Extra Class. Continually kept up to date. 50 c
- ★ LEARNING THE RADIOTELEGRAPH CODE For those who find it difficult to master the code. Designed to help the beginner. Contains practice material for home study and classroom use. 50 c.
- ★ THE ARRL ANTENNA BOOK Profusely illustrated, the Antenna Book includes information on theory and operation of antennas for all amateur bands; simple doublets, multi-element arrays, rotaries, long wires, rhombics, mobile whips, etc. \$2.00 U.S.A. proper, \$2.25 elsewhere.
- ★ SINGLE SIDEBAND FOR THE RADIO AMATEUR A digest of the best SSB articles from QST. Includes discussions of theory and practical "how-to-build-it" descriptions of equipment. \$1.50 U.S.A. proper, \$1.75 elsewhere.
- ★THE MOBILE MANUAL FOR RADIO AMATEURS It's a collection of articles on tried and tested equipment that have appeared in QST. A "must" for the bookshelf of anyone interested in the installation, maintenance and operation of mobile stations. \$2.50 U.S.A. proper, \$3.00 elsewhere.
- ★HINTS AND KINKS If you build equipment and operate an amateur radio station, you'll find this a mighty valuable book in your shack and workshop. More than 300 practical ideas. \$1 U.S.A. proper, \$1.25 elsewhere.



QST BINDERS

No need to let your copies of QST rest in a disordered pile. A QST binder will keep them neat and orderly, Each holds a one-year file. \$3.00 (avoiloble in U.S. and Possessions only).



SUPPLIES

Active amoteurs need these supplies: ARRL Logbook, 50¢ U.S.A., 60¢ elsewhere. Minilog, 30¢ U.S.A., 35¢ elsewhere. Rodiogrom blanks, 35¢ per pad postpaid. Message delivery cords, 5¢ each stamped, 2¢ eoch unstamped, Members' stotionery, 100 sheets \$1.00; 250 sheets \$2.00; 500 sheets \$3.00.



Application for Membership



AMERICAN RADIO RELAY LEAGUE

Administrative neadquarters: West Hartford, Connecticut, U. S. A.
19
American Radio Relay League, West Hartford 7, Conn., U.S.A.
Being genuinely interested in Amateur Radio, I hereby apply for membership in the American Radio Relay League, and enclose \$5.00* in payment of one year's dues. \$2.50 of which is for a subscription to QST for the same period. [Subscription to QST alone cannot be entered for one year for \$2.50, since membership and subscription are inseparable.] Please begin my subscription with theissue.
The call of my station is
The class of my operator's license is
I belong to the following radio societies
Send my Certificate of Membership or Membership Card (Indicate which) to the address below:
Name

A bond fide interest in amateur radio is the only essential requirement, but full voting membership is granted only to licensed radio amateurs of the United States and Canada. Therefore, if you have a license, please be sure to indicate it above.

*\$5.00 in the United States and Possessions. \$5.25, U. S. funds, in Canada. \$6.00, U. S. funds, in all other countries. How Mosley can help choose the antenna for you


n amateur, commercial and military communications systems

How can you select an antenna that you know is right for you? You can know for sure if you investigate before you invest. Asking other hams or other engineers which antenna they have used or recommend is a very effective way to investigate the relative merits of any antenna or antenna system.


Hams who own one of the famous Mosley line of amateur antennas will tell you that they perform as well, or better, than advertised. But after you have talked with other hams, see your distributor. He will be glad to explain the relative merits of such famous Mosley antennas as those shown on the right.

Electronic engineers, too, who have used one of Mosley's new line of commercial antennas will agree that they are built to the same high standards of engineering, material and workmanship as the world famous Mosley amateur antennas.

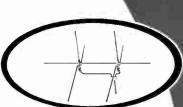
We will gladly supply the names of dozens of leading commercial, military and industrial organizations who have installed Mosley point-to-point antennas in standard configurations which are available "off the shelf" and "customized" antennas in HF and VHF ranges. Write our Government and Industrial Division for our new catalog" Antenna / Systems 1961 /62".



Bi-Directional Vertical Ground Plane

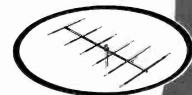

Yagi Six Element

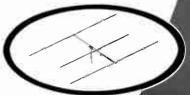


Model TA-20-40



Look for this black and yellow decal in the windows of nearly 250 amateur and industrial electronic equipment dealers. These signs Identify dealers who carry in stock the Mosley antenna for you.

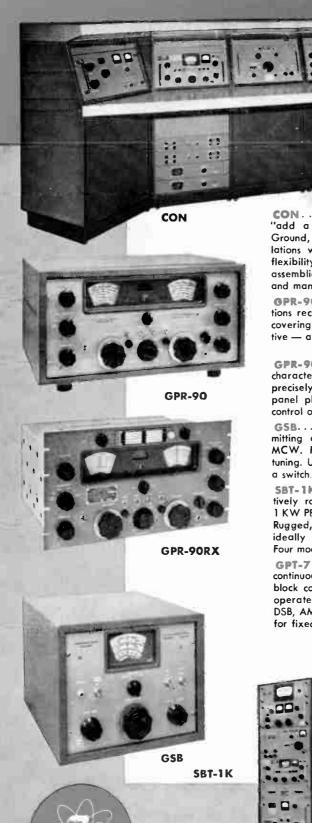4610 N. LINDBERGH BLVD. BRIDGETON, MISSOURI



GPR-90 (R-825 /URR) . . . a general purpose communications receiver of the double conversion superheterodyne type covering the frequency range of .54 to 31 mcs. Stable — selective — accurate — built-in crystal calibrator.

Bulletin (179) 3005

SSB

• DSE

GPT-750 () 2(AN/URT-17A) . . . is a fully bandswitched, continuously tunable (2-32MC) radio transmitter. The building block concept makes this transmitter versatile, easy to install, operate and maintain. Nineteen models available. SSB, ISB, DSB, AM, CW, FAX, FS. The GPT-750 (.....)2 is ideally suited for fixed station, mobile and shipboard operation.

Bulletin 227 (1007)



GPT-750



HF/LF communications it's TMC

· ISB · CW · MCW · AM · FS

VOX (0-330B/FR)... a direct reading, high stability, Variable Frequency Oscillator providing continuously variable output over the frequency range of 2—64 mcs.

Bulletin (134A) 2010

XFL-2 . . . The TMC Frequency Shift Exciter System, Model XFL-2 is combined low and high frequency shift system. The system combines the TMC Low Frequency Adapter, Model LFA with TMC Frequency Shift Exciter, Model XFK to provide versatile operation over a wide range of frequencies—1 to 6.9 mcs. and 50 to 500 Kcs. Bulletin (154) 2021

PTE-3 (AN/GRM-33A)... Single Sideband Analyzer designed for the specific purpose of tuning and aligning single sideband exciters and transmitters permitting a visual analysis of intermodulation distortion products, hum and noise The PTE-3 consists of 3 basic TMC units: Spectrum Analyzer Model FSA (AN/URM-116A); A VFO TMC Model VOX (0-330B/FR) and a Two-tone Generator TMC Model TTG (0-579A/URT).


Bulletin (231) 6001

GPT-10K (AN FRT-39) . . . is a conservatively rated general purpose radio transmitter capable of at least 10 KW PEP output from 2-28 mcs. All power amplifier stages are linear and the final incorporates a ceramic tube for greater efficiency and reliability. All components housed within a single attractive enclosure including sideband exciter — VFO, spectrum analyzer, F.S. Exciter and complete "on the air" testing circuitry.


Bulletin (207C) 1008



VOX

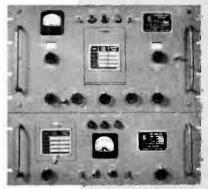

XFI-2

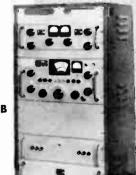


SBT-350 B

MAMARONECK, NEW YORK

The TECHNICAL MATERIEL CORP.

and Subsidiaries:

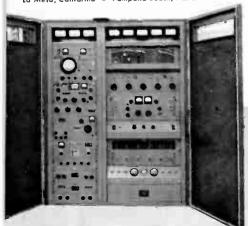Ottawa, Ontaria, Canada • Alexandria, Virginia • Garland, Texas La Mesa, Califarnia • Pampana Beach, Florida.



GPT-10K



PTE-3



SPECIALISTS IN PRECISION RADIO CRYSTALS AND QUALITY

ELECTRONIC EQUIPMENT

QUALITY ELECTRONIC **EQUIPMENT FROM** INTERNATIONAL



Single stage triode amplifier. Inductive neutralization. Available 26 mc through 160 mc

Kit	\$5.95
Wired and tested	\$9.95
Coupling section(each)	.95
Mounting Chassis(each)	\$2.00



CONVERTERS

TRC 4 Crystal controlled. Three transistors. RF stage. Available all amateur bands 6 through 80 meters.* 600-1600 kc IF or 6 mc IF for use with TRB-I....\$16.50 * See catalog for other frequencies.

Crystal controlled. Three transistors. Available for any 1 mc band of frequencies between 54 mc and 160 mc. 600-1600 kc IF or 6 mc IF for use with TRB-I.

54	mc	to	100	mc\$20.50
				mc\$20.50

FM-5000 **EREQUENCY** METER Beat frequency measuring device. Incorporates a transistor counter circuit, self contained batteries. low RF output for receiver checking, audio oscillator, trans-

mitter keying circuit, and plug-in oscilla-tors, including heating circuit. Frequency meter, including batteries, accessories and complete instruction manual. less oscillators and crystals....\$375.00

* * * * * * * * * * * * * * * * * * *	\$25.00	ea.
5 - 24	15.00	ea.
25 to 99	9.00	ea.
100 or more	8.25	
"less crystal Crystals for Oscillators 100 kc - 1999 kc	\$8.75	03
2000 kc - 60 mc	6.75	



TRANSMITTER UNIT (TRT-2) Three transistors. Crystal controlled. Switch for two frequencies. 10 meter range. Transmitter less transistors \$10.00

OSCILLATORS. Three separate transistor units with total of 8 frequency ranges (100 kc to 60 mc). TRO-1 100 kc and 200-2000 kc.

TRO-2 2000 - 20,000 kc. Overtone 15 mc to 60 mc in 5 ranges. Specify frequency (each) \$4.00



FO-1L 100 kc OSCILLATOR Printed circuit oscillator for band edge calibrator and frequency standard. Power: 150 vdc @ 8 ma, 6.3 vac @ 150 ma.

Kit, complete with tube and crystal Wired and Tested

\$15.95

FO-1A FO-1B OSCILLATORS FO-1A (fundamental operation) 200 kc to 15,000 kc. Tolerances of .01% and .005% with appro-Wired and tested (less tube and crystal) \$6.95

F0-11 CRYSTAL OSCILLATOR



VFA-1

CASE



COMPLETE LINE TRANSIS-TOR SUB-ASSEMBLIES FOR COMPACT RECEIVER/TRANS-MITTER CONSTRUCTION

CONVERTER (TRC-1) Three transistors, crystal controlled 6 mc IF standard. 10 meters. Wired and tested with crystal \$14.50

AUDIO UNIT (TRA-2) Three transistors. Input 100,000 ohms and 50 ohms. Speech input for dynamic microphone. Push-pull power amp. Wired and tested \$14.50

MIXER IF UNIT (TRB-1) Six transistors, 2 diodes. Crystal controlled

local oscillator. Noise limiter and squelch. 6 mc input. Wired and tested with 2 crystals \$32.50

sary for installation in vehicle......\$4.95

Transistor Kit \$ 9.00

CASCODE PRE-AMPLIFIER For 2 meters or 6 meters. Mounts in standard 3" x 4" x 5" minibox. Power 250 vdc @ 10 to 15 ma, 6.3 vac @ 400 ma. Tube 6BQ7A.

50 mc Kit with tube \$4.95 Wired with tube \$8.95 144 mc Kit with tube \$4.95 Wired with tube \$8.95

World Radio History

FOR DEPENDABILITY IN COMMUNICATIONS...SELECT INTERNATIONAL CRYSTALS

AMATEUR CRYSTALS

Types FA-5, FA-9, FM-9 1000 kc to 137 mc .01% Tolerance Wire mounted plated crystals for the Amateur or Experimenter where tolerance of .01% is permissible and wide range temperatures are not encountered.

Designed to operate into a load capacitance of 32 mmf on the fundamental between 1000 kc and 15 mc. Designed to operate anti-resonance on 3rd overtone modes into grid circuit without additional capacitance load. Fifth overtone crystals and seventh overtone crystals operate at series resonance.

HOLDERS: Metal hermetically sealed. FA-5 and FA-9 are HC/6U pin type. FM-9 is HC/18U pin type. CALIBRATION TOLERANCE: ± .01% of nominal at 30 C

TEMPERATURE RANGE: -40° to 70 C. ± .01% of frequency at 30°C. DRIVE LEVEL: Recommended, maximum 3 milliwatts for overtones; up

to 80 milliwatts for fundamentals, depending on frequency.

FREQUENCY RANGE: FA-5 and FA-9 1000 to 20,000 kc fundamental; 10 mc to 60 mc third overtone; 60 mc to 137 mc fifth and seventh overtone. FM-9 8000 kc to 20,000 kc fundamental; 20,000 kc to 60 mc third overtone; 60 mc to 110 mc fifth overtone; fifth overtone.

COMMERCIAL CRYSTALS 70 kc to 137 mc-Type F-6 Wire mounted, plated crystals for use in commercial equipment where close tolerances must be observed. All units are calibrated for specific load presented by equipment. Crystals are available for all major two-way equipment and in most cases the necessary correlation data is on file. Prices on request.

DESCRIPTION AND DATA. Low drift Al-cut blanks are used in these units above 500 kc, and low drift DT and CT-cut blanks are used in units below 500 kc; any crystal can be supplied for operation with or without an oven


TEMPERATURE TOLERANCE: +90 C. +002% from -30 to +60° C.

DT-CT= $\pm.01\%$ from -40° to $+70^{\circ}$ C.

CALIBRATION TOLERANCE:
AT ...0025% of nominal at +30° C.
DT-CT ...01% of nominal at +30° C. DRIVE LEVELS: Maximum, AT —

aximum, A1 — 10 millwatts 500 kc to 999 kc 4 milliwatts 10,000 kc to 24,000 kc 2 milliwatts 25 mc to 137 mc

DT-CT - 2 milliwatts

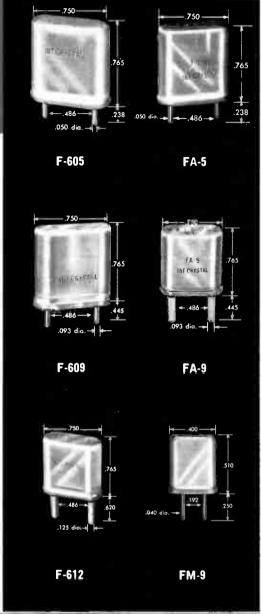



MODEL C-12 ALIGNMENT OSCILLATOR

Crystal controlled for generating standard signals in alignment of IF and RF circuits. Accommodates FX-1 crystals from 200 kc to 15,000 kc. Special oscillators for frequencies to 60 mc. Complete with power supply for 115 vac. Oscillator with case, cover and carrying handle (less crystals) crystals)



18 NORTH LEE - OKLA. CITY, OKLA.



CRYSTALS FOR USE IN MILITARY **EQUIPMENT CAN BE SUPPLIED TO MEET** SPECIFICATIONS OF MIL - C - 3098B.

SAVE UP TO 50%

ON THE NEWEST, FINEST AMATEUR RADIO GEAR WITH

HEATHKIT

New Kits

Forty new kits have joined the Heathkit line this fall...choose from over 250 quality kits...the world's most complete line!

New Guarantee

We guarantee you can build any Heathkit and have it perform to factory specifications . . . now you can buy in complete confidence!

New No-Money Down Terms

Now it's even easier to buy from Heath! Any order from \$25 to \$600 can be paid for on Heath's time-pay plan with no down payment!

New 1962 Heathkit Catalog

It's the world's biggest kit catalog ... 100 pages ... complete descriptions, specifications and many schematics. It's yours FREE!



Specially-designed for CW work ... new novice CW TRANSMITTER KIT HX-11

An excellent transmitter for the novice or CW amateur who appreciates a clean, quality signal and real distance getting power! Features 50 watt RF power input on 80 through 10 meters, built-in low pass filter, single-knob bandswitching, switched antenna relay power and pi-network output coupling for complete operating convenience. A "tune-operate" switch allows off-the-air tuning and a large "clear view" meter indicates final grid or plate current. Easy access to crystal socket is provided by a metal pull-out cabinet plug. Power supply is built-in. Careful design and high-quality components used throughout make this kit easy to assemble and assures long, reliable and trouble-free performance for years to come. An outstanding "watts-per-dollar" value in amateur gear. 17 lbs.

Kit HX-11... NO MONEY DOWN, \$5 mo.......\$43.50

The DX-60 Surpasses Quality and Performance of Transmitters Costing Far More!

This outstanding phone and cw transmitter offers far more in quality and performance than any other unit in its price and power class! A front panel switch selects any of four crystal positions or external VFO. Controlled carrier modulator and silicon diode power supply are built in. Single knob bandswitching for 80 through 10 meters and pi-network output coupling provide complete operating convenience. Panel meter shows final grid or plate current for easy tuning. Assembly is a marvel of simplicity with clean, rugged construction and thoughtful circuit layout. A precut, cabled wiring harness eliminates tedious wiring and the informative instructions furnished make it an ideal kit for the novice. May be run at reduced power for novice operation. Less crystals. 25 lbs.

Kit DX-60...NO MONEY DOWN, \$9 mo.......\$82.95





New low cost, broad coverage Heathkit VFO HG-10

Covers 80 through 2 meters with each band separately calibrated on a rotating drum-type slide-rule dial. Uses a series tuned Clapp oscillator with regulated plate voltage for stability and a cathodefollower output stage for load isolation. Features 28:1 vernier gear drive, and "spotting" switch for off-the-air tuning. Powered by transmitter. Styled like the Heathkit DX-60 and plugs into it directly. Easy to build. 12 lbs.


Kit HG-10...NO MONEY DOWN, \$5 mo........\$34.95



Improve your receiver performance with this new Heathkit "Q" MULTIPLIER

May be used with any receiver having an IF frequency between 450 and 460 kc. This "electronic filter," with effective "Q" of approximately 4,000, provides either a sharply-peaked IF curve for CW, a broad peaked IF curve for AM or SSB, or a deep sharp notch for rejecting heterodynes on CW, AM and SSB. Both peak or notch positions are tunable to any point in the receiver's IF bandpass. Ideal for CW reception and heterodyne rejection on receivers or transceivers employing fixed bandwidth mechanical filters such as the Collins 75S-1. Power supply is built-in. 2 lbs.


Kit HD-11...

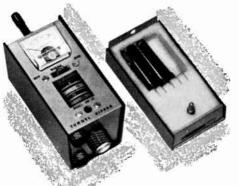

New! . . . nothing else like it anywhere the Heathkit "TUNNEL-DIPPER" ... exclusive tunnel-diode oscillator!

settings. 3 lbs.

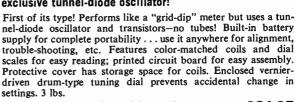Kit HM-10...NO MONEY DOWN, \$5 mo......\$34.95





Tree Catalog

Send For Your FREE 1962 Heathkit Catalog now! It details the complete Heathkit line of quality kits . . . over 250 . . . the world's largest selection. We'll send your friends free copies too!

	HEATHKIT®
EATH	COMPANY

Benton Harbor 9, Michigan

Please send the Free Heathkit catalog.

Name

Address__

____State_





STEP UP TO QUALITY...

RECEIVERS, TRANSMITTERS

In Stock RIGHT NOW at Your HAMMARLUND Distributor

Thrill to the stability and precision of professionally designed, carefully manufactured equipment for amateur use. Scan these pages, and you are sure to find the unit you want.



\$399.50 AMATEUR NET

NEW! HX-50

The first BIG STEP in transmitter history—Hammarlund quality-plus features that literally burst forth in this new, compact filter-type transmitter. Power input 130 watts, P.E.P. Two tone output...50 watts at 10 meters...75 watts or better at 80 meters. Features slide rule dial with band-in-use neon indication.



HQ 100A

Single Conversion

General coverage receiver with extra convenience and performance through independently controlled, continuously variable BFO and Q-Multiplier.

\$189 Amateur Net*



HQ 145X

Dual Conversion Above 10 MC

Pin-point accuracy with single-crystal controlled fixed frequency channel plus top-quality general coverage reception. \$269 Amateur Net

*24 hour clock-timer-\$10 optional

HAMMARLUND QUALITY...

AND ACCESSORIES



MR 30X **MR 50X**

True split channel crystal controlled monitor receiver. Factory tuned to any specific channel within the frequency limits of the instruments. Multiple channels available, MR 30X-25 to 54 MCS. MR 50X-147 to 174 MCS. \$199.50 Amateur Net



HQ 170

Optimum reception of SSB amateur bands. Triple conversion. Razor sharp slot filter with up to 60 db attenuation. The amateur band Specialist.

\$359 Amateur Net



HQ 180

Triple Conversion

The quality standard for the industry. The very finest general coverage receiver available. 18 tube superheterodyne unit for the best in SSB, AM and CW reception. \$429 Amateur Net



HO 110

For the amateur bands. Optimum selectivity. Dual conversion 12 tube superheterodyne. \$249 Amateur Net



HX 500

100 watt output of the best performance you ever heard. Advanced design SSB transmitter that offers every feature you want—and more. \$595 Amateur Net



HO 105TR

Citizen-Ham band transceiver that incorporates a full-coverage receiver. Now available with built-in speaker in place of 24 hour clock-timer. \$219.50*†

tHQ 105TRS (Built-in speaker) \$224.50



S-100 S-200 SPEAKERS

Matching speakers for use with HQ 100A, HQ 110, HQ 105TR and HQ 145X, HQ 170 and HQ 180 respectively. Extended coverage. S-100 \$14.95 S-200 \$19.95



NEW ELECTRONIC KEYER EK-1B

contained, battery operated unit with its own built-in speaker. Features ratio control which permits personal "touch" and a full range of speeds for novice or expert operation. \$39.95 Amateur Net

IMPROVED NOISE SILENCER

Complete, ready to install unit that suppresses impulse noise level in any loca-tion for HQ 170 and HQ 180 receivers. Eliminates ignition or other pulse-type noise that would otherwise obliterate \$33.50 Amateur Net

CRYSTAL CALIBRATOR-XC 100

New plug-in type—provides markers every 100 KCS. HQ 145X, HQ 170, and HQ 180 chassis factory prepared for XC-100 in-\$15.95 Amateur Net stallation.



MANUFACTURING COMPANY, INC., an affiliate of Telechrome

53 West 23rd Street, New York 10, N, Y.

LEO I. MEYERSON, WOCFQ, SAYS:

Now You Pay "NO MONEY DOW

WITH OUR NEW CHARG-A-PLAN CREDIT PROGRAM® (\$20.00 Min.)

- ADD-ON PURCHASES AS YOUR CREDIT GROWS
- SMALL MONTHLY PAYMENTS

WRL's New Comet Kits and

TC-6

Transmits ALL BAND VERTICAL ANTENNA KIT

80-10 Meters

Designed as a space and money saver.
. Ground or roof mounted, self - supmounted, self-sup-porting; handles up to I KW on 10-80M; band change by tap-ping clip. No guys; no radials; 23 feet overall. Heavy wall aluminum tubing. 52 ohm coax fed.

> NO MONEY **DOWN**

Only



Handsome, functional desk with sloping top, designed for Amateur or Experimenter use. Durable 3/4" Nova-Ply. Easily assembled in a few minutes without glue. Holds over 500 lbs. Handy, slide-out leaf. Wood-Mosaic finish. Full size: 49½x-29½x31". Shpg. wt.: 99 lbs. Shipped truck or expresse. truck or express.

FIXED OR MOBILE

6M Transceiver

Kit Only \$3995

New WRL TechCeiver-6 has superhet receiver, built-in noise limiter, is tunable 48-54 MC. Crystal controlled Xmttr. using std. Xtals. (FT 243-8MC). Over 1 watt output. Built-in push-to-talk. 9-tube performance. Smallest Transceiver available: 529/4x6".

Matching 115VAC supply, Kit \$15.95 Matching 12VDC supply, Kit \$24.95

SS-3



SIGNAL SLICER

Only \$1595

\$7.95

Boosts weak signals by narrow bandpass. For any 455 Kc Receiver IF, with no modification. Self-powered for 115VAC. Ultra high "Q" coils. Step-by-step instructions.

DUO-DOUBLETS NEW WRL

Dual band operation, single 52-ohm feed, copperweld wire. Weather proof insulators included. Usable on 15M. Full half wave, each band.

ALL COPPERWELD FOR STRENGTH

Model 84 (80 & 40 meters) Model 42 (40 & 20 meters)

MONEY DOWN

"ON-THE-A BOX

Easily installed, heavy gauge steel, grey fin-ish. 115 volts. Bulb included. Simply at-tach cord to terminals of 115V antenna relay.

LARGE UNIT (101/2x31/2x3")

\$495 \$2.49

SMALL UNIT (13/4x27/8x63/4")

erates with any Xmttr. of power input 100w CW, 75w Fone or less. Matches to high impedance anten-nas. Unbalanced input and output. High quality ma-terials & assembly manual.

New Mini-Matcher Kit op-

Antenna Tuner

\$1095 MM-100

NO MONEY DOWN

COLINEAR 6-METER VERTICAL

Self-supporting vertical, 13 ft. high. DX power gain from the ½ electrical wave vertical radiator. Uses ¼-wave radials. Clamps to std. masts up to 1½° O.D. 3 DB gain on 6M, 52 ohm coax fed ohm coax fed.

Only \$2995

LOW COST 6-M BEAM

Only \$1295

Light weight, spaced for Light weight, spaced for maximum gain (7 db). F/B 18 db. Rugged 4½ ft. boom. Aluminum. May be rotated with TV rotator. Can be shipped parcel post.

Regular 10% down payment plan still available to our customers!

Hallicrafter Equipment

From "the house the hams built" OFFICIAL HALLICRAFTERS WARRANTY SERVICE STATION



for Novice, Technician, General!

MODEL SX140

A high performance, low cost ham band receiver, 80-6 meters. AM/CW/SSB, BFO/Q multiplier, antenna trimmer, ANL, "S" Meter and many other features. Wired, \$124.95. Kit, \$89.95

MODEL HT40

Carefully designed AM/CW transmitter for 80-6 Meters, Crystal, or external VFO control (with HA5 VFO). 52 ohm pi output with TVI shielding. Dual range metering. Excellent CW keying. 75 watts maximum input power.



MODEL

HT32B

JUST \$72500

Amateur Net

A new table top, high efficiency amateur band transmitter, providing SSB/AM/CW/FSK output on 80-10 meters (full 10M coverage). A new dial calibrated directly to 1 KC. New sealed crystal filter for best performance. 144 watts input (PEP). Both sidebands on AM. 52 ohm pi output. Full VOX and break in CW.

Companions for the Most Discriminating Amateur Operation SSB / AM / CW / FSK

Complete ham band coverage 80-10 meters plus tuning range for external 2 and 6 meter converters. Dual conversion, SB selection, built-in calibrator. Every feature carefully designed to result in top performance on reception, be it AM/CW/SSB/FSK.

MODEL

SX101A

JUST

\$44500

Amateur Net



You Can Rely On HALLICRAFTERS For Superior Products!

BUY WRL USED GEAR WITH CONFIDENCE

2 WEEK TRIAL AFTER PURCHASE. We guarantee you must be satisfied with performance or you may return the equipment within 2 weeks for refund.

90 DAY PARTS WARRANTY. We guarantee your investment 90 days by our "Same as New" 90 day warranty on all parts.

BONUS FEATURE! Full 90 day return credit: WRL offers a 90 day return privilege whereby you can trade back equipment for full credit (subject to equipment not being damaged) on any of our NEW equipment of higher value. All shipping F.O.B. WRL.



50¢ each

Giant Wall Maps HAM OR CITIZENS BAND

Send for these Call Area maps for your Ham Shack today! 28x36", in multiple colors, showing various call areas for either Amateur Radio or Citizens Band, time zones, monitorizzettenen et leth pour avail. ing stations, etc. Both now available at 50c each.

			_		
			•	1	
١.	A	' A		4	
		_	_ A		

WORLD RADIO LABORATORIES

3415 WEST BROADWAY

COUNCIL BLUFFS, IOWA $^{\mathrm{H}\mathrm{B}}$ 62

LEO:	PLEASE	RUSH	ΜE	THE	FOLLOWING	COMET	KITS
			_				

HALLICRAFTERS GEAR:

SEND

LATEST FREE RECONDITIONED EQUIPMENT LISTS:

FREE FLYER NAME: CALL: .

ADDRESS: _ _ CITY & STATE:_ RHEOSTATS

when you specify Ohmite components..

you build reliability into your product

RESISTORS

OHMITE®

RELAYS

TAP SWITCHES

INDUSTRY-PREFERRED COMPONENTS

TANTALUM CAPACITORS

VARIABLE TRANSFORMERS

GERMANIUM DIODES



RHEOSTATS—Insure permanently smooth, close control. All-ceramic, vitreous-enameled: $12\frac{1}{2}$, 25, 50, 75, 100, 150, 225, 300, 500, 750, and 1000-watt sizes.

OHMITE RELAYS—Five stock models—DOS, DO, DOSY, CRU, new GR, in 235 different types, three of which are enclosed. At115 VAC or 32 VDC, noninductive load, Models DOS and DOSY have a contact rating at 15 amp; Model DO, 10 amp; Models GR and CRU, 5 amp. Wide range of coil operating voltages.

TANTALUM CAPACITORS—Units are available in three types: subminiature, insulated, wire-type, in 13 sizes. All 5 MIL sizes of foil-type. Four sizes of slug-type tantalum capacitors. All feature high performance in minimum space and a wide range of capacitance and voltage ratings.

Write for Stock Catalog

POWER RESISTORS—Wire-wound, vitreous-enameled resistors. Stock sizes: 25, 50, 100, 160, 200 watts; values 1 to 250,000 ohms. "Brown Devil" fixed resistors in 5, 10, and 20-watt sizes; values from 0.5 to 100,000 ohms. Adjustable power resistors; quickly adjustable to the value needed. Sizes 10 to 200 watts, to 100,000 ohms. Wire-wound axial lead resistors in stock sizes of 1, 3, 5, & 10 watts; values, 1 to 50,000 ohms.

R. F. CHOKES — Single-layerwound on low power factor cores with moistureproof coating. Seven stock sizes, 3 to 520 mc. Two units rated 600 ma; others, 1000 ma.

BE RIGHT WITH

OHMITE®

World Radio History

TAP SWITCHES—Compact, highcurrent rotary selectors for a-c use. All-ceramic. Self-cleaning, silver-to-silver contacts. Rated at 10. 15, 25, 50, and 100 amperes.

PRECISION RESISTORS—Four types available: molded siliconeceramic, vacuum-impregnated, encapsulated, or metal film. Tolerances to \pm 0.1% in $\frac{1}{8}$, $\frac{1}{4}$, $\frac{1}{2}$, $\frac{3}{4}$, 1, and 2-watt sizes, from 0.1 to 2,000,000 ohms.

VARIABLE TRANSFORMERS—Model VT2, 1½ amp rating, output voltage, 0-120/132V; Model VT4, 3½ amp rating, output voltage 0-120/140V; Model VT8, 7½ amp rating, output voltage 0-120/140V; Model VT20, 20 amp rating, output voltage, 0-120/140V. Also 36-volt units. Input voltage all models, 120V, 60 cycles. Thirty-nine stock models, cased and uncased.

OHMITE MANUFACTURING COMPANY 3608 Howard Street, Skokie, Illinois

MASTER MOBILE-TOPS IN QUALITY & PERFORMANCE

NEW DELUXE HI-"O" COILS



New wide space deluxe antenna coil. Greater efficiency on individ. bands. Easily handles 750 W. P.E.P. Lightest coil of its kind commercially available. Use with 36" base sect. 60" whip.

			 	r	-		
15M						. 5	5.95
20M							6.95
40M 75M				٠			7.95 9.95
160M				٠			14.95



\$R-500-6 \$12.95 \$R-500-2 10.95 SR-500-10 \$24.95 SR-500-11 24.95

NEW! SLIM-JIM

FOR 10, 11,

15, 20, 40, 80

METERS

SIZE 1%"x 19"

Positive action, just slide whip in or out to loading point and lock nut

into position.

NO.

B-1080

\$1795

961

WHIP

FIBRE-GLAS ANTENNA

The Feather-Weight with Spring-Steel Strength. pletely weatherproof. glas covering, minimizes electrostatic noises generated by heat, moisture and foreign particles in the air.

FG-80 60" \$4.95 FG-72 72" \$4.95 FG-84 84" \$5.15 FG-96 96" \$5.25 FG-103 103" \$6.95

MASTER-MAGIC TUNABLE WAND

easy-to-install, single top-loaded, plastic co-Newl hand vered fiber-glas antenna. Maximum performance on the desired band

10 Met.- 5 Ft. L \$8.95 11 Met.- 5 Ft. L. 8.95 8.95 15 Met.- 5 Ft. L. 20 Met.- 5 Ft. L. 8.95 9.95 40 Met.- 6 Ft. L. 80 Met.- 6 Ft. L. 9.95




6 or 12 volt models

Complete \$24⁹⁵

MASTER MATCHER & FIELD STRENGTH METER. Automatically tunes entire band by remote control.

MULTI-BAND COILS

TWIN 6 - 2 METER BEAM

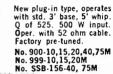

YOUR CHOICE

\$1495



May be rotated by TV rotor. Complete with baluns, match. harness to 52 ohm. Vertical or horiz. pol. Trem. forward gain. Excell. front to back ratio. Lightweight, sturdy.

With PL-259 COAX \$1695

ALL-BAND BASE LOADING MONOPOLE ANTENNA ANTENNA COIL

SR-600

Folded radioting element for installation requiring a graund plane configuration and a wider useful range.

SR-600-2 2 Met... \$14.95 SR-600-6 6 Met... 16.95 SR-600-10 10 Met... 24.50 SR-600-11 11 Met... 24.50


WRITE FOR FREE CATALOG



UNIVERSAL MOUNTS

Heavy duty comm. ant. mts. Can be attached through opening as small as 3/16". For spring or whip. Pheno insulators. %"-24 th. 530 Double SS. \$21.95

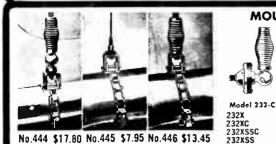531 Single SS. 11.95 520 Db, S-Cad. Pl. 7.95 519 SI. S. Cad. Pl. 4.95



Adjustable to any bumper. No holes to drill.

MOUNTS



232 Series







No. I-11 Swivel Mount Fits all antennas 3/4"-24th. \$2.95

100WX

Base Mount—H.D.—Dble. Tpred. Spring—Swivel Base \$ 9.85
Base Mount—H.D.—Dble. Tpred. Spring—Coax, Conn. 9.85
Base Mount—H.D.—D. Tpd. Sg.—Sp. Sless—Coax Conn. 14.95 232KSS Base Mount—H.D.—Dble. Tpd. Spg.—Spec. Stainless...
321 or 321C Base Mount—Where no spg. des.—w. sp. rig. type ball jt.

140

All products are for Universal Use-Mobile, Home, Marine, C.A.P., Civil Defense, Emergency, etc.



Master Mobile Mounts, Inc. 4125 W. JEFFERSON BLVD. . LOS ANGELES 16, CALIF.

AT LEADING RADIO JOBBERS **EVERYWHERE**

BELDEN-

Wire and Cable for every Ham Application


Ham Transmission Lines—RG/U Type

Belden 72-ohm RG/U Cables are designed for lowest losses, longer service life, and maximum dependability. Cables are essentially flat with no peaks in attenuation to reduce signal on either high or low frequencies.




Ham Transmission Lines— Parallel Type

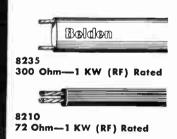Belden transmission line cables are made with brown virgin polyethylene for best weather resistance and lowest losses. Uniform quality control prevents standing waves and mismatches.



Power Supply Cables

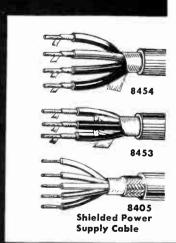Provide dependable service as power supply cords, interconnecting cables on electronic equipment, remote control circuits, special press-to-talk microphone circuits, and other ham applications. Designed for long service life with excellent mechanical and electrical characteristics, and uniform quality. Special jacket offers maximum resistance to abrasion and ozone.




Service Rated-Quality Controlled-Easy-to-Use-**Packaged Lengths**




High Voltage Lead

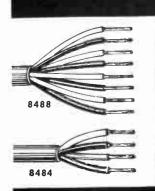New, improved lead offers smaller diameter and greater flexibility and voltage .150" OD, 25,000 V working voltage and 50,000 V breakdown.



Antenna Rotor Cables

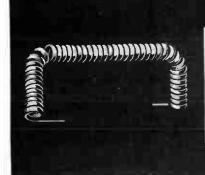Sturdy, flexible, plastic insulated cable for all Ham antenna rotor applications. Cables are color coded for easier hook-up. Chrome, vinyl plastic jacket resists sun and aging.



Coiled Retractile Cables Microphone — Telephone

A variety of types and lengths for most applications. Microphone cables offered with 1, 3, and 4 conductors in vinyl and neoprene—telephone cords with 3 and 4 conductors, vinyl only.

Hook-Up Wire

All colors, types, sizes, insulations, and temperature ranges in stock at your jobber. Available in packaged lengths for easy handling.

8525

Magnet Wire · Lead Wire · Power Supply Cords · Cord Sets and Portable Cord · Electrical Household Cords · Electronic Wires • Welding Cable • Automotive Wire and Cable

orld Radio History

electron tubes

HELPFUL CHARTS & LITERATURE FREE: Write for CONDENSED TUBE CATALOG, information at a glance, rapid tube data reference tables, 25 pages of condensed information arranged for quick reference, Address your distributor or Amperex direct.

COMMUNICATION

RECTIFICATION

SPECIAL PURPOSE

RADIATION DETECTION

AMATEUR

ELECTRO-MEDICAL

SEMICONDUCTORS

Detailed Data Sheets on any of the tubes, and applications engineer service are yours for the aski

RADIATOR CREOIT FOR FORCED AIR-COOLED TUBES

-	_	 _	 -	 -	 _	 		_	
Tube 1									owar
889RA									
891R,									
5604									
5667									
6445									
6447									
6757									
6801		•							75

**Price on request. ‡Price includes 10% Fed. Excise Ti ALL PRICES SUBJECT TO CHANI WITHOUT NOTICE

........... ask Amperex about AMPLIFRAME tube

*AMPLIFRAME, a new concept electron tubes, designed and ma produced exclusively by Ampere incorporates the unique FRAME GR ...the closest approach to the ide "Physicists' grid"-electrical chara teristics but no physical dimension The FRAME GRID results in: . high transconductance per milliampere tighter Gm and plate current toli ance . low transit time . low capa tances . lower microphonics . rugg construction



















7093


6977









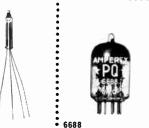





7459

The prices shown here are suggested list prices. For original equipment manufacturer prices, please write directly to the factory.

ELECTRONIC CORP. HICKSVILLE, L. I., N. Y.

IN CANADA: PHILIPS ELECTRONICS INDUSTRIES LTD., TUBE, SEMICON-DUCTOR & COMPONENT DEPTS., 116 VANDERHOOF AVENUE, TOR DNTO, 17.

Suggested Type No. Resale Price	Suggested Type No. Resale Price	Suggested Type No. Resale Price
BEAM POWER TUBES	PENTODES (Con't)	TETRODES (Con't)
807 \$3.50	*t6EJ7 2.90	4CX250F 39.35
6146 5.90	‡8BQ5 2.60	4X150A 29.35
6146 5.90 6159 5.90 PE06/40N 5.95	‡45B5 · · · · · · 3.50	4X150D 29.35
	*16EJ7 2.90 18BQ5 2.60 145B5 3.50 828 27.60 5654/6AK5W . 3.45 *5847 17.50	4CX250F . 39.35 4X150A . 29.35 4X150D . 29.35 4X250B . 36.50 4X250F . 36.50 4X500A . 128.50 6075 . 250.00 6076 . 305.00 6079 . 60.00 6155 . 36.00 6156 . 46.50
DIODE, CLIPPER	*5847 17.50	4X500A 128.50
339 \$44.50	6007 1.50	6076
COUNTERS, GEIGER	6083	6079 60.00
N \$16.50 NB3 16.50	6084 3.75	6155 36.00
INB 27.00	6227 3./5	6156 46.50
NB 27.00 NB3 27.00 NB4 27.00	6375 11.50	6883 . 5.90 6979 . 42.50 7527 . 48.00 7609 . 29.35 17699 . 16.00
NB4 27.00 27.00	6686 5.00	7527 48.00
oc 54.00	6688 8.00 6688A 8.06	17699 16.00
OCB 58.00	6688A 8.06 6689 4.50 17189 3.60 *7534 16.50 7693 4.20 *7737 9.00 EFP60 8.75 EF 127 5.75	TETRODES, BEAM
OHB 54.00	17189 3.60	813 \$21.10
NB 46.00	7693 4.20	813 \$21.10 7378 45.00
2 90.00	7694 4.20	TWIN TETRODES
N 95.00	*7737 9.00	829B \$19.00
B 95.00	‡EL37 5.75	832A 15.90
1 61.00	PENTODE, DUO-DIODE	5894 COMM 32.40
91.00	\$6DC8 \$3.25	5895 18.50
č :::::: 67.00		829B
CB 71.00	TRIODE-PENTODES	6360 COMM 6.30 6360 MIL 6.70 6907 32.40 6939 14.00 7377 25.00
N 56.00	16BM8 3.20	6907 32.40
NB 58.50	‡6DX8 3.20	6939 14.00
oc 43.00	16U8 3.30	/3// 25.00
ON 41.00	\$16BL8 . \$3.80 \$16BM8 . 3.20 \$16DX8 . 3.20 \$16U8 . 3.30 \$150BM8 . 3.50 \$7643 . 5.25	I THYRATRONS I
27.00 27.00 CC		2D21 \$ 1.85
2NB 53.00	PHOTOMULTIPLIERS 50AVP . \$ 62.00 50AVP.SP 78.00 51UVP 308.00 52AVP 120.00 53AVP 80.00 53AVP 462.00 53AVP 158.00 55AVP 158.00 55AVP 210.00 55AVP 496.00 56AVP 496.00 56UVP 696.00 57AVP 850.00 58AVP 850.00 150AVP 62.00 150AVP 76.00 150AVP 76.00 150AVP 84.00	3C23
COUNTING,	50AVP-SP 78.00	5632/C3J 15.50
INDICATOR TURES	51UVP 308.00	5684/C3JA 19.80
2C \$11.80	53AVP 80.00	5727 2.70
3C 10.65	53AVP-X 88.00	5727 2.70 AX260 150.00
OM 11.00	53UVP 462.00	THYRATRONS, HYDROGEN
ом 12.00	55AVP 210.00	6268 \$32.50 6279 45.00
51 61.00	56AVP 496.00	6279 45.00
NOILATOR TUBES	56UVP · · · · · 696.00	THYRATRONS, MERCURY
DIODES, DAMPER	58AVP 850.00	5557/FG17 \$ 9.50
L3 \$2.80	150AVP 62.00	5560/FG95 33.00
123 \$2.80 13/EY81 2.80 103 2.60	150AVP-SP . 76.00	5869 25.00
	DECTIFIED	5870 100.00
TWIN DIODE		187KAIKUNS, MERCURT 5557/FG17 . \$ 9.50 5559 23.00 5560/FG95 . 33.00 5869 25.00 5870 100.00 6786 200.00 AX105/FG105 . 53.33
26/6AL5W \$2.10	\$1\$2A \$ 2.75 \$5AR4 4.20 \$5RAGY 1.90 \$6CA4 2.10	THYRATRONS, XENON
DIODE, VTVM	15RAGY 1.90	2050 \$ 3.35
23 \$13.00	1 16CA4 2.10	2050 \$ 3.35 5544 30.50 5545 29.30
IGNITRONS	16CA4 2.10 16V4 1.50 16X4 1.65 575A 22.15 673 22.15 8020AX 24.00	5545 29.30
51A \$ 65.00	575A 22.15	TRIODES
52A 99.00 53B 245.00	8020AX 24.00	*IZER5 \$ 2.80 *t2FY5 2.80
55 316.00	RECTIFIERS, MERCURY	*12ER5 \$ 2.80 *12FY5 2.80 *13ER5 2.80 *13FY5 2.80 16AT6 1.90 16AV6 1.65 ************************************
316.00 22A 116.00 55 99.00	857B \$235.00	*13FY5 2.80
	857B \$235.00 866AX 3.10	16AV6 1.90
TUNING INDICATORS		
3 \$1.95 R5 2.45	8698 160.00	*16ER5 2.45
	869BL 160.00	*16ER5 2.45 *16FY5 2.80
D7 3.65	869BL 160.00 869BL 160.00 872AX 11.65 6508 80.00	*16FY5 2.80 16Q4 6.00 16R4 5.10
77	869B 160.00 869BL 160.00 872AX 11.65 6508 80.00 6693 25.00	*16FY5 2.80 ±6Q4 6.00 ±6R4 5.10 356 660.00
7 2.45 5 2.45 6 2.95	869B 160.00 869BL 160.00 872AX 11.65 6508 80.00 6693 25.00	*15FY5 2.80 16Q4 6.00 16R4 5.10 356 660.00 450TH 77.00
/1 <u>2.00</u>	869BL 160.00 869BL 160.00 872AX 11.65 6508 80.00 6693 25.00 7136 25.00 8008AX 10.65	*i6FY5 2.80 i6Q4 6.00 i6R4 5.10 356 660.00 450TH 77.00 450TL 77.00 501R 225.00
KLYSTRON, REFLEX	869BL 160.00 872AX 11.65 6508 80.00 6693 25.00 7136 25.00 8008AX 10.65 RECTIFIERS, XENON	*i6FY5 2.80 i6Q4 6.00 i6R4 5.10 356 660.00 450TH 77.00 450TL 77.00 501R 225.00
LYSTRON, REFLEX	869BL 160.00 869BL 160.00 872AX 11.65 6508 80.00 6693 25.00 7136 25.00 8008AX 10.65	*16FY5 2.80 16Q4 6.00 16R4 5.10 356 660.00 450TH 77.00 501R 225.00 502 210.00 502R 235.00
KLYSTRON, REFLEX 5 \$39.50 MAGNETRONS	869BL 160.00 869BL 160.00 872AX 11.65 6508 80.00 6693 25.00 7136 25.00 8008AX 10.65 RECTIFIERS, XENON 3B28 \$ 7.60 4B32 13.50	*16FY5 2.80 16Q4 6.00 16R4 5.10 356 660.00 450TH 77.00 450TL 77.00 501R 225.00 502 210.00 502R 235.00 504R 245.00 805 20.10
KLYSTRON, REFLEX 15 \$39.50 MAGNETRONS 26 \$417.00	869BL 160.00 872AX 11.65 6508 80.00 6693 25.00 7136 25.00 7136 10.65 RECTIFIERS, XENON 3B28 \$7.60 4B32 13.50 VOLTAGE REFERENCE TUBES	*16FY5 2.80 16Q4 6.00 16R4 5.10 356 660.00 450TH 77.00 501R 225.00 502 210.00 502R 235.00 504R 245.00 805 20.10 810 25.65
KLYSTRON, REFLEX 15 \$39.50 MAGNETRONS 2 \$ ** 6 \$417.00 2 325.00	869BL 160.00 872AX 11.65 6508 80.00 6693 25.00 7136 25.00 7136 10.65 RECTIFIERS, XENON 3B28 \$7.60 4B32 13.50 VOLTAGE REFERENCE TUBES	*16FY5 2.80 16Q4 6.00 16R4 5.10 356 660.00 450TH 77.00 450TL 77.00 501R 225.00 502 210.00 502R 235.00 504R 245.00 805 20.10 810 25.65 811A 8.10
KLYSTRON, REFLEX KLYSTRON, REFLEX 55 \$39.50 MAGNETRONS 12 \$ ** 16 417.00 12 325.00	869BL 160.00 872AX 11.65 6508 80.00 6693 25.00 7136 25.00 8008AX 10.65 RECTIFIERS, XENON 3B28 57.60 4B32 13.50 VOLTAGE REFERENCE TUBES 85A1/OE3 \$2.75 85A2/OG3 2.50	*16FY5 2.80 16Q4 6.00 16R4 5.10 356 660.00 450TH 77.00 501R 225.00 502 210.00 502R 235.00 504R 245.00 805 20.10 810 25.65 811A 8.10
KLYSTRON, REFLEX 25 \$39.50 MAGNETRONS 12 \$ ** 16 417.00 17	869BL 160.00 872AX 11.65 6508 80.00 6693 25.00 7136 25.00 7136 10.65 RECTIFIERS, XENON 3B28 \$ 7.60 4B32 13.50 VOLTAGE REFERENCE TUBES 85A1/OE3 \$2.75 85A2/OG3 \$2.50 5651 2.50	*16FY5 2.80 16Q4 6.00 16R4 5.10 356 660.00 450TH 77.00 501R 225.00 502 210.00 502R 235.00 504R 245.00 504R 245.00 805 20.10 810 25.65 811A 8.10 812A 8.10 8334 53.65
	869BL 160.00 872AX 11.65 6508 80.00 6693 25.00 7136 25.00 7136 10.65 RECTIFIERS, XENON 3B28 \$7.60 4B32 13.50 VOLTAGE REFERENCE TUBES 85A1/OE3 \$2.75 85A2/OG3 2.50 VOLTAGE REGULATORS	*16FY5 2.80 16Q4 6.00 16R4 5.10 356 660.00 450TH 77.00 501R 225.00 502 210.00 502R 235.00 504R 245.00 504R 245.00 805 20.10 810 25.65 811A 8.10 812A 8.10 8334 53.65
KLYSTRON, REFLEX (225 \$39.50 MAGNETRONS 42 \$** 86 417.00 772 325.00 91 **	869BL 160.00 872AX 11.65 6508 80.00 6693 25.00 7136 25.00 7136 10.65 RECTIFIERS, XENON 3B28 \$7.60 4B32 13.50 VOLTAGE REFERENCE TUBES 85A1/OE3 \$2.75 85A2/OG3 2.50 5551 2.50 VOLTAGE REGULATORS OA2 \$1.75	*16FY5 2.80 16Q4 6.00 16R4 5.10 356 660.00 450TH 77.00 501R 225.00 502 210.00 502R 235.00 504R 245.00 504R 245.00 805 20.10 810 25.65 811A 8.10 812A 8.10 833A 53.65 834 19.30 838 20.00 845 20.80 849 185.00
KLYSTRON, REFLEX 25 \$39.50 MAGNETRONS 42 \$** 86 417.00 72 325.00 91 **	869BL 160.00 872AX 11.65 6508 80.00 6693 25.00 7136 25.00 7136 10.65 RECTIFIERS, XENON 3B28 \$7.60 4B32 13.50 VOLTAGE REFERENCE TUBES 85A1/OE3 \$2.75 85A2/OG3 2.50 5551 2.50 VOLTAGE REGULATORS OA2 \$1.75	*16FY5 2.80 16Q4 6.00 16R4 5.10 356 660.00 450TH 77.00 450TL 77.00 501R 225.00 502 210.00 502R 235.00 504R 245.00 805 20.10 810 25.65 811A 8.10 812A 8.10 833A 53.65 834 19.30 838 20.00 845 20.80 849 185.00
KLYSTRON, REFLEX 25 \$39.50 MAGNETRONS 42 \$** 86 417.00 72 325.00 91 ** PENTODES 3ELT7 \$2.90 3ELT7 2.90 4ELT7 2.90 4EJ7 2.90 4EJ7 2.90 4EJ7 2.90	869BL 160.00 872AX 11.65 6508 80.00 6693 25.00 7136 25.00 7136 10.65 RECTIFIERS, XENON 3B28 \$7.60 4B32 13.50 VOLTAGE REFERENCE TUBES 85A1/OE3 \$2.75 85A2/OG3 2.50 5551 2.50 VOLTAGE REGULATORS OA2 \$1.75	*16FY5 2.80 16Q4 6.00 16R4 5.10 356 660.00 450TH 77.00 450TL 77.00 501R 225.00 502 210.00 502R 235.00 504R 245.00 805 20.10 810 25.65 811A 8.10 812A 8.10 833A 53.65 834 19.30 838 20.00 845 20.80 849 185.00
KLYSTRON, REFLEX 25 \$39.50 MAGNETRONS 42 \$** 36 417.00 72 325.00 91	869BL 160.00 872AX 11.65 6508 80.00 6693 25.00 7136 25.00 7136 10.65 RECTIFIERS, XENON 3B28 \$ 7.60 4B32 13.50 VOLTAGE REFERENCE TUBES 85A2/OG3 \$2.75 85A2/OG3 \$2.50 5651 2.50 VOLTAGE REGULATORS OA2 \$1.75 OB2 1.90 90C1 2.50 150B2/6354 3.00 6354 3.00	*16FY5 2.80 16Q4 6.00 16R4 5.10 356 660.00 450TH 77.00 501R 225.00 502 210.00 502R 235.00 504R 245.00 504R 245.00 805 20.10 810 25.65 811A 8.10 833A 55.65 834 19.30 838 20.00 845 20.80 849 185.00 849A 165.00 880 555.00
KLYSTRON, REFLEX STATE OF THE NUMBER OF THE	869BL 160.00 872AX 11.65 6508 80.00 6693 25.00 7136 25.00 7136 10.65 RECTIFIERS, XENON 3B28 \$7.60 4B32 13.50 VOLTAGE REFERENCE TUBES 85A1/OE3 \$2.75 85A2/OG3 2.50 VOLTAGE REGULATORS OA2 \$1.75 OB2 1.90 90C1 2.50 150B2/6354 3.00 6354 3.00 TETRODES	*16FY5 2.80 16Q4 6.00 16R4 5.10 356 660.00 450TL 77.00 450TL 77.00 501R 225.00 502 210.00 504R 245.00 805 20.10 810 25.65 811A 8.10 812A 8.10 812A 8.10 833A 53.65 834 19.30 838 20.00 845 20.80 849 185.00 849 185.00 849A 165.00 889A 235.00 889A 235.00
KLYSTRON, REFLEX KLYSTRON, REFLEX MAGNETRONS 2	869BL 160.00 872AX 11.65 6508 80.00 6693 25.00 7136 25.00 7136 25.00 7136 10.65 RECTIFIERS, XENON 3B28 \$7.60 4B32 13.50 VOLTAGE REFERENCE TUBES 85A2/OG3 2.50 5651 2.50 VOLTAGE REGULATORS OA2 \$1.75 OB2 1.90 90C1 2.50 150B2/6354 3.00 6354 3.00 TETRODES 4-125A \$36.00	*16FY5 2.80 16Q4 6.00 16R4 5.10 356 660.00 450TH 77.00 450TL 77.00 501R 225.00 502 210.00 502R 235.00 805 20.10 810 25.65 811A 8.10 812A 8.10 812A 8.10 833A 53.65 834 19.30 838 20.00 845 120.80 849 185.00 849 185.00 889 595.00 889A 235.00 889RA 370.00 889RA 370.00 891 275.00
KLYSTRON, REFLEX Solution State	869BL 160.00 872AX 11.65 6508 80.00 6693 25.00 7136 25.00 7136 10.65 RECTIFIERS, XENON 3B28 \$7.60 4B32 13.50 VOLTAGE REFERENCE TUBES 85A1/OE3 \$2.75 85A2/OG3 2.50 VOLTAGE REGULATORS OA2 \$1.75 OB2 1.90 90C1 2.50 150B2/6354 3.00 6354 3.00 TETRODES	*16FY5 2.80 16Q4 6.00 16R4 5.10 356 660.00 450TL 77.00 450TL 77.00 501R 225.00 502 210.00 504R 245.00 805 20.10 810 25.65 811A 8.10 812A 8.10 812A 8.10 833A 53.65 834 19.30 838 20.00 845 20.80 849 185.00 849 185.00 849A 165.00 889A 235.00 889A 235.00

Suggested	Suggested
Type No. Resale Price	Type No. Resale Price
retrodes (Con't)	TRIODES (Con't)
ICX250F 39.35	5619 423.00 5658 595.00
X150D 29.35	5666 280.00
1X250B 36.50	5771 660.00
X500A 128.50	5823 2.50
5075 250.00	5866 20.00
60.00	5867 30.00
5156 46.50	5923 165.00
883 5.90	5924 231.00
7527 48.00	6333 290.00
7609 29.35	6445 455.00
IETRODES (Con't) ICX250F 39.35 IX150A 29.35 IX150D 29.35 IX250B 36.50 IX250B 36.50 IX250F 36.50 IX500A 128.50 IX500A 128.50 IX500A 128.50 IX500A 305.00 IX500 46.50 IX500 46.50 IX500 46.50 IX50 46.50	6447 465.00
TETRODES, BEAM 313 \$21.10 7378 45.00	6757 535.00
7378 45.00	6758 173.00
TWIN TETRODES	6800 350.00
332A 15.90	6960 150.00
5894 COMM 32.40	6961 210.00
5895 18.50	7004 160.00
5252 32.40 6360 COMM 6.30	7092 125.00
WIN ILINUIS 19.00 32.40 35.40 35.40 35.40 35.40 36.5252 32.40 36.60 36	5619 423.00 5658 595.00 5666 280.00 5666 280.00 55667 370.00 5771 660.00 5823 2.50 *5842 17.50 5866 20.00 5866 30.00 5868 55.00 5923 165.00 5924 231.00 5924A 275.00 6333 290.00 6445 455.00 6445 455.00 6446 305.00 6447 465.00 6446 305.00 6756 388.00 6757 535.00 6758 173.00 6759 206.00 6800 350.00 6800 350.00 6801 505.00 6961 210.00 6961 210.00 6961 210.00 6961 210.00 6961 210.00 7092 125.00 704 160.00 7092 125.00 7237 180.00 7459 230.00 7459 230.00 7459 230.00 7459 230.00 7804 440.00 7805 402.00 7805 402.00 7806 795.00 7807 584.00 HF200 49.50 HF200 49.50 HF300 40.50 TBL2/400 250.00 TBL2/500 270.00 ZB3200 395.00 TRIODE, INDICATOR
6939 14.00	7804 440.00
7377 25.00	7806 795.00
THYRATRONS	7807 584.00 HF200 49.50
2D21 \$ 1.85 3C23 11.98	HF300 40.50
632B 36.00	TBL2/500 250.00
5684/C3JA 19.80	ZB3200 395.00
5685/C6JA 27.80	TRIODE, INDICATOR
AX260 150.00	6977 \$3.50
THYRATRONS 2D21 \$ 1.85 3C23 11.98 632B 36.00 65632/C3J 15.50 5684/C3JA 19.80 5685/C6JA . 27.80 5727 2.70 AX260 150.00 THYRATRONS, HYDROGEN 6328	TWIN TRIODES *14ES8 \$4.55 6AL5W 2.10 166AQ8 2.60 *16DJ8 2.45 *16ES8 4.55 *16GM8 4.55 *16J6 2.80 19AQ8 3.10 112AT7 3.05 112AU7 2.45 112AV7 2.45 112AV7 2.50 5920 2.95 6085 3.75 6201 4.20 6211 2.35 6463 3.50 *6922 MIL 5.50 *6922 MIL 5.50 *6922 MIL 5.50 *7025 2.90 7062 2.40 7119 3.15 *7308 6.00 7316 2.00 7316 2.00 7316 2.00 7316 2.00 7316 2.00 7316 2.00 7316 2.00 7316 2.00
6268 \$32.50 6279 45.00	6AL5W 2.10
TUVDATDONS MEDCILLY	#16AQ8 2.60
5557/FG17 \$ 9.50	*16ES8 4.55
5559 23.00	16J6 2.80
5869 25.00	19AQ8 3.10
5870 100.00 6786 200.00	112AU7 2.45
THYRATRONS, MERCURY 5557/FG17 . \$ 9.50 5559 23.00 5560/FG95 . 33.00 5869 100.00 6786 200.00 AX105/FG105 . 53.33	112AX7 2.55 117EW8 2.60
INYKAIKUNS, XENUN I	5920 2.95
2050 \$ 3.35 5544 30.50 5545 29.30	6201 4.20
5545 29.30 TRIODES	6211 2.35
TRINNES	*6922 5.50
*12ER5 \$ 2.80 *12FY5 2.80 *13ER5 2.80 *13FY5 2.80 *13FY5 2.80 16A76 1.90 16A76 1.95	17025 2.90
*13ER5 2.80	7062 2.40
16AT6 1.90	*7308 6.00
‡6AV6 1.65 *16ER5 2.45	7316 2.00 E92CC 2.40
*i6FY5 2.80	TRIGGER TUBES
16Q4 6.00 16R4 5.10	COLD CATHODE
356 660.00	7710 \$1.95 7713 4.30 250T 2.20 270U/7710 1.35 270W/7709 2.10
450TL 77.00	7713 4.30 Z50T 2.20
501R 225.00 502 210.00	Z70U/7710 1.35 Z70W/7709 2.10
502R 235.00	Z/1U///11 1.95
504R 245.00 805 20.10	Z300T 4.95 Z803U 5.50
810 25.65	Z805U/7714 2.35
811A 8.10 812A 8.10	PHOTO
833A 53.65 834 19.30	CONDUCTIVE CELLS ORP11 \$ 2.95
838 20.00	ORP30 3.80
845 20.80 849 185.00	ORP50 1.95 ORP60
849A 165.00	OKP61/5
889A 235.00	ORP90 1.95 61SV 22.00
889RA 370.00 891 275.00	PENTAGRID
891R 430.00	6687 \$1.55
892 270.00 892R 425.00	BEAM DEFLECTOR TUBE
5604 570.00	6218 \$15.00

Surprise!

WALTER ASHE TRADES HIGHER

the always has since 19221

You always save money dealing with Walter Ashe Radio... because we always offer you more for your used transmitters, receiver or other surplus amateur gear*. Find out for yourself... tell us what you have to trade and what you want. We guarantee you'll be genuinely surprised by the Walter Ashe deal! Use the coupon below... mail it today!

DO YOU HAVE OUR NEW 144 PAGE AMATEUR CATALOG?



Check the coupon
...get the amateur's
most complete
catalog of the newest
in equipment, parts
and supplies ...
everything

Made since 1945

Catalogs mailed only to U.S. and Canada stnut 1-1125

you need!

WALTER ASHE RADIO CO.

Dept. H-62, 1123 Pine St., St. Louis 1, Mo.

WALTER ASHE RADIO	COMPANY
Dept. H-62, 1123 Pine	Street, St. Louis, Missouri
I am interested in	
What is the Ashe "Surpr	ise" allowance on
Name	
Address	
City	ZoneState
	Send Reconditioned Bulletin

9mportant

AOVERTISING IN THE 1963 HANDBOOK AT NO CHARGE TO QST ADVERTISERS WHO QUALIFY

TO ALL ADVERTISERS IN QST AND THE RADIO AMATEUR'S HANDBOOK AND THEIR AD-VERTISING AGENCIES

- a. An advertiser who uses a total of 6 pages but not as many as 15 pages in QST during the twelve months of November 1961 through October 1962 can run a half-page in the 1963 HAND-BOOK at no charge. The ad can be vertical or horizontal and either black & white or black & white and red.
- b. An advertiser who uses a total of 15 pages or more in QST during the twelve months of November 1961 through October 1962 and who buys one page or more in the 1963 HAND-BOOK can run one additional full page in the HANDBOOK at no charge. The additional page can be either black & white or black & white and red. Or, if the advertiser does not buy a page in the 1963 HANDBOOK he qualifies for a half-page as outlined in the preceding paragraph a.

QST and the Handbook —
The combination covering
the electronic markets:
Amateur, Industrial, Government

Advertising Department
AMERICAN RADIO RELAY
LEAGUE

38 La Salle Rd. West Hartford 7, Conn.



E-Z WAY QUALITY SERVES YOU BEST... ear After Year!



- NO GUYS
- TILTS OVER
- CRANKS UP & DOWN

55,000 PSI HIGH TENSILE STEEL FOR MAXIMUM STRENGTHI

CHALLENGER

Standard duty two section Tower. Cranks up to 40' and down to 24'. Will support 3 el., 15 M Mini-beam or 3 el. tribander at 40° in winds up to 50 mph without guys.

Model RBD 40-P (painted)	\$ 99.50
Model RBD-40-G (golv.)	134.50
Model with GPK D-40	50.00
or BAK-D (building attach kit).	6.75

RBD-40

HOT DIPPED GALVANIZED AFTER FABRICATION.

MEDALIST "40" ₹

Sturdy two section tower. Cranks up to 41 ft. and down to 24 ft. Supports a triband or equivalent at 41' in 70 mph winds or 125 mph when cranked down.

Model	RBS-40P	(painted)\$	169.50
Model	RBS-40G	(galv.)	209.50
Model	GPK-S40	(ground post)	75.00
		(building attach)	

SATELLITE "60"

A 3 section tower. Cranks up to 58' and down to 25', Will support a 4 el., 20M full size beam or a 6 el. triband at 60' in wind up to 60mph. . NO GUYS! 140mph cranked down.

Model	RBX 60-3p (painted)\$	335.00
	RBX 60-3G (Galv.)	
Model	GPK 60-3 (ground post)	120.00
Model	BAK-X (building ottoch)	17.00

RBX-60-3

RBS-40

- Self-supporting to 34 ft.
- Famous E-Z Way Rotor Head.
- * Light weight 10 ft. section weighs only 29 lbs.
- # Climbable ladder on three sides.

NEW "HP" Economy Series

The HP series is a low cost Ham tower that is built to take it. The famous E-Z Way design has incorporated 55,000 PSI steel into the manufacture of all towers. Light weight and easy to erect. Hot dipped galvanized, electric arc welded and comes complete with base plate and wall bracket.

Model HP-34

Model HP-44.____ Model HP-54.....

G-10

G-10... FOR HAM, CB, TV or TWO WAY.

E-Z Way's "G-10" is all NEW! Here is the Tower designed to take it, with durability built-in every inch of its superb construction. 55,000 PSI steel ... X-Type bracing ... Light weight, 10 ft. sections weigh only 29 lbs. These are only a few outstanding features that make this tower the strongest of its kind in the field. Fast, easy erection, up to 280 ft. guyed, or 40 ft. self-supporting. Completely electric arc welded and hot dipped galvanized after fabrication.

The NEW "Stack Pole" lets you really get up there! **DETAILS TO BE ANNOUNCED**

WRITE FOR COMPLETE DETAILS ON ALL E-Z WAY TOWERS.

Z WAY TOWERS, Inc.

P.O. BOX 5767

TAMPA 5, FLORIDA



& handling. ENGINEERS: Excellent career opportunities in creative electronics design. Write to the Chief Engineer,

Export Dept., Roburn Agencies Inc. 431 Greenwich St., N. Y. 13, N. Y.

. ZoneState.....

Add 5% in the West.

✓ City.

A General Electric Two-Way Radio to solve every communication need



General Electric's TPL: Extra-feature performance leader

General Electric's Transistorized Progress Line offers highest performance . . . plus standby battery drain so low that you never have to turn off your TPL unit . . . fits in more places, in more positions, than any other two-way mobile radio you can buy.



The Progress Line: Proven performance leader

Since 1955 General Electric's tubed Progress Line has served customers with economical, high power, high reliability two-way radio. A wide range of models satisfies every mobile communication requirement. For field-proved performance and low maintenance cost even under the most rugged conditions, specify the Progress Line.

The General Electric Pacer: Compact economy leader

The General Electric Pacer gives you every advantage of quality FM communication for limited range applications at the exceptionally low price of \$419.00 . . . and the lowest battery drain of any mobile radio in its class means important additional savings.



Many successful General Electric mobile radio authorized service stations were founded by licensed radio amateurs, and many now utilize the skills of hams on a part-time or full-time basis. Find out how you can become a General Electric service technician. Write National Service Manager, General Electric Company, Communication Products Department, Section 31, Mountain View Road, Lynchburg, Va.





If It's Shown In This Handbook Henry Has It!

HENRY gets the new equipment First you get the world's best Terms!

Low Terms

You get the best terms anywhere because Henry finances all the terms with his easy time payment plan. 10% down (or your trade-in accepted as down payment), 20 months to pay.

Long Trades

Henry wants to trade and he trades big. YOU get truly liberal allowances on your equipment. Tell us what you want to trade. We also pay cash for used equipment.

Complete Stocks

Henry has everything in the amateur equipment field, new or used . . . transmitters or receivers, and Henry has the NEW equipment FIRST.

Low Prices

Henry's large purchasing power means low prices to you. You just can't beat our wholesale prices.

100% Satisfaction

Henry gives you a guarantee of "100% satisfaction" or your money back at the end of a 10 day trial.

rite, phone or visit a Henry Store Today!



Norld's Largest Distributors of Short Wave Receivers "







Ted Henry W6UOU 11240 West Olympic Blvd. Los Angeles 64, Calif. GRante 7-6701

Walter Henry 931 North Euclid Anaheim, Colif



Learn Code the EASY Way

Beginners, Amateurs and Experts alike recommend the INSTRUCTOGRAPH, to learn code and increase speed.

Learning the INSTRUCTOGRAPH way will give you a decided advantage in qualifying for Amateur or Commercial examinations, and to increase your words per minute to the standard of an expert. The Government uses a machine in giving examinations.

Motor with adjustable speed and spacing of characters on tapes permit a speed range of from 3 to 40 words per minute. A large variety of tapes are available—elementary, words, messages, plain language and coded groups. Also an "Airways" series for those interested in Aviation.

MAY BE PURCHASED OR RENTED

The INSTRUCTOGRAPH is made in several models to suit your purse and all may be purchased on convenient monthly payments if desired. These machines may also be rented on very reasonable terms and if when renting you should decide to buy the equipment the first three months rental may be applied in full on the purchase price.

ACQUIRING THE CODE

It is a well-known fact that practice and practice alone constitutes ninety per cent of the entire effort necessary to "Acquire the Code," or, in other words, learn telegraphy either wire or wireless. The Instructograph supplies this ninety per cent. It takes the place of an expert operator in teaching the student. It will send slowly at first, and gradually faster and faster, until one is just naturally copying the fastest sending without conscious effort.

BOOK OF INSTRUCTIONS

Other than the practice afforded by the Instructograph, all that is required is well directed practice instruction, and that is just what the Instructograph's "Book of Instructions" does. It supplies the remaining ten per cent necessary to acquire the code. It directs one how to practice to the best advantage, and how to take advantage of the few "short cuts" known to experienced operators, that so materially assists in acquiring the code in the quickest possible time. Therefore, the Instructograph, the tapes, and the book of instructions is everything needed to acquire the code as well as it is possible to acquire it.

MACHINES FOR RENT OR SALE



The Instructograph

ACCOMPLISHES THESE PURPOSES:

FIRST: It teaches you to receive telegraph symbols, words and messages.

SECOND: It teaches you to send perfectly.


THIRD: It increases your speed of sending and receiving after you have learned the code.

With the Instructograph it is not necessary to impose on your friends. It is always ready and waiting for you. You are also free from Q.R.M. experienced in listening through your receiver. This machine is just as valuable to the licensed amateur for increasing his speed as to the beginner who wishes to obtain his amateur license.

Postal Card WILL BRING FULL PARTIC-ULARS IMMEDIATELY

THE INSTRUCTOGRAPH CO.

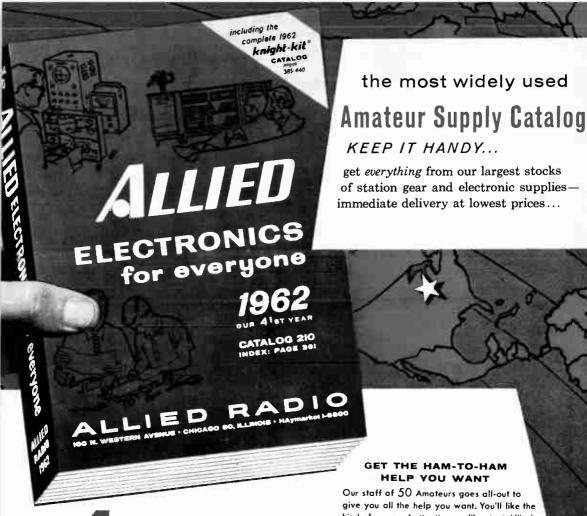4707 SHERIDAN ROAD 4700 S. CRENSHAW BLVD. CHICAGO 40, ILLINOIS
LOS ANGELES 43. CALIFORNIA



ALLIED

gives you every advantage

HIGHEST TRADES: Get the absolute most for your old equipment. Tell us what you've got and what you want-we'll come up fast with the best deal anywhere.

RECONDITIONED GEAR: Large selection, new set guarantee. Ask for latest list of top reconditioned equipment at lowest prices.

NO MONEY DOWN: Easiest terms ever with Allied's new Credit Fund Plan-up to 50% more buying power; up to 24 months to pay. Extra: 15-day trial on all ham gear.

ALLIED RADIO

100 N. WESTERN AVE., CHICAGO 80, ILL.

Sewing the amateur for 41 years



GET THE HAM-TO-HAM HELP YOU WANT

Our staff of 50 Amateurs goes all-out to give you all the help you want. You'll like the kind of personal attention you'll get at Allied. You'll get to know helpful Hams like:



WOWHE Jim Sommerville (Ham Division Manager)



WOHLA Joe Gizzi



Tasker Day (Ham Shack)



WOVH



W9BHD Joe Huffman (Ham Shack)



In Milwaukee W9NGV Lowell Warshawsky



RADIO HANDBOOK

-gives comprehensive, up-to-the-minute data for designing and building radio equipment

Extensive theory—the Radio Handbook covers practically every phase of radio theory, in simplified, easyto-grasp form.

Latest design data - all original material-enables you to design any standard type of transmitting and receiving equipment, from medium to ultra-high frequencies.

Latest construction data—broadest coverage in the field. You get complete original information on how to build and operate advanced high performance equipment. Plans include details on attractive styling. All data clearly indexed. 800 pages all editorial — with hard cover. The largest RADIO HANDBOOK ever published.

at your dealer, plus any tax \$8.50



*Order from your favorite electronic parts distributor If he cannot supply, send us his name and your remittance, and we will supply; foreign, add 10%.

EDITORS and ENGINEERS, Ltd. Summerland 4, California

Dealers: Electronic distributors, order from us. Bookstores, libraries, newsdealers order from Baker & Taylor, Hillside, N.J. Export (exc. Canada), order from H.M. Snyder Co., 440 Park Ave. So., N.Y. 16.

RADIO SHACK

Your Headquarters For Amateur Gear!

HIGHEST TRADES . Correspondent trade-in deal!

Call or write W1RY, Art Bates Amateur Radio Correspondent, c/o Radio Shack for a terrific

EASIEST TERMS . Use Radio Shack's New Revolving Charge! There's NO MDNEY DOWN and up to 24 months to pay on anything you nurchase.

HAM EXPERTS . .

Everyone you talk to or write to concerning Amateur equipment will be a "Ham" himself, knowledgable, courteous ready to serve you!



NC-155

NEW! NATIONAL RADIO COMPANY

.. For The Finest In Amateur Performance

NC-270 RECEIVER

\$15 monthly

A true performance pace-setter! Patented ferrite filter and instant sideband selection provide for upper and lower sideband with linear heterodyne detector and separate carrier reinsertion. Dual conversion 80 through 6 meter coverage, crystal calibrator, #440X750

NC-190 RECEIVER

\$13 monthly

Advanced design general coverage receiver! Instant choice of calibrated amateur or popular foreign broadcast bands. Sensitivity better than 1.0 μv for 10 db S/N ratio. Ferrite filter provides 600 cy., CW, 3 KC SSB, 5 DC AM bandwidths. #450X380

NC-155 RECEIVER

RADIO SHACK CORPORATION, Dept. RA-H


730 Commonwealth Ave., Boston 17, Moss. Please "QUOTE BIG" on my model

Address

City

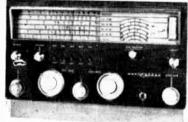Designed exclusively for ham band operation, NC-155 features superb sensitivity (1 $\mu\nu$ for 10 db S/N on all bands), top stability and shaped selectivity! Double conversion on 80 through 6 meters. SSB/CW AGC, separate product detector, #450X739





NC-190

NTS₋₃ SPEAKERS

For All Of The Above Receivers

I would like to trade in toward I would like to purchose State Check Money Order C.O.D.

- Modern Design
- Top Performance

Designed from a single sheet of aluminum, the NTS-3 speakers are perfectly damned, low distortion reproducers, 4 cone diameter. Imp. 3.2Ω. #44DX751

NOW THERE ARE EIGHT RADIO SHACKS TO SERVE YOU

BOSTON, MASS. Commonwealth Ave. REgent 4-1000

WEST HARTFORD, CONN. 39 South Main St. ADams 6-5441

BOSTON, MASS. 167 Washington St. REgent 4-1000

STAMFORD, CONN. 29 High Ridge Rd.

SAUGUS, MASS. N. E. Shopping Center CEnter 3-5350

NEW HAVEN, CONN.


BRAINTREE, MASS.

PROVIDENCE-CRANSTON, R. I. 1301 Reservoir Ave.

SEND FOR BRAND NEW 1962 RADIO SHACK CATALOG! 336 BARGAIN-FILLED PAGES!

VIBROPLE X

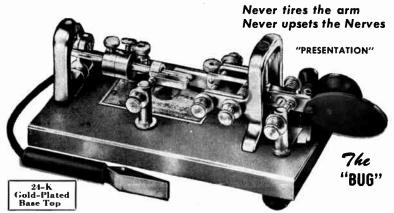THE PIONEER AND ALWAYS THE LEADER WORLD'S NO. 1 KEY SEMI-AUTOMATIC



New Super DeLuxe VIBROPLEX Presentation

The Super DeLuxe model's JEWEL MOVEMENT completely revolutionizes sending. Makes it easy for every operator.

It has SUPER-SPEED CONTROL mainspring; you go from slowest to highest speed without changing weights.

Vibroplex has TOUCH CONTROL, adjustable to your individual desire.

Vibroplex has FIRM STANCE, a very important item. The rubber feet are so placed the key stays in position.

RICHLY DESIGNED — 24k goldplated base top, polished chromlum machine parts, red trim and jeweled movement. DeLuxe, only \$33.95.


ALL LABOR TAKEN OUT OF SENDING

SEND BETTER — Vibroplex makes uniformly good signals at any speed. They are sharp and easy to read. You will like them.

SEND EASIER—Vibroplex is a perfectly balanced key. You are relieved of all nervous and muscular tension.

SEND FASTER — Vibroplex gives you greater speed. More speed than you can ever use. But it's there if you need it.

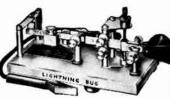SEND LONGER — Vibroplex keys last longer. Many keys are still in use after 30 or more years. Nothing to get out of order.



Vibroplex Lightning Bug

Improved design with alotted weights that can't work loose. A bridged damper frame that protects key against damage. Instantly adjustable dot contact spring may be removed without disturbling speed weights. Precision machining, trouble proof and adjustable to any speed. Standard, with circuit closer, gray base and chrome top parts, prieed at \$25.95.*



Vibroplex Original

Praised by its many thousands of satisfied users for ease of operation, sharp, clear signals and all around excellence. They are precision machined and trouble proof. A strong favorite of the elite. Standard, with circuit closer, chrome top parts and gray base, \$19.95. DeLuxe, with red trim, lewel movement and polished chrome base, \$23.95.



Vibroplex Blue Racer

A duplicate of the Original Vibroplex except for being only half the size, weight 2 lbs, 8 ozs. Does the same fine work as the larger models. Standard, with circuit closer, chrome top parts and gray base, \$22.45. DeLuxe, with chromium base and top parts, red trim and jewel movement, priced at \$26.95.*

Avoid imitational The "BUG" Trade Mark identifies the Genuine Vibroplex. Accept no substitute Replace your old-fashioned key with all its annoyances with an improved NEW VIBROPLEX. Enjoy sending as never before. Choose yours from those illustrated here.

"VIBRO-KEYER"

Supplies the answer to many years of requests for Vibroplex parts for a keying mechanism in constructing an electronic transmitting unit. Features a beautiful base, size 3½" by 4½" and weighing 2½ pounds. Red finger and thumb pleese, same large ½% contacts on main frame and trunion lever as used in Vibroplex. A real beauty, adjustable to suit your speed requirements. Standard model, priced at \$17.95; Deluxe model, with Chrome Plated Base, priced at only \$22.45.

*Cord and wedge. \$1.75 additional.



NEW SPECIAL ENLARGED Edition of PHILLIPS CODE, \$2.75 Postpoid

Also includes: Radio Code Signals International Morse American Morse Russian, Greek, Arabic Turkish and Japanese Morse Codes World Time Chart United States Time Chart Commercial "Z' Code Aeronautical "Q' Code Miscellaneous Abbreviations. Used international wire, submarine cable and radio telegraph circuits.

Get your copy today!

Prices subject to change without notice



Keeps key like new. Black simulated morocco. Flexible leather handle. Protects key against dust, dirt and moisture. Insures safe-keeping when not in use. With lock and key, \$6.75.

Every Vibroplex key has 3/16 contacts and is available for lefthand operation, \$2.50 extra.




THE VIBROPLEX CO., Inc., 833 Broadway, New York 3, N. Y.

W. W. ALBRIGHT, President

IF YOU SEND YOU SHOULD USE THE VIBROPLEX

Buy Vibroplex for the easiest sending of your life

Certified Performance

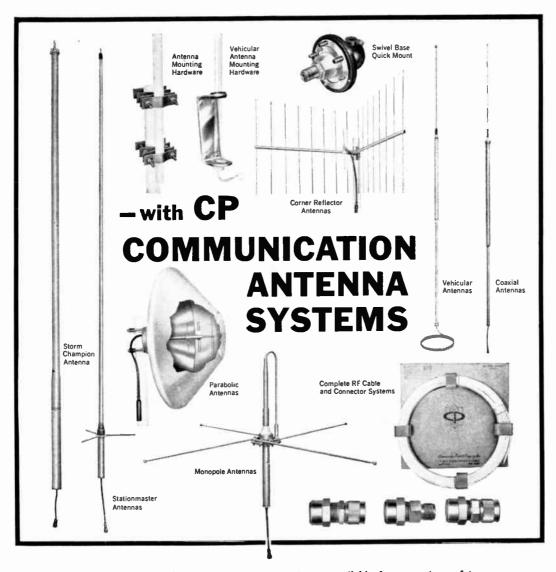

CP "certified performance" components are available for every type of two-way communication installation. Specify CP for base station and vehicular antennas, coaxial cable systems, hardware and accessories. Consult CP for recommendations on your specific requirements.

New catalog available! Contains complete information on CP antennas and accessories plus a handy technical data section. Write on company letterhead for your copy, today!



COMMUNICATION PRODUCTS COMPANY, Suc. COMMUNICATION ANTENNA SYSTEMS FOR AMERICAN BUSINESS MARLBORO, NEW JERSEY, U.S.A. - Telephone; HOpkins 2-1880 (Area Code 201)





6th Edition

RADIO OPERATOR'S LICENSE Q & A MANUAL

-by Milton Kaufman-

Completely up-to-date to Mny 15, 1961 with new supplement. All FCC question revisions and question re-numbering.

More people have earned their commercial radio licenses with this famous book than with any other available today. —It is the best book for other available today. —It is the best book for FCC license preparation! It is just as indispensable to anyone who desires a commercial 'ticket' as it is to the licensed operator, as a reference volume. Truly, it is a book anyone interested in radio operation can't afford to be without. The Q&A Manual covers elements 1 through 8. It is the only book giving the question—the answer and a detailed follow-through discussion on every vital technical question in the FCC Study Guide. This makes it very easy to answer correctly multiple choice questions!

It is so effective as a teaching aid that it is the It is so enecure as a teaching and that it is the standard text in schools teaching commercial radio operating as well as by industrial organizations. All fundamentals required for all kinds of commercial licenses are included. Numerical examples in the follow-through discussion show how problems are solved and answers arrived at. There are many illustrations to make the technical questions and answers picture-clear. The manual is based on government study guide and supplementary FCC releases. In every regard,

there is no equal to this book. Here is what leading publications in the communications field say about the Q&A Manual. "Thorough treatment"—QST.

up-to-the-minute . . presentation Method is clear, logical and easy to read . ."
WIRE AND RADIO COMMUNICATIONS.

#130, Cloth Bound, 736 pp.Only \$7.10

Get it at your electronic parts distributor ar backstare, ar order direct from





Amateur Net \$675.

TRANSMITTER FOR 6 & 2

Have vou heard about these new Clegg advances in VHF?

Spectacular advances in the field of electronics in recent years are presenting outstanding opportunities to manufacturers and the serious VHF amateur alike.

Research and development at Clegg Laboratories have played a consistent role in the design and engineering of superior VHF equipment for the serious operators on these bands. From this continuing research have come such products as the Clegg ZEUS transmitter for 6 and 2 meters, the INTERCEP-TOR VHF receiver, the 99'er transceiver for 6 meters, and the 2 x 4 audio oscillator.

Each of these units is outstanding in its field. The ZEUS, for example, provides 185 power-packed watts on both 6 and 2 meters. Automatic feedback control of low level speech clipping permits maximum talk power without splatter. The INTERCEPTOR receiver, using the latest nuvistors in r.f. stages, provides a noise figure of less than 2 db. and sensitivity of better than .25 microvolts.

The 99'er provides a complete VHF station for the ham with a limited budget.

Ask your distributor about these new Clegg VHF units today. Or write for complete information.

LABORATORIES

502 RT. 53, MT. TABOR, N. J. **OAkwood 7-6800**



Amateur Net \$139.95.

CLEGG 99'FR 6 METER TRANSCEIVER



FORT ORANGE Radio Distributing lam.

904 BROADWAY ALBANY 4 N. Y. U. S.A. AMATEUR HEADQUARTERS

Cable Address "Uncledave"

CALL ALBANY HE 6-8411

NITES GR 7-5891

NOW THAT LONG WINTER EVENINGS ARE COMING, YOU WILL WANT THAT SHACK OF YOURS TO BE IN SHAPE TO HANDLE THE INCREASING ACTIVITY OF THE BANDS WITH THIS HALLICRAFTERS EQUIPMENT



MODEL HT-37. The HT-37 has been carefully engineered ta give yau the best phasing unit at a maderate price. Camplete tabletap high effi-



MODEL HT-41.

Truly a ham's dream! The HT-41 linear amplifier is an ideal companion for the HT-37 in price, style, and performance. Complete coverage 80 thru 10 meters; adjustable

pi-network output; all circuits metered; built-in R.F. output meter ta aid tune-up; standby bias supply. High efficiency, grounded-grid circuit; new 7094 beam-pawer. \$395.00



MODEL HA-4 "T. O. Keyer." "The Stradivarius of Electronic Keyers." Hallicrafters offers this equipment for the discriminating e.w. operator who wants perfection. The



MODEL S-120. Anather papular Hallicrafters precisian-built receiver with many desirable features: Cavers braadcast band 550-1600 kc. plus three shart-wave bands 1600 kc-30 Mc. Slide



MODEL SX-115.
This is a new tripleconversian heterodyne
type communication
receiver. Combines
highest accuracy, stability, sensitivity; linear
tuning, constant tuning
rate, built-in 100 Kc
crystal calibrator, sen-

sitivity less than 1 micravolt, selectable side bands, image rejection better than 60 db. band gain equalization, audia inverse feedback, and many other features. Covers nine 500 Kc segments.

3.5- 4.0 Mc 7.0- 7.5 14.0-14.5

21.0-21.5 28.0-30.0 (4 segments) WWV

\$595.00



MODEL HA-5 DELUXE VFO. High stability heterodyne-type for all bands. Three tubes plus voltage regulator and silicon rectifiers. Extreme stability. Illuminated dial calibrated for all amateur bands, 80 through 2 meters. Output

frequency range: 3.5 Mc. to

4.0 Mc., 7.0 Mc. ta 7.5 Mc.,

7.8 Mc. to 8.3 Mc., and 8.333 Mc. to 8.833 Mc. Excellent keying; 30 ta 1 tuning ratio permits precise tuning \$79.95

Write Uncledave W2APF with your needs and problems. TRADE-INS ACCEPTED AND FOREIGN TRADE SOLICITED BANK FINANCING

TIME PAYMENTS 18 Months to pay. Life

UNCLE DAVE'S
RADIO SHACK
A SUBSIDIARY OF
FORT ORANGE RADIO

air dux

AIR WOUND COILS






air dux®BALUN

Unbalanced caax lines used an mast transmitters can be matched to balanced lines af either 75 ar 300 ahms impedance by using the B2009 air dux cails. May be used with transmitters and receivers withaut adjustment over the frequency range of 80 through 10 meters, and will handle pawer inputs up to 200 watts.

 Illumitronic has the most complete line of PLASTIC ROD. TUBING and SHEET.





Cail with hardware Maunting plate



Standard Air Dux!

A wide selection is available from Jobbers nationally.

Also HARNESSING and CABLING materials:



2 new pi dux assemblies

The 500 and 1000 watt pi dux assemblies are campact yet conservatively rated. The high frequency cail sections are silver plated for high tank circuit efficiency. A camplete technical sheet is included with each assembly.



1 KW pi dux

#195-1 500 watt pi dux Assembly #195-2 1 KW pi dux Assembly

indented pi dux®

ZIPPERTUBING SPIRAL WRAP SPIRAL COVER VINYL SLEEVING LACING CORD CABLE CLAMPS



Length of Colf L uh. Cat. No. Dia 816A 18 3% 18.0 1014A 18 225/32 18.3 23/4 25/8 1212A 18.3 1411A 18.0 1609A 18.1 2007A 12 18.6 2406A 187





vari-pitch pi dux®

	-	-			
820D10	3	20 & 10	18	31/4	18.0
1212D6	11/2	12 & 6	14	313/16	18.6
1608D6	2	8 & 6	12	41/8	18.1
2008D5	21/2	8 & 5	12	33/4	18.2
2408D4	3	8 & 4	10	33/4	18.6

illumitronic

sunnyvale,



california

engineering

Special Designs?

That's our business! We now supply a majority of the air wound coils used by leading equipment manufacturers.

EXPORT DEPT : 15 MOORE ST., NEW YORK 4, N. Y. CABLE ADDRESS: MINTHORNE - NEW YORK, TEL. BO 9-6272 CANADIAN REP .: LEN FINKLER CO., TORONTO



Amateur Accessories always available at ARROW



TX-86, ONE OF THE MOST VERSATILE HAM XMTRS EVER MADE

90 W. CW, 90 W peak Phone 80 through 6 meters, easily adjusted for notice use
Mobile or fixed use, size: 5" x 7" x 7"
Xtal controlled or can take VFO
Final 6146 runs straight through on Pi-net output ckt, TVI suppressed

\$84⁹⁵ Complete kit, specify 6 or 12v fil.....

\$10995

MODEL PS-3 AC POW, SUPPLY FOR TX-86 Completely wired and tested \$44.95

AC-1, NOVICE CW XMTR

Xtal controlled for 40 and 80 meters CW Pi-net output ckt, TVI sup-


Includes heavy duty AC Power

Supply 15 w. input; 6V6 osc., 6X5 rect.

Mod. AC. i complete kit for any 1 band Extra coil kit for other band



\$19⁹⁵

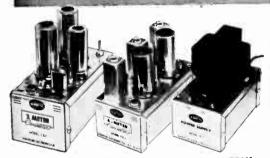

& 6 METER CONVERTERS & POWER SUPPLY

Features included on both models: Crystal Controlled Crystal Controlled RF Rejection: over 70 db spurious & image Gain: over 30 db

IF Rejection: over 100 db

Noise Figure: better than 4 db Tube Lineup: 2 meter Converter has new, imported 6ES8 high gain, low noise, cascode 1st RF Amp., 6U8A 2nd RF Amp. & Mixer, 6J6 Osc.—Multiplier.

6 meter Converter has 6BSS Cascode RF Amp and 6USA Mixer and Osc. 6 meter 2 meter 6 meter 2 meter Model Model

Converter complete with tubes and stal for 7-11 or 14-18 mc. IF output in Kit form with instructions Wired and tested CB-6 CB-2 \$19.95 \$23.95 \$27.50 \$33.95

Kit or Wired models for any other output frequencies (30.5-34.5 mc, 28-30 mc, etc.) \$1.00 extra Power Supply for CB-6 or CB-2

Mod. PS-1K, Kit Mod. PS-IW. Wired and Tested



LEARN CODE & THEORY FAST



TRANSISTORIZED CODE PRACTICE OSCILLATOR AND MONITOR

Serves as code practice osc, and phone-CW monitor without making any changes. Builds into small 2-piece satin finish copper case. Power required: 2 Eveready #912 cells.

\$485 CPS.MTK kit \$575 CPS.MTW wired



CODE PRACTICE OSCILLATOR, KITS

Available in kit or wired form. Produces a pure, steady tone without clicks or chirps. Will handle a large number of headphones or keys. Converts easily to an excellent CW monitor. Variable tone control and volume control. Built-in 4" speaker. Operates on 110 volts AC or DC.

Ameco No. CPS-KT—Kit, including tubes. Net Each...\$13.75

AUTHORIZED DISTRIBUTORS OF **ELECTRONIC PARTS & EQUIPMENT**

Arrow's Export Dept. Ships To All Parts Of The World

ARROW_ELECTRONICS

65 Cortlandt Street, New York 7, N. Y. • Digby 9-4730 525 Jericho Turneike, Mineola, N. Y. • Ploneer, 6:8686 Trade-ins Welcomed

Your old equipment is worth money at Arrow. Get Arrow's deal before you buy.

With SPRAGUE CAPACITORS and RESISTORS you build Reliability into your equipment!

CAN-TYPE ELECTROLYTICS



Twist-Lok® Capacitors

Hermetically sealed in aluminum cases. Withstand high temperatures (85°C), high surge voltages, high ripple currents.



Screwbase Capacitors

Aluminum cases, Will withstand high a-c ripple. Available with lugs or Insulated wire leads. Common or separate negative terminals.



High µF Capacitors

Molded phenolic cases. Ratings to 10,000 μ F. Designed for low voltage (to 50V) filter circuits.

TUBULAR ELECTROLYTICS



Atom® Capacitors

Tiny, dependable single or multiple section units. Have low leakage, long shelf life. Metal case construction with outer Kraft tube.



Littl-Lytic® Capacitors

Ultra-small, excellent for transistorized circuitry. All-welded construction-no pressure joints to cause 'opens". Low leakage, extremely long shelf life.

HYPASS® CAPACITORS



Exclusive 3-terminal feed-thru units which effectively by-pass vhf cur-rents. Suppress TVI from transmitters, diathermy, line-conducted radiation, etc.

PAPER-FILM TUBULARS



Black Beauty® Capacitors

Dual dielectric (polyester film and paper) combines best features of both. Solid impregnant, nothing to leak or drip. Molded case. Withstand high temperatures, high humidity.



Orange Drop® Capacitors

Dual dielectric (polyester film and paper), with solid impregnant. Double dipped in epoxy resin. Radial leads. ideal for printed wiring boards.

OIL CAPACITORS



Rectangular Oils

For transmitter power supplies and other high voltage applications. Hermetically sealed in rugged metal cases. Oil-impregnated, oilfilled. High insulation resistance.



Screwbase Oils

Cylindrical screwbase can for easy single hole mounting. Oil-impregnated, oil filled. Small size, will fit tight spaces.

SK-1 SUPPRESSIKIT®



Contains everything needed for effective mobile radio noise suppression of R-F interference beyond 400 mc. For autos with 6 or 12 V gen-

For complete data on these and other Sprague components, get Catalog C-614 from your Sprague Distributor, or write to Sprague Products Company, 505 Marshall St., North Adams, Massachusetts.

CERAMIC CAPACITORS



Cera-mite® Ceramics

Silvered flat-plate design for high by-pass efficiency, high self-resonant frequency. Tough moisture-proof coating. Available in general application. high-K, temperature stable, and temperature-compensating types.



Buttonhead Ceramics

Flat-disc capacitor element sealed in top of hex head for easy screw-mounting. Low self-inductance, high selfresonant frequency. Available for by-pass or feed-thru applications.

MICA CAPACITORS



"Postage-stamp" Micas

Silvered (\pm 5% cap.tol.) or standard (\pm 20% cap. tol.). Carefully-selected, electrically graded raw mica assures maximum quality



Transmitting Micas

Voltage ratings to 2500 WVDC, 5000 V Test. R-F current tested before and after molding.

WIREWOUND RESISTORS



Koolohm® Resistors

Insulated shell power resistors wound with ceramic-insulated wire. Completely moisture-proof. Ratings to 120 watts in inductive and non-inductive types.



Blue Jacket® Resistors

Vitreous enamel coating guards against humidity and failure from electrolysis. Ratings from 2 to 10 W.

world's largest capacitor manufacturer

EARN ONEY BIG MONEY

MOBILE-RADIO MAINTENANCE

Get into this rapidly growing field with 2nd Class Ticket and LAMPKIN MOBILE-SERVICE METERS



LAMPKIN 105-B MICROMETER FREQUENCY METER

I'REQUENCY RANGE on local transmitters 0.1 to 175 MC – to 3000 MC by measuring in multiplier stages. ACCURACY conservatively guaranteed better than 0.0025%—actually 9 out of 10 results come within 0.001%. CALIBRATION table for each meter; charts show percentage off-frequency from FCC assignment. DIAL 4" diameter, 40 turns, totals 8000 divisions spread over 42 feet—resettable better than 5 parts per million. CRYSTAL thermometer on panel automatically indicates dial checkpoint. SIGNAL GENERATOR—a pinpoint CW source for mobile-receiver final alignment.



LAMPKIN 205-A FM MODULATION METER

FREQUENCY RANGE — Continuous 25 MC to 500 MC. No coils to change. Rough and vernier tuning controls. PEAK FM swing shows directly on indicating meter—calibrated 0-12.5 or 0-25.0 peak KC, positive or negative. No charts or tables. ACCURATE—within 10% at full scale. FIELD STRENGTH METER—Reads relative transmitter output. PROTECTED—Panel components recessed behind edges of the case, PORTABLE—Just a 2-finger load.

JUST THESE TWO METERS—WITH NO ADDITIONAL CRYSTALS OR FACTORY ADJUSTMENTS—WILL CHECK FREQUENCY AND FM MODULATION ON HUNDREDS OF TRANSMITTERS. LAMPKIN METERS ARE PREFERRED TEST EQUIPMENT—BY MUNICIPALITIES, 46 OUT OF 50 STATES, BY MOST 2-WAY RADIO MANUFACTURERS, AND BY THOUSANDS OF INDEPENDENT MOBILE-SERVICE ENGINEERS.

NEW . THE PPM METER . AN ACCESSORY FOR THE TYPE 105-B . ACCURACY BETTER THAN 0 0001%, AMPLE FOR SPLIT-CHANNEL FREQUENCY CHECKS.

FREE BOOKLET—with facts and figures—send for "HOW TO MAKE MONEY IN MOBILE-RADIO MAINTENANCE".

MAIL COUPON TODAY!

LAMPKIN LABORATORIES, INC.
BRADENTON, FLORIDA

Measurements Section Lampkin Laboratories, Inc. Bradenton, Florida

At no obligation to me, please send

- ☐ "Haw To Make Money in Mobile-Radio Maintenancel"
- ☐ Technical data and prices on Lampkin Meters

lame_____

City_____

Zone___State__

World Radio Histor

DIRECTIONAL RF WATTMETERS



Model 43 and Rigid Line Series

Direct reading . . . "thru" type measure forward or reflected power in complete systems under operating conditions . . . inserted between transmitter and antenna or load . . full scale power and frequency range determined by plug-in elements.

50-Ohm nominal



		ELEMENTS				
Model	Connectors	Frequency (mc)	Power Ranges			
		2-30	50, 100, 250, 500 1000 watts			
43	QC Type#	25-60; 50-125; 100-250; 200-500; 400-1000	5, 10, 25, 50 100, 250, 500 1000 watts			
4712 4715°	1 % " EIA Flanged	2-30; 25-60; 50-125; 100-250; 200-500; 400-1000	.25, .5, 1, 2.5, 5KW			
460 4610°	31/8" EIA Flanged	2-30; 25-60; 50-125; 100-250; 200-500; 400-1000	1, 2.5, 5, 10, 25KW			
4902	61/8" EIA Flanged	2-30; 25-60; 50-125; 100-250; 200-500; 400-1000	2.5, 5, 10, 25, 50KW			
4910	9" Flanged	Per Customer Specifi	cations			

Double Socket Thruline for monitoring of forward and reflected power.

to measure rf power... THRULINE

TERMALINE ... to absorb rf power

Model	Freq. Range	Max. Power	Power Range Scales	Input Connector
6254	30-500 mc	1 w	25, 50, 100, 250, 500 and 1000 milliwatts	Female "BNC"
61	30-500 mc	80 w	Choice of two compatible scales. Lowest .5 watt	Female "N"
611	30-500 mc	60 w	Duat Range 0-15/60 w	Female ''N'
612	30-500 mc	80 w	Dual Range 0-20/80 w	Female ''N''
67	30-500 mc	500 w	0-25/100/500 watt	Female ''N''
694	2. 30 mc	1000 w	0/1000 watt	QC Type∗
6835	30-500 mc	1200 w	0-120/600/ 1200 watt	QC Type★
67C*	30-500 mc	2500 w	0-100/500/ 2500 watt	Female "N"

*Water Cooled on High Range

Model	74	718	72R	72-2	
Positions	Six	Eight Reversing Switch		Two	
Coaxial Circuits	One	One	Two	Two	
Connector	models	to receive U	ectors are stand IG-21/U series cables and c	plug. Use	

Model	Max. Power	Frequency Range	*Max. VSWR	Input Connector
80 Series	5 w	0-4 KMC	1.25	Male or Female, N; C; BNC
80 A	20 w	0-2 KMC	1.2	Female "N"
8130	50 w	0-4 KMC	1.2	QC Type★
818	80 w	0-4 KMC	1.2	Female "N"
8135	150 w	0-4 KMC	1.2	QC Type#
82A	500 w	0-3.3 KMC	1.2	Female "N"
8201	500 w	0-2,5 KMC	1.25	QC Type★
8833	1000 w	0-2.5 KMC	1.25	QC Type±
8813	1000 w	0-2.0 KMC	1.25	1% EIA Flanged
888	1200 w	0-2.0 KMC	1.25	31/ EIA Flanged
8890	2500 w	0-2.5 KMC	1.25	QC Types
82C**	2500 w	0-3.3 KMC	1.2	Female "N"
8950***	5000 w	0-2.5 KMC	1.25	OC Type★

Other water-cooled loads up to 50KW can be supplied.

*VSWR is 1.1 or less to 1000 mc on all models — with ''N'' connectors,

Water Cooled *Forced Air

★QC TYPE: Bird Quick-Change Connector, designed for rapid change. Available in following types:

Available in following types:
Female or Male N, C, HN, BNC, LC, LT,
UHF, and 7/8" EtA flanged.

Complete Specifications on request.







RF ABSORPTION WATTMETERS

Portable -- Non Radiating

Portable . . . direct reading . . . non-radiating "load" type wattmeter . . . used in field or laboratory to measure and absorb power . . . accuracy ±5% of full scale . . VSWR 1.1 to 1 maximum over operating range.

COAXWITCH

COAXIAL SELECTOR SWITCHES

Dependable, manually operated switches for selecting antennas, receivers, transmitters or other apparatus with coaxial connections. Ideal as a system component in electronic equipment where reliable, repeated channel switching is required; pull knob, rotate, and push in to make contact.

TERMALINE

RF LOAD RESISTORS

Quick-Change Connectors

Reflection-free terminations for 50-ohm coaxial lines . . . low VSWR . . . non-radiating . . . water cooled rating 2500 W to 50 KW . . air cooled rating to 2.5 KW . . forced air to 5 KW. Quick-Change Connectors (*QC Type) available on many models.

COAXIAL RF FILTERS

Our extensive engineering and manufacturing facilities are at your command for the custom design and manufacture of filters to your specifications. Intelligent design, skillfull manufacture assure you of highest performance and reliability. New miniature filters, as light as five ozs., are available and can be produced in quantity.

ELECTRONIC CORPORATION


30303 Aurora Rd., Cleveland 39 (Solon), Ohio CHurchill 8-1200 TWX CGN FS 679

Western Representative:
VAN GROOS COMPANY, Woodland Hills, Calif.



COAXIAL RELAYS

4 different models, A.C. or D.C.

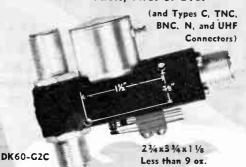

DK60 SERIES RELAYS PRICED FROM . . . \$12.45

See any one of our 700 Dealers and Distributors in U. S. and Canada for catalog sheets or write:

STANDARD RELAYS INCLUDE:

DK60 - SPDT r.f. switch.

DK60-G i0-G — SPDT r.f. switch with special "isolation" con-nector in de-energized position.

DK60-2C - SPDT r.f. switch with DPDT auxiliary contacts. DK60-G2C — SPDT r.f. switch with DPDT auxiliary contacts and special "isolation" connector in de-energized position.

- ★ Relays available in weatherproof boxes for exterior installation.
- Ganged, multiple position switch arrangement available for remote control selection of antennas.
- Unconditional guarantee for period of one year. (We will repair if faulty within one year.)

r.f. SPECIFICATIONS:

r.i. Specifications:

Low VSWR: less than 1.15:1 from 0 to 500 mc. Low

Losses: Pure silver contacts. Parts in crucial positions
plated with fine silver. Low Cross-Talk (greater than 80
db) (in energized position) in DK60-GG and DK60-G2C

through use of patented "isolation connector". High Power
Rating: (a) 1 kw through straight connectors (b) to 10w

through "isolation connector"—excellent for video switchlog. SPDT r.f. Contacts: r.f. leakage extremely low, below typical r.f. connectors.

MECHANICAL SPECIFICATIONS:

High Contact Pressures: Long life expectancy greater than 1 million operations. Continuous Duty: Teflon feed-through terminals used on coil to provide connection ease.

ELECTRICAL SPECIFICATIONS:

Wide Variety of Coil Voltages: 6.12.24.32.48.110.220 D.C. volts at 2.0 watts; 6.12.24.110.220 A.C. volts at 6 voltamps, 50-60 cps. (Special voltage or resistance available on request.) Less Than 50°C Temperature Rise Above Amblent: Maximum operating temperature is 100°C except on special order. Auxiliary contacts available for power control—DPDT at 5a. 110 v A.C. on DK60-2C and DK60-G2C.

Manufactured by DOW-KEY COMPANY. Thief River Falls, Minnesota



TRANSISTORIZED TELEPHONE INTERCOM SYSTEM

Model SA-10W

\$23.95 2-unit set



Ideal for few feet or up to 9 miles. Each phone has separate red button, which when depressed sends pleasing signal tone; black button for talking. Receiver is transistorized crystal unit; transmitter is carbon unit. Each unit has spiral phone cord. Operation requires no switching. Use several units tagether, Imported,

ALCO R.F. FIELD

STRENGTH METER Single Band I to 250 MC.

\$6.95

Model PSI-1 21/16 x 31/16 x 11/16" Compact! Sensitive! Checks antenna efficiency, Campact! Sensitive! Checks antenna efficiency, lood matching, etc. Requires no battery or other power source. RF measured on accurate meter. Telescoping antenna ta 103½", Earphane jack provided for monitoring; case has powerful magnet ta grip fender, etc. Imported.

SEND FOR FREE CATALOG Available direct or through your local distributor



GRID DIP METER WIRED - READY TO USE

Completely calibrated Freq. coverage 1.5 to 300 MC in 6 ranges

\$36.99

Ronges color-coded to motch coils, undomped 1 MA meter. Variable sensitivity control for op-timum grid current adjustment. Calibrated dial, adjustable hairline, allows precise accuracy, Phone jack permits use as modulation monitor. Oscillator tube is 6AF4. 6½ x 31/₈ x 11/₂". 6 cails supplied. 117V, 50-60 cps. 2 lbs. Imported.

WITH FREE LEATHER CASE

Model TS-60

20,000 ohms per volt MULTITESTER

– 20,000Ω/V

- High sensitivity New design; wide scale arc Campares with $4\frac{1}{2}$ " meter Measures $3\frac{1}{4}$ "W x $4\frac{1}{2}$ " meters
- Compact black bakelite case

DC V. ranges: 5-25-250-500-2500 DC V. ranges: 10-50-100-500-1000 @ 10,000Ω per V. DC current: 50 μα, 2.5 ma. Imported



ELECTRONIC PRODUCTS, INC. Dept. 666 - 3 Wolcott Ave., Lawrence, Mass.

PENTA

HIGH-EFFICIENCY

POWER TUBES

Penta power tubes are used by the leading manufacturers of amateur, commercial, and military communications equipment. Follow the example of those who know the wisdom of using only the best. Specify Penta tubes whenever you want long life, reliability, and maximum efficiency.

	Fil. Volts	Fil. Current Amps.	Plate Diss. Max. W.	Plate Voltage Max.	Plate Current Ma. Max.	Screen Voltage Max.	Price
PL-172 BEAM PENTODE	6.0	8.2	1000	3000	1000	600	\$135.00
PL-175A BEAM PENTODE	5.0	14.5	400	4000	350	800	\$ 50.00
PL-177A BEAM PENTODE	6.0	3.2	75	2000	175	600	\$ 29.00
PL-6549 BEAM PENTODE	6.0	3.2	75	2000	175	600	\$ 29.00
PL-4E27A BEAM PENTODE	5.0	7.5	125	4000	200	750	\$ 45.00
PL-4D21 POWER TETRODE	5.0	6.5	125	3000	225	600	\$ 36.00
PL-4D21A POWER TETRODE	5.0	6.5	175	3000	225	600	\$ 37.50
PL-5D22 POWER TETRODE	5.0	14.5	250	4000	350	800	\$ 46.50
PL-4-65A POWER TETRODE	6.0	3.5	65	2000	150	600	\$ 27.00
PL-4-400A POWER TETRODE	5.0	14.5	400	4000	350	800	\$ 48.00
PL-4-1000A POWER TETRODE	7.5	21.0	1000	6000	700	1000	\$132.00
PL-250R RECTIFIER	5.0	10.5		60,000	250		\$ 36.00
	Fil. Volts	Fil. Current Amps.	Plate Diss. Max. W.	Plate Voltage Max.	Plate Current Ma. Max.	μ	Price
PL-254W POWER TRIODE	5.0	7.5	100	4000	225	25	\$25.00
PL-6569 POWER TRIODE	5.0	14.5	250	4000	300	45	\$37.50
PL-6580 POWER TRIODE	5.0	14.5	400	4000	350	45	\$45.00





PL-175A Beam Pentode



PL-177A Beam Pentode



PL-4E27A Beam Pentode



PL-4D21A Power Tetrode



PL-5D22 Power Tetrode



PL-4-65A Power Tetrode



PL-4-400A Power Tetrode



PL-4-1000A Power Tetrode



PL-6569 Power Triode



PL-6580 Power Triode



PL-184A Socket and Chimney

Santa Barbara, California


FIELD ENGINEERING REPRESENTATIVES AND DISTRIBUTORS SERVING MAJOR CITIES. For further information write for complete Penta catalog.





FOCAL POINT

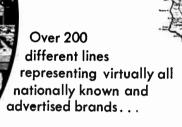for the newest and finest equipment for the radio amateur



Liberal trade-in allowances...

An excellent time-payment plan...

Courteous, friendly service by our staff which includes over fifteen licensed radio amateurs...

A complete, well staffed department to give you excellent service on your mail orders.





great response

Naturally. This smart ham is using a University Model 70. It's dynamic! Now his QSO's are more frequent with better quality. You'd be surprised at the compliments he gets. He's also improved his SSB transmissions... found the perfect budget-minded way to increase peak power and intelligibility. And he doesn't have to swallow this microphone to be heard. All he does is sit back, relax and speak normally. The Model 70 does the rest. Why not let it do the same for you. Comes complete with integral 15-foot 3-conductor shielded cable, Model SA10 slide-on stand adapter and cloth carrying bag. Check the 'specs'. No other dynamic of its type can match the great Model 70! Only \$29.95*

SPECIFICATIONS


Frequency Response: 50-14,000 cps (which extends to a usable limit in the 18,000 cycle region). Impedance: 30/50; 20,000 ohms. Output Level: 30/50 ohms: —50 db/1 mw/10 dynes/cm²; —143 db E1A sensitivity rating; 20,000 ohms into high impedance input: 28 mv/10 dynes/cm². Hum Reference: —120 db/.001 gauss. Dimensions: 1-5/32" maximum diameter, 6" maximum length. Shipping Weight: 2½ lbs. Finish: Acrylic silver-gray and non-reflecting black.

*Model 71 also available with on-off slide switch \$34.95.

Write for new 12-page catalog with complete details on the entire University Modular Microphone line. Desk 00-11 University Loudspeakers, Inc., 80 South Kensico Ave., White Plains, New York.



Laboratory Standards

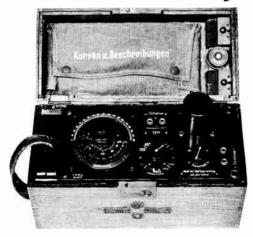

A SOUVENIR OF WORLD WAR I

TELEFUNKEN WAVEMETER TYPE K.W. 61g

Frequency Range: 40 kc-2000 kc

Accuracy: 5%

This instrument was calibrated just 23 days before the end of World War I

THE BEST THERE IS TODAY —

MEASUREMENTS' NEW MODEL 760 STANDARD FREQUENCY METER

Frequency Ranges: 25-50 mc

150-175 mc 450-475 mc

Accuracy: at 25 mc .0004%

at 475 mc .00002%

with crystal adjusted

to WWV

Crystal: oven temp. controlled



Price **\$980.00** F.O.B. Boonton

SINCE 1939 — MANUFACTURERS OF FINE PRECISION ELECTRONIC TEST EQUIPMENT

Measurements "FAMOUS FIRSTS" Include:

- First commercial signal generator with built in tuning motor
- · First commercially produced electronic peak voltmeter
- · First commercially built pulse generator
- World famous Megacycle Meter, covering 100 kc to 940 mc
- First commercially successful FM testing equipment designed especially for Mobile Communications
- And now a completely new concept of frequency measurements

Write for complete catalog

MEASUREMENTS

A McGraw-Edison Division

BOONTON, NEW JERSEY

National Master Mobile

RME Electro Voice



BIG NAMES

IN AMATEUR EQUIPMENT
IN STOCK AT

HEADQUARTERS



SHOP OF AMERICA'S LARGEST COMPLETE RADIO SUPPLY HOUSES

Everything in electronics...you name it—we have it!
Every known and trusted brand...every type of radio
equipment and parts always in stock to assure you of
prompt service and delivery. We ship around the Globe
...guaranteed complete satisfaction on all orders.

Call or write about your needs. Near new and used equipment. List sent on request.

TRADE IN your old equipment for Liberal Allowance.

CONVENIENT CHARGE PLAN — 10% DOWN



FREE

LARGE, FULL SIZE
WORLD WALL MAP
SHOWING RADIO PREFIXES AND

TIME AROUND THE GLOBE
Send 50¢ in coin for your wall map. Enjoy the thrills and fun of contacting more than 2,000,000 licensed statlons all over the world. 50¢ will be refunded with your next order.

RCA)
ELECT

Autopoducts

antenna products







FOR SPEEDY SERVICE call or write

Joe Hotch, KØUFE, Manager

Hamateur Dept.

•	Includes: listening	to S.W.	broadcast,	ship	to	shore,	etc.;	also	more	than	390,000
	amateurs-potentia	1 QSOs fo	r you.								

*Copyright, 1960

-USE THIS COUPON TODAY FOR FREE MAP ----Gentlemen: I am enclosing 50c in coin — Please send me map. I understand 50c will be refunded with my first order.

NAME.

ADDRESS

CITY
I am interested in the following equipment.

☐ Send me literature and price list

HB-62

THE Lew & Bonn

LEADERS IN ELECTRONICS FOR MORE THAN 35 YEARS COMPANY

STATE

1211 LaSalle Avenue • Minneapolis 3, Minn. FEDERAL 9-6351



TWO-WAY RADIO

communications equipment

VHF-FM FOR:

AIRCRAFT MARINE MOTORCYCLE PORTABLE BASE

VHF-AM FOR: AIRPORT VEHICLES GROUND STATIONS

ANTENNAS REMOTE CONTROLS **ACCESSORIES**



NEW! "680 BASECOM"

FOR VHF-FM TWO WAY MOBILE RADIO

the new 680 series offers

HIGH PERFORMANCE at **MODERATE COST with** LOW MAINTENANCE!



"680" FEATURES AND OPTIONS:

- * PROVEN PERFORMANCE . . . all the outstanding features of the popular "580" series, plus the following.
- ★ HIGH POWER... 100 watts output 25 to 50 mc, 75 watts 144 to 174 mc, both base and mobile
- ★ TONE SQUELCH . . . two way tone squelch compatible with other systems to EIA standards.
- ★ Meets all FCC and OCDM requirements.
- * SIMULTANEOUS RECEPTION ... dual front end receiver for monitoring two frequencies anywhere in the band.
- ★ TRANSMITTER FILAMENT SWITCH . . . re-
- duces battery drain when on "stand-by".

 MONITORS REMOTE CONTROL ... base station monitors remote transmissions. Intercom provided. All functions available at remote position.

680 FLEETCO

COMBINATION

- MOBILE CONTROL HEAD
- SPEAKER
- TRANSISTOR 'POWER SUPPLY

ATTENTION DEALERS! Write for available territories. 188



DESIGNERS AND MANUFACTURERS OF

RADIO COMMUNICATIONS EQUIPMENT

FOUNDED 1938

CORAL GABLES. MIAMI 34, FLORIDA

BARRY ELECTRONICS

HIGH VOLTAGE PLATE TRANSFORMER:

Input: 115 VAC @ 60 CPS.
Secondary: 3000-2500-0-2500-3000 VAC @ 350 Ma.
Insulated for 10 KV. New, factory lopen-frame)
construction.

Size: 5"H x 7"W x 6-1/2"D. Wt: 25 lbs.

\$34.95 VERY SPECIAL . . . ONLY

VHF TRANSMITTER:

Perfect for 2 meter and/or 1-1/4 meter conversionlate, modern design. Uses two 6201's into single Amperex 6360 twin Tetrode. Xmtr only 4" x 4" x 11". Only 3-3/4 lbs. Complete with 10-1/2" chrome antenna. Furnished complete with A and B Battery pack, & connection cable and schematic & conversion info. with case: Battery weight: 23 lbs.

RCA PRECISION 500 KC CRYSTAL OSCILLATOR:

Accuracy plus 'or minus 0.0012%. Contains Precision 500 KC crystal, BMS Labs Crystal oven, 5840 subminiature tube. Hermetically sealed nickel plated

rectangular case. Mounts in standard 7 pln miniature socket. Requires 6.3 VAC or DC, 75 to 100 V.D.C. With schematic, RCA Type A8838300-1. Size: $4-1/2^{\prime\prime}$ H x $1-7/16^{\prime\prime}$ W x $1-1/8^{\prime\prime}$ D. Wt: 1 lb. Cat.

#4-500 CRV. (Orig. Govt. Cost: \$172.00)

PRICE: \$15.00 with all tubes.

(We can ship without battery - same price \$15.00).

HI-VOLTAGE DYNAMOTOR:

Input: 12.6 VDC.

Output: 700 VDC @ 260 Ma.

Brand new. Compact. Mfd. by Sangamo. Looks just like famous Carter compact Dynamotor. With mounting brackets. \$13.95

2.5 KW MODULATION REACTOR TRANSFORMER:

Primary Impedance: 12,000 Ohms.
Secondary Impedance: 7500 or 5000 Ohms.
Made for use with single power supply for Class B
Audio and Class C R.F. For use with separate power
supplies; use one 5 to 10 Henry Choke and one
1 Mfd. capacitor. New original boxed. Net wt:
102 lbs. \$42.50

BRAND NEW MODEL 61720 FALLOUT DETECTION METER:

Lightweight, hand operated, detects and measures dangerous levels of radioactive fallout. Citizens version of the official fallout detection meter used by Office of Civil Defense. Unit is transistorized and runs on only 2 flashlight batteries. Measures gamma radiation dose rates as high as 500 roentgens per hour. Designed to be used in determining radioactive contamination levels that may result from an enemy attack. \$49.95

30 WATT MOBILE TRANSMITTER:

Uses 5618 crystal oscillator into CBS 5516 amplifier. Modern design. Only 7 lbs. net weight including bullt-in 6 V. vibrator power supply. Completely enclosed in aluminum cabinet 15-1/2"H x 7"W x 8"Dl. Furnished with crystal that doubles near 10 meter band. Will require slight and easy modification for 10 meter operation. A real beauty.

With tubes — \$11.95

JENNINGS UCS VACUUM VARIABLE CAPACITOR

Capacity: 10 to 300 Mmf. at 10 KV. Complete, less shaft. Originally sealed Jennings.

Government carton. Shpg. Weight: 5 lbs.

Reg. Net Approx. SALE PRICE:

\$141.00 \$49.00

\$3,75

COAXIAL CABLE

COAXIAL CABLE - FACTORY FRESH STOCK!

Туре	Nominal Impedance	Price Per 100'	Price Per 1000'
RG-8/U	52 Ohms	\$8.50	\$80.00
RG-8A/U	52 Ohms	12.00	115.00
RG-11/U	72 Ohms	8.00	75.00
RG-11A/U	72 Ohms	9.00	85.00
RG-58/U	52 Ohms	4.50	40.00
RG-58A/U	52 Ohms	5.00	44.00
RG-59/U	72 Ohms	4.50	40.00
RG-59A/U	72 Ohms	5.00	44.00

AUTHORIZED DISTRIBUTOR FOR:
NATIONAL, HAMMARLUND, JOHNSON, C-D,
WESTINGHOUSE, MOSLEY, B & W, CENTRAL
ELECTRONICS, TMC, AND OTHERS.

TUBE HEADQUARTERS OF THE WORLD!!! Complete inventory of Transmitting Special-Purpose, Radio, TV, Foreign, C.R. — 1st Quality Tubes, Name Brands Only. Guaranteed. Sensible Prices.

(We carry complete line of Westinghouse tubes).

WRITE FOR THE "GREENSHEET" CATALOG (excellent values on Ham Gear, components, equipment, electron tubes, etc.) A must for every Ham and buyer of electronic parts.

BARRY ELECTRONICS CORP.	DEPT. QA
512 Broadway, New York 12, N. Y.	
☐ Enclosed is money order or check	and my order.
Send copy of the Exciting "Greens	sheet" Catalog.
Name	Title
Address	
City	

INDUSTRY-PROVED SEMICONDUCTORS FOR YOUR HAM APPLICATIONS



PLUG-IN SILICON RECTIFIER CELLS
Ratings: to 500 ma -200 to 800 PRV. Diffused junction...high power capability (to 750 ma)...
lots containing standard clipholders and hardware also available ... 5M series.

Battlets 52.718



SO 500 KIT, TV REPLACEMENT


Rating: 500 ma at 130 vac. All-purpose silicon replacement kit offers radio-TV men simple means of replacing all existing silicon rectifier types. Hermetically sealed diode can be wired in or plugged into fuse-clip. To 100 C; needs no heat sink.

Buildeli IR 505



UNISTAC SILICON TV RECTIFIER
Rating: 750 ma at 130 vac. A direct and universal
replacement for all existing selenium stacks up to
500 ma. Eyelet construction. No "special socket,"
conversion kit or drilling required. Especially
suited to the elevated operating temperatures
inherent in most TV sets.

Bulletin TV-500

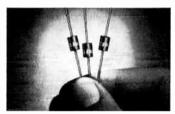


MINIATURE SILICON RECTIFIER CELLS
Ratings: to 750 ma – 200 to 600 PRV. High power
capability (to 750 ma) ... peak surge current
capacity (to 50 amps) ... ideal for TV diode
replacements ... 5A series.
Bullatus SR-212



SILCON RECTIFIER TUBE EQUIVALENTS
Ratings: 85 to 1250 ma - 1500 to 10,500 PIV. Highly reliable series of tube replacement rectifiers rated from 1500 to 10,500 PIV; 85 to 1250 na ofter the superior characteristics of silicon on a wide range of high voltage applications.


Bulletin SR-209

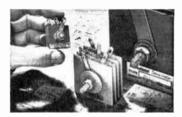

SELENIUM RECTIFIER STACKS

Ratings: From 100 ma te 50 amps. Low forward voltage drop and low leakage characteristics make this series ideal for a wide variety of power applications.

Bulletin SR-170

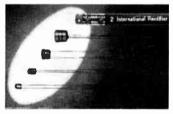

SUBMINIATURE SELENIUM DIODES
Ratings: to 28 ma – 48 to 384 PRV. High efficiency/
low cost diodes provide stable operation over
—50°C to +100°C range...reverse resistance
to 30 megohms at 30 volts...withstand 1 second
surges to 550 ma...1N1625 series.

Bulletis SR-163A



Ratings: Frem 250 milliwatts to 10 watts. A complete series including sub-miniature glass types, miniature single junction types, multiple junction types and double anode units.

250 and 400 mw glass types.* 750 milliwatt and 1 watt types, 35 and 10 watt types.*

Bulletins SR-265° and SR-260°°



Wide range of silicen and selenium types. Silicon solar cells with conversion efficiencies to 13%...silicon readout photocells with response times to 5 usec...selenium photocells in wide variety of sizes and shapes.

Bulletins SR-280 (Silicen) and PC-849 (Selenlem)

For complete technical data on these or other IR products, see your local IR distributor. He can supply you with most of these items right off the shelf.

INTERNATIONAL TORRESPONDENCIAS RECTIFIER

INTERNATIONAL RECTIFIER CORPORATION: EL SEGUNDO, CALIFORNIA • PHONE OREGON 8-6281 • CABLE RECTUSA

WORLD'S LARGEST SUPPLIER OF INDUSTRIAL SEMICONDUCTORS AND RECTIFIERS



or receiver to improve the noise figure and gain. Image and spurious rejection will also be improved as the Model PV has two tuned circuits. Compact, easily connected, low power requirements. Model PV with tube, wired and tested.

State which band

For any band, 80, 40, 20, 15 or 10 meters, the Ameco Modet PH Preamplifier has a better noise figure than most multiband receivers, 23 db. minimum gain, will improve image and spurious rejection with its two tuned circuits. Especially effective on 10 or 15 meters. Model PH with tube, wired and tested.

State which band Write Dept HB 62

AMERICAN ELECTRONICS CO HERRICKS ROAD, MINEOLA, L.I., N.Y.



The new deluxe "Cadillac" line of Ameco VHF Converters uses three RCA Nuvistors—two as RF amplifiers, the third as the mixer. This combination produces an extremely low noise figure, high gain, high image, spurious and IF rejection. These converters do not become obsolete as the output frequency is easily changed when a new receiver is acquired. The CN Converters are built on a compact (2"%2½"(x6¾") satin finished copper chassis. A gain control is included. Power requirements: 100 to 300V. at 30 ma. and 6.3V. at 1A. The Ameco PS-1 Power Supply is ideal, available in Kit form (PS-1K) at \$10.50 or Wired and Tested (PS-1W) at \$11.50.

Model CN-50W, CN-144W, CN-220W Nuvistor Converter, wired and tested for any one band (specify IF output).

Model CN-SOK, CN-144K, CN-220K Nuvistor Converter, in kit form, for any one band (specify IF output)\$31.95 Write Dept. HB-62

AMERICAN ELECTRONICS 178 HERRICKS ROAD, MINEOLA,



n o

2 0

0

10

S

ARE

CALL TERS A

ΣĒ



BIRTCHER

Tube / Transistor / Component / Cooling and/or Retention Devices

NOW AVAILABLE FROM AUTHORIZED DISTRIBUTORS FROM COAST TO COAST

KOOL KLAMPS

TOP HOLDING RETAINERS

TRANSISTOR RADIATORS

TUBE CLAMPS

TRANSISTOR CLIPS

DIODE RADIATORS

JAN SHIELD INSERTS

TYPE 2 TUBE CLAMPS

PRINTED CIRCUIT **BOARD RETAINERS**

CALIFORNIA, Gardena **Bell Electronics** FAculty 1-5802

CALIFORNIA, Los Angeles Bell Radio Supply PLeasant 3-4495

CALIFORNIA, Palo Alto Zack Electronics DAvenport 6-5432

CALIFORNIA, San Diego **Bell Electronics** BRowning 8-4350

CALIFORNIA, San Francisco Zack Electronics MArket 1-1422

CONNECTICUT, Hamden 14 Cramer Electronics ATwater 8-3581

D.C., Washington Capitol Radio Wholesalers Inc. HObart 2-0800

FLORIDA, Miami **Airwork Corporation** TUxedo 7-8253

ILLINOIS, Chicago 50 Merquip Electronics, Inc. AUstin 7-6274

MARYLAND, Baltimore 1 Wholesale Radio Parts Co. Inc. MUIberry 5-2134

MASSACHUSETTS, Newton 64 Cramer Electronics, Inc. WO 9-7700

MICHIGAN, Detroit 35 S. Sterling Company BRoadway 3-2900

MINNESOTA, Minneapolis George Spencer, Inc. LI 5-8811

MISSOURI, St. Louis 32 Interstate Industrial Electronics WYdown 4-7585

NEW JERSEY. Summit R. P. Luce and Company CRestview 3-9250

NEW YORK. Buffalo 2 **Summit Distributors** TT 4-3100

OHIO, Dayton 4 Srepco, Inc. **BAldwin 4-3871**

OKLAHOMA, Tulsa 19 Radio, Inc. LU 7-9124

TEXAS, Dallas 1 Adleta Company Riverside 1-3152

TEXAS, Houston 19 Busacker Electronics JA 6-4661

WASHINGTON, Seattle Seattle Radio Supply, Inc. MAin 4-2341

THE BIRTCHER CORPORATION

WEDTO Call letters of Charles Booher, sales manager of The Birtcher



745 S. Monterey Pass Rd. •

Monterey Park, California

ANgelus 8-8584

You get more for your money from **NEWARK** Check these HAMMARLUND values—

(with these Newark extras)

- Top trade-in allowance on your present equipment
- Immediate delivery from Newark's complete stocks
- Complete experienced technical assistance



FOR TOP PERFORMANCE AT MODERATE COST


New HX-50 Transmitter. Brand new, with ultra-modern circuitry, using Compactron and Nuvistor tubes, and all the latest features. A truly versatile unit with up to 75 watts output on SSB-CW, 15 watts AM, covering all bands, 80 thru 10 meters, plus MARS frequencies. Accurate calibration, readable to 500 cycles. With built-in antenna changeover relay. Measures a compact 9%" H x 9%" D x 17%" W.

Newark Catalog No. 97F430 net...... \$39950

HQ-110C Receiver. Dual conversion, 12-tube superheterodyne unit covers all 7 amateur bands, 6 thru 160 meters. Has many features of higher priced receivers . . . separate linear detector for SSB and CW, Q-multiplier for continuously variable high selectivity, built-in 100KC crystal calibrator. With 24-hour clock timer, die-cast aluminum front panel.

Newark Catalog No. 97F427 net...... \$25900

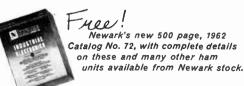HQ-110 (Without clock) No. 97F429 net \$24900



AN AMATEUR STATION OF UNEXCELLED PERFORMANCE

HX-500 Transmitter. Top performance. Filter type sideband transmitter delivers power output of 100 watts PEP on SSB, CW, NBFM, RTTY, on the entire 80 thru 10 meter bands, 25 watts AM output. Stability below 100 cycles. Built-in keying and antenna relays. Automatic level control prevents overloading and increases talk power. Can be rack-mounted. Many other important

Newark Catalog No. 97F431 net...... \$69500

HQ-170C Triple Conversion Receiver. This 17-tube receiver provides best possible reception of SSB, CW, and AM signals on the 160 thru 6 meter bands. Bandwidth selectivity is variable from 0.5KC to 3KC; SSB and CW sensitivity 0.5 microvolts for 10:1 signal:noise ratio, Adjustable 445KC slot filter eliminates heterodyne interference. 24-hour clock timer.

Newark Catalog No. 97F433, net

HQ-170 (Without clock) No. 97F434 net. \$35900



Write Dept. HB-62, Attention Ham Shack for trade-ins. 223 W. Madison St. . Chicago 6, Ill. . STate 2-2944

In Inglewood, California call: OR 8-0441 In Detroit call: UN 1-6700

In Grand Rapids, Michigan call: CH 1-5695

In New York City call: AL 5-4600 In Denver call: SK 7-3371

PANORAMIC

proven performers for amateur, laboratory and production use

Single Side Band & **Communications** Systems Analyzers



SSB-3a SINGLE SIDE BAND spectrum analyzer

2 mc-40 mc. 100 cps - 40 mc with Optional REC-1. Set up, adjust, manitar and trauble shoot SSB and AM transmitters and receivers . . . with ane convenient, campact and camprehensive package. Uniform sensitivity over entire range.

Quick, accurate measurement and display af

- 2-Tane distartion tests
 - Vestigial carrier amplitude
- Dynamic transmission bandwidth
 Out-of-band radiations etc. Residual hum sidebands



MODEL PR-1

PANADAPTOR for amateur use

PR-1, for ham operation, features simultaneous visual observation of many signals on 3-in. CR tube over a band of frequencies up to 200 kc. For spotting replies to your CQ's...selecting QRM-free spots...second aural receiver for 3-way QSO's...and a host of other uses.

PANADAPTORS provide continuous monitaring ta find and analyze interference (splatter, harmonics), RF parasitics, irregular transmissions. They are tuning aids far SSB and telemetry signals. Twa madels (SA-8b and SA-3, in many types. Please specify receiver IF when inquiring or ardering.



MODEL SB-12a

PANALYZORS

Law cast RF spectrum analysis ta 1000 mc (higher with external mixers).

Analyze AM, FM, SSB transmitters

Investigate pulsed RF signals

Spot spurious ascillations and madulation

3 models, SB-3, SB-8b, and SB-12a, in many types far narraw and broad band manitoring and analysis.

Measurement theory and applications are discussed in THE PANORAMIC ANALYZER. Get on our mailing list for this free, helpful publication.

Write taday, far detailed specifications and applications of these versa tile, ecanamical Panaramic instruments ... and NEW CATALOG DIGEST Attractive professional career opportunities available.

PANORAMIC ELECTRONICS, INC.

576 So. Fulton Ave., Mt. Vernon, New York • OWens 9-4600 TWX: MT-V-NY-5229 • Cables: Panaramic, Mt. Vernan N. Y. State



Formerly Panaramic Radio Praducts, Inc.

Learn Code

vourself for your big opportunity

THE Candler WAY IS THE

Champion WAY!



SCIENTIFIC CODE COURSE

Especially designed for the beginner. Teaches the bosic principles of code operation scientifically.

Here's your chance to learn quickly and easily...to get maximum speed and proficiency in code ... right in your own home. You can save time and money learning the fundomentals of code sending and receiving and the principles of fast, efficient operating with the world-famous CANDLER SYSTEM.

Picture yourself at your own transmitter . . . sending out radio code, messages that will be received around the globe. Yes, operators are waiting to communicate with you today, tonight or any time. The knowledge of the world . . intimate friendships you will gain . . . may help you in your business, may be a stepping stone to success.

Wouldn't you like to be the invaluable link with the outside world in time of disaster? Or to serve in a national or local emergency? Be ready for service when the opportunity arises! Learn radio and telegraphy now — the Candler

For 50 years the CANDLER SYSTEM has trained beginners for all telegraphing requirements, all operator licenses, highest ratings, and FCC specifications, both amateur and commercial. The record of famous amateurs and expert operators who learned the Candler way is proof of what the Candler System offers you. Send for details today!

CANDLER SYSTEM

Dept. 58, 2077 Locust \$t. Denver 7, Colorado

YOU COULD WORK WONDERS WITH **GOTHAM VERTICAL** ANTENNA!

FREE

Send a card for our valuable catalog of 50 different antennas with specifications and characteristics. Gives bands and frequencies covered, element information, size of tubing used, boom length, shipping weight, feed line used, polarization, and other data.

Airmail Order Today — We Ship Tomorrow
GOTHAM Dept. RAH
1805 PURDY AVE., MIAMI BEACH, FLA.
Enclosed find check or money-order for:
V40 VERTICAL ANTENNA FOR 40, 20, 15, 10 AND 6 METER BANDS. ESPECIALLY SUITED FOR THE NOVICE WHO OPERATES 40 AND 15 \$14.95
V80 VERTICAL ANTENNA FOR B0, 40, 20,
V80 VERTICAL ANTENNA FOR 80, 40, 20, 15, 10 AND 6 METER BANDS. MOST POPULAR OF THE VERTICALS. USED BY THOUSANDS OF NOVICES, TECHNICIANS, AND GENERAL LICENSE HAMS \$16.95 V160 VERTICAL ANTENNA FOR 160, 80, 40, 20, 15, 10 AND 6 METER BANDS. SAME AS THE OTHER VERTICAL ANTENNAS, EX- CEPT THAT A LARGER LOADING COIL PERMITS OPERATION ON THE 160 METER BAND ALSO \$18.95
HOW TO ORDER. Send check or money order directly to Gotham. Immediate shipment by Railway Express, charges collect. Foreign orders accepted.
Name
Address
City Zone State



TV STATION PACKAGE

Ling-Mitter TV Transmitter
Ling Spectator TV Camera
Ling-TV Videa Manitar
1" f 1.9 Lens
Yagaflector Transmitting Antenna
Transmission Line
UHF Converter
Dual Bow Tie Receiving Antenna

OPERATE YOUR OWN TV STATION

LOW COST


AMATEUR'S
TELEVISION STATION
COMPLETELY
PACKAGED
FOR OPERATION IN
THE FCC ASSIGNED
420-450 MC BAND

- Unconditionally Guaranteed
- Amateur Net Package Price
 \$199500
- Suitable Financing May Be Arranged

ELECTRON CORPORATION

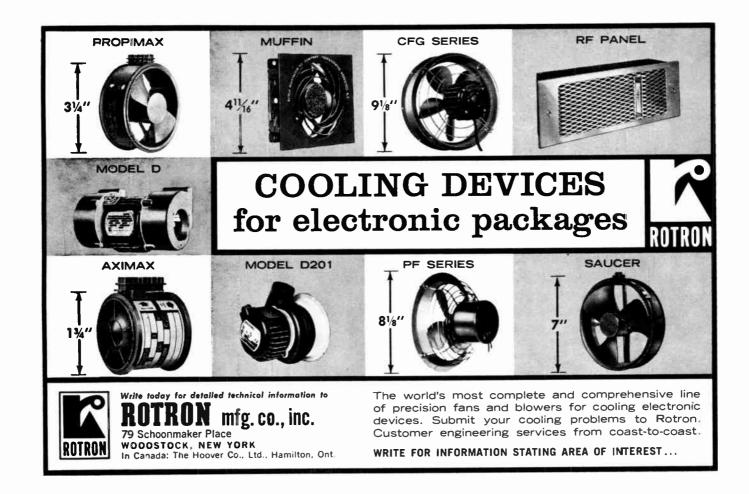Designers And Manufacturers Of Quality Television Systems
P.O. Box 5570 • Dallas, Texas
A SUBSIDIARY OF LING-TEMCO-VOUGHT, INC.





COMPLETE OUTFITTERS

FOR THE

- ► HAM
- **COMMUNICATIONS**
- ► ELECTRONIC ENGINEERS

EUGENE G. WILE

218-220 South 11th St.

Philadelphia 7, Pa.

WAlnut 3-1343

Distributors of


Nationally Advertised Lines of RADIO, TELEVISION and ELECTRONIC Parts

MODERN EQUIPMENT

FOR LEARNING MORSE CODE

PERFORATORS, TRANSMITTERS, ETC.



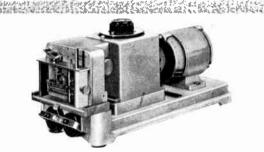

GNT TRANSMITTER MODEL 115

Ideal for learning Morse code, permitting insertion of extended pauses between letters and words.



GNT MORSEINKER MODEL 1532

Operates from tone frequency signals or by Morse Key. Especially designed for training purposes.

"HOW TO LEARN MORSE"



Booklet describing

Morse training

Write for free copy



GNT KEYBOARD PERFORATOR MODEL 50

An instrument for preparing a perforated Morse code slip for use in a transmitter. Maximum speed of operation 750 characters per minute. Provided with a special locking device preventing the simultaneous depression of two keys.

ALSO COMPLETE RANGE OF AUTOMATIC INSTRUMENTS FOR HIGH SPEED MORSE TELEGRAPHY.



TELCOLAB CORPORATION

CHRYSLER BUILDING NEW YORK 17, N. Y.

U.S., Representatives of:



GREAT NORTHERN TELEGRAPH WORKS, COPENHAGEN, DENMARK,


THE HAMS' NO. 1 CHOICE

in clear plastic or metal cases...

Shurite. **METERS**



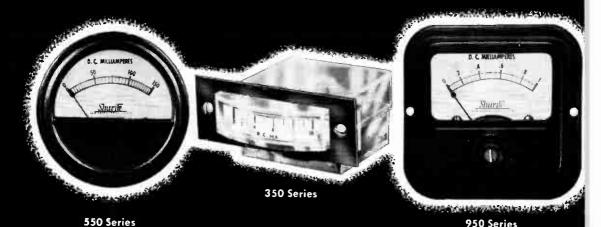850 Series Shown actual size, zero adjuster optional



Shown approximately three quarter size

CLEAR-PLASTIC CASES: One look will make every ham enthusiastic about the modern, expensive-looking 850 series . . . and you will be pleased to find the meters cost only 20¢ more than the equivalent metal cased meter. Equally good news will be the longer, more visible scale arc...the removable front ... and the availability of zero adjusters on all AC or DC ranges.

ATTRACTIVE METAL CASES: In certain applications—for panel appearance or specialized service conditions, you may prefer to select from the long-time metal favorites, the basic Models 550 or 950 as illustrated. Although all have been modernized in appearance recently, each continues to fit 2 5/32" mounting hale. See Catalog 94 covering all types, including many with zero adjuster.

CHOICE OF MANY TYPES: AC and DC Ammeters, Milliameters, Voltmeters and Resistance Meters. AC meters are double-vane repulsion type with jeweled bearing. DC are polarized-vane solenoid type, or moving magnet construction. Well over 200 ranges and types. Among the most popular are a 0-3 DC Milliammeter with 500 ohms internal resistance and built-in zera adjuster, and a 0-1 DC Milliammeter with 1,000 ohms internal resistance and zero adjuster.

NEW EDGEWISE METER: The 350 series pravides an ideal we to dress up a panel. The clear jewel-like plastic frant is ver rich looking and gathers light far easy reading af its long scal Yet it takes very little panel space and costs much less tha you would expect.

DEPENDABLE PERFORMANCE: By far the best torque-to-weigl ratio in its field gives you a sturdy meter with fast response and ability to duplicate readings. Accuracy well within th standard 5%.

REASONABLE PRICES: Typical of the exceptional values ar the meters illustrated, 0-150 DC Ma, \$2.15 in the 550 or 95 Series, \$2.35 in the 850 Series; 0-10 DC Ma in the 350 Serie \$3.45; 0-1 DC Ma (with zero adjuster), \$3.75 in 550 or 95 Series, \$3,95 in the 850 Series; -20 to 3VU in the 850 Series \$5.85. Other meters are correspondingly low in price. You get th benefit of low costs made possible by large, quantity production

GUARANTEED: For ane year against defective workmanship and material. Will be repaired or replaced if sent postpaid t the factory with 40¢ handling charge.

WIDELY AVAILABLE: Stocked by leading electronic part distributors for prompt deliveries.

TURITE METERS 130 Wallace Street • New Haven 8, Connectice

P. O. Box 1818




Increase both performance and reliability of your ham equipment with these Amphenol products

Polyfoam® Coaxial Cable can boost your signal strength as much as 35%. Uses an inert-gas-expanded polyethylene to increase dielectric constant to 1.50 instead of the usual 2.26. Your Amphenol distributor carries RG-8, 11, and 59 in stock.



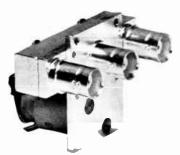RF Connectors. The most complete line available anywhere—and your Amphenol distributor has the type and size you need on the shelf available for immediate delivery.



DK Coaxial Switches for antenna switching and similar applications. 14 basic models meet every ham requirement for low cost, high reliability and long life. 100% inspected. Your Amphenol distributor has all commonly used types in stock. Ask for Catalog No. S4.



Do you have this catalog? Amphenol catalog IEC-4 shows virtually every type of connector and coaxial cable you'll ever need, plus technical specs. Your copy is free from your Amphenol distributor, or write us direct at 2803 S. 25th Ave., Broadview, Illinois.



PHENDD Distributor Division / Amphenol-Borg Electronics Corporation



DOC AULWURM, W6BBC, maintains contact with other Raytheon field engineers and headquarters staff personnel from his Piedmont, California home.

FIELD ENGINEERING WITH A FUTURE

Doc Aulwurm and his "traveling" ham rig

Arthur (Doc) C. Aulwurm, Senior Field Engineer, and his compact ham rig have traveled the world working on a wide variety of challenging assignments for Raytheon. Doc's story is highly typical of the Raytheon Field Engineer.

Since Doc joined Submarine Signal Company (a predecessor of the present Raytheon organization) in 1945, he has tackled specialized tasks in Karachi, Pakistan; Lakehurst, N. J.; and San Diego, California, among other places.

Doc is now working on sonar equipment at Mare Island Naval Shipyard, California. Future assignments may carry him to other parts of the world or to headquarters in Massachusetts.

Perhaps you too can qualify for a Raytheon field engineering future. Requirements are previous experience plus an E.E. degree or equivalent in practical know-how in guided missiles, fire control, ground and bombing radar or sonar.

Benefits: attractive salary, insurance, educational programs, relocation assistance, opportunity for advancement. For details, forward your resume to Ronald Guittarr, Electronic Services Division, Raytheon, Northwest Industrial Park, Burlington, Massachusetts.



RAYTHEON COMPANY

ELECTRONIC SERVICES DIVISION



World Radio History


N. MAZE 39TH EDITION · 1962

The radio amateur's handbook

THE STANDARD MANUAL OF AMATEUR
RADIO COMMUNICATION




\$3.50 U.S.A. Proper

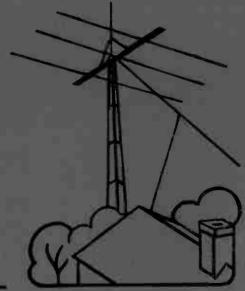

UBLISHED BY THE AMERICAN RADIO RELAY LEAGUE

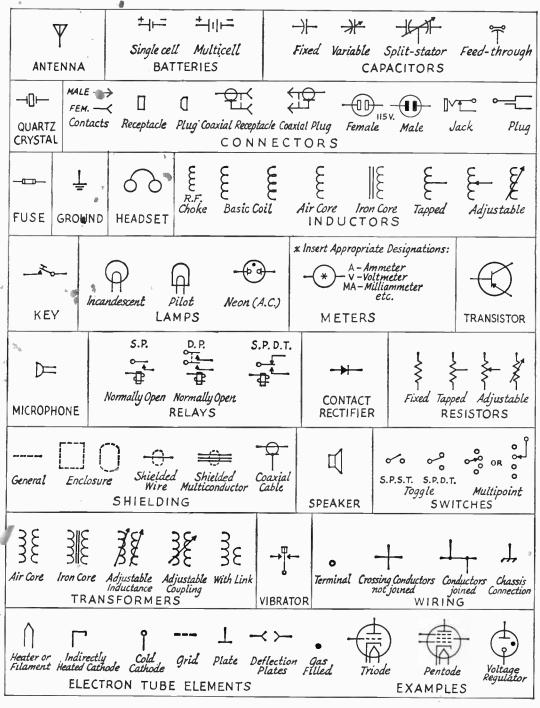SCHEMATIC SYMBOLS USED IN CIRCUIT DIAGRAMS



Where it is necessary or desirable to identify the electrodes or capacitors, the curved element represents the *outside* electrode (marked "outside foil," "ground," etc.) in fixed paperand ceramic-dielectric capacitors, and the *negative* electrode in electrolytic capacitors. In variable or adjustable capacitors (regardless

of dielectric), the curved line indicates the moving element (rotor plates).

In the case of switches, jacks, etc., only the basic combinations are shown. Any combination of these symbols may be assembled as required, following the elementary forms shown.

The Radio Amateur's Handbook

By the HEADQUARTERS STAFF of the

AMERICAN RADIO RELAY LEAGUE WEST HARTFORD, CONN., U.S.A.



1962

Thirty-ninth Edition

COPYRIGHT 1962 BY
THE AMERICAN RADIO RELAY LEAGUE, INC.

Copyright secured under the Pan-American Convention

International Copyright secured

This work is Publication No. 6 of The Radio Amateur's Library, published by the League. All rights reserved. No part of this work may be reproduced in any form except by written permission of the publisher. All rights of translation are reserved. Printed in U. S. A.

Quedan reservados todos los derechos Library of Congress Catalog Card Number: 41-3345 Thirty-ninth Edition

\$3.50 in U. S. A. proper. \$4.00 in U. S. Possessions and Canada. \$5.00 elsewhere.

Clothbound edition \$6.00 U.S.A., Possessions and Canada, \$6.50 Elsewhere.

FOREWORD

In over thirty-five years of continuous publication *The Radio Amateur's Handbook* has become as much of an institution as amateur radio itself. Produced by the amateur's own organization, the American Radio Relay League, and written with the needs of the practical amateur constantly in mind, it has earned universal acceptance not only by amateurs but by all segments of the technical radio world. This wide dependence on the *Handbook* is founded on its practical utility, its treatment of radio communication problems in terms of how-to-do-it rather than by abstract discussion.


Virtually continuous modification is a feature of the *Handbook*—always with the objective of presenting the soundest and best aspects of current practice rather than the merely new and novel. Its annual revision, a major task of the head-quarters group of the League, is participated in by skilled and experienced amateurs well acquainted with the practical problems in the art.

The use of modern printing techniques, together with extensive and useful catalog advertising by manufacturers producing equipment for the radio amateur and industry, makes it possible to distribute for a very modest charge a work which in volume of subject matter and profusion of illustration surpasses most available radio texts selling for several times its price.

The *Handbook* has long been considered an indispensable part of the amateur's equipment. We earnestly hope that the present edition will succeed in bringing as much assistance and inspiration to amateurs and would-be amateurs as have its predecessors.

John Huntoon General Manager, ARRL

West Hartford, Conn.

 

CONTENTS

		Circuit Symbols frontis	piece
		The Amateur's Code	8
Chapter	1	Amateur Radio	9
•	2	Electrical Laws and Circuits	15
	3	Vacuum-Tube Principles	5 9
	4	Semiconductor Devices	79
	5	High-Frequency Receivers	86
	6	High-Frequency Transmitters	144
	7	Power Supplies	218
	8	Keying and Break-In	243
	9	Speech Amplifiers and Modulators	255
	10	Amplitude Modulation	283
	11	Suppressed-Carrier and Single-Sideband Techniques	303
	12	Specialized Communication Systems	329
	13	Transmission Lines	341
	14	Antennas	360
	15	Wave Propagation	394
	16	V.H.F. Receivers	402
	17	V.H.F. Transmitters	424
	18	V.H.F. Antennas	453
	19	Mobile and Portable-Emergency Equipment .	465
	20	Construction Practices	502
	21	Measurements	512
	22	Assembling a Station	545
	23	BCI and TVI	552
	24	Operating a Station	572
	25	Vacuum Tubes and Semiconductors	V1
		Index	

Catalog Section

The Amateur's Code

ONE

The Amateur is Gentlemanly . . . He never knowingly uses the air for his own amusement in such a way as to lessen the pleasure of others. He abides by the pledges given by the ARRL in his behalf to the public and the Government.

TWO

The Amateur is Loyal . . . He owes his amateur radio to the American Radio Relay League, and he offers it his unswerving loyalty.

THREE

The Amateur is Progressive . . . He keeps his station abreast of science. It is built well and efficiently. His operating practice is clean and regular.

FOUR

The Amateur is Friendly . . . Slow and patient sending when requested, friendly advice and counsel to the beginner, kindly assistance and cooperation for the broadcast listener; these are marks of the amateur spirit.

FIVE

The Amateur is Balanced . . . Radio is his hobby. He never allows it to interfere with any of the duties he owes to his home, his job, his school, or his community.

SIX

The Amateur is Patriotic . . . His knowledge and his station are always ready for the service of his country and his community.

-Paul M. Segal

Amateur Radio

Amateur radio is a scientific hobby, a means of gaining personal skill in the fascinating art of electronics and an opportunity to communicate with fellow citizens by private short-wave radio. Scattered over the globe are over 250,000 amateur radio operators who perform a service defined in international law as one of "self-training, intercommunication and technical investigations carried on by . . . duly authorized persons interested in radio technique solely with a personal aim and without pecuniary interest."

From a humble beginning at the turn of the century, amateur radio has grown to become an established institution. Today the American followers of amateur radio number over 200,000, trained communicators from whose ranks will come the professional communications specialists and executives of tomorrow-just as many of today's radio leaders were first attracted to radio by their early interest in amateur radio communication. A powerful and prosperous organization now provides a bond between amateurs and protects their interests; an internationally respected magazine is published solely for their benefit. The military services seek the cooperation of the amateur in developing communications reserves. Amateur radio supports a manufacturing industry which, by the very demands of amateurs for the latest and best equipment, is always up-to-date in its designs and production techniques-in itself a national asset. Amateurs have won the gratitude of the nation for their heroic performances in times of natural disaster; traditional amateur skills in emergency communication are also the stand-by system for the nation's civil defense. Amateur radio is, indeed, a magnificently useful institution.

Although as old as the art of radio itself, amateur radio did not always enjoy such prestige. Its first enthusiasts were private citizens of an experimental turn of mind whose imaginations went wild when Marconi first proved that messages actually could be sent by wireless. They set about learning enough about the new scientific marvel to build homemade spark transmitters. By 1912 there were numerous Government and commercial stations, and hundreds of amateurs; regulation was needed, so laws, licenses and wavelength specifications appeared. There was then no amateur organization nor spokesman. The official viewpoint toward amateurs was something like this:

"Amateurs?... Oh, yes.... Well, stick 'em on 200 meters and below; they'll never get out of their backyards with that."

But as the years rolled on, amateurs found out how, and DX (distance) jumped from local to 500-mile and even occasional 1000-mile two-way contacts. Because all long-distance messages had to be relayed, relaying developed into a fine art—an ability that was to prove invaluable when the Government suddenly called hundreds of skilled amateurs into war service in 1917. Meanwhile U.S. amateurs began to wonder if there were amateurs in other countries across the seas and if, some day, we might not span the Atlantic on 200 meters.

Most important of all, this period witnessed the birth of the American Radio Relay League, the amateur radio organization whose name was to be virtually synonymous with subsequent amateur progress and short-wave development. Conceived and formed by the famous inventor, the late Hiram Percy Maxim, ARRL was formally launched in early 1914. It had just begun to exert its full force in amateur activities when the United States declared war in 1917, and by that act sounded the knell for amateur radio for the next two and a half years. There were then over 6000 amateurs. Over 4000 of them served in the armed forces during that war.

Today, few amateurs realize that World War I not only marked the close of the first phase of amateur development but came very near marking its end for all time. The fate of amateur radio was in the balance in the days immediately following the signing of the Armistice. The



HIRAM PERCY MAXIM President ARRL, 1914-1936

Government, having had a taste of supreme authority over communications in wartime, was more than half inclined to keep it. The war had not been ended a month before Congress was considering legislation that would have made it impossible for the amateur radio of old ever to be resumed. ARRL's President Maxim rushed to Washington, pleaded, argued, and the bill was defeated. But there was still no amateur radio; the war ban continued. Repeated representations to Washington met only with silence. The League's offices had been closed for a year and a half, its records stored away. Most of the former amateurs had gone into service: many of them would never come back. Would those returning be interested in such things as amateur radio? Mr. Maxim, determined to find out, called a meeting of the old Board of Directors. The situation was discouraging: amateur radio still banned by law, former members scattered, no organization, no membership, no funds. But those few determined men financed the publication of a notice to all the former amateurs that could be located, hired Kenneth B. Warner as the League's first paid secretary, floated a bond issue among old League members to obtain money for immediate running expenses, bought the magazine QST to be the League's official organ, started activities, and dunned officialdom until the wartime ban was lifted and amateur radio resumed again, on October 1, 1919. There was a headlong rush by amateurs to get back on the air. Gangway for King Spark! Manufacturers were hard put to supply radio apparatus fast enough. Each night saw additional dozens of stations crashing out over the air. Interference? It was bedlam!

But it was an era of progress. Wartime needs had stimulated technical development. Vacuum tubes were being used both for receiving and transmitting. Amateurs immediately adapted the new gear to 200-meter work. Ranges promptly increased and it became possible to bridge the continent with but one intermediate relay.

TRANSATLANTICS

As DX became 1000, then 1500 and then 2000 miles, amateurs began to dream of transatlantic work. Could they get across? In December, 1921, ARRL sent abroad an expert amateur, Paul F. Godley, 2ZE, with the best receiving equipment available. Tests were run, and thirty American stations were heard in Europe. In 1922 another transatlantic test was carried out and 315 American calls were logged by European amateurs and one French and two British stations were heard on this side.

Everything now was centered on one objective: two-way amateur communication across the Atlantic! It must be possible—but somehow it couldn't quite be done. More power? Many already were using the legal maximum. Better receivers? They had superheterodynes. Another wavelength? What about those undisturbed wavelengths below 200 meters? The engineering world thought they were worthless—but they had

said that about 200 meters. So, in 1922, tests between Hartford and Boston were made on 130 meters with encouraging results. Early in 1923, ARRL-sponsored tests on wavelengths down to 90 meters were successful. Reports indicated that as the wavelength dropped the results were better. Excitement began to spread through amateur ranks.

Finally, in November, 1923, after some months of careful preparation, two-way amateur transatlantic communication was accomplished, when Schnell, 1MO, and Reinartz, 1XAM (now W4CF and K6BJ, respectively) worked for several hours with Deloy, 8AB, in France, with all three stations on 110 meters! Additional stations dropped down to 100 meters and found that they, too, could easily work two-way across the Atlantic. The exodus from the 200-meter region had started. The "short-wave" era had begun!

By 1924 dozens of commercial companies had rushed stations into the 100-meter region. Chaos threatened, until the first of a series of national and international radio conferences partitioned off various bands of frequencies for the different services. Although thought still centered around 100 meters, League officials at the first of these frequency-determining conferences, in 1924, wisely obtained amateur bands not only at 80 meters but at 40, 20, and even 5 meters.

Eighty meters proved so successful that "forty" was given a try, and QSOs with Australia, New Zealand and South Africa soon became commonplace. Then how about 20 meters? This new band revealed entirely unexpected possibilities when 1XAM worked 6TS on the West Coast, direct, at high noon. The dream of amateur radio—daylight DX!—was finally true.

PUBLIC SERVICE

Amateur radio is a grand and glorious hobby but this fact alone would hardly merit such wholehearted support as is given it by our Government at international conferences. There are other reasons. One of these is a thorough appreciation by the military and civil defense authorities of the value of the amateur as a source of skilled radio personnel in time of war. Another asset is best described as "public service."

About 4000 amateurs had contributed their skill and ability in '17-'18. After the war it was only natural that cordial relations should prevail between the Army and Navy and the amateur. These relations strengthened in the next few years and, in gradual steps, grew into cooperative activities which resulted, in 1925, in the establishment of the Naval Communications Reserve and the Army-Amateur Radio System (now the Military Affiliate Radio System). In World War II thousands of amateurs in the Naval Reserve were called to active duty, where they served with distinction, while many other thousands served in the Army, Air Forces, Coast Guard and Marine Corps. Altogether, more than 25,000 radio amateurs served in the armed forces of the United States. Other thousands were engaged in vital civilian electronic research, develPublic Service 11

opment and manufacturing. They also organized and manned the War Emergency Radio Service, the communications section of OCD.

The "public-service" record of the amateur is a brilliant tribute to his work. These activities can be roughly divided into two classes, expeditions and emergencies. Amateur cooperation with expeditions began in 1923 when a League member, Don Mix, 1TS, of Bristol, Conn. (now assistant technical editor of QST), accompanied MacMillan to the Arctic on the schooner Bowdoin with an amateur station. Amateurs in Canada and the U.S. provided the home contacts. The success of this venture was so outstanding that other explorers followed suit. During subsequent years a total of perhaps two hundred voyages and expeditions were assisted by amateur radio, the several explorations of the Antarctic being perhaps the best known.

Since 1913 amateur radio has been the principal, and in many cases the only, means of outside communication in several hundred storm, flood and earthquake emergencies in this country. The 1936 and 1937 eastern states floods, the Southern California flood and Long Island-New England hurricane disaster in 1938, the Florida-Gulf Coast hurricanes of 1947, and the 1955 flood disasters called for the amateur's greatest emergency effort. In these disasters and many others-tornadoes, sleet storms, forest fires, blizzards-amateurs played a major role in the relief work and earned wide commendation for their resourcefulness in effecting communication where all other means had failed. During 1938 ARRL inaugurated a new emergency-preparedness program, registering personnel and equipment in its Emergency Corps and putting into effect a comprehensive program of cooperation with the Red Cross, and in 1947 a National Emergency Coordinator was appointed to fulltime duty at League headquarters.

The amateur's outstanding record of organized preparation for emergency communications and performance under fire has been largely responsible for the decision of the Federal Government to set up special regulations and set aside special frequencies for use by amateurs in providing auxiliary communications for civil defense purposes in the event of war. Under the banner, "Radio Amateur Civil Emergency Service," amateurs are setting up and manning community and area networks integrated with civil defense functions of the municipal governments. Should a war cause the shut-down of routine amateur activities, the RACES will be immediately available in the national defense, manned by amateurs highly skilled in emergency communication.

TECHNICAL DEVELOPMENTS

Throughout these many years the amateur was careful not to slight experimental development in the enthusiasm incident to international DX. The experimenter was constantly at work on ever-higher frequencies, devising improved apparatus, and learning how to cram several stations where previously there was room for only

one! In particular, the amateur pressed on to the development of the very high frequencies and his experience with five meters is especially representative of his initiative and resourcefulness and his ability to make the most of what is at hand. In 1924, first amateur experiments in the vicinity of 56 Mc. indicated that band to be practically worthless for DX. Nonetheless, great "short-haul" activity eventually came about in the band and new gear was developed to meet its special problems. Beginning in 1934 a series of investigations by the brilliant experimenter, Ross Hull (later QST's editor), developed the theory of v.h.f. wave-bending in the lower atmosphere and led amateurs to the attainment of better distances: while occasional manifestations of ionospheric propagation, with still greater distances, gave the band uniquely erratic performance. By Pearl Harbor thousands of amateurs were spending much of their time on this and the next higher band, many having worked hundreds of stations at distances up to several thousand miles. Transcontinental 6-meter DX is not uncommon; during solar peaks, even the oceans have been bridged! It is a tribute to these indefatigable amateurs that today's concept of v.h.f. propagation was developed largely through amateur research.

The amateur is constantly in the forefront of technical progress. His incessant curiosity, his eagerness to try anything new, are two reasons. Another is that ever-growing amateur radio continually overcrowds its frequency assignments, spurring amateurs to the development and adoption of new techniques to permit the accommodation of more stations. For examples, amateurs turned from spark to c.w., designed more selective receivers, adopted crystal control and pure d.c. power supplies. From the ARRL's own laboratory in 1932 came James Lamb's "singlesignal" superheterodyne-the world's most advanced high-frequency radiotelegraph receiverand, in 1936, the "noise-silencer" circuit. Amateurs are now turning to speech "clippers" to reduce bandwidths of phone transmissions and "single-sideband suppressed-carrier" systems as well as even more selectivity in receiving



A corner of the ARRL laboratory.

equipment for greater efficiency in spectrum

During World War II, thousands of skilled amateurs contributed their knowledge to the development of secret radio devices, both in Government and private laboratories. Equally as important, the prewar technical progress by amateurs provided the keystone for the development of modern military communications equipment. Perhaps more important today than individual contributions to the art is the mass cooperation of the amateur body in Government projects such as propagation studies; each participating station is in reality a separate field laboratory from which reports are made for correlation and analysis. An outstanding example was varied amateur participation in several activities of the International Geophysical Year program. ARRL, with Air Force sponsorship, conducted an intensive study of v.h.f. propagation phenomena-DX transmissions via little-understood methods such as meteor and auroral reflections, and transequatorial scatter. ARRL-affiliated clubs and groups have operated precision receiving antennas and apparatus to help track earth satellites via radio. For volunteer astronomers searching visually for the satellites, other amateurs have manned networks to provide instant radio reports of sightings to a central agency so that an orbit might be computed.

Emergency relief, expedition contact, experimental work and countless instances of other forms of public service—rendered, as they always have been and always will be, without hope or expectation of material reward—made amateur radio an integral part of our peacetime national life. The importance of amateur participation in the armed forces and in other aspects of national defense have emphasized more strongly than ever that amateur radio is vital to our national existence.

THE AMERICAN RADIO RELAY LEAGUE

The ARRL is today not only the spokesman for amateur radio in this country but it is the largest amateur organization in the world. It is strictly of, by and for amateurs, is noncommercial and has no stockholders. The members of the League are the owners of the ARRL and QST.

The League is pledged to promote interest in two-way amateur communication and experimentation. It is interested in the relaying of messages by amateur radio. It is concerned with the advancement of the radio art. It stands for the maintenance of fraternalism and a high standard of conduct. It represents the amateur in legislative matters.

One of the League's principal purposes is to keep amateur activities so well conducted that the amateur will continue to justify his existence. Amateur radio offers its followers countless pleasures and unending satisfaction. It also calls for the shouldering of responsibilities—the maintenance of high standards, a cooperative loyalty to the traditions of amateur radio, a dedi-



The operating room at WIAW.

cation to its ideals and principles, so that the institution of amateur radio may continue to operate "in the public interest, convenience and necessity."

The operating territory of ARRL is divided into one Canadian and fifteen U. S. divisions. The affairs of the League are managed by a Board of Directors. One director is elected every two years by the membership of each U.S. division, and one by the Canadian membership. These directors then choose the president and vicepresident, who are also members of the Board. The secretary and treasurer are also appointed by the Board. The directors, as representatives of the amateurs in their divisions, meet annually to examine current amateur problems and formulate ARRL policies thereon. The directors appoint a general manager to supervise the operations of the League and its headquarters, and to carry out the policies and instructions of the Board.

ARRL owns and publishes the monthly magazine, QST. Acting as a bulletin of the League's organized activities, QST also serves as a medium for the exchange of ideas and fosters amateur spirit. Its technical articles are renowned. It has grown to be the "amateur's bible," as well as one of the foremost radio magazines in the world. Membership dues include a subscription to OST.

ARRL maintains a model headquarters amateur station, known as the Hiram Percy Maxim Memorial Station, in Newington, Conn. Its call is W1AW, the call held by Mr. Maxim until his death and later transferred to the League station by a special government action. Separate transmitters of maximum legal power on each amateur band have permitted the station to be heard regularly all over the world. More important, W1AW transmits on regular schedules bulletins of general interest to amateurs, conducts code practice as a training feature, and engages in two-way work on all popular bands with as many amateurs as time permits.

At the headquarters of the League in West Hartford, Conn., is a well-equipped laboratory to assist staff members in preparation of technical material for QST and the Radio Amateur's Handbook. Among its other activities, the League maintains a Communications Department concerned with the operating activities of League members. A large field organization is headed by a Section Communications Manager in each of the League's seventy-three sections. There are appointments for qualified members in various fields, as outlined in Chapter 24. Special activities and contests promote operating skill. A special section is reserved each month in OST for amateur news from every section of the country.

AMATEUR LICENSING IN THE UNITED STATES

Pursuant to the law, The Federal Communications Commission (FCC) has issued detailed regulations for the amateur service.

A radio amateur is a duly authorized person interested in radio technique solely with a personal aim and without pecuniary interest. Amateur operator licenses are given to U. S. citizens who pass an examination on operation and apparatus and on the provisions of law and regulations affecting amateurs, and who demonstrate ability to send and receive code. There are four available classes of amateur license—Novice, Technician, General (called "Conditional" if exam taken by mail), and Amateur Extra Class. Each has different requirements, the first two being the simplest and consequently conveying limited privileges as to frequencies available. Exams for Novice, Technician and Conditional classes are taken by mail under the supervision of a volunteer examiner. Station licenses are granted only to licensed operators and permit communication between such stations for amateur purposes, i.e., for personal noncommercial aims flowing from an interest in radio technique. An amateur station may not be used for material compensation of any sort nor for broadcasting. Narrow bands of frequencies are allocated exclusively for use by amateur stations. Transmissions may be on any frequency within the assigned bands. All the frequencies may be used for c.w. telegraphy; some are available for radiotelephone, others for special forms of transmission such as teletype, facsimile, amateur television or radio control. The input to the final stage of amateur stations is limited to 1000 watts and on frequencies below 144 Mc. must be adequately filtered direct current. Emissions must be free from spurious radiations. The licensee must provide for measurement of the transmitter frequency and establish a procedure for checking it regularly. A complete log of station operation must be maintained, with specified data. The station license also authorizes the holder to operate portable and mobile stations subject to further regulations. All radio licensees are subject to penalties for violation of regulations.

Amateur licenses are issued entirely free of charge. They can be issued only to citizens but that is the only limitation, and they are given without regard to age or physical condition to anyone who successfully completes the examination. When you are able to copy code at the required speed, have studied basic transmitter theory and are familiar with the law and amateur regulations, you are ready to give serious thought to securing the Government amateur licenses which are issued you, after examination by an FCC engineer (or by a volunteer, depending on the license class), through FCC at Washington. A complete up-to-the-minute discussion of license requirements, the FCC regulations for the amateur service, and study guides for those preparing for the examinations, are to be found in an ARRL publication, The Radio Amateur's License Manual, available from the American Radio Relay League, West Hartford 7, Conn., for 50¢, postpaid.

LEARNING THE CODE

A didah

In starting to learn the code, you should consider it simply another means of conveying information. The spoken word is one method, the printed page another, and typewriting and shorthand are additional examples. Learning the code is as easy-or as difficult-as learning to type.

The important thing in beginning to study code is to think of it as a language of sound, never as combinations of dots and dashes. It is easy to "speak" code equivalents by using "dit" and "dah," so that A would be "didah" (the "t" is dropped in such combinations). The sound "di"

N dahit

В	dahdididit	0	dah dah dah
С	dahdidahdit	P	di <u>dahdah</u> dit
D	dahdidit	Q	dahdahdidah
E	dit	R	didahdit
F	dididahdit	S	dididit
G	dahdahdit	T	dah
Н	didididit	U	dididah
Ι	didit	V	didididah
J	didahdahdah	W	didahdah
K	dahdidah	X	<u>dahdididah</u>
L	didahdidit	Y	dahdidahdah
M	dahdah	Z	dahdahdidit
1	didahdahdah	6	<u>dah</u> didididit
2	dididahdahdah	7	dahdahdididit
3	dididahdah	8	<u>dahdahdahdidit</u>
4	didididah	9	dahdahdahdahdit
5	didididit	0	dahdahdahdah

Period: didahdidahdidah. Comma: dahdahdididahdah. Question mark: dididahdahdidit. Error: dididididididit. Double dash: dahdidididah. Wait: didahdididit. End of message: didahdidahdit. Invitation to transmit: dahdidah. End of work: didididahdidah. Fraction bar: dahdididah-

Fig. 1-1—The Continental (International Morse) code.

should be staccato; a code character such as "5" should sound like a machinegun burst: dididididit! Stress each "dah" equally; they are underlined or italicized in this text because they should be slightly accented and drawn out.

Take a few characters at a time. Learn them thoroughly in didah language before going on to new ones. If someone who is familiar with code can be found to "send" to you, either by whistling or by means of a buzzer or code oscillator, enlist his cooperation. Learn the code by listening to it. Don't think about speed to start; the first requirement is to learn the characters to the point where you can recognize each of them without hesitation. Concentrate on any difficult letters. Learning the code is not at all hard; a simple booklet treating the subject in detail is another of the beginner publications available from the League, and is entitled, Learning the Radiotelegraph Code, 50¢ postpaid.

Code-practice transmissions are sent by W1AW every evening at 0230 GMT (0130 May through October). See Chapter 24, "Code Proficiency."

INTRODUCTION TO RADIO THEORY

As you start your studies for an amateur license, you may wish to have the additional help available in *How to Become a Radio Amateur* (50¢). It features an elementary description of radio theory and constructional details on a simple receiver and transmitter.

Another aid is A Course in Radio Fundamentals (\$1.00), a study guide using this Handbook as its text. There are experiments, discussions, and quizzes to help you learn radio fundamentals.

Both booklets are available postpaid from ARRL, West Hartford, Conn.

THE AMATEUR BANDS

Amateurs are assigned bands of frequencies at approximate harmonic intervals throughout the spectrum. Like assignments to all services, they are subject to modification to fit the changing picture of world communications needs. Modifications of rules to provide for domestic needs are also occasionally issued by FCC, and in that respect each amateur should keep himself informed by W1AW bulletins, QST reports, or by communication with ARRL Hq. concerning a specific point.

In the adjoining table is a summary of the U. S. amateur bands on which operation is permitted as of our press date. Figures are megacycles. AØ means an unmodulated carrier, A1 means c.w. telegraphy, A2 is tone-modulated c.w. telegraphy, A3 is amplitude-modulated phone (n.f.m. may also be used in such bands, except on 1.8-2.0 Mc.), A4 is facsimile, A5 is television, n.f.m. designates narrow-band frequency- or phase-modulated radiotelephony, f.m. means frequency modulation, phone (including n.f.m.) or telegraphy, and F1 is frequency-shift keying.

```
80
          3.500-4.000 -A1
          3.500-3.800 ---F1
meters
          3.800-4.000 -A3
          7.000-7.300 -A1
         7.000-7.200 -F1
  40 m.
         7.200-7.300 -A3
         14.000-14.350 -A1
  20 m. 14.000-14.200-F1
        14.200-14.350-A3
        21.000-21.450 -A1
  15 m. 21.000-21.450 -F1
        21.250-21.450-A3
        28.000-29.700-A1
  10 m. 28.500-29.700—A3
29.000-29.700—f.m.
          50.0-50.1
                       -A1
   6 m.
          50.1-54
                     -A1, A2, A3, A4
            51-54
                     ---AØ
          52.5-54
           144-147.9 --- AØ, A1, A2, A3, A4,
   2 m
                       fm
         147.9-148
                     -A1
           220-225
                    -AØ, A1, A2, A3, A4,
           420-4501
                       AØ, A1, A2, A3, A4,
         1,215-1,300
                       A5, f.m.
         2,300- 2,450
         3,500- 3,700
        5,650- 5,925
                       AØ, A1, A2, A3, A4,
       10.000-10.5002
                         A5, f.m., pulse
       21,000-22,000
     All above 30,000
```

1 Input power must not exceed 50 watts.

² No pulse permitted in this band.

Note: The bands 220 through 10,500 Mc. are shared with the Government Radio Positioning Service, which has priority.

In addition, A1 and A3 (except no n.f.m.) on portions of 1.800-2.000, as follows:

Power (watts)
Area Band, kc. Day Night
Minn., Iowa, Wis., Mich., Pa., 1800-1825 500 200
Md., Del. and states to north

N. D., S. D., Nehr., Colo., N. 1975-2000 500* 200* Mex., and states west, including Hawaiian Ids.

Okla., Kans., Mo., Ark., Ill., 1800-1825 200 50 Ind., Ky., Tenn., Ohio., W. Va., Va., N. C., S. C., and Texas (west of 99° W or north of 32° N)
No operation elsewhere.

* Except in state of Washington, 200 watts day, 50 watts night.

Novice licensees may use the following frequencies, transmitters to be crystal-controlled and have a maximum power input of 75 watts.

3.700-3.750 A1 21.100-21.250 A1 7.150-7.200 A1 145-147 A1, A2, A3, f.m.

Technician licensees are permitted all amateur privileges in 50 Mc., 145-147 Mc. and in the bands 220 Mc. and above.

Except as otherwise specified, the maximum amateur power input is 1000 watts.

Electrical Laws and Circuits

ELECTRIC AND MAGNETIC FIELDS

When something occurs at one point in space because something else happened at another point, with no visible means by which the "cause" can be related to the "effect," we say the two events are connected by a field. In radio work, the fields with which we are concerned are the electric and magnetic, and the combination of the two called the electromagnetic field.

A field has two important properties, intensity (magnitude) and direction. The field exerts a force on an object immersed in it; this force represents potential (ready-to-be-used) energy, so the potential of the field is a measure of the field intensity. The direction of the field is the direction in which the object on which the force is exerted will tend to move.

An electrically charged object in an electric field will be acted on by a force that will tend to move it in a direction determined by the direction of the field. Similarly, a magnet in a magnetic field will be subject to a force. Everyone has seen demonstrations of magnetic fields with pocket magnets, so intensity and direction are not hard to grasp.

A "static" field is one that neither moves nor changes in intensity. Such a field can be set up by a stationary electric charge (electrostatic field) or by a stationary magnet (magnetostatic field). But if either an electric or magnetic field is moving in space or changing in intensity, the motion or change sets up the other kind of field. That is, a changing electric field sets up a magnetic field, and a changing magnetic field generates an electric field. This interrelationship between magnetic and electric fields makes possible such things as the electromagnet and the electric motor. It also makes possible the electromagnetic waves by which radio communication is carried on, for such waves are simply traveling fields in which the energy is alternately handed back and forth between the electric and magnetic fields.

Lines of Force

Although no one knows what it is that composes the field itself, it is useful to invent a picture of it that will help in visualizing the forces and the way in which they act.

A field can be pictured as being made up of lines of force, or flux lines. These are purely imaginary threads that show, by the direction in which they lie, the direction the object on which the force is exerted will move. The number

of lines in a chosen cross section of the field is a measure of the *intensity* of the force. The number of lines per unit of area (square inch or square centimeter) is called the flux density.

ELECTRICITY AND THE ELECTRIC CURRENT

Everything physical is built up of atoms, particles so small that they cannot be seen even through the most powerful microscope. But the atom in turn consists of several different kinds of still smaller particles. One is the electron, essentially a small particle of electricity. The quantity or charge of electricity represented by the electron is, in fact, the smallest quantity of electricity that can exist. The kind of electricity associated with the electron is called negative.

An ordinary atom consists of a central core called the nucleus, around which one or more electrons circulate somewhat as the earth and other planets circulate around the sun. The nucleus has an electric charge of the kind of electricity called positive, the amount of its charge being just exactly equal to the sum of the negative charges on all the electrons associated with that nucleus.

The important fact about these two "opposite" kinds of electricity is that they are strongly attracted to each other. Also, there is a strong force of repulsion between two charges of the same kind. The positive nucleus and the negative electrons are attracted to each other, but two electrons will be repelled from each other and so will two nuclei.

In a normal atom the positive charge on the nucleus is exactly balanced by the negative charges on the electrons. However, it is possible for an atom to lose one of its electrons. When that happens the atom has a little less negative charge than it should - that is, it has a net positive charge. Such an atom is said to be ionized, and in this case the atom is a positive ion. If an atom picks up an extra electron, as it sometimes does, it has a net negative charge and is called a negative ion. A positive ion will attract any stray electron in the vicinity, including the extra one that may be attached to a nearby negative ion. In this way it is possible for electrons to travel from atom to atom. The movement of ions or electrons constitutes the electric current.

The amplitude of the current (its intensity or magnitude) is determined by the rate at which electric charge — an accumulation of electrons or ions of the same kind — moves past a point in a circuit. Since the charge on a single electron or

ion is extremely small, the number that must move as a group to form even a tiny current is almost inconceivably large.

Conductors and insulators

Atoms of some materials, notably metals and acids, will give up an electron readily, but atoms of other materials will not part with any of their electrons even when the electric force is extremely strong. Materials in which electrons or ions can be moved with relative ease are called conductors, while those that refuse to permit such movement are called nonconductors or insulators. The following list shows how some common materials are classified:

Conductors	Insulators	
Metals	Dry Air	Glass
Carbon	Wood	Rubber
Acids	Porcelain	Resins
	Textiles	_

Electromotive Force

The electric force or potential (called electromotive force, and abbreviated e.m.f.) that causes current flow may be developed in several ways. The action of certain chemical solutions on dissimilar metals sets up an e.m.f.; such a combination is called a cell, and a group of cells forms an electric battery. The amount of current that such cells can carry is limited, and in the course of current flow one of the metals is eaten away. The amount of electrical energy that can be taken from a battery consequently is rather small. Where a large amount of energy is needed it is usually furnished by an electric generator, which develops its e.m.f. by a combination of magnetic and mechanical means.

Direct and Alternating Currents

In picturing current flow it is natural to think of a single, constant force causing the electrons to move. When this is so, the electrons always move in the same direction through a path or circuit made up of conductors connected together in a continuous chain. Such a current is called a direct current, abbreviated d.c. It is the type of current furnished by batteries and by certain types of generators.

It is also possible to have an e.m.f. that periodically reverses. With this kind of e.m.f. the current flows first in one direction through the circuit and then in the other. Such an e.m.f. is called an alternating e.m.f., and the current is called an alternating current (abbreviated a.c.). The reversals (alternations) may occur at any rate from a few per second up to several billion per second. Two reversals make a cycle; in one cycle the force acts first in one direction, then in the other, and then returns to the first direction to begin the next cycle. The number of cycles in one second is called the frequency of the alternating current.

The difference between direct current and alternating current is shown in Fig. 2-1. In these graphs the horizontal axis measures time, in-

creasing toward the right away from the vertical axis. The vertical axis represents the amplitude or strength of the current, increasing in either the up or down direction away from the horizontal axis. If the graph is above the horizontal axis the current is flowing in one direction through the circuit (indicated by the + sign) and if it is below the horizontal axis the current is flowing in the reverse direction through the circuit (indicated by the - sign). Fig. 2-1A shows that, if we close the circuit — that is, make the path for the current complete - at the time indicated by X, the current instantly takes the amplitude indicated by the height A. After that, the current continues at the same amplitude as time goes on. This is an ordinary direct current.

In Fig. 2-1B, the current starts flowing with the amplitude A at time X, continues at that amplitude until time Y and then instantly ceases. After an interval YZ the current again begins to flow and the same sort of start-and-stop performance is repeated. This is an intermittent direct current. We could get it by alternately closing and opening a switch in the circuit. It is a direct current because the direction of current flow does not change; the graph is always on the + side of the horizontal axis.

In Fig. 2-1C the current starts at zero, increases in amplitude as time goes on until it reaches the amplitude A_1 while flowing in the + direction, then decreases until it drops to zero amplitude once more. At that time (X) the direction of the current flow reverses; this is indicated by the fact that the next part of the graph is below the axis. As time goes on the amplitude increases, with the current now flowing in the — direction, until it reaches amplitude A_2 . Then

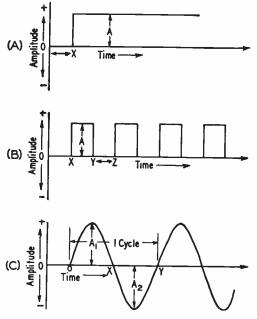


Fig. 2-1—Three types of current flow. A—direct current; B—intermittent direct current; C—alternating current.

Frequency and Wavelength

the amplitude decreases until finally it drops to zero (Y) and the direction reverses once more. This is an alternating current.

Waveforms

The type of alternating current shown in Fig. 2-1C is known as a sine wave. The variations in many a.c. waves are not so smooth, nor is one half-cycle necessarily just like the preceding one in shape. However, these complex waves can be shown to be the sum of two or more sine waves of frequencies that are exact integral (whole-number) multiples of some lower frequency. The lowest frequency is called the fundamental frequency, and the higher frequencies (2 times, 3 times the fundamental frequency, and so on) are called harmonics.

Fig. 2-2 shows how a fundamental and a second harmonic (twice the fundamental) might add to form a complex wave. Simply by changing the relative amplitudes of the two waves, as well as the times at which they pass through zero amplitude, an infinite number of waveshapes can be constructed from just a fundamental and second harmonic. Waveforms that are still more complex can be constructed if more harmonics are used.

Electrical Units

The unit of electromotive force is called the volt. An ordinary flashlight cell generates an e.m.f. of about 1.5 volts. The e.m.f. commonly supplied for domestic lighting and power is 115 volts, usually a.c. having a frequency of 60 cycles per second. The voltages used in radio receiving and transmitting circuits range from a few volts (usually a.c.) for filament heating to as high as several thousand d.c. volts for the operation of power tubes.

The flow of electric current is measured in amperes. One ampere is equivalent to the movement of many billions of electrons past a point in the circuit in one second. Currents in the neighborhood of an ampere are required for heating the filaments of small power tubes. The direct currents used in amateur radio equipment usually are not so large, and it is customary to measure such currents in milliamperes. One milliampere is equal to one one-thousandth of an ampere, or 1000 milliamperes equal one ampere.

A "d.c. ampere" is a measure of a steady current, but the "a.c. ampere" must measure a current that is continually varying in amplitude and periodically reversing direction. To put the two on the same basis, an a.c. ampere is defined as the current that will cause the same heating effect as one ampere of steady direct current. For sine-wave a.c., this effective (or r.m.s., for root mean square, the mathematical derivation) value is equal to the maximum (or peak) amplitude $(A_1 \text{ or } A_2 \text{ in Fig. 2-1C})$ multiplied by 0.707. The instantaneous value is the value that the current (or voltage) has at any selected instant in the cycle. If all the instantaneous values in a sine wave are averaged over a half-cycle, the resulting figure is the average value. It is equal to 0.636 times the maximum amplitude.

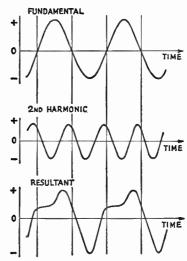


Fig. 2-2—A complex waveform. A fundamental (top) and second harmonic (center) added together, point by point at each instant, result in the waveform shown at the bottom. When the two components have the same polarity at a selected instant, the resultant is the simple sum of the two. When they have opposite polarities, the resultant is the difference; if the negative-polarity component is larger, the resultant is negative at that instant.

FREQUENCY AND WAVELENGTH

Frequency Spectrum

Frequencies ranging from about 15 to 15,000 cycles per second are called audio frequencies, because the vibrations of air particles that our ears recognize as sounds occur at a similar rate. Audio frequencies (abbreviated a.f.) are used to actuate loudspeakers and thus create sound waves.

Frequencies above about 15,000 cycles are called radio frequencies (r.f.) because they are useful in radio transmission. Frequencies all the way up to and beyond 10,000,000,000 cycles have been used for radio purposes. At radio frequencies the numbers become so large that it becomes convenient to use a larger unit than the cycle. Two such units are the kilocycle, which is equal to 1000 cycles and is abbreviated kc., and the megacycle, which is equal to 1,000,000 cycles or 1000 kilocycles and is abbreviated Mc.

The various radio frequencies are divided off into classifications for ready identification. These classifications, listed below, constitute the frequency spectrum so far as it extends for radio purposes at the present time.

Frequency	Classification	Abbreviation
10 to 30 kc.	Very-low frequencies	v.l.f.
30 to 300 kc.	Low frequencies	1.f.
300 to 3000 kc.	Medium frequencies	m.f.
3 to 30 Mc.	High frequencies	h.f.
30 to 300 Mc.	Very high frequencies	v.h.f.
300 to 3000 Mc.	Ultrahigh frequencies	u.h.f.
3000 to 30,000 Mc.	Superhigh frequencies	s.h.f.

Wavelength

Radio waves travel at the same speed as light —300,000,000 meters or about 186,000 miles a

second in space. They can be set up by a radiofrequency current flowing in a circuit, because the rapidly changing current sets up a magnetic field that changes in the same way, and the varying magnetic field in turn sets up a varying electric field. And whenever this happens, the two fields move outward at the speed of light.

Suppose an r.f. current has a frequency of 3,000,000 cycles per second. The fields will go through complete reversals (one cycle) in 1/3,000,000 second. In that same period of time the fields—that is, the wave—will move 300,000,000/3,000,000 meters, or 100 meters. By the time the wave has moved that distance the next cycle has begun and a new wave has started out. The first wave, in other words, covers a distance of 100 meters before the beginning of the next, and so on. This distance is the wavelength.

The longer the time of one cycle—that is, the lower the frequency—the greater the distance occupied by each wave and hence the longer the wavelength. The relationship between wavelength and frequency is shown by the formula

$$\lambda = \frac{300,000}{f}$$

where $\lambda = \text{Wavelength in meters}$ f = Frequency in kilocycles

or

$$\lambda = \frac{300}{f}$$

where $\lambda = \text{Wavelength in meters}$ f = Frequency in megacycles

Example: The wavelength corresponding to a frequency of 3650 kilocycles is

$$\lambda = \frac{300,000}{3650} = 82.2 \text{ meters}$$

RESISTANCE

Given two conductors of the same size and shape, but of different materials, the amount of current that will flow when a given e.m.f. is applied will be found to vary with what is called the resistance of the material. The lower the resistance, the greater the current for a given value of e.m.f.

Resistance is measured in ohms. A circuit has a resistance of one ohm when an applied e.m.f. of one volt causes a current of one ampere to flow. The resistivity of a material is the resistance, in ohms, of a cube of the material measuring one centimeter on each edge. One of the best conductors is copper, and it is frequently convenient, in making resistance calculations, to compare the resistance of the material under consideration with that of a copper conductor of the same size and shape. Table 2-I gives the ratio of the resistivity of various conductors to that of copper.

The longer the path through which the current flows the higher the resistance of that conductor. For direct current and low-frequency alternating currents (up to a few thousand cycles per second) the resistance is *inversely* proportional to the cross-sectional area of the path the current must travel; that is, given two conductors of the same material and having the same length, but differing in cross-sectional area, the one with the larger area will have the lower resistance.

Resistance of Wires

The problem of determining the resistance of a round wire of given diameter and length—or its opposite, finding a suitable size and length of wire to supply a desired amount of resistance—can be easily solved with the help of the copperwire table given in a later chapter. This table gives the resistance, in ohms per thousand feet, of each standard wire size.

Example: Suppose a resistance of 3.5 ohms is needed and some No. 28 wire is on hand. The wire table in Chapter 20 shows that No. 28 has a resistance of 66.17 ohms per thousand feet. Since the desired resistance is 3.5 ohms, the length of wire required will be

$$\frac{3.5}{66.17} \times 1000 = 52.89$$
 feet.

Or, suppose that the resistance of the wire in the circuit must not exceed 0.05 ohm and that the length of wire required for making the connections totals 14 feet. Then

$$\frac{14}{1000} \times R = 0.05 \text{ ohm}$$

where R is the maximum allowable resistance in ohms per thousand feet. Rearranging the formula gives

$$R = \frac{0.05 \times 1000}{14} = 3.57 \text{ ohms/1000 ft.}$$

Reference to the wire table shows that No. 15 is the smallest size having a resistance less than this value.

When the wire is not copper, the resistance values given in the wire table should be multiplied by the ratios given in Table 2-I to obtain the resistance.

TABLE 2-I

Relative Resistivity of Metals		
***	Resistivity	
Material	Compared to Copper	
Aluminum (pure)	1.6	
Brass	3.7–4.9	
Cadmium	4.4	
Chromium	1.8	
Copper (hard-drawn)	1.03	
Copper (annealed)	1.00	
Gold	1.4	
Iron (pure)	5.68	
Lead	12.8	
Nickel	5.1	
Phosphor Bronze	2.8–5.4	
Silver	0.94	
Steel		
Tin	6.7	
Zinc	3.4	

Types of resistors used in radio equipment. Those in the foreground with wire leads are carbon types, ranging in size from ½ watt at the left to 2 watts at the right. The larger resistors use resistance wire wound on ceramic tubes; sizes shown range from 5 watts to 100 watts. Three are of the adjustable type, having a sliding contact on an exposed section of the resistance winding.



Example: If the wire in the first example were iron instead of copper the length required for 3.5 ohms would be

$$\frac{3.5}{66.17 \times 5.65} \times 1000 = 9.35 \text{ feet.}$$

Temperature Effects

The resistance of a conductor changes with its temperature. Although it is seldom necessary to consider temperature in making resistance calculations for amateur work, it is well to know that the resistance of practically all metallic conductors increases with increasing temperature. Carbon, however, acts in the opposite way; its resistance decreases when its temperature rises. The temperature effect is important when it is necessary to maintain a constant resistance under all conditions. Special materials that have little or no change in resistance over a wide temperature range are used in that case.

Resistors

A "package" of resistance made up into a single unit is called a resistor. Resistors having the same resistance value may be considerably different in size and construction. The flow of current through resistance causes the conductor to become heated; the higher the resistance and the larger the current, the greater the amount of heat developed. Resistors intended for carrying large currents must be physically large so the heat can be radiated quickly to the surrounding air. If the resistor does not get rid of the heat quickly it may reach a temperature that will cause it to melt or burn.

Skin Effect

The resistance of a conductor is not the same for alternating current as it is for direct current. When the current is alternating there are internal effects that tend to force the current to flow mostly in the outer parts of the conductor. This decreases the effective cross-sectional area of the conductor, with the result that the resistance increases.

For low audio frequencies the increase in resistance is unimportant, but at radio frequencies this skin effect is so great that practically all the

current flow is confined within a few thousandths of an inch of the conductor surface. The r.f. resistance is consequently many times the d.c. resistance, and increases with increasing frequency. In the r.f. range a conductor of thin tubing will have just as low resistance as a solid conductor of the same diameter, because material not close to the surface carries practically no current.

Conductance

The reciprocal of resistance (that is, 1/R) is called conductance. It is usually represented by the symbol G. A circuit having large conductance has low resistance, and vice versa. In radio work the term is used chiefly in connection with vacuum-tube characteristics. The unit of conductance is the mho. A resistance of one ohm has a conductance of one mho, a resistance of 1000 ohms has a conductance of 0.001 mho, and so on. A unit frequently used in connection with vacuum tubes is the micromho, or one-millionth of a mho. It is the conductance of a resistance of one megohm.

OHM'S LAW

The simplest form of electric circuit is a battery with a resistance connected to its terminals, as shown by the symbols in Fig. 2-3. A complete circuit must have an unbroken path so current

Fig. 2-3—A simple cricuit consisting of a battery and resistor.



can flow out of the battery, through the apparatus connected to it, and back into the battery. The circuit is **broken**, or **open**, if a connection is removed at any point. A **switch** is a device for making and breaking connections and thereby closing or opening the circuit, either allowing current to flow or preventing it from flowing.

The values of current, voltage and resistance in a circuit are by no means independent of each other. The relationship between them is known as Ohm's Law. It can be stated as follows: The

Conver	TABLE 2-11 Conversion Factors for Fractional and Multiple Units		
To change from	To	Divide by	Multiply by
Units	Micro-units Milli-units Kilo-units Mega-units	1000 1,000,000	1,000,000
Micro-units	Milli-units Units	1000	
Milli-units	Micro-units Units	1000	1000
Kilo-units	Units Mega-units	1000	1000
Mega-units	Units Kilo-units		1,000,000 1000

current flowing in a circuit is directly proportional to the applied e.m.f. and inversely proportional to the resistance. Expressed as an equation, it is

$$I \text{ (amperes)} = \frac{E \text{ (volts)}}{R \text{ (ohms)}}$$

The equation above gives the value of current when the voltage and resistance are known. It may be transposed so that each of the three quantities may be found when the other two are known:

$$E = IR$$

(that is, the voltage acting is equal to the current in amperes multiplied by the resistance in ohms) and

$$R = \frac{E}{I}$$

(or, the resistance of the circuit is equal to the applied voltage divided by the current).

All three forms of the equation are used almost constantly in radio work. It must be remembered that the quantities are in volts, ohms and amperes; other units cannot be used in the equations without first being converted. For example, if the current is in milliamperes it must be changed to the equivalent fraction of an ampere before the value can be substituted in the equations.

Table 2-II shows how to convert between the various units in common use. The prefixes attached to the basic-unit name indicate the nature of the unit. These prefixes are:

For example, one microvolt is one-millionth of a volt, and one megohm is 1,000,000 ohms. There are therefore 1,000,000 microvolts in one volt, and 0.000001 megohm in one ohm.

The following examples illustrate the use of Ohm's Law:

The current flowing in a resistance of 20,000 ohms is 150 milliamperes. What is the voltage? Since the voltage is to be found, the equation to use is E=IR. The current must first be converted from milliamperes to amperes, and reference to the table shows that to do so it is necessary to divide by 1000. Therefore,

$$E = \frac{150}{1000} \times 20,000 = 3000 \text{ volts}$$

When a voltage of 150 is applied to a circuit the current is measured at 2.5 amperes. What is the resistance of the circuit? In this case R is the unknown, so

$$R = \frac{E}{I} = \frac{150}{2.5} = 60 \text{ ohms}$$

No conversion was necessary because the voltage and current were given in volts and amperes.

How much current will flow if 250 volts is applied to a 5000-ohm resistor? Since I is unknown

$$I = \frac{E}{R} = \frac{250}{5000} = 0.05$$
 ampere

Milliampere units would be more convenient for the current, and 0.05 amp. \times 1000 = 50 milliamperes.

SERIES AND PARALLEL RESISTANCES

Very few actual electric circuits are as simple as the illustration in the preceding section. Commonly, resistances are found connected in a

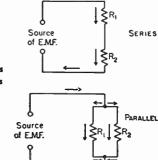


Fig. 2-4—Resistors connected in series and in parallel.

variety of ways. The two fundamental methods of connecting resistances are shown in Fig. 2-4. In the upper drawing, the current flows from the source of e.m.f. (in the direction shown by the arrow, let us say) down through the first resistance, R₁, then through the second, R₂, and then back to the source. These resistors are connected in series. The current everywhere in the circuit has the same value.

In the lower drawing the current flows to the common connection point at the top of the two resistors and then divides, one part of it flowing through R_1 and the other through R_2 . At the lower connection point these two currents again combine; the total is the same as the current that flowed into the upper common connection. In this case the two resistors are connected in parallel.

Resistors in Series

When a circuit has a number of resistances connected in series, the total resistance of the circuit is the sum of the individual resistances. If these are numbered R_1 , R_2 , R_3 , etc., then

 $R(\text{total}) = R_1 + R_2 + R_3 + R_4 + \dots$ where the dots indicate that as many resistors as necessary may be added.

Series and Parallel Resistance

Example: Suppose that three resistors are connected to a source of e.m.f. as shown in Fig. 2-5. The e.m.f. is 250 volts, R_1 is 5000 ohms, R_2 is 20,000 ohms, and R_8 is 8000 ohms. The total resistance is then

$$R = R_1 + R_2 + R_3 = 5000 + 20,000 + 8000$$

= 33,000 ohms

The current flowing in the circuit is then

$$I = \frac{E}{R} = \frac{250}{33,000} = 0.00757 \text{ amp.} = 7.57 \text{ ma.}$$

(We need not carry calculations beyond three significant figures, and often two will suffice because the accuracy of measurements is seldom better than a few per cent.)

Voltage Drop

Ohm's Law applies to any part of a circuit as well as to the whole circuit. Although the current is the same in all three of the resistances in the example, the total voltage divides among them. The voltage appearing across each resistor (the voltage drop) can be found from Ohm's Law.

Example: If the voltage across R_1 (Fig. 2-5) is called E_1 , that across R_2 is called E_2 , and that across R_3 is called E_3 , then

$$E_1 = IR_1 = 0.00757 \times 5000 = 37.9 \text{ volts}$$

 $E_2 = IR_2 = 0.00757 \times 20,000 = 151.4 \text{ volts}$
 $E_3 = IR_3 = 0.00757 \times 8000 = 60.6 \text{ volts}$

The applied voltage must equal the sum of the individual voltage drops:

$$E = E_1 + E_2 + E_3 = 37.9 + 151.4 + 60.6$$

= 249.9 volts

The answer would have been more nearly exact if the current had been calculated to more decimal places, but as explained above a very high order of accuracy is not necessary.

In problems such as this considerable time and trouble can be saved, when the current is small enough to be expressed in milliamperes, if the

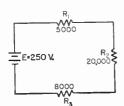


Fig. 2-5—An example of resistors in series. The solution of the circuit is worked out in the text.

resistance is expressed in kilohms rather than ohms. When resistance in kilohms is substituted directly in Ohm's Law the current will be in milliamperes if the e.m.f. is in volts.

Resistors in Parallel

In a circuit with resistances in parallel, the total resistance is *less* than that of the *lowest* value of resistance present. This is because the total current is always greater than the current in any individual resistor. The formula for finding the total resistance of resistances in parallel is

$$R = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} + \dots}$$

where the dots again indicate that any number

of resistors can be combined by the same method. For only two resistances in parallel (a very common case) the formula becomes

$$R = \frac{R_1 R_2}{R_1 + R_2}$$

Example: If a 500-ohm resistor is paralleled with one of 1200 ohms, the total resistance is

$$R = \frac{R_1 R_2}{R_1 + R_2} = \frac{500 \times 1200}{500 + 1200} = \frac{600,000}{1700}$$

It is probably easier to solve practical problems by a different method than the "reciprocal of reciprocals" formula. Suppose the three re-

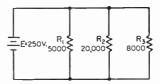


Fig. 2-6—An example of resistors in parallel. The solution is worked out in the text.

sistors of the previous example are connected in parallel as shown in Fig. 2-6. The same e.m.f., 250 volts, is applied to all three of the resistors. The current in each can be found from Ohm's Law as shown below, I_1 being the current through R_1 , I_2 the current through R_2 and I_3 the current through R_3 .

For convenience, the resistance will be expressed in kilohms so the current will be in milliamperes.

$$I_1 = \frac{E}{R_1} = \frac{250}{5} = 50 \text{ ma.}$$

$$I_3 = \frac{E}{R_2} = \frac{250}{20} = 12.5 \text{ ma.}$$

$$I_4 = \frac{E}{R_2} = \frac{250}{8} = 31.25 \text{ ma.}$$

The total current is

$$I = I_1 + I_2 + I_3 = 50 + 12.5 + 31.25$$

= 93.75 ma.

The total resistance of the circuit is therefore

$$R = \frac{E}{I} = \frac{250}{93.75} = 2.66 \text{ kilohms (} = 2660 \text{ ohms)}$$

Resistors in Series-Parallel

An actual circuit may have resistances both in parallel and in series. To illustrate, we use the same three resistances again, but now connected as in Fig. 2-7. The method of solving a circuit such as Fig. 2-7 is as follows: Consider R_2 and R_3 in parallel as though they formed a single resistor. Find their equivalent resistance. Then this resistance in series with R_1 forms a simple series circuit, as shown at the right in Fig. 2-7. An example of the arithmetic is given under the illustration.

Using the same principles, and staying within the practical limits, a value for R_2 can be computed that will provide a given voltage drop across R_3 or a given current through R_1 . Simple algebra is required.

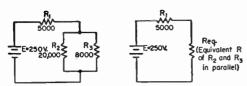


Fig. 2-7—An example of resistors in series-parallel. The equivalent circuit is at the right. The solution is worked out in the text.

Example: The first step is to find the equivalent resistance of R_3 and R_3 . From the formula for two resistances in parallel,

$$R_{\text{eq.}} = \frac{R_2 R_3}{R_2 + R_3} = \frac{20 \times 8}{20 + 8} = \frac{160}{28}$$

= 5.71 kilohms

The total resistance in the circuit is then

$$R = R_1 + R_{eq} = 5 + 5.71 \text{ kilohms}$$

= 10.71 kilohms

The current is

$$I = \frac{E}{R} = \frac{250}{10.71} = 23.3 \text{ ma.}$$

The voltage drops across R_1 and R_{eq} , are $E_1 = IR_1 = 23.3 \times 5 = 117$ volts $E_3 = IR_{eq}$, $= 23.3 \times 5.71 = 133$ volts

with sufficient accuracy. These total 250 volts, thus checking the calculations so far, because the sum of the voltage drops must equal the applied voltage. Since E_2 appears across both R_3 and R_5 .

$$I_1 = \frac{E_2}{R_1} = \frac{133}{20} = 6.65 \text{ ma.}$$

$$I_2 = \frac{E_2}{R_4} = \frac{133}{8} = 16.6 \text{ ma.}$$

where $I_3 = \text{Current through } R_3$ $I_3 = \text{Current through } R_3$

The total is 23.25 ma., which checks closely enough with 23.3 ma., the current through the whole circuit.

POWER AND ENERGY

Power—the rate of doing work—is equal to voltage multiplied by current. The unit of electrical power, called the watt, is equal to one volt multiplied by one ampere. The equation for power therefore is

$$P = EI$$
where $P = Power in watts$

$$E = E.m.f. in volts$$

$$I = Current in amperes$$

Common fractional and multiple units for power are the milliwatt, one one-thousandth of a watt, and the kilowatt, or one thousand watts.

Example: The plate voltage on a transmitting vacuum tube is 2000 volts and the plate current is 350 milliamperes. (The current must be changed to amperes before substitution in the formula, and so is 0.35 amp.) Then

$$P = EI = 2000 \times 0.35 = 700$$
 watts

By substituting the Ohm's Law equivalents for E and I, the following formulas are obtained for power:

$$P = \frac{E^3}{R}$$
$$P = I^2 R$$

These formulas are useful in power calculations when the resistance and either the current or voltage (but not both) are known.

Example: How much power will he used up in a 4000-ohm resistor if the voltage applied to it is 200 volts? From the equation

$$P = \frac{E^2}{R} = \frac{(200)^2}{4000} = \frac{40,000}{4000} = 10$$
 watts

Or, suppose a current of 20 milliamperes flows through a 300-ohm resistor. Then

$$P = I^{3}R = (0.02)^{3} \times 300 = 0.0004 \times 300$$

= 0.12 watt

Note that the current was changed from milliamperes to amperes before substitution in the formula.

Electrical power in a resistance is turned into heat. The greater the power the more rapidly the heat is generated. Resistors for radio work are made in many sizes, the smallest being rated to "dissipate" (or carry safely) about 1/4 watt. The largest resistors used in amateur equipment will dissipate about 100 watts.

Generalized Definition of Resistance

Electrical power is not always turned into heat. The power used in running a motor, for example, is converted to mechanical motion. The power supplied to a radio transmitter is largely converted into radio waves. Power applied to a loudspeaker is changed into sound waves. But in every case of this kind the power is completely "used up"-it cannot be recovered. Also, for proper operation of the device the power must be supplied at a definite ratio of voltage to current. Both these features are characteristics of resistance, so it can be said that any device that dissipates power has a definite value of "resistance." This concept of resistance as something that absorbs power at a definite voltage/current ratio is very useful, since it permits substituting a simple resistance for the load or power-consuming part of the device receiving power, often with considerable simplification of calculations. Of course, every electrical device has some resistance of its own in the more narrow sense, so a part of the power supplied to it is dissipated in that resistance and hence appears as heat even though the major part of the power may be converted to another form.

Efficiency

In devices such as motors and vacuum tubes, the object is to obtain power in some other form than heat. Therefore power used in heating is considered to be a loss, because it is not the useful power. The efficiency of a device is the useful power output (in its converted form) divided by the power input to the device. In a vacuum-tube transmitter, for example, the object is to convert power from a d.c. source into a.c. power at some radio frequency. The ratio of the r.f. power output to the d.c. input is the efficiency of the tube. That is,

$$Eff. = \frac{P_0}{P_1}$$

where Eff. = Efficiency (as a decimal) $P_{\circ} = \text{Power output (watts)}$

 $P_1 =$ Power input (watts)

Example: If the d.c. input to the tube is 100 watts and the r.f. power output is 60 watts, the efficiency is

$$Eff. = \frac{P_0}{P_1} = \frac{60}{100} = 0.6$$

Efficiency is usually expressed as a percentage; that is, it tells what per cent of the input power will be available as useful output. The efficiency in the above example is 60 per cent.

Energy

In residences, the power company's bill is for electric energy, not for power. What you pay for is the work that electricity does for you, not the rate at which that work is done. Electrical work

is equal to power multiplied by time; the common unit is the watt-hour, which means that a power of one watt has been used for one hour. That is,

$$W = PT$$

where W =Energy in watt-hours


P =Power in watts T =Time in hours

Other energy units are the **kilowatt-hour** and the **watt-second**. These units should be self-explanatory.

Energy units are seldom used in amateur practice, but it is obvious that a small amount of power used for a long time can eventually result in a "power" bill that is just as large as though a large amount of power had been used for a very short time.

CAPACITANCE

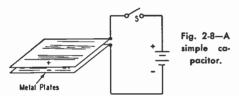Suppose two flat metal plates are placed close to each other (but not touching) and are connected to a battery through a switch, as shown in Fig. 2-8. At the instant the switch is closed, electrons will be attracted from the upper plate to the positive terminal of the battery, and the same number will be repelled into the lower plate from



the negative battery terminal. Enough electrons move into one plate and out of the other to make the e.m.f. between them the same as the e.m.f. of the battery.

If the switch is opened after the plates have been charged in this way, the top plate is left with a deficiency of electrons and the bottom plate with an excess. The plates remain charged despite the fact that the battery no longer is connected. However, if a wire is touched between the two plates (short-circuiting them) the excess electrons on the bottom plate will flow through the wire to the upper plate, thus restoring electrical neutrality. The plates have then been discharged.

The two plates constitute an electrical capacitor, and from the discussion above it should be clear that a capacitor possesses the property of storing electricity. (The energy actually is stored in the electric field between the plates.) It should also be clear that during the time the electrons are moving—that is, while the capacitor is being charged or discharged—a current is flowing in the circuit even though the circuit is "broken" by the gap between the capacitor plates. However, the current flows only during the time of charge and discharge, and this time is usually very short. There can be no continuous flow of direct current "through" a capacitor.

The charge or quantity of electricity that can be placed on a capacitor is proportional to the applied voltage and to the capacitance of the capacitor. The larger the plate area and the smaller the spacing between the plate the greater the capacitance. The capacitance also depends upon the kind of insulating material between the plates; it is smallest with air insulation, but substitution of other insulating materials for air may increase the capacitance many times. The ratio of the capacitance with some material other than air between the plates, to the capacitance of the same capacitor with air insulation, is called the dielectric constant of that particular insulating material. The material itself is called a dielectric. The dielectric constants of a number of materials commonly used as dielectrics in capacitors are

	Table 2-III			
Dielectric	Constants	and	Breakdown	Voltages

Dielectric

Puncture

Material	Constant *	Voltage **
Air	1.0	
Alsimag 196	5.7	240
Bakelite	4.4–5.4	300
Bakelite, mica-filled	4.7	325-375
Cellulose acetate	3.3-3.9	250-600
Fiber	5-7.5	150-180
Formica	4.6-4.9	450
Glass, window	7.6-8	200-250
Glass, Pyrex	4.8	335
Mica, ruby	5.4	3800-5600
Mycalex	7.4	250
Paper, Royalgrey	3.0	200
Plexiglass	2.8	990
Polyethylene	2.3	1200
Polystyrene	2.6	500-700
Porcelain	5.1-5.9	40-100
Quartz, fused	3.8	410
Steatite, low-loss	5.8	150-315
Teflon	2.1	1000-2000

given in Table 2-III. If a sheet of photographic glass is substituted for air between the plates of a capacitor, for example, the capacitance will be increased 7.5 times.

Units

The fundamental unit of capacitance is the farad, but this unit is much too large for practical work. Capacitance is usually measured in microfarads (abbreviated μf .) or micromicrofarads ($\mu \mu f$.). The microfarad is one-millionth



Fig. 2-9—A multiple-plate capacitor. Alternate plates are connected together.

of a farad, and the micromicrofarad is onemillionth of a microfarad. Capacitors nearly always have more than two plates, the alternate plates being connected together to form two sets as shown in Fig. 2-9. This makes it possible to attain a fairly large capacitance in a small space, since several plates of smaller individual area can be stacked to form the equivalent of a single large plate of the same total area. Also, all plates, except the two on the ends, are exposed to plates of the other group on both sides, and so are twice as effective in increasing the capacitance.

The formula for calculating capacitance is:

$$C = 0.224 \, \frac{KA}{d} \, (n - 1)$$

where $C = \text{Capacitance in } \mu \mu f$.


K = Dielectric constant of material between plates

A = Area of one side of one plate in square inches

d = Separation of plate surfaces in inches

n =Number of plates

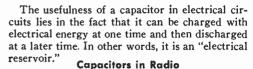
If the plates in one group do not have the same area as the plates in the other, use the area of the *smaller* plates.



The types of capacitors used in radio work differ considerably in physical size, construction, and capacitance. Some representative types are shown in the photograph. In variable capacitors (almost always constructed with air for the dielectric) one set of plates is made movable with respect to the other set so that the capacitance can be varied. Fixed capacitors—that is, assemblies having a single, non-adjustable value of capacitance—also can be made with metal plates and with air as the dielectric, but usually are constructed from plates of metal foil with a thin solid or liquid dielectric sandwiched in between. so that a relatively large capacitance can be secured in a small unit. The solid dielectrics commonly used are mica, paper and special ceramics. An example of a liquid dielectric is mineral oil. The electrolytic capacitor uses aluminum-foil plates with a semiliquid conducting chemical compound between them; the actual dielectric is a very thin film of insulating material that forms on one set of plates through electrochemical action when a d.c. voltage is applied to the capacitor. The capacitance obtained with a given plate area in an electrolytic capacitor is very large, compared with capacitors having other dielectrics, because the film is so extremely thin-much less than any thickness that is practicable with a solid dielectric.

Voltage Breakdown

When a high voltage is applied to the plates of a capacitor, a considerable force is exerted on the electrons and nuclei of the dielectric. Because the dielectric is an insulator the electrons do not become detached from atoms the way they do in conductors. However, if the force is great enough the dielectric will "break down"; usually it will puncture and may char (if it is solid) and permit current to flow. The breakdown voltage depends upon the kind and thickness of the dielectric, as shown in Table 2-III. It is not directly proportional to the thickness; that is, doubling

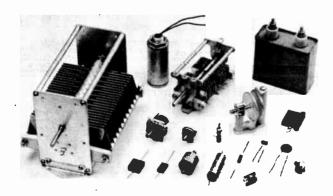

Fixed and variable capacitors. The large unit at the left is a transmitting-type variable capacitor for r.f. tank circuits. To its right are other airdielectric variables of different sizes ranging from the midget "air padder" to the medium-power tank capacitor at the top center. The cased capacitors in the top row are for power-supply filters, the cylindrical-can unit being an electrolytic and the rectangular one a paper-dielectric capacitor. Various types of mica, ceramic, and paper-dielectric capacitors are in the foreground.

the thickness does not quite double the breakdown voltage. If the dielectric is air or any other gas, breakdown is evidenced by a spark or arc between the plates, but if the voltage is removed the arc ceases and the capacitor is ready for use again. Breakdown will occur at a lower voltage between pointed or sharp-edged surfaces than between rounded and polished surfaces; consequently, the breakdown voltage between metal plates of given spacing in air can be increased

by buffing the edges of the plates.

Since the dielectric must be thick to withstand high voltages, and since the thicker the dielectric the smaller the capacitance for a given plate area, a high-voltage capacitor must have more plate area than a low-voltage one of the same capacitance. High-voltage high-capacitance capacitors are physically large.

cupacitors are physically large.

CAPACITORS IN SERIES AND PARALLEL

The terms "parallel" and "series" when used with reference to capacitors have the same circuit meaning as with resistances. When a number of capacitors are connected in parallel, as in Fig. 2-10, the total capacitance of the group is equal to the sum of the individual capacitances, so

$$C \text{ (total)} = C_1 + C_2 + C_3 + C_4 + \dots$$

However, if two or more capacitors are connected in series, as in the second drawing, the total capacitance is less than that of the smallest capacitor in the group. The rule for finding the capacitance of a number of series-connected capacitors is the same as that for finding the resistance of a number of parallel-connected resistors. That is,

C (total) =
$$\frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \frac{1}{C_4} + \cdots}$$

and, for only two capacitors in series,

$$C \text{ (total)} = \frac{C_1 C_2}{C_1 + C_2}$$

The same units must be used throughout; that is, all capacitances must be expressed in either μf . or $\mu \mu f$.; both kinds of units cannot be used in the same equation.

Capacitors are connected in parallel to obtain a larger total capacitance than is available in one unit. The largest voltage that can be applied safely to a group of capacitors in parallel is the voltage that can be applied safely to the one having the *lowest* voltage rating.

When capacitors are connected in series, the applied voltage is divided up among them; the situation is much the same as when resistors are in series and there is a voltage drop across each. However, the voltage that appears across each capacitor of a group connected in series is in


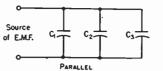


Fig. 2-10—Capacitors in parollel ond in series.

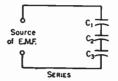

inverse proportion to its capacitance, as compared with the capacitance of the whole group.

Example: Three capacitors having capacitances of 1, 2, and 4 μ f., respectively, are connected in series as shown in Fig. 2-11. The total capacitance is

$$C = \frac{1}{\frac{1}{C_1} + \frac{1}{C_1} + \frac{1}{C_4}} = \frac{1}{\frac{1}{1} + \frac{1}{2} + \frac{1}{4}} = \frac{1}{\frac{7}{4}} = \frac{4}{\frac{7}{7}}$$

$$= 0.571 \text{ uf.}$$

The voltage across each capacitor is proportional to the total capacitance divided by the capacitance of the capacitor in question, so the voltage across C₁ is

$$E_1 = \frac{0.571}{1} \times 2000 = 1142 \text{ volts}$$

Similarly, the voltages across Cs and Cs are

$$E_2 = \frac{0.571}{2} \times 2000 = 571 \text{ volts}$$

 $E_3 = \frac{0.571}{4} \times 2000 = 286 \text{ volts}$

totaling approximately 2000 volts, the applied voltage.

Capacitors are frequently connected in series to enable the group to withstand a larger voltage (at the expense of decreased total capacitance) than any individual capacitor is rated to stand. However, as shown by the previous example, the applied voltage does not divide equally among the capacitors (except when all the capacitances are the same) so care must be taken to see that the voltage rating of no capacitor in the group is exceeded.

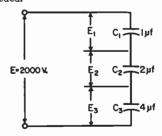


Fig. 2-11—An example of copacitors connected in series.

The solution to this arrangement is worked out in the

INDUCTANCE

It is possible to show that the flow of current through a conductor is accompanied by magnetic effects; a compass needle brought near the conductor, for example, will be deflected from its

normal north-south position. The current, in other words, sets up a magnetic field.

The transfer of energy to the magnetic field represents work done by the source of e.m.f. Power is required for doing work, and since power is equal to current multiplied by voltage, there must be a voltage drop in the circuit during the time in which energy is being stored in the field. This voltage "drop" (which has nothing to do with the voltage drop in any resistance in the circuit) is the result of an opposing voltage "induced" in the circuit while the field is building up to its final value. When the field becomes constant the induced e.m.f. or back e.m.f. disappears, since no further energy is being stored.

Since the induced e.m.f. opposes the e.m.f. of the source, it tends to prevent the current from rising rapidly when the circuit is closed. The amplitude of the induced e.m.f. is proportional to the rate at which the current is changing and to a constant associated with the circuit itself, called the inductance of the circuit.

Inductance depends on the physical characteristics of the conductor. If the conductor is formed into a coil, for example, its inductance is increased. A coil of many turns will have more inductance than one of few turns, if both coils are otherwise physically similar. Also, if a coil is placed on an iron core its inductance will be greater than it was without the magnetic core.

The polarity of an induced e.m.f. is always such as to oppose any change in the current in the circuit. This means that when the current in the circuit is increasing, work is being done against the induced e.m.f. by storing energy in the magnetic field. If the current in the circuit tends to decrease, the stored energy of the field returns to the circuit, and thus adds to the energy being supplied by the source of e.m.f. This tends to keep the current flowing even though the applied e.m.f. may be decreasing or be removed entirely.

The unit of inductance is the henry. Values of inductance used in radio equipment vary over a wide range. Inductance of several henrys is required in power-supply circuits (see chapter on

Power Supplies) and to obtain such values of inductance it is necessary to use coils of many turns wound on iron cores. In radio-frequency circuits, the inductance values used will be measured in millihenrys (a millihenry is one one-thousandth of a henry) at low frequencies, and in microhenrys (one one-millionth of a henry) at medium frequencies and higher. Although coils for radio frequencies may be wound on special iron cores (ordinary iron is not suitable) most r.f. coils made and used by amateurs are of the "air-core" type; that is, wound on an insulating support consisting of nonmagnetic material.

Every conductor has inductance, even though the conductor is not formed into a coil. The inductance of a short length of straight wire is small, but it may not be negligible because if the current through it changes its intensity rapidly enough the induced voltage may be appreciable. This will be the case in even a few inches of wire when an alternating current having a frequency of the order of 100 Mc. or higher is flowing. However, at much lower frequencies the inductance of the same wire could be left out of any calculations because the induced voltage would be negligibly small.

Calculating Inductance

The approximate inductance of single-layer air-core coils may be calculated from the simplified formula

$$L (\mu h.) = \frac{a^2 n^2}{9a + 10b}$$

where L = Inductance in microhenrys


a = Coil radius in inches


b = Coil length in inches

n =Number of turns

The notation is explained in Fig. 2-12. This

Fig. 2-12—Coil dimensions used in the inductance formula. The wire diameter does not enter into the formula.

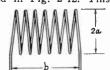

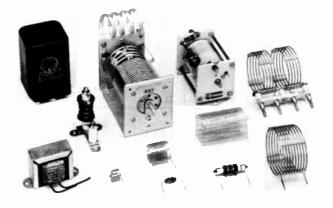

Inductors for power and radio frequencies. The two iron-core coils at the left are "chokes" for power-supply filters. The mounted air-core coils at the top center are adjustable inductors for transmitting tank circuits. The "pie-wound" coils at the left and in the foreground are radio-frequency choke coils. The remaining coils are typical of inductors used in r.f. tuned circuits, the larger sizes being used principally for transmit-

ters

Inductance

formula is a close approximation for coils having a length equal to or greater than 0.8a.

Example: Assume a coil having 48 turns wound 32 turns per inch and a diameter of $\frac{1}{2}$ 4 inch. Thus $a = 0.75 \div 2 = 0.375$, $b = 48 \div 32 = 1.5$, and a = 48. Substituting,

$$L = \frac{.375 \times .375 \times 48 \times 48}{(9 \times .375) + (10 \times 1.5)} = 17.6 \,\mu\text{h}.$$

To calculate the number of turns of a singlelayer coil for a required value of inductance,

$$n = \sqrt{\frac{L\left(9a + 10b\right)}{a^2}}$$

Example: Suppose an inductance of $10\mu h$. Is required. The form on which the coil is to be wound has a diameter of one inch and is long enough to accommodate a coil of $1\frac{1}{4}$ inches. Then a=0.5, b=1.25, and L=10. Substituting.

$$n = \sqrt{\frac{10(4.5 + 12.5)}{.5 \times .5}} = \sqrt{680} = 26.1 \text{ turns}$$

A 26-turn coil would be close enough in practical work. Since the coil will be 1.25 inches long, the number of turns per inch will be 26.1 ÷ 1.25 = 20.8. Consulting the wire table, we find that No. 17 enameled wire (or anything smaller) can be used. The proper inductance is obtained by winding the required number of turns on the form and then adjusting the spacing between the turns to make a uniformly-spaced coil 1.25 inches long.

Inductance Charts

Most inductance formulas lose accuracy when applied to small coils (such as are used in v.h.f. work and in low-pass filters built for reducing harmonic interference to television) because the conductor thickness is no longer negligible in comparison with the size of the coil. Fig. 2-13 shows the measured inductance of v.h.f. coils, and may be used as a basis for circuit design. Two curves are given: curve A is for coils wound to an inside diameter of ½ inch; curve B is for coils of ¾-inch inside diameter. In both curves the wire size is No. 12, winding pitch 8 turns to the inch (½ inch center-to-center turn spacing). The inductance values given include leads ½ inch long.

The charts of Figs. 2-14 and 2-15 are useful for rapid determination of the inductance of coils of the type commonly used in radio-frequency circuits in the range 3-30 Mc. They are of sufficient accuracy for most practical work. Given the coil length in inches, the curves show the multiplying factor to be applied to the inductance value given in the table below the curve for a coil of the same diameter and number of turns per inch.

Example: A coil 1 inch in diameter is $1\frac{1}{4}$ inches long and has 20 turns. Therefore it has 16 turns per inch, and from the table under Fig. 2-15 it is found that the reference inductance for a coil of this diameter and number of turns per inch is $16.8 \ \mu h$. From curve B in the figure the multiplying factor is 0.35, so the inductance is

$$16.8 \times 0.35 = 5.9 \mu h.$$

The charts also can be used for finding suitable dimensions for a coil having a required value of inductance.

Example: A coil having an inductance of 12 μ h. is required. It is to be wound on a form having a diameter of 1 inch, the length available for the winding being not more than 1½ inches. From Fig. 2-15, the multiplying factor for a 1-inch diameter coil (curve B) having the maximum possible length of 1½ inches is 0.35. Hence the number of turns per inch must be chosen for a reference inductance of at least 12/0.35, or 34 μ h. From the Table under Fig. 2-15 it is seen that 16 turns per inch (reference inductance 16.8 μ h.) is too small. Using 32 turns per inch, the multiplying factor is 12/68, or 0.177, and from curve B this corresponds to a coil length of ¾ inch. There will be 24 turns in this length, since the winding "pitch" is 32 turns per inch.

Machine-wound coils with the diameters and turns per inch given in the tables are available in many radio stores, under the trade names of "B&W Miniductor" and "Illumitronic Air Dux."

IRON-CORE COILS

Permeability

Suppose that the coil in Fig. 2-16 is wound on an iron core having a cross-sectional area of 2 square inches. When a certain current is sent through the coil it is found that there are 80,000 lines of force in the core. Since the area is 2 square inches, the flux density is 40,000 lines per square inch. Now suppose that the iron core is removed and the same current is maintained in the coil, and that the flux density without the iron core is found to be 50 lines per square inch. The ratio of the flux density with the given core material to the flux density (with the same coil and same current) with an air core is called the permeability of the material. In this case the permeability of the iron is 40,000/50 = 800. The inductance of the coil is increased 800 times by inserting the iron core since, other things being equal, the inductance will be proportional to the magnetic flux through the coil.

The permeability of a magnetic material varies with the flux density. At low flux densities (or with an air core) increasing the current through

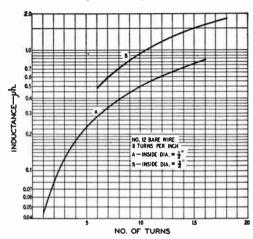


Fig. 2-13—Measured inductance of coils wound with No. 12 bare wire, 8 turns to the inch. The values include half-inch leads.

the coil will cause a proportionate increase in flux, but at very high flux densities, increasing the current may cause no appreciable change in the flux. When this is so, the iron is said to be saturated. Saturation causes a rapid decrease in permeability, because it decreases the ratio of flux lines to those obtainable with the same current and an air core. Obviously, the inductance of an iron-core inductor is highly dependent upon the current flowing in the coil. In an air-core coil, the inductance is independent of current because air does not saturate.

Iron core coils such as the one sketched in Fig. 2-16 are used chiefly in power-supply equipment. They usually have direct current flowing through the winding, and the variation in induct-

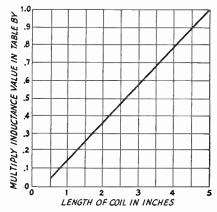


Fig. 2-14—Factor to be applied to the inductance of coils listed in the table below, for coil lengths up to 5 inches.

Coil diameter, Inches	No. of turns per inch	Inductance in µh.
11/4	4 6 8 10 16	2.75 6.3 11.2 17.5 42.5
11/2	4 6 8 10 16	3.9 8.8 15.6 24.5 63
134	4 6 8 10 16	5.2 11.8 21 33 85
2	4 6 8 10 16	6.6 15 26.5 42 108
21/2	4 6 8 10	10.2 23 41 64
3	4 6 8 10	14 31.5 56 89

ance with current is usually undesirable. It may be overcome by keeping the flux density below the saturation point of the iron. This is done by opening the core so that there is a small "air gap," as indicated by the dashed lines. The magnetic "resistance" introduced by such a gap is so large—even though the gap is only a small fraction of an inch—compared with that of the iron that the gap, rather than the iron, controls the

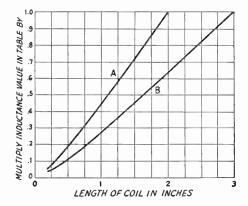


Fig. 2-15—Factor to be applied to the inductance of coils listed in the table below, as a function of coil length.

Use curve A for coils marked A, curve B for coils marked B.

Coil diameter, Inches	No. of turns per inch	Inductance in µh.
3/2	4	0.18
1/2 (A)	6	0.40
	8	0.72
	10	1.12
	16	2.9
	32	12
3-fs	4	0.28
(A)	6	0.62
	8	1.1
	10	1.7
	16	4.4
	32	18
3/4	4	0.6
(B)	6	1.35
	8	2.4
	10	3.8
	16	9.9
	32	40
1	4	1.0
(B)	6 8	2.3
		4.2
	10	6.6
	16	16.8
	32	68

flux density. This reduces the inductance, but makes it practically constant regardless of the value of the current.

Eddy Currents and Hysteresis

When alternating current flows through a coil wound on an iron core an e.m.f. will be induced, as previously explained, and since iron is a conductor a current will flow in the core. Such currents (called eddy currents) represent a waste

Inductance 29

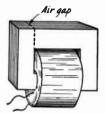


Fig. 2-16—Typical construction of an iron-core inductor. The small air gap prevents magnetic saturation of the iron and thus maintains the inductance at high currents.

of power because they flow through the resistance of the iron and thus cause heating. Eddy-current losses can be reduced by laminating the core; that is, by cutting it into thin strips. These strips or laminations must be insulated from each other by painting them with some insulating material such as varnish or shellac.

There is also another type of energy loss: the iron tends to resist any change in its magnetic state, so a rapidly-changing current such as a.c. is forced continually to supply energy to the iron to overcome this "inertia." Losses of this sort are called hysteresis losses.

Eddy-current and hysteresis losses in iron increase rapidly as the frequency of the alternating current is increased. For this reason, ordinary iron cores can be used only at power and audio frequencies—up to, say, 15,000 cycles. Even so, a very good grade of iron or steel is necessary if the core is to perform well at the higher audio frequencies. Iron cores of this type are completely useless at radio frequencies.


For radio-frequency work, the losses in iron cores can be reduced to a satisfactory figure by grinding the iron into a powder and then mixing it with a "binder" of insulating material in such a way that the individual iron particles are insulated from each other. By this means cores can be made that will function satisfactorily even through the v.h.f. range—that is, at frequencies up to perhaps 100 Mc. Because a large part of the magnetic path is through a nonmagnetic material, the permeability of the iron is low compared with the values obtained at power-supply frequencies. The core is usually in the form of a "slug" or cylinder which fits inside the insulating form on which the coil is wound. Despite the fact that, with this construction, the major portion of the magnetic path for the flux is in air, the slug is quite effective in increasing the coil inductance. By pushing the slug in and out of the coil the inductance can be varied over a considerable range.

INDUCTANCES IN SERIES AND PARALLEL

When two or more inductors are connected in series (Fig. 2-17, left) the total inductance is equal to the sum of the individual inductances, provided the coils are sufficiently separated so that no coil is in the magnetic field of another. That is,

$$L_{\text{total}} = L_1 + L_2 + L_3 + L_4 + \dots$$

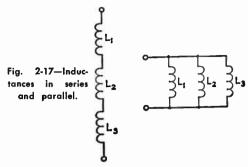If inductors are connected in parallel (Fig. 2-17, right)—and the coils are separated sufficiently,



the total inductance is given by

$$L_{\text{total}} = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \frac{1}{L_4} + \dots}$$

and for two inductances in parallel,

$$L=\frac{L_1L_2}{L_1+L_2}$$

Thus the rules for combining inductances in series and parallel are the same as for resistances, if the coils are far enough apart so that each is unaffected by another's magnetic field. When this is not so the formulas given above cannot be used.

MUTUAL INDUCTANCE

If two coils are arranged with their axes on the same line, as shown in Fig. 2-18, a current sent through Coil 1 will cause a magnetic field which "cuts" Coil 2. Consequently, an e.m.f. will be induced in Coil 2 whenever the field strength is changing. This induced e.m.f. is similar to the e.m.f. of self-induction, but since it appears in the second coil because of current flowing in the first, it is a "mutual" effect and results from the mutual inductance between the two coils.

If all the flux set up by one coil cuts all the turns of the other coil the mutual inductance has its maximum possible value. If only a small part of the flux set up by one coil cuts the turns of the other the mutual inductance is relatively small. Two coils having mutual inductance are said to be coupled.

The ratio of actual mutual inductance to the maximum possible value that could theoretically be obtained with two given coils is called the coefficient of coupling between the coils. It is frequently expressed as a percentage. Coils that

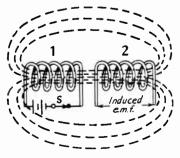


Fig. 2-18—Mutu al inductance. When the switch, S, is closed current flows through coil No. 1, setting up a magnetic field that induces an e.m.f. in the turns of coil No. 2.

have nearly the maximum possible (coefficient = 1 or 100%) mutual inductance are said to be closely, or tightly, coupled, but if the mutual inductance is relatively small the coils are said to be loosely coupled. The degree of coupling depends upon the physical spacing between the coils and how they are placed with respect to each other. Maximum coupling exists when they have a common axis and are as close together as pos-

sible (one wound over the other). The coupling is least when the coils are far apart or are placed so their axes are at right angles.

The maximum possible coefficient of coupling is closely approached only when the two coils are wound on a closed iron core. The coefficient with air-core coils may run as high as 0.6 or 0.7 if one coil is wound over the other, but will be much less if the two coils are separated.

TIME CONSTANT

Capacitance and Resistance

Connecting a source of e.m.f. to a capacitor causes the capacitor to become charged to the full e.m.f. practically instantaneously, if there is no resistance in the circuit. However, if the circuit contains resistance, as in Fig. 2-19A, the resistance limits the current flow and an appreciable length of time is required for the e.m.f. between the capacitor plates to build up to the same value as the e.m.f. of the source. During this "building-up" period the current gradually decreases from its initial value, because the increasing e.m.f. stored on the capacitor offers increasing opposition to the steady e.m.f. of the source.

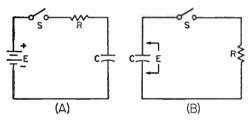


Fig. 2-19—Illustrating the time constant of an RC circuit.

Theoretically, the charging process is never really finished, but eventually the charging current drops to a value that is smaller than anything that can be measured. The time constant of such a circuit is the length of time, in seconds, required for the voltage across the capacitor to reach 63 per cent of the applied e.m.f. (this figure is chosen for mathematical reasons). The voltage across the capacitor rises with time as shown by Fig. 2-20.

The formula for time constant is

$$T = RC$$

where T = Time constant in seconds C = Capacitance in faradsR = Resistance in ohms

If C is in microfarads and R in megohms, the time constant also is in seconds. These units usually are more convenient.

Example: The time constant of a 2-\(\mu f. \) capabitor and a 250,000-ohm (0.25 megohm) resistor is

 $T = RC = 0.25 \times 2 = 0.5$ second If the applied e.m.f. is 1000 volts, the voltage between the capacitor plates will be 630 volts at the end of $\frac{1}{2}$ second.


If a charged capacitor is discharged through a

resistor, as indicated in Fig. 2-19B, the same time constant applies. If there were no resistance, the capacitor would discharge instantly when S was closed. However, since R limits the current flow the capacitor voltage cannot instantly go to zero, but it will decrease just as rapidly as the capacitor can rid itself of its charge through R. When the capacitor is discharging through a resistance, the time constant (calculated in the same way as above) is the time, in seconds, that it takes for the capacitor to lose 63 per cent of its voltage; that is, for the voltage to drop to 37 per cent of its initial value.

Example: If the capacitor of the example above is charged to 1000 volts, it will discharge to 370 volts in ½ second through the 250,000-ohm resistor.

Inductance and Resistance

A comparable situation exists when resistance and inductance are in series. In Fig. 2-21, first consider L to have no resistance and also assume that R is zero. Then closing S would tend to

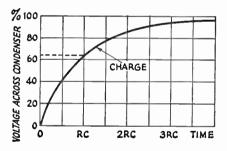

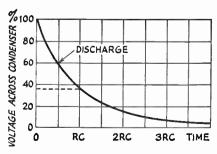


Fig. 2-20—How the voltage across a capacitor rises, with time, when charged through a resistor. The lower curve shows the way in which the voltage decreases across the capacitor terminals on discharging through the same resistor.

Time Constant 31

send a current through the circuit. However, the instantaneous transition from no current to a finite value, however small, represents a very rapid *change* in current, and a *back e.m.f.* is developed by the self-inductance of L that is practically equal and opposite to the applied e.m.f. The result is that the initial current is very small.

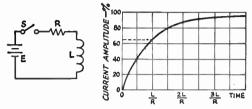


Fig. 2-21-Time constant of an LR circuit.

The back e.m.f. depends upon the *change* in current and would cease to offer opposition if the current did not continue to increase. With no resistance in the circuit (which would lead to an infinitely large current, by Ohm's Law) the current would increase forever, always growing just fast enough to keep the e.m.f. of self-induction equal to the applied e.m.f.

When resistance is in series, Ohm's Law sets a limit to the value that the current can reach. The back e.m.f. generated in L has only to equal the difference between E and the drop across R, because that difference is the voltage actually applied to L. This difference becomes smaller as the current approaches the final Ohm's Law value. Theoretically, the back e.m.f. never quite disappears and so the current never quite reaches the Ohm's Law value, but practically the difference becomes unmeasurable after a time. The time constant of an inductive circuit is the time in seconds required for the current to reach 63 per cent of its final value. The formula is

$$T = \frac{L}{R}$$

where T = Time constant in seconds

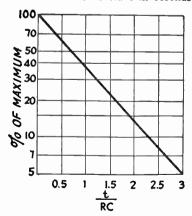


Fig. 2-22—Voltage across capacitor terminals in a discharging RC circuit, in terms of the initial charged voltage. To obtain time in seconds, multiply the factor t/RC by the time constant of the circuit.

L = Inductance in henrysR = Resistance in ohms

The resistance of the wire in a coil acts as if it were in series with the inductance.

Example: A coil having an inductance of 20 henrys and a resistance of 100 ohms has a time constant of

$$T = \frac{L}{R} = \frac{20}{100} = 0.2$$
 second

if there is no other resistance in the circuit. If a d.c. e.m.f. of 10 volts is applied to such a coil, the final current, by Ohm's Law, is

$$I = \frac{E}{R} = \frac{10}{100} = 0.1$$
 amp. or 100 ma,

The current would rise from zero to 63 milliamperes in 0.2 second after closing the switch.

An inductor cannot be "discharged" in the same way as a capacitor, because the magnetic field disappears as soon as current flow ceases. Opening S does not leave the inductor "charged." The energy stored in the magnetic field instantly returns to the circuit when S is opened. The rapid disappearance of the field causes a very large voltage to be induced in the coil-ordinarily many times larger than the voltage applied, because the induced voltage is proportional to the speed with which the field changes. The common result of opening the switch in a circuit such as the one shown is that a spark or arc forms at the switch contacts at the instant of opening. If the inductance is large and the current in the circuit is high, a great deal of energy is released in a very short period of time. It is not at all unusual for the switch contacts to burn or melt under such circumstances. The spark or arc at the opened switch can be reduced or suppressed by connecting a suitable capacitor and resistor in series across the contacts.

Time constants play an important part in numerous devices, such as electronic keys, timing and control circuits, and shaping of keying characteristics by vacuum tubes. The time constants of circuits are also important in such applications as automatic gain control and noise limiters. In nearly all such applications a resistance-capacitance (RC) time constant is involved, and it is usually necessary to know the voltage across the capacitor at some time interval larger or smaller than the actual time constant of the circuit as given by the formula above. Fig. 2-22 can be used for the solution of such problems, since the curve gives the voltage across the capacitor, in terms of percentage of the initial charge, for percentages between 5 and 100, at any time after discharge begins.

Example: A 0.01- μ f. capacitor is charged to 150 volts and then allowed to discharge through a 0.1-megohm resistor. How long will it take the voltage to fall to 10 volts? In percentage, 10/150 = 6.7%. From the chart, the factor corresponding to 6.7% is 2.7. The time constant of the circuit is equal to $RC = 0.1 \times 0.01 = 0.001$. The time is therefore 2.7 $\times 0.001 = 0.0027$ second, or 2.7 milliseconds.

ALTERNATING CURRENTS

PHASE

The term phase essentially means "time," or the time interval between the instant when one thing occurs and the instant when a second related thing takes place. The later event is said to lag the earlier, while the one that occurs first is said to lead. In a.c. circuits the current amplitude changes continuously, so the concept of phase or time becomes important. Phase can be measured in the ordinary time units, such as the second, but there is a more convenient method: Since each a.c. cycle occupies exactly the same amount of time as every other cycle of the same frequency, we can use the cycle itself as the time unit. Using the cycle as the time unit makes the specification or measurement of phase independent of the frequency of the current, so long as only one frequency is under consideration at a time. When two or more frequencies are to be considered, as in the case where harmonics are present, the phase measurements are made with respect to the lowest, or fundamental, frequency.

The time interval or "phase difference" under consideration usually will be less than one cycle. Phase difference could be measured in decimal parts of a cycle, but it is more convenient to divide the cycle into 360 parts or degrees. A phase degree is therefore 1/360 of a cycle. The reason for this choice is that with sine-wave alternating current the value of the current at any instant is proportional to the sine of the angle that corresponds to the number of degrees—that is, length of time—from the instant the cycle began. There is no actual "angle" associated with an alternating current. Fig. 2-23 should help make this method of measurement clear.

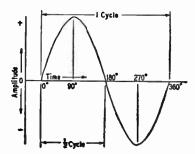


Fig. 2-23—An a.c. cycle is divided off into 360 degrees that are used as a measure of time or phase.

Measuring Phase

The phase difference between two currents of the same frequency is the time or angle difference between corresponding parts of cycles of the two currents. This is shown in Fig. 2-24. The current labeled A leads the one marked B by 45 degrees, since A's cycles begin 45 degrees earlier in time. It is equally correct to say that B lags A by 45 degrees.

Two important special cases are shown in

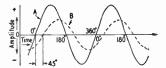


Fig. 2-24—When two waves of the same frequency start their cycles at slightly different times, the time difference or phase difference is measured in degrees. In this drawing wave B starts 45 degrees (one-eighth cycle) later than wave A, and so lags 45 degrees behind A.

Fig. 2-25. In the upper drawing B lags 90 degrees behind A; that is, its cycle begins just one-quarter cycle later than that of A. When one wave is passing through zero, the other is just at its maximum point.

In the lower drawing A and B are 180 degrees out of phase. In this case it does not matter which one is considered to lead or lag. B is always positive while A is negative, and vice versa. The two waves are thus *completely* out of phase.

The waves shown in Figs. 2-24 and 2-25 could represent current, voltage, or both. A and B might be two currents in separate circuits, or A might represent voltage and B current in the same circuit. If A and B represent two currents in the same circuit (or two voltages in the same circuit) the total or resultant current (or voltage) also is a sine wave, because adding any number of sine waves of the same frequency always gives a sine wave also of the same frequency.

Phase in Resistive Circuits

When an alternating voltage is applied to a resistance, the current flows exactly in step with the voltage. In other words, the voltage and current are in phase. This is true at any frequency if the resistance is "pure"—that is, is free from the reactive effects discussed in the next section. Practically, it is often difficult to obtain a purely

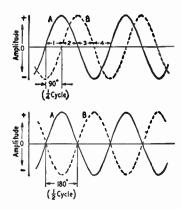


Fig. 2-25—Two important special cases of phase difference. In the upper drawing, the phase difference between A and B is 90 degrees; in the lower drawing the phase difference is 180 degrees.

Alternating Currents

resistive circuit at radio frequencies, because the reactive effects become more pronounced as the frequency is increased.

In a purely resistive circuit, or for purely resistive parts of circuits, Ohm's Law is just as valid for a.c. of any frequency as it is for d.c.

REACTANCE

Alternating Current in Capacitance

In Fig. 2-26 a sine-wave a.c. voltage having a maximum value of 100 volts is applied to a capacitor. In the period OA, the applied voltage increases from zero to 38 volts; at the end of this period the capacitor is charged to that voltage. In interval AB the voltage increases to 71 volts; that is, 33 volts additional. In this interval a smaller quantity of charge has been added than in OA, because the voltage rise during interval AB is smaller. Consequently the average current during AB is smaller than during OA. In the third interval, BC, the voltage rises from 71 to 92 volts, an increase of 21 volts. This is less than the voltage increase during AB, so the quantity of electricity added is less; in other words, the average current during interval BC is still smaller. In the fourth interval, CD, the voltage increases only 8 volts; the charge added is smaller than in any preceding interval and therefore the current also is smaller.

By dividing the first quarter cycle into a very large number of intervals it could be shown that the current charging the capacitor has the shape of a sine wave, just as the applied voltage does. The current is largest at the beginning of the cycle and becomes zero at the maximum value of the voltage, so there is a phase difference of 90 degrees between the voltage and current. During the first quarter cycle the current is flowing in the normal direction through the circuit, since the capacitor is being charged. Hence the current is positive, as indicated by the dashed line in Fig. 2-26.

In the second quarter cycle—that is, in the time from D to H, the voltage applied to the capacitor decreases. During this time the capacitor loses its charge. Applying the same reasoning, it is plain that the current is small in interval DE and continues to increase during each succeeding interval. However, the current is flowing against the applied voltage because the capacitor is discharging into the circuit. The current flows in

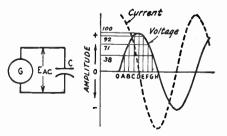


Fig. 2-26—Voltage and current phase relationships when an alternating voltage is applied to a capacitor.

the negative direction during this quarter cycle.

The third and fourth quarter cycles repeat the events of the first and second, respectively, with this difference—the polarity of the applied voltage has reversed, and the current changes to correspond. In other words, an alternating current flows in the circuit because of the alternate charging and discharging of the capacitance. As shown by Fig. 2-26, the current starts its cycle 90 degrees before the voltage, so the current in a capacitor leads the applied voltage by 90 degrees.

Capacitive Reactance

The quantity of electric charge that can be placed on a capacitor is proportional to the applied e.m.f. and the capacitance. This amount of charge moves back and forth in the circuit once each cycle, and so the *rate* of movement of charge—that is, the current—is proportional to voltage, capacitance and frequency. If the effects of capacitance and frequency are lumped together, they form a quantity that plays a part similar to that of resistance in Ohm's Law. This quantity is called reactance, and the unit for it is the ohm, just as in the case of resistance. The formula for it is

 $X_{\rm C} = \frac{1}{2\pi fC}$

where X_0 = Capacitive reactance in ohms f = Frequency in cycles per second

C =Capacitance in farads

 $\pi = 3.14$

Although the unit of reactance is the ohm, there is no power dissipation in reactance. The energy stored in the capacitor in one quarter of the cycle is simply returned to the circuit in the next.

The fundamental units (cycles per second, farads) are too large for practical use in radio circuits. However, if the capacitance is in microfarads and the frequency is in megacycles, the reactance will come out in ohms in the formula.

Example: The reactance of a capacitor of 470 $\mu\mu$ f. (0.00047 μ f.) at a frequency of 7150

$$X = \frac{1}{2\pi fC} = \frac{1}{6.28 \times 7.15 \times 0.00047} = 47.4 \text{ ohms}$$

Inductive Reactance

When an alternating voltage is applied to a pure inductance (one with no resistance—all practical inductors have resistance) the current is again 90 degrees out of phase with the applied voltage. However, in this case the current lags 90 degrees behind the voltage—the opposite of the capacitor current-voltage relationship.

The primary cause for this is the back e.m.f. generated in the inductance, and since the amplitude of the back e.m.f. is proportional to the rate at which the current changes, and this in turn is proportional to the frequency, the amplitude of the current is inversely proportional to the applied frequency. Also, since the back e.m.f. is proportional to inductance for a given rate of current change, the current flow is inversely propor-

tional to inductance for a given applied voltage and frequency. (Another way of saying this is that just enough current flows to generate an induced e.m.f. that equals and opposes the applied voltage.)

The combined effect of inductance and frequency is called inductive reactance, also expressed in ohms, and the formula for it is

$$X_L = 2\pi f L$$

where $X_L =$ Inductive reactance in ohms f = Frequency in cycles per second L = Inductance in henrys $\pi = 3.14$

Example: The reactance of a coil having an inductance of 8 henrys, at a frequency of 120 cycles, is

 $X_L = 2\pi f L = 6.28 \times 120 \times 8 = 6029$ ohms

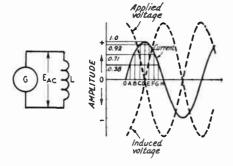


Fig. 2-27—Phase relationships between voltage and current when an alternating voltage is applied to an inductance.

In radio-frequency circuits the inductance values usually are small and the frequencies are large. If the inductance is expressed in millihenrys and the frequency in kilocycles, the conversion factors for the two units cancel, and the formula for reactance may be used without first conversion is necessary if the inductance is in microhenrys and the frequency is in megacycles.

Example: The reactance of a 15-microhenry coil at a frequency of 14 Mc. is

 $X_L = 2\pi f L = 6.28 \times 14 \times 15 = 1319$ ohms

The resistance of the wire of which the coil is wound has no effect on the reactance, but simply acts as though it were a separate resistor connected in series with the coil.

Ohm's Law for Reactance

Ohn's Law for an a.c. circuit containing only reactance is

$$I = \frac{E}{X}$$

$$E = IX$$

$$X = \frac{E}{I}$$

where E = E.m.f. in volts I = Current in amperes X = Reactance in ohms

The reactance in the circuit may, of course, be

either inductive or capacitive.

Example: If a current of 2 amperes is flowing through the capacitor of the earlier example (reactance = 47.4 ohms) at 7150 kc., the voltage drop across the capacitor is

$$E = IX = 2 \times 47.4 = 94.8 \text{ volts}$$

If 400 volts at 120 cycles is applied to the 8henry inductor of the earlier example, the current through the coil will be

$$I = \frac{E}{X} = \frac{400}{6029} = 0.0663$$
 amp. (66.3 ma.)

Reactance Chart

The accompanying chart, Fig. 2-28, shows the reactance of capacitances from 1 $\mu\mu$ f. to 100 μ f., and the reactance of inductances from 0.1 μ h. to 10 henrys, for frequencies between 100 cycles and 100 megacycles per second. The approximate value of reactance can be read from the chart or, where more exact values are needed, the chart will serve as a check on the order of magnitude of reactances calculated from the formulas given above, and thus avoid "decimal-point errors".

Reactances in Series and Parallel

When reactances of the same kind are connected in series or parallel the resultant reactance is that of the resultant inductance or capacitance. This leads to the same rules that are used when determining the resultant resistance when resistors are combined. That is, for series reactances of the same kind the resultant reactance is

$$X = X_1 + X_2 + X_3 + X_4$$

and for reactances of the same kind in parallel the resultant is

$$X = \frac{1}{\frac{1}{X_1} + \frac{1}{X_2} + \frac{1}{X_4} + \frac{1}{X_4}}$$

or for two in parallel,

$$X = \frac{X_1 X_2}{X_1 + X_2}$$

The situation is different when reactances of opposite kinds are combined. Since the current in a capacitance leads the applied voltage by 90 degrees and the current in an inductance lags the applied voltage by 90 degrees, the voltages at the terminals of opposite types of reactance are 180 degrees out of phase in a series circuit (in which the current has to be the same through all elements), and the currents in reactances of opposite types are 180 degrees out of phase in a parallel circuit (in which the same voltage is applied to all elements). The 180-degree phase relationship means that the currents or voltages are of opposite polarity, so in the series circuit of Fig. 2-29A the voltage E_L across the inductive reactance X_L is of opposite polarity to the voltage E_0 across the capacitive reactance X_0 . Thus if we call X_L "positive" and X_0 "negative" (a common convention) the applied voltage E_{A0} is $E_L - E_0$. In the parallel circuit at B the total current, I, is equal to $I_L - I_C$, since the currents are 180 degrees out of phase.

In the series case, therefore, the resultant re-

Reactance 35

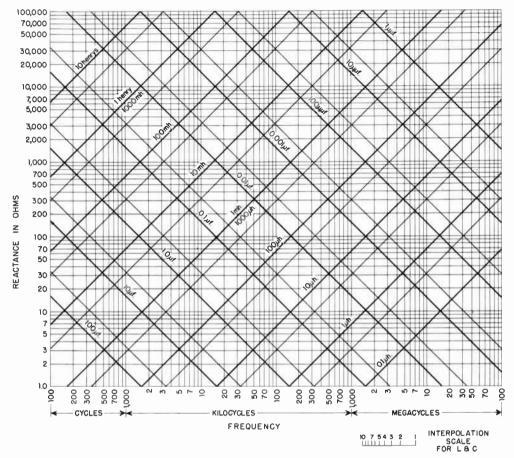


Fig. 2-28—Inductive and capacitive reactance vs. frequency. Heavy lines represent multiples of 10, intermediate light lines multiples of 5; e.g., the light line between 10 μ h. and 100 μ h. represents 50 μ h., the light line between 0.1 μ f. and 1 µf. represents 0.5 µf., etc. Intermediate values can be estimated with the help of the interpolation scale shown.

Reactances outside the range of the chart may be found by applying appropriate factors to values within the chart range. For example, the reactance of 10 henrys at 60 cycles can be found by taking the reactance to 10 henrys at 600 cycles and dividing by 10 for the 10-times decrease in frequency.

actance of X_L and X_0 is

$$X = X_L - X_Q$$

and in the parallel case
$$X = \frac{-X_{\rm L}X_{\rm C}}{X_{\rm L}-X_{\rm C}}$$

Note that in the series circuit the total reactance is negative if X_0 is larger than X; this indicates that the total reactance is capacitive in such a case. The resultant reactance in a series circuit is always smaller than the larger of the two individual reactances.

In the parallel circuit, the resultant reactance is negative (i.e., capacitive) if X_L is larger than X_{c} , and positive (inductive) if X_{L} is smaller than X_0 , but in every case is always larger than the smaller of the two individual reactances.

In the special case where $X_L = X_C$ the total reactance is zero in the series circuit and infinitely large in the parallel circuit.

Reactive Power

In Fig. 2-29A the voltage drop across the inductor is larger than the voltage applied to the circuit. This might seem to be an impossible condition, but it is not; the explanation is that while energy is being stored in the inductor's

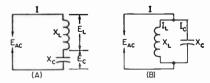


Fig. 2-29—Series and parallel circuits containing opposite kinds of reactance.

magnetic field, energy is being returned to the circuit from the capacitor's electric field, and vice versa. This stored energy is responsible for the fact that the voltages across reactances in series can be larger than the voltage applied to them.

In a resistance the flow of current causes heating and a power loss equal to I^2X . The power in a reactance is equal to I^2X , but is not a "loss"; it is simply power that is transferred back and forth between the field and the circuit but not used up in heating anything. To distinguish this "nondissipated" power from the power which is actually consumed, the unit of reactive power is called the volt-ampere-reactive, or var, instead of the watt. Reactive power is sometimes called "wattless" power.

IMPEDANCE

When a circuit contains both resistance and reactance the combined effect of the two is called impedance, symbolized by the letter Z. (Impedance is thus a more general term than either resistance or reactance, and is frequently used even for circuits that have only resistance or reactance, although usually with a qualification—such as "resistive impedance" to indicate that the circuit has only resistance, for example.)

The reactance and resistance comprising an impedance may be connected either in series or in parallel, as shown in Fig. 2-30. In these circuits the reactance is shown as a box to indicate that it may be either inductive or capacitive. In the series circuit the current is the same in both elements, with (generally) different voltages appearing across the resistance and reactance. In the parallel circuit the same voltage is applied to both elements, but different currents flow in the two branches.

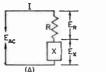




Fig. 2-30—Series and parallel circuits containing resistance and reactance.

Since in a resistance the current is in phase with the applied voltage while in a reactance it is 90 degrees out of phase with the voltage, the phase relationship between current and voltage in the circuit as a whole may be anything between zero and 90 degrees, depending on the relative amounts of resistance and reactance.

Series Circuits

When resistance and reactance are in series, the impedance of the circuit is

$$Z = \sqrt{R^2 + X^2}$$

where Z = impedance in ohms

R = resistance in ohms

X = reactance in ohms.

The reactance may be either capacitive or inductive. If there are two or more reactances in the circuit they may be combined into a resultant

by the rules previously given, before substitution into the formula above; similarly for resistances.

The "square root of the sum of the squares" rule for finding impedance in a series circuit arises from the fact that the voltage drops across the resistance and reactance are 90 degrees out of phase, and so combine by the same rule that applies in finding the hypothenuse of a right-angled triangle when the base and altitude are known.

Parallel Circuits

With resistance and reactance in parallel, as in Fig. 2-30B, the impedance is

$$Z = \frac{RX}{\sqrt{R^2 + X^2}}$$

where the symbols have the same meaning as for series circuits.

Just as in the case of series circuits, a number of reactances in parallel should be combined to find the resultant reactance before substitution into the formula above; similarly for a number of resistances in parallel.

Equivalent Series and Parallel Circuits

The two circuits shown in Fig. 2-30 are equivalent if the same current flows when a given voltage of the same frequency is applied, and if the phase angle between voltage and current is the same in both cases. It is in fact possible to "transform" any given series circuit into an equivalent parallel circuit, and vice versa.

Transformations of this type often lead to simplification in the solution of complicated circuits. However, from the standpoint of practical work the usefulness of such transformations lies in the fact that the impedance of a circuit may be modified by the addition of either series or parallel elements, depending on which happens to be most convenient in the particular case. Typical applications are considered later in connection with tuned circuits and transmission lines.

Ohm's Law for Impedance

Ohm's Law can be applied to circuits containing impedance just as readily as to circuits having resistance or reactance only. The formulas are

$$I = \frac{E}{Z}$$

$$E = IZ$$

$$Z = \frac{E}{Z}$$

where E = E.m.f. in volts

I = Current in amperes

Z = Impedance in ohms

Fig. 2-31 shows a simple circuit consisting of a resistance of 75 ohms and a reactance of 100 ohms in series. From the formula previously given, the impedance is

$$Z = \sqrt{R^2 + X_L^2} = \sqrt{(75)^2 + (100)^2} = 125$$

If the applied voltage is 250 volts, then

$$I = \frac{E}{Z} = \frac{250}{125} = 2$$
 amperes.

This current flows though both the resistance and reactance, so the voltage drops are

$$E_R = IR = 2 \times 75 = 150$$
 volts
 $E_{XL} = IX_L = 2 \times 100 = 200$ volts

The simple arithmetical sum of these two drops, 350 volts, is greater than the applied voltage because the two voltages are 90 degrees out of phase. Their actual resultant, when phase is taken into account, is

$$\sqrt{(150)^2 + (200)^2} = 250$$
 volts.

Power Factor

In the circuit of Fig. 2-31 an applied e.m.f. of 250 volts results in a current of 2 amperes, giving an apparent power of $250 \times 2 = 500$ watts. However, only the resistance actually consumes power. The power in the resistance is

$$P = I^2R = (2)^2 \times 75 = 300$$
 watts

The ratio of the power consumed to the apparent power is called the **power factor** of the circuit, and in this example the power factor would be 300/500 = 0.6. Power factor is frequently expressed as a percentage; in this case, it would be 60 per cent.

"Real" or dissipated power is measured in watts; apparent power, to distinguish it from real power, is measured in volt-amperes. It is simply the product of volts and amperes and has no direct relationship to the power actually used up or dissipated unless the power factor of the circuit is known. The power factor of a purely resistive circuit is 100 per cent or 1, while the power factor of a pure reactance is zero. In this

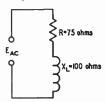


Fig. 2-31—Circuit used as an example for impedance calculations.

illustration, the reactive power is $VAR = I^{\bullet}X = (2)^{2} \times 100 = 400$ volt-amperes.

Reactance and Complex Waves

It was pointed out earlier in this chapter that a complex wave (a "nonsinusoidal" wave) can be resolved into a fundamental frequency and a series of harmonic frequencies. When such a complex voltage wave is applied to a circuit containing reactance, the current through the circuit will not have the same wave shape as the applied voltage. This is because the reactance of an inductor and capacitor depend upon the applied frequency. For the second-harmonic component of a complex wave, the reactance of the inductor is twice and the reactance of the capacitor onehalf their respective values at the fundamental frequency; for the third harmonic the inductor reactance is three times and the capacitor reactance one-third, and so on. Thus the circuit impedance is different for each harmonic com-

Just what happens to the current wave shape depends upon the values of resistance and reactance involved and how the circuit is arranged. In a simple circuit with resistance and inductive reactance in series, the amplitudes of the harmonic currents will be reduced because the inductive reactance increases in proportion to frequency. When capacitance and resistance are in series, the harmonic current is likely to be accentuated because the capacitive reactance becomes lower as the frequency is raised. When both inductive and capacitive reactance are present the shape of the current wave can be altered in a variety of ways, depending upon the circuit and the "constants," or the relative values of L, C, and R, selected.

This property of nonuniform behavior with respect to fundamental and harmonics is an extremely useful one. It is the basis of "filtering," or the suppression of undesired frequencies in favor of a single desired frequency or group of such frequencies.

TRANSFORMERS FOR AUDIO FREQUENCIES

Two coils having mutual inductance constitute a transformer. The coil connected to the source of energy is called the primary coil, and the other is called the secondary coil.

The usefulness of the transformer lies in the fact that electrical energy can be transferred from one circuit to another without direct connection, and in the process can be readily changed from one voltage level to another. Thus, if a device to be operated requires, for example, 115 volts a.c. and only a 440-volt source is available, a transformer can be used to change the source voltage to that required. A transformer can be used only with a.c., since no voltage will be induced in the secondary if the magnetic field is not changing. If d.c. is applied to the primary of a transformer, a voltage will be induced in the secondary only at the instant of closing or open-

ing the primary circuit, since it is only at these times that the field is changing.

THE IRON-CORE TRANSFORMER

As shown in Fig. 2-32, the primary and secondary coils of a transformer may be wound on a core of magnetic material. This increases the inductance of the coils so that a relatively small number of turns may be used to induce a given value of voltage with a small current. A closed core (one having a continuous magnetic path) such as that shown in Fig. 2-32 also tends to insure that practically all of the field set up by the current in the primary coil will cut the turns of the secondary coil. However, the core introduces a power loss because of hysteresis and eddy currents so this type of construction is normally practicable only at power and audio frequencies.

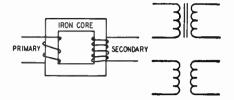


Fig. 2-32—The transformer. Power is transferred from the primary coil to the secondary by means of the magnetic field. The upper symbol at right indicates an ironcore transformer, the lower one an air-core transformer.

The discussion in this section is confined to transformers operating at such frequencies.

Voltage and Turns Ratio

For a given varying magnetic field, the voltage induced in a coil in the field will be proportional to the number of turns in the coil. If the two coils of a transformer are in the same field (which is the case when both are wound on the same closed core) it follows that the induced voltages will be proportional to the number of turns in each coil. In the primary the induced voltage is practically equal to, and opposes, the applied voltage, as described earlier. Hence,

$$E_8 = \frac{n_8}{n_p} E_p$$

where $E_{\bullet} = \text{Secondary voltage}$

 $E_P =$ Primary applied voltage

 $n_{\bullet} = \text{Number of turns on secondary}$

 $n_P = \text{Number of turns on primary}$

The ratio n_r/n_p is called the secondary-to-primary turns ratio of the transformer.

Example: A transformer has a primary of 400 turns and a secondary of 2800 turns, and an e.m.f. of 115 volts is applied to the primary. The secondary voltage will be

$$E_{\rm u} = \frac{n_{\rm u}}{n_{\rm p}} E_{\rm p} = \frac{2800}{400} \times 115 = 7 \times 115$$

= 805 volts

Also, if an e.m.f. of 805 volts is applied to the 2800-turn winding (which then becomes the primary) the output voltage from the 400-turn winding will be 115 volts.

Either winding of a transformer can be used as the primary, providing the winding has enough turns (enough inductance) to induce a voltage equal to the applied voltage without requiring an excessive current flow.

Effect of Secondary Current

The current that flows in the primary when no current is taken from the secondary is called the magnetizing current of the transformer. In any properly-designed transformer the primary inductance will be so large that the magnetizing current will be quite small. The power consumed by the transformer when the secondary is "open"—that is, not delivering power—is only the amount necessary to supply the losses in the iron core and in the resistance of the wire with which the primary is wound.

When power is taken from the secondary winding, the secondary current sets up a magnetic field that opposes the field set up by the primary current. But if the induced voltage in the primary is to equal the applied voltage, the original field must be maintained. Consequently, the primary must draw enough additional current to set up a field exactly equal and opposite to the field set up by the secondary current.

In practical calculations on transformers it may be assumed that the entire primary current is caused by the secondary "load." This is justifiable because the magnetizing current should be very small in comparison with the primary "load" current at rated power output.

If the magnetic fields set up by the primary and secondary currents are to be equal, the primary current multiplied by the primary turns must equal the secondary current multiplied by the secondary turns. From this it follows that

$$I_{p} = \frac{n_{8}}{n_{p}} I_{8}$$

where $I_P = Primary$ current

 $I_{\bullet} = Secondary current$

 $n_p = \text{Number of turns on primary}$

 $n_0 = \text{Number of turns on secondary}$

Example: Suppose that the secondary of the transformer in the previous example is delivering a current of 0.2 ampere to a load. Then the primary current will be

$$I_p = \frac{n_a}{n_p} I_a = \frac{2800}{400} \times 0.2 = 7 \times 0.2 = 1.4 \text{ amp.}$$

Although the secondary voltage is higher than the primary voltage, the secondary current is lower than the primary current, and by the same ratio.

Power Relationships; Efficiency

A transformer cannot create power; it can only transfer it and change the e.m.f. Hence, the power taken from the secondary cannot exceed that taken by the primary from the source of applied e.m.f. There is always some power loss in the resistance of the coils and in the iron core, so in all practical cases the power taken from the source will exceed that taken from the secondary. Thus,

$$P_{\circ} = nP_{1}$$

where P_{\circ} = Power output from secondary

 $P_i = Power input to primary$

n = Efficiency factor

The efficiency, n, always is less than 1. It is usually expressed as a percentage; if n is 0.65, for instance, the efficiency is 65 per cent.

Example: A transformer has an efficiency of 85% at its full-load output of 150 watts. The power input to the primary at full secondary load will be

$$P_{\rm i} = \frac{P_{\rm o}}{n} = \frac{150}{0.85} = 176.5 \text{ watts}$$

A transformer is usually designed to have its highest efficiency at the power output for which it is rated. The efficiency decreases with either lower or higher outputs. On the other hand, the losses in the transformer are relatively small at low output but increase as more power is taken.

Transformers 39

The amount of power that the transformer can handle is determined by its own losses, because these heat the wire and core. There is a limit to the temperature rise that can be tolerated, because too-high temperature either will melt the wire or cause the insulation to break down. A transformer can be operated at reduced output, even though the efficiency is low, because the actual loss also will be low under such conditions.

The full-load efficiency of small power transformers such as are used in radio receivers and transmitters usually lies between about 60 and 90 per cent, depending upon the size and design.

Leakage Reactance

In a practical transformer not all of the magnetic flux is common to both windings, although in well-designed transformers the amount of flux that "cuts" one coil and not the other is only a small percentage of the total flux. This leakage flux causes an e.m.f. of self-induction; consequently, there are small amounts of leakage inductance associated with both windings of the transformer. Leakage inductance acts in exactly the same way as an equivalent amount of ordinary inductance inserted in series with the circuit.

Fig. 2-33—The equivalent circuit of a transformer includes the effects of leakage inductance and resistance of both primary and secondary windings. The resistance R_0 is an equivalent resistance representing the core losses, which are essentially constant for any given applied voltage and frequency. Since these are comparatively small, their effect may be neglected in many approximate calculations.

It has, therefore, a certain reactance, depending upon the amount of leakage inductance and the frequency. This reactance is called leakage reactance.

Current flowing through the leakage reactance causes a voltage drop. This voltage drop increases with increasing current, hence it increases as more power is taken from the secondary. Thus, the greater the secondary current, the smaller the secondary terminal voltage becomes. The resistances of the transformer windings also cause voltage drops when current is flowing; although these voltage drops are not in phase with those caused by leakage reactance, together they result in a lower secondary voltage under load than is indicated by the turns ratio of the transformer.

At power frequencies (60 cycles) the voltage at the secondary, with a reasonably well-designed transformer, should not drop more than about 10 per cent from open-circuit conditions to full load. The drop in voltage may be considerably more than this in a transformer operating at audio frequencies because the leakage reactance increases directly with the frequency,

Impedance Ratio

In an ideal transformer—one without losses or leakage reactance—the following relationship is true:

$$Z_p = Z_n N^a$$

where Z_p = Impedance looking into primary terminals from source of power

 $Z_{\bullet} =$ Impedance of load connected to secondary

N = Turns ratio, primary to secondary

That is, a load of any given impedance connected to the secondary of the transformer will be transformed to a different value "looking into" the primary from the source of power. The impedance transformation is proportional to the square of the primary-to-secondary turns ratio.

Example: A transformer has a primary-tosecondary turns ratio of 0.6 (primary has 6/10 as many turns as the secondary) and a load of 3000 ohms is connected to the secondary. The impedance looking into the primary then will

$$Z_p = Z_n N^3 = 3000 \times (0.6)^2 = 3000 \times 0.36$$

= 1080 ohms

By choosing the proper turns ratio, the impedance of a fixed load can be transformed to any desired value, within practical limits. The transformed or "reflected" impedance has the same phase angle as the actual load impedance; thus if the load is a pure resistance the load presented by the primary to the source of power also will be a pure resistance.

The above relationship may be used in practical work even though it is based on an "ideal" transformer. Aside from the normal design requirements of reasonably low internal losses and low leakage reactance, the only requirement is that the primary have enough inductance to operate with low magnetizing current at the voltage applied to the primary.

The primary impedance of a transformer—as it appears to the source of power—is determined wholly by the load connected to the secondary and by the turns ratio. If the characteristics of the transformer have an appreciable effect on the impedance presented to the power source, the transformer is either poorly designed or is not suited to the voltage and frequency at which it is being used. Most transformers will operate quite well at voltages from slightly above to well below the design figure.

Impedance Matching

Many devices require a specific value of load resistance (or impedance) for optimum operation. The impedance of the actual load that is to dissipate the power may differ widely from this value, so a transformer is used to change the actual load into an impedance of the desired value. This is called impedance matching. From the preceding,

 $N = \sqrt{\frac{Z_{\rm p}}{Z_{\rm s}}}$

where N = Required turns ratio, primary to secondary

 $Z_p =$ Primary impedance required $Z_s =$ Impedance of load connected to secondary

Example: A vacuum-tube a.f. amplifier requires a load of 5000 ohms for optimum performance, and is to be connected to a loud-speaker having an impedance of 10 ohms. The turns ratio, primary to secondary, required in the coupling transformer is

$$N = \sqrt{\frac{Z_p}{Z_a}} = \sqrt{\frac{5000}{10}} = \sqrt{500} = 22.4$$

The primary therefore must have 22.4 times as many turns as the secondary.

Impedance matching means, in general, adjusting the load impedance-by means of a transformer or otherwise-to a desired value. However, there is also another meaning. It is possible to show that any source of power will deliver its maximum possible output when the impedance of the load is equal to the internal impedance of the source. The impedance of the source is said to be "matched" under this condition. The efficiency is only 50 per cent in such a case; just as much power is used up in the source as is delivered to the load. Because of the poor efficiency, this type of impedance matching is limited to cases where only a small amount of power is available and heating from power loss in the source is not important.

Transformer Construction

Transformers usually are designed so that the magnetic path around the core is as short as possible. A short magnetic path means that the transformer will operate with fewer turns, for a given applied voltage, than if the path were long.



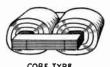


Fig. 2-34—Two common types of transformer construction. Core pieces are interleaved to provide a continuous magnetic path.

A short path also helps to reduce flux leakage and therefore minimizes leakage reactance.

Two core shapes are in common use, as shown in Fig. 2-34. In the shell type both windings are placed on the inner leg, while in the core type the primary and secondary windings may be placed on separate legs, if desired. This is some-

times done when it is necessary to minimize capacitive effects between the primary and secondary, or when one of the windings must operate at very high voltage.

Core material for small transformers is usually silicon steel, called "transformer iron." The core is built up of laminations, insulated from each other (by a thin coating of shellac, for example) to prevent the flow of eddy currents. The laminations are interleaved at the ends to make the magnetic path as continuous as possible and thus reduce flux leakage.

The number of turns required in the primary for a given applied e.m.f. is determined by the size, shape and type of core material used, and the frequency. The number of turns required is inversely proportional to the cross-sectional area of the core. As a rough indication, windings of small power transformers frequently have about six to eight turns per volt on a core of 1-square-inch cross section and have a magnetic path 10 or 12 inches in length. A longer path or smaller cross section requires more turns per volt, and vice versa.

In most transformers the coils are wound in layers, with a thin sheet of treated-paper insulation between each layer. Thicker insulation is used between coils and between coils and core.

Autotransformers

The transformer principle can be utilized with only one winding instead of two, as shown in Fig. 2-35; the principles just discussed apply

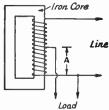


Fig. 2-35—The autotransformer is based on the transformer principle, but uses only one winding. The line and load currents in the common winding (A) flow in opposite directions, so that the resultant current is the difference between them. The voltage across A is proportional to the turns ratio.

equally well. A one-winding transformer is called an autotransformer. The current in the common section (A) of the winding is the difference between the line (primary) and the load (secondary) currents, since these currents are out of phase. Hence if the line and load currents are nearly equal the common section of the winding may be wound with comparatively small wire. This will be the case only when the primary (line) and secondary (load) voltages are not very different. The autotransformer is used chiefly for boosting or reducing the power-line voltage by relatively small amounts. Continuously-variable autotransformers are commercially available under a variety of trade names; "Variac" and "Powerstat" are typical examples.

THE DECIBEL

In most radio communication the received signal is converted into sound. This being the case, it is useful to appraise signal strengths in terms of relative loudness as registered by the ear. A peculiarity of the ear is that an increase or decrease in loudness is responsive to the ratio of the amounts of power involved, and is practically independent of absolute value of the power. For example, if a person estimates that the signal is "twice as loud" when the transmitter power is increased from 10 watts to 40 watts, he will also estimate that a 400-watt signal is twice as loud as a 100-watt signal. In other words, the human ear has a logarithmic response.

This fact is the basis for the use of the relative-power unit called the decibel (abbreviated db.) A change of one decibel in the power level is just detectable as a change in loudness under ideal conditions. The number of decibels corresponding to a given power ratio is given by the following formula:

$$Db. = 10 \log \frac{P_1}{P_1}$$

Common logarithms (base 10) are used.

Voltage and Current Ratios

Note that the decibel is based on power ratios. Voltage or current ratios can be used, but only when the impedance is the same for both values of voltage, or current. The gain of an amplifier cannot be expressed correctly in db. if it is based on the ratio of the output voltage to the input voltage unless both voltages are measured across the same value of impedance. When the impedance at both points of measurement is the same, the following formula may be used for voltage or current ratios:

$$Db. = 20 \log \frac{V_a}{V_1}$$
or 20 log $\frac{I_a}{I_1}$

Decibel Chart

The two formulas are shown graphically in Fig. 2-36 for ratios from 1 to 10. Gains (increases) expressed in decibels may be added arithmetically; losses (decreases) may be subtracted. A power decrease is indicated by prefixing the decibel figure with a minus sign. Thus +6 db. means that the power has been multiplied by 4, while -6 db. means that the power has been divided by 4.

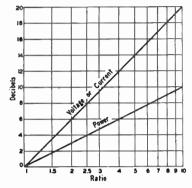


Fig. 2-36—Decibel chart for power, voltage and current ratios for power ratios of 1:1 to 10:1. In determining decibels for current or voltage ratios the currents (or voltages) being compared must be referred to the same value of impedance.

The chart may be used for other ratios by adding (or subtracting, if a loss) 10 db. each time the ratio scale is multiplied by 10, for power ratios; or by adding (or subtracting) 20 db. each time the scale is multiplied by 10 for voltage or current ratios. For example, a power ratio of 2.5 is 4 db. (from the chart). A power ratio of 10 times 2.5, or 25, is 14 db. (10+4), and a power ratio of 100 times 2.5, or 250, is 24 db. (20+4). A voltage or current ratio of 4 is 12 db., a voltage or current ratio of 40 is 32 db. (20+12), and one of 400 is 52 db. (40+12).

RADIO-FREQUENCY CIRCUITS

RESONANCE IN SERIES CIRCUITS

Fig. 2-37 shows a resistor, capacitor and inductor connected in series with a source of alternating current, the frequency of which can be varied over a wide range. At some low frequency the capacitive reactance will be much larger than the resistance of R, and the inductive reactance will be small compared with either the reactance of C or the resistance of R. (R is assumed to be the same at all frequencies.) On the other hand, at some very high frequency the reactance of C will be very large. In either case the current will be small, because the net reactance is large.

At some intermediate frequency, the reactances of C and L will be equal and the voltage drops across the coil and capacitor will be equal and



Fig. 2-37.—A series circuit containing L, C and R is "resonant" at the applied frequency when the reactance of C is equal to the reactance of L.

180 degrees out of phase. Therefore they cancel each other completely and the current flow is determined wholly by the resistance, R. At that frequency the current has its largest possible value, assuming the source voltage to be constant regardless of frequency. A series circuit in which the inductive and capacitive reactances are equal is said to be resonant.

The principle of resonance finds its most extensive application in radio-frequency circuits. The reactive effects associated with even small inductances and capacitances would place drastic limitations on r.f. circuit operation if it were not possible to "cancel them out" by supplying the right amount of reactance of the opposite kind—in other words, "tuning the circuit to resonance."

Resonant Frequency

The frequency at which a series circuit is resonant is that for which $X_L = X_C$. Substituting the formulas for inductive and capacitive reactance gives

$$f = \frac{1}{2\pi\sqrt{LC}}$$

where f = Frequency in cycles per second

 $\dot{L} = Inductance in henrys$

C =Capacitance in farads

 $\pi = 3.14$

These units are inconveniently large for radiofrequency circuits. A formula using more appropriate units is

$$f = \frac{10^6}{2\pi\sqrt{LC}}$$

where f = Frequency in kilocycles (kc.)

 $L = Inductance in microhenrys (\mu h.)$

C =Capacitance in micromicrofarads

 $\pi = 3.14^{(\mu\mu f.)}$

Example: The resonant frequency of a series circuit containing a 5- μ h. inductor and a 35- μ μ f. capacitor is

$$f = \frac{10^6}{2\pi\sqrt{LC}} = \frac{10^6}{6.28 \times \sqrt{5 \times 35}}$$
$$= \frac{10^6}{6.28 \times 13.2} = \frac{10^8}{83} = 12,050 \text{ kc.}$$

The formula for resonant frequency is not affected by the resistance in the circuit.

Resonance Curves

If a plot is drawn of the current flowing in the circuit of Fig. 2-37 as the frequency is varied (the applied voltage being constant) it would look like one of the curves in Fig. 2-38. The shape of the resonance curve at frequencies near resonance is determined by the ratio of reactance to resistance.

If the reactance of either the coil or capacitor is of the same order of magnitude as the resistance, the current decreases rather slowly as the frequency is moved in either direction away from resonance. Such a curve is said to be broad. On the other hand, if the reactance is considerably larger than the resistance the current decreases

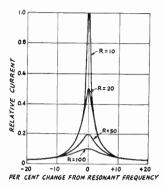


Fig. 2-38—Current in a series-resonant circuit with various values of series resistance. The values are arbitrary and would not apply to all circuits, but represent a typical case. It is assumed that the reactances (at the resonant frequency) are 1000 ohms. Note that at frequencies more than plus or minus ten per cent away from the resonant frequency the current is substantially unaffected by the resistance in the circuit.

rapidly as the frequency moves away from resonance and the circuit is said to be sharp. A sharp circuit will respond a great deal more readily to the resonant frequency than to frequencies quite close to resonance; a broad circuit will respond almost equally well to a group or band of frequencies centering around the resonant frequency.

Both types of resonance curves are useful. A sharp circuit gives good selectivity—the ability to respond strongly (in terms of current amplitude) at one desired frequency and discriminate against others. A broad circuit is used when the apparatus must give about the same response over a band of frequencies rather than to a single frequency alone.

Most diagrams of resonant circuits show only inductance and capacitance; no resistance is indicated. Nevertheless, resistance is always present. At frequencies up to perhaps 30 Mc. this resist-

0.8

Q=10

Q=10

Q=10

Q=10

Q

Fig. 2-39—Current in series-resonant circuits having different Qs. In this graph the current at resonance is assumed to be the same in all cases. The lower the Q, the more slowly the current decreases as the applied frequency is moved away from resonance.

Radio-Frequency Circuits

ance is mostly in the wire of the coil. Above this frequency energy loss in the capacitor (principally in the solid dielectric which must be used to form an insulating support for the capacitor plates) also becomes a factor. This energy loss is equivalent to resistance. When maximum sharpness or selectivity is needed the object of design is to reduce the inherent resistance to the lowest possible value.

The value of the reactance of either the inductor or capacitor at the resonant frequency of a series-resonant circuit, divided by the resistance in the circuit, is called the Q (quality factor) of the circuit, or

$$Q = \frac{X}{R}$$

where Q = Quality factor

 $\tilde{X} = \tilde{R}$ eactance of either coil or capacitor in ohms

R = Series resistance in ohms

Example: The inductor and capacitor in a series circuit each have a reactance of 350 ohms at the resonant frequency. The resistance is 5 ohms. Then the Q is

$$Q = \frac{X}{R} = \frac{350}{5} = 70$$

The effect of Q on the sharpness of resonance of a circuit is shown by the curves of Fig. 2-39. In these curves the frequency change is shown in percentage above and below the resonant frequency. Qs of 10, 20, 50 and 100 are shown; these values cover much of the range commonly used in radio work.

Voltage Rise at Resonance

When a voltage of the resonant frequency is inserted in series in a resonant circuit, the voltage that appears across either the inductor or capacitor is considerably higher than the applied voltage. The current in the circuit is limited only by the resistance and may have a relatively high value; however, the same current flows through the high reactances of the inductor and capacitor and causes large voltage drops. The ratio of the reactive voltage to the applied voltage is equal to the ratio of reactance to resistance. This ratio is also the Q of the circuit. Therefore, the voltage across either the inductor or capacitor is equal to QE, where E is the voltage inserted in series with the circuit.

Example: The inductive reactance of a circuit is 200 ohms, the capacitive reactance is 200 ohms, the resistance 5 ohms, and the applied voltage is 50. The two reactances cancel and there will be but 5 ohms of pure resistance to limit the current flow. Thus the current will be 50/5, or 10 amperes. The voltage developed across either the inductor or the capacitor will be equal to its reactance times the current, or $200 \times 10 = 2000$ volts. An alternate method: The Q of the circuit is X/R = 200/5 = 40. The reactive voltage is equal to Q times the applied voltage, or $40 \times 50 = 2000$ volts.

RESONANCE IN PARALLEL CIRCUITS

When a variable-frequency source of constant voltage is applied to a parallel circuit of the type shown in Fig. 2-40 there is a resonance effect

similar to that in a series circuit. However, in this case the "line" current (measured at the point indicated) is smallest at the frequency for which the inductive and capacitive reactances are equal. At that frequency the current through L is exactly canceled by the out-of-phase current through C, so that only the current taken by R flows in the line. At frequencies below resonance the current through L is larger than that through C, because the reactance of L is smaller and that of C higher at low frequencies; there is only partial cancellation of the two reactive currents and the line current therefore is larger than the current taken by R alone. At frequencies above resonance the situation is reversed and more current flows through C than through L. so the line current again increases. The current at resonance, being determined wholly by R, will be small if R is large and large if R is small.

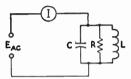


Fig. 2-40—Circuit illustrating parallel resonance.

The resistance R shown in Fig. 2-40 is not necessarily an actual resistor. In most cases it will be an "equivalent" resistance that represents the energy loss in the circuit. This loss can be inherent in the coil or capacitor, or may represent energy transferred to a load by means of the resonant circuit. (For example, the resonant circuit may be used for transferring power from a vacuum-tube amplifier to an antenna system.)

Parallel and series resonant circuits are quite alike in some respects. For instance, the circuits given at A and B in Fig. 2-41 will behave identically, when an external voltage is applied, if (1) L and C are the same in both cases; and (2) $R_{\mathfrak{p}}$ multiplied by $R_{\mathfrak{p}}$ equals the square of the reactance (at resonance) of either L or C. When these conditions are met the two circuits will have the same Qs. (These statements are approximate, but are quite accurate if the Q is 10 or more.) The circuit at A is a series circuit if it is viewed from the "inside"—that is, going around the loop formed by L, C and R—so its Q can be found from the ratio of X to $R_{\mathfrak{p}}$.

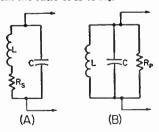


Fig. 2-41—Series and parallel equivalents when the twa circuits are resanant. The series resistar, $R_{\rm e}$, in A can be replaced by an equivalent parallel resistar, $R_{\rm p}$, in B and vice versa.

Thus a circuit like that of Fig. 2-41A has an equivalent parallel impedance (at resonance)

of
$$R_p = \frac{X^2}{R_o}$$
; X is the reactance of either the

inductor or the capacitor. Although $R_{\rm P}$ is not an actual resistor, to the source of voltage the parallel-resonant circuit "looks like" a pure resistance of that value. It is "pure" resistance because the inductive and capacitive currents are 180 degrees out of phase and are equal; thus there is no reactive current in the line. In a practical circuit with a high-Q capacitor, at the resonant frequency the parallel impedance is

$$Z_r = QX$$

where $Z_r =$ Resistive impedance at resonance

Q = Quality factor of inductor

X =Reactance (in ohms) of either the inductor or capacitor

Example: The parallel impedance of a circuit with a coil Q of 50 and having inductive and capacitive reactances of 300 ohms will be $Z_T = QX = 50 \times 300 = 15,000$ ohms.

At frequencies off resonance the impedance is no longer purely resistive because the inductive and capacitive currents are not equal. The off-resonant impedance therefore is complex, and is lower than the resonant impedance for the reasons previously outlined.

The higher the Q of the circuit, the higher the parallel impedance. Curves showing the variation of impedance (with frequency) of a parallel circuit have just the same shape as the curves showing the variation of current with frequency in a series circuit. Fig. 2-42 is a set of such curves.

Parallel Resonance in Low-Q Circuits

The preceding discussion is accurate only for Qs of 10 or more. When the Q is below 10, resonance in a parallel circuit having resistance in series with the coil, as in Fig. 2-41A, is not so easily defined. There is a set of values for L and C that will make the parallel impedance a pure resistance, but with these values the impedance


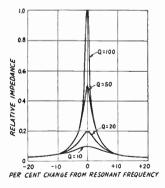


Fig. 2-42.—Relative impedance of parallel-resonant circuits with different Qs. These curves are similar to those in Fig. 2-42 for current in a series-resonant circuit. The effect of Q on impedance is most marked near the resonant frequency.

does not have its maximum possible value. Another set of values for L and C will make the parallel impedance a maximum, but this maximum value is not a pure resistance. Either condition could be called "resonance," so with low-Q circuits it is necessary to distinguish between maximum impedance and resistive impedance parallel resonance. The difference between these L and C values and the equal reactances of a series-resonant circuit is appreciable when the Q is in the vicinity of 5, and becomes more marked with still lower Q values.

Q of Loaded Circuits

In many applications of resonant circuits the only power lost is that dissipated in the resistance of the circuit itself. At frequencies below 30 Mc. most of this resistance is in the coil. Within limits, increasing the number of turns in the coil increases the reactance faster than it raises the resistance, so coils for circuits in which the Q must be high may have reactances of 1000 ohms or more at the frequency under consideration.

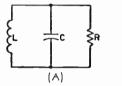

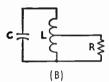


Fig. 2-43—The equivalent circuit of a resonant circuit delivering power to a load. The resistor R represents the load resistance. At B the load is tapped across part of L, which by transformer action is equivalent to using a higher load resistance across the whole circuit.

However, when the circuit delivers energy to a load (as in the case of the resonant circuits used in transmitters) the energy consumed in the circuit itself is usually negligible compared with that consumed by the load. The equivalent of such a circuit is shown in Fig. 2-43A, where the parallel resistor represents the load to which power is delivered. If the power dissipated in the load is at least ten times as great as the power lost in the inductor and capacitor, the parallel impedance of the resonant circuit itself will be so high compared with the resistance of the load that for all practical purposes the impedance of the combined circuit is equal to the load resistance. Under these conditions the Q of a parallelresonant circuit loaded by a resistive impedance is

$$Q = \frac{R}{X}$$

where Q = Quality factor

R = Parallel load resistance (ohms)

X =Reactance (ohms) of either the inductor or capacitor

Example: A resistive load of 3000 ohms is connected across a resonant circuit in which the inductive and capacitive reactances are each 250 ohms. The circuit Q is then

$$Q = \frac{R}{X} = \frac{3000}{250} = 12$$

Radio-Frequency Circuits

The "effective" Q of a circuit loaded by a parallel resistance becomes higher when the reactances are decreased. A circuit loaded with a relatively low resistance (a few thousand ohms) must have low-reactance elements (large capacitance and small inductance) to have reasonably high Q.

Impedance Transformation

An important application of the parallelresonant circuit is as an impedance-matching device in the output circuit of a vacuum-tube r.f. power amplifier. As described in the chapter on vacuum tubes, there is an optimum value of load resistance for each type of tube and set of operating conditions. However, the resistance of the load to which the tube is to deliver power usually is considerably lower than the value required for proper tube operation. To transform the actual load resistance to the desired value the load may be tapped across part of the coil as shown in Fig. 2-43B. This is equivalent to connecting a higher value of load resistance across the whole circuit, and is similar in principle to impedance transformation with an iron-core transformer. In high-frequency resonant circuits the impedance ratio does not vary exactly as the square of the turns ratio, because all the magnetic flux lines do not cut every turn of the coil. A desired reflected impedance usually must be obtained by experimental adjustment.

When the load resistance has a very low value (say below 100 ohms) it may be connected in series in the resonant circuit (as in Fig. 2-41A, for example), in which case it is transformed to an equivalent parallel impedance as previously described. If the Q is at least 10, the equivalent parallel impedance is

$$Z_{\rm r} = \frac{X^2}{R}$$

where $Z_r =$ Resistive parallel impedance at resonance

X = Reactance (in ohms) of either the coil or capacitor

R = Load resistance inserted in series If the Q is lower than 10 the reactance will have to be adjusted somewhat, for the reasons given in the discussion of low-Q circuits, to obtain a resistive impedance of the desired value.

Reactance Values

The charts of Figs. 2-44 and 2-45 show reactance values of inductances and capacitances in the range commonly used in r.f. tuned circuits for the amateur bands. With the exception of the 3.5-4 Mc. band, limiting values for which are shown on the charts, the change in reactance over a band, for either inductors or capacitors, is small enough so that a single curve gives the reactance with sufficient accuracy for most practical purposes.

The formula for resonant frequency of a circuit shows that the same frequency always will be obtained so long as the *product* of L and C is con-

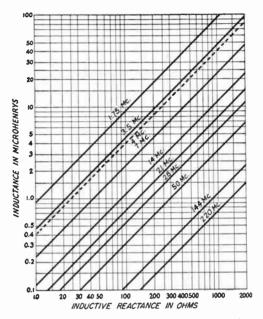


Fig. 2-44—Reactance chart for inductance values commonly used in amateur bands from 1.75 to 220 Mc.

stant. Within this limitation, it is evident that L can be large and C small, L small and C large, etc. The relation between the two for a fixed frequency is called the L/C ratio. A high-C circuit is one that has more capacitance than "normal" for the frequency; a low-C circuit one that has less than normal capacitance. These terms depend to a considerable extent upon the particular ap-

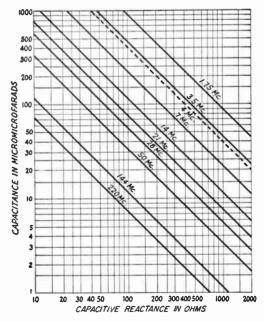


Fig. 2-45—Reactance chart for capacitance values commonly used in amateur bands from 1.75 to 220 Mc.

plication considered, and have no exact numerical meaning.

LC Constants

It is frequently convenient to use the numerical value of the LC constant when a number of calculations have to be made involving different L/C ratios for the same frequency. The constant for any frequency is given by the following equation:

25,330

 $LC = \frac{25,330}{f^2}$

f = Frequency in megacycles

Example: Find the inductance required to resonate at 3650 kc. (3.65 Mc.) with capacitances of 25, 50, 100, and 500 $\mu\mu f$. The LC constant is

$$LC = \frac{25,330}{(3.65)^2} = \frac{25,330}{13.35} = 1900$$
With 25 $\mu\mu f$. $L = 1900/C = 1900/25$
 $= 76 \mu h$.
$$50 \mu\mu f$$
. $L = 1900/C = 1900/50$
 $= 38 \mu h$.
$$100 \mu\mu f$$
. $L = 1900/C = 1900/100$
 $= 19 \mu h$.
$$500 \mu\mu f$$
. $L = 1900/C = 1900/500$
 $= 3.8 \mu h$.

COUPLED CIRCUITS

Energy Transfer and Loading

Two circuits are coupled when energy can be transferred from one to the other. The circuit delivering power is called the primary circuit; the one receiving power is called the secondary circuit. The power may be practically all dissipated in the secondary circuit itself (this is usually the case in receiver circuits) or the secondary may simply act as a medium through which the power is transferred to a load. In the latter case, the coupled circuits may act as a radiofrequency impedance-matching device. The matching can be accomplished by adjusting the loading on the secondary and by varying the amount of coupling between the primary and secondary.

Coupling by a Common Circuit Element

One method of coupling between two resonant circuits is through a circuit element common to both. The three common variations of this type of coupling are shown in Fig. 2-46; the circuit element common to both circuits carries the subscript M. At A and B current circulating in L_1C_1 flows through the common element, and the voltage developed across this element causes current to flow in L_2C_2 . At C, C_M and C_2 form a capacitive voltage divider across L_1C_1 , and some of the voltage developed across L_1C_1 is applied across L_2C_2 .

If both circuits are resonant to the same frequency, as is usually the case, the value of coupling reactance required for maximum energy transfer can be approximated by the following, based on $L_1 = L_2$, $C_1 = C_2$ and $Q_1 = Q_3$:

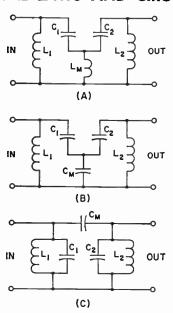


Fig. 2-46-Three methods of circuit coupling.

(A) $L_{\text{M}} \approx L_1/Q_1$; (B) $C_{\text{M}} \approx Q_1C_1$; (C) $C_{\text{M}} \approx C_1/Q_1$.

The coupling can be increased by increasing the above coupling elements in A and C and decreasing the value in B. When the coupling is increased, the resultant bandwidth of the combination is increased, and this principle is sometimes applied to "broad-band" the circuits in a transmitter or receiver. When the coupling elements in A and C are decreased, or when the coupling element in B is increased, the coupling between the circuits is decreased below the critical coupling value on which the above approximations are based. Less than critical coupling will decrease the bandwidth and the energy transfer; the principle is often used in receivers to improve the selectivity.

Inductive Coupling

Figs. 2-47 and 2-48 show inductive coupling, or coupling by means of the mutual inductance between two coils. Circuits of this type resemble the iron-core transformer, but because only a part of

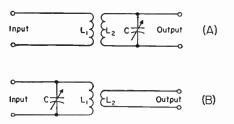


Fig. 2-47—Single-tuned inductively coupled circuits.

the magnetic flux lines set up by one coil cut the turns of the other coil, the simple relationships between turns ratio, voltage ratio and impedance ratio in the iron-core transformer do not hold.

Two types of inductively-coupled circuits are shown in Fig. 2-47. Only one circuit is resonant. The circuit at A is frequently used in receivers for coupling between amplifier tubes when the tuning of the circuit must be varied to respond to signals of different frequencies. Circuit B is used principally in transmitters, for coupling a radio-frequency amplifier to a resistive load.

In these circuits the coupling between the primary and secondary coils usually is "tight"—that is, the coefficient of coupling between the coils is large. With every tight coupling either circuit operates nearly as though the device to which the untuned coil is connected were simply tapped across a corresponding number of turns on the tuned-circuit coil, thus either circuit is approximately equivalent to Fig. 2-43B.

By proper choice of the number of turns on the untuned coil, and by adjustment of the coupling, the parallel impedance of the tuned circuit may be adjusted to the value required for the proper operation of the device to which it is connected. In any case, the maximum energy transfer possible for a given coefficient of coupling is obtained when the reactance of the untuned coil is equal to the resistance of its load.

The Q and parallel impedance of the tuned circuit are reduced by coupling through an untuned coil in much the same way as by the tapping arrangement shown in Fig. 2-43B.

Coupled Resonant Circuits

When the primary and secondary circuits are both tuned, as in Fig. 2-48, the resonance effects

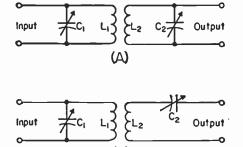


Fig. 2-48—Inductively-coupled resonant circuits. Circuit A is used for high-resistance loads (load resistance much higher than the reactance of either L_2 or C_2 at the resonant frequency). Circuit B is suitable for low resistance loads (load resistance much lower than the reactance of either L_2 or C_2 at the resonant frequency).

in both circuits make the operation somewhat more complicated than in the simpler circuits just considered. Imagine first that the two circuits are not coupled and that each is independently tuned to the resonant frequency. The impedance of each will be purely resistive. If the primary circuit is connected to a source of r.f. energy of the resonant frequency and the secondary is then loosely coupled to the primary, a current will flow in the

secondary circuit. In flowing through the resistance of the secondary circuit and any load that may be connected to it, the current causes a power loss. This power must come from the energy source through the primary circuit, and manifests itself in the primary as an increase in the equivalent resistance in series with the primary coil. Hence the Q and parallel impedance of the primary circuit are decreased by the coupled secondary. As the coupling is made greater (without changing the tuning of either circuit) the coupled resistance becomes larger and the parallel impedance of the primary continues to decrease. Also, as the coupling is made tighter the amount of power transferred from the primary to the secondary will increase to a maximum at one value of coupling, called critical coupling, but then decreases if the coupling is tightened still more (still without changing the tuning).

Critical coupling is a function of the Qs of the two circuits. A higher coefficient of coupling is required to reach critical coupling when the Qs are low; if the Qs are high, as in receiving applications, a coupling coefficient of a few per cent may give critical coupling.

With loaded circuits such as are used in transmitters the Q may be too low to give the desired power transfer even when the coils are coupled as tightly as the physical construction permits. In such case, increasing the Q of either circuit will be helpful, although it is generally better to increase the Q of the lower-Q circuit rather than the reverse. The Q of the parallel-tuned primary (input) circuit can be increased by decreasing the L/C ratio because, as shown in connection with Fig. 2-43, this circuit is in effect loaded by a parallel resistance (effect of coupled-in resistance). In the parallel-tuned secondary circuit, Fig. 2-48A, the Q can be increased, for a fixed value of load resistance, either by decreasing the L/C ratio or by tapping the load down (see Fig. 2-43). In the series-tuned secondary circuit, Fig. 2-48B, the Q may be increased by increasing the L/C ratio. There will generally be no difficulty in securing sufficient coupling, with practicable coils, if the product of the Qs of the two tuned circuits is 10 or more. A smaller product will suffice if the coil construction permits tight coupling.

Selectivity

In Fig. 2-47 only one circuit is tuned and the selectivity curve will be essentially that of a single resonant circuit. As stated, the effective Q depends upon the resistance connected to the untuned coil.

In Fig. 2-48, the selectivity is the same as that of a single tuned circuit having a Q equal to the product of the Qs of the individual circuits—if the coupling is well below critical (this is not the condition for optimum power transfer discussed immediately above) and both circuits are tuned to resonance. The Qs of the individual circuits are affected by the degree of coupling, because each couples resistance into the other; the

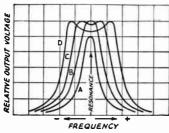


Fig. 2-49—Showing the effect on the output voltage from the secondary circuit of changing the coefficient of coupling between two resonant circuits independently tuned to the same frequency. The voltage applied to the primary is held constant in amplitude while the frequency is varied, and the output voltage is measured across the secondary.

tighter the coupling, the lower the individual Qs and therefore the lower the over-all selectivity.

If both circuits are independently tuned to resonance, the over-all selectivity will vary about as shown in Fig. 2-49 as the coupling is varied. With loose coupling, A, the output voltage (across the secondary circuit) is small and the selectivity is high. As the coupling is increased the secondary voltage also increases until critical coupling, B, is reached. At this point the output voltage at the resonant frequency is maximum but the selectivity is lower than with looser coupling. At still tighter couple, C, the output voltage at the resonant frequency decreases, but as the frequency is varied either side of resonance it is found that there are two "humps" to the curve, one on either side of resonance. With very tight coupling, D, there is a further decrease in the output voltage at resonance and the "humps" are farther away from the resonant frequency. Curves such as those at C and D are called flattopped because the output voltage does not change much over an appreciable band of frequencies.

Note that the off-resonance humps have the same maximum value as the resonant output voltage at critical coupling. These humps are caused by the fact that at frequencies off resonance the secondary circuit is reactive and couples reactance as well as resistance into the primary. The coupled resistance decreases off resonance, and each hump represents a new condition of critical coupling at a frequency to which the primary is tuned by the additional coupled-in reactance from the secondary.

Fig. 2-50 shows the response curves for various degrees of coupling between two circuits tuned to a frequency f_0 . Equals Q_0 s are assumed in both circuits, although the curves are representative if the Q_0 s differ by ratios up to 1.5 or even 2 to 1. In these cases, a value of $Q = \sqrt{Q_1Q_2}$ should be used.

Band-Pass Coupling

Over-coupled resonant circuits are useful where substantially uniform output is desired over a continuous band of frequencies, without read-

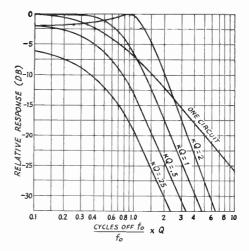


Fig. 2-50—Relative response for a single tuned circuit and for coupled circuits. For inductively-coupled circuits

(Figs. 2-46A and 2-48A),
$$k=\frac{M}{\sqrt{L_1L_2}}$$
 where M is the mutual inductance. For capacitance-coupled circuits (Figs. 2-46B and 2-46C), $k\cong\frac{\sqrt{C_1C_2}}{C_M}$ and $k\cong\frac{C_M}{\sqrt{C_1C_2}}$ respectively.

justment of tuning. The width of the flat top of the resonance curve depends on the Qs of the two circuits as well as the tightness of coupling; the frequency separation between the humps will increase, and the curve become more flat-topped, as the Qs are lowered.

Band-pass operation also is secured by tuning the two circuits to slightly different frequencies, which gives a double-humped resonance curve even with loose coupling. This is called stagger tuning. To secure adequate power transfer over the frequency band it is usually necessary to use tight coupling and experimentally adjust the circuits for the desired performance.

Link Coupling

A modification of inductive coupling, called link coupling, is shown in Fig. 2-51. This gives the effect of inductive coupling between two coils that have no mutual inductance; the link is simply a means for providing the mutual inductance. The total mutual inductance between two coils coupled by a link cannot be made as great as if the coils themselves were coupled. This is because the coefficient of coupling between air-

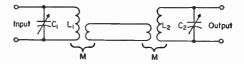


Fig. 2-51—Link coupling. The mutual inductances at both ends of the link are equivalent to mutual inductance between the tuned circuits, and serve the same purpose.

Impedance Matching

core coils is considerably less than 1, and since there are two coupling points the over-all coupling coefficient is less than for any pair of coils. In practice this need not be disadvantageous because the power transfer can be made great enough by making the tuned circuits sufficiently high-Q. Link coupling is convenient when ordinary inductive coupling would be impracticable for constructional reasons.

The link coils usually have a small number of turns compared with the resonant-circuit coils. The number of turns is not greatly important, because the coefficient of coupling is relatively independent of the number of turns on either coil; it is more important that both link coils should have about the same inductance. The length of the link between the coils is not critical if it is very small compared with the wavelength, but if the length is more than about one-twentieth of a wavelength the link operates more as a transmission line than as a means for providing mutual inductance. In such case it should be treated by the methods described in the chapter on Transmission Lines.

IMPEDANCE-MATCHING CIRCUITS

The coupling circuits discussed in the preceding section have been based either on inductive coupling or on coupling through a common circuit element between two resonant circuits. These are not the only circuits that may be used for transferring power from one device to another.

(A)
$$R_{in} \rightarrow C$$
 $C \Rightarrow R$
 $X_{L} = \sqrt{RR_{in} - R^{2}}$
 $X_{C} = \frac{R R_{in}}{X_{L}}$

(B) $R_{in} \rightarrow C \Rightarrow R$
 $X_{L} = \sqrt{RR_{in} - R^{2}}$
 $X_{L} = \frac{RR_{in}}{X_{L}}$

(C) $R_{1} \Rightarrow C \Rightarrow R_{2}$
 $X_{C} = \frac{R_{1}}{X_{C}}$
 $X_{C} = \frac{R_{1}}{Q}$
 $X_{C} = \frac{QR_{1} + (R_{1}R_{2}/X_{C})}{Q^{2} + 1}$

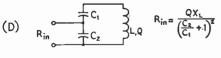


Fig. 2-52—Impedance-matching networks adaptable to amateur work. (A) L network for transforming to a higher value of resistance. (B) L network for transforming to a lower resistance value. (C) Pi network. R₁ is the larger of the two resistors; Q is defined as R₁/Xc₁. (D) Tapped tuned circuit used in some receiver applications. The impedance of the tuned circuit is transformed to a lower value, R_{1nz}, by the capacitive divider.

There is, in fact, a wide variety of such circuits available, all of them being classified generally as impedance-matching networks. Several networks frequently used in amateur equipment are shown in Fig. 2-52.

The L Network

The L network is the simplest possible impedance-matching circuit. It closely resembles an ordinary resonant circuit with the load resistance, R, Fig. 2-52, either in series or parallel. The arrangement shown in Fig. 2-52A is used when the desired impedance, $R_{\rm IN}$, is larger than the actual load resistance, R, while Fig. 2-52B is used in the opposite case. The design equations for each case are given in the figure, in terms of the circuit reactances. The reactances may be converted to inductance and capacitance by means of the formulas previously given or taken directly from the charts of Figs. 2-44 and 2-45.

When the impedance transformation ratio is large—that is, one of the two impedances is of the order of 100 times (or more) larger than the other—the operation of the circuit is exactly the same as previously discussed in connection with impedance transformation with a simple *LC* resonant circuit.

The Q of an L network is found in the same way as for simple resonant circuits. That is, it is equal to X_L/R or R_{IN}/X_C in Fig. 2-52A, and to X_L/R_{IN} or R/X_C in Fig. 2-52B. The value of Q is determined by the ratio of the impedances to be matched, and cannot be selected independently. In the equations of Fig. 2-52 it is assumed that both R and R_{IN} are pure resistances.

The Pi Network

The pi network, shown in Fig. 2-52C, offers more flexibility than the L since the operating Q may be chosen practically at will. The only limitation on the circuit values that may be used is that the reactance of the series arm, the inductor L in the figure, must not be greater than the square root of the product of the two values of resistive impedance to be matched. As the circuit is applied in amateur equipment, this limiting value of reactance would represent a network with an undesirably low operating Q, and the circuit values ordinarily used are well on the safe side of the limiting values.

In its principal application as a "tank" circuit matching a transmission line to a power amplifier tube, the load R_2 will generally have a fairly low value of resistance (up to a few hundred ohms) while R_1 , the required load for the tube, will be of the order of a few thousand ohms. In such a case the Q of the circuit is defined as R_1/X_{c_1} , so the choice of a value for the operating Q immediately sets the value of X_{c_1} and hence of C_1 . The values of X_{c_2} and X_L are then found from the equations given in the figure.

Graphical solutions for practical cases are given in the chapter on transmitter design in the discussion of plate tank circuits. The L and C values may be calculated from the reactances or read from the charts of Figs. 2-44 and 2-45.

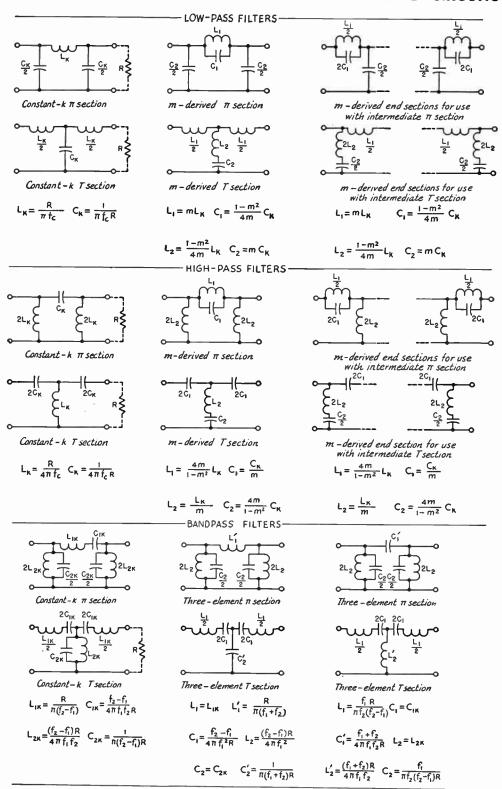


Fig. 2-53—Basic filter sections and design formulas. In the above formulas R is in ohms, C in farads, L in henrys, and f in cycles per second.

Tapped Tuned Circuit

The tapped tuned circuit of Fig. 2-52C is useful in some receiver applications, where it is desirable to use a high-impedance tuned circuit as a lower-impedance load. When the Q of the inductor has been determined, the capacitors can be selected to give the desired impedance transformation and the necessary resultant capacitance to tune the circuit to resonance.

FILTERS

A filter is an electrical circuit configuration (network) designed to have specific characteristics with respect to the transmission or attenuation of various frequencies that may be applied to it. There are three general types of filters: low-pass, high-pass, and band-pass.

A low-pass filter is one that will permit all frequencies below a specified one called the cutoff frequency to be transmitted with little or no
loss, but that will attenuate all frequencies above

the cut-off frequency.

A high-pass filter similarly has a cut-off frequency, above which there is little or no loss in transmission, but below which there is considerable attenuation. Its behavior is the opposite of that of the low-pass filter.

A band-pass filter is one that will transmit a selected band of frequencies with substantially no loss, but that will attenuate all frequencies either higher or lower than the desired band.

The pass band of a filter is the frequency spectrum that is transmitted with little or no loss. The transmission characteristic is not necessarily perfectly uniform in the pass band, but the variations usually are small.

The stop band is the frequency region in which attenuation is desired. The attenuation may vary in the stop band, and in a simple filter usually is least near the cut-off frequency, rising to high values at frequencies considerably removed from the cut-off frequency.

Filters are designed for a specific value of purely resistive impedance (the terminating impedance of the filter). When such an impedance is connected to the output terminals of the filter, the impedance looking into the input terminals has essentially the same value, throughout most of the pass band. Simple filters do not give perfectly uniform performance in this respect, but the input impedance of a properly-terminated filter can be made fairly constant, as well as closer to the design value, over the pass band by using m-derived filter sections.

A discussion of filter design principles is beyond the scope of this Handbook, but it is not difficult to build satisfactory filters from the circuits and formulas given in Fig. 2-53. Filter circuits are built up from elementary sections as shown in the figure. These sections can be used alone or, if greater attenuation and sharper cutoff (that is, a more rapid rate of rise of attenuation with frequency beyond the cut-off frequency) are required, several sections can be connected in series. In the low- and high-pass filters, fo repre-

sents the cut-off frequency, the highest (for the low-pass) or the lowest (for the high-pass) frequency transmitted without attenuation. In the band-pass filter designs, f_1 is the low-frequency cut-off and f_2 the high-frequency cut-off. The units for L, C, R and f are henrys, farads, ohms and cycles per second, respectively.

All of the types shown are "unbalanced" (one side grounded). For use in balanced circuits (e.g., 300-ohm transmission line, or push-pull audio circuits), the series reactances should be equally divided between the two legs. Thus the balanced constant-k π -section low-pass filter would use two inductors of a value equal to $L_k/2$, while the balanced constant-k π -section high-pass filter would use two capacitors each equal to $2C_k$.

If several low- (or high-) pass sections are to be used, it is advisable to use m-derived end sections on either side of a constant-k center section, although an m-derived center section can be used. The factor m determines the ratio of the cut-off frequency, f_c , to a frequency of high attenuation, f_∞ . Where only one m-derived section is used, a value of 0.6 is generally used for m, although a deviation of 10 or 15 per cent from this value is not too serious in amateur work. For a value of m = 0.6, f_∞ will be $1.25f_c$ for the low-pass filter and $0.8f_c$ for the high-pass filter. Other values can be found from

$$m = \sqrt{1 - \left(\frac{f_c}{f_{\infty}}\right)^2}$$
 for the low-pass filter and

$$m = \sqrt{1 - \left(\frac{f_{\infty}}{f_{c}}\right)^{2}}$$
 for the high-pass filter.

The output sides of the filters shown should be terminated in a resistance equal to R, and there should be little or no reactive component in the termination.

PIEZOELECTRIC CRYSTALS

A number of crystalline substances found in nature have the ability to transform mechanical strain into an electrical charge, and vice versa. This property is known as the piezoelectric effect. A small plate or bar cut in the proper way from a quartz crystal and placed between two conducting electrodes will be mechanically strained when the electrodes are connected to a source of voltage. Conversely, if the crystal is squeezed between two electrodes a voltage will be developed between the electrodes.


Piezoelectric crystals can be used to transform mechanical energy into electrical energy, and vice versa. They are used in microphones and phonograph pick-ups, where mechanical vibrations are transformed into alternating voltages of corresponding frequency. They are also used in headsets and loudspeakers, transforming electrical energy into mechanical vibration. Crystals of Rochelle salts are used for these purposes.

Crystal Resonators

Crystalline plates also are mechanical resonators that have natural frequencies of vibration ranging from a few thousand cycles to tens of megacycles per second. The vibration frequency depends on the kind of crystal, the way the plate is cut from the natural crystal, and on the dimensions of the plate. The thing that makes the crystal resonator valuable is that it has extremely high Q, ranging from 5 to 10 times the Qs obtainable with good LC resonant circuits.

Analogies can be drawn between various mechanical properties of the crystal and the electrical characteristics of a tuned circuit. This leads to an "equivalent circuit" for the crystal. The electrical coupling to the crystal is through the holder plates between which it is sandwiched; these plates form, with the crystal as the dielectric, a small capacitator like any other capacitor constructed of two plates with a dielectric between. The crystal itself is equivalent to a series-resonant circuit, and together with the capacitance of the holder forms the equivalent circuit shown in Fig. 2-54. At frequencies of the order of

Fig. 2-54—Equivalent circuit of a crystal resonator. L, C and R are the electrical equivalents of mechanicol properties of the crystal; Ch is the capacitance of the holder plates with the crystal plate between them.

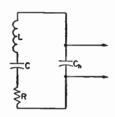

450 kc., where crystals are widely used as resonators, the equivalent L may be several henrys and the equivalent C only a few hundredths of a micromicrofarad. Although the equivalent R is of the order of a few thousand ohms, the reactance at resonance is so high that the Q of the crystal likewise is high.

A circuit of the type shown in Fig. 2-54 has a series-resonant frequency, when viewed from the circuit terminals indicated by the arrowheads, determined by L and C only. At this frequency the circuit impedance is simply equal to R, providing the reactance of C_h is large compared with R (this is generally the case). The circuit also

has a parallel-resonant frequency determined by L and the equivalent capacitance of C and C_h in series. Since this equivalent capacitance is smaller than C alone, the parallel-resonant frequency is higher than the series-resonant frequency. The separation between the two resonant frequencies depends on the ratio of C_h to C, and when this ratio is large (as in the case of a crystal resonator, where C_h will be a few $\mu\mu$ f. in the average case) the two frequencies will be quite close together. A separation of a kilocycle or less at 455 kc. is typical of a quartz crystal.

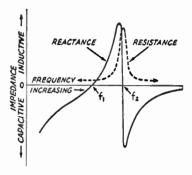


Fig. 2-55—Reactance and resistance vs. frequency of a circuit of the type shown in Fig. 2-54. Actual values of reactance, resistance and the separation between the series- and parallel-resonant frequencies, f₁, and f₂, respectively, depend on the circuit constants.

Fig. 2-55 shows how the resistance and reactance of such a circuit vary as the applied frequency is varied. The reactance passes through zero at both resonant frequencies, but the resistance rises to a large value at parallel resonance, just as in any tuned circuit.

Quartz crystals may be used either as simple resonators for their selective properties or as the frequency-controlling elements in oscillators as described in later chapters. The series-resonant frequency is the one principally used in the former case, while the more common forms of oscillator circuit use the parallel-resonant frequency.


PRACTICAL CIRCUIT DETAILS

COMBINED A.C. AND D.C.

Most radio circuits are built around vacuum tubes, and it is the nature of these tubes to require direct current (usually at a fairly high voltage) for their operation. They convert the direct current into an alternating current (and sometimes the reverse) at frequencies varying from well down in the audio range to well up in the superhigh range. The conversion process almost invariably requires that the direct and alternating currents meet somewhere in the circuit.

In this meeting, the a.c. and d.c. are actually combined into a single current that "pulsates" (at the a.c. frequency) about an average value equal to the direct current. This is shown in Fig. 2-56. It is convenient to consider that the alter-

Fig. 2-56—Pulsating d.c., composed of an alternating current or voltage superimposed on a steady direct current or voltage.

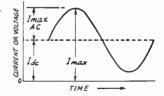

nating current is **superimposed** on the direct current, so we may look upon the actual current as having two components, one d.c. and the other a.c.

In an alternating current the positive and negative alternations have the same average amplitude, so when the wave is superimposed on a direct current the latter is alternately increased and decreased by the same amount. There is thus

no average change in the direct current. If a d.c. instrument is being used to read the current, the reading will be exactly the same whether or not the a.c. is superimposed.

However, there is actually more power in such a combination current than there is in the direct current alone. This is because power varies as the square of the instantaneous value of the current, and when all the instantaneous squared values are averaged over a cycle the total power is greater than the d.c. power alone. If the a.c. is a sine wave having a peak value just equal to the d.c., the power in the circuit is 1.5 times the d.c. power. An instrument whose readings are proportional to power will show such an increase.

Series and Parallel Feed

Fig. 2-57 shows in simplified form how d.c. and a.c. may be combined in a vacuum-tube circuit. In this case, it is assumed that the a.c. is at radio frequency, as suggested by the coil-and-capacitor tuned circuit. It is also assumed that r.f. current can easily flow through the d.c. supply; that is, the impedance of the supply at radio frequencies is so small as to be negligible.

In the circuit at the left, the tube, tuned circuit, and d.c. supply all are connected in series. The direct current flows through the r.f. coil to get to the tube; the r.f. current generated by the tube

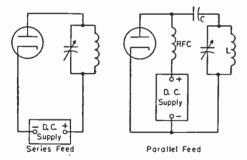


Fig. 2-57—Illustrating series and parallel feed.

flows through the d.c. supply to get to the tuned circuit. This is series feed. It works because the impedance of the d.c. supply at radio frequencies is so low that it does not affect the flow of r.f. current, and because the d.c. resistance of the coil is so low that it does not affect the flow of direct current.

In the circuit at the right the direct current does not flow through the r.f. tuned circuit, but instead goes to the tube through a second coil, RFC (radio-frequency choke). Direct current cannot flow through L because a blocking capacitance, C, is placed in the circuit to prevent it. (Without C, the d.c. supply would be short-circuited by the low resistance of L.) On the other hand, the r.f. current generated by the tube can easily flow through C to the tuned circuit because the capacitance of C is intentionally chosen to have low reactance (compared with the impedance of the tuned circuit) at the radio frequency. The r.f. current cannot flow through the

d.c. supply because the inductance of RFC is intentionally made so large that it has a very high reactance at the radio frequency. The resistance of RFC, however, is too low to have an appreciable effect on the flow of direct current. The two currents are thus in parallel, hence the name parallel feed.

Either type of feed may be used for both a.f. and r.f. circuits. In parallel feed there is no d.c. voltage on the a.c. circuit, a desirable feature from the viewpoint of safety to the operator, because the voltages applied to tubes—particularly transmitting tubes—are dangerous. On the other hand, it is somewhat difficult to make an r.f. choke work well over a wide range of frequencies. Series feed is often preferred, therefore, because it is relatively easy to keep the impedance between the a.c. circuit and the tube low.


Bypassing

In the series-feed circuit just discussed, it was assumed that the d.c. supply had very low impedance at radio frequencies. This is not likely to be true in a practical power supply, partly because the normal physical separation between the supply and the r.f. circuit would make it necessary to use rather long connecting wires or leads. At radio frequencies, even a few feet of wire can have fairly large reactance—too large to be considered a really "low-impedance" connection.

An actual circuit would be provided with a bypass capacitor, as shown in Fig. 2-58. Capacitor C is chosen to have low reactance at the operating frequency, and is installed right in the circuit where it can be wired to the other parts with quite short connecting wires. Hence the r.f. current will tend to flow through it rather than through the d.c. supply.

To be effective, the reactance of the bypass

Fig. 2-58—Typical use of a bypass capacitor and r.f. choke in a series-feed circuit.

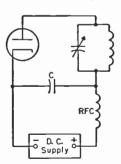

capacitor should not be more than one-tenth of the impedance of the bypassed part of the circuit. Very often the latter impedance is not known, in which case it is desirable to use the largest capacitance in the bypass that circumstances permit. To make doubly sure that r.f. current will not flow through a non-r.f. circuit such as a power supply, an r.f. choke may be connected in the lead to the latter, as shown in Fig. 2-58.

The same type of bypassing is used when audio frequencies are present in addition to r.f. Because

the reactance of a capacitor changes with frequency, it is readily possible to choose a capacitance that will represent a very low reactance at radio frequencies but that will have such high reactance at audio frequencies that it is practically an open circuit. A capacitance of $0.001~\mu f$, is practically a short circuit for r.f., for example, but is almost an open circuit at audio frequencies. (The actual value of capacitance that is usable will be modified by the impedances concerned.) Bypass capacitors also are used in audio circuits to carry the audio frequencies around a d.c. supply.

Distributed Capacitance and Inductance

In the discussions earlier in this chapter it was assumed that a capacitor has only capacitance and that an inductor has only inductance. Unfortunately, this is not strictly true. There is always a certain amount of inductance in a conductor of any length, and a capacitor is bound to have a little inductance in addition to its intended capacitance. Also, there is always capacitance between two conductors or between parts of the same conductor, and thus there is appreciable capacitance between the turns of an inductance coil.

This distributed inductance in a capacitor and the distributed capacitance in an inductor have important practical effects. Actually, every capacitor is a tuned circuit, resonant at the frequency where its capacitance and distributed inductance have the same reactance. The same thing is true of a coil and its distributed capacitance. At frequencies well below these natural resonances, the capacitor will act like a normal capacitance and the coil will act like a normal inductance. Near the natural resonant points, the coil and capacitor act like self-tuned circuits. Above resonance, the capacitor acts like an inductor and the inductor acts like a capacitor. Thus there is a limit to the amount of capacitance that can be used at a given frequency. There is a similar limit to the inductance that can be used. At audio frequencies, capacitances measured in microfarads and inductances measured in henrys are practicable. At low and medium radio frequencies, inductances of a few millihenrys and capacitances of a few thousand micromicrofarads are the largest practicable. At high radio frequencies, usable inductance values drop to a few microhenrys and capacitances to a few hundred micromicrofarads.

Distributed capacitance and inductance are important not only in r.f. tuned circuits, but in bypassing and choking as well. It will be appreciated that a bypass capacitor that actually acts like an inductance, or an r.f. choke that acts like a low-reactance capacitor, cannot work as it is intended they should.

Grounds

Throughout this book there are frequent references to ground and ground potential. When a connection is said to be "grounded" it does not necessarily mean that it actually goes to earth.

What it means is that an actual earth connection to that point in the circuit should not disturb the operation of the circuit in any way. The term also is used to indicate a "common" point in the circuit where power supplies and metallic supports (such as a metal chassis) are electrically tied together. It is general practice, for example, to "ground" the negative terminal of a d.c. power supply, and to "ground" the filament or heater power supplies for vacuum tubes. Since the cathode of a vacuum tube is a junction point for grid and plate voltage supplies, and since the various circuits connected to the tube elements have at least one point connected to cathode, these points also are "returned to ground." Ground is therefore a common reference point in the radio circuit. "Ground potential" means that there is no "difference of potential"-no voltage-between the circuit point and the earth.

Single-Ended and Balanced Circuits

With reference to ground, a circuit may be either single-ended (unbalanced) or balanced. In a single-ended circuit, one side of the circuit is connected to ground. In a balanced circuit, the electrical midpoint is connected to ground, so that the circuit has two ends each at the same voltage "above" ground.

Typical single-ended and balanced circuits are shown in Fig. 2-59. R.f. circuits are shown in the upper row, while iron-core transformers

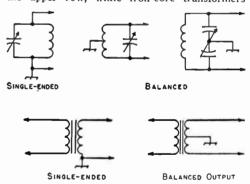


Fig. 2-59—Single-ended and balanced circuits.

(such as are used in power-supply and audio circuits) are shown in the lower row. The r.f. circuits may be balanced either by connecting the center of the coil to ground or by using a "balanced" or "split-stator" capacitor and connecting its rotor to ground. In the iron-core transformer, one or both windings may be tapped at the center of the winding to provide the ground connection.

Shielding

Two circuits that are physically near each other usually will be coupled to each other in some degree even though no coupling is intended. The metallic parts of the two circuits form a small capacitance through which energy can be transferred by means of the electric field. Also, the magnetic field about the coil or wiring of

one circuit can couple that circuit to a second through the latter's coil and wiring. In many cases these unwanted couplings must be prevented if the circuits are to work properly.

Capacitive coupling may readily be prevented by enclosing one or both of the circuits in grounded low-resistance metallic containers, called **shields**. The electric field from the circuit components does not penetrate the shield. A metallic plate, called a **baffle shield**, inserted between two components also may suffice to prevent electrostatic coupling between them. It should be large enough to make the components invisible to each other.

Similar metallic shielding is used at radio frequencies to prevent magnetic coupling. The shielding effect for magnetic fields increases with frequency and with the conductivity and thickness of the shielding material.

A closed shield is required for good magnetic shielding; in some cases separate shields, one about each coil, may be required. The baffle shield is rather ineffective for magnetic shielding, al-

though it will give partial shielding if placed at right angles to the axes of, and between, the coils to be shielded from each other.

Shielding a coil reduces its inductance, because part of its field is canceled by the shield. Also, there is always a small amount of resistance in the shield, and there is therefore an energy loss. This loss raises the effective resistance of the coil. The decrease in inductance and increase in resistance lower the Q of the coil, but the reduction in inductance and Q will be small if the spacing between the sides of the coil and the shield is at least half the coil diameter, and if the spacing at the ends of the coil is at least equal to the coil diameter. The higher the conductivity of the shield material, the less the effect on the inductance and Q. Copper is the best material, but aluminum is quite satisfactory.

For good magnetic shielding at audio frequencies it is necessary to enclose the coil in a container of high-permeability iron or steel. In this case the shield can be quite close to the coil without harming its performance.

U.H.F. CIRCUITS

RESONANT LINES

In resonant circuits as employed at the lower frequencies it is possible to consider each of the reactance components as a separate entity. The fact that an inductor has a certain amount of self-capacitance, as well as some resistance, while a capacitor also possesses a small self-inductance, can usually be disregarded.

At the very-high and ultrahigh frequencies it is not readily possible to separate these components. Also, the connecting leads, which at lower frequencies would serve merely to join the capacitor and coil, now may have more inductance than the coil itself. The required inductance coil may be no more than a single turn of wire, yet even this single turn may have dimensions comparable to a wavelength at the operating frequency. Thus the energy in the field surrounding the "coil" may in part be radiated. At a sufficiently high frequency the loss by radiation may represent a major portion of the total energy in the circuit.

For these reasons it is common practice to utilize resonant sections of transmission line as tuned circuits at frequencies above 100 Mc. or so. A quarter-wavelength line, or any odd multiple thereof, shorted at one end and open at the other exhibits large standing waves, as described in the section on transmission lines. When a voltage of the frequency at which such a line is resonant is applied to the open end, the response is very similar to that of a parallel resonant circuit. The equivalent relationships are shown in Fig. 2-60. At frequencies off resonance the line displays qualities comparable with the inductive and capacitive reactances of a conventional tuned circuit, so sections of transmission line can be used in much the same manner as inductors and capacitors.

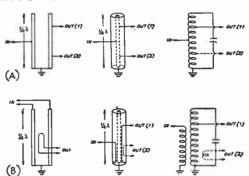


Fig. 2-60—Equivalent coupling circuits for parallel-line, coaxial-line and conventional resonant circuits.

To minimize radiation loss the two conductors of a parallel-conductor line should not be more than about one-tenth wavelength apart, the spacing being measured between the conductor axes. On the other hand, the spacing should not be less than about twice the conductor diameter because of "proximity effect," which causes eddy currents and an increase in loss. Above 300 Mc. it is difficult to satisfy both these requirements simultaneously, and the radiation from an open line tends to become excessive, reducing the Q. In such case the coaxial type of line is to be preferred, since it is inherently shielded.

Representative methods for adjusting coaxial lines to resonance are shown in Fig. 2-61. At the left, a sliding shorting disk is used to reduce the effective length of the line by altering the position of the short-circuit. In the center, the same effect is accomplished by using a telescoping tube in the end of the inner conductor to vary its length and thereby the effective length of the line. At the right, two possible methods of using

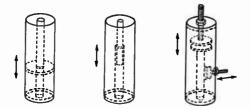


Fig. 2-61—Methods of tuning coaxial resonant lines.

parallel-plate capacitors are illustrated. The arrangement with the loading capacitor at the open end of the line has the greatest tuning effect per unit of capacitance; the alternative method, which is equivalent to tapping the capacitor down on the line, has less effect on the Q of the circuit. Lines with capacitive "loading" of the sort illustrated will be shorter, physically, than unloaded lines resonant at the same frequency.

Two methods of tuning parallel-conductor lines are shown in Fig. 2-62. The sliding short-

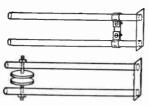


Fig. 2-62—Methods of tuning parallel-type resonant lines.

circuiting strap can be tightened by means of screws and nuts to make good electrical contact. The parallel-plate capacitor in the second drawing may be placed anywhere along the line, the tuning effect becoming less as the capacitor is located nearer the shorted end of the line. Although a low-capacitance variable capacitor of ordinary construction can be used, the circular-plate type shown is symmetrical and thus does not unbalance the line. It also has the further advantage that no insulating material is required.

WAVEGUIDES

A waveguide is a conducting tube through which energy is transmitted in the form of electromagnetic waves. The tube is not considered as carrying a current in the same sense that the wires of a two-conductor line do, but rather as a boundary which confines the waves to the enclosed space. Skin effect prevents any electromagnetic effects from being evident outside the guide. The energy is injected at one end, either through capacitive or inductive coupling or by radiation, and is received at the other end. The waveguide then merely confines the energy of the fields, which are propagated through it to the receiving end by means of reflections against its inner walls.

Analysis of waveguide operation is based on the assumption that the guide material is a perfect conductor of electricity. Typical distributions of electric and magnetic fields in a rectangular guide are shown in Fig. 2-63. It will be observed that the intensity of the electric field is greatest (as indicated by closer spacing of the lines of force) at the center along the x dimension, Fig. 2-63 (B), diminishing to zero at the end walls. The latter is a necessary condition, since the existence of any electric field parallel to the walls at the surface would cause an infinite current to flow in a perfect conductor. This represents an impossible situation.

Modes of Propagation

Fig. 2-63 represents a relatively simple distribution of the electric and magnetic fields.

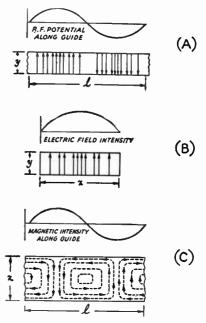


Fig. 2-63—Field distribution in a rectangular waveguide. The $IE_{1/0}$ mode of propagation is depicted.

There is in general an infinite number of ways in which the fields can arrange themselves in a guide so long as there is no upper limit to the frequency to be transmitted. Each field configuration is called a mode. All modes may be separated into two general groups. One group, designated TM (transverse magnetic), has the magnetic field entirely transverse to the direction of propagation, but has a component of electric field in that direction. The other type, designated TE (transverse electric) has the electric field entirely transverse, but has a component of magnetic field in the direction of propagation. TM waves are sometimes called E waves, and TE waves are sometimes called H waves, but the TM and TE designations are preferred.

The particular mode of transmission is identified by the group letters followed by two subscript numerals; for example, $TE_{1,0}$, $TM_{1,1}$, etc. The number of possible modes increases with

Waveguides 57

frequency for a given size of guide. There is only one possible mode (called the dominant mode) for the lowest frequency that can be transmitted. The dominant mode is the one generally used in practical work.

Waveguide Dimensions

In the rectangular guide the critical dimension is x in Fig. 2-63; this dimension must be more than one-half wavelength at the lowest frequency to be transmitted. In practice, the y dimension usually is made about equal to $\frac{1}{2}x$ to avoid the possibility of operation at other than the dominant mode.

Other cross-sectional shapes than the rectangle can be used, the most important being the circular pipe. Much the same considerations apply as in the rectangular case.

Wavelength formulas for rectangular and circular guides are given in the following table, where x is the width of a rectangular guide and r is the radius of a circular guide. All figures are in terms of the dominant mode.

Re	ctangula	r Circular
Cut-off wavelength	2.	3.41r
Longest wavelength trans-		
mitted with little atten-		
uation	1.6.	3.2r
Shortest wavelength before		
next mode hecomes pos-		
sible	1.1x	2.8r

Cavity Resonators

Another kind of circuit particularly applicable at wavelengths of the order of centimeters is the cavity resonator, which may be looked upon as a section of a waveguide with the dimensions chosen so that waves of a given length can be maintained inside.

Typical shapes used for resonators are the cylinder, the rectangular box and the sphere, as shown in Fig. 2-64. The resonant frequency depends upon the dimensions of the cavity and the mode of oscillation of the waves (comparable to

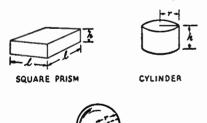


Fig. 2-64—Forms of cavity resonators.

the transmission modes in a waveguide). For the lowest modes the resonant wavelengths are as follows:

Cylinder	2.61r
Square box	1.41/
Sphere	2.28r

The resonant wavelengths of the cylinder and square box are independent of the height when the height is less than a half wavelength. In other modes of oscillation the height must be a multiple of a half wavelength as measured inside the cavity. A cylindrical cavity can be tuned by a sliding shorting disk when operating in such a mode. Other tuning methods include placing adjustable tuning paddles or "slugs" inside the cavity so that the standing-wave pattern of the electric and magnetic fields can be varied.

A form of cavity resonator in practical use is the re-entrant cylindrical type shown in Fig. 2-65. In construction it resembles a concentric line closed at both ends with capacitive loading at the top, but the actual mode of oscillation may

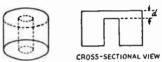


Fig. 2-65—Re-entrant cylindrical cavity resonator.

differ considerably from that occurring in coaxial lines. The resonant frequency of such a cavity depends upon the diameters of the two cylinders and the distance d between the cylinder ends.

Compared with ordinary resonant circuits, cavity resonators have extremely high Q. A value of Q of the order of 1000 or more is readily obtainable, and Q values of several thousand can be secured with good design and construction.

Coupling to Waveguides and Cavity Resonators

Energy may be introduced into or abstracted from a waveguide or resonator by means of either the electric or magnetic field. The energy transfer frequently is through a coaxial line, two methods for coupling to which are shown in Fig. 2-66. The probe shown at A is simply a short extension of the inner conductor of the coaxial line, so oriented that it is parallel to the electric lines of force. The loop shown at B is arranged so that it encloses some of the magnetic lines of force. The point at which maximum coupling will be secured depends upon the particular mode of propagation in the guide or cavity; the coupling will be maximum when the coupling device is in the most intense field.

Coupling can be varied by turning the probe or loop through a 90-degree angle. When the probe is perpendicular to the electric lines the coupling will be minimum; similarly, when the plane of the loop is parallel to the magnetic lines the coupling will have its minimum value.

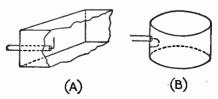


Fig. 2-66—Coupling to waveguides and resonators.

MODULATION, HETERODYNING AND BEATS

Since one of the most widespread uses of radio frequencies is the transmission of speech and music, it would be very convenient if the audio spectrum to be transmitted could simply be shifted up to some radio frequency, transmitted as radio waves, and shifted back down to audio at the receiving point. Suppose the audio signal to be transmitted by radio is a pure 1000-cycle tone, and we wish to transmit it at 1 Mc. (1,000,000 cycles per second). One possible way might be to add 1.000 Mc. and 1 kc. together, thereby obtaining a radio frequency of 1.001 Mc. No simple method for doing this directly has been devised, although the *effect* is obtained and used in "single-sideband transmission."

When two different frequencies are present simultaneously in an ordinary circuit (specifically, one in which Ohm's Law holds) each be-

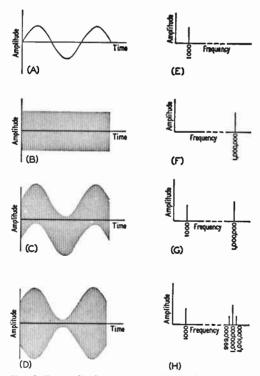


Fig. 2-67—Amplitude-vs.-time and amplitude-vs.-frequency plots of various signals. (A) $1\frac{1}{2}$ cycles of an audio signal, assumed to be 1000 c.p.s. in this example. (B) A radio-frequency signal, assumed to be 1 Mc.; 1500 cycles are completed during the same time as the $1\frac{1}{2}$ cycles in A, so they cannot be shown accurately. (C) The signals of A and B in the same circuit; each maintains its own identity. (D) The signals of A and B in a circuit where the amplitude of A can control the amplitude of B. The 1-Mc. signal is modulated by the 1000-cycle signal.

E, F, G and H shaw the spectrums far the signals in A, B, C and D, respectively. Nate the new frequencies in H, resulting from the madulation process.

haves as though the other were not there. The total or resultant voltage (or current) in the circuit will be the sum of the instantaneous values of the two at every instant. This is because there can be only one value of current or voltage at any single point in a circuit at any instant. Figs. 2-67A and B show two such frequencies, and C shows the resultant. The amplitude of the 1-Mc. current is not affected by the presence of the 1-kc. current, but the axis is shifted back and forth at the 1-kc. rate. An attempt to transmit such a combination as a radio wave would result in only the radiation of the 1-Mc. frequency, since the 1-kc. frequency retains its identity as an audio frequency and will not radiate.

There are devices, however, which make it possible for one frequency to control the amplitude of the other. If, for example, a 1-kc. tone is used to control a 1-Mc. signal, the maximum r.f. output will be obtained when the 1-kc. signal is at the peak of one alternation and the minimum will occur at the peak of the next alternation. The process is called amplitude modulation, and the effect is shown in Fig. 2-67D. The resultant signal is now entirely at radio frequency, but with its amplitude varying at the modulation rate (1 kc.). Receiving equipment adjusted to receive the 1-Mc. r.f. signal can reproduce these changes in amplitude, and reveal what the audio signal is, through a process called detection.

It might be assumed that the only radio frequency present in such a signal is the original 1.000 Mc., but such is not the case. Two new frequencies have appeared. These are the sum (1.000 + .001) and the difference (1.000 - .001) of the two, and thus the radio frequencies appearing after modulation are 1.001, 1.000 and .999 Mc.

When an audio frequency is used to control the amplitude of a radio frequency, the process is generally called "amplitude modulation," as mentioned, but when a radio frequency modulates another radio frequency it is called heterodyning. The processes are identical. A general term for the sum and difference frequencies generated during heterodyning or amplitude modulation is "beat frequencies," and a more specific one is upper side frequency, for the sum, and lower side frequency for the difference.

In the simple example, the modulating signal was assumed to be a pure tone, but the modulating signal can just as well be a band of frequencies making up speech or music. In this case, the side frequencies are grouped into the upper sideband and the lower sideband. Fig. 2-67H shows the side frequencies appearing as a result of the modulation process.

Amplitude modulation (a.m.) is not the only possible type nor is it the only one in use. Such signal properties as phase and frequency can also be modulated. In every case the modulation process leads to the generation of a new set (or sets) of radio frequencies symmetrically disposed about the original radio (carrier) frequency.

Vacuum-Tube Principles

CURRENT IN A VACUUM

The outstanding difference between the vacuum tube and most other electrical devices is that the electric current does not flow through a conductor but through empty space—a vacuum. This is only possible when "free" electrons—that is, electrons that are not attached to atoms—are somehow introduced into the vacuum. Free electrons in an evacuated space will be attracted to a positively charged object within the same space, or will be repelled by a negatively charged object. The movement of the electrons under the attraction or replusion of such charged objects constitutes the current in the vacuum.

The most practical way to introduce a sufficiently large number of electrons into the evacuated space is by thermionic emission.

Thermionic Emission

If a thin wire or filament is heated to incandescence in a vacuum, electrons near the surface are given enough energy of motion to fly off into the surrounding space. The higher the temperature, the greater the number of electrons emitted. A more general name for the filament is cathode.

If the cathode is the only thing in the vacuum, most of the emitted electrons stay in its immediate vicinity, forming a "cloud" about the cath-



Representative tube types. Transmitting tubes having up to 500-watt capability are shown in the back row. The tube with the top cap in the middle row is a low-power transmitting type. Others are receiving tubes, with the exception of the one in the center foreground which is a v.h.f. transmitting type.

ode. The reason for this is that the electrons in the space, being negative electricity, form a negative charge (space charge) in the region of the cathode. The space charge repels those electrons nearest the cathode, tending to make them fall back on it.

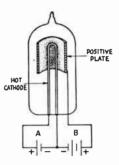


Fig. 3-1—Conduction by thermionic emission in a vacuum tube. The A battery is used to heat the filament to a temperature that will cause it to emit electrons. The B battery makes the plate positive with respect to the filoment, thereby causing the emitted electrons to be attracted to the plate. Electrons coptured by the plate flow back through the B battery to the filoment.

Now suppose a second conductor is introduced into the vacuum, but not connected to anything else inside the tube. If this second conductor is given a positive charge by connecting a source of e.m.f. between it and the cathode, as indicated in Fig. 3-1, electrons emitted by the cathode are attracted to the positively charged conductor. An electric current then flows through the circuit formed by the cathode, the charged conductor, and the source of e.m.f. In Fig. 3-1 this e.m.f. is supplied by a battery ("B" battery); a second battery ("A" battery) is also indicated for heating the cathode or filament to the proper operating temperature.

The positively charged conductor is usually a metal plate or cylinder (surrounding the cathode) and is called an anode or plate. Like the other working parts of a tube, it is a tube element or electrode. The tube shown in Fig. 3-1 is a two-element or two-electrode tube, one element being the cathode or filament and the other the anode or plate.

Since electrons are negative electricity, they will be attracted to the plate *only* when the plate is positive with respect to the cathode. If the plate is given a negative charge, the

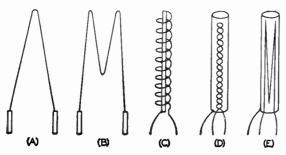


Fig. 3-2—Types of cathode construction. Directly heated cathodes or filaments are shown at A, B, and C. The inverted V filament is used in small receiving tubes, the M in both receiving and transmitting tubes. The spiral filament is a transmitting tube type. The indirectly-heated cathodes at D and E show two types of heater construction, ane a twisted loop and the other bunched heater wires. Both types tend to cancel the magnetic fields set up by the current through the heater.

electrons will be repelled back to the cathode and no current will flow. The vacuum tube therefore can conduct only in one direction.

Cathodes

Before electron emission can occur, the cathode must be heated to a high temperature. However, it is not essential that the heating current flow through the actual material that does the emitting; the filament or heater can be electrically separate from the emitting cathode. Such a cathode is called indirectly heated, while an emitting filament is called directly heated. Fig. 3-2 shows both types in the forms in which they are commonly used.

Much greater electron emission can be obtained, at relatively low temperatures, by using special cathode materials rather than pure metals. One of these is **thoriated tungsten**, or tungsten in which thorium is dissolved. Still greater efficiency is achieved in the **oxide-coated** cathode, a cathode in which rare-earth oxides form a coating over a metal base.

Although the oxide-coated cathode has much the highest efficiency, it can be used successfully only in tubes that operate at rather low plate voltages. Its use is therefore confined to receiving-type tubes and to the smaller varieties of transmitting tubes. The thoriated filament, on the other hand, will operate well in high-voltage tubes.

Plate Current

If there is only a small positive voltage on the plate, the number of electrons reaching it will be small because the space charge (which is negative) prevents those electrons nearest the cathode from being attracted to the plate. As the plate voltage is increasingly overcome and the number of electrons attracted to the plate becomes larger. That is, the plate current increases with increasing plate voltage.

Fig. 3-3 shows a typical plot of plate current vs. plate voltage for a two-element tube or diode. A curve of this type can be obtained with the circuit shown, if the plate voltage is increased in small steps and a current reading taken (by means of the current-indicating instrument-a milliammeter) at each voltage. The plate current is zero with no plate voltage and the curve rises until a saturation point is reached. This is where the positive charge on the plate has substantially overcome the space charge and almost all the electrons are going to the plate. At higher voltages the plate current stays at practically the same value.

The plate voltage multiplied by the plate current is the **power input** to the tube. In a circuit like that of Fig. 3-3 this power is all used in heating the plate. If

the power input is large, the plate temperature may rise to a very high value (the plate may become red or even white hot). The heat developed in the plate is radiated to the bulb of the tube, and in turn radiated by the bulb to the surrounding air.

RECTIFICATION

Since current can flow through a tube in only one direction, a diode can be used to change alternating current into direct current. It does this by permitting current to flow when the plate is positive with respect to the cathode, but by shutting off current flow when the plate is negative.

Fig. 3-4 shows a representative circuit. Alternating voltage from the secondary of the transformer, T, is applied to the diode tube in series with a load resistor, R. The voltage varies as is usual with a.c., but current flows through the tube and R only when the plate is positive with respect to the cathode—that is, during the half-cycle when the upper end of the transformer winding is positive. During the negative half-cycle there is simply a gap in the current flow. This rectified alternating current therefore is an intermittent direct current.

The load resistor, R, represents the actual circuit in which the rectified alternating current does work. All tubes work with a load of one type or another; in this respect a tube is much like a generator or transformer. A circuit that did not

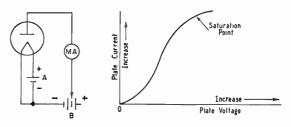


Fig. 3-3—The diode, or two-element tube, and a typical curve showing how the plate current depends upon the valtage applied to the plate.

Vacuum-Tube Amplifiers

provide a load for the tube would be like a short-circuit across a transformer; no useful purpose would be accomplished and the only result would be the generation of heat in the transformer. So it is with vacuum tubes; they must cause power to be developed in a load in order to serve a useful purpose. Also, to be efficient most of the power must do useful work in the load and not be

used in heating the plate of the tube. Thus the voltage drop across the load should be much higher than the drop across the diode.

With the diode connected as shown in Fig. 3-4,


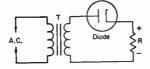


Fig. 3-4—Rectification in a diode.
Current flows only when the plate
is positive with respect to the cathode, so that only half-cycles of
current flow through the load resistor, R.

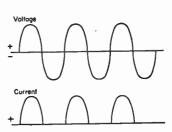

the polarity of the voltage across the load is as indicated. If the diode were reversed, the polarity of the voltage developed across the load R would be reversed.

VACUUM-TUBE AMPLIFIERS

TRIODES

Grid Control

If a third element—called the control grid, or simply grid—is inserted between the cathode and plate as in Fig. 3-5, it can be used to control the effect of the space charge. If the grid is given a positive voltage with respect to the cathode, the positive charge will tend to neutralize the negative space charge. The result is that, at any

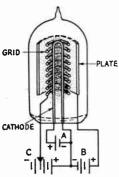


Fig. 3-5—Construction of an elementary triode vacuum tube, showing the filament, grid (with an end view of the grid wires) and plate. The relative density of the space charge is indicated roughly by the dot density.

selected plate voltage, more electrons will flow to

the plate than if the grid were not present. On the other hand, if the grid is made negative with respect to the cathode the negative charge on the grid will add to the space charge. This will reduce the number of electrons that can reach the plate at any selected plate voltage.

The grid is inserted in the tube to control the space charge and not to attract electrons to itself, so it is made in the form of a wire mesh or spiral. Electrons then can go through the open spaces in the grid to reach the plate.

Characteristic Curves


For any particular tube, the effect

of the grid voltage on the plate current can be shown by a set of characteristic curves. A typical set of curves is shown in Fig. 3-6, together with the circuit that is used for getting them. For each value of plate voltage, there is a value of negative grid voltage that will reduce the plate current to zero; that is, there is a value of negative grid voltage that will cut off the plate current

The curves could be extended by making the grid voltage positive as well as negative. When the grid is negative, it repels electrons and therefore none of them reaches it; in other words, no current flows in the grid circuit. However, when the grid is positive, it attracts electrons and a current (grid current) flows, just as current flows to the positive plate. Whenever there is grid current there is an accompanying power loss in the grid circuit, but so long as the grid is negative no power is used.

It is obvious that the grid can act as a value to control the flow of plate current. Actually, the grid has a much greater effect on plate current flow than does the plate voltage. A small change in grid voltage is just as effective in bringing about a given change in plate current as is a large change in plate voltage.

The fact that a small voltage acting on the grid

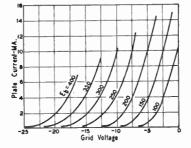

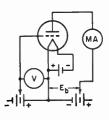


Fig. 3-6—Grid-voltage-vs.-plate-current curves at various fixed values of plate voltage (E_b) for a typical small triode. Characteristic curves of this type can be taken by varying the battery voltages in the circuit at the right.

is equivalent to a large voltage acting on the plate indicates the possibility of amplification with the triode tube. The many uses of the electronic tube nearly all are based upon this amplifying feature. The amplified output is not obtained from the tube itself, but from the source of e.m.f. connected between its plate and cathode. The tube simply controls the power from this source, changing it to the desired form.

To utilize the controlled power, a load must be connected in the plate or "output" circuit, just as in the diode case. The load may be either a resistance or an impedance. The term "impedance" is frequently used even when the load is purely resistive.

Tube Characteristics

The physical construction of a triode, determines the relative effectiveness of the grid and plate in controlling the plate current. If a very small change in the grid voltage has just as much effect on the plate current as a very large change in plate voltage, the tube is said to have a high amplification factor. Amplification factor is commonly designated by the Greek letter μ . An amplification factor of 20, for example, means that if the grid voltage is changed by I volt, the effect on the plate current will be the same as when the plate voltage is changed by 20 volts. The amplification factors of triode tubes range from 3 to 100 or so. A high- μ tube is one with an amplification factor of perhaps 30 or more; medium-µ tubes have amplification factors in the approximate range 8 to 30, and low-µ tubes in the range below 7 or 8.

It would be natural to think that a tube that has a large μ would be the best amplifier, but to obtain a high μ it is necessary to construct the grid with many turns of wire per inch, or in the form of a fine mesh. This leaves a relatively small open area for electrons to go through to reach the plate, so it is difficult for the plate to attract large numbers of electrons. Quite a large change in the plate voltage must be made to effect a given change in plate current. This means that the resistance of the plate-cathode path-that is, the plate resistance—of the tube is high. Since this resistance acts in series with the load, the amount of current that can be made to flow through the load is relatively small. On the other hand, the plate resistance of a low- μ tube is relatively low.

The best all-around indication of the effectiveness of the tube as an amplifier is its grid-plate transconductance—also called mutual conductance. This characteristic takes account of both amplification factor and plate resistance, and therefore is a figure of merit for the tube. Transconductance is the change in plate current divided by the change in grid voltage that causes the plate-current change (the plate voltage being fixed at a desired value). Since current divided by voltage is conductance, transconductance is measured in the unit of conductance, the mho. Practical values of transconductance are very small, so the micromho (one-millionth of a mho)

is the commonly-used unit. Different types of tubes have transconductances ranging from a few hundred to several thousand. The higher the transconductance the greater the possible amplification.

AMPLIFICATION

The way in which a tube amplifies is best shown by a type of graph called the dynamic characteristic. Such a graph, together with the circuit used for obtaining it, is shown in Fig. 3-7.

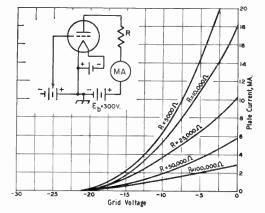


Fig. 3-7—Dynamic characteristics of a small triode with various load resistances from 5000 to 100,000 ohms.

The curves are taken with the plate-supply voltage fixed at the desired operating value. The difference between this circuit and the one shown in Fig. 3-6 is that in Fig. 3-7 a load resistance is connected in series with the plate of the tube. Fig. 3-7 thus shows how the plate current will vary, with different grid voltages, when the plate current is made to flow through a load and thus do useful work.

The several curves in Fig. 3-7 are for various values of load resistance. When the resistance is small (as in the case of the 5000-ohm load) the plate current changes rather rapidly with a given change in grid voltage. If the load resistance is high (as in the 100,000-ohm curve), the change in plate current for the same grid-voltage change is relatively small; also, the curve tends to be straighter.

Fig. 3-8 is the same type of curve, but with the circuit arranged so that a source of alternating voltage (signal) is inserted between the grid and the grid battery ("C" battery). The voltage of the grid battery is fixed at -5 volts, and from the curve it is seen that the plate current at this grid voltage is 2 milliamperes. This current flows when the load resistance is 50,000 ohms, as indicated in the circuit diagram. If there is no a.c. signal in the grid circuit, the voltage drop in the load resistor is $50,000 \times 0.002 = 100$ volts, leaving 200 volts between the plate and cathode.

When a sine-wave signal having a peak value of 2 volts is applied in series with the bias voltage in the grid circuit, the instantaneous voltage at the grid will swing to -3 volts at the instant the

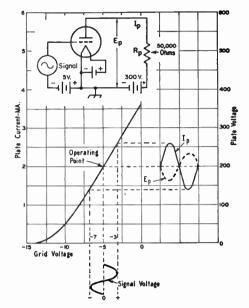


Fig. 3-8—Amplifier operation. When the plate current various in response to the signal applied to the grid, a varying voltage drop appears across the load, R_p , as shown by the dashed curve, E_p . I_p is the plate current.

signal reaches its positive peak, and to -7 volts at the instant the signal reaches its negative peak. The maximum plate current will occur at the instant the grid voltage is -3 volts. As shown by the graph, it will have a value of 2.65 milliamperes. The minimum plate current occurs at the instant the grid voltage is -7 volts, and has a value of 1.35 ma. At intermediate values of grid voltage, intermediate plate-current values will occur.

The instantaneous voltage between the plate and cathode of the tube also is shown on the graph. When the plate current is maximum, the instantaneous voltage drop in $R_{\rm p}$ is 50,000 \times 0.00265 = 132.5 volts; when the plate current is minimum the instantaneous voltage drop in $R_{\rm p}$ is 50,000 \times 0.00135 = 67.5 volts. The actual voltage between plate and cathode is the difference between the plate-supply potential, 300 volts, and the voltage drop in the load resistance. The plate-to-cathode voltage is therefore 167.5 volts at maximum plate current and 232.5 volts at minimum plate current.

This varying plate voltage is an a.c. voltage superimposed on the steady plate-cathode potential of 200 volts (as previously determined for nosignal conditions). The peak value of this a.c. output voltage is the difference between either the maximum or minimum plate-cathode voltage and the no-signal value of 200 volts. In the illustration this difference is 232.5 — 200 or 200 — 167.5; that is, 32.5 volts in either case. Since the grid signal voltage has a peak value of 2 volts, the voltage-amplification ratio of the amplifier is 32.5/2 or 16.25. That is, approximately 16 times as much voltage is obtained from

the plate circuit as is applied to the grid circuit.

As shown by the drawings in Fig. 3-8, the alternating component of the plate voltage swings in the negative direction (with reference to the no-signal value of plate-cathode voltage) when the grid voltage swings in the positive direction, and vice versa. This means that the alternating component of plate voltage (that is, the amplified signal) is 180 degrees out of phase with the signal voltage on the grid.

Bias

The fixed negative grid voltage (called grid bias) in Fig. 3-8 serves a very useful purpose. One object of the type of amplification shown in this drawing is to obtain, from the plate circuit, an alternating voltage that has the same waveshape as the signal voltage applied to the grid. To do so, an operating point on the straight part of the curve must be selected. The curve must be straight in both directions from the operating point at least far enough to accommodate the maximum value of the signal applied to the grid. If the grid signal swings the plate current back and forth over a part of the curve that is not straight, as in Fig. 3-9, the shape of the a.c. wave in the plate circuit will not be the same as the shape of the grid-signal wave. In such a case the output wave shape will be distorted.

A second reason for using negative grid bias is that any signal whose peak positive voltage does not exceed the fixed negative voltage on the grid cannot cause grid current to flow. With no current flow there is no power consumption, so the tube will amplify without taking any power from the signal source. (However, if the positive peak of the signal does exceed the negative bias, current will flow in the grid circuit during the time the grid is positive.)

Distortion of the output wave shape that results

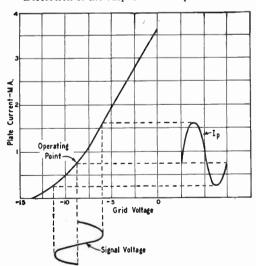


Fig. 3-9—Harmonic distortion resulting from choice of an operating point on the curved part of the tube characteristic. The lower half-cycle of plate current does not have the same shape as the upper half-cycle.

from working over a part of the curve that is not straight (that is, a nonlinear part of the curve) has the effect of transforming a sine-wave grid signal into a more complex waveform. As explained in an earlier chapter, a complex wave can be resolved into a fundamental and a series of harmonics. In other words, distortion from nonlinearity causes the generation of harmonic frequencies—frequencies that are not present in the signal applied to the grid. Harmonic distortion is undesirable in most amplifiers, although there are occasions when harmonics are deliberately generated and used.

Amplifier Output Circuits

The useful output of a vacuum-tube amplifier is the alternating component of plate current or plate voltage. The d.c. voltage on the plate of the tube is essential for the tube's operation, but it almost invariably would cause difficulties if it were applied, along with the a.c. output voltage, to the load. The output circuits of vacumm tubes are therefore arranged so that the a.c. is transferred to the load but the d.c. is not.


Three types of coupling are in common use at audio frequencies. These are resistance coupling, impedance coupling, and transformer coupling. They are shown in Fig. 3-10. In all three cases the output is shown coupled to the grid circuit of a subsequent amplifier tube, but the same types of circuits can be used to couple to other devices than tubes.


In the resistance-coupled circuit, the a.c. voltage developed across the plate resistor $R_{\rm p}$ (that is, the a.c. voltage between the plate and cathode of the tube) is applied to a second resistor, $R_{\rm g}$, through a coupling capacitor, $C_{\rm c}$. The capacitor "blocks off" the d.c. voltage on the plate of the first tube and prevents it from being applied to the grid of tube B. The latter tube has negative grid bias supplied by the battery shown. No current flows on the grid circuit of tube B and there is therefore no d.c. voltage drop in $R_{\rm g}$; in other words, the full voltage of the bias battery is applied to the grid of tube B.

The grid resistor, $R_{\rm g}$, usually has a rather high value (0.5 to 2 megohms). The reactance of the coupling capacitor, $C_{\rm e}$, must be low enough compared with the resistance of $R_{\rm g}$ so that the a.c. voltage drop in $C_{\rm e}$ is negligible at the lowest frequency to be amplified. If $R_{\rm g}$ is at least 0.5 megohm, a 0.1- μ f. capacitor will be amply large for the usual range of audio frequencies.

So far as the alternating component of plate voltage is concerned, it will be realized that if the voltage drop in C_e is negligible then R_p and R_g are effectively in parallel (although they are quite separate so far as d.c. is concerned). The resultant parallel resistance of the two is therefore the actual load resistance for the tube. That is why R_g is made as high in resistance as possible; then it will have the least effect on the load represented by R_p .

The impedance-coupled circuit differs from that using resistance coupling only in the substitution of a high-inductance coil (usually sev-

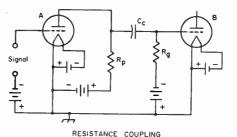

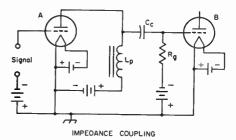

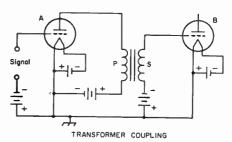


Fig. 3-10—Three basic forms of coupling between vacuum-tube amplifiers.

eral hundred henrys for audio frequencies) for the plate resistor. The advantage of using an inductance rather than a resistor is that its impedance is high for alternating currents, but its resistance is relatively low for d.c. It thus permits obtaining a high value of load impedance for a.c. without an excessive d.c. voltage drop that would use up a good deal of the voltage from the plate supply.

The transformer-coupled amplifier uses a transformer with its primary connected in the plate circuit of the tube and its secondary connected to the load (in the circuit shown, a following amplifier). There is no direct connection between the two windings, so the plate voltage on tube A is isolated from the grid of tube B. The transformer-coupled amplifier has the same advantage as the impedance-coupled circuit with respect to loss of d.c. voltage from the plate supply. Also, if the secondary has more turns than the primary, the output voltage will be "stepped up" in proportion to the turns ratio.

Resistance coupling is simple, inexpensive, and will give the same amount of amplification—or voltage gain—over a wide range of frequencies; it will give substantially the same amplification

at any frequency in the audio range, for example. Impedance coupling will give somewhat more gain, with the same tube and same plate-supply voltage, than resistance coupling. However, it is not quite so good over a wide frequency range; it tends to "peak," or give maximum gain, over a comparatively narrow band of frequencies. With a good transformer the gain of a transformer-coupled amplifier can be kept fairly constant over the audio-frequency range. On the other hand, transformer coupling in voltage amplifiers (see below) is best suited to triodes having amplification factors of about 20 or less, for the reason that the primary inductance of a practicable transformer cannot be made large enough to work well with a tube having high plate resistance.

Class A Amplifiers

An amplifier in which voltage gain is the primary consideration is called a voltage amplifier. Maximum voltage gain is secured when the load resistance or impedance is made as high as possible in comparison with the plate resistance of the tube. In such a case, the major portion of the voltage generated will appear across the load.

Voltage amplifiers belong to a group called Class A amplifiers. A Class A amplifier is one operated so that the wave shape of the output voltage is the same as that of the signal voltage applied to the grid. If a Class A amplifier is biased so that the grid is always negative, even with the largest signal to be handled by the grid, it is called a Class A_1 amplifier. Voltage amplifiers are always Class A_1 amplifiers, and their primary use is in driving a following Class A_1 amplifier.

Power Amplifiers

The end result of any amplification is that the amplified signal does some work. For example, an audio-frequency amplifier usually drives a loudspeaker that in turn produces sound waves. The greater the amount of a.f. power supplied to the speaker the louder the sound it will produce.

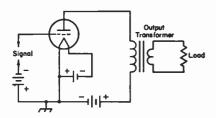


Fig. 3-11—An elementary power-amplifier circuit in which the power-consuming load is coupled to the plate circuit through an impedance-matching transformer.

Fig. 3-11 shows an elementary power-amplifier circuit. It is simply a transformer-coupled amplifier with the load connected to the secondary. Although the load is shown as a resistor, it actually would be some device, such as a loud-speaker, that employs the power usefully. Every power tube requires a specific value of load re-

sistance from plate to cathode, usually some thousands of ohms, for optimum operation. The resistance of the actual load is rarely the right value for "matching" this optimum load resistance, so the transformer turns ratio is chosen to reflect the proper value of resistance into the primary. The turns ration may be either step-up or step-down, depending on whether the actual load resistance is higher or lower than the load the tube wants.

The power-amplification ratio of an amplifier is the ratio of the power output obtained from the plate circuit to the power required from the a.c. signal in the grid circuit. There is no power lost in the grid circuit of a Class A1 amplifier, so such an amplifier has an infinitely large poweramplification ratio. However, it is quite possible to operate a Class A amplifier in such a way that current flows in its grid circuit during at least part of the cycle. In such a case power is used up in the grid circuit and the power amplification ratio is not infinite. A tube operated in this fashion is known as a Class A2 amplifier. It is necessary to use a power amplifier to drive a Class A2 amplifier, because a voltage amplifier cannot deliver power without serious distortion of the wave shape.

Another term used in connection with power amplifiers is power sensitivity. In the case of a Class A₁ amplifier, it means the ratio of power output to the grid signal voltage that causes it. If grid current flows, the term usually means the ratio of plate power output to grid power input.


The a.c. power that is delivered to a load by an amplifier tube has to be paid for in power taken from the source of plate voltage and current. In fact, there is always more power going into the plate circuit of the tube than is coming out as useful output. The difference between the input and output power is used up in heating the plate of the tube, as explained previously. The ratio of useful power output to d.c. plate input is called the plate efficiency. The higher the plate efficiency, the greater the amount of power that can be taken from a tube having a given plate-dissipation rating.

Parailel and Push-Puli

When it is necessary to obtain more power output than one tube is capable of giving, two or more similar tubes may be connected in parallel. In this case the similar elements in all tubes are connected together. This method is shown in Fig. 3-12 for a transformer-coupled amplifier. The power output is in proportion to the number of tubes used; the grid signal or exciting voltage required, however, is the same as for one tube.

If the amplifier operates in such a way as to consume power in the grid circuit, the grid power required is in proportion to the number of tubes used.

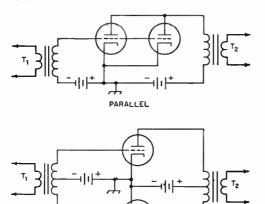An increase in power output also can be secured by connecting two tubes in push-pull. In this case the grids and plates of the two tubes are connected to opposite ends of a balanced circuit as shown in Fig. 3-12, At any instant the



PUSH-PULL

Fig. 3-12—Parallel and push-pull a.f. amplifier circuits.

ends of the secondary winding of the input transformer, T_1 , will be at opposite polarity with respect to the cathode connection, so the grid of one tube is swung positive at the same instant that the grid of the other is swung negative. Hence, in any push-pull-connected amplifier the voltages and currents of one tube are out of phase with those of the other tube.

In push-pull operation the even-harmonic (second, fourth, etc.) distortion is balanced out in the plate circuit. This means that for the same power output the distortion will be less than with parallel operation.

The exciting voltage measured between the two grids must be twice that required for one tube. If the grids consume power, the driving power for the push-pull amplifier is twice that taken by either tube alone.

Cascade Amplifiers

It is readily possible to take the output of one amplifier and apply it as a signal on the grid of a second amplifier, then take the second amplifier's output and apply it to a third, and so on. Each amplifier is called a stage, and stages used successively are said to be in cascade.

Class B Amplifiers

Fig 3-13 shows two tubes connected in a pushpull circuit. If the grid bias is set at the point where (when no signal is applied) the plate current is just cut off, then a signal can cause plate current to flow in either tube only when the signal voltage applied to that particular tube is positive with respect to the cathode. Since in the balanced grid circuit the signal voltages on the grids of the two tubes always have opposite polarities, plate current flows only in one tube at a time.

The graphs show the operation of such an amplifier. The plate current of tube B is drawn inverted to show that it flows in the opposite direction, through the primary of the output transformer, to the plate current of tube A. Thus each

half of the output-transformer primary works alternately to induce a half-cycle of voltage in the secondary. In the secondary of T_2 , the original waveform is restored. This type of operation is called **Class B** amplification.

The Class B amplifier has considerably higher plate efficiency than the Class A amplifier. Furthermore, the d.c. plate current of a Class B amplifier is proportional to the signal voltage on the grids, so the power input is small with small signals. The d.c. plate power input to a Class A amplifier is the same whether the signal is large, small, or absent altogether; therefore the maximum d.c. plate input that can be applied to a Class A amplifier is equal to the rated plate dissipation of the tube or tubes. Two tubes in a Class B amplifier can deliver approximately twelve time as much audio power as the same two tubes in a Class A amplifier.

A Class B amplifier usually is operated in such a way as to secure the maximum possible poweroutput. This requires rather large values of plate current, and to obtain them the signal voltage must completely overcome the grid bias during at least part of the cycle, so grid current flows and the grid circuit consumes power. While the power requirements are fairly low (as compared with the power output), the fact that the grids are positive during only part of the cycle means that the load on the preceding amplifier or driver stage varies in magnitude during the cycle; the effective load resistance is high when the grids are not drawing current and relatively low when they do take current. This must be allowed for when designing the driver.

Certain types of tubes have been designed specifically for Class B service and can be operated without fixed or other form of grid bias (zero-bias tubes). The amplification factor is so high that the plate current is small without signal. Because there is no fixed bias, the grids start drawing current immediately whenever a

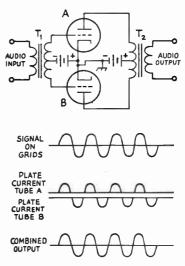


Fig. 3-13—Class B amplifier operation.

Class B Amplifiers

signal is applied, so the grid-current flow is countinuous throughout the cycle. This makes the load on the driver much more constant than is the case with tubes of lower μ biased to plate-current cut-off.

Class B amplifiers used at radio frequencies are known as linear amplifiers because they are adjusted to operate in such a way that the power output is proportional to the square of the r.f. exciting voltage. This permits amplification of a modulated r.f. signal without distortion. Pushpull is not required in this type of operation; a single tube can be used equally well.

Class AB Amplifiers

A Class AB amplifier is a push-pull amplifier with higher bias than would be normal for pure Class A operation, but less than the cut-off bias required for Class B. At low signal levels the tubes operate practically as Class A amplifiers, and the plate current is the same with or without signal. At higher signal levels, the plate current of one tube is cut off during part of the negative cycle of the signal applied to its grid, and the plate current of the other tube rises with the signal. The plate current for the whole amplifier also rises above the no-signal level when a large signal is applied.

In a properly designed Class AB amplifier the distortion is as low as with a Class A stage, but the efficiency and power output are considerably higher than with pure Class A operation. A Class AB amplifier can be operated either with or without driving the grids into the positive region. A Class AB, amplifier is one in which the grids are never positive with respect to the cathode; therefore, no driving power is required—only voltage. A Class AB₂ amplifier is one that has gridcurrent flow during part of the cycle if the applied signal is large; it takes a small amount of driving power. The Class AB₂ amplifier will deliver somewhat more power (using the same tubes) but the Class AB1 amplifier avoids the problem of designing a driver that will deliver power, without distortion, into a load of highly variable resistance.

Operating Angle

Inspection of Fig. 3-13 shows that either of the two tubes actually is working for only half the a.c. cycle and idling during the other half. It is convenient to describe the amount of time during which plate current flows in terms of electrical degrees. In Fig. 3-13 each tube has "180-degree" excitation, a half-cycle being equal to 180 degrees. The number of degrees during which plate current flows is called the operating angle of the amplifier. From the descriptions given above, it should be clear that a Class A amplifier has 360-degree excitation, because plate current flows during the whole cycle. In a Class AB amplifier the operating angle is between 180 and 360 degrees (in each tube) depending on the particular operating conditions chosen. The greater the amount of negative grid bias, the smaller the operating angle becomes.

An operating angle of less than 180 degrees leads to a considerable amount of distortion, because there is no way for the tube to reproduce even a half-cycle of the signal on its grid. Using two tubes in push-pull, as in Fig 3-13, would merely put together two distorted half-cycles. An operating angle of less than 180 degrees therefore cannot be used if distortionless output is wanted.

Class C Amplifiers

In power amplifiers operating at radio frequencies distortion of the r.f. wave form is relatively unimportant. For reasons described later in this chapter, an r.f. amplifier must be operated with tuned circuits, and the selectivity of such circuits "filters out" the r.f. harmonics resulting from distortion.

A radio-frequency power amplifier therefore can be used with an operating angle of less than 180 degrees. This is call Class C operation. The advantage is the that plate efficiency is increased, because the loss in the plate is proportional, among other things, to the amount of time during which the plate current flows, and this time is reduced by decreasing the operating angle.

Depending on the type of tube, the optimum load resistance for a Class C amplifier ranges from about 1500 to 5000 ohms. It is usually secured by using tuned-circuit arrangements, of the type described in the chapter on circuit fundamentals, to transform the resistance of the actual load to the value required by the tube. The grid is driven well into the positive region, so that grid current flows and power is consumed in the grid circuit. The smaller the operating angle, the greater the driving voltage and the larger the grid driving power required to develop full output in the load resistance. The best compromise between driving power, plate efficiency, and power output usually results when the minimum plate voltage (at the peak of the driving cycle, when the plate current reaches its highest value) is just equal to the peak positive grid voltage. Under these conditions the operating angle is usually between 150 and 180 degrees and the plate efficiency lies in the range of 70 to 80 percent. While higher plate efficiencies are possible, attaining them requires excessive driving power and grid bias, together with higher plate voltage than is "normal" for the particular tube type.

With proper design and adjustment, a Class C amplifier can be made to operate in such a way that the power input and output are proportional to the square of the applied plate voltage. This is an important consideration when the amplifier is to be plate-modulated for radiotelephony, as described in the chapter on amplitude modulation.

FEEDBACK

It is possible to take a part of the amplified energy in the plate circuit of an amplifier and insert it into the grid circuit. When this is done the amplifier is said to have feedback.

If the voltage that is inserted in the grid circuit is 180 degrees out of phase with the signal


VACUUM-TUBE PRINCIPLES

voltage acting on the grid, the feedback is called negative, or degenerative. On the other hand, if the voltage is fed back in phase with the grid signal, the feedback is called positive, or regenerative.

Negative Feedback

With negative feedback the voltage that is fed back opposes the signal voltage. This decreases the amplitude of the voltage acting between the grid and cathode and thus has the effect of reducing the voltage amplification. That is, a larger exciting voltage is required for obtaining the same output voltage from the plate circuit.

The greater the amount of negative feedback (when properly applied) the more independent the amplification becomes of tube characteristics and circuit conditions. This tends to make the frequency-response characteristic of the amplifier flat—that is, the amplification tends to be the same at all frequencies within the range for which the amplifier is designed. Also, any distortion generated in the plate circuit of the tube tends to "buck itself out." Amplifiers with negative feedback are therefore comparatively free from harmonic distortion. These advantages are worth while if the amplifier otherwise has enough voltage gain for its intended use.

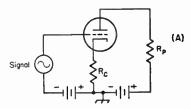

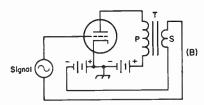


Fig. 3-14-Simple circuits for producing feedbock.

In the circuit shown at A in Fig. 3-14 resistor $R_{\rm e}$ is in series with the regular plate resistor, $R_{\rm p}$ and thus is a part of the load for the tube. Therefore, part of the output voltage will appear across $R_{\rm e}$. However, $R_{\rm e}$ also is connected in series with the grid circuit, and so the output voltage that appears across $R_{\rm e}$ is in series with the signal voltage. The output voltage across $R_{\rm e}$ opposes the signal voltage, so the actual a.c. voltage between the grid and cathode is equal to the difference between the two voltages.

The circuit shown at B in Fig. 3-14 can be used to give either negative or positive feedback. The secondary of a transformer is connected back into the grid circuit to insert a desired amount of

feedback voltage. Reversing the terminals of either transformer winding (but not both simultaneously) will reverse the phase.

Positive Feedback

Positive feedback increases the amplification because the feedback voltage adds to the original signal voltage and the resulting larger voltage on the grid causes a larger output voltage. The amplification tends to be greatest at one frequency (which depends upon the particular circuit arrangement) and harmonic distortion is increased. If enough energy is fed back, a selfsustaining oscillation—in which energy at essentially one frequency is generated by the tube itself-will be set up. In such case all the signal voltage on the grid can be supplied from the plate circuit; no external signal is needed because any small irregularity in the plate current-and there are always some such irregularities—will be amplified and thus give the oscillation an opportunity to build up. Positive feedback finds a major application in such "oscillators," and in addition is used for selective amplification at both audio and radio frequencies, the feedback being kept below the value that causs self-oscillation.

INTERELECTRODE CAPACITANCES

Each pair of elements in a tube forms a small capacitor, with each element acting as a capacitor "plate." There are three such capacitances in a triode—that between the grid and cathode, that between the grid and plate, and that between the plate and cathode. The capacitances are very small—only a few micromicrofarads at most—but they frequently have a very pronounced effect on the operation of an amplifier circuit.

Input Capacitance

It was explained perviously that the a.c. grid voltage and a.c. plate voltage of an amplifier having a resistive load are 180 degrees out of phase, using the cathode of the tube as a reference point. However, these two voltages are *in* phase going around the circuit from plate to grid as shown in Fig. 3-15. This means that their sum is acting between the grid and plate; that is, across the grid-plate capacitance of the tube.

As a result, a capacitive current flows around the circuit, its amplitude being directly proportional to the sum of the a.c. grid and plate

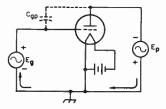


Fig. 3-15—The o.c. voltage appearing between the grid and plate of the amplifier is the sum of the signal voltage and the output voltage, os shown by this simplified circuit. Instantaneous polarities are indicated.

Screen-Grid Tubes

voltages and to the grid-plate capacitance. The source of grid signal must furnish this amount of current, in addition to the capacitive current that flows in the grid-cathode capacitance. Hence the signal source "sees" an effective capacitance that is larger than the grid-cathode capacitance. This is known as the Miller Effect.

The greater the voltage amplification the greater the effective input capacitance. The input capacitance of a resistance-coupled amplifier is given by the formula

$$C_{input} = C_{gk} + C_{gp}(A + 1)$$

where $C_{\rm gx}$ is the grid-to-cathode capacitance, $C_{\rm gp}$ is the grid-to-plate capacitance, and A is the voltage amplification. The input capacitance may be as much as several hundred micromicrofarads when the voltage amplification is large, even though the interelectrode capacitances are quite small.

Output Capacitance

The principal component of the output capacitance of an amplifier is the actual plate-to-cathode capacitance of the tube. The output capacitance usually need not be considered in audio amplifiers, but becomes of importance at radio frequencies.

Tube Capacitance at R.F.

At radio frequencies the reactances of even very small interelectrode capacitances drop to very low values. A resistance-coupled amplifier gives very little amplification at r.f., for example, because the reactances of the interlectrode "capacitors" are so low that they practically short-circuit the input and output circuits and thus the tube is unable to amplify. This is overcome at radio frequencies by using tuned circuits for the grid and plate, making the tube capacitances part of the tuning capacitances. In this way the circuits can have the high resistive impedances necessary for satisfactory amplification.

The grid-plate capacitance is important at radio frequencies because its reactance, relatively low at r.f., offers a path over which energy can be fed back from the plate to the grid. In practically every case the feedback is in the right phase and of sufficient amplitude to cause self-oscillation, so the circuit becomes useless as an amplifier.

Special "neutralizing" circuits can be used to prevent feedback but they are, in general, not too satisfactory when used in radio receivers. They are, however, used in transmitters.

SCREEN-GRID TUBES

The grid-plate capacitance can be reduced to a negligible value by inserting a second grid between the control grid and the plate, as indicated in Fig. 3-16. The second grid, called the screen grid, acts as an electrostatic shield to prevent capacitive coupling between the control grid and plate. It is made in the form of a grid or coarse screen so that electrons can pass through it.

Because of the shielding action of the screen

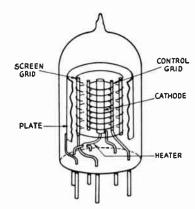


Fig. 3-16—Representative arrangement of elements in a screen-grid tetrade, with part of plate and screen cut away. This is "single-ended" construction with a button base, typical of miniature receiving tubes. To reduce capacitance between control grid and plate the leads fram these elements are brought aut at opposite sides; actual tubes prabably would have additional shielding between these leads.

grid, the positively charged plate cannot attract electrons from the cathode as it does in a triode. In order to get electrons to the plate, it is necessary to apply a positive voltage (with respect to the cathode) to the screen. The screen then attracts electrons much as does the plate in a triode tube. In traveling toward the screen the electrons acquire such velocity that most of them shoot between the screen wires and then are attracted to the plate. A certain proportion do strike the screen, however, with the result that some current also flows in the screen-grid circuit.

To be a good shield, the screen grid must be connected to the cathode through a circuit that has low impedance at the frequency being amplified. A bypass capacitor from screen grid to cathode, having a reactance of not more than a few hundred ohms, is generally used.

A tube having a cathode, control grid, screen grid and plate (four elements) is called a tetrode.

Pentodes

When an electron traveling at appreciable velocity through a tube strikes the plate it dislodges other electrons which "splash" from the plate into the interelement space. This is called secondary emission. In a triode the negative grid repels the secondary electrons back into the plate and they cause no disturbance. In the screen-grid tube, however, the positively charged screen attracts the secondary electrons, causing a reverse current to flow between screen and plate.

To overcome the effects of secondary emission, a third grid, called the suppressor grid, may be inserted between the screen and plate. This grid acts as a shield between the screen grid and plate so the secondary electrons cannot be attracted by the screen grid. They are hence attracted back to the plate without appreciably obstructing the regular plate-current flow. A five-element tube of this type is called a pentode.

Although the screen grid in either the tetrode or pentode greatly reduces the influence of the plate upon plate-current flow, the control grid still can control the plate current in essentially the same way that it does in a triode. Consequently, the grid-plate transconductance (or mutual conductance) of a tetrode or pentode will be of the same order of value as in a triode of corresponding structure. On the other hand, since a change in plate voltage has very little effect on the plate-current flow, both the amplification factor and plate resistance of a pentode or tetrode are very high. In small receiving pentodes the amplification factor is of the order of 1000 or higher, while the plate resistance may be from 0.5 to 1 or more megohms. Because of the high plate resistance, the actual voltage amplification possible with a pentode is very much less than the large amplification factor might indicate. A voltage gain in the vicinity of 50 to 200 is typical of a pentode stage.

In practical screen-grid tubes the grid-plate capacitance is only a small fraction of a micromicrofarad. This capacitance is too small to cause an appreciable increase in input capacitance as described in the preceding section, so the input capacitance of a screen-grid tube is simply the sum of its grid-cathode capacitance and control-grid-to-screen capacitance. The output capacitance of a screen-grid tube is equal to the capacitance between the plate and screen.

In addition to their applications as radio-frequency amplifiers, pentodes or tetrodes also are used for audio-frequency power amplification. In tubes designed for this purpose the chief function of the screen is to serve as an accelerator of the electrons, so that large values of plate current can be drawn at relatively low plate voltages. Such tubes have quite high power sensitivity compared with triodes of the same power output, although harmonic distortion is somewhat greater.

Beam Tubes

A beam tetrode is a four-element screen-grid tube constructed in such a way that the electrons are formed into concentrated beams on their way to the plate. Additional design features overcome the effects of secondary emission so that a suppressor grid is not needed. The "beam" construction makes it possible to draw large plate currents at relatively low plate voltages, and increases the power sensitivity.

For power amplification at both audio and radio frequencies beam tetrodes have largely supplanted the non-beam types because large power outputs can be secured with very small amounts of grid driving power.

Variable-µ Tubes

The mutual conductance of a vacuum tube decreases when its grid bias is made more negative, assuming that the other electrode voltages are held constant. Since the mutual conductance controls the amount of amplification, it is possible to adjust the gain of the amplifier by adjusting

the grid bias. This method of gain control is universally used in radio-frequency amplifiers designed for receivers.

The ordinary type of tube has what is known as a sharp-cutoff characteristic. The mutual conductance decreases at a uniform rate as the negative bias is increased. The amount of signal voltage that such a tube can handle without causing distortion is not sufficient to take care of very strong signals. To overcome this, some tubes are made with a variable- μ characteristic—that is, the amplification factor decreases with increasing grid bias. The variable- μ tube can handle a much larger signal than the sharp-cutoff type before the signal swings either beyond the zero grid-bias point or the plate-current cutoff point.

INPUT AND OUTPUT IMPEDANCES

The input impedance of a vacuum-tube amplifier is the impedance "seen" by the signal source when connected to the input terminals of the amplifier. In the types of amplifiers previously discussed, the input impedance is the impedance measured between the grid and cathode of the tube with operating voltages applied. At audio frequencies the input impedance of a Class A1 amplifier is for all practical purposes the input capacitance of the stage. If the tube is driven into the grid-current region there is in addition a resistance component in the input impedance, the resistance having an average value equal to E^2/P , where E is the r.m.s. driving voltage and P is the power in watts consumed in the grid. The resistance usually will vary during the a.c. cycle because grid current may flow only during part of the cycle; also, the grid-voltage/grid-current characteristic is seldom linear.

The output impedance of amplifiers of this type consists of the plate resistance of the tube shunted by the output capacitance.


At radio frequencies, when tuned circuits are employed, the input and output impedances are usually pure resistances; any reactive components are "tuned out" in the process of adjusting the circuits to resonance at the operating frequency.

OTHER TYPES OF AMPLIFIERS

In the amplifier circuits so far discussed, the signal has been applied between the grid and cathode and the amplified output has been taken from the plate-to-cathode circuit. That is, the cathode has been the meeting point for the input and output circuits. However, it is possible to use any one of the three principal elements as the common point. This leads to two additional kinds of amplifiers, commonly called the grounded-grid amplifier (or grid-separation circuit) and the cathode follower.

These two circuits are shown in simplified form in Fig. 3-17. In both circuits the resistor R represents the load into which the amplifier works; the actual load may be resistance-capacitance-coupled, transformer-coupled, may be a tuned circuit if the amplifier operates at radio

Cathode Circuits and Grid Bias

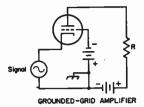

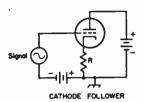


Fig. 3-17—In the upper circuit, the grid is the junction point between the input and output circuits. In the lower drowing, the plate is the junction. In either case the output is developed in the load resistor, R, and may be coupled to a following amplifier by the usual methods.

frequencies, and so on. Also, in both circuits the batteries that supply grid bias and plate power are assumed to have such negligible impedance that they do not enter into the operation of the circuits.

Grounded-Grid Amplifier

In the grounded-grid amplifier the input signal is applied between the cathode and grid, and the output is taken between the plate and grid. The grid is thus the common element. The a.c. component of the plate current has to flow through the signal source to reach the cathode. The source of signal is in series with the load through the plate-to-cathode resistance of the tube, so some of the power in the load is supplied by the signal source. In transmitting applications this fed-through power is of the order of 10 per cent of the total power output, using tubes suitable for grounded-grid service.

The input impedance of the grounded-grid amplifier consists of a capacitance in parallel with an equivalent resistance representing the power furnished by the driving source of the grid and to the load. This resistance is of the order of a few hundred ohms. The output impedance, neglecting the interelectrode capacitances, is equal to the plate resistance of the tube. This is the same as in the case of the grounded-cathode

amplifier.

The grounded-grid amplifier is widely used at v.h.f. and u.h.f., where the more conventional

amplifier circuit fails to work properly. With a triode tube designed for this type of operation, an r.f. amplifier can be built that is free from the type of feedback that causes oscillation. This requires that the grid act as a shield between the cathode and plate, reducing the plate-cathode capacitance to a very low value.

Cathode Follower

The cathode follower uses the plate of the tube as the common element. The input signal is applied between the grid and plate (assuming negligible impedance in the batteries) and the output is taken between cathode and plate. This circuit is degenerative; in fact, all of the output voltage is fed back into the input circuit out of phase with the grid signal. The input signal therefore has to be larger than the output voltage; that is, the cathode follower gives a loss in voltage, although it gives the same power gain as other circuits under equivalent operating conditions.

An important feature of the cathode follower is its low output impedance, which is given by the formula (neglecting interelectrode capaci-

$$Z_{\text{out}} = \frac{r_{\text{p}}}{1 + \mu}$$

tances) where r_p is the tube plate resistance and μ is the amplification factor. Low output impedance is a valuable characteristic in an amplifier designed to cover a wide band of frequencies. In addition, the input capacitance is only a fraction of the grid-to-cathode capacitance of the tube, a feature of further benefit in a wide-band amplifier. The cathode follower is useful as a step-down impedance transformer, since the input impedance is high and the output impedance is low.

CATHODE CIRCUITS AND GRID BIAS

Most of the equipment used by amateurs is powered by the a.c. line. This includes the filaments or heaters of vacuum tubes. Although supplies for the plate (and sometimes the grid) are usually rectified and filtered to give pure d.c. — that is, direct current that is constant and without a superimposed a.c. component — the relatively large currents required by filaments and heaters usually make a rectifier-type d.c. supply impracticable.

Filament Hum

Alternating current is just as good as direct current from the heating standpoint, but some of the a.c. voltage is likely to get on the grid and cause a low-pitched "a.c. hum" to be superimposed on the output.

Hum troubles are worst with directly-heated cathodes or filaments, because with such cathodes there has to be a direct connection between the source of heating power and the rest of the circuit. The hum can be minimized by either of

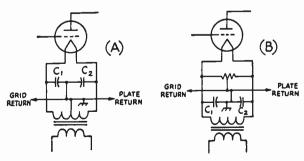


Fig. 3-18—Filoment center-topping methods for use with directly heated tubes.

the connections shown in Fig. 3-18. In both cases the grid- and plate-return circuits are connected to the electrical midpoint (center tap) of the filament supply. Thus, so far as the grid and plate are concerned, the voltage and current on one side of the filament are balanced by an equal and opposite voltage and current on the other side. The balance is never quite perfect, however, so filament-type tubes are never completely humfree. For this reason directly-heated filaments are employed for the most part in power tubes, where the amount of hum introduced is extremely small in comparison with the power-output level.

With indirectly heated cathodes the chief problem is the magnetic field set up by the heater. Occasionally, also, there is leakage between the heater and cathode, allowing a small a.c. voltage to get to the grid. If hum appears, grounding one side of the heater supply usually will help to reduce it, although sometimes better results are obtained if the heater supply is center-tapped and the center-tap grounded, as in Fig. 3-18.

Cathode Bias

In the simplified amplifier circuits discussed in this chapter, grid bias has been supplied by a battery. However, in equipment that operates from the power line cathode bias is very frequently used.

The cathode-bias method uses a resistor (cathode resistor) connected in series with the cathode, as shown at R in Fig. 3-19. The direction of plate-current flow is such that the end of the resistor nearest the cathode is positive. The voltage drop across R therefore places a negative voltage on the grid. This negative bias is obtained from the steady d.c. plate current.

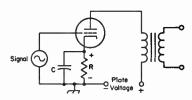


Fig. 3-19—Cathode biasing. R is the cathode resistor and C is the cathode bypass capacitor.

If the alternating component of plate current flows through R when the tube is amplifying, the voltage drop caused by the a.c. will be degenerative (note the similarity between this circuit and that of Fig. 3-14A). To prevent this the resistor is bypassed by a capacitor, C, that has very low reactance compared with the resistance of R. Depending on the type of tube and the particular kind of operation, R may be between about 100 and 3000 ohms. For good bypassing at the low audio frequencies, C should be 10 to 50 microfarads (electrolytic capacitors are used for this purpose). At radio frequencies, capacitances of about 100 $\mu\mu$ f. to 0.1 μ f. are used; the small values are sufficient at very high frequencies and the largest at low and medium frequencies. In

VACUUM-TUBE PRINCIPLES

the range 3 to 30 megacycles a capacitance of 0.01 μ f. is satisfactory.

The value of cathode resistor for an amplifier having negligible d.c. resistance in its plate circuit (transformer or impedance coupled) can easily be calculated from the known operating conditions of the tube. The proper grid bias and plate current always are specified by the manufacturer. Knowing these, the required resistance can be found by applying Ohm's Law.

Example: It is found from tube tables that the tube to be used should have a negative grid bias of 8 volts and that at this bias the plate current will be 12 milliamperes (0.012 amp.). The required cathode resistance is then

$$R = \frac{E}{I} = \frac{8}{0.012} = 667 \text{ ohms.}$$

The nearest standard value, 680 ohms, would be close enough. The power used in the resistor is

$$P = EI = 8 \times 0.012 = 0.096$$
 watt.

A 1/4-watt or 1/2-watt resistor would have ample rating.

The current that flows through R is the total cathode current. In an ordinary triode amplifier this is the same as the plate current, but in a screen-grid tube the cathode current is the sum of the plate and screen currents. Hence these two currents must be added when calculating the value of cathode resistor required for a screen-grid tube.

Example: A receiving pentode requires 3 volts negative bias. At this bias and the recommended plate and screen voltages, its plate current is 9 ma. and its screen current is 2 ma. The cathode current is therefore 11 ma. (0.011 amp.). The required resistance is

$$R = \frac{E}{I} = \frac{3}{0.011} = 272 \text{ ohms.}$$

A 270-ohm resistor would be satisfactory. The power in the resistor is

$$P = EI = 3 \times 0.011 = 0.033$$
 watt.

The cathode-resistor method of biasing is self-regulating, because if the tube characteristics vary slightly from the published values (as they do in practice) the bias will increase if the plate current is slightly high, or decrease if it is slightly low. This tends to hold the plate current at the proper value.

Calculation of the cathode resistor for a resistance-coupled amplifier is ordinarily not practicable by the method described above, because the plate current in such an amplifier is usually much smaller than the rated value given in the tube tables. However, representative data for the tubes commonly used as resistance-coupled amplifiers are given in the chapter on audio amplifiers, including cathode-resistor values.

"Contact Potential" Bias

In the absence of any negative bias voltage on the grid of a tube, some of the electrons in the space charge will have enough velocity to reach the grid. This causes a small current (of the order of microamperes) to flow in the external Oscillators 73

circuit between the grid and cathode. If the current is made to flow through a high resistance—a megohm or so—the resulting voltage drop in the resistor will give the grid a negative bias of the order of one volt. The bias so obtained is called contact-potential bias.

Contact-potential bias can be used to advantage in circuits operating at low signal levels (less than one volt peak) since it eliminates the cathode-bias resistor and bypass capacitor. It is principally used in low-level resistance-coupled audio amplifiers. The bias resistor is connected directly between grid and cathode, and must be isolated from the signal source by a blocking capacitor.

Screen Supply

In practical circuits using tetrodes and pentodes the voltage for the screen frequently is taken from the plate supply through a resistor. A typical circuit for an r.f. amplifier is shown in Fig. 3-20. Resistor R is the screen dropping resistor, and C is the screen bypass capacitor. In flowing through R, the screen current causes a voltage drop in R that reduces the plate-supply voltage to the proper value for the screen. When the plate-supply voltage and the screen current are known, the value of R can be calculated from Ohm's Law.

Example: An r.f. receiving pentode has a rated screen current of 2 milliamperes (0.002 amp.) at normal operating conditions. The rated screen voltage is 100 volts, and the plate supply gives 250 volts. To put 100 volts on the screen, the drop across R must be equal to the difference between the plate-supply

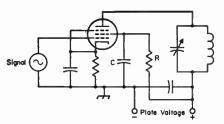


Fig. 3-20—Screen-voltage supply for a pentode tube through a dropping resistor, R. The screen bypass capacitor, C, must have low enough reactance to bring the screen to ground potential for the frequency or frequencies being amplified.

voltage and the screen voltage; that is, 250 - 100 = 150 volts. Then

$$R = \frac{E}{I} = \frac{150}{0.002} = 75,000 \text{ ohms.}$$

The power to be dissipated in the resistor is

$$P = EI = 150 \times 0.002 = 0.3$$
 watt.

A 1/2. or 1-watt resistor would be satisfactory.

The reactance of the screen bypass capacitor, C, should be low compared with the screen-to-cathode impedance. For radio-frequency applications a capacitance in the vicinity of 0:01 μ f. is amply large.


In some vacuum-tube circuits the screen voltage is obtained from a voltage divider connected across the plate supply. The design of voltage dividers is discussed at length in Chapter 7 on Power Supplies.

OSCILLATORS

It was mentioned earlier that if there is enough positive feedback in an amplifier circuit, self-sustaining oscillations will be set up. When an amplifier is arranged so that this condition exists it is called an oscillator.

Oscillations normally take place at only one frequency, and a desired frequency of oscillation can be obtained by using a resonant circuit tuned to that frequency. For example, in Fig. 3-21A the circuit LC is tuned to the desired frequency of oscillation. The cathode of the tube is connected to a tap on coil L and the grid and plate are connected to opposite ends of the tuned circuit. When an r.f. current flows in the tuned circuit there is a voltage drop across L that increases progressively along the turns. Thus the point at which the tap is connected will be at an intermediate potential with respect to the two ends of the coil. The amplified current in the plate circuit, which flows through the bottom section of L, is in phase with the current already flowing in the circuit and thus in the proper relationship for positive feedback.

The amount of feedback depends on the position of the tap. If the tap is too near the grid end the voltage drop between grid and cathode is too small to give enough feedback to sustain oscillation, and if it is too near the plate end the impedance between the cathode and plate is too small to permit good amplification. Maximum

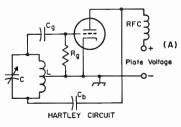

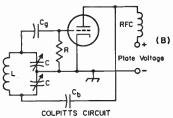


Fig. 3-21—Basic oscillator circuits. Feedback voltage is obtained by tapping the grid and cathode across a portion of the tuned circuit. In the Hartley circuit the tap is on the coil, but in the Colpitts circuit the voltage is obtained from the drop across a capacitor.

feedback usually is obtained when the tap is somewhere near the center of the coil.

The circuit of Fig. 3-21A is parallel-fed, C_b being the blocking capacitor. The value of C_b is not critical so long as its reactance is low (not more than a few hundred ohms) at the operating frequency.

Capacitor $C_{\mathbf{g}}$ is the grid capacitor. It and $R_{\mathbf{g}}$ (the grid leak) are used for the purpose of obtaining grid bias for the tube. In most oscillator circuits the tube generates its own bias. During the part of the cycle when the grid is positive with respect to the cathode, it attracts electrons. These electrons cannot flow through L back to the cathode because Cz "blocks" direct current. They therefore have to flow or "leak" through $R_{\rm g}$ to cathode, and in doing so cause a voltage drop in R_g that places a negative bias on the grid. The amount of bias so developed is equal to the grid current multiplied by the reistance of $R_{\rm g}$ (Ohm's Law). The value of grid-leak resistance required depends upon the kind of tube used and the purpose for which the oscillator is intended. Values range all the way from a few thousand to several hundred thousand ohms. The capacitance of $C_{\rm g}$ should be large enough to have low reactance (a few hundred ohms) at the operating frequency.

The circuit shown at B in Fig. 3-21 uses the voltage drops across two capacitors in series in the tuned circuit to supply the feedback. Other than this, the operation is the same as just described. The feedback can be varied by varying the ratio of the reactance of C_1 and C_2 (that is, by varying the ratio of their capacitances).

Another type of oscillator, called the tunedplate tuned-grid circuit, is shown in Fig. 3-22.

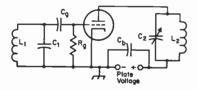


Fig. 3-22—The tuned-plate tuned-grid oscillotor.

Resonant circuits tuned approximately to the same frequency are connected between grid and cathode and between plate and cathode. The two coils, L_1 and L_2 , are not magnetically coupled. The feedback is through the grid-plate capacitance of the tube, and will be in the right phase to be positive when the plate circuit, C_1L_2 , is tuned to a slightly higher frequency than the grid circuit, L_1C_1 . The amount of feedback can be adjusted by varying the tuning of either circuit. The frequency of oscillation is determined by the tuned circuit that has the higher Q. The grid leak and grid capacitor have the same functions as in the other circuits. In this case it is convenient to use series feed for the plate circuit, so C_b is a bypass capacitor to guide the r.f. current around the plate supply.

There are many oscillator circuits (examples

of others will be found in later chapters) but the basic feature of all of them is that there is positive feedback in the proper amplitude and phase to sustain oscillation.

Oscillator Operating Characteristics

When an oscillator is delivering power to a load, the adjustment for proper feedback will depend on how heavily the oscillator is loaded—that is, how much power is being taken from the circuit. If the feedback is not large enough—grid excitation too small—a small increase in load may tend to throw the circuit out of oscillation. On the other hand, too much feedback will make the grid current excessively high, with the result that the power loss in the grid circuit becomes larger than necessary. Since the oscillator itself supplies this grid power, excessive feedback lowers the over-all efficiency because whatever power is used in the grid circuit is not available as useful output.

One of the most important considerations in oscillator design is frequency stability. The principal factors that cause a change in frequency are (1) temperature, (2) plate voltage, (3) loading, (4) mechanical variations of circuit elements. Temperature changes will cause vacuum-tube elements to expand or contract slightly, thus causing variations in the interelectrode capacitances. Since these are unavoidably part of the tuned circuit, the frequency will change correspondingly. Temperature changes in the coil or the tuning capacitor will alter the inductance or capacitance slightly, again causing a shift in the resonant frequency. These effects are relatively show in operation, and the frequency change caused by them is called drift.

A change in plate voltage usually will cause the frequency to change a small amount, an effect called dynamic instability. Dynamic instability can be reduced by using a tuned circuit of high effective Q. The energy taken from the circuit to supply grid losses, as well as energy supplied to a load, represent an increase in the effective resistance of the tuned circuit and thus lower its Q. For highest stability, therefore, the coupling between the tuned circuit and the tube and load must be kept as loose as possible. Preferably, the oscillator should not be required to deliver power to an external circuit, and a high value of grid leak resistance should be used since this helps to raise the tube grid and plate resistances as seen by the tuned circuit. Loose coupling can be effected in a variety of ways - one, for example, is by "tapping down" on the tank for the connections to the grid and plate. This is done in the "series-tuned" Colpitts circuit widely used in variable-frequency oscillators for amateur transmitters and described in a later chapter. Alternatively, the L/C ratio may be made as small as possible while sustaining stable oscillation (high C) with the grid and plate connected to the ends of the circuit as shown in Figs. 3-21 and 3-22. Using relatively high plate voltage and low plate current also is desirable.

In general, dynamic stability will be at maxi-

Clipping Circuits

mum when the feedback is adjusted to the least value that permits reliable oscillation. The use of a tube having a high value of transconductance is desirable, since the higher the transconductance the looser the permissible coupling to the tuned circuit and the smaller the feedback required.

Load variations act in much the same way as plate-voltage variations. A temperature change in the load may also result in drift.

Mechanical variations, usually caused by vibration, cause changes in inductance and/or capacitance that in turn cause the frequency to "wobble" in step with the vibration.

Methods of minimizing frequency variations in oscillators are taken up in detail in later chapters.

Ground Point

In the oscillator circuits shown in Figs. 3-21 and 3-22 the cathode is connected to ground. It is not actually essential that the radio-frequency circuit should be grounded at the cathode; in fact, there are many times when an r.f. ground on some other point in the circuit is desirable. The r.f. ground can be placed at any point so long as proper provisions are made for feeding the supply voltages to the tube elements.

Fig. 3-23 shows the Hartley circuit with the plate end of the circuit grounded. No r.f. choke is

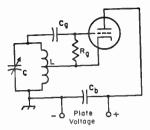



Fig. 3-23—Shawing how the plate may be grounded for r.f. in a typical ascillator circuit (Hartley).

needed in the plate circuit because the plate already is at ground potential and there is no r.f. to choke off. All that is necessary is a bypass capacitor, C_b , across the plate supply. Direct current flows to the cathode through the lower part of the tuned-circuit coil, L. An advantage of such a circuit is that the frame of the tuning capacitor can be grounded.

Tubes having indirectly heated cathodes are more easily adaptable to circuits grounded at other points than the cathode than are tubes having directly heated filaments. With the latter tubes special precautions have to be taken to prevent the filament from being bypassed to ground by the capacitance of the filament-heating transformer.

CLIPPING CIRCUITS

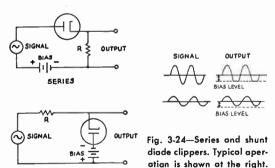Vacuum tubes are readily adaptable to other types of operation than ordinary (without substantial distortion) amplification and the genera-



tion of single-frequency oscillations. Of particular interest is the clipper or limiter circuit, because of its several applications in receiving and other equipment.

SHUNT

Diode Clipper Circuits

Basic diode clipper circuits are shown in Fig. 3-24. In the series type a positive d.c. bias voltage is applied to the plate of the diode so it is normally conducting. When a signal is applied the current through the diode will change proportionately during the time the signal voltage is positive at the diode plate and for that part of

the negative half of the signal during which the instantaneous voltage does not exceed the bias. When the negative signal voltage exceeds the

positive bias the resultant voltage at the diode plate is negative and there is no conduction. Thus part of the negative half cycle is clipped as shown in the drawing at the right. The level at which clipping occurs depends on the bias voltage, and the proportion of signal clipping depends on the signal strength in relation to the bias voltage. If the peak signal voltage is below the bias level there is no clipping and the output wave shape, as shown in the lower sketch. The output voltage results from the current flow through the load resistor R.

In the shunt-type diode clipper negative bias is applied to the plate so the diode is normally nonconducting. In this case the signal voltage

is fed through the series resistor R to the output circuit (which must have high impedance compared with the resistance of R). When the negative half of the signal voltage exceeds the bias voltage the diode conducts, and because of the voltage drop in R when current flows the output voltage is reduced. By proper choice of R in relationship to the load on the output circuit the clipping can be made equivalent to that given by the series circuit. There is no clipping when the peak signal voltage is below the bias level.

Two diode circuits can be combined so that both negative and positive peaks are clipped.

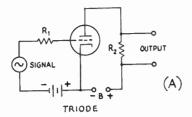


Fig. 3-25—Triode clippers. A—Single triode, using shunt-type diode clipping in the grid circuit for the positive peak and plate-current cut-off clipping for the negative peak. B—Cathode-coupled clipper, using plate-current cut-off clipping for both positive and negative peaks.

R₂ OUTPUT V₁ V₂ (B) CATHODE - COUPLED

Triode Clippers

The circuit shown at A in Fig. 3-25 is capable of clipping both negative and positive signal peaks. On positive peaks its operation is similar to the shunt diode clipper, the clipping taking place when the positive peak of the signal voltage is large enough to drive the grid positive. The positive-clipped signal is amplified by the tube as a resistance-coupled amplifier. Negative peak clipping occurs when the negative peak of the signal voltage exceeds the fixed grid bias and thus cuts off the plate current in the output circuit.

In the cathode-coupled clipper shown at B in Fig. 3-25 V_1 is a cathode follower with its output circuit directly connected to the cathode of

 V_{2} , which is a grounded-grid amplifier. The tubes are biased by the voltage drop across R_1 , which carries the d.c. plate currents of both tubes. When the negative peak of the signal voltage exceeds the d.c. voltage across R1 clipping occurs in V_1 , and when the positive peak exceeds the same value of voltage V_2 's plate current is cut off. (The bias developed in R₁ tends to be constant because the plate current of one tube increases when the plate current of the other decreases.) Thus the circuit clips both positive and negative peaks. The clipping is symmetrical, providing the d.c. voltage drop in R₂ is small enough so that the operating conditions of the two tubes are substantially the same. For signal voltages below the clipping level the circuit operates as a normal amplifier with low distortion.

U.H.F. AND MICROWAVE TUBES

At ultrahigh frequencies, interelectrode capacitances and the inductance of internal leads determine the highest possible frequency to which a vacuum tube can be tuned. The tube usually will not oscillate up to this limit, however, because of dielectric losses, transit time and other effects. In low-frequency operation, the actual time of flight of electrons between the cathode and the anode is negligible in relation to the duration of the cycle. At 1000 kc., for example, transit time of 0.001 microsecond, which is typical of conventional tubes, is only 1/1000 cycle. But at 100 Mc., this same transit time represents 1/10 of a cycle, and a full cycle at 1000 Mc. These limiting factors establish about 3000 Mc. as the upper frequency limit for negative-grid tubes.

With most tubes of conventional design, the upper limit of useful operation is around 150 Mc. For higher frequencies tubes of special construction are required. About the only means available for reducing interelectrode capacitances is to reduce the physical size of the elements, which is practical only in tubes which do not have to handle appreciable power. However, it is possible to reduce the internal lead inductance very materially by minimizing the lead length and by using two or more leads in parallel from an electrode.

In some types the electrodes are provided with

up to five separate leads which may be connected in parallel externally. In double-lead types the plate and grid elements are supported by heavy single wires which run entirely through the envelope, providing terminals at either end of the

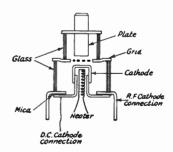


Fig. 3-26—Sectional view of the "lighthouse" tube's construction. Close electrode spacing reduces transit time while the disk electrode connections reduce lead inductance.

bulb. With linear tank circuits the leads become a part of the line and have distributed rather than lumped constants.

In "lighthouse" tubes or disk-seal tubes, the plate, grid and cathode are assembled in parallel planes, as shown in Fig. 3-26, instead of co-

U.H.F. and Microwave Tubes

axially. The disk-seal terminals practically eliminate lead inductance.

Velocity Modulation

In conventional tube operation the potential on the grid tends to reduce the electron velocity during the more negative half of the cycle, while on the other half cycle the positive potential on the grid serves to accelerate the electrons. Thus the electrons tend to separate into groups, those leaving the cathode during the negative halfcycle being collectively slowed down, while those leaving on the positive half are accelerated. After passing into the grid-plate space only a part of the electron stream follows the original form of the oscillation cycle, the remainder traveling to the plate at differing velocities. Since these contribute nothing to the power output at the operating frequency, the efficiency is reduced in direct proportion to the variation in velocity, the output reaching a value of zero when the transit time approaches a half-cycle.

This effect is turned to advantage in velocity-modulated tubes in that the input signal voltage on the grid is used to change the velocity of the electrons in a constant-current electron beam, rather than to vary the intensity of a constant-velocity current flow as is the method in ordinary tubes.

The velocity modulation principle may be used in a number of ways, leading to several tube designs. The major tube of this type is the "klystron."

The Klystron

In the klystron tube the electrons emitted by the cathode pass through an electric field established by two grids in a cavity resonator called the buncher. the high-frequency electric field between the grids is parallel to the electron stream.

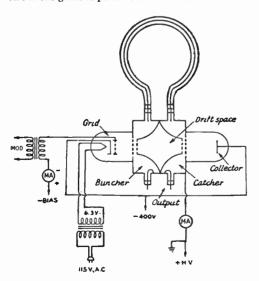


Fig. 3-27—Circuit diagram of the klystron oscillator, showing the feedback loop coupling the frequency-controlling cavities.

This field accelerates the electrons at one moment and retards them at another, in accordance with the variations of the r.f. voltage applied. The resulting velocity-modulated beam travels through a field-free "drift space," where the slower-moving electrons are gradually overtaken by the faster ones. The electrons emerging from the pair of grids therefore are separated into groups or "bunched" along the direction of motion. The velocity-modulated electron stream then goes to a catcher cavity where it again passes through two parallel grids, and the r.f. current created by the bunching of the electron beam induces an r.f. voltage between the grids. The catcher cavity is made resonant at the frequency of the velocity-modulated electron beam, so that an oscillating field is set up within it by the passage of the electron bunches through the grid aperture.

If a feedback loop is provided between the two cavities, as shown in Fig. 3-27, oscillations will occur. The resonant frequency depends on the electrode voltages and on the shape of the cavities, and may be adjusted by varying the supply voltage and altering the dimensions of the cavities. Although the bunched beam current is rich in harmonics the output wave form is remarkable pure because the high Q of the catcher cavity suppresses the unwanted harmonics.¹

Magnetrons

A magnetron is fundamentally a diode with cylindrical electrodes placed in a uniform magnetic field, with the lines of magnetic force parallel to the axes of the elements. The simple cy-

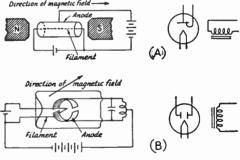


Fig. 3-28—Conventional magnetrons, with equivalent schematic symbols at the right. A, simple cylindrical magnetron. B, split-anode negative-resistance magnetron.


lindrical magnetron consists of a cathode surrounded by a concentric cylindrical anode. In the more efficient split-anode magnetron the cylinder is divided lengthwise.

Magnetron oscillators are operated in two

¹ A discussion of the operation of a three-cavity transmitting klystron operating above 1000 Mc. will be found in QST for August, 1961 (Badger, "An Introduction to the Klystron."). Practical Information on klystron operation will be found in QST for August, 1960 (Prechtel, "An Experimental Transceiver for 5660 Mc.") and May, 1959 (Sharbaugh and Watters, "The World Above 20,000 Mc.").

different ways. Electrically the circuits are similar, the difference being in the relation between electron transit time and the frequency of oscillation.

In the negative-resistance or dynatron type of magnetron oscillator, the element dimensions and anode voltage are such that the transit time is short compared with the period of the oscillation frequency. Electrons emitted from the cathode are driven toward both halves of the anode. If the potentials of the two halves are unequal, the effect of the magnetic field is such that the majority of the electrons travel to the half of the anode that is at the lower potential. That is, a decrease in the potential of either half of the anode results in an increase in the electron current flowing to that half. The magnetron consequently exhibits negative-resistance characteristics. Negative-resistance magnetron oscillators are useful between 100 and 1000 Mc. Under the

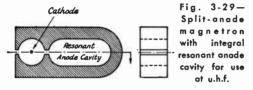

best operating conditions efficiencies of 20 to 25 per cent may be obtained.

In the transit-time magnetron the frequency is determined primarily by the tube dimensions and by the electric and magnetic field intensities rather than by the tuning of the tank circuits. The intensity of the magnetic field is adjusted so that, under static conditions, electrons leaving the cathode move in curved paths which just fail to reach the anode. All electrons are therefore deflected back to the cathode, and the anode current is zero. An alternating voltage applied between the two halves of the anode will cause the potentials of these halves to vary about their

it. Meanwhile other electrons gain energy from the field and are returned to the cathode. Since those electrons that lose energy remain in the interelectrode space longer than those that gain energy, the net effect is a transfer of energy from the electrons to the electric field. This energy can be used to sustain oscillations in a resonant transmission line connected between the two halves of the anode.

Split-anode magnetrons for u.h.f. are constructed with a cavity resonator built into the tube structure, as illustrated in Fig. 3-29. The assembly is a solid block of copper which assists in heat dissipation. At extremely high frequencies operation is improved by subdividing the anode structure into 4 to 16 or more segments, the resonant cavities for each anode being coupled to the common cathode region by slots of critical dimensions.


The efficiency of multisegment magnetrons reaches 65 or 70 per cent. Slotted-anode magnetrons with four segments function up to 30,000 Mc. (1 cm.), delivering up to 100 watts at efficiencies greater than 50 per cent. Using larger multiples of anodes and higher-order modes, performance can be attained at 0.2 cm.

Traveling-Wave Tubes

Gains as high as 23 db. over a bandwidth of 800 Mc. at a center frequency of 3600 Mc. have been obtained through the use of a traveling-wave amplifier tube shown schematically in Fig. 3-30. An electromagnetic wave travels down the helix, and an electron beam is shot through the helix parallel to its axis, and in the direction of propagation of the wave. When the electron velocity is about the same as the wave velocity in the absence of the electrons, turning on the electron beam causes a power gain for wave propagation in the direction of the electron motion.

The portions of Fig. 3-30 marked "input" and "output" are waveguide sections to which the

Fig. 3-30—Schematic drawing af a traveling-wave amplifier tube.

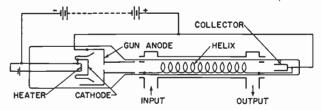

average positive values. If the period (time required for one cycle) of the alternating voltage is made equal to the time required for an electron to make one complete rotation in the magnetic field, the a.c. component of the anode voltage reverses direction twice with each electron rotation. Some electrons will lose energy to the electric field, with the result that they are unable to reach the cathode and continue to rotate about

ends of the helix are coupled. In practice two electromagnetic focusing coils are used, one forming a lens at the electron gun end, and the other a solenoid running the length of the helix.

The outstanding features of the traveling-wave amplifier tube are its great bandwidth and large power gain. However, the efficiency is rather low. Typical power output is of the order of 200 milliwatts.

Semiconductor Devices

Certain materials whose resistivity is not high enough to classify them as good insulators, but is still high compared with the resistivity of common metals, are known as semiconductors. These materials, of which germanium and silicon are examples, have an atomic structure that normally is associated with insulators. However, when small amounts of impurities are introduced during the manufacture of germanium or silicon crystals, it is possible for free electrons to exist and to move through the crystals under the influence of an electric field. It is also possible for some of the atoms to be deficient in an electron, and these electron deficiencies or holes can move from atom to atom when urged to do so by an applied electric force. (The movement of a hole is actually the movement of an electron, the electron becoming detached from one atom, making a hole in that atom, in order to move into an existing hole in another atom.) The holes can be considered to be equivalent to particles carrying a positive electric charge, while the electrons of course have negative charges. Holes and electrons are called charge carriers in semiconductors.

Electron and Hole Conduction

Material which conducts by virtue of a deficiency in electrons — that is, by hole conduction - is called p-type material. In n-type material, which has an excess of electrons, the conduction is termed "electronic." If a piece of ptype material is joined to a piece of n-type material as at A in Fig. 4-1 and a voltage is applied to the pair as at B, current will flow across the boundary or junction between the two (and also in the external circuit) when the battery has the polarity indicated. Electrons, indicated by the minus symbol, are attracted across the junction from the n material through the p material to the positive terminal of the battery, and holes, indicated by the plus symbol, are attracted in the opposite direction across the junction by the negative potential of the battery. Thus current flows through the circuit by means of electrons moving one way and holes the other.

If the battery polarity is reversed, as at C, the excess electrons in the n material are attracted away from the junction and the holes in the p material are attracted by the negative potential of the battery away from the junction. This leaves the junction region without any current carriers, consequently there is no conduction.

In other words, a junction of p- and n-type materials constitutes a rectifier. It differs from the tube diode rectifier in that there is a measurable, although comparatively very small, reverse current. The reverse current results from the presence of some carriers of the type opposite to those which principally characterize the material. The principal ones are called majority carriers, while the lesser ones are minority carriers.

The process by which the carriers cross the junction is essentially diffusion, and takes place comparatively slowly. This, together with the fact that the junction forms a capacitor with the two plates separated by practically zero spacing and hence has relatively high capacitance, places a limit on the upper frequency at which semiconductor devices of this construction will operate, as compared with vacuum tubes. Also, the number of excess electrons and holes in the material depends upon temperature, and since the conductivity in turn depends on the number of excess holes and electrons, the device is more temperature sensitive than is a vacuum tube.

Capacitance may be reduced by making the contact area very small. This is done by means of a point contact, a tiny p-type region being formed under the contact point during manufacture when n-type material is used for the main body of the device.

SEMICONDUCTOR DIODES

Diodes of the point-contact type are used for many of the same purposes for which tube diodes

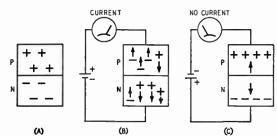


Fig. 4-1—A p-n junction (A) and its behavior when conducting (B) and non-conducting (C).

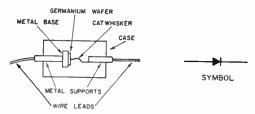


Fig. 4-2—Construction of a germanium-point-contact diode. In the circuit symbol for a contact rectifier the arrow points in the direction of minimum resistance measured by the conventional method—that is, going from the positive terminal of the voltage source through the rectifier to the negative terminal of the source. The arrow thus corresponds to the plate and the bar to the cathode of a tube diode.

are used. The construction of such a diode is shown in Fig. 4-2. Germanium and silicon are the most widely used materials, the latter principally in the u.h.f. region.

As compared with the tube diode for r.f. applications, the crystal diode has the advantages of very small size, very low interelectrode capacitance (of the order of 1 $\mu\mu$ f. or less) and requires no heater or filament power.

Characteristic Curves

The germanium crystal diode is characterized by relatively large current flow with small applied voltages in the "forward" direction, and small, although finite, current flow in the reverse or "back" direction for much larger applied voltages. A typical characteristic curve is shown in Fig. 4-3. The dynamic resistance in either the forward or back direction is determined by the change in current that occurs, at any given point on the curve, when the applied voltage is changed by a small amount. The forward resistance shows some variation in the region of very small applied voltages, but the curve is for the most part quite straight, indicating fairly constant dynamic resistance. For small applied voltages, the forward resistance is of the order of 200 ohms in most such diodes. The back resistance shows considerable variation, depending on the particular voltage chosen for the measurement. It may run from a few hundred thousand ohms to over a megohm. In applications such as meter rectifiers for r.f. indicating instruments (r.f. voltmeters, wavemeter indicators, and so on) where the load resistance may be small and the applied voltage of the order of several volts, the resistance vary with the value of the applied voltage and are considerably lower.

Junction Diodes

Junction-type diodes made of germanium or silicon are employed principally as power rectifiers, in applications similar to those where selenium rectifiers are used. Depending on the design of the particular diode, they are capable of rectifying currents up to several hundred milliamperes. The safe inverse peak voltage of a junction is relatively low, so an appropriate


SEMICONDUCTOR DEVICES

number of rectifiers must be connected in series to operate safely on a given a.c. input voltage.

Ratings

Crystal diodes are rated primarily in terms of maximum safe inverse voltage and maximum average rectified current. Inverse voltage is a voltage applied in the direction opposite to that which causes maximum current flow. The average current is that which would be read by a d.c. meter connected in the current path.

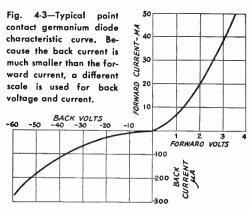It is also customary to specify standards of performance with respect to forward and back current. A minimum value of forward current is usually specified for one volt applied. The voltage at which the maximum tolerable back current is specified varies with the type of diode.



Zener Diodes

The "zener diode" is a special type of silicon junction diode that has a characteristic similar to that shown in Fig. 4-4. The sharp break from non-conductance to conductance is called the Zener Knee; at applied voltages greater than this

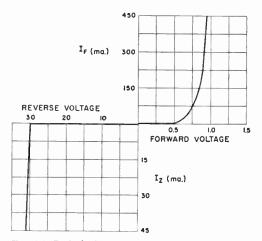


Fig. 4-4—Typical characteristic of a zener diode. In this example, the voltage drop is substantially constant at 30 volts in the (normally) reverse direction. Compare with Fig. 4-3. A diode with this characteristic would be called a "30-volt zener diode."

Transistors 81

breakdown point, the voltage drop across the diode is essentially constant over a wide range of currents. The substantially constant voltage drop over a wide range of currents allows this semiconductor device to be used as a constant voltage reference or control element, in a manner somewhat similar to the gaseous voltage-regulator tube. Voltages for zener diode action range from a few volts to several hundred and power ratings run from a fraction of a watt to 50 watts.

Zener diodes can be connected in series to advantage; the temperature coefficient is improved over that of a single diode of equivalent rating and the power-handling capability is increased.

Two zener diodes connected in opposition, Fig. 4-5, form a simple and highly effective clipper.

Voltage-Variable Capacitors

Voltage-variable capacitors are p-n junction diodes that behave as capacitors of reasonable Q (35 or more) up to 50 Mc. and higher. They are useful in many applications because the actual capacitance value is dependent upon the d.c. bias voltage that is applied. In a typical capacitor the capacitance can be varied over a 10-to-1 range with a bias change from 0 to -100 volts. The current demand on the bias supply is on the order of a few microamperes.

Typical applications include remote control of tuned circuits, automatic frequency control of

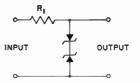


Fig. 4-5—Full-wave clipping action with two zener diodes in opposition. The output level would be at a peak-to-peak voltage of twice the zener rating of a single diode. R₁ should have a resistance value sufficient to limit the current to the zener diode rating.

receiver local oscillators, and simple frequency modulators for communications and for sweeptuning applications.

Tunnel Diode

Much hope is held for the future use of the "tunnel diode," a junction semiconductor of special construction that has a "negative resistance" characteristic at low voltages. This characteristic (decrease of current with increase of voltage) permits the diode to be used as an oscillator and as an amplifier. Since electrical charges move through the diode with the speed of light, in contrast to the relatively slow motion of electrical charge carriers in other semiconductors, it has been possible to obtain oscillations at 2000 Mc. and higher.

TRANSISTORS

Fig. 4-6 shows a "sandwich" made from two layers of p-type semiconductor material with a thin layer of n-type between. There are in effect two p-n junction diodes back to back. If a positive bias is applied to the p-type material at the left, current will flow through the left-hand junction, the holes moving to the right and the electrons from the n-type material moving to the left. Some of the holes moving into the n-type material will combine with the electrons there and be neutralized, but some of them also will travel to the region of the right-hand junction.

If the p-n combination at the right is biased negatively, as shown, there would normally be no current flow in this circuit (see Fig. 4-1C). However, there are now additional holes available at the junction to travel to point B and electrons can travel toward point A, so a current

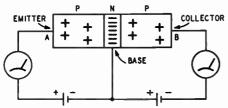


Fig. 4-6—The basic arrangement of a transistor. This represents a junction-type p-n-p unit.

can flow even though this section of the sandwich considered alone is biased to prevent conduction. Most of the current is between A and B and does not flow out through the common connection to the n-type material in the sandwich.


A semiconductor combination of this type is called a **transistor**, and the three sections are known as the **emitter**, base and collector, respectively. The amplitude of the collector current depends principally upon the amplitude of the emitter current; that is, the collector current is controlled by the emitter current.

Power Amplification

Because the collector is biased in the back direction the collector-to-base resistance is high. On the other hand, the emitter and collector currents are substantially equal, so the power in the collector circuit is larger than the power in the emitter circuit $(P = I^2 R)$, so the powers are proportional to the respective resistances, if the currents are the same). In practical transistors emitter resistance is of the order of a few hundred ohms while the collector resistance is hundreds or thousands of times higher, so power gains of 20 to 40 db. or even more are possible.

Types

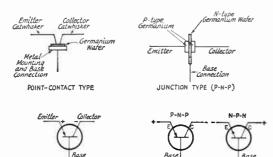The transistor may be one of the several types shown in Fig. 4-7. The assembly of p- and n-type materials may be reversed, so that p-n-p and n-p-n transistors are both possible,



N- type Germanı**um Wafer** Fig. 4-7—Point-contact. Plated Indium lated Induum Dot junction-type and surface-barrier types of Emitte. transistors with their Base Connection circuit symbols. The plus and minus signs SURFACE BARRIER TYPE associated with the symbols indicate polarities of voltages, with respect to the

base, to be applied to the elements.

SEMICONDUCTOR DEVICES

Point-Contact Transistors

SYMBOLS

SYMBOL

The point-contact transistor, shown at the left in Fig. 4-7, has two "cat whiskers" placed very close together on the surface of a germanium wafer. It is principally of historical interest and is now superseded by the junction type. It is difficult to manufacture, since the two contact points must be extremely close together if good high-frequency characteristics are to be secured.

Junction Transistors

The junction transistor, shown at the center in Fig. 4-7, has higher capacitances and higher power-handling capacity than the point-contact type. The "electrode" areas and thickness of the intermediate layer have an important effect on the upper frequency limit. Ordinary junction transistors may have cut-off frequencies (see next section) up to 50 Mc. or so. The types used for audio and low-radio frequencies usually have cut-off frequencies ranging from 500 to 1000 kc.

The upper frequency limit is extended considerably in the drift transistor. This type has a particular form of distribution of impurities in the base material resulting in the creation of an internal electric field that accelerates the carriers across the junction. Typical drift transistors have cut-off frequencies of the order of 100 Mc.

Another type of transistor useful in high-frequency work is the surface barrier transistor, using plated emitter and collector electrodes on a wafer of n-type material, as shown at the right in Fig. 4-7. Surface-barrier transistors will operate as amplifiers and oscillators at frequencies of 250 Mc. or higher.

TRANSISTOR CHARACTERISTICS

An important characteristic of a transistor is its current amplification factor, usually designated by the symbol α . This is the ratio of the change in collector current to a small change in emitter current, measured in the common-base circuit described later, and is comparable with the voltage amplification factor (μ) of a vacuum tube. The current amplification factor is almost, but not quite, 1 in a junction transistor. It is larger than 1 in the point-contact type, values in the neighborhood of 2 being typical.

The a cut-off frequency is the frequency at

which the current amplification drops 3 db. below its low-frequency value. Cut-off frequencies range from 500 kc, to frequencies in the v.h.f. region. The cut-off frequency indicates in a general way the frequency spread over which the transistor is useful.

SYMBOL

Each of the three elements in the transistor has a resistance associated with it. The emitter and collector resistances were discussed earlier. There is also a certain amount of resistance associated with the base, a value of a few hundred to 1000 ohms being typical of the base resistance.

The values of all three resistances vary with the type of transistor and the operating voltages. The collector resistance, in particular, is sensitive to operating conditions.

Characteristic Curves

The operating characteristics of transistors can be shown by a series of characteristic curves. One such set of curves is shown in Fig. 4-8. It


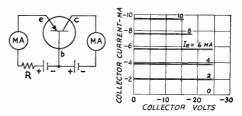


Fig. 4-8—A typical collector-current vs. collector-voltage characteristic of a junction-type transistor, for various emitter-current values. The circuit shows the setup for taking such measurements. Since the emitter resistance is low, a current-limiting resistor, R, is connected in series with the source of current. The emitter current can be set at a desired value by adjustment of this resistance.

shows the collector current vs. collector voltage for a number of fixed values of emitter current. Practically, the collector current depends almost entirely on the emitter current and is independent of the collector voltage. The separation between curves representing equal steps of emitter current is quite uniform, indicating that almost distortionless output can be obtained over the useful operating range of the transistor.

Another type of curve is shown in Fig. 4-9, together with the circuit used for obtaining it. This also shows collector current vs. collector

voltage, but for a number of different values of base current. In this case the emitter element is used as the common point in the circuit. The collector current is not independent of collector voltage with this type of connection, indicating that the output resistance of the device is fairly

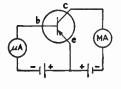

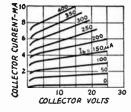


Fig. 4-9—Collector current vs. collector voltage for various volues of base current, for a junction-type transistor.

The values are determined by means of the circuit shown.

low. The base current also is quite low, which means that the resistance of the base-emitter circuit is moderately high with this method of connection. This may be contrasted with the high values of emitter current shown in Fig. 4-8.

Ratings

The principal ratings applied to transistors are maximum collector dissipation, maximum collector voltage, maximum collector current, and maximum emitter current. The voltage and current ratings are self-explanatory.

The collector dissipation is the power, usually expressed in milliwatts, that can safely be dissipated by the transistor as heat. With some types of transistors provision is made for transferring heat rapidly through the container, and such units usually require installation on a heat "sink," or mounting that can absorb heat.

The amount of undistorted output power that can be obtained depends on the collector voltage, the collector current being practically independent of the voltage in a given transistor. Increasing the collector voltage extends the range of linear operation, but must not be carried beyond the point where either the voltage or dissipation ratings are exceeded.

TRANSISTOR AMPLIFIERS

Amplifier circuits used with transistors fall into one of three types, known as the grounded-base, grounded-emitter, and grounded-collector circuits. These are shown in Fig. 4-10 in elementary form. The three circuits correspond approximately to the grounded-grid, grounded-cathode and cathode-follower circuits, respectively, used with vacuum tubes.

The important transistor parameters in these circuits are the short-circuit current transfer ratio, the cut-off frequency, and the input and output impedances. The short-circuit current transfer ratio is the ratio of a small change in output current to the change in input current that causes it, the output circuit being short-circuited. The cut-off frequency is the frequency

at which the amplification decreases by 3 db. from its value at some frequency well below that at which frequency effects begin to assume importance. The input and output impedances are, respectively, the impedance which a signal source working into the transistor would see, and the internal output impedance of the transistor (corresponding to the plate resistance of a vacuum tube, for example).

Grounded-Base Circuit

The input circuit of a grounded-base amplifier must be designed for low impedance, since the emitter-to-base resistance is of the order of $25/I_{\bullet}$ ohms, where I_{\bullet} is the emitter current in milliamperes. The optimum output load impedance, $R_{\rm L}$, may range from a few thousand ohms to 100,000, depending upon the requirements.

The current transfer ratio is a and the cut-off frequency is as defined previously.

In this circuit the phase of the output (collector) current is the same as that of the input (emitter) current. The parts of these currents that flow through the base resistance are likewise in phase, so the circuit tends to be regenerative and will oscillate if the current amplification factor is greater than 1. A junction transistor is stable in this circuit since α is less than 1, but a point-contact transistor will oscillate.

Grounded-Emitter Circuit

The grounded-emitter circuit shown in Fig. 4-10 corresponds to the ordinary grounded-cathode vacuum-tube amplifier. As indicated by the curves of Fig. 4-9, the base current is small and the input impedance is therefore fairly high—several thousand ohms in the average case. The collector resistance is some tens of thousands of ohms, depending on the signal source impedance. The current transfer ratio in the common-emitter circuit is equal to

$$\frac{a}{1-a}$$

Since α is close to 1 (0.98 or higher being representative), the short-circuit current gain in the grounded-emitter circuit may be 50 or more. The cut-off frequency is equal to the α cut-off frequency multiplied by $(1 - \alpha)$, and therefore is relatively low. (For example a transistor with an α cut-off of 1000 kc. and $\alpha = 0.98$ would have a cut-off frequency of $1000 \times 0.02 = 20$ kc. in the grounded-emitter circuit.)

Within its frequency limitations, the groundedemitter circuit gives the highest power gain of the three.

In this circuit the phase of the output (collector) current is opposite to that of the input (base) current so such feedback as occurs through the small emitter resistance is negative and the amplifier is stable with either junction or point-contact transistors.

Grounded-Collector Circuit

Like the vacuum-tube cathode follower, the grounded-collector transistor amplifier has high

SEMICONDUCTOR DEVICES

input impedance and low output impedance. The latter is approximately equal to the impedance of the signal input source multiplied by $(1-\alpha)$. The input resistance depends on the load resistance, being approximately equal to the load resistance divided by $(1-\alpha)$. The fact that input resistance is directly related to the load resistance is a disadvantage of this type of amplifier if the load is one whose resistance or impedance varies with frequency.


The current transfer ratio with this circuit is

$$\frac{1}{1-\alpha}$$

and the cut-off frequency is the same as in the grounded-emitter circuit. The output and input currents are in phase.

Practical Circuit Details

The transistor is essentially a low-voltage device, so the use of a battery power supply rather than a rectified-a.c. supply is quite common. Usually, it is more convenient to employ a single battery as a power source in preference to the two-battery arrangements shown in Fig. 4-10, so most circuits are designed for single-battery operation. Provision must be included, therefore, for obtaining proper biasing voltage for the emitter-base circuit from the battery that supplies the power in the collector circuit.

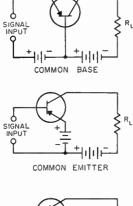

or by resistance-capacitance coupling. In any case it is to be understood that a d.c. path must exist between the base and emitter.

P-n-p transistors are shown in these circuits. If n-p-n types are used the battery polarities

must be reversed.

Fig. 4-10-Basic tran-

sistor amplifier circuits.

RL, the load resist-

ance, may be an ac-

tual resistor or the pri-

mary of a transformer.

The input signal may


be supplied from a

transformer secondary

COMMON COLLECTOR

SIGNAL

Coupling arrangements for introducing the input signal into the circuit and for taking out the amplified signal are similar to those used with vacuum tubes. However, the actual component values will in general be quite different from those used with tubes. This is because the impedances associated with the input and output circuits of transistors may differ widely from the comparable impedances in tube circuits. Also, d.c. voltage drops in resistances may require more

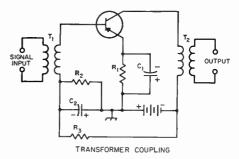

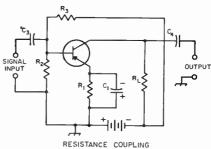


Fig. 4-11—Practical grounded-emitter circuits using transformer and resistance coupling. A combination of either also can be used—e.g., resistance-coupled input and transformer-coupled output. Tuned transformers may be used for r.f. and i.f. circuits.

With small transistors used for low-level amplification the input impedance will be of the order of 1000 ohms and the input circuit should be designed for an impedance step-down, if necessary. This can be done by appropriate choice of turns ratio for T_1 or, in the case of tuned circuits, by tapping the base down on the tuned secondary circuit. In the resistance-coupled circuit R_2 should be large compared with the input impedance, values of the order of 10,000 ohms being used.

In low-level circuits R_1 will be of the order of 1000 ohms. R_3 should be chosen to bias the transistor to the desired no-signal collector current; its value depends on R_1 and R_2 (see text).

careful attention with transistors because of the much lower voltage available from the ordinary battery power source. Battery economy becomes an important factor in circuit design, both with respect to voltage required and to overall current drain. A bias voltage divider, for example, easily may use more power than the transistor with which it is associated.

Typical single-battery grounded-emitter circuits are shown in Fig. 4-11. R_1 , in series with the emitter, is for the purpose of "swamping out" the resistance of the emitter-base diode; this swamping helps to stabilize the emitter current. The resistance of R_1 should be large compared with that of the emitter-base diode, which, as stated earlier, is approximately equal to 25 divided by the emitter current in ma.

Since the current in R_1 flows in such a direction as to bias the emitter negatively with respect to the base (a p-n-p transistor is assumed), a base-emitter bias slightly greater than the drop in R_1 must be supplied. The proper operating point is

Transistor Circuits

achieved through adjustment of voltage divider R_2R_3 , which is proportioned to give the desired value of no-signal collector current.

In the transformer-coupled circuit, input signal currents flow through R1 and R2, and there would be a loss of signal power at the base-emitter diode if these resistors were not bypassed by C1 and C2. The capacitors should have low reactance compared with the resistances across which they are connected. In the resistance-coupled circuit R2 serves as part of the bias voltage divider and also as part of the load for the signalinput source. As seen by the signal source, Rs is in parallel with R2 and thus becomes part of the input load resistance. C. must have low reactance compared with the parallel combination of R2, R8 and the base-to-emitter resistance of the transistor. The load impedance will determine the reactance of C_4 .

The output load resistance in the transformer-coupled case will be the actual load as reflected at the primary of the transformer, and its proper value will be determined by the transistor characteristics and the type of operation (Class A, B, etc.). The value of $R_{\rm L}$ in the resistance-coupled case is usually such as to permit the maximum a.c. voltage swing in the collector circuit without undue distortion, since Class A operation is usual with this type of amplifier.

Bias Stabilization

Transistor currents are sensitive to temperature variations, and so the operating point tends to shift as the transistor heats. The shift in operating point is in such a direction as to increase the heating, leading to "thermal runaway" and possible destruction of the transistor. The heat developed depends on the amount of power dissipated in the transistor, so it is obviously advantageous in this respect to operate with as little internal dissipation as possible: i.e., the d.c. input should be kept to the lowest value that will permit the type of operation desired and should never exceed the rated value for the particular transistor used.

A contributing factor to the shift in operating point is the collector-to-base leakage current (usually designated I_{co}) — that is, the current that flows from collector to base with the emitter connection open. This current, which is highly temperature sensitive, has the effect of increasing the emitter current by an amount much larger than I_{co} itself, thus shifting the operating point in such a way as to increase the collector current. This effect is reduced to the extent that I_{co} can be made to flow out of the base terminal rather than through the base-emitter diode. In the circuits of Fig. 4-11, bias stabilization is improved by making the resistance of R_1 as large as possible and both R2 and R3 as small as possible, consistent with gain and battery economy.

TRANSISTOR OSCILLATORS

Since more power is available from the output circuit than is necessary for its generation in the input circuit, it is possible to use some of the output power to supply the input circuit and thus

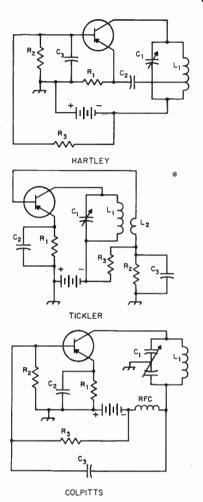


Fig. 4-12—Typical transistor oscillator circuits. Component values are discussed in the text.

sustain self-oscillation. Representative oscillator circuits are shown in Fig. 4-12.

The upper frequency limit for oscillation is principally a function of the cut-off frequency of the transistor used, and oscillation will cease at the frequency at which there is insufficient amplification to supply the energy required to overcome circuit losses. Transistor oscillators usually will operate up to, and sometimes well beyond, the α cut-off frequency of the particular transistor used.

The approximate oscillation frequency is that of the tuned circuit, L_1C_1 . R_1 , R_2 and R_3 have the same functions as in the amplifier circuits given in Fig. 4-11. Bypass capacitors C_2 and C_3 should have low reactances compared with the resistances with which they are associated.

Feedback in these circuits is adjusted in the same way as with tube oscillators: position of the tap on L_1 in the Hartley, turns and coupling of L_2 in the tickler circuit, and ratio of the sections of C_1 in the Colpitts.

High-Frequency Receivers

A good receiver in the amateur station makes the difference between mediocre contacts and solid QSOs, and its importance cannot be overemphasized. In the less crowded v.h.f. bands, sensitivity (the ability to bring in weak signals) is the most important factor in a receiver. In the more crowded amateur bands, good sensitivity must be combined with selectivity (the ability to distinguish between signals separated by only a small frequency difference). To receive weak signals, the receiver must furnish enough amplification to amplify the minute signal power delivered by the antenna up to a useful amount of power that will operate a loudspeaker or set of headphones. Before the amplified signal can operate the speaker or phones, it must be converted to audio-frequency power by the process of detection. The sequence of amplification is not too important-some of the amplification can take place (and usually does) before detection, and some can be used after detection.

There are major differences between receivers for phone reception and for code reception. An a.m. phone signal has sidebands that make the signal take up about 6 or 8 kc. in the band, and the audio quality of the received signal is impaired if the bandwidth is less than half of this. A code signal occupies only a few hundred cycles at the most, and consequently the bandwidth of a code receiver can be small. A single-sideband phone signal takes up 3 to 4 kc., and the audio quality can be impaired if the bandwidth is much less than 3 kc. although the intelligibility will hold up down to around 2 kc. In any case, if the bandwidth of the receiver is more than nec-

essary, signals adjacent to the desired one can be heard, and the selectivity of the receiver is less than maximum. The detection process delivers directly the audio frequencies present as modulation on an a.m. phone signal. There is no modulation on a code signal, and it is necessary to introduce a second radio frequency, differing from the signal frequency by a suitable audio frequency, into the detector circuit to produce an audible beat. The frequency difference, and hence the beat note, is generally made on the order of 500 to 1000 cycles, since these tones are within the range of optimum response of both the ear and the headset. There is no carrier frequency present in an s.s.b. signal, and this frequency must be furnished at the receiver before the audio can be recovered. The same source that is used in code reception can be utilized for the purpose. If the source of the locally generated radio frequency is a separate oscillator, the system is known as heterodyne reception; if the detector is made to oscillate and produce the frequency, it is known as an autodyne detector. Modern superheterodyne receivers generally use a separate oscillator (beat oscillator) to supply the locally generated frequency. Summing up the differences, phone receivers can't use as much selectivity as code receivers, and code and s.s.b. receivers require some kind of locally generated frequency to give a readable signal. Broadcast receivers can receive only a.m. phone signals because no beat oscillator is included. Communications receivers include beat oscillators and often some means for varying the selectivity. With high selectivity they often have a slow tuning rate.

RECEIVER CHARACTERISTICS

Sensitivity

In commercial circles "sensitivity" is defined as the strength of the signal (in microvolts) at the input of the receiver that is required to produce a specified audio power output at the speaker or headphones. This is a satisfactory definition for broadcast and communications receivers operating below about 20 Mc., where atmospheric and man-made electrical noises normally mask any noise generated by the receiver itself.

Another commercial measure of sensitivity defines it as the signal at the input of the receiver required to give a signal-plus-noise output some stated ratio (generally 10 db.) above the noise output of the receiver. This is a more

useful sensitivity measure for the amateur, since it indicates how well a weak signal will be heard and is not merely a measure of the over-all amplification of the receiver. However, it is not an absolute method, because the bandwidth of the receiver plays a large part in the result.

The random motion of the molecules in the antenna and receiver circuits generates small voltages called **thermal-agitation noise** voltages. Thermal-agitation noise is independent of frequency and is proportional to the (absolute) temperature, the resistance component of the impedance across which the thermal agitation is produced, and the bandwidth. Noise is generated in vacuum tubes by random irregularities in the current flow within them; it is convenient to ex-

press this shot-effect noise as an equivalent resistance in the grid circuit of a noise-free tube. This equivalent noise resistance is the resistance (at room temperature) that placed in the grid circuit of a noise-free tube will produce platecircuit noise equal to that of the actual tube. The equivalent noise resistance of a vacuum tube increases with frequency.

An ideal receiver would generate no noise in its tubes and circuits, and the minimum detectable signal would be limited only by the thermal noise in the antenna. In a practical receiver, the limit is determined by how well the amplified antenna noise overrides the other noise in the plate circuit of the input stage. (It is assumed that the first stage in any good receiver will be the determining factor; the noise contributions of subsequent stages should be insignificant by comparison.) At frequencies below 20 or 30 Mc. the site noise (atmospheric and man-made noise) is generally the limiting factor.

The degree to which a practical receiver approaches the quiet ideal receiver of the same bandwidth is given by the noise figure of the receiver. Noise figure is defined as the ratio of the signal-to-noise power ratio of the ideal receiver to the signal-to-noise power ratio of the actual receiver output. Since the noise figure is a ratio, it is usually given in decibels; it runs around 5 to 10 db. for a good communications receiver below 30 Mc. Although noise figures of 2 to 4 db. can be obtained, they are of little or no use below 30 Mc. except in extremely quiet locations or when a very small antenna is used. The noise figure of a receiver is not modified by changes in bandwidth.

Selectivity

Selectivity is the ability of a receiver to discriminate against signals of frequencies differing from that of the desired signal. The over-all selectivity will depend upon the selectivity of the individual tuned circuits and the number of such circuits.

The selectivity of a receiver is shown graphically by drawing a curve that gives the ratio of signal strength required at various frequencies off resonance to the signal strength at resonance, to give constant output. A resonance curve of this type is shown in Fig. 5-1. The bandwidth is the width of the resonance curve (in cycles or kilocycles) of a receiver at a specified ratio: in the typical curve of Fig. 5-1 the bandwidths for response ratios of 2 and 1000 (described as "-6

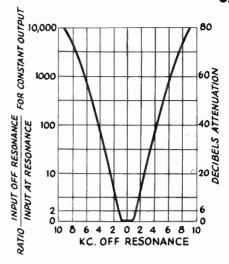


Fig. 5-1—Typical selectivity curve of a modern superheterodyne receiver. Relative response is plotted against deviations above and below the resonance frequency. The scale at the left is in terms of voltage ratios, the corresponding decibel steps are shown at the right.

db." and "-60 db.") are 2.4 and 12.2 kc. respectively.

The bandwidth at 6 db. down must be sufficient to pass the signal and its sidebands if faithful reproduction of the signal is desired. However, in the crowded amateur bands, it is generally advisable to sacrifice fidelity for intelligibility. The ability to reject adjacent-channel signals depends upon the skirt selectivity of the receiver, which is determined by the bandwidth at high attenuation. In a receiver with excellent skirt selectivity, the ratio of the 6-db. bandwidth to the 60-db, bandwidth will be about 0.25 for code and 0.5 for phone. The minimum usable bandwidth at 6 db. down is about 150 cycles for code reception and about 2000 cycles for phone.

Stability

The stability of a receiver is its ability to "stay put" on a signal under varying conditions of gaincontrol setting, temperature, supply-voltage changes and mechanical shock and distortion. The term "unstable" is also applied to a receiver that breaks into oscillation or a regenerative condition with some settings of its controls that are not specifically intended to control such a condition.

DETECTION AND DETECTORS

Detection is the process of recovering the modulation from a signal (see "Modulation, Heterodyning and Beats", page 58). Any device that is "nonlinear" (i.e., whose output is not exactly proportional to its input) will act as a detector. It can be used as a detector if an impedance for the desired modulation frequency is connected in the output circuit.

Detector sensitivity is the ratio of desired detector output to the input. Detector linearity is a measure of the ability of the detector to reproduce the exact form of the modulation on the incoming signal. The resistance or impedance of the detector is the resistance or impedance it presents to the circuits it is connected to. The input resistance is important in receiver design, since if it is relatively low it means that the detector will consume power, and this power must be furnished by the preceding stage. The signalhandling capability means the ability to accept signals of a specified amplitude without overloading or distortion.

Diode Detectors

The simplest detector for a.m. is the diode. A galena, silicon or germanium crystal is an imperfect form of diode (a small current can pass in the reverse direction), and the principle of detection in a crystal is similar to that in a vacuumtube diode.

Circuits for both half-wave and full-wave diodes are given in Fig. 5-2. The simplified halfwave circuit at 5-2A includes the r.f. tuned circuit, L_2C_1 , a coupling coil, L_1 , from which the r.f. energy is fed to L_2C_1 , and the diode, D,

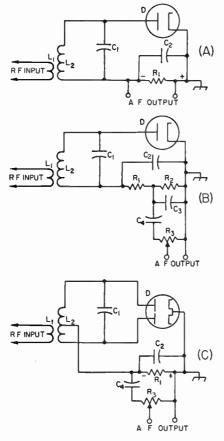


Fig. 5-2—Simplified and practical diode detector circuits. A, the elementary half-wave diode detector; B, a practical circuit, with r.f. filtering and audio output coupling; C, full-wave diode detector, with output coupling indicated. The circuit, L2C1, is tuned to the signal frequency; typical values for C2 and R1 in A and C are 250 $\mu\mu$ f. and 250,000 ohms, respectively; in B, C_2 and C_3 are 100 $\mu\mu$ f. each; R_1 , 50,000 ohms; and R_2 , 250,000 ohms. C₄ is 0.1 μ f. and R₈ may be 0.5 to 1 megohm.

HIGH-FREQUENCY RECEIVERS

with its load resistance, R₁, and bypass capacitor, C2. The flow of rectified r.f. current causes a d.c. voltage to develop across the terminals of R_1 . The — and + signs show the polarity of the voltage. The variation in amplitude of the r.f. signal with modulation causes corresponding variations in the value of the d.c. voltage across R_1 . In audio work the load resistor, R_1 , is usually 0.1 megohm or higher, so that a fairly large voltage will develop from a small rectifiedcurret flow.

The progress of the signal through the detctor or rectifier is shown in Fig. 5-3. A typical modulated signal as it exists in the tuned

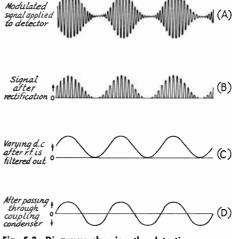


Fig. 5-3—Diagrams showing the detection process.

circuit is shown at A. When this signal is applied to the rectifier tube, current will flow only during the part of the r.f. cycle when the plate is positive with respect to the cathode, so that the output of the rectifier consists of half-cycles of r.f. These current pulses flow in the load circuit comprised of R_1 and C_2 , the resistance of R_1 and the capacity of C_2 being so proportioned that C2 charges to the peak value of the rectified voltage on each pulse and retains enough charge between pulses so that the voltage across R_1 is smoothed out, as shown in C. C2 thus acts as a filter for the radio-frequency component of the output of the rectifier, leaving a d.c. compoent that varies in the same way as the modulation on the original signal. When this varying d.c. voltage is applied to a following amplifier through a coupling capacitor (C_4 in Fig. 5-2), only the variations in voltage are transferred, so that the final output signal is a.c., as shown in D.

In the circuit at 5-2B, R₁ and C₂ have been divided for the purpose of providing a more effective filter for r.f. It is important to prevent the appearance of any r.f. voltage in the output of the detector, because it may cause overloading of a succeeding amplifier tube. The audiotrequency variations can be transferred to another circuit through a coupling eapacitor, C_4 , to a load resistor, R_8 , which usually is a

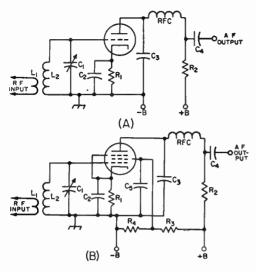


Fig. 5-4—Circuits for plate detection. A, triode; B, pentode. The input circuit, L_2C_1 , is tuned to the signal frequency. Typical values for the other components are:

ро	nent Circuit A	Circuit B
C ₂	0.5 μf. or larger.	0.5 μf. or larger.
Сз	0.001 to 0.002 μf.	250 to 500 μμf.
C4	0.1 μf.	0.1 μf.
Сб		0.5 μ f, or larger.
R ₁	25,000 to 150,000 ohms.	10,000 to 20,000 ohms.
R ₂	50,000 to 100,000 ohms.	100,000 to 250,000 ohms.
Rз		50,000 ohms.
R4		20,000 ohms.
RF	C 2.5 mh.	2.5 mh.

Plate voltages from 100 to 250 volts may be used. Effective screen voltage in B should be about 30 volts.

"potentiometer" so that the audio volume can be adjusted to a desired level.

Coupling to the potentiometer (volume control) through a capacitor also avoids any flow of d.c. through the control. The flow of d.c. through a high-resistance volume control often tends to make the control noisy (scratchy) after a short while.

The full-wave diode circuit at 5-2C differs in operation from the half-wave circuit only in that both halves of the r.f. cycle are utilized. The full-wave circuit has the advantage that r.f. filtering is easier than in the half-wave circuit. As a result, less attenuation of the higher audio frequencies will be obtained for any given degree of r.f. filtering.

The reactance of C_2 must be small compared to the resistance of R_1 at the radio frequency being rectified, but at audio frequencies must be relatively large compared to R_1 . If the capacity of C_2 is too large, response at the higher audio frequencies will be lowered.

Compared with other detectors, the sensitivity of the diode is low, normally running around 0.8 in audio work. Since the diode consumes power, the Q of the tuned circuit is reduced,

bringing about a reduction in selectivity. The loading effect of the diode is close to one-half the load resistance. The detector linearity is good, and the signal-handling capability is high.

Plate Detectors

The plate detector is arranged so that rectification of the r.f. signal takes place in the plate circuit of the tube. Sufficient negative bias is applied to the grid to bring the plate current nearly to the cut-off point, so that application of a signal to the grid circuit causes an increase in average plate current. The average plate current follows the changes in signal in a fashion similar to the rectified current in a diode detector.

Circuits for triodes and pentodes are given in Fig. 5-4. C_8 is the plate bypass capacitor, and, with RFC, prevents r.f. from appearing in the output. The cathode resistor, R_1 , provides the operating grid bias, and C_2 is a bypass for both radio an audio frequencies. R_2 is the plate load resistance and C_4 is the output coupling capacitor. In the pentode circuit at B, R_8 and R_4 form a voltage divider to supply the proper screen potential (about 30 volts), and C_6 is a bypass capacitor. C_2 and C_6 must have low reactance for both radio and audio frequencies.

In general, transformer coupling from the plate circuit of a plate detector is not satisfactory, because the plate impedance of any tube is very high when the bias is near the plate-curret cut-off point. Impedance coupling may be used in place of the resistance coupling shown in Fig. 5-4. Usually 100 henrys or more inductance is required.

The plate detector is more sensitive than the diode because there is some amplifying action in the tube. It will handle large signals, but is not so tolerant in this respect as the diode. Linearity, with the self-biased circuits, shown, is good. Up to the overload point the detector takes no power from the tuned circuit, and so does not affect its Q and selectivity.

Infinite-Impedance Detector

The circuit of Fig. 5-5 combines the high signal-handling capabilities of the diode detector

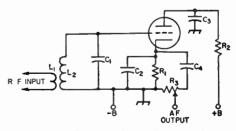


Fig. 5-5—The infinite-impedance detector. The input circuit, L_2C_1 , is tuned to the signal frequency. Typical values for the other components are:

 $\begin{array}{lll} {\rm C_2-250~\mu\mu f.} & {\rm R_1-0.15~megohm.} \\ {\rm C_3-0.5~\mu f.} & {\rm R_2-25,000~ohms.} \end{array}$

 C_4 -0.1 μ f. R₃-0.25-megohm volume control.

A tube having a medium amplification factor (about 20) should be used. Plate voltage should be 250 volts.

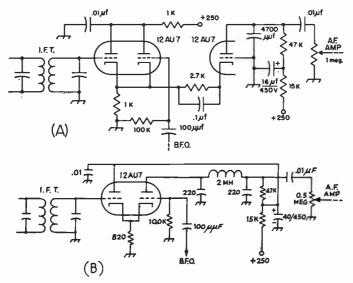


Fig. 5-6—Two versions of the "product detector" circuit. In the circuit at A separate tubes are used for the signal circuit cathode follower, the b.f.o. cathode follower and the mixer tube. In B the mixer and b.f.o. follower are combined in one tube, and a low-pass filter is used in the out-put.

with low distortion and, like the plate detector, does not load the tuned circuit it connects to. The circuit resembles that of the plate detector, except that the load resistance, R_1 , is connected between cathode and ground and thus is common to both grid and plate circuits, giving negative feedback for the audio frequencies. The cathode resistor is bypassed for r.f. but not for audio, while the plate circuit is bypassed to ground for both audio and radio frequencies. An r.f. filter can be connected between the cathode and C_4 to eliminate any r.f. that might otherwise appear in the output.

The plate current is very low at no signal, increasing with signal as in the case of the plate detector. The voltage drop across R_1 consequently increases with signal. Because of this and the large initial drop across R_1 , the grid usually cannot be driven positive by the signal, and no grid current can be drawn.

Product Detector

The product detector circuits of Fig. 5-6 are useful in s.s.b. and code reception because they minimize intermodulation at the detector. In Fig. 5-6A, two triodes are used as cathode followers, for the signal and for the b.f.o., working into a common cathode resistor (1000 ohms). The third triode also shares this cathode resistor and consequently the same signals, but it has an audio load in its plate circuit and it operates at a higher grid bias (by virtue of the 2700-ohm resistor in its cathode circuit). The signals and the b.f.o. mix in this third triode. If the b.f.o. is turned off, a modulated signal running through the signal cathode follower should yield little or no audio output from the detector, up to the overload point of the signal cathode follower. Turning on the b.f.o. brings in modulation, because now the detector output is the product of the two signals. The plates of the cathode followers are grounded and filtered for the i.f. and the 4700- $\mu\mu$ f. capacitor from plate to ground in the output triode furnishes a bypass at the i.f. The b.f.o. voltage should be about 2 r.m.s., and the signal should not exceed about 0.3 volts r.m.s.

The circuit in Fig. 5-6B is a simplification requiring one less triode. Its principle of operation is substantially the same except that the additional bias for the output tube is derived from rectified b.f.o. voltage across the 100,000-ohm resistor. More elaborate r.f. filtering is shown in the plate of the output tube (2-mh. choke and the $220-\mu\mu$ f. capacitors), and the degree of plate filtering in either circuit will depend upon the frequencies involved. At low intermediate frequencies, more elaborate filtering is required.


REGENERATIVE DETECTORS

By providing controllable r.f. feedback (regeneration) in a triode or pentode detector circuit, the incoming signal can be amplified many times, thereby greatly increasing the sensitivity of the detector. Regeneration also increases the effective $\mathcal Q$ of the circuit and thus the selectivity. The grid-leak type of detector is most suitable for the purpose.

The grid-leak detector is a combination diode rectifier and audio-frequency amplifier. In the circuit of Fig. 5-7A, the grid corresponds to the diode plate and the rectifying action is exactly the same as in a diode. The d.c. voltage from rectified-current flow through the grid leak, R_1 , biases the grid negatively, and the audio-frequency variations in voltage across R_1 are amplified through the tube as in a normal a.f. amplifier. In the plate circuit, R_2 is the plate load resistance and C_3 and RFC a filter to eliminate r.f. in the output circuit.

A grid-leak detector has considerably greater sensitivity than a diode. The sensitivity is further increased by using a screen-grid tube instead of a triode. The operation is equivalent to that of the triode circuit. The screen bypass capacitor should have low reactance for both radio and audio frequencies.

Regenerative Detectors

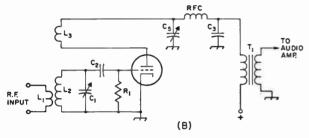

The circuit in Fig. 5-7B is regenerative, the feedback being obtained by feeding some signal from the plate circuit back to the grid by inductive coupling. The amount of regeneration must be controllable, because maximum regenerative amplification is secured at the critical point where the circuit is just about to oscillate. The critical point in turn depends upon circuit conditions, which may vary with the frequency to which the detector is tuned. An oscillating detector can be detuned slightly from an incoming c.w. signal to give autodyne reception.

The circuit of Fig. 5-7B uses a variable bypass capacitor, C_5 , in the plate circuit to control regeneration. When the capacitance is small the tube does not regenerate, but as it increases toward maximum its reactance becomes smaller until there is sufficient feedback to cause oscillation. If L_2 and L_3 are wound end-to-end in the same direction, the plate connection is to the outside of the plate or "tickler" coil, L_3 , when the grid connection is to the outside end of L_2 .

Although the regenerative grid-leak detector is more sensitive than any other type, its many disadvantages commend it for use only in the simplest receivers. The linearity is rather poor, and the signal-handling capability is limited. The signal-handling capability can be improved by reducing R_1 to 0.1 megohm, but the sensitivity will be decreased. The degree of antenna coupling is often critical.

Tuning

For c.w. reception, the regeneration control is advanced until the detector breaks into a "hiss," which indicates that the detector is oscillating. Further advancing the regeneration control will result in a slight decrease in the hiss.

The proper adjustment of the regeneration control for best reception of code signals is where the detector just starts to oscillate. Then code signals can be tuned in and will give a tone with each signal depending on the setting of the Fig. 5-7—(A) Triode grid-leak detector combines diode detection with triode amplification. Although shown here with resistive plate load, R_{2} , an audio choke coil or transformer could be used.

(B) Feeding some signal from the plate circuit back to the grid makes the circuit regenerative. When feedback is sufficient, the circuit will oscillate. Feedback is controlled here by varying reactance at C_{6j} with fixed capacitor at that point regeneration could be controlled by varying plate voltage or coupling between L_2 and L_3 .

tuning control. As the receiver is tuned through a signal the tone first will be heard as a very high pitch, then will go down through "zero beat" and rise again on the other side, finally disappearing at a very high pitch. This behavior is shown in Fig. 5-8. A low-pitched beat-note cannot be obtained from a strong signal because the detector "pulls in" or "blocks"; that is, the signal forces the detector to oscillate at the

signal frequency, even though the circuit may not be tuned exactly to the signal. It usually can be corrected by advancing the regeneration control until the beat-note is heard again, or by reducing the input signal.

The point just after the detector starts oscillating is the most sensitive condition for code reception. Further advancing the regeneration control makes the receiver less prone to blocking, but also less sensitive to weak signals.

If the detector is in the oscillating condition and a phone signal is tuned in, a steady audible beat-note will result. While it is possible to listen to phone if the receiver can be tuned to exact zero beat, it is more satisfactory to reduce the regeneration to the point just before the receiver goes into oscillation. This is also the most sensitive operating point.

Single-sideband phone signals can be received

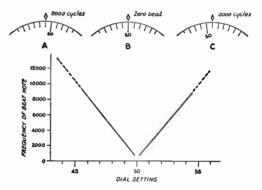


Fig. 5-8—As the tuning dial of a receiver is turned past a code signal, the beat-note varies from a high tone down through "zero beat" (no audible frequency difference) and back up to a high tone, as shown at A, B and C. The curve is a graphical representation of the action. The beat exists past 8000 or 10,000 cycles but usually is not heard because of the limitations of the audio system.

92

with a regenerative detector by advancing the regeneration control to the point used for code reception and tuning carefully across the s.s.b. signal. The tuning will be very critical, however, and the operator must be prepared to just

"creep" across the signal. A strong signal will pull the detector and make reception impossible, so either the regeneration must be advanced far enough to prevent this condition, or the signal must be reduced by using loose antenna coupling.

TUNING AND BAND-CHANGING METHODS

Band Chanaina


The same coil and tuning capacitor cannot be used for, say, 14 Mc. to 3.5 Mc., because of the impracticable maximum-to-minimum capacity ratio required, and also because the tuning would be excessively critical with such a large frequency range. It is necessary, therefore, to provide a means for changing the circuit constants for various frequency bands. As a matter of convenience the same tuning capacitor usually is retained, but new coils are inserted in the circuit for each band.

One method of changing inductances is to use a switch having an appropriate number of contacts, which connects the desired coil and disconnects the others. The unused coils are sometimes short-circuited by the switch, to avoid the possibility of undesirable self-resonances in the unused coils. This is not necessary if the coils are separated from each other by several coil diameters, or are mounted at right angles to each other.

Another method is to use coils wound on forms with contacts (usually pins) that can be plugged in and removed from a socket. These plug-in coils are advantageous when space in a multiband receiver is at a premium. They are also very useful when considerable experimental work is involved, because they are easier to work on than coils clustered around a switch.

Bandspreading

The tuning range of a given coil and variable capacitor will depend upon the inductance of the coil and the change in tuning capacity. For ease of tuning, it is desirable to adjust the tuning

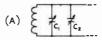

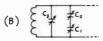


Fig. 5-9—Essentials of the three basic bandspread tuning systems.



range so that practically the whole dial scale is occupied by the band in use. This is called bandspreading. Because of the varying widths of the bands, special tuning methods must be devised to give the correct maximum-minimum capacity ratio on each band. Several of these methods are shown in Fig. 5-9.

In A, a small bandspread capacitor, C_1 (15-to 25- $\mu\mu$ f. maximum capacity), is used in par-

allel with capacitor, C_2 , which is usually large enough (100 to 140 $\mu\mu$ f.) to cover a 2-to-1 frequency range. The setting of C_2 will determine the minimum capacity for bandspread tuning will be the maximum capacity of bandspread tuning will be the maximum capacity of C_1 plus the setting of C_2 . The inductance of the coil can be adjusted so that the maximum-minimum ratio will give adequate bandspread. It is almost impossible, because of the non-harmonic relation of the various band limits, to get full bandspread on all bands with the same pair of capacitors. C_2 is variously called the band-setting or main tuning capacitor. It must be reset each time the band is changed.

If the capacitance change of a tuning capacitor is known, the approximate total fixed shunt capacitance (Fig. 5-9A) for covering an amateur band is given by

$$C_2 = \frac{C_1 F}{2f}$$

where C_1 = capacitance *change* C_2 = total shunt capacitance F = low-frequency limit of band f = width of band

Example: What fixed shunt capacitance will allow a capacitor with a range of 5 to 15 $\mu\mu$ f. to tune 6.95 to 7.35 Mc.?

$$C_2 = \frac{(15-5)\times7}{2\times(7.35-6.95)} = \frac{70}{.8} = 88 \,\mu\mu\text{f}.$$

The 5- $\mu\mu$ f, minimum of the tuning capacitor, the tube capacitance and any stray capacitance must be included in the 88 $\mu\mu$ f.

The method shown at B makes use of capacitors in series. The tuning capacitor, C_1 , may have a maximum capacitance of $100~\mu\mu$ f. or more. The minimum capacitance is determined principally by the setting of C_3 , which usually has low capacitance, and the maximum capacitance by the setting of C_2 , which is of the order of 25 to 50 $\mu\mu$ f. This method is capable of close adjustment to practically any desired degree of bandspread. Either C_2 and C_3 must be adjusted for each band or separate preadjusted capacitors must be switched in.

The circuit at C also gives complete spread on each band. C_1 , the bandspread capacitor, may have any convenient value; $50~\mu\mu$ f. is satisfactory. C_2 may be used for continuous frequency coverage ("general coverage") and as a bandsetting capacitor. The effective maximum-minimum capacitance ratio depends upon C_2 and the point at which C_1 is tapped on the coil. The nearer the tap to the bottom of the coil, the greater the tap, the bandspread will be greater if C_2 is set at bandspread, and vice versa. For a given coil and higher capacitance. C_2 may be connected permanently across the individual inductor and preset,

Superhetrodyne

if desired. This requires a separate capacitor for each band, but eliminates the necessity for resetting C_2 each time.

Ganged Tuning

The tuning capacitors of the several r.f. circuits may be coupled together mechanically and operated by a single control. However, this operating convenience involves more complicated construction, both electrically and mechanically. It becomes necessary to make the various circuits track—that is, tune to the same frequency at each setting of the tuning control.

True tracking can be obtained only when the inductance, tuning capacitors, and circuit inductances and minimum and maximum capacities are identical in all "ganged" stages. A small trimmer or padding capacitor may be connected across the coil, so that variations in minimum capacity can be compensated. The use of the trimmer necessarily increases the minimum circuit capacity, but it is a necessity for satisfactory tracking. Midget capacitors having maximum capacities of 15 to 30 $\mu\mu f$. are commonly used.

The same methods are applied to bandspread circuits that must be tracked. The circuits are identical with those of Fig. 5-9. If both general-coverage and bandspread tuning are to be avail-

able, an additional trimmer capacitor must be connected across the coil in each circuit shown. If only amateur-band tuning is desired, however, the C_3 in Fig. 5-9B, and C_2 in Fig. 5-9C, serve as trimmers.

The coil inductance can be adjusted by starting with a larger number of turns than necessary and removing a turn or fraction of a turn at a time until the circuits track satisfactorily. An alternative method, provided the inductance is reasonably close to the correct value initially, is to make the coil so that the last turn is variable with respect to the whole coil.

Another method for trimming the inductance is to use an adjustable brass (or copper) or powdered-iron core. The brass core acts like a single shorted turn, and the inductance of the coil is decreased as the brass core, or "slug," is moved into the coil. The powdered-iron core has the opposite effect, and increases the inductance as it is moved into the coil. The Q of the coil is not affected materially by the use of the brass slug, provided the brass slug has a clean surface or is silverplated. The use of the powdered-iron core will raise the Q of a coil, provided the iron is suitable for the frequency in use. Good powdered-iron cores can be obtained for use up to about 50 Mc.

THE SUPERHETERODYNE

For many years (until about 1932) practically the only type of receiver to be found in amateur stations consisted of a regenerative detector and one or more stages of audio amplification. Receivers of this type can be made quite sensitive but strong signals block them easily and, in our present crowded bands, they are seldom used except in emergencies. They have been replaced by superheterodyne receivers, generally called "superhets."

The Superheterodyne Principle

In a superheterodyne receiver, the frequency of the incoming signal is heterodyned to a new radio frequency, the intermediate frequency (abbreviated "i.f."), then amplified, and finally detected. The frequency is changed by modulating the output of a tunable oscillator (the high-frequency, or local, oscillator) by the incoming signal in a mixer or converter stage (first detector) to produce a side frequency equal to the intermediate frequency. The other side frequency is rejected by selective circuits. The audio-frequency signal is obtained at the second detector. Code signals are made audible by autodyne or heterodyne reception at the second detector.

As a numerical example, assume that an intermediate frequency of 455 kc. is chosen and that the incoming signal is at 7000 kc. Then the high-frequency oscillator frequency may be set to 7455 kc., in order that one side frequency (7455 minus 7000) will be 455 kc. The high-frequency oscillator could also be set to 6545 kc. and give

the same difference frequency. To produce an audible code signal at the second detector of, say, 1000 cycles, the autodyning or heterodyning oscillator would be set to either 454 or 456 kc.

The frequency-conversion process permits r.f. amplification at a relatively low frequency, the i.f. High selectivity and gain can be obtained at this frequency, and this selectivity and gain are constant. The separate oscillators can be designed for good stability and, since they are working at frequencies considerably removed from the signal frequencies (percentage-wise), they are not normally "pulled" by the incoming signal.

images

Each h.f. oscillator frequency will cause i.f. response at two signal frequencies, one higher and one lower than the oscillator frequency. If the oscillator is set to 7455 kc. to tune to a 7000-kc. signal, for example, the receiver can respond also to a signal on 7910 kc., which likewise gives a 455-kc. beat. The undesired signal is called theimage. It can cause unnecessary interference if it isn't eliminated.

The radio-frequency circuits of the receiver (those used before the signal is heterodyned to the i.f.) normally are tuned to the desired signal, so that the selectivity of the circuits reduces or eliminates the response to the image signal. The ratio of the receiver voltage output from the desired signal to that from the image is called the signal-to-image ratio, or image ratio.

The image ratio depends upon the selectivity of the r.f. tuned circuits preceding the mixer

noise ratio is wanted, particularly if the mixer is the first tube in the receiver.

tube. Also, the higher the intermediate frequency, the higher the image ratio, since raising the i.f. increases the frequency separation between the signal and the image and places the latter further away from the resonance peak of the signal-frequency input circuits. Most receiver designs represent a compromise between economy (few input tuned circuits) and image rejection (large number of tuned circuits).

A change in oscillator frequency caused by tuning of the mixer grid circuit is called pulling. Pulling should be minimized, because the stability of the whole receiver depends critically upon the stability of the h.f. oscillator. Pulling decreases with separation of the signal and h.f.-oscillator frequencies, being less with high intermediate frequencies. Another type of pulling is caused by regulation in the power supply. Strong signals cause the voltage to change, which in turn shifts the oscillator frequency.

HIGH-FREQUENCY RECEIVERS

Other Spurious Responses

Circuits


In addition to images, other signals to which the receiver is not ostensibly tuned may be heard. Harmonics of the high-frequency oscillator may beat with signals far removed from the desired frequency to produce output at the intermediate frequency; such spurious responses can be reduced by adequate selectivity before the mixer stage, and by using sufficient shielding to prevent signal pick-up by any means other than the antenna. When a strong signal is received, the harmonics generated by rectification in the second detector may, by stray coupling, be introduced into the r.f. or mixer circuit and converted to the intermediate frequency, to go through the receiver in the same way as an ordinary signal. These "birdies" appear as a heterodyne beat on the desired signal, and are principally bothersome when the frequency of the incoming signal is not greatly different from the intermediate frequency. The cure is proper circuit isolation and shielding.

If the first detector and high-frequency oscillator are separate tubes, the first detector is called a "mixer." If the two are combined in one en-


I F TRANS

TO OSC

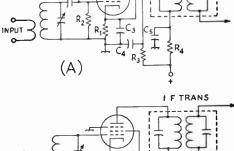
Harmonics of the beat oscillator also may be converted in similar fashion and amplified through the receiver; these responses can be reduced by shielding the beat oscillator and operating it at a low power level.



The Double-Conversion Superheterodyne

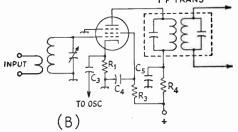

At high and very-high frequencies it is difficult to secure an adequate image ratio when the intermediate frequency is of the order of 455 kc. To reduce image response the signal frequently is converted first to a rather high (1500, 5000, or even 10,000 kc.) intermediate frequency, and then — sometimes after further amplification—reconverted to a lower i.f. where higher adjacent-channel selectivity can be obtained. Such a receiver is called a double-conversion superheterodyne.

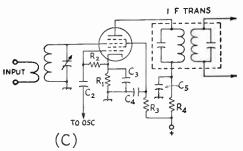

FREQUENCY CONVERTERS

Fig. 5-10—Typical circuits for separately excited mixers. Grid injection of a pentode mixer is shown at A, cathode injection at B, and separate excitation of a pentagrid converter is given in C. Typical values for C will be found in Table 5-1—the values below are for the pentode mixer of A and B.

A circuit tuned to the intermediate frequency is placed in the plate circuit of the mixer, to offer a high impedance load for the i.f. voltage that is developed. The signal- and oscillator-frequency voltages appearing in the plate circuit are rejected by the selectivity of this circuit. The i.f. tuned circuit should have low impedance for these frequencies, a condition easily met if they do not approach the intermediate frequency.

 C_1-10 to 50 $\mu\mu f$. R₂-1.0 megohm. C_2-5 to 10 $\mu\mu f$. R₃-0.47 megohm. C_3 , C_4 , C_5 -0.001 μf . R₄-1500 ohms.

The conversion efficiency of the mixer is the ratio of i.f. output voltage from the plate circuit to r.f. signal voltage applied to the grid. High conversion efficiency is desirable. The mixer tube noise also should be low if a good signal-to-

Positive supply voltage can be 250 volts with a 6AH6, 150 with a 6AK5.

Frequency Converters

velope (as is often done for reasons of economy or efficiency), the first detector is called a "converter." In either case the function is the same.


Typical mixer circuits are shown in Fig. 5-10. The variations are chiefly in the way in which the oscillator voltage is introduced. In 5-10A, a pentode functions as a plate detector; the oscillator voltage is capacity-coupled to the grid of the tube through C_2 . Inductive coupling may be used instead. The conversion gain and input selectivity generally are good, so long as the sum of the two voltages (signal and oscillator) impressed on the mixer grid does not exceed the grid bias. It is desirable to make the oscillator voltage as high as possible without exceeding this limitation. The oscillator power required is negligible. If the signal frequency is only 5 or 10 times the i.f., it may be difficult to develop enough oscillator voltage at the grid (because of the selectivity of the tuned input circuit). However, the circuit is a sensitive one and makes a good mixer, particularly with high-transconductance tubes like the 6AH6, 6AK5 or 6U8 (pentode section). Triode tubes can be used as mixers in grid-injection circuits, but they are commonly used only at 50 Mc. and higher, where mixer noise may become a significant factor. The triode mixer has the lowest inherent noise, the pentode is next, and the multigrid converter tubes are the noisiest.

The circuit in Fig. 5-10B shows cathode injection at the mixer. Operation is similar to the grid-injection case, and the same considerations

apply.

It is difficult to avoid "pulling" in a triode or pentode mixer, and a pentagrid mixer tube provides much better isolation. A typical circuit is shown in Fig. 5-10C, and tubes like the 6SA7, 6BA7 or 6BE6 are commonly used. The oscillator voltage is introduced through an "injection" grid. Measurement of the rectified current flowing in R_2 is used as a check for proper oscillator-voltage amplitude. Tuning of the signalgrid circuit can have little effect on the oscillator frequency because the injection grid is isolated from the signal grid by a screen grid that is at r.f. ground potential. The pentagrid mixer is much noisier than a triode or pentode mixer, but its isolating characteristics make it a very useful device.

Many receivers use pentagrid converters, and two typical circuits are shown in Fig. 5-11. The

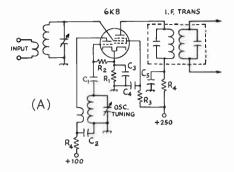

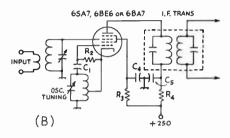


Fig. 5-11—Typical circuits for triode-hexode (A) and pentagrid (B) converters. Values for R_1 , R_2 and R_3 can be found in Table 5-1; others are given below.

C₁—47 μμf. C₂, C₄, C₅—0.001 μf. C_8 =0.01 μ f. R₄=1000 ohms.

circuit shown in Fig. 5-11A, which is suitable for the 6K8, is for a "triode-hexode" converter. A triode oscillator tube is mounted in the same envelope with a hexode, and the control grid of the oscillator portion is connected internally to an injection grid in the hexode. The isolation between oscillator and converter tube is reasonably good, and very little pulling results, except on signal frequencies that are quite large compared with the i.f.

The pentagrid-converter circuit shown in Fig. 5-11B can be used with a tube like the 6SA7, 6BA7 or 6BE6. Generally the only care necessary is to adjust the feedback of the oscillator circuit to give the proper oscillator r.f. voltage. The condition is checked by measuring the d.c. current flowing in grid resistor R_2 .

A more stable receiver generally results, par-

		TABLE 5-I				
Plate voltage == 250	ircuit and Operatin Screen voltage :	•			tor from 250	volts
	SELF-EXCITED		a	SEPARATE	Excitation	C

	DEGF-EXCITED				Darring Director			
Tube	Cathode Resistor	Screen Resistor	Grid Leak	Grid Current	Cathode Resistor	Screen Resistor	Grid Leak	Grid Current
6BA71	0	12,000	22,000	0.35 ma.	68	15,000	22,000	0.35 ma.
6BE6 ¹	0	22,000	22,000	0.5	150	22,000	22,000	0.5
6K8 ²	240	27,000	47,000	0.15 - 0.2			_	
6SA72	0	18,000	22,000	0.5	150	18,000	22,000	0.5

¹ Miniature tube ² Octal base, metal.

ticularly at the higher frequencies, when separate tubes are used for the mixer and oscillator. Practically the same number of circuit components is required whether or not a combination tube is used, so that there is very little difference to be realized from the cost standpoint.

Typical circuit constants for converter tubes are given in Table 5-I. The grid leak referred to is the oscillator grid leak or injection-grid return, R_2 or Figs. 5-10C and 5-11.

The effectiveness of converter tubes of the type just described becomes less as the signal frequency is increased. Some oscillator voltage will be coupled to the signal grid through "spacecharge" coupling, an effect that increases with frequency. If there is relatively little frequency difference between oscillator and signal, as for example a 14- or 28-Mc. signal and an i.f. of 455 kc., this voltage can become considerable because the selectivity of the signal circuit will be unable to reject it. If the signal grid is not returned directly to ground, but instead is returned through a resistor or part of an a.v.c. system, considerable bias can be developed which will cut down the gain. For this reason, and to reduce image response, the i.f. following the first converter of a receiver should be not less than 5 or 10 per cent of the signal frequency, for best results.

Transistors in Mixers

Typical transistor circuitry for a mixer operating at frequencies below 20 Mc. is shown in Fig. 5-12. The local oscillator current is injected in the emitter circuit by inductive coupling to L_1 ; L_1 should have low reactance at the oscillator frequency. The input from the r.f. amplifier

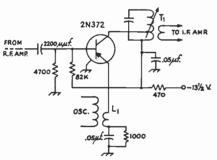


Fig. 5-12—Typical transistor mixer circuit.

L₁—Low-impedance inductive coupling to oscillator.

T₁—Transistor i.f. transformer. Primary impedance of 50,000 ohms, secondary impedance of 800 ohms (Miller 2066).

should be at low impedance, obtained by inductive coupling or tapping down on the tuned circuit. The output transformer T_1 has the collector connection tapped down on the inductance to maintain a high Q in the tuned circuit.

Audio Converters

Converter circuits of the type shown in Fig. 5-11 can be used to advantage in the reception of code and single-sideband suppressed-carrier sig-

nals, by introducing the local oscillator on the No. 1 grid, the signal on the No. 3 grid, and working the tube into an audio load. Its operation can be visualized as heterodyning the incoming signal into the audio range. The use of such circuits for audio conversion has been limited to selective i.f. amplifiers operating below 500 kc. and usually below 100 kc. An ordinary a.m. signal cannot be received on such a detector unless the tuning is adjusted to make the local oscillator zero-beat with the incoming carrier.

Since the beat oscillator modulates the electron stream completely, a large beat-oscillator component exists in the plate circuit. To prevent overload of the following audio amplifier stages, an adequate i.f. filter must be used in the output of the converter.

The "product detector" of Fig. 5-6 is also a converter circuit, and the statements above for audio converters apply to the product detector.

THE HIGH-FREQUENCY OSCILLATOR

Stability of the receiver is dependent chiefly upon the stability of the h.f. oscillator, and particular care should be given this part of the receiver. The frequency of oscillation should be insensitive to mechanical shock and changes in voltage and loading. Thermal effects (slow change in frequency because of tube or circuit heating) should be minimized. They can be reduced by using ceramic instead of bakelite insulation in the r.f. circuits, a large cabinet relative to the chassis (to provide for good radiation of developed heat), minimizing the number of high-wattage resistors in the receiver and putting them in the separate power supply, and not mounting the oscillator coils and tuning capacitor too close to a tube. Propping up the lid of a receiver will often reduce drift by lowering the terminal temperature of the unit.

Sensitivity to vibration and shock can be minimized by using good mechanical support for coils and tuning capacitors, a heavy chassis, and by not hanging any of the oscillator-circuit components on long leads. Tie-points should be used to avoid long leads. Stiff *short* leads are excellent because they can't be made to vibrate.

Smooth tuning is a great convenience to the operator, and can be obtained by taking pains with the mounting of the dial and tuning capacitors. They should have good alignment and no back-lash. If the capacitors are mounted off the chassis on posts instead of brackets, it is almost impossible to avoid some back-lash unless the posts have extra-wide bases. The capacitors should be selected with good wiping contacts to the rotor, since with age the rotor contacts can be a source of erratic tuning. All joints in the oscillator tuning circuit should be carefully soldered, because a loose connection or "rosin joint" can develop trouble that is sometimes hard to locate. The chassis and panel materials should be heavy and rigid enough so that pressure on the tuning dial will not cause torsion and a shift in the frequency.

In addition, the oscillator must be capable of

I.F. Amplifiers

Fig. 5-13—High-frequency oscillator circuits. A, pentode grounded-plate oscillator; B, triode grounded-plate oscillator; C, triode oscillator with tickler circuit. Coupling to the mixer may be taken from points X and Y. In A and B, coupling from Y will reduce pulling effects, but gives less voltage than from X; this type is best adapted to mixer circuits with small oscillator-voltage requirements. Typical values for components are as follows:

Circuit A	Circuit B	Circuit C
C ₁ —100 μμf.	100 μμf.	100 μμf.
C ₂ 0.01 μf.	0.01 μf.	0.01 μf.
C ₃ —0.01 μf.		
R ₁ -47,000 ohms.	47,000 ohms.	47,000 ohms.
R ₂ -47,000 ohms.	10,000 to	10,000 to
	25,000 ohms.	25,000 ohms.

The plate-supply voltage should be 250 volts. In circuits B and C, R_2 is used to drop the supply voltage to 100–150 volts; it may be omitted if voltage is obtained from a voltage divider in the power supply.


furnishing sufficient r.f. voltage and power for the particular mixer circuit chosen, at all frequencies within the range of the receiver, and its harmonic output should be as low as possible to reduce the possibility of spurious responses.


The oscillator plate power should be as low as is consistent with adequate output. Low plate power will reduce tube heating and thereby lower the frequency drift. The oscillator and mixer circuits should be well isolated, preferably by shielding, since coupling other than by the intended means may result in pulling.


If the h.f.-oscillator frequency is affected by changes in plate voltage, a voltage-regulated plate supply (VR tube) can be used.

Circuits

Several oscillator circuits are shown in Fig. 5-13. Circuits A and B will give about the same results, and require only one coil. However, in these two circuits the cathode is above ground potential for r.f., which often is a cause of hum modulation of the oscillator output at 14 Mc. and higher frequencies when a.c.-heated-cathode tubes are used. The circuit of Fig. 5-13C reduces hum because the cathode is grounded. It is simple to adjust, and it is also the best circuit to use with filament-type tubes. With filament-type

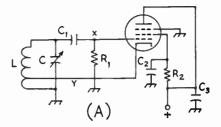

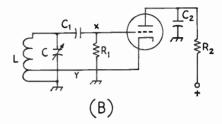

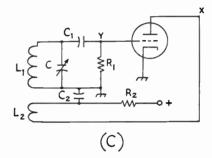

tubes, the other two circuits would require r.f. chokes to keep the filament above r.f. ground.

Besides the use of a fairly high C/L ratio in the tuned circuit, it is necessary to adjust the feedback to obtain optimum results. Too much feedback may cause "squegging" of the oscillator and the generation of several frequencies simultaneously; too little feedback will cause the output to be low. In the tapped-coil circuits (A, B), the feedback is increased by moving the tap toward the grid end of the coil. In C, more feedback is obtained by increasing the number of turns on L_2 or moving L_2 closer to L_1 .

THE INTERMEDIATE-FREQUENCY AMPLIFIER

One major advantage of the superhet is that high gain and selectivity can be obtained by using a good i.f. amplifier. This can be a one-stage affair in simple receivers, or two or three stages in the more elaborate sets.

Choice of Frequency

The selection of an intermediate frequency is a compromise between conflicting factors. The lower the i.f. the higher the selectivity and gain, but a low i.f. brings the image nearer the desired signal and hence decreases the image ratio. A low i.f. also increases pulling of the oscillator frequency. On the other hand, a high i.f. is beneficial to both image ratio and pulling, but the gain is lowered and selectivity is harder to obtain by simple means.

An i.f. of the order of 455 kc. gives good selectivity and is satisfactory from the standpoint of image ratio and oscillator pulling at frequencies up to 7 Mc. The image ratio is poor at 14 Mc. when the mixer is connected to the antenna, but

HIGH-FREQUENCY RECEIVERS

adequate when there is a tuned r.f. amplifier between antenna and mixer. At 28 Mc. and on the very high frequencies, the image ratio is very poor unless several r.f. stages are used. Above 14 Mc., pulling is likely to be bad without very loose coupling between mixer and oscillator.

With an i.f. of about 1600 kc., satisfactory image ratios can be secured on 14, 21 and 28 Mc. with one r.f. stage of good design. For frequencies of 28 Mc. and higher, a common solution is to use double conversion, choosing one high i.f. for image reduction (5 and 10 Mc. are frequently used) and a lower one for gain and selectivity.

In choosing an i.f. it is wise to avoid frequencies on which there is considerable activity by the various radio services, since such signals may be picked up directly on the i.f. wiring. Shifting the i.f. or better shielding are the solutions to this interference problem.

Fidelity; Sideband Cutting

Modulation of a carrier causes the generation of sideband frequencies numerically equal to the carrier frequency plus and minus the highest modulation frequency present. If the receiver is to give a faithful reproduction of modulation that contains, for instance, audio frequencies up to 5000 cycles, it must at least be capable of amplifying equally all frequencies contained in a band extending from 5000 cycles above or below the carrier frequency. In a superheterodyne, where all carrier frequencies are changed to the fixed intermediate frequency, the i.f. amplification must be uniform over a band 5 kc. wide, when the carrier is set at one edge. If the carrier is set in the center, a 10-kc. band is required. The signal-frequency circuits usually do not have enough over-all selectivity to affect materially the "adjacent-channel" selectivity, so that only the i.f.-amplifier selectivity need be considered.

If the selectivity is too great to permit uniform amplification over the band of frequencies occupied by the modulated signal, some of the sidebands are "cut." While sideband cutting reduces fidelity, it is frequently preferable to sacrifice naturalness of reproduction in favor of communications effectiveness.

The selectivity of an i.f.-amplifier, and hence the tendency to cut sidebands, increases with the number of amplifier stages and also is greater the lower the intermediate frequency. From the standpoint of communication, sideband cutting is never serious with two-stage amplifiers at frequencies as low as 455 kc. A two-stage i.f. ampli-

Fig. 5-14—Typical intermediate-frequency amplifier circuit for a superheterodyne receiver. Representative values for components are as follows: C₁, C₃, C₄, C₅—0.02 µf. at 455 kc; 0.01 µf. at 1600 kc. and higher.

 C_2 —0.01 μ f. R_1 , R_2 —See Table 5-11. R_3 , R_5 —1500 ohms. R_4 —0.1 megohm. fier at 85 or 100 kc. will be sharp enough to cut some of the higher-frequency sidebands, if good transformers are used. However, the cutting is not at all serious, and the gain in selectivity is worthwhile in crowded amateur bands.

Circuits

I.f. amplifiers usually consist of one or two stages. At 455 kc. two stages generally give all the gain usable, and also give suitable selectivity for phone reception.

A typical circuit arrangement is shown in Fig. 5-14. A second stage would simply duplicate the circuit of the first. The i.f. amplifier practically always uses a remote cut-off pentode-type tube operated as a Class A amplifier. For maximum selectivity, double-tuned transformers are used for interstage coupling, although single-tuned circuits or transformers with untuned primaries can be used for coupling, with a consequent loss in selectivity. All other things being equal, the selectivity of an i.f. amplifier is proportional to the number of tuned circuits in it.

In Fig. 5-14, the gain of the stage is reduced by introducing a negative voltage to the lead marked "AGC" or a positive voltage to R_1 at the point marked "manual gain control." In either case, the voltage increases the bias on the tube and reduces the nutual conductance and hence the gain. When two or more stages are used, these voltages are generally obtained from common sources. The decoupling resistor, R_8 , helps to prevent unwanted interstage coupling. C_2 and R_4 are part of the automatic gain-control circuit (described later); if no a.g.c. is used, the lower end of the i.f.-transformer secondary is connected to chassis.

Tubes for I.F. Amplifiers

Variable- μ (remote cut-off) pentodes are almost invariably used in i.f. amplifier stages, since grid-bias gain control is practically always applied to the i.f. amplifier. Tubes with high plate resistance will have least effect on the selectivity of the amplifier, and those with high mutual conductance will give greatest gain. The choice of i.f. tubes normally has no effect on the signal-to-noise ratio, since this is determined by the preceding mixer and r.f. amplifier.

Typical values of cathode and screen resistors for common tubes are given in Table 5-II. The 6BA6, 6BJ6 and 6BZ6 are recommended for i.f. work because they have desirable remote cut-off characteristics. The indicated screen resistors

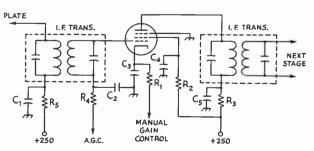


TABLE 5-II

Cathode and Screen-Dropping
Resistors for R.F. or I.F. Amplifiers

Tube	Plate Volts	Screen Volts	Cathode Resistor B	Screen 1. Resistor Rs
6AC71	300		160	62,000
6AH62	300	150	160	62,000
6AK5 ²	180	120	200	27,000
6AU62	250	150	68	33,000
6BA62*	250	100	68	33,000
6BH6 ²	250	150	100	33,000
6BJ62*	250	100	82	47,000
6BZ62*	200	150	180	20,000
6CB6	200	150	180	56,000
6DC6 ^a	200	135	18	24,000
6SG71*	250	125	68	27,000
6SH71	250	150	68	39,000
6SJ71	250	100	820	180,000
6SK71*	250	100	270	56,000

¹ Octal base, metal. ² Miniature tube

* Remote cut-off type.

drop the plate voltage to the correct screen voltage, as R_2 in Fig. 5-14.

When two or more stages are used the high gain may tend to cause instability and oscillation, so that good shielding, bypassing, and careful circuit arrangement to prevent stray coupling between input and output circuits are necessary.

When single-ended tubes are used, the plate and grid leads should be well separated. With these tubes it is advisable to mount the screen bypass capacitor directly on the bottom of the socket, crosswise between the plate and grid pins, to provide additional shielding. If a paper capacitor is used, the outside foil should be grounded to the chassis.

I.F. Transformers

The tuned circuits of i.f. amplifiers are built up as transformer units consisting of a metal shield container in which the coils and tuning capacitors are mounted. Both air-core and powdered iron-core universal-wound coils are used, the latter having somewhat higher Qs and hence greater selectivity and gain. In universal windings the coil is wound in layers with each turn traversing the length of the coil, back and forth, rather than being wound perpendicular to the axis as in ordinary single-layer coils. In a straight multilayer winding, a fairly large capacitance can exist between layers. Universal winding, with its "criss-crossed" turns, tends to reduce distributed-capacity effects.

For tuning, air-dielectric tuning capacitors are preferable to mica compression types because their capacity is practically unaffected by changes in temperature and humidity. Iron-core transformers may be tuned by varying the inductance (permeability tuning), in which case stability comparable to that of variable air-capacitor tuning can be obtained by use of high-stability fixed mica or ceramic capacitors. Such stability is of great importance, since a circuit whose frequency "drifts" with time eventually will be tuned to a different frequency than the other circuits, thereby reducing the gain and

selectivity of the amplifier. Typical i.f.-transformer construction is shown in Fig. 5-15.

The normal interstage i.f. transformer is loosely coupled, to give good selectivity consistent with adequate gain. A so-called diode transformer is similar, but the coupling is tighter, to give sufficient transfer when working into the finite load presented by a diode detector. Using a diode transformer in place of an interstage transformer would result in loss of selectivity; using an interstage transformer to couple to the diode would result in loss of gain.

Besides the type of i.f. transformer shown in Fig. 5-15, special units to give desired selectivity characteristics are available. For higher-than-ordinary adjacent-channel selectivity triple-tuned transformers, with a third tuned circuit inserted between the input and output windings, are sometimes used. The energy is transferred from the input to the output windings via this tertiary winding, thus adding its selectivity to the over-all selectivity of the transformer.

A method of varying the selectivity is to vary the coupling between primary and secondary, overcoupling being used to broaden the selectivity curve. Special circuits using single tuned circuits, coupled in any of several different ways, are used in some advanced receivers.

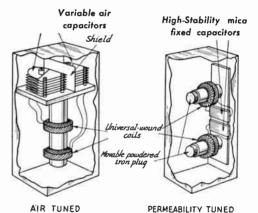


Fig. 5-15—Representative i.f.-transformer construction. Coils are supported on insulating tubing. The shield in the air-tuned transformer prevents capacity coupling between the tuning capacitors. In the permeability-tuned transformer the cores consist of finely-divided iron particles supported in an insulating binder, formed

into cylindrical "plugs." The tuning capacitance is fixed, and the inductances of the coils are varied by moving the iron plugs in and out.

Selectivity

The over-all selectivity of the i.f. amplifier will depend on the frequency and the number of stages. The following figures are indicative of the bandwidths to be expected with good-quality circuits in amplifiers so constructed as to keep regeneration at a minimum:

Fig. 5-16—Typical circuit for a twostage transistor i.f. amplifier. The stages are neutralized by the 5- and 8.2- $\mu\mu$ f. capacitors. Unless specified otherwise, capacitances are in μ f.

T₁—50K to 800-ohm secondary (Miller 2066).

T₂—30K to 500-ohm secondary (Miller 2067).

T_s-20K to 5K secondary (Miller 2068).

	1000			0 -
150K	₹.01	≥100K	₸.05	9v.
-	Suut.		7/ //	
主君	T2N218]	B + 8.2 must.	<u> </u>	***
T ₁		T ₂	T ₃ 1N34A	
\equiv		2N218	ر کی از	VOLUME
.05 🛨	1 1 105 2	.01 = \$18K = \$100	00 ,	Ţ ₹25 K
4	T T_}^^	00 T 05 T 5100		4
	h 4	יין יין		
		*18.K		

Tuned	(ircu	Bandwidth, kc.		
Circuits	Frequency	Q	-6 db.	-20 db.	−60 db.
4	50 kc.	60	0.5	0.95	2.16
4	455 kc.	75	3.6	6.9	16
6	1600 kc.	90	8.2	15	34

Transistor I. F. Amplifier

A typical circuit for a two-stage transistor i.f. amplifier is shown in Fig. 5-16. Constants are given for a 455-kc. amplifier, but the same general circuitry applies to an amplifier at any frequency within the operating range of the transistors. When high frequencies are used, it is generally advisable to neutralize the amplifier to avoid overall oscillation; this is done by connecting the small capacitors of a few $\mu\mu$ f. from base to primary, as shown in the diagram.


Automatic gain control is obtained by using


the developed d.c. at the 1N34A diode detector to modify the emitter bias current on the first stage. As the bias current changes, the input and output impedances change, and the resultant impedance mismatches causes a reduction in gain. Such a.g.c. assumes, of course, that the amplifier is set up initially in a matched condition.

THE SECOND DETECTOR AND BEAT OSCILLATOR

Detector Circuits

The second detector of a superheterodyne receiver performs the same function as the detector in the simple receiver, but usually operates at a higher input level because of the relatively great amplification ahead of it. Therefore, the ability

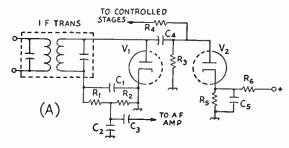

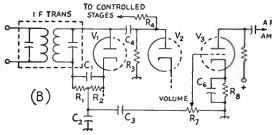

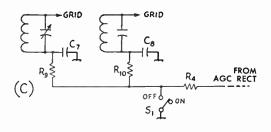


Fig. 5-17—Delayed automatic gain-control circuits using a twin diode (A) and a dual-diode triode. The circuits are essentially the same and differ only in the method of biasing the a.g.c. rectifier. The a.g.c. control voltage is applied to the controlled stages as in (C). For these circuits typical values are:

C₁, C₂, C₄-100 μμf.

C₃, C₆, C₇, C₈--0.01 µf.

C6-5-µf. electrolytic.

 R_1 , R_9 , R_{10} —0.1 megohm.

 R_2 -0.47 megohm.

R₃-2 megohms.

R₄-0.47 megohm.

 R_{δ} , R_0 —Voltage divider to give 2 to 10 volts bias at 1 to 2 ma. drain.

R7-0.5-megohm volume control.

R₈—Correct bias resistor for triode section of dual-diode triode.

Automatic Gain Control

to handle large signals without distortion is preferable to high sensitivity. Plate detection is used to some extent, but the diode detector is most popular. It is especially adapted to furnishing automatic gain or volume control. The basic circuits have been described, although in many cases the diode elements are incorporated in a multipurpose tube that contains an amplifier section in addition to the diode.

Audio-converter circuits and product detectors are often used for code or s.s.b. detectors.

The Beat Oscillator

Any standard oscillator circuit may be used for the beat oscillator required for heterodyne reception. Special beat-oscillator transformers are available, usually consisting of a tapped coil with adjustable tuning; these are most conveniently used with the circuits shown in Fig. 5-13A and B, with the output taken from Y. A variable capacitor of about 25- $\mu\mu$ f. capacitance can be connected between cathode and ground to provide fine adjustment of the frequency. The beat oscillator usually is coupled to the second-detector tuned circuit through a fixed capacitor of a few $\mu\mu$ f.

The beat oscillator should be well shielded, to prevent coupling to any part of the receiver except the second detector and to prevent its harmonics from getting into the front end and being amplified along with desired signals. The b.f.o. power should be as low as is consistent with sufficient audio-frequency output on the strongest signals. However, if the beat-oscillator output is too low, strong signals will not give a proportionately strong audio signal. Contrary to some opinion, a weak b.f.o. is never an advantage.

AUTOMATIC GAIN CONTROL

Automatic regulation of the gain of the receiver in inverse proportion to the signal strength is an operating convenience in phone reception, since it tends to keep the output level of the receiver constant regardless of input-signal strength. The average rectified d.c. voltage, developed by the received signal across a resistance in a detector circuit, is used to vary the bias on the r.f. and i.f. amplifier tubes. Since this voltage is proportional to the average amplitude of the signal, the gain is reduced as the signal strength becomes greater. The control will be more complete and the output more constant as the number of stages to which the a.g.c. bias is applied is increased. Control of at least two stages is advisable.

Circuits

Although some receivers derive the a.g.c. voltage from the diode detector, the usual practice is to use a separate a.g.c. rectifier. Typical circuits are shown in Figs. 5-17A and 5-17B. The two rectifiers can be combined in one tube, as in the 6H6 and 6AL5. In Fig. 5-17A V_1 is the diode detector; the signal is developed across R_1R_2 and coupled to the audio stages through C_3 . C_1 , R_1 and C_2 are included for r.f. filtering, to prevent

a large r.f. component being coupled to the audio circuits. The a.g.c. rectifier, V_2 , is coupled to the last i.f. transformer through C_4 , and most of the rectified voltage is developed across R_3 . V_2 does not rectify on weak signals, however; the fixed bias at R_5 must be exceeded before rectification can take place. The developed negative a.g.c. bias is fed to the controlled stages through R_4 .

The circuit of Fig. 5-17B is similar, except that a dual-diode triode tube is used. Since this has only one common cathode, the circuitry is slightly different but the principle is the same. The triode stage serves as the first audio stage, and its bias is developed in the cathode circuit across R_8 . This same bias is applied to the a.g.c. rectifier by returning its load resistor, R_8 , to ground. To avoid placing this bias on the detector, V_1 , its load resistor R_1R_2 is returned to cathode, thus avoiding any bias on the detector and permitting it to respond to weak signals.

The developed negative a.g.c. bias is applied to the controlled stages through their grid circuits, as shown in Fig. 5-17C. C_7R_0 and C_8R_{10} serve as filters to avoid common coupling and possible feedback and oscillator. The a.g.c. is disabled by closing switch S_1 .

The a.g.c. rectifier bias in Fig. 5-17B is set by the bias required for proper operation of V_3 . If less bias for the a.g.c. rectifier is required, R_3 can be tapped up on R_8 instead of being returned to chassis ground. In Fig. 5-17A, proper choice of bias at R_5 depends upon the over-all gain of the receiver and the number of controlled stages. In general, the bias at R_5 will be made higher for receivers with more gain and more stages.

Time Constant

The time constant of the resistor-capacitor combinations in the a.g.c. circuit is an important part of the system. It must be long enough so that the modulation on the signal is completely filtered from the d.c. output, leaving only an average d.c. component which follows the relatively slow carrier variations with fading. Audio-frequency variations in the a.g.c. voltage applied to the amplifier grids would reduce the percentage of modulation on the incoming signal. But the time constant must not be too long or the a.g.c. will be unable to follow rapid fading. The capacitance and resistance values indicated in Fig. 5-17 will give a time constant that is satisfactory for average reception.

C.W. and S.S.B.

A.g.c. can be used for c.w. and s.s.b. reception but the circuit is usually more complicated. The a.g.c. voltage must be derived from a rectifier that is isolated from the beat-frequency oscillator (otherwise the rectified b.f.o. voltage will reduce the receiver gain even with no signal coming through). This is done by using a separate a.g.c. channel connected to an i.f. amplifier stage ahead of the second detector (and b.f.o.) or by rectifying the audio output of the detector. If the selectivity ahead of the a.g.c. rectifier isn't good, strong adjacent-channel signals may de-

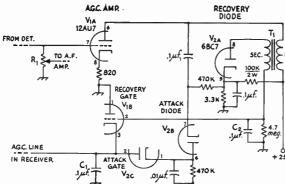


Fig. 5-18—Audio "hang" a.g.c. system. Resistors are ½ watt unless specified otherwise.

R₁—Normal audio volume control in receiver.

T₁—1:3 step-up audio transformer (Stancor A-53 or equiv.)

The hang time can be adjusted by changing the value of the recovery diode load resistor (4.7 megohms shown here). The a.g.c. line in the receiver must have no d.c. return to ground and the receiver should have good skirt selectivity for maximum effectiveness of the system.

velop a.g.c. voltages that will reduce the receiver gain while listening to weak signals. When clear channels are available, however, c.w. and s.s.b. a.g.c. will hold the receiver output constant over a wide range of signal inputs. A.g.c. systems designed to work on these signals should have fast-attack and slow-decay characteristics to work satisfactorily, and often a selection of time constants is made available.

The a.g.c. circuit shown in Fig. 5-18 is applicable to many receivers without too much modification. Audio from the receiver is amplified in V_{1A} and rectified in V_{2B} . The resultant voltage is applied to the a.g.c. line through V_{2C} . The capacitor C_1 charges quickly and will remain charged until discharged by V_{1B} . This will occur some time after the signal has disappeared,

because the audio was stepped up through T_1 and rectified in V_{2A} , and the resultant used to charge C_2 . This voltage holds V_{1B} cut off for an appreciable time, until C_2 discharges through the 4.7-megohm resistor. The threshold of compression is set by adjusting the bias on the diodes (changing the value of the 3.3K or 100K resistors). There can be no d.c. return to ground from the a.g.c. line, because C_1 must be discharged only by V_{1B} . Even a v.t.v.m. across the a.g.c. line will be too low a resistance, and the operation of the system must be observed by the action of the S meter.

Occasionally a strong noise pulse may cause the a.g.c. to hang until C_2 discharges, but most of the time the gain should return very rapidly to that set by the signal. A.g.c. of this type is very helpful in handling netted s.s.b. signals of widely varying strengths.

NOISE REDUCTION

Types of Noise

In addition to tube and circuit noise, much of the noise interference experienced in reception of high-frequency signals is caused by domestic or industrial electrical equipment and by automobile ignition systems. The interference is of two types in its effects. The first is the "hiss" type, consisting of overlapping pulses similar in nature to the receiver noise. It is largely reduced by high selectivity in the receiver, especially for code reception. The second is the "pistol-shot" or "machine-gun" type, consisting of separated impulses of high amplitude. The "hiss" type of interference usually is caused by commutator sparking in d.c. and series-wound a.c. motors, while the "shot" type results from separated spark discharges (a.c. power leaks, switch and key clicks, ignition sparks, and the like).

The only known approach to reducing tube and circuit noise is through better "front-end" design and through more over-all selectivity.

Impulse Noise

Impulse noise, because of the short duration of the pulses compared with the time between them, must have high amplitude to contain much average energy. Hence, noise of this type strong enough to cause much interference generally has


an instantaneous amplitude much higher than that of the signal being received. The general principles of devices intended to reduce such noise is to allow the desired signal to pass through the receiver unaffected, but to make the receiver inoperative for amplitudes greater than that of the signal. The greater the amplitude of the pulse compared with its time of duration, the more successful the noise reduction.

Another approach is to "silence" (render inoperative) the receiver during the short duration time of any individual pulse. The listener will not hear the "hole" because of its short duration, and very effective noise reduction is obtained. Such devices are called "silencers" rather than "limiters."

In passing through selective receiver circuits, the time duration of the impulses is increased, because of the Q of the circuits. Thus the more selectivity ahead of the noise-reducing device, the more difficult it becomes to secure good pulse-type noise suppression.

Audio Limiting

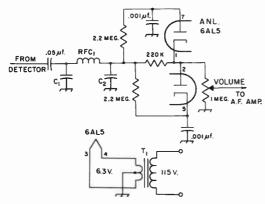A considerable degree of noise reduction in code reception can be accomplished by amplitude-limiting arrangements applied to the audio-output circuit of a receiver. Such limiters also maintain the signal output nearly constant



during fading. These output-limiter systems are simple, and they are readily adaptable to most receivers without any modification of the receiver itself. However, they cannot prevent noise peaks from overloading previous stages.

SECOND-DETECTOR NOISE LIMITER CIRCUITS

Most audio limiting circuits are based on one of two principles. In a series limiting circuit, a normally conducting element (or elements) is connected in the circuit in series and operated in such a manner that it becomes non-conductive above a given signal level. In a shunt limiting circuit, a non-conducting element is connected in shunt across the circuit and operated so that it becomes conductive above a given signal level, thus short-circuiting the signal and preventing its being transmitted to the remainder of the amplifier. The usual conducting element will be a forward-biased diode, and the usual non-conducting element will be a back-biased diode. In many applications the value of bias is set manually by the operator; usually the clipping level will be set at about 5 to 10 volts.

A full-wave clipping circuit that operates at a low level (approximately 1/2 volt) is shown in Fig. 5-19. Each diode is biased by its own contact potential, developed across the 2.2-megohm resistors. The .001-µf. capacitors become charged to close to this value of contact potential. A negative-going signal in excess of the bias will be shorted to ground by the upper diode; a positive-going signal will be conducted by the lower diode. The conducting resistance of the diodes is small by comparison with the 220,000 ohms in series with the circuit, and little if any of the excessive signal will appear across the 1-megohm volume control. In order that the clipping does not become excessive and cause distortion, the input signal must be held down by a gain control ahead of the detector. This circuit finds good application following a low-level detector.

To minimize hum in the receiver output, it is desirable to ground the center tap of the heater transformer, as shown, instead of the more common practice of returning one side of the heater circuit to chassis.

Fig. 5-19—Full-wave shunt limiter using contact-potential-biased diodes. A low-level limiter (½ volt), this circuit finds greatest usefulness following a product detector.

C₁, C₂—Part of low-pass filter with cutoff below i.f. RFC₁—Part of low-pass filter; see C₁. T₁—Center-tapped heater transformer.

A circuit for a higher-level audio limiter is shown in Fig. 5-20. Because it operates at a higher level, it is ideal for use between receiver output and headphones, requiring no alteration to the receiver. The principle of operation is similar to that of the preceding limiter; when the signal level exceeds the level of the bias provided by the flashlight cells, the diodes conduct and short-circuit the signal.

Second-detector noise-limiting circuits that automatically adjust themselves to the received carrier level are shown in Fig. 5-21. In either circuit, V_1 is the usual diode second detector, R_1R_2 is the diode load resistor, and C_1 is an r.f. bypass. A negative voltage proportional to the carrier level is developed across C_2 , and this voltage cannot change rapidly because R_3 and C_2 are both large. In the circuit at A, diode V_2 acts as a conductor for the audio signal up to the point where its anode is negative with respect to the cathode. Noise peaks that exceed the maximum carrier-modulation level will drive the anode negative instantaneously, and during this time the diode does not conduct. The long time constant of C_2R_3 prevents any rapid change of the reference voltage. In the circuit at B, the diode V2 is inactive until its cathode voltage exceeds its anode voltage. This condition will obtain under noise peaks and when it does, the diode V_2 short-circuits the signal and no voltage is passed on to the audio amplifier. Diode rectifiers such as the 6H6 and 6AL5 can be used for these types of noise limiters. Neither circuit is useful for c.w. or s.s.b. reception, but they are both quite effective for a.m. phone work. The series circuit (A) is slightly better than the shunt circuit.

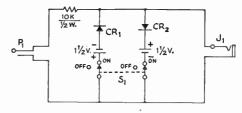


Fig. 5-20—Circuit diagram of a simple audio limiter, to be plugged into the headphone jack of a receiver. The flashlight cells draw very little current (it depends upon the back resistance of the crystal diodes), but it is advisable to open S₁ when the limiter is not in use.

Crystal diodes can be 1N34As or similar.

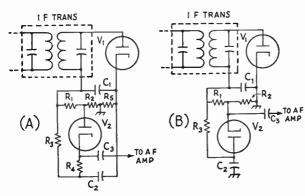


Fig. 5-21—Self-adjusting series (A) and shunt (B) noise limiters. The functions of V₁ and V₂ can be combined in one tube like the 6H6 or 6AL5.

 $C_1-100~\mu\mu f$. $C_2,C_3-0.05~\mu f$. $R_1-0.27~meg$. in A; 47,000 ohms in B. $R_2-0.27~meg$. in A; 0.15 meg. in B. $R_3-1.0~meg$ ohm. $R_4-0.82~meg$ ohm, $R_6-6800~ohms$.

I.F. NOISE SILENCER

The i.f. noise silencer circuit shown in Fig. 5-22 is designed to be used in a receiver as far along from the antenna stage as possible but ahead of the high-selectivity section of the receiver. Noise pulses are amplified and rectified, and the resulting negative-going d.c. pulses are used to cut off an amplifier stage during the pulse. A manual "threshold" control is set by the operator to a level that only permits rectification of the noise pulses that rise above the peak amplitude of the desired signal. The clamp diode, V_{1A} , short circuits the positive-going pulse "overshoots." Running the 6BE6 controlled i.f. amplifier at low screen voltage makes it possible for the No. 3 grid (pin 7) to cut off the stage at a lower voltage than if the screen were operated at the more-normal 100 volts, but it also reduces the available gain through the stage. It is necessary to avoid i.f. feedback around the 6BE6 stage, and the closer RFC_1 can be to self-resonant at the i.f. the better will be the filtering. The filtering cannot be improved by increasing the values of the $150-\mu\mu f$. capacitors because this will tend to "stretch" the pulses and reduce the signal strength when the silencer is operative.

SIGNAL-STRENGTH AND TUNING INDICATORS

The simplest tuning indicator is a milliammeter connected in the d.c. plate lead of an a.g.c.-controlled r.f. or i.f. stage. Since the plate current is reduced as the a.g.c. voltage becomes higher with a stronger signal, the plate current is a measure of the signal strength. The meter can have a 0-1, 0-2 or 0-5 ma. movement, and it should be shunted by a 25-ohm rheostat which is

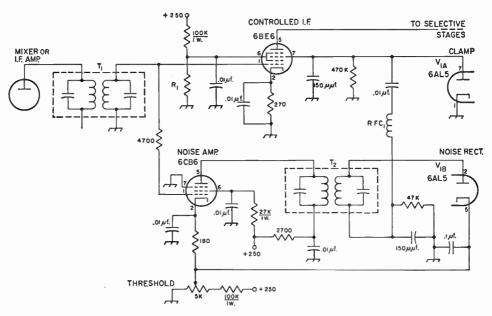


Fig. 5-22—Practical circuit diagram of an i.f. noise silencer. For best results the silencer should be used ahead of the high-selectivity portion of the receiver. T₂—Interstage i.f. transformer

T₂—Diode i.f. transformer.

 $R_1{=}33{,}000$ to $68{,}000$ ohms, depending upon gain up to this stage.

RFC1-R.f. choke, preferably self-resonant at i.f.

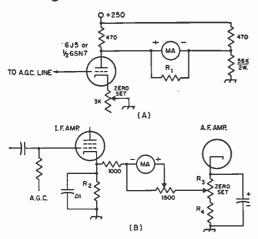


Fig. 5-23—Tuning indicator or S-meter circuits for superheterodyne receivers.

MA-0-1 or 0-2 milliammeter. R₁-R₄-See text.

used to set the no-signal reading to full scale on the meter. If a "forward-reading" meter is desired, the meter can be mounted upside down.

Two other S-meter circuits are shown in Fig. 5-23. The system at A uses a milliammeter in a bridge circuit, arranged so that the meter readings increase with the a.g.c. voltage and signal strength. The meter reads approximately in a linear decibel scale and will not be "crowded."

To adjust the system in Fig. 5-23A, pull the tube out of its socket or otherwise break the cathode circuit so that no plate current flows, and adjust the value of resistor R_1 across the meter until the scale reading is maximum. The value of resistance required will depend on the internal resistance of the meter, and must be determined by trial and error (the current is approximately 2.5 ma.). Then replace the tube, allow it to warm up, turn the a.g.c. switch to "off" so the grid is shorted to ground, and adjust the 3000-ohm variable resistor for zero meter current. When the a.g.c. is "on," the meter will follow the signal variations up to the point where the voltage is high enough to cut off the meter tube's plate current. With a 6J5 or 6SN7GT this will occur in the neighborhood of 15 volts, a high-amplitude signal.

The circuit of Fig. 5-23B requires no additional tubes. The resistor R_2 is the normal cathode resistor of an a.g.c.-controlled i.f. stage; its cathode resistor should be returned to chassis and not to the manual gain control. The sum of R_3 plus R_4 should equal the normal cathode resistor for the audio amplifier, and they should be proportioned so that the arm of R_3 can pick off a voltage equal to the normal cathode voltage for the i.f. stage. In some cases it may be necessary to interchange the positions of R_3 and R_4 in the circuit.

The zero-set control R_3 should be set for no reading of the meter with no incoming signal, and the 1500-ohm sensitivity control should be

set for a full meter reading with the i.f. tube removed from its socket.

Neither of these S-meter circuits can be "pinned," and only severe misadjustment of the zero-set control can injure the meter.

HEADPHONES AND LOUDSPEAKERS

There are two basic types of headphones in common use, the magnetic and the crystal. A magnetic headphone uses a small electromagnet that attracts and releases a steel diaphragm in accordance with the electrical output of the radio receiver; this is similar to the "receiver" portion of the household telephone. A crystal headphone uses the piezoelectric properties of a pair of Rochelle-salt or other crystals to vibrate a diaphragm in accordance with the electrical output of the radio receiver. Magnetic headphones can be used in circuits where d.c. is flowing, such as the plate circuit of a vacuum tube, provided the current is not too heavy to be carried by the wire in the coils; the limit is usually a few milliamperes. Crystal headphones can be used only on a.c. (a steady d.c. voltage will damage the crystal unit), and consequently must be coupled to a tube through a device, such as a capacitor or transformer, that isolates the d.c. but passes the a.c. Most modern receivers have a.c. coupling to the headphones and hence either type of headphone can be used, but it is wise to look first at the circuit diagram in the instruction book and make sure that the headphone jack is connected to the secondary of the output transformer, as is usually the case.

In general, crystal headphones will have considerably wider and "flatter" audio response than will magnetic headphones (except those of the "hi-fi" type that sell at premium prices). The lack of wide response in the magnetic headphones is sometimes an advantage in code reception, since the desired signal can be set on the peak and be given a boost in volume over the undesired signals at slightly different frequencies.

Crystal headphones are available only in highimpedance values around 50,000 ohms or so, while magnetic headphones run around 10,000 to 20,000 ohms, although they can be obtained in values as low as 15 ohms. Usually the impedance of a headphone set is unimportant because there is more than enough power available from the radio receiver, but in marginal cases it is possible to improve the acoustic output through a better match of headphone to output impedance. When headphone sets are connected in series or in parallel they must be of similar impedance levels or one set will "hog" most of the power.

Loud speakers are practically always of the low-impedance permanent-field dynamic variety, and the loudspeaker output connections of a receiver can connect directly to the voice coil of the loudspeaker. Some receivers also provide a "500-ohm output" for connection to a long line to a remote loudspeaker. A loudspeaker requires mounting in a suitable enclosure if full low-frequency response is to be obtained.

IMPROVING RECEIVER SELECTIVITY

INTERMEDIATE-FREQUENCY AMPLIFIERS

As mentioned earlier in this chapter, one of the big advantages of the superheterodyne receiver is the improved selectivity that is possible. This selectivity is obtained in the i.f. amplifier, where the lower frequency allows more selectivity per stage than at the higher signal frequency. For phone reception, the limit to useful selectivity in the i.f. amplifier is the point where so many of the sidebands are cut that intelligibility is lost, although it is possible to remove completely one full set of sidebands without impairing the quality at all. Maximum receiver selectivity in phone reception requires good stability in both transmitter and receiver, so that they will both remain "in tune" during the transmission. The limit to useful selectivity in code work is around 100 or 200 cycles for hand-key speeds, but this much selectivity requires good stability in both transmitter and receiver, and a slow receiver tuning rate for ease of operation.

Single-Signal Effect

In heterodyne c.w. reception with a superheterodyne receiver, the beat oscillator is set to give a suitable audio-frequency beat note when the incoming signal is converted to the intermediate frequency. For example, the beat oscillator may be set to 454 kc. (the i.f. being 455 kc.) to give a 1000-cycle beat note. Now, if an interfering signal appears at 453 kc., or if the receiver is tuned to heterodyne the incoming signal to 453 kc., it will also be heterodyned by the beat oscillator to produce a 1000cycle beat. Hence every signal can be tuned in at two places that will give a 1000-cycle beat (or any other low audio frequency). This audiofrequency image effect can be reduced if the i.f. selectivity is such that the incoming signal, when heterodyned to 453 kc., is attenuated to a very low level.

When this is done, tuning through a given signal will show a strong response at the desired beat note on one side of zero beat only, instead of the two beat notes on either side of zero beat characteristic of less-selective reception, hence the name: single-signal reception.

The necessary selectivity is not obtained with nonregenerative amplifiers using ordinary tuned circuits unless a low i.f. or a large number of circuits is used.

Regeneration

Regeneration can be used to give a single-signal effect, particularly when the i.f. is 455 kc. or lower. The resonance curve of an i.f. stage at critical regeneration (just below the oscillating point) is extremely sharp, a bandwidth of 1 kc. at 10 times down and 5 kc. at 100 times down being obtainable in one stage. The audio-frequency image of a given signal thus can be re-

duced by a factor of nearly 100 for a 1000-cycle beat note (image 2000 cycles from resonance).

Regeneration is easily introduced into an i.f. amplifier by providing a small amount of capacity coupling between grid and plate. Bringing a short length of wire, connected to the grid, into the vicinity of the plate lead usually will suffice. The feedback may be controlled by the regular cathode-resistor gain control. When the i.f. is regenerative, it is preferable to operate the tube at reduced gain (high bias) and depend on regeneration to bring up the signal strength. This prevents overloading and increases selectivity.

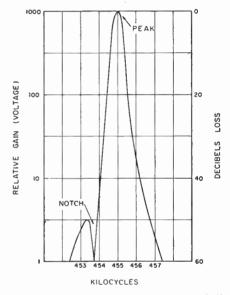


Fig. 5-24—Typical response curve of a crystal filter. The notch can be moved to the other side of the response peak by adjustment of the "phasing" control. With the above curve, setting the b.f.o. at 454 kc. would give goad single-signal c.w. reception.

The higher selectivity with regeneration reduces the over-all response to noise generated in the earlier stages of the receiver, just as does high selectivity produced by other means, and therefore improves the signal-to-noise ratio. However, the regenerative gain varies with signal strength, being less on strong signals.

Crystal-Filters; Phasing

Probably the simplest means for obtaining high selectivity is by the use of a piezoelectric quartz crystal as a selective filter in the i.f. amplifier. Compared to a good tuned circuit, the Q of such a crystal is extremely high. The crystal is ground resonant at the i.f. and used as a selective coupler between i.f. stages.

Fig. 5-24 gives a typical crystal-filter reso-

nance curve. For single-signal reception, the audio-frequency image can be reduced by 50 db. or more. Besides practically eliminating the a.f. image, the high selectivity of the crystal filter provides good discrimination against adjacent signals and also reduces the noise.

Two crystal-filter circuits are shown in Fig. 5-25. The circuit at A (or a variation) is found in many of the current communications receivers. The crystal is connected in one side of a bridge circuit, and a phasing capacitor, C_1 is connected in the other. When C_1 is set to balance the crystal-holder capacitance, the resonance curve of the filter is practically symmetrical; the crystal acts as a series-resonant circuit of very high Q and allows signals over a narrow band of frequencies to pass through to the following tube. More or less capacitance at C_1 introduces the "rejection notch" of Fig. 5-24 (at 453.7 kc. as drawn). The Q of the load circuit for the filter is adjusted by the setting of R_1 , which in turn varies the bandwidth of the filter from "sharp" to a bandwidth suitable for phone reception. Some of the components of this filter are special and not generally available to amateurs.

BAND-PASS FILTERS

A single high-Q circuit (e.g., a quartz crystal or regenerative stage) will give adequate single-signal reception under most circumstances. For phone reception, however, either single-sideband or a.m., a band-pass characteristic is more desirable. A band-pass filter is one that passes without unusual attenuation a desired band of frequencies and rejects signals outside this band. A good band-pass filter for single-sideband reception might have a bandwidth of 2500 cycles at -6 db. and 10 kc. at -60 db.; a filter for a.m. would require twice these bandwidths if both sidebands were to be accommodated.

The simplest band-pass crystal filter is one using two crystals, as in Fig. 5-25B. The two crystals are separated slightly in frequency. If the frequencies are only a few hundred cycles apart the characteristic is a good one for c.w. reception. With crystals about 2 kc. apart, a reasonable phone characteristic is obtained. Fig. 5-1 shows a selectivity characteristic of an amplifier with a bandpass (at -6 db.) of 2.4 kc., which is typical of what can be expected from a two-crystal band-pass filter. Compare this with the single-crystal characteristic of Fig. 5-24.

More elaborate crystal filters, using four and six crystals, will give reduced bandwidth at -60 db. without decreasing the bandwidth at -6 db. The resulting increased "skirt selectivity" gives better rejection of adjacent-channel signals. "Crystal-lattice" filters of this type are available commercially for frequencies up to 10 Mc. or so, and they have also been built by amateurs from inexpensive transmitting-type crystals. (See Vester, "Surplus-Crystal High-Frequency Filters," QST, January, 1959; Healey, "High-Frequency Crystal Filters for S.S.B.," QST, October, 1960.)

"Mechanical" filters can be built at frequen-

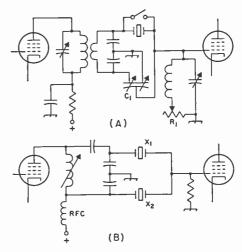


Fig. 5-25—A variable-selectivity crystal filter (A) and a band-pass crystal filter (B).

cies below 1 Mc. These are made up of three sections: an input transducer, a mechanicallyresonant filter section, and an output transducer. The transducers use the principle of magnetostriction to convert the electrical signal to mechanical energy and back again. The mechanically-resonant section consists of carefullymachined metal disks supported and coupled by thin rods. Each disk has a resonant frequency dependent upon the material and its dimensions, and the effective Q of a single disk may be in excess of 2000. Consequently a mechanical filter can be built for either narrow or broad bandpass with a nearly rectangular curve. Mechanical filters are available commercially and are used in both receivers and single-sideband transmitters.

The signal-handling capability of a mechanical filter is limited by the magnetic circuits to from 2 to 15 volts r.m.s., a limitation that is of no practical importance provided it is recognized and provided for. Crystal filters are limited in their signal-handling ability only by the voltage breakdown limits, which normally would not be reached before the preceding amplifier tube was overloaded. A more serious practical consideration in the use of any high-selectivity component is the prevention of coupling "around" the filter (coupling from input to output outside the filter), which can only degrade the action of the filter.

Band-pass filters can also be made by using a number of high-Q inductance-and-capacitance circuits, but their use is generally restricted to frequencies around 100 kc. At higher frequencies it is easier to get desirable selectivity by other means.

Q Multiplier

The "Q Multiplier" is a stable regenerative stage that is connected in parallel with one of the i.f. stages of a receiver. In one condition it narrows the bandwidth and in the other condi-

tion it produces a sharp "null" or rejection notch. A "tuning" adjustment controls the frequency of the peak or null, moving it across the normal pass band of the receiver i.f. amplifier. The shape of the peak or null is always that of a single tuned circuit (Fig. 2-50) but the effective Q is adjustable over a wide range. A Q Multiplier is most effective at an i.f. of 500 kc. or less; at higher frequencies the rejection notch becomes wide enough (measured in cycles per second) to reject a major portion of a phone signal. Within its useful range, however, the Q Multiplier will reject an interfering carrier without degrading the quality of the desired signal

In the "peak" condition the Q Multiplier can be made to oscillate by advancing the "peak" (regeneration) control far enough, and in this condition it can be made to serve as a beat-frequency oscillator. However, it cannot be made to serve as a selective element and as a b.f.o. at the same time. Some inexpensive receivers may combine either a Q Multiplier or some other form of regeneration with the b.f.o. function, and the reader is advised to check carefully any inexpensive receiver he intends to buy that offers a regenerative type of selectivity, in order to make sure that the selectivity is available when the b.f.o. is turned on.

Vacuum-tube versions of the Q Multiplier for 455-kc. i.f. amplifiers are available in kit form; a transistorized version is described later in this chapter. A Q Multiplier will be of no use on c.w. or s.s.b. reception when used with a receiver that employs an oscillating i.f. stage for the b.f.o. Some of the inexpensive "communications" receivers are of this type.

Tee Notch Filter

At low intermediate frequencies (50 – 100 kc.) the T notch filter of Fig. 5-26 will provide a sharp tunable null without an extra vacuum tube.

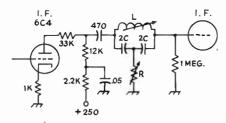


Fig. 5-26—Typical T-notch filter, to provide a sharp rejection notch at a low i.f. Adjustment of L changes the frequency of the notch; adjustment of R controls the depth.

The inductor L resonates with C at the rejection frequency, and when $R=4X_{\rm L}/Q$ the rejection is maximum. ($X_{\rm L}$ is the coil reactance and Q is the coil Q). In a typical 50-kc. circuit, C might be 3900 $\mu\mu{\rm f.}$, making L approximately 2.6 mh. When R is greater than the maximum-

attenuation value, the circuit still provides some rejection, and in use the inductor is detuned or shorted out when the rejection is not desired.

At higher frequencies, the T-notch filter is not sharp enough with available components to reject only a narrow band of frequencies.

Additional I.F. Selectivity

Many commercial communications receivers, and particularly the older ones, do not have sufficient selectivity for amateur use, and their performance can be improved by additional i.f. selectivity. One method is to loosely couple a BC-453 aircraft receiver (war surplus, tuning 190 to 550 kc.) to the front end of the 455-kc. i.f. amplifier in the communications receiver and use the resultant output of the BC-453. The aircraft receiver uses an 85-kc. i.f. amplifier that is sharp for voice work (6.5 kc. wide at -60 db.) and it helps considerably in backing up single-crystal filters for improved c.w. recention.

The BC-453—sometimes called "The Poor Man's Q-Fiver"—uses 12-volt heater tubes and is designed for 24-volt operation. If a 24-volt transformer is available, no wiring changes will be necessary. If a 12-volt transformer is available, the heaters can be rewired. It is usually less expensive to obtain the proper transformer than it is to buy 6.3-volt tubes for the receiver. Any plate-voltage source of 125 to 250 volts at 40 to 80 ma. will be adequate for the B+ supply. A b.f.o. switch and audio and i.f. gain controls should be added to the BC-453 before it is used with the short-wave receiver. Its performance can be checked by tuning in aircraft beacons or low-frequency broadcast stations.

Maximum selectivity will be obtained from the BC-453 when the plungers in the i.f. cans, accessible by unscrewing the caps, are pulled up as far as they will go.

The BC-453 can be coupled to the receiver through a length of shielded wire or small coaxial line. The inner conductor is connected to the antenna post of the BC-453 and the shield is connected to the case. The shield should be connected at the other end to the short-wave receiver chassis, and the inner conductor, suitably insulated, should be wrapped once or twice around the plate pin of the first i.f. amplifier tube in the short-wave receiver. It may require a little experimentation before the proper coupling is obtained; the objective is enough coupling so that the short-wave receiver noise will mask any BC-453 noise, but not so much coupling that the BC-453 is overloaded. Reports of poor performance when using the BC-453 have practically always reduced to overload of the surplus aircraft receiver through too much coupling or coupling at a high-level point in the short-wave receiver.

If a BC-453 is not available, one can still enjoy the benefits of improved selectivity. It is only necessary to heterodyne to a lower frequency the 455-kc. signal existing in the receiver i.f. amplifier and then rectify it after passing it through the sharp low-frequency amplifier. The J. W. Miller Company offers 50-kc. transformers for this application.

RADIO-FREQUENCY AMPLIFIERS

While selectivity to reduce audio-frequency images can be built into the i.f. amplifier, discrimination against radio-frequency images can only be obtained in tuned circuits or other selective elements ahead of the first mixer or converter stage. These tuned circuits are usually used as the coupling networks for one or more vacuum tubes or transistors, and the combinations of circuits and amplifying devices are called radio-frequency amplifiers. The tuned circuits contribute to the r.f. image rejection and the amplifying device(s) determines the noise figure of the receiver.

Knowing the Q of the coil in each tuned circuit between the antenna and the first mixer or converter stage, the image rejection capability can be computed by using the chart in Fig. 2-50. The Q of the input tuned circuit (coupled to the antenna) should be taken as about one-half the unloaded Q of that circuit, and the Q of any other tuned circuit can be assumed to be the unloaded Q to a first approximation (the vacuum tubes will reduce the circuit Q to some extent, especially at 14 Mc. and higher).

In general, receivers with an i.f. of 455 kc. can be expected to have some noticeable image response at 14 Mc. and higher if there are only two tuned circuits (one r.f. stage) ahead of the mixer or converter. Regeneration in the r.f. amplifier will reduce image response, but regeneration usually requires frequent readjustment when tuning across a band. Regeneration is, however, a useful device for improving the selectivity of an r.f. amplifier without requiring a multiplicity of tuned circuits; a practical example will be found later in this chapter.

With three tuned circuits between the antenna and the first mixer, and an i.f. of 455 kc., no images should be encountered up to perhaps 25 Mc. Four tuned circuits or more will eliminate any images at 28 Mc. when an i.f. of 455 kc. is used.


Obviously, a better solution to the r.f. selectivity problem (elimination of image response) is to use an i.f. higher than 455 kc., and most modern receivers use an i.f. of 1600 kc. or higher. The owner of a receiver with a 455-kc i.f. amplifier can enjoy image-free reception on the higher frequencies by using a crystal-controlled converter ahead of the receiver and utilizing the receiver as a "tunable i.f. amplifier" at 3.5 or 7.0 Mc.

For best selectivity r.f. amplifiers should use high-Q circuits and tubes with high input and output resistance. Variable- μ pentodes are practically always used, although triodes (neutralized or otherwise connected so that they won't oscillate) are often used on the higher frequencies because they introduce less noise. However, their lower plate resistance will load the tuned circuits. Pentodes are better where maximum im-

age rejection is desired, because they have less loading effect on the tuned circuits.

Transistor R. F. Amplifier

A typical r.f. amplifier circuit using a 2N370 transistor is shown in Fig. 5-27. Since it is desirable to maintain a reasonable Q in the tuned circuits, to reduce r.f. image response, the base and collector are both tapped down on their tuned circuits. An alternative method, using low-impedance inductive coupling, is shown in Fig. 5-27B; this method is sometimes easier to adjust than the taps illustrated in Fig. 5-27A. The tuned circuits, L_1C_1 and L_2C_2 , should resonate at the operating frequency, and they should be mounted or shielded to eliminate inductive coupling between each other.

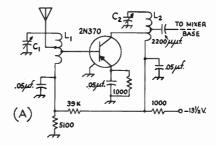

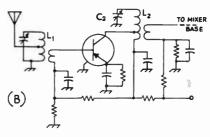


Fig. 5-27—Transistor r.f. amplifier circuit. The low-impedance connections to the base and collector can be
 (A) taps on the inductors or (B) low-impedance coupling links. L₁C₁, L₂C₂—Resonant at signal frequency.

FEEDBACK

Feedback giving rise to regeneration and oscillation can occur in a single stage or it may appear as an over-all feedback through several stages that are on the same frequency. To avoid feedback in a single stage, the output must be isolated from the input in every way possible, with the vacuum tube furnishing the only coupling between the two circuits. An oscillation can be obtained in an r.f. or i.f. stage if there is any undue capacitive or inductive coupling between output and input circuits, if there is too high an impedance between cathode and ground or screen and ground, or if there is any appreciable impedance through which the grid and plate currents can flow in common. This means

110

good shielding of coils and tuning capacitors in r.f. and i.f. circuits, the use of good bypass capacitors (mica or ceramic at r.f., paper or ceramic at i.f.), and returning all bypass capacitors (grid, cathode, plate and screen) for a given stage with short leads to one spot on the chassis. When single-ended tubes are used, the screen or cathode bypass capacitor should be mounted across the socket, to serve as shield between grid and plate pins. Less care is required as the frequency is lowered, but in high-impedance circuits, it is sometimes necessary to shield grid and plate leads and to be careful not to run them close together.

To avoid over-all feedback in a multistage amplifier, attention must be paid to avoid running any part of the output circuit back near the input circuit without first filtering it carefully. Since the signal-carrying parts of the circuit (the "hot" grid and plate leads) can't be filtered, the best design for any multistage amplifier is a straight line, to keep the output as far away from the input as possible. For example, an r.f. amplifier might run along a chassis in a straight line, run into a mixer where the frequency is changed, and then the i.f. amplifier could be run back parallel to the r.f. amplifier, provided there was a very large frequency difference between the r.f. and the i.f. amplifiers. However, to avoid any possible coupling, it would be better to run the i.f. amplifier off at right angles to the r.f.amplifier line, just to be on the safe side. Good shielding is important in preventing over-all oscillation in high-gain-per-stage amplifiers, but it becomes less important when the stage gain drops to a low value. In a high-gain amplifier, the power leads (including the heater circuit) are common to all stages, and they can provide the over-all coupling if they aren't properly filtered. Good bypassing and the use of series isolating resistors will generally eliminate any possibility of coupling through the power leads. R.f. chokes, instead of resistors, are used in the heater leads where necessary.

CROSS-MODULATION

Since a one- or two-stage r.f. amplifier will have a bandwidth measured in hundreds of kc. at 14 Mc. or higher, strong signals will be amplified through the r.f. amplifier even though it is not tuned exactly to them. If these signals are strong enough, their amplified magnitude may be measurable in volts after passing through several r.f. stages. If an undersired signal is strong enough after amplification in the r.f. stages to shift the operating point of a tube (by driving the grid into the positive region), the undesired signal will modulate the desired signal. This effect is called cross-modulation, and is often encountered in receivers with several r.f. stages working at high gain. It shows up as a superimposed modulation on the signal being listened to, and often the effect is that a signal can be tuned in at several points. It can be reduced or eliminated by greater selectivity in the antenna and r.f. stages (difficult to obtain), the

HIGH-FREQUENCY RECEIVERS

use of variable- μ tubes in the r.f. amplifier, reduced gain in the r.f. amplifier, or reduced antenna input to the receiver. The 6BJ6, 6BA6 and 6DC6 are recommended for r.f. amplifiers where cross-modulation may be a problem.

A receiver designed for minimum cross-modulation will use as little gain as possible ahead of the high-selectivity stages, to hold strong unwanted signals below the cross-modulation point. Cross-modulation often takes place in double-conversion superlieterodynes at the second converter stage because there is insufficient selectivity up to this point and at this point the signals have quite appreciable amplitudes. Whenever interference drops out quite suddenly with a reduction in the setting of the gain control, cross-modulation should be suspected. Normally, of course, the interference would reduce in amplitude in proportion to the desired signal as the gain setting is reduced.

Gain Control

To avoid cross-modulation and other overload effects in the mixer and r.f. stages, the gain of the r.f. stages is usually made adjustable. This is accomplished by using variable-µ tubes and varying the d.c. grid bias, either in the grid or cathode circuit. If the gain control is automatic, as in the case of a.g.c., the bias is controlled in the grid circuit. Manual control of r.f. gain is generally done in the cathode circuit. A typical r.f. amplifier stage with the two types of gain control is shown in schematic form in Fig. 5-28. The a.g.c. control voltage (negative) is derived from rectified carrier or signal at the detector before the audio amplifier, or in the case of a c.w. or s.s.b. receiver it can be derived from rectified audio. The manual gain control voltage (positive with respect to chassis) is usually derived from a potentiometer across the B+ supply, since the bias can be changed even though little plate current is being drawn.

Tracking

In a receiver with no r.f. stage, it is no incon-

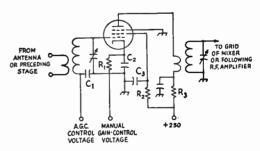


Fig. 5-28—Typical radia-frequency amplifier circuit far a superheteradyne receiver. Representative values far campanents are as fallaws:

 C_1 ta $C_4-0.01~\mu f.$ belaw 15 Mc., 0.001 $\mu f.$ at 30 Mc. $R_1,~R_2-See$ Table 5-II. R_3-1800 ohms.

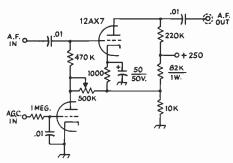


Fig. 5-29—A practical squelch circuit for cutting off the receiver output when no signal is present.

venience to adjust the high-frequency oscillator and the mixer circuit independently, because the mixer tuning is broad and requires little attention over an amateur band. However, when r.f. stages are added ahead of the mixer, the r.f. stages and mixer will require retuning over an entire amateur band. Hence most receivers with one or more r.f. stages gang all of the tuning controls to give a single-tuning-control receiver. Obviously there must exist a constant difference in frequency (the i.f.) between the oscillator and the mixer/r.f. circuits, and when this condition is achieved the circuits are said to track.

In amateur-band receivers, tracking is simplified by choosing a bandspread circuit that gives practically straight-line-frequency tuning (equal frequency change for each dial division), and then adjusting the oscillator and mixer tuned circuits so that both cover the same total number of kilocycles. For example, if the i.f. is 455 kc. and the mixer circuit tunes from 7000 to 7300 kc. between two given points on the dial, then the oscillator must tune from 7455 to 7755 kc. between the same two dial readings. With

the bandspread arrangement of Fig. 5-9A, the tuning will be practically straight-line-frequency if C_2 (bandset) is 4 times or more the maximum capacity of C_1 (bandspread), as is usually the case for strictly amateur-band coverage. C_1 (semicircular plates).

Squelch Circuits

An audio squelch circuit is one that cuts off the receiver output when no signal is coming through the receiver. It is useful in mobile or net work where the no-signal receiver noise may be as loud as the signal, causing undue operator fatigue during no-signal periods.

A practical squelch circuit is shown in Fig. 5-29. A dual triode (12AX7) is used as an amplifier and as a control tube. When the a.g.c. voltage is low or zero, the lower (control) triode draws plate current. The consequent voltage drop across the adjustable resistor in the plate circuit cuts off the upper (amplifier) triode and no signal or noise is passed. When the a.g.c. voltage rises to the cut-off value of the control triode, the tube no longer draws current and the bias on the amplifier triode is now only its normal operating bias, furnished by the 1000-ohm resistor in the cathode circuit. The tube now functions as an ordinary amplifier and passes signals. The relation between the a.g.c. voltage and the signal turn-on point is adjusted by varying the resistance in the plate circuit of the control triode.

Connections to the receiver consist of two a.f. lines (shielded), the a.g.c. lead, and chassis ground. The squelch circuit is normally inserted between detector output and the audio volume control of the receiver. Since the circuit is used in the low-level audio point, its plate supply must be free from a.c. or objectionable hum will be introduced.

IMPROVING RECEIVER SENSITIVITY

The sensitivity (signal-to-noise ratio) of a receiver on the higher frequencies above 20 Mc. is dependent upon the band width of the receiver and the noise contributed by the "front end" of the receiver. Neglecting the fact that image rejection may be poor, a receiver with no r.f. stage is generally satisfactory, from a sensitivity point, in the 3.5- and 7-Mc. bands. However, as the frequency is increased and the atmospheric noise becomes less, the advantage of a good "front end" becomes apparent. Hence at 14 Mc. and higher it is worth while to use at least one stage of r.f. amplification ahead of the first detector for best sensitivity as well as image rejection. The multigrid converter tubes have very poor noise figures, and even the best pentodes and triodes are three or four times noisier when used as mixers than they are when used as amplifiers.

If the purpose of an r.f. amplifier is to improve the receiver noise figure at 14 Mc. and higher, a high- g_m pentode or triode should be used. Among the pentodes, the best tubes are the 6AH6, 6AK5 and the 6BZ6, in the order named. The 6AK5 takes the lead around 30 Mc. The 6J4, 6J6, and triode-connected 6AK5 are the best of the triodes. For best noise figure, the antenna circuit should be coupled a little heavier than optimum. This cannot give best selectivity in the antenna circuit, so it is futile to try to maximize sensitivity and selectivity in this circuit.

When a receiver is satisfactory in every respect (stability and selectivity) except sensitivity on 14 through 30 Mc., the best solution for the amateur is to add a preamplifier, a stage of r.f. amplification designed expressly to improve the sensitivity. If image rejection is lacking in the receiver, some selectivity should be built into the preamplifier (it is then called a preselector). If, however, the receiver operation is poor on the higher frequencies but is satisfactory on the lower ones, a "converter" is the best solution.

Some commercial receivers that appear to lack sensitivity on the higher frequencies can be improved simply by tighter coupling to the antenna. This can be accomplished by changing the antenna feed line to the right value (as determined from the receiver instruction book) or by using a simple matching device as described later in this chapter. Overcoupling the input circuit will often improve sensitivity but it will, of course, always reduce the image-rejection contribution of the antenna circuit.

Regeneration

Regeneration in the r.f. stage of a receiver (where only one stage exists) will often improve the sensitivity because the greater gain it provides serves to mask more completely the first-detector noise, and it also provides a measure of automatic matching to the antenna through tighter coupling. However, accurate ganging becomes a problem, because of the increased selectivity of the regenerative r.f. stage, and the receiver almost invariably becomes a two-handed-tuning device. Regeneration should not be overlooked as an expedient, however, and amateurs have used it with considerable success.

HIGH-FREQUENCY RECEIVERS

High- g_m tubes are the best as regenerative amplifiers, and the feedback should not be controlled by changing the operating voltages (which should be the same as for the tube used in a highgain amplifier) but by changing the loading or the feedback coupling. This is a tricky process and another reason why regeneration is not too widely used.

Gain Control

In a receiver front end designed for best signal-to-noise ratio, it is advantageous in the reception of weak signals to eliminate the gain control from the first r.f. stage and allow it to run "wide open" all of the time. If the first stage is controlled along with the i.f. (and other r.f. stages, if any), the signal-to-noise ratio of the receiver will suffer. As the gain is reduced, the g_m of the first tube is reduced, and its noise figure becomes higher. A good receiver might well have two gain controls, one for the first r.f. stage and another for the i.f. (and any other r.f.) stages. The first r.f. stage gain would be reduced only for extremely strong signals.

TUNING A RECEIVER

C.W. Reception

For making code signals audible, the beat oscillator should be set to a frequency slightly different from the intermediate frequency. To adjust the beat-oscillator frequency, first tune in a moderately weak but steady carrier with the beat oscillator turned off. Adjust the receiver tuning for maximum signal strength, as indicated by maximum hiss. Then turn on the beat oscillator and adjust its frequency (leaving the receiver tuning unchanged) to give a suitable beat note. The beat oscillator need not subsequently be touched, except for occasional checking to make certain the frequency has not drifted from the initial setting. The b.f.o. may be set on either the high- or low-frequency side of zero beat.

The best receiver condition for the reception of code signals will have the first r.f. stage running at maximum gain, the following r.f., mixer and i.f. stages operating with just enough gain to maintain the signal-to-noise ratio, and the audio gain set to give comfortable headphone or speaker volume. The audio volume should be controlled by the audio gain control, not the i.f. gain control. Under the above conditions, the selectivity of the receiver is being used to best advantage, and cross-modulation is minimized. It precludes the use of a receiver in which the gains of the r.f. and i.f. stages are controlled simultaneously.

Tuning with the Crystal Filter

If the receiver is equipped with a crystal filter the tuning instructions in the preceding paragraph still apply, but more care must be used both in the initial adjustment of the beat oscillator and in tuning. The beat oscillator is set as described above, but with the crystal filter set at its sharpest position, if variable selectivity is available. The initial adjustment should be made with the phasing control in an intermediate position. Once adjusted, the beat oscillator should be left set and the receiver tuned to the other side of zero beat (audio-frequency image) on the same signal to give a beat note of the same tone. This beat will be considerably weaker than the first, and may be "phased out" almost completely by careful adjustment of the phasing control. This is the adjustment for normal operation; it will be found that one side of zero beat has practically disappeared, leaving maximum response on the other.

An interfering signal having a beat note differing from that of the a.f. image can be similarly phased out, provided its frequency is not too near the desired signal.

Depending upon the filter design, maximum selectivity may cause the dots and dashes to lengthen out so that they seem to "run together." It must be emphasized that, to realize the benefits of the crystal filter in reducing interference, it is necessary to do all tuning with it in the circuit. Its high selectivity often makes it difficult to find the desired station quickly, if the filter is switched in only when interference is present.

A.M. Phone Reception

In reception of a.m. phone signals, the normal procedure is to set the r.f. and i.f. gain at maximum, switch on the a.g.c., and use the audio gain control for setting the volume. This insures maximum effectiveness of the a.g.c. system in compensating for fading and maintaining constant audio output on either strong or weak signals. On occasion a strong signal close to the

Alignment and Servicing

frequency of a weaker desired station may take control of the a.g.c., in which case the weaker station may disappear because of the reduced gain. In this case better reception may result if the a.g.c. is switched off, using the manual r.f. gain control to set the gain at a point that prevents "blocking" by the stronger signal.

When receiving an a.m. signal on a frequency within 5 to 20 kc. from a single-sideband signal it may also be necessary to switch off the a.g.c. and resort to the use of manual gain control, unless the receiver has excellent skirt selectivity. No ordinary a.g.c. circuit can handle the syllabic bursts of energy from the sideband station, but there are special circuits that will.

A crystal filter will help reduce interference in phone reception. Although the high selectivity cuts sidebands and reduces the audio output at the higher audio frequencies, it is possible to use quite high selectivity without destroying intelligibility. As in code reception, it is advisable to do all tuning with the filter in the circuit. Variable-selectivity filters permit a choice of selectivity to suit interference conditions.

An undesired carrier close in frequency to a desired carrier will heterodyne with it to produce a beat note equal to the frequency difference. Such a heterodyne can be reduced by adjustment of the phasing control in the crystal filter

A tone control often will be of help in reducing the effects of high-pitched heterodynes, sideband splatter and noise, by cutting off the higher audio frequencies. This, like sideband cutting with high selectivity circuits, reduces naturalness.

Spurious Responses

Spurious responses can be recognized without a great deal of difficulty. Often it is possible to identify an image by the nature of the transmitting station, if the frequency assignments applying to the frequency to which the receiver is tuned are known. However, an image also can be recognized by its behavior with tuning. If the signal causes a heterodyne beat note with the desired signal and is actually on the same frequency, the beat note will not change as the receiver is tuned through the signal; but if the interfering signal is an image, the beat will vary in pitch as the receiver is tuned. The beat oscillator in the receiver must be turned off for this test. Using a crystal filter with the beat oscillator on, an image will peak on the side of zero beat opposite that on which desired signals peak.

Harmonic response can be recognized by the "tuning rate," or movement of the tuning dial required to give a specified change in beat note. Signals getting into the i.f. via high-frequency oscillator harmonics tune more rapidly (less dial movement) through a given change in beat note than do signals received by normal means.

Harmonics of the beat oscillator can be recognized by the tuning rate of the beat-oscillator pitch control. A smaller movement of the control will suffice for a given change in beat note than that necessary with legitimate signals. In poorly-designed or inadequately-shielded and -filtered receivers it is often possible to find b.f.o. harmonics below 2 Mc., but they should be very weak or non-existent at higher frequencies.

ALIGNMENT AND SERVICING OF SUPERHETERODYNE RECEIVERS

I.F. Alignment

A calibrated signal generator or test oscillator is a useful device for alignment of an i.f. amplifier. Some means for measuring the output of the receiver is required. If the receiver has a tuning meter, its indications will serve. Lacking an S meter, a high-resistance voltmeter or a vacuum-tube voltmeter can be connected across the second-detector load resistor, if the second detector is a diode. Alternatively, if the signal generator is a modulated type, an a.c. voltmeter can be connected across the primary of the transformer feeding the speaker, or from the plate of the last audio amplifier through a 0.1-µf. blocking capacitor to the receiver chassis. Lacking an a.c. voltmeter, the audio output can be judged by ear, although this method is not as accurate as the others. If the tuning meter is used as an indication, the a.g.c. of the receiver should be turned on, but any other indication requires that it be turned off. Lacking a test oscillator, a steady signal tuned through the input of the receiver (if the job is one of just touching up the i.f. amplifier) will be suitable. However, with no oscillator and tuning an amplifier for the first time, one's only recourse is to try to peak the i.f. transformers on "noise," a difficult task if the transformers are badly off resonance, as they are apt to be. It would be much better to haywire together a simple oscillator for test purposes.

Initial alignment of a new i.f. amplifier is as follows: The test oscillator is set to the correct frequency, and its output is coupled through a capacitor to the grid of the last i.f. amplifier tube. The trimmer capacitors of the transformer feeding the second detector are then adjusted for maximum output, as shown by the indicating device being used. The oscillator output lead is then clipped on to the grid of the next-to-the-last i.f. amplifier tube, and the second-from-the-last transformer trimmer adjustments are peaked for maximum output. This process is continued, working back from the second detector, until all of the i.f. transformers have been aligned. It will be necessary to reduce the output of the test oscillator as more of the i.f. amplifier is brought into use. It is desirable in all cases to use the minimum signal that will give useful output readings. The i.f. transformer in the plate circuit of the mixer is aligned with the signal introduced to the grid of the mixer. Since the tuned circuit feeding the mixer grid may have a very low impedance at the i.f., it may be necessary to boost the test generator output or to disconnect the tuned circuit temporarily from the mixer grid.

If the i.f. amplifier has a crystal filter, the filter should first be switched out and the alignment carried out as above, setting the test oscillator as closely as possible to the crystal frequency. When this is completed, the crystal should be switched in and the oscillator frequency varied back and forth over a small range either side of the crystal frequency to find the exact frequency, as indicated by a sharp rise in output. Leaving the test oscillator set on the crystal peak, the i.f. trimmers should be realigned for maximum output. The necessary readjustment should be small. The oscillator frequency should be checked frequently to make sure it has not drifted from the crystal peak.

A modulated signal is not of much value for aligning a crystal-filter i.f. amplifier, since the high selectivity cuts sidebands and the results may be inaccurate if the audio output is used as the tuning indication. Lacking the a.g.c. tuning meter, the transformers may be conveniently aligned by ear, using a weak unmodulated signal adjusted to the crystal peak. Switch on the beat oscillator, adjust to a suitable tone, and align the i.f. transformers for maximum audio output.

An amplifier that is only slightly out of alignment, as a result of normal drift or aging, can be realigned by using any steady signal, such as a local broadcast station, instead of the test oscillator. One's 100-kc. standard makes an excellent signal source for "touching up" an i.f. amplifier. Allow the receiver to warm up thoroughly, tune in the signal, and trim the i.f. for maximum output.

If you bought your receiver instead of making it, be sure to read the instruction book carefully before attempting to realign the receiver. Most instruction books include alignment details, and any little special tricks that are peculiar to the receiver will also be described in detail.

R.F. Alignment

The objective in aligning the r.f. circuits of a gang-tuned receiver is to secure adequate tracking over each tuning range. The adjustment may be carried out with a test oscillator of suitable frequency range, with harmonics from your 100-kc. standard or other known oscillator, or even on noise or such signals as may be heard. First set the tuning dial at the high-frequency end of the range in use. Then set the test oscillator to the frequency indicated by the receiver dial. The test-oscillator output may be connected to the antenna terminals of the receiver for this test. Adjust the oscillator trimmer capacitor in the receiver to give maximum response on the test-oscillator signal, then reset the receiver

dial to the low-frequency end of the range. Set the test-oscillator frequency near the frequency indicated by the receiver dial and tune the test oscillator until its signal is heard in the receiver. If the frequency of the signal as indicated by the test-oscillator calibration is higher than that indicated by the receiver dial, more inductance (or more capacity in the tracking capacitor) is needed in the receiver oscillator circuit; if the frequency is lower, less inductance (less tracking capacity) is required in the receiver oscillator. Most commericial receivers provide some means for varying the inductance of the coils or the capacity of the tracking capacitor, to permit aligning the receiver tuning with the dial calibration. Set the test oscillator to the frequency indicated by the receiver dial, and then adjust the tracking capacity or inductance of the receiver oscillator coil to obtain maximum response. After making this adjustment, recheck the highfrequency end of the scale as previously described. It may be necessary to go back and forth between the ends of the range several times before the proper combination of inductance and capacity is secured. In many cases, better overall tracking will result if frequencies near but not actually at the ends of the tuning range are selected, instead of taking the extreme dial set-

After the oscillator range is properly adjusted, set the receiver and test oscillator to the high-frequency end of the range. Adjust the mixer trimmer capacitor for maximum hiss or signal, then the r.f. trimmers. Reset the tuning dial and test oscillator to the low-frequency end of the range, and repeat; if the circuits are properly designed, no change in trimmer settings should be necessary. If it is necessary to increase the trimmer capacity in any circuit, more inductance is needed; conversely, if less capacity resonates the circuit, less inductance is required.

Tracking seldom is perfect throughout a tuning range, so that a check of alignment at intermediate points in the range may show it to be slightly off. Normally the gain variation will be small, however, and it will suffice to bring the circuits into line at both ends of the range. If most reception is in a particular part of the range, such as an amateur band, the circuits may be aligned for maximum performance in that region, even though the ends of the frequency range as a whole may be slightly out of alignment.

Oscillation in R.F. or I.F. Amplifiers

Oscillation in high-frequency amplifier and mixer circuits shows up as squeals or "birdies" as the tuning is varied, or by complete lack of audible output if the oscillation is strong enough to cause the a.g.c. system to reduce the receiver gain drastically. Oscillation can be caused by poor connections in the common ground circuits. Inadequate or defective bypass capacitors in cathode, plate and screen-grid circuits also can cause such oscillation. A metal tube with an ungrounded shell may cause trouble. Improper

Improving Performance

screen-grid voltage, resulting from a shorted or too-low screen-grid series resistor, also may be responsible for such instability.

Oscillation in the i.f. circuits is independent of high-frequency tuning, and is indicated by

a continuous squeal that appears when the gain is advanced with the c.w. beat oscillator on. It can result from defects in i.f.-amplifier circuits. Inadequate screen or plate bypass capacitance is a common cause of such oscillation.

IMPROVING THE PERFORMANCE OF RECEIVERS

Frequently amateurs unjustly criticize a receiver's performance when actually part of the trouble lies with the operator, in his lack of knowledge about the receiver's operation or in his inability to recognize a readily curable fault. The best example of this is a complaint about "lack of selectivity" when the receiver contains an i.f. crystal filter and the operator hasn't bothered to learn how to use it properly. "Lack of sensitivity" may be nothing more than poor alignment of the r.f. and mixer tuning. The cures for these two complaints are obvious, and the details are treated both in this chapter and in the receiver instruction book.

However, many complaints about selectivity, sensitivity, and other points are justified. Inexpensive, and most second-hand, receivers cannot be expected to measure up to the performance standards of some of the current and toppriced receivers. Nevertheless, many amateurs overlook the possibility of improving the performance of these "bargains" (they may or may not be bargains) by a few simple additions or modifications. From time to time articles in QST describe improvements for specific receivers, and it may repay the owner of a newly-acquired second-hand receiver to examine past issues and see if an applicable article was published. The annual index in each December issue is a help in this respect.

Where no applicable article can be found, a few general principles can be laid down. If the complaint is the inability to separate stations, better i.f. (and occasionally audio) selectivity is indicated. The answer is not to be found in better bandspread tuning of the dial as is sometimes erroneously concluded. For code reception the addition of a "Q Multiplier" to the i.f. amplifier is a simple and effective attack; a Q Multiplier is at its best in the region 100 to 900 kc., and higher than this its effectiveness drops off. The Selectoject is a selective audio device based on similar principles. For phone reception the addition of a Q Multiplier will help to reject an interfering carrier, and the use of a BC-453 as a "Q5-er" will add adjacent-channel selectivity.

With the addition of more i.f. selectivity, it may be found that the receiver's tuning rate (number of kc. tuned per dial revolution) is too high, and consequently the tuning with good i.f. selectivity becomes too critical. If this is the case, a 5-to-1 reduction planetary dial drive mechanism may be added to make the tuning rate more favorable. These drives are sold by the larger supply houses and can usually be added to the receiver if a suitable mounting bracket is

made from sheet metal. If there is already some backlash in the dial mechanism, the addition of the planetary drive will magnify its effect, so it is necessary to minimize the backlash before attempting to improve the tuning rate. While this is not possible in all cases, it should be investigated from every angle before giving up. Replacing a small tuning knob with a larger one will add to ease of tuning; in many cases after doing so it will then be desirable or necessary to raise the receiver higher above the table.

If the receiver appears to lack the ability to bring in the weak signals, particularly on the higher-frequency bands, the performance can often be improved by the addition of an antenna coupler (described elsewhere in this chapter); it will always be improved by the addition of a preselector (also described elsewhere in this chapter).

If the receiver shortcoming is inadequate r.f. selectivity, as indicated by r.f. "images" on the higher-frequency bands, a simple antenna coupler will often add sufficient selectivity to cure the trouble. However, if the images are severe, it is likely that a preselector will be required, preferably of the regenerative type. The preselector will also add to the ability of the receiver to detect weak signals at 14 Mc. and higher.

In many of the inexpensive receivers the frequency calibration of the dial is not very accurate. The receiver's usefulness for determining band limits will be greatly improved by the addition of a 100-kc. crystal-controlled frequency standard. These units can be built or purchased complete at very reasonable prices, and no amateur station worthy of the name should be without one

Some receivers that show a considerable frequency drift as they are warming up can be improved by the simple expedient of furnishing more ventilation, by propping up the lid or by drilling extra ventilation holes. In many cases the warm-up drift can be cut in half. A 7-watt 115-volt lamp mounted under the receiver chassis and wired so that it is turned on when the receiver is turned off will maintain the receiver temperature above the room temperature and will reduce the warm-up drift. The auxiliary heat source is also of help in reducing or eliminating the ill effects of condensation in the receiver, where the receiver is used in a damp location.

Receivers that show frequency changes with line-voltage or gain-control variations can be greatly improved by the addition of regulated voltage on the oscillators (high-frequency and b.f.o.) and the screen of the mixer tube. There is usually room in any receiver for the addition of a VR tube of the right rating.

THE "SimpleX Super Mark II" THREE-TUBE RECEIVER

The name of the receiver shown in Figs. 5-30 and 5-33 derives from "simple," "X" for crystal (filter) and "super" for superheterodyne; hence a "simple crystal-filter superheterodyne." It is an improved version of an earlier model (QST, December, 1958), hence the "Mark II." For less than fifty dollars and a few nights at the workbench, this little receiver will allow you to copy practically any c.w. or s.s.b. signal in the 40- or 80-meter band that a much more expensive receiver might bring in. By the throw of a switch you can tune in WWV on 5.0 Mc. for time signals and standard-frequency transmissions.

Referring to the circuit diagram in Fig. 5-31, the receiver is a superheterodyne with an intermediate frequency of 1700 kc. With the h.f. oscillator tuning 5.2. to 5.7 Mc., the 3.5- or 7-Mc. amateur bands can be tuned merely by retuning the input circuit. Since C_2 is large enough to hit the two bands without a coil change, the bandchanging process consists of turning C_2 to the low- or high-capacitance end of its range. To copy WWV at 5 Mc., the oscillator must be tuned to 3.3 Mc., and this is done by switching in (via S_{2A}) a preset capacitor, C_8 , across the oscillator circuit.

The advantage of a two-band receiver of this type is that the absence of coil switching makes it easy to build a stable high-frequency oscillator, and the stability of this oscillator then determines the stability of the receiver. Higher-frequency bands (14, 21 and 28 Mc.) can be listened to by adding a crystal-controlled converter; the construction of such a converter is described later in this chapter.

Selectivity at the i.f. is obtained through the use of a single crystal. This, in conjunction with the regeneration provided by the detector, is sharp enough to provide a fair degee of single-signal c.w. reception and yet is broad enough for copy of an s.s.b. phone signal.

In the detector stage, the pentode section of a 6U8A is used as a regenerative detector, and the triode section serves as the b.f.o. Stray coupling at the socket and in the tube provides adequate injection. The regeneration control is not mounted on the panel because, once set below the threshold of oscillation, it is not touched. The

regeneration is not essential to good c.w. or s.s.b. reception, but it helps considerably on a.m. reception. Audio amplification is obtained from the two triode sections of a 6CG7. The primary of a small output transformer, T_1 , serves as the coupling for high-impedance headphone output, and a small loudspeaker or low-impedance headphones can be connected to the secondary.

The power supply uses a small transformer and two selenium rectifiers in a full-wave voltage-doubling circuit. This is about as inexpensive a power supply as can be built, and it also has the advantages of not occupying much space and not generating much heat.

A switch, S_{1A} , at the input of the receiver is included so that the receiver can be used to listen to one's own transmitter without too severe blocking. Another section of the same switch, S_{1B} , shifts the mixer screen voltage from its operating value to zero, to reduce further the sensitivity of the receiver while one is transmitting. If it reduces it so much that the receiver has too little gain, this section of the switch can be omitted from the circuit and the mixer operated at full screen voltage at all times.

An $8 \times 12 \times 3$ -inch aluminum chassis takes all of the parts without crowding, and the location of the components can be seen in the photographs. The receiver is shown with a 7-inch high standard relay-rack panel, which leaves room at one end of the panel for auxiliary equipment or a small transmitter. If desired, a shorter panel of 32-inch aluminum can be used. The panel is held to the chassis by the two switches and the headphones jack. The tuning capacitor, C3, is mounted on a small aluminum bracket, and the capacitor is driven by a Jackson Brothers Planetary Vernier (Arrow Electronics, N.Y.C.) via a Millen 39016 coupling. Before the bracket is finally fastened to the chassis the capacitor and bracket should be used to locate the center for the vernier hole. It pays to take care in mounting the tuning capacitor and its drive, since a smooth tuning drive is essential to any receiver. A National HRT knob is used to turn the vernier, and a paper scale is made as can be seen in one of the photographs.

Tie points are used liberally throughout the

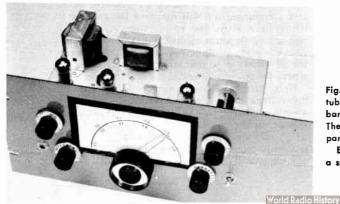


Fig. 5-30—The SimpleX Super receiver uses three dual tubes and a crystal filter to cover the 80- and 40-meter bands, and it can tune to 5 Mc. for copying WWV. The dial scale is made from white paper held to the panel by black tape; the index is clear plastic.

Extra panel space is provided for control circuits or a small transmitter.

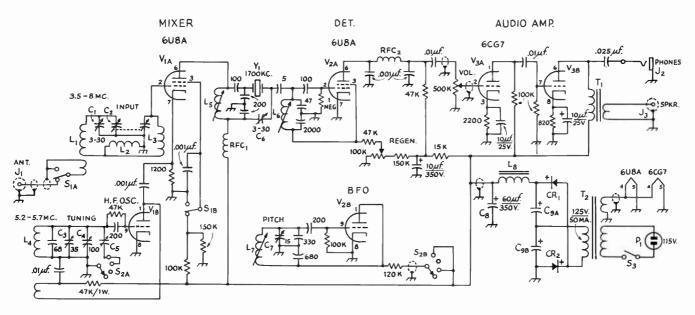


Fig. 5-31—Circuit diagram of the SimpleX Super receiver. Unless otherwise indicated, capacitances are in μμf., resistances are in ohms, resistors are ½ watt. Polarity is shown on electrolytic capacitors, 680 μμf. or less are silver mica or NPO ceramic, 2000-μμf. fixed capacitor is mica. Capacitors specified in decimal-μf. values are ceramic.

 C_1 —3- to 30- $\mu\mu$ f, mica compression trimmer.

C₂-140-140 dual variable (Hammarlund HFD-140).

C₈-35-µµf. midget variable (Hammarlund HF-35).

 C_4 —100- $\mu\mu$ f. midget trimmer (Hammarlund MAPC-100).

 C_5 —180- $\mu\mu$ f, silver mica in parallel with 150- $\mu\mu$ f, mica-

compression trimmer (Arco 424).

 C_6 —3- to 30- $\mu\mu$ f, mica compression trimmer with adjustment screw removed.

 C_7 —15- $\mu\mu$ f. midget variable (Hammarlund HF-15).

C₈-60-\(mu\)f. 350-v. electrolytic (Mallory TC-68 or equiv.).

C₉-40-40-μf. 150-v. electrolytic, negative not common (Mallory TCS-48 or equiv.).

CR₁, CR₂-50-ma, 130-v, selenium rectifier (Tarzian 50 or equiv.).

J₁, J₃-Phono jack.

J₂-Phone jack.

L₁, L₃, L₄,—See Fig. 5-32.

L₂-18 t. No. 22 enam., closewound on ¼-diam. form (1-watt resistor, 100K or more).

L₅, L₆-105-200 μh. shielded inductor (North Hills SE-120-H).

L₇-36-64 µh. shielded inductor (North Hills SE-120-F).

L₈-16-henry 50-ma. filter choke (Knight 62G137 or equiv.).

P₁—A.c. line plug, preferably fused.

S₁-D.p.d.t. togale.

S2-Two-pole 6-position (4 used) rotary switch (Centralab PA-2003 or equiv.).

S₃-S.p.s.t. toggle

RFC₁, RFC₂—1-mh. r.f. choke (Millen J300-1000).

T₁-Small output transformer, 10K plate to voice coil (Stancor A-3879 or equiv.).

T₂-125-v, 50-ma, and 6.3-v, 2-amp, power transformer (Knight 61G411 or equiv.).

Y₁-1700-kc. crystal (International Crystal FA-5 or equiv.) (All radio stores do not handle all of the above components. For prices and names of dealers, write to North Hills Electronics Inc., Glen Cove, L.I., N.Y.; Knight is handled by Allied Radio, 100 N. Western Ave., Chicago 80, III.)

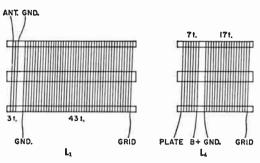


Fig. 5-32—Details of the coil construction. Each one is made from B & W 3012 Miniductor or Illumitronic 632 stock, which is wound 32 t.p.i. and $\frac{3}{4}$ -inch diameter. The separation between coils in L_1 is $1\frac{1}{2}$ turns; the separation between coils in L_4 is 1 turn. L_3 is 43 turns of the same stock.

It is important that the coils be connected as indicated. The coil stock can be cut to the required lengths by pushing in a turn, cutting it inside the coil and then pushing the newly cut ends through to outside the coil. Once outside, the wire can be peeled away with the help of long-nose pliers. When sufficient turns have been removed, the support bars can be cut with a fine saw.

receiver, as junctions for components and interconnecting wires. The coils L_8 and L_4 are mounted on tie points, using short leads, and L_1 is mounted on S_{1A} . If the leads from L_4 are too long, the coil will be "floppy" and the receiver may be unstable. Fig. 5-32 shows how the coils are constructed and connected. The leads from C_2 are brought through the chassis in insulating rubber grommets. The 3- to $30-\mu\mu f$. mica compression trimmer across L_1 is soldered to the associated section of C2. C2 is mounted on top of the chassis and surrounded by a Bud CU-3002-A Minibox, which serves as a dust cover. The partition between the two sections of C2 should be grounded to the chassis, to prevent capacitive coupling between the two sections. The coil L_2 is wound on a high-resistance 1-watt resistor: the ends of the coil are soldered to the leads of the resistor, and the winding will stay in place readily if the resistor is notched at each end before the winding is started.

The receiver is wired with shielded wire for many of the leads, in an effort to minimize hum



HIGH-FREQUENCY RECEIVERS

in the audio and feedthrough around the crystal filter. The shielded leads are marked in Fig. 5-31 where feasible; the simple rule to follow is to shield all B+ leads along with those shown shielded in Fig. 5-31. For ease of wiring, these shielded leads should be installed first or at least early in the construction. As the wiring progresses, a neat-looking unit can be obtained by dressing the leads and components in parallel lines or at right angles. D.c. and a.c. leads can be tucked out of the way along the edges of the chassis, while r.f. leads should be as direct as is reasonable.

If this is a first receiver or construction job, there are several pitfalls to be avoided. When installing a tube socket, orient the socket so the grid and plate leads will be direct and not cross over the socket.

Another thing is to avoid stranded wire for making connections throughout the receiver. Where stranded wire must be used, be careful to avoid wild strands that stray over to an adjacent socket terminal. No. 20 or 22 insulated solid tinned copper wire should be used for connections wherever no shielding is used. Long bare leads from resistors or capacitors should be covered with insulating tubing unless they go to chassis grounds.

The final bugaboo is a poorly-soldered connection. If this is first venture, by all means practice soldering before starting to wire this receiver. Read an article or two on how to solder, or get a friend to demonstrate. A good soldering iron is an essential; there have been instances of a first venture having been "soldered" with an iron that would just barely melt the solder; the iron was incapable of heating the solder and work to where the solder would flow properly.

When the wiring has been completed and checked once more against the circuit diagram, plug in the tubes and the line cord and turn on the receiver through S_s. The tube heaters should light up and nothing should start to smoke or get hot. If you have a voltmeter you should measure about 270 volts on the B+ line.

With headphones plugged in the receiver, you should be able to hear a little hum when the volume control is advanced all the way. If you can't hear any hum, touching a screwdriver to Pin 2 of V_{2A} should produce hum and a loud click. This shows that the detector and audio amplifier are working. The 100K regeneration control should be set at mid range.

The next step is to tune L_5 , L_6 and L_7 to 1700 kc., the crystal frequency. If you have or can

Fig. 5-33—Top view of the SimpleX Super. The tube at the left is the mixer-oscillator 6U8A; the 6CG7 audio amplifier is at the far right. The black knob is on the regeneration control. Toggle switch under the a.c. line cord is the a.c. line switch, S₈. Phono jack at left is the antenna terminal; phono jack at right near volume control is speaker jack, J₈.

borrow a signal generator, put 1700-kc. r.f. in at the grid of the 6U8A mixer and peak L_6 and L_6 . Lacking a signal generator, you may be lucky enough to find a strong signal by tuning around with C3, but it isn't likely. Your best het is to tune a broadcast receiver to around 1245 kc.; if the receiver has a 455-kc. i.f. the oscillator will then be on 1700 kc. Don't depend upon the calibration of the broadcast receiver; make your own by checking known stations. The oscillator of the broadcast receiver will furnish a steady carrier that can be picked up by running a wire temporarily from the grid of the 6U8A mixer to a point near the chassis of the b.c. receiver. Adjust L_7 until you get a beat with the 1700-kc. signal, and then peak L_5 and L_6 . If the signal gets too loud, reduce the signal by moving the wire away from the b.c. receiver. Now slowly swing the signal frequency back and forth with the b.f.o. turned off; a spot should be found where the noise rushes up quickly and then drops off. This is the crystal frequency, and Lo and Lo should be peaked again on this frequency.

An antenna connected to the receiver should now permit the reception of signals. With C2 nearly unmeshed, the input tuning will be in the region of the 7-Mc. band, and with C2 almost completely meshed, the input circuits will be near 3.5 Mc. Do the tuning with the C_4 in the oscillator circuit, until a known frequency is found (it can be a signal from the station transmitter). Let's say the transmitter has a crystal at 3725 kc. Set C_3 at half capacitance and tune with C_4 until the transmitter is heard. No antenna should be needed on the receiver for this test. Once C₄ is set, put the antenna on the receiver and look around for other known signals. (CHU, the Canadian standard-frequency station at 7335 kc., is a good marker.) With luck the tuning should just be able to cover the 80-meter band; if it covers one end but not the other, a minor readjustment of the trimmer is indicated.

Once the receiver is aligned to receive signals,

switch S_2 so that the b.f.o. is turned off. Advance the regeneration control (turn arm away from grounded end) and a point will be found where the noise increases and a slight "thump" is heard. This is the point where the detector oscil-

Fig. 5-34—Shielded wire, used for most of the d.c. and 60-cycle leads, lends to the clean appearance underneath the chassis. Toggle switch at the left shorts the input of the receiver, and the adjacent rotary switch handles the b.f.o. and the padding capacitor for WWV.

The pitch control, C₇, is at the right, next to the headphone jack. Power supply components (C₈, C₉ and CR₁, CR₂) are mounted on or near rear wall of chassis.

lates; just below this is the most sensitive condition for the reception of a.m. phone signals. Set the regeneration control at this point.


Turn the b.f.o. back on and tune in a c.w. signal. Tuning through the signal with the tuning knob on C_0 , note that the signal is louder on one side of zero beat than on the other. Experiment with the setting of the PITCH control until the maximum single-signal effect (louder one side than the other) is obtained. It may be necessary to pull up the plate of C_0 and to retune L_0 and L_0 before this is accomplished. After a little adjustment, however, the single-signal effect should be quite apparent.

All that remains is to install the dial scale and calibrate it. A 100-kc. oscillator is ideal for this job; lacking one or the ability to borrow one, other signals must be used. If the crystal filter is 1700 kc. exactly, the 80- and 40-meter calibrations will coincide as they do on the scale shown in Fig. 5-30; if not, the calibration marks will be offset on the two bands.

To find WWV at 5 Mc., set S_2 so that C_6 is switched in and the b.f.o. is on and adjust C_6 so that WWV falls on scale.

It may be noticed that tuning C_2 has a slight effect on the tuning of the signal. In other words, tuning C_2 "pulls" the oscillator slightly. To remedy this would have made the receiver more complicated, and the simple solution is merely to first peak C_2 on noise and then tune with C_3 . If two peaks of noise are found in the 80- or 40-meter bands, adjust C_1 until they coincide.

This will be found to be a practical receiver in every way for the c.w. (or s.s.b.) operator. The tuning rate is always the same on 80 or 40, or 15 with a converter, and 21-Mc. s.s.b. signals tune as easily as those on 3.9 Mc. The warm-up drift is negligible, and the oscillator is surprisingly insensitive to voltage changes. Whether or not the oscillator is insensitive to shock and vibration will depend upon the care with which the components are anchored to their respective tie points.

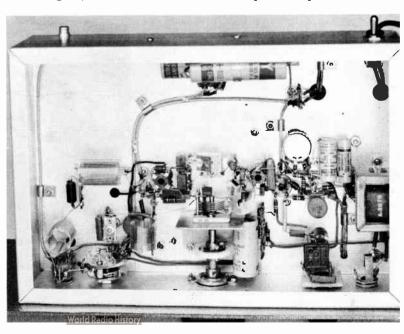

THE 2X4+1 SUPERHETERODYNE

The receiver shown in Figs. 5-35, 5-37 and 5-38 is a two-band four-tube (2X4) receiver with a transistor (+1) 100-kc. frequency standard. Other features include the ability to tune to 5 Mc., for the reception of WWV, and a dual-cystal filter for single-sideband and single-signal c.w. reception. Tuning the 40- and 80-meter amateur bands with good stability and selectivity, the receiver can be used on other bands by the addition of crystal-controlled converters ahead of it.

Referring to the circuit in Fig. 5-36, the pentode section of a 6U8-A is used as a mixer, with the triode portion of the same tube serving as the oscillator. The i.f. is 1700 kc. and the oscillator tunes 5.2 to 5.7 Mc.; tuning the input circuit to the 80-meter band brings in 80-meter signals, and all that is required to hear 40-meter signals is to swing the input tuning, C_1 , to the low-capacitance end of its range. Although, e.g., a 7.05-Mc. (5.35 + 1.7) and a 3.65-Mc. (5.35 -1.7) signal will appear at the same setting of the tuning dial, the two signals cannot be received simultaneously because the double-tuned circuit, C_{1A} , L_1 , and C_{1B} , L_3 , between antenna and mixer grid provides the necessary rejection. Coupling between the two circuits is provided by a small common inductor, L2. To make the two circuits track over the entire range, a 3- to 30-µµf trimmer is provided to compensate for the input capacitance of the mixer. For WWV reception, capacitance Co is added to the oscillator circuit to bring its frequency to 3.3 Mc.

The mixer is followed by the dual crystal filter at 1700 kc. and a stage of i.f. amplification. I.f.

gain is manually controlled by a variable bias control in the cathode circuit of the 6BA6 i.f. amplifier stage. A triode section of a 6CG7, V_{2A} , serves as a grid-leak detector, and the other section is used as the b.f.o. A two-stage audio amplifier follows, providing high-impedance output for headphones or low-impedance output for a loudspeaker. The audio power is sufficient to give more than enough high-impedance headphone volume and quite adequate loudspeaker volume in a quiet room.

The power supply includes a 0C3 to supply regulated 105 volts for the two oscillators and the screen of the mixer.

The transistor 100-kc. calibration oscillator uses for its power source the 8 volts developed across the cathode resistor of $V_{\rm 3B}$. Switch S_1 turns the oscillator on and off and also adds the capacitance to the oscillator circuit that permits WWV reception. The four positions of S_1 are off—wwv (only)—CAL (oscillator only)—Both. Although the 100-kc. standard as not essential to the operation of the receiver, its inclusion will be found to be quite valuable.

Construction

The receiver is built on an $8 \times 12 \times 3$ -inch aluminum chassis. A panel can be made from .080-inch thick sheet aluminum or from a standard $8\frac{3}{4}$ -inch rack panel. While the rack panel will be more substantial, it really isn't necessary, and the sheet stock will be adequate. The panel is held to the chassis by the b.f.o. capacitor, C_8 , the line/b.f.o. switch, S_2 , the dial, and an extra pair of 6-32 screws.



Fig. 5-35—The 2X4 + 1 superheterodyne is a four-tube receiver with 7-tube performance. It tunes the 80- and 40meter amateur bands, and provision is included for receiving WWV on 5 Mc. A built-in crystal oscillator provides 100-kc. frequency markers throughout the bands. Black knob on the left-hand side controls the calibration oscillator and the WWV reception.

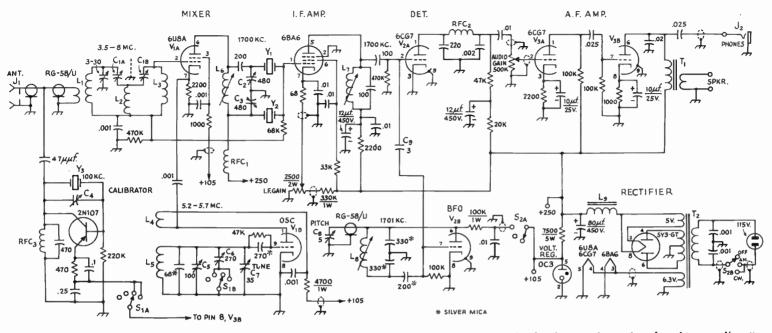


Fig. 5-36—Circuit diagram of the 2X4 + 1 super-heterodyne. Unless indicated otherwise, decimal capacitances are in μf., other capacitances in μμf., resistors are ½ watt.

- C_1 -Dual variable, 140 $\mu\mu$ f. per section (Hammarlund MCD-140-M).
- C_{2} , C_{3} —480- $\mu\mu$ f. mica compression trimmer (Arco-Elmenco 466).
- C4-4-30 µµf, trimmer (Erie TS2A),
- C₅-100-μμf, midget variable (Hammarlund HF-100).
- C₆-240 $\mu\mu$ f. \pm 5% mica in parallel with 30- $\mu\mu$ f. mica compression trimmer.
- C_T 35- $\mu\mu$ f, midget variable (Hammarlund HF-35).
- C₈-5-μμf, midget variable (Hammarlund HF-15 with 3 plates removed).
- C₈-3 μμf. approx, Insulated wires twisted together for 3 turns.

- J1-Phono jack.
- L1. L2-43 turns No. 24, 34-inch diam., 32 t.p.i. (B&W 3012 or Illumitronic 632). Coupling coil on L1 is 5 turns, spaced 1 turn from L1.
- La-16 turns No. 20 enam., closewound on 1/4-inch diam. form (100K or higher 1-watt resistor).
- L-7 turns No. 24, part of L5 stock, 1/32 inch from Ls. L-17 turns No. 24, 34-inch diam., 32 t.p.i. (B&W 3012 or Illumitronic 632).
- Ls, L7-64 to 105 μ h., adjustable (North Hills 120-G in North Hills S-120 shield can).
- L_8 -36 to 64 μ h., adjustable (North Hills 120-F in North Hills S-120 shield can).
- Le-15-henry, 75-ma. filter choke (Stancor C-1002).

- RFC1, RFC2-2.2 mh., self resonant at 1.6 Mc. (Miller 9350-36 or Miller J300-1500).
- RFC_s-10 mh. (National R-50-I).
- S₁-2-pole 6-position (4 used) miniature ceramic switch (Centralab PA-3 with Centralab PA-301 index, 21/2 inches used).
- S₂-2-pole 3-position rotary switch (Centralab 1472). T₁-3-watt, 8000 to 3.2 ohms, output transformer (Stancor A-3329).
- T₂-650 v.c.t. at 55 ma., 5 v., 6.3 v. at 2 amp. (Stancor PC-8407).
- Y1. Y-1700-kc. crystals, FT-243 holders.
- Ys-100-kc. (James Knight H-93 or equiv.)

122

It is worth while to mount the tuning capacitor, C_7 , as accurately as possible with respect to the National ICN dial. For minimum backlash and maximum strength, C_7 is mounted on a three-sided aluminum housing that is securely fastened to the chassis on three sides by $\frac{3}{6}$ -inch lips. A good flexible insulated coupling should be used between dial and capacitor shaft—a Millen 39006 is shown is the photograph.

The location of most of the major components can be determined by reference to the photographs. The inductors L_1 , L_3 and L_4 , L_5 are supported by suitable tie strips, as are the two 480- $\mu\mu$ f. mica compression trimmers, C_2 and C_3 , in the crystal filter circuit and the pair of 330- $\mu\mu$ f. capacitors in the b.f.o. L_1 should be wired so that the outside ends go to antenna and grid, and L_4 , L_5 should be wired with outside ends to plate and grid. L_2 is supported by its leads in a hole in the chassis; a rubber grommet prevents a short to chassis

Since the rotor of C_1 must not make contact with the panel, a large clearance hole must be provided for the shaft bushing, and a pair of extruded fiber washers used to insulate the bushing from the panel. A brass screw or bayonet lug should be set into the chassis at the shield partition between the two stators of C_1 , and the shield soldered to this chassis connection. The

HIGH-FREQUENCY RECEIVERS

3- to 30- $\mu\mu$ f, compression trimmer across C_{1A} can be soldered between rotor and shield partition.

Many of the connections are made with shielded leads, to minimize hum and chances for feedback or feedthrough. The shielded leads are indicated in Fig. 5-36. The lead from the antenna jack is run in RG-58/U coaxial cable, as is the short lead from C_8 to a 330- $\mu\mu$ f. capacitor. Heater leads to the tubes are made of shielded wire. The shielded leads to the dial lamps are not indicated in Fig. 5-36 but they can be seen in Fig. 5-37

Alignment

The alignment procedure can be simplified if a short-wave receiver or a signal generator can be borrowed. Lacking these, a grid-dip meter can be used to provide a signal source and to check the resonances of the tuned circuits. If the 100-kc. oscillator can be checked on another receiver, it can be used to align the receiver. A broadcast receiver will tell if the 100-kc. oscillator is functioning—it should be possible to identify several of the oscillator's harmonics at 100-kc. intervals in the broadcast band, by the reduction in noise at those points.

The audio amplifier of the receiver can be checked by turning on the receiver and listening

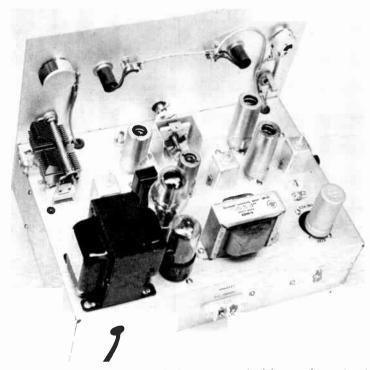


Fig. 5-37—Top view of the 2X4 + 1 receiver. The dual capacitor at the left tunes the receiver input. The main tuning capacitor, rear center, is mounted on a three-sided aluminum bracket for maximum stability. The tube to the left of the bracket is the 6U8-A mixer-oscillator stage, and the 6BA6 i.f. stage is in front of the main tuning capacitor. The remaining tubes in shields are the 6CG7 detector/b.f.o. and the audio 6CG7 (near panel). Metal can plugged in socket above antenna jack houses 100-kc. calibrating crystal.

2X4 + 1 Superhet

to the headphones as the audio gain control is advanced. When it is full clockwise a low-pitched hum should be just audible in the headphones. A further check can be made by bringing a finger near the arm of the audio gain control—the hum should increase.

If a means is available for checking the frequency of the b.f.o., it should be turned on at S_2 and set on or about 1700 kc. by means of the slug in L₈. Do this with C₈ set at half scale. If a broadcast receiver is the only measuring equipment you have, a 1700-kc. signal can be derived from it by tuning the receiver to 1245 kc., which puts its oscillator on 1700 kc. if the standard 455-kc. i.f. is used. A wire from around the receiver to the 2X4 + 1 should provide sufficient signal. Feeding a 1700-kc. signal into the detector by laying the source wire near the grid of the 6BA6 (i.f. gain arm at ground), it should be possible to peak L_7 for maximum signal and, as the signal frequency is changed slightly, a change in pitch of the whistle should be heard. With no incoming signal, a slight rushing noise should be heard in the headphones when the b.f.o. is switched on by S_2 . If this rushing noise is just barely discernible increase the capacitance at Co by adding a few more twists.

If the oscillator $V_{1\rm B}$ is operating, a voltmeter connected across the 4700-ohm 1-watt resistor in its plate lead should show an increase in voltage

when the stator of C_8 or C_7 is shorted to ground momentarily with a screwdriver or other conductor. Connect the + lead of the voltmeter to the side of the resistor running to + 105 and the —connection to the .001-μf. side. If the oscillator doesn't work, it may be because the outside turns of L_4 and L_5 are not connected to plate and grid respectively. With the b.f.o. on and C1 almost fully meshed, set the tuning capacitor C_7 at about 90 per cent full capacitance. Run C₆ to full capacitance and slowly reduce capacitance. At one point you should hear a loud signal, the second harmonic of the b.f.o. at 3400 kc. If the b.f.o. is reasonably close to frequency, turning on the calibration oscillator should give a weaker signal nearby (on the main tuning dial). Tune C7 to a higher frequency (less capacitance) and you should hear another weaker signal, the 35th harmonic of the oscillator (3500 kc.). Peak C_1 for maximum signal and leave it. Run C₇ back to about 90 per cent full capacitance and then slowly reduce capacitance at C_5 until the 35th harmonic of the oscillator is again heard. If a 3500-kc. signal is available the adjustment can be made in a more straightforward manner.

Once the oscillator trimmer C_6 has been set to give the proper tuning range of the oscillator circuit (5.2 to 5.7 Mc.), the next problem is that of adjusting the crystal filter circuit. With a capacitance bridge, or a grid-dip meter and an in-

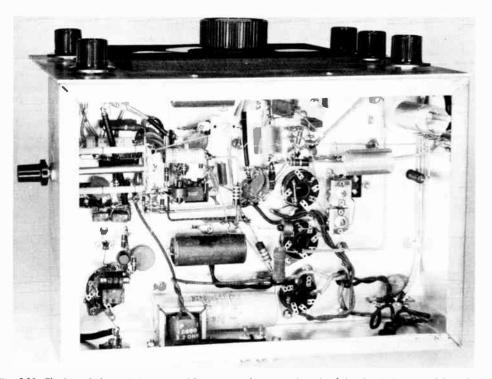


Fig. 5-38—The input inductor L_1 is supported by a terminal strip on the side of the chassis (upper right), and L_3 is supported nearby by a terminal strip mounted on the chassis. The coils are at right angles to minimize inductive coupling. L_2 is supported by the grommet in the chassis. The oscillator inductors, L_1L_5 , are also supported by a terminal strip (top center). A mica compression trimmer to the left of the oscillator inductors is used to center WWV on the tuning dial; the pair of compression trimmers below L_3 are in the crystal filter circuit.

ductance, are set the two capacitors C_2 and C_8 at the same capacitance (near maximum compression) before soldering them in the receiver. The actual value of capacitance isn't important. Lacking these instruments, tighten the capacitors to full compression and then loosen their screws by 3/4 turn. Tune in a signal—it can be from the 100-kc. oscillator or any other steady source—and peak L₀ for maximum response. Tune off the signal until it disappears and set the pitch control. C₈, to a point where the background noise is reasonably high-pitched. This is easy to determine because at the lowest-pitched point there will be an increase in hum; make the lowest-pitched point the center of the knob scale by adjustment of L₈, and then set the pitch control to one end of its range. Tune back to the signal and "rock" the tuning, C1, as you change the adjustment of L₆. Look for a condition that gives considerably more response on one side of zero beat than on the other. It is a good idea to buy several extra 1700-kc. crystals and try them in different combinations. Small changes in the setting of C2 or C3 will have an effect on the selectivity characteristic, but bear in mind that a change in C2 or C3 must be compensated for by a readjustment of L₆. With a little patience it should be possible to obtain a marked difference in the output strength on the two sides of zero beat. This will "flip over" to the other side if the pitch control is set at the other end of its range.

The remaining alignment job consists of bringing the input circuits into resonance on both bands. With a signal tuned in at 40 meters, "rock" C_1 back and forth to see if there are two (close-together) points where the signal peaks. If there are, adjust the 3-30- $\mu\mu$ f. trimmer across L_1 until only one peak is found. Check on 80 meters in a similar fashion. If for any reason it is found that the two-peak condition can be eliminated on only one band at a time, it indicates an abnormal amount of antenna reactance, and a compromise adjustment will have to be made. It can also mean that the antenna is not coupled tightly enough to L_1 , which will require increasing the number of turns in the antenna coil.

The antenna coil on L_1 is of necessity a compromise. The 5 turns specified in Fig. 5-36 is

HIGH-FREQUENCY RECEIVERS

correct for an impedance level of about 100 ohms. If the antenna used with the receiver has a 50-or 75-ohm feedline (coaxial line or Twin-Lead), a 3-turn coil is recommended. If the feedline is 300-ohm Twin-Lead, the antenna coil should be 11 turns. With a "random" wire for the receiving antenna, the 5-turn coil is as good a compromise as any.

In operation, the receiver input control, C_1 , should be set for maximum volume on the incoming signal or noise. The i.f. gain should be run at close to minimum on all but the weakest signals, and the audio gain control should be set for comfortable headphone or speaker volume. If an antenna changeover relay is used, it may be possible to monitor your own transmitter by detuning the input circuit to another band; this ability will depend upon the transmitter power and field in the vicinity of the receiver.

Frequency Standard

No trouble should be encountered with the 100-kc. oscillator if care is exercised in handling the transistor. When soldering its leads in place, hold the lead with a pair of pliers; the metal of the pliers will absorb heat and prevent injury to the transistor.


To tune the receiver to WWV, set C_7 to mid scale, set S_1 at the WWV position, peak C_1 on noise and slowly tune with C_6 . On a busy day a wide variety of signals will be heard in this region look for one with steady tone modulation and time ticks. If it can't be found within the range of C_6 , set C_7 near one end of its range and try again. An alternate method is to disconnect the antenna, establish the position on the tuning dial (C_1) of several 100-kc. harmonics, connect the antenna and investigate each one of these frequencies. Depending upon one's geographical location, there will be times when WWV cannot be heard on 5 Mc., so don't be discouraged by failure on the first try. Once WWV has been located with good strength, the 50th harmonic of the 100-kc. crystal can be brought to zero beat with WWV by adjustment of C_4 . If the harmonics are too loud and tend to overload the receiver, use a smaller capacitor (10 to 22 $\mu\mu$ f.) than the 47 $\mu\mu$ f. shown in Fig. 5-36.

ADAPTOR PLUG

The sketch below shows an exploded view of an adaptor plug which adapts a conventional u.h.f. series connector for mating with a phono jack. To assemble the plug, solder a 1-inch length of No. 12 copper wire to the center conductor of an SO-239 connector. Next sweat-solder the cap end of a phono plug into the small end of an 83-1H hood. Slip the hood and plug assembly onto the SO-239 connector so that the No. 12 wire inserts in the center conductor of the phono plug. Attach the hood to the connector

with machine screws and solder the wire that is in the tip of the phono plug.

—Robert J. Jarnutowski, K9ITS

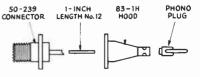

U.h.f. series-to-phono-plug adaptor.

A SELECTIVE CONVERTER FOR 80 AND 40 METERS

Many inexpensive "communications" receivers are lacking in selectivity and bandspread. The 80- and 40-meter performance of such a receiver can be improved considerably by using ahead of it the converter shown in Figs. 5-39 and 5-41. This converter is not intended to be used ahead of a broadcast receiver except for phone reception, because the b.c. set has no b.f.o. or manual gain control, and both of these features are necessary for good c.w. reception. The converter can be built for less than \$20, and that cost can be cut

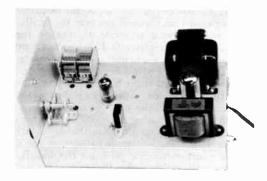


Fig. 5-39—Used ahead of a small receiver that tunes to 1700 kc., this converter will add tuning ease and selectivity on the 80- and 40-meter bands. The input capacitor is the dual section unit at the upper left-hand corner. The crystal and the tuning slug for L₆ are near the center at the foreground edge.

appreciably if the power can be "borrowed" from another source.

The converter uses the tuning principle employed in the two-band superheterodynes described earlier in this chapter. A double-tuned input circuit with large capacitors covers both 80 and 40 meters without switching, and the oscillator tunes from 5.2 to 5.7 Mc. Consequently with an i.f. of 1700 kc. the tuning range of the converter is 3.5 to 4.0 Mc. and 6.9 to 7.4 Mc. Which band is being heard will depend upon the setting of the input circuit tuning (C_1 in Fig. 5-40). The converter output is amplified in the receiver, which must of course be set to 1700 kc. To add selectivity, a 1700-kc. quartz crystal is used in series with the output connection. A small power supply is shown with the converter, and some expense can be eliminated if 300 volts d.c. at 15 ma, and 6.3 volts a.c. at 0.45 ampere is available from an existing supply.

Construction

The unit is built on a $7 \times 11 \times 2$ -inch aluminum chassis. The front panel is made from a 6×7 -inch piece of aluminum. The power supply is mounted to the rear of the chassis and the converter components are in the center and front. The layout shown in the bottom view should be followed, at least for the placement of L_1 , L_2 L_3 and L_4 .

The input and oscillator coils are made from a single length of B & W Miniductor stock, No. 3016. Count off 31 turns of the coil stock and

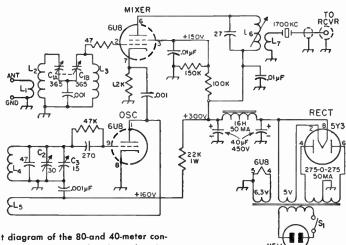


Fig. 5-40—Circuit diagram of the 80-and 40-meter converter. All capacitances given in $\mu\mu$ f. unless otherwise noted.

 C_1 —365- $\mu\mu$ f. dual variable, t.r.f. type.

 C_2 —3-30- $\mu\mu$ f. trimmer.

C₈—15-μμf. variable (Bud 1850, Cardwell ZR-15AS, Millen 20015).

 $L_{\rm L},~L_{\rm S},~L_{\rm S},~L_{\rm t},~L_{\rm S}{\rm -B}$ & W No. 3016 Miniductor, 1-inch diameter, 32 turns per inch, No. 22 wire, cut as below.

 L_1 —8 turns separated from L_2 by one turn (see text). L_2 , L_3 —19 turns.

L₄-21 turns separated from L₅ by one turn.

L₅-8 turns.

 L_0 —105–200- μ h. slug-tuned coil (North Hills Electric 120H).

L7-See text.

Crystal-1700 kc. (E. B. Lewis Co. Type EL-3).


bend the 32nd turn in toward the axis of the coil. Cut the wire at this point and then unwind the 32nd turn from the support bars. Using a hacksaw blade, carefully cut the polystyrene support bars and separate the 31-turn coil from the original stock. Next, count off 9 turns from the 31-turn coil and cut the wire at the 9th turn. At the cut unwind a half turn from each coil, and also unwind a half turn at the outside ends. This will leave two coils on the same support bars, with half-turn leads at their ends. One coil has 21 turns and the other has 8 turns, and they are separated by the space of one turn. These coils are L_4 and L_5 .

The input coils L_1 and L_2 are made up in the same manner. Standard bakelite tie points are used to mount the coils. Two 4-terminal tie points are needed for L_1L_2 and L_4L_5 , and a one-terminal unit is required for L_3 . The plate load inductance L_6 is a 105-200 μ h, variable-inductance coil (North Hills 120H). The coupling coil L_7 is 45 turns of No. 32 enam. scramble-wound adjacent to L_6 . If the constructor should have difficulty in obtaining No. 32 wire, any size small enough to allow 45 turns on the coil form can be substituted.

The input capacitor, C_1 , is a 2-gang t.r.f. variable, 365 $\mu\mu$ f. per section. As both the stators and rotor must be insulated from the chassis, extruded fiber washers should be used with the screws that hold the unit to the chassis. The panel shaft hole should be made large enough to clear the rotor shaft.

A National type O dial assembly is used to tune C_3 . One word of advice when drilling the holes for the dial assembly: the template furnished with the unit is in error on the 2-inch dimension (it is slightly short) so use a ruler to measure the hole spacing.

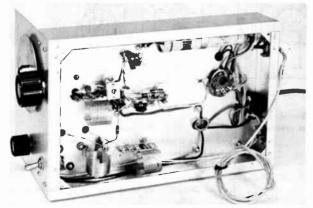It is important that the output lead from the crystal socket be run in shielded wire. A phono jack is mounted on the back of the chassis, and a piece of shielded lead connects from the jack to the crystal socket terminal. The leads from the stators of C_1 and C_3 are insulated from the chassis by means of rubber grommets.



.

Testing and Adjustment

A length of shielded wire is used to connect the converter to the receiver: the inner conductor of the wire is connected to one antenna terminal; the shield is connected to the other terminal and grounded to the receiver chassis. The use of shielded wire helps to prevent pickup of unwanted 1700-kc. signals. Turn on the converter and receiver and allow them to warm up. Tune the receiver to the 5.2-Mc. region and listen for the oscillator of the converter. The b.f.o. in the receiver should be turned on. Tune around until the oscillator is heard. Once you spot it, tune C₃ to maximum capacitance and the receiver to as close to 5.2 Mc. as you can. Adjust the oscillator trimmer capacitor, C2, until you hear the oscillator signal. Put your receiving antenna on the converter, set the receiver to 1700 kc., and tune the input capacitor, C_1 , to near maximum capacitance. At one point you'll hear the background noise come up. This is the 80-meter tuning. The point near minimum capacitance - where the noise is loudest — is the 40-meter tuning.

With the input tuning set to 80 meters, turn on your transmitter and tune in the signal. By spotting your crystal-controlled frequency you'll have one sure calibration point for the dial. By listening in the evening when the band is crowded you should be able to find the band edges.

You'll find by experimenting that there is one point at or near 1700 kc. on your receiver where the background noise is the loudest. Set the receiver to this point and adjust the slug on L_6 for maximum noise or signal. When you have the receiver tuned exactly to the frequency of the crystal in the converter, you'll find that you have quite a bit of selectivity. Tune in a c.w. signal and tune slowly through zero beat. You should notice that on one side of zero beat the signal is strong, and on the other side you won't hear the signal or it will be very weak (if it isn't, off-set the b.f.o. a bit). This is single-signal c.w. reception.

When listening to phone signals, it may be found that the use of the quartz crystal destroys some of the naturalness of the voice signal. If

this is the case, the crystal should be unplugged and replaced by a 10- or $20-\mu\mu f$. capacitor.

Fig. 5-41—Bottom view of the converter showing placement of parts. The coil at the lower left is L_3 , and the input coil, L_1L_2 , is just to the right of L_3 . The oscillator coil L_4L_5 , is at the left near the center. The output coil, L_6 , is near the top center.

A CRYSTAL-CONTROLLED CONVERTER FOR 20, 15 AND 10 METERS

The cure for most of the high-frequency ills of many receivers is the installation of a good crystal-controlled converter between the antenna and the receiver. The converter shown in Figs. 5-42 and 5-44 is intended to be used ahead of a receiver that tunes from 3.5 to 4.0 Mc., although its output range can be modified merely by changing the crystal frequencies. Used with a receiver tuning the 80-meter band only, the 14- and 21-Mc. bands are covered with something left over, but only 500-kc. segments of the 28-Mc. band can be covered without switching crystals. If complete coverage without switching is desired, a wider-range receiver can be used; e.g., the BC-454 surplus receiver, which tunes 3 to 6 Mc.

Referring to Fig. 5-43, the converter consists of an r.f. amplifier, mixer and oscillator stages, and an inexpensive power supply. A cathodebias control (R_1) on the r.f. stage determines the stage gain and prevents overloading on strong signals. The signal circuits, tuned by C_1 and C_2 , cover 14 to 30 Mc. and are peaked by the operator for the band in use. The selector switch, S_2 , is used to switch to the required crystal and output circuit; on 10 meters the same output circuit is used for several crystals. No tuned output from the mixer is included; the tuned circuit (s) of the receiver following the converter being all that is necessary.

The converter is built on a $4 \times 7 \times 2$ -inch chassis and is housed in a $5 \times 9 \times 6$ grey hammertone aluminum utility cabinet. Although the construction is straightforward and should present no particular problems, there are places where caution should be exercised. For example, r.f. leads and bypassing at the 6BZ6 socket should be made as short and direct as possible, to minimize the chance for oscillation of this high-gain stage. Grounding should be done with soldering lugs to the screws that hold the socket to the chassis. Generous use of tie points is advisable, so that both ends of resistors and capacitors will be supported.

Coils L_1 and L_2 are made from a single piece of B&W 3011 Miniductor stock. Start with a 20-turn length of stock. With a pin or knife push in the 6th turn from one end and cut it. Push the cut ends back out and unwind each approximately a half turn to the support bar. Unwind the ends to give the specified turns in each coil (see Fig. 5-43). The coils are supported by standard ticpoint strips; on L_1 the outside ends go to antenna (small coil) and grid, and on L_2 the outside ends go to plate (small coil) and grid. When


Fig. 5-42—A 3-band crystal-controlled converter, to be used ahead of a receiver tuning the 80-meter band. The converter is shown out of its cabinet. Mixer tuning control at right, gain control and line switch at left. The tube in the center is the 6U8A mixer-oscillator.

the coils are mounted, they should be positioned at least $\frac{1}{2}$ inch away from the chassis or panel.

Ceramic or mica capacitors can be used across L_3 , L_4 and L_6 . The $3-\mu\mu$ f. coupling capacitor between pins 1 and 2 of the 6U8A can be a small ceramic or it can be made from two 1-inch lengths of plastic-covered wire twisted together.

When the wiring has been completed and checked, plug the tubes into their sockets and turn the adjustment screws of L3, L4 and L5 until the screws are out of the coil ends as far as they will go. Use a length of coaxial line and suitable plugs to connect the output of the converter to the antenna terminals of the receiver, and connect an antenna to the antenna terminals of the converter. Plug in the line plug (fused with $\frac{1}{2}$ -ampere fuses) and turn on S_1 . The tube heaters should light up. With S₂ switched to the 20-meter position, screw in the slug of L_s as the knob of C2 is rocked back and forth about the maximum-capacitance end of its range. When an increase in noise is heard as C2 is rocked through a particular point, hold up on the adjustment of L_3 and turn the knob of C_1 . Peak C_1 on noise and tune around with the receiver for any signals. If for any reason the crystal or oscillator is suspected of not operating properly, it can be checked by connecting a voltmeter across the 1000-ohm resistor running to the arm of S_{2A} (+ side of meter to power-supply side). If the oscillator is functioning properly, when Y_1 is removed from its socket the voltage measured across the 1000-ohm resistor should increase.

The slugs in L_4 and L_5 are adjusted in a similar manner, with S_2 in the proper position. After one slug has been adjusted, it may be necessary to touch up the others slightly. A compromise setting will be found for L_5 that allows good operation of either Y_5 or Y_4 .

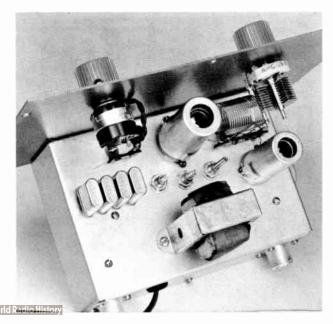

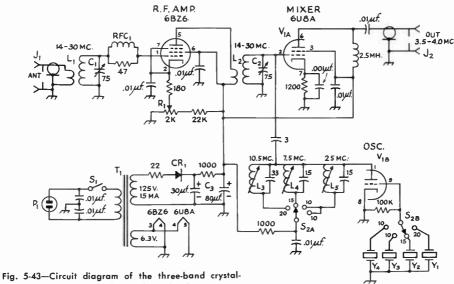


Fig. 5-43—Circuit diagram of the three-band crystalcontrolled converter. Unless indicated otherwise, capacitances are in $\mu\mu f$., resistors are $\frac{1}{2}$ watt.


C₁, C₂—75-μμf. variable (Hammarlund APC-75-B).
C₃—30-80-μf. dual electrolytic, 150-volt, common negative.

CR₁—50-ma. 130-v. selenium rectifier (International Rectifier TO65).

J₁, J₂—Chassis-mounting coaxial connector (SO-239).
 L₁, L₂—12 turns No. 20, 16 t.p.i., ¾-inch diam. (See text). Primary on L₁ is 3 turns, 4 turns on L₂. Separation of 1/16 inch between primary and sec-

 L_3 -3.1- to 6.8- μ h., slug-tuned (Miller 4405). L_4 , L_5 -1.5- to 3.2- μ h., slug-tuned (Miller 4404).

ondary.

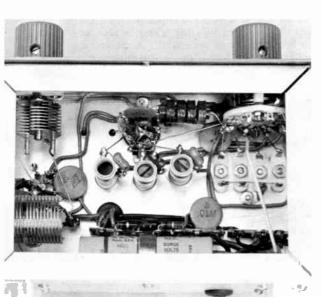

P₁-Fused plug (El Menco).

R₁—2000-ohm 1-watt potentiometer, with switch (CTS-IRC Q11-110 with IRC 76-1 switch).

 S_1 —Part of R_1 , see above.

 S_2 —2-pole 5-position (4 used) rotary switch (Centralab PA-2003).

RFC₁—7 turns No. 20 wound on 47-ohm ½-watt resistor. T₁—125 v. at 15 ma., 6.3 v. at 0.6 amp. (Allied Radio's Knight 61 G 410 or equiv.)

Y₁—10.5-Mc. crystal (International Crystal Co., Type FA-9).

Y2-17.5-Mc. crystal.

Y₃—24.5-Mc. crystal.

Y₄-25.0-Mc. crystal.

Fairly sharp tuning of C_1 and C_2 is normal, and it may be found that any given settings will suffice for a receiver tuning range of only a portion of an amateur band. If the gain control cannot be advanced to the maximum-gain position (arm at chassis end of R_1) without oscillation, take a second look at the wiring of the 6BZ6 socket. The grid and plate leads should not be able to "see" each other, and the center post of the socket should be grounded to the chassis by a short length of wire.

With this converter, the 80-meter receiver is serving as a tunable i.f. system. The signal frequency is the indicated receiver frequency plus the crystal frequency; e.g., on 20 meters a 14.1-Mc. signal will appear at 3.6 Mc. (3.6 + 10.5 = 14.1) on the receiver. The over-all system hecomes a double-conversion superheterodyne with a crystal-controlled "front end," a popular arrangement found in many high-priced receivers.

Fig. 5-44—A view underneath the chassis of the three-band converter. Input tuned circuit at left, oscillator coils at center, and band switch and output connector at right. The selenium rectifier is hidden by the lip of the $4 \times 6 \times 2$ -inch chassis.

THE "SELECTOJECT"

The Selectoject is a receiver adjunct that can be used as a sharp amplifier or as a single-frequency rejection filter. The frequency of operation may be set to any point in the audio range by turning a single knob. The degree of selectivity (or depth of the null) is continuously adjustable and is independent of tuning. In phone work, the rejection notch can be used to reduce or eliminate a heterodyne. In c.w. reception, interfering signals may be rejected or, alternatively, the desired signal may be picked out and amplified. The Selectoject may also be operated as a low-distortion variable-frequency audio oscillator suitable for amplifier frequency-response measurements, modulation tests, and the like, by advancing the "selectivity" control far enough in the selectiveamplifier condition. The Selectoject is connected in a receiver between the detector and the first audio stage. Its power requirements are 4 ma. at 150 volts and 6.3 volts at 0.6 ampere. For proper operation, the 150 volts should be obtained from across a VR-150 or from a supply with an output capacity of at least 20 μf.

The wiring diagram of the Selectoject is shown in Fig. 5-45. Resistors R_2 and R_3 , and R_4 and R_6 , can be within 10 per cent of the nominal value but

they should be as close to each other as possible. An ohmmeter is quite satisfactory for doing the matching. One-watt resistors are used because the larger ratings are usually more stable over a long period of time.

If the station receiver has an "accessory socket" on it, the cable of the Selectoject can be made up to match the connections to the socket, and the numbers will not necessarily match those shown in Fig. 5-45. The lead between the second detector and the receiver gain control should be broken and run in shielded leads to the two pins of the socket corresponding to those on the plug marked "A.F. Input" and "A.F. Output." If the receiver has a VR-150 included in it for voltage stabilization there will be no problem in getting the plate voltage — otherwise a suitable voltage divider should be incorporated in the receiver, with a 20- to 40-µf. electrolytic capacitor connected from the + 150-volt tap to ground.

In operation, overload of the receiver or the Selectoject should be avoided, or all of the possible selectivity may not be realized.

The Selectoject is useful as a means for obtaining much of the performance for a "Q Mulitplier" from a receiver lacking one.

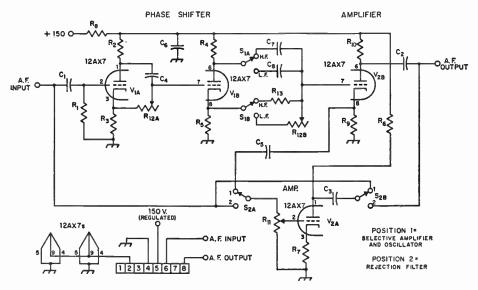


Fig. 5-45—Complete schematic of Selectoject using 12AX7 tubes.

C1-0.01-µf. mica, 400 volts.

C₂, C₃—0.1-µf. paper, 200 volts.

C₄, C₈--0.002-µf. paper, 400 volts.

 C_5 —0.05- μ f. paper, 400 volts.

C₆-16-µf. 150-volt electrolytic.

 C_7 —0.0002- μ f. mica.

R₁—1 megohm, ½ watt.

R₂, R₃—1000 ohms, 1 watt, matched as closely as possible (see text).

R₄, R₅—2000 ohms, 1 watt, matched as closely as possible (see text). R₆-20,000 ohms, ½ watt.

R7-2000 ohms, 1/2 watt.

R₆-10,000 ohms, 1 watt.

R₀-6000 chms, ½ watt.

R₁₀—20,000 ohms, ½ watt.

R₁₁-0.5-megohm ½-watt potentiometer (selectivity).

R₁₂—Ganged 5-megohm potentiometers (tuning control) (IRC PQ11-141 with IRC M11-141.)

R₁₃-0.12 megohm, ½ watt.

S₁, S₈-D.p.d.t. toggle (can be ganged).

ANTENNA COUPLER FOR RECEIVING

In many instances reception can be improved by the addition of an antenna coupler between the antenna feedline and the receiver, and in all cases the r.f. image rejection will be increased. The unit shown on this page consists of one series-tuned circuit and one parallel-tuned circuit; usually its best performance is obtained with the parallel-tuned circuit connected to the receiver input, as indicated in Fig. 5-46. However, the coupler should also be tried with the connections reversed, to see which gives the better results. The desired connection is the one that gives the sharper peak or louder signals when the circuits are resonated.

The coupler is built on one section of a $5 \times 4 \times 3$ -inch Minibox (Bud CU-2105A). Tuning capacitors C_1 and C_2 are mounted directly on the Minibox face, since there is no need to insulate the rotors. The arrangement of the components can be seen in Fig. 5-47.

The coils L_1 and L_2 are made from a single length of B & W 3011 Miniductor. The wire is snipped at the center of the coil and unwound in both directions until there are three empty spaces on three support bars and two empty spaces on the bar from which the snipped ends project. These inner ends run to the connectors J_1 and J_2 . (Fig. 5-46). Unwind turns at the ends of the coils until each coil has a total of 22 turns. When soldering the leads to the 3rd, 6th, 8th and 12th turns from the inside ends of the coils, protect the adjacent turns from solder and flux by placing strips of aluminum cooking foil between the turns. An iron with a sharp point will be required for the soldering.

The "panel" side of the box can be finished off with decals indicating the knob functions and switch positions.

The antenna coupler should be mounted within a few feet of the receiver, to minimize the length of RG-59/U between coupler and receiver. In crowded quarters, the use of M-359A right-angle

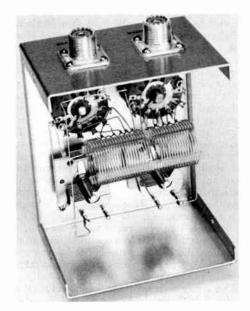


Fig. 5-47—Receiver antenna coupler, with cover removed from case. Unit tunes 6 to 30 Mc. The coil is supported by the leads to the capacitors and switches.

adapters (Amphenol 83-58) and J_1 and J_2 will make it possible to bring out the cables in better lines.

Normally the coupler will be adjusted for optimum coupling or maximum image rejection, but by detuning the coupler it can be used as an auxiliary gain control to reduce the overloading effects of strong local signals. The coupler circuits do not resonate below 6 Mc., but a coupler of this type is seldom if ever used in the 80-meter band; its major usefulness will be found at the higher frequencies.

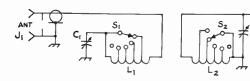


Fig. 5-46—Circuit diagram of the receiver antenna coupler.

C₁, C₂—100-μμf. midget variable (Hammarlund HF-100).
J₁, J₂—Coaxial cable connector, SO-239.

L₁, L₂—22 turns No. 20, ¾-inch diameter, 16 t.p.i. Tapped 3, 6, 8 and 12 turns from inside end. See text on spacing and tapping.

S₁, S₂—Single-pole 11-position switch (5 used) rotary switch (Centralab PA-1000).

Preselector 131

A REGENERATIVE PRESELECTOR FOR 7 TO 30 Mc.

The performance of many receivers begins to drop off at 14 Mc. and higher. The signal-tonoise ratio is reduced, and unless double conversion is used in the receiver there is likely to be increased trouble with r.f. images at the higher frequencies. The preselector shown in Figs. 5-48 and 5-49 can be added ahead of any receiver without making any changes within the receiver, and a self-contained power supply eliminates the problem of furnishing heater and plate power. The poorer the receiver is at the higher frequencies, the more it will benefit by the addition of the preselector.

A truly good receiver at 28 Me. will show little or no improvement when the pre-

selector is added, but a mediocre receiver or one without an r.f. stage will be improved greatly through the use of the preselector.

A 6CG7 dual triode is used in the preselector, one triode as a bandswitched regenerative r.f. stage and the other as a cathode follower. A conventional neutralizing circuit is used in the amplifier; by upsetting this circuit enough the stage can be made to oscillate. Smooth control of regeneration up to this point is obtained by varying one of the capacitances in the neutralizing circuit.

If and when it becomes necessary to reduce gain (to avoid overloading the receiver), the

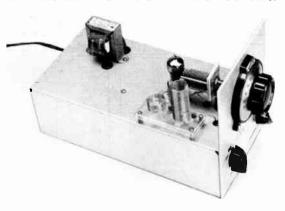


Fig. 5-48—The regenerative preselector covers the range 7 to 30 Mc.; it can be used ahead of any receiver to improve gain, image rejection and, in many cases, sensitivity. A dual triode 6CG7 is used a r.f. amplifier and cathode follower.

regeneration control can be retarded. One position of the bandswitch permits straight-through operation, so the preselector unit can be left connected to the receiver even during low-frequency reception.

The preselector is built on a $5 \times 10 \times 3$ -inch chassis (Bud AC-404). A $5 \times 6\frac{1}{2}$ -inch aluminum panel is held to the chassis by the extension-shaft bushing for the regeneration-control capacitor, C_3 , and the bushing for the rotary switch. The coils, L_1 and L_2 , are supported on a small staging of $1\frac{1}{4} \times 3$ -inch clear plastic. (It can be made from the lid of the box that the Sprague 5GA-S1

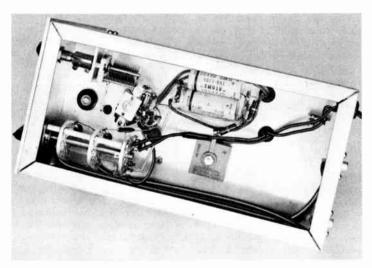


Fig. 5-49—The r.f. components are bunched around the 9-pin miniature tube socket. Power supply components are supported by screws and tie points.

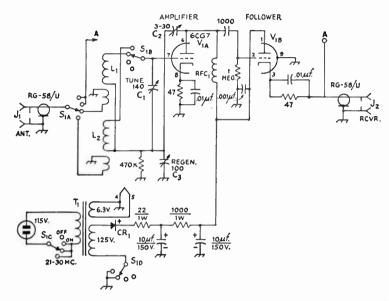


Fig. 5-50—Circuit diagram of the regenerative preselector. Unless otherwise specified, resistors are $\frac{1}{2}$ watt, capacitors are in $\mu\mu f$., capacitors marked in polarity are electrolytic.

 C_1 —140- $\mu\mu$ f. midget variable (Hammarlund HF-140).

 C_2 -3- to 30- $\mu\mu$ f. mica compression trimmer.

C₃—100-µµf. midget variable (Hammarlund MAPC-100-

CR₁—50-ma. selenium rectifier (International Rectifier TO50).

J₁, J₂—Phono jack.

L₁—19 turns, 7-turn primary.

L₂-5 turns, 2-turns primary. Coils are %-inch diameter, 16 t.p.i., No. 20 Wire (B & W 3011 Miniductor).

.01-µf. disk ceramic capacitors come in.) All coils can be made from a single length of B&W 3011 Miniductor. They are cemented to the plastic staging with Duco cement.

The rotor of C_1 can be insulated from the chassis by mounting the capacitor bracket on insulating bushings (National XS-6 or Millen 37201); its shaft is extended through the use of an insulated extender shaft (Allied Radio No. 60 H 355). The bandswitch S_1 is made from the specified sections (see Fig. 5-50).

The first section is spaced 3/4 inch from the indexing head, there is 1-inch separation between this and the next section (S_{1B}) , and the next section (S_{1C}, S_{1D}) is spaced 21/2 inches from S_{1B} .

The regeneration control, C_3 , is mounted on a small aluminum bracket. Its shaft does not have to be insulated from the chassis, so either an insulated or a solid shaft connector can be used. The small neutralizing capacitor, C_2 , is supported by soldering one lead of it to a stator bar of C_3 and running a wire from the other lead to pin 6 of the tube socket. The rotor and stator connections from C_1 are brought through the chassis deck through small rubber grommets.

Power supply components, resistors and capacitors are supported by suitable lugs and tie

One-turn spacing between coils and primaries. S1—Three-wafer switch. S_{1A} and S_{1B} are 1-pole 12-position (4 used) miniature ceramic switch sections (Centralab PA-1); S_{1C} and S_{1D} are 2-pole 6-position (4 used) miniature switch (Centralab PA-3). Sections mounted on Centralab PA-301 index assembly.

T₁—125 v. at 15 ma., 6.3 v. at 0.6 amp. (Stancor PS-8415 or Knight 61G410).

RFC₁—100-μh. r.f. choke (National R-33).

points. Phono jacks are used for the input and output connectors.

Adjustment

Assuming that the wiring is correct and that the coils have been constructed properly and cover the required ranges, the only preliminary adjustment is the proper setting of C2. Connect an antenna to the input jack and connect the receiver to the output jack through a suitable length of RG-58/U. Turn on the receiver b.f.o. and tune to 28 Mc. with S_1 in the on position. Now turn S₁ to the 21- to 30-Mc. range. Swing the TUNE capacitor, C_1 , and listen for a loud rough signal which indicates that the preselector is oscillating. If nothing is heard, advance the regeneration control toward the minimum capacitance end and repeat. If no oscillation is heard, it may be necessary to change the setting of C2. Once the oscillating condition has been found, set the regeneration control at minimum capacitance and slowly adjust C2 until the preselector oscillates only when the regeneration control is set at minimum capacitance. You can now swing the receiver to 21 Mc. and peak the preselector tuning capacitor. It will be found that the regeneration capacitance will have to be increased to avoid oscillation.

DCS-500 133

Check the performance on the lower range by tuning in signals at 14 and 7 Mc. and peaking the preselector. It should be possible to set the regeneration control in these two ranges to give both an oscillating and a non-oscillating condition of the preselector.

A little experience will be required before you

can get the best performance out of the preselector. Learn to set the regeneration control so that the preselector is selective, but not so selective that it must be retuned every 10 kc. or so. Changing to another antenna may modify the best regeneration control setting because the loading on the preselector is changed.

DCS-500 DOUBLE-CONVERSION SUPERHETERODYNE

The receiver shown in Fig. 5-51 was designed to meet a need for a better-than-average ham receiver requiring a minimum of mechanical work and using standard and easily obtainable parts. It incorporates such features as a 100-kc. calibrator, provision for reception on all ham bands from 80 through 10 meters, adequate selectivity for today's crowded bands, and stability high enough for copying s.s.b. signals. Dubbed the DCS-500 because of its 500-cycle selectivity in the sharpest i.f. position, it is a double-conversion superheterodyne receiver capable of giving good results on either a.m., c.w. or s.s.b.

The Circuit

Referring to the circuit diagram, Figs. 5-52 and 5-53, a 6BA6 r.f., stage is followed by a 6U8A mixer-oscillator. The 4.5-Mc. mixer output is amplified by a 6BA6 and filtered by a two-stage crystal filter, after which a 6U8A second mixer-oscillator, crystal-controlled, heterodynes the signal to 50 kc.

The combination of i.f. amplifiers may appear rather unusual at first glance, since one might expect that a cascade crystal filter in the highfrequency i.f. would make further selectivity unnecessary. This would be true with highly developed filters, but two filters are needed if the best possible job is to be done on both phone and c.w., and such filters are expensive. With inexpensive surplus crystals such as are used in this receiver it would be difficult, if not impossible, to match the performance of the high-class filters; in addition, special test equipment and extreme care in adjustment would be necessary. The approach used here is to use the surplus crystals without such special adjustment, thereby achieving a good, if not quite optimum, degree of selectivity against strong signals near the desired one, and then to back up the filter by a low-frequency i.f. amplifier that will give the "close-in" straightsided selectivity needed in present-day operation. The over-all result is a high order of protection against strong interfering signals at considerably less cost, for the entire double-i.f. system, than that of two high-performance filters alone. The

Fig. 5-51—The DCS-500 double-conversion superheterodyne. Left bottom, antenna trImmer, 100-kc. calibrator switch; center, left, top to bottom, noise-limiter switch, volume control, sensitivity control; center, right, b.f.o. switch, a.g.c. speed, selectivity; right, headphone jack, b.f.o. pitch control. The dial is a National ICN. Front panel is 8% inches high; the receiver is mounted in a Bud CR-1741 rack cabinet.

choice of 4.5 Mc., approximately, for the first i.f. was based on the availability of surplus crystals around this frequency, with due consideration for minimizing spurious responses. A second i.f. of 50 kc. was chosen because it lent itself nicely to the utilization of low-cost TV horizontal-oscillator coils as i.f. transformers.

The two i.f. amplifiers at 50 kc. contribute the necessary adjacent-channel selectivity. Three degrees of selectivity are available, depending on the degree of capacitive coupling between the two windings of each i.f. transformer. The greater the number of capacitors switched in parallel—that is, the larger the coupling capacitance—the lower the coupling between the windings and thus the greater the selectivity.

A standard diode detector develops the audio output for all reception modes. The output of the detector is simultaneously applied to both the first audio amplifier and the audio a.g.c. circuit. A series-type noise limiter can be used on a.m. to reduce impulse-noise interference, but this type is ineffective on c.w. or s.s.b. because of the large amplitude of the b.f.o. injection voltage.

The b.f.o., a Hartley-type oscillator, can be tuned from 3 kc. above to 3 kc. below its 50-kc. center frequency by the tuning capacitor.

The first audio stage is a normal Class A voltage amplifier with its output either coupled to the grid circuit of the audio output tube or to a phone jack. High-impedance head-phones (20,000 ohns a.c. impedance or higher) are required. Plugging in the phones automatically disconnects the speaker. If low-impedance headphones are used, they can be connected to the speaker terminals. Capacitances shunting the grid resistors restrict the audio response to an upper limit of about 4000 cycles.

The audio output transformer couples to a lowimpedance (3.2-ohm) speaker. The 47-ohm resistor across the secondary protects the transformer in the absence of a speaker load.

The audio output of the detector is also amplified separately in the audio a.g.c. circuit and then



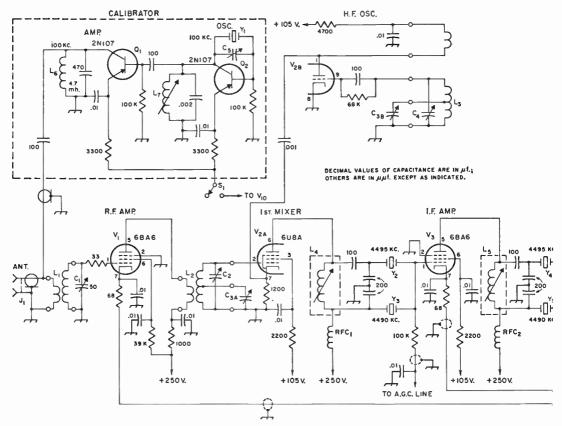


Fig. 5-52—Front-end circuit of the receiver. Unless otherwise specified, resistors are ½ watt; 0.01 and 0.02-μf. capacitors are disk ceramic, 600 volts; 0.5 capacitors are tubular paper or Mylar; capacitors below 0.01 μf. are mica; capacitors marked with polarities are electrolytic.

 C_1 —50- $\mu\mu$ f. variable (Hammarlund HF-50).

C2, C4—See coil table.

 C_3 —2-section variable, 5—28.5 $\mu\mu$ f. per section, double spaced (Hammarlund HFD-30-X).

C5-3-30-µµf. ceramic trimmer.

J₁—Coaxial receptacle, chassis mounting (SO-239).

L1, L2, L3-See coil table.

L₄, L₅—18-36-μh. slug-tuned (North Hills 120E coil mounted in North Hills S-120 shield can).

rectified to develop a negative voltage that can be used for a.g.c. on c.w. and s.s.b. Two different time constants are used in the rectifier filter circuit, for either fast- or slow-decay a.g.c.

The 100-kc. calibrator employs two 2N107 p-n-p transistors, one as the oscillator and the second as a 100-kc. amplifier. Its transistors obtain the necessary operating potential from the cathode resistor of the audio output tube. Output from the 100-kc. unit is capacity-coupled to the antenna winding of the r.f. coil. Calibrating signals at 100-kc. intervals are available on all frequencies covered by the receiver.

The calibrator unit is constructed in a separate Minibox so that it can be plugged into the accessory socket of the receiver or used as an individual unit powered by penlite cells.

The power supply, Fig. 5-54, is a full-wave rec-

L_s-4.7 mh. (Miller 6304).

L7-1-2-mh. slug-tuned (North Hills 120K).

RFC₁, RFC₂—100-µh. r.f. choke resonant at 4.4 Mc. (Miller 70F104A1).

S1-Single-pole rotary.

Y₁-100 kc. (James Knights H-93).

Y2, Y4-4495 kc. (surplus).

Ya, Y5-4490 kc. (surplus).

tifier with a choke-input filter. It provides approximately 250 volts d.c. under load. A 0.25- μf . capacitor is shunted across the 10-henry filter choke to form a parallel-resonant circuit at 120 cycles; this provides an increased impedance to the ripple component and thus reduces hum in the output of the supply.

The power-supply requirements are 250 volts at 110 milliamperes, and 6.3 volts at approximately 5 amperes. Any transformer-choke combination fulfilling the requirements can be used.

Front End

The use of plug-in coils for the front end eliminated the mechanical problems of a band-switching tuner, and also offered the possibility of realizing higher-Q tuned circuits. Ganged tuning of the r.f. amplifier along with the h.f.

DCS-500 135

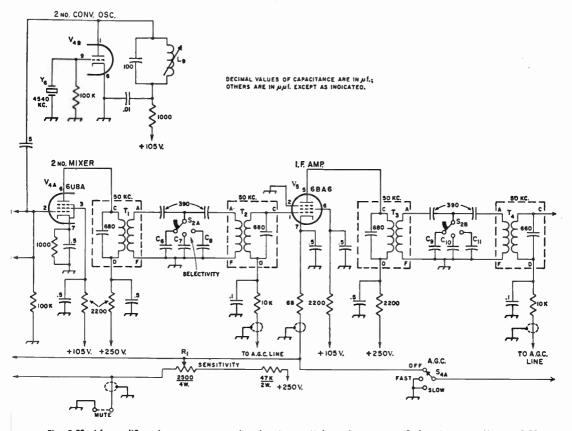


Fig. 5-53—1.f. amplifier, detector, a.g.c. and audio circuits. Unless otherwise specified, resistors are ½ watt; 0.01-and 0.02-μf. capacitors are disk ceramic, 600 volts; 0.5-μf. capacitors are tubular paper or Mylar; capacitors below 0.01 μf. are mica; capacitors marked with polarities are electrolytic.

C₆, C₇, C₈, C₉, C₁₀, C₁₁—0.01 mica (Aerovox CM-30B-103).

C₁₂--9-180-\(\mu\mu\mathre{f}\), mica compression trimmer.

 C_{13} -50- $\mu\mu$ f. variable (Hammarlund HF-50).

 C_{14} —0.1- μ f. paper (Sprague 2TM-P1).

J2-Phono jack.

J₈—Closed-circuit phone jack.

L₈-125 mh. (Meissner 19-6848).

L₉-9-18 μh., slug-tuned (North Hills 120D).

M1-0-1 d.c. milliammeter (Triplett 227-PL).

R₁-2500-ohm, 4-watt control, wire-wound.

R₂--0.5-megohm control, audio taper with push-pull type switch (S_0) (Mallory No. PP55DT1683).

R₈-1000-ohm, 1-watt control, wire-wound.

RFC₃-10 mh. (National R-50-1).

S₁, S₈-Rotary, 1 section, 1 pole, 2 position.

oscillator and mixer circuits was decided against because of the complexities it would cause in coil construction and the problem of keeping three stages tracking with each other. The r.f. amplifier has to be peaked separately by the antenna trimmer, but separate peaking insures maximum performance at all frequencies.

Construction

The receiver is constructed on a 12 \times 17 \times 2-inch aluminum chassis with an $8\frac{3}{4} \times$ 19-inch aluminum front panel, which permits it to be

S₂—Rotary, 2 section, 1 pole per section, progressively shorting. Switch section Centralab PA-12, index Centralab PA-302.

S₄—Rotary, 1 section, 5 poles per section (4 poles used), 3-position rotary switch (Centralab PA-2015).

 S_{δ} —Rotary, 1 section, 2 poles per section, 2 positions used. (Centralab PA-2003).

T₁-T₅, inc.—50-kc. i.f. transformers made from TV components (Miller 6183); see text.

Te-B.f.o. transformer (Miller 6183); see text.


T_T—Audio interstage transformer, 1:2 ratio (Thordarson 20A16).

T₈—Audio output transformer, 5000 to 4 ohms (Stancor 3856).

Ye-4540 kc. (surplus).

installed in a table-top rack cabinet. The general layout of components can be seen in Figs. 5-55 and 5-57. A good procedure to follow when starting to wire the receiver is first to complete the power supply and heater wiring, and then start wiring from the antenna toward the speaker. This allows proceeding in a logical order so that the work can be picked up readily at any time after an intermission.

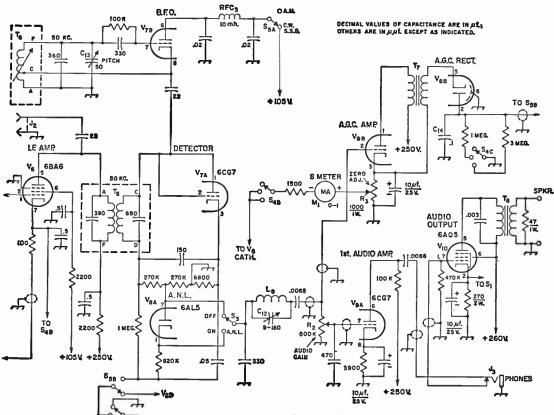In the front end (r.f. amplifier and first mixer), the use of short leads coupled with good quality ceramic tube and coil sockets, is highly



recommended. When mounting the sockets orient them so that the leads to the various points in the circuit will be as short as possible.

A.G.C. LINE


Millen coil shields (80008) are used around the plug-in coils in the front end - i.e., the r.f., mixer and oscillator - and the shield bases are mounted with the same screws that hold the ceramic coil sockets. All plug-in coils are wound with No. 26 enameled wire on Amphenol polystyrene forms, and Hammarlund APC-type airpadder capacitors are mounted in the recesses at the tops of the coil forms. After finishing a coil it is a good idea to fasten the winding and the trimmer capacitor in place with Duco cement. Decal each set of coils for a particular band and mount them on small wooden bases that have holes to take the pins. Then paint or stain each of the coil-set bases. The final result will be a neat and convenient arrangement for holding the coils for each band (Fig. 5-56). Plug-in coil data for each band are given in the coil table.

The tuning capacitor, C_{s} , is mounted on the chassis and reinforced by a bracket to minimize any rocking movement. This bracket is triangular in shape with a right-angle flange at the bottom. It is drilled to take the front bearing sleeve of the tuning capacitor and held firmly to it by the capacitor mounting nut and a lock washer, as

shown in Fig. 5-55. Flexing of the chassis can be minimized by the use of lengths of angle stock bolted to the chassis at strategic points throughout the receiver. Exact alignment of the tuning capacitor with the dial shaft is not always possible, so a flexible coupling (Millen 39016) is used.

When wiring the crystal filter keep leads as short and direct as possible, as this will minimize stray coupling between the input and output ends, which would deteriorate the performance of the crystal-filter circuits.

The 50-kc. i.f. circuits used Miller 6183 TV horizontal-oscillator replacement coils as i.f. transformers. These coils must be altered before they can be used. As they are supplied, the terminal lugs are brought out at the top of the can; these lugs must be reversed before the can is mounted. By applying slight pressure to the phenolic coil form the assembly will slide out of the aluminum shield can and then can be reversed. However, before reassembling the unit a few slight changes must be made. There are actually two separate windings; each one will be tuned and used either as a primary or secondary for the 50-kc. i.f. transformer. The tap on the large winding must be lifted off the soldering lug C, taped, and tucked away, being careful not to break it; this leaves just the lead from the small winding on terminal C. Terminals A and F represent the large winding. The small coil is tuned by connecting a 680-μμf. mica capacitor between terminals C and D; these capacitors should be DCS-500 137

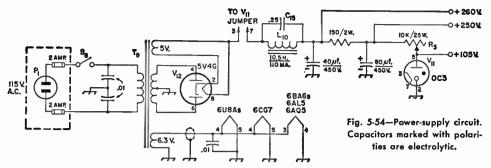

 C_{18} —0.25- μ f. paper, 600 volts. L_{10} —Filter choke, 10.5 henry, 110 ma. (Knight 62 G 139). P_{1} —Fuse plug.

S₀—See R₂, Fig. 5-55.
T₉—Power tronsformer, 700 v. c.t., 120 ma.; 5 v., 3 amp.;
6.3 v., 4.7 amp. (Knight 62 G 044).

fastened on the soldering lugs inside the shield can. The can is then slipped back over the coil and capacitor, keeping in mind that the lugs must come out the bottom, and the assembly is ready for mounting on the chassis.

The b.f.o. coil is also a Miller 6183, and the procedure for reversing the assembly before mounting is identical to that followed with the 50-kc. transformers. However, it is not necessary to alter any of the wiring in the b.f.o. transformer, since only the large winding (A-F) and its tap (C) is used.

Point-to-point wiring is recommended, along with generous use of both insulated tie points and ground lugs. Use of shielded wire facilitates routing wires throughout the receiver as the shields can be spot-soldered to ground lugs and to each other in bundles. When wiring, mount components at right angles to the chassis sides wherever possible; this helps give the finished unit a neat appearance. In critical circuits, however, do not sacrifice short and direct leads for the sake of making the unit look pretty.

Placing the receiver in a rack cabinet and

Fig. 5-55—The power supply is built along the back of the chassis; filter capacitor and VR tube are just in back of the filter choke in this view. The crystal calibrator unit at right is cushioned by rubber bumpers mounted on the receiver chassis. C5 is on top of the calibrator unit. Front-end coil shields are at the top right in this photograph, along with the tuning capacitor brocket and flexible coupling. The on-off switch, Se, on rear of the audio gain control, is a new push-pull type. Filter crystals are grouped behind the volume control, and the second conversion oscillator crystal is slightly to their left. The 4.5-Mc. i.f. transformers (in the small shield cans) are close to the filter crystals. The b.f.o. coil is at the extreme left in this view; all other large cans contain the 50-kc. i.f. transformers. Connections on the back chassis wall, left to right, are the muting terminals. B-plus output for auxiliary use, speaker terminals, i.f. output (phono jack), and antenna input connector.


marking all controls on the front panel with decals also helps in giving the finished receiver a neat and "commercial" appearance.

The Calibrator

The 100-kc. calibrator is built in a separate $4 \times 4 \times 2$ -inch aluminum box and plugs into the accessory socket at the left rear of the receiver chassis. Fig. 5-58 shows the internal construction. The accessory socket provides the necessary operating voltage for the transistors and offers a convenient means for coupling the 100-kc. harmonics out of the calibrator into the receiver. If the calibrator is to be used as a self-contained unit it must be supplied with 7 to 10 volts.

I.F. Alignment

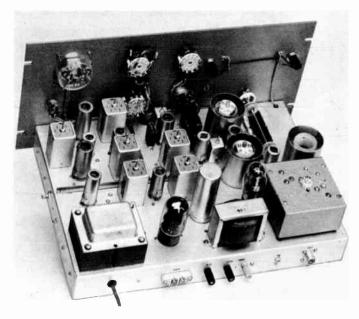Before starting alignment of the receiver, first determine whether the audio stages are functioning correctly. An audio signal should be coupled to the top end of the volume control, and varying the control should change the output level of the audio signal. If an audio signal is not available, the 60-cycle heater voltage will provide a convenient audio signal for checking.



DCS-500 COIL TABLE


All coils wound with No. 26 enameled wire on 1½-inch diameter polystyrene forms. R.f. coil forms are four-prong (Amphenol 24-4P); mixer and oscillator coils are five-prong (Amphenol 24-5P). C₂ and C₄ are Hammarlund APC-50 except on 3.5 Mc., which takes APC-75. Taps are counted from ground end. Primaries and ticklers are close-wound in the same direction as the main coil at bottom of coil form; grid and plate (or antenna) connections at outside ends.

, Barrella, commentations at outside citas.		
Band	Secondary	Primary or Tickler
3.5 Mc.	L1, 45¼ turns close-wound. L2, 36¼ turns close-wound, tapped at 26¼ turns. L3, 28¼ turns close-wound, tapped at 19 turns.	1034 turns, 36-inch spacing from secondary. 1134 turns, 36-inch spacing from secondary. 734 turns, 36-inch spacing from secondary.
7 Mc.	L1, 26¼ turns, close-wound. L2, 18¾ turns spaced to 1 inch. Tapped at 9¾ turns. L3, 17¾ turns spaced to ¾ inch. Tapped at 4¾ turns.	734 turns, ¼-inch spacing from secondary. 634 turns, ¾-inch spacing from secondary. 734 turns, ¼-inch spacing from secondary.
14 Mc.	L_1 , 13¼ turns spaced to $\frac{6}{10}$ inch. L_2 , 10¾ turns spaced to 1 inch. Tapped at 3 turns. L_3 , 5¾ turns spaced to $\frac{15}{16}$ inch. Tapped at 1¼ turns.	634 turns, \$\footnote{1}_6\text{-inch spacing from secondary.} 534 turns, \$\footnote{1}_6\text{-inch spacing from secondary.}
21 Mc.	L_1 , 9½ turns spaced to ½ inch. L_2 , 7¾ turns spaced to $1\frac{1}{2}$ inches. Tapped at 2 turns. L_3 , 6¼ turns spaced to $\frac{15}{2}$ inch. Tapped at 2 turns.	634 turns, \$\forall_{16}\text{-inch spacing from secondary.} 534 turns, \$\forall_{16}\text{-inch spacing from secondary.} 334 turns, \$\forall_{16}\text{-inch spacing from secondary.}
28 Mc.	L_1 , 6½ turns spaced to $\frac{7}{16}$ -inch. L_2 , 5½ turns spaced to $\frac{1}{2}$ inches. Tapped at 2 turns. L_3 , 4¾ turns spaced to ¾ inch. Tapped at $\frac{1}{2}$ turns.	5¾ turns, ¼-inch spacing from secondary. 4¾ turns, ¼-inch spacing from secondary. 2¾ turns, ¼-inch spacing from secondary.

Fig. 5-56—Each set of coils is provided with a wooden base for storage. C₂ and C₄ are mounted in the recesses at the tops of the oscillator and mixer coil forms.



Fig. 5-57—The potentiometer for S-meter adjustment and the audio output transformer are on the right chassis wall in this view. The 50-kc. i.f. trap is located just above the power transformer in the lower right-hand corner. The antenna trimmer is located at extreme life center. The crystal filter sockets are at top center, and to their left on the front wall is the calibrator switch S₁. To the right of the calibrator switch is the sensitivity control, followed to the right by the selectivity switch S₂ and the b.f.o. pitch-control capacitor. The octal accessory socket for the calibrator is at the lower left. As shown, shielded wire spot-soldered together in bundles can be routed conveniently to various points in the receiver. Ceramic sockets are used throughout the front end (center left). Mounting components parallel with the chassis sides helps give the finished unit a neat appearance.

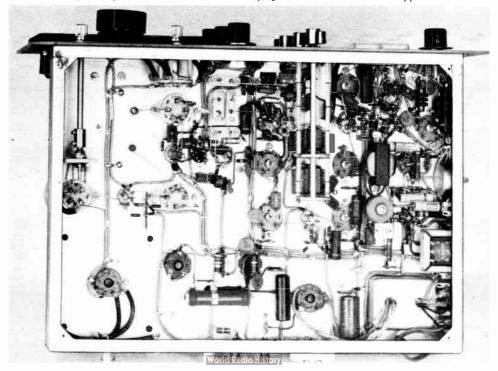


There are various ways to approach the alignment problem. A 50-kc. signal generator can be used; however, these are hard to come by. Some of the better audio oscillators go as high as 50 kc. and can be used for alignment purposes. A second, and possibly superior, method is to use any of the numerous signal generators which will deliver 4.5-Mc. output; fed into the first i.f. amplifier grid, the 4.5-Mc. signal will beat against the second conversion oscillator to produce a 50-kc. i.f. signal which then can be used for alignment. This method also insures that the first i.f. signal will fall within the crystal filter bandpass in case the crystal frequencies are not exact. When aligning, connect a d.c. voltmeter (preferably a v.t.v.m.) across the detector load resistor (point D of T_6 and chassis), set S_2 for high selectivity, (all capacitors in), turn the i.f. gain control about three-quarters open, and tune both the plate circuit of the second conversion oscillator and the 50-kc, i.f. transformers for maximum output, as indicated on the meter. The output of the signal generator should not be modulated, and at the start will most likely be "wide open." However, as alignment progresses the output of the generator will have to be progressively decreased. When aligning the i.f. transformers there should be a definite peak in output as each circuit is brought through resonance. If a particular coil does not peak, that coil and its associated circuits should be checked. After peaking one winding of a transformer, recheck the other; it may need touching up. After alignment of all the 50-kc. coils is completed, go back and "rock" each coil slug to be sure it is peaked for maximum output. This completes the 50-kc. alignment.

Leave the signal generator on, set the b.f.o. pitch control at half capacitance, turn the b.f.o. on, and adjust its coil slug for zero beat with the 50-kc. i.f. signal. Varying the pitch control over its range should produce a tone with a maximum frequency of 3 kc. either side of zero beat.

Next, the 50-kc. trap on the output of the detector should be adjusted. Connect the vertical input terminals of an oscilloscope between the plate of the first audio amplifier and chassis, turn on the b.f.o., and adjust C_{12} for minimum 50-kc. signal on the scope. This trap, made up of C_{12} and L_{8} , attenuates any 50-kc. feed-through.

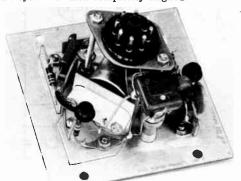The first-i.f. coils at 4.5-Mc. should next be adjusted. Couple the signal generator to the grid of the first mixer and peak L_4 and L_5 for maximum deflection of the v.t.v.m. at the detector. The i.f. system is then completely aligned.



Front-End Alignment

To adjust the front end, plug in a set of coils and check the oscillator frequency range either with a calibrated g.d.o. or on a calibrated general-coverage receiver, the latter being preferable. Keep in mind that the oscillator works 4.5 Mc. above the signal on 80, 40 and 20 meters, and 4.5 Mc. below the signal frequency on the 15- and 10-meter bands. This means that on 15 and 10 meters the oscillator trimmer capacitor, C4, must be at the larger-capacitance setting of the two that bring in signals. After establishing the correct frequency range of the oscillator, inject a signal at the low end of the band into the antenna terminals and peak the mixer capacitor, C2, and the antenna trimmer, C_1 , for maximum signal. Then move the test signal to the high end of the band and recheck the mixer trimmer capacitor (the antenna trimmer also will have to be repeaked) for correct tracking. If C2 has to be readjusted, spread the mixer coil turns apart or compress them together until the signal strength is uniform at both ends of the band, without readjustment of C_2 . If the mixer trimmer capacitance had to be increased at the high-frequency end of the band to maintain tracking, the coil tap is too far up the coil and the turns below the tap must be spread apart or the tap itself must be moved down. If the trimmer capacitance has to be decreased the tap is too low. Coil specifications might possibly have to be altered slightly from those given in the table, particularly on the higher frequencies, because of variations in strays from one receiver to another.

General .

Adjustment of the calibrator is relatively straightforward, and should present no problems. Turn on the calibrator and you should hear the 100-kc. harmonics on whatever band you happen to be using. Once it is determined that the unit is working correctly, the only adjustment necessary is to set the frequency of the calibrator exactly. The usual reference is WWV or any broadcast station that is on a frequency which is a wholenumber multiple of 100 kc. The frequency tolerance for standard broadcast stations is 20 cycles, thus b.c. stations represent a source for accurate frequency determination.

Using a general-coverage or b.c. receiver, tune in either WWV or a known broadcast station and adjust the calibrator trimmer C_{δ} for zero beat. The calibrator will then provide accurate 100-kc.

Fig. 5-58—Inside view of the calibrator unit. The 100-kc. oscillator coil, L_{18} , is at the right, the oscillator transistor, Q_2 , is in the foreground mounted to the crystal socket, and the amplifier transistor, Q_1 , is mounted at the right on a terminal strip. The 100-kc. crystal is mounted horizontally between the plate and the octal plug. The plug can be mounted on 2-inch screws as shown in the photograph, or on the bottom plate of the Minibox, with flexible leads to the circuit. If the calibrator is to be used as a self-contained unit (see text) the octal plug is not necessary.

140

signals that can be used for frequency determination and band-edge marking.

The first intermediate frequency can be altered slightly to facilitate the use of particular sets of crystals available. However, if the deviation is more than 20 kc. or so, slight changes may be needed in the h.f. oscillator coil specifications to maintain the proper bandspread.

If the receiver is to be worked in a rack cabinet as shown in Fig. 5-51, or if a cover plate is attached to the bottom of the receiver chassis, minor alignment touch-up may be necessary.

Spraying the receiver chassis with a light coat of clear plastic lacquer before mounting any of

HIGH-FREQUENCY RECEIVERS

the components will prevent fingerprints and oxidation of the chassis.

The audio output stage has adequate power to drive a 5- or 6-inch speaker, which may be mounted in a small open-back metal utility box.

The i.f. output jack at the rear provides a convenient way of attaching accessory devices such as an oscilloscope for modulation checking.

A side-by-side comparison of the finished receiver with some of the better-quality commercial units will show that this receiver can hold its own in sensitivity, selectivity and stability. Needless to say, the more care taken in construction, wiring and alignment the better the results.

A TRANSISTORIZED Q MULTIPLIER

A "Q multiplier" is an electronic device that boosts the Q of a tuned circuit many times beyond its normal value. In this condition the single tuned circuit has much greater selectivity than normal, and it can be utilized to reject or amplify a narrow band of frequencies. There are vacuumtube versions of the Q-multiplier circuit, but the transistorized Q multiplier to be described has the advantage that it eliminates a power-supply problem and is very compact.

Circuit and Theory

Parallel-tuned circuits have been used for years as "suck-out" trap circuits. Properly coupling a parallel-tuned circuit loosely to a vacuum-tube amplifier stage, it will be found that the amplifier stage has no gain at the frequency to which the trap circuit is tuned. The additional tuned circuit puts a "notch" in the response of the amplifier. The principle is used in TV and other amplifiers to minimize response to a narrow band of frequencies. Increasing the Q of the trap circuit reduces the width of the rejection notch.

The transistorized Q multiplier makes use of the above effect for its operation. A tuned circuit is made regenerative to increase its Q and is coupled into the i.f. stage of a receiver. By changing the frequency of the regenerative circuit, the sharp notch can be moved about across the passband of the receiver. The width of the notch is changed by controlling the amount of regeneration.

Fig. 5-59—Circuit diagram of the 455-kc. transistorized Q multiplier. Unless otherwise indicated, capacitances are in $\mu\mu f$., resistances are in ohms, resistors are $\frac{1}{2}$ watt.

MIXER WI CA

C₁—15-μμf. variable capacitar (Hammarlund HF-15).
L₁—1000–2000-μh. slug-tuned coil (North Hills 120-K.
North Hills Electric Co., Mineola, N. Y.).
L₂—500–1000-μh. slug-tuned coil (Narth Hills 120-J).
Q₁—CK768 PNP junctian transistar.
S₁—Part of R₁.
W₁—Three-faat length of RG-58/U cable.


Although it seems paradoxical, the transistorized Q multiplier with no change in circuitry will also permit "peaking" an incoming signal the way a vacuum-tube Q multiplier does. The mode of operation is selected by adjustment of the regeneration control, and this then usually requires a slight readjustment of the frequency control. The peaking effect is not quite as pronounced as the notch, but it is still adequate to give fairly good single-signal c.w. reception with a receiver of otherwise inadequate selectivity.

The regenerative circuit builds up the signal and feeds it back to the amplifier at a higher level and in the proper phase to add to the original signal. The notch effect described earlier works in a similar manner except that the tuning of the regenerative circuit is such that it feeds back the signal out of phase.

The schematic diagram of the Q multiplier is shown in Fig. 5-59. The inductor L_1 furnishes coupling from the receiver to the Q multiplier, and C_4 is required to prevent short-circuiting the receiver's plate supply. The multiplier proper consists of the tunable circuit $C_1C_3L_2$ connected to a transistor in the collector-tuned commonbase oscillator circuit using capacitive feedback via C_2 . Regeneration is controlled by varying the d.c. operating voltage through dropping resistor R_1 .

Layout

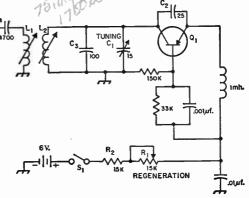The unit and power supply are built in a small



aluminum "Minibox" measuring $5 \times 2\frac{1}{4} \times 2\frac{1}{4}$ inches (Bud CU-3004) and the operating controls are mounted on a lucite or aluminum subpanel. All parts of the unit are built on one half of the box. This feature not only simplifies construction but makes a battery change a simple job, even if this is required only a couple of times a year.

All major components, such as the two slugtuned coils, tie point, battery holder, regeneration and tuning controls, are mounted directly on the box and subpanel. The remaining resistors, capacitors and the single transistor are supported by their connections to the above parts.

The two slug-tuned coils, L_1 and L_2 , are centered on the box and spaced one inch apart on centers. Operating controls C_1 and R_1 are placed $1\frac{1}{4}$ inches from the ends of the subpanel and centered. The tie point mounts directly behind tuning control C_1 .

Power for the unit is supplied by four penlight cells (type 912) which are mounted in the battery holder (Lafayette Radio Co. Stock No. MS-170) directly behind regeneration control R_1 . Total drain on the battery never exceeds 0.2 ma.

Connection to the receiver is made with a threefoot length of RG-58/U cable brought through the rear wall of the Minibox. A rubber grommet should be placed in the hole to prevent chafing of the cable insulation.

When soldering the transistor in place, be sure to take the usual precautions against heat damage.

Alignment

After completing the wiring (and double-checking it) connect the open end of the three-foot cable to the plate circuit of the receiver mixer tube. This can be done in a permanent fashion by soldering the inner conductor of the cable to the plate pin on the tube socket or any point that is connected directly to this pin, and by soldering the shield to any convenient nearby ground point. If you are one of those people who is afraid to take the bottom plate off his receiver, and you have a receiver with octal tubes, a "chicken connection" can be made by removing the mixer tube and wrapping a short piece of small wire around the plate pin. Reinsert the tube in its socket and solder the center conductor of the coax to the small wire coming from the plate pin. Now ground the coax shield to the receiver chassis. It is important to keep the lead from the tube pin to the coax as short as possible, to prevent stray pickup.

Check the schematic diagram of the receiver for help in locating the above receiver connections.

Turn on the receiver and tune in a signal strong enough to give an S-meter reading. Any decent signal on the broadcast band will do. Next, tune the slug on L_1 until the signal peaks up. You are tuning out the reactance of the connecting cable, and effectively peaking up the i.f. If the receiver has no S meter, use an a.c. voltmeter across the audio output. When this step has been successfully completed the Q multiplier is properly connected to the receiver and when



Fig. 5-60—View of the Q multiplier showing its single connecting cable to the receiver. The box can be placed in any convenient spot on or around the receiver.


switched to "off" (S_1 opened) will not affect normal receiver operation.

The next step is to bring the multiplier into oscillation, and to adjust its frequency to a useful range. Set the tuning control to half capacity and advance the regeneration control to about half open. This latter movement also turns the power on. Tune the receiver to a clear spot and set the receiver b.f.o. to the center of the pass-band. Now adjust the slug of L_2 . The multiplier should be oscillating, and somewhere in the adjustment of L_2 a beat note will be heard from the receiver. This indicates the frequency of oscillation is somewhere on or near the i.f. Swing this into zero beat with the b.f.o.

Final Adjustment

One of the best ways to make final alignment is to simulate an unwanted heterodyne in the receiver and adjust the Q multiplier for maximum

Fig. 5-61—The Q multiplier and its battery supply are combined in one small Minibox. The single transistor is visible near the top right corner.

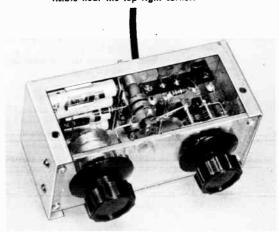

attenuation of the unwanted signal. To do this, tune in a moderately weak signal with the b.f.o. on. A broadcast station received with the antenna disconnected will do. The b.f.o. will beat with the incoming signal, producing an audio tone. Adjust the b.f.o. for a tone of about 1 kc. or so.

Back off on control R_1 until the oscillator becomes regenerative. By alternately adjusting the tuning control, C_1 , and the regeneration control, R_1 , a point can be found where the audio tone disappears, or at least is attenuated. Some slight retouching of L_2 may have to be done in the above alignment, since the movement of any one control tends to "pull" the others. The optimum situation is to have the tuning control C_1 set at

about half capacity when the notch is in the center of the passband.

If you happen to get a super active transistor and the regeneration control does not have the range to stop oscillator action, increase the value of the series resistor R_2 . Conversely, if the unit fails to oscillate, reduce the value of R_2 .

Note that the audio tone can be peaked as well as nulled. If it can not be peaked, a little more practice with the controls should produce this condition. In the unit shown here, the best null was produced with the regeneration control turned only a few degrees. Optimum peak position was obtained with the regeneration control almost at the point of oscillation.

CONELRAD

Effective January 2, 1957, the "Conelrad" rules became part of the amateur regulations. Essentially, compliance with the rules consists of monitoring a broadcast station — standard band, f.m. or TV — either continuously or at intervals not exceeding ten minutes, during periods in which the amateur transmitter is in use. On receipt of a Conelrad Alert all transmitting must cease, except as authorized in 12.193 and 12.194 of the FCC regulations.

The existence of an Alert may be determined as outlined in 12.192(b)(3). Operation during

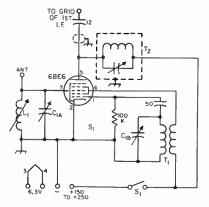


Fig. 5-62—Converter circuit for monitoring broadcast stations in connection with a communications receiver. Capacitances are in $\mu\mu$ f.

C_{1A}, C_{1B}—Two-gang broadcast capacitor, oscillator section according to i.f. to be used.

L₁-Loop stick.

T₁—B.c. oscillator transformer (for i.f. to be used).

T₃—I.f. coil and trimmer. This can be taken from an i.f. transformer, or the transformer can be used intact, the output being taken from the secondary.

Note: If only one broadcast station is to be monitored C_{1A} and C_{1B} can be padder-type capacitors (or a combination of padding and fixed capacitance as required) adjusted for the desired station and intermediate frequencies. Other types of tubes may be used. Power can be taken from the receiver.

hours when local broadcast stations are not on the air will require tuning through the standard broadcast band to determine if operation appears to be normal. The presence of any U. S. broadcast stations on frequencies other than 640 and 1240 kc. indicates normal operation.

Perhaps the simplest form of compliance is by means of a simple converter working into the i.f. amplifier of the regular station receiver. A typical circuit is shown in Fig. 5-62. The converter can be built in a small metal case and mounted at a convenient spot on the receiver to that S_1 can be closed at regular intervals for checking the broadcast station. As an alternative, the converter can be mounted out of the way at the rear of the receiver and the switch leads brought out to a convenient spot.


A "FAIL-PROOF" CONELRAD ALARM

The conelrad alarm shown in Fig. 5-63 uses a small b.c. receiver to furnish both audible and visible indications of a Conelrad Alert (the receiver may still be used for normal reception).

With the receiver tuned to a broadcast carrier and the alarm circuit in operation, a green "safe" light indicates that all is well on the broadcast band. When the broadcast carrier goes off, as it will in a Conelrad Radio Alert, the green light goes out, a red "danger" light comes on, a buzzer sounds, and the 115-volt a.c. line to the transmitter is opened up. In other words, the device puts you off the air! The audible and visible warnings also are given in the event of a component failure in either the control receiver or the alarm. Even the disappearance of the 115-volt supply will not go unnoticed, since in that case the green "safe" light will go out, indicating that the alarm is inoperative.

The alarm requires a minimum of 0.7 volts (negative) from the receiver's a.g.c. (automatic gain control) circuit for dependable operation. Receivers having one stage of i.f. amplification will develop at least this much a.g.c. voltage when tuned to a signal of reasonable strength. But watch out for the "superhets" that do not have an i.f. stage; they are of little value as a source of control voltage for the alarm. You

Conelrad 143

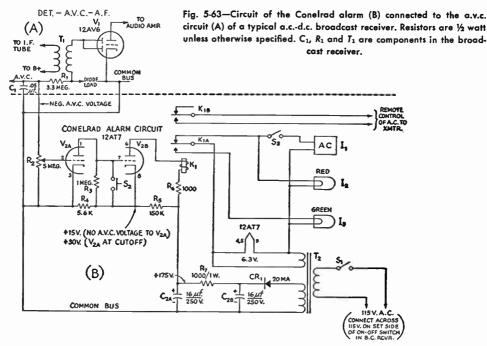

l₁—6-volt a.c. buzzer (Edwards 725). l₂, l₈—6-volt pilot lamp, No. 47. K₁—D.p.d.t. sensitive relay, 5000-ohm coil. R₂—5-megohm potentiometer.

can usually find out if the receiver has an i.f. stage by looking at the tube list pasted on either the chassis or the inside of the cabinet.

The circuit of the alarm is shown in section B, Fig. 5-63. Section A is a typical a.g.c.-detector-first audio stage of an a.c.-d.c. receiver, and shows how the alarm circuit is tied into a receiver.

Although a 12AV6 is shown as the detector, other tubes may be used in some receivers. However, the basic circuit will be much the same.

Finding the a.g.c. (a.v.c.) line in the jumble beneath the chassis of the ordinary a.c.-d.c. receiver is not always easy. Here are a few hints:

Using section A, Fig. 5-63, as a guide, locate the detector tube socket. Trace out the leads going to the secondary of the last i.f. transformer, T_1 . This transformer usually will be adjacent to the detector tube. The lower end of the secondary winding will be connected to several different resistors, one of these being the diode-load filter resistor (approximately 50K in most circuits) and another the a.g.c. filter resistor, R_1 . The value of the latter resistor is ordinarily above one megohm. Trace through R_1 in the direction of the arrow (Fig. 5-63), until you locate the fairly high value (0.05 μ f. or so) a.g.c. filter capacitor, C_1 . Now you have the a.g.c. line clearly identified and the tap for the alarm circuit may be made.

Notice that the cathode of V_1 and the cold side of C_1 are both returned to a common bus or -B line, not directly to the chassis. Also observe that the return for the alarm circuit is made to the common bus in the receiver, not to the chassis of

S₁, S₂—S.p.s.t. rotary switch.
S₂—Momentary-contact switch (Switchcraft 101).
T₂—Replacement-type power transformer, 150 volts, 25
ma.; 6.3 volts, 0.5 amp. (Merit P-3046).

the set. Do not ground this lead to the chassis or connect it to any exposed metal parts. If there is any difficulty in locating the common bus in the vicinity of the detector stage, check back from the negative side of the power-supply filter capacitors, as this point is always attached to the common bus.

The monitor should be built in an insulated box of some kind and not in a metal case. The box can be made of plywood, or a bakelite instrument case. The bakelite case is ideal for the application, but it must be handled with care during construction to avoid scratching, chipping, or breakage. Be especially careful when drilling large holes such as those used in mounting the pilot-lamp assemblies and switches, because a large drill tends to bind and crack the case.

The chances are pretty good that right after the receiver and the monitor have been turned on the red lamp will light and - if you haven't had the foresight to open S_{\bullet} to prevent the noise the buzzer will sound. Tune the receiver to a broadcast station and see if the red light goes out and the green light comes on. If this happens, close S, and you're all set for conelrad compliance. If the "safe" light does not come on, tune around for a signal strong enough to actuate the alarm. Should the signal of greatest apparent strength fail to trigger the monitor, leave the receiver tuned to this signal and then momentarily press S_3 . The alarm should now lock on "safe." provided the a.g.c. circuit delivers 0.7 volt or more to V_{\perp} .

High-Frequency Transmitters

The principal requirements to be met in c.w. transmitters for the amateur bands between 1.8 and 30 Mc. are that the frequency must be as stable as good practice permits, the output signal must be free from modulation and that harmonics and other spurious emissions must be eliminated or reduced to the point where they do not cause interference to other stations.

The over-all design depends primarily upon the bands in which operation is desired, and the power output. A simple oscillator with satisfactory frequency stability may be used as a transmitter at the lower frequencies, as indicated in Fig. 6-1A, but the power output obtainable is small. As a general rule, the output of the oscillator is fed into one or more amplifiers to bring the power fed to the antenna up to the desired level, as shown in B.

An amplifier whose output frequency is the same as the input frequency is called a straight amplifier. A buffer amplifier is the term sometimes applied to an amplifier stage to indicate that its primary purpose is one of isolation, rather than power gain.

Because it becomes increasingly difficult to maintain oscillator frequency stability as the frequency is increased, it is most usual practice in working at the higher frequencies to operate the oscillator at a low frequency and follow it with one or more frequency multipliers as required to arrive at the desired output frequency. A frequency multiplier is an amplifier that delivers output at a multiple of the exciting frequency. A doubler is a multiplier that gives output at twice the exciting frequency is tripler multiplies the exciting frequency by three, etc. From the viewpoint of any particular stage in a transmitter, the preceding stage is its driver.

As a general rule, frequency multipliers should not be used to feed the antenna system directly, but should feed a straight amplifier which, in turn, feeds the antenna system, as shown in Fig. 1-C, D and E. As the diagrams indicate, it is often possible to operate more than one stage from a single power supply.

Good frequency stability is most easily obtained through the use of a crystal-controlled oscillator, although a different crystal is needed for each frequency desired (or multiples of that frequency). A self-controlled oscillator or v.f.o. (variable-frequency oscillator) may be tuned to any frequency with a dial in the manner of a receiver, but requires great care in

design and construction if its stability is to compare with that of a crystal oscillator.

In all types of transmitter stages, screen-grid tubes have the advantage over triodes that they require less driving power. With a lower-power exciter, the problem of harmonic reduction is made easier. Most satisfactory oscillator circuits use a screen-grid tube.

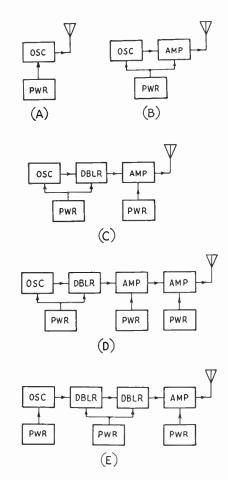


Fig. 6-1—Block diagrams showing typical cambinations of ascillatar and amplifiers and pawer-supply arrangements for transmitters. A wide selection is passible, depending upon the number of bands in which aperation is desired and the power autput.

Oscillators 145

CRYSTAL OSCILLATORS

The frequency of a crystal-controlled oscillator is held constant to a high degree of accuracy by the use of a quartz crystal. The frequency depends almost entirely on the dimensions of the crystal (essentially its thickness); other circuit values have comparatively negligible effect. However, the power obtainable is limited by the heat the crystal will stand without fracturing. The amount of heating is dependent upon the r.f. crystal current which, in turn, is a function of the amount of feedback required to provide proper excitation. Crystal heating short of the danger point results in frequency drift to an extent depending upon the way the crystal is cut. Excitation should always be adjusted to the minimum necessary for proper operation.

Crystal-Oscillator Circuits

The simplest crystal-oscillator circuit is shown in Fig. 6-2A. An equivalent circuit is shown in Fig. 6-2B, where C_4 represents the grid-cathode capacitance and C_5 indicates the plate-cathode, or output capacitance. The ratio of these capacitors controls the excitation for the oscillator, and good practice generally requires that both of these capacitances be augmented

factorily minimized by proper choice of the oscillator tube.

The circuit of Fig. 6-3A is known as the Tritet. The oscillator circuit is that of Fig. 6-2C. Excitation is controlled by adjustment of the tank L_1C_1 , which should have a low L/C ratio, and be tuned considerably to the high-frequency side of the crystal frequency (approximately 5 Mc. for a 3.5-Mc. crystal) to prevent over-excitation and high crystal current. Once the proper adjustment for average crystals has been found, C_1 may be replaced with a fixed capacitor of equal value.

The oscillator circuit of Fig. 6-3B is that of Fig. 6-2A. Excitation is controlled by C_9 .

The oscillator of the grid-plate circuit of Fig. 6-3C is the same as that of Fig. 6-3B, except that the ground point has been moved from the cathode to the plate of the oscillator (in other words, to the screen of the tube). Excitation is adjusted by proper proportioning of C_6 and C_7 .

When most types of tubes are used in the circuits of Fig. 6-3, oscillation will stop when the output plate circuit is tuned to the crystal frequency, and it is necessary to operate with the plate tank circuit critically detuned for maximum output with stability. However, when the 6AG7, 5763, or the lower-power 6AH6 is used

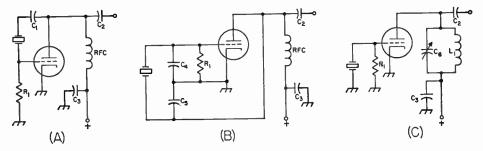


Fig. 6-2—Simple crystal oscillator circuits. A—Pierce. B—Equivalent of circuit A. C—Simple triode oscillator. C_1 is a plate blocking capacitor, C_2 an output coupling capacitor, and C_3 a plate bypass. C_4 and C_5 are discussed in the text. C_6 and L_1 should tune to the crystal fundamental frequency. R_1 is the grid leak.

by external capacitors, to provide better control of the excitation.

The circuit shown in Fig. 6-2C is the equivalent of the tuned-grid tuned-plate circuit discussed in the chapter on vacuum-tube principles, the crystal replacing the tuned grid circuit.

The most commonly used crystal-oscillator circuits are based on one or the other of these two simple types, and are shown in Fig. 6-3. Although these circuits are somewhat more complicated, they combine the functions of oscillator and amplifier or frequency multiplier in a single tube. In all of these circuits, the screen of a tetrode or pentode is used as the plate in a triode oscillator. Power output is taken from a separate tuned tank circuit in the actual plate circuit. Although the oscillator itself is not entirely independent of adjustments made in the plate tank circuit when the latter is tuned near the fundamental frequency of the crystal, the effects can be satis-

with proper adjustment of excitation, it is possible to tune to the crystal frequency without stopping oscillation. The plate tuning characteristic should then be similar to Fig. 6-4. These tubes also operate with less crystal current than most other types for a given power output, and less frequency change occurs when the plate circuit is tuned through the crystal frequency (less than 25 cycles at 3.5 Mc.).

Crystal current may be estimated by observing the relative brilliance of a 60-ma. dial lamp connected in series with the crystal. Current should be held to the minimum for satisfactory output by careful adjustment of excitation. With the operating voltages shown, satisfactory output should be obtained with crystal currents of 40 ma. or less.

In these circuits, output may be obtained at multiples of the crystal frequency by tuning the plate tank circuit to the desired harmonic, the output dropping off, of course, at the higher harmonics. Especially for harmonic operation, a low-C plate tank circuit is desirable.

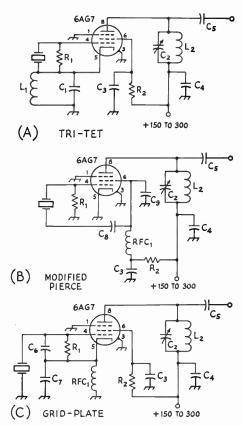


Fig. 6-3—Commonly used crystal-controlled oscillator circuits. Values are those recommended for a 6AG7 or 5763 tube. (See reference in text for other tubes.) C₁—Feedback-control capacitor—3.5-Mc. crystals—approx. 220-μμt. mica—7-Mc. crystals—approx. 150-μμt. mica.

C₂—Output tank capacitor—100- $\mu\mu$ f, variable for single-band tank; 250- $\mu\mu$ f, variable for two-band tank.

C₃-Screen bypass-0.001-\(mu f\). disk ceramic.

 $C_4-Plate\ bypass-0.001-\mu f.\ disk\ ceramic.$

 C_6 —Output coupling capacitor—50 ta 100 $\mu\mu$ f.

Co-Excitation-cantrol capacitor—30-µµf, trimmer.

C₇-Excitation capacitor-220- $\mu\mu$ f. mica for 6AG7; 100- $\mu\mu$ f. for 5763.

C₈-D.c. blocking capacitor-0.001-\mu f. mica.

Co-Excitation-control capacitar-220-µµf, mica.

R₁-Grid leak-0.1 megohm, 1/2 watt.

R₂-Screen resistor-47,000 ohms, 1 watt.

L₁—Excitation-control inductance—3.5-Mc. crystals—approx. 4 μh.; 7-Mc. crystals—approx. 2 μh.

L₂—Output-circuit coil—single band:—3.5 Mc.—17 μ h.; 7 Mc.—8 μ h.; 14 Mc.—2.5 μ h.; 28 Mc.—1 μ h. Two-band operation: 3.5 & 7 Mc.—7.5 μ h.; 7 & 14 Mc.—2.5 μ h.

RFC₁-2.5-mh. 50-ma. r.f. choke.

For best performance with a 6AG7 or 5763, the values given under Fig. 6-3 should be followed closely.

VARIABLE-FREQUENCY OSCILLATORS

The frequency of a v.f.o. depends entirely on the values of inductance and capacitance in the circuit. Therefore, it is necessary to take careful steps to minimize changes in these values not under the control of the operator. As examples, even the minute changes of dimensions with temperature, particularly those of the coil, may result in a slow but noticeable change in frequency called drift. The effective input capacitance of the oscillator tube, which must be connected across the circuit, changes with variations in electrode voltages. This, in turn, causes a change in the frequency of the oscillator. To make use of the power from the oscillator, a load, usually in the form of an amplifier, must be coupled to the oscillator, and variations in the load may reflect on the frequency. Very slight mechanical movement of the components may result in a shift in frequency, and vibration can cause modulation.

V.F.O. Circuits

Fig. 6-5 shows the most commonly used circuits. They are all designed to minimize the effects mentioned above. All are similar to the crystal oscillators of Fig. 6-3 in that the screen of a tetrode or pentode is used as the oscillator plate. The oscillating circuits in Figs. 6-5A and B are the Hartley type; those in C and D are Colpitts circuits. (See chapter on vacuum-tube principles.) In the circuits of A, B and C, all of the above-mentioned effects, except changes in inductance, are minimized by the use of a high-Q tank circuit obtained through the use of large tank capacitances. Any uncontrolled changes in capacitance thus become a very small percentage of the total circuit capacitance.

In the series-tuned Colpitts circuit of Fig. 6-5D (sometimes called the Clapp circuit), a high-Q circuit is obtained in a different manner. The tube is tapped across only a small portion of the oscillating tank circuit, resulting in very loose coupling between tube and circuit. The taps are provided by a series of three capacitors across the coil. In addition, the tube capacitances are shunted by large capacitors, so the effects of the tube—changes in electrode voltages and loading—are still further reduced. In contrast to the preceding circuits, the resulting tank circuit has a high L/C ratio and therefore the tank current is much lower than in the circuits using high-C tanks. As a result, it will usually

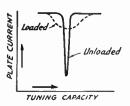


Fig. 6-4—Plate tuning characteristic of circuits of Fig. 6-3 with preferred types (see text). The plate-current dip at resonance broadens and is less pronounced when the circuit is loaded.

Oscillators 147


be found that, other things being equal, drift will be less with the low-C circuit.

For best stability, the ratio of C_{12} or C_{13} (which are usually equal) to $C_{10} + C_{11}$ should be as high as possible without stopping oscillation. The permissible ratio will be higher the higher the Q of the coil and the mutual conductance of the tube. If the circuit does not oscillate over the desired range, a coil of higher Q must be used or the capacitance of C_{12} and C_{13} reduced.


Load Isolation

In spite of the precautions already discussed, the tuning of the output plate circuit will cause a noticeable change in frequency, particularly in the region around resonance. This effect can be reduced considerably by designing the oscillator for half the desired frequency and doubling frequency in the output circuit. It is desirable, although not a strict necessity


if detuning is recognized and taken into account, to approach as closely as possible the condition where the adjustment of tuning controls in the transmitter, beyond the v.f.o. frequency control, will have negligible effect on the frequency. This can be done by substituting a fixed-tuned circuit in the output of the oscillator, and adding isolating stages whose tuning is fixed between the oscillator and the first tunable amplifier stage in the transmitter. Fig. 6-6 shows such an arrangement that gives good isolation. In the first stage, a 6C4 is connected as a cathode follower. This

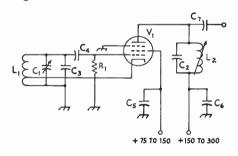


(A) HARTLEY

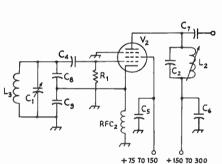

(c)COLPITTS

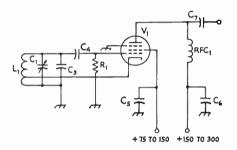

(B) HARTLEY - UNTUNED OUTPUT

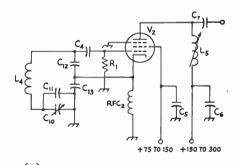

(D) SERIES - TUNED COLPITTS

Fig. 6-5-V.f.o. circuits. Approximate values for 3.5-4.0-Mc. output are given below. Grid circuits are tuned to half frequency (1.75 Mc.).

C1-Oscillator bandspread tuning capacitor-200-\(mu\mu\mi\)f.

C₂-Output-circuit tank capacitor-47-μμf.

C₃-Oscillator tank capacitor-600-\(\mu\mu\mathre{\psi}\), zero-temperature-coefficient mica.

C₄-Grid coupling capacitor-100-μμf. zero-temperature-coefficient mica.

C₅-Screen bypass-0.001-\mu f. disk ceramic.

C₆-Plate bypass-0.001-\mu f. disk ceramic.

 C_7 -Output coupling capacitor-50 to 100- $\mu\mu$ f. mica.

C₈—Oscillator tank capacitor—750-µµf. zero-temperature-coefficient mica.

Co-Oscillator tank capacitor-0.0033-4f. zero-temperature-coefficient mica.

C₁₀-Oscillator bandspread padder-100-\(mu\mu f\), variable air.

C11-Oscillator bandspread tuning capacitor-50-µµf. variable.

C₁₂, C₁₃—Tube-coupling capacitor—0.002-µf. zero-temperature-coefficient mica.

 $R_1=47,000 \text{ ohms, } \frac{1}{2} \text{ watt.}$

L1-Oscillator tank coil-10 \(mu\)h., tapped about onethird-way from grounded end.

L2-Output-circuit tank coil-20-40 \(\mu h., \) adjustable.

L3-Oscillator tank coil-10 µh.

L3-Oscillator tank coil-10 µh.

L-Oscillator tank coil-70 µh.

L5-Output coil-100-140 µh., adjustable.

RFC1-100 µh. r.f. choke.

V1-6AG7, 5763 or 6AH6 preferred; other types

V2-6AG7, 5763 or 6AH6 required for feedback capacitances shown.

drives a 5763 buffer amplifier whose input circuit is fixed-tuned to the approximate band of the v.f.o. output. For best isolation, it is important that the 6C4 does not draw grid current. The output of the v.f.o., or the cathode resistor of the 6C4 should be adjusted until the voltage across the cathode resistor of the 6C4 (as measured with a high-resistance d.c. voltmeter with an r.f. choke in the positive lead) is the same with or without excitation from the v.f.o. L_1 should be adjusted for most constant output from the 5763 over the band.

Chirp

In all of the circuits shown there will be some change of frequency with changes in screen and plate voltages, and the use of regulated voltages for both usually is necessary. One of the most serious results of voltage instability occurs if the oscillator is keyed, as it often is for break-in operation. Although voltage regulation will supply a steady voltage from the power supply and therefore is still desirable, it cannot alter the fact that the voltage on the tube must rise from zero when the key is open, to full voltage when the key is closed, and must fall back again to zero when the key is opened. The result is a chirp each time the key is opened or closed,

unless the time constant in the keving circuit is reduced to the point where chirp takes place so rapidly that the receiving operator's ear cannot detect it. Unfortunately, as explained in the chapter on keying, a certain minimum time constant is necessary if key clicks are to be minimized. Therefore it is evident that the measures necessary for the

reduction of chirp and clicks are in opposition, and a compromise is necessary. For best keying characteristics, the oscillator should be allowed to run continuously while a subsequent amplifier is keyed. However, a keyed amplifier represents a widely variable load and unless sufficient isolation is provided between the oscillator and the keyed amplifier, the keying characteristics may be little better than when the oscillator itself is keyed. (See keying chapter for other methods of break-in keying.)

Frequency Drift

Frequency drift is further reduced most easily by limiting the power input as much as possible and by mounting the components of the tuned circuit in a separate shielded compartment, so that they will be isolated from the direct heat from tubes and resistors. The shielding also will eliminate changes in frequency caused by movement of nearby objects, such as the operator's hand when tuning the v.f.o. The circuit of Fig. 6-5D lends itself well to this arrangement, since relatively long leads between the tube and the tank circuit have negligible effect on frequency because of the large shunting capacitances. The grid, cathode and ground leads to the tube can be bunched in a cable up to several feet long.

Variable capacitors should have ceramic insulation, good bearing contacts and should preferably be of the double-bearing type, and fixed capacitors should have zero temperature coefficient. The tube socket also should have ceramic insulation and special attention should be paid to the selection of the coil in the oscillating section.

Oscillator Coils

The Q of the tank coil used in the oscillating portion of any of the circuits under discussion should be as high as circumstances (usually space) permit, since the losses, and therefore the heating, will be less. With recommended care in regard to other factors mentioned previously, most of the drift will originate in the coil. The coil should be well spaced from shielding and other large metal surfaces, and be of a type that radiates heat well, such as a commercial air-

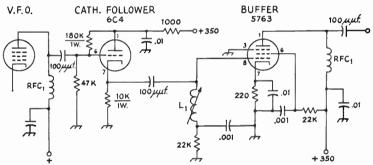


Fig. 6-6—Circuit af an isalating amplifier far use between v.f.a. and first tunable stage. Unless atherwise specified, all capacitances are in μf ., all resistars are $\frac{1}{2}$ watt. L_1 , for the 3.5-Mc. band, consists of 100-140 μh . adjustable inductor. RFC₁ is 100 μh . All capacitars are disk ceramic.

wound type, or should be wound tightly on a threaded ceramic form so that the dimensions will not change readily with temperature. The wire with which the coil is wound should be as large as practicable, especially in the high-*C* circuits.

Mechanical Vibration

To eliminate mechanical vibration, components should be mounted securely. Particularly in the circuit of Fig. 6-5D, the capacitor should preferably have small, thick plates and the coil braced, if necessary, to prevent the slightest mechanical movement. Wire connections between tank-circuit components should be as short as possible and flexible wire will have less tendency to vibrate than solid wire. It is advisable to cushion the entire oscillator unit by mounting on sponge rubber or other shock mounting.

Tuning Characteristic

If the circuit is oscillating, touching the grid of the tube or any part of the circuit connected to it will show a change in plate current. In tuning the plate output circuit without load, the plate current will be relatively high until it is tuned near resonance where the plate current will dip to a low value, as illustrated in Fig. 6-4. When the output circuit is loaded, the dip should still be found, but broader and much less pronounced as indicated by the dashed line. The circuit should not be loaded beyond the point where the dip is still recognizable.

Checking V.F.O. Stability

A v.f.o. should be checked thoroughly before it is placed in regular operation on the air. Since succeeding amplifier stages may affect the signal characteristics, final tests should be made with the complete transmitter in operation. Almost any v.f.o. will show signals of good quality and stability when it is running free and not connected to a load. A well-isolated monitor is a necessity. Perhaps the most convenient, as well as one of the most satisfactory, well-shielded monitoring arrangements is a receiver combined with a crystal oscillator, as shown in Fig. 6-7. (See "Crystal Oscillators," this chapter.) The crystal frequency should lie in the band of the lowest frequency to be checked and in the frequency range where its harmonics will fall in the higher-frequency bands. The receiver b.f.o. is turned off and the v.f.o. signal is tuned to beat with the signal from the crystal oscillator instead. In this way any receiver instability caused by overloading of the input circuits, which may result in "pulling" of the h.f. oscillator in the receiver, or by a change in line voltage to the receiver when the transmitter is keyed, will not affect the reliability of the check. Most crystals have a sufficiently low temperature coefficient to give a check on drift as well as on chirp and signal quality if they are not overloaded.

Harmonics of the crystal may be used to beat with the transmitter signal when monitoring at the higher frequencies. Since any chirp at the lower frequencies will be magnified at the higher frequencies, accurate checking can best be done by monitoring at a harmonic.

The distance between the crystal oscillator and receiver should be adjusted to give a good beat between the crystal oscillator and the transmitter signal. When using harmonics of the crystal oscillator, it may be necessary to attach a piece

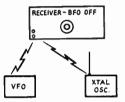


Fig. 6-7—Setup for checking v.f.o. stability. The receiver should be tuned preferably to a harmonic of the v.f.o. frequency. The crystal oscillator may operate somewhere in the band in which the v.f.o. is operating. The receiver b.f.o. should be turned off,

of wire to the oscillator as an antenna to give sufficient signal in the receiver. Checks may show that the stability is sufficiently good to permit oscillator keying at the lower frequencies, where break-in operation is of greater value, but that chirp becomes objectionable at the higher frequencies. If further improvement does not seem possible, it would be logical in this case to use oscillator keying at the lower frequencies and amplified keying at the higher frequencies.

R.F. POWER-AMPLIFIER TANKS AND COUPLING

In the remainder of this chapter the vacuum tubes will be shown, for the most part, with indirectly-heated cathodes. However, many transmitting tubes used directly-heated filaments for the cathodes; when this is done the filament "center-tap" connection will be used, as shown in Fig. 6-8.


PLATE TANK Q

R.f. power amplifiers used in amateur transmitters are operated under Class-C or -AB conditions (see chapter on tube fundamentals). The main objective, of course, is to deliver as much fundamental power as possible into a load, R, without exceeding the tube ratings. The load resistance R may be in the form of a transmission line to an antenna, or the grid circuit of another amplifier. A further objective is to minimize the harmonic energy (always generated by a Class C amplifier) fed into the load circuit. In attaining these objectives, the Q of the tank circuit is of importance. When a load is coupled inductively, as in Fig. 6-10, the Q of the tank circuit

will have an effect on the coefficient of coupling necessary for proper loading of the amplifier. In respect to all of these factors, a tank Q of 10 to 20 is usually considered optimum. A much lower Q will result in less efficient operation of the amplifier tube, greater harmonic output, and greater difficulty in coupling inductively to a load. A much higher Q will result in higher tank current with increased loss in the tank coil.

The Q is determined (see chapter on electrical

Fig. 6-8—Filament center-tap connections to be substituted in place of cathode connections shown in diagrams when filament-type tubes are substituted. T₁ is the filament transformer. Filament bypasses, C₁, should be 0.01-\(mu f\). disk ceramic capacitors. If a self-biasing (cathode) resistor is used, it should be placed between the center tap and ground.

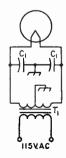

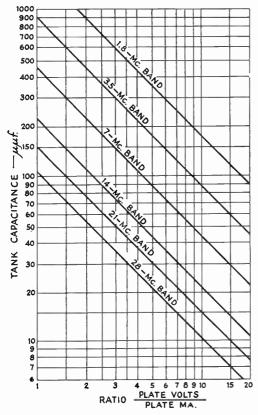


Fig. 6-9—Chart showing plate tank capacitance required for a Q af 10. Divide the tube plate voltage by the plate current in milliamperes. Select the vertical line correspanding to the answer abtained. Follow this vertical line to the diagonal line for the band in question, and thence horizontally to the left to read the capacitance. For a given ratio of plate-voltage/plate current, doubling the capacitance shown doubles the Q, etc. When a split-stator capacitor is used in a balanced circuit, the capacitance of each section may be one half of the value given by the

laws and circuits) by the L/C ratio and the load resistance at which the tube is operated. The tube load resistance is related, in approximation, to the ratio of the d.c. plate voltage to d.c. plate current at which the tube is operated.

The amount of C that will give a Q of 10 for various ratios is shown in Fig. 6-9. For a given plate-voltage/plate-current ratio, the Q will vary directly as the tank capacitance, twice the capacitance doubles the Q, etc. For the same Q, the capacitance of each section of a split-stator capacitor in a balanced circuit should be half the value shown.

These values of capacitance include the output capacitance of the amplifier tube, the input capacitance of a following amplifier tube if it is coupled capacitively, and all other stray capacitances. At the higher plate-voltage/plate-current ratios, the chart may show values of capacitance,

for the higher frequencies, smaller than those attainable in practice. In such a case, a tank Q higher than 10 is unavoidable.

In low-power exciter stages, where capacitive coupling is used, very low-Q circuits, tuned only by the tube and stray circuit capacitances are sometimes used for the purpose of "broadbanding" to avoid the necessity for retuning a stage across a band. Higher-order harmonics generated in such a stage can usually be attenuated in the tank circuit of the final amplifier.

INDUCTIVE-LINK COUPLING

Coupling to Flat Coaxial Lines

When the load R in Fig. 6-10 is located for convenience at some distance from the amplifier, or when maximum harmonic reduction is desired, it is advisable to feed the power to the load through a low-impedance coaxial cable. The shielded construction of the cable prevents radiation and makes it possible to install the line in any convenient manner without danger of unwanted coupling to other circuits.

If the line is more than a small fraction of a wavelength long, the load resistance at its output end should be adjusted, by a matching circuit if necessary, to match the impedance of the cable. This reduces losses in the cable and makes the coupling adjustments at the transmitter independent of the cable length. Matching circuits for use between the cable and another transmission line are discussed in the chapter on transmission lines, while the matching adjustments when the load is the grid circuit of a following

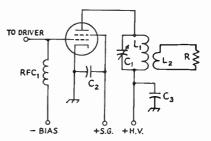


Fig. 6-10—Inductive-link output coupling circuits.

C1—Plate tank capacitor—see text and Fig. 6-9 for capacitance, Fig. 6-33 for voltage rating.

C₂—Screen bypass—voltage rating depends on method of screen supply. See paragraphs on screen cansiderations. Voltage rating same as plate voltage will be safe under any condition.

C₃-Plate bypass-0.001-µf. disk ceramic or mica.

Voltage rating same as C₁, plus safety factor.
L₁-To resonate at operating frequency with C₁. See.

LC chart and inductance farmula in electrical-laws chapter, or use ARRL Lightning Calculator.

L2—Reactance equal to line impedance. See reactance chart and inductance formula in electrical-laws chapter, or use ARRL Lightning Calculator.

R-Representing load.

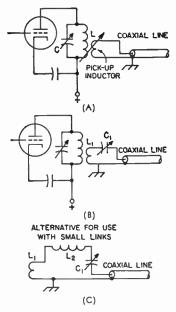


Fig. 6-11—With flat transmission lines, power transfer is obtained with looser coupling if the line input is tuned to resonance. C_1 and L_1 should resonate at the operating frequency. See table for maximum usable value of C_1 . If circuit does not resonate with maximum C_1 or less, inductance of L_1 must be increased, or added in series at L_2 .

amplifier are described elsewhere in this chapter.
Assuming that the cable is properly terminated, proper loading of the amplifier will be assured, using the circuit of Fig. 6-11A, if

1) The plate tank circuit has reasonably high value of Q. A value of 10 is usually sufficient.

2) The inductance of the pick-up or link coil is close to the optimum value for the frequency and type of line used. The optimum coil is one whose self-inductance is such that its reactance at the operating frequency is equal to the characteristic impedance, Z_0 , of the line.

3) It is possible to make the coupling between the tank and pick-up coils very tight.

The second in this list is often hard to meet. Few manufactured link coils have adequate inductance even for coupling to a 50-ohm line at low frequencies.

Capacitance in $\mu\mu$ f. Required for Coupling to Flot Cooxial Lines with Tuned Coupling Circuit

requency	Characteristic I:	mpedance of Line
Band	52	75
Mc.	ohms1	ohms1
3.5	450	300
7	230	150
14	115	75
21	80	50
28	60	40

¹ Capacitance values are maximum usable. *Note:* Inductance in circuit must be adjusted to resonate at operating frequency.

If the line is operating with a low s.w.r., the system shown in Fig. 6-11A will require tight coupling between the two coils. Since the secondary (pick-up coil) circuit is not resonant, the leakage reactance of the pick-up coil will cause some detuning of the amplifier tank circuit. This detuning effect increases with increasing coupling, but is usually not serious. However, the amplifier tuning must be adjusted to resonance, as indicated by the plate-current dip, each time the coupling is changed.

Tuned Coupling

The design difficulties of using "untuned" pick-up coils, mentioned above, can be avoided by using a coupling circuit tuned to the operating frequency. This contributes additional selectivity as well, and hence aids in the suppression of spurious radiations.

If the line is flat the input impedance will be essentially resistive and equal to the Z_0 of the line. With coaxial cable, a circuit of reasonable Q can be obtained with practicable values of inductance and capacitance connected in series with the line's input terminals. Suitable circuits are given in Fig. 6-11 at B and C. The Q of the coupling circuit often may be as low as 2, without running into difficulty in getting adequate coupling to a tank circuit of proper design. Larger values of Q can be used and will result in increased ease of coupling, but as the Q is increased the frequency range over which the circuit will operate without readjustment becomes smaller. It is usually good practice, therefore, to use a coupling-circuit Q just low enough to permit operation, over as much of a band as is normally used for a particular type of communication, without requiring retuning.

Capacitance values for a Q of 2 and line impedances of 52 and 75 ohms are given in the accompanying table. These are the maximum values that should be used. The inductance in the circuit should be adjusted to give resonance at the operating frequency. If the link coil used for a particular band does not have enough inductance to resonate, the additional inductance may be connected in series as shown in Fig. 6-11C.

Characteristics

In practice, the amount of inductance in the circuit should be chosen so that, with somewhat loose coupling between L_1 and the amplifier tank coil, the amplifier plate current will increase when the variable capacitor, C_1 is tuned through the value of capacitance given by the table. The coupling between the two coils should then be increased until the amplifier loads normally, without changing the setting of C1. If the transmission line is flat over the entire frequency band under consideration, it should not be necessary to readjust C1 when changing frequency, if the values given in the table are used. However, it is unlikely that the line actually will be flat over such a range, so some readjustment of C_1 may be needed to compensate for changes in the input impedance of the line. If the input impedance variations are not large, C_1 may be used as a loading control, no changes in the coupling between L_1 and the tank coil being necessary.

The degree of coupling between L_1 and the amplifier tank coil will depend on the coupling-circuit Q. With a Q of 2, the coupling should be tight—comparable with the coupling that is typical of "fixed-link" manufactured coils. With a swinging link it may be necessary to increase the Q of the coupling circuit in order to get sufficient power transfer. This can be done by increasing the L/C ratio.

PI-SECTION OUTPUT TANK

A pi-section tank circuit may also be used in coupling to an antenna or transmission line, as shown in Fig. 6-12. The optimum values of capacitance for C_1 and C_2 , and inductance for L_1 are dependent upon values of tube power input and output load resistance.

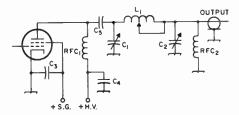


Fig. 6-12—Pi-section output tank circuit.

C1—Input or plate tuning capacitar. See text or Fig.
6-13 for reactance. Voltage rating equal to
d.c. plate voltage; twice this for plate modulation.

C₂—Output or loading capacitor. See text ar Fig. 6-15 for reactance. See text for voltage rating.

C₃—Screen bypass, See Fig. 6-10.

C₄—Plate bypass. See Fig. 6-10.

 C_5 —Plate blocking capacitor—0.001- μ f, disk ceramic or mica. Valtage rating same as C_1 .

L₁—See text or Fig. 6-14 far reactance.

RFC1—See later paragraph on r.f. chakes.

RFC₂=2.5-mh. receiving type (to reduce peak voltage across both C_1 and C_2 and to blow plate power supply fuse if C_5 fails).

Values of reactance for C_1 , L_1 and C_2 may be taken directly from the charts of Figs. 6-13, 6-14 and 6-15 if the output load resistance is the usual 52 or 72 ohms. It should be borne in mind that these values apply only where the output load is resistive, i.e., where the antenna and line have been matched.

Output-Capacitor Ratings

The voltage rating of the output capacitor will depend upon the s.w.r. If the load is resistive, receiving-type air capacitors should be adequate for amplifier input powers up to 1 kw. with plate modulation when feeding 52- or 72-ohm loads. In obtaining the larger capacitances re-

PI-NETWORK DESIGN CHARTS FOR FEEDING 52-OR 72-OHM COAXIAL TRANSMISSION LINES

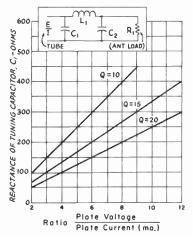


Fig. 6-13—Reactance of input capacitar, C₁, as a function the ratio of plate voltage to plate current.

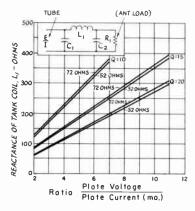


Fig. 6-14—Reactance of tank cail, L₁, as a function of plate voltage and current, for pi networks.

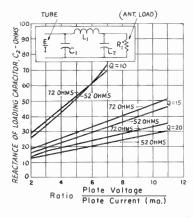


Fig. 6-15—Reactance of loading capacitor, C₂, as a function of plate voltage and current, for pi networks.

Pi-Section Output Tanks

Fig. 6-16—Multiband tuner circuits. In the unbalanced circuit of A, C₁ and C₂ are sections of a single split-stator capacitor. In the balanced circuit of D, the two split-stator capacitors are ganged to a single control with an insulated shaft coupling between the two. In D, the two sections of L₂ are wound on the same form, with the inner ends connected to C₂. In A, each section of the capacitor should have a voltage rating the same as Fig. 6-33A. In D, C₁ should have a rating the same as Fig. 6-33H (or Fig. 6-33E if the feed system corresponds). C₂ may have the rating of Fig. 6-33E so long as the rotor is not grounded or bypassed to ground.


quired for the lower frequencies, it is common practice to switch fixed capacitors in parallel with the variable air capacitor. While the voltage rating of a mica or ceramic capacitor may not be exceeded in a particular case, capacitors of these types are limited in current-carrying capacity. Postage-stamp silver-mica capacitors should be adequate for amplifier inputs over the range from about 70 watts at 28 Mc. to 400 watts at 14 Mc. and lower. The larger mica capacitors (CM-45 case) having voltage ratings of 1200 and 2500 volts are usually satisfactory for inputs varying from about 350 watts at 28 Mc. to 1 kw. at 14 Mc. and lower. Because of these current limitations, particularly at the higher frequencies, it is advisable to use as large an air capacitor as practicable, using the micas only at the lower frequencies. Broadcast-receiver replacement-type capacitors can be obtained very reasonably. They are available in triple units totaling about 1100 µµf., or dual units totaling about 900 µµf. Their insulation should be sufficient for inputs of 500 watts or more. Air capacitors have the additional advantage that they are seldom permanently damaged by a voltage break-down.

Neutralizing with Pi Network

Screen-grid amplifiers using a pi-network output circuit may be neutralized by the system shown in Figs. 6-23 B and C.

MULTIBAND TANK CIRCUITS

Multiband tank circuits provide a convenient means of covering several bands without the need for changing coils. Tuners of this type consist essentially of two tank circuits, tuned simultaneously with a single control. In a tuner designed to cover 80 through 10 meters, each circuit has a sufficiently large capacitance variation to assure an approximately 2-to-1 frequency range. Thus, one circuit is designed so that it covers 3.5 through 7.3 Mc., while the other covers 14 through 29.7 Mc.

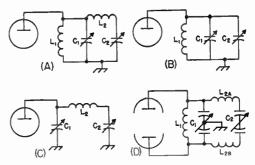

A single-ended, or unbalanced, circuit of this type is shown in Fig. 6-16A. In principle, the reactance of the high-frequency coil, L_2 , is small enough at the lower frequencies so that it can be largely neglected, and C_1 and C_2 are in parallel across L_1 . Then the circuit for low frequencies becomes that shown in Fig. 6-16B. At the high frequencies, the reactance of L_1 is high, so that it may be considered simply as a choke shunting C_1 . The high-frequency circuit is essentially that of Fig. 6-16C, L_2 being tuned by C_1 and C_2 in series.

In practice, the effect of one circuit on the other cannot be neglected entirely. L_2 tends to increase the effective capacitance of C_2 , while L_1 tends to decrease the effective capacitance of C_1 . This effect, however, is relatively small. Each circuit must cover somewhat more than a 2-to-1 frequency range to permit staggering the two ranges sufficiently to avoid simultaneous responses to a frequency in the low-frequency range, and one of its harmonics lying in the range of the high-frequency circuit.

In any circuit covering a frequency range as great as 2 to 1 by capacitance alone, the circuit Q must vary rather widely. If the circuit is designed for a Q of 12 at 80, the Q will be 6 at 40, 24 at 20, 18 at 15, and 12 at 10 meters. The increase in tank current as a result of the increase in Q toward the low-frequency end of the high-frequency range may make it necessary to design the high-frequency coil with care to minimize loss in this portion of the tuning range. It is generally found desirable to provide separate output coupling coils for each circuit.

Fig. 6-16D shows a similar tank for balanced circuits. The same principles apply.

Series or parallel feed may be used with either balanced or unbalanced circuits. In the balanced circuit of Fig. 6-16D, the series feed point would be at the center of $L_{1\bullet}$ with an r.f. choke in series.

(For further discussion see QST, July, 1954.)

R.F. AMPLIFIER-TUBE OPERATING CONDITIONS

In addition to proper tank and output-coupling circuits discussed in the preceding sections, an r.f. amplifier must be provided with suitable electrode voltages and an r.f. driving or excitation voltage (see vacuum-tube chapter).

All r.f. amplifier tubes require a voltage to operate the filament or heater (a.c. is usually permissible), and a positive d.c. voltage between the plate and filament or cathode (plate voltage). Most tubes also require a negative d.c. voltage

(biasing voltage) between control grid (Grid No. 1) and filament or cathode. Screen-grid tubes require in addition a positive voltage (screen voltage or Grid No. 2 voltage) between screen and filament or cathode.

Biasing and plate voltages may be fed to the tube either in series with or in parallel with the associated r.f. tank circuit as discussed in the chapter on electrical laws and circuits.

It is important to remember that true plate, screen or biasing voltage is the voltage between the particular electrode and filament or cathode. Only when the cathode is directly grounded to the chassis may the electrode-to-chassis voltage be taken as the true voltage.

The required r.f. driving voltage is applied between grid and cathode.

Power Input and Plate Dissipation

Plate power input is the d.c. power input to the plate circuit (d.c. plate voltage \times d.c. plate current).—Screen power input likewise is the d.c. screen voltage \times the d.c. screen current.

Plate dissipation is the difference between the r.f. power delivered by the tube to its loaded plate tank circuit and the d.c. plate power input. The screen, on the other hand, does not deliver any output power, and therefore its dissipation is the same as the screen power input.

TRANSMITTING-TUBE RATINGS

Tube manufacturers specify the maximum values that should be applied to the tubes they produce. They also publish sets of typical operating values that should result in good efficiency and normal tube life.

Maximum values for all of the most popular transmitting tubes will be found in the tables of transmitting tubes in the last chapter. Also included are as many sets of typical operating values as space permits. However, it is recommended that the amateur secure a transmitting-tube manual from the manufacturer of the tube or tubes he plans to use.

CCS and ICAS Ratings

The same transmitting tube may have different ratings depending upon the manner in which the tube is to be operated, and the service in which it is to be used. These different ratings are based primarily upon the heat that the tube can safely dissipate. Some types of operation, such as with grid or screen modulation, are less efficient than others, meaning that the tube must dissipate more heat. Other types of operation, such as c.w. or single-sideband phone are intermittent in nature, resulting in less average heating than in other modes where there is a continuous power input to the tube during transmissions. There are also different ratings for tubes used in transmitters that are in almost constant use (CCS-Continuous Commercial Service), and for tubes that are to be used in transmitters that average only a few hours of daily operation (ICAS-Intermittent Commercial and Amateur Service). The latter are the ratings used by amateurs who

wish to obtain maximum output with reasonable tube life.

Maximum Ratings

Maximum ratings, where they differ from the values given under typical operating values, are not normally of significance to the amateur except in special applications. No single maximum value should be used unless all other ratings can simultaneously be held within the maximum values. As an example, a tube may have a maximum plate-voltage rating of 2000, a maximum plate-current rating of 300 ma., and a maximum plate-power-input rating of 400 watts. Therefore, if the maximum plate voltage of 2000 is used, the plate current should be limited to 200 ma. (instead of 300 ma.) to stay within the maximum power-input rating of 400 watts.

SOURCES OF ELECTRODE VOLTAGES

Filament or Heater Voltage

The filament voltage for the indirectly heated cathode-type tubes found in low-power classifications may vary 10 per cent above or below rating without seriously reducing the life of the tube. But the voltage of the higher-power filament-type tubes should be held closely between the rated voltage as a minimum and 5 per cent above rating as a maximum. Make sure that the plate power drawn from the power line does not cause a drop in filament voltage below the proper value when plate power is applied.

Thoriated-type filaments lose emission when the tube is overloaded appreciably. If the overload has not been too prolonged, emission sometimes may be restored by operating the filament at rated voltage with all other voltages removed for a period of 10 minutes, or at 20 per cent above rated voltage for a few minutes.

Plate Voltage

D.c. plate voltage for the operation of r.f. amplifiers is most often obtained from a transformer-rectifier-filter system (see power-supply chapter) designed to deliver the required plate voltage at the required current. However, batteries or other d.c.-generating devices are sometimes used in certain types of operation (see portable-mobile chapter).

Bigs and Tube Protection

Several methods of obtaining bias are shown in Fig. 6-17. In A, bias is obtained by the voltage drop across a resistor in the grid d.c. return circuit when rectified grid current flows. The proper value of resistance may be determined by dividing the required biasing voltage by the d.c. grid current at which the tube will be operated. Then, so long as the r.f. driving voltage is adjusted so that the d.c. grid current is the recommended value, the biasing voltage will be the proper value. The tube is biased only when excitation is applied, since the voltage drop across the resistor depends upon grid-current flow. When excitation is removed, the bias falls to

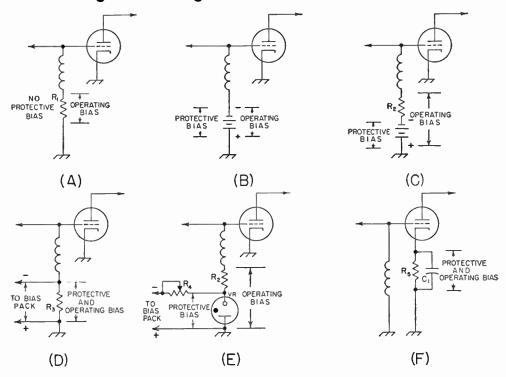


Fig. 6-17—Various systems for obtaining protective and operating bias for r.f. amplifiers. A—Grid-leak. B—Battery. C—Combination battery and grid leak. D—Grid leak and adjusted-voltage bias pack. E—Combination grid leak and voltage-regulated pack. F—Cathode bias.

zero. At zero bias most tubes draw power far in excess of the plate-dissipation rating. So it is advisable to make provision for protecting the tube when excitation fails by accident, or by intent as it does when a preceding stage in a c.w. transmitter is keyed.

If the maximum c.w. ratings shown in the tube tables are to be used, the input should be cut to zero when the key is open. Aside from this, it is not necessary that plate current be cut off completely but only to the point where the rated dissipation is not exceeded. In this case platemodulated phone ratings should be used for c.w. operation, however.

With triodes this protection can be supplied by obtaining all bias from a source of fixed voltage, as shown in Fig. 6-17B. It is preferable, however, to use only sufficient fixed bias to protect the tube and obtain the balance needed for operating bias from a grid leak, as in C. The grid-leak resistance is calculated as above, except that the fixed voltage is subtracted first.

Fixed bias may be obtained from dry batteries or from a power pack (see power-supply chapter). If dry batteries are used, they should be checked periodically, since even though they may show normal voltage, they eventually develop a high internal resistance. Grid-current flow through this battery resistance may increase the bias considerably above that anticipated. The life of batteries in bias service will be approximately the same as though they were subject to a drain equal to the grid current, despite the fact that the

grid-current flow is in such a direction as to charge the battery, rather than to discharge it.

In Fig. 6-17F, bias is obtained from the voltage drop across a resistor in the cathode (or filament center-tap) lead. Protective bias is obtained by the voltage drop across R_5 as a result of plate (and screen) current flow. Since plate current must flow to obtain a voltage drop across the resistor, it is obvious that cut-off protective bias cannot be obtained. When excitation is applied, plate (and screen) current increases and the grid current also contributes to the drop across R₅, thereby increasing the bias to the operating value. Since the voltage between plate and cathode is reduced by the amount of the voltage drop across R_5 , the over-all supply voltage must be the sum of the plate and operating-bias voltages. For this reason, the use of cathode bias usually is limited to low-voltage tubes when the extra voltage is not difficult to obtain.

The resistance of the cathode biasing resistor R_5 should be adjusted to the value which will give the correct operating bias voltage with rated grid, plate and screen currents flowing with the amplifier loaded to rated input. When excitation is removed, the input to most types of tubes will fall to a value that will prevent damage to the tube, at least for the period of time required to remove plate voltage. A disadvantage of this biasing system is that the cathode r.f. connection to ground depends upon a bypass capacitor. From the consideration of v.h.f. harmonics and stability with high-perveance tubes, it is preferable

to make the cathode-to-ground impedance as close to zero as possible.

Screen Voltage

For c.w. operation, and under certain conditions of phone operation (see amplitude-modulation chapter), the screen may be operated from a power supply of the same type used for plate supply, except that voltage and current ratings should be appropriate for screen requirements. The screen may also be operated through a series resistor or voltage-divider from a source of higher voltage, such as the plate-voltage supply, thus making a separate supply for the screen unnecessary. Certain precautions are necessary, depending upon the method used.

It should be kept in mind that screen current varies widely with both excitation and loading. If the screen is operated from a fixed-voltage source, the tube should never be operated without plate voltage and load, otherwise the screen may be damaged within a short time. Supplying the screen through a series dropping resistor from a higher-voltage source, such as the plate supply, affords a measure of protection, since the resistor causes the screen voltage to drop as the current increases, thereby limiting the power drawn by the screen. However, with a resistor, the screen voltage may vary considerably with excitation, making it necessary to check the voltage at the screen terminal under actual operating conditions to make sure that the screen voltage is normal. Reducing excitation will cause the screen current to drop, increasing the voltage; increasing excitation will have the opposite effect. These changes are in addition to those caused by changes in bias and plate loading, so if a screen-grid tube is operated from a series resistor or a voltage divider, its voltage should be checked as one of the final adjustments after excitation and loading have been set.

An approximate value for the screen-voltage dropping resistor may be obtained by dividing the voltage *drop* required from the supply voltage (difference between the supply voltage and rated screen voltage) by the rated screen current in decimal parts of an ampere. Some further adjustment may be necessary, as mentioned above, so an adjustable resistor with a total resistance above that calculated should be provided.

Protecting Screen-Grid Tubes

Screen-grid tubes cannot be cut off with bias unless the screen is operated from a fixed-voltage supply. In this case the cut-off bias is approximately the screen voltage divided by the amplification factor of the screen. This figure is not always shown in tube-data sheets, but cut-off voltage may be determined from an inspection of tube curves, or by experiment.

When the screen is supplied from a series dropping resistor, the tube can be protected by the use of a clamper tube, as shown in Fig. 6-18. The grid-leak bias of the amplifier tube with excitation is supplied also to the grid of the clamper tube. This is usually sufficient to cut off

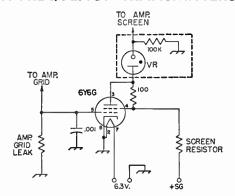


Fig. 6-18—Screen clomper circuit for protecting screen-grid power tubes. The VR tube is needed only for complete cut-off.

the clamper tube. However, when excitation is removed, the clamper-tube bias falls to zero and it draws enough current through the screen dropping resistor usually to limit the input to the amplifier to a safe value. If complete screenvoltage cut-off is desired, a VR tube may be inserted in the screen lead as shown. The VR-tube voltage rating should be high enough so that it will extinguish when excitation is removed.

FEEDING EXCITATION TO THE GRID

The required r.f. driving voltage is supplied by an oscillator generating a voltage at the desired frequency, either directly or through intermediate amplifiers or frequency multipliers.

As explained in the chapter on vacuum-tube fundamentals, the grid of an amplifier operating under Class C conditions must have an exciting voltage whose peak value exceeds the negative biasing voltage over a portion of the excitation cycle. During this portion of the cycle, current will flow in the grid-cathode circuit as it does in a diode circuit when the plate of the diode is positive in respect to the cathode. This requires that the r.f. driver supply power. The power required to develop the required peak driving voltage across the grid-cathode impedance of the amplifier is the r.f. driving power.

The tube tables give approximate figures for the grid driving power required for each tube under various operating conditions. These figures, however, do not include circuit losses. In general, the driver stage for any Class C amplifier should be capable of supplying at least three times the driving power shown for typical operating conditions at frequencies up to 30 Mc., and from three to ten times at higher frequencies.

Since the d.c. grid current relative to the biasing voltage is related to the peak driving voltage, the d.c. grid current is commonly used as a convenient indicator of driving conditions. A driver adjustment that results in rated d.c. grid current when the d.c. bias is at its rated value, indicates proper excitation to the amplifier when it is fully loaded.

In coupling the grid input circuit of an amplifier to the output circuit of a driving stage the

Feeding the Grid

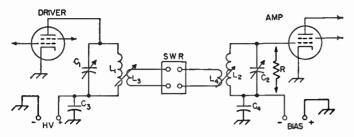


Fig. 6-19—Coupling excitation to the grid of an r.f. power amplifier by means of a low-impedance coaxial line.

C1, C3, L1, L3-See corresponding components in Fig. 6-10.

 C_2 —Amplifier grid tank capacitor—see text and Fig. 6-20 for capacitance, Fig. 6-34 for voltage rating. C_4 —0.001- μ f. disk ceramic.

L₂-To resonate at operating frequency with C₂. See LC chart inductance formula in electrical-laws chapter, or use ARRL Lightning Calculator.

L4—Reactance equal to line impedance—see reactance chart and inductance formula in electrical-laws chapter, or use ARRL Lightning Calculator.

R is used to simulate grid impedance of the amplifier when a low-power s.w.r. indicator, such as a resistance bridge, is used. See formula in text for calculating value. Standing-wave indicator SWR is inserted only while line is made flat.

objective is to load the driver plate circuit so that the desired amplifier grid excitation is obtained without exceeding the plate-input ratings of the driver tube.

Driving Impedance

The grid-current flow that results when the grid is driven positive in respect to the cathode over a portion of the excitation cycle represents an average resistance across which the exciting voltage must be developed by the driver. In other words, this is the load resistance into which the driver plate circuit must be coupled. The approximate grid input resistance is given by:

Input impedance (ohms)
$$= \frac{driving \ power \ (watts)}{d.c. \ grid \ current \ (ma.)^2} \times 620,000$$

For normal operation, the driving power and grid current may be taken from the tube tables.

Since the grid input resistance is a matter of a few thousand ohms, an impedance step-down is necessary if the grid is to be fed from a low-impedance transmission line. This can be done by the use of a tank as an impedance-transforming device in the grid circuit of the amplifier as shown in Fig. 6-19. This coupling system may be considered either as simply a means of obtaining mutual inductance between the two tank coils, or as a low-impedance transmission line. If the line is longer than a small fraction of a wave length, and if a s.w.r. bridge is available, the line is more easily handled by adjusting it as a matched transmission line.

Inductive Link Coupling with Flat Line

In adjusting this type of line, the object is to make the s.w.r. on the line as low as possible over as wide a band of frequencies as possible so that power can be transferred over this range without retuning. It is assumed that the output coupling considerations discussed earlier have been observed in connection with the driver plate

circuit. So far as the amplifier grid circuit is concerned, the controlling factors are the Q of the tuned grid circuit, L_2C_2 , (see Fig. 6-20) the inductance of the coupling coil, L_4 , and the degree of coupling between L_2 and L_4 . Variable coupling between the coils is convenient, but not strictly necessary if one or both of the other factors can be varied. An s.w.r. indicator (shown as "SWR" in the drawing) is essential. An indi-

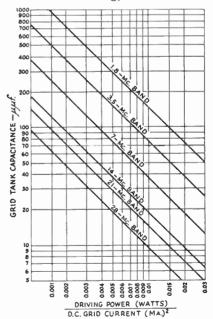


Fig. 6-20—Chart showing required grid tank capacitance for a Q of 12. To use, divide the driving power in watts by the square of the d.c. grid current in milliamperes and proceed as described under Fig-6-9. Driving power and grid current may be taken from the tube tables. When a split-stator capacitor is used in a balanced grid circuit, the capacitance of each section may be half that shown.

cator such as the "Micromatch" (a commercially available instrument) may be connected as shown and the adjustments made under actual operating conditions; that is, with full power applied to the amplifier grid.

Assuming that the coupling is adjustable, start with a trial position of L_4 with respect to L_2 , and adjust C_2 for the lowest s.w.r. Then change the coupling slightly and repeat. Continue until the s.w.r. is as low as possible; if the circuit constants are in the right region is should not be difficult to get the s.w.r. down to 1 to 1. The Q of the tuned grid circuit should be designed to be at least 10, and if it is not possible to get a very low s.w.r. with such a grid circuit the probable reason is that L_4 is too small. Maximum coupling, for a given degree of physical coupling will occur when the inductance of L_4 is such that its reactance at the operating frequency is equal to the characteristic impedance of the link line. The reactance can be calculated as described in the chapter on electrical fundamentals if the inductance is known; the inductance can either be calculated from the formula in the same chapter or measured as described in the chapter on measurements.

Once the s.w.r. has been brought down to 1 to 1, the frequency should be shifted over the band so that the variation in s.w.r. can be observed, without changing C_2 or the coupling between L_2 and L4. If the s.w.r. rises rapidly on either side of the original frequency the circuit can be made "flatter" by reducing the Q of the tuned grid circuit. This may be done by decreasing C2 and correspondingly increasing L2 to maintain resonance, and by tightening the coupling between L_2 and L4, going through the same adjustment process again. It is possible to set up the system so that the s.w.r. will not exceed 1.5 to 1 over, for example, the entire 7-Mc. band and proportionately on other bands. Under these circumstances a single setting will serve for work anywhere in the band, with essentially constant power transfer from the line to the power-amplifier grids.

If the coupling between L_2 and L_4 is not adjustable the same result may be secured by varying the L/C ratio of the tuned grid circuit — that is, by varying its Q. If any difficulty is encountered it can be overcome by changing the number of turns in L_4 until a match is secured. The two coils should be tightly coupled.

When a resistance-bridge type s.w.r. indicator (see measurements chapter) is used it is not possible to put the full power through the line when making adjustments. In such case the operating conditions in the amplified grid circuit can be simulated by using a carbon resistor (½ or 1 watt size) of the same value as the calculated amplifier grid impedance, connected as indicated by the arrows in Fig. 6-19. In this case the amplifier tube must be operated "cold"— without filament or heater power. The adjustment process is the same as described above, but with the driver power reduced to a value suitable for operating the s.w.r. bridge.

When the grid coupling system has been ad-

justed so that the s.w.r. is close to 1 to 1 over the desired frequency range, it is certain that the power put into the link line will be delivered to the grid circuit. Coupling will be facilitated if the line is tuned as described under the earlier section on output coupling systems.

Link Feed with Unmatched Line

When the system is to be treated without regard to transmission-line effects, the link line must not offer appreciable reactance at the operating frequency. Any appreciable reactance will in effect reduce the coupling, making it impossible to transfer sufficient power from the driver to the amplifier grid circuit. Coaxial cables especially have considerable capacitance for even short lengths and it may be more desirable to use a spaced line, such as Twin-Lead, if the radiation can be tolerated.

The reactance of the line can be nullified only by making the link resonant. This may require changing the number of turns in the link coils, the length of the line, or the insertion of a tuning capacitance. Since the s.w.r. on the link line may be quite high, the line losses increase because of the greater current, the voltage increase may be sufficient to cause a breakdown in the insulation of the cable and the added tuned circuit makes adjustment more critical with relatively small changes in frequency.

These troubles may not be encountered if the link line is kept very short for the highest frequency. A length of 5 feet or more may be tolerable at 3.5 Mc., but a length of a foot at 28 Mc. may be enough to cause serious effects on the functioning of the system.

Adjusting the coupling in such a system must necessarily be largely a matter of cut and try. If the line is short enough so as to have negligible reactance, the coupling between the two tank circuits will increase within limits by adding turns to the link coils, or by coupling the link coils more tightly, if possible, to the tank coils. If it is impossible to change either of these, a variable capacitor of 300 $\mu\mu$ f. may be connected in series with or in parallel with the link coil at the driver end of the line, depending upon which connection is the most effective.

If coaxial line is used, the capacitor should be connected in series with the inner conductor. If the line is long enough to have appreciable reactance, the variable capacitor is used to resonate the entire link circuit.

The size of the link coils and the length of the line, as well as the size of the capacitor, will affect the resonant frequency, and it may take an adjustment of all three before the capacitor will show a pronounced effect on the coupling.

When the system has been made resonant, coupling may be adjusted by varying the link capacitor.

Simple Capacitive Interstage Coupling

The capacitive system of Fig. 6-21A is the simplest of all coupling systems. In this circuit, the plate tank circuit of the driver, C_1L_1 , serves

Interstage Coupling


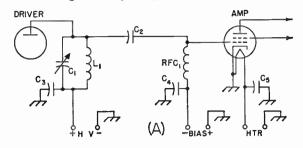


Fig. 6-21—Capacitive-coupled amplifiers.

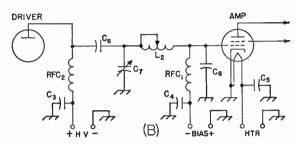A—Simple capacitive coupling. B—Pi-section coupling.



C₁-Driver plate tank capacitor—see text and Fig. 6-9 for capacitance, Fig. 6-33 for voltage rating.

 C_2 —Coupling capacitor—50 to 150 $\mu\mu$ f. mica, as necessary for desired coupling. Voltage rating sum of driver plate and amplifier biasing voltages, plus safety factor.

C₃-Driver plate bypass capacitor-0.001-\mu f. disk ceramic or mica. Voltage rating same as plate voltage.

C4-Grid bypass-0.001-4f. disk ceramic.

C₅-Heater bypass-0.001- μ f, disk ceramic.

C₈-Driver plate blocking capacitor-0.001-\(mu f\), disk ceramic or mica. Voltage rating same as C₂.

 C_7 —Pi-section input capacitor—see text referring to Fig. 6-12 for capacitance. Voltage rating—see Fig. 6-33A. C_8 —Pi-section output capacitor—100- $\mu\mu$ f. mica. Voltage rating same as driver plate voltage plus safety factor. L_1 —To resonate at operating frequency with C_1 . See LC chart and inductance formula in electrical-laws chapter,

L₁—To resonate at operating frequency with C₁. See LC chart and inductance formula in electrical-laws chapter or use ARRL Lightning Calculator.

L₂—Pi-section inductor—See Fig. 6-12. Approx. same as L₁.

RFC1-Grid r.f. choke-2.5-mh.

RFC₂-Driver plate r.f. choke-2.5 mh.

also as the grid tank of the amplifier. Although it is used more frequently than any other system, it is less flexible and has certain limitations that must be taken into consideration.

The two stages cannot be separated physically any appreciable distance without involving loss in transferred power, radiation from the coupling lead and the danger of feedback from this lead. Since both the output capacitance of the driver tube and the input capacitance of the amplifier are across the single circuit, it is sometimes difficult to obtain a tank circuit with a sufficiently low Q to provide an efficient circuit at the higher frequencies. The coupling can be varied by altering the capacitance of the coupling capacitor, C2. The driver load impedance is the sum of the amplifier grid resistance and the reactance of the coupling capacitor in series, the coupling capacitor serving simply as a series reactor. The driver load resistance increases with a decrease in the capacitance of the coupling capacitor.

When the amplifier grid impedance is lower than the optimum load resistance for the driver, a transforming action is possible by tapping the grid down on the tank coil, but this is not recommended because it invariably causes an increase in v.h.f. harmonics and sometimes sets up a parasitic circuit.

So far as coupling is concerned, the *Q* of the circuit is of little significance. However, the other considerations discussed earlier in connection with tank-circuit *Q* should be observed.

Pi-Network Interstage Coupling

A pi-section tank circuit, as shown in Fig. 6-21B, may be used as a coupling device between screen-grid amplifier stages. The circuit can also be considered a coupling arrangement with the grid of the amplifier tapped down on the circuit by means of a capacitive divider. In contrast to the tapped-coil method mentioned previously, this system will be very effective in reducing v.h.f. harmonics, because the output capacitor, C_8 , provides a direct capacitive slunt for harmonics across the amplifier grid circuit.

To be most effective in reducing v.h.f. harmonics, C_8 should be a mica capacitor connected directly across the tube-socket terminals. Tapping down on the circuit in this manner also helps to stabilize the amplifier at the operating frequency because of the grid-circuit loading

provided by C_8 . For the purposes both of stability and harmonic reduction, experience has shown that a value of $100~\mu\mu f$, for C_8 usually is sufficient. In general, C_7 and L_2 should have values approximating the capacitance and inductance used in a conventional tank circuit. A reduction in the inductance of L_2 results in an increase in coupling because C_7 must be increased to retune the circuit to resonance. This changes the ratio of C_7 to C_8 and has the effect of

moving the grid tap up on the circuit. Since the coupling to the grid is comparatively loose under any condition, it may be found that it is impossible to utilize the full power capability of the driver stage. If sufficient excitation cannot be obtained, it may be necessary to raise the plate voltage of the driver, if this is permissible. Otherwise a larger driver tube may be required. As shown in Fig. 6-21B, parallel driver plate feed and amplifier grid feed are necessary.

R.F. POWER AMPLIFIER CIRCUITRY

STABILIZING AMPLIFIERS

A straight amplifier operates with its input and output circuits tuned to the same frequency. Therefore, unless the coupling between these two circuits is brought to the necessary minimum, the amplifier will oscillate as a tuned-plate tuned-grid circuit. Care should be used in arranging components and wiring of the two circuits so that there will be negligible opportunity for coupling external to the tube itself. Complete shielding between input and output circuits usually is required. All r.f. leads should be kept as short as possible and particular attention should be paid to the r.f. return paths from plate and grid tank circuits to cathode. In general, the best arrangement is one in which the cathode connection to ground, and the plate tank circuit are on the same side of the chassis or other shielding. The "hot" lead from the grid tank (or driver plate tank) should be brought to the socket through a hole in the shielding. Then when the grid tank capacitor or bypass is grounded, a return path through the hole to cathode will be encouraged, since transmission-line characteristics are simulated.

A check on external coupling between input and output circuits can be made with a sensitive indicating device, such as the one diagrammed in Fig. 6-22. The amplifier tube is removed from its socket and if the plate terminal is at the

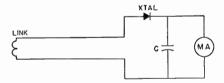



Fig. 6-22—Circuit of sensitive neutralizing indicatar.


Xtal is a 1N34 crystal detector, MA a 0-1 directcurrent milliammeter and C a 0.001-μf. mica bypass
capacitar.

socket, it should be disconnected. With the driver stage running and tuned to resonance, the indicator should be coupled to the output tank coil and the output tank capacitor tuned for any indication of r.f. feedthrough. Experiment with shielding and rearrangement of parts will show whether the isolation can be improved.

Screen-Grid Tube Neutralizing Circuits

The plate-grid capacitance of screen-grid tubes

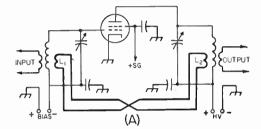

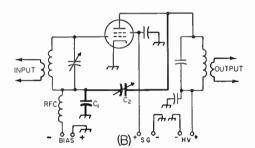

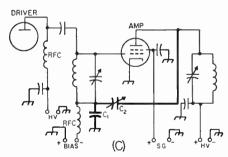


Fig. 6-23—Screen-grid neutralizing circuits. A—Inductive neutralizing. B-C—Capacitive neutralizing.

C₁—Grid bypass capacitar—apprax. 0.001-\(\mu t\). mica.

Valtage rating same as biasing valtage in

B, same as driver plate valtage in C.

C₂—Neutralizing capacitor—approx. 2 to 10 $\mu\mu$ f.—see text. Valtage rating same as amplifier plate valtage for c.w., twice this value far plate madulation.

 L_1 , L_2 —Neutralizing link—usually a turn ar twa will be sufficient.

is reduced to a fraction of a micromicrofarad by the interposed grounded screen. Nevertheless, the power sensitivity of these tubes is so great that only a very small amount of feedback is necessary to start oscillation. To assure a stable amplifier, it is usually necessary to load the grid circuit, or to use a neutralizing circuit.

Fig. 6-23A shows how a screen-grid amplifier may be neutralized by the use of an inductive link line coupling the input and output tank circuits in proper phase. If the initial connection proves to be incorrect, connections to one of the link coils should be reversed. Neutralizing is adjusted by changing the distance between the link coils and the tank coils. In the case of capacitive coupling between stages, one of the link coils will be coupled to the plate tank coil of the driver stage.

A capacitive neutralizing system for screengrid tubes is shown in Fig. 6-23B. C_2 is the neutralizing capacitor. The capacitance should be chosen so that at some adjustment of C_2 ,

$$\frac{C_2}{C_1} = \frac{Tube\ grid-plate\ capacitance\ (or\ C_{gp})}{Tube\ input\ capacitance\ (or\ C_{IN})}$$

The tube interelectrode capacitances $C_{\rm gp}$ and $C_{\rm IN}$ are given in the tube tables in the last chapter. The grid-cathode capacitance must include all strays directly across the tube capacitance, including the capacitance of the tuning-capacitor stator to ground. This may amount to 5 to 20 $\mu\mu$ f. In the case of capacitance coupling, as shown in Fig. 6-23C, the output capacitance of the driver tube must be added to the grid-cathode capacitance of the amplifier in arriving at the value of C_2 . If C_2 works out to an impractically large or small value, C_1 can be changed to compensate by using combinations of fixed mica capacitors in parallel.

Neutralizing Adjustment

The procedure in neutralizing is essentially the same for all types of tubes and circuits. The filament of the amplifier tube should be lighted and excitation from the preceding stage fed to the grid circuit. Both screen and plate voltages should be disconnected at the transmitter terminals.

The immediate objective of the neutralizing process is reducing to a minimum the r.f. driver voltage fed from the input of the amplifier to its output circuit through the grid-plate capacitance of the tube. This is done by adjusting carefully, bit by bit, the neutralizing capacitor or link coils until an r.f. indicator in the output circuit reads minimum.

The device shown in Fig. 6-22 makes a sensitive neutralizing indicator. The link should be coupled to the output tank coil at the low-potential or "ground" point. Care should be taken to make sure that the coupling is loose enough at all times to prevent burning out the meter or the rectifier. The plate tank capacitor should be readjusted for maximum reading after each change in neutralizing.

The grid-current meter may also be used as a neutralizing indicator. With plate and screen voltages removed as described above, there will be a change in grid current as the plate tank circuit is tuned through resonance. The neutralizing capacitor should be adjusted until this deflection is brought to a minimum. As a final adjustment, plate and screen voltages should be applied and the neutralizing capacitance adjusted to the point where minimum plate current, maximum grid current and maximum screen current occur simultaneously. An increase in grid current when the plate tank circuit is tuned slightly on the high-frequency side of resonance indicates that the neutralizing capacitance is too small. If the increase is on the low-frequency side, the neutralizing capacitance is too large. When neutralization is complete, there should be a slight decrease in grid current on either side of resonance.

Grid Loading

The use of a neutralizing circuit may often be avoided by loading the grid circuit if the driving stage has some power capability to spare. Loading by tapping the grid down on the grid tank coil (or the plate tank coil of the driver in the case of capacitive coupling), or by a resistor from grid to cathode is effective in stabilizing an amplifier, but either device may increase v.h.f. harmonics. The best loading system is the use of a pi-section filter, as shown in Fig. 6-21B. This circuit places a capacitance directly between grid and cathode. This not only provides the desirable loading, but also a very effective capacitive short for v.h.f. harmonics. A 100-μμf. mica capacitor for C8, wired directly between tube terminals, will usually provide sufficient loading to stabilize the amplifier.

V.H.F. Parasitic Oscillation

Parasitic oscillation in the v.h.f. range will take place in almost every r.f. power amplifier. To test for v.h.f. parasitic oscillation, the grid tank coil (or driver tank coil in the case of ca-

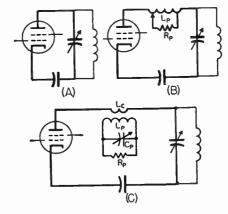


Fig. 6-24—A—Usual parasitic circuit. B—Resistive loading of parasitic circuit. C—Inductive coupling of loading resistance into parasitic circuit.

pacitive coupling) should be short-circuited with a clip lead. This is to prevent any possible t.g.t.p. oscillation at the operating frequency which might lead to confusion in identifying the parasitic. Any fixed bias should be replaced with a grid leak of 10,000 to 20,000 ohms. All load on the output of the amplifier should be disconnected. Plate and screen voltages should be reduced to the point where the rated dissipation is not exceeded. If a Variac is not available, voltage may be reduced by a 115-volt lamp in series with the primary of the plate transformer.

With power applied only to the amplifier under test, a search should be made by adjusting the input capacitor to several settings, including minimum and maximum, and turning the plate capacitor through its range for each of the grid-capacitor settings. Any grid current, or any dip or flicker in plate current at any point, indicates oscillation. This can be confirmed by an indicating absorption wavemeter tuned to the frequency of the parasitic and held close to the plate lead of the tube.

The heavy lines of Fig. 6-24A show the usual parasitic tank circuit, which resonates, in most cases, between 150 and 200 Mc. For each type of tetrode, there is a region, usually below the parasitic frequency, in which the tube will be selfneutralized. By adding the right amount of inductance to the parasitic circuit, its resonant frequency can be brought down to the frequency at which the tube is self-neutralized. However, the resonant frequency should not be brought down so low that it falls close to TV Channel 6 (88 Mc.). From the consideration of TVI, the circuit may be loaded down to a frequency not lower than 100 Mc. If the self-neutralizing frequency is below 100 Mc., the circuit should be loaded down to somewhere between 100 and 120 Mc. with inductance. Then the parasitic can be suppressed by loading with resistance, as shown in Fig. 6-24B. A coil of 4 or 5 turns, 1/4 inch in diameter, is a good starting size. With the tank capacitor turned to maximum capacitance, the circuit should be checked with a g.d.o. to make sure the resonance is above 100 Mc. Then, with the shortest possible leads, a noninductive 100ohm 1-watt resistor should be connected across the entire coil. The amplifier should be tuned up to its highest-frequency band and operated at low voltage. The tap should be moved a little at a time to find the minimum number of turns required to suppress the parasitic. Then voltage should be increased until the resistor begins to feel warm after several minutes of operation, and the power input noted. This input should be compared with the normal input and the power rating of the resistor increased by this proportion; i.e., if the power is half normal, the wattage rating should be doubled. This increase is best made by connecting 1-watt carbon resistors in parallel to give a resultant of about 100 ohms. As power input is increased, the parasitic may start up again, so power should be applied only momentarily until it is made certain that the parasitic is still suppressed. If the parasitic starts

up again when voltage is raised, the tap must be moved to include more turns. So long as the parasitic is suppressed, the resistors will heat up only from the operating-frequency current.

Since the resistor can be placed across only that portion of the parasitic circuit represented by L_p , the latter should form as large a portion of the circuit as possible. Therefore, the tank and bypass capacitors should have the lowest possible inductance and the leads shown in heavy lines should be as short as possible and of the heaviest practical conductor. This will permit L_p to be of maximum size without tuning the circuit below the 100-Mc. limit.

Another arrangement that has been used successfully is shown in Fig. 6-24C. A small turn or two is inserted in place of L_p and this is coupled to a circuit tuned to the parasitic frequency and loaded with resistance. The heavy-line circuit should first be checked with a g.d.o. Then the loaded circuit should be tuned to the same frequency and coupled in to the point where the parasitic ceases. The two coils can be wound on the same form and the coupling varied by sliding one of them. Slight retuning of the loaded circuit may be required after coupling. Start out with low power as before, until the parasitic is suppressed. Since the loaded circuit in this case carries much less operating-frequency current, a single 100-ohm 1-watt resistor will often be sufficient and a 30-µµf. mica trimmer should serve as the tuning capacitor, C_p .

Low-Frequency Parasitic Oscillation

The screening of most transmitting screen-grid tubes is sufficient to prevent low-frequency parasitic oscillation caused by resonant circuits set up by r.f. chokes in grid and plate circuits. Should this type of oscillation (usually between 200 and 1200 kc.) occur, see paragraph under triode amplifiers.

PARALLEL-TUBE AMPLIFIERS

The circuits for parallel-tube amplifiers are the same as for a single tube, similar terminals of the tubes being connected together. The grid impedance of two tubes in parallel is half that of a single tube. This means that twice the grid tank capacitance shown in Fig. 6-20 should be used for the same Q.

The plate load resistance is halved so that the plate tank capacitance for a single tube (Fig. 6-10) also should be doubled. The total grid current will be doubled, so to maintain the same grid bias, the grid-leak resistance should be half that used for a single tube. The required driving power is doubled. The capacitance of a neutralizing capacitor, if used, should be doubled and the value of the screen dropping resistor should be cut in half.

In treating parasitic oscillation, it is often necessary to use a choke in each plate lead, rather than one in the common lead to avoid building in a push-pull type of v.h.f. circuit, a factor in obtaining efficient operation at higher frequencies.

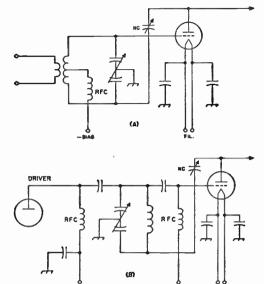


Fig. 6-25—When a pi-network output circuit is used with a triode, a balanced grid circuit must be provided for neutralizing. A—Inductive-link input. B—Capacitive input caupling.

PUSH-PULL AMPLIFIERS

Basic push-pull circuits are shown in Fig. 6-26C and D. Amplifiers using this circuit are cumbersome to bandswitch and consequently are not very popular below 30 Mc. However, since the push-pull configuration places tube input and output capacitances in series, the circuit is widely used at 50 Mc. and higher.

TRIODE AMPLIFIERS

Circuits for triode amplifiers are shown in Fig. 6-26. Neglecting references to the screen, all of the foregoing information applies equally well to triodes. All triode straight amplifiers must be neutralized, as Fig. 6-26 indicates. From the tube tables, it will be seen that triodes require considerably more driving power than screengrid tubes. However, they also have less power sensitivity, so that greater feedback can be tolerated without the danger of instability.

Low-Frequency Parasitic Oscillation

When r.f. chokes are used in both grid and plate circuits of a triode amplifier, the split-stator tank capacitors combine with the r.f. chokes to form a low-frequency parasitic circuit, unless the amplifier circuit is arranged to prevent

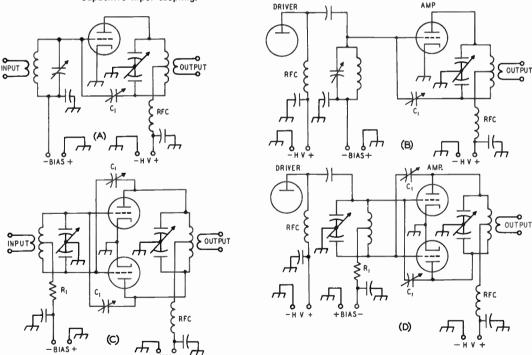


Fig. 6-26—Triade amplifier circuits. A—Link coupling, single tube. B—Capacitive coupling, single tube. C—Link coupling, push-pull. D—Capacitive coupling, push-pull. Aside from the neutralizing circuits, which are mandatory with triodes, the circuits are the same as for screen-grid tubes, and should have the same values throughout. The neutralizing capacitor, C₁, should have a capacitance somewhat greater than the grid-plate capacitance af the tube. Voltage rating should be twice the d.c. plate valtage for c.w., or four times for plate modulation, plus safety factor. The resistance R₁ should be at least 100 ohms and it may consist of part or preferably all of the grid leak. Far other component values, see similar screen-grid diagrams.

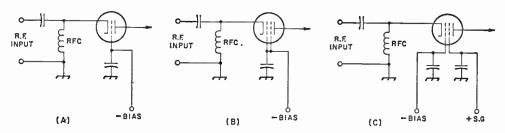


Fig. 6-27—A—Graunded-grid triade input circuit. B—Tetrade input circuit with grid and screen directly in parallel. C—Tetrade circuit with d.c. valtage applied to the screen. Plate circuits are conventional.

it. In the circuit of Fig. 6-26B, the amplifier grid is series fed and the driver plate is parallel fed. For low frequencies, the r.f. choke in the driver plate circuit is shorted to ground through the tank coil. In Figs. 6-26C and D, a resistor is substituted for the grid r.f. choke. This resistance should be at least 100 ohms. If any grid-leak resistance is used for biasing, it should be substituted for the 100-ohm resistor.

Triode Amplifiers with Pi-Network Output

Pi-network output tanks, designed as described earlier for screen-grid tubes, may also be used with triodes. However, in this case, a balanced input circuit must be provided for neutralizing. Fig. 6-25A shows the circuit when inductive-link input coupling is used, while B shows the circuit to be used when the amplifier is coupled capacitively to the driver. Pi-network circuits cannot be used in *both* input and output circuits, since no means is provided for neutralizing.

GROUNDED-GRID AMPLIFIERS

Fig. 6-27A shows the input circuit of a grounded-grid triode amplifier. In configuration it is similar to the conventional grounded-cathode circuit except that the grid, instead of the cathode, is at ground potential. An amplifier of this type is characterized by a comparatively low input impedance and a relatively high driver-power requirement. The additional driver power is not consumed in the amplifier but is "fed through" to the plate circuit where it combines with the normal plate output power. The total r.f. power output is the sum of the driver and amplifier output powers less the power normally required to drive the tube in a grounded-cathode circuit.

Positive feedback is from plate to cathode through the plate-cathode, or plate-filament, capacitance of the tube. Since the grounded grid is interposed between the plate and cathode, this capacitance is very small, and neutralization usually is not necessary.

A disadvantage of the grounded-grid circuit is that the cathode must be isolated for r.f. from ground. This presents a practical difficulty especially in the case of a filament-type tube whose filament current is large. Another disadvantage in plate-modulated phone operation is that the driver power fed through to the output is not modulated.

The chief application for grounded-grid amplifiers in amateur work at frequencies below 30 Mc. is in the case where the available driving power far exceeds the power that can be used in driving a conventional grounded-cathode amplifier.

D.c. electrode voltages and currents in grounded-grid triode-amplifier operation are the same as for grounded-cathode operation. Approximate values of driving power, driving impedance, and total power output in Class C operation can be calculated as follows, using information normally provided in tube data sheets. R.m.s. values are of the fundamental components:

$$E_{D} = r.m.s. \ value \ of r.f. \ plate \ voltage$$

$$= \frac{d.c. \ plate \ volts + d.c. \ bias \ volts - }{peak \ r.f. \ grid \ volts}$$

$$= \frac{1.41}{}$$

$$I_{p} = r.m.s.$$
 value of r.f. plate current
$$= \frac{rated \ power \ output \ watts}{E_{p}}$$

$$E_{g} = r.m.s.$$
 value of grid driving voltage
= $\frac{peak \ r.f. \ grid \ volts}{1.41}$

$$I_g = r.m.s.$$
 value of r.f. grid current
$$= \frac{rated \ driving \ power \ watts}{F_{rr}}$$

Then,

Driving power (watts) = $E_g (I_p + I_g)$

Driving impedance (ohms) =
$$\frac{E_g}{I_g + I_D}$$

Power fed through from driver stage (watts) = $E_g I_p$ Total power output (watts) = I_p ($E_g + E_p$)

Screen-grid tubes are also used sometimes in grounded-grid amplifiers. In some cases, the screen is simply connected in parallel with the grid, as in Fig. 6-27B, and the tube operates as a high- μ triode. In other cases, the screen is bypassed to ground and operated at the usual d.c. potential, as shown at C. Since the screen is still in parallel with the grid for r.f., operation is very much like that of a triode except that the positive voltage on the screen reduces driver-power requirements. Since the information usually fur-

Grounded-Grid Amplifiers

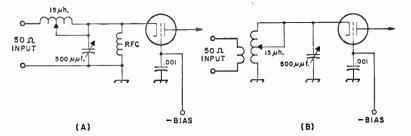


Fig. 6-28—Two
methods of caupling a law-impedance driver to a
graunded-grid input. A—L netwark.
B — Link - caupled
tank circuit.

nished in tube-data sheets does not apply to triode-type operation, operating conditions are usually determined experimentally. In general, the bias is adjusted to produce maximum output (within the tube's dissipation rating) with the driving power available.

Fig. 6-28 shows two methods of coupling a grounded-grid amplifier to the 50-ohm output of an existing transmitter. At A an L network is used, while a conventional link-coupled tank is shown at B. The values shown will be approximately correct for most triode amplifiers operating at 3.5 Mc. Values should be cut in half each time frequency is doubled, i.e., 250 $\mu\mu$ f. and 7.5 μ h. for 7 Mc., etc.

Filament Isolation

Since the filament or cathode of the grounded-grid amplifier tube operates at some r.f. potential above ground, it is necessary to isolate the filament from the power line. In the case of low-power tubes with indirectly heated cathodes, it is sometimes feasible to depend on the small capacitance existing between the heater and cathode, although it is preferable to provide additional isolation.


In Fig. 6-29A, isolation is provided by a special low-capacitance filament transformer. RFC_1 carries only the cathode current. However, since transformers of this type are not generally available, other means must usually be employed.


In Fig. 6-29B, chokes are used to isolate the filament from the filament transformer. The reactance of the chokes should be several times the input impedance of the amplifier and must be wound with conductor of sufficient size to carry the filament current. It is usually necessary to use a transformer delivering more than the rated filament voltage to compensate the voltage drop across the chokes. In Fig. 6-29C, r.f. chokes are placed in the primary side of the transformer. This reduces the current that the chokes must handle, but the filament transformer must be mounted so that it is spaced from the chassis and other grounded metal to minimize the capacitance of the transformer to ground, RFC1 carries cathode current only.


In the case of the input circuit of Fig. 6-28B, it is sometimes feasible to wind the tank inductor with two conductors in parallel, and feed the filament voltage to the tube through the two conductors, as shown in Fig. 6-29D. This arrangement does not lend itself well to bandchanging, however.


Fig. 6-29—Methods of isolating filament from ground.

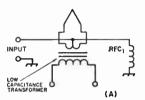A—Special low-capacitance filament transformer. B—
R.f. chokes in filament circuit. C—R.f. chokes in transformer primary. D—Filament fed through input tank inductor.



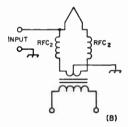

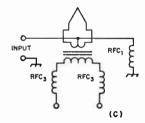

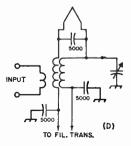

FREQUENCY MULTIPLIERS

Single-Tube Multiplier

Output at a multiple of the frequency at which it is being driven may be obtained from an amplifier stage if the output circuit is tuned to a harmonic of the exciting frequency instead of to the fundamental. Thus, when the frequency at the grid is 3.5 Mc., output at 7 Mc., 10.5 Mc., 14 Mc., etc., may be obtained by tuning the plate tank circuit to one of these frequencies. The circuit otherwise remains the same as that for a straight amplifier, although some of the values and operating conditions may require change for maximum multiplier efficiency.

Efficiency in a single- or parallel-tube multiplier comparable with the efficiency obtainable when operating the same tube as a straight amplifier involves decreasing the operating angle in proportion to the increase in the order of frequency multiplication. Obtaining output comparable with that possible from the same tube as a straight amplifier involves greatly increasing the plate voltage. A practical limit as to efficiency and output within normal tube ratings is reached when the multiplier is operated at maximum permissible plate voltage and maximum permissible grid current. The plate current should be reduced as necessary to limit the dissipation to the rated value by increasing the bias. High efficiency in multipliers is not often required in practice, since the purpose is usually served if the frequency multiplication is obtained without an appreciable gain in power in the stage.

Multiplications of four or five sometimes are used to reach the bands above 28 Mc. from a lower-frequency crystal, but in the majority of lower-frequency transmitters, multiplication in a single stage is limited to a factor of two or three, because of the rapid decline in practicably obtainable efficiency as the multiplication factor is increased. Screen-grid tubes make the best frequency multipliers because their high power-sensitivity makes them easier to drive properly than triodes.

Since the input and output circuits are not tuned close to the same frequency, neutralization usually will not be required. Instances may be encountered with tubes of high trans-conductance, however, when a doubler will oscillate in t.g.t.p. fashion, requiring neutralization. The link neutralizing system of Fig. 6-23A is convenient in such a contingency.

Push-Push Multipliers

A two-tube circuit which works well at even harmonics, but not at the fundamental or odd harmonics, is shown in Fig. 6-30. It is known as the push-push circuit. The grids are connected in push-pull while the plates are connected in parallel. The efficiency of a doubler using this circuit may approach that of a straight amplifier, because there is a plate-current pulse for each cycle of the output frequency.

This arrangement has an advantage in some applications. If the heater of one tube is turned off, its grid-plate capacitance, being the same as that of the remaining tube, serves to neutralize

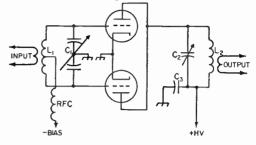


Fig. 6-30—Circuit of a push-push frequency multiplier for even harmonics.

C₁L₁ and C₂L₂—See text.

C₃-Plate bypass-0.001-\(mu f\), disk ceramic or mica. Voltage rating equal to plate voltage plus safety factor.

RFC-2.5-mh. r.f. choke.

the circuit. Thus provision is made for either straight amplification at the fundamental with a single tube, or doubling frequency with two tubes as desired.

The grid tank circuit is tuned to the frequency of the driving stage and should have the same constants as indicated in Fig. 6-20 for balanced grid circuits. The plate tank circuit is tuned to an even multiple of the exciting frequency, and should have the same values as a straight amplifier for the harmonic frequency (see Fig. 6-10), bearing in mind that the total plate current of both tubes determines the C to be used.

Push-Pull Multiplier

A single- or parallel-tube multiplier will deliver output at either even or odd multiples of the exciting frequency. A push-pull multiplier does not work satisfactorily at even multiples because even harmonics are largely canceled in the output. On the other hand, amplifiers of this type work well as triplers or at other odd harmonics. The operating requirements are similar to those for single-tube multipliers, the plate tank circuit being tuned, of course, to the desired odd harmonic frequency.

METERING

Fig. 6-31 shows how a voltmeter and milliammeter should be connected to read various voltages and currents. Voltmeters are seldom installed permanently, since their principal use is in preliminary checking. Also, milliammeters are not normally installed permanently in all of the positions shown. Those most often used are the ones reading grid current and plate current, or grid current and cathode current.

Milliammeters come in various current ranges. Current values to be expected can be taken from the tube tables and the meter ranges selected accordingly. To take care of normal overloads and pointer swing, a meter having a current

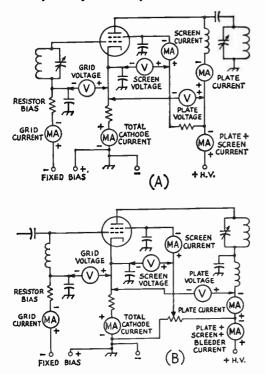


Fig. 6-31—Diagrams showing placement of voltmeter and milliammeter to obtain desired measurements. A—Series grid feed, parallel plate feed and series screen voltage-dropping resistor. B—Parallel grid feed, series plate feed and screen voltage divider.

range of about twice the normal current to be expected should be selected.

Meter Installation

Grid-current meters connected as shown in Fig. 6-31 and meters connected in the cathode circuit need no special precautions in mounting on the transmitter panel so far as safety is concerned. However, milliammeters having zeroadjusting screws on the face of the meter should be recessed behind the panel so that accidental contact with the adjusting screw is not possible, if the meter is connected in any of the other positions shown in Fig. 6-31. The meter can be mounted on a small subpanel attached to the front panel with long screws and spacers. The meter opening should be covered with glass or celluloid. Illuminated meters make reading easier. Reference should also be made to the TVI chapter of this Handbook in regard to wiring and shielding of meters to suppress TVI.

Meter Switching

Milliammeters are expensive items and therefore it is seldom feasible to provide even gridcurrent and plate-current meters for all stages. The exciter stages in a multistage transmitter often do not require metering after initial adjustments. It is common practice to provide a meter-switching system by which a single milliammeter may be switched to read currents in as many circuits as desired. Such a meter-switching circuit is shown in Fig. 6-32. The resistors, R, are connected in the various circuits in place of the milliammeters shown in Fig. 6-31. Since the resistance of R is several times the internal resistance of the milliammeter, it will have no practical effect upon the reading of the meter.

When the meter must read currents of widely differing values, a meter with a range sufficiently low to accommodate the lowest values of current to be measured may be selected. In the circuits in which the current will be above the scale of the meter, the resistance of R can be adjusted to a lower value which will give the meter reading a multiplying factor. (See chapter on Measurements.) Care should be taken to observe proper polarity in making the connections between the resistors and the switch.

A variation of the foregoing method uses the low-current meter as a voltmeter to measure the voltage drop across various low resistances placed in the lines where the currents are to be measured. Both the line resistor and the higher resistance running to the meter (corresponding to a normal voltmeter multiplier) can be varied, to give a wide range for the single meter. Standard values of resistors can usually be found for any desired range.

AMPLIFIER ADJUSTMENT

Earlier sections in this chapter have dealt with the design and adjustment of input (grid) and output (plate) coupling systems, the stabilization of amplifiers, and the methods of obtaining the

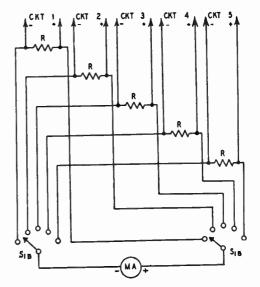


Fig. 6-32—Switching a single milliammeter. The resistors, R, should be 10 to 20 times the internal resistance of the meter; 47 ohms will usually be satisfactory. S_1 is a 2-section rotary switch. Its insulation should be ceramic for high voltages, and an insulating coupling should always be used between shaft and control.

required electrode voltages. Reference to these sections should be made as necessary in following a procedure of amplifier adjustment.

The objective in the adjustment of an intermediate amplifier stage is to secure adequate excitation to the following stage. In the case of the output or final amplifier, the objective is to obtain maximum power output to the antenna. In both cases, the adjustment must be consistent with the tube ratings as to voltage, current and

dissipating ratings.

Adequate drive to a following amplifier is normally indicated when rated grid current in the following stage is obtained with the stage operating at rated bias, the stage loaded to rated plate current, and the driver stage tuned to resonance. In a final amplifier, maximum output is normally indicated when the output coupling is adjusted so that the amplifier tube draws rated plate current when it is tuned to resonance.

Resonance in the plate circuit is normally indicated by the dip in plate-current reading as the plate tank capacitor is tuned through its


range. When the stage is unloaded, or lightly loaded, this dip in plate current will be quite pronounced. As the loading is increased, the dip will become less noticeable. See Fig. 6-4. However, in the base of a screen-grid tube whose screen is fed through a series resistor, maximum output may not be simultaneous with the dip in plate current. The reason for this is that the screen current varies widely as the plate circuit is tuned through resonance. This variation in screen current causes a corresponding variation in the voltage drop across the screen resistor. In this maximum output may occur at an adjustment that results in an optimum combination of screen voltage and nearness to resonance. This effect will seldom be observed when the screen is operated from a fixedvoltage source.

The first step in the adjustment of an amplifier is to stabilize it, both at the operating frequency by neutralizing it if necessary, and at parasitic frequencies by introducing suppression circuits.

If "flat" transmission-line coupling is used, the output end of the line should be matched, as described in the chapter for the case where the amplifier is to feed the grid of a following stage, or in the transmission-line chapter if the amplifier is to feed an antenna system. After proper match has been obtained, all adjustments in coupling should be made at the input end of the line.

Until preliminary adjustments of excitation have been made, the amplifier should be operated with filament voltage on and fixed bias, if it is required, but screen and plate voltages off. With the exciter coupled to the amplifier, the coupling to the driver should be adjusted until the amplifier draws rated grid current, or somewhat above the rated value. Then a load (the antenna grid of the following stage, or a dummy load) should be coupled to the amplifier.

With screen and plate voltages (preferably reduced) applied, the plate tank capacitor should be adjusted to resonance as indicated by a dip in plate current. Then, with full screen and plate voltages applied, the coupling to the load should be adjusted until the amplifier draws rated plate current. Changing the coupling to the load will usually detune the tank circuit, so that it will be necessary to readjust for resonance each time a change in coupling is made. An amplifier should not be operated with its plate circuit off reso-

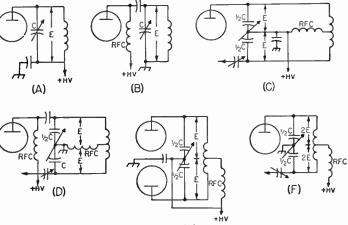

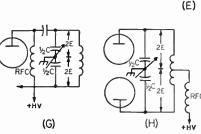


Fig. 6-33—Diagrams showing the peak voltage for which the plate tank capacitor should be rated for c.w. operation with various circuit arrangements. E is equal to the d.c. plate voltage. The values should be doubled for plate modulation. The circuit is assumed to be fully loaded. Circuits A, C and E require that the tank capacitor be insulated from chassis or ground, and from the control.

nance for any except the briefest necessary time, since the plate dissipation increases greatly when the plate circuit is not at resonance. Also, a screen-grid tube should not be operated without normal load for any appreciable length of time. since the screen dissipation increases.

It is normal for the grid current to decrease when the plate voltage is applied, and to decrease again as the amplifier is loaded more heavily. As the grid current falls off, the coupling to the

Component Ratings

driver should be increased to maintain the grid current at its rated value.

COMPONENT RATINGS AND INSTALLATION


Plate Tank-Capacitor Voltage

In selecting a tank capacitor with a spacing between plates sufficient to prevent voltage breakdown, the peak r.f. voltage across a tank circuit under load, but without modulation, may be taken conservatively as equal to the d.c. plate voltage. If the d.c. plate voltage also appears across the tank capacitor, this must be added to the peak r.f. voltage, making the total peak voltage twice the d.c. plate voltage. If the amplifier is to be plate-modulated, this last value must be doubled to make it four times the d.c. plate voltage, because both d.c. and r.f. voltages double with 100-per-cent plate modulation. At the higher plate voltages, it is desirable to choose a tank circuit in which the d.c. and modulation voltages do not appear across the tank capacitor, to permit the use of a smaller capacitor with less plate spacing. Fig. 6-33 shows the peak voltage, in terms of d.c. plate voltage, to be expected across the tank capacitor in various circuit arrangements. These peak-voltage values are given assuming that the amplifier is loaded to rated plate current. Without load, the peak r.f. voltage will run much higher.

The plate spacing to be used for a given peak voltage will depend upon the design of the variable capacitor, influencing factors being the mechanical construction of the unit, the insulation used and its placement in respect to intense fields, and the capacitor plate shape and degree of polish. Capacitor manufacturers usually rate their products in terms of the peak voltage between plates. Typical plate spacings are shown in the following table.

Typical Tank-Capacitar Plate Spacings						
Spacing	Peak	Spacing	Peak	Spacing Peak		
(In.)	Voltage	(In.)	Voltage	(In.) Voltage		
0.015	1000	0.07	3000	0.175 7000		
0.02	1200	0.08	3500	0.25 9000		
0.03	1500	0.125	4500	0.35 11000		
0.05	2000	0.15	6000	0.5 13000		

Plate tank capacitors should be mounted as close to the tube as temperature considerations will permit, to make possible the shortest capacitive path from plate to cathode. Especially at the higher frequencies where minimum circuit capacitance becomes important, the capacitor should be mounted with its stator plates well spaced from the chassis or other shielding. In circuits where the rotor must be insulated from ground, the capacitor should be mounted on ceramic insulators of size commensurate with the plate voltage involved and — most important of all, from the viewpoint of safety to the operator — a well-insulated coupling should be used between the capacitor shaft and the dial. The sec-

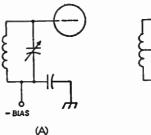

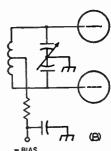


Fig. 6-34—The valtage rating of the grid tank capacitar in A should be equal to the biasing valtage plus about 20 per cent of the plate valtage.

tion of the shaft attached to the dial should be well grounded. This can be done conveniently through the use of panel shaft-bearing units.

Grid Tank Capacitors

In the circuit of Fig. 6-34A, the grid tank capacitor should have a voltage rating approximately equal to the biasing voltage plus 20 per cent of the plate voltage. In the balanced circuit of B, the voltage rating of each section of the capacitor should be this same value.

The grid tank capacitor is preferably mounted with shielding between it and the tube socket for isolation purposes. It should, however, be mounted close to the socket so that a short lead can be passed through a hole to the socket. The rotor ground lead or bypass lead should be run directly to the nearest point on the chassis or other shielding. In the circuit of Fig. 6-34A, the same insulating precautions mentioned in connection with the plate tank capacitor should be used.

Plate Tank Coils

The inductance of a manufactured coil usually is based upon the highest plate-voltage/ plate-current ratio likely to be used at the maximum power level for which the coil is designed. Therefore in the majority of cases, the capacitance shown by Figs. 6-9 and 6-20 will be greater than that for which the coil is designed and turns must be removed if a Q of 10 or more is needed. At 28 Mc., and sometimes 21 Mc., the value of capacitance shown by the chart for a high plate-voltage/plate-current ratio may be lower than that attainable in practice with the components available. The design of manufactured coils usually takes this into consideration also and it may be found that values of capacitance greater than those shown (if stray capacitance is included) are required to tune these coils to the band.

Manufactured coils are rated according to the plate-power input to the tube or tubes when the stage is loaded. Since the circulating tank current is much greater when the amplifier is unloaded, care should be taken to operate the amplifier conservatively when unloaded to prevent damage to the coil as a result of excessive heating.

Tank coils should be mounted at least their diameter away from shielding to prevent a marked loss in Q. Except perhaps at 28 Mc., it is not important that the coil be mounted quite close to the tank capacitor. Leads up to 6 or 8 inches are permissible. It is more important to keep the tank capacitor as well as other components out of the immediate field of the coil. For this reason, it is preferable to mount the coil so that its axis is parallel to the capacitor shaft, either alongside the capacitor or above it.

There are many factors that must be taken into consideration in determining the size of wire that should be used in winding a tank coil. The considerations of form factor and wire size that will produce a coil of minimum loss are often of less importance in practice than the coil size that will fit into available space or that will handle the required power without excessive heating. This is particularly true in the case of screen-grid tubes where the relatively small driving power required can be easily obtained even if the losses in the driver are quite high. It may be considered preferable to take the power loss if the physical size of the exciter can be kept down by making the coils small.

The accompanying table shows typical conductor sizes that are usually found to be adequate for various power levels. For powers under 25 watts, the minimum wire sizes shown are largely a matter of obtaining a coil of reasonable Q. So far as the power is concerned, smaller wire could be used.

Wire Sizes for Transmitting Coils					
Power Input (Watts)	Band (Mc.)	Wire Size			
1000	28-21 14-7 3.5-1.8	6 8 10			
500	28-21 14-7 3,5-1.8	8 12 14			
150	28-21 14-7 3.5-1.8	12 14 18			
75	28-21 14-7 3.5-1.8	14 18 22			
25 or less*	28-21 14-7 3.5-1.8	18 24 28			
*Wire size limited principally by consideration of Q.					

Space-winding the turns invariably will result in a coil of higher Q, especially at frequencies above 7 Mc., and a form factor in which the turns spacing results in a coil length between 1 and 2 times the diameter is usually considered satisfactory. Space winding is especially desirable at the higher power levels because the heat developed is dissipated more readily. The power lost in a tank coil that develops appreciable heat

at the higher-power levels does not usually represent a serious loss percentagewise. A more serious consequence, especially at the higher frequencies, is that coils of the popular "air-wound" type supported on plastic strips may deform. In this case, it may be necessary to use wire (or copper tubing) of sufficient size to make the coil self-supporting. Coils wound on tubular forms of ceramic or mica-filled bakelite will also stand higher temperatures.

Plate-Blocking and Bypass Capacitors

Plate-blocking and bypass capacitors should have low inductance. Between 3.5 and 30 Mc. a capacitance of 0.001 μ f. is commonly used. The voltage rating should be 50% above the peak supply voltage.

Disk ceramic capacitors are to be preferred as bypass capacitors, since when they are applied correctly (see TVI chapter), they are series resonant in the TV range and thus very useful in filtering power leads.

R. F. Chokes

The characteristics of any r.f. choke will vary with frequency, from characteristics resembling those of a parallel-resonant circuit, of high impedance, to those of a series-resonant circuit, where the impedance is lowest. In between these extremes, the choke will show varying amounts of inductive or capacitive reactance.

In series-feed circuits, these characteristics are of relatively small importance because the r.f. voltage across the choke is negligible. In a parallel-feed circuit, however, the choke is shunted across the tank circuit, and is subject to the full tank r.f. voltage. If the choke does not present a sufficiently high impedance, enough power will be absorbed by the choke to cause it to burn out.

To avoid this, the choke must have a sufficiently high reactance to be effective at the lowest frequency, and yet have no series resonances near the higher-frequency bands.

Universal pie-wound chokes of the "receiver" type (2.5 mh., 125 ma.) are usually satisfactory if the plate voltage does not exceed 750. For higher voltages, a single-layer solenoid-type choke of correct design has been found satisfactory. The National type R-175A and Raypar RL-100, RL-101 and RL-102 are representative manufactured types.

Since the characteristics of a choke will be affected by any metal in its field, it should be checked when mounted in the position in which it is to be used, or in a temporary set-up simulating the same conditions. The plate end of the choke should not be connected, but the power-supply end should be connected directly, or by-passed, to the chassis. The g.d.o. should be coupled as close to the ground end of the choke as possible. Series resonances, indicating the frequencies of greatest loss, should be checked with the choke short-circuited with a short piece of wire. Parallel resonances, indicating frequencies of least loss, are checked with the short removed.

A THREE-BAND OSCILLATOR TRANSMITTER FOR THE NOVICE

The novice transmitter shown in Figs. 6-35-6-38, inclusive, is easy to build and get working. It is a crystal-controlled, one-tube oscillator capable of running at 30 watts input on the 3.5-, 7-, and 21-Mc. Novice bands. A special feature of the transmitter is a built-in keying monitor which permits the operator to listen to his own sending.

Regulated voltage is used on the screen of the oscillator. This minimizes frequency shift of the oscillator with keying, which is the cause of chirp. In addition, a small amount of cathode bias (R_4) is used on the oscillator. This also tends to improve the keying characteristics in a cathode-keyed simple-oscillator transmitter.

Circuit Details

The oscillator circuit used is the grid-plate type, and the tube is a 6DQ6A pentode. The power output is taken from the plate circuit of the tube. On 80 meters, an 80-meter crystal is needed. On 40, either 80- or 40-meter crystals can be used, although slightly more output will be obtained by using 40-meter crystals. To operate on 15 meters, a 40-meter crystal is used.

The tank circuit is a pi network. The plate tank capacitor is the variable C_6 , and the tank inductance is L_2L_3 . C_8 is a two-section variable, approximately 365 $\mu\mu$ f. per section, with the stators connected together to give a total capacitance of about 730 $\mu\mu$ f. This range of capacitance is adequate for coupling to 50 or 75 ohms on 7 and 21 Mc. When operating on 3.5 Mc., an additional 1000 $\mu\mu$ f. (C₇) is added to furnish the needed range of capacitance. L_1 and R_2 are essential for suppressing v.h.f. parasitic oscillations.

The keying-monitor circuit uses a neon bulb (type NE-2) audio-frequency oscillator connected to the cathode of the 6DQ6A at the key jack, J_1 . The headphones are plugged into J_2 , a jack mounted on the back of the transmitter chassis. Another jack, J_3 , is used as a terminal for the leads that go to the headphone jack on the receiver.

The power supply uses a 5U4G in a full-wave circuit. A capacitor-input filter is used and the output voltage is approximately 370 volts with a cathode current of 90 milliamperes. A 0-150 milliammeter reads cathode current. The screen and grid currents are approximately 4 ma. when the oscillator is loaded.


Power Supply

Construction

All of the components, including the power supply, are mounted on a $2 \times 7 \times 13$ -inch aluminum chassis that is in turn enclosed in a 7 × 9 × 15-inch aluminum box. (Premier AC-1597). One of the removable covers of the box is used as the front panel, as shown in Fig. 6-35. The box has a 1/2-inch lip around both openings, so the bottom edge of the chassis should be placed one inch from the bottom of the panel. The sides of the chassis are also one inch from the sides of the panel. The chassis is held to the panel by S_2 , J_1 , and the mounting screws for the crystal socket, so both the front edge of the chassis and the panel must be drilled alike for these components. S_1 , at the left in the front view, is one inch from the edge of the chassis (that is, two inches from the edge of the panel) and centered vertically on the chasis edge. Thus it is one inch from the bottom of the chassis edge and two inches from the bottom edge of the panel. The hole for J_1 is centered on the chassis edge and the holes for the crystal socket are drilled at the right-hand end of the chassis to correspond with the position of S_1 at the left.

There is nothing critical about the placement of the meter or the shafts for C_6 , C_8 and S_1 . As shown in Fig. 6-38, C6 is mounted directly above J_1 and approximately two inches from the top of the panel. C8 similarly is above the crystal socket and on the same horizontal line as C_6 . S_1 is about at the middle of the square formed by these four components.

Fig. 6-35-This 30-watt three-band Novice transmitter is enclosed in a 7 × 9 × 15-inch aluminum box. A group of 1/4-inch-diameter holes should be drilled in the top of the box over the oscillator tube, as shown, to provide ventilation. A similar set of holes should be drilled in the back cover behind the oscillator circuit.

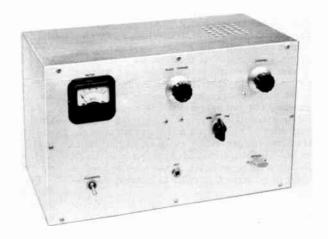

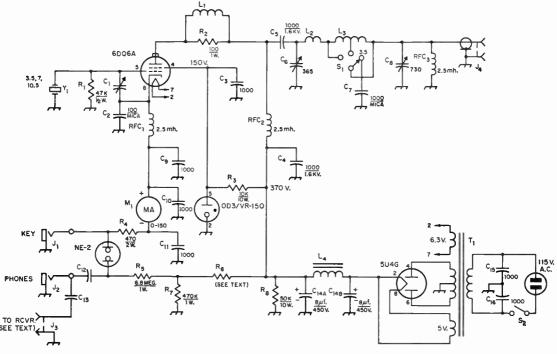


Fig. 6-36—Circuit diagram of the three-band transmitter. Unless otherwise specified, capacitances are in $\mu\mu$ f. Resistances are in ohms (K = 1000).

 C_1 -3-30- $\mu\mu$ f, trimmer.

 $C_2-100-\mu\mu f.$ mica.

 C_3 , C_9 , C_{10} , C_{11} , C_{15} , C_{16} —0.001- μf . disk ceramic.

 C_4 , C_8 =0.001- μ f. 1600-volt disk ceramic.

C_e—365-μμf. variable capacitor, single section, broadcast-replacement type.

C7-0.001-#f. 600-volt mica.

 C_8 -365- $\mu\mu f$, variable capacitor, dual section, broad-cast-replacement type.

 C_{12} -500- $\mu\mu$ f. mica or ceramic.

 C_{13} -0.01- μ f. disk ceramic.

 $C_{14}-8/8-\mu f$. 450-volt dual electrolytic capacitor.

J1, J2-Open-circuit phone jack.

J₃-Phono jack, RCA type.

J₄-Coaxial chassis connector, SO-239.

L₁-10 turns No. 18 wire space-wound on R₂.

The holes on the rear edge of the chassis for the coaxial connector J_4 , phone jack J_2 , receiver connector J_3 , and for the a.c. cord are drilled at the same height as those on the front edge. Access holes should be cut in the rear cover of the box at the corresponding positions; these holes may be large enough to clear the components, but not larger than is necessary for this purpose. The cover fits tightly against the rear edge of the chassis and thus maintains the shielding for preventing radiation of harmonics in the television bands. However, it is advisable to fasten the cover to the chassis edge with a few sheet-metal screws, in order to insure good electrical contact.

There are several different types of broadcastreplacement variable capacitors on the market. L₂-6 turns No. 16 wire, 8 turns per inch, 11/4 inches diam. (B & W 3018).

 L_3 -23 turns No. 16 wire, 8 turns per inch, 11/4 inches diam. (B & W 3018). The 7-Mc. tap is 18 turns from the junction of L_2 and L_3 .

L₄-8-h. 150-ma. filter choke (Thordarson 20C54).

M₁-0-150 ma (Shurite 950).

R₁-R₈ inc.-As specified.

RFC₁, RFC₂, RFC₃—2.5-mh. r.f. choke (National R-50 or similar).

 S_1 —Single-pole 3-position switch (Centralab 1461).

S2-Single-pole single-throw toggle switch.

T₁-Power transformer: 360-0-360 volts, 120 ma.; 6.3 volts, 3.5 amp.; 5 volts, 3 amp. (Stancor PM-8410).

Y₁-Crystal (see text).

Some of these have holes tapped in the front of the frame, and this type can be mounted directly on the panel using machine screws and spacers. Others have mounting holes only in the bottom. In this case, the capacitor can be mounted on a pair of L-shaped brackets made from strips of aluminum.

Both L_2 and L_3 are supported by their leads. One end of L_3 is connected to the stator of C_8 and the other end is connected to a junction on top of a one-inch-long steatite stand-off insulator. L_2 has one end connected to the stator of C_6 and the other end to one of the terminals on S_1 .

The voltage-dividing network consisting of R_6 and R_7 provides the correct voltage for operating the keying monitor, R_6 is 1.65 megohms, a value obtained by using two 3.3-megohm 1-watt



Fig. 6-37—Rear view of the transmitter showing the placement of components above chassis. The loading capacitor, C_8 , is at the left, L_3 is the vertical coil and L_2 the horizontal one. Rubber grommets are used to prevent chafing and ta furnish additional insulation on the leads coming from below chassis.

resistors in parallel. These resistors and other small components may be mounted on standard bakelite tie points.

Adjustment and Testing

When the unit is ready for testing, a 15- or 25-watt electric light will serve as a dummy load. One side of the lamp should be connected to the output lead and the other side to chassis ground. A crystal appropriate for the band to be used should be plugged into the crystal socket, and a key connected to the key jack. S_1 should be set to the proper band. S_2 may then be closed and the transmitter allowed to warm up.


Set C_8 at maximum capacitance (plates completely meshed) and close the key. Quickly tune C_6 to resonance, as indicated by a dip in the cathode-current reading. Gradually decrease the capacitance of C_8 , while retouching the tuning of C_6 as the loading increases. Increased loading will be indicated by increasing lamp brightness and by larger values of cathode current. Tune

for maximum lamp brilliance. The cathode current should read between 90 and 100 milliamperes when the oscillator is fully loaded.

 C_1 should be adjusted for the best keying characteristics consistent with reasonably good power output. It is not advisable to attempt to adjust C_1 with a lamp dummy load, since the lamp resistance will change during the heating and cooling that take place during keying, and this will affect the keying characteristic of the oscillator. Use a regular antenna, with or without an antenna coupler or matching network as the antenna system may require, and listen to the keying on the station receiver. Remove the antenna from the receiver to prevent overloading, and adjust the r.f. gain control for a signal level comparable with that at which signals on that band are normally heard. Further details on checking keying will be found in the chapter on keying and break-in.

(Originally described in *QST* December, 1957.)

Fig. 6-38—Below-chassis view. Power-supply components are mounted in the lefthand side and the oscillator section is at the right-hand side, Mounted on the back wall of the chassis is the keying monitor. Although not visible in this view, the monitor companents are mounted on a fourterminal tie point.

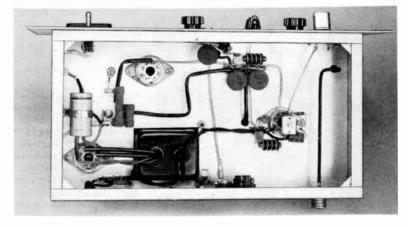

AN INEXPENSIVE 75-WATT FIVE-BAND TRANSMITTER

The transmitter shown in Figs. 6-39 and 6-41 combines the efficiency and flexibility of plug-in coils with good shielding for TVI prevention. It is a two-stage transmitter using a 6AG7 crystal oscillator and an inexpensive 1625 tetrode amplifier. The latter tube is quite inexpensive in surplus and probably represents the least "dollars per watt" of any available tube. Provision is included for crystal-controlled operation, and terminals are provided for connecting v.f.o.

Referring to the circuit diagram of the transmitter, Fig. 6-40, a 6AG7 grid-plate type crystal-controlled oscillator is used. The output can be tuned to the crystal frequency or to multiples of it, depending upon the coil plugged in at L_1 .

Both 80- and 40-meter crystals are used; for 80-meter operation a 3.5-Mc. crystal is used (L1 is not required on this band because RFC₂ serves the purpose.) The same crystal will furnish adequate drive on 40 meters, with the oscillator stage working as a doubler, and it can even be stretched to 20 meters by quadrupling in the oscillator. A 40-meter crystal can be used for 7-Mc. work, and it can be used on 20 by doubling in the oscillator, on 21 Mc. by tripling and on 28 Mc. by quadrupling. With some crystals it will not be possible to get adequate drive by quadrupling to 28 Mc., and in these cases both oscillator and amplifier should be operated as doubler stages. The small trimmer, C_1 , in the grid circuit is an excitation control, and is set at a position that gives best keying (when the oscillator is keyed) consistent with adequate

The amplifier tank circuit is a pi network designed primarily for working into a low impedance (50 to 75 ohms) load. A 140- $\mu\mu$ f. capacitor, C_s , is used for plate tuning on all bands; on 80 meters it is shunted by an additional 100 $\mu\mu$ f. This is done automatically by a jumper connection in the coil. The loading capacitor is a midget two-section capacitor designed for use in small receivers, but by connecting the two stators in parallel a 500- $\mu\mu$ f. variable is ob-

tained at low cost. On 80 meters it is shunted by a 1000- $\mu\mu$ f. fixed capacitor. RFC_5 and the associated 100-ohm resistor in the plate lead of the 1625 are for suppressing parasitic oscillations.

Two methods of keying are provided. The oscillator and amplifier can be keyed simultaneously, by using the connections of Fig. 6-43A, or the amplifier only can be keyed, with the oscillator running all the time during transmitting, by using the connections of Fig. 6-43C.

The latter keying system should be used if reports of a chirpy signal are obtained. Although it is not shown, it is possible to incorporate a "spotting" switch with the system of Fig. 6-43A; S₁ will serve that purpose in Fig. 6-43C.

A 0-5 milliammeter is used to meter the grid and cathode circuits of the 1625 amplifier stage. When the meter is switched to the grid circuit, it reads directly (0 to 5 ma.), but when it is switched across RFC_s in the cathode circuit, the 0.1-ohm resistance of the choke serves as a shunt to convert the full-scale reading of the meter to 375 ma.

Construction Details

Before drilling any holes for the components, it would be wise to study the arrangement of parts on the $10\times12\times3$ -inch aluminum chassis. While the location of components is not critical, some initial planning will permit leads to be made direct and as short as possible.

The only unusual construction in the transmitter will be the bracket that holds the 1625 socket and the installation of the shield around the meter. The bracket is made from a piece of aluminum that can be bent in a vise. It is cut in the shape of a symmetrical trapezoid, and a ½-inch wide lip is first bent along the long side. Notches are then cut in the lip to permit the sides to be bent in, to form the bracket as shown in Fig. 6-41. The platform the socket is mounted on measures $2\frac{1}{2} \times 2\frac{3}{4}$ inches, and the sides taper from nothing to 1 inch.

The shield around the meter is a 2½/ ×2½/8×15½-inch "Minibox" (Bud CU-3000A).

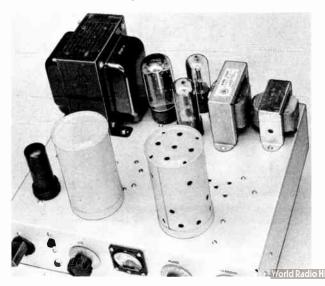


Fig. 6:39—An inexpensive 75-watt transmitter using plug-in coils and an "economy" power supply. The oscillator (left) is a 6AG7; the 1625 output tube is mounted underneath the chassis. Shield cans are baking-powder tins painted gray; the can for the output coil (right) is ventilated for better cooling, as is the chassis behind the can.

Complete transmitter is built on $10\times12\times3$ -inch aluminum chassis. At the rear of the chassis, from left to right: power transformer, 5U4-GB, 6DE4s, 150-ma. choke, 12.6-volt filament transformer.

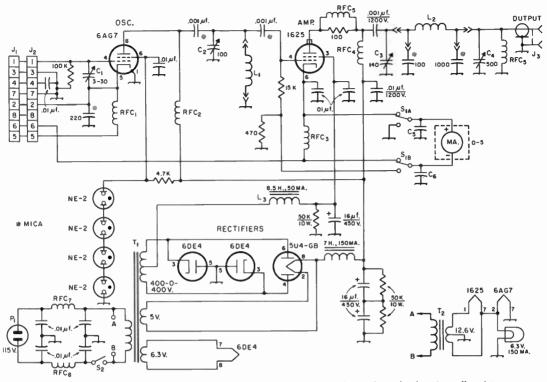


Fig 6-40—Circuit diagram of the inexpensive 75-watt transmitter. Unless indicated otherwise, all resistors are $\frac{1}{2}$ watt, all resistances are in ohms, all capacitances are in $\mu\mu$ f. Electrolytic capacitors are marked with polarity, mica capacitors are marked with *, other fixed capacitors are ceramic.

 C_1 —3- to 30- $\mu\mu$ f. mica compression trimmer.

C2-100-µµf. midget variable (Hammarlund APC-100B).

 C_3 —140- $\mu\mu$ f. midget variable (Hammarlund APC-140B). C_4 —Midget superhet two-gang variable, 365 and 135

C₆—Midget superhet two-gang variable, 305 and 135 μμf., sections connected in parallel (Allied Radio, Chicago, 61 H 008).

 C_5 , C_6 —1500- $\mu\mu$ f. feedthrough capacitor (Centralab FT-1500).

J₁, J₂—Octal tube sockets.

J₈-Coaxial receptacle (SO-239).

L₁, L₂—See coil table.

L_s-8½-h. 50-ma. filter choke (Knight 62 G 136).

L₄-7-h. 150-ma. choke (Stancor C-1710).

MA₁-0-5 milliammeter, 1%-inch square (Micronta).

The section with the lips has a clearance hole for the meter drilled in it, and it is held to the front of the chassis by the meter mounting screws. The other section of the Minibox has two 1500- $\mu\mu$ f. feedthrough capacitors mounted in it. At assembly flexible leads from the meter are soldered to the inner ends of the capacitors, and when assembly is completed, the external connections to the meter can be made at the protruding capacitor leads.

No other special construction is required, since all of the components can be mounted with accompanying hardware or by means of 6-32 screws and nuts. Reference to Fig. 6-41 will show how multiple tie points have been provided at every opportunity for the support of

P1-Fused line plug, 11/2-amp. fuses.

RFC₁, RFC₄, RFC₆-2.5-mh. 100-ma. (National R-50).

RFC₂-100 μh. r.f. choke (Millen 34300-100).

RFC₈-0.82- μ h. r.f. choke, 0.1 ohms (Millen 34300-0.82).

RFC₆—8 turns No. 18 enam. wound on 100-ohm (Sprague 5KT1015) resistor.

RFC₇, RFC₈—16 turns No. 18 enam., self-supporting, wound on %-inch diam. form before removing and spacing to occupy % inch length.

S₁-D.p.d.t. toggle.

S2-S.p.s.t. slide or toggle switch.

T₁—800-v.c.t. power transformer, 5 v. at 3 a., 6.3 v. at 5 a. (Thordarson 24RO7-U or Knight 61 G 414).
T₂—12.6 v. at 2.0 amp. (Knight 61 G 420).

resistors, r.f. choke coils, filter capacitors and other components. RFC_7 and RFC_8 are supported between tie points that also serve as terminals for the line cord and associated 0.01- μ f. capacitors. These r.f. choke coils are first wound on a $\frac{1}{2}$ 8-inch diameter form (a drill is excelent) and then removed and stretched slightly. RFC_8 is wound directly over the associated 100-ohm resistor and its ends are soldered to the leads of the resistor.

The two shield cans for L_1 and L_2 are made from baking-powder (Calumet) tins that have clearance holes for the ceramic tube sockets punched in their covers. To dress them up a bit, the cans may be sprayed with gray paint. The can for L_2 was drilled in a few spots to provide ventilation, since the coil may get warm on 80 meters. To provide for the addition of extra capacitors at L_2 in the 80-meter range, a 5-pin socket is used at L_2 and a 4-pin socket at L_1 . A hood (Amphenol 83-765) is used at the back of J_2 to maintain the shielding.

Information on the plug-in coils is given in the coil table. The coils are mounted inside the polystyrene forms. When cutting the coils from the original stock allow a few extra turns for the leads that are run down through the coilform pins. An easy way to cut the coils from the original stock is to heat a razor blade and use it to slice through the polystyrene bars. Ventilation holes are included in the base of the 80-meter coil. Before soldering to the pins of the coil forms, clean the inside of the pins with a drill or Swiss file; it will make soldering a lot easier. When soldering, hold the pin with a pair of pliers, to prevent too much heat from reaching the coil form proper and softening the polystyrene. After the solder has cooled, clean off any rosin with a knife or some alcohol. The coils can be finished off by sliding an identification slip between the coil and the form.

Tune-Up Procedure

For the initial testing, a 60-watt lamp bulb will make a suitable dummy load. Connect it at J_8 through a short length of cable or wires and a plug. Plug in an 80-meter crystal at Pins 1 and 3 or 1 and 7 at J_1 , and connect the telegraph key to Pins 5 and 7 of J_2 . Set C_2 at minimum capacitance, and unscrew the adjustment on C_1 until the plates just begin to separate visibly. Plug in the 80-meter L_2 and the tubes and rectifiers.

With S_2 in the "off" position, plug P_1 (properly fused) into a wall outlet and turn on S_1 . The pilot lamp should light and the cathodes of the rectifiers should warm up. After a half minute or so, close the telegraph key and on a warmed-up receiver tuned to the crystal frequency listen for the oscillator. If you find the oscillator isn't working, check the wiring for errors.

When the oscillator has been checked and is working properly, turn off the transmitter and connect a jumper between Pins 5 and 6 in the plug in J_2 . Now when the key is closed both the oscillator and amplifier will be keyed. Set C_3

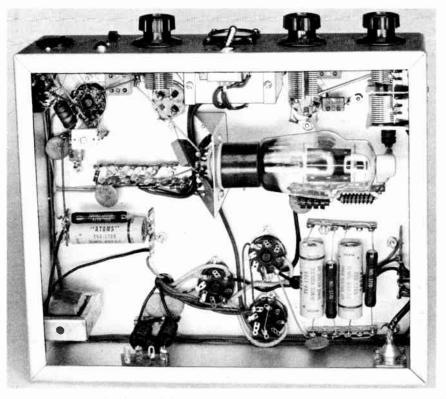


Fig. 6-41—View underneath the chassis of the 75-watt transmitter. The 1625 amplifier tube is mounted horizontally; the tube socket is supported by an aluminum bracket (center). The string of NE-2 neon bulbs, supported by their leads on a multiple tie point, is to the left of the bracket.

At the upper left-hand corner, the panel socket, J_1 , is duplicated by the side socket, J_2 , mounted nearby. The panel socket is used for a crystal socket or for v.f.o. input, and the side socket is for keying and control circuits. Note at the top center that the meter is shielded by the small Minibox.

The a.c. line cord is brought in at the rear of the chassis through a rubber grommet, and the associated 0.01- μ f. capacitors and RFC₈ and RFC₇ are mounted at this point. The r.f. output jack, J_8 , is at the lower right.


Cail Table for 75-Watt Transmitter

All coils except 10-meter L_2 are made from 1-inch diameter 16 t.p.i. No. 20 wire stock (B&W 3015 or Illumitronics 816). L_1 coils are mounted inside 4-pin polystyrene form (Allied Radio 71 H 713) and L_2 coils are mounted inside 5-pin polystyrene (Allied Radio 71 H 714). 10-meter L_2 stock is 34-inch diameter 8 t.p.i. No. 18 wire stock (B&W 3010 or Illumitronics 608).

Band	L_{1}	L_2
80 m.	none	301/2 turns *
40 m.	21 turns	20½ turns
20 m.	10½ turns	10½ turns
15 m.	5½ turns	7½ turns
10 m.	Same as 20 m.	7 turns

^{*}With jumpers to connect auxiliary capacitors; see Fig. 6-40. Six 1/4-inch diameter ventilation holes drilled near bottom of coil form.

and C4 at about three-fourths fully meshed and turn on the transmitter again. When the tubes have warmed up, close the telegraph key and tune C₈ between half and fully meshed. A point should be found where the dummy load will show some light. Open the key and switch S_1 to read grid current if it isn't there already. Close the key and observe the grid current; it should be about 3 ma. If it is more it can be reduced by adjustment of C_2 . Switching S_1 to read cathode current, it should read about 1.6 ma. on the meter, corresponding to a cathode current of 120 ma. (The full-scale reading of the meter in this condition is 375 ma.; thus 1.0 = 75 ma., 2.0 = 150 ma., and so on.) If the cathode current at resonance (dip in current as C_3 is tuned) is higher than 1.6 on the meter, the loading can be reduced by turning C_4 in the direction of more capacitance (plates meshed further). Since the

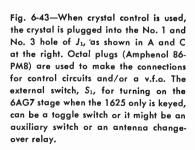


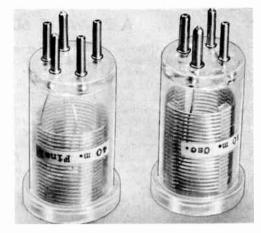


Fig. 6-42—All coils are mounted in (or on) polystyrene plug-in coil forms. The 7-Mc. coils are shown here.

plate voltage runs about 670 volts with this supply, the proper cathode-current reading for 75 watts input is 1.6 (120 ma., allowing 11 ma. for grid and screen-grid currents).

When the transmitter has been checked on 80 meters, the coils for 40 meters can be plugged in and the checking process can be repeated. In this case, and in all others except the 80-meter case, the oscillator tuning C_2 will be relatively sharp. When setting C_2 on the higher ranges (20, 15 and ·10 meters), the output should be carefully checked to insure that a wrong harmonic of the crystal is not selected. Use a receiver to check or, better yet, an absorption wavemeter or other selective device.

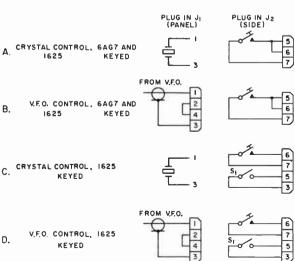When a certain familiarity has been obtained with the operation of the transmitter, plug in a 7-Mc. crystal and tune up the transmitter on 15 meters. Then adjust C_1 so that the amplifier grid current is no more than 3 ma. with C_2 peaked for maximum reading. This adjustment need not be changed after it has been set, with crystals of ordinary activity.



A 75-WATT 6DQ5 TRANSMITTER

The transmitter shown in Fig. 6-44 is designed to satisfy the requirements of either a Novice or General Class licensee. As described here it is capable of running the full 75 watts limit in the 80-, 40- and 15-meter Novice bands, with band switching, crystal switching and other operating features. The General license holder can use the transmitter in any band 80 through 10 meters, and he can add v.f.o. control or amplitude modulation at any time without modifying the 6DQ5 transmitter. Crystal switching is a convenience for rapidly shifting frequency within a band to dodge QRM, and a SPOT position on the operate switch permits identifying one's frequency relative to others in a band. An accessory socket, X_3 , furnishes a convenient point for borrowing power for a v.f.o. or for controlling the oscillator by an external switch.

Referring to Fig. 6-45, the circuit diagram of the transmitter, the crystal selector switch, S_1 , is used to choose the desired crystal. For crystal-controlled operation crystals would be plugged in pins 1 and 3 and 5 and 7 of socket X_1 . Similar sockets (not shown in the diagram) are used to hold the other crystals. When v.f.o. operation is desired, the v.f.o. output is connected to J_1 , the plug P_1 is inserted in socket X_1 and the former 6AG7 crystal oscillator stage becomes an amplifier or multiplier stage when switch S_1 is turned to position 1.

Since the output of the 6AG7 stage will vary considerably with the bands in use, an excitation control, R_1 , is included to allow for proper adjustment of the drive to the 6DQ5 amplifier. The 6DQ5, a highly sensitive tube, is neutralized to avoid oscillation; the small variable capacitor C_2 and the 390- $\mu\mu$ f. mica capacitor form the neutralizing circuit. Screen or screen and plate modulation power can be introduced at socket X_2 ; for radiotelegraph operation these connections are completed by P_2 . Grid or plate current of the 6DQ5 can be read by proper positioning of S_5 ;

the 0-15 milliansmeter reads 0-15 ma. in the gridcurrent position and 0-300 ma. in the platecurrent position.

The transmitter is keyed at J_3 , and a keyclick filter (100-ohm resistor and C_5) is included to give substantially click-free keying. The v.f.o. jack, J_4 , allows a v.f.o. to be keyed along with the transmitter for full break-in operation.

Construction

A $10 \times 17 \times 3$ -inch aluminum chassis is used as the base of the transmitter, with a standard 83/4-inch aluminum relay rack panel held in place by the bushings of the pilot light, excitation control and other components common to the chassis and panel. The panel was cut down to 17 inches in length so that the unit would take a minimum of room on the operating table. A good idea of the relative location of the parts can be obtained from the photographs. The support for the r.f. portion housing is made by fastening strips of 1-inch aluminum angle stock (Reynolds aluminum, available in many hardware stores) to the panel and to a sheet of aluminum 9½ inches long that is held to the rear chassis apron by screws and the key jack, J_3 . A piece of aluminum angle must also be cut to mount on the chassis and hold the cane-metal (Reynolds aluminum) housing. Fig. 6-47 shows the three clearance holes for the screws that hold this latter angle to the chassis after the cane metal is in place. Build the cane-metal housing as though the holes weren't there and the box has to hold water; this will minimize electrical leakage and the chances for TVI. To insure good electrical contact between panel and angle stock, remove the paint where necessary by heavy applications of varnish remover, with the rest of the panel masked off. The paint will blister and be easy to remove; wash the panel and then drill the holes for the components and screws. (If the holes are drilled first, the remover may leak

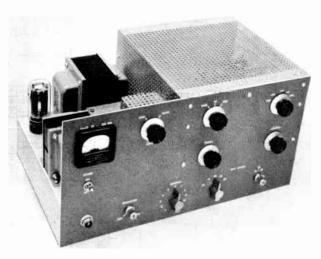


Fig. 6-44—This 75-watt crystal-controlled transmitter has provision for the addition of v.f.o. control. A 6AG7 oscillator drives a 6DQ5 amplifier on 80 through 15 meters.

As a precaution against electrical shock, the meter switch, to the immediate right of the meter, is protected by a cane-metal housing. The switch to the right of the meter switch handles the spot-operate function, and the switch at the far top right is the plate-circuit band switch.

Along the bottom, from left to right: pilot light, excitation control, crystal switch, grid circuit band switch, and grid circuit tuning.



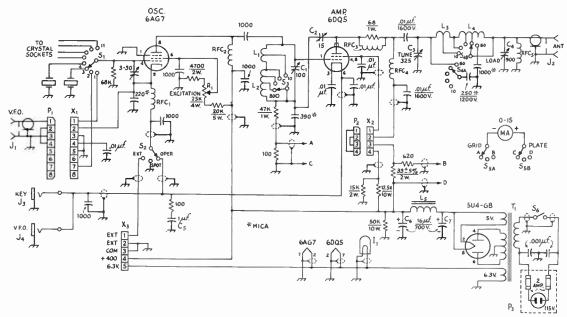


Fig. 6-45—Circuit diagram of the 75-watt 6DQ5 transmitter. Unless specified otherwise, capacitance is in μμf., resistance is in ohms, resistors are ½ watt. C₁—100-μμf. midget variable (Hammarlund HF-100). C₂—15-μμfd. midget variable, .025 inch spacing (Johnson 15J12).

C₃—325-μμf. variable (Hammarlund MC-325-M).
C₄—Dual 450-μμf. broadcast replacement variable, two sections connected in parallel. (Allied Radio 61H059).

C₅-1-\mu f. 400-volt tubular.

 C_{6} , C_{7} —16- μ f. 700-volt electrolytic (Aerovox PRS).

11-6-volt pilot lamp.

J₁--Phono iack.

J₂—Coaxial connector, chassis mounting, type SO-239.
J₃. J₄—Open-circuit phone jack.

L₁-7½ t. No. 18, % inch diam., 8 t.p.i., tapped 5½ turns from grid end (B&W 3006).

L₂-38 t. No. 32, 1 inch diam., 32 t.p.i., tapped 23 and 31 turns up (B&W 3016).

 L_3 -5 turns No. 14, 1-inch diam., 4 t.p.i., self-supporting, tapped $3\,V_2$ turns from plate end.

L₄-15 turns No. 14, 1¾ inch diam., 4 t.p.i., tapped 6¼ and 10¼ from output end (B&W 3021).

L₅-10-henry 200-ma. filter choke (Triad C-16A).

P₁—Octal plug (Amphenol 86-PM8).

P₂-4-pin plug (Amphenol 86-PM4).

P₃-Fused line plug.

R₁—25,000-ohm 4-watt potentiometer (Mallory M25MPK).

RFC1, RFC2 $-750-\mu h$, 100-ma, r.f. choke (National R-33).

RFC₃—3 turns No. 14 around 68-ohm 1-watt composition resistor.

RFC₄-1-mh. r.f. choke, 500 ma. (Johnson 102-752). RFC₈-2.5-mh. r.f. choke (National R-1008).

S₁—1-pole 11-position rotary ceramic switch Centralab Y section on P-121 index assembly).
S₂—Single-pole 11-position (3 used) non-shorting rotary switch (Centralab PA-1001).

S₃—Single-pole 12-position (5 used) rotary ceramic switch (Centralab PA-1 on PA-301 index assembly).

S₄—2-pole 5-position rotary ceramic switch (Centralab 2505).

S₆—2-pole 6-position (3 used) non-shorting ceramic rotary switch (Centralab PA-2003).

S₆-S.p.s.t. toggle.

T₁-800 v.c.t. 200-ma. power transformer (Triad R-121-A).

X1-Octal tube socket.

X2-4-pin tube socket.

X₃-5-pin tube socket.

through and spoil the paint on the front of the panel.)

From a suitable piece of cane metal, make the four-sided $2\frac{1}{4} \times 2\frac{1}{4} \times 2\frac{1}{4}$ -inch box that covers S_5 , and fasten it to the utility-box cover with sheet-metal screws. Don't forget J_1 on the side of the box.

The self-supporting coil, L4, can be wound on the envelope of the 6AG7 and then pulled apart to give the correct winding length.

Installation of the electrical components should present no problems. To insulate it from the chassis, capacitor C_1 is mounted on a small ceramic cone insulator (Johnson 135–500 or National GS-10). The socket for the 6DQ5 is mounted above the chassis on a pair of $\frac{34}{2}$ -inch sleeves, with a large clearance hole under the socket for the several leads running from under the chassis. Cathode and screen bypass capacitors for the 6DQ5 connect to the chassis at soldering lugs under the sleeves.

Taps on L_2 are readily made by first pushing the wire on either side of the desired turn toward the center of the coil.

Note that shielded wire is used for many of the a.c. and d.c. (but not r.f.) power leads; this is done to minimize the chances for stray radiation and it also contributes to the stability of the transmitter.

Adjustment

When the wiring is completed and checked,

disable the amplifier stage by removing P_2 , plug in P_3 and turn on S_5 . The tube heaters and filaments should light up. If a voltmeter is available and connected across C_6 , it should indicate over 500 volts. Later on, with full loading, the plate voltage will run around 400.

With S_1 switched to an 80-meter crystal, S_3 switched to 80 or 40 and S_5 switched to GRID, flip S_2 to spot and tune C_1 through its range. If the crystal is oscillating the meter should give an indication at some setting of C_1 . The grid current reading should vary with the setting of C_1 (maximum at resonance) and with the setting of R_1 (maximum with arm at 20K end). If a key is plugged in at J_3 and S_2 is set to open, the grid current should appear only when the key is closed. Listen to the signal on a receiver (no antenna); if the signal is chirpy try adjusting the 3–30 $\mu\mu$ f. compression trimmer between grid and cathode of the 6 Λ G7.

With a 40-meter crystal switched in, check for grid current at 14 and 21 Mc., by switching S_3 to the desired band and tuning with C_1 . These settings should be checked with an absorption-type waveneter, since it is possible in some cases to find more than one harmonic in the range of C_1 . The 28-Mc. range can also be checked, but the 4th harmonic of the 7-Mc. crystal will yield only about 1 ma. of grid current.

Next check the neutralization on the 15-meter band. With 21-Mc. grid current indicating, switch S_4 to 15, set C_4 at half scale, and swing C_3

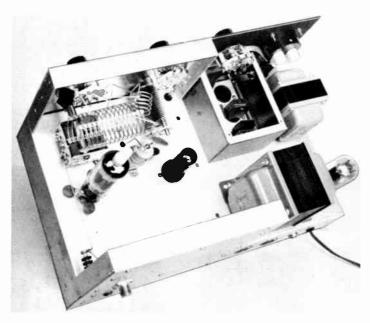


Fig. 6-46—Top view of the 6DQ5 transmitter with cane-metal cover removed. A $3\times4\times5$ -inch utility box (upper right) serves as a shield for the crystals; the cane-metal protection for the meter switch is fastened to the box cover. Phono jack mounted on the meter-side of the box receives v.f.o. output; short length of Twin-Lead from this jack to octal plug brings v.f.o. output to crystal socket. For protection against high voltage, meter terminals are covered by ceramic tube plate caps (Millen 36001).

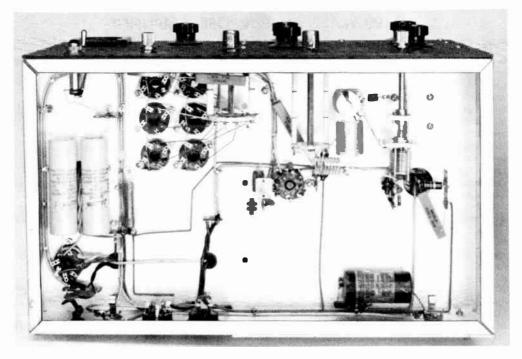


Fig. 6-47—Group of six octal sockets (upper left) serves as crystal sockets. Socket at center of chassis holds 6AG7 oscillator tube; the 3-30- $\mu\mu$ f. mica compression trimmer mounted alongside is excitation control for oscillator stage. Small midget capacitor above coil is neutralizing capacitor adjusted from above chassis; this capacitor and grid tuning capacitor to right must be insulated from chassis.

through its range. Watch closely for a flicker in grid current. If one is observed, try a different setting of C_2 . Work carefully until the flicker is a minimum. A more sensitive indication of neutralization can be obtained by using a germanium diode and a 0-1 milliammeter in the output at J_2 ; adjust C_2 for minimum meter indication. If using this sensitive test, it is wise to start out with R_1 set at half range or less, until it has been determined that the meter will not swing off scale. Under no circumstances use this test with P_2 in place; the 6DQ5 output is quite likely to destroy the crystal diode.

When the amplifier has been neutralized, connect a dummy load (a 60-watt lamp will do) at J_2 and replace P_2 . Set S_5 to plate and send a few dots as C_3 is tuned through its range. At resonance the lamp should light up and the plate current should dip. The plate current can be made to increase, along with the lamp brilliance, by decreasing the capacitance at C_4 . The 6DQ5 plate current can be run up to 180 ma. (9 ma. on the meter) for Novice work; the grid current should be held at 2 to 4 ma. Crystals in the 3.5-to 4.0-Mc. range should be used for 80- and 40-

meter operation, and 7-Mc. crystals should be used on 40, 20 and 15 meters. For 10-meter operation, it is recommended that a v.f.o. with 20-meter output be used to drive the 6AG7; trying to drive the 6DQ5 with the 4th harmonic of a 7-Mc. crystal is too marginal for all but the most experienced operators. With v.f.o. control, always frequency multiply (double or triple) in the 6AG7 stage to the desired band.

Because the 6DQ5 is capable of drawing high values of plate current when not tuned properly, it will pay to take care in learning how to adjust the transmitter. Once the controls have been "calibrated" and the approximate settings for each band become known, it should no longer be necessary to tune up with the "series-of-dots" technique mentioned above. However, in the early stages of familiarization with the transmitter, the dots, or a fast hand on the key, may save a tube or power supply. The fact that the 6DQ5 can draw such heavy currents at low plate voltages makes it an excellent tube for an effective inexpensive transmitter, but the tube is not as tolerant of careless tuning habits as are some other tubes.

A 90-WATT ALL-PURPOSE AMPLIFIER

The amplifier shown in Figs. 6–48 through 6–51 will serve as a Class- AB_1 linear amplifier or as a Class-C power amplifier with no changes other than the proper adjustment of excitation and loading. To accomplish this, a stabilized bias supply provides proper Class- AB_1 bias; the bias increases to the correct value for Class-C operation when the excitation is brought up to the point that yields normal grid current. A stabilized screen supply is included to insure good linear operation.

Referring to the amplifier circuit in Fig. 6-50, excitation on the desired band is introduced at J_1 . The grid circuit is a commercial assembly, Z_1 , that can be switched to the correct band by S_1 and tuned by C_1 . A pi-network coupler is used in the output, switched by S_2 and tuned by C_3 . Proper loading is obtained by adjustment of C_4 ; to provide sufficient output capacitance in the 80-meter band an additional 680 $\mu\mu$ f. is added. A neutralizing circuit, C_2 and a 680- $\mu\mu$ f. capacitor, adds to the fundamental stability at the higher frequencies. Parasitic suppressors were found to be necessary in the grid and plate circuits.

Overload protection is provided by a 250-ma. fuse in the cathode circuit. The grid, plate or screen current can be metered by a suitable setting of S_3 ; with the resistances shown the meter provides a full-scale reading 5 ma. on grid current, 25 ma. on screen current, and 250 ma. on plate current.

If it is desired to plate- or screen-modulate the amplifier for a.m. operation, the necessary audio power can be introduced at J_3 .





Fig. 6-48—Front view of the 6146 all-purpose amplifier. The upper panel is part of an $8\times6\times31/2$ -inch Minibox (Bud CU-2109); the ventilated shielding of Reynalds Aluminium cane metal is fastened to the Minibox and base with sheet-metal screws.

Plate-circuit tuning controls and switch are mounted on the Minibox, and the grid-circuit controls, power switches and meter are mounted on the end of the 8 \times 12 \times 3-inch aluminum chassis that serves as a base.

The power-supply circuit is shown separately (Fig. 6-52) for convenience only, since the amplifier and power supply are all built on the same

 $8 \times 12 \times 3$ -inch chassis. High voltage for the plate of the 6146 is provided by a bridge rectifier using a 5U4-GB and two 6DE4 rectifiers; stabilized screen voltage is obtained from the same supply and two voltage-regulator tubes.

Fig. 6-49—Rear view of the 90-watt ollpurpose amplifier with the cone-metal cover removed. One voltage-regulator tube has been removed from its socket (right edge of tronsformer) to allow the neutralizing capacitor and plate blocking capacitor to be seen. The plate r.f. choke (RFC₃ in Fig. 6-50) is mounted on one side wall, and the load capacitor and safety choke (C₄ and RFC₄ in Fig. 6-50) are mounted on the far side wall.

The reor apron of the chassis (fore-ground) corries the input ond output coaxiol-connector jacks, the 6146 cathode fuse, and the socket for the a.m. modulator connections. A shorting plug is shown in the socket.

Most

and components Construction

collars few can

construction

RG-58/U 6146 100 Zį 7250 July GRID 15 1W. 680µµt X20 X, o 20 1 5% 53 200 0-5 MA -^^^-Y₂ +700

Fig. 6-50—Circuit diagram of the all-purpose amplifier and its bias supply. Unless otherwise indicated, resistors are ½ watt.

C₁-140-\(\mu\mu\mi\), midget variable (Hammarlund APC-140-B).

 C_{2} --10- $\mu\mu$ f, midget variable (Hammarlund HF-15X with one stator plate removed).

C₈-250-µµf. variable (Hammarlund MC-250M).

C4-730-µµf, variable (Broadcast receiver replacement, 365) $\mu\mu$ f, each section, connected in parallel).

CR₁—20-ma, 130-volt selenium rectifier.

J₁, J₂—Coaxial cable connector, SO-239.

J₃-4-pin tube socket.

L₁-3³/₄ turns No. 18 at grid end of L₂, tapped 2 turns from ground end.

L_s-50 turns No. 24, 1% inches long on %-inch diameter threaded ceramic form, Tapped at 5, 8, 13 and 25 turns from arid end.

L₈-4½ turns No. 14, 1¾6 diam., % inch long.

L-18 turns No. 16, 2-inch diameter, 10 t.p.i. Tapped at 11/8, 51/s and 111/s turns from plate end. (B&W 3907-1).

P₁-4-prong plug, with jumper connections as shown.

RFC₁-2.5-mh. 100-ma. r.f. choke (National R-50).

RFC₂-5 turns No. 16 wire, wound on 100-ohm 1-watt resistor. RFC₃-1-mh. 500-ma. r.f. choke (Johnson 102-752).

RFC4-2.5-mh. 125-ma. r.f. choke (National R-100S).

S₁-2-pole 6-position (5 used) miniature ceramic switch (Centralab PA-2002).

S₂—1-pole 6-position (5 used) ceramic switch (Centralab 2501). S₂-2-pole 6-position (5 used) non-shorting miniature ceramic switch. (Centralab PA-2003). Alternate contacts used only, to increase voltage rating.

S₄—S.p.s.t. toggle switch.

T₁-6.3-volt filament transformer (Stancor P-6134).

Z₁, comprising C₁, L₂ and S₁, is Harrington Electronics GP-20L unit. Capacitors showing polarity are electrolytic; 680-44f. capacitors are silver mica, .001-4f, are ceramic.

Connection from the chassis washers controls Ç LOIOL by mounting soldering made

terminal connected between through place and at the

mounting screws

ceramic capacitors

well-insulated

feed-through

 RFC_3

ground to

screen and heater

grounded side of the grid-circuit

neutralizing

capacitor,

C2,

inside of the cable and not the outside the available compartment via

hardware stores, and it is an easy matter to bend a piece of it to form the cover. Make the cover with lips on the vertical portion that slip tightly over the sides of the Minibox, and with a bend at the bottom that can be fastened to the chassis. Another piece of cane metal should be cut to serve as a bottom cover; mounting the chassis on rubber feet lifts it above the table and permits good air circulation through the unit.

The self-supported inductor L_3 can be wound on the envelope of one of the 6DE4 rectifiers, removed and pulled apart slightly to give the specified winding length. The taps on L_4 are made by first bending inward the wire on either side of the turn to be tapped, then looping the tap wire around the turn and soldering it securely in place. Both L_3 and L_4 are supported only by their leads.

Testing and Adjustment

With all tubes in their sockets except the 6146, the line cord should be plugged in and the power switch turned on. The bias-supply 0A3 should glow immediately and the rectifier filament and

heaters should light up. The screen-supply regulators should glow. If a voltmeter is available, the high-voltage supply should show first around 400 volts, and then rise slowly to about 950 volts. Switch off the power; the plate supply voltage should decay to less than 100 in under 20 seconds, indicating that the 40,000-ohm resistors are "bleeding" the supply. Note also how long it takes for the voltage to reach a value of only a few volts: this will demonstrate forcefully how long it takes to discharge a high-capacitance filter.

When the power supply has discharged, plug in the 6146, connect the plate cap, and set S_4 to STAND BY. Set the neutralizing capacitor C_2 at half capacitance and the band switches on 80 meters. Turn on the power and set the meter switch, S_3 , to read plate current. The 6146 heater should warm up. Now flip S_4 to operate; the meter should read 10–20 ma. (.2–4 on the scale). Switching to read screen current, the meter should show under 1 ma. (2 divisions on the meter). There should be no grid current.

Turn off the power and remove the three

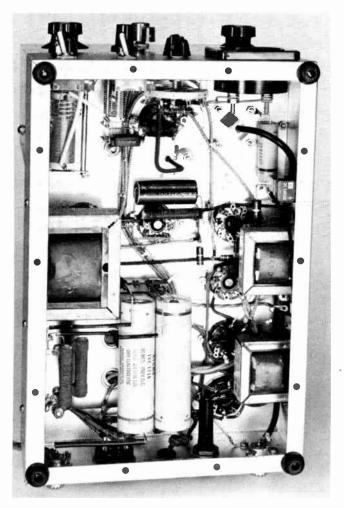


Fig. 6-51—Battam view af the all-purpose amplifier. The 150-ma, filter chake is maunted on the left-hand wall; the smaller filter chake, the small filament transfarmer (Ta in Fig. 6-50) and the selenium rectifier are maunted an the righthand wall. The strap of aluminum, visible below the meter at the tap right, pravides additional support for the length of RG-58/U cable that runs to the output coaxial cannectar. All power leads except the high voltage to the plate are run in shielded wire.

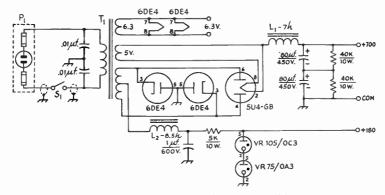


Fig. 6-52—Power supply section of the all-purpose amplifier.

L₁—7-henry 150-ma. choke (Stancor C-1710).

 L_2 -8½-henry 50-ma. choke (Stancor C-1279).

P₁-Fused line plug, 3-ampere fuses.

S₁-S.p.s.t. toggle.

T₁-800 v.c.t. at 200 ma., 6.3 v. at 5 amp., 5 v. at 3 amp. (Allied Radio Knight 62 G 033).

rectifier tubes. Connect at J_1 the driver or excitation source to be used - less than a watt is required for linear operation, and only a shade more for Class C. Use the drive at a high frequency, such as 21 or 28 Mc. Turn on the amplifier and switch the band switches to the band corresponding to the excitation-source frequency. Adjust the grid tuning capacitor for a show of grid current; peak the tuning and (if necessary) adjust the excitation for a half-scale reading of grid current. With the loading capacitor C_4 set at half scale, swing the tuning capacitor C3 through its range. Watch carefully for a slight flicker in grid current. If one is found, adjust the neutralizing capacitor C_2 until the flicker is minimized. The amplifier is now neutralized. Alternatively, a sensitive detector of r.f. can be coupled at the output connector, J_2 , and used instead of the grid-current flicker. Adjust C2 for minimum r.f. in the output when the plate circuit is tuned through resonance. Turn off the power switch and disconnect the excitation source.

Remove the sensitive detector, if used, and replace the rectifier tubes. Turn on the power and switch the meter to read plate current. With the grid and plate circuits switched to the same band (10, 15, 20 or 40) it should be possible to swing the grid and plate tuning to any combination of settings with no change in plate current reading. This indicates that the amplifier is stable and free from oscillation. (The amplifier can be made to oscillate on 80 meters with no grid or plate loading, but in loaded operation it will be stable.)

The antenna and excitation can now be connected and the amplifier used in normal fashion. Used as a linear amplifier, the excitation should be adjusted just below the level that would kick the grid-current indication on signal peaks. Proper loading will be obtained when a steady carrier just under the grid-current level is used for drive and the loading at resonance is set for

about 100 ma. plate current. Under these conditions of loading, a sideband signal will kick the plate current to about 40 or 50 ma. on peaks. Measured p.e.p. input before clipping should be 60 to 70 watts.

When used as a Class-C amplifier, the drive should be increased to where about 2 to 3 ma. grid current is drawn, and the loading to where the 6146 draws about 125 ma. If the amplifier is plate modulated, the plate current should be reduced to 95 ma., to stay within the tube ratings.

Since the amplifier uses a fixed and "stiff" screen supply, it is good practice always to bring up the excitation and loading together, while checking to see that the screen current never exceeds about 15 ma. In normal Class-C operation the screen current will run around 10 ma.

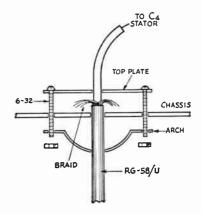


Fig. 6-53—Exploded view of the cable clamp used to hold the coaxial cable running to J_2 . The top plate is a $1\frac{1}{2}$ -inch square of sheet aluminum with holes at the four corners for 6-32 screws. The arch is a $\frac{1}{16}$ -inch wire strap that mounts diagonally under the chassis. When tightened, the top plate clamps the cable braid to the chassis; the arch lends support to the cable.

A SELF-CONTAINED 500-WATT TRANSMITTER

Figs. 6-54 through 6-59 show the details of a 500-watt c.w. transmitter, completely self-contained except for the external remote v.f.o. tuning box shown in Figs. 6-58 and 6-59. Provision is made for introducing s.s.b. input at the grid of the driver stage. While plate modulation can be applied to the final amplifier in the usual manner, ratings of the plate power supply limit the safe input to about 250 watts.

The circuit is shown in Fig. 6-57. Switch S_2 permits either v.f.o. or crystal-controlled operation using a 6AH6 oscillator. Either 80- or 40-meter crystals may be used. The v.f.o. circuit is in the 80-meter band and S_1 selects either of two frequency ranges — 3.5 to 4 Mc. for complete coverage of all bands, and 3.5 to 3.6 Mc. for greater bandspread over the low-frequency ends of the wider bands. The plate circuit of the oscillator is on 40 meters for all output bands except 80 meters where it is non-resonant.

A 6CL6 buffer separates the oscillator and the first keyed stage. This stage doubles to 20 meters for 20- and 10-meter output and triples to 15 meters. The driver is a 2E26 which doubles to 10 meters and works straight through on all other bands. This stage is neutralized and a potentiometer in its screen circuit serves as an excitation control.

The final is a 7094, also neutralized, with a pi-network output circuit using a B&W 851 band-switching inductor unit.

A differential break-in keying system using a 12AU7 is included. Both the final amplifier and driver are keyed by the grid-block method. The differential is adjusted by R_1 . Clicks are prevented by envelope-shaping circuits which include C_7 , C_{11} and the grid-leak resistances.

The 100-ohm meter shunts give a full-scale reading of 50 ma., the 51-ohm shunts a full-scale reading of 100 ma., and the 10-ohm resistor in the negative high-voltage lead provides a 500-ma. scale.

Power Supply

The plate transformer in the high-voltage supply uses a transformer designed for a con-

ventional full-wave rectifier circuit with an ICAS d.c. output rating of 300 ma. at 750 volts. A bridge rectifier is used with this transformer so that an output voltage of 1500 is obtained. The short duty cycle of c.w. or s.s.b. operation makes it possible to draw up to the rated maximum of the 7094 (330 ma.) through a choke-input filter without a prohibitive rise in transformer temperature.

The low-voltage supply has two rectifiers. A full-wave rectifier with a capacitive-input filter provides 400 volts for the plate of the driver and the screen of the final amplifier. A tap on a voltage divider across 400 volts provides 300 volts for the plates of the oscillator, buffer and keyer tubes. A half-wave rectifier with a choke-input filter supplies 250 volts of bias for the keyer and fixed bias for the 2E26 and 7094 when they are operating as Class AB₁ linear amplifiers.

Control Circuits

 S_7 is the main power switch. It turns on the low-voltage, filament and bias supplies. Until it has been closed, the high-voltage supply cannot be turned on. In addition to turning on the high-voltage supply, S_8 operates the relay K_1 which applies screen voltage to the final amplifier. Thus, to protect the screen, screen voltage cannot be applied without applying plate voltage simultaneously. J_8 is in parallel with S_8 so that the high-voltage supply can be controlled remotely from an external switch. Also, in parallel with the primary of the high-voltage transformer is another jack, J_7 , which permits control of an antenna relay or other device by S_8 if desired.

The v.f.o.-set switch S_5 turns on the exciter and grounds the screen of the final amplifier.

 S_2 has three positions. One is for crystal control, the second for v.f.o. operation, and the third position is for operating the last two stages of the transmitter as linear amplifiers with an external s.s.b. exciter. In addition to shifting the input of the driver stage from the buffer amplifier to an s.s.b. input connector, fixed bias is provided for AB_1 operation of both stages.

Construction

The transmitter is assembled on a 17 imes 13 imes

Fig. 6-54—A 500-wott transmitter. Power supplies and a differential keyer are included. It aperates with the external v.f.o. tuner shown in Fig. 6-59. Cantrols along the battam, from left to right, are for law-voltage pawer, v.f.a./crystals/s.s.b. switch, driver tank switch, driver tank capacitor, final loading, v.f.o. set switch, and high-voltage. Above, from left to right, are controls for excitation, finol tank switch, final tank capacitor and meter switch. The band-switch pointer is made by cutting down the metal skirt of a dial similar to the one to the right.



World Radio History

Fig. 6-55—The only shielding required on top of the chassis is the amplifier enclosure shown. A perforated cover for the enclosure is not shown.

4-inch aluminum chassis with a 19 X 12½-inch panel. The amplifier enclosure measures 8½ inches wide, 8½ inches deep and 7½ inches high. The three permanent sides shown in Fig. 6-55 can be bent up from a single sheet of solid aluminum stock. The top and back (not shown) are made from a sin-

gle piece of Reynolds perforated sheet aluminum. The tube socket is mounted on $\frac{3}{4}$ -inch ceramic cones over a large hole cut in the chassis and covered with a patch of perforated sheet. The tank capacitor C_{15} is mounted on metal spacers to bring its shaft level up to that of the switch on the B&W inductor which is mounted directly on the chassis. The two shafts are spaced 4 inches.

Exciter

A 4 \times 5 \times 6-inch aluminum box is used as the foundation for the exciter. The driver tank capacitor is centered on the chassis with its center approximately 3 inches back from the front edge of the chassis. The capacitor specified has an insulated mounting. If an uninsulated capacitor is substituted, an insulating mounting must be provided. The shafts of S_2 and S_3 are spaced $2\frac{1}{2}$ inches and centered on the front end of the box. On the side of the box toward the tuning capacitor, the oscillator tube, the buffer tube, the low-frequency section (L_6) of the driver tank coil, and the 2E26 are lined up so as to clear the tank capacitor and its shaft. The

latter is fitted with an insulated coupling and a panel-bearing unit. The slug-tuned coils are mounted in holes near the bottom edge of the box. Neutralizing capacitor C_8 is mounted at the rear end of the box, close to the 2E26 socket. The high-frequency section (L_5) of the tank coil is suspended be-

Fig. 6-56—The exciter is assembled using a standard aluminum box as the foundation. The perforated cover has been removed. The bottom of the chassis should also have a perforated metal cover.




tween the outer end of the low-frequency section and the plate cap of the 2E26. Coil-tap leads run through small feed-through points or grommeted clearance holes in the side of the box.

The loading capacitor C_{16} is placed so that its shaft is symmetrical with the shaft of S_3 , and S_5 is spaced from it to balance S_2 at the other end.

The V.F.O. Tuner

The v.f.o. tuner is assembled in a 5 \times 6 \times 9-inch aluminum box (Premier AC-596). The dual tuning capacitor C_2 has 7 plates, 4 rotor and 3 stationary, in each section. In the front section, which is used to cover the entire 80-meter band, the two rotor plates nearest the front should be removed. This leaves two rotor plates and two active stator plates, the front stator plate being inactive. In the rear section, the front rotor plate and the last two rotor plates are removed. This leaves one rotor plate riding between two stators.

The capacitor is mounted on a bracket fastened against the bottom of the box, although it could be mounted from the front cover with spacers to clear the hub of the Millen 10035 dial. The shaft of the capacitor should be central on

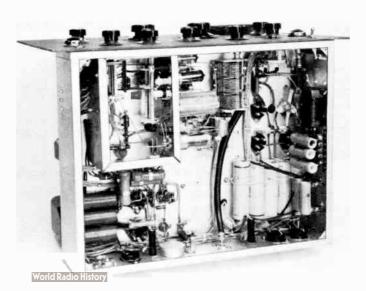

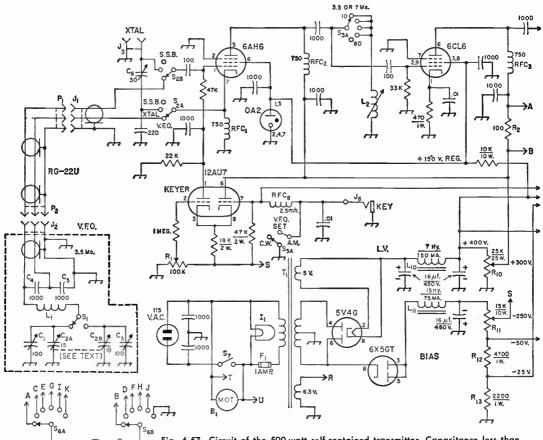


Fig. 6-57—Circuit of the 500-watt self-contained transmitter. Capacitance less than 0.001 μ f. are in $\mu\mu$ f. Fixed capacitors of capacitance greater than 100 $\mu\mu$ f. should be disk ceramic, except as noted below. Fixed capacitors of 100 $\mu\mu$ f. and 220 μμf. should be mica. Capacitors marked with polarity are electrolytic. Resistors not otherwise marked are $\frac{1}{2}$ watt. R.f. chokes in μ h. unless otherwise marked.

B₁-Blower (Allied 72P715).

 C_1 , C_3 -100- $\mu\mu$ f. air trimmer (Hammarlund APC-100-

C₂-Midget dual variable, 25 μμf. per section (Johnson 167-51 altered as described in the text). C_4 , C_5 -0.001- μ f. silver mica.

C₆-30-\(mu\)f. mica trimmer (National M-30).

C₇, C₁₁-0.1-\mu f. paper (keyer shaping).

 $C_8-30-\mu\mu f$, miniature variable (Johnson 160-130).

 $C_0-100-\mu\mu f$. midget variable (Johnson 167-11).

 C_{10} -330- $\mu\mu$ f. mica.

 C_{12} -10- $\mu\mu$ f. neutralizing capacitor (Johnson 159-125).

C₁₃-0.001-\mu f. 3000-volt disk ceramic.

C14-0.001-\(mu f.\) 5000-volt ceramic (CRL 858S).

 C_{15} -250- $\mu\mu f$. 2000-volt variable (Johnson 154-1).

 C_{16} —Triple-gang broadcast variable, 365 $\mu\mu$ f. or more per section, sections connected in parallel.

l₁, l₂-One-inch 115-volt panel lamp.

J₁, J₂-Cable connector for RG-22/U (Amphenol 83-22R, UG-103/U).

J₃-Crystal socket (Millen 33102).

J₄, J₅-Coaxial receptacle (\$O-239).

J₆—Key jack, open circuit.

J₇, J₈—Chassis-mounting a.c. receptacle (Amphenol 61-F).

K₁-S.p.s.t. 115-volt a.c. relay (Advance GHA/1C/ 115VA or similar).

 L_1 =35 μ h.=32 turns No. 18, 2 inches diameter, 2 inches long (Airdux 1616).

L₂-Approx. 10 μh.-65 turns No. 26 enam., on 3/8inch iron-slug form (Waters CSA-1011-3).

L₃-Approx. 2 μh.-16 turns No. 26 enam., closewound at center of form similar to L_2 .


L-Approx. 1 μ h.-13 turns No. 26 enam., $\frac{1}{2}$ inch long at center of form similar to L_2 .

L₅-16 turns No. 20, 3/4 inch diameter, 1 inch long, tapped at 10 turns and 13 turns from L_6 end (Airdux 616).

L₆-40 turns No. 16, 11/4 inches diameter, 23/4 inches long, tapped at mid point and at Ls end (Airdux 1016).

L₁-3 turns No. 14, 1/2 inch diameter, 3/4 inch long. L_8-4 turns $\frac{1}{6}$ \times $\frac{1}{6}$ -inch copper strip, $1\frac{1}{8}$ inches diameter, 21/2 inches long (part of B&W 851 coil unit).

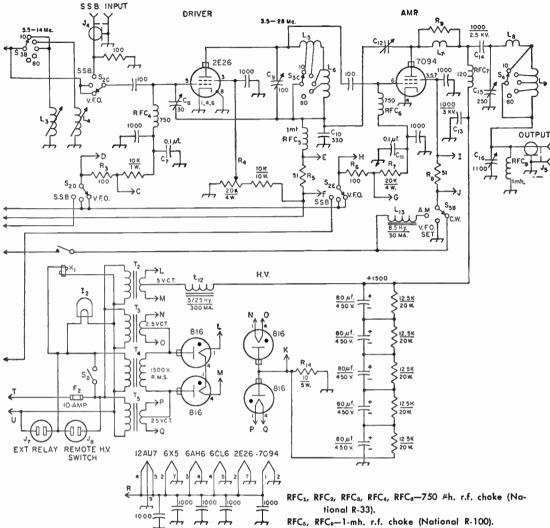L₉-43/4 turns No. 8, 21/2 inches diameter, 13/4 inches long, tapped at 13/4 turns from Ls end, plus $9\frac{1}{2}$ turns No. 12, $2\frac{1}{2}$ inches diameter, $1\frac{1}{2}$ inches long, tapped at 6 turns from output end (part of B&W 851 coil unit).



L₁₀-7-hy. 150-ma. filter choke (Stancor C-1710). L₁₁-15-hy. 75-ma. filter choke (Stancor C-1002). $L_{12}-5/25$ -hy. 300-ma. swinging filter choke (Triad C-33A).

M1-Shielded 0- 5-ma. d.c. milliammeter, 31/2-inch rectangular (Phaostron).

P₁, P₂-Plug for RG-22/U cable (Amphenol 83-22SP). R₁-100,000-ohm potentiometer.

 R_2 , R_3 , R_6 —100 ohms, 5%.

R_s-20,000-ohm 4-watt potentiometer (Mallory M20-MPK).

Rs, R8-51 ohms, 1 watt, 5%.

R₇-Two 10,000-ohm 2-watt resistors in series.

R₀-Three 100-ohm 1-watt noninductive resistors in parallel.

R₁₀-25,000 ohms, 25 watts with slider.

R₁₁-15,000 ohms, 20 watts, with slider.

R₁₂-4700 ohms, 1 watt.

 R_{13} -2200 ohms, 1 watt.

R₁₄-10 ohms (Five 51-ohm 1-watt 5% resistors in parallel).

R₁₆-1000 ohms, 1/2 watt 5%.

RFC₇-120 μ h. r.f. choke (Raypar RL-101).

RFC₈-2.5-mh. r.f. choke (National R-100).

S₁-Single-pole ceramic rotary switch (Centralab 2000, 2 of 12 positions used).

S₂-Two-wafer ceramic rotary switch (Centralab PA-300 index, PA-4 wafers. S2A and S2B are on one wafer, S_{2C} , S_{2D} nd S_{2E} on second wafer).

S₈-Three-wafer ceramic rotary switch (Centralab PA-301 index, wafers PA-0, 5 positions used). S4-Part of B&W 851 coil unit.

S₈-2-pole 3-position ceramic rotary switch (Centralab

2003, two positions used). Se-Double-pole ceramic rotary switch (Centralab 2003).

S7, S8-S.p.s.t. toggle switch.

T₁—Power transformer: 750 v.a.c., c.t., 150 ma.; 5 volts 3 amps.; 6.3 volts, 4.7 amps. (Thordarson 22R06).

T₂, T₈—Filament transformer: 2:5 volts, c.t., 3 amps. (Triad F-1X).

T₄-Plate transformer: 1780 volts, c.t., 310 ma., center tap not used (Triad P-14A).

T₅-Filament transformer: 5 volts, c.t., 3 amps. (Triad F-7X).

HIGH-FREQUENCY TRANSMITTERS

the front cover. The coil is suspended between a pair of $2\frac{1}{2}$ -inch ceramic pillars (Millen 31002). It is placed immediately to the rear of the tuning capacitor. The two air trimmers, C_1 and C_3 , are mounted on the top side of the box with their shafts protruding so that they can be adjusted from the top. The bandspread switch is mounted in one end of the box and the cable connector at the other end.

The unit is housed in a standard cabinet (Bud C-1781) having an 8 × 10-inch panel. The dial should be fastened to the panel, making sure that the hub of the dial lines up accurately with the shaft of the tuning capacitor. Then the box is inserted in the cabinet through the front opening. The switch shaft goes out through a hole drilled in the side of the cabinet, and the cable



Fig. 6-58—The remote v.f.o. tuning unit is housed in a stondord metal cobinet. The cable at the right plugs into the main chassis.

goes through a hole in the opposite end to the cable connector. The dial should be set to read zero at maximum capacitance of the tuning capacitor. The box should be supported on spacers.

Adjustment

With all tubes except the rectifiers out of their sockets, the power supplies should be checked first to be sure that they are functioning properly. The voltage output of the low-voltage supply should be in excess of 400 volts, the biasing voltage 300 or more and the high voltage above 1500. The slider on the low-voltage bleeder should be set at approximately three quarters of the way from ground. The slider on the bias-supply bleeder should be set for a reading of -250 volts to ground.

Plug in the oscillator and buffer tubes and an 80-meter crystal if one is available; otherwise connect the v.f.o. tuner. With the low-voltage supply turned on, the 0A2 should glow. When the key is closed, the 0A2 should dim but stay ignited. If it does not, the value of the 10K VR resistor should be reduced.

The v.f.o. can now be adjusted to frequency. Set C_2 at maximum capacitance. Set S_1 to the 80-meter position. Adjust the 80-meter trimmer until a signal is heard at 3500 kc. on a calibrated

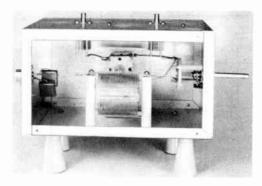


Fig. 6-59—Interior of the v.f.o. tuning box showing the mounting of the coil and other components.

receiver. Then set the receiver to 4000 kc. and tune the v.f.o. until the signal is heard. If the signal is not close to 100 on the dial, carefully bend the rear rotor plate of the 80-meter section of \mathcal{C}_2 outward a little at a time to get the desired bandspread. Each time this adjustment is made, the trimmer should be reset to bring 3500 kc. at zero on the dial.

The same procedure should be followed in adjusting for the other v.f.o. range, aiming for 3600 kc. (or above if desired) at 100 on the dial.

The 2E26 should now be plugged in and the excitation control R_4 set at the ground end (zero screen voltage). S_2 should be set in the v.f.o. position. With low voltage on and the key closed, a 2E26 grid-current reading should be obtained with the band switch in the 80-meter position. With the switch in the 40-meter position, the slug of L_2 should be adjusted for maximum grid current to the 2E26. With the band switch in the 20-meter position, L_3 should be adjusted for maximum grid current, and then the slug of L_4 should be adjusted for maximum grid current with the band switch in the 15-meter position.

Now insert the 7094 in its socket and neutralize the 2E26 as described earlier in this chapter.

Testing of the final amplifier requires a load applied to the output connector. Two 150-watt lamps connected in parallel should serve the purpose. Turning on the high voltage will also apply screen voltage through the relay K_1 . With both band switches set to 10 meters, and C_{16} set at about half capacitance, quickly tune the output circuit to resonance as indicated by the plate-current dip. The load lamp should show an indication of output. Switch the meter to read grid current and neutralize as described earlier in this chapter. After neutralization the amplifier can be loaded to rated plate current. If it is above the rated maximum value, increase C_{16} and retune to resonance, or decrease C_{16} if the plate current is below the rated value.

With the final adjusted and the entire transmitter operating, make a final check on the voltage at the tap on the low-voltage supply, adjusting the slider if necessary to bring the voltage to 300 with the key closed. Be sure to turn off all voltages each time an adjustment is made.

The last adjustment is in the keyer. Adjust the potentiometer R_1 to the point where the oscil-

lator cannot be heard between dots and dashes at normal keying speed.

AN ALL-PURPOSE 813 AMPLIFIER

Figs. 6-60 through 6-63 show the circuit and photographs of an 813 amplifier designed for c.w., a.m., or s.s.b. operation. Provision has been made for convenient changing from one mode to another as well as to any of the bands from 80 through 10 meters.

The circuit is shown in 6-61. A turret-type grid circuit is used and the output circuit is a pi network designed to work into coax cable. The inductor is the rotary-type variable. Provision for neutralizing is included. R_1 is a parasitic

suppressor.

For Class-C c.w. or phone operation, S_4 is open. The 90 volts of fixed bias, furnished by a small bias supply and regulated by the VR90, is augmented by a drop of about 50 volts across the grid-leak resistor R_2 at a normal grid current of 15 ma. This brings the total bias to 140 volts. With S_4 closed, the grid leak is short-circuited and the 90 volts of fixed bias alone remains for AB₂ s.s.b. operation. (An advantage in AB₂ for c.w. operation is that it preserves the keying characteristics of the exciter better than with Class-C operation.) R_3 should be adjusted so that the VR90 just ignites with no excitation.

Screen voltage is regulated at 750 volts by a string of five 0A2s for s.s.b. operation. When the grid drive is increased for Class-C operation, the screen current increases, increasing the drop across the screen resistor R_5 , and the screen voltage falls to 400. The regulators then lose control and the amplifier is ready for plate-screen modulation.

The screen is protected against excessive input, should the load or plate voltage be removed, by the overload relay K_1 . The tripping point is set at 40 ma. by the variable shunt resistor R_4 . If the relay trips, current through R_6 will hold the screen circuit open until plate voltage is removed. One meter, M_1 , measures cathode cur-

rent, while the other meter, M_2 , may be switched to read either grid current or screen current.

Forced-air ventilation is always advisable for a medium- or high-power amplifier if it is buttoned up tight to suppress TVI. A surplus 100 c.f.m. blower does the job more than adequately.

Construction


The amplifier is built on a $13 \times 17 \times 4$ -inch aluminum chassis fastened to a standard 1234×19 -inch rack panel. The r.f. output portion is enclosed in a $12\frac{1}{2} \times 13 \times 8\frac{1}{2}$ -inch box made of aluminum angle and sheet. The VR tubes, relay, blower and meters are mounted external to the

The grid tank-circuit components are mounted underneath the chassis and are shielded with a $5 \times 7 \times 3$ -inch aluminum box. A standard chassis of these dimensions might be substituted. The bias and filament transformers are in a second box measuring 6 by 3 by 3 inches. This type of construction, together with the use of shielded wire for all power circuits, was followed to reduce TVI to a minimum. Each wire was bypassed at both ends with 0.001-\mu f. ceramic disk capacitors. L_4 can be adjusted to series resonate with the $600-\mu\mu f$, capacitor at the frequency of the most troublesome channel. A Bud low-pass filter completes the TVI treatment. As a result, the amplifier is completely free of TVI on all channels even in most fringe areas.

Adjustment

In the pi network, the output capacitors are fixed. However, the adjustment of the network is similar to that of the more conventional arrangement using a variable portion of the output capacitance. The only difference is that the "fine" loading adjustment is done with the variable inductor.

Fig. 6-60-W4SUD's all-purpose 813 amplifier. The output-capacitor switch (coarse loading) is above the turns counter for the variable inductor. Dials near the center are for the plate tank capacitor C4 (above) and the grid tank capacitor C1 (below). To the right of the dials are the controls for the plate padder switch S₃ (above) and the grid band switch S₁ (below). The toggle switch below the meters is the mode switch S₄ with the meter switch S₅ to the left. Ventilating hales are drilled in the cover in the area above the tube. The output connector is on the left-hand wall of the shielding box.

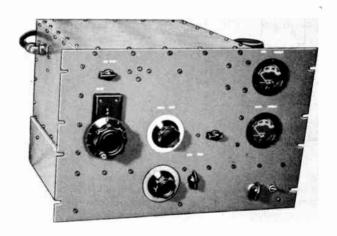

3.5-28 Mc R.F. OUTPUT 813 SIB O 0 INPUT O 514 o FILTER OA2 OA2 \mathcal{A} 馮 MA) 10-500 OAS Tiooo 0-50 ma. 40,uf. 115 V.A.C. 115 V. A.C. +2000~2500V

R. F. AMPLIFIER

B₁-Ventilating blower, 100 c.f.m. (surplus).

C₁-250-\(\mu\mu\mathre{\psi}\), variable (Hammarlund MC-250-M).

 $C_2 = 1000 - \mu \mu f$. mica.

Capacitors marked

 C_3 -Neutralizing capacitor, 10 $\mu\mu$ f, maximum (Johnson 159-250).

 $C_4 = 150 - \mu \mu f$, 6000-volt variable (Johnson 153-12).

 $C_5 = 100 - \mu \mu f$, 5000-volt fixed capacitor (surplus vacuum Amperex VC-100, or two 200-μμf. 5000volt micas in series).

CR₁-130-volt 50-ma. selenium rectifier.

J₁, J₂—Coaxial receptacle (SO-239).

K₁-Screen overload relay, 2500 ohms, 7 ma. (Potter & Brumfield KCP5).

L₁-3.5 Mc.-32 turns No. 20, 1-inch diam., 2 inches long, 5-turn link (B&W 3015 or Airdux 816).

-7 Mc.-18 turns No. 20, 3/4-inch diam., 11/8 inches long, 3-turn link (B&W 3011 or Airdux 616).

-14 Mc.-10 turns No. 18, 5%-inch diam., 11/4

inches long, 2-turn link (B&W 3006 or Airdux 508).

-21 Mc.-7 turns No. 18, %-inch diam., % inch long, 1-turn link (B&W 3006 or Airdux 508).

-28 Mc.-5 turns No. 18, %-inch diam., % inch long, 1-turn link (B&W 3006 or Airdux 508).

L₂-3 turns $\frac{3}{16}$ -inch copper tubing, 1-inch diam., 1 $\frac{3}{16}$ inches long.

L₁-15-µh, variable inductor (B&W 3852).

L-See text.

M1, M2-31/2-inch d.c. milliammeter.

R₁-39 ohms, ½-watt carbon.

R₂-3300 ohms, 2 watts.

R_a-15,000 ohms, 10 watts with slider.

R₄-2000-ohm 4-watt voriable resistor (Mallory M2-MPK).

RFC₁ RFC₃-2.5-mh, r.f. choke (National R-50 or similar). World Radio History

RFC2-Plate r.f. choke (National R-175-A).

RFC4-V.h.f. choke (National R-60).

S₁-Rotary switch: 3 wafers, 3 poles, 11 positions per pole, 5 positions used (Centralab PA-0 wafers, PA-301 index).

S2-Rotary switch: single pole, 10 positions, progressively shorting, 6 positions used (Centralab PA-2042).

S₃-Rotary switch: s.p.s.t., ceramic (antenna link switch from BC-375 tuning unit, or Communications Products Model 65).

S₄-S.p.s.t. toggle switch.


S₅-D.p.d.t. rotary switch (Centralab 1405).

T₁-Filament transformer: 10 volts, 5 amp, (Thordarson 21F18).

T₂-Bigs transformer: 120 volts, 50 ma.; 6.3 volts, 2 amp., filament winding not used; could be used for pilot light (Merit P-3045).

813 Amplifier

Fig. 6-62-This view shows the placement of components on the chassis. The 813 socket is mounted on spacers over a large clearance hole in the chassis. The several mica output capacitors are assembled in a stack on a threaded rod fastened to the left-hand wall of the shielding box. The neutralizing capacitor and the 80meter plate padder are to the right of the tank capacitor. To the right of the box are the five OA2s (the front one hidden), the screen overload relay and the VR90, the blower and meters.

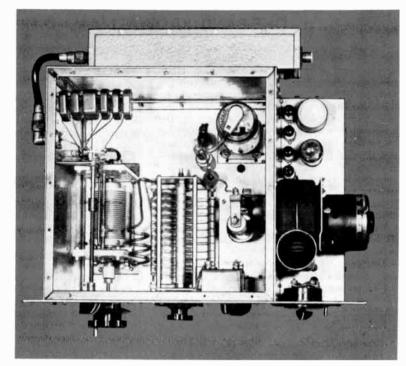


The inductor is fitted with a Groth turns counter, making it easy to return to the proper setting for each band. Until the settings for each band have been found, S_3 should be turned so that all of the output capacitance is in circuit. The inductor should be set near maximum for 80, and approximately half maximum for 40. On the higher-frequency bands, the inductor should be set so that the circuit resonates with the tank capacitor near minimum capacitance. Loading

should increase as the output capacitance is decreased. A change in output capacitance requires a readjustment of \mathcal{C}_4 for resonance. When the loading is near the desired point, final adjustment can be made by altering the inductance slightly.

A 20-A or similar exciter is well suited as a driver for this amplifier on all modes. The 813 runs cool at 500 watts input on c.w. and at a little over 500 watts p.e.p. on s.s.b. (Originally described in *QST* for August, 1958.)

Fig. 6-63-Bottom view of the all-purpose 813 amplifier. The grid tank-circuit components within dashed lines in Fig. 6-62 are enclosed in the box at lower center. Input links are wound over ground ends of grid coils. Filament and bias transformers are in the secand bax. The large resistor to the left of the grid bax is the screen resistor. The variable resistor in the upper left-hand carner is the relay shunt R4. The selenium bias rectifier is fastened against the left-hand wall af the chassis.

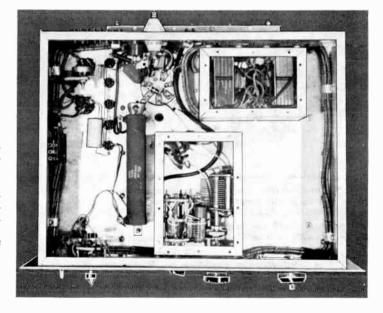

ONE-BAND KILOWATT AMPLIFIERS

Separate kilowatt amplifiers on each of the bands 80 through 10 meters has always been the ne plus ultra of transmitter construction. However, space limitations and cost are the two key factors that have prevented many from realizing this goal. The amplifiers to be described are compact and are constructed economically; the builder may wish to construct one amplifier for his favorite band or the group of five for versatile all-band operation. Advantages of the separate-amplifier philosophy include optimum circuit Q for every band, simplified construction and band switching, less chance for tube failure because each amplifier is pretuned, and fast band changing for the contest-minded. The supply voltages remain on all the amplifiers; only the filament and excitation power are switched to the desired final amplifier.

The availability and proven dependability of the 813 make a pair of them the logical choice for the kilowatt amplifier. A shrewd amateur should have no trouble procuring the tubes through surplus channels or by bartering with local hams.

Referring to the circuit diagram, Fig. 6-65, the

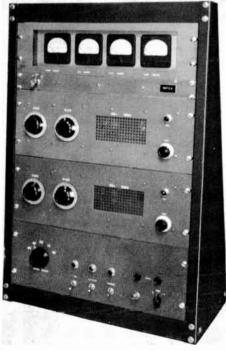


Fig. 6-64—Individual kilowatt amplifiers for two bands plus complete metering and all control circuits and power supplies (except plate) fit handily into a table rack. Amplifiers for five bands plus the plate supply will mount in floor rack. Band switch at lower left (S_B in Fig. 6-65) switches filament supply, excitation and output connections to all amplifiers in use; screen and plate supplies are connected to all amplifiers at all times.

amplifier control unit contains the filament, bias and screen supplies. A 3-position mode switch, S_2 , selects the bias for either Class AB_1 or C operation, and in the third position grounds the screen grids, to limit the plate current during initial tuning. Another 3-position switch, S_1 , allows the total or individual screen currents to be read. The latter position is useful in matching tubes. The high-voltage supply should furnish from 1750 to 2250 volts.

Construction

Each amplifier is assembled on a 13×17 -inch aluminum bottom plate. Two $5 \times 13 \times 3$ -inch aluminum chassis are used as the sides of the enclosure. The paint is removed from the back of a 7-inch aluminum rack panel, and a piece of Reynolds cane metal is sandwiched between the panel and the two chassis. A rectangular window in the panel provides additional ventilation and a means for inspecting the color of the tube plates. The top and back of the enclosure are formed from a single piece of cane metal, bent to fit the chassis rear and top. Three lengths of $1 \times 1 \times \frac{1}{16}$ -inch aluminum angle stock are used in the corners of the enclosure, as can be seen in Figs. 6-67 and 6-68.


The variable tank capacitors, C_4 , are mounted on 1-inch stand-off insulators, to bring the shafts to the proper panel height. In the 10-meter amplifier the capacitor shaft must remain above r.f. ground, and a suitable insulated shaft coupling is used. On the other bands, the rotors of the capacitors are grounded to the chassis through metal straps.

On 20, 15 and 10 meters the tank coils are wound self-supporting of ¼-inch diameter soft-drawn copper tubing, and they are supported by their leads. On 80 and 40 the coils are lengths of Air-Dux stock, and they are supported by small ceramic insulators.

The special plate r.f. chokes, RFC₂, are constructed by close-winding No. 24 enameled wire on ¾-inch diameter ceramic insulators. Four-inch long insulators (National GS-4) are used on the 80- and 40-meter bands, and 2-inch long insulators (National GS-3) are used on the other bands. In each case the original base of the insulator is removed and the insulator is mounted on a stand-off (Johnson 135 20). The high-voltage lend and the "cold" end of the choke are connected to a soldering lug mounted between the two insulators.

Bridge neutralization is included in the 20-, 15- and 10-meter amplifiers. The neutralizing capacitors are made from two $\frac{1}{2}$ -inch wide aluminum strips 5 inches long. One strip is connected directly to the plate lead at C_3 and the other is supported by a ceramic feed-through insulator that connects to the rotor of C_1 . The amplifiers are neutralized by adjusting the spacing between the aluminum strips.

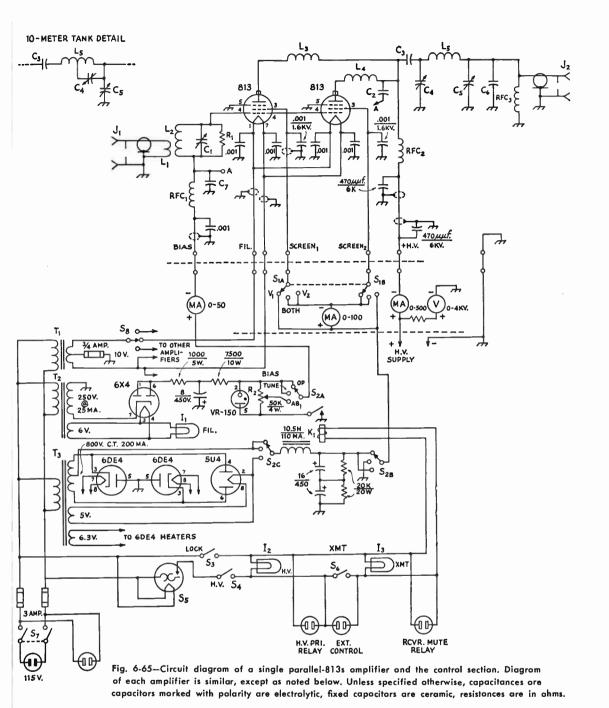The metal ring surrounding the base of the 813



C₂-Not used on 80 or 40 meters; see text.

C₃—Two 500-μμf. 20-kv. ceromic (Centralab TV-207) in parallel on 80 m.; single 500-μμf. 20-kv. ceromic on other bonds.

C₁--0.001-μf. 1-kv. ceramic on 80 and 40 m.; 240-μμf. silver mico on other bands.

I1, I2, I3-115-v. pilot lomp.

J₁, J₂--Coaxial coble receptacle.

K₁-S.p.d.t. relay, 115-v. a.c. coil.

L₂, L₄-Not required on 80 or 40 m.; 6 turns No. 14 on 1/4-inch diam.

R₁--10,000 ahms, 2 watts, composition (not wirewound).

R2-50,000 ahms, 4 watts (Mallary M50MPK).

RFC₁-2.5-mh, 75-ma, r.f. choke.

RFC2-See text.

RFC₃--2.5-mh. 300-ma. r.f. chake.

 S_1 —Two-pole 3-position rotary switch, shorting type.

S₂—Two-pole 3-position rotary switch, non-shorting type.

S3-S.p.s.t. lock switch (AHH 81715-L).

S_s-Time delay relay (Amperite 115N060).

S7-Heavy duty d.p.s.t. taggle.

T₁-10-volt 10-ampere filament transformer (Thordarson 21F19).

T₂--250-volt 25-ma. tronsformer (Stancor PS-8416). T₈--800-v.c.t. 200-ma., 5- and 6.3-v. heater windings.

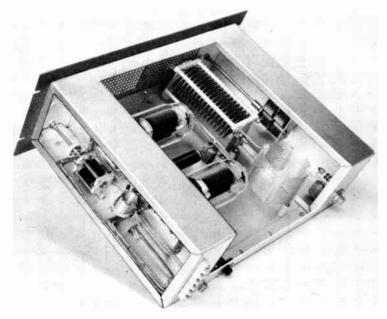


Fig. 6-66—View of the 40-meter amplifier with its cane-metal covering removed. As in each amplifier, the chassis is made from two 5 × 13 × 3-inch chassis and a 13 × 17-inch base plate. Input and low-voltage leads make up to terminals and jack in center foreground.

should be grounded to the chassis. A piece of Eimac Finger Stock or a homemade contact can be used for the purpose.

All power wiring is done with shielded wire and bypassed as described in Chapter Twenty-Three. The filament leads should be made from No. 14 (or heavier) shielded wire.

The screen and bias supplies plus station control circuits are built on a rack-mounting chassis (Bud CB-1373) behind a 7-inch panel. In the

Class-C position of S_2 , +400 volts is applied to the screens and -150 is connected to the grids. In the Class AB_1 position, the screen voltage is increased to 700 and the grid bias is dropped to a value determined by the setting of R_2 . This latter setting should be one that gives best linearity without exceeding a no-signal plate input of 150 watts for the two 813s; it depends on the plate voltage available. A heavy bleed on the screen supply helps the regulation.

		Coil	and Capacitor Table		
Band	80	40	20	15	10
C1	100 μμf. (Johnson 100L15)	100 μμf. (Johnson 100L15)	50 μμf. (Johnson 50L15)	50 μμf. (Johnson 50L15)	50 μμf. (Johnson 50L15)
Ca	150 μμf. (Johnson 150E45)	150 μμf. (Johnson 150E45)	35 μμf. (Johnson 35E45)	35 μμf. (Johnson 35E45)	50 μμf. (Hammarlund MC·50-MS)
Съ	710 μμf. (2-gang 365 μμf.)	325 μμf. (Hammarlund MC-325-M)	325 μμf. (Hammarlund MC·325·M)	325 μμf. (Hammarlund MC-325-M)	325 μμf. (Hammarlund MC-325-M)
Св	500 μμf. (Centralab TV-207)	100 μμf. (CRL 850S-100N)			
L_1	4 t. No. 22*	3 t. No. 22*	2 t. No. 22*	1 t. No. 22*	1 t. No. 22*
L ₂	32 t.p.i. No. 24, 1 inch long, 1 inch diam. (B&W 3016)	16 t.p.i. No. 20 1¼ inch long, 1 inch diam. (B&W 3015)	8 t.p.i No. 18 136 inch long, 1 inch diam. (B&W 3014)	8 t.p.i. No. 18 34 inch long 1 inch diam. (B&W 3014)	8 t.p.i. No. 18 ½ inch long, 1 inch diam. (B&W 3014)
L ₅	6 t.p.i. No. 12, 3 inch long, 3 inch diam. (Air Dux 2406)	4 t.p.i. No. 12, 3¾ inch long, 2½ inch diam. (Air Dux 2004)	2 t.p.i. ¼-inch copper tubing, 4½ inch long, 2½ i.d.	2 t.p.i. ¼-inch Copper tubing, 3 inch long, 2½ i.d.	2 t.p.i. ½-inch copper tubing, 2 inch long, 2½ i.d. C ₄ tap 2 turns.

^{*} Insulated hookup wire, wound over C_{τ} end of L_{2} .

One-Band Kilowatts

The unit shown in Fig. 6-65 uses an Ohmite Model 111 switch at S_8 . This is ganged with antenna and excitation switches to permit one-control bandswitching. The relay K_1 is actuated

when the plate supply is turned on; when the relay is open a high bias is applied to the 813s to reduce the plate current to 0 ma. and eliminate receiver noise caused by static plate current.

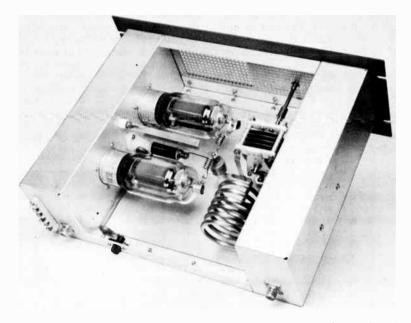


Fig. 6-67—Top view of the 15-meter amplifier. The neutralizing capacitor consists of two strips of aluminum, supported by the plate-blocking capacitor and a feedthrough insulator. It is mounted over the r.f. choke between the two 813 tubes.

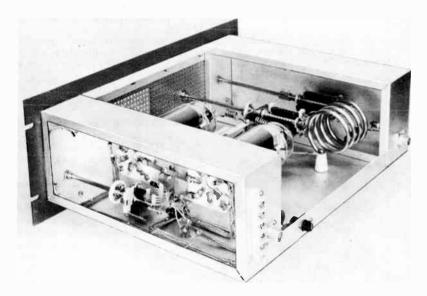


Fig. 6-68—As in the other amplifiers, the 10-meter final uses shielded wires in the filament, screen, and grid-return circuits. For tuning this amplifier uses a small variable capacitor connected across half of the plate coil, to maintain a favorable L/C ratio.

A GROUNDED-GRID HALF KILOWATT

The amplifier shown in Figs. 6-69, 6-71 and 6-72 will run at about 500 watts input on c.w.—or p.e.p. input as an s.s.b. linear — on all bands from 80 through 10 meters. The unit is small enough to sit on the operating table right along with the rest of the station equipment; no need for big racks here.

Using a pair of 811As in parallel in the grounded-grid circuit, this rig is a good one to use following transmitters such as the Viking Ranger, DX-40, Globe Scout, and others of similar power class, for a worth-while increase in power output on c.w. As a linear amplifier following an s.s.b. exciter it requires no swamping because the 811A grids provide a fairly constant load in themselves, and also the fed-through power with grounded-grid presents an additional constant load to the driver. The total driving power needed on any band is less than 20 watts.

An additional useful feature is a built-in directional coupler using a version of the "Mickey Match." Besides its obvious application for checking the s.w.r. on the transmission line to the antenna or for help in tuning up a coaxcoupled antenna coupler, it is practically indispensable as an indicator of relative power output in tuning the amplifier.

The Circuit

A number of tube types could be used in an amplifier of this power class, but the 811As are a good choice because they do not need a bias supply and are not expensive. (Surplus 811s can be used; the ratings are not quite as high but they can be pushed a bit in intermittent service such as c.w. and s.s.b.)

The complete circuit is shown in Fig. 6-70. To save trouble and work, standard components are used throughout — the only special construction is the shielding and a few simple r.f. chokes. The tube filaments are driven directly from coax input from the driver; no tuning is used or is needed in this circuit. The filaments are kept above ground by the B & W type FC15 choke.

The plate tank is the familiar pi network, using a B & W type 851 tapped coil and band-switch assembly. This assembly has been modified slightly in two respects: First, the copper-strip 10-meter coil normally mounted at the top of the rear plate is taken off and moved so that it is supported between the tank assembly and the stator of the tank tuning capacitor as shown in Fig. 6-71. A short length of copper strip is bolted between the free end of the coil and the righthand stator connection of the tuning capacitor, to support the free end. This change is made in order to avoid the long lead that would have to be run from the capacitor to the regular input terminal on the tank assembly, since this terminal is at the right-hand side of the assembly as viewed from the top. The turns of the 10-meter coil are also squeezed together a bit to increase the inductance, because it was found that a rather large amount of capacitance had to be used to tune the circuit to the band with the coil at its original length. The length is now 15% inches between mounting holes.

The second modification is the addition of a pair of switch contacts on the rear switch plate of the tank assembly. There is an extra position on this plate with holes already provided for contacts, and the additional set of contacts is used to switch in fixed output loading capacitance on 80 meters, where a large output capacitance is needed. The variable loading capacitor, C_3 , with the five fixed mica capacitors, C_5 to C_9 inclusive, give continuous variation of capacitance up to 1275 $\mu\mu$ f. on all bands, including the regular switch position for the 80-meter band. However, if the switch is turned to the extra position an additional 1000-µµf. mica capacitor is connected in parallel, so that continuous variation of capacitance to over 2200 $\mu\mu$ f. is possible on 80. This takes care of cases where the load resistance happens to be unusually low or reactive.1

¹These contacts can be obtained directly from the manufacturer of the tank assembly. To secure a set of contacts with mounting hardware, send one dollar to



Fig. 6-69—This amplifier operates at a plate input of approximately 500 watts, uses a pair of 811As in grounded-grid, and is complete with power supply on a 13 imes 17 imes 4-inch chassis. The rack panel is 10½ by 19 inches. Front-panel controls include the plate tuning capacitor and band switch in the center, filament and plate power switches with their pilot lights at the lower left, sensitivity control and forward-reflected power switch for the directional coupler at the lower right, variable loading capacitor and auxiliary loadingcapacitor switch underneath the 0-1 milliammeter at the right, and the grid-cathode milliammeter with its switch at the upper left. The filter choke, 866As and plate transformer occupy the rear section of the chassis.

A 500-ma. d.c. meter is used for reading either total cathode current or grid current alone. The

Barker & Williamson, Beaver Dam and Canal, Bristol, Penna., specifying the type of tank assembly for which they are wanted. The contacts are not catalog items and are not available through dealers. cathode current is read in preference to plate current because of safety considerations. Putting the meter in the hot d.c. plate lead leaves nothing but a little plastic insulation between the high voltage and the meter adjusting screw. It is a bit of a nuisance to have to subtract the grid

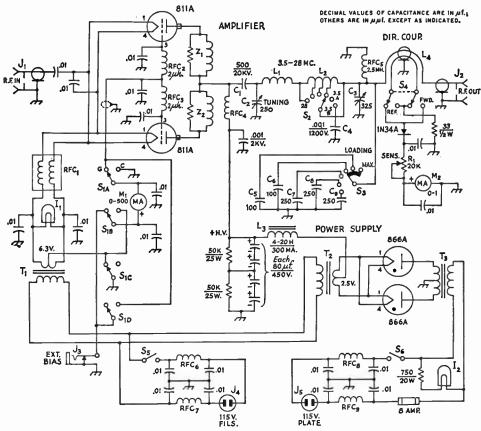


Fig. 6-70—Circuit diagram of the parallel-811A grounded-grid amplifier. Unless otherwise specified, fixed capacitors are disk ceramic, 600-volt rating.

C₁=500 $\mu\mu$ f., 20,000 volts (TV "doorknob" type). C₂=250- $\mu\mu$ f. variable, 2000 volts (Johnson 250E20).

 C_3 =325- $\mu\mu$ f. variable, receiving type (Hammarlund) MC-325-M).

C4-C0, inc.-1200-volt mica, case style CM-45.

1₁, 1₂-6.3-volt dial lamp, 150-ma. (No. 47).

J₁, J₂-Coax connector, chassis mounting.

J₃-Closed-circuit phone jack.

J₄, J₅—115-volt male connector, chassis mounting (Amphenol 61-M1).

L₁, L₂, S₂—5-band pi-network coil-switch assembly; see text (B & W 851).

L₈—Swinging choke, 4-20 henrys, 300 ma. (UTC S-34).
L₄—Section of coax line with extra conductor inserted; see measurements chapter for construction references.

M₁, M₂-Milliammeter, 3½-inch plastic case (Triplett 327-PL).

R₁—20,000-ohm composition control, linear taper.

RFC₁—Filament-choke assembly, to carry 8 amp. (B & W FC15).

RFC2, RFC3-2 µh. (National R-60).

RFC₄-90 μh.; 4%-inch winding of No. 26, 40 t.p.i., on ¾-inch ceramic form (B & W 800).

RFC₅-2.5 mh., any type.

RFC₆-RFC₉, Incl.—18 turns No. 14 enam., close-wound, 1/2-inch diam., self-supporting.

S₁—4-pole 2-position rotary, nonshorting (Mallory 3242J or Centralab 1450).

S₂—Part of tank assembly; see L₁ L₂.

S₂—Miniature ceramic rotary, 1 section, 1 pole, 6 positions used, progressive shorting (Centralab 2042).

S₄—Miniature ceramic rotary, 1 section, 2 poles, 2 positions used, nonshorting (Centralab 2003).
S₅, S₆—S.p.s.t. toggle.

T₁—Filament transformer, 6.3 volts, 8 amp. min. (UTC S-61).

T₂—Filament transformer, 2.5 volts, 10 amp. (UTC \$ 57)

T₂-Plate transformer, 3000 volts center-tapped, 300 ma. d.c. (UTC S-47).

Z₁, Z₂-2½ t. No. 16 ½-inch diam., over 100-ohm 2watt carbon resistor. current from the cathode current in order to find the plate current, but it isn't serious. The d.c. grid circuit has a jack, J_3 , for introducing external bias either for blocked-grid keying or for cutting off the plate current during receiving, and a four-pole switch, S_1 , is therefore needed for handling the meter switching while keeping all circuits functioning normally.

The power supply uses 866As with a plate transformer giving 1500 volts each side of the center tap, and working into a single-section choke-input filter. The filter capacitor consists of four 80-µf. electrolytics connected in series to handle the voltage, giving an effective filter capacitance of 20 µf. This supply is running well below its capabilities in the intermittent type of operation represented by c.w. and s.s.b., and the amplifier is somewhat "over-powered" in this respect. A lighter plate transformer can be used since the average current in regular operation is only about half the maximum tube rating of 350 ma. for the pair.

The a.c. inputs to both filaments and plates have TVI filters installed right at the a.c. connectors. The chokes in these filters, RFC_0 to RFC_0 inclusive, are homemade by winding 18 turns of No. 14 enameled wire close-wound on a half-inch dowel or drill,

Construction

The only space available for the filament transformers is below chassis, so these are mounted on the front wall of the chassis as shown in Fig. 6-72. There is plenty of room for all other power-supply parts below chassis, and the photographs make any further comment on this section unnecessary.

The r.f. layout shown in Fig. 6-71 is almost an exact copy of the circuit layout as given in Fig. 6-70. The plate blocking capacitor, C_1 , is mounted on a small right-angle bracket fastened to the left-hand stator connection of the tank capacitor, C_2 . The tube plates are connected to C_1 through individual parasitic-suppressor assemblies, Z_1 and Z_2 . The hot end of the plate

choke, RFC4, also connects to this same point. The tank capacitor is mounted on 34-inch ceramic pillars to bring its shaft to the same height as the switch shaft on the tank-coil assembly. The capacitor is grounded by connecting the bottom of its frame through a half-inch wide strip of aluminum to essentially the same point at which the plate-choke bypass capacitor, a $0.001-\mu f$. 2000-volt disk, is grounded. The ground end of the aluminum strip actually is under the bottom of the plate choke, and the ground lug for the bypass capacitor is just to the left. This strip, plus short leads in the circuit from the tube plates through the tank capacitor to ground, keep the resonant frequency of the loop thus formed well up in the v.h.f. region; this is important because it permits using low-inductance parasitic chokes in shunt with the suppressor resistors, and thus tends to keep the r.f. plate current at the regular operating frequencies out of the resistors. With other tank grounding arrangements originally tried, larger parasitic chokes had to be used and it was impossible to prevent the resistors from burning up when operating on 10, 15 and even 20 meters. Now they do not overheat on any frequency, and v.h.f. parasitics are nonexistent although without the suppressors the parasitics are only too much in evidence.

The output loading capacitors, C_3 through C_9 , are mounted toward the rear so the leads from the tank coil can be kept as short as possible. A length of copper strip is used between the coil and the stator of C_3 ; originally this lead was No. 14 wire but on 10 meters the tank current was enough to heat it to the point of discoloration. The ground lead from the fixed units, made to the rear bearing connection of C_3 , is also copper strip. C_3 and S_3 are operated through extension shafts, using Millen flexible couplings to simplify the alignment problem.

Underneath the chassis, each 811A grid is bypassed directly to the socket-mounting screw nearest the plate choke (right-hand side of the socket in Fig. 6-72). The d.c. leads have small

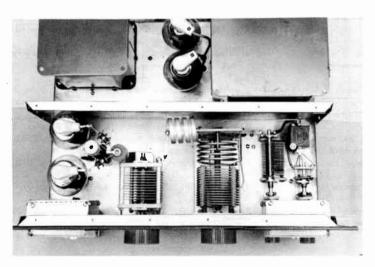


Fig. 6-71—The r.f. section with the shield cover removed. Components here are readily identifiable by reference to the circuit diagram. The meters are enclosed in rectangular boxes made from thin aluminum sheet, formed to be fastened by the meter mounting screws. The back covers on these boxes are made from perforated aluminum, folded over at the edges and held on the boxes by sheet-metal screws. The switch for shifting the 0-500 milliammeter (left) from grid to cathode is concealed by the box which encloses

the meter.

Grounded-Grid Half Kilowatt

chokes, RFC_2 and RFC_3 , with additional bypasses for good r.f. filtering, particularly at v.h.f. since grid rectification generates harmonics in the TV bands. The filament choke, RFC_1 , is mounted so that the filament side is close to the filament terminals on the tube sockets; the other end is bypassed directly to the chassis.

The shielding around the amplifier consists of two pieces of sheet aluminum and a perforated aluminum ("do-it-yourself" type) cover having the shape of an inverted U. Fig. 6-71 shows how the rear wall is made. Its edges are bent to provide flanges for fastening the cover with sheet-metal screws, and there is a similar flange projecting to the rear at the bottom for fastening the wall to the chassis. The front piece extends the full height of the panel and is identically drilled and cut out for meters and controls. It has flanges at the top and extending down the sides from the top to the chassis. The cover itself extends down over the sides of the chassis for about one inch. Numerous screws hold down the cover, to prevent leakage of harmonics.

The shields over the meters are made as described in the caption for the inside top view. Meter leads are bypassed to the shield boxes where they emerge.

Construction of the directional coupler parallels that given for the antenna coupler in Chapter Thirteen.

Operating Conditions and Tuning

The voltage delivered by the power supply is approximately 1500 volts with no drive and with the tubes taking only the no-bias static plate current, which is about 60 ma. At the full load of 350 ma. the voltage is slightly under 1400. Optimum operating conditions for 1400 volts at 350 ma. peak-envelope power input as an s.s.b. linear call for a peak-envelope grid current of 60 ma. The peak-envelope tube power output is close


to 350 watts under these conditions. The same conditions are also about optimum for c.w.

The behavior of the cathode current when tuning a grounded-grid triode amplifier is somewhat confusing, and the meter is principally useful as a check on operating conditions rather than as a tuning indicator. The best indicator of proper tuning of the plate tank capacitor is the forward-power reading of the directional coupler. For any trial setting of the loading controls and driving power, always set the plate tank capacitor control at the point which results in a maximum reading on the power-output indicator.

The power indications are only relative, of course, and the sensitivity control should be set to give a reading in the upper half of the scale of the meter.

The objective in adjusting loading and drive is to arrive at maximum power output simultaneously with a plate current of 350 ma. and a grid current of 60 ma. — that is, a total cathode current of 410 ma. when the grid current reading is 60 ma. The loading is critical. If the amplifier is not loaded heavily enough the grid current will be too high and the right value of total cathode current either will not be reached or, if reached, the amplifier will be operating in the "flattening" region as an s.s.b. linear. (It can be operated this way on c.w., however, since linearity is unimportant here.) If the loading is too heavy, the grid current will be low when the cathode current reaches the proper value, but the efficiency will be low. Getting the knack of tuning takes practice, but when done right the tubes will run cool on all bands in regular operation. Running key-down over a period of time may show just a trace of dark red color on the plates since the input and dissipation are somewhat over ratings under these operating conditions, although perfectly satisfactory with keying or s.s.b. voice.

Fig. 6-72-In this below-chossis view, the two filament transformers are at the top, mounted on the chassis wall. The 811A sockets are at the upper left. The rectangular box on the left-hand wall contains the FC15 filament-choke assembly. The "Mickey Match" directional coupler is at the upper right. Filter capacitors and the bleeder resistors are in the lower section. A.c. inlets, fuse holder, bias jack, and the 115volt line TVI filters are on the bottom chassis wall.

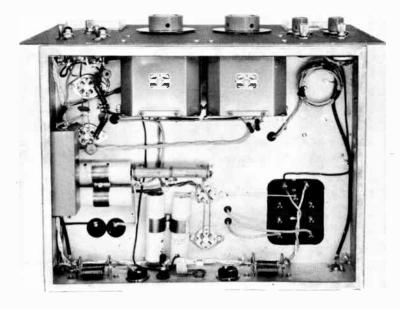

A KILOWATT GROUNDED-GRID AMPLIFIER

The amplifier shown in Figs. 6-73, 6-75 and 6-76 is built around the Penta PL-6580, a high-\$\mu\$ triode designed especially for grounded-grid Class-B r.f. amplifier service. With a plate voltage of from 3000 to 4000, from 700 to 900 watts p.e.p. output can be obtained with about 75 watts driving power. A stabilized bias supply is included that will provide the correct bias for any operating plate voltage between 2500 and 4000.

Referring to the circuit diagram, Fig. 6-74, the cathode (filament) is maintained above ground by the filament chokes RFC_1 and RFC_2 . An L network, tuned by C_1 , provides voltage step-up to the cathode. On 80 meters the capacitor C_1 , together with fixed capacitor C_2 , tunes the filament chokes. On the other bands the fixed capacitor is removed and the proper inductance is shunted across the chokes.

To insure good r.f. grounding of the grid, three 0.001- μ f. disk ceramic capacitors are used between the grid pins and the chassis. The bias supply uses a high-current low- μ 6080 twin triode to stabilize the bias, in conjunction with the 6AU6 control tube and the 0A2 voltage-reference tubes. The bias voltage is set by the position of the arm of R_1 .

The plate circuit of the amplifier departs from more conventional practice in several ways. The output capacitance in the 80-meter condition is relatively small; this is a result of using a low capacitance at C_3 , which in turn lowers the circuit Q and requires a lower output capacitance for proper loading. If a low plate voltage (2500) is to be used, it would be better to increase the capacitance value of C_3 and the capacitance switched across the output on 80 meters. On all of the other frequency ranges the capacitances are more in line with normal Q values. On 15

and 10 meters S_{2B} shorts part of L_4 , to break up a resonance in the unused coil.

Although the PL-6580 requires 5 volts on the filament, a 6.3-volt filament transformer is used. The resistance of RFC_1 and RFC_2 is sufficient to drop the voltage to the correct value. The 6080 regulator and the 6X4 rectifier heaters are also connected to the filament transformer, T_1 .

Construction

Referring to Figs. 6-75 and 6-76, the amplifier is built on a $12 \times 17 \times 3$ -inch chassis, with a standard 101/2 × 19-inch relay rack panel. Aluminum angle stock is used to form a framework for the perforated-metal sides (not shown in the photographs). To cool the PL-6580, a blower is mounted on the chassis so that the air is pulled in through a perforated-metal side and blown down under the chassis. The chassis, sealed off with an aluminum bottom plate, can only exhaust the air past the tube and, to facilitate this, the tube socket is mounted in a 3½-inch-diameter hole. The combination of the large hole, the ventilated socket (Johnson 122-275) and the glass chimney (Penta PL-Cl) gives sufficient cooling with any blower of 50 c.f.m. or more.

The plate-circuit band switch, S_2 , is mounted on the chassis and controlled via a right-angle drive. Leads from the switch to L_3 and L_4 are best made with copper tubing or strap. Various 500- $\mu\mu$ f. 5-kv. capacitors in the plate and output circuit are high-voltage ceramic (Centralab 858S-500), mounted on the tuning capacitors or on metal straps.

While meters with integral metal shields (Phaostron Co., Pasadena, Calif.) are shown in Fig. 6-76, an alternative is to use regular meters and small aluminum boxes, as described in Chapter 23.

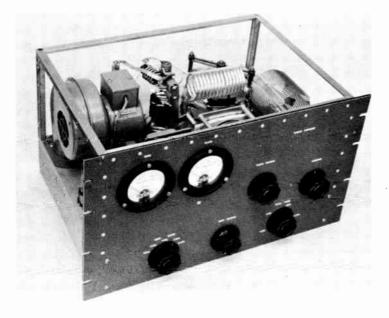


Fig. 6-73-A grounded grid amplifier using the PL-6580 triode. Able to handle a kilowatt p.e.p. input with 3000 volts on the plate, and even more with a higher plate voltage, a chimney surrounds the tube to improve the forced ventilation. In this view the side and top cane-metal panels have been removed.

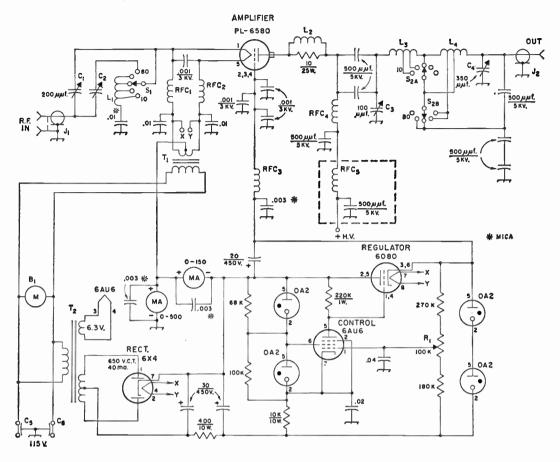


Fig. 6-74—Circuit diagram of the kilowatt graunded-grid linear amplifier. Unless indicated oherwise, capacitances are in μf., resistances are in ohms, resistors are ½ watt. Capacitors marked with polarity are electrolytic, capacitors marked * are mica.

B₁-Ventilating blower, at least 50 c.f.m. (surplus).

 C_1 =200- $\mu\mu$ f. variable (Johnson 200L15).

C₂—200-μμf. variable, locked at full capacitance (Johnson 200L15).

C₈-100-μμf. variable, 0.175-inch spacing (Johnson 100D70).

C₄—350-µµf. variable, 0.075-inch spacing (Johnson 350E30).

 C_6 , C_6 —0.1- μ f. feedthrough, 600 volts (Sprague 80P3). J_1 , J_2 —SO-239 caaxial jack.

L₁-20½ turns No. 18, 8 t.p.i., 1-inch diam. Tapped at 2½, 4½ and 9½ turns from ground end (B&W 3014).

L₂-5 turns No. 12, ½ diam., 1½ long, wound around (but not touching) 10-ohm 25-watt resistor. L₂-13¾ turns ¾₆-inch copper tubing, 4½ t.p.i., 1½ inch i.d., silver plated. Tapped at 4¾ and

Adjustment

The bias voltage should be set, with R_1 , to give a no-signal plate input of 150 to 160 watts. The maximum-signal grid current should be about 95 ma. for 2500 volts on the plate to 65 ma. at 4000

7¾ turns from plate end.

L₄-191/₂ turns No. 12, 6 t.p.i., 3 inch diam., 40-meter tap 81/₂ turns fram plate end, anti-resonance tap 3 turns from plate end (Illumitronic 2406).

RFC₁, RFC₂—34 turns No. 14 enam., clasewound on same 1¼ diam. phenolic tubing.

RFC₃--2-mh. 400-ma. r.f. choke (Miller 4550).

RFC₄-225- μ h. r.f. choke, 800-ma. (National R-175A). RFC₆-28 turns No. 20, 16 t.p.i., $\frac{4}{3}$ diam. (B&W 3007).

S₁--5-position single-pole rotary ceramic, non-sharting (Centralab 2550).

S₂—5-position 2-pole rotary ceramic (two sections Communications Products Model 88).

T₂--6.3 v., 20-amp. filament transformer (Triad F-22A)
T₂--650 v.c.t., 40-ma. power transformer (Stancor PC-8406, 5-v. secondary not used).

plate volts. The input limit is 875 watts at 2500 volts to 1200 watts at 4000 volts.

It is desirable to tune up with an output indicator of some kind. The description of the lowerpowered amplifier earlier in this chapter carries details of the tune-up procedure.

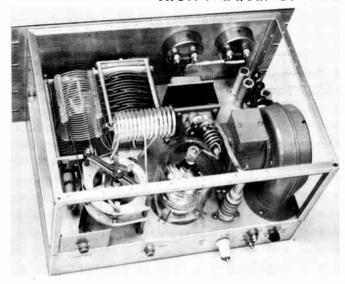


Fig. 6-75—Another view of the grounded-grid amplifier, showing the large switch used in the plate circuit. Tubes visible in the upper right are used in a regulated grid-bias supply. Metal shields on the two panel meters minimize radiation.

High voltage for the plate is brought to the jack on the stand-off insulator at the lower right; the a.c. line is connected to the filter terminals to the right of the insulator.

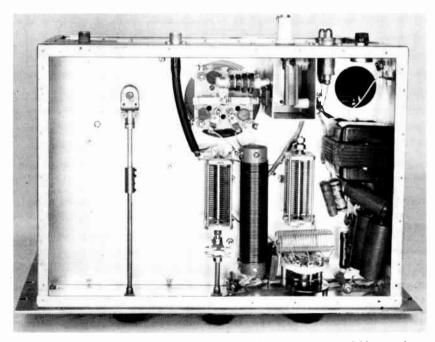


Fig. 6-76—A view under the chassis shows the filament choke between the two variable capacitors, with the input tuning coil mounted on the input band switch. The small shield compartment at the top surrounds a filter in the B+ lead.

Air from the blower is forced through the hole at the upper right, and it finds its way past the socket and up the chimney as a result of the cut-out area around the socket. The three grid connections on the socket are connected together by a copper strap and bypassed to chassis at three places. An r.f. choke in the grid lead mounts on the socket.

A right-angle drive (National RAD) turns the large band switch mounted above the chassis.

A KILOWATT 4-400A AMPLIFIER

Any transmitter delivering about ten watts will drive the amplifier shown in Figs. 6-77 through 6-82. When used as a Class AB₁ linear for sideband, a peak driving voltage of about 150 is required. The plate tank circuit of the amplifier is homemade from readily available parts.

Referring to Fig. 6-78, the amplifier uses the conventional neutralized grounded-cathode amplifier circuit. Switch S_{1B} shorts out the unused part of grid coil L_2 , and S_{1A} modifies the input link coupling. A Harrington Electronics GP-20L subassembly is shown, but an equivalent circuit can be built from standard parts. The output circuit is a shunt-fed pi network for the amateur bands 3.5 to 30 Mc. The smaller tuning capacitor, C_{10} , is used on 20, 15 and 10 meters, and the larger C_{11} is added for tuning on 40 and 80 meters. Having two tuning capacitors allows the optimum L/C ratio to be maintained on all bands without resorting to an expensive vacuum variable.

A 17-c.f.m. blower supplies adequate forced air cooling for the 4-400A base and plate seals. The blower is connected across the 4-400A filament transformer primary and operates whenever the filament is energized.

All required control and metering circuits are mounted on a separate chassis. Meters are provided for amplifier grid current, screen current, cathode current and plate voltage, to comply with the FCC rule regarding measurement of input powers over 900 watts.

The amplifier is fixed biased at -225 volts for Class C and -150 volts for Class AB₁ operation. The full-wave rectifiers in the bias supply are silicon diodes, with no warm-up time, and full operating bias is applied as soon as the power switch, S_0 , is closed. Time-delay relay K_1 operates K_2 , which is in series with the screen supply primary. Thus there is a 60-second delay before screen potential can be applied to the amplifier tube.

The accessory a.c. socket, J_8 , and the high-voltage filament transformer socket, J_9 , are energized as soon as power switch S_1 is closed. The h.v. plate transformer is turned on by a relay plugged into J_{10} and controlled by the time-delay relay. With this arrangement, it is impossible to apply a.c. to the h.v. rectifier plates before their filaments have had a chance to warm up.

A variable autotransformer in series with the screen-supply primary allows the screen voltage to be adjusted from zero to about 800 volts under load. This makes a convenient arrangement for setting the screen voltage when changing from Class C to Class AB₁ or vice versa, and for adjusting the power input of the amplifier.

A screen overload protection circuit is included. If excessive screen current flows, K_3 is energized and is kept energized by the current

through R_8 . To reset the relay the screen voltage must be momentarily disconnected so that the relay will return to its unenergized condition. This can be done by opening S_7 . The current at which the overload relay throws is set with shunt resistor R_7 ; maximum allowable screen dissipation is 35 watts.

Contruction

The amplifier is built on a $4 \times 13 \times 17$ -inch chassis and uses a 14-inch rack panel. All major components are visible in the photographs. The Harrington grid circuit, output loading capacitors and switch, and filament transformer are all below the chassis.

An insulated coupling must be used between the rotor of C_1 and the shaft going to the grid tuning knob. Leads from the grid circuit are brought out through the 3×5 -inch aluminum back plate via a feed-through capacitor and bushings. The input link is connected to the coax receptacle through a length of RG-58/U. The flanged cover of a $5 \times 4 \times 3$ -inch Minibox is slipped over the grid assembly, and this cover is secured to the back plate with four self-tapping screws and to the main chassis with four 6-32 spade bolts.

The ganged loading capacitors (C_{12}) are mounted off the chassis on 1-inch spacers. Connections in the output circuit are made with



Fig. 6-77—The kilowatt 4-400A amplifier and its control unit are mounted in a 21-inch gray hammertone rack cabinet (Bud CR-1727). Shelf brackets (Bud SA-1350) are mounted on both sides of the cabinet to hold the amplifier chassis. Below the meters, from left to right: filament pilot light, key-type a.c. switch,

Class AB₁/C bias switch, screen autotransformer, plate switch and plate pilot light.

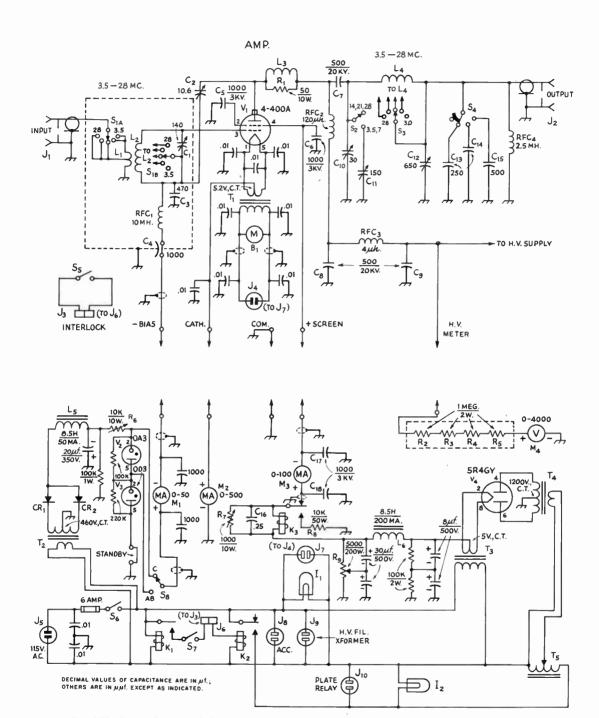


Fig. 6-78—Circuit diagram of the 4-400A amplifier (abave the dashed line) and power supply/cantrol unit.

Resistances are in ahms, and resistars are ½-watt unless atherwise indicated. Capacitars nat listed are 600-valt disk ceramic except far those marked with palarity, which are electralytic.

A Kilowatt 4-400A Amplifier

copper or brass strapping to provide low-inductance leads.

The blower is mounted on the rear apron of the chassis by four 6-32 spade lugs attached to the walls of the blower output housing. A 1½ X 1½-inch hole cut in the rear apron of the chassis accommodates the blower; a cork gasket is used between the plastic blower housing and the amplifier chassis.

The chassis should be as airtight as possible to provide maximum air flow to the 4-400A tube, and any small holes should be sealed by covering them with tape.

Plate Tank and Enclosure

The plate tank coil, L_4 , band switch, S_3 , and plate tuning capacitor switch, S_2 , are mounted on two Lucite plates in the center of the chassis. The tank coil comes prewound on one Lucite plate which is positioned $3\frac{1}{2}$ inches above the chassis on ceramic spacers. Hard rubber washers (the type used for packing faucets) are inserted between the ceramic spacers and the Lucite plates to provide a tight fit.

Counting from the blocking capacitor end, the

B₁—Blower-mator assembly, 17 c.f.m. (Ripley, Inc., Middletown, Conn., type 8433).

C₁-140-μμf, midget variable (Hammarlund APC-140-B), Part of Harringtan Electronics GP-20L.

C₂-10.6-µµf. neutralizing (Johnson N250).

C₃-500-volt mica.

 $C_4=0.001-\mu f$. feed-through (Centralab FT-1000).

 C_{δ} , C_{δ} , C_{17} , C_{18} =0.001- μ f., 3000-volt disk ceramic Centralab DD30-120).

C₁, C₈, C₉-500- $\mu\mu$ f., 20,000-valt ceramic (Centralab TV-207).

C₁₀—30-μμf. variable, 0.25-inch spacing (Barker & Williamson CX-45-C butterfly, one section used), ar Jahnsan 50D90 with two stator plates removed).

 C_{11} =150- $\mu\mu$ f. variable, 0.25-inch spacing (Johnson 150D90).

C₁₂-650-µµf. variable (two Hammarlund MC-325M ganged and paralleled).

C13, C14, C15-2500-valt mica (Aerovox 1652L).

C₁₆-200-volt malded paper.

CR₁, CR₂—500-ma. 600-valt peak inverse silicon diode (Sarkes Tarzian F-6).

J₁, J₂-Coaxial receptacle, chassis mounting (SO-239).

Ja, Je-2-contact socket (Cinch-Jones S-202-B).

J₄, J₅—115-valt plug, chassis mounting (Amphenol 61-M1).

J7-J10, incl.-115-volt socket (Amphenol 61-F1).

K₁-115-volt 60-second time-delay, normally open (Amperite 115N060).

K₂—S.p.d.t. relay, 115-volt a.c. coil (Potter & Brumfield KA5AY).

K₃—\$.p.d.t. relay, 2500-ohm 7.2-ma. coil (Advance GHE/1C/2500).

L₁-3¾ turns No. 18 insulated wire on cold end of L₂; tapped 2 turns from graund end.

L₂-50 turns No. 24 tinned, 1¾ inches long on ¾inch diam. ceramic form; tapped 5, 8, 13

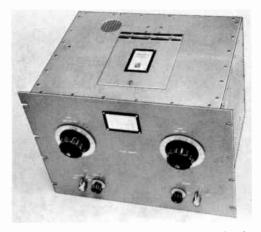


Fig. 6-79—This view of the amplifier shows the bandswitch trap daar, air-exhaust part and hale far adjusting neutralization, all in the tap of the shielding enclasure. The large knab an the left of the panel is for the 20/15/10-meter plate tuning capacitor, and the matching knob adjusts the capacitar used an 80 and 40. Farther down, fram left to right: grid band switch, grid tuning control, variable loading adjustment and loading switch.

and 25 turns from grid end. (Part of Harrington GP-20L).

L₃-3 turns No. 10 tinned, %-inch diam., 1 inch long, mounted an R₁.

L₄—Pi-netwark coil assembly (Air Dux 195-2 available fram Illumitronics Engineering, Sunnydale, Calif.); see text.

P₁-2-contact plug (Cinch-Jones P-202-CCT).

 R_1 =50-ohm 5-watt noninductive wire-wound (Sprague 5KT).

 R_6 , R_7 —10-watt adjustable.

R₉-200-watt adjustable; set tap at midpoint.

RFC₁-10-mh. r.f. choke (National R-50-I).

RFC₂-120-\(mu\)h. plate r.f. choke (Raypar RL-101).

RFC3-4-\(mu\)h. r.f. choke (National R-60).

RFC₄-2.5 mh. r.f. choke (National R-50).

S₁—Miniature ceramic rotary, 2 poles, 6 positions, 1 section, shorting, 5 positions used (Centralab PA-2002), Part of GP-20L.

 S_2 , S_3 —Homemade, see text and Fig. 6-82.

S₄—Ceramic rotary, 9 positions, 1 section, progressively shorting, 4 positions used (Centralab PISD section and P-270 index assembly).

S₈—S.p.d.t. microswitch (Unimax 2HBW-1).

S₆—S.p.s.t. lock switch (Arrow-Hart & Hegeman 81715-L).

S₇-S.p.s.t. toggle.

T₁-Filament transformer, 5.2 volts, c.t., 24 amp. (Triad F-11U).

T₂—Power transformer, 460 volts, c.t., 50 ma. (Stanco PC-8418).

T₃—Filament transformer, 5 volts c.t., 3 amp. (Thordarson 21FO3).

T₄-Power transformer, 1200 volts, c.t., 200 ma. (Thordarson 22R36).

T₈—Variable autotransformer, 0-132 volts, 1.75 amp. (Superior 10B).

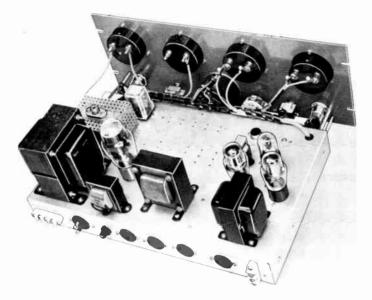


Fig. 6-80—Tap view of the cantral unit. The valtmeter multiplier resistars are haused in a cane-metal protective shield (upper left). Resistars R₈ and R₉ are maunted under the sets af ventilation hales (center near panel).

plate coil is tapped at 4 turns (0.4 μ h.) for 10 meters; 7.5 turns (1 μ h.) for 15 meters; 10.5 turns (2.33 μ h.) for 20 meters, 14 turns (5.2 μ h.) for 40 meters, and 24 turns (16.4 μ h.) for 80 meters. (All the figures include the 4-turn coil made of $\frac{1}{2}$ 6-incli strap.) The lugs provided with the tank coil assembly should be securely soldered to the coil at these points. Strapping should then be run from these taps to the appropriate bandswitch terminals. It should be noted that the

band-switch terminals do not progress in consecutive order, but are arranged to provide the shortest possible lead lengths.

Be sure no iron or steel hardware is used in the band-switch assembly, or for that matter, anywhere in the plate tank circuitry of the amplifier. Each piece of hardware should be checked first with a magnet to insure that it is neither iron nor steel before being used in the plate circuit.

In order to get to the band switch and capacitor


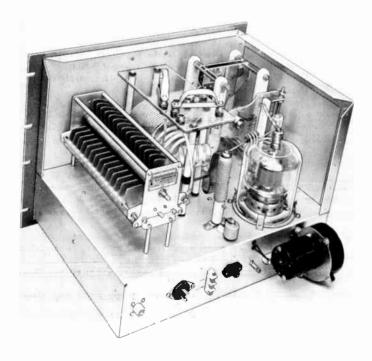


Fig. 6-81—Mast af the enclasure has been removed to show the low- and highfrequency plate tuning capacitars, the cail and bandswitch assembly (center) and the 4-400A in its glass chimney (Eimac SK-406). The neutralizing capacitar is behind the tube in this view. A cork gasket is used between chimney and chassis. Acrass the rear apran: output jack, filament a.c. plua. cathade and ground terminals, high-valtage cannector, graund post and blower. The blawer hides another terminal strip (far bias and screen cannections) and the input jack. The band switch Is made from a $4 \frac{1}{8} \times 8$ inch strip of 1/4-inch thick Lucite and Jahnson 108-760 jacks and 108-770 plugs. The plugs are mounted on two 31/8-inch utility handles (Bud UH-71A) strengthened by straps of aluminum.

Fig. 6-82—Bottom view of the amplifier. The Minibox shield has been removed from the grid circuit (lower right). Loading capacitors, switch and "safety" choke are at the left. The filament transformer is in the center. Amplifier tube socket is mounted on four tabs spaced evenly around the circular cutout.

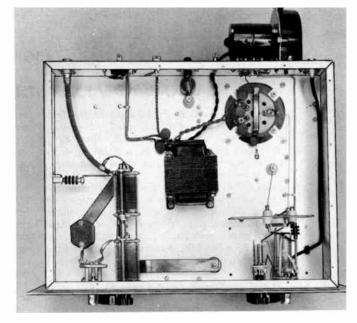

switch, a trap door is provided in the top of the enclosure. Microswitch S_5 is installed so that it is actuated by the trap door. The leads from S_5 are brought out to a jack, J_3 , located on the back wall of the enclosure, and from there to J_6 on the control unit. The trap door measures $6\frac{1}{4}$ by 7 inches and the rectangular cutout in the top of the enclosure is $4\frac{1}{8}$ by $6\frac{1}{4}$ inches. This provides adequate overlap to prevent any leakage of r.f.

Adjustment and Operation

First, determine that the control unit is operating correctly. Apply 115 volts to J_5 , insert the tubes, and turn on the key switch, S_6 . The green filament pilot light should go on immediately. There should also be power at receptacles J_7 , J_8 and J_9 . J_7 and J_9 are for the amplifier and plate supply filament transformers; J_8 , an accessory socket, is provided so that external equipment such as the station receiver can be controlled by S_6 . There should be no power at J_{10} , the plate transformer control socket.

Next, adjust R_6 until the VR tubes just begin to glow. Be sure the standby terminal jumper from Pin 5 of V_3 to ground is in place. Turning S_5 should change the bias from —150 volts in the Class AB₁ position to —225 volts for Class C in the other. With S_5 in the linear position (AB), and leaving a voltmeter on the output of the bias supply, temporarily lift the standby jumper from ground. The output voltage should rise from —150 to approximately —300 volts. The standby terminals provide a convenient way to bias the 4-400A beyond cutoff during standby and receiving periods. This will prevent any annoying diode noise generation.

Open S_6 and again connect an a.c. voltmeter to J_{10} . Put a temporary jumper between the two contacts of J_6 . Close S_6 and S_7 , and after 60 seconds there should be power at J_{10} and the red plate pilot lamp should light. Replace the jumper across J_6 with the leads from the microswitch interlock. Lifting the trap door should

deenergize J_{10} , and the plate pilot bulb should extinguish.

Next, connect a d.c. voltmeter to the output of the screen supply. By adjusting T_5 it should be possible to vary the output from 0 to approximately 850 volts. Finally, adjust R_7 so that K_3 trips when 40 ma. is drawn from the screen supply. This can be checked by connecting a resistor (620 ohms or less, 1 watt) across the supply output and running the voltage up from zero until the drain is 40 ma. This completes the testing of the control unit.

The amplifier must now be neutralized. Set the grid and plate band switches for 28 Mc., and disconnect the screen and plate leads at the amplifier terminals. Couple a sensitive indicating wavemeter to the output end of the plate tank circuit and apply the required -225 volts of bias. Apply drive, resonate the grid circuit and adjust the output of the exciter for rated 4-400A grid current. Neutralizing capacitor C2 should then be adjusted for minimum r.f. in the plate tank circuit. The plate tuning capacitor should be retuned for maximum wavemeter reading after each change of C2. After rated plate and screen voltages have been applied and the amplifier loaded, the neutralizing capacitor should be touched up so that minimum plate current and maximum grid and screen currents occur simultaneously as the plate tank is tuned through resonance.

If the amplifier is to be used for s.s.b., the h.v. power supply should have a minimum output capacitance of 8 \(\mu f\). For best voltage regulation the plate transformer should have a 220-volt primary. The output of the h.v. power supply should include a \(\frac{1}{2}\)-ampere fuse to protect the supply from excessive overloads.

If the amplifier is to be plate modulated, a choke, approximately 10 hy. at 50 or 100 ma., should be inserted in series with the screen lead of the 4-400A. An external switch can be used to short out the choke when using the amplifier for c.w. or s.s.b.

A TWO-BAND V.F.O. WITH DIFFERENTIAL KEYER

The v.f.o shown in Figs 6-83, 6-85 and 6-86 is intended to replace the 3.5- and 7-Mc. crystals used in many transmitters. It will deliver 30 to 50 volts on these two bands, sufficient to drive any normal crystal-oscillator stage as an amplifier or frequency multiplier. To simplify the addition of this v.f.o. to an existing transmitter, the v.f.o. includes a differential keying circuit that can be applied to any subsequent transmitter without modification. When used as a substitute for 80-meter crystals, the output of the v.f.o. unit is 3.5 to 40 Mc. When used as a substitute for 40-meter crystals, the output is 7.0 to 7.43 Mc.

Referring to the circuit diagram, Fig. 6-84, the oscillator uses a 12AT7 triode in the seriestuned Colpitts circuit. Actually two oscillators are included, one operating on 1.8 Mc. and the other on 3.5 Mc. Each triode and its associated tuning circuit is permanently connected, and the one to be used is switched on in the cathode circuit by switch $S_{1\text{A}}$. Another section of the switch, $S_{1\text{B}}$, shifts the differential keying lead to the active triode. The oscillator is followed by a cathode follower, $V_{2\text{A}}$, the triode section of a 6CX8. The cathode follower works with reduced plate voltage (200) obtained from a voltage divider that serves as a bleeder for the power

supply and also drops the screen voltage for the output stage. The output stage is the pentode section of the 6CX8. The bandswitch, S_1 , shorts out part of the output tuning coil for 40-meter operation.

The differential-keying circuit uses a d.p.d.t. relay. One arm of the relay keys the following transmitter in a normal manner, via J_2 and a length of cable. The other arm of the relay, K_{1A} , turns on the oscillator immediately the relay closes, but it doesn't turn off the oscillator immediately when the relay opens because the oscillator blocking bias, developed across a 10K resistor, is not available until the 0A3 conducts. The 0A3 does not conduct until the voltage across the 0.5-uf. capacitor has charged to about -100 volts, and it takes an appreciable fraction of a second for the capacitor to charge through the 100K resistor. Negative voltage for the circuit is obtained from a half-wave rectifier circuit using two small silicon rectifiers in series. The plate-voltage supply is conventional and uses a 5V4-GA rectifier and capacitor-input filter to deliver about 425 volts. A d.c. supply for the keying relay is obtained from the heater voltage and a half-wave rectifier. A d.c. relay was used for keying because it was found among the inexpensive relays that were tested, the d.c. relays

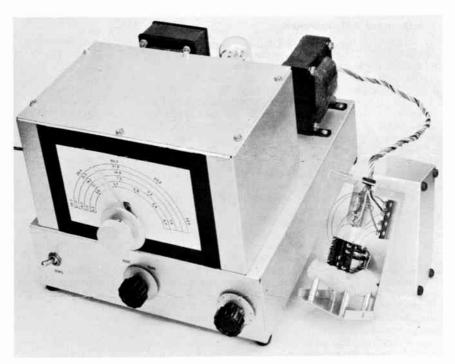


Fig. 6-83—The two-band v.f.o. provides suitable output to drive a former crystal-oscillator stage on 80 or 40 meters. A differential-keying circuit is included that requires no modification of the transmitter following the v.f.o.

The drive is a British planetary drive, with a plastic pointer added. The dial is paper, held in place by black electrical Scotch tape. Lower controls, from left to right, are frequency-spotting switch, band switch, and output peaking.

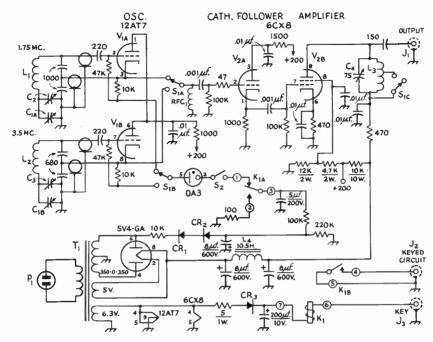


Fig. 6-84—Circuit diagram of the two-band v.f.o. Unless specified otherwise, resistances are in ohms, resistors are $\frac{1}{2}$ watt, capacitances are in $\mu\mu$ f. Fixed capacitors associated with V_1 are silvered mica, all decimal capacitors are ceramic, capacitors marked with polarity are electrolytic.

 C_1 —Originally 100- $\mu\mu$ f, per section dual variable (Johnson 167-53). C_{1A} section modified to have 7 stator and 6 rotor plates; C_{1B} section modified to have 4 stator and 4 rotor plates.

C₂—140-μμf. midget variable (Hammarlund APC-140).
 C₃—100-μμf. midget variable (Hammarlund APC-100).
 C₄—75-μμf. midget variable (Hammarlund APC-75-B).
 CR₁, CR₂—400 p.i.v. 200-ma. silicon rectifier (International Rectifier 2E4 or equiv.).

CR₃—25-v. 250-ma, selenium rectifier (International Rectifier C1H).

J₁, J₂, J₃—Phono jack.

K₁—D.p.d.t. relay, 6-v.d.c. coil (Potter & Brumfield KA-11D). Numbers on the leads correspond to socket (not shown) pin numbers.

keyed faster than the a.c.-actuated ones. The relay is mounted external to the v.f.o. proper, to reduce noise and vibration. No a.c. switch is included because it is assumed that the v.f.o. will obtain its a.c. from a source switched somewhere else. The power supply is fused in the line plug.

Construction

The v.f.o. is built on a $10 \times 12 \times 3$ -inch aluminum chassis. Since the aluminum from which the chassis is built is somewhat flexible, a strengthening rib of 1-inch aluminum angle is bolted across the 10-inch wide front of the chassis (see Fig. 6-85). The chassis is also strengthened by the $6 \times 9 \times 5$ -inch aluminum utility cabinet (Bud AU-1040) that serves as the shield compartment for the tuning capacitor, C_{1} , and

L₁-94 turns No. 24, 32 t.p.i., 1-inch diam. (B & W 3016).

L₂-47 turns No. 20, 16 t.p.i., 1-inch diam. (B & W 3015).

L₃-36 turns No. 24, 32 t.p.i., 1-inch diam. (B & W 3016). Tapped 14 turns from plate end.

L₄-10½-henry 110-ma. choke (Knight 62 G 139).

P₁—Fused (1½ amp.) line plug.

RFC₁-2.5 mh.

S₁—Two-section rotary switch, each section is 2-pole 6-position (2 used) steatite, total of 3 poles used (Centralab PA-301 index assembly with 2 PA-3 sections).

S2-S.p.s.t. toggle switch.

T₁—700 v.c.t. at 90 ma., 5 v. at 3 a., 6.3 v. at 3.5 a. (Knight 61 G 429).

the associated capacitors and inductors. A spare side of the utility box furnishes aluminum for several small brackets.

Care in construction of the v.f.o. will be rewarded by maximum stability. Of prime importance is the support of the tuning capacitor, C_1 . As can be seen in Fig. 6-86, the capacitor is supported above the chassis at each end by a suitable aluminum bracket. The front bracket is a shallow U-shaped one; one side of the U is the lip fastened to the chassis, and the other side of the U is a lip that supports C_2 and C_3 . The front of the capacitor is held to the bracket by the single-hole mounting provision of the capacitor. The rear bracket for the capacitor is bolted to the capacitor at two points, and a clearance hole is provided for the back bearing of the capacitor. The rotor of the capacitor is electrically con-

nected to the chassis via the front bracket only, and all connections to the chassis from the capacitors and lengths of coaxial cable (see Fig. 6-84) are made to the front rotor terminal of C_1 .

The drive for C_1 is a planetary reduction unit (Jackson Bros. Precision Planetary, available from Arrow Electronics, New York); a short length of $\frac{1}{2}$ -inch diameter rod and an insulated coupling (Millen 39016) connect the drive to the capacitor. Care spent in aligning the capacitor and the drive will be repaid by smooth operation and no backlash. Before installation, check the capacitor and make sure that it turns with reasonable torque. If it binds or is tight, free it by working, loosening the rear bearing slightly, or by oiling (rear bearing only!).

The mica capacitors across each tuned circuit are mounted on multiple tie points that are soldered to the stator supports of C_1 . Coils L_1 and L_2 are supported by sliding strips of sheet polystyrene into the coils and then cementing the strips to the insulating material in the coils. The strips are then supported 1 inch above the chassis by ceramic insulators (Johnson 135-501).

The location of the other components is not too critical, and a little study of Fig. 6-85 will show their location. Switch S_1 is mounted on an aluminum bracket, and the rectifier CR_8 is mounted on a ceramic standoff insulator. The inductor L_8 is mounted in the same manner as L_1 and L_2 , and the tap is made prior to final installation by pushing in two turns each side of the desired turn, thus leaving room for soldering a wire to the turn. Capacitor C_4 is supported by an aluminum bracket; its shaft is at plate d.c. potential and must be insulated from the chassis.

The relay K_1 is mounted on foam rubber in a small "Minibox." The stud of the relay is held to the rubber by a washer and nut, and the rubber is held to the box by screws at the corners. The stud of the relay, or any other part of the relay, must not touch the box. Flexible leads from the relay and its coil run through a rubber grommet to an octal plug (Amphenol 86-CP8 with 3-13 cap), which in turn is plugged into an octal socket at the rear of the v.f.o. In Fig. 6-84, numbers on the leads to the relay correspond to the pin numbers of the plug and socket.



Fig. 6-85—Under the chassis of the two-band v.f.o. Fixed capacitors at the upper right are filter capacitors for the power supply and a 0.5- μ f. capacitor used in the differential keying circuit. The socket for the relay connections mounted on the back wall of the chassis (right in this view), and the filter capacitor for the negative supply is at the bottom right. The lengths of coaxial cable running to the oscillator tube socket (seen below ceramic switch at center) are pieces of RG-58/U coming from the oscillator tuning compartment above the chassis. Their outer conductors are grounded to the chassis near the tube socket.

Adjustment

If the unit is properly wired, the only adjustment necessary will be that of C_2 and C_3 to bring the circuits into proper range. With C_1 fully meshed, set C_2 and C_3 so that the signal falls 5 to 10 kc. lower than 3.5 and 7.0 Mc. respectively. At the high ends (C_1 at minimum capacitance) the signal should be slightly higher than 4.0 and 7.425 Mc. The measurements should be made with the cover in place, although whether the cover is on or off should have very little effect on the frequency. The presence of the cover, securely fastened with sheet metal screws, does contribute to the over-all rigidity of the unit, however.

With nothing connected to J_1 , the output circuit should tune 3.5 and 7.0 Mc. with C_4 almost fully meshed. When a foot or two of coaxial line is used between J_1 and the transmitter to be driven, the setting of C_4 will be changed by the capacitance of the connecting line. If of necessity a long line must be used, it will be necessary to compensate by modification of the inductance of L_8 . RG-59/U has a capacitance of L_9 . RG-59/U has a capacitance of L_9 . PG-59/U has a capacitance of L_9 .

For an example of how the usual crystaloscillator circuit can be modified for use with this v.f.o., see the 75-watt transmitter earlier in this chapter.

Keying

When the v.f.o. is connected to a subsequent amplifier, the keying can be checked by opening S_2 , to allow the v.f.o. to run steadily. The keying can then be monitored and tested by the methods outlined in Chapter Eight. If the keying has strong key clicks, they should be reduced to a satisfactory level by the methods outlined. If a chirp is detected, it is a fault of the v.f.o. unit, and is probably caused by a severe line-voltage change or too much "pulling" through the 6CX8 stage. However, if the v.f.o. has been built carefully, it should be possible to swing C_4 through resonance without changing the frequency of the v.f.o., and this test will show that the buffer effect is adequate.

Once the keyed signal of the subsequent amplifier is satisfactory with S_2 open, the check for good differential keying can be made with S_2 closed. The keying should sound the same with S_2 open or closed, except that when S_2 is open a "back wave" will be heard locally. If the subsequent amplifier has more than one stage and two or more stages are keyed, no back wave should be heard in either position of S_2 .


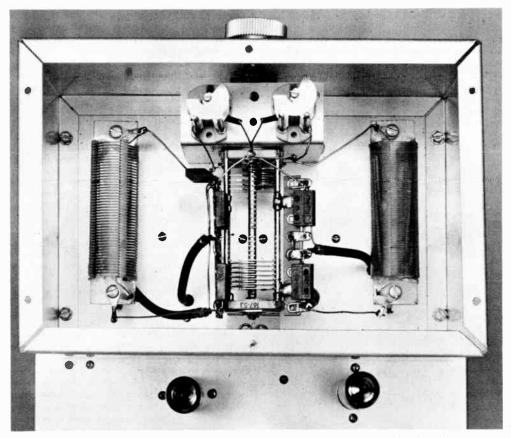


Fig. 6-86—Close-up view of the oscillator tuning compartment. Multiple tie points soldered to the tuning capacitor (center) provide rigid support for the silvered-mica capacitors. All ground (chassis) connections within this compartment are made to the front rotor connection; this includes the outer conductors of the coaxial line.

CONVERTING SURPLUS TRANSMITTERS FOR NOVICE USE

War-surplus radio equipment, available in many radio stores, is a good source of radio parts. Some of the transmitters and receivers can be made to operate in the amateur bands with little or no modification. It would be hard to find a more economical way for a Novice to get started on 40 or 80 meters than by adapting a normally-v.f.o.-controlled surplus "Command Set" to crystal control.

The "Command Sets" are parts of the SCR-274N and AN/ARC-5 equipments, transmitters and receivers designed for use in military aircraft. The two series are substantially identical in circuit and construction. Of the transmitters, two are of particular interest to the Novice. These are the BC-696 (part of 274N) or T19 (ARC-5) covering 3 to 4 Mc., and the BC-459 or T22. 7 to 9.1 Mc. The transmitter circuit consists of a 1626 triode variable-frequency oscillator that drives a pair of 1625s in parallel, which for Novice use can be run at 75 watts input. In addition to the 1626 and 1625s the transmitters include a 1629 magic-eye tube, which was used as a resonance indicator with a crystal for checking the dial calibration. The tubes have 12-volt heaters connected in series-parallel for 24-volt battery operation. The BC-696 and 459 are available from surplus dealers at prices ranging from five to fifteen dollars each, depending on condition.

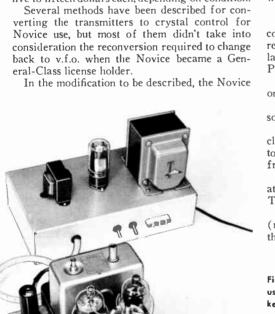

requirement for crystal control is met by using a separate crystal-controlled oscillator. The output of the external oscillator is fed into the transmitter through a plug that fits into the 1626 oscillator socket. The 1626 is not used. The transmitter modifications are such that when it is desired to restore the transmitter to v.f.o. operation the external oscillator is unplugged and the 1626 is put back in its socket. No wiring changes are needed to go from crystal control to v.f.o.

In addition to the external oscillator, a power supply is required for the oscillator and transmitter (Fig. 6-88), and certain wiring changes are needed to make the transmitter itself suitable for amateur use. These changes consist primarily of removing two relays, changing the tube heater circuit for operation on 12 volts instead of 24 volts, and the addition of a power plug.

Transmitter Modifications

The 80- and 40-meter transmitters are practically identical except for frequency range, and the modifications are the same in both. Remove the top cover and bottom plate. Remove the tubes and crystal from their sockets so there will be no danger of breaking them as you work on the transmitter. If the sockets are not marked by tube types, mark them yourself so you'll know which tube goes where.

The following modifications are required:

- 1) Remove the antenna relay (front panel) and control relay (side of chassis) and unsolder and remove all wires that were connected to the relays with the exception of the wire going to Pin 4 on the oscillator socket.
- 2) Remove the wire-wound resistor mounted on the rear wall of the transmitter.
- 3) Unsolder the wire from Pin 7 of the 1629 socket and move it to Pin 2. Ground Pin 7.
- 4) Unsolder the wires from Pin 1 of the 1625 closest to the drive shaft for the variable capacitors and solder the wires to Pin 7. Run a lead from the same Pin 1 to the nearest chassis ground.
- 5) Unsolder all leads from the power socket at the rear of the chassis and remove the socket. The socket can be pried off with a screwdriver.
- 6) Unsolder the end of the 20-ohm resistor (red-black-black) that is connected to Pin 4 on the oscillator socket and connect it to Pin 6

Fig. 6-87—The complete Novice setup, in this case using the 80-meter (BC-696) transmitter. Note the key jack at the lower-left corner of the transmitter panel. The crystal oscillatar is connected to the transmitter oscillator-tube socket with a shart length of cable terminating in an octal plug. A small notch should be cut in the transmitter caver to provide clearance for the cable when the cover is installed.

The power transformer, rectifier, and choke are mounted on top of the power-supply chassis at the rear, and the control switches are mounted on the wall as shown. Remaining components are underneath.

orld Radio History

Converting Surplus

of the calibration crystal socket. There is also a lead on Pin 4 that was connected to the keying relay; connect this lead to the nearest chassis ground point.

7) Mount an octal socket (Amphenol 78-RS8) in the hole formerly occupied by the power socket. Install a solder lug under one of the nuts holding the socket mounting.

8) Wire the octal socket as shown in Fig. 6-88. One of the leads unsoldered from the original power socket is red with a white tracer. This is the B+ lead for the 1625s. The yellow lead is the screen lead for the 1625s and the white lead is the heater lead. Although the manuals covering this equipment specify these colors, it's safer not to take them for granted; check where each lead actually goes before connecting it to the new power socket. The lead from Pin 1 on the power socket to Pin 6 on the calibration-crystal socket is the oscillator plate-voltage lead. The leads from Pins 7 and 8 on the power plug to Pins 1 and 6 on the oscillator socket are new leads to carry power to the external crystal-controlled oscillator. The lead from Pin 4 of the power socket to Pin 2 on the 1629 (resonance indicator) socket is the 12-volt heater lead.

9) Mount a closed-circuit phone jack at the lower left-hand corner of the front panel. Connect a lead from the ungrounded phone jack terminal to Pin 6 (cathode) of either of the 1625 sockets. This completes the modification.

Crystal-Controlled Oscillator Details

The external crystal-controlled oscillator circuit, shown in Fig. 6-89, uses a 6AG7 in the grid-plate oscillator circuit. Either 80- or 40-meter crystals are required, depending on the band in

R₁-25,000 ohms, 25 watts, with slider.
S₁, S₂-Single-pole, single-throw toggle switch.
T₁-Power transformer, 800 volts center-tapped, 200 ma.; 5 volts, 3 amp.; 6.3 volts, 6 amp. (Knight

61G414, Triad R-21A, or equivalent).

use. A tuned plate circuit is not required in the oscillator; it was found that more than adequate grid drive could be obtained with the setup as shown


Output from the oscillator is fed to the transmitter through an 8-inch length of RG-58 coax cable. The cable is terminated in an octal plug, P_2 , which is plugged into the oscillator tube socket in the transmitter. Power for the external oscillator is obtained through this socket.

The crystal-controlled oscillator is built in and on a $4 \times 2 \times 234$ -inch aluminum box. The tube and crystal sockets are mounted on top of the box and the remaining components inside. Layout of parts is not particularly critical but the general arrangement shown in Figs. 6-87 and 6-90 should be followed to insure good results.

In the completed setup, oscillator and amplifier, the cathodes of the 1625s are keyed and the crystal oscillator runs continuously during transmissions. It is thus necessary to turn the oscillator off during standby periods, and this is accomplished by opening the B-plus switch on the power supply. This method is used in preference to keying the oscillator and amplifier simultaneously because keying the oscillator is likely to make the signal chirpy. With amplifier keying the signal is a real T9X.

Power Supply

Fig. 6-88 shows the circuit of the power supply, which uses a 5U4G rectifier and a capacitor-input filter. The power transformer, T_1 , is a type made by several manufacturers. To obtain the necessary 12.6 volts for the heaters, a 6.3-volt filament transformer is connected in series with the 6.3-volt winding on T_1 . This setup also will

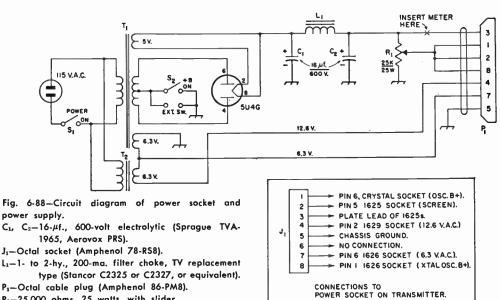

T₂—Filament transformer, 6.3 volts, 3 amp. (Triad F-16X, Knight 62-G-031, or equivalent).

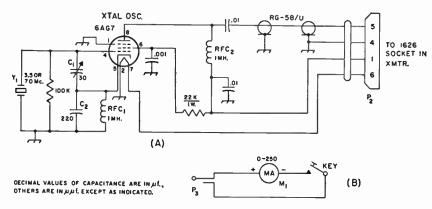


Fig. 6-89—(A) Circuit diagram of external crystal-controlled oscillator. Unless otherwise specified, resistances are in ohms, resistors are $\frac{1}{2}$ watt. The 0.01- and 0.001- μ f. capacitors are disk ceramic. (B) Method of connecting the milliammeter in series with the key.

 $C_1-3-30-\mu\mu f$. trimmer. $C_2-220-\mu\mu f$. fixed mica. $M_1-0-250$ d.c. milliammeter. P_2- Octal plug, male (Amphenol 86-PM8).

provide 6.3 volts for the heater of the 6AG7. Current requirement for the 6AG7 heater is 0.65 amp. and for the 1625s, 0.9 amp. total.

To turn off the plate voltages on the transmitter during stand-by periods, the center tap of T_1 is opened. This can be done in two ways; by S_2 , or by a remotely-mounted switch whose leads are connected in parallel with S_2 . A two-terminal strip is mounted on the power-supply chassis, the terminals being connected to S_2 which is also on the chassis. The remotely-mounted switch can be installed in any convenient location at the operating position. A single-pole, single-throw switch can be used for this purpose or, if desired, a multicontact switch can be used to perform simultaneously this and other functions, such as controlling an antenna-changeover relay.

The high-voltage and heater leads are brought out in a cable to an octal plug, P_1 , that connects to J_1 on the transmitter. The length of the cable will, of course, depend on where you want to install the power supply. Some amateurs prefer to have the supply on the floor under the operating desk rather than have it take up room at the operating position.

The supply shown here was constructed on a $3 \times 6 \times 10$ -inch chassis. The layout is not critical, nor are there any special precautions to take during construction other than to observe polarity in wiring the electrolytic capacitors and to see that the power leads are properly insulated. Never have P_1 unplugged from J_1 when the power supply is turned on; there is danger of electrical shock at several pins of P_1 . Interchanging the inserts of P_1 and J_1 will remove this hazard.

When wiring P_1 don't connect the B-plus lines to Pins 2 or 3, the amplifier plates and screens, at first. It is more convenient to test the oscillator without plate and screen voltages on the amplifier.

When the supply is completed, check between

 $P_3-Phone$ plug. $RFC_1,\,RFC_2-1-mh.\,\,r.f.$ chokes. $Y_1-3.5-$ or 7-Mc. Novice-band crystal, as required.

chassis ground and the 12.6-volt lead with an a.c. voltmeter to see if the two 6.3-volt windings are connected correctly. If you find that the voltage is zero, reverse one of the windings. If you don't have an a.c. meter you can check by observing the heaters in the 1625s. They will light up if you have the windings connected correctly. Incidentally, leave B plus off, by opening S_2 , for this check.

Next, set the slider on the bleeder resistor, R_1 , at about one-quarter of the total resistor length, measured from the B-plus end of the bleeder. Be sure to turn off the power when making this adjustment. With the tap set about one-quarter of the way from the B-plus end of the bleeder the oscillator plate and amplifier screen voltages will be approximately 250 volts.

Testing the Transmitter

A key and meter connected as shown in Fig. 6-89 are needed for checking the transmitter. When P_3 is plugged into the jack in the transmitter it will measure the cathode current of the 1625s. The cathode current is the sum of the plate, screen and control-grid currents. Some amateurs prefer to install the meter in the plate lead so it reads plate current only. This can be done by opening the B-plus line at the point marked "X" in Fig. 6-88, and inserting the meter in series with the line. However, unless more than one meter is available, don't install it in the power supply setup in this way until after the tests described below have been made.

Insert the external oscillator plug, P_2 , into the 1626 socket and connect P_1 to the transmitter. Plug P_1 into the key jack on the front panel of the transmitter. With S_2 open, turn on the power and allow a minute or two for the tubes to warm up. Next, close the center-tap connection, S_2 , on the power transformer. Set the transmitter dial to the same frequency as that of the crystal in

Converting Surplus

use and close the key. A slight indication of grid current should show on the meter. There is no plate or screen current because there are no screen or plate voltages on the amplifier. If no grid current is obtained, adjust C_1 until grid current shows, or try another crystal.

The next step is to peak the amplifier grid circuit — that is, the 1626 v.f.o tank — for maximum grid-current reading. The v.f.o. trimmer capacitor is in an aluminum box on the top of the chassis at the rear. There is a ½-inch diameter hole in the side of the box; loosen the small screw visible through this hole, thus unlocking the rotor shaft of the trimmer capacitor. Move the rotor-arm shaft in either direction, observing the meter reading, and find the position that gives the highest reading. This should be something more than 10 ma.

Now connect the plate and screen voltage leads to P_1 . Be sure to turn off the power supply before making the connections!

The first test of the rig should be with a dummy load; a 115-volt, 60-watt light bulb can be used for this purpose. The lamp should be connected between the antenna terminal and chassis ground. However, to make the lamp take power it may be necessary to add capacitance in parallel with it. A receiving-type variable capacitor having 250 µµf. or more maximum capacitance will be adequate for the job.

Turn on the power and allow the tubes to warm up, but leave the key open. Set the antenna coupling control on the transmitter to 7 or 8, and set the variable capacitor connected across the dummy load to about maximum capacitance. Next, close the key and adjust the antenna inductance control for an increase in cathode current. Turn the frequency control for a dip in current reading. The indicated frequency will probably differ from that of the crystal in use, but don't worry about it.

Adjust the three transmitter controls, antenna inductance, antenna coupling, and frequency, along with the variable capacitor across the lamp load, until the lamp lights up to apparently full brilliance. The cathode current should be between 150 and 200 ma. With the transmitter fully loaded, adjust C_1 in the crystal oscillator so that the lamp brilliance just starts to decrease. This is the optimum setting for C_1 and no further adjustments are required.

If a d.c. voltmeter is available, check the different voltages in the setup. Using the power supply shown here, the plate voltage on the 1625s is approximately 400 with the amplifier fully loaded. With the plate voltage on the oscillator and screen voltage on the 1625s adjusted to 250 volts (tap on R_1), the oscillator screen voltage is 160 volts. The oscillator takes approximately 30 ma. and the 1625 amplifier screens about 10 ma. when the amplifier is fully loaded.

Getting on the Air

To put the transmitter on the air it is necessary only to connect an antenna to the antenna post and connect a ground lead from the transmitter chassis to a water-pipe ground or to a metal stake driven in the ground. Almost any length of antenna will work, but for best results the minimum length should not be less than about ½8 wavelength for the band in use. This is approximately 33 feet for 80 meters and 16 feet for 40 meters. It is of course better to make the antenna longer — and to be sure to get the far end as high as possible.

An output indicator will prove to be a handy device for knowing when power is actually going into the antenna. For this purpose use a 6.3-volt, 150-ma. dial lamp. Connect two leads, each about one foot long, to the shell and base of the bulb, respectively. Clip one lead to the antenna post and the other lead on the antenna wire two feet from antenna post. A small amount of power will go through the bulb and this will provide a visual indication of output. Follow the same tuning procedure as outlined above for the dummy antenna. If the bulb gets so bright that it is in danger of burning out, move the leads closer together to reduce the pickup.

It may be found that certain antenna lengths won't work — that is, the amplifier won't load — no matter where the antenna coupling and inductance are set. In such a case, connect a variable capacitor — like the one used with the lamp dummy — between the antenna post and the transmitter chassis. Adjust the capacitor and antenna inductance for maximum brilliance of the output indicator.

A superior antenna system uses a two-wire feeder system and an antenna coupler; examples are given in Chapters 13 and 14. If a coupler is used, the transmitter and coupler should be connected together with coax line. The inner conductor of the coax should be connected to the antenna terminal and the outer braid to the transmitter case, as close to the antenna terminal as possible. If desired, the antenna terminal can be removed and a coax fitting substituted.

When the coveted General Class ticket is obtained, it is only necessary to unplug the crystal oscillator, put the original tube back in the rig, and move out of the Novice band.

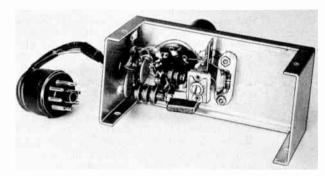


Fig. 6-90—This bottom view of the crystal oscillator shows the arrangement of components. Terminal strips are used for the cable connections and also as a support for C₁, the feedback capacitor.

Power Supplies

Essentially pure direct-current plate supply is required to prevent serious hum in the output of receivers, speech amplifiers, modulators and transmitters. In the case of transmitters, pure d.c. plate supply is also dictated by government regulation.


The filaments of tubes in a transmitter or modulator usually may be operated from a.c. However, the filament power for tubes in a receiver (excepting power audio tubes), or those in a speech amplifier may be a.c. only if the tubes are of the indirectly-heated-cathode type, if hum is to be avoided.

Wherever commercial a.c. lines are available, high-voltage d.c. plate supply is most cheaply and conveniently obtained by the use of a transformer-rectifier-filter system. A typical power supply is shown in Fig. 7-1.

In this system, the plate transformer, T_1 , steps up the a.c. line voltage to the required high voltage.

The a.c. is changed to pulsating d.c. by the rectifiers, V_1 and V_2 . Pulsations in the d.c. appearing at the output of the rectifier (points A and B) are smoothed out by the filter composed of L_1 and C_1 . R_1 is a bleeder resistor. Its chief function is to discharge C_1 , as a safety measure, after the supply is turned off. By proper selection of value,

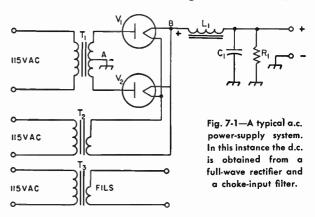 R_1 also helps to minimize changes in output voltage with changes in the amount of current drawn from the supply. T_2 is a step-down transformer to provide filament voltage for the rectifier tubes. It must have sufficient insulation between the filament winding and the core and pri-



mary winding to withstand the peak value of the rectified voltage. T_s is a similar transformer to supply the filaments or heaters of the tubes in the equipment operating from the supply. Frequently these three transformers are combined in a single unit having the 115-volt primary winding and the three secondary windings on one core.

RECTIFIER CIRCUITS

Half-Wave Rectifier

Fig. 7-2 shows three rectifier circuits covering most of the common applications in amateur equipment. Fig. 7-2A is the circuit of a half-wave rectifier. During that half of the a.c. cycle when the rectifier plate is positive with respect to the cathode (or filament), current will flow through the rectifier and load. But during the other half of the cycle, when the plate is negative with respect to the cathode, no current can flow. The shape of the output wave is shown in (A) at the right. It shows that the current always flows in the same direction but that the flow of current is not continuous and is pulsating in amplitude.

The average output voltage—the voltage read by the usual d.c. voltmeter—with this circuit is 0.45 times the r.m.s. value of the a.c. voltage delivered by the transformer secondary. Because the frequency of the pulses in the output wave is relatively low (one pulsation per cycle), consid-

erable filtering is required to provide adequately smooth d.c. output, and for this reason this circuit is usually limited to applications where the current involved is small, such as in supplies for cathode-ray tubes and for protective bias in a transmitter.

Another disadvantage of the half-wave rectifier circuit is that the transformer must have a considerably higher primary volt-ampere rating (approximately 40 per cent greater), for the same d.c. power output, than in other rectifier circuits.

Full-Wave Center-Tap Rectifier

The most universally used rectifier circuit is shown in Fig. 7-2B. Being essentially an arrangement in which the outputs of two half-wave rectifiers are combined, it makes use of both halves of the a.c. cycle. A transformer with a centertapped secondary is required with the circuit. When the plate of V_1 is positive, current flows through the load to the center tap. Current can-

not flow through V_2 because at this instant its cathode (or filament) is positive in respect to its plate. When the polarity reverses, V_2 conducts and current again flows through the load to the center-tap, this time through V_2

The average output voltage is 0.45 times the r.m.s. voltage of the entire transformersecondary, or 0.9 times the voltage across half of the transformer secondary. For the same total secondary voltage, the average output voltage is the same as that delivered with a half-wave rectifier. However, as can be seen from the sketches of the output wave form in (B) to the right, the frequency of the output pulses is twice that of the half-wave rectifier. Therefore much less filtering is required. Since the rectifiers work alternately, each handles half of the average load current. Therefore the loadcurrent rating of each rectifier need be only half the total load current drawn from the supply.

Two separate transformers, with their primaries connected in parallel and secondaries connected in series (with the proper polarity) may be used in this circuit. However, if this substitution is made, the primary volt-ampere rating must be reduced to about 40 per cent less than twice the rating of one transformer.

Full-Wave Bridge Rectifier

Another full-wave rectifier circuit is shown in Fig. 7-2C. In this arrangement, two rectifiers operate in series on each half of the cycle, one rectifier being in the lead to the load, the other being in the return lead. Over that portion of the cycle when the upper end of the transformer secondary is positive with respect to the other end, current flows through V_1 , through the load and thence through V_2 . During this period current cannot flow through rectifier V_4 because its plate is negative with respect to its cathode (or filament). Over the other half of the cycle, current flows through V_4 , through the load and

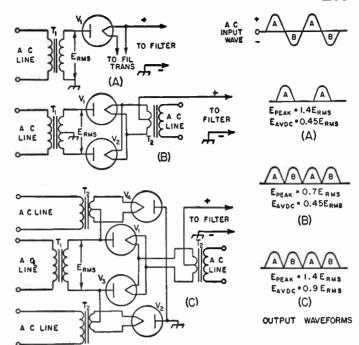


Fig. 7-2—Fundamental vacuum-tube rectifier circuits. A—Half-wave. B—Full-wave. C—Full-wave bridge. A.c.-input and pulsating-d.c. output wave forms are shown at the right. Output-voltage values indicated do not include rectifier drops. Other types of rectifiers may be substituted.

thence through V_4 . Three filament windings are needed-one for V1 and V8 and one each for V_3 and V_4 . The output wave shape (C), to the right, is the same as that from the simple center-tap rectifier circuit. The output voltage obtainable with this circuit is 0.9 times the r.m.s. voltage delivered by the transformer secondary. For the same total transformer-secondary voltage, the average output voltage when using the bridge rectifier will be twice that obtainable with the center-tap rectifier circuit. However, when comparing rectifier circuits for use with the same transformer, it should be remembered that the power which a given transformer will handle remains the same regardless of the rectifier circuit used. If the output voltage is doubled by substituting the bridge circuit for the center-tap rectifier circuit, only half the rated load current can be taken from the transformer without exceeding its normal rating. Each rectifier in a bridge circuit should have a minimum load-current rating of one half the total load current to be drawn from the supply.

Rectifiers

High-Vacuum Rectifiers

High-vacuum rectifiers depend entirely upon the thermionic emission from a heated filament and are characterized by a relatively high internal resistance. For this reason, their application usually is limited to low power, although there are a few types designed for medium and high power in cases where the relatively high internal voltage drop may be tolerated. This high internal resistance make them less susceptible to damage from temporary overload and they are free from the bothersome electrical noise sometimes associated with other types of rectifiers.

Some rectifiers of the high-vacuum full-wave type in the so-called receiver-tube class will handle up to 275 ma. at 400 to 500 volts d.c. output. Those in the higher-power class can be used to handle up to 500 ma. at 2000 volts d.c. in full-wave circuits. Most low-power high-vacuum rectifiers are produced in the full-wave type, while those for greater power are invariably of the half-wave type, two tubes being required for a full-wave rectifier circuit. A few of the lower-voltage types have indirectly heated cathodes, but are limited in heater-to-cathode voltage rating.

Mercury-Vapor Rectifiers

The voltage drop through a mercury-vapor rectifier is practically constant at approximately 15 volts regardless of the load current. For high power they have the advantage of cheapness. Rectifiers of this type, however, have a tendency toward a type of oscillation which produces noise in nearby receivers, sometimes difficult to eliminate. R.f. filtering in the primary circuit and at the rectifier plates as well as shielding may be required. As with high-vacuum rectifiers, full-wave types are available in the lower-power ratings only. For higher power, two tubes are required in a full-wave circuit.

Selenium and Other Semiconductor Rectifiers

Selenium, germanium and silicon rectifiers are finding increasing application in power supplies for amateur equipment. These units have the advantages of compactness, low internal voltage drop (about 5 volts per unit) and low operating temperature. Also, no filament transformers are required.

Individual units of all three types are available with input ratings of 130 volts r.m.s. Selenium units are rated at up to 1000 ma. or more d.c. load current; germanium units have ratings up to 400 ma., and silicon units up to several amperes. In full-wave circuits these load-current figures can be doubled.

The extreme compactness of silicon types makes feasible the stacking of several units in series for higher voltages. Standard stacks are available that will handle up to 2000 volts r.m.s. input at a d.c. load current of 325 ma. Two of these stacks in a full-wave circuit will handle 650 ma., although they are comparatively expensive.

Semiconductor rectifiers may be substituted in any of the basic circuits shown in Fig. 7-2, the terminal marked "+" or "cathode" corresponding to the filament connection. Advantage may be taken of the voltage-multiplying circuits discussed in a later section of this chapter in adapting rectifiers of this type.

Rectifier Ratings

All rectifiers are subject to limitations as to breakdown voltage and current-handling capability. Some tube types are rated in terms of the maximum r.m.s. voltage that should be applied to the rectifier plate. This is sometimes dependent

on whether a choke- or capacitive-input filter is used. Others, particularly mercury-vapor and semiconductor types, are rated according to maximum peak inverse voltage (p.i.v.)—the peak voltage between anode and cathode while the rectifier is not conducting. In the circuits of Fig. 7-2, the p.i.v. across each rectifier is 1.4 times the r.m.s. value of the voltage delivered by the entire transformer secondary, except that if a capacitive-input filter is used with the half-wave rectifier circuit of Fig. 7-2A, the multiplying factor becomes 2.8.

Rectifiers are rated also as to maximum d.c. load current, and some may carry peak-current ratings in addition. To assure normal life, all ratings should be carefully observed. Staying within their ratings, rectifiers will deliver more current at a given output voltage with a chokeinput filter than with capacitor input. However a higher a.c. voltage is required when the chokeinput filter is used.


Operation of Rectifiers

In operating rectifiers requiring filament or cathode heating, care should be taken to provide the correct filament voltage at the tube terminals. Low filament voltage can cause excessive voltage drop in high-vacuum rectifiers and a considerable reduction in the inverse peak-voltage rating of a mercury-vapor tube. Filament connections to the rectifier socket should be firmly soldered, particularly in the case of the larger mercuryvapor tubes whose filaments operate at low voltage and high current. The socket should be selected with care, not only as to contact surface but also as to insulation, since the filament usually is at full output voltage to ground. Bakelite sockets will serve at voltages up to 500 or so, but ceramic sockets, well spaced from the chassis, always should be used at the higher voltages. Special filament transformers with high-voltage insulation between primary and secondary are required for rectifiers operating at potentials in excess of 1000 volts inverse peak.

The rectifier tubes should be placed in the equipment with adequate space surrounding them to provide for ventilation. When mercury-vapor tubes are first placed in service, and each time after the mercury has been disturbed, as by removal from the socket to a horizontal position, they should be run with filament voltage only for 30 minutes before applying high voltage. After that, a delay of 30 seconds is recommended each time the filament is turned on.

Rectifiers may be connected in parallel for current higher than the rated current of a single

Fig. 7-3—Connecting mercury-vapor rectifiers in parallel for heavier currents. R₁ and R₂ should have the same value, between 50 and 100 ohms, and corresponding filament terminals should be connected together.

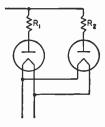

Filters

unit. This includes the use of the sections of a double diode for this purpose. With mercury-vapor types, equalizing resistors of 50 to 100 ohms

should be connected in series with each plate, as shown in Fig. 7-3, to help maintain an equal division of current between the two rectifiers.

FILTERS

The pulsating d.c. waves from the rectifiers shown in Fig. 7-2 are not sufficiently constant in amplitude to prevent hum corresponding to the pulsations. Filters consisting of capacitances and inductances are required between the rectifier and the load to smooth out the pulsations to an essentially constant d.c. voltage. Also, upon the design of the filter depends to a large extent the d.c. voltage output, the voltage regulation of the power supply and the maximum load current that can be drawn from the supply without exceeding the peak-current rating of the rectifier.

Power-supply filters fall into two classifications, depending upon whether the first filter element following the rectifier is a capacitor or a choke. Capacitive-input filters are characterized by relatively high output voltage in respect to the transformer voltage, but poor voltage regulation. Choke-input filters result in much better regulation, when properly designed, but the output voltage is less than would be obtained with a capacitive-input filter from the same transformer.

Voltage Regulation

The output voltage of a power supply always decreases as more current is drawn, not only because of increased voltage drops on the transformer, filter chokes and the rectifier (if high-vacuum rectifiers are used) but also because the output voltage at light loads tends to soar to the peak value of the transformer voltage as a result of charging the first capacitor. By proper filter design the latter effect can be eliminated. The change in output voltage with load is called voltage regulation and is expressed as a percentage.

Per cent regulation =
$$\frac{100 (E_1 - E_2)}{E_2}$$

Example: No-load voltage = E_1 = 1550 volts. Full-load voltage = E_2 = 1230 volts. Percentage regulation = $\frac{100 (1550 - 1230)}{1230}$

 $=\frac{32,000}{1230}$ =26 per cent.

Regulation may be as great as 100% or more with a capacitive-input filter, but by proper design can be held to 20% or less with a choke-input filter.

Good regulation is desirable if the load current varies during operation, as in a keyed stage or a Class B modulator, because a large change in voltage may increase the tendency toward key clicks in the former case or distortion in the latter. On the other hand, a steady load, such as is represented by a receiver, speech amplifier or unkeyed stages in a transmitter, does not require good regulation so long as the proper voltage is obtained under load conditions. Another consideration that makes good voltage regulation desirable is that the filter capacitors must have a voltage rating safe for the highest value to which

the voltage will soar when the external load is removed.

When essentially constant voltage, regardless of current variation is required (for stabilizing an oscillator, for example), special voltage-regulating circuits described elsewhere in this chapter are used.

Load Resistance

In discussing the performance of power-supply filters, it is sometimes convenient to express the load connected to the output terminals of the supply in terms of resistance. The load resistance is equal to the output voltage divided by the total current drawn, including the current drawn by the bleeder resistor.

Input Resistance

The sum of the transformer impedance and the rectifier resistance is called the input resistance. The approximate transformer impedance is given by

$$Z_{\text{TR}} = N^2 R_{\text{PRI}} + R_{\text{SEO}}$$

where N is the transformer turns ratio, primary to secondary (primary to ½ secondary in the case of a full-wave rectifier), and R_{PRI} and R_{SEO} are the primary and secondary resistances respectively. R_{SEO} will be the resistance of half of the secondary in the case of a full-wave circuit.

Bleeder

A bleeder resistor is a resistance connected across the output terminals of the power supply (see Fig. 7-7). Its functions are to discharge the filter capacitors as a safety measure when the power is turned off and to improve voltage regulation by providing a minimum load resistance. When voltage regulation is not of importance, the resistance may be as high as 100 ohms per volt. The resistance value to be used for voltage-regulating purposes is discussed in later sections. From the consideration of safety, the power rating of the resistor should be as conservative as possible, since a burned-out bleeder resistor is more dangerous than none at all!

Ripple Frequency and Voltage

The pulsations in the output of the rectifier can be considered to be the resultant of an alternating current superimposed upon a steady direct current. From this viewpoint, the filter may be considered to consist of shunting capacitors which short-circuit the a.c. component while not interfering with the flow of the d.c. component, and series chokes which pass d.c. readily but which impede the flow of the a.c. component.

The alternating component is called the ripple. The effectiveness of the filter can be expressed in terms of per cent ripple, which is the ratio of the r.m.s. value of the ripple to the d.c. value in terms of percentage. For c.w. transmitters, the output ripple from the power supply should not exceed 5 per cent. The ripple in the output of supplies for voice transmitters should not exceed 1 per cent. Class B modulators require a ripple reduction to about 0.25%, while v.f.o.'s, high-gain speech amplifiers, and receivers may require a reduction in ripple to 0.01%.

Ripple frequency is the frequency of the pulsations in the rectifier output wave—the number of pulsations per second. The frequency of the ripple with half-wave rectifiers is the same as the frequency of the line supply—60 cycles with 60-cycle supply. Since the output pulses are doubled with a full-wave rectifier, the ripple frequency is doubled—to 120 cycles with 60-cycle supply.

The amount of filtering (values of inductance and capacitance) required to give adequate smoothing depends upon the ripple frequency, more filtering being required as the ripple frequency is lowered.

CAPACITIVE-INPUT FILTERS

Capacitive-input filter systems are shown in Fig. 7-4. Disregarding voltage drops in the chokes, all have the same characteristics except

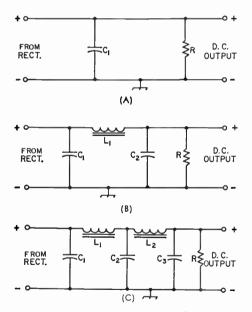


Fig. 7-4—Capacitive-input filter circuits. A—Simple capacitive. B—Single-section. C—Double-section.

in respect to ripple. Better ripple reduction will be obtained when *LC* sections are added, as shown in Figs. 7-4B and C.

Output Voltage

To determine the approximate d.c. voltage output when a capacitive-input filter is used, reference should be made to the graph of Fig. 7-5.

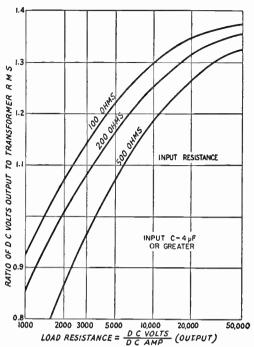


Fig. 7-5—Chart showing approximate ratio of d.c. output voltage across filter input capacitor to transformer r.m.s. secondary voltage for different load and input resistances.

Example:
Transformer r.m.s. voltage — 350
Input resistance — 200 ohms
Maximum load current, including bleeder
current — 175 ma.

Load resistance = $\frac{350}{0.175}$ = 2000 ohms approx.

From Fig. 7-5, for a load resistance of 2000 ohms and an input resistance of 200 ohms, the d.c. output voltage is given as slightly over 1 times the transformer r.m.s. voltage, or about 350 volts.

Regulation

If a bleeder resistance of 50,000 ohms is used, the d.c. output voltage, as shown in Fig. 7-5, will rise to about 1.35 times the transformer r.m.s. value, or about 470 volts, when the external load is removed. For greater accuracy, the voltage drops through the input resistance and the resistance of the chokes should be subtracted from the values determined above. For best regulation with a capacitive-input filter, the bleeder resistance should be as low as possible without exceeding the transformer, rectifier or choke ratings when the external load is connected.

Maximum Rectifier Current

The maximum current that can be drawn from a supply with a capacitive-input filter without exceeding the peak-current rating of the rectifier may be estimated from the graph of Fig. 7-6. Using values from the preceding example, the ratio of peak rectifier current to d.c. load current

Filters 223

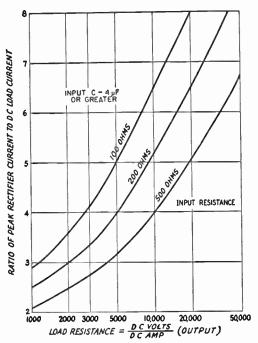


Fig. 7-6—Graph showing the relationship between the d.c. load current and the rectifier peak plate current with capacitive input for various values of load and input resistance.

for 2000 ohms, as shown in Fig. 7-6 is 3. Therefore, the maximum load current that can be drawn without exceeding the rectifier rating is $\frac{1}{3}$ the peak rating of the rectifier. For a load current of 175 ma., as above, the rectifier peak current rating should be at least $3 \times 175 = 525$ ma.

With bleeder current only, Fig. 7-6 shows that the ratio will increase to over 8. But since the bleeder draws less than 10 ma. d.c., the rectifier peak current will be only 90 ma. or less.

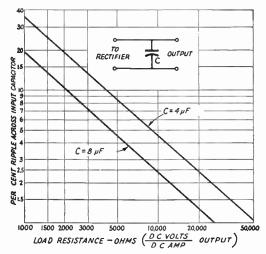


Fig. 7-7—Showing approximate 120-cycle percentage ripple across filter input capacitor for various loads.

Ripple Filtering

The approximate ripple percentage after the simple capacitive filter of Fig. 7-4A may be determined from Fig. 7-7. With a load resistance of 2000 ohms, for instance, the ripple will be approximately 10% with an 8- μ f. capacitor or 20% with a 4- μ f. capacitor. For other capacitances, the ripple will be in inverse proportion to the capacitance, e.g., 5% with 16 μ f., 40% with 2 μ f., and so forth.

The ripple can be reduced further by the addition of LC sections as shown in Figs. 7-4B and C. Fig. 7-8 shows the factor by which the ripple from any preceding section is reduced depending on the product of the capacitance and inductance added. For instance, if a section composed of a choke of 5 h. and a capacitor of 4 μ f. were to be added to the simple capacitor of Fig. 7-4A, the product is $4 \times 5 = 20$. Fig. 7-8 shows that the original ripple (10% as above with 8 μ f. for example) will be reduced by a factor of about 0.09. Therefore the ripple percentage after the new section will be approximately $0.09 \times 10 = 0.9\%$. If another section is added to the filter, its reduction factor from Fig. 7-8 will be applied to the

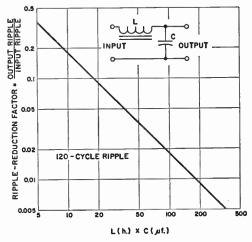


Fig. 7-8—Ripple-reduction factor for various values of L and C in filter section. Output ripple = input ripple × ripple factor.


0.9% from the preceding section; $0.9 \times 0.09 = 0.081\%$ (if the second section has the same *LC* product as the first).

CHOKE-INPUT FILTERS

Much better voltage regulation results when a choke-input filter, as shown in Fig. 7-9, is used. Choke input also permits better utilization of the rectifier, since a higher load current usually can be drawn without exceeding the peak current rating of the rectifier.

Minimum Choke Inductance

A choke-input filter will tend to act as a capacitive-input filter unless the input choke has at

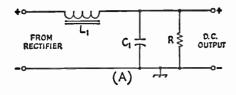

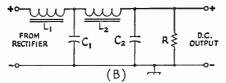


Fig. 7-9—Choke-input filter circuits. A—Single-section.

B—Double-section.

least a certain minimum value of inductance called the **critical** value. This critical value is given by

$$L_{\rm h} = \frac{E_{\rm VOLTS}}{I_{\rm MA}}$$

where E is the output voltage of the supply, and I is the current being drawn from the supply.

If the choke has at least the critical value, the output voltage will be limited to the average value of the rectified wave at the input to the choke (see Fig. 7-2) when the current drawn from the supply is small. This is in contrast to the capacitive-input filter in which the output voltage tends to soar toward the peak value of the rectified wave at light loads. Also, if the input choke has at least the critical value, the rectifier peak plate current will be limited to about twice the d.c. current drawn from the supply. Most rectifier tubes have peak-current ratings of three to four times their maximum d.c. output-current ratings. Therefore, with an input choke of at least critical inductance, current up to the maximum output-current rating of the rectifier may be drawn from the supply without exceeding the peak-current rating of the rectifier.

Minimum-Load-Bleeder Resistance

From the formula above for critical inductance, it is obvious that if no current is drawn from the supply, the critical inductance will be infinite. So that a practical value of inductance may be used, some current must be drawn from the supply at all times the supply is in use. From the formula we find that this minimum value of current is

$$I_{\text{MA.}} = \frac{E_{\text{VOLTS}}}{L_{\text{h}}}$$

Thus, if the choke has an inductance of 20 h., and the output voltage is 2000, the minimum load current should be 100 ma. This load may be provided, for example, by transmitter stages that draw current continuously (stages that are not keyed). However, in the majority of cases it will be most convenient to adjust the bleeder resistance so that the bleeder will draw the required minimum current. In the above example, the bleeder resistance should be 2000/0.1 = 20,000 ohms.

From the formula for critical inductance, it is seen that when more current is drawn from the supply, the critical inductance becomes less. Thus, as an example, when the total current, including the 100 ma. drawn by the bleeder rises to 400 ma., the choke need have an inductance of only 5 h. to maintain the critical value. This is fortunate, because chokes having the required inductance for the bleeder load only and that will maintain this value of inductance for much larger

Swinging Chokes

currents are very expensive.

Less costly chokes are available that will maintain at least critical value of inductance over the range of current likely to be drawn from practical supplies. These chokes are called swinging chokes. As an example, a swinging choke may have an inductance rating of 5/25 h, and a current rating of 225 ma. If the supply delivers 1000 volts, the minimum load current should be 1000/25 = 40 ma. When the full load current of 225 ma, is drawn from the supply, the inductance will drop to 5 h. The critical inductance for 225 ma. at 1000 volts is 1000/225 = 4.5 h. Therefore the 5/25-h. choke maintains at least the critical inductance at the full current rating of 225 ma. At all load currents between 40 ma. and 225 ma., the choke will adjust its inductance to at least the approximate critical value.

Table 7-I shows the maximum supply output voltage that can be used with commonly-available swinging chokes to maintain critical inductance at the maximum current rating of the choke. These chokes will also maintain critical inductance for any lower values of voltage, or current down to the required minimum drawn by a proper bleeder as discussed above.

In the case of supplies for higher voltages in particular, the limitation on maximum load re-

TABLE 7-I						
	Max. ma.	Max.	Max. R1	Min. ma.2		
3.5/13.5	150	525	13.5K	39		
5/25	175	875	25K	35		
2/12	200	400	12K	33		
5/25	200	1000	25K.	40		
5/25	225	1125	25K	45		
2/12	250	500	12K	42		
4/20	300	1200	20 K	60		
5/25	300	1500	25 K	60		
3/17	400	1200	17K	71		
4/20	400	1600	20K	80		
5/25	400	2000	25K	80		
4/16	500	2000	16K	125		
5/25	500	2500	25K	100		
5/25	550	2750	25K	110		
		٠.	•	1411 1-		

¹ Maximum bleeder resistance for critical in-

² Minimum current (bleeder) for critical inductance.

Component Ratings

sistance may result in the wasting of an appreciable portion of the transformer power capacity in the bleeder resistance. Two input chokes in series will permit the use of a bleeder of twice the resistance, cutting the wasted current in half. Another alternative that can be used in a c.w. transmitter is to use a very high-resistance bleeder for protective purposes and only sufficient fixed bias on the tubes operating from the supply to bring the total current drawn from the supply, when the key is open, to the value of current that the required bleeder resistance should draw from the supply. Operating bias is brought back up to normal by increasing the grid-leak resistance. Thus the entire current capacity of the supply (with the exception of the small drain of the protective bleeder) can be used in operating the transmitter stages. With this system, it is advisable to operate the tubes at phone, rather than c.w., rating, since the average dissipation is increased.

Output Voltage

Provided the input-choke inductance is at least the critical value, the output voltage may be calculated quite closely by the following equation:

$$E_o = 0.9E_t - (I_B + I_L) (R_1 + R_2) - E_r$$

where E_o is the output voltage; E_t is the r.m.s. voltage applied to the rectifier (r.m.s. voltage between center-tap and one end of the secondary in the case of the center-tap rectifier); I_B and I_L are the bleeder and load currents, respectively, in amperes; R_1 and R_2 are the resistances of the first and second filter chokes; and E_r is the drop between rectifier plate and cathode. The various voltage drops are shown in Fig. 7-12. At no load I_L is zero, hence the no-load voltage may be calculated on the basis of bleeder current only. The voltage regulation may be determined from

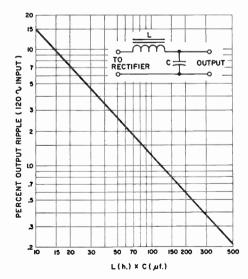


Fig. 7-10—Graph showing combinations of inductance and capacitance that may be used to reduce ripple with a single-section choke-input filter.

the no-load and full-load voltages using the formula previously given.

Ripple with Choke Input

The percentage ripple output from a singlesection filter (Fig. 7-9A) may be determined to a close approximation, for a ripple frequency of 120 cycles, from Fig. 7-10.

> Example: L = 5 h., $C = 4 \mu f.$, LC = 20. From Fig. 7-10, percentage ripple = 7 per cent.

Example: L=5 h. What capacitance is needed to reduce the ripple to 1 per cent? Following the 1-per-cent line to the right to its intersection with the diagonal, thence downward to the LC scale, read LC=120, 120/5=24 uf.

In selecting values for the first filter section, the inductance of the choke should be determined by the considerations discussed previously. Then the capacitor should be selected that when combined with the choke inductance (minimum inductance in the case of a swinging choke) will bring the ripple down to the desired value. If it is found impossible to bring the ripple down to the desired figure with practical values in a single section, a second section can be added, as shown in Fig. 7-9B and the reduction factor from Fig. 7-8 applied as discussed under capacitive-input filters. The second choke should not be of the swinging type, but one having a more or less constant inductance with changes in current (smoothing choke).

OUTPUT CAPACITOR

If the supply is intended for use with an audiofrequency amplifier, the reactance of the last filter capacitor should be small (20 per cent or less) compared with the other audio-frequency resistance or impedance in the circuit, usually the tube plate resistance and load resistance. On the basis of a lower a.f. limit of 100 cycles for speech amplification, this condition usually is satisfied when the output capacitance (last filter capacitor) of the filter has a capacitance of 4 to 8 μ f., the higher value of capacitance being used in the case of lower tube and load resistances.

RESONANCE

Resonance effects in the series circuit across the output of the rectifier which is formed by the first choke (L_1) and first filter capacitor (C_1) must be avoided, since the ripple voltage would build up to large values. This not only is the opposite action to that for which the filter is intended, but also may cause excessive rectifier peak currents and abnormally high inverse peak voltages. For full-wave rectification the ripple frequency will be 120 cycles for a 60-cycle supply, and resonance will occur when the product of choke inductance in henrys times capacitor capacitance in microfarads is equal to 1.77. The corresponding figure for 50-cycle supply (100-cycle ripple frequency) is 2.53, and for 25cycle supply (50-cycle ripple frequency) 13.5. At least twice these products of inductance and capacitance should be used to ensure against resonance effects. With a swinging choke, the minimum rated inductance of the choke should be used.

RATINGS OF FILTER COMPONENTS

Although filter capacitors in a choke-input filter are subjected to smaller variations in d.c. voltage than in the capacitive-input filter, it is advisable to use capacitors rated for the peak transformer voltage in case the bleeder resistor should burn out when there is no load on the power supply, since the voltage then will rise to the same maximum value as it would with a filter of the capacitive-input type.

In a capacitive-input filter, the capacitors should have a working-voltage rating at least as high, and preferably somewhat higher, than the peak-voltage rating of the transformer. Thus, in the case of a center-tap rectifier having a transformer delivering 550 volts each side of the center-tap, the minimum safe capacitor voltage rating will be 550×1.41 or 775 volts. An 800-volt capacitor should be used, or preferably a 1000-volt unit.

Filter Capacitors in Series

Filter capacitors are made in several different types. Electrolytic capacitors, which are available for peak voltages up to about 800, combine high capacitance with small size, since the dielectric is an extremely thin film of oxide on aluminum foil. Capacitors of this type may be connected in series for higher voltages, although the filtering capacitance will be reduced to the resultant of the two capacitances in series. If this arrangement is used, it is important that each of the capacitors be shunted with a resistor of about 100 ohms per volt of supply voltage, with a power rating adequate for the total resistor current at that voltage. These resistors may serve as all or part of the bleeder resistance (see choke-input filters). Capacitors with higher-voltage ratings usually are made with a dielectric of thin paper impregnated with oil. The working voltage of a capacitor is the voltage that it will withstand continuously.

Filter Chokes

The input choke may be of the swinging type, the required minimum no-load and full-load inductance values being calculated as described above. For the second choke (smoothing choke) values of 4 to 20 henrys ordinarily are used. When filter chokes are placed in the positive leads, the negative being grounded, the windings should be insulated from the core to withstand the full d.c. output voltage of the supply and be capable of handling the required load current.

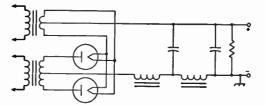


Fig. 7-11—In most applications, the filter chokes may be placed in the negative instead of the positive side of the circuit. This reduces the danger of a voltage breakdown between the choke winding and core.

Filter chokes or inductances are wound on iron cores, with a small gap in the core to prevent magnetic saturation of the iron at high currents. When the iron becomes saturated its permeability decreases, consequently the inductance also decreases. Despite the air gap, the inductance of a choke usualy varies to some extent with the direct current flowing in the winding; hence it is necessary to specify the inductance at the current which the choke is intended to carry. Its inductance with little or no direct current flowing in the winding may be considerably higher than the value when full load current is flowing.

NEGATIVE-LEAD FILTERING

For many years it has been almost universal practice to place filter chokes in the positive leads of plate power supplies. This means that the insulation between the choke winding and its core (which should be grounded to chassis as a safety measure) must be adequate to withstand the output voltage of the supply. This voltage requirement is removed if the chokes are placed in the negative lead as shown in Fig. 7-11. With this connection, the capacitance of the transformer secondary to ground appears in parallel with the filter chokes tending to bypass the chokes. However, this effect will be negligible in practical application except in cases where the output ripple must be reduced to a very low figure. Such applications are usually limited to low-voltage devices such as receivers, speech amplifiers and v.f.o.'s where insulation is no problem and the chokes may be placed in the positive side in the conventional manner. In higher-voltage applications, there is no reason why the filter chokes should not be placed in the negative lead to reduce insulation requirements. Choke terminals, negative capacitor terminals and the transformer center-tap terminal should be well protected against accidental contact, since these will assume full supply voltage to chassis should a choke burn out or the chassis connection fail.

PLATE AND FILAMENT TRANSFORMERS


Output Voltage

The output voltage which the plate transformer must deliver depends upon the required

d.c. load voltage and the type of filter circuit.

With a choke-input filter, the required r.m.s. secondary voltage (each side of center-tap for a

Fig. 7-12—Diagrom showing various voltage drops that must be taken into consideration in determining the required transformer voltage to deliver the desired output voltage.

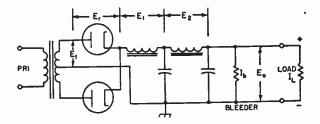

center-tap rectifier) can be calculated by the equation:

$$E_{\rm t} = 1.1 \Big[E_{\rm o} + I(R_1 + R_2) + E \Big]$$

where E_{\circ} is the required d.c. output voltage, I is the load current (including bleeder current) in amperes, R_1 and R_2 are the d.c. resistances of the chokes, and E_r is the voltage drop in the rectifier. E_t is the full-load r.m.s. secondary voltage; the open-circuit voltage usually will be 5 to 10 per cent higher than the full-load value.

The approximate transformer output voltage required to give a desired d.c. output voltage with a given load with a capacitive-input filter system can be calculated with Fig. 7-12.

Example:

Required d.c. output volts — 500

Load current to be drawn — 100 ma. (0.1 amp)

Load resistance =
$$\frac{500}{0.1}$$
 = 5000 ohms.

If the rectifier resistance is 200 ohms, Fig. 7-5 shows that the ratio of d.c. volts to the required transformer r.m.s. voltage is approximately 1.15.

The required transformer terminal voltage under load with chokes of 200 and 300 ohms is

$$E_{1} = \frac{E_{0} + I\left(R_{1} + R_{2} + R_{r}\right)}{1.15}$$

$$= \frac{500 + 0.1\left(200 + 300 + 200\right)}{1.15}$$

$$= \frac{570}{1.15} = 495 \text{ volts.}$$

Volt-Ampere Rating

The volt-ampere rating of the transformer depends upon the type of filter (capacitive or choke input). With a capacitive-input filter the heating effect in the secondary is higher because of the high ratio of peak to average current, consequently the volt-amperes handled by the transformer may be several times the watts delivered to the load. With a choke-input filter, provided the input choke has at least the critical inductance, the secondary volt-amperes can be calculated quite closely by the equation:

Sec.
$$V.A. = 0.00075EI$$

where E is the *total* r.m.s. voltage of the secondary (between the outside ends in the case of a center-tapped winding) and I is the d.c. output current in milliamperes (load current plus bleeder

current). The primary volt-amperes will be 10 to 20 per cent higher because of transformer losses

Broadcast & Television Replacement Transformers in Amateur Transmitter Service

Small power transformers of the type sold for replacement in broadcast and television receivers are usually designed for service in terms of use for several hours continuously with capacitor-input filters. In the usual type of amateur transmitter service, where most of the power is drawn intermittently for periods of several minutes with equivalent intervals in between, the published ratings can be exceeded without excessive transformer heating.

With capacitor input, it should be safe to draw 20 to 30 per cent more current than the rated value. With a choke-input filter, an increase in current of about 50 per cent is permissible. If a bridge rectifier is used (with a choke-input filter) the output voltage will be approximately doubled. In this case, it should be possible in amateur transmitter service to draw the rated current, thus obtaining about twice the rated output power from the transformer.

This does not apply, of course, to amateur transmitter plate transformers which are usually already rated for intermittent service.

Filament Supply

Except for tubes designed for battery operation, the filaments or heaters of vacuum tubes used in both transmitters and receivers are universally operated on alternating current obtained from the power line through a step-down transformer delivering a secondary voltage equal to the rated voltage of the tubes used. The transformer should be designed to carry the current taken by the number of tubes which may be connected in parallel across it. The filament or heater transformer generally is center-tapped, to provide a balanced circuit for eliminating hum.

For medium- and high-power r.f. stages of transmitters, and for high-power audio stages, it is desirable to use a separate filament transformer for each section of the transmitter, installed near the tube sockets. This avoids the necessity for abnormally large wires to carry the total filament current for all stages without appreciable voltage drop. Maintenance of rated filament voltage is highly important, especially with thoriated-filament tubes, since under- or over-voltage may reduce filament life.

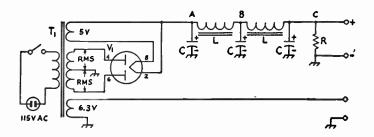


Fig. 7-13—Typical a.c. powersupply circuit for receivers, exciters, or low-power transmitters. Representative values will be found in Table 7-II. The 5-volt winding of 71 should have a current rating of at least 2 amp. for types 5Y3-GT and 5V4-GA, and 3 amp. for 5U4-GB,

TYPICAL POWER SUPPLIES

Figs. 7-13 and 7-14 show typical power-supply circuits. Fig. 7-13 is for use with transformers commonly listed as broadcast or television replacement power transformers. In addition to the high-voltage winding for plate supply, these transformers have windings that supply filament voltages for both the rectifier tube and the 6.3-volt tubes in the receiver or low-power transmitter or exciter. Transformers of this type may be obtained in ratings up to 1200 volts r.m.s. centertapped, 200 d.c. ma. output.

Fig. 7-13 shows a two-section filter with capacitor input. However, depending upon the maximum hum level that may be allowable for a particular application, the last capacitor and choke may not be needed. In some low-current applications, the first capacitor alone may provide adequate filtering. Table 7-II shows the

approximate full-load and bleeder-load output voltages and a.c. ripple percentages for several representative sets of components. Voltage and ripple values are given for three points in the circuit—Point A (first capacitor only used), Point B (last capacitor and choke omitted), and Point C (complete two-section filter in use). In each case, the bleeder resistor R should be used across the output.

Table 7-II also shows approximate output voltages and ripple percentages for choke-input filters (first filter capacitor omitted), for Point B (last capacitor and choke omitted), and Point C (complete two-section filter, first capacitor omitted).

Actual full-load output voltages may be somewhat lower than those shown in the table, since the voltage drop through the resistance of the transformer secondary has not been included.

							TA	BLE 7-1	1							
						Capac	itor-Inp	out Pow	er Su	pplie	3					
T ₁ Rating		V ₁ Tube		с		L	R	!	Ful	broxin l-load Tolts	d.c.		pproxin Ripple at	% A	pprox.	Usefu
Total Volts R.M.S.	Ma. D.C.	Type	μf.	Volts	Н.	Ohms	Ohms	Watts	A	В	c	A	В	B	Volts Bleeder Load	Output Ma.*
650	40	5Y3-GT	8	600	8	400	90K	5	375	360	345	2.5	0.08	0.002	450	36
650	40	5V4-GA	8	600	8	400	90K	5	410	395	375	2.5	0.08	0.002	450	36
700	90	5Y3.GT	8	600	10	225	46K	10	370	350	330	6	0.1	0.002	460	82
700	90	5V4-GA	8	600	10	225	46K	10	410	390	370	6	0.1	0.002	460	82
750	150	5U4-GB	8	700	8	145	25K	10	375	350	330	9	0.2	0.006	500	136
750	150	5V4-GA	8	700	8	145	25K	10	425	400	380	9	0.2	0.006	500	136
800	200	5U4-GB	8	700	8	120	22K	20	375	350	325	12	0.3	0.008	550	184
						Chol	e-Inpu	Power	Sup	plies						
650	40	5Y3-GT	8	450	15	420	18K	10	—	240	225	—	0.8	0.01	265	25
650	40	5V4-GA	8	450	15	420	18K	10	_	255	240	_	0.8	0.01	280	25
700	90	5Y3-GT	8	450	10	225	11K	10	-	240	220	_	1.25	0.02	250	68
700	90	5V4-GA	8	450	10	225	11K	10	_	270	250	_	1.25	0.02	280	68
750	150	5Y3-GT	8	450	12	150	13K\	20		265	245	_	1	0.015	325	125
750	150	5V4-GA	8	450	12	150	13K	20		280	260	_	1	0.015	340	125
800	200	5U4-GB	8	450	12	140	14K	20		275	250		1	0.015	350	175

Voltage Dropping

Fig. 7-14 shows the conventional circuit of a transmitter plate supply for higher powers. A full-wave rectifier circuit, half-wave rectifier tubes, and separate transformers for high voltage, rectifier filaments and transmitter filaments are

used. The high-voltage transformers used in this circuit are usually rated directly in terms of d.c. output voltage, assuming rectifiers and filters of the type shown in Fig. 7-14. Table 7-III shows typical values for representative supplies, based

Fig. 7-14—Conventional powersupply circuit for higher-power transmitters.

C₁, C₂—4 μ f. for approximately 0.5% output ripple; 2 μ f. for approximately 1.5% output ripple, C₂ should be 4 μ f. if supply is for modulator.


R-25,000 ohms.

L₁—Swinging choke: 5/25 h., current rating same as T₂.

La—Smoothing choke: current rating same as 72.

T₁-2.5 volts, 4 amp., 2500-v. ins. for type 816; 2.5 volts, 10 amp., 10,000-v. ins. for 866A.

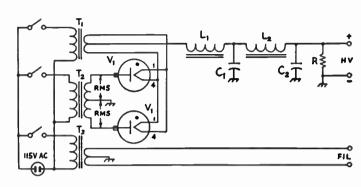T_s—D.c. voltage rating same as output voltage.
T_s—Voltage and current rating to suit transmitter-tube requirements.



V₁—Type 816 for 400/500-volt supply; 866A far athers shown in Table 7-III. See Table 7-III for other values.

on commonly available Transcomponents. former voltages shown are representative for units with dual-voltage secondaries. The bleeder-load voltages shown may be somewhat lower than actually found in practice. Ripple at the output of the first filter section will be approximately 5 per cent with a $4-\mu f$. capacitor, or 10 per cent with a 2-µf. capac-Transformers made for amateur service are designed for choke-input. If a capacitor-input is used rating should be reduced about 30%.

			TABLE 7	-111			
Approx. Out		T ₁ Rati	Ls	Voltage	R Watts	Approx. Bleeder-	
Volts	Ma. 1	Approx. V.R.M.S.	Ma.	H. Rating C1, C2		Load Output Volts	
400/500	230	520/615	250	4	700	20	440/540
600/750	260	750/950	300	8	1000	50	650/800
1250/1500	240	1500/1750	300	8	2000	150	1300/1600
1250/1500	440	1500/1750	500	6	2000	150	1315/1615
2000/2500	200	2400/2900	300 4	8	3000	320 *	2050/2550
2000/2500	400	2400/2900	500	6	3000	320 °	2065/2565
2500/3000	380	2500/3450	500 B	6	4000	500 \$	2565/3065

- ¹ Balance of transformer current rating consumed by bleeder resistor.
- *Use two 160-watt, 12,500-ohm units in series.
- ^{\$} Use five 100-watt, 5000-ohm units in series.
- 4 Regulation will be somewhat better with a 400 or 500-ma. choke.
- ⁸ Regulation will be somewhat better with a 550-ma. choke.

VOLTAGE DROPPING

Series Voltage-Dropping Resistor

Certain plates and screens of the various tubes in a transmitter or receiver often require a variety of operating voltages differing from the output voltage of an available power supply. In most cases, it is not economically feasible to provide a separate power supply for each of the required voltages. If the current drawn by an electrode, or combination of electrodes operating at the same voltage, is reasonably constant under

normal operating conditions, the required voltage may be obtained from a supply of higher voltage by means of a voltage-dropping resistor in series, as shown in Fig. 7-15A. The value of the series, resistor, R_1 , may be obtained from Ohm's Law, $R = \frac{E_d}{I}$, where E_d is the voltage drop required from the supply voltage to the desired voltage and I is the total rated current of the load.

Example: The plate of the tube in one stage and the screens of the tubes in two other stages

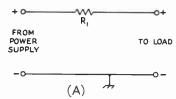


Fig. 7-15—A—A series voltage-dropping resistor. B—Simple voltage divider.

$$R_2 = \frac{E_1}{I_2}$$
; $R_1 = \frac{E - E_1}{I_1 + I_2}$.

I₂ must be assumed.C—Multiple divider circuit.

$$R_3 = \frac{E_2}{I_3}$$
, $R_2 = \frac{E_1 - E_2}{I_2 + I_3}$, $R_1 = \frac{E - E_1}{I_1 + I_2 + I_3}$


require an operating voltage of 250. The nearest available supply voltage is 400 and the total of the rated plate and screen currents is 75 ma. The required resistance is

$$R = \frac{400 - 250}{0.075} = \frac{150}{0.075} = 2000 \text{ ohms.}$$

The power rating of the resistor is obtained from P (watts) = $l^2R = (0.075)^2$ (2000) = 11.2 watts. A 20-watt resistor is the nearest safe rating to be used.

Voltage Dividers

The regulation of the voltage obtained in this manner obviously is poor, since any change in current through the resistor will cause a directly proportional change in the voltage drop across the resistor. The regulation can be improved somewhat by connecting a second resistor from the low-voltage end of the first to the negative power-supply terminal, as shown in Fig. 7-15B. Such an arrangement constitutes a voltage divider. The second resistor, R_2 , acts as a constant load for the first, R1, so that any variation in current from the tap becomes a smaller percentage of the total current through R_1 . The heavier the current drawn by the resistors when they alone are connected across the supply, the better will be the voltage regulation at the tap.

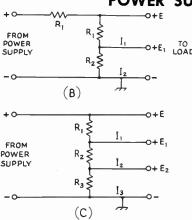

Such a voltage divider may have more than a single tap for the purpose of obtaining more than one value of voltage. A typical arrangement is shown in Fig. 7-15C. The terminal voltage is E, and two taps are provided to give power voltages, E_1 and E_2 , at currents I_1 and I_2 respectively. The smaller the resistance between taps in proportion to the total resistance, the smaller the voltage between the taps. For convenience, the voltage divider in the figure is considered to be made up of separate resistances R_1 , R_2 , R_3 , between taps. R₃ carries only the bleeder current, I₃; R₂ carries I_2 in addition to I_3 ; R_1 carries I_1 , I_2 and I_3 . To calculate the resistances required, a bleeder current, I₃, must be assumed; generally it is low compared with the total load current (10 per cent or so). Then the required values can be calculated as shown in the caption of Fig. 7-15C, I being in decimal parts of an ampere.

The method may be extended to any desired number of taps, each resistance section being calculated by Ohm's Law using the needed voltage drop across it and the total current through it. The power dissipated by each section may be calculated either by multiplying I and E or I^2 and R,

VOLTAGE STABILIZATION

Gaseous Regulator Tubes

There is frequent need for maintaining the voltage applied to a low-voltage low-current circuit at a practically constant value, regardless of the voltage regulation of the power supply or variations in load current. In such applications,

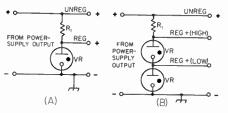


Fig. 7-16—Voltage-stabilizing circuits using VR tubes.

gaseous regulator tubes (0C3/VR105, 0D3/VR150, etc.) can be used to good advantage. The voltage drop across such tubes is constant over a moderately wide current range. Tubes are available for regulated voltages near 150, 105, 90 and 75 volts.

The fundamental circuit for a gaseous regulator is shown in Fig. 7-16A. The tube is connected in series with a limiting resistor, R_1 , across a source of voltage that must be higher than the starting voltage. The starting voltage is about 30 to 40 per cent higher than the operating voltage. The load is connected in parallel with the tube. For stable operation, a minimum tube current of 5 to 10 ma. is required. The maximum permissible current with most types is 40 ma.; consequently, the load current cannot exceed 30 to 35 ma. if the voltage is to be stabi-

Voltage Stabilization

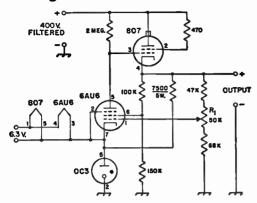


Fig. 7-17—Electronic voltage-regulator circuit. Resistors are ½ watt unless specified otherwise.

lized over a range from zero to maximum load current.

The value of the limiting resistor must lie between that which just permits minimum tube current to flow and that which just passes the maximum permissible tube current when there is no load current. The latter value is generally used. It is given by the equation:

$$R = \frac{(E_{\rm o} - E_{\rm r})}{I}$$


where R is the limiting resistance in ohms, E_8 is the voltage of the source across which the tube and resistor are connected, E_r is the rated voltage drop across the regulator tube, and I is the maximum tube current in amperes, (usually 40 ma., or 0.04 amp.).

Fig. 7-16B shows how two tubes may be used

in series to give a higher regulated voltage than is obtainable with one, and also to give two values of regulated voltage. The limiting resistor may be calculated as above, using the sum of the voltage drops across the two tubes for Er. Since the upper tube must carry more current than the lower, the load connected to the low-voltage tap must take small current. The total current taken by the loads on both the high and low taps should not exceed 30 to 35 milliamperes.

Voltage regulation of the order of 1 per cent can be obtained with these regulator circuits.

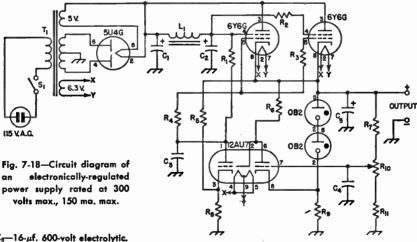A single VR tube may also be used to regulate the voltage to a load current of almost any value so long as the variation in the current does not exceed 30 to 35 ma. If, for example, the average load current is 100 ma., a VR tube may be used to hold the voltage constant provided the cur-



C1, C2, C5-16-µf. 600-volt electrolytic.

 C_8 —0.015- μ f. paper.

C₄-0.1-µf. paper.

R₁-0.3 megohm, ½ watt.

R₂, R₃-100 ohms, ½ watt.

R4-510 ohms, 1/2 watt.

R₅, R₈-30,000 ohms, 2 watts.

R₆-0.24 megohm, ½ watt.

R₇-0.15 megohm, ½ watt.

R₉-9100 ohms, 1 watt.

R₁₀-0.1-megohm potentiometer.

R₁₁-43,000 ohms, ½ watt.

L₁--8-hy., 40-ma. filter choke.

\$1-S.p.s.t. toggle.

T₁-Power transformer: 375-375 voltsr.m.s., 160 ma.; 6.3 volts, 3 amps.; 5 volts, 3 amps.

(Thor. 22R33).

rent does not fall below 85 ma. or rise above 115 ma. In this case, the resistance should be calculated to drop the voltage to the VR-tube rating at the maximum load current to be expected plus about 5 ma. If the load resistance is constant, the effects of variations in line voltage may be eliminated by basing the resistance on the load current plus 15 ma. Voltage-regulator tubes may also be connected in parallel as described later in this chapter.

Electronic Voltage Regulation

Several circuits have been developed for regulating the voltage output of a power supply electronically. While more complicated than the VRtube circuits, they will handle higher voltages currents and the output voltage may be varied continuously over a wide range. In the circuit of Fig. 7-17, the 0C3 regulator tube supplies a reference of approximately +105 volts for the 6AU6 control tube. When the load connected across the output terminals increases, the output voltage tends to decrease. This makes the voltage on the control grid of the 6AU6 less positive, causing the tube to draw less current through the 2megohm plate resistor. As a consequence the grid voltage on the 807 series regulator becomes more positive and the voltage drop across the 807 decreases, compensating for the reduction in output voltage. With the values shown, adjustment of R1 will give a regulated output from 150 to 250 volts, at up to 60 or 70 ma. A 6L6-GB can be substituted for the type 807; the available output current can be increased by adding tubes in parallel with the series regulator tube. When this is done, 100-ohm resistors should be wired to

Table	Table of Performance for Circuit of Fig. 7-18										
I	II	III	Output voltage - 300								
450 v.	22 ma.	3 mv.	150 ma. 2.3 mv.								
425 v.	45 ma.	4 mv.	125 ma. 2.8 mv.								
400 v.	72 ma.	6 mv.	100 ma. 2.6 my.								
375 v.	97 ma.	8 mv.	75 ma. 2.5 mv.								
350 v.	122 ma.	9.5 mv.	50 ma. 3.0 mv.								
325 v.	150 ma.	3 my.	25 ma. 3.0 mv.								
300 v.	150 ma.	2.3 mv.	10 ma. 2.5 mv.								

each control grid and plate terminal, to reduce the chances for parasitic oscillations.

Another similar regulator circuit is shown in Fig. 7-18. The principal difference is that screengrid regulator tubes are used. The fact that a screen-grid tube is relatively insensitive to changes in plate voltage makes it possible to obtain a reduction in ripple voltage adequate for many purposes simply by supplying filtered d.c. to the screens with a consequent saving in weight and cost. The accompanying table shows the performance of the circuit of Fig. 7-18. Column I shows various output voltages, while Column II shows the maximum current that can be drawn at that voltage with negligible variation in output voltage. Column III shows the measured ripple at the maximum current. The second part of the table shows the variation in ripple with load current at 300 volts output.

High-Voltage Regulators

Regulated screen voltage is required for screengrid tubes used as linear amplifiers in single-sideband operation. Figs. 7-19 through 7-22 show various different circuits for supplying regulated voltages up to 1200 volts or more.

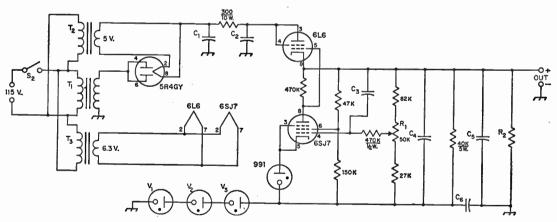


Fig. 7-19—High-voltage regulator circuit by W4PRM. Resistors are 1 watt unless indicated otherwise. C₁, C₂—4-μf. paper, voltage rating above peak-voltage

output of T_1 .

 C_8 -0.1- μ f. paper, 600 volts. C4-12-µf. electroyltic, 450 volts.

 C_{δ} —40 μ f., voltage rating above d.c. output voltage. Can be made up of a combination of electrolytics in series, with equalizing resistor. (See section on ratings of filter components.)

C₆—4-µt. paper, voltage rating above voltage rating of VR string.

R₁-50,000-ohm, 4-watt potentiometer.

R₂—Bleeder resistor, 50,000 to 100,000 ohms, 25 watts (not needed if equalizing resistors mentioned above are used).

T₁-See text.

T2-Filament transformer; 5 volts, 2 amp.

T₃—Filament transformer; 6.3 volts, 1.2 amp.

V₁, V₂, V₃—See text.

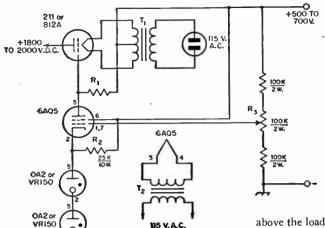


Fig. 7-20—Screen regulator circuit designed by W9OKA. Resistances are in ohms (K = 1000).

R1-6000 ohms for 211; 2300 ohms for 812A, 20 watts.

R2-25,000 ohms, 10 watts.

R₈-Output voltage control, 0.1-megohm, 2-watt potentiometer.

T₁-Filament transformer: 10 volts, 3.25 amp. for 211; 6.3 volts, 4 amp. for 812A.

T₂-Filament transformer: 6.3 volts, l amp.

In the circuit of Fig. 7-19, gas-filled regulator tubes are used to establish a fixed reference voltage to which is added an electronically regulated variable voltage. The design can be modified to give any voltage from 225 volts to 1200 volts, with each design-center voltage variable by plus or minus 60 volts.

The output voltage will depend upon the number and voltage ratings of the VR tubes in the string between the 991 and ground. The total VR-tube voltage rating needed can be determined by subtracting 250 volts from the desired output voltage. As examples, if the desired output voltage is 350, the total VR-tube voltage rating should be 350 - 250 = 100 volts. In this case, a VR-105 would be used. For an output voltage of 1000, the VR-tube voltage rating should be 1000 - 250 = 750 volts. In this case, five VR-150s would be used in series.

The maximum voltage output that can be obtained is approximately equal to 0.7 times the r.m.s. voltage of the transformer T_1 . The current rating of the transformer must be somewhat above the load current to take care of the voltage dividers and bleeder resistances.

A single 6L6 will handle 90 ma. For larger currents, 6L6s may be added in parallel.

The heater circuit supplying the 6L6 and 6SJ7 should not be grounded. The shaft of R1 should be grounded. When the output voltage is above 300 or 400, the potentiometer should be provided with an insulating mounting, and should be controlled from the panel by an extension shaft with an insulated coupling and grounded control.

In some cases where the plate transformer has

Fig. 7-21—This regulator circuit used by W1SUN operates from the plate supply and requires no VR string. A small supply provides screen voltage and reference bias for the control tube.

Unless otherwise marked, resistances are in ohms.

(K = 1000). Capacitors are electrolytic.

R₁-50,000-ohm, 50-watt adjustable resistor.

R₂-0.1-megohm 2-watt potentiometer.

R₃-4.7 megohms, 2 watts.

R₄-0.1 megohm, ½ watt.

T₁-Power transformer: 470 volts center tapped, 40 ma.; 5 volts, 2 amps.; 6.3 volts, 2 amps.

T₂—Filament transformer: 7.5 volts, 3.25 amp. (for V-70D).


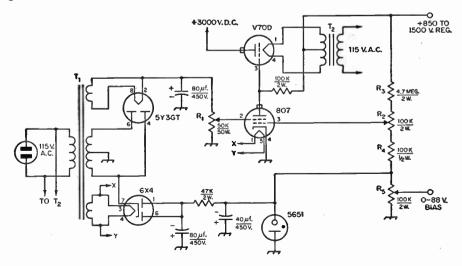


Fig. 7-22—Shunt screen regulator used by W2AZW. Resistances are in ohms (K == 1000). C₁-0.01 µf., 400 volts if needed to suppress

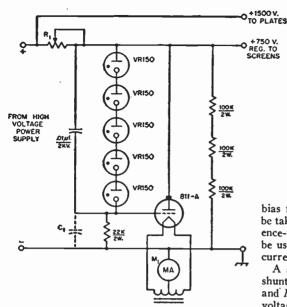R₁---Adjustable wire-wound resistor, resistance and wattage as required.



bias for a Class A or Class AB, amplifier may be taken from the potentiometer across the refer-

oscillation.

current. A somewhat different type of regulator is the shunt regulator shown in Fig. 7-22. The VR tubes and R2 in series are across the output. Since the voltage drop across the VR tubes is constant. any change in output voltage appears across R2. This causes a change in grid bias on the 811-A grid, causing it to draw more or less current in inverse proportion to the current being drawn by the amplifier screen. This provides a constant load for the series resistor R_1 .

The output voltage is equal to the sum of the VR drops plus the grid-to-ground voltage of the 811-A. This varies from 5 to 20 volts between full load and no load. The initial adjustment is made by placing a milliammeter in the filament center-tap lead, as shown, and adjusting R_1 for a reading of 15 to 20 ma, higher than the mormal peak screen current. This adjustment should be made with the amplifier connected but with no excitation, so that the amplifier draws idling current. After the adjustment is complete, the meter may be removed from the circuit and the filament center tap connected directly to ground. Adjustment of the tap on R₁ should, of course, be made with the high voltage turned off.

Any number of VR tubes may be used to provide a regulated voltage near the desired value. The maximum current through the 811-A should be limited to the maximum plate-current rating of the tube. If larger currents are necessary, two 811-As may be connected in parallel. Over a current range of 5 to 60 ma., the regulator holds the output voltage constant within 10 or 15 volts.

sufficient current-handling capacity, it may be desirable to operate a screen regulator from the plate supply, rather than from a separate supply. This can be done if a regulator tube is used that can take the required voltage drop. In Fig. 7-20, a type 211 or 812A is used, the control tube being a 6AQ5. With an input voltage of 1800 to 2000, an output voltage of 500 to 700 can be obtained with a regulation better than 1 per cent over a current range of 0 to 100 ma.

In the circuit of Fig. 7-21, a V-70D (or 8005) is used as the regulator, and the control tube is an 807 which can take the full output voltage, making it unnecessary to raise it above ground with VR tubes. If taps are switched on R1, the output voltage can be varied over a wide range. Increasing the screen voltage decreases the output voltage. For each position of the tap on R_1 , decreasing the value of R_s will lower the minimum output voltage as R2 is varied, and decreasing the value of R₄ will raise the maximum output voltage. However, if these values are made too small, the 807 will lose control.

At 850 volts output, the variation over a current change of 20 to 80 ma. should be negligible. At 1500 volts output with the same current change, the variation in output voltage should be less than three per cent. Up to 88 volts of grid

BIAS SUPPLIES

As discussed in Chapter 6 on high-frequency transmitters, the chief function of a bias supply for the r.f. stages of a transmitter is that of providing protective bias, although under certain circumstances, a bias supply, or pack, as it is sometimes called, can provide the operating bias if desired.

Simple Bias Packs

Fig. 7-23A shows the diagram of a simple bias supply. R₁ should be the recommended grid leak for the amplifier tube. No grid leak should be used in the transmitter with this type of supply. The output voltage of the supply, when amplifier

World Radio History

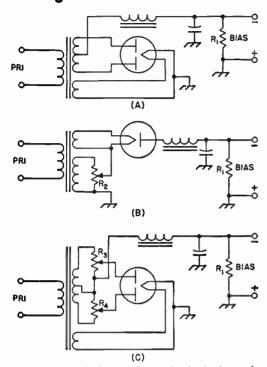


Fig. 7-23—Simple bias-supply circuits. In A, the peak transformer voltage must not exceed the operating value of bias. The circuits of B (half-wave) and C (full-wave) may be used to reduce transformer voltage to the rectifier. R₁ is the recommended grid-leak resistance.

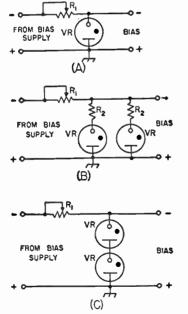


Fig. 7-24—Illustrating the use of VR tubes in stabilizing protective-bias supplies. R₁ is a resistor whose value is adjusted to limit the current through each VR tube to 5 ma. before amplifier excitation is applied. R and R₈ are current-equalizing resistors of 50 to 1000 ohms.


grid current is not flowing, should be some value between the bias required for plate-current cutoff and the recommended operating bias for the amplifier tube. The transformer peak voltage (1.4 times the r.m.s. value) should not exceed the recommended operating-bias value, otherwise the output voltage of the pack will soar above the operating-bias value with rated grid current.

This soaring can be reduced to a considerable extent by the use of a voltage divider across the transformer secondary, as shown at B. Such a system can be used when the transformer voltage is higher than the operating-bias value. The tap on R_2 should be adjusted to give amplifier cut-off bias at the output terminals. The lower the total value of R_2 , the less the soaring will be when grid current flows.

A full-wave circuit is shown in Fig. 7-23C. R_8 and R_4 should have the same total resistance and the taps should be adjusted symmetrically. In all cases, the transformer must be designed to furnish the current drawn by these resistors plus the current drawn by R_1 .

Regulated Bias Supplies

The inconvenience of the circuits shown in Fig. 7-23 and the difficulty of predicting values in practical application can be avoided in most cases by the use of gaseous voltage-regulator tubes across the output of the bias supply, as shown in Fig. 7-24A. A VR tube with a voltage

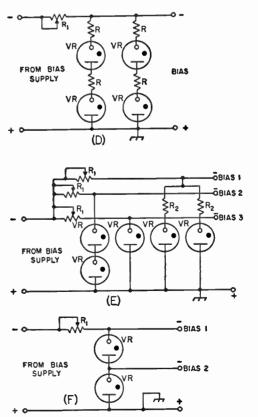

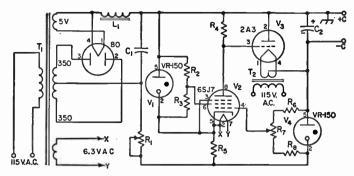


Fig. 7-25—Circuit diagram of an electronically-regulated bias supply.

C₁—20- μ f. 450-volt electrolytic. C₂—20- μ f. 150-volt electrolytic. R₁—5000 ohms, 25 watts. R₂—22,000 ohms, ½ watt. R₃—68,000 ohms, ½ watt. R₄—0.27 megohm, ½ watt. R₆—3000 ohms, 5 watts. R₉—0.12 megohm, ½ watt.

R;—0.1-megohm potentiometer.

Rs—27,000 ohms, ½ watt.

L1—20-hy. 50-ma. filter choke.

T1—Power transformer: 350 volts r.m.s.
each side of center 50 ma.; 5 volts,
2 amp.; 6.3 volts, 3 amp.

T3—2.5-volt filament transformer
(Thordarson 21F00).

rating anywhere between the biasing-voltage value which will reduce the input to the amplifier to a safe level when excitation is removed, and the operating value of bias, should be chosen. R_1 is adjusted, without amplifier excitation, until the VR tube ignites and draws about 5 ma. Additional voltage to bring the bias up to the operating value when excitation is applied can be obtained from a grid leak resistor, as discussed in the transmitter chapter.

Each VR tube will handle 40 ma. of grid current. If the grid current exceeds this value under any condition, similar VR tubes should be added in parallel, as shown in Fig. 7-24B, for each 40 ma., or less, of additional grid current. The resistors R_2 are for the purpose of helping to maintain equal currents through each VR tube, and should have a value of 50 to 1000 ohms or more.


If the voltage rating of a single VR tube is not sufficiently high for the purpose, other VR tubes may be used in series (or series-parallel if required to satisfy grid-current requirements) as shown in the diagrams of Fig. 7-24C and D.

If a single value of fixed bias will serve for more than one stage, the biasing terminal of each such stage may be connected to a single supply of this type, provided only that the total grid current of all stages so connected does not exceed the current rating of the VR tube or tubes. Alternatively, other separate VR-tube branches may be added in any desired combination to the same supply, as in Fig. 7-24E, to adapt them to the needs of each stage.

Providing the VR-tube current rating is not exceeded, a series arrangement may be tapped for lower voltage, as shown at F.

The circuit diagram of an electronically regulated bias-supply is shown in Fig. 7-25. The output voltage may be adjusted to any value between 40 volts and 80 volts and the unit will handle grid currents up to 35 ma. over the range of 50 to 80 volts, and 25 ma. over the remainder

of the range. If higher current-handling capacity is required, more 2A3s can be connected in parallel with V_s . The regulation will hold to about 0.01 volt per milliampere of grid current. The regulator operates as follows: Since the voltage drop across V_s and V_s is in parallel with the voltage drop across V_s will appear across R_s because the voltage drops across both VR tubes remain constant. R_s is a cathode biasing resistor for V_s , so any voltage change across it appears as a grid-voltage change on V_s . This change in grid voltage is amplified by V_s and appears across R_s which is connected to the plate of V_s and the grids of V_s . This change in voltage swings the grids of V_s . This change in voltage swings the grids of V_s .

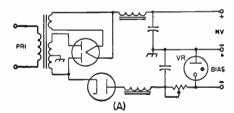

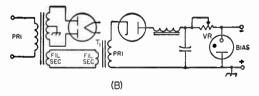


Fig. 7-26—Convenient means of obtaining biasing voltage. A—From a low-voltage plate supply. B—From spare filament winding. I, is a filament transformer, of a voltage output similar to that of the spare filament winding, connected in reverse to give 115 volts r.m.s. output. If cold-cathode or selenium rectifiers are used, no additional filament supply is required.

Voltage Multiplying

more positive or negative, and thus varies the internal resistance fo Vs, maintaining the voltage drop across V_s practically constant.

Other Sources of Biasing Voltage

In some cases, it may be convenient to obtain the biasing voltage from a source other than a separate supply. A half-wave rectifier may be connected with reversed polarization to obtain biasing voltage from a low-voltage plate supply, as shown in Fig. 7-26A. In another arrangement, shown at B, a spare filament winding can be used to operate a filament transformer of similar voltage rating in reverse to obtain a voltage of about 130 from the winding that is customarily the primary. This will be sufficient to operate a VR75 or VR90 regulator tube.

A bias supply of any of the types discussed requires relatively little filtering, if the outputterminal peak voltage does not approach the operating-bias value, because the effect of the supply is entirely or largely "washed out" when grid current flows.

VOLTAGE-MULTIPLYING CIRCUITS

Although vacuum-tube rectifiers can be used in voltage-multiplying circuits, the more common application is with selenium, silicon and germanium diodes. The choice of diodes is based on the voltage and current requirements; selenium is

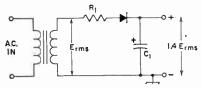


Fig. 7-27—If the current demand is low, a simple halfwave rectifier will deliver a slight voltage increase. Typical values, for Erms = 117 and a load current of 75 ma.:

C1-50-µf., 150-v. electrolytic.

Eoutput-130 volts.

R₁-22 ohms.

normally used up to a source voltage of 130, and above that it becomes necessary to use silicon.

A simple half-wave rectifier circuit is shown in Fig. 7-27. Strictly speaking this is not a voltage-multiplying circuit. However, if the current demand is low (a milliampere or so), the d.c. output voltage will be close to the peak voltage of the source, or 1.4E_{rms}. A typical application of the circuit would be to obtain a low bias voltage from a heater winding; the + side of the output can be grounded by reversing the polarity of the rectifier and capacitor. As with all halfwave rectifiers, the output voltage drops quickly with increased current demand.

The resistor R_1 in Fig. 7-27 is included to limit the current through the rectifier, in accordance with the manufacturer's rating for the diode. If the resistance of the transformer winding is sufficient, R_1 can be omitted.

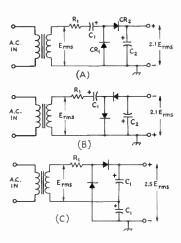



Fig. 7-28—Voltage-doubling circuits. Typical values, for $E_{\rm rms} = 117$ and a load current of 75 ma.: C1-50-µf. 150-v. electrolytic.


C2-50-µf. 250-v. electrolytic.

Eoutput-245 volts.

R₁-22 ohms.

Voltage-doubling circuits are shown in Fig. 7-28. If the current demand is extremely low, the output voltage will be higher than indicated,

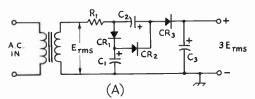

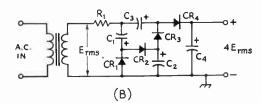

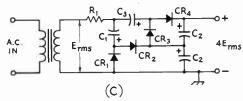


Fig. 7-29—(A) Voltage-tripling and (B, C) voltagequadrupling circuits. Typical values, for $E_{rms} = 117$ and a load current of 75 ma.:

C₁-50-µf. 150-v. electrolytic.

C2-50-µf. 250-v. electrolytic.

C₈, C₄--50-\(mu f. 450-v. electrolytic.

R1-22 ohms.

but with any reasonable current drain the output voltage will be slightly over twice the a.c. input. In Fig. 7-28A, C_1 charges through CR_1 during one half of the a.c. cycle; CR_2 is nonconductive at this time. During the other half of the cycle CR_2 conducts and C_2 becomes charged; they see as the source the transformer plus the charge in C_1 . By reversing the polarities of the capacitors and diodes, as shown in Fig. 7-28B, the + side of the output can be grounded.

The circuit in Fig. 7-28C is a full-wave voltage-doubling circuit that has several advantages over most other circuits. For a given output voltage, compared to the usual full-wave rectifier circuit (Fig. 7-2B) the full-wave doubler rectifiers require only half the p.i.v. rating. Again for a given output voltage, compared to a full-wave bridge circuit (Fig. 7-2C) only half as many rectifiers (of the same p.i.v. rating) are required.

A voltage-tripling circuit is shown in Fig. 7-29A. On one half of the a.c. cycle CR_1 conducts and C_1 is charged to the source voltage. On the opposite half of the cycle CR_2 conducts and C_3 is charged to twice the source voltage, because it sees the transformer plus the charge in C_1 as the source. At the same time CR_3 conducts and, with the transformer and the charge in C_2 as the

source, C_0 is charged to three times the transformer voltage. The + side of the output can be grounded if the polarities of all of the capacitors and diodes are reversed.

A voltage-quadrupling circuit is shown in Fig. 7-29B. On the negative half of the a.c. cycle, when E_{rms} is negative with respect to ground, C1 charges through CR1. On the positive half of the cycle, C2 charges through CR2 to twice Erms, seeing E_{rms} and C_1 as the source. On the negative half of the cycle, Ca charges through CRa to $3E_{rms}$, seeing E_{rms} and C_s as the source. On the positive half of the cycle the output capacitance, C_4 , charges to $4E_{rmo}$ through CR_4 , seeing E_{rmo} and C_3 as the source. The variation in Fig. 7-29C is similar, except that the output capacitor is made up of the two C_2 in series. The lower C_3 serves the function of C2 in Fig. 7-29B. The polarity of the output can be reversed, to permit grounding of the + terminal, by reversing the polarities of all diodes and capacitors.

The values of capacitance given for the voltage-multiplying circuits are what might be required for $E_{rms} = 115$ and a load of 75 ma.

Larger values will improve the voltage regulation, and smaller values may be used at a sacrifice in regulation.

POWER-LINE CONSIDERATIONS

POWER LINE CONNECTIONS

If the transmitter is rated at much more than 100 watts, special consideration should be given to the a.c. line running into the station. In some residential systems, three wires are brought in from the outside to the distribution board, while in other systems there are only two wires. In the three-wire system, the third wire is the neutral which is grounded. The voltage between the other two wires normally is 230, while half of this voltage (115) appears between each of these wires and neutral, as indicated in Fig. 7-30A. In systems of this type, usually it will be found that the 115-volt household load is divided as evenly as possible between the two sides of the circuit. half of the load being connected between one wire and the neutral, while the other half of the load is connected between the other wire and

neutral. Heavy appliances, such as electric stoves and heaters, normally are designed for 230-volt operation and therefore are connected across the two ungrounded wires. While both ungrounded wires should be fused, a fuse should never be used in the wire to the neutral, nor should a switch be used in this side of the line. The reason for this is that opening the neutral wire does not disconnect the equipment. It simply leaves the equipment on one side of the 230-volt circuit in series with whatever load may be across the other side of the circuit, as shown in Fig. 7-30B. Furthermore, with the neutral open, the voltage will then be divided between the two sides in inverse proportion to the load resistance, the voltage on one side dropping below normal, while it soars on the other side, unless the loads happen to be equal.

The usual line running to baseboard outlets

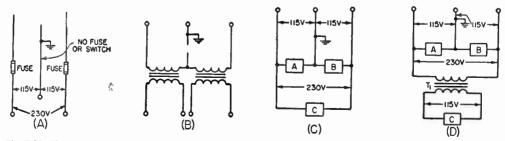


Fig. 7-30—Three-wire power-line circuits. A—Normol 3-wire-line terminotion. No fuse should be used in the gounded (neutrol) line. B—Showing that a switch in the neutral does not remove voltage from either side of the line. C—Connections for both 115- and 230-volt transformers. D—Operating a 115-volt plate transformer from the 230-volt line to avoid light blinking. I₁ is a 2-to-1 step-down transformer.

Power-Line Considerations

is rated at 15 amperes. Considering the power consumed by filaments, lamps, modulator, receiver and other auxiliary equipment, it is not unusual to find this 15-ampere rating exceeded by the requirements of a station of only moderate power. It must also be kept in mind that the same branch may be in use for other household purposes through another outlet. For this reason, and to minimize light blinking when keying or modulating the transmitter, a separate heavier line should be run from the distribution board to the station whenever possible. (A three-volt drop in line voltage will cause noticeable light blinking.)

If the system is of the three-wire type, the three wires should be brought into the station so that the load can be distributed to keep the line balanced. The voltage across a fixed load on one side of the circuit will increase as the load current on the other side is increased. The rate of increase will depend upon the resistance introduced by the neutral wire. If the resistance of the neutral is low, the increase will be correspondingly small. When the currents in the two circuits are balanced, no current flows in the neutral wire and the system is operating at maximum efficiency.

Light blinking can be minimized by using transformers with 230-volt primaries in the power supplies for the keyed or intermittent part of the load, connecting them across the two ungrounded wires with no connection to the neutral, as shown in Fig. 7-30C. The same can be accomplished by the insertion of a step-down transformer whose primary operates at 230 volts and whose secondary delivers 115 volts. Conventional 115-volt transformers may be operated from the secondary of the step-down transformer (see Fig. 7-30D).

When a special heavy-duty line is to be installed, the local power company should be consulted as to local requirements. In some localities it is necessary to have such a job done by a licensed electrician, and there may be special requirements to be met in regard to fittings and the manner of installation. Some amateurs terminate the special line to the station at a switch box, while others may use electric-stove receptacles as the termination. The power is then distributed around the station by means of conventional outets at convenient points. All circuits should be properly fused.

Fusing

All transformer primary circuits should be properly fused. To determine the approximate current rating of the fuse to be used, multiply each current being drawn from the supply in amperes by the voltage at which the current is being drawn. Include the current taken by bleeder resistances and voltage dividers. In the case of series resistors, use the source voltage, not the voltage at the equipment end of the resistor. Include filament power if the transformer is supplying filaments. After multiplying the various voltages and currents, add the individual products. Then divide by the line voltage and

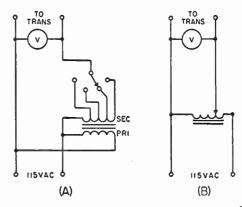


Fig. 7-31—Two methods of transformer primary control. At A is a tapped toy transformer which may be connected so as to boost or buck the line voltage as required. At B is indicated a variable transformer or autotransformer (Variac) which feeds the transformer primaries.

add 10 or 20 per cent. Use a fuse with the nearest larger current rating.

LINE-VOLTAGE ADJUSTMENT

In certain communities trouble is sometimes experienced from fluctuations in line voltage. Usually these fluctuations are caused by a variation in the load on the line and, since most of the variation comes at certain fixed times of the day or night, such as the times when lights are turned on at evening, they may be taken care of by the use of a manually operated compensating device. A simple arrangement is shown in Fig. 7-31A. A toy transformer is used to boost or buck the line voltage as required. The transformer should have a tapped secondary varying between 6 and 20 volts in steps of 2 or 3 volts and its secondary should be capable of carrying the full load current of the entire transmitter, or that portion of it fed by the toy transformer.

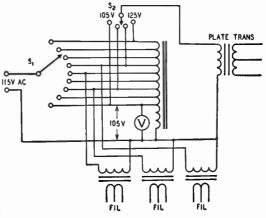


Fig. 7-32—With this circuit, a single adjustment of the tap switch S_1 places the correct primary voltage on all transformers in the transmitter.

The secondary is connected in series with the line voltage and, if the phasing of the windings is correct, the voltage applied to the primaries of the transmitter transformers can be brought up to the rated 115 volts by setting the toy-transformer tap switch on the right tap. If the phasing of the two windings of the toy transformer happens to be reversed, the voltage will be reduced instead of increased. This connection may be used in cases where the line voltage may be above 115 volts. This method is preferable to using a resistor in the primary of a power transformer since it does not affect the voltage regulation as seriously. The circuit of 7-31B illustrates the use of a variable autotransformer (Variac) for adjusting line voltage.

Another scheme by which the primary voltage of each transformer in the transmitter may be adjusted to give a desired secondary voltage, with a master control for compensating for changes in line voltage, is shown in the autotransformer circuit of Fig. 7-32.

This arrangement has the following features: 1) Adjustment of the switch S_1 to make the voltmeter read 105 volts automatically adjusts all transformer primaries to the predetermined correct voltage.

- 2) The necessity for having all primaries work at the same voltage is eliminated. Thus, 110 volts can be applied to the primary of one transformer, 115 to another, etc., as required to obtain the desired output voltage.
- 3) Independent control of the plate transformer is afforded by the tap switch S₂. This permits power-input control and does not require an extra autotransformer.

Constant-Voltage Transformers

Although comparatively expensive, special transformers called constant-voltage transformers are available for use in cases where it is necessary to hold line voltage and/or filament voltage constant with fluctuating supply-line voltage. They are rated over a range of 17 v.a. at 6.3 volts output, for small tube-heater demands, up to several thousand volt-amperes at 115 or 230 volts. In average figures, such transformers will hold their output voltages within one per cent under an input-voltage variation of 30 per cent.

CONSTRUCTION OF POWER SUPPLIES

The length of most leads in a power supply is unimportant, so that the arrangement of components from this consideration is not a factor in construction. More important are the points of good high-voltage insulation, adequate conductor size for filament wiring, proper ventilation for rectifier tubes and — most important of all — safety to the operator. Exposed highvoltage terminals or wiring which might be bumped into accidentally should not be permitted to exist. They should be covered with adequate insulation or placed inaccessible to contact during normal operation and adjustment of the transmitter. Power-supply units should be fused individually. All negative terminals of plate supplies and positive terminals of bias sup-

Fig. 7-33—A typical low-valtage pawer supply. The two a.c. connectors permit independent control of filament and high voltage.

plies should be securely grounded to the chassis, and the chassis connected to a waterpipe or radiator ground. All transformer, choke, and capacitor cases should also be grounded to the chassis. A.c. power cords and chassis connectors should be arranged so that exposed contacts are never "live." Starting at the conventional a.c. wall outlet which is female, one end of the cord should be fitted with a male plug. The other end of the cord should have a female receptacle. The input connector of the power supply should have a male receptacle to fit the female receptacle of the cord. The power-output connector on the power supply should be a female socket. A male plug to fit this socket should be connected to the cable going to the equipment. The opposite end of the cable should be fitted with a female connector, and the series should terminate with a male connector on the equipment. If connections are made in this manner, there should be no "live" exposed


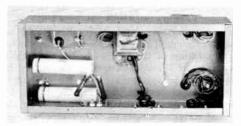


Fig. 7-34. A battom view of the low-voltage pawer supply. The separate filament transfarmer is mounted against the lawer wall af the chassis. The electralytic filter capacitors are mounted on terminal strips. Rubber grommets are used where wires pass through the chassis.

Fig. 7-35—A typical high-voltage supply. The sockets for the 866A mercury-vapor rectifier tubes are spaced from the metal chassis by small cone insulators. Note the insulated tube plate connectors, the safety high-voltage output terminal and the fuse.

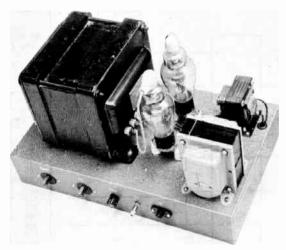

contacts at any point, regardless of where a disconnection may be made.

Rectifier filament leads should be kept short to assure proper voltage at the rectifier socket. Through a metal chassis, grommet-lined clearance holes will serve for voltages up to 500 or 750, but ceramic feed-through insulators should be used for higher voltages. Bleeder and voltage-dropping resistors should be placed where they are open to air circulation. Placing them in confined space reduces the rating.


It is highly preferable from the standpoint of operating convenience to have separate filament transformers for the rectifier tubes, rather than to use combination filament and plate transformers, such as those used in receivers. This permits the transmitter plate voltage to be switched on without the necessity for waiting for rectifier filaments to come up to temperature after each time the high voltage has been turned off. When using a combination power transformer, high voltage may be turned off

without turning the filaments off by using a switch between the transformer center tap and chassis. The switch should be of the rotary type with good insulation between contacts. The shaft of the switch *must* be grounded.

SAFETY PRECAUTIONS

All power supplies in an installation should be fed through a single main power-line switch so that all power may be cut off quickly, either before working on the equipment, or in case of an accident. Spring-operated switches or relays are not sufficiently reliable for this important service. Foolproof devices for cutting off all power to the transmitter and other equipment are shown in Fig. 7-37. The arrangements shown in Fig. 7-37A and B are similar circuits for two-wire (115-volt) and three-wire (230-volt) systems. S is an enclosed double-throw knife switch of the sort usually used as the entrance switch in house installations. J is a standard a.c. outlet and P a shorted plug to fit the outlet. The switch

Fig. 7-36-Bottom view of the highvoltage supply. The electrolytic capacitors (connected in series) are mounted on an insulating board. Voltageequalizing resistors are connected across each capacitor. Separate input connectors are provided for filament and plate power.

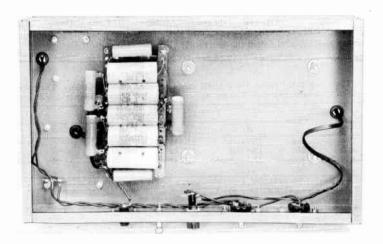

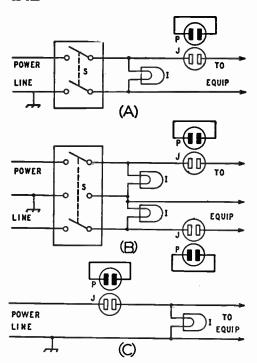


Fig. 7-37—Reliable arrangements for cutting off all power to the transmitter. S is an enclosed double-pole knife-type switch, J a standard a.c. outlet. P a shorted plug to fit the outlet and I a red lamp.

A is for a two-wire 115-volt line, B for a three-wire 230-volt system, and C a simplified arrangement for low-power stations.

should be located prominently in plain sight and members of the household should be instructed in its location and use. I is a red lamp located alongside the switch. Its purpose is not so much to serve as a warning that the power is on as it is to help in identifying and quickly locating the switch should it become necessary for someone else to cut the power off in an emergency.

The outlet J should be placed in some corner out of sight where it will not be a temptation for children or others to play with. The shorting plug can be removed to open the power circuit if there are others around who might inadvertently throw

Selenium-Rectifier Table

All types listed below are rated as follows: Max. input r.m.s. volts — 130, Max. peak innerse volts — 380. Series resistors of 47 ohms are recommended for units rated at less than 65 ma., 22 ohms for 75 and 100-ma. units, 15 ohms for 150-ma. units, and 5 ohms for all higher-current units.

D.C. Ma.	Manufacturer									
Output	A	В	С	D	E	F				
20	1159		8S20							
30			• • • •	8Y1						
35	• • • •		8S35		 .					
50		RS65Q			50					
65	1002A	RS65	6S65	8J1	65	NA-5				
75	1003A	RS75	6S75	5M4	75	NB-5				
100	1004A	RS100	6S100	5M1	100	NC-5				
150	1005A	RS150	6S150	5P1	150	ND-5				
200	1006A	RS200	6S200	5R1	200	NE-5				
250	1028A	RS250	6S250	5Q1	250	NF-5				
300	1090A	RS300	6S300	6Q4	300					
350	1023	RS350	6S350	5QS1		NK-5				
400	1130	RS400	6S400	5S2	400	NH-5				
450		RS450	6S450			NJ-5				
500	1179	RS500	6S500	5S1	500					
600					600					
1000		RS1000				l				

A — Federal.
 B — International.
 C — Mallory
 D — Radio Receptor.
 E — Sarkes-Tarzian.
 F — Sylvania.

the switch while the operator is working on the rig. If the operator takes the plug with him, it will prevent someone from turning on the power in his absence and either injuring themselves or the equipment or perhaps starting a fire. Of utmost importance is the fact that the outlet *I must* be placed in the *ungrounded* side of the line.

Those who are operating low power and feel that the expense or complication of the switch isn't warranted can use the shorted-plug idea as the main power switch. In this case, the outlet should be located prominently and identified by a signal light, as shown in Fig. 7-37C.

The test bench ought to be fed through the main power switch, or a similar arrangement at the bench, if the bench is located remote from the transmitter.

A bleeder resistor with a power rating giving a considerable margin of safety should be used across the output of all transmitter power supplies so that the filter capacitors will be discharged when the high-voltage transformer is turned off.

Silicon Rectifier Table

The types listed below are a small sampling of available rectifiers. They are rated at 750 ma. to a resistive or inductive load, 550 ma. to a capacitive load. VRMs is halved with capacitive-input filter.

P.I.V.	Vrms—		Mar	ufacturer		
	V 5E5	A	В	С		E
200	140	1N441B	1N538	1N3193	1N2485/20H	1N2069
400	280	1N443B	1N540	1N3194	1N2487/40H	1N2070
600	420	1N 547	1N547	1N3195	1N2489/60H	1N2071
800	560			1N3196	******	

A - General Electric, 50° C.

B - International Rectifier, 50° C.

C — RCA, 75° C.

D - Sarkes-Tarzian, 100° C.

E — Sylvania.

Keying and Break-In

Section 12.133 of the FCC regulations says "...The frequency of the emitted...wave shall be as constant as the state of the art permits." It also says "...spurious radiation shall not be of sufficient intensity to cause interference in receiving equipment of good engineering design including adequate selectivity characteristics, which is tuned to a frequency or frequencies outside the frequency band of emission normally required for the type of emission being employed by the amateur station."

There are four factors that have to be considered in the keying of a transmitter. They are envelope shape, r.f. clicks, chirp and backwave.

Envelope Shape

The key clicks that go out on the air with the signal are controlled by the shape of the envelope of the signal. The envelope is the outline of the oscilloscope pattern of your transmitter output, but an oscilloscope isn't needed to observe the effects. Fig. 8-1 shows representative scope pat-

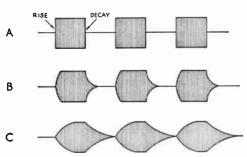


Fig. 8-1—Typical oscilloscope displays of a code transmitter. The rectangular-shaped dots or dashes (A) have serious key clicks extending many kc. either side of the transmitter frequency. Using proper shaping circuits increases the rise and decay times to give signals with the envelope form of B. This signal would have practically no key clicks. Carrying the shaping process too far, as in C, results in a signal that is too "soft" and is not easy to copy.


Oscilloscope displays of this type are obtained by coupling the transmitter r.f. to the vertical plates (Chapter 21) and using a slow sweep speed synchronized to the dot or dash speed of an automatic key.

terns that might be obtained with a given transmitter under various conditions.

It must be emphasized that the on-the-air clicks are determined by the shaping, while the r.f. clicks caused by the spark at the key can only be heard in the station receiver and possibly a broadcast receiver in the same house or apartment.

R.F. Clicks

When any circuit carrying d.c. or a.c. is closed or broken, the small or large spark (depending upon the voltage and current) generates r.f. during the instant of make or break. This r.f. covers a frequency range of many megacycles. When a transmitter is keyed, the spark at the key (and relay, if used) causes a click in the receiver. This click has no effect on the transmitted signal. Since it occurs at the same time that a click (if any) appears on the transmitter output, it must be removed if one is to listen critically to his own signal within the shack. A small r.f. filter is required at the contacts of the key (and relay); typical circuits and values are shown in Fig. 8-2.

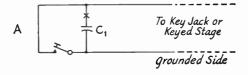



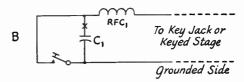


Fig. 8-2—Typical filter circuits to apply at the key (and relay, if used) to minimize r.f. clicks. The simplest circuit (A) is a small capacitor mounted at the key. If this proves insufficient, an r.f. choke can be added to the ungrounded lead (B). The value of C_1 is .001 to .01 μf ., RFC1 can be 0.5 to 2.5 mh., with a current-carrying ability sufficient for the current in the keyed circuit. In difficult cases another small capacitor may be required on the other side of the r.f. choke. In all cases the r.f. filter should be mounted right at the key or relay terminals; sometimes the filter can be concealed under the key. When cathode or center-tap keying is used, the resistance of the r.f. choke or chokes will add cathode bias to the keyed stage, and in this case at highcurrent low-resistance choke may be required, or compensating reduction of the grid-leak bias (if it is used) may be needed. Shielded wire or coaxial cable makes a good keying lead.

A visible spark on "make" can often be reduced by the addition of a small (10 to 100 ohms) resistor in series with C₁ (inserted at point "x"). Too high a value of resistor reduces the arc-suppressing effect on "break."

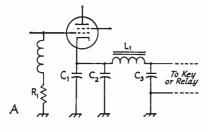To check the effectiveness of the r.f. filter, listen on a lower-frequency band than the transmitter is tuned to, with a short antenna and the receiver gain backed off.



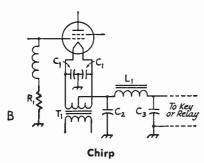

The frequency-stability reference in the opening paragraph refers to the "chirp" observed on many signals. This is caused by a change in frequency of the signal during a single dot or dash.

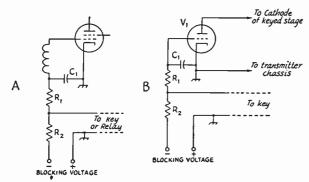


Fig. 8-4—The basic circuit for blocked-grid keying is shown at A. R_1 is the normal grid leak, and the blocking voltage must be at least several times the normal grid bias. The click on make can be reduced by making C_1 larger, and the click on break can be reduced by making R_2 larger. Usually the value of R_2 will be 5 to 20 times the resistance of R_1 . The power supply current requirement depends upon the value of R_2 , since closing the key circuit places R_2 across the blocking voltage supply.

An allied circuit is the vacuum-tube keyer of B. The tube V_1 is connected in the cathode circuit of the stage to be keyed. The values of C_1 , R_1 and R_2 determine the keying envelope in the same way that they do for blocked-grid keying. Values to start with might be 0.47 megohm for R_1 , 4.7 megohm for R_2 and 0.0047 μ f. for C_1 .

The blocking voltage supply must deliver several hundred volts, but the current drain is very low. The 2A3 or other low plateresistance triode is suitable for V_1 . To increase the current-carrying ability of a tube keyer, several tubes can be connected in parallel.

A vacuum-tube keyer adds cathode bias and drops the supply voltages to the keyed stage and will reduce the output of the stage. In oscillator keying it may be impossible to use a v.t. keyer without changing the oscillator d.c. grid return from ground to cathode.

Fig. 8-3—The basic cathode (A) and center-tap (B) keying circuits. In either case C_1 is the r.f. return to ground, shunted by a larger capacitor, C_2 , for shaping. Voltage ratings at least equal to the cut-off voltage of the tube are required. I_1 is the normal filament transformer. C_1 and C_3 can be about 0.01 μ f.

The shaping of the signal is controlled by the values of L_1 and C_2 . Increased capacitance at C_2 will make the signal softer on break; increased inductance at L_1 will make the signal softer on make. In many cases the make will be satisfactory without any inductance.

Values at C_2 will range from 0.5 to 4 μf ., depending upon the tube type and operating conditions. The value of L_1 will also vary with tube type and conditions, and may range from a fraction of a henry to several henrys. When tetrodes or pentodes are keyed in this manner, a smaller value can sometimes be used at C_2 if the screenvoltage supply is fixed and not obtained from the plate supply through a dropping resistor.

Oscillators keyed in the cathode circuit cannot be softened on break indefinitely by increasing the value of C₂ because the grid-circuit time constant enters into the action.

Chirp is an easy thing to detect if you know how to listen for it, although it is amazing how some operators will listen to a signal and say it has no chirp when it actually has. The easiest way to detect chirp is to tune in the code signal at

a low beat note and listen for any change in frequency during a dash. The lower the beat note, the easier it is to detect the frequency change. Listening to a harmonic of the signal will accentuate the frequency change.

The main reason for minimizing chirp, aside from complying with the letter of the regulations, is one of pride, since a properly shaped chirp-free signal is a pleasure to copy and is likely to attract attention by its rarity. Chirps cannot be observed on an oscilloscope pattern of the envelope.

Backwave

The last factor is "backwave," a signal during key-up conditions from some amplifier-keyed transmitters. Some operators listening in the shack to their own signals and hearing a backwave think that the backwave can be heard on the air. It isn't necessarily so, and the best way to check is with an amateur a mile or more away. If he can't hear a backwave on the S9 + signal, you can be sure that it isn't there when the signal is weaker. Backwave is undesirable because it makes a signal harder to copy, even with acceptable shaping and no chirp.

Amplifier Keying

Many two-, three- and even fourstage transmitters are utterly incapable of completely chirp-free amplifier keying because keying the output stage has an effect on the oscillator frequency

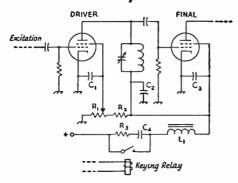


Fig. 8-5—When the driver stage plate voltage is roughly the same as the screen voltage of a tetrode final amplifier, combined screen and driver keying is an excellent system. The envelope shaping is determined by the values of L_1 , C_4 , and R_3 , although the r.f. bypass capacitors C_1 , C_2 and C_3 also have a slight effect. R_1 serves as an excitation control for the final amplifier, by controlling the screen voltage of the driver stage. If a triode driver is used, its plate voltage can be varied for excitation control.

The inductor L_1 will not be too critical, and the secondary of a spare filament transformer can be used if a low-inductance choke is not available. The values of C_4 and R_3 will depend upon the inductance and the voltage and current levels, but good starting values are 0.1 μ f. and 50 ohms.

To minimize the possibility of electrical shock, it is recommended that a keying relay be used in this circuit, since both sides of the circuit are "hot." As in any transmitter, the signal will be chirp-free only if keying the driver stage has no effect on the oscillator frequency.

(The Sigma 41FZ-35-ACS-SIL 6-volt a.c. relay is wellsuited for keying applications.)

and "pulls" through the several stages. This is particularly true when the oscillator stage is on the same frequency as the keyed output stage, but it can also happen when frequency multiplying is involved. Another source of reaction is the variation in oscillator supply voltage under keying conditions, although this can usually be handled by stabilizing the oscillator supply with a VR tube. If the objective is a completely chirp-free transmitter, the first step is to make sure that keying the amplifier stage (or stages) has no effect on the oscillator frequency. This can be checked by listening on the oscillator frequency while the amplifier stage is keyed. Listen for chirp on either side of zero beat to eliminate the possible effect of a chirpy receiver

caused by line-voltage changes or pulling. If no chirp of the steadily running oscillator can be chirp in the stage or stages used for the test. detected, the transmitter can be keyed without This is no assurance that the transmitter can be keyed without chirp in an earlier stage until the same test is passed by the earlier stage.

An amplifier can be keyed by any method that reduces the output to zero. Neutralized stages can be keyed in the cathode circuit, although where powers over 50 or 75 watts are involved it is often desirable to use a keying relay or vacuum tube keyer, to minimize the chances for electrical shock. Tube keying drops the supply voltages and adds cathode bias, points to be considered where maximum output is required. Blocked-grid keying is applicable to many neutralized stages, but it presents problems in high-powered amplifiers and requires a source of negative voltage. Output stages that aren't neutralized such as many of the tetrodes and pentodes in widespread use, will usually leak a little and show some backwave regardless of how they are keyed. In a case like this it may be necessary to key two stages to eliminate backwave. They can be keyed in the cathodes, with blocked-grid keying, or in the screens. When screen keying is used, it is not always sufficient to reduce the screen voltage to zero; it may have to be pulled to some negative value to bring the key-up plate current to zero, unless fixed negative control-grid bias is used. It should be apparent that where two stages are keyed, keying the earlier stage must have no effect on the oscillator frequency if completely chirp-free output is the goal.

Shaping of the keying is obtained in several ways. Blocked-grid and vacuum-tube keyers get suitable shaping with proper choice of resistor and capacitor values, while cathode and screengrid keying can be shaped by using inductors and capacitors. Sample circuits are shown in Figs. 8-3, 8-4 and 8-5, together with instructions for their adjustment. There is no "best" adjustment, since this is a matter of personal preference and what you want your signal to sound like. Most operators seem to like the make to be heavier than the break. All of the circuits shown here are capable of a wide range of adjustment.

If the negative supply in a grid-block keyed stage fails, the tube will draw excessive key-up current. To protect against tube damage in this eventuality, an overload relay can be used or, more simply, a fast-acting fuse can be included in the cathode circuit.

VACUUM-TUBE KEYERS

The practical tube-keyer circuit of Fig. 8-6 can be used for keying any stage of any transmitter. Depending upon the power level of the keyed stage, or more or fewer Type 2A3 tubes can be connected in parallel to handle the necessary current. The voltage drop through a single 2A3 varies from about 70 volts at 50 ma. to 40 volts at 20 ma. Tubes added in parallel will reduce the drop in proportion to the number of tubes used.

When connecting the output terminals of the keyer to the circuit to be keyed, the grounded output terminal of the keyer must be connected to the transmitter ground. Thus the keyer can be used only in negative-lead or cathode keying. When used in cathode keying, it will introduce cathode bias to the stage and reduce the output. This can be compensated for by a reduction in the grid-leak bias of the stage. If an oscillator

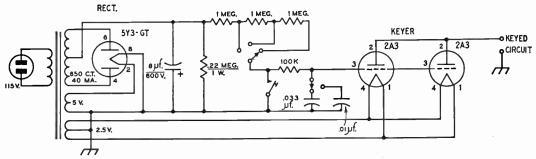


Fig. 8-6—Wiring diagram of a practical vacuum-tube keyer.

stage is keyed, the keyer should be connected in the negative lead, not the cathode.

The negative-voltage supply can be eliminated if a negative voltage is available from some other source, such as a bias supply. A simplified version of this circuit could eliminate the switches and

associated resistors and capacitors, since they are incorporated only to allow the operator to select the combination he prefers. But once the values have been selected, they can be soldered permanently in place. Adjustment of the keying characteristic is the same as with blocked-grid keying.

OSCILLATOR KEYING

One may wonder why oscillator keying hasn't been mentioned earlier, since it is widely used. A sad fact of life is that excellent oscillator keving is infinitely more difficult to obtain than is excellent amplifier keying. If the objective is no detectable chirp, it is probably impossible to obtain with oscillator keying, particularly on the higher frequencies. The reasons are simple. Any keyed-oscillator transmitter requires shaping at the oscillator, which involves changing the operating conditions of the oscillator over a significant period of time. The output of the oscillator doesn't rise to full value immediately so the drive on the following stage is changing, which in turn may reflect a variable load on the oscillator. No oscillator has been devised that has no change in frequency over its entire operating voltage range and with a changing load. Furthermore, the shaping of the keyed-oscillator envelope usually has to be exaggerated, because the following stages will tend to sharpen up the keying and introduce clicks unless they are operated as linear amplifiers.

Acceptable oscillator keying can be obtained on the lower-frequency bands, and the methods used to key amplifiers can be used, but chirpfree clickless oscillator keying is probably not possible at the higher frequencies. Often some additional shaping of the signal will be introduced on "make" through the use of a clamp tube in the output amplifier stage, because the time constant of the screen bypass capacitor plus screen dropping resistor increases the screenvoltage rise time, but it is of no help on the "break" portion of the signal.

Break-In Keying

The usual argument for oscillator keying is that it permits break-in operation, which is true. If break-in operation is not contemplated and as near perfect keying as possible is the objective, then keying an amplifier or two by the methods outlined earlier is the solution. For operating convenience, an automatic transmitter "turner-onner" (see Campbell, QST, Aug., 1956), which will turn on the power supplies and switch antenna relays and receiver muting devices, can be used. The station switches over to the complete "transmit" condition where the first dot is sent, and it holds in for a length of time dependent upon the setting of the delay. It is equivalent to voice-operated phone of the type commonly used by s.s.b. stations. It does not permit hearing the other station whenever the key is up, as does full break-in.

Full break-in with excellent keying is not easy to come by, but it is easier than many amateurs think. Many use oscillator keying and put up with a second-best signal.

Differential Keying

The principle behind "differential" keying is to turn the oscillator on fast before a keyed amplifier stage can pass any signal and turn off the oscillator fast after the keyed amplifier stage has cut off. A number of circuits have been devised for accomplishing the action. One of the simplest can be applied to any grid-block keyed amplifier or tube-keyed stage by the addition of a triode and a VR tube, as in Fig. 8-7. Using this keying system for break-in, the keying will be chirpfree if it is chirp-free with the VR tube removed from its socket, to permit the oscillator to run all of the time. If the transmitter can't pass this test, it indicates that more isolation is required between keyed stage and oscillator.

Another VR-tube differential keying circuit, useful when the screen-grid circuit of an amplifier is keyed, is shown in Fig. 8-8. The normal screen keying circuit is made up of the shaping capacitor C_1 , the keying relay (to remove dangerous voltages from the key), and the resistors R_1 and R_2 .

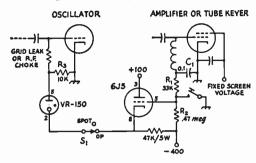


Fig. 8-7—When satisfactory blocked-grid or tube keying of an amplifier stage has been obtained, this VR-tube break-in circuit can be applied to the transmitter to furnish differential keying. The constants shown here are suitable for blocked-grid keying of a 6146 amplifier; with a tube keyer the 6J5 and VR tube circuitry would be the same.

With the key up, sufficient current flows through Rs to give a voltage that will cut off the oscillator tube. When the key is closed, the cathode voltage of the 6J5 becomes close to ground potential, extinguishing the VR tube and permitting the oscillator to operate. Too much shunt capacity on the leads to the VR tube, and too large a value of grid capacitor in the oscillator, may slow down this action, and best performance will be obtained when the oscillator (turned on and off this way) sounds "clicky." The output envelope shaping is obtained in the amplifier, and it can be made softer by increasing the value of C1. If the keyed amplifier is a tetrade or pentade, the screen valtage should be obtained from a fixed voltage source or stiff voltage divider, not from the plate supply through a dropping resistor.

The + supply should be 50 to 100 volts higher than the normal screen voltage, and the - voltage should be sufficient to ignite the VR tube, V_2 , through the drop in R_2 and R_3 . Current through R_2 will be determined by voltage required to cut off oscillator; if 10 volts will do it the current will be 1 ma. For a desirable keying characteristic, R_2 will usually have a higher value than R_1 . Increasing the value of C_1 will soften both "make" and "break."

The tube used at V_2 will depend upon the available negative supply voltage. If it is between 120 and 150, a 0A3/VR75 is recommended. Above this a 0C3/VR105 can be used. The diode, V_1 , can be any diode operated within ratings. A 6AL5 will suffice with screen voltages under 250 and bleeder currents under 5 ma. For maximum life a separate heater transformer should be used for the diode, with the cathode connected to one side of the heater winding.

Clicks in Later Stages

It was mentioned earlier that key clicks can be generated in amplifier stages following the keyed stage or stages. This can be a puzzling problem to an operator who has spent considerable time adjusting the keying in his exciter unit for clickless keying, only to find that the clicks are bad

when the amplifier unit is added. There are two possible causes for the clicks: low-frequency parasitic oscillations and amplifier "clipping."

Under some conditions an amplifier will be momentarily triggered into low-frequency parasitic oscillations, and clicks will be generated when the amplifier is driven by a keyed exciter. If these clicks are the result of low-frequency parasitic oscillations, they will be found in "groups" of clicks occurring at 50- to 150-kc. intervals either side of the transmitter frequency. Of course low-frequency parasitic oscillations can be generated in a keyed stage, and the operator should listen carefully to make sure that the output of the exciter is clean before he blames a later amplifier. Low-frequency parasitic oscillations are usually caused by poor choice in r.f. choke values, and the use of more inductance in the plate choke than in the grid choke for the same stage is recommended.

When the clicks introduced by the addition of an amplifier stage are found only near the transmitter frequency, amplifier "clipping" is indicated. It is quite common when fixed bias is used on the amplifier and the bias is well past the "cut-off" value. The effect can usually be minimized by using a combination of fixed and gridleak bias for the amplifier stage. The fixed bias should be sufficient to hold the key-up plate current only to a low level and not to zero.

A linear amplifier (Class AB₁, AB₂ or B) will amplify the excitation without adding any clicks, and if clicks show up a low-frequency parasitic oscillation is probably the reason.

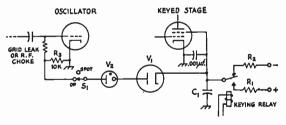


Fig. 8-8—VR-tube differential keying in an amplifier screen circuit.

With key up and current flowing through V1 and V2, the oscillator is cut off by the drop through R₃. The keyed stage draws no current because its screen grid is negative. C1 is charged negatively to the value of the source. When the relay is energized, C1 charges through R_1 to a + value. Before reaching zero (on its way +) there is insufficient voltage to maintain ionization in V2, and the current is broken in R₃, turning on the oscillator stage. As the screen voltage goes positive, the VR tube, V₂, cannot reignite because the diade, V₁, will not conduct in that direction. The oscillator and keyed stage remain on as long as the relay is closed. When the relay opens, the voltage across C1 must be sufficiently negative for V2 to ionize before any bleeder current will pass through Rs. By this time the screen of the keyed stage is so far negative that the tube has stopped conducting. (See Fig. 8-5 for suitable relay.)

TESTING YOUR KEYING

The choice of a keying circuit is not as important as its testing. Any of the circuits shown in this chapter can be made to give satisfactory keying, but must be adjusted properly.

The easiest way to find out what your keyed signal sounds like on the air is to trade stations with a near-by ham friend some evening for a short QSO. If he is a half mile or so away, that's fine, but any distance where the signals are still S9 will be satisfactory.

After you have found out how to work his rig, make contact and then have him send slow dashes, with dash spacing. (The letter "T" at about 5 w.p.m.) With minimum selectivity, cut the r.f. gain back just enough to avoid receiver overloading (the condition where you get crisp signals instead of mushy ones) and tune slowly from out of beat-note range on one side of the signal through to zero and out the other side. Knowing the tempo of the dashes, you can readily identify any clicks in the vicinity as yours or someone else's. A good signal will have a thump on "make" that is perceptible only where you can also hear the beat note, and the click on "break" should be practically negligible at any point. If your signal is like that, it will sound good, provided there are no chirps. Then have him run off a string of fast dots with the bug - if they are easy to copy, your signal has no "tails" worth worrying about and is a good one for any speed up to the limit of manual keying. Make one last check with the selectivity in, to see that the clicks off the signal are negligible even at high signal level.

If you don't have any convenient friends with whom to trade stations, you can still check your keying, although you have to be a little more careful. The first step is to get rid of the r.f. click at the key, as described earlier.

So far you haven't done a thing for your signal on the air and you still don't know what it sounds like, but you may have cleaned up some clicks in the broadcast set. Now disconnect the antenna from your receiver and short the antenna

terminals with a short piece of wire. Tune in your own signal and reduce the r.f. gain to the point where your receiver doesn't overload. Detune any antenna trimmer the receiver may have. If you can't avoid overload within the r.f. gain-control range, pull out the r.f. amplifier tube and try again. If you still can't avoid overload, listen to the second harmonic as a last resort. An overloaded receiver can generate clicks.

Describing the volume level at which you should set your receiver for these "shack" tests is a little difficult. The r.f. filter should be effective with the receiver running wide open and with an antenna connected. When you turn on the transmitter and take the other steps mentioned to reduce the signal in the receiver, run the audio up and the r.f. down to the point where you can just hear a little "rushing" sound with the b.f.o. off and the receiver tuned to the signal. This is with the selectivity in. At this level, a properly adjusted keying circuit will show no clicks off the rushing-sound range. With the b.f.o. on the same gain setting, there should be no clicks outside the beat-note range. When observing clicks, make the slow-dash and fast dot tests outlined previously.

Now you know how your signal sounds on the air, with one possible exception. If keying your transmitter makes the lights blink, you may not be able to tell too accurately about the chirp on your signal. However, if you are satisfied with the absence of chirp when tuning either side of zero beat, it is safe to assume that your receiver isn't chirping with the light flicker and that the observed signal is a true representation. No chirp either side of zero beat is fine. Don't try to make these tests without first getting rid of the r.f. click at the key, because clicks can mask a chirp.

The least satisfactory way to check your keying is to ask another ham on the air how your keying sounds. It is the least satisfactory because most hams are reluctant to be highly critical of another amateur's signal. In a great many cases they don't actually know what to look for or how to describe any aberrations they may observe.

MONITORING OF KEYING

In general, there are two common methods for monitoring one's "fist" and signal. The first, and perhaps less common type, involves the use of an audio oscillator that is keyed simultaneously with the transmitter.

The second method is one that permits receiving the signal through one's receiver, and this generally requires that the receiver be tuned to

the transmitter (not always convenient unless working on the same frequency) and that some method be provided for preventing overloading of the receiver, so that a good replica of the transmitted signal will be received. Except where quite low power is used, this usually involves a relay for simultaneously shorting the receiver input terminals and reducing the receiver gain.

BREAK-IN OPERATION

Break-in operation is most easily obtained with a separate receiving antenna, since none of the available antenna change-over relays is fast enough to follow keying. The receiving antenna should be installed as far as possible from the transmitting antenna. It should be mounted at right angles to the transmitting antenna and fed with low pick-up lead-in material such as co-

axial cable or 300-ohm Twin-Lead, to minimize pick-up.

If a low-powered transmitter is used, it is often quite satisfactory to use no special equipment for break-in operation other than the separate receiving antenna, since the transmitter will not block the receiver too seriously. Even if the transmitter keys without clicks, some clicks will be heard when the receiver is tuned to the transmitter frequency because of overload in the receiver. An output limiter, as described in Chapter Five, will wash out these clicks and permit good break-in operation even on your transmitter frequency.

When powers above 25 or 50 watts are used, special treatment is required for quiet break-in on the transmitter frequency. A means should be provided for shorting the input of the receiver when the code characters are sent, and a means for reducing the gain of the receiver at the same time is often necessary. The system shown in Fig. 8-9 permits quiet break-in operation for higher-powered stations. It requires a simple operation on the receiver but otherwise is perfectly straightforward. R_1 is the regular receiver r.f. and i.f. gain control. The ground lead is lifted on this control and run to a rheostat, R_2 , that goes to ground. A wire from the junction runs outside the receiver to the keying relay, K_1 . When the key

is up, the ground side of R_1 is connected to ground through the relay arm, and the receiver is in its normal operating condition. When the key is closed, the relay closes, which breaks the ground connection from R_1 and applies additional bias to the tubes in the receiver. This bias is controlled by R_2 . When the relay closes, it also closes the circuit to the transmitter oscillator. A filter at the key suppresses the clicks caused by the relay current.

The keying relay should be mounted on the receiver as close to the antenna terminals as possible, and the leads shown heavy in the diagram should be kept short, since long leads will allow too much signal to get through into the receiver. Use a good high-speed keying relay.

A few of the recent communications receivers bring the return lead from the r.f. gain control to a normally shorted terminal at the rear of the receiver. The preceding break-in system can be readily applied to a receiver of this type, and it will repay the receiver owner to study the instruction book and determine if his receiver already has this connection made in it. Other receivers have provision for reducing the gain or for blanking the receiver; one popular model has provision for bringing in negative bias from a transmitter grid leak to cut off an audio stage during transmit periods.

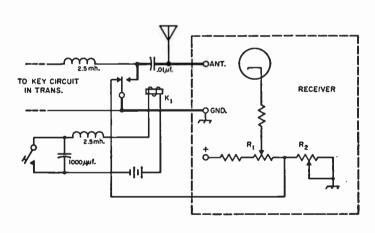


Fig. 8-9—Wiring diagram for smooth break-in operation. The lead shown as a heavy line and the lead from bottom relay contact to ANT post on receiver should be kept as short as possible for minimum pickup of transmitter signal. R₁—Receiver manual gain control.

R₂—5000- or 10,000-ohm wire-wound potentiometer. K₁—S.p.d.t. keying relay. (Sigma 41FZ-35-ACS-SIL or equiv.) Although battery and d.c. relay are shown, any suitable a.c. or d.c. relay and power source can be used.

RECEIVER MUTING AND GRID-BLOCK KEYING

The muting system shown in Fig. 8-10 can be used with any grid-block or tube-keyed transmitter, and it is particularly applicable to the VR-tube differential keying circuit of Fig 8-7. Referring to Fig. 8-10, R_1 , R_2 and C_1 have the same values and functions that the similarly designated components in Figs. 8-4 and 8-7 have. When the key is open, a small current will flow through R_3 , the 0A2 and R_2 , and the voltage drop across R_3 will be sufficient to cut off the 6C4. With the 6C4 cut off, there is no current through R_4 and consequently no voltage appearing across R_4 . The voltage of the receiver a.g.c. bus is zero with respect to ground.

When the key is closed, there is insufficient voltage across the 0A2 to maintain conduction, and consequently there is no current flow through R_3 . With zero voltage between grid and cathode, the 6C4 passes current. The drop across R_4 , and thus the negative voltage applied to the a.g.c. line in the receiver, is determined by the value of R_4 . Thus the key-down gain of the receiver can be adjusted to permit listening to one's own signal, by increasing the value of R_4 until the receiver output level is a comfortable one. To utilize the same antenna for transmitting and receiving, and thus benefit during receiving from any directional properties of the antenna, an electronic transmit-

TO GRID OF KEYED STAGE

C1

R1

OA2

GC4

R2

R3

R3

R4

R5C1

TO RCV
A.V.C
BUS

Fig. 8-10—Circuit diagram of a receiver muter for use with grid-block or tube keying.

C₁—Shaping capacitor, see text.

R₁, R₂—Shaping resistors, see text.

R₈-0.1 megohm.

R₄-15,000-ohm 2-watt potentiometer.

RFC₁-1 mh. or less.

receive switch can be used (see later in this chapter).

The receiver a.g.c. bus can be located by reference to the receiver instruction manual, and connection be made to it through a length of shielded wire. The a.g.c. switch in the receiver must be turned to on for the muter to be effective.

If desired, the muting circuit can be built into the transmitter, or it can be mounted on a shelf or small chassis behind the receiver. The two negative voltages can be furnished by one supply and a reasonably heavy voltage divider; the main requirement of the supply is that the nominal—125 volts remain below the normal voltage drop of the 0A2 (150 volts). Installation of the muting circuits should have little or no effect on the keying characteristic of the transmitter; if it does the characteristic can be restored by proper values for R_1 , R_2 and C_1 .

THE "MATCHTONE"

The "Matchtone" is a c.w. tone-generating monitor using a transistor audio oscillator. A diode rectifier in the antenna circuit or the d.c. from a "Monimatch" (see Chap. 13) serves as the keyed source of d.c. power. In addition to the usual function it can be used by the sightless amateur as an audible transmitter-antenna tuning indicator.

While direct monitoring of c.w. transmissions via the receiver is a preferred method because it can reveal much about the keying characteristics, transmissions offset from the receiving frequency call for a separate monitor. The self-powered transistorized monitor fills the bill nicely. The use of the r.f bridge, already connected in the r.f. transmission line, as a source of power for the monitor is a logical choice.

The circuit of the Matchtone and the connections to the Monimatch and the receiver are shown in Fig. 8-11. A small 2- or 3-to-1 push-pull grid-to-plate audio interstage transformer is used for feedback as well as for coupling to the receiver. If a transformer having a p.p. grid winding is not available from the junk box, the audio coupling to the receiver can be obtained by connecting C_2 to the ungrounded end of R_1 . While use of a low value of capacitance for C_2 is necessary to avoid excessive shunting of the high impedance receiver audio circuit, the value shown will provide sufficient coupling for a good audio tone level from the monitor. A third possibility for the audio out-put connection from the monitor is to substitute the headphones for R1, together with a singlepole double-throw switch or relay to switch the phones between the monitor and the receiver. The on-off switch, S_1 , can be made a part of R_2 by use of a volume control switch attachment.

The value shown for C_1 gives an audio pitch in the 500-1000 cycle range, depending somewhat on the particular transformer, the setting of R_2 and the transmitter output power. Other values of C_1 can be used to adjust the pitch to the

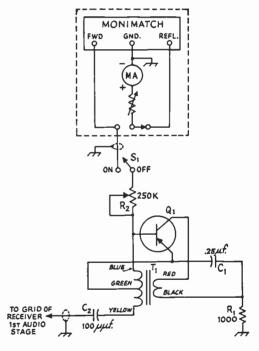


Fig. 8-11—Circuit of the Matchtone. Section enclosed in dashed line is the Monimatch and its indicating circuit; a simple r.f. rectifier will also serve as the d.c. source. Braid of shielded lead to audio grid should connect to receiver chassis.

C₁-Paper.

C₂—Mica or ceramic.

Q1-2N109, CK722 or similar.

R₁-1000 ohms, ½ watt.

R₂-0.25-megohm volume control.

S₁—S.p.s.t. toggle.

T₂—Push-pull interstage audio transformer, 2:1 or 3:1 total grid to plate.

Speed Keys 251

operator's individual preference. R_2 may be adjusted to compensate for the changes in the d.c. current from the rectifier or Monimatch caused by a change in transmitter frequency band or power. Using either a 2N109 or a CK722 transistor, the circuit should oscillate with usable audio level with as little as 0.1 ma. d.c. flowing to ground through the monitor. Other low-cost transistors such as the 2N107 and the 2N170 should work equally well.

Because the pitch of the audio tone is to some degree dependent upon the d.c. voltage obtained from the source, the pitch gives a reasonably accurate indication of correct final amplifier plate circuit tuning (maximum power output) and, if an antenna tuner is used, will also indicate resonance of the tuner to the transmitter output frequency. This characteristic of the Matchtone should be of considerable aid to sightless amateurs. (From QST, January, 1958.)

SPEED KEYS

The average operator finds that a speed of 20 to 25 words per minute is the limit of his ability with a straight hand key. However, he can increase his speed to 30 to 40 w.p.m. by the use of a "speed key." The mechanical speed keys, available in most radio stores, give additional speed by making strings of dots when the key lever is pushed to the right; dashes are made manually by closing the key to the left. After practicing with the speed key, the operator obtains the correct "feel" for the key, which allows him to release the dot lever at exactly the right time to make the required number of dots. A speed key can deliver practically perfect code characters

when used by an operator who knows what good code sounds like; however, one will not compensate for an operator's poor code ability.

An electronic speed key will not compensate for an operator's poor sending ability, either. However, the electronic speed key has the feature that it makes strings of both dots and of dashes, by proper manipulation of the key lever, and in current designs the dashes are self-completing. This means that it is impossible to send anything but the correct length of dash when the key lever is closed on the dash side. It is, of course, possible to send an incorrect number of dashes through poor operator timing.

KEYING SPEEDS

In radio telegraphy the basic code element is the dot, or unit pulse. A dot and space is two unit pulses, and a dash is three unit pulses long. The space between letters is three unit pulses, and the space between words is seven unit pulses. A speed of one baud is one pulse per second.

Assuming that a speed key is adjusted to give

the proper dot, space and dash values mentioned above, the code speed can be found from

Speed (w.p.m.) =
$$\frac{dots/min.}{25}$$

E.g.: A properly adjusted electronic key gives a string of dots that counts to 10 dots per second. Speed = $(60 \times 10) \div 25 = 24 \text{ w.p.m.}$

AN ELECTRONIC SPEED KEY

The unit shown in Figs. 8-12 and 8-14 represents one of the simpler designs of an electronic key. The total cost of the key, in dollars and construction time, is quite low. The keying lever is made from parts taken from two straight telegraph keys; these are available at less than a dollar each in the war-surplus version (J-38). A more elegant keying lever can be built from a (more-expensive) war-surplus mechanical speed key.

Referring to Fig. 8-13, the timing of the key is provided by the oscillator V_{1A} . When the key is closed, a sawtooth wave is generated by the fast charge and slow discharge of the .25- μ f. capacitor in the cathode circuit. The rate of discharge is set by the total resistance across the capacitor, and the voltage to which the capacitor is charged is determined by the setting of R_1 . The sawtooth wave, applied to the grid of V_{2A} , cannot drive the grid very positive because the 3.3-megohm resistor limits the current; the effect is to "clip the tops" of the sawtooth cycles. The voltage at which V_{2A} passes enough current to close

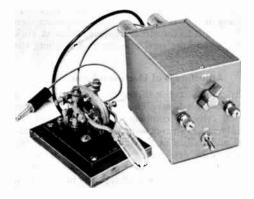


Fig. 8-12—This electronic speed key has a range of approximately 8 to 35 w.p.m., set by the speed control at top center. It has relay output and can be used with any transmitter that can be keyed by a hand key. The key (left) is made from two telegraph keys and a pair of 1/2-inch thick sheet plastic paddles.

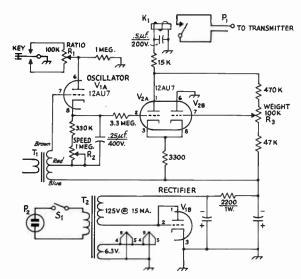


Fig. 8-13—Circuit diagram of the electronic speed key. Unless otherwise specified, resistors are ½ watt. Polarity-marked capacitors are electrolytic, others are tubular paper.

K₁--5000-ohm 3-ma. relay (Sigma 41F-5000S-SIL).

P₁—Phone plug.

P2-A.c. line plug.

R₁, R₃—100,000-ohm potentiometer, linear taper.

 R_2 -1-megohm potentiometer, linear taper.

S₁—S.p.s.t. toggle.

T₁—5-watt 25,000-to-4-ohm output transformer, secondary not used (Stancor A-38.57).

T₂—125-v. 15-ma. and 6.3-v. 0.6-amp. transformer (Stancor PS-8415 or similar).

the relay is set by the position of the arm of R_a .

Except for the tubes, the keyer circuit is housed in a grey Hammertone $6 \times 5 \times 4$ -inch Minibox (Bud CU-2107), as shown in Fig. 8-14. The tube sockets are mounted so that the two tubes project outside at the rear of the unit. The power transformer is mounted on the rear wall, and the toggle switch and the three controls are mounted on the "front" panel. The power line to P_2 , the two-wire cable to P_1 , and the three-wire cable to the key leave the cabinet at the rear through individual rubber grommets. Use multiple tie points generously for the support of the fixed resistors and capacitors.

To make the key, first remove the keys from their bases and strip the bases of their remaining hardware. The four support legs for the key are formed from the original tie strips and shorting switch arms. At the front they bolt to the key frame at the countersunk holes; at the rear they make up to the binding posts. The three-wire cable connects to two binding posts and a supporting leg. A heavy base of ½-inch thich steel adds weight to the structure, and rubber or cork feet glued to the steel prevent its scratching the table.

Adjustment of Electronic Speed Key

In operation, the three controls will serve as their labels indicate. There is a unique (but not highly critical) combination of settings of the weight and ratio controls that will give automatic dots and dashes at the same speed; this setting can only be determined by ear and will be dependent on how well the operator can recognize good code. If the operator taps his foot to count groups of four dots or two dashes, the dots and dashes will have the same speed when the beat is

the same. It is easy to determine whether dots or dashes are too heavy or too light. Connect an ohmmeter to P_1 ; holding the dot lever closed should make the ohmmeter needle hover around half scale, and holding the dash lever closed should make the ohmmeter hover around 75 per cent of the short-circuit reading. Lacking an ohmmeter, the transmitter plate milliammeter can be used; dots and dashes should give 50 per cent and 75 per cent of the key-down value when the keyer controls have been properly adjusted.

QST articles describing other types of electronic speed keys include:

Bartlett, "Compact Automatic Key Design," Dec., 1951. Old "Transistorized Electronic Key and Monitor," May,

1959.
Kanda, "The 'Ultimatic'——Transistorized," Sept., Oct., 1960.

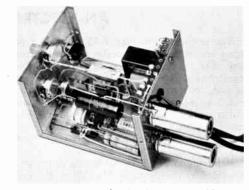


Fig. 8-14—Components for the electronic speed key are mounted on the three walls of a Minibox section, with the tubes projecting out the back. Keep wires away from screw holes, to prevent short circuits when the box is assembled.

ELECTRONIC TRANSMIT-RECEIVE SWITCHES

No antenna relay is fast enough to switch an antenna from transmitter to receiver and back

at normal keying speeds. As a consequence, when it is desired to use the same antenna for trans-

mitting and receiving (a "must" when directional antennas are used) and to operate c.w. break-in or voice-controlled sideband, and electronic switch is used in the antenna. The word "switch" is a misnomer in this case; the transmitter is connected to the antenna at all times and the t.r. "switch" is a device for preventing burn-out of the receiver by the transmitter.

One of the simplest approaches is the circuit shown in Fig. 8-15. The 6C4 cathode follower couples the incoming signal on the line to the receiver input with only a slight reduction in gain. When the transmitter is "on," the grid of the 6C4 is driven positive and the rectified current biases the 6C4 so that it can pass very little power on to the receiver. The factors that limit the r.f voltage the circuit can handle are the voltage break-down rating of the 47- $\mu\mu$ f. capaci-


Fig. 8-15—Schematic diagram of cathode-follower t.r. switch. Resistors are ½-watt. The unit should be assembled in a small chassis or shield can and mounted on or very close to the receiver antenna terminals. The transmitter transmission line can be connected at the coaxial jack with an M-358 Tee adapter.

The heater and plate power can be "borrowed" from the receiver in most cases.

tor and the voltage that may be safely applied between the grid and cathode of the tube.

To avoid stray pick-up on the lead between the cathode and the antenna terminal of the receiver, this lead should be kept as short as possible. The entire unit should be shielded and mounted on the receiver near the antenna terminals. In wiring the tube socket, input and output circuit components and wiring should be separated to reduce feed-through by stray coupling.

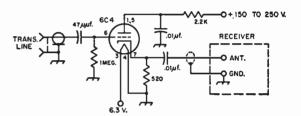The switch should be connected to the transmitter by as short a length of coaxial cable as possible, particularly if the higher-frequency bands (21 and 28 Mc.) are commonly used. If this rule is not observed, there may be conditions where a loss of received signal will be noticed, caused by resonant conditions in the cable and the transmitter output circuit.



SELF-CONTAINED ALL-BAND ELECTRONIC T.R. SWITCH



The t.r. switch shown in Fig. 8-16 differs in several ways from the preceding example. It contains its own power supply and consequently can be used with any transmitter/receiver combination without "borrowing" power. It will add gain and front-end selectivity to the receiver. A commercial switch-coil-capacitor combination is shown in the unit, although the constructor could-build his own if desired.

Referring to the circuit diagram in Fig. 8-17, one triode of a 12AU7 is used as an amplifier stage, followed by the other triode as a cathode-follower stage to couple between the tuned circuit and the receiver. As in the simpler switch, the triodes are biased during transmission periods by rectified grid current, and insufficient power is passed along to the receiver to injure its input circuit.

The t.r. switch is intended to mount behind the transmitter near its output terminal, so that the connecting cable is short. The lead from the t.r. switch to the receiver can be any reasonable length. Components are mounted on the sides and walls of the chassis, although a small bracket will be needed to support the tube socket and another is required to hold the far end of the coil L_1 . The single coil bracket, aided by panel bushings for

Fig. 8-16—The electronic t.r. switch is built in a $5 \times 9 \times 2\frac{1}{2}$ -inch chassis; the bottom plate has been removed to show the placement of parts. Although two receiver outlets are shown on the near face (a phono jack and a coaxial receptacle), only one is required, depending upon one's choice of cable termination.

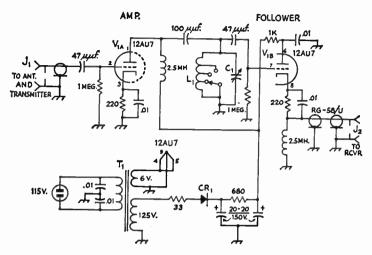


Fig. 8-17—Circuit diagram of the electronic t.r. switch. Unless otherwise specified, resistances are in ohms, resistors are $\frac{1}{2}$ watt, capacitances are in μ f.

C₁—140-μμf. variable (part of Harrington GP-20 tuner). CR₁—200-ma. 360-p.i.v. silicon rectifier (Sarkes Tarzian K-200).

 $J_1\text{--}\text{Coaxial}$ receptacle and tee fitting (SO-239 and M-358).

J₃-Coaxial receptacle or phono jack.

the switch and capacitor C_1 shafts, is sufficient support for the coil-and-capacitor assembly. In wiring the switch, a length of RG-58/U should be used between the cathode-follower load (resistor and r.f. choke) and the output jack J_2 , to minimize "feedthrough" around the tube. A pair of 0.01 μ f. disk ceramic capacitors across the a.c. line where it enters the chassis helps to hold down the r.f. that might otherwise ride in on the a.c. line.

In operation, it is only necessary to switch the unit to the band in use and peak capacitor C_1 for

L₁—52 turns No. 24 on ¾-inch diam. form, 28 t.p.i.

Tapped at 5½, 8½, 13 and 24 turns from grounded end. (Part of Harrington GP-20 tuner).

T₁—125-v. 15-ma., 6-v. 0.6-amp. transformer (Stancor PS-8415) (GP-20 tuner available from Harrington Electronics, Box 189, Topsfield, Mass.).

maximum signal or background noise. A significant increase in signal or background noise should be observed on any band within the range of the coil/capacitor combination.

TVI and T.R. Switches

The preceding t.r. switches generate harmonics when their grid circuits are driven positive, and these harmonics can cause TVI if steps are not taken to prevent it. Either switch should be well-shielded and used in the antenna transmission line between transmitter and low-pass filter.

Speech Amplifiers and Modulators

The audio amplifiers used in radiotelephone transmitters operate on the principles outlined earlier in this book in the chapter on vacuum tubes. The design requirements are determined principally by the type of modulation system to be used and by the type of microphone to be employed. It is necessary to have a clear understanding of modulation principles before the problem of laying out a speech system can be approached successfully. Those principles are discussed under appropriate chapter headings.

The present chapter deals with the design of audio amplifier systems for communication purposes. In voice communication the primary objective is to obtain the most effective transmission; i.e., to make the message be understood at the receiving point in spite of adverse conditions created by noise and interference. The methods used to accomplish this do not necessarily coincide with the methods used for other purposes,

such as the reproduction of music or other program material. In other words, "naturalness" in reproduction is distinctly secondary to intelligibility.

The fact that satisfactory intelligibility can be maintained in a relatively narrow band of frequencies is particularly fortunate, because the width of the channel occupied by a phone transmitter is directly proportional to the width of the audio-frequency band. If the channel width is reduced, more stations can occupy a given band of frequencies without mutual interference.

In speech transmission, amplitude distortion of the voice wave has very little effect on intelligibility. The importance of such distortion in communication lies almost wholly in the fact that many of the audio-frequency harmonics caused by it lie outside the channel needed for intelligible speech, and thus will create unnecessary interference to other stations.

SPEECH EQUIPMENT

In designing speech equipment it is necessary to know (1) the amount of audio power the modulation system must furnish and (2) the output voltage developed by the microphone when it is spoken into from normal distance (a few inches) with ordinary loudness. It then becomes possible to choose the number and type of amplifier stages needed to generate the required audio power without overloading or undue distortion anywhere in the system.

MICROPHONES

The level of a microphone is its electrical output for a given sound intensity. Level varies greatly with microphones of different types, and depends on the distance of the speaker's lips from the microphone. Only approximate values based on averages of "normal" speaking voices can be given. The values given later are based on close talking; that is, with the microphone about an inch from the speaker's lips.

The frequency response or fidelity of a microphone is its relative ability to convert sounds of different frequencies into alternating current. For understandable speech transmission only a limited frequency range is necessary, and intelligible speech can be obtained if the output of the microphone does not vary more than a few decibels at any frequency within a range of about 200 to 2500 cycles. When the variation expressed in terms of decibels is small between two fre-

quency limits, the microphone is said to be flat between those limits.

Carbon Microphones

The carbon microphone consists of a metal diaphragm placed against an insulating cup containing loosely-packed carbon granules (microphone button). When used with a vacuum-tube amplifier, the microphone is connected in the cathode circuit of a medium- μ triode, as shown in Fig. 9-1A.

Sound waves striking the diaphragm cause it to vibrate in accordance with the sound, and the pressure on the granules alternately increases and decreases, causing a corresponding decrease and increase in the electrical resistance of the microphone. The instantaneous value of this resistance determines the instantaneous value of plate current through the tube, and as a consequent the voltage drop across the plate load resistor increases and decreases with the increases and decreases in granule pressure.

The carbon microphone finds its major amateur application in mobile and portable work; a good microphone in the circuit of Fig. 9-1A will deliver 20 to 30 volts peak output.

Piezo-electric Microphones

The crystal microphone makes use of the piezoelectric properties of Rochelle salts crystals. This type of microphone requires no battery or

transformer and can be connected directly to the grid of an amplifier tube. It is a popular type of microphone among amateurs, for these reasons as well as the fact that it has good frequency response and is available in inexpensive models. The input circuit for the crystal microphone is shown in Fig. 9-1B.

Although the level of crystal microphones varies with different models, an output of 0.03 volt or so is representative for communication types. The level is affected by the length of the cable connecting the microphone to the first amplifier stage; the above figure is for lengths of 6 or 7 feet. The frequency characteristic is unaffected by the cable, but the load resistance (amplifier grid resistor) does affect it; the lower frequencies are attenuated as the value of load resistance is lowered. A grid-resistor value of at least 1 megohm should be used for reasonably flat response, 5 megohms being a customary figure.

The ceramic microphone utilizes the piezoelectric effect in certain types of ceramic materials to achieve performance very similar to that of the crystal microphone. It is less affected by temperature and humidity. Output levels are similar to those of crystal microphones for the same type of frequency response.

Velocity and Dynamic Microphones

In a velocity or "ribbon" microphone, the element acted upon by the sound waves is a thin corrugated metallic ribbon suspended between the poles of a magnet.

Velocity microphones are built in two types, high impedance and low impedance, the former being used in most applications. A high-impedance microphone can be directly connected to the grid of an amplifier tube, shunted by a resistance of 0.5 to 5 megohms (Fig. 9-1C). Low-impedance microphones are used when a long connecting cable (75 feet or more) must be employed. In such a case the output of the microphone is coupled to the first amplifier stage through a suitable step-up transformer, as shown in Fig. 9-1D.

The level of the velocity microphone is about 0.03 to 0.05 volt. This figure applies directly to the high-impedance type, and to the low-impedance type when the voltage is measured across the secondary of the coupling transformer.

The dynamic microphone somewhat resembles a dynamic loud-speaker. A lightweight voice coil is rigidly attached to a diaphragm, the coil being suspended between the poles of a permanent magnet. Sound causes the diaphragm to vibrate, thus moving the coil back and forth between the magnet poles and generating an alternating voltage.

The dynamic microphone usually is built with high-impedance output, suitable for working directly into the grid of an amplifier tube. If the connecting cable must be unusually long, a low-impedance type should be used, with a step-up transformer at the end of the cable.

In general, the dynamic microphones have the

smoothest peak-free response and widest frequency range, and they are also the least susceptible to damage from shock and extremes of temperature and humidity.

THE SPEECH AMPLIFIER

The audio-frequency amplifier stage that causes the r.f. carrier output to be varied is called the modulator, and all the amplifier stages preceding it comprise the speech amplifier. Depending on the modulator used, the speech amplifier may be called upon to deliver a power output ranging from practically zero (only voltage required) to 20 or 30 watts.

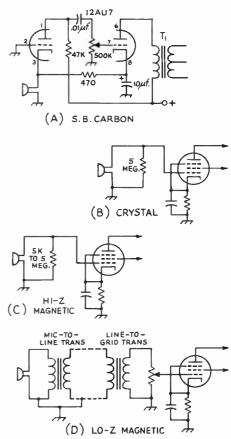


Fig. 9-1—Speech input circuits used with various types of microphones.

Before starting the design of a speech amplifier, therefore, it is necessary to have selected a suitable modulator for the transmitter. This selection must be based on the power required to modulate the transmitter, and this power in turn depends on the type of modulation system selected, as described in Chapter 10. With the modulator picked out, its driving-power requirements (audio power required to excite the modulator to full output) can be determined from the tube tables in a later chapter. Generally speaking, it is advisable to choose a tube or tubes for

Speech Equipment

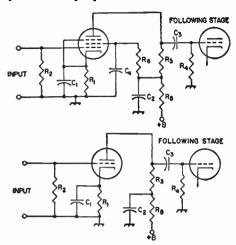


Fig. 9-2—Resistance-coupled voltage-amplifier circuits. A, pentode; B, triode. Designations are as follows:

C₁-Cathode bypass capacitor.

C₂-Plate bypass capacitor.

C3-Output coupling capacitor (blocking capacitor).

C₄-Screen bypass capacitor.

R₁-Cathode resistor.

R2-Grid resistor.

R₃-Plate resistor.

R₄-Next-stage grid resistor.

R₅-Plate decoupling resistor.

R₆-Screen resistor.

Values for suitable tubes are given in Table 9-1. Values in the decoupling circuit, C₂R₅ are not critical. R₅ may be about 10% of R₃; an 8- or 10-\mu f. electrolytic capacitor is usually large enough at C₂.

the last stage of the speech amplifier that will be capable of developing at least 50 per cent more power than the rated driving power of the modulator. This will provide a factor of safety so that losses in coupling transformers, etc., will not upset the calculations.

Voltage Amplifiers

If the last stage in the speech amplifier is a Class AB_2 or Class B amplifier, the stage ahead of it must be capable of sufficient power output to drive it. However, if the last stage is a Class AB_1 or Class A amplifier the preceding stage can be simply a voltage amplifier. From there on back to the microphone, all stages are voltage amplifiers.

The important characteristics of a voltage amplifier are its voltage gain, maximum undistorted output voltage, and its frequency response. The voltage gain is the voltage-amplification ratio of the stage. The output voltage is the maximum a.f. voltage that can be secured from the stage without distortion. The amplifier frequency response should be adequate for voice reproduction; this requirement is easily satisfied.

The voltage gain and maximum undistorted output voltage depend on the operating conditions of the amplifier. Data on the popular types of tubes used in speech amplifiers are given in Table 9-I, for resistance-coupled amplification. The output voltage is in terms of *peak* voltage rather than r.m.s.; this makes the rating independent of the waveform. Exceeding the peak value causes the amplifier to distort, so it is more useful to consider only peak values in working with amplifiers.

Resistance Coupling

Resistance coupling generally is used in voltage-amplifier stages. It is relatively inexpensive, good frequency response can be secured, and there is little danger of hum pick-up from stray magnetic fields associated with heater wiring. It is the most satisfactory type of coupling for the output circuits of pentodes and high- μ triodes, because with transformers a sufficiently high load impedance cannot be obtained without considerable frequency distortion. Typical circuits are given in Fig. 9-2 and design data in Table 9-I.

Transformer Coupling

Transformer coupling between stages ordinarily is used only when power is to be transferred (in such a case resistance coupling is very inefficient), or when it is necessary to couple between a single-ended and a push-pull stage. Triodes having an amplification factor of 20 or less are used in transformer-coupled voltage amplifiers. With transformer coupling, tubes should be operated under the Class A conditions given in the tube tables at the end of this book.

Representative circuits for coupling singleended to push-pull stages are shown in Fig. 9-3.

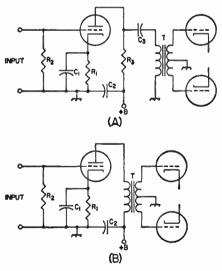


Fig. 9-3—Transformer-coupled amplifier circuits for driving a push-pull amplifier. A is for resistance-transformer coupling; B for transformer coupling. Designations correspond to those in Fig. 9-2. In A, values can be taken from Table 9-1. In B, the cathode resistor is calculated from the rated plate current and grid bias as given in the tube tables for the particular type of tube used.

TABLE 9-I-RESISTANCE-COUPLED VOLTAGE-AMPLIFIER DATA

Data are given for a plate supply of 300 valts. Departures of as much as 50 per cent from this supply valtage will not materially change the operating conditions or the voltage gain, but the output voltage will be in proportion to the ratio of the new voltage to 300 volts. Voltage gain is measured at 400 cycles. Capacitor values given are based on 100-cycle cutoff. For increased low-frequency response, all capacitars may be made larger than specified (cut-off frequency in inverse proportion to capacitor values provided all are changed in the same proportion). A variation of 10 per cent in the values given has negligible effect on the performance.

	Plate Resistor Megohms	Next-Stage Grid Resistor Megahms	Screen Resistor Megohms	Cathode Resistor Ohms	Screen Bypass µf.	Cathode Bypass µf.	Blocking Capacitor µf.	Output Volts (Peak) ¹	Valtage Gain ²
ĺ	0.1	0.1 0.25 0.5	0.35 0.37 0.47	500 530 590	0.10 0.09 0.09	11.6 10.9 9.9	0.019 0.016 0.007	72 96 101	67 98 104
6SJ7, 12SJ7	0.25	0.25 0.5 1.0	0.89 1.10 1.18	850 860 910	0.07 0.06 0.06	8.5 7.4 6.9	0.011 0.004 0.003	79 88 98	139 167 185
	0.5	0.5 1.0 2.0	2.0 2.2 2.5	1300 1410 1530	0.06 0.05 0.04	6.0 5.8 5.2	0.004 0.002 0.0015	64 79 89	200 238 263
	0.1	0.1 0.25 0.5	0.44 0.5 0.53	500 450 600	0.07 0.07 0.06	8.5 8.3 8.0	0.02 0.01 0.006	55 81 96	61 82 94
6J7, 7C7, 12J7-GT	0.25	0.25 0.5 1.0	1.18 1.18 1.45	1100 1200 1300	0.04 0.04 0.05	5.5 5.4 5.8	0.008 0.005 0.005	81 104 110	104 140 185
	0.5	0.5 1.0 2.0	2.45 2.9 2.95	1700 2200 2300	0.04 0.04 0.04	4.2 4.1 4.0	0.005 0.003 0.0025	75 97 100	161 200 230
	0.1	0.1 0.22 0.47	0.2 0.24 0.26	500 600 700	0.13 0.11 0.11	18.0 16.4 15.3	0.019 0.011 0.006	76 103 129	109 145 168
SAU6, 6SH7, 2AU6, 12SH7	0.22	0.22 0.47 1.0	0.42 0.5 0.55	1000 1000 1100	0.1 0.098 0.09	12.4 12.0 11.0	0.009 0.007 0.003	92 108 122	164 230 262
	0.47	0.47 1.0 2.2	1.0 1.1 1.2	1800 1900 2100	0.075 0.065 0.06	8.0 7.6 7.3	0.0045 0.0028 0.0018	94 105 122	248 318 371
6AQ6, 6AQ7, 6AT6, 6Q7,	0.1	0.1 0.22 0.47		1500 1800 2100		4.4 3.6 3.0	0.027 0.014 0.0065	40 54 63	34 38 41
6AT6, 6Q7, 6\$L7-GT T8-A, 12AT6, 12Q7-GT,	0.22	0.22 0.47 1.0		2600 3200 3700		2.5 1.9 1.6	0.013 0.0065 0.0035	51 65 77	42 46 48
12SL7-GT (one triade)	0.47	0.47 1.0 2.2		5200 6300 7200		1.2 1.0 0.9	0.006 0.0035 0.002	61 74 85	48 50 51
	0.1	0.1 0.22 0.47	\equiv	1300 1500 1700		4.6 4.0 3.6	0.027 0.013 0.006	43 57 66	45 52 57
AV6, 12AV6, 12AX7 {one triade}	0.22	0.22 0.47 1.0		2200 2800 3100		3.0 2.3 2.1	0.013 0.006 0.003	54 69 79	59 65 68
	0.47	0.47 1.0 2.2		4300 5200 5900	=	1.6 1.3 1.1	0.006 0.003 0.002	62 77 92	69 73 75
	0.1	0.1 0.25 0.5		750 930 1040			0.033 0.014 0.007	35 50 54	29 34 36
SC7,8 12SC7 8 (one triode)	0.25	0.25 0.5 1.0		1400 1680 1840		=	0.012 0.006 0.003	45 55 64	39 42 45
	0.5	0.5 1.0 2.0		2330 2980 3280		=	0.006 0.003 0.002	50 62 72	45 48 49
6CG7, 6J5, 7A4, 7N7, 6SN7-GTB,	0.047	0.047 0.1 0.22		1300 1580 1800		3.6 3.0 2.5	0.061 0.032 0.015	59 73 83	14 15 16
6\$N7-GTB, 12J5-GT, 12SN7-GT	0.1	0.1 0.22 0.47	=	2500 3130 3900		1.9 1.4 1.2	0.031 0.014 0.0065	68 82 96	16 16 16
(one triode)	0.22	0.22 0.47 1.0	=	4800 6500 7800		0.95 0.69 0.58	0.015 0.0065 0.0035	68 85 96	16 16 16
	0.047	0.047 0.1 0.22	=	870 1200 1500		4.1 3.0 2.4	0.065 0.034 0.016	38 52 68	12 12 12
6C4, 12AU7-A {one triode}	0.1	0.1 0.22 0.47		1900 3000 4000		1.9 1.3 1.1	0.032 0.016 0.007	44 68 80	12 12 12
	0.22	0.22 0.47 1.0	\equiv	5300 8800 11000	=	0.9 0.52 0.46	0.015 0.007 0.0035	57 82 92	12 12 12

¹ Voltage across next-stage grid resistor at grid-current point.

² At 5 volts r.m.s. output.

⁸ Cathode-resistor values are for phase-inverter service.

Designing the Speech Amplifier

The circuit at A combines resistance and transformer coupling, and may be used for exciting the grids of a Class A or AB₁ following stage. The resistance coupling is used to keep the d.c. plate current from flowing through the transformer primary, thereby preventing a reduction in primary inductance below its no-current value; this improves the low-frequency response. With medium- μ triodes (6C5, 6J5, etc.), the gain is equal to that with resistance coupling multiplied by the secondary-to-primary turns ratio of the transformer.

In B the transformer primary is in series with the plate of the tube, and thus must carry the tube plate current. When the following amplifier operates without grid current, the voltage gain of the stage is practically equal to the μ of the tube multiplied by the transformer ratio. This circuit also is suitable for transferring power

Fig. 9-4—Self-balancing phase-inverter circuits. V₁ and V₂ may be a double triode such as the 12AU7 or 12AX7. V₃ may be any of the triodes listed in Table 9-1, or one section of a double triode.

R₁-Grid resistor (1 megohm or less).

R₂—Cathode resistor; use one-half value given in Table 9-1 for tube and operating conditions chosen.

R_s, R₄—Plate resistor; select from Table 9-1.

 R_{δ} , R_{δ} —Following-stage grid resistor (0.22 to 0.47 megohm).

R₇-0.22 megohm.

R₈-Cathode resistor; select from Table 9-1.

R₀, R₁₀—Each one-half of plate load resistor given in Table 9-1.

C₁-10-\mu f. electrolytic.

C₂, C₂-0.01- to 0.1-\(mu f.\) paper.

(within the capabilities of the tube) to a following Class AB₂ or Class B stage.

Phase Inversion

Push-pull output may be secured with resistance coupling by using phase-inverter or phase-splitter circuits as shown in Fig. 9-4.

The circuits shown in Fig. 9-4 are of the "selfbalancing" type. In A, the amplified voltage from V_1 appears across R_5 and R_7 in series. The drop across R_7 is applied to the grid of V_2 , and the amplified voltage from V_2 appears across R_6 and R_7 in series. This voltage is 180 degrees out of phase with the voltage from V_1 , thus giving push-pull output. The part that appears across R_7 from V_2 opposes the voltage from V_1 across R_7 , thus reducing the signal applied to the grid of V2. The negative feedback so obtained tends to regulate the voltage applied to the phaseinverter tube so that the output voltages from both tubes are substantially equal. The gain is slightly less than twice the gain of a single-tube amplifier using the same operating conditions.

In the single-tube circuit shown in Fig. 9-4B the plate load resistor is divided into two equal parts, R_0 and R_{10} , one being connected to the plate in the normal way and the other between cathode and ground. Since the voltages at the plate and cathode are 180 degrees out of phase, the grids of the following tubes are fed equal a.f. voltages in push-pull. The grid return of V_3 is made to the junction of R_8 and R_{10} so normal bias will be applied to the grid. This circuit is highly degenerative because of the way R_{10} is connected. The voltage gain is less than 2 even when a high- μ triode is used at V_3 .

Gain Control

A means for varying the over-all gain of the amplifier is necessary for keeping the final output at the proper level for modulating the transmitter. The common method of gain control is to adjust the value of a.c. voltage applied to the grid of one of the amplifiers by means of a voltage divider or potentiometer.

The gain-control potentiometer should be near the input end of the amplifier, at a point where the signal voltage level is so low there is no danger that the stages ahead of the gain control will be overloaded by the full microphone output. With carbon microphones the gain control may be placed directly across the microphone-transformer secondary. With other types of microphones, however, the gain control usually will affect the frequency response of the microphone when connected directly across it. Also, in a high-gain amplifier it is better to operate the first tube at maximum gain, since this gives the best signal-to-hum ratio. The control therefore is usually placed in the grid circuit of the second stage.

DESIGNING THE SPEECH AMPLIFIER

The steps in designing a speech amplifier are as follows:

1) Determine the power needed to modulate

the transmitter and select the modulator. In the case of plate modulation, a Class B amplifier may be required. Select a suitable tube type and determine from the tube tables at the end of this book the grid driving power required, if any.

2) As a safety factor, multiply the required driver power by at least 1.5.

3) Select a tube, or pair of tubes, that will deliver the power determined in the second step. This is the last or output stage of the speechamplifier. Receiver-type power tubes can be used (beam tubes such as the 6L6 may be needed in some cases) as determined from the receiving-tube tables. If the speech amplifier is to drive a Class B modulator, use a Class A or AB₁ amplifier.

4) If the speech-amplifier output stage is also the modulator and must operate Class AB₂ to develop the required power output, use a low-or medium- μ triode to drive it. If more power is needed than can be obtained from one tube, use two in push-pull, in the driver. In either case transformer coupling will have to be used, and transformer manufacturers' catalogs should be consulted for a suitable type.

5) If the speech-amplifier output stage operates Class A or AB₁, it may be driven by a voltage amplifier. If the output stage is push-pull, the driver may be a single tube coupled through a transformer with a balanced secondary, or may be a dual-triode phase inverter. Determine the signal voltage required for full output from the last stage. If the last stage is a single-tube Class A amplifier, the peak signal is equal to the gridbias voltage; if push-pull Class A, the peak-topeak signal voltage is equal to twice the gridbias; if Class AB₁, twice the bias voltage when fixed bias is used; if cathode bias is used, twice the bias figured from the cathode resistance and the maximum-signal cathode current.

6) From Table 9-I, select a tube capable of giving the required output voltage and note its rated voltage gain. A double-triode phase inverter (Fig. 9-4A) will have approximately twice the output voltage and twice the gain of one triode operating as an ordinary amplifier. If the driver is to be transformer-coupled to the last stage, select a medium-μ triode and calculate the gain and output voltage as described earlier in this chapter.

7) Divide the voltage required to drive the output stage by the gain of the preceding stage. This gives the peak voltage required at the grid of the next-to-the-last stage.

8) Find the output voltage, under ordinary conditions, of the microphone to be used. This information should be obtained from the manufacturer's catalog. If not available, the figures given in the section on microphones in this chapter will serve.

9) Divide the voltage found in (7) by the output voltage of the microphone. The result is the over-all gain required from the microphone to the grid of the next-to-the-last stage. To be on the safe side, double or triple this figure.

10) From Table 9-I, select a combination of

tubes whose gains, when multiplied together, give approximately the figure arrived at in (9). These amplifiers will be used in cascade. If high gain is required, a pentode may be used for the first speech-amplifier stage, but it is not advisable to use a second pentode because of the possibility of feedback and self-oscillation. In most cases a triode will give enough gain, as a second stage, to make up the total gain required. If not, a medium-µ triode may be used as a third stage.

A high- μ double triode with the sections in cascade makes a good low-level amplifier, and will give somewhat greater gain than a pentode followed by a medium- μ triode. With resistance-coupled input to the first section the cathode of that section may be grounded (contact potential bias), which is helpful in reducing hum.

SPEECH-AMPLIFIER CONSTRUCTION

Once a suitable circuit has been selected for a speech amplifier, the construction problem resolves itself into avoiding two difficulties—excessive hum, and unwanted feedback. For reasonably humless operation, the hum voltage should not exceed about 1 per cent of the maximum audio output voltage—that is, the hum and noise should be at least 40 db. below the output level.

Unwanted feedback, if negative, will reduce the gain below the calculated value; if positive, is likely to cause self-oscillation or "howls." Feedback can be minimized by isolating each stage with decoupling resistors and capacitors, by avoiding layouts that bring the first and last stages near each other, and by shielding of "hot" points in the circuit, such as grid leads in lowlevel stages.

Speech-amplifier equipment, especially voltage amplifiers, should be constructed on steel chassis, with all wiring kept below the chassis to take advantage of the shielding afforded. Exposed leads, particularly to the grids of low-level high-gain tubes, are likely to pick up hum from the electric field that usually exists in the vicinity of house wiring. Even with the chassis, additional shielding of the input circuit of the first tube in a highgain amplifier usually is necessary. In addition, such circuits should be separated as much as possible from power-supply transformers and chokes and also from any audio transformers that operate at fairly high power levels; this will minimize magnetic coupling to the grid circuit and thus reduce hum or audio-frequency feedback. It is always safe, although not absolutely necessary, to separate the speech amplifier and its power supply, building them on separate chassis.

If a low-level microphone such as the crystal type is used, the microphone, its connecting cable, and the plug or connector by which it is attached to the speech amplifier, all should be shielded. The microphone and cable usually are constructed with suitable shielding; this should be connected to the speech-amplifier chassis, and it is advisable — as well as necessary — to connect

Modulators and Drivers

the chassis to a ground such as a water pipe. With the top-cap tubes, complete shielding of the grid lead and grid cap is a necessity.

Heater wiring should be kept as far as possible from grid leads, and either the center-tap or one side of the heater-transformer secondary winding should be connected to the chassis. If the center-tap is grounded, the heater leads to each tube should be twisted together to reduce the magnetic field from the heater current. With either type of connection; it is advisable to lay heater leads in the corner formed by a fold in the chassis, bringing them out from the corner to the tube socket by the shortest possible path.

When metal tubes are used, always ground the shell connection to the chassis. Glass tubes used in the low-level stages of high-gain amplifiers

must be shielded; tube shields are obtainable for that purpose. It is a good plan to enclose the entire amplifier in a metal box, or at least provide it with a cane-metal cover, to avoid feedback difficulties caused by the r.f. field of the transmitter. R.f. picked up on exposed wiring, leads or tube elements causes overloading, distortion, and self-oscillation of the amplifier.

When using paper capacitors as bypasses, be sure that the terminal marked "outside foil" is connected to ground. This utilizes the outside foil of the capacitor as a shield around the "hot" foil. When paper capacitors are used for coupling between stages, always connect the outside foil terminal to the side of the circuit having the lowest impedance to ground. Usually, this will be the plate side rather than the following-grid side.

MODULATORS AND DRIVERS

CLASS AB AND B MODULATORS

Class AB or B modulator circuits are basically identical no matter what the power output of the modulator. The diagrams of Fig. 9-5 therefore will serve for any modulator of this type that the amateur may elect to build. The triode circuit is given at A and the circuit for tetrodes at B. When small tubes with indirectly heated cath-

DRIVER PLATES

OR LINE

OR LINE

OR LINE

OR LINE

OR LIN

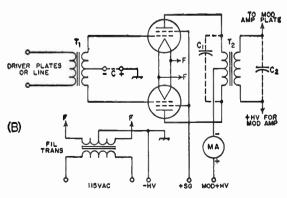


Fig. 9-5—Madulatar circuit diagrams. Tubes and circuit considerations are discussed in the text.

odes are used, the cathodes should be connected to ground.

Modulator Tubes

The audio ratings of various types of transmitting tubes are given in the chapter containing the tube tables. Choose a pair of tubes that is capable of delivering sine-wave audio power equal to somewhat more than half the d.c. input

to the modulated Class C amplifier. It is sometimes convenient to use tubes that will operate at the same plate voltage as that applied to the Class C stage, because one power supply of adequate current capacity may then suffice for both stages.

In estimating the output of the modulator, remember that the figures given in the tables are for the tube output only, and do not include output-transformer losses. To be adequate for modulating the transmitter, the modulator should have a theoretical power capability 15 to 25 per cent greater than the actual power needed for modulation.

Matching to Load

In giving audio ratings on power tubes, manufacturers specify the plate-to-plate load impedance into which the tubes must operate to deliver the rated audio power output. This load impedance seldom is the same as the modulating impedance of the Class C r.f. stage, so a match must be brought about by adjusting the turns ratio of the coupling transformer. The required turns ratio, primary to secondary, is

$$N = \sqrt{\frac{Z_{\rm p}}{Z_{\rm m}}}$$

where N = Turns ratio, primary to secondary

 $Z_{\rm m} = {\rm Modulating impedance of}$

Class C r.f. amplifier

 Z_p = Plate-to-plate load impedance for Class B tubes

Example: The modulated r.f. amplifier is to operate at 1250 volts and 250 ma. The power input is

$$P = EI = 1250 \times 0.25 = 312$$
 watts

so the modulating power required is 312/2 = 156 watts. Increasing this by 25% to allow for losses and a reasonable operating marging gives $156 \times 1.25 = 195$ watts. The modulating impedance of the Class C stage is

$$Z_{\rm m} = \frac{E}{-} = \frac{1250}{0.25} = 5000 \text{ ohms.}$$

From the tube tables a pair of Class B tubes is selected that will give 200 watts output when working into a 6900-ohm load, plate-to-plate. The primary-to-secondary turns ratio of the modulation transformer therefore should be

$$N = \sqrt{\frac{Z_p}{Z_m}} = \sqrt{\frac{6900}{5000}} = \sqrt{1.38} = 1.175:1.$$

The required transformer ratios for the ordinary range of impedances are shown graphically in Fig. 9-6.

Many modulation transformers are provided with primary and secondary taps, so that various turns ratios can be obtained to meet the requirements of particular tube combinations. However, it may be that the exact turns ratio required cannot be secured, even with a tapped modulation transformer. Small departures from the proper turns ratio will have no serious effect if the modulator is operating well within its capabilities; if the actual turns ratio is within 10 per cent of the ideal value, the system will operate satisfactorily. Where the discrepancy is larger, it is usually possible to choose a new set of operating conditions for the Class C stage to give a modulating impedance that can be matched by the turns ratio of the available transformer. This may require operating the Class C amplifier at higher voltage and less plate current, if the modulating impedance must be increased, or at lower voltage and higher current if the modulating impedance must be decreased. However, this process cannot be carried very far without exceeding the ratings of the Class C tubes for either plate voltage or plate current, even though the power input is kept at the same figure.

Suppressing Audio Harmonics

Distortion in either the driver or Class B modulator will cause a.f. harmonics that may lie outside the frequency band needed for intelligible speech transmission. While it is almost impossible to avoid some distortion, it is possible to cut down the amplitude of the higher-frequency harmonics.

The purpose of capacitors C_1 and C_2 across the primary and secondary, respectively, of the Class B output transformer in Fig. 9-5 is to reduce the strength of harmonics and unnecessary

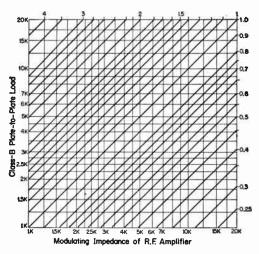


Fig. 9-6—Transformer ratios for matching a Class C modulating impedance to the required plate-to-plate load for the Class B modulator. The ratios given on the curves are from total primary to secondary. Resistance values are in kilohms.

high-frequency components existing in the modulation. The capacitors act with the leakage inductance of the transformer winding to form a rudimentary low-pass filter. The values of capacitance required will depend on the load resistance (modulating impedance of the Class C amplifier) and the leakage inductance of the particular transformer used. In general, capacitances between about 0.001 and 0.01 \(mu f.\) will be required; the larger values are necessary with the lower values of load resistance. The voltage rating of each capacitor should at least be equal to the d.c. voltage at the transformer winding with which it is associated. In the case of C_2 , part of the total capacitance required will be supplied by the plate bypass or blocking capacitor in the modulated amplifier.

A still better arrangement is to use a low-pass filter as shown later, even though clipping is not deliberately employed.

Grid Bias

Certain triodes designed for Class B audio work can be operated without grid bias. Besides eliminating the grid-bias supply, the fact that grid current flows over the whole audio cycle means that the load resistance for the driver is fairly constant. With these tubes the grid-return lead from the center-tap of the input transformer secondary is simply connected to the filament center-tap or cathode.

When the modulator tubes require bias, it should always be supplied from a fixed voltage source. Cathode bias or grid-leak bias cannot be used with a Class-B amplifier. When only a small amount of bias is required it can be obtained conveniently from a few dry cells. The battery is charged by the grid current rather than discharged, but nevertheless it will deteriorate with time. It should be replaced if the voltage meas-

ured across it varies with the signal by more than 10 per cent or so.

As an alternative to batteries, a regulated bias supply may be used. This type of supply is described in the power supply chapter.

Plate Supply

In addition to adequate filtering, the voltage regulation of the plate supply should be as good as it can be made. If the d.c. output voltage of the supply varies with the load current, the voltage at maximum current determines the amount of power that can be taken from the modulator without distortion. A supply whose voltage drops from 1500 at no load to 1250 at the full modulator plate current is a 1250-volt supply, so far as the modulator is concerned, and any estimate of the power output available should be based on the lower figure.

Good dynamic regulation—i.e., with suddenly applied loads—is equally as important as good regulation under steady loads, since an instantaneous drop in voltage on voice peaks also will limit the output and cause distortion. The output ca-

pacitor of the supply should have as much capacitance as conditions permit. A value of at least $10~\mu f$, should be used, and still larger values are desirable. It is better to use all the available capacitance in a single-section filter rather than to distribute it between two sections.

It is particularly important, in the case of a tetrode Class B stage, that the screen-voltage power-supply source have excellent regulation, to prevent distortion. The screen voltage should be set as exactly as possible to the recommended value for the tube. The audio impedance between screen and cathode also must be low.

Overexcitation

When a Class B amplifier is overdriven in an attempt to secure more than the rated power, distortion increases rapidly. The high-frequency harmonics which result from the distortion modulate the transmitter, producing spurious sidebands which can cause serious interference over a band of frequencies several times the channel width required for speech. (This can happen even though the modulation percentage, as defined in the chapter on amplitude modulation, is less than 100 per cent, if the modulator is incapable of delivering the audio power required to modulate the transmitter.)


As shown later, such a condition may be reached by deliberate design, in case the modulator is to be adjusted for peak clipping. But whether it happens by accident or intention, the splatter and spurious sidebands can be eliminated by inserting a low-pass filter (Fig. 9-13) between the modulator and the modulated amplifier, and then taking care to see that the actual modulation of the r.f. amplifier does not exceed 100 per cent.

Operation Without Load

Excitation should never be applied to a Class B modulator until after the Class C amplifier is turned on and is drawing the value of plate current required to present the rated load to the modulator. With no load to absorb the power, the primary impedance of the transformer rises to a high value and excessive audio voltages may be developed in the primary — frequently high enough to break down the transformer insulation.

DRIVERS FOR CLASS-B MODULATORS

Class AB₂ and Class B amplifiers are driven into the grid-current region, so power is con-

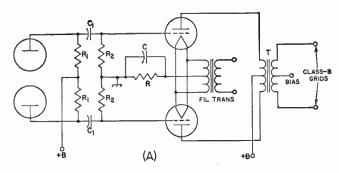

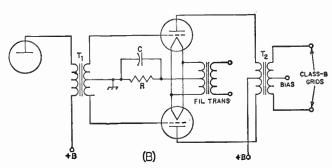


Fig. 9-7—Triode driver circuits far Class B modulators. A, resistance coupling to grids; B, transformer coupling. R_1 in A is the plate resistor for the preceding stage, value determined by the type of tube and aperating canditions as given in Table 9-1. C_1 and R_2 are the coupling capacitor and grid resistor, respectively; values also may be taken from Table 9-1.

In both circuits the output transformer, (T_1T_2) should have the proper turns ratio to couple between the driver tubes and the Class B grids. T_1 in B is usually a 2:1 transformer, secondary to primary. R, the cathode resistor, should be calculated for the particular tubes used. The value of C, the cathode bypass, is determined as described in the text.

264

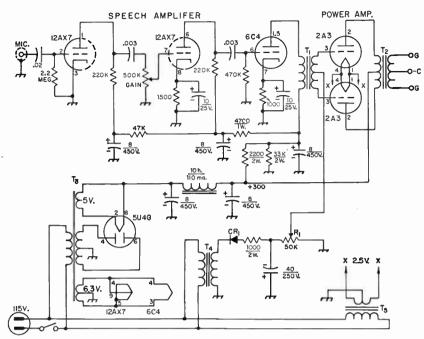


Fig. 9-8—Speech-amplifier driver for 10-15 watts output. Capacitances are in μf. Resistors are ½ watt unless specified otherwise. Capacitors with polarity indicated are electrolytic; others may be paper or ceramic. CR₁—Selenium rectifier, 20 ma.

Class-B tubes used; 15 watt rating.

R₁-50,000-ohm potentiometer, preferably wire wound.
T₁-Interstage audio transformer, single plate to pushpull grids, turns ratio 2 to 1 or 3 to 1, total secondary to primary.

T₂—Class-B driver transformer, 3000 ohms plate-toplate; secondary impedance as required by

sumed in the grid circuit. The preceding stage or driver must be capable of supplying this power at the required peak audio-frequency grid-to-grid voltage. Both of these quantities are given in the manufacturer's tube ratings. The grids of the Class B tubes represent a varying load resistance over the audio-frequency cycle, because the grid current does not increase directly with the grid voltage. To prevent distortion, therefore, it is necessary to have a driving source that will maintain the wave form of the signal without distortion even though the load varies. That is, the driver stage must have good regulation. To this end, it should be capable of delivering somewhat more power than is consumed by the Class B grids, as previously described in the discussion on speech amplifiers.

Driver Tubes

To secure good voltage regulation the internal impedance of the driver, as seen by the modulator grids, must be low. The principal component of this impedance is the plate resistance of the driver tube or tubes as reflected through the driver transformer. Hence for low driving-source impedance the effective plate resistance of the driver tubes should be low and the turns ratio of the driver transformer, primary to secondary, should be as large as possible. The maximum

T₃-Power transformer, 700 volts c.t., 110 ma.; 5 volts, 3 amp.; 6.3 volts, 4 amp.

T₄—Power transformer, 125 volts, 20 ma.; 6.3 volts, 0.6 amp.

T₅-2.5-volt 5-ampere filament transformer (Thordarson 21F00).

turns ratio that can be used is that value which just permits developing the modulator grid-to-grid a.f. voltage required for the desired power output. The rated tube output as shown by the tube tables should be reduced by about 20 per cent to allow for losses in the Class B input transformer.

Low- μ triodes such as the 2A3 have low plate resistance and are therefore good tubes to use as drivers for Class AB2 or Class B modulators. Tetrodes such as the 6V6 and 6L6 make very poor drivers in this respect when used without negative feedback, but with such feedback the effective plate resistance can be reduced to a value comparable with low- μ triodes.

Fig. 9-7 shows representative circuits for a push-pull triode driver using cathode bias. If the amplifier operates Class A the cathode resistor need not be bypassed, because the a.f. currents from each tube flowing in the cathode resistor are out of phase and cancel each other. However, in Class AB operation this is not true; considerable distortion will be generated at high signal levels if the cathode resistor is not bypassed. The bypass capacitance required can be calculated by a simple rule: the cathode resistance in ohms multiplied by the bypass capacitance in microfarads should equal at least 25,000. The voltage rating of the capacitor should be equal

to the maximum bias voltage. This can be found from the maximum-signal plate current and the cathode resistance.

> Example: A pair of 2A3s is to be used in Class AB1 self-biased. From the tube tables, the cathode resistance should be 780 ohms and the maximum-signal plate current 100 ma. From Ohm's Law,

$$E = RI = 780 \times 0.10 = 78.6$$
 volts

From the rule mentioned previously, the bypass capacitance required is

 $C = 25,000/R = 25,000/780 = 32 \mu f.$

A 40- or 50-µf. 100-volt electrolytic capacitor would be satisfactory.

Fig. 9-8 is a typical circuit for a speech amplifier suitable for use as a driver for a Class AB2 or Class B modulator. An output of about 13 watts can be realized with the power supply circuit shown (or any similar well-filtered supply delivering 300 volts under load). This is sufficient for driving any of the power triodes commonly used as modulators. The 2A3s in the output stage are operated Class AB1. The circuit provides several times the voltage gain needed for communications-type crystal or ceramic microphones.

The two sections of a 12AX7 tube are used in the first two stages of the amplifier. These are resistance coupled, the gain control being in the grid circuit of the second stage. Although the cathode of the first stage is grounded and there is no separate bias supply for the grid, the grid

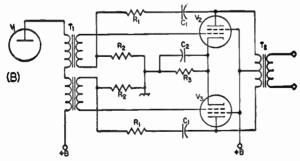


Fig. 9-9—Negotive-feedback circuits for drivers for Closs B modulotors. A-Single-ended beam-tetrode driver. If V1 and V2 are a 615 and 6V6, respectively, or one section of a 6CG7 and a 6AQ5, the following values are suggested: R₁, 47,000 ohms; R_2 , 0.47 megohm; R_3 , 250 ohms; R_4 , R_5 , 22,000 ohms; C_1 , 0.01 μf.; C2, 50 μf.

B-Push-pull beom-tetrode driver. If V₁ is a 6J5 or 6CG7 and V₂ and V₃ 6L6s, the following values are suggested: R₁, 0.1 megohm; R_2 , 22,000 ohms; R_3 , 250 ohms; C_1 , 0.1 μ f.; C_2 , 100 μ f.

bias actually is about one volt because of "contact potential."

The third stage uses a medium-µ triode which is coupled to the 2A3 grids through a transformer having a push-pull secondary. The ratio may be of the order of 2 to 1 (total secondary to primary) or higher; it is not critical since the gain is sufficient without a high step-up ratio.

The output transformer, T_2 , should be selected to couple between push-pull 2A3s and the grids of the particular modulator tubes used.

The power supply has a capacitor-input filter the output of which is applied to the 2A3 plates through T2. For the lower-level stages, additional filtering is provided by successive RC filters which also serve to prevent audio feedback through the plate supply.

Grid bias for the 2A3s is furnished by a separate supply using a small selenium rectifier and a TV "booster" transformer, T4. The bias may be adjusted by means of R_1 , and should be set to -62 volts or to obtain a total plate current of 80 ma. (as measured in the lead to the primary center tap of T_2) for the 2A3s.

In building an amplifier of this type the constructional precautions outlined earlier should be observed. The Class AB₁ modulators described subsequently in this chapter are representative of good constructional practice.

Negative Feedback

Whenever tetrodes or pentodes are used as drivers for Class B modulators, negative feedback should be used in the driver stage, for the reason

already discussed.

Suitable circuits for single-ended and push-pull tetrodes are shown in Fig. 9-9. Fig. 9-9A shows resistance coupling between the preceding stage and a single tetrode, such as the 6V6, that operates at the same plate voltage as the preceding stage. Part of the a.f. voltage across the primary of the output transformer is fed back to the grid of the tetrode, V_2 , through the plate resistor of the preceding tube, V_1 . The total resistance of R_4 and R_5 in series should be ten or more times the rated load resistance of V_2 . Instead of the voltage divider, a tap on the transformer primary can be used to supply the feedback voltage, if such a tap is available.

The amount of feedback voltage that appears at the grid of tube V_2 is determined by R_1 , R_2 and the plate resistance of V_1 , as well as by the relationship between R_4 and R_5 . Circuit values for typical tube combinations are given in detail in

Fig. 9-9.

The push-pull circuit in Fig. 9-9B requires an audio transformer with a split secondary. The feedback voltage is obtained from the plate of each output tube by means of the voltage divider, R_1 , R_2 . The blocking capacitor, C_1 , prevents the d.c. plate voltage from being applied to R_1 , R_2 ; the reactance of this capacitor should be low, compared with the sum of R_1 and R_2 , at the lowest audio frequency to be amplified. Also, the sum of R_1 and R_2 should be high (ten times or more) compared with the rated load resistance for V_2 and V_3 .

In this circuit the feedback voltage that is developed across R_2 appears at the grid of V_2 (or V_3) through the transformer secondary and grid-cathode circuit of the tube, provided the tubes are not driven to grid current. The per cent feedback is

$$n=\frac{R_2}{R_1+R_2}\times 100$$

where n is the feedback percentage, and R_1 and

 R_2 are connected as shown in the diagram. The higher the feedback percentage, the lower the effective plate resistance. However, if the percentage is made too high the preceding tube, V_1 , may not be able to develop enough voltage, through T_1 , to drive the push-pull stage to maximum output without itself generating harmonic distortion. Distortion in V_1 is not compensated for by the feedback circuit.

If V_2 and V_3 are 6L6s operated self-biased in Class AB_1 with a load resistance of 9000 ohms, V_1 is a 6J5 or similar triode, and T_1 has a turns ratio of 2-to-1, total secondary to primary, it is possible to use over 30 per cent feedback without going beyond the output-voltage capabilities of the triode. Twenty per cent feedback will reduce the effective plate resistance to the point where the output voltage regulation is better than that of 2A3s without feedback. The power output under these conditions is about 20 watts.

INCREASING THE EFFECTIVENESS OF THE PHONE TRANSMITTER

The effectiveness of an amateur phone transmitter can be increased to a considerable extent by taking advantage of speech characteristics. Measures that may be taken to make the modulation more effective include band compression (filtering), volume compression, and speech clipping.

Compressing the Frequency Band

Most of the intelligibility in speech is contained in the medium band of frequencies; that is, between about 500 and 2500 cycles. On the other hand, a large portion of speech power is normally found below 500 cycles. If these low frequencies are attenuated, the frequencies that carry most of the actual communication can be increased in amplitude without exceeding 100-per cent modulation, and the effectiveness of the transmitter is correspondingly increased.

One simple way to reduce low-frequency response is to use small values of coupling capacitance between resistance-coupled stages, as shown in Fig. 9-10A. A time constant of 0.0005 second for the coupling capacitor and following-stage grid resistor will have little effect on the amplification at 500 cycles, but will practically halve it at 100 cycles. In two cascaded stages the gain will be down about 5 db. at 200 cycles and 10 db. at 100 cycles. When the grid resistor is ½ megohm a coupling capacitor of 0.001 µf. will give the required time constant.

The high-frequency response can be reduced by using "tone control" methods, utilizing a capacitor in series with a variable resistor connected across an audio impedance at some point in the speech amplifier. The best spot for the tone control is across the primary of the output transformer of the speech amplifier, as in Fig. 9-10B. The capacitor should have a reactance at 1000 cycles about equal to the load resistance required by the amplifier tube or tubes, while the variable resistor in series may have a value equal to four

or five times the load resistance. The control can be adjusted while listening to the amplifier, the object being to cut the high-frequency response without unduly sacrificing intelligibility.

Restricting the frequency response not only puts more modulation power in the optimum frequency band but also reduces hum, because the low-frequency response is reduced, and helps reduce the width of the channel occupied by the transmission, because of the reduction in the amplitude of the high audio frequencies.

Volume Compression

Although it is obviously desirable to modulate the transmitter as completely as possible, it is

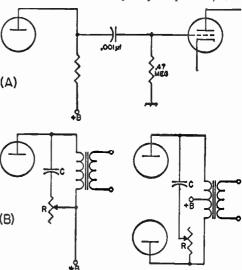


Fig. 9-10—A, use of a small coupling capacitor to reduce low-frequency response; B, tone-control circuits for reducing high-frequency response. Values for C and R are discussed in the text; 0.01 μ f, and 25,000 ohms are typical.

difficult to maintain constant voice intensity when speaking into the microphone. To overcome this variable output level, it is possible to use automatic gain control that follows the average (not instantaneous) variations in speech amplitude. This can be done by rectifying and filtering some of the audio output and applying the rectified and filtered d.c. to a control electrode in an early stage in the amplifier.

A practical circuit for this purpose is shown in Fig. 9-11. V₁, a medium-µ triode, has its grid connected in parallel with the grid of the last speech amplifier tube (the stage preceding the power stage) through the gain control R_1 . The amplified output is coupled to a full-wave rectifier, V2. The rectified audio output develops a negative d.c. voltage across C1R3, which has a sufficiently long time constant to hold the voltage at a reasonably steady value between syllables and words. The negative d.c. voltage is applied as control bias to the suppressor grid of the first tube in the speech amplifier (this circuit requires a pentode first stage), effecting a reduction in gain. The gain reduction is substantially proportional to the average microphone output and thus tends to hold the amplifier output at a constant level.

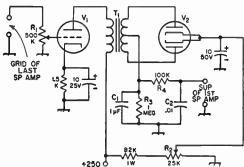


Fig. 9-11—Speech-amplifier output compression circuit.

 V_1 -6C4, 6C5, 6CG7, 6J5, 12AU7, etc. V_2 -6H6, 6AL5, etc.

T₁-Interstage audio, single plate to p.p. grids.

An adjustable bias is applied to the cathodes of V_2 to cut off the tube at low levels and thus prevent rectification until a desired output level is reached. R_2 is the "threshold control" which sets this level. R_1 , the gain control, determines the rate at which the gain is reduced with increasing signal level.

The hold-in time can be increased by increasing the resistance of R_3 . C_2 and R_4 may not be necessary in all cases; their function is to prevent too-rapid gain reduction on a sudden voice peak. The "rise time" of this circuit can be increased by increasing C_2 or R_4 , or both.

The over-all gain of the system must be high enough so that full output can be secured at a moderately low voice level.

Speech Clipping and Filtering

In speech wave forms the average power content is considerably less than in a sine wave of the same peak amplitude. Since modulation per-

centage is based on peak values, the modulation or sideband power in a transmitter modulated 100 per cent by an ordinary voice wave form will be considerably less than the sideband power in the same transmitter modulated 100 per cent by a sine wave. In other words, the modulation percentage with voice wave forms is determined by peaks having relatively low average power content.

If the low-energy peaks are clipped off, the remaining wave form will have a considerably higher ratio of average power to peak amplitude. More sideband power will result, therefore, when such a clipped wave is used to modulate the transmitter 100 per cent. Although clipping distorts the wave form and the result therefore does not sound exactly like the original, it is possible to secure a worth-while increase in modulation power without sacrificing intelligibility. Once the system is properly adjusted it will be impossible to overmodulate the transmitter because the maximum output amplitude is fixed.

By itself, clipping generates the same highorder harmonics that overmodulation does, and therefore will cause splatter. To prevent this, the audio frequencies above those needed for intelligible speech must be filtered out, after clipping and before modulation. The filter required for this purpose should have relatively little attenuation at frequencies below about 2500 cycles, but high attenuation for all frequencies above 3000 cycles.

It is possible to use as much as 25 db. of clipping before intelligibility suffers; that is, if the original peak amplitude is 10 volts, the signal can be clipped to such an extent that the resulting maximum amplitude is less than one volt. If the original 10-volt signal represented the amplitude that caused 100-per-cent modulation on peaks, the clipped and filtered signal can then be amplified up to the same 10-volt peak level for modulating the transmitter.

There is a loss in naturalness with "deep" clipping, even though the voice is highly intelligible. With moderate clipping levels (6 to 12 db.) there is almost no change in "quality" but the voice power is increased considerably.

Before drastic clipping can be used, the speech signal must be amplified several times more than is necessary for normal modulation. Also, the hum and noise must be much lower than the tolerable level in ordinary amplification, because the noise in the output of the amplifier increases in proportion to the gain.

One type of clipper-filter system is shown in Fig. 9-12. The clipper is a peak-limiting rectifier of the same general type that is used in receiver noise limiters. It must clip both positive and negative peaks. The gain or clipping control sets the amplitude at which clipping starts. Following the low-pass filter for eliminating the harmonic distortion frequencies is a second gain control, the "level" or modulation control. This control is set initially so that the amplitude-limited output of the clipper-filter cannot cause more than 100 per cent modulation.

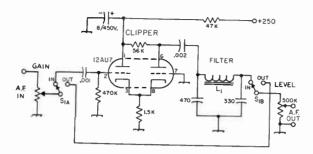


Fig. 9-12—Practical speech clipper circuit with law-pass filter. Capacitances belaw 0.001 μ f. are in $\mu\mu$ f. Resistars are ½ watt. L₁—20 henrys, 900 ohms (Stancar C-1515). S₁—D.p.d.t. taggle ar ratary.

It should be noted that the peak amplitude of the audio wave form actually applied to the modulated stage in the transmitter is not necessarily held at the same relative level as the peak amplitude of the signal coming out of the clipper stage. When the clipped signal goes through the filter, the relative phases of the various frequency components that pass through the filter are shifted, particularly those components near the cut-off frequency. This may cause the peak amplitude out of the filter to exceed the peak amplitude of the clipped signal applied to the filter input terminals. Similar phase shifts can occur in amplifiers following the filter, especially if these amplifiers, including the modulator, do not have good low-frequency response. With poor low-frequency response the more-or-less "square" waves resulting from clipping tend to be changed into triangular waves having higher peak amplitude. Best practice is to cut the lowfrequency response before clipping and to make all amplifiers following the clipper-filter as flat and distortion-free as possible.

The best way to set the modulation control in such a system is to check the actual modulation percentage with an oscilloscope connected as described in the section on modulation. With the gain control set to give a desired clipping level with normal voice intensity, the level control should be adjusted so that the maximum modulation does not exceed 100 per cent no matter how much sound is applied to the microphone.

The practical clipper-filter circuit shown in Fig. 9-12 may be inserted between two speech-amplifier stages (but after the one having the gain control) where the level is normally a few volts. The cathode-coupled clipper circuit gives some over-all voltage gain in addition to performing the clipping function. The filter constants are such as to give a cut-off characteristic that combines reasonably good fidelity with adequate high-frequency suppression.

High-Level Clipping and Filtering

Clipping and filtering also can be done at high level—that is, at the point where the modulation is applied to the r.f. amplifier—instead of in the lowlevel stages of the speech amplifier. In one rather simple but effective arrangement of this type the clipping takes place in the Class-B modulator itself. This is accomplished by carefully adjusting the plate-to-plate load resistance for the

modulator tubes so that they saturate or clip peaks at the amplitude level that represents 100 per cent modulation. The load adjustment can be made by choice of output transformer ratio or by adjusting the plate-voltage/plate-current ratio of the modulated r.f. amplifier. It is best done by examining the output wave form with an oscilloscope.

The filter for such a system consists of a choke coil and capacitors as shown in Fig. 9-13. The values of L and C should be chosen to form a low-pass filter section having a cut-off frequency of about 2500 cycles, using the modulating impedance of the r.f. amplifier as the load resistance. For this cut-off frequency the formulas are

$$L_1 = \frac{R}{7850}$$
 and $C_1 = C_2 = \frac{63.6}{R}$

where R is in ohms, L_1 in henrys, and C_1 and C_2 in microfarads. For example, with a plate-modulated amplifier operating at 1500 volts and 200 ma. (modulating impedance 7500 ohms) L_1 would be 7500/7850 = 0.96 henry and C_1 or C_2 would be 63.6/7500 = 0.0085 μ f. Bypass capacitors in the plate circuit of the r.f. amplifier should be included in C_2 . Voltage ratings for C_1 and C_2 when connected as shown must be the same as for the plate blocking capacitor — i.e., at least twice the d.c. voltage applied to the plate of the modulated amplifier. L and C values can vary 10 per cent or so without seriously affecting the operation of the filter.

Besides simplicity, the high-level system has the advantage that high-frequency components

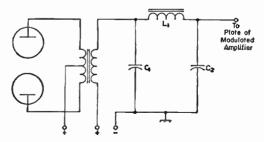


Fig. 9-13—Splatter-suppression filter for use at high level, shawn here connected between a Class B modulator and plate-modulated r.f. amplifier. Values for L_1 , C_1 and C_2 are determined as described in the text.

A Low-Power Modulator

of the audio signal fed to the modulator grids, whether present legitimately or as a result of amplitude distortion in lower-level stages, are suppressed along with the distortion components that arise in clipping. Also, the undesirable effects of poor low-frequency response following clipping and filtering, mentioned in the preceding

section, are avoided. Phase shifts can still occur in the high-level filter, however, so adjustments preferably should be made by using an oscilloscope to check the actual modulation percentage under all conditions of speech intensity. (For further discussion see Bruene, "High-Level Clipping and Filtering," *QST*, November, 1951.)

A LOW-POWER MODULATOR

A modulator suitable for plate modulation of low-power transmitters or for screen or control-grid modulation of high-power amplifiers is pictured in Figs. 9-14 and 9-16. As shown in Fig. 9-15, it uses a pair of Class A₁ 6AQ5's in pushpull in the output stage. These are driven by a 6C4 phase inverter. A two-stage preamplifier using a 12AX7 brings the output voltage of a crystal or ceramic microphone up to the proper level for the 6C4 grid. A power supply is included on the same chassis.

The undistorted audio output of the amplifier is 7-8 watts. This is sufficient for modulating the plate of an r.f. amplifier running 10 to 15 watts input, or for modulating the control grids or screens of r.f. amplifiers using tubes having plate-dissipation ratings up to 250 watts. When screen modulation is used the screen power for the modulated amplifier (up to 250 volts) can be taken from the modulator power supply. The wiring shown in Fig. 9-15 provides for this, through an adjustable tap on the 25,000-ohm bleeder resistor, R_5 , in the power supply. If a separate screen supply is used, or if the modulator is used for grid-bias or plate modulation of an r.f. amplifier, the d.c. circuit should be opened at point "X" in Fig. 9-15.

The amplifier uses resistance coupling up to the output-stage grids. The first section, V_{1A} , of the 12AX7 has "contact-potential" bias. The gain control, R_1 , is in the grid circuit of the second section, V_{1B} , of the 12AX7. Negative feedback from the secondary of the output transformer, T_1 , is introduced at the cathode of this tube section. The feedback voltage is dependent on the

ratio of R_2 to R_3 , approximately, and with the constants given is sufficient to result in a considerable reduction in distortion along with improved regulation of the audio output voltage. The latter is important when the unit is used for modulating a screen or control grid, as described in the chapter on amplitude modulation.


The phase inverter is of the split-load type described earlier in this chapter. It drives the push-pull 6AQ5's in the power amplifier. The output transformer used in the power stage is a multitap modulation transformer suitable for any of the types of modulation mentioned above.

Capacitor C_1 across the secondary of the output transformer, T_1 , is used to reduce the high-frequency response of the amplifier. Without it, self-oscillation is likely to occur at a high audio frequency (usually above audibility) because phase shift in the output transformer at the end of its useful frequency range causes the feedback to become positive.

The power supply uses a replacement-type transformer and choke with a capacitor-input filter. Voltage under the modulator and speech-amplifier load is 250. The decoupling resistance-capacitance networks in the plate circuits of V_{1A} and V_{1B} contribute additional smoothing of the d.c. for these low-level stages.

The unit includes provision for send-receive switching, S_1 being used for that purpose. S_{1B} can be used to control the r.f. section — for example, by being connected in parallel with the key used for c.w. operation. Simultaneously S_{1A} short-circuits the secondary of T_1 so the transformer will not be damaged by being left without

Fig. 9-14—Speech amplifier and low-power modulator suitable for screen or control-grid modulation of high-power amplifiers, or for plate modulation of an r.f. stage with up to 15 watts plate input. It is assembled on a 7 × 9 × 2-inch steel chossis, with the power supply occupying the left-hand section and the audio circuits the right. The 12AX7 preamplifier is at the lower right-hand corner, the 6C4 phase inverter is to its left, and the 6AQ5 power amplifiers are behind the two. Controls along the chassis edge are, left to right, the power switch, send-receive switch, gain control, and microphone jack.

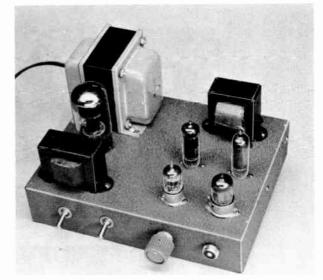

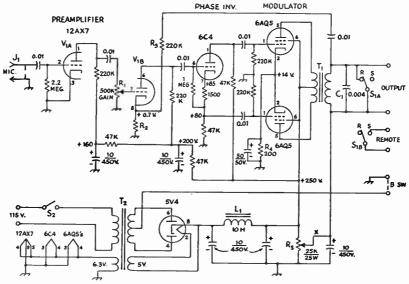


Fig. 9-15—Circuit of the speech amplifier and modulator. All capacitances are in μf .; capacitors with polarities marked are electrolytic, others are ceramic. Resistors are $\frac{1}{2}$ watt except as noted below. Voltages measured to chassis with v.t. voltagetre.

J1-Microphone connector (Amphenol 75-PC1M).

L₁-10 henrys, 90 ma. (Triad C-7X).

\$1-D.p.d.t. toggle.

S₂-S.p.s.t. toggle.

T₁—Modulation transformer, tapped secondary, primary 10,000 ahms plate to plate (Thordar-

load. If S_{1B} is connected across the transmitter key, S_1 also can be used as a phone-c.w. switch, being left in the "R" position for c.w. operation.

The terminals marked "B Switch" should be short circuited (indicated by the dashed line) if S_1 is used as a send-receive switch. If a switch on the transmitter is used for send-receive, these terminals may be used for turning the plate voltage in the modulator on and off through an extra pair of contacts on the transmitter send-receive

son 21M68).


T₂—Power transformer, 525 v.c.t., 90 ma.; 6.3 v., 5 amp.; 5 v., 2 amp. (Triad R-10A).

 $R_2{-}1500$ ohms, $1\!/_{\!2}$ watt.

R₄—App. 200 ahms, 2 watts (two 390-ohm 1-watt resistors in parallel).

switch. In that case S_1 should be left in the "send" position for phone operation.

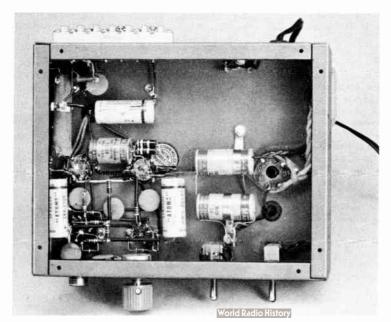The proper secondary taps to use on T_1 will depend on the impedance of the load to which the amplifier is connected. Methods for determining the modulating impedance with various types of modulation are given in the section on amplitude modulation, together with information on connecting the modulator to the r.f. stage.



9-16—Below-chassis Fia. view of the modulator. The rectifier tube socket and electrolytic filter capacitors are at the right in this view. The 12AX7 socket is at the lower left. Bleeder resistor R5 is at the upper left, near the 6-terminal connection strip on the rear edge of the chassis. Placement of components is not critical, but the leads in the first two stages should be kept short and close to the chassis to minimize hum troubles

A 25-WATT MODULATOR USING PUSH-PULL 6BQ6GTs

The speech amplifier-modulator shown in Figs. 9-17 to 9-19, inclusive, can be used for plate modulation of low-power transmitters running 25 to 50 watts input to the final stage. The circuit as shown is capable of an audio output of 25 watts, but this can be increased to 30 watts by a simple modification. The 6BQ6s in the output stage are operated in Class AB1. Inexpensive receiver-type replacement components are used throughout, except for the modulation transformer.

The speech amplifier uses a pentode first stage resistance-coupled to a triode second stage. This combination gives sufficient gain for a crystal microphone. The pentode and triode are the two sections of a dual tube, the 6AN8. Transformer coupling is used between the triode and the modulator tubes, in order to get push-pull voltage for the 6BQ6GT grids. Cathode bias is used on the final stage.

The coupling capacitance between the first and second stages is purposely made small to reduce the low-frequency response, and the primary of the output transformer is shunted by C_2 to reduce the amplification at the high-frequency end. C1, on the first stage, also tends to reduce highfrequency response in addition to bypassing any r.f. that might be picked up on the microphone cord. These measures confine the frequency response to the most useful portion of the voice range.

 S_2 is the "send-receive" switch. One section opens the power transformer center tap, thus cutting off the plate voltage during receiving periods. The other section can be connected to the key terminals on the transmitter, as indicated in the circuit diagram, to turn the transmitter on and off along with the modulator. If the transmitter is one in which the oscillator is not keyed, S_{2B} may be used to control the transmitter plate voltage, usually by being connected in the 115-volt circuit to the plate-supply transformer.

The "phone-c.w." switch, S_3 , short-circuits the secondary of the modulation transformer, T_3 , when the transmitter is to be keyed, and also opens the center-tap of T_1 so plate voltage cannot be applied to the modulator.

The power supply uses a receiver replacementtype transformer with a capacitor-input filter. Additional filtering for the speech-amplifier stages is provided by the 10-µf. capacitors and the series resistors in the plate circuits. Hum is also reduced by the VR-150 used to regulate the modulator screen voltage. Note that the regulator tube is connected between the screens and cathodes so that the actual screen voltage is 150 and is not reduced by the drop in the cathode bias resistor. Maintaining full screen voltage is important if the rated output is to be secured.


Operating

The 6BQ6GT amplifier requires a plate-toplate load of 4000 ohms, and the output transformer ratio must be chosen to reflect this load to the plates (see later section on matching a modulator to its load). For most small transmitters running 30 to 50 watts input to the final stage a 1-to-1 transformer ratio will be satisfactory, since the modulating impedance of such transmitters usually is in the neighborhood of 4000 ohms. The secondary of T_3 is connected in series with the d.c. lead to the plate (and screen, if a screen-grid tube) of the Class C amplifier to be modulated. For further details, see the chapter on amplitude modulation.

For checking the modulator operation a milliammeter (0-200 range satisfactory) may be connected in the lead to the center-tap of the primary of T_3 . Without voice input to the microphone the plate current should be approximately

Fig. 9-17—A modulator for transmitters operating at plate inputs up to 50 watts. The speech amplifier and modulator are at the left in this view; power supply components are at the right. The chassis is 7 imes 11 imes 2 inches.



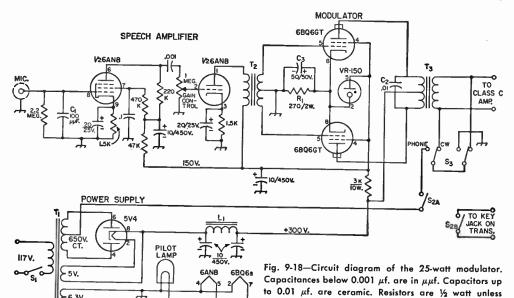

otherwise specified.

L₁-8 henrys, 150 ma.

S₁-S.p.s.t. toggle.

S2-D.p.d.t. toggle.

S₈-2-pole 2-position rotary (Centralab PA-2003).

 \overline{A}

T₁-Power transformer, 650 valts c.t., 150 ma. 5 volts 3 amp.; 6.3 volts, 5 amp.

T₂—Interstage audio, single plate to p.p. grids, pri, to total sec. ratio 1 to 3.

T₈—Modulation transformer, multimatch type (UTC S-19).

50 ma. When modulating the transmitter, the current should "kick" to 60 or 70 ma.; this will usually represent 100 per cent modulation. If the amplifier can be tested with a single-tone signal replacing the microphone, the plate current will be about 165 ma. at full output.

The audio power output can be increased to about 30 watts, sufficient for modulating an 807

at its full phone rating, if the 6BO6GT cathodes are grounded and bias of about 30 volts from a fixed source such as a small battery is applied to the grids. The battery may be substituted for the cathode resistor if the ground connection is moved from the center tap of the secondary of T_2 to the cathodes of the 6BQ6GTs.

(From QST, December, 1955.)

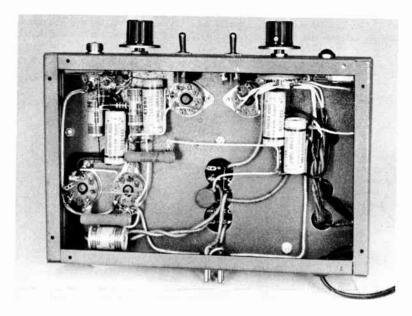


Fig. 9-19-Underchassis view of the 6BQ6GT modulator. The two large capacitors at the right are the filter capacitors in the power supply. The modulator bias resistor and bypass capacitor (R_1C_3) are at lower left. Leads from the modulation transformer go through the three holes in the chassis. Shielded wire is used for heater, microphone input, and gaincontrol leads.

A 50-WATT CLASS AB1 MODULATOR

Four type 1625 tubes were used in the output stage of the modulator shown in Figs. 9-20 and 9-22 for several good reasons. These tubes, 12-volt heater versions of the popular 807, are widely available on the surplus market at attractive prices. With the economical power supply shown here, four 1625s will deliver up to 50 watts of audio, sufficient to modulate a 100-watt transmitter. At higher plate voltages, four 1625s in Class AB₁ will furnish up to 140 watts (at 750 plate volts), sufficient to modulate a 280-watt transmitter.

Referring to the circuit diagram, the speech amplifier consists of a 6AV6 triode and the two triodes of a 6CG7. Transformer coupling between V_{1B} and the modulator tubes gives adequate signal for the 1625s at any rated plate voltage. A built-in bias supply, using a voltage-tripling circuit and selenium rectifiers CR_1 , CR_2 and CR_3 , furnishes operating bias that can be set to the proper value by R_2 . During standby conditions, the modulator is turned off by opening the circuit at J_3 or by adding additional bias through

 J_4 . Since connecting four tetrodes in push-pull parallel can often yield parasitic oscillations, resistors are connected in both control and screen grid circuits of the modulator tubes. With these resistors present, there should be no instabilities of any kind. The low- and high-frequency responses are restricted to good communications levels by proper proportioning of the coupling capacitors and the shunt capacitors. The 0.004- μ f. capacitor across the secondary of T_2 will have a greater effect on restricting high-frequency response if a high-voltage low-current amplifier is being modulated than if a low-voltage high-current r.f. stage is used. The 0.004- μ f. value was selected for use with a 400-volt 200-ma. amplifier.

Provision for connecting an external modulation monitor (see Chapter 10) is included, as well as a power outlet, J_5 , for the monitor or other auxiliary equipment.

Construction

The modulator is built on a $17 \times 10 \times 3$ -inch steel chassis, although an aluminum chassis would

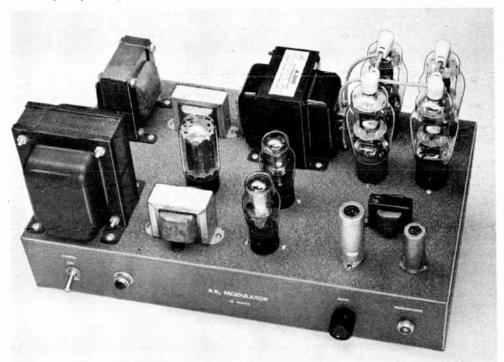


Fig. 9-20—A 50-watt modulator, using four 1625-type tubes in Class AB₁. With higher plate voltage and a larger modulation transformer, the tubes can deliver up to 140 watts of audio power.

Speech amplifier tubes and coupling transformer are at the right, in front of the four 1625s. The two voltage-regulator tubes in the center, in front of the modulation transformer, stabilize the screen voltage on the 1625s.

Power-supply filter choke is at the upper left-hand corner, and the small choke to the immediate right is connected in the screen circuit if a screen-grid r.f. amplifier is used. If desired, a cane-metal housing can be used over the modulator, but the use of high-voltage wire and insulated plate caps practically eliminates the danger of electrical shock when the unit is in its normal position.

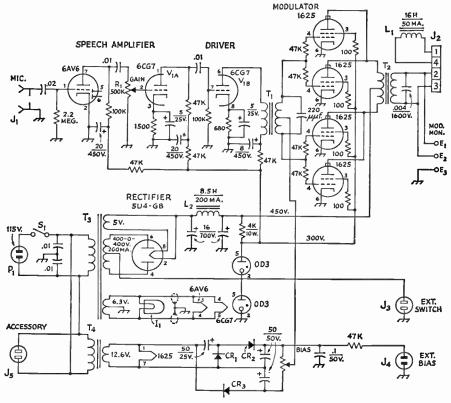


Fig. 9-21—Circuit diagram of the 50-watt modulator. Unless specified otherwise, capacitances are in μ f., resistors are $\frac{1}{2}$ watt.

 $C_1-0.004~\mu f.$, but subject to modification. See text. CR₁, CR₂, CR₃-20-ma. 130-v. selenium rectifier. E₁, E₂, E₃-Nylon tip jacks (Johnson 105-601, 105-602 105-603).

I₁-6.3-volt pilot lamp.

 J_1 -Microphone connector (Amphenol 75-PC1M), J_2 -4-prong tube socket.

J_a, J_a—2-pin chassis-mounting a.c. receptacle (Amphenol 61-F1).

J₄—Phono jack.

L₁—Screen choke, used when modulating tetrode amplifier.

probably be almost as strong and would be definitely easier to drill and punch. The components were arranged to keep a.c. leads a reasonable distance away from the speech-amplifier circuits, and the heater leads to the 6AV6 and 6CG7 were run in shielded wire. These shielded leads, and the shielded leads carrying 115 v. a. c., were run along the folded corners of the chassis. Another precaution in wiring the modulator is to keep the leads to and from T_2 away from the speech-amplifier portion of the modulator, to reduce the chances for feedback and consequent audio oscillation. The leads to and from T_2 should be made with well-insulated wire, and wherever they pass through the chassis rubber grommets should be used.

The connections to T_2 will depend upon the voltage-to-current ratio of the d.c. input to the

L₂-8.5-henry 200-ma. filter choke (Knight 61 G 409 or equiv.).

P1-A.c. line plug.

R₁-Volume control, audio taper.

R2-2-watt wire-wound control, linear taper.

S1-S.p.s.t. toggle switch.

T₁—1:3 ratio interstage transformer (Triad A-31X).

 T_2 —60-watt modulatian transformer (Stancor A-3893). T_8 —400-0-400 v, at 200 ma., 5 v. at 3 a., 6.3 v. at

5 a (Knight 61 G 414 or equiv.). T₄—12.6 v. at 2 a. (Knight 61 G 420 or equiv.).

modulated stage. With the power supply shown, the modulator is well suited to work with the 75-watt 6DQ5 transmitter and the 90-watt allpurpose amplifier described in Chapter Six. The proper load for the four 1625s, with 450 volts on the plates, is 3800 ohms, rising to 6000 ohms with 750 volts on the plates. An instruction sheet is furnished with the transformer; to determine the transformer taps to be used, first measure the plate voltage and current of the modulated stage. Divide the voltage by the current in amperes, to determine the secondary load, and from the instruction sheet select the connections that come closest to matching the secondary load to 3800 ohms. Although it is not likely that an exact match will be possible, it is of little or no consequence. The ratio of the impedance is the important consideration.

Operation

When the modulator is completed, connect a key or other external switch temporarily at J_3 , and short-circuit J_4 . Plug P_1 into an a.c. outlet, plug in the 5U4-GB and the 0D3s, and turn on S_1 . The filament of the 5U4-GB should glow. Close the key or switch at J_3 ; the 0D3s should light. Open the external switch and plug in the speech amplifier tubes. After allowing time for the 6AV6 and 6CG7 to warm up, as indicated by the heater glow, turn on the external switch and turn off S_1 . Allow a half minute for the filter capacitors to be discharged by the speech amplifier tubes, and then check with a voltmeter that no charge is left in the filter. Open the external switch, plug in the 1625s, and close S_1 . After the heaters warm up, set the arm of R2 to give a voltage of -32 between arm and chassis. Connect the transmitter or a dummy load to the modulator output (never operate the modulator without a load; the modulation transformer insulation may break down). Set the volume control at minimum (arm of R_1 at chassis end) and close J_3 . With a microphone connected at J_1 , speaking into the mike and slowly opening R_1 should deliver audio output from the modulator.

To obtain more power from the four 1625s, it is necessary to use a higher-powered modulation transformer at T_2 and to raise the plate voltage and grid bias. At 750 volts on the plates, the bias should be -35 volts.

The modulator should be turned on and off with the transmitter, so that a load is always furnished for the transformer. The modulator can be placed on standby by opening the circuit at J_3 , or by adding additional negative voltage at J_4 , depending upon the basic station control circuitry.

If a number of 1625s are available, it is desirable to select four that have substantially the same plate current (28 ma.) for the -32 volts bias. The plate currents of the individual tubes can be measured between insulating plate cap and the tube plate cap, connecting the + terminal of the milliammeter to the transformer lead. Turn off the equipment between measurements to avoid the possibility of a dangerous electrical shock.

As with any modulator using an output transformer, the secondary winding should be short-circuited (or the modulator disconnected) when the r.f. amplifier is used for c.w. or as a linear amplifier.

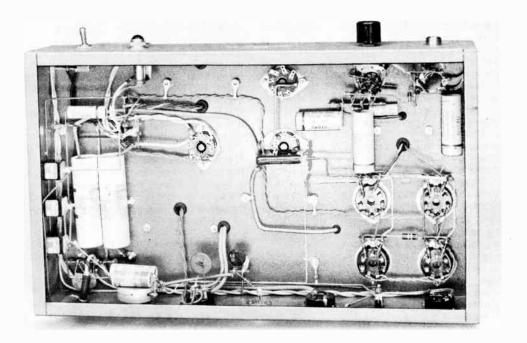


Fig. 9-22—Under the chassis of the 50-watt madulator. Three selenium rectifiers in the bias supply are mounted on the left-hand wall of the chassis. Associated camponents are grouped around the speech-amplifier sockets (upper right).

Components mounted on the rear apron of the chassis, from left to right, are bias potentiometer, audio power socket J_2 , external bias connection J_4 , external switch connection J_3 , modulation monitor terminals E_2 , E_2 and E_3 , and the accessory socket J_3 .

Shielded wire is used on 60-cycle a.c. leads in the power transformer primaries and secondaries to reduce the possibility of hum pick-up in the speech amplifier section.

A 6146 MODULATOR AND SPEECH AMPLIFIER

The modulator shown in Figs. 9-23 to 9-25, inclusive, uses a pair of 6146s in AB_1 , and is complete with power and bias supplies on a $10 \times 17 \times 3$ -inch chassis. The modulator also is equipped with an audio take-off for scope monitoring.

The audio power that can be obtained (based on measurements) is as follows:

Nominal Plate Voltage	Power Output	Plate-tp-Plate Load Resistance
500 volts	75 watts	4200 ohms
600 volts	95 watts	5200 ohms
750 volts	120 watts	6700 ohms

Suitable sets of components for all three of the voltages listed above are readily available, so the power level can be selected to suit the Class C amplifier to be modulated. The modulator shown in the photographs is set up for 750-volt operation, but aside from the power and modulation transformers all components are the same regardless of the voltage level.

Audio Circuits

As shown in the circuit diagram, Fig. 9-24, the audio system consists of a 12AX7 preamplifier with the two tube sections in cascade, followed by a 6C4 voltage amplifier which is transformer-coupled to the grids of the Class AB_1 modulator tubes. The combination provides ample gain for a communications-type crystal, ceramic, or dynamic microphone.

The first stage of the amplifier is "contact-potential" biased, and is resistance-coupled to the second stage. The gain control, R_1 , is in the grid circuit of the second stage. Decoupling resistors and capacitors are included in the plate-supply circuits of these two stages; these decoupling circuits also provide additional plate-supply hum filtering for the two low-level stages.

The secondary of T_1 , the transformer coupling the third speech stage to the modulator grids, is shunted by a 470- $\mu\mu$ f. capacitor to reduce high-

frequency response. The optimum value of capacitance will depend on the particular type of audio transformer selected, as well as on the high-frequency characteristics of the microphone employed. Different values should be tried, to reduce the high-frequency response as much as possible, consistent with intelligibility.

The modulation transformer is of the multimatch type, and the taps should be selected to reflect the proper plate-to-plate load impedance, as given earlier, for the desired power output. The impedance ratio, secondary to primary, will depend on the modulating impedance of the modulated r.f. amplifier, as described earlier in this chapter. The secondary of the modulation transformer is shunted by C_1 to reduce output at the higher audio frequencies, particularly for attenuating high-frequency harmonics that might be generated in the modulator at high output levels. The value suggested (0.005 μ f.) is an average figure and should be modified according to the modulating impedance of the Class-C stage as discussed earlier in this chapter.

Power Supply

Plate power for all tubes in the unit is supplied by a single power transformer. Mercury-vapor rectifiers are used because good voltage regulation is desirable. The filter is a single section with choke input and a large (over $25~\mu f$.) output capacitance. The filter capacitor consists of three $80-\mu f$. 450-volt electrolytic capacitors in series for 750-volt d.c. output. If the output voltage is 600 or less only two capacitors in series will be needed. These capacitors are shunted by 0.1-megohm resistors to help equalize the d.c. voltages across them.

The 200-volt (approximately) supply for the 6146 screens and the plates of the speech-amplifier tubes is taken from the main supply through a dropping resistor, and is regulated by two 0B2 voltage-regulator tubes in series. A 20-µf. capacitor is connected across the VR tubes to im-

Fig. 9-23—Class-AB₁ modulator using 6146s, complete with speech amplifier and power supply. The relay-rack panel is 101/2-inches high. Plate- and filament-supply primary switches, each with its own pilot lamp, are near the lower edge of the panel. The gain control is at lower center. Along the front of the chassis, just behind the panel, are the plate power transformer, filter choke, and modulation transformer, going from left to right. The tubes at the left are the 816 rectifiers, with the 6146s at the right. Along the rear edge are the two voltageregulator tubes, the 12AX7 and 6C4 speech amplifier tubes, and the interstage audio transformer, T1.



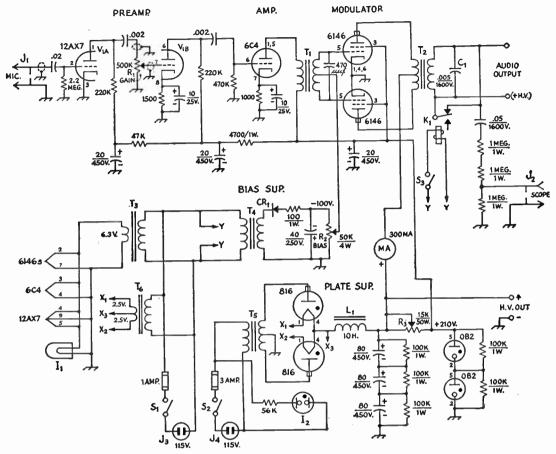


Fig. 9-24—Circuit diagram of the 6146 modulator and power supply. Capacitances are in μ f. unless indicated otherwise; capacitors marked with polarity are electrolytic, others may be paper or ceramic as convenient.

Resistances are in ohms; resistors are $\frac{1}{2}$ watt except as indicated.

C₁-See text.

CR₁-Selenium rectifier, 20 ma. ar higher, 130 volts.

1,-6.3-volt pilot lamp.

12-Neon lamp, NE-51.

J₁-Microphone connector (Amphenol 75-PC1M).

J2-Phono jack.

J₃, J₄—115-volt chassis-mounting plug (Amphenol 61-M1).

K₁—Antenna changeover relay, 115-volt cail (Advance AH/2C/115VA; type AM also suitable).

L₁-Filter choke, 10 henrys, 300 ma. (Triad C-19A).

R₁-0.5-megohm control, audio taper.

R₂-50,000-ohm wire-wound control, 4 watts.

R₃-15,000-ohm adjustable, 50 watts.

S₁, S₂-S.p.s.t. toggle.

S3-S.p.s.t. mounted on R1.

prove the dynamic regulation in the 6146 screen circuit, since the peak instantaneous screen current exceeds the regulating capacity (30 ma.) of the VR tubes when the modulator is driven to maximum output.

Fixed bias for the 6146 grids is taken from a built-in bias supply using a TV "booster" transformer with a selenium rectifier. This bias is

T₁—Interstage audio, single plate ta p.p. grids, 3-to-1 secandary-to-primary ratio (Stancor A-63-C). T₂—Multimatch modulation transformer, 125 watts

(Triad M-12AL).

T₃—Filament transformer, 6.3 volts at 4 amp. (Triad F-53X).

T₄—Power transformer, 117 volts at 20 ma.; 6.3-volt winding unused (Thordarson 26R32).

T₈—Plate transformer. For 500 volts d.c.: 1235 volts c.t., 310 ma. (Triad P-7A); for 600 volts d.c.: 1455 volts c.t., 310 ma (Triad P-11A). Transformer shown is for either 600 or 750 volts d.c. output at 310 ma.; sec. voltage 1780 c.t. for 750 volts (Triad P-14A).

T₆--Filament transformer, 5 volts at 3 amp., 2500-volt insulation (Stancor P-4088).

adjustable by means of R_2 . The bias supply and filament transformer are on the same a.c. circuit so that bias is applied to the modulator grids whenever the tube heaters are energized.

Control and Auxiliary Circuits

The modulator includes an oscilloscope takeoff circuit consisting of the 0.05-µf. capacitor and

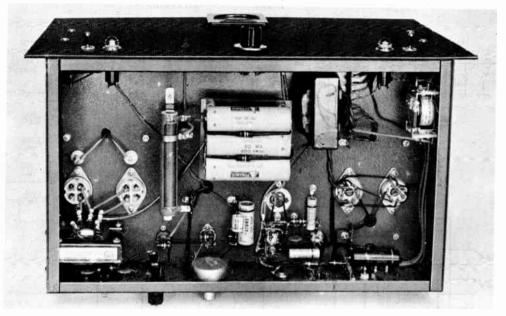


Fig. 9-25—Below-chassis view of the 6146 modulator. The 816 sockets and filament transformer (T_6) are at the lower left. The chassis wall at the bottom has on it, left to right, the 115-volt a.c. plugs, fuse holders, bias control (R_2), microphone input connector (J_1), scope take-off connector (J_2) and a three-terminal strip (Millen 37303) for audio output and positive high voltage connections. The high-voltage filter capacitor bank is in the center, mounted on a plate of plastic insulation which is supported away from the chassis on small pillars. The 6.3-volt transformer (T_2) is to the right of the capacitors. The antenna changeover relay used for shorting the modulation-transformer secondary is on the right-hand chassis wall,

three 1-megohm resistors in series. This can be used for horizontal deflection of a c.r. tube to give the trapezoidal modulation pattern (see chapter on amplitude modulation). Usually, it will be necessary to use an external control for adjusting the amplitude of the sweep voltage so obtained. If desired, a 1-megohm control can be substituted for the fixed resistor at the bottom of the string, thus avoiding the necessity for an external control.

The normally closed contacts of an antennatype relay, K_1 , are used to short-circuit the secondary of the modulation transformer when the transmitter is to be used for c.w. work. The switch, S_3 , that controls the relay is mounted on the gain control, R_1 , so that when the gain is turned all the way off, thus opening the switch, the relay contacts close. This insures that the modulator is inoperative and cannot be driven by accidental voice input (which would result in excessive plate current) when the transformer secondary is short-circuited.

Separate a.c. inputs are provided for the filament-bias and plate power circuits. The plate supply can thus be controlled by an external switch without disturbing the operation of the filament circuits or requiring a modification of the 115-volt wiring.

Terminals are provided for taking out highvoltage d.c. for an external unit. The powersupply equipment has more capacity than is needed by the modulator unit itself (the rating for amateur-type service is somewhat over 300 ma.) and may in some cases be sufficient for operation of the modulated r.f. amplifier as well. At least 200 ma. should be available for this purpose, since the average plate-supply current in the modulator unit alone is less than 100 ma., including the speech-amplifier and VR-tube drain.

Operating Data

The dropping resistor in the screen-supply circuit should be adjusted so that the current through 0B2s is 30 ma. with the bias on the 6146 grids adjusted so that the no-signal plate current is approximately 50 ma. The current through the VR tubes may be measured by opening the lead to the upper 0B2 at pin 5 and inserting a milliammeter of appropriate range.

If a sine-wave signal is used for testing the modulator, full output should be secured with a modulator plate current of approximately 240 ma. This value will be the same for all plate voltages, provided the screen voltage is maintained at approximately 200 volts and the values of plate-to-plate load resistance as specified earlier are used. With voice input the plate current will kick up to about 100 ma. on peaks, depending on the characteristics of the speaker's voice and those of the microphone used. This peak value should be determined under actual operating conditions with an oscilloscope, after which the plate milliammeter can be used as a modulation indicator.

CLASS B MODULATOR WITH FILTER

Representative Class B modulator construction is illustrated by the unit shown in Figs. 9-26 and 9-28. This modulator includes a splatter



Fig. 9-26—A typical Class B modulator arrangement. This unit uses a pair of 811As, capable of an audio power output of 340 watts, and includes a splatter filter. The modulation transformer is at the left and the splatter choke at the right. All high-voltage terminals are covered so they cannot be touched accidentally.

filter, $C_1C_2L_1$ in the circuit diagram, Fig. 9-27, and also has provision for short-circuiting the modulation transformer secondary when c.w. is to be used.

The audio input transformer is not built into

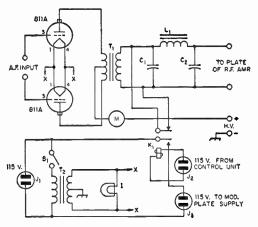


Fig. 9-27—Circuit diagram of the Class B modulator. C₁, C₂, L₁—See text. (L₁ is Chicago Transformer type SR-300).

K₁—D.p.d.t. relay, high-voltage insulation (Advance type 400).

M—0-500 d.c. milliammeter, bakelite case.
T₁—Variable-ratio modulation transformer (Chicago
Transformer type CMS-1).

T₂—Filament transformer, 6.3 v., 8 omp. 1₁—6.3-volt pilot light.

X₁, X₂—Chassis-type 115-volt plugs, male. X₃—Chassis-type 115-volt receptacle, female.

S₁-S.p.s.t. toggle.

this unit, it being assumed that this transformer will be included in the driver assembly as is customary. If the modulator and speech amplifier-driver are mounted in the same rack or cabinet, the length of leads from the driver to the modulator grids presents no problem. The bias required by the modulator tubes at their higher plate-voltage ratings should be fed through the center tap on the secondary of the driver transformer. At a plate voltage of 1250 or less no bias is needed and the center-tap connection on the transformer can be grounded.

The values of C_1 , C_2 and L_1 depend on the modulating impedance of the Class C r.f. amplifier. They can be determined from the formulas given in this chapter in the section on high-level clipping and filtering. The splatter filter will be effective regardless of whether the modulator operating conditions are chosen to give high-level clipping, but it is worth while to design the system for clipping at 100 per cent modulation if the tube curves are available for that purpose. The voltage ratings for C_1 and C_2 should at least equal the d.c. voltage applied to the modulated r.f. amplifier.

A relay with high-voltage insulation is used to short-circuit the secondary of T_1 when the

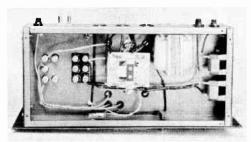


Fig. 9-28—The relay and filament transformer are mounted below the chassis. C₁, C₂ and K₁ are mounted on small stand-off insulators.

relay coil is not energized. A normally closed contact is used for this purpose. The other arm is used to close the primary circuit of the modulator plate supply when the relay is energized. Shorting the transformer secondary is necessary when the r.f. amplifier is keyed, to prevent an inductive discharge from the transformer winding that would put "tails" on the keyed characters and, with cathode keying of the amplifier, would cause excessive sparking at the key contacts. The control circuit should be arranged in such a way that K_1 is not energized during c.w. operation but is energized by the send-receive switch during phone operation.

Careful attention should be paid to insulation since the instantaneous voltages in the secondary circuit of the transformer will be at least twice the d.c. voltage on the r.f. amplifier. If a "hi-fi" amplifier of 10 watts or more output is available, it can be used as the driver for the 811As by coupling as shown in Fig. 9-29.

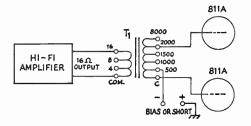


Fig. 9-29—A "hi-fi" audio amplifier will drive a Class-B modulator; a suitable coupling transformer is required. The connections shown here are for a pair of 811As. The amplifier should have an output rating of at least 10 watts.

T₁—10-watt line-to-voice-coil transformer (Stancor A-8104).

CHECKING AMPLIFIER OPERATION

An adequate job of checking speech equipment can be done with equipment that is neither elaborate nor expensive. A typical setup is shown in Fig. 9-30. The construction of a simple audio oscillator is described in the chapter on measurements. The audio-frequency voltmeter can be either a vacuum-tube voltmeter or a multirange volt-ohm-milliammeter that has a rectifier-type a.c. range. The headset is included for aural checking of the amplifier performance.

An audio oscillator usually will have an output control, but if the maximum output voltage is in excess of a volt or so the output setting may be rather critical when a high-gain speech amplifier is being tested. In such cases an attenuator such as is shown in Fig. 9-30 is a convenience.

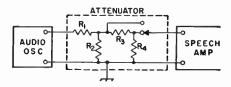


Fig. 9-30—Simple oscillator-attenuator test setup for checking a speech amplifier. It is not necessary that the frequency range of the audio oscillator be continuously variable; one or more "spot frequencies" will be satisfactory. Suitable resistor values are: R₁ and R₃, 10,000 ohms; R₂ and R₄, 1000 ohms.

Each of the two voltage dividers reduces the voltage by a factor of roughly 10 to 1, so that the over-all attenuation is about 100 to 1. The relatively low value of resistance, R_4 , connected across the input terminals also will minimize stray hum pickup on the connecting leads.

The output of a power amplifier such as a modulator or driver for a Class B stage may be checked by using a resistance load of the rated value for the amplifier. A useful circuit arrangement is shown in Fig. 9-31. The load resistance, R_1 , may be a single adjustable unit of appropriate power rating or may be made up of several resistors in series or parallel to give the required resistance. If measurement of the resistance is necessary an ohmmeter will be sufficiently accurate. In the case of a multimatch output transformer the taps should be those that will actually be used with the Class C amplifier with which the modulator is intended to work. R_1 then should have a value equal to the modulating impedance of the r.f. amplifier.

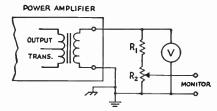


Fig. 9-31—Circuit for measuring power and making qualitative checks of the amplifier output. Values to be used for R_1 and R_2 are discussed in the text. The secondary winding of the output transformer in the amplifier should be disconnected from any d.c. source in the unit and one end connected to chassis as shown. An earth ground should be used on the system.

If an audio oscillator generating a good sine wave is used as the signal source the output power of the amplifier may be measured by an audio-frequency voltmeter as indicated by V. Either a vacuum-tube voltmeter on its a.c. scale or a rectifier-type a.c. voltmeter will be satisfactory, the principal requirements being relatively high impedance (1000 ohms per volt or more) and a reasonably accurate calibration. The power output will be equal to E^2/R_1 , where E is the r.m.s. value of the voltage across the resistor (a.c. instruments usually are calibrated in r.m.s. values). This assumes that the distortion generated in the amplifier is small; if distortion is high, the voltmeter reading will be inaccurate.

If the amplifier is a driver for a Class B modulator, the value of R_1 should be calculated from R/N^2 , where N is the turns ratio, primary to total secondary, of the class B input transformer, and R is the rated plate-to-plate load for the driver tube or tubes. R_1 should of course be connected across the total secondary in this case.

For a qualitative check on distortion, provision is made in Fig. 9-31 for monitoring the output of the amplifier. R_2 should be a wire-wound potentiometer having a resistance of 10 or 20 ohms. A headset may be connected to the "Monitor" terminals. Using the audio oscillator as a signal source, start with the gain control at minimum and then advance it slowly while listening carefully to the tone signal in the headset. When it begins to sound like a musical octave instead of a single tone, or when higher harmonically related tones can be heard along with the desired one, distortion is starting to become ap-

Checking Speech Equipment

preciable. This effect usually will be detectable, but not serious, at full output of the amplifier as indicated by the voltmeter reading. Keep the signal in the headset at a moderate level by adjusting R_2 when necessary. If the amplifier passes the distortion test satisfactorily, reduce the audio input to zero and note whether any hum is audible in the headset. There should be none, if the tone level in the headset at full sine-wave output was no more than moderately high.

After completing these checks with satisfactory results, substitute the microphone for the oscillator input to the amplifier and have someone speak into it at a moderate level. The headset will serve to indicate the speech quality at various output levels. A tape recorder, if available, is useful at this stage since it can be substituted for the headset and will provide a means for comparing the effect of changes and adjustments in the amplifier as well as giving a better over-all

in which it is occurring can be located by working from the last stage toward the front end of the amplifier, applying a signal to each grid in turn from the audio oscillator and adjusting the signal voltage for maximum output. In the case of push-pull stages, the signal may be applied to the primary of the interstage transformer—after disconnecting it from the plate-voltage source and the amplifier tube. Assuming that normal design principles have been followed and that all stages are theoretically working within their capabilities, the probable causes of distortion are wiring errors (such as accidental short-circuit of a cathode resistor), defective components, or use of wrong values of resistance in cathode and plate circuits.

Using the Oscilloscope

Speech-amplifier checking is facilitated considerably if an oscilloscope of the type having

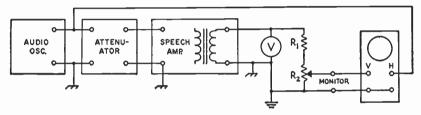


Fig. 9-32—Test setup using the oscilloscope to check for distortion. These connections will result in the type of pattern shown in Fig. 9-33, the horizontal sweep being provided by the audio input signal. For waveform patterns, omit the connection between the audio oscillator and the horizontal amplifier in the scope, and use the horizontal linear sweep.

check on speech quality than the average headset. The effect of measures taken to attenuate high- or low-frequency response in the amplifier is readily observed by comparing recordings made before and after changes. The output quality of the amplifier also can be compared with the original output of the microphone as registered on the recorder. In using a recorder care must be taken to set R_2 so that the first stage in the recorder amplifier is not overloaded. Use the normal gain setting of the recorder and adjust R_2 to give normal level indications.

Amplifier Troubles

If the hum level is too high, the amplifier stage that is causing the trouble can be located by temporarily short-circuiting the grid of each tube to ground, starting with the output amplifier. When shorting a particular grid makes a marked decrease in hum, the hum presumably is coming from a preceding stage, although it is possible that it is getting its start in that particular grid circuit. If shorting a grid does not decrease the hum, the hum is originating either in the plate circuit of that tube or the grid circuit of the next. Aside from wiring errors, a defective tube, or inadequate plate-supply filtering, objectionable hum usually originates in the first stage of the amplifier.

If distortion occurs below the point at which the expected power output is secured the stage amplifiers and a linear sweep circuit is available. A typical setup for using the oscilloscope is shown in Fig. 9-32. With the connections shown, the sweep circuit is not required but horizontal and vertical amplifiers are necessary. Audio voltage from the oscillator is fed directly to one oscilloscope amplifier (horizontal in this case) and the output of the speech amplifier is connected to the other. The scope amplifier gains should be adjusted so that each signal gives the same line length with the other signal shut off.

Under these conditions, when the input and output signals are applied simultaneously they are compared directly. If the speech amplifier is distortion-free and introduces no phase shift, the resulting pattern is simply a straight line, as shown at the upper left in Fig. 9-33, making an angle of about 45 degrees with the horizontal and vertical axes. If there is no distortion but there is phase shift, the pattern will be a smooth ellipse, as shown at the upper right. The greater the phase shift the greater the tendency of the ellipse to grow into a circle. When there is evenharmonic distortion in the amplifier one end of the line or ellipse becomes curved, as shown in the second row in Fig. 9-33. With odd-harmonic distortion such as is characteristic of overdriven push-pull stages, the line or ellipse is curved at

Patterns such as these will be obtained when the input signal is a fairly good sine wave. They will tend to become complicated if the input wave form is complex and the speech amplifier introduces appreciable phase shifts. It is therefore advisable to test for distortion with an input signal that is as nearly as possible a sine wave. Also, it is best to use a frequency in the 500–1000 cycle range, since improper phase shift in the amplifier is usually least in this region. Phase shift in itself is not of great importance in an audio amplifier of ordinary design because it does not change the character of speech so far as the ear is concerned. However, if a complex signal is used for testing, phase shift may make it difficult to detect distortion in the oscilloscope pattern.

Since the oscilloscope amplifiers themselves may introduce phase shift and possibly distortion as well, it is advisable to check the scope before attempting to make checks on the speech amplifier. Apply the signal from the audio oscillator simultaneously to the horizontal and vertical amplifier input terminals. If both amplifiers have the same phase characteristics and negligible distortion the pattern, after suitable adjustment of the gains, will be a straight line as shown at the upper left in Fig. 9-33. If distortion is visible, note whether it changes when the scope gain controls are reduced; if not, the signal voltage from the audio oscillator is too great and should be reduced to the point where the input amplifiers are not overloaded. After finding the proper settings for signal input and scope gains, leave the latter alone in making checks on the speech equipment and adjust the input to the scope by means of R_2 and the output of the audio oscillator. Phase shift in the scope itself is not serious since the presence of distortion in the speech amplifier can be detected by the patterns shown at the right in Fig. 9-33.

In amplifiers having negative feedback, excessive phase shift within the feed-back loop may cause self-oscillation, since the signal fed back may arrive at the grid in phase with the applied signal voltage instead of out of phase with it. Such a phase shift is most likely to be associated with the output transformer. Oscillation usually occurs at some frequency above 10,000 cycles, although occasionally it will occur at a very low frequency. If the pass band in the stage in which the phase shift occurs is deliberately restricted to the optimum voice range, as described earlier, the gain at both very high and very low frequencies will be so low that selfoscillation is unlikely, even with large amounts of feedback.

Generally speaking, it is easier to detect small amounts of distortion with the type of pattern shown in Fig. 9-33 than it is with the wave-form pattern obtained by feeding the output signal to the vertical plates and making use of the linear sweep in the scope. However, the wave-form pattern can be used satisfactorily if the signal from the audio oscillator is a reasonably good sine wave. One simple method is to examine the output of the oscillator alone and trace the pattern on a sheet of transparent paper. The pattern

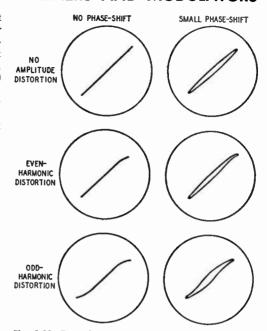


Fig. 9-33—Typical patterns obtained with the connections shown in Fig. 9-32. Depending on the number of stages in the amplifier, the pattern may slope upward to the right, as shown, or upward to the left. Also, depending on where the distortion originates, the curvature in the second row may appear either at the top or bottom of the line or ellipse.

given by the output of the amplifier can then be compared with the "standard" pattern by adjusting the oscilloscope gains to make the two patterns coincide as closely as possible. The pattern discrepancies are a measure of the distortion.

In using the oscilloscope care must be taken to avoid introducing hum voltages that will upset the measurements. Hum pickup on the scope leads or other exposed parts such as the amplifier load resistor or the voltmeter can be detected by shutting off the audio oscillator and speech amplifier and connecting first one and then the other to the vertical plates of the scope, setting the internal horizontal sweep to an appropriate width. The trace should be a straight horizontal line when the vertical gain control is set at the position used in the actual measurements. Waviness in the line indicates hum. If the hum is not in the scope itself (check by disconnecting the leads at the instrument) make sure that there is a good ground connection on all the equipment and, if necessary, shield the hot leads.

The oscilloscope can be used to good advantage in stage-by-stage testing to check wave forms at the grid and plate of each stage and thus to determine rapidly where a source of trouble may be located. When the scope is connected to circuits that are not at ground potential for d.c., a capacitor of about 0.1 μ f. should be connected in series with the hot oscilloscope lead. The probe lead should be shielded to prevent hum pickup.

Amplitude Modulation

As described in the chapter on circuit fundamentals, the process of modulation sets up groups of frequencies called **sidebands**, which appear symmetrically above and below the frequency of the unmodulated signal or carrier. If the instantaneous values of the amplitudes of all these separate frequencies are added together, the result is called the modulation envelope. In amplitude modulation (a.m.) the modulation envelope follows the amplitude variations of the audio-frequency signal that is being used to modulate the wave.

For example, modulation by a 1000-cycle tone will result in a modulation envelope that varies in amplitude at a 1000-cycle rate. The actual r.f. signal that produces such an envelope consists of three frequencies - the carrier, a side frequency 1000 cycles higher, and a side frequency 1000 cycles lower than the carrier. These three frequencies easily can be separated by a receiver having high selectivity. In order to reproduce the original modulation the receiver must have enough bandwidth to accept the carrier and the sidebands simultaneously. This is because an a.m. detector responds to the modulation envelope rather than to the individual signal components, and the envelope will be distorted in the receiver unless all the frequency components in the signal go through without change in their relative am-

In the simple case of tone modulation the two side frequencies and the carrier are constant in amplitude—it is only the envelope amplitude that varies at the modulation rate. With more complex modulation such as voice or music the amplitudes and frequencies of the side frequencies vary from instant to instant. The amplitude of the modulation envelope varies from instant to instant in the same way as the complex audio-frequency signal causing the modulation. Nevertheless, even in this case the *carrier* amplitude is constant if the transmitter is properly modulated.

A.M. Sidebands and Channel Width

Speech can be electrically reproduced, with high intelligibility, in a band of frequencies lying between approximate¹y 100 and 3000 cycles. When these frequencies are combined with a radio-frequency carrier, the sidebands occupy the frequency spectrum from about 3000 cycles below the carrier frequency to 3000 cycles above—a total band or channel of about 6 kilocycles.

Actual speech frequencies extend up to 10,000 cycles or more, so it is possible to occupy a 20-kc.

channel if no provision is made for reducing its width. For communication purposes such a channel width represents a waste of valuable spectrum space, since a 6-kc. channel is fully adequate for intelligibility. Occupying more than the minimum channel creates unnecessary interference. Thus speech equipment design and transmitter adjustment and operation should be pointed toward maintaining the channel width at the minimum.

THE MODULATION ENVELOPE

In Fig. 10-1 the drawing at A shows the unmodulated r.f. signal, assumed to be a sine wave of the desired radio frequency. The graph can be taken to represent either voltage or current.

In B, the signal is assumed to be modulated by the audio frequency shown in the small drawing above. This frequency is much lower than the carrier frequency, a necessary condition for good modulation. When the modulating voltage is "positive" (above its axis) the envelope amplitude is increased above its unmodulated amplitude; when the modulating voltage is "negative" the envelope amplitude is decreased. Thus the envelope grows larger and smaller with the polarity and amplitude of the modulating voltage.

The drawings at C shows what happens with stronger modulation. The envelope amplitude is doubled at the instant the modulating voltage reaches its positive peak. On the negative peak of the modulating voltage the envelope amplitude just reaches zero; in other words, the signal is completely modulated.

Percentage of Modulation

When a modulated signal is detected in a receiver, the detector output follows the modulation envelope. The stronger the modulation, therefore, the greater is the useful receiver output. Obviously, it is desirable to make the modulation as strong or "heavy" as possible. A wave modulated as in Fig. 10-1C would produce considerably more useful audio output than the one shown at B.

The "depth" of the modulation is expressed as a percentage of the unmodulated carrier amplitude. In either B or C, Fig. 10-1, X represents the unmodulated carrier amplitude, Y is the maximum envelope amplitude on the modulation uppeak, and Z is the minimum envelope amplitude on the modulation downpeak.

In a properly operating modulation system the modulation envelope is an accurate reproduction of the modulating wave, as can be seen in Fig.

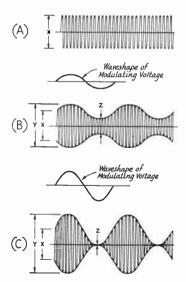


Fig. 10-1—Graphical representation of (A) r.f. output unmodulated, (B) modulated 50%, (C) modulated 100%. The modulation envelope is shown by the thin outline on the modulated wave.

10-1 at B and C by comparing one side of the outline with the shape of the modulating wave. (The lower outline duplicates the upper, but simply appears upside down in the drawing.)

The percentage of modulation is

% Mod. =
$$\frac{Y-X}{X} \times 100$$
 (upward modulation), or % Mod. = $\frac{X-Z}{X} \times 100$ (downward modulation)

If the wave shape of the modulation is such that its peak positive and negative amplitudes are equal, then the modulation percentage will be the same both up and down. If the two percentages differ, the larger of the two is customarily specified.

Power in Modulated Wave

The amplitude values shown in Fig. 10-1 correspond to current or voltage, so the drawings may be taken to represent instantaneous values of either. The power in the wave varies as the square of either the current or voltage, so at the peak of the modulation up-swing the instantaneous power in the envelope of Fig. 10-1C is four times the unmodulated carrier power (because the current and voltage both are doubled). At the peak of the down-swing the power is zero, since the amplitude is zero. These statements are true of 100 per cent modulation no matter what the wave form of the modulation. The instantaneous envelope power in the modulated signal is proportional to the square of its envelope amplitude at every instant. This fact is highly important in the operation of every method of amplitude modulation.

It is convenient, and customary, to describe the operation of modulation systems in terms of sine-wave modulation. Although this wave shape is seldom actually used in practice (voice wave shapes depart very considerably from the sine form) it lends itself to simple calculations and its use as a standard permits comparison between systems on a common basis. With sine-wave modulation the average power in the modulated signal over any number of full cycles of the modulation frequency is found to be 1½ times the power in the unmodulated carrier. In other words, the power output increases 50 per cent with 100 per cent modulation by a sine wave.

This relationship is very useful in the design of modulation systems and modulators, because any such system that is capable of increasing the average power output by 50 per cent with sinewave modulation automatically fulfills the requirement that the instantaneous power at the modulation up-peak be four times the carrier power. Consequently, systems in which the additional power is supplied from outside the modulated r.f. stage (e.g., plate modulation) usually are designed on a sine-wave basis as a matter of convenience. Modulation systems in which the additional power is secured from the modulated r.f. amplifier (e.g., grid modulation) usually are more conveniently designed on the basis of peak envelope power rather than average power.

The extra power that is contained in a modulated signal goes entirely into the sidebands, half in the upper sideband and half into the lower. As a numerical example, full modulation of a 100-watt carrier by a sine wave will add 50 watts of sideband power, 25 in the lower and 25 in the upper sideband. Supplying this additional power for the sidebands is the object of all of the various systems devised for amplitude modulation.

No such simple relationship exists with complex wave forms. Complex wave forms such as speech do not, as a rule, contain as much average power as a sine wave. Ordinary speech wave forms have about half as much average power as a sine wave, for the same peak amplitude in both wave forms. Thus for the same modulation percentage, the sideband power with ordinary speech will average only about half the power with sine-wave modulation, since it is the peak envelope amplitude, not the average power, that determines the percentage of modulation.

Unsymmetrical Modulation

In an ordinary electric circuit it is possible to increase the amplitude of current flow indefinitely, up to the limit of the power-handling capability of the components, but it cannot very well be decreased to less than zero. The same thing is true of the amplitude of an r.f. signal; it can be modulated *upward* to any desired extent, but it cannot be modulated *downward* more than 100 per cent.

When the modulating wave form is unsymmetrical it is possible for the upward and downward modulation percentages to be different. A simple case is shown in Fig. 10-2. The positive peak of the modulating signal is about 3 times the amplitude of the negative peak. If, as shown

The Modulation Envelope

in the drawing, the modulating amplitude is adjusted so that the peak downward modulation is just 100 per cent (Z=0) the peak upward modulation is 300 per cent (Y=4X). The carrier amplitude is represented by X, as in Fig. 10-1. The modulation envelope reproduces the wave form of the modulating signal accurately, hence there is no distortion. In such a modulated signal the increase in power output with modulation is considerably greater than it is when the modulation is symmetrical and therefore has to be limited to 100 per cent both up and down.

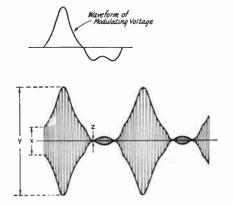


Fig. 10-2—Modulation by an unsymmetrical wave form. This drawing shows 100% downward modulation along with 300% upward modulation. There is no distortion, since the modulation envelope is an accurate reproduction of the wave form of the modulating voltage.

In Fig. 10-2 the peak envelope amplitude, Y, is four times the carrier amplitude, X, so the peakenvelope power is 16 times the carrier power. When the upward inodulation is more than 100 per cent the power capacity of the modulating system obviously must be increased sufficiently to take care of the much larger peak amplitudes.

Overmodulation

If the amplitude of the modulation on the

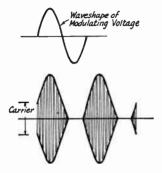


Fig. 10-3—An overmodulated signal. The modulation envelope is not an accurate reproduction of the wave form of the modulating voltage. This or any type of distortion occurring during the modulation process generates spurious sidebands or "splatter."

downward swing becomes too great, there will be a period of time during which the r.f. output is entirely cut off. This is shown in Fig. 10-3. The shape of the downward half of the modulating wave is no longer accurately reproduced by the modulation envelope, consequently the modulation is distorted. Operation of this type is called overmodulation. The distortion of the modulation envelope causes new frequencies (harmonics of the modulating frequency) to be generated. These combine with the carrier to form new side frequencies that widen the channel occupied by the modulated signal. These spurious frequencies are commonly called "splatter."

It is important to realize that the channel occupied by an amplitude-modulated signal is dependent on the shape of the modulation envelope. If this wave shape is complex and can be resolved into a wide band of audio frequencies, then the channel occupied will be correspondingly large. An overmodulated signal splatters and occupies a much wider channel than is necessary because the "clipping" of the modulating wave that occurs at the zero axis changes the envelope wave shape to one that contains high-order harmonics of the original modulating frequency. These harmonics appear as side frequencies separated by, in some cases, many kilocycles from the carrier frequency.

Because of this clipping action at the zero axis, it is important that care be taken to prevent applying too large a modulating signal in the downward direction. Overmodulation downward results in more splatter than is caused by most other types of distortion in a phone transmitter.

GENERAL REQUIREMENTS

For proper operation of an amplitude-modulated transmitter there are a few general requirements that must be met no matter what particular method of modulation may be used. Failure to meet these requirements is accompanied by distortion of the modulation envelope. This in turn increases the channel width as compared with that required by the legitimate frequencies contained in the original modulating wave.

Frequency Stability

For satisfactory amplitude modulation, the carrier frequency must be entirely unaffected by modulation. If the application of modulation causes a change in the carrier frequency, the frequency will wobble back and forth with the modulation. This causes distortion and widens the channel taken by the signal. Thus unnecessary interference is caused to other transmissions.

In practice, this undesirable frequency modulation is prevented by applying the modulation to an r.f. amplifier stage that is isolated from the frequency-controlling oscillator by a buffer amplifier. Amplitude modulation applied directly to an oscillator always is accompanied by frequency modulation. Under existing FCC regulations amplitude modulation of an oscillator is permitted only on frequencies above 144 Mc. Below that frequency the regulations require that

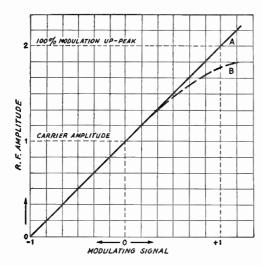


Fig. 10-4—The modulotion chorocteristic shows the relotionship between the instantaneous envelope amplitude of the r.f. output (or voltage) and the instantaneous omplitude of the modulating voltage. The ideal charocteristic is a straight line, as shown by curve A.

an amplitude-modulated transmitter be completely free from frequency modulation.

Linearity

At least up to the limit of 100 per cent upward modulation, the amplitude of the r.f. output should be directly proportional to the amplitude of the modulating wave. Fig. 10-4 is a graph of an ideal modulation characteristic, or curve showing the relationship between r.f. output amplitude and instantaneous modulation amplitude. The modulation swings the r.f. amplitude back and forth along the curve A, as the modulating voltage alternately swings positive and negative. Assuming that the negative peak of the modulating wave is just sufficient to reduce the r.f. output to zero (modulating voltage equal to -1 in the drawing), the same modulating voltage peak in the positive direction (+1) should cause the r.f. amplitude to reach twice its unmodulated value. The ideal is a straight line, as shown by curve A. Such a modulation characteristic is perfectly linear.

A nonlinear characteristic is shown by curve B. The r.f. amplitude does not reach twice the unmodulated carrier amplitude when the modu-

lating voltage reaches its positive peak. A modulation characteristic of this type gives a modulation envelope that is "flattened" on the uppeak; in other words, the modulation envelope is not an exact reproduction of the modulating wave. It is therefore distorted and harmonics are generated, causing the transmitted signal to occupy a wider channel than is necessary. A nonlinear modulation characteristic can easily result when a transmitter is not properly designed or is misadjusted.

The modulation capability of the transmitter is the maximum percentage of modulation that is possible without objectionable distortion from nonlinearity. The maximum capability can never exceed 100 per cent on the down-peak, but it is possible for it to be higher on the up-peak. The modulation capability should be as close to 100 per cent as possible, so that the most effective signal can be transmitted.

Plate Power Supply

The d.c. power supply for the plate or plates of the modulated amplifier should be well filtered; if it is not, plate-supply ripple will modulate the carrier and cause annoying hum. The ripple voltage should not be more than about 1 per cent of the d.c. output voltage.

In amplitude modulation the plate current of the modulated r.f. amplifier varies at an audiofrequency rate; in other words, an alternating current is superimposed on the d.c. plate current. The output filter capacitor in the plate supply must have low reactance, at the lowest audio frequency in the modulation, if the transmitter is to modulate equally well at all audio frequencies. The capacitance required depends on the ratio of d.c. plate current to plate voltage in the modulated amplifier. The requirements will be met satisfactorily if the capacitance of the output capacitor is at least equal to

$$C = 25 \frac{I}{E}$$

where C = Capacitance of output capacitor in μ_f .

I = D.c. plate current of modulated amplifier in milliamperes

E = Plate voltage of modulated amplifier

Example: A modulated amplifier operates at 1250 volts and 275 ma. The capacitance of the output capacitor in the plate-supply filter should be at least

$$C = 25 \frac{I}{E} = 25 \times \frac{275}{1250} = 25 \times 0.22 = 5.5 \text{ uf}.$$

AMPLITUDE MODULATION METHODS

MODULATION SYSTEMS

As explained in the preceding section, amplitude modulation of a carrier is accompanied by an increase in power output, the additional power being the "useful" or "talk power" in the sidebands. This additional power may be supplied from an external source in the form of audio-

frequency power. It is then added to the unmodulated power input to the amplifier to be modulated, after which the combined power is converted to r.f. This is the method used in plate modulation. It has the advantage that the r.f. power is generated at the high efficiency characteristic of Class C amplifiers — of the order of 65 to 75 per cent — but has the accom-

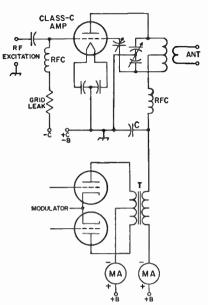


Fig. 10-5—Plate modulation of a Class C r.f. amplifier. The r.f. plate bypass capacitor, C, in the amplifier stage should have reasonably high reactance at audio frequencies. A value of the order of 0.001 μ f. to 0.005 μ f. is satisfactory in practically all cases. (See chapter on modulators.)

panying disadvantage that generating the audiofrequency power is rather expensive.

An alternative that does not require relatively large amounts of audio-frequency power makes use of the fact that the power output of an amplifier can be controlled by varying the potential of a tube element - such as a control grid or a screen grid - that does not, in itself, consume appreciable power. In this case the additional power during modulation is secured by sacrificing carrier power; in other words, a tube is capable of delivering only so much total power within its ratings, and if more must be delivered at full modulation, then less is available for the unmodulated carrier. Systems of this type must of necessity work at rather low efficiency at the unmodulated carrier level. As a practical working rule, the efficiency of the modulated r.f. amplifier is of the order of 30 to 35 per cent, and the unmodulated carrier power output obtainable with such a system is only about one-fourth to one-third that obtainable from the same amplifier with plate modulation.

It is well to appreciate that no simple modulation scheme that purports to get around this limitation of grid modulation ever has actually done so. Methods have been devised that have resulted in modulation at high over-all efficiency, without requiring audio power, by obtaining the necessary additional power from an auxiliary r.f. amplifier. This leads to circuit and operating complexities that make the systems unsuitable for amateur work, where rapid frequency change and simplicity of operation are almost always essential.

The method discussed in this section are the basic ones. Variants that from time to time attain passing popularity can readily be appraised on the basis of the preceding paragraphs. A simple grid modulation system that claims high efficiency should be looked upon with suspicion, since it is almost certain that the high efficiency, if actually achieved, is obtained by sacrificing the linear relationship between modulating signal and modulation envelope that is the first essential of a good modulation method.

PLATE MODULATION

Fig. 10-5 shows the most widely used system of plate modulation, in this case with a triode r.f. tube. A balanced (push-pull Class A, Class AB or Class B) modulator is transformer-coupled to the plate circuit of the modulated r.f. amplifier. The audio-frequency power generated by the modulator is combined with the d.c. power in the modulated-amplifier plate circuit by transfer through the coupling transformer, T. For 100 per cent modulation the audio-frequency power output of the modulator and the turns ratio of the coupling transformer must be such that the voltage at the plate of the modulated amplifier varies between zero and twice the d.c. operating plate voltage, thus causing corresponding variations in the amplitude of the r.f. output.

Audio Power

As stated earlier, the average power output of the modulated stage must increase during modulation. The modulator must be capable of supplying to the modulated r.f. stage sine-wave audio power equal to 50 per cent of the d.c. plate input. For example, if the d.c. plate power input to the r.f. stage is 100 watts, the sine-wave audio power output of the modulator must be 50 watts.

Modulating Impedance; Linearity

The modulating impedance, or load resistance presented to the modulator by the modulated r.f. amplifier, is equal to

$$Z_{
m m}=rac{E_{
m b}}{I_{
m p}} imes 1000~{
m ohms}$$

where $E_b = D.c.$ plate voltage $I_p = D.c.$ plate current (ma.)

 $E_{\rm b}$ and $I_{\rm p}$ are measured without modulation.

The power output of the r.f. amplifier must vary as the square of the instantaneous plate voltage (the r.f. output voltage must be proportional to the plate voltage) for the modulation to be linear. This will be the case when the amplifier operates under Class C conditions. The linearity depends upon having sufficient grid excitation and proper bias, and upon the adjustment of circuit constants to the proper values.

Adjustment of Plate-Modulated Amplifiers

The general operating conditions for Class C operation are described in the chapter on transmitters. The grid bias and grid current required

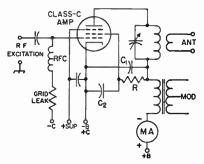


Fig. 10-6—Plate and screen modulation of a Class C r.f. amplifier using a screen-grid tube. The plate r.f. bypass capacitor, C_{1} , should have reasonably high reactance at oll audio frequencies; a value of 0.001 to 0.005 μ f. is generally satisfactory. The screen bypass, C_{2} , should not exceed 0.002 μ f. in the usual case.

When the modulated amplifier is a beam tetrode the suppressor connection shown in this diagram may be ignored. If a base terminal is provided on the tube for the beam-forming plates, it should be connected as recommended by the tube manufacturer.

for plate modulation usually are given in the operating data supplied by the tube manufacturer; in general, the bias should be such as to give an operating angle of about 120 degrees at the d.c. plate voltage used, and the grid excitation should be great enough so that the amplifier's plate efficiency will stay constant when the plate voltage is varied over the range from zero to twice the unmodulated value. For best linearity, the grid bias should be obtained from a fixed-bias source of about the cut-off value, supplemented by enough grid-leak bias to bring the total up to the required operating bias.

The maximum permissible d.c. plate power input for 100 per cent modulation is twice the sine-wave audio-frequency power output available from the modulator. This input is obtained by varying the loading on the amplifier (keeping its tank circuit tuned to resonance) until the product of d.c. plate voltage and plate current is the desired power. The modulating impedance

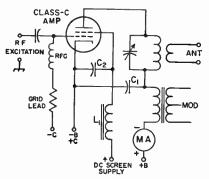


Fig. 10-7—Plate modulation of a beam tetrode, using an audio impedance in the screen circuit. The value of L_1 discussed in the text. See Fig. 10-6 for data on bypass capacitors C_1 and C_2 .

AMPLITUDE MODULATION

under these conditions must be transformed to the proper value for the modulator by using the correct output-transformer turns ratio. This point is considered in detail in the chapter on modulator design.

Neutralization, when triodes are used, should be as nearly perfect as possible, since regeneration may cause nonlinearity. The amplifier also must be completely free from parasitic oscillations.

Although the total power input (d.c. plus audio-frequency a.c.) increases with modulation, the d.c. plate current of a plate-modulated amplifier should not change when the stage is modulated. This is because each increase in plate voltage and plate current is balanced by an equivalent decrease in voltage and current on the next half-cycle of the modulating wave. D.c. instruments cannot follow the a.f. variations, and since the average d.c. plate current and plate voltage of a properly operated amplifier do not change, neither do the meter readings. A change in plate current with modulation indicates nonlinearity. On the other hand, a thermocouple r.f. ammeter connected in the antenna or transmission line will show an increase in r.f. current with modulation, because instruments of this type respond to power rather than to current or voltage.

Screen-Grid Amplifiers

Screen-grid tubes of the pentode or beamtetrode type can be used as Class C plate-modulated amplifiers by applying the modulation to both the plate and screen grid. The usual method of feeding the screen grid with the necessary d.c. and modulation voltages is shown in Fig. 10-6. The dropping resistor, R, should be of the proper value to apply normal d.c. voltage to the screen under steady carrier conditions. Its value can be calculated by taking the difference between plate and screen voltages and dividing it by the rated screen current.

The modulating impedance is found by dividing the d.c. plate voltage by the sum of the plate and screen currents. The plate voltage multiplied by the sum of the two currents gives the power input to be used as the basis for determining the audio power required from the modulator.

Modulation of the screen along with the plate is necessary because the screen voltage has a much greater effect on the plate current than the plate voltage does. The modulation characteristic is nonlinear if the plate alone is modulated. However, some beam tetrodes can be modulated satisfactorily by applying the modulating power to the plate circuit alone, provided the screen is connected to its d.c. supply through an audio impedance. Under these conditions the screen becomes self-modulating, because of the variations in screen current that occur when the plate voltage is varied. The circuit is shown in Fig. 10-7. The choke coil L_1 is the audio impedance in the screen circuit; its inductance should be large enough to have a reactance (at the lowest desired audio frequency) that is not less than the impedance of the screen. The screen impedance can be taken to be approximately equal to the d.c. screen voltage divided by the d.c. screen current in amperes.

Choke-Coupled Modulator

The choke-coupled Class A modulator is shown in Fig. 10-8. Because of the relatively low power output and plate efficiency of a Class A amplifier, this method is seldom used except for a few special applications. There is considerably less freedom in adjustment, since no transformer is available for matching impedances.

The modulating impedance of the r.f. amplifier must be adjusted to the value of load impedance required by the particular modulator tube used, and the power input to the r.f. stage should not exceed twice the rated a.f. power output of the modulator for 100 per cent modulation. The plate voltage on the modulator must be higher than the plate voltage on the r.f. amplifier, for

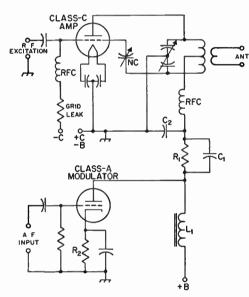


Fig. 10-8—Choke-coupled Class A modulator. The cathode resistor, R₂, should have the normal value for operation of the modulator tube as a Class A power amplifier. The modulation choke, L₁, should be 5 henrys or more. A value of 0.001 to 0.005 μf. is satisfactory at C₂, the r.f. amplifier plate bypass capacitor. See text for discussion of C₁ and R₁.

100 per cent modulation, because the a.f. voltage developed by the modulator cannot swing to zero without a great deal of distortion. R_1 provides the necessary d.c. voltage drop between the modulator and r.f. amplifier. The d.c. voltage drop through R_1 must equal the minimum instantaneous plate voltage on the modulator tube under normal operating conditions. C_1 , an audio-frequency bypass across R_1 , should have a capacitance such that its reactance at 100 cycles is not more than about one-tenth the resistance of R_1 . Without R_1C_1 the percentage of modulation is limited to 70 to 80 per cent in the average case.

GRID MODULATION

The principal disadvantage of plate modulation is that a considerable amount of audio power is necessary. This requirement can be avoided by applying the modulation to a grid element in the modulated amplifier. However, serious disadvantages of grid modulation are the reduction in the carrier power output obtainable from a given r.f. amplifier tube and the more rigorous operating requirements and more complicated adjustment.

The term "grid modulation" as used here applies to all types—control grid, screen, or suppressor—since the operating principles are exactly the same no matter which grid is actually modulated. With grid modulation the plate voltage is constant, and the increase in power output with modulation is obtained by making both the plate current and plate efficiency vary with the modulating signal as shown in Fig. 10-9. For 100 per cent modulation, both plate current and efficiency must, at the peak of the modulation up-swing, be twice their carrier values. Thus at the modulation-envelope peak the power input is doubled, and since the plate efficiency also is doubled at the same instant the peak envelope

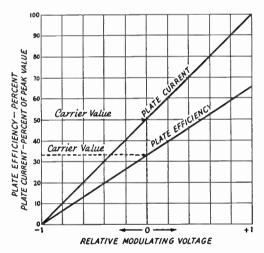


Fig. 10-9—In a perfect grid-modulated amplifier both plate current and plate efficiency would vary with the instantaneous modulating voltage as shown. When this is so the modulation characteristic is as given by curve A in Fig. 10-4, and the peak envelope output power is four times the unmodulated carrier power. The variotions in plate current with modulation, indicated above, do not register on a d.c. meter, so the plote meter shows no change when the signol is modulated.

output power will be four times the carrier power. The efficiency obtainable at the envelope peak depends on how carefully the modulated amplifier is adjusted, and sometimes can be as high as 80 per cent. It is generally less when the amplifier is adjusted for good linearity, and under average conditions a round figure of %, or 66

per cent, is representative. The efficiency without modulation is only half the peak efficiency, or about 33 per cent. This low average efficiency reduces the permissible carrier output to about one-fourth the power obtainable from the same tube in c.w. operation, and to about one-third the carrier output obtainable from the tube with plate modulation.

The modulator is required to furnish only the audio power dissipated in the modulated grid under the operating conditions chosen. A speech amplifier capable of delivering 3 to 10 watts is usually sufficient.

Grid modulation does not give quite as linear a modulation characteristic as plate modulation, even under optimum operating conditions. When misadjusted the nonlinearity may be severe, resulting in bad distortion and splatter.

Plate-Circuit Operating Conditions

The d.c. plate power input to the grid-modulated amplifier, assuming a round figure of \(\frac{1}{3} \) (33) per cent) for the plate efficiency, should not exceed 11/2 times the plate dissipation rating of the tube or tubes used in the modulated stage. Use the maximum plate voltage permitted by the manufacturer's ratings, because the optimum operating conditions are more easily achieved with high plate voltage and the linearity also is improved.

Example: Two tubes having plate dissipation ratings of 55 watts each are to be used with grid

The maximum permissible power input, at 33%

efficiency, is $P=1.5 \times (2 \times 55)=1.5 \times 110=165$ watts The maximum recommended plate voltage for these tubes is 1500 volts. Using this figure, the average plate current for the two tubes will be

$$I = \frac{P}{E} = \frac{165}{1500} = 0.11 \text{ amp.} = 110 \text{ ma.}$$

At 33% efficiency, the carrier output to be expected is 55 watts.

The plate-voltage/plate-current ratio at twice carrier plate current is

$$\frac{1500}{220} = 6.8$$

The tank-circuit L/C ratio should be chosen on the basis of twice the average or carrier plate current. If the L/C ratio is based on the plate voltage/plate current ratio under carrier conditions the Q may be too low for good coupling to the output circuit.

Screen Grid Modulation

Screen modulation is probably the simplest form of grid modulation and the least critical of adjustment. The most satisfactory way to apply the modulating voltage to the screen is through a transformer, as shown in Fig. 10-10. With practical tubes it is necessary to drive the screen somewhat negative with respect to the cathode to get complete cut-off of r.f. output. For this reason the peak modulating voltage required for 100 per cent modulation is usually 10 per cent or so greater than the d.c. screen voltage. The latter, in turn, is approximately half the rated screen voltage recommended by the manufacturer under

AMPLITUDE MODULATION

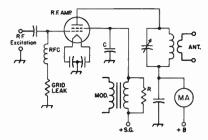


Fig. 10-10—Screen-grid madulation of beam tetrade. Capacitar C is an r.f. bypass capacitar and should have high reactance at audia frequencies. A value af 0.002 μ f, is satisfactory. The grid leak can have the same value that is used far c.w. aperation af the tube.

maximum ratings for radiotelegraph operation.

The audio power required for 100 per cent modulation is approximately one-fourth the d.c. power input to the screen in c.w. operation, but varies somewhat with the operating conditions. A receiving-type audio power amplifier will suffice as the modulator for most transmitting tubes. The relationship between screen voltage and screen current is not linear, which means that the load on the modulator varies over the audiofrequency cycle. It is therefore highly advisable to use negative feedback in the modulator circuit. If excess audio power is available, it is also advisable to load the modulator with a resistance (R in Fig. 10-10) its value being adjusted to dissipate the excess power. There is no simple way to determine the proper resistance except experimentally, by observing its effect on the modulation envelope with the aid of an oscilloscope.

On the assumption that the modulator will be fully loaded by the screen plus the additional load resistor R, the turns ratio required in the coupling transformer may be calculated as follows :

$$N = \frac{E_{\rm d}}{2.5\sqrt{PR_{\rm L}}}$$

where N is the turns ratio, secondary to primary; $E_{\rm d}$ is the rated screen voltage for c.w. operation; P is the rated audio power output of the modulator; and R_L is the rated load resistance for the modulator.

Adjustment

A screen-modulated amplifier should be adjusted with the aid of an oscilloscope connected to give a trapezoid pattern (see later in chapter). A tone source for modulating the transmitter is a convenience, since a steady tone will give a steady pattern on the oscilloscope. A steady pattern is easier to study than one that flickers with voice modulation.

Having determined the permissible carrier plate current as previously described, apply r.f. excitation and d.c. plate and screen voltages. Without modulation, adjust the plate loading to give the required plate current, keeping the plate tank circuit tuned to resonance. Next, apply modulation and increase the modulating voltage until the modulation characteristic shows curvature (see later in this chapter for use of the oscilloscope). If curvature occurs well below 100 per cent modulation, the plate efficiency is too high at the carrier level. Increase the plate loading slightly and readjust the r.f. grid excitation to maintain the same plate current; then apply modulation and check the characteristic again. Continue until the characteristic is as linear as possible from zero to twice the carrier amplitude.

In general, the amplifier should be heavily loaded. Under proper operating conditions the plate-current dip as the amplifier plate circuit is tuned through resonance will be little more than just discernible. Operate with the grid current as low as possible, since this reduces the screen current and thus reduces the amount of power re-

quired from the modulator.

With proper adjustment the linearity is good up to about 90 per cent modulation. When the screen is driven negative for 100 per cent modulation there is a kink in the modulation characteristic at the zero-voltage point. This introduces a small amount of envelope distortion. The kink can be removed and the over-all linearity improved by applying a small amount of modulating voltage to the control grid simultaneously with screen modulation.

In an alternative adjustment method not requiring an oscilloscope the r.f. amplifier is first tuned up for maximum output without modulation and the rated d.c. screen voltage (from a fixed-voltage supply) for c.w. operation applied. Use heavy loading and reduce the grid excitation until the output just starts to fall off, at which point the resonance dip in plate current should be small. Note the plate current and, if possible,

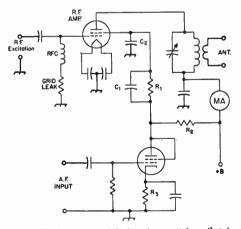


Fig. 10-11—Screen modulation by a "clomp" tube. The grid leak is the normal value for c.w. operation and C_2 should be 0.002 μ f. or less. See text for discussion of C_1 , R_1 , R_2 and R_3 . R_3 should have the proper value for Closs A operation of the modulator tube, but cannot be colculated unless triade curves for the tube are available.

the r.f. output current, and then reduce the d.c. screen voltage until the plate current is one-half its previous value. The r.f. output current should also be one-half its previous value at this screen voltage. The amplifier is then ready for modulation, and the modulating voltage may be increased until the plate current just starts to shift upward, which indicates that the amplifier is modulated 100 per cent. With voice modulation the plate current should remain steady, or show just an occasional small upward kick on intermittent peaks.

"Clamp-Tube" Modulation

A method of screen-grid modulation that is convenient in transmitters provided with a screen protective tube ("clamp" tube) is shown in Fig. 10-11. An audio-frequency signal is applied to the grid of the clamp tube, which then becomes a modulator. The simplicity of the circuit is somewhat deceptive, since it is considerably more difficult from a design standpoint than the transformer-coupled arrangement of Fig. 10-10.

For proper modulation the clamp tube must be operated as a triode Class A amplifier; the method is essentially identical with the choke-coupled Class A plate modulator of Fig. 10-8 except that a resistance, R_2 , is substituted for the choke. R_2 , in the usual case, is the screen dropping resistor normally used for c.w. operation. Its value should be at least two or three times the load resistance required by the Class A modulator tube for optimum audio-frequency output.

Like the choke-coupled modulator, the clamptube modulator is incapable of modulating the r.f. stage 100 per cent unless the dropping resistor, R_1 , and audio bypass, C_1 , are incorporated in the circuit. The same design considerations hold, with the addition of the fact that the screen must be driven negative, not just to zero voltage, for 100 per cent modulation. The modulator tube must thus be operated at a voltage ranging from 20 to 40 per cent higher than the modulated screen.

Adjustment with this system, once the design voltages have been determined, is carried out in the same way as with transformer-coupled screen modulation, preferably with the oscilloscope. Without the oscilloscope, the amplifier may first be adjusted for c.w. operation as described earlier, but with the modulator tube removed from its socket. The modulator is then replaced, and the cathode resistance, R_3 , adjusted to reduce the amplifier plate current to one-half its c.w. value. The amplifier plate current should remain constant with modulation, or show just a small upward flicker on occasional voice peaks.

Controlled Carrier

As explained earlier, a limit is placed on the output obtainable from a grid-modulation system by the low r.f. amplifier plate efficiency (approximately 33 per cent) under unmodulated carrier conditions. The plate efficiency increases with modulation, since the output increases while the d.c. input remains constant, and reaches a maximum obtained to the output increases a maximum or constant, and reaches a maximum of the output increases.

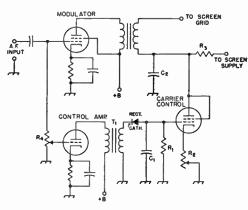


Fig. 10-12—Circuit far carrier cantral with screen madulation. A small triade such as the 6C4 can be used as the cantral amplifier and a 6Y6G is suitable as a carrier-cantral tube. T_1 is an interstage audia transfarmer having a 1-ta-1 ar larger turns ratia. R_4 is a 0.5-megahm valume cantral and alsa serves as the grid resistar far the madulatar. A germanium crystal may be used as the rectifier. Other values are discussed in the text.

mum in the neighborhood of 50 per cent with 100 per cent sine-wave modulation. If the power input to the amplifier can be reduced during periods when there is little or no modulation, thus reducing the plate loss, advantage can be taken of the higher efficiency at full modulation to obtain higher effective output. This can be done by varying the d.c. power input to the modulated stage in accordance with average variations in voice intensity, in such a way as to maintain just sufficient carrier power to keep the modulation high, but not exceeding 100 per cent, under all conditions. Thus the carrier amplitude is controlled by the average voice intensity. Properly utilized, controlled carrier permits increasing the carrier output at maximum level to a value about equal to the rated plate dissipation of the tube. twice the output obtainable with constant carrier.

It is desirable to control the power input just enough so that the plate loss, without modulation, is safely below the tube rating. Excessive control is disadvantageous because the distant receiver's a.v.c. system must continually follow the variations in average signal level. The circuit of Fig. 10-12 permits adjustment of both the maximum and minimum power input, and although somewhat more complicated than some circuits that have been used is actually simpler to operate because it separates the functions of modulation and carrier control. A portion of the audio voltage at the modulator grid is applied to a Class A "control amplifier" which drives a rectifier circuit to produce a d.c. voltage negative with respect to ground. C_1 filters out the audio variations, leaving a d.c. voltage proportional to the average voice level. This voltage is applied to the grid of a "clamp" tube to control the d.c. screen voltage and thus the r.f. carrier level. Maximum output is obtained when the carrier-

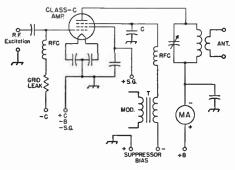


Fig. 10-13—Suppressar-grid madulation of an r.f. amplifier using a pentade-type tube. The suppressar-grid r.f. bypass capacitar, C, shauld be the same as the grid bypass capacitar in cantral-grid madulation.

control tube grid is driven to cut-off, the voice level at which this occurs being determined by the setting of R_4 . The input without modulation is set to the desired level (usually about equal to the plate dissipation rating of the modulated stage) by adjusting R_2 . R_3 may be the normal screen-dropping resistor for the modulated beam tetrode, but in case a separate screen supply is used the resistance need be just large enough to give sufficient voltage drop to reduce the no-modulation power input to the desired value.

 C_1R_1 and C_2R_3 should have a time constant of about 0.1 second. An oscilloscope is required for proper adjustment.

Suppressor Modulation

Pentode-type tubes do not, in general, modulate well when the modulating voltage is applied to the screen grid. However, a satisfactory modulation characteristic can be obtained by applying the modulation to the suppressor grid. The circuit arrangement for suppressor-grid modulation of a pentode tube is shown in Fig. 10-13.

The method of adjustment closely resembles that used with screen-grid modulation. If an oscilloscope is not available, the amplifier is first adjusted for optimum c.w. output with zero bias on the suppressor grid. Sufficient negative bias is then applied to the suppressor to drop the plate current and r.f. output current to half their original values. The amplifier is then ready for modulation.

Since the suppressor is always negatively biased, the modulator is not required to furnish any power and a voltage amplifier can be used. The suppressor bias will vary with the type of pentode and the operating conditions, but usually will be of the order of —100 volts. The peak a.f. voltage required from the modulator is equal to the suppressor bias.

Control-Grid Modulation

Although control-grid modulation may be used with any type of r.f. amplifier tube, it is seldom used with tetrodes and pentodes because screen or suppressor modulation is generally

Types of Modulation

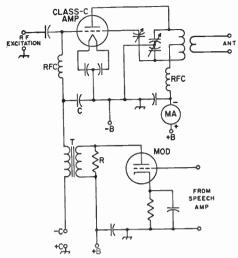


Fig. 10-14—Control-grid modulation of a Class C amplifier. The r.f. grid bypass capacitor, C, should have high reactance at audio frequencies (0.005 μ f. or less).

simpler to adjust. However, control-grid modulation is the only form of grid modulation that is applicable to triode amplifiers. A typical triode circuit is given in Fig. 10-14.

In control-grid modulation the d.c. grid bias is the same as in normal Class C amplifier service, but the r.f. grid excitation is somewhat smaller. The audio voltage superimposed on the d.c. bias changes the instantaneous grid bias at an audio rate, thus varying the operating conditions in the grid circuit and controlling the output and efficiency of the amplifier.

The change in instantaneous bias voltage with modulation causes the rectified grid current of the amplifier to vary, which places a variable load on the modulator. To reduce distortion, resistor R in Fig. 10-14 is connected in the output circuit of the modulator as a constant load, so that the over-all load variations will be minimized. This resistor should be equal to or somewhat higher than the load into which the modulator tube is rated to work at normal audio output. It is also recommended that the modulator circuit incorporate as much negative feedback as possible, as a further aid in reducing the internal resistance of the modulator and thus improving the "regulation"—that is, reducing the effect of load variations on the audio output voltage. The turns ratio of transformer T should be about 1 to 1 in most cases.

The load on the r.f. driving stage also varies with modulation. This in turn will cause the excitation voltage to vary and may cause the modulation characteristic to be nonlinear. To overcome it, the driver should be capable of two or three times the r.f. power output actually required to drive the amplifier. The excess power may be dissipated in a dummy load (such as an incandescent lamp of appropriate power rating) that then performs the same function in the r.f.

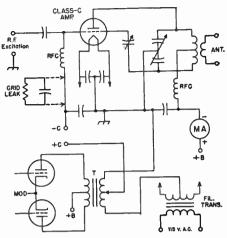


Fig. 10-15-Circuit arrangement for cathade modulation of a Class C r.f. amplifier. Values of bypass capacitors in the r.f. circuits should be the same as for other modulation methods.

circuit that resistor R does in the audio circuit. The d.c. bias source in this system should have low internal resistance. Batteries or a voltageregulated supply are suitable. Grid-leak bias should not be used.

Satisfactory adjustment of a control-grid modulated amplifier requires an oscilloscope. The scope connections are similar to those for screengrid modulation, with audio from the modulator's output transformer secondary applied to the horizontal plates through a blocking capacitor and volume control, and with r.f. from the plate tank circuits coupled to the vertical plates. The adjustment procedure follows that for screen modulation as previously described.

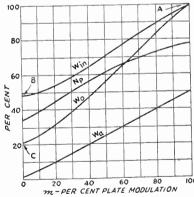


Fig. 10-16—Cathode-modulation performance curves, in terms of percentage of plate modulation plotted against percentage of Class C telephony tube ratings. W_{in}-D.c. plate input watts in terms of percentage of plate-modulation rating.

Wo —Carrier output watts in per cent of plate-modulation rating (based on plate efficiency of 77.5%).

Wa -Audio power in per cent of d.c. watts input.

N_p —Plate efficiency of the amplifier in percentage.

AMPLITUDE MODULATION

CATHODE MODULATION

The fundamental circuit for cathode modulation is shown in Fig. 10-15. It is a combination of the plate and grid methods, and permits a carrier efficiency midway between the two. Audio power is introduced in the cathode circuit, and both grid bias and plate voltage are modulated.

Because part of the modulation is by the control-grid method, the plate efficiency of the modulated amplifier must vary during modulation. The carrier efficiency therefore must be lower than the efficiency at the modulation peak. The required reduction in efficiency depends upon the proportion of grid modulation to plate modulation; the higher the percentage of plate modulation, the higher the permissible carrier efficiency, and vice versa. The audio power required from the modulator also varies with the percentage of plate modulation, being greater as this percentage is increased.

The way in which the various quantities vary is illustrated by the curves of Fig. 10-16. In these curves the performance of the cathode-modulated r.f. amplifier is plotted in terms of the tube ratings for plate-modulated telephony, with the percentage of plate modulation as a base. As the percentage of plate modulation is decreased, it is assumed that the grid modulation is increased to make the over-all modulation reach 100 per cent. The limiting condition, 100 per cent plate modulation and no grid modulation, is at the right (A); pure grid modulation is represented by the left-hand ordinate (B and C).

Modulating Impedance

The modulating impedance of a cathodemodulated amplifier is approximately equal to

$$m\frac{E_b}{I_b}$$

where m =Percentage of plate modulation (expressed as a decimal)

 $E_b = D.c.$ plate voltage on modulated amplifier

I_b = D.c. plate current of modulated amplifier

The modulating impedance is the load into which the modulator must work, just as in the case of pure plate modulation. This load must be matched to the load required by the modulator tubes by proper choice of the turns ratio of the modulation transformer.

Conditions for Linearity

R.f. excitation requirements for the cathodemodulated amplifier are midway between those for plate modulation and control-grid modulation. More excitation is required as the percentage of plate modulation is increased. Grid bias should be considerably beyond cut-off; fixed bias from a supply having good voltage regulation is preferred, especially when the percentage of plate modulation is small and the amplifier is operating more nearly like a grid-bias modulated stage. At the higher percentages of plate modulation a combination of fixed and grid-leak bias can be used, since the variation in rectified grid current is smaller. The grid leak should be bypassed for audio frequencies. The percentage of grid modulation may be regulated by choice of a suitable tap on the modulation-transformer secondary.

The cathode circuit of the modulated stage must be independent of other stages in the transmitter. When directly heated tubes are modulated their filaments must be supplied from a separate transformer. The filament bypass capacitors should not be larger than about $0.002 \, \mu f$, to avoid bypassing the a.f. modulation.

Adjustment of Cathode-Modulated Amplifiers

In most respects, the adjustment procedure is similar to that for grid-bias modulation. The critical adjustments are antenna loading, grid bias, and excitation.

Adjustments should be made with the aid of an oscilloscope connected in the same way as for grid-bias modulation. With proper antenna loading and excitation, the normal wedge-shaped pattern will be obtained at 100 per cent modulation. As in the case of grid-bias modulation, too light antenna loading will cause flattening of the upward peaks of modulation as also will too high excitation. The cathode current will be practically constant with or without modulation when the proper operating conditions have been established.

LINEAR AMPLIFIERS

If a signal is to be amplified after modulation has taken place, the shape of the modulation envelope must be preserved if distortion is to be avoided. This requires the use of a linear amplifier—that is, one that will reproduce, in its output circuit, the exact form of the signal envelope applied to its grid.

The amplitude-modulated driving signal for a linear amplifier can at no time be permitted to swing below cutoff on the modulation downpeaks. To do so would mean that the part of the modulation envelope near the zero axis (see Fig. 10-1C) would be clipped, since there would be times when the instantaneous signal voltage would be below the minimum value that would cause plate-current flow (see Fig. 10-3).

However, the grid bias may be set at any value less than cutoff. Usually, such amplifiers are operated at or near the Class B condition — that is, with the grid bias at or somewhat less than cutoff. Although Class B operation results in considerable distortion of the individual r.f. cycles applied to the grid, the modulation *cnvelope* is not distorted if the operating conditions are chosen properly. The r.f. distortion produces only r.f. harmonics, and these can be eliminated by the selectivity of the output tank circuit.

A linear amplifier used for a.m. has the same

Oscilloscope Patterns

disadvantages with respect to efficiency that grid modulation does. The reason also is much the same: since the amplifier must handle a peak-envelope power four times as great as the unmodulated carrier power, it cannot be operated at its full capabilities when it is amplifying only the unmodulated carrier. The plate efficiency of the amplifier varies with the instantaneous value of the modulation envelope (Fig. 10-9). The efficiency at the unmodulated carrier level is only of the order of 30-35 per cent.

Because of this low efficiency, linear amplifiers have not had much application in amateur transmitters, especially since equivalent efficiency can be obtained with grid modulation, along with a less critical adjustment procedure. Recently there has been some increase in use of a.m. linears, particularly at v.h.f., as a means of stepping up the modulated power output of very low power transmitters with a minimum of complication in over-all equipment and operation. To obtain a useful increase in power output by this means the linear amplifier must use a tube or tubes capable of relatively large plate dissipation, since about two-thirds of the d.c. power input to the amplifier is consumed in heating the plate and only about one-third is converted to useful carrier output.

CHECKING A.M. PHONE OPERATION

USING THE OSCILLOSCOPE

Proper adjustment of a phone transmitter is aided immeasurably by the oscilloscope. The scope will give more information, more accurately, than almost any collection of other instruments that might be named. Furthermore, an oscilloscope that is entirely satisfactory for the purpose is not necessarily an expensive instrument; the cathode-ray tube and its power supply are about all that are needed. Amplifiers and linear sweep circuits are by no means necessary.

In the simplest scope circuit, radio-frequency voltage from the modulated amplifier is applied to the vertical deflection plates of the tube, usually through blocking capacitors as shown in the oscilloscope circuit in the chapter on measurements, and audio-frequency voltage from the modulator is applied to the horizontal deflection plates. As the instantaneous amplitude of the audio signal varies, the r.f. output of the transmitter likewise varies, and this produces a wedge-shaped pattern or trapezoid on the screen. If the oscilloscope has a built-in horizontal sweep, the r.f. voltage can be applied to the vertical plates as before (never through an amplifier) and the sweep will produce a pattern that follows the modulation envelope of the transmitter output, provided the sweep frequency is lower than the modulation frequency. This produces a wave-envelope modulation pattern.

The Wave-Envelope Pattern

The connections for the wave-envelope pattern are shown in Fig. 10-17A. The vertical deflection plates are coupled to the amplifier tank coil (or an antenna coil) through a low-impedance (coax, twisted pair, etc.) line and pick-up coil. As shown in the alternative drawing, a resonant circuit tuned to the operating frequency may be connected to the vertical plates, using link coupling between it and the transmitter. This will eliminate r.f. harmonics, and the tuning control is a means for adjustment of the pattern height.

If it is inconvenient to couple to the final tank coil, as may be the case if the transmitter is tightly shielded, the pick-up loop may be coupled to the tuned tank of a matching circuit or an-

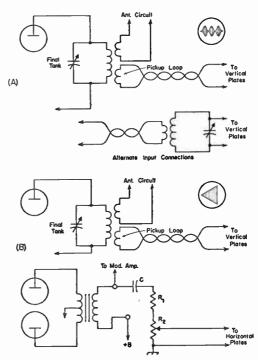


Fig. 10-17—Methods of connecting the oscilloscope for modulation checking. A—connections for wave-envelope pottern with any modulation method; B—connections for trapezoidol pottern with plote or screen modulation.

tenna coupler. Any method (even a short antenna coupled to the tuned circuit shown in the "alternate input connections" of Fig. 10-17A) that will pick up enough r.f. to give a suitable pattern height may be used.

The position of the pick-up coil should be varied until an unmodulated carrier pattern, Fig. 10-18B, of suitable height is obtained. The horizontal sweep voltage should be adjusted to make the width of the pattern somewhat more than half the diameter of the screen. When voice modulation is applied, a rapidly changing pattern of varying height will be obtained. When the

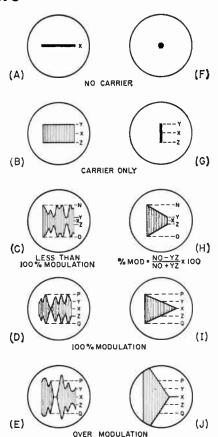


Fig. 10-18—Wave-envelope and trapezoidal patterns representing different conditions of modulation.

maximum height of this pattern is just twice that of the carrier alone, the wave is being modulated 100 per cent. This is illustrated by Fig. 18-18D, where the point X represents the horizontal sweep line (reference line) alone, YZ is the carrier height, and PQ is the maximum height of the modulated wave.

If the height is greater than the distance PQ, as illustrated in E, the wave is overmodulated in the upward direction. Overmodulation in the downward direction is indicated by a gap in the pattern at the reference axis, where a single bright line appears on the screen. Overmodulation in either direction may take place even when the modulation in the other direction is less than 100 per cent.

The Trapezoidal Pattern

Connections for the trapezoid or wedge pattern as used for checking a.m. are shown in Fig. 10-17B. The vertical plates of the c.r. tube are coupled to the transmitter tank through a pick-up loop, preferably using a tuned circuit, as shown in the upper drawing, adjustable to the operating frequency. Audio voltage from the modulator is applied to the horizontal plates through a voltage divider, R_1R_2 . This voltage should be

AMPLITUDE MODULATION

adjustable so a suitable pattern width can be obtained; a 0.25-megohm volume control can be used at R_2 for this purpose.

The resistance required at R_1 will depend on the d.c. voltage on the modulated element. The total resistance of R_1 and R_2 in series should be about 0.25 megohm for each 100 volts. For example, if a plate-modulated amplifier operates at 1500 volts, the total resistance should be 3.75 megohms, 0.25 megohm at R_2 and the remainder, 3.5 megohms, in R_1 . R_1 should be composed of individual resistors not larger than 0.5 megohm each, in which case 1-watt resistors will be satisfactory.

For adequate coupling at 100 cycles the capacitance, in microfarads, of the blocking capacitor, C, should be at least 0.05/R, where R is the total resistance $(R_1 + R_2)$ in megohms. In the example above, where R is 3.75 megohms, the capacitance should be $0.05/3.75 = 0.013 \mu f$, or

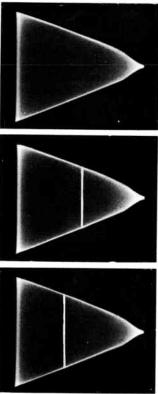


Fig. 10-19—Top—A typical trapezoidal pattern obtained with screen modulation adjusted for optimum conditions. The sudden change in slope near the point of the wedge occurs when the screen voltage passes through zero. Center—If there is no oudio distortion, the unmodulated carrier will have the height and position shown-by the white line superimposed on the sine-wave modulation pattern. Bottom—Even-harmonic distortion in the audio system, when the audio signal applied to the speech amplifier is a sine wave, is indicated by the fact that the modulation pattern does not extend equal horizontal distances on both sides of the unmodulated carrier.

more. The voltage rating of the capacitor should be at least twice the d.c. voltage applied to the modulated element.

Trapezoidal patterns for various conditions of modulation are shown in Fig. 10-18 at F to J, each alongside the corresponding wave-envelope pattern. With no signal, only the cathode-ray spot appears on the screen. When the unmodulated carrier is applied, a vertical line appears; the length of the line should be adjusted, by means of the pick-up coil coupling, to a convenient value. When the carrier is modulated, the wedge-shaped pattern appears; the higher the modulation percentage, the wider and more pointed the wedge becomes. At 100 per cent modulation it just makes a point on the axis, X, at one end, and the height, PQ, at the other end is equal to twice the carrier height, YZ. Overmodulation in the upward direction is indicated by increased height over PQ, and downward by an extension along the axis X at the pointed end.

CHECKING TRANSMITTER PERFORMANCE

The trapezoidal pattern is generally more useful than the wave-envelope pattern for checking the operation of a phone transmitter. However, both types of patterns have their special virtues, and the best test setup is one that makes both available. The trapezoidal pattern is better adapted to showing the performance of a modulated amplifier from the standpoint of inherent linearity, without regard to the wave form of the audio modulating signal, than is the wave-envelope pattern. Distortion in the audio signal also can be detected in the trapezoidal pattern, although experience in analyzing scope patterns is required to recognize it.

If the wave-envelope pattern is used with a

sine-wave audio modulating signal, distortion in the modulation envelope is easily recognizable; however, it is difficult to determine whether the distortion is caused by lack of linearity of the r.f. stage or by a.f. distortion in the modulator. If the trapezoidal pattern shows good linearity in such a case the trouble obviously is in the audio system. It is possible, of course, for both defects to be present simultaneously. If they are, the r.f. amplifier should be made linear first; then any distortion in the modulation envelope will be the result of improper operation in the speech amplifier or modulator, or in coupling the modulator to the modulated r.f. stage.

R. F. Linearity

The trapezoidal pattern is a graph of the modulation characteristic of the modulated amplifier. The sloping sides of the wedge show the r.f. amplitude for every value of instantaneous modulating voltage, exactly the type of curve plotted in Fig. 10-4. If these sides are perfectly straight lines, as drawn in Fig. 10-18 at H and I, the modulation characteristic is linear. If the sides show curvature, the characteristic is nonlinear to an extent shown by the degree to which the sides depart from perfect straightness. This is true regardless of the modulating wave form.

Audio Distortion

If the speech system can be driven by a good audio sine-wave signal instead of a microphone, the trapezoidal pattern also will show the presence of even-harmonic distortion (the most common type, especially when the modulator is overloaded) in the speech amplifier or modulator. If there is no distortion in the audio system, the trapezoid will extend horizontally equal distances on each side of the vertical line representing the

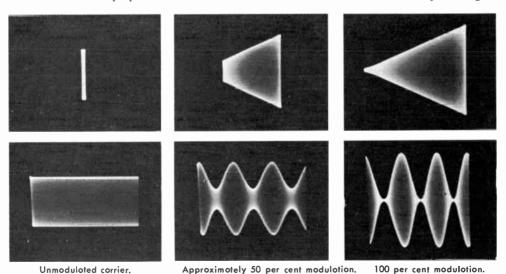


Fig. 10-20—Oscilloscope potterns showing proper modulotion of a plote-ond-screen moduloted tetrode r.f. omplifier. Upper row, tropezoidal patterns; lower row, corresponding wave-envelope potterns. In the lotter a lineor sweep hoving o frequency one-third that of the sine-wave outloo moduloting frequency was used, so that three cycles of the modulotion envelope show in the pottern.

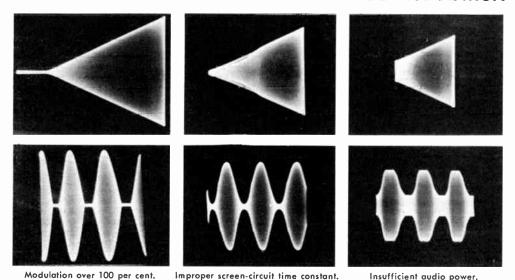


Fig. 10-21—Improper operation or design. These pictures are to the same scale as those in Fig. 20-20, on the same transmitter and with the same test setup.

unmodulated carrier. If there is even-harmonic distortion the trapezoid will extend farther to one side of the unmodulated-carrier position than to the other. This is shown in Fig. 10-19. The probable cause is inadequate power output from the modulator, or incorrect load on the modulator.

An audio oscillator having reasonably good sine-wave output is highly desirable for testing both speech equipment and the phone transmitter as a whole. With an oscillator and the scope, the pattern is steady and can be studied closely to determine the effects of adjustments.

In the case of the wave-envelope pattern, distortion in the audio system will show up in the modulation envelope (with a sine-wave input signal) as a departure from the sine-wave form, and may be checked by comparing the envelope with a drawing of a sine-wave. Attributing any such distortion to the audio system assumes, of course, that a check has been made on the linearity of the modulated r.f. amplifier, preferably by use of the trapezoidal pattern.

Typical Patterns

Figs. 10-19, 10-20 and 10-21 show some typical scope patterns of modulated signals for different conditions of operation. The screen-modulation patterns, Fig. 10-19, also show how the presence of even-harmonic audio distortion can be detected in the trapezoidal pattern. The pattern to be sought in adjusting the transmitter is the one at the top in Fig. 10-20, where the top and bottom edges of the pattern continue in straight lines up to the point representing 100 per cent modulation. If these edges tend to bend over toward the horizontal at the maximum height of the wedge the amplifier is "flattening" on the modulation up-peaks. This is usually caused by attempting to get too large a carrier output, and can be corrected by tighter coupling to the antenna or by a decrease in the d.c. screen voltage.

Fig. 10-20 shows patterns indicating proper operation of a plate-and-screen modulated tetrode r.f. amplifier. The slight "tailing off" at the modulation down peak (point of the wedge) can be minimized by careful adjustment of excitation and plate loading.

Several types of improper operation are shown in Fig. 10-21. In the photos at the left the linearity of the r.f. stage is good but the amplifier is being modulated over 100 per cent. This is shown by the maximum height of the pattern (compare with the unmodulated carrier of Fig. 10-20) and by the bright line extending from the point of the wedge (or between sections of the envelope).

The patterns in the center, Fig. 10-21, show the effect of a too-long time constant in the screen circuit, in an amplifier getting its screen voltage through a dropping resistor, both plate and screen being modulated. The "double-edged" pattern is the result of audio phase shift in the screen circuit combined with varying screen-tocathode resistance during modulation. The overall effect is to delay the rise in output amplitude during the up-sweep of the modulation cycle, slightly distorting the modulation envelope as shown in the wave-envelope pattern. This effect, which becomes more pronounced as the audio modulating frequency is increased, is usually absent at low modulation percentages but develops rapidly as the modulation approaches 100 per cent. It can be reduced by reducing the screen bypass capacitance, and also by connecting resistance (to be determined experimentally, but of the same order as the screen dropping resistance) between screen and cathode.

The right-hand pictures in Fig. 10-21 show the effect of insufficient audio power. Although the trapezoidal pattern shows good linearity in the r.f. amplifier, the wave-envelope pattern shows

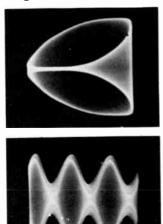


Fig. 10-22—Upper photo—Audio phose shift in coupling circuit between transmitter and harizantal deflection plates. Lower photo—Hum an vertical deflection plates.

flattened peaks (both positive and negative) in the modulation envelope even though the audio signal applied to the amplifier was a sine wave. More speech-amplifier gain merely increases the flattening without increasing the modulation percentage in such a case. The remedy is to use a larger modulator or less input to the modulated r.f. stage. In some cases the trouble may be caused by an incorrect modulation-transformer turns ratio, causing the modulator to be overloaded before its maximum power output capabilities are reached.

Faulty Patterns

The pattern defects shown in Fig. 10-21 are only a few out of many that might be observed in the testing of a phone transmitter, all capable of being interpreted in terms of improper operation in some part of the transmitter. However, it is not always the transmitter that is at fault when the scope shows an unusual pattern. The trouble may be in some defect in the test setup.

Patterns representative of two common faults of this nature are shown in Fig. 10-22. The upper picture shows the trapezoidal pattern when the audio voltage applied to the horizontal plates of the c.r. tube is not exactly in phase with the modulation envelope. The normal straight edges of the wedge are transformed into ellipses which in the case of 100 per cent modulation (shown) touch at the horizontal axis and reach maximum heights equal to the height of the normal wedge at the modulation up-peak. Such a phase shift can occur (and usually will) if the audio voltage applied to the c.r. tube deflection plates is taken from any point in the audio system other than where it is applied to the modulated r.f. stage. The coupling capacitor shown in Fig. 10-17 must have very low reactance compared with the resistance of R_1 and R_2 in series — not larger than

a few per cent of the sum of the two resistances.

The wave-envelope pattern in Fig. 10-22 shows the effect of hum on the vertical deflection plates. This may actually be on the carrier or may be introduced in some way from the a.c. line through stray coupling between the scope and the line or because of poor grounding of the scope, transmitter or modulator.

It is important that r.f. from the *modulated stage only* be coupled to the oscilloscope, and then only to the vertical plates. If r.f. is present also on the horizontal plates, the pattern will lean to one side instead of being upright. If the oscilloscope cannot be moved to a position where the unwanted pick-up disappears, a small bypass capacitor (10 $\mu\mu$ f. or more) should be connected across the horizontal plates as close to the cathode-ray tube as possible. An r.f. choke (2.5 mh. or smaller) may also be connected in series with the ungrounded horizontal plate.

MODULATION CHECKING WITH THE PLATE METER

The plate milliammeter of the modulated amplifier provides a simple and fairly reliable means for checking the performance of a phone transmitter, although it does not give nearly as definite information as the oscilloscope does. If the modulated amplifier is perfectly linear, its plate current will not change when modulation is applied if

1) the upward modulation percentage does not exceed the modulation capability of the amplifier,

2) the downward modulation does not exceed 100 per cent, and

3) there is no change in the d.c. operating voltages on the transmitter.

The plate current should be constant, ideally, with any of the methods of modulation discussed in this chapter, with the single exception of the controlled-carrier system. The plate meter cannot give a reliable check on the performance of the latter system because the plate current increases with the intensity of modulation.

Plate Modulation

With plate modulation, a downward shift in plate current may indicate one or more of the following:

- 1) Insufficient excitation.
- 2) Insufficient grid bias.
- 3) R.f. amplifier not loaded properly.
- Insufficient output capacitance in the filter of the modulated-amplifier plate supply.
- Excessive d.c. input to the r.f. amplifier, under carrier conditions. Alternately, the cathode emission of the amplifier tubes may be low.
- 6) In plate-and-screen modulation of tetrodes or pentodes, the screen is not being sufficiently modulated along with the plate. If the d.c. screen voltage is obtained through a dropping resistor, a dip in plate current may occur if the screen bypass capacitance is large enough to bypass audio frequencies.
- 7) Poor voltage regulation of the modulated-

amplifier plate supply. It is readily checked by measuring the voltage with and without modulation. Poor line regulation will be shown by a drop in filament voltage with modulation.

Any of the following may cause an upward shift in plate current:

- 1) Overmodulation (excessive audio power, audio gain too high).
- Incomplete neutralization of the modulated amplifier.
- Parasitic oscillation in the modulated amplifier.

Grid Modulation

With any type of grid modulation, any of the following may cause a downward shift in modulated-amplifier plate current:

- 1) Too much r.f. excitation.
- Insufficient grid bias with control-grid modulation. Grid bias is usually not critical with screen and suppressor modulation.
- 3) With control-grid modulation, excessive resistance in the bias supply.
- Insufficient output capacitance in platesupply filter.
- 5) Amplifier is not loaded heavily enough.

Because grid modulation is not perfectly linear, (always less so than plate modulation) an amplifier that is properly designed and operated may show a small upward plate-current shift with modulation, 10 per cent or less with sinewave modulation and amounting to an occasional upward flicker with voice. An upward plate current shift in excess of this may be caused by

- 1) Overmodulation (excessive modulating
- 2) Regeneration (incomplete neutralization).
- With control-grid or suppressor modulation, bias too great.
- With screen modulation, d.c. screen voltage too low.
- 5) Audio distortion in modulator.

In grid-modulation systems the modulator is not *necessarily* operating linearly if the plate current stays constant with or without modulation. It is readily possible to arrive at a set of operating conditions in which flattening of the up-peaks is just balanced by overmodulation downward. The oscilloscope provides the only certain check on grid modulation.

COMMON TROUBLES IN THE PHONE TRANSMITTER

Noise and Hum on Carrier

Noise and hum may be detected by listening to the signal on a receiver, provided the receiver is far enough away from the transmitter to avoid overloading. The hum level should be low compared with the voice at 100 per cent modulation. Hum may come either from the speech amplifier and modulator or from the r.f. section of the transmitter. Hum from the r.f. section can be detected by completely shutting off the modulator; if hum remains, the power-supply filters

for one or more of the r.f. stages have insufficient smoothing. With a hum-free carrier, hum introduced by the modulator can be checked by turning on the modulator but leaving the speech amplifier off; power-supply filtering is the likely source of such hum. If carrier and modulator are both clean, connect the speech amplifier and observe the increase in hum level. If the hum disappears with the gain control at minimum, the hum is being introduced in the stage or stages preceding the gain control. The microphone also may pick up hum, a condition that can be checked by removing the microphone from the circuit but leaving the first speech-amplifier grid circuit otherwise unchanged. A good ground (to a cold water pipe, for example) on the microphone and speech system usually is essential to humfree operation.

Spurious Sidebands

A superheterodyne receiver having good selectivity (bandwidth of less than 1 kc.) is needed for checking spurious sidebands outside the normal communication channel. The r.f. input to the receiver must be kept low enough, by removing the antenna or by adequate separation from the transmitter, to avoid overloading and consequent spurious receiver responses. An "S"-meter reading of about half scale is satisfactory. With the selectivity at its sharpest, tune through the region outside the normal channel limits (3 to 4 kilocycles each side of the carrier) while another person talks into the microphone. Spurious sidebands will be observed as intermittent "clicks" or crackles well away from the carrier frequency. Sidebands more than 3 to 4 kc. from the carrier should be of negligible strength, compared with the carrier, in a properly modulated phone transmitter. The causes are overmodulation or nonlinear operation.

With sine-wave modulation the relative intensities of sidebands can be observed if a tone of 1000 cycles or so is used. The "S"-meter will show how the spurious side frequencies (those spaced more than the modulating frequency from the carrier) compare with the carrier itself. Without an "S"-meter, the a.v.c. should be turned off and the b.f.o. turned on; then the r.f. gain should be set to give a moderately strong beat note with the carrier. The intensity of the side frequencies can be estimated from their relative strengths as the receiver is tuned through them.

Receivers having steep-sided band-pass filters for single-sideband reception can be used, but the technique is more difficult. If the band pass is, say, 3 kc., the signal should first be tuned in with the carrier placed at one edge of the pass band. If it is placed at the low edge, for example, the receiver should then be tuned 3 kc. higher so its response will be in the region just outside the normal spectrum space occupied by one sideband. Any "crackles" heard in this region represent the results of nonlinearity of over-modulation. This assumes that the precautions mentioned above with respect to receiver overloading have been carefully observed.

R.F. in Speech Amplifier

A small amount of r.f. current in the speech amplifier — particularly in the first stage, which is most susceptible to such r.f. pickup — will cause overloading and distortion in the low-level stages. Frequently also there is a regenerative effect which causes an audio-frequency oscillation or "howl" to be set up in the audio system. In such cases the gain control cannot be advanced very far before the howl builds up, even though the amplifier may be perfectly stable when the r.f. section of the transmitter is not turned on.

Complete shielding of the microphone, microphone cord, and speech amplifier is necessary to prevent r.f. pickup, and a ground connection separate from that to which the transmitter is connected is advisable.

If the transmitter is "hot" with r.f., the cause usually is to be found in the method of coupling to the antenna. Any form of coupling that involves either a direct or capacitive connection between the transmitter and the transmission line is likely to cause the transmitter chassis to assume an r.f. potential above ground because of "parallel" type currents on the line. An earth connection to the transmitter does not always help in such a case. The best remedy is to use inductive coupling between the transmitter and line

MODULATION MONITORING

It is always desirable to modulate as fully as possible, but 100 per cent modulation should not be exceeded — particularly in the downward direction — because harmonic distortion will be generated and the channel width increased. This causes unnecessary interference to other stations. The oscilloscope is the best instrument for continuously checking the modulation. However, simpler indicators may be used for the purpose, once calibrated.

A convenient indicator, when a Class B modulator is used, is the plate milliammeter in the Class B stage, since the plate current of the modulator fluctuates with the voice intensity. Using the oscilloscope, determine the gain-control setting and voice intensity that give 100 per cent modulation on voice peaks, and simultaneously observe the maximum Class B plate-milliammeter reading on the peaks. When this maximum reading is obtained, it will suffice to adjust the gain so that it is not exceeded.

A high-resistance (1000-ohms-per-volt or more) rectifier-type voltmeter (copper-oxide or germanium type) also can be used for modulation monitoring. It should be connected across the output circuit of an audio driver stage where the power level is a few watts, and similarly calibrated against the oscilloscope to determine the reading that represents 100 per cent modulation.

The plate milliammeter of the modulated r.f. stage also is of value as an indicator of overmodulation, as explained earlier.

A. M. MODULATION MONITOR

The modulation monitor shown in Figs. 10-23 and 10-25 uses two magic-eye tubes and a dual diode. One eye closes whenever the modulation reaches 50 per cent or more, and the second eye closes when the modulation hits 85 per cent or more. In operation, the operator controls his speech to close the "50%" eye much of the time without closing the "85%" eye except on rare occasions. No adjustment of the monitor is required other than the setting of two intensity controls for the ambient light condition. The monitor, with the constants to be described, will work with any plate-modulated amplifier at volt-

ages between 300 and 500; with a slight modification it can be extended to 750 volts.

The circuit diagram is shown in Fig. 10-24. A voltage divider, consisting of R_1 , R_2 plus R_3 , and R_4 , is connected across the plate supply of the modulated stage. The cathodes of two diodes are connected to the modulated voltage applied to the r.f. amplifier, and the anodes of the two diodes are connected through 100K resistors to the junctions on the voltage divider. The voltage divider is proportioned so that the cathode of V_1 is at approximately 50 per cent of the plate supply voltage and the cathode of V_2 is at 15 per cent of the voltage. When the instantaneous voltage is 50 per cent or less of the idling plate voltage, as during the negative portion of a modulation cycle, the upper diode of V_3 will conduct and the voltage drop across the associated 100K resistor will close the eye of V_1 . If during the negative portion of the cycle the instantaneous



Fig. 10-23—An a.m. modulation indicator using two inexpensive magic eye tubes. It is to be connected to the plate supply and modulation transformer of the plate-modulated transmitter stage. The monitor is built in one half of a Minibox and the entire assembly is supported by a cane-metal housing. Heater transformers hang down from the Minibox, inside the housing.

voltage goes as low as 15 per cent of the supply voltage, the lower diode of V_3 will conduct and the drop across the associated 100K resistor will close the eye of V_2 . Capacitors at the grids of V_1 and V_2 make the edges of the closing eyes readily visible.


Type 1629 magic eye tubes are used because they are common tubes in radio surplus stores and are quite inexpensive. Because they have a limited cathode-to-heater voltage rating, it is necessary to use a separate heater transformer with its center tap connected to a midpoint on the voltage divider. For similar insulation reasons, a separate heater transformer is used for the twin diode, V_3 .

Construction

With the exception of the transformers, all components are mounted inside a $5 \times 7 \times 3$ -inch Minibox. A supporting housing for the chassis is made from a small piece of Reynolds No. 33 aluminum mesh, available in many hardware stores. A 3/8-inch lip bent in on the bottom edge provides greater rigidity for the structure and a surface to which four rubber feet can be attached. The monitor is built within one half of the Minibox and the two transformers are mounted on the other side of this half. Two Amphenol 58-MEA8 assemblies are used to support the magic eye tubes; these include the mounting brackets, the sockets and wires, the light shields and the metal escutcheons. The 6H6 socket is supported off the chassis by two 3/4-inch ceramic insulators.

Operation

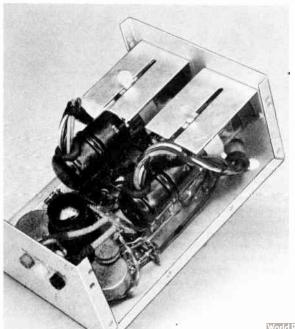When using the monitor with a transmitter, the only adjustment necessary is that of the two 100K intensity controls. The "50%" eye will start to close at about 50 per cent modulation and will be completely closed at around 70 per cent. The "85%" eye will start to close at about



AMPLITUDE MODULATION

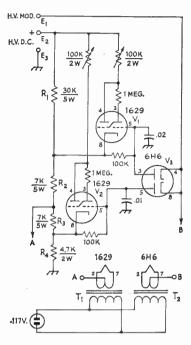


Fig. 10-24—Circuit diagram of the modulatian manitor. Unless specified otherwise, resistars are $\frac{1}{2}$ watt, resistances are in ahms, capacitances are in μf .

C1, C2-Disk ceramic.

E₁, E₂, E₃—Insulated tip jacks (Jahnson 105—601, —602, —603)

 T_1 -12.6-v. 2-a. transformer (Knight 61 G 420) T_2 -6.3-v. 0.6-a. transformer (Knight 61 G 416) 85 per cent and be completely closed at 100 per cent modulation.

Higher Voltages

If the monitor is to be used at supply voltages between 500 and 750, several alterations are required. Either the "50%" eye must be eliminated or a second 12.6-volt transformer must be added (so that each 1629 has its own heater supply). At the higher voltage, additional 47K 2-watt resistors should be connected in series with the intensity controls. The voltage divider R_1 through R_4 must be modified for the higher dissipation.

Fig. 10-25—Madulatian manitar with hausing and case remaved. Tie strips and adequately-insulated wire are required. Cable clamps hold the wires fram the magic-eye sackets, ta avaid strain an the tubes. Transfarmers cannat be seen in this view because they are an the ather side of the assembly. Note ventilation hales at right-hand carner.

World Radio History

Suppressed-Carrier and Single-Sideband Techniques

A fully modulated a.m. signal has two-thirds of its power in the carrier and only one-third in the sidebands. The sidebands carry the intelligence to be transmitted; the carrier "goes along for the ride" and serves only to demodulate the signal at the receiver. By eliminating the carrier and transmitting only the sidebands or just one sideband, the available transmitter power is used to greater advantage. The carrier must be reinserted at the receiver, but this is no great problem, as explained later under "Receiving Suppressed-Carrier Signals."

Assuming that the same final-amplifier tube or tubes are used either for normal a.m. or for single sideband, carrier suppressed, it can be shown that the use of s.s.b. can give an effective gain of up to 9 db. over a.m. — equivalent to increasing the transmitter power 8 times. Eliminating the carrier also eliminates the heterodyne interference that so often spoils communication in congested phone bands.

DOUBLE-SIDEBAND GENERATORS

The carrier can be suppressed or nearly eliminated by an extremely sharp filter or by using a balanced modulator. The basic principle in any balanced modulator is to introduce the carrier in such a way that it does not appear in the output but so that the sidebands will. This requirement is satisfied by introducing the audio in push-pull and the r.f. drive in parallel, and connecting the output in push-pull. Balanced modulators can also be connected with the r.f. drive and audio inputs in push-pull and the output in parallel with equal effectiveness. The choice of a balanced modulator circuit is generally determined by constructional considerations and the method of modulation preferred by the builder. Vacuum-tube balanced modulators can be operated at high power levels and the double-sideband output can be used directly into the antenna. A d.s.b. signal can be copied by the same methods that are used for single-sideband signals, provided the receiver has sufficient selectivity to reject one of the sidebands.

In any balanced-modulator circuit there will be no output with no audio signal. When audio is applied, the balance is upset, and one branch will conduct more than the other. Since any modulation process is the same as "mixing" in receivers, sum and difference frequencies (sidebands) will be generated. The modulator is not balanced for the sidebands, and they will appear in the output.

In the rectifier-type balanced modulators

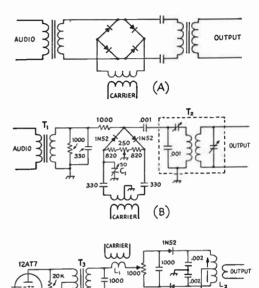


Fig. 11-1—Typical rectifier-type balanced modulators.

The circuit at A is called a "bridge" balanced modulator and has been widely used in commercial work.

(c)

The balanced modulator at B is shown with constants suitable for operation at 450 kc. It is useful for warking into a crystal bandpass filter. T_1 is a transformer designed to work from the audio source into a 600-ohm load, and T_2 is an ordinary i.f. transformer with the trimmer recannected in series with a 0.001- μ f. capacitor, for impedance-matching purposes from the modulator. The capacitor C_1 is for carrier balance and may be found unnecessary in some instances—it should be tried connected on either side of the carrier input circuit and used where it is more effective. The 250-ohm potentiometer is normally all that is required for carrier balance. The carrier input should be sufficient to develop several volts across the resistor string.

The circuit at C is shown with constants suitable for operation at 3.9 Mc. T_3 is a step-down output transformer (Stancor A3250, 10,000 to 200 ohms), shunt-fed to eliminate d.c. from the windings. L_1 can be a small coupling coil wound an the "cold" end of the carrier-oscillator tank coil, with sufficient coupling to give two or three valts of r.f. across its output. L_2 is a slug-tuned coil that resonates to the carrier frequency with the effective 0.001 μ f. across it. The 1000-ohm potentio-

meter is for carrier balance.

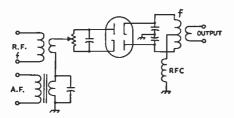


Fig. 11-2—A twin-diode balanced-modulator circuit. This is essentially the same as the circuit in Fig. 11-1C, and differs only in that a twin diode is used instead of dry rectifiers. The heater circuit for the twin diode can be connected in the usual way (one side grounded or center tap grounded).

shown in Fig. 11-1, the diode rectifiers are connected in such a manner that, if they have equal forward resistances, no r.f. can pass from the carrier source to the output circuit via either of the two possible paths. The net effect is that no r.f. energy appears in the output. When audio is applied, it unbalances the circuit by biasing the diode (or diodes) in one path, depending upon the instantaneous polarity of the audio, and hence some r.f. will appear in the output. The r.f. in the output will appear as a double-sideband suppressed-carrier signal. (For a more complete description of diode-modulator operation, see "Diode Modulators," QST, April, 1953, p. 39.)

In any diode modulator, the r.f. voltage should be at least 6 or 8 times the peak audio voltage, for minimum distortion. The usual operation involves a fraction of a volt of audio and several volts of r.f. The diodes should be matched as closely as possible — ohmmeter measurements of their forward resistances is the usual test.

(The circuit of Fig. 11-1B is described more fully in Weaver and Brown, "Crystal Lattice Filters for Transmitting and Receiving," QST, August, 1951. The circuit of Fig. 11-1C is suitable for use in a double-balanced-modulator circuit and is so described in "SSB, Jr.," General Electric Ham News, September, 1950.)

Vacuum-tube diodes can also be used in the two- and four-diode balanced-modulator circuits, and many operators consider them superior to the dry rectifier circuits. A typical balanced modulator circuit using a twin diode (6AL5, 6H6, etc.) is shown in Fig. 11-2. In phasing-type s.s.b. generators (described later) two of these modulators are required, and they are usually worked into a common output circuit. (For a description of a complete s.s.b. exciter using 6AL5 balanced modulators, see Vitale, "Cheap and Easy S.S.B.," QST, March, 1956, and May, 1958.)


Another form of balanced modulator uses the type 7360 "beam-deflection" tube, and it is capable of a high order of carrier suppression (60 db.) with good output (4 volts peak-topeak) and low distortion (45 db.). A typical application is shown in the s.s.b. generators described later in this chapter.

SINGLE-SIDEBAND GENERATORS

Two basic systems for generating s.s.b. signals are shown in Fig. 11-3. One involves the use of a bandpass filter having sufficient selectivity to pass one sideband and reject the other. Filters having such characteristics can only be constructed for relatively low frequencies, and most filters used by amateurs are designed to work somewhere around 500 kc. Good sideband filtering can be done at frequencies as high as 5 Mc. by using multiple-crystal filters. The lowfrequency oscillator output is combined with the audio output of a speech amplifier in a balanced modulator, and only the upper and lower sidebands appear in the output. One of the sidebands is passed by the filter and the other rejected, so that an s.s.b. signal is fed to the mixer. The signal is there mixed with the output of a high-frequency r.f. oscillator to produce the desired output frequency. For additional amplification a linear r.f. amplifier (Class A or Class B) must be used. When the s.s.b. signal is generated around 500 kc. it may be necessary to convert twice to reach the operating frequency, since this simplifies the problem of rejecting the "image" frequencies resulting from the heterodyne process. The problem of image frequencies in the frequency conversions of s.s.b. signals differs from the problem in receivers because the beating-oscillator frequency becomes important. Either balanced modulators or sufficient selectivity must be used to attenuate these frequencies in the output and hence minimize the possibility of unwanted radiations. (Examples of filter-type exciters can be found in QST for June, 1958, and January, 1956.)

The second system is based on the phase relationships between the carrier and sidebands in a modulated signal. As shown in the diagram. the audio signal is split into two components that are identical except for a phase difference of 90 degrees. The output of the r.f. oscillator (which may be at the operating frequency, if desired) is likewise split into two separate components having a 90-degree phase difference. One r.f. and one audio component are combined in each of two separate balanced modulators. The carrier is suppressed in the modulators, and the relative phases of the sidebands are such that one sideband is balanced out and the other is augmented in the combined output. If the output from the balanced modulators is high enough, such an s.s.b. exciter can work directly into the antenna, or the power level can be increased in a following amplifier.

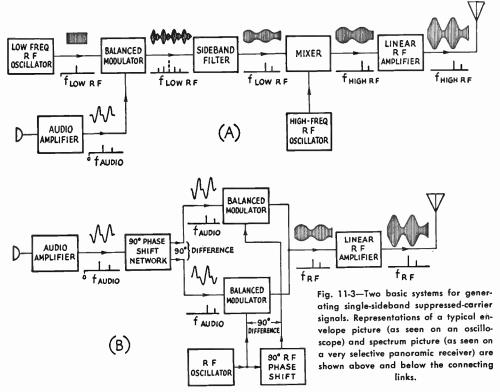Properly adjusted, either system is capable of good results. Arguments in favor of the filter system are that it is somewhat easier to adjust without an oscilloscope, since it requires only a receiver and a v.t.v.m. for alignment, and it is more likely to remain in adjustment over a long period of time. The chief argument against it,



from the amateur viewpoint, is that it requires quite a few stages and at least one frequency conversion after modulation. The phasing system requires fewer stages and can be designed to require no frequency conversion, but its alignment and adjustment are often considered to be a little "trickier" than that of the filter system. This probably stems from lack of familiarity with the system rather than any actual difficulty, and now that commercial preadjusted audio-phasing networks are available,

most of the alignment difficulty has been eliminated. In most cases the phasing system will cost less to apply to an existing transmitter.

Regardless of the method used to generate a s.s.b. signal of 5 or 10 watts, the minimum cost will be found to be higher than for an a.m. transmitter of the same low power. However, as the power level is increased, the s.s.b. transmitter becomes more economical than the a.m. rig, both initially and from an operating standpoint.

FILTER-TYPE S.S.B. EXCITERS

The basic configuration of a filter-type s.s.b. exciter was shown in Fig. 11-3. Suitable filters, sharp enough to reject the unwanted side frequencies a few hundred cycles and above from the carrier frequency, can be built in the range 20 kc. to 10 Mc. The low-frequency filters generally use iron-cored inductors, and the new toroid forms find considerable favor at frequencies up to 50 or 60 kc. These filters are of normal band-pass constant-k and m-derived configuration. In the range 450 to 500 kc., either crystal-lattice or electro-mechanical filters are used. Low-frequency filters are manufactured by Barker & Williamson and by Burnell & Co., and electro-mechanical filters are made by the Collins Radio Co. Crystal filters are available from Hermes Electronics and McCoy Electronics in the megacycles range; homemade filters generally utilize war-surplus crystals. The frequency of the filter determines how many conversions must be made before the operating frequency is reached. If the filter frequency is 30 kc. or so, it is wise to convert first to 500 or 600 kc. and then convert to the 3.9-Mc. band, to avoid the image that would almost surely result if the conversion from 30 to 3900 kc. were made without the intermediate step. When a filter at 500 kc. is used, only one conversion is necessary to operate in the 3.9-Mc. band, but 14-Mc. and higher-frequency operation would require at least two conversions to hold down the images (and local-oscillator signals if balanced mixers aren't used) and make them easy to eliminate.

The choice of converter circuit depends largely on the frequencies involved and the im-

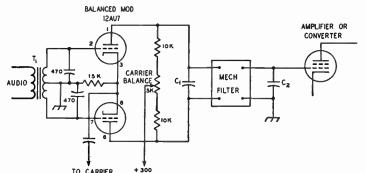


Fig. 11-4—One type of balanced-modulator circuit that can be used with a mechanical filter (Collins F455-31 or F500-31 series) in the i.f. range. The filters are furnished in various types of mountings, and the values of C₁ and C₂ will depend upon the type of filter selected.

T₁-Plate-to-push-pull grids audio transformer.

pedance level. At low frequencies (up to 500 kc.) and low impedances, rectifier-type balanced modulators are often used for mixers, because the balanced modulator does not show the local-oscillator frequency in its output and one source of spurious signal is minimized. At high impedance levels, and at the higher frequencies, vacuum tubes are generally used, in straight converter or balanced-modulator circuits, depending upon the need for minimizing the local-oscillator frequency in the output.

Sideband filters in the 30- to 50-kc. range are usually low-impedance devices, and rectifier-type balanced modulators are common practice. Sideband filters in the i.f. range are higher-impedance circuits and vacuum-tube balanced modulators are the rule in this case. An example of one that can be used with the high-impedance (15,000 ohms) mechanical filter is shown in Fig. 11-4. The filter can be followed by a converter or amplifier tube, depending upon the signal level. Some models of the mechanical filters have a 23-db. insertion loss, while others have only 10.

Crystal-lattice filters are also used to reject the unwanted sideband. These filters can be made from crystals in the i.f. range — many of these are still available from stores selling military surplus. A popular configuration is the "cascaded half lattice" shown in Fig. 11-5. The crystals used in this filter can be obtained at frequencies in the i.f. range, and ones that are within the ranges of the modified i.f. transformers will be satisfactory. Two 100-µµf. capacitors are connected across the secondary winding of two of the transformers to give push-pull output. The crystals should be obtained in pairs 1.8 kc. apart. The i.f. trans-

formers can be either capacitor-tuned as shown, or they can be slug-tuned.

A variable-frequency signal generator of some kind is required for alignment of the filter, but this can be nothing more elaborate than a shielded b.f.o. unit. The signal should be introduced at the balanced modulator, and an output indicator connected to the plate circuit of the vacuum tube following the filter. With the crystals out of the circuit, the transformers can be brought close to frequency by plugging in small capacitors (2 to 5 $\mu\mu$ f.) in one crystal socket in each stage and then tuning the transformers for peak output at one of the two crystal frequencies. The small capacitors can then be removed and the crystals replaced in their sockets.

Tuning the signal source slowly across the pass band of the filter and watching the output indicator will show the selectivity characteristic of the filter. The objective is a fairly flat response for about two kc. and a rapid drop-off outside this range. It will be found that small changes in the tuning of the transformers will change the shape of the selectivity characteristic, so it is wise to make a small adjustment of one trimmer, swing the frequency across the band, and observe the characteristic. After a little experimenting it will be found which way the trimmers must be moved to compensate for the peaks that will rise when the filter is out of adjustment.

The (suppressed) carrier frequency must be adjusted so that it falls properly on the slope of the filter characteristic. If it is too close to the filter mid-frequency the sideband rejection will be poor; if it is too far away there will be a lack of "lows" in the signal.

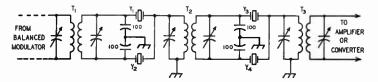


Fig. 11-5—A cascaded half-lattice crystal filter that can be used for sideband selection. The crystals are surplus type of FT-243A holders. Y₁ and Y₃ should be the same frequency and Y₂ and Y₄ should be 1.8 kc. higher. T₁, T₂, T₃—450-kc. i.f. transformers.

A HIGH-FREQUENCY CRYSTAL-FILTER SIDEBAND EXCITER

When a sideband signal is generated at 500 kc. or below, several frequency conversions are usually required to move the signal to the 14-Mc. band without danger of "image" signals. By generating the sideband signal at a high frequency, only one frequency conversion is required. The sideband transmitter shown in Figs. 11-6 through 11-9 is built around a commercial 9-Mc. crystal filter and, with a 6DQ5 in the output stage, it will deliver 50 watts p.e.p. on 75, 40 and 20 meters. The crystal filter is furnished with two matching crystals for the oscillator, so that upper or lower sideband can be obtained by shifting the (suppressed) carrier frequency to one side or the other of the crystal-filter pass band.

To facilitate construction and adjustment, the exciter has none of the "frills" to be found in some commercial equipment, although they can of course be added by the experienced amateur. Plug-in coils and crystal control are used, although there is provision for "pulling" the crystal frequency by means of a "VXO" circuit. Voicecontrolled break-in has been omitted in the interests of simplicity (and perhaps a better type of operation), and the transmitter is turned on or off by a foot switch or key. No operating conveniences have been omitted, however, other than the ability to make sudden large frequency changes. A "Calibrate" position of the mode switch permits accurate setting of one's frequency at a level that does not block the receiver, and in the "standby" condition a bias voltage of -100 is available to be applied to any subsequent amplifier that might generate undesirable diode noise without the additional bias.


Referring to the wiring diagram in Fig. 11-7, the two triode sections of a 6CG7 are used in cascade for the speech amplifier, to bring the voice signal up to the desired level of about 1 volt. This is used to modulate the beam of the 7360 balanced-modulator stage. The 7360 is also used as the (suppressed) carrier oscillator, by raising its cathode above r.f. ground and connecting the carrier-frequency crystal between control grid and ground. Two crystals are furnished with the crystal filter; in this case they have nominal frequencies of 8,998500 and 9.001500 Mc. The 12-µµf. adjustable ceramic capacitors (Centralab 827-B) in shunt with the crystals are used to pull the frequencies into correct relationship to the filter pass band. Since the good linearity of the 7360 is destroyed if the grid is driven positive, a 1N34A diode is used to provide bias in addition to that produced by the cathode resistor. Carrier balance is obtained through adjustment of the relative positive biases (about +20 volts) on the deflection plates, and also through the capacitive balance made possible by the range of C_1 . Upsetting the balance by changing the bias on one deflection plate provides a "calibration" signal or, by changing the unbalance still more by closing S2, sufficient carrier for c.w. operation.

The 9-Mc. crystal filter, FL_1 , is a low-impedance device (560 ohms), and the double-sideband signal appearing in L_1 is coupled to FL_1 through a low-impedance winding. A suitable termination for the filter is obtained by the properly-transformed self impedance of the circuit made up of L_2 and the 47- $\mu\mu$ f. capacitor; since the correct


Fig. 11-6—This single-sideband exciter unit uses a 9-Mc. crystal filter and a choice of oscillator frequencies to obtain the upper or lower sideband. The output tube (right) is a 6DQ5. For simplicity, plug-in coils are used, and two of them are shielded by grocery-store products painted gray (center).

One side has been removed for the photograph; the top plate is "plug on" at the four corners through jacks mounted on the four corners of the top plate.

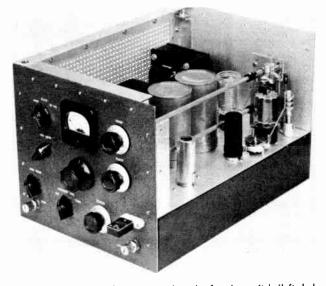The frequency control for the unit is a "VXO," a crystal-controlled oscillator that can be pulled several kc. by a panel control (large knob under meter). The crystal in use is plugged in at the lower right, just



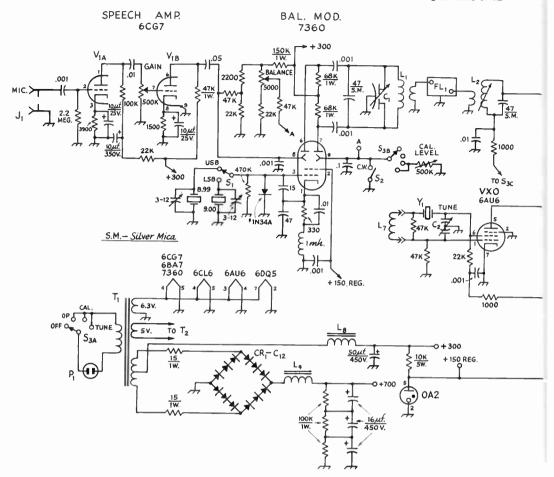above a small CAL control knob that sets the signal level into the receiver when the function switch (left, below VXO control) is on "Calibrate." Small knob at lower left is sideband-selector switch. Switch to left of meter switches meter to grid or cathode of output tube or to r.f. voltmeter on output line; knob just below adjusts sensitivity of r.f. voltmeter.



determination of the coupling is a job for an impedance bridge, it is suggested that the builder use the coil specified for L_2 unless he has facilities for designing his own.

The single-sideband signal from the filter is heterodyned to the operating frequency in a 6BA7 mixer stage operating in the normal maner. The local oscillator (heterodyning) signal is obtained from the 6AU6 VXO* stage in which a variable capacitor is used to pull the crystal frequency lower with an increase in capacitance. Since the value of inductance has some effect on the degree of effectiveness of the pulling, L_{τ} is made plug-in and is changed with (wide) changes in crystal frequencies. If v.f.o. operation is desired, the circuit can be modified to accept a v.f.o. signal by eliminating C_2 , L_7 , Y_1 and the 47,000-ohm resistor across L₇, and moving the 0.001-µf. capacitor to Pin 6. A 100-ohm cathode resistor would be required, and the v.f.o. signal would be introduced between grid and ground.

The output from the 6BA7 mixer is coupled to the 6CL6 driver through one or two tuned cir-

*Shall, "VXO-A Variable Crystal Oscillator," QST, Jan., 1958.

cuits, depending upon the band. On 3.9 and 7.2 Mc. only one tuned circuit is necessary, and a jumper in the plug-in coil form connects the plate lead of L_3 to the pin connected to the 0.001- μ f. coupling capacitor. On 14 Mc., where the 3rd harmonic from the VXO is fairly close in frequency to the desired signal frequency, two tuned circuits are used, connected as shown in Fig. 11-7. The plate circuit of the 6CL6 driver stage is tuned by C_4 , which is ganged to C_3 to facilitate adjustment and to reduce clutter on the front panel.

The output stage is a 6DQ5 operated in Class AB₁. The stage is neutralized to obtain good stability with high gain, and a pi circuit is used to couple to any low-impedance load. Since the loading capacitor, C_8 , does not have sufficient capacitance for correct loading on some bands, the additional capacitance is mounted in the L_8 plug-in form. As a measure of the output, an r.f. voltmeter is connected across the output, deriving its signal from the 10-10- $\mu\mu$ f. capacitance divider.

Metering is provided for in the output stage grid and cathode, and the r.f. voltmeter just mentioned.

In the power supply, an 800-v. c.t. transformer

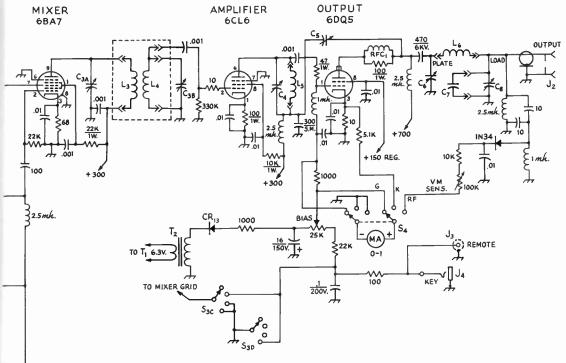


Fig. 11-7—Circuit diagram of the crystal-filter sideband generator. Unless specified otherwise, capacitances are in μμf., decimal capacitances are in μf., resistors are ½ watt, resistances are in ohms. Capacitors marked with polarity are electrolytic.

 C_1 —15- $\mu\mu$ f. differential capacitor (Johnson 160-308).

 C_2 —Dual 50- $\mu\mu$ f. variable (Johnson 167-52).

C₃—Dual 50-μμf. variable (Hammarlund HFD-50). Each section has 30-μμf. mica compression trimmer in parallel.

 C_4 —50- $\mu\mu$ f. miniature variable (Hammarlund APC-50B).

 $C_5-11-\mu\mu f$. variable (Johnson 167-1).

 C_6 —100- $\mu\mu$ f. variable (Hammarlund HFA-100A).

C7-Mounted in L6 form. See coil table.

 C_8 —365- $\mu\mu$ f. midget variable (Allied Radio 61 H 009 or Lafayette Radio MS-261).

CR₁-CR₁₃-400 p.i.v. 500-ma. silicon (Lafayette Radio SP-196).

FL₁—9.0-Mc. crystal filter (McCoy Electronics 32 B1). J₁—Microphone jack (Amphenol 75 PC-1M).

J₂—Coaxial receptacle (SO-239).

J₈—Phono jack.

J₄-Open-circuit phone jack.

provides 700 volts for the output stage, 300 volts for the low-level stages, and regulated 150 volts for the oscillators. Inexpensive silicon rectifiers are used in a combination circuit that provides a basic 700 and 300 volts under load. A small filament transformer, T_2 , is connected to the (otherwise) unused 5-volt winding of the power tranformer, and the resulting 90 volts at the secondary is rectified to furnish the bias voltage for the output stage.

The mode switch, S_3 , turns on the power supply, and places the transmitter in readiness to be controlled at J_4 . In its third position, S_3 unbal-

L₁, L₂—3.1-6.8-μh. variable inductor (Miller M-4405). Coupling coil is 4 t. No. 22 enam. closewound over "cold" end.

L₃-L₇—See coil table, next page.

L₈-5-henry 100-ma. choke (Stancor C-2305).

L_e-2-henry 200-ma. choke (Stancor C-2325).

P₁—Line plug, preferably fused, 1½ amp.

RFC₁—5 t. No. 22 spacewound on 100-ohm 1-watt resistor.

S₁—2-pole 6-position (2 used) rotary switch (Centralab PA-2003).

S2-S.p.s.t. toggle.

S₃—4-pole 5-position (4 used) 2-section rotary switch (Centralab PA-1013).

T₁—800 v.c.t. 200-ma. power transformer with 6.3- and 5-v. filament windings (Knight 61 G 414).

 T_x —6.3-v.0.6-amp. fil. transformer (Knight 61 G 416). Y_1 —See coil table, next page.

ances the balanced modulator but keeps the output stage biased off, for calibration purposes, and in the fourth position it unbalances the modulator and turns on the final, for tune-up purposes.

Construction

The transmitter is built on a $10 \times 14 \times 3$ -inch aluminum chassis, with front and rear panels made of sturdy sheet aluminum 9 inches high. The cane-metal sides are bolted to aluminum angle stock that is bolted to the panels; this can be seen in Figs. 11-6 and 11-8. A lip bent inward

310 SIDEBAND

on the bottom of each side plate of cane metal rests on the chassis; see Fig. 11-8. The top plate of cane metal has a banana jack set in each corner, which engages a corresponding banana plug mounted on the angle stock (see Fig. 11-6).

The placement of most of the major components can be seen in the several photographs. The 7360 beam-deflection modulator tube should be mounted well away from transformers or chokes that might be surrounded by an a.c. field, because the tube is sensitive to these a.c. fields and lowfrequency sidebands can be generated by these stray fields. Aluminum brackets made of scrap sheet material will be required to mount Co and C_8 , C_3 and C_4 , and the tie-point strips supporting CR₁ through CR₁₂. The bracket supporting C₃ has two National TPB feedthrough bushings mounted on the side to shorten the leads between stators and related tube sockets. The neutralizing capacitor, C_5 , must be insulated from the chassis, and another National TPB feedthrough is used from the rotor terminal to the underside of the chassis.

The coil shield cans are made from bakingpowder (Calumet) cans emptied and sprayed on the outside with grey lacquer. A hole is cut in

the cover and the cover is held to the chassis by the same screws that secure the socket. The two black tube shields visible in one of the pictures are ordinary tube shields sprayed with flat black.

Alignment

During the first stages of testing the transmitter, it is suggested that the 10- and 5100-ohm resistors be disconnected from Pin 3 of the 6DO5 socket. This will open the cathode circuit for d.c. and the tube will be inactive in the socket. At the same time, open the lead from L_0 to the rectifiers.

With the tubes in place, and coils and crystals for a band plugged in, the unit should first be tuned as a c.w. transmitter. First checks for output and resonance can be made with S3 in the "calibrate" position, using the 500,000-ohm Calibrate Level control as an excitation control. A useful tool at this point is a pick-up loop and a shielded lead to a receiver (see Fig. 11-14). Checking at L₅ should show r.f. of the desired frequency that is controllable in amplitude by the setting of the Calibrate Level control. With an insulated screwdriver on the padder across C_{84} , adjust the ganged shafts of C3 and C4 and the screwdriver on the padder for maximum output

			•
Band (Mc.)	3.8-4.0	7.2-7.3	14.2-14.35
Crystal Y1	5.2-5.0	16.2-16.3	5.2-5.35
L_3	46 t.*	22 t.**	10 t.**
Shunt	10,000 ohms	10,000 ohms	None
L_4	None	None	10 t.** ½ inch from L ₃
L_{5}	46 t.*	22 t.**	10 t.**
Shunt	4700 ohms	4700 ohms	47,000 ohms
L_6	46 t.**	24 t.**	12 t.***
L_7	72 t.*	20 t.**	Same as 3.8 Mc.
C ₇ (μμf.)	1000	330	_



Fig. 11-8-Another view of the top of the filter sideband exciter. The variable capacitor in the VXO circuit is under the meter; the small box to the right of this capacitor is the crystal filter, and the two matched oscillator crystals supplied with the filter are near the panel. The 7360 beam-deflection modulator is in the black tube shield near the filter; a grommet on the shaft (next to the 7360) of the balance potentiometer serves as a knob.

Tubes in the foreground, from left to right, are 6AU6 VXO, 6BA7 mixer, 6CL6 (black shield) amplifier and 6DQ5 output stage. The long extension shafts behind the tubes control plate tuning and output loading capacitors.

^{*}No. 24, 32 t.p.i., 1-inch diam. (B&W 3016). **No. 20, 16 t.p.i., 1-inch diam. (B&W 3015). ***No. 18, 8 t.p.i., 1-inch diam. (B&W 3014).

Coils are mounted in 1½-inch o.d. polystyrene plug-in coil forms (Allied Radio 24-4P and 24-5P). Shunt resistors are ½-watt except 4700 ohms, which are 1-watt.

A Filter Sideband Exciter

as indicated by the receiver. The object is to set the padder so that its capacitance is equal to the circuit capacitance across L_b , thus enabling the circuits to track. If this alignment is done on 20 meters (preferable), the padder across C_{BB} will also have to be adjusted at the same time.

If S_4 is set to the position for measuring the r.f. output, resonating the output circuit may show a slight amount of r.f. even though the cathode circuit is open. If r.f. is indicated, the stage can be roughly neutralized by setting C_8 for minimum output under these conditions. The receiver, connected at J_2 or coupled to L_8 , is a much more sensitive neutralization indicator, however.

Switching now to "operate", it should be found that there is a setting of the 5000-ohm "balance" control that gives very low output. Test this first with C_1 set at equal capacitances; after finding the minimum setting for the potentiometer try adjusting the capacitor. If the wiring is reasonably symmetrical, it may be found that C_1 has little effect, but this is nothing to worry about. If the tone of the (apparently) suppressed carrier suddenly changes as the potentiometer reaches the null point, it indicates the presence of 60-or 120-cycle residual sidebands, stemming from a.c. at the deflection plates or a magnetic field around the tube.

If the two crystals in the 7360 balanced modulator had exactly the same activity, it might be possible to set their frequencies by adjusting the trimmers across the crystals until, in the testing in the "calibrate" setting of S_8 , exactly the same output was obtained for either setting of S_1 . Since this equal-output condition is not necessarily the case, it becomes necessary to adjust the two trimmers, until, judging by ear, the sideband signal sounds the same for either setting of S_1 (and proper tuning of the receiver). A more sophisticated and accurate approach is to borrow an audio oscillator (if one is lacking) and measure the relative outputs at various audio frequencies for the two settings of S_1 . The output should start to fall off fast below about 400 cycles and above about 3000; the exact figures will be determined by the filter characteristics and by personal preferences of the operator.

When an acceptable sideband signal can be obtained, the transmitter can be turned off long enough to reconnect L₀ and also the resistors in the 6DQ5 cathode circuit. Before turning on the power, a dummy load should be connected at J₃


Fig. 11-9—Underneath the chassis of the sideband exciter. The twelve silicon rectifiers of the power supply are hung between tie points mounted on an aluminum bracket (upper right). The ganged capacitors, C_3 , C_4 that tune the excitation stages are mounted on an aluminum bracket (lower left center); the shaft of C_4 is insulated to keep it above ground potential.

Controls and outlets along the back panel (top) are, left to right: S_2 , output jack, microphone jack, key jack, bias control, remote jack J_3 , and the a.c. line con-

and the 25,000-ohm bias control should be set to give maximum bias (arm closest to capacitor side). Set S_4 to read cathode current (full scale is 200 ma.) and turn on the transmitter. With a key plugged in at J_4 , close the key and turn the bias potentiometer arm until a cathode current of about 30 ma. (reading of 0.15) is obtained. Swinging C_6 around should give no change in cathode current; if the cathode current suddenly kicks up it means the stage is not completely neutralized and needs touching up.

Switching to the "tune" position and using the "calibrate level" control for an excitation control, it should be possible to drive the 6DQ5 into grid current on any of the three bands. With the excitation backed off just below the point of grid current, the output stage should be loaded to draw about 120 ma. cathode current. Switching to "operate" and speaking into the microphone, the gain should be set to where voice peaks kick the cathode current to peaks of 50 ma. (0.25) or so. A much finer adjustment of loading conditions and a better control of speech level before distortion can be obtained by using an oscilloscope to observe the effects of tuning, loading and level.

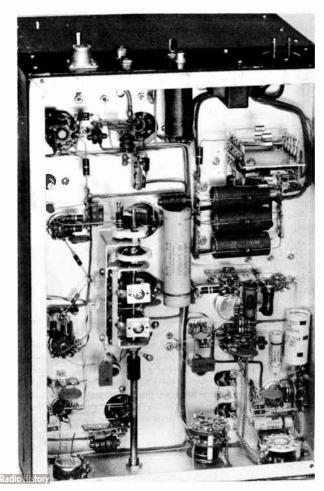No values are given for 10- and 15-meter operation because full output cannot be obtained on these bands without an additional stage of amplification.



312 SIDEBAND

A PHASED SINGLE-SIDEBAND EXCITER

The sideband generator shown in Figs. 11-10 and 11-11 uses the phasing principle outlined earlier (Fig. 11-3B) to produce an upper or lower single-sideband signal. It will also generate a double-sideband signal, with or without carrier. The generator features the new beam-deflection 7360 tube in the balanced modulator portion of the circuit, and it is complete (with power supply) except for the frequency-controlling source. A watt or two of r.f. from a v.f.o. or crystal-controlled oscillator is sufficient for the unit.

Referring to the circuit diagram in Fig. 11-12, a 12AT7 twin triode serves as the speech amplifier. An audio phase-shift network (Barker & Williamson Model 350 2Q4) plugs in the octal socket J2. This preadjusted network has the property of delivering two audio signals differing in phase by 90 degrees ± 1.5 degrees over the range 300 to 3000 cycles. The audio network is protected against low- and high-frequency components outside this range by the couplingcapacitance values and the low-pass filter $C_1C_2L_1L_2$. The two audio signals from the network are equalized by the PHASE control and amplified by V_{2A} and V_{2B} and applied to the deflection plates of the 7360 balanced modulators. The r.f. introduced at J_4 is split and shifted +

and — 45 degrees in the r.f. phase-shift network to give a net difference of 90 degrees.

The output of the balanced modulators is amplified by a Class-A 6CL6, which has sufficient output to drive two or three 6146s in Class AB₁. The tube complement and power supply shown in the circuit diagram are such that the 6CL6 can be overdriven on 75, 40 and 20 meters (but Class-A operation demands that the tube never be driven into grid current). On 15 and 10 meters this reserve gain is lacking, and consequently inductor and phase-shift values for these bands are not given.

For ease of adjustment the grid, screen and plate currents of the 6CL6 can be measured, by proper settings of S₄. Further, the input and output r.f. voltages can be metered, for convenience in setting the excitation and the output tuning.

To simplify the construction and adjustment, plug-in coils and r.f. phase-shift networks are used (Fig. 11-13). The r.f. network is made up of 100-ohm resistors and suitable capacitors (100-ohms reactance at the operating frequency); once adjusted it will hold sufficiently over an amateur band.

The mode switch, S₁, shifts from one sideband output to another by shifting the deflection

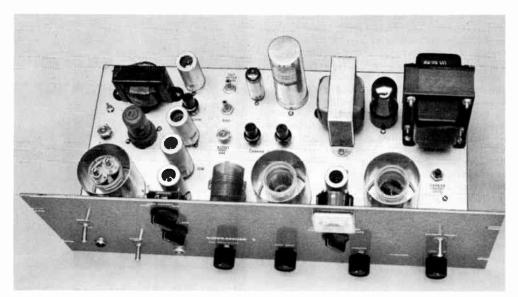


Fig. 11-10—This phasing-type single (and double) sideband generator features the 7360 beam-deflection tube in the balanced-modulator section. The 6CL6 output amplifier (behind meter) delivers sufficient output to drive one or more 6146 amplifier tubes in Class AB₁. Plug-in coils are used to simplify construction.

The r.f. phase-shift network (coil form at extreme left, with two capacitor shafts visible) is plug-in for each band. The audio phase-shift network (B & W Type 2Q4 No. 350) is housed in the tube envelope in front of the audio transformer at rear left. The unshielded tube at rear center is a voltage-regulator tube; two black knobs in front of the VR tube are on the carrier balance controls.

Toggle switches on the panel, left to right, are transmit-receive, power and spotting (carrier insert). Iwo knobs at left, above the microphone jack, turn the mode (lower) and the tune-operate switches. Knob under the meter is on the 5-position meter switch.

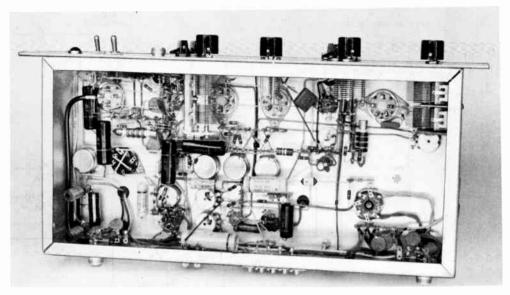


Fig. 11-11—View underneath the chassis of the sideband generator. Tuning capacitors are mounted close under the sockets for the associated plug-in coils. At rear of the chassis (bottom in this view), two terminals are used for bias measurement, and the 4-terminal barrier strip is for making connection to remote control and v.f.o. on-off circuits. Two inductors, part of the low-pass audio filter that protects the audio phase-shift network, are mounted near the r.f. input jack (lower left).

plate to which the audio is applied in one of the balanced modulators. A third position of the switch disables one of the balanced modulators, resulting in double-sideband output from the generator. A spotting switch, S_2 , is used to momentarily unbalance a balanced modulator and allow r.f. to feed through in an amount sufficient to be heard in the receiver. The amount of unbalance is determined by the setting of the SPOT LEVEL resistor. A second circuit of S_2 is available to turn on the external oscillator at the same time. The TUNE-OPERATE switch, S_3 , is used to ground the 6CL6 screen during tune-up procedures.

The power supply includes a bias supply for the 6CL6 amplifier stage. When switch S_{\bullet} is closed, normal operating bias is applied to the 6CL6, but when it is opened the bias will rise to the power-supply level and reduce the 6CL6 plate current to zero. This is useful if the 6CL6 generates "diode noise" on standby that is audible in the receiver. REMOTE connections allow the same bias to be applied to a following amplifier during standby, or they can be used to open and close the circuit normally controlled by S_{\bullet} .

Construction

The physical arrangement of the major components is shown in Figs. 11-10 and 11-11. The generator is built on an 8 × 17 × 3-inch aluminum chassis, with a 7-inch high relay rack panel held to it by the components along the bottom front. Millen 80008 2½-inch diameter aluminum shields are used at the sockets for L₄, L₅ and the r.f. phase-shift network. A minor departure

from convention is the location of the AUDIO GAIN control on the chassis instead of the front panel, but the control is used so soldom that the location is justified.

No special considerations are required in wiring the audio section other than the usual precautions against hum pickup. Before installing L_1 and L_2 they should be set to their correct value of 25 mh. An impedance bridge or Q meter can be used for the purpose, if available. If not, they can be set with an audio oscillator and v.t.v.m. (or oscilloscope). Connect an inductor in parallel with one of the 0.1-\mu f. capacitors, and connect the combination to the audio oscillator output through a high resistance (100K or so). Connect the v.t.v.m. (or 'scope) across the parallel tuned circuit, and adjust the inductor for maximum voltage across the combination when the audio oscillator is set at 3200 cycles. Repeat for the other inductor and capacitor, and do not change the slug settings again. The filter will have a cut-off frequency of 3200 cycles.

R.f. wiring should be made short and direct wherever possible. Input and output are run to jacks J_3 and J_4 in RG-58/U coaxial cable. Try to maintain symmetry of leads in the balanced-modulator portion of the circuit.

Coil and r.f. phase-shift network dimensions are given in the coil table. L_8 is a manufactured product used as is; L_4 and L_6 are made from coil stock and mounted inside the polystyrene plug-in coil forms. The L_6 form also carries padding capacitors for C_7 (these aren't shown in Fig. 11-12). A $39-\mu\mu$ f. padder for C_6 , used only on 75 meters, can be connected to a spare

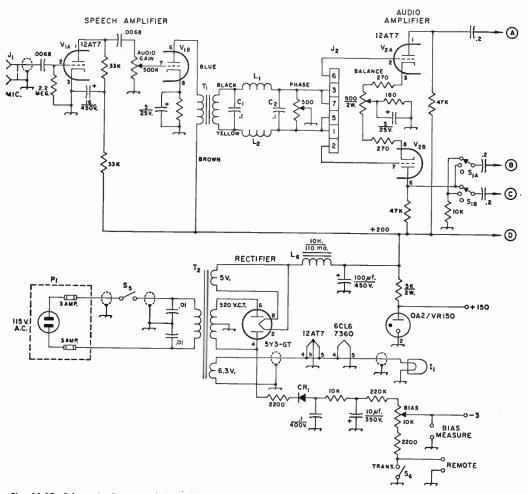


Fig. 11-12—Schematic diagram of the sideband generator. Unless specified otherwise, resistors are ½-watt, .01and .002-µf. capacitors are disk ceramic, 600 volts; .1- and .2-µf. capacitors are tubular paper, 400 volts; capacitors marked with polarities are electrolytic.

 C_1 , C_2 =0.1- μ f. 200-v. paper \pm 10 per cent (Sprague 2TM-P1).

C₈—Dual 100- $\mu\mu$ f. variable (Hammarlund HFD-100).

C₄—15-μμf. variable (Hammarlund MAPC-15).

C₅-100-μμf. variable (Hammarlund APC-100B).

C₆-100-μμf. variable (Hammarlund HFA-100A).

C_τ—Dual 365-μμf. variable, stators in parallel (broadcast replacement type).

C₈, C₁₀—See coil table.

 C_0 , C_{11} —32- $\mu\mu$ f. variable (Johnson 30M8 160-130).

CR₁-360 p.i.v. 200-ma. silicon (Sarkes-Tarzian K-200).

l₁-6.3-v. panel light.

J1-Microphone connector (Amphenol 75-PC1M).

J2-Octal tube socket, for phase-shift network.

pin on the socket for L_6 , with the other capacitor terminal connected to the chassis. A jumper in the 75-meter L_6 will then connect the padder across C_6 .

By cutting a small notch in each side of the coil form, the two trimmer capacitors C_0 and C_{11} can be mounted side by side in the coil form.

J₃, J₄—Coaxial-plug receptacle (SO-239).

L₁, L₂—4—30 mh. slug-tuned coil (Miller 6315) adjusted to 25 mh. See text.

L₃, L₄, L₅—See coil table.

L₆—10-henry 110-ma. filter choke (Knight 62G139).

P₁—Fuse plug.

S₁-3-pole 3-position rotary switch.

S2-D.p.d.t. toggle.

S3-Single-pole 2-position non-shorting rotary switch.

S.—Two-pole 5-position rotary switch, non-shorting.

S₅, S₆-S.p.s.t. toggle.


 T_1 —20,000-to-600 ohms tube-to-line transformer (Thordarson 22S91).

T₂—520 v.c.t. at 90 ma., 5 v., 6.3 v. (Knight 61G412).

Since the rotor terminals of C_0 and C_{11} would normally touch each other when the two capacitors are in place, each terminal must be snipped off close to the ceramic. A piece of tinned wire is then soldered to the remaining portion of the terminal and led across the ceramic and up through the hole that will be farther from the

IN52

OUTPUT

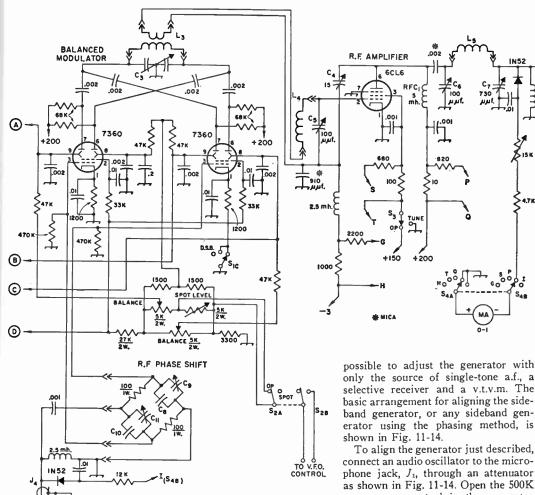

other trimmer capacitor when the two are in place. The connections to C_8 , C_{10} and the two 100-ohm 1-watt (composition, not wirewound) resistors must be made before the wires are snaked through the coil-form pins and soldered. Before soldering to the coil-form pins, the lengths of leads to the stators of C_9 and C_{11} can be measured and soldered. The leads to the rotors from the coil-form pins are long leads that are led up from the pins through the holes in the ceramic end supports. When these long leads have been soldered to the leads from the rotors they will serve to hold C_9 and C_{11} in place. Any surplus length should be snipped off. See Fig. 11-13. When soldering to the pins of the polystyrene coil forms, hold the pin in pliers or a vise, to prevent heat from reaching the polystyrene.

Adjustment

An audio oscillator or other source of lowdistortion single-tone audio is a necessity in the preliminary adjustment of the sideband generator. An oscilloscope is also very useful, but it is

possible to adjust the generator with only the source of single-tone a.f., a selective receiver and a v.t.v.m. The basic arrangement for aligning the sideband generator, or any sideband generator using the phasing method, is

connect an audio oscillator to the microphone jack, J_1 , through an attenuator as shown in Fig. 11-14. Open the 500K AUDIO GAIN control in the generator about half way and apply a 1000-cycle audio tone. Adjust the input level for

approximately 1 volt a.c. at the plates of V_{2A} and V_{2B} , with the 500-ohm balance control set at half resistance. It will be found that the PHASE control will be offset under these conditions; this is perfectly natural since the attenuations through the two channels of the audio phase-shift network are not equal. If a good oscilloscope is available (identical phase shifts through vertical and horizontal amplifiers), the outputs from V_{2A} and V_{2B} should give a circle on the scope face when the vertical and horizontal gains are equalized.

Apply r.f. from the v.f.o. or crystal-controlled oscillator at J_4 , and increase its amplitude until the meter shows full scale with S4 turned full clockwise. A full-scale reading will be close to 10 volts r.m.s. at the No. 3 pins of the 7360 balanced-modulator tubes. With S3 in the TUNE position, and S4 switched to read the grid current of the 6CL6, it should be possible to tune C_3 and C_5 and get an indication of grid current. Turn off the generator by pulling the line plug and temporarily open one side of the 10-ohm



Fig. 11-13—Plug-in coils and r.f. phase-shift networks for the sideband generator. Output tank coils (right) include additional padding capacitor for C₇, as given in the coil table. Polystyrene coil forms are 4-pin (Allied Radio 24-4P) and 5-pin (Allied Radio 24-4P).

resistor in the plate-voltage lead to the 6CL6. The 6CL6 stage can now be neutralized, using for an indicator a receiver connected to the output jack J_a. Use a length of coaxial cable from J_a to the receiver, and install an attenuator network at the receiver antenna terminals, as shown in Fig. 11-14. Adjust the neutralizing capacitor for minimum signal at the receiver, with all circuits resonated, S_a on Tune, and the signal backed off below the grid-current level.

Turn off the power, reconnect the 10-ohm resistor, and connect a dummy load to the output of the sideband generator. Couple the scope and/or receiver to the dummy load or L₈, as shown in Fig. 11-14. When connecting to an oscilloscope, a tuned circuit is required, and the r.f. voltage developed across the tuned circuit is applied directly to the vertical deflection plates. The receiver is connected by coupling loosely through a loop and length of shielded cable; when further attenuation is required it is obtained through the use of resistors at the receiver input terminals.

With the oscillator running, tune the balanced

modulator and 6CL6 circuits for maximum output — this resonates these circuits. Next adjust the 5K BALANCE potentiometers for minimum output. Then introduce a single audio tone of around 1000 cycles at the microphone terminal. Here again it may be necessary to use a resistance voltage divider to hold the signal down and prevent overload. Advance the gain control and look at or listen to the output signal from the 6CL6. It is most likely to be a heavily modulated signal. Try various settings of Co and Cu until the modulation is minimized, and experiment as well with slight touches on the BALANCE and PHASE controls. So should be in the OPERATE positions during these adjustments. With the v.t.v.m. check the r.f. voltages at the No. 3 pins of the 7360s - they should be the same within a few per cent. If not, they can be brought into this condition by readjustment of C_0 and C_{11} , consistent with minimum modulation on the output signal.

The s.s.b. signal with single-tone audio input is a steady unmodulated signal. While it may not be possible to eliminate the modulation en-

Band (meters)	La	L ₄	Ls	C1 pad***	C8 C10***
75	47 t. No. 24, 32 t.p.i., 11/4 diam.; 3 turn link (B & W 80 MCL)	41 turns*	27 turns*	910 μμf.	390 μμf.
40	25 t. No. 22, 16 t.p.i., 1¼ diam.; 3 turn link (B & W 40 MCL)	20 turns*	19 turns*	470 μμf.	200 μμf.
20	13 t. No. 18, 8 t.p.i., 1¼ diam.; 2 turn link (B & W 10 MCL)	17 turns**	16 turns**	270 µµf.	91 μμf.

^{*32} t.p.i. No. 24, 1 inch diam. (B & W 3016 Miniductor).

***Silver mica, ± 5 per cent tolerance.

^{**16} t.p.i. No. 20, 3/4 inch diam. (B & W 3011 Miniductor).

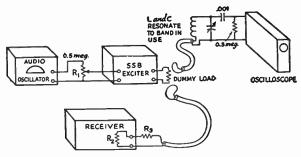


Fig. 11-14—Fundamental arrangement for using an oscilloscope and/or receiver when testing an s.s.b. exciter or transmitter. An audio oscillator is required to furnish the audio signal, and its output is best controlled by the external control R_1 . The audio volume control in the s.s.b. exciter should not be turned on too far, or it should be set at the normal position if you know that position, and all volume controlling should then be done with R_1 and the output attenuator of the audio oscillator. This will reduce the chances of overloading the audio and other amplifier stages in the exciter, a common cause of distortion.

The oscilloscope is coupled to the dummy load through a loop, length of coaxial line, and an L-C circuit tuned to the operating frequency. It is necessary to go directly to the vertical deflection plates of the oscilloscope rather than through the vertical amplifier.

The receiver is coupled to the dummy load through a loop and a length of shielded line. If too much signal is obtained this way, an attenuator, R_2R_3 , can be added to the input terminals of the receiver. Small values of R_3 and large values of R_3 give the most attenuation: in some cases R_2 might be merely a few inches of solid wire.

tirely, it will be possible to get it down to a satisfactorily low level. Conditions that will prevent this are improper r.f. phasing, lack of carrier balance (suppression), distortion in the audio signal (at the source or through overload in the speech amplifier), and lack of audio balance at the 12AT7 audio amplifier. Of these, the r.f. phasing and the audio balance are perhaps the most critical.

A final check on the signal can be made with the receiver in its most selective condition. The spectrum testing described below cannot be done with a broad receiver. Examining the spectrum near the signal, the side signals other than the main one (carrier, unwanted sidebands, and sidebands from audio harmonics) should be at least 30 db. down from the desired signal. This checking can be done with the S-meter

and the a.g.c. on—in the earlier tests the a.g.c. should be off but the r.f. gain reduced low enough to avoid receiver overload.

Examples of the proper and improper scope patterns are shown in Fig. 11-15.

The bias potentiometer for the 6CL6 amplifier should be set initially for a bias of about —3 volts, which should correspond to plate and screen currents of about 30 and 7 ma., respectively. Under maximum-signal conditions, just short of running into grid current, the plate current will kick up slightly. The best indicator of proper modulation level is the output meter.

(For an extensive treatment of the alignment of commercial phasing-type s.s.b. exciters, see Ehrlich, "How to Adjust Phasing-Type S.S.B. Exciters," QST, November, 1956.)

AMPLIFICATION OF S.S.B. SIGNALS

When an s.s.b. signal is generated at some frequency other than the operating frequency, it

is necessary to change frequency by heterodyne methods. These are exactly the same as those

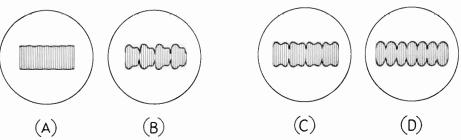


Fig. 11-15—Sketches of the oscilloscope face showing different conditions of adjustment of the exciter unit. (A) shows the substantially clean carrier obtained when all adjustments are at optimum and a sine-wave signal is fed to the audio input. (B) shows improper r.f. phase and unbalance between the outputs of the two balanced modulators. (C) shows improper r.f. phasing but outputs of the two balanced modulators equal. (D) shows proper r.f. phasing but unbalance between outputs of two balanced modulators.

used in receivers, and any of the normal mixer or converter circuits can be used. One exception to this is the case where the heterodyning oscillator frequency is close to the desired output frequency. In this case, a balanced mixer should be used, to eliminate the heterodyning oscillator frequency in the output.

To increase the power level of an s.s.b. signal, a linear amplifier must be used. A linear amplifier is one that operates with low distortion, and the low distortion is obtained by the proper choice of tube and operating conditions. Physically there is little or no difference between a linear amplifier and any other type of r.f. amplifier stage. The circuit diagram of a tetrode r.f. amplifier is shown in Fig. 11-16; it is no different basically than the similar ones in Chapter Six. The practical differences can be found in the supply voltages for the tube and their special requirements. The proper voltages for a number of suitable tubes can be found in Table 11-I; filament-type tubes will require the addition of the filament bypass capacitors C_9 and C_{10} and the completion of the filament circuit by grounding the filament-transformer center tap. The grid bias, E_1 , is furnished through an r.f. choke, although a resistor can be used if the tube is operated in Class AB₁ (no grid current). The screen voltage, E_2 , must be supplied from a "stiff" source (little or no voltage change with current change) which eliminates the use of a dropping resistor from the plate supply unless a voltage-regulator tube is used to stabilize the screen voltage.

Any r.f. amplifier circuit can be adapted to linear operation through the proper choice of operating conditions. For example, the circuit in Fig. 11-16 can be modified by the use of difby the use of another neutralizing scheme, and the resultant amplifier will still be linear if the proper operating conditions are observed. A triode or pentode amplifier circuit will differ in

The simplest form of linear amplifier is the Class A amplifier, which is used almost without exception throughout receivers and low-level speech equipment. (See Chapter Three for an explanation of the classes of amplifier operation.) While its linearity can be made relatively

detail; typical circuits can be found in Chapter

an explanation of the classes of amplifier operation.) While its linearity can be made relatively good, it is inefficient. The theoretical limit of efficiency is 50 per cent, and most practical amplifiers run 25-35 per cent efficient at full output.

At low levels this is not worth worrying about, but when the 2- to 10-watt level is exceeded something else must be done to improve this efficiency and reduce tube, power-supply and operating costs.

Class AB_1 amplifiers make excellent linear amplifiers if suitable tubes are selected. Primary advantages of Class AB_1 amplifiers are that they give much greater output than straight Class A amplifiers using the same tubes, and they do not require any grid driving power (no grid current drawn at any time).

Although triodes can be used for Class AB₁ operation, tetrodes or pentodes are usually to be preferred, since Class AB₁ operation requires high peak plate current without grid current, and this is easier to obtain in tetrodes and pentodes than in most triodes.

To obtain maximum output from tetrodes, pentodes and most triodes, it is necessary to operate them in Class AB_2 . Although this produces maximum peak output, it increases the driving-power requirements and, what is more important, requires that the **driver regulation** (ability to maintain wave form under varying load) be good or excellent. The usual method to improve the driver regulation is to connect a fixed resistor, R_1 , across the grid circuit of the driven stage, to offer a load to the driver that is modified only slightly by the additional load of the tube when

Fig. 11-16—Circuit diagram of a tetrode linear amplifier using link-coupled input tuning and pi network output coupling. The grid, screen and plate voltages (E_1 E_2 and E_3) are given in Table 11-1 for a number of tubes. Although the circuit is shown for an indirectly-heated cathode tube, the only change required when a filament type tube is used is the addition of the filament bypass capacitors C_9 and

 C_{10} . Minimum voltage ratings for the capacitors are given in terms of the power supply voltages.

C₁—Grid tuning capacitor, 3E₁.
C₂—Neutralizing capacitor, 2E₃.


C₃—Grid-circuit bypass capacitor, part of neutralizing circuit, 3E₁.

C4-Plate tuning capacitor, 1.5E3.

C₅—Output loading capacitor. 0.015 spacing for kilowatt peak.

C₆—Plate coupling capacitor, 2E₈.

C₇—Screen bypass capacitor, 2E₂.

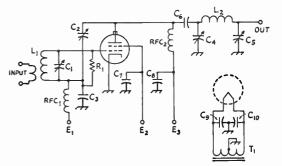

C₈—H.v. bypass capacitor, 2E₃.

C₉, C₁₀—Filament bypass capacitor.

L1-Grid inductor.

L2-Plate inductor.

 R_1 —Grid circuit swamping resistor, required for AB₂. See text.

RFC1-Grid-circuit r.f. choke.

RFC2-Plate r.f. choke.

T₁—Filament transformer.

TABLE 11-I-LINEAR-AMPLIFIER TUBE-OPERATION DATA FOR SINGLE SIDEBAND-GROUNDED-CATHODE CIRCUIT

Unless otherwise noted, rotings are manufacturers' for audio operation. Values given are for one tube. Driving powers represent tube losses only—circuit losses will increase the figures.

Tube	Class	Plate Voltage	Screen Voltage	D.C. Grid Voltage ¹	Zero-Sig, D.C. Plate Current	MaxSig. D.C. Plate Current	Zera-Sig, D.C. Screen Current	MaxSig. D.C. Screen Current	Peak R.F. Grid Voltage	Max,-Sig, D.C. Grid Current	Max,-Sig. Driving Power	Max,-Rated Screen Dissipation	Max,-Rated Grid Dissipation	Avg. Plate Dissipation	Max,-Sig, Useful Power Output
2E26	AB ₁	500	200	- 25	9	45		10	25	0	0	2.5			1.5
6146 6883	AB ₁	600 750	200 195	- 50 - 50	14 12	115 110	.5 .5	14 13	50 50	0	0	3		25 25	47 60
807 1625	AB ₁	600 750	300 300	- 34 - 35	18 15	70 70	.3 .3	8 8	34 35	_	0	3.5 3.5		25 30	28 36
811-A	В	1000 1250 1500	=	0 0 - 4.5	22 27 16	175 175 157	=	=	93 88 85	13	3.8 3.0 2.2	Ξ		65 65 65	124 155 170
4-65A ²	AB ₁	1500 2000 2500 3000	500 500 400 400	- 90 -105 - 85 - 90	30 20 15 15	83 75 66 60		5 3 3 3	70 80 77 77		=	10 10 10 10	=	=	60 85 100 120
PL-177A2	AB ₁	1 500 2000	600 600	-110 -115	30 25	175 175	0	8 7	108 112	0	0	10 10	_ =	110 125	140 210
7094	AB ₁	2000	400	_ 50	30	200		3.5	44	0	42	20			250
	AB ₁	2500	7505	95	25	145		27	90	0	0			l	245
813	AB ₂	2250 2500	750s 750s	- 90 - 95	23 18	1 58 1 80	.8 .6	29 28	115 118		.1	22 22		100 125	258 325
	AB ₁	2000 2500 3000	615 555 510	-105 -100 - 95	40 35 30	135 (100)4 120 (85)4 105 (75)4	=	14 (4.0) ⁴ 10 (3.0) ⁴ 6.0 (1.5) ⁴	105 100 95	0 0 0	0 0 0	20 20 20	=	=	150 180 200
4-125A	AB ₂	1500 2000 2500	350 350 350	- 41 - 45 - 43	44 36 47	200 150 130	0	17 3 3	141 105 89	9 7 6	1.25 .7 .5	20 20 20	5 5 5	125 125 122	175 175 200
7034/ 4X150A	ABı	1000 1500 1800	300 300 300	- 50 - 50 - 50	50 50 50	225 225 225	0 0	11 11 11	50 50 50	0 0	0	12 12 12	=	=	115 200 250
	AB ₁	2500 3000 3500 4000	600 600 555 510	-115 -110 -105 -100	65 55 45 40	230 (170) ⁴ 210 (150) ⁴ 185 (130) ⁴ 165 (115) ⁴	=	15 (3.5)4 12 (2.5)4 9.5 (2.0)4 7.5 (1.5)4	115 110 105 100	0 0 0	0 0 0	35 35 35 35		=	335 400 425 450
4-250A	AB ₂	1500 2000 2500 3000	300 300 300 300	- 48 - 48 - 51 - 53	50 60 60 63	243 255 250 237	0 0 0	17 13 12 17	96 99 100 99	11 12 11 10	1,1 1,2 1,1 1	35 35 35 35 35	10 10 10 10	150 185 205 190	214 325 420 520
30 4 TL	AB ₁	1500 2000 2500 3000	=	-118 -170 -230 -290	135 100 80 65	286 273 242 222	=		118 170 230 290	0 0 0	0 0 0			=	128 245 305 365
PL-175A3	AB ₁	2500 3000 3500	750 750 750	-143 -150 -160	100 80 75	350 350 350	1 1 1	35 29 24	143 150 160	0 0 0	0 0 0	25 25 25	=	265 305 345	570 680 790
PL-172	AB ₁	2000 2500 3000	500 ⁶ 500 ⁶ 500 ⁶	-110 -110 -115	200 220 220	800 800 780	9 9 9	48 43 41	110 110 110	0 0 0	0 0 0	35 35 35	=	<u> </u>	1020 1280 1540
4CX1000A	AB ₁	2000 3000	325 325	- 60 - 60	250 250	1000 900	-2 -2	35 35	60 60	=	0	12 12	0		1020 1680

¹Approximate; adjust to give stated zero-signal plate current.
³Single-sideband suppressed-carrier ratings, voice signal.

860 Mc.
 4Values in parentheses are with two-tone test signal,

⁸0 v. suppressor grid 6十75 v. suppressor grid. SIDEBAND

	TABLE 11-II-CLA	I-CLASS-B LINEAR	-AMPLIFIER TUBE	OPERATION DATA	OR SINGLE SIDEB	SS-B LINEAR-AMPLIFIER TUBE OPERATION DATA FOR SINGLE SIDEBAND—GROUNDED-GRID CIRCUIT	RID CIRCUIT	
Tube	Plate Valtage	D.C. Grid Voltage	Zero-Sig. D.C. Plate Current	MaxSig. D.C. Plate Current	Peak R.F. Grid Voltage	MaxSig. D.C. Grid Current	MaxSig. Driving Power	MaxSig. Useful Power Output
4-125A ¹	2000 2500 3000	000	10 15 20	105 (30) ² 110 (30) ² 115 (30) ²	111	5555	9 1 8 1 8	145 190 240
4-400A1	2000 2500 3000	000	70 80 90	265 (55) ² 270 (55) ² 280 (55) ²		001	38 39 40	325 435 555
3-4002	2000 2500 3000	000	62 73 100	400 (265) ³ 400 (274) ³ 333	111	148 (87) ³ 142 (82) ³ 120	32	4454 5608 655
PL-6569	2500 3500 4000	- 60 ⁶ - 90 ⁶ - 105 ⁶	40 30 24	300 270 250	180 220 205	80 68 42	701 751 601	550 760 800
PL-6580	2500 3500 4000	- 50 - 85 - 100	60 45 40	350 300 300	195 210 230	95 65 65	751 687 727	610 765 910
3-1000Z	3000	00	162 240	800 (550) ³ 670		254 (147) ³ 300	65	10504
¹ Grid and screen connected together. ³ Screen current.	nected together.	[§] Two-tone signal. ⁴ Minimum distorti	[§] Two-tone signal. (Minimum distortion products.	% 8 A M	vinimum distortion produ pproximate, adjust to c cludes bias loss, grid d	*Minimum distortion products at 1 k.w., p.e.p. input. *Approximate; adjust to give stated zero-signal plate current. Includes bias loss, grid dissipation, and feed-through power.	te current. Ih power.	

320

it is driven into the grid-current region. This increases the driver's output-power requirements. Further, it is desirable to make the grid circuit of the Class AB₂ stage a high-C circuit, to improve regulation and simplify coupling to the driver. A "stiff" bias source is also required, since it is important that the bias remain constant, whether or not grid current is drawn.

Class B amplifiers are theoretically capable of 78.5 per cent efficiency at full output, and practical amplifiers run at 60-70 per cent efficiency at full output. Triodes normally designed for Class B audio work can be used in r.f. linear amplifiers and will operate at the same power rating and efficiency provided, of course, that the tube is capable of operation at the radio frequency. The operating conditions for r.f. are substantially the same as for audio work — the only difference is that the input and output transformers are replaced by suitable r.f. tank circuits. Further, in r.f. circuits it is readily possible to operate only one tube if only half the power is wanted - pushpull is not a necessity in Class B r.f. work, However, the r.f. harmonics may be higher in the case of the single-ended amplifier, and this should be taken into consideration if TVI is a problem.

For proper operation of Class AB2 and B amplifiers, and to reduce harmonics and facilitate coupling, the input and output circuits should not have a low C-to-L ratio. A good guide to the proper size of tuning capacitor will be found in Chapter Six; use the voltage-to-current ratio existing under p.e.p. conditions. When zero-bias tubes are used, it may not be necessary to add much "swamping" resistance across the grid circuit, because the grids of the tubes load the circuit at all times. However, in AB2 operation, the swamping resistor should be such that it dissipates from five to ten times the power required by the grids of the tubes, insuring an almost constant load on the driver stage and good regulation of the r.f. grid voltage. In turn this means that at least five to ten times more driving power will be required than is indicated in Table 11-I. Where an excess of driving power is available, it is generally better to increase the loading (decrease the resistance of the swamping resistor) to the point where the maximum available driver power is utilized on peaks.

Before going into detail on the adjustment and loading of the linear amplifier, a few general considerations should be kept in mind. If proper operation is expected, it is essential that the amplifier be so constructed, wired and neutralized that no trace of regeneration or parasitic instability remains. Needless to say, this also applies to the stages ahead of it.

The bias supply to the Class AB_2 or B linear amplifier should be quite stiff, such as batteries or some form of voltage regulator. If nonlinearity is noticed when testing the unit, the bias supply may be checked by means of a large electrolytic capacitor. Simply shunt the supply with $100 \ \mu f$, or so of capacity and see if the linearity improves. If so, rebuild the bias supply for better regula-

Amplification of S.S.B. Signals

tion. Do not rely alone on using a large capacitor.

Where tetrodes or pentodes are used, the screen supply should have good regulation and its voltage should remain constant under the varying current demands. If the maximum screen current does not exceed 30 or 35 ma., a string of VR tubes in series can be used to regulate the screen voltage. If the current demand is higher, it may be necessary to use an electronically regulated power supply or a heavily bled power supply with a current capacity of several times the current demand of the screen circuit.

Where VR tubes are used to regulate the screen supply, they should be selected to give a regulated voltage as close as possible to the tube's rated voltage, but it does not have to be exact. Minor differences in idling plate current can be made up by readjusting the grid bias.

The plate voltage applied to the linear amplifier should be held as constant as possible under the varying current-demand conditions. This condition can be met by using low-resistance transformers and inductors and by using a large value of output capacitor in the power-supply filter. An output capacitor value three or four times the minimum required for normal filtering (Chapter Seven) is reasonable. Although some slight improvement can be obtained by using still higher values of capacitance, the problem of turning on the supply without blowing fuses (on the initial surge) starts to become significant.

One should bear in mind that the same amplifier can be operated in several classes of operation by merely changing the operating conditions (bias, loading, drive, screen voltage, etc.). However, when the power sensitivity of an amplifier is increased, as by changing the operation from Class AB₂ to Class AB₃, the stability requirements for the amplifier become stringent.

From the standpoint of ease of adjustment and availability of proper operating voltages, a linear amplifier with Class AB₁ tetrodes or pentodes or one with zero-bias Class B triodes would be first choice. The Class B amplifier would require more driving power. (For examples of Class AB₁ tetrode amplifiers, see Russ, "The 'Little Firecracker' Linear Amplifier," QST, Sept., 1953; Eckhardt, "The Single Side-Saddle Linear," QST, Nov., 1953; Wolfe and Romander, "A 4X-250B Linear," QST, Nov., 1956; Muir, "Grounded-Grid Tetrode Kilowatt," QST, April, 1957; and Rinaudo, "Compact AB₁ Kilowatt," QST, Nov., 1957.)

Tables 11-I and 11-II list a few of the more

popular tubes commonly used for s.s.b. linear-amplifier operation. Except where otherwise noted, these ratings are those given by the manufacturer for audio work and as such are based on a sine-wave signal. These ratings are adequate ones for use in s.s.b. amplifier design, but they are conservative for such work and hence do not necessarily represent the maximum powers that can be obtained from the tubes in voice-signal s.s.b. service. In no case should the average plate dissipation be exceeded for any considerable length of time, but the nature of a s.s.b. signal is such that the average plate dissipation of the tube will run well below the peak plate dissipation.

Getting the most out of a linear amplifier is done by increasing the peak power without exceeding the average plate dissipation over any appreciable length of time. This can be done by raising the plate voltage or the peak current (or both), provided the tube can withstand the increase. However, the manufacturers have not released any data on such operation, and any extrapolation of the audio ratings is at the risk of the amateur. A 35- to 50-per cent increase above plate-voltage ratings should be perfectly safe in most cases. In a tetrode or pentode, the peak plate current can be boosted some by raising the screen voltage.

When running a linear amplifier at considerably higher than the audio ratings, the "two-tone test signal" (described later) should never be applied at full amplitude for more than a few seconds at any one time. The above statements about working tubes above ratings apply only when a voice signal is used — a prolonged whistle or two-tone test signal may damage the tube. (For a method of adjusting amplifiers safely at high input, see Goodman, "Linear Amplifiers and Power Ratings," QST, August, 1957.)

Linear amplifiers are rated in "p.e.p. input" or "p.e.p. output." The "p.e.p." stands for peak envelope power. P.e.p. input is not indicated by the maximum reading the plate milliammeter kicks to (see "Adjustment of Amplifiers" below); it is the input that would be indicated by the plate milliammeter and voltmeter if the amplifier were driven continuously by a single r.f. signal of the peak amplitude the amplifier can handle within its allowable distortion limits. The p.e.p. output is the r.f. output under these same conditions. As implied in the preceding paragraph, it may be impossible to measure the p.e.p. input or output directly without injuring the tube or tubes.

GROUNDED-GRID AMPLIFIERS WITH FILAMENT-TYPE TUBES

It is not necessary to use indirectly heated cathode type tubes in grounded-grid circuits, and filament-type tubes can be used just as effectively. However, it is necessary to raise the filament above r.f. ground, and one way is shown in Fig. 11-17. Here filament chokes are used between the filament transformers and the tube

socket. The inductance of the r.f. chokes does not have to be very high, and 5 to $10 \mu h$, will usually suffice from 80 meters on down. The current-carrying capacities of the r.f. chokes must be adequate for the tube or tubes in use, and if the resistance of the chokes is too high the filament voltage at the tube socket may be too low and the

tube life will be endangered. In such a case, a higher-voltage filament transformer can be used, with its primary voltage cut down until the voltage at the tube socket is within the proper limits.

Filament chokes can be wound on ceramic or wooden forms, using a wire size large enough to carry the filament current without undue heating. Large cylindrical ceramic antenna insulators can be used for the forms. If enameled wire is used, it should be spaced from half the diameter to the diameter of the wire; heavy string can be used for this purpose. The separate chokes indicated in Fig. 11-17 are not essential; the two windings can be wound in parallel. In this case it is not necessary to space all windings; the two parallel wires can be treated as one wire, winding them together with a single piece of string to space the turns. Enameled wire can be used because the enamel is sufficient insulation to handle the filament voltage.

When considerable power is available for driving the grounded-grid stage, the matching between driver stage and the amplifier is not too important. However, when the driving power is marginal or when the driver and amplifier are to be connected by a long length of coaxial cable, a pi network matching circuit can be used in the input of the grounded-grid amplifier. The input impedance of a grounded-grid amplifier is in the range of 100 to 400 ohms, depending upon the tube or tubes and their operating conditions.

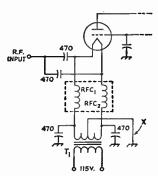


Fig. 11-17—When filament-type tubes are used in a grounded-grid circuit, it is necessary to use filament chokes to keep the filament above r.f. ground. In the portion of a typical circuit shown here, the filament chokes. RFC1 and RFC2, can be a manufactured unit (e.g., B&W FC15 and FC30) or homemade as described in the text. Total plate and grid current can be read on a milliammeter inserted at x.

When data for grounded-grid operation is available (see Table 11-II), the input impedance can be computed from

$$Z_{in} = \frac{(peak \ r.f. \ driving \ voltage)^2}{2 \times driving \ power}$$

From this and the equations for a pi network, a suitable network can be devised.

ADJUSTMENT OF AMPLIFIERS

One of the more important features of the linear amplifier is that the ordinary plate and grid meters are at best only a poor indicator of what is going on. As the meters bounce back and forth, even a person who is thoroughly familiar with this kind of amplifier would be hard put to sense whether the input power registered is attributable to (a) overdrive and underload, which yield distortion, splatter, TVI, etc., or (b) underdrive and too-heavy loading, resulting in inefficiency and loss of output.

The simplest and best way to get the whole story is to make a linearity test; that is, to send through the amplifier a signal whose amplitude varies from zero up to the peak level in a certain known manner and then observe, by means of an oscilloscope, whether this same waveform comes out of the amplifier at maximum ratings.

Test Equipment

Even the simplest type of cathode-ray oscilloscope can be used for linearity tests, so long as it has the regular internal sweep circuit. If this instrument is not already part of the regular station equipment, it might be well to purchase one of the several inexpensive kits now on the market, so that it will be on hand not only to make initial tests but also as a permanent monitor during all operation. Barring a purchase, it is recommended at least that a scope be borrowed to make the line-up checks, whereupon the regular

plate and grid meters can serve thereafter to indicate roughly changes in operating conditions.

All linearity tests require that the vertical plates of the scope be supplied with r.f. from the amplifier output. To avoid interaction within the instrument, it is usually best to connect directly to the cathode-ray tube terminals at the back of the cabinet. A pick-up device and its connections to the oscilloscope are shown in Fig. 11-14. Normally, the pick-up loop should be coupled to the dummy load, antenna tuner, or transmission line; i.e., to a point in the system beyond where any tuning adjustments are to be made.

The only other piece of test equipment will be an audio oscillator. Since only one frequency

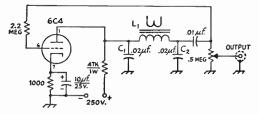


Fig. 11-18—Fixed-frequency audio oscillator having good output waveform. The frequency can be varied by changing the values of C₁ and C₂.

 L_1 —Small speaker output transformer, secondary not used.

Adjustment of Amplifiers

is needed, the simple circuit of Fig. 11-18 works quite well. Some equipment has a circuit similar to this one built right into the exciter audio system.

Two-Tone Test

The two-tone test involves sending through the amplifier or the system a pair of r.f. signals of equal amplitude and a thousand cycles or so apart in frequency. The combined envelope of two such signals looks like two sine waves folded on one another. If this waveform comes out of the final, well and good; if not, there is work to do.

There are two commonly used ways to generate the two-tone signal, and the choice of which to use depends on the particular type of exciter available.

Method A — for Filter or Phasing Exciters:

- 1) Turn up the carrier insertion until a carrier is obtained at about half the expected output amplitude.
- 2) Connect an audio oscillator to the microphone input and advance audio gain until (when the carrier and the one sideband are equal) the scope pattern takes on the appearance of full modulation; i.e., the cusps just meet at the center line. See Fig. 11-19, photo No. 1.
- 3) To change the drive through the system, increase or decrease the carrier and audio settings together, maintaining equality of the two signals.


Method B — for Phasing Exciters:

- 1) Disable the audio input to *one* balanced modulator, by removing a tube or by temporarily short-circuiting an audio transformer.
- 2) Connect the audio oscillator and advance audio gain to get the desired drive. Note that with one balanced modulator cut out, the resultant signal will be double-sideband with no carrier, hence two equal r.f. signals.


Double-Trapezoid Test

When Method B can be used with phasing exciters, it is possible to derive a somewhat more informative pattern by making a connection from the exciter audio system to the horizontal signal input of the oscilloscope and using this audio signal, instead of the regular internal sweep, to cause the horizontal deflection. Those who are familiar with the regular trapezoid test for a.m. transmitters will recognize this set-up as being the same, except that instead of one trapezoid, this test produces two triangles pointing toward each other.


Each individual triangle is subject to the same analysis as the regular trapezoid pattern; i.e., the sloping sides of the pattern should be straight lines for proper operation. Since it is much easier to tell whether a line is straight or not than to judge the correctness of a sine curve, the double trapezoid has the advantage of being somewhat more positive and sensitive to slight departures from linearity than is the regular two-tone pattern.

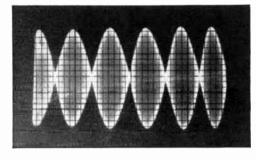

(1)

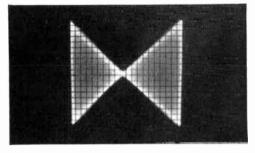

(2)

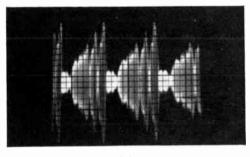

(3)

Fig. 11-19—Correct Potterns. 1—Desired two-tone test pattern. 2—Desired double-trapezoid test pattern. 3—Typical voice pattern in a correctly adjusted amplifier, scope set for 30-cycle sweep. Note that peaks are clean and sharp.

If the audio can be picked off at the plate of the audio modulator tube that is still working, the input signal need not be a pure sine wave; merely whistling or talking into the microphone should produce the appropriate pattern. If, because of the exciter layout, it is necessary to pick up the audio signal ahead of the phase-shift network, it will then be necessary to use a good sine-wave audio oscillator as before. Also, with the latter set-up, the pattern will probably have a loopy appearance at first, and phase correction will be needed to make the figure close up. This can be done either by varying the audio frequency or by putting a phaser in series with the horizontal input to the scope, as shown in Fig. 11-20.

324 SIDEBAND

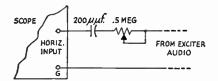


Fig. 11-20—"Phaser" circuit for the oscilloscope.

Ratings

Before proceeding with linearity tests, it is well to have in mind the current and power levels to expect. A suppressed-carrier signal is exactly like an audio signal, except for its frequency, so the audio ratings for any tube are

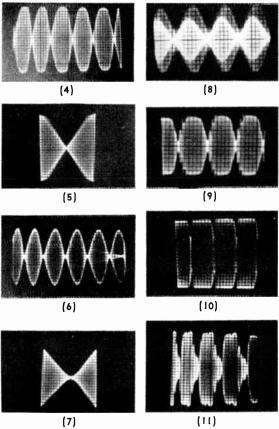


Fig. 11-22—Improper Amplifier Operation. 4—Overdrive, indicated by flattening of peaks. 5—Same as 4, double-trapezoid test. 6—Too much bias, causing crossover to become pinched together rather than cutting straight across center line. 7—Same as 6, double-trapezoid test. 8—Two-tone test with v.h.f. parasitics. Note fuzzy halo or fringe. In milder cases the fuzziness will appear just at the peaks. 9—Two-tone test with fundamental frequency parasitics, accompanied by overdrive. 10—Severe overdrive and parasitics. 11—Voice pattern showing flattening of peaks due to overdrive. When flattening is apparent on the voice pattern, the case is a severe one.

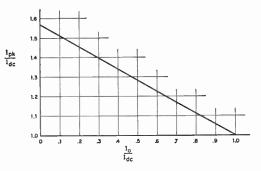


Fig. 11-21—When the two-tone test signal is used for checking the linearity of an amplifier, the peak current is higher than the current indicated by the plate meter. The ratio of these values depends upon the ratio of the idling (no-signal) current to the indicated current.

The graph shows the relationship.

Io = no-signal (idling) current,

 $I_{
m de} =$ meter reading with two-tone test signal,

 $I_{\rm pk} \equiv$ actual peak current.

perfectly applicable for linear r.f. service where no carrier is involved. On the other hand, the ratings sometimes shown for Class B r.f. telephony are *not* what is wanted, because they are for conventional a.m. transmission with carrier.

If audio ratings are not given for the desired tube type, it will be safe to assume that the maximum-signal input for Class B or AB₂ service is about 10 per cent less than the key-down Class C c.w. conditions. The input will have to be held somewhat lower in Class AB₁ operation because the average efficiency is lower and, also, the tube can draw only a limited amount of current at zero grid voltage.

The maximum-signal conditions determined from tube data correspond in s.s.b. work to the very peak of the r.f. envelope; when a two-tone test signal (or voice) is used, the plate milliammeter does not indicate the peak plate current. The relationship between peak current and indicated current is variable with voice signals, but with the two-tone test signal applied there is a definite relationship between indicated (d.c.) current and peak current. This relationship is plotted in Fig. 11-21. Knowing the ratio of the idling current to the plate current with the twotone test signal, I_o/I_{de} , one can find the factor that can be applied to give the peak current. For example, an amplifier draws 50 ma, with no signal and 250 ma. (before flattening) with the two-tone test signal. $I_o/I_{de} = 0.2$, and $I_{pk}/I_{de} =$ 1.45, from Fig. 11-21. Thus $I_{pk} = 1.45 \times 250 =$ 363 ma.

Should the resulting peak input (0.363 × plate voltage) be different than the design value for the particular amplifier tube, the drive and loading adjustments can be changed in the proper directions (always adjusting the loading so that the peaks of the envelope are on the verge of flattening) and the proper value reached.

Using the Linearity Tests

The photos (Figs. 11-19, 11-22 and 11-23) have been taken to show many of the typical patterns that may be encountered with either of the test arrangements described previously. They are classified separately as to those representing correct conditions (Fig. 11-19), faulty operation of the r.f. amplifier (Fig. 11-22), and various other patterns that look irregular but which really represent a peculiarity in the test set-up or the exciter but not in the final (Fig. 11-23).

Aside from the problem of parasitics, which may or may not be a difficult one, it should be possible without much difficulty to achieve the correct linearity pattern by taking action as indicated by the captions accompanying the photos. It can then be assumed that the amplifier is not contributing any distortion to the signal so long as the peak power level indicated by the test is not exceeded. It is entirely possible, however, that good linearity will be obtained only by holding the power down to a level considerably below what is expected, or conversely that there will be signs of excessive plate dissipation at a level that the tubes should handle quite easily. In such cases, some attention should be given to the plate loading, as discussed below.

The several patterns of Fig. 11-24 show how loading affects the output and efficiency of a linear amplifier. In the first two, loading is relatively light and limiting takes place in the final plate circuit. Reserve power is still available in the driver, evidenced by the fact that heavier loading on the final allows the peak output to increase up to the optimum level of the third pattern. With still heavier loading the output ceases to increase but in fact drops somewhat; even though the input power goes up all the time, the efficiency goes down rapidly. In the last two patterns, the driver is the limiting element in the system, and the extra powerhandling capability of the final, due to heavier loading, is wasted by inability of the driver to do it justice.

1) For good efficiency, the final itself must be the limiting element in the power-handling capability of the system.

2) If the final is not being driven to its limit, it should be loaded less heavily until such is the case.

3) If the power level obtained above is less than should be expected, more driving power is needed.

There are several ways to tell whether or not the final is being driven to its limit. One way is to advance the drive until peak limiting is apparent in the output, then move the oscilloscope coupling link over to the driver plate tank and see whether or not the same limiting appears there. Another way is to decrease or increase the final loading slightly and note whether the limiting output level increases or decreases correspondingly. If it does not, the final is not controlling the system. Still another but similar


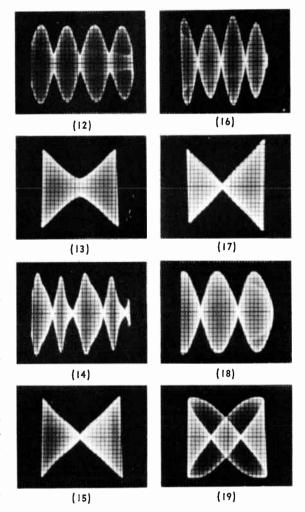


Fig. 11-23—Improper Test Setup. 12—Two r.f. signals unequal. In Method A, caused by improper settings of either carrier or audio control. Method B, either carrier leakage through disabled modulator or unequal sidebands due to selective action of some high-Q circuit off resonance, 13—Same as 12, double-trapezoid test (Method B), 14—Distorted audio, A clue to this defect is that successive waves are not identical, 15-Same distortion as 14, but switched to double trapezoid test pattern. Note that correct pattern prevails regardless of poor audio signal. 16—Carrier leakage through working modulator (Method B only). 17—Same as 16, double trapezoid. 18—(Note tilt to left.) Caused by incomplete suppression of unwanted sideband (Method A) or by r.f. leakage into horizontal circuits of scope. 19-Double trapezoid with audio phase shift in test setup.

method is to detune the final slightly while limiting is apparent, and if proper drive conditions prevail the pattern will improve when the amplifier plate is detuned.

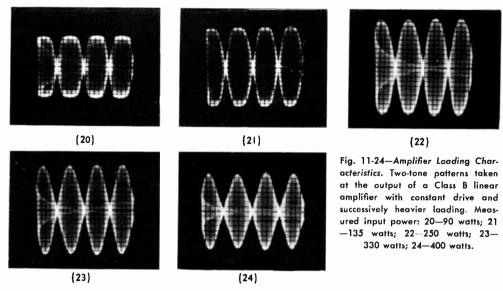The intermediate and driver stages will follow the same laws, except that what is called "load326 SIDEBAND



ing" on a final is often referred to as "impedance matching" when going between tubes. More often than not, an apparent lack of power transfer from a driver to its succeeding stage is due to a poor match. In Class AB_2 or B service, a step-down type of coupling is required between power stages, and a person accustomed to the conventional plate-to-grid coupling capacitor technique will be surprised to find how effective it is to tap the driven stage down on its tank—or otherwise to decouple the system. For example, an 807 driving a pair of 811s requires a voltage step-down of about 3 or 4 to 1 from plate to each grid.

Dummy Load

For the sake of everyone concerned, linearity tests should be kept off the air as much as possible. They make quite a racket and spurious signals are plentiful in earlier stages of misadjustment. Ordinary lamp bulbs make a fine dummy load so long as it is recognized that their impedance is not exactly the same as the antenna and that this impedance changes somewhat as the bulbs light up. These factors can be taken into account by making careful note of plate and grid currents after the transmitter has

been adjusted and is operating with a linearity test signal at maximum linear output into the lamp load. Then, having reconnected the regular antenna, the same loading conditions for the final will be reproduced by adjusting its tuning and loading until the identical combination of plate and grid currents can be obtained. This process will require only a few moments of onthe-air operation.

When the final on-the-air checks are made, it will be convenient to make a few reference marks on the oscilloscope screen to indicate the peak height of the pattern. The scope will then serve as a permanent output monitor for all operations. For best results the sweep should be set for about 30 cycles, in which case the voice patterns will stand out clearly and can easily be kept just within the reference lines. Incidentally, the pattern is really fascinating to watch.

Don't be a "meter bender." Input power isn't everything. If you have to cut your input in half to avoid overload, the fellow at the other end will hardly notice the difference in level. At the same time, your neighbors, both those on the ham band and those next door trying to watch TV, will appreciate the difference right away.

FREQUENCY CONVERSION

The preferred s.s.b. transmitter is probably one that generates the s.s.b. signal at some suitable frequency and then heterodynes the signal into the desired amateur bands, although a few designs exist that generate the s.s.b. signal at the operating frequency and consequently eliminate the need for heterodyning. When the heterodyning is done at low level (involving an s.s.b. signal of not more than a few volts), standard receiving techniques are satisfactory. Normal receiver converter tubes run at manu-

facturer's ratings leave little to be desired. When high-level heterodyning is required, as when an exciter delivering from 5 to 20 watts on a single band is available and multiband operation is desired, a high-level converter is used. Since the efficiency of a converter is only about one-fourth that of the same tube or tubes used in Class AB₂, using a converter stage as the output stage is not very economical, and the high-level converter is generally used to drive the output stage.

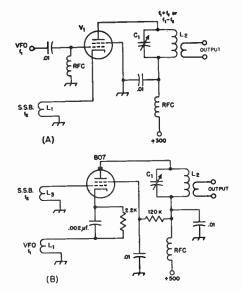


Fig. 11-25—Two examples of "high-level" mixer circuits. The circuit at A has been used with 6V6, 6L6, 6AQ5 and 6Y6 type tubes. With 300 volts on the plate the idling current is about 15 ma., kicking as high as 30 ma. with the s.s.b. signal.

The circuit in B operates with a positive screen voltage and some cathode bias, and is capable of somewhat more output than the circuit shown in A.

In either case the output circuit, C_1L_2 , is tuned to the sum or difference frequency of the oscillator and s.s.b. signal. Coupling coils L_1 and L_3 will usually be three or four turns coupled to their respective driving sources.

Reference to tube manuals will disclose no information of the operation of small transmitting tubes as mixers. However, it has been found that most of the tetrodes in the 15- to 35-watt plate-dissipation class make acceptable mixers, and tubes like the 6V6, 6L6, 807 and 6146 have been used successfully. The usual procedure is to feed one of the signals (oscillator or s.s.b.) to the control grid and the other to the cathode or screen grid. Typical circuits are shown in Fig. 11-25.

(Suggestions for converting to and operating in the 50- and 144-Mc. bands can be found in Tilton, "Single-Sideband Ideas for the V.H.F. Man," QST, May, 1957.)

VOICE-CONTROLLED BREAK-IN

Although it is possible for two s.s.b. stations operating on widely different frequencies to work "duplex" if the carrier suppression is great enough (inadequate carrier suppression would be a violation of the FCC rules), most s.s.b. operators prefer to use voice-controlled break-in and operate on the same frequency. This overcomes any possibility of violating the FCC rules and permits "round table" operation.

Many various systems of voice-controlled break-in are in use, but they are all basically the same. Some of the audio from the speech ampli-

fier is amplified and rectified, and the resultant d.c. signal is used to key an oscillator and one or more stages in the s.s.b. transmitter and "blank" the receiver at the time that the transmitter is on. Thus the transmitter is on at any and all times that the operator is speaking but is off during the intervals between sentences. The voice-control circuit must have a small amount of "hold" built into it, so that it will hold in between words, but it should be made to turn on rapidly at the slightest voice signal coming through the speech amplifier. Both tube and relay keyers have been used with good success. Some voice-control systems require the use of headphones by the operator, but a loudspeaker can be used with the proper circuit. (See Nowak, "Voice-Controlled Break-In . . . and a Loudspeaker," QST, May, 1951, and Hunter, "Simplified Voice Control with a Loudspeaker," QST, October, 1953.)

If an antenna relay is used to switch the antenna from the receiver to the transmitter and back again, it is often possible to operate the output linear amplifier stage with some idling current and experience no difficulty with the "diode noise" generated by the amplifier plate current. However, when the receiver, transmitter and antenna are always connected together, as when an electronic transmit-receive switch is used (see Chapter Eight), weak signals will not be heard through the diode noise of the transmitter. To overcome this difficulty, the idling current of the amplifier must be reduced to zero during listening periods. This can be accomplished through the use of the circuit in Fig. 11-26. Here K_1 is a relay controlled by

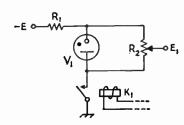


Fig. 11-26—Bias-switching circuit for use with a Class AB₁ linear amplifier and an electronic t.r. switch.
 R₁—4700 ohms, 1 watt.
 R₂—100,000 ohms, 2 watts.
 K₁—VOX relay or relay controlled by VOX circuit.

V₁—0A2 or 0B2, depending upon amplifier requirements.

the voice-controlled break-in circuit. When the relay is closed, the operating bias E_1 for the linear amplifier is determined by the setting of the arm on R_2 . When the relay is open, the grid bias jumps to the value E, which should be high enough to cut off the amplifier stage. The voltage regulator tube should be one with a nominal voltage drop in excess of the normal bias for the amplifier tube, and the negative supply voltage E should be at least 25 per cent higher than the