

electronics data
handbook elec
tronics data hand
book·electronics
data handbook

MARTIN CLIFFORD

GERNSBACK LIBRARY NO. 118



electronics

data

handbook

MARTIN CLIFFORD

GERNSBACK LIBRARY, INC.,

NEW YORK, N. Y. 10011

This book is dedicated
to the memory of
PHILIP I. PRYZANT



© 1964 Martin Clifford
*All rights reserved under Universal,
International, and Pan-American
Copyright Conventions.*

Library of Congress Catalog Card No. 64-23823

Contents

CHAPTER		PAGE
1	DC	7
	Resistors. Resistors in series. Resistors in parallel. Resistors in series-parallel. Conductance. Preferred values of resistors. Resistor color code. Resistance of wire. Temperature. Centigrade-Fahrenheit conversion. Coefficient of resistance. Ohm's law. Basic units. Power. Efficiency. Power units. Power vs energy. Phase. The shunt law. Voltage divider. Voltages in series aiding and opposing. Kirchhoff's voltage law. Kirchhoff's current law. Time constants.	
2	AC	29
	Wavelength and frequency. Period. Velocity of a wave. Voltage and current measurements. Average value. Instantaneous values. Effective or rms values of a sine wave of voltage or current. Capacitors. Multiples and submultiples. Capacitors in parallel. Capacitors in series. Capacitors in series-parallel. Charge of a capacitor. Energy stored in a capacitor. Working voltage of a capacitor. Capacitors as voltage dividers. Capacitive reactance. Ohm's law for a capacitive circuit. Impedance of an $R-C$ circuit. Voltages in a series $R-C$ circuit. Inductors. Inductors in series. Inductors in parallel. Coefficient of coupling and mutual inductance. Inductors in series aiding. Inductors in series opposing. Inductors in parallel aiding. Inductors in parallel opposing. Reactance of an inductor. Ohm's law for an inductive circuit. Impedance in an $R-L$ circuit. Voltages in a series $R-L$ circuit. Effective resistance. Q of a coil. Q of a capacitor. Voltage transformers, step up and step down. Current transformers, step up and step down. Impedance transformers. Transformer color codes. Phase angle. Series circuits: $R-L$; $R-C$; $L-C$; $R-L-C$. Parallel circuits: $R-L$; $R-C$; $L-C$; $R-L-C$; $R-L$ shunted by R ; $R-L$ shunted by C . Admittance of a series circuit. Susceptance. Conductance. Ohm's law for ac. Power in ac circuits. Apparent power. Power factor. Resonance in a series circuit. Q of a series resonant circuit. Decibels and Nepers. Volume units. Filters (constant K): Low-pass; High-pass; Band-pass; Band-elimination; T -type low-pass. π -type low-pass; π -type high-pass; m -derived. types of m -derived.	

3

Vacuum Tubes and Vacuum Tube Circuits 81

Amplification factor. Plate resistance. Mutual conductance. Voltage amplifiers. Cathode followers. Resistance-coupled audio amplifiers (triodes). Amplification at medium frequencies (triodes). Amplification at low frequencies (triodes). Amplification at high frequencies (triodes). Resistance-coupled audio amplifiers (pentodes). Amplification at medium frequencies (pentodes). Amplification at low frequencies (pentodes). Amplification at high frequencies (pentodes). Negative feedback. Power amplifiers. Power sensitivity. Power output. Maximum transfer of power. Power in the plate load. Undistorted power output. Single pentode audio power output. Second-harmonic distortion of a power amplifier.

4

Transistors 95

Current amplification. Resistance gain. Voltage gain. Power gain. Basic circuits. Current amplification factor. Alpha cutoff frequency. Input and output resistances.

5

Antennas and Transmission Lines 103

Full wave antennas. Antenna impedance. Radiated power. Power gain. Transmission lines. Two-wire open transmission line. Attenuation. Concentric transmission line (air insulated). Resistance of coaxial transmission line. Resistance of open two-wire copper line. Standing wave ratio (*SWR*). Characteristic impedance. Matching impedances. Velocity factor. Length of transmission line. Antenna types.

6

Measurements 117

Shunt resistance. Multiplier resistance. Resistance measurements. Bridges. Wheatstone bridge. Slide wire bridge. Ac bridge. The slope. Frequency measurements. Lissajous patterns.

7

Tables and Data 125

Conversion factors. Electronic abbreviations. Decimal equivalents of fractions of an inch. Wavelength and frequency bands. Mathematical symbols. Mathematical data. Greek alphabet. Powers of two. Fundamentals of Boolean algebra. Squares, cubes and roots. Powers of numbers. Trigonometric functions. Conversion of inches to millimeters. Conversion of millimeters to inches. Common logarithms of numbers. Binary numbers. Decimal to binary conversion rules. Fusing currents of wires. Roman numerals. Numerical data. Common integrals. Linear measure. Square measure. Cubic measure. Liquid measure. Dry measure. Circular measure. Electronic symbols used in communications and industrial electronics.

Introduction

The amount of data faced by those who become involved in the study of electronics is simply staggering. Some of it, once purely the province of the electrical engineer, has become necessary even for those who have made electronics their avocation, their hobby.

Where is this data? Every book on electronics is filled with it. There is no scarcity of information. There is a definite problem, though, in being able to reach it with minimum effort and minimum time. The research, however, generally involves considerable reliance on memory, on the availability of a number of text books, and the ability to use the contents pages or indexes of these books to best advantage.

This brings us directly to the purpose of this book. Its function is to help minimize the research needed to find specific electronics information. No claim is made for completeness, but every effort has been made to include those formulas which are commonly used.

What is a formula? It is just an extremely convenient, shorthand way of writing information. There is nothing unusual or special about formulas, but because they often make use of mathematical symbols, the impression is sometimes raised that they represent the height of accuracy and that the answers they yield are beyond question or challenge. Nothing of the sort. Quite often a formula will represent nothing more than a reasonably good approximation. Similarly, calculating a formula to several decimal places is ridiculous, when slide rule accuracy would be all that is required.

The solution to a problem in electronics may involve the use of several formulas. The ability to solve such a problem will require judgment in the selection of the formulas and their use in the proper sequence. A knowledge of elementary algebra and trigonometry and some skill in handling algebraic functions will be of considerable help. Quite often the stumbling block in electronics is not electronics but the failure to realize that electronics relies on mathematics as a tool.

Every book requires that the author make certain assumptions—assumptions of prior knowledge on the part of his readers. This book is no exception. This is not a book of electronic theory. Since a formula is usually the end product of theory, the only intent here is to provide formulas in an easily accessible manner. Where explanatory material is given in this text its function is to clarify the use of a formula, or its derivation.

Many additional and useful formulas can be obtained through the use of transpositions and/or substitutions. Ohm's law is a notable example since, basically, we have just one formula. Practically speaking, though, we have three by transposing quantities from one side of the formula to the other. Substituting equal quantities from one formula into another also produces "new" formulas that may lend themselves very nicely to particular applications.

Our special thanks must go to Mr. Arnold Rudahl, editor of *ELECTRO-TECHNOLOGY* Magazine for his helpful criticisms and to Kenneth Clifford who did yeoman work throughout in collecting and checking the material.

New York, N.Y..

MARTIN CLIFFORD

Chapter 1

DC

For the purpose of this book we are going to consider that there are only five basic components used in any electronic apparatus – whether a small receiver or a complex computer. These basic components are resistors, capacitors, inductors (or coils), tubes and transistors.* But these components lend themselves to a tremendous number of variations and combinations. The rules, the laws and the formulas of electronics help us understand the behavior of these components, taken together or separately, and to predict their behavior.

RESISTORS

Resistors enable us to control the flow of electric currents. With their help we can divide voltages. In combination with other com-

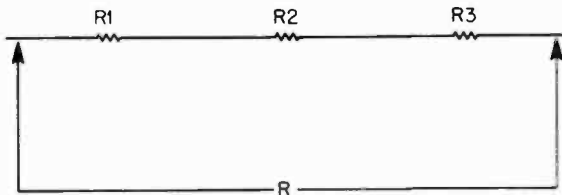


Fig. 1-1. When wiring resistors in series, the total resistance is not affected by the order in which the resistors are connected.

*A battery might be considered as still another component, but it is not regarded so here.

ponents we use them to make electrical waves into shapes most suited for our needs. Resistors can be used individually, in series, in parallel, in series-parallel.

Resistors in series. See Fig. 1-1.

$$R = R_1 + R_2 + R_3 \dots \dots \quad (1-1)$$

R is the total resistance. R_1 , R_2 and R_3 are the individual resistors. The dots indicate that you can have any number of resistors. The resistors can be arranged in any order and their values can be added in any order. Before using the formula, make sure that the resistors are in the same units—ohms, kilohms or megohms.

Resistors in parallel. See Fig. 1-2.

$$R = \frac{R_1 \times R_2}{R_1 + R_2} \quad (1-2)$$

This formula is useful only for two resistors in parallel. R is the total resistance. R_1 and R_2 are the individual resistors.

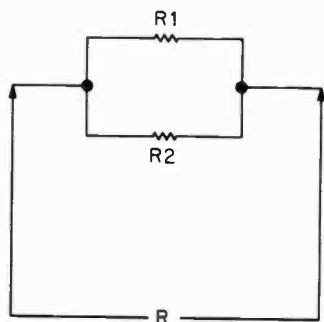


Fig. 1-2. For resistors in parallel, the total resistance is less than the value of either resistor.

Resistors in parallel. See Fig. 1-3.

$$R = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \dots \dots \dots} \quad (1-3)$$

R is the total resistance. This formula is suitable for adding as many resistors in parallel as you wish, as indicated by the dots. It can also be used for adding two resistors in parallel.

An algebraic variation of the same formula is:

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \dots \dots \dots \quad (1-4)$$

Resistors in parallel.

$$R = \frac{R_1}{1 + R_1/R_2 + R_1/R_3 + R_1/R_4} \quad (1-5)$$

This formula can be extended to include any number of parallel resistors. It can also be combined with the formula for series resistors to supply the answer to a series-parallel combination. To make the work easier when using this formula, make R_1 the largest resistor in the parallel combination.

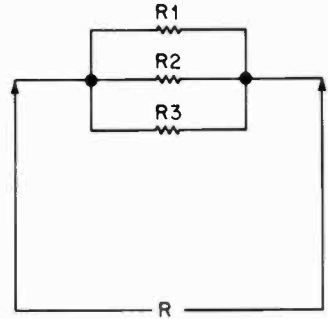


Fig. 1-3. Several formulas are available for calculating the total resistance of three or more resistors in parallel. The total resistance will always be less than the value of any resistor in the parallel combination.

Tables 1-1 and 1-2 are charts which can be conveniently used to find the total resistance of two resistors in parallel. However, for values of resistors not shown in the charts, it will still be necessary to use a formula.

Table 1-1. Total resistance, R , for two resistors, R_1 and R_2 , in parallel, with resistance values from 1 to 100 ohms (kilohms, megohms).

R_1	1	1.5	2.2	3.3	4.7	6.8	10	15	22	33	47	68
R_2												
1	0.50	0.60	0.69	0.77	0.83	0.87	0.91	0.93	0.95	0.97	0.98	0.99
1.5	0.60	0.75	0.89	1.03	1.14	1.22	1.30	1.36	1.40	1.43	1.45	1.46
2.2	0.69	0.89	1.10	1.32	1.50	1.66	1.82	1.92	2.00	2.06	2.10	2.13
3.3	0.77	1.03	1.32	1.65	1.94	2.22	2.48	2.70	2.87	3.00	3.08	3.14
4.7	0.83	1.14	1.50	1.94	2.35	2.78	3.20	3.58	3.87	4.12	4.27	4.39
6.8	0.87	1.22	1.86	2.22	2.78	3.40	4.05	4.58	5.79	5.64	5.94	6.18
10	0.91	1.30	1.82	2.48	3.20	4.05	5.0	6.0	6.9	7.7	8.3	8.7
15	0.93	1.35	1.92	2.70	3.58	4.68	6.0	7.50	8.9	10.3	11.4	12.2
22	0.95	1.40	2.00	2.87	3.87	5.19	6.9	8.90	11.0	13.2	15.0	16.6
33	0.97	1.43	2.06	3.00	4.12	5.64	7.7	10.3	13.2	16.5	19.4	22.2
47	0.98	1.45	2.10	3.08	4.27	5.94	8.3	11.4	15.0	19.4	23.5	27.8
68	0.99	1.45	2.13	3.14	4.39	6.18	8.7	12.2	16.6	22.2	27.8	34.0

Table 1-2. Total resistance, R , for two resistors, R_1 and R_2 in parallel, with resistance values from 10 to 1,000 ohms (kilohms, megohms).

R_1	10	15	22	33	47	68	100	150	220	330	470	680
R_2												
10	5.0	6.0	6.9	7.7	8.3	8.7	9.1	9.3	9.5	9.7	9.8	9.9
15	6.0	7.5	8.9	10.3	11.4	12.2	13.0	13.6	14.0	14.3	14.5	14.6
22	6.9	8.9	11.0	13.2	15.0	16.6	18.2	19.2	20.0	20.6	21.0	21.3
33	7.7	10.3	13.2	16.5	19.4	22.2	24.8	27.0	28.7	30.0	30.8	31.4
47	8.3	11.4	15.0	19.4	23.5	27.8	32.0	35.8	38.7	41.2	42.7	43.9
68	8.7	12.2	16.6	22.2	27.8	34.0	40.5	46.8	51.9	56.4	59.4	61.8
100	9.1	13.0	18.2	24.8	32.0	40.5	50	60	69	77	83	87
150	9.3	13.6	19.2	27.0	25.8	46.8	60	75	89	103	114	122
220	9.5	14.0	20	28.7	38.7	51.9	69	89	110	132	150	166
330	9.7	14.3	20.6	30.0	41.2	56.4	77	103	132	165	194	222
470	9.8	14.5	21.0	30.8	42.7	59.4	83	114	150	194	235	278
680	9.9	14.6	21.3	31.4	43.9	61.8	87	122	166	222	278	340

CONDUCTANCE

Conductance and resistance are the same. They are the *inverse* of each other.

$$G = \frac{1}{R} \quad (1-6)$$

and

$$R = \frac{1}{G} \quad (1-7)$$

The basic unit of resistance is the ohm. The basic unit of conductance is the mho. The mho is simply the ohm spelled backward.

Resistors in parallel (conductance method) See Fig. 1-4.

$$G = G_1 + G_2 + G_3 \dots \dots \quad (1-8)$$

This formula regards the components shown in Fig. 1-4 as conductors.

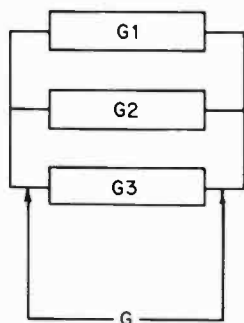


Fig. 1-4. The solution of a problem involving parallel resistors is often made easier by considering them as conductors.

G is the total conductance in mhos. Conversion can be made to the more familiar resistance form by dividing each term into the number 1.

$$G = G_1 + G_2 + G_3 = \frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \quad (1-9)$$

Which leads us directly back to formula given in (1-4).

Resistors in series-parallel. See Fig. 1-5.

The formula for resistors in series can be combined with any of the

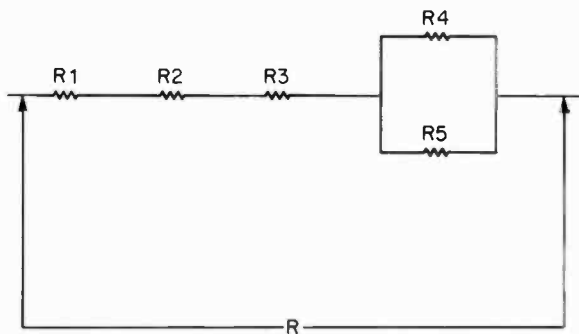


Fig. 1-5. Basically, finding the total resistance of a circuit of this type involves the use of two different formulas.

formulas for resistors in parallel to supply the answer to problems involving resistors in series-parallel combinations.

$$R = R_1 + R_2 + R_3 + \frac{R_4 \times R_5}{R_4 + R_5} \quad (1-10)$$

Often, working with three or more resistors in parallel, calculation of the total resistance can be tedious. It may be desirable to round off resistance values to make the arithmetic easier, keeping in mind that the resistance, as indicated in the circuit, will not take the tolerance into consideration.

In any parallel combination, if there is a 10 to 1 ratio, or better, between resistor values, the total resistance will be only slightly lower than the value of the smallest resistor.

PREFERRED VALUES OF RESISTORS

Values of resistors follow the recommendations of the Electronics Industries Association (EIA). Table 1-3 shows the values for molded composition resistors. All the values in this list are available in a

tolerance of $\pm 5\%$. The values shown in bold-face type are for resistors with a tolerance of $\pm 10\%$.

Table 1-3. Preferred resistor values.

Ohms						Megohms			
2.7	13	68	360	1800	9100	47000	0.24	1.1	5.1
3.0	15	75	390	2000	10000	51000	0.27	1.2	5.6
3.3	16	82	430	2200	11000	56000	0.30	1.3	6.2
3.6	18	91	470	2400	12000	62000	0.33	1.5	6.8
3.9	20	100	510	2700	13000	68000	0.36	1.6	7.5
4.3	22	110	560	3000	15000	75000	0.39	1.8	8.2
4.7	24	120	620	3300	16000	82000	0.43	2.0	9.1
5.1	27	130	680	3600	18000	91000	0.47	2.2	10.0
5.6	30	150	750	3900	20000	100000	0.51	2.4	11.0
6.2	33	160	820	4300	22000	110000	0.56	2.7	12.0
6.8	36	180	910	4700	24000	120000	0.62	3.0	13.0
7.5	39	200	1000	5100	27000	130000	0.68	3.3	15.0
8.2	43	220	1100	5600	30000	150000	0.75	3.6	16.0
9.1	47	240	1200	6200	33000	160000	0.82	3.9	18.0
10	51	270	1300	6800	36000	180000	0.91	4.3	20.0
11	56	300	1500	7500	39000	200000	1.0	4.7	22.0
12	62	330	1600	8200	43000	220000			

RESISTOR COLOR CODE

The color code for resistors (Fig. 1-6) is that established by the EIA.

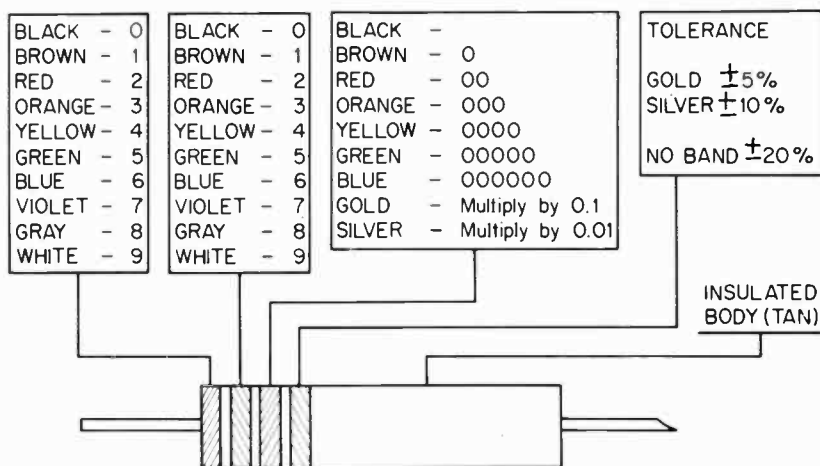



Fig. 1-6. The first three color bands supply the total resistance. The fourth color [if any] gives the tolerance. Example: A 5,600-ohm resistor would be green [first color-5], blue [second color-6] and red [third color-00].

RESISTANCE OF WIRE

The resistance of any copper wire depends upon its length and cross-sectional area—that is, upon its volume. Resistance increases with length, decreases as the cross-sectional area becomes greater. Expressed in a formula, we have:

$$R = \rho \frac{l}{A} \quad (1-11)$$

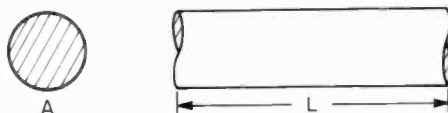R is the resistance in ohms, l is the length and A is the cross-sectional area. (See Fig. 1-7). The length l is in feet and the area is in circular



Volume = length x cross-sectional area

Fig. 1-7. The resistance of a conductor is based upon its length and cross-sectional area—that is, upon its volume. Other factors, such as voltage and temperature, material of which the resistor is made, will also determine the resistance. The value of a resistor, not connected, and measured in open space, will not necessarily be the value of that resistor connected, and working in a circuit.

mils. 1 mil = 0.001 inch. The Greek letter ρ (rho) is the specific resistance or the resistivity of a metal—in this case, copper. The specific resistivity of copper is 10.4. The resistivity of most other metals is higher—aluminum is 17, brass is 45. Silver is 9.8, making it a better conductor than copper. To find the area of a copper wire when the diameter is given in mils, square the diameter (multiply it by itself). A diameter of 5 mils is an area of 25 circular mils. This means that formula (1-11) can be written as:

$$R = \rho \frac{l}{d^2} \quad (1-12)$$

The resistance of copper wire varies with temperature. The resistivity of 10.4 for copper wire is at 20° Centigrade. Table 1-4 lists the diameter in mils and the area in circular mils of copper wire from No. 1 gauge to No. 44 gauge.

The formula for the resistance of copper wire does not take the effects of temperature into consideration. The resistance value, obtained by using the formula, is for wire in free space, not carrying current. The information given in Table 1-4 is for bare, annealed copper wire at 20 degrees Centigrade, corresponding to 68 degrees Fahrenheit.

1000 Cir Mil / AMP

Table 1-4. Diameter in mils and area in circular mils of copper wire. AWG (American Wire Gauge) or B & S (Browne and Sharpe) Measured at 20°C.

Gauge	Diameter	Area	Gauge	Diameter	Area
1	289.3	83,690.0	23	22.57	509.5
2	257.6	66,370.0	24	20.10	404.0
3	229.4	52,640.0	25	17.90	320.4
4	204.3	41,740.0	26	15.94	254.1
5	181.9	33,100.0	27	14.20	201.5
6	162.0	26,250.0	28	12.64	159.8
7	144.3	20,820.0	29	11.26	126.7
8	128.5	16,510.0	30	10.03	100.5
9	114.4	13,090.0	31	8.93	79.70
10	101.9	10,380.0	32	7.95	63.21
11	90.74	8,234.0	33	7.08	50.13
12	80.81	6,530.0	34	6.31	39.75
13	71.96	5,178.0	35	5.62	31.52
14	64.08	4,107.0	36	5.00	25.00
15	57.07	3,257.0	37	4.45	19.83
16	50.82	2,583.0	38	3.96	15.72
17	45.26	2,048.0	39	3.53	12.47
18	40.30	1,624.0	40	3.14	9.89
19	35.89	1,288.0	41	2.80	7.84
20	31.96	1,022.0	42	2.50	6.22
21	28.46	810.1	43	2.22	4.93
22	25.35	642.4	44	1.98	3.91

Table 1-4 shows that the smaller the gauge number, the thicker the wire. You will find it convenient to keep in mind that the area of wire approximately doubles for every three gauge numbers. Thus, No. 20 wire has double the area of No. 23. The significance here is that the current-carrying capacity is also doubled.

Wires having a diameter greater than 289.3 mils have gauge numbers 0, 00, 000 and 0000.

TEMPERATURE

In common practice, temperature is given in degrees Fahrenheit or Centigrade. (Other scales, more often found in laboratory rather than commercial or industrial use, include Kelvin, Reaumur and Rankine.)

To change degrees Centigrade to degrees Fahrenheit:

$$F = (C \times 9/5) + 32 \quad (1-13)$$

To change degrees Fahrenheit to degrees Centigrade:

$$C = (F - 32) \times 5/9 \quad (1-14)$$

F is in degrees Fahrenheit and C is in degrees Centigrade. (Also see Table 1-5.)

Table 1-5. Centigrade-Fahrenheit conversion.

Deg. C.	Deg. F.	Deg. C.	Deg. F.	Deg. C.	Deg. F.	Deg. C.	Deg. F.
-40	-40.0	80	176.0	210	410	310	590
-30	-22.0	90	194.0	220	428	320	608
-20	- 4.0	100	212.0	230	446	330	626
-10	14.0	110	230.0	240	464	340	644
0	32.0	120	248.0	250	482	350	662
10	50.0	130	266.0	260	500	360	680
20	68.0	140	284.0	270	518	370	698
30	86.0	150	302.0	280	536		
40	104.0	160	320.0	290	554		
50	122.0	170	338.0	300	572		
60	140.0	180	356.0				
70	158.0	190	374.0				
		200	392.0				

COEFFICIENT OF RESISTANCE

Resistors can change their value, the amount of change depending on how the resistors were made, the temperature and the voltage across the resistors.

The term, coefficient of resistance, is used to describe a change in the value of resistance. A positive temperature coefficient means that the resistor will increase in value with an increase in temperature. A negative temperature coefficient means a decrease. Zero temperature coefficient means no change whether temperature goes up or down. Resistors can have either a positive or a negative temperature coefficient, depending on how the component is manufactured. The voltage coefficient for composition resistors is negative, that is, the resistance decreases with increasing voltage.

OHM'S LAW

More widely used than any other formula in electronics (see Fig. 1-8) Ohm's law is simply:

$$E = I \times R \quad (1-15)$$

E is the voltage (in volts), I is the current in amperes and R is the resistance in ohms. By dividing both sides of this formula by R , we get:

$$I = \frac{E}{R} \quad (1-16)$$

Or, by dividing both sides by I , we get:

$$R = \frac{E}{I} \quad (1-17)$$

By common practice, the unknown value (the value we are looking for) is placed on the left-hand side of the equation. These three forms

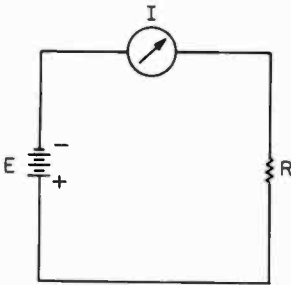


Fig. 1-8. Simple circuit showing three factors involved—voltage, current and resistance. When any two of these are known, the third and unknown value can be found by using Ohm's law.

of Ohm's law can be used to find any one value (such as voltage) when the other two values (current and resistance) are known.

BASIC UNITS

The basic units used in Ohm's law are the volt, the ampere and the ohm. Multiples and submultiples of these units are often convenient.

The numbers used in problems involving Ohm's law are often very large whole numbers or large decimals. When this happens it is more convenient to use exponents. The relationships between the ohm, volt and ampere in both numerical and exponential form is:

In Terms of Numbers

Unit	Symbol	Multiple	Value
volt	E	kilovolt (kv)	1,000 volts
volt	E	millivolt (mv)	1/1,000 volt
volt	E	microvolt (μv)	1/1,000,000 volt
ohm	R	kilohm	1,000 ohms
ohm	R	megohm	1,000,000 ohms
ampere	I	milliampere (ma)	1/1,000 ampere
ampere	I	microampere (μa)	1/1,000,000 ampere

In Terms of Exponents

1 volt	= 10^3 millivolts	= 10^6 microvolts
1 millivolt	= 10^{-3} volt	= 10^3 microvolts
1 microvolt	= 10^{-6} volt	= 10^{-3} millivolt
1 ohm	= 10^{-3} kilohm	= 10^{-6} megohm
1 kilohm	= 10^3 ohms	= 10^{-3} megohm
1 megohm	= 10^6 ohms	= 10^3 kilohms
1 ampere	= 10^3 milliamperes	= 10^6 microamperes
1 milliampere	= 10^{-3} ampere	= 10^3 microamperes
1 microampere	= 10^{-6} ampere	= 10^{-3} milliamperes

The two triangles shown in Fig. 1-9a are memory aids for remembering Ohm's law. Cover the *unknown* value with a finger tip and the triangle automatically reveals the correct formula to use. If you want

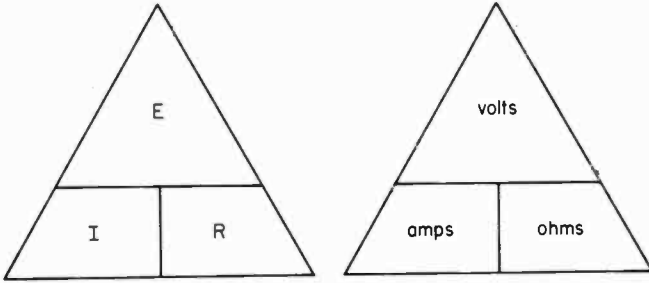


Fig. 1-9a. These are memory aids for remembering Ohm's law. Ohm's law is one of the most widely used formulas in electronics.

to find the current in a circuit (just as an example) cover the letter *I* or the word "amps" and the formula is revealed as either *E* divided by *R* or volts divided by ohms.

POWER

The power in a dc circuit involves values of voltage, current and resistance. In the basic power formula (Fig. 1-9b):

$$P = E \times I \quad (1-18)$$

power (*P*) is in watts, voltage (*E*) is in volts and the current (*I*) is in

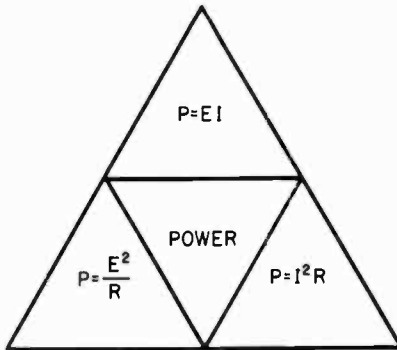


Fig. 1-9b. These are the three basic power laws. The power laws can be combined with Ohm's law to yield other useful formulas.

amperes. This formula, like the Ohm's law formula, is of the $A = B \times C$ type. Knowing any two of the three values in this formula always yields the answer to the unknown. $A = B \times C$; $B = A/C$ and $C = A/B$. Similarly, $P = E \times I$; $E = P/I$ and $I = P/E$.

We can easily derive other power formulas from the basic power formula and use of Ohm's law.

$$P = E \times I \quad \text{But } E = I \times R$$

substituting $I \times R$ for E in the power formula we have:

$$P = I \times R \times I \quad \text{Note that } I \times I = I^2$$

$$\text{Thus, } P = I^2 R \text{ or } I^2 \times R \quad (1-19)$$

This formula is still of the $A = B \times C$ type and so any two known values can be made to reveal the unknown quantity.

We can make another substitution in our power formula.

$$P = E \times I \quad \text{But } I = E/R$$

substituting E/R for I in the power formula we have:

$$P = E \times E/R \quad E \times E = E^2$$

$$P = E^2/R \quad (1-20)$$

Since E , I and R are always used in some form of the power laws and in Ohm's law as well, a little algebraic manipulation leads to some new formulas:

$$E = I \times R \text{ and } P = E \times I \text{ or } I = \frac{P}{E}$$

then $E = \frac{P \times R}{E}$ multiplying both sides by E we have:

$$E^2 = P \times R \text{ or } E = \sqrt{P \times R} \quad (1-21)$$

Other formulas can be obtained more directly:

$$P = I^2 R \quad I^2 = \frac{P}{R} \quad I = \sqrt{\frac{P}{R}} \quad (1-22)$$

Similarly:

$$E = \frac{P}{I} \quad (1-23)$$

$$R = \frac{P}{I^2} \quad (1-24)$$

$$R = \frac{E^2}{P} \quad (1-25)$$

The formulas used in Ohm's law and in problems involving power can be conveniently summarized and are shown in Table 1-6.

WORK

Power used per unit of time is called work. That is, $\text{work} = P \times t$. The basic unit is the watt-hour.

Table 1-6. Summary of power and Ohm's law formulas for dc.

<i>Watts</i>	<i>Amperes</i>	<i>Ohms</i>	<i>Volts</i>
$P =$	$I =$	$R =$	$E =$
E^2/R	E/R	E/I	IR
I^2R	P/E	E^2/P	P/I
EI	$\sqrt{P/R}$	P/I^2	\sqrt{PR}

EFFICIENCY

Note that power always involves either voltage or current, but voltage or current *alone* do not represent an expenditure of energy. A battery is a voltage source but there is no utilization of the electrical energy stored in the battery until the battery is connected to a circuit component, such as a resistor.

Electronic circuits receive power from a battery (or a power supply), use this power (called input power) to perform some function. The power may be modified or changed in some way and then, called output power, may be delivered to a load. The load may be a resistor, some other component, or another circuit.

Since part of the power will be used in the circuit itself, the output power will always be less than the input. The ratio of these two powers is called the efficiency:

$$\eta = P_o/P_i \quad (1-26)$$

η is the efficiency, P_o is output power while P_i is input power. Since P_o is always less than P_i , the answer must always be decimal—that is, less than one. To obtain efficiency in terms of percentage rather than a decimal, multiply the answer by 100.

POWER UNITS

The basic unit of power is the watt. As in the case of Ohm's law large whole numbers or decimals may be involved, making the use of

exponents desirable. The power formulas given are valid only for linear resistors—that is, resistors which obey Ohm's law.

In Terms of Numbers			
<i>Unit</i>	<i>Symbol</i>	<i>Multiple</i>	<i>Value</i>
watt	<i>P</i>	microwatt	1/1,000,000 watt
watt	<i>P</i>	milliwatt	1/1,000 watt
watt	<i>P</i>	megawatt	1,000,000 watts
In Terms of Exponents			
1 watt		= 10 ³ milliwatts	= 10 ⁶ microwatts
1 milliwatt		= 10 ⁻³ watt	= 10 ³ microwatts
1 microwatt		= 10 ⁻⁶ watt	= 10 ⁻³ milliwatt

POWER vs ENERGY

Energy is the ability to do work. The rate at which that work is done is called power. The unit of energy or work is the joule. The unit of power is the joule/second or watt. In electronics, electrical power is usually measured in watts. Electrical energy can be stored, but not in resistors. Electrical energy put into a resistor is given off by that resistor as heat.

PHASE

The dc voltage across a resistor and the dc current through it are always in step or in phase. If the voltage increases, the current will also increase, assuming that the value of resistance remains constant. Under the same conditions, a decrease in voltage always results in a decrease in current.

THE SHUNT LAW

When a voltage is applied to resistors connected in parallel, the same voltage appears across each of the resistors. Since the voltage E is equal to $I \times R$, we can make the same statement in the shape of a formula:

$$I_1 \times R_1 = I_2 \times R_2 \quad (1-27)$$

If we get the current terms on one side of this equation and the resistance terms on the other side, we will have:

$$\frac{I_1}{I_2} = \frac{R_2}{R_1}$$

This new arrangement shows us that the ratio of the currents (see Fig. 1-10) is inversely proportional to the ratio of the resistances. This is just another way of saying that the larger the resistance, the smaller

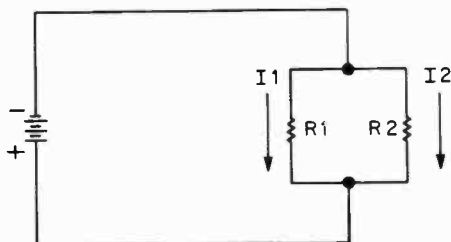


Fig. 1-10 While the currents flowing through $R1$ and $R2$ might not be equal, the voltages across each resistor are identical. Actually, there is only one voltage across the parallel units, but it is convenient to regard it as two equal voltages.

the current flowing through it. A formula, such as that above is just another application of Ohm's law.

Formulas of this kind are of the $A \times B = C \times D$ type. They can be rearranged to supply four additional formulas. In each instance, though, there must be only one unknown—that is, you must have values for three of the four items in the formula. Using $I1 \times R1 = I2 \times R2$, we have:

in terms of current

$$I1 = \frac{I2 \times R2}{R1} \quad (1-28)$$

$$I2 = \frac{I1 \times R1}{R2} \quad (1-29)$$

in terms of resistance

$$R1 = \frac{I2 \times R2}{I1} \quad (1-30)$$

$$R2 = \frac{I1 \times R1}{I2} \quad (1-31)$$

VOLTAGE DIVIDER (Potentiometer)

A fixed voltage, such as that supplied by a battery, is often not suitable for a particular circuit or component. Resistors can be used as voltage dividers to obtain any value of voltage less than that of

the source. See Fig. 1-11. The smaller voltage, e , is equal to the source voltage multiplied by the ratio of the resistances:

$$e = E \times \frac{R1}{R1 + R2} \quad (1-32)$$

As $R2$ is made smaller, the output voltage e becomes larger, reaching the value of E as a limit. The input voltage E remains constant. Since

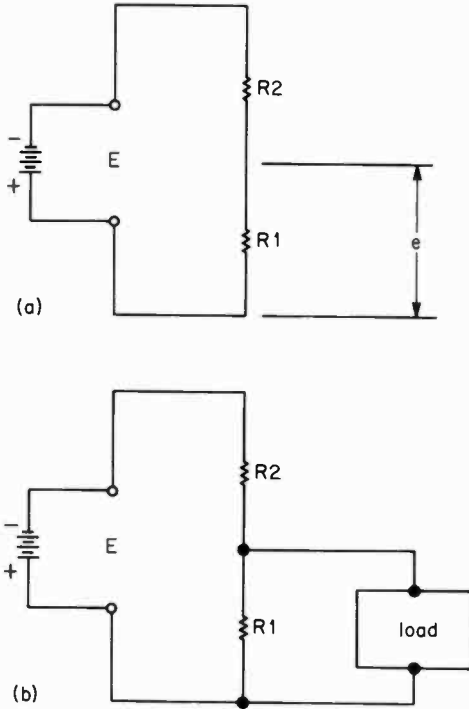


Fig. 1-11. It is often convenient to be able to calculate the voltage across a single resistor of a network.

the resistors, $R1$ and $R2$ are in series, the same current flows through them.

Suppose a load is placed across $R1$. If the load does not draw current, then the formula can be used as is to find the value of e . If the load does draw current, and if the resistance of the load is known, then $R1$ and the load may be considered as a pair of parallel resistors. Calculate the equivalent value of this parallel pair, substitute this value for $R1$, and the formula can then be used to determine the amount of e .

VOLTAGES IN SERIES AIDING AND OPPOSING

Voltages in series aiding are additive (see Fig. 1-12). The total

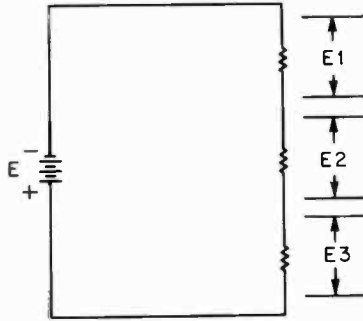


Fig. 1-12. The voltage across each resistor may be added to obtain the total voltage. See Fig. 1-15 on the following page for the polarities of the voltage drops.

voltage is equal to the sum of the individual voltages;

$$E = E1 + E2 + E3 \dots \dots \quad (1-33)$$

Voltages can be connected in series opposing. The total voltage

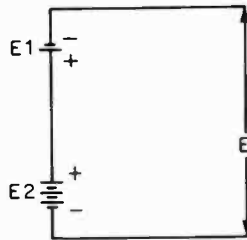


Fig. 1-13. The total voltage is equal to the difference of the two voltages.

(see Fig. 1-13) is equal to the larger voltage minus that of the smaller one.

$$E = E2 - E1$$

If the two voltages are equal, but opposing, the total effective output voltage is zero. This is true, even though the individual voltages may be large.

KIRCHHOFF'S VOLTAGE LAW

The algebraic sum of the voltages around a closed circuit or network is zero. More simply stated, the sum of the voltages in a closed circuit

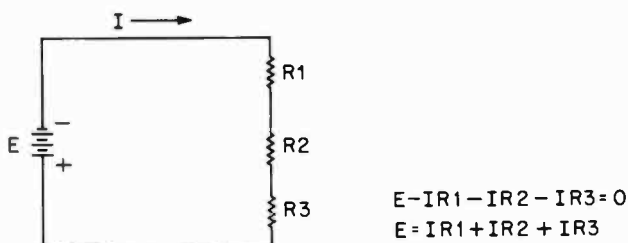


Fig. 1-14. If the voltage drops across each resistor are added, their sum will be equal to the voltage of the battery. If this sum is subtracted from the battery voltage, the result will be zero.

or network is equal to the applied emf (electromotive force or voltage). See Fig. 1-14.

Consider Fig. 1-15. The sum of the voltage drops across the resistors

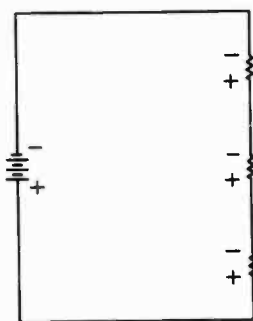


Fig. 1-15. The polarity of the battery voltage and the polarity of the voltage drops across the resistors are opposite.

is equal to that of the battery. Note the voltage polarities of the resistors and the battery. They oppose each other, but since the voltages are equal, the algebraic sum is zero.

More practically, in electronics we consider the sum of the voltage drops equal to the source voltage (Fig. 1-16). That is:

$$E_{\text{battery}} = I_1R_1 + I_1R_2 + I_1R_3$$

Since this is a series circuit, the same current (I_1) flows through each of the resistors.

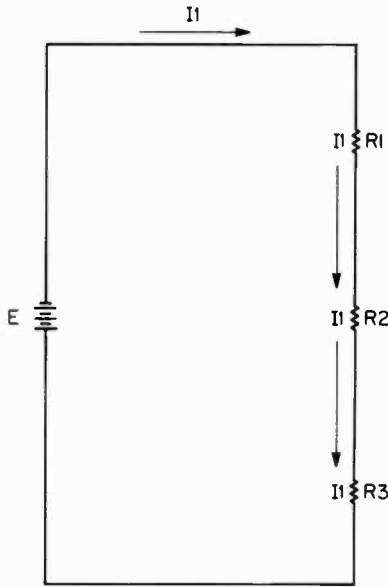


Fig. 1-16. In a series circuit, the same current flows through each component.

KIRCHHOFF'S CURRENT LAW

The algebraic sum of the currents flowing toward a junction is equal

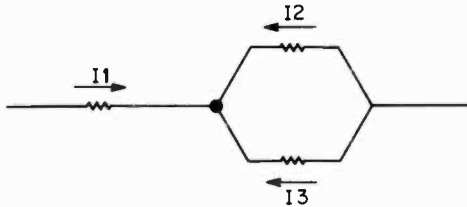


Fig. 1-17. The heavy dot represents the junction toward which the currents are flowing. The algebraic sum of these currents is zero.

to zero. See Fig. 1-17. If we take the conditions existing in this circuit and set it up as an equation, we will have:

$$I_1 - I_2 - I_3 = 0$$

While the conditions shown in Fig. 1-17 may be algebraically pos-

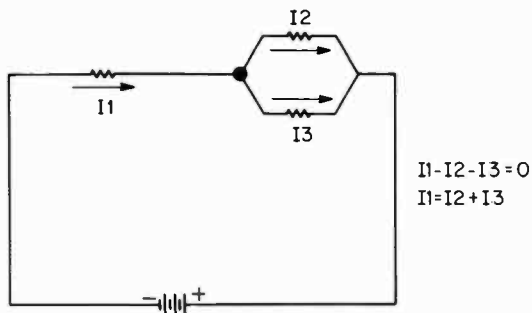


Fig. 1-18. The sum of the currents moving away from a junction is equal to the current flowing toward it.

sible, it isn't a practical circuit condition. We can change Fig. 1-17 so that it looks like Fig. 1-18. We now have:

$$I_1 = I_2 + I_3$$

If we put this into words it simply means that we have as much current flowing away from the junction (or meeting point of the three conductors) as we have flowing toward it. Obviously, if this were not the case, we would have an accumulation of current at the junction. What about the minus signs in front of I_2 and I_3 ? These indicate direction of current flow. If we use a plus sign to show current flowing from left to right, then a minus sign serves nicely to represent current moving from right to left. The transposition of I_2 and I_3 from the left side to the right side is an elementary algebraic operation.

TIME CONSTANTS

Combinations of resistors and capacitors, or resistors and coils (known as $R-C$ or $R-L$ circuits) can be used to control the time for a voltage or current to reach its peak value (see Fig. 1-19). The time, in seconds, required for the current or the voltage to reach 63.2 percent of its final value, is known as the time constant of the circuit.

For a series *R-L* circuit:

$$t = \frac{L}{R} \quad (1-34)$$

L is the total inductance in the circuit, in henrys; *R* is the total resistance, in ohms. The time constant, *t*, is the time required for the current to attain 63.2 percent of its ultimate peak amount.

For a series *R-C* circuit:

$$t = R \times C \quad (1-35)$$

R and *t* are the same as described for the series *R-L* circuit. *C* is the total capacitance in the circuit, in farads.

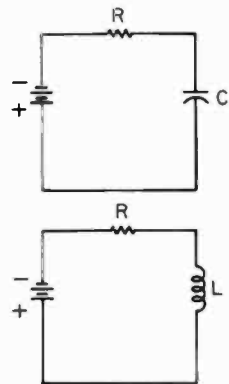


Fig. 1-19. *The charge and discharge of a capacitor through a resistor is not something that takes place instantaneously. Similarly, in a circuit involving a coil and a resistor, it takes a definite amount of time for a current to reach its maximum value.*

If, instead of charging through a resistor, a fully-charged capacitor is allowed to discharge through a resistor, the formula for the time constant in an *R-C* circuit would still apply. In this case, though, a time constant would be the time it takes for the capacitor to *lose* 63.2 percent of its full charge, or, to drop to 36.8 percent of its initial charge.

Generally, a capacitor is considered to be fully charged or fully discharged, after five time constants.

THE R-L CIRCUIT

The behavior of the *R-L* circuit (Fig. 1-19) is equally interesting. At the moment the circuit is closed, the current in the circuit is minimum, the voltage drop across the resistor is also minimum, while the induced voltage across the coil, *L*, is maximum.

As time moves forward (in fractions of a second), the voltage drop across the resistor increases, while the induced voltage goes down, both exponentially. Kirchhoff's voltage law (page 24) is applicable at

any instant since the voltage across the resistor and that across the coil must be equal to the applied emf.

At the end of five time constants, or more, the induced voltage is zero, the voltage drop across the resistor is equal to the battery voltage, the current is maximum, the magnetic field around the coil is maximum, but is not changing. This clearly illustrates that the induced emf across the coil is due to the *rate* of change of the current and not its amount.

The energy delivered to the resistor, because of the current flow, is dissipated by the resistor as heat. The energy delivered to the coil is stored in its magnetic field.

If, through some switching arrangement, the battery is disconnected and the coil is shunted across resistor R , the current flow curve will be exponential downward—that is, the current will be decreasing. Both the current and the voltage across the resistor will drop to 36.8 percent of their maximum amounts in L/R seconds.

Chapter 2

AC

One of the characteristics of a direct current (as the name implies) is its motion in one direction. Although this current is often of constant strength, it can also vary, depending on voltage changes in the circuit. But whether constant or changing (or pulsing) it is still unidirectional. A characteristic of a direct voltage is that it does not change its polarity. This is true, even if the voltage is a fluctuating one.

An alternating current is bidirectional. It will flow first in one direction, and then reverse and move in the other. An alternating voltage is one whose polarity changes.

WAVELENGTH AND FREQUENCY

The wave shown in Fig. 2-1 is a sine wave of current or voltage. This is a periodic type of wave, meaning that the current (or voltage)

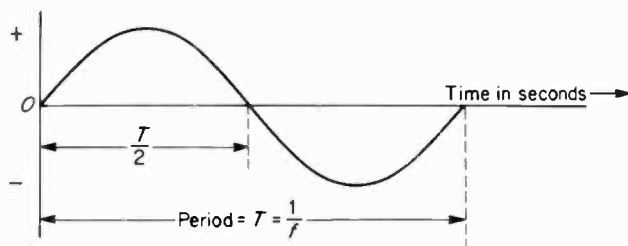


Fig. 2-1. This sine wave can represent either voltage or current.

changes its direction of flow at regular time intervals, and that the voltage assumes equal alternate positive and negative values. The length of a wave (or the wavelength) is the distance from the beginning of a single wave to its end. The wavelength is also the distance between successive positive peaks or successive negative peaks. The symbol for wavelength is the Greek letter lambda (λ).

The frequency of a periodic wave is the number of wavelengths per unit of time—generally taken as one second. As the number of waves per second increases, the length of the wave decreases. We can express this as an inverse relationship:

$$f = \frac{1}{\lambda} \text{ or } \lambda = \frac{1}{f} \quad (2-1)$$

All that this means is that frequency and wavelength act as opposites. When one increases, the other decreases. And vice versa.

We can convert frequency to wavelength or wavelength to frequency by using these formulas:

To change wavelength to frequency:

$$f \text{ (in kilocycles)} = \frac{3 \times 10^5}{\lambda \text{ (in meters)}} \quad (2-2)$$

$$f \text{ (in megacycles)} = \frac{3 \times 10^4}{\lambda \text{ (in centimeters)}}$$

$$f \text{ (in megacycles)} = \frac{984}{\lambda \text{ (in feet)}}$$

To change frequency to wavelength:

$$\lambda \text{ (in meters)} = \frac{3 \times 10^5}{f \text{ (in kilocycles)}} \quad (2-3)$$

$$\lambda \text{ (in centimeters)} = \frac{3 \times 10^4}{f \text{ (in megacycles)}}$$

$$\lambda \text{ (in feet)} = \frac{984}{f \text{ (in megacycles)}}$$

In these formulas, f is the frequency and λ is the wavelength. (Wavelength is usually expressed in meters, or in some multiple or submultiple of a meter.)

While wavelength is in meters, frequency can be in cycles, kilocycles (thousands of cycles) or megacycles (millions of cycles). While not always stated, frequency is always in terms of time units—that is,

kilocycles means kilocycles per second and megacycles means megacycles per second.

PERIOD

Frequency may also be regarded as the time duration of a number of waves. A wave having a frequency of 30 cps has 30 complete waves in one second. The time duration of a single cycle, or period, would be $1/30$ second. In terms of a formula, the period would be:

$$T = \frac{1}{f} \quad (2-4)$$

In this formula, T is in seconds and f is in cycles per second.

VELOCITY OF A WAVE

The distance covered by a wave in a certain amount of time is known as its velocity. That is:

$$\text{Velocity} = \frac{\text{Distance}}{\text{Time}}$$

We can write this much more conveniently in a formula, as:

$$V = \frac{D}{T} \quad V = V t$$

Defining the period as the time it takes a wave to travel a distance equal to its wavelength (λ), we can then make a substitution in the above formula and get:

$$V = \frac{\lambda}{T}$$

But we also know that $T = 1/f$. Making another substitution, we have:

$$V = \frac{\lambda}{1/f}$$

or

$$V = f \times \lambda \quad (2-5)$$

The velocity of a radio wave (or a light wave) in space is approximately 300,000,000 meters per second (3×10^8), or 186,000 miles per second, or 984 feet per microsecond. Note the use of these numbers in formulas 2-2 and 2-3.

angles from zero to 360° in 15-degree steps.

Table 2-1. Sines of angles in steps of 15°.

Angle, in degrees	Sine Value	Angle, in degrees	Sine Value
0	0.000	195	-0.259
15	0.259	210	-0.500
30	0.500	225	-0.707
45	0.707	240	-0.866
60	0.866	255	-0.966
75	0.966	270	-1.000
90	1.000	285	-0.966
105	0.966	300	-0.866
120	0.866	315	-0.707
135	0.707	330	-0.500
150	0.500	345	-0.259
165	0.259	360	0.000
180	0.000		

Note that the sine of the angle increases as the angle approaches 90 degrees. Values of the sine above 180° simply repeat values lower than 180°. Thus the sine of 195° is the same as the sine of 180° + 15°.

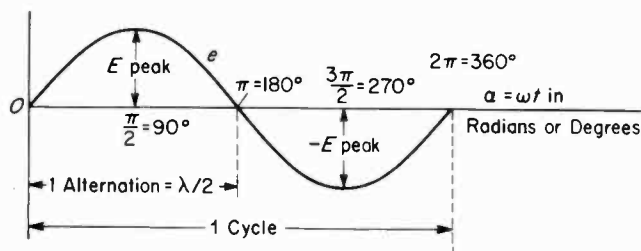


Fig. 2-3. The full length of a wave is the distance from start to finish of the wave. There are two peaks: one positive; one negative.

The base line in Fig. 2-3 is shown in angular degrees. We can select any angle we want and represent it by the letter α . Then:

$$\alpha = \omega t$$

We can substitute this in our formula for instantaneous values and get:

$$e = E_{\text{peak}} \sin \alpha$$

Fig. 2-4 shows two instantaneous values of voltage, e_1 and e_2 , selected at random. Note that for a particular sine wave, peak values

and average values are fixed. Instantaneous values are fixed only in

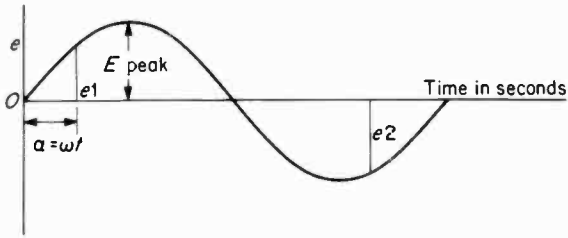


Fig. 2-4. Instantaneous values can be represented by any vertical line, such as e_1 or e_2 .

relationship to a particular instant of time. The same formula can be used for instantaneous values of current:

$$i = I_{\text{peak}} \sin \alpha$$

EFFECTIVE OR RMS VALUES OF A SINE WAVE OF VOLTAGE OR CURRENT

Measuring peak, average and instantaneous voltages or currents of an ac wave are simply attempts to measure a changing waveform. It is true that the peak and average values are fixed, but these are only

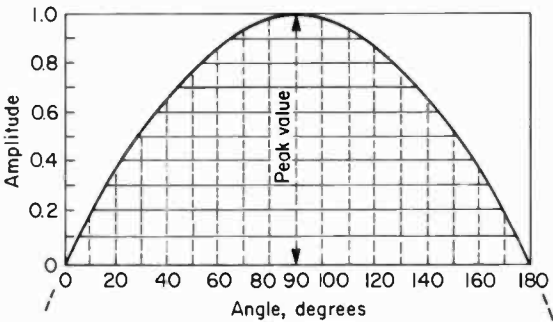


Fig. 2-5. The effective value of a sine wave of voltage or current is obtained from instantaneous values.

two points on the waveform, and while valuable, cannot be said to be truly representative of the entire wave. To get a more commonly used and much more representative value, we make a comparison between ac and dc. A direct current flowing through a resistor produces heat. So does an alternating current. The *effective value* of an alternating sine current or voltage is that value which will produce the same

amount of heat in a resistor as a direct voltage or current of the same numerical value.

Fig. 2-5 shows how we get the effective value. Each vertical line represents an instantaneous value of current. We take each of these values and square them. We add these squared values and then find the average value. The square root of this average value gives us the *effective* value. We also call this the RMS or root-mean-square value. RMS simply describes, in an abbreviated way, the steps we took to get the effective value from the instantaneous values. For any sine wave the effective value is:

$$I_{\text{effective}} = 0.707 \times I_{\text{peak}} \quad (2-11)$$

and

$$E_{\text{effective}} = 0.707 \times E_{\text{peak}}$$

If we assign a value of one (unity) to the effective value, then:

$$E_{\text{peak}} = \frac{1}{.707} = 1.414 E_{\text{effective}}$$

and, in the case of peak-to-peak values:

$$E_{\text{p-p}} = 2 \times 1.414 E_{\text{effective}} = 2.828 E_{\text{effective}}$$

(Note that 0.707 is the same as $\frac{1}{2} \sqrt{2}$ and $1.414 = \sqrt{2}$.)

RELATIONSHIPS

We now have four ways to measure or define the value of a sine wave of voltage or current. Table 2-2 summarizes the relationships between these values.

Table 2-2. Relationships between average, effective, peak and peak-to-peak (p-p) values of sine voltages or currents.

Given This Value	Multiply by this value to get			
	Average	Effective	Peak	P-P
Average	—	1.11	1.57	1.274
Effective	0.9	—	1.414	2.828
Peak	0.637	0.707	—	2.0
P-P	0.3185	0.3535	0.50	—

CAPACITORS

A capacitor is a device for storing an electrostatic charge and in its elementary form may consist of a pair of metal plates separated by a gas (such as air), a solid material (such as mica) or by space (vacuum). As in the case of resistors, capacitors come in a tremendous variety of sizes, shapes, construction and also like resistors, may be combined in parallel, in series, or in series-parallel.

The basic unit of capacitance is the farad. The farad is the unit used in electronic formulas, but since it is such a large unit, submultiples such as the microfarad (μf) and the micromicrofarad ($\mu\mu f$) are the units you will find in practice. The submultiple micromicrofarad is gradually giving way to a simpler term, the picofarad (pf).

MULTIPLES AND SUBMULTIPLES

Table 2-3 is a summary of the multiples and submultiples used in electronic formulas and suggested by the International Committee of Weights and Measurements and accepted by the U.S. National Bureau of Standards.

Table 2-3. Electronic prefixes, symbols and multiples

<i>Prefix</i>	<i>Symbol</i>	<i>Numerical Value</i>	<i>Exponential Value</i>
tera	<i>T</i>	1,000,000,000,000	10^{12}
giga	<i>G</i>	1,000,000,000	10^9
mega	<i>M</i>	1,000,000	10^6
kilo	<i>K</i>	1,000	10^3
hecto	<i>H</i>	100	10^2
deka	<i>dk</i>	10	10^1 or 10
deci	<i>d</i>	0.1	10^{-1}
centi	<i>c</i>	0.01	10^{-2}
milli	<i>m</i>	0.001	10^{-3}
micro	μ	0.000,001	10^{-6}
nano	<i>n</i>	0.000,000,001	10^{-9}
pico	<i>p</i>	0.000,000,000,001	10^{-12}

EXPONENTS

Table 2-3 shows that the numerical values of multiples and submultiples used in formulas have a tremendous range, covering the gamut from extremely small decimals to large whole numbers. Working with such numbers is awkward, time consuming and subject to error. Knowing how to use exponents is essential.

Table 2-4 shows how to convert from any one of these values to another.

	Pico—	Nano—	Micro—	Milli—	Centi—	Deci—	Units	Deka—	Hekto—	Kilo—	Myria—	Mega—	Giga—	Tera—
Pico—		0.001	10^{-6}	10^{-9}	10^{-10}	10^{-11}	10^{-12}	10^{-13}	10^{-14}	10^{-15}	10^{-16}	10^{-19}	10^{-21}	10^{-24}
Nano—	1000		0.001	10^{-5}	10^{-7}	10^{-4}	10^{-9}	10^{-10}	10^{-11}	10^{-12}	10^{-13}	10^{-15}	10^{-18}	10^{-21}
Micro—	10^6	1000		0.001	0.0001	10^{-5}	10^{-6}	10^{-7}	10^{-4}	10^{-9}	10^{-10}	10^{-12}	10^{-15}	10^{-18}
Milli—	10^9	10^6	1000		0.1	0.01	0.001	0.0001	10^{-5}	10^{-6}	10^{-7}	10^{-9}	10^{-12}	10^{-15}
Centi—	10^{10}	10^7	10,000	10		0.1	0.01	0.001	0.0001	10^{-5}	10^{-6}	10^{-9}	10^{-11}	10^{-14}
Deci—	10^{11}	10^8	10^5	100	10		0.1	0.01	0.001	0.0001	10^{-5}	10^{-7}	10^{-10}	10^{-13}
Units	10^{12}	10^9	10^6	1000	100	10		0.1	0.01	0.001	0.0001	10^{-6}	10^{-9}	10^{-12}
Deka—	10^{13}	10^{10}	10^7	10,000	1000	100	10		0.1	0.01	0.001	10^{-5}	10^{-8}	10^{-11}
Hekto—	10^{14}	10^{11}	10^8	10^5	10,000	1000	100	10		0.1	0.01	0.0001	10^{-7}	10^{-10}
Kilo—	10^{15}	10^{12}	10^9	10^6	10^3	10,000	1000	100	10		0.1	0.001	10^{-6}	10^{-9}
Myria—	10^{16}	10^{13}	10^{10}	10^7	10^4	10^1	10,000	1000	100	10		0.01	10^{-5}	10^{-8}
Mega—	10^{18}	10^{15}	10^{12}	10^9	10^6	10^3	10^6	10^5	10,000	1000	100		0.001	10^{-6}
Giga—	10^{21}	10^{18}	10^{15}	10^{12}	10^{11}	10^{10}	10^9	10^8	10^7	10^6	100		1000	0.001
Tera—	10^{24}	10^{21}	10^{18}	10^{15}	10^{14}	10^{13}	10^{12}	10^{11}	10^{10}	10^9	10^8	10^6	1000	

Table 2-4. Conversion factors for electronic multiples and submultiples.

CAPACITORS IN PARALLEL

The total capacitance of these components connected in shunt is

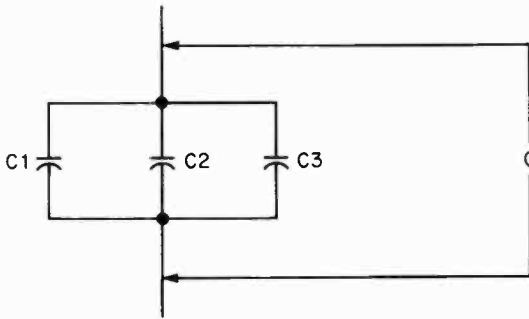


Fig. 2-6. *Capacitors in parallel or shunt.*

equal to the sum of the individual capacitances. See Fig. 2-6.

$$C = C1 + C2 + C3 \dots \quad (2-12)$$

Before using the formula, convert the capacitances to identical sub-multiples of a farad.

CAPACITORS IN SERIES

All of the formulas for resistors in parallel can be used for capacitors

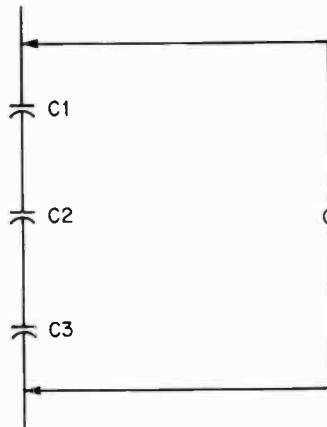


Fig. 2-7. *Capacitors in series. The total capacitance is always less than that of the smallest capacitor.*

in series. (See Fig. 2-7) Simply substitute the symbol C for R .

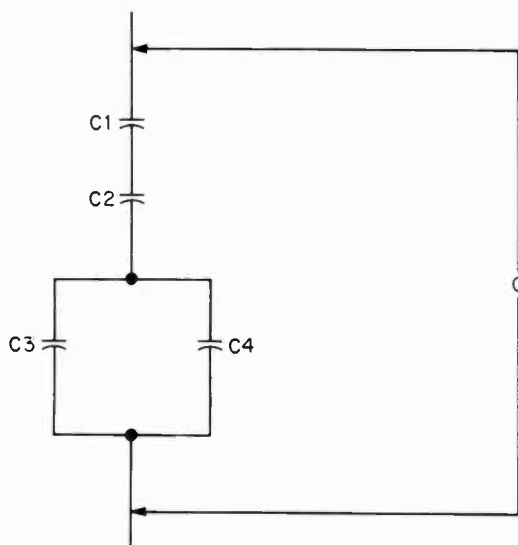


Fig. 2-8. *Series-parallel network. The parallel capacitances, C_3 and C_4 , are added, forming an equivalent single capacitor which is then considered in series with C_1 and C_2 .*

For two capacitors in series:

$$C = \frac{C_1 \times C_2}{C_1 + C_2} \quad (2-13)$$

For any number of capacitors in series:

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \dots \quad (2-14)$$

It is often convenient to change all capacitances to the basic unit, the farad, before using these formulas. This need not be done, but the capacitances must be in the same submultiples.

Formulas are seemingly permissive, that is, having a variety of capacitors on hand we can apparently use any combination to get a desired amount of capacitance. But the formulas for series and parallel capacitors are concerned solely with how capacitors may be connected to get a particular value. The formulas assume perfect capacitors, identical in all respects except capacitance. From a practical viewpoint we may also need to consider working voltage, leakage, tolerance, temperature coefficient, physical size, cost, availability.

CAPACITORS IN SERIES-PARALLEL

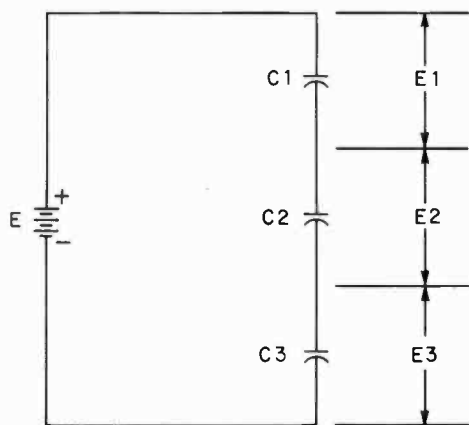


Fig. 2-9. *Capacitors used as a voltage divider in a dc circuit.*

This is just a combination of the formulas for capacitors in series and in parallel. See Fig. 2-8.

$$C = C_1 + C_2 + \frac{C_3 \times C_4}{C_3 + C_4}$$

CHARGE OF A CAPACITOR

The electric charge of a capacitor in coulombs (Q) is:

$$Q = C \times E \quad (2-15)$$

In this formula, E is the voltage across the capacitor and C is the capacitance in farads. A coulomb is an electrical charge and a single coulomb represents the electric charge of 6.28×10^{18} electrons. A flow past a given point of one coulomb per second is an ampere.

ENERGY STORED IN A CAPACITOR

In the following formula, the energy, W , is given in joules. A joule is the energy used in passing one coulomb through a resistance of 1 ohm.

$$W = \frac{1}{2} C \times E^2 \quad (2-16)$$

C is the capacitance in farads and E is the voltage across the capacitor.

WORKING VOLTAGE OF A CAPACITOR

While sine wave ac voltages are often designated in terms of their effective or RMS values, the working voltage of a capacitor is the peak or maximum. Thus:

$$E_{\text{working}} = E_{\text{rms}} \times 1.414 \quad (2-17)$$

This formula is obtained from Table 2-2, given earlier.

CAPACITORS AS VOLTAGE DIVIDERS

Like resistors, capacitors can be used as voltage dividers in ac or dc circuits. Fig. 2-9 shows three capacitors in a voltage divider arrangement. The applied voltage (or source voltage) is distributed among the capacitors in inverse proportion to their capacitance. That is, the largest amount of voltage will be across the unit having the smallest capacitance. For each of the capacitors shown in Fig. 2-9:

$$E_1 = \frac{\text{total capacitance}}{C_1} \times \text{applied voltage}$$

$$E_2 = \frac{\text{total capacitance}}{C_2} \times \text{applied voltage}$$

$$E_3 = \frac{\text{total capacitance}}{C_3} \times \text{applied voltage}$$

$$E \text{ (applied voltage)} = E_1 + E_2 + E_3$$

CAPACITIVE REACTANCE

Capacitive reactance is conveniently regarded as opposition to the flow of alternating current. For a non-varying direct current the opposition to current flow is infinite and the capacitor can be viewed as an open circuit. The opposition of a capacitor to a pulsating direct current or to an alternating current is measured in ohms. The formula is given as:

$$X_c = \frac{1}{2\pi \times f \times C} \quad (2-18)$$

In this formula, f is the frequency in cycles per second and C the capacitance in farads. This formula may also be written as:

$$X_c = \frac{159.2}{f \times C}$$

Here the frequency is in kilocycles per second and the capacitance is in microfarads. The same formula may be used where the frequency is in megacycles and C is in millimicrofarads (thousandths of a microfarad). 1 millimicrofarad = 0.001 μf . On occasion you may see a minus sign preceding the right-hand side of the above formulas. The negative sign simply means that this type of reactance always opposes another type of reactance known as inductive reactance.

OHM'S LAW FOR A CAPACITIVE CIRCUIT

Although reactance and resistance have the same basic unit—the ohm—they are not the same. Resistance does not store electrical energy. In the resistor, electrical energy is changed to heat energy which is then given off or dissipated. A capacitor stores electrical energy—receives it during one part of the ac cycle, returns it during the next. However, we can use capacitive reactance in an Ohm's law formula:

$$E_c = I \times X_c \quad (2-19)$$

The voltage across a capacitor (E_c) is equal to the alternating current multiplied by the capacitive reactance. The voltage is in volts, the current in amperes, and the reactance in ohms. And, like Ohm's law for resistive circuits, the formula can be rearranged to read:

$$I = E_c / X_c$$

and

$$X_c = E_c / I$$

IMPEDANCE OF AN R-C CIRCUIT

In a series R - C circuit (see Fig. 2-10) the total opposition to the

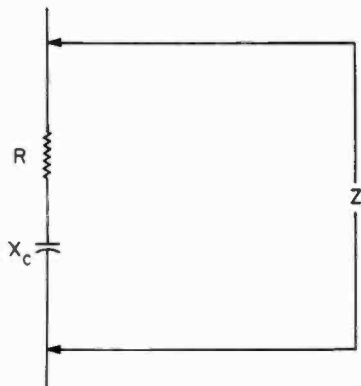


Fig. 2-10. Series R - C circuit. The impedance is the vector sum of the resistance and the capacitive reactance.

flow of current, consisting of the resistance of the resistor and the reactance of the capacitor, is known as impedance. Impedance is represented by the letter Z and is always in ohms. The addition of the resistance and capacitive reactance is done vectorially.

$$Z = \sqrt{R^2 + X_c^2} \quad (2-20)$$

VOLTAGES IN A SERIES R-C CIRCUIT

Whether ac or dc (Fig. 2-11) the current flowing in a series R-C

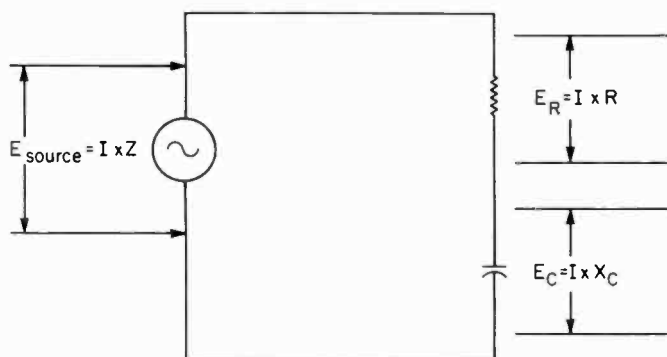


Fig. 2-11. Voltage distribution in a series R-C circuit. The source voltage is equal to the vector sum of the voltages across the resistor and capacitor.

circuit is the same in all parts of the circuit. If we multiply each of the terms in the formula by I (representing the current in the circuit) we will have:

$$IZ = \sqrt{I^2R^2 + I^2X_c^2} \text{ or } E_{\text{source}} = \sqrt{E_R^2 + E_C^2} \quad (2-21)$$

What do these terms signify? IZ is the generator or source voltage. That is:

$$E = I \times Z \quad (2-22)$$

By transposing, we can obtain two other forms of this formula:

$$I = E/Z$$

and

$$Z = E/I$$

INDUCTORS (COILS)

Like resistors and capacitors, inductors can be connected in series,

in parallel and in series-parallel. However, with inductors there is an additional factor to consider—the magnetic field surrounding the coil. The magnetic fields around two or more inductors can act to aid or oppose each other. Inductors can be mounted sufficiently far apart, or at right angles or covered completely on all sides by some shielding material so that the magnetic fields can be ignored.

Like a capacitor, an inductor stores electrical energy—receives it during one part of the ac cycle, returns it during the next. Neither capacitors nor inductors are perfect—that is, they may be considered as having some resistive component which does use or dissipate a small part of the electrical energy.

The basic unit of capacitance is the henry. Submultiples are the millihenry (thousandth of a henry, *mh*) and the microhenry (millionth of a henry, μh).

INDUCTORS IN SERIES

For inductors in series (no magnetic interaction):

$$L = L_1 + L_2 + L_3 \dots \dots \quad (2-23)$$

INDUCTORS IN PARALLEL

For inductors in parallel (no magnetic interaction)

$$L = \frac{L_1 \times L_2}{L_1 + L_2} \quad \text{for two coils} \quad (2-24)$$

$$L = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} \dots \dots} \quad \text{for three or more coils} \quad (2-25)$$

Note that formulas for inductors having no magnetic field interaction are the same as for resistors in series or parallel.

COEFFICIENT OF COUPLING AND MUTUAL INDUCTANCE

The inductance of a coil (more properly called self-inductance) is that property of a coil which causes a voltage to be produced across it when the current through the coil is changed. But a coil can have a voltage induced across it, not because of its own varying current, but because of the changing current in some adjacent coil. This property is called mutual inductance, and like self-inductance, is measured in henrys.

The magnetic fields between a pair of coils may aid each other, or

oppose each other, depending on their relative polarities (Fig. 2-12). If they aid, the mutual inductance is added to the self inductance of the

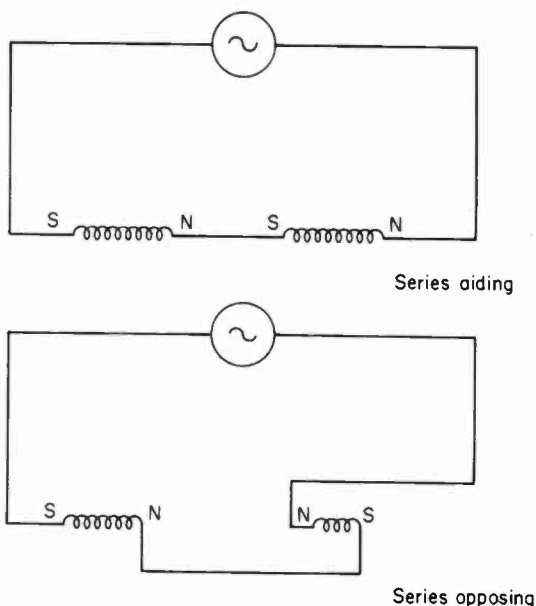


Fig. 2-12. If coils are coupled so that their magnetic fields interact, the overall inductance is dependent upon the coupling arrangement. In the upper drawing, the current flows in the same direction through each coil; the magnetic fields reinforce each other. In the lower circuit, they oppose.

coils. If they oppose, the total self inductance is reduced by the mutual inductance.

The mutual inductance depends upon how closely the coils are coupled and upon the self inductance of the coils. The coefficient of coupling is a measure of how substantially the magnetic flux of one coil links with the turns of an adjacent coil. 100% linkage is known as unity coupling and while it is not reached because there is always some leakage flux, values close to unity coefficient of coupling are often reached.

The mutual inductance of two coils can be calculated from:

$$M = k\sqrt{L_1 \times L_2} \quad (2-26)$$

k is the coefficient of coupling and is a decimal. L_1 and L_2 represent the self inductance (in henrys or some submultiple) of two coils.

The formula for mutual inductance can easily be rearranged to supply the coefficient of coupling:

$$k = \frac{M}{\sqrt{L_1 \times L_2}}$$

INDUCTORS IN SERIES AIDING

Where the mutual inductance aids the total inductance of two coils connected in series:

$$L = L_1 + L_2 + 2M \quad (2-27)$$

L is the total inductance; L_1 and L_2 are the two coils and M is the

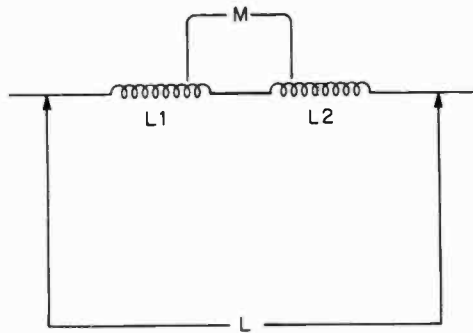


Fig. 2-13. Mutual inductance refers to the electromagnetic linkage between coils.

mutual inductance existing between them. See Fig. 2-13.

INDUCTORS IN SERIES OPPOSING

Where two coils are connected in series and are magnetically coupled but with magnetic fields opposing each other, the total inductance is:

$$L = L_1 + L_2 - 2M \quad (2-28)$$

INDUCTORS IN PARALLEL AIDING

For two coupled coils in shunt, with magnetic fields aiding:

$$L = \frac{1}{\frac{1}{L_1 + M} + \frac{1}{L_2 + M}} \quad (2-29)$$

INDUCTORS IN PARALLEL OPPOSING

For two coupled coils in shunt, with magnetic fields opposing:

$$L = \frac{1}{\frac{1}{L_1 - M} + \frac{1}{L_2 - M}} \quad (2-30)$$

REACTANCE OF AN INDUCTOR

The inductance of a coil opposes the flow of a varying current through it. This opposition is known as inductive reactance, and like its counterpart, capacitive reactance, is measured in ohms:

$$X_L = 2\pi f \times L \quad (2-31)$$

X_L is the inductive reactance in ohms, 2π equals 6.28, f is the frequency in cycles per second and L is the inductance of the coil in henrys. When ω is used to represent $2\pi f$ (as indicated earlier) the formula simplifies to:

$$X_L = \omega L$$

Note that inductive reactance varies directly with frequency while capacitive reactance varies inversely.

The reactance of a coil is a function of frequency. However, a coil will also have a certain amount of dc resistance, depending on the number of turns, gauge of the wire, resistance of the solder joints at the terminals of the coil, and, in the case of stranded wire, the number of broken strands. Whether a coil will be effective in a circuit is often dependent on how successfully these factors have been considered or kept under control.

OHM'S LAW FOR AN INDUCTIVE CIRCUIT

Inductive reactance, measured in ohms, can be substituted directly into the Ohm's law formula:

$$E_L = I \times X_L \quad (2-32)$$

The voltage across a coil is equal to the alternating current through it multiplied by the inductive reactance. To find the current through the coil, we can rearrange the formula to read:

$$I = E_L / X_L$$

and

$$X_L = E_L / I$$

IMPEDANCE IN AN R-L CIRCUIT

In a series R - L circuit, the total opposition to the flow of current,

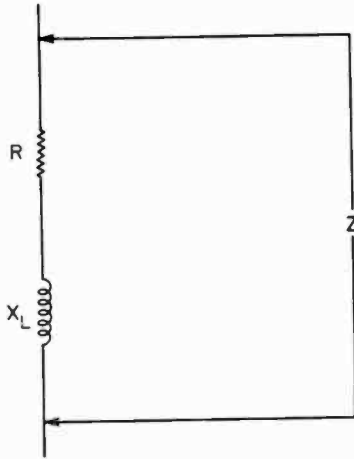


Fig. 2-14. Series R - L circuit. The impedance is the vector sum of the resistance and inductive reactance.

known as the impedance, is the vector sum of the resistance and the inductive reactance. See Fig. 2-14.

$$Z = \sqrt{R^2 + X_L^2} \quad (2-33)$$

In this formula, all units are in ohms.

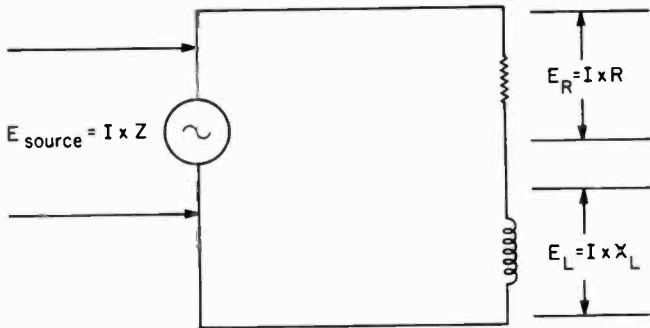


Fig. 2-15. The source voltage in this series R - L circuit is equal to the vector sum of the voltages across the resistor and the coil.

VOLTAGES IN A SERIES R-L CIRCUIT

Since the current is the same in all parts of a series R - L circuit, we can multiply each of the terms in the formula and get:

$$\begin{aligned} \text{or } IZ &= \sqrt{I^2R^2 + I^2X_L^2} \\ E_{\text{source}} &= \sqrt{E_R^2 + E_L^2} \end{aligned} \quad (2-34)$$

Since the resistance and reactance are added vectorially, the voltages involved as a result of these components are also added vectorially. See Fig. 2-15.

EFFECTIVE RESISTANCE

The resistance of a coil as measured with an ohmmeter, is its dc resistance—that is, this is the resistance the coil would have to the flow of an unvarying direct current. For an alternating current, the resistance (known as effective or ac resistance) will not only be due to the inherent dc resistance but will be somewhat higher because of such factors as hysteresis loss, eddy currents, magnetic skin effect. The effective resistance acts like a resistor in series with the coil.

Q OF A COIL

It is frequently desirable to make coils having as low an effective resistance as possible. The ratio of the inductive reactance of a coil to its effective resistance is known as the figure of merit or quality of the coil (Q). Stated as a formula, we have:

$$Q = \frac{X_L}{R} \text{ or } Q = \frac{\omega L}{R} \quad (2-35)$$

R is considered as being in series with the coil.

Q OF A CAPACITOR

The Q of a capacitor is the ratio of its reactance to its effective resistance. Expressed as a formula:

$$Q = \frac{X_c}{R}$$

In an L - C circuit, we are usually concerned only with the Q of the coil, since the Q of the capacitor is ordinarily much higher. However, if the dielectric of the capacitor is such that there are losses in it, power will be dissipated in the dielectric and the capacitor will have a large effective resistance, lowering the Q .

VOLTAGE TRANSFORMERS, STEP UP AND STEP DOWN

The ratio of secondary turns (N_s) to the primary turns (N_p) of a transformer is known as the turns ratio. The voltage step up or step

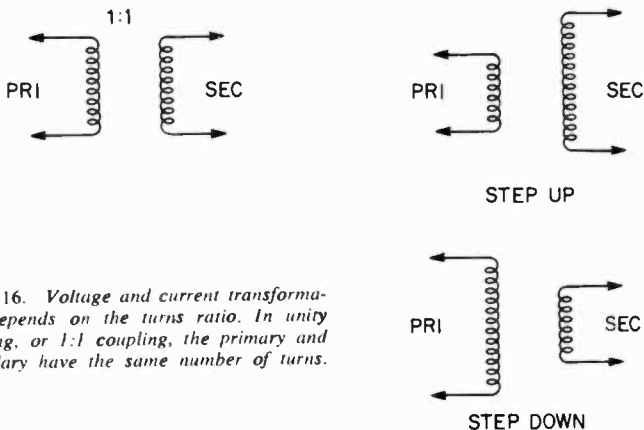


Fig. 2-16. Voltage and current transformation depends on the turns ratio. In unity coupling, or 1:1 coupling, the primary and secondary have the same number of turns.

down (Fig. 2-16) of a transformer depends on this turns ratio.

$$\frac{E_s}{E_p} = \frac{N_s}{N_p}$$

E_p is the primary voltage; E_s the secondary voltage; N_p the number of primary turns; N_s the number of secondary turns. A formula of this type can be arranged in six different ways (including the one shown).

$$E_p \times N_s = N_p \times E_s \quad (2-36)$$

$$E_p = \frac{N_p \times E_s}{N_s}$$

$$E_s = \frac{E_p \times N_s}{N_p}$$

$$N_s = \frac{N_p \times E_s}{E_p}$$

$$N_p = \frac{E_p \times N_s}{E_s}$$

If information concerning the turns ratio is known, the actual number of primary and secondary turns isn't required. Thus:

$$E_s = \text{turns ratio} \times E_p \quad (2-37)$$

CURRENT TRANSFORMERS, STEP UP AND STEP DOWN

In transformers, the effects on current and voltage are inverse. A transformer will step down current by the same ratio that it steps up voltage.

$$\frac{I_p}{I_s} = \frac{N_s}{N_p} \quad (2-38)$$

I_p and I_s represent primary and secondary currents. The current formula can be rearranged in the same manner as the voltage formula, and in as many different ways. As in the case of voltage transformation, N_s/N_p is the turns ratio.

IMPEDANCE TRANSFORMERS

The ratio of secondary to primary impedance of a transformer varies as the square of the turns ratio.

$$\frac{Z_s}{Z_p} = \frac{N_s^2}{N_p^2} \quad (2-39)$$

POWER TRANSFORMER COLOR CODE

Primary (not tapped)	two black leads
Primary (tapped)	black (common) black-red black-yellow (tap)
Secondary (high voltage)	red red red-yellow (tap)
Secondary (rectifier filament)	yellow yellow yellow-blue (tap)
Secondary (amplifier filament)	green green green-yellow (tap)
Secondary (amplifier filament)	brown brown brown-yellow (tap)
Secondary (amplifier filament)	slate slate slate-yellow (tap)

In power transformers (Fig. 2-17) a tapped lead always has two colors and yellow is always one of these colors.

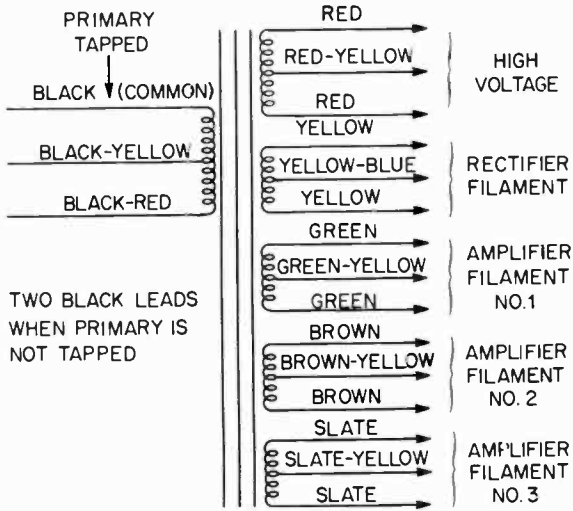


Fig. 2-17. Color code for power transformers.

I.F. TRANSFORMER COLOR CODE

See Fig. 2-18.

- | | |
|--|-------------------|
| Primary (plate) | blue |
| Primary (B-plus) | red |
| Secondary (grid or diode) | green |
| Secondary (grid or diode return, AVC, or ground) | black |
| Secondary (full-wave diode) | green-black (tap) |

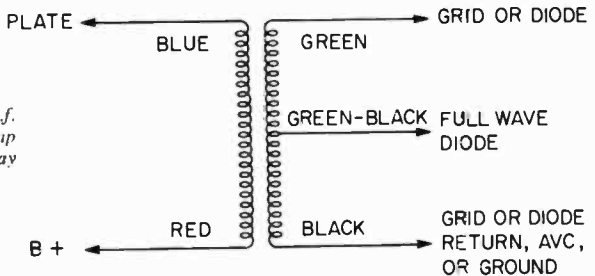


Fig. 2-18. Color code for i.f. transformers. The center tap on the secondary may or may not be included.

AUDIO and OUTPUT TRANSFORMER COLOR CODE (single ended)

See Fig. 2-19.


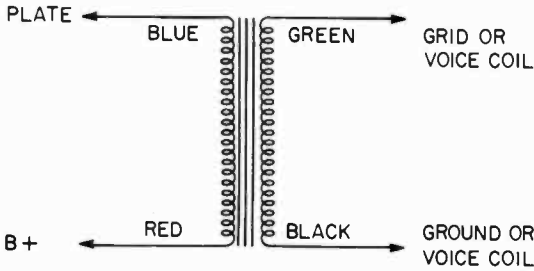


Fig. 2-19. Color code for audio transformers. They may be step up or step down, depending on use.

Primary (plate)	blue
Primary (B plus)	red
Secondary (grid or voice coil)	green
Secondary (ground or voice coil)	black

AUDIO and OUTPUT TRANSFORMER COLOR CODE (pushpull)

See Fig. 2-20.

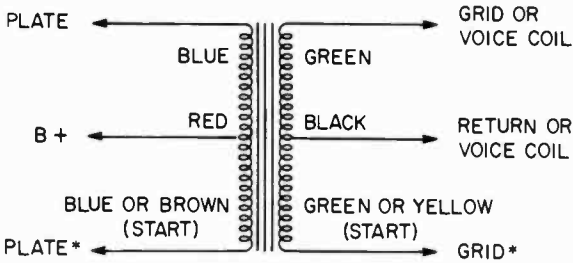

*FOUND ONLY ON PUSH-PULL PRIMARY OR SECONDARY WINDINGS

Fig. 2-20. Color code for pushpull audio transformers.

Primary (plate)	blue
Primary (B plus)	red (tap)
Primary (plate)	blue or brown
Secondary (grid or voice coil)	green
Secondary (grid return or voice coil)	black
Secondary (grid)	green or yellow

PHASE ANGLE

A pair of voltages, a voltage and a current, or a pair of currents need not necessarily be in step with each other. (These voltages and currents are all ac.) And, since we are talking about a periodic waveform such as a sine wave, we can conveniently measure their relationships between the points at which they cross the X-axis. An example is shown in Fig. 2-21.

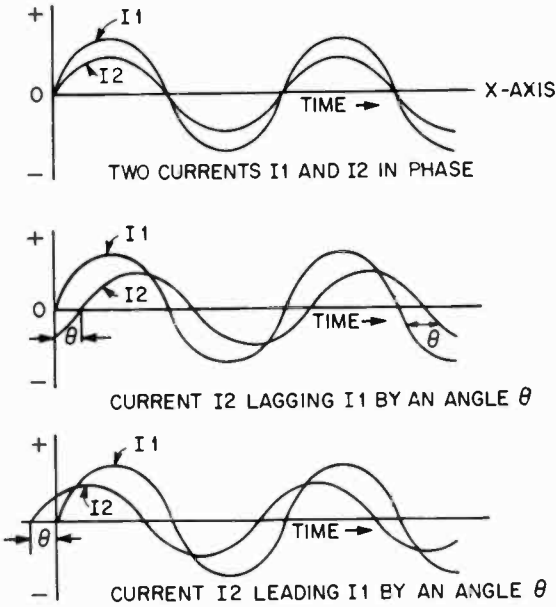


Fig. 2-21. A pair of alternating currents may be in step or phase, or one current may lead or lag the other.

One voltage may lead or lag another voltage. Similarly, one current may lead or lag another current. More commonly, we are concerned with whether a particular voltage leads or lags a current. The amount of lead (or lag) is measured in degrees along the X-axis and is referred to as the phase angle. It is most usually designated by the Greek letter θ .

Whether a voltage will lead or lag a current will depend upon the amount of capacitance and/or inductance in the circuit.

Out of phase voltages (or out of phase currents) can be added vectorially to produce a resultant voltage or current.

PHASE ANGLE IN RESISTIVE CIRCUITS

For a resistive circuit consisting of a single resistor (Fig. 2-22), a number of resistors in series, in parallel, or in a series-parallel combi-

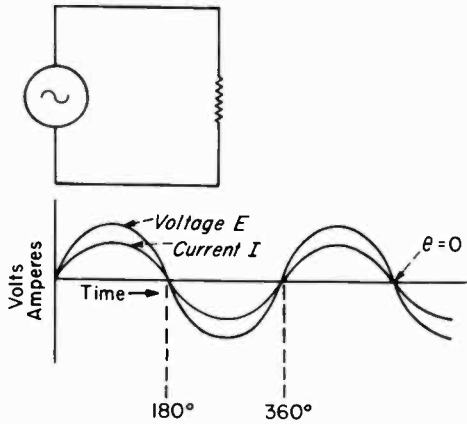


Fig. 2-22. In a resistive circuit, the voltage and current are in phase.

nation, the voltage and current are always in step, rise and fall at the same time, and are said to be in phase. Thus,

$$\theta = 0^\circ$$

PHASE ANGLE IN INDUCTIVE CIRCUITS

For an inductive circuit, consisting of a single or any combination

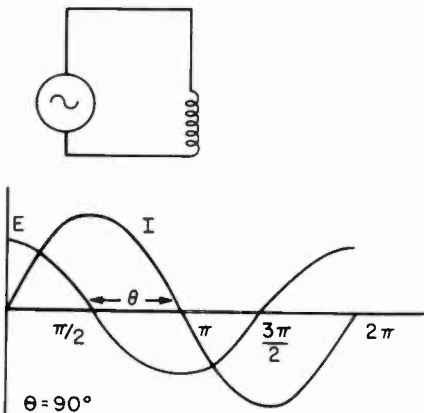


Fig. 2-23. In an inductive circuit, the current may lag the voltage by as much as 90 degrees. The amount of lag decreases as the resistance in the circuit increases.

of inductors, the current lags the voltage by a maximum of 90° . Thus,

$$\theta = +90^\circ$$

If the inductor contains resistance, and in practice it always does, then the phase angle is less than 90° , depending upon the amount of resistance compared to inductive reactance. (Fig. 2-23)

PHASE ANGLE IN CAPACITIVE CIRCUITS

In a capacitive circuit, consisting of any combination of capacitors, the current leads the voltage by a maximum of 90° . Thus:

$$\theta = -90^\circ$$

The plus and minus signs preceding the phase angles may be omitted. They are just convenient reminders that inductors and capacitors have directly opposite effects in ac circuits.

Depending upon the resistance inherent in a particular type of capacitor, the phase angle may be somewhat less than 90° .

PHASE ANGLE OF A SERIES R-L CIRCUIT

For a circuit (see Fig. 2-24) consisting of an inductor in series

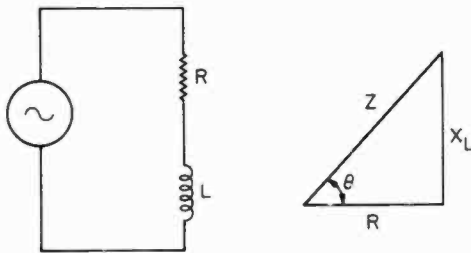


Fig. 2-24. The phase angle depends on the ratio of inductive reactance to resistance. As the reactance is reduced, the phase angle becomes smaller.

with a resistor, the phase angle:

$$\theta = \text{arc tan } \frac{X_L}{R} \quad (2-40)$$

(read this as "theta is the angle whose tangent is X_L divided by R ").

PHASE ANGLE OF A SERIES R-C CIRCUIT

For a circuit (see Fig. 2-25) consisting of a capacitor in series with

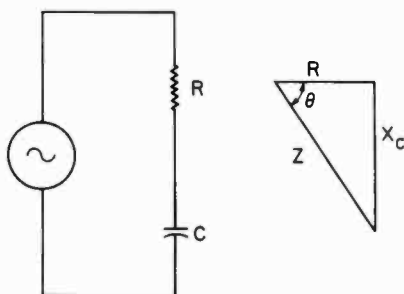


Fig. 2-25. The phase angle depends on the ratio of capacitive reactance to resistance. Note the triangle is drawn upside-down (compare with Fig. 2-24) emphasizing that inductive and capacitive reactance are opposing vectors.

a resistor, the phase angle:

$$\theta = \text{arc tan } \frac{X_c}{R} \quad (2-41)$$

IMPEDANCE AND PHASE ANGLE OF A SERIES L-C CIRCUIT

$$Z = X_L - X_c \quad \theta = +90^\circ$$

or

$$Z = X_c - X_L \quad \theta = -90^\circ$$

Either formula may apply, depending on which reactance is larger. Simply subtract the smaller reactance from the larger. In this circuit the resistance is so small compared to the reactances that it may be disregarded. Impedance, resistance, inductive and capacitive reactance are always in ohms.

IMPEDANCE AND PHASE ANGLE OF A SERIES R-L-C CIRCUIT

When the resistance is a factor that must be considered, then the impedance (Fig. 2-26):


$$\text{(if } X_L \text{ is larger than } X_c) \quad Z = \sqrt{R^2 + (X_L - X_c)^2} \quad (2-42)$$

$$\theta = \text{arc tan } \frac{X_L - X_c}{R}$$


(if X_c is larger than X_l) $Z = \sqrt{R^2 + (X_c - X_l)^2}$ (2-43)

$$\theta = \arctan \frac{X_c - X_l}{R}$$

$$X_L > X_C$$

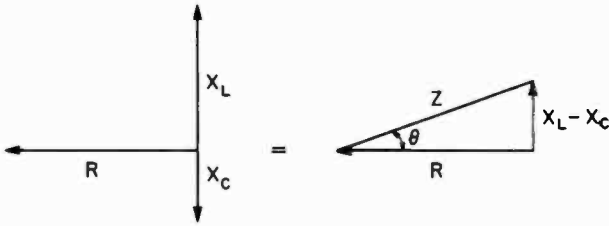

$$X_L < X_C$$

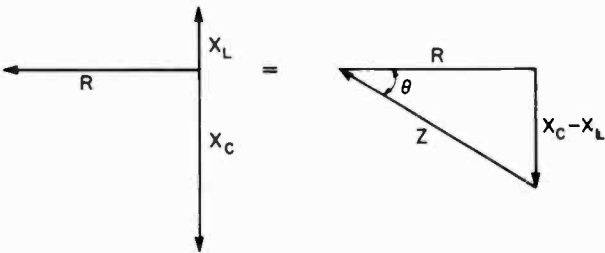

$$X_L = X_C$$

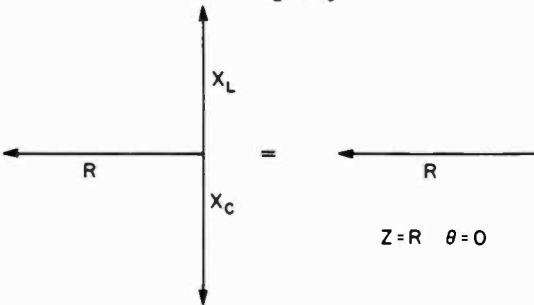


Fig. 2-26. Various conditions that may exist in a series R-L-C circuit.

If the inductive and capacitive reactances are equal, we have a condition of resonance and:

$$Z = R \text{ and } \theta = 0$$

IMPEDANCE AND PHASE ANGLE OF A PARALLEL R-L CIRCUIT

(Fig. 2-27)

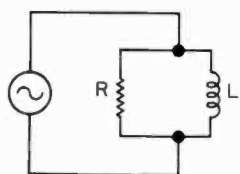


Fig. 2-27. In a parallel R-L circuit, the phase angle is determined by the ratio of resistance to inductive reactance.

$$Z = \frac{R \times X_L}{\sqrt{R^2 + X_L^2}} \quad (2-44)$$

$$\theta = \text{arc tan } \frac{R}{X_L}$$

IMPEDANCE AND PHASE ANGLE OF A PARALLEL R-C CIRCUIT

(Fig. 2-28)

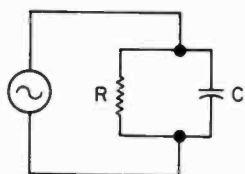


Fig. 2-28. In this circuit, as in the parallel R-L circuit, the impedance is determined by the frequency.

$$Z = \frac{R \times X_c}{\sqrt{R^2 + X_c^2}} \quad (2-45)$$

$$\theta = -\text{arc tan } \frac{R}{X_c}$$

IMPEDANCE AND PHASE ANGLE OF PARALLEL L-C CIRCUIT

(Fig. 2-29)

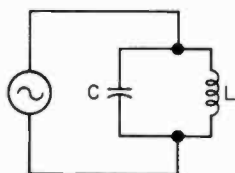


Fig. 2-29. In a parallel L-C circuit, the impedance is maximum at resonance.

When X_L is larger than X_c

$$Z = \frac{X_L \times X_c}{X_L - X_c} \quad (2-46)$$

When X_c is larger than X_L


$$Z = \frac{X_c \times X_L}{X_c - X_L} \quad (2-47)$$

At resonance, $X_L = X_c$ and the denominator becomes zero. The impedance reaches an extremely large value. At resonance the phase angle is zero.

IMPEDANCE AND PHASE ANGLE OF A PARALLEL R-L-C CIRCUIT

(Fig. 2-30)

Fig. 2-30. Parallel R-L-C circuit.

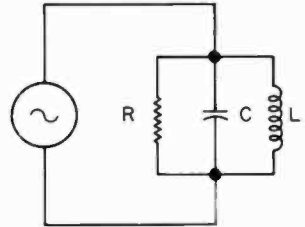


$$Z = \frac{R \times X_L \times X_c}{\sqrt{X_L^2 \times X_c^2 + R(X_L - X_c)^2}} \quad (2-48)$$

$$\theta = \text{arc tan} \frac{R(X_c - X_L)}{X_L \times X_c}$$

IMPEDANCE AND PHASE ANGLE OF SERIES R-L SHUNTED BY R

(Fig. 2-31)

Fig. 2-31. Series R-L circuit shunted by a resistor.

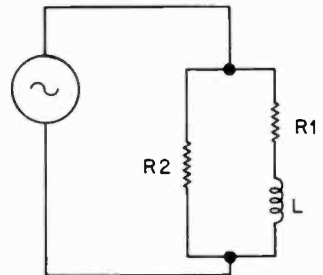

$$Z = R_2 \sqrt{\frac{R_1^2 + X_L^2}{(R_1 + R_2)^2 + X_L^2}} \quad (2-49)$$

$$\theta = \text{arc tan} \frac{X_L R_2}{R_1^2 + X_L^2 + R_1 R_2}$$

IMPEDANCE AND PHASE ANGLE OF SERIES R-L SHUNTED BY C

(Fig. 2-32)

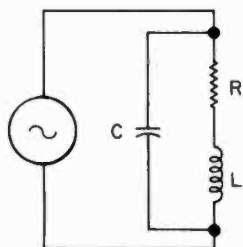


Fig. 2-32. Series R-L circuit shunted by a capacitor.

$$Z = X_c \sqrt{\frac{R^2 + X_L^2}{R^2 + (X_L - X_c)^2}} \quad (2-50)$$

$$\theta = \text{arc tan} \frac{X_L (X_c - X_L) - R^2}{R X_c}$$

REACTANCE/RESISTANCE RATIO

The tangent of an angle (theta) is the altitude (reactance) divided by the base (resistance). Thus, the tangent is a ratio—the ratio of reactance to resistance. This ratio determines the magnitude of the phase angle. With increasing values of reactance, the phase angle increases. The table at the top of page 63 gives this ratio (tangent) for phase angles ranging from zero to 89 degrees.

ADMITTANCE OF A SERIES CIRCUIT

Admittance is the reciprocal of impedance. Since impedance is measured in ohms, admittance is in mhos.

$$Y = \frac{1}{Z} \quad (2-51)$$

but since Z is $\sqrt{R^2 + X^2}$, then:

$$Y = \frac{1}{\sqrt{R^2 + X^2}} \quad (2-52)$$

The ratio $\tan X/R$ and corresponding values of phase angle, θ .

<i>Phase Angle (in degrees)</i>	<i>Ratio</i>	<i>Phase Angle (in degrees)</i>	<i>Ratio</i>	<i>Phase Angle (in degrees)</i>	<i>Ratio</i>
0	0.0000	30	0.5774	60	1.7321
1	0.0175	31	0.6009	61	1.8040
2	0.0349	32	0.6249	62	1.8807
3	0.0524	33	0.6494	63	1.9626
4	0.0699	34	0.6745	64	2.0503
5	0.0875	35	0.7002	65	2.1445
6	0.1051	36	0.7265	66	2.2460
7	0.1228	37	0.7536	67	2.3559
8	0.1405	38	0.7813	68	2.4751
9	0.1584	39	0.8098	69	2.6051
10	0.1763	40	0.8391	70	2.7475
11	0.1944	41	0.8693	71	2.9042
12	0.2126	42	0.9004	72	3.0777
13	0.2309	43	0.9325	73	3.2709
14	0.2493	44	0.9657	74	3.4874
15	0.2679	45	1.0000	75	3.7321
16	0.2867	46	1.0355	76	4.0108
17	0.3057	47	1.0724	77	4.3315
18	0.3249	48	1.1106	78	4.7046
19	0.3443	49	1.1504	79	5.1446
20	0.3640	50	1.1918	80	5.6713
21	0.3839	51	1.2349	81	6.3138
22	0.4040	52	1.2799	82	7.1154
23	0.4245	53	1.3270	83	8.1443
24	0.4452	54	1.3764	84	9.5144
25	0.4663	55	1.4281	85	11.43
26	0.4877	56	1.4826	86	14.30
27	0.5095	57	1.5399	87	19.08
28	0.5317	58	1.6003	88	28.64
29	0.5543	59	1.6643	89	57.29

SUSCEPTANCE

Susceptance is the reciprocal of reactance, and is given in mhos. Just as we can have resistive ohms (due to a resistor) and reactive ohms (due to a coil or capacitor) so too do we have resistive and reactive mhos. In a series circuit, the susceptance is:

$$B = \frac{X}{R^2 + X^2} \quad (2-53)$$

B is the susceptance in mhos, R is resistive ohms, and X is reactive ohms. The reactive component may be either a coil or a capacitor.

We usually consider inductive reactance as positive and capacitive reactance as negative. These polarities are purely conventional and indicate the 180° out-of-phase relationships of these units. But since

Multiplying apparent power ($E \times I$) by the cosine of the phase angle will produce a number representing the true power in the circuit, or; $P = E \times I \times \cos \theta$. This can also be written as:

$$\text{True power (P)} = E \times I \times \cos \frac{R}{Z} \quad (2-59)$$

POWER FACTOR

The ratio between the true power and the apparent power is a value less than one since the true power is always less than the apparent power. This ratio is referred to as the power factor and is often abbreviated as *pf*. Stated as a formula we have:

$$pf = \frac{E \times I \times \cos \theta}{E \times I} \quad (2-60)$$

or

$$pf = \cos \theta = \cos \frac{R}{Z}$$

In ac circuits where power factor is not a consideration (such as in a purely resistive circuit) the formula for power is identical with that used in dc.

$$P = I^2 \times R$$

$$I = \sqrt{\frac{P}{R}}$$

Where the relationship between voltage and current (the phase angle) is a factor, Ohm's law for ac circuits can take a variety of forms. These can be expressed in terms of power, current, voltage or impedance.

POWER

$$P = I^2 Z \cos \theta$$

$$P = \frac{E^2 \cos \theta}{Z}$$

CURRENT

$$I = \frac{P}{E \cos \theta}$$

$$I = \sqrt{\frac{P}{Z \cos \theta}}$$

Table 2-5 is a summary of Ohm's law and power formulas for ac.

VOLTAGE

$$E = \frac{\sqrt{PR}}{\cos \theta}$$

$$E = \sqrt{\frac{PZ}{\cos \theta}}$$

$$E = \frac{P}{I \cos \theta}$$

IMPEDANCE

$$Z = \frac{E^2 \cos \theta}{P}$$

$$Z = \frac{P}{I^2 \cos \theta}$$

$$Z = \frac{R}{\cos \theta}$$

Table 2-5. Summary of power and Ohm's law formulas for ac.

<i>Watts</i>	<i>Amperes</i>	<i>Volts</i>	<i>Impedance</i>
$P =$	$I =$	$E =$	$Z =$
$I^2 R$	E/Z	$I Z$	E/I
$E I \cos \theta$	$\frac{P}{E \cos \theta}$	$\frac{P}{I \cos \theta}$	$\frac{E^2 \cos \theta}{P}$
$\frac{E^2 \cos \theta}{Z}$	$\sqrt{\frac{P}{Z \cos \theta}}$	$\sqrt{\frac{P Z}{\cos \theta}}$	$\frac{P}{I^2 \cos \theta}$
$I^2 Z \cos \theta$	$\sqrt{\frac{P}{R}}$	$\frac{\sqrt{P R}}{\cos \theta}$	$\frac{R}{\cos \theta}$

RESONANCE IN A SERIES CIRCUIT

In a series L - C circuit a condition of equal values of inductive and capacitive reactance is known as resonance. The resonant frequency is identified by the letter f and sometimes by f_r .

$$f = \frac{1}{2\pi \sqrt{LC}} \quad (2-61)$$

or

$$f = \frac{0.159}{\sqrt{LC}}$$

Basic units are used in this formula. f is the frequency in cycles per second; L the inductance in henrys and C the capacitance in farads. For most applications these are not practical values, but the formula is easily modified to:

$$f = \frac{10^6}{2\pi \sqrt{LC}}$$

f is now the frequency in kilocycles (kc) per second; L is the inductance in microhenrys (μh) and C is the capacitance in micromicrofarads ($\mu\mu f$).

The same formula is a reasonable approximation for parallel L - C circuits having a circuit Q of 10 or more.

If the inductance and the capacitance are both in microunits, that is, microhenrys and microfarads (with the frequency, f , in kilocycles), then the basic resonance formula can be modified to:

$$f = \frac{159.2}{\sqrt{LC}}$$

If the frequency is known, then the basic formula for resonance can be rearranged to find either the inductance, L , or the capacitance C .

$$L = \frac{1}{4\pi^2 f^2 C}$$

and

$$C = \frac{1}{4\pi^2 f^2 L}$$

In both of these formulas L is the inductance in henrys, C is the capacitance in farads, f is the frequency in cycles per second. These can be modified to reflect more practical values.

$$L = \frac{25,330}{f^2 C}$$

and

$$C = \frac{25,330}{f^2 L}$$

Here the inductance is in microhenrys, the capacitance, C , is in microfarads, and the frequency, f , is in kilocycles.

Q OF A SERIES RESONANT CIRCUIT

The ratio of inductive reactance to the effective resistance of a

coil is known as the figure of merit, or Q —a concept that can also be applied to a tuned circuit.

$$Q = \frac{f_r}{f - f_r} \quad (2-62)$$

In this formula, f_r is the resonant frequency. The circuit is then detuned until the resonant voltage drops to 0.707 of its peak value (its value at resonance). This supplies the value of f .

DECIBELS and NEPERS

The bel represents the logarithm (to the base 10) of a comparison or ratio of two powers. Expressed as a formula:

$$N_b = \log_{10} \frac{P_2}{P_1} \quad (2-63)$$

N_b is the number of bels. P_2 and P_1 represent the two powers (in watts). P_2 is generally used to indicate the output; P_1 the input. When P_2 is larger than P_1 , the power gain is positive and the number of bels may be preceded by a plus sign. The plus sign may be omitted, however. If P_2 is less than P_1 , the output is obviously less than the input and we have a loss of power. The answer, should then be preceded by a minus sign.

As in the case of other units in electronics formulas (such as the farad for capacitance) the bel is much too large, and so a more convenient unit, the decibel (tenth of a bel) is used. That is:

$$1 \text{ bel} = 10 \text{ decibels}$$

Substituting this information in our formula, we have:

$$N_{db} = 10 \log_{10} \frac{P_2}{P_1}$$

Since power (in watts) is the product of current and resistance ($P = I^2R$), we can modify the formula for decibels:

$$\begin{aligned} N_{db} &= 10 \log_{10} \frac{P_2}{P_1} \\ &= 10 \log_{10} \frac{I_2^2 R_2}{I_1^2 R_1} \end{aligned}$$

If R_2 and R_1 are equal (that is, if the input and output resistances are identical) resistance terms cancel:

$$N_{db} = 10 \log_{10} \frac{I_2^2}{I_1^2}$$

and since logarithms obey the following relationship:

$$\log x^n = n \log x$$

we have:

$$N_{db} = 20 \log \frac{I_2}{I_1} \quad (2-64)$$

(\log_{10} is abbreviated simply as \log .)

Also, since power $P = E^2/R$, we have

$$N_{db} = \log \frac{E_2^2 R_1}{E_1^2 R_2}$$

While the resistance terms are inverse of what they were previously, they too cancel if they are equal and the formula is commonly used as:

$$N_{db} = 20 \log \frac{E_2}{E_1} \quad (2-65)$$

A similar group of formulas with the natural base e (2.718281) can also be used. The unit is called the Neper. When working with two power levels:

$$N_n = 1/2 \log_e \frac{P_2}{P_1}$$

The relationship between nepers and decibels is such that

$$\begin{aligned} 1 \text{ db} &= 0.1151 \text{ neper} \\ 1 \text{ neper} &= 8.686 \text{ db} \end{aligned}$$

When using formulas involving decibels, it will be more convenient to have the larger value of power, voltage, or current appearing in the numerator. This will avoid the necessity for working with decimal values.

REFERENCE LEVELS

All of these formulas are concerned with power, voltage and current relationships where input and output are clearly specified. However, there are a number of arbitrary reference levels which can be used. 6 milliwatts across 500 ohms is one of these; others are 10 and 100 milliwatts.

VOLUME UNITS (VU)

A volume unit is one in which the reference level is clearly specified. Thus:

$$N_{vu} = 10 \log_{10} \frac{P_2}{.001} \quad (2-66)$$

$$N_{vu} = 10 \log \frac{P_2}{10^{-3}}$$

This can be rearranged to read:

$$N_{vu} = 10 \log 10^3 P_2$$

or

$$N_{vu} = 30 \log P_2$$

(since the log of 10^3 or 1,000 is 3). In all of these formulas, common logs (logs to the base 10) are used.

Decibel Table

<i>DB</i>	<i>Power Ratio</i>	<i>Voltage or Current Ratio</i>	<i>DB</i>	<i>Power Ratio</i>	<i>Voltage or Current Ratio</i>
0	1.00	1.00	10	10.0	3.2
0.5	1.12	1.06	15	31.6	5.6
1.0	1.26	1.12	20	100	10
1.5	1.41	1.19	25	316	18
2.0	1.58	1.26	30	1,000	32
3.0	2.00	1.41	40	10,000	100
4.0	2.51	1.58	50	10^5	316
5.0	3.16	1.78	60	10^6	1,000
6.0	3.98	2.00	70	10^7	3,162
7.0	5.01	2.24	80	10^8	10,000
8.0	6.31	2.51	90	10^9	31,620
9.0	7.94	2.82	100	10^{10}	10^5

FILTERS

A filter is a combination of resistors, coils and capacitors to permit the passage of some frequencies (generally a band of frequencies) and to suppress others. The upper and/or lower limit of such a band is known as the cutoff frequency.

While filters range from the extremely simple to the very complex, they can usually be categorized as low pass, high pass, band pass and band elimination types. The input and output connections of filters are terminated in source and load resistances or impedances equal in value to the impedance of the filter.

HIGH-PASS FILTER (Constant K)

A high-pass filter (Fig. 2-33) is one in which frequencies higher than

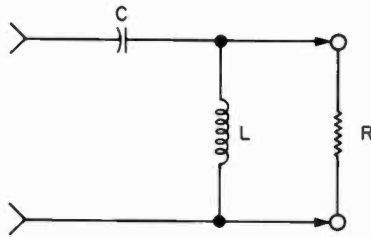


Fig. 2-33. High-pass filter. The inductor bypasses lower frequencies, has increasing reactance as the frequency is increased.

the cutoff frequency (f) are passed, while frequencies lower than the cutoff frequency are attenuated. For a constant K type:

$$C = \frac{1}{4 \pi f R} \quad (2-67)$$

$$L = \frac{R}{4\pi f} \quad (2-68)$$

$$R = \sqrt{\frac{L}{C}} \quad (2-69)$$

C is the series capacitance in farads; L the shunt inductance in henrys and R is the terminating resistance. The cutoff frequency is f .

The high pass filter in Fig. 2-33 consists of two elements—a series capacitor and a shunt coil. Filters can be made up of various combinations of series and shunt components. A constant- K filter is so named since the product of its series and shunt impedances is a constant at all frequencies.


Filters of all types take advantage of the fact that coils and capacitors behave inversely in the presence of ac. Thus, in the high pass filter, the series unit, a capacitor in series with the line, has a decreasing reactance as the frequency is increased. The coil, shunted across the line, acts as a bypass to low frequencies but has an increasing reactance as the frequency is increased.

LOW-PASS FILTER (Constant K)

A low-pass filter (Fig. 2-34) is one which passes all frequencies

below a selected value and attenuates higher frequencies. Its action, then, is exactly the opposite of a high-pass filter, so it isn't surprising

Fig. 2-34. *Low-pass filter. As the frequency is increased, the bypassing action of the capacitor becomes more and more effective.*

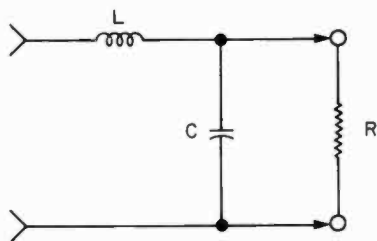

to find that its circuit arrangement is also exactly opposite. For a low-pass filter:

$$C = \frac{1}{\pi f R} \quad (2-70)$$

$$L = \frac{R}{\pi f} \quad (2-71)$$

and

$$R = \sqrt{\frac{L}{C}} \quad (2-72)$$

In this formula, the shunting element is C , L is the series inductance. R is the terminating resistance while f is the cutoff frequency.

BAND-PASS FILTER (Constant K)

This type of filter, as its name suggests, permits the passage of a

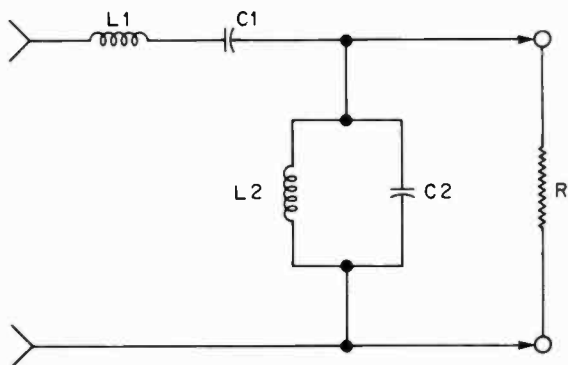


Fig. 2-35. *Band-pass filter. A filter of this kind attenuates frequencies above and below the desired band.*

selected band of frequencies while attenuating lower and higher frequencies.

A band-pass filter takes advantage of the differing impedance characteristics of series and parallel-tuned circuits. A series circuit has minimum impedance at its resonant frequency. A parallel circuit has maximum impedance at its resonant frequency. These two circuits are combined in the band-pass filter of Fig. 2-35.

The series arm has minimum impedance at the center frequency of the desired band. The impedance increases on either side of resonance. Exactly the opposite behavior is given by the shunt arm—in this case, a parallel tuned circuit.

$$C1 = \frac{f2 - f1}{4 \pi f1 f2 R} \quad (2-73)$$

$$C2 = \frac{1}{\pi (f2 - f1) R} \quad (2-74)$$

$$L1 = \frac{R}{\pi (f2 - f1)} \quad (2-75)$$

$$L2 = \frac{(f2 - f1) R}{4 \pi f1 f2} \quad (2-76)$$

$L1$ and $C1$ form the series-tuned circuit inserted in the line; $L2$ and $C2$ are the elements of the parallel-tuned circuit shunting the line. $f1$ is the lower cutoff frequency and $f2$ is the upper cutoff frequency.

BAND-ELIMINATION FILTER (Constant K)

Also known as a band-rejection, band-stop or band suppression filter, it also utilizes the particular characteristics of parallel-tuned and series-tuned circuits. As you can see in Fig. 2-36, the arrangement is exactly the opposite of a band-pass filter.

$$C1 = \frac{1}{4 \pi (f2 - f1) R} \quad (2-77)$$

$$C2 = \frac{f2 - f1}{\pi f1 f2 R} \quad (2-78)$$

$$L1 = \frac{(f2 - f1) R}{\pi f1 f2} \quad (2-79)$$

$$L2 = \frac{R}{4 \pi (f2 - f1)} \quad (2-80)$$

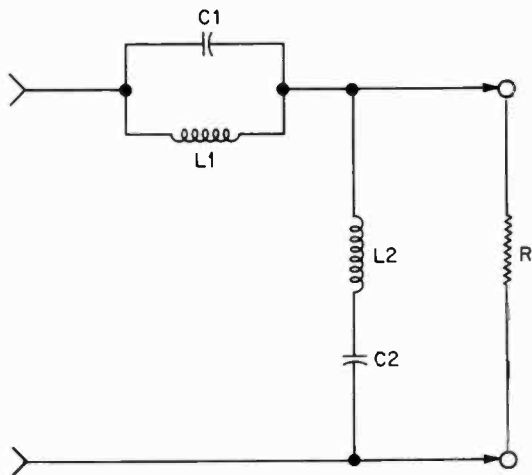


Fig. 2-36. *Band-elimination filter. Note that the circuit arrangement is exactly the opposite of that shown in Fig. 2-35.*

As in the band-pass filter, f_1 and f_2 represent the lower and upper cutoff frequencies, respectively.

T-TYPE LOW-PASS FILTER (Constant K)

It is difficult to produce sharp frequency cutoff with single section filters. A single coil can be added to the low-pass filter (Fig. 2-37) to

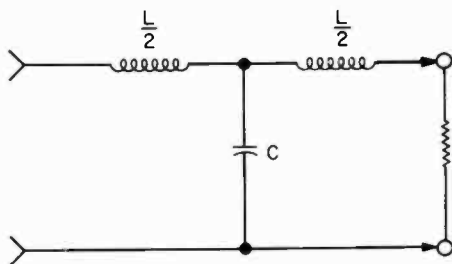


Fig. 2-37. *This is an improved version of the low-pass filter. Additional units, inductors and capacitors, can be added to increase the effectiveness of the filtering action.*

produce the T-type (so-named because of its appearance). Two T-type low-pass filters can be combined as shown in Fig. 2-38. The coils can

be combined into a single inductor. Assuming no coupling between these coils, the replacement coil would have a value of $L = L_1 + L_2$. Because of its appearance the filter is known as a π -type.

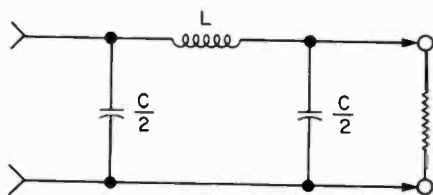


Fig. 2-38. This circuit represents the combination of two T-type low-pass filters into a single unit.

A high-pass filter can also be made into a T-type by inserting another series capacitor into the line. A multi-section T-type, made by joining two such units, would have a pair of immediately connected capacitors,

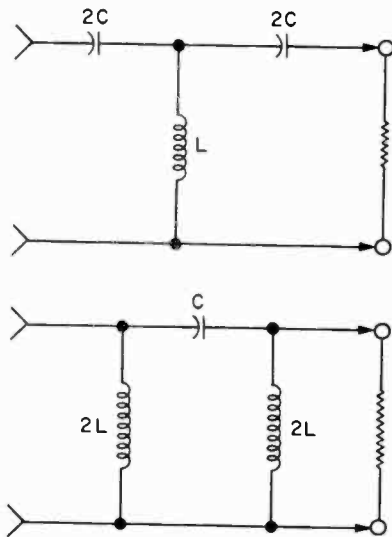


Fig. 2-39. T-type (above) and π -type high-pass filters.

(see Fig. 2-39). These capacitors can be replaced by a single unit having an equivalent value.

Multi-section band-pass and band-elimination filters can be made by joining additional sections.

π -TYPE LOW-PASS FILTER

T-type filters are made by putting in additional series elements. A π -type filter is obtained by adding another shunt element. As in the method used in T-type filters, multi-section units can be formed.

π -TYPE HIGH-PASS FILTER

Adding another shunt inductor, as in Fig. 2-39, gives us a single-section, π -type, high-pass filter. A two-section unit can be made by joining two single units. If the two inductors are identical, they can be replaced by a single unit having half the value of either.

The impedance of the circuit or the component connected across the input of a filter is called the source impedance. The circuit or component across the output of the filter is the load impedance.

The filter itself represents an impedance—that is, it has its own input and output impedances. These impedances, at each end of the filter, are known as image impedances. For maximum transfer of energy from the source to the load, the image impedances should be equal to the source and load impedances.

m-DERIVED FILTERS

In Fig. 2-40 we have an elementary low-pass constant K type filter. This filter will pass all frequencies below the cutoff frequency, f . That

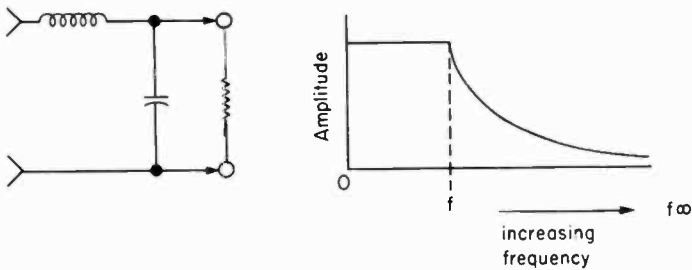


Fig. 2-40. Low-pass constant K type filter. The curve shown at the right is idealized. The cutoff is by no means as sharp, nor is the bandpass as flat as indicated.

is, the attenuation of all frequencies starting with zero (considering dc as our starting point, or zero frequency) up to the cutoff frequency will be zero. This is just another way of saying that all these frequencies will be passed. But, as shown in the graph, attenuation gradually increases with a rise in frequency. At some frequency the attenuation

will be so large that we consider it infinite. This frequency is designated as f_{∞} .

The ratio of the cutoff frequency, f , to the infinite attenuation frequency, f_{∞} , is a factor which is designated by the letter m . For a low-pass filter:

$$m = \sqrt{1 - \left(\frac{f^2}{f_{\infty}^2}\right)} \quad (2-81)$$

and for a high-pass filter

$$m = \sqrt{1 - \left(\frac{f_{\infty}^2}{f^2}\right)} \quad (2-82)$$

An m -derived filter is one that is derived from or obtained from one of the constant K types. m -derived filters have additional impedances and so have a much sharper cutoff. The type of derived filter we get

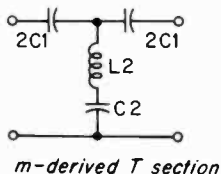
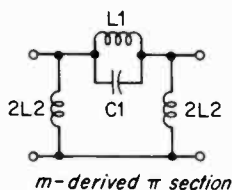
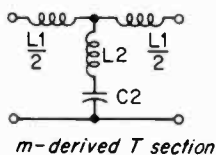
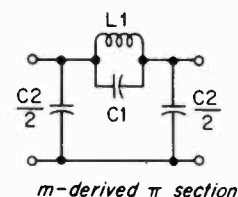


Fig. 2-41. Filters of the m -derived type can be T-type, π type, or may contain several such sections in the filter.

depends on the kind of modification we make to the basic constant K type.

If we add an impedance to the shunt arm of the basic filter, we obtain a filter that is known as a series derived m -type filter. If we connect an impedance in the series arm, the modified filter is called a shunt derived m -type. The additional impedances may be coils or capacitors, or series-parallel combinations.

TYPES OF m -DERIVED FILTERS

m -derived filters may be low-pass, high-pass or bandpass. Within these three main categories we will find single- and multi-element and T sections. Fig. 2-41 shows several m -derived filters.

NONSINUSOIDAL WAVES

Unless otherwise specified, alternating current formulas are based on the use of pure sine waves of constant frequency and amplitude — that is, waves which follow the equation for a sine curve, whose positive and negative halves are symmetrical and which repeat in a periodic manner (Table 2-6).

While the sine wave is the simplest type of ac waveform, there are many other waveforms that are nonsinusoidal. However, if a wave is a steadily recurring one, it can be resolved into two or more sine waves. Conversely, a pair of pure sine waves can be combined or added to yield either a symmetrical or a nonsymmetrical wave.

Whether the resultant wave, produced by the vector addition of sine waves, is symmetrical or nonsymmetrical, depends on the frequency of the sine waves. If the sine waves consist of a fundamental, plus even-order harmonics (f , $2f$, $4f$, etc.) the resultant will be a nonsinusoidal wave which will also be asymmetrical (nonsymmetrical). However, if the sine waves are odd-order harmonics (f , $3f$, $5f$, etc.) the nonsinusoidal resultant waves will be symmetrical.

Table 2-6. Sine and e values for selected amounts of θ .

θ	0	30	60	90	120	150	180
$\sin \theta$	0.00	0.500	0.866	1.00	0.866	0.500	0.00
e	0.00	50.0	86.6	100	86.6	50.0	0.00
θ	210	240	270	300	330	360	
$\sin \theta$	-0.500	-0.866	-1.00	-0.866	-0.500	0.00	
e	-50.0	-86.6	-100	-86.6	-50.0	0.00	

The sine wave having the lowest frequency (f) is referred to as the fundamental, or is sometimes called the first harmonic. The second harmonic is a wave having twice the frequency of the fundamental ($2f$); the third harmonic ($3f$) has three times the fundamental frequency, etc.

As a general rule, the amplitude of a harmonic is less than that of the fundamental. However, it is entirely possible for a harmonic, such as the third, to be stronger (have more amplitude) than a lower-frequency harmonic, such as the second.

FUNDAMENTAL and HARMONIC RELATIONSHIPS

The instantaneous value of a sine wave of voltage or current was given on page 33, formula 2-10 as:

$$e = E_{\text{peak}} \sin \omega t$$

If we are concerned with a fundamental and a number of harmonics, we can identify the peak voltages by numbering them. Thus, the fundamental would now be:

$$e = E1_{\text{peak}} \sin \omega t$$

The second harmonic would be:

$$e = E2_{\text{peak}} \sin 2 \omega t \quad (2-83)$$

And the third harmonic:

$$e = E3_{\text{peak}} \sin 3 \omega t \quad (2-84)$$

Chapter 3

VACUUM TUBES and VACUUM TUBE CIRCUITS

The behavior of a tube can be predicted from a graph of its characteristics. Static characteristics are found by applying only dc voltages to the elements of the tube. A dynamic characteristic is an attempt to obtain information about the tube's behavior under simulated working conditions. A controlled ac signal of a particular frequency is injected into the grid, and the plate of the tube works into its specified load. The dc voltages on the various elements are those which would normally be used.

From the characteristics of a tube, plotted in graph form, we can obtain the tube's constants. These constants are amplification factor (μ), plate resistance (r_p), also known as ac plate resistance or dynamic plate resistance and the mutual conductance (g_m), also known as the plate conductance.

AMPLIFICATION FACTOR

Amplification factor is an electronic yardstick, letting us measure how effectively the grid and plate control the flow of tube current.

$$\mu = \frac{\Delta E_p}{\Delta E_g} \quad (3-1)$$

(with constant plate current)

Δ means "change of". E_p and E_g refer to changes in plate and grid dc voltages. An increase in plate voltage (ΔE_p) increases the plate current. An increase in bias voltage (ΔE_g) can be adjusted so that the plate current decreases to its original value. The ratio of the two

is the amplification factor of the tube. Amplification factor is simply expressed as a number.

PLATE RESISTANCE

Whenever we have a voltage across two points and a current flow produced as a result of this voltage, we have resistance. Ohm's law makes the same statement, but much more concisely, as $R = E/I$.

In a tube, current flows between cathode and plate as a result of the voltage placed across these two elements. This meets the condition established by Ohm's law and so we can consider the space between cathode and plate as a resistor. But this is by no means an ordinary resistor, nor can it be compared to a physical resistor except in a very limited sense. Thus, we cannot obtain the resistance of the tube (resistance between cathode and plate) by dividing the plate voltage by the plate current.

Although the current in a tube is unidirectional—that is, it moves in but one direction—from cathode to plate, we regard it as ac, not dc, since the current changes with changes in input signal voltage.

The plate resistance (r_p) of a tube (also known as the dynamic plate resistance) is the resistance (in ohms) offered by the space between cathode and plate to the flow of a changing current. Its value is obtained by making a *small* change in plate voltage and then dividing this by the resulting change in the plate current. Expressed as a formula, we have:

$$r_p = \frac{\Delta E_p}{\Delta I_p} \quad (3-2)$$

The grid voltage is kept constant during any plate resistance measurement.

MUTUAL CONDUCTANCE

Since conductance is the reciprocal of resistance, we might expect the formula for mutual conductance (g_m) to be the inverse of the formula for plate resistance. It is, with one change. We use the grid (E_g) instead of the plate voltage (E_p). Thus:

$$g_m = \frac{\Delta I_p}{\Delta E_g} \quad (3-3)$$

(with plate voltage constant)

This formula is intended to test the effectiveness of a change in grid

voltage on plate current. Mutual conductance is measured in mhos, or, more practically, in micromhos.

RELATIONSHIPS OF μ , r_p and g_m

The relationships between these tube constants can be obtained by multiplying the mutual conductance by plate resistance.

$$g_m \times r_p = \frac{I_p}{E_g} \times \frac{E_p}{I_p}$$

Since we have similar terms (I_p) in numerator and denominator, these cancel, and we have:

$$g_m \times r_p = \frac{E_p}{E_g}$$

But $E_p/E_g = \mu$. Hence, we have:

$$\mu = g_m \times r_p \quad (3-4)$$

We can rearrange this formula in terms of mutual conductance and plate resistance:

$$g_m = \frac{\mu}{r_p} \quad r_p = \frac{\mu}{g_m}$$

VOLTAGE AMPLIFIERS

The voltage amplification of a vacuum-tube stage is the ratio of the output signal voltage to the input signal voltage:

$$\text{voltage amplification} = \frac{e_o}{e_g} \quad (3-5)$$

The output voltage can be measured across some value of plate load resistor (R_p) or a reactive element such as a plate load impedance, Z .

The voltage amplification with resistive load is:

$$\text{amplification} = \frac{\mu \times R_L}{r_p + R_L} \quad (3-6)$$

The amplification factor is μ , r_p is the plate resistance of the tube and R_L is the plate load resistor. But since the ratio e_o/e_g also represents the amplification of the tube, we can set this up to read:

$$\frac{e_o}{e_g} = \frac{\mu \times R_L}{r_p + R_L}$$

By multiplying both sides by e_g we can have our formula supply us with information in terms of output voltage.

$$e_o = e_g \times \frac{\mu \times R_L}{r_p + R_L}$$

This is quite satisfactory for a triode but tube manuals do not, as a rule, list the amplification factor of tubes other than triodes. But since $\mu = g_m \times r_p$, we can substitute this in our formula:

$$\text{amplification} = \frac{g_m \times r_p \times R_L}{r_p + R_L} \quad (3-7)$$

In this formula, g_m is the transconductance and is in mhos. For this purpose the mho is an inconveniently large unit. Tube manuals list transconductance in micromhos. We can conveniently modify our formula this way:

$$\text{voltage amplification} = \frac{g_m \times r_p \times R_L}{10^6 \times (r_p + R_L)}$$

In this formula, g_m is the transconductance in micromhos. Resistance (both plate and load) remains in ohms.

The formula for the output voltage across a load impedance is similar to that given earlier for a resistive load.

$$e_o = e_g \times \frac{\mu \times Z}{Z + r_p} \quad (3-8)$$

CATHODE FOLLOWERS

The formulas we have given would indicate that the voltage amplification is directly dependent upon the amplification factor, the plate resistance and the value of the load. However, it also depends on how we connect the load. In the cathode follower we transfer the load from the plate to the cathode circuit. In such circuits the voltage amplification is always less than one (unity). However, for this sacrifice in voltage amplification we get a circuit that can be used for impedance transformation—connecting a high impedance circuit at the input to a low impedance circuit at the output of the cathode follower. For triode cathode followers, the voltage amplification is:

$$\text{voltage amplification} = \frac{\mu \times R_L}{r_p + R_L \times (\mu + 1)} \quad (3-9)$$

For a pentode used as a cathode follower:

$$\text{voltage amplification} = \frac{g_m \times R_L}{1 + (g_m \times R_L)} \quad (3-10)$$

RESISTANCE-COUPLED AUDIO AMPLIFIERS (TRIODES)

For the sake of convenience, audio frequencies may be divided into three ranges—low, medium and high. We can arbitrarily select the center of each range as 100 cycles for the low-frequency range, 1,000 cycles for the intermediate or center frequency and 10,000 cycles for the high range.

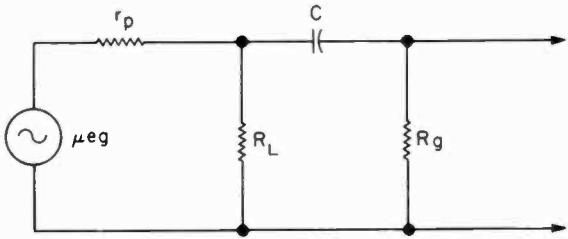


Fig. 3-1. Equivalent circuit for the low-frequency range.

In R-C amplifiers we may consider the resistive elements as constant for the three audio ranges. The frequency sensitive component is capacitive. Ignoring stray capacitances, such as the capacitance

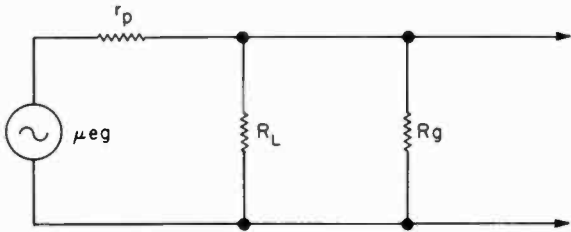


Fig. 3-2. Equivalent circuit for the intermediate-frequency range. The reactance of the coupling capacitor is now low enough so that it may be disregarded.

between adjacent wires and wiring and the chassis, the interelectrode capacitances of the tube and the coupling capacitor between the driver and driven tube will affect the gain.

At low frequencies, capacitive reactance is high. Its effect on a circuit will be serious or negligible, depending on how it is connected. For a series arrangement, the high reactance must be considered. Where the capacitance is a shunt element, the high reactance means we may disregard it safely.

For the low-frequency range, the equivalent circuit may be drawn as shown in Fig. 3-1. Note that for the low range we are not concerned with the shunting interelectrode capacitances of the tube. The dominant element is the coupling capacitor C .

For the intermediate frequency range, the reactance of the coupling capacitor C has such a low value that we may disregard it. Note, in the equivalent circuit (Fig. 3-2) for the intermediate frequencies that all capacitances have been omitted.

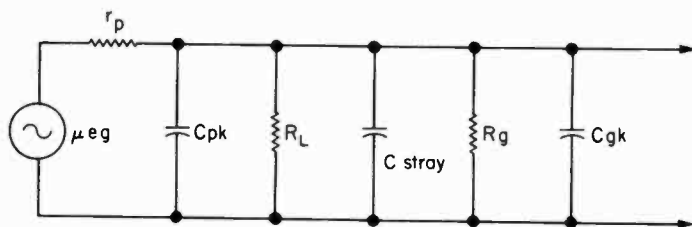


Fig. 3-3. Equivalent circuit for the high-frequency range. The shunting effect of miscellaneous capacitances now becomes important.

For the high frequency range, the interelectrode capacitances enter the picture. The capacitance between plate and cathode (C_{pk}) is now a shunting element across the plate load resistor, R_L . Similarly, the

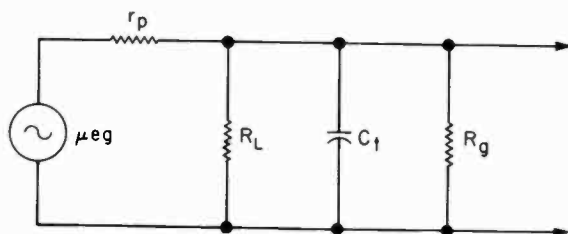


Fig. 3-4. The equivalent circuit for the high-frequency range may be simplified by lumping all the capacitances.

interelectrode capacitance (C_{gk}) between the grid and cathode of the driven tube is a shunting element across the grid leak R_g . (Fig. 3-3)

Now, depending on how the unit is constructed, the wiring capacitances may be significant. And, since all these capacitances are in shunt, we may lump them all into a single element, C_L . The equivalent circuit is shown in Fig. 3-4.

AMPLIFICATION AT INTERMEDIATE OR MEDIUM FREQUENCIES (TRIODES)

The output impedance for a triode at intermediate frequencies is:

$$Z_o = \frac{R_L \times R_g}{R_L + R_g} \quad (3-11)$$

(Note that this is the same as our formula for two resistors in parallel.) The impedance is resistive since the capacitive element is disregarded. The amplification at intermediate frequencies is:

$$A = \frac{\mu \times Z_o}{Z_o + r_p} \quad (3-12)$$

The simplicity of this formula is due to the absence of a reactive element.

AMPLIFICATION AT LOW FREQUENCIES (TRIODES)

We can get an approximate value for the gain at low audio frequencies using triodes by:

$$A = \frac{\mu \times R_g}{\sqrt{R_g^2 + X_c^2} \left(\frac{r_p (R_L + R_g)}{R_L \times R_g} + 1 \right)} \quad (3-13)$$

AMPLIFICATION AT HIGH FREQUENCIES (TRIODES)

The gain at high frequencies becomes even more complex since the various interelectrode capacitances of both tubes, and the wiring capacitances, now come into play. The value obtained for the gain will just be a reasonable approximation.

$$A = \frac{\mu \times R_g}{\sqrt{R_g^2 + X_c^2} \left(\frac{r_p (R_L + R_g)}{R_L \times R_g} + 1 \right)} \quad (3-14)$$

RESISTANCE-COUPLED AUDIO AMPLIFIERS (PENTODES)

The equivalent circuits for resistance-coupled pentodes at low, intermediate and high frequencies is shown in Fig. 3-5. The plate resistance is now regarded as a shunt element instead of being in series

with the source. Again, at intermediate frequencies the equivalent circuit may be considered as being purely resistive. The three resistances, the plate resistance (r_p), the load resistance (R_L) and the grid

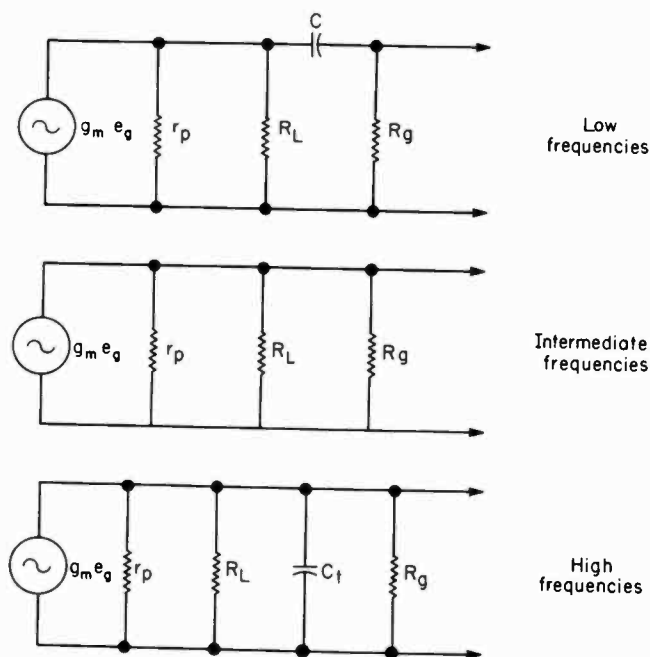


Fig. 3-5. Equivalent circuits for pentodes for low, intermediate and high frequencies.

(or grid leak) resistor, R_g are in shunt. The equivalent value (R_{eq}) of this combination can be obtained by using any one of the various formulas given earlier for combining parallel resistors.

$$R_{eq} = \frac{1}{\frac{1}{r_p} + \frac{1}{R_L} + \frac{1}{R_g}} \quad (3-15)$$

AMPLIFICATION AT MEDIUM FREQUENCIES (PENTODES)

The gain at medium frequencies is:

$$A = g_m \times R_{eq} \quad (3-16)$$

R_{eq} , as shown above, is the combined total shunt value of the plate load, the plate resistance and the grid-leak of the following stage.

AMPLIFICATION AT LOW FREQUENCIES (PENTODES)

As in the case of triodes, the amplification at low frequencies is affected by the value of the coupling capacitor, C .

$$A = \frac{g_m \times R_{eq}}{\sqrt{1 + \left(\frac{X_c}{R}\right)^2}} \quad (3-17)$$

X_c is the capacitive reactance of the coupling capacitor at the center value of the low-frequency range. For low frequencies, the grid-leak resistor, R_g is considered to be in series with the parallel combination of plate load (R_p) and plate resistance (r_p). That is:

$$R = \frac{r_p \times R_L}{r_p + R_L} + R_g \quad (3-18)$$

If the combined parallel equivalent value of r_p and R_L is small compared to the amount of grid-leak resistance, it may be ignored and R may be considered as equal in value to R_g .

The formula for pentode amplification at low frequencies has some unusual points of interest. Note that the numerator ($g_m \times R_{eq}$) is identical with our formula for the gain at medium frequencies. And, in the denominator, if the value of R should become exactly equal to the value of X_c , then the numerical amount of the denominator would be the square root of 2 or 1.414. That is, the voltage amplification, under these conditions, will be 70.7 percent of the amplification at medium frequencies. This is a 3 db drop in gain and is noticeable. The change in sound volume becomes even more apparent as the reactance of the capacitor increases. Thus, when $X_c = 2R$, the voltage amplification drops 7 db. The importance of not using too small a value of coupling capacitance becomes obvious.

AMPLIFICATION AT HIGH FREQUENCIES (PENTODES)

For both triodes and pentodes, the shunting capacitances are important, and for both types of tubes, the total shunting capacitance is:

$$C_t = C_{stray} + C_{pk} + C_i \quad (3-19)$$

C_{stray} represents the miscellaneous stray wiring capacitances of the circuit. C_{pk} is the interelectrode capacitance between the plate and the cathode of the driver tube. C_i is the input capacitance of the driven tube.

We cannot consider C_i as the sum of the interelectrode capacitances of the driven tube. The value of C_i can be obtained from:

$$C_i = C_{gk} + C_{gp} (1 + A) \quad (3-20)$$

C_{gk} is the capacitance between grid and cathode; C_{gp} is the capacitance between grid and plate. A is the amplification of the circuit. A reasonable value for A is to consider it as being equal to one-half the amplification factor of the tube.

For the high-frequency range for pentodes, the voltage amplification is:

$$A = \frac{g_m \times R_{eq}}{\sqrt{1 + (R_{eq}/X_t)^2}} \quad (3-21)$$

X_t represents the capacitive reactance of C_i . Note, in this formula, the effect the equivalent resistance, R_{eq} , and the reactance of the shunting capacitances on the gain. When these two are equal, the denominator will reduce to the square root of 2 and the gain will be equal to 70.7 of the gain at the medium frequencies. Under these conditions, the gain at the high frequencies will be 3 db down from the medium frequency gain.

The formula also shows us that if we let C_i (the total shunting capacitance) get out of hand, the gain at higher audio frequencies will suffer.

NEGATIVE FEEDBACK

In audio amplifiers a portion of the output voltage is fed back, out of phase, to the input. Known as negative, inverse or degenerative feedback, its effect is to reduce distortion at the expense of gain.

For an amplifier without feedback, the amplification A , is:

$$A = \frac{e_o}{e_g}$$

e_o is the amplified version of the input signal voltage, e_g .

We can rearrange this formula to read:

$$e_o = A \times e_g$$

If we now take a fraction of the output voltage (we will call it β) and feed it back to the input then our output voltage will now be:

$$e_o = A (e_g + \beta e_o)$$

Performing the indicated multiplication, we will get:

$$e_o = Ae_g + \beta Ae_o$$

If we now transpose βAe_o , we will have:

$$e_o - \beta Ae_o = Ae_g$$

We can simplify the left-hand expression:

$$e_o (1 - \beta A) = Ae_g$$

There are two terms in this equation in which we are now interested. One of these is the input voltage, e_g , and the other is the output voltage, e_o . We can get their ratio by dividing and transposing:

$$\frac{e_o}{e_g} = \frac{A}{1 - \beta A} = K \quad (3-22)$$

This is now our formula for the gain of an amplifier with feedback. K is used to represent a condition of amplification with negative feedback.

POWER AMPLIFIERS

The efficiency of any device is the ratio of what we get out to what we put in. In the case of a power amplifier, the efficiency (η) is the ratio of the ac power output (P_o) to the dc power input. Since this measurement must be taken with an input signal on the grid, the dc power is obtained by multiplying the average dc plate voltage by the average dc plate current.

$$\eta = \frac{P_o}{E_p \times I_p} \times 100 \quad (3-23)$$

Here P_o is the ac output power, E_p is the average plate voltage and I_p is the average plate current. Since the formula is multiplied by 100, the answer is directly in terms of percentage.

POWER SENSITIVITY

We can get a measure of the power sensitivity of a tube by comparing the ac output power (P_o) to the square of the ac input signal.

$$\text{Power sensitivity} = \frac{P_o}{E_g^2} \quad (3-24)$$

E_g is the input signal in volts rms. P_o is the ac output power. The power sensitivity is given in mhos.

POWER OUTPUT

We can regard the plate current of a power amplifier tube, when driven by a signal, as varying dc or as dc with an ac component. The output power (P_o) is the product of the ac component (i_p) of the plate current and the effective plate load (R_L). If the load is resistive and distortion is negligible:

$$P_o = (i_p)^2 \times R_L \text{ or } P_o = E_p \times i_p$$

The ac component of the plate current is sometimes referred to as the dynamic plate current. The formula shown here is for rms values of dynamic plate current and voltage. For peak-to-peak values:

$$P_o = \frac{(i_p^2) \times R_L}{2 \sqrt{2}} \quad (3-25)$$

The rms value of the ac component of the plate current of an audio amplifier power triode can be written in terms of the maximum (or peak) and the peak-to-peak values in this way:

$$i_p = \frac{i_{\max}}{\sqrt{2}} = \frac{i_{\max} - i_{\min}}{2 \sqrt{2}} \quad (3-26)$$

We can handle the ac component of the plate voltage in the same way:

$$e_p = \frac{e_{\max}}{\sqrt{2}} = \frac{e_{\max} - e_{\min}}{2 \sqrt{2}} \quad (3-27)$$

but, since power is the product of voltage and current, we can get another expression for power (but this time in terms of maximum and minimum values of voltage and current).

$$\begin{aligned} P_o &= \frac{i_{\max} - i_{\min}}{2 \sqrt{2}} \times \frac{e_{\max} - e_{\min}}{2 \sqrt{2}} \\ &= \frac{(i_{\max} - i_{\min})(e_{\max} - e_{\min})}{8} \end{aligned} \quad (3-28)$$

In a class-A triode power amplifier working into a resistive load, R_L , the plate current, i_p , is:

$$i_p = \frac{\mu \times e_g}{r_p + R_L}$$

If we substitute this for i_p in our formula for output power, we will get:

$$P_o = \left(\frac{\mu \times e_g}{r_p + R_L} \right)^2 \times R_L \quad (3-29)$$

MAXIMUM TRANSFER OF POWER TO THE LOAD

We will get maximum transfer of power from the source (the tube) to the load (R_L) when the resistance of the source and the load are equal, provided the amplification factor (μ), the plate resistance (r_p) and the signal voltage, e_g , are constant. Thus, when $R_L = r_p$,

$$P_o \text{ max} = \left(\frac{\mu \times e_g}{2 \times r_p} \right)^2 \times r_p$$

(note that r_p has been substituted for R_L)

By squaring and dividing, the formula can be simplified to:

$$P_o \text{ max} = \frac{\mu^2 \times e_g^2}{4 \times r_p} \quad (3-30)$$

While the transfer of power to the load is maximum when $R_L = r_p$, the peak transfer is not critical. That is, the value of R_L may be varied as much as 25% above or below its selected value, without seriously affecting the transfer of power from the tube to the load.

POWER IN THE PLATE LOAD

Where the source and load values in a power amplifier are not equal, the transfer of power to the load is:

$$P = \left(\frac{\mu \times e_g}{r_p + R_p} \right)^2 \quad (3-31)$$

UNDISTORTED POWER OUTPUT

The maximum undistorted power output when the plate load resistor (R_p) is twice the value of the plate resistance (r_p) is:

$$P_{\text{undistorted}} = \frac{2(\mu \times e_g)^2}{9 \times r_p} \quad (3-32)$$

SINGLE PENTODE AUDIO POWER OUTPUT

The audio power output of a single pentode may be fairly well approximated by:

$$P = 0.33 \times E_p \times I_p \quad (3-33)$$

The product, $E \times I$, represents the dc power input to the tube, E_p is the dc plate voltage and I_p is the dc plate current.

SECOND-HARMONIC DISTORTION OF A POWER AMPLIFIER

The greatest portion of distortion is due to the second harmonic, but because it is an even-order harmonic, it lends itself nicely to cancellation.

$$\text{percentage of Second-harmonic distortion} = \frac{2(i_p \text{ max} + i_p \text{ min}) - i_p}{(i_p \text{ max} - i_p \text{ min})} \times 100 \quad (3-34)$$

$i_p \text{ max}$ is the maximum of the ac component. $i_p \text{ min}$ is the minimum of

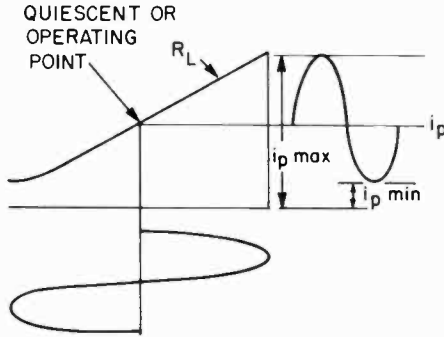


Fig. 3-6. The position of the quiescent or operating point is determined by the amount of bias used. Here the operating point is at the center of the characteristic curve.

the ac component. i_p is the amount of plate current that flows at the operating or quiescent point, (the bias point) as shown in Fig. 3-6.

Chapter 4

TRANSISTORS

Compared to a vacuum tube, the impedances associated with the input and output circuits of a transistor are low. We can regard vacuum tubes as voltage operated components; transistors as current operated.

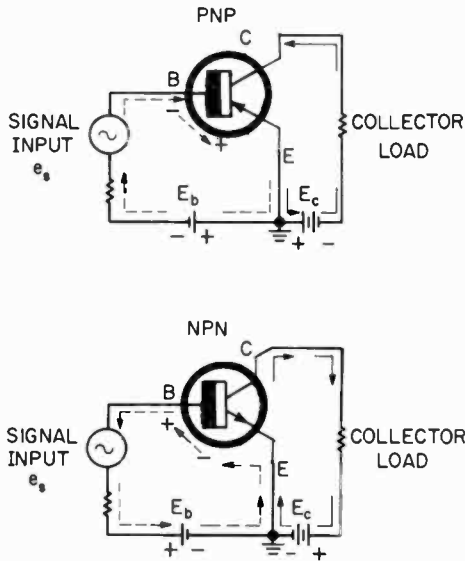


Fig. 4-1. In a vacuum tube, electron current moves only from cathode to plate. In a transistor, current can move to or from the collector, depending on the type of transistor used.

Although triodes are not uncommon, most tubes are multi-element—that is, are usually pentode or beam power. Most transistors, though, are triodes. The elements of the transistor triode are the emitter, base and collector and while, for the sake of analogy, these are often compared to the cathode, grid and plate of a vacuum tube, there is little other similarity. A vacuum tube is a unilaterally conducting device—that is, electron current moves from cathode to plate and in that direction only.

In a transistor, depending on its arrangement, electrons and “holes” can move in either direction, from emitter to collector or collector to emitter (Fig. 4-1).

CURRENT AMPLIFICATION

Since, the transistor, like the tube, is an amplifying device, we may look for comparable parameters. But because of the completely different nature of tubes and transistors, we cannot apply the analysis used for tubes to transistors.

In a transistor not all of the current carriers injected by the emitter reach the collector. The maximum, approached but not attained, would be 100 percent or 1. The ratio of a change (Δ) in collector current (i_c) to a change in emitter current (i_e) is called current gain and is represented by the Greek lowercase letter α (alpha). Thus:

$$\alpha = \frac{\Delta i_c}{\Delta i_e} \quad (4-1)$$

If all carriers leaving the emitter reached the collector, the collector current change (Δi_c) would be equal to the emitter current change (Δi_e) and the current amplification, or α , would be 1. For transistors other than point-contact types (forerunners of our present-day transistors) values of alpha are 0.99 or less.

RESISTANCE GAIN

The term current amplification or current gain or alpha of a transistor might tend to be misleading since there is no current gain at all, but a loss. However, the amplification possibilities of transistors become evident when we consider the resistance gain—that is, the ratio of the output and the input resistances.

$$\text{Resistance gain} = \frac{r_o}{r_i} \quad (4-2)$$

r_o is the output resistance and r_i is the input resistance. In a representa-

tive transistor, the output resistance is much higher than the input resistance, and the word *gain* is used in this sense. Thus, in working with transistors, we can get a rough approximation of the gain by making a comparison of the output and input resistances—that is, by determining their ratio.

VOLTAGE GAIN

As in the case of a tube, the voltage gain of a transistor is the ratio of the output (e_o) to the input voltage (e_i), or:

$$\text{Voltage gain} = \frac{e_o}{e_i}$$

Voltage is the product of current and resistance:

$$\text{Voltage gain} = \frac{e_o}{e_i} = \frac{i_c \times r_o}{i_e \times r_i}$$

But the ratio of i_c to i_e is alpha. Thus, we have:

$$\text{Voltage gain} = \alpha \frac{r_o}{r_i} \quad (4-3)$$

POWER GAIN

We can get a term for power gain by considering that power is the product of voltage and current.

$$\text{Power gain} = \frac{e_o \times i_c}{e_i \times i_e} \quad (4-4)$$

Note that the voltage gain (e_o/e_i) is part of this formula. But the formula shows that voltage gain is equal to $\alpha \times R_o/R_i$. We can substitute this in our formula for power gain:

$$\text{Power gain} = \alpha \frac{r_o \times i_c}{r_i \times i_e}$$

We can simplify this power formula by considering that alpha is equal to the ratio i_c to i_e . We now have:

$$\text{Power gain} = \alpha \times \alpha \frac{r_o}{r_i} = \alpha^2 \times \frac{r_o}{r_i} \quad (4-5)$$

Where alpha is very close to unity, we can disregard it and recognize that the power gain is the ratio of the output impedance to the input impedance.

BASIC CIRCUITS

Commonly, transistor circuits are arranged so that the base and emitter form the input circuit, with collector and emitter as the output

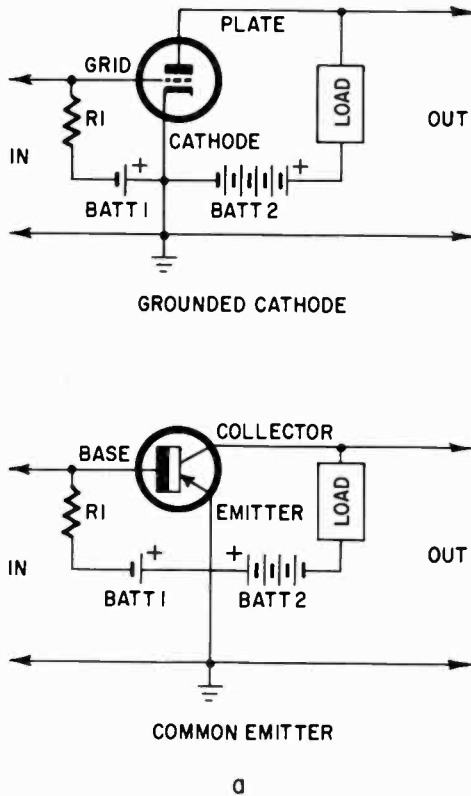




Fig. 4-2a. The common emitter circuit resembles the grounded cathode vacuum tube amplifier.

circuit. This most nearly resembles a vacuum tube circuit in which the cathode is the common element to input and output circuits. Fig. 4-2 shows three basic arrangements of transistor circuits plus their nearest vacuum-tube equivalents.

The circuit shown in Fig. 4-2a is a common emitter, comparable to the grounded cathode vacuum tube circuit. The common emitter (also known as a grounded emitter) has a low input resistance and a fairly high output resistance. The input resistance may range from about 300 ohms to 1,000 or more; output from 5,000 to 50,000 or higher.

The common base (grounded base) in Fig. 4-2b is similar to a grounded grid vacuum tube amplifier. The input resistance is about the same as the common emitter, but the output resistance is much higher, ranging from 100,000 ohms up to and beyond a half megohm.

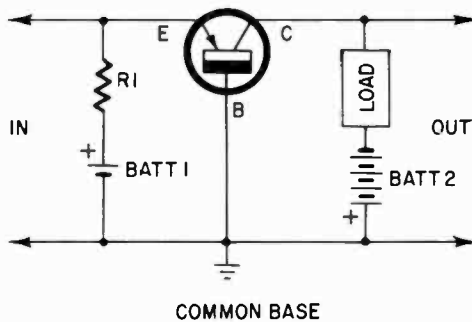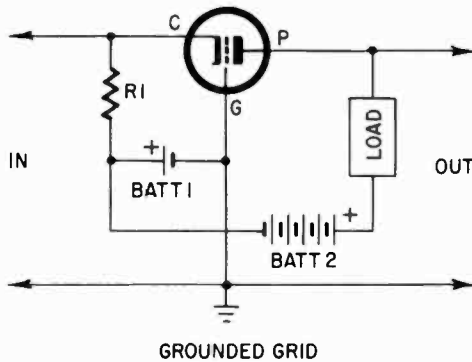
The common collector (grounded collector) in Fig. 4-2c, has a very high input resistance (100,000 ohms or more) and a much lower output resistance (1,000 ohms and higher). Like its counterpart, the cathode follower, the common collector can be used to match a high impedance to a much lower one.




b

Fig. 4-2b. The common base transistor circuit is similar to the grounded grid vacuum tube amplifier.

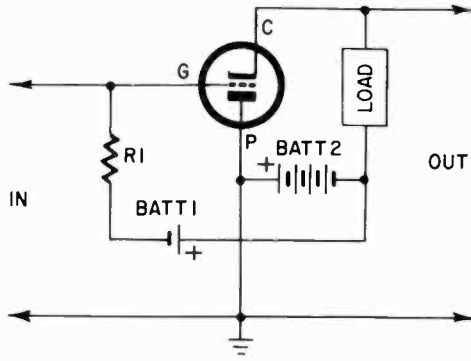The grounded collector has its nearest equivalent in the grounded plate vacuum tube circuit, more popularly known as a cathode follower.



CATHODE FOLLOWER

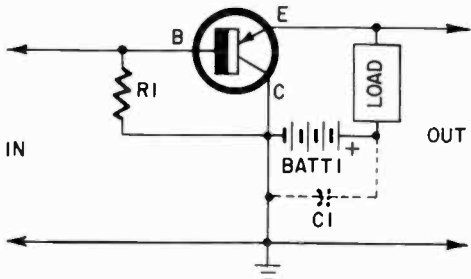

COMMON COLLECTOR

C

Fig. 4-2c. The common collector can be compared to a cathode follower. A capacitor, C1, is sometimes shunted across the battery to act as a bypass. As batteries get older, their internal resistance increases and they tend to behave as coupling elements. The shunting capacitor minimizes this effect.

lower. As in the case of the cathode follower, the grounded collector circuit has a very high input resistance and a comparatively lower output resistance.

PHASE REVERSAL

As shown in Fig. 4-3, it is possible to get phase reversal of the input signal with a transistor circuit, just as in the case of a vacuum-tube circuit. This is shown in Fig. 4-3.

The grounded-emitter circuit is the only one of the three in which there is phase reversal of the signal. In the grounded base and grounded collector circuits, the output and input signals are in phase.

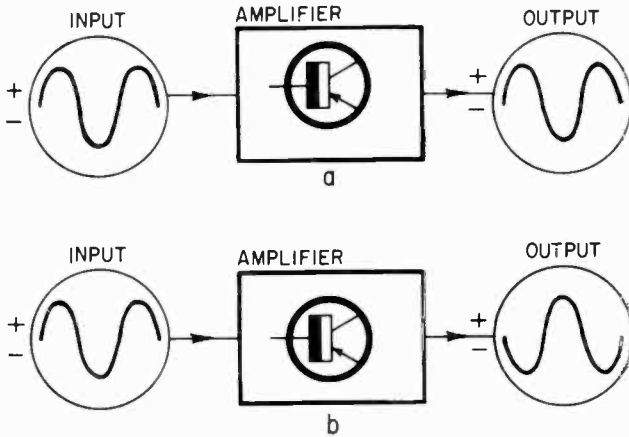


Fig. 4-3. The illustration at the top (a) represents the grounded base and grounded collector circuits. Input-output are in phase. The lower drawing (b) indicates a grounded emitter. This circuit supplies phase reversal.

CURRENT AMPLIFICATION FACTOR

We can get another ratio of current gain by comparing the change in collector current to the change in base current. Known as beta and represented by the Greek letter β it is shown as:

$$\beta = \frac{\Delta i_c}{\Delta i_b} \quad (4-6)$$

Beta can also be expressed in terms of alpha:

$$\beta = \frac{\alpha}{1 - \alpha} \quad (4-7)$$

ALPHA CUTOFF FREQUENCY

The limitation of the use of transistors at high frequencies is the transit time of current from emitter to collector (or collector to emitter). Alpha cutoff frequency is that frequency at which alpha drops to 0.707 (3 db) of its value at lower frequencies.

$$\text{Alpha cutoff frequency} = 0.707 \times \alpha \quad (4-8)$$

INPUT AND OUTPUT RESISTANCES

There is no isolation between the output and input circuits of a transistor. The transistor can be looked on as an active resistance

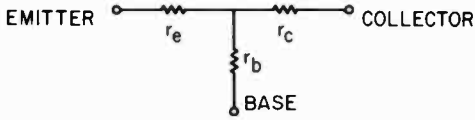


Fig. 4-4. A transistor resembles an active resistive network.

network. The input and output circuits are related through their respective resistances, as shown in Fig. 4-4.

<i>Circuit</i>	<i>Input resistance</i>	<i>Output resistance</i>
Common base	$r_e + r_b$	$r_c + r_b$
Common emitter	$r_b + r_e$	$r_c + r_e$
Common collector	$r_b + r_c$	$r_e + r_c$

Chapter 5

ANTENNAS AND TRANSMISSION LINES

The basic antenna consists of a single wire having a length equal to one-half of the length of the wave being transmitted. In practice, because of the capacitance effects between the ends of the antenna and ground, the antenna is cut a little shorter than this.

An approximation of antenna length in feet can be had by dividing 492 by the frequency (in megacycles) of the wave being transmitted. The relationship between the wavelength, λ , (in feet) and the frequency, f , (in megacycles) is:

$$\lambda = \frac{984}{f} \quad (5-1)$$

Since we are seldom concerned with full-wave antennas, we can divide both sides of the equation by 2 (for a half-wave antenna):

$$\frac{\lambda}{2} = \frac{492}{f}$$

The length obtained will be somewhat longer than practical because of antenna end effects. A more accurate figure can be obtained by multiplying the answer by a correction factor, k , depending on the frequency. For frequencies of 3 *mc* or less, k is 0.96. For 3 to 30 *mc*, k drops to 0.95 and for frequencies above 30 *mc*, k is 0.94. We can thus modify our formula for the length of an antenna in feet to read:

$$l = \frac{492 \times k}{f} \quad (5-2)$$

For *uhf*, where wavelengths are very short, it is more practical to

work in inches, rather than in fractions of a foot. The length of a half-wave antenna (l) in inches is:

$$l = \frac{5906}{f} \quad (5-3)$$

The value of f is still in megacycles. Note that without the correction factor, reference is to the electrical length of the antenna rather than its actual physical length. End effects, or capacitance effects at the ends of the antenna, require that we reduce the actual length of the antenna. A 4 to 6 percent reduction (k ranges between 0.96 and 0.94) is typical.

To find the length of a half-wave antenna in *meters*:

$$l = 1/2 \times \frac{3 \times 10^8}{f} \quad (5-4)$$

The length, l , is in meters. The frequency, f , in in cycles.

FULL WAVE ANTENNAS

For a full-wave antenna or for an antenna having a multiple amount of half waves the formula for antenna length is somewhat modified because of the lesser influence of end effects.

$$l = \frac{492 (n - 0.05)}{f} \quad (5-5)$$

l is the length in feet; f the frequency in megacycles; n is the number of half wave sections comprising the antenna. For a full-wave antenna, n would have a value of 2.

The formula shown above and the one given earlier for a half-wave antenna indicate that an antenna operated on some harmonic of its fundamental frequency will not be cut exactly right for that harmonic.

ANTENNA IMPEDANCE

The impedance of an antenna is the ratio of the voltage to the current – that is, $Z = E/I$. Fig. 5-1 shows the relationship between the current and the voltage along the length of a half-wave antenna. The current is maximum at the center and zero at the ends. The voltage is zero at the center and maximum at the ends. This means that the impedance is not constant along the length of antenna but varies from a maximum at the ends (maximum voltage, minimum current) to a minimum at the center.

The drawing in Fig. 5-1 shows that the impedance at the center should be zero. Practically, the impedance is about 72 ohms.

What is this impedance? Since we try to cut our antenna length so that the antenna will be resonant at the transmission frequency, we

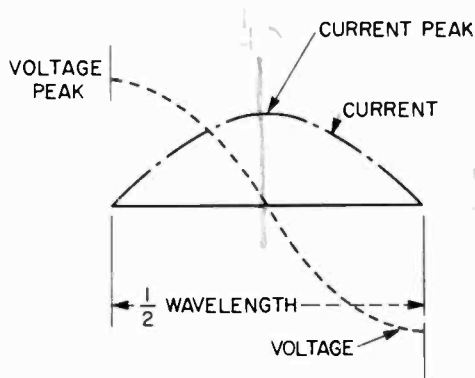


Fig. 5-1. Voltage and current distribution along the length of a half-wave antenna. The impedance is minimum at the center; maximum along the ends.

can consider this impedance as resistive—that is, it contains no reactive component such as inductance or capacitance. The ohmic or dc resistance of the antenna is usually very small in comparison with the impedance and so may be disregarded.

Ignoring the ohmic resistance, then, the impedance may be regarded as the radiation resistance of the antenna.

RADIATED POWER

For the power (P_r) in watts radiated by the antenna, we have:

$$P_r = I_a^2 \times R_r \quad (5-6)$$

I_a is the antenna current, in amperes and R_r is the radiation resistance in ohms.

POWER GAIN

The field strength of an antenna is directly related to the amount of current flowing in it. A comparison between a standard antenna and the antenna being used is called the power gain and is given in *db*. The standard or comparison antenna has the same height, length and polarization (that is, vertical or horizontal) as the antenna being tested.

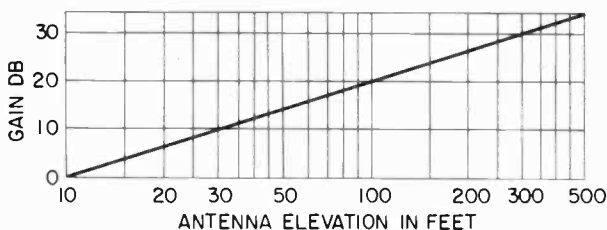


Fig. 5-2. Antenna gain is increased with height.

The elevation of an antenna (height above ground) has a pronounced effect on its gain, as shown in the graph, Fig. 5-2.


TRANSMISSION LINES

The purpose of a transmission line is to deliver maximum power from the transmitter to the antenna. Ideally, such a line would have no losses (that is, would consume no power), would match the impedance of the output tank of the transmitter to the impedance of the antenna; would be perfectly “flat” – that is, would have no reflections along its length.

The impedance of a transmission line, known as surge or characteristic impedance, is a function of the inductance and capacitance of the line and may be approximately represented by:

$$Z = \sqrt{L/C} \quad (5-7)$$

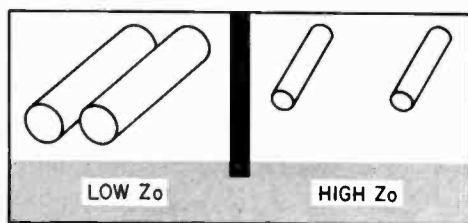There is a certain amount of dc resistance in the transmission line but this is generally negligible. The inductance and capacitance of the



Effect of Conductor Size and Spacing

Fig. 5-3. Impedance of a transmission line is controlled by spacing and wire thickness.

line depends on the amount of spacing between the wires of the line and the size of the wires (Fig. 5-3).

Thus, the impedance is determined by the conductor size and spacing as shown in Fig. 5-3.

TWO-WIRE OPEN TRANSMISSION LINE

Where the impedance of the transmission line matches that of the antenna, energy delivered by the line is absorbed by the load (the antenna). No energy, under these conditions, is reflected to the source. For a two-wire, open line, using air insulation:

$$Z = 276 \log \frac{s}{r} \quad (5-8)$$

Reference here (and in other formulas, unless otherwise stated, is to common logs—base 10). Z is the surge impedance (in ohms); s is the spacing between the wire centers in inches and r is the radius of the wire (in inches). (This formula is not applicable to a two-wire line using a solid dielectric as a means of separating the two wires.)

ATTENUATION

The attenuation of a line is directly proportional to the dc resistance of the line and inversely proportional to the impedance. Obviously, the lower the resistance of the line, the smaller will be the power losses.

$$A = 4.35 \frac{R}{Z} \quad (5-9)$$

A is the attenuation in *db* (per 100 feet of transmission line); R is the resistance in ohms (per 100 feet) and Z is the surge impedance (in ohms).

CONCENTRIC TRANSMISSION LINE

A concentric transmission line (also known as a coaxial line) has a center conductor, either solid or stranded wire. The outer conductor completely surrounds the center conductor and is concentric to it. The space between the two conductors may be any insulator, but is usually air or some form of polyethylene dielectric. The impedance:

$$Z = 138 \log \frac{D}{d} \quad (5-10)$$

Z is the characteristic impedance, in ohms; D is the inside diameter of the outside conductor, in inches; d is the outside diameter of the inside conductor in inches.

RESISTANCE OF COAXIAL TRANSMISSION LINE

$$R = 0.1 \left(\frac{1}{d} + \frac{1}{D} \right) \sqrt{f} \quad (5-11)$$

R is the resistance, in ohms, per 100 feet of line; f is the frequency in megacycles; d is the outside diameter of the inside conductor, in inches; D is the inside diameter of the outside conductor, in inches.

RESISTANCE OF OPEN TWO-WIRE COPPER LINE

$$R = \frac{\sqrt{f}}{5 \times d} \quad (5-12)$$

R is the resistance, in ohms, per 100 feet of line; f is the frequency in megacycles; d is the diameter of the copper line, in inches.

STANDING WAVE RATIO (SWR)

The SWR of a transmission line is an excellent indicator of the effectiveness of the impedance match between the transmission line and the antenna. The SWR is the ratio of the maximum to the minimum current along the length of the transmission line, or the ratio of the maximum to the minimum voltage. When the line is absolutely matched the SWR is unity. In other words, we get unity SWR when there is no variation in voltage or current along the transmission line. The greater the number representing SWR , the larger is the mismatch. Also, I^2R losses increase with increasing SWR .

For a purely resistive load:

$$SWR = \frac{Z_r}{Z_o} \quad (5-13)$$

Z_o is the characteristic impedance of the transmission line; Z_r is the impedance of the load.

SWR is optimum when Z_r is equal to Z_o . It is unimportant as to which of these terms is in the numerator. Since SWR cannot be a decimal, it is advisable to put the larger of the two numbers in the numerator.

CHARACTERISTIC IMPEDANCE

Characteristic impedance can be determined in a number of ways:

$$Z_o = \sqrt{\frac{R + j 2\pi f L}{G + j 2\pi f C}} \quad (5-14)$$

The numerator $(R + j 2\pi f L)$ represents the series impedance while the denominator $(G + j 2\pi f C)$ is the shunt admittance.

MATCHING IMPEDANCES

We can match two different values of impedances by connecting them with a quarter-wave section of transmission line, provided the matching section has an impedance equal to the square root of the two impedances to be matched. In terms of a formula, we have:

$$Z_0 = \sqrt{Z1 \times Z2} \quad (5-15)$$

VELOCITY FACTOR

The velocity of a wave along a conductor, such as a transmission line, is not the same as the velocity of that wave in free space. The ratio of the two (actual velocity vs velocity in space) is known as the velocity factor. Obviously, velocity factor must always be less than 1, and, in typical lines varies from 0.6 to 0.97.

<i>Type of Line</i>	<i>Velocity factor (V)</i>
Two-wire open line (wire with air dielectric)	0.975
Parallel tubing (air dielectric)	0.95
Coaxial line (air dielectric)	0.85
Coaxial line (solid plastic dielectric)	0.66
Two-wire line (wire with plastic dielectric)	0.68-0.82
Twisted-pair line (rubber dielectric)	0.56-0.65

LENGTH OF TRANSMISSION LINE

Specification of the length of a transmission line in terms of quarter wave, half wave, etc. is a reference to electrical, not physical length. The physical length of a transmission line can be determined from:

$$L = \frac{984}{f} \times V \quad (5-16)$$

L is the length of the transmission line, in feet; f the frequency in megacycles and V is the velocity factor.

The above formula is for a line a full wavelength long. For a half wavelength:

$$L = \frac{492}{f} \times V$$

and for a quarter wavelength:

$$L = \frac{246}{f} \times V$$

TABLE OF ANTENNA TYPES

Type of Antenna	Description	Application
PARABOLIC REFLECTOR ANTENNAS	A radiator placed at the focus of a parabola which forms a reflecting surface. Variations in the shape of the parabola provide changes in the shape of the beam produced.	Used for radar.
COSECANT-SQUARED REFLECTORS	A reflector shaped to produce a beam pattern in which signal strengths which are proportional to the square of the cosecant of the angle between the horizontal and the line to the target.	Used for surface search by airborne radar sets.
HORN ANTENNAS	Consists of a waveguide with its mouth flared into a horn or funnel-like shape. The horn usually radiates into a reflector to provide the required beam shape.	Widely used for radar applications.

TABLE OF ANTENNA TYPES—Continued

Type of Antenna	Description	Application
<p>END-FED HERTZ (Zepp)</p>	<p>Half wavelength voltage-fed radiator fed at one end with tuned, open-wire feeders.</p>	<p>For receiving and transmitting in the 1.6- to 30-mc range. Most useful for multi-band operation where space is limited. Used for fixed-station installations.</p>
<p>CENTER-FED HERTZ (tuned doublet or center-fed Zepp)</p>	<p>A center-fed, half-wave doublet usually employing spaced feeders. Current fed on fundamental and voltage fed on all even harmonics.</p>	<p>For receiving and transmitting in the 1.6- to 30-mc range. Can be used on any frequency if the system as a whole can be tuned to that frequency.</p>
<p>FUCHS ANTENNA</p>	<p>Long-wire, voltage-fed radiator an even number of quarter waves long. One end of radiator brought directly to the transmitter or tuning unit without using a transmission line.</p>	<p>For transmitting and receiving on any frequency where simplicity and convenience are desired.</p>
<p>CORNER REFLECTOR</p>	<p>A half-wave radiator with two large metal sheets or screens arranged so their surfaces meet at an angle whose apex lies behind the radiator.</p>	<p>Used in the VHF and UHF ranges to provide directivity in the plane which bisects the angle formed by the reflector.</p>

TABLE OF ANTENNA TYPES—Continued

Type of Antenna	Description	Application
<p>MARCONI</p>	<p>A vertical radiator approximately one-quarter wavelength long at operating frequency. One end is grounded or worked against ground. May be fed at or near base with low-impedance line. Electrical length may be increased by using loading coil in series with base or near center of radiator or by using capacitive loading at the top.</p>	<p>Widely used for medium- and low-frequency receiving and transmitting where vertical polarization is desirable.</p>
<p>PARASITIC ARRAY</p>	<p>Consists of a radiator with a reflector behind and/or one or more directors in front. Produces a unidirectional radiation pattern. May be either vertically or horizontally polarized.</p>	<p>Used to develop high gain in one direction with little or no radiation or pickup in other directions. Used on all frequencies where these characteristics are desired and space is available.</p>
<p>RHOMBIC ANTENNA</p>	<p>A system consisting of four long-wire radiators arranged in the form of a diamond and fed at one end. If the corner opposite the feed point is open, response is bidirectional in a line running through these two corners. If the open end is terminated with the proper resistance, response is unidirectional in the direction of the terminated end. Gain may vary from 20 to 40 times that of a dipole, depending on the number of wavelengths in each leg.</p>	<p>Widely used where high gain and directivity is required. Can be used over a wide range of frequencies and is particularly useful when each leg is two or more wavelengths long on lowest frequency. Angle of radiation is lowered and vertical directivity narrowed by increasing length of legs and/or increasing operating frequency.</p>

TABLE OF ANTENNA TYPES — Continued

Type of Antenna	Description	Application
<p>VERTICAL ANTENNA</p>	<p>A one-half wavelength vertical radiator fed at the bottom through a quarter-wave matching stub. It is omnidirectional, produces vertical polarization, and can be fed conveniently from a wide range of feed-line impedances.</p>	<p>Practical for use at frequencies above about 7 mc. Normally used for fixed-frequency applications because of its extreme sensitivity to frequency changes. Efficiency falls off as frequency is raised.</p>
<p>COAXIAL ANTENNA (sleeve antenna)</p>	<p>Vertical radiator one-half wavelength long. Upper half consists of a relatively thin radiator and the bottom half a large diameter cylinder. Fed at the center from coaxial cable of 70 to 120 ohms.</p>	<p>Practical for frequencies above about 7 mc. Normally used for fixed frequency applications. Changes in frequency require that the antenna be retuned by varying length of the two halves of the radiator. Practical for operation up to about 100 mc.</p>
<p>GROUND-PLANE ANTENNA</p>	<p>Omnidirectional quarter-wave vertical radiator mounted above a horizontal reflecting surface. Its impedance is approximately 36 ohms or less.</p>	<p>Practical for producing vertically polarized waves at frequencies above about 7 mc and frequently used at frequencies as high as 300 mc.</p>
<p>CROW-FOOT ANTENNA</p>	<p>A low-frequency antenna consisting of a comparatively short vertical radiator with a 3-wire V-shaped flat top and a counterpoise having the same shape and size as the flat top.</p>	<p>Normally used where it is impractical to erect a quarter-wave vertical radiator. Used most frequently for reception and transmission in the 200 to 500-kc range.</p>

TABLE OF ANTENNA TYPES—Continued

Type of Antenna	Description	Application
<p>TURNSTILE ANTENNA</p>	<p>An omnidirectional, horizontally polarized antenna consisting of two half-wave radiators mounted at right angles to each other in the same horizontal plane. They are fed with equal currents 90 degrees out of phase. Gain is increased by stacking. Dipoles may be simple, folded, or special broadband types.</p>	<p>Normally used for transmission of FM and television broadcast signals.</p>
<p>SKIN ANTENNAS</p>	<p>Usually consist of an insulated section of the skin of an aircraft. Its radiation pattern varies with frequency, size of the radiating section, and position of the radiator on the aircraft.</p>	<p>Used for VHF and UHF reception and transmission in high-speed aircraft. Often used to replace fixed-wire antennas used in the 2 to 25-mc range.</p>
<p>ILAS ANTENNAS</p>	<p>Localizer antennas are of several different types. One type consists of two or more square loops. Glide path is usually produced by two stacked antennas. The lower antenna is usually a horizontal loop bisected by a metal screen and supported about 6 feet off the ground. The upper antenna is a V-shaped dipole radiator with a parasitic element. Marker beacon antennas may consist of colinear dipoles or arrays.</p>	<p>Used to enable pilots to locate the airport and to land the plane on the desired runway when weather conditions would prohibit a landing under visual flight reference.</p>

TABLE OF ANTENNA TYPES—Continued

Type of Antenna	Description	Application
<p>OMNI-RANGE (VOR)</p>	<p>Consists of two pairs of square-loop radiators surrounding a single square-loop radiator.</p>	<p>Used to provide navigation signals for aircraft in all directions from the range station.</p>
<p>ADCOCK ANTENNA</p>	<p>Consists of vertical radiators which produce bidirectional vertically polarized radiation.</p>	<p>Used in low-frequency radio ranges and for direction finding.</p>
<p>LOOP ANTENNAS</p>	<p>A loop of wire consisting of one or more turns arranged in the shape of a square, circle, or other convenient form. It produces a bidirectional pattern along the plane of the loop.</p>	<p>Normally used for direction-finding applications, particularly in ships and aircraft.</p>
<p>STUB MAST</p>	<p>A quarter-wave vertical radiator consisting of a metal sheath over a hardwood supporting mast. Fed with 50-ohm line with the outer conductor connected to a large metal ground surface.</p>	<p>Used for wide-band reception and transmission of frequencies above 100 mc. Normally used in aircraft installations.</p>

TABLE OF ANTENNA TYPES — Continued

Type of Antenna	Description	Application
<p>HALF RHOMBIC (inverted V or tilted wire)</p>	<p>A two-wire antenna with the legs in a vertical plane and in the shape of an inverted V. Directivity is in the plane of the legs. Feeding one end and leaving the other open result in bidirectivity. Terminating the free end with a suitable resistor produces unidirectional radiation in the direction of the termination. Gain and angle between legs depend on frequency and the number of wavelengths in each leg.</p>	<p>Used to provide high gain. Used where low angle of radiation is desirable. Usable over a wide frequency range. Bandwidth is greatest for terminated type. Angle of radiation is lowered as leg length and/or operating frequency is increased.</p>
<p>BEVERAGE ANTENNA</p>	<p>A directional long-wire horizontal antenna, two or more wavelengths long. The end nearest the distant receiving station is terminated with a 500-ohm resistor connected to a good counterpoise.</p>	<p>Used for transmitting and receiving vertically polarized waves. Often used for long-wave transoceanic broadcasts. Its input impedance is fairly constant so it can be used over a wide frequency range. Useful for frequencies between 300 kc and 3 mc. Highly suitable for use over dry, rocky soil. Never use over salt marshes or water.</p>
<p>FOLDED DIPOLE</p>	<p>A simple center-fed dipole with a second half-wave conductor connected across its ends. Spacing between the conductors is a very small fraction of a wavelength.</p>	<p>Its impedance is higher than that of a simple dipole. Applications same as simple dipole. Often used in parasitic arrays to raise the feedpoint impedance to a value which can be conveniently matched to transmission line.</p>

Chapter 6

MEASUREMENTS

While many types of instruments are used in electronics, one of the most popular is the D'Arsonval or moving-coil meter. Basically a current-measuring device, it can be easily adapted for the measurement of voltage and resistance.

SHUNT RESISTANCE

The range of a current-measuring meter—microammeter, milli-ammeter or ammeter—can easily be extended by shunting the meter

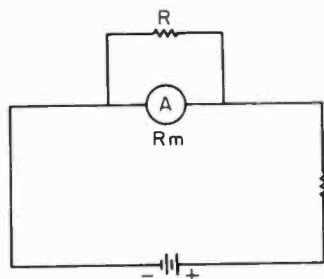


Fig. 6-1. The range of an ammeter can be extended by using shunts.

(Fig. 6-1) so that a large proportion of the current to be measured is bypassed around the meter.

$$R = \frac{R_m}{n - 1} \quad (6-1)$$

R is the value of shunt resistance; R_m the internal resistance of the meter. n is the multiplication factor of the original scale.

Since the shunt and the meter are in parallel, the same voltage drop must appear across both. That is:

$$E_{\text{shunt}} = E_{\text{meter}}$$

Considering this voltage as an IR drop, we can express the same thought as:

$$I_{\text{shunt}} \times R_{\text{shunt}} = I_{\text{meter}} \times R_{\text{meter}}$$

Dividing both sides by the shunt current, we will get:

$$R_{\text{shunt}} = \frac{I_{\text{meter}} \times R_{\text{meter}}}{I_{\text{shunt}}}$$

And, because a formula worded in this way is a bit awkward, we can conveniently abbreviate it to:

$$R = \frac{I_m \times R_m}{I_{sh}} \quad (6-2)$$

MULTIPLIER RESISTANCE

Both shunts and multipliers are resistors. The nature of a shunt is such that it must carry a large current load, hence its resistance value is low. A shunt, as its name implies, is put in parallel with the meter. A multiplier is put in series with it. Multipliers have large values of

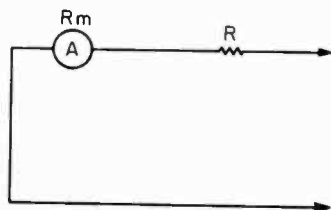


Fig. 6-2. Current-reading meter is changed to voltmeter by using series multiplier.

resistance compared to shunts. The purpose of a shunt is to extend the current-reading range of the meter. That of the multiplier (Fig. 6-2) is to permit the use of the ammeter as a voltage measuring device.

$$R = R_m (n - 1) \quad (6-3)$$

R is the value of multiplier resistance; R_m is the total resistance of

the meter; and n is the multiplication factor (factor by which the scale reading is to be multiplied.)

The required value of multiplier for a milliammeter can easily be found from:

$$R = \frac{1,000 \times E}{I}$$

I represents the full scale current reading of the meter (in milliamperes); C is the full-scale voltage reading that is required.

Alternatively, the multiplying value of a resistor can be found from:

$$M = \frac{R + R_m}{R_m} \quad (6-4)$$

Here M is the multiplication that will result from using the resistor; R is the resistance of the multiplier resistor, and R_m is the resistance of the meter. All resistance values are in ohms.

RESISTANCE MEASUREMENTS

An ammeter can have its range extended by using one or more shunts and it can be used to measure a variety of voltages by using a selection of multiplier resistors. In both instances, the voltage source is supplied by the unit under measurement.

An ammeter can be used for the measurement of resistance by including a cell or battery as part of the instrument. The simplest type

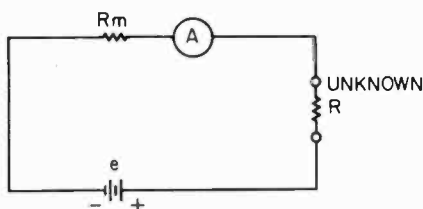


Fig. 6-3. Current-reading meter can be used for the measurement of resistance.

of ohmmeter is shown in Fig. 6-3. For this circuit, the value of the unknown resistance, R , can be measured by:

$$R = \frac{R_m \times e}{E} - R_m \quad (6-5)$$

R is the unknown whose value is being checked; e is the voltage

supplied by the battery; R_m is the resistance of the meter and E is the voltage indicated by the meter with R connected.

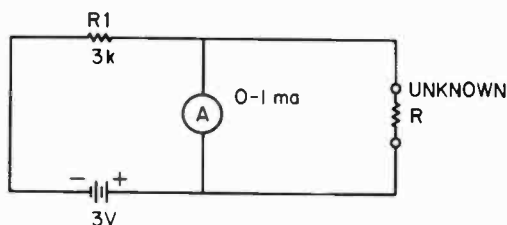


Fig. 6-4. Simple ohmmeter circuit. The resistance to be measured is in shunt with the milliammeter.

The circuit is not suited for the measurement of low values of resistance.

Fig. 6-4 shows another ohmmeter circuit. In this arrangement, the formula for finding the value of the unknown resistor is:

$$R = \frac{R_m \times I_2}{I_1 - I_2} \quad (6-6)$$

If a meter having a full-scale deflection of 1 milliampere is used, then the battery can be 3 volts and R_1 3,000 ohms.

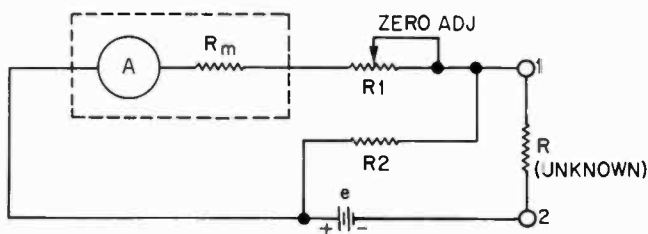


Fig. 6-5. More elaborate ohmmeter circuit using meter having a higher sensitivity.

I_1 is the open circuit current—that is, with the unknown resistor disconnected. I_2 is the current with the unknown resistor in place.

For use with a higher sensitivity meter, the circuit of Fig. 6-5 is preferable.

$$R = \frac{R_2 \times e}{E} - R_2 \quad (6-7)$$

In this formula, e is the meter reading with terminals 1 and 2 shorted;

E is the meter reading with the unknown resistor R , connected in place. The value of R_2 is experimentally selected and is determined by the resistance range to be measured.

BRIDGES

Bridges are resistive networks, or networks consisting of combinations of resistance, capacitance and inductance. Bridge circuits are used for making more precise measurements of resistance than is possible with an ohmmeter. Bridge circuits are also used for making measurements of inductance and capacitance.

WHEATSTONE BRIDGE

Bridges can be conveniently arranged into two major groups: those using dc as the source voltage and those using ac. A greater number of bridges, by far, use ac.

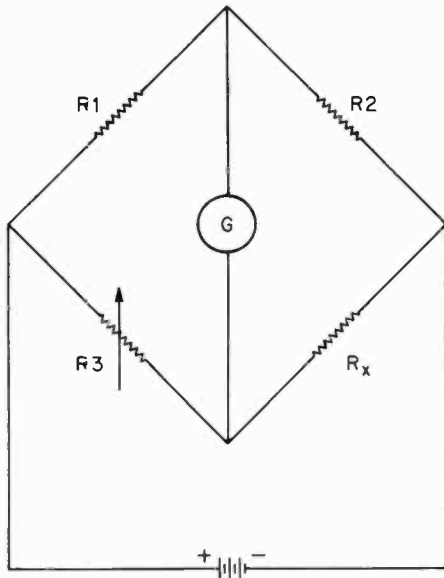


Fig. 6-6. When the Wheatstone bridge is balanced, the voltage across the galvanometer is zero.

Probably the best known of all dc bridges is the Wheatstone, shown in Fig. 6-6. The indicating meter is a galvanometer. R_3 is adjusted

until the galvanometer (a zero-center reading type) is at zero. The value of the unknown is then read from a scale or a calibrated dial. In Fig. 6-6, R_3 is a calibrated resistor.

$$R_x = R_3 \times \frac{R_2}{R_1} \quad (6-8)$$

SLIDE WIRE BRIDGE

The slide-wire bridge (Fig. 6-7) makes use of a resistance on which

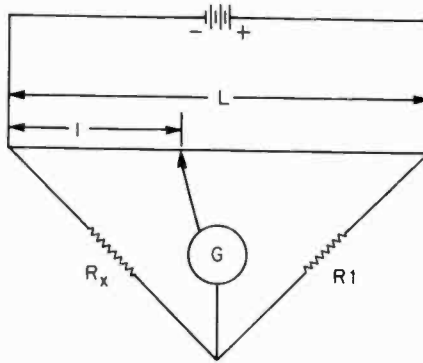


Fig. 6-7. Slide-wire circuit is a dc bridge.

is mounted a slider. The slider is adjusted until the galvanometer reads zero. The value of the unknown resistance is then computed by:

$$R_x = \frac{l}{L-l} \times R_1 \quad (6-9)$$

AC BRIDGE

The ac bridge shown in Fig. 6-8 is a modified form of a Wheatstone. It uses an ac voltage in the audible range and a pair of phones as a null indicator. Although Z_1 and Z_2 are shown as impedances, they are non-inductive resistors. Z_3 is a standard capacitor or coil. Z_x is the unknown impedance. Z_3 and Z_4 must be similar in that they must be the same type of reactance (that is inductive or capacitive) and must have similar phase angles.

$$Z_x = Z_3 \times \frac{Z_1}{Z_2} \quad (6-10)$$

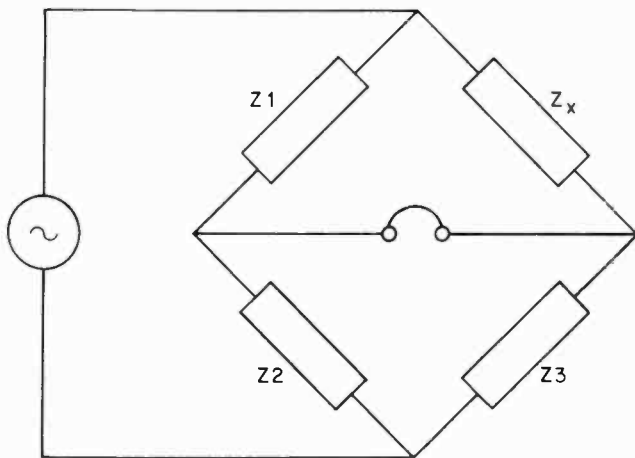


Fig. 6-8. *Wheatstone bridge using ac as the source voltage and earphones as an indicator. Earphones are not as good for null indication as a meter.*

THE SCOPE

The scope can be used for the measurement of spot frequencies by using the test setup shown in Fig. 6-9. The unknown frequency, in

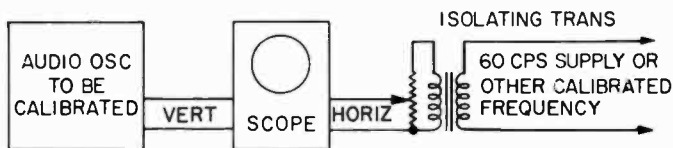


Fig. 6-9. *Scope setup for the calibration of unknown frequencies.*

this illustration from an audio oscillator in need of calibration, is fed into the vertical terminals of the scope. The known frequency can be the 60-cycle power line [for calibration up to about 500 cycles]. For calibration of higher frequencies, a 1,000-cycle standard can be used.

Fig. 6-10 shows a number of frequency ratios. A circle indicates that the frequencies of the known and unknown are the same.

To calculate the frequency ratio, count all the loops along the

horizontal and vertical edges. To find the ratio, divide the number of vertical edge loops by the number of horizontal edge loops. This will

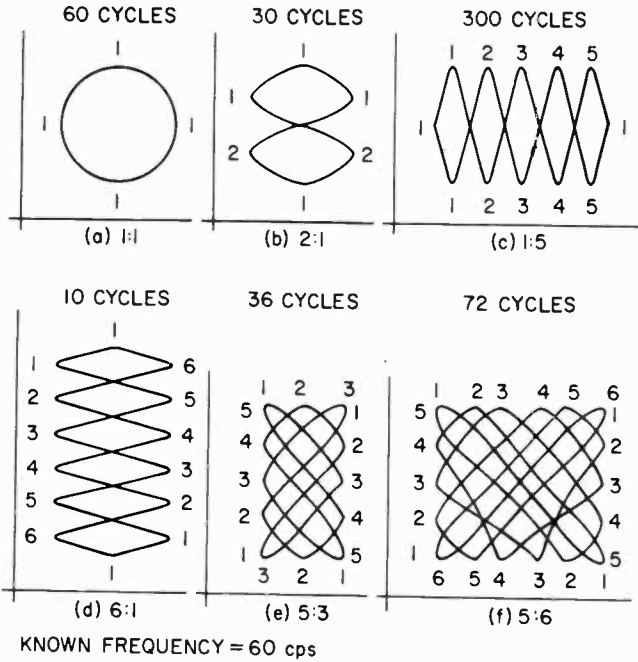


Fig. 6-10. Lissajous patterns obtained by comparing 60 cycles with various other frequencies.

give you the ratio of the standard to the unknown frequency. Thus, in Fig. 6-10-b, the unknown frequency is 30 cycles.

Chapter 7

TABLES AND DATA

Conversion Factors

<i>To Change</i>			<i>To Change Back</i>		
<i>From</i>	<i>To</i>	<i>Multiply by</i>	<i>From</i>	<i>To</i>	<i>Multiply by</i>
LENGTH			LENGTH		
Mils	Mm.	.0254	Mm.	Mils	39.37
Mils	In.	.001	In.	Mils	1,000.
Mm.	In.	.03937	In.	Mm.	25.4
Cm.	In.	.3937	In.	Cm.	2.54
Cm.	Ft.	.03281	Ft.	Cm.	30.48
In.	M.	.0254	M.	In.	39.37
Ft.	M.	.3048	M.	Ft.	3.2808
Yds.	M.	.9144	M.	Yds.	1.0936
Kilometer	Miles	.6214	Miles	Kilometer	1.6093
AREA			AREA		
Cir. Mils	Sq. In.	.0000007854	Sq. In.	Cir. Mils	1,273,240.
Cir. Mils	Sq. Mils	.7854	Sq. Mils	Cir. Mils	1.2732
Cir. Mils	Sq. Mm.	.0005066	Sq. Mm.	Cir. Mils	1,973.51
Sq. Mm.	Sq. In.	.00155	Sq. In.	Sq. Mm.	645.16
Sq. Mils	Sq. In.	.000001	Sq. In.	Sq. Mils	1,000,000.
Sq. Cm.	Sq. In.	.155	Sq. In.	Sq. Cm.	6.4516
Sq. Ft.	Sq. M.	.0929	Sq. M.	Sq. Ft.	10.764
VOLUME			VOLUME		
Cu. In.	Liters	.01639	Liters	Cu. In.	61.023
Cu. In.	Gals.	.004329	Gals.	Cu. In.	231.
Liters	Gals.	.26417	Gals.	Liters	3.7854
Cu. Cm.	Cu. In.	.06102	Cu. In.	Cu. Cm.	16.387
Cu. Cm.	Gal.	.000264	Gal.	Cu. Cm.	3,785.4

POWER			POWER		
Ft.-Lbs.			Ft.-Lbs.		
per Min.	H.P.	.0000303	per Min.		33,000.
Ft.-Lbs.			H.P.	Ft.Lbs.	
per Sec.	H.P.	.001818	per Min.		550.
Ft.-Lbs.			Watts	Ft.-Lbs.	
per Min.	Watts	.0226	per Min.		44.25
Ft.-Lbs.			Watts	Ft.-Lbs.	
per Sec.	Watts	1.356	per Sec.		.7373
Watts	H.P.	.001341	H.P.	Watts	746.
B.T.U. per Hr.	H.P.	.000393	H.P.	B.T.U. per Hr.	2.545.

ENERGY			ENERGY		
Ergs	Joules	.0000001	Joules	Ergs	10,000,000.
Joules	Gram-Calories	.2388	Gram-Calories	Joules	4.186
Joules	Kg.-M.	10198	Kg.-M.	Joules	9.8117
Joules	Ft.-Lbs.	.7375	Ft.-Lbs.	Joules	1.356
Ft.-Lbs.	Kg.-M.	.1383	Kg.-M.	Ft.-Lbs.	7.233
Gram-Calories	B.T.U.	.003968	B.T.U.	Gram-Calories	252.
Joules	B.T.U.	.000947	B.T.U.	Joules	1,055.
Ft.-Lbs.	B.T.U.	.001285	B.T.U.	Ft.-Lbs.	778.
B.T.U.	Watt-Hrs.	.293	Watt-Hrs.	B.T.U.	3.416

WEIGHTS			WEIGHTS		
Lbs. (Avdp.)	Kgs.	.4536	Kgs.	Lbs. (Avdp.)	2.2046
Oz. (Avdp.)	Lbs. (Avdp.)	.0625	Lbs. (Avdp.)	Oz. (Avdp.)	16.
Oz. (Troy)	Lbs. (Troy)	.0833	Lbs. (Troy)	Oz. (Troy)	12.
Oz. (Avdp.)	Oz. (Troy)	.9115	Oz. (Troy)	Oz. (Avdp.)	1.097
Lbs. (Troy)	Lbs. (Avdp.)	.82286	Lbs. (Avdp.)	Lbs. (Troy)	1.2153
Oz. (Avdp.)	Lbs. (Troy)	.0759	Lbs. (Troy)	Oz. (Avdp.)	13.166
Oz. (Troy)	Lbs. (Avdp.)	.0686	Lbs. (Avdp.)	Oz. (Troy)	14.58
Grains	Oz. (Troy)	.00209	Oz. (Troy)	Grains	480.
Grains	Oz. (Avdp.)	.002285	Oz. (Avdp.)	Grains	437.5
Milligrams	Carats	.005	Carats	Milligrams	200.

MISCELLANEOUS			MISCELLANEOUS		
Ohms per Ft.	Ohms per Meter	.3048	Ohms per Meter	Ohms per Ft.	3.2808
Ohms per Kilometer	Ohms per 1000 Ft.	.3048	Ohms per 1000 Ft.	Ohms per Kilometer	3.2808
Ohms per Kilometer	Ohms per 1000 Yds.	.9144	Ohms per 1000 Yds.	Ohms per Kilometer	1.0936
Kg. per Kilometer	Lbs. per 1000 Ft.	.6719	Lbs. per 1000 Ft.	Kg. per Kilometer	1.488
Lbs. per 1000 Yds.	Kg. per Kilometer	.4960	Kg. per Kilometer	Lbs. per 1000 Yds.	2.016

Equivalents			
<i>Unit</i>	<i>Equivalents</i>	<i>Unit</i>	<i>Equivalents</i>
1 H.P.	.746 Watts	1 Kw	1,000 Joules per Sec.
1 H.P.	.746 Kw.	1 Kw	1.34 H.P.
1 H.P.	33,000 Ft.-Lbs. per Min.	1 Kw	44,250 Ft.-Lbs. per Min.
1 H.P.	550 Ft.-Lbs. per Sec.	1 Kw	737.3 Ft.-Lbs. per Sec.
1 H.P.	2.545 B.T.U. per Hr.	1 Kw	3.412 B.T.U. per Hr.
1 H.P.	0.175 Lbs. Carbon oxidized per Hr.	1 Kw	0.227 Lbs. Carbon oxidized per Hr.
1 H.P.	17 Lbs. Water per Hr. heated from 62-212° F.	1 Kw	22.75 Lbs. Water per Hr. heated from 62-212° F.
1 H.P.	2.64 Lbs. Water per Hr. evaporated from and at 212° F.	1 Kw	3.53 Lbs. Water per Hr. evaporated from and at 212° F.

This is a list of abbreviations used in the formulas and data presented in this book. Of necessity, letters may often represent various (and quite unrelated) ideas.

<i>Electronic Abbreviations</i>		<i>Electronic Abbreviations</i>	
<i>R</i>	resistance	<i>db</i>	decibels
<i>G</i>	conductance	<i>N_n</i>	nepers
ρ	specific resistance or resistivity	ϵ	natural base (2.718281)
<i>F</i> [°]	degrees Fahrenheit	<i>vu</i>	volume unit
<i>C</i> [°]	degrees Centigrade	<i>E_p</i>	plate voltage
<i>E</i>	voltage	<i>E_g</i>	grid voltage
<i>I</i>	current	Δ	change of
<i>P</i>	power	μ	amplification factor
<i>P_o</i>	output power	<i>r_p</i>	plate resistance
<i>P_i</i>	input power	<i>g_m</i>	mutual conductance
η	efficiency	<i>I_p</i>	plate current
dc	direct current	<i>C_i</i>	input capacitance
ac	alternating current	<i>C_{pk}</i>	interelectrode capacitance, plate to cathode
<i>L</i>	inductance	<i>C_{gk}</i>	interelectrode capacitance, grid to cathode
<i>C</i>	capacitance	<i>A</i>	amplification
<i>t</i>	time constant	β	feedback voltage
<i>T</i>	time	<i>K</i>	amplification with negative feedback
λ	wavelength	<i>i_c</i>	collector current
<i>f</i>	frequency	<i>i_e</i>	emitter current
<i>f_r</i>	resonant frequency	α	current gain
<i>cps</i>	cycles per second	β	current gain
<i>kc</i>	kilocycles	<i>k</i>	correction factor
<i>mc</i>	megacycles	<i>SWR</i>	standing wave ratio
μf	microfarad	<i>j</i>	$\sqrt{-1}$ (j-operator)
<i>pf</i>	picofarad (same as micromicrofarad)	<i>R_m</i>	meter resistance
<i>E_{p-p}</i>	peak-to-peak voltage	<i>n</i>	multiplication factor
<i>V</i>	velocity		
<i>D</i>	distance		
π	3.1416		
ω	$2 \times \pi \times f$		
α	ωt		
<i>Q</i>	coulomb		
<i>RMS</i>	root-mean-square		
<i>Z</i>	impedance		
<i>X_L</i>	inductive reactance		
<i>X_C</i>	capacitive reactance		
<i>M</i>	mutual inductance		
<i>k</i>	coefficient of coupling		
<i>N_p</i>	primary turns		
<i>N_s</i>	secondary turns		
<i>N_s/N_p</i>	turns ratio		
θ	phase angle		
<i>B</i>	susceptance		
<i>Y</i>	admittance		
<i>pf</i>	power factor		
<i>N_b</i>	bels		

Decimal Equivalents of Fractions of an Inch

Decimal	Fractions of an Inch				
	64th	32nd	16th	1/8th	1/4th
.015625	1				
.031250	2	1			
.046875	3				
.062500	4	2	1		
.078125	5				
.093750	6	3			
.109375	7				
.125000	8	4	2	1	
.140625	9				
.156250	10	5			
.171875	11				
.187500	12	6	3		
.203125	13				
.218750	14	7			
.234375	15				
.250000	16	8	4	2	1
.265625	17				
.281250	18	9			
.296875	19				
.312500	20	10	5		
.328125	21				
.343750	22	11			
.359375	23				
.375000	24	12	6	3	
.390625	25				
.406250	26	13			
.421875	27				
.437500	28	14	7		
.453125	29				
.468750	30	15			
.484375	31				
.500000	32	16	8	4	2
.515625	33				
.531250	34	17			
.546875	35				
.562500	36	18	9		
.578125	37				
.593750	38	19			
.609375	39				
.625000	40	20	10	5	

Decimal Equivalents of Fractions of an Inch—Continued

<i>Fractions of an Inch</i>					
<i>Decimal</i>	<i>64th</i>	<i>32nd</i>	<i>16th</i>	<i>1/8th</i>	<i>1/4th</i>
.640625	41				
.656250	42	21			
.671875	43				
.687500	44	22	11		
.703125	45				
.718750	46	23			
.734375	47				
.750000	48	24	12	6	3
.765625	49				
.781250	50	25			
.796875	51				
.812500	52	26	13		
.828125	53				
.843750	54	27			
.859375	55				
.890625	57	28	14	7	
.906250	58	29			
.921875	59				
.937500	60	30	15		
.953125	61				
.968750	62	31			
.984375	63				
1.000000	64	32	16	8	4

Wavelength and Frequency Bands

<i>Frequency</i>	<i>Description</i>	<i>Abbreviation</i>
Below 30 kc	very-low frequency	VLF
30 to 300 kc	low frequency	LF
300 to 3,000 kc	medium frequency	MF
3,000 to 30,000 kc	high frequency	HF
30 to 300 mc	very-high frequency	VHF
300 to 3,000 mc	ultra-high frequency	UHF
3,000 to 30,000 mc	super-high frequency	SHF
30,000 to 300,000 mc (30 gc to 300 gc)*	extremely-high frequency	EHF

*gc = gigacycle. A gigacycle is 10^9 cycles (Formerly kilomegacycles. Has common usage in microwaves.)

Math Symbols

\times or \cdot	Multiplied by
\div or $:$	Divided by
$+$	Positive. Plus. Addition
$-$	Negative. Minus. Subtraction
\pm	Positive or negative. Plus or minus
\mp	Negative or positive. Minus or plus
$=$ or $::$	Equals
\equiv	identify
\approx	Is approximately equal to
\neq	Does not equal
$>$	Is greater than
\gg	Is much greater than
$<$	Is less than
\ll	Is much less than
\geq	Greater than or equal to
\leq	Less than or equal to
\therefore	Therefore
\sphericalangle	Angle
\sphericalangle	Angles
\triangle	Change. Increase or decrease
\perp	Perpendicular to
\parallel	Parallel to
$ n $	Absolute value of n
$\sqrt{\quad}$	Square root
$\sqrt[3]{\quad}$	cube root

Math Data

$\pi = 3.14$	$\sqrt{\frac{\pi}{2}} = 1.25$
$2\pi = 6.28$	$\sqrt{2} = 1.41$
$(2\pi)^2 = 39.5$	$\sqrt{3} = 1.73$
$4\pi = 12.6$	$\frac{1}{\sqrt{2}} = 0.707$
$\pi^2 = 9.87$	$\frac{1}{\sqrt{3}} = 0.577$
$\frac{\pi}{2} = 1.57$	$\log \pi = 0.497$
$\frac{1}{\pi} = 0.318$	$\log \frac{\pi}{2} = 0.196$
$\frac{1}{2\pi} = 0.159$	$\log \pi^2 = 0.994$
$\frac{1}{\pi^2} = 0.101$	$\log \sqrt{\pi} = 0.248$
$\frac{1}{\sqrt{\pi}} = 0.564$	Base of natural logs $e = 2.718$
$\sqrt{\pi} = 1.77$	1 radian = $180^\circ/\pi = 57.3^\circ$
	$360^\circ = 2\pi$ radians

Greek Alphabet

<i>Greek Capital Letter</i>	<i>Greek Lowercase Letter</i>	<i>Greek Name</i>
Α	α	Alpha
Β	β	Beta
Γ	γ	Gamma
Δ	δ	Delta
Ε	ε	Epsilon
Ζ	ζ	Zeta
Η	η	Eta
Θ	θ	Theta
Ι	ι	Iota
Κ	κ	Kappa
Λ	λ	Lambda
Μ	μ	Mu
Ν	ν	Nu
Ξ	ξ	Xi
Ο	ο	Omicron
Π	π	Pi
Ρ	ρ	Rho
Σ	σ	Sigma
Τ	τ	Tau
Υ	υ	Upsilon
Φ	φ	Phi
Χ	χ	Chi
Ψ	ψ	Psi
Ω	ω	Omega

Comparison of electric and magnetic circuits.

	<i>Electric circuit</i>	<i>Magnetic circuit</i>
Force.....	Volt, E, or e.m.f.	Gilberts, F, or m.m.f.
Flow.....	Ampere, I	Flux, Φ, in maxwells
Opposition.....	Ohms, R	Reluctance, R, or rels
Law.....	Ohm's law, $I = \frac{E}{R}$	Rowland's law, $\Phi = \frac{F}{R}$
Intensity of force.....	Volts per cm. of length	$H = \frac{1.257IN}{l}$, gilberts per centimeter of length.
Density.....	Current density – for example, amperes per cm. ² .	Flux density – for example, lines per cm. ² , or gauss.

POWERS OF TWO

n	2^n	n	2^n
1	2	41	21990 23255 552
2	4	42	43980 46511 104
3	8	43	87960 93022 208
4	16	44	17592 18604 4416
5	32	45	35184 37208 8832
6	64	46	70368 74417 7664
7	128	47	14073 74883 55328
8	256	48	28147 49767 10656
9	512	49	56294 99534 21312
10	1024	50	11258 99906 84262 4
11	2048	51	22517 99813 68524 8
12	4096	52	45035 99627 37049 6
13	8192	53	90071 99254 74099 2
14	16384	54	18014 39850 94819 84
15	32768	55	36028 79701 89639 68
16	65536	56	72057 59403 79279 36
17	13107 2	57	14411 51880 75855 872
18	26214 4	58	28823 03761 51711 744
19	52428 8	59	57646 07523 03423 488
20	10485 76	60	11529 21504 60684 6976
21	20971 52	61	23058 43009 21369 3952
22	41943 04	62	46116 86018 42738 7904
23	83886 08	63	92233 72036 85477 5808
24	16777 216	64	18446 74407 37095 51616
25	33554 432	65	36893 48814 74191 03232
26	67108 864	66	73786 97629 48382 06464
27	13421 7728	67	14757 39525 89676 41292 8
28	26843 5456	68	29514 79051 79352 82585 6
29	53687 0912	69	59029 58103 58705 65171 2
30	10737 41824	70	11805 91620 71741 13034 24
31	21474 83648	71	23611 83241 43482 26068 48
32	42949 67296	72	47223 66482 86964 52136 96
33	85899 34592	73	94447 32965 73929 04273 92
34	17179 86918 4	74	18889 46593 14785 80854 784
35	34359 73836 8	75	37778 93186 29571 61709 568
36	68719 47673 6	76	75557 86372 59143 23419 136
37	13743 89534 72	77	15111 57274 51828 64683 8272
38	27487 79069 44	78	30223 14549 03657 29367 6544
39	54975 58138 88	79	60446 29098 07314 58735 3088
40	10995 11627 776	80	12089 25819 61462 91747 06176

n	2^n
81	24178 51639 22925 83494 12352
82	48357 03278 45851 66988 24704
83	96714 06556 91703 33976 49408
84	19342 81311 38340 66795 29881 6
85	38685 62622 76681 33590 59763 2
86	77371 25245 53362 67181 19526 4
87	15474 25049 10672 53436 23905 28
88	30948 50098 21345 06872 47810 56
89	61897 00196 42690 13744 95621 12
90	12379 40039 28538 02748 99124 224
91	24758 80078 57076 05497 98248 448

POWERS OF TWO

Continued

n	2^n
92	49517 60157 14152 10995 96496 896
93	99035 20314 28304 21991 92993 792
94	19807 04062 85660 84398 38598 7584
95	39614 08125 71321 68796 77197 5168
96	79228 16251 42643 37593 54395 0336
97	15845 63250 28528 67518 70879 00672
98	31691 26500 57057 35037 41758 01344
99	63382 53001 14114 70074 83516 02688
100	12676 50600 22822 94014 96703 20537 6

FUNDAMENTALS OF BOOLEAN ALGEBRA

Definitions

- $a, b, c, \text{ etc.}$ Symbols used in symbolic logic
- $a \cdot b$ or ab Read as: a and b
- $a + b$ Read as: a or b
- a' or \bar{a} Read as: not a
- 1..... "True" or "On"
- 0..... "False" or "Off"

Relations and Rules of Operation

1. $a + b = (a'b)'$; $ab = (a' + b)'$
DeMorgan's Theorem
2. $1 = 0'$; $0 = 1'$
3. $a + a = a$; $a \cdot a = a$
4. $a + 1 = 1$; $a \cdot 1 = a$
5. $a + b = b + a$; $ab = ba$
Commutative Laws
6. $(a + b) + c = a + (b + c)$
 $(ab)c = a(bc)$
Associative Laws
7. $a(b + c) = ab + ac$
8. $(a + b)(a + c) = a + bc$
Special Distributive Law
9. $a + a' = 1$; $a \cdot a' = 0$
10. $(a')' = a$

SQUARES, CUBES AND ROOTS

n	n^2	\sqrt{n}	$\sqrt{10n}$	n^3
1	1	1.000000	3.162278	1
2	4	1.414214	4.472136	8
3	9	1.732051	5.477226	27
4	16	2.000000	6.324555	64
5	25	2.236068	7.071068	125
6	36	2.449490	7.745967	216
7	49	2.645751	8.366600	343
8	64	2.828427	8.944272	512
9	81	3.000000	9.486833	729
10	100	3.162278	10.00000	1,000
11	121	3.316625	10.48809	1,331
12	144	3.464102	10.95445	1,728
13	169	3.605551	11.40175	2,197
14	196	3.741657	11.83216	2,744
15	225	3.872983	12.24745	3,375
16	256	4.000000	12.64911	4,096
17	289	4.123106	13.03840	4,913
18	324	4.242641	13.41641	5,832
19	361	4.358899	13.78405	6,859
20	400	4.472136	14.14214	8,000
21	441	4.582576	14.49138	9,261
22	484	4.690416	14.83240	10,648
23	529	4.795832	15.16575	12,167
24	576	4.898979	15.49193	13,824
25	625	5.000000	15.81139	15,625
26	676	5.099020	16.12452	17,576
27	729	5.196152	16.43168	19,683
28	784	5.291503	16.73320	21,952
29	841	5.385165	17.02939	24,389
30	900	5.477226	17.32051	27,000
31	961	5.567764	17.60682	29,791
32	1,024	5.656854	17.88854	32,768
33	1,089	5.744563	18.16590	35,937
34	1,156	5.830952	18.43909	39,304
35	1,225	5.916080	18.70829	42,875
36	1,296	6.000000	18.97367	46,656
37	1,369	6.082763	19.23538	50,653
38	1,444	6.164414	19.49359	54,872
39	1,521	6.244998	19.74842	59,319
40	1,600	6.324555	20.00000	64,000
41	1,681	6.403124	20.24846	68,921
42	1,764	6.480741	20.49390	74,088
43	1,849	6.557439	20.73644	79,507
44	1,936	6.633250	20.97618	85,184
45	2,025	6.708204	21.21320	91,125
46	2,116	6.782330	21.44761	97,336
47	2,209	6.855655	21.67948	103,823
48	2,304	6.928203	21.90890	110,592
49	2,401	7.000000	22.13594	117,649
50	2,500	7.071068	22.36068	125,000

SQUARES, CUBES AND ROOTS—Continued

n	n^2	\sqrt{n}	$\sqrt{10n}$	n^3
50	2,500	7.071068	22.36068	125,000
51	2,601	7.141428	22.58318	132,651
52	2,704	7.211103	22.80351	140,608
53	2,809	7.280110	23.02173	148,877
54	2,916	7.348469	23.23790	157,464
55	3,025	7.416198	23.45208	166,375
56	3,136	7.483315	23.66432	175,616
57	3,249	7.549834	23.87467	185,193
58	3,364	7.615773	24.08319	195,112
59	3,481	7.681146	24.28992	205,379
60	3,600	7.745967	24.49490	216,000
61	3,721	7.810250	24.69818	226,981
62	3,844	7.874008	24.89980	238,328
63	3,969	7.937254	25.09980	250,047
64	4,096	8.000000	25.29822	262,144
65	4,225	8.062258	25.49510	274,625
66	4,356	8.124038	25.69047	287,496
67	4,489	8.185353	25.88436	300,763
68	4,624	8.246211	26.07681	314,432
69	4,761	8.306624	26.26785	328,509
70	4,900	8.366600	26.45751	343,000
71	5,041	8.426150	26.64583	357,911
72	5,184	8.485281	26.83282	373,248
73	5,329	8.544004	27.01851	389,017
74	5,476	8.602325	27.20294	405,224
75	5,625	8.660254	27.38613	421,875
76	5,776	8.717798	27.56810	438,976
77	5,929	8.774964	27.74887	456,533
78	6,084	8.831761	27.92848	474,552
79	6,241	8.888194	28.10694	493,039
80	6,400	8.944272	28.28427	512,000
81	6,561	9.000000	28.46050	531,441
82	6,724	9.055385	28.63564	551,368
83	6,889	9.110434	28.80972	571,787
84	7,056	9.165151	28.98275	592,704
85	7,225	9.219544	29.15476	614,125
86	7,396	9.273618	29.32576	636,056
87	7,569	9.327379	29.49576	658,503
88	7,744	9.380832	29.66479	681,472
89	7,921	9.433981	29.83287	704,969
90	8,100	9.486833	30.00000	729,000
91	8,281	9.539392	30.16621	753,571
92	8,464	9.591663	30.33150	778,688
93	8,649	9.643651	30.49590	804,357
94	8,836	9.695360	30.65942	830,584
95	9,025	9.746794	30.82207	857,375
96	9,216	9.797959	30.98387	884,736
97	9,409	9.848858	31.14482	912,673
98	9,604	9.899495	31.30495	941,192
99	9,801	9.949874	31.46427	970,299
100	10,000	10.00000	31.62278	1,000,000

SQUARES, CUBES AND ROOTS—Continued

$\sqrt[3]{n}$	$\sqrt[3]{10n}$	$\sqrt[3]{100n}$	n
1.000000	2.154435	4.641589	1
1.259921	2.714418	5.848035	2
1.442250	3.107233	6.694330	3
1.587401	3.419952	7.368063	4
1.709976	3.684031	7.937005	5
1.817121	3.914868	8.434327	6
1.912931	4.121285	8.879040	7
2.000000	4.308869	9.283178	8
2.080084	4.481405	9.654894	9
2.154435	4.641589	10.00000	10
2.223980	4.791420	10.32280	11
2.289428	4.932424	10.62659	12
2.351335	5.065797	10.91393	13
2.410142	5.192494	11.18689	14
2.466212	5.313293	11.44714	15
2.519842	5.428835	11.69607	16
2.571282	5.539658	11.93483	17
2.620741	5.646216	12.16440	18
2.668402	5.748897	12.38562	19
2.714418	5.848035	12.59921	20
2.758924	5.943922	12.80579	21
2.802039	6.036811	13.00591	22
2.843867	6.126926	13.20006	23
2.884499	6.214465	13.38866	24
2.924018	6.299605	13.57209	25
2.962496	6.382504	13.75069	26
3.000000	6.463304	13.92477	27
3.036589	6.542133	14.09460	28
3.072317	6.619106	14.26043	29
3.107233	6.694330	14.42250	30
3.141381	6.767899	14.58100	31
3.174802	6.839904	14.73613	32
3.207534	6.910423	14.88806	33
3.239612	6.979532	15.03695	34
3.271066	7.047299	15.18294	35
3.301927	7.113787	15.32619	36
3.332222	7.179054	15.46680	37
3.361975	7.243156	15.60491	38
3.391211	7.306144	15.74061	39
3.419952	7.368063	15.87401	40
3.448217	7.428959	16.00521	41
3.476027	7.488872	16.13429	42
3.503398	7.547842	16.26133	43
3.530348	7.605905	16.38643	44
3.556893	7.663094	16.50964	45
3.583048	7.719443	16.63103	46
3.608826	7.774980	16.75069	47
3.634241	7.829735	16.86865	48
3.659306	7.883735	16.98499	49
3.684031	7.937005	17.09976	50

SQUARES, CUBES AND ROOTS—Continued

$\sqrt[3]{n}$	$\sqrt[3]{10n}$	$\sqrt[3]{100n}$	<i>n</i>
3.684031	7.937005	17.09976	50
3.708430	7.989570	17.21301	51
3.732511	8.041452	17.32478	52
3.756286	8.092672	17.43513	53
3.779763	8.143253	17.54411	54
3.802952	8.193213	17.65174	55
3.825862	8.242571	17.75808	56
3.848501	8.291344	17.86316	57
3.870877	8.339551	17.96702	58
3.892996	8.387207	18.06969	59
3.914868	8.434327	18.17121	60
3.936497	8.480926	18.27160	61
3.957892	8.527019	18.37091	62
3.979057	8.572619	18.46915	63
4.000000	8.617739	18.56636	64
4.020726	8.662391	18.66256	65
4.041240	8.706588	18.75777	66
4.061548	8.750340	18.85204	67
4.081655	8.793659	18.94536	68
4.101566	8.836556	19.03778	69
4.121285	8.879040	19.12931	70
4.140818	8.921121	19.21997	71
4.160168	8.962809	19.30979	72
4.179339	9.004113	19.39877	73
4.198336	9.045042	19.48695	74
4.217163	9.085603	19.57434	75
4.235824	9.125805	19.66095	76
4.254321	9.165656	19.74681	77
4.272659	9.205164	19.83192	78
4.290840	9.244335	19.91632	79
4.308869	9.283178	20.00000	80
4.326749	9.321698	20.08299	81
4.344481	9.359902	20.16530	82
4.362071	9.397796	20.24694	83
4.379519	9.435388	20.32793	84
4.396830	9.472682	20.40828	85
4.414005	9.509685	20.48800	86
4.431048	9.546403	20.56710	87
4.447960	9.582840	20.64560	88
4.464745	9.619002	20.72351	89
4.481405	9.654894	20.80084	90
4.497941	9.690521	20.87759	91
4.514357	9.725888	20.95379	92
4.530655	9.761000	21.02944	93
4.546836	9.795861	21.10454	94
4.562903	9.830476	21.17912	95
4.578857	9.864848	21.25317	96
4.594701	9.898983	21.32671	97
4.610436	9.932884	21.39975	98
4.626065	9.966555	21.47229	99
4.641589	10.00000	21.54435	100

POWERS OF NUMBERS

n	n^2	n^3	n^4	n^5	n^6
1	1	1	1	1	1
2	16	32	64	128	256
3	81	243	729	2187	6561
4	256	1024	4096	16384	65536
5	625	3125	15625	78125	390625
6	1296	7776	46656	279936	1679616
7	2401	16807	117649	823543	5764801
8	4096	32768	262144	2097152	16777216
9	6561	59049	531441	4782969	43046721
$\times 10^8$					
10	10000	100000	1000000	10000000	1.000000
11	14641	161051	1771561	19487171	2.143589
12	20736	248832	2985984	35831808	4.299817
13	28561	371293	4826809	62748517	8.157307
14	38416	537824	7529536	105413504	14.757891
15	50625	759375	11390625	170859375	25.628906
16	65536	1048576	16777216	268435456	42.949673
17	83521	1419857	24137569	410338673	69.757574
18	104976	1889568	34012224	612220032	110.199606
19	130321	2476099	47045881	893871739	169.835630
$\times 10^9$					
20	160000	3200000	64000000	1.280000	2.560000
21	194481	4084101	85766121	1.801089	3.782286
22	234256	5153632	113379904	2.494358	5.487587
23	279841	6436343	148035889	3.404825	7.831099
24	331776	7962624	191102976	4.586471	11.007531
25	390625	9765625	244140625	6.103516	15.258789
26	456976	11881376	308915776	8.031810	20.882706
27	531441	14348907	387420489	10.460353	28.242954
28	614656	17210368	481890304	13.492929	37.780200
29	707281	20511149	594823321	17.249876	50.024641
$\times 10^{10}$					
30	810000	24300000	7.290000	2.187000	6.561000
31	923521	28629151	8.875037	2.751261	8.528910
32	1048576	33554432	10.737418	3.435974	10.995116
33	1185921	39135393	12.914680	4.261844	14.064086
34	1336336	45435424	15.448044	5.252335	17.857939
35	1500625	52521875	18.382656	6.433930	22.518754
36	1679616	60466176	21.767823	7.836416	28.211099
37	1874161	69343957	25.657264	9.493188	35.124795
38	2085136	79235168	30.109364	11.441558	43.477921
39	2313441	90224199	35.187438	13.723101	53.520093
$\times 10^{11}$					
$\times 10^9$					
40	2560000	102400000	4.096000	16.384000	6.553600
41	2825761	115856201	4.750104	19.475427	7.984925
42	3111696	130691232	5.489032	23.053933	9.682652
43	3418801	147008443	6.321363	27.181861	11.688200
44	3748096	164916224	7.256314	31.927781	14.048224
45	4100625	184528125	8.303766	37.366945	16.815125
46	4477456	205962976	9.474297	43.581766	20.047612
47	4879681	229345007	10.779215	50.662312	23.811287
48	5308416	254803968	12.230590	58.706834	28.179280
49	5764801	282475249	13.841287	67.822307	33.232931
$\times 10^{12}$					
50	6250000	312500000	15.625000	78.125000	39.062500

POWERS OF NUMBERS—Continued

n	n^1	n^2	n^3	n^4	n^5	n^6
				$\times 10^9$	$\times 10^{11}$	$\times 10^{13}$
50	6250000	312500000	15.6250000	7.812500	3.906250	
51	6765201	345025251	17.596288	8.974107	4.576794	
52	7311616	380204032	19.770610	10.280717	5.345973	
53	7890481	418195493	22.164361	11.747111	6.225969	
54	8503056	459165024	24.794911	13.389252	7.230196	
55	9150625	503284375	27.680641	15.224352	8.373394	
56	9834496	550731776	30.840979	17.270948	9.671731	
57	10556001	601692057	34.296447	19.548975	11.142916	
58	11316496	656356768	38.068693	22.079842	12.806308	
59	12117361	714924299	42.180534	24.886515	14.683044	
		$\times 10^8$	$\times 10^{10}$	$\times 10^{11}$	$\times 10^{13}$	
60	12960000	7.776000	4.665600	27.993600	16.796160	
61	13845841	8.445963	5.152037	31.427428	19.170731	
62	14776336	9.161328	5.680024	35.216146	21.834011	
63	15752961	9.924365	6.252350	39.389806	24.815578	
64	16777216	10.737418	6.871948	43.980465	28.147498	
65	17850625	11.602906	7.541889	49.022279	31.864481	
66	18974736	12.523326	8.265395	54.551679	36.004061	
67	20151121	13.501251	9.045838	60.607116	40.606768	
68	21381376	14.539336	9.886748	67.229888	45.716324	
69	22667121	15.640313	10.791816	74.463533	51.379337	
		$\times 10^8$	$\times 10^{10}$	$\times 10^{12}$	$\times 10^{14}$	
70	24010000	16.807000	11.764900	8.235430	5.764801	
71	25411681	18.042294	12.810028	9.095120	6.457535	
72	26873856	19.349176	13.931407	10.030613	7.222041	
73	28398241	20.730716	15.133423	11.047399	8.064501	
74	29986576	22.190066	16.420649	12.151280	8.991947	
75	31640625	23.730469	17.797852	13.348389	10.011292	
76	33362176	25.355254	19.269993	14.645195	11.130348	
77	35153041	27.067842	20.842238	16.048523	12.357363	
78	37015056	28.871744	22.519960	17.565569	13.701144	
79	38950081	30.770564	24.308746	19.203909	15.171088	
		$\times 10^8$	$\times 10^{10}$	$\times 10^{12}$	$\times 10^{14}$	
80	40960000	32.768000	26.214400	20.971520	16.777216	
81	43046721	34.867844	28.242954	22.876792	18.530202	
82	45212176	37.073984	30.400667	24.928547	20.441409	
83	47458321	39.390406	32.694037	27.136051	22.522322	
84	49787136	41.821194	35.129803	29.509035	24.787589	
85	52200625	44.370531	37.714952	32.057709	27.249053	
86	54700816	47.042702	40.456724	34.792782	29.921793	
87	57289761	49.842092	43.362620	37.725479	32.821167	
88	59969536	52.773192	46.440409	40.867560	35.963452	
89	62742241	55.840594	49.698129	44.231335	39.365388	
		$\times 10^9$	$\times 10^{11}$	$\times 10^{13}$	$\times 10^{15}$	
90	65610000	5.904900	5.314410	4.782969	4.304572	
91	68574961	6.240321	5.678693	5.167610	4.702525	
92	71639296	6.590815	6.063550	5.578466	5.132189	
93	74805201	6.956884	6.469902	6.017009	5.595318	
94	78074896	7.339040	6.898698	6.484776	6.095689	
95	81450625	7.737809	7.350919	6.983373	6.634204	
96	84934656	8.153727	7.827578	7.514475	7.213396	
97	88529281	8.587340	8.329720	8.079828	7.837434	
98	92236816	9.039208	8.858424	8.681255	8.507630	
99	96059601	9.509900	9.414801	9.320653	9.227447	
100	100000000	10.000000	10.000000	10.000000	10.000000	

TRIGONOMETRIC FUNCTIONS

Degrees	Sine	Tangent	Cotangent	Cosine	
0	.0000	.0000	1.0000	90
1	.0175	.0175	57.29	.9998	89
2	.0349	.0349	28.636	.9994	88
3	.0523	.0524	19.081	.9986	87
4	.0698	.0699	14.301	.9976	86
5	.0872	.0875	11.430	.9962	85
6	.1045	.1051	9.5144	.9945	84
7	.1219	.1228	8.1443	.9925	83
8	.1392	.1405	7.1154	.9903	82
9	.1564	.1584	6.3138	.9877	81
10	.1736	.1763	5.6713	.9848	80
11	.1908	.1944	5.1446	.9816	79
12	.2079	.2126	4.7046	.9781	78
13	.2250	.2309	4.3315	.9744	77
14	.2419	.2493	4.0108	.9703	76
15	.2588	.2679	3.7321	.9659	75
16	.2756	.2867	3.4874	.9613	74
17	.2924	.3057	3.2709	.9563	73
18	.3090	.3249	3.0777	.9511	72
19	.3256	.3443	2.9042	.9455	71
20	.3420	.3640	2.7475	.9397	70
21	.3584	.3839	2.6051	.9336	69
22	.3746	.4040	2.4751	.9272	68
23	.3907	.4245	2.3559	.9205	67
24	.4067	.4452	2.2460	.9135	66
25	.4226	.4663	2.1445	.9063	65
26	.4384	.4877	2.0503	.8988	64
27	.4540	.5095	1.9626	.8910	63
28	.4695	.5317	1.8807	.8829	62
29	.4848	.5543	1.8040	.8746	61
30	.5000	.5774	1.7321	.8660	60
31	.5150	.6009	1.6643	.8572	59
32	.5299	.6249	1.6003	.8480	58
33	.5446	.6494	1.5399	.8387	57
34	.5592	.6745	1.4826	.8290	56
35	.5736	.7002	1.4281	.8192	55
36	.5878	.7265	1.3764	.8090	54
37	.6018	.7536	1.3270	.7986	53
38	.6157	.7813	1.2799	.7880	52
39	.6293	.8098	1.2349	.7771	51
40	.6428	.8391	1.1918	.7660	50
41	.6561	.8693	1.1504	.7547	49
42	.6691	.9004	1.1106	.7431	48
43	.6820	.9325	1.0724	.7314	47
44	.6947	.9657	1.0355	.7193	46
45	.7071	1.0000	1.0000	.7071	45
	Cosine	Cotangent	Tangent	Sine	Degrees

CONVERSION OF INCHES TO MILLIMETERS

Inches	Milli- meters	Inches	Milli- meters	Inches	Milli- meters
0.001	0.025	0.290	7.37	0.660	16.76
0.002	0.051	0.300	7.62	0.670	17.02
0.003	0.076	0.310	7.87	0.680	17.27
0.004	0.102	0.320	8.13	0.690	17.53
0.005	0.127	0.330	8.38	0.700	17.78
0.006	0.152	0.340	8.64	0.710	18.03
0.007	0.178	0.350	8.89	0.720	18.29
0.008	0.203	0.360	9.14	0.730	18.54
0.009	0.229	0.370	9.40	0.740	18.80
0.010	0.254	0.380	9.65	0.750	19.05
0.020	0.508	0.390	9.91	0.760	19.30
0.030	0.762	0.400	10.16	0.770	19.56
0.040	1.016	0.410	10.41	0.780	19.81
0.050	1.270	0.420	10.67	0.790	20.07
0.060	1.524	0.430	10.92	0.800	20.32
0.070	1.778	0.440	11.18	0.810	20.57
0.080	2.032	0.450	11.43	0.820	20.83
0.090	2.286	0.460	11.68	0.830	21.08
0.100	2.540	0.470	11.94	0.840	21.34
0.110	2.794	0.480	12.19	0.850	21.59
0.120	3.048	0.490	12.45	0.860	21.84
0.130	3.302	0.500	12.70	0.870	22.10
0.140	3.56	0.510	12.95	0.880	22.35
0.150	3.81	0.520	13.21	0.890	22.61
0.160	4.06	0.530	13.46	0.900	22.86
0.170	4.32	0.540	13.72	0.910	23.11
0.180	4.57	0.550	13.97	0.920	23.37
0.190	4.83	0.560	14.22	0.930	23.62
0.200	5.08	0.570	14.48	0.940	23.88
0.210	5.33	0.580	14.73	0.950	24.13
0.220	5.59	0.590	14.99	0.960	24.38
0.230	5.84	0.600	15.24	0.970	24.64
0.240	6.10	0.610	15.49	0.980	24.89
0.250	6.35	0.620	15.75	0.990	25.15
0.260	6.60	0.630	16.00	1.000	25.40
0.270	6.86	0.640	16.26
0.280	7.11	0.650	16.51

CONVERSION OF MILLIMETERS TO INCHES

Milli- meters	Inches	Milli- meters	Inches	Milli- meters	Inches
0.01	0.0004	0.35	0.0138	0.68	0.0268
0.02	0.0008	0.36	0.0142	0.69	0.0272
0.03	0.0012	0.37	0.0146	0.70	0.0276
0.04	0.0016	0.38	0.0150	0.71	0.0280
0.05	0.0020	0.39	0.0154	0.72	0.0283
0.06	0.0024	0.40	0.0157	0.73	0.0287
0.07	0.0028	0.41	0.0161	0.74	0.0291
0.08	0.0031	0.42	0.0165	0.75	0.0295
0.09	0.0035	0.43	0.0169	0.76	0.0299
0.10	0.0039	0.44	0.0173	0.77	0.0303
0.11	0.0043	0.45	0.0177	0.78	0.0307
0.12	0.0047	0.46	0.0181	0.79	0.0311
0.13	0.0051	0.47	0.0185	0.80	0.0315
0.14	0.0055	0.48	0.0189	0.81	0.0319
0.15	0.0059	0.49	0.0193	0.82	0.0323
0.16	0.0063	0.50	0.0197	0.83	0.0327
0.17	0.0067	0.51	0.0201	0.84	0.0331
0.18	0.0071	0.52	0.0205	0.85	0.0335
0.19	0.0075	0.53	0.0209	0.86	0.0339
0.20	0.0079	0.54	0.0213	0.87	0.0343
0.21	0.0083	0.55	0.0217	0.88	0.0346
0.22	0.0087	0.56	0.0220	0.89	0.0350
0.23	0.0091	0.57	0.0224	0.90	0.0354
0.24	0.0094	0.58	0.0228	0.91	0.0358
0.25	0.0098	0.59	0.0232	0.92	0.0362
0.26	0.0102	0.60	0.0236	0.93	0.0366
0.27	0.0106	0.61	0.0240	0.94	0.0370
0.28	0.0110	0.62	0.0244	0.95	0.0374
0.29	0.0114	0.63	0.0248	0.96	0.0378
0.30	0.0118	0.64	0.0252	0.97	0.0382
0.31	0.0122	0.65	0.0256	0.98	0.0386
0.32	0.0126	0.66	0.0260	0.99	0.0390
0.33	0.0130	0.67	0.0264	1.00	0.0394
0.34	0.0134

COMMON LOGARITHMS OF NUMBERS

N	0	1	2	3	4	5	6	7	8	9
10	0000	0043	0086	0128	0170	0212	0253	0294	0334	0374
11	0414	0453	0492	0531	0569	0607	0645	0682	0719	0755
12	0792	0828	0864	0899	0934	0969	1004	1038	1072	1106
13	1139	1173	1206	1239	1271	1303	1335	1367	1399	1430
14	1461	1492	1523	1553	1584	1614	1644	1673	1703	1732
15	1761	1790	1818	1847	1875	1903	1931	1959	1987	2014
16	2041	2068	2095	2122	2148	2175	2201	2227	2253	2279
17	2304	2330	2355	2380	2405	2430	2455	2480	2504	2529
18	2553	2577	2601	2625	2648	2672	2695	2718	2742	2765
19	2788	2810	2833	2856	2878	2900	2923	2945	2967	2989
20	3010	3032	3054	3075	3096	3118	3139	3160	3181	3201
21	3222	3243	3263	3284	3304	3324	3345	3365	3385	3404
22	3424	3444	3464	3483	3502	3522	3541	3560	3579	3598
23	3617	3636	3655	3674	3692	3711	3729	3747	3766	3784
24	3802	3820	3838	3856	3874	3892	3909	3927	3945	3962
25	3979	3997	4014	4031	4048	4065	4082	4099	4116	4133
26	4150	4166	4183	4200	4216	4232	4249	4265	4281	4298
27	4314	4330	4346	4362	4378	4393	4409	4425	4440	4456
28	4472	4487	4502	4518	4533	4548	4564	4579	4594	4609
29	4624	4639	4654	4669	4683	4698	4713	4728	4742	4757
30	4771	4786	4800	4814	4829	4843	4857	4871	4886	4900
31	4914	4928	4942	4955	4969	4983	4997	5011	5024	5038
32	5051	5065	5079	5092	5105	5119	5132	5145	5159	5172
33	5185	5198	5211	5224	5237	5250	5263	5276	5289	5302
34	5315	5328	5340	5353	5366	5378	5391	5403	5416	5428
35	5441	5453	5465	5478	5490	5502	5514	5527	5539	5551
36	5563	5575	5587	5599	5611	5623	5635	5647	5658	5670
37	5682	5694	5705	5717	5729	5740	5752	5763	5775	5786
38	5798	5809	5821	5832	5843	5855	5866	5877	5888	5899
39	5911	5922	5933	5944	5955	5966	5977	5988	5999	6010
40	6021	6031	6042	6053	6064	6075	6085	6096	6107	6117
41	6128	6138	6149	6160	6170	6180	6191	6201	6212	6222
42	6232	6243	6253	6263	6274	6284	6294	6304	6314	6325
43	6335	6345	6355	6365	6375	6385	6395	6405	6415	6425
44	6435	6444	6454	6464	6474	6484	6493	6503	6513	6522
45	6532	6542	6551	6561	6571	6580	6590	6599	6609	6618
46	6628	6637	6646	6656	6665	6675	6684	6693	6702	6712
47	6721	6730	6739	6749	6758	6767	6776	6785	6794	6803
48	6812	6821	6830	6839	6848	6857	6866	6875	6884	6893
49	6902	6911	6920	6928	6937	6946	6955	6964	6972	6981
50	6990	6998	7007	7016	7024	7033	7042	7050	7059	7067
51	7076	7084	7093	7101	7110	7118	7126	7135	7143	7152
52	7160	7168	7177	7185	7193	7202	7210	7218	7226	7235
53	7243	7251	7259	7267	7275	7284	7292	7300	7308	7316
54	7324	7332	7340	7348	7356	7364	7372	7380	7388	7396

COMMON LOGARITHMS OF NUMBERS—Continued

N	0	1	2	3	4	5	6	7	8	9
55	7404	7412	7419	7427	7435	7443	7451	7459	7466	7474
56	7482	7490	7497	7505	7513	7520	7528	7536	7543	7551
57	7559	7566	7574	7582	7589	7597	7604	7612	7619	7627
58	7634	7642	7649	7657	7664	7672	7679	7686	7694	7701
59	7709	7716	7723	7731	7738	7745	7752	7760	7767	7774
60	7782	7789	7796	7803	7810	7818	7825	7832	7839	7846
61	7853	7860	7868	7875	7882	7889	7896	7903	7910	7917
62	7924	7931	7938	7945	7952	7959	7966	7973	7980	7987
63	7993	8000	8007	8014	8021	8028	8035	8041	8048	8055
64	8062	8069	8075	8082	8089	8096	8102	8109	8116	8122
65	8129	8136	8142	8149	8156	8162	8169	8176	8182	8189
66	8195	8202	8209	8215	8222	8228	8235	8241	8248	8254
67	8261	8267	8274	8280	8287	8293	8299	8306	8312	8319
68	8325	8331	8338	8344	8351	8357	8363	8370	8376	8382
69	8388	8395	8401	8407	8414	8420	8426	8432	8439	8445
70	8451	8457	8463	8470	8476	8482	8488	8494	8500	8506
71	8513	8519	8525	8531	8537	8543	8549	8555	8561	8567
72	8573	8579	8585	8591	8597	8603	8609	8615	8621	8627
73	8633	8639	8645	8651	8657	8663	8669	8675	8681	8686
74	8692	8698	8704	8710	8716	8722	8727	8733	8739	8745
75	8751	8456	8762	8768	8774	8779	8785	8791	8797	8802
76	8808	8814	8820	8825	8831	8837	8842	8848	8854	8859
77	8865	8871	8876	8882	8887	8893	8899	8904	8910	8915
78	8921	8927	8932	8938	8943	8949	8954	8960	8965	8971
79	8976	8982	8987	8993	8998	9004	9009	9015	9020	9025
80	9031	9036	9042	9047	9053	9058	9063	9069	9074	9079
81	9085	9090	9096	9101	9106	9112	9117	9122	9128	9133
82	9138	9143	9149	9154	9159	9165	9170	9175	9180	9186
83	9191	9196	9201	9206	9212	9217	9222	9227	9232	9238
84	9243	9248	9253	9258	9263	9269	9274	9279	9284	9289
85	9294	9299	9304	9309	9315	9320	9325	9330	9335	9340
86	9345	9350	9355	9360	9365	9370	9375	9380	9385	9390
87	9395	9400	9405	9410	9415	9420	9425	9430	9435	9440
88	9445	9450	9455	9460	9465	9469	9474	9479	9484	9489
89	9494	9499	9504	9509	9513	9518	9523	9528	9533	9538
90	9542	9547	9552	9557	9562	9566	9571	9576	9581	9586
91	9590	9595	9600	9605	9609	9614	9619	9624	9628	9633
92	9638	9643	9647	9652	9657	9661	9666	9671	9675	9680
93	9685	9689	9694	9699	9703	9708	9713	9717	9722	9727
94	9731	9736	9741	9745	9750	9754	9759	9763	9768	9773
95	9777	9782	9786	9791	9795	9800	9805	9809	9814	9818
96	9823	9827	9832	9836	9841	9845	9850	9854	9859	9863
97	9868	9872	9877	9881	9886	9890	9894	9899	9903	9908
98	9912	9917	9921	9926	9930	9934	9939	9943	9948	9952
99	9956	9961	9965	9969	9974	9978	9983	9987	9991	9996

BINARY NUMBERS

16 8 4 2 1					16 8 4 2 1					16 8 4 2 1						
0					0	11	1	0	1	1	22	1	0	1	1	0
1					1	12	1	1	0	0	23	1	0	1	1	1
2				1	0	13	1	1	0	1	24	1	1	0	0	0
3				1	1	14	1	1	1	0	25	1	1	0	0	1
4			1	0	0	15	1	1	1	1	26	1	1	0	1	0
5			1	0	1	16	1	0	0	0	27	1	1	0	1	1
6			1	1	0	17	1	0	0	0	28	1	1	1	0	0
7			1	1	1	18	1	0	0	1	29	1	1	1	0	1
8			1	0	0	19	1	0	0	1	30	1	1	1	1	0
9			1	0	0	20	1	0	1	0	31	1	1	1	1	1
10			1	0	1	0	21	1	0	1	0	1				

DECIMAL TO BINARY CONVERSION RULES

- (a) Write number $n + 0$ if even or $(n - 1) + 1$ if odd.
- (b) Divide even number obtained in (a) by 2.
Write answer (m) below in same form:
 $m + 0$ if even, $(m - 1) + 1$ if odd.
- (c) Continue until m or $(m - 1)$ becomes zero.
- (d) Column of ones and zeros so obtained is binary equivalent of n with least significant digit at the top.

EXAMPLE: $n = 327$

$326 + 1$
 $162 + 1$
 $80 + 1$
 $40 + 0$
 $20 + 0$
 $10 + 0$
 $4 + 1$
 $2 + 0$
 $0 + 1$

Therefore the binary equivalent of 327 is 101000111

BINARY TO DECIMAL CONVERSION RULES

- (a) Start at left with first significant digit—double it if the next digit is a zero or "dibble" it (double and add one) if the next digit is a one.
- (b) If the 3rd digit is a zero, double value obtained in (a), if it is a one "dibble" value obtained in (a).
- (c) Continue until operation indicated by least significant digit has been performed.

FUSING CURRENTS OF WIRES

This table gives the fusing currents in amperes for 5 commonly used types of wires. The current I in amperes at which a wire will melt can be calculated from $I = Kd^{3/2}$ where d is the wire diameter in inches and K is a constant that depends on the metal concerned. A wide variety of factors influence the rate of heat loss and these figures must be considered as approximations.

AWG B & S gauge	d in inches	copper $K =$ 10,244	alum- inum $K =$ 7585	german silver $K =$ 5230	iron $K =$ 3143	tin $K =$ 1642
40	0.0031	1.77	1.31	0.90	0.54	0.28
38	0.0039	2.50	1.85	1.27	0.77	0.40
36	0.0050	3.62	2.68	1.85	1.11	0.58
34	0.0063	5.12	3.79	2.61	1.57	0.82
32	0.0079	7.19	5.32	3.67	2.21	1.15
30	0.0100	10.2	7.58	5.23	3.15	1.64
28	0.0126	14.4	10.7	7.39	4.45	2.32
26	0.0159	20.5	15.2	10.5	6.31	3.29
24	0.0201	29.2	21.6	14.9	8.97	4.68
22	0.0253	41.2	30.5	21.0	12.7	6.61
20	0.0319	58.4	43.2	29.8	17.9	9.36
19	0.0359	69.7	51.6	35.5	21.4	11.2
18	0.0403	82.9	61.4	42.3	25.5	13.3
17	0.0452	98.4	72.9	50.2	30.2	15.8
16	0.0508	117	86.8	59.9	36.0	18.8
15	0.0571	140	103	71.4	43.0	22.4
14	0.0641	166	123	84.9	51.1	26.6
13	0.0719	197	146	101	60.7	31.7
12	0.0808	235	174	120	72.3	37.7
11	0.0907	280	207	143	86.0	44.9
10	0.1019	333	247	170	102	53.4
9	0.1144	396	293	202	122	63.5
8	0.1285	472	349	241	145	75.6
7	0.1443	561	416	287	173	90.0
6	0.1620	668	495	341	205	107

ROMAN NUMERALS*

1	I	8	VIII
2	II	9	IX
3	III	10	X
4	IV	50	L
5	V	100	C
6	VI	500	D
7	VII	1000	M

The chief symbols are I = 1; V = 5; X = 10; L = 50; C = 100; D = 500; and M = 1000. Note that IV = 4, means 1 short of 5; IX = 9, means 1 short of 10; XL = 40, means 10 short of 50; and XC = 90, means 10 short of 100. Any symbol following one of equal or greater value adds its value—II = 2. Any symbol preceding one of greater value subtracts its value—IV = 4. When a symbol stands between two of greater value its value is subtracted from the second and the remainder is added to the first—XIV = 14; LIX = 59. Of two equivalent ways of representing a number, that in which the symbol of larger denomination preceded is preferred—XIV instead of VIX for 14.

**Used currently to determine dates of cornerstones and vintage of T.V. films.*

NUMERICAL DATA

1 cubic foot of water at 4° C (weight).....	.62.43 lb
1 foot of water at 4° C (pressure).....	0.4335 lb/in ²
Velocity of light in vacuum, c.....	186,280 mi/sec = 2.998 × 10 ¹⁰ cm/sec
Velocity of sound in dry air at 20° C, 76 cm Hg....	1127 ft/sec
Degree of longitude at equator.....	69.173 miles
Acceleration due to gravity at sea-level, 40° Latitude, g.....	32.1578 ft/sec ²
√2g.....	8.020
1 inch of mercury at 4° C.....	1.132 ft water = 0.4908 lb/in ²
Base of natural logs e.....	2.718
1 radian.....	180° ÷ π = 57.3°
360 degrees.....	2 π radians
π.....	3.1416
Sine 1'.....	0.00029039
Arc 1°.....	0.01745 radian
Side of square.....	0.707 × (diagonal of square)

COMMON INTEGRALS

1. $\int a \, dx = ax.$
2. $\int a \cdot f(x) \, dx = a \int f(x) \, dx.$
3. $\int \phi(y) \, dx = \int \frac{\phi(y)}{y'} \, dy,$ where $y' = dy/dx.$
4. $\int (u + v) \, dx = \int u \, dx + \int v \, dx,$ where u and v are any functions of $x.$
5. $\int u \, dv = uv - \int v \, du.$
6. $\int u \frac{dv}{dx} \, dx = uv - \int v \frac{du}{dx} \, dx.$
7. $\int x^n \, dx = \frac{x^{n+1}}{n+1},$ except $n = -1.$
8. $\int \frac{f'(x) \, dx}{f(x)} = \log f(x),$ [$d f(x) = f'(x) \, dx$].
9. $\int \frac{dx}{x} = \log x,$ or $\log (-x).$
10. $\int \frac{f'(x) \, dx}{2\sqrt{f(x)}} = \sqrt{f(x)},$ [$d f(x) = f'(x) \, dx$].
11. $\int e^x \, dx = e^x.$
12. $\int e^{ax} \, dx = e^{ax}/a.$
13. $\int b^{ax} \, dx = \frac{b^{ax}}{a \log b}.$
14. $\int \log x \, dx = x \log x - x.$
15. $\int a^x \log a \, dx = a^x.$
16. $\int \frac{dx}{a^2 + x^2} = \frac{1}{a} \tan^{-1} \left(\frac{x}{a} \right),$ or $-\frac{1}{a} \cot^{-1} \left(\frac{x}{a} \right).$
17. $\int \frac{dx}{a^2 - x^2} = \frac{1}{a} \tanh^{-1} \left(\frac{x}{a} \right),$ or $\frac{1}{2a} \log \frac{a+x}{a-x}$

COMMON INTEGRALS—Continued

$$18. \int \frac{dx}{x^2 - a^2} = -\frac{1}{a} \coth^{-1} \left(\frac{x}{a} \right), \text{ or } \frac{1}{2a} \log \frac{x-a}{x+a}.$$

$$19. \int \frac{dx}{\sqrt{a^2 - x^2}} = \sin^{-1} \left(\frac{x}{a} \right), \text{ or } -\cos^{-1} \left(\frac{x}{a} \right).$$

$$20. \int \frac{dx}{\sqrt{x^2 \pm a^2}} = \log (x + \sqrt{x^2 \pm a^2}).$$

$$21. \int \frac{dx}{x \sqrt{x^2 - a^2}} = \frac{1}{a} \cos^{-1} \left(\frac{a}{x} \right).$$

$$22. \int \frac{dx}{x \sqrt{a^2 \pm x^2}} = -\frac{1}{a} \log \left(\frac{a + \sqrt{a^2 \pm x^2}}{x} \right).$$

$$23. \int \frac{dx}{x \sqrt{a + bx}} = \frac{2}{\sqrt{-a}} \tan^{-1} \sqrt{\frac{a+bx}{-a}}, \text{ or } \frac{-2}{\sqrt{a}} \tanh^{-1} \sqrt{\frac{a+bx}{a}}.$$

LINEAR MEASURE

- 12 inches = 1 foot
- 3 feet = 1 yard = 36 inches
- 5½ yards = 1 rod or pole = 16½ feet
- 40 rods = 1 furlong = 220 yards = 660 feet = ¼ mile
- 8 furlongs = 1 statute mile = 1760 yards = 5280 feet
- 3 miles = 1 league = 5280 yards = 15,840 feet

SQUARE MEASURE

- 144 square inches = 1 square foot
- 9 square feet = 1 square yard = 1296 square inches
- 30¼ square yards = 1 square rod = 272¼ square feet
- 160 square rods = 1 acre = 4840 square yards
- 640 acres = 1 square mile = 3,097,600 square yards

CUBIC MEASURE

- 1728 cubic inches = 1 cubic foot
- 27 cubic feet = 1 cubic yard
- 144 cubic inches = 1 board foot
- 128 cubic feet = 1 cord

LIQUID MEASURE

- 4 gills = 1 pint
- 2 pints = 1 quart = 8 gills
- 4 quarts = 1 gallon = 8 pints = 32 gills
- 31½ gallons = 1 barrel = 126 quarts
- 2 barrels = 1 hogshead = 63 gallons = 252 quarts

DRY MEASURE




























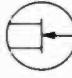



- 2 pints = 1 quart
- 8 quarts = 1 peck = 16 pints
- 4 pecks = 1 bushel = 32 quarts = 64 pints
- 105 quarts = 1 barrel (for fruits, vegetables, and other dry commodities) = 7056 cubic inches

CIRCULAR MEASURE

- 60 seconds (") = 1 minute (')
- 60 minutes = 1 degree (°)
- 90 degrees = 1 quadrant
- 4 quadrants = 1 circle of circumference

COMMUNICATIONS	INDUSTRIAL	COMMUNICATIONS	INDUSTRIAL
ANTENNA		PILOT LAMP LETTER FOR COLOR	
BATTERY		WIRES CROSSING (NO CONNECTION)	
FIXED CAPACITOR		WIRES CROSSING (CONNECTED)	
VARIABLE CAPACITOR		POWER WIRE	
RESISTOR (FIXED)		GROUND BUS	
RESISTOR (VARIABLE)		EARPHONES	
TAPPED FIXED RESISTOR		CONTROL WIRE	
OPEN CIRCUIT JACK		FUSE	
N.O. N.C.	N.O. N.C.		
PUSHBUTTON SWITCHES		GROUND	
MANUAL SWITCH		THERMOCOUPLE	

COMMUNICATIONS	INDUSTRIAL	COMMUNICATIONS	INDUSTRIAL
CIRCUIT BREAKER		RELAY COIL	
NONE			
MAGNETIC OVERLOAD		RELAY (SLOW CLOSING)	
NONE			
THERMAL OVERLOAD		RELAY (SLOW-RELEASE)	
INDUCTOR (AIR CORE)		RELAY (SLOW-ACTING)	
INDUCTOR (SLUG TUNED)		RELAY CONTACT NORMALLY CLOSED (N.C.)	
TRANSFORMER (IRON-CORE)		RELAY CONTACT NORMALLY OPEN (N.O.)	
NONE			
3-PHASE TRANSFORMER		RELAY CONTACT SPDT	
NONE			
REACTOR (SATURABLE)		RELAY CONTACT (DELAYED-OPENING)	
		RELAY CONTACT (DELAYED-CLOSING)	
		LIMIT SWITCH	

COMMUNICATIONS	INDUSTRIAL	COMMUNICATIONS	INDUSTRIAL
			
DIODE (KENOTRON)		SEMICONDUCTOR DIODE	
			
DUO-DIODE (FULL-WAVE RECT)		PNP TRANSISTOR	
			
TRIODE (PLIOTRON)		NPN TRANSISTOR	
			
PENTODE		PNP TETRODE TRANSISTOR	
			
NEON LAMP		CONTROLLED RECTIFIER	
			
PHOTOCELL		PNP FIELD-EFFECT TRANSISTOR	
			
THYRATRON		UNIUNCTION TRANSISTOR	
NONE			
IGNITRON		THERMISTOR	

index

A		
Abbreviations, electronic.....	127	
Ac.....	29	
Ac:		
bridge.....	122	
circuits, power in.....	65	
Ohm's law for.....	64	
Adcock antenna.....	115	
Admittance of a series circuit.....	62	
Alpha.....	96	
Alpha, cutoff frequency.....	101	
Alphabet, Greek.....	131	
Amplification:		
at high frequencies (pentodes).....	89	
at high frequencies (triodes).....	87	
at intermediate or medium frequencies (triodes).....	87	
at low frequencies (pentodes).....	89	
at low frequencies (triodes).....	87	
at medium frequencies (pentodes).....	88	
current.....	96	
factor.....	81	
factor, current.....	101	
voltage.....	83	
Amplifier, second harmonic distortion of ...	94	
Amplifiers:		
power.....	91	
resistance-coupled audio.....	85	
voltage.....	83	
Angle, phase.....	55	
Angles.....	34	
Antenna:		
Adcock.....	115	
Beverage.....	116	
center-fed Hertz.....	111	
coaxial.....	113	
corner reflector.....	111	
cosecant-squared reflector.....	110	
crow-foot.....	113	
elevation.....	106	
end-fed Hertz.....	111	
folded dipole.....	116	
Fuchs.....	111	
full wave.....	104	
ground-plane.....	113	
half rhombic.....	116	
horn.....	110	
ilas.....	114	
impedances.....	104	
inverted V.....	111	
length.....	103	
loop.....	115	
Marconi.....	112	
omni-range.....	115	
parabolic reflector.....	110	
parasitic array.....	112	
rhombic.....	112	
skin.....	114	
sleeve.....	113	
standard.....	105	
stub mast.....	115	
tilted wire.....	111	
tuned doublet.....	110	
turnstile.....	114	
vertical J.....	113	
vor.....	115	
Zepp.....	110	
Antennas.....	103	
Apparent power.....	65	
Area of wire.....	14	
Attenuation.....	107	
Audio amplifiers:		
resistance-coupled (pentodes).....	87	
resistance-coupled (triodes).....	85	
Audio power output, single pentode.....	93	
Audio transformer color code.....	54	
Average value.....	32	
B		
Band-elimination filter.....	74	
Band-pass filter (constant K).....	73	
Basic transistor circuits.....	98	
Basic units.....	16	
Beta.....	101	
Beverage antenna.....	116	
Binary numbers.....	145	
Binary to decimal conversion rules.....	145	
Bridge:		
ac.....	122	
slide wire.....	122	
Wheatstone.....	121	
C		
Capacitive:		
circuit, Ohm's law for a.....	43	
circuits, phase angle in.....	57	
reactance.....	42	
Capacitor:		
charge of.....	41	
energy stored in a.....	41	
Q of a.....	50	
working voltage of a.....	42	
Capacitors:		
as voltage dividers.....	42	
in parallel.....	39	
in series.....	39	
in series-parallel.....	41	
Cathode follower.....	84, 100	
Cathode-ray oscilloscope.....	123	
Center-fed Hertz.....	111	
Centigrade-Fahrenheit conversion.....	15	
Characteristic impedance.....	106, 108	
Charge of a capacitor.....	41	
Circuits, vacuum tube.....	81	
Circular measure.....	148	
Coaxial antenna.....	113	

Coaxial transmission line, resistance of	106
Coefficient of coupling	45
Coefficient of resistance	15
Coil, Q of a	50
Coils	44
Color code:	
audio transformer	54
i.f. transformer	53
output transformer	54
power transformer	52
pushpull transformer	54
resistor	12
Common:	
base circuit	99
collector circuit	100
emitter circuit	98
integrals	150
logarithms of numbers	143
Concentric transmission line (air insulated)	107
Conductance	64
mutual	82
time	26
Conversion factors	125
Conversion factors for electronic multiples	38
Corner reflector	111
Cosecant-squared reflectors	110
Coupling, coefficient of	45
Crow-foot antenna	113
Cube root of numbers	132
Cubes of numbers	132
Cubic measure	148
Current:	
amplification	96
amplification factor	101
and voltage measurements	32
average	33
effective	35
law, Kirchhoff's	25
peak-to-peak	36
rms	35
transformers	52
Cutoff frequency, alpha	101
D	
Data and tables	125
Db	69
Dc	7
Decibels and Nepers	69
Decimal equivalents	128
Decimal to binary conversion rules	145
Degenerative feedback	90
Diameter of wire	14
Distortion, second-harmonic	94
Dry measure	148
E	
Effective:	
current	35
resistance	50
voltage	35
Efficiency	19
EHF	129
Electronic:	
abbreviations	127
prefixes	37
symbols	37, 152
End-fed Hertz	111
Energy stored in a capacitor	41
Energy vs power	20
Extremely high frequency	129

F	
Factor:	
amplification	81
power	66
velocity	109
Fahrenheit-Centigrade conversion	15
Feedback, negative	90
Filter:	
band-elimination	74
(constant K) band-pass	73
pi-type, high-pass	77
pi-type, low-pass	77
T-type, low-pass	75
Filters	71
Filters:	
(constant K), high-pass	72
(constant K), low-pass	72
m-derived	77
types of m-derived	79
Folded dipole	116
Frequency:	
alpha cutoff	101
and wavelength	29
measurements	123
Fuchs antenna	111
Full wave antennas	104
Fundamental and harmonic relationships	79, 80
Fusing currents of wires	149
G	
Gain:	
power	97, 105
resistance	96
voltage	97
Gauge of wire	14
Gigacycle	129
Greek alphabet	131
Ground-plane antenna	113
Grounded cathode circuit	98
Grounded grid circuit	99
H	
Half rhombic	116
Harmonic and fundamental relationships	79, 80
Height of antenna	106
High-frequency	129
High-frequency range	86
High-pass filter, pi-type	77
High-pass filters (constant K)	72
Horn antenna	110
I	
I.f. transformer color code	53
Ilas antennas	114
Impedance:	
characteristic	108
impedance and phase angle of series R-L shunted by C	62
impedance and phase angle of series R-L shunted by R	61
in an R-L circuit	49
of a parallel L-C circuit	60
of a parallel R-C circuit	60
of a parallel R-L circuit	60
of a parallel R-L-C circuit	61
of a series L-C circuit	58
of a series R-L-C circuit	58
of a transmission line	106
of an R-C circuit	43

surge	106
transformers	52
Impedances, antenna	104
Impedances, matching	109
Inches to millimeters	141
Inductance, mutual	45
Inductive:	
circuit, Ohm's law for an	48
circuits, phase angle in	56
reactance	48
Inductor Q	50
Inductor, reactance of	48
Inductors:	44
Inductors:	
in parallel	45
in parallel aiding	47
in parallel opposing	48
in series	45
in series aiding	47
in series opposing	47
Input resistance	102
Instantaneous value	33
Integrals, common	150
Inverse feedback	90
Inverted V antenna	111
K	
Kirchhoff's current law	25
Kirchhoff's voltage law	24
L	
L-C circuit:	
impedance of a parallel	60
impedance of a series	58
phase angle of a parallel	60
phase angle of a series	58
Length of transmission line	109
Levels, reference	70
LF	129
Linear measure	148
Lines, transmission	103, 106
Liquid measure	148
Load, maximum transfer of power to the	93
Load, power in the plate	93
Logarithms of numbers, common	143
Logs, common	143
Loop antenna	115
Low-frequency	129
Low-frequency range	86
Low-pass filter, pi-type	77
Low-pass filter, T-type	75
Low-pass filters, (constant K)	72
M	
Marconi antenna	112
Matching impedances	109
Mathematical symbols	130
Maximum transfer of power	93
Maximum voltage	33
M-derived filters	77
M-derived filters, types of	79
Measurements	117
Measurements:	
resistance	119
voltage and current	32
Medium frequency	129
Medium frequency range	86
MF	129
Millimeters to inches	142
Multiples and submultiples	37
Multiplier resistance	118
Mutual conductance	82

Mutual inductance	45
N	
Negative feedback	90
Neper and decibels	69
Nonsinusoidal waves	79
Numbers:	
binary	145
common logarithms of	143
Numerals, Roman	146
Numerical data	146
O	
Ohm's law	15
Ohm's law for:	
a capacitive circuit	43
ac	64
an inductive circuit	48
summary of	19
Omni-range antenna	115
Oscilloscope	123
Output:	
power	92
resistance	102
transformer color code	54
undistorted power	93
P	
Parabolic reflector antenna	110
Parallel:	
aiding, inductors in	47
capacitors	39
inductors	45
L-C circuit, impedance of a	60
L-C circuit, phase angle of	60
opposing, inductors in	48
R-C circuit, impedance of a	60
resistors in	8, 9
R-L circuit, impedance of	60
R-L circuit, phase angle of	60
R-L-C circuit, impedance of a	61
R-L-C circuit, phase angle of a	61
Parallel-series capacitors	41
Parallel-series, resistors in	11
Parasitic array	112
Peak-to-peak current	36
Peak-to-peak voltage	36
Peak voltage	33
Period	31
Phase	20
Phase angle	55
Phase angle:	
and impedance of series R-L shunted	
by C	62
and impedance of series R-L shunted	
by R	61
in capacitive circuits	57
in inductive circuits	56
in resistive circuits	56
of a parallel L-C circuit	60
of a parallel R-L circuit	60
of a parallel R-L-C circuit	61
of a series L-C circuit	58
of a series R-L circuit	57
of a series R-L-C circuit	58
Pi-type high-pass filter	77
Pi-type low-pass filter	77
Plate load, power in the	93
Plate resistance	82
Potentiometer voltage divider	21
Power	17

Power:		Resonant circuit, Q of a series.....	68
amplifier, second-harmonic		Rhombic antenna.....	112
distortion of.....	94	R-L:	
amplifiers.....	91	circuit, impedance in an.....	49
apparent.....	65	circuit, impedance of a parallel.....	60
factor.....	66	circuit, phase angle of a parallel.....	60
gain.....	105	circuit, phase angle of a series.....	57
gain, transistor.....	97	circuit, voltages in a series.....	50
in ac circuits.....	65	series.....	27
in the plate load.....	93	shunted by C, impedance and phase	
laws, summary of.....	19	angle of.....	62
maximum transfer of.....	93	shunted by R, impedance and phase	
output.....	92	angle of series.....	61
output, single pentode audio.....	93	R-L-C:	
output, undistorted.....	93	circuit, impedance of a parallel.....	61
radiated.....	105	circuit, impedance of a series.....	58
sensitivity.....	91	circuit, phase angle of.....	58, 61
transformer color code.....	52	Rms:	
units.....	19	current.....	35
vs energy.....	20	voltage.....	35
Powers of numbers.....	138	Roman numerals.....	146
Preferred values of resistors.....	11, 12		
Pushpull transformer color code.....	54	S	
Q		Scope.....	123
Q of a:		Second-harmonic distortion.....	94
capacitor.....	50	Sensitivity, power.....	91
coil.....	50	Series:	
series resonant circuit.....	68	aiding, inductors in.....	47
R		aiding, voltages in.....	23
Radiated power.....	105	capacitors.....	39
Radiation resistance.....	105	circuit, admittance of.....	62
Ratio:		circuit, resonance in.....	67
standing wave.....	108	inductors.....	45
turns.....	51	L-C circuit, impedance of.....	58
R-C:		L-C circuit, phase angle of a.....	58
audio amplifiers, (pentode).....	87	opposing, inductors in.....	47
audio amplifiers, (triodes).....	85	parallel capacitors.....	41
circuit, impedance of a parallel.....	60	parallel, resistors in.....	11
circuit, impedance of an.....	43	R-C.....	27
circuit, phase angle of a series.....	58	R-C circuit, phase angle of.....	58
circuit, voltages in a series.....	44	R-C circuit, voltages in a.....	44
series.....	27	resistors in.....	8
Reactance:		resonant circuit, Q of a.....	68
capacitive.....	42	R-L.....	27
of an inductor.....	48	R-L circuit, phase angle of.....	57
Reference levels.....	70	R-L circuit, voltages in.....	50
Resistance:		R-L shunted by C, impedance and	
coefficient of.....	15	phase angle of.....	62
coupled audio amplifiers (pentodes).....	87	R-L shunted by R, impedance and	
coupled audio amplifiers (triodes).....	85	phase angle of.....	61
effective.....	50	R-L-C circuit, impedance of a.....	58
gain.....	96	R-L-C circuit, phase angle of.....	58
input and output.....	102	SHF.....	129
measurements.....	119	Shunt:	
multiplier.....	118	law.....	20
of a coaxial transmission line.....	108	resistance.....	117
of open two-wire copper line.....	108	Sine values.....	34, 79
of wire.....	13	Single pentode audio power output.....	93
plate.....	82	Skin antennas.....	114
radiation.....	105	Sleeve antenna.....	113
shunt.....	117	Slide-wire bridge.....	122
Resistive circuits, phase angle in.....	56	Square:	
Resistor color code.....	12	measure.....	148
Resistors.....	7	root of numbers.....	132
Resistors:		Squares of numbers.....	132
in parallel.....	8, 9	Standard antenna.....	105
in series.....	8	Standing wave ratio.....	108
in series-parallel.....	11	Step down transformers.....	51
preferred values of.....	11, 12	Step up transformers.....	51
Resonance in a series circuit.....	67	Stub mast antenna.....	115
		Super-high frequency.....	129

Surge impedance.....	106	Undistorted power output.....	93
Susceptance.....	63	Units, volume.....	71
SWR.....	108	V	
Symbols:		Vacuum tube circuits.....	81
electronic.....	152	Vacuum tubes.....	81
mathematical.....	130	Velocity factor.....	109
T		Velocity of a wave.....	31
Tables and data.....	125	Vertical J antenna.....	113
Temperature.....	14	Very-high frequency.....	129
Time constants.....	26	Very-low frequency.....	129
Transformer color code:		VHF.....	129
audio.....	54	VLF.....	129
i.f.....	53	Voltage:	
output.....	54	amplification.....	83
power.....	52	amplifiers.....	83
pushpull.....	54	and current measurements.....	32
turn ratio.....	51	average.....	32
Transformers:		divider (potentiometer).....	21
current.....	52	dividers, capacitors as.....	42
impedance.....	52	effective.....	35
step down.....	51	gain of transistor.....	97
step up.....	51	law, Kirchhoff's.....	24
voltage.....	51	of a capacitor, working.....	42
Transistor:		peak.....	33
circuits, basic.....	98	peak-to-peak.....	36
power gain.....	97	rms.....	35
voltage gain.....	97	transformers.....	51
Transistors.....	95	Voltages:	
Transmission line:		in a series R-C circuit.....	44
concentric.....	107	in a series R-L circuit.....	50
line, length of.....	109	in series, aiding.....	23
two-wire open.....	107	Volume units.....	71
Transmission lines.....	103, 106	VU.....	71
Trigonometric functions.....	140	W	
Triode resistance-coupled audio amplifier... 85		Wave, velocity of.....	31
T-type low-pass filter.....	75	Wavelength and frequency.....	29
Tube circuits, vacuum.....	81	Wavelength and frequency bands.....	129
Tubes, vacuum.....	81	Waves, nonsinusoidal.....	79
Tuned doublet.....	111	Wheatstone bridge.....	121
Turns ratio.....	51	Wire, resistance of.....	13
Turnstile antenna.....	114	Wire table.....	14
Two-wire:		Wires, fusing currents of.....	149
copper line, resistance of open.....	108	Working voltage of a capacitor.....	42
open transmission line.....	107	Z	
U		Zepp.....	111
UHF.....	129		
Ultra-high frequency.....	129		

SOME FACTS ABOUT THIS BOOK

This book was set in Times Roman, 10 point type on a 12 point body using Linofilm composition. Composition by COMPUTER COMPOSITION, Flourtown, Penna. Printing by Goodway Printing Co., Philadelphia, Pa., art work by DBN Technical Art Services. Paperback binding by Sendor Bindery, Inc., New York, N.Y. and edition binding by Book Press, Brattleboro, Mass.

Our special thanks to Automatic Electric Co. (division of General Telephone & Electronics) for permission to reproduce material supplied by them.

Printed in the United States of America





OTHER GERNSBACK LIBRARY BOOKS


Basic TV Course

By George Kravitz

A book on TV as it is today. Even transistorized portables are discussed. A thorough practical discussion of circuit operation, sync methods, sweep systems, tuners, amplifiers, variations in power supply styles. Presentation of technical detail in easy-to-follow writing style.

No. 105

\$4.10

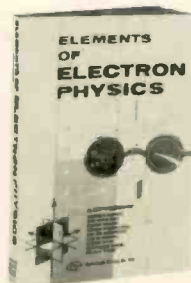

Elements of Electron Physics

By Norman H. Crowhurst

Explains in simple understandable language the how and why of electronics. Covers beginning of electronics, electron theory, solid-state semiconductors, tubes for electronics, electronic circuits.

No. 113

\$3.95

Basic Transistor Course

By Paul R. Kenian

Teaches transistor fundamentals clearly, simply. Discusses transistors all the way from elementary circuits to radio receivers.

No. 111

\$4.10



The Oscilloscope

(Revised Edition)

By George Zwick

Enables technicians to become masters of the scope. Incorporates newest uses and techniques. Fully illustrated.

No. 108

\$3.65

Hints and Kinks for TV, Radio and Audio

Edited by Martin Clifford

Hundreds of ideas and suggestions to make servicing easier, faster. Time-saving and money-saving gadgets you can make to help you in servicing. From Radio-Electronics Magazine.

No. 103

\$2.35



Oscilloscope Techniques

By Alfred Haas

How to use the scope in scores of new applications. Explains how to make tests and measurements, how to interpret patterns. Hundreds of photos of actual waveforms to help you.

No. 72

\$2.50

Electronics Data Handbook \$ 2.95

GERNSBACK LIBRARY, Inc.

New York, N. Y.