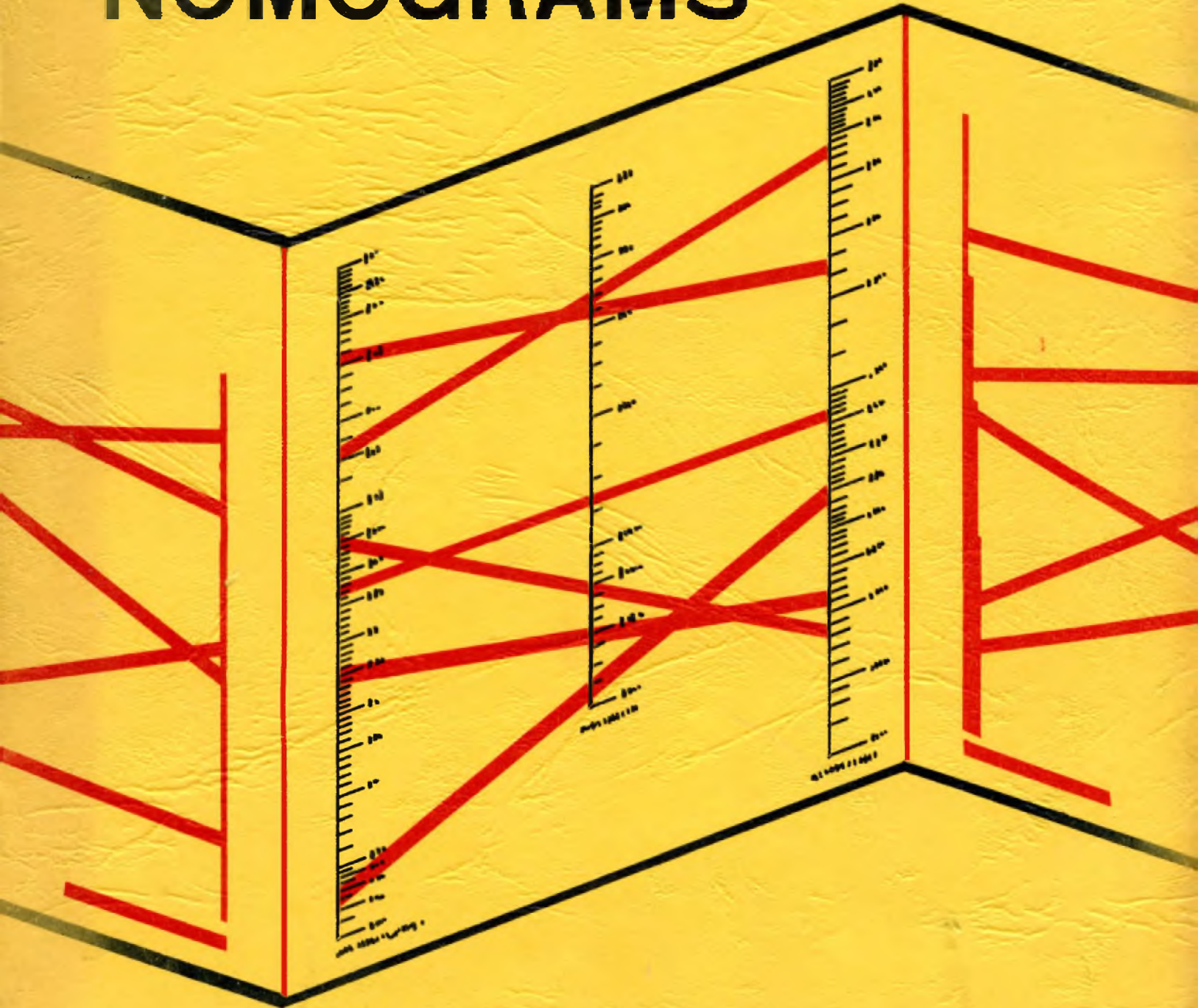




TAB BOOKS - NO. 254

\$9.95

# ELECTRONIC ENGINEERING NOMOGRAMS



By Max H. Applebaum

# **ELECTRONIC ENGINEERING NOMOGRAMS**

**By Max H. Applebaum**



**TAB BOOKS**

BLUE RIDGE SUMMIT, PA. 17214

FIRST EDITION

FIRST PRINTING—FEBRUARY 1968  
SECOND PRINTING—SEPTEMBER 1969  
THIRD PRINTING—SEPTEMBER 1972

Copyright © 1968 by TAB Books

Printed in the United States  
of America

Reproduction or publication of the content in any manner, without express permission of the publisher, is prohibited. No liability is assumed with respect to the use of the information contained herein.

Library of Congress Card Number: 68-21592

# Preface

Because of its simplicity, the nomogram or nomograph is often used by members of technical professions. Although computers are being relied upon to obtain rapid solutions to complicated equations which demand a high degree of accuracy, the nomogram has wide usage and will continue to be used for years to come. The nomograms presented in this book are based upon equations commonly used by engineers and technicians. Chapter One consists of simple, often-used equations and conversion charts for quick reference. Chapter Two, the largest section in the book, deals with the design of passive attenuator pads and filters. This chapter has been expanded to include many variations of simplified filters used at higher frequencies.

Characteristics of various types of transmission lines are included in Chapter Three. In addition to the more common lines, balanced shielded and the four-wire balanced lines are dealt with. In Chapter Four, passive electronic components are covered. Some design equations are given and several of the nomograms aid in test procedures. Chapter Five is devoted to vacuum tubes and transistors. An R-C coupled amplifier analysis is presented as a means of solving for component values. Other nomograms relate physical dimensions to component characteristics.

Finally, Chapter Six includes many nomograms which could possibly fit into several other chapters. That they are in the miscellaneous section is not meant to minimize their importance. On the contrary, several are among those most often used.

The author is grateful to the following publications for permission to reprint nomograms which first appeared in their magazines: Circuits Manufacturing, Simplified Inductance Test of Incoming Inspection, May/June 1965; EE (formerly Electronic Industries) A Chilton Publication, Coefficient of Coupling, August 1965—Rise Time Calculations, June 1965; EEE Magazine, Nonsymmetrical Pi and O Pads, June 1966—Low-Pass R-C Filters, April 1966—Low-Pass L-R Filters, August 1966—Low-Pass L-C Filters, May 1966—High-Pass L-R Filters, February 1967—Parallel-T Filters, November 1965—Bypass Capacitors, March 1966; EDN Magazine, Low-Pass Filters: Constant K, March 1967—Low-Pass Filters: M-Derived, April 1967—High-Pass Filters: Constant K and M-Derived (scheduled for publication)—VSWR, September 1965; Electronic Design, Life of Pilot Lights, December 1966; Electronic Products, Finding Characteristic Impedance of Transmission Lines (Nomograms 3-1, 3-4, 3-12,

3-15, 3-16), April 1966; Electronics World, Parallel Resistors, September 1965—Symmetrical Attenuator Pads, September 1966—T and H Attenuator Pads, March 1966 Transformer Turns Ratio, November 1965—Capacitance Measuring, January 1966—Amplifier Gain, August 1965—Power Output, May 1965—Percentage of Modulation, January 1967—UHF-TV Shorting Stub, June 1965; Electro-Technology (A Conover-Mast Publication), Ripple Current in Electrolytic Capacitors, August 1966—Frequency, Ratio of Frequency to Thickness in Quartz Crystals, July/August 1965—Volt/Age (now Electrical Apparatus Service — Volt/Age, Mulville-Barks Publications, Inc.), AC Motor-Starting Capacitor Measurement, April 1966. Special thanks to the following: William A. Stocklin, editor of Electronics World the first to except one of my nomographs for publications; George Rostky, editor of EEE Magazine, who offered encouragement in the writing of the book; all of the engineers at the Thomas Organ Company, who cheerfully took time from their busy schedule to offer help; and Esther Collen, for helping to type the final manuscript.

Special thanks is due Frank Caplan, my brother-in law, for introducing me to nomography, supplying me with reference material in the study of the subject, and helping me in every way possible. Last, but not least, I wish to express loving gratitude to my wife Helen and to my daughters Janet and Wanda. Their cheerful demeanor aided me psychologically during the periods of depression and melancholy which befell this neophyte author. To them, this book is dedicated.

Max H. Applebaum  
March 1968

# Table of Contents

<u>TITLE</u>	<u>NOMOGRAM</u>	<u>PAGE</u>
Chapter I - CONVERSION CHARTS AND OFTEN USED NOMOGRAMS.....		9
1. Peak, Average and RMS Conversion.....	1-1.....	11
2. Frequency vs Wavelength.....	1-2.....	13
3. Temperature Conversion.....	1-3.....	15
4. Parallel Resistors.....	1-4.....	17
5. db for Voltage, Current and Power Ratios.....	1-5.....	19
6. Reactance.....	1-6.....	21
7. Figure of Merit.....	1-7.....	23
8. Resonant Frequency.....	1-8.....	25
9. Tuned Circuit "Q".....	1-9.....	27
Chapter II - ATTENUATORS AND FILTERS.....		29
1. Symmetrical Attenuator Pads		
"T" and "H".....	2-1.....	31
"Pi" and "O".....	2-2.....	31
2. Non-Symmetrical "T" and "H" Attenuator Pads		
Solution of $R_3$ .....	2-3.....	33
Solution of $R_1$ and $R_2$ .....	2-4.....	33
3. Non-Symmetrical "Pi" and "O" Attenuator Pads		
Minimum Possible Pad Attenuation.....	2-5.....	35
Solution of $R_3$ .....	2-6.....	35
"B" Factors for $R_1$ and $R_2$ .....	2-7A.....	37
Solution of $R_1$ and $R_2$ .....	2-7B.....	37
4. Elementary Low Pass R-C Filter.....	2-8.....	39
5. Elementary Low Pass L-R Filter.....	2-9.....	41
6. Elementary Low Pass L-C Filter.....	2-10.....	43
7. Elementary High Pass L-R Filter.....	2-11.....	45
8. Elementary High Pass R-C Filter.....	2-12.....	47
9. Elementary High Pass L-C Filter.....	2-13.....	49
10. Low Pass Filters		
Constant $k$ .....	2-14.....	51
Series and Shunt $m$ -Derived		
Solution of $m$ .....	2-15.....	53
Solution of Component Values.....	2-16.....	53
11. High Pass Filters		
Constant $k$ .....	2-17.....	57
Series and Shunt $m$ -Derived		
Solution of $m$ .....	2-18.....	59
Solution of Component Values.....	2-19.....	61

12. Band Pass Filters		
Constant k		
Solution of $L_1$ and $C_2$ .....	2-14.....	51
Solution of $L_2$ and $C_1$ .....	2-20.....	63
Series and Shunt m-Derived		
Solution of $f_m$ and $N$ .....	2-21.....	65
Solution of $F_A$ and $F_B$ (To determine m).....	2-22A....	67
Solution of $m$ .....	2-22B....	67
Solution of $L_3$ and $C_3$ .....	2-19.....	61
Solution of $L_4$ and $C_5$ .....	2-23.....	67
Solution of $L_5$ and $C_4$ .....	2-24.....	69
Solution of $L_6$ and $C_7$ .....	2-25.....	71
Solution of $L_7$ and $C_6$ .....	2-26.....	71
Solution of $L_8$ and $C_8$ .....	2-19.....	61
13. Parallel-T Filter .....	2-27.....	73
Constant k		
Solution of $L_1$ and $C_2$ .....	2-28.....	75
Solution of $L_2$ and $C_1$ .....	2-17.....	57
Series and Shunt m-Derived		
Solution of $f_m$ .....	2-21.....	65
Solution of $F_A$ and $F_B$ (To determine m).....	2-22A....	67
Solution of $m$ .....	2-22B....	67
Solution of $L$ and $C$ values .....	2-19.....	61
14. Band Elimination Filters		

Chapter III - TRANSMISSION LINES ..... 77

1. RF Transmission Lines		
Solution of $Z_0$ .....	3-1.....	79
Solution of Alpha .....	3-2.....	79
Solution of Beta .....	3-3.....	81
2. Open Two-Wire Transmission Lines		
Solution of $Z_0$ .....	3-4.....	83
Solution of $L$ and $C$ .....	3-5.....	83
Solution of $r$ .....	3-6.....	85
3. Single Wire Above Ground		
Solution of $Z_0$ .....	3-7.....	87
Solution of $L$ and $C$ .....	3-8.....	87
Solution of $r$ .....	3-9.....	89
4. Four-Wire Transmission Line		
Solution of $Z_0$ .....	3-10.....	91
Solution of $L$ and $C$ .....	3-11.....	91
Solution of $r$ .....	3-9.....	89
5. Co-Axial Cable		
Solution of $Z_0$ .....	3-12.....	93
Solution of $L$ and $C$ .....	3-13.....	93
Solution of $r$ .....	3-14.....	95
6. Balanced Shielded Line		
Solution of Secondary Values		
Solution of $Z_0$ .....	3-15.....	97

Chapter IV - PASSIVE COMPONENTS ..... 99

1. Single Layer Air-Core Coil .....	4-1.....	101
2. Cefficient of Coupling .....	4-2.....	103

3.	Mutual Inductance.....	4-3.....	103
4.	Transformer Turns Ratio .....	4-4.....	107
5.	Inductive Impedance Test Procedure .....	4-5.....	109
6.	Electrolytic Energy Storage.....	4-6.....	111
7.	Electrolytic Capacitance Measurement .....	4-7.....	113
8.	AC Motor Starter Capacitance Measurement .....	4-8.....	115
9.	Temperature Coefficient.....	4-9.....	117
10.	Maximum Allowable Power Dissipation.....	4-10.....	119
11.	DC Watts and Leakage Current .....	4-11.....	121
12.	Equivalent Series Resistance and Dissipation Factor.....	4-12.....	121
13.	Bypass Capacitor .....	4-13 .....	123
Chapter V - VACUUM TUBES AND TRANSISTORS .....			125
1.	R-C Coupled Amplifier		
	Parallel Resistance (Aid in solutions) .....	5-1.....	127
	Triode Tube Characteristics.....	5-2.....	129
	Pentode Tube Characteristics .....	5-3.....	131
	Mid-Frequency Stage Gain for Triode Amp. ....	5-4.....	131
	Mid-Frequency Stage Gain for Pentode Amp. ....	5-5.....	133
	High-Frequency Stage Gain .....	5-6 A & B	135
	Low-Frequency Stage Gain .....	5-7 A & B	137
2.	Rectification Efficiency .....	5-8.....	139
3.	Heat Sink for Transistors .....	5-9.....	141
4.	Transistor Frequency vs Base Width.....	5-10.....	143
5.	Frequency Thickness for Quartz Crystals.....	5-11.....	145
Chapter VI - MISCELLANEOUS .....			147
1.	Nyquist Noise Voltage .....	6-1 .....	149
2.	Amplifier Gain .....	6-2.....	151
3.	Amplifier Power Output .....	6-3.....	153
4.	Percent Modulation.....	6-4.....	155
5.	Tuning Fork Frequency .....	6-5.....	157
6.	Light Intensity Nomogram.....	6-6.....	157
7.	Wire Stranding Chart .....	6-7.....	161
8.	Time Constant and Rise Time .....	6-8.....	163
9.	Separation Loss in a Magnetic Recording System .....	6-9.....	165
10.	Deflection Yoke Conversion		
	Current vs Deflection Angle .....	6-10.....	167
	Current vs Anode Voltage .....	6-11.....	169
	Current vs Yoke Inductance.....	6-12.....	169
11.	Pilot Light Nomogram .....	6-13.....	171
12.	UHF TV Shorting Stub .....	6-14.....	173
13.	VSWR Nomogram .....	6-15.....	175






## CHAPTER 1

# Conversion Charts and Often-Used Nomograms
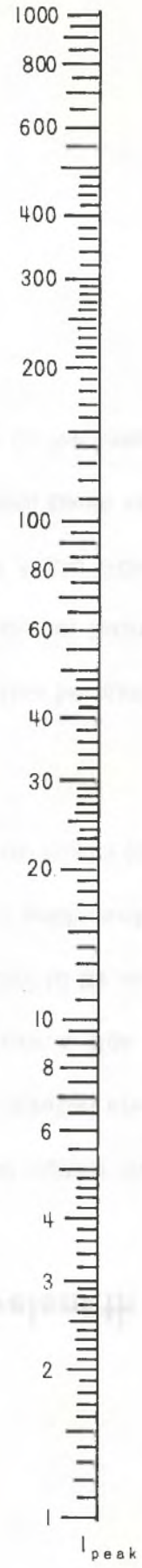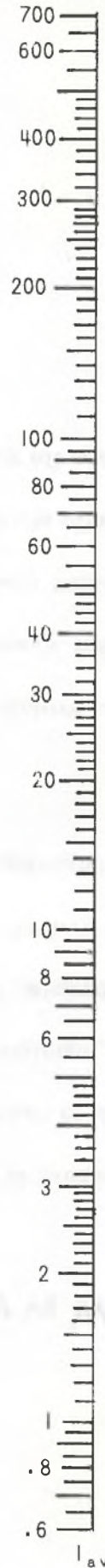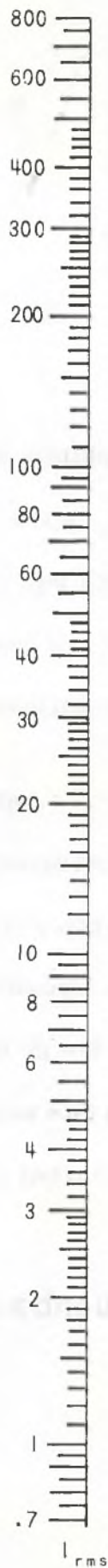
## Peak, Average, and rms Conversion


When one of the values of a sine-wave current or voltage is known, the other two may be found simply by drawing a straight line, perpendicular to all three scales, through the value of the known. Values other than those shown may be determined by merely multiplying all scales by the same factor.



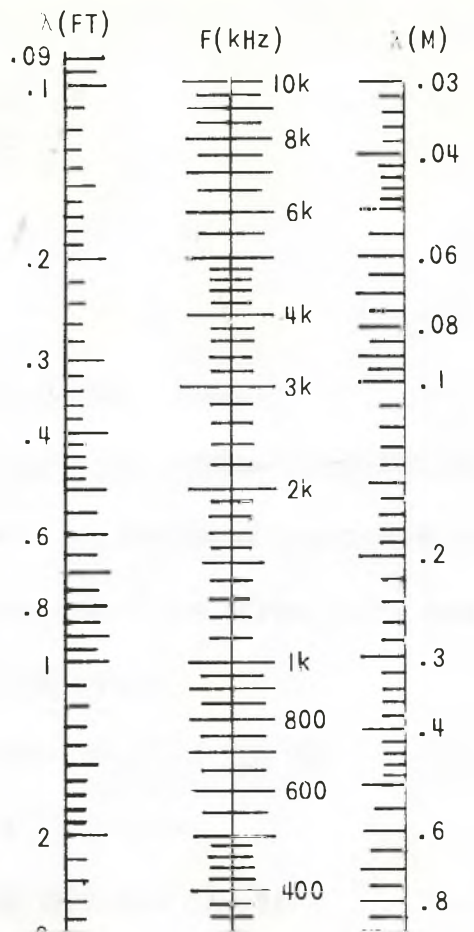
## Frequency vs Wavelength

Frequency in Hertz can be converted rapidly to wavelength in meters or feet with the use of this parallel chart. To find the wavelength of any frequency, draw a line through the value of the frequency, and perpendicular to its scale. Wavelength in feet is found on the left-hand scale and wavelength in meters is found on the right-hand scale where the line intersects each scale.

Conversion from feet to meters can also be made by drawing a perpendicular line through both scales intersecting the known value. The unknown value is found where this line intersects its scale. Values other than those shown may be used by merely multiplying all scales by the same factor.



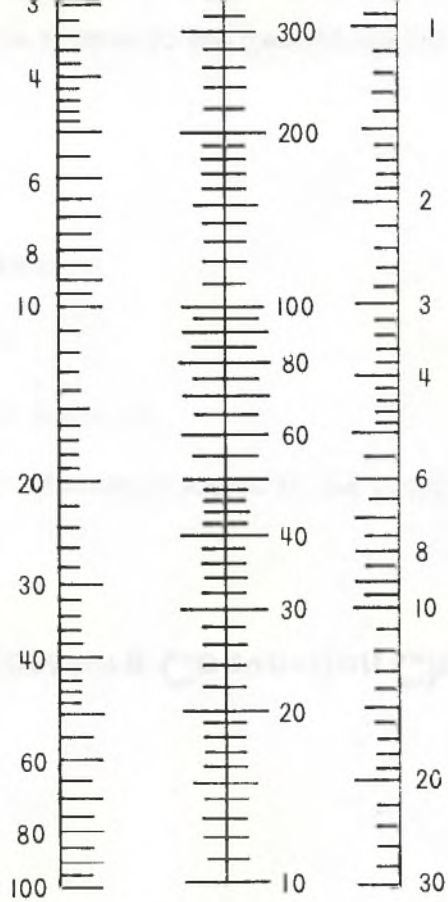

## Temperature Conversion Chart


The five major temperature scales in use today are:

1. Centigrade (Celsius)
2. Fahrenheit
3. Kelvin (Absolute)
4. Rankine
5. Reamur

The other four are related to the Centigrade scale as follows:

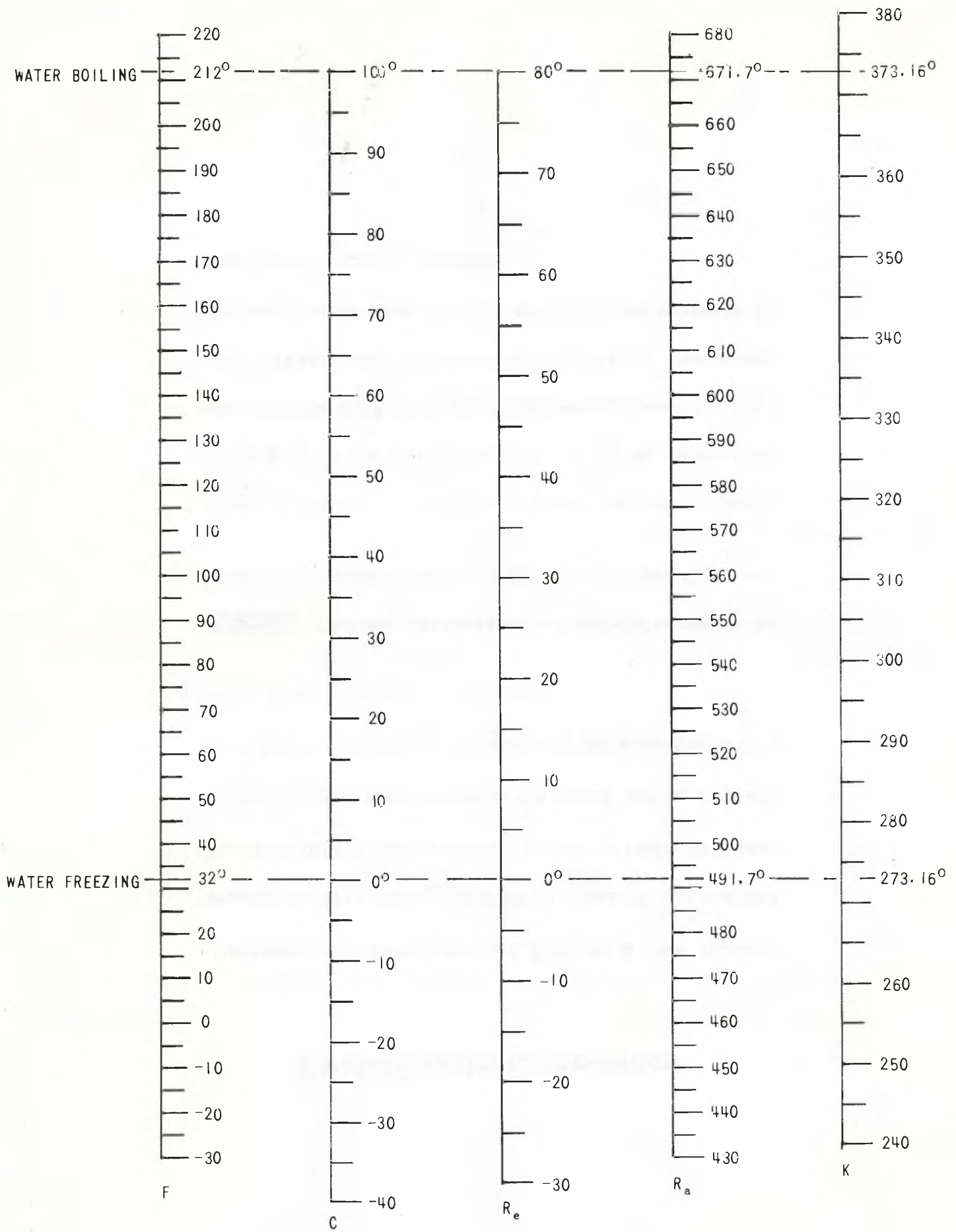1. Fahrenheit (F) =  $(9/5 C) + 32$
2. Kelvin (K) =  $C + 273.16$
3. Rankine (Ra) =  $1.8 (C + 273.16)$
4. Reamur (Re) =  $4/5 C$

Conversion from any of the scales to all others is easily done by drawing a perpendicular line through all scales simultaneously. The chart includes all temperatures between water boiling and freezing points.






## Parallel Resistor Computation

Engineers and technicians will find this a most valuable nomogram. It is unique, insofar as standard EIA resistor values are indicated on all scales. Values of resistors larger or smaller than those shown on the scales can be mentally calculated by multiplying all scales by the same factor  $10^n$ , where  $n$  may be positive or negative.

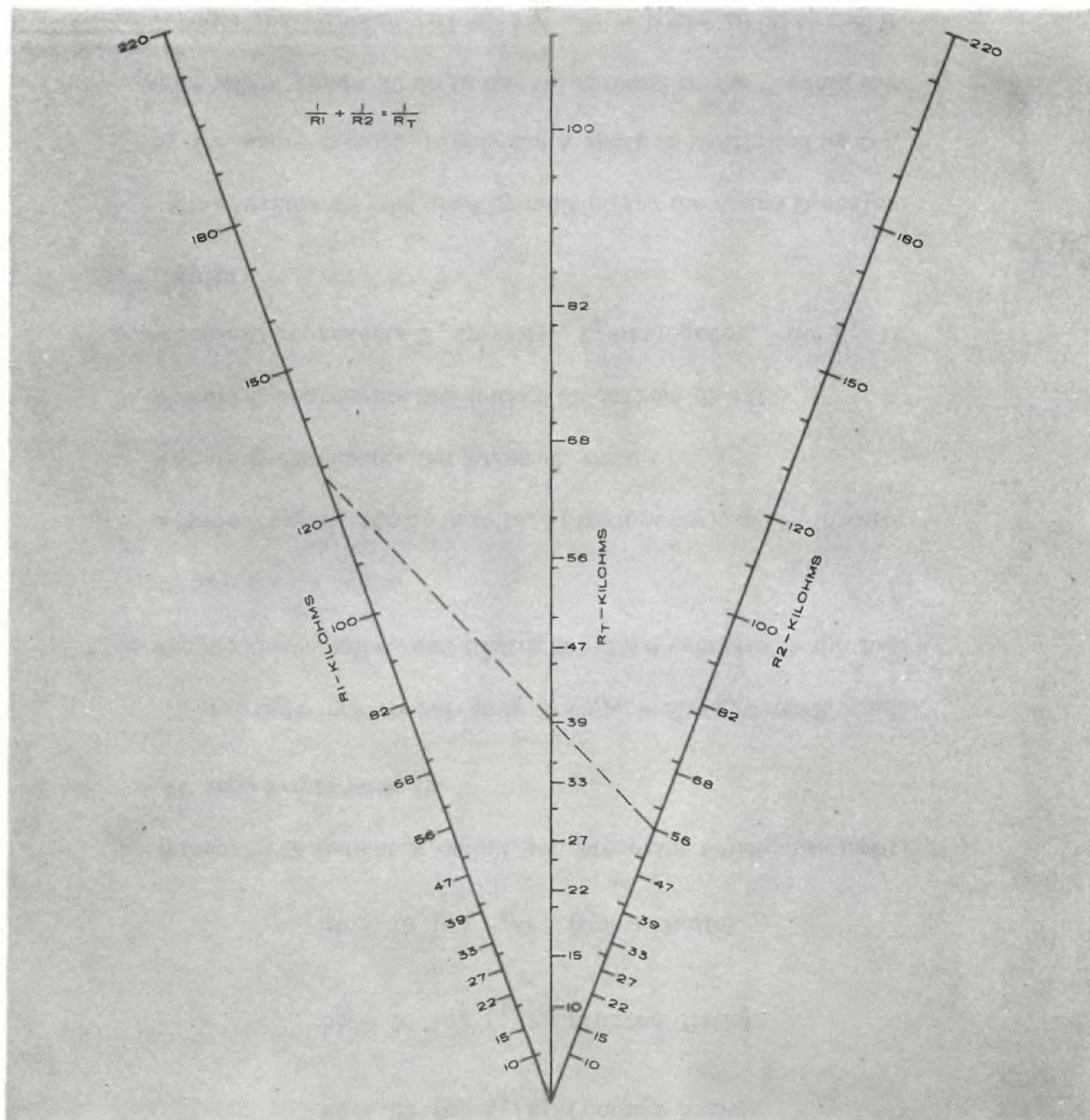Example: Find the correct value of a resistor necessary to shunt a 560,000-ohm resistor to get a total of 390,000 ohms.

Solution: Place a straight-edge across the three scales, crossing 56 on the  $R_2$  scale and 39 on the  $R_T$  scale. The solution is the point where the straight-edge crosses the  $R_1$  scale. In this case, it crosses just below 130. The closest EIA value on the scale is 120. Multiplying all scales by 10 gives an answer of 1.2 megohms.



# db Conversion

Decibel gain or loss for voltage, current, and power are found from the following equations:

$$\text{db} = 20 \log E_2/E_1 \text{ (Voltage Ratio)}$$

$$\text{db} = 20 \log I_1/I_2 \text{ (Current Ratio)}$$


$$\text{db} = 10 \log P_2/P_1 \text{ (Power Ratio)}$$

Subscript 2 indicates output and subscript 1 indicates input. All logs are to base 10.

These equations are solved by drawing a straight line through the two known values and finding the third value where the line intersects its scale.

- Scale A represents  $E_2$  in volts,  $I_1$  in amperes, and  $P_2$  in watts
- Scale B represents the power db ratio
- Scale C represents the voltage or current db ratio
- Scale D represents  $E_1$  in volts,  $I_2$  in amperes, and  $P_1$  in watts

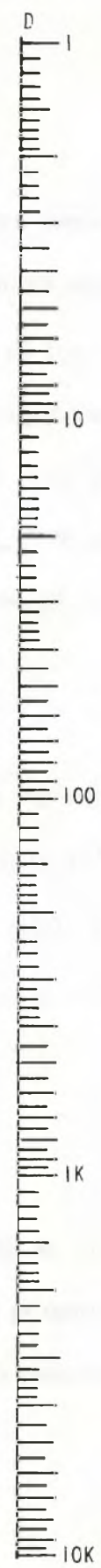Other values may be used by multiplying the A and D scales by the same factor. If only the A scale is multiplied by  $10^n$ , then add  $n$  times 20 db to the value found on the C scale for voltage and current ratios, and add  $n$  times 10 db to the B scale for power ratios.



## Reactance Calculation

The equations for inductive and capacitive reactance are:

$$X_L = 2 \pi fL$$

and

$$X_C = \frac{1}{2 \pi fC}$$


When the values of  $f$ ,  $L$ , and  $C$  are known,  $X_L$  and  $X_C$  are found by drawing two lines between the appropriate values on the given scales.  $X_L$  is found on the right side of the center scale for the line extended to  $L$ , and  $X_C$  is found on the left side of the center scale for the line extended to  $C$ .

For values other than those shown on the scales, multiply the appropriate scale by  $10^n$ , where  $n$  may be positive or negative. For inductive reactance calculations, when either  $L$  or  $f$  is multiplied by  $10^n$ , the  $X_L$  value found on the chart must also be multi-

plied by  $10^n$ . For capacitive reactance calculations, when either  $C$  or  $f$  is multiplied by  $10^n$ , then the  $X_C$  value found on the chart must be multiplied by  $10^{-n}$ .

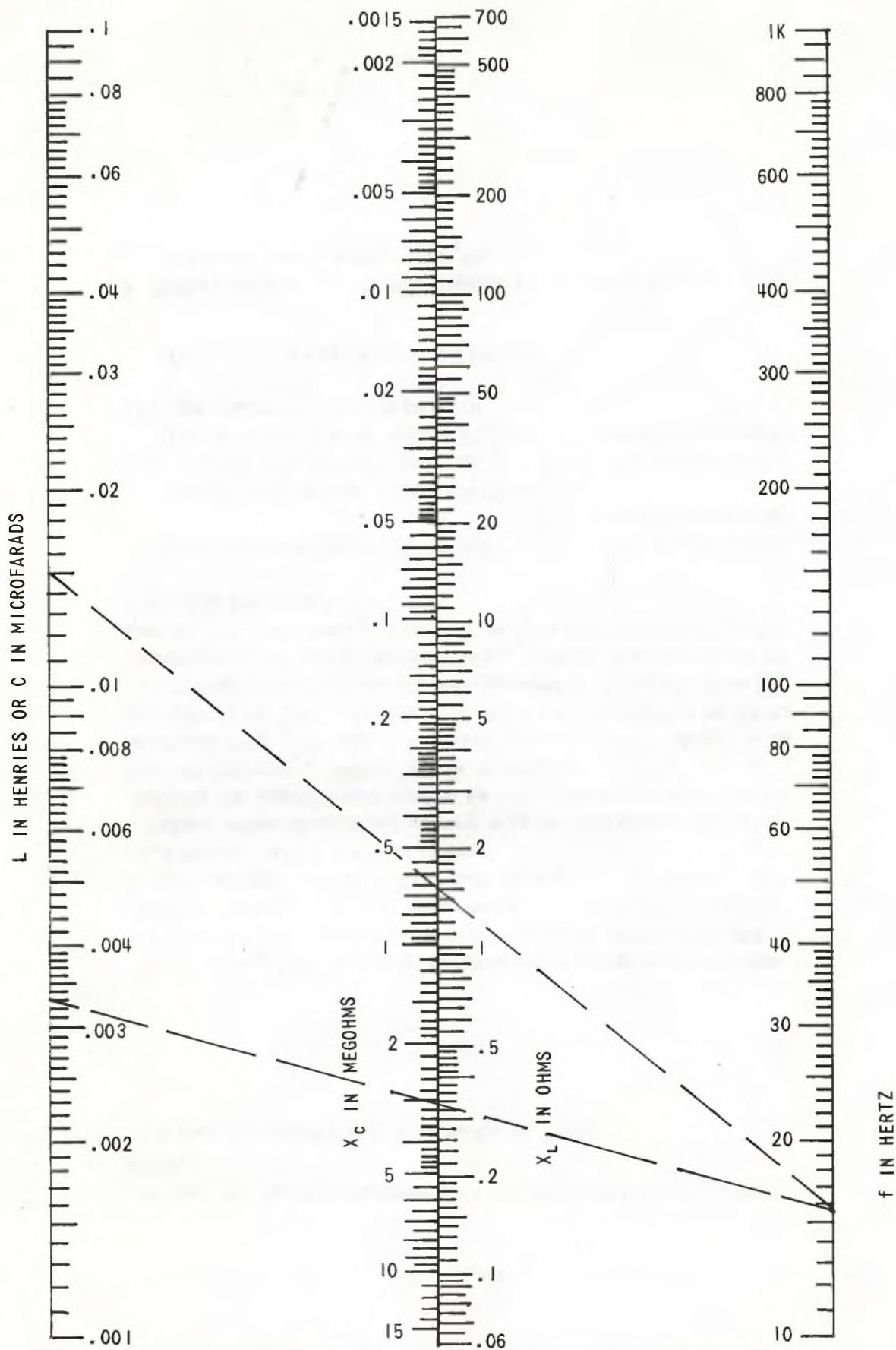Example: Find  $X_C$  for a .0033 microfarad capacitor and  $X_L$  for a .15-henry coil at a frequency of 15,750 Hz. (The solution is shown by the broken line.)

NOTE: Since  $f$  was multiplied by  $10^3$ , then  $X_C$  must be multiplied by  $10^{-3}$ , giving a capacitive reactance of 3.1K. For inductive reactance the  $L$  scale was multiplied by  $10^1$  and the  $f$  scale was multiplied by  $10^3$ . Therefore, the value of  $X_L$  found on its scale must be multiplied by  $10^4$ , and the inductive reactance is calculated as 15K.



## Figure of Merit

The figure of merit (Q) of a coil is defined by the equation:

$$Q = X_L / R$$

Where:  $X_L$  is the reactance of the coil and R is its resistance.

The coil impedance can then be found from:

$$Z = QX_L$$


Q and Z can both be found by merely drawing one line from the values of  $X_L$  and R on their respective scales. Q and Z are found where the line intersects the appropriate scale. In the example shown,  $X_L = 500$  ohms,  $R = 40$  ohms,  $Q = 12.5$  ohms, and  $Z = 6,250$  ohms.

Values other than those shown may be determined by multiplying the appropriate scales by  $10^n$ , where n may be positive or negative. When  $X_L$  is multiplied by  $10^n$ , then Q is multiplied by  $10^n$  and Z is multiplied by  $10^{2n}$ . When R is multiplied by  $10^n$ , then both Q and Z are multiplied by  $10^{-n}$ .

Q values greater than 10 are generally desired. For the convenience of scale modification, values of Q are given as low as .01. However, accuracy of Q is determined from the following factors.\*

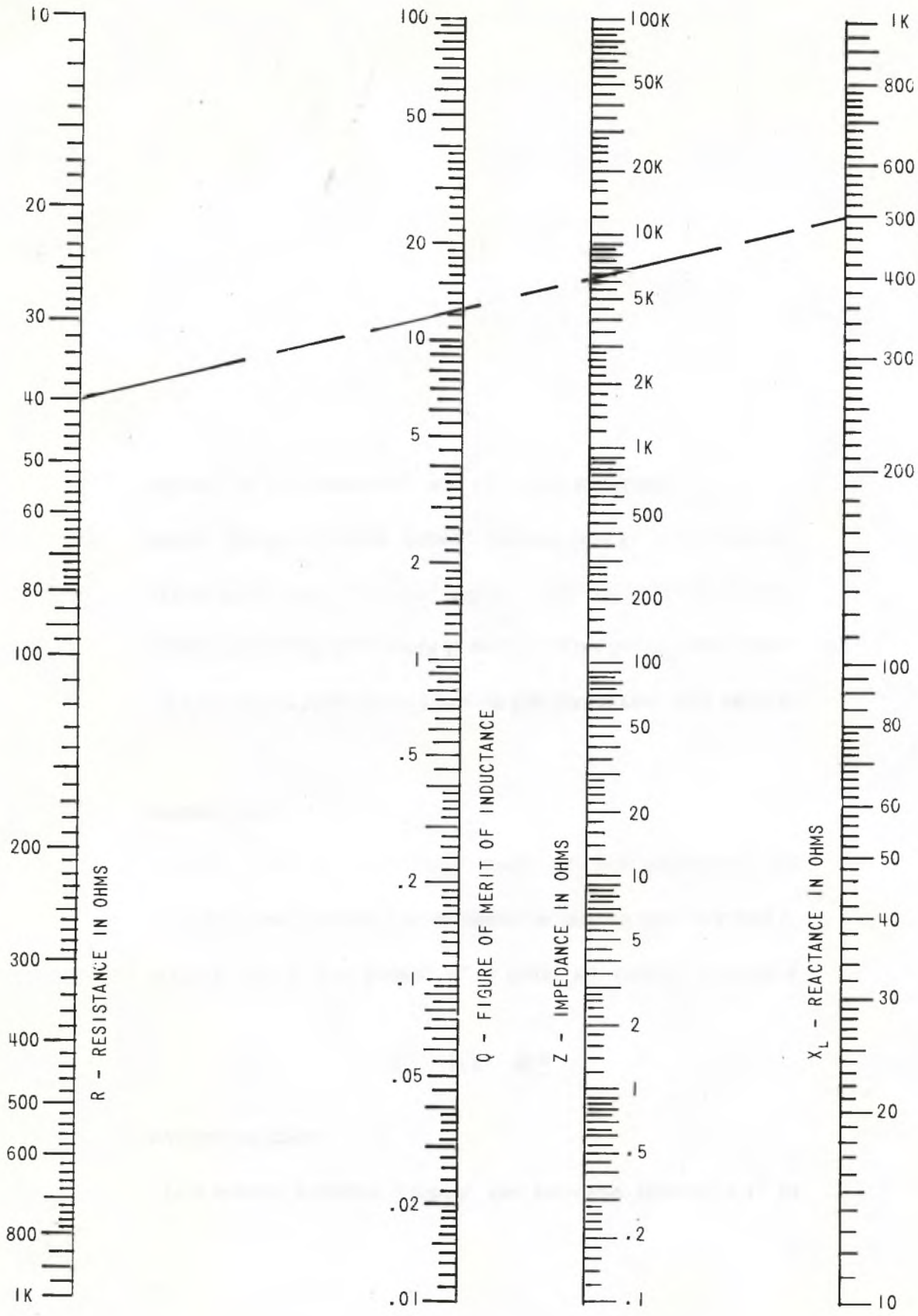- (1) Approximate error in percent =  $-\frac{100}{Q^2}$  (for small resistive components)  
for  $Q = 10$ , error equals 1% (low)
- (2) Approximate error in percent =  $-100 Q^2$  (for small reactive components)  
for  $Q = 0.1$ , error equals 1% (low)
- (3) Approximate error in percent =  $+\frac{50}{Q^2}$   
for  $Q = 7$ , error equals 1% (high)

\* Reference Data for Radio Engineers, second edition, J.J. Little and Ives, 1946, page 70






## Resonant Frequency Calculation

In a series resonant circuit, the resonant frequency  $f_0$  is calculated from:

$$f_0 = 1/2\pi \sqrt{LC}$$

When L and C are known,  $f_0$  is found by simply drawing a straight line through the appropriate values on the L and C scales. Read the value of  $f_0$  where the line intersects the center scale.

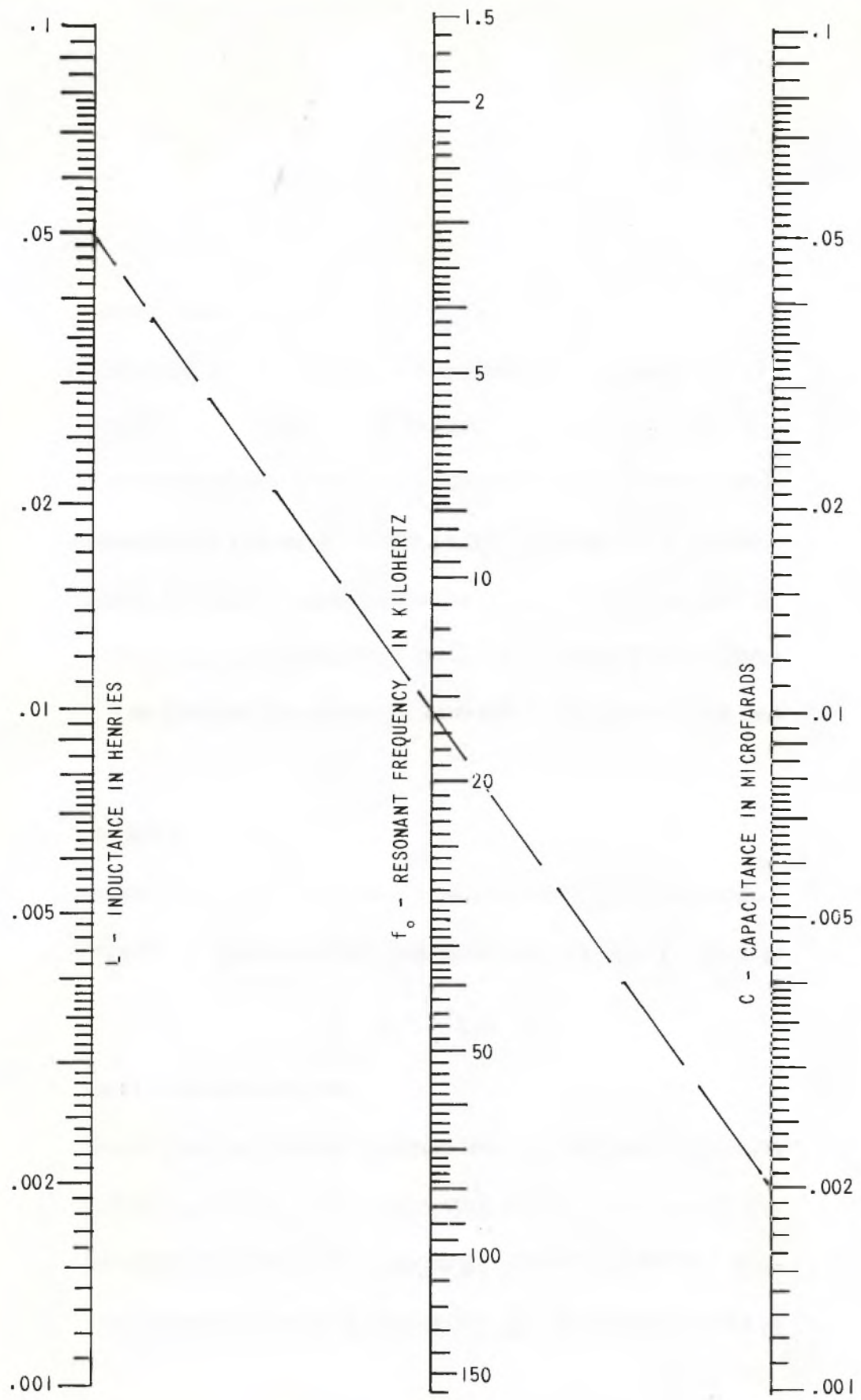Values other than those given on the nomogram may be calculated by multiplying both L and C scales by  $10^n$  and multiplying the  $f_0$  scale by  $10^{-n}$ , where  $n$  may be positive or negative. In the example shown, broken line C = .002 microfarads, L = .05 henries, and  $f_0 = 15.9$  kiloHertz.




## Tuned Circuit "Q" Determination

An accurate method of finding the "Q" of a tuned circuit is to sweep the tuned circuit about its resonant frequency, finding the frequencies above and below resonance which are 3 db down from the voltage at resonance, and calculating the value of Q from the equation:

$$Q = f_o / \Delta f$$

where:  $f_o$  is the resonant frequency and  $\Delta f = f_H - f_L$  the 3 db bandwidth, ( $f_H$  is the upper 3 db point and  $f_L$  is the lower 3 db point).

The equation is solved by drawing a line through the two known values and finding the third value where the line intersects its scale. Other values of  $f_o$  and  $\Delta f$  may be used by multiplying the scale values by  $10^n$ , where  $n$  may be negative or positive. When  $f_o$  is multiplied by  $10^n$ , then Q is multiplied by  $10^n$ . When  $\Delta f$  is multiplied by  $10^{-n}$ , then Q is multiplied by  $10^{-n}$ . In the example shown:  $\Delta f = 700$  Hz,  $f_o = 10$  k Hz, and  $Q = 14.5$ .

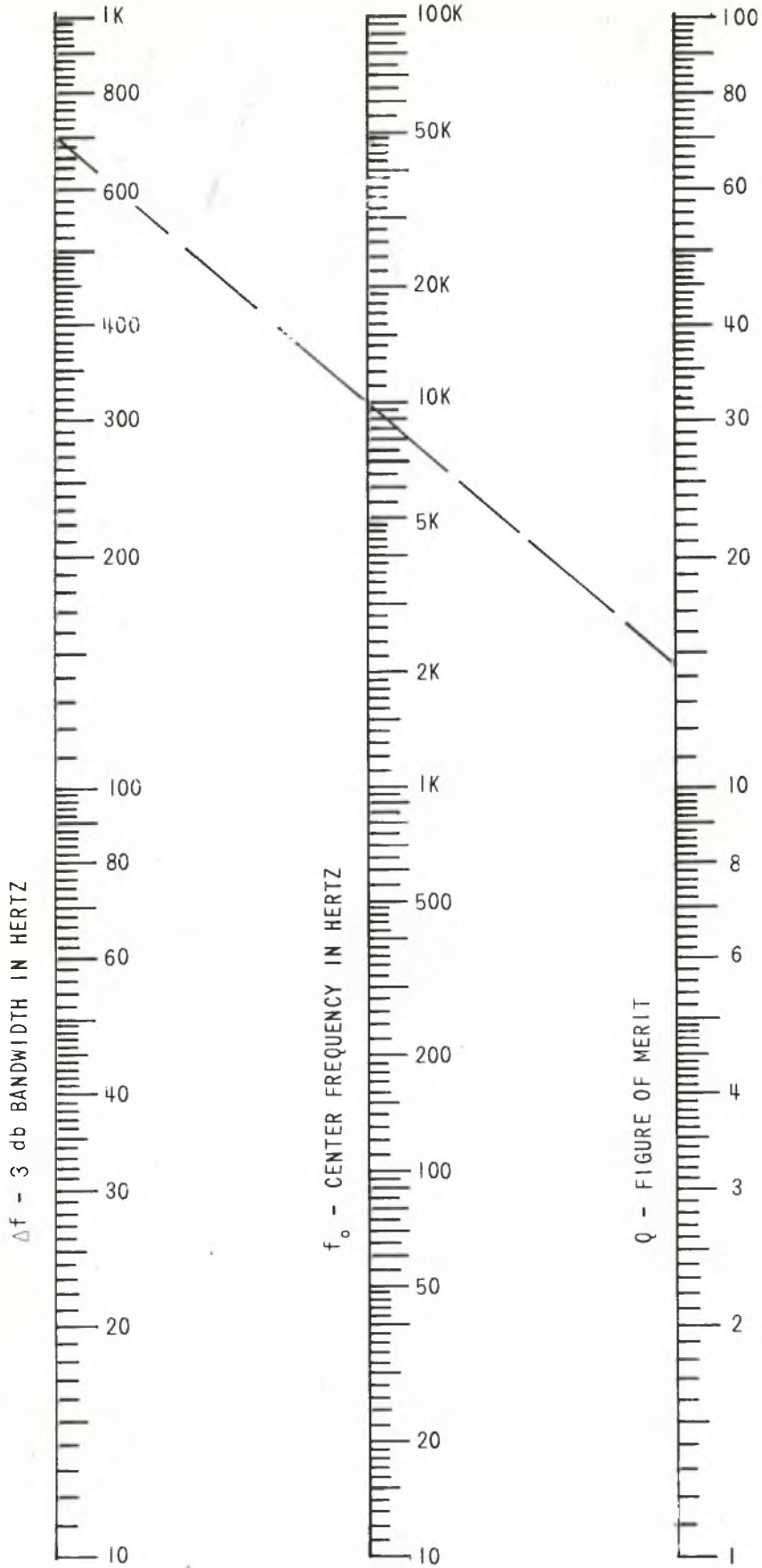

## CHAPTER 2

# Attenuators and Filters

## Symmetrical Attenuator Pads (T, H, Pi, O)

Resistive pads are a common means of attenuating audio, video, and radio frequencies without disturbing the circuit impedances. These nomograms provide a rapid method of determining the values of resistors to make up such pads. The nomograms are for symmetrical pads in which the impedances looking into the pads from both sides are equal.

Nomogram 2-1 is for the solution of symmetrical T and H pads where  $Z_1 = Z_2 = Z$ .  $R_1$  and  $R_3$  are the same for both pads and are found in the following manner:

(1) From the value of  $Z$  in the left-hand column draw a line to the number of db attenuation desired on the  $N(R_3)$  scale. Find the value of  $R_3$  where the line crosses its scale.

(2) From the same value of  $Z$  draw a line to the same number of db attenuation in the  $N(R_1)$  scale. Find the value of  $R_1$  where the line crosses its scale.

Example: Design a 10 db pad for an unbalanced 75-ohm coaxial cable terminating in its own impedance.

Solution: (1) Extend a line from 75 on the  $Z$  scale to 10 on the  $N(R_3)$  scale. The line

crosses the  $R_3$  scale at 52, which is the value of  $R_3$  in ohms.



(2) Extend a second line from 75 on the  $Z$  scale to 10 on the  $N(R_1)$  scale. The line crosses the  $R_1$  scale at 39, which is the value of  $R_1$  in ohms.

Nomogram 2-2 is for the solution of symmetrical Pi and O pads where  $Z_1 = Z_2 = Z$ .  $R_1$  and  $R_3$  are the same for both pads and are found in a similar manner to Nomogram 2-1.


Example: Design a 6 db pad (O type) to attenuate a strong signal causing overload on all channels in a TV receiver. The wire used is 300-ohm twin-lead and connects to a balanced 300-ohm input at the antenna terminals of the tuner.

Solution: (1) Extend a line from 300 on the  $Z$  scale to 6 on the  $N(R_1)$  scale. This line crosses the  $R_1$  scale at 900, which is the value of  $R_1$  in ohms.

(2) Extend a second line from 300 on the  $Z$  scale to 6 on the  $N(R_3)$  scale. This line crosses the  $R_3$  scale at 225 which is the value of  $R_3$  in ohms.

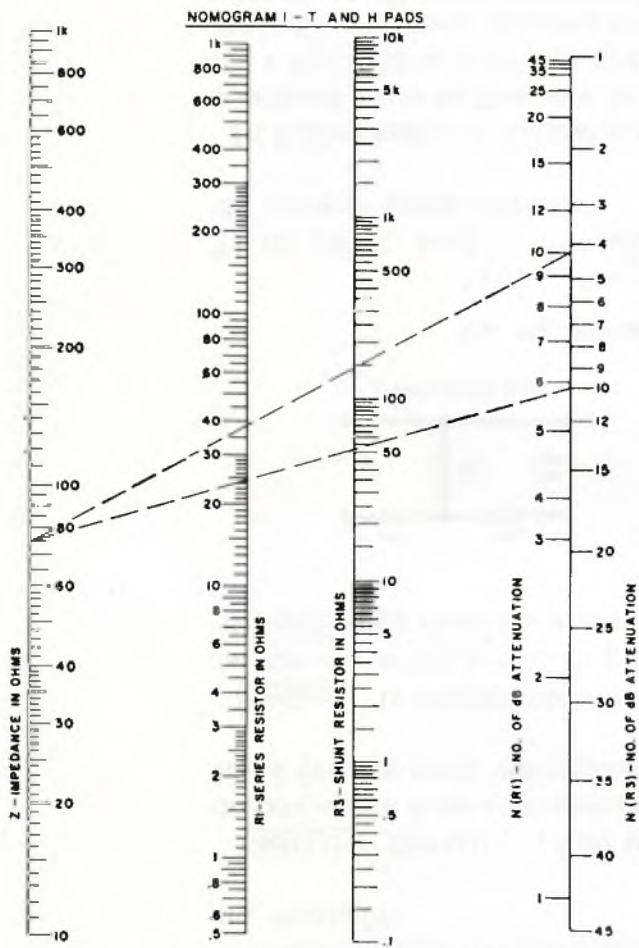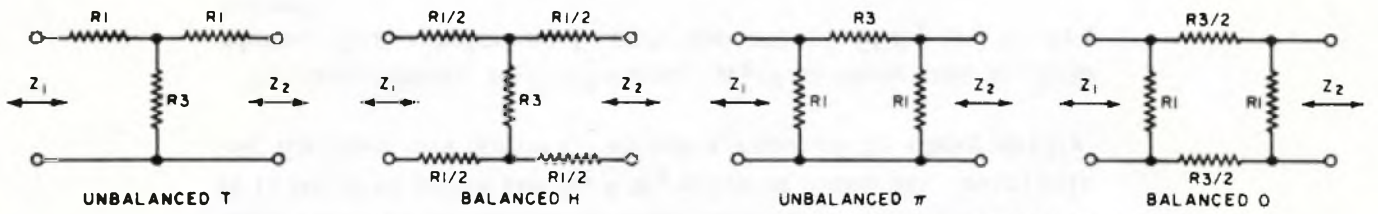

Nomogram 2-1

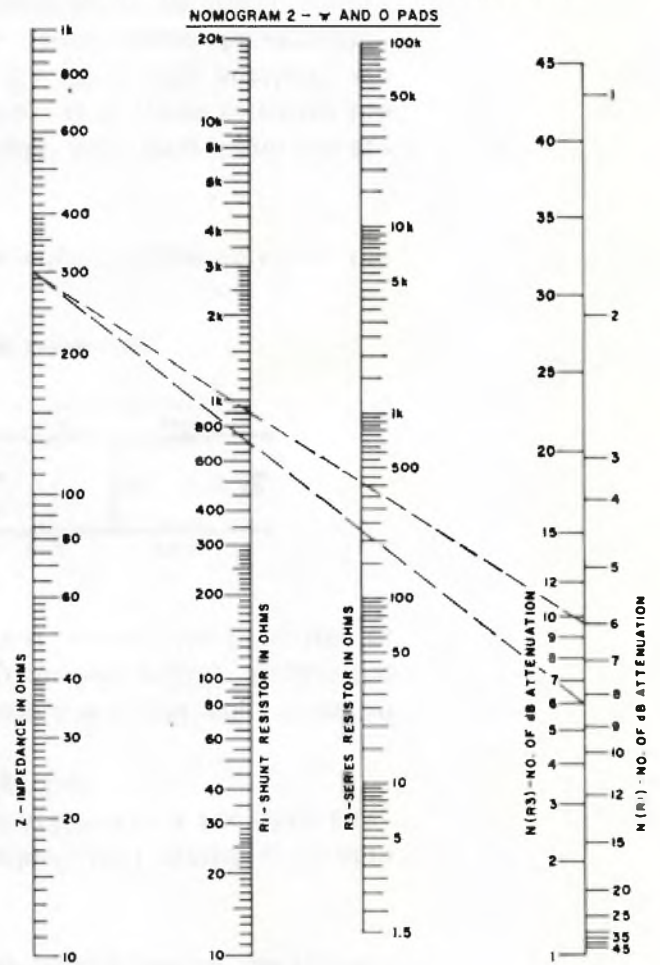

Nomogram 2-2

## I and H Attenuator Pads

The use of Nomograms 2-3 and 2-4 provide a simplified and rapid means of calculating component values for unbalanced T and balanced H nonsymmetrical attenuator pads for audio or RF applications. These pads have different value impedances looking into and out of the circuit. Schematics of the pads are shown in Fig. 2-3. The formulas used for the nomograms are adaptations of standard equations. The method of using the nomograms is illustrated in the following example.

**Example:** Design a 12 db pad which will match a 75-ohm coaxial cable from a distribution amplifier to a receiver having a 50-ohm input unbalanced to ground.

**Solution:** In Nomogram 2-3, extend a straight-edge from 50 on the  $Z_2$  scale to 12 on the attenuation scale. Rotate the straight-edge about the point where it crosses the pivot line to

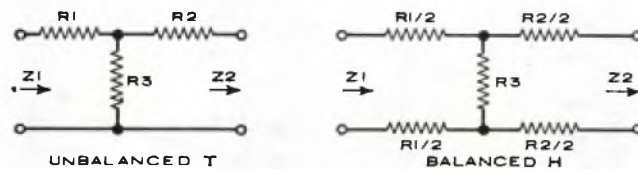


Fig. 2-3. Typical pad schematics.


75 on the  $Z_1$  scale. The straight-edge is found to cross the  $R_3$  scale at about 33 ohms.

In Nomogram 2-4, extend a straight-edge from 12 on the attenuation scale to 75 on the  $Z_1$  scale. It is found to cross the  $R_1 + R_3$  scale at 85. Subtracting  $R_3$  from this number, we get a value of about 52 ohms for  $R_1$ . Now extend the straight-edge from 12 on the attenuation scale to 50 on the  $Z_2$  scale. It is found to cross the  $R_2 + R_3$  scale at about 56. Subtracting  $R_3$  from this number, we get a value of 23 ohms for  $R_2$ .


To summarize,  $R_1 \approx 52$  ohms,  $R_2 \approx 23$  ohms and  $R_3 \approx 33$  ohms. For a balanced H pad, the values of  $R_1$  and  $R_2$  are halved.

NOTE: In Nomogram 2-3, the  $Z_1$  scale is used in conjunction with the  $R_1 + R_3$  scale, and the  $Z_2$  scale is used in conjunction with the  $R_2 + R_3$  scale.



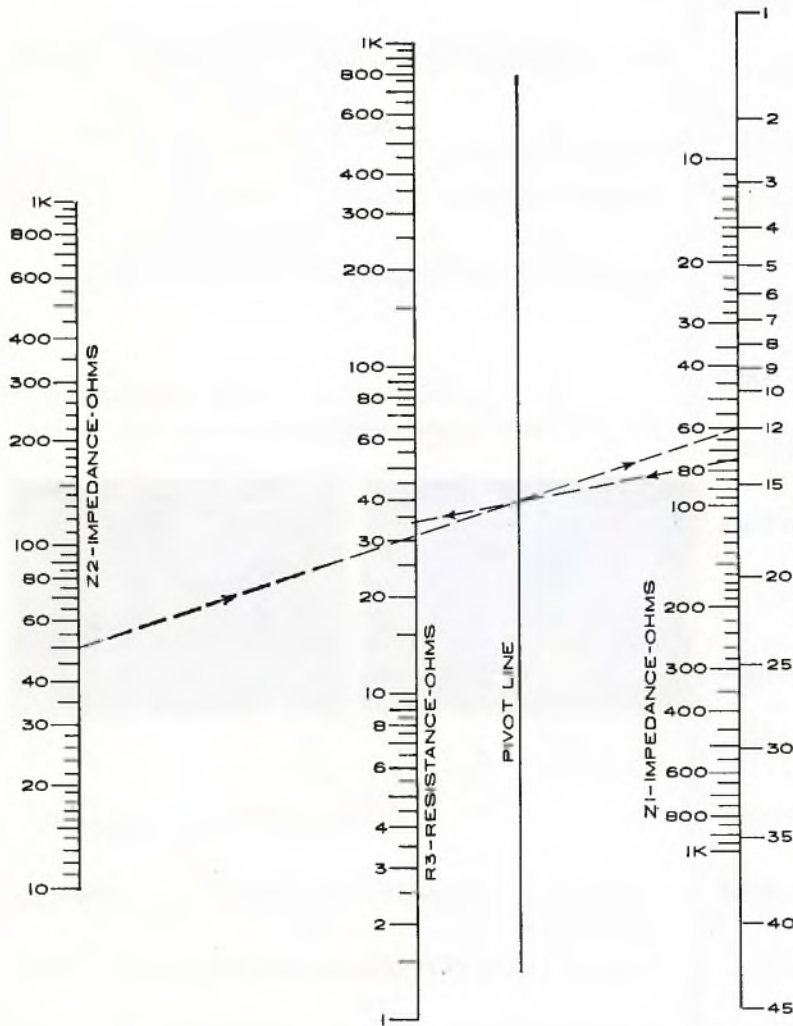

Nomogram 2-3

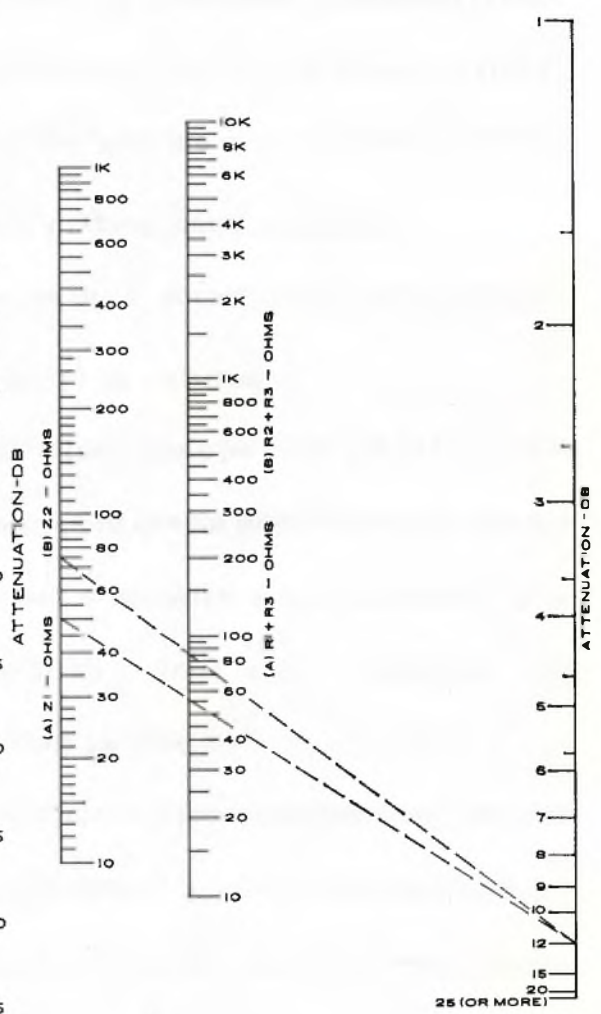

Nomogram 2-4

## Nonsymmetrical Pi and O Pads

Nonsymmetrical matching pads are called for when a signal must be attenuated between a generator with one impedance and a load with another. Among the simpler and more popular pads, we have the unbalanced Pi (Fig. 2-4A) and the balanced O (Fig. 2-4B). These can be quickly and easily designed with the help of Nomogram 2-5.

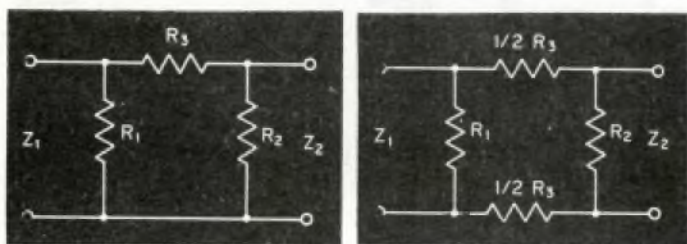


Fig. 2-4. Two very popular matching pads, the unbalanced Pi (a) and the balanced O (b).

In Fig. 2-4,  $R_1$ ,  $R_2$ , and  $R_3$  have the same values for both pads. (These resistors should be noninductive RF typed for best performance.) Their values can be calculated from three equations:

$$R_3 = \frac{N-1}{2} \sqrt{\frac{Z_1 Z_2}{N}} \quad (1)$$

$$\frac{1}{R_1} = \frac{N+1}{Z_1(N-1)} - \frac{1}{R_3} \quad (2)$$

$$\frac{1}{R_2} = \frac{N+1}{Z_2(N-1)} - \frac{1}{R_3} \quad (3)$$

where:  $N$  is the ratio of generated power to output power.

Nomogram 2-5 shows the minimum possible attenuation as a function of the  $Z_1/Z_2$  ratio, where  $Z_1$ , always considered larger than  $Z_2$ , can represent either the source or the load impedance. When it's necessary to design a minimum-loss matching pad, the loss can never be zero unless of course  $Z_1 = Z_2$ ,


which gives a unity ratio. Obviously, for this case a matching pad isn't needed. It is impossible to design these pads with less attenuation than shown because negative resistance would be required.

The use of the nomograms is best illustrated with a typical design problem.


**Problem:** Assume it is necessary to design a 12 db attenuator to match a 75-ohm line to a 300-ohm TV input using a balanced O configuration.

**Solution:** First use Nomogram 2-5 and notice that a  $Z_1/Z_2$  ratio of four (from 300/75) has a minimum possible attenuation of


(Continued on next page)

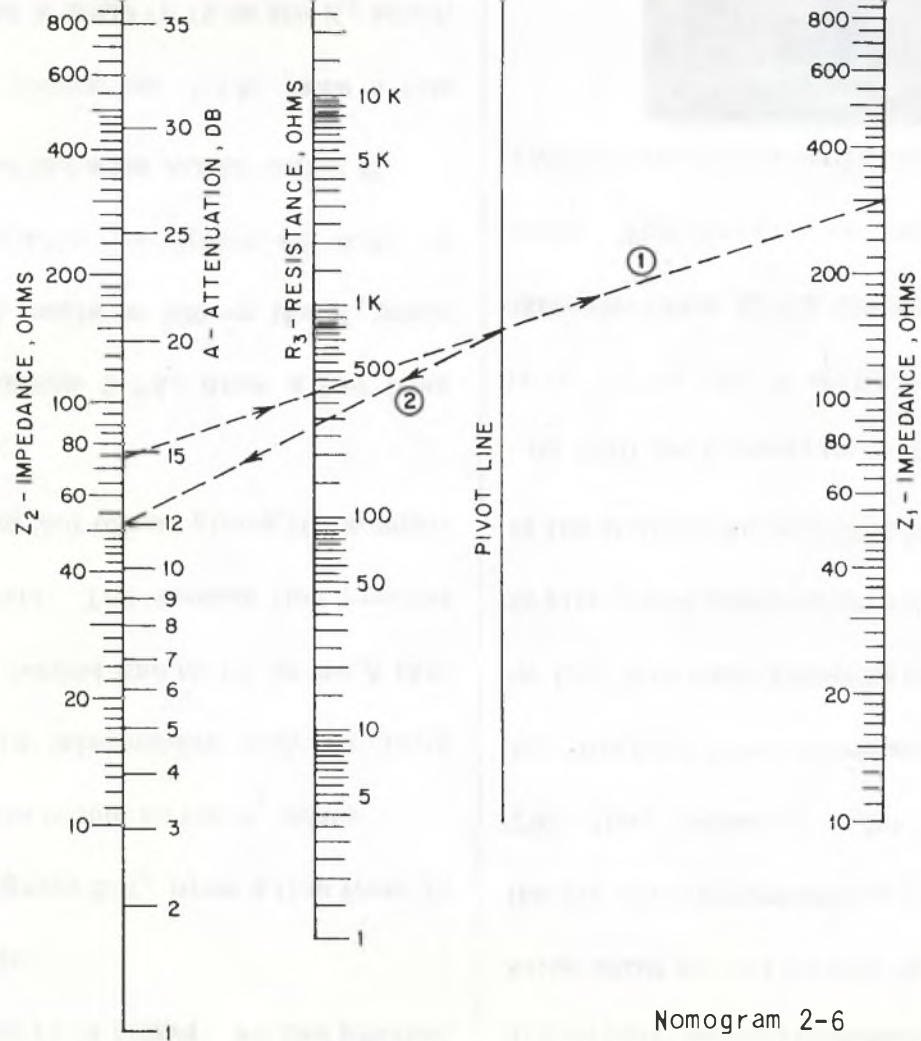

Nomogram 2-6

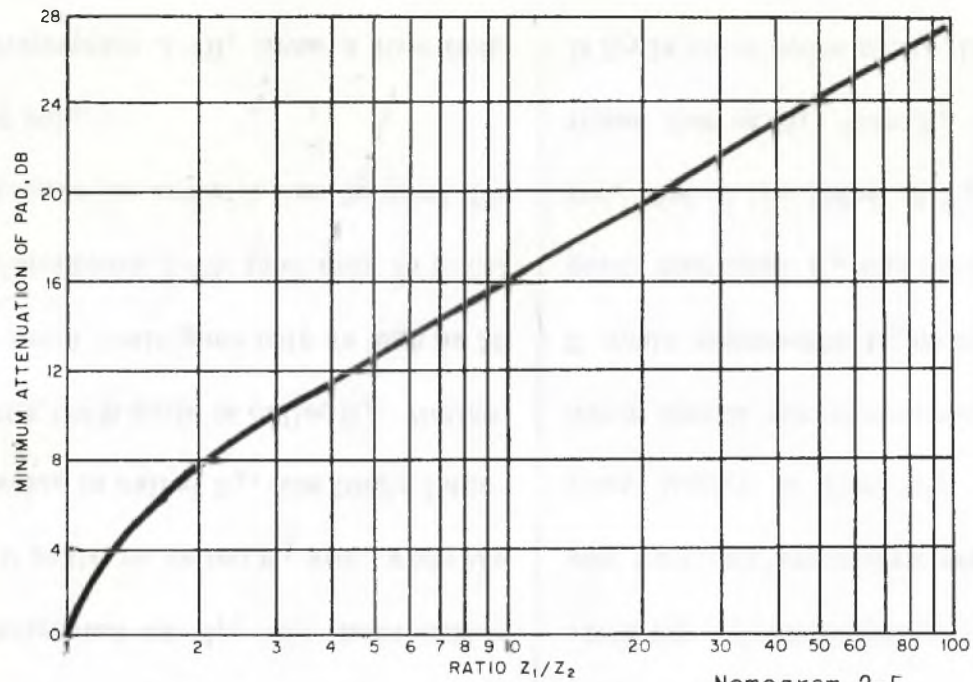

Nomogram 2-5

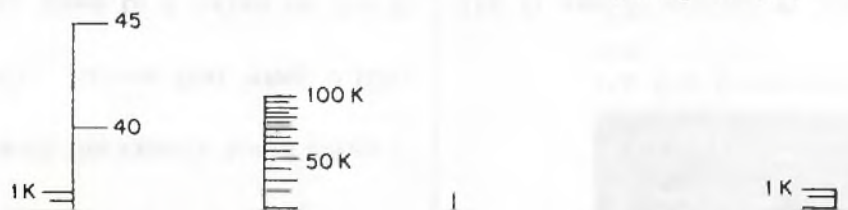

11.6 db. Since 12 is larger, we can proceed with the design.

(1) In Nomogram 2-6, draw a line from 75 on the  $Z_2$  scale to 300 on the  $Z_1$  scale.

(2) From its intersection with the pivot line, draw a second line to 12 on the A (Attenuation) scale. The second line crosses the  $R_3$  scale at 280 ohms, giving the solution to equation 1.

(3) In Nomogram 2-7A, draw a line from 12 on the A scale to 300 on the  $Z_1$  scale. This line crosses the center (B) scale at 270, the value for what can be called  $B_1$ .

(4) Still on Nomogram 2-7A, draw a line from 12 on the A scale to 75 on the  $Z_2$  scale. Its intersection with the center scale gives a value of  $B_2$  of 67. Notice that when a line from the A scale goes to a value on the Z scale, designated as  $Z_1$ , the intersection with the B scale is called  $B_1$  and, when the Z scale value is called  $Z_2$ , the line's intersection with the B scale is called  $B_2$ . Notice, too, that the A scale goes only as high as 30 db. In Nomogram 2-7A (and only in 2-7A) the 30 db mark on scale A can be used for all higher values.

(5) In Nomogram 2-7B, draw a line from

2.8 on the C scale (representing the 280-ohm value found for  $R_3$  in step 2) through 2.7 on the  $B_1$  scale (representing 270 from step 3). This line, extended to the D scale, gives 48. Since the C and B values were multiplied by 100, this value should be multiplied by 100 to give 4,800 ohms as the value for  $R_1$  (which is the solution for equation 2).

(6) Still on Nomogram 2-7B, draw a line from 28 on the D scale (representing the 280-ohm value of  $R_3$ ) through 6.7 on the  $B_2$  scale. This line crosses the C scale at 8.6. This value should be multiplied by 10 (as were



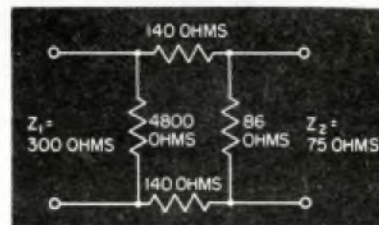


Fig. 2-5. A completely designed pad.

the D and B scales) to give 86 ohms as the value for  $R_2$  (which solves equation 3). We now have all necessary resistance values. They appear in Fig. 2-5. Notice that the outer scales can be reversed. Thus, if the C scale represents  $R_1$  or  $R_2$ , the D scale must represent  $R_3$  and vice versa. Notice, too, that if the value of  $R_3$  is 10 or more times that of  $B_1$ , then  $R_1 = B_1$ . Similarly, if  $R_3$  is 10 or more times  $B_2$ , then  $R_2 = B_2$ !

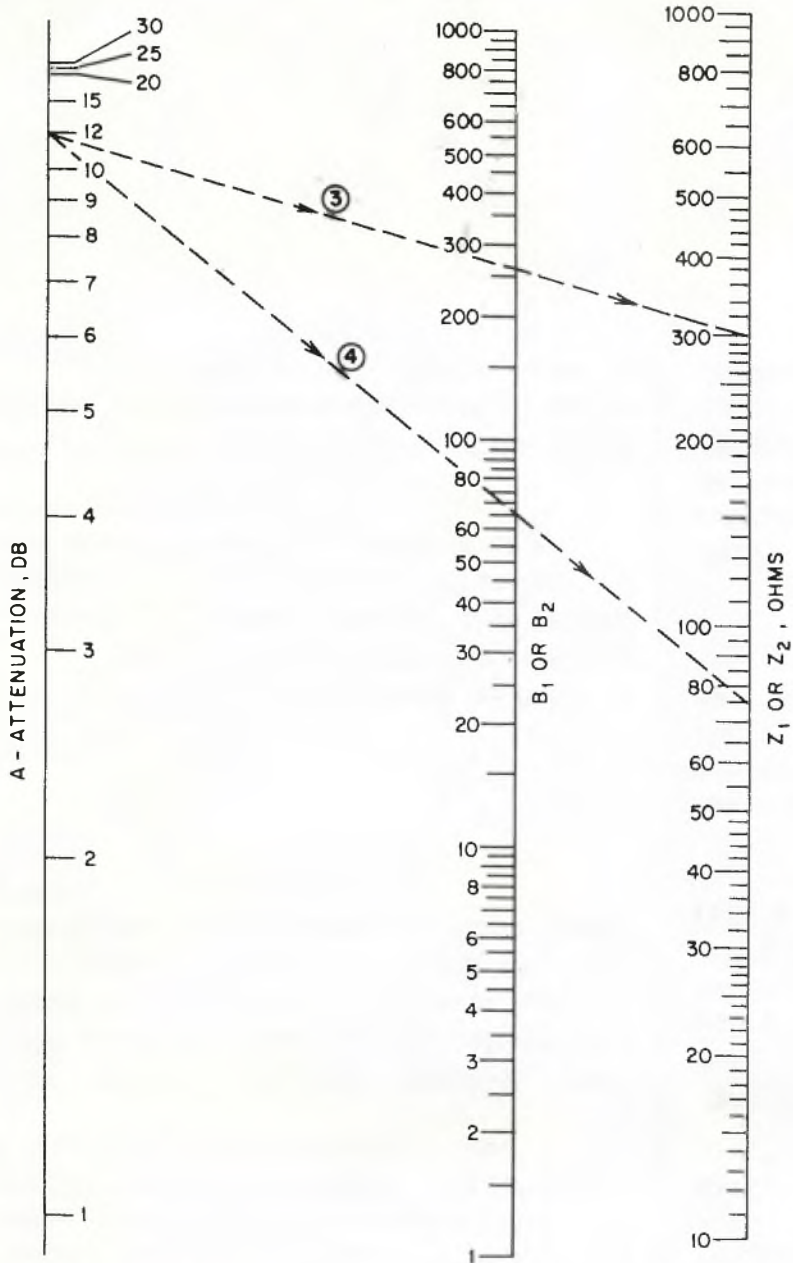

Nomogram 2-7A

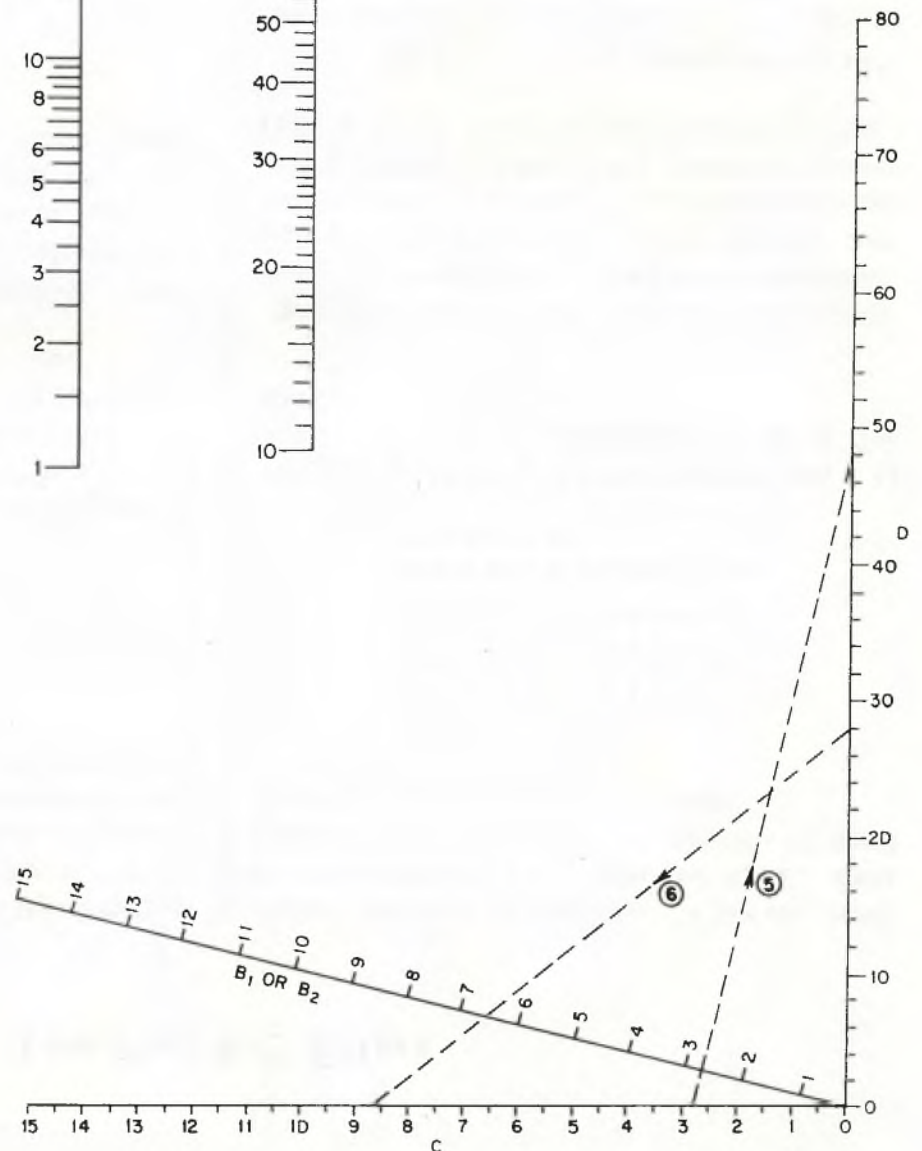

Nomogram 2-7B

## Low-Pass R-C Filters

Here's a nomogram to speed the design of an elementary R-C filter, or to determine the attenuation of a given elementary R-C filter at any frequency. In the R-C network of Fig. 2-6, the ratio of output to input voltage is given by:

$$\frac{E_o}{E_i} = \frac{1}{\sqrt{1 + \omega^2 T^2}} \quad (1)$$

where:  $\omega = 2\pi f$  and  $T = RC$ . An analysis of the equation shows that as  $\omega^2 T^2$  approaches zero, the  $E_o/E_i$  ratio approaches unity, and as  $\omega^2 T^2$  approaches infinity, the output-to-input voltage ratio approaches zero.

For practical purposes, however, when  $\omega^2 T^2$  is much less than one, the voltage ratio equals one, and when  $\omega^2 T^2$  is at least 10, the voltage ratio becomes equal to  $1/\omega T$ . This is the approximation on which Nomogram 2-8 is based:

$$\frac{E_o}{E_i} = \frac{1}{\omega T} \quad (2)$$

It's necessary to bear in mind the fact that the nomogram is accurate only for values of  $\omega T$  equal to or greater than 10. It is further assumed that the output load impedance is high compared to the impedance of the filter's shunt capacitor.

Values other than those given on the scales for R, C, and f can be used by multiplying the appropriate scale by  $10^n$ , where n can be

either negative or positive. When any scale is multiplied by  $10^n$ , then the  $E_o/E_i$  ratio must be multiplied by  $10^{-n}$ , and  $20n$  db must be added to the adjacent db scale.

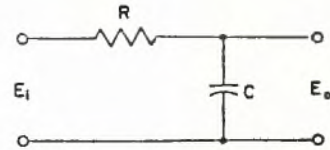



Fig. 2-6. The elementary low-pass RC filter.

Example: If R has a value of 800K and C is 0.2  $\mu$ f, what is the attenuation in db at 300 Hertz?

Solution: Draw a line from 8K on the R scale to 0.2 on the C scale. Through its intersection with the pivot line, draw another line from 300 on the f scale to the attenuation and voltage-ratio scale. This gives a voltage ratio of 0.33, which is equivalent to 9.7 db.

Since the R scale was multiplied by  $10^2$ , the ratio must be multiplied by  $10^{-2}$ , giving a ratio of 0.0033. To the db reading add 20 times 2, making a total attenuation of 49.7 db. This is verified by checking the db value adjacent to 0.0033 on the ratio scale.

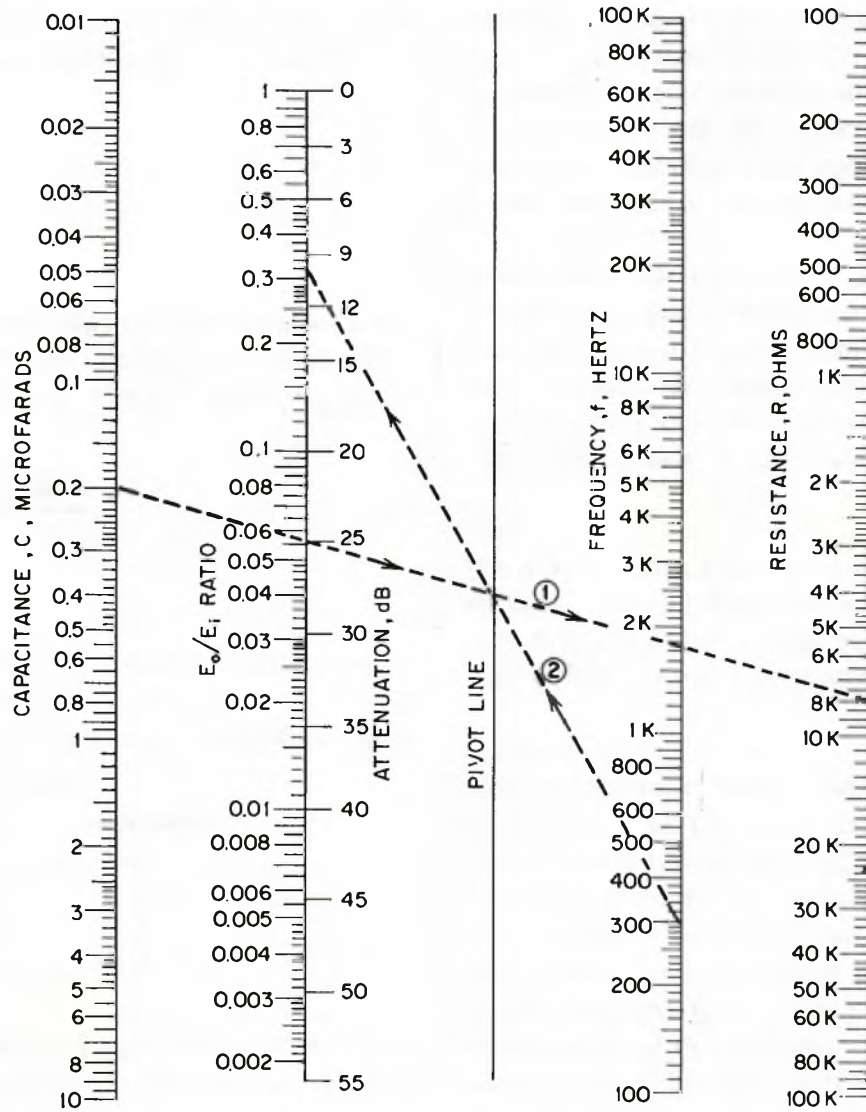The nomogram can be used in reverse by rotating a straight-edge about the pivot point (on the pivot line) of a line drawn from the frequency to the attenuation or voltage-ratio scale. The rotating line gives a selection of suitable R and C combinations.





## Low-Pass L-R Filters

Here's a nomogram to help speed the design of an elementary L-R filter or determine

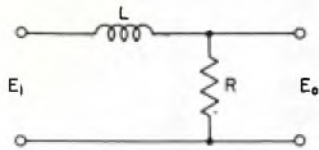


Fig. 2-7. The elementary L-R filter.

the attenuation of a given elementary L-R filter at any frequency. In the L-R network of Fig. 2-7, the ratio of output to input voltage is given by:

$$\frac{E_o}{E_i} = \frac{1}{\sqrt{1 + \omega^2 T^2}} \quad (1)$$

where:  $\omega = 2\pi f$  and  $T = L/R$ . When  $\omega^2 T^2$  is greater than 10, the equation is closely approximated by  $1/\omega T$  which gives us to a close approximation:

$$\frac{E_o}{E_i} = \frac{R}{\omega L} \quad (2)$$


The accuracy of Nomogram 2-9 depends on  $\omega T$  having values of 10 or greater and on the

output load impedance being high compared to the shunt R of the filter. Values other than those given for R, L, and f on the nomogram can be used by multiplying the scale value by  $10^n$ , where n can be positive or negative. When the R scale is multiplied by  $10^n$  the voltage ratio must be multiplied by  $10^n$ . When either the L or f scale is multiplied by  $10^n$ , then the voltage ratio scale must be multiplied by  $10^{-n}$ .

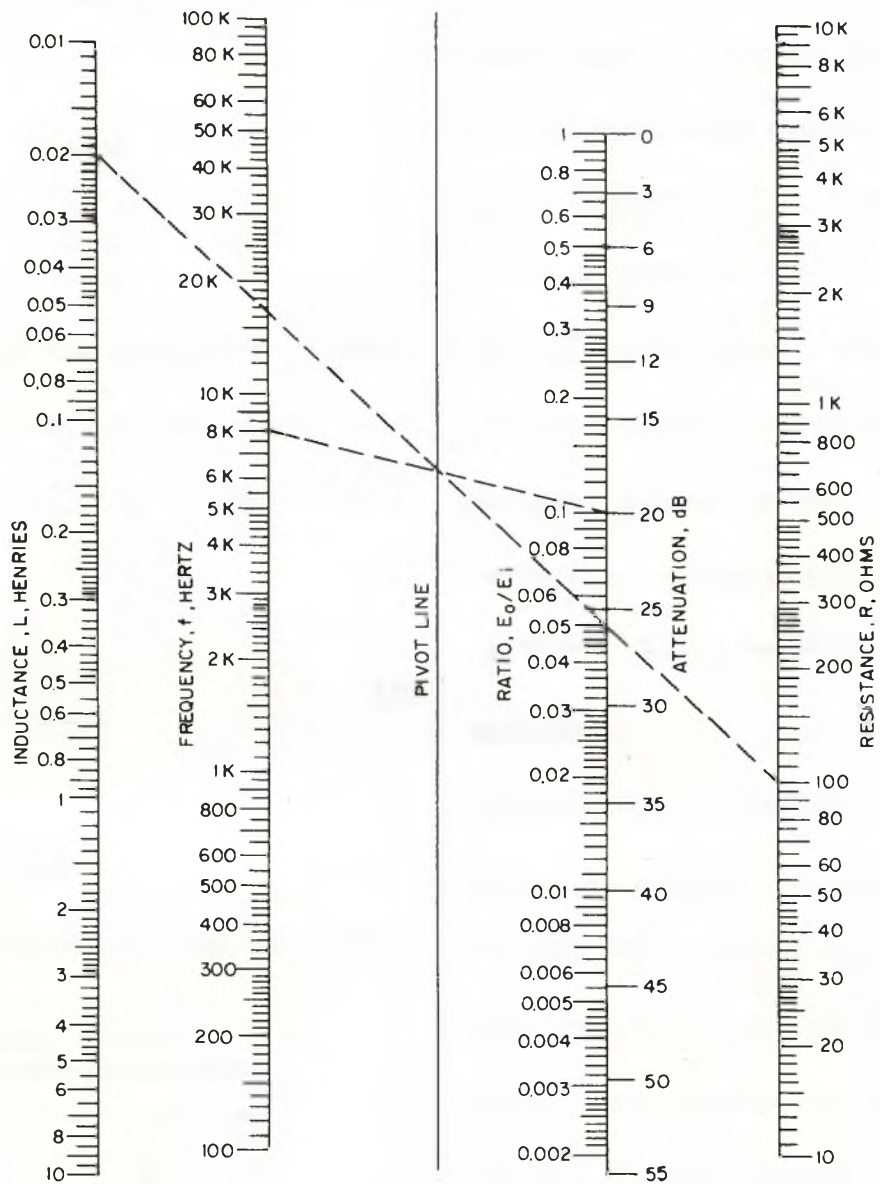**Example:** Find the attenuation at 8 kHz of an elementary low-pass filter whose series element has an inductance of 0.02 henries and whose shunt element is a 100-ohm resistor.

**Solution:** Draw a line from 0.02 on the L scale to 100 on the R scale. Draw another line through its intersection with the pivot line from 8,000 on the f scale to the attenuation scale. The attenuation is 20 db and the output-to-input ratio is 0.1.

The nomogram can be used in reverse by rotating a straight-edge about the pivot point (on the pivot line) of a line drawn from the frequency to the attenuation or voltage-ratio scale. The rotating line gives a selection of suitable R and L combinations.



## Low-Pass L-C Filters

Nomogram 2-10 helps one check the attenuation characteristics of the elementary low-

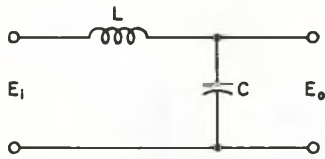


Fig. 2-8. The elementary low-pass L-C filter.

pass L-C filter in Fig. 2-8. The basic equation for this filter is:

$$\frac{E_o}{E_i} = \frac{1}{\frac{f^2}{f_o^2} - 1} \quad (1)$$

where:  $f_o = 1/(2\pi\sqrt{LC})$ . For simplification of the voltage-ratio equation, the constant term in the denominator can be dropped, making the equation:

$$E_o/E_i = f_o^2/f^2 \quad (2)$$


This simplified equation makes the nomogram quite accurate for  $f$  values at least five times greater than  $f_o$ . It must be assumed that the output load impedance is high com-

pared to the impedance of the filter's shunt capacitor.

For a given filter, the nomogram gives the solution in terms of the  $E_o/E_i$  voltage ratio as well as the equivalent attenuation in db. Other values of  $L$ ,  $C$ , and  $f$  may be used by multiplying all scales by  $10^n$ , where  $n$  can be positive or negative. When this is done, the voltage-ratio and attenuation scales remain unchanged.

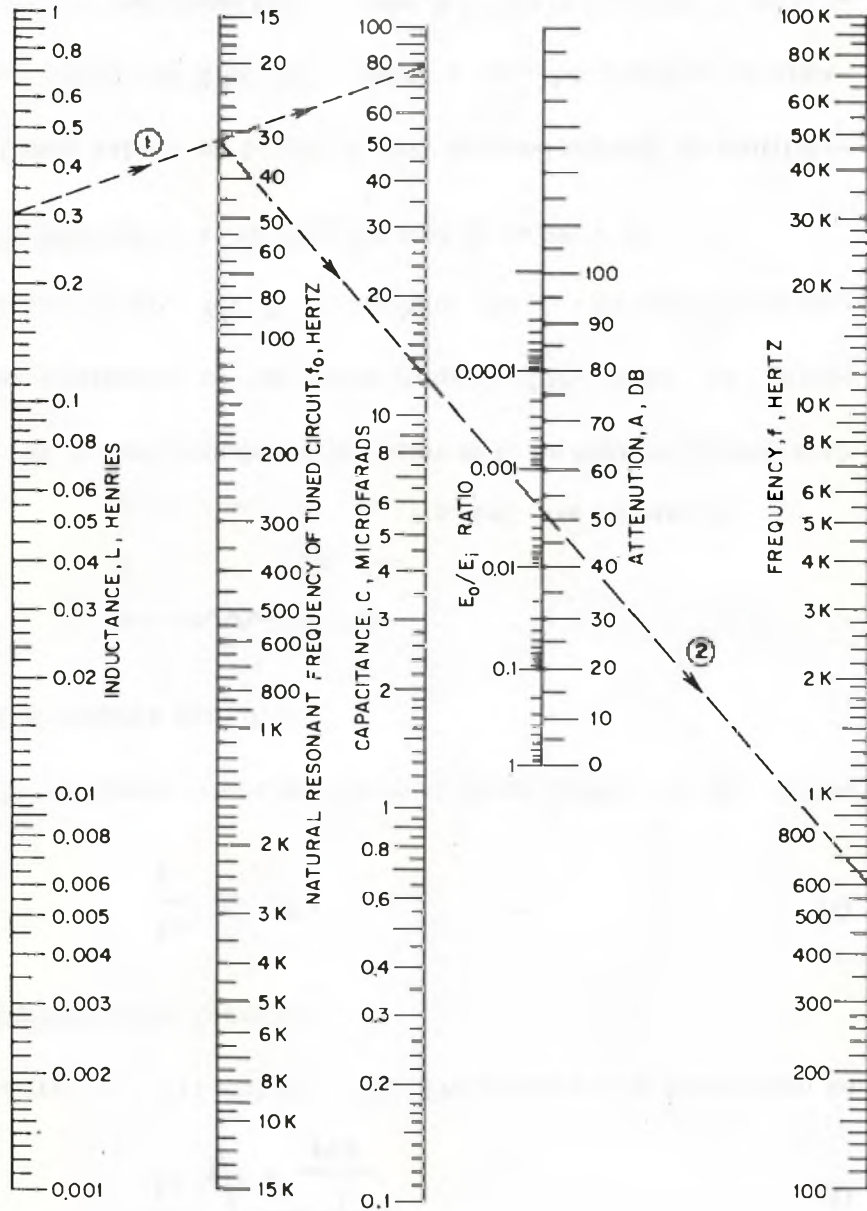Example: For a low-pass filter having an inductor of 0.3 henries and an 80  $\mu$ f capacitor, find the output-to-input voltage ratio and the attenuation in db at 600 Hertz.

Solution: Draw a line between the  $L$  and  $C$  values on Nomogram 2-10. From its intersection with the  $f_o$  scale (which, incidentally, gives the natural resonant frequency of a series-tuned L-C circuit) draw another line to 600 Hz on the  $f$  scale. This line crosses the voltage-ratio and attenuation scale at a ratio of 0.0028, equivalent to an attenuation of 51 db.



## High-Pass R-L Filters

In the R-L network shown in Fig. 2-9, the ratio of output to input voltages is:

$$\frac{E_o}{E_i} = \frac{1}{\sqrt{1 + \frac{1}{\omega^2 T^2}}} \quad (1)$$

where:  $\omega = 2\pi f$  and  $T = L/R$ . The nomogram is based upon an approximation formula:

$$\frac{E_o}{E_i} \approx \omega T \quad (2)$$

This approximation formula is accurate within 10% for values of T smaller than 0.5.


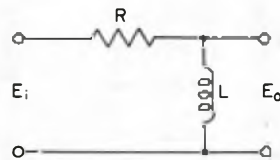


Fig. 2-9. The R-L network.

The output impedance is assumed to be high compared with the impedance of the shunt element of the filter. In the example shown, for  $R = 550$  ohms and  $L = 80$  microhenries, the attenuation at 60 kHz is found to be 25.9 db.

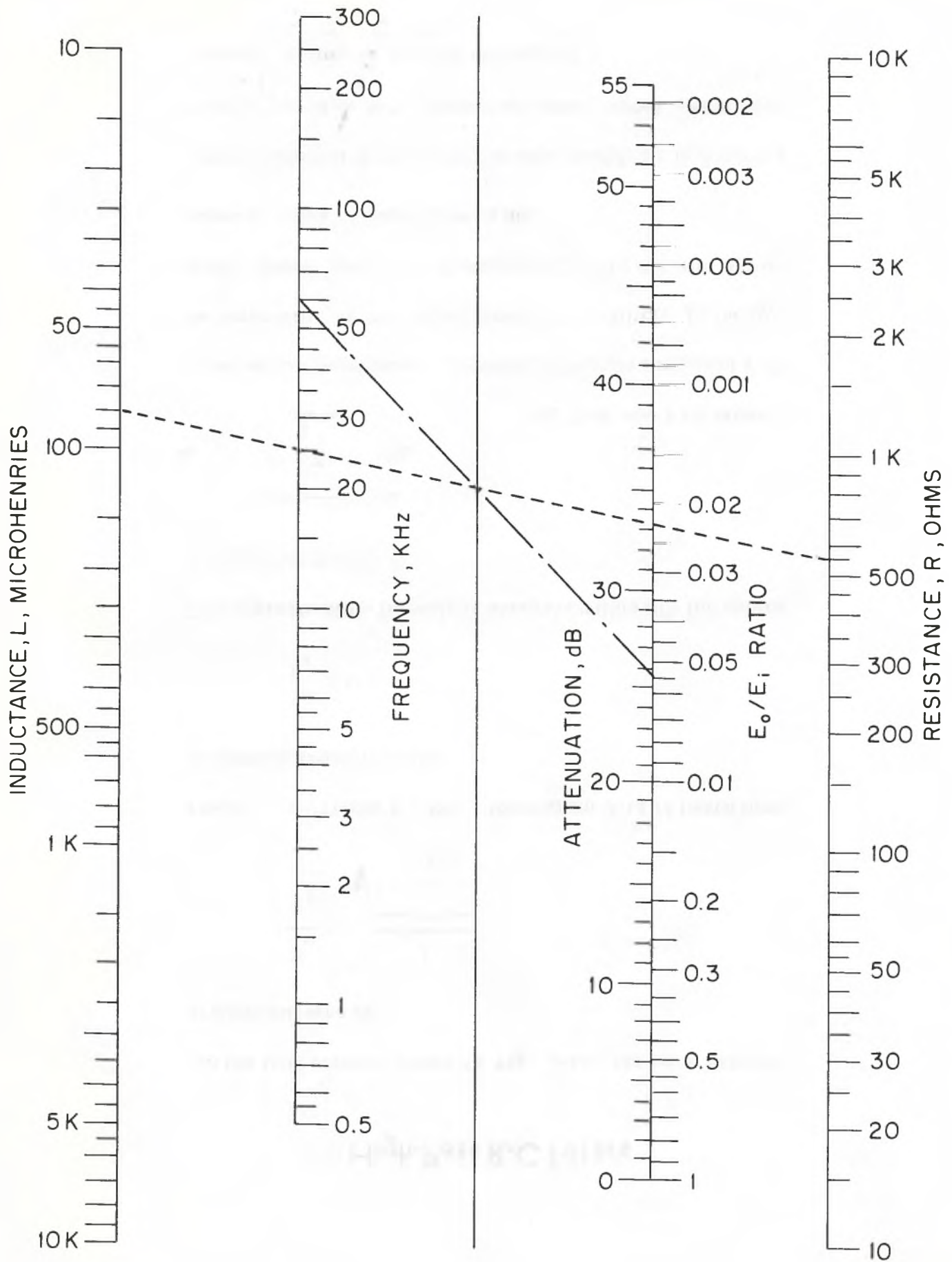Other values of L and R may be used merely by multiplying both L and R by  $10^n$ , where n may be positive or negative. In the nomogram, scale A is the inductance in microhenries, scale B is the frequency in Hertz, scale C is the attenuation in db, scale D is the ratio  $E_o/E_i$ , and scale E is the series resistance in ohms.



## High-Pass R-C Filters

In the R-C network shown in Fig. 2-10, the ratio of output to input voltages is:

$$\frac{E_o}{E_i} = \frac{1}{\sqrt{1 + \frac{1}{\omega^2 T^2}}}$$

where:  $\omega = 2\pi f$  and  $T = RC$ . Nomogram 2-12 is based upon an approximation formula:

$$\frac{E_o}{E_i} \approx \omega T$$

This approximation formula is accurate within 10% for values of  $T$  smaller than 0.5.

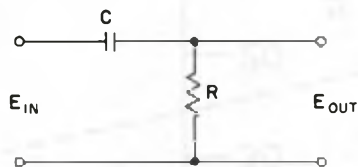


Fig. 2-10. Simple R-C network.

The output impedance is assumed to be high compared with the impedance of the shunt element of the filter. In the example shown, for  $f = 1,020$  ohms and  $C = .015 \mu f$ , the attenuation at 1 kHz is found to be 20 db.

Other values of  $R$  and  $C$  may be used merely by multiplying  $C$  by  $10^n$  and  $R$  by  $10^{-n}$ , where all other scales remain unchanged. ( $n$  may be positive or negative.)

R IN OHMS

10K

5K

1K

500

f IN Hz

100

500

1K

ATT. IN db  $E_o/E_i$

3

6

9

12

15

20

25

30

.7

.5

.1

.05

C IN  $\mu$ f

.1

.05

.01

.005


①

②



②

①



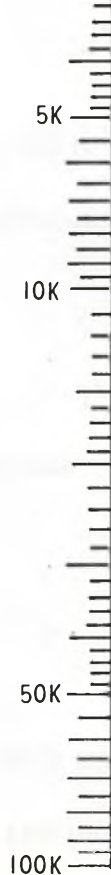

PIVOT LINE

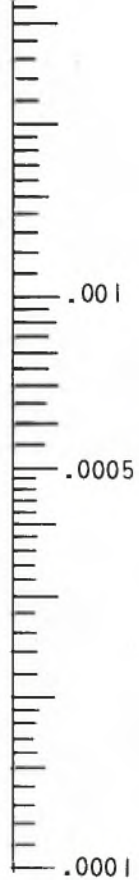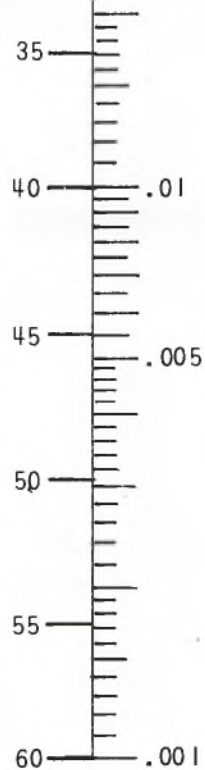

# High-Pass L-C Filters

For the L-C network shown in Fig. 2-11, the ratio of output to input voltages is:

$$\frac{E_o}{E_i} = \frac{1}{\omega^2 LC} = \frac{1}{\frac{f_o^2}{f}}$$

where:  $\omega = 2\pi f$

$f_o$  = resonant frequency

$f$  = frequency

Nomogram 2-13 is based upon an approximation of the above formula:

$$E_o/E_i \approx f^2/f_o^2$$

This approximation formula is accurate within 10% for a ratio of  $f_o/f$  greater than 5. The output impedance is assumed to be high compared with the impedance of the shunt element of the filter. In the example shown, for  $L = .2$  h and  $C = .015$   $\mu$ f, the attenuation at 1 kHz is 20 db.


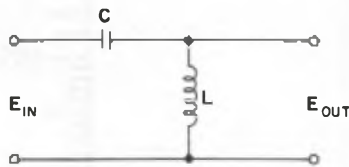
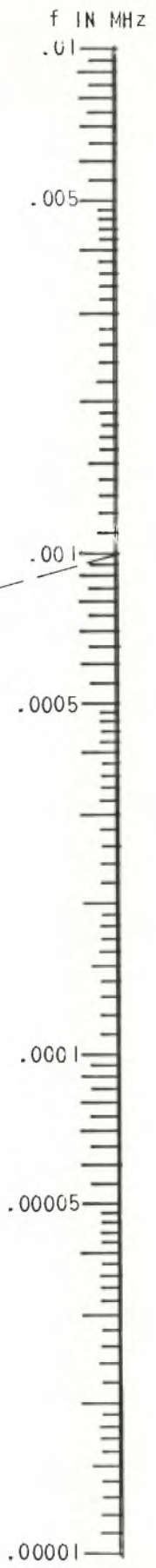
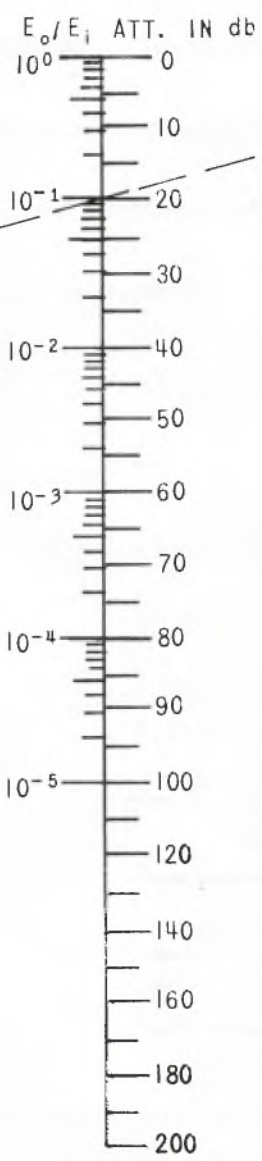


Fig. 2-11. The L-C network.

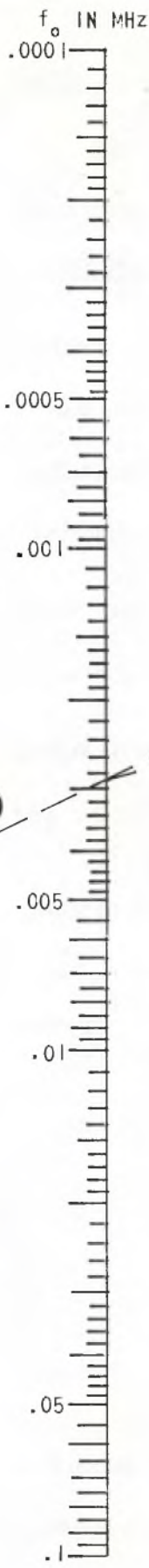Other values for  $L$  and  $C$  may be used if  $L$  is multiplied by  $10^n$  and  $C$  is multiplied by  $10^{-n}$ , where all other scales remain unchanged. ( $n$  may be positive or negative.)



①

②

## Low-Pass Filters: Constant-K Types

The low-pass filter has a passband from DC to the cutoff frequency,  $f_c$ . Beyond this frequency, the signal is attenuated excessively as shown by the graph in Fig. 2-12.

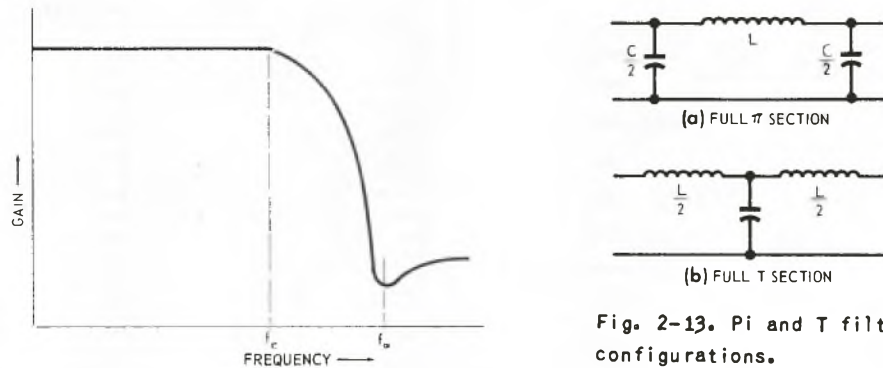


Fig. 2-12. Graph showing attenuation of constant-k low-pass filters.

The Pi and T configurations for the constant-k filters are shown in Fig. 2-13. For these circuits:


$$L = R/\pi f_c$$

and  $C = 1/\pi R f_c$

where:  $R$  is the nominal terminating resistance.

Nomogram 2-14 provides a graphical solution to these equations. The values of  $L$  and  $C$  can be determined by aligning a straight-edge from  $f_c$  on the left-hand scale to  $R(L)$  or  $R(C)$ , respectively, on the right-hand scale. The values of  $L$  and  $C$  are found where the straight-edge intersects the center scales.

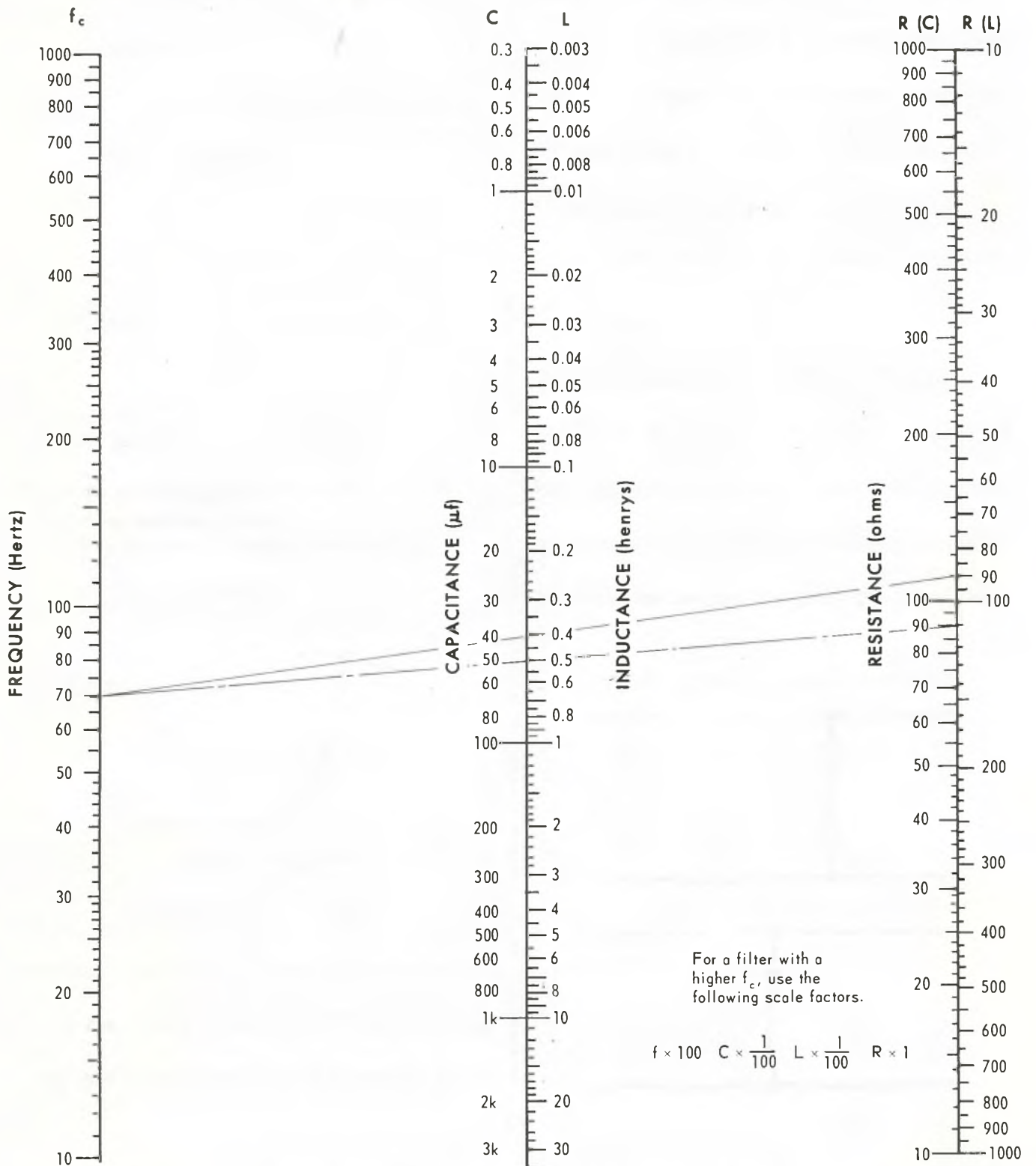Example: Design a low-pass constant-k filter with a cutoff of 7 kHz and terminating in 90 ohms. In Nomogram 2-14,  $f_c = 7$  kHz,  $R = 90$  ohms, values of  $L$  and  $C$  are:  $L = 4.1$  mh and  $C = 0.51$   $\mu$ f.



## Low-Pass Filters: M-Derived Types

The low-pass filter has a passband from DC to the cutoff frequency  $f_c$ . Beyond this frequency the signal is attenuated considerably to  $f_\infty$  as shown by the graph in Fig. 2-14. The T-section configuration used in

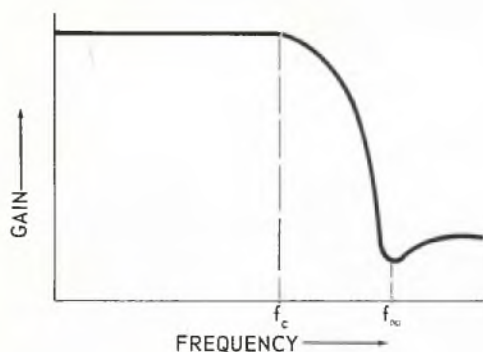


Fig. 2-14. Graph showing attenuation of m-derived low-pass filter.

series m-derived filters is shown in Fig. 2-15. The design formulas for these circuits are:

$$L_A = mL$$

$$L_B = (1-m^2)L/4m$$

$$C_B = mC$$

$$\text{and } m = \sqrt{1 - (f_c/f_\infty)^2}$$

where:  $f_\infty$  is the frequency of maximum attenuation.

The correct value of  $m$  can be found by using Nomogram 2-15. No units are given for  $f_c$  and  $f_\infty$  because any frequency can be used,


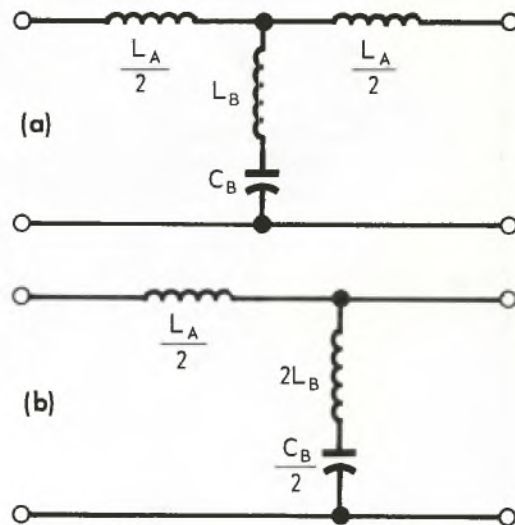


Fig. 2-15. T-section filter configuration.

provided that both scales use the same units. The value of  $m$  is found by aligning a straight-edge from the value of  $f_\infty$  on its scale through the value of  $f_c$  on its scale. The value of  $m$  is found where the straight-edge intersects the  $m$  scale.

The values of  $L_A$ ,  $L_B$ , and  $C_B$  are found by using Nomogram 2-16. Notice that  $L_A$  and  $C_B$  are found by using the left-hand scales and  $L_B$  is found by using the right-hand scales. By extending a straight-edge from either  $L$  or  $C$  to the value of  $m$  (as found in Nomogram 2-15) on their appropriate scales.

(Continued on next page)

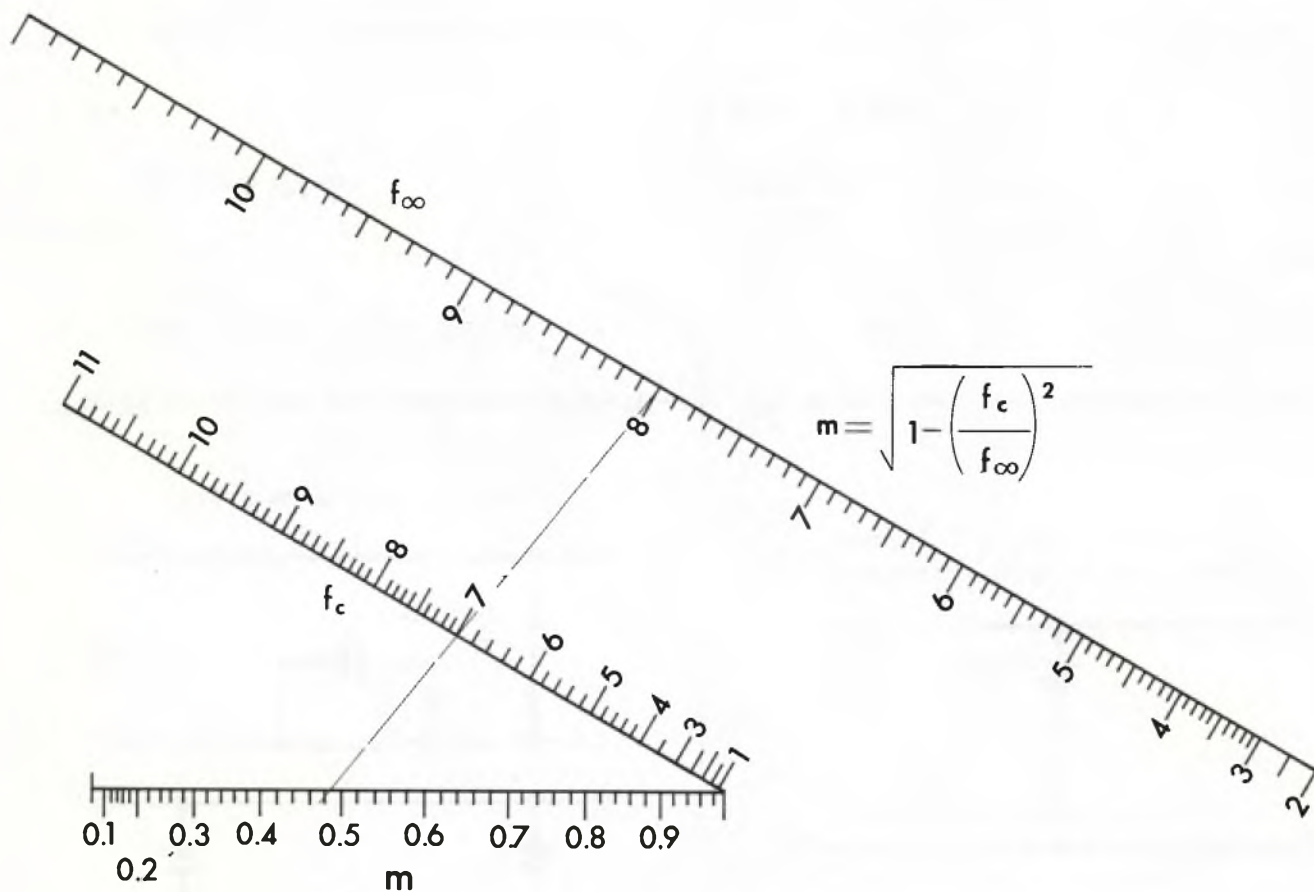

Nomogram 2-15

The values of  $L_A$ ,  $L_B$ , and  $C_B$  are found where this line intersects the center scale. Any units may be used for  $C$  or  $L$ , provided that the same units are used for  $C_B$  or  $L_A$  and  $L_B$ , respectively.

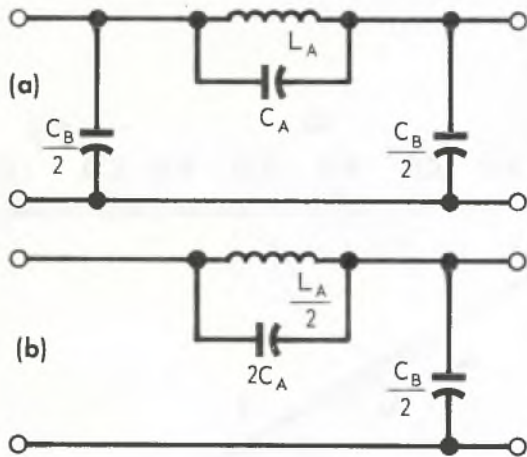


Fig. 2-16. Pi section filter.

The Pi section for the shunt  $m$ -derived filter is shown in Fig. 2-16. For this circuit:

$$L_A = mL$$

$$C_A = (1-m^2) C / 4m$$

$$C_B = mC$$

The values of these components are found by using Nomograms 2-15 and 2-16, just as with

the series  $m$ -derived filter.

Example: Design a series  $m$ -derived low-pass filter with a cutoff frequency of 7 kHz, a maximum attenuation at 8 kHz, and terminating in 90 ohms. Using Nomogram 2-15,  $m$  is determined to be 0.485.


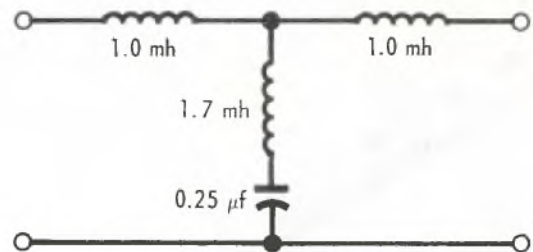


Fig. 2-17. Filters for the example in text.

On Nomogram 2-14 (constant- $k$ ), using  $f_c = 7$  kHz and  $R = 90$  on both  $R(C)$  and  $R(L)$  scales, the values of  $L$  and  $C$  are determined to be:  $L = 4.1$  mh,  $C = 0.51$   $\mu$ f. Therefore, on Nomogram 2-16,  $L_A = 2$  mh,  $C_B = 0.25$   $\mu$ f and  $L_B = 1.7$  mh. The final filter is as shown in Fig. 2-17.

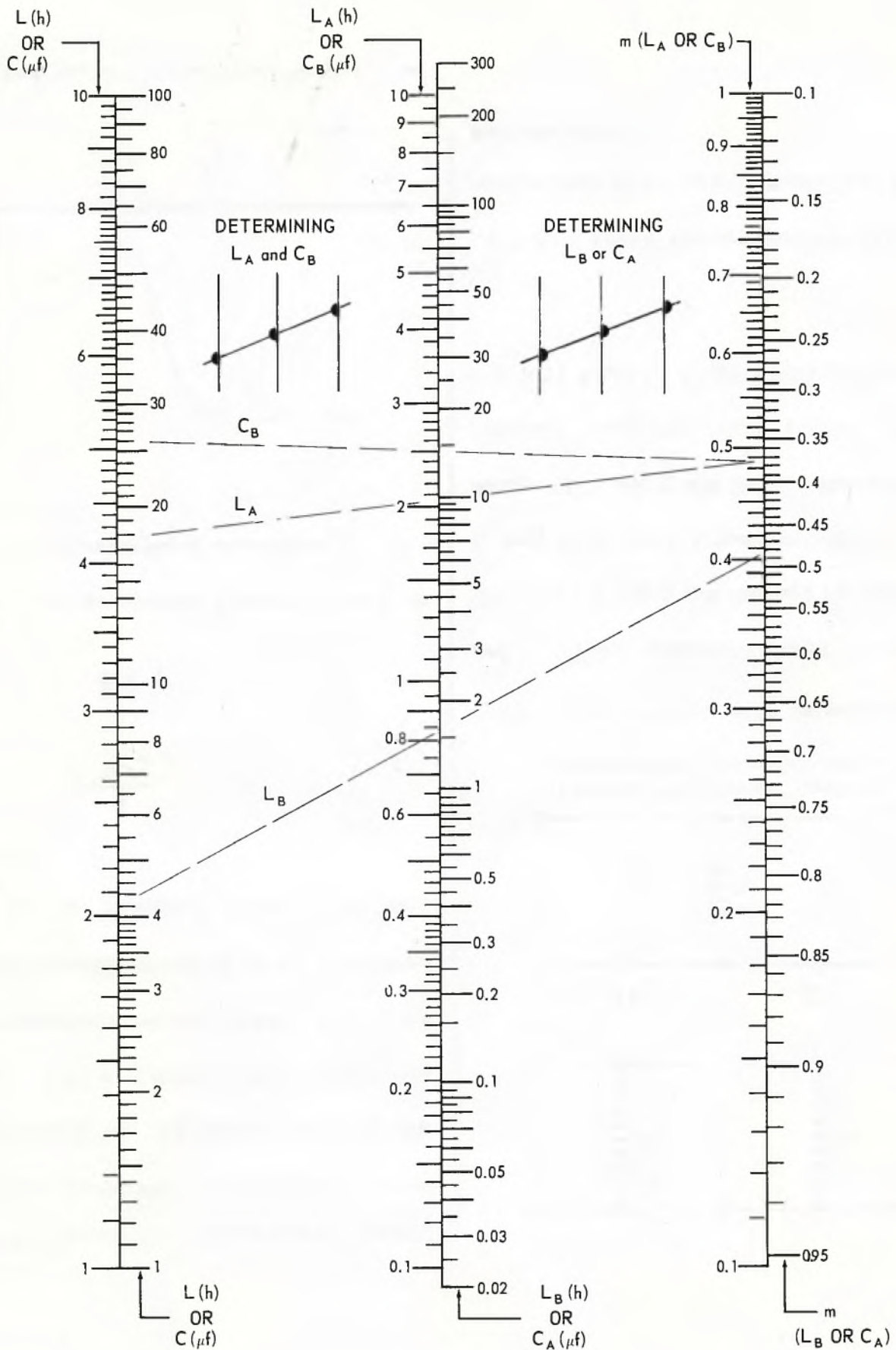



Nomogram 2-16

# High-Pass Filters

The high-pass filter attenuates all signals in the frequency range from DC up to the cut-off frequency  $f_c$ . All signals above  $f_c$  are passed. Fig. 2-18 shows a typical high-pass filter frequency response curve. Fig. 2-19 shows the configurations of Pi and T sections used in the constant-k filters. For these circuits:

$$L = \frac{R}{4\pi f_c}$$

$$C = \frac{1}{4\pi f_c R}$$

where:  $f_c$  is the cut-off frequency and R is the nominal terminating resistance.

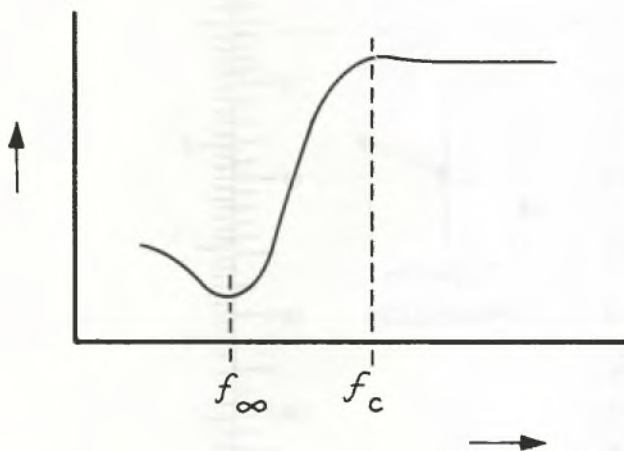


Fig. 2-18. Typical high-pass filter response curve.

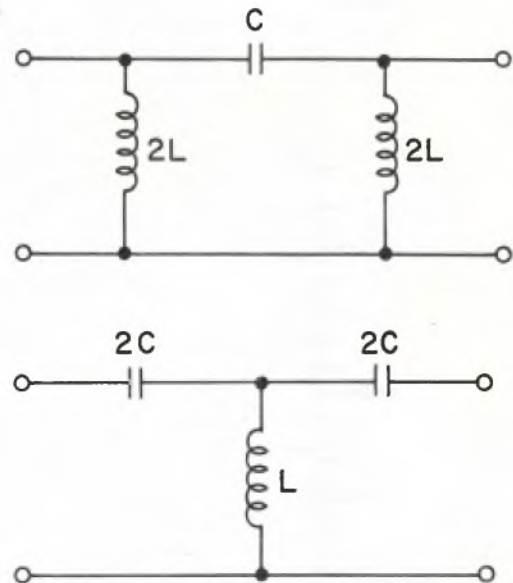





Fig. 2-19. Pi (top) and T (bottom) configurations, constant-k filters.

Nomogram 2-17 is used in the solution of L and C. Their values are found by merely drawing a straight line through the values of  $f_c$  and R on their respective scales. The values of L and C are found where the lines intersect their respective scales. NOTE: Use R(C) scale for C and R(L) scale for L.

Fig 2-20 shows the configuration of the T section used in the series m-derived filter.

For this circuit:

(Continued on next page)

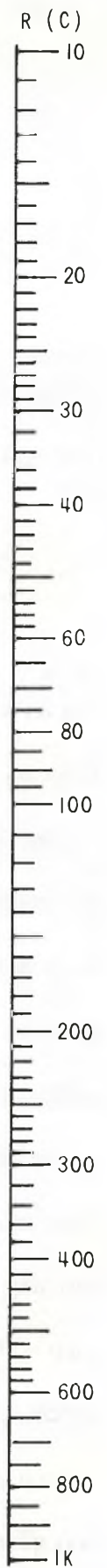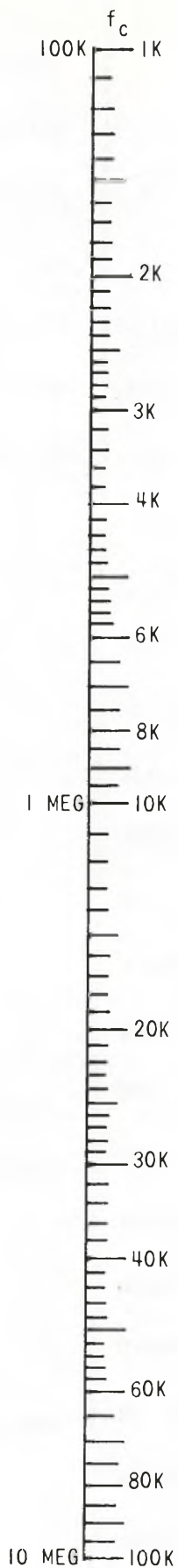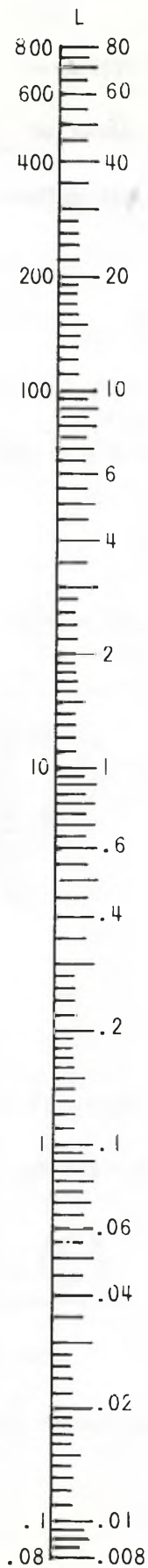

Nomogram 2-17

$$C_A = \frac{C}{m}$$

$$L_B = \frac{L}{m}$$

$$C_B = \frac{4m}{1-m^2} C$$

Where: L and C are the values found in the constant-k nomogram, and:

$$m = \sqrt{1 - \left(\frac{f_\infty}{f_c}\right)^2}$$

In this equation  $f_c$  is the cut-off frequency and  $f_\infty$  is the frequency of maximum attenuation.

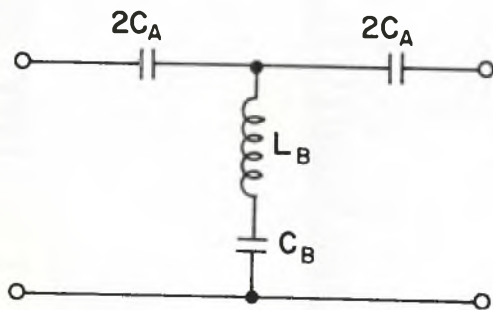


Fig. 2-20. T configuration, series m-derived filter.

Nomogram 2-18 is used to find the value of m. No units are given for  $f_c$  or  $f_\infty$ . Any unit of frequency may be used, provided that the same units are used on both scales. To solve for m, draw a straight line through the values of  $f_c$  and  $f_\infty$  on their respective scales. m is found where this line intersects its scale.

The values of  $L_B$  and  $C_A$  are found in Nomogram 2-19 by drawing a straight line from the value of m on the  $m_1$  scale through the values of L and C on the B scale. The points of intersection of these lines with the A scale determine the values of  $L_B$  and  $C_A$ . Any units may be used for C, provided that the same unit is used for  $C_A$ . Similarly, any unit may be used for L, provided that the same unit is used for  $L_D$ . By extending a straight line, in Nomogram 2-19, from the value of m on the  $m_2$  scale through the value of C on the C scale,  $C_B$  can be found at the point of intersection of this line with the D scale. Values other than those shown may be used by multiplying both the C and D scales by the same factor.

Fig. 2-21 shows the configuration of the Pi section used in the shunt m-derived filter.


For this circuit:

$$L_A = \frac{4mL}{(1-m^2)}$$

$$L_B = \frac{L}{m}$$

$$C_A = \frac{C}{m}$$

(Continued on next page)

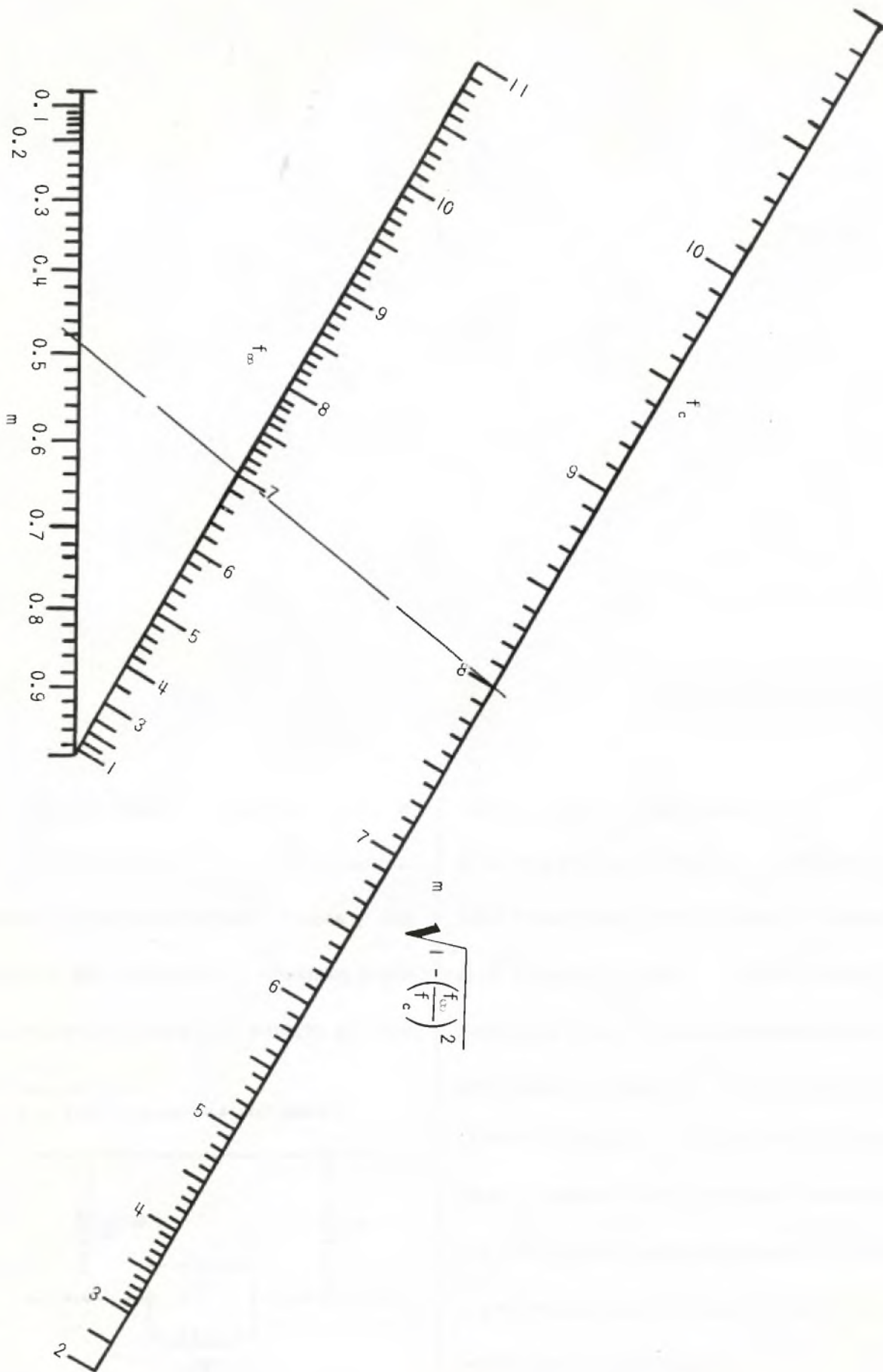

Nomogram 2-18


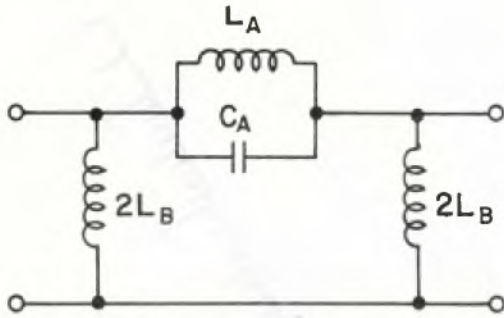


Fig. 2-21. Pi configuration, shunt m-derived filter.

These values are found in a similar manner to that used for the series m-derived filter by using the same nomograms, where  $L$  and  $C$  are the values found in the constant- $k$  nomogram and  $m$  is found as described for the

series m-derived filter.

The solution of  $L_B$  and  $C_A$  was described for the series m-derived filter.  $L_A$  is found in Nomogram 2-19 by drawing a straight line from the value of  $m$  on the  $m_2$  scale through the value of  $L$  on the  $C$  scale. Read off the value of  $L_A$  at the point of intersection of this line with the  $D$  scale. Again, other values than those shown on the scales may be used, provided that the respective equation scales are multiplied by the same factor

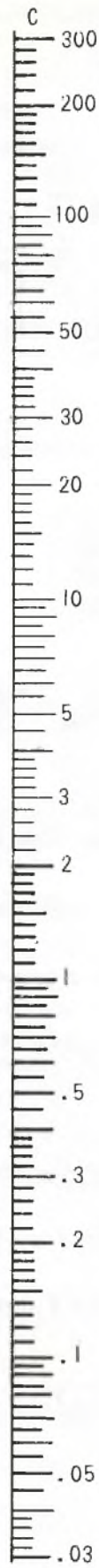

Nomogram 2-19

# Bandpass Filters

The band-pass filter has the characteristic of transmitting a specific band of frequencies and attenuating all frequencies above and below it. Fig. 2-22 shows a typical bandpass frequency response curve.

The Pi and T configurations for the constant-k filters are shown in Fig. 2-23. For these circuits:

$$L_1 = \frac{R}{\pi (f_2 - f_1)}$$

$$C_1 = \frac{(f_2 - f_1)}{4\pi f_1 f_2 R}$$

$$L_2 = \frac{(f_2 - f_1) R}{4\pi f_1 f_2}$$

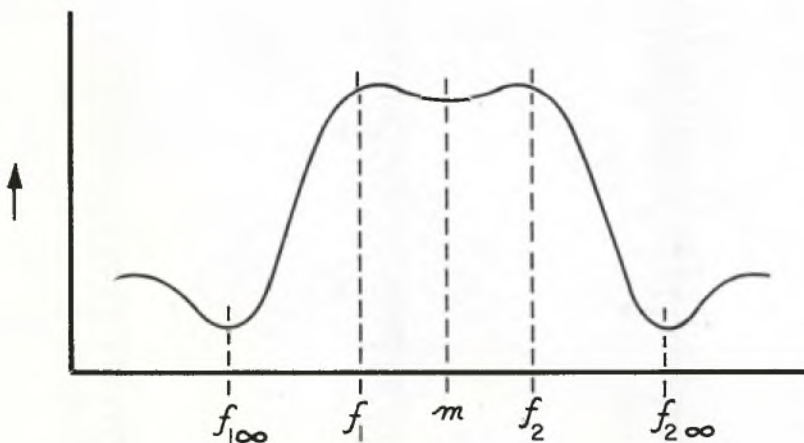


Fig. 2-22. Typical bandpass response curve.

$$C_2 = \frac{1}{\pi (f_2 - f_1) R}$$

The equations for  $L_1$  and  $C_2$  are solved in Nomogram 2-14 in the low-pass filter section, with the values of  $(f_2 - f_1)$  substituted for the  $f_c$  scale.

$L_2$  and  $C_1$  are found in Nomogram 2-20.

These equations are solved as follows:

1. Draw a straight line through the values of  $f_1$  and  $f_2$  on their respective scales to the X scale.

*(Continued on next page)*



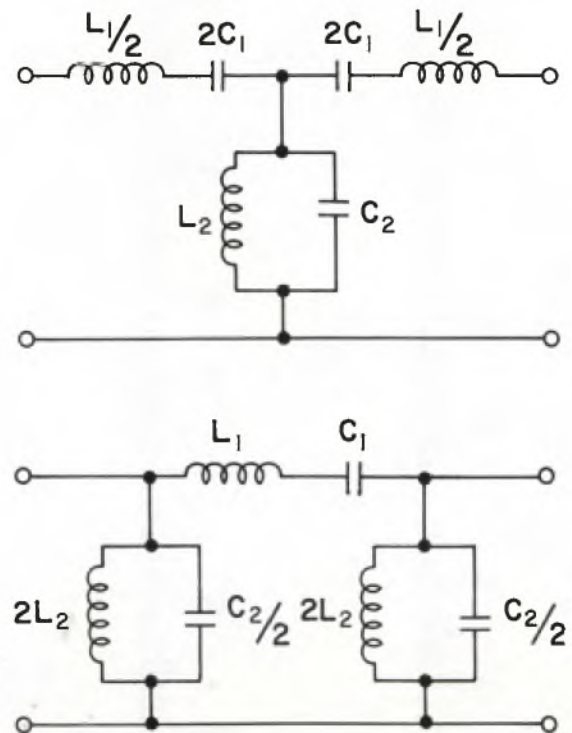


Fig. 2-23. T (top) and Pi (bottom) configurations, bandpass constant-k filter.

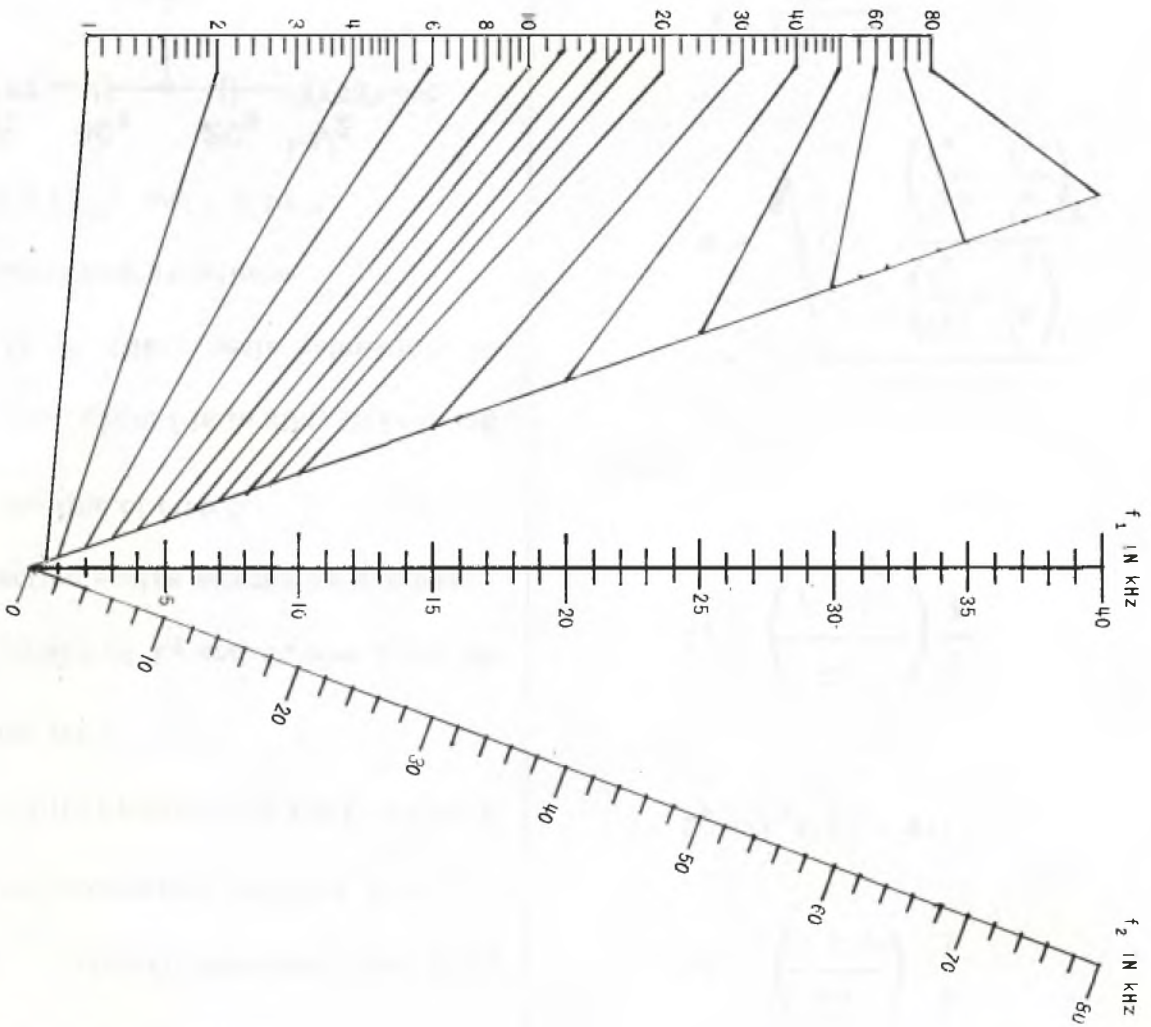

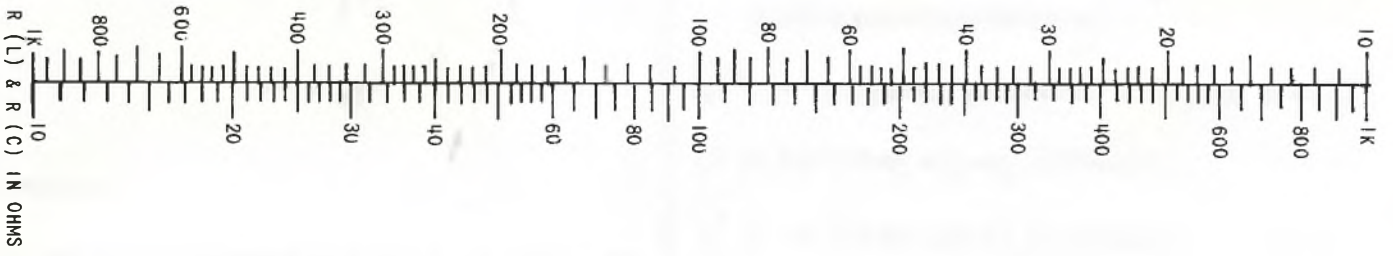

Nomogram 2-20

2. Transpose this value to the  $X_{10g}$  scale as indicated in the nomogram.

3. Draw a straight line from the  $X_{10g}$  scale to the appropriate value of R on its scale. Use R(L) when solving for L and R(C) when solving for C.

4. The values of  $L_2$  and  $C_1$  are found on their respective scales where they are intersected by the line of step 3.

For this nomogram  $f$  is in kHz,  $L$  is in mh and  $C$  is in  $\mu f$ . Other scale values may be used by multiplying as follows:

$f \times 10^n$ ,  $L \times 10^{-n}$ , and  $C \times 10^{-n}$ .

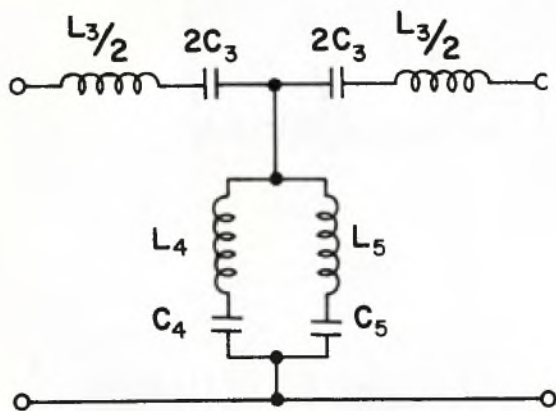


Fig. 2-24. T configuration, series m-derived filter.

The T configuration for the series m-derived filter is shown in Fig. 2-24. For this circuit:

$$L_3 = mL_1$$

$$C_3 = \frac{C_1}{m}$$

$$L_4 = L_1 A \left( 1 + \frac{1}{N^2} \right)$$

$$C_4 = \left( \frac{C_1}{1 + N^2} \right) \frac{1}{A}$$

$$L_5 = L_1 A (1 + N^2)$$

$$C_5 = \left( \frac{C_1}{1 + \frac{1}{N^2}} \right) \frac{1}{A}$$

Where:

$$m = \sqrt{1 - \frac{\left( \frac{f_2}{f_m} - \frac{f_m}{f_2} \right)^2}{\left( \frac{f_{2\infty}}{f_m} - \frac{f_m}{f_{2\infty}} \right)^2}}$$

$$A = \frac{(1 - m^2)}{4m}$$

$$N = \frac{f_{2\infty}}{\sqrt{f_1 f_2}} = \frac{f_{2\infty}}{f_m}$$

$$f_m = \sqrt{f_1 f_2} = \sqrt{f_{1\infty} f_{2\infty}}$$



For the above equations:

$f_1$  is the lower cut-off frequency.


$f_2$  is the upper cut-off frequency.

$f_{1\infty}$  is the lower frequency at which maximum attenuation occurs.

(Continued on next page)

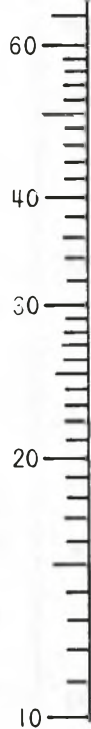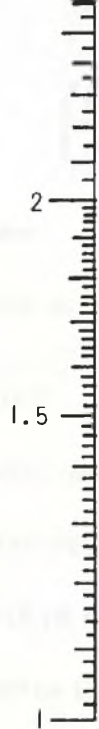

Nomogram 2-21

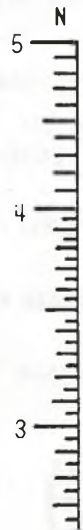

$f_{2\infty}$  is the upper frequency at which maximum attenuation occurs.

The values of  $f_m$  and  $N$  are found in Nomogram 2-21 by drawing a straight line through the values of  $f_{1\infty}$  and  $f_{2\infty}$ .  $f_m$  and  $N$  are found where this line intersects their respective scales.

Solve for  $m$  in Nomograms 2-22A and 2-22B as follows:

$$\text{Let } f_A = \left( \frac{f_2}{f_m} - \frac{f_m}{f_2} \right)$$

$$\text{and } f_B = \left( \frac{f_{2\infty}}{f_m} - \frac{f_m}{f_{2\infty}} \right)$$

$f_A$  and  $f_B$  are found in Nomogram 2-22A by drawing a straight line between the values of  $f_m$  on the right-hand scale and  $f_2$  or  $f_{2\infty}$  on the left-hand scale.  $f_A$  and  $f_B$  are found where these lines cross the diagonal scale.

NOTE: Use the  $f_2$  scale when solving for  $f_A$  and the  $f_{2\infty}$  scale when solving for  $f_B$ . Draw a straight line through the values of  $f_A$  and  $f_B$  in Nomogram 2-22B.  $m$  is found where this line intersects its scale.

Solve for  $L_3$  and  $C_3$  in Nomogram 2-19 as follows:

1. Draw a straight line through  $L_1$  on the

B scale and the value of  $m$  on the  $m_1$  scale.  $L_3$  is found on the A scale where this line intersects it.

2. Draw a straight line through  $C_1$  on the A scale and the value of  $m$  on the  $m_1$  scale.  $C_3$  is found on the B scale where this line intersects it.





Solve for  $L_4$  and  $C_5$  in Nomogram 2-23 as follows:

1. Draw a straight line through  $L_1$  and  $m$  on their respective scales. From the point where this line intersects the pivot scale, extend a second line through the value of  $N$ .  $L_4$  is found where this line intersects its scale.

2. Draw a straight line through  $C_1$  and  $N$  on their respective scales. From the point where this line intersects the pivot scale, extend a second line through the value of  $m$ .  $C_5$  is found where this line intersects its scale.

Solve for  $L_5$  and  $C_4$  in Nomogram 2-24 as follows:

1. Draw a straight line through  $m$  and  $N$  on their respective scales. From the point

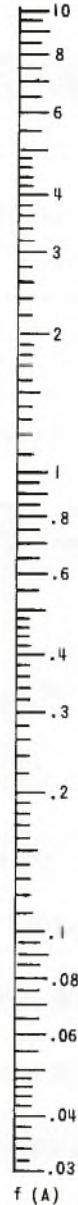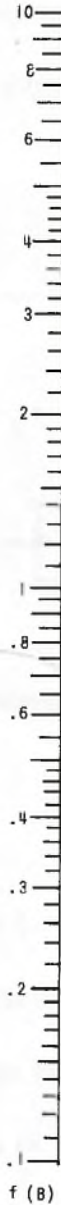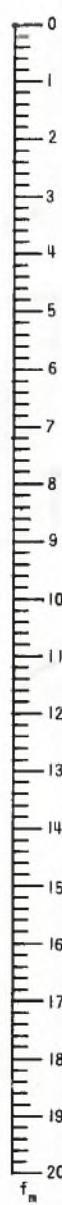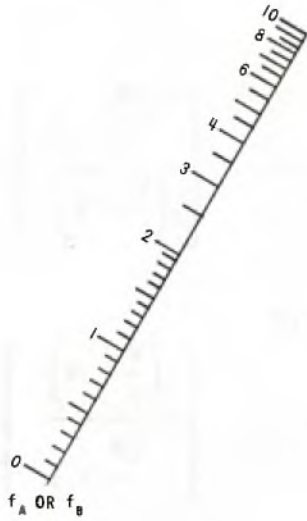

Nomogram 2-22A

Nomogram 2-22B

where this line intersects the pivot scale, extend a second line through the value of  $L_1$  on its scale.  $L_5$  is found where the second line intersects the  $L_5$  scale.

2.  $C_4$  is found in a similar manner to that described for  $L_5$ .

The Pi configuration for the shunt m-derived filter is shown in Fig. 2-25. For this circuit:

$$L_6 = mL_1 \left[ \frac{\left(N - \frac{1}{N}\right)^2}{1 + N^2} \right]$$

$$C_6 = \frac{C_1}{m} \left[ \frac{1 + \frac{1}{N^2}}{\left(N - \frac{1}{N}\right)^2} \right]$$

$$L_7 = mL_1 \left[ \frac{\left(N - \frac{1}{N}\right)^2}{1 + \frac{1}{N^2}} \right]$$

$$C_7 = \frac{C_1}{m} \left[ \frac{1 + N^2}{\left(N - \frac{1}{N}\right)^2} \right]$$

$$L_8 = \frac{L_2}{m}$$

$$C_8 = mC_2$$

Where:  $m$  and  $N$  are the same as for the series m-derived filter.

Solve for  $L_6$  and  $C_7$  in Nomogram 2-25 as follows:

1. Draw a straight line through the values of  $m$  and  $N$  on their respective scales. From the point where this line intersects the pivot scale, extend a second line through the value of  $L_1$ .  $L_6$  is found where the second line intersects its scale.

2.  $C_7$  is found in a similar manner to that described for  $L_6$ .

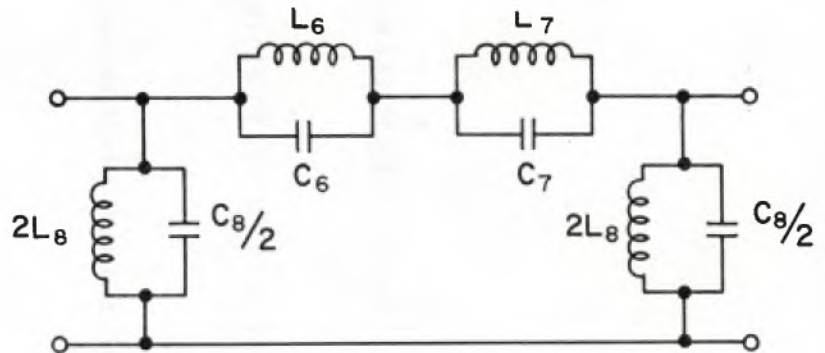


Fig. 2-25. Pi configuration, shunt m-derived filter.



Solve for  $L_7$  and  $C_6$  in Nomogram 2-26 as follows:

1. Draw a straight line through the values of  $m$  and  $N$  on their respective scales. From the point where this line intersects the pivot scale, extend a second line through the value


(Continued on next page)



PIVOT LINE

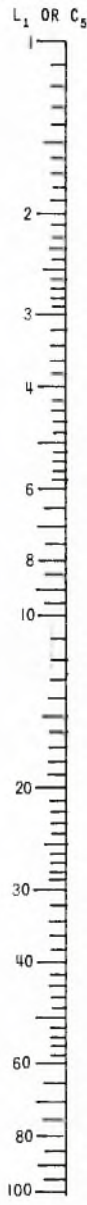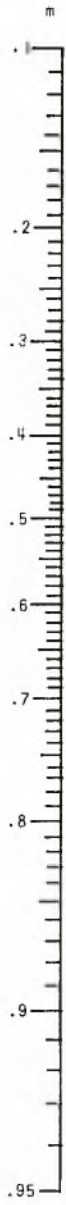

PIVOT LINE

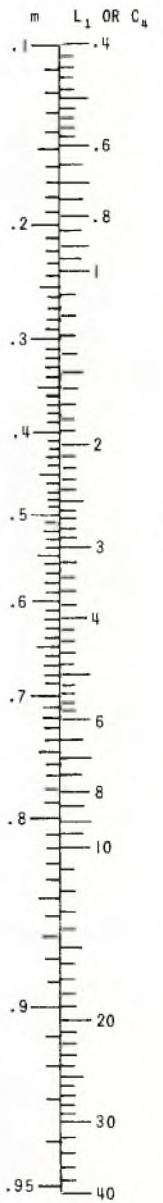

Nomogram 2-23

Nomogram 2-24



of  $L_1$  on its scale.  $L_7$  is found where this line intersects its scale.

2.  $C_6$  is found in a manner similar to that described for  $L_7$ .

Solve for  $L_8$  and  $C_8$  in Nomogram 2-19 as follows:


1. Draw a straight line through  $L_2$  on the A

scale and the value of  $m$  on the  $m_1$  scale.  $L_8$  is found on the B scale where this line intersects it.

2. Draw a straight line through  $C_2$  on the B scale and the value of  $m$  on the  $m_1$  scale.  $C_8$  is found on the A scale where this line intersects it.



Nomogram 2-25

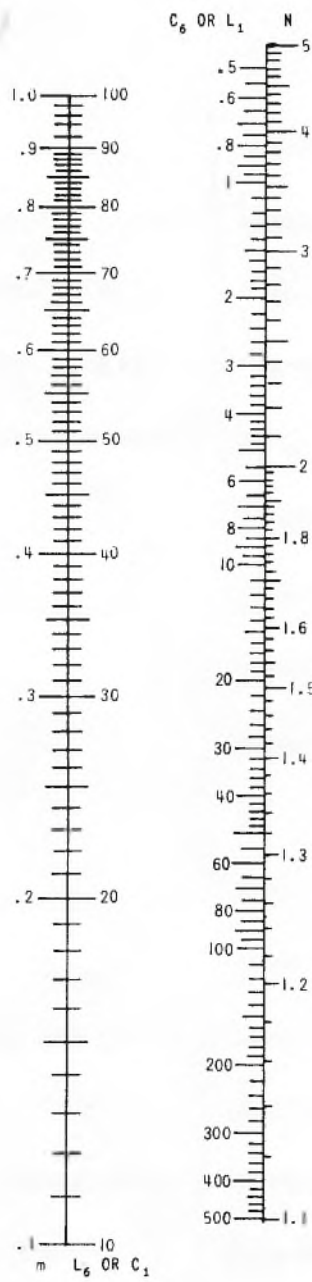

Nomogram 2-26



## Parallel-T Filters

The parallel-T (or twin-T) filter continues to enjoy the wide use that began to greet it since H. W. Augustadt filed his patent for it in May 1936. One of the few limitations of the network is that calculating component values is somewhat cumbersome and time consuming. Nomogram 3-27 eliminates the limitation. The trap or null frequency of the parallel-T shown here is:

$$f_o = 1/[2\pi R_1 C_1]$$


Where:  $R_1 = 2R_2$

and  $C_2 = 2C_1$

The nomogram gives values for all components so that one can determine the trap frequency for any RC combination involved or RC combinations for any trap frequency required.

For a desired trap frequency, various combinations of components can be found directly by rotating a straight-edge about a frequency pivot point on the center scale. Values of R and C can be found where the straight-edge crosses the outer scales. Values other than those shown can be found by multiplying one scale value by any factor and dividing the other scale value by the same factor. Thus, if the R scales are multiplied by 10, the C scales must be divided by 10. It is recommended that capacitor values be selected first from available stock, since values found on the nomogram may be difficult to procure.

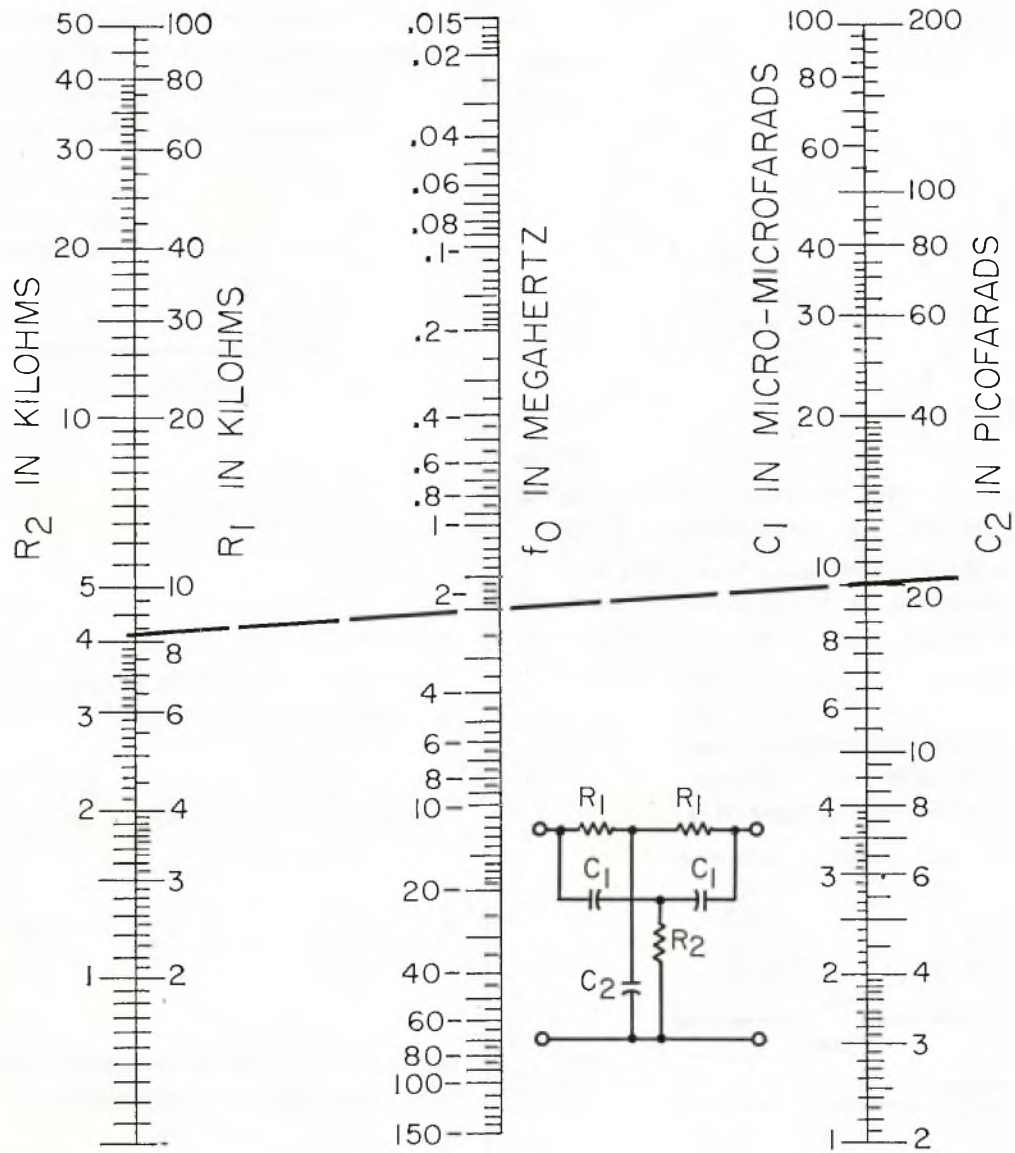The example shown on the nomogram is for a parallel-T filter with sharp rejection at 2 MHz using 10 pf for  $C_1$ . The nomogram gives a value for  $R_1$  of 8.2K.



## Band-Elimination Filters

The band-elimination filter has the characteristic of attenuating a specific band of frequencies and transmitting all frequencies above and below it. Fig. 2-26 shows a typical band-elimination frequency response curve.

The Pi and T configurations for the constant-k filters are shown in Fig. 2-27. For these circuits:

$$L_1 = \frac{(f_2 - f_1) R}{\pi f_1 f_2} \quad C_1 = \frac{1}{4\pi (f_2 - f_1) R}$$

$$L_2 = \frac{R}{4\pi (f_2 - f_1)} \quad C_2 = \frac{(f_2 - f_1)}{\pi f_1 f_2 R}$$

The equations for  $L_2$  and  $C_1$  are solved in Nomogram 2-17 of the high-pass filter section with the values of  $(f_2 - f_1)$  substituted for the  $f_c$  scale.

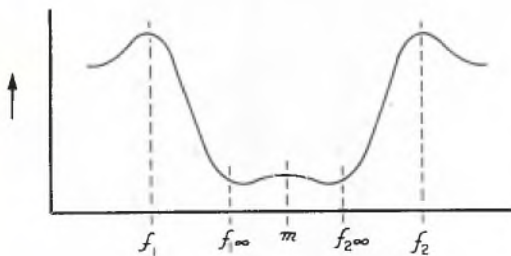


Fig. 2-26. Band-elimination filter response curve.

$L_1$  and  $C_2$  are found in Nomogram 2-28. Their equations are solved as follows:

1. Draw a straight line through the values of  $f_2$  and  $f_1$  on their respective scales to the X scale.

2. Transpose this value to the  $X_{10g}$  scale as indicated on the nomogram.

3. Draw a straight line from the  $X_{10g}$  scale to the appropriate value of  $R$  on its scale. Use  $R(L)$  scale when solving for  $L$  and  $R(C)$  scale when solving for  $C$ .

4. The values of  $L$  and  $C$  are found on their respective scales where they are intersected by the line of step 3.

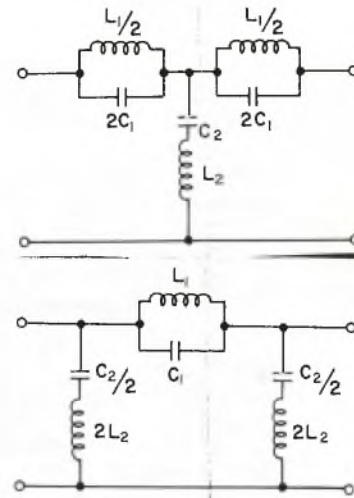


Fig. 2-27. T (top) and Pi (bottom) configuration, band elimination constant  $-k$  filter.

For this nomogram,  $f$  is in kHz,  $L$  is in mh and  $C$  is in  $\mu$ f. Other scale values may be used by multiplying as follows:

$$f \times 10^n, \quad L \times 10^{-n} \text{ and } C \times 10^{-n}$$

The T configuration for the series  $m$ -derived filter is shown in Fig. 2-28. For this circuit:

$$L_3 = mL_1 \quad C_3 = \frac{C_1}{m}$$

$$L_4 = \frac{(1 - m^2) L_1}{4m} \quad C_4 = \frac{4m C_1}{(1 - m^2)}$$



$$L_5 = \frac{L_2}{m} \quad C_5 = mC_2$$

Where:

$$m = \sqrt{1 - \frac{\left(\frac{f_{2\infty}}{f_m} - \frac{f_m}{f_{2\infty}}\right)^2}{\left(\frac{f_2}{f_m} - \frac{f_m}{f_2}\right)^2}}$$

and  $f_m = \sqrt{f_1 f_2} = \sqrt{f_{1\infty} f_{2\infty}}$

(Continued on next page)

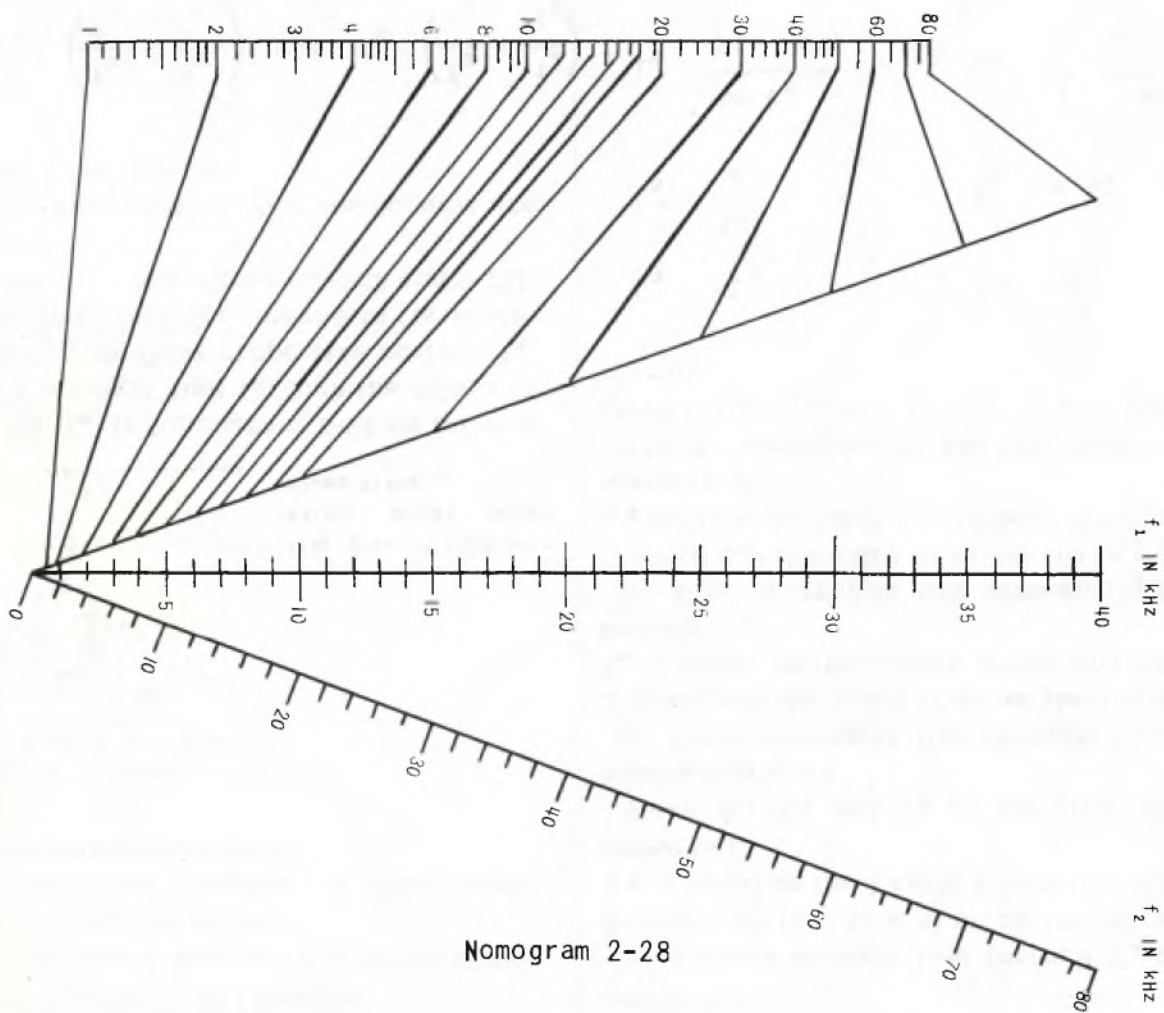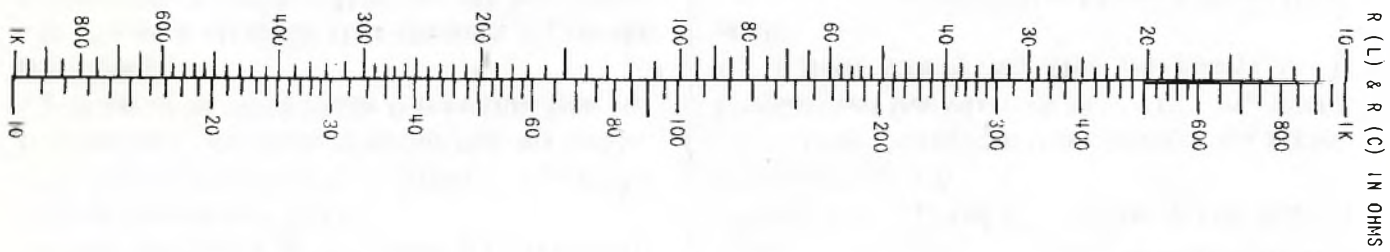

Nomogram 2-28

For the above equations:

$f_1$  is the lower cut-off frequency.

$f_2$  is the upper cut-off frequency.

$f_{1\infty}$  is the lower frequency at which maximum attenuation occurs.

$f_{2\infty}$  is the upper frequency at which maximum attenuation occurs.

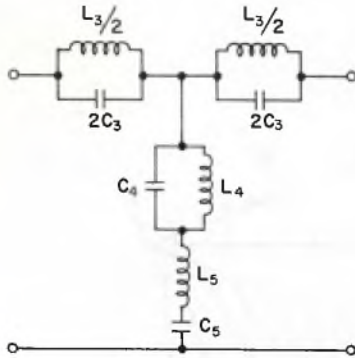


Fig. 2-28. T configuration, series m-derived filter.

Solve for  $f_m$  in Nomogram 2-21 as follows: Extend a straight line through the values of  $f_{1\infty}$  and  $f_{2\infty}$  on their respective scales.  $f_m$  is found where this line intersects its scale.

Solve for  $m$  in Nomograms 2-22A and 2-22B as follows:

1. For simplification, two nomograms are required in the solution.

$$\text{Let } f_A = \left( \frac{f_{2\infty}}{f_m} - \frac{f_m}{f_{2\infty}} \right) \text{ and } f_B = \left( \frac{f_2}{f_m} - \frac{f_m}{f_2} \right)$$

$f_A$  and  $f_B$  are found in Nomogram 2-22A by drawing a straight line between the values of  $f_m$  on the right-hand scale and  $f_2$  or  $f_{2\infty}$  on the left-hand scale.  $f_A$  and  $f_B$  are found where these lines cross the diagonal scale. NOTE: Use the  $f_2$  scale when solving for  $f_B$  and the  $f_{2\infty}$  scale when solving for  $f_A$ . Draw a straight line through the values of  $f_A$  and  $f_B$  in Nomogram 2-22B.  $m$  is found where this line intersects its scale.

Solve for  $L_3$ ,  $C_3$ ,  $L_5$ , and  $C_5$  on the left side of Nomogram 2-19:

1. Draw a straight line through  $L_1$  on the B scale and the value of  $m$  on the  $m_1$  scale.  $L_3$  is found on the A scale where this line intersects it.

2. Draw a straight line through  $C_1$  on the A scale and the value of  $m$  on the  $m_1$  scale.  $C_3$  is found on the B scale where this line intersects it.

3. Draw a straight line through  $L_2$  on the

A scale and the value of  $m$  on the  $m_1$  scale.  $L_5$  is found on the B scale where this line intersects it.

4. Draw a straight line through  $C_2$  on the B scale and the value of  $m$  on the  $m_1$  scale.  $C_5$  is found on the A scale where this line intersects it.

Solve for  $L_4$  and  $C_4$  on the right side of Nomogram 2-19:

1. Draw a straight line through  $L_1$  on the D scale and the value of  $m$  on the  $m_2$  scale.  $L_4$  is found on the C scale where this line intersects it.

2. Draw a straight line through  $C_1$  on the C scale and the value of  $m$  on the  $m_2$  scale.  $C_4$  is found on the D scale where this line intersects it.

The Pi configuration for the shunt m-derived filter is shown in Fig. 2-29. For this circuit:

$$L_3 = mL_1 \qquad C_3 = \frac{C_1}{m}$$

$$L_5 = \frac{L_2}{m} \qquad C_5 = mC_2$$

$$L_6 = \frac{4mL_2}{(1-m^2)} \qquad C_6 = \frac{(1-m^2)C_2}{4m}$$

Where:  $m$  is the same as for the series m-derived filters described in the previous section.  $L_3$ ,  $C_3$ ,  $L_5$ , and  $C_5$  are the same as for the series m-derived filter described in the previous section.

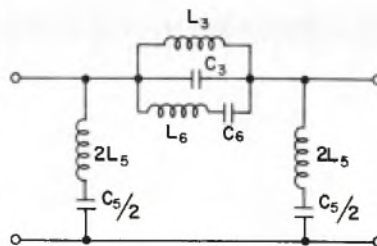


Fig. 2-29. Pi configuration, shunt m-derived filter.

Solve for  $L_6$  and  $C_6$  on the right side of Nomogram 2-19:

1. Draw a straight line through  $L_2$  on the C scale and the value of  $m$  on the  $m_2$  scale.  $L_6$  is found where this line intersects the D scale.

2. Draw a straight line through  $C_2$  on the D scale and the value of  $m$  on the  $m_2$  scale.  $C_6$  is found where this line intersects the C scale.

## CHAPTER 3

# Transmission Lines



## RF Transmission Lines

When the type of transmission line is known, its characteristic impedance as well as other constants can be found from available charts. However, the type of line is not always known. Therefore, calculations must be made to determine its constants.


The nomograms in this chapter simplify the calculations of constants for several of the more common types of uniform transmission lines. It must be kept in mind that negligible losses are assumed for all the types presented. The following assumptions are also made:

1. There is skin effect present.
2. Distance between conductors is large compared to the diameter of the conductor.
3. Distance between conductors is small compared to the wavelength.
4. Line length is large compared to distance between conductors.
5. The height of the conductor above ground is large compared to the distance between conductors.


The reader is referred to Landee et al, Electronic Designers Handbook, New York, Mc-Graw-Hill Book Company, 1957.

*(Continued on next page)*

Nomogram 3-2

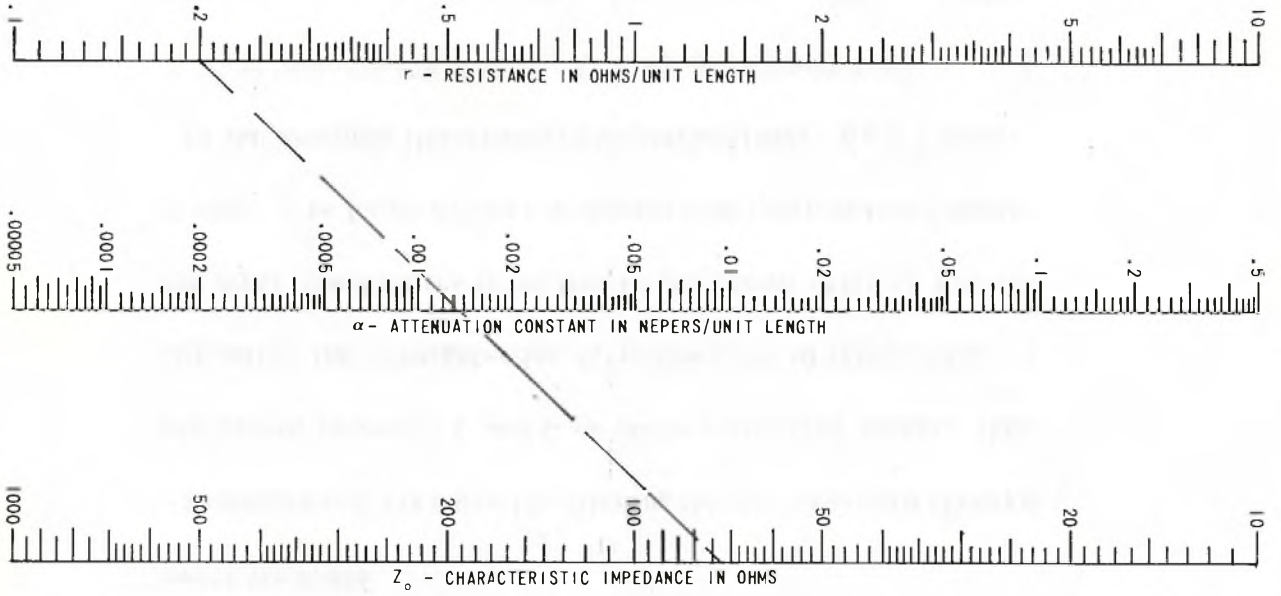

Nomogram 3-1

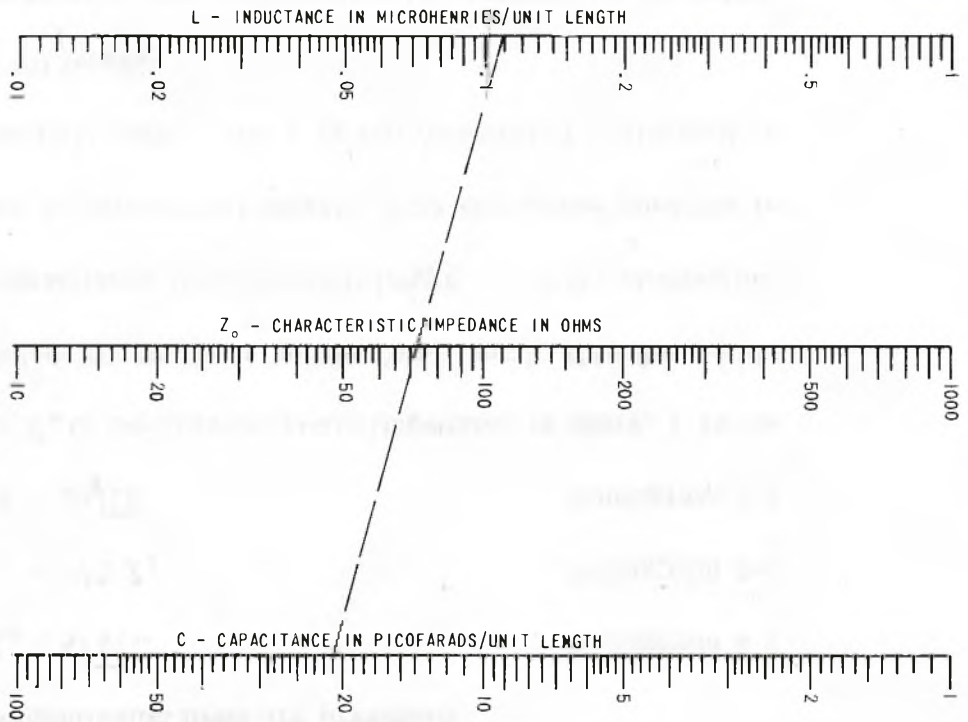

First, some general relationships which apply to parallel-wire transmission lines are presented.

$$(1) \quad Z_0 = \sqrt{L/C} \quad \text{Nomogram 3-1}$$

$$(2) \quad \alpha = r/2 Z_0 \quad \text{Nomogram 3-2}$$


$$(3) \quad \beta = \omega \sqrt{LC} \quad \text{Nomogram 3-3}$$

Where:  $Z_0$  is the characteristic impedance in ohms,  $L$  is the distributed inductance in henries/unit length,  $C$  is the distributed capacitance in farads/unit length,  $\alpha$  is the attenuation constant in nepers/unit length,  $\beta$  is the phase constant in radians/unit length, and  $r$  is the distributed resistance in ohms/unit length.

Nomograms 3-1 and 3-2 are solved by extending a straight-edge through the two known values on their respective scales and locating the third value where the straight-edge intersects its scale.

Nomogram 3-3 is solved by aligning the straight-edge through the known values of  $L$  and  $C$  on their respective scales, then extending the straight-edge from the point of intersection of the first line with the pivot line to the known value of  $f$  on its scale.  $\beta$  is found where the second line intersects its scale.

In the example illustrated by the dashed lines,  $Z_0 = 73$  ohms,  $L = .11$  microhenries/foot,  $C = 21$  picofarads/foot,  $r = .2$  ohms per foot,  $f = 50$  kiloHertz,  $\alpha = .00137$ , and  $\beta = .00477$ .

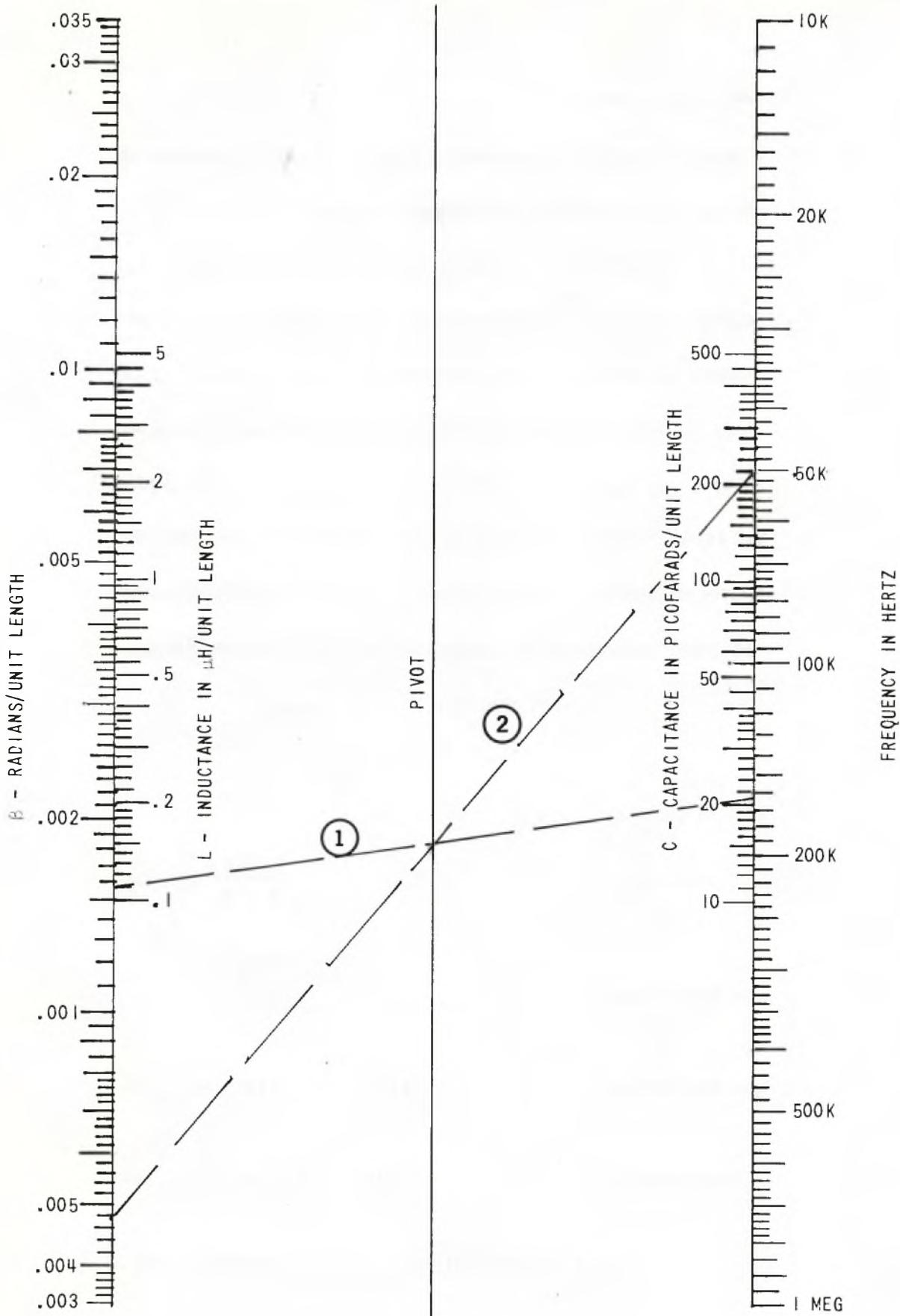

Nomogram 3-3

# Open Two-Wire Lines

The configuration of this line is shown in Fig. 3-1

$$(4) \quad Z_o = 276 \log_{10} 2D/d \quad \text{Nomogram 3-4}$$

$$(5) \quad L = 0.921 \log_{10} 2D/d \quad \text{Nomogram 3-5}$$

$$(6) \quad C = \frac{12.06}{\log_{10} 2D/d} \quad \text{Nomogram 3-5}$$

$$(7) \quad r = \frac{8.3 \sqrt{f}}{(d/2)} \quad \text{Nomogram 3-6}$$

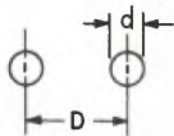



Fig. 3-1. Open two-wire line.

Nomograms 3-4 and 3-5 are solved by extending a straight-edge through the values of  $D$  and  $d$  on their respective scales and locating the unknown value where this line intersects the center scale. Notice that in Nomogram 3-5, the left side of the centerline is the scale of  $L$  and the right side is the scale for  $C$ . Values other than those given may be used by simultaneously multiplying the  $D$  and  $d$  scales by the same factor. The values of the center scales remain unchanged.


Nomogram 3-6 is solved by extending a straight-edge through the values of  $f$  and  $d$  on their respective scales and locating  $r$

*(Continued on next page)*

Nomogram 3-4

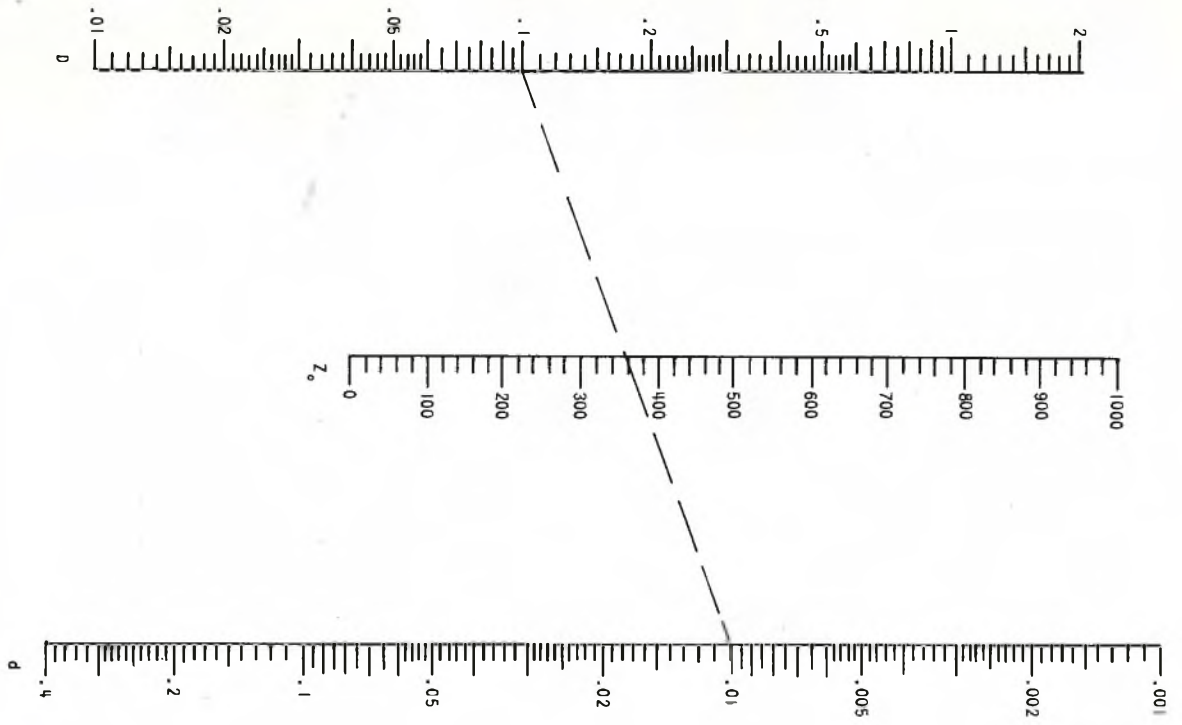


Nomogram 3-5

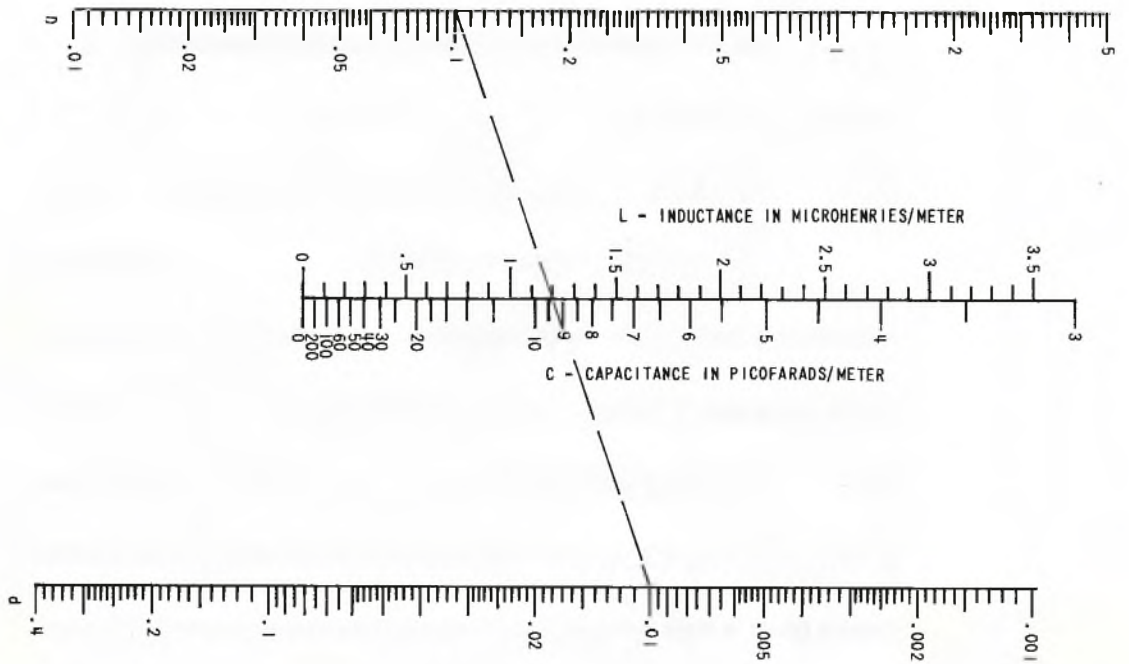

where this line intersects its scale. Values other than those shown may be used by simultaneously multiplying the f and d scales by the same factor without changing the values of the r scale. If only d is multiplied by  $10^n$ , then r must be multiplied by  $10^{-n}$ . If only f is multiplied by  $10^n$ , then r must be multiplied by  $10^{n/2}$ . ( $n$  may be positive or negative.)

In the example illustrated by the dashed lines,  $D = .1$  cm,  $d = .01$  cm,  $Z_0 = 359$  ohms,  $L = 1.2$  microhenries/meter,  $c = 9.3$  picofarads/meter, and  $r = .37$  ohms/meter.

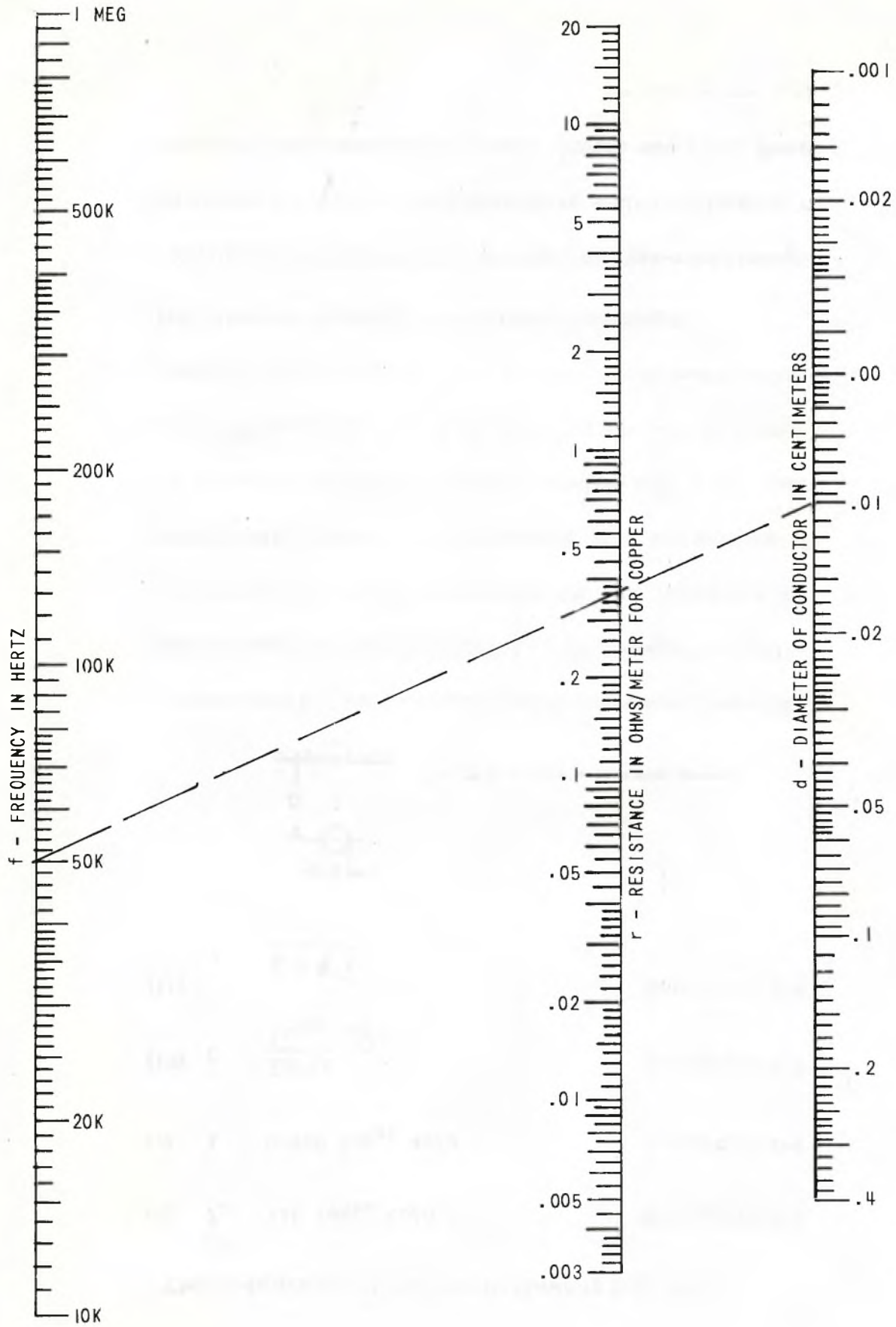

Nomogram 3-6



# Single-Wire Above Ground

The configuration of this line is shown in Fig. 3-2.

(8)  $Z_0 = 138 \log_{10} 4D/d$  Nomogram 3-7

(9)  $L = 0.460 \log_{10} 4D/d$  Nomogram 3-8

(10)  $C = \frac{24.12}{\log_{10} 4D/d}$  Nomogram 3-8

(11)  $r = \frac{8.3 \sqrt{f}}{d}$  Nomogram 3-9

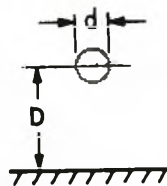



Fig. 3-2. Single wire above ground.

Nomograms 3-7 and 3-8 are solved by extending a straight-edge through the values of  $D$  and  $d$  on their respective scales and locating the unknown value where the line intersects the center scale. Notice that in Nomogram 3-8, the left side of the centerline is the scale for  $L$  and the right side is the scale for  $C$ . Values other than those given may be used by simultaneously multiplying the  $D$  and  $d$  scales by the same factor. The values of the center scales remain unchanged.


Nomogram 3-9 is solved by extending a straight-edge through the values of  $f$  and  $d$  on their respective scales and locating  $r$  where this line intersects its scale. Values other than those

*(Continued on next page)*

Nomogram 3-7

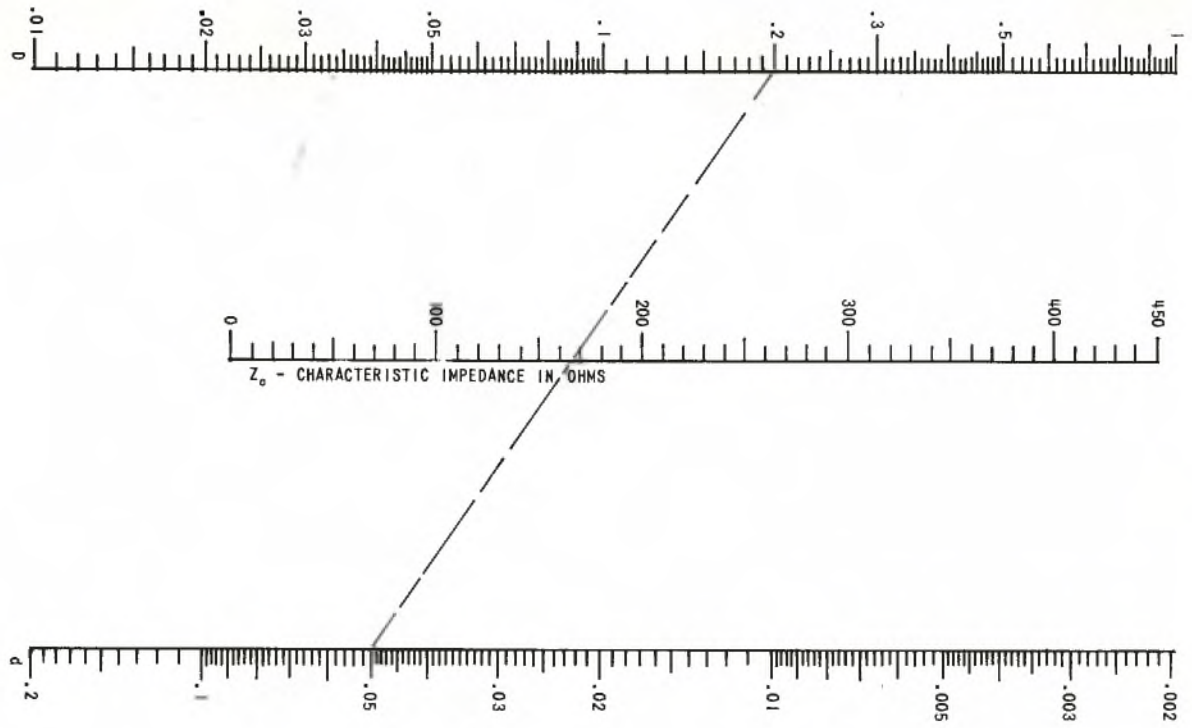


Nomogram 3-8

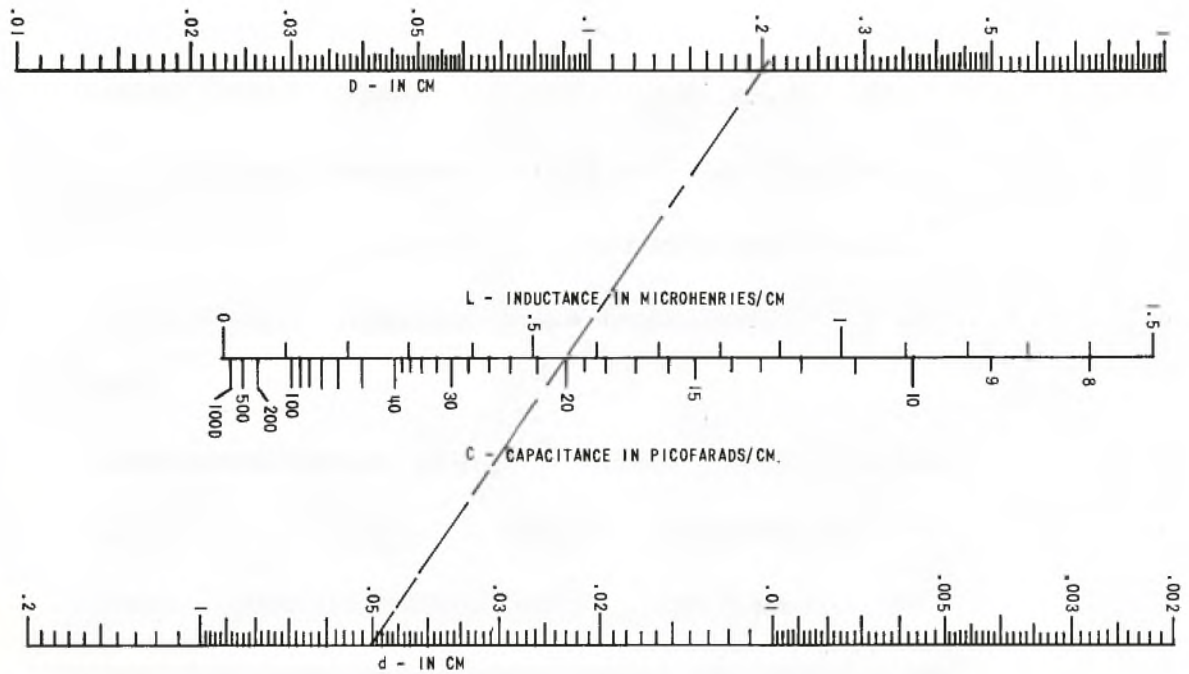

shown may be used by simultaneously multiplying the  $f$  and  $d$  scales by the same factor without changing the values of the  $r$  scale. If only  $d$  is multiplied by  $10^n$ , then  $r$  must be multiplied by  $10^{-n}$ . If only the  $f$  scale is multiplied by  $10^n$ , then  $r$  must be multiplied by  $10^{n/2}$ . ( $n$  may be positive or negative.)

In the example illustrated by the dashed lines  $D = .2$  cm,  $d = .05$  cm,  $Z_0 = 166$  ohms,  $L = .554$  microhenries/meter, and  $c = 20$  picofarads/meter. In the example illustrated by the large dashed lines  $d = .02$  cm,  $f = \text{kHz}$ , and  $r = .092$  ohms/meter for copper.

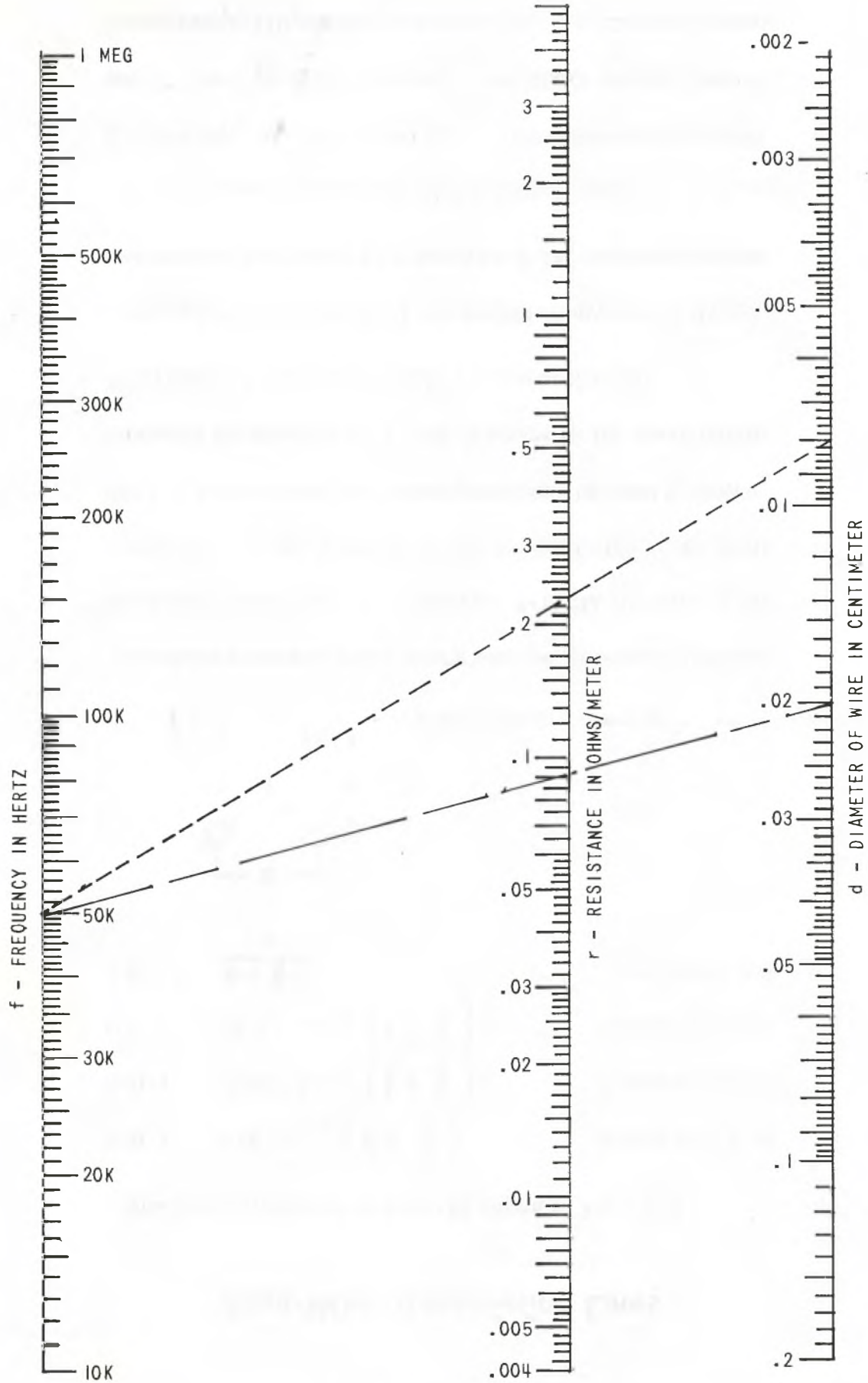

Nomogram 3-9

## Four-Wire Transmission Lines

The configuration of this line is shown in Fig. 3-3.

(12) $Z_o = 138 \log_{10} \left( \sqrt{2} \frac{D}{d} \right)$	Nomogram 3-10
(13) $L = 0.460 \log_{10} \left( \sqrt{2} \frac{D}{d} \right)$	Nomogram 3-11
(14) $C = 24.1 / \log_{10} \left( \sqrt{2} \frac{D}{d} \right)$	Nomogram 3-11
(15) $r = \frac{8.3 \sqrt{f}}{d}$	Nomogram 3-9

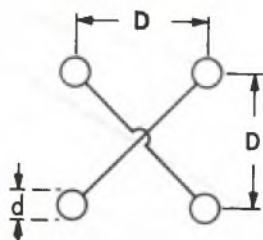



Fig. 3-3. Four-wire transmission line.

The unknown value is found where the line intersects the center scale. Notice that in Nomogram 3-11 the left side of the center line is the scale for  $L$  and the right side is the scale for  $C$ . Values other than those given may be used by simultaneously multiplying the  $D$  and  $d$  scales by the same factor. The values of the center scales remain unchanged.


Nomograms 3-10 and 3-11 are solved by drawing a straight line through the values of  $D$  and  $d$  on their respective scales.

In the example illustrated by the dashed lines,  $D = 2$  cm,  $d = .008$  cm,  $Z_o = 352$  ohms,  $L = 1.17$  microhenries/meter, and  $c = 9.4$  picofarads/meter. The short dashed lines in Nomogram 3-9 illustrate the solution for  $r = .23$  ohms/meter at  $f = 50$  kHz.

Nomogram 3-10

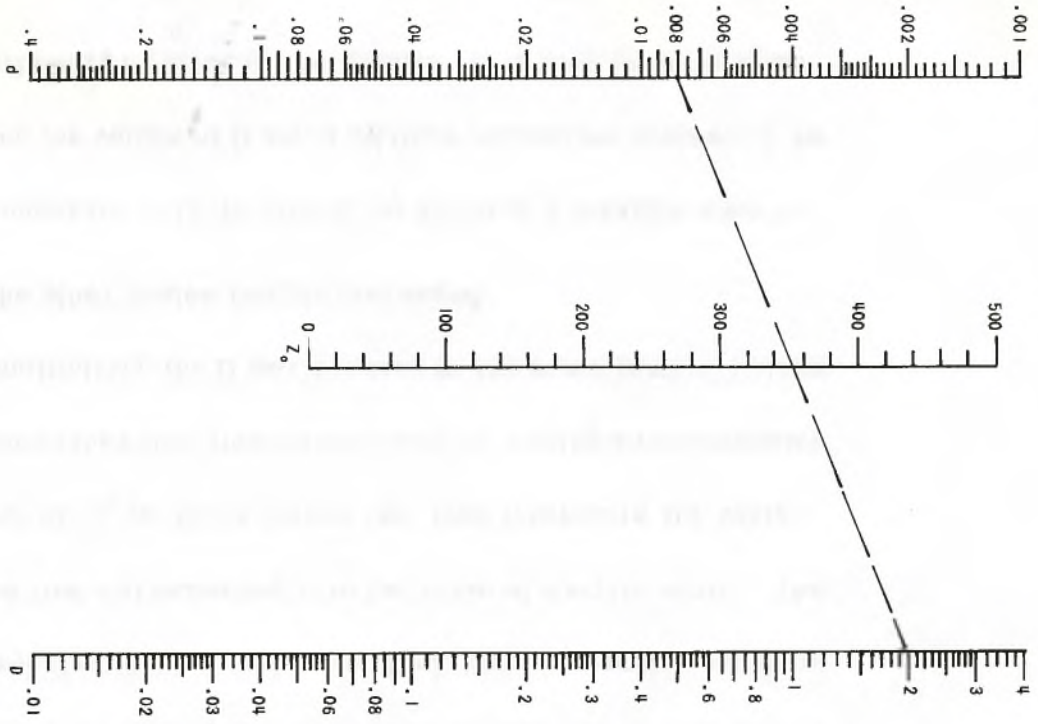

Nomogram 3-11

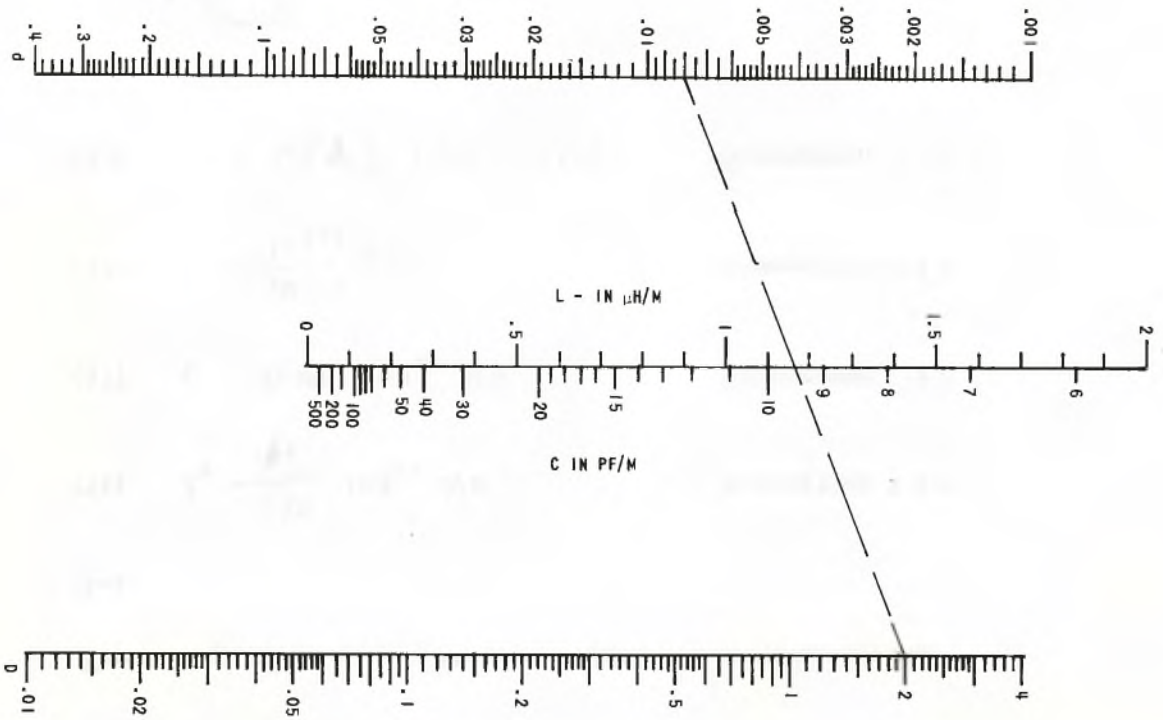

# Coaxial Cable

The configuration of this transmission line is shown in Fig. 3-4.

$$(16) \quad Z_o = \frac{138}{\sqrt{e}} \log_{10} D/d \quad \text{Nomogram 3-12}$$

$$(17) \quad L = 0.460 \log_{10} D/d \quad \text{Nomogram 3-13}$$

$$(18) \quad C = \frac{24.1e}{\log_{10} D/d} \quad \text{Nomogram 3-13}$$

$$(19) \quad r = 8.3 \sqrt{f} (1/D + 1/d) \quad \text{Nomogram 3-14}$$

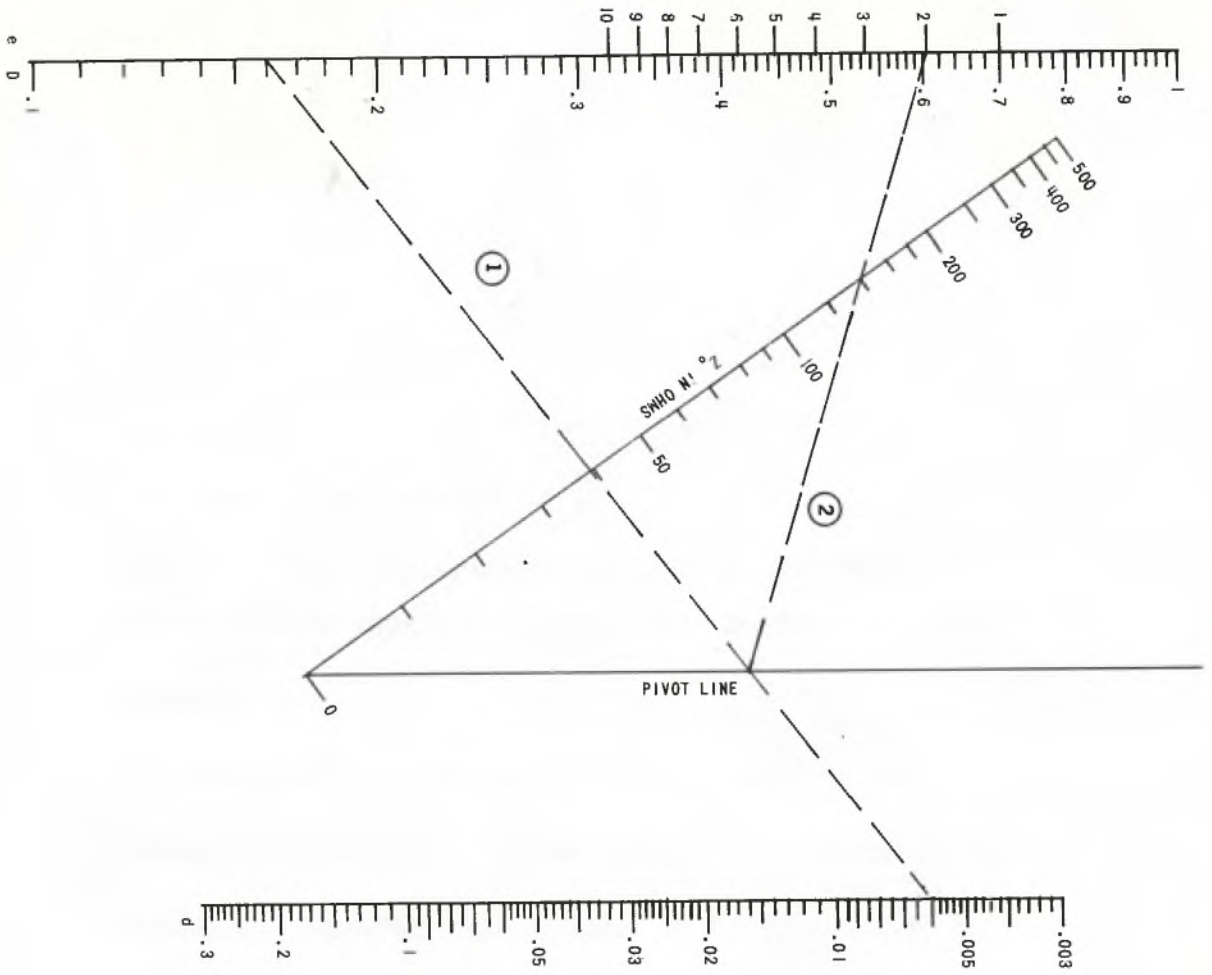


Fig. 3-4. Coaxial cable.


Nomogram 3-12 is solved by aligning a straight-edge between the values of  $D$  and  $d$  on their respective scales, then by rotating the straight-edge about the intersecting point on pivot line and extending it to the value of  $e$  on its scale. The value of  $Z_o$  is found where this line intersects its scale. Values other than those shown may be used by simultaneously multiplying the  $D$  and  $d$  scales by the same factor. Values of the other scales remain unchanged.

Nomogram 3-13 is solved by aligning a straight-edge between the values of  $D$  and  $d$  on their respective scales.  $L$  is found where its scale is intersected.  $C$  is then found by align-

(Continued on next page)



Nomogram 3-12

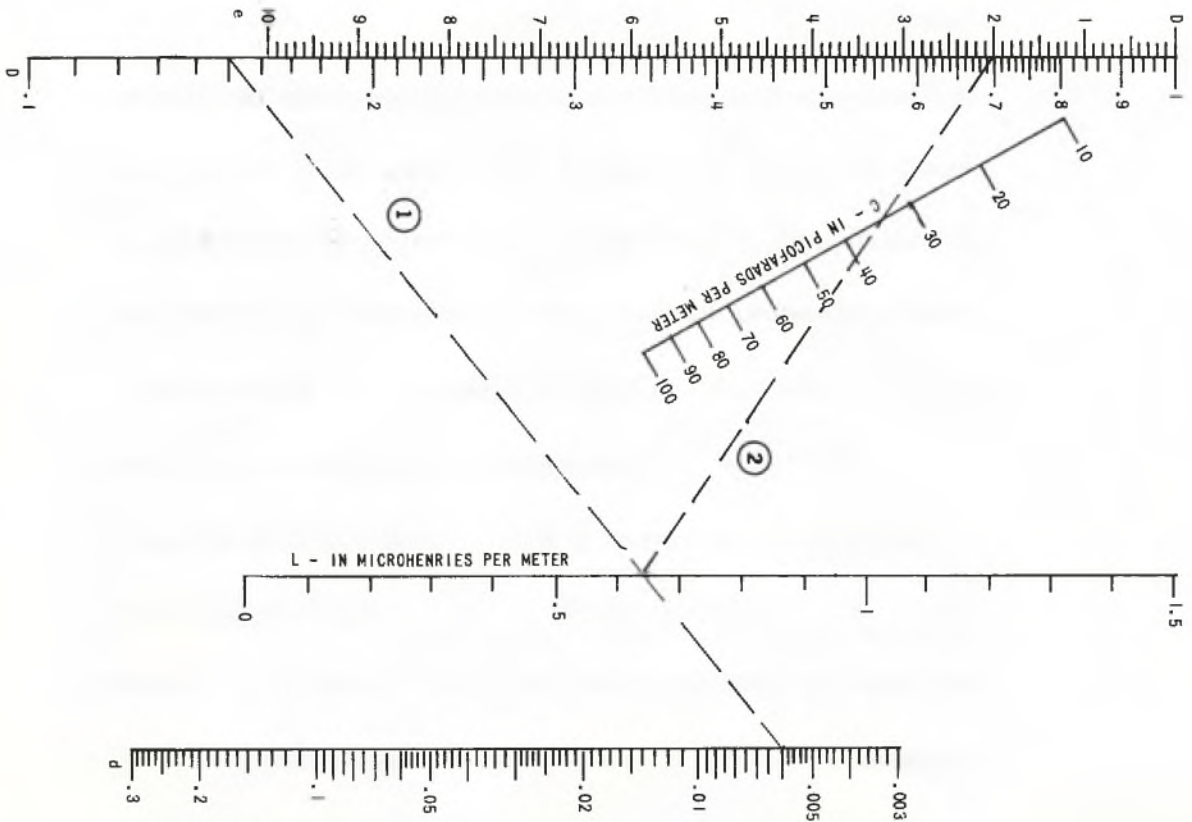


Nomogram 3-13



ing the straight-edge between L and e on their respective scales. C is found where this line intersects the diagonal scale. Values other than those shown may be used by simultaneously multiplying the D and d scales by the same factor. Other scale values remain unchanged.

Nomogram 3-14 is solved as follows: (a) Draw a straight line between the values of D and d on their respective scale. (b) Transpose the value of X from the point of intersection of the first line to the same value on the log X scale. (c) Draw another line from the point on the log X scale to the value of f on its scale. r is found where this line intersects its scale. Values other than those given may be used by simultaneously multiplying the D and d scales by  $10^n$ . When this is done, r must be multiplied by  $10^{-n}$ . If the value of f is multiplied by  $10^n$ , then r must be multiplied by  $10^{n/2}$ . (n may be positive or negative.)

In the examples shown,  $D = .16$  cm,  $d = .006$  cm,  $Z_0 = 140$  ohms,  $L = .655$  microhenries/m,  $C = 33$  picofarads/m,  $e = 2$ , and  $r = .31$  ohms/m.

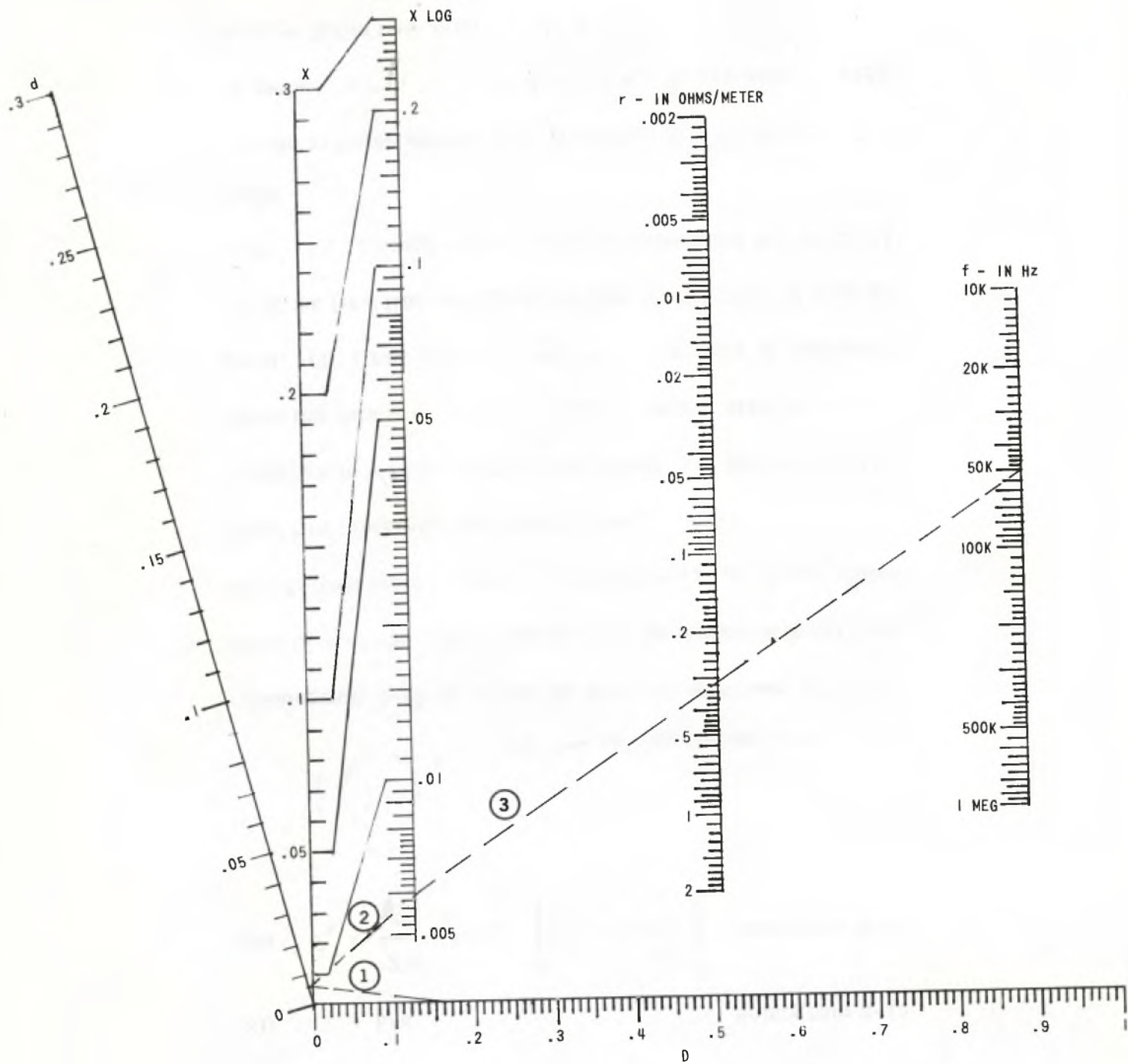

Nomogram 3-14

## Balanced Shielded Lines

The configuration of this line is shown in Fig. 3-5.

$$(20) \quad \sigma = h/D \quad \text{Nomogram 3-15}$$

$$(21) \quad v = h/d \quad \text{Nomogram 3-15}$$

$$(22) \quad * Z_0 = \frac{276}{\sqrt{e}} \log_{10} \left[ 2v \frac{1 - \sigma^2}{1 + \sigma^2} \right] \quad \text{Nomogram 3-16}$$

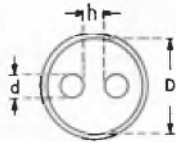



Fig. 3-5. Balanced shielded line.

Nomogram 3-15 is solved by drawing two lines from the value of  $h$  on the right-hand scale to the values of  $d$  and  $D$  on the left-hand scale.  $v$  and  $\sigma$ , respectively, are found where these lines intersect the center scale.


Nomogram 3-16 is solved in two steps. (1) Draw a line between the values of  $v$  and  $\sigma$ , found from the previous nomogram. (2) Draw a second line, from the point of intersection of the first line with the pivot line, to the value of  $e$  on its scale.  $Z_0$  is found where this line intersects the diagonal scale.

In the example shown:  $h = .25$  inches,  $d = .05$  inches,  $D = .3$  inches,  $v = 5$ ,  $\sigma = .83$ ,  $e = .7$ , and  $Z_0 = 84$  ohms. This equation holds true for  $D \gg d$ ,  $h \gg d$ .

\* Reference Data for Radio Engineers, J. J. Little & Ives Company, New York, 1946.

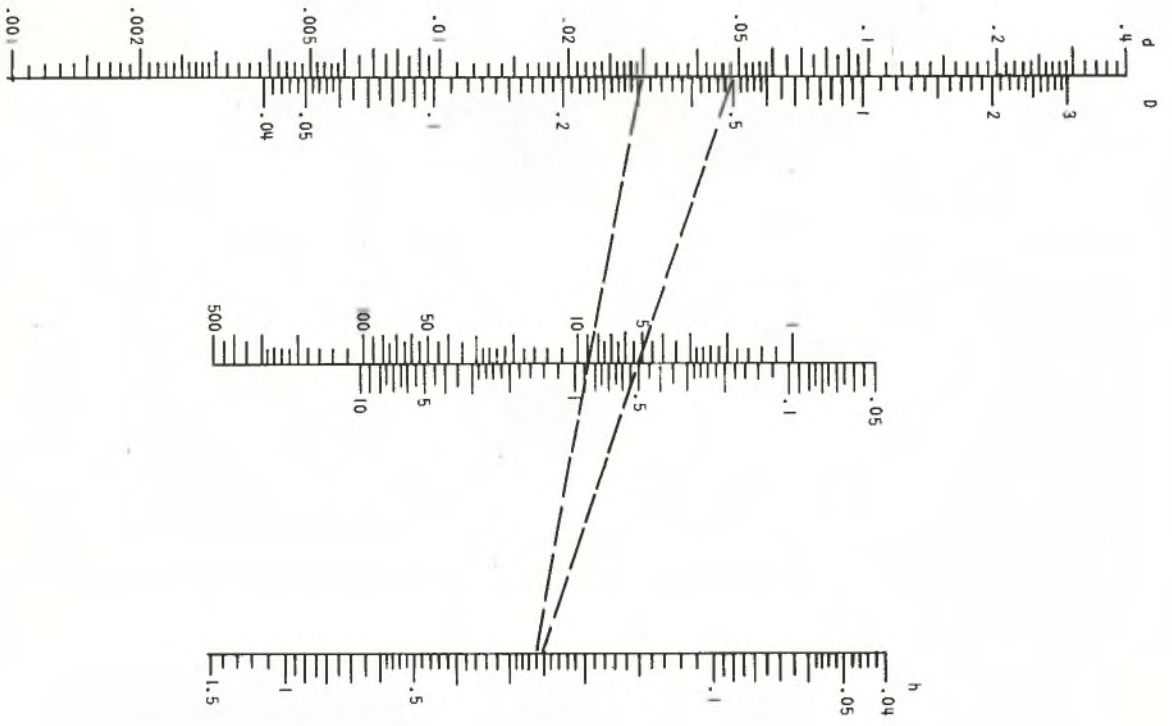

Nomogram 3-15

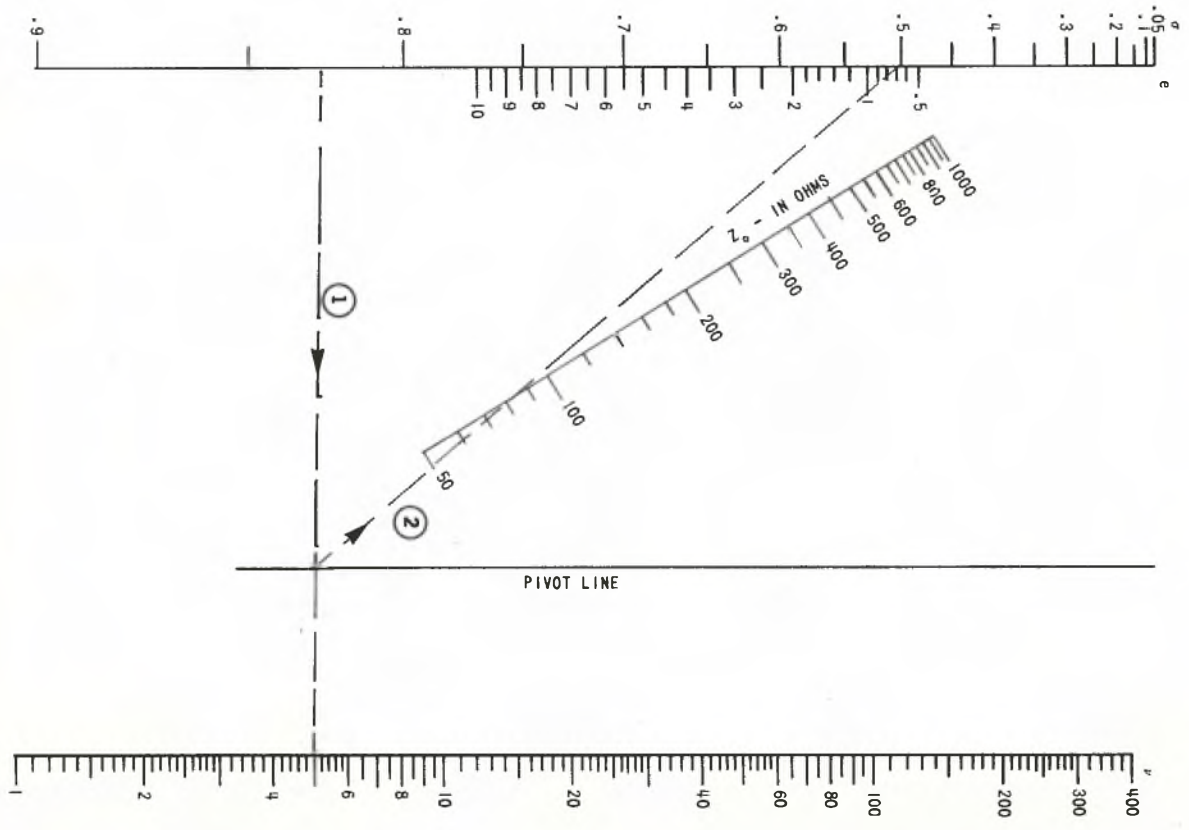

Nomogram 3-16

## CHAPTER 4

# Passive Components

# Single Layer Air-Core Coil

The design of a single layer air-core coil is simplified with the use of this nomogram. Nagoaka's formula is expressed by:



$$L = \frac{.03948 a^2 n^2 k}{b}$$

Where: L is the inductance in microhenries,  
 a is the radius of the coil in cm  
 b is the length of the coil in cm  
 n is the number of turns, and  
 k is Nagoaka's constant (a function of d/b. See Table.)


In the example illustrated by the dashed lines: b = 2 cm, n = 100, a = .5 cm, d = 1 cm (from the table, k = .8181 for d/b = .5) L = 40.4 microhenries.

TABLE OF VALUES FOR K IN NAGOAKA'S FORMULA

<u>Ratio d/b</u>	<u>K</u>	<u>Ratio d/b</u>	<u>K</u>
0.05	0.979	3.8	0.376
0.1	0.959	4.0	0.365
0.2	0.92	4.2	0.355
0.3	0.884	4.4	0.346
0.4	0.850	4.6	0.336
0.5	0.818	4.8	0.328
0.6	0.789	5.0	0.320
0.7	0.761	5.2	0.312
0.8	0.735	5.4	0.305
0.9	0.711	5.6	0.298
1.0	0.688	5.8	0.292
1.1	0.667	6.0	0.285
1.2	0.648	6.2	0.280
1.3	0.629	6.4	0.274
1.4	0.612	6.6	0.269
1.5	0.595	6.8	0.263
1.6	0.580	7.0	0.258
1.7	0.565	7.2	0.254
1.8	0.551	7.4	0.249
1.9	0.538	7.6	0.245
2.0	0.526	7.8	0.241
2.2	0.503	8.0	0.237
2.4	0.482	8.5	0.227
2.6	0.463	9.0	0.219
2.8	0.445	10.0	0.203
3.0	0.429	11.0	0.190
3.2	0.415	12.0	0.179
3.4	0.401	13.0	0.169
3.6	0.388		

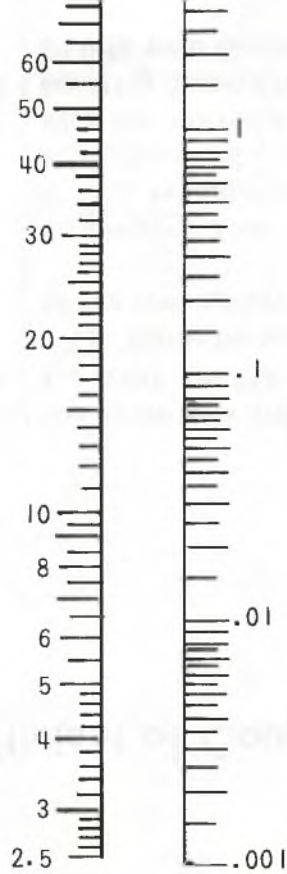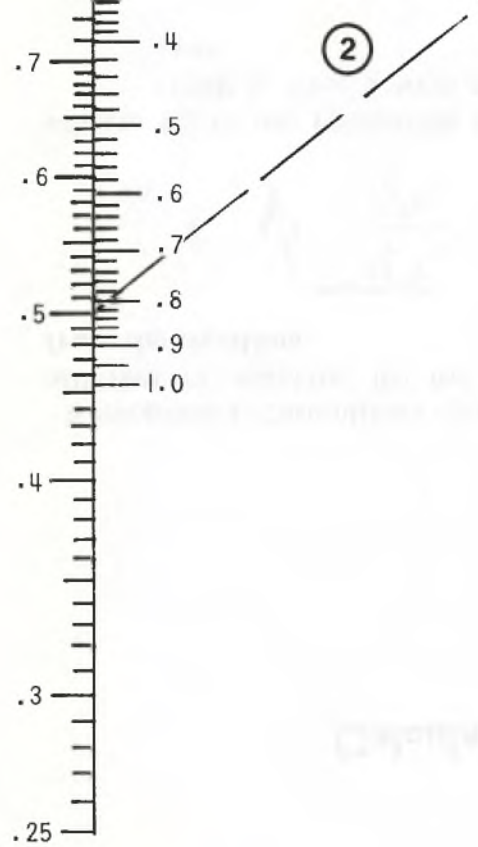

d  
CM K

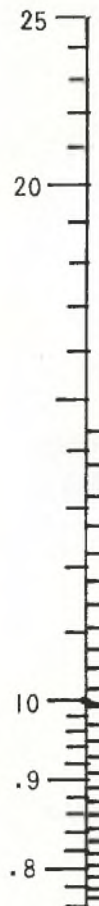

N



L - IN μH



b  
CM





## Calculating Coefficient of Coupling

Nomogram 4-2 simplifies calculation of coefficient of coupling (K) for transformers from the equation:

$$K = \sqrt{1 - \frac{f_o^2 C_o}{f_s^2 C_s}}$$

Where:  $C_o$  is the resonating capacitance of winding No. 1 with winding No. 2 open.

$C_s$  is the resonating capacitance of winding No. 1 with winding No. 2 shorted.

$f_o$  is the frequency with winding No. 2 open.

$f_s$  is the frequency with winding No. 2 shorted.

Any unit may be used for the scales, provided that both the  $f_o$  scale and  $f_s$  scale use

the same unit and that both the  $C_o$  scale and  $C_s$  scale use the same unit.

The following example will illustrate the use of the nomogram.

Example: Find the coefficient of coupling K of a transformer which has a resonating capacitance of 3 pf at a frequency of 90 kHz with the secondary winding open, and a resonating capacitance of 9 pf at a frequency of 80 kHz with the secondary winding shorted.


Solution:

(1) Draw a straight line from 80 on the  $f_s$  scale to 90 on the  $f_o$  scale.

(2) Draw a second line from 3 on the  $C_o$  scale to the point where the first line crosses the diagonal scale and extend it to the pivot line.

(3) From the junction of the second line and the pivot line, draw a third line to 9 on the  $C_s$  scale.

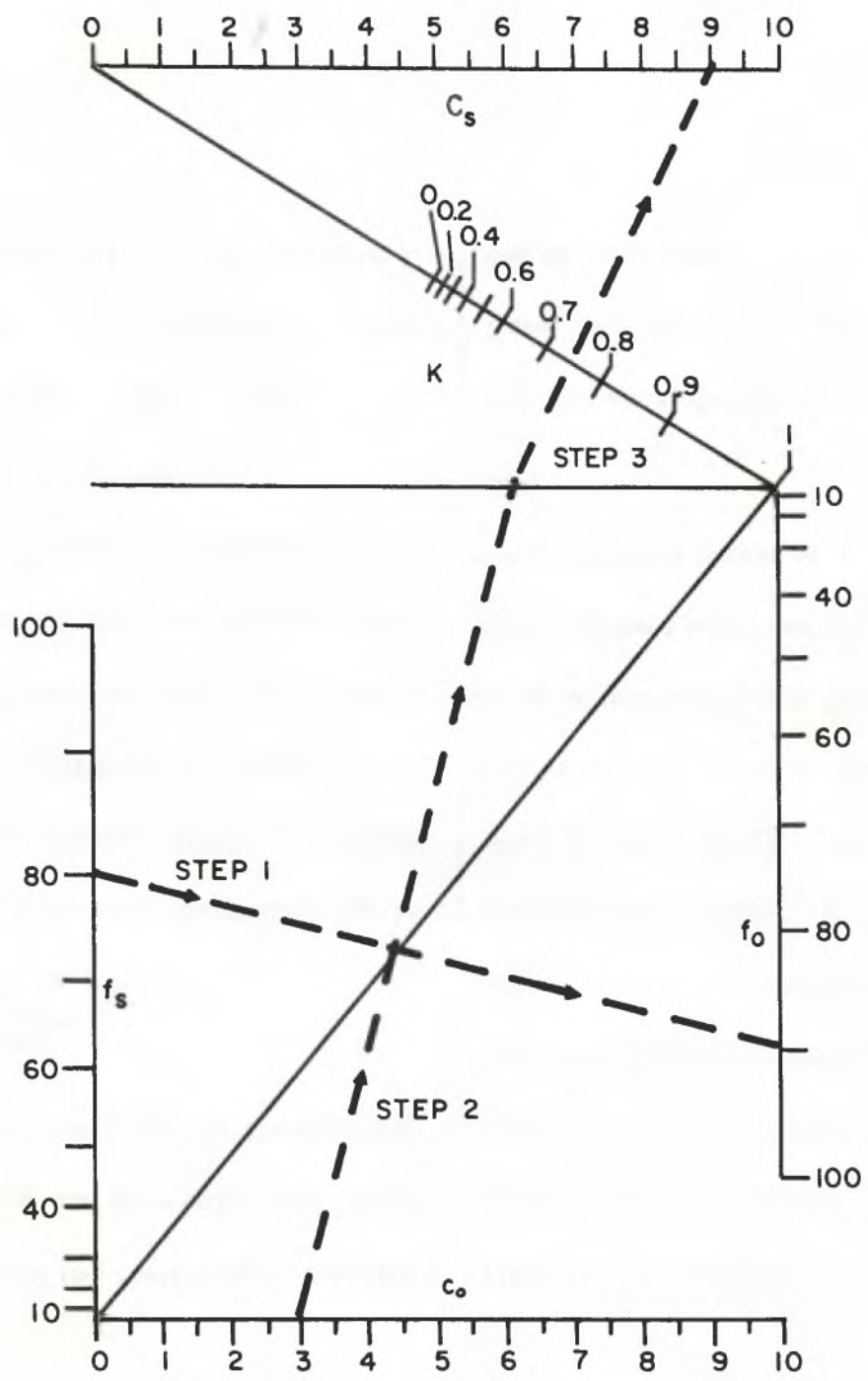(4)  $K = 0.76$  is found where the third line crosses the K scale.



# Mutual Inductance

The calculation of the coefficient of coupling can be frustrating and time consuming, even with the use of the slide rule. In the equation:


$$K = \frac{M}{\sqrt{L_1 L_2}}$$

Where:  $L_1$  is the primary inductance,  $L_2$  is the secondary inductance, and  $M$  is the mutual inductance. The coefficient of coupling  $K$  can be found rapidly with the use of this nomogram by simply drawing two straight lines. The method of solution is illustrated in the example shown in the nomogram.

For loose coupling, where values of  $K$  are between .01 and .1, both the  $K$  and  $M$  values must be multiplied by  $10^{-1}$ . For values of  $L$

other than those shown, the  $L_1$ ,  $L_2$ , and  $M$  scales must all be multiplied by  $10^n$ , where  $n$  may be positive or negative. When this is done the values of  $K$  remain unchanged. When only  $L_1$  and  $L_2$  are multiplied by  $10^n$  and  $M$  remains unchanged,  $K$  must be multiplied by  $10^{-n}$ . NOTE: The  $M$  and  $L_1$  scales can be used for finding squares and square roots of numbers where the  $L_1$  scale is equivalent to the  $A$  scale and the  $M$  scale is equivalent to the  $D$  scale on a normal 10" slide rule.

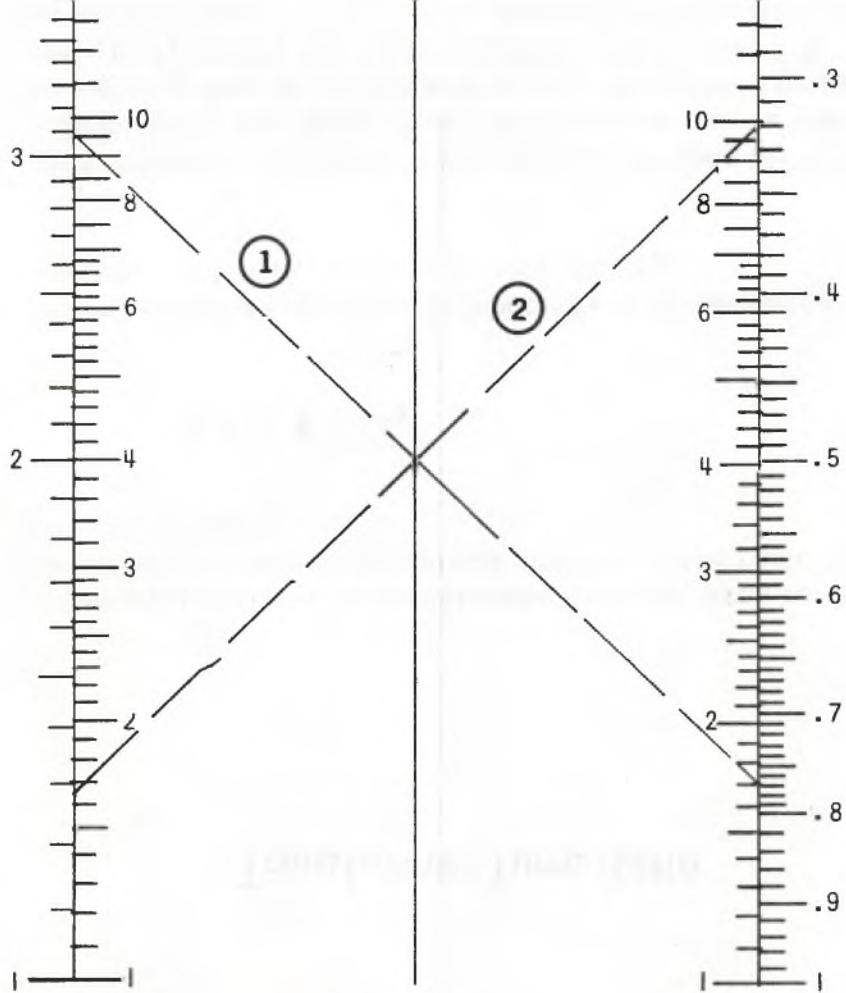In the example illustrated by the dashed lines,  $L_1 = 9.5$  mh,  $L_2$  is 1.7 mh,  $k = .32$ , and  $M = 1.28$  mh.



M  $L_1$  - IN H

10 100

9 80

8 60

7

6 40

6 30

5

4 20

4

$L_2$  - IN H K

100 . 1

80

60

40

30

. 2

20

## Transformer Turns Ratio

Nomogram 4-4 aids in the computation of the turns ratio for transformers used for impedance matching. The basic equation for the turns ratio is:



$$\text{T.R.} = \sqrt{Z_1/Z_2}$$


Where:  $Z_1$  is the primary impedance,  $Z_2$  is the secondary impedance, and T.R. is the turns ratio  $N_1/N_2$ .

The method of solution is illustrated in the example below. Values other than those shown on the scales may be used by multiplying them by  $10^n$ , where  $n$  may be positive or negative. If  $Z_1$  and  $Z_2$  are both multiplied by  $10^n$ , then T.R. remains unchanged. If only  $Z_1$  is multiplied by  $10^n$ , then T.R. is multiplied by  $10^{n/2}$ . If only  $Z_2$  is multiplied by  $10^n$ , then T.R. is multiplied by  $10^{-n/2}$ . Using even values of  $n$  will simplify the conversion of scales.

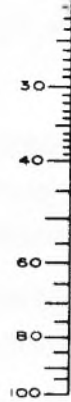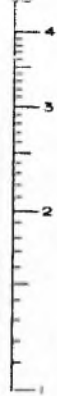Example: Find the turns ratio required for an audio output transformer to match a plate impedance of 500,000 ohms to a speaker where impedance is 8 ohms.

Solution: Draw a straight line from 5,000 on the  $Z_1$  scale to 8 on the  $Z_2$  scale. The line crosses the T.R. scale at 25. Since  $Z_1$  was multiplied by 100, T.R. must be multiplied by 10. The turns ratio is 250/1.



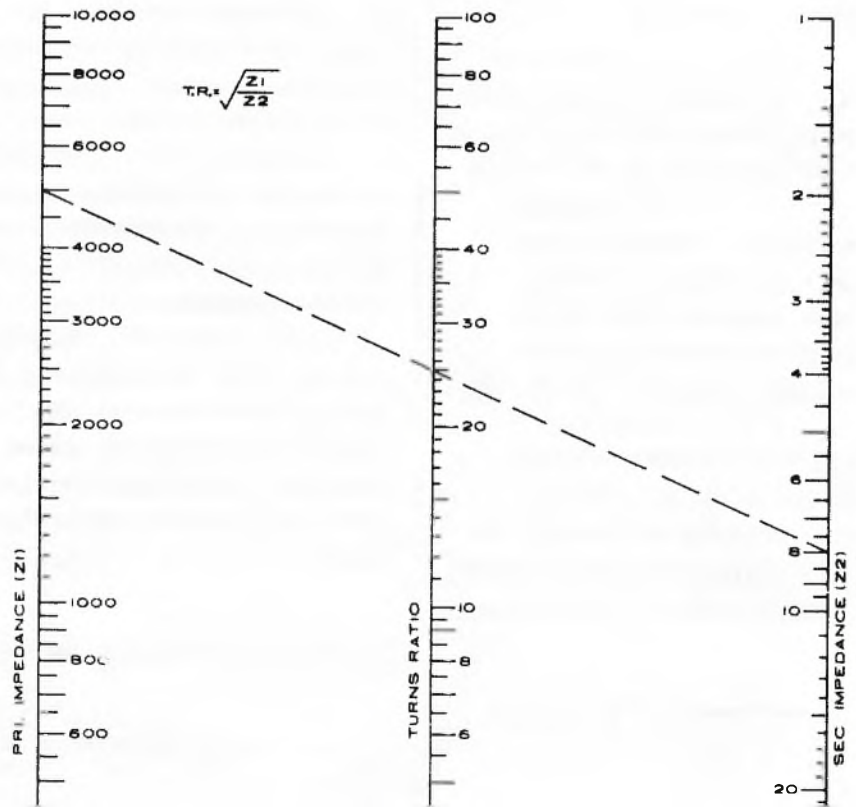



## Impedance Test Procedure for Incoming Inspection

With the use of this procedure and the included nomogram, nonskilled operators may be employed in the incoming inspection testing of low-frequency chokes and transformers for radios, television receivers, and other consumer products. The procedure described is a general test method for impedance measurements and originality is not implied. However, simplified methods are described which allow the use of unskilled help, resulting in a labor cost saving.

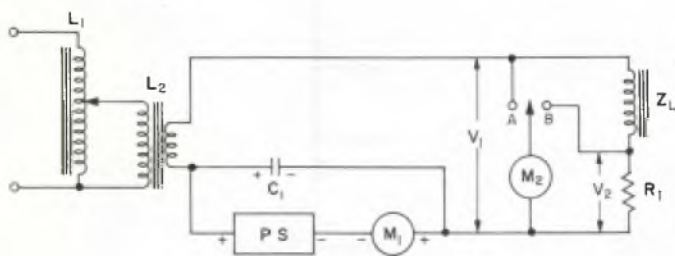


Fig. 4-1. Impedance test procedure test setup.

The engineering prints for the components may specify certain conditions for the tests which should be strictly adhered to. In most cases, 60 Hz will be specified as the test frequency; therefore, the illustration is shown using a variable transformer that is fed from a 120-volt source. Isolation is obtained with the use of a 12-volt stepdown transformer when low voltages are specified and a 1:1 ratio isolation transformer for higher voltages. Where other frequencies are specified, an audio oscillator may be used. In those cases where a DC bias is required as a prerequisite for the test, a low impedance DC supply should be used as illustrated. (Refer to Fig. 4-1.) The accuracy of the test is dependent upon the following conditions:

- (1)  $R_1$  should be selected so that its resistance is very much smaller than the impedance of the inductor under test.
- (2)  $R_1$  should be smaller than the DC resistance of the inductor.

- (3)  $R_1$  should be within 5% accuracy.

With the circuit hooked up as shown in the illustration, proceed with the test as follows:

- (1) Starting from zero, adjust the variable transformer for the test voltage specified.
- (2) Starting from zero, adjust the DC supply for the required DC bias if specified.
- (3) Readjust the variable transformer if necessary. (This reading is  $V_1$ ).
- (4) Throw the meter switch to position "B" and read  $V_2$ .
- (5) The impedance  $Z_L$  can be calculated from the following equation:



$$Z_L = \frac{V_1 R_1}{V_2}$$


With the use of Nomogram 4-5,  $Z_L$  can be rapidly found as follows:

- (1) Draw a straight line from the measured value of  $V_1$  on the left-hand scale to the measured value of  $V_2$  on the right-hand scale.
- (2) Draw a second line from  $R_1$  on its appropriate scale to the point where the first line crosses the pivot line, and extend the line to the  $Z_L$  scale where the unknown impedance can be read directly.

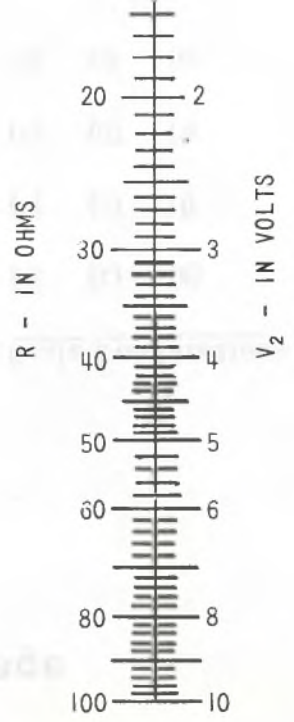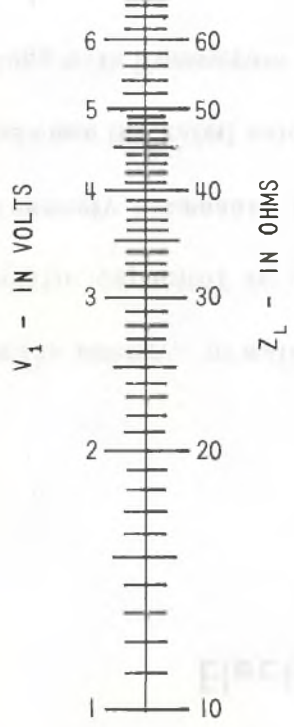**Example:** In the test of an audio output transformer primary, find the impedance where  $R_1 = 8$  ohms,  $V_1 = 12$  volts, and  $V_2 = .14$  volts.

**Solution:** (1) Draw a straight line from 12 on the  $V_1$  scale to .14 on the  $V_2$  scale. (2) Draw a second line from 8 on the  $R_1$  scale through the point where the first line crossed the pivot line and extend it to the  $Z_L$  scale. Read 680 ohms on the  $Z_L$  scale. This is the impedance. (The answer is within slide rule accuracy.)



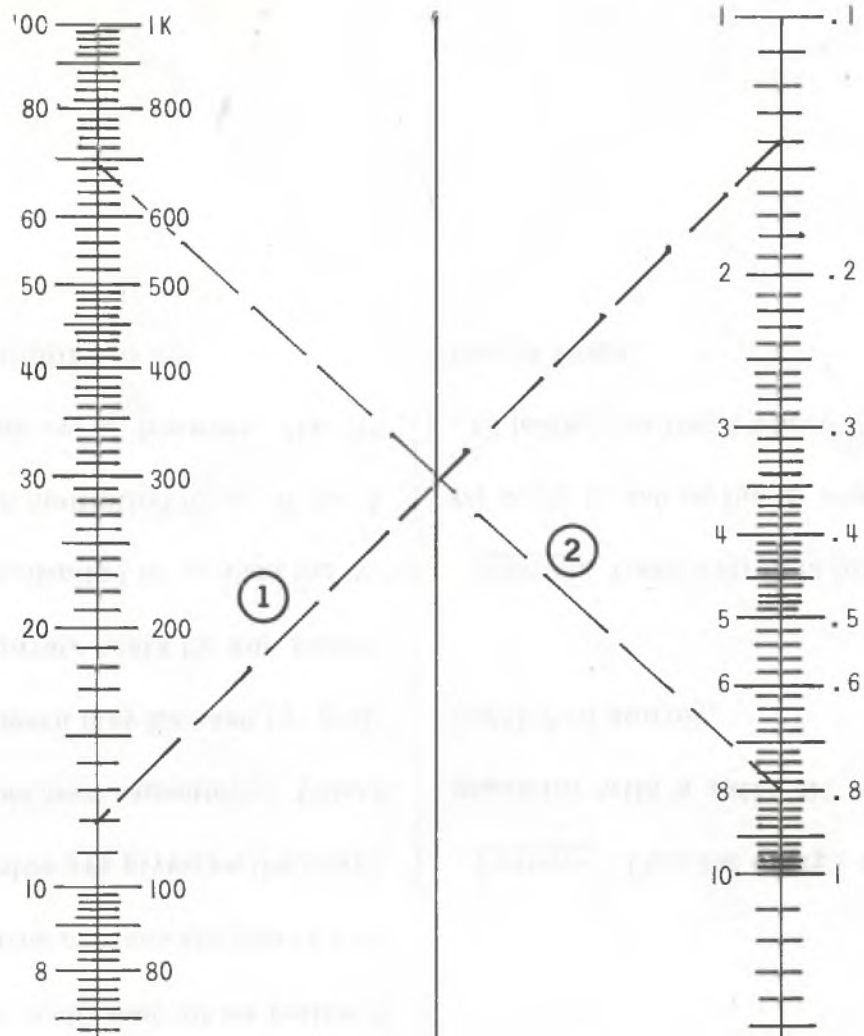

# Electrolytic Energy Storage

To determine the energy, in watt-seconds, that an electrolytic capacitor is capable of storing, it is merely necessary to draw a straight line between the rated values of capacity and voltage with Nomogram 4-6. The energy storage in watt-seconds or joules is found where this line crosses the center column. Several scales are given on the chart, which should include most capacitors. Values other than those shown may be used by multiplying the appropriate scale by any factor. If the C scale is multiplied by  $n$ , then the WS scale must also be multiplied by  $n$ . If the E scale is multiplied by  $n$ , however, the WS scale must be multiplied by  $n^2$ .

## Scale Combinations

(a) (c) (g)

(b) (c) (f)


(a) (d) (f)

(b) (e) (g)

Example: Find the energy an 8-microfarad capacitor with a rated DC voltage of 350 is capable of storing.

Solution: Draw a straight line from 8 on the (a) scale to 350 on the (g) scale. The answer, .49 joules, is found where this line crosses the (c) scale.


C - CAPACITY IN MICROFARADS

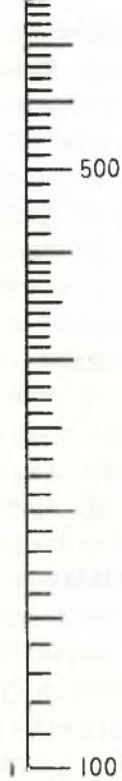

(a)

(b)

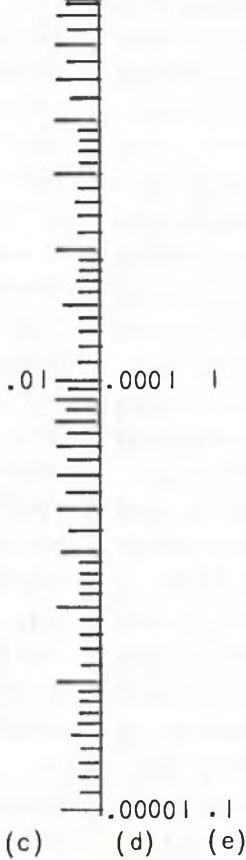WS - ENERGY STORAGE IN WATT/SECONDS OR JOULES




(c)

(d)


(e)

E - DC VOLTS

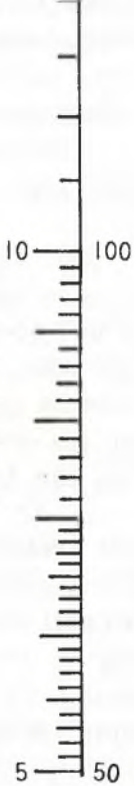

(f)

(g)

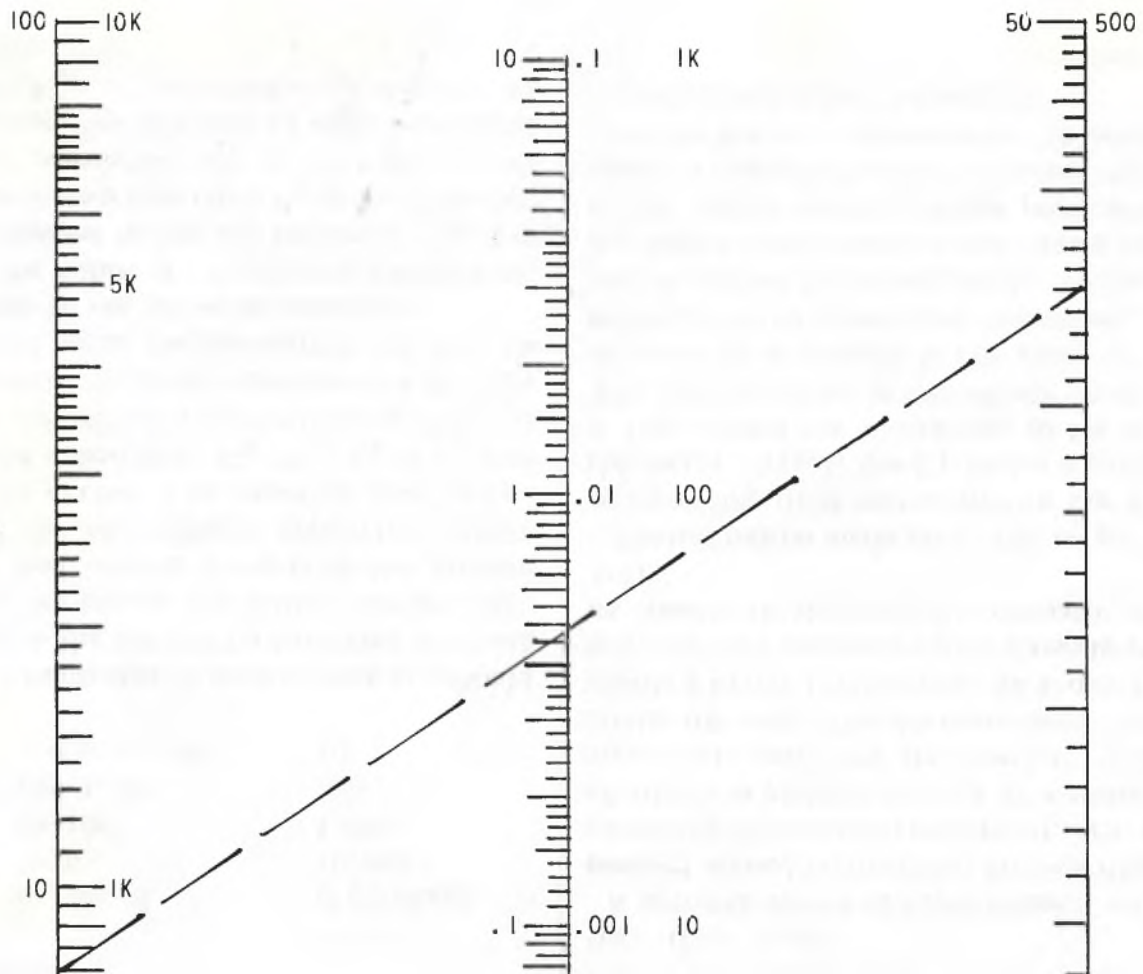

# Capacitance Measurement

This capacitance test will find its maximum usefulness when applied to incoming inspection testing of electrolytics.

Fig. 4-2 shows the basic circuit of the tester. An AC voltage, equal to the product of the nominal rated AC ripple current and the approximate reactance resulting from the sum of the reactances of the capacitors at 60 Hz, is applied to the circuit. (In most cases approximately 30 volts rms may be used. Slightly higher voltage may be used for large values of capacitance.)  $E_{DC}$  is a polarizing potential equal to the rated DC working voltage of the unknown capacitor ( $C_X$ ). This potential is applied across  $C_X$  through the series resistor  $R$  to prevent  $C_X$  from being shorted by the DC supply.  $R$  should have a value of about 20 times the reactance at 60 Hz. The limiting factor in determining the maximum value of  $R$  is the capacitor charging time, which should be short for rapid testing. The following chart shows some suggested values of resistance for various ranges of capacitance:

$C_X$ (in $\mu f$ )	$R$ (in ohms)
1-10	10,000
10-100	1,000
100-1,000	100
1,000-10,000	10

$C_K$  is a capacitor of known value and should be close to the value of  $C_X$  for more accurate results. By taking the ratio of the two capacitors and setting it equal to the inverse ratio of the AC voltages appearing across them, we arrive at an equation from which  $C_X$  can be calculated.  $C_X/C_K = E_K/E_X$ . The task of calculating  $C_X$  can be done quickly and conveniently by using Nomogram 4-7. The method of using the nomogram can best be described by the following example:

Find the value of an unknown electrolytic ( $C_X$ ) measured in the test fixture of Fig. 4-3 when the known capacitor  $C_K$  is 10  $\mu f$  the AC voltages measured are 9 volts across the known capacitor ( $E_K$ ) and 11 volts across the unknown ( $E_X$ ). The solution is obtained in two steps.

(1) Align a straight-edge from 9 on the  $E_K$  scale to 11 on the  $E_X$  scale, and

(2) Align a straight-edge from 10 on the  $C_K$  scale and the point where the straight-edge crosses the pivot line in step 1. Extend this line. The answer, 8.2  $\mu f$ , can be found on the  $C_X$  scale where the second line crosses it. For higher values of capacitance than those shown on the scales, merely multiply both  $C$  scales by  $10^n$ .

The need for calculation of  $C_X$  can be eliminated and the value can be read off directly from the meter in the following manner:

(1) Adjust the AC input voltage until  $E_X$  appearing across  $C_X$  is equal to  $C_K$  in microfarads. Whether  $E_X$  is in volts or millivolts doesn't matter, as long as  $E_X$  and  $E_K$  are both in the same unit.

(2) Read  $E_K$  across  $C_K$ . This value in volts is equal to  $C_X$  in microfarads.

When it is necessary to measure large quantities of electrolytic capacitors, as in the case of incoming inspection departments, a test fixture can be constructed for rapid testing. (Fig. 4-3.)

A suitable means of rapid connect and disconnect should be provided for inserting and removing the capacitor under test. The meter should be a reliable type of AC vacuum-tube voltmeter, such as the Hewlett - Packard Model HP 400. The decision must be made whether to use two meters, as shown in Fig. 4-3, or only one meter with a toggle switch, as shown in the partial schematic of Fig. 4-2B.

The test can be made on a "go/ no go" basis by providing limit indications on the face of the meter. First, the  $E_X$  meter should have a line drawn on it parallel to the needle. This line should be on the voltage point which is equal in magnitude to the value of  $C_K$  in microfarads as previously described. This can be called the set-up point. Second, the  $E_K$  meter should have a line drawn parallel to the needle at the voltage point which is equal in magnitude to the minimum value acceptable for  $C_X$ . Another can be added for the maximum value if specified.

(Continued below)

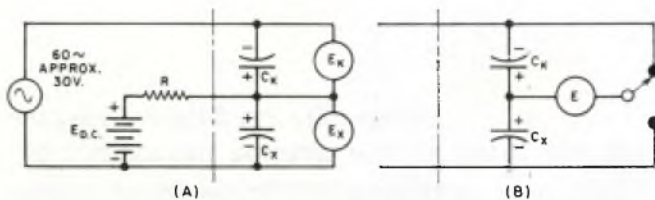
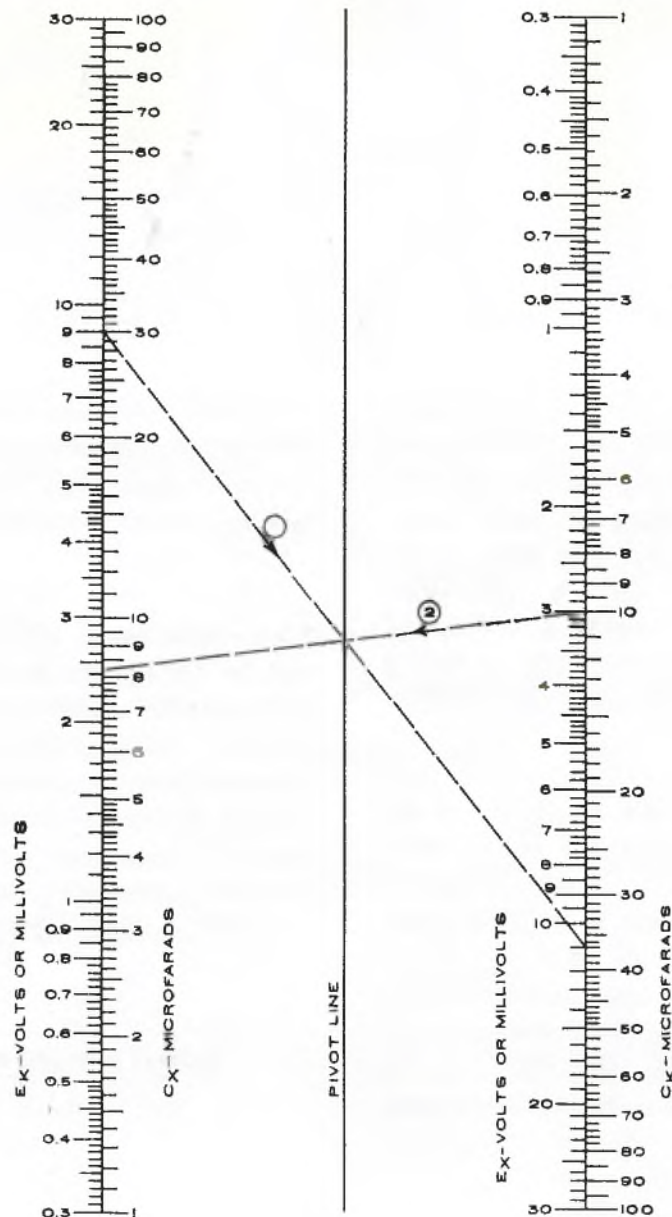


Fig. 4-2. (A) Basic circuit and (B) meter-switching arrangement.

The test for each capacitor can now be made in a matter of seconds by using the following procedure:

- (1) Insert the capacitor into its holder, observing the proper polarity.
- (2) Turn the "on-off" switch to its "on" position.
- (3) Adjust the variable transformer until the needle on the  $E_X$  meter comes to the set-up mark.
- (4) Observe the position of the needle on the  $E_K$  meter. It should fall on or between the two limit marks. If not, reject the capacitor.
- (5) Turn the "on-off" switch to the "off" position.
- (6) Remove the capacitor.

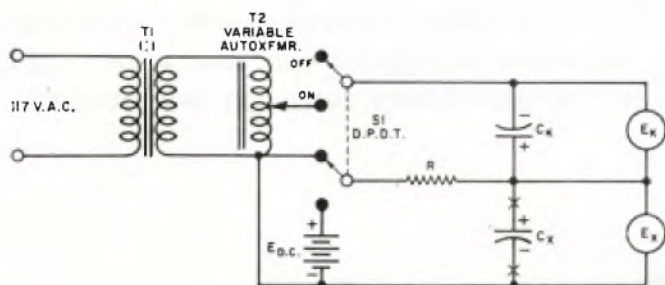


Fig. 4-3. Circuit diagram of the electrolytic test fixture.



# AC Motor-Starting Capacitance Chart

Commercial DC filter electrolytic capacitor testers are not capable of accurately checking AC motor-starting capacitors. This test should be made under simulated actual working conditions. In other words, they should be tested at line voltage by measuring the impressed voltage across them and the current passing through them.

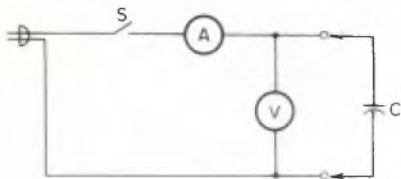


Fig. 4-4. Capacitor test circuit.

Fig. 4-4 shows the circuit for the suggested test. The switch should be of the thermal type that will release itself in case of a short. To obtain accuracy of less than one microfarad, care should be taken in the selection of the voltmeter and the ammeter. It is also recommended that the unit under test be maintained at a temperature of 25° C for two hours just prior to testing. Proceed with the test as follows:


- (1) Connect the capacitor to the test leads.
- (2) Throw the switch to the "on" position. Do not allow the capacitor to remain connected for more than 5 seconds.

- (3) Record the readings taken from the ammeter and voltmeter during the 5-second period.
- (4) Throw the switch to the "off" position and compute the capacity from the formula:  $C = I \times 2,654/\text{volts}$ .

The capacity is rapidly computed with the use of the nomogram by merely extending a straight-edge through the recorded values of current and voltage on their respective scales. The value of capacity is found on the appropriate capacity scale where this line crosses it. Several scales are given for current and capacity and the proper scale combinations to be used are shown on the nomogram. Values other than those shown on the various scales may be used merely by multiplying the desired scale by  $n$ . If current scales are multiplied by  $n$ , capacity scales must also be multiplied by  $n$ . If voltage scales are multiplied by  $n$ , capacity scales must be divided by  $n$ .  $n$  may be any number, either whole or fraction.

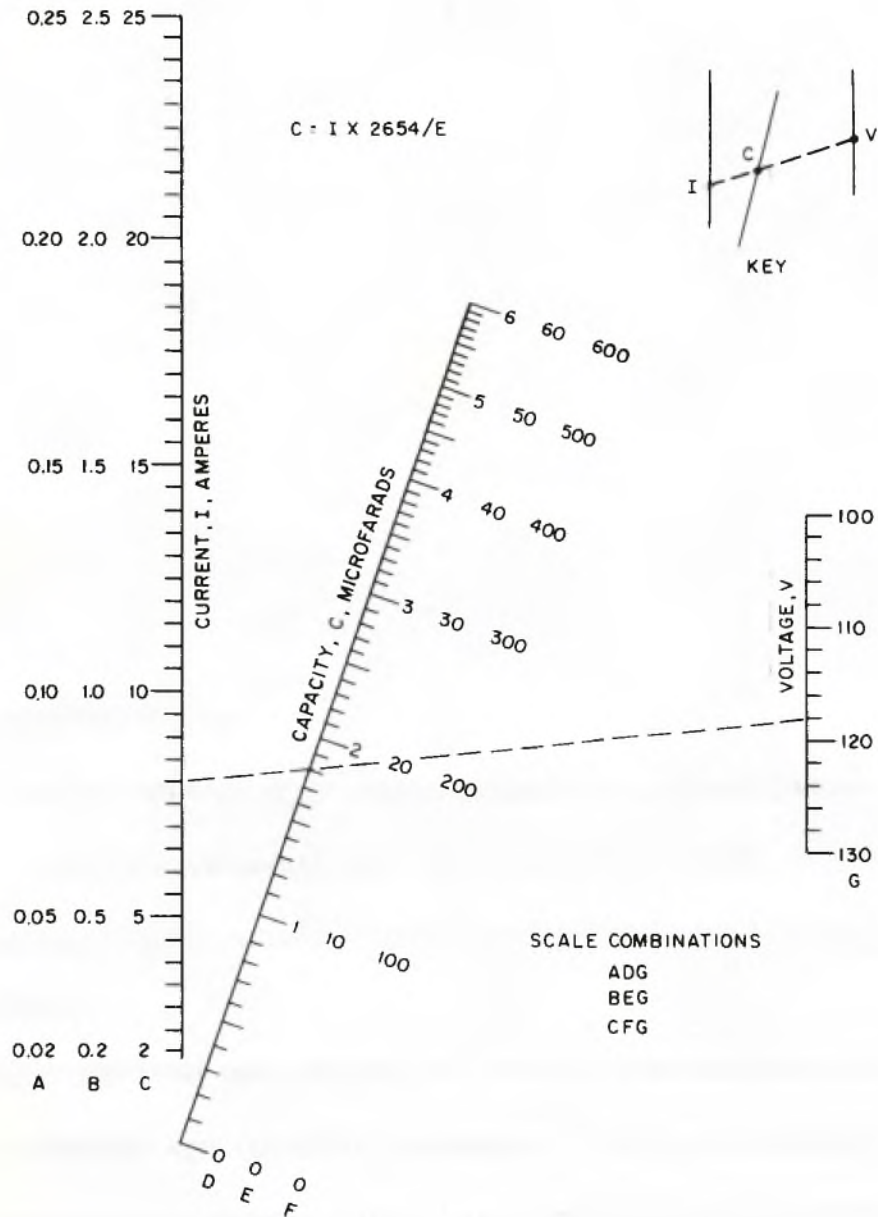Example: Determine the capacity of a unit tested as described above where the current reading is 8 amperes and the voltage is 118.

Solution: Extend a straight-edge from 8 on the C scale of the left-hand column to 118 of the G scale on the right-hand column. The answer, 180 microfarads, is found where this line crosses the F scale of the diagonal column.




## Capacitor Temperature Coefficient

The temperature coefficient of a capacitor is related to its temperature stability. That is, it is a measurement of change in capacity with change in temperature. For this nomogram it is assumed that the test was made at room temperature ( $25^{\circ}\text{C}$ ).

In the example illustrated by the dashed line, there is a  $40^{\circ}$  change in temperature from  $25^{\circ}\text{C}$  for an 8% capacity change from its value at  $25^{\circ}\text{C}$ , which results in a temperature coefficient of 2,000.

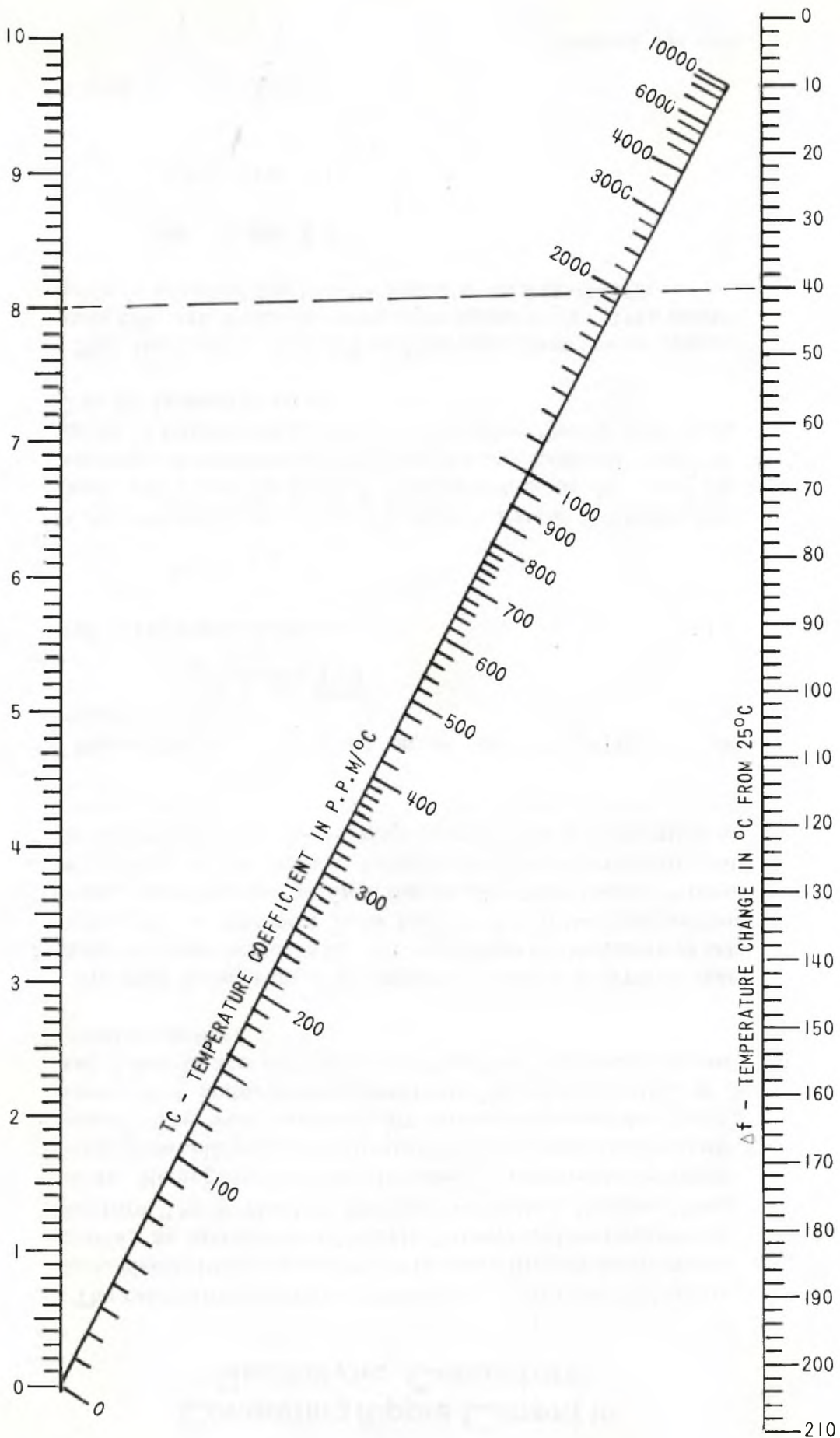$\Delta C$  - % CHANGE OF CAPACITY FROM VALUE @ 25° C



## Computing Ripple Current in Electrolytic Capacitors

The calculation of ripple current in a polarized DC aluminum electrolytic capacitor can be simplified by using nomograms, as discussed in "Ripple Current in Electrolytic Capacitors," by J. Meek in *Electro-Technology* (January 1964, p104). Nomogram 4-10 can be used to determine the maximum allowable power dissipation  $W$  within the capacitor container. The basic equation for the nomogram is  $W = 2A/T$ , where  $T$  is ambient temperature in  $^{\circ}\text{C}$ ,  $A = 2\pi r(L + r)$ , and  $r$  and  $L$  are the radius and length of the capacitor container in inches.

To read Nomogram 4-10 properly, extend a straight line from the point on scale  $L$ , corresponding to the length of the container, to intersect pivot line  $P$ . From the intersection point, extend another straight line to the point of scale  $T$  corresponding to the ambient temperature. The intersection of the line with scale  $W$  is the maximum allowable dissipation in watts.

Nomogram 4-11 is based on an equation in MIL-C-62B where:

$$I_{ma} = 0.003 \sqrt{CV}$$

and on the power formula:

$$W_{dc} = I_{ma} V$$

It can be used to determine DC watts. Extend a straight line from the point on scale  $A$  corresponding to the rated DC working volts to the point on scale  $D$  corresponding to the capacity in microfarads. The intersection of the line with scale  $C$  is the leakage current.


The dissipation factor  $DF$  and the equivalent series resistance  $ESR$  are found by using Nomogram 4-12. This nomogram is based on the 120-Hz formulas in MIL-C-62B:

$$DF = 0.006 \sqrt{C}$$

$$ESR = 1326 DF/C$$

Where:  $C$  is in microfarads.

*(Continued on next page)*

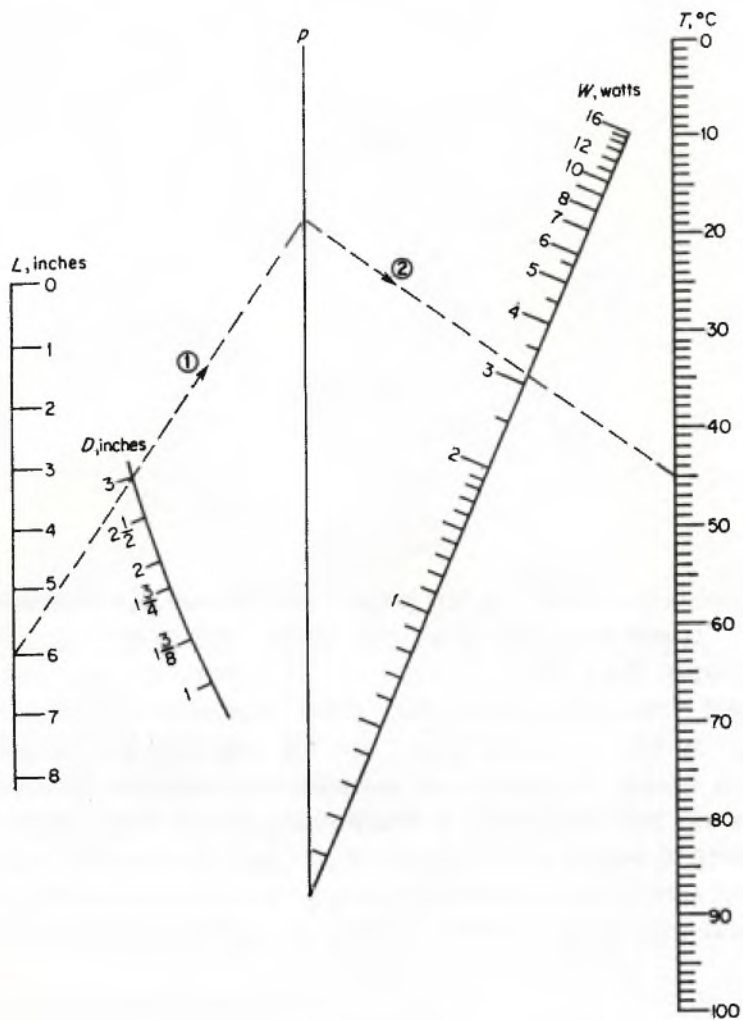


Nomogram 4-10


The procedure for using the nomogram depends on the value of the capacitor. If the capacitance is less than 1,000  $\mu\text{f}$ , extend a straight line from the point on scale  $C_B$ , corresponding to the capacitance, to point B on scale  $DF_R$ . The intersection of the line with scale  $ESR_B$  is the equivalent series resistance.

If the capacitance is greater than 1,000  $\mu\text{f}$ , locate its value on scale  $C_A$ . This point also corresponds to the dissipation factor on the adjacent scale  $DF_L$ . Extend a straight line from the capacitance value on  $C_A$  to the point on scale  $DF_R$  that corresponds to the value of dissipation factor found on scale  $DF_L$ . The intersection of the line with scale  $ESR_A$  is the equivalent series resistance.

Consider the example in Meek's article: A 90,000-microfarad capacitor rated at 10 working volts DC is to be subjected to an ambient of  $45^\circ\text{C}$ . The container is 3 inches in diameter x 6 inches long. From Nomogram 4-10 we find that the maximum allowable power dissipation is 3.18 watts. From Nomogram 4-11 we find that  $W_{dc}$  is 0.029 watts. Then  $W - W_{dc} = W_{ac} = 3.151$  allowable watts. In Nomogram 4-12, the line from 90,000 on scale  $C_A$  to 1.8 on scale  $DF_R$  intersects scale  $ESR_A$  at 0.026. Since we know the ESR and  $W_{ac}$ , we can use Meek's nomogram to find the AC ripple current.

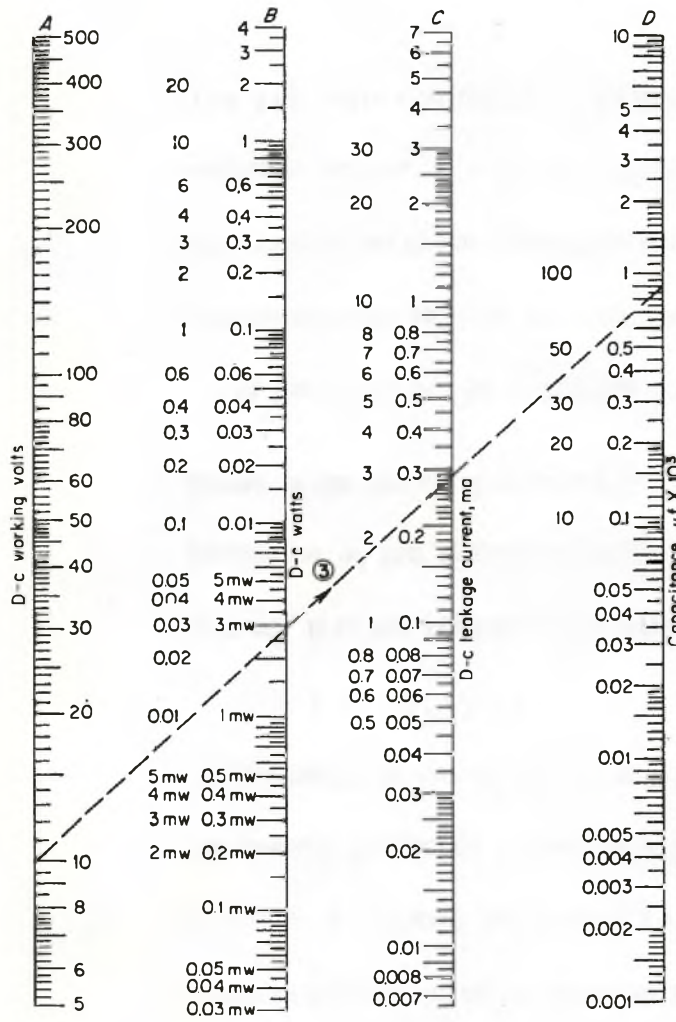

Nomogram 4-11

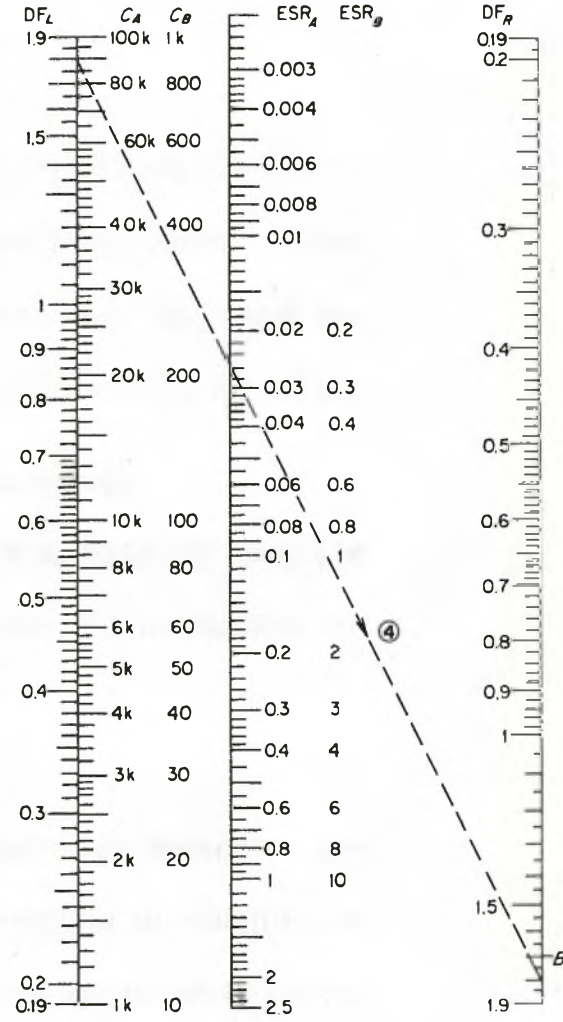

Nomogram 4-12



## Bypass Capacitor Determination

Though Nomogram 4-13 is based on an equation derived originally for use in vacuum-tube audio amplifier design, it is useful in many bypass applications. A prime use of the nomogram is to determine the nominal value of capacitance needed to bypass a cathode (or emitter) resistor of an amplifier so the lowest frequency to be down 3 db can be specified. The nomogram is based on the equation:

$$C = 10^7 / 2\pi fR$$

Where: R is the resistor to be bypassed, C is the nominal capacitance of the bypass capacitor in microfarads, and f in Hertz is the lowest frequency to be bypassed.

C is found simply by extending a straight-edge from f in the left-hand scale to R in the right-hand scale, and noting the intersection with the capacitance scale in the center. In the example shown, f is 60 Hz, R is 180 ohms, and C is 146  $\mu$ f. The AHI scale combination is used.

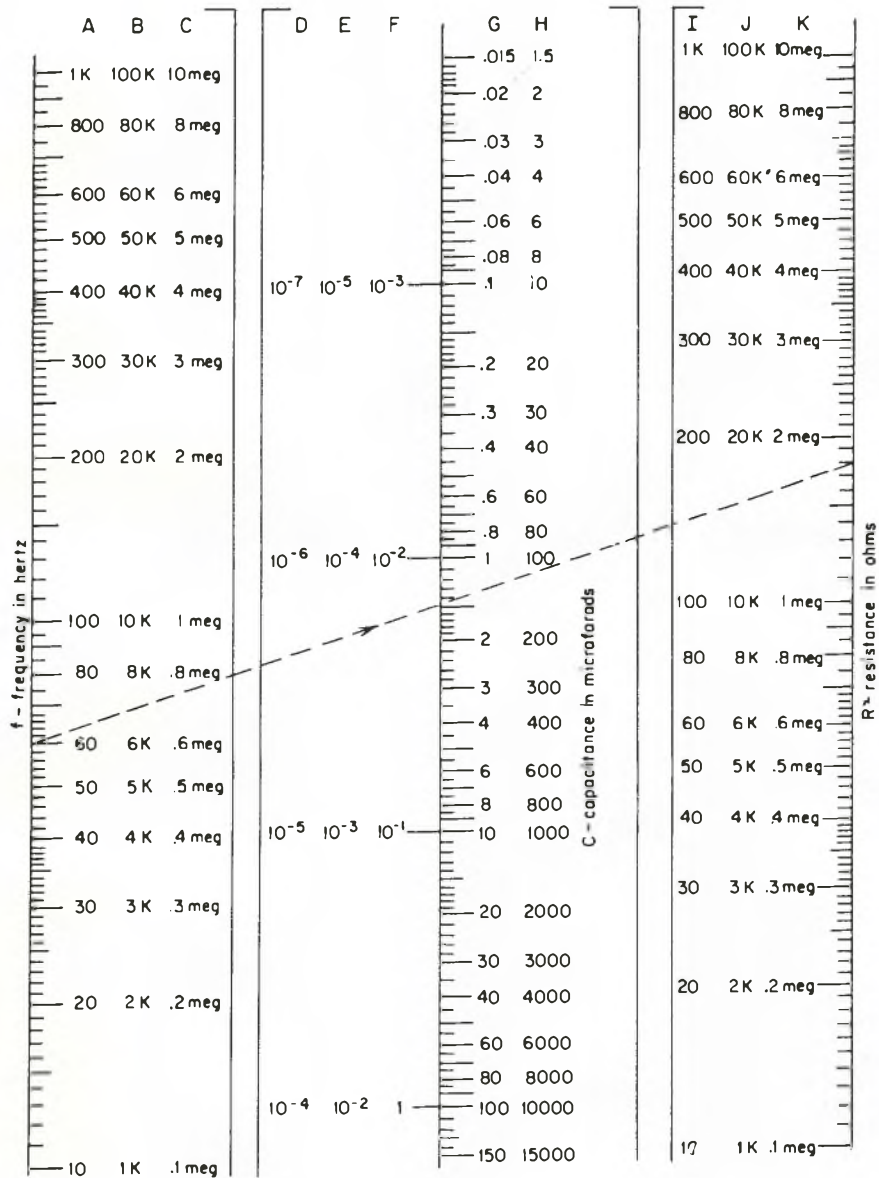


Chart of Scale Combination

AFK	BEK	CDK
AGJ	BFJ	CEJ
AHI	BGI	CFI

CHAPTER 5

**Vacuum Tubes  
and  
Transistors**

# R-C Coupled Amplifier Analysis

These nomograms will be found, by engineers and technicians alike, to be of time-saving value in the analysis and design of R-C coupled amplifiers. They do not eliminate the trial and error method normally encountered in such designs, but they do eliminate the calculation of many equations which are tedious and repetitious. Although they are based on vacuum tube design, many analogies and direct applications can be made to transistor circuitry.

Fig. 5-1(a) is a schematic of a simple triode R-C coupled amplifier, and Fig. 5-1(b)


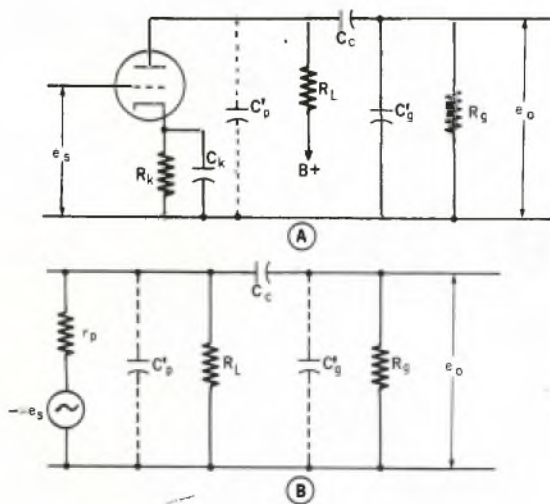


Fig. 5-1. (a) Triode R-C coupled amplifier.  
(b) Equivalent circuit of a.

is its equivalent circuit from which we may more readily analyze the amplifier. From Thevenin's theorem the tube was replaced by an AC voltage source with an output equal to  $\mu$  (the amplification factor) times the input signal  $e_s$ . The AC plate resistance of the tube,  $r_p$ , is shown in series with the signal source. The amplified signal voltage is developed across  $R_L$ , the plate load resistor of the triode stage. This signal is in turn coupled through  $C_c$  to the grid of the following stage. Grid leak resistor  $R_g$  of the following stage is included, since the output voltage  $e_o$  appears across it.  $C'_p$  is the output shunt capacitance of the tube under analysis and includes  $C_{pk}$  (the plate-to-cathode inter-electrode capacitance) plus stray wiring capacitances.  $C'_g$  is the input shunt capacitance of the tube of the following stage. If the voltage is being delivered to a pentode,  $C'_g$  is equal to the sum of  $C_{gk}$  (grid-to-cath-

(Continued on next page)

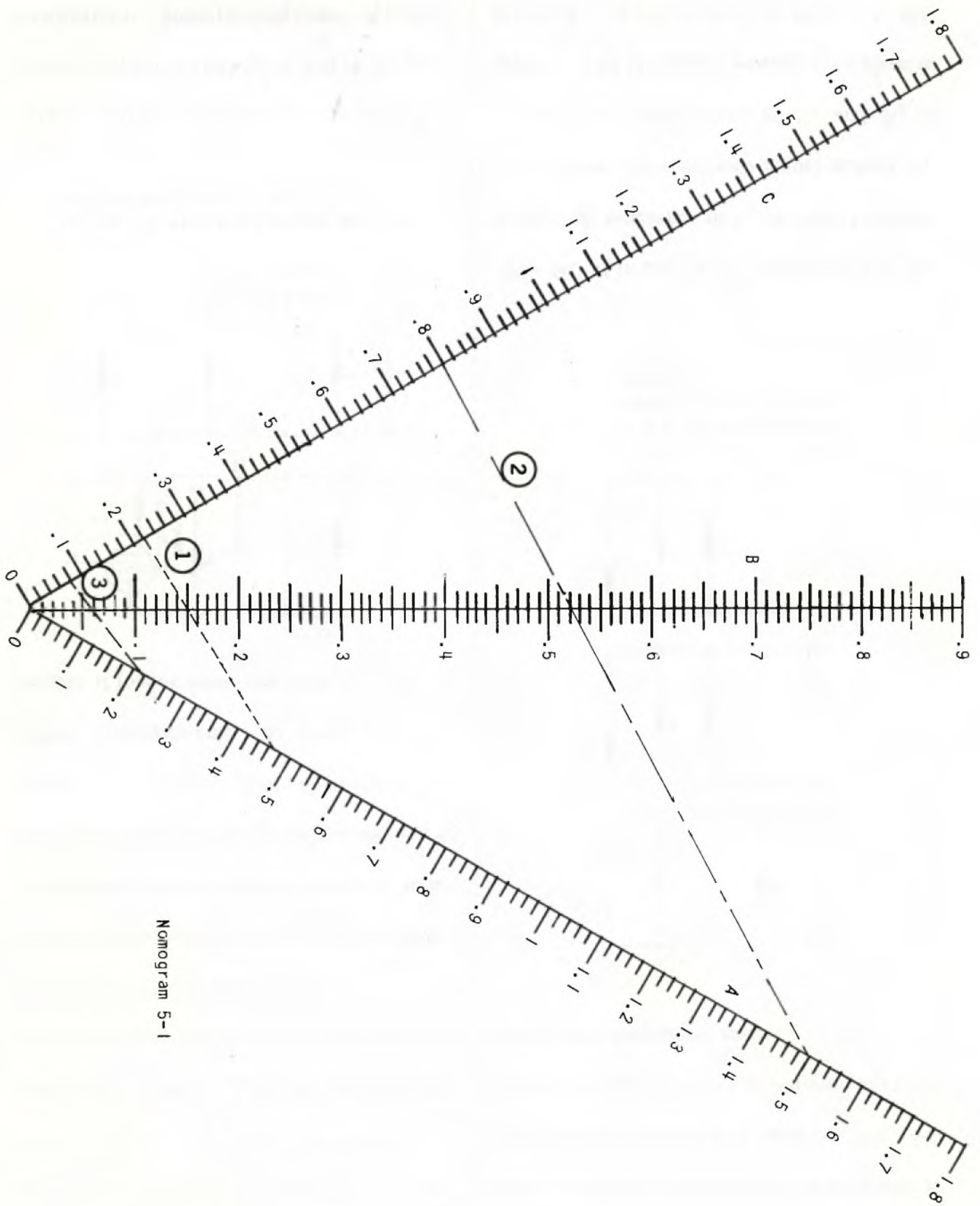

Nomogram 5-1

ode capacitance),  $C_{gs}$  (grid-to screen capacitance), and stray wire capacitances. If the voltage is being delivered to a triode, then  $C'_g = C_{gk} + C_{gp}(1+A) + \text{stray wire capacitances}$ , where  $C_{gp}$  is the grid-to plate capacitance and  $A$  is the gain of the stage and will normally be at least  $1/2$  times  $\mu$ . The interelectrode capacitances are built into the tube and we have no control over them. However, the stray wiring capacitances can be kept down to between 4 and 10 picofarads by careful arrangement. (It could be much greater if longer leads are used.)

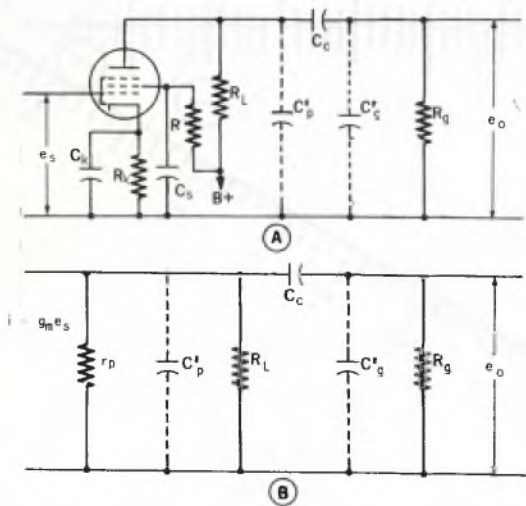


Fig. 5-2. (a) Pentode R-C coupled amplifier. (b) Equivalent circuit of a.

Fig. 5-2(a) is a schematic of a pentode R-C coupled amplifier and Fig. 5-2(b) is its equivalent circuit. Since pentode tubes have higher plate resistance and amplification factors

it is simpler to use the constant-current generator form, while the constant-voltage generator is more convenient to use for triodes. For simplification of this analysis, Fig. 5-3 shows the equivalent circuit broken down for the various frequency ranges.


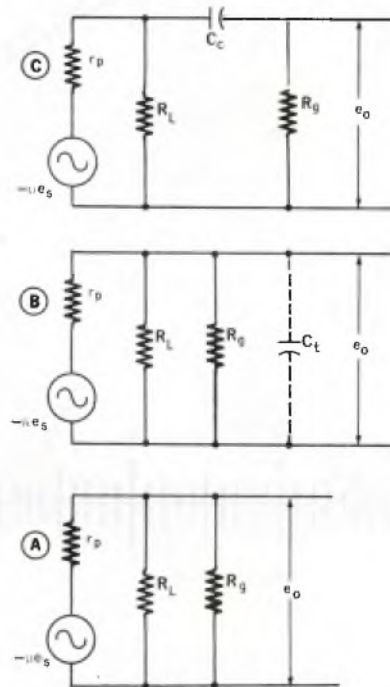


Fig. 5-3. (a) Mid-frequency. (b) High-frequency. (c) Low-frequency.

The falloff in gain at low frequencies is due to the high reactance of  $C_c$  at these frequencies. Since the developed signal across  $R_L$  is fed to the combination of  $C_c$  and  $R_g$  in series, with the output voltage  $e_o$  appearing across  $R_g$ , it can be seen in Fig. 5-4 that

(Continued on next page)

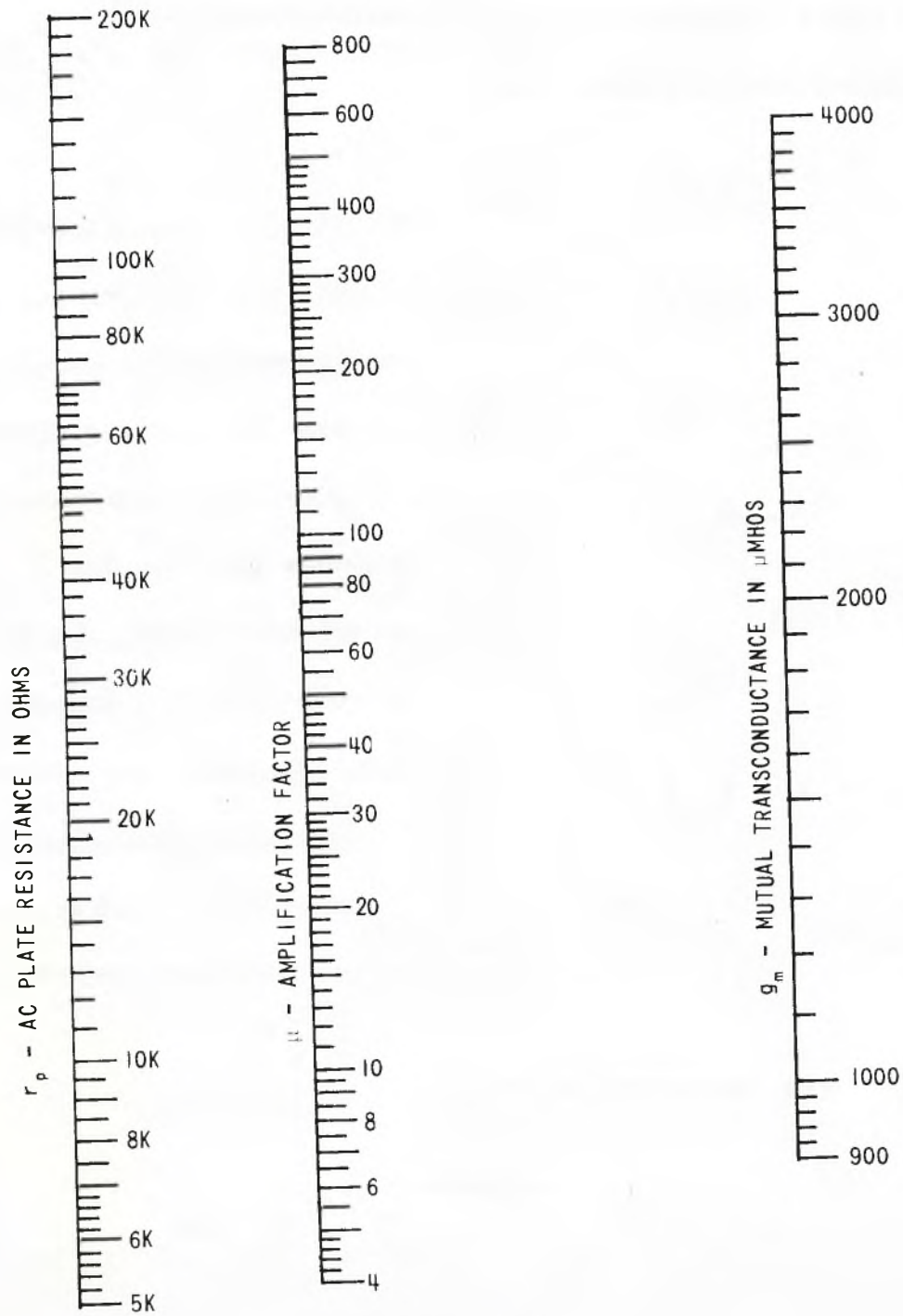

Nomogram 5-2

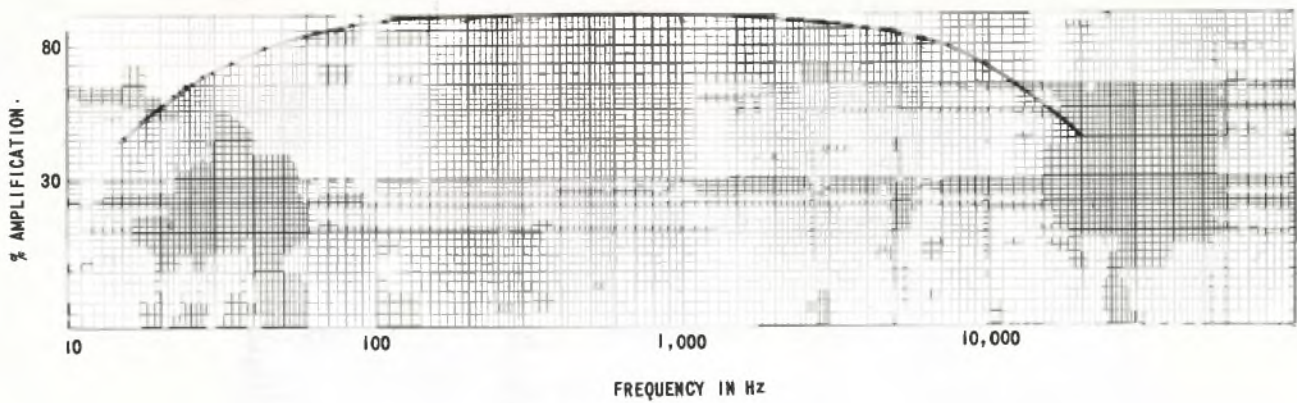


Fig. 5-4. Typical response curve of a pentode R-C coupled amplifier.

the larger  $X_c$  becomes, the smaller  $e_o$  will be. The fall-off in gain at high frequencies is due to the lumped shunt capacitance, previously discussed, which effectively shunts  $R_g$ , thereby lowering the effective load impedance. At the mid-frequency range the reactance of  $C_c$  is very small with respect to  $R_g$  and may be considered to be a short circuit. The reactance of  $C_t$  is very high with respect to  $R_g$  and may be considered to be an open circuit. The stage gain  $A$  is given for the various frequency ranges by the following equations:

$$(1) \quad A_m = \mu R / (R + r_p) \quad \text{Medium frequencies for triode amplifiers}$$

$$(2) \quad A_m = g_m r \quad \text{Medium frequencies for pentode amplifiers}$$

$$(3) \quad A_h = \frac{A_m}{\sqrt{1 + (r/X_t)^2}} \quad \text{High frequencies for both amplifiers}$$

$$(4) \quad A_L = \frac{A_m}{\sqrt{1 + (X_c/\rho)^2}} \quad \text{Low frequencies for both amplifiers}$$

$$(5) \quad \text{Where: } R = R_L R_g / (R_L + R_g)$$

$$(6) \quad r = R r_p / (R + r_p) \\ = r_p R_L R_g / (r_p R_L + r_p R_g + R_L R_g)$$

$$(7) \quad \rho = R_g + \frac{R_L r_p}{R_L + r_p}$$

$$(8) \quad X_t = 1 / (\omega C_t)$$

$$(9) \quad C_t = C'_p + C'_g$$


$$(10) \quad X_c = 1 / (\omega C_c)$$

In the analysis of pentode amplifiers, where  $r_p$  is very much greater than  $R_L$  and  $R_g$ , it may be assumed that  $r = R_L$ , and  $A_m$  is approximately equal to  $g_m R_L$ . Only a very small error is introduced by this assumption.


(Continued on next page)



Nomogram 5-3

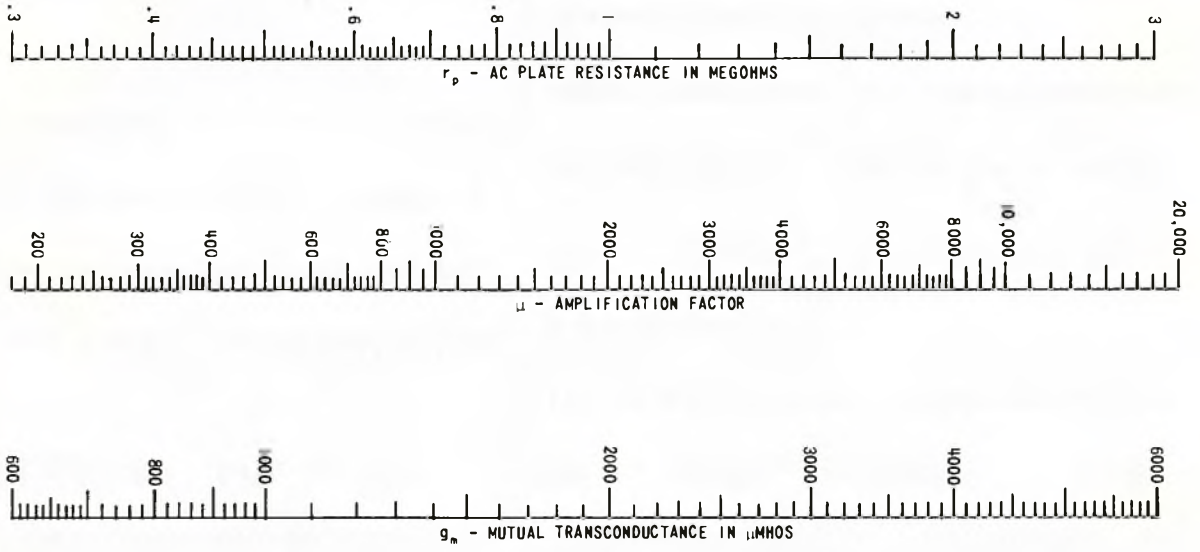

Nomogram 5-4

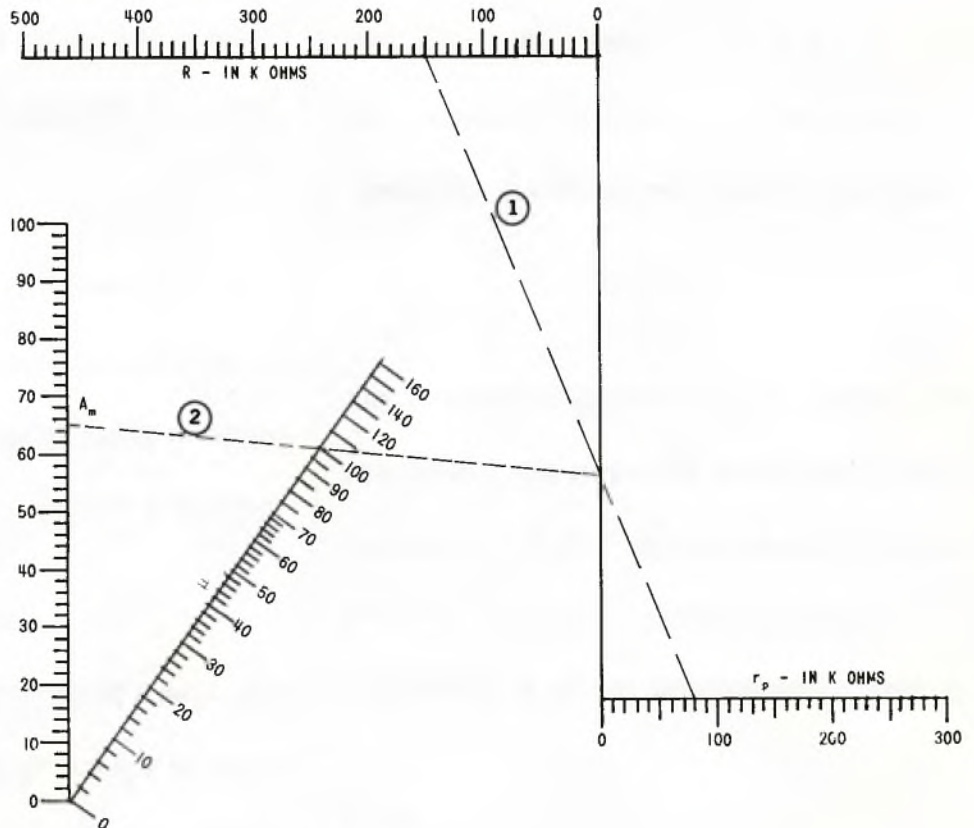

Nomogram 5-1 is for the solution of parallel resistors.

Equation (5) is solved by drawing a straight line through the values of  $R_L$  on the A scale and  $R_g$  on the C scale.  $R$  is found where this line intersects the B scale.

Equation (6) is solved by drawing a straight line through the values of  $R$  (as found in equation 1) on the A scale and  $r_p$  on the C scale.  $r$  is found where this line intersects the B scale.

Equation (7) is solved by drawing a straight line through the values of  $R_L$  on the A scale and  $r_p$  on the C scale. Mentally add the value of  $R_g$  to the value found where the line intersects the B scale. This is the value of  $\rho$ .

Nomograms 5-2 and 5-3 may be used to find the third tube characteristic when only two are given in the tube manual. Nomogram 5-2 is for triodes and Nomogram 5-3 is for pentodes.

Mid-frequency gain  $A_m$  is found in Nomogram 5-4 for triode amplifiers and in Nomogram 5-5 for pentode amplifiers.

High-frequency gain  $A_h$  is found in Nomograms 5-6A and 5-6B, while the low-frequency gain  $A_L$  is found in Nomograms 5-7A and 5-7B.

Example: Find the mid-frequency gain  $A_m$  and the 3 db falloff frequencies for the circuit of Fig. 5-1(a), where the tube used is a 12AV6 and the following stage uses a 50C5. The component values are  $R_L = 220K$ ,  $R_g = 470K$ , and  $C_c = .006$  mfd.




Solution: From the tube manual the following constants are found for the 12AV6:  $\mu = 100$ ,  $r_p = 80K$ , and  $C_{pk} = .8$  pf. For the 50C5:  $C_{gs} = 13$  pf and  $C_{gk} = 13$  pf.

Stray capacitance is estimated as 10 pf each for  $C'_g$  and  $C'_p$ ; therefore:  $C_t = .8 + 10 + 13 + 13 + 10 = 46.8$  pf. In Nomogram 5-1 we find the values of:

(a)  $R = R_L R_g / (R_L + R_g)$  as follows: Draw a straight line from 220K on the C scale to 470K on the A scale.  $R = 150K$  is found where this line crosses the B scale.

(b)  $r = R r_p / (R + r_p)$  as follows: Draw a straight line from 150K on the C scale to 80K

(Continued on next page)

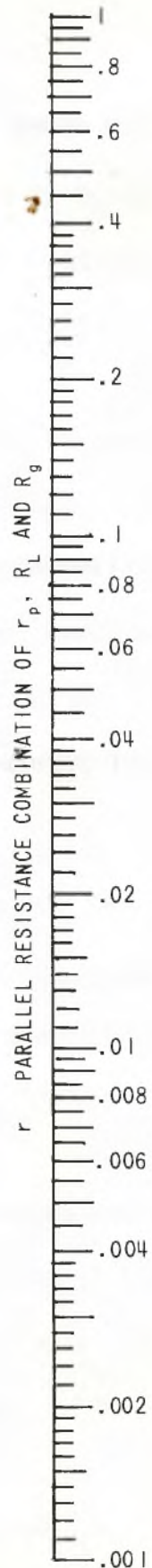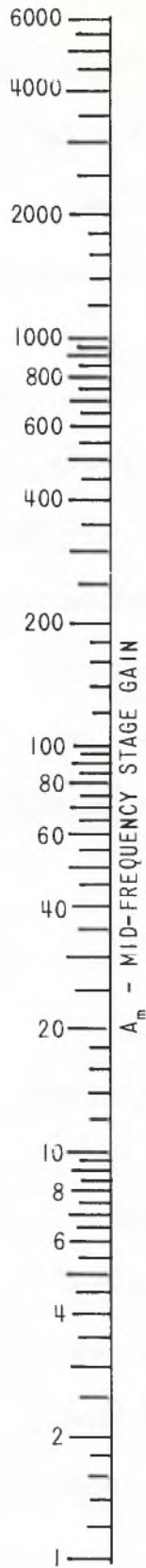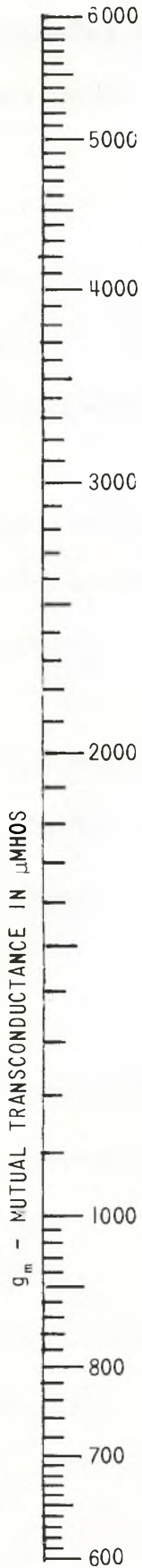

Nomogram 5-5

on the A scale.  $r = 52K$  is found where the line crosses the B scale.

(c)  $\rho = R_g + R_L r_p / (R_L + r_p)$  as follows:

Draw a straight line from 80K on the A scale to 220K on the C scale. Find 58K where this line crosses the B scale. Add to 470K and  $\rho = 525K$ .

In Nomogram 5-4 the mid-frequency gain  $A_m$  is found as follows: Draw a straight line from 150K on the R scale to 80K on the  $r_p$  scale. Now draw a straight line from the point where the first line crosses the pivot scale through 100 on the  $\mu$  scale.  $A_m = 65$  is found where this line crosses its scale.

In Nomogram 5-6A we can find the high frequency at which the gain falls off to 3 db below that of the mid-frequency gain.

Analyzing equation (3), it can be seen that when  $r = X_t$ ,  $\omega C_t r = 1$ , the ratio  $A_h/A_m$  is equal to .707 and  $A_h$  is 3 db down from  $A_m$ .

Draw a straight line from 46.8 on the  $C_t$  scale through 1 on the  $\omega C_t r$  scale. Draw a second line from the point where the first line

intersected the pivot line to 52K on the r scale.  $f_{3db} = 65$  kHz is found where the second line crossed the f scale.


In Nomogram 5-6B we find the gain at the 3 db frequency by drawing a straight line from 1 on the  $\omega C_t r_2$  scale to 65 on the  $A_m$  scale.  $A_h = 46$  is found where this line crosses the  $A_{h2}$  scale.

From equation (4) it can be seen that when  $\rho = X_c$ , the ratio  $A_L/A_m = .707$ , and  $A_L$  is 3 db down from  $A_m$ .


In Nomogram 5-7A draw a straight line from 520K on the  $\rho$  scale through 1 on the  $\omega c \rho$  scale. Now draw a straight line from the point where the first line intersected the pivot scale through .006 on the C scale.  $f_{3db} = 47$  Hz is found where this line intersects the f scale.

In Nomogram 5-7B draw a straight line from 1 on the  $\omega c \rho$  scale to 65 on the  $A_m$  scale.  $A_L = 46$  is found where this line crosses the  $A_{L2}$  scale.

Nomogram 5-6A

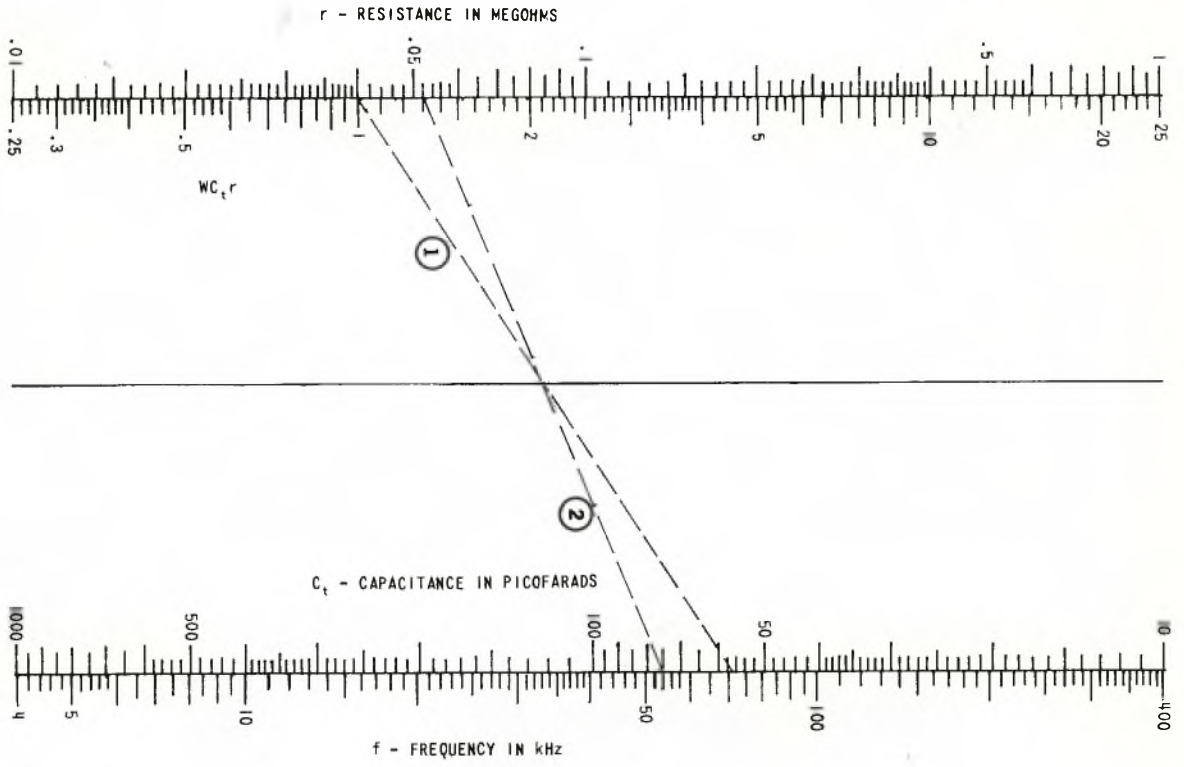



Nomogram 5-6B

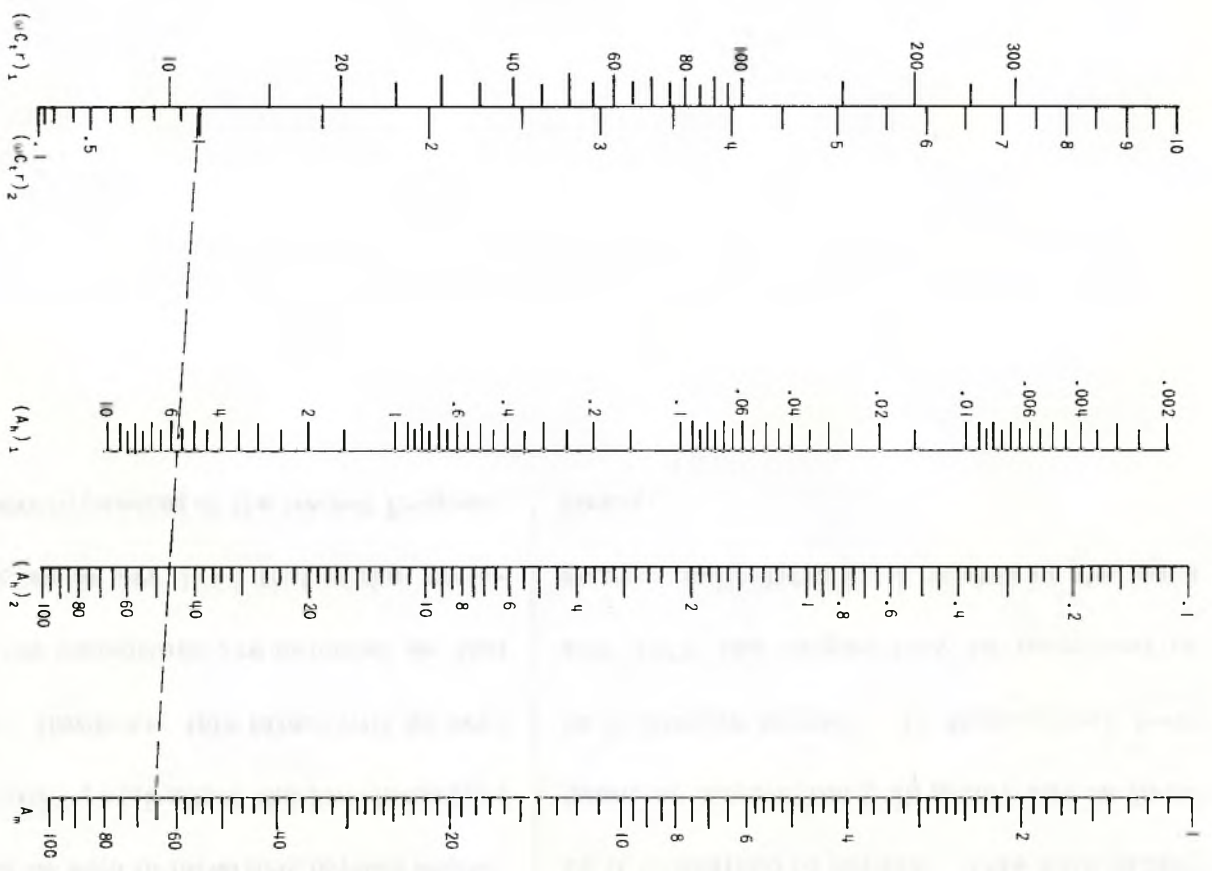

It should be kept in mind that bypass capacitors  $C_k$  and  $C_s$  will affect the low-frequency response. However, this effect will be negligible if the capacitors are selected so that their reactances are 1/10 that of the resistors they are bypassing at the lowest frequen-

cy it is desired to bypass. This gain at frequencies beyond the 3 db points can be found in a similar manner. In Nomograms 5-6B and 5-7B the ranges may be increased by merely multiplying all A scales by the same factor.

Nomogram 5-7A

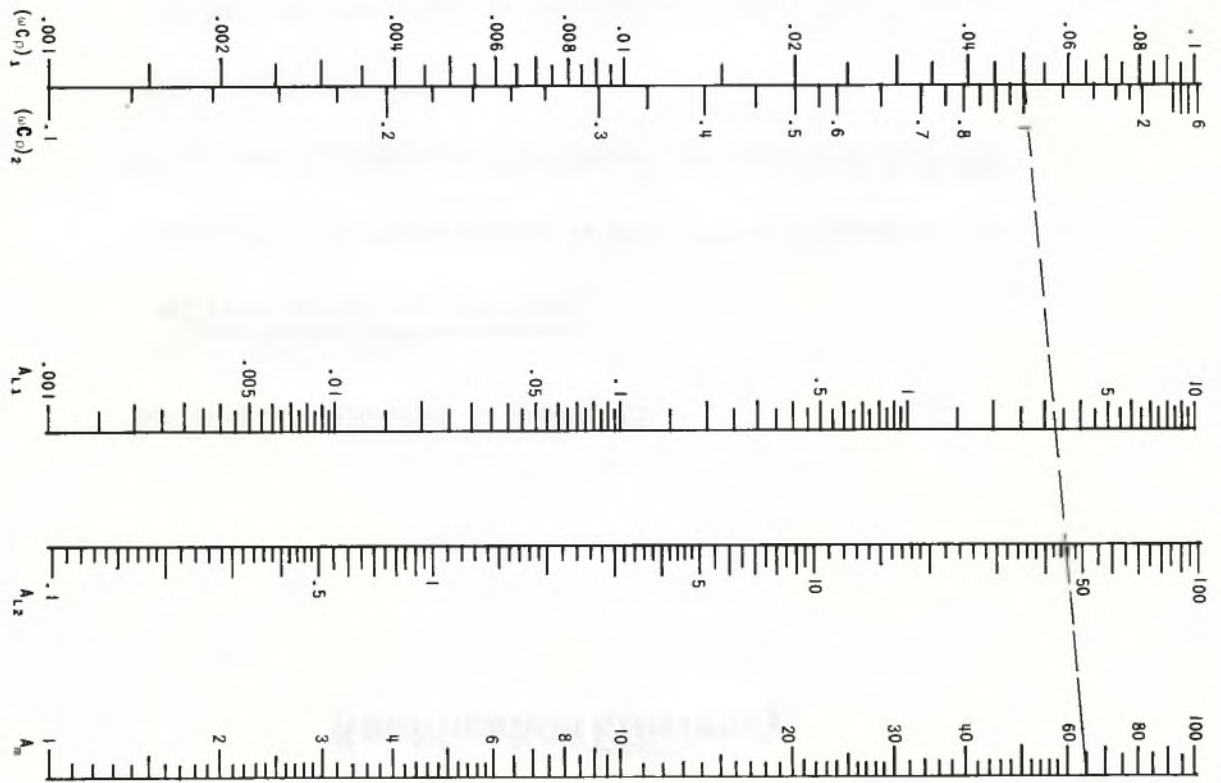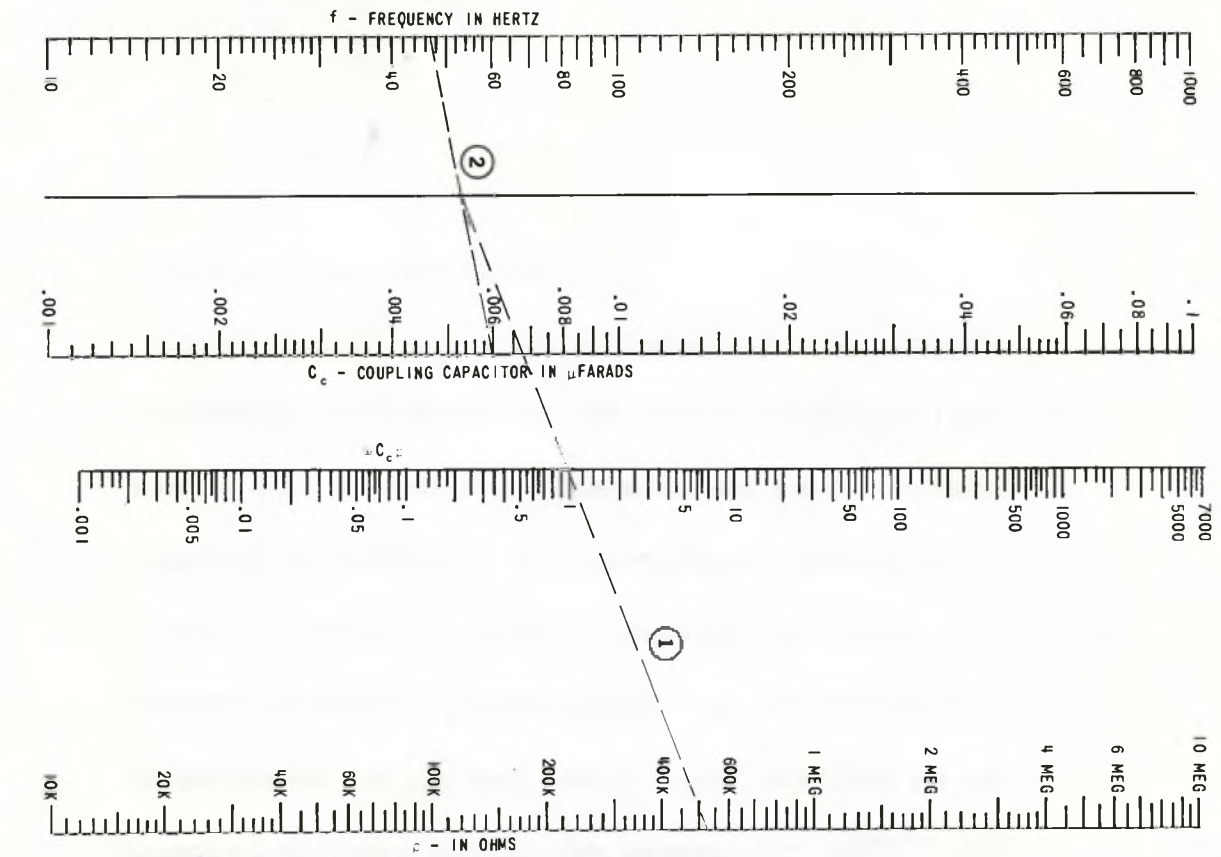

Nomogram 5-7B

## Rectification Efficiency


Rectification efficiency is defined as:

$$\frac{\text{DC output voltage}}{\sqrt{2} \text{ (rms supply voltage/plate)}}$$

Where: The DC output voltage is measured at the input to the filter, and the plate supply voltages are measured with the transformer unloaded.

To find the efficiency of the rectifier tube, it is merely necessary to draw a straight line between the values of DC output voltage and the rms supply voltage per plate on the appropriate scales in Nomogram 5-8. The rectification efficiency is found where this line intersects the center scale. This may be expressed in % if the efficiency scale is multiplied by 100. This equation is found on page 1 of 5 in Sylvania Engineering Data Service for the 5AS4A, dated April 1959. For other values, both voltage scales may be simultaneously multiplied by the same factor.



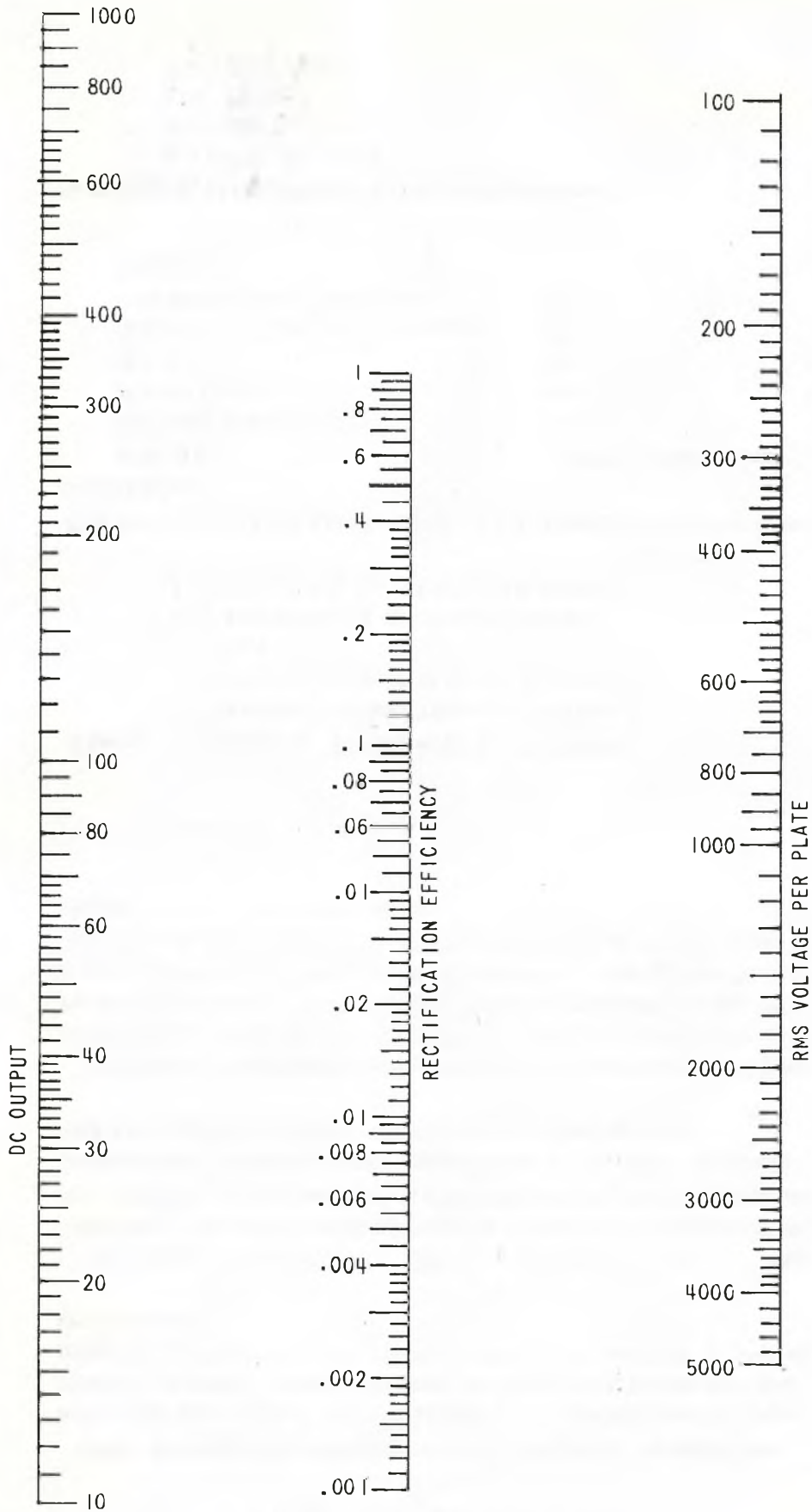

## Heat Sink Calculation

When the engineer designs a power amplifier he must consider the problem of "heat sinking" in the selection of transistors. In many cases, the cost of a heat sink could far surpass the savings obtained in the selection of certain types of transistors.

The power transistor is often mounted directly to the chassis. This allows heat from the transistor to transfer to the chassis. Heat transfer can be improved by using a metallic oxide-filled silicone grease which fills in the tiny scratches and air gaps between the case and mounting surface.

This topic is thoroughly covered by Wayne Goldman, of Wakefield Engineering Inc., in an article entitled "9 Ways to Improve Heat Sink Performance," which appeared in the October 1966 issue of Electronic Products. Nomogram 5-9 is based upon the equation for thermal resistance which appears in the article. The equation is:

$$\theta = \frac{\rho t}{A}$$

Where:  $\theta$  = thermal resistance in  $^{\circ}\text{C}/\text{watt}$   
 $\rho$  = specific thermal resistance of the interface material in  $^{\circ}\text{C inches}/\text{watt}$   
 $t$  = thickness of the film in inches  
 $A$  = area of the film in square inches

The following chart gives values of  $\rho$  for some commonly used materials:

Still Air	1200	$^{\circ}\text{C inches}/\text{watt}$
Silicone Grease	204	"
Mylar Film	236	"
Mica	66	"
Wakefield Type 120 Compound	56	"
Wakefield Delta Bond 152	47	"
Anodize	5.6	"


In the example illustrated by the dashed lines:


$$\rho = 56^{\circ}\text{C in.}/\text{watt}$$

$$t = .003 \text{ in.}$$

$$A = .75 \text{ in.}^2$$
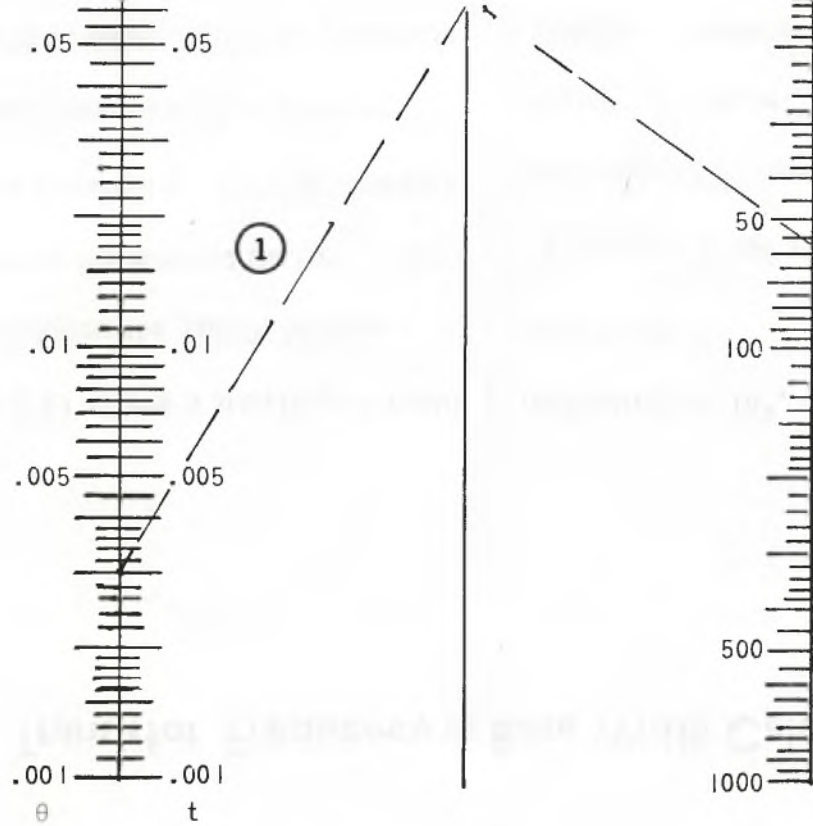
$$\theta = .25^{\circ}\text{C}/\text{watt}$$



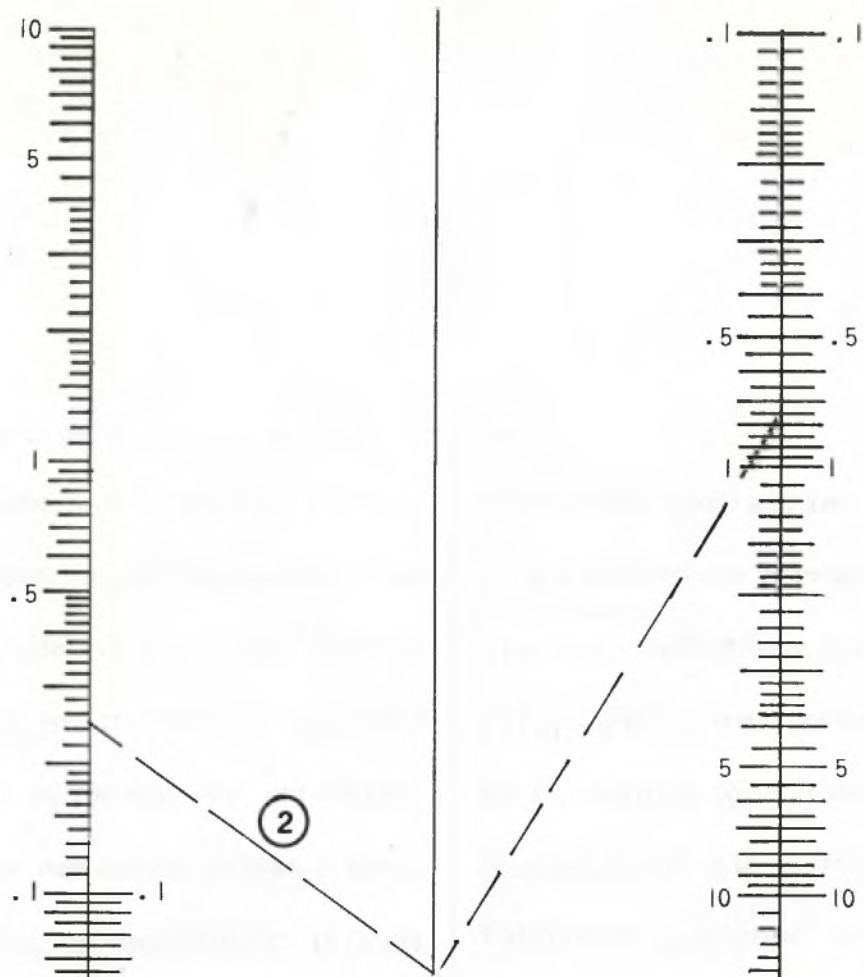

## Transistor Frequency vs Base Width Calculations

Nomogram 5-10 offers a simple and rapid means of calculating the cutoff frequency of a transistor when the width of the base region is known. The formula\* is:  $f_{\alpha} = C/W^2$ , where  $f_{\alpha}$  is the cutoff frequency,  $W$  is the width of the base region in mils, and  $C$  is a constant which was empirically determined. It is not the intent of this nomogram to give a theoretical analysis of the formula, but merely to provide a tool for its solution. Although the nomogram shows a base width range of .1 to 1 mils, other widths can be substituted by multiplying the  $W$  scale by  $10^n$ , where  $n$  may be negative or positive. When  $W$  is


multiplied by  $10^n$ , then  $f_{\alpha}$  must be multiplied by  $10^{-2n}$ .

Example: Find the cutoff frequency of a germanium NPN transistor whose base width region is 4.8 mils.

Solution: Extend a straight-edge from the germanium NPN point on the  $C$  scale to .48 on the  $W$  scale. The straight-edge will cross the  $f_{\alpha}$  scale at 25. Since  $W$  was multiplied by  $10^1$ , then  $f_{\alpha}$  must be multiplied by  $10^{-2}$ . The cutoff frequency is therefore .25 mHz.

---

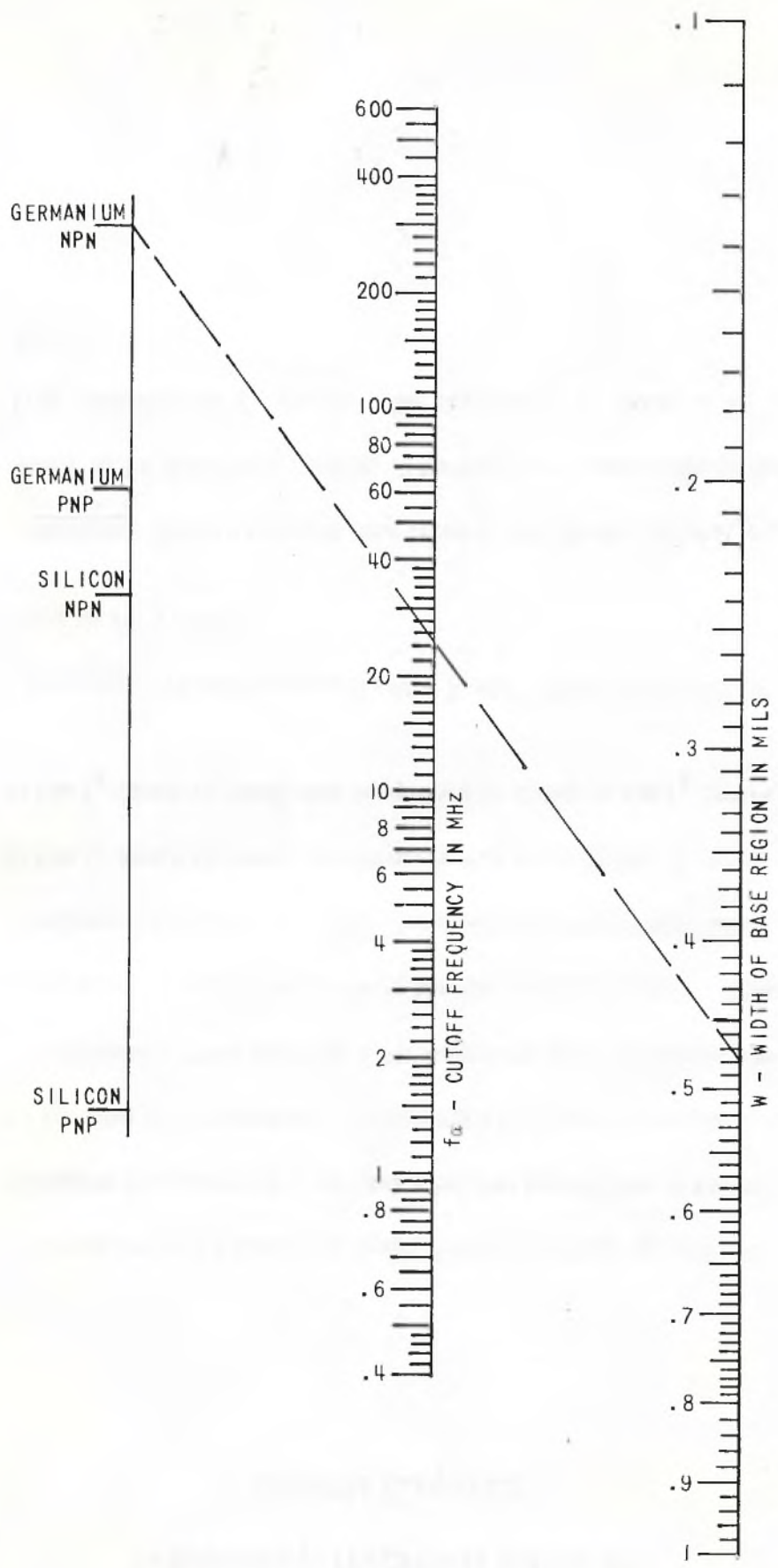\* This formula can be found in the 4th edition of Reference Data for Radio Engineers, page 497.



## Frequency-Thickness Ratio for Quartz Crystals

Nomogram 5-11 comes in handy for calculating the primary resonant frequency of a crystal when the type of cut is known. It is done by measuring the thickness of the crystal with a micrometer, then drawing a straight line from the thickness scale to the crystal cut scale at the appropriate points. The frequency is found where this line intersects the center scale. If the  $t_A$  scale is used, the frequency is found in the  $f_A$  scale. If the  $t_B$  scale is used, the frequency is found in the  $f_B$  scale.

Example: Find the frequency of a Y-cut crystal whose thickness is 38.5 mils.

Solution: Draw a straight line from Y-cut on the crystal cut scale to 38.5 on the  $t_A$  scale. The answer is found where the line crosses the  $f_A$  scale. The frequency is found to be 2 MHz.

X CUT  
 BT CUT  
 Y CUT  
 AT CUT





## CHAPTER 6

# Miscellaneous

## Nyquist Noise Voltage

One of the more important types of noise that the electronics engineer must deal with is termed thermal noise. A random motion of free electrons sets up a thermal agitation in any conductor. This causes small random voltages, called thermal or Johnson noise, to appear across the terminals of the conductor. The energy spectrum of noise is uniform over all frequencies—i. e., the voltage has a "flat" or "white" characteristic which is independent of frequency. Thermal noise voltage is expressed by:

$$E_n = \sqrt{4kTRB}$$

Where:  $E_n$  is the rms value of the thermal noise in volts

$k$  is Boltzman's constant =  $1.372 \times 10^{-23}$  joules/ $^{\circ}$ K

$T$  is the temperature in  $^{\circ}$ K (Degrees Kelvin)

$B$  is the noise bandwidth in Hz


$R$  is the resistance in ohms

At room temperature,  $T = 25^{\circ}$ C =  $298.16^{\circ}$ K.

The noise equation then becomes:

$$E_n = \sqrt{1.636 \times 10^{-20} BR}$$

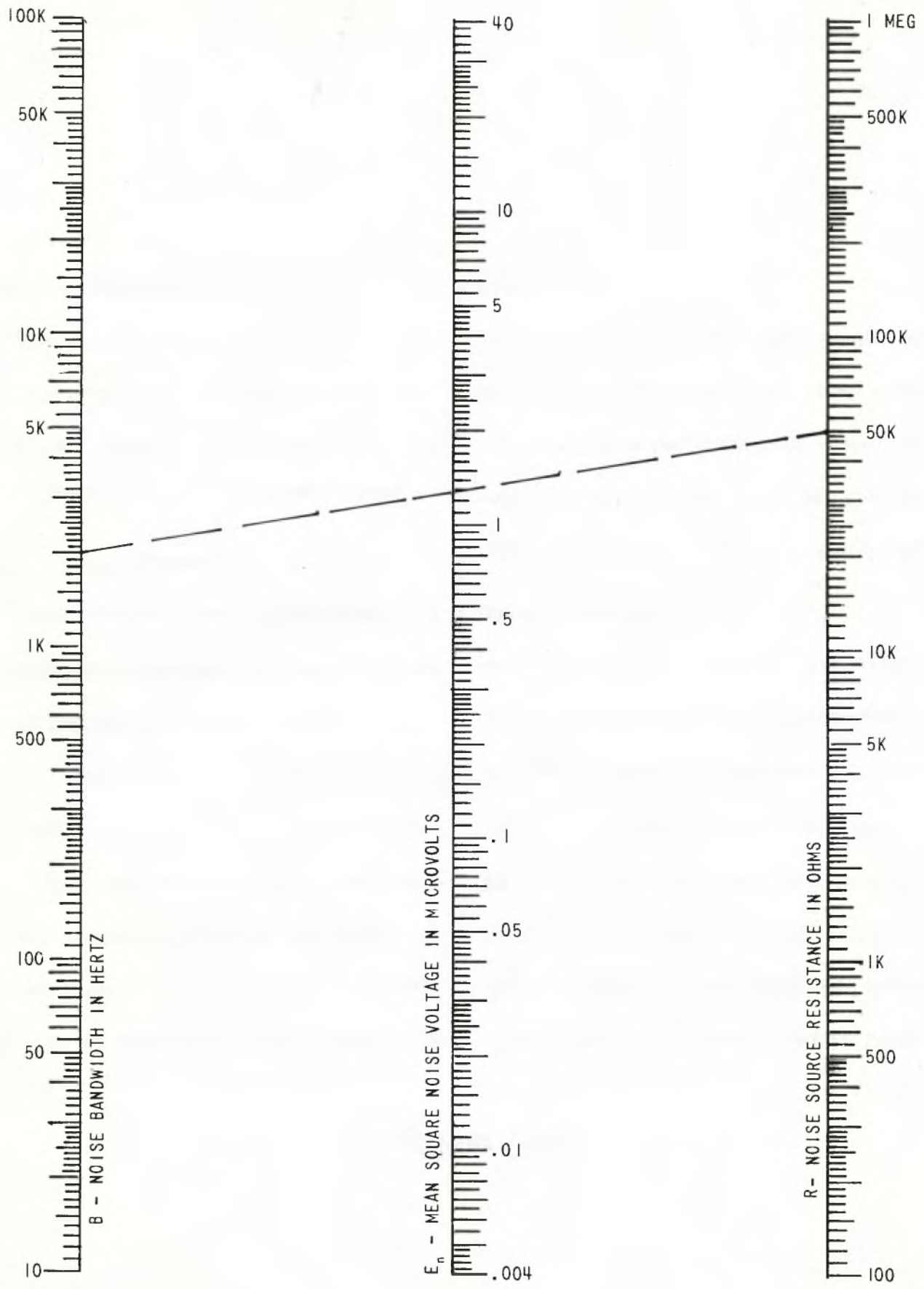Values other than those shown on the scales may be used by multiplying all scales simultaneously by  $10^n$ , where  $n$  may be either positive or negative. If only the  $B$  or  $R$  scale is multiplied by  $10^n$ , then the  $E_n$  scale must be multiplied by  $10^{n/2}$ . In the example illustrated by the dashed line,  $B = 2$  kHz,  $R = 50$  K and  $E_n = 1.28 \mu$ v.



## Amplifier Gain


To find the power gain of an amplifier, it is necessary to compute the ratio of its output to input power (take the log and multiply by 10). When the input and output resistances are equal, the voltage gain of the amplifier can be calculated by multiplying 20 times the log of the output to input voltages. Nomogram 6-2 eliminates the tedious calculations involved, and gain can be determined in a much simpler manner.

For values of  $10^n$  or  $10^{-n}$  times those on  $E_1$  scale, subtract or add respectively,  $n$  times 20 db from or to the values on the voltage gain scale. ( $n$  times 10 db from or to the power gain scale when the  $P_1$  scale is used.)

For values of  $10^n$  or  $10^{-n}$  times those on the  $E_2$  or  $P_2$  scales, add or subtract, respectively,  $n$  times 20 db to or from the values on the voltage gain scale and  $n$  times 10 db to or from the values on the power gain scale.

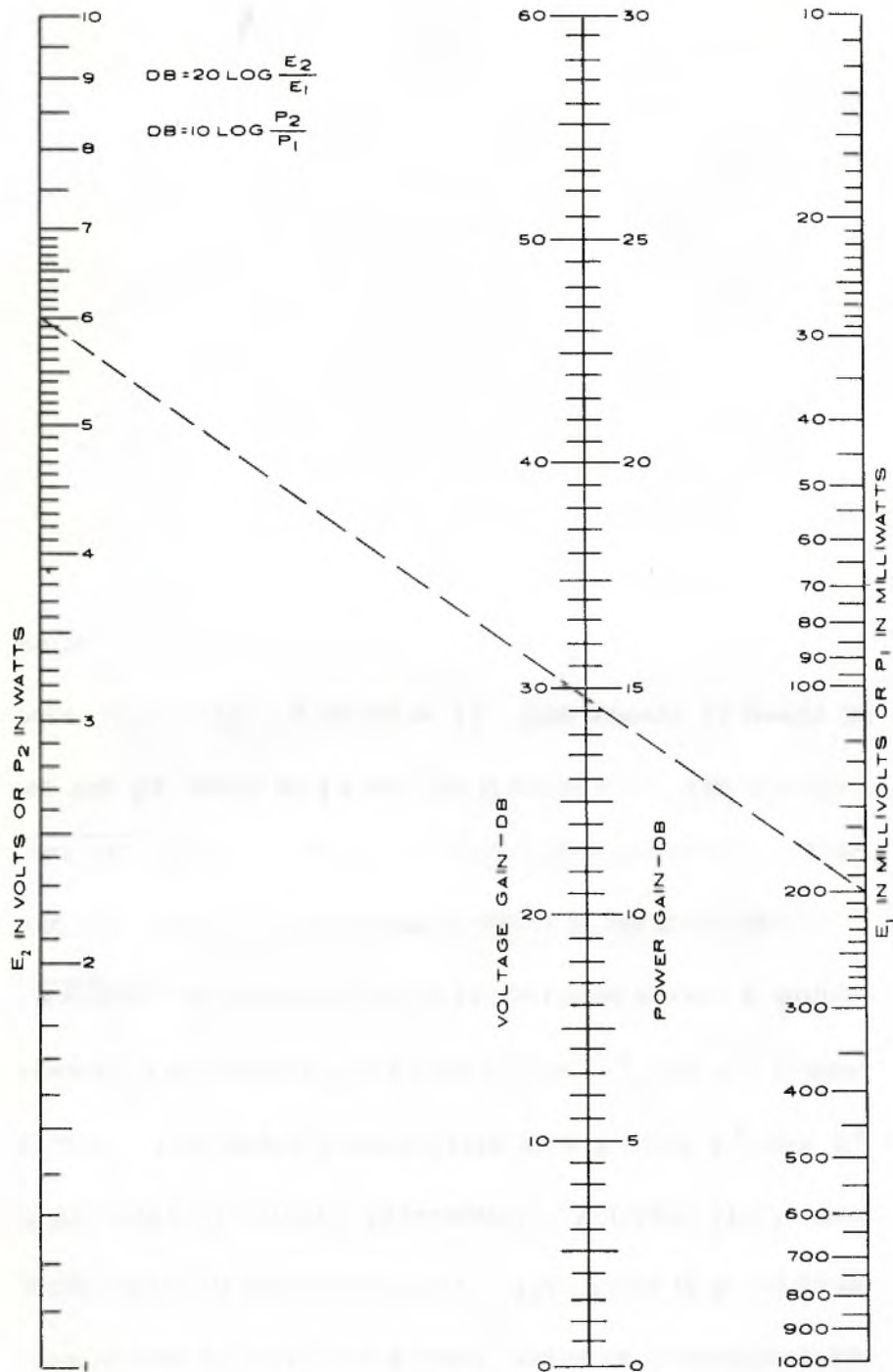Example: Find the voltage gain of an amplifier whose input and output resistances are equal when 6 volts output is measured for 200 millivolt input.

Solution: Place one end of a straight-edge over 6 on the left-hand scale and the other end over 200 on the right-hand scale. Find 29.6 at the point where the straight-edge crosses the center scale. This is the voltage gain in db.




## Amplifier Power Output

Nomogram 6-3 provides a rapid means of determining the output power of audio amplifiers. The values of  $R$  are given in the range of speaker impedances. Voltages are in rms values. For output voltages less than 6, use  $E_A$  and  $P_A$  scales. For voltages more than 6, use  $E_B$  and  $P_B$  scales.

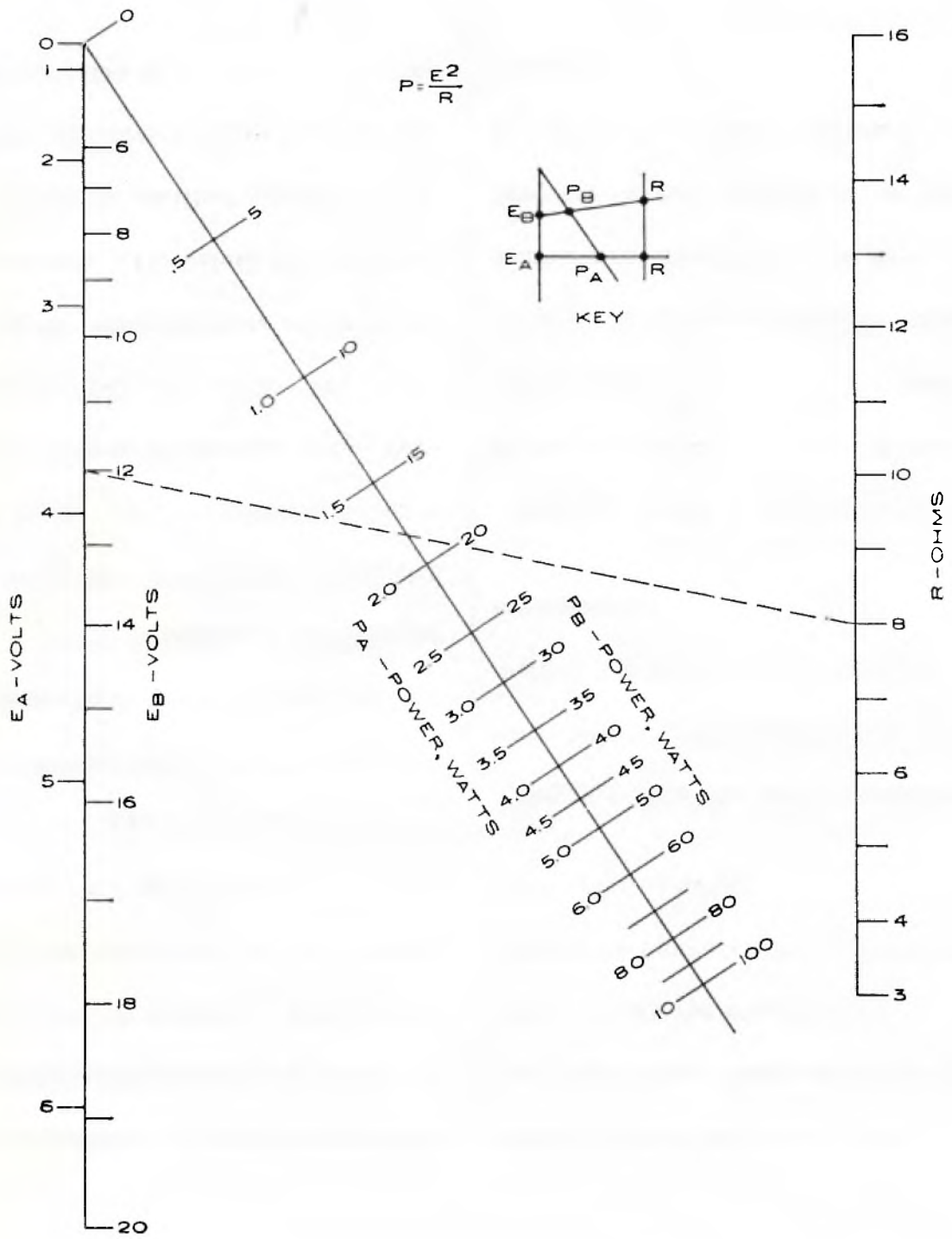Example: An amplifier has a 12-volt drop across a dummy load of 8 ohms. Find the power output of the amplifier.

Solution: Lay a straight-edge across the three scales, touching the  $E_B$  scale at 12 and the  $R$  scale at 8. The straight-edge crosses the  $P_B$  scale at 18. The answer is power in watts.



## Modulation Percentage

In AM transmitters, it is necessary to check the modulation percentage so that limits set by the FCC are not exceeded. The methods of obtaining the waveforms are not discussed here since they can be found in any standard text. Nomogram 6-4 does, however, offer a simplified means of determining the percent modulation from the waveforms.

Fig. 6-1 shows a series of oscilloscope patterns of an RF carrier being modulated by a sine wave. Fig. 6-2 shows a series of trapezoidal patterns of the same waves. Percent Modulation (M) =  $((A-B)/(A+B)) \times 100$ , where A is the crest amplitude and B is the trough amplitude. The values of A and B are measured from the oscilloscope patterns. M is found by extending a straight-edge from the measured value of A on its scale to the

measured value of B on its scale. The percent modulation is found where the straight-edge crosses the diagonal scale. A and B may be in any units as long as both are measured in the same units.

Example: Find the percent modulation of a wave whose crest amplitude is 6.3 centimeters and whose trough amplitude is 2.7 centimeters.

Solution: Extend a straight-edge from 6.3 on the A scale to 2.7 on the B scale. The straight-edge crosses the M scale at 40, which is the percent modulation. Note: For symmetrical modulation, the above equation produces the same results as the equations:  $M = (A-C)/C$  or  $(C-B)/C$ , where C = carrier amplitude.)



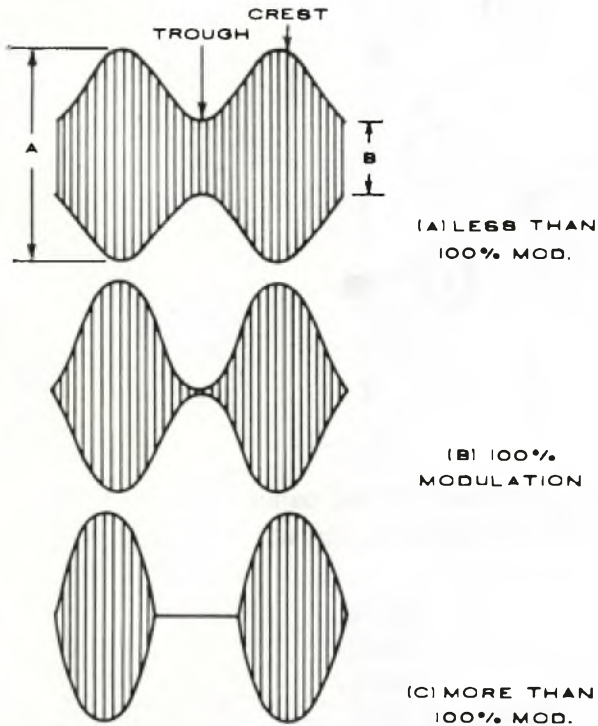


Fig. 6-1. Amplitude modulated RF carrier waveforms.


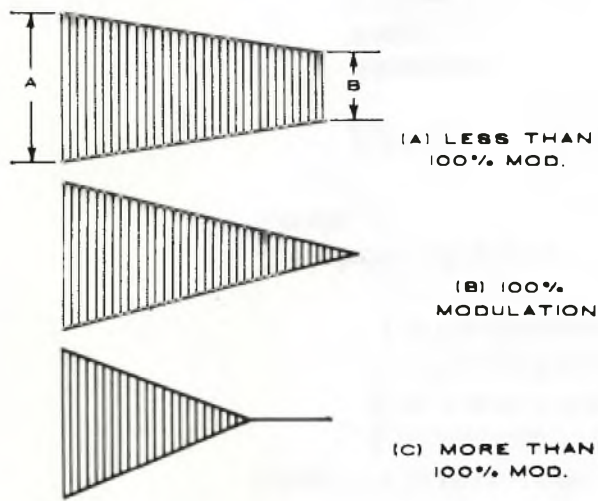


Fig. 6-2. Trapezoidal modulation patterns seen on scope.

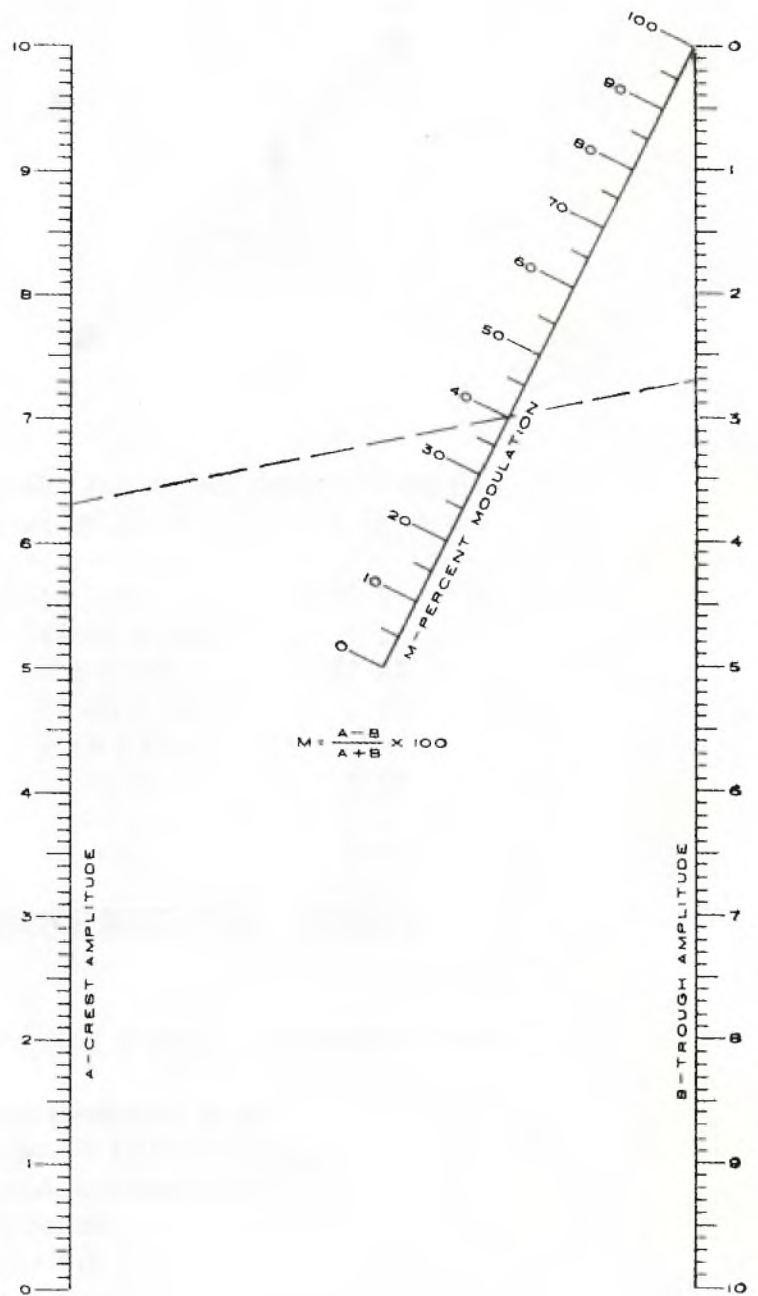

# Tuning Fork Frequency

The physical dimensions of a tuning fork resonator determine its natural resonance frequency which is given by the equation:


$$f = \frac{0.55966 d}{L^2} \sqrt{\frac{E}{12\rho}}$$

Where:  $d$  is the tine thickness in cm  
 $L$  is the tine length in cm  
 $E$  is Young's Modulus in dynes/cm<sup>2</sup>  
 $\rho$  is the material density in grams/cm<sup>3</sup>  
 $f$  is the fundamental frequency in Hz.




The chart below gives values of  $E$  and  $\rho$  for some common metals.

<u>METAL</u>	<u>YOUNG'S MODULUS</u>	<u>DENSITY</u>
Aluminum	$7 \times 10^{11}$	2.699
Brass	$9.2 \times 10^{11}$	8.6
Copper	$10-12 \times 10^{11}$	8.89
Iron (Cast)	$8-10 \times 10^{11}$	7.2
Iron (Wrought)	$18-20 \times 10^{11}$	7.85
Lead	$1.5 \times 10^{11}$	11.37
Steel	$19-21 \times 10^{11}$	7.7
Nickel	$22 \times 10^{11}$	8.9

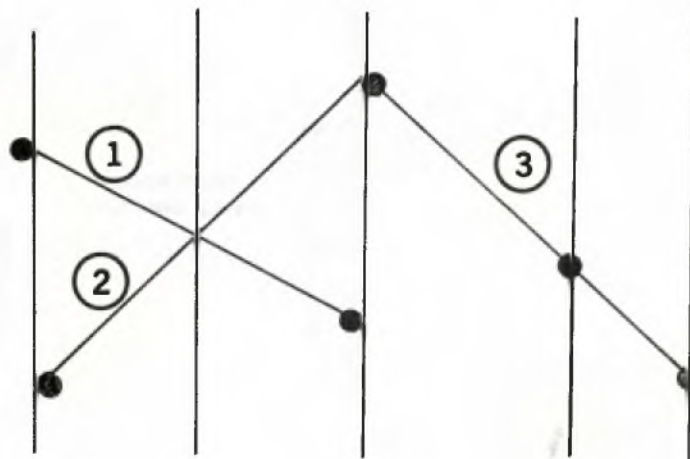
In the example illustrated by the dashed lines for an aluminum tuning fork:  $d = 1.8$  cm,  $L = 12$  cm, and  $f = 1020$  Hz.



Key

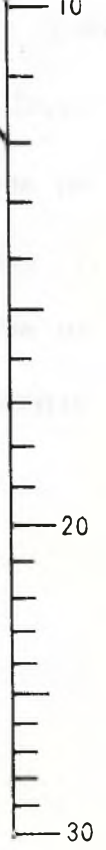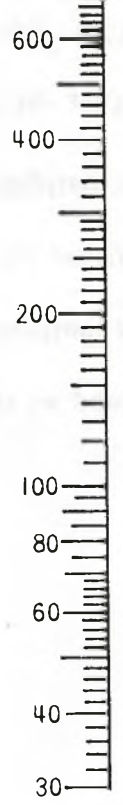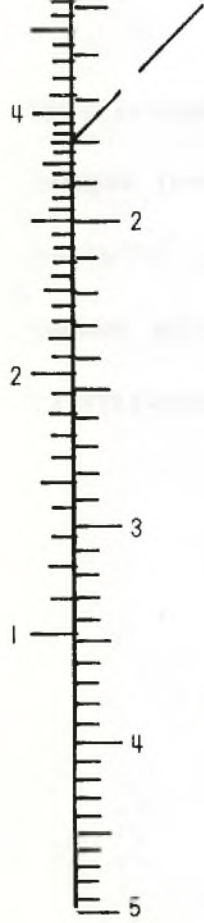


E d - IN CM

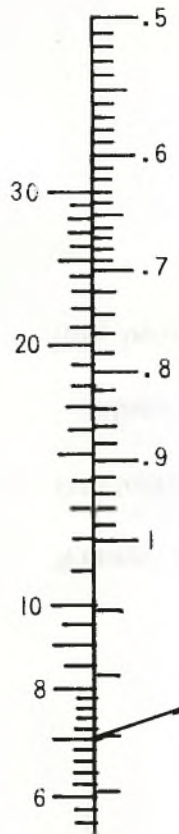


f - IN Hz



L - IN CM

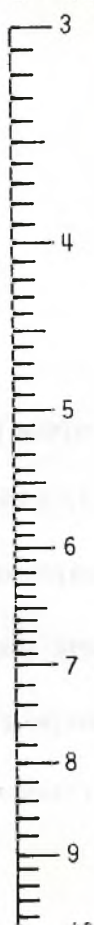

p

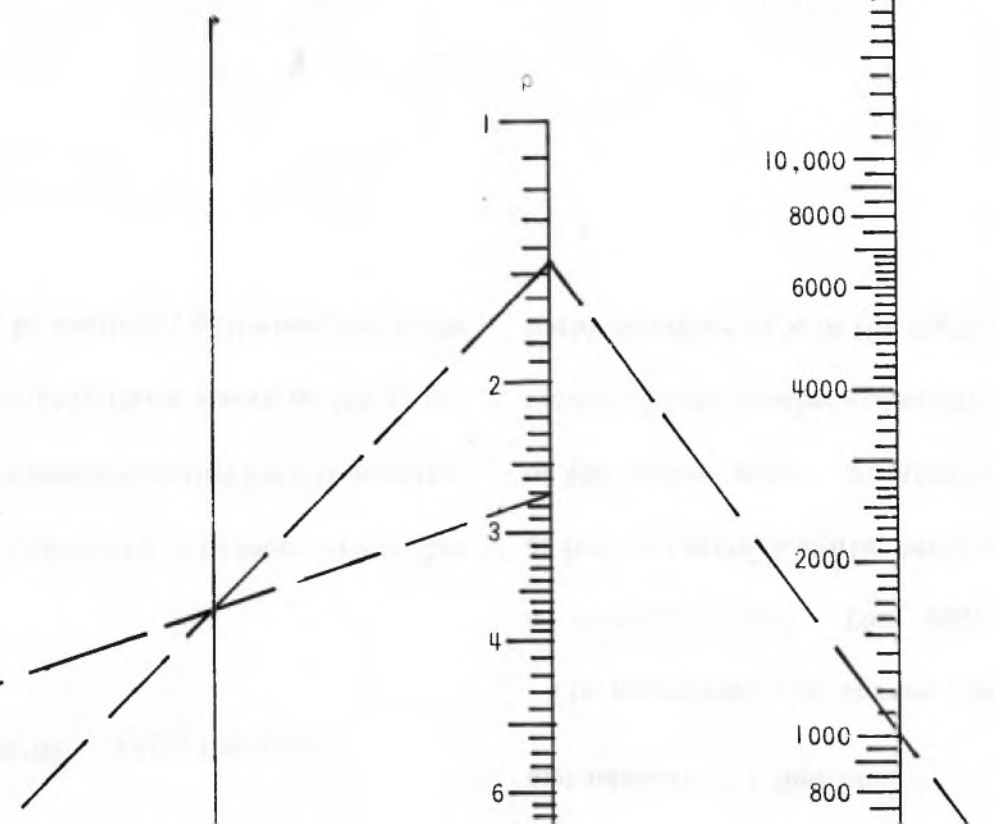

## Light Intensity

Light intensity to a given object from a light source with a signified horizontal candle power may be found in foot-candles or meter-candles (Lux) with Nomogram 6-6. This chart is based upon the equation:

$$\text{HCP}/D^2 = \text{Light Intensity}$$

Where: Light intensity is in foot-candles for D in feet and in meter-candles for D in meters.



Values other than those shown on the graph may be used by multiplying the desired scale


by  $10^n$ , where  $n$  may be positive or negative.

When HCP is multiplied by  $10^n$ , the intensity scale must be multiplied by  $10^n$ . If the D scale is multiplied by  $10^n$ , the intensity scale must be multiplied by  $10^{-2n}$ .

In the example shown: HCP = 10, D = .1 m and intensity = 1,000 Lux.

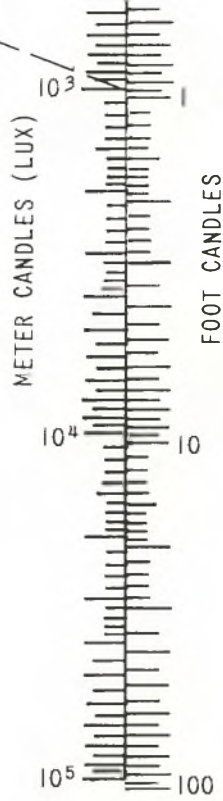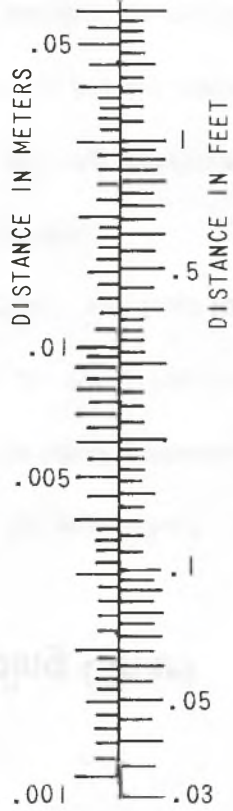The nomogram also serves the function of a conversion chart. The equivalent values of feet and meters can be found on either side of the center scale. Similarly, equivalent values of foot-candles and meter-candles are found on either side of the right-hand scale.



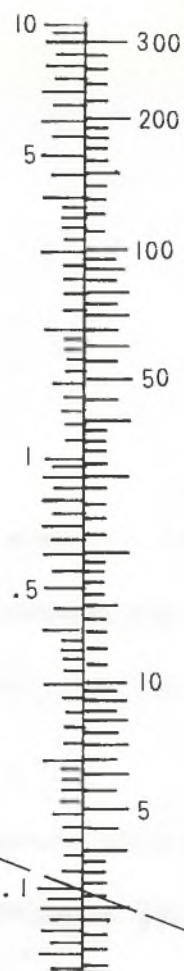


## Wire Stranding Chart

It is often desirable to know the equivalent area and AWG number of a stranded cable. The usual procedure for finding this value is to first determine the AWG number or the area of a single strand in circular mils, and then to multiply this figure by the total number of strands,

With Nomogram 6-7, it is merely necessary to draw a straight line from the AWG number (or its equivalent area in circular mils) on the left-hand scale to the number of strands on the right-hand scale. The equivalent AWG number and area of the bunch is found on the center scale where it is intersected by the line.

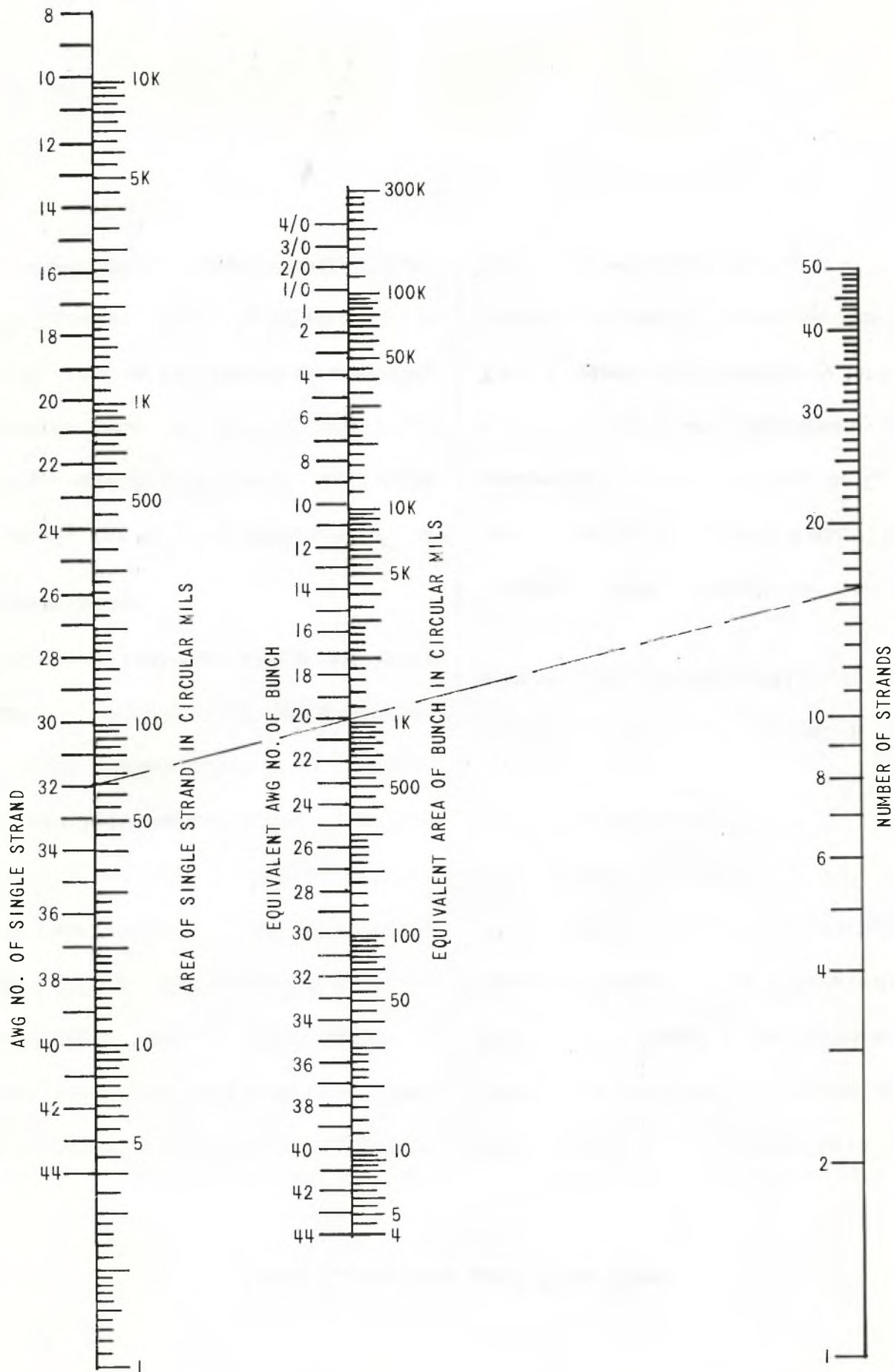In the example shown by the dashed line: 16 strands of #32 wire is the equivalent of a single strand of #20 wire. Use the closest AWG number to the point where the center scale is intersected.





## Time Constant and Rise Time



Time constant and rise time are rapidly calculated for both R-C and L-R circuits with Nomogram 6-8. Only one step is needed. In the R-C circuit, time constant  $T$  is defined as the time it takes to charge the capacitor to 63.2% of the maximum voltage. In the L-R circuit it is defined as the time it takes for the current to reach 63.2% of its maximum value. Rise time  $T_R$  is the time it takes for the charge to rise from 10% to 90% of its maximum value.

$T$  and  $T_R$  can be found simultaneously by drawing a straight line from  $R_L$  to  $L$  at the respective values for the L-R circuit and from  $R_C$  to  $C$  at the respective values for the R-C circuit.  $T$  and  $T_R$  for each case is found where this line crosses the center scale.

Other values of  $L$ ,  $C$ , and  $R$  can be substituted in the nomogram by multiplying any value by  $10^n$ , where  $n$  may be positive or negative. When  $L$ ,  $C$ , or  $R_C$  are multiplied by  $10^n$ , then  $T$  and  $T_R$  are also multiplied by  $10^n$ . When  $R_L$  is multiplied by  $10^n$ , then  $T$  and  $T_R$  are multiplied by  $10^{-n}$ .

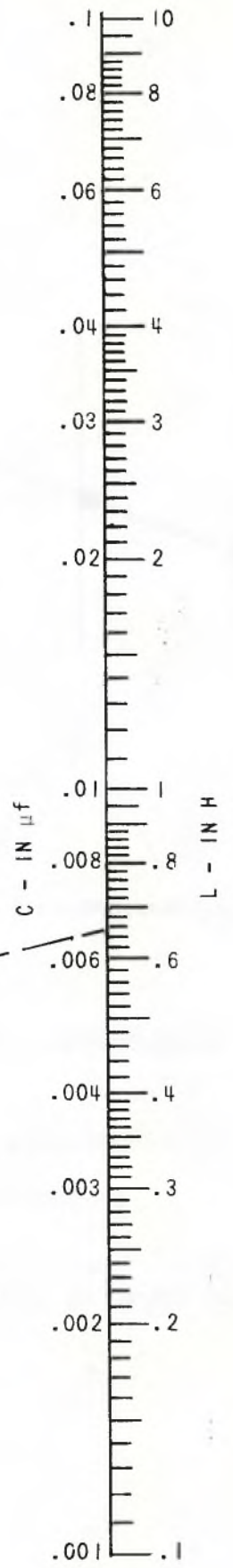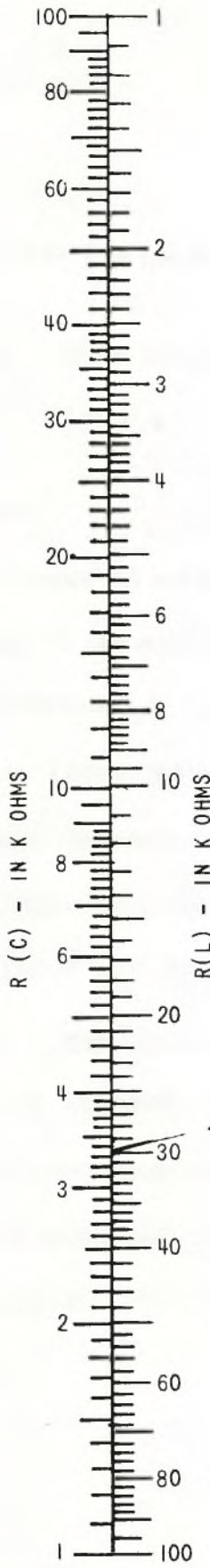Example: Find  $T$  and  $T_R$  of an L-R circuit, when  $R_L$  is 300,000 ohms and  $L$  is .65 henries.

Solution: Draw a straight line from 30 on the  $R_L$  scale to .65 on the  $L$  scale. The line crosses the  $T$  scale at 0.022 and the  $T_R$  scale at 0.048. Since  $R_L$  was multiplied by  $10^4$  the  $T$  and  $T_R$  values are multiplied by  $10^{-4}$ . The answers are then 2.2 micro-seconds for  $T$  and 4.8 micro-seconds for  $T_R$ .



# Separation Loss in a Magnetic Recording System

Magnetic tape recorders require precision tape resolution. This is so because of the high frequencies that are being recorded. A slight variation in tape-to-head separation may cause excessive loss in signal. This problem was discussed in "Magnetic Tape Trends" published by Ampex Corp. Two formulas appeared in Bulletin #10, September 1965 Issue, which are presented here as Nomogram 6-9. The first one is used to determine the wavelength of the signal being recorded and the second calculates the signal loss.

(1)  $\lambda = S / f$

(2) Signal loss =  $55d / \lambda$

Where:  $\lambda$  is the wavelength in mils

S is the tape speed in inches per second


f is the frequency in Hertz

d is the tape-to-head separation in mils


The nomogram is solved by following the Key below.

Note: A & C scales are used simultaneously

B & D	"	"	"	"
F & H	"	"	"	"
G & J	"	"	"	"

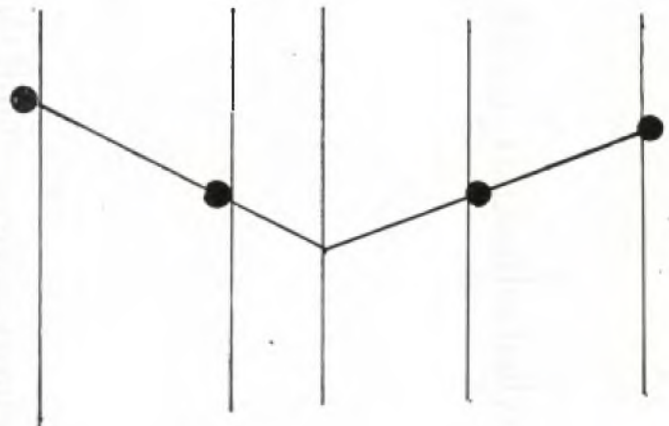

Key

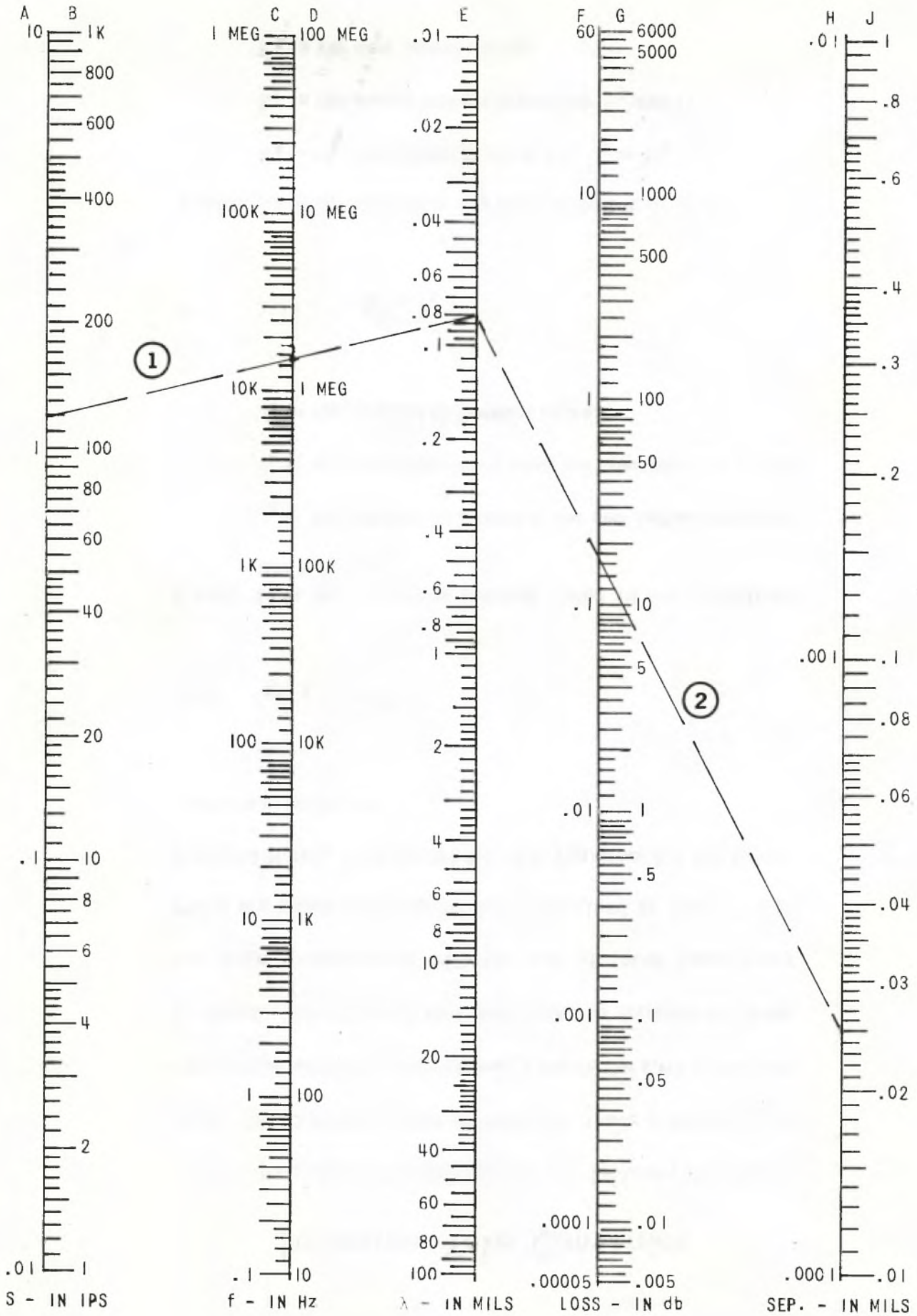

## Deflection Yoke Conversion

Deflection yoke specifications generally include yoke inductance, sweep current, and acceleration anode potential, as well as the deflection angle through which the CRT beam will be swept. The engineer may make precise departures from the given specifications with the use of these nomograms which are based upon information described in CELCO Application Notes, Data Sheet Y2G. The equations for the nomograms are as follows:

$$6-10: \quad I_2/I_1 = \theta_2/\theta_1$$

Where:  $I_1$  is the deflection current listed in the specifications at  $\theta_1$ .

$I_2$  is the deflection current at the new deflection angle.

$\theta_1$  is the deflection angle from the specification sheet.

$\theta_2$  is the desired deflection angle.


$$6-11 \quad I_2/I_1 = \sqrt{E_2/E_1}$$

Where:  $I_1$  is the deflection current listed for  $\theta_1$  at  $E_1$ .

$I_2$  is the deflection current for  $\theta_1$  at  $E_2$ .

$E_1$  is the anode voltage listed for  $\theta_1$  and  $I_1$ .

$E_2$  is the new anode voltage.

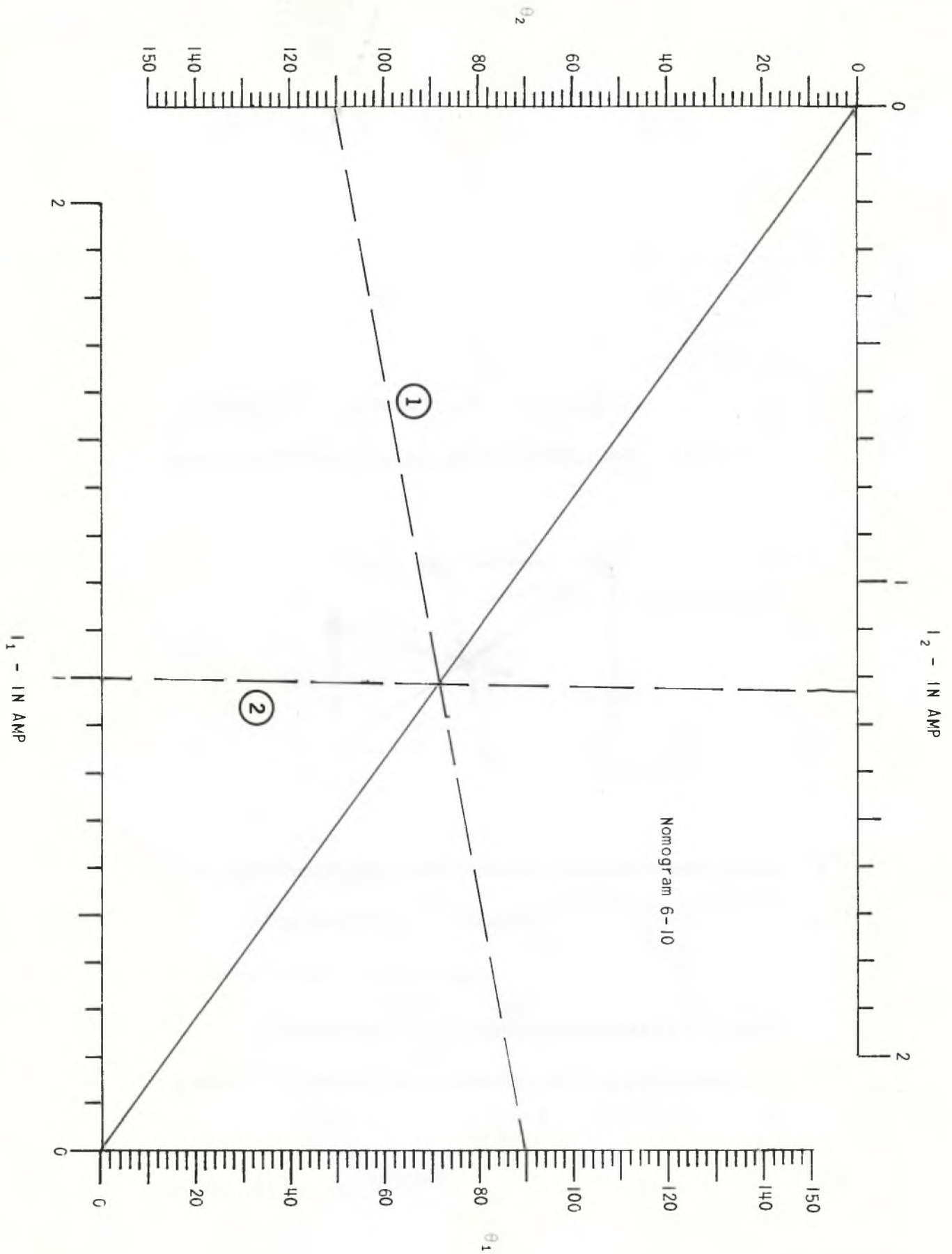

$$6-12 \quad (I_2/I_1)^2 = L_1/L_2$$


Where:  $I_1$  is the deflection current from the specifications.

$I_2$  is the deflection current at the desired inductance.

$L_1$  is the inductance at  $I_1$ .

$L_2$  is the desired yoke inductance.

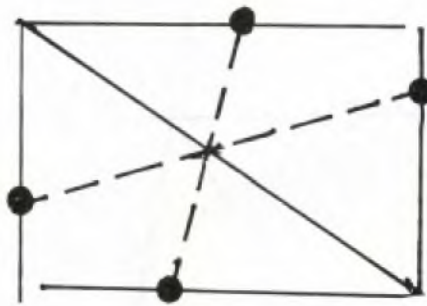All three nomograms are similarly solved as shown in the Key below.




Key


For the example illustrated by the dashed lines:  $\theta_2 = 110^\circ$ ,

$\theta_1 = 90^\circ$ ,  $I_1 = 1$  ampere and  $I_2 = 1.22$  amperes.



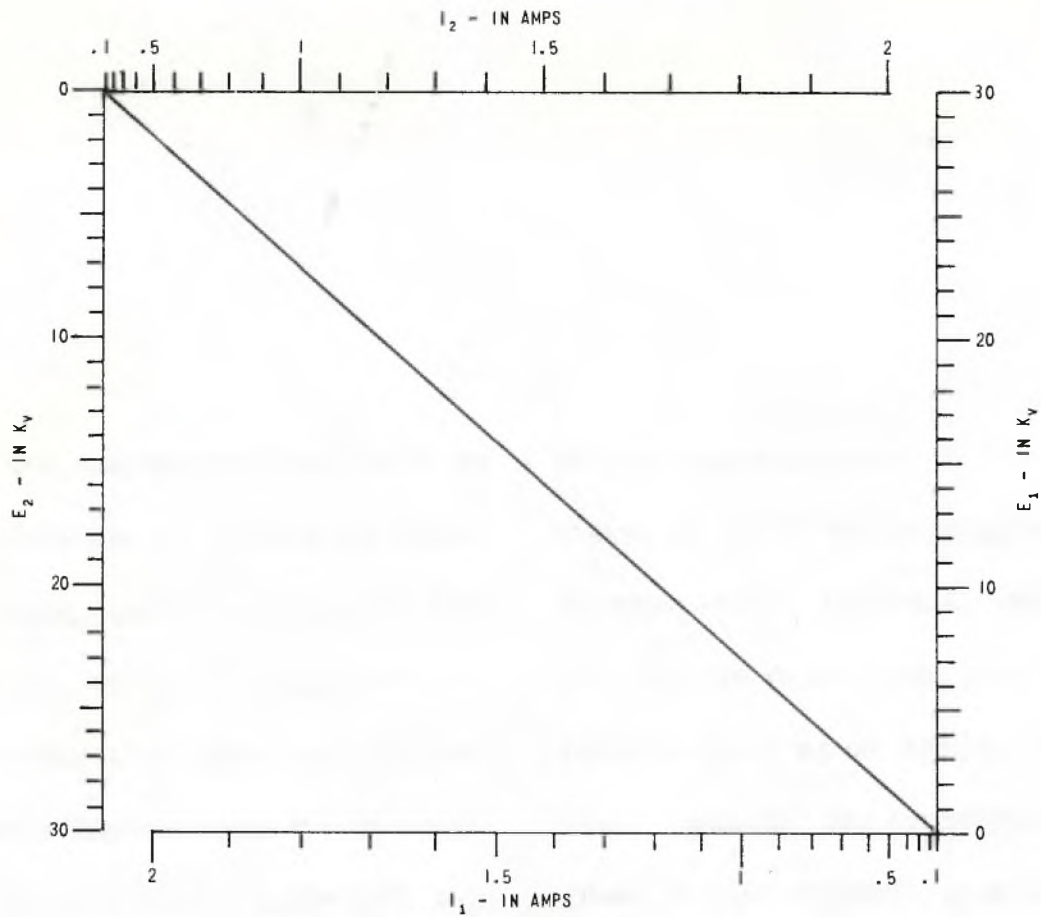

Nomogram 6-11

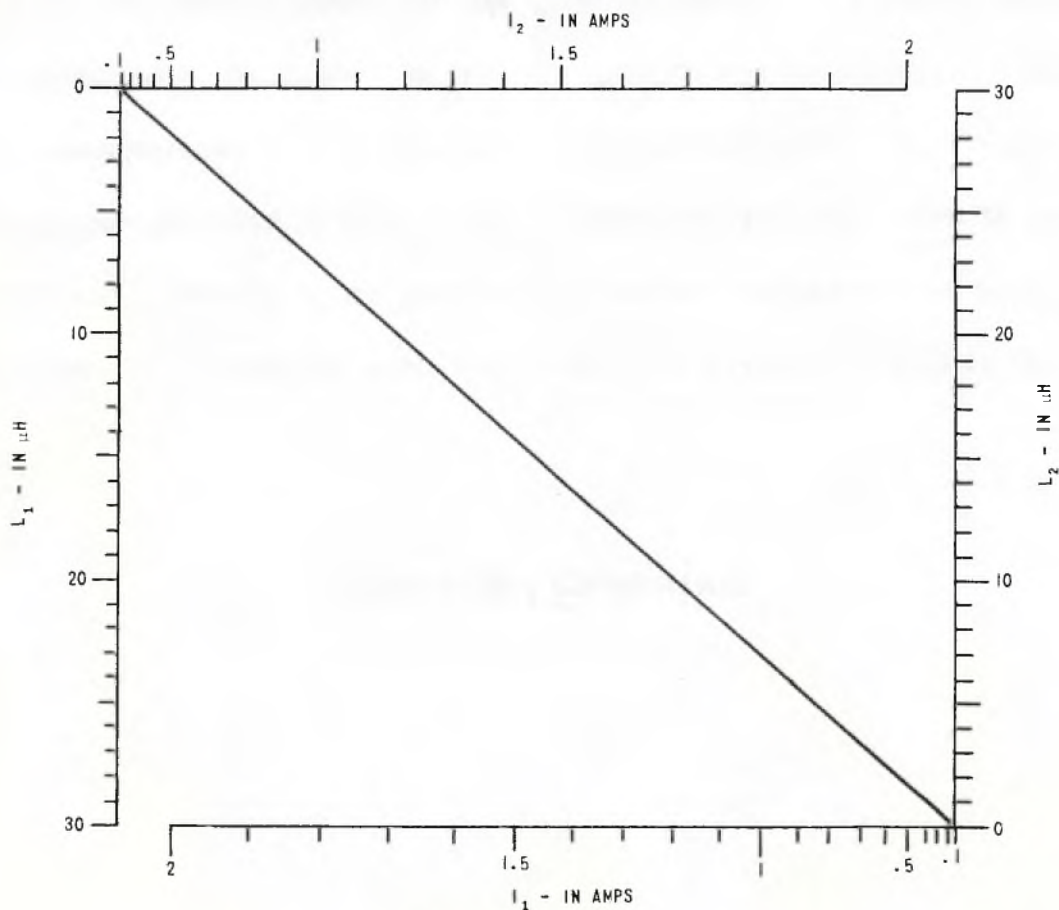

Nomogram 6-12


## Pilot Light Evaluation

Even the humble incandescent lamp may create intriguing problems if its lifetime must be evaluated rigorously in terms of its operating characteristics. The questions are: To what degree do the voltage, the current, and the candlepower change the life factor of the pilot light? Nomogram 6-13 supplies the answers in a few simple steps.

Manufacturers recommend that the rated voltage of the lamps be 10 to 20% higher than intended applied voltage. This obviously does not apply where the duty cycle of the applied voltage is such that the lamp will be on for

only short periods, where brightness is not important, and where blue lenses are used, since the blue light output is low for low-temperature lamps.

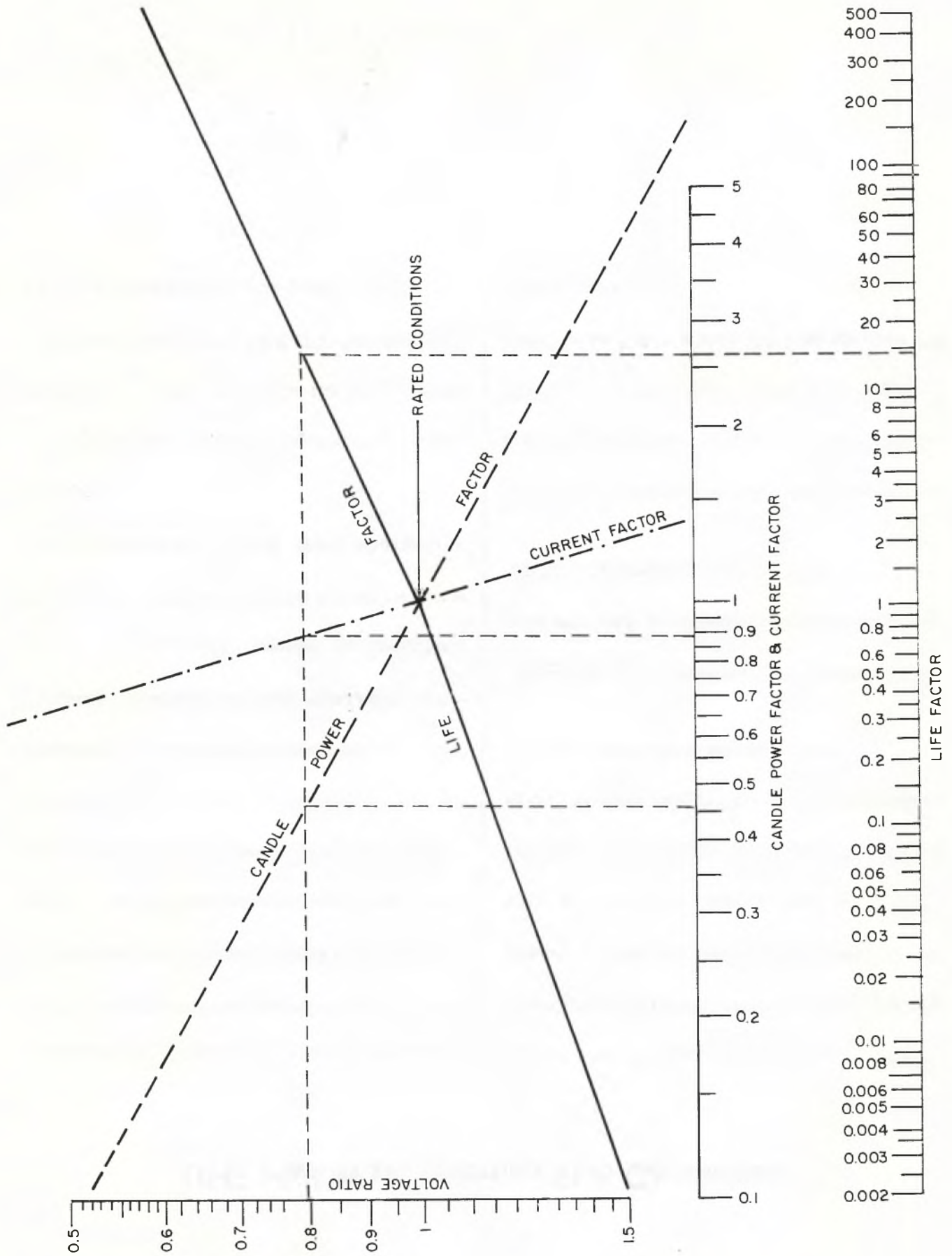To illustrate the use of the charts, consider this problem. A lamp is operated at 0.8 times its rated voltage. How will the life factor, current, and candlepower change? From the graph we can read off the following: The life factor increase to 14.5 times its rated value, the current decreases to 0.88 of its rating and the candlepower drops to 0.46 of the rated value.



## UHF Half-Wave Shorting Stub Calculation


Nomogram 6-14 permits rapid determination of the length of half-wave shorting stubs to eliminate interference in the UHF television range. Most technicians are acquainted with the method of making these stubs and probably know the exact length of 300-ohm twinlead required to eliminate interference on VHF channels. However, with the increasing number of UHF channels opening up throughout the country, they may have to resort to some fancy guesswork or else start sharpening pencils.

Assuming that the technician knows his service area, he will also know the frequencies of potential sources of UHF-TV interference. With this information, the length of the re-

quired stub is found by drawing a straight line through all three scales, from the frequency in the left-hand scale to the "V" column at the point indicated for the type of lead-in wire used to construct the shorting stub. The stub length is found in the diagonal column where the line crosses it.

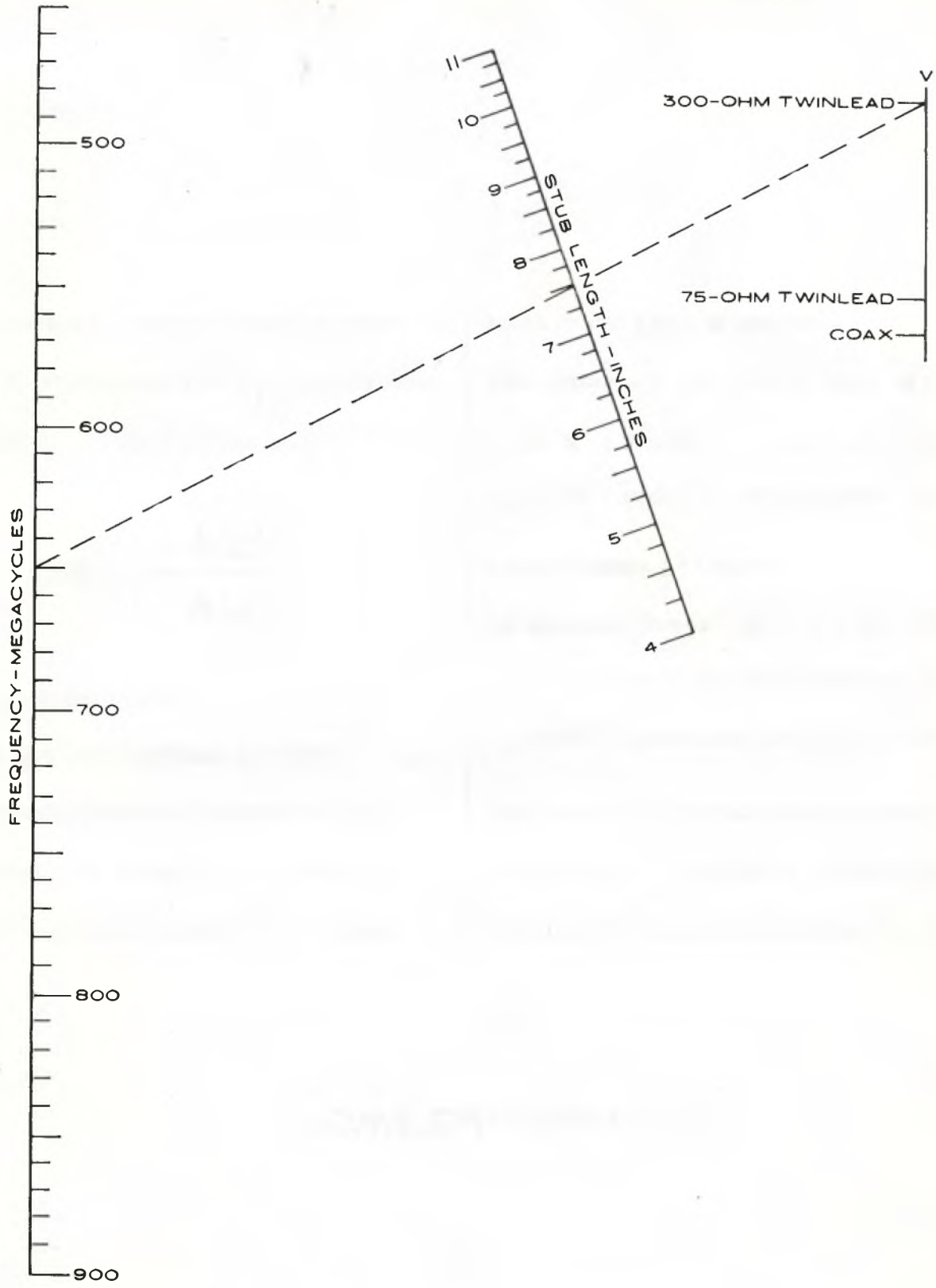Example: Find the length of a piece of 300-ohm twinlead necessary to eliminate an interference frequency of 650 MHz.

Solution: Draw a straight line from 650 on the frequency scale to the 300-ohm twinlead point on the "V" scale. The stub length is found to be 7.45" where the line crosses the center scale.



## VSWR Calculations

Nomogram 6-15 permits a rapid means of calculating the VSWR of a transmission line after having measured the powers of the incident ( $P_f$ ) and reflected ( $P_r$ ) waves. The solution of the equation:

$$\text{VSWR} = \frac{1 + \sqrt{P_r/P_f}}{1 - \sqrt{P_r/P_f}}$$

is cumbersome even with the use of a slide rule. By using Nomogram 6-15, the equation can be solved by merely aligning a straight-

edge through the measured points on the  $P_r$  and  $P_f$  scales. The VSWR is located where the straight-edge intersects the center scale.

Example: Determine the VSWR of a transmission line for the following recorded power; (a) reflected power,  $P_r = 2.7$  w, and (b) forward power  $P_f = 180$  w.

Solution: Align a straight-edge through points  $P_r = 2.7$  and  $P_f = 180$ . The straight-edge intersects the center scale at 1.27, which is the VSWR of the line.

