

Electronics Today



June 1984

\$2.95
MM70924




Canada's Magazine for Electronics & Computing Enthusiasts

Modem Auto-Answer Project

Convert your modem 

**Genealogy
of the Microchip**

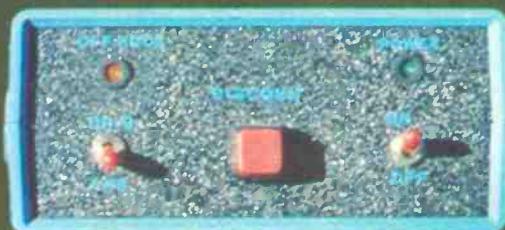

**Circuit
Supplement**
Pages of Useful
Circuitry!

**Echo Reverb
Project**
All solid state 

**Coping With
Components**
Parts primer

AUTO ANSWER ADD-ON PROJECT
AWAITING HOBBYIST



**Computer
Review:**
Multitech MPF III



EXCELTRONIX (416) 921-8941 1-800-268-3798

Bulletin Bd. (416) 921-4013 Telex 065-24218

319 College St., Toronto, Ont. M5T 1S2

Catalogue shipping rates are incorrect. Please call us for correct charges. Prices in catalogue are fluctuating. Use as guideline.

Now Open

JUST RELEASED
New Smith-Corona
Typewriter/Printer
Call for information
and Unbeatable Pricing

Visit our new Ottawa location
217 Bank Street, (613) 230-9000

Store hours 9:30 to 6:00 Monday-Saturday: to 9:00 p.m. Thursday and Friday.

PRINTERS

Star Gemini 10X	\$359
Gemini 15X	\$599
Delta 10 (160 cps)	\$739
Epson MX100	\$995
Epson RX80 (Replaces MX80)	\$495
Epson FX80 (New)	\$798
Epson FX100 (New)	\$1069
TTX (Daisy Wheel)	\$649
Microtek	\$139

APPLE CARDS

16K card - Multiflex	\$58.00
128K card	\$210.00
Proto Board	\$15.00
80-Column Card	\$84.00
Z80 Card	\$59.00
EPROM Programmer	from \$69.00
(for 2716, 2732, 2732A, 2764, with software) Parallel Printer Card with cable	\$69.00
Wizard Parallel Card	\$95.00

Joysticks

Economodel	\$19.95
Wico Red Ball	\$42.95
Self-Centering with two adjustable controls	
Super offer	\$64.00
Kraft Joystick (Apple, PC)	\$64.95
Kraft Paddles	\$48.95
TG Joystick	
Deluxe Model	\$75.00
TG Paddles Deluxe Model	\$64.95
Hayes Mach III	\$58.95
Model Deluxe Table Top	\$59.00
Hayes Mach II	\$48.95

MONITORS

Zenith ZVM-122 Amber	\$148
Amdek Amber-300	\$139
Zenith ZVM-123 Green	\$129
Amdek Colour 1	\$445
Roll and DG	\$419

Apple //e™ Package Includes: 80 x 24 Card, Multiflex IPI, Z80 Card, Multiflex Disk Drive and Controller \$1599

Apple //e™ Package Includes: Apple //e, ZVM 123 Monitor, Apple Drive & controller card & DOS software, 80 x 24 Multiflex card, Apple manuals \$2099

NEW Macintosh, based on 68000 with 3" Disk Drive (smaller version of Lisa™), 3" Diskette Software now available \$3595

MODEMS

EPM 310	\$99
Smart Modem (300 Baud, IBM Comp)	\$359
Apple a la Modem (300 Baud)	\$215
Micromodem (Apple Comp)	\$475
Signalman (300 & 1200 Baud)	\$495
Smart Modem 1200 Baud	\$899

FAMOUS MULTIFLEX Z80 STARTER KIT: SPECIAL \$349.00

Ideal Learning Tool, with EPROM programmer A&T \$349.00
see page 18 of catalogue

Super Computer Case

Ideal for 8088 or 6502 boards
Unmatchable quality, all-Canadian made

\$87.00!



IBM Compatible Keyboard \$189.00

Maxiswitch or cherry super



Memory Chips

4164-150nS (1x64K single +5V)	
Motorola	\$9.95
T.I.	\$7.95
4116-200ns (1x16k)	\$1.74
4116-150ns (1x16k)	\$1.99
2114L-200 ns (1kx4 static)	\$2.49
6116-150 ns (2kx8 static RAM)	\$8.94
(Pin compatible with 2716 uses negligible amount of power)	
2016-150 ns (2kx8 static)	\$8.74
2102L-200 ns (1kx1 static)	\$1.94
5101-CMOS RAM	\$3.84
2708-(1kx8 EPROM)	\$6.74
2716-(2kx8 EPROM single +5V)	\$5.50
2732-(4kx8 EPROM single +5V)	\$8.95
2532-(4kx8 EPROM single 5V)	\$8.74
2764-(8kx8 EPROM single 5V)	\$12.95

HUGE STOCK OF LS

UNIVERSITY OF TORONTO/MULTIFLEX 6809 Board, great for learning about 6809 and computing in general with A & T \$499.00
Economy Terminal A&T \$369.00
Package Deal A&T \$849.00

Featuring the Multiflex Apple™ Compatible Drive

only \$249

Package Deals:
A1 Drive & Controller \$310
B2 Drives & Controller \$549
Controller only \$69
with software \$119
VISTA DRIVE \$299
QUENTIN DRIVE \$299

1 year warranty

Special!



Controller \$89
With Apple™ Software \$119

Superb Power Supply

Uncased Dual 12V:
(one at 2.8A, one at 2A).
—12V at 0.5A, +5V at 5A plus

\$69.00!

Cased model, with fan, cord and switch

\$139.00!

These supplies are ideal for IBM compatibles, they fit beautifully into IBM compatible cases.

IBM is registered trade mark of IBM Canada Limited.

Diskettes

5 1/4" Diskettes. Boxes of 10	
Maxell MD1	\$34.00
Maxell MD2	\$52.95
Verbatim	\$34.00
CDC	\$26.95
3M	\$32.95
Accutrak	\$26.95
2 Ectype Diskettes in a plastic binder sheet	\$5.89
Flip N File 50	\$44.95
Diskminder (75)	\$33.95
Dysan	\$39.00
BASF	\$34.00
BASF with case	\$35.00

PRICE POLICY

Remember that at Exceltronix all prices are negotiable for quantity purchases. If you cannot afford large quantities on your own how about starting a Co-op.

CHARGE X

MAIL ORDERS
Send a certified cheque or money order (do not send cash). Minimum order is \$10 plus \$3 minimum for shipping. Ontario residents must add 7% provincial sales tax. Visa, Mastercard and American Express accepted: send card No., signature, expiry date and name of bank.



Head Office: 319 COLLEGE STREET, TORONTO, ONTARIO, CANADA. M5T 1S2 (416) 921-8941

Circle No. 27 on Reader Service Card.

SURPLUSTRONICS

we will not be undersold



Canadian Made

AS
Reviewed
in ETI
May 1983:
Send for a
FREE COPY

OUR FAMOUS 6502 BOARD

NOW NEW & IMPROVED VIDEO SECTION



This 6502 board is a vast improvement on others available:

- 64K RAM (8-4164 chips)
- 80 x 24 video included on board
- Floppy Disk Controller included
- FIVE additional slots
- Z80 blank PCB included
- Powerful power supply (5V 5A, +12V 2 up to 3A peak, -5V 0.5A, -12V 0.5A)
- Hydro-approved whereas many others are not!
- Superb quality plastic case
- Excellent keyboard including numeric keypad
- EPROMS (blank) included
- Available preassembled by special order only.
- Ideal for educational applications.

\$679

Our prices are low due to our mass production assembly, which makes it hard for others to compete.

NOW you receive a **FREE** Z80 PC BOARD AND **FREE** 128K RAM DISK PC BOARD when you order the complete package (either Kit or A&T) (BLANK

Our boards are professionally made, flow soldering & cleaned & use only high quality prime parts.



Introductory Offer

8088 System \$1,989

Best Prices in Canada

Complete System with 64K, expandable to 256K. Comes with Colour Graphics, Floppy Controller and one DS, DD 5 1/4" Disk Drive, Keyboard, Case and Extra Heavy-Duty, Fan Cooled Power Supply.

System comes with 5 peripheral slots. Optional 8087 arithmetic processor available. Floppy controller can handle up to 4 drives and as an option can a serial port and real-time clock. Completely built and tested and sold with a blank EPROM. Compatible with You-Know-Who. Systems are now in stock but due to extraordinary demand at time of going to press, order now to prevent delays. Please Note: We do not sell any proprietary software.



Peripheral Boards for your IBM PC

- Prototyping Card \$33.00
- Floppy Controller Card \$289.00
- Colour Video Card \$299.00
- Parallel & Game Port Card . . . \$149.00
- EPROM Programmer. Starts at \$149.00
- Expansion Card with many options \$Call

- Attractive Case (as shown above) \$85.00
- Keyboard (as shown above) . . \$187.00
- Super Power Supply, made to fit above case, with cooling fan. \$135.00

8088 Board, with 64K on board (provision for 256K), as described in our 8088 System.

Call for best prices in Canada! ! ! ! !

Huge variety of Surplus stock at low, low prices. New shipments arriving. No reasonable offers refused. Prices subject to change without notice!

Surplustronics, 310 College Street, Toronto, Ontario, M5T 1S3

Monitors

- ZVM-122 Amber \$149.00
- ZVM-123 Green \$129.00
- Roland Colour 1 \$395.00

EPS Keyboard \$399.00

Apple Compatible. IBM Module available. Distributor for Ogivar

Apple Peripherals Assembled and Tested

- Serial Card \$ 85.00
- Z80 Card \$ 58.00
- 80 x 24 \$ 84.00
- 16K RAM \$ 58.00
- Prototyping Board \$ 14.50
- Parallel Printer Card \$ 59.00
- ... with cable & connector . . . \$ 69.00
- 123K Board (No IC's) \$ 49.00
- ...with IC's & 64K RAM \$129.00
- ...with IC's & 128K RAM \$210.00
- Crazy Card \$ 58.00
- Eprom Programmer \$ 68.00

Disk Drives

- Apple Compatible \$249.00
- Controller \$ 59.00
- ...w/software \$119.00

One year warranty

All prices subject to change

Printers

- A. Gemini 10x \$359.00
- B. Special Multiflex parallel card with cable. Shop and compare . . . \$ 69.00
- Package price of A and B \$415.00
- Gemini 15x \$598.00

5" Green Screen Monitors. \$59

**Telex No.
065-24218**

Mail Orders add \$5.00 minimum for shipping & handling. Ontario residents add 7% P.S.T. Visa, Mastercard and American Express cards accepted: send card number, expiry data, name of bank and signature. Send certified cheque or money order, do not send cash.

Circle No. 29 on Reader Service Card
More lines to serve you better
(416) 960-1350

ETI Special Reader Offer

ZX81/TS1000 Products at Genuine 50%-80% Savings!



1. ZX FORTH

Programming language

FORTH is an inter-active compiled language with the simplicity of BASIC at ten times the speed. ZX FORTH is a full implementation, with 250 commands. It works on 16-bit numbers, has some 32 bit routines, includes a 60-page user/programmer manual.

Regular \$39.95 **\$14.95**

The withdrawal of Timex from the home computer market means that support products for the ZX81 and TS1000 will be in short supply in the future. We know from reader surveys that about 5,000 readers already have one of these computers - so we have made special arrangements to supply ETI readers with a selection of these products at very special prices.

We honestly believe that readers will not want to miss out on these very special prices but it is a time limited offer, we must receive your orders by July 6th, 1984.

2. HOME & BUSINESS MANAGEMENT

VU-CALC. Financial Spreadsheet. Turns ZX81 into a powerful tool to generate and calculate large tables for budgets, financial analyses and projections.

VU-FILE. Data Storage and Filing System. Ideal for name/address files, lists, catalogue of items, etc. You can enter, list, search and print records.

Regular \$39.90 **\$14.95**

3. PROGRAMMING AIDS

ZX ASSEMBLER. Full Editor/ Assembler and Monitor. Comprehensive instruction book included.

ZX BUG. Machine Code Monitor and Disassembler. Adds 28 commands. Complete instruction book.

Z AID. Adds 5 new BASIC instructions.

Regular \$59.85 **\$19.95**

4. GAMES PACK

GALAXIA - Arcade classic

INCA CURSE - Adventure word game

CONCENTRATION - Family strategy and memory test

CHESS - Simple 1K version

(We reserve right to substitute similar games)

Regular \$79.80 **\$19.95**

5. BASIC LEARNING COURSE

with 2 software cassettes. Complete comprehensive learning guide and reference text. Covers every command and function. Actual programme samples are provided in text and on accompanying tapes. Supplied in a 3 - ring vinyl binder.

Regular \$39.95 **\$19.95**

6. PROFESSIONAL KEYBOARD & CASE

Adds full space bar and touch typing convenience for word-processing and other applications. ZX81 fits inside case. Keys rated 20 million cycles.



Regular \$144.95 **\$69.95**

7. 64K RAM

The ICs alone are worth more than the cost of this complete cased 64K memory expansion (8 x MK 4564). Plugs directly to ZX81 or TS1000. Expands the Z80A CPU to its addressable maximum.



Regular \$159.95 **\$69.95**

Send to: ZX81/TS1000 Offer, Moorshead Publications, 25 Overlea Boulevard, Suite 601 Toronto, Ontario, M4H 1B1

Please send me the following. I enclose payment (cheque or money order) made out to Moorshead Publications.

- # 1 ZX Forth at **\$14.95**
- # 2 Home and Business Management Software at **\$14.95**
- # 3 Programming Aids at **\$19.95**
- # 4 Games Pack at **\$19.95**
- # 5 Basic Learning Course at **\$19.95**
- # 6 Professional Keyboard and Case at **\$69.95**
- # 7 64K RAM Pack at **\$69.95**

Sub-Total

Ontario Residents add 7%

Shipping. \$1.50 1st item, \$1.00 for each extra

Total

Name

Address

City

Province

Postal Code

Items are ex-stock but please allow reasonable time for delivery

Offer expires July 6th, 1984

Please use this coupon or a photocopy to place your order.

Electronics Today




Audit Bureau
of Circulation

June 1984

INTERNATIONAL

Vol. 8, No. 6 ISSN 07038984

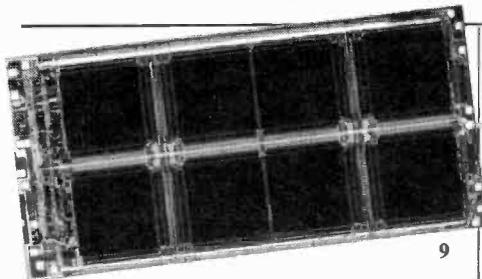

9

Features

9

Genealogy Of The Microchip

The history of the development of those little silicon wonders, by Roger Allan.

19

Computer Review

The MPF-III revealed. A kind of semi-clone?

24

Operation Plowshare

Nuclear landscaping and mining, what is (was) it all about? Roger Allan uses conventional writing techniques to dig up the facts.

33

Circuit Supplement

Circuits, circuits and more circuits!

42

Computing Today:

Is your ZX81 starving for new programs? Here's a few to keep its CPU from grumbling.

45

Coping With Components

Part one, how to make heads or tails of the megatypes of resistors available.


62

Machine Language Series Part 1

Thinking of communicating with your CPU? Try speaking its language.



24

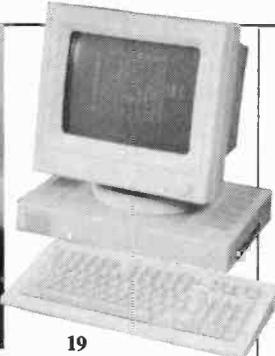

19

Projects

14

Echo Reverb

Get that big hall sound with this little marvel... marvel... marvel...

30

Modem Auto Answer Add-on

It's time you taught your "dumb" modem a new trick.

53

Low Cost Dwell Meter

If you've been pondering tuning up your car, don't dwell on it any longer. Here's a gadget that'll help save you time and \$\$\$

Columns, News and Information

For Your Information	6
Binders	51
Order Form	51
Book of the Month	52
Subscriptions	52
ETI Bookshelf	57
Next Month	61
Tech Tips	67
Fun of Electronics	69
Product Mart	70

Our Cover

The Auto-Answer modem converter project appears on page 30 and the Multiflex computer review on page 19; photos by Bill Markwick.

Electronics Today is Published by:

Moorshead Publications
Editorial and Advertising Offices
Suite 601, 25 Overlea Boulevard,
Toronto, Ontario, M4H 1B1
Telephone (416) 423-3262

Editor:
Editorial Assistant:
Director of Production:
Creative Manager:
Production:

William Markwick
Edward Zapletal
Erik Blomkwist
Ann Rodrigues
Douglas Goddard
Neville Williams
Naznin Sunderji
Deedee Whitehead

Circulation Manager:
Advertising:

Lisa Salvatori
Omar Vogt

Advertising (Que.): **John McGowan & Associates**
(514) 735-5191

Publisher: H.W. Moorshead; **Executive Vice-President:** V.K. Marskell; **General Manager:** S. Harrison; **Controller:** B. Shankman; **Accounts:** P. Dunphy; **Reader Services:** C. Wyatt, S. Halladay, H. Brooks, K. Adams; **Advertising Services:** C. Zyvitski, **Dealer Services:** A. Nagels.

Newsstand Distribution:
Master Media, Oakville, Ontario

Subscriptions
\$19.95 (one year), \$34.95 (two years). For US add \$3.00 per year, other countries add \$5.00 per year. Please specify if subscription is new or a renewal.

Postal Information
Second Class Mail Registration No. 3955. Mailing address for subscription orders, undeliverable copies and change of address notice is:
Electronics Today International, Suite 601, 25 Overlea Blvd., Toronto, Ontario, M4H 1B1.

Advertisers' Index

Active Components Sales Corp.	10
Alps International & Co.	68
Arkon Electronics Ltd.	37
Audiovision	65
BCS Electronics Limited	15, 22
Brunelle Instruments Inc.	44
Budgetron Inc.	63
Computer Parts Galore Inc.	23
Daetron	44
Electronic Book Club	25
Electronic Control Systems	52, 67
Electronic Packaging Systems Ltd.	46
Exceltronix	2, 72
H. Rogers Electronic Instruments Ltd.	50
J.A.C. Electronics	18
Kaientai Electronics Merchants Ltd.	29
Kitstronic International Ltd.	48
Locast Computer Systems Corporation	12
McGraw-Hill	13, 21
Metermaster	55
Orion Electronics Supplies Inc.	8
Perfect Electronics Inc.	46
Protec Microsystemes Inc.	7
Surplustronics	3

for your information

Copyright

All material is subject to worldwide copyright protection. All PCB patterns are copyright and no company can sell boards to our design without our permission.

Liability

While every effort has been made to ensure that all constructional projects referred to in this magazine will operate as indicated efficiently and properly and that all necessary components are available, no responsibility whatsoever is accepted in respect of the failure for any reason at all of the project to operate efficiently or at all whether due to any fault in the design or otherwise and no responsibility is accepted for the failure to obtain component parts in respect of any such project. Further no responsibility is accepted in respect of any injury or damage caused by any fault in design of any such project as aforesaid.

Editorial Queries

Written queries can only be answered when accompanied by a self-addressed, stamped envelope. These must relate to recent articles and not involve the staff in any research. Mark such letter ETI Query. We cannot answer telephone queries.

Binders

Binders made especially for ETI are available for \$9.25 including postage and handling. Ontario residents please add provincial sales tax.

Back Issues and Photocopies

Previous issues of ETI Canada are available direct from our office for \$4.00 each; please specify by month, not by feature you require. See order card for issue available.

We can supply photocopies of any article published in ETI Canada; the charge is \$2.00 per article, regardless of length. Please specify both issue and article.

Component Notation and Units

We normally specify components using an international standard. Many readers will be unfamiliar with this but it's simple, less likely to lead to error and will be widely used everywhere sooner or later. ETI has opted for sooner!

Firstly decimal points are dropped and substituted with the multiplier: thus 4.7uF is written 4u7. Capacitors also use the multiplier nano (one nanofarad is 1000pF). Thus 0.1 uF is 100nF, 5600pF is 5n6. Other examples are 5.6pF = 5p6 and 0.5pF = 0p5.

Resistors are treated similarly: 1.8Mohms is 1M8, 56kohms is the same, 4.7kohms is 4k7, 100ohms is 100R and 5.6ohms is 5R6.

PCB Suppliers

ETI magazine does NOT supply PCBs or kits but we do issue manufacturing permits for companies to manufacture boards and kits to our designs. Contact the following companies when ordering boards.

Please note we do not keep track of what is available from who so please don't contact us for information on PCBs and kits. Similarly do not ask PCB suppliers for help with projects.

K.S.K. Associates, P.O. Box 266, Milton, Ont. L9T 4N9.

B—C—D Electronics, P.O. Box 6326, Stn. F, Hamilton, Ont. L9C 6L9.

Wentworth Electronics, R.R. No. 1 Waterdown, Ont. L0R 2H0.

Danocinths Inc., P.O. Box 261, Westland MI 48185, USA.

Arkon Electronics Ltd., 409 Queen Street W., Toronto, Ont., M5V 2A5.


Beyer & Martin Electronic Ltd., 2 Jodi Ave., Unit C, Downsview, Ontario M3N 1H1.

Spectrum Electronics, 14 Knightswood Crescent, Brantford, Ontario N3R 7E6.

A New Apple

The Apple IIc, a 7½ pound computer, compatible with more than 10,000 productivity, education and entertainment applications, has been introduced by Apple Canada Inc. Aimed primarily at the serious home computer market, the IIc is also appropriate for business or educational applications. The new computer is a miniaturized transportable addition to the popular Apple II line of personal computers. The IIc has 128 kilobytes of built-in memory, which is ample for a wide variety of personal-productivity applications, such as word processing, tax planning and home budgeting. Because of the existing base of educational software for the Apple II product line, the IIc is also appropriate for home educational applications. In addition, the new computer runs a variety of entertainment programs. For only \$1,895, the IIc includes the central processor, keyboard and disk drive in one unit. A disk-based owner's manual/computer-literacy course teaches those unfamiliar with computers what they can do with the IIc and how to do it. The course helps users learn about the IIc while actually using the computer. Once the IIc is hooked up to a television set or separate monitor, the user has everything necessary to get started.

Circle No. 60 on Reader Service Card.

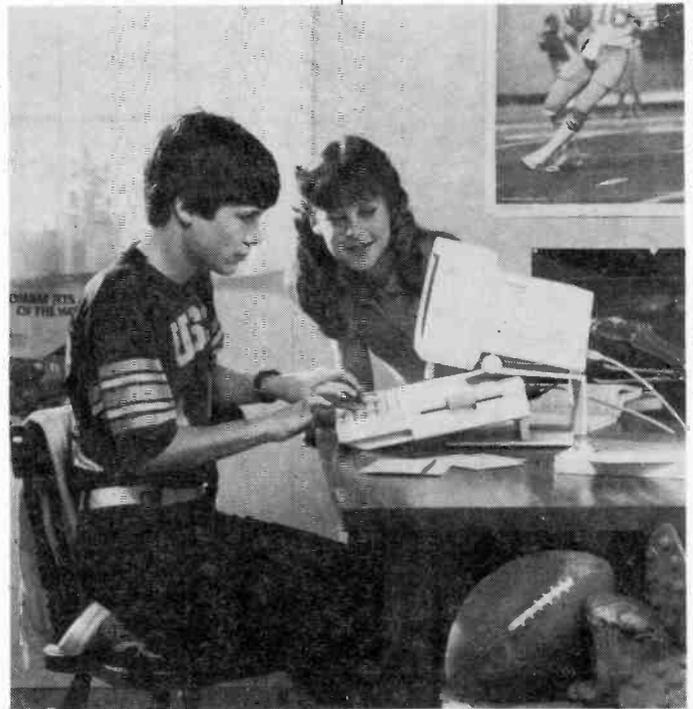

Protection Device

Motorola has introduced its first SMARTpower™ II device, which combines the best qualities of high speed CMOS logic and high-current TMOS vertical power structuring on a single chip. The MPC2005, an overvoltage and temperature protection circuit, is the first Motorola device to utilize this new technology. Previous Motorola SMARTpower™ efforts


combined CMOS and bipolar characteristics. Capable of discharging capacitors with peak currents of 150 amps, the MPC2005 can operate at up to 15 amps of continuous anode current. When voltage exceeds 6.2 V or the junction temperature rises over 125°C, the device will trip and remove the voltage from the system. A single device can replace three resistors, an SCR, and an IC.


Circle No. 58 on Reader Service Card.

Bi-Amplified Car Speaker

A bi-amplified speaker component system which represents a departure from traditional car speaker design configurations is being introduced to the Canadian market by Sparkomatic Canada, Inc., 265 Hood Rd., Markham, Ont. The new Amplidyne Series speakers are designed for the electronics market as well as for the company's established automotive after-market retailers. Included in the series are a coaxial speaker system, two deck-mount systems and a subwoofer. Each of the speaker systems incorporates separate amplifiers for the woofers and tweeter, with each pair offering 120 Watts of additional power.

Circle No. 59 on Reader Service Card

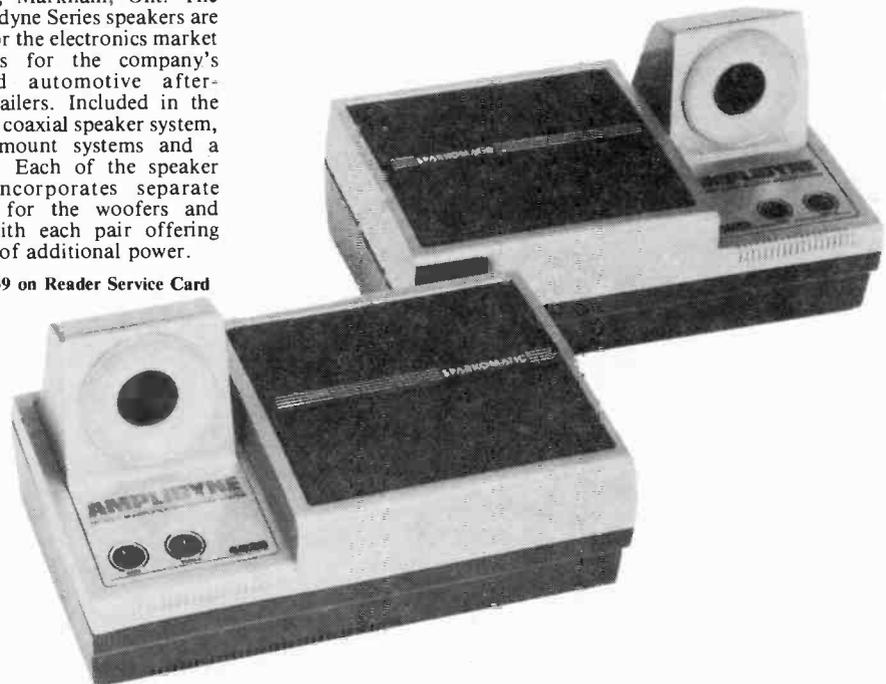

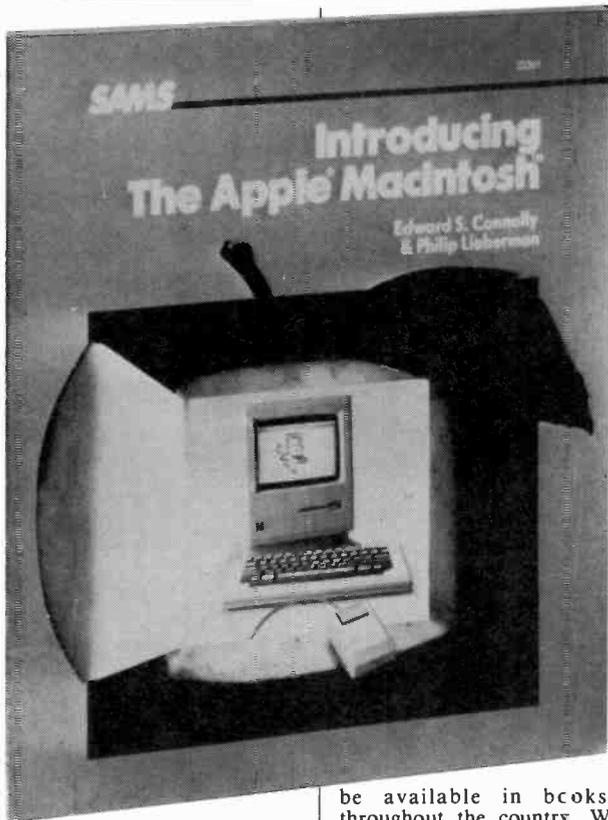

Macintosh Manual

Howard W. Sams and Co., Inc., a Subsidiary of ITT Corporation, has released one of the industry's first books which thoroughly describes Apple Computer Inc.'s new Macintosh microcomputer for both new users and prospective buyers. *Introducing the Apple® Macintosh™* (ISBN 0-672-22361-9) is a comprehensive look at this new machine. The 189-page, illustrated volume will

be available in bookstores throughout the country. Written by Edward S. Connolly and Philip Lieberman, experts in the fields of system integration, operation and microcomputer design, *Introducing the Apple Macintosh* thoroughly explains all there is to know about the Macintosh. Both Connolly and Lieberman worked closely with Apple in their research for the book, enabling them to include accurate information on all the hardware and software elements of the Macintosh.

Circle No. 57 on Reader Service Card.


Instrumentation Amplifier

A single-chip instrumentation amplifier introduced by Analog Devices, Inc. replaces expensive modular and hybrid programmable gain amplifiers (PGA) in switched-gain applications. With the addition of an inexpensive CMOS multiplexer and resistor network, the AD625 facilitates designing 12-bit accurate software programmable gain amplifiers (SPGA) for under \$20 (U.S.). This capability, combined with the industry's best nonlinearity of 0.001% maximum, lowest gain tempco of 5 ppm/°C maximum, and lowest input noise of $4nV/\sqrt{Hz}$ makes the AD625 well

suited for precision applications including weigh scales, industrial measurement systems and laboratory instrumentation.

The AD625 can be configured as either a resistor programmable gain amplifier (RPGA) or as an SPGA. An AD625-based RPGA can be configured for gains between 1 and 10,000 with three external resistors. With precision low temperature coefficient resistors, users can achieve 14-bit performance. In addition, the AD625's gain sense pin has 130 dB of common-mode-rejection regardless of feedback resistor matching. Contact: Tracam Electronics, 1200 Aerowood Dr., Mississauga, Ont. (416) 625-7752.


Circle No. 56 on Reader Service Card.

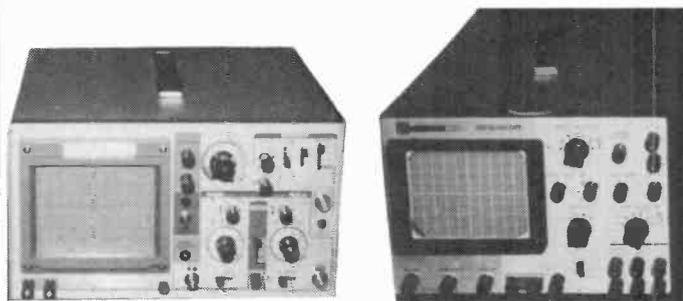

Test Equipment


KB Electronics, 1289 Marlborough Crescent, Unit 12, Oakville, Ont., L6H 2R9, have a wide range of test gear available, including the 905 Sweep/Marker Generator, the 605 RF Signal Generator, the 505 Oscilloscope, the G431 Function Generator, and more. The low-cost 505 is of particular interest to the experimenter. Contact them at the above address, or phone (416) 842-6888.

Circle No. 55 on Reader Service Card

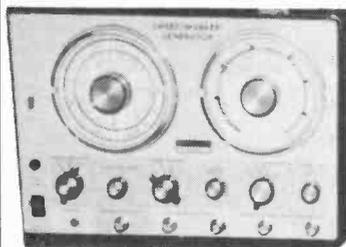

PLEASE MENTION ETI WHEN REPLYING TO ADVERTISEMENTS.

SELF-CONTAINED EPROM COPIER/PRO-GRAMMER

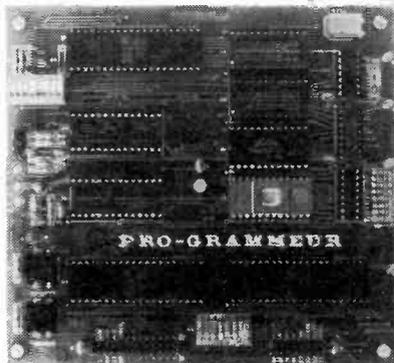

- Includes its own Z80-A processor
- Needs no personality module
- Copies: 1, 2, 4 & 8K bytes single supply EPROMs
- Comes with a powerful 4K bytes-monitor

ONLY \$99.00* (kit)


FREE

Call or write for your free copy of the products catalogue we manufacture

With this KBH interface, you can modify your EPROM content or load a new code in the PRO-GRAMMER's RAM before transferring on EPROM. You can also access several operation modes such as:

- Memory and register examine and change
- Insert/delete one or many bytes anywhere in a program
- Break point execution mode
- Block transfer mode
- and much, much more

ONLY \$59.00 kit

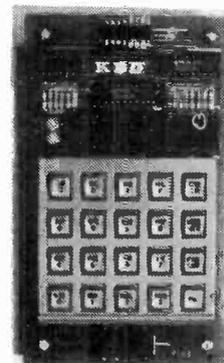

PROTEC MICROSYSTEMES INC.


725 Decarie Suite 202, St. Laurent, Que. H4L 3L4
(514) 744-3363

*Add 3% shipping and handling. Quebec residents: add 9% P.S.T. Cheque, money order, visa accepted. Please print your name, visa no. expiration date & signature.

Circle No. 16 on Reader Service Card

ETI—JUNE—1984—7

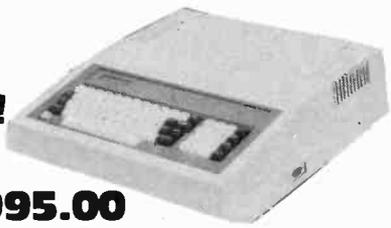**WINNER:
Ultra-modern!
Super-efficient!
Fully Apple
Compatible \$995.00**




Please note the distinct features
Winner offers:

- *Dual microprocessors 6502 & Z-80A
- *RS-232 built in
- *Disk drive Interface card built in
- *40/80 column text display and auto change video output port by soft switch
- *76K RAM with 4 expansion slots

- *16K ROM
- *DOS 3.2 & DOS 3.3 capability
- *Apple & CP/M compatible
- *ASCII keyboard with function keys and a numeric keypad
- *Upper/lower case
- *Streamline case
- *OS could be changed when desired without affecting other memory RAM

**CP80 DOT MATRIX
PRINTER**

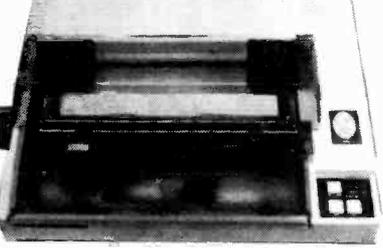

7X8 DOT MATRIX
80 CPS, 640 dots/line per second
Bidirectional
80 Column normal **\$495.00**
142 Compressed
Friction & Tractor Feed
Standard Centronics Parallel
Same as EPSON 80

TTX™ 1014



\$595.00

RELIABLE DAISY
WHEEL RO PRINTER

1014 FEATURES

- SERIAL AND PARALLEL INTERFACE
- WORDSTAR™ COMPATIBLE
- QUIET OPERATION
- PROGRAMMABLE PITCH AND LINE SPACING
- COMPACT AND DURABLE
- MICRO, MINI, MAINFRAME COMPATIBLE
- INTEGRAL PIN FEED GUIDE (ADJUSTABLE)
- RIBBON CARTRIDGES AND PRINT-WHEELS READILY AVAILABLE.

SEE OR CALL ABOUT OUR EXTENSIVE LINE OF PRINTERS.

**APPLE COMPATIBLE
COMPUTERS**

- 48K Color Computer with numeric keys & function keys \$549.95**
- 64K Color Computer with numeric and function keys \$598.95**
- 64K Color Computers (Dual-6502 & Z80A, CP/M), Numeric & function keys \$649.95**
- For systems one 12" Green Monitor, 1 Disk Drive & Disk Controller card \$500.00**

**All above Systems
with New IBM™
Styling 100.00 extra**



- Detachable Keyboard
- Programmable Function Keys
- Built in Key Words for Apple™ Soft, DOS
- Room for two Slim Line Drives



Mini Modem \$99.45

Parts

DB-25P Connector	\$ 4.95
DB-25S Connector	\$ 5.95
Covers for 25's	\$ 2.25
DB-9P	\$ 3.95
DB-9S	\$ 4.95
Covers for 9's	\$ 1.98
2716 EPROMS	\$ 6.95
2764 EPROMS	\$14.95
4164 RAMS 200 N/S	\$ 9.75
4116 RAMS 200 N/S	\$ 1.75
2016 RAMS	\$ 9.75
EPROM ERASERS P.E. 14	
8 at a time	\$129.95

Disk Holders

Disk Bank (50 Disks)	\$39.95
DX 85 (55 Disks)	\$39.95
Data Defender (70 Disks)	\$39.95
Flip "N" File 10	\$ 8.95
Flip "N" File 15	\$13.95
Flip "N" File 25	\$34.95
Flip "N" File 50	\$44.95
Flip "N" File Original 50	\$29.95

Diskettes

Xidex SS/DD	\$29.95
Xidex (Plain Box) SS/DD	\$24.95
Xidex DS/DD	\$39.95
3M Diskette SS/DD	\$29.95
Verbatim (Datalife) SS/DD	\$34.95
Maxell MD 1-DS/DD	\$34.95
Maxell MD 2-DD/DD	\$49.95
Dysan SS/SD 104-1	\$29.95
Dysan SS/DD 104-2	\$34.95
Dysan DS/DD 204-2	\$49.95
Disk Cleaning Kit Recoton	\$34.95

6502 BOARDS & ACCESSORIES Timex Sinclair 1000



**Swivell
Monitor
Amber
GM 1211 \$165.00**

More Monitors

Roland CB 141 Colour	\$395.95
Amdek Colour	\$395.95
GM 1201 Green 12"	\$149.95
GM 1201 Amber 12"	\$159.95
Zenith Green 12"	\$139.95
Zenith Amber 12"	\$149.95

More Available

ABB-1	\$45.00	AKB-2	\$99.00
APPLE II Compatible.		Keyboard: Numeric	
Dual CPU Bare Board		Keypad with Function	
Comm Card	\$99.00	Keys, replacement for	
Serial Interface RS232C		APPLE II.	
Card for APPLE II c/w		AC 2	\$89.00
Cable & Manual.		Beige APPLE II Case (for	
AIC-1	\$89.00	above Keyboard)	
Integer Card		Case & Keyboard	
AEC-1	\$89.00	Numeric	\$175.00
80 Column Card		APS-2	\$99.00
AZC-1	\$79.00	Switching Power Supply	
Z80A (CPM) Card		for APPLE II, + 5V 5	
APC-1	\$89.00	amps, + 12V @33 amps	
Parallel Printer Card		5V @ 1/2 amp, 12V @ 1/2	
ASC-1	\$89.00	amps; c/w on-off switch &	
Serial Printer Card		connecting wires	
ALC-1	\$89.00	AAA-2	
16K RAM (Language Card		Dis Drives 5 1/4", APPLE II	
Speech Card	\$75.00	Compatible, Excluding	
Wild Card	\$80.00	Controller Card	\$299.00
Modem Card	\$175.00	With Controller	\$365.00
(Network)		ADC-1	\$89.00
40 Column Switch	\$9.95	Disc Drive Controller	
Colour RF Modulator		Card for two drives; Apple	
Set	\$25.00	II Compatible	
		APPLE II is a registered	
		trade mark of Apple Com	
		puter Inc.	

**Assembled
\$39.95
ZX81 Printer
\$99.00**

16K Sinclair Memory \$35.00

Books		Hardware	
COMPLETE ZX81 BASIC COURSE - Inc. 2	39.95	Sinclair Printers	99.00
1apes	19.95	Timex Printer	125.00
NOT ONLY 30 PROGRAMS, 1K	19.95	64K RAM (Memotech)	149.00
MACHINE LANGUAGE MADE SIMPLE	24.95	32K RAM (Memotech)	79.00
ZX81 ROM DISASSEMBLY PART A & PART B	24.95	16K RAM (Sinclair)	35.00
UNDERSTANDING ZX81 ROM	19.95	Memotech 16K RAM	39.95
1/5 1000 "PROGRAMS, GAMES and		500MA	8.95
GRAPHIC3	16.95	Memopak Centronics Type	
LEARNING TIS BASIC	8.95	Parallel Printer Interface	119.00
THE BASI2 HANDBOOK	29.95	Memopak ZX81 Keyboard	119.00
49 EXPLODING GAMES	16.95		
COMPUTER FOR KITS SINCLAIR EDITION	8.95		
MASTERING MACHINE CODE ON YOUR ZX81	24.95		
TIS 1000 USERS GUIDE (Vol 1)	16.95		
EXPLORER'S GUIDE TO THE ZX81	16.95		
ZX81 POCKET BOOK	16.95		
GETAWAY GUIDE	16.95		
GETTING AQUAINTED WITH YOUR ZX81	16.95		

**Additional Hardware & Software
for the SINCLAIR ZX81
AVAILABLE ON REQUEST.**

**Orion Electronic
Supplies Inc.**
40 Lancaster Street West
Kitchener, Ontario N2H 4S9
(519) 576-9902


Master Charge & Visa, COD, Cheque,
Money Orders accepted. COD's, shipping & insurance extra. Write for our FREE FLYER.

Prices subject to change without notice.

Genealogy of the Chip

Roger Allan looks at bells, whistles and family trees.

by Roger Allan

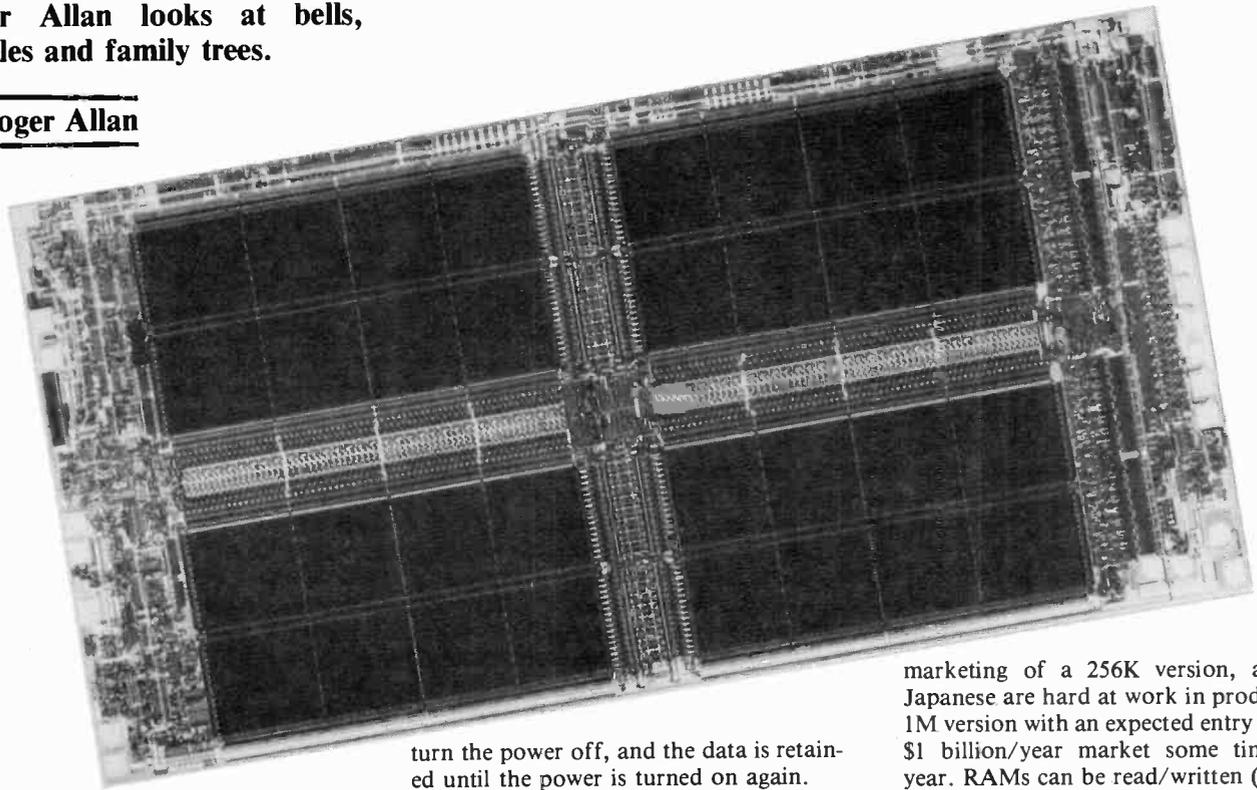

EXAMINING THE background of integrated circuit chips is a bit like engaging in family genealogy — the deeper one delves, the more the branches and rootlets appear to have relevance. When the rootlets become intertwined, matters can momentarily become somewhat complicated. The next few years, if researchers' predictions are correct, will see the advent of whole new orders and classes of IC memories — whether direct or indirect products of the Japanese Fifth Generation Computer, or from such companies as Motorola, Harris, Xicor, Intel, United Technologies — the list seems endless. As such, a quick overview of what there is, what it can do, and where it is leading us seems appropriate.

In a magazine of this type, it is all but trite to mention RAMs and ROMs — one is almost expected to know what they mean before opening the cover. But in the interest of completeness, and as the Red King said to Alice, "begin at the beginning, proceed to the end, and then stop."

Random Access Memories (RAMs) lose their data when power is removed, that is, they are volatile. Read Only Memories (ROMs) are non-volatile —

turn the power off, and the data is retained until the power is turned on again.

There are two types of RAMs — dynamic and static. Dynamic RAMs are the most widely used of memory chips in computers. They are very simple — each cell, which determines the 1 or 0 in binary code, consists of a single transistor and a single capacitor. The transistor pumps electrical charge into and out of the capacitor — that is, they read and write the cells into 1's or 0's. The capacitor stores the charge, providing the memory. If the capacitor is charged, when read it will produce a 1, if uncharged, when read it will produce a 0. They are called dynamic because they need to be refreshed. That is, the charge held in the capacitor leaks off in a very short period of time, milliseconds at most. As such, between normal data reading and writing operations, this type of RAM must be read out, amplified, and re-written back into the cell. This refreshing program requires an additional circuit, and hence more power input. For a small device, such as a microcomputer, this additional circuitry burdens the total system. However, in large mainframe computers, a single refresh circuit is all that is required. To date, dynamic RAMs customarily involve 64K of memory, though this year we will see the mass

marketing of a 256K version, and the Japanese are hard at work in producing a 1M version with an expected entry into the \$1 billion/year market some time next year. RAMs can be read/written ('accessed') at the same high speed. They are mainly used as the prime data storage memories for micro-, mini- and mainframe computers, as they are very cheap to produce and quite reliable.

The second type of Random Access Memory is the static RAM. The advantage of this type is that while volatile, they do not need refreshing. The disadvantage is that they are rather complicated — unlike dynamic RAMs which require only a single transistor and a single capacitor per cell, static RAMs require six components — two voltage adjusting resistors, and four transistors per cell. The two transistors are cross-wired into a 'latch'. Each of these two latch transistors is in turn connected to a resistor and another transistor conforming a cell. The configuration is such that when one of the latch transistors is on, it generates sufficiently high voltage levels that the other latch transistor is automatically turned off. As such, the cell is either powered or unpowered, producing the 1 or 0 of binary code. The largest device of this type to date is a 64K memory, which involves some 400,000 transistors, resistors and peripheral circuitry components. The peripheral circuitry performs signal-conditioning and interfacing functions.

Genealogy of the Chip

Static RAMs are currently used for low-power versions of portable computers, high speed versions of mini-computers, and microcomputers utilizing small amounts of read/write memory storage. They cost two to four times as much as dynamic RAMS of comparable memory.

While all RAMs are volatile, all Read Only Memories (ROMs) are non-volatile. They have a further difference in that the speed with which their memories can be written, is far slower than the speed with which they can be read (usually — the rootlets are now becoming intertwined).

There are a number of types, predicated on their writing mechanisms.

The simplest is just called a ROM, though more technically, it should be called a mask ROM. When the ROM is being designed and manufactured, a lithographic mask, specific to the final memory content program is drawn. As such, a ROM can only contain one memory program or set of data. It's memory cannot be erased, nor can it be modified. Costing somewhat less than a dynamic RAM, a ROM is customarily used for program storage, storage for character sets in displays and

printers and function programs in pocket calculators, etc. While each cell consists of only one transistor, recent research has expanded ROM's capabilities. To do this each cell, in the newer versions, consists of four transistors, each with a different current carrying capability. The reading process consists of determining what the current level is. As such, each cell in effect carries the memory equivalent of two binary bits of information (eg. two sets of 1s and 0s).

The second type of ROM is called a fuse Programmable Read Only Memory, or PROM. It is similar to a ROM in that once it is programmed, the memory cannot be changed. It differs in writing technique however, in that all PROMs manufactured are identical and contain no memory. Their internal geometry is similar to a ROM, with the addition of what is essentially a fuse. When the PROM is programmed, after manufacture and sequentially by individual cell, this minute fuse is blown if the cell is to contain a 1 and not blown if the cell is to contain a 0, thereby permanently storing the memory on the chip. Costing about the same as a dynamic RAM, it is not used much these days, except for experimental work in designing computers (where the housekeeping routines and internal software programs may have to be changed as development proceeds), some automobile applications, some military applications — in general, where a small number of non-volatile ROMs are needed, bypassing the set-up costs of the masks for ROMs. More recent designs align the fuse vertically rather than horizontally, thereby saving space and increasing density.

The third version of ROMs are the Erasable Programmable Read Only Memories or EPROMs — well known to those involved with computers, as they can be erased by exposing their internal circuitry to ultra-violet light. While EPROM's internal structure consists of only one transistor, they do require an additional electrode for erasure purposes, resulting in less density per chip. However, a new Intel EPROM structures it's internal geometry vertically, resulting in a density all but the same for a single transistor ROM.

The EPROM's internal construction is similar to a PROM minus the fuse. In this instance, when the EPROM is programmed, the electrical charge is captured by the individual cell, electrically altering its characteristics. When read, this change is detected and read as a 1; or if there is no change, then the program is read as a 0. While exposing the EPROM to ultra-violet light before re-programming is cumbersome (one has to take the IC physically out of the computer for a start), they do have the advantage of being re-programmed. To date, the highest



The One Stop Shop For All Your Electronic Needs!

Conveniently located across Canada

Montréal
5651 Rue Ferrier
Montréal, Québec
H4P 1N1
(514) 731-7441

Ottawa
1023 Merivale Road
Ottawa, Ontario
K1Z 6A6
(613) 728-7900

Toronto
14 Carlton Street
Toronto, Ontario
M5B 1K5
(416) 977-7692

Calgary
3220-5th Ave. N.E.
Bay 2
Calgary, Alberta
T2A 5N1
(403) 235-5300


Downsview
86 St. Regis Cr. N.
Downsview, Ontario
M3J 1Y8
(416) 630-0400

Vancouver
3070 Kingsway
Vancouver, B.C.
V5R 5J7
(604) 438-3321

* Mail Orders to Montreal Address.

Visit your nearest Active store, call, write or circle
the Reader Service Card for your copy of Active's new catalog.

Circle No. 25 on Reader Service Card

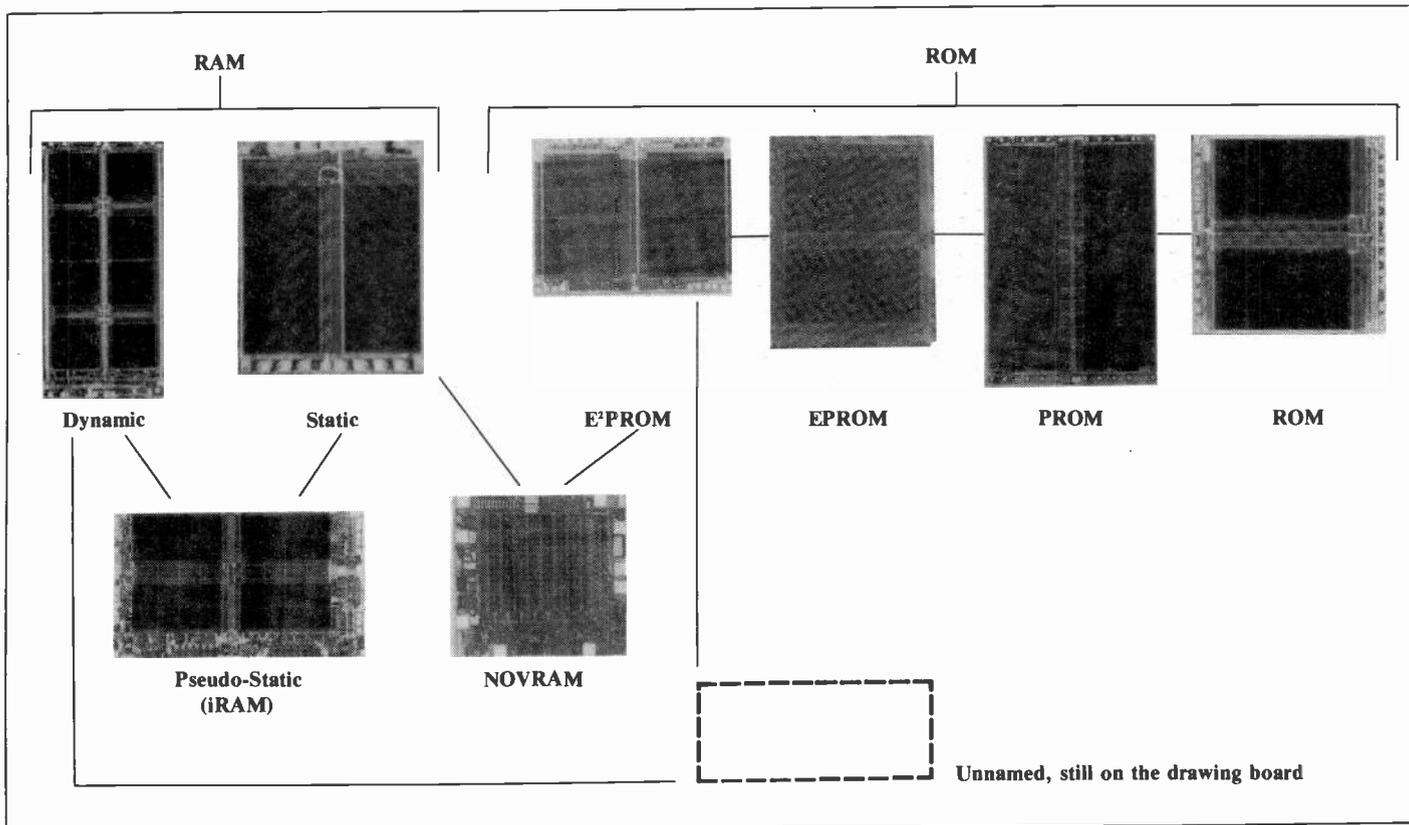

The history of the Chip family

density has been achieved by Intel's 256K EPROM, though larger devices are in the design stage. Customarily, they are used for the same sort of purposes as the ROM, plus extensive usage in the design stages of computers when software debugging is a problem.

The fourth version of ROMs are the Electrically Erasable Read Only Memories, or E²PROMs. Similar to EPROMs, E²PROMs require an externally applied current charge to transform the charges trapped in the individual cells, as opposed to removing them, exposing them to ultra-violet light, and reprogramming them. The erasure process can be done internally and electrically. The difficulty with this type of ROM is that the electrical voltage required to transform the cell's configuration must be substantially higher than the 5 volts customarily used in computer memories. For years, the voltage had to be upwards of 20 volts, though more contemporary designs have lowered the level to 12.5 volts. As such, a separate power supply and appropriate circuitry is required, increasing the cost.

E²PROMs have passed through a number of generations. The earliest ones were merely Electrically Alterable ROMs (EAROMs). They were/are reprogrammable only after an entire memory array (or at least one page of an array) was electrically erased. In other words, to make a single change in one cell, one had to wipe the entire memory clean and start all over.

Second generation E²PROMs required erasure of individual bytes before reprogramming serially. That is, one had to start with the first cell and work through until one reached the cell one wished to modify, change it, then go back to the beginning and re-program all cells up till the one you just modified. Third generation E²PROMs automatically and internally erase a to-be-written byte as part of the write cycle, and they also contain much of the required voltage generating and pulse-shaping functions internally on the chip.

The fourth generation E²PROMs have on-chip generation of all high-voltage and wave-shaping functions, in addition to their use of on-chip latches and self-timing features. Their byte-write requirements are identical to those of a static RAM except that the E²PROM write cycle takes as long as 10 msec. Once a byte-write operation begins, the E²PROMs are self-supporting, freeing the processor and all external circuitry for other tasks. Read timing of the E²PROM is identical to that of a standard EPROM, RAM or ROM.

One of the more interesting characteristics of the E²PROM is that an EPROM or ROM based system only needs an additional Write Enable line to each socket to provide retro-fitting of an E²PROM. The E²PROM's internal architecture is a two transistor floating latch arrangement with 64K versions currently

marketed. Their main usage is for program or data updating, such as warehouse stocks or pricing lists.

Hybrids

Having covered the major generic forms of RAMs and ROMs, one now approaches the hybrids — IC memories which do not 'fit' the generic forms, pulling strengths and weaknesses from more than one generic type.

The first is a hybrid, crossing a dynamic RAM and a static RAM. It is called, not surprisingly, a pseudo-static RAM, though in its most popular version (a 64K chip manufactured by Intel, soon to be increased to 256K), it is known as an iRAM.

The major advantage of a dynamic RAM is its simplicity — it requires only a single transistor and a single capacitor, thereby permitting a high density configuration. Its major disadvantage is that its memory needs refreshing via an external circuit. The major advantage of a static RAM is that they do not need refreshing. Its major disadvantage is that it requires a complicated internal geometry consisting of four transistors and two resistors.

An iRAM cross-breeds the advantages of both, while minimizing the disadvantages of both. Its internal geometry consists of a single transistor per cell, permitting high density like that of a dynamic RAM. However, it also has an on-board

refresh circuit which operates at the same voltage as the IC, but does not require an external circuit. In other words, during idle periods (that is, when the individual cell is either not being read nor written), the chip automatically refreshes itself. The question of when to refresh is answered by an on-board 'arbitration' circuit. As such, the iRAM combines a density almost equal to a dynamic RAM, with the refreshing ability of a static RAM. It is primarily used in medium-sized computer systems due to its relatively high cost.

The second form of hybrid comes under a variety of names — shadow RAM, non-volatile shadow RAM, etc. In its most complete form to date (in a 1K version manufactured by Xicor), it is known as NOVRAM.

A major advantage of static RAM is its fast read-write cycle; a major disadvantage is its volatility. The major advantage of an E²PROM is its nonvolatility and re-programmability, a major disadvantage is that it can be re-written only a finite number of times before wearing out (i.e., it only needs a single cell, among the tens of thousands that compose the IC, to fail to render the entire chip redundant).

Essentially, the NOVRAM consists of marrying a static RAM with an

E²PROM, cell by cell — eg., the combination of two memory technologies on a single chip. In the NOVRAM, data gets read and written exactly as in a standard static RAM. In addition, the Store signal transfers each of the RAM's cell data into a shadowing E²PROM cell and the E²PROM's cell's stored data is reloaded into the RAM portion of the chip via a Recall signal. This device's most powerful feature is its ability to transfer the entire RAM contents into non-volatile storage in one operation (eg., in parallel, rather than in series). This operation takes less than 10 msec., and once data is stored in this fashion, only another Store operation can alter it even if the chip loses power. Generating Store in the event of a power failure therefore saves the entire RAM contents, subject only to the power remaining on the chip for 10 msec. In the event of a power failure, one has between 20 and 40 msec. to play with. An on-board circuit can detect this, and thereby automatically initiate the 'saving' operation. As such, the NOVRAM combines the speed of a static RAM with the non-volatility of an E²PROM, and since the E²PROM is not used very often (only when there is a power failure or when the machine is turned off), it increases the life

expectancy of the chip.

The NOVRAM also contains another unique piece of circuitry. An E²PROM requires an external circuit producing some 12.5 volts to change a cell's content. This requires two currents into the IC — a 5 volt one for its general workings and a 12.5 volt one to change the individual cell's state. In the NOVRAM, an on-board circuit automatically generates the 12.5 volts from the 5 volt input with sufficient amperage to change the individual cell's state, but without requiring a separate external power circuit. In other words, everything is on one chip: a static RAM, an E²PROM and a voltage generator.

There is however, a disadvantage — size. Each double cell consists of six transistors and two resistors (for its static RAM portion) plus two transistors for the E²PROM portion of the double cell. With increased size comes decreased density.

And Finally . . .

The final hybrid may or may not exist, depending on who you talk to. Essentially, it consists of the marrying of a dynamic RAM (with its fast read/write cycle) and an E²PROM (with its non-volatility), the linkage between them being on a cell by cell basis. The advantage of such a device is that its density would be higher than the NOVRAM — dynamic RAMs only need two elements per cell (one transistor and one capacitor) rather than the static RAM's six (two resistors and four transistors). As such, this currently unnamed device would result in the speed of a dynamic RAM and the non-volatility of an E²PROM in a device consisting of only five elements per cell. There have been recent reports (erroneous) that such a device exists. However, upon investigation, one finds that such a device does not currently exist, but that the Mostek subsidiary of United Technologies in Texas is working on the fabrication problems involved. According to Tim Curran, of Mostek's Non-volatile Memory Group, while there is "no established program" to market such a device, Mostek is "doing the spade work" with respect to the fabrication problems involved.

Should such a device be built, it would be as close to a "perfect" IC memory as is currently envisionable. Should the technology then develop, and there is no real reason to believe that it won't be done sooner rather than later, the reality of marrying a pseudo-static RAM (with its automatic refresh circuits and high read/write speeds) and an E²PROM (with its non-volatility, power failure detection system and automatic 'save' all on-board) will have been achieved, possibly giving us the ultimate in IC memories.

ETI

Advanced PAL & EPROM CAD System

- PAL & EPROM programming system
- Program PAL's from standard logic equations
- On line manual available at all times
- Full screen editor for entering PAL equations
- Interactive PAL logic simulator
- Standard PAL assemblers for 20 & 24 pin PAL's
- Programs MMI, NATIONAL, TI, AMD PAL devices
- Programs all 5-volt JEDEC pin-out EPROMs (2716 through 27256)
- Uses new fast programming algorithm for larger EPROMs (2764 to 27256)
- New devices can be added to library through software updates
- Allows user to blow verify-protect fuse for PAL design security
- Includes card, diskette and external box with Zero Insertion-Force sockets

Requires IBM® PC® or XT® with 128k, 1 drive
Compatible with all PC/DOS releases

\$659.00

PROGGER by
Locust Computer Systems Corporation
622 Gladstone Avenue
Ottawa, Ontario
CANADA K1R 5P4 (613) 235-2294

send \$3.00 for demonstration diskette

Ont. res. add you-know-what for you-know-who.

© IBM, PC and XT are registered trade marks of IBM Canada Ltd.

Circle No. 18 on Reader Service Card

Learn robotics and industrial control as you build this robot

New NRI home training prepares you for a rewarding career in America's newest high-technology field.

The wave of the future is here. Already, advanced robotic systems are producing everything from precision electronic circuits to automobiles and giant locomotives. By 1990, over 100,000 "smart" robots will be in use.

Over 25,000 New Jobs

Keeping this robot army running calls for well-trained technicians. . . people who understand advanced systems and controls. By the end of the decade, conservative estimates call for more than 25,000 new technical jobs. These are the kind of careers that pay \$25,000 to \$35,000 a year right now. And as demand continues to grow, salaries have no place to go but up!

Build Your Own Robot As You Train at Home

Now, you can train for an exciting, rewarding career in robotics and industrial control right at home in your spare time. NRI, with 70 years of experience in technology training, offers a new world of opportunity in one of the most fascinating growth fields since the computer.

You need no experience, no special education. NRI starts you at the beginning, takes you in easy-to-follow, bite-size lessons from basic electronics right on through key subjects like instrumentation, digital and computer controls, servomotors and feedback systems, fluidics, lasers, and optoelectronics. And it's all reinforced with practical, hands-on experience to give you a priceless confidence as you build a programmable, mobile robot.

Program Arm and Body Movement, Even Speech

Designed especially for training, your robot duplicates all the key elements of industrial robotics. You learn to operate, program, service, and troubleshoot using the same techniques you'll use in the field. It's on-the-job training at home!

Building this exciting robot will take you beyond the state of the art into the next generation of industrial robotics.

You'll learn how your completely self-powered robot interacts



You get and keep Hero 1 robot with gripper arm and speech synthesizer, NRI Discovery Lab for electronic experimentation, professional multimeter with 3 1/2-digit LCD readout, 51 fast-track training lessons.

with its environment to sense light, sound, and motion.

You program it to travel over a set course, avoid obstacles using its sonar ranging capability. Program in complex arm and body movements using its special teaching pendant. Build a wireless remote control device demonstrating independent robot control in hazardous environments.

You'll even learn to synthesize speech using the top-mounted hexadecimal keyboard.

Training to Build a Career On

NRI training uniquely incorporates hands-on building experience to reinforce your learning on a real-world basis. You get professional instruments, including a digital multimeter you'll use in experiments and demonstrations, use later in your work. And you get the exclusive NRI Discovery Lab*, where you examine and prove out theory from basic electrical concepts to the most advanced solid-state digital electronics and microprocessor technology. Devised by an experienced team of engineers and educators, your experiments, demonstrations, and equipment are carefully integrated with 51 clear and concise lessons to give you complete confidence as you progress. Step-by-step, NRI takes you from the beginning, through today, and into an amazing tomorrow.

Send for Free Catalog Now

Send for NRI's big free catalog describing Robotics and Industrial Control plus over a dozen other high-technology courses. You'll see all the equipment you get in detail, get complete descriptions of every lesson, find out more about career opportunities for trained technicians. There's no cost or obligation, so send today. Your action today could mean your future tomorrow.




NRI SCHOOLS

McGraw-Hill Continuing
Education Center
330 Progress Avenue
Scarborough, Ontario M1P 2Z5
or telephone 416-293-8787

WE'LL GIVE YOU TOMORROW.

Echo-Reverb Unit

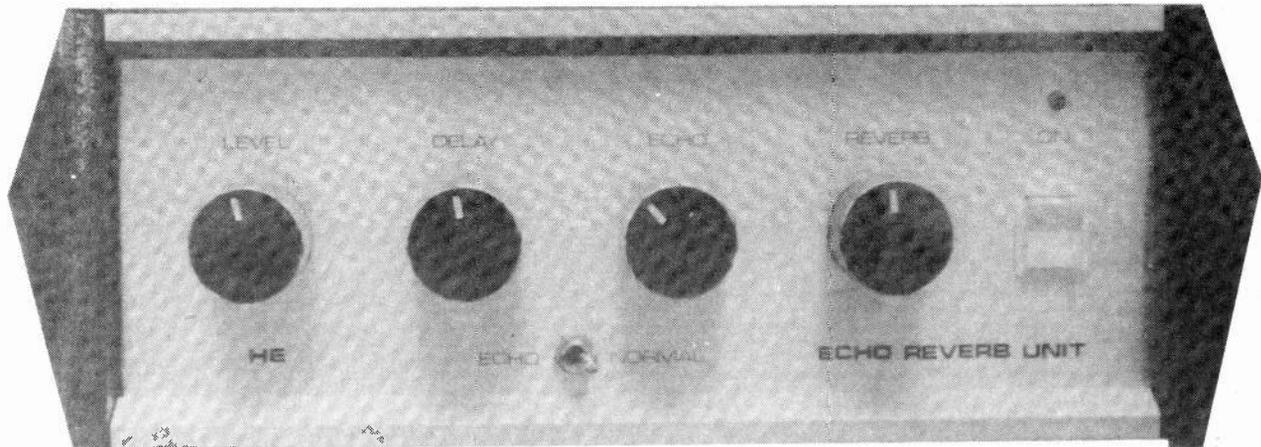

A superb project for creative musicians and audiophiles.

AN ECHO-REVERB unit is an accessory that can be added to virtually any existing audio or electronic music system and used to impart new life to existing sounds. In any audio system, the unit is simply interposed between the output of the preamp and the input of the main amplifier, so that the audio signals have to pass through the echo-reverb unit on their way to the main amplifier.

Some modestly-priced echo-reverb units use a crude mechanical spring-line to create the time-delayed echo-reverb and provide only a single, fixed delay time. Commercial (all electronic) echo-reverb units can be rather expensive, but provide fully-variable delay times. Many use clocked CCD (charge-coupled device) analogue ICs to implement the delays (see **How It Works**). The best commercial units use digital techniques to implement the delays, but these are extremely expensive!

We have used the analogue CCD technique to implement the time delays and the Echo-Reverb gives a performance that is at least as good as some commercial units using CCDs. The important thing about our unit, however, is that the design uses some clever techniques to reduce the hardware costs of its circuitry, while at the same time enhancing the overall performance and facilities.

Echo-Reverb

As the audio signals enter the echo-reverb unit they split into two paths which are reunited again near the output of the unit via a built-in-low-distortion audio mixer. One of these paths is a direct link from the input of the echo-reverb to the input of the mixer stage; the other path is via a variable signal-delay network. By varying the signal delay and then the mixture of direct and delayed signals, a variety of interesting effects can be obtained. Here are a few ideas to try:

- (1) With equal levels of direct and delayed signals, and a few milliseconds of delay, a 'double-tracking' or 'minichorus' effect is obtained. This makes a single input sound like a pair of independent but time-synchronised outputs. Thus, a single violin can be made to sound like a duet and a duet is made to sound like a quartet.
- (2) With a reduced level of delayed signal in the mix, and with a delay time of tens of milliseconds, a simple echo effect is obtained. The audio sounds as if it were being played in a softly furnished room where there is a single hard wall or reflective surface, facing the sound source. The apparent size of this room is directly proportional to the milliseconds delay time of the echo

unit, and is fully variable up to 50 feet (50 mS delay).

A standard feature of most echo units (including ours) is a Reverb facility. This allows a fraction of the output signal from the delay line *input*, so that you end up getting echoes of the echoes of echoes: By using only small amounts of feedback (often called 'Recirculation' or 'Regeneration' on commercial units), you get 'soft' reverb or, by adding lots of feedback, you get 'hard' reverb. A variety of impressive effects can be obtained from the reverb facility, as follows:



- (3) When equal levels of mixing are used with maximum (50 mS) delay and maximum feedback, the sounds seem as if they are being played in a large hard-faced cave or chamber. The apparent dimensions of this 'chamber' can be varied via the delay-time control, while the apparent 'hardness' of the chamber can be varied by altering either the mixing or reverb level controls. Thus, the apparent sounds can be varied from those of a hard cave, to a small church, or down to a large but softly furnished lounge.
- (4) When equal levels of mixing are used with short (a few mS) delays and a

HOW IT WORKS


THE STAGES for producing the various reverb effects from the Echo-Reverb, are shown in the block diagram. The main signal path comes from the output of the first mixer and through a 7 kHz low-pass filter. This filter is necessary to limit the audio band width to less than half the clock frequency, because the audio input is being *sampled* at the clock frequency (variable, to change the length of delay), and it is a fundamental principle of sampling that the sampling frequency must be at least twice the maximum input frequency. The filtered signal then passes through the delay line to a second low pass filter (at 15 kHz), which removes any clock signal residuals. This second filter includes a buffer amplifier to give the unit an overall gain of one. The output then splits into two paths; one is sent back to the input, to provide the reverb effect, the other goes to a final mixer via a switch. In the other position, the final mix can be varied from 'straight through' to full reverberation.

The delay circuitry comprises two charge coupled devices (CCD's) with 1024 delay stages. The diagram right shows an example of the internal structure of a MOS CCD IC. The principle may be compared to a line of firemen passing buckets of water from one end to the other — hence the name 'buckets' are capacitors and the 'water' is an electric charge which is pro-

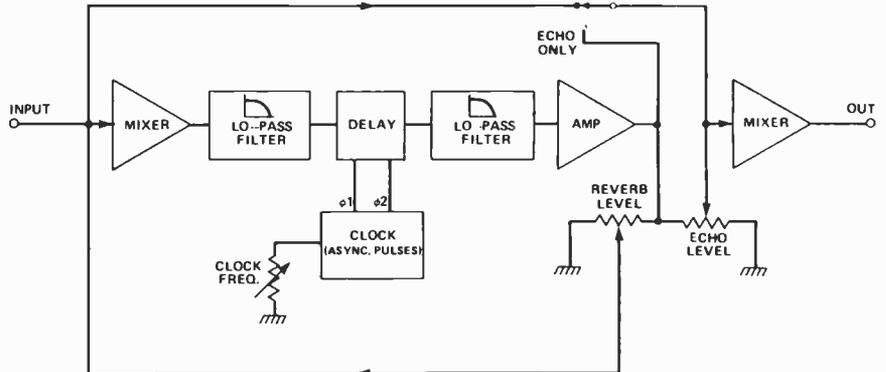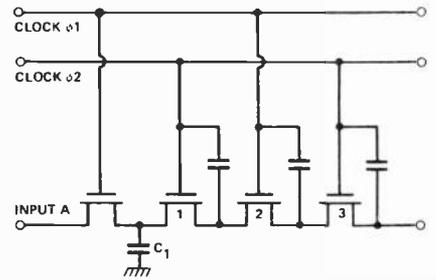portional to an instantaneous value of the input waveform — a sample. Each sample is stored briefly, then passed on to the next stage at the time of a clock pulse. Although each sample is stored for a very short time, at each stage, the time taken to 'clock' a sample from input to output can be as much as 50mS.



MODULAR PROBES FOR SALE

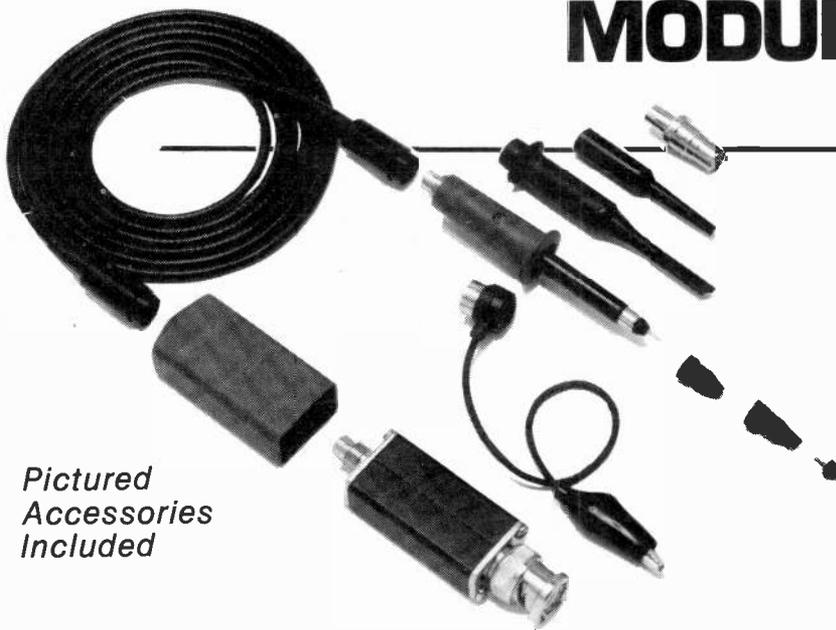

Pictured Accessories Included

For All Oscilloscopes
To 300MHz
X1 to X100
Attenuation

INSTANT REPAIR

Probe tip, Head, BNC and Cable
all screw into place
easily and quickly.



980 Ainess St. Unit 7,
Downsview, Ontario.
M3J 2S2
(416) 661-5585
TELEX 065-28169

Your Probe Specialists

COMPARE PRICE — COMPARE PERFORMANCE

Model	Attenuation	Bandwidth	Price
M12SW	X1-X10 Switchable	X1-10MHz X10-250MHz	\$56.80
M12X10	X10	250MHz	50.10
M12X10AP	X10 with Readout	250MHz	67.70
M15X100	X100	250MHz	56.80
M15X10HF	X10	300MHz	80.30
M12X1	X1	30MHz	42.40

Coline Canadian Sales & Stocking Source

via RV2 and the reverb can be varied with RV3.

The setting-up procedure is now complete and the unit can be cased and made ready for use, as already described.

PARTS LIST

RESISTORS

(all ¼ W 5% carbon)

R1	1k5
R2, 3	1k2
R4, 5, 11, 13, 23, 24, 25	100k
R6, 21	82k
R7	22k
R8	22k7
R9 16	6k8
R10	1k0
R12, 14	47k
R15	27k
R17	10k
R18, 20	180k
R19	120k
R22	4k7
R26	15k

POTENTIOMETERS

RV1	47 linear carbon
RV2	100k linear carbon
RV3, 4	22k linear carbon
PR1	4k 7 miniature pre-set
PR2	1M0 miniature pre-set
PR3	220k miniature pre-set

CAPACITORS


C1	1000u 40V electrolytic (axial)
C2	10u 35v tantalum
C3	680n polycarbonate
C4, 11, 12, 18, 19	220n polycarbonate
C5	150p ceramic
C6, 9, 14	100n
C7	330p polystyrene
C8, 10	100n polyester
C13	470p ceramic
C15, 17	220p ceramic
C16	33p ceramic
C20	1uO 35V tantalum

SEMICONDUCTORS

IC1	78L 15 voltage regulator
IC2, 6, 7	741 op-amp
IC3, 4	TDA1022 (Signetics) or DAC1022 (National) or TMS1022 (TI)
IC5	4046B CMOS phase locked loop
BR1	50V 1A bridge rectifier
DI1, 2	1N4148 signal diode

MISCELLANEOUS


T1	15 volt, 200 or 300 MA transformer
SW1	DPDT miniature rocker switch
SW2	SPDT miniature toggle switch
Sk1, 2	Phono Sockets
Case, PCB, bolts, knobs etc.		

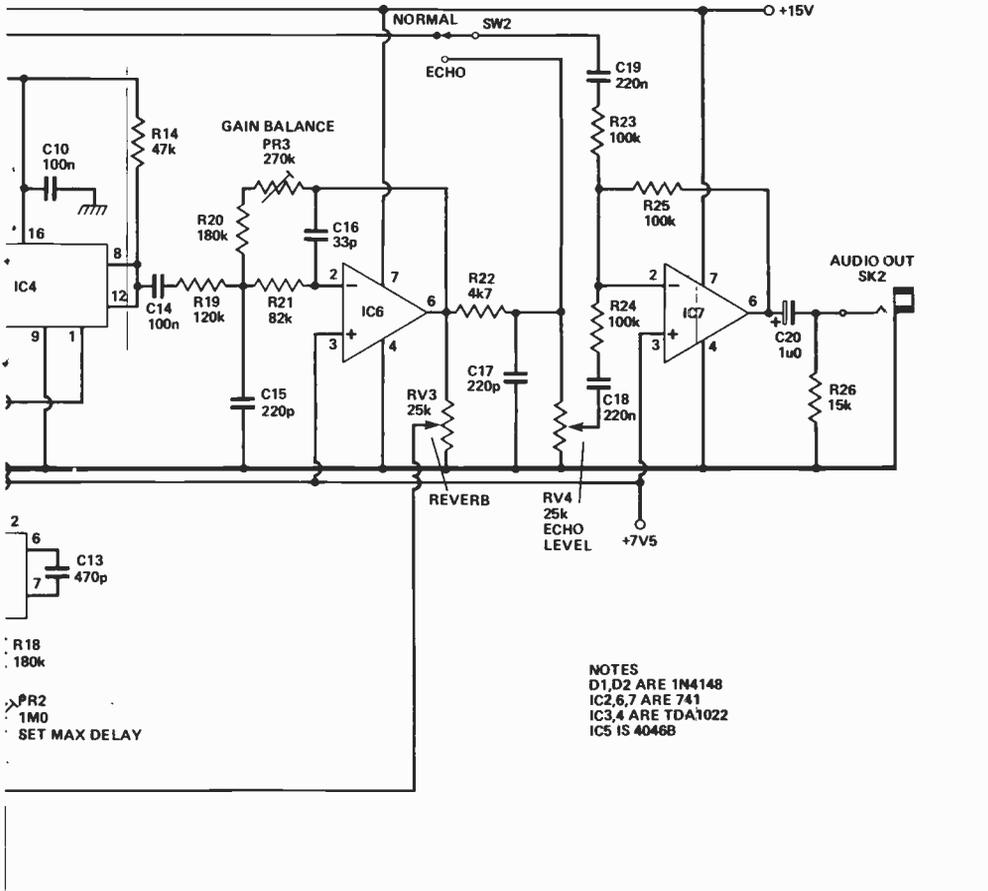

NOTES
D1,D2 ARE 1N4148
IC2,6,7 ARE 741
IC3,4 ARE TDA1022
IC5 IS 4046B


set to mid-range but with RV3 (Reverb) and RV4 (Echo Level) set to zero, connect a voice-range (350 Hz — 3k5 Hz) input signal of about 1 V peak-to-peak between the Normal and Echo Only positions, adjusting PR3 so that equal output levels are obtained in both positions (this test can be done with test gear or simply 'by ear', using a tape or disc signal source). When this adjustment is complete, set SW2 to the Echo Only position. Pass a music/voice signal through the system and use RV2 to check the Reverb sound is satisfactory.

Max Delay Time: Set SW2 to Normal, RV3 (Reverb) to zero, RV4 (Echo Level) to maximum (wiper at zero volts). Adjust PR2 while monitoring the output of the unit and note that high-pitched tone (whistle) is produced when PR2 is turned beyond a certain point. Now pass a voice signal through the unit; note that the echo effect is obtained, then trim PR2 to find a compromise setting at which a good delay (echo) is obtained with minimum acceptable intrusion from the 'whistle' sound. Finally, check that the delay can be varied over a wide range (roughly 2 mS to 50 mS)

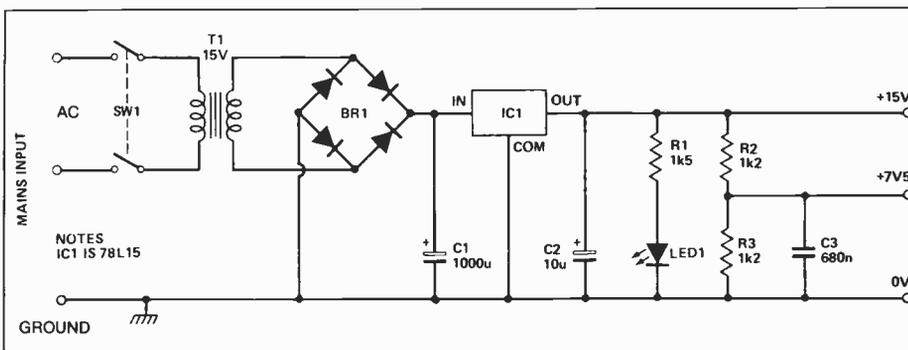

Circuit diagram of the regulated power supply.

ECHO - REVERB

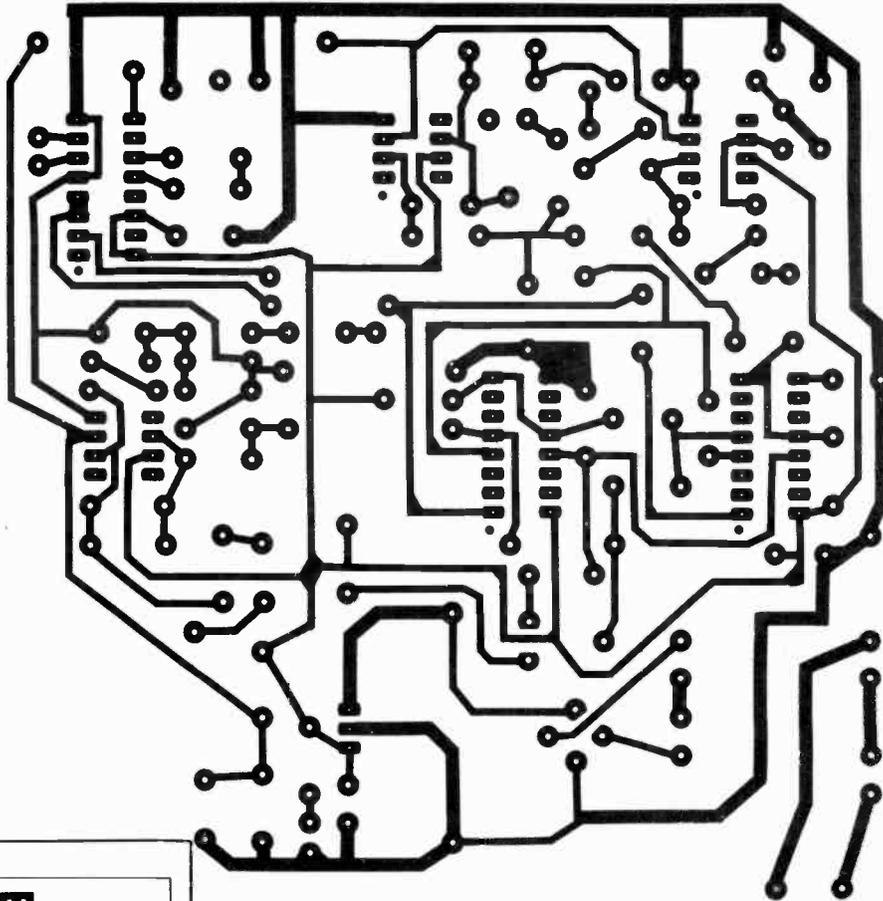

The printed circuit board.

MEET JACE

JACE is: - 100% compatible to Apple™
 -super expandable
 -very affordable
 -complete with Numeric key board

Options: -CP/M
 -128K
 -80 col.
 -speech
 -and more

ONLY
\$499.95
 introductory price


SPECIAL THIS MONTH

(while they last)

Z80 (CP/M™) card	\$ 52.95
80 Col. card	\$ 85.00
Flip n File 50	\$ 35.00
Zenith monitor amber	\$159.95
Nashua diskettes	\$ 22.95
-Slim disk drive	\$289.95
-Regular drive	\$279.95
-Disk controller	\$ 52.95
-16K ram card	\$ 52.95
-"Despiker" kit (4 outlet)	\$ 35.95


Send \$1.00 (refundable) for our catalogue full of other fine products.

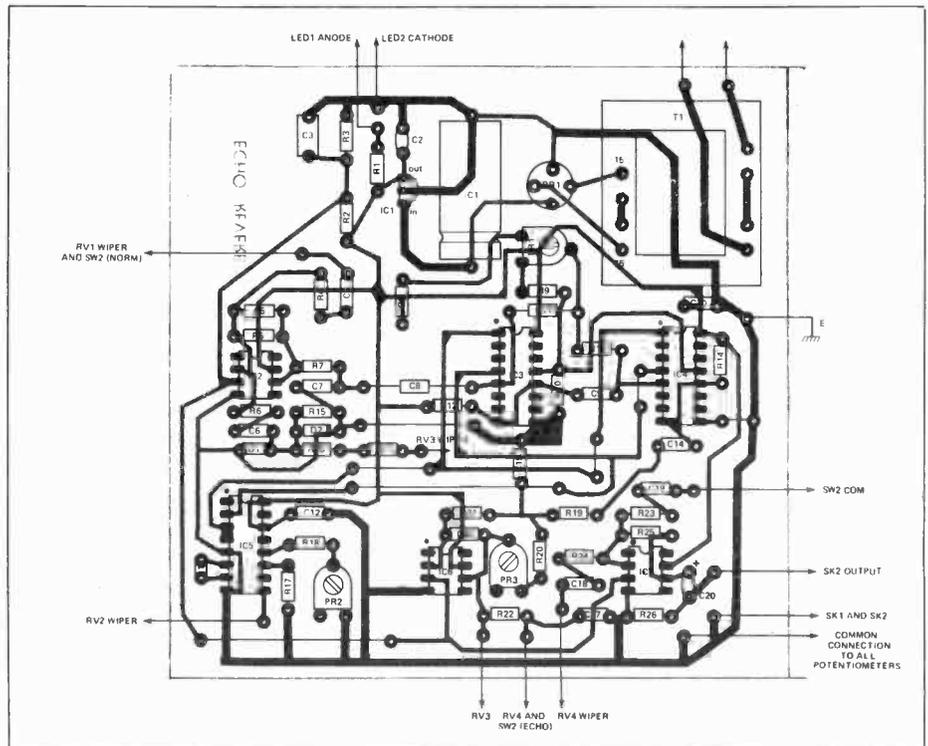Send cheque or money order:
 J.A.C. Electronics P.O. Box 83, Stn. "E"
 Montreal, Quebec, H2T 3A5 (514) 270-6730
 Tel: (514) 270-6730
 Que. res. please add 9% P.S.T.
 (add 5% Shipping & Handling)



The component location diagram. Transformer T1 may have to be located off the PCB and wires connected to the points labelled "15".

Multitech MPF-III

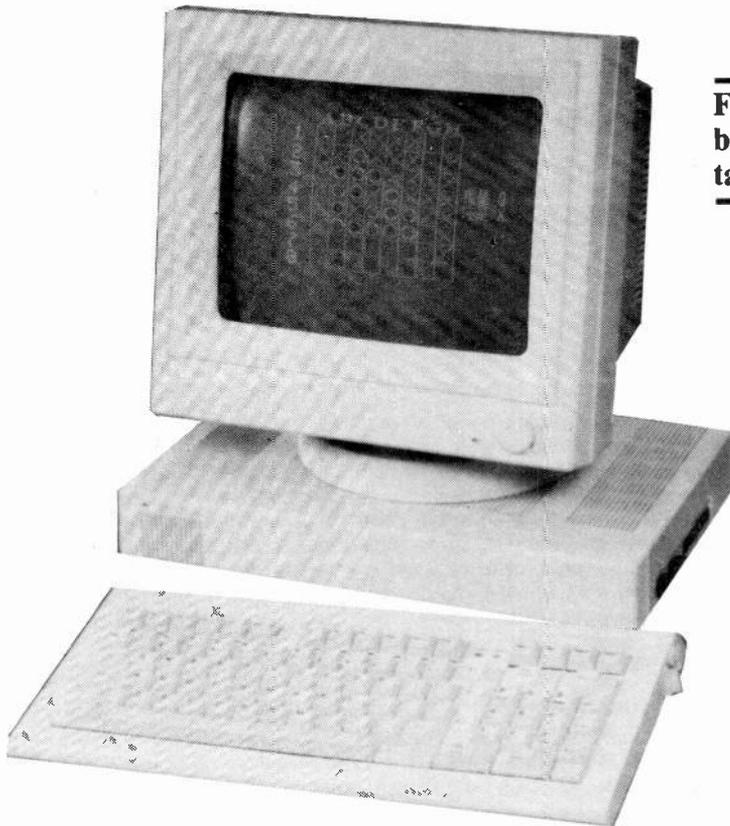

Fresh from the clone orchards in Taiwan, we bring you the MPF-III. Anthony DeBoer takes a look at the latest in imported fruit.

LOOK AT that keyboard, will you? Looks like we're reviewing another IBM compatible this month... Well, let's turn it on. Uh, sorry folks, it's an Apple clone. Well, I was close.

What we have here is the Multitech Micro-Professor III, Multitech's latest entry into the computing market, and quite a different machine from the MPF-1, that cute little bare-board computer that you may have seen. No, this time the good folks in Taiwan have brought you a full-sized micro, and a significant contender in the works--just-like-you-know-who market.

The Hard Facts

The main, essential part of the Multitech is a box-shaped box (well, they usually are, aren't they?) only about two and a half inches tall. Inside lurks most of the electronics. The keyboard is detachable, linked by a coiled cord. The Multitech video monitor sits on top or nearby or generally wherever you put it.

The Multitech doesn't really use real Apple peripheral cards. An 80-column card is built in, along with 64k of RAM, and Multitech offers specially-designed

printer, serial, disk, and Z-80 cards to fit inside the low-profile case. Some of the literature also pictured a pair of slimline drives mounted in a box the same size as the main unit, although the disk connectors are standard and regular drives will also work with this computer.

Slot #2 is set up in the normal configuration, so you can plug in one normal card if you want to, but it sticks out of the right side of the machine, and, without proper support, looks like all it would take to snap it off in its socket is for the cat to pounce on it.

Next to the peripheral slot, on the right side of the machine, are a pair of nine-pin connectors for the keyboard and the joystick. Around back are the power cord, power switch, video connectors (TV and monitor), volume control (which needs a screwdriver, if you find it too loud), connectors for an external speaker, printer, disk drives, and the vestigial cassette in and out plugs.

The 80-column generator in the Multitech deserves mention. It's a treat for anyone who's ever had to stand up repeatedly to reach behind his or her computer to switch patch cords between the

40-column output and a normal 80-column card. Being built right in, the 80-column screen becomes much more integrated into how things work in and about the computer. Type PR#3 and the 80-column screen gets activated. ESC-4 and ESC-8 will switch you back and forth now. As with the ile, you can go straight into graphics from 80-column, with the text window at the bottom of the screen still in 80 columns, which is something the good old Apple II never did.

There is one slight weirdness with the 80-column screen: you can't use it and the second graphics page at the same time. If you're in 80 columns and you run a program with a statement like HGR2 (or even POKE 49237,0) that accesses the second screen, for animation or whatever, you get a ?SYNTAX ERROR, of all things. Okay, so the manual does note that you only get one screen with 80 columns, but the first time you run up against that syntax error, it's guaranteed to send you around the bend trying to figure out what went wrong.

The keyboard should also be mentioned. To quote John, the office clone connoisseur, the keys are "like loose teeth". To be perfectly frank, they do jiggle and wiggle and go in a lot more directions than just up and down. The IBM-like design, with the backslash key where the shift key is supposed to go and the reverse-quote where the return key belongs, doesn't help either. At least they replaced that huge plus key at the right end with a smaller plus key and a return key.

The Multitech keyboard has twelve function keys, along with a break key (which gives out a control-C), a numeric keypad, and a few others. Unlike the original Apple, this one can generate the entire ASCII character set, including the tilde and the vertical-bar symbols. Like on the IBM, the keypad can also be used for cursor functions when you're editing program lines.

But it's still a bubblegum keyboard.

The Multitech video monitor is a fairly good piece of equipment, as such things go. The display is glare-free, and a duller shade of green than the Zenith monitors that everyone else seems to use. It sits on a nice round base, and will rotate and tilt as desired.

Multitechsoft?

In an almost commendable attempt not to violate any of Apple's copyrights, the folks at Multitech have rewritten Applesoft BASIC and the system monitor from the ground up. Part of this is good, because it lets them integrate the 80-column screen, the sound generator, and so on, but it does leave the system necessarily less than 100% Apple-compatible.

The big added feature in Multitech BASIC is sound. First off, you get the EFFECT command. Type EFFECT 0 : EFFECT 1 on a normal Apple and you get a syntax error. Try it here and you get the sound of a bomb dropping (or of all the air being squeezed out of a cat, your choice) followed by an explosion (presumably of the bomb or the cat, as the case may be). The other effects, 2 and 3, are supposed to be laser guns and ordinary mechanical machine guns respectively.

In case your musical tastes run more to real music than to sound effects, the Multitech also gives you something more melodic. The SOUND, PLAY, BASS, TEMPO, and INSTR statements let you feed songs through the computer's sound chip. SOUND and PLAY let you feed notes into the sound system, BASS lets you add a bit of bass (the results are suspiciously like those of the rhythm sections of those anyone-can-play-it electronic organs), TEMPO lets you adjust the note duration, and INSTR lets you choose between simulated piano, bell, xylophone, or organ.

The machine even has a rich, full-bodied control-G bleep that sounds like it comes through the computer's sound system as well.

Program editing changes here too. On the real Apple, you have to fool around with the I, J, K, and M keys to move around the screen. Here, however, with the IBM-style keyboard, there's a "NUM LOCK" key that lets the numeric keypad become cursor arrow keys and so on. What really makes editing program lines here easy are a few of the other keys here — an insert character key slides the rest of the line over to the right, making insertions less of a splice job than they used to be, a delete key does the opposite, and another key copies automatically to the end of the statement you're editing. Editing works in the 80-column mode only, which is not really a hassle, because



given the choice, you'll probably want to use the 80-column screen to do programming on anyway.

Battle of the Clones

On the less bright side, this rewritten BASIC is slower than good old Applesoft. Two sample programs were run. The first simply counted from one to ten thousand, to test the speed of BASIC, and the second spat out four K of text to the screen. Both times, a more conventional clone (the Unitron) beat the Multitech.

The random number generator is probably the worst feature of this version of Applesoft. The "real" random generator generates a properly pseudo-random sequence of numbers, but the Multitech's generates a much poorer sequence. It repeats itself every few hundred times. This may not sound like much, but try running an Applesoft program, almost any program, that runs along and uses random numbers by the bushelfull. On a real Apple, or a blatant clone thereof, you get sufficiently random numbers, but the Multitech gives a repeating series. The practical upshot of this is that a program that draws random lines, for example, will start doing the same lines over and over and lock itself into a loop, rather than continuing to draw lines all over until the screen is full.

This rewritten version of Applesoft does bring up an interesting point: that of the legal battles surrounding the various clones on the market. Franklin lost a court case a while back, and now has to rewrite its BASIC and monitor and stop illegally copying Apple's. After winning that case and setting a legal precedent, Apple will probably now go after the smaller clones.

Multitech seems to have seen this coming a while back already, though, and they already have a rewritten system. According to some of the documentation that came with the review machine, Apple

is suing Multitech too, but Multitech is claiming that Apple has no case because all the software got rewritten.

But then Shakespeare noted quite a while back that a rose by any other name would smell as sweet. If it looks very much like an Apple and it smells very much like an Apple, then it is an Apple for most practical purposes (except, Multitech hopes, for legal purposes). On the other hand, all that glitters is not gold, and all that runs DOS might not necessarily be an Apple. 'Twill be interesting to see what comes of it.

CP/M?

Somewhere along the line an ETI tradition got started that we would use the name of the CP/M operating system as a sub-head once in every computer review. Well, here's this month's entry.

The Multitech's manufacturers, as one might expect, claim that it runs CP/M. Being an Apple-compatible machine, using a 6502 microprocessor, the Multitech, like the True Fruit, requires a Z-80 card before it will peacefully accept CP/M disks. As noted previously, Multitech offers a special card that fits inside their machine's case, but they do claim that a normal card will work in the slot on the side of the machine.

Among the documentation we got with the machine was a list of 151 pieces of popular Apple software that the Multitech would run and 19 that it wouldn't. Lots of CP/M software was on the first list and SpellStar somehow made the second one, but the fine print noted that they used their own Z-80 card (the one that fits inside the machine) for the tests. Since our review model didn't have this option, we tried a good old regular-type Z-80 card in the external slot. No dice. Fed a CP/M disk, the Multitech crashed like a ZX-81 flung off the CN Tower. It sprayed characters all over the screen and everything.

Now NRI takes you inside the new TRS-80 Model 4 microcomputer with disk drive to train you at home as the new breed of computer specialist!

NRI teams up with Radio Shack advanced technology to teach you how to use, program and service state-of-the-art microcomputers...

It's no longer enough to be just a programmer or a technician. With microcomputers moving into the fabric of our lives (over 1 million of the TRS-80™ alone have been sold), interdisciplinary skills are demanded. And NRI can prepare you with the first course of its kind, covering the complete world of the microcomputer.

Learn At Home In Your Spare Time

With NRI training, the programmer gains practical knowledge of hardware, enabling him to design simpler, more effective programs. And, with advanced programming skills, the technician can test and debug systems



Now training includes either the TRS-80 Model 4 Microcomputer with Disk Drive or TRS-80 Color Computer with Computer Access Card; professional LCD multimeter; the NRI Discovery Lab; and hundreds of demonstrations and experiments.

(TRS-80 is a trademark of the Radio Shack division of Tandy Corp.)



quickly and easily.

Only NRI gives you both kinds of training with the convenience of learning at home. No classroom pressures, no night school, no gasoline wasted. You learn at your convenience, at your own pace. Yet you're always backed by the NRI staff and your instructor, answering questions and giving you guidance.

TRS-80 Model 4 Plus Disk Drive To Learn On and Keep

NRI gives you hands-on training on the latest model in the most popular line of Radio Shack microcomputers: the TRS-80 Model 4.

You not only learn to program your Model 4, you learn all about it... how circuits interact... interface with other systems... gain a real insight into its nature. Under NRI's expert guidance, you even install a disk drive, verifying its operation at each step.

You also work with a professional 4-function digital multimeter and the NRI Discovery Lab,® performing over 60 separate experiments.

The powerful, versatile TRS-80 Model 4 microcomputer disk drive and other equipment you train with are yours to use and keep!

Same Training Available With Color Computer

NRI offers you the opportunity to train with the TRS-80 Color Computer as an alternative to the Model 4. The same technique for getting inside is enhanced by using the new NRI-developed Computer Access Card. Only NRI offers you a choice to fit your specific training needs.

The Catalog is Free. The Training is Priceless.

Get all the details on this exciting course in NRI's free, 104 page catalog. It shows all equipment, lesson outlines, and facts on other electronics courses such as Electronic Design, Industrial Electronics, Video/Audio Servicing... 12 different career opportunities in all. Keep up with the latest technology as you learn on the latest model of the world's most popular computer. If card has been used, write to:



NRI Schools


McGraw-Hill Continuing
Education Center
330 Progress Avenue
Scarborough, Ontario M1P 2Z5
or telephone 416-293-8787

We'll give you tomorrow.

HAMEG®

Oscilloscopes

For Field Service
and Laboratory

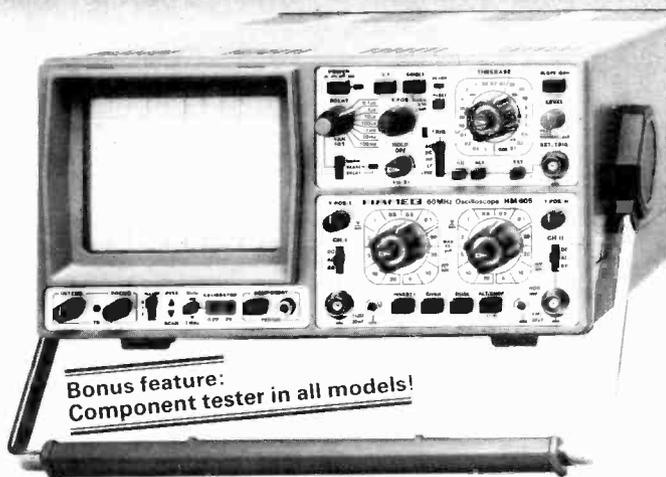

HM 605 60 MHz Dual Trace - \$1550,-

Sensitivity 5mV-20V/div at 60MHz, 1mV at 15MHz • Automatic peak-value or normal triggering to 80MHz • Delay line • Variable sweep delay from 100ns-1s • Timebase range from 2.5s/div to max. 5ns/div • Unique fast-rise-time 1kHz/1MHz calibrator • Bright high-resolution 14kV CRT.

HM 204 20 MHz Dual Trace - \$1120,-

Sensitivity 2mV-20V/div • Timebase range 2s/div-20ns/div • Automatic peak-value triggering to 50MHz • Variable sweep delay • Single sweep mode • Y-Output • Z-modulation • Over-scan indicator.

HM 203 20 MHz Dual Trace - \$835,-


Western Europe's best selling 20MHz-Scope! • Sensitivity 2mV-20V/div • Triggerbandwidth 40MHz • Timebase range 0.2s - max. 40ns/div

HM 103 10 MHz Single Trace - \$550,-

Small, compact service scope • Sensitivity 2mV-20V/div • Timebase range 0.2µs-0.2s/div • TV-V and TV-H triggering.

»Modular System« HM 8000

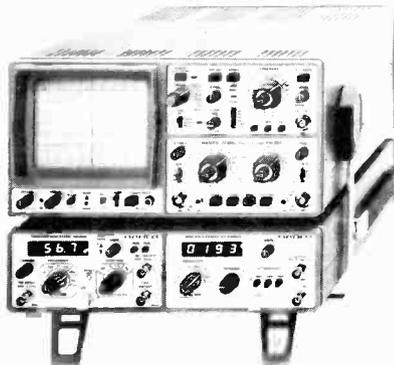An expanding range of signal generators, multimeters, counter/timers, etc....



For more details
write or call collect:

BCS
ELECTRONICS
LIMITED

980 Alness St. Unit 7,
Downsview, Ontario.
M3J 2S2
(416) 661-5585
TELEX 065-28169

Almost as an afterthought, it must be mentioned that CP/M is not the only operating system the Multitech can run. There's something called DOS, too, that is actually designed to run on computers such as this one. Standard Apple DOS runs quite nicely on the Multitech, although there's a special Multitech DOS, in keeping with the rewritten BASIC and monitor. According to the docs, the big difference is that the function keys across the top of the keyboard become words like CATALOG and so on when you're running their DOS. Unfortunately, the review copy came on an unbootable disk (a hasty copy by the good folks that lent us the computer), so we had to settle for looking at the files, after booting normal DOS. There were the usual graphics demos, a sound demo, something similar to FID except for being written in BASIC, just the usual boring stuff, but to make up for it, there was a Chinese version of the board game Othello. Fun stuff, the prompts come up in genuine high-res Chinese letters, but unfortunately no one here reads Chinese. Well, now we know the Chinese for "It's your move, sucker". You learn something new every day.

Manual Labour

The manuals that came with the computer did the job they were supposed to. Well, they explained what the computer could do and how to get it to do it. They were written in Foreign Technical Manual English, a variant on the Queen's English in which quaint wordings and aleatoric spellings are used. Such manuals should, of course, be kept away from elderly English professors, in whom they are likely to cause coronaries. But if you're willing to forgive the style, they are as helpful as computer manuals ever are. The reasonably detailed tables of contents make up for the utter lack of an index, although it would still be nice to have one. They, like most other computer manuals, are not designed to teach you how to program — prior knowledge seems to be assumed — but they do cover the BASIC language and the computer itself quite well.

Conclusions

Being priced in the vicinity of \$1300, the Multitech is somewhere in between the Real Apple and its other competitors. Although the extra features — the integrated 80-column software, the editing functions, the sound effects generator, and so on — are worth something, this computer may suffer from being in the middle of the market. Anyone wanting a computer and not wanting to pay very much will probably want a cheaper clone, and those computer connoisseurs who want the Real Thing will probably go those extra hundreds for an authentic //e.

The differences between this machine and the one Woz designed might also tip the balance in favour of either an Apple or one of the ones that feel no shame in copying it. As noted earlier, there are some subtle differences between the Apple system and Multitech's that will confuse a few pieces of software. In the vast majority of cases, there will be no problem, but those few cases where there is a problem will, according to Murphy's Law, inevitably crop up.

The final caveat that must be raised, as with all computers, is to try out the keyboard before trying out your Visa limit. That's where the interface between man and machine happens, and if you can't stand it, you won't be able to stand the rest of the computer very well either. IBM lovers will probably enjoy it, but the rest of humanity might not.

But it is still a respectable example of Far Eastern ingenuity. If you're looking for an Apple-compatible system with a few extra features, this might be the one for you.

Quick Reference

Multitech MPF-III	
Mfg:	Multitech Industrial Corp.
Price:	\$1300
CPU:	6502
RAM:	64k
Screen:	40x24, 80x24
Graphics:	280x192
Colour:	Yes
Sound:	Yes
Video:	TV and monitor

ETI

COMPUTER PARTS GALORE INC.
 316 College St.
 Toronto, Ontario M5T 1S3

Toll Free Orders Only
1-800-387-1385
 Order Checking (416)925-8291
 Technical Data (416)925-1105

DTC™ DISPLAY TELECOMMUNICATIONS CORPORATION

NEW FROM MAXISWITCH™



The finest most cost effective keyboard for the IBM™ PC or the APPLE™ that we have ever seen. The IBM model has all of the standard features of the IBM KB plus an improved return key for true typewriter emulation (For word-processing) Full N key roll-over, auto-repeat and more. The APPLE version has a lot more than the run of the mill APPLE keyboard, 10 function keys, cursor pad, numeric pad, and 21 preprogrammed commands to save a lot of typing. Just like the picture and just as pretty.

ONLY \$169.95

Please specify APPLE, or IBM PC, XT
 NOTE: Complements our IBM look-alike case exactly.

DEALERS AND OEM MANUFACTURERS QUANTITY DISCOUNTS AVAILABLE

Ideal for

- COMPUTERISTS
- OEM MANUFACTURERS
- DEVELOPMENT LABS
- UNIVERSITIES
- INDUSTRIAL APPLICATIONS

THE ULTIMATE OEM/PC COMPATIBLE SINGLE BOARD COMPUTER

- MEGA-BOARD™** with full assembly instructions \$99.95
- USERS MANUAL** with theory of operation, schematics, block diagram, application notes \$19.95
- MEGA-BIOS™** fully compatible MS-DOS/PC-DOS/BIOS \$29.95

ORDER NOW!!!

ONLY!
\$99.95 MEGA-BOARD™
 Evaluation Board Kit

FULL IBM - PC™ COMPATIBILITY!

Evaluation Board Kit!
 (Blank board with full assembly instructions and parts list.)

Includes highest quality PC board with gold plating, silk screen, solder mask

new!

MEGA-BOARD™


IBM is a registered trademark of International Business Machines

Eight Compatible I/O Interface Connectors
 (Full PC compatible) (compatible with all IBM-PC* plug-in cards)

Special J1 Interface
 (Allows horizontal mounting of compatible mounting of compatible expansion cards for easy bus expansion and custom configuring) (Board has 62 pin gold plated compatible connector)

Extended ROM Capability
 (Runs all compatible PC ROMS) (Jumper programmable to accommodate all popular 8K, 16K, 32K and 64K ROM chips and NEW EE ROMS! VPP power pin available for EP ROM burning!) (External VPP voltage required)

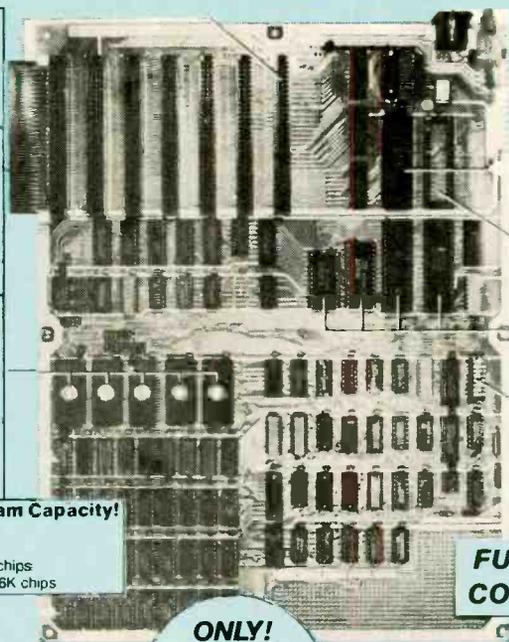Full Mega-Byte Ram Capacity! On board!
 (With parity)
 256K Bytes using 64K chips
 1 Mega Bytes using 256K chips



- Standard Keyboard Interface**
 (Full PC compatible)
- Hardware Reset**
 (Overcomes reset flaw in PC)
- Power Connector**
 (Full IBM* pinout compatible)
- 8088 Processor**
 (Same as PC)
- 8087 Numeric Processor**
 (Same as PC)
- Peripheral Support Circuits**
 (Same as PC)
- Configuration Switches**
 (Same as PC)
- Speaker/Audio Port**
 (Same as PC)
- Wire Wrap Area**
 To facilitate special custom applications!

HARD TO GET PARTS

14.318 MHZ XTAL	\$ 2.95
17.43 MHZ XTAL	\$ 4.95
1.8432 MHZ XTAL	\$ 4.95
MPSA13 TRANSISTOR	\$ 0.75
2N3904	\$ 0.35
2N3906	\$ 0.45
2N4258	\$ 0.75
MPSU51	\$ 1.00
1K, 9 PIN SIP	\$ 0.75
1K, 8 PIN SIP	\$ 0.75
10K, 10 PIN SIP	\$ 0.75
4 POS DIP SWITCH	\$ 1.75
20 PIN MALE RT ANGLE	\$ 2.95
20 PIN FEMALE, FOR ABVS	\$ 2.00
6 PIN POWER CONNECTOR	\$ 1.00
RCA JACK, PCB MOUNT.	\$ 0.75
50 P1 TRIMCAP	\$ 1.00
220 OHM TRIMPOT	\$ 0.75
68A45, VIDEX IC	\$ 16.00
MC3242, 128K IC	\$ 16.00

BARE PCB

(A) REAL TIME CLOCK PCB	\$14.95
(B) QUAD DRIVE CARD (RANA)	\$24.95
(C) 9 VOICE MUSIC PCB	\$14.95
(D) BUFFER PRINTER PCB	\$19.95
(E) GRAPPLER PCB	\$19.95
(F) CABLE FOR D, E, SPECIFY	\$24.95
(G) 80 COLUMN, SOFTSWITCH	\$14.95
(H) DISC CONTROLLER PCB	\$12.95
(I) Z-80 PCB	\$12.95
(J) SSM MODEM PCB	\$24.95
(K) MOUNTAIN MULTIFUNCTION	\$24.95
(L) 128K (SATURN) PCB	\$19.95
(M) RGB COLOR PCB	\$24.95
(N) EPROM PROGRAMMER PCB	\$12.95
(O) PIA PCB	\$14.95
(P) WILD CARD PCB	\$12.95
(Q) SAM TALKING CARD	\$12.95
(R) RS-232 PRINTER PCB	\$12.95
(S) RS-232 MODEM (COMM) PCB	\$12.95
(T) RS-232 ASYNCHRONOUS PCB	\$14.95
(U) SPRITE GRAPHICS PCB	\$17.95

6502 STUFF

BB POWER SUPPLY	\$ 99.00
ABS NUMERIC CASE	\$ 59.95
ASCII NUM KEYBOARD	\$ 99.00
SYSTEM SAVIOUR FAN	\$ 55.00
GREAT DEAL	\$275.00
Z-80 WIRED	\$ 55.00
80 COLUMN WIRED	\$ 75.00
16K WIRED	\$ 50.00
DISC CONTROL WIRED	\$ 59.95
WILDCARD WIRED	\$ 45.00
SAM TALKER WIRED	\$ 45.00
128K WIRED, NO KC'S	\$ 39.95
128K WIRED, 64K	\$119.00
128K WIRED, 128K	\$199.00
DISK(3) FOR 128K	\$ 20.00

BARE PCB FIRMWARE ETC.

(A) REAL TIME CLOCK DISK	\$ 8.00
(B) 9 VOICE MUSIC, 2 DISKS	\$16.00
(C) GRAPPLER EPROM	\$ 8.00
(D) 80 COLUMN, 3 EPROMS	\$24.00
(E) SSM MODEM EPROM	\$ 8.00
(F) MULTIFUNCTION EPROM	\$ 8.00
(G) 128K, 3 DISKS	\$20.00
(H) RGB CARD PROM	\$ 9.00
(I) RGB CARD DISK	\$ 8.00
(J) EPROM PROG. EPROM	\$ 8.00
(K) WILD CARD EPROM	\$ 8.00
(L) WILD CARD DISK	\$ 8.00
(M) SAM TALKER DISK	\$ 8.00
(N) SPRITE DISK	\$ 8.00

WE'VE GOT EM!
5-1/4" HALF SIZE DRIVES

- 40 Track per side
- Double-sided, double density
- Same as SA455
- Latest head & drive technology
- Fast access time

Two of These Half Size Drives will Fit in the Same Space as 1 Full Size Drive!

\$269.00

MEGA BOARD PARTS


(A) MAXI SWITCH KB	\$199.00
(B) IBM CASE	\$ 59.95
(C) ALL THE 82 IC'S & 8088	\$159.00
(D) 8253-5	\$ 11.95
(E) 8259A	\$ 11.50
(F) 8237A-5	\$ 34.95
(G) 8255A-5	\$ 7.95
(H) 8288	\$37.50
(I) 8284	\$ 7.95
(J) 8088	\$ 34.95
(K) 100 NS DELAY	\$ 14.95
(L) 7 NS DELAY	\$ 14.95
(M) BUS, BARS, SET OF 2	\$ 4.95
(N) 6.35 pf trimcap	\$ 1.50
(O) 62 PIN EDGE CONNECTOR	\$ 4.95
(P) 5 PIN DIN CONN, KB	\$ 3.50
(Q) POWER CONNECTOR, M/F	\$ 2.50
(R) 4.7K x 6 SIP	\$ 0.75
(S) 4.7K, 16 PIN RES NTWK	\$ 1.50
(T) 8.2K, 16 PIN RES NTWK	\$ 1.50
(U) 33 OHM, 16 PIN RES NTWK	\$ 2.50
(V) TBP 24s10 PROM	\$ 8.95

MAIL ORDERS

We accept: Personal Cheques, Postal Money Orders, Certified Cheques, Travelers Cheques, Visa, American Express, Mastercard, Bank Draft. We ship C.O.D. only by CANPAR and Truck. We do not use Canada Post C.O.D. We will send your goods via CANPAR or Canada Post unless you say otherwise. You will be charged a min. \$3.00 for delivery and handling or more if your goods are heavier than the \$3.00 weight or if you specify another delivery service that charges more. All Ont. res + 7% sales tax. We sell wholesale to any retail store or other reseller with a sales tax exemption no. as long as a realistic quantity is bought. We ship within a week if in stock and we will cancel any back-orders over 4 weeks unless otherwise instructed. 20% Restocking Charge.

Operation Plowshare

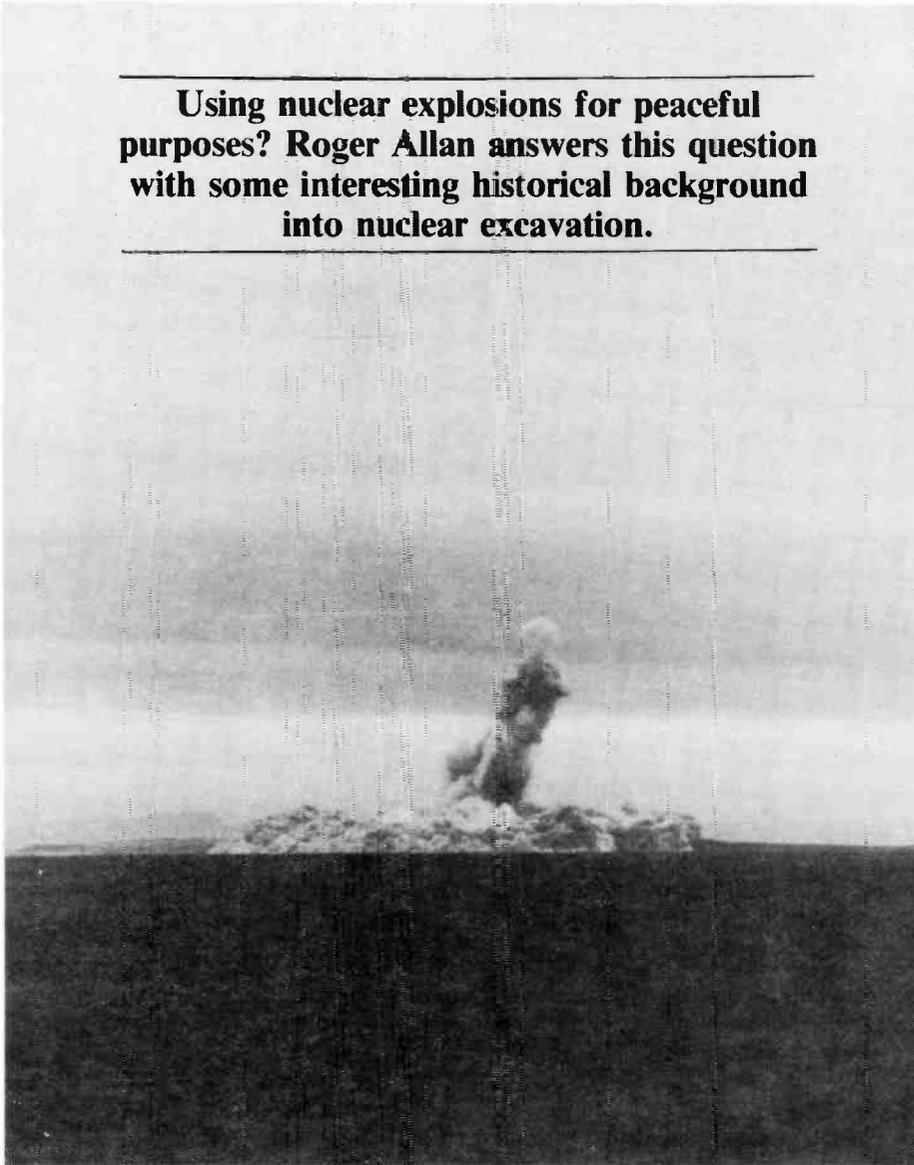Using nuclear explosions for peaceful purposes? Roger Allan answers this question with some interesting historical background into nuclear excavation.



DESPITE THE enormous destructive forces that chemical explosives have added to the conduct of wars, it can be arguably demonstrated that explosives have been used for more good than evil. If one thinks about it for a moment, one finds that explosions of one variety or another permeate our entire lives — whether massively such as the construction of the Panama, Erie, Corinth or Suez canals, or microscopically such as the explosions in a cylinder head driving a car's piston engine.

Recognizing the advantages of explosions, coupled with the Suez Crisis in 1956, led Harold Brown, then director of

the Lawrence Livermore Radiation Laboratory, to consider the possibility of using nuclear explosions to dig a sea-level canal across Israel, as well as one across the root of the Florida Peninsula. In the same year, Camille Rougeron, a French engineer, published his book *Les Applications de L'Explosion Thermonucleaire* a study on the peaceful applications of nuclear explosives.

Conjointly, their arguments were persuasive. The advent of the nuclear age, and U.S. testing of thermonuclear devices for military applications meant that sufficient data had been generated to permit economic feasibility studies to be cast.

The figures produced seemed rather good — earth could be excavated for a few cents per cubic yard in some projects where conventional methods would cost 20¢ to \$5 per cubic yard.

In the early part of the following year, a meeting of interested parties from the American Atomic Energy Commission (AEC) was convened to study the possibility of using thermonuclear devices for peaceful purposes. The *Proceedings* of this meeting, and subsequent ones, roughly at two year intervals, demonstrated that a number of avenues lay open to research and development, all at apparently cost effective prices.

The first consideration was for another Panama Canal, later known as the Isthmian Project. It was shown that using nuclear devices to do the cratering would result in a canal larger than the current one, not dependent on locks (they'd just blast through the mountains), would be more useful, require less maintenance, and militarily less vulnerable. If the route were between Sasaki and Marti in Panama (half way between the current canal and the Columbian border) its cost would be about \$650 million (U.S./1964), while a canal between Atrato and Truando (fluctuating around the Panama-Columbian border) would cost about \$1.25 billion (U.S./1964).

Another concern was for petroleum recovery. In particular, the Athabaska Tar Sands formation underlying 16,000 square miles of Alberta was investigated by the Richfield Oil Company in this regard. Calculations indicated that a 9-kiloton nuclear explosion would release enough heat so that several hundred thousand barrels of oil would be recoverable in a free-flowing state. Mining was also considered, with particular regard to the removal of overburden to prepare ore bodies either for mining by conventional methods or by the leaching-in-place of minerals — such as copper ore by sulphuric acid.

Studies by the U.S. Bureau of Mines showed that gas fields, from which little or no gas can be produced due to the low permeability of the host rock, could be 'freed up' by thermonuclear explosions. Essentially, the detonation would fracture large volumes of rock to the extent that economic recovery of gas might be possible.

In North Africa there are two massive depressions — the 8,000 square mile Qattar in west Egypt (only 35 miles



ELECTRONICS BOOK CLUB

The Best Source for Hobbyists and Professionals
for Over 18 Years!

Time- and Money-Saving Advice . . .
Practical Troubleshooting & Repair Tips . . .
State-of-the-art Technology . . . Hundreds
of Projects . . . Plus, Exceptional Savings


Select 5 Books for Only \$2⁹⁵



1503
List \$21.95



1499
List \$21.95

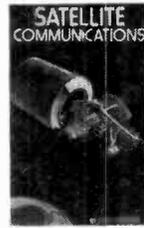

1632
List \$16.95



1409
List \$15.95



1497
List \$15.95



1536
List \$14.95



1665
List \$21.95



1183
List \$15.95




1431
List \$17.95



1529
List \$21.95



1473
List \$19.95

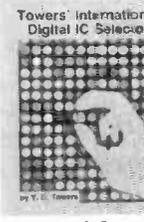

1616
List \$19.95



1537
List \$16.95



1543
List \$17.95



1557
List \$14.95



1449
List \$19.95



1507
List \$15.95



1583
List \$19.95



1531
List \$17.95



1487
List \$15.95



1337
List \$10.95



1671
List \$21.95



1667
List \$19.95



1498
List \$18.95



1199
List \$19.95



1465
List \$15.95



1296
List \$18.95



1539
List \$19.95

FREE guide to
mail order sources
for electronic parts
and components
A \$6.95
Value!



FREE When You Join Now

7 very good reasons to join the Electronics Book Club

- **Big Savings.** Save 20% to 75% on books sure to increase your electronics know-how
- **No-Risk Guarantee.** All books returnable within 10 days without obligation
- **Club News Bulletins.** All about current selections—mains, alternates, extras—plus bonus offers. Comes 13 times a year with hundreds of up-to-the-minute titles you can pick from
- **"Automatic Order."** Do nothing, and the Main selection will be shipped automatically! But . . . if you want an Alternate selection—or no books at all—we'll follow the instructions you give on the reply form provided with every News Bulletin
- **Bonus Books.** Immediately get a Dividend Certificate with every book purchased and qualify for big discounts of 60% to 80%
- **Extra Bonuses.** Take advantage of added-value promotions, plus special discounts
- **Exceptional Quality.** All books are first-rate publisher's editions selected by our Editorial Board and filled with useful, up-to-the-minute information

ELECTRONICS BOOK CLUB

P.O. Box 10
Blue Ridge Summit, PA 17214

Please accept my membership in the Electronics Book Club and send the 5 volumes circled below, plus, my FREE copy of *The Electronics Buyer's Guide*, billing me \$2.95 plus shipping and handling charges (payable in U.S. dollars). If not satisfied, I may return the books within ten days without obligation and have my membership cancelled. I agree to purchase 3 or more books at reduced Club prices (plus shipping/handling) during the next 12 months, and may resign any time thereafter.

1183 1199 1296 1337 1409 1431 1449 1465 1473
1487 1497 1498 1499 1503 1507 1529 1531 1536 1537
1539 1543 1557 1583 1616 1632 1665 1667 1671

Name _____ Phone _____
 Address _____
 City _____
 State _____ Zip _____

Valid for new members only. Foreign applicants will receive special ordering instructions. Canada must remit in U.S. currency. This order subject to acceptance by the Electronics Book Club.

ETY-684

The Electronics Today Almost Free Software Offer

The most difficult thing about understanding new software is understanding how you're going to pay for it. Even simple programs cost a mint. Thus it was that we were pretty fascinated to find that there is a vast library of really good software in the public domain.

Public domain software is free. Much of it has been written by the finest programmers around and then enhanced by dozens of other users until a lot of it is better than those nasty little disks you have to mortgage the cat to buy.

There are many splendidly useful public domain programs which have no commercial counterparts.

Unfortunately for many users, public domain software is very hard to find sources for. For this reason, we have created the Electronics Today Almost Free Software Offer.

For a limited time only . . . until the disk labels run out . . . you can get a disk formatted for your system packed with a selection of some of the finest works of the public domain. The directory includes games, programming aids, utilities and documentation files that are simply unobtainable any other way.

All of this software is free. We are charging only for the cost of the disks and the time taken to put the files on them. You can copy the programs, modify them, give them to your friends or print them out as posters . . . they are all totally free of restrictions, save that they cannot be resold for profit.

The Catalogue Of The Almost Free Volume One Is:

- **MODEM7** This program will allow you to communicate with any CP/M based system and download files. See the article in this month's CN! for complete details. MODEM7 will be provided in versions for each system.
- **FINANCE** is a fairly sophisticated financial package written in easily understandable, modifiable Microsoft BASIC.
- **PACMAN** You can actually do PACMAN without graphics, and it clips along pretty well.
- **BADLIM** Ever have to trash a disk for just one bad sector? End your BDOS errors with this little troll. It isolates the bad sectors into an invisible file and makes the rest of the disk useable again.
- **FORTH** This is a complete up-to-date version of FIG FORTH, complete with its own internal DOS.
- **DISK** This is a splendid program which allows you to move whole masses of files from disk to disk without having to do every one by hand. You can also view and erase files, all without a lot of typing.
- **DUU** The ultimate disk utility; this program allows you to recover accidentally erased disk files, fix garbled files, rebuild and modify your system. We recently saved a 300K dBase II file with this little gem.
- **QUEST** Life is not meaningful without dungeons and dragons.
- **D** This is a sorted directory program that immediately tells you how big all your files are and how much space is left on your disk.
- **STOCKS** This is a complete stock management program in BASIC. It's pretty fierce the way it is, but you can easily fine tune it if you feel moved to do so.
- **USQ/SQ** allows you to compress and uncompress files. You can actually pack about forty percent more stuff on a disk with this system.
- **SEE** This program, also known as TYPE17 will TYPE any file, squeezed or not, allowing you to keep documents in compressed form and still be able to read them.

The Electronics Today Almost Free Software Offer

In addition to the above, we will be providing Apple users with a program which can be used to patch the Apple CP/M BIOS to increase the display speed of the popular Videx eighty column card. Users of other formats will receive ALIENS11, a fairly fiendish video game package . . . which is too large to get on an Apple disk.

Some or all of these files may be provided squeezed in order to accommodate your disk format. While we make every effort to ensure that the programs are completely debugged, we can offer no guarantee that they will function properly for your application.

Our almost free volume one is available for the Apple II + running CP/M, and the Nelma Persona for \$12.95 per disk and on eight inch single sided single density diskettes for \$16.95. Ontario residents please add seven percent provincial sales tax. The files are provided on pristine brand new high quality disks which are fully formatted and checked out prior to shipment.

Whether you are up for running a business, hacking bytes, or just learning about micro-computers, these programs will be a good trip.

The Electronics Today Almost Free Software Offer
25 Overlea Boulevard, Suite 601
Toronto, Ontario
M4H 1B1

Name _____

Address _____

City _____ Province _____

Postal Code _____


Apple Nelma 8" SSSD

from the sea), and the 50,000 square mile Chotts Depression whose northern edge is just 20 miles from the Tunisian coast. It was thought that by creating large channels between the Mediterranean Sea and those depressions, that the inflow could power large hydroelectric stations. Natural evaporation from the new inland seas would reduce their level rapidly enough to assure a continuous inflow from the sea for many years.

Portions of Africa, Australia and South America have the reality of large mineral deposits located near the sea, but a coastline without harbours. It was felt that nuclear explosions would permit the cheap construction of harbours and thereby decrease the shipment costs of the minerals.

In the realm of water supply and its control and conservation, nuclear explosions were suggested to alter watersheds, interconnect aquifers, create or eliminate connections between surface and underground water supplies and where evaporation loss is high, create underground reservoirs.

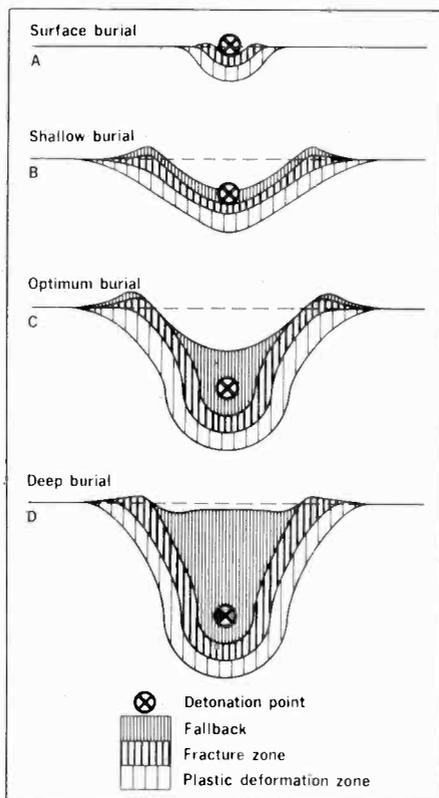
Relatively minor uses were suggested to bring down canyon walls to form dams, to aid in releasing natural geothermal heat to produce steam for desalting sea water or electric power, and for the *in situ* synthesis of chemicals in the ground — for example, calcium carbide might be produced from an explosion in a formation of coal and limestone, then by adding water, acetylene gas could be made.



In cratering explosions, the depth at which the explosion occurs is important. If it is too close to the surface (B), much of the energy escapes into the air and only a shallow crater results. If it is too deep (D), much rock is shattered and moved, but most of it fails to clear the crater rim and again only a shallow crater results.

With possibilities such as these, and recognizing that by the heady standards of the day, nuclear explosions were considered largely acceptable by both the government and general populace, the AEC in 1957 established *Operation Plowshare*. Composed of elements from the AEC's Division of Peaceful Nuclear Explosives, the Lawrence Livermore Laboratory and the Nuclear Cratering Group of the Army Corps of Engineers, *Plowshare* was to undertake the study of how 'best' nuclear explosions could be adapted to civilian purposes.

Although no nuclear test, designed specifically for *Plowshare* purposes, had been conducted by the time the U.S. voluntarily began a nuclear test moratorium in late 1958, more than 150 nuclear explosions of all types — atmospheric, surface and underground — had occurred prior to that time. They provided a data base of information for the *Plowshare* scientists. Analysis of data from these tests yielded information on such phenomena as cavity formation, diminution of earth motion with distance, heat transfer to the surrounding materials, rock fracturing and containment of radioactivity. To help fill in the blanks, while fulfilling the U.S. obligations under the moratorium, between 1958 and 1961, the AEC conducted experiments with high explosives. More than 100 charges, ranging in size from 256 to 1,000,000 lbs. were set off at the AEC Nevada Test Site. One of the oddest things determined from these explosions,

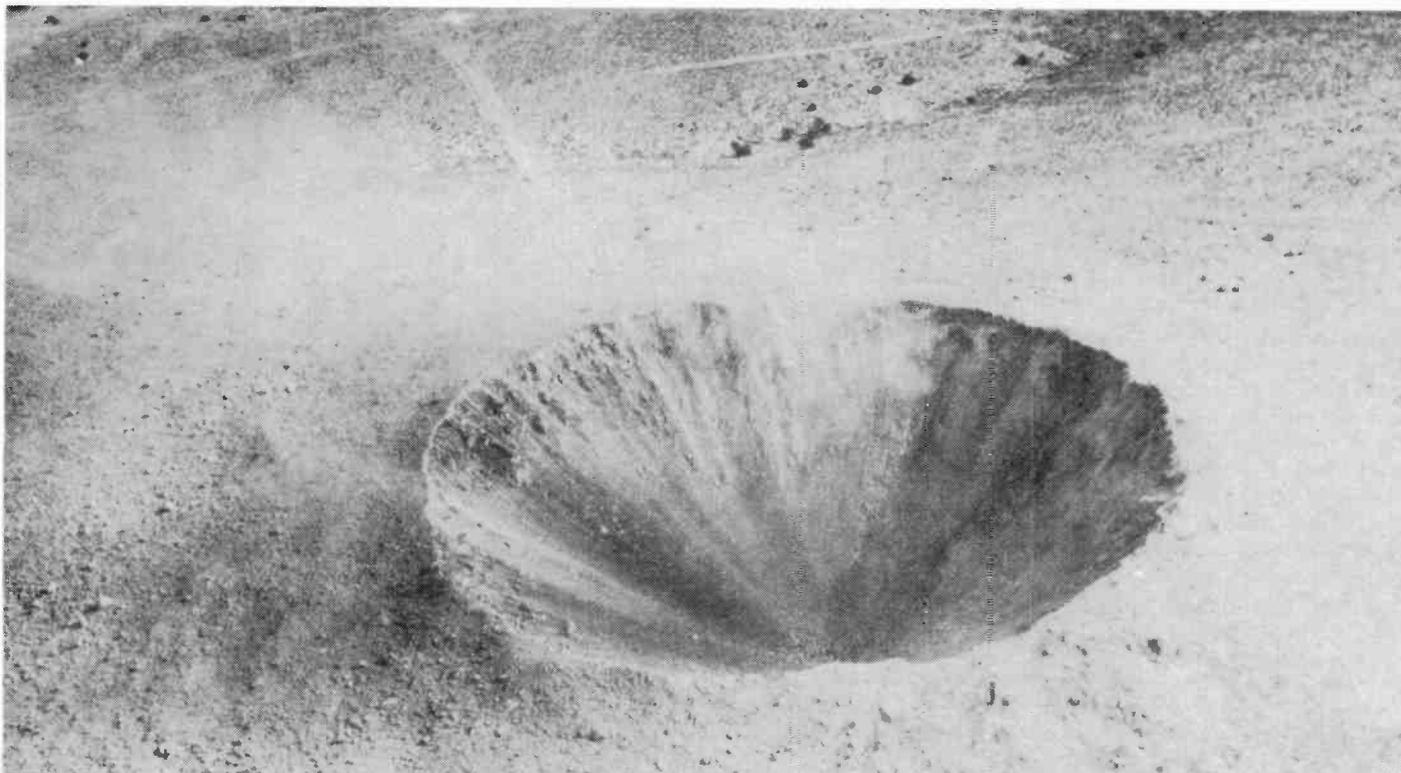

The result of Project Cabrioleet. A low-yield nuclear excavation experimental blast on January 26, 1968 produced this crater 125 feet deep and 400 feet in diameter. Photo courtesy of U.S. Department of Energy.


and subsequently verified when nuclear devices were used, was that when a number of charges are placed in a row and detonated simultaneously, an elongated ditch is formed with the usual 'lip' of thrown-out material along the sides, but little or none at the ends — creating, essentially, a perfect canal.

On December 10, 1961, following the end of the nuclear test moratorium, *Plowshare* became more active. A nuclear explosion with a yield of 3.1 kilotons was detonated in a salt formation 1,200 feet beneath the earth's surface at Carlsbad, New Mexico. Known as *Project Gnome*, the explosion produced an enormous cavity (134 by 196 by 75 feet), involving some 960,000 cubic feet of rock and melted salt. The purpose of the experiment was to study the possibility of recovering heat deposited in the salt formation by the explosion. The idea was the water would be pumped into the hot cavity after the explosion and the quality of the resulting steam measured. The experiment was a failure, as the heat was dispersed into a greater volume of rock than had been anticipated, and the heat recovery was not appreciable. Further, follow-up studies demonstrated that if steam had been produced, it would have been very salty and hence highly corrosive.

The following year, in July, *Project Sedan* was undertaken. This explosion involved a 100 kiloton cratering experiment. It was planned as the first of a series of thermonuclear explosions to develop techniques of nuclear excavation and to extend knowledge of cratering effects from explosions into the 100 kiloton range. The problem was that smaller explosions cannot necessarily be scaled up by bigger explosions. The explosion resulted in a crater some 1,200 feet in diameter and 320 feet deep, with a volume of some 6.5 million cubic yards — about the size of a small harbour.

In February of 1962, the AEC conducted the *Hardhat* experiment — the first attempt to provide information on the use of nuclear explosives to break and crush mineral deposits preparatory to extracting the ore by conventional techniques. It involved a 4.5 kiloton explosion at 950 feet. Following the detonation, a horizontal tunnel was driven through the rubble filled chimney and some 2,700 tons of broken rock were withdrawn in a simulated mining operation. Apparently, no hazardous amounts of radioactivity were encountered.

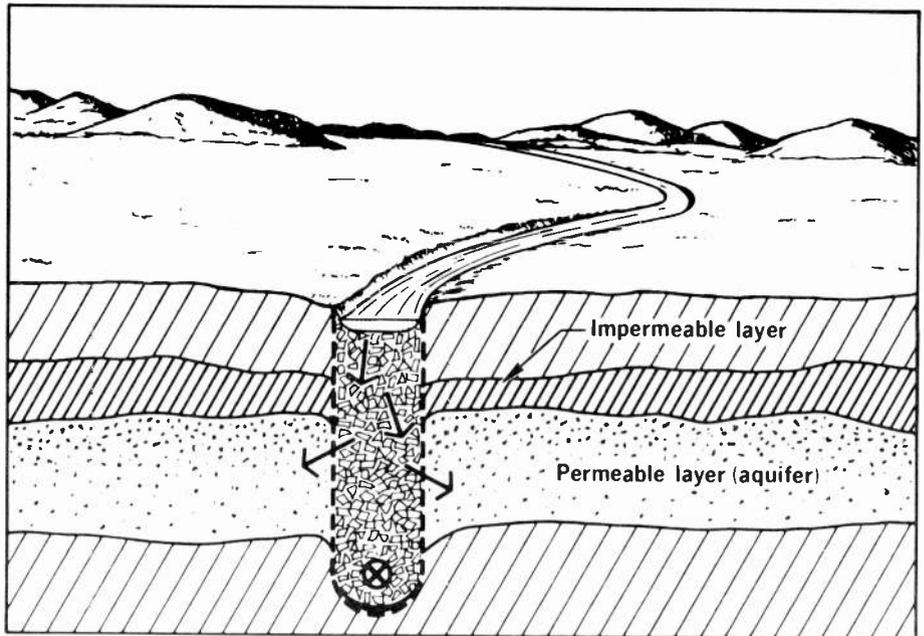By 1964, the AEC had reached the point of being able to release a policy statement and project charges for *Plowshare* thermonuclear explosives for use by industry in conducting studies of economic and technical feasibility. For \$350,000 (U.S./1964), one could purchase a bomb of 10 kilotons, and for a mere





A nuclear explosion might be used to break through a barrier to permit run-off water to be used to recharge underground aquifers.

\$600,000 (U.S./1964) one could obtain one's very own 2 megaton bomb. Concurrent with this policy statement and fee schedule, the U.S.S.R. announced that they too had a similar program, though they called it the "Nuclear Explosives for the National Economy" project. Bilateral talks immediately ensued, with the swapping of technical data, etc.

It is not the purpose of this article to dissect the entrails of *Plowshare* over its 16-year lifespan. But a few points are in order. There were some 40 plus tests, in-

dry rock and study the dispersion pattern of airborne radionucleotides under these conditions." It apparently was a success. The "Classified" test, at least according to what little information is available (nobody at the Department of Energy — the AEC's descendant — is talking much — apparently there was a liberal use of the "Secret" rubber stamp all over everything), was a device which ranged somewhere between 20 and 200 kilotons. Known as *Project Flask*, it was detonated in May of 1970 to meet the "objective of improving

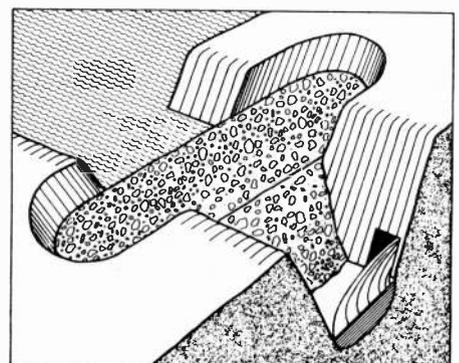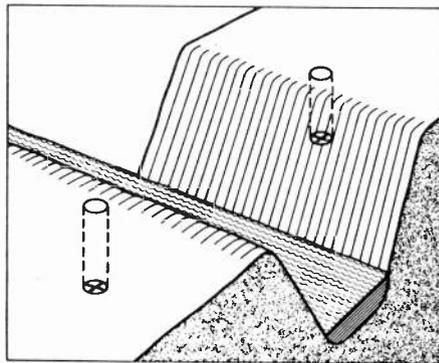

Mountain sides might be collapsed into valleys to make dams, with properly planned nuclear explosions.

volving thermonuclear devices and nitromethane compositions. They came under a variety of names — *Planquin*, *Pre-Schooner*, *Cabriole*, *Simms*, *Switch*, et., with all of the explosions taking place at the AEC's Nevada Test Site.

The thermonuclear devices ranged from an 85 ton yield to "Classified." The 85 ton one was known as Project Sulky and detonated in December of 1964. It was designed to meet the "objective of exploring the cratering mechanics in hard,

nuclear explosives for excavation purposes." Most of the thermonuclear explosions detonated in the later 60s and early 70s are simply listed as having a 'low' or 'medium' yield — probably in the order of 2 to 5 kilotons.

As for the major, most economically viable (or at least so it seemed initially) project, the Isthmian Project, it quietly died. The Atlantic-Pacific Interoceanic Canal Study Commission presented its final report later in 1970 and stated that:

"although we are confident that some day nuclear explosions will be used in a wide variety of massive earth-moving projects, no current decision on U.S. canal policy should be made in the expectation that nuclear excavation technology will be available for canal construction." The report further recommended that: "the U.S. pursue development of the nuclear excavation technology but not postpone Isthmian Canal policy decisions because of the possible establishment of feasibility of nuclear excavation at some later date." In other words, it was a dead duck.

As for *Plowshare* itself, according to Prentice Dean, Historian at the Department of Energy, it wound down fairly quickly in the early 1970s. First came the *National Environmental Quality Act* of 1970 which put strings on the use of nuclear devices of all sorts. Then, due to inflation, it was found that the AEC couldn't really offer anything that was cost effective, within the parameters of the above Act. Environmental concerns by the general public and many in government with respect to nuclear devices, meant that proposed projects were increasingly greeted with scepticism. The death blow, if a single point in time must be elucidated, came in 1973 with a project to use thermonuclear devices for gas stimulation. The gas field was stimulated all right, but it also was highly radioactive.

To date, there has been no further research in the peaceful applications of thermonuclear devices, though the military, with its Nuclear Cratering Group continued studies of a military nature, the data from which can be applied to civilian cratering operations. The point being, that with the increasing loss of water for the central U.S. agricultural heartland — its aquifer is drying out rapidly due to prolonged misuse — and large scale diversion projects under study — how to bring water down from Canada — coupled with the viciously high costs of such projects using conventional methods — the prospect arises of using such devices to 'move the dirt' as it were. While it is extremely unlikely that such a project could get past the environmentalists and government lobby groups, the data exists to demonstrate that it can be done and how to do it.

ETI

**ELECTRONICS
TODAY
BOOKSHELF
Page 57**



A canister containing the 26-kiloton explosive for Project Gasbuggy is lowered to a depth of 4240 feet and covered to within 50 feet of the surface with cement. Gasbuggy was an effort to determine the feasibility of recovering natural gas using nuclear explosive techniques. Photo courtesy of U.S. Department of Energy.

K.E.M. COMPUTER AND ELECTRONICS

ELECTRONICS KITS		• Digital Capacitance Meter 10pF~999uF ----- 42.95
• FM Wireless Mike ----- 16.95	• Music Synthesizer for Alarm, etc. -- 19.95	ASSEMBLED & TESTED P.C. BOARD UNITS
• Motion Alarm Sensor ----- 24.95	• Sensor Training Kit ----- 16.95	
• Mini Audio Amplifiers 5Watts RMS Output ----- 8.95	• Ultra Sonic Remote 1ch ----- 29.95 Controller 4ch ----- 49.95	• ICL8038 Function Generator - 36.95
• 4 Digit Resettable UP/DOWN Counter ----- 49.00	• Digital Frequency Counters ----- 69.95	• LCD Digital Panel Meter ±199.9mV FS. ----- 49.95
• 6-digit LED, 1Hz ~ 10MHz High Sensitivity 30mV rms	• Pre-scaler for Frequency Counter ±100 200MHz ----- 19.95	• Voltage Divider ----- 21.95
• 100. 550MHz(A&T) with Case 99.00	• Stepping Motor & Driver Controlled By Computer (APPLE II etc) with Program ----- \$65.00	• Ohm-Volt Converter ----- 24.95
		• Temp-Volt Converter ----- 19.95
		• 6 Digit Presettable UP/DOWN Counter -- 99.00
		• Data Readout I/F for our Freq.Counter (Peripheral for APPLE) --- 55.00

Full documents including
circuit diagram for every
kit --- \$4.00
(incl. postage)

EPROM PROGRAMMER (Peripheral for APPLE)

one touch operation (No software required) to
program 2716, 2732, 2532, 2732A, 2764 & 2564.
Industrial specifications. Assembled & Tested.
Metal case mounted ----- \$158.00

Plus \$3.00 each item for
postage & handling charge,
except \$8.00 for EPROM
Programmer.
Plus provincial sales tax.
C.O.D. mail order accepted

Super Toaster

KAIENTAI ELECTRONICS MERCHANTS LTD

2111 KINGSWAY, VANCOUVER, B.C. V5N 2T4
MAIL TO: P.O. BOX 6@126 STATION 'K'
VANCOUVER, B.C., CANADA V5K4W4
PHONE: (604) 435-9697

Circle No. 12 on Reader Service Card

Modem Auto-Answer



Auto-Tector. An auto-answer add-on for your Modem.

By K. Willmott

THE AUTO-TECTOR is a general purpose telephone line interface that is capable of operating with any device that normally connects to the phone line such as a dumb modem, or any other limited feature modem. Its purpose is to detect an incoming ring signal on the line and connect the device on its equipment jack to the line until either the device or the calling party hangs up.

This is useful when a computer is operated remotely, with timesharing or bulletin board systems for example. With some additional logic, it could also function as the front end for a voice type answering machine.

When its digital interface is connected to a computer, the unit is also capable of auto-dialing and delayed answer modes. A status output informs the computer of when an off-hook is presented to the line; unfiltered pulses are brought out also so that the answer mode may be over-ridden.

All connections to the phone line are electrically isolated from the timing circuit and computer interface. Internal time constants ensure that the device will work reliably on a standard phone line.

Line Side Operation

Referring to fig. 1, bridge rectifier BR1, fed through C1, supplies a rectified voltage corresponding to A.C. fluctuations in line voltage. Zener diodes Z1 and Z2 ensure that only a large amplitude signal such as a ringing voltage (about 100Vrms) will produce enough current through limiting resistor R2 and opto-isolator I1. Incoming tip and ring are brought out to another jack so a phone can be attached to the line side which is never disconnected. Relay contacts K1 and K2 connect the equipment side to the line when operated by the timer.

Bridge rectifier BR2 rectifies the line current so that the line current detector comprising R3, D1-D4, and I2 is in the proper polarity regardless of line polarity. Diodes D1-D4 clamp the voltage across the series combination of R3 and I2 to about 2.6 volts so that the max current rating of I2 won't be exceeded. The max voltage drop across the detector will never be more

than about 3.6 V. It is important that the voltage drop across the diodes be greater than the drop across I2 so that R3 has a drop sufficient to supply current to I2. For example, if the diode drop is 2.6V, the isolator drop is 1.6 V, R3 is 180 ohms, then the current will be $(2.6-1.6)/180$ or 5.6 ma.

Timer/Digital interface

Refer to fig 2. The unit has two operating modes—**answer** and **originate**. With the answer/orig switch S3 closed the 555 timer-IC1 is continuously triggered and holds the connect relay K1 operated. This closes contacts K1 in the line circuit to provide continuity to the modem from the line. The digital input signal ORIG going low will also put the circuit in the originate mode, after time delay T1.

In the answer mode the timer is triggered by pulses from the ring detection opto-isolator I1, and are buffered by a section of an open-collector buffer IC#3, these in turn are filtered by R9, R13 and C9 to remove the noise spikes that occur when (phone) line current is switched. The time constant T1 is set by the RC-diode network on pins 6 and 7 of IC1 and is approximately equal to:

$$0.6(1/(1/(R4 + R5) + 1/R6))C2$$

The reason for the delay is to hold the line until steady line current has been established. When this occurs (before IC1 times out), current in the output of line current detector, opto-isolator I2, holds the threshold pin (6) low and prevents the

timer from finishing its cycle until (phone) line current is interrupted. Since this happens at the end of a call or within a timed period thereafter, the circuit will connect the modem upon receipt of a call and automatically release it when the caller hangs up. The holding current from pin 5 of IC2 is blocked from C2 by diode D5. This means that after holding current is established, C2 continues to charge to +5. through R5 + R6 so that the cycle will end immediately after holding current is released and not after another time period T1 caused by C2's reactance.

The output of the 555 IC is amplified by transistor Q1 in order to drive the coil of relay K1. Almost any 12 volt relay will do, as long as the current demand is not excessive and it is reasonably fast (about 20 ms. or less). Diodes D6 and D8 clamp the inductive surges on the coil of K1.

A 7405 hex open collector buffer, IC2, provides two digital inputs and two digital outputs which may be used to control the box's functions from a computer or other control device. The inputs ORIG and BRK are activated by either applying a low level from an open collector gate output or by grounding them with a switch. They simply duplicate the action of the front panel switches "originate" and "disconnect".

The output OFF HOOK reflects the state of the OFF HOOK LED and the output RING DET supplies rough unfiltered ring pulses. If the latter signal is used externally, it has to be debounced.

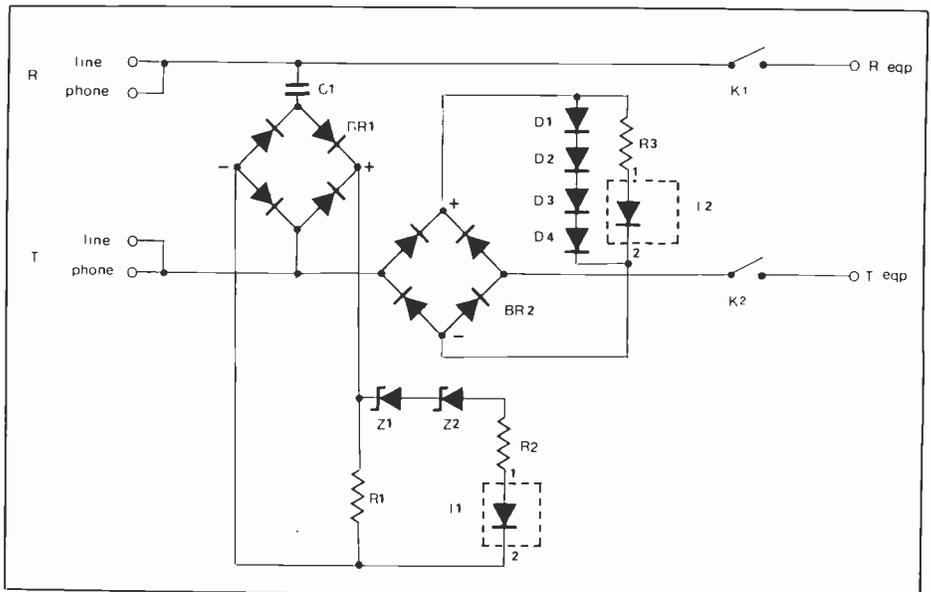


Fig 1. Line side schematic


Circuit Supplement

A circuit for every occasion. From beginner to advanced, a whole bunch to keep you busy 'til next month.

BALANCED INPUT PREAMP

THE circuit is a relatively straightforward instrumentation amplifier. The main differential stage is formed by IC3, the TL071. This is a biFET op-amp with good common mode rejection ratio (CMRR) figures. This stage is buffered from the inputs by a pair of NE5534A op-amps that also provide additional gain and determine the overall noise performance of the preamp. The overall gain of the preamp is determined by the gain of the first and second stages. The gain of the second stage is determined by the ratio of R11 to R9, and is around 10. The gain of the first stage is approximately 20, giving an overall gain of about 200, or 46 dB. If you require a different gain to this, try to keep the ratios of gain in the first and second stages the same. The amount of gain provided here should be suitable for most microphones, providing around 100 mV output from a 0.5 mV input signal level.

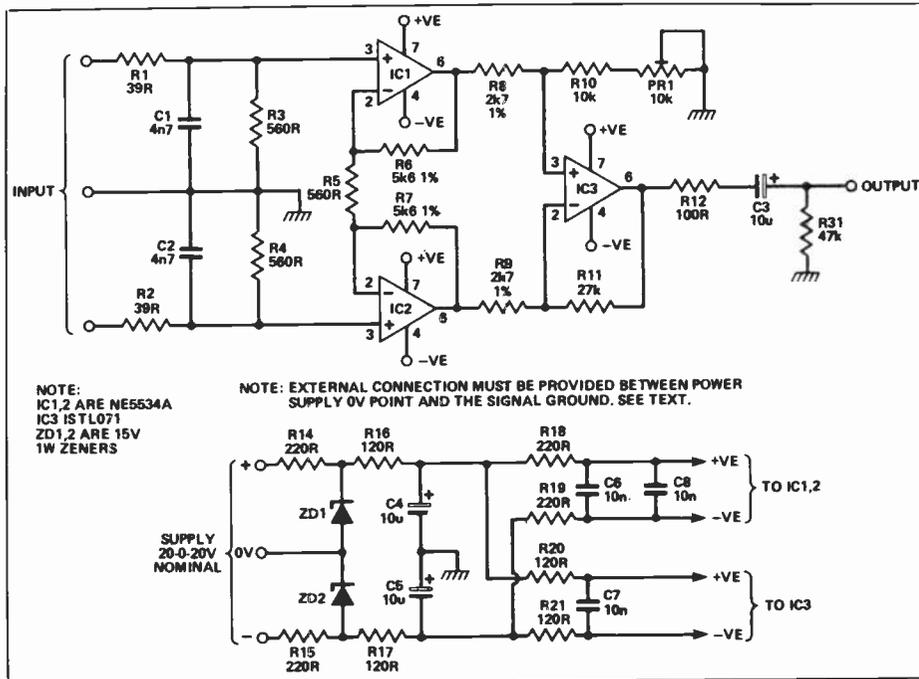The circuit is DC-coupled at the input. This assumes that the driving source will be transformer or capacitively coupled at the output, which should be a safe assumption. The input impedance of the stage is set by the two input resistors R3 and R4. To increase the input impedance, simply increase the value of these resistors.



The RC networks consisting of R1-C1 and R2-C3 are high frequency filters to reduce the circuit's susceptibility to Rf interference.


The split power supply is provided either from two zener regulators or from a

well-regulated and filtered DC source. The supply pins to each IC are decoupled by 1k0 resistors and 10n capacitors to prevent IC-to-IC interaction and possible feedback via the supply rails.

TONE CONTROL

THE type of tone control fitted to most hi-fi equipment is far from ideal, usually being much too dramatic in operation — for example, if it is required to lift frequencies below about 100 Hz, the effect is usually to lift by varying amounts, everything up to at least 1 kHz, and even higher.

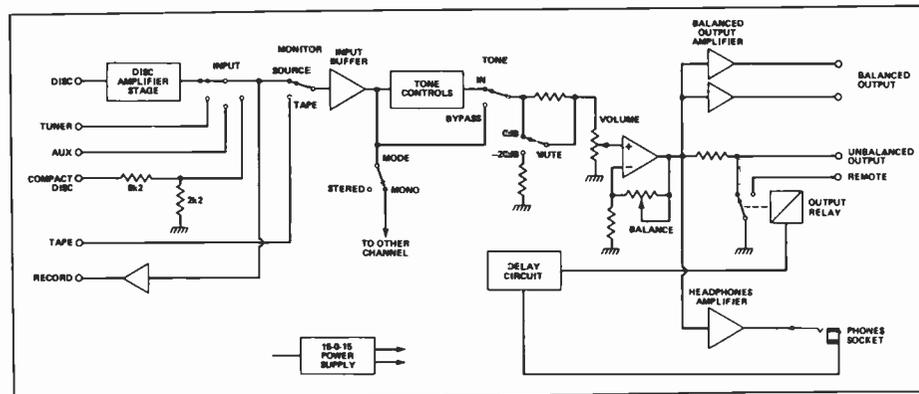The circuit shown is somewhat more sophisticated than usual, possessing in addition to the normal lift and cut controls, adjustment of the turnover frequencies of the two sections.



Circuit diagram of the tone control module.

ZERO CROSSING SWITCH

MOST of the functions of this switch are contained inside the IC, so let's take a look at the zero-voltage switch IC first.

Three zero-voltage switches are made by RCA — the CA3058, CA3059 and CA3079. They are all designed to control a thyristor in a variety of AC power switching applications for AC input voltages of 24,230, 230 and 277 V at 50, 60 and 400 Hz. Each incorporates four functional blocks as follows (refer to the block diagram here):

- Limited-Power Supply — permits operation directly from an AC line.
- Directional On/Off Sensing Amplifier — tests the condition of external sensor or command signals. Hysteresis or proportional control capability may easily be implemented in this section.
- Zero-Crossing Detector — synchronizes the output pulses of the circuit at the time when the AC cycle is at zero voltage point; thereby eliminating radio-frequency interference (RFI) when used with resistive loads.
- Triac Gating Circuit — provides high-current pulses to the gate of the power controlling thyristor.


In addition, the CA3058 and CA3059 provide the following important auxiliary functions:

- A built-in protection circuit that may be actuated to remove drive from the triac if the sensor opens or shorts.
- High power DC comparator operation is provided by overriding the action of the zero-crossing detector. This is accomplished by connecting pin 12 to pin 7. Gate current to the thyristor is continuous when pin 13 is positive with respect to pin 9.

Because the CA3079 does not incorporate the built-in protection circuit, the CA3058 or CA3059 have been specified for this project. If the project is used to control a fish tank heater, one doesn't want to boil one's finny friends in the event of a thermistor failure!


Now we know what's inside the IC, how is it put to work in the circuit?

Initially, consider the triac to be turned off. Some current flows into pin 5 of the IC and this is limited by R1-3 and rectified within the IC to provide about 8 V DC for the operation of the circuit. Capacitor C1 smooths this supply. Inside the IC are a number of separate sub-circuits centered on a comparator ('On/Off Sensing Amp'). Connection of pins 9, 10 and 11 uses internal resistors to establish half supply rail (about 4 V) as one of the levels to be compared. When the voltage on pin 13 exceeds half rail potential, the comparator activates a cir-

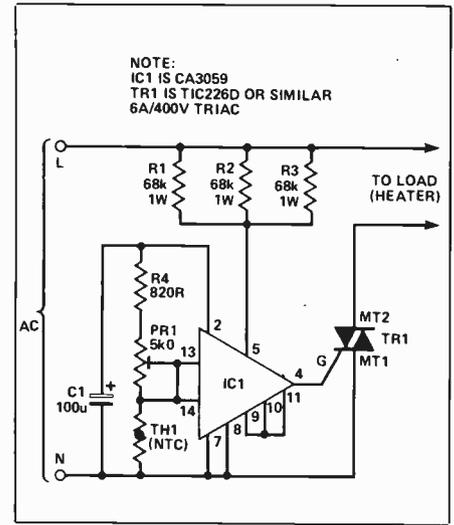

cuit which turns the triac on at the next supply zero, and each subsequent zero until the voltage falls below half rail.

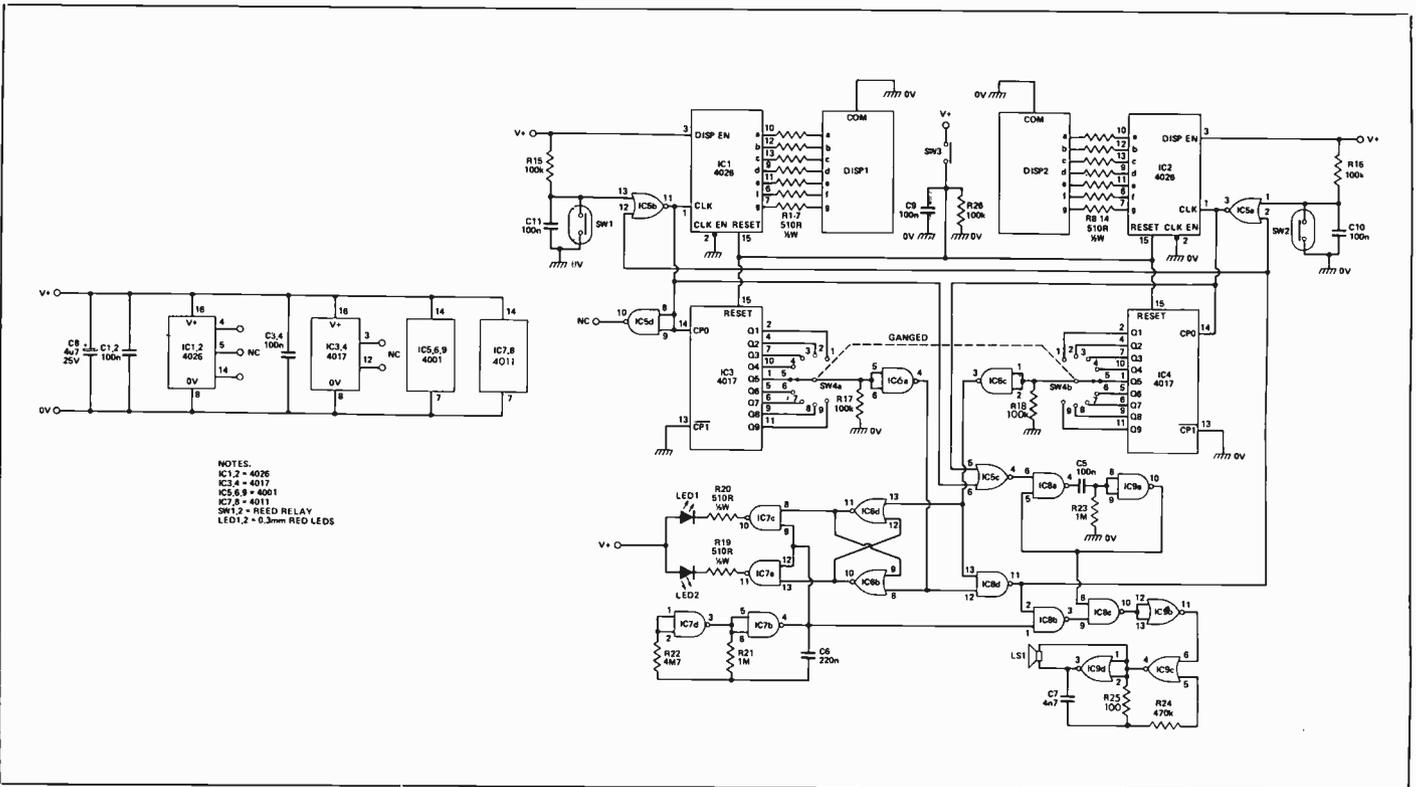Clearly then, PR1/R4 must be selected so that they add up to the resistance of the sensing thermistor at the temperature for which it is desired to regulate. Thus, then the temperature reaches the preset point, the voltage across TH1 corresponds to half rail potential on pin 13.



SLOT CAR LAP COUNTER

The counter is operated via SW1 and SW2, using small magnets cemented to the underside of the cars. The supply voltage can be 9 V DC to 15 V DC unregulated.

COMPUTER OUTPUT DRIVER


FIRST of all, note that the component values shown on the circuit diagram are for the 2A output version. Other output current versions are possible, but basic circuit operation is the same.

The host processor connects to the driver board via the 16-pin DIL socket. IC5 compares the logic levels present on the DIL socket pins 14(A1), 11(A2), 13(A3) and 12(STROBE) to the settings of SW1a-d respectively. When a match is found, pin 10 of IC1 goes high. The STROBE input should receive a pulse edge timed to coincide with a valid data bus (pins 1 to 8 of the DIL socket) and a valid address (pins 11, 13, 14). Note that either a positive-going or a negative-going edge of the strobe pulse may be used, according to whether the setting of SW1d is closed or open, respectively.

The A0 input on pin 10 of the DIL socket determines which of the two on-board latches are being addressed. When pin 10 is low, IC4 is selected ('B outputs active'), if high, then IC3 ('C outputs active').

Each driver circuit buffers one of the 16 latch outputs and provides an open collector current sink of up to 3A.

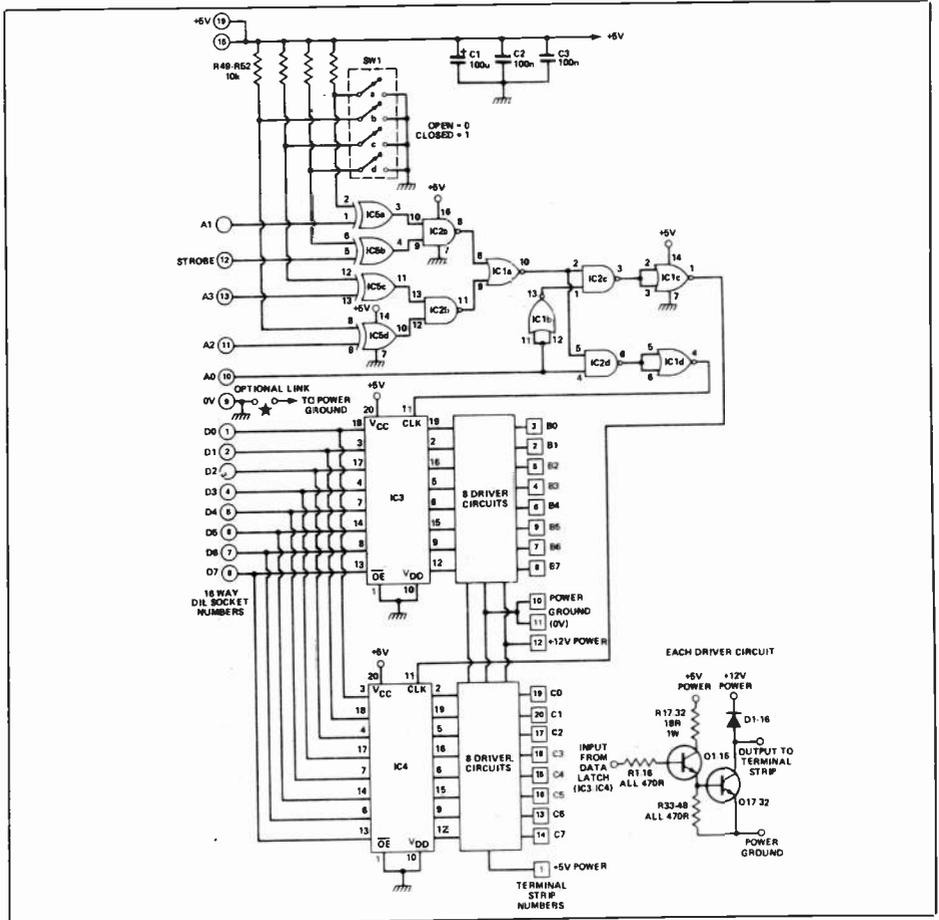To simplify the description of the driver circuits, consider the one comprising R1, Q1, R17, R33, Q17 and D1. Diode D1 is a flywheel diode and protects transistor Q17 from excess back emf voltage when turning off inductive loads, such as a solenoid. When the latch output is low, Q1 is held off via R1 and Q17 is held off by R33. Resistor R33 speeds up the turn-



Circuit diagram for the ETI Computer Output Driver. Our artist drew the line (!) at reproducing 16 identical driver circuits, so we've shown just the one.

off time of Q17 by providing a path to remove stored charge in the base-emitter junction.

When the latch output is high, about 5 mA of current flows into the base of Q1, thus turning it on. R17 sets the base cur-


rent of Q17 and is chosen according to the output current requirement. Transistor Q17 must be saturated in order to reduce power dissipation and up to 300 mA of base current may be required for 3A loads.

OFFBEAT METRONOME

THIS is a metronome with a difference. The initial requirement was for a simple metronome which would enable the musician or musicians to practise playing to an even rhythm, instead of succumbing to the inevitable temptation to play faster and faster until collapse from exhaustion ensues. The project became more ambitious when we decided to add a rhythm accent or offbeat to give a variety of rhythm 'feels' to play against.

The required variable offbeat was achieved by inserting another note between the regular beats, which can be adjusted to fall anywhere between the two beats, or in unison with one beat to give a stronger accent on that beat, or not to occur at all.

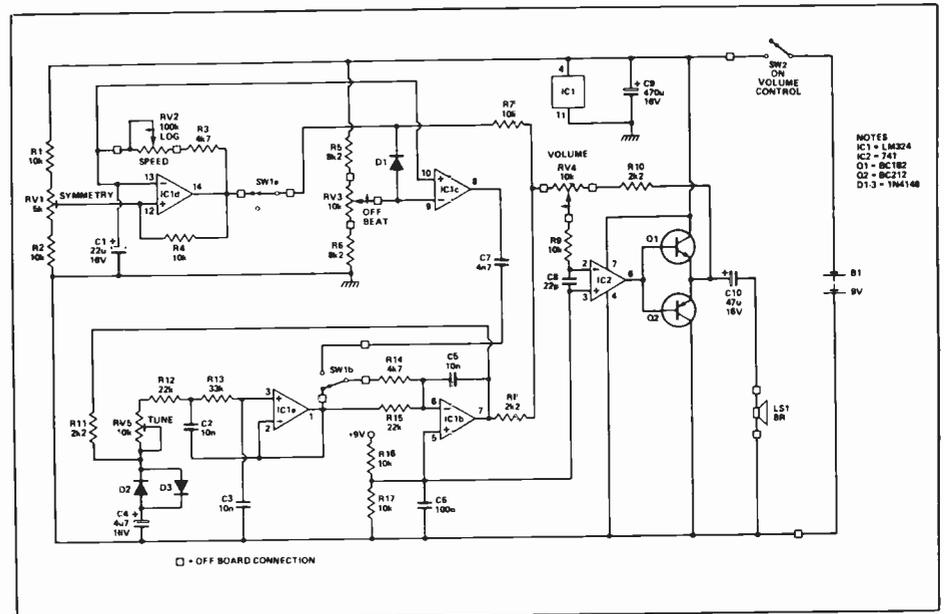The final embellishment was the addition of a pure 'A' tone for tuning purposes.




COMPUTER TEMPERATURE CHECKER

ANALOG Devices' AD590 temperature sensor is used to provide an output in degrees Centigrade of the temperature inside the computer console. Zener diodes ZD1,2 and preset PR1 provide the conversion voltage of -2.732 V needed to change the degrees K to degrees C. PR2 is used to zero the AD590 sensor linear output at some point of its scale (-50 to +150°C). I suggest the 0.00 V output should be set with the sensor in a beaker of a crushed melting ice. The sensor output is best displayed on a digital voltmeter (0.01 V per degree C) or on the specialized DVM chip (see previous circuit).

A voltage comparator (IC1) is used to compare the temperature sensor output with a value preset by PR3 and trigger the high temperature alarm when this value (65°C-70°C for most TTL and CMOS) is exceeded. This alarm output can be connected to a suitable optional alarm circuit.

AUDIO POWER METER

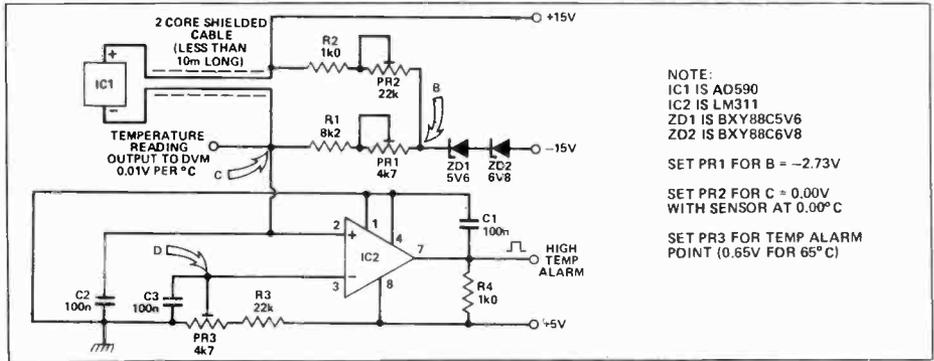POWER is provided by a very simple dual rail supply derived from a centre tapped transformer and bridge rectifier. The output from this is smoothed by C5,6 and



Circuit diagram for the temperature sensor and alarm.

NOTE:
IC1 IS AD590
IC2 IS LM311
ZD1 IS BXY88C5V6
ZD2 IS BXY88C6V8

SET PR1 FOR B = -2.73V

SET PR2 FOR C = 0.00V
WITH SENSOR AT 0.00°C

SET PR3 FOR TEMP ALARM
POINT (0.65V FOR 65°C)

regulated to + and - 15 V by IC5,6. C7,8 remove any residual noise and improve transient performance.


The main part of the circuit is in two identical parts, so we shall only consider one of them. The signal whose power is to be measured enters SK1 and leaves SK2. En route it passes through R1 which develops a voltage across it proportional to the instantaneous current flowing. At the same time the voltage across the input is also sampled. Two sections of SW1 tap off portions of the voltage and current signals and pass them to IC2a and IC1a respectively. The resistors R2 to 8 are

chosen to give the ranges indicated on the panel. IC1a amplifies the current signal by a factor of just under 60, while R11 and 12 enable a small amount of common-mode signal on the ground lines to be eliminated if desired. From IC1a, the current signal passes to IC1b which is a buffer whose gain can be set to approximately 2, 2.8, or 4. IC2a performs a similar job on the voltage signal except that when the gain of IC1b is 2 that of IC2a is 4 and vice versa. The diode network (D1 to 4 and ZD1,2) together with IC2b detect overload conditions. If the peak signal exceeds the zener voltage, then either the + input of IC2b

One-Stop Electronics Shopping

First-time shoppers at Arkon are often amazed at the sheer volume of items and services we offer. We can provide the best in price, quality and selection to the professional and hobbyist alike.

POWER SUPPLY
SPECIAL
\$59.95

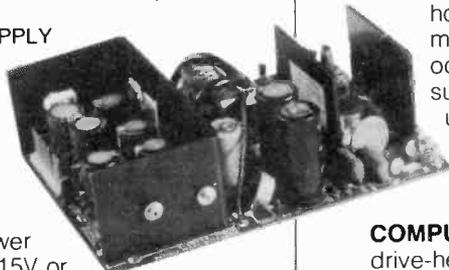

SIERRACIN

Switching power supply with 115V or 230V input and taps at 0V, -5V @ .5A, +5 @ 4A, ±12V @ .5V, and +15V @ 1A. Threaded standoffs make for easy mounting in one of our many Hammond cases.

A FULL SELECTION OF COMPONENTS

is one of the things we're noted for. Semiconductors, (TTL, CMOS, Linear, CPU, memory, transistors, rectifiers, SCRs, triacs), capacitors, (tantalum, film, electrolytic, ceramic), connectors, (telephone, audio, video, RF, edge, ribbon, etc.), potentiometers, trimmers, fixed resistors, cases, surplus parts. Everything you need for your project including tools, manuals and test equipment.

CUSTOM CABLES

are available from our in-house factory. You can now make full use of those oddball peripherals you got such a great deal on. If you're unsure of which pin goes where, we also have the manuals and expertise to help you out.

COMPUTER CORNER - We have drive-head cleaning kits, power supplies, ribbons, and drafting aids for designing PCBs. Also the best selection of software, books, and magazines around. Various computers on sale too.

KITS

CODE OSCILLATOR	\$2.00
LED BLINKER	2.00
FM WIRELESS TRANSMITTER	3.00
VIDEO MODULATOR	3.00
SIREN	3.50
UNIVERSAL TIMER	3.00


UNPOPULATED BOARDS

COLOUR ORGAN	1.50
SHUTTER TIMER	2.00
300 WATT AMPLIFIER	3.50
CASSETTE INTERFACE	2.00
GUITAR EFFECTS	1.00
STROBE	1.00
GRAPHIC EQUALIZER	2.00
DIGITAL THERMOMETER	2.00

MAIL ORDERING is encouraged. Call or write for our catalogue (indicate your interests). Computer shopping is also available through Networks Canada (416) 593-7460. VISA, Mastercharge, and American Express are welcome. Call the store at (416) 593-9653, or write to Arkon Electronics, 409 Queen Street West, Toronto, Ontario, M5V 2A5.

arkon

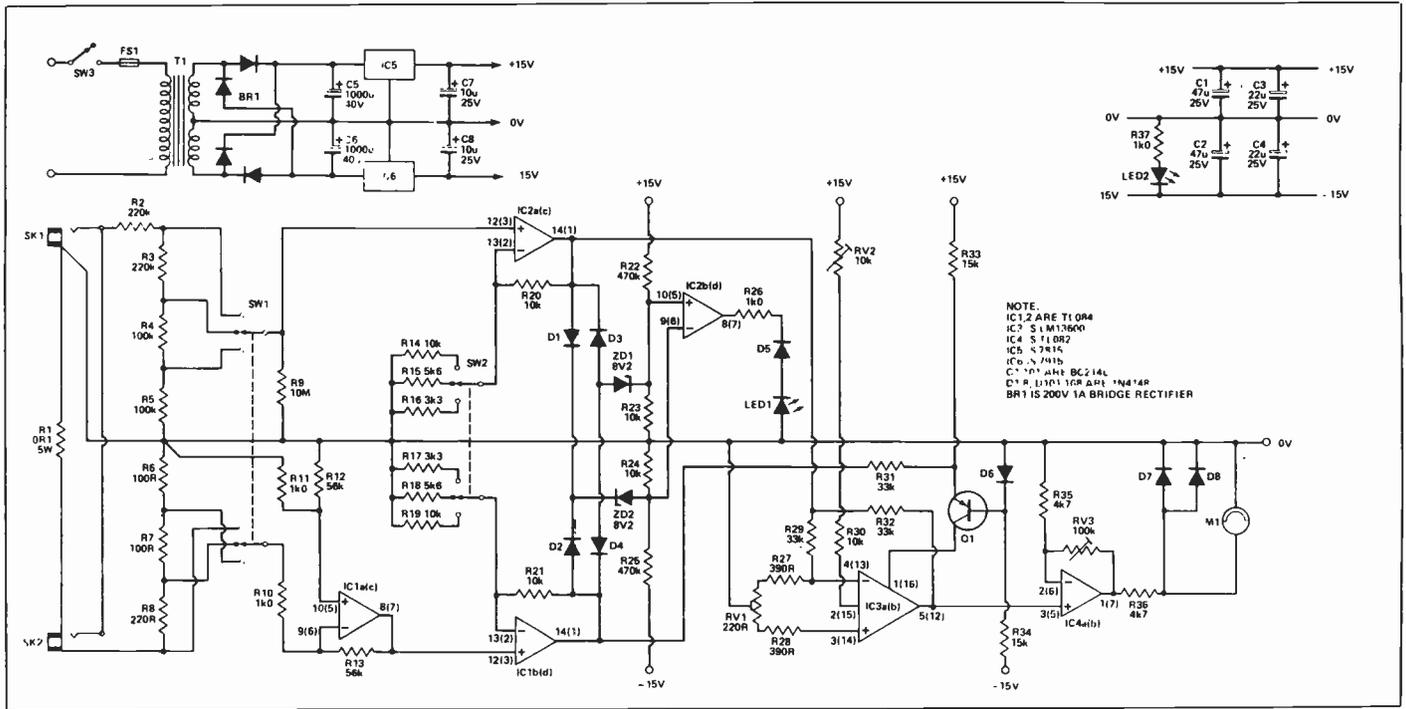ARKON ELECTRONICS LTD. 409 QUEEN ST. W. TORONTO, ONTARIO



Circuit diagram of the audio power meter. Note that only one meter channel is shown (PSU section is common).

will be pulled low, or the - input pulled high. Either of these conditions will cause the output of IC2b to switch from the positive supply rail to the negative supply rail and illuminate LED1. R26 and D5 limit the current and prevent reverse voltage on the LED.

The next section is the multiplier and

this is constructed around one half of an LM14600 transconductance amplifier. The part we use for this project has the property that its output current is proportional to the product of the input current and the bias current, and inversely proportional to the current through the linearizing diodes on the device. R34, D6


and Q1 form a simple virtual earth summing point for producing the bias current, which is a constant (via R33) plus a signal component (via R31). The other input to the device is via R29, which converts the voltage signal into a suitable current.

SUPPLY VOLT CHECKER

THIS simple scanning circuit is used to check the status of the multitude of DC supply lines in a typical computer/peripherals system. A continuous clock input is divided by IC1 (more 7493s can be used if only fast clocks are available) and decoded by IC2.

The various supply voltages are divided down by the resistor networks R2-R9 and R10-R17 to provide safe levels for the analogue multiplexer IC3, a CMOS 4051B, which passes the selected supply line voltage to the standard DVM circuit. In this case the Intersil ICL 7107 single chip voltmeter is used together with four 7-segment LEDs to provide an accurate visual check on the DC supply lines.

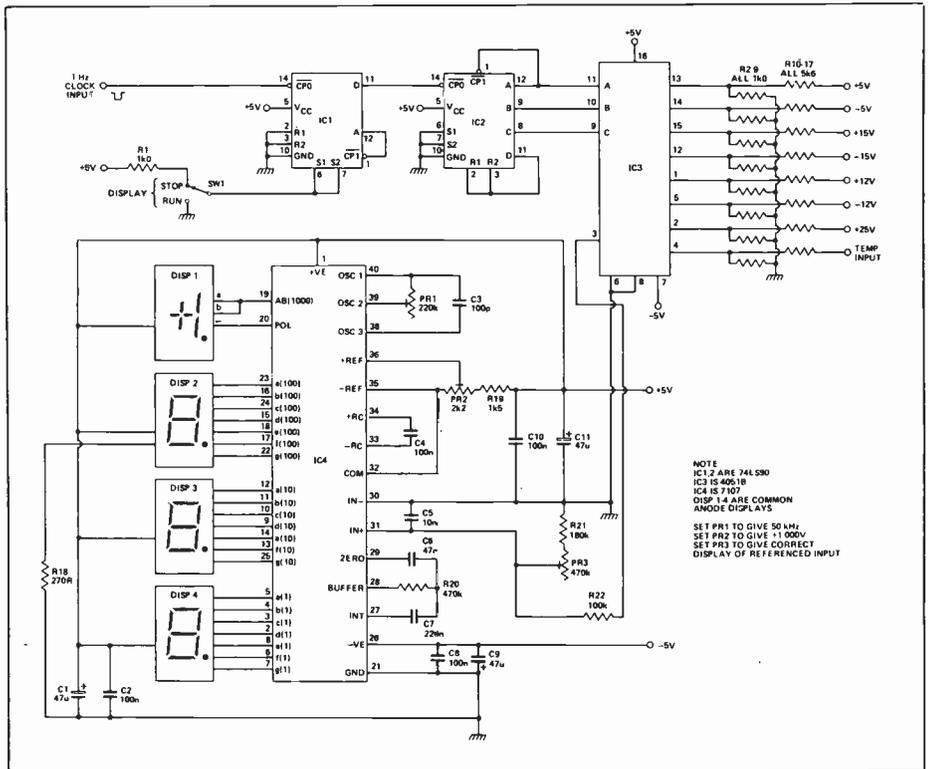The last input is used to display (in °C) the temperature reading taken by the following circuit.



BENCH POWER SUPPLY

PARTS LIST

Resistors (all 1/4 W, 5%, unless otherwise stated)

R1,10	100R
R2	10R
R3,5,15,18, 19,22,29,30, 33,36	47R
R4,23,28, 31,32,41	1k0
R6	R33, 3W wirewound
R7,8	330R
R9,34,38	2k2
R11	100k
R12	10R, 1/2W
R13	47R, 1W
R14	1k0, 3W wirewound
R16	5k6
R17	220R
R20,35,37	1R8, 4W wirewound
R21	10k
R24,25,39	470R, 1/2W
R26	1k2
R27	1k5

R40	680R, 1/2W
R42	12k
RV1	100R
RV2	1k0
PR1,3,5,6, 7,9,10,11	470R horizontal skeleton preset
PR2	2k5 horizontal skeleton preset
PR4,8,12	10k vertical skeleton preset

Capacitors


C1	5000u 16V electrolytic
C1	100u 25 V electrolytic
C3,8,9,12, 13	10n 50 V ceramic
C4	1000u 25 V radial elec- trolytic
C5,11	1000u 40 V radial elec- trolytic
C6	470u 40 V radial electrolytic
C7	10u 63 V radial electrolytic
C10,14	220u 25 V radial electrolytic

Semiconductors

IC1,2	MC1723
Q1,4,9	2N3232
Q2,5,8,11	2N3053
Q3,6,7	2N3904
Q10,12,13, 19	MM4002
D1,2,3,4,5, 6,12,13,18, 19	
D7,8,9,10, 14,15,16,17	1N5401
D11	1N4148


Miscellaneous

M1,2	1mA FSD meter
SW1	toggle, 2A
SW2	3 pole, 3 way rotary switch
PCB; IC sockets; M4 fibre washers; Heat- sinks; insulated terminals; mains fuseholder and fuse; knobs; mains neon; Case, mains cable and strain-relief bush; solder tags; in- sulating kits for the power transistors; nuts, bolts, washers, etc.	

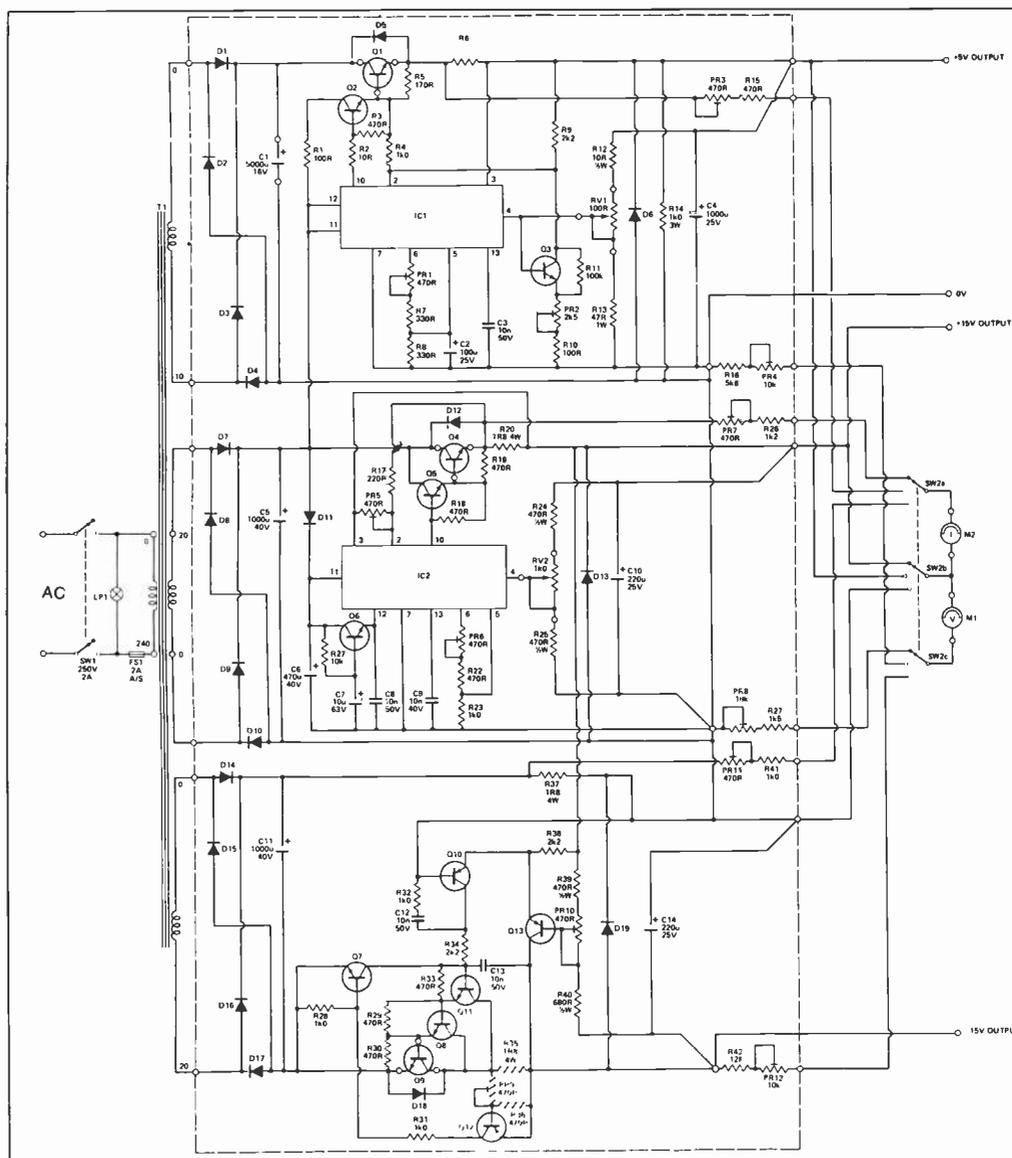

Circuit diagram of the bench power supply unit. Separate 3 amp transformers can be used.

ETI

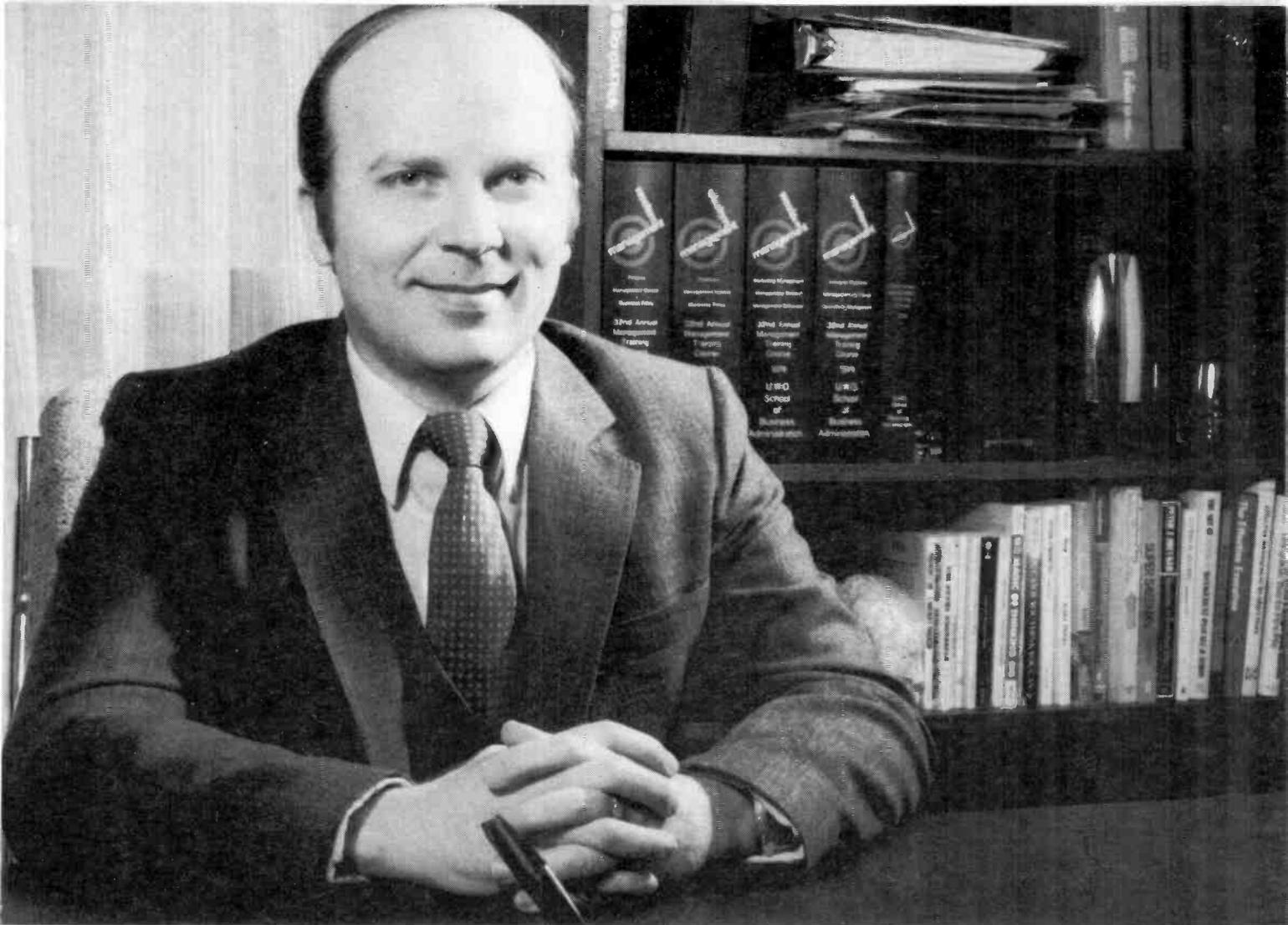

Electronics Today helped John Bergeron build his business.

John Bergeron of Daetron Digital Capacitance Meters has a simple philosophy about advertising. The publication delivers sales or he doesn't advertise.

Electronics Today is the cornerstone of Mr. Bergeron's and Daetron's marketing plan. He doesn't communicate with Electronics Today readers spasmodically, but every month. In fact, Mr. Bergeron says, "Electronics Today is the best publication I ever advertised in. It delivers better than U.S. magazines I have tested with ten times the circulation at three times the price."

This tells you a great deal about Electronics Today and its readers. They are informed, educated, and they buy. Next month is the month you should rethink your marketing plan and move to Electronics Today . . . every month.

Let our Electronics Today Account Executive show you how it can deliver for you.

**Electronics
Today** **can help build your business as well.**
INTERNATIONAL

For Advertising Information Call (416) 423-3262

In Quebec (514) 735-5191

Computing today



ZX 80-81 Programs

Are you starving your ZX80 or ZX81? Here's more food for that voracious little devil.

Trigonometric Fourier Synthesis Program (ZX81 with 16K RAM)

by Michael Krochmal

ANY periodic waveform can be expressed as the sum of a number of sinusoidal functions, provided that it satisfies certain conditions known as the Dirichlet conditions. These are that:

- 1) The waveform must have only a finite number of discontinuities per period;
- 2) The waveform has a finite average value for the period, and
- 3) The waveform has a finite number of positive and negative maxima.

Unfortunately, it is not immediately obvious to the neophyte that a few sinusoids thrown together can really end up producing squarewaves, sawtooth waves and all manner of marvellous shapes!

My encounter during undergraduate days with Fourier analysis and synthesis was limited to a series of tedious manual calculations, and frankly, left me cold. Insight into principles lagged far behind. (Sorry, lecturers).

The accompanying program, for a ZX81 with 16K expanded RAM, graphically illustrates Fourier trigonometric synthesis. The program is largely self-

explanatory, and is intended as a framework for exploration of the mysteries of Fourier methods. Although the present listing produces a squarewave, modifications are given for production of a sawtooth, and similar modifications will enable generation of any periodic shape desired.

Note that since calculation of the resultant occurs point-by-point, the limit to the number of harmonic components is very large (approximately 65,000 I believe). Naturally, calculations involving such a large number of components might take a little longer!

FOURIER TRIGONOMETRIC SYNTHESIS PROGRAM.

```
10 REM COPYRIGHT M.S. KROCHMAL 1982
20 SLOW
30 PRINT "FOURIER TRIG SYNTHESIS"
40 PRINT "ENTER NUMBER OF ODD HARMONIC COMPONENTS"
50 INPUT B
60 PRINT B
70 PRINT "IF YOU ONLY WISH TO VIEW COMPONENTS, THEN ENTER
"\"C\"". IF YOU ONLY WISH TO VIEW RESULTANT, THEN ENTER \"\"R\"\". TO
VIEW BOTH, ENTER \"\"B\"\" "
80 INPUT W$
90 PAUSE 100
100 CLS
110 DIM X (2*B)
120 DIM Z (64)
130 FOR N = 0 TO 63
140 FOR C = 1 TO 2*B STEP 2
150 LET X(C) = (1/C)* SIN (C*(N/32)* PI)
160 NEXT C
170 IF W$ = "R" THEN GOTO 220
180 FOR E = 1 TO 2*B STEP 2
190 PLOT N, 22 + 20*X(E)
200 NEXT E
210 IF W$ = "C" THEN GOTO 320
220 LET Y = 0
230 FOR D = 1 TO 2*B STEP 2
240 LET Y = Y + X(D)
250 NEXT D
260 LET Z(N+1) = Y
270 PLOT N, 22 + 20*Y
280 NEXT N
290 IF W$ = "FINISH" THEN GOTO 410
300 IF W$ = "R" THEN GOTO 410
310 IF W$ = "B" THEN GOTO 390
320 IF W$ = "C" THEN NEXT N
330 PRINT "DO YOU WANT TO PLOT RESULTANT NOW ? (YES OR NO)"
340 INPUT W$
350 IF W$ = "NO" THEN GOTO 450
360 LET W$ = "FINISH"
370 LET N = 0
380 GOTO 220
390 PRINT
400 PRINT
410 PRINT "ANOTHER SYNTHESIS ? (YES OR NO)"
420 INPUT A$
430 CLS
440 IF A$ = "YES" THEN GOTO 30
450 PRINT "DO YOU WANT TO PRINT A LIST OF RESULTANT MAGNITUDES
VERSUS PHASE ANGLE ? (YES OR NO)"
460 INPUT B$
470 IF B$ = "NO" THEN STOP
480 PRINT "POSITION";TAB 10;"DEGREES";TAB 20;"VALUE"
490 FOR N = 1 TO 64
500 PRINT N;TAB 10;(N-1)/64*360;TAB 20;Z(N)
510 NEXT N
520 STOP
NOTES:
1 THESE LINES DEFINE THE RESULTANT WAVESHAPES.
2 PLOT OF COMPONENTS.
3 THESE LINES "BUILD UP" THE RESULTANT FROM THE COMPONENTS.
ONE POINT AT A TIME.
4 PLOT OF RESULTANT.
POSTSCRIPT:
FOR A SAWTOOTH GENERATOR, MAKE THE FOLLOWING CHANGES:
140 FOR C = 1 TO B
150 LET X(C) = (0.5/C)* SIN(C*(N/32)* PI)
180 FOR E = 1 TO B
190 FOR D = 1 TO B
```

Program Labels, for ZX81 With Printer

by W. Herlihy

THE following is a program which can be used to generate labels for cassette programs. The paper from the ZX printer is just the right width to fit inside a standard cassette case and this program gives the correct spacing of folds and titles; the re-

THE PRINT-OUT FROM THIS PROGRAM, WHEN FOLDED ALONG THE DASHED (---) LINES, WILL FIT NEATLY INTO THE STANDARD CASSETTE CASE. LEAVE A LITTLE BLANK PAPER AT THE START AND END OF THE RUN TO BE FOLDED OVER. THE LABEL CAN BE FASTENED WITH A LITTLE STICKY TAPE.

```

1 LPRINT "-----"
2 LPRINT " "
3 LPRINT " "
4 LPRINT " "
5 LPRINT TAB 5;"CASSETTE NAME"
6 LPRINT " "
7 LPRINT " "
8 LPRINT " "
9 LPRINT "-----"
10 LPRINT " "
11 LPRINT TAB 5;"CASSETTE NAME"

```

quired names and tape counter readings are quickly inserted into the program using the edit facility.

The dashed lines given by lines 1, 19,

```

12 LPRINT "-----"
13 LPRINT " "
14 LPRINT " "
15 LPRINT "NAME + MORE INFORMATION, ETC"
16 LPRINT " "
17 LPRINT "*****"
18 LPRINT "SIDE 1"
19 LPRINT " "
20 LPRINT "0-20 TRACK NAME"
21 LPRINT "20-35 ETC,ETC"
22 LPRINT " "
23 LPRINT "*****"
24 LPRINT " "
25 LPRINT "SIDE 2:"
26 LPRINT " "
27 LPRINT "0-20 TRACK NAME"
28 LPRINT "20-35 ETC,ETC"
29 LPRINT " "
30 LPRINT " "
31 LPRINT " "
32 LPRINT " "
33 LPRINT " "
34 LPRINT " "
35 LPRINT "-----"
36 LPRINT " "
37 REM :A LIMITED AMOUNT (ABOUT 11 LINES OF INFORMATION CAN BE ENTERED HERE AND CAN BE READ WITH THE CASSETTE CASE OPEN.

```

NOTE THAT THE LINE NUMBERS OF THE DASHED LINES ARE THE ONLY ONE'S THAT SHOULD NOT BE CHANGED. THE OTHERS CAN BE ALTERED TO FIT THE PROGRAMS ON THE CASSETTE.

13 and 35 in the program create just the right spacing for folds to enable the label to fit snugly in a cassette case. A sample is shown below the program.

```

-----
ZX81 GAMES (1)
-----
ZX81 GAMES (1)
-----
GAMES FOR ZX81. (32K RAM NEEDED FOR MOST.)
*****
0-15 INDEX
15-30 SLIDING LETTERS
30-45 MAZE GAME
45-60 DRAUGHTS
60-95 ESCAPE
*****
SIDE 2
0-50 GOLF
50-75 ZX81 CIPHER
75-90 HANGMAN

```

MOST GAMES ARE SELF EXPLANATORY. IN "GOLF" THE DIRECTION IS GIVEN AS CLOCK MARKINGS; FRACTIONAL DIRECTIONS (E.G.2.7) ARE ALLOWED.

'Dodge' Game For The ZX81, 1K (or 16K)

by Benjamin Smith

'DODGE' is a fast, real-time moving graphics game in which the player must try to guide his spacecraft (represented by 'V' across an enemy space zone without being hit by one of the missiles which constantly emerge from the lower part of the screen. The keys '5' and '8' are used to move the craft left and right respectively. If the ship is hit, a score appears, along with the highest score so far. In the next game (which begins as soon as a key is pressed), the player must attempt to beat this record. The program may be terminated by BREAK.

This particular version is designed for the 1K ZX81, hence the use of expressions instead of numbers in lines 20 and 30 (numeric literals on the Sinclair chew up an additional six bytes). If 16K is available, however, the following modifications should be made:

```

20 LET B = 0
30 LET S = -1
60 PRINT AT 0, 31
70 IF PEEK (16928+P)<>0 THEN GOTO 130
85 PRINT AT 9, P+RND-RND-1;
90 IF RND<.3 THEN PRINT "☐";
95 PRINT TAB 31

```

Beware of making any other alterations as the address reference in line 70 will be invalidated.

```

10 POKE 16418, 14
20 LET B = PI-PI
30 LET S = -PI/PI
40 LET P = INT (RND*12+2)
50 LET S = S + 1
60 PRINT AT 0, 14
70 IF PEEK (16897+P)<>0 THEN GOTO 130
80 PRINT AT 0, P; "V"
90 IF RND<.3 THEN PRINT AT 9, P+RND-RND-1; "☐"
100 LET P = P+(INKEY$ = "8")*(P<13)-(INKEY$ = "5")*(P>1)
110 SCROLL
120 GOTO 50.
130 CLS
140 IF S>B THEN LET B = S
150 PRINT "YOU SCORE "; S; ", BEST SO FAR "; B
160 PAUSE 550
170 CLS
180 GOTO 30

```



"Rapid Descent" For The 1K ZX80

by R.A. Chalmers

THE program starts by giving the height and acceleration, in this case 1,000 feet and acceleration of 32 ft/sec/sec*, the pull of gravity. After inputting both the period of time one wishes to check, and the initial velocity at the 1,000 ft. mark,

the program will give adjusted height and new velocity. The catch now is to bring the vehicle to zero height and velocity. Input F is the accelerator, and -F will allow the vehicle to move towards the surface, while F will increase height by applying sufficient retard acceleration to reverse the vehicle.

The program is based on the calculations of acceleration and velocities, and as it stands, is stretching the memory to its limits. However, as the calculations remain the same, the program is eminently

suitable for expansion and use on larger computers.

Notes:

U = initial velocity

F = given acceleration

V = velocity at end of time, T, in feet/second.

* The program is run in feet as the equivalent in metric to 1 ft/s/s is 981 cm/second/second. The ZX80 has limited maths ability. The reason for the program's name will be immediately obvious to anyone attempting to land safely!

```

5 LET H=1000
10 PRINT " INITIAL HEIGHT = ";H;"FEET AND ACC.OF 32 FT/S/S"
12 PRINT " INPUT T(FLIGHT TIME IN SECONDS)"
13 PRINT "AND U(INITIAL VELOCITY)"
15 INPUT T
16 INPUT U
18 CLS
40 LET T=T
55 LET F=32
56 LET V=U+F*T
65 IF U<0 THEN LET S=((U+V)*T)/2
70 LET H=H-S
80 PRINT " HEIGHT NOW ";H;" FEET"
85 PRINT
90 PRINT "VELOCITY = ";V;" FEET/SECOND"
95 PRINT
100 PRINT "DISTANCE TRAVELLED ";S;" FEET"
107 PRINT "INPUT F +/- ACC. TO RETARD FLIGHT"
    
```

```

105 INPUT F
106 CLS
120 PRINT H; " = LAST KNOWN HEIGHT"
130 PRINT
200 LET S= U*T+(-F)*T**2
300 PRINT
400 PRINT S;" FEET = DISTANCE TRAVELLED TOWARDS EARTH"
500 LET V= U+(-F)*T
501 PRINT
555 PRINT V; " FT/SECOND = VELOCITY AFTER ";T;" SECONDS WHEN
    ACC. IS RETARDED BY ";F;" FT/S/S"
556 PRINT
560 LET H=H-S
567 IF S AND V<0 THEN PRINT" VEHICLE IN REVERSE "
568 PRINT
570 PRINT H; " = NEW HEIGHT "
580 GO TO 102
    
```

ETI

BRUNELLE presents THE Commander SERIES Model 4060 Digital ALL THAT THE NAME IMPLIES

The Multimeter you've been waiting for...
at the price you've been hoping for!

\$99.00

- Handheld 7-function, 35 ranges with 200 uA AC and DC. Hi-low ohms diode check.
- Built-in transistor test function.
- Overload protection. 2 amp fuse protects all meter ranges.
- Safety designed input jacks and test leads, tilt stand for bench use. Easy external battery access.
- Calibration certificate traceable to NRC supplied with meter.
- 1 year parts/labor guarantee.

SEE IT, TEST IT, COMPARE IT!

**BRUNELLE
INSTRUMENTS INC.**

826 Belvedere St., Sherbrooke,
Quebec. J1H 4B8
1-819-569-1335 Telex 05-836266

Mail Orders accepted: Send certified cheque or money order. Quebec residents add 9% P.S.T. add \$3.00 for shipping.



WHY SPEND A FORTUNE ON A DIGITAL CAPACITANCE METER?

The MC100A comes completely assembled and calibrated and at \$89.95 is an outstanding value. The extensive range of 1 pF to 9,999 uF (no external meters required) and true hand held portable size (only 4 3/4" x 2 1/2" x 1 1/2") make the MC100A an extremely practical and easy to use instrument for the hobbyist technician or engineer.


CHECK THESE OTHER FEATURES

- * Basic accuracy 1% (± one count) on pF, nF ranges, 3% (± one count) on uF range.
- * Uses single 9V battery (not included).
- * Decimal points light up when battery is low or when capacitor is overrange.
- * Full 4 digit high efficiency LED display uses special circuitry to save on batteries.
- * Constructed with a tough impact resistant plastic case.

**ONE YEAR PARTS &
LABOUR WARRANTY**



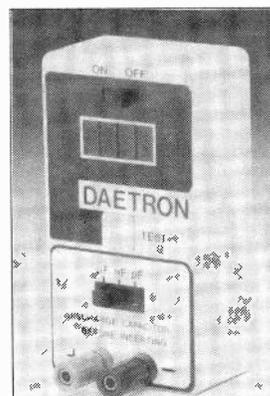DAETRON
935 THE QUEENSWAY
BOX 641
TORONTO ONTARIO M8Z 5Y9
(416) 255-9701
DEALER ENQUIRIES INVITED



***1 pF to 9,999 uF**

\$89.95

PLEASE SEND ME

____ (Quantity) MC100A(s) @ \$89.95

Ontario residents add 7% PST

Postage — \$1.85 (per instrument) (C.O.D. orders add \$1.59)

I ENCLOSE CHEQUE MONEY ORDER BILL MY VISA

VISA CARD NO. _____

EXPIRY DATE _____ SIGNATURE _____

Immediate shipping on orders with money orders, VISA or certified cheque.

Personal cheques please allow 2 to 3 weeks for clearance.

NAME _____

ADDRESS _____

CITY _____

PROV. _____

POSTAL CODE _____

MAIL TO DAETRON 935 THE QUEENSWAY BOX 641 TORONTO ONTARIO M8Z 5Y9

Circle No. 17 on Reader Service Card

Circle No. 14 on Reader Service Card

Coping with Components

Part I

In Part I of this two-part series, Tony Bailey looks at resistors in all their various forms and applications, and show how to identify them when it comes to selecting them.

HOW MANY TIMES have you looked at a strange capacitor bearing a legend such as "102", or a resistor with more identifying bands than normal, and wondered what value it is? Or do you have a collection of resistors and capacitors that you never use because you aren't quite sure what type they are, or whether they will be suitable for the application you have in mind?


In this article we hope to pass on enough information to enable selection and identification of suitable components for the job in hand. Those of you laying hands on a soldering iron for the first time will find this of special interest, and hopefully there is some information also for the seasoned constructor.

During the past decade, the changes in components have not been so much in their type, but the sizes, with such items as IF transformers now obtainable in cans 5mm square, whereas ten years ago, the standard was at least 1 inch square for most people — not that the smaller type weren't around, they were just virtually unobtainable for the average constructor.

A Little Change

The same happened with resistors and capacitors, with very small sizes now common, a result of the need to miniaturize for high density printed circuit work, together with the introduction of different constructions. Also, the power consumption of the active devices we now all use can be measured in microwatts, with commensurate decrease in the power dissipation of the passive devices supporting them. Consider that even on standby, the average tube consumed a good few watts of heater power alone, and a pair of 813s would need a massive 100 watts per pair just to keep the heaters going!

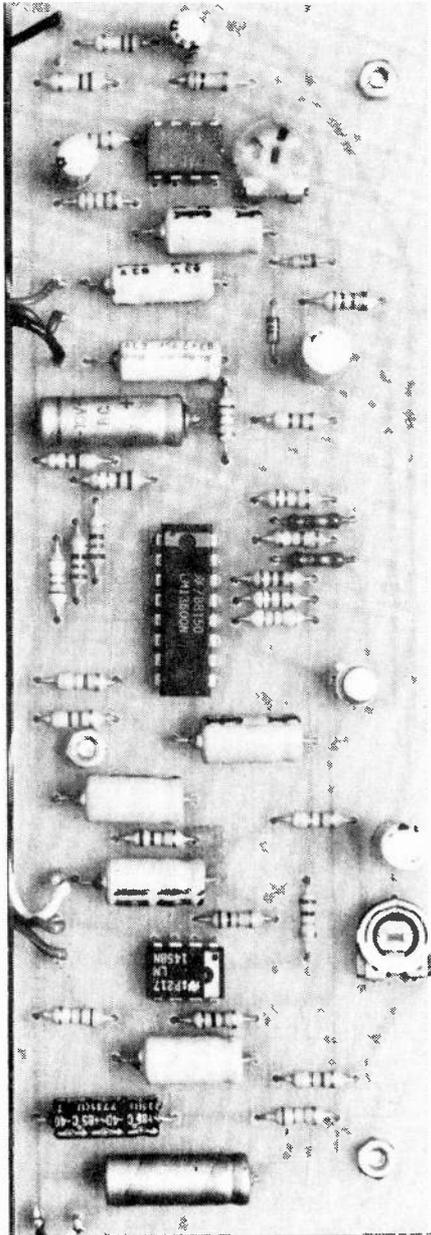Another consequence of miniaturization is that all the components needed for the higher power applications are increasingly difficult to obtain. The average con-



structor of a new linear amplifier has to attend rallies and surplus shops (Second World War surplus is of course also drying up) to find the air spaced capacitors he needs, and high voltage/current capacitors: Tube bases cost an arm and leg, without even mentioning the tubes themselves.

There are of course, many applications still requiring the higher power components. However, most of the constructional projects published today will use either discrete semiconductors, or an array of integrated circuits, with a require-

ment for suitable support components. It is here that the problems start.

The average junkbox may contain a high proportion of what appear to be 'almost' suitable components i.e., "the circuit calls for a 330pF silver mica capacitor, but I have a 330pF polystyrene which will fit into the same space, so lets use that." If value is the only consideration then this may well be suitable, but there is probably another reason why the mica may have been specified. A good article should tell you of any critical needs, but very few actually do, and you are left to your own devices. Similarly, will a wire-wound resistor do instead of the carbon composition specified?

So, with these points in mind let's have a look at the various classes of resistor and capacitor you are likely to come across and how to identify and select them. We will also quickly look at how they are manufactured and constructed.

Resistors


The humble resistor is an essential part of almost all electronic design, but comes in a variety of sizes and compositions, all intended for specific applications, but with a degree of overlap from the practical viewpoint.

One of the major points to remember when selecting any resistor is the power rating. As all resistors convert electrical energy into heat, care needs to be taken to ensure a safe rating within any circuit. For most solid state designs, this power dissipation is very small, and a 0W25 rating will usually suffice.

For higher power work, calculate the maximum power dissipation ($P = I^2 \times R$) and select a resistor rated at least two times this value if ventilation is good — higher if not. Several hot resistors placed next to each other will require a higher rating as radiated heat from resistor to resistor has to be taken into account. Bear in mind that the cooler a resistor can be kept (especially non-wirewound types) the longer its life will be, and adjacent components will not suffer from thermal effects (reduced drift in oscillators for example).


Carbon Composition

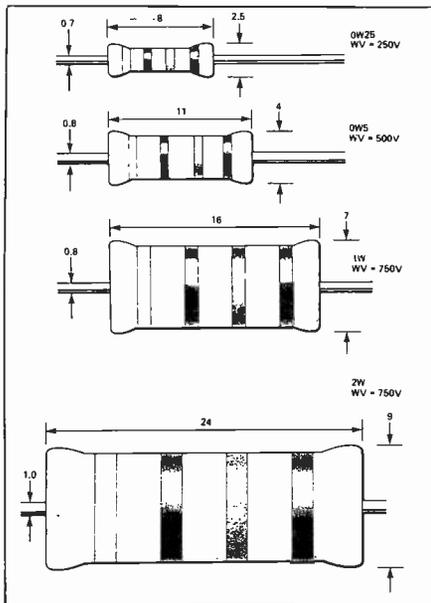These are the cheapest resistor to manufacture, and were once the most common type, although generally carbon film types now see more usage. They are



Carbon Film: The standard "1/4 watt 5% carbon" type, has almost completely replaced older carbon composition resistors. Noise level is typically 1.0uV/V for any value, which is adequate for most purposes. N.B.: All dimensions are in millimeters.

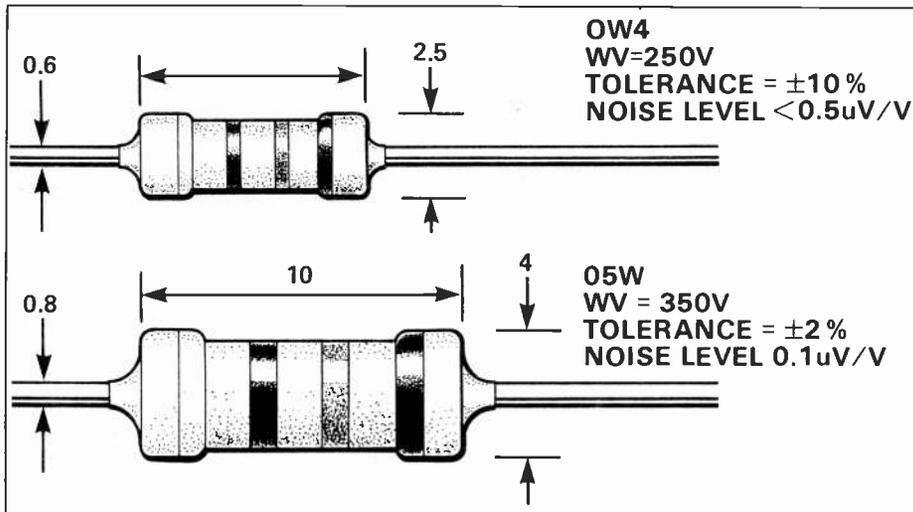reliable, and seldom suffer from failure, except through excessive heating, usually first seen as smoking followed eventually



Metal Film: General purpose high stability types with low temperature coefficient. Five-band colour code gives three significant figures, multiplier and tolerance. Metal Oxide: Used where a low noise figure is required.

by total failure. A major advantage is in RF circuits, as they have very low inductance and capacitance, and are the type to choose when making dummy loads.

At audio, composition resistors generate appreciable noise, due to thermal and current effects between the carbon particles. If low noise is a requirement, use film types instead.


For high voltage work, carbon composition types are better than film types, and the higher the wattage rating, the higher the voltage rating. A typical 0W125 resistor may have a voltage rating of 150V, whereas a 2S type will be around 750 V.

These resistors are manufactured from a compressed and bonded mixture

FOR THE PROFESSIONAL AND HOBBYIST

**VEROBOARD·CIRCUIT BOARDS
ACCESSORIES· WIRE WRAPPING
CASES & BOXES**

WRITE FOR YOUR FREE CATALOGUE TODAY

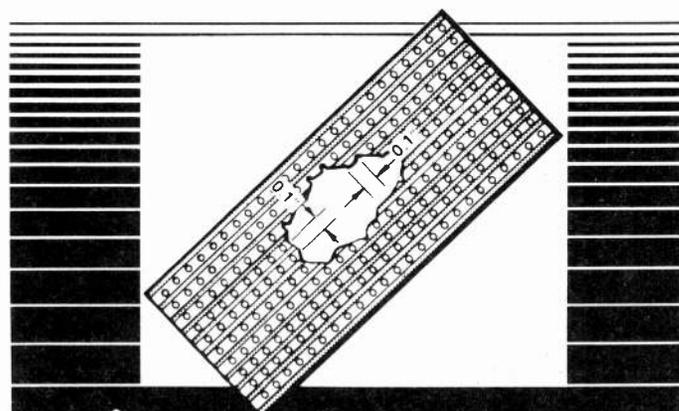

Electronic Packaging Systems Ltd.
P.O. BOX 481, KINGSTON, ONTARIO, K7L 4W5
PHONE (613) 384-1142 TELEX 066-3243

Circle No. 11 on Reader Service Card

PERFECT ELECTRONICS INC.

315 Queen St. W., Toronto, Ontario, M5V 2A4 Tel: (416) 598-2831

COMPUTER

48K 6502 Computer with Function Keyboard and 5 AMP Power Supply assembled and tested \$495
188 Function Intelligent Keyboard and Case \$150
5 AMP Power Supply \$95

PERIPHERALS

16K Ram Card \$55
Controller Card \$55
Z-80 Card \$55
80 Column Card \$80
Graphic Printer Card \$89
128K Ram Card \$225
Eprom Writer Card \$75
Communication Card \$75
Music Card \$99
Wild Card \$59
Clock Card \$99
Speech Card \$40

MONITORS

Amdek 300A \$235
Zenith ZVM-123 \$129
YJE Amber \$159
YJE Green \$150
YJE Amber w/Swivel \$179
YJE Green w/Swivel \$175
Mackintosh \$159

PRINTERS

Star Gemini 10-X \$359
TTX 1014 \$599
Epson Call

MISCELLANEOUS

Quentin \$299
EMP 101
Manual Modem \$85
RF Modulator w/o sound \$15
40-80 Column Switch \$7.50
40-80 Column
Soft Switch \$15
Monitor Swivel Stand \$29
Power Bar \$30
Cooling Fan \$55
Printer Stand \$55
48K 6502 Bare-Board \$29

DEALER ENQUIRIES INVITED.

Mail Order: Send Certified Cheque, Money Order, VISA or MASTER CARD Plus 5% Delivery Charge. Ontario Residents Add 7% P.S.T.

Circle No. 10 on Reader Service Card

Table 1
Standard Colour Code

Band Colour	Figure	Multiplier	Tolerance (±)
Black	0	1	not used
Brown	1	10	—
Red	2	100	2%
Orange	3	1000	—
Yellow	4	10000	—
Green	5	100000	—
Blue	6	1000000	—
Violet	7	10000000	not used
Grey	7	.01	—
White	9	.1	—
Gold	—	—	5%
Silver	—	—	10%

No tolerance band colour = ±20%

Metal film/oxide types have an additional value band to give the three significant figures rather than two, so that a standard 47k resistor would be coded yellow/violet/orange, whereas this type would be coded yellow/violet black/red (i.e., 47,000/4,7000).

An alternative system uses letters to identify the multiplier as follows (recognize it from ETI?):

0.22 ohms = R22	
1.0 ohms = 1R0	
2.2 ohms = 2R2	
22 ohms = 22R	
220 ohms = 220R	F = ±1%
2.2k ohms = 2K2	J = ±5%
220k ohms = 220K	K = ±10%
1.5 ohms = 1M5	M = ±20%

If a letter follows the value, it indicates the tolerances:

of powdered graphite, a filler, and a resin binder — the more carbon, the lower the resistance. A moulded case protects the inner core against environmental effects, although moisture pick-up can be a problem (moisture can be removed by heating). Leads are inserted in each end for connection for the external circuit.

Carbon Film


For standard electronic work, the most common is the 0W25 carbon film variety, and ordering a value of resistor without any further specification would probably result in supply of these.

As the name implies, this type is made by depositing pure carbon onto a ceramic rod used as a former, usually by high temperature decomposition of gaseous hydrocarbons. The thickness of the coating controls the resistance value, and without further treatment, values of up to 1000 ohms are possible.

To achieve higher resistance values, a technique known as spiralling is used. The tube element is rotated, and a very thin track (around ten thousandths of an inch wide) cut around the tube in a helical fashion, using a laser, or cutting wheel. This increases the path length through which the current flows, thus increasing the resistance.

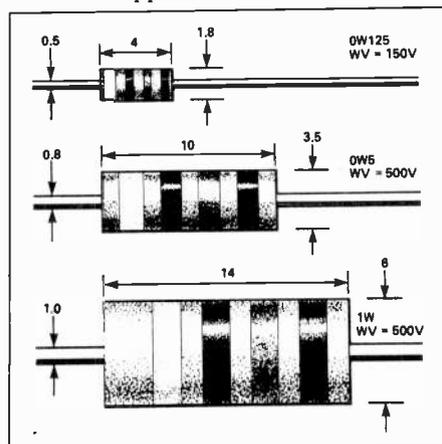Problems arising from this method of construction are that the resistor cannot withstand even small overloads, with the track fusing open circuit (although this ef-

fect can be used to advantage). Also, above about 2MHz, the spiralling introduces capacitive reactance, which may be a problem at higher frequencies. However, the improved stability, low cost and lower resistance change over a long period make these a popular choice in solid state applications.




Carbon Composition: Older type resistor, for general use where temperature coefficient and tolerance are not critical; noise levels generally greater than 2µV/V. Carbon comp resistors are not usually available in values below 10R.

Metal Film/Oxide

For more precise values, these are the normal choice, and are easily available in two and one percent tolerance selections. Precision types come as low as 0.01%, depending on the exact construction, and

of course you pay more for this sort of specification figure.

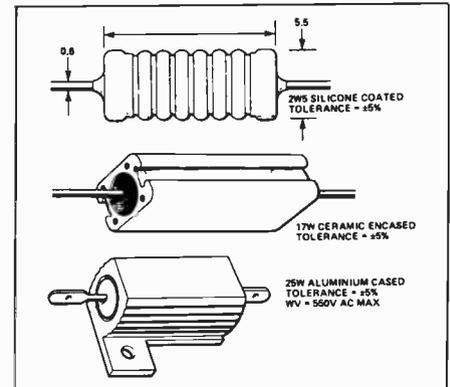Like carbon film, a ceramic (or glass) tube acts as a former, with a thin film of metal, or metal oxide as the resistive element. Spiralling is normal, and the overload factor is better than that of carbon film. They are very reliable, and should be used where dependability and close tolerance are required.



Wirewound: Silicone coated types (top) suitable for general use up to 10W rating. Ceramic encased (middle) types are useful where high insulation resistance is needed (eg., power circuits); also supplied at 4W, 7W and 11W ratings. Aluminum-clad resistors (bottom) will rarely be used by the home constructor!

A number of metal films can be used — nickel-chromium being usual, but cermet and tin oxides will also be met. Cermet resistors are exceptionally stable, generally found as high (megohm ranges) value types, and of value under adverse climatic conditions — more often met as variable preset types than fixed. These thick cermet film types are also used for the dual in-line package types, of value for high density PCB work, for instance as LED display dropping resistors.


Again, capacitive reactance is a problem at higher frequencies. This type of resistor has a slightly different coding system to the composition and carbon film types, with an extra band introduced for the third figure (see Table 1) which makes the value decoding difficult if you haven't used them before.

Wirewound

For applications of high power ratings, low noise or low resistance values, the wirewound resistor, in one of its many forms is the answer. Also, high pulse currents are better handled by these. Tolerance values range from 10% down to .05% for precision work, such as divider networks on test instruments.

Construction is by using a spirally wound high resistance wire element on a ceramic former (sometimes fibreglass on low wattage types). The outer casing is very variable, depending on the application, but typically ceramic, vitreous enamel, plastic, or silicone. Types with

Coping with Components

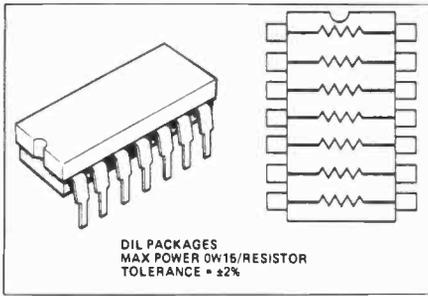


DIL Package: Compact resistor form offering considerable space savings, and very convenient for eg. current limiting LED arrays, 7-segment displays, pull-up/down in logic circuits etc. Also supplied containing 13 commoned resistors.

metal sheathing, which can be screwed to a chassis are available with ratings up to 50 watts.

Power types, often seen as dropping resistors on TV chassis are primarily designed for heat dissipation rather than electrical performance, with wide tolerances. Types used in consumer applications are generally flameproof, for safety reasons, with an outer ceramic coating.

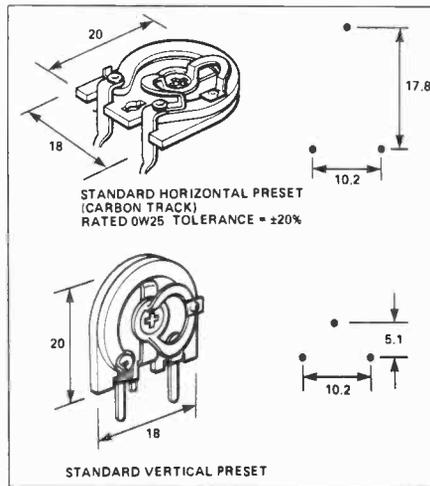
By the nature of the construction, wirewound resistors are highly inductive and should not be used in high frequency



Standard Horizontal Preset (top): miniature types have pin spacings of 10.2 and 5.1mm in the same pattern.

Standard Vertical Preset (bottom): miniature variety pin spacing is 5.1 and 2.54mm, in the same pattern.

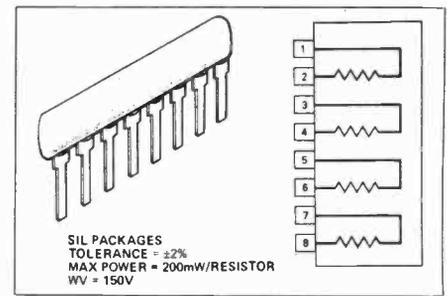circuitry. It is possible to obtain non-inductive types, where two parallel windings are made on the same core, but in opposite directions, to reduce the inductance to around 1/100th of normal. Precision wirewound types are often made by this method, although a typical 0.1%



SIL Package: Also available with 7 or 8 commoned resistors. As with DIL resistors, values are limited and all resistors in the package are the same value.

value will set you back \$4.00 or more each.

Variable Resistors

To vary the voltage in an electrical circuit, a variable resistor is required, otherwise known as a potentiometer or trimmer resistor. All function in a similar manner, having one terminal at each end of a resistive track, and another terminal connected to some form of flap that can be slide up and down the resistive element. One other form of potentiometer is the Rheostat which is strictly a two terminal device of high power capability, but the term is often applied to a three terminal

MEMORY SPECIAL

4116 150nS NEC	\$1.99
4864 1x64K Hitachi 150NS	\$7.75
4164 C-3 150NS NEC	\$8.99
2716 2Kx8 Hitachi, NEC	\$4.99
2732 4Kx8 HITACHI, NEC	\$8.25
2764 8Kx8 Mitsubishi	\$11.75
6532	\$7.99
2532	\$7.65
2114 200nS (Hitachi)	\$2.25
2128-2, 2116, 4016	\$8.25

4164 1x64K OKI 200NS	\$ 8.25
6116 150 NS Hitachi	\$ 8.75

Call for quantity price
OEM Enquiries Invited.


GOLD Switching Power Supply \$95.00

(+5V, 5 AMP, +12V, 2.5 AMPS, -5, ½ AMP, -12V - ½ AMP). Heavy duty.
HYDRO APPROVED. Run 2 drives and lots of peripherals. Circuit diagram included. 90 Days Warranty.



Japanese Parts Specialists PARTS 100% GUARANTEED

CPU	Peripherals		
Z80	UPD 7220D	\$ 5.99	\$59.95
Z80A NEC	8741 NEC	\$ 6.75	\$39.95
6502A 2MHz	8251 NEC	6.99	\$12.00
6502	8253 NEC	\$ 6.50	\$12.00
6845 CRT Controller (Hitachi)	8257 NEC	\$10.99	\$12.00
6522	8086 MIT	\$ 6.99	\$19.95
6850	8085 OKI	\$ 4.99	\$12.00
8088		\$32.95	

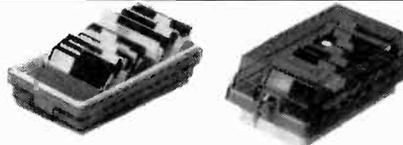

5 1/4 Floppy Disk Case (storage up to 150 diskettes) Lock included	\$39.95
1. YJE High Res non-glare Amber Monitor	\$189.00
2. 52 function numeric keyboard (electronic touch) upper/lower case)	\$119.00

Call for low price
Japanese TTL (Date Code 83, 84)

Store Hours: 9:30 to 6:00
Monday-Saturday 7:00 pm
Thursday and Fridays:

1. 40-80 Column Switch	\$ 5.00
2. Colour R.F. Modulator	\$15.00
3. Joystick (Self-centering) two adjustable controls	\$39.00
a) 128K RAM Card	\$225.00
b) 16K RAM Card	\$ 59.00
c) 80 Column Card	\$ 79.00
d) Disk Controller Card	\$ 59.00
e) Z80 Card	\$ 60.00
f) Communication Card	\$ 79.00
g) 40/80 Col. soft switch	\$ 19.95

Toll Free Orders Only
1-800 268-5619
General Inquiries (416) 298-3280

IBM™ Compatible
5 1/4" Disk Drive Special
(Panasonic Matsushita) \$279.00

Panasonic Drive for Apple™ \$329.00

Teac Drive for Apple™ \$299.00

IBM Compatible
keyboard & case \$CALL


Service Centre and Retail Outlet, 4051 Sheppard Avenue East (at Kennedy), Agincourt, Ontario M1S 1S8 (416) 298-3280

INTERNATIONAL LTD.

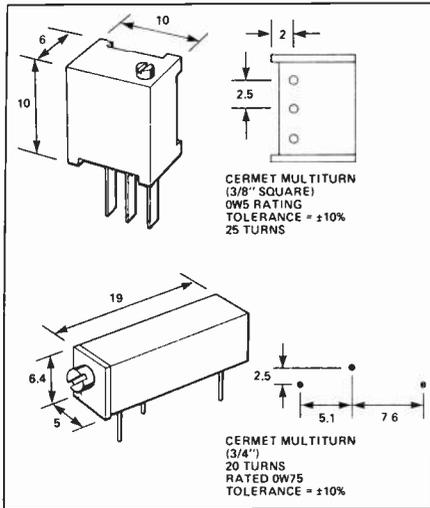(416) 298-3280
Telex - 065-26150

Kitstronic

Mail Orders: Send a certified cheque or money order plus \$3.00 for shipping and handling. For Special Delivery, please add \$1.00 extra. Ontario residents add 7% P.S.T. Visa & Mastercard accepted.



Cermet Multiturn Presets: Essential for precision adjustment. A large range of single-turn cermet trimmers are also available, eg. square, vertical, horizontal and round.


device of similar high power. They are normally used for current limiting purposes.

Like fixed resistors, these come in a variety of shapes and sizes, often with switches attached. Caution should be observed when using switched types that the switch contacts are rated for the job in hand — especially when AC power is involved as the DC rating is very different to the AC. Details of the rating will normally be found on a unit.

Multiple section types are often encountered and used for such applications as ganged stereo balance controls. Many of the types imported from the Far East have additional features such as centre click stops, for the preceding application, or multiple click stops for the type of volume control now popular on hi-fi equipment.


Selection of the variable resistor to suit the application will involve deciding on the type of taper the device has. Taper is a term referring to the track law, or in what manner the resistance changes as the control is rotated. Linear types vary in a linear fashion so that the centre position would be expected to have held the total resistance. Logarithmic law varies slowly at first as the control is rotated from its fully anticlockwise position and then more and more rapidly as the other end is reached, thus obeying a logarithmic law (these are normally used in volume controls).

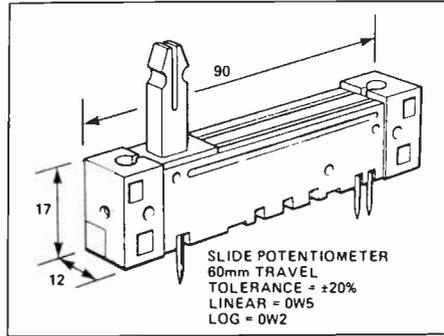Reverse log laws vary in the same manner but in the opposite direction, and a mix of linear and log termed semi-log can be obtained for special purposes. There are other types but they are not frequently met by hobbyists. All of these tapers are formed by varying the mix used to form the resistive element over the element length.



Slide Potentiometers: Favoured for application where controls are being operated continuously.

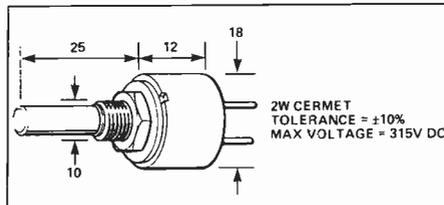The power rating of a potentiometer will vary with its size and construction. Unlike a fixed resistor, you cannot look at one and say what the power rating will be, so inspection of the manufacturers data is advised if in doubt.



Rotary Cermet: The cermet track provides good electrical and temperature stability, and linearity.

Carbon Composition

These were one of the earliest types to be introduced and can still be found. There are two types of construction — moulded and film coated. The former are made by filling a cavity in a moulded base with a carbon composition mix, with the slider formed as a pure carbon brush. The outer case is usually made as an environmental seal, making this type useful under adverse conditions. Track life is long, with low wiper noise.

Conductive Plastic


These are the type more normally met in day-to-day applications, usually in the form of a thick film carbon-resin mix screened onto a base of plastic, phenolic or ceramic material. The wiper is made from a variety of metals, depending on the specification, normally in the form of a spring loaded skeleton.

In use the track eventually wears producing erratic voltage variations or noise in audio circuits. Very short term relief can be obtained by using switch or contact cleaning liquids, but it is usually best to replace the faulty unit without delay. Many of the low cost potentiometers of this type are not sealed against dust contamination which can lead to premature failure under adverse conditions, such as dusty environments.

Wirewound

For higher powers, wirewound types are a natural choice, but their inductive construction limits them to DC and some audio applications. All are made by winding a length of bare resistance wire around a core of insulating material, with the resistance value controlled by varying the type of wire, size of the core, turns spacing and/or wire diameter. A rotating metal wiper pressing on one edge of the former then acts as the resistance control.

The main disadvantage of this type of construction is that the resistive increment as the control is rotated will vary in discrete steps, termed the 'resolution'. This parameter is determined by the diameter and spacing of the wire, and by the contact area of the wiper. In many applications, a fairly high resolution is required as in varicap control voltage applications, and this can only be achieved by using finer wire with closer spacing, which means a more fragile winding. There is also a practical limit to the wiper size.

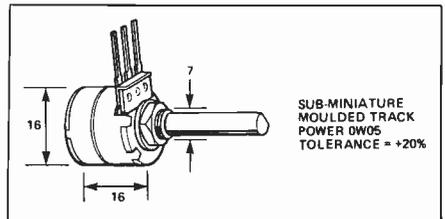

Sub-miniature Carbon: Suitable for panel or PCB mounting where space saving is important.


Precision Types

While single turn precision potentiometers are available (with much longer element lengths and special wipers), it is normally a multi-turn unit which will be encountered for precision applications. The construction and housing are varied, with the elements invariably made from wire, although it is possible to use cermet or conductive plastic in smaller types.

The housings usually incorporate much better shaft arrangements, often with ball bearings, and precious metal wipers. The method of winding the coil gives much higher resolution over single turn types, although there is still a practical limit — for a ten-turn unit, this would be about .01% for a 10kR value. The linearity of the winding is also vastly improved to about = 0.25% at any point on the track.

Trimmer Resistors

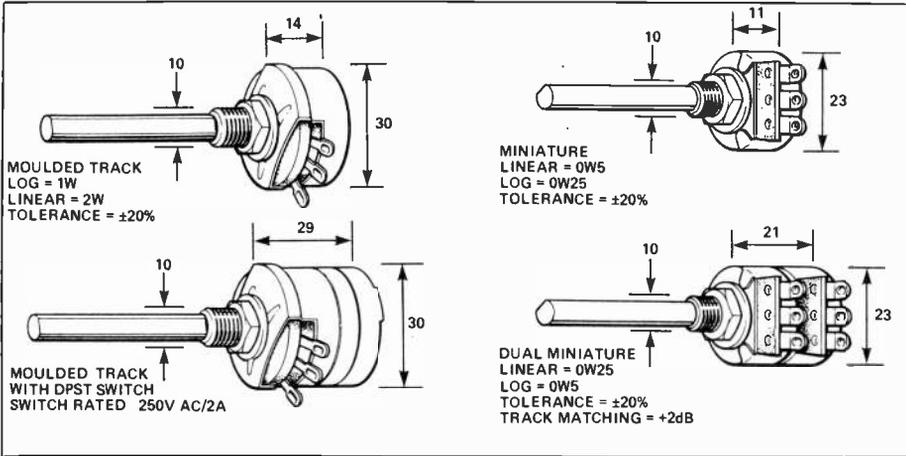Most of the preceding types of variable resistors have their small trimmer equivalents. Nowadays, virtually all trimmer types come as printed circuit board mounting types, with sizes varying down to 6mm diameter. The skeleton preset is



Moulded Carbon Track: The usual potentiometer chosen for panel mounting in non-critical applications. Also available with DPST switch rated for mains voltage (bottom).

Miniature of "Midget": Carbon track potentiometers for general purposes. Dual (aka 'tandem' or 'ganged' pots) have closely matched tracks.

familiar to most readers, and is used in many non-critical applications. For higher reliability, cermet track types should be used — these also have a lower temperature coefficient.

Totally enclosed types are available where environmental conditions are hazardous or where long life is required.

Multi-turn trimmers normally come

in a long rectangular case, with a screwdriver adjustment at one end, and a slipping clutch arrangement to prevent damage to the unit. If you want to panel mount these types, it is possible to obtain special holders with a panel mounting bush. The actual sliding wiper is usually carried on a screw or wormgear arrangement. Note that all these types have a

limited dissipation, and are not designed for continual adjustment — use a proper variable type if you continually need to adjust the value or the operational life will be poor.

Next month, an investigation into capacitors.


ETI

Announcing

PRINTOUT
Canada's Microcomputing Newsletter

See page 66

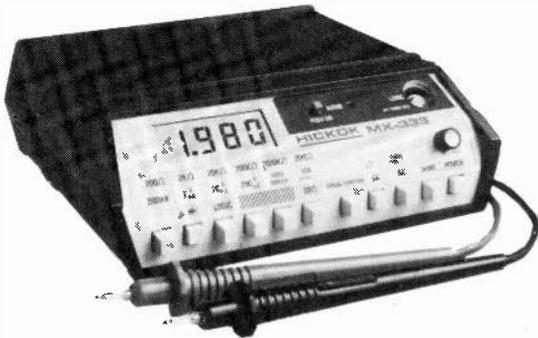HICKOK MX SERIES DMM's World's Fastest Troubleshooters



MX333 \$370.00
MX331 \$258.00

Compact size, unique shape and easy-to-read-from-almost-any-angle sloped display facilitates use as a hand held, bench top or belt mounted instrument.

VARI-PITCH, audible signal on MX333 provides instant indication of the resistance, voltage or current measured for quick and easy troubleshooting. The audible response is instantaneous and proportional to the reading.

- 0.1% Basic Accuracy
- LCD Display In Unique Wide View Case
- Uses Single 9V Battery
- Compact Size, Rugged Construction
- Superior Overload Protection
- Exclusive VARI-PITCH Audible Output (MX333)
- Fast LOGI-TRAK Logic Function (MX333)
- 20Ω Range (MX333)

LOGI-TRAK function on MX333 combines the features of a high performance logic probe and voltmeter in one convenient function. Use any 10:1 high frequency scope probe to measure all logic signals and DC voltages from 10mV to 20V. Audible tone output identifies logic Hi's, Lo's, pulses as narrow as 5 nsec as well as marginal and faulty logic states and pulse trains.

Duty and FST included. Charge (VISA) accepted. Ont. res. add 7% sales tax. Shipping Extra

ROGERS electronic instruments Ltd.

P O Box 310, 595 Mackenzie Avenue Units 1 & 2
Ajax, Ontario L1S 3C5. Tel (416) 683-4211

CONDENSED SPECIFICATIONS: MX331 and MX333

DC VOLTS (5 RANGES): 200mV to 1000V full scale. RESOLUTION: 0.1mV, ACCURACY: ±0.1% + 1 digit. INPUT IMPEDANCE: 10MΩ, OVERLOAD PROTECTION: 1000V DC or peak AC + up to 6kV transients all ranges.

AC VOLTS (5 RANGES): 200mV to 1000V full scale. RESOLUTION: 0.1mV, ACCURACY: ±1% + 2 digits, 45 Hz to 1kHz, ±5% + 5 digits to 5 kHz, INPUT IMPEDANCE: 10mΩ, OVERLOAD PROTECTION: 1000V DC/750 RMS.

RESISTANCE (7 RANGES): 20Ω to 20MΩ full scale except no 20Ω range on MX331, RESOLUTION: 0.01Ω on MX333, 0.1Ω on MX331, ACCURACY: 0.1% + 1 digit except 0.2% on 200Ω, 1% on 20MΩ, and 3% on 20Ω ranges. OVERLOAD PROTECTION: 500V DC on RMS all ranges plus 2A fuse on 20Ω range. TEST VOLTAGE: Low power, 0.25V max of full scale.

DIODE TEST (1 RANGE): Measures forward voltage drop across diode and transistor junctions at 2mA nominal current.

AC/DC CURRENT (5 RANGES): 2mA to 10A full scale. RESOLUTION: 1μA, ACCURACY: ±1.2% + 1 digit DC, ±2.5% + 1 digit AC, OVERLOAD PROTECTION: 250V @ 2A all ranges except 10A, max 15A on 10A range.

VARI-PITCH (MX333 ONLY): Variable pitch proportionate to reading, off at open circuit. Increasing frequency as resistance approaches "0" on ohms function. Increasing frequency as input increases on volts and current functions. RESPONSE: Instantaneous (less than 100 msec.)

LOGI-TRAK (MX333 ONLY): 0-20V range using Hickok SP-7 (not incl.) or other 10:1 scope probe. HI/LO INDICATION: High or low audible tone, PULSE INDICATION: Audible "chirp" plus lighted colon on display. MIN PULSE WIDTH: 5 nsec typical. MAX FREQUENCY: 80 MHz, ACCURACY: ±0.25% + 1 digit + probe accuracy. INPUT IMPEDANCE: 10MΩ, INPUT PROTECTION: 300V DC or RMS.

GENERAL: Dimensions: 2.2x6, 7x6 in. (5.6x17x15.2 cm); Weight: 22 oz. (7kg); Power: 9V battery (incl.) or Hickok AC adapter; Battery Life: 200 Hrs. typical. Temperature 0-50°C operating, -35 to +60°C storage. INCLUDES: Deluxe safety test leads, battery, manual and belt clip.

ACCESSORIES

- SP-7 10:1 Divider Probe for Logi-Trak Input ... **\$70.00**
- TP-20 (C or F) Temperature Probe ... **\$96.00**
- VP-14 RF Probe (0.25V to 40V RMS) ... **\$81.25**
- VP-40 40KV DC Probe (0 to 40KVDC) ... **\$88.25**
- CC-4 Deluxe Vinyl Carrying Case ... **\$27.75**
- RC-3 AC Adapter ... **\$17.75**

BE SURE OF YOUR ISSUE EACH MONTH. SUBSCRIBE TODAY.



BOOKS, BACK ISSUES, SPECIAL PUBLICATIONS, BINDERS — SEE OVER

Book of the Month


Master Handbook of 1001 more practical Circuits

List Price \$23.95

Here are transistors and IC circuits for just about any application you might have. An ideal source book for the engineer, technician or hobbyist. Circuits are classified according to function, and all sections appear in alphabetical order.

Available from: Moorshead Publications 25 Overlea Blvd. Suite 601, Toronto, Ontario M4H 1B1 (416) 423-3262

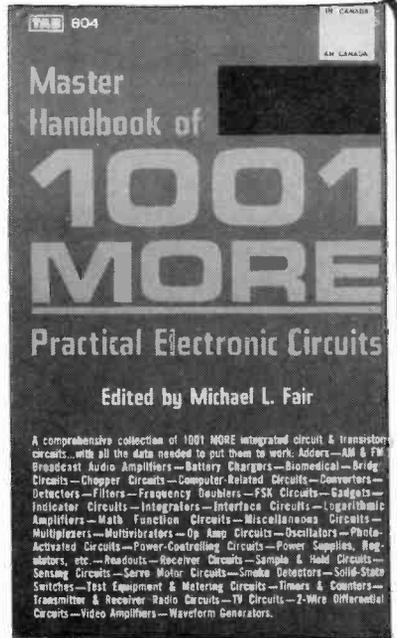See order form in this issue. All prices include shipping. No sales tax applies.



Moorshead Publications

Suite 601, 25 Overlea Blvd., Toronto, Ontario M4H 1B1.

ORDER Please fill out form overleaf
 SUBSCRIPTIONS: NEW SUBSCRIPTION? Or... RENEWAL? Please check one.
 Electronics Today
 One year subscription (12 issues) \$19.95 Two year subscription (24 issues) \$34.95.
 Computing Now!
 One year subscription (12 issues) \$22.95 Two year subscription (24 issues) \$37.95.
 Postage and handling in Canada is included, for U.S. please add \$3 per year other countries add \$5 per year

NAME _____
 ADDRESS _____
 TOWN/CITY _____ PROVINCE/STATE _____
 CODE _____ DATE _____
 Signature _____
 Expiry Date _____


Cheque enclosed. DO NOT send cash
 Bill Mastercard A/C No. _____
 Bill Visa A/C No. _____
 Bill American Express A/C No. _____

PLEASE PRINT CLEARLY

PLEASE ALLOW 6-8 WEEKS FOR YOUR FIRST MAGAZINE TO ARRIVE.


SPECIAL SALE

RX 6600
For \$479.00

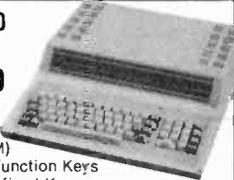

- 64K Ram
- Z80 (CP/M)
- Special Function Keys
- User's Defined Keys
- Apple II + compatible

DISK DRIVE
For \$239.00

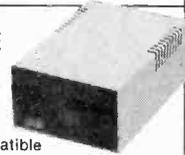

- Apple II Compatible Shugart 390L
- Slim Line Teac \$249.00
- IBM Slim Line Double Side DD \$249.00

CARDS & PERIPHERALS

- Z80 \$ 49.00
- 16K Ram \$ 55.00
- Disk Controller \$ 45.00
- 80 Column \$ 69.00
- Light Pen \$199.00
- Joy Stick \$ 38.00
- 5 Amps Power Supply \$ 79.00

PRINTERS

- Mannesmannally Sprit 80 \$475.00
- TTX Daisy Wheel \$575.00

IBM MAIN BOARD
For \$479.00



- IBM Compatible bare Board \$ 39.00
- Mega Board (Bare) \$ 59.00
- IBM Compl. Case \$ 69.00
- IBM Compl. Power Supply 10 amps 85 watts \$119.00
- IBM Compl. Drive DSDD \$249.00

IBM PC COMPATIBLE KEYBOARD



Enhance your IBM PC* Compatible Computer System with K150 Keyboard.

Use Cherry TS-M0001 switch with life time 20 million operations.

*IBM is Trade Mark of International Business
 *Apple is a registered Trade Mark of Machines Apple Canada inc.
\$179.00

ELECTRONIC CONTROL SYSTEMS

1890 Meyerside Drive, Mississauga, Ontario L5T 1B4
 (416) 673-1302 Hours — Mon. to Fri. 10-7, Sat. 10-2

Circle No. 21 on Reader Service Card

Low-Cost Dwell Meter



You can do your own vehicle tune-ups at home and save the cost and inconvenience of sending it to the garage. A dwell meter can be bought 'over the counter', but you save even more money and increase your personal satisfaction by building your own.


THE FACT THAT you've started to read this article means you probably know quite well what *dwell* is, and the advantages of owning a dwell meter, rather than letting your regular mechanic do the adjustment periodically. (If not, please see the section explaining dwell in automotive ignition systems, because that is where the automotive content of this article is dealt with).

You are possibly also aware that one can readily buy a tacho/dwell meter in local automotive or electronic shops for around \$25 to \$30, which is marginally more than the cost of this project, box and large meter included. So why describe a project that merely reads dwell?

The reasons are threefold: First, if you have ever dissected one of the commercial units, you may be aghast to note the lack of any transistors — often they rely on diodes alone, and a few quarter-watt resistors on a small board. The circuit, though ingenious, is rather simple and does not inspire this author to praise the accuracy or long-term stability.

This project, once calibrated carefully (emphasis on this, as there are pitfalls, outlined later), will be as good as the components you use, which is comparatively very good. In addition, if you have built the thing yourself, it is easy to repair should anything go wrong, from a blown transistor to a crushed meter, and there is a good chance of that if you throw it around like other car tools.

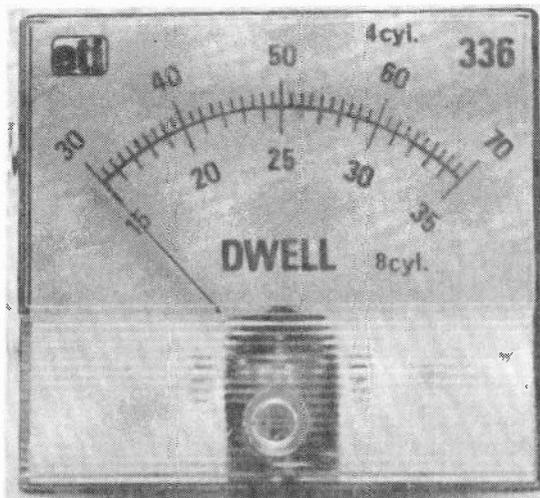Secondly, this project can be quite cheap. The major expense is the meter, so if you wish to build it as an addition to a multimeter and house it in something cheap, or not at all, it becomes very economical. None of the components is critical, except those resistors specified as high-stability types (readily available these days), so it can be a junk-box job if you need.



All you require in addition, is a microamp-to-degrees conversion scale (see later) and you're away.

A second advantage occurred to me as I wandered from car to car testing the prototype. The board is sufficiently cheap that you could leave one connected permanently to the car (it does not effect the running) and, if you are into stacks of dials on your dash, have another one!

Finally, many cars have tachometers of the electronic genre already, and offer more accurate rpm indication than the cheap commercial tacho/dwell units anyway. If you have such a car, there is no incentive to have a second tachometer function which clutters up the scales etc.

Construction

Construction of the Dwell Meter is very straightforward. The first step, if you are going to mount it in a case, is to cut the meter mounting holes. Once you are satisfied that the case is prepared, check the printed circuit board to ensure that the holes on it are of a suitable size. If you intend to mount the board on the rear of the meter itself, as I intended, ensure that the meter connection holes are large enough to fit the meter posts.

Once prepared, mount the components on the PC board, taking care to orientate the IC and other semiconductors correctly. Also check that the electrolytic and tantalum capacitors are the correct way around. Reversing C4 could produce devious and subtle problems! While attaching the components, tin the copper areas around the meter mount holes so that the meter post nuts make good con-

tact on to the board. If you do not do this, the lacquer put on the PC board to stop corrosion could insulate the meter posts completely.

Connect lengths of hookup wire to the battery and points connections. These will be led out of a hole in the case, and alligator or other suitable clips attached to them for connection to the car electricals.

Next fit the meter in the case, then fit the PC board to the meter, leaving the

PARTS LIST

Resistors (All 1/4 W, 5% unless noted)

R1	68R
R2,R3	4k7
R4	180R
R5	10k
R6	1k selected, see text
R7,R8,R9	10k (1% or 2%)
RV1	5k (min. trimpot)

Capacitors

C1,C2	10u/25 V tantalum
C3	2n2
C4	10u/10 V electro

Semiconductors


D1	1N4001, 1N4002 etc.
D2	1N914, 1N4148 etc.
IC1	7805 or 78L05 etc.
Q1	2N3904 or equiv.

Miscellaneous

M1	100uA panel meter, eg., Minipa MU-65, University TD86
----	---

PC board; case to suit; three alligator clips; hookup wire; meter scale to requirements, etc.

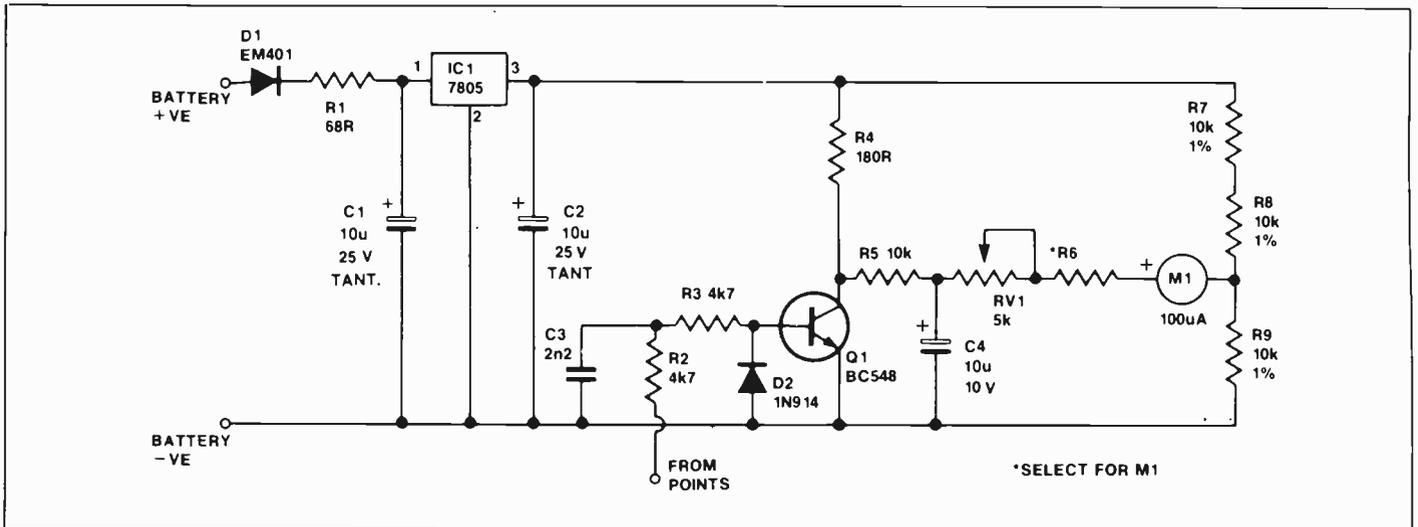* R6 selected so that R6 + meter resistance equals a little under 3k



The dwell meter schematic diagram

HOW IT WORKS

The dwell meter is simply a 'duty cycle' meter with a zero offset and suitable scale markings on the meter face. It measures the closed-to-open ratio of the vehicle points.

Referring to the circuit diagram, D1 and R1, in conjunction with IC1, provide a reverse polarity protected +5 volt supply from the car battery. Capacitors C1 and C2 remove interfering pulses and ensure that IC1 remains stable.

The square wave voltage created by the 'points' opening and closing is filtered to remove the inductive 'spikes' by R2, R3 and C3. Diode D2 protects Q1 from negative voltages which may appear at the input. The square wave is then inverted and set to a fixed amplitude by Q1, which alternately turns hard

on (saturates) and cuts off as the points open and close respectively.

The average voltage appearing on the collector of Q1 is thus proportional to the time the points spend closed, ranging from almost zero for open points to +5 volts when the points are closed. Resistor R5 and capacitor C4 filter this square wave to reveal a relatively steady level. Meter M1 and surrounding components are set to give a minimum scale reading of 33% and a FSD reading of about 78%. This corresponds to a range of 30-70 for four cylinder engines; 20-47 for six cylinders; 15-35 for eight; 24-56 for five; 10-23 for twelve, etc. It is simple to calculate the duty cycle given the formula:

$$\% \text{ duty cycle} = (\text{degrees of dwell}) \times (\text{no. of cylinders}) \times (100/360).$$

Resistor R7 is selected to allow for the internal resistance of the meter. The meter type used in the prototype had a resistance of about 1,800 ohms. The sum of meter resistance and R7 should equal a little under 3,000 ohms. The trimpot, RV1, is set to calibrate the meter full-scale deflection (FSD). Meter zero is held correct by the resistors R7, R8 and R9 which provide an 'offset' voltage.

Without the points connected, the meter needle goes to full scale as the positive terminal is returned to +5 via R4, R5, RV1 and R6, while the negative terminal is at a lower voltage via the R7-8-9 voltage divider. This will not damage the meter.

trimpot accessible. Final assembly should be left until the calibration has been completed.

Calibration

A known calibrating signal will be required to set up the meter. It is not advisable to use a sine wave source (such as from a low voltage power transformer) as this can introduce some error. A square waveform is desirable. This must be of known duty cycle. If you have a signal generator which delivers a known duty cycle square wave, typically 50%, set it to deliver 10 to 30 volts peak-to-peak output, and adjust the trimpot for the correct reading.

The calibrating signal must have a duty cycle of between 40% and 78%. The higher the better, for accuracy.

If you do not have access to a suitable source, proceed as follows. You will need a sine wave of between 30 and 50 volts peak. If you have a transformer delivering nominally between 7 and 20 volts RMS, it will do nicely. Connect the transformer to put the full AC voltage between the 'batt-' terminal and the 'points' input. Adjust the trimpot for a reading of 50% duty


cycle, or 45° dwell on the four-cylinder range. If an oscilloscope is available, it may be used to check the duty cycle at the collector of Q1, and the trimpot used to set the meter to agree with the measurement taken by the oscilloscope. The frequency of the input is not important, of course, provided it is less than a few hundred Hertz.

Using It

Use of the dwell meter, if you have never used one before, is elementary. Simply place the meter in a convenient location near the engine bay. Note that the typical panel meter changes its calibration when it is moved from the horizontal to the vertical, so it should be used in the position in which it was calibrated initially.

Connect the 'batt+' lead to the car battery positive terminal, and the 'batt-' lead to the battery negative connection. Connect the points lead to the junction of the ignition coil and the points in the distributor. When the car is running the meter reads dwell. Adjustments should be made according to the manual for the particular car, but in an emergency, all cars are likely to have dwell specifications

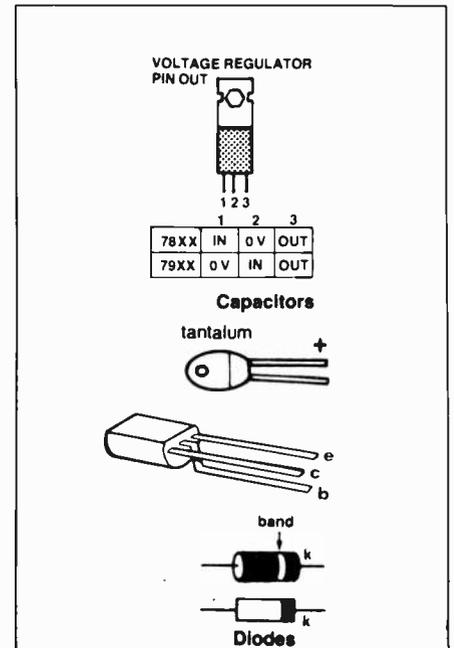which lie roughly at the half-scale point on the meter.




Pin designations for IC1, capacitors, and diodes.

OSCILLOSCOPES!

The Best Buys Available

Model 65810
100 MHz Bench/Portable Scope

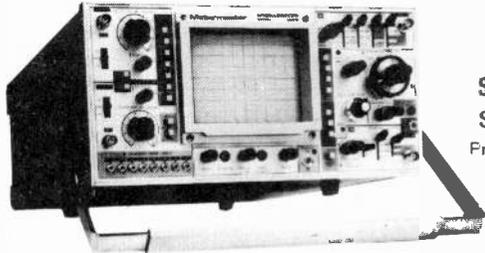

NOW
\$2595.00!
~~\$2695.00~~


Probes & FST
included

A HYBRID COMBINING ANALOG AND
LOGIC FUNCTIONS

VERSATILITY +

- Will Display 4 Analog Traces (independently adjustable) or 8 Logic Channels, or 3 Analog and 8 Logic
- 2ns/Div. Sweep Speed
- 16 kV CRT Potential for A Bright Clear Display
- Scale Illumination
- Delayed Triggered Sweep

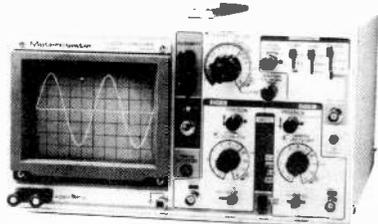Model 65601
Dual Trace Bench/Portable Scope




\$795.00
Probes & FST
included

Featuring at no extra cost 'The Component Tester'

- 20 MHz (-3dB) Bandwidth
- Trace Rotator
- 6" CRT Display
- 5 mV Vertical Sensitivity
- Fully Automatic Triggering
- HF Rejection

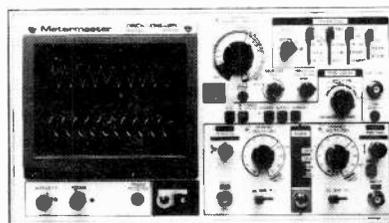Model 65635
Dual Trace Bench/Portable Scope



\$995.00
Probes & FST
included

- 35 MHz (-3dB) Bandwidth
- Delayed Sweep (selectable)
- Single Sweep (selectable)
- 6" CRT Display
- 1 mV Optimal Sensitivity
- X-Y or X-Y-Z Operation
- 120V AC Line Operation
- x5 Sweep Magnifier

MULTIMETERS!

Go for Quality ... Go for The Best Value

REDUCED PRICES... INCREASES YOUR VALUE

Models 78020, 78021, 78022

- AUTO ZERO
- AUTO POLARITY
- 3½ DIGIT LCD
- FULL OVERLOAD PROTECTION ON ALL RANGES
- RECESSED - SAFETY DESIGNED INPUT TERMINALS

- Supplied with:
- 28 Page Operating and Maintenance Manual
 - Calibration Certificate Traceable to NRC
 - Schematic with complete Parts Listing
 - Safety Test Leads
 - One-year Warranty

"Students 10% discount with Student Card!"

Metermaster



\$139.00*

\$99.00*

\$89.00*

- ♦ ±0.1% DC
- ♦ 2000 hrs Bat. life

- ♦ ±0.25% DC
- ♦ 10 Amps AC+DC
- ♦ 200 hrs Bat. life

- ♦ ±0.25% DC
- ♦ 200 hrs Bat. life

* FST Included



5% Discount for Cash,
Certified Cheque, or Money Order
DEALER INQUIRIES INVITED

All prices F.O.B.
Downsview, Ontario
subject to change with-
out notice. P.S.T. extra
where applicable.

Head Office: 214 Dolomite Drive, Downsview, Ontario M3J 2P8

TORONTO (416) 661-3190 MONTREAL (514) 337-0425 EDMONTON (403) 432-7746 OTTAWA (613) 238-7007

Circle No. 26 on Reader Service Card


Dwell In Automotive Ignition Systems

The distributor in the standard type of car has two functions. First, it 'distributes' the spark energy from the ignition coil to each spark plug in turn by means of the rotor and cap of the assembly. This is the most obvious job of the distributor, and the one from which it gets its name. But it is not the most critical, or the one requiring the most attention and adjustment.



It also contains a mechanism for opening and closing the points, which interrupt the ignition-coil primary current and generates the spark itself.

These points are subject to considerable wear, and as they effect both the spark strength and its timing, they are perhaps one of the weakest links in the ignition system.

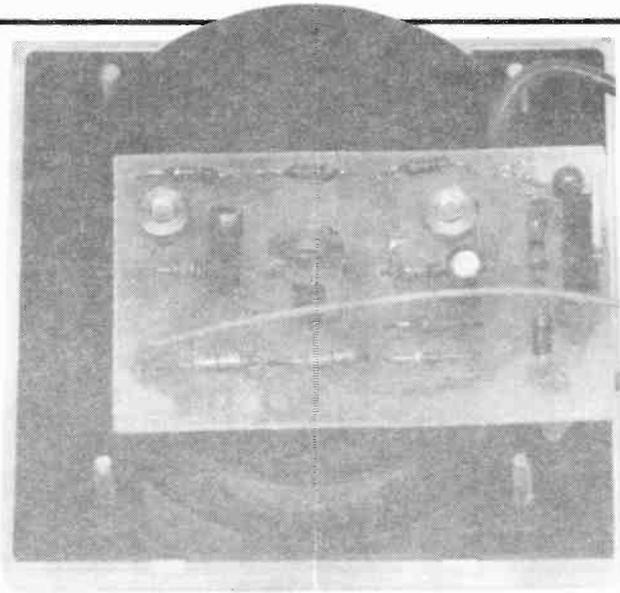The lower assembly of the distributor must open and close the points *once* for each cylinder for each *two* revolutions of the main engine shaft. Each time it is responsible for ensuring that the coil has



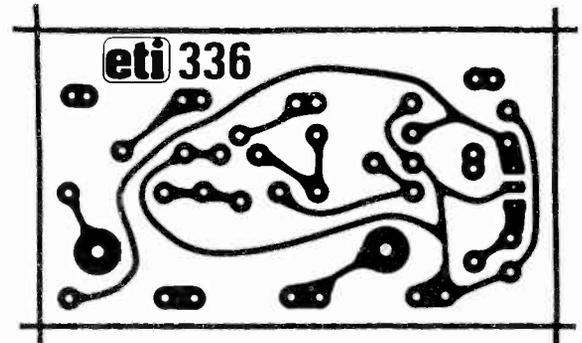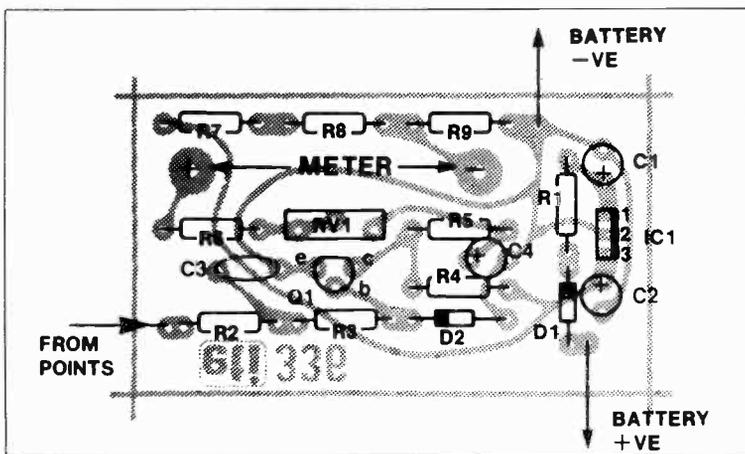Rear view. The board mounts directly on the terminals of a University TD-86 meter. On other types, use heavy-gauge tinned copper wire to secure the board to the meter terminals.



PCB Overlay.

enough time to build up primary current, and that the opening occurred at the correct moment, accounting for engine RPM and possibly also the degree of vacuum fed to it down a small pipe from the inlet side of the engine carburetor.

The two functions which must be adjusted are *dwell* and *timing*. These are analogous to the duty cycle and phase of the square wave (current) generated by the regular opening of the points. Dwell actually means the amount of time, per revolution of the distributor shaft, which the points spend closed.

Timing means the relative phase, referred to the moment when the piston is at the position of maximum compression (top dead centre of 'TDC') of the moment of delivery of the spark energy. The latter can be set statically by aligning marks at various positions, and the former by judicious use of feeler gauges on the points, but neither method is as accurate as the electronic methods.

A stroboscope is used for the timing adjustment, and a duty-cycle meter, called a dwell meter, with special scales, is used for the dwell measurement.

Dwell is specified, not by the kind of figure that an electrical engineer would expect — namely a % duty cycle or a number of electrical degrees — but by the actual number of mechanical degrees traversed by the distributor shaft while the points are closed. Thus, although the actual duty cycle may be similar in all engines, irrelevant of number of cylinders, the degrees of dwell specified appears to change with the number of cylinders. This is because the distributor must deliver one spark for each cylinder each 360 degrees of revolution.


A four-cylinder car has 90 degrees (360/4) of a revolution, so a specified figure of 50 degrees of dwell means 50/90 or 56% duty cycle. A 12-cylinder car has only 30 degrees per cylinder, so 17 degrees of dwell means about the same duty cycle.

Clearly, it is possible to convert any quoted dwell figure into duty cycle by knowing the number of cylinders, then a universal scale of duty cycle on a duty cycle meter would suffice. However, it is usual practice to have several scales on the meter face to achieve the same thing.

Also, since doubling the number of cylinders merely means that the scale reads twice the actual mechanical reading, scales for four and six cylinders enable easy use on eight and twelve cylinder cars, merely by halving the read value.

Equations for converting dwell into duty cycle and vice versa are given in the 'How it Works' section, so if you happen to have an engine with an unusual number of cylinders, you may construct a scale for yourself, or convert the manufacturers specified dwell for, say, a five cylinder car into what the meter will read on the scale for a four cylinder car.

ETI

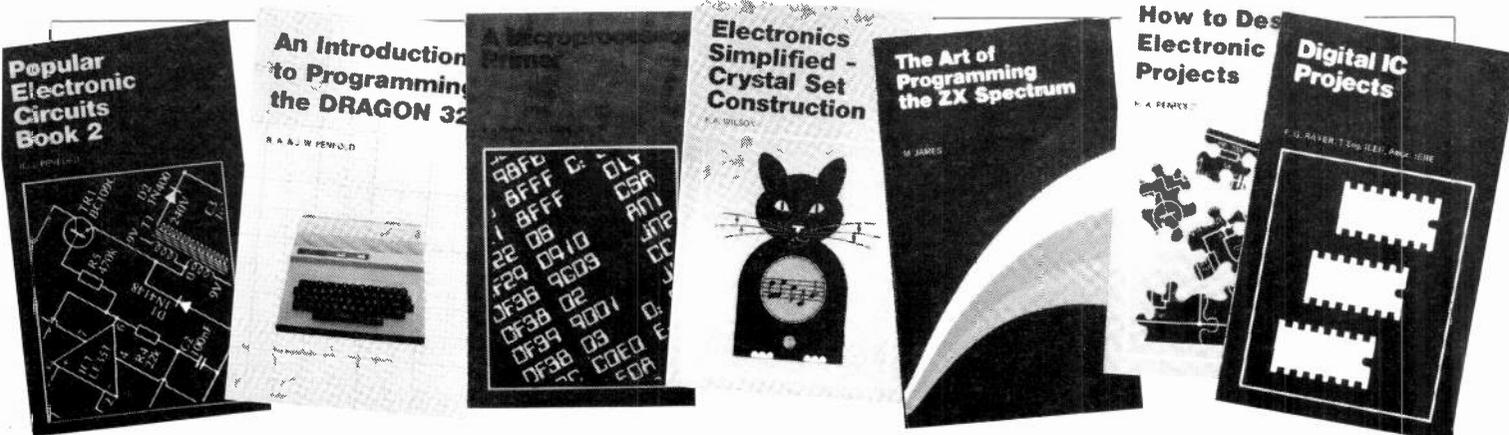

Electronics Today Bookshelf

ELECTRONICS BEGINNERS

PH25S: COMPLETE GUIDE TO READING SCHEMATIC DIAGRAMS, 2nd Edition
J. DOUGLAS-YOUNG \$9.95
 Packed with scores of easy-to-understand diagrams and invaluable troubleshooting tips as well as a circuit finder chart and a new section on logic circuits.

PH25I: BEGINNER'S HANDBOOK OF IC PROJECTS
D. HEISERMAN \$16.95
 Welcome to the world of integrated circuit (IC) electronic projects. This book contains over 100 projects (each including a schematic diagram, parts list, and descriptive notes.)

PH25J: DIGITAL ICs: HOW THEY WORK AND HOW TO USE THEM
A. BARBER \$10.95
 The dozens of illustrations included in this essential reference book will help explain time-saving test procedures, interpreting values, performing voltage measurements, and much more!

PH249: THE BEGINNER'S HANDBOOK OF ELECTRONICS
G. OLSEN & M. MIMS, III \$10.95
 In this basic book, the authors cover the entire spectrum of modern electronics, including the use of such components as integrated circuits and semiconductor devices in record players, radio receivers, airplane guidance systems, and many others.

THE BEGINNER'S HANDBOOK OF ELECTRONICS
AB003 \$10.95
 An excellent textbook for those interested in the fundamentals of Electronics. This book covers all major aspects of power supplies, amplifiers, oscillators, radio, television and more.

ELECTRONIC THEORY

ELEMENTS OF ELECTRONICS - AN ON-GOING SERIES
F.A. WILSON, C.G.I.A., C.Eng.

BP62: BOOK 1. The Simple Electronic Circuit and Components \$8.45

BP63: BOOK 2. Alternating Current Theory \$8.45

BP64: BOOK 3. Semiconductor Technology \$8.45

BP77: BOOK 4. Microprocessing Systems and Circuits \$11.70

BP89: BOOK 5. Communication \$11.70

The aim of this series of books can be stated quite simply — it is to provide an inexpensive introduction to modern electronics so that the reader will start on the right road by thoroughly understanding the fundamental principles involved.

Although written especially for readers with no more than ordinary arithmetical skills, the use of mathematics is not avoided, and all the mathematics required is taught as the reader progresses.

Each book is a complete treatise of a particular branch of the subject and, therefore, can be used on its own with one proviso, that the later books do not duplicate material from their predecessors, thus a working knowledge of the subjects covered by the earlier books is assumed.

BOOK 1. This book contains all the fundamental theory necessary to lead to a full understanding of the simple electronic circuit and its main components.

BOOK 2: This book continues with alternating current theory without which there can be no comprehension of speech, music, radio, television or even the electricity utilities.

BOOK 3: Follows on semiconductor technology, leading up to transistors and integrated circuits.

BOOK 4: A complete description of the internal workings of microprocessor.

BOOK 5: A book covering the whole communication scene.

PH241: DC ELECTRONICS \$16.95
 Covers everything from voltage current, and resistance relationships to more advanced studies of electrical measurements, circuits, resistors, capacitors, and inductors.

PH242: AC ELECTRONICS \$16.95
 Covers AC fundamentals and theory. Includes discussions and experiments in resonance and reactance; RC, RL, and RLC circuits; and how to work with formulas to analyze the operations of AC circuitry.

PH243: ELECTRONICS CIRCUITS \$16.95
 Covers all of the most popular electronic circuits, with emphasis on integrated circuits.

PH244: SEMICONDUCTOR DEVICES \$16.95
 Covers semiconductor fundamentals, diodes, zeners, bipolar transistor operation and characteristics, FETs, thyristors, ICs, and optoelectronics.

PH247: DIGITAL TECHNIQUES \$19.95
 Covers logic circuits, Boolean Algebra, flip-flops, registers, combinational logic circuitry, and digital design.

Tab1531: CONCEPTS OF DIGITAL ELECTRONICS \$21.95
 This book erases the mysteries surrounding digital electronics theory. Understand and use low-cost 7400 series IC's to produce working digital devices including a power supply and a breadboard experimenter.

PROJECTS

BP48: ELECTRONIC PROJECTS FOR BEGINNERS \$7.75
F.C. RAYER, T.Eng.(CEI), Assoc.IERE

Another book written by the very experienced author — Mr. F.C. Rayer — and in it the newcomer to electronics, will find a wide range of easily made projects. Also, there are a considerable number of actual component and wiring layouts, to aid the beginner.

Furthermore, a number of projects have been arranged so that they can be constructed without any need for soldering and, thus, avoid the need for a soldering iron.

Also, many of the later projects can be built along the lines as those in the 'No Soldering' section so this may considerably increase the scope of projects which the newcomer can build and use.

221: 28 TESTED TRANSISTOR PROJECTS
R.TORRENS \$5.00

Mr. Richard Torrens is a well experienced electronics development engineer and has designed, developed, built and tested the many useful and interesting circuits included in this book. The projects themselves can be split down into simpler building blocks, which are shown separated by boxes in the circuits for ease of description, and also to enable any reader who wishes to combine boxes from different projects to realise ideas of his own.

BP49: POPULAR ELECTRONIC PROJECTS \$7.75
R.A. PENFOLD

Includes a collection of the most popular types of circuits and projects which, we feel sure, will provide a number of designs to interest most electronics constructors. The projects selected cover a very wide range and are divided into four basic types. Radio Projects, Audio Projects, Household Projects and Test Equipment.

EXPERIMENTER'S GUIDE TO SOLID STATE ELECTRONIC PROJECTS
AB007 \$9.95

An ideal sourcebook of Solid State circuits and techniques with many practical circuits. Also included are many useful types of experimenter gear.

BP71: ELECTRONIC HOUSEHOLD PROJECTS \$7.20
R. A. PENFOLD

Some of the most useful and popular electronic construction projects are those that can be used in or around the home. The circuits range from such things as '2 Tone Door Buzzer', Intercom, through Smoke or Gas Detectors to Baby and Freezer Alarms.

BP94: ELECTRONIC PROJECTS FOR CARS AND BOATS \$0.10
R.A. PENFOLD \$7.60

Fifteen in all, which use a 12V supply are the basis of this book. Included are projects on Windscreen Wiper Control, Courtesy Light Delay, Battery Monitor, Cassette Power Supply, Lights Timer, Vehicle Immobiliser, Gas and Smoke Alarm, Depth Warning and Shaver Inverter.

BP69: ELECTRONIC GAMES \$7.05
R.A. PENFOLD

In this book Mr. R. A. Penfold has designed and developed a number of interesting electronic game projects using modern integrated circuits. The text is divided into two sections, the first dealing with simple games and the latter dealing with more complex circuits.

BP95: MODEL RAILWAY PROJECTS \$7.60

Electronic projects for model railways are fairly recent and have made possible an amazing degree of realism. The projects covered include controllers, signals and sound effects: striboard layouts are provided for each project.

BP93: ELECTRONIC TIMER PROJECTS \$7.60
F.C. RAYER

Windscreen wiper delay, darkroom timer and metronome projects are included. Some of the more complex circuits are made up from simpler sub-circuits which are dealt with individually.

110 OP-AMP PROJECTS
MARSTON \$12.95

This handbook outlines the characteristics of the op-amp and present 110 highly useful projects — ranging from simple amplifiers to sophisticated instrumentation circuits.

110 IC TIMER PROJECTS
GILDER \$10.95

This sourcebook maps out applications for the 555 timer IC. It covers the operation of the IC itself to aid you in learning how to design your own circuits with the IC. There are application chapters for timer-based instruments, automotive applications, alarm and control circuits, and power supply and converter applications.

BP110: HOW TO GET YOUR ELECTRONIC PROJECTS WORKING
R.A. PENFOLD \$7.60

We have all built circuits from magazines and books only to find that they did not work correctly, or at all, when first switched on. The aim of this book is to help the reader overcome just these problems by indicating how and where to start looking for many of the common faults that can occur when building up projects.

PH250: EXPERIMENTER'S GUIDE TO SOLID STATE ELECTRONICS PROJECTS
A. BARBER \$9.95

This book takes the mystery out of solid state electronics and enables the reader to build such useful devices as series regulated power supplies, light dimmers, solar cell operated radios, hi-fi amplifiers, light indicators for battery operated equipment and much more.

110 THYRISTOR PROJECTS USING SCRs AND TRIACS
MARSTON \$12.95

A grab bag of challenging and useful semiconductor projects for the hobbyist, experimenter, and student. The projects range from simple burglar, fire, and water level alarms to sophisticated power control devices for electric tools and trains. Integrated circuits are incorporated wherever their use reduces project costs.

See order form in this issue.

Electronics Today Bookshelf

110 CMOS DIGITAL IC PROJECTS
MARSTON \$11.25
HB23
 Outlines the operating characteristics of CMOS digital ICs and then presents and discusses 110 CMOS digital IC circuits ranging from inverter gate and logic circuits to electronic alarm circuits. Ideal for amateurs, students and professional engineers.

BP76: POWER SUPPLY PROJECTS \$7.75
R.A. PENFOLD
 Line power supplies are an essential part of many electronics projects. The purpose of this book is to give a number of power supply designs, including simple unregulated types, fixed voltage regulated types, and variable voltage stabilised designs, the latter being primarily intended for use as bench supplies for the electronics workshop. The designs provided are all low voltage types for semiconductor circuits.
 There are other types of power supply and a number of these are dealt with in the final chapter, including a cassette power supply, Ni-Cad battery charger, voltage step up circuit and a simple inverter.

BP84: DIGITAL IC PROJECTS \$7.60
F.G. RAYER, T.Eng.(CEI), Assoc.IERE
 This book contains both simple and more advanced projects and it is hoped that these will be found of help to the reader developing a knowledge of the workings of digital circuits. To help the newcomer to the hobby the author has included a number of board layouts and wiring diagrams. Also, the more ambitious projects can be built and tested section by section and this should help avoid or correct faults that could otherwise be troublesome. An ideal book for both beginner and more advanced enthusiast alike.

BP67: COUNTER DRIVER AND NUMERAL DISPLAY PROJECTS \$7.05
F.G. RAYER, T.Eng.(CEI), Assoc. IERE
 Numerical indicating devices have come very much to the forefront in recent years and will, undoubtedly, find increasing applications in all sorts of equipment. With present day integrated circuits, it is easy to count, divide and display numerically the electrical pulses obtained from a great range of driver circuits.
 In this book many applications and projects using various types of numeral displays, popular counter and driver IC's etc. are considered.

BP73: REMOTE CONTROL PROJECTS \$8.10
OWEN BISHOP
 This book is aimed primarily at the electronics enthusiast who wishes to experiment with remote control. Full explanations have been given so that the reader can fully understand how the circuits work and can more easily see how to modify them for other purposes, depending on personal requirements. Not only are radio control systems considered but also infra-red, visible light and ultrasonic systems as are the use of Logic ICs and Pulse position modulation etc.

BP99: MINI—MATRIX BOARD PROJECTS \$7.60
R.A. PENFOLD
 Twenty useful projects which can all be built on a 24 x 10 hole matrix board with copper strips. Includes Doorbuzzer, Low-voltage Alarm, AM Radio, Signal Generator, Projector Timer, Guitar Headphone Amp, Transistor Checker and more.

BP103: MULTI-CIRCUIT BOARD PROJECTS \$7.60
R.A. PENFOLD
 This book allows the reader to build 21 fairly simple electronic projects, all of which may be constructed on the same printed circuit board. Wherever possible, the same components have been used in each design so that with a relatively small number of components and hence low cost, it is possible to make any one of the projects or by re-using the components and P.C.B. all of the projects.

Tab1431: DIGITAL ELECTRONIC PROJECTS \$20.95
 Build a deluxe code oscillator, a digital game called Climb-the-Mountain, a clock with alarm, a metric measuring wheel, a modular decade counter, even a 14-note music generator. 17 projects in all.

BP107: 30 SOLDERLESS BREADBOARD PROJECTS — BOOK 1 \$8.85
R.A. PENFOLD
 A "Solderless Breadboard" is simply a special board on which electronic circuits can be built and tested. The components used are just plugged in and unplugged as desired. The 30 projects featured in this book have been specially designed to be built on a "Verobloc" breadboard. Wherever possible the components used are common to several projects, hence with only a modest number of reasonably inexpensive components it is possible to build, in turn, every project shown.

BP106: MODERN OP-AMP PROJECTS \$7.60
R.A. PENFOLD
 Features a wide range of constructional projects which make use of op-amps including low-noise, low distortion, ultra-high input impedance, high slew-rate and high output current types.

CIRCUITS

BP80: POPULAR ELECTRONIC CIRCUITS — BOOK 1 \$7.75
R.A. PENFOLD
 Another book by the very popular author, Mr. R.A. Penfold, who has designed and developed a large number of various circuits. These are grouped under the following general headings: Audio Circuits, Radio Circuits, Test Gear Circuits, Music Project Circuits, Household Project Circuits and Miscellaneous Circuits.

BP98: POPULAR ELECTRONIC CIRCUITS, BOOK 2 \$8.85
R.A. PENFOLD
 70 plus circuits based on modern components aimed at those with some experience.

The GIANT HANDBOOK OF ELECTRONIC CIRCUITS
TAB No.1300 \$27.95
 About as twice as thick as the Webster's dictionary, and having many more circuit diagrams, this book is ideal for any experimenter who wants to keep amused for several centuries. If there isn't a circuit for it in here, you should have no difficulty convincing yourself you don't really want to build it.

BP39: 50 (FET) FIELD EFFECT TRANSISTOR PROJECTS \$6.75
F.G. RAYER, T.Eng.(CEI), Assoc.IERE
 Field effect transistors (FETs), find application in a wide variety of circuits. The projects described here include radio frequency amplifiers and converters, test equipment and receiver aids, tuners, receivers, mixers and tone controls, as well as various miscellaneous devices which are useful in the home.
 This book contains something of particular interest for every class of enthusiast — short wave listener, radio amateur, experimenter or audio devotee.

BP87: SIMPLE L.E.D. CIRCUITS \$5.40
R.N. SOAR
 Since it first appeared in 1977, Mr. R.N. Soar's book has proved very popular. The author has developed a further range of circuits and these are included in Book 2. Projects include a Transistor Tester, Various Voltage Regulators, Testers and so on.

BP42: 50 SIMPLE L.E.D. CIRCUITS \$3.05
R.N. SOAR
 The author of this book, Mr R.N. Soar, has compiled 50 interesting and useful circuits and applications, covering many different branches of electronics, using one of the most inexpensive and freely available components — the Light Emitting Diode (LED). A useful book for the library of both beginner and more advanced enthusiast alike.

BP82: ELECTRONIC PROJECTS USING SOLAR CELLS \$7.60
OWEN BISHOP
 The book contains simple circuits, almost all of which operate at low voltage and low currents, making them suitable for being powered by a small array of silicon cells. The projects cover a wide range from a bicycle speedometer to a novelty 'Duck Shoot', a number of power supply circuits are included.

BP37: 50 PROJECTS USING RELAYS, SCR'S & TRIACS \$7.75
F.G. RAYER, T.Eng.(CEI), Assoc.IERE
 Relays, silicon controlled rectifiers (SCR's) and bi-directional triodes (TRIACs) have a wide range of applications in electronics today. This book gives tried and practical working circuits which should present the minimum of difficulty for the enthusiast to construct. In most of the circuits there is a wide latitude in component values and types, allowing easy modification of circuits or ready adaptation of them to individual needs.

BP24: 50 PROJECTS USING IC741 \$3.75
RUDI & UWE REDMER
 This book, originally published in Germany by TOPP, has achieved phenomenal sales on the Continent and Babani decided, in view of the fact that the integrated circuit used in this book is inexpensive to buy, to make this unique book available to the English speaking reader. Translated from the original German with copious notes, data and circuitry, a "must" for everyone whatever their interest in electronics.

BP83: V MOS PROJECTS \$7.70
R.A. PENFOLD
 Although modern bipolar power transistors give excellent results in a wide range of applications, they are not without their drawbacks or limitations. This book will primarily be concerned with V MOS power FETs although power MOSFETs will be dealt with in the chapter on audio circuits. A number of varied and interesting projects are covered under the main headings of: Audio Circuits, Sound Generator Circuits, DC Control Circuits and Signal Control Circuits.

BP44: IC 555 PROJECTS \$7.75
E.A. PARR, B.Sc., C.Eng., M.I.E.E.
 Every so often a device appears that is so useful that one wonders how life went on before without it. The 555 timer is such a device. Included in this book are Basic and General Circuits, Motor Car and Model Railway Circuits, Alarms and Noise Makers as well as a section on the 556, 558 and 559 timers.

BP65: SINGLE IC PROJECTS \$6.05
R.A. PENFOLD
 There is now a vast range of ICs available to the amateur market, the majority of which are not necessarily designed for use in a single application and can offer unlimited possibilities. All the projects contained in this book are simple to construct and are based on a single IC. A few projects employ one or two transistors in addition to an IC but in most cases the IC is the only active device used.

BP97: IC PROJECTS FOR BEGINNERS \$7.60
F.G. RAYER
 Covers power supplies, radio, audio, oscillators, timers and switches. Aimed at the less experienced reader, the components used are popular and inexpensive.

BP88: HOW TO USE OP AMPS \$8.85
E.A. PARR
 A designer's guide covering several op amps, serving as a source book of circuits and a reference book for design calculations. The approach has been made as non-mathematical as possible.

IC ARRAY COOKBOOK
JUNG \$13.75
HB26
 A practical handbook aimed at solving electronic circuit application problems by using IC arrays. An IC array, unlike specific-purpose ICs, is made up of uncommitted IC active devices, such as transistors, resistors, etc. This book covers the basic types of such ICs and illustrates with examples how to design with them. Circuit examples are included, as well as general design information useful in applying arrays.

BP50: IC LM3900 PROJECTS \$5.40
H.KYBETT, B.Sc., C.Eng.
 The purpose of this book is to introduce the LM3900 to the Technician, Experimenter and the Hobbyist. It provides the groundwork for both simple and more advanced uses, and is more than just a collection of simple circuits or projects.
 Simple basic working circuits are used to introduce this IC. The LM3900 can do much more than is shown here, this is just an introduction. Imagination is the only limitation with this useful and versatile device. But first the reader must know the basics and that is what this book is all about.

223: 50 PROJECTS USING IC CA3130 \$5.00
R.A. PENFOLD
 In this book, the author has designed and developed a number of interesting and useful projects which are divided into five general categories: I — Audio Projects II — R.F. Projects III — Test Equipment IV — Household Projects V — Miscellaneous Projects.

224: 50 CMOS IC PROJECTS \$3.75
R.A. PENFOLD
 CMOS IC's are probably the most versatile range of digital devices for use by the amateur enthusiast. They are suitable for an extraordinary wide range of applications and are also some of the most inexpensive and easily available types of IC.
 Mr. R.A. Penfold has designed and developed a number of interesting and useful projects which are divided into four general categories: I — Multivibrators II — Amplifiers and Oscillators III — Trigger Devices IV — Special Devices.

THE ACTIVE FILTER HANDBOOK \$13.95
TAB No.1133
 Whatever your field — computing, communications, audio, electronic music or whatever — you will find this book the ideal reference for active filter design.
 The book introduces filters and their uses. The basic math is discussed so that the reader can tell where all design equations come from. The book also presents many practical circuits including a graphic equalizer, computer tape interface and more.

DIGITAL IC'S — HOW THEY WORK AND HOW TO USE THEM \$10.95
AB004
 An excellent primer on the fundamentals of digital electronics. This book discusses the nature of gates and related concepts and also deals with the problems inherent to practical digital circuits.

MASTER HANDBOOK OF 1001 PRACTICAL CIRCUITS \$19.95
TAB No.800
MASTER HANDBOOK OF 1001 MORE PRACTICAL CIRCUITS \$23.95
TAB No.804
 Here are transistor and IC circuits for just about any application you might have. An ideal source book for the engineer, technician or hobbyist. Circuits are classified according to function, and all sections appear in alphabetical order.

See order form in this issue.

Electronics Today Bookshelf

THE MASTER IC COOKBOOK \$17.95
TAB No.1199
 If you've ever tried to find specs for a so called 'standard' chip, then you'll appreciate this book. C.L. Hallmark has compiled specs and pinout for most types of ICs that you'd ever want to use.

ELECTRONIC DESIGN WITH OFF THE SHELF INTEGRATED CIRCUITS \$12.95
AB016

This practical handbook enables you to take advantage of the vast range of applications made possible by integrated circuits. The book tells how, in step by step fashion, to select components and how to combine them into functional electronic systems. If you want to stop being a "cookbook hobbyist", then this is the book for you.

BP117: PRACTICAL ELECTRONIC BUILDING BLOCKS BOOK 1 \$7.60

Virtually any electronic circuit will be found to consist of a number of distinct stages when analysed. Some circuits inevitably have unusual stages using specialised circuitry, but in most cases circuits are built up from building blocks of standard types.

This book is designed to aid electronics enthusiasts who like to experiment with circuits and produce their own projects rather than simply follow published project designs.

The circuits for a number of useful building blocks are included in this book. Where relevant, details of how to change the parameters of each circuit are given so that they can easily be modified to suit individual requirements.

PH253: ELECTRONIC DESIGN WITH OFF-THE-SHELF INTEGRATED CIRCUITS \$12.95
Z. MEIKEN & P. TACKRAY

A real help for do-it-yourselfers, this handy guide tells professionals and hobbyists alike, how to take components off the shelves, arrange them into circuitry, and make any system perform its desired function.

RADIO AND COMMUNICATIONS

BP79: RADIO CONTROL FOR BEGINNERS \$6.80
F.G. RAYER, T.Eng.(CEI),Assoc.IERE.

The aim of this book is to act as an introduction to Radio Control for beginners to the hobby. The book will commence by dealing with the conditions that are allowable for such things as frequency and power of transmission. This is followed by a "block" explanation of how control-device and transmitter operate and receiver and actuator(s) produce motion in a model.

Details are then given of actual solid state transmitting equipment which the reader can build. Plain and loaded aerials are then discussed and so is the field-strength meter to help with proper setting up.

The radio receiving equipment is then dealt with which includes a simple receiver and also a crystal controlled superhet. The book ends with the electro-mechanical means of obtaining movement of the controls of the model.

BP96: CB PROJECTS \$7.60
R.A. PENFOLD

Projects include speech processor, aerial booster, cordless mike, aerial and harmonic filters, field strength meter, power supply, CB receiver and more.

222: SOLID STATE SHORT WAVE RECEIVERS FOR BEGINNERS \$4.70
R.A. PENFOLD

In this book, R.A. Penfold has designed and developed several modern solid state short wave receiver circuits that will give a fairly high level of performance, despite the fact that they use only relatively few and inexpensive components.

BP91: AN INTRODUCTION TO RADIO DXing \$7.60

This book is divided into two main sections one to amateur band reception, the other to broadcast bands. Advice is given to suitable equipment and techniques. A number of related constructional projects are described.

MOORSHEAD PUBLICATIONS

Return Policy

If, within 10 days of receiving a book from our Book Service, you decide that the title is not suitable or what you expected, you may return it, in marketable condition, for a refund or credit (your choice). We would appreciate a reason for the return but even if this is not given, refunds will be made promptly and cheerfully.

BP105: AERIAL PROJECTS \$7.60
R.A. PENFOLD

The subject of aerials is vast but in this book the author has considered practical designs including active, loop and ferrite aerials, which give good performances and are reasonably simple and inexpensive to build. The complex theory and math of aerial design are avoided.

BP46: RADIO CIRCUITS USING IC's \$5.40
J.B. DANCE, M.Sc.

This book describes integrated circuits and how they can be employed in receivers for the reception of either amplitude or frequency modulated signals. The chapter on amplitude modulated (a.m.) receivers will be of most interest to those who wish to receive distant stations at only moderate audio quality, while the chapter on frequency modulation (f.m.) receivers will appeal to those who desire high fidelity reception.

BP92: ELECTRONICS SIMPLIFIED—CRYSTAL SET CONSTRUCTION \$6.80
F.A. WILSON

Aimed at those who want to get into construction without much theoretical study. Homewound coils are used and all projects are very inexpensive to build.

PH245: ELECTRONIC COMMUNICATIONS \$16.95

Covers amplitude modulation, AM and FM transmitters, pulse modulation, and antennas. Includes discussions of applications.

BP70: TRANSISTOR RADIO FAULT-FINDING CHART \$1.90
CHAS. E. MILLER

Across the top of the chart will be found four rectangles containing brief descriptions of various faults, viz. — sound weak but undistorted, set dead; sound low or distorted and background noises. One then selects the most appropriate of these and following the arrows, carries out the suggested checks in sequence until the fault is cleared.

AUDIO

BP90: AUDIO PROJECTS \$7.60
F.G. RAYER

Covers in detail the construction of a wide range of audio projects. The text has been divided into preamplifiers and mixers, power amplifiers, tone controls and matching and miscellaneous projects.

205: FIRST BOOK OF HI-FI LOUDSPEAKER ENCLOSURES \$3.05
B.B. BABANI

This book gives data for building most types of loudspeaker enclosure. Includes corner reflex, bass reflex, exponential horn, folded horn, tuned port, klipschorn labyrinth, tuned column, loaded port and multi speaker panoramic. Many clear diagrams for every construction showing the dimensions necessary.

BP47: MOBILE DISCOTHEQUE HANDBOOK \$5.40
COLIN CARSON

The vast majority of people who start up "Mobile Discos" know very little about their equipment or even what to buy. Many people have wasted a "small fortune" on poor, unnecessary or badly matched apparatus.

The aim of this book is to give you enough information to enable you to have a better understanding of many aspects of "disco" gear.

HOW TO BUILD A SMALL BUDGET RECORDING STUDIO FROM SCRATCH \$15.95
TAB No.1166

The author, F. Alton Everest, has gotten studios together several times, and presents twelve complete, tested designs for a wide variety of applications. If all you own is a mono cassette recorder, you don't need this book. If you don't want your new four track to wind up sounding like one, though, you shouldn't be without it.

BP51: ELECTRONIC MUSIC AND CREATIVE TAPE RECORDING \$7.75
M.K. BERRY

Electronic music is the new music of the Twentieth Century. It plays a large part in "pop" and "rock" music and, in fact, there is scarcely a group without some sort of synthesiser or other effects generator.

This book sets out to show how electronic music can be made at home with the simplest and most inexpensive of equipment. It then describes how the sounds are generated and how these may be recorded to build up the final composition.

BP74: ELECTRONIC MUSIC PROJECTS \$7.20
R.A. PENFOLD

Although one of the more recent branches of amateur electronics, electronic music has now become extremely popular and there are many projects which fall into this category. The purpose of this book is to provide the constructor with a number of practical circuits for the less complex items of electronic music equipment, including such things as a Fuzz Box, Waa-Waa Pedal, Sustain Unit, Reverberation and Phaser-Units, Tremelo Generator etc.

BP81: ELECTRONIC SYNTHESISER PROJECTS \$6.80
M.K. BERRY

One of the most fascinating and rewarding applications of electronics is in electronic music and there is hardly a group today without some sort of synthesiser or effects generator. Although an electronic synthesiser is quite a complex piece of electronic equipment, it can be broken down into much simpler units which may be built individually and these can then be used or assembled together to make a complete instrument.

ELECTRONIC MUSIC SYNTHESIZERS \$10.95
TAB No.1167

If you're fascinated by the potential of electronics in the field of music, then this is the book for you. Included is data on synthesizers in general as well as particular models. There is also a chapter on the various accessories that are available.

TAB1364: DESIGNING, BUILDING AND TESTING YOUR OWN SPEAKER SYSTEM ... WITH PROJECTS \$13.95

Covers the theory of speaker construction and describes a variety of plans for speaker system projects ranging from simple setups to complex multi-driver systems. Enclosure design is covered in very good detail.

BP68: CHOOSING AND USING YOUR HI-FI \$6.75
MAURICE L. JAY

The main aim of this book is to provide the reader with the fundamental information necessary to enable him to make a satisfactory choice from the extensive range of hi-fi equipment now on the market.

Help is given to the reader in understanding the equipment he is interested in buying and the author also gives his own opinion of the minimum standards and specifications one should look for. The book also offers helpful advice on how to use your hi-fi properly so as to realise its potential. A Glossary of terms is also included.

TEST EQUIPMENT

BP75: ELECTRONIC TEST EQUIPMENT CONSTRUCTION \$6.80
F.G. RAYER, T.Eng. (CEI), Assoc. IERE

This book covers in detail the construction of a wide range of test equipment for both the Electronics Hobbyists and Radio Amateur. Included are projects ranging from an FET Amplified Voltmeter and Resistance Bridge to a field Strength Indicator and Heterodyne Frequency Meter. Not only can the home constructor enjoy building the equipment but the finished projects can also be usefully utilised in the furtherance of his hobby.

99 TEST EQUIPMENT PROJECTS YOU CAN BUILD \$15.95
TAB No.805

An excellent source book for the hobbyist who wants to build up his work bench inexpensively. Projects range from a simple signal tracer to a 50MHz frequency counter. There are circuits to measure just about any electrical quantity voltage, current, capacitance, impedance and more. The variety is endless and includes just about anything you could wish for!

HOW TO GET THE MOST OUT OF LOW COST TEST EQUIPMENT \$9.95
AB017

Whether you want to get your vintage 1960 'TestRite' signal generator working, or you've got something to measure with nothing to measure it with, this is the book for you. The author discusses how to maximize the usefulness of cheap test gear, how to upgrade old equipment, and effective test set ups.

THE POWER SUPPLY HANDBOOK \$15.95
TAB No 806

A complete one stop reference for hobbyists and engineers. Contains high and low voltage power supplies of every conceivable type as well mobile and portable units.

PM246: ELECTRONIC TEST EQUIPMENT \$19.95

Covers analog and digital meters, oscilloscopes, frequency generation and measurement, and special measuring instruments.

TAB1532: THE COMPLETE BOOK OF OSCILLOSCOPES \$19.95

This totally up-to-date handbook is both an in-depth reference source and a practical applications guide. Information is included on both ordinary service and laboratory scopes, waveform analysis, vectors, vectorscopes, high and low frequency analysis, sampling, storage, digital scopes, and signature analysis. The author, Stan Prentiss is one of the leading technical writers in the U.S.

See order form in this issue.

Electronics Today Bookshelf

REFERENCE

BP85: INTERNATIONAL TRANSISTOR EQUIVALENTS GUIDE

ADRIAN MICHAELS \$11.75
This book will help the reader to find possible substitutes for a popular user-orientated selection of modern transistors. Also shown are the material type, polarity, manufacturer selection of modern transistors. Also shown are the material type, polarity, manufacturer and use. The Equivalents are sub-divided into European, American and Japanese. The products of over 100 manufacturers are included. An essential addition to the library of all those interested in electronics, be they technicians, designers, engineers or hobbyists. Fantastic value for the amount of information it contains.

BP108: INTERNATIONAL DIODE EQUIVALENTS GUIDE

ADRIAN MICHAELS \$8.95
This book is designed to help the user in finding possible substitutes for a large user orientated selection of the many different types of semiconductor diodes that are available today. Besides simple rectifier diodes also included are Zener diodes, LEDs, Diacs, Triacs, Thyristors, Photo diodes and Display diodes.

BP1: FIRST BOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES

B.B. BABANI \$5.75
This guide covers many thousands of transistors showing possible alternatives and equivalents. Covers transistors made in Great Britain, USA, Japan, Germany, France, Europe, Hong Kong, and includes types produced by more than 120 different manufacturers.

BP14: SECOND BOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES

B.B. BABANI \$6.75
The "First Book of Transistor Equivalents" has had to be reprinted 15 times. The "Second Book" produced in the same style as the first book, in no way duplicates any of the data presented in it. The "Second Book" contains only additional material and the two books complement each other and make available some of the most complete and extensive information in this field. The interchangeability data covers semiconductors manufactured in Great Britain, USA, Germany, France, Poland, Italy, East Germany, Belgium, Austria, Netherlands and many other countries.

TOWER'S INTERNATIONAL OP-AMP LINEAR IC SELECTOR

TAB No. 1216 \$12.95
This book contains a wealth of useful data on over 5,000 Op-amps and linear ICs — both pinouts and essential characteristics. A comprehensive series of appendices contain information on specs, manufacturers, case outlines and so on.

CMOS DATABOOK

TAB No. 984 \$9.45
There are several books around with this title, but most are just collections of manufacturers' data sheets. This one, by Bill Hunter, explains all the intricacies of this useful family of logic devices — the missing link in getting your own designs working properly. Highly recommended to anyone working with digital circuits.

Tab1538: ELECTRONIC DATABOOK — 3RD EDITION \$29.50

Any electronic job will be easier and less time consuming when you have instant access to exactly the nomogram, table, chart or formula you need, when you need it. All this and much more is included in this completely revised and updated version of one of the most respected information sources in the electronics field. Generously indexed, this handbook is divided into six sections: Frequency Data; Communication; Passive Components; Active Components; Mathematical Data; Formulas and Symbols and Physical Data.

Tab1516: TOWERS INTERNATIONAL MICROPROCESSOR SELECTOR

\$30.95
Towers Selector books have gained an international reputation for completeness and usefulness. This volume gives you all the data you will normally need to select the right chip.

ROBOTICS

THE COMPLETE HANDBOOK OF ROBOTICS

TAB No. 1071 \$15.95
All the information you need to build a walking, talking mechanical friend appears in this book. Your robot can take many forms and various options — light, sound, and proximity sensors — are covered in depth.

HOW TO BUILD YOUR OWN SELF PROGRAMMING ROBOT

TAB No. 1241 \$13.95
A practical guide on how to build a robot capable of learning how to adapt to a changing environment. The creature developed in the book, Rodney, is fully self programming, can develop theories to deal with situations and apply those theories in future circumstances.

Tab1421: HANDBOOK OF ADVANCED ROBOTICS \$23.95

Here's the key to learning how today's sophisticated robot machines operate, how they are controlled, what they can do and how you can put this modern technology to work. Also included are details on building your own hobby robot.

BUILD YOUR OWN WORKING ROBOT

TAB No. 841 \$10.95
Contains complete plans — mechanical, schematics, logic diagrams and wiring diagrams — for building Buster. Buster is a sophisticated experiment in cybernetics you can build in stages. There are two phases involved: first Buster is leashed, dependent on his creator for guidance; the second phase makes Buster more independent and able to get out of tough situations.

VIDEO

BP100: AN INTRODUCTION TO VIDEO

D.K. MATHEWSON \$7.60
Presents in as non-technical a way as possible how a video recorder works and how to get the best out of it and its accessories. Among the items discussed are the pros and cons of the various systems, copying and editing, international tape exchange and understanding specifications.

Tab1519: ALL ABOUT HOME SATELLITE TELEVISION

\$22.95
Covers such aspects as where to buy, problems in setting up your TVRO station and how to solve them, antenna siting and equipment selection.

Tab1490: VIDEO CASSETTE RECORDERS: BUYING, USING AND MAINTAINING

\$14.95
A complete handbook for the video enthusiast. You'll learn about how the systems work and how to choose as well as take a technical look at the inside workings. There are also sections on making your own video recordings.

MISCELLANEOUS

BP101: HOW TO IDENTIFY UNMARKED IC'S

K.H. RECORR \$2.20
Originally published as a feature in "Radio Electronics", this chart shows how to record the particular signature of an unmarked IC using a test meter, this information can then be used with manufacturer's data to establish the application.

AUDIO AND VIDEO INTERFERENCE CURES

KAHANER \$8.95
HB21
A practical work about interference causes and cures that affect TV, radio, hi-fi, CB, and other devices. Provides all the information needed to stop interference. Schematic wiring diagrams of filters for all types of receivers and transmitters are included. Also, it supplies simple filter diagrams to eliminate radio and TV interference caused by noisy home appliances, neon lights, motors, etc.

BASIC TELEPHONE SWITCHING SYSTEMS

TALLEY \$15.50
HB27
The Revised Second Edition of this book, for trainee and engineer alike, includes updated statistical data on telephone stations, and new and improved signaling methods and switching techniques. It also includes E & M signaling interface for electronic central offices and automatic number identification methods used in step-by-step, panel and crossbar central offices.

INTERRELATED INTEGRATED ELECTRONICS CIRCUITS FOR THE RADIO AMATEUR, TECHNICIAN, HOBBYIST AND CB'ER

MEDELSON \$10.95
HB29

This book provides a variety of appealing projects that can be constructed by anyone from the hobbyist to the engineer. Construction details, layouts, and photographs are provided to simplify duplication. While most of the circuits are shown on printed circuit boards, every one can be duplicated on hand-wired, perforated boards. Each project is related to another projects so that several may be combined into a single package. The projects, divided into five major groups, include CMOS audio modules, passive devices to help in benchwork, test instruments, and games.

BASIC CARRIER TELEPHONY, THIRD EDITION

TALLEY \$15.95
HB28
A basic course in the principles and applications of carrier telephony and its place in the overall communications picture. It is abundantly illustrated, with questions and problems throughout, and requires a minimum of mathematics.

Tab1309: THE ACOUSTIC AND ELECTRIC GUITAR REPAIR HANDBOOK


\$24.50
Literally everything the amateur or professional musician needs to know to properly maintain his instruments, plus all the how-to's for making repairs from simple tuning to major overhauls.

BP110: HOW TO GET YOUR ELECTRONIC PROJECTS WORKING

R.A. PENFOLD \$7.60
We have all built circuits from magazines and books only to find that they did not work correctly, or at all, when first switched on. The aim of this book is to help the reader overcome just these problems by indicating how and where to start looking for many of the common faults that can occur when building up projects.


ELECTRONIC TROUBLESHOOTING HANDBOOK

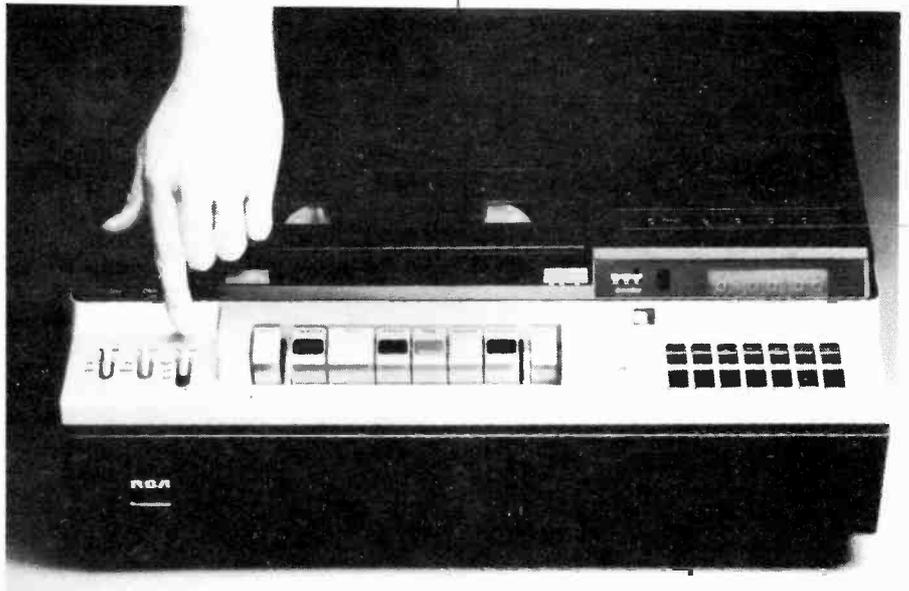AB019 \$11.95
This workbench guide can show you how to pinpoint circuit troubles in minutes, how to test anything electronic, and how to get the most out of low cost test equipment. You can use any and all of the time-saving shortcuts to rapidly locate and repair all types of electronic equipment malfunctions.



See order form in this issue.

NEXT MONTH

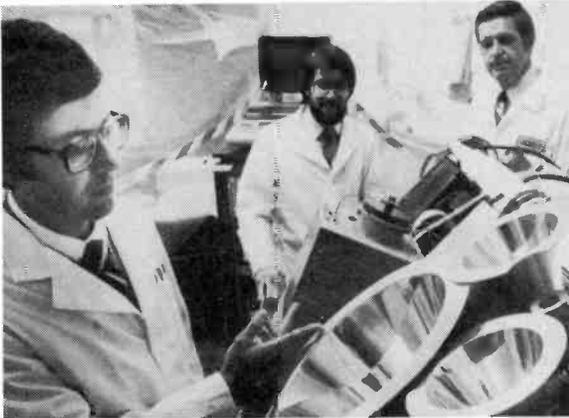


VLFs and the Magnetosphere

Roger Allan reports on how radio waves can be guided and amplified using the Earth's magnetic field.




Stylus Timer Project

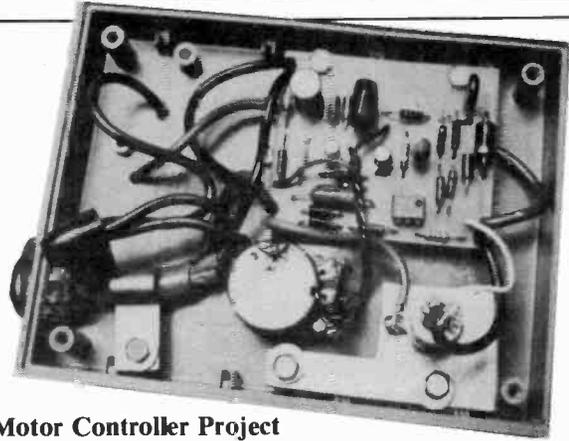If you're wondering why your records sound like the audio equivalent of steel wool, this timer will keep track of the stylus hours-in-use.



Motor Controller Project

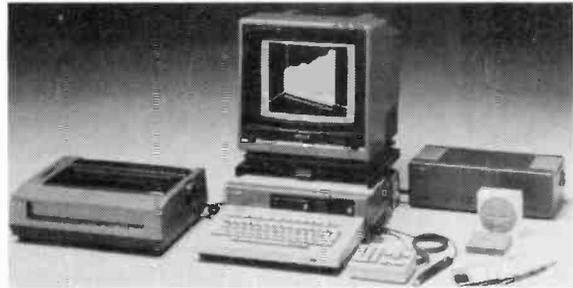Convert your regular drill to a variable speed or use a blender to slowly rotate your gerbils - precision motor control with next month's project.



Sony SMC-70 Review

Add a special graphics capability to a CP/M-based computer and you've got next month's look at the SMC-70.

Expand

If you've been enjoying the micro computing features in Electronics Today . . . or if you're just interested in the continuing development of this powerful new technology . . . you'll want to consider a subscription to Computing Now!, Canada's largest micro computer publication.

Whether you are a beginner, a business user, a programmer or a bleary eyed hacker up to your clavical in lost bytes you'll find something of interest in every issue of Computing Now! In the next few months we'll be looking at, among other things, computer aided drafting packages for personal computers, telecommunications, macro assemblers, programming in other higher level languages . . . there'll also be a massive directory of computer products in an upcoming issue which you won't want to miss.

A subscription to Computing Now! costs \$22.95 for one year (12 issues), or \$37.95 for two years (24 issues). This not only assures you of getting every copy fresh from the hairy palms of the post office, but saves you money - you'll save \$12.45 with a one-year subscription, and \$32.85 for two - plus getting the satisfying feeling of beating the gum-mint for the sales tax.



Computing Now! Subscriptions
25 Overlea Boulevard, Suite 601
Toronto, Ontario
M4H 1B1

Machine Code Programming

Part One

Machine code programming has two uses: firstly, as a way of getting your (normally BASIC-loving) microcomputer to go faster; and secondly, it's the only way to get a 'naked' microprocessor to do what you want. However, it's pretty difficult to learn on a bare micro, so in this short series, Bob Bennett will be showing us how it's done on a home computer, with some comments on using a microprocessor in the raw.

THE BEST way to learn to program using machine code is to have a go. After all, that was how you learned to program in BASIC. But then, BASIC does bear some resemblance to everyday English, and machine code looks like . . . well . . . code, so how is it done? To answer that, you need to have an insight into what is happening inside the computer — not a lot, just enough to make machine code programming clearer. I'll start with a short recap of some of the points relevant to machine code programming.

Deep In The Heart (of Texas?)

At the heart of any computer is a processor, and in most home computers it is a single chip. Many use a Z80 type, the processor in the Vic 20, Apple, etc., is a type 6502. Each processor has its own instruction set, which is a repertoire of instructions the processor will obey, and each processor has a register set, most of which can be used directly by the programmer. It is by the judicious use of the instruction set that the programmer manipulates the data in the registers to execute, in a controlled sequence, the various effects which constitute the desired aim of the overall program.

CPUs differ quite a lot in both the sizes of their instruction repertoires and in the number of registers that they contain. We'll be looking at registers in a moment.

The two more common types of memory used in home computers are random access memory (RAM), and read only memory (ROM). Fundamentally they appear the same in general makeup, inasmuch as they both have a number of locations (called addresses) where data can be placed, but in ROM that data is sealed in and cannot be altered, hence read only. It is in the ROM where the designer has put the rout-

ines to control all the effects I mentioned earlier, such goodies as PRINT, PLOT, SCROLL, etc., in fact everything your computer can do. RAM is where the machine code programmer (that's you!) places the instructions (program) which the processor hopefully will obey. The designation random is a bit of a misnomer: there is nothing random in the way the memory is accessed, at least, not (we hope) in a computer!

Bits And Pieces

So what's the connection between RAM, ROM, registers and the processor? The answer is a bus. Not the number 8 to the office, but another name for a connecting wire, or, as is more usual in a computer, a group of wires (or tracks on a PCB). These wires carry information in the form of electrical signals, and it is the level of the voltages present on the bus which conveys the meaning of the signals. An acceptable high level can be taken to mean a 1, and an acceptable low level can signify a 0, which leads us to use binary notation on computing (convenient isn't it?).

If there are n wires making up a bus, then the total information on the bus can be represented as 2^n . Most home computers have eight-bit registers (where bit is a contraction of Binary digIT), so the highest number this register can hold is $2^8 - 1$ which is 255 if all the bits are 1s. These eight bits are known as a byte.

255 is not a very high number to play around with, so it is arranged that registers can be used in pairs, but only in certain

combinations. This combination broadens our horizons somewhat because we can now use numbers up to 2^{16} which is equal to 65,536 decimal. The normal way to present data is one byte at a time, so our data bus usually has only eight wires. However, because we need a lot of memory, we use 16 wires on the address bus which allows up to 65,536 addresses, or locations to be used. This is known as 16K or 16 Kilobytes because it gets tedious writing out complicated binary numbers in decimal all the time. A K is 2^{10} , and this is equal to 1024 — it's the nearest convenient binary number to 1000, but note that a capital K is used to distinguish it from the decimal k (= 1000).

When you see advertisements extolling the virtues of home computers you will probably notice something along the lines of "16K ROM and 16K RAM". You will know that the ROM is for the routines that the designers have built into the machine. The start of the ROM area is usually (but not always!) address 0, so in the example given, it will extend up to address $16 \times 1024 - 1$, ie 16383 (the - 1 is because we've started counting at 0 rather than 1 as is usual outside computers — think of a street with 16 houses, if the first is numbered 0, the last will be number 15).

Unfortunately, this doesn't leave the RAM entirely free for the user to place all his or her programs, data, etc, because the computer needs some space to use for its own internal housekeeping (it stores what are known as the systems variables). It is very important not to over-write or corrupt the areas that the computer needs for this

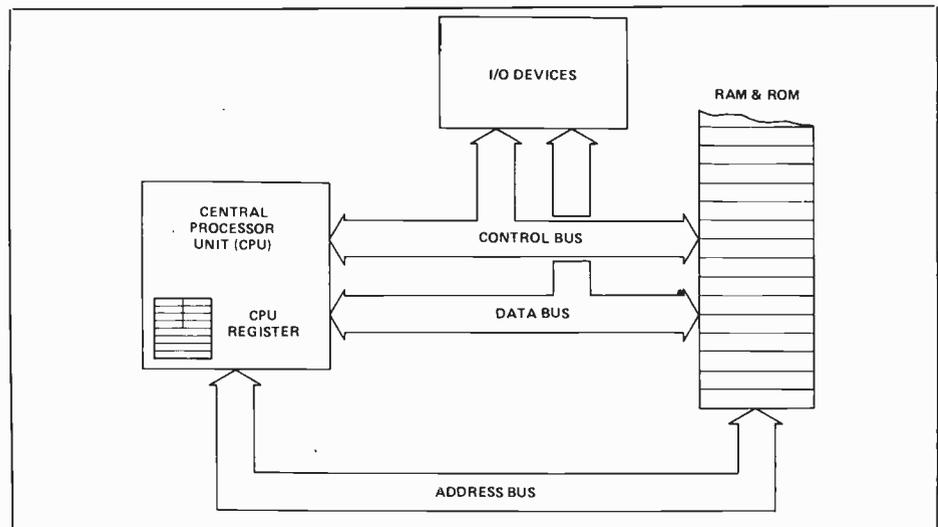


Fig. 1 Layout of a minimal computer.

CONVERSIONS

CONVERSION OF HEXADECIMAL TO DECIMAL

A single hexadecimal register holds up to 256, and, as we do when counting in tens, we split this into a 16¹ figure and a 16⁰ figure (as in tens and units). A register pair would hold figures for 16³, 16², 16¹ and 16⁰.

hex	16 ³	16 ²	16 ¹	16 ⁰
0	0	0	0	0
1	4096	256	16	1
2	8192	512	32	2
3	12288	768	48	3
4	16384	1024	64	4
5	20480	1280	80	5
6	24576	1536	96	6
7	28672	1792	112	7
8	32768	2048	128	8
9	36864	2304	144	9
A	40960	2560	160	10
B	45056	2716	176	11
C	49152	3072	192	12
D	53248	3328	208	13
E	57344	3584	224	14
F	61440	3840	240	15

Using the table: decimal 15 in a register pair = 000F whereas 240 decimal in a single register would = F0.

A0B0 hex = 40960 + 176 = 41136 decimal

FEDC hex = 61440 + 3854 + 208 + 12 = 65514

CONVERSION OF DECIMAL TO BINARY OR HEXADECIMAL

Conversion can be achieved in two ways, successive division or by spotting powers of two. Let's look at an example:

To convert 365 into binary by successive division goes as follows:

365 divided by 2 is 182 remainder 1
 182 divided by 2 is 91 remainder 0
 91 divided by 2 is 45 remainder 1
 45 divided by 2 is 22 remainder 1
 22 divided by 2 is 11 remainder 0
 11 divided by 2 is 5 remainder 1
 5 divided by 2 is 2 remainder 1
 2 divided by 2 is 1 remainder 0
 1 divided by 2 is 0 remainder 1

all successive divisions by 2 will yield the result 0 and the remainder 0.

The very first remainder we obtained the value of 2⁰, the next is 2¹, the next is 2², etc

So the binary for 365 is 0001 0110 1101 and the hex is 01 6D.

Spotting the powers of two would work as follows:

365 is over 256 (2⁸) but under 512 (2⁹) so the binary bit corresponding to 2⁸ is 1

365 - 256 = 109

109 is less than 128, so the bit for 2⁷ is 0

109 is greater than 64 so the bit for 2⁶ is 1

109 - 64 = 45

45 is greater than 32 so the bit for 2⁵ is 1

45 - 32 = 13

13 is less than 16, so the bit for 2⁴ is 0

13 is greater than 8 so the bit for 2³ is 1

13 - 8 = 5

5 is greater than 4 so the bit for 2² is 1

5 - 4 = 1

1 is less than 2 so the bit for 2¹ is 0

1 is equal to 1 so the bit for 2⁰

We follow this through in the same way as before.

UNLEASH THE POWER OF

ATOM



ATOM Model: AT-1 Disk Drive

MORE THAN JUST ANOTHER APPLE® COMPATIBLE DISK DRIVE

HIGH PERFORMANCE FEATURES

- High precision Ball Bearing Head Carriage, almost **NO NOISE**;
- **DIRECT DRIVE** Brushless Spindle Motor;
- 163 K Bytes, 40 Track capability;
- Half Track Capability;
- Fast Access Time (6ms track to track);
- Enhanced Read/Write Circuitry;
- Simplified High Technology Board for Lower MTBF
- **One Year Labour & Parts Warranty**

**THE ATOM AT-1 WILL READ MANY
MARGINAL DISKETTES OTHER
DISK DRIVES CANNOT ACCESS ...**

APPLE is a Registered Trade Mark of
Apple Computer Inc.
ATOM is a Trade Mark of Budgetron Inc.

We are signing up Dealers across
Canada. Call us now for
FREE DEALER DISK DRIVE PROGRAM

ATOM

is a Trademark of

Budgetron Inc.

1601 Matheson Blvd., Unit 3
Mississauga, Ontario, Canada L4W 1H9
Tel.: (416) 624-7323 Telex: 06-960172 Budgetron MSGA

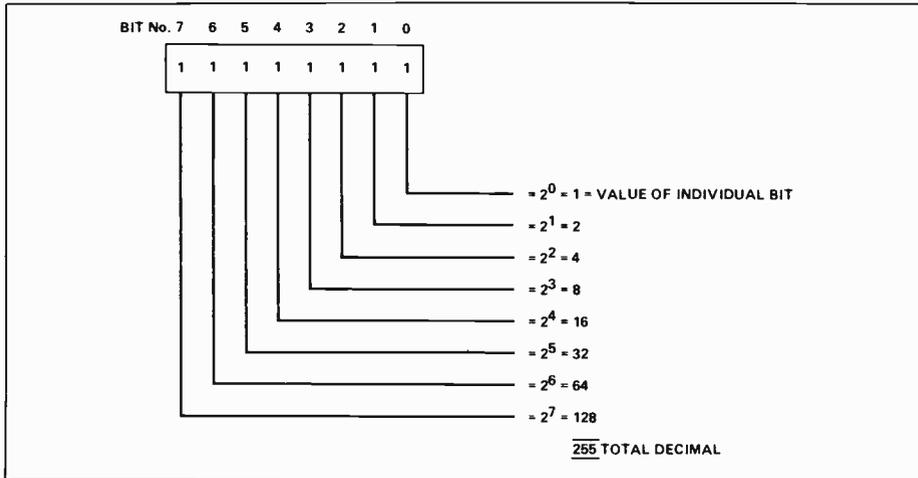


Fig. 2 The make-up of an eight-bit register.

purpose — doing so is a very effective way of bringing your micro to its knees (or whatever the micro equivalent of knee is). However, even in the most modest of systems, there will be more than enough space left for a decent machine code program.

Do You Do Voodoo?

If you are a student of the occult you may have come across the word hex before (I believe it has something to do with casting a spell), but in computing circles it is a word that machine code buffs drop all over the place. Actually it is short for hexadecimal, where hexa is from the Greek per-training to six, and decimal of course is all about tens, so putting them both together means we are counting using the base 16. Some people may believe that this is the Martian base of counting because they have sixteen fingers! Starting at zero (written as 0) we count up to 9 and then we go from A to F where A = 10 decimal and F = 15 decimal.

Note that we would write down 10 decimal as OA hex (or OAH), and 15 decimal is OF hex (or OFH): you must get used to the idea of writing hexadecimal numbers as two characters; for example, F on its own is meaningless whereas OF equals 15 decimal, and FO equals 240 decimal. FF hex equals 255 decimal which, if you remember, is the maximum that a register can hold, and also the number that eight bits would represent if they were all 1s which in turn represents one byte (see how it all fits in?), so two hex characters equal one byte. All this means that it is possible to write a machine code program in either binary, decimal or hexadecimal and still get the same result, but I think that you can discount using binary because it's far too cumbersome (although a knowledge of the binary system is essential for some applications as you will see).

To sum up so far: a machine code program is written to (or placed in) addresses

in RAM one byte at a time, some bytes representing instructions, and some representing data. Registers, either singly or in pairs, are used to manipulate the instructions and data, and the processor sorts it all out. According to the information in the program, different routines in ROM are called into used to give different effects. This is a very simplified explanation, but essentially correct, and although I have only been talking about typical home computers, very much the same sort of process happens in larger computers, only on a much grander scale.

I mentioned earlier that I would discuss register in greater detail, so here we go. Using the Z80 set as a model (Fig. 3), the A register is historically called the accumulator because it was used to accumulate the results of computations. It is still a hard worked register, and there are certain operations that can only be carried out using the A register, but more of that later. The F register is the flags register alias the status register. This is so important to machine code programming that it warrants a section to itself. The B, C, D, E, H, and L registers are general purpose registers which are not found in a lot of CPUs.

When an input device requires the attention of the CPU it sends out a signal called an interrupt. What happens then depends on the CPU type, but usually an indicator signals the fact that an interrupt has occurred, and then the interrupt routine is entered. The Z80 has a rather unique way of dealing with an interrupt, however. Once an interrupt has been acknowledged, the device puts the low byte of an address onto the data bus. The high part of the address is in the I register, the two parts forming the address of a routine to handle the interrupt.

The R register is a simple counter (0 to 255) which is used to periodically refresh memory cells in RAM in order not to lose the contents. When a GOSUB is used in BASIC the computer uses portion of RAM

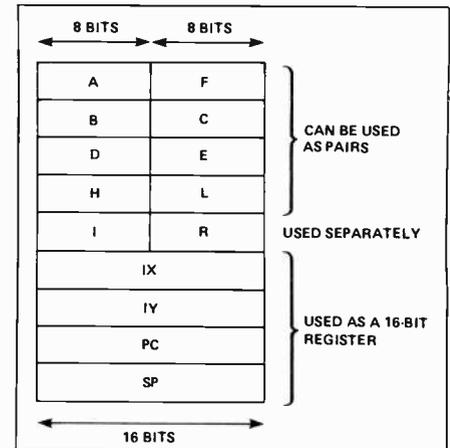


Fig. 3 The Z80 register set. Note that there is also an alternate set of registers A',B',C',D',E',F',H',L', usually referred as A',B', etc.

as a stack to store the address of the next instruction to be executed after meeting a RETURN. The stack is also used when pushing and popping (more later) to keep tabs on the addresses. It seems quite logical therefore to have a stack pointer to hold the address of the last item to be put onto the stack; this is the SP pair. The last registers in this set are the two used as a program counter (PC); the PC holds the address of the current instruction.

I have saved the two sets of register pairs IC and IY until now because not many CPUs have the sets. They are used for indexed addressing which, very simply, is this, using IX as an example. The IX pair are made to hold the address of a table where information relating to your program has been stored; this is known as the base address. When required the IX pair will meet instructions pertaining to their role in the program. These instructions are in two parts, the first part is a number, which is added to, so subtracted from the base address. This will point to an address in the table. The second part is an instruction relating to what will happen at that address, and this may, or may not influence what happens next in your program.

A Bit Of Flag Waving

As well as the general purpose registers, each processor will have a **flag**, or **status register**. These are constructed in exactly the same way as any other register, but the bits are used as indicators, or **flags**, to signal whether or not certain conditions have been met. The convention is that when a bit is set it is 1, and when reset, it 0; when the condition has been met the flag is set, and reset otherwise.

Every micro I know of has a zero flag of some sort — one that is set when the contents of a particular register are Zero. As an example, let's look at what is involved in the execution of a FOR-NEXT loop;

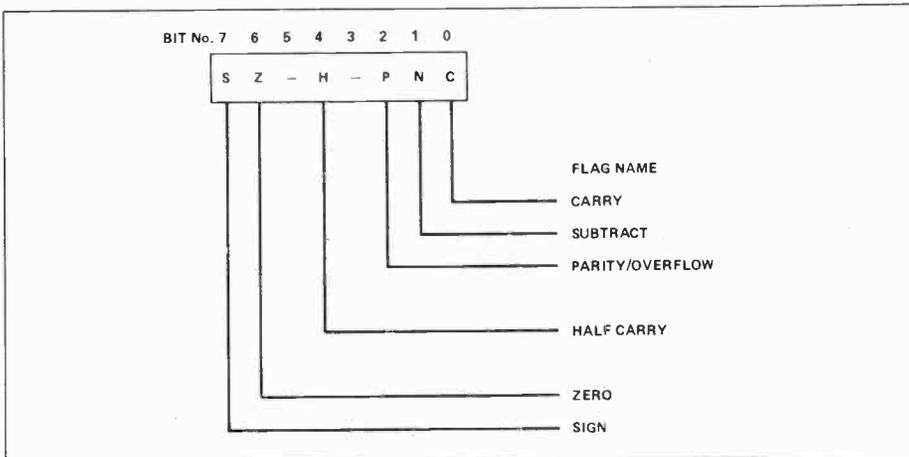


Fig 4. The flags available in register F.

something like this will be taking place: load a register with n (the loop count); do the task contained in the loop; decrement the count ($n = n - 1$); test the flag to see if the register is zero. If it is not, then go back and do the task again; if it is, go on to the next task. Note that both conditions of the flag can apply, and we program the computer to do one thing if the flag is set, another if it isn't.

The more usual flags are zero, parity/overflow, sign, carry, half-carry,

subtract, and others may be interrupt, decimal and break. Whatever flags your processor uses, get to know them along with the instruction set. Any good computer handbook should give the instruction set, and any good library will have a computer section with a good selection of books on micros.

Other registers will include the stack pointer (SP) which may be a pair or a single register, which is used as a pointer to the stack area of memory. Index registers may

come singly or in pairs, and are usually designated X and Y singly, and prefixed with I in pairs. As their names implies, these are used for indexing along tables of data. If you remember, a program is stored in a number of addresses, so a **program counter (PC)** is used as a pointer to these addresses. One last register: dynamic RAM will need refreshing (electrically) every now and again so that information isn't lost, so there is a **refresh register** (they think of everything). This list isn't exhaustive and don't worry if it isn't all completely clear what's going on. However, I hope that your appetite is whetted enough to probe further into your computer.

ETI

Continued in the next issue.

Announcing

PRINTOUT
Canada's Microcomputing Newsletter

See page 66

AUDIOVISION

COMPUTING/ELECTRONICS

MAIL ORDER: Certified cheque, money order, VISA or Master Card plus 5% delivery charge. Ontario residents add 7% P.S.T. We send Canada Post, or Purolator freight collect.

6502 COMPUTER SYSTEMS

SPECIAL PACKAGES SALE

90 DAY WARRANTY

PACKAGE 1: \$949.00 **PACKAGE 2: \$1,550.00**

- 64K Computer with Multi-Function Keyboard, Upper/Lower Case and Numeric Keypad
- Disk Drive (Shugart)
- Controller Card
- Zenith 12" Green or Amber Monitor

PACKAGE 3: \$1,700.00

- Same as package 2 but with IBM look-alike case and Multi-Function detachable Keyboard

(We send Computer Systems via Purolator Freight Collect)

ACCESSORIES

1. 128K Card \$195.00	8. Delux Self Centered Joystick 45.00
2. 300 Baud Modem 155.00	9. Disk Drive (Quentin) 299.00
3. Talk Card 40.00	10. Disk Drive (Shugart) 259.00
4. Musician Card 155.00	11. Light Pen System 225.00
5. RS232 Card 70.00	12. Graphic Tablet 109.00
6. RF Modulator 15.00	13. Nashua Diskette, SS/DD 25.00
7. Joystick (Self-Centered) 20.00	

ELECTRONIC KITS

DIGITAL DESIGNER FOR COMPUTER TECHNOLOGY

Supplies all necessary signals, voltages and read-outs to design or construct any digital circuit.

Kit \$54.95

REGULATED POWER SUPPLY KITS
(Transformer not Included)

Variable Voltage: **Kit \$14.50**
0-15V, 5A

Kit \$14.50
0-35V, 3A

Variable Voltage & Current **Kit \$21.50**
0-50V, 0.5-3A

SUPER FM WIRELESS MIKE

Complete unit fits into a plastic cigarette case. Picks up and transmits sound up to 300 ft. through a FM Radio

Kit \$9.50

SOUND/LIGHT ACTIVATED SWITCH

Selectable Sound/Light Control. Works as an On/Off switch activated by intensity of light or sound. Can control up to 200 watts.

Kit \$11.50

ELECTRONIC CLOCK

Green Led Display with dual tone alarm. Runs on 12VDC (0.2A) or 18VAC.

Kit \$19.50

COLOR ORGAN/LIGHT CHASER

Features variable speed 3 sequence light chaser, or direct hook up to speaker as color organ for Control up to 1500 watt lights.

Kit \$79.50

TELEPHONE CONVERSATION RECORDING UNIT

Easy hook up to Telephone and Recorder for automatic recording of telephone conversation. No battery required.

Not A Kit \$14.50

LOGIC PROBE

\$29.50

For Quick servicing and checking of integrated logic system. Features unique Multi-Lamp readouts, pulse detection, and input overload protection. Max. input Freq. display: 30 MHz. Min. detachable pulse width: 20 ns.

LOGIC PULSER

\$33.50

Allows injection of pulses into circuit nodes without cutting traces, removing ICs; and monitoring circuit response with a logic probe.

DESOLDERING TOOL

\$14.50

Makes parts removal from PC Board a Breeze.

I.C. EXTRACTION TOOL

\$2.50

Extracts all LSI, MSI and SSI devices from 8 to 40 pins.

1984 Catalogue **\$1.00**

MINI-DRILL WITH STAND

Operates on 4 penlite batteries or a AC adaptor (6-12V, 2A)

Speed 2200 RPM
Ideal for Drilling and Grinding P.C. Boards, Aluminum and Copper Sheets.

\$45.00

POWER TRANSFORMERS

110VCT, 0.5A	13.50
64 VCT, 0.5A	8.70
30 VCT, 2A	9.50
18VCT, 3A	12.50

TRANSISTORS

MOSFET 2SK134	\$12.95
MOSFET 2SJ149	12.95
MJ15003	6.50
MJ15004	6.50
2N3055	1.45
MJ2955	1.45

ELECTROLYTIC CAPACITORS

10,000 MFD 50V	\$ 8.50
10,000 MFD 80V	15.00

BOOKS

Apple II & IIe User's Guide	\$17.50
Apple II Circuit Description	27.00
DOS Manual	15.00

RACK MOUNT CABINETS

Black Anodized Aluminum Front Panel with Steel Box, Hardware, Ventilation Slots and Instruction

Panel Size (inch)	Box size (inch)	Price
19 x 7	17 x 8.5 x 12	\$43.50
19 x 6	17 x 5.5 x 12	42.50
19 x 5	17 x 4.5 x 12	39.50
19 x 4	17 x 3.5 x 12	36.50
19 x 3	17 x 2.5 x 10	33.50
19 x 2.5	17 x 2 x 10	32.50
17 x 6	15.5 x 5.5 x 9	37.50
17 x 4	15.5 x 3.5 x 9	32.50
17 x 2	15.5 x 1.5 x 9	30.50
12 x 6	11.5 x 5.5 x 7	28.50
12 x 4	11.5 x 3.5 x 7	22.50
12 x 2	11.5 x 1.75 x 7	21.50

While Audiotwords for Cabinets \$2.50

EASTERN CANADA
578 MARLEE AVE.
TORONTO, ONT., M6B 3J5
TEL: (416) 781-3263

WESTERN CANADA
P.O. BOX AMF23561
VANCOUVER, B.C.
TEL: (604) 271-7939

PRINTOUT

Suite 601
25 Overlea Boulevard
Toronto, Ontario
M4H 1B1
(416) 423-3262

Canada's Microcomputing Newsletter

How much do you value accurate, objective, timely information about what is happening in microcomputing in Canada? Certainly highly, but where do you get such advice? We have the answer.

That is why we are launching PRINTOUT, Canada's Microcomputing Newsletter, the finest publication of its type. It has one aim and one aim only - to keep you informed and abreast of current developments, new products, people, companies looking for retail outlets, outlets looking for products, and more.

PRINTOUT is a true newsletter - it carries NO ADVERTISING or paid information. It is concise, informed and published by the company that knows what is happening in the Canadian Microcomputing field - Moorshead Publications, publishers of Computing Now!, Electronics Today, and Computers in Education. PRINTOUT as a newsletter, however, will not be a consumer magazine since it will contain the urgent information you need to obtain or maintain market share. You need it quickly and that's how you will receive it.

It is not inexpensive, good information never is, but neither is it expensive at \$8.48 per issue. It appears 23 times a year, sent by FIRST CLASS POST in the middle and at the end of each month. That makes PRINTOUT \$195 a year, but isn't it worth it to know what is going on? Each issue will contain contacts and information that is going to make you a lot of money. That's what it's all about.

As an introduction to PRINTOUT, however, if we receive payment this month, there is a \$50 discount: you pay \$145 for a full year or \$95 for six months.

We are so sure that PRINTOUT is good value that we will refund your complete subscription if you cancel before your third issue is mailed, thereafter we will refund the unexpired portion if you don't think we are doing the job. That demonstrates the confidence we have.

Don't miss out. Send off your cheque today.

Sincerely,

Halvor Moorshead

Halvor W. Moorshead,
Publisher.

Introductory Offer
SAVE UP TO 25%
Expires this month

PRINTOUT

Canada's Microcomputing Newsletter

<input type="checkbox"/> 1 Year	\$145.00	<input type="checkbox"/> 6 Months	\$ 95.00
Regular	\$195.00	Regular	\$120.00
You save	\$ 50.00	You save	\$ 25.00

(Outside Canada — Payments in U.S. Dollars)

Cheque Enclosed (send with card in envelope)

Bill me Subscription will commence upon receipt of payment

Charge My Visa Mastercard AMEX

Card No. _____

Expiry Date _____

Signature _____

Name _____

Company (if applicable) _____

Address _____

City _____ Province _____

Postal Code _____ Date _____

Moorshead Publications, Suite 601, 25 Overlea Blvd. Toronto, Ontario M4H 1B1 Tel: (416) 423-3262


TECH TIPS

Signal Generator

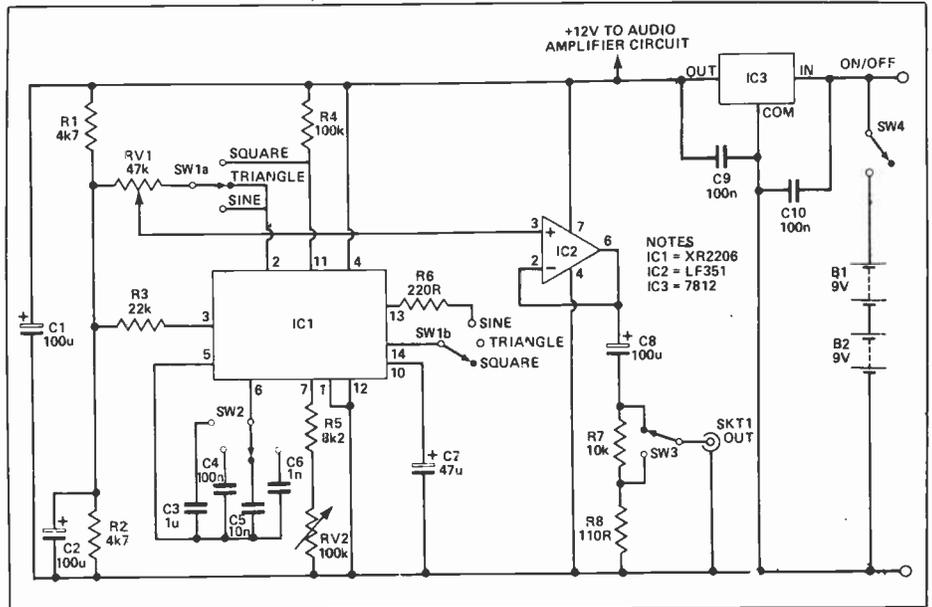G. Teesdale

THIS unit is based on the XR2206 function generator integrated circuit, as can be seen from the circuit. The charge/discharge capacitor connects between pins 5 and 6 of IC1, and in this case four switched capacitors are used to give the unit its four frequency ranges. Variable resistor RV2 is the fine frequency control and C7 is a bypass capacitor for an internal circuit of IC1. The sinewave/triangular output is taken from pin 2 of IC1, and the output from this is normally the triangular waveform. The sinewave signal is obtained by connecting a resistor (R6) between pins 13 and 14 of IC1.

Rather than having separate amplifiers for the triangular output buffer and the sinewave shaping circuit, the XR2206 uses the same amplifier for both functions, and switching in R6 connects the shaping components into the feedback circuit of the amplifier. This resistor could be replaced with a preset resistor, which would then be adjusted to optimize performance, but results should be more than adequate using the specified (fixed) value.




Peak Level Indicator

David Hamill

This peak level indicator is useful for recording when it is more important to know what the peak level of a signal is, rather than its average level.

VU meters are normally used for this purpose; however, you will find that the LED output of this circuit is easier to interpret and makes the recording more accurate as the distortion will be reduced.

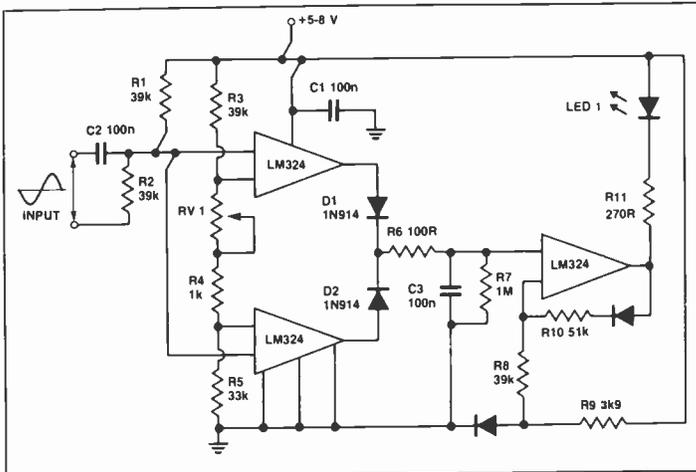IC1a gauges the positive peaks while IC1b does the same for the negative peaks. Both positive and negative are set by RV1. You can select any threshold from ± 1 V. Whenever the input exceeds the positive of the negative level LED1 lights for about 0.1 second.



Complete System +



for
\$875.00

- Fully Apple™// compatible • 48K memory • Disk drive • Disk controller card • Upper/lower case • Hi-res Amber monitor • Color graphics • 90 days warranty

I.B.M. Compatible



ECS1
\$1995.00

- 8088 processor • optional Intel 8087 numeric coprocessor • 64K memory exp. to 256K on board • double sided double density disk drive • detachable keyboard • colour-graphic board • support IBM® software • 90 day warranty

Complete System Model 2200



for
\$999.00

- Fully Apple // compatible • dual processor 6502 and Z80 • 64K RAM • 24K ROM • 80 or 40 column soft switch • controller card • disk drive • Hires amber monitor • colour graphics • detachable keyboard • 90 days warranty

ECS2 Systems



\$1295.00

- Fully Apple // compatible • dual processor 6502 and Z80 • 64K RAM • 24K ROM • controller card • disk drive • Hi-res lilt amber monitor • colour graphics • detachable keyboard with special function • 90 days warranty

ELECTRONIC CONTROL SYSTEMS

1890 Meyerside Drive, Mississauga, Ontario L5T 1B4
(416)673-1302 Hours — Mon. to Fri. 10-7, Sat. 10-2

Circle No. 6 on Reader Service Card

ETI—JUNE—1984—67


Two circuits for the 74LS241

Brian O'Conner

These circuits use the 74LS241 and in each case pin 1 is tied to ground and pin 19 to Vcc.


The first circuit is for a DC motor driver suitable for use with 400 mA/6 V motors. Little or no heatsink is required as all transistors are either saturated or off.

The second circuit is for a very simple 8-bit digital to analogue converter which can be built from scrap box components. It will give a linear output of 8 V p-p and the ramp produced by an 8-bit increment is quite smooth.

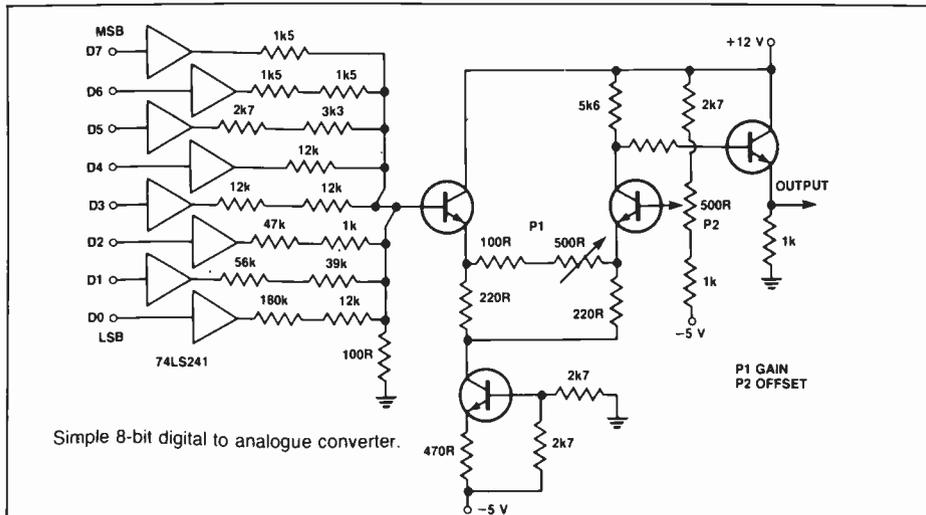

Simple 8-bit digital to analogue converter.

Input A	Input B	M _A	M _B	Result
0	0	+5V	+5V	no operation
0	1	+5V	GND	motor turns
1	0	GND	+5V	motor turns opposite
1	1	GND	GND	no operation

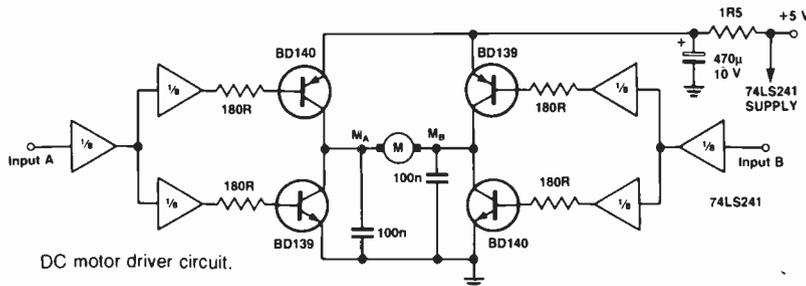

DC motor driver circuit.

GET THEM FROM THE SOURCE

FOR *APPLE II/III/IIIe/COMPATIBLES

	Price Can. + Postage Dollars & Insurance	Air = Price CIF
Standard Disk Drive	230	+ 25 = 255.00
SLIM DIRECT DRIVE	240	+ 25 = 265.00
Drive Controller Card	33	+ 3 = 36.00
DP-80 Printer (220V + Transformer)	315	+ 40 = 355.00
Super-5 Printer (220V + Transformer)	360	+ 40 = 400.00
80-P Printer (Eqv. Epson MX80FT/3)	472	+ 40 = 512.00
RS-232 Serial Interface Card	48	+ 8 = 56.00
Parallel Interface Card	48	+ 8 = 56.00
Z-80 A Card	31	+ 6 = 37.00
16K Ram Card	35	+ 6 = 41.00
128K Ram Card	146	+ 8 = 154.00
Eprom Writer Card	49	+ 6 = 55.00
RF Modulator with Sound	10	+ 5 = 15.00
80/40 Column Switch	5	+ 3 = 8.00
Cooling Fan	28	+ 8 = 36.00
5 AMP Heavy Duty Power Supply	39	+ 20 = 59.00
Joystick (self centred)	17	+ 5 = 22.00

* Quantity discount available upon request * Import duty 0 to 5.1%, FST 9%, payable at destination * 90 days guaranteed on all items.

Send Bankdraft or Money Order to:

ALPS INTERNATIONAL & CO.,
1313A Ocean Centre
5 Canton Rd.,
Kowloon, Hong Kong

*APPLE II is a registered trade mark of APPLE COMPUTER INC.


Incremental Timer

R.A. Penfold

THE LM3914 LED display drive, IC1, is connected as a zero to 5V (full scale) voltmeter to display in the bargraph mode. Thus, each LED will turn on at increments of 0V5 as the input of IC1 is driven by the voltage across capacitor C1. This is charged with a constant current so that the voltage across it will rise linearly with time. That is, the voltage across C1 rises, the LEDs will light up one by one until the voltage reaches 5V or until C1 is

discharged.

A relay and alarm circuit is built around IC2 plus Q3 and associated components. SW2 selects at which 'increment' the relay and alarm are operated by selecting one of the outputs of IC1. When the output goes 'active' (when the LED lights), the alarm sounds, the relay drops out and the timer is reset by discharging C1. For example, if the third increment is selected (pin 17, IC1), then LEDs 2, 3 and 4 only will light, the alarm sounding when LED4 lights. C1 is then discharged at that time, resetting the timer ready for its next use.

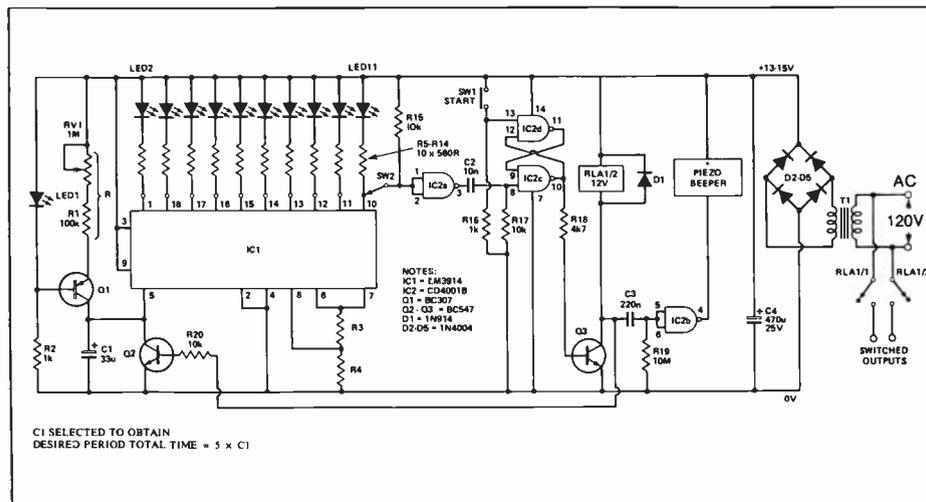

C1 SELECTED TO OBTAIN DESIRED PERIOD TOTAL TIME = 5 x C1

The complete circuit of the Incremental Timer. T1 is 9 to 12 V, 6 VA

ETI

Circle No. 1 on Reader Service Card

The Fun of Electronics



"It's a new type of memory chip, manufactured in California. It doesn't have a definite access time; it finds your data as soon as you stop hassling it and let it get its head together."



"The Neighbours' committee has come up with two possible courses of action. The first is to ask you to stop your HAM Radio from interfering with our TV reception."



"I think I've been playing with my strobelight too much."



"What's this roll of toilet paper doing in my adding machine, and where's my expensive calculator paper?"



"I think your father's been working with computers for too long. He left a message that says 'If I am Late, then store dinner in fridge. Else go to oven and heat dinner.'"



"We have to take the pictures over again. I was so busy working the Automatic Light Meter, the Digital Shutter Speed Control, the Ultrasonic Focuser and the Electronic Flash, that I forgot to take the lens cap off."

Product Mart *Where Buyers Find Sellers*

J&J ELECTRONICS Ltd., P.O. Box 1437E, Winnipeg, Manitoba R3C 2Z4. Surplus and Semiconductor Specialists. Do you get our bargain flyer? Send \$1.00 to receive the current literature and specials and to be placed on the mailing list for future publications.

1984 WORLD RADIO-TV HANDBOOKS \$23 + \$2 S&H, WSI 1984 Catalogue \$2.00, WSI RADIO, Box 400, Kitchener, Ontario N2G 3Y9.

COMMODORE 64 Owners. We offer a fine selection of programs. Send for our new free catalogue. **SANDISON SOFTWARE**, Box 1403, Chatham, Ontario N7M 5W8.

FOR \$10 per kit \$2 handling, receive free flyer and any of the following. #1: 1000 asst'd pcs, choke - capacitor - resistor - transistor - hardware - etc. Capacitor specials: #2: 200 asst'd ceramic - #3: 100 asst'd silver mica - #4: 100 asst'd mylar ! #5: 50 asst'd tantalum - #6: 50 asst'd electrolytic - #7: 50 asst'd feed-through - #8: 50 asst'd metallic silver mica (Elmenco) - #9: 25 asst'd variable. All new material. Unconditional guarantee. **SURPLUS ELECTRO QUEBEC**, 2264 Montee Gagnon, Blainville, Quebec J7E 4H5.

UNUSUAL BOOKS: Intelligence & Investigative electronics and other covert technologies, (the real James Bond stuff.) Fascinating, hard-to-find technical information on many subjects. Free brochures: **MENTOR PUBLICATIONS**, Dept. CIA, 135-53 No. Blvd., Flushing, New York, 11354.

8088 BOARD IC's. Plus more at competitive prices. New price list free. HN482764(300NS) — \$10.00. **M.O. ENTERPRISES**, Box 2066, Bramalea, Ont. L6T 3S3

LASER surplus: Helium-Neon systems from \$110.00; Ruby rods; Infra-red "Night vision" devices from \$30.00. Free catalog. **MEREDITH INSTRUMENTS** 6517 W. Eva Glendale, Az. 85302.

DIGITAL Logic kits. Each one builds on previous. Introductory package includes wire-wrap tool, wiring board, IC's, hardware, manual and more. Send \$37.95 + \$3.00 P&H for package or \$1.00 for more info. **LAMANTIA PRODUCTS**, P.O. Box 690, Lindsay, Ont. K9V 4W9

SPECIAL KITS — (1) Rumble filters \$13.52, (2) Mag/Cer preamp \$8.15, (3) 741 amp \$14.30, (4) variable timer \$18.51, (5) loudness control \$11.23, (6) simulated stereo \$17.75, (7) dice-LED \$14.40, (8) scratch filter \$18.33, (9) 3 channel mixer \$13.92, (10) doorbell \$32.25. Schematic & instructions included. Free sample parts pak w/order. New parts price list available. Incl \$0.60 for mailing. Add 10% P&H, Ont. Res. add 7% P.S.T. Send cheque / Moneyorder to **ELECTRON COMPUTERS**, P.O. Box 613, Stn. 'U', Toronto, Ontario. M8Z 5X9. (416) 259-8709.

ZX81/TS1000 HIGH RESOLUTION PROGRAMS.

High resolution graphics program (128 by 192) \$5.00. Word processor with lower case on printer \$6.00. High resolution space invaders program \$9.00. 25 machine code programs \$4.00. All programs on cassette. **C. BIRD** 2091 Carrick St., Victoria, B.C. V8R 2M5.

PAY TV Descramblers. Manuals and PC's for all types used in Canada. Send self-addressed stamped envelope for free details. **STEEL CITY ELECTRONICS**, Box 887, "A", Hamilton, Ont., L8N 3P6.

DESCRAMBLERS, radar detectors, phasers, lasers, surveillance equipment, infinity transmitter, and lots more. Send \$2 (refundable) for catalogue. **F.T.S. ELECTRONICS**, Box 574, Brantford, Ont. N3T 5N9.

EPROMS. 2764 \$12.00; 2732 \$8.50; 2716 \$6.00; 8088 \$32.95; Z80A \$6.00. Apple IIe compatible system - MPF III - 64K, slim drive, amber monitor, 40-80 columns \$1395. Add 10% postage. **RAITRONIC COMPONENTS**, 6650 Ross St., Vancouver, B.C. V5X 4B2.

C64 Assembler \$15.95, disk version \$19.95. RS232 interface coming soon. VIC20 8K battery powered RAM cartridge clearance priced at \$59.95. Ont. res. add 7% P.S.T., **CANADIAN MICRO PERIPHERALS**, Box 123, Waterloo, Ont. N2J 3Z9.

TI-99/4(A) OWNERS! — We offer a fine variety of original games on cassette. Send for free list. **GIGO SOFTWARE**, P.O. Box 673, Niagara Falls, Ontario L2E 6V5 Canada.

AUDIO Kits: graphic equalizers, 12-24 bands/channel \$89-200 (U.S.); noise filters, many others — **SSS 856T Lynnrose**, Santa Rosa, CA 95404, U.S.A.


Z80 MICRO-CONTROLLER ... parallel I/O ports. Runs XYZ motors with encoders via keypad commands. An introduction to automation. Schematics, X-Y grid wiring lists, and software monitor in ROM, \$110.00 Source and doc on 8" SSSD disk for further software customizing via your 64K CPM computer, \$84.00. Do-it-yourself. Money-orders only. Man. res. add 6% tax, **Z80-CONTROLLER**, P.O. Box 3775, Stn. B., Winnipeg, Man., R2W 3R6.

NEW Software ... A 100 question quiz to tune-up your Z80 assembly language know-how. Use it as a fast review, a serious study, or as a game. Makes learning easy. Self-prompting. Choice answer questions. Keeps track of your score. On 8" SSSD floppy disk. Runs on 64K CPM computers. \$64.25 Money-orders only. Man. res. add 6% tax. **Z-QUIZ**, P.O. Box 3775, Stn. B., Winnipeg, Man. R2W 3R6.


DISCOUNT SOFTWARE for the Commodore VIC-20 and Apple II+. VIC-20 Software: Snakman (\$10.00), Crazy Kong (\$10.00), Exterminator (\$11.00), Amok (\$10.00), Cricket (\$10.00), Escape (\$10.00), Bomber (\$10.00), Rescue From Nufon (\$10.00), Cosmic Brewers (\$11.00), Dog Race (\$8.45), Fuel Pirates (\$10.00), Blowup (\$10.00), Skiing (\$6.40), Superclimber (\$10.00), Surfing Sun (\$9.50), Draw (\$7.15), Spell Master (\$8.95), Memory (\$7.95), Correct Change (\$7.25), Ultimate Math Drill (\$7.15). Disk add \$3.00. **APPLE SOFTWARE:** Cannonball Blitz (\$15.00), Choplifter (\$15.00), David's Midnight Magic (\$15.00), Flight Simulator (\$15.00), Olympic Decathlon (\$15.00), Swashbuckler (\$15.00), Zaxxon (\$16.00), Zork I (\$16.00), Aztec (\$16.00), One on One Basketball (\$18.00), Stargate (\$16.00), Night Mission Pinball (\$14.00), Rearguard (\$15.00), Ribbit (\$13.00), Super Puckman (\$16.00), Ultima (\$17.00), Graphics Magician (\$29.00), Locksmith 5.0 (\$44.00), Nibbles Away (\$29.00), and much more. Specify Apple or Vic-20. To order, write **DISCOUNT SOFTWARE**, P.O. Box 1489, Niagara-on-the-Lake, Ontario, L0S 1J0.

RADIO SUPPLY & SERVICE (1977) LTD. — Phone (306) 352-8642, Telex 071-2661. 3033 Saskatchewan Drive, Regina, Sask., S4T 1H5. Distributors of radio, T.V., electronic parts and industrial components. Ham radio specialists.

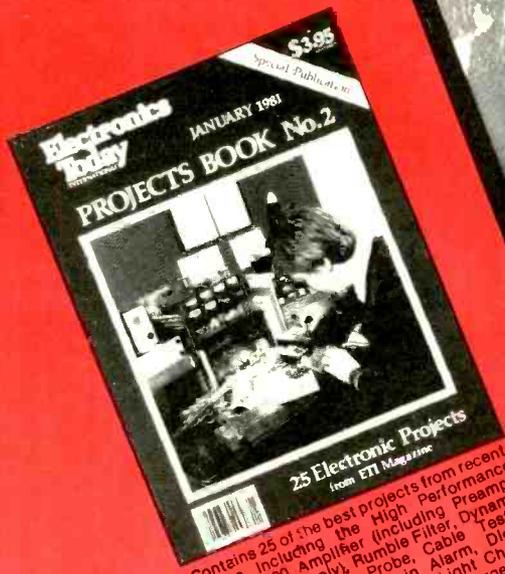
Advertising in the Product Mart section allows you to reach over 30,000 Canadian readers nation wide for \$1.00 per word (minimum 25 words). Please contact us for further details on the various sizes and styles available. Moorshead Publications, Suite 601, 25 Overlea Blvd., Toronto, Ontario M4H 1B1, (416) 423-3262



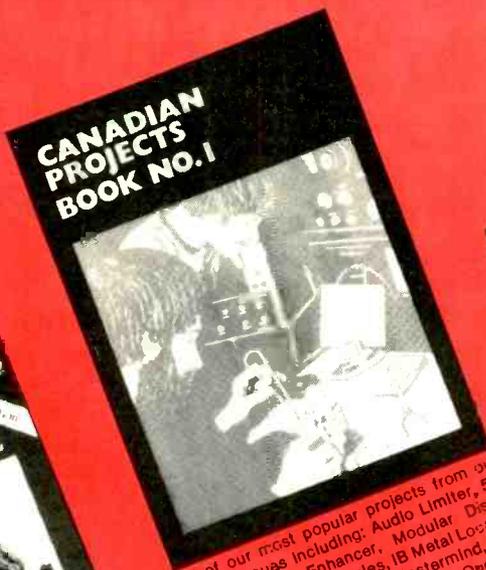
Contains 25 of the best projects from recent issues including the High Performance Series 4000 Amplifier (including Preamps and Power Supply), Rumble Filter, Dynamic Noise Filter, Logic Probe, Cable Tester, Function Generator, Rain Alarm, Digital Tacho, Teo Octave Organ, Light Chaser, Shutter Speed Timer, Ni-Cad Charger and more. First published January 1981.



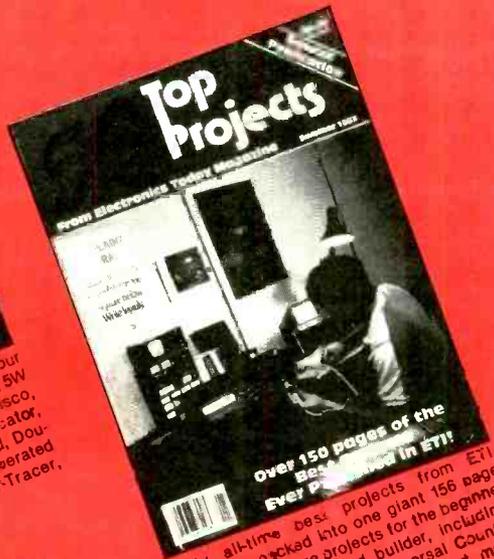25 of our most popular projects from our earlier issues including: Audio Limiter, 5W Stereo, Bass Enhancer, Modular Disco, 50W/100W Amp Modules, IB Metal Locator, Touch Organ, Electronic Mastermind, Double Dice, Reaction Tester, Sound Operated Flash, Burglar Alarm, Light Chaser, Digital Voltmeter, Injector-Tracer.



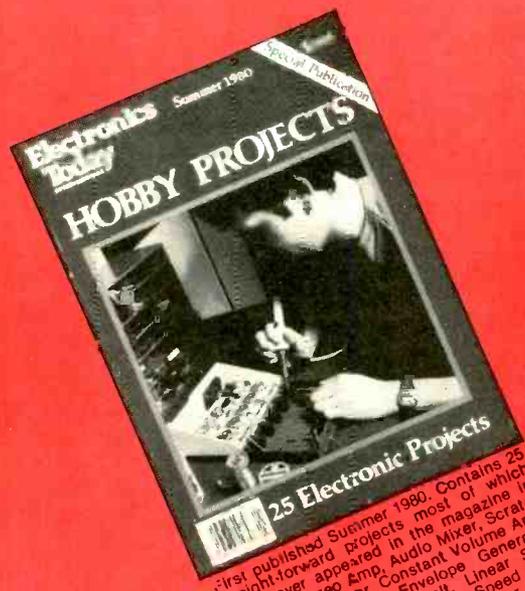Fifty all-time best projects from ETI magazine packed into one giant 156 page special. There are projects for the beginner to the more advanced builder, including: Semiconductor Tester, Universal Counter, LED Level Meter, AM radio, and much, much more.



First published Summer 1980. Contains 25 straight-forward projects most of which have never appeared in the magazine including: Stereo Amp, Audio Mixer, Scratch and Rumble Filter, Constant Volume Amp, Graphic Equaliser, Envelope Generator, White Noise Effects Unit, Linear Scale Ohmmeter, Intercom, Drill Speed Controller, LED Tacho, Parking Meter Timer, Electronic Organ, Touch Switch, Electronic Dice, Siren, Simple Receivers.

A Special Offer On 4 Special "Specials"!

On a time limited basis you can build a library of Electronics Today all time best projects for the beginner to the more advanced builder at a very special price.

Retail value of the 4 Specials shown totals \$16.80. Order now (cheque or credit details must accompany order) and you receive all four for just \$12.00 plus \$1.00 for postage and handling.

Write today to Moorshead Publications, Suite 601, 25 Overlea Blvd., Toronto, Ontario M4H 1B1.

To expedite your order call (416) 423-3262 with credit card details.

EXCELTRONIX (416) 921-8941

Bulletin Bd. (416) 921-4013 Telex 065-24218
319 College St., Toronto, Ont. M5T 1S2

Toll-Free Number:
1-800-268-3798

The "BEST"

IBM Compatible Microcomputer

See the Review
In March 1984
Computing Now!

\$1995

Not a kit — a complete system



This price includes:

- 64K of RAM with pre-socketed provision for 256K
- One disk drive. SA455. Double Sided. Double Density
- Colour Video Board
- Floppy controller capable of handling up to four DS, DD 5 1/4" disk drives and socketed for optional serial port and real time clock
- Monitor not included

Warranty:
Full 120 day
Warranty

Prices does NOT include
IBM (Microsoft) BASIC

OR The Loaded "BEST"

Everything in our \$1995 System plus:

- Two DS, DD 5 1/4" Disk Drives
- On-board 256K of RAM
- RS232 Port

\$2595

OR 10 Meg Hard Disk Version

Everything in our \$1995 system plus:

- 10 Meg Hard Disk Drive & Controller
- On-board 256K of RAM
- RS232 Port

\$3995

SOFTWARE FOR YOUR IBM

- Lotus 1, 2, 3 \$439
- Wordstar \$399
- Multiplan \$219
- dBASE II \$479
- Flight Simulator \$62.95

Great Selection of other software for your IBM available.

IBM is a Trade Mark of IBM Canada Limited

PERIPHERALS FOR YOUR IBM

- Color Video Board \$339
- Floppy Controller Board \$299
Has provision optional RS232 port and real time clock.
- Parallel and Game Port Card \$149
Will also drive parallel printer
- 256K Memory Expansion Card and real time clock. Allows you to add a further 256K to your IBM's existing 256K capacity for 1/2 Megabyte of total memory.
- With 64K RAM on board \$289
- With 128K RAM on board \$369
- With full 256K RAM on board \$530
- EPROM Programmer \$149
For 2732, 2769 and 27128.
- Disk Drive - SA4555 \$299
- IBM Compatible Case \$ 99
- IBM Compatible Keyboard \$189
- Super Heavy Duty Power Supply \$ 69

See our other ads for monitors, printers etc.,

Mail Order: Call for shipping costs. Rate will depend on methods chosen and distance.

Call our TOLL-FREE number for more information.

1-800 268-3798

(Toronto area call 921-8941)

Call in and let us demonstrate the "BEST" to you at 319 College Street, Toronto. Store hours 9:30 to 6:00 Monday-Saturday; to 9:00 p.m. Thursday and Friday.