

Electronics Today

INTERNATIONAL

February 1982

\$1.95
MM70924

The Magazine for
Electronics & Computing
Enthusiasts

Sound Bender



A Ring-modulator
for your Guitar

Enlarger Timer



A Project for
the Darkroom

A Touch of Class


The ABC of
Amplifier
Classification

Flash Sequencer



Special Effects
for the
Photographer

circuits

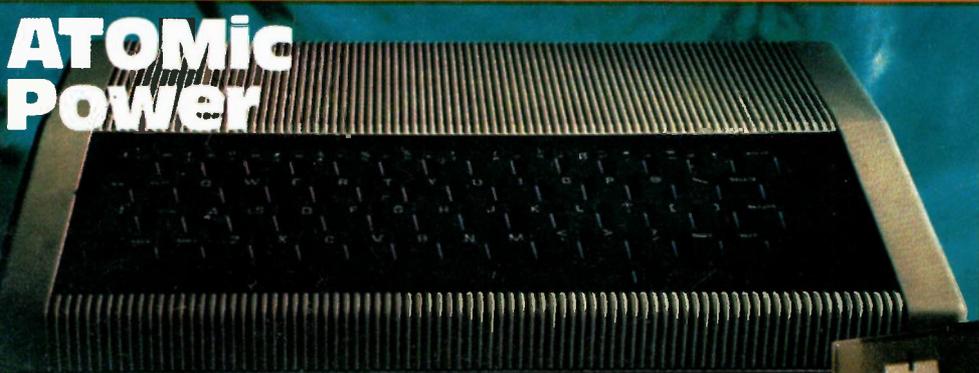

Industrial Robots



What you should know about the Multiflex Z80A computer


Exceltronix
Component & Computing Inc.

MULTIFLEX is a young, fast-growing Canadian computer company. Most people have only just heard of us within the past year, because previous to that we were involved in intensive, low-profile research and development.

THE Z80A SYSTEM was developed over a two-year period. The company's intent was to produce a computer suitable for both hobbyists and industry, capable of functioning as a stand-alone trainer yet infinitely expandable. That goal has been attained, with the added benefit of a very low price.

STAND-ALONE FEATURES Selected for maximum usefulness and lowest cost, include the following:

- Separate motherboard and CPU card**, which communicate over the industry-standard S-100 bus. The motherboard can accommodate up to four S-100 cards.
- Space on the CPU card** for up to 4K of RAM and up to 16K of EPROM. The RAM is organized as two blocks of 2K bytes each, (200 nS 2114 devices are used) which can be located within any 2K block in the address-space by hardware jumpers. An 8K or 16K block size may be selected for the EPROMs and this, too, may be located at any address. 2708 and 2716 devices may be used exclusively or in combinations.
- A resident 3.5K Monitor** which facilitates machine-language program entry, execution and debugging, and controls all input/output hardware on the motherboard. The Monitor is in two 2716 EPROMs which may be removed and re-used if the user wishes to implement a more powerful operating system.
- A hex keyboard**, fourteen Monitor function keys, and two unassigned keys for user routines.
- A six-digit hex LED display** organized as a four-digit address field and a two-digit data field.
- An interface** to a conventional cassette recorder, which sends and receives data at 2000 bits per second with exceptional reliability. The Monitor includes a special routine which simplifies precise calibration of the recorder and interface.
- An EPROM programmer** for 2708 and 2716 devices. The contents of any block of system memory may be written out to EPROM, and programmed EPROMs may also be read into RAM through the programming socket for duplication. Many industrial buyers have used Multiflex Z80A systems just to download data from larger computers, to be programmed into EPROMs.
- A parallel interface** based on the 8255 PPI chip. Twenty-four I/O lines are available, which can be programmed in several configurations.

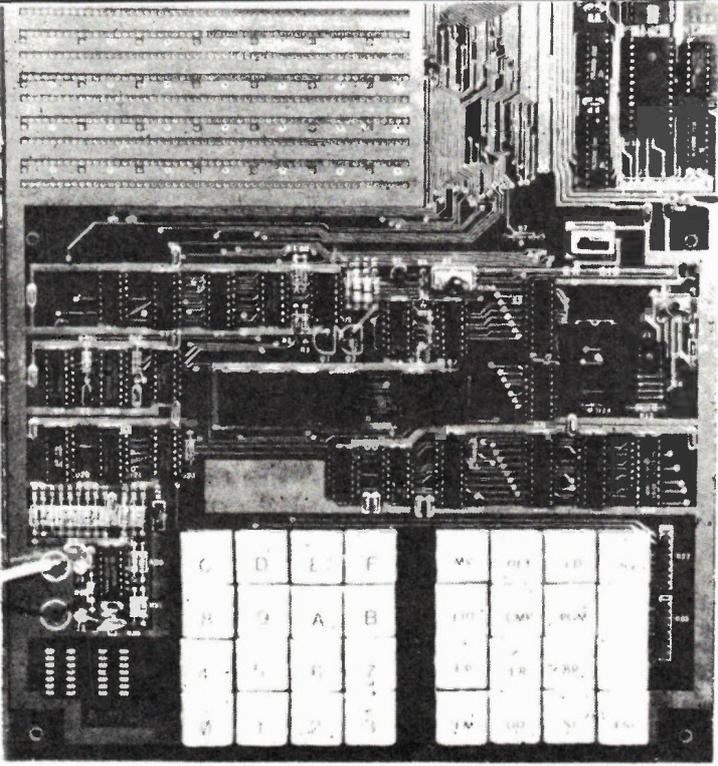

Read the independent review of this product in ETI May 1981.

- An optional RS-232C serial interface**, already wired on the motherboard. The components for this may be purchased and installed at any time, allowing communication with a modem, printer, or other device using the RS-232C standard. Eight jumper-selectable baud rates are available, from 110 to 9600 baud.
- A 40-chip wire-wrap area** on the motherboard for custom hardware development or modifications. The wire-wrap plane is centrally located for easy access to bus signals and all I/O hardware.

\$375. in kit form.
\$450. Assembled & tested.

EXPANDABILITY is assured by the use of the S-100 bus system. Almost any product, made by any manufacturer for use with S-100 computer systems, may be used with the Multiflex Z80A. Also, all bus signals are heavily buffered in the Multiflex computer, to facilitate expansion to many extra boards. Multiflex is now developing an entire line of support products designed specifically for the Z80A. These include:

- A 64K dynamic memory board** with automatic refresh, based on the Intel 8202 Dynamic Memory Controller chip. Each board may be loaded with 16K, 32K, 48K or 64K of 4116 RAM devices, and up to eight full boards may be used on the same bus because of the bank-select feature.
- A low-cost video board** for displaying text on an ordinary black-and-white television set, with an interface to a standard ASCII keyboard.
- A high-resolution colour text/graphics board** and I/O subsystem, based on the Motorola 6847 Video Display

Controller. The video circuitry offers eight display modes and can be interfaced to a standard ASCII keyboard. The I/O section includes two 8255 PPI chips for up to 48 bits of parallel I/O, an 8253 programmable real-time clock, a fully handshaked RS-232C interface with baud rate programmable through the 8253, and up to 6K of static RAM. The board may be used with any colour television set, because a complete RF modulator is provided on-board.

An EPROM emulator for use in the development of stand-alone microprocessor systems. This board appears to a host computer as ordinary RAM on the S-100 bus, but to an external device connected to it by a 24-pin DIP jumper, it completely simulates a 2716 or 2732 EPROM.

A bipolar PROM programmer which connects directly to the EPROM programming socket of the Z80A system. This board and the software package sold with it, are capable of programming all of the popular Schottky PROMs.

All of the above-mentioned products except the PROM programmer may be interfaced to any S-100 computer, regardless of manufacturer.

SEND FOR OUR FREE CATALOGUE

SPECIAL THIS MONTH
EXTRA 3K OF MEMORY
IN BASIC
PRICE EXPIRES
FEB. 28TH 1982



MAIL ORDERS
Send a certified cheque or money order (do not send cash). Minimum order is \$10 plus \$3 for shipping. Ontario residents must add 7% provincial sales tax. Visa and Mastercard accepted: send card No., signature, expiry date and name of bank.

PRICE POLICY
Remember that at Exceltronix, all prices are negotiable for quantity purchases. If you cannot afford large quantities on your own, how about starting a Co-op.



319 COLLEGE STREET, TORONTO, ONTARIO, CANADA, M5T 1S2 (416) 921-5295
ALL PRICES ARE IN CANADIAN FUNDS. 9% FEDERAL SALES TAX INCLUDED

Circle No. 7 on Reader Service Card.

DON'T HESITATE TO CONTACT US
ON OUR PRICE HOTLINE
921-4114 FOR THE MOST
COMPETITIVE PRICES IN
CANADA!

**YOU CAN'T BEAT
THE BEST!**

6809 SINGLE BOARD COMPUTER

We are pleased to announce the arrival of this versatile new computer, which is extensively used by the University of Toronto for teaching purposes. Among its standard features are: 16K of RAM memory (expandable to 48K on board), 2 serial ports, 2 6522 parallel ports, a cassette interface, and an extremely powerful monitor. This month we are offering this state-of-the-art computer, with an extra 16K of RAM (32K in total), in kit form for the special price of

Kit Price **\$460**
Assembled **\$660**

MEMORY SUPER SPECIALS

very good stock

- 4164-150ns 13.95
(1 x 64K single (+5V) supply)
- 4116-150ns (1x16k) 2.79
- 4116-200ns (1x16k) 2.50
- 4116-300ns (1x16k) 1.69
- 2114L-200ns low power 2.95
- TMM 2016 (2k x 8 static RAM) 13.95
- NOTE: 1 of these can do the job of 4 2114's but uses only one 24 pin socket
- 6116 (2k x 8) 14.95
(same as above but CMOS)
- 2102 CFPC 1.57
- 5101 CMOS 3.85
- 2708 EPROM (1k) 4.25
- 2716 EPROM (2k) 6.35
- 2732 EPROM (4k) 11.99
- 2532 EPROM (4k) 14.95
- 2764 EPROM 89.00

FOR QUANTITY PRICES CONTACT US FOR REALLY SUPER PRICES

Rockwell AIM-65 Computer \$635

Good stock of Aardvark software available at super prices
Ohio Scientific SUPERBOARD II with 8K of memory only **\$439⁰⁰**
RF Modulator kit only \$8.95 extra



64K Memory board
Using 4164s, 150ns, dynamic RAMS requiring only single +5V
Kit price **\$249.00**



SPECIAL ON FLOPPY CONTROLLERS
1771B **\$17.95**
1791B **\$58.95**
1795B **\$79.50**

GOOD STOCK ON MICROPROCESSORS AND SUPPORT SPECIALS

1802	\$13.50	6502 CPU	8.95	8228	5.00
1822	8.50	8504 CPU	8.95	8251	5.00
1824	4.00	6505	3.25	8253	7.99
1852	2.50	8520	8.99	8256	5.00
1853	1.80	6522	8.99	8257	8.75
		6532	13.50	8259	8.89
6800	5.89	6551	13.95		
6802	8.75			Z80A CPU	7.95
6809	21.95	8080A CPU	4.99	Z80A PIO	8.75
6810	3.39	8085 CPU	6.99	Z80A CTC	8.50
6820	3.95	8212	2.10	Z80A DMA	19.75
6821	3.35	8214	3.75	Z80A SIA1	26.75
6845	17.99	8216	2.10	Z80A SIOF2	36.95
6850	3.39	8224	3.75	Z80A SIOF9	21.50
6852	3.37	8226	2.10	Z80A DART	16.75

Hameg Oscilloscopes

The specials continue on German-made Hameg scopes:
model reg. sale price
HM307 \$550.00 \$495.00
HM312 \$855.00 \$769.00
HM412 \$1277.00 \$1149.00
HM512 \$2000.00 \$1795.00

Floppy Disk Drives

10% OFF ON ANY 2 DRIVES

- CDC 9406 \$650**
— Double sided, single or double density 8" floppy drive— hard or soft-sectored
Shugart
- SA400 \$390**
— Single sided, single or double density 5 1/4" floppy drive
— Soft or hard sectored
- SA450 \$580**
— All the features of the SA400 (above) except double sided
- SA801R \$685**
— Single sided, single or double density 8" floppy drive
— Hard or soft-sectored
— Designed for side-by-side mounting of two drives in a standard 19-inch rack
- SA851R \$950**
— All the features of the SA801R (above) but double sided



SAVE ... now we have an Interface making the SA400 disk drives fully compatible with your Apple II
Contact us for more information.



SALE CONTACT US FOR BEST PRICES ON SD SYSTEMS AND SSM PRODUCTS

ZENITH MONITORS COMPLETE WITH HOUSING AND POWER SUPPLY READY-TO-USE WITH ANY COMPOSITE VIDEO SIGNAL 12" GREEN PHOSPHORUS SCREEN SWITCH SELECTABLE FOR 40 OR 80 CHARACTERS
SALE PRICE \$185.00

S100 Back Plane with 7 slots \$25.00
(S100 connectors extra \$5.00 each)
S100 Back Plane with active termination 13 slots .. \$48.50
(Signal line isolation)
S100 Prototyping Board — \$34.95

Apple II + with 48K
This month only **\$1779.00**
Apple drive with controller **\$785.00**

Centronics Printers
730-1 **\$945.00**
730-3 Serial interface **979.00**
739-1 Parallel .. **1195.00**
EPSON MX80... **819.00**



PRICE POLICY
Remember that at Exceltronix, all prices are negotiable for quantity purchases. If you cannot afford large quantities on your own, how about starting a Co-op.

MAIL ORDERS
Send a certified cheque or money order (do not send cash). Minimum order is \$10 plus \$3 for shipping. Ontario residents must add 7% provincial sales tax. Visa and Mastercard accepted. send card No., signature, expiry date and name of bank.

319 COLLEGE STREET, TORONTO, ONTARIO, CANADA, M5T 1S2 (416) 921-5295
ALL PRICES ARE IN CANADIAN FUNDS, 9% FEDERAL SALES TAX INCLUDED

Circle no. 5 on Reader Service Card.

Electronics Today International
 Editorial and Advertising Offices
 Unit 6, 25 Overlea Boulevard,
 Toronto, Ontario, M4H 1B1
 Telephone (416) 423-3262

Publisher and Editor
 HALVOR W. MOORSHEAD

Assistant Editor
 STEVE RIMMER

Advertising Manager

SENGA HARRISON

Advertising Services

CAROLYN WYATT

Subscription Department

BEBE LALL

NADIA MARAR

Accounts Department

NANCY ALLEN

Art Director

TERRY FLETCHER

Production

CINDY BAKER



INTERNATIONAL EDITIONS
 Electronics Today International,
 145 Charing Cross Road,
 London WC2H 0EE, UK

Electronics Today International,
 Rylee House, 15 Boundary Street,
 Rushcutters Bay, Sydney, Australia

Eirad
 Kommanditgesellschaft, Bissendorfer
 Strasse 8, 3000 Hannover 61, Germany

Electronica Top Internationaal
 Postbus 93, Bilthoven, Holland

ETI Magazine is Published by:

Electronics Today International (Canada) Limited

Newsstand Distribution: Master Media, Oakville,
 Ontario

SUBSCRIPTIONS

\$16.95 (one year), \$29.95 (two years). For US
 add \$3/yr., other countries add \$5/yr. Please
 specify if subscription is new or a renewal.

BACK ISSUES AND PHOTOCOPIES

Previous issues of ETI Canada are
 available direct from our offices for
 \$3.00 each; please specify by month, not by
 feature you require. See order card
 for issues available.

We can supply photocopies of any article
 published in ETI Canada; the charge is
 \$2.00 per article, regardless of length. Please
 specify both issue and article.

POSTAL INFORMATION

Second Class Mail Registration No.3955.
 Mailing address for subscription orders, undeliverable
 copies and change
 of address notice is:
 Electronics Today International, Unit 6,
 25 Overlea Blvd., Toronto,
 Ontario, M4H 1B1.

COPYRIGHT

All material is subject to worldwide copyright protec-
 tion. All PCB patterns are copyright and no company
 can sell boards to our design without our permission.

LIABILITY

While every effort has been made to ensure that all
 constructional projects referred to in this magazine
 will operate as indicated efficiently and properly and
 that all necessary components are available, no
 responsibility whatsoever is accepted in respect of the
 failure for any reason at all of the project to operate
 efficiently or at all whether due to any fault in the
 design or otherwise and no responsibility is accepted
 for the failure to obtain component parts in respect of
 any such project. Further no responsibility is accepted
 in respect of any injury or damage caused by any fault
 in design of any such project as aforesaid.

Electronics Today

INTERNATIONAL

FEBRUARY 1982 Vol. 6 No. 2

Features

50 Circuits 10
 Half a hundred small projects to
 try, each devised by circuit wizard
 Tim Orr. Build them all and wind up
 very short of solder.

ATOMIC Power 29
 The operating system of the Acorn
 ATOM unveiled. Steve Rimmer
 POKEs beneath the case of this power-
 ful little machine.




Signs 35
 While not exactly a breakthrough
 in flat screen technology, Versa-
 Digital's LED matrix sign display
 represents an unusual application
 of state of the art technology. By
 Steve Rimmer.

POKEing the ZX-80 36
 More marvelous memory modifica-
 tions for this splendid little
 machine. Also included is a short
 program to try.

Industrial Robots 38
 Far from being relegated to
 1960's science fiction flicks,
 robots are very much a thing of the
 present. They are doing a lot of the
 work that humans would rather
 avoid, as Roger Allan explains.


Amplifier Class 61
 Unless you've got one of those
 Distort-o-phone Stereos with a
 speaker in the lid, your amp has
 some kind of class. Wally Parsons
 explains why.

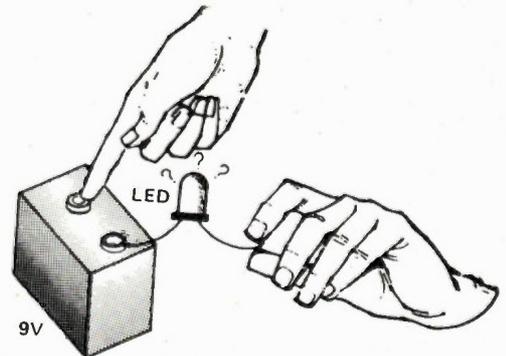dbx 64
 The astounding part about dbx is
 what you don't hear; plug in a
 dynamic range expander and all
 your tape noise vanishes. The
 secret of silence, by Peter Green.




Can enough current pass through your fingers to light an LED?

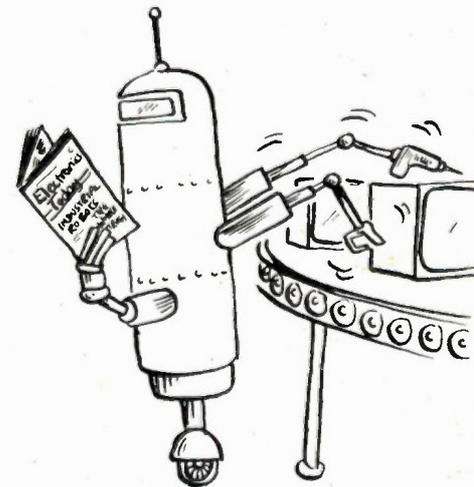Into Linear ICs 69
 This month, Ian Sinclair deals with
 the 741 op amp, crafting it into a
 number of illustrative circuits.



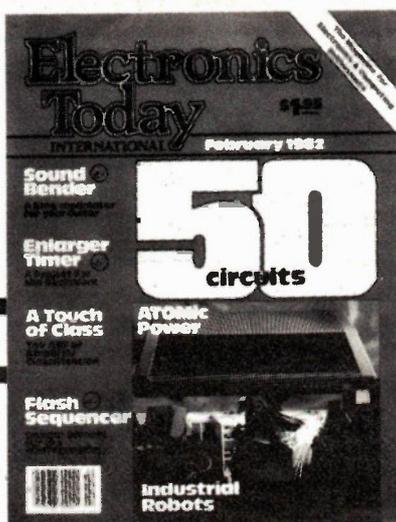Short Wave Aerials 66
 A well designed aerial is almost as
 good as being there. . . better if
 "there" is under attack.



Our Cover: Fifty circuits, each one certain to be more useful than either a digital water clock or a four slice, pop up salad drier, page 10

ISSN 0703-8984

Projects



Flash Sequencer 23

Yes, you can hook nine flash units up to this thing for exciting stop action photography. Locating nine flashes is entirely up to you.




Enlarger Timer 59

This little project will precisely time the exposure of any print for up to four minutes and fifteen seconds. Something to bring joy to the heart of any photographer.



Sound Bender 75

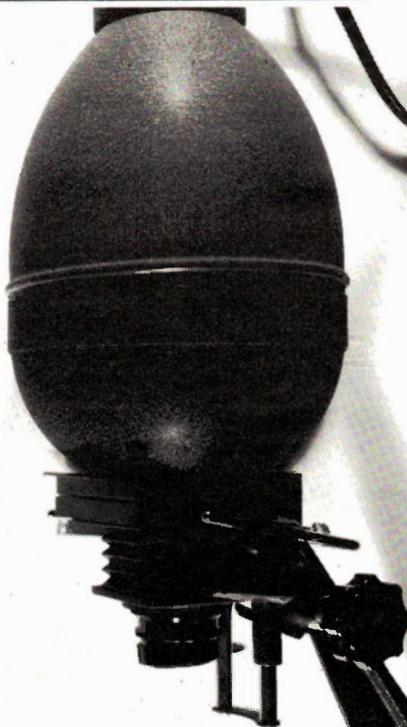Make your guitar sound like a cathedral bell, a gong, or any of a number of percussive chimes with this amazing effect.



Columns, News and Information

News	7
Next Month in ETI	26
Order Form	27
Subscriptions	28
Fun of Electronics	32
Reader Service Card	48
Books From ETI	52
Computing Today	55
Binders	74

Aaron-Gavin	78
Active Component Sales Corp ..	47
Active Surplus Annex	45
Audiovision	73
BCS Electronics	74
Classified	77
Electronic Packaging Systems ..	37
Electronics 2001	73
Exceltronix	2,3
General Electronics	45
Gladstone	
Electronics Centre Section	
Hammond Manufacturing	45
International School	
of Electronics	34
Len Finkler Limited	73
McGraw-Hill	33
Metermaster	8
Mode	79
Nu West Video Systems Ltd	37
Omnitronix	37
Orion Electronic Supplies	6
R-A-E Industrial	
Electronics Ltd	37
H. Rogers Electronic	
Instruments	6
Selco Electronics	73
Torch International	
Computers Ltd	80

Editorial Queries

Written queries can only be answered when accompanied by a self-addressed, stamped envelope. These must relate to recent articles and not involve the staff in any research. Mark such letters ETI-Query. We cannot answer telephone queries.

Binders

Binders made especially for ETI are available for \$6.75 including postage and handling. Ontario residents please add provincial sales tax.

Sell ETI and ETI Special Publications

ETI is available for resale by component stores. We can offer a good discount when the minimum order of 15 copies is placed. Readers having trouble in obtaining the magazine could ask their local electronics store to stock the magazine.

Component Notation and Units

We normally specify components using an international standard. Many readers will be unfamiliar with this but it's simple, less likely to lead to error and will be widely used everywhere sooner or later. ETI has opted for sooner!

Firstly decimal points are dropped and substituted with the multiplier; thus 4.7uF is written 4u7. Capacitors also use the multiplier nano (one nanofarad is 1000pF). Thus 0.1uF is 100nF, 5600pF is 5n6. Other examples are 5.6pF = 5p6 and 0.5pF = 0p5.

Resistors are treated similarly: 1.8Mohms is 1M8, 56kohms is the same, 4.7kohms is 4k7, 100ohms is 100R and 5.60ohms is 5R6.

PCB Suppliers

ETI magazine does NOT supply PCBs or kits but we do issue manufacturing permits for companies to manufacture boards and kits to our designs. Contact the following companies when ordering boards.

Please note we do not keep track of what is available from who so please don't contact us for information on PCBs and kits. Similarly do not ask PCB suppliers for help with projects.

K.S.K. Associates, P.O. Box 54, Morriston, Ont. N0B 2C0.

B&R Electronics, P.O. Box 6326F, Hamilton, Ont., L9C 6L9.

Wentworth Electronics, R.R.No.1, Waterdown, Ont., L0R 2H0.

Danocinths Inc., P.O. Box 261, Westland MI 48185, USA.

Arkon Electronics Ltd., 409 Queen Street W., Toronto, Ont., M5V 2A5.

A-1 Electronics, 5062 Dundas Street W., Islington, Ont., M9A 1B9.

Beyer & Martin Electronic Ltd., 2 Jodi Ave., Unit C, Downsview, Ontario M3N 1H1.

Spectrum Electronics, Box 4166, Stn 'D', Hamilton, Ontario L8V 4L5.

ORION

Electronic Supplies Inc.

ELECTRONIC DISTRIBUTOR
INDUSTRIAL — EDUCATIONAL — COMMERCIAL — HOBBYIST

START WITH ORION FOR
A NEW ERA IN THE WORLD
OF ELECTRONICS
We have the most complete selection
of electronic components.

Full line of TTL, CMOS, Linear,
ICs, Computer Interface, Support Chips
and CPUs.

INTERACT COMPUTER
16K LEVEL II



Just
\$595.

Write for our
flyer on Interact
Computer

A powerful microcomputer with a full standard 53 key typewriter style keyboard and built-in cassette recorder for use in entering and storing programs. Utilizing the versatile Intel 8080A microprocessor, the Interact computer has 16K of RAM and 2K of ROM at its disposal. Output is in color on your own TV screen. Sound is also generated through your TV set and can consist of exhilarating computer beeps or two full octaves of music. This is truly a powerful computer capable of developing and handling a variety of programs, and with available software provides true educational stimulus (examples: Star Track, Chess, Concentration, etc.). The Interact computer offers the ideal opportunity to learn BASIC, the most popular computer language for small business and hobbyists, and with the use of the 84 page manual, you learn at your own pace.

INSTALLATION: Attach to antenna terminals of your color TV set and plug into 120 VAC wall outlet. Computer includes built-in RF modulator, FCC approved and UL and CSA listed.

PROGRAMMING: Most micro-computers start you off with an abbreviated 4K BASIC, and then later you have to relearn the more powerful language. Since this computer has 16K of RAM, we start you with Level II Microsoft 4.7 BASIC. BASIC is the most popular micro-computer language using commands that are words we are ordinarily used to: such as, PRINT, NEW, GOTO (For go to), END, COLOR, JOY, INPUT, etc. To help you learn programming we have included an 84 page instruction manual, plus a 20 page book of program examples.

Educational and Entertaining

ASCII Keyboard Fully encoded, 128-character ASCII alphanumeric keyboard, 58 light touch keys (2 user defined), Selectable "Upper-Case-Only" **\$109.75**



VP-601

ASCII/Numeric Keyboard ASCII Keyboard identical to VP-601, plus 16 key numeric entry keyboard for **\$149.75**

VP-611

Cable: ASCII Keyboards to VP-711 Flat ribbon cable, 24 in. length, 101 connecting VP-601 or VP-611 and VP-711. Includes matching connector on both ends. **\$27.50**


VP-620

Cable: ASCII Keyboards Flat ribbon cable, 36 in. length with mating connector for VP-601 or VP-611 Keyboards. Other end is unterminated. **\$27.50**

VP-623



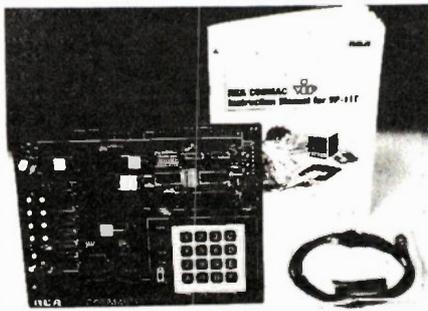Authorized distributor for RCA, COSMAC, VIP



New! VP 111
Microcomputer... **\$139.50**

Features

- RCA 1802 Microprocessor
- 1K Bytes static RAM
- Expandable on-board to 4K
- Expandable to 32K Bytes total
- 512 Byte ROM operating system
- CHIP-5 interpretive language or machine language programmable
- Hexadecimal keypad
- Audio tone generator
- Single 5-volt operation

Assembled* and tested.

- Video output to monitor or modulator
- Cassette interface — 100 Bytes/sec.
- Instruction Manual with 5 video game listings, schematics, CHIP-8, much more
- Ideal for low-cost control applications
- Expandable to full VIP capability with VP-114 Kit.

*User need only connect cables (included) a 5-volt power supply, and speaker.

The ZX81 \$149.95 Personal Computer Kit **NEW**

The ZX81's advanced capability.

The ZX81 uses the same fast microprocessor (Z80A), but incorporates a new, more powerful 8K BASIC ROM — the "trained intelligence" of the computer. This chip works in decimals, handles logs and trig, allows you to plot graphs, and builds up animated displays. And the ZX81 incorporates other operation refinements — the facility to load and save named programs on cassette, or to select a program off a cassette through the keyboard.

New, improved specification.

*Unique "one-touch" key word entry: eliminates a great deal of tiresome typing. Key words (PRINT, LIST, RUN, etc.) have their own single-key entry. *Unique syntax-check and report codes identify programming errors immediately. *Full range of mathematical and scientific functions accurate

to eight decimal places.

*Graph-drawing and animated-display facilities. *Multi-dimensional string and numeric arrays. *Up to 26 FOR/NEXT loops. *Randomize function. *Programmable in machine code. *Cassette LOAD and SAVE with named programs. *1K-byte RAM expandable to 16K. *Full editing facilities. *Able to drive the new Sinclair ZX Printer (to be available shortly).

If you own a ZX80...

The new 8K BASIC ROM as used in the ZX81 is available as a drop-in replacement chip. (Complete with new keyboard template and operating manual). With the exception of animated graphics, all the advanced features of the ZX81 are now available on your ZX80 — including the ability to drive the Sinclair ZX Printer.

Circle No. 6 on Reader Service Card.

Orion Electronic Supplies Inc.


40 Lancaster Street West
Kitchener, Ontario N2H 4S9
(519) 576-9902

Master Charge & Visa, COD, Cheque,
Money Orders accepted. CODs, shipping
& insurance extra. Write for our FREE
catalogue!



LX304 digital multimeter with automatic decimal point, built in low battery indicator and transistor testing capability. **\$129.00**

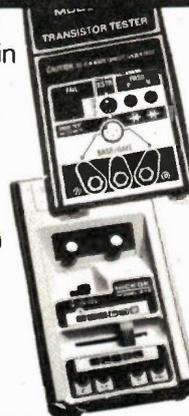LX303 digital multimeter with easy-to-read LCD display. Only **\$110.00**



Model 216 Transistor Tester with fast, automatic switching for instant good-bad analysis of NPN's, PNP's, FET's, diodes and SCR's in or out of circuit. **\$165.00**

Model 240 Video Generator with 10 step gray scale staircase for VTR, CCTV monitor and TV applications. **\$215.00**

HICKOK
the value innovator

ROGERS electronic instruments Ltd.

P.O. Box 310, 595 Mackenzie Ave. Units 1&2
Ajax, Ontario L1S 3C5. Tel. (416) 683-4211

Duty and FST included. ChargeX (Visa) accepted.
Ontario residents add 7% sales tax. Shipping extra.

FOR THOSE
ON THE GO
FROM...

HICKOK
the value innovator


ROGERS electronic instruments Ltd.

Your Toolbox Test Bench

Circle No. 1 on Reader Service Card.

ETI—February 1982

News

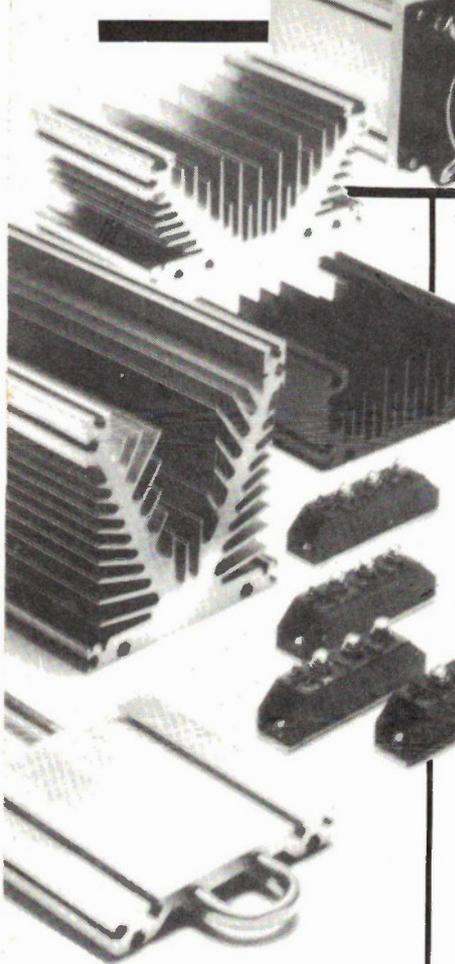

Power Module Coolers

Designed specifically for power module cooling applications, EG&G Wakefield Engineering announces the availability of a new family of heat sinks for cooling power modules. Four aluminum extrusions, three air-cooled and one liquid-cooled, use industry standardized spacing and mounting configurations to offer a versatile approach to power module related cooling tasks.

Three different lengths are available for each series of both the air- and liquid-cooled heat sinks. Single high power or combinations of lower power devices may be mounted on a single heat sink. In addition to the individual extrusions, kits are available, which convert three of them into confined, forced convection systems to further increase their power handling capabilities.

Additional information on these new extrusions may be obtained by contacting Melvin Tracey at EG&G Wakefield Engineering, 60 Audubon Road, Wakefield, MA 01880, telephone (617) 245-5900.

Transducer Pressure Sensors

Motorola has announced two new silicon piezoresistive pressure sensors designed for medical, automotive and industrial applications. The "X-ducer"™ pressure sensor elements are the MPX50D — 0 to 50 kPa (0 to 7.3 PSI) pressure range, and the MPX200A — 0 to 200 kPa (0 to 29 PSI) pressure range. A or D refers to absolute or differential pressure types.

The MPX50D has an unconditioned output of up to 100mV (@ 5V excitation). It is particularly useful for medical applications such as bloodpressure measurement, although it is also suitable for environment and industrial controls. It is sensitive enough for

measurement of inches of water column. Overpressure capability is 200 kPa (29 PSI). The new part is also available as a temperature compensated and signal-conditioned "gauge" sensor.

The MPX200A is an absolute pressure transducer having an operating pressure range from 0 to 200 kPa (0 to 30 PSI), 100% overpressure capability and typical linearity of $\pm 0.05\%$ full scale. This device is especially suited to automotive uses in turbo-chargers, as well as many other industrial applications requiring good repeatability over a broad pressure range. The device is also available as a signal-conditioned and temperature-compensated sensor module, the MPX200MA.

Motorola has also designed a universal receptacle for quick connection to 1/8" diameter or 1/16" diameter hoses. This pressure "port" fitting permits printed circuit board, chassis, and panel mounting. The hose fitting is barbed to prevent hose ejection due to pressure changes. The pressure port is supplied with metal rivets to secure the package for reliable chassis type mounting, and long term protection against vibration. The universal feature of the port fitting allows the MPX50D to be used as a gauge, vacuum gauge, or true differential sensor. A double-port fitting is used in applications where a true differential pressure reading is required.

The output signal is directly compatible with most microprocessor inputs and the part has virtually no "popcorn" noise.

Prices, including the optional new single and double hose ports, are:

Device	1-24
MPX50D	\$26.00
MPX200A	\$26.00

All parts are now in inventory and are available through the factory and authorized Motorola distributors.

Versatile Instrumentation Peripheral

Automated Control Systems has announced a multifunction S100 card that supports both analog and digital I/O. The V.I.P.—Versatile Instrumentation Peripheral enables the designer of S100-based process control or data acquisition systems to save card cage space and money. It combines 12-bit analog and high current, high voltage digital I/O, functions which previously required up to three card slots. Two dual utility relays are also included.

The analog portion is software configurable. It includes the following four elements:

1. An instrumentation amplifier input with resistor programmable gains from .1 to 1000.

2. An analog gain block with trimmer adjustable offset.

3. A 12-bit A/D converter offering 25 micro-second conversion time and software selectable input ranges.

4. A 12-bit multiplying D/A converter with simultaneous voltage and current source outputs, double buffered for signal synthesis capabilities.

These functions can be variously configured, offering maximum versatility. The board is capable of self-check as well as parametric measurement.

The digital features include 8 TTL inputs and 48 TTL-compatible 30-volt, 100 mA open collector outputs. Selectable ROM decoding allows BCD programming of 5 digits of 7 segment LED displays. The board occupies 16 contiguous read and write I/O locations and offers switch selectable addressing. There are full Z80 interrupt and WAIT state capabilities.

Additionally, the V.I.P. has two uncommitted dual utility relays that can be used for multiplexing and other switching. A small IC patch area allows further customization.

The V.I.P. is ideal for use in stand alone instrumentation as a system "housekeeper" card, combining the functions of an LED display controller, utility volt meter, voltage and current sources, parametric measurement system, utility relays, and front panel interface. The V.I.P. can also be used as a component of industrial and scientific data acquisition and process control systems.

For more information contact Automated Control Systems, 1105 Broadway, Somerville, MA 02144, telephone (617) 628-5373.

Demand for ZX81 outstrips supply


When the history of the microcomputer is written, the ZX81 is going to deserve a prominent mention: it could well be the watershed for introducing computers into the home.

From the first day it was launched in Britain, sales have been at 1000 units a day and worldwide sales in October are reported at 40,000!

The demand has quite outstripped supply. Gladstone Electronics, who import the ZX81 direct from Britain placed the first order from North America but still have an enormous backlog of orders. "We've managed to keep the good will of most of those ordering by being totally honest about the supply situation," said Howard Gladstone. "We feel bad about customers who have been waiting now up to 2½ months but there's nothing we can do. People are being remarkably patient and they do understand that they'll all be supplied in order. We're hoping that the situation will be much better by the time your readers see their February issue of ETI".


A printer for these computers is now on sale in Britain and is expected to be available in North America in the near future.

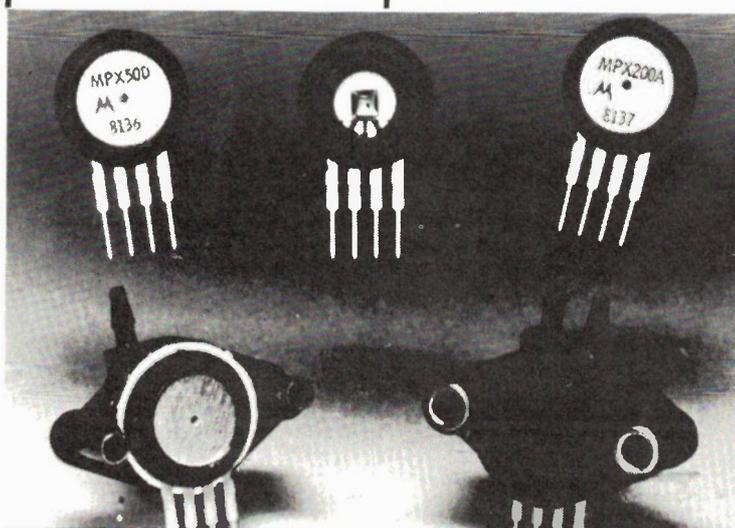For the complete inner workings of the ZX81, see the review in next month's ETI.




OSCILLOSCOPES!


The Best Buys Available

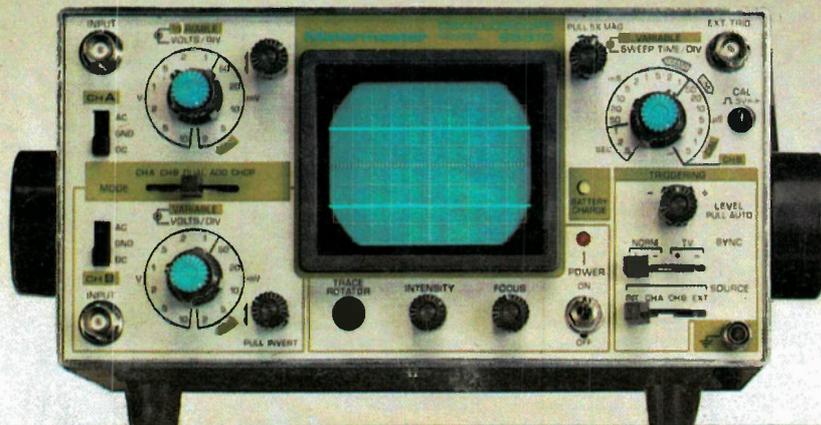

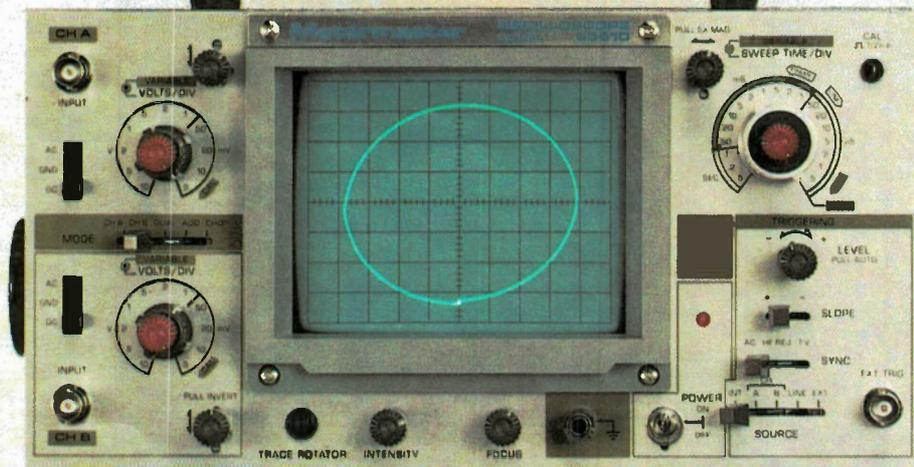- Model 65310**
Dual Trace Portable
- ▶ 15MHz (-3dB) Bandwidth
 - ▶ X5 Sweep Magnifier
 - ▶ Battery, 12VDC & AC Operation
 - ▶ 2mV Vertical Sensitivity
 - ▶ Trace Rotator
 - ▶ Price \$775.00 taxes not included



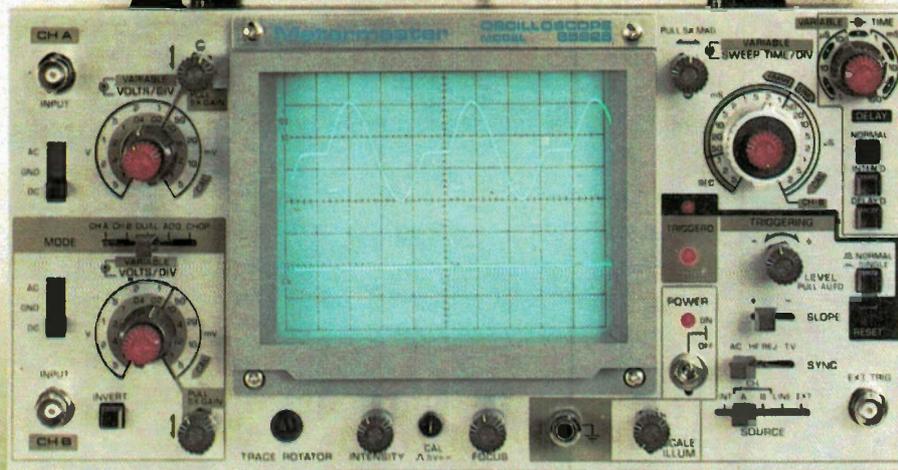- Model 65610**
Dual Trace Bench
- ▶ 15MHz (-3dB) Bandwidth
 - ▶ 5" CRT Display
 - ▶ 120VAC & 12VDC Operation
 - ▶ Fully Automatic Triggering
 - ▶ Trace Rotator
 - ▶ 5mV Vertical Sensitivity
 - ▶ HF Rejection
 - ▶ Price \$795.00 taxes not included



- Model 65625**
Dual Trace Bench
- ▶ 45MHz (-3dB) Bandwidth
 - ▶ Delayed Sweep (selectable)
 - ▶ Single Sweep (selectable)
 - ▶ Extremely Bright 5" CRT
 - ▶ Illuminated Internal Graticule
 - ▶ Optimal Sensitivity of 1mV
 - ▶ X-Y or X-Y-Z Operation
 - ▶ 120VAC Line Operation
 - ▶ Price \$1630.00 taxes not included


Metermaster
R.H. NICHOLS



All prices F.O.B.
 Downsview, Ontario
 subject to change with-
 out notice. P.S.T. extra
 where applicable.

Head Office: 214 Dolomite Drive, Downsview, Ontario M3J 2P8
 TORONTO (416)661-3190 • MONTREAL (514)337-0425 • EDMONTON (403)432-7746 • OTTAWA (613)238-7007

Circle No. 11 on Reader Service Card.

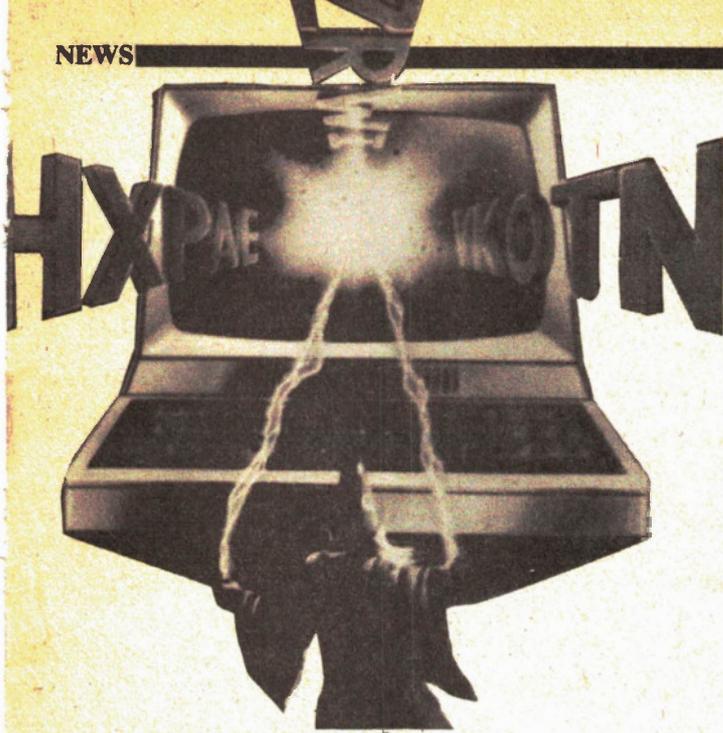

Introduction to Word Processing

Introduction to Word Processing by Hal Glatzer has just been released by Sybex. No longer a luxury reserved for the corporate environment, affordable word processing is now accessible to the personal user. This book is the first of its kind to explain in non-technical language what word processing is and why and how using it can increase personal productivity. The author presents an easy, step-by-step guide on how to use a word processor and provides a complete, feature-by-feature comparative analysis of currently available equipment for anyone considering buying a system.

Why process words? Why not just type? A typewriter — even the best — can only perform one job: convert keystrokes into letters on paper. But a word processor is a computer. With memory, the word processor can not only automatically type faster than any human, but also edit and correct spelling errors. For executives, researchers, secretaries, authors, students, and countless others, the use of word processing can result in dramatic increases in both personal and business productivity.

Introduction to Word Processing reveals to us all in understandable terms the why and hows and what-ifs connected with the world of word processing. For anyone who is thinking about buying a word processor, or who has just started using one and wants to get the most mileage from it, this book is required reading.

For more information, contact Sybex, 2344 Sixth Street, Berkeley, CA 94710, telephone (415) 848-8233.

Switching Power Supplies

A new MK Series of NJE switching power supplies is reportedly designed for continuous and extended operation in critical applications. To back up this claim, the manufacturer warrants each of 40 standard models against defects in materials and workmanship for five years from date of shipment.

With the supplies housed in industry standard cases (5" x 8" x 11"), features include loss of sense protection, remote sensing, remote inhibit, power fail signal, overload and overvoltage protection, plus inrush limiting on turn-on. Also available is an optional crowbar for use along with OVP.

MK Series power supplies come with inputs ranging from 120 VAC (+10%-25%), 47-63 Hz to 240 VAC (+10%-25%), 47-63 Hz. Outputs vary from 2 V at 150 to 300 A up to 48 V at 18 to 36 A. Voltage adjustment is $\pm 5\%$ minimum. Line regulation is 0.2% for 100% full line change. Load regulation is 0.2% for 100% load change.

The output recovers to within 1% in less than 400 microseconds for a load change of 25% within the range of 25% to 100% load. Output will also remain within the regulation limits for 20 milliseconds after loss of AC input power (from nominal line voltage) at full load.

The new supplies will operate at full output from 0° to 50°C and at full output derated 2% per °C from 51° to 71°C. Units can be stored at temperatures from -20°C to 85°C.

More detailed information can be obtained without charge by requesting Product Data Bulletin MK-101 from NJE, P.O. Box 50, Culver Road, Dayton, N.J. 08810. Telephone (201) 329-4611.

DATALink service

A new circuit switched digital data communications service has been announced by CCG, The Computer Communications Group of the TransCanada Telephone System. Information on the new network service, called DATALink™, was released to computer specialists and other management attendees at the Canadian Computer show.

Aimed at data users who must have the ability to access a host computer from remote sites and transmit data into the centralized processing unit in a batch or remote job entry (RJE) fashion, DATALink will be most efficient for the low-to-medium volume users requiring a transparent service to move data within this structure. A pay-as-you-use, end-to-end digital, circuit-switched data service, DATALink offers an upgrade to digital technology for current Multicom 2 data service users. It provides synchronous, full-duplex data transmission at speeds of 2400, 4800 and 9600 bits-per-second (bps), with half-duplex (single direction) transmission also accommodated.

DATALink provides the high reliability and accuracy of digital transmission plus a range of basic features including alternate routing, itemized billing, auto answer and multi-frequency signalling.

Touch-Tone signalling provides simple seven-digit access to all stations. Access to the network is via a dedicated loop from the customer's location to the DATALink switch.

Enhanced network security is possible through a closed user group option which prevents unauthorized users from accessing a DATALink customer database. Another option is fixed reverse charging which automatically transfers the charges for all calls to the receiving terminal.

DATALink will employ the Canadian-designed and manufactured DMS-100 digital multiplex system from Northern Telecom Limited. The DMS-100 switcher will take the computer communications signals from the customer's premises and switch them into the national digital data network. Any city in Canada which is designated a DATApac Serving Area constitutes a DATALink access location and can subscribe to all the features and benefits of this digital service. Initially, DMS-100 switchers will be located in Toronto, Hamilton, Ottawa and Montreal to handle the circuit-switching requirements of DATALink traffic. Over the next decade, additional DMS-100 switching systems will be phased into the network to handle the increasing volume of circuit-switched data communications traffic.

Rates for the new service will be filed early next year with appropriate federal (CRTC) and provincial regulatory agencies, with start of commercial DATALink service requested for the second quarter of 1982. For further information, contact Brian M. Fraser, CCG Public Relations, telephone (613) 567-3748.

Graph Array With 101 LED's

A new red 101-element LED bar graph array, the HDSP-8820, has been announced by Hewlett-Packard (Canada) Ltd. This 10.58 centimetre (4.16 inch) display is an easy to read alternative to mechanical meters. Its 1% resolution and wide LED elements (1.52 mm or 0.06 inches) offer accurate and reliable meter indication.

Package design and drive requirements make the HDSP-8820 easy and economical to design into a system or instrument. Standard SIP sockets and PC board layouts are accommodated by the single-in-line package. The common cathode LED arrangement simplifies microprocessor interface for support electronics. The inherent low power requirements of LED's keeps drive requirements economical.

The HDSP-8820 101 element bar graph array is particularly suited to industrial process control systems as a status or position in-

dicator for controller panels. It is also well suited for instrument and panel meter applications.

For more information, write Inquiries Manager, Hewlett-Packard (Canada) Ltd., 6877 Goreway Drive, Mississauga, Ontario L4V 1M8.


Measurement Error

Due to general crossing of wires (we generally try to blame our mistakes on technology), there was an error in our oscilloscope survey in the October 1981 issue. Thumbing through your carefully bound back issues, you will find that we said that we couldn't get any prices for Hitachi Denshi's 'scopes because they were in the process of being raised. In fact, this is only partially true, as some of them were actually reduced by as much as 20%.

For more information contact Hitach Denshi, Ltd. (Canada), 65 Melford Drive, Scarborough, Ontario, M1B 2G6 telephone (416) 299-5900.

50 circuits


1 Precision VCO

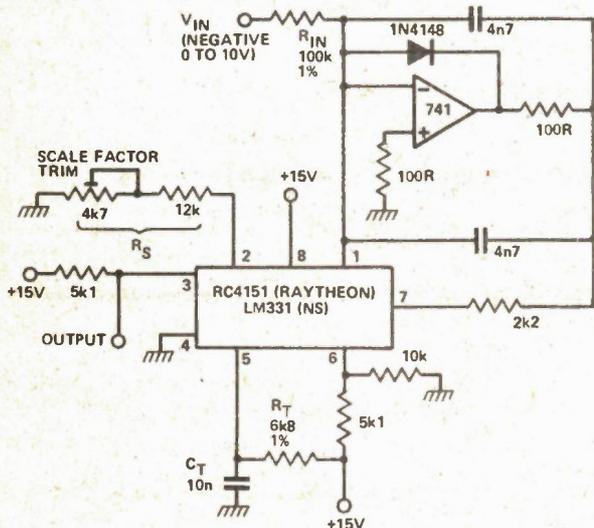

$$F = (-V_{IN}) / 2.09 \times (R_S / R_{IN}) \times 1 / (R_T C_T) \text{ Hz}$$


Maximum frequency = 10 kHz
 Linearity = 0.05%
 Response time = 10 us
 Op-amp powered from ± 15 V

2 Triangle/Square Wave Oscillator

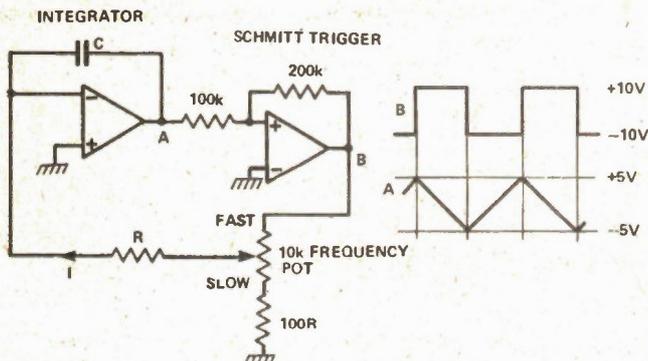


Output frequency $F = (\text{pot fraction}) / 2RC$
 Pot fraction can be 1/1 to 1/100, giving a 100 to 1 range from the pot
 Suitable frequency range = 0.01 Hz to 50 kHz
 Run op-amps from ± 12 V

3 Low Dissipation Regulator

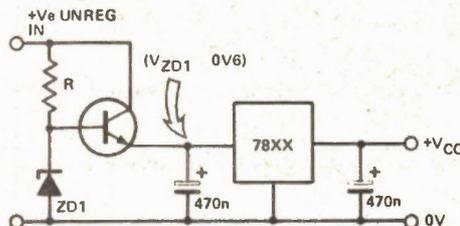



Using an external transistor to reduce the input voltage and power dissipation to a safe level.

4 Basic Op-amp Building Blocks


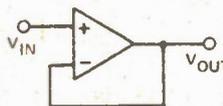


Voltage follower/buffer
 Input must have a DC path to ground

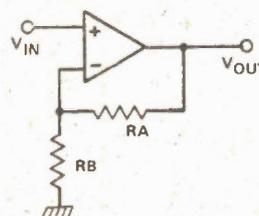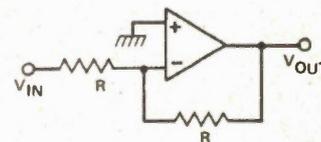Inverter
 Voltage gain = -1
 input impedance = R




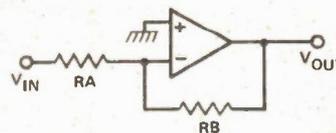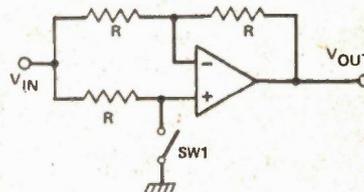Inverter/non-inverter amplifier
 Voltage gain = +1 with SW1 open
 Voltage gain = -1 with SW1 closed




Inverting Amplifier
 Voltage gain = -RB/RA
 Input impedance = RA

5 Audio Power Amp

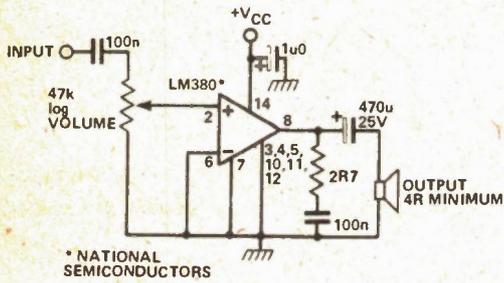

Voltage gain (fixed) = $\times 50$ (34 dB)
 $+V_{CC}$ range = +8 V to +22 V
 Typical quiescent current = 7 mA
 Output power = 2W5 (with speaker = 8R, heatsink fitted)

6 Linear VCO

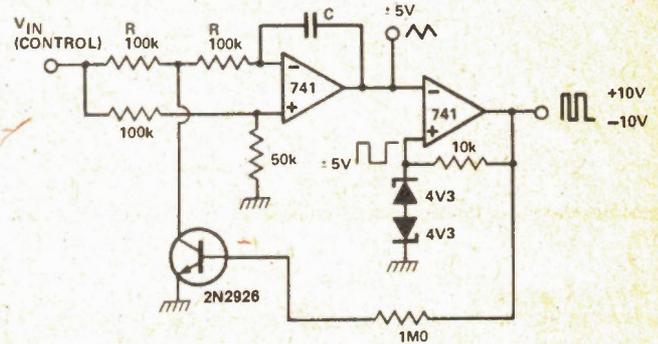

Triangle and square wave outputs


$$\text{Output frequency } F = (1.667 \times 10^{-7} \times V_{IN})/C \text{ Hz}$$

If $C = 1n0$ and $V_{IN} = 10V$, then $F = 1.66 \text{ kHz}$


Changing both R's from 100k to 10k will increase F by $\times 10$

For low frequencies use TL081 op-amps
 Frequency range 0.1 Hz to 10 kHz

8

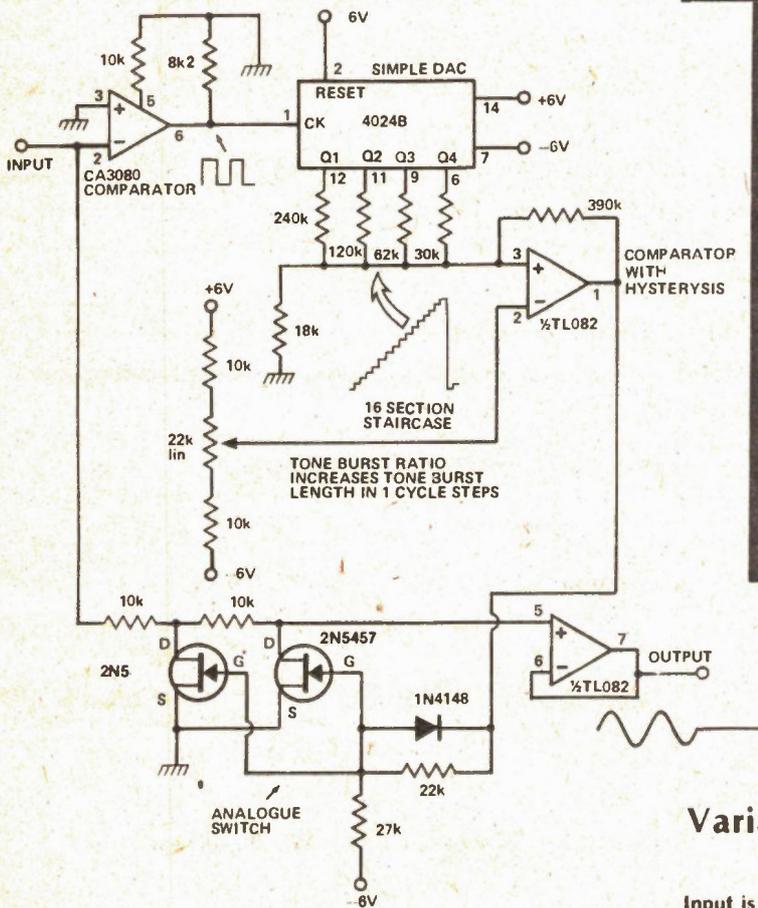


7 Two Chip VCA

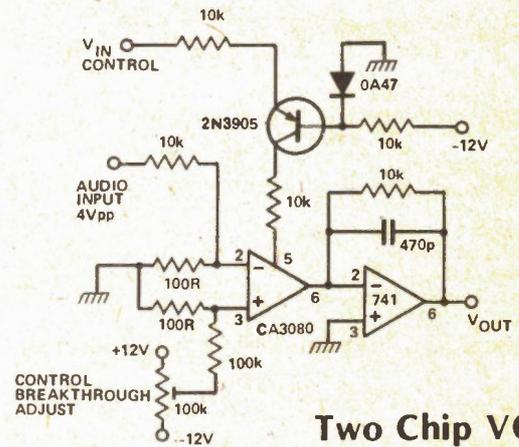

Input is a sine wave or any other periodic waveform, maximum level ± 2 V, maximum frequency 100 kHz
 Output is a tone burst variable from one cycle on, 15 cycles off to 15 cycles on, one cycle off
 All devices powered from ± 6 V

9


Digital Clock

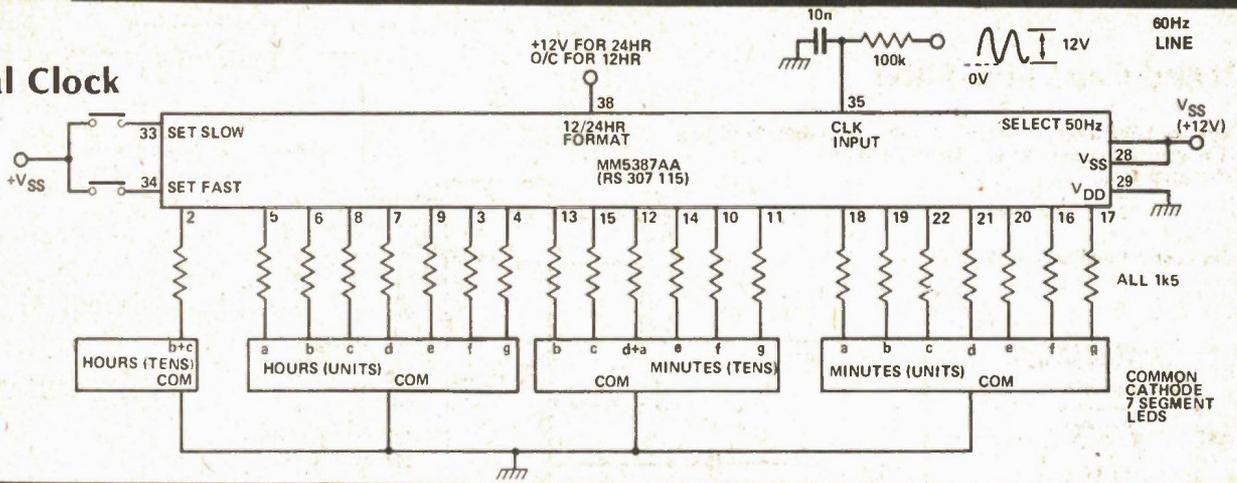

10

Keyboard Encoder And Display

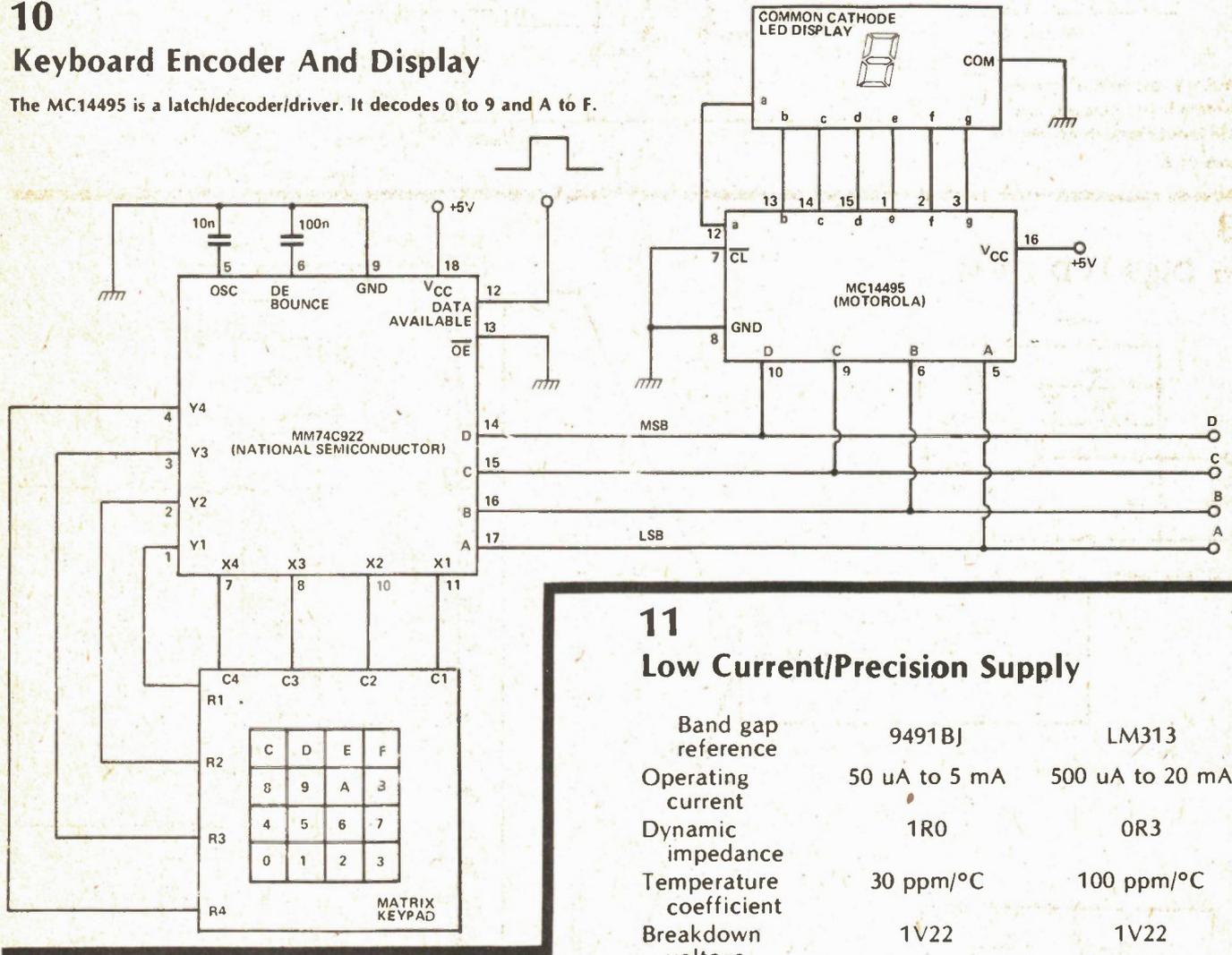The MC14495 is a latch/decoder/driver. It decodes 0 to 9 and A to F.




11

Low Current/Precision Supply

Band gap reference	9491BJ	LM313
Operating current	50 uA to 5 mA	500 uA to 20 mA
Dynamic impedance	1R0	0R3
Temperature coefficient	30 ppm/°C	100 ppm/°C
Breakdown voltage	1V22	1V22

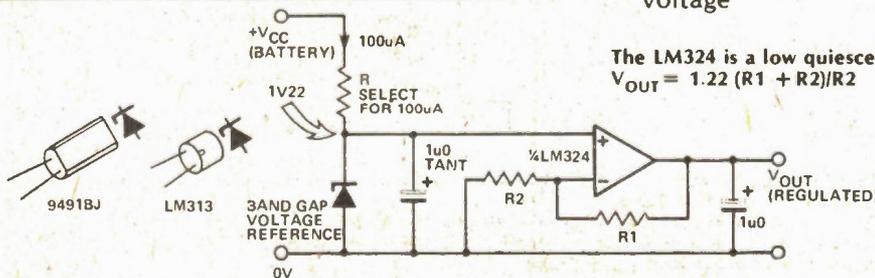The LM324 is a low quiescent current, ground sensing op-amp
 $V_{OUT} = 1.22 (R1 + R2)/R2$



Very useful for battery equipment where only low current and low voltages are available. Also used as voltage references in DVM units.


12

Switched Capacitor Filter


The R5604 contains three 1/3 octave, 6 pole Chebyshev band pass filters. The centre frequencies are determined by the relationship

$$\frac{F_{CLK}}{135}, \frac{F_{CLK}}{108}, \frac{F_{CLK}}{86.5}$$

Maximum centre frequency = 10 kHz

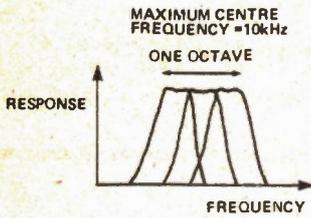


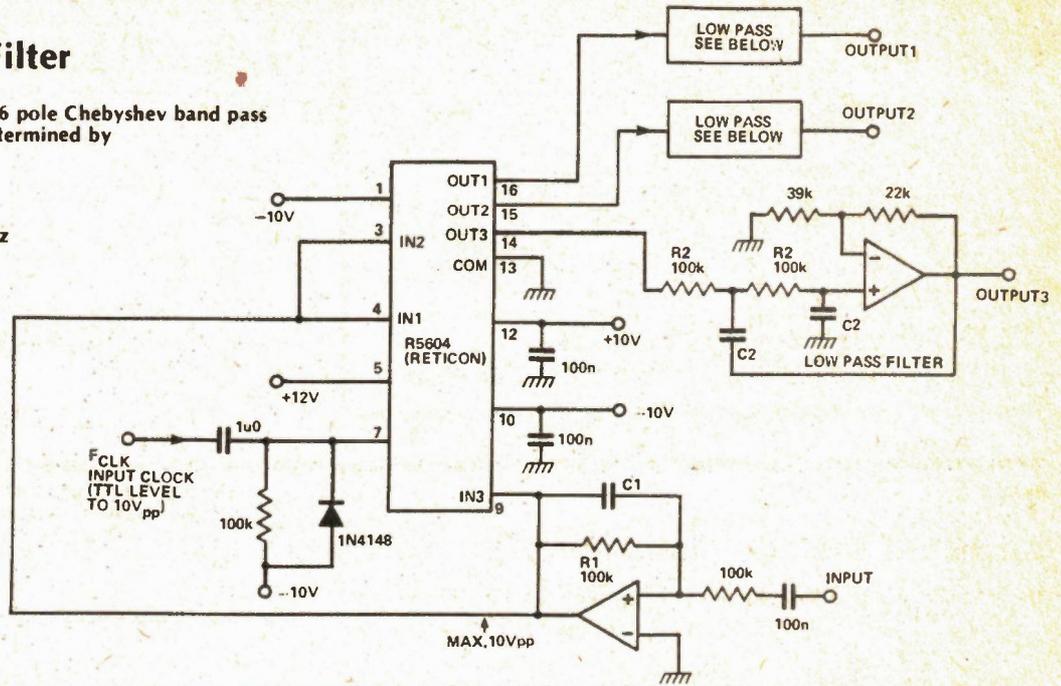Frequency response of one device. To obtain lower octaves, merely divide input clock frequency by factors of 2.




13


3 1/2 Digit LCD DVM

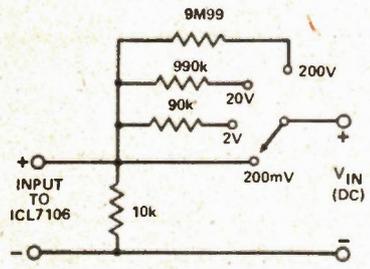

DC voltage inputs

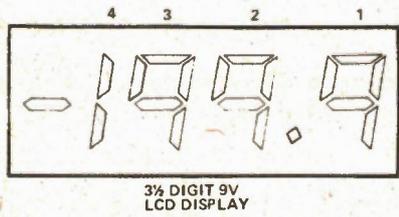


3 1/2 DIGIT 9V LCD DISPLAY

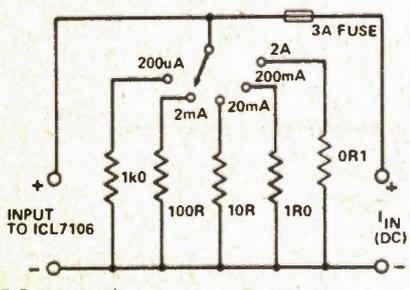


DC current inputs

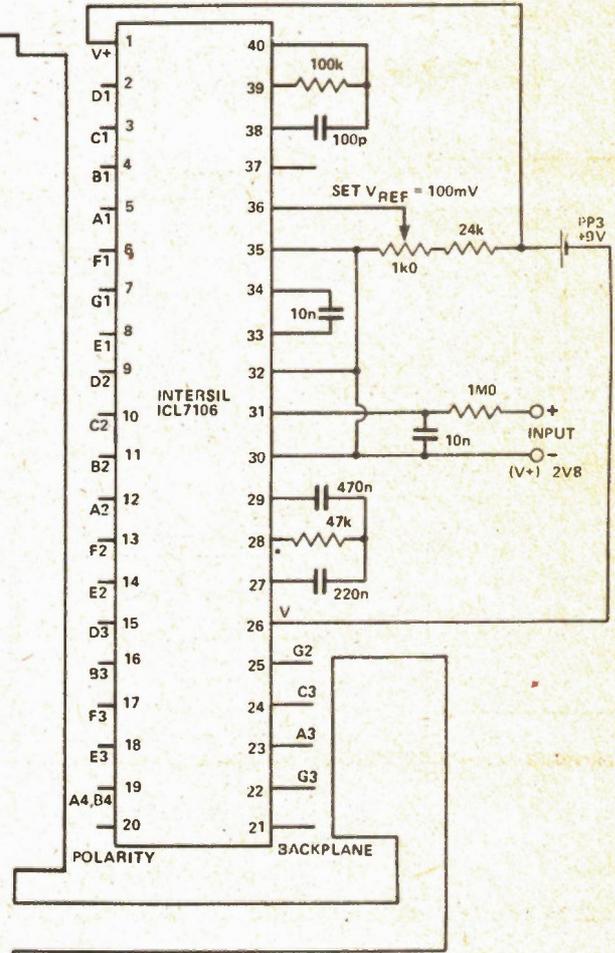
Input voltage range = ± 200 mV
 Quiescent current = 0.8 mA
 Common mode input range = (V+) - 0V5 to (V-) + 1V
 Decimal point must be driven externally by EXORing the decimal point data with the backplane strobe



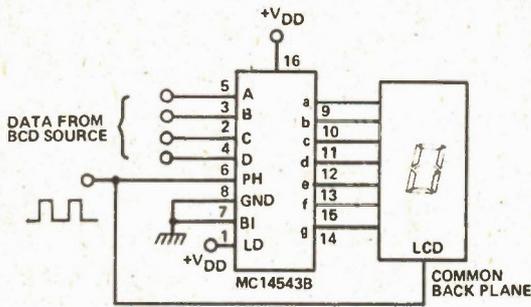
14 BCD-to-seven-segment Latch/Decoder/Driver for LCD Display




16 Magnetic Field Detector

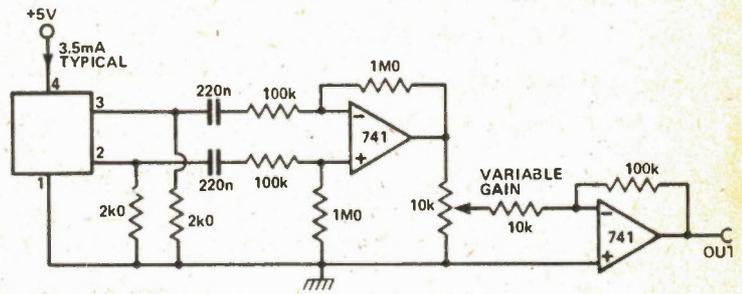

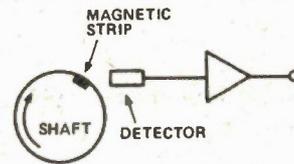Circuit is AC-coupled
 The linear Hall effect IC is the 6345S2
 Maximum gain = +40 dB
 Detector sensitivity = 7.5 mV to 10.6 mV/mT
 Detector frequency response = DC to 100 kHz




Circuit can be used as a tachometer

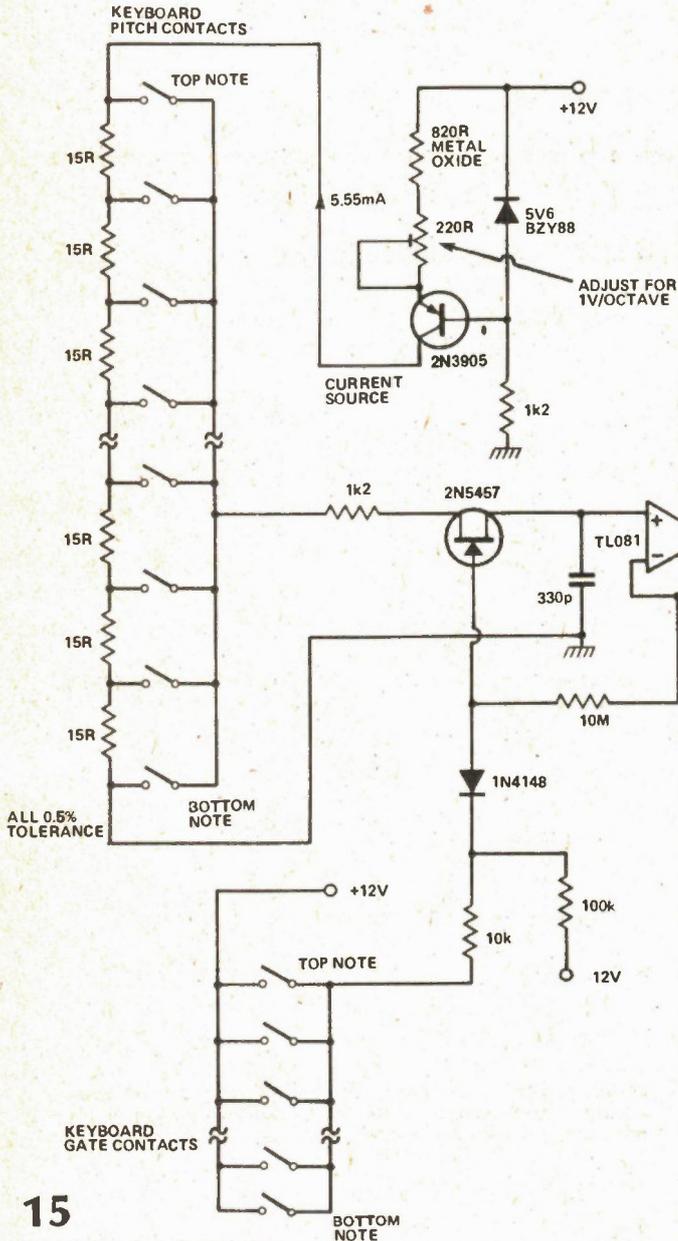

15 Keyboard Unit

Adjust the keyboard contacts so that the pitch contacts make before the gate contacts

17 Linear VCO (Ramp Waveform)

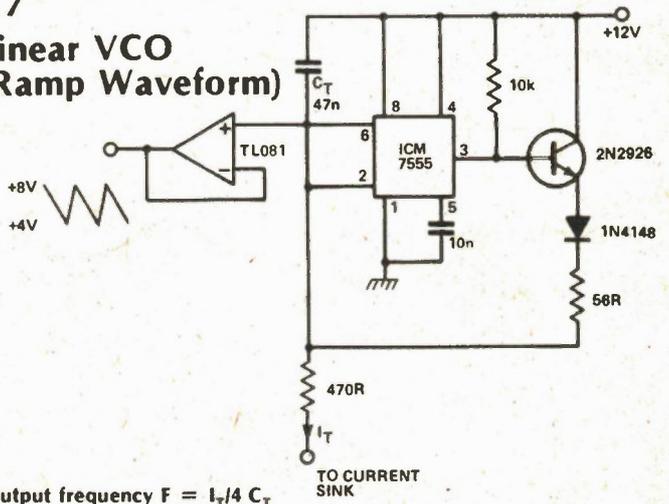

Output frequency $F = I_T / 4 C_T$
 If $I_T = 1\text{mA}$, $C_T = 47\text{n}$, then $F = 5.3\text{ kHz}$

18


Fast VCO

Oscillation frequency $F = I_T / 3C_T$ Hz

If $I_T = 2$ mA, $C_T = 330$ p, then $F = 2$ MHz

Alter C_T to increase F


Maximum frequency = 10 MHz

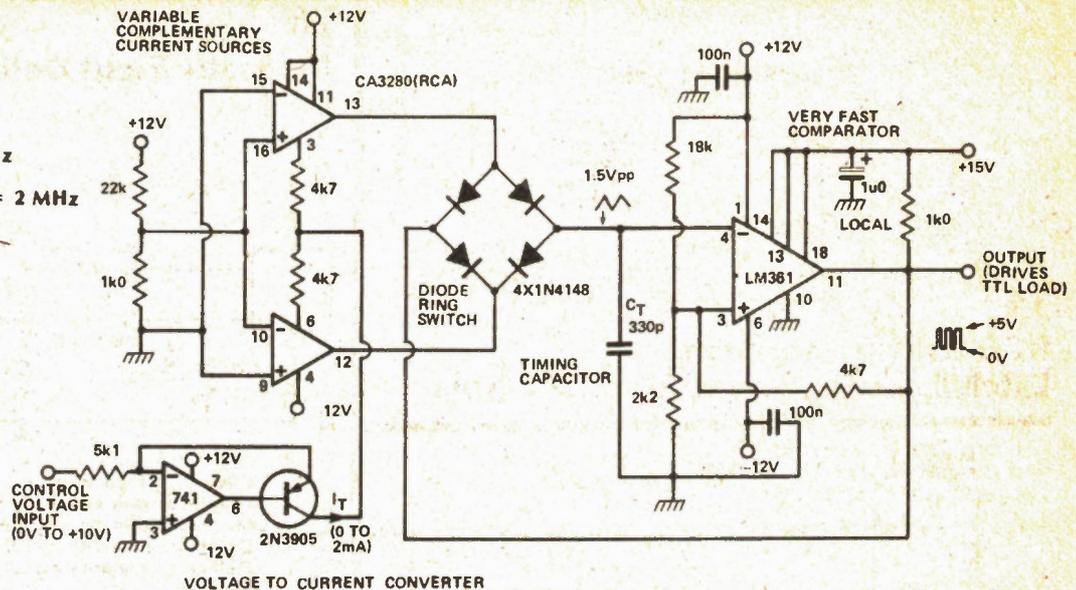

VOLTAGE TO CURRENT CONVERTER

19

Precision Full Wave Rectifier

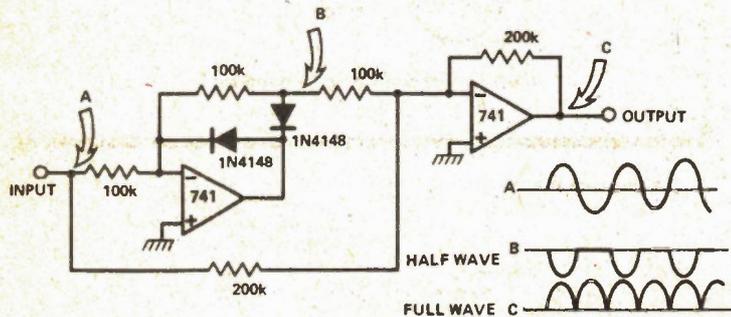


20

Band Pass Active Filter

$F_c = 1 / 2\pi C \sqrt{R_A + R_B}$

$Q = 1 / 2 \sqrt{R_A / R_B}$

Gain = $2Q^2$

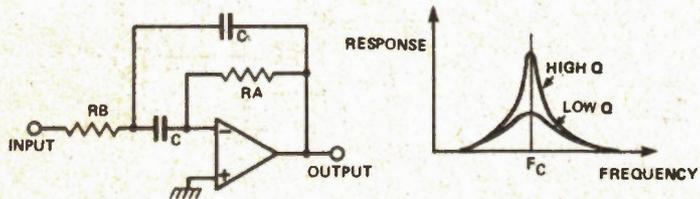


$F_c = 1$ kHz, $C = 15$ n


RA	RB	Q	GAIN
10k6	10k6	0.5	x 0.5
21k2	5k3	1.0	x 2.0
42k4	2k65	2.0	x 8.0
84k8	1k32	4.0	x 32.0

21

Battery Regulator

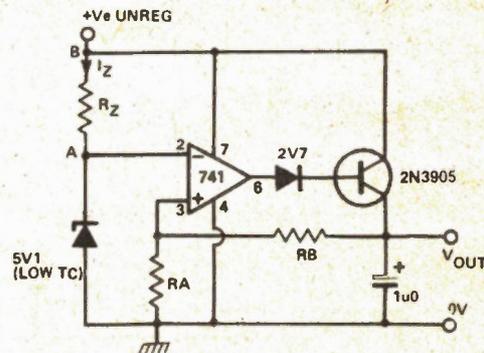

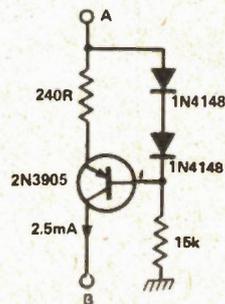A very low dropout voltage can be obtained by allowing Q1 to saturate. This gives maximum lifetime on battery power.



Better regulation can be obtained by replacing RZ with this 2.5 mA current source. However, the unregulated supply rail must not drop below $(5V1 + 1V2) = 6V3$

Select R_z for an I_z of about 2.5 mA

$V_{OUT} = 5V1 \times (R_A + R_B) / R_A$


Minimum $V_{OUT} \sim 6V$

Dropout voltage = $V_{CE}(Q1 \text{ saturated}) \sim 0V3$

Keep I_{OUT} less than 50 mA

22

Generating Negative Supply Rails

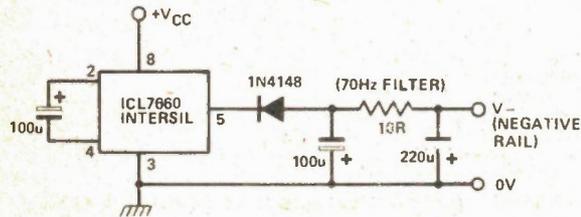


$V_- = (+V_{CC} - 0V7)$
 Typical efficiency = 98%
 Quiescent current = 170 μ A
 $+V_{CC}$ range = 3 to 10 V
 Maximum output current = 40 mA
 Output resistance = 55R


23

Low Impedance Source Preamp

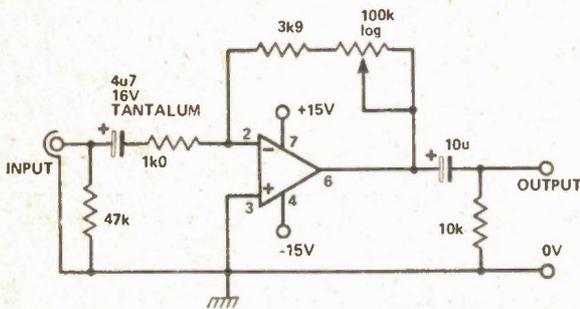Very low input noise
 Input noise = 4 nV/\sqrt{Hz}
 Equivalent input noise voltage = 0.56 μV_{RMS} (20 kHz bandwidth)
 Input impedance = 1k Ω (suitable for microphone)



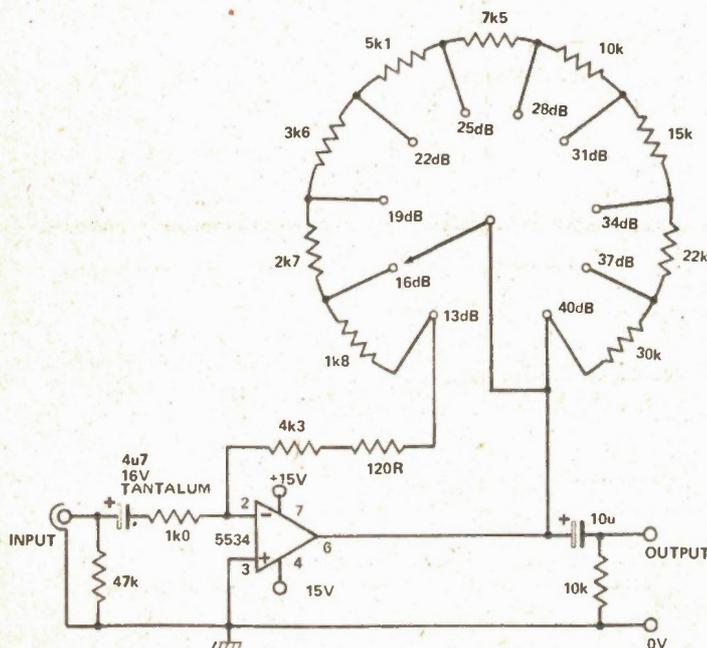Variable gain; x 3.9 to x 100 (12 dB to 40 dB)




Switched gain; 3 dB steps


24

Precision Power Supplies

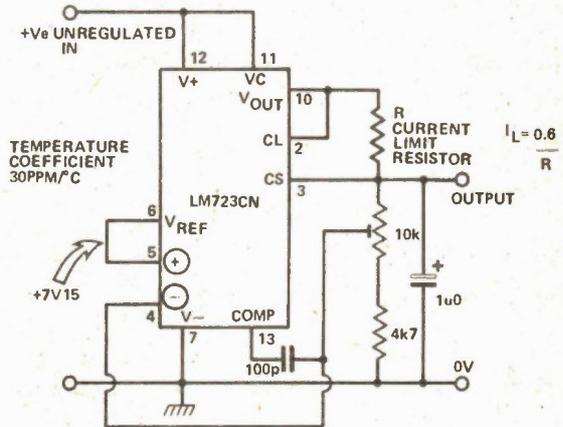723 general specifications:
 Maximum input voltage = 40 V
 Maximum current output = 150 mA
 Output voltage range = 2 to 37 V



Adjustable +7 V to +21 V

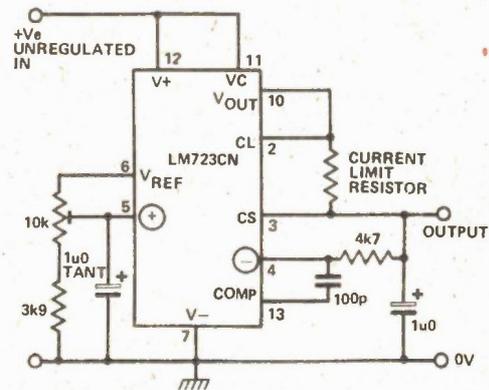


Adjustable +2 V to +7 V

25

True RMS Measurement

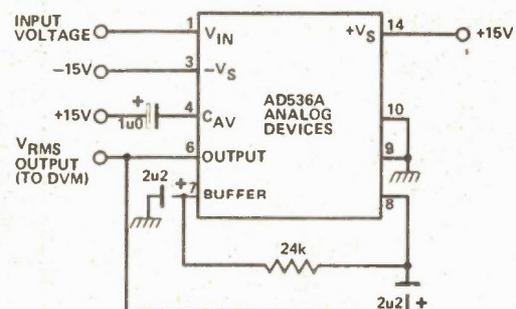Input voltage 7 V_{RMS} maximum
 Bandwidth: 300 kHz, $V_{RMS} > 0V1$
 Error of 1% for a crest factor of 7
 Quiescent current = 1mA
 60 dB range



26

Unregulated Power Supplies

* Smoothing capacitor must have a voltage rating greater than the rail voltage.


TRANSFORMER
SECONDARY
VOLTAGE (V_{RMS})

TYPICAL
UNREGULATED
DC VOLTAGE


4.5	6.3
6.0	8.4
9.0	12.6
12.0	16.8
15.0	21.0
20.0	28.0

APPROXIMATE RIPPLE VOLTAGES (V_{pp})

OUTPUT CURRENT	C = 470u	C = 1000u	C = 2200u
30 mA	0.42	0.21	0.10
100 mA	1.4	0.7	0.32
300 mA	4.2	2.1	0.96
1 A	14.0	7.0	3.20

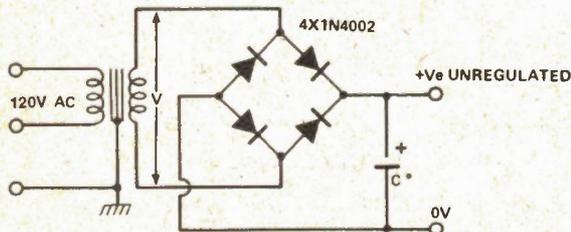

Single Rail

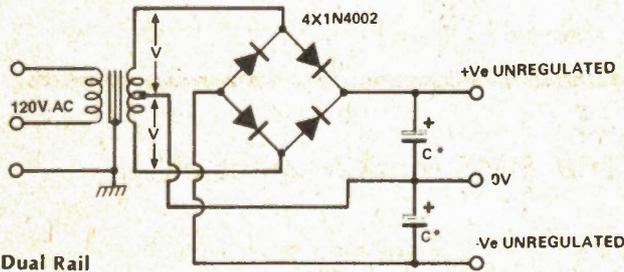


Dual Rail

28

Current Limiter


$$0R4 < R < 120R$$

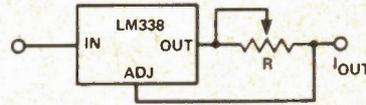

29



Simple Mixer

INPUT	MAX GAIN	INPUT IMPEDANCE	SOURCE
1	+6 dB	10k	line level
2	+20 dB	5 to 10k	line level
3	+46 dB	1k0	low impedance microphone input
4	+6 dB	1M0	high impedance input

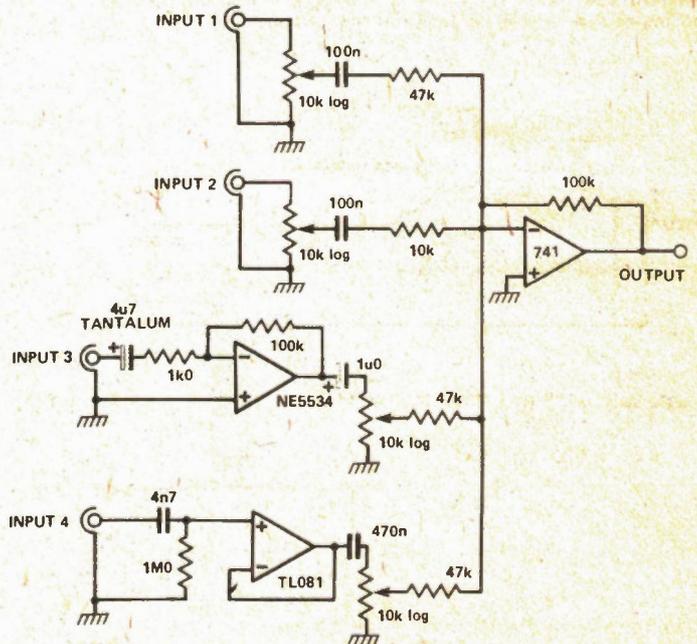


27

Parametric Equaliser

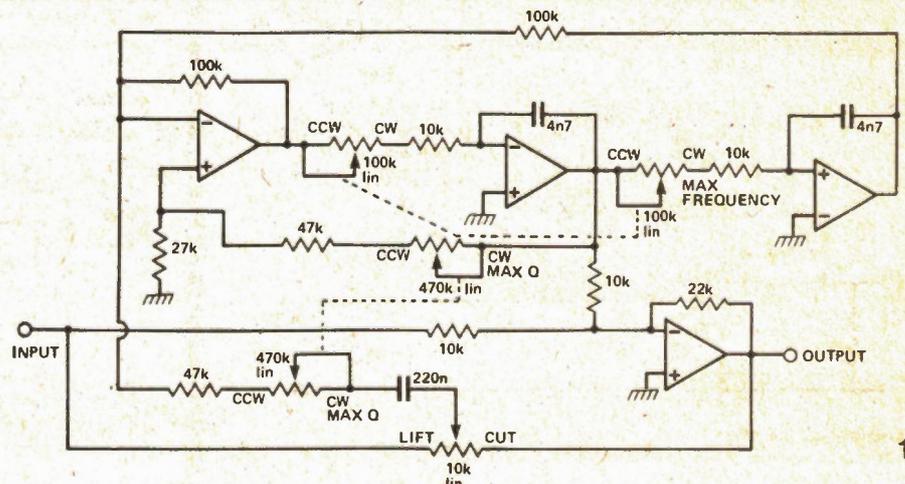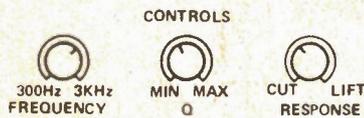


30

Schmitt Triggers

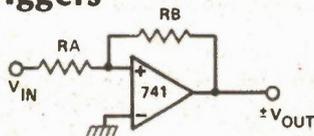


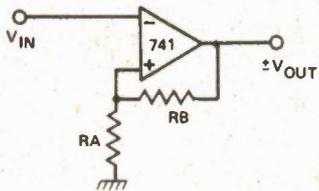Non-inverting; input hysteresis levels = $\pm (RA/RB) \times V_{OUT}$



Inverting; input hysteresis levels = $\pm (RA/(RA + RB)) \times V_{OUT}$

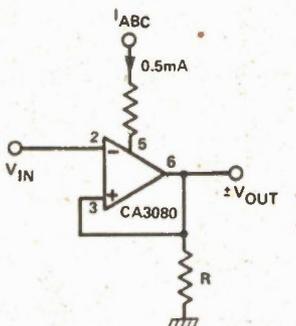Note that V_{OUT} depends on the supply voltage and the individual op-amp




Transconductance type; input hysteresis levels = $\pm V_{OUT}$; $V_{OUT} = R \times I_{ABC}$

R can be replaced by two 1N4148 diodes back-to-back

32


Power Supply Unit

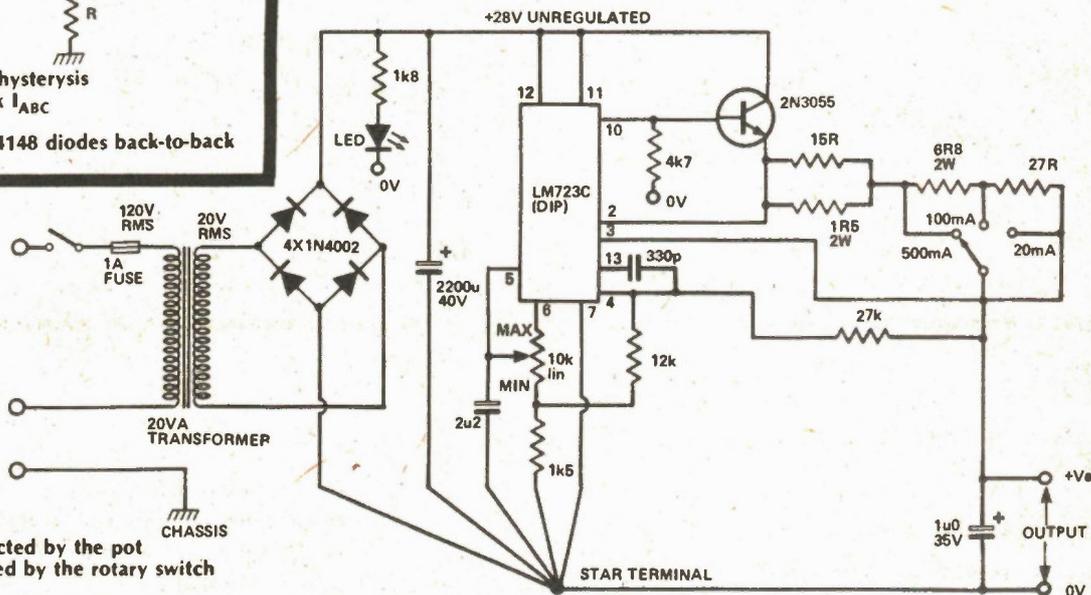

Variable output voltage is selected by the pot
Variable current limit is selected by the rotary switch
Output voltage is 0 to +20 V

31

Fast Oscillator

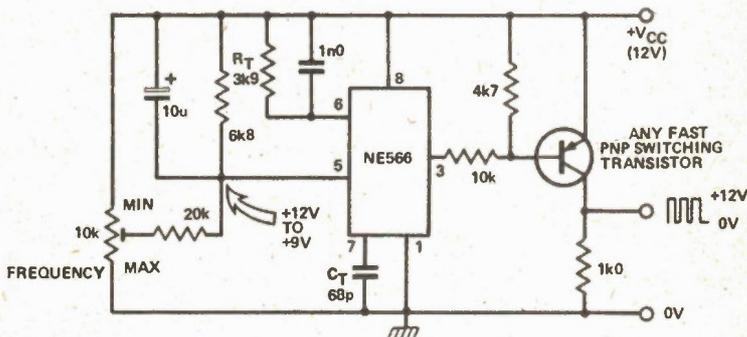


Bias voltage on pin 5, $V_B = \frac{1}{4} V_{CC}$ to V_{CC}

V_B gives a 10 to 1 control range

Typical frequency = 1 MHz

33

Standard Eight-bit DAC

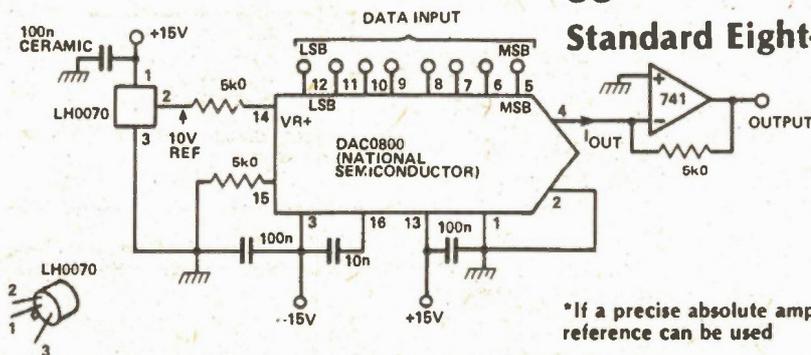


*If a precise absolute amplitude is not needed, then a zener diode reference can be used

34

Heavy Duty DC Motor Control

The DC motor should not take more than 3 to 4 A continuous current. Taking STOP low stops motor. This input can be used for mark/space modulation control of speed.

A	B	W	X	Y	Z	
0	0	1	1	0	0	REVERSE
0	1	0	0	1	1	FORWARD
1	0	1	0	1	0	OFF
1	1	1	0	1	0	OFF

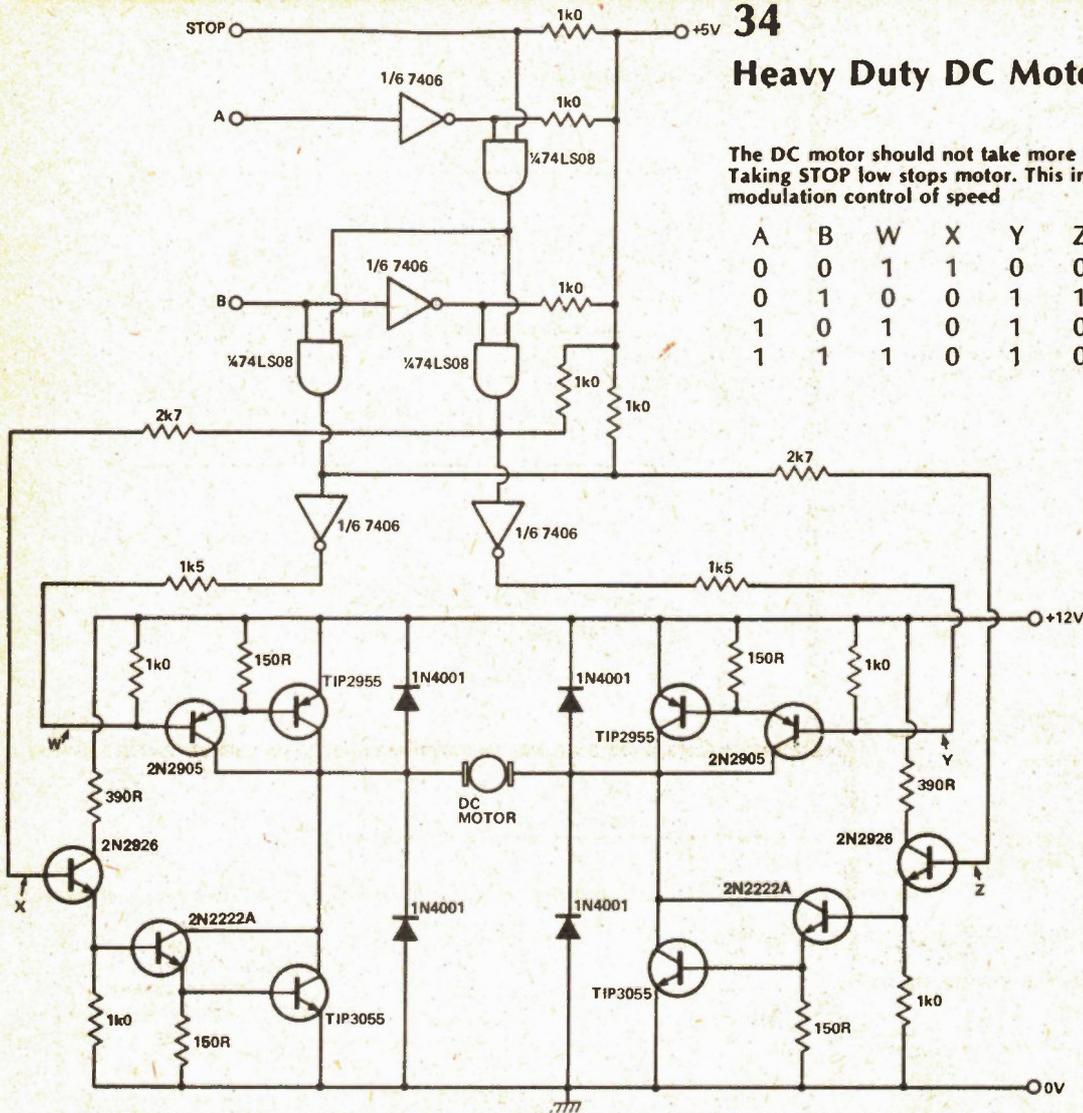


35


Current Mirrors

If $\beta = 100, I_2/I_1 = 0.98$

*Matched transistors with the same β

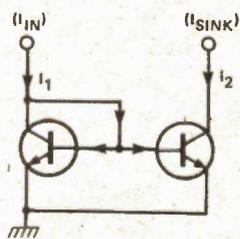


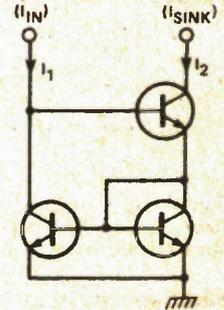This improved mirror gives a better I_2/I_1 performance with lower values of β . Also the I_{SINK} current sink has a much higher output slope resistance.



36


Increasing Regulator Voltages

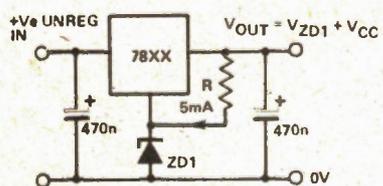

Increasing the output voltage using a zener diode.

37


Increasing Regulator Currents

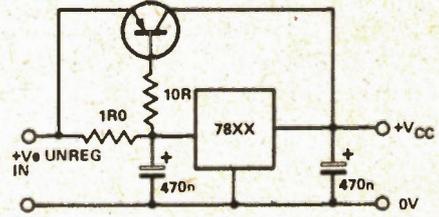


Using a bypass transistor to increase the output current drive. The first 600 mA flows through the regulator, the rest via the external transistor.

38

Rumble Filter

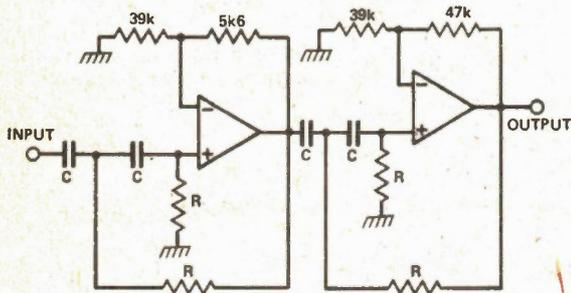

4th ORDER HIGH PASS

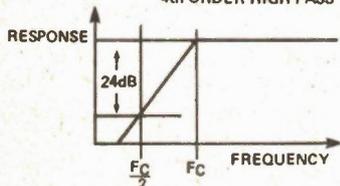


Roll-off slope = 24dB/octave
 Overall voltage gain = x 2.6 (8.3 dB)
 Op-amps are 741's or RC4558

F _c	C	R
25 Hz	100n	62k
50 Hz	100n	30k
100 Hz	100n	15k
200 Hz	100n	7k5


(5% tolerance)

40

Scratch Filter

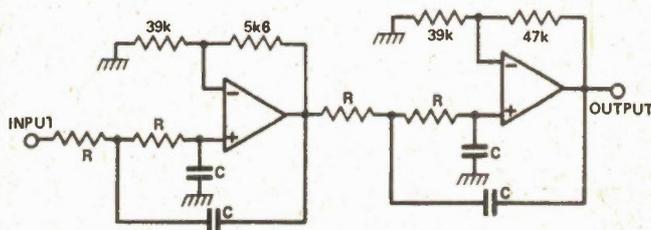

4th ORDER LOW PASS


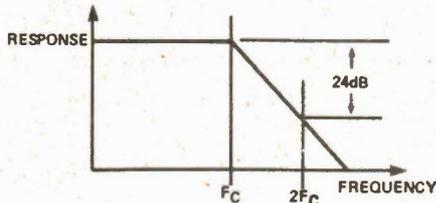


Input must have a DC path to ground
 Roll-off slope = 24 dB/octave
 Overall voltage gain = x 2.6 (8.3 dB)
 Op-amps are 741's or RC4558


F _c	C	R
10 kHz	1n5	10k
7.5 kHz	1n5	14k
5 kHz	1n5	20k

(5% tolerance)

39 Monostables

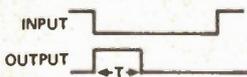
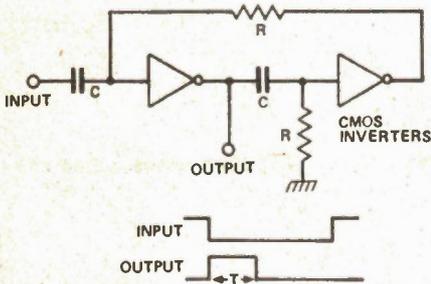


CMOS inverters
 $T = 1.38RC$
 Keep R greater than 47k


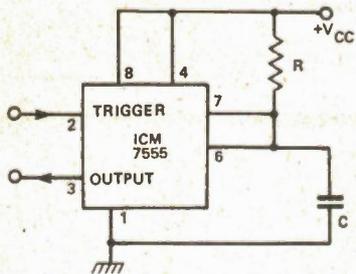


CMOS 555
 $T = 1.1RC$

41 Comparators

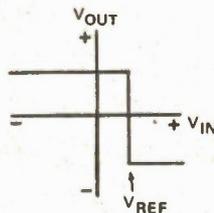
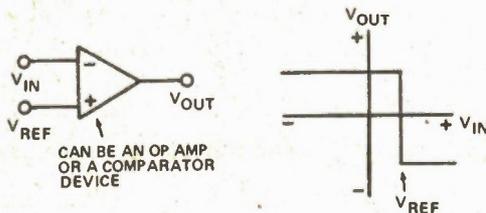


Response of a simple comparator

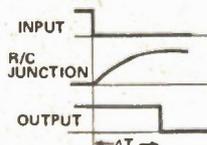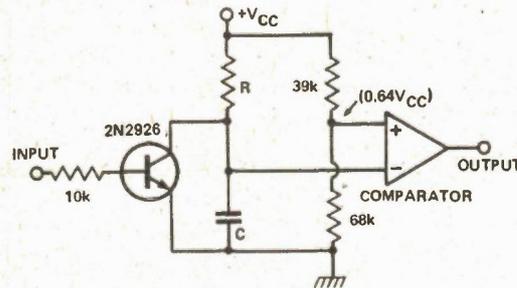

Time delay generator; $\Delta T = RC$

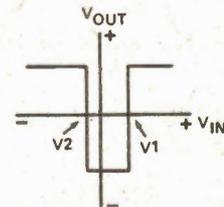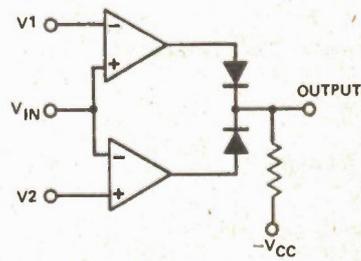Window comparator
 V1 and V2 can be defined by resistors
 or can be set by any voltage
 Note that V1 must be more positive
 than V2





Standard comparators
 LM311 single
 LM339 quad
 LM361 very fast single
 LM3914 linear 10-section
 LM3915 log 10-section

42

Triangle To Sine Wave Converter

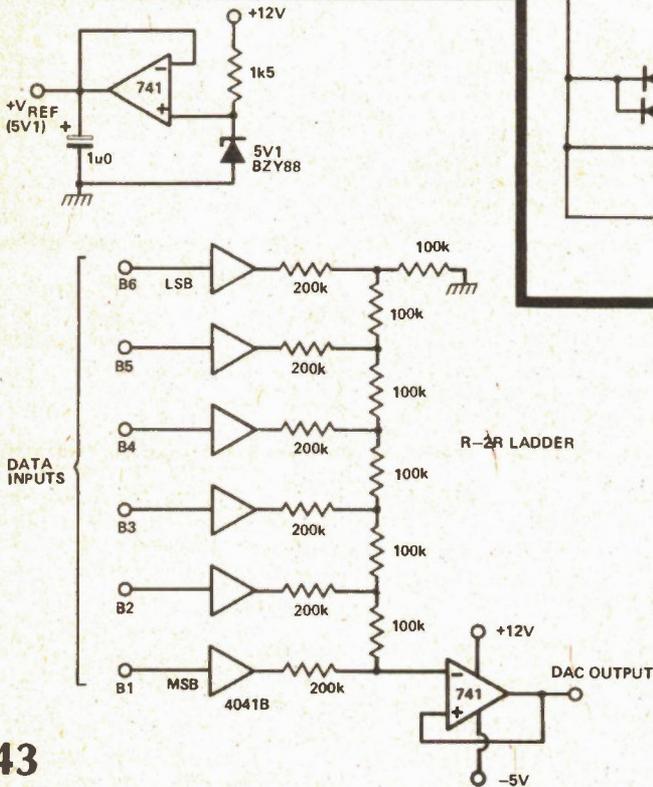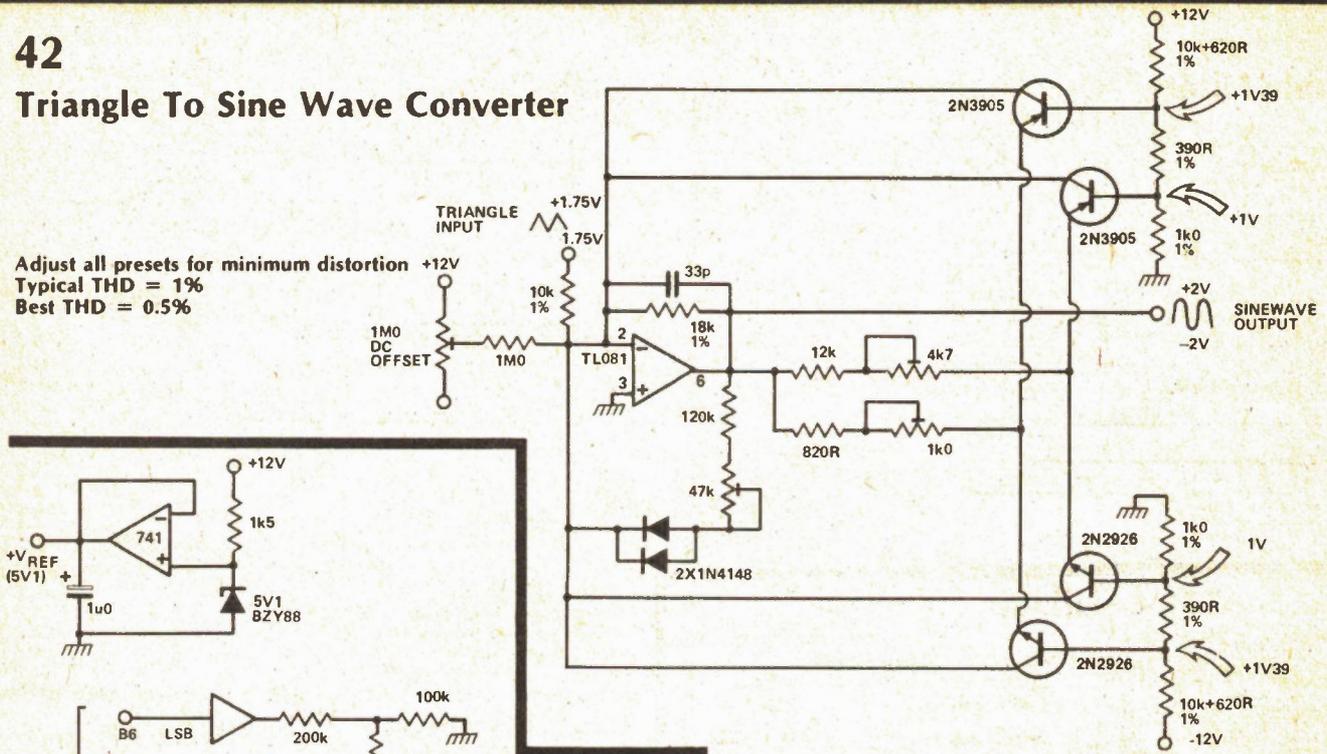
Adjust all presets for minimum distortion
 Typical THD = 1%
 Best THD = 0.5%



43



Six-bit DAC — 10-bit Precision

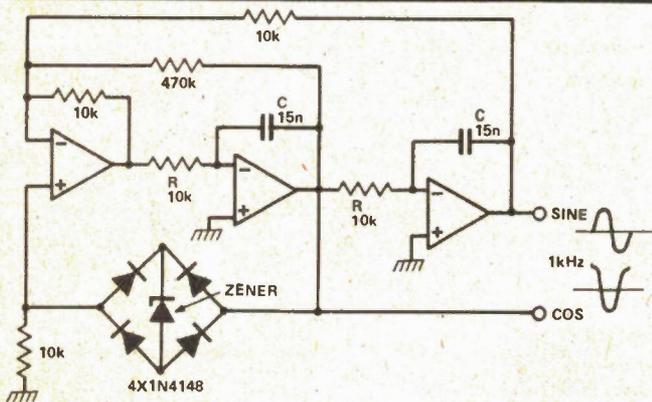Buffers powered from 0 V and +V_{REF}
 Resistors in ladder need 0.1% tolerance
 DAC output has 64 steps



44

60 Hz Notch, Variable Q

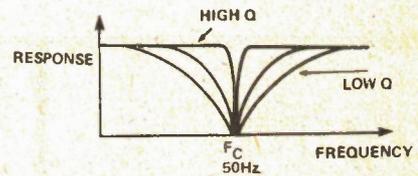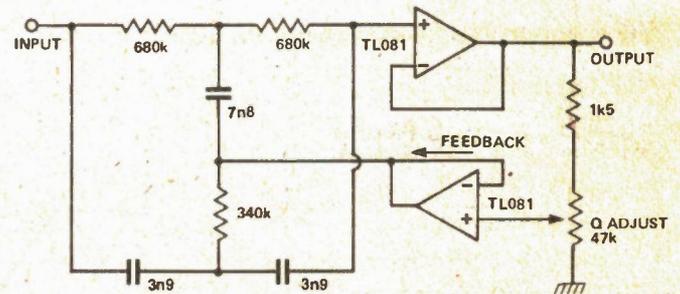

45

Dual Integrator Oscillator

Quadrature outputs (ie sine and cosine)



$$\text{Output frequency } F = \frac{1}{2\pi RC} \text{ Hz}$$

To change frequency, change both R's or both C's.
 Maximum frequency ~ 20 kHz
 Minimum frequency ~ 0.016 Hz using C = 1u0, R = 10M, and TL081 op-amps
 Oscillation amplitude = 2x(zener voltage + 1V2) V_{pp}

46


Multiple Time Delay Generator

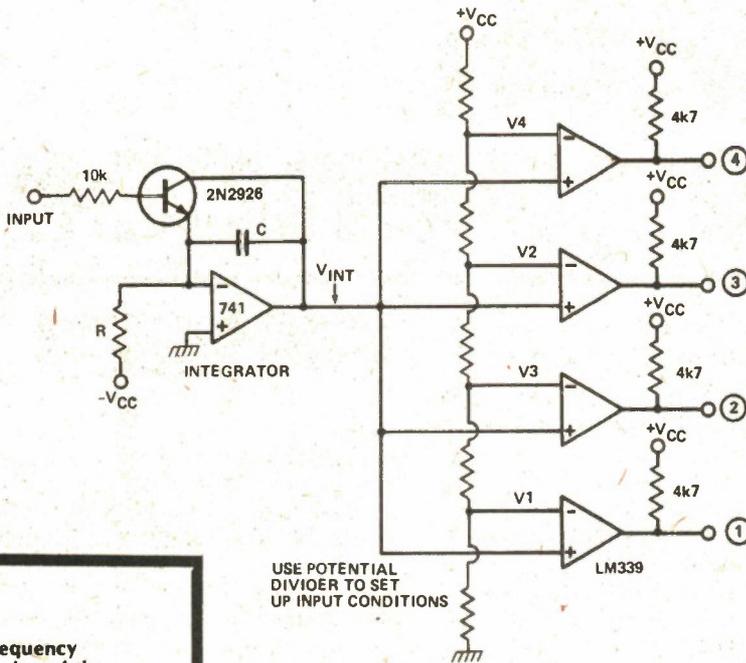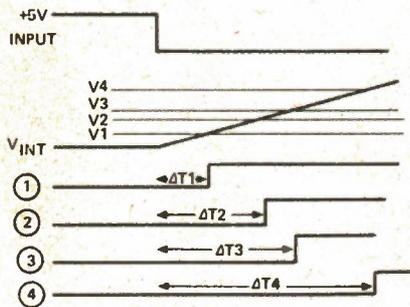Ramp rate = $-(-V_{CC} / CR)$ volts per second



47

TTL Oscillator

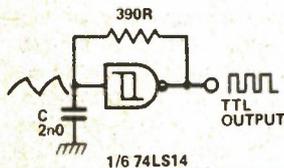

Vary C to change frequency
Do not increase the size of the 390R resistor

Frequency range = 1 Hz to 1 MHz

48



Low Pass Active Filters

Inputs must have a DC path to ground


$$F_c = \frac{1}{2\pi RC}$$

2 pole roll-off = -12 dB/octave
4 pole roll-off = -24 dB/octave

R	C	F _c
107k	15n	100 Hz
10k7	15n	1 kHz
10k7	1n5	10 kHz

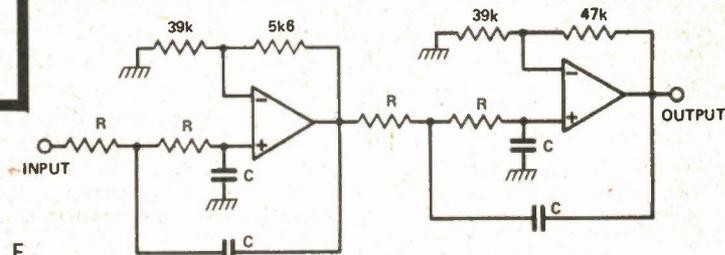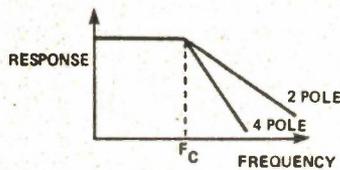

4 pole Butterworth

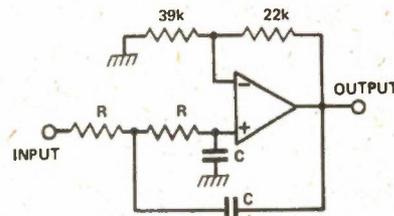


2 pole Butterworth

49

Inverting Peak Voltage Detector

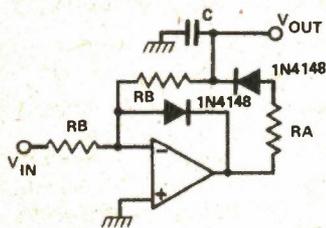Attack time constant = C.RA
Decay time constant = C.RB



This circuit works well at high frequencies


50

Non-inverting Peak Voltage Detector

Input must have a DC path to ground

Keep RA greater than 1k0 to avoid dumping large currents to ground via C

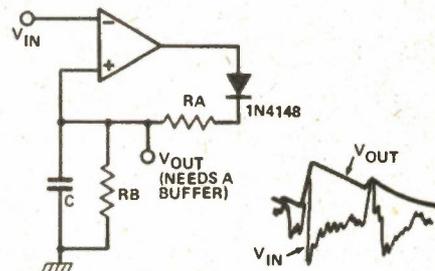Attack time constant = C.RA
Decay time constant = C.RB



This circuit is not suited for high frequency operation

If you liked this article, please circle Reader Service Card number 51. If you didn't, circle number 52.

Flash Sequencer

Here's a project that lets you do something new with a flashgun, or nine. Make mobile matter into marvellous multiple images.

THE HUMAN eye is an extremely complex sensor, capable of discriminating shapes and colours in an extremely high optical noise environment. Researchers are only just realising the computational complexity of image analysis, shape recognition, perspective compensation, telemetry and all the other tasks that our eyes and brain perform continuously.

Yet, probably because of this complexity, there is one area in which the eye's performance is rather poor: speed. Any discrete movement shorter than an eighth of a second becomes blurred and at a repetition rate of 18 to 25 events per second, everything blends into a continuous movement. Unfortunately, in real life,

The sensor is a simple level crossing comparator, the signal source being selected by SW1. Resistor R6 at the offset compensation input of IC1 provides an imbalance of the input differential stage, so that RV1 can set the threshold level both over and under 0V. LED1 is an aid to adjustment and should be just flickering when RV1 is properly set.

A manual trigger is provided for test purposes. Irrespective of the input conditions of IC1, when PBI is activated the strobe pin (pin 8) has direct control of the output. Thus pin 6 of IC1 is sent high and the flash sequence is triggered.

The next two stages are the pre-and sequence timers. They work in the same way, except for the enable conditions. The difficulty here is a reliable and repeatable delay. In all monostables, energy is charged and discharged between two levels. Our problem is that the stable level must be the same as the power off state; it must be reached in a much shorter time than the shortest delay (100 μ S) without a negative supply to draw on; and the time control must be linear.

The stage works as follows: IC2a and IC2b lock to the charging position (low and high outputs respectively) as soon as an impulse is received through C1. C2 begins to charge through the range resistor. The output of IC3a is high, so IC4's inverting input is higher than its non-inverting input and its output is low. This output is fed back to IC3a's input so we have a steady state. As soon as the voltage on C2 reaches the limit set by RV2, IC4 switches high; IC3a swit-

If you liked this project, please circle Reader Service Card number 57. If you didn't, circle number 58.

events happen a lot faster than that and to try to analyse and understand them, we need some device that can effectively reduce the flow rate of information.

Strobe Shots


When the number of images of the subject is small, we can simply superimpose them. The result is strobography. The pioneers of this method (Mach, Foucault, Helmholtz) used the high intensity discharges of Leyden jars (the first capacitors) as the light sources. Nowadays, you can obtain much more accurate results with a battery of electronic flashes, a camera and our flash sequencer!

The basic idea is that when an event

ches low; the voltage at the inverting input of IC4 is zero, giving a Schmitt trigger action. A change of state can only occur now when C2 is discharged to 0V (power off state). This is done by IC3b and C3, which was initially positively charged. As IC4 goes high, IC3b goes low. The voltage on the negative side of C3 is driven below zero potential. D4 is now forward biased and passes a current from C2 into C3. D3 and IC2b suppress the charging current. This continues until the voltage on C2 is just under 0V, at which point IC4 switches over to its low position again.

The low to high transition of IC4 has been transmitted through IC2c and IC2d to the IC6 clock input. This results in the 'O' output, which was at logic 1, going low, thus disabling the pre-delay stage and enabling the sequence timer through IC3c. At the same time output '1' goes high, triggering triac SCR1 and firing the first flash. The sequence timer (still enabled) operates in the same way as the previous stage, except that the charging current is continuously enabled and astable operation results. Each one of the impulses shifts the high output of IC6, successively triggering the following flashes until the '0' output is reached again. This disables the sequence timer and allows the pre-timer to receive a new impulse from the sensor, ready for a new cycle.

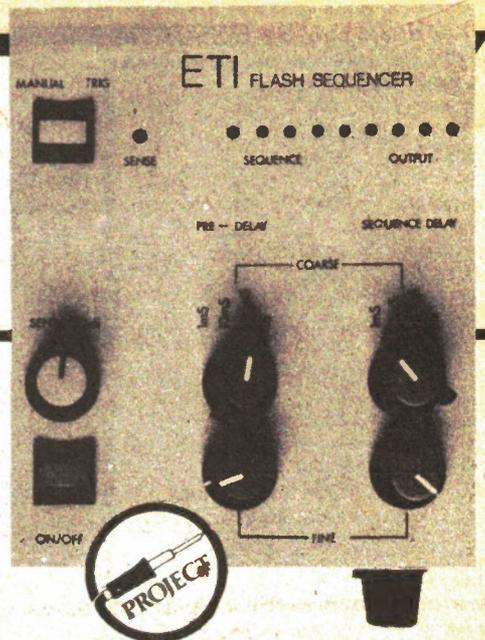The output control elements are triacs, rather than SCRs, because not all electronic flashes conform to the 'positive centre/ground shield' standard connection.



occurs, it triggers a series of flashes at a constant and known rate. Being of very short duration (on the order of a microsecond), the flashes effectively immobilise the subject in its consecutive positions, which can be recorded with a camera. As an example of possible analysis, the change in position during a known time can give the velocity. The change of velocity to the next frame gives the acceleration, and so on. The position, intensity and colour of each flash can give further meaning to the recorded positions.

Multi-option Multiflash

One of the basic practical problems in strobography is the triggering of the sequence. The most useful sensors are contact, audio and optical, and all three are provided for in our design. Furthermore, an adjustable pre-delay allows the flash sequence to commence a short time after the triggering pulse, should this be necessary for the right effect. Both the pre-delay and sequence delay can be continuously adjusted from 100 μ S to 1 S per flash and thus practically all situations are allowed for. A manual trigger and LED readout are provided to make the time settings for a particular picture easier to adjust. A camera X flash socket allows for a sequence to be triggered from the camera, in exactly the same way as a single flash. In this case, make sure that the exposure time is longer than the total sequence time.

Using The Unit

There are two possible modes of operation for this device. It is either:

- Triggered by the event to be recorded, using a suitable sensor (adjusted just below the triggering point) and the pre-and sequence delays being set for the desired effect. In this case, the camera shutter has to be open during the whole of

HOW IT WORKS

Resistors (all 1/4 W, 5%)

R1	1M5
R2,4,44	1M0
R3,9	22k
R5	680k
R6,16,17,	10k
R18,19	
R7,26-34	1k0
R8,12,22	470k
R10,20	4k7
R11,21	47k
R13,23	4M7
R14,24	120k
R15,25	12k
R35-43	470R

POTENTIOMETERS

RV1	100k logarithmic
RV2,3	100k linear

CAPACITORS

C1	100n polycarbonate
C2,5	1u0 polycarbonate
C3,6	100u 10V tantalum
C4	47u 16V tantalum
C7	100n ceramic

SEMICONDUCTORS


IC1,4,5	CA3140
IC2	4001B
IC3	4049B
IC6	4017B
SCR1-9	TIC206D
D1-6	1N4148
LED1	0.125" yellow LED
LED2-10	0.125" red LED

MISCELLANEOUS

PB1	push-button N.O.
PB2	push-button N.C.
SW1,2,3	one-pole rotary switch
SK1,3	phono socket
SK2,4-12	3mm coaxial flashgun sockets
9v battery holder, case	

PARTS LIST

Fig. 1 Circuit diagram of the Flash Sequencer.

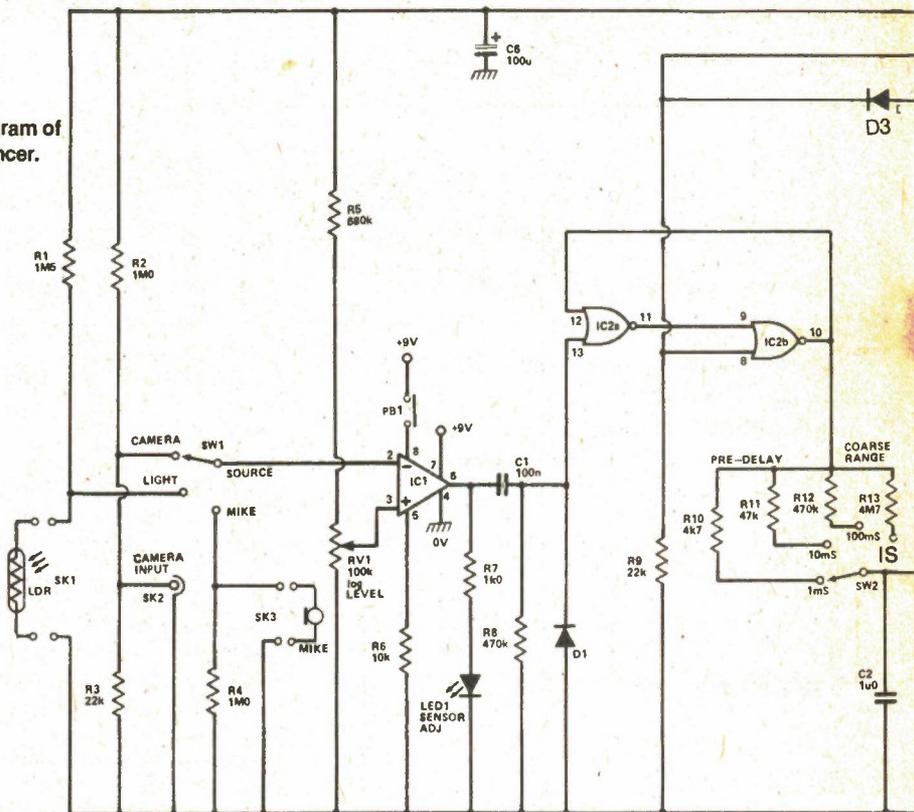

type or at least of the same intensity. In the case of flashes with auto-exposure circuitry ('computer' flashes), the setting should be to manual (or the sensors masked with opaque tape), in order to avoid interactions from the previous flash.


CONSTRUCTION

Construction should be fairly straightforward, as all the components (except PB1, SW1, SW4 and the LEDs) are mounted on a single PCB to minimise interwiring.

Note that the number of output stages is entirely up to you; if you want less than nine flashguns to be triggered, leave out the unwanted triacs together with their associated LEDs, resistors and sockets.

When fitting the rotary switches, the tags will have to be trimmed off to fit the PCB holes. Some of the unused tags have been cut off completely — the overlay shows which ones remain.


Fig. 2 Overlay for the sequencer. Some of the tags of SW2 and SW3 are cut off before mounting — the dots indicate which tags remain.

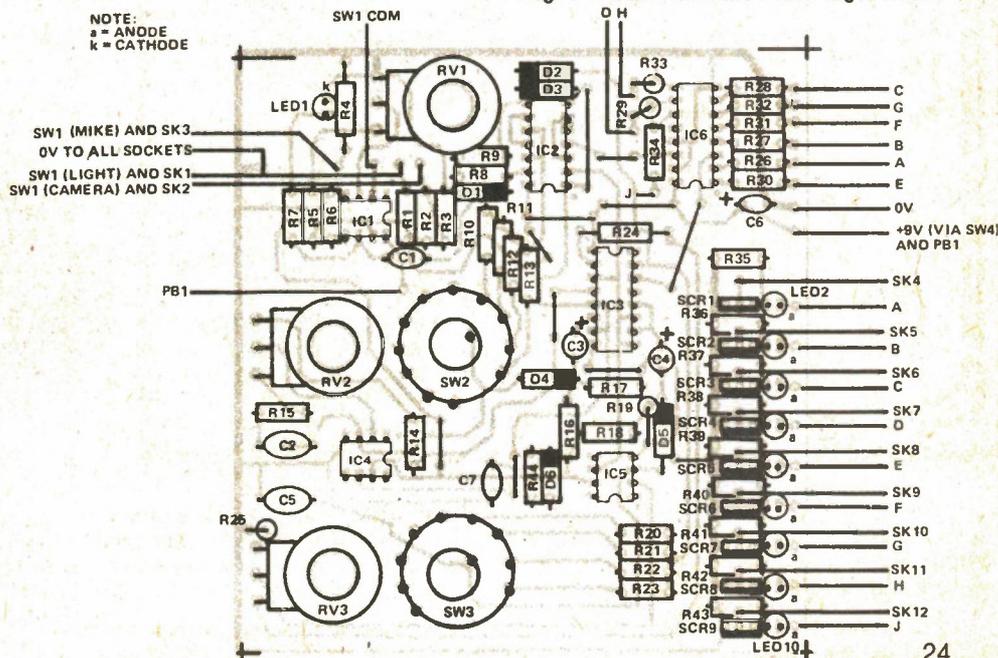


the sequence. Therefore a manual operation of the shutter (B setting) and very little or no ambient light will be necessary. The diaphragm should be set to one stop less than the calculated aperture for the flash and subject-camera distance used.

● Set off by the camera in exactly the same way as a single flash. This method is somewhat more flexible for event durations of the same order as the human reaction time (about a tenth of a second). In that case, the synchronisation is made through an ordinary extension lead from the X socket of the camera to the 'contact' input of the sequencer. Care must be taken to set an exposure time longer than the total sequence time. The diaphragm setting is determined in the same way as in the previous method.

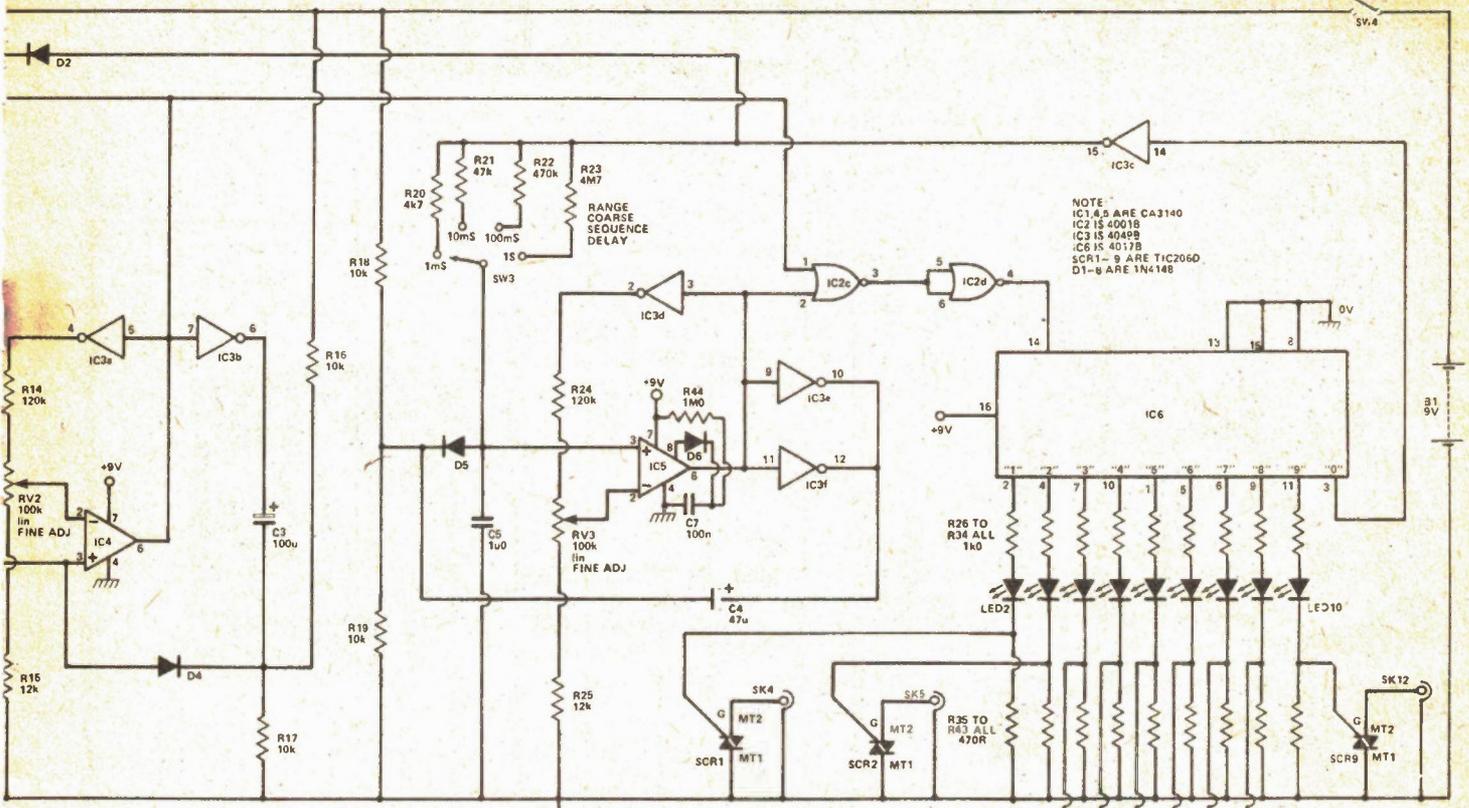In both cases, the flashes are connected to the sequencer either directly or through ordinary extension leads, and can be distributed along the path of the subject or grouped as a battery. It is generally easier to work with flashes of the same




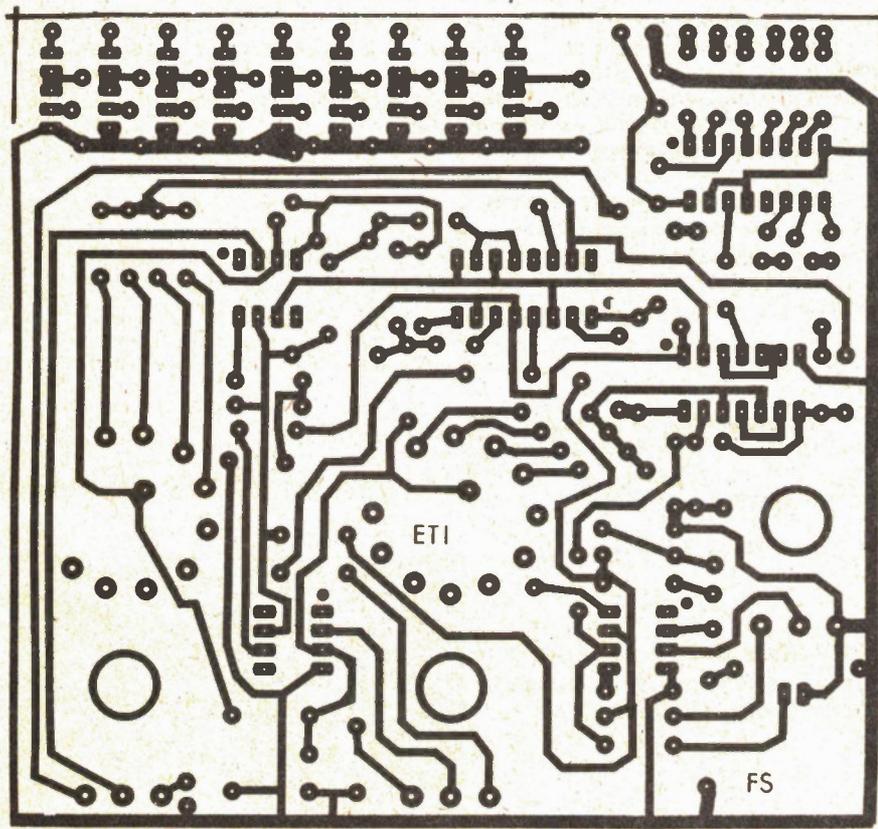NOTE
 IC1, 4, 5 ARE CA3140
 IC2 IS 4001B
 IC3 IS 4049B
 IC6 IS 4017B
 SCR1-9 ARE TIC206D
 D1-9 ARE 1N4148



The board can now be mounted on 3/4" spacers and holes marked out and drilled to accommodate the LEDs and switch and potentiometer spindles.

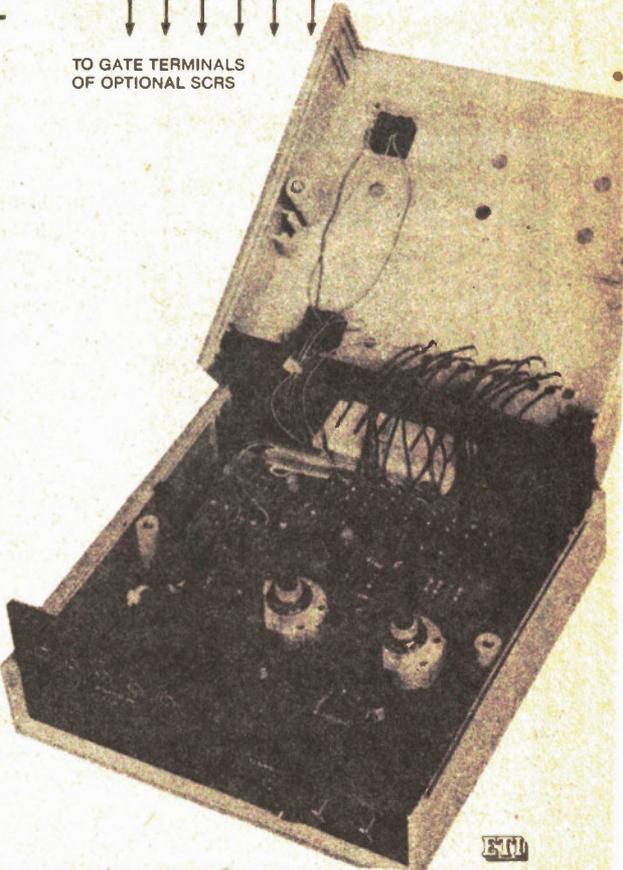The next stage is to wire the LEDs, sockets and off-board switches. When this is completed a visual check of the whole project should be made.



TO GATE TERMINALS OF OPTIONAL SCRS

Fig. 3 inside the sequencer. Although the overlay shows the LEDs mounted on the PCB for clarity, they are actually mounted on the case top and connected to the board by flying leads.

next month



Music Processor

It's a flanger, phaser, automatic double tracker and echo box all in one, and, if you glue a sixteen bit micro-processor to the bottom of the board it'll have one of those, too.

Ni-Cads

When regular batteries die, there is naught for them but to blow "taps" and plant them. Ni-Cads, however, can be re-incarnated. . . and, if you don't know how to use them right, may return to haunt you.




Printers

It is very often the case that a printer costs more than the computer it's hooked to. Thus, it is highly worthwhile finding out just what these expensive little peripherals are all about *before* whipping out the Visa card. Stay your hand 'til next month.



Gluons

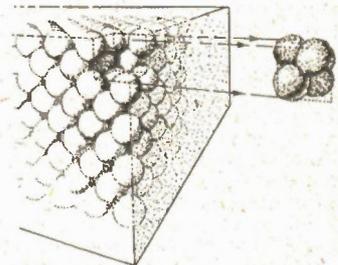Gluons are the theoretical particles which stick all matter together. Extremely dense matter is comprised of a slightly different variety, called Crazy-gluons.



Crystal Marker

A simple circuit for short wave listeners to keep from getting hopelessly lost in the E layer.



COMING TO ETI

THE ONLY WAY TO BE SURE YOU GET YOUR ISSUE EACH MONTH



SUBSCRIBE

**BOOKS, BACK ISSUES
BINDERS—SEE OVER**

Code _____

Electronics Today Magazine, Unit 6, 25 Overlea Blvd., Toronto, Ontario M4H 1B1.

ORDER Please fill out form overleaf
SUBSCRIPTIONS: NEW SUBSCRIPTION? Or... RENEWAL? Please check one.

One year subscription (12 issues) \$16.95 Two year subscription (24 issues) \$29.95 Postage and handling to Canada is included, for U.S. please add \$3 other countries add \$5/yr.

NAME _____

ADDRESS _____

TOWN/CITY _____ PROVINCE/STATE _____

CODE _____ DATE _____

Signature _____
 Expiry Date _____

Cheque enclose DO NOT send cash
 Bill Mastercard A/C No. _____
 Bill Visa/A/C No. _____



PLEASE ALLOW 6—8 WEEKS FOR YOUR FIRST MAGAZINE TO ARRIVE

CRISIS!



Having discovered that our offices are not actually haunted, and that toenail clippers do not cause cancer of anything at all, our manager in charge of editorial paranoia has decided to begin fearing an impending paper shortage. In the event that one should actually take place (it would certainly come as a surprise to us), we would be forced to reduce the size of ETI. We don't really want to cut down on the number of pages, as we use the back issues for stabilizing furniture, and they'd be no real good for this if they were very thin. We have therefore made plans to produce the magazine as shown in this life size illustration, at 12.5% of its current size.

Needless to say, we have considered the difficulty some readers may have in actually attempting to read the resulting 1 point type, or trying to build things from circuit diagrams smaller than the IC's they contain. Many of you might be concerned about this too.

Well, we certainly don't intend to use these mouse sized magazines for ourselves, and we will always have some full sized ones available. We are thus in a position to make the following amazing offer. Subscribe to ETI for one year, at just \$16.95, or two years, just \$29.95, and we will guarantee that you will receive all your issues full size, even if everyone around you is getting theirs glued to the back of a stamp.


Send your money (no Canadian Tire coupons, please) to

**ETI Subscriptions
25 Overlea Boulevard, Unit 6
Toronto, Ontario
M4H 1B1**

(If you choose not to avail yourself of this amazing offer, we would like to take this opportunity to suggest that you avoid sneezing when reading ETI.)

ATOMIC POWER

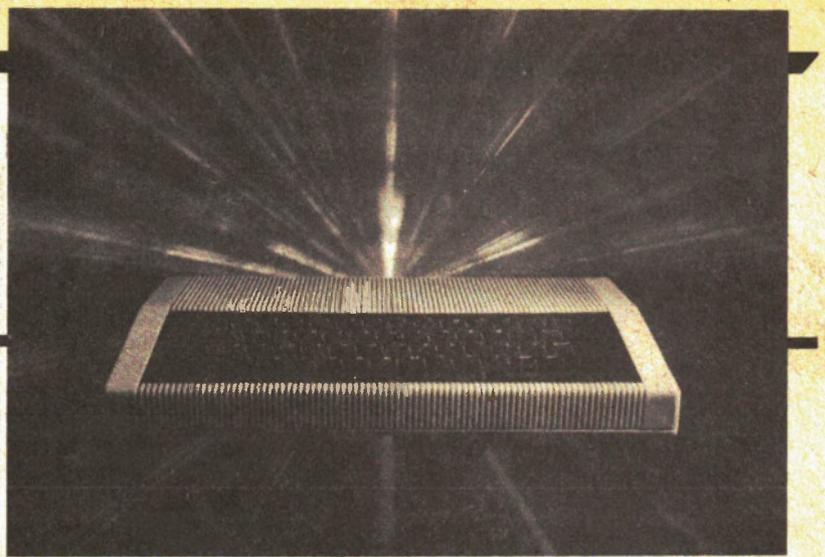The further adventures of the mighty ATOM computer, faster than a speeding bullet and able to leap tall buildings if shot out of a cannon. By Steve Rimmer.



LAST MONTH, we had a brief peek at the Acorn ATOM, one of the newest small computers to show its face. However, aside from having great thundering herds of externals and dandies to play with, the ATOM has a splendid, if slightly weird, operating system, which we're going to have a peer at this month. Ultimately much more powerful than the architectures of many popular systems, an unadorned 12K ATOM can do such things as high resolution graphics, machine language in BASIC, and sophisticated string manipulation.

It does take some getting used to, though. (Gadzooks... not another new language!)

Another New Language

The ATOM comes with a resident BASIC, but it isn't the familiar Microsoft BASIC by any means. If you thought the variations between, say, PET BASIC and TRS-80 BASIC were arduous, this one will very nearly fry your senses. Combining aspects of BASIC, FORTRAN and C, plus a few totally unique variations, ATOM BASIC will provide you with a rather impressive assortment of error messages if you try to use the machine with Microsoft syntax. You can get away with quite a lot if you use the proper BASIC forms, such as PRINT, LIST, etc, but the little fellow really gets upset on abbreviations. One of the most potentially troublesome is the "?" symbol; a PRINT to any of us, but a combination PEEK and POKE to ATOM (oh, really), which likes "P." for PRINT. Most of its abbreviations are, in fact, the first letter of the expanded keyword followed by a period. Much easier than the complexities of, say PET tokenization, but still demanding of a bit of instinct suppression.

If you're a seasoned BASIC programmer, it will probably take about

two hours to get fully comfortable with the ATOM, but after that you should begin to see the magnificence of it all.

The first interesting variation in the BASIC is the aforementioned combination PEEK and POKE deal, "?". Exactly which it is at any given time is determined by which side of the equal sign it finds itself on. POKE X,255 would translate to ?255=X. X=PEEK(255) would become X=?255. It's actually fairly reasonable this way, as, in effect, PEEK and POKE are complementary functions.

Another newcomer to BASIC is the DO UNTIL loop. The ATOM also has the more familiar FOR NEXT loop structure. The DO UNTIL loop, or just DO loop, is a refugee from FORTRAN. It takes the form of DO UNTIL K, where K is a variable and presumably there are statements modifying K in between the DO and the UNTIL. If the UNTIL condition of K is that K=255, and there's a statement in there incrementing K by 1, the loop will repeat 255 times and then proceed to the next statement. However, K need not be incremented, or even mentioned within the loop to produce loops of indeterminate, or infinite, length. DO loops are a lot more flexible as to jumping in and out of them.

The WAIT statement in ATOM BASIC is quite a bit different than that in most other systems. When encountered, it will sit and vegetate until the next video flyback on the TV monitor, or for about a sixtieth of a second. This has two very important functions. First off, for animated graphics, it permits one to conveniently hold off doing anything until the picture is being blanked, virtually eliminating snow and picture glitches. Secondly, it allows the insertion of meaningful time delay loops, as the ATOM's BASIC is so fast that

the usual FOR X=0 TO 10000: NEXT X approach just wouldn't hang on long enough.

The ATOM system also permits the use of labels on statements. This means that instead of saying GOSUB 1000, one can (if you'd rather), use GOSUB a. The first statement of the subroutine would then be labeled 1000aREM CAMEL KILLER, or whatever.

String manipulation and its associated trappings have also been mutated to a degree. To extract, say, the leftmost five characters from the string A\$, one doesn't just resort to the familiar LEFT\$(A\$,5) approach. Instead, the machine lets you play with the string pointer to actually extract specific bytes from where it happens to be storing A\$ in RAM. Hence, you would move the pointer to the beginning of A\$ in RAM, and then over five more. This permits a great deal more flexibility in string handling, as you can extract and insert stuff with relative ease.

Perhaps one of the most important statements in ATOM BASIC is one that doesn't actually exist anywhere else; "[".

The Mighty "["

One of the things one realizes about the ATOM fairly early on is that its higher level language isn't quite so higher level as many of its peers. In fact, there is considerably more interrelation with the actual internals of the machine's 6502 processor than one would find on almost any other system. For instance, you can choose to specify constants as hexadecimal at any point simply by placing a "#" in front of the number. This is because the ATOM is very much into machine language programming, and contains one of most sophisticated assemblers around.

Machine code is programmed right into BASIC text. The first line of a machine code section must be a "[", and the last a "]". In between these, all coding can be done in 6502 mnemonics. The ATOM manual has an excellent section to introduce you to ML programming.

If you've ever tried to machete your way through the undergrowth of ML programming unassisted, the ATOM will be like a flamethrower in the jungle. You don't, for instance, have to calculate relative branches; all branching is to labels. There are no op codes to deal with; the system figures them out from the mnemonics and a bit of syntax. The system assembles all machine code modules when the program is run, checking for any heavy errors, and will print a complete (annotated) assembly if desired. (Printing a NAK character suppresses listing the assembly.) Best of all, if you totally fry the thing, and send the system into a time warp loop, the BREAK key will get you out of it *without* losing your program. There's a statement, OLD, that lets you retrieve it.

The capacity of this kind of thing is quite staggering. ML programming is orders of magnitude faster than BASIC, and, using this system, not much harder to do. Thus, the higher mathematical functions of BASIC can be combined with the speed of ML code for much more effective programs.

Pitchurs

The graphics of the ATOM are of a resolution equal to that of the APPLE in high resolution mode; 256 X 192 pixels. The BASIC graphics commands are DRAW, MOVE and PLOT, plus CLEAR X, where X is a graphics mode from 0 (regular mode: graphics off) to 4 (high resolution, very slow). The in-betweens trade off resolution for speed.

The graphics instructions are very easy to use, and probably don't require much explanation. Points are specified in whatever size matrix has been selected by the CLEAR command; (0,0) is in the lower left. To produce a vertical line down the middle of the screen in high resolution mode, one would first MOVE (128,0) and then DRAW (128,192). PLOT, of which DRAW and MOVE are subsets, offers several different options, but is slightly more complex to use.

Interesting effects can be achieved with a DO loop and a DRAW

statement in which both co-ordinates are random.

While the system does not have CIRCLE and ARC functions per se, you can illuminate individual pixels easily enough, and thus generate non-straight lines. Three dimensional plotting routines are also quite easy.

Bits and Nibbles

Actually using the ATOM... you knew we'd get to this eventually... is fairly easy. While there are a few operating systems that are easier to use in this respect, the ATOM's is by no means unpleasant to work with. Text is entered in the usual way. Shifted characters come up reversed out. In fact, the reversed upper case characters can very easily be replaced by lower case, un-reversed ones, and Acorn sells a software package that provides a full upper-lower character set plus a character programming routine to generate your own symbols. Character sets, nothing more than a string of bytes, can be saved on tape.

The character set also contains a moderate group of graphics characters, including some that are grey. Neat, that.

Screen editing is where most systems fall down; the ATOM does stumble a bit. In order to change a line, one cursor up to it, and uses a key marked COPY to enter it back into the BASIC line buffer along with any changes. This is not quite so convenient as the PET/VIC system (which spoils one), but not nearly so bad as having to retype every line you want to change.

There are a number of control characters for use on the ATOM which live in the lower range of the ASCII character set. These do things like cause the internal speaker to beep, suppress and unsuppress the listing of ML code assemblies, and set and unset the page listing mode. This last bit is quite convenient for debugging programs, as it allows you to list a program 32 lines at a time: striking any key moves on down to the next page. The control characters never show up as PRINTable symbols, and, even if you type one between quotes, you just get what appears to be a null set. They do exist in these circumstances though, ghostly and haunting, and, for instance, you can use the ASC function on them and get real live numbers back.

The ATOM's error messages print out error codes, as opposed to word messages like "SYNTAX ER-



ROR". However, it doesn't take long to learn them (they are, of course, all listed in the manual), and they're good for beguiling friends and family into thinking you know what you're doing. Foolish friends and family.

Each and every ATOM comes with a little plastic card with all the error codes on it, and, if you don't use it as a bookmark somewhere, it comes in most handy.

All in all, the ATOM's operating system is quite workable. It represents a useful tradeoff between ease of operation and flexibility (as must all systems). Our ATOM didn't flash a "TILT" sign and emit smoke, even once. Must be a good sign.

ATOM vs VIC

One question that's bound to come up is which of the two small systems we've reviewed to date is better. Both the VIC and the ATOM are in same price range, and have many of the same features, but there are, obviously, differences.

The VIC has several advantages and a few failings. First off, its operating system, specifically, its screen editor, is easier to use. Its cassette system is second to none, although, at \$120.00 for a bona fide Commodore cassette recorder to take advantage of this, it's also fairly costly. It has four sound generators to the ATOM's one, although they can't be as accurately programmed. The VIC's sound is also not dependant upon an internal squeaker-speaker, but plays through the TV (which may well have its own internal squeaker-speaker). The VIC can accept games-in-ROM, while the ATOM must have them loaded from tape.

The advantages of the ATOM are also fairly impressive. The graphics commands are all on board, while they must be purchased separately and plugged into the VIC. In addition, the ATOM's resolution is higher — 256 X 192 to the VIC's 160 X 160. (The VIC's claim to 1024 X 1024 point graphics is a bit tricky; you can specify plotting in this size plane, and VIC picks the nearest dot in its 160 X 160 matrix.) The VIC's plug-ins hang outside the machine, while the ATOM manages to contain most of its within its case. The ATOM's machine code assembler is a big plus, and, even though one can be bought for the VIC and plugged in, it is not as sophisticated, and doesn't allow ML programming in BASIC (yes, I was rather impressed with that bit). While the ATOM does not have a games port with A/D converters like the VIC,

it does have two general I/O ports which could easily be used to implement a joystick, or any of a number of other functions. For about the same price, the ATOM comes with 12K of RAM, while the VIC has only 5K. Both are, of course, expandable.

The VIC utilizes an external VHF modulator to feed a TV. The ATOM's modulator is built in, and runs on UHF channel 36. This latter approach is nice, because one need not switch between the computer and broadcast TV signals (unless you actually want to look at something on UHF).

ATOMic Software

Aside from the ATOM, Torch Computers, Acorn's Canadian manifestation, also offer a flock of software. When you review a computer, computer makers are prone to lending you a bunch of this to mess with. The following is a list of some of our favourites.

● *Green Things* According to its description, this should be an exceedingly dull game, but, in fact, it's wholly captlvating. You wander through a deserted space ship, the map of which is provided. There are small green things, big green things and eggs here, there and everywhere. There are also weapons, of which you can carry two, with which to fry the filthy things. They shrink, they shrivel, and, in time, you usually snuff it. Good family fun. A bit like Devil's Dungeon.

● *Space Invaders* The pub game of all pub games, and nicely done. Save Earth and the human race in the privacy of your own home. The machine also does sound effects. What more needs be said?

● *Dodgems* A game in which you try to steer your car around a track without getting mashed by other traffic. Fast, but too much like real life at 5:00 in the afternoon for my taste. Besides, there're no pedestrians to hit.

● *Asteroids* In fairness, not quite as good as the pub Asteroids, but really close. You pilot a tiny space ship around the galaxy mindlessly blowing up helpless rocks, trying not to get crunched yourself. Intensely stupid, but satisfying to play.

● *Breakout* As near as I have ever been able to figure, Breakout simulates playing squash with a ball made out of anti-matter. Every time you fling it against the wall a brick vanishes. A bit of a classic, and if you buy Asteroids you get it anyway.

● *Zombie* Right up there with In-

The ATOM's cassette system is not as easy to use as the VIC's, 'tis true, but this may not be too heavy a trip if you're eventually going to spring for a disk. Disks are getting cheaper all the time.

At the moment, the ATOM is a black and white machine, although a colour card will be available shortly, and will, according to the machine's masters, be very cheap.

The answer to the question of which is better is, of course, dynamically fuzzy. If you're new to computers, and want an easy system

Continued on page 78

terstellar Camel Killer for sensible plots, *Zombie* is based on the premise that your plane crash lands on *Zombie* island, which is populated by, yes, you've guessed it, *Zombies!*. Your only hope of surviving is to lure them into the swamp or jump into hyper-space. Still, there are very few good computer games around with swamps in them. The only other one that comes quickly to mind is bog chess.

● *Soft VDU* In the non-game category, Acorn has several very nicely put together utilities. *Soft VDU* replaces the ATOM's regular character set with upper and lower case letters in your choice of either black on white or the obvious white on black. A third program on the tape lets you generate your own characters.


● *Utility Pack 1* This tape has three useful programs, which, though not so exciting as *Space Invaders*, are, none the less, quite valuable once you get into all this. *Disassembler* digs out machine language op code and turns it back into source code. *Fast COS* increases the baud rate of the cassette operating system by a factor of four. *Renumber* takes that horrible mess of a BASIC program you wrote last night at 5:00 AM and makes it come out looking almost logical, with statements at fixed intervals.

The software tapes each cost about \$29.00, and come with complete operating instructions. The games are, for the most part, very good. On the average, of the three games on each tape, one is superb and the other two make you feel like you're getting a little extra for your bread.

Torch Computers informs us that more software is even now spied upon the horizon, and should be docking shortly.

The Fun of Electronics

TESTING DEPT.

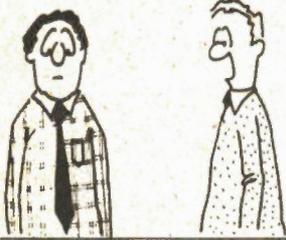


GEIGER

After we test them electrically,
we give them a short
written exam.



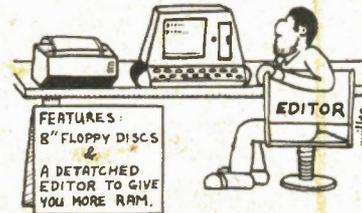No I'm not de-bugging my program
I'm searching for a contact lense.



FEATURES:
8" FLOPPY DISCS
&
A DETACHED
EDITOR TO GIVE
YOU MORE RAM.

EDITOR




ACKWELL

Oh, that? It was a computer for Revenue Canada.




GEIGER

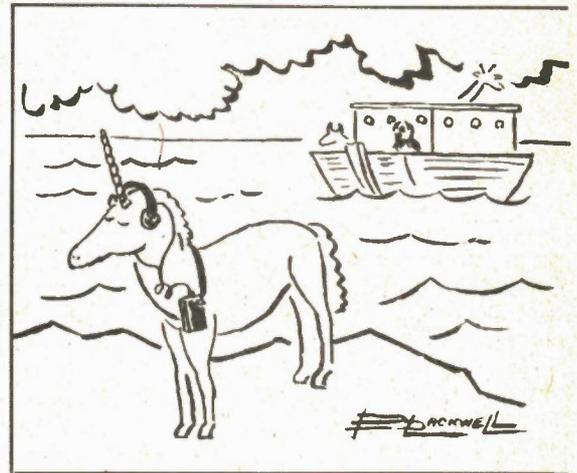
And here's where we manufacture our new "Flat-type"
Batteries.



ACKWELL

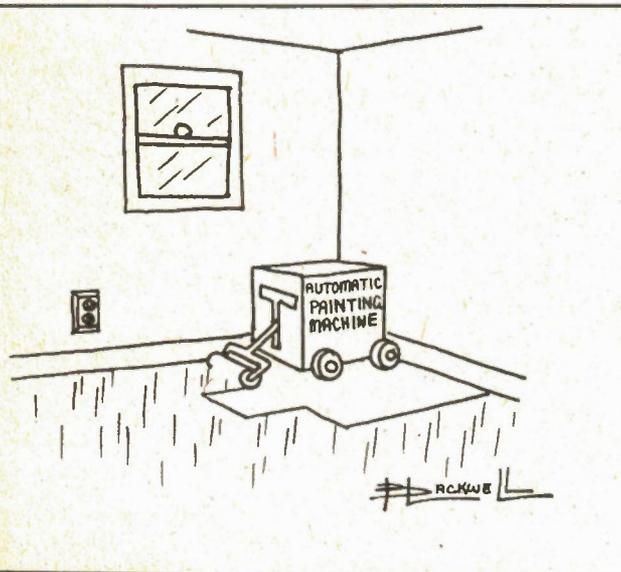

ACKWELL

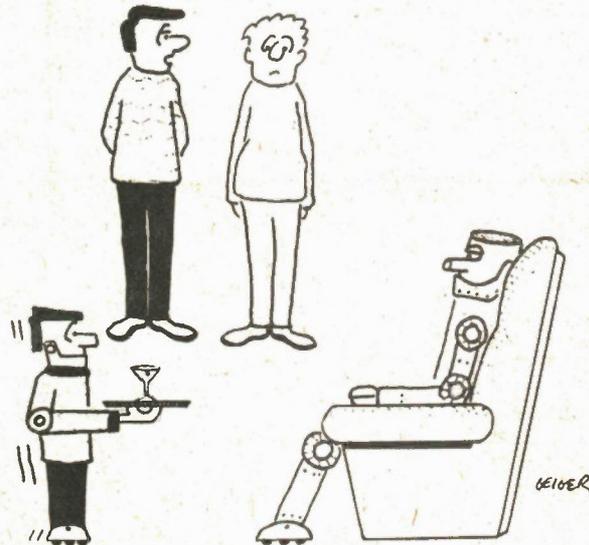

GEIGER

That robot servant I built is too intelligent — he built
his own robot servant.


Now NRI takes you inside the new TRS-80 Model III microcomputer to train you at home as the new breed of computer specialist!

NRI teams up with Radio Shack advanced technology to teach you how to use, program and service state-of-the-art microcomputers...

It's no longer enough to be just a programmer or a technician. With microcomputers moving into the fabric of our lives (over 250,000 of the TRS-80™ alone have been sold), interdisciplinary skills are demanded. And NRI can prepare you with the first course of its kind, covering the complete world of the microcomputer.

Learn At Home in Your Spare Time

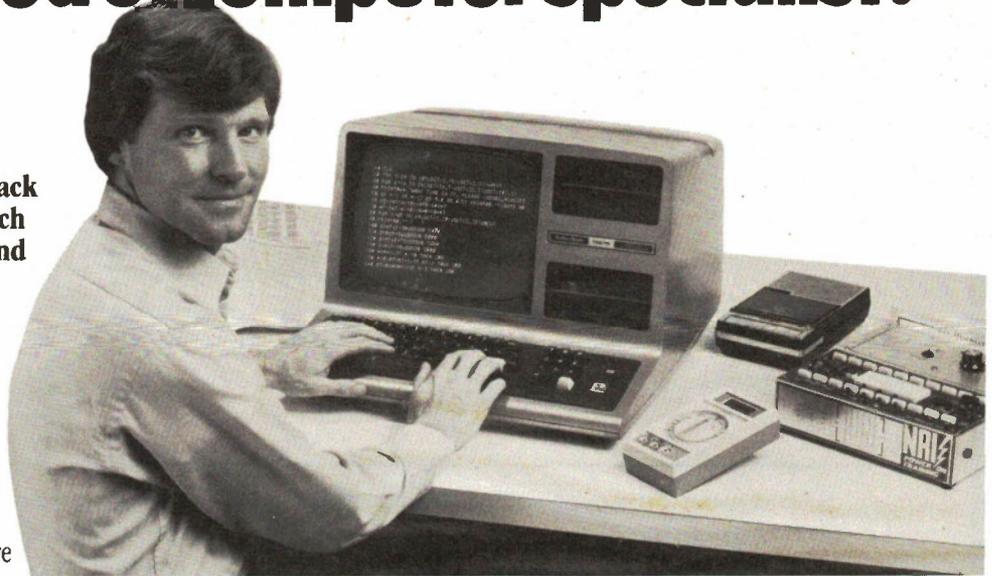With NRI training, the programmer gains practical knowledge of hardware, enabling him to design simpler,



more effective programs. And, with advanced programming skills, the technician can test and debug systems quickly and easily.

Only NRI gives you both kinds of training with the convenience of home study. No classroom pressures, no night school, no gasoline wasted. You learn at your convenience, at your own pace. Yet you're always backed by the NRI staff and your instructor, answering questions, giving you guidance, and available for special help if you need it.

You Get Your Own Computer to Learn On and Keep

NRI training is hands-on training, with practical experiments and demonstrations as the very foundation of your knowledge. You don't just program your computer, you go inside it... watch how circuits interact... interface with other systems... gain a real insight into its nature.

You also work with an advanced liquid crystal display hand-held multimeter and the NRI Discovery Lab, performing over 60 separate experiments. You learn troubleshooting procedures

and gain greater understanding of the information. Both microcomputer and equipment come as part of your training for you to use and keep.

Rush Card for Free Catalog

Get all the details on this exciting course in NRI's free, 100-page catalog. It shows all equipment, lesson outlines, and facts on other electronics courses such as Complete Communications with CB, TV/Audio and Video, Digital Electronics, and more. Keep up with the latest technology as you learn on the latest model of the world's most popular computer. If card has been used, write to:

NRI Schools
McGraw-Hill Continuing
Education Center
330 Progress Avenue
Scarborough, Ontario M1P 2Z5
or telephone 416-293-1911

We'll give you tomorrow.



Training includes new TRS-80 Model III microcomputer, 6-function LCD Beckman multimeter, and the NRI Discovery Lab with hundreds of tests and experiments.

(TRS-80 is a trademark of the Radio Shack division of Tandy Corp.)




INSTITUT SUPERIEUR D'ELECTRONIQUE INTERNATIONAL SCHOOL OF ELECTRONICS

Proudly Presents:

Correspondence Courses in Electronics and Programming with VIDEO TAPES Given in ENGLISH OR FRENCH.

Your course will be just like you are in a live classroom with your teacher. Learn with your TV and VIDEO TAPES. If you don't understand a lesson, just rewind your video tape and play your lesson again and again until you fully understand your course.


ELECTRONICS

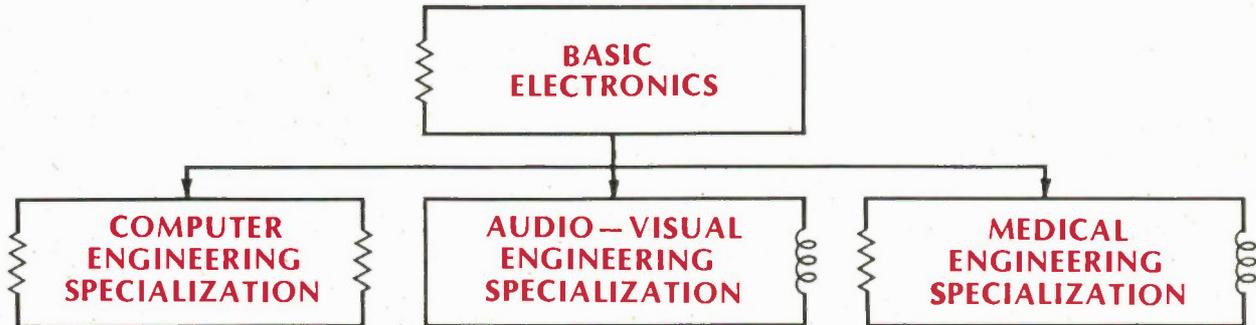

Upon completion of Basic Electronics you can choose one of the specializations mentioned above: COMPUTER ENGINEERING, AUDIO VISUAL ENGINEERING, MEDICAL ELECTRONIC ENGINEERING. Included are three electronic instruments in kit form.

— Instruments and Computer Kit included with the course.

PROGRAMMING

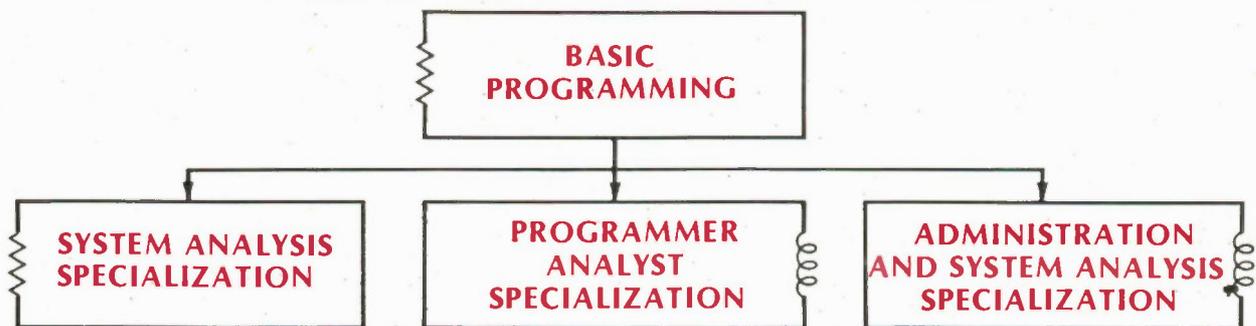

Upon completion of Basic Programming you can choose one of the specializations mentioned above: SYSTEM ANALYSIS, PROGRAMMER ANALYST, ADMINISTRATION AND SYSTEM ANALYSIS. A Microcomputer is included in the course.

OTTAWA: St. Patrick School
290 Nepean Street
Ottawa, Ont.
K1R 5G2
Phone: (613) 232-2647.

MONTREAL: 1435 Bleury,
Suite 501
Montreal, Que.
H3A 2H7

SEND FOR FREE BROCHURE

Send to: St. Patrick School, 290 Nepean Street,
Ottawa, Ont., K1R 5G2

NAME _____

STREET _____ APT _____

CITY/TOWN _____ STATE/PROV. _____

POSTAL CODE _____ DATE _____

Signs of the Times

Imagine a teeny tiny Times Square sign made out of a truckload of LEDs. Decidedly *not* a construction project, but a fascinating application of technology. Steve Rimmer observes.

If you liked this article, please circle Reader Service Card number 49. If you didn't, circle number 50.

MOST OF US REGARD computers as the universally programmable sorts of machines one usually runs into. By their definition, computers are not dedicated to single tasks, but are capable of being "taught" to do any one of many. However, this is not always true; microprocessors are so cheap and so powerful that it's eminently practical to utilize them for other than general computer functions. They are frequently found incorporated into non-computer applications, often in place of more primitive mechanical devices. The result is usually a twofold improvement in whatever is happening; power consumption, noise, heat, time delay and down time are reduced, and the overall sophistication of the system is frequently increased.

We found a really nice example of this in a group of electronic signs offered by Versa-Digital Technology Incorporated of Toronto. Essentially "Times Square" type moving character displays made up of rather large arrays of LEDs (or incandescent bulbs for larger signs), these things seem to represent electronic sign technology taken to its most extreme limit. For example, how often does one see a plain neon sign... with an RS-232 interface?

The basic sign consists of an extruded aluminum case with decorator-type wood ends, and a glass front panel covering a PCB just encrusted with red LEDs. It can display a single row of twenty-one characters created by 5 x 8 dot matrixes of illuminated LEDs. The 5x8 matrix, as opposed to the more common 5x7 approach used with some CRT dot matrix character generators, allows for proper descenders on lower case characters.

The LED display is most easily thought of as a CRT, actually, and many of the functions found on the signs are equivalent to those encountered when using a small computer hooked up to the tube.

The signs are available in larger arrays, too. Thus, the single 21 character display can be extended to a single row of 42, and four 21

character boards can be arranged to produce two lines of 42 characters each. In this case, the display can also produce a single row of characters which are double sized. More on the permutations in a second.

Now, at one time, the news sign in Times Square, the great granddaddy of these things, was, in fact, operated by a revolving wooden disk that used nail heads as contacts to switch on the lights. Fig. 1, a block diagram of the internals of one of these signs, will give you an idea of just how far things have come since then. The controller for the LED display is a Z80A based computer, and not a shabby one at that.

A far cry from shirt cardboard and a Doodle-Art pen, to be sure.

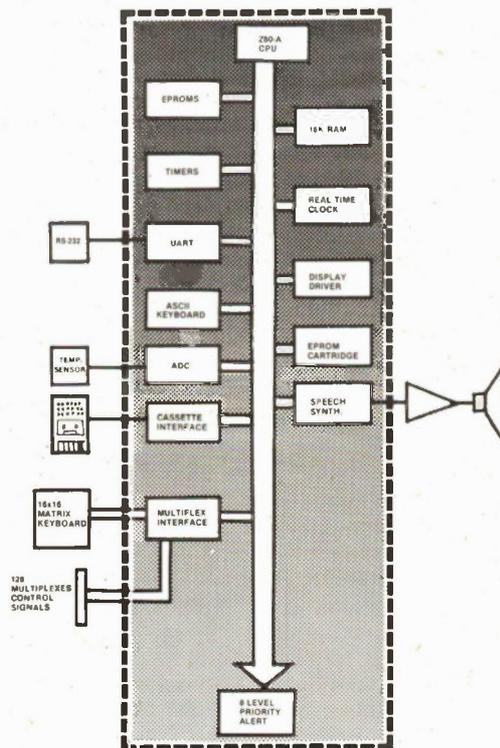


Fig. 1 Block diagram of the Versa Digital Electronic Sign.

Hardware

The stuff that hangs off the Z80A bus is really only moderately sophisticated; it's just so unusual to find it in one box, and that for the sole purpose of advertising a sale on Coke. Let's have a look at all this regalia.

- The EPROMS hold the operating system, which, as we'll see, is quite something. They also hold any basic messages that the user wishes to have available all the time, plus the character set. There are 100 user definable characters which the manufacturer can set up to suit any application.

- The 16K of RAM is partially used by the operating system. However, 13K is available to hold up to 128 user defined messages, which can be entered via an ASCII keyboard.

- The three software programmable timers are involved with the speed with which things on the display happen, such as crawl and scroll rates, message change rate, and so forth.

- The real time clock will provide a display of the correct time and date. As well, it permits programmed sequences of messages to be set up for months in advance.

- The UART will feed an optional RS-232 interface so that the sign can be re-programmed over a phone or radio link.

- The ASCII keyboard allows the user to program and change messages. Messages can also be loaded via pre-programmed EPROM packs. One example of a use for this latter feature is that if every MacDonald's had one of these signs and Ronald MacDonald died of a special sauce overdose, head office could send out proper obituaries to all the locations on chips.

- The Analog to Digital Converter allows the sign to display as a message any analog quantity, such as the temperature, as reported by a remotely located sensor.

- The cassette interface allows messages and other programming to be loaded from tape... useful if you have a whole raft of different

SIGN OF THE TIMES

things to display under different circumstances.

● Now for the weirdies. The 256 key input keyboard is separate from the ASCII keyboard, and is used so that people looking at the sign can communicate with it. Oh, really? Yes, well, signs like conversation too, you know. For example, the sign might display a general message about a list of items. Passers by could hit a key on the keyboard corresponding to an item of interest, which would interrupt the general message for more detailed information regarding whatever it is they're interested in.

● Next, we have 128 multiplexed output lines, which can control other sorts of attention getting displays. For instance, if the sign were to be displaying a directory of a store, and someone was to ask it for the location of the elephant gun section, some of these lines might be used to light up an arrow pointing the way. The arrow to be made up out of red LEDs, of course; it goes with the decor.

● No intelligent sign would be complete without a speech synthesizer, of course. Ah, you don't think so, either. Well, then, you'll be



Fig. 2 A sign in real life, with two rows of 42 characters each.

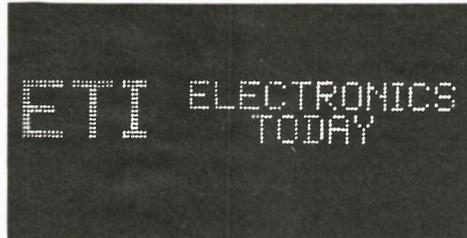


Fig. 3 Advertising.



Fig. 4 More advertising.

pleased to find one herein, as well. It uses the TI voice synthesis chip set, which is ROM programmable, and can emit any sorts of verbalizations the user desires. Custom speech sets can be ROM'd by TI from a tape. The processor can announce at any programmed time to proclaim store specials, 8 bit ballyhoo or the end of civilization.

The bus also controls the display, of course.

Furthermore

Versa-Digital also custom build signs, if their standard ones aren't sufficiently strange for a particular application. Variations are available to drive incandescent bulbs instead of LEDs, and we've heard rumours of a four foot high version. More LED display boards can also be stacked to increase the width or depth of the screen.

Versa Digital Technology is a relation of Exeltronix, which produces the Multiflex Z80A computer system (see ETI May 1981). The signs start at \$1350.00 Canadian. For more information contact Exeltronix Components and Computing Inc., 319 College Street., Toronto, Ontario M5T 1S2, telephone (416) 921-5295

ETI

POKEing on the ZX80 again

A few months back we showed you the basics of using screen POKES on your ZX80. This month we round it all off with an example program.

Graphic Example

Just for fun, here is a simple program that demonstrates the features discussed in the last article. It just fits in the 1K ZX80. The

computer prints up a display consisting of black and grey squares in a pattern determined by a number input at the beginning of each series of games. The object of the game is to get the "woodworm" (an asterisk), which first appears at line 8 column 1, to eat its way across the screen to column 32 in the least number of moves. The snag is that the black squares represent a particularly tough kind of wood and each time one is eaten a penalty of 5

moves is incurred. Numerals 6, 7 or 8 are input as pseudo-cursor controls to move the insect down, up, or forwards respectively. The computer keeps track of the number of moves to reach column 32 and displays the total at the end of each game together with the best performance in the present series. Pressing NEWLINE after a game sets up another game in the same series. Entering a character starts a new series.

```

2 LET Y = 32000
4 INPUT R

8 LET P = 0
10 LET W = 0
12 LET B = 1
14 LET A = 8
16 LET Z = -1
18 LET M = 0
20 RANDOMISE R

22 FOR N = 1 TO 352
24 LET D = 9
26 LET X = RND(2)
28 IF X = 1 THEN LET D = 128
30 PRINT CHR$(D);

32 NEXT N
34 GOSUB 500
36 POKE W + 232, 20
38 LET Z = Z + 1
40 INPUT C
42 GOSUB 500
44 LET M = W + (A - 1)*33 + B
    
```

No. of moves — best so far!
Seed for random number generator

Assign variables prior to PEEK and POKE

Set seed for random number generator

Print eleven lines with black and grey squares at random. Pattern determined by R.

Locate display-file
Insect in initial position
Count No. of moves
Which way?
Locate display-file

```

46 POKE M, 0
48 IF C = 6 AND A < 11 OR C = 7 AND A > 1 THEN LET A = A - 2 * C + 13

50 IF C = 8 THEN LET B = B + 1
52 LET M = W + (A - 1)*33 + B

54 IF PEEK(M) = 128 THEN LET Z = Z + 5

56 POKE M, 20
58 IF B = 32 THEN GOTO 62
60 GOTO 38
62 IF Z < Y THEN LET Y = Z
64 PRINT "END OF GAME IN " Z; " MOVES"
66 PRINT "BEST SO FAR " Y; " MOVES"
68 INPUT XS
70 CLS
72 IF XS = " " THEN GOTO 8
74 RUN
500 LET P = PEEK(16397)
510 IF P > 127 THEN LET P = P - 256
520 LET W = PEEK(16396) + P * 256
530 RETURN
    
```

Put a space where insect is
Set A and way and make sure we don't POKE off-screen

Set M to next insect location address
If there's a black square in the way, add penalty
Put insect in next location
Watch for end of game
Next move
Set Y to best so far

NEWLINE for another game
Any character for another series

Subroutine for setting W to address of start of display-file

ETI

RAEKIT

STROBE LIGHT KIT



\$29.95
#1606-2

- Adjustable flash rate
- Audio input with sensitivity control — flashes to music
- Includes parts, pc board, case, polished aluminum reflector
- Easy to build!

\$19.95

#1606-1 less case & reflector

MAIL ORDER INFORMATION

Payment by, VISA/Mastercard (Include signature, number and expiry date), cheque or money order. Add \$2.00 for shipping, B.C. residents add 6% Sales Tax.

Visit our new Edmonton store

RA-E Industrial Electronics Ltd.
3455 Gardner Court, Burnaby, B.C.
V5G 4J7 Phone: (604) 291-8866



Circle No. 4 on Reader Service Card.

VERO

For the Professional Amateur

VERO can offer a complete package to help you build your product to a truly professional standard. Full range of veroboards, accessories and housings. For your free catalogue circle no. 14 on Reader Service Card.

ELECTRONIC PACKAGING SYSTEMS LIMITED
Retail Department
P.O. Box 481, Kingston, Ontario K7L 4W5
Telephone: (613) 384-1142
Dealers reply on letterhead.

Circle No. 14 on Reader Service Card.

ETI—February 1982

SATELLITE TV

DEXCEL DXP 1000 SATELLITE SYSTEM

\$2995

The DXP 1000 system is the latest in state-of-the-art satellite communication components from DEXCEL. The system consists of the DXR 1000 Receiver and the Dexcel low-noise amplifier/down-converter. It is designed for audio and video reception superior to standard earth facilities.

A six-channel audio selector allows the complete selection of six subcarriers, and the DXP 1000 is able to receive 24 distinct channels with amazing clarity. The 70-MHz Input connector accepts standard coaxial termination from the antenna.

604) 324-3343 Nu. West Video Systems Ltd.
6590 VICTORIA DRIVE, VANCOUVER B.C. V5P 3X9

Circle No. 13 on Reader Service Card.

omnitronix Ltd.

INJECTORALL

FINGERS TO DONUTS

KIT 650

Photo-Etch Kit for Printed Circuits with Negative Acting Resist

KIT 650 is a complete kit using a photographic method to produce professional quality printed circuits. No dark room is necessary. Contains 2 photo-sensitized 3 x 4" phenolic boards, a photographic test negative & an ultraviolet light source. Materials are included to make negatives of magazine layouts. Also contains exposure glass, clamps, developer, etchant, trays, resist remover, drill and complete instructions. Ideal for solid-state and integrated circuits. Packed in a display box. Weight 3 lbs.

No. 650 KIT • Photo-Etch Kit for single-sided boards with negative acting resist.


2056 Trans Canada Hwy. Unit 7, 6295 Shawson Dr.
Dorval, Quebec. Mississauga, Ontario.
H9P 2N4 L5T 1H4
(514) 683-6993 (416) 678-7170
Telex: 05-822692 Telex: 06-968653

Circle No. 3 on Reader Service Card.

37

Industrial Robots

Roger Allan
Reports

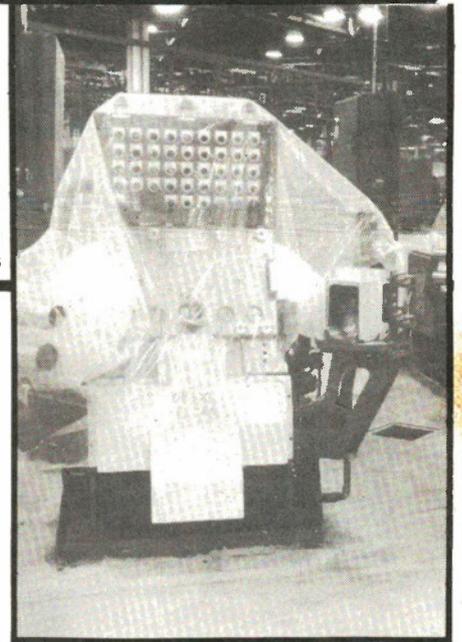

Robots in Waiting; new piston ring assembly machines at the Ford plant in Windsor, Ontario.

ROBOT: a more than humanly efficient automaton — Chambers Twentieth Century Dictionary.

ROBOT: a machine in the form of a human being that performs the mechanical functions of a human being — Websters Dictionary.

ROBOT: a reprogrammable multifunctional manipulator designed to move material, parts, tools or specialized devices through variable programmed motions for the performance of a variety of tasks — Robot Institute of America.

ROBOT: a manipulator whose function is similar to that of human upper limbs — Japanese industrial definition.

SO WHAT IS A ROBOT? Best, as the Red King said to Alice, to "Begin at the beginning, proceed to the end and then stop."

Actually, the word robot is derived from the Czech word 'robotus' meaning 'forced labour'. It first appeared in 1921 in the title for the stage play R.U.R. (Rossum's Universal Robots) by Karel Capek — a self styled 'fantastic melodrama' in which robots, constructed without any feelings or soul ("God hasn't the slightest notion of modern engineering") do all the world's work, wage all the world's wars and finally rebel and destroy their makers. After all, as the leader of the robot rebels tells the General Manager of the factory that produced him (it?), "You are neither as strong nor as skillful as we robots. I want to be master."

But despite the 60 year age of the word 'robot', robots have been cropping up in history for quite some time. In about 375 BC Archytas of Tarentum built a robot bird which flew, or at least so he records. *De Automattis* written by Hero of Alexandria in the 2nd century BC tells of a theatre in which robot figures danced for temple ceremonies. Johan Nepomuk Maelzel in the early 1800's built a robot orchestra of some seven instruments, for which he commissioned Beethoven to compose his *Vit-toria Symphony*. Regretfully, Maelzel's other robot, this one a robot chess player and taken on a grand

tour through Europe and North America, left something to be desired. It was actually operated from the inside by a hunchbacked Alsatian dwarf named Schlumberger. But giving credit where credit is due, Maelzel's Panharmonium did work.

There are many other examples of descriptions of robots in history. In the realm of mythology the first humans were robots formed out of clay by the Titan Prometheus. In the realm of literature, perhaps the most noted example, courtesy of the fertile mind of Mary Shelley, is Dr. Victor Frankenstein's triumph in creating The Monster. And so on.

With such a panoply of possible definitions to be derived from history, combined with the apparent inability of the dictionaries to agree on a definition, compounded by the unwillingness of American and Japanese industrialists to agree on a definition, coupled with the layman's mental image of an R2D2 or a 3CP0 running around in the midst of an intergalactic civil war, it is perhaps best to just arbitrarily pick a definition: in this case the Robot Institute of America's: a reprogrammable multifunctional manipulator designed to move (things) through variable programmed motions for the performance of a variety of tasks.

Not very elegant, but certainly utilitarian. Just like a robot.

Six Different Types.

If one takes the RIA general definition, one then has to divide robots into six different types, based on coordinate systems used and the incorporation of servo units.

Basically, robots can be either servo-operated or non-servo operated. In a non-servo operated system there are only two positions for each axis to assume, eg. either end. Occasionally it's possible to incorporate intermediate stops on some axes to provide more than two positions, but this is rare. They are therefore limited to the performance of a single program. Programming is determined by setting up the desired sequence of moves and adjusting the

end stops of the various axes. They are customarily cheaper than servo operated robots, as they are simpler in their mechanics and cheaper to maintain and program.

The servo-operated robots have the fundamental difference in that they can be programmed to move and stop within their limits of axis at any point. The number of axes may number up to seven. Due to the servos it is possible to control the acceleration, and velocity of movement. Further, as the memory is larger, more positions can be programmed into the memory, permitting them to adjust to different needs. An example is the truck spraying robot at the GM plant in Oshawa which has memorized the configuration of four different truck bodies, can automatically determine which body is currently to be sprayed, and therefore which combination of movements of the spray head are necessary. Further, the robot automatically determines which of 20 different colors are to be used, making a grand total of 80 different combinations of movement and color. Needless to say, servo operated industrial robots are far more expensive than non-servo operated ones.

The next major division of industrial robots is based on the coordinate system. Basically, there are three types. In the Cylindrical Coordinate System, the arm moves horizontally and vertically about a hypothetical column shape. All the

thandar

Professional quality at hobbyist prices!



Was \$529.95 **\$419.95**


SC110 SINGLE TRACE LOW POWER 2" OSCILLOSCOPE	
Bandwidth:	DC to 10MHz
Sensitivity:	10mV/division to 50V/division
Sweep Speeds:	0.1µsecs/division to 0.5 secs/division
Power Requirements:	4 to 10V DC from 4°C cells or AC adaptor
Size:	255 x 150 x 40mm
Weight:	800gms excluding batteries
Accessory probes for SC110 Oscilloscope:	
x1 Proba	\$27.95
x10 Proba	\$29.95
Special Package: SC110 Scope, x1 probe, x10 probe, AC adaptor, carrying case. Save \$15.00! Complete for \$512.00	



PULSE GENERATOR
TG105 Was \$315.00 **\$249.95**

TG105 5MHz PULSE GENERATOR	
Period:	200nsec to 200ms (5MHz to 5Hz)
Pulse Width:	100nsec to 100ms, independent of period.
Operating Modes:	Run, Triggered, Gated, One Shot, Square Wave and Complement
Outputs:	0.1V to 10V variable 50Ω output; Separate TTL output; Sync. output
Power Requirements:	120V or 240V AC (nominal) 50/60Hz
Size:	255 x 150 x 50mm
Weight:	1200gms

FUNCTION GENERATORS

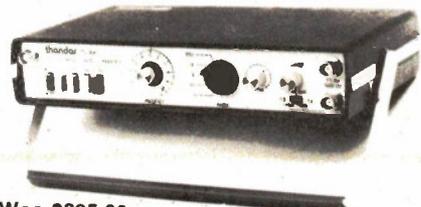

Was \$325.00
TG100 **\$255.00**

TG100 100kHz FUNCTION GENERATOR	
Frequency Range:	1Hz to 100kHz
Functions:	Sine, Square, Triangle and DC from variable 600Ω output. External sweep input permits >=300:1 linear sweep below range maximum, i.e. below 0.1Hz on 10Hz range.
Outputs:	1mV to 10V from variable 600Ω output; variable DC offset to +5V. TTL output.
Power Requirements:	120V or 240V AC (nominal) 50/60Hz
Size & Weight:	255 x 150 x 50mm : 1200gms

TG102 2MHz FUNCTION GENERATOR \$465.00	
Frequency:	< 0.2Hz to 2MHz
Functions:	Sine, Square, Triangle and DC from variable 50Ω output. External sweep: >=1000:1 linear range.
Outputs:	60mV-20V from variable 50Ω output; variable DC offset to +10V. TTL output.
Power Requirements:	120V or 240V AC (nominal) 50/60Hz
Size & Weight:	255 x 150 x 50mm : 1200gms

THANDAR's amazing SC110 OSCILLOSCOPE is less than 2 inches thick and weighs under 2 pounds, yet has the performance of a standard bench scope. Has full trigger facilities including Bright Line and Auto with TV Line and Frame filtering. The SC110 can operate for very long periods of time on low cost disposable cells as well as on rechargeables (has built-in recharger).

TWO NEW INSTRUMENTS! Thandar Brings Low Cost to Temperature Measurement!

The TH301 is a hand-held LCD digital thermometer designed to accept any standard type K (NiCr-NiAl) sensor and offering measurement range of -50 C to 750 C with 1 degree resolution. Accuracy better than 0.5%. 1000 hours battery life from 9V alkaline battery. Price: **\$199.00.**

THANDAR TA2080 20 MHz 8 channel Portable Logic Analyzer

Offers comprehensive triggering, recording, and display capabilities at an affordable price. The TA2080 is controlled by a Z80 microprocessor linked to an interactive keyboard. Full system status is shown at all times in the top lines of a 5-inch CRT and simplicity of operation is achieved by display prompting.

Recording memory depth is 252 bytes and a 252 byte reference memory is provided which can be loaded directly from the recording memory or from keyboard.

Extensive triggering capabilities include 23 bit trigger recognition facility, powerful compound trigger delay by trigger event and/or clocks, a selectable trigger position, variable trigger filter, and an input arm.

Price: under \$7000. Please contact us for a brochure.



TM353 3 1/2 DIGIT	
Measurement Capability:	
DC and AC volts :	100µV to 1000V (750V AC rms)
DC and AC current :	100nA to 10A (20A for 10 secs)
Resistance :	100mΩ to 20MΩ
Accuracy: Basic accuracy: ±(0.1% of reading + 1 digit)	
Battery life: Up to 4000 hours from 6 alkaline 'C' cells	
Size: 255 x 150 x 50mm	
Weight: 1200gms including batteries	



TM353 3 1/2 DIGIT	
Measurement Capability:	
DC and AC volts :	100µV to 1000V (750V AC rms)
DC and AC current :	100nA to 2A
Resistance :	1Ω to 20MΩ
Accuracy: Basic accuracy: ±(0.25% of reading + 1 digit)	
Battery life: Typically 3000 hours from 6 alkaline 'C' cells	
Size: 255 x 150 x 50mm	
Weight: 1200gms including batteries	

TEST INSTRUMENTS

Gladstone Electronics Sales Policy on Thandar Instruments:

- TEN-DAY TRIAL.** You may return any Thandar test instruments within 10 days of purchase for full refund, (provided unit is in original packing in new condition).
- NEW LOWER PRICING POLICY.** Gladstone Electronics is the importer, and by selling direct to the end-user we are able to sell at lower prices ... typically 25 to 45% lower than comparable quality instruments from other manufacturers.
- ONE-YEAR WARRANTY.** Parts and labour on Thandar instruments (except sales items — 90 day warranty).
- QUANTITY PRICING AVAILABLE.** Industry and educational institutions are invited to contact us for details.
- COMMITMENT TO QUALITY.** Thandar Electronics has an ongoing programme of product development and improvement, with an absolute commitment to producing a high quality product at the lowest possible price.



\$447.00

TF200 8-DIGIT LCD FREQUENCY METER	
Frequency Range:	10Hz-200MHz (To 600 MHz when used with TP600 prescaler)
Resolution:	Better than 1ppm across whole range with selection of suitable Gate time.
Sensitivity:	10mV rms 20Hz-100MHz, 30mV rms 10Hz-20Hz, 100MHz-200MHz
Functions:	Frequency, Time-Average Period, Totalize and Reset. 2 ranges, 5 Gate times. External clock facility. Power take-off for optional TP600 prescaler.
Accuracy:	±(1 count + timebase accuracy). Timebase factory set within ±0.3ppm.
Battery life:	Typically 200 hours from 6 alkaline 'C' cells.
Size:	255 x 150 x 50mm
Weight:	1200gms with batteries

\$149.95

PFM200 8-DIGIT LED POCKET FREQUENCY METER

Frequency Range:	20Hz-200MHz (To 600 MHz when used with TP600 prescaler)
Resolution:	Down to 0.1 Hz
Sensitivity:	Typically 10mV rms
Functions:	Frequency only in 2 ranges, 4 Gate times
Accuracy:	±(1 count + timebase accuracy) Timebase factory set within ±2ppm
Battery life:	Typically 10 hours from 9V MN1604
Size:	155 x 75 x 30mm
Weight:	180gms excluding batteries

TP600 — 600 MHz prescaler . . . **\$109.95**

LCD MULTIMETERS

Was \$385.00

\$279.95



Was \$145.00

TM354 3 1/2 DIGIT	
Measurement capability:	
DC volts :	1mV to 1000V
AC volts :	1V to 500V AC rms
DC current :	1µA to 2A
Resistance :	1Ω to 2MΩ
Accuracy: Basic accuracy: ±(0.75% of reading + 1 digit)	
Battery life: Typically 2000 hours from 9V MN1604	
Size: 155 x 75 x 30mm	
Weight: 165gms excluding battery	

GLADSTONE ELECTRONICS

Circle No. 20 on Reader Service Card.

(416) 787-1448

1736 AVENUE RD., TORONTO, ONT., M5M 3Y7

New! Acorn Atom 12K Colour Computer

Telephone orders:
(416) 787-1448
Use Visa, Mastercard
or American Express

Fully assembled
only

\$549.00

complete with manual
(prices valid until
February 28, 1982)



Also available:
**8K ROM/ 2K RAM
Black & White ATOM**
only

\$399.00

Extra memory and colour
may be added!

**ACORN SOFTWARE ON
CASSETTE.**

GAMES PACKS:

Each cassette consists of 3 programs all at one low price. All feature high resolution graphics; challenging and fun!

1. Asteroids. Sub Hunt. Breakout.
 2. Dogfight. Mastermind. Zombie.
 3. Rat Trap. Lunar Lander. Black Box.
 4. Star Trek. Four Row. Space Attack.
 5. Invaders. Wumpus. Reversi.
 6. Dodgems. Simon. Amoeba.
 7. Green Things. Ballistics. Snake.
- Price each pack **\$29.00**

SOFT VDU: provides 128 characters with mathematical symbols. Can be mixed with high resolution graphics, and **DESIGN** program allows new characters to be created. **\$29.00**

MATHS PACKS 1: Plot. Simultaneous equations. Regression. **\$29.00**

UTILITY PACK 1: Disassembler. Fast COS (increases cassette speed to 1200 baud). Renumber. **\$29.00**

WORD PACK ROM: A 4K ROM chip which plugs into the ATOM's utility ROM socket. Ideal for preparation of leaflets, documents, etc. Adds the commands **EDIT** and **TEXT** to ATOM's command set. **TEXT EDITOR** enables upper/lower case, allows insertions/deletions and moving text. **WORD PROCESSOR** enables pages to be printed in any format, justified as required, automatic insertion of page numbers, and many more. All for only **\$75.00**

Will support **PASCAL FORTH**, an **LISP**.

SPECIFICATION

All types are only suitable for +5V single-rail systems.
GR2516—2kBytes, located in the lower half of the 4k slot. 2516 pin-out, suitable for PET/ATOM. **\$109.00**

GR253—4kBytes, occupies the entire 4k slot. 2532 pin-out, suitable for PET/ATOM. **\$157.00**

GR2716—2kBytes, located in the lower half of the 4k slot. 2716 pin-out, in very wide use. **\$109.00**


GR2732—4kBytes, occupies the entire 4k slot. 2732 pin-out, in very wide use. **\$157.00**

The Acorn Atom is a powerful, full facility computer at an extraordinary low price. It has a full size professional keyboard and a hardware/software combination of incredible power and versatility. And it's easy to use! Just connect directly to any domestic TV and you are ready to begin. (AC Adapter optional extra)

FREE MANUAL

**ATOMIC THEORY
AND PRACTICE**

David Johnson-Davies

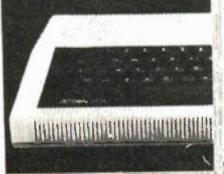

Free with every ATOM is a computer manual. The first section explains and teaches you **BASIC**, the language that most personal computers and the ATOM operate in. The instructions are simple and learning is a pleasure. You'll soon be writing your own programs. The second section is a reference section giving a full description of the ATOM's facilities and how to use them. Both sections are fully illustrated with sample programs.

THE ACORN ATOM 12K COLOUR COMPUTER includes:

Hardware

*Full-sized QWERTY keyboard *6502 microprocessor *Rugged injection molded case *12K RAM *12K ROM *Audio cassette interface *TV output with high resolution Colour Graphics *Sound

Software

*32 bit arithmetic *10 digit floating point math routines *High speed execution *43 BASIC commands *Variable length strings (up to 256 characters) *String manipulation functions *27 additional arrays *Random number function (useful for games & simulations) *Mnemonic assembler *16 letter file names *PUT and GET byte *WAIT command for timing *DO-UNTIL Instruction * Logical operators (AND, OR, EX-OR) *PLOT commands, DRAW and MOVE *Direct printer drive *Link to machine code programs *ASSEMBLER and BASIC may be combined *Many more.

*Expandable internally to 40K RAM.


INSTANT ROM is 2K or 4K of CMOS memory with battery back-up. Just plug it into the socket provided on your PET. Then write your program into it as if it were RAM. Or load programs into **INSTANT ROM** from tape, disc, or some other part of memory. Then remove the Write Enable lead, and your program is there, permanently.

HOW YOU USE IT

You need access to the Write Enable signal in your microcomputer. This is easy in the **PET** — we provide the lead, adaptor, and instructions. There is no soldering or hardware modification. You only need to know how to lift the lid.

OTHER MICROCOMPUTERS

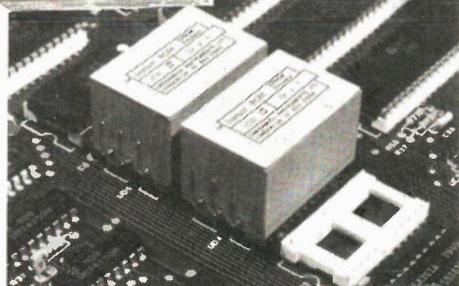We're working on adaptors for other microcomputers, and we can probably advise you. But any microcomputer owner with sockets for 2516/2532 or 2716/2732 EPROMS can consider using **INSTANT ROM**. 3-year guarantee



INSTANT ROM®

(for PET and other microcomputers)

JUST ANNOUNCED: VIC-20 Software Development and Memory Expansion System. ROM-Cartridge Emulator. Write for details!

GLADSTONE ELECTRONICS

Circle No. 24 on Reader Service Card

1736 AVENUE RD., TORONTO, ONT., M5M 3Y7 (416) 787-1448

Sinclair ZX81 Kit.

The heart of a personal computer system that grows with you!

The personal computer that took Canada (and the world) by storm!

Lower price: higher capability.

Sinclair's new ZX81 personal computer is a tremendous advance over the highly successful ZX80. It offers far more computer capability, yet Gladstone Electronics is able to offer the ZX81 in kit form at half the ZX80 price! How is it possible? Quite simply, by design. The ZX81 uses only 4 chips (as opposed to 21 in the original ZX80). The secret lies in the totally new Master chip. Designed by and custom-manufactured for Sinclair, this unique chip replaces 18 chips from the ZX80.

Easy-to-build Kit.

And because the chips have been reduced to only four, the kit is incredibly simple to build. A couple of hours work with a fine-tipped soldering iron and the ZX81 is ready to use.

The ZX81's advanced capability.

The ZX81 uses the same fast microprocessor (Z80A), but incorporates a new, more powerful 8K BASIC ROM — the "trained intelligence" of the computer. This chip works in decimals, handles logs and trig, allows you to plot graphs, and builds up animated displays. And the ZX81 incorporates other operation refinements — the facility to load and save named programs on cassette, or to select a program off a cassette through the keyboard.

New BASIC Manual.

Every ZX81 comes with a comprehensive manual — a complete course in BASIC from first principles to complete programs.

Uses standard TV & cassette.

New, Improved specification.

- * Unique 'one-touch' key word entry: eliminates a great deal of tiresome typing. Key words (PRINT, LIST, RUN, etc.) have their own single-key entry.
- * Unique syntax-check and report codes identify programming errors immediately.
- * Full range of mathematical and scientific functions accurate to eight decimal places.
- * Graph-drawing and animated-display facilities.
 - * Multi-dimensional string and numeric arrays.
- * Up to 26 FOR/NEXT loops.
- * Randomize function.
- * Programmable in machine code.
- * Cassette LOAD and SAVE with named programs.
- * 1K-byte RAM expandable to 16K.
- * Full editing facilities.
- * Able to drive the new Sinclair ZX Printer (to be available shortly).

Kit builder guarantee:

If for any reason should you be unable to complete your ZX81 kit, you may return it with a cheque for \$25.00, and it will be completed and returned to you.

If you own a ZX80 . . .

The new 8K BASIC ROM as used in the ZX81 is available as a drop-in replacement chip. (Complete with new keyboard template and operating manual). With the exception of animated graphics, all the advanced features of the ZX81 are now available on your ZX80 — including the ability to drive the Sinclair ZX Printer. **\$59.95**

Sinclair ZX81 Software on Cassette

- Cass. #1 (ZX81) 5 Games
 - Cass. #2 (ZX81/16K RAM) Junior Education
 - Cass. #3 (ZX81/16K RAM) Business & Household
 - Cass. #4 (ZX81/16K RAM) 6 Games
 - Cass. #5 (ZX81) Junior Education ZXAS Machine Code Assembler (ZX81/16K RAM)
- Your choice, any of above. **\$12.95**

\$149.95

Telephone Orders
(416) 787-1448

Use Visa,
Mastercharge or
American
Express



**16K
RAM
PACK
\$169.95**

**SPECIAL
INTRODUCTORY OFFER**

Sinclair ZX81 Computer Kit PLUS 16K RAM memory expansion module for only \$299.95! Save \$20.00 from individual prices! Due to anticipated high demand, we suggest you order now to avoid disappointment. Allow 14-28 days for delivery. Mail coupon or order by phone.

Gladstone's BUG-BYTE Tapes
GAMES PACK #1. For 1K ZX81, Digiclock, 9 Lives, Sketchpad, Dice and 4 more. **\$12.95**
GAMES PACK #2. For 16K ZX81, Pontoon, Bio-Rhythms, OXO, Fruit Machine. **\$12.95**

ZXDB Disassembler/Debugger (ZX81/16K RAM)

MULTIFILE Data Storage System. A flexible menu-driven system catering for both numerical and string variables. Complete with three data cassettes in attractive case. Extensive documentation and examples. 16K RAM. **\$39.95**

ZX CHESS! Six levels of play with sophisticated features like en passant and castling. 16k **\$29.95**

ADVENTURE: Damsel and the Beast. A game of concentration and suspense. Complex, occasionally frustrating, and entertaining! 16K **\$19.95**


BOOKS ABOUT THE ZX81
Getting Acquainted with Your ZX81 **\$16.95**
50 Rip-Roaring GAMES for ZX81 (and ZX80) **\$16.95**
Understanding Your Sinclair ROM **\$23.95**
Machine Language Made Simple for ZX80 and ZX81 **\$23.95**
ZX81 Pocketbook **\$16.95**
Not Only 30 Programs for ZX81. . . But Also. . . **\$16.95**

GLADSTONE ELECTRONICS

Circle No. 23 on Reader Service Card.

(416) 787-1448

1736 AVENUE RD., TORONTO, ONT., M5M 3Y7

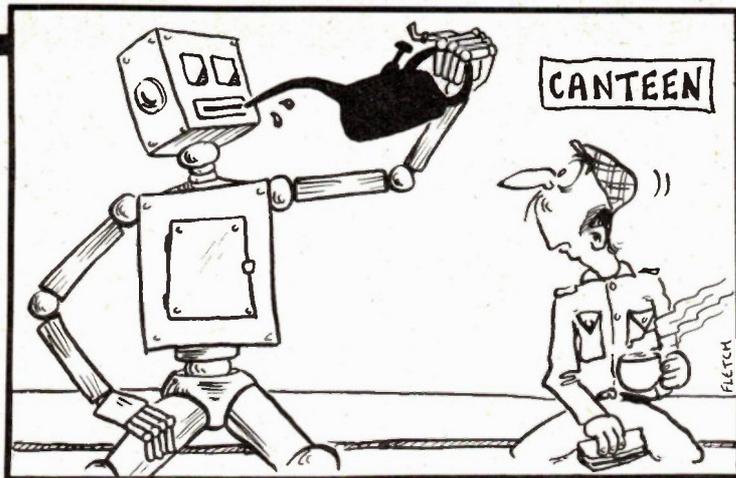

positions at the extremity of the arm describe a portion of a cylinder. In a Spherical Co-ordinate System, the movements are up/down, left/right and in/out. All movements at the end of the arm therefore describe a portion of a sphere. In a Jointed Spherical System the co-ordinates produced are roughly similar to a Spherical Co-ordinate System, but the movements are obtained through arms which roughly approximate the human upper torso: forearm, elbow, upper arm and shoulder. The positions described by the movements are portions of a sphere.

Within the context of servo or non-servo operated robots, the next prime consideration is their means of control. Essentially, there are four general control processes ranging from simplistic to state of the art, with appropriate price tags to match.

The least common control mechanism is the numerically controlled robot. Its command sequence is dependent upon numerical data contained on punched tapes, cards and digital switches. A very simple command structure.

The next most popular system is called a "play back robot" which produces from memory operations originally executed under human control. All the information necessary to run the robot is inscribed in its memory, the information is played back resulting in the operations being repetitively executed.

The most popular control system is the variable sequence robot whereby a robot repetitively repeats the steps of a given predetermined operation. The advantage of this system is that the control program can be very easily changed.

The top of the line, state of the art, control system is the so called intelligent robot. This is a robot with sensory perception primarily visual or tactile but also heat sensitive and chemical composition sensitive,

which is capable of detecting changes in the working condition and environment and thus, by computation within its own memory, proceed with the operation by modifying its movements to fit the changed reality. Very expensive.

Selling Points

The economic justification of robot utilization is both its strongest selling point and rational for existence at all: they save money — lots of it. The average industrial robot is operational 98% of the time, whereas workers in precise heavy machinery can rarely better 80% uptime. It will work where men can't or won't or prefer not to — in areas of high heat, where continuous heavy lifting is required, and in areas that are dangerous to human health. In fact, among the first industrial robots introduced into Canada removed jobs that the workers and their union didn't like doing: spray painting (GM plant in Oshawa) and heavy lifting (Ford plant in St. Catherines). They don't take holidays, require pension and health plans and can be run three shifts a day. Their tolerances are far superior to a working man, who tends to slow down and become sloppy over an eight hour shift, and their rejection rate is infinitesimal. So reliable are their tolerances and lack of down time that industrial robots can be left unattended for long periods leaving them to work away with only an occasional night security guard wandering around on hourly patrols to make sure the factory hasn't burnt down in his absence. The state of the art of this element in robotic money saving opened in February 1981 by the Fujitsu Fanuc company in Japan, where they created an automatic factory to produce industrial robots at the rate of 100 a month (later scheduled to rise to 360/month) using industrial robots for the assembly of other industrial

robots. The firm operates 24 hours a day, is unmanned at night when the robots continue to work, and saves enormous sums of peripheral support money by not having the factory heated, lit or air conditioned during the night shift. After all, what robot is going to launch a union grievance because it's too dark or too chilly? Further, with robots, model changes can be made easily — the machines need not be rebuilt or replaced, only the memory program need be modified. This has enormous cost saving benefits particularly in the automotive industry that customarily has to shut down for weeks on end to incorporate new model changes. Combined with the low average running costs (1975 \$5.00/hr: 1980 \$5.25/hr) and the average high industrial worker's pay and fringe benefit package (1980 average \$16.40/hr) the reasonably high prices (\$10,000 to \$105,000) can be amortized over three years at the worst. With an average life expectancy of eight years an industrial robot, while not quite a licence to print money, certainly makes more than economic sense.

But what of the workers the robot replaces?

Three World Models

There are, essentially, three managerial models: the Japanese, the Communist and The Rest of Us.

The simplest to define is the Communist: To each according to his need, from each according to his ability. Every worker displaced is automatically guaranteed a job, with no loss of benefits. One's replacement job may not be in the same company, nor may it be a job one might wish to hold — but at least it's a job. There is no worker resistance to the introduction of industrial robots as the robots do not threaten one's livelihood. Enough said.

The Japanese model might be subtitled Communalistic: one joins a company as a young person and the company looks after you for the rest of your life. Japanese workers don't get fired for anything other than criminal actions or gross dereliction of duty. Further, there is an added support to the introduction of industrial robots due to their union agreements. Every employee in a Japanese industry has a stake in the profits of the company derived from two annual bonuses. If the company is profitable by the formula worked out by their union negotiators, the

sum total of each bonus can be as high as five months pay. The lowest general bonus is about two months pay. If the company loses money, one receives no bonus. Therefore, every decrease in production costs per unit product, every increase in production output, every instance of gaining a further edge on the market, directly results in an increase in the workers' bi-annual bonus. It is therefore unsurprising that Japanese industrial workers are clamouring for more robots, are frequently the proposers of where in a production process a robot can be used, and have not once complained about them.

A second element in the Japanese model is government policy: it encourages the development of a worker-free manufacturing environment, believing that by taking the workers out of the manufacturing sector they can lead happier and more productive lives doing those things that machines can't do — though specifically what those things are the government doesn't mention, only speaking in generalities such as, "freeing the person to do higher things than repetitive work" (composing Haiku, perhaps?).

The third element in the Japanese model is a derivative of the economic philosophy that you work for a company for life (generally to age 55-60). As such, workers are shifted around from one job to another, trained, re-trained, and re-re-trained over the course of their careers. They tend to be generalists, as are the managers who are frequently shifted to head departments, even to head subsidiary companies, the internal workings of which they may have no prior knowledge. As such, there is an implicit understanding on the part of workers and management that outside specialists will not be hired for specific jobs, but rather that internal workers will be trained for the jobs — such as running the robots.

So far, the system has worked, and worked well — the Japanese being the acknowledged leaders in industrial robots both as to manufacturing them and the absolute numbers employed. However, Japanese economists are already warning that the success of this economic model is dependent on expanding export markets and a permanent shortage of workers — an economic reality which they warn will not exist after 1990 when the manufacturing sector becomes saturated with industrial robots. If,

after the 1990 saturation point is reached Japanese industrialists continue to include more industrial robots on their production lines, then unemployment will of necessity result with catastrophic social consequences.

The model I term The Rest of Us includes North American and European industrial management realities. Workers are not loyal to an individual company, they only work where they can get what they think is the best job, 'best' customarily being defined as the highest paid. They are 'loyal' not to the company but to their trade and their union — an electrician is an electrician first and an employee of the XYZ Company second. (In Japan, a worker might reply that he works for, say, Kowasaki Heavy Industries with eight years seniority currently doing electrical work). They are not tied into the company's profitability — any decrease in cost per unit due to the introduction of robots doesn't increase their take home pay, it only takes away their job.

With the lack of cross fertilization in our industries (e.g. an electrician if he loses his job as an electrician has to go to another company to work as their electrician, rather than losing his job and being re-trained for something else), the potential for resistance to the introduction of industrial robots is very real, though it has not appeared in any widespread way. Primarily the lack of the appearance of Luddite-like violence (when British crofters smashed the cloth looms, c1812, believing them to be a threat to their jobs at home and thereby their way of life) has been due to the introduction of industrial robots to do jobs that nobody wants: spray painting trucks which can affect health and is a bad strain on the back, lifting heavy items into and out of heat treatment furnaces, repetitive spot welding, work in environmentally dangerous areas, etc.


Mork and Mindy Employed

There has been very little unemployment caused by industrial robots, the workers being shifted into vacancies elsewhere in the plants, vacancies created by natural attrition. No unions have as yet propounded policies which deny the introduction of robots, believing them, as yet, not to be a threat to their workers. So much so, that those that have been introduced tend to be treated quite fondly by the workers, being given names such as Laverne and Shirley at GM Oshawa, or Mork and Mindy at the Ford plant in St. Catherines, as well as being treated somewhat as friends. When a University of Florida robot ran amuck, attacked and tore off its own shoulder, it is reported that it received a number of Get Well Quick cards; and when a robot in an electrical company in the States was put out of action due to a passing fork lift truck crashing into it, the workers held a party to 'cheer it up'.

The difficulties that have arisen, and there are many instances, involve lower and middle management personnel feeling threatened by this new technology, believing the industrial robots represent an undermining of their traditional authority and job stature. In fact, a GM study in the States showed that those who truly feared the introduction of industrial robots were not the workers, who believed that if the crunch ever came between robots and human jobs that their union would protect them, nor among upper echelon managers who could take the broad view and can read a ledger sheet, but among lower and lower-middle management personnel. So much so, that there are many instances of quarrels between production engineers attempting to introduce the new technology and production managers fighting a rear guard action to protect the inherent


Continued on page 46

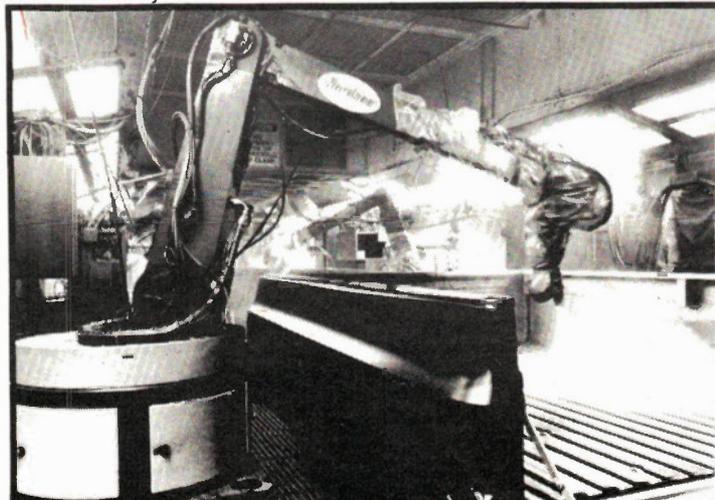Laverne and Shirley GM (Oshawa) robot spray painters.



SABTRONICS

 "making performance affordable"

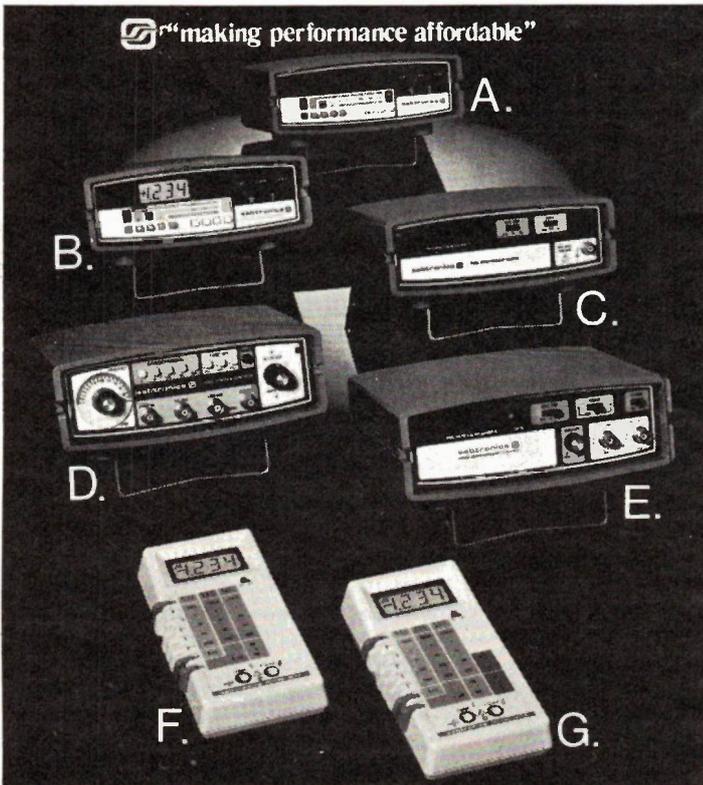

Circle No. 10 on Reader Service Card.

TEST EQUIPMENT

Now available from:

General Electronics 5511 Yonge Street,
Willowdale, Ont., M2N 5S3, (416) 221-6174

Model No.	Description	Kit	Assembled
(A) 2010A	LED Bench DMM	\$166.32	\$216.72
(B) 2015A	LCD Bench DMM	\$199.92	\$250.32
(F) 2035A	LCD Hand Held DMM	\$132.72	\$166.32
(G) 2037A	LCD Hand Held DMM/ Thermometer & Probe	\$167.93	\$199.92
(C) 8110A	100MHz Frequency Counter	\$149.52	\$183.12
(C) 8610A	600MHz 8 Digit Fre- quency Counter	\$199.92	\$250.32
(E) 8610B	600MHz 9 Digit Fre- quency Counter	\$233.52	\$284.43
(E) 8000B	1GHz Frequency Counter	N/A	\$399.95
(D) 5020A	1Hz - 200 KHz Func- tion Generator	N/A	\$216.72
PSC-65	600MHz Prescaler	N/A	\$ 89.95
THP-20	Touch & Hold Probe	N/A	\$ 33.60
HVP-30	High Voltage Probe	N/A	\$ 49.95
AC-110	Battery Eliminator	N/A	\$ 16.95
AC-120	AC Adapter/Charger	N/A	\$ 13.95
NB-120	NiCd Batteries (set of 4)	N/A	\$ 39.95
LFP-10	Audio Frequency Probe	N/A	\$ 33.95
RFA-10	Telescopic RF Pick-up Antenna	N/A	\$ 16.95

Send Certified Cheque or Money Order. Ont. Residents please add 7% to your cost price. 9% Federal Sales Tax is included. All orders will be shipped F.O.B. our warehouse Best Way. Prices subject to change without notice.

Full Factory Service at 5511 Yonge St. Willowdale, Ont.

To see our other products - Send \$1.50 for **GENERAL ELECTRONICS** Full Line Catalogue.


ACTIVE SURPLUS ANNEX
345 QUEEN ST. W.
TORONTO, ONTARIO
M5V 2A4
368-7936

**THE LARGEST VARIETY OF
ELECTRONICS RELATED ITEMS
AT THE LOWEST PRICES IN
TOWN!**

<p>SONY TVS</p> <ul style="list-style-type: none"> - 5" - \$45.00, 7" - \$55.00 - OPERATE ON 12 VOLT dc ONLY - VHF & UHF TUNERS - BLACK AND WHITE PICTURE - MONITOR FOR COMPUTER - TV'S ARE USED AND DO REQUIRE SOME WORK - TEST FACILITIES ARE PROVIDED - SCHEMATICS INCLUDED 	<p>64K RAM BOARD</p> <p>PROVIDES A LOW COST MEANS FOR EXPANDING RAM CAPABILITY FOR COMPUTERS UTILIZING THE S-100 BUS SYSTEM COMPLETE DATA AVAILABLE. CAN BE INTERFACED TO</p> <ul style="list-style-type: none"> - IMSAI - ALTAIR A - ALTAIR B - SOL-8 - CROMEMCO - SBC-100 - Z80 CPU-B <p>AFTER CHRISTMAS SPECIAL</p> <p>\$250.00</p>
<p>• ETI BOARDS • OVER 140 IN STOCK</p>	
<p>12" HITACHI MONITOR REQUIRES COMPOSITE VIDEO 12 MHz BANDWIDTH</p> <p>\$85.00</p> <p>NI-CAD BATTERY PACKS 4 SUB-C BATTERIES 4.8 VOLT 1.2 AL</p> <p>\$5.00</p>	<p>CASSETTE TAPE \$1.00 TANTALUM CAPACITORS 5/\$1.00 IN 4007 DIODES 10¢ each /100/\$6.50 MUFFIN FANS \$6 to \$10.00 ea. ZENER DIODES 20¢ to \$1.75 WE ALSO CARRY A WIDE AND ALWAYS CHANGING SUPPLY OF SEMICONDUCTORS, RESISTORS AND CAPACITORS</p>
<p>FOR MAIL ORDER INFORMATION WRITE P.O. BOX 683, STATION Q, TORONTO, CANADA M4T 2N5</p>	

Circle No. 18 on Reader Service Card.

DIECAST BOXES

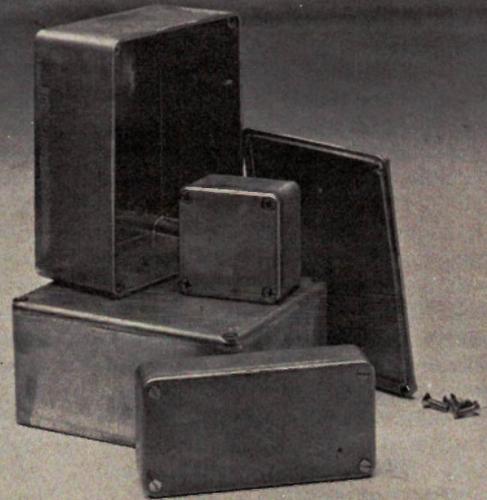

An improved diecast aluminum box with an attractive ground and tumbled surface. Comes drilled and tapped with countersunk interlocking lid and necessary screws. R F shielding properties make the smaller sizes excellent for R F connectors. Seven sizes from 2" x 2" to 7" x 7" approx. Available from authorized distributors coast to coast.

FREE CATALOGUE



**HAMMOND
MANUFACTURING**

Hammond Manufacturing
Co. Ltd.
394 Edinburgh Rd., Guelph,
Ontario N1H 1E5

Ph. (519) 822-2960 or
(416) 456-3770
Tx., 069-56523

Circle No. 9 on Reader Service Card.

INDUSTRIAL ROBOTS


characteristics of their jobs whereby they hold traditional power over their workers. After all, how can one gain the respect of or discipline a robot?

A Booming Market

Fortunately, or unfortunately if you happen to be an industrial robot salesman over the past few years, the number of such devices currently in use in the western world is not very high, though the market is booming with an expected annual increase of 25-30%. Canada has about 150 scattered here and there in ones and twos (the largest group being at a Ford plant in St. Thomas where there are 14 spot welders), and as this writer can report, they're the devil to track down and find. The United States, which was the world leader in industrial robotics (Unimation producing the first one in 1961 on patents granted in 1954), has about 4,500 tops, manufactured by about 25 companies. Japan, which commenced manufacturing industrial robots fully eight years after the Americans now leads the pack with 11,000+ using the RIA Definition or 45,000+ using their own definition, manufactured by some 139 companies. Europe, which commenced producing them two years after the Japanese has about 4,525. Unfortunately, the actual numbers are somewhat inexact, not only due to the inherent difficulties in determining what actually is an industrial robot, but due to the difficulties in gaining production data from source: so much so that the actual numbers tends to depend on who one asks, and is usually out of date by the time the data reaches publication.

However, be that as it may, nothing can excuse such poor reportage as occurred in the feature article on robotics in the prestigious TIME Magazine in Dec/80 which stated that the USSR only had 25 of them, an error analogous to the blunder committed by our own sister publication, ETI International (UK), which not only grossly understated the USSR robot population but reported a decrease in their robot population from a high of 400 in 1975 to a low of 150+ in 1980.

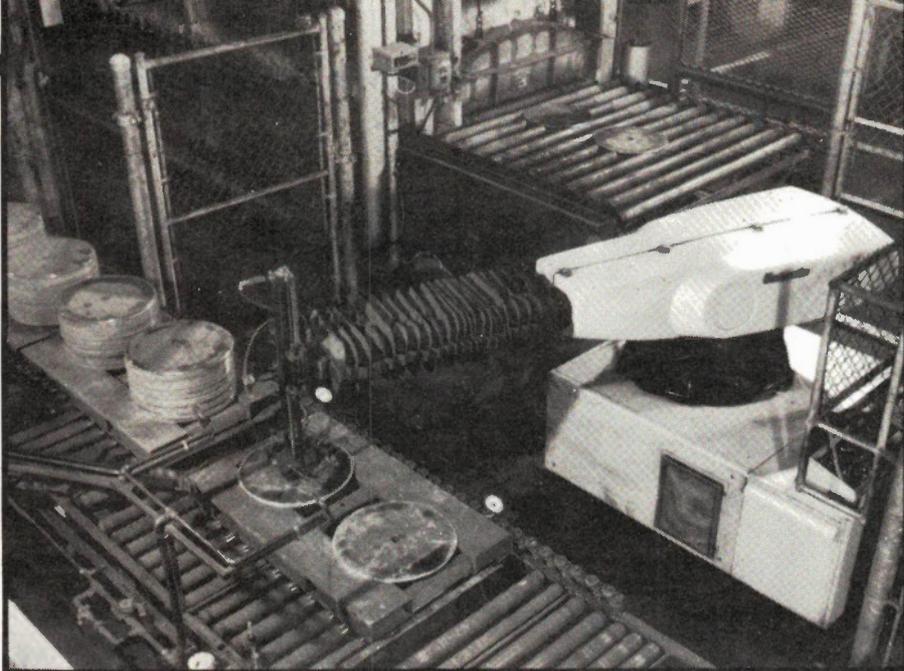In fact, the USSR has developed over 200 prototype industrial robots, of which no less than 72 models are in production. In the Five Year Plan 1976-80 they produced some 3,500 with another 25,000 to be built over the next Five Year Plan. Hence, far from being deficient in robotics, in actual numbers the USSR is only slightly behind the US. The only comforting



An industrial robot at International Harvester's Hamilton Plant.

thought, (western strategic industrial considerations coming to the fore), is that the Soviet industrial robots tend to be less technologically subtle than their Western counterparts, customarily being big solid machines capable of lifting heavy weights, and do not possess the memory elegance found in Western or Asian models. This is primarily due to the USSR's current relative poverty in microprocessing capability on a massed scale, and results in their control systems being less universally applicable and harder to program. Having said that, as an accompanying photograph shows, the Soviet's can turn out small, elegant robots apparently in quantity. But all things considered, the Soviet industrial robots remain relatively primitive by current world wide standards and can only improve dramatically with the passage of time.

It is interesting to note just in passing that the Soviet's expect to displace between 150,000 and 200,000 workers by the introduction of industrial workers over the next five years — mostly in jobs that require heavy lifting, are life threatening or just plain unpleasant. No comparable figures are available for Canadian or American industry — though with only 150 robots in place, the Canadian experience to date would suggest that some 6-800 workers have been shifted to other jobs, jobs customarily higher paying and more personally rewarding. An extrapolation to American industry would suggest that some 20-25,000 American workers have been shifted to date.

All in a Day's Work

So what, in fact, are they used for?

Pretty near anything that a human being can do, at least in theoretical terms involving repetitive actions. Western experience has generally been in jobs that require heavy lifting, such as moving metal parts into and out of heat treatment furnaces, such as at the international Harvester Plant in Hamilton, spray painting of automotive products, repetitive spot welding such as at the Ford plant in St. Thomas, grinding of heavy machine parts such as the wheel grinder at the CN repair shop in Winnipeg, the movement of pallets, and so on.

It is to the Japanese experience that one must look to see the shape of things to come. There, industrial robots not only do the above, but other things ranging from the complicated to the sublime. They are used in the manufacture of pens and pencils, furniture, a window cleaner designed for skyscrapers (with the reported added advantage that it protects the privacy of offices and hotel rooms while doing its job), a dry noodle factory, underwater geological surveying, welding and machining (under 300 meters), underwater bridge building, and are being designed for building construction (especially multi-storied office blocks, which could be useful in the Canadian climate) and road construction. In the service industry, robots are being developed to clean walls and floors, clean boat hulls, clean electrical insulators and in the nuclear industry. In Australia, technicians are testing robots to shear sheep. To date

Continued on page 49

Active Component Sales Corp

NEW 1982 IC MASTER

Two full volumes of product data.

- Deluxe 2-Volume Set (Hard Cover)
- New Section on PROM Programmers
- 62 Manufacturers Data Sheets
- 2400 Data Sheets

REGULAR PRICE \$134.95

Active's Special Introductory Offer \$99.99



FREE ACTIVE'S NEW Comprehensive Catalog
Write for a free copy

Name _____

Address _____

City _____

Prov. _____ Postal Code _____

TTL STANDARD AND LOW POWER SCHOTTKY

7400N	32	74165N	83	74LS125N	57
7401N	33	74166N	88	74LS126N	57
7402N	31	74170N	255	74LS130N	70
7403N	31	74172N	644	74LS133N	218
7404N	34	74173N	103	74LS136N	56
7405N	34	74174N	86	74LS138N	73
7406N	47	74175N	75	74LS139N	73
7407N	47	74176N	100	74LS145N	142
7408N	34	74178N	152	74LS147N	255
7409N	36	74179N	176	74LS148N	186
7410N	33	74180N	98	74LS151N	55
7412N	51	74182N	307	74LS153N	123
7413N	55	74184N	311	74LS155N	123
7414N	55	74185N	307	74LS156N	123
7416N	59	74190N	88	74LS157N	73
7417N	59	74191N	94	74LS158N	73
7420N	38	74192N	88	74LS160N	90
7422N	48	74193N	94	74LS161N	109
7423N	48	74194N	94	74LS162N	143
7425N	42	74195N	72	74LS163N	75
7426N	51	74196N	103	74LS164N	75
7427N	42	74197N	94	74LS165N	116
7428N	52	74198N	195	74LS166N	286
7430N	29	74199N	202	74LS170N	207
7432N	55	74201N	88	74LS173N	77
7433N	55	74246N	187	74LS174N	57
7434N	49	74247N	168	74LS175N	57
7435N	49	74251N	103	74LS181N	258
7437N	43	74252N	311	74LS189N	579
7442N	57	74273N	311	74LS190N	94
7445N	124	74276N	155	74LS191N	94
7446N	124	74278N	155	74LS192N	83
7447N	85	74279N	177	74LS193N	83
7450N	33	74283N	143	74LS194N	83
7451N	38	74284N	116	74LS197N	114
7453N	38	74298N	109	74LS221N	116
7454N	38	74351N	286	74LS240N	95
7472N	47	74372N	309	74LS241N	95
7473N	49	74366N	80	74LS242N	177
7474N	47	74367N	75	74LS243N	177
7475N	55	74370N	116	74LS244N	238
7476N	55	74390N	125	74LS245N	399
7483N	52	74393N	168	74LS247N	109
7484N	177	74394N	168	74LS248N	142
7485N	86	74LS00N	25	74LS249N	142
7486N	51	74LS01N	29	74LS251N	96
7489N	55	74LS02N	29	74LS253N	99
7491N	57	74LS03N	29	74LS254N	116
7492N	49	74LS04N	35	74LS258N	73
7493N	49	74LS05N	29	74LS259N	188
7494N	48	74LS06N	29	74LS260N	188
7495N	40	74LS09N	36	74LS266N	47
7496N	77	74LS10N	29	74LS273N	213
7497N	246	74LS11N	36	74LS279N	82
74100N	203	74LS12N	31	74LS279N	82
74104N	83	74LS13N	38	74LS280N	255
74107N	57	74LS14N	55	74LS283N	155
74109N	57	74LS20N	29	74LS290N	94
74110N	68	74LS21N	36	74LS293N	57
74111N	94	74LS22N	47	74LS296N	114
74116N	179	74LS27N	38	74LS299N	376
74120N	179	74LS30N	23	74LS320N	358
74121N	62	74LS32N	47	74LS321N	128
74122N	70	74LS37N	38	74LS322N	644
74123N	62	74LS38N	38	74LS323N	707
74125N	90	74LS42N	90	74LS324N	423
74126AN	62	74LS47N	88	74LS328N	345
74128N	83	74LS48N	129	74LS352N	289
74133N	58	74LS49N	31	74LS353N	115
74136N	68	74LS54N	47	74LS361N	181
74141N	109	74LS55N	31	74LS366N	68
74142N	425	74LS73N	37	74LS368N	68
74143N	493	74LS74N	47	74LS369N	68
74144N	493	74LS75N	47	74LS368N	68
74145N	87	74LS76N	55	74LS373N	213
74147N	172	74LS78N	42	74LS378N	213
74148N	116	74LS83N	80	74LS379N	83
74150N	187	74LS85N	108	74LS377N	163
74151N	57	74LS89N	62	74LS384N	128
74153N	49	74LS90N	51	74LS390N	142
74154N	187	74LS91N	116	74LS390N	127
74155N	52	74LS92N	62	74LS393N	156
74157N	68	74LS93N	51	74LS396N	155
74159N	136	74LS95N	62	74LS447N	48
74160N	62	74LS96N	75	74LS459N	246
74161AN	83	74LS107N	55	74LS630N	830
74162N	83	74LS109N	47	74LS669N	109
74163AN	83	74LS112N	47	74LS670N	213
74164N	83	74LS122N	62	74LS670N	213
		74LS123N	109		

CMOS

CD4001BE	29	CD4073BE	36
CD4002BE	23	CD4075BE	36
CD4006BE	77	CD4076BE	77
CD4007BE	31	CD4078BE	36
CD4008BE	87	CD4510BE	75
CD4009BE	51	CD4511BE	87
CD4010BE	51	CD4512BE	94
CD4011BE	29	CD4514BE	218
CD4012BE	51	CD4515BE	218
CD4013BE	47	CD4516BE	98
CD4014BE	73	CD4519BE	68
CD4015BE	73	CD4520BE	90
CD4016BE	42	CD4522BE	101
CD4017BE	70	CD4526BE	163
CD4018BE	68	CD4527BE	207
CD4019BE	62	CD4528BE	94
CD4020BE	88	CD4531BE	109
CD4021BE	74	CD4532BE	109
CD4022BE	103	CD4539BE	117
CD4023BE	25	CD4543BE	187
CD4024BE	57	CD4553BE	389
CD4025BE	26	CD4555BE	75
CD4026BE	189	CD4556BE	75
CD4027BE	55	CD4581BE	246
CD4028BE	70	CD4582BE	90
CD4029BE	98	CD4584BE	55
CD4030BE	49	CD4585BE	103
CD4032BE	217	CD4702BE	2113
CD4034BE	317	CD4081BE	33
CD4035BE	98	CD4082BE	33
CD4040BE	83	CD4085BE	61
CD4041BE	116	CD4086BE	77
CD4042BE	70	CD4093BE	73
CD4043BE	77	CD4099BE	228
CD4044BE	68	CD4104BE	307
CD4046BE	103	40097PC	108
CD4047BE	94	40096PC	126
CD4049BE	60	74C00N	53
CD4050BE	42	74C14N	95
CD4051BE	72	74C20N	36
CD4052BE	111	74C75N	53
CD4053BE	103	74C83N	163
CD4060BE	116	74C107N	46
CD4066BE	70	74C181N	181
CD4068BE	31	74C163N	181
CD4069BE	64	74C173N	99
CD4070BE	38	74C175N	135
CD4071BE	38	74C192N	182
CD4072BE	25	74C193N	172

★★★ MEMORY SPECIALS ★★★

ONE TIME PRICES ONLY — Any order over \$50 receive free — MOS Memory Data Book

STATIC RAM'S

2101-35	(350NS) (256 x 4) 1K	3.84
2102-25	(250NS) (1K x 1) 1K	1.63
P2111-45	(450NS) (256 x 4) 1K	3.45
P2112-35	(350NS) (256 x 4) 1K	2.93
2114L-30	(300NS) (1024 x 4) 4K	2.25
2147	(55NS) (4K x 1) 4K	11.25
2147	(70NS) (4K x 1) 4K	9.69
P2016-15	(150NS) (2K x 8) 16K	25.94
P2016-20	(200NS) (2K x 8) 16K	19.34

DYNAMIC RAM'S

P4060-30	4K (4K x 1) 300NS 22 PIN	3.45
P4116-20	16K (16K x 1) 200NS 16 PIN	3.12
C4164-15	64K (64K x 1) 150NS 16 PIN	31.20
C4164-20	64K (64K x 1) 200NS 16 PIN	28.60

PROM'S

74S188N	32 x 8	16 PIN	2.28
74S288N	32 x 8	16 PIN	2.28
93417/82S126	256 x 4	16 PIN	3.19
93427/82S129	256 x 4	16 PIN	3.19
93446/7621	512 x 4	16 PIN	5.98
93448/7641	512 x 8	24 PIN	9.69
93453/7643	1024 x 4	18 PIN	8.71
93451/82S181	1024 x 8	24 PIN	9.69
82S185/7128	2048 x 4	18 PIN	23.34
82S191/7138	2048 x 8	24 PIN	88.40

SHIFT REGISTERS

1404A	TO-5 Single 1024 bit	3.87
3341APC	FIFO 1MHz	5.79
3342PC	64 bit	5.14
3347PC	80 bit	5.14

AP PRODUCTS TERMINAL AND DISTRIBUTION STRIPS

923285	12 Four Tie Point Terminals	3.12
	Distribution Strip 3.5" x .35"	.35
923281	18 Four Tie Point Terminals	3.64
	Distribution Strip 4.9" x .35"	.35
923277	24 Four Tie Point Terminals	4.55
	Distribution Strip 6.5" x .35"	.35
923293	36 Four Tie Point Terminals	5.14
	Distribution Strip 6.5" x .43"	.43
923273	34 Five Tie Point Terminals	6.96
	Terminal Strip 1.8" x 1.36"	.36
923291	54 Five Tie Point Terminals	8.78
	Terminal Strip 6.5" x .63"	.63
923269	68 Five Tie Point Terminals	12.42
	Terminal Strip 3.5" x 1.36"	.36
923265	86 Five Tie Point Terminals	14.56
	Terminal Strip 4.9" x 1.36"	.36
923261	128 Five Tie Point Terminals	18.20
	Terminal Strip 1.8" x 1.36"	.36

1 AMP VOLTAGE REGULATORS

78XXUC	Positive TO-220 Pkg.	.99
	Voltages 5, 6, 8, 12, 15, 18, 24.	
78XXKC	Positive TO-3 Pkg.	2.20
	Voltages 5, 8, 12, 15, 18, 24.	
79XXUC	Negative TO-220 Pkg.	1.16
	Voltages 5, 6, 8, 12, 15, 18, 24.	
79XXKC	Negative TO-3 Pkg.	2.20
	Voltages 5, 8, 12, 15, 18, 24.	
LINEAR INTERFACE CIRCUITS		
SN75107AN	1.63 SN75365N	1.81
SN75110AN	1.63 SN75452BP	4.99
SN75150P	1.92 SN75491N	1.56
SN75154N	1.92 SN75492N	1.56

Microprocessor Chip Sets

6800 FAMILY		6500 FAMILY		8080 FAMILY	
6800 CPU	7.35	6502 CPU	9.04	8035 CPU	9.43 8224
6802 CPU	11.25	6504 CPU	9.69	8039 CPU	10.34 8226
6808 CPU	10.99	6505 CPU	9.69	8080A CPU	6.44 8228
6809 CPU	25.94			8085 CPU	10.34 8251
6810	3.45	6520	7.09	8155	11.70 8253
6821	3.45	6522	10.21	8748	46.80 8255
6845	35.69	6532	14.11	8755	41.60 8257
6850	3.84	6551	15.15	8212	2.93 8259
6852	7.48			8214	5.53 8279
				8216	2.57

SCR'S and TRIAC'S

TIC106D	SCR 5 amp	400V TO-202	.51
TIC47	SCR 0.6 amp	200V TO-92	.77
TIC116B	SCR 8 amp	200V TO-220	1.38
TIC1160	SCR 8 amp	400V TO-220	1.55
TIC126B	SCR 12 amp	200V TO-220	1.53
TIC126D	SCR 12 amp	400V TO-220	1.92
TIC216B	Triac 6 amp	200V TO-220	1.46
TIC216D	Triac 6 amp	400V TO-220	1.22
TIC226D	Triac 8 amp	400V TO-220	1.43
TIC236D	Triac 12 amp	400V TO-220	1.69
TIC246D	Triac 16 amp	400V TO-220	2.08
2N1595	SCR 1 amp	50V TO-220	.85
2N6401	SCR 16 amp	100V TO-220	1.46

PLASTIC POWER TRANSISTORS


TIP298	.60	TIP41C	1.01	TIP125	.95
TIP29C	.65	TIP42B	1.00	TIP126	1.21
TIP30B</					

CANADIAN PROJECTS BOOK NO. 1

Canadian Projects Book No. 1
100 pages

\$3.00

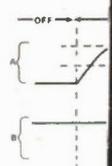25 of our most popular projects from our earlier issues including: Audio Limiter, 5W Stereo, Bass Enhancer, Modular Disco, 50W/100W Amp Modules, IB Metal Locator, Touch Organ, Electronic Mastermind, Double Dice, Reaction Tester, Sound Operated Flash, Burglar Alarm, Injector-Tracer, Digital Voltmeter.



Electronics Today
INTERNATIONAL

JANUARY 1981

PROJECTS BOOK No. 2

\$3.95

Projects Book No. 2
100 pages

\$3.95

Contains 25 of the best projects from recent issues including the High Performance Series 4000 Amplifier (including Preamps and Power Supply), Rumble Filter, Dynamic Noise Filter, Logic Probe, Cable Tester, Function Generator, Rain Alarm, Digital Tacho, Two Octave Organ, Light Chaser, Shutter Speed Timer, Ni-Cad Charger and more. First published January 1981.

Electronics Today
INTERNATIONAL



SUMMER 1980

ELECTRONIC CIRCUIT DESIGN

Electronic Circuit Design
92 pages

\$3.95

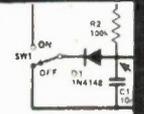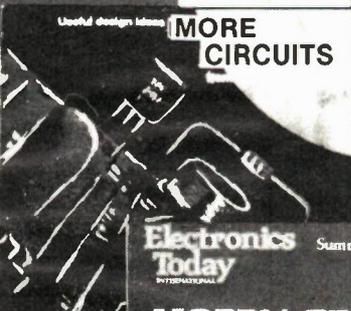A collection of major articles on various aspects of circuit design including CMOS, Audio Amplifiers, Power Supplies, SCR's, Op-Amps, Using the 3080 and Temperature Control. A large number of useful circuits are given but the emphasis is on guidance and how to tackle the design for yourself.



More Circuits
108 pages

\$4.50

Over 150 circuits plus articles on Circuit Construction, Test Gear, a project on a Digital Panel Meter, Design notes on Speaker Crossovers, TTL pin-outs, Design notes on Crystal Oscillators.

Hobby Projects
100 pages

\$3.95

First published Summer 1980. Contains 25 straight-forward projects most of which have never appeared in the magazine including: Stereo Amp, Audio Mixer, Scratch and Rumble Filter, Constant Volume Amp, Graphic Equaliser, Envelope Generator, White Noise Effects Unit, Linear Scale Ohmmeter, Intercom, Drill Speed Controller, LED Tacho, Parking Meter Timer, Electronic Organ, Touch Switch, Electronic Dice, Siren, Simple Receivers.

Electronics Today
INTERNATIONAL

SUMMER 1980

HOBBY PROJECTS



25 Electronic Projects

NEED MORE INFORMATION?

If you would like more information on the products or services mentioned in the advertisements:

1. Fill in the attached card with your name, address, etc.
2. Circle the appropriate Reader Service number for further information about advertised products.
3. Mail the card and the advertiser will send you literature free of charge. If the card has been removed, or if you want the information in a hurry, phone or write direct to the advertiser and refer to the ETI issue and page number.

Your Company Classification (if applicable):

- A. Manufacturer
- B. Retailer
- C. Government
- D. R&D
- E. Servicer/Installer
- F. Distributor/Representative
- G. Educational Institution

In the field of:

1. Computer and Related Equipment
2. Communications Equipment & Systems
3. Navigation, guidance or Control Systems
4. Test & Measurement Equipment
5. Consumer Products
6. Industrial Controls & Equipment
7. Components & Subassemblies
8. Other (Please specify on the card)

Your major job function (if applicable):

- A. Buying
- B. Technologist
- C. Educator
- D. Not employed in an electronics-related field
- E. Engineering
- F. Technician
- G. Management
- H. Sales
- I. Other (Please specify on the card)

What interests you most about ETI? (your favourite five or less):



- A. Audio
- B. Video
- C. Ham Radio
- D. Shortwave Listening
- E. Servicing
- F. Components & Technology
- G. Reports on the Electronic Industry
- H. Microcomputers
- J. Projects
- K. News Digest
- L. Other (Please specify on the card)
- M. Tech Tips

ETI SPECIALS

Available from your local electronic parts store or direct from ETI (please add 45c each to cover postage).



Send money to:

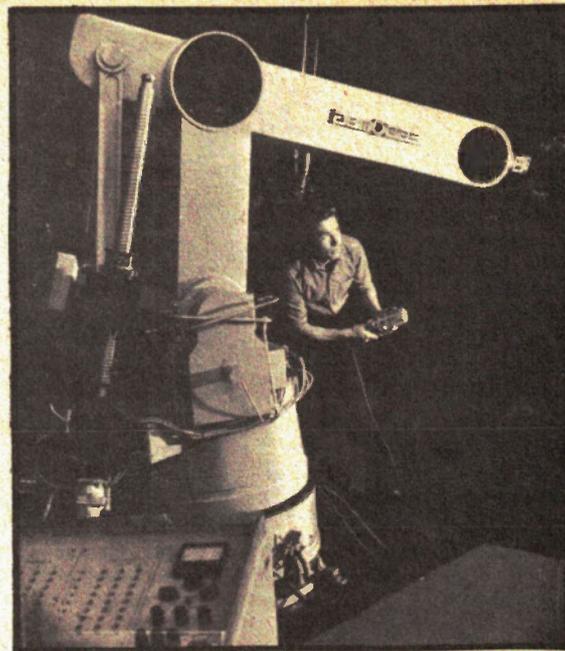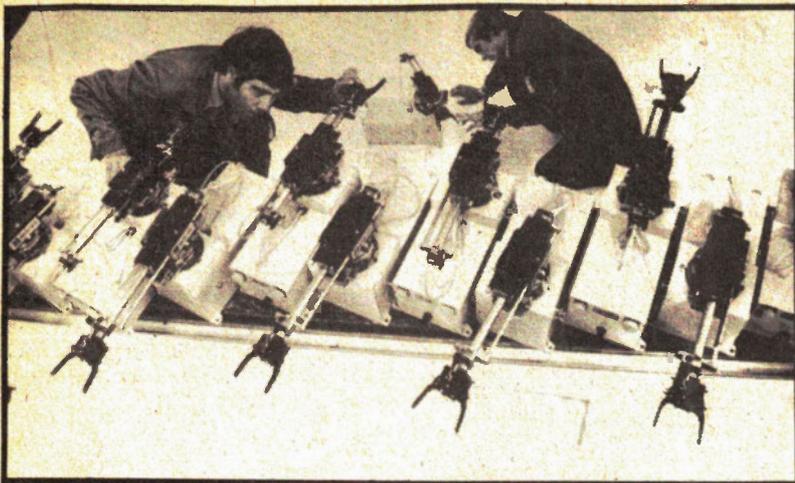Electronics Today Magazine,
Unit 6, 25 Overlea Blvd.,
Toronto, Ont.,
M4H 1B1



Russian

Robotics

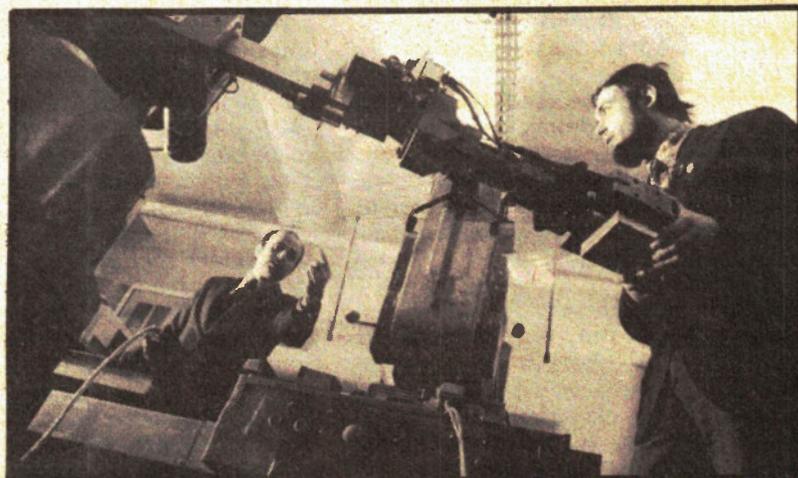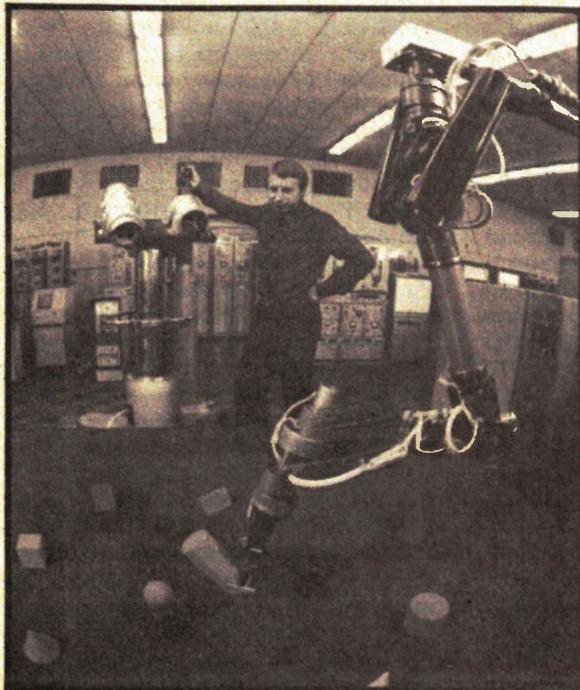

**SEEN HERE FOR THE FIRST TIME
 IN NORTH AMERICA AN ETI
 CANADA EXCLUSIVE!**

Upper left: Foreman Alexei Gaiton and inspector Alexei Ovchinnikov checking robots produced at the LADA auto production association. The use of such robots at Leningrad's enterprises has released some 500 skilled workers. Photo by Yu. Belozerov (TASS)

Upper right: Viktor Borisov, head of the adjustments section, checks the operation of the experimental robot intended to lift and move loads of up to 30 kg. Photo by Yu. Belozerov (TASS)

Lower left: Institute of Cybernetics under the UkrSSR Academy of Sciences at the laboratory of the "arm — eye" type robots.

Lower right: Designers Yevgeny Vronsky III and Sergei Lukashevich adjust the ITEKAR automated control unit operating drilling and milling machines. Photo by Arkady Nikolayev (TASS)

**ROBOT POPULATION BY COUNTRY
 BEST AVAILABLE FIGURES TO END
 OF 1981.**

JAPAN	11,000
USA	4,500
USSR	3,500
SWEDEN	1,500
W. GERMANY	1,350
ITALY	500
FRANCE	375
POLAND	350
UK	300
FINLAND	150
CANADA	150



Fujitsu Fanuc's state of the art robot assembly plant that utilizes industrial robots to build other industrial robots. Completed assemblies are to the left of the picture.

they report that they have no difficulty in clipping the back and sides but the neck and head sequences currently elude them — so much so that there are unconfirmed reports of malfunctions resulting in a flock of earless sheep. Right the way across to what this writer considers to be the current intellectual ultimate: the Fujitsu Fanuc's factory that uses industrial robots to assemble other industrial robots.

Robots can be used for anything that is repetitive, from putting bottles into cartons, to drilling holes and tightening bolts, with increased accuracy and a decrease in the rejection rate and a marked decrease in the scrap produced.

But Can They Think?

Yet despite the ever increasing utilization of robots in all sorts of jobs, there remains a big stumbling block, the overcoming of which represents the major thrust in industrial robots R and D — the robots' lack of intelligence.

Current robots are just plain dumb and are totally dependent on the input from the programmers. The major stumbling block is the lack of vision which currently appears to be stuck at the two dimensional level. But advances are being made.

General Motors has developed a system it calls Consight which consists of a robot equipped with an electronic camera. The camera surveys parts on a conveyor belt, identifies them, and transfers them in the proper sequence to another conveyor belt. As yet it is still too slow to work on an assembly line. The Machine Intelligence Corp. has developed a

system which scans objects against a brightly lit background, transmits the hundreds of pixels (the dots that make up a television image) to a computer. The computer translates the pixels into binary code and compares the data with recorded descriptions of various objects. As yet it is only capable of differentiating between nine different objects. The Lockheed Missile and Space Co. are testing a technique called 'gray imaging' which uses 100,000 different pixels each graded from 0 (pure white) to 255 (pure black). This enables the robot to have a much better three dimensional image of objects.

In the realm of touch, robots as yet remain very insensitive. They will grasp with a pre-determined pressure, but as yet the technology to grasp an item and identify it by touch eludes researchers. But to that end, the Lord Corp. hopes to market (withing 5 years) a hand made out of a spongy material with a grid of many sensitive wires embedded in it. It is hoped that these sensitive wires will permit a reasonable facsimile of touch to be achieved.

Yet despite the advances in computers and television cameras the interface between the two still remains the major stumbling block, for while computers can compute mathematical formulas the state of the art remains plateaued at the level of a robot which will waste enormous amounts of time inspecting cubes and cylinders when instructed to find a triangle, for instance.

In broad based industrial applications, the shape of things to come is the fully automated factory which can manufacture large

numbers of different items in small batch quantities of each — just by changing the programming in the robot's memory. To date, the most definitive example is the Japanese completely unmanned computer-run dry noodle factory — which includes an automatic warehouse, battery operated cars, loading and unloading robots, automatic manufacturing and inspection, and packing. A close second is Fujitsu Fanuc's robot factory. Nothing like them exists in the western world.

Threat to Mankind?

It is in the fully automated factories that industrial robots perhaps present their greatest threat to mankind in general. For no matter how successful our diplomats may be in achieving SALT agreements, even with fully acceptable international inspection processes, with factories capable of being switched over from manufacturing one item to another merely by a quick re-programming, the spectre arises of the XYZ Hula Hoop Company being transformed, almost immediately into an armaments factory capable of producing weapons three shifts a day, seven days a week with superior accuracy and reliability. A further element in this spectre is that in the event of a national military emergency those robot utilizing factories producing non-strategic items can be almost immediately switched over to the manufacture and assembly of other industrial robots which in turn can be used either to manufacture still more industrial robots which in turn can be switched directly to the manufacture of arms. Hence, a weak, non-threatening nation possessing a high degree of industrial robot capabilities, and the necessary blueprints for strategic arms, could transform itself into a major world power literally in a matter of months, or possibly even weeks. Verily, a pussycat today, a Hitler tomorrow.

Hopefully not, but then industrial robots are already being used in the manufacture of tanks, warplanes and gun pieces. And much of the R and D money originates in military budgets.

After all, the initial rationale for the Lockheed 'gray imaging' process, which if successful will be very useful in commercial applications, was to check for defective artillery shells.

February 1977

Features: CN Tower, Biorythm Calculator, VCT, 555 Timer Applications, Yamaha B1 Review, Scope Test Your Car.
Projects: 5W Stereo Amp, Philips Speaker System, Reaction Tester, Patch Detector, Heads or Tail, SCR Tester.

August 1978

Features: Getting into Shortwave, Using a 'Scope, Semiconductor Guide, Intro to Amateur Radio 2.
Projects: Sound Level Meter, 2 Chip Siren, Induction Balance Metal Locator, Porch Light.

November 1978

Features: Bally Arcade, PCM Explained, Danger of Lightning, Easy PCB Making.
Projects: Hi-Fi Amp with CMOS Switching, Capacitance Meter, Stars-n-Dots Game.

January 1979

Features: Robots: some Facts, Robots: Brain Power, Robots: Building Guide, VCT, Getting into Video.
Projects: Digital Tacho, Log-Exponential Converter, FM Broadcaster.

February 1979

Features: Quarks, Op-Amps, Binary to Decimal and Back.
Projects: SW Radio, Phasemeter, Light Chaser.

August 1979

Features: Casing Survey, Smoke Detectors, TV Antennas, Reed Switches, Magnetic Field Audio Amp, Industrial Electronics.
Projects: Audio Power Meter, Shoot-out, ETI-Wet Plant Waterer.

September 1979

Features: OSI Superboard Review, Solar Power from Satellites, Reed Switches.
Projects: Field Strength Meter, Digital Wind Meter, Up/Down Counter.

October 1979

Features: SW Receiver Survey, Ultra Fidelity, Computer Speech.
Projects: Simple Graphic Equaliser, Digital Dial, Variable Windscreen Wiper, Cable Tester.

January 1980

Features: LM10 Applications, Guide to Triac's, History of Car Ignition.
Projects: Guitar Effects Unit, Series 4000 Stereo Amplifier, Logic Probe.

February 1980

Features: Simple Radio Control, Gain Control, Guide to Triac's.
Projects: Series 4000 Moving Coil Preamp, Egg Timer, Power Supply.



March 1980

Features: Biofeedback, Gain Control, Power Supplies, Self Resonant Capacitors.
Projects: Electromyogram (pr.1), Battery Condition Indicator, Wire Tracer.

May 1980

Features: Delay Lines, Standing Waves, Microwave Cooking, Artificial Intelligence.
Projects: Click Eliminator, Soil Moisture Indicator, Fuel Level Monitor, 16k RAM Card.

June 1980

Features: Electronic Warfare, PLL Synthesis, CA3130 Circuits, Canadian Sound Archives, Magnetic Power Control, CLIP.
Projects: Function Generator, Dynamic Noise Filter, Overspeed Alarm.

July 1980

Features: CMOS 555 Circuits, Capacitors, Electronics in the Studio, Tesla Controversy.
Projects: Hebot Robot (pt.1), Photographic Timer, Analogue Frequency Meter, Accentuated Beat Metronome.

ETI

BACK ISSUES

August 1980

Features: \$100 Bus System, Introduction to Test Gear, Designer Circuits, FET Special, Life Out There?
Projects: 300W Amp, Hebot (pt.2), Transistor Tester, Passionmeter.

November 1980

Features: Designer Circuits Special, Cassette Decks and Tapes, Attenuators, Project Daedalus, Thermistors.
Projects: Guitar Practice Amplifier, 6W Siren, Infra-Red Remote Control.

March 1981

Features: The Ubiquitous Oscilloscope, VFET Applications, Photocells, Test Gear.
Projects: Hum Filter, Drum Synthesiser, Shark Game.

April 1981

Features: Introduction to Lasers, Test Meter Circuits, Eddy Currents, Modern Turntable Technology, Honeycomb Speakers.
Projects: Stereo Image Coordinator, Ultrasonic Switch, Autoprobe.

June 1981

Features: Project Galileo, Story Behind Stereo, Solder, Computerese.
Projects: 1573A VCA, High Speed Cassette Interface, Double Dice, Bicycle Speedometer.

The Back Issues shown here are available from ETI. Back issues are not just unsold issues; each month about 500 copies are held in reserve for later interest. The order form in this issue gives a complete list of issues still available.

Price is \$3.00 each, any five for \$10

ETI Back Issues,
Unit 6
25 Overlea Blvd,
Toronto, Ontario,
M4J 1B1

EMM BOOKS

COMPUTERS

(HARDWARE)

A BEGINNER'S GUIDE TO COMPUTERS AND MICROPROCESSORS — WITH PROJECTS

TAB No.1015 \$13.45
Here's a plain English introduction to the world of microcomputers — its capabilities, parts and functions... and how you can use one. Numerous projects demonstrate operating principles and lead to the construction of an actual working computer capable of performing many useful functions.

BP66: BEGINNERS GUIDE TO MICROPROCESSORS AND COMPUTING

E.F. SCOTT, M.Sc., C.Eng. \$7.55
As indicated by the title, this book is intended as an introduction to the basic theory and concepts of binary arithmetic, microprocessor operation and machine language programming.

There are occasions in the text where some background information might be helpful and a Glossary is included at the end of the book.

BP72: A MICROPROCESSOR PRIMER

E.A. PARR, B.Sc., C.Eng., M.I.E.E. \$7.70
A newcomer to electronics tends to be overwhelmed when first confronted with articles or books on microprocessors. In an attempt to give a painless approach to computing, this small book will start by designing a simple computer and because of its simplicity and logical structure, the language is hopefully easy to learn and understand. In this way, such ideas as Relative Addressing, Index Registers etc. will be developed and it is hoped that these will be seen as logical progressions rather than arbitrary things to be accepted but not understood.

BEGINNERS GUIDE TO MICROPROCESSORS

TAB No.995 \$10.45
If you aren't sure exactly what a microprocessor is, then this is the book for you. The book takes the beginner from the basic theories and history of these essential devices, right up to some real world hardware applications.

HOW TO BUILD YOUR OWN WORKING MICROCOMPUTER

TAB No.1200 \$16.45
An excellent reference or how-to manual on building your own microcomputer. All aspects of hardware and software are developed as well as many practical circuits.

BP78: PRACTICAL COMPUTER EXPERIMENTS

E.A. PARR, B.Sc., C.Eng., M.I.E.E. \$7.30
Curiously most published material on the microprocessor tends to be of two sorts, the first treats the microprocessor as a black box and deals at length with programming and using the "beast". The second type of book deals with the social impact. None of these books deal with the background to the chip, and this is a shame as the basic ideas are both interesting and simple.

This book aims to fill in the background to the microprocessor by constructing typical computer circuits in discrete logic and it is hoped that this will form a useful introduction to devices such as adders, memories, etc. as well as a general source book of logic circuits.

HANDBOOK OF MICROPROCESSOR APPLICATIONS

TAB No.1203 \$14.45
Highly recommended reading for those who are interested in microprocessors as a means of accomplishing a specific task. The author discusses two individual microprocessors, the 1802 and the 6800, and how they can be put to use in real world applications.

MICROPROCESSOR/MICROPROGRAMMING HANDBOOK

TAB No.785 \$14.45
A comprehensive guide to microprocessor hardware and programming. Techniques discussed include subroutines, handling interrupts and program loops.

DIGITAL INTERFACING WITH AN ANALOG WORLD

TAB No.1070 \$14.45
You've bought a computer, but now you can't make it do anything useful. This book will tell you how to convert real world quantities such as temperature, pressure, force and so on into binary representation.

MICROPROCESSOR INTERFACING HANDBOOK: A/D & D/A

TAB No.1271 \$14.45
A useful handbook for computerists interested in using their machines in linear applications. Topics discussed include voltage references, op-amps for data conversion, analogue switching and multiplexing and more.

COMPUTER TECHNICIAN'S HANDBOOK

TAB No.554 \$17.45
Whether you're looking for a career, or you are a service technician, computer repair is an opportunity you should be looking at. The author covers all aspects of digital and computer electronics as well as the mathematical and logical concepts involved.

THE ESSENTIAL COMPUTER DICTIONARY AND SPELLER

AB011 \$9.45
A must for anyone just starting out in the field of computing, be they a businessman, hobbyist or budding computerist. The book presents and defines over 15,000 computer terms and acronyms and makes for great browsing.

HOW TO TROUBLESHOOT AND REPAIR MICROCOMPUTERS

AB013 \$10.45
Learn how to find the cause of a problem or malfunction in the central or peripheral unit of any microcomputer and then repair it. The tips and techniques in this guide can be applied to any equipment that uses the microprocessor as the primary control element.

TROUBLESHOOTING MICROPROCESSORS AND DIGITAL LOGIC

TAB No.1183 \$13.45
The influence of digital techniques on commercial and home equipment is enormous and increasing yearly. This book discusses digital theory and looks at how to service Video Cassette Recorders, microprocessors and more.

HOW TO DEBUG YOUR PERSONAL COMPUTER

AB012 \$10.45
When you feel like reaching for a sledge hammer to reduce your computer to fiberglass and epoxy dust, don't. Reach for this book instead and learn all about program bug tracking, recognition and elimination techniques.

THE COMPLETE HANDBOOK OF ROBOTICS

TAB No.1071 \$13.45
All the information you need to build a walking, talking mechanical friend appears in this book. Your robot can take many forms and various options — light, sound, and proximity sensors — are covered in depth.

HOW TO BUILD YOUR OWN SELF PROGRAMMING ROBOT

TAB No.1241 \$13.45
A practical guide on how to build a robot capable of learning how to adapt to a changing environment. The creature developed in the book, Rodney, is fully self programming, can develop theories to deal with situations and apply those theories in future circumstances.

BUILD YOUR OWN WORKING ROBOT

TAB No.841 \$11.45
Contains complete plans — mechanical, schematics, logic diagrams and wiring diagrams — for building Buster. There are two phases involved: first Buster is leashed led, dependent on his creator for guidance; the second phase makes Buster more independent and able to get out of tough situations.

COMPUTERS

(SOFTWARE)

BEGINNER'S GUIDE TO COMPUTER PROGRAMMING

TAB No.574 \$16.45
Computer programming is an increasingly attractive field to the individual, however many people still overlook it as a career. The material in this book has been developed in a logical sequence, from the basic steps to machine language.

BP86: AN INTRODUCTION TO BASIC PROGRAMMING TECHNIQUES

S. DALY \$8.25
This book is based on the author's own experience in learning BASIC and in helping others, mostly beginners, to program and understand the language. Also included are a program library containing various programs, that the author has actually written and run. These are for biorhythms, plotting a graph of Y against X, standard deviation, regression, generating a musical note sequence and a card game. The book is complemented by a number of appendices which include test questions and answers on each chapter and a glossary.

THE BASIC COOKBOOK

TAB No.1055 \$9.45
BASIC is a surprisingly powerful language... if you understand it completely. This book picks up where most manufacturers' documentation gives up. With it, any computer owner can develop programs to make the most out of his or her machine.

PET BASIC — TRAINING YOUR PET COMPUTER

AB014 \$16.45
Officially approved by Commodore, this is the ideal reference book for long time PET owners or novices. In an easy to read and humorous style, this book describes techniques and experiments, all designed to provide a strong understanding of this versatile machine.

PROGRAMMING IN BASIC FOR PERSONAL COMPUTERS

AB015 \$10.45
This book emphasizes the sort of analytical thinking that lets you use a specific tool — the BASIC language — to transform your own ideas into workable programs. The text is designed to help you to intelligently analyse and design a wide diversity of useful and interesting programs.

COMPUTER PROGRAMS IN BASIC

AB001 \$14.45
A catalogue of over 1,600 fully indexed BASIC computer programs with applications in Business, Math, Games and more. This book lists available software, what it does, where to get it, and how to adapt it to your machine.

PET GAMES AND RECREATION

AB002 \$12.45
A variety of interesting games designed to amuse and educate. Games include such names as Capture, Tic Tac Toe, Watchperson, Motie, Sinners, Martian Hunt and more.

BRAIN TICKLERS

AB005 \$8.00
If the usual games such as Bug Stomp and Invaders from the Time Warp are starting to pale, then this is the book for you. The authors have put together dozens of stimulating puzzles to show you just how challenging computing can be.

PASCAL

TAB No.1205 \$16.45
Aimed specifically at TRS-80 users, this book discusses how to load, use and write PASCAL programs. Graphic techniques are discussed and numerous programs are presented.

PASCAL PROGRAMMING FOR THE APPLE

AB008 \$16.45
A great book to upgrade your programming skills to the UCSD Pascal as implemented on the Apple II. Statements and techniques are discussed and there are many practical and ready to run programs.

APPLE MACHINE LANGUAGE PROGRAMMING

AB009 \$16.45
The best way to learn machine language programming the Apple II in no time at all. The book combines colour, graphics, and sound generation together with clear cut demonstrations to help the user learn quickly and effectively.

Z80 USERS MANUAL

AB010 \$14.45
The Z80 MPU can be found in many machines and is generally acknowledged to be one of the most powerful 8 bit chips around. This book provides an excellent "right hand" for anyone involved in the application of this popular processor.

HOW TO PROGRAM YOUR PROGRAMMABLE CALCULATOR

AB006 \$10.45
Calculator programming, by its very nature, often is an obstacle to effective use. This book endeavours to show how to use a programmable calculator to its full capabilities. The TI 57 and the HP 33E calculators are discussed although the principles extend to similar models.

BP33: ELECTRONIC CALCULATOR USERS' HANDBOOK

M.H. BABANI, B.Sc.(Eng.) \$4.25
An invaluable book for all calculator users whatever their age or occupation, or whether they have the simplest or most sophisticated of calculators. Presents formulae, data, methods of calculation, conversion factors, etc. with the calculator user especially in mind, often illustrated with simple examples. Includes the way to calculate using only a simple four function calculator: Trigonometric Functions (Sin, Cos, Tan), Hyperbolic Functions (Sinh, Cosh, Tanh) Logarithms, Square Roots and Powers.

PROJECTS

BP48: ELECTRONIC PROJECTS FOR BEGINNERS

F.G. RAYER, T.Eng.(CEI), Assoc.IERE \$5.90
Another book written by the very experienced author — Mr. F.G. Rayer — and in it the newcomer to electronics, will find a wide range of easily made projects. Also, there are a considerable number of actual component and wiring layouts, to aid the beginner.

Furthermore, a number of projects have been arranged so that they can be constructed without any need for soldering and, thus, avoid the need for a soldering iron.

Also, many of the later projects can be built along the lines as those in the 'No Soldering' section so this may considerably increase the scope of projects which the newcomer can build and use.

221: 28 TESTED TRANSISTOR PROJECTS

R.TORRENES \$5.50
Mr. Richard Torrenes is a well experienced electronics development engineer and has designed, developed, built and tested the many useful and interesting circuits included in this book. The projects themselves can be split down into simpler building blocks, which are shown separated by boxes in the circuits for ease of description, and also to enable any reader who wishes to combine boxes from different projects to realise ideas of his own.

BP49: POPULAR ELECTRONIC PROJECTS

R.A. PENFOLD \$6.25
Includes a collection of the most popular types of circuits and projects which, we feel sure, will provide a number of designs to interest most electronics constructors. The projects selected cover a very wide range and are divided into four basic types: Radio Projects, Audio Projects, Household Projects and Test Equipment.

EXPERIMENTER'S GUIDE TO SOLID STATE ELECTRONIC PROJECTS

AB007 \$9.45
An ideal sourcebook of Solids State circuits and techniques with many practical circuits. Also included are many useful types of experimenter gear.

BP71: ELECTRONIC HOUSEHOLD PROJECTS

R. A. PENFOLD \$7.70
Some of the most useful and popular electronic construction projects are those that can be used in or around the home. The circuits range from such things as '2 Tone Door Buzzer', Intercom, through Smoke or Gas Detectors to Baby and Freezer Alarms.

BP94: ELECTRONIC PROJECTS FOR CARS AND BOATS

R.A. PENFOLD \$8.10
Projects, fifteen in all, which use a 12V supply are the basis of this book. Included are projects on Windscreen Wiper Control, Courtesy Light Delay, Battery Monitor, Cassette Power Supply, Lights Timer, Vehicle Immobiliser, Gas and Smoke Alarm, Depth Warning and Shaver Interfer.

BP69: ELECTRONIC GAMES

R.A. PENFOLD \$7.55
In this book Mr. R. A. Penfold has designed and developed a number of interesting electronic game projects using modern integrated circuits. The text is divided into two sections, the first dealing with simple games and the latter dealing with more complex circuits.

BP95: MODEL RAILWAY PROJECTS

\$8.10
Electronic projects for model railways are fairly recent and have made possible an amazing degree of realism. The projects covered include controllers, signals and sound effects: strobboard layouts are provided for each project.

PROJECTS (CONTINUED)

BP76: POWER SUPPLY PROJECTS \$7.30 R.A. PENFOLD

Line power supplies are an essential part of many electronics projects. The purpose of this book is to give a number of power supply designs, including simple unregulated types, fixed voltage regulated types, and variable voltage stabilised designs, the latter being primarily intended for use as bench supplies for the electronics workshop. The designs provided are all low voltage types for semiconductor circuits.

There are other types of power supply and a number of these are dealt with in the final chapter, including a cassette power supply, Ni-Cad battery charger, voltage step up circuit and a simple inverter.

BP84: DIGITAL IC PROJECTS \$8.10 F.G. RAYER, T.Eng.(CEI), Assoc.IERE

This book contains both simple and more advanced projects and it is hoped that these will be found of help to the reader developing a knowledge of the workings of digital circuits. To help the newcomer to the hobby the author has included a number of board layouts and wiring diagrams. Also the more ambitious projects can be built and tested section by section and this should help avoid or correct faults that could otherwise be troublesome. An ideal book for both beginner and more advanced enthusiast alike.

BP67: COUNTER DRIVER AND NUMERICAL DISPLAY PROJECTS \$7.55 F.G. RAYER, T.Eng.(CEI), Assoc. IERE

Numerical indicating devices have come very much to the forefront in recent years and will, undoubtedly, find increasing applications in all sorts of equipment. With present day integrated circuits, it is easy to count, divide and display numerically the electrical pulses obtained from a great range of driver circuits.

In this book many applications and projects using various types of numerical displays, popular counter and driver IC's etc. are considered.

213: ELECTRONIC CIRCUITS FOR MODEL RAILWAYS \$4.50 M.H. BABANI, B.Sc.(Eng.)

The reader is given constructional details of how to build a simple model train controller, controller with simulated inertia and a high power controller. A signal system and lighting for model trains is discussed as is the suppression of RF interference from model railways. The construction of an electronic steam whistle and a model train chuffer is also covered.

BP73: REMOTE CONTROL PROJECTS \$8.60 OWEN BISHOP

This book is aimed primarily at the electronics enthusiast who wishes to experiment with remote control. Full explanations have been given so that the reader can fully understand how the circuits work and can more easily see how to modify them for other purposes, depending on personal requirements. Not only are radio control systems considered but also infra-red, visible light and ultrasonic systems as are the use of Logic ICs and Pulse position modulation etc.

CIRCUITS

BP80: POPULAR ELECTRONIC CIRCUITS — BOOK 1 \$8.25 R.A. PENFOLD

Another book by the very popular author, Mr. R.A. Penfold, who has designed and developed a large number of various circuits. These are grouped under the following general headings; Audio Circuits, Radio Circuits, Test Gear Circuits, Music Project Circuits, Household Project Circuits and Miscellaneous Circuits.

THE GIANT HANDBOOK OF ELECTRONIC CIRCUITS \$24.45 TAB No.1300

About as thick as thick as the Webster's dictionary, and having many more circuit diagrams, this book is ideal for any experimenter who wants to keep amused for several centuries. If there isn't a circuit for it in here, you should have no difficulty convincing yourself you don't really want to build it.

BP39: 50 (FET) FIELD EFFECT TRANSISTOR PROJECTS \$5.50

F.G. RAYER, T.Eng.(CEI), Assoc.IERE
Field effect transistors (FETs), find application in a wide variety of circuits. The projects described here include radio frequency amplifiers and converters, test equipment and receiver aids, tuners, receivers, mixers and tone controls, as well as various miscellaneous devices which are useful in the home.

This book contains something of particular interest for every class of enthusiast — short wave listener, radio amateur, experimenter or audio devotee.

BP87: SIMPLE L.E.D. CIRCUITS \$5.90 R.N. SOAR

Since it first appeared in 1977, Mr. R.N. Soar's book has proved very popular. The author has developed a further range of circuits and these are included in Book 2. Projects include a Transistor Tester, Various Voltage Regulators, Testers and so on.

BP42: 50 SIMPLE L.E.D. CIRCUITS \$3.55 R.N. SOAR

The author of this book, Mr. R.N. Soar, has compiled 50 interesting and useful circuits and applications, covering many different branches of electronics, using one of the most inexpensive and freely available components — the Light Emitting Diode (L.E.D.). A useful book for the library of both beginner and more advanced enthusiast alike.

BP82: ELECTRONIC PROJECTS USING SOLAR CELLS \$8.10 OWEN BISHOP

The book contains simple circuits, almost all of which operate at low voltage and low currents, making them suitable for being powered by a small array of silicon cells. The projects cover a wide range from a bicycle speedometer to a novelty "Duck Shoot", a number of power supply circuits are included.

BP37: 50 PROJECTS USING RELAYS, SCR'S & TRIACS \$5.50 F.G. RAYER, T.Eng.(CEI), Assoc.IERE

Relays, silicon controlled rectifiers (SCR's) and bi-directional triodes (TRIACS) have a wide range of applications in electronics today. This book gives tried and practical working circuits which should present the minimum of difficulty for the enthusiast to construct. In most of the circuits there is a wide latitude in component values and types, allowing easy modification of circuits or ready adaptation of them to individual needs.

BP44: IC 555 PROJECTS \$7.55 E.A. PARR, B.Sc., C.Eng., M.I.E.E.

Every so often a device appears that is so useful that one wonders how life went on before without it. The 555 timer is such a device. Included in this book are Basic and General Circuits, Motor Car and Model Railway Circuits, Alarms and Noise Makers as well as a section on the 556, 558 and 559 timers.

BP24: 50 PROJECTS USING IC741 \$4.25 RUDI & UWE REDMER

This book, originally published in Germany by TOPP, has achieved phenomenal sales on the Continent and Babani decided, in view of the fact that the integrated circuit used in this book is inexpensive to buy, to make this unique book available to the English speaking reader. Translated from the original German with copious notes, data and circuitry, a "must" for everyone whatever their interest in electronics.

BP83: VMOS PROJECTS \$8.20 R.A. PENFOLD

Although modern bipolar power transistors give excellent results in a wide range of applications, they are not without their drawbacks or limitations. This book will primarily be concerned with VMOS power FETs although power MOSFETs will be dealt with in the chapter on audio circuits. A number of varied and interesting projects are covered under the main headings of: Audio Circuits, Sound Generator Circuits, DC Control Circuits and Signal Control Circuits.

BP65: SINGLE IC PROJECTS \$6.55 R.A. PENFOLD

There is now a vast range of ICs available to the amateur market, the majority of which are not necessarily designed for use in a single application and can offer unlimited possibilities. All the projects contained in this book are simple to construct and are based on a single IC. A few projects employ one or two transistors in addition to an IC but in most cases the IC is the only active device used.

BP 50: IC LM3900 PROJECTS \$5.00 H.KYBETT, B.Sc., C.Eng.

The purpose of this book is to introduce the LM3900 to the Technician, Experimenter and the Hobbyist. It provides the groundwork for both simple and more advanced uses, and is more than just a collection of simple circuits or projects.

Simple basic working circuits are used to introduce this IC. The LM3900 can do much more than is shown here, this is just an Introduction. Imagination is the only limitation with this useful and versatile device. But first: the reader must know the basics and that is what this book is all about.

223: 50 PROJECTS USING IC CA3130 \$5.50 R.A. PENFOLD

In this book, the author has designed and developed a number of interesting and useful projects which are divided into five general categories: I — Audio Projects II — R.F. Projects III — Test Equipment IV — Household Projects V — Miscellaneous Projects.

224: 50 CMOS IC PROJECTS \$4.25 R.A. PENFOLD

CMOS IC's are probably the most versatile range of digital devices for use by the amateur enthusiast. They are suitable for an extraordinary wide range of applications and are also some of the most inexpensive and easily available types of IC.

Mr. R.A. Penfold has designed and developed a number of interesting and useful projects which are divided into four general categories: I — Multivibrators II — Amplifiers and Oscillators III — Trigger Devices IV — Special Devices.

THE ACTIVE FILTER HANDBOOK \$11.45 TAB No.1133

Whatever your field — computing, communications, audio, electronic music or whatever — you will find this book the ideal reference for active filter design. The book introduces filters and their uses also presents many practical circuits including a graphic equalizer, computer tape interface and more.

DIGITAL IC'S — HOW THEY WORK AND HOW TO USE THEM \$10.45 AB004

An excellent primer on the fundamentals of digital electronics. This book discusses the nature of gates and related concepts and also deals with the problems inherent to practical digital circuits.

MASTER HANDBOOK OF 1001 PRACTICAL CIRCUITS \$20.45 TAB No.800

MASTER HANDBOOK OF 1001 MORE PRACTICAL CIRCUITS \$19.45 TAB No.804

Here are transistor and IC circuits for just about any application you might have. An ideal source book for the engineer, technician or hobbyist. Circuits are classified according to function, and all sections appear in alphabetical order.

THE MASTER IC COOKBOOK \$16.45 TAB No.1199

If you've ever tried to find specs for a so called 'standard' chip, then you'll appreciate this book. C.L. Hallmark has compiled specs and pinouts for most types of ICs that you'd ever want to use.

ELECTRONIC DESIGN WITH OFF THE SHELF INTEGRATED CIRCUITS \$10.45 AB016

This practical handbook enables you to take advantage of the vast range of applications made possible by integrated circuits. The book tells how, in step by step fashion, to select components and how to combine them into functional electronic systems. If you want to stop being a "cookbook hobbyist", then this is the book for you.

AUDIO

BP90: AUDIO PROJECTS \$8.10 F.G. RAYER

Covers in detail the construction of a wide range of audio projects. The text has been divided into preamplifiers and mixers, power amplifiers, tone controls and matching and miscellaneous projects.

HOW TO DESIGN, BUILD, AND TEST COMPLETE SPEAKER SYSTEMS. \$13.45 TAB No.1064

By far the greatest savings in assembling an audio system can be realized from the construction of speakers. This book contains information to build a variety of speakers as well as instructions on how to design your own.

BOS: FIRST BOOK OF HI-FI LOUDSPEAKER ENCLOSURES \$3.55 B.B. BABANI

This book gives data for building most types of loudspeaker enclosure. Includes corner reflex, bass reflex, exponential horn, folded horn, tuned port, klipschorn labyrinth, tuned column, loaded port and multi speaker panoramic. Many clear diagrams for every construction showing the dimensions necessary.

BP35: HANDBOOK OF IC AUDIO PREAMPLIFIER AND POWER AMPLIFIER CONSTRUCTION \$5.50 F.G. RAYER, T.Eng.(CEI), Assoc.IERE

This book is divided into three parts: Part I, understanding audio IC's, Part II, Preamplifiers, Mixers and Tone Controls, Part III Power Amplifiers and Supplies. Includes practical constructional details of pure IC and Hybrid IC and Transistor designs from about 250mW to 100W output.

BP47: MOBILE DISCOTHEQUE HANDBOOK \$5.90 COLIN CARSON

The vast majority of people who start up "Mobile Discos" know very little about their equipment or even what to buy. Many people have wasted a "small fortune" on poor, unnecessary or badly matched apparatus.

The aim of this book is to give you enough information to enable you to have a better understanding of many aspects of "disco" gear.

HOW TO BUILD A SMALL BUDGET RECORDING STUDIO FROM SCRATCH. \$16.45 TAB No.1166

The author, F. Alton Everest, has gotten studios together several times, and presents twelve complete, tested designs for a wide variety of applications. If all you own is a mono cassette recorder, you don't need this book. If you don't want your new four track to wind up sounding like one, though, you shouldn't be without it.

BP51: ELECTRONIC MUSIC AND CREATIVE TAPE RECORDING \$5.50 M.K. BERRY

Electronic music is the new music of the Twentieth Century. It plays a large part in "pop" and "rock" music and, in fact, there is scarcely a group without some sort of synthesiser or other effects generator.

This book sets out to show how electronic music can be made at home with the simplest and most inexpensive of equipment. It then describes how the sounds are generated and how these may be recorded to build up the final composition.

BP74: ELECTRONIC MUSIC PROJECTS \$7.70 R.A. PENFOLD

Although one of the more recent branches of amateur electronics, electronic music has now become extremely popular and there are many projects which fall into this category. The purpose of this book is to provide the constructor with a number of practical circuits for the less complex items of electronic music equipment, including such things as a Fuzz Box, Waa-Waa Pedal, Sustain Unit, Reverberation and Phaser-Units, Tremelo Generator etc.

BP81: ELECTRONIC SYNTHESISER PROJECTS \$7.30 M.K. BERRY

One of the most fascinating and rewarding applications of electronics is in electronic music and there is hardly a group today without some sort of synthesiser or effects generator. Although an electronic synthesiser is quite a complex piece of electronic equipment, it can be broken down into much simpler units which may be built individually and these can then be used or assembled together to make a complete instrument.

ELECTRONIC MUSIC SYNTHESIZERS \$10.45 TAB No.1167

If you're fascinated by the potential of electronics in the field of music, then this is the book for you. Included is data on synthesizers in general as well as particular models. There is also a chapter on the various accessories that are available.

See the order form on page 27

TEST EQUIPMENT

BP75: ELECTRONIC TEST EQUIPMENT CONSTRUCTION

F.G. RAYER, T.Eng. (CEI), Assoc. IERE \$7.30
This book covers in detail the construction of a wide range of test equipment for both the Electronics Hobbyists and Radio Amateur. Included are projects ranging from an FET Amplified Voltmeter and Resistance Bridge to a Field Strength Indicator and Heterodyne Frequency Meter. Not only can the home constructor enjoy building the equipment but the finished projects can also be usefully utilised in the furtherance of his hobby.

99 TEST EQUIPMENT PROJECTS YOU CAN BUILD

TAB No.805 \$14.45
An excellent source book for the hobbyist who wants to build up his work bench inexpensively. There are circuits to measure just about any electrical quantity. The variety is endless and includes just about anything you could wish for!

HOW TO GET THE MOST OUT OF LOW COST TEST EQUIPMENT

AB017 \$9.45
Whether you want to get your vintage 1960 TestRite signal generator working, or you've got something to measure with nothing to measure it with, this is the book for you. The author discusses how to maximize the usefulness of cheap test gear, how to upgrade old equipment, and effective test set ups.

THE POWER SUPPLY HANDBOOK

TAB No.806 \$16.45
A complete one stop reference for hobbyists and engineers. Contains high and low voltage power supplies of every conceivable type as well mobile and portable units.

BP70: TRANSISTOR RADIO FAULT-FINDING CHART

CHAS. E. MILLER \$2.40
Across the top of the chart will be found four rectangles containing brief descriptions of various faults; viz: — sound weak but undistorted; set dead; sound low or distorted and background noises. One then selects the most appropriate of these and following the arrows, carries out the suggested checks in sequence until the fault is cleared.

ELECTRONIC TROUBLESHOOTING HANDBOOK

AB019 \$9.45
This workbench guide can show you how to pinpoint circuit troubles in minutes, how to test anything electronic, and how to get the most out of low cost test equipment. You can use any and all of the time-saving shortcuts to rapidly locate and repair all types of electronic equipment malfunctions.

COMPLETE GUIDE TO READING SCHEMATIC DIAGRAMS

AB018 \$9.45
A complete guide on how to read and understand schematic diagrams. The book teaches how to recognize basic circuits and identify component functions. Useful for technicians and hobbyists who want to avoid a lot of headscratching.

RADIO AND COMMUNICATIONS

BP79: RADIO CONTROL FOR BEGINNERS

F.G. RAYER, T.Eng. (CEI), Assoc. IERE. \$7.30
The aim of this book is to act as an introduction to Radio Control for beginners to the hobby. The book will commence by dealing with the conditions that are allowable for such things as frequency and power of transmission. This is followed by a "block" explanation of how control-device and transmitter operate and receiver and actuator(s) produce motion in a model.

Details are then given of actual solid state transmitting equipment which the reader can build. Plain and loaded aerials are then discussed and so is the field-strength meter to help with proper setting up.

The radio receiving equipment is then dealt with which includes a simple receiver and also a crystal controlled superhet. The book ends with the electro-mechanical means of obtaining movement of the controls of the model.

BP91: AN INTRODUCTION

TO RADIO DXing \$8.10
This book is divided into two main sections one to amateur band reception, the other to broadcast bands. Advice is given to suitable equipment and techniques. A number of related constructional projects are described.

No. 215: Shortwave Circuits & Gear For Experimenters & Radio Hams

\$3.70
Covers constructional details of a number of projects for the shortwave enthusiast and radio "Ham". Included are: an add-in crystal filter, adding an "S" meter in your receiver; crystal locked H.F. Receiver; AM tuner using phase locked loop; converter for 2MHz, 40 to 800 MHz RF amplifier, Aerials for the 52, 144MHz bands, Solid State Crystal Frequency Calibrator, etc.

BP46: RADIO CIRCUITS USING IC's

J.B. DANCE, M.Sc. \$5.90
This book describes integrated circuits and how they can be employed in receivers for the reception of either amplitude or frequency modulated signals. The chapter on amplitude modulated (a.m.) receivers will be of most interest to those who wish to receive distant stations at only moderate audio quality, while the chapter on frequency modulation (f.m.) receivers will appeal to those who desire high fidelity reception.

BP1: FIRST BOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES

B.B. BABANI \$2.80
This guide covers many thousands of transistors showing possible alternatives and equivalents. Covers transistors made in Great Britain, USA, Japan, Germany, France, Europe, Hong Kong, and includes types produced by more than 120 different manufacturers.

BP14: SECOND BOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES

B.B. BABANI \$4.80
The "First Book of Transistor Equivalents" has had to be reprinted 15 times. The "Second Book" produced in the same style as the first book, in no way duplicates any of the data presented in it. The "Second Book" contains only additional material and the two books complement each other and make available some of the most complete and extensive information in this field. The interchangeability data covers semiconductors manufactured in Great Britain, USA, Germany, France, Poland, Italy, East Germany, Belgium, Austria, Netherlands and many other countries.

TOWER'S INTERNATIONAL OP-AMP LINEAR IC SELECTOR

TAB No.1216 \$13.45
This book contains a wealth of useful data on over 5 000 Op-amps and linear ICs — both pinouts and essential characteristics. A comprehensive series of appendices contain information on specs, manufacturers, case outlines and so on.

CMOS DATABOOK

TAB No.984 \$14.45
There are several books around with this title, but most are just collections of manufacturers' data sheets. This one, by Bill Hunter, explains all the intricacies of this useful family of logic devices. . . the missing link in getting your own designs working properly. Highly recommended to anyone working with digital circuits.

BP68: CHOOSING AND USING YOUR HI-FI MAURICE L JAY

\$7.25
The main aim of this book is to provide the reader with the fundamental information necessary to enable him to make a satisfactory choice from the extensive range of hi-fi equipment now on the market.

Help is given to the reader in understanding the equipment he is interested in buying and the author also gives his own opinion of the minimum standards and specifications one should look for. The book also offers helpful advice on how to use your hi-fi properly so as to realise its potential. A Glossary of terms is also included.

REFERENCE

THE BEGINNER'S HANDBOOK OF ELECTRONICS

AB003 \$9.45
An excellent textbook for those interested in the fundamentals of Electronics. This book covers all major aspects of power supplies, amplifiers, oscillators, radio, television and more.

ELEMENTS OF ELECTRONICS — An on-going series

F.A. WILSON, C.G.I.A., C.Eng.,

BP62: BOOK 1. The Simple Electronic Circuit and Components \$8.95

BP63: BOOK 2. Alternating Current Theory \$8.95

BP64: BOOK 3. Semiconductor Technology \$8.95

BP77: BOOK 4. Microprocessing Systems and Circuits \$12.30

BP89: BOOK 5. Communication \$12.30

The aim of this series of books can be stated quite simply — it is to provide an inexpensive introduction to modern electronics so that the reader will start on the right road by thoroughly understanding the fundamental principles involved.

Although written especially for readers with no more than ordinary arithmetical skills, the use of mathematics is not avoided, and all the mathematics required is taught as the reader progresses.

Each book is a complete treatise of a particular branch of the subject and, therefore, can be used on its own with one proviso, that the later books do not duplicate material from their predecessors, thus a working knowledge of the subjects covered by the earlier books is assumed.

BOOK 1: This book contains all the fundamental theory necessary to lead to a full understanding of the simple electronic circuit and its main components.

BOOK 2: This book continues with alternating current theory without which there can be no comprehension of speech, music, radio, television or even the electricity utilities.


BOOK 3: Follows on semiconductor technology, leading up to transistors and integrated circuits.

BOOK 4: A complete description of the internal workings of microprocessor.

BOOK 5: A book covering the whole communication scene.

BP85: INTERNATIONAL TRANSISTOR EQUIVALENTS GUIDE

ADRIAN MICHAELS \$12.25
This book will help the reader to find possible substitutes for a popular user-oriented selection of modern transistors. Also shown are the material type, polarity, manufacturer selection of modern transistors. Also shown are the material type, polarity, manufacturer and use. The Equivalents are sub-divided into European, American and Japanese. The products of over 100 manufacturers are included. An essential addition to the library of all those interested in electronics, be they technicians, designers, engineers or hobbyists. Fantastic value for the amount of information it contains.

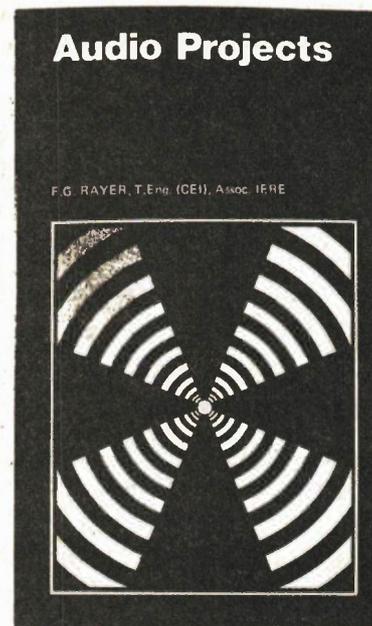

Book of the Month

Audio Projects BP90 \$8.10

You can always tell a guy with a good stereo set. He's the one down near the subway stop with a guitar and a sign that says "Throw money here". Even moderately decent audio is mind wrenchingly expensive; when you go for stuff where the knobs don't fall off it's really time to think about mortgaging the goldfish. Not surprising that sound projects are among the most popular things we run in ETI.

If you want to build your own sound system, or just play with pieces of it, *Audio Projects* is the ideal book. It covers the theory and construction of pre-amps, power amps, tone controls and audio test equipment. There are projects to suit everyone from the beginner to the real dedicated constructor who chants part numbers in his sleep.

Buy this book, truck on down to your favourite audio store and have a good sneer.

Do video-PONG players get testy and smash their rackets? Learn the untold story of this high powered sport.

PROBABLY THE BIGGEST attraction of the latest generation of home computers is that they can play video games, and one need not go down to the local saloon and shovel quarters into the pub attractions. The art of devising these games has risen to an astounding level, and the complexity of some of them boggles the mind. Video PONG seems like something they played back in the stone age.

Unfortunately, games like Asteroids and Allen Attack are almost always wholly written in machine code: this is the only way to get up the speed and complexity required to make the games fast and

PROGRAM 1

```

10 REM Basic Ballistic Ga
mes (Program 1)
20 PRINTCHR$(27):X=10:Y=40:J=1
:K=2:X1=10:Y1=40
30 GOSUB170
40 GOSUB100
50 PRINT@ (X1,Y1),CHR$(2) "
60 PRINT@ (X,Y),CHR$(2)CHR$(26)
" CHR$(25)
70 GOTO40
80 REM Decide Ball Direction a
nd Angles
90 REM J and K are ball direct
ion vectors
100 X1=X:Y1=Y
110 IFX<2THENJ=1
120 IFX>20THENJ=-1
130 IFY<4THENK=2
140 IFY>75THENK=-2
150 X=X+J:Y=Y+K
160 RETURN
170 REM print frame
180 PRINTCHR$(2)CHR$(128)::FOR
T=0TO75:PRINTCHR$(150)::NEXTT:
PRINTCHR$(129)
190 FORT=0TO20:PRINTCHR$(149)T
AB(77)CHR$(149)::NEXTT
200 PRINTCHR$(131)::FORT=0TO75
:PRINTCHR$(150)::NEXTT:PRINTCH
R$(130)
210 RETURN
    
```

exciting. In fact, as we saw last month, machine code is not completely unfathomable, but it is a much more cumbersome medium than are the higher level languages like BASIC. One would have to be a bit fanatical or fairly well paid to want to write an Asteroids-class game in ML code.

The fundamentals of video games, however, can be explored in BASIC very easily. It's difficult to do complex real time animation in BASIC because, as one adds more and more operations to a game program, the time delay inherent in each operation begins to catch up with the thing, and the whole works starts to drag. Simple ball movings and misse firings, on the other hand, are well within the scope of even moderately fast BASICs. The techniques, once understood, can later be applied to machine code programs if you really want to get into it.

The video games we're going to have a look at involve the manipulation of projectiles and targets, and are called ballistic games. All the following programs were written on a TRS-80 Model II in Microsoft BASIC, and will run, with a few modifications, on most machines. The only thing that might present a problem is that some BASICs don't have the PRINT@ statement, which allows you to PRINT beginning at any location on the screen specified by the X and Y co-ordinates in the brackets after the PRINT@. PETs, for example, don't have this. However, the PRINT@ can be replaced with a regular PRINT by POKEing the page zero memory locations corresponding to the cursor row and column positions with the X and Y values prior to PRINTing.

Log Table Tennis

Program 1 is the simplest iteration of PONG. It prints a boundary, the frame, and then makes a "ball", a white square, bounce around it. The way the ball works is fundamental to the operation of ballistic games.

First off, the ball is made to move by alternately printing it and erasing it. . . after it's been erased, it can be moved slightly and reprinted, giving the illusion that it's actually traversing the screen. Figuring out where the ball is going to be printed is what takes most of the time, so the idea is to have the ball

"on" while this is happening. We want to erase it just before reprinting it to minimize the flicker. Thus, all the calculations for the new ball co-ordinates and old ball erase co-ordinates are done after reprinting the ball. The printing and erasing part of the program is actually just lines 40 to 70. GOSUB100 is the co-ordinate calculation routine, and heart of the ballistics part of it all.

The ball has two qualities: position and direction. Direction is really just the delta position. The direction is provided by constantly adding to or subtracting from the two position determining variables, X and Y. If the ball starts out in the centre, and we keep incrementing X and Y by one, it will eventually hit one of the boundary walls, for the sake of discussion, let's say the bottom one. We can detect this by observing that the Y co-ordinate has become as large as the line number, or the Y co-ordinate, of the bottom line. At this point, we want to begin decrementing the Y variable, and keep on incrementing the X variable. This will give the appearance of the ball having bounced off the wall.

These increments and decrements are handled by repetitively adding the direction vectors J and K to X and Y. J and K can be either positive or negative, depending upon the last boundary X and Y hit. The values of J and K are determined by lines 100 to 140.

Coincidence

Program 2 adds to program 1 the facility of being able to intercept the ball with a bat and redirect it. The bat is moved up and down the right hand side of the screen by the F1 and F2 keys (you can use any two keys that strike your fancy by changing the CHR\$ values in lines 160 and 170). The bat works just like a ball, except that one co-ordinate is always fixed. Note that this co-ordinate must be an even number, as, since the ball moves horizontally by increments of two, it would never actually hit a bat that moved on an odd numbered column.

This type of approach eliminates a lot of heavy calculations while the game is actually running, and speeds things up considerably.

The tricky part about getting a ball and bat game to work is to find out when the ball and bat are occupying the same space, i.e., when they are co-incident. Since the TRS-80 Model II doesn't permit screen PEEKing, one must do this wholly within the program. Since the bat is always

being erased and reprinted, unlike the frame, which is only done at the onset of the game, it doesn't matter if the ball actually hits the bat. Thus, to detect co-incident, we have to see if the vertical co-ordinate of the ball is less than 3 greater than the upper limit of the bat, i.e., the co-ordinate where it's actually printed, at any time when the ball's horizontal co-ordinate is the same as that of the bat. Line 220 handles this.

The way the bat is printed is quite important, too. It is three characters stacked one on top of the other. We could just use three PRINT@ statements, but this would be quite slow. Instead, at the onset of the game, the program creates a string, B\$, which consists of one bat character, a cursor move down character, a cursor move left character, another bat character, and so on. A similar erase character, E\$, is also produced. Thus, anywhere B\$ is printed, a bat shows up.

PROGRAM 2

```

R10 REM Basic Ballistic Games (Program 2)
20 PRINTCHR$(27):X=10:Y=40:J=1:K=2:X1=10:Y1=40:Q=10:Q1=10
30 GOSUB240
40 GOSUB90
50 PRINT@ (X1,Y1),CHR$(2) " * :PRINT@ (X,Y),CHR$(2)CHR$(26) " *CHR$(25)
60 GOSUB150:GOTO40
70 REM Decide Ball Direction and Angles
80 REM J and K are ball direction vectors
90 X1=X:Y1=Y
100 IFX<2THENJ=1
110 IFX>20THENJ=-1
120 IFY<4THENK=2
130 IFY>75THENK=-2
140 X=X+J:Y=Y+K:RETURN
150 REM bat mover
160 Q$=INKEY$:IFQ$=CHR$(0)THENZ=-1
170 IFQ$=CHR$(0)THENZ=1
180 Q1=Q:Q=Q+Z
190 IFQ<3THENQ=3
200 IFQ>18THENQ=18
210 PRINT@ (Q1,64),E$:PRINT@ (Q,64),B$
220 IFY=64ANDX-Q>-1ANDX-Q<4THENJ=J*-1:K=K*-1
230 RETURN
240 REM print frame
250 PRINTCHR$(2)CHR$(128)::FORT=0TO75:PRINTCHR$(150)::NEXTT:PRINTCHR$(129)
260 FORT=0TO20:PRINTCHR$(149)TAB(77)CHR$(149):NEXTT
270 PRINTCHR$(131)::FORT=0TO75:PRINTCHR$(150)::NEXTT:PRINTCHR$(130)
280 B$=CHR$(148)+CHR$(255)+CHR$(252)
290 B$=B$+B$
300 E$=" "+CHR$(255)+CHR$(252)
310 E$=E$+E$
320 RETURN
    
```



TRS-80 to English Dictionary

The following are what the codes peculiar to the TRS-80 Model II do in these programs.

- CHR\$(1) is the F1 key.
- CHR\$(2) is the F2 key and turns off the cursor.
- CHR\$(13) is carriage return.
- CHR\$(25) turns off the reversed character mode
- CHR\$(26) turns on the reversed character mode
- CHR\$(27) is clear screen.
- CHR\$(32) is a blank space.
- CHR\$(128) is the upper left frame corner
- CHR\$(129) is the upper right frame corner.
- CHR\$(130) is the lower left frame corner
- CHR\$(131) is the lower right frame corner (and the camel's tail).
- CHR\$(148) is a vertical post (the camel's legs).
- CHR\$(149) is a thin vertical line character.
- CHR\$(150) is a horizontal line character.
- CHR\$(153) is a box that's about 1/2 filled in.
- CHR\$(155) is a box that's about 3/4 filled in.
- CHR\$(158) is a box that's all filled in.
- CHR\$(159) is an upwards arrow character.
- CHR\$(252) moves the cursor left.
- CHR\$(255) moves the cursor down.

SYSTEM"TIME 00.00" sets the computer's internal clock to 0.
 TIME\$ returns the time from the clock.
 RANDOM seeds the random number generator (might as well use it).
 SPACES(X) is a string of spaces X long.

Kill a Camel

Now for the crazy bit. Video PONG, educational though it may be, is dull, man. Therefore, program 4 contains a real game; "Kill a Camel". It was going to be "Kill a Cow", but the tall characters on the TRS-80 made my cow into a dromedary. It might be more suitable as "Atomize a Martian", but I felt like some senseless slaughter when I wrote this.

You are the Galactic Commander Thrak, sent to Earth by a clerical error to kill all the camels you can. You have landed your ship in a gulch in the desert (or whatever), in

PROGRAM 3

```

10 REM Kill the Camel
20 PRINTCHR$(27):Q=40:Q1=40:I=
100:N$="":M$=""
30 GOSUB 270
40 GOSUB 80
50 IF F1=0 AND INT(RND(10))=5 THEN
GOSUB 450:PRINT@(0,10),N" Dead
camels so far.":N=N+1
60 IF I<1 THEN GOTO 540
70 GOTO 40
80 REM bat mover
90 Q$=INKEY$:IF Q$=CHR$(01) THEN
Z=-1
100 IF Q$=CHR$(2) THEN Z=1
110 IF Q$=CHR$(13) THEN Y=Q:X=20:
GOSUB 170:PRINT@(0,40),I" Photo
n Torpedos left.":I=I-1
120 Q1=Q:Q=Q+Z
130 IF Q<2 THEN Q=2
140 IF Q>72 THEN Q=72
150 PRINT@(21,Q1),CHR$(2)" ":
PRINT@(21,Q),CHR$(2)CHR$(153)C
HR$(153)
160 RETURN
170 REM bomb mover
180 J=ABS((Q-40)/5):IF Q<40 THEN
J=J*-1
190 IF Y<30RY>70 THEN J=J*-1
200 Y1=Y:Y=Y+J:IF Y<1 THEN Y=1
210 X1=X:X=X-2
220 PRINT@(X1,Y1),CHR$(2)" ";;
PRINT@(X,Y),CHR$(2)CHR$(159)
230 XT=ABS(XC-X):YT=ABS(YC-Y):
IF XT<2 AND YT<2 THEN GOSUB 500:PRIN
T@(X,Y),"":X=X-0
240 IF X>2 THEN 190
250 PRINT@(2,Y),CHR$(2)" "
260 RETURN
270 REM print frame
280 PRINTCHR$(2)CHR$(128)::FOR
T=0 TO 75:PRINTCHR$(150)::NEXTT:
PRINTCHR$(129)
290 FORT=0 TO 20:PRINTCHR$(149)T
AB(77)CHR$(149):NEXTT
300 PRINTCHR$(131)::FORT=0 TO 75
:PRINTCHR$(150)::NEXTT:PRINTCH
R$(130)
310 REM Camel
320 DATA 32,32,155,153,131,150
,158,32,32,148,148,32
330 FORR=1 TO 3
340 FORT=1 TO 4
350 READH
360 N$=N$+CHR$(H)
370 NEXTT

```

which a whole herd of very stupid camels are sleeping. Every time one wakes up, you have opportunity to atomize it with a photon torpedo. . . . overkill to be sure. You have one hundred photon torpedos. For some reason I haven't made up yet, if you are closer to one wall of the gulch than the other, your photon torpedo will be attracted to the wall and, if it hits it, will ricochet off. The camels wake up and appear on the screen at random.

This program is offered as a representative of what you can do with BASIC ballistic games above and beyond PONG. It should be clear, in looking at it, that it uses many of the same elements and works in much the same way. The bat, representing Commander Thrak hiding behind a sand dune, works the same way except that it slides along the bottom. The photon torpedo (an arrow character in this case) is just a ball with a predetermined start and destination, and a more or less fixed direction. It does have a direction vec-

tor, though, which is a factor of the horizontal position of Commander Thrak. At 40, the centre of the screen, it has no lateral vector at all. Below 40 it gets increasingly negative and above 40, increasingly positive. At the extreme ends of the bat's travel, the photon torpedo rebounds off the wall immediately upon being discharged, so it actually appears to have the opposite vector.

The camel character and its erasure are set up prior to the start of the game, just like the PONG bat. The DATA statement at 320 holds the characters that make up the camel; these will be unique to the Model II, and you'll probably have to devise a camel of your own. Or be daring: kill gnus.

As will be apparent, the location and appearance of the camels are both random, and you must plug one before you get another one. The coincidence window, set in line 230, is fairly small, making it possible to wound a camel, and knock off a few of its parts, without actually causing it to evaporate. You gotta hit 'em square in da middle fer that.

```


380 FORT=1 TO 4:N$=N$+CHR$(252):
NEXTT:N$=N$+CHR$(255)
390 NEXTR
400 FORR=1 TO 3
410 FORT=1 TO 4:M$=M$+"":NEXTT
420 FORT=1 TO 4:M$=M$+CHR$(252):
NEXTT:M$=M$+CHR$(255)
430 NEXTR
440 RETURN
450 REM Print a camel
460 XC=RND(10)+2:YC=RND(60)+3
470 PRINT@(XC,YC),N$
480 F1=1
490 RETURN
500 REM Evaporate a camel
510 PRINT@(XC,YC),M$
520 F1=0
530 RETURN
540 REM finish game
550 PRINTCHR$(27):PRINT@(10,20
),"The sands are strewn with "
N" dead camels!":PRINT@(11,20)
,"Do you want to "CHR$(26)"R"C
HR$(25)"return to the ship"
560 PRINT@(12,20),"or "CHR$(26)
)"K"CHR$(25)"ill some more":I
NPUTW$
570 IF W$<>"R" AND W$<>"K" THEN 550
580 IF W$="R" THEN PRINTCHR$(27):
END
590 IF W$="K" THEN RESTORE:GOTO 10

```

Send us stuff. . .

If you have a favourite software bit, hardware modification, or a good design for a device to make data processing available to camel killers, send it to *Computing Today* and you could become a millionaire. We pay up to \$30.00 for good bits; thirty or forty thousand submissions and you're on your way. For full details, check out the December issue or PRINT us a letter.

END

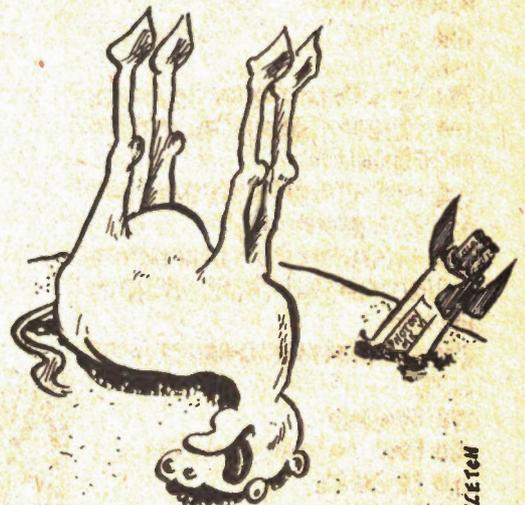

FILED

Designer Circuits

THE CA3080 USED AS A VCA

A simple voltage controlled amplifier (VCA) can be made using a CA3080 which is an Operational Transconductance Amplifier made by RCA. This is basically an op-amp with an extra input at pin 5. A current I_{ABC} is injected into this input and this controls the gain of the device linearly. Thus by inserting an audio signal (± 10 MV) between pin 2 and 3 and by controlling the current on pin 5, the level of the signal output (pin 6) is controlled.



In effect, the audio signal is multiplied by the current I_{ABC} . The output of the CA3080 is a current output and so a resistive load (R5) is needed; R5 in fact becomes the output impedance of the circuit.

The current controlling the CA3080 is generated with a voltage to current converter IC1, Q1, R1. This circuit linearly converts $V_{IN C}$ into a current (I_{ABC}) where:

$$I_{ABC} = \frac{V_{IN C}}{R1}$$

When $V_{IN C} = 0V$, I_{ABC} is 0 so the CA3080 is turned off. When $V_{IN C}$ is positive, I_{ABC} is generated and so the VCA is turned on. When $V_{IN C}$ goes negative, I_{ABC} is off so no output is produced from the VCA (see diagram).

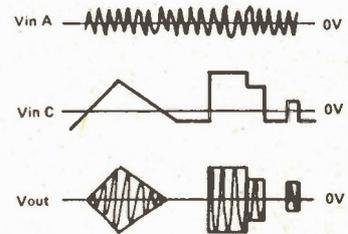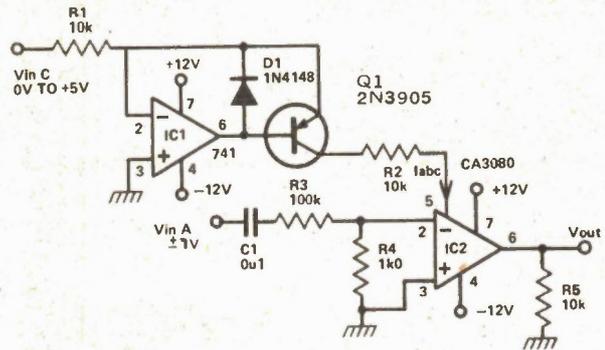The VCA finds many uses in the automatic control of signal levels and in generating envelope contours in electronic musical equipment.



NOTE: NO OUTPUT WHEN $V_{IN C}$ IS NEGATIVE

Teaching Electronics & Computing

If you're a teacher or lecturer in electronics or computing (in Canada), you should be receiving a FREE copy of our new publication in the second half of January. TEC will be mailed to all High Schools, Universities and School Boards.

The contents of TEC will be specifically aimed at this market and will include features on teaching techniques and experiences, reviews of equipment and books plus projects and technical notes free of the usual copyright restrictions and in fact designed for photocopying for use in the classroom.

If you feel that you qualify to receive TEC and don't see a copy by mid-February (to allow time for the mails) please write to us giving your position and establishment. If you qualify your name will be considered for inclusion.

Circulation Dept.,
Teaching Electronics and Computing,
Unit 6, 25 Overlea Boulevard,
Toronto, Ontario, M4H 1B1

Enlarger Timer

At last — an enlarger timer designed for the photographer by a photographer.


MOST ENLARGER TIMERS use either potentiometers or rotary switches for time period selection; however, both these methods suffer from some drawbacks. First, the potentiometers, although inexpensive, are generally difficult to line up with a timing mark, especially under darkroom conditions, and also tend to wear out after long usage. The rotary switch overcomes the alignment problem but the timing period range is normally limited to the number of click stop positions — mostly 12 ways, maximum 18 ways. The ETI Enlarger Timer does not suffer from either of these problems; it uses only eight toggle switches in conjunction with the 2240 programmable timer IC to offer a wide range of accurate and easily selected timing periods ranging from one second to 4 minutes 15 seconds in one-second steps.

This flexibility is due to the programmable eight bit counter, oscillator and control flip/flop featured within the timer IC. Having set the time base to 1S using PR1, R4 and C2, each single switch (SW1-8) will give the basic timing periods of 1,2,4,8,16,32,64 and 128 s; by switching in more than one switch, any combination of timing periods can be achieved as previously mentioned.

Construction.

As can be seen from the photographs, all switches and push-buttons are mounted on the front panel together with the LED Indicator. Suitable AC power input and output sockets are mounted on the rear case panel, input nearest the transformer, output (for the enlarger) by the PCB. The PCB design will enable an easier and neater assembly, but make sure to orientate components D1-D5, Q1, IC1, C2, C3 and LED1 as shown in the overlay diagram. Note that C2 must be a tantalum bead type.

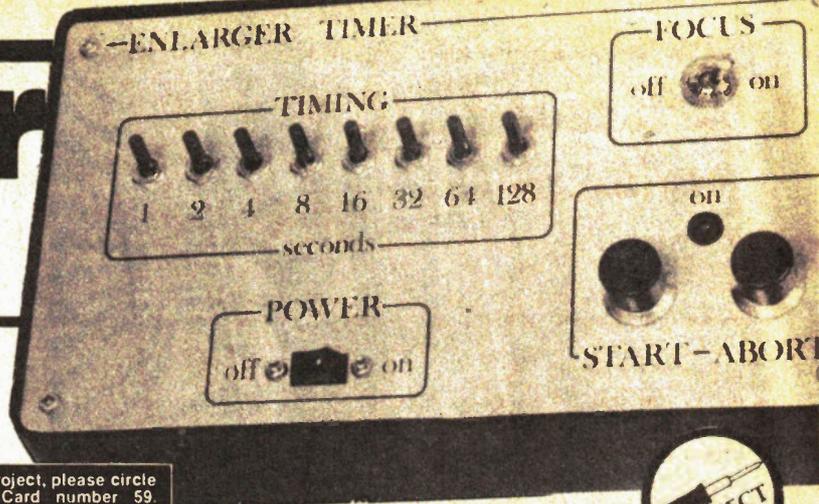Once all the components are mounted on the PCB and the switches, LED1, sockets and transformer are wired to the board, make sure that the panel assembly does not hit the transformer or the relay when fitted into the case.



If you liked this project, please circle Reader Service Card number 59. If you didn't, circle number 60.

Setting Up

This couldn't be easier; having checked all connections, connect the timer to the AC and the enlarger to the unit. First put switches SW1-8 and SW10 in the "off" positions, put SW9 (on/off switch) in the "on" position, operate focus switch SW10 and the enlarger lamp will light. Switch SW10 to the "off" position. Adjustment to the timing range can now be made; switch SW1 only (1 s switch) to "on" and adjust PR1 to give a timing period of 1 s after PB1 (start) is pushed — a stopwatch or digital watch is ideal for this.

Using The Timer

Switch on SW9 (on/off switch) and power will be applied to the circuitry. SW10 can be used for focusing the enlarger; switch off SW10 once this is done. Select the timing period required using a combination of SW1-8, push PB1 and the enlarger lamp timing cycle will commence; after this period the timer will stop/reset. LED1 will be on during timing period as a visual indication. If cancellation of a timing period is needed press PB2, which will abort and reset the timer. If any interference from RLA/2 is experienced, fit a 100nF 600V capacitor as marked on the circuit and overlay diagrams (C4).

HOW IT WORKS

The heart of the ETI Enlarger Timer is the 2240 programmable timer IC which features a time base oscillator, programmable eight bit counter and a control flip-flop that can be used in monostable or astable mode. Here it is used in the monostable mode.

On application of a positive pulse to pin 11 (trigger) via PB1 and R1, the timing cycle is started. The trigger input activates the time base oscillator, enables the counter section and sets the counter outputs low from their normally high states. This switches on Q1 and activates RLA for the time duration as set by the SW1-8 combination. The timing sequence is completed when a positive pulse is applied to pin 10 (reset) via R3 from the output bus, disabling the time base and counter sections and returning the counter outputs to a high state.

The duration of the timing cycle T_0 is given as:

$$T_0 = nT = nRC \text{ seconds} \\ (R \text{ in ohms, } C \text{ in farads})$$

where $T (= RC)$ is the time base period as set by the timing components at pin 13 (PR1, R4 and C2) and n is an integer in the range of 1 less than or equal to n less than or equal to 255 as determined by the combination of counter outputs (pins 1-8) via SW1-8 to the output bus. The time base as set by PR1, R4 and C2 is 1S.

The binary-counter outputs are the open collector type and can be shorted together to the common pull-up resistor R6. Thus the time delays associated with each counter input can be added together; for example, if pin 6 is connected by SW6 to the output bus the duration of the timing cycle, T_0 is 32 T. (T is 1S as previously stated). Similarly, if pins 1, 5, and 6 are all connected to the output bus via their appropriate switches SW1, SW5 and SW6, the total time delay is 49T (1 + 16 + 32). In this manner the timing cycle can be programmed to be from 1 S to 255 S (four minutes 15 S) in 1 S steps by proper choice of switches SW1-8.

The enlarger lamp is powered from the AC outlet socket and receives its current via the RLA/2 contacts for the duration of the selected timing period. An LED is incorporated as a visual indicator; it is switched on by RLA/1 and remains on for the timing period. Manual cancellation is provided for by PB2 which applies a positive pulse to pin 10; this can be used at any point in the timing period. SW10, the focusing switch, over-rides the RLA/2 contact regardless the output state of IC1 thus enabling the enlarger to be focused.

The power supply consists of T1, D2-D5 and C3 which provides filtering.

PARTS LIST

Resistors (all 1/4 W, 5%)

R1,2,6	10k
R3	47k
R4	33k
R5	22k
R7	1k5

Potentiometer

PR1	22k miniature horizontal preset
-----	---------------------------------

Capacitors

C1	10n disc ceramic
C2	22u 16V tantalum
C3	1000u 25V axial electrolytic
C4	100n 600V mixed dielectric


Semiconductors

IC1	uA2240CP
Q1	2N3702
D1	1N4148
D2-5	1N4001
LED1	0.2" red LED

Miscellaneous


PB1,2	momentary action push-button
SW1-8	SPST miniature toggle
SW9	SPST 240V 3A miniature rocker
SW10	SPST 240V 3A toggle
RLA	12V DPDT PCB-mounting, 205R coil

Transformer (12V, 250mA or similar); AC outlet socket; PCB ; power cord; case to suit.

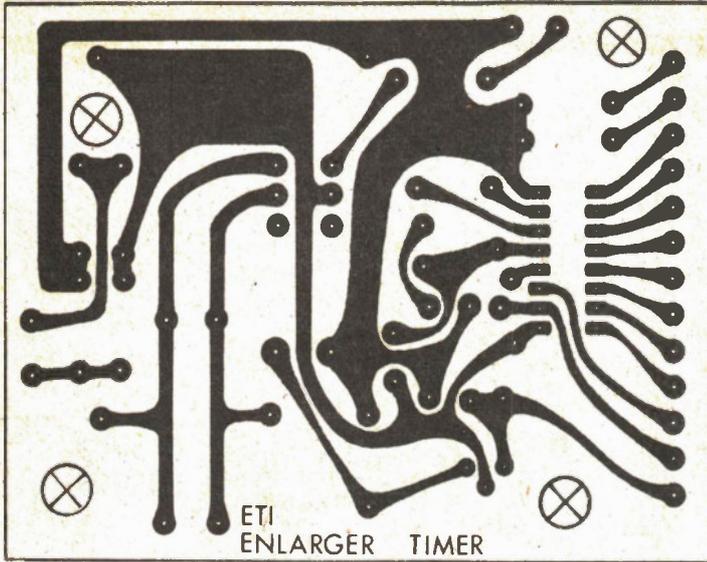


ET1
ENLARGER TIMER

Fig. 1 Component overlay of the Enlarger Timer.

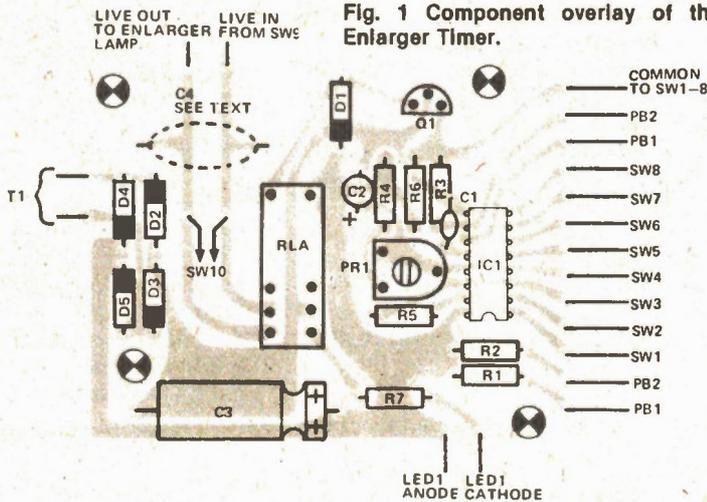

- COMMON TO SW1-8
- PB2
- PB1
- SW8
- SW7
- SW6
- SW5
- SW4
- SW3
- SW2
- SW1
- PB2
- PB1

LED1 ANODE CATHODE

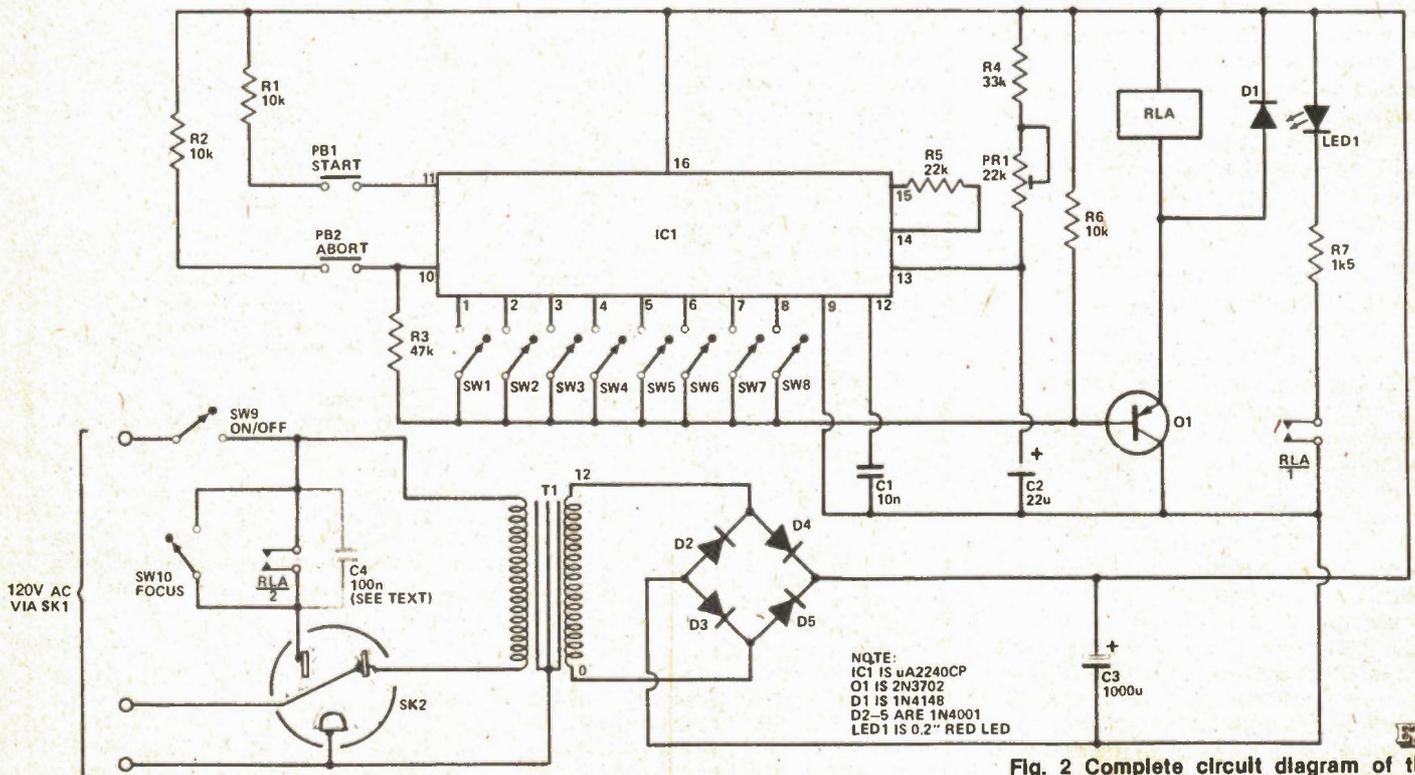

NOTE:
IC1 IS uA2240CP
Q1 IS 2N3702
D1 IS 1N4148
D2-5 ARE 1N4001
LED1 IS 0.2" RED LED

Fig. 2 Complete circuit diagram of the timer. C4 may be necessary to suppress switching noise from the relay contacts.

A Touch of Class

Our society need never be classless so long as we have power amplifiers. Wally Parsons explains.

EVEN SINCE THE EARLY TUBE DAYS, audio enthusiasts have been concerned about the relationship between efficiency, power output, sensitivity, and distortion of audio amplifying devices. Dissatisfied with the limited output capabilities of their simple 2A3 triode tubes, various circuit arrangements and operating conditions were developed to increase output and/or reduce distortion, although it was often felt that the two simply didn't go together.

The availability of better devices, first tubes, and later transistors, made life simpler, but the parallel development of loudspeakers of low efficiency increased the power requirements, thus effectively cancelling any benefits.

Today we have speakers of greater efficiency than was common a decade ago, but now we have programme sources of greater dynamic range, coupled with the desire, especially among rock fans, to play music very loud.

As Demosthenes might have said: "Plus ca change, c'est la meme chose".

One of the most important characteristics of amplifier design is the class of operation of each stage.

Any amplifier stage may be operated as a class A, class B, or class C amplifier. In addition, a tube stage may also operate in class B₁ or class B₂. Operation may even be described as class AB, with tubes offering AB₁ and AB₂ options.

To add to the confusion of all this alphabet soup, manufacturers advertise their products as "class A" or "class AB" amplifiers in a manner such as to imply that "class" was synonymous with "quality". Many have even taken more letters from the alphabet and dragged in OPEC and the anticipated energy crisis to justify a preoccupation with efficiency without the loss of quality alleged to accompany other classes of operation.

In an effort to clear up the confusion we shall examine the three principal classes and their characteristics.

As Simple As ABC

Class of operation is often thought of as a description of bias conditions, but in reality the term describes that fraction of a signal period during which the active device conducts. A period, for a single frequency, is one cycle, and can be divided into 360°, as shown in Fig. 1.


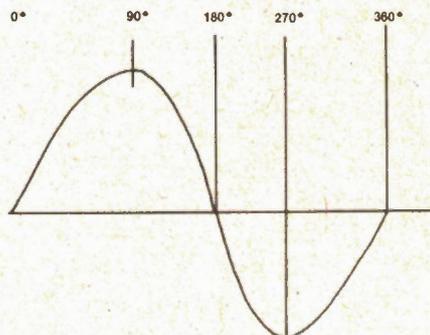


Fig. 1 One period.

Suppose that a tube or transistor is set up with electrode voltages such that with no signal input, a certain amount of current flows through the device. If a signal such as that shown in Fig. 1 is applied to the control electrode, that electrode's voltage or current will rise and fall around the quiescent point, causing the output current to rise and fall in step. Provided that the instantaneous sum of the signal and the quiescent voltage is never such as to cause the device to cut off, current will be passed during all portions of the input signal. The device is said to be operating in class A.

Class A is that condition of operation in which output current flows during 360° of the input signal cycle.

Fig. 2 and Fig. 2a show a family of curves and a transfer characteristic, respectively, for a hypothetical device. They are plotted for various values of grid voltage or base current against plate or collector voltage in the horizontal co-ordinates, and plate or collector current in the vertical co-ordinates. In ad-

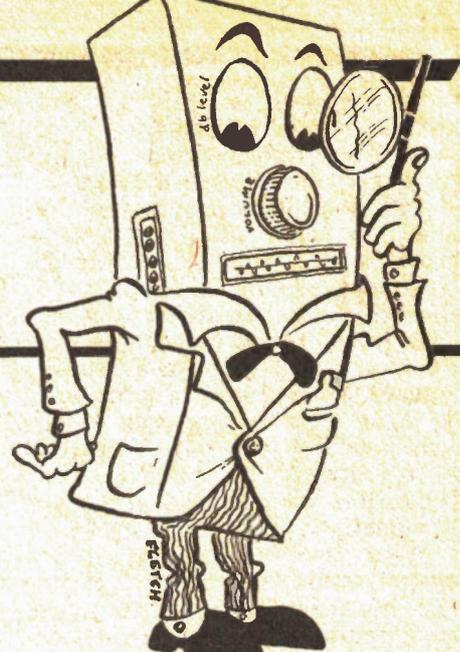

dition, a load line has been drawn, so that, by following the changes in control electrode voltage or current where they intersect the load line, changes in plate or collector voltage or current can be read. The transfer characteristic redraws this showing control electrode change in the horizontal co-ordinate and output voltage in the vertical.

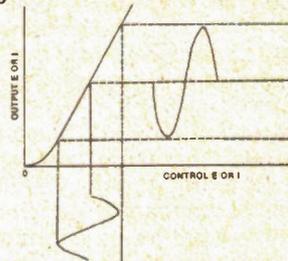


Fig. 2 Family of curves.

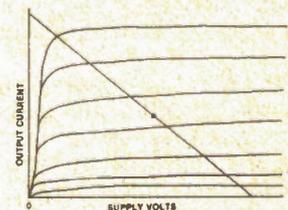


Fig. 2a Transfer curve.

It can be seen from Fig. 2 and 2a that maximum signal handling capacity occurs when bias is set at a point half way between cut-off and maximum current output. This has given rise to the popular concept of operation class which defines it in terms of bias.

What are the advantages of such a simple arrangement? Well, for one thing, it makes possible some pretty simple voltage and power amplifier circuitry. As long as the transfer characteristic is linear low distortion is possible at all levels.

Examination of Fig. 2a will disclose that, for symmetrical signal and a linear transfer characteristic the output current rises and falls by an equal amount above and below the quiescent level. The net result, through a period of one cycle, is that the average current is equal to the quiescent current no matter what the signal level. Consequently, the power supply can be quite simple, as it does not have to accommodate current demand variations greater than a one cycle period of the lowest period to be reproduced. This holds true as long as it is not required to amplify a DC signal.

And the disadvantages? In straight voltage amplifier applications, none. But getting a lot of power into a load can be a bit tricky, whether you use a single ended or a push-pull circuit. It's not just a question of getting current swing, but of internal power dissipation versus power delivered to a load. Consider what happens under zero signal conditions: current is constantly flowing through the device and may or may not be flowing through the load. Most power amplifiers use a push-pull circuit based on the "totem pole" arrangement with the load connected at the mid or zero point. No power is dissipated in the load, yet the transistors or tubes are required to dissipate all the input power. As signal levels increase a greater proportion of the input power is dissipated in the load. This increased efficiency at high levels might seem like an asset except for the fact that the ability to get rid of heat under idle conditions imposes a real limit on how much power we can get out of our device.

In addition, the power supply must be able to deliver full output at all times, imposing severe demands on power transformers and rectifiers, as well as any other series pass devices which may be used in the supply circuit.

A Different Class

The most common method of increasing the power output of a single active device is to use a pair of them in push pull. Because the input and output signals are opposite in phase, it is not necessary for each stage to handle the entire signal.

Referring again to Fig. 2 and Fig. 2a, consider the effect of moving the bias point to the extreme right of the load line. Under these conditions no current will flow in the output circuit. For a bi-polar transistor this occurs

when no bias current is caused to flow in the base circuit, while for a vacuum tube it occurs at some value of negative grid bias determined by the design of the tube. If a sine wave is applied to the input, one half of the signal will cause an increase in current flow, while the other half cycle will force the device further into cut-off. Thus, current will flow only during one half cycle.

Class B is that condition of operation in which output current flows only during 180° of the input cycle.

Since only half the signal is passed, the output is obviously quite distorted by any standards. Therefore, for any linear applications such operation is only used in push-pull circuitry.

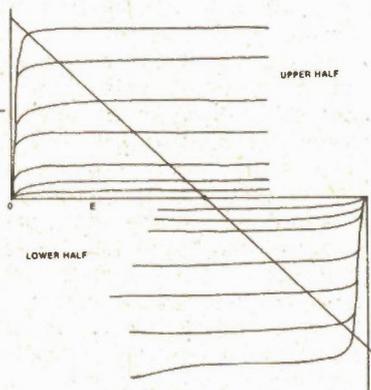


Fig. 3 Push-pull curves.

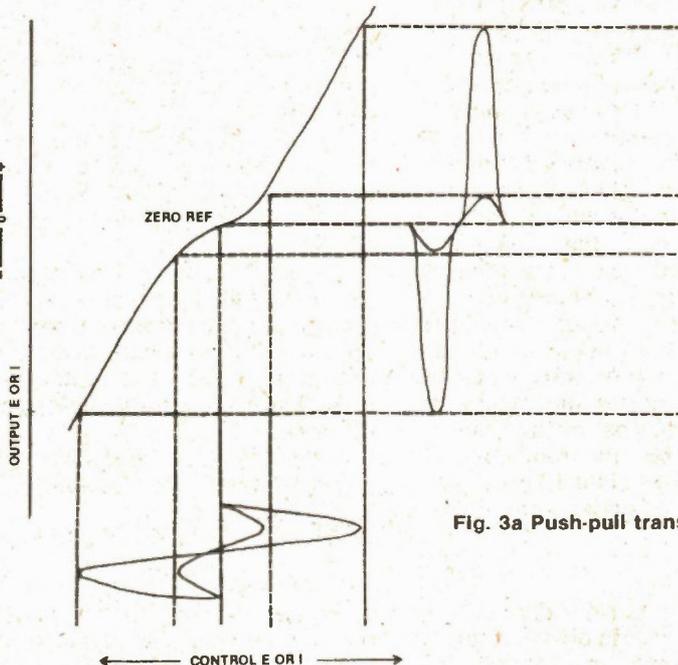


Fig. 3a Push-pull transfer curves.

Figs. 3 and 3a are the same as Figs. 2 and 2a, only redrawn for a pair of devices in push-pull. Notice in the transfer curve how the curvature at the bottom of the curve results in severe waveform distortion at the point of crossover from positive to negative going signal. Because it occurs at the crossover point it is referred to as crossover distortion, and is the basis for the principal objection to this class of operation. To aggravate this condition, a transistor does not go smoothly to cut-off, but has a small voltage, usually about 0.5V, required just to turn on the device. Consequently, there is a region of about 0.5V on either side of the zero axis of the signal in which no conduction occurs at all. Because this is a non-linear condition, harmonic distortion is generated, and because it is constant level for all values of signal level, the distortion components are of constant value, resulting in a distortion figure due to this mechanism which increases at low levels.

Much has been made of this distortion mechanism and its contribution to amplifier quality, or lack of quality, but examination of Figs. 3 and 3a will indicate, and inspection of a real circuit on an oscilloscope will prove, that this is easily eliminated by shifting the bias point in such a way that, instead of cutting the device off completely at zero signal condition, it rests just on the junction point of the toe of the transfer curve (the curvature to the extreme left) and the linear portion.

Much of this is also prejudice carried over from tube days, when poor coupling between halves of the output transformer winding would cause ringing at the cross-over, and early transistor devices whose high base-emitter capacitance would discharge through the load at each crossover.

Most problems with Class B operation involve the power supply. Because output current does not swing symmetrically around a reference point, the load current *increases* with signal level. Consequently, the power supply must maintain good regulation over a wide range of load conditions, and be capable of delivering large amounts of current quickly when transients demand.

Advantages

All of the above problems can readily be dealt with by good design, and refraining from giving in to the temptation to do things on the cheap.

In return for all this trouble there are real benefits. The first of these is greater power.

In a push-pull circuit the instantaneous output voltage is taken between the two devices. Class B operation allows twice as much voltage swing on one device, but provides for zero swing on the opposite side of the circuit since they are out of phase. Consequently there is no voltage, and hence no power increase. However, the optimum load under class B conditions is different from class A and can be arranged to allow greater output swing without running into an area of excessive dissipation. Moreover, since at low signal levels little current is drawn, the device generates less heat. Since amplifiers spend most of their lives running at low levels, it's comparatively easy to get rid of the heat generated at higher levels. As a matter of fact, for reasons beyond the scope of this article, it is possible to show that maximum dissipation occurs at about 30% of maximum output. Therefore, an amplifier operated in such a way as to provide at least 10 dB of headroom most of the time will also be operating well below the maximum dissipation level most of the time.

This is a far cry from class A which is operating close to maximum dissipation even under zero signal conditions.

Class AB

The variations in current drawn from the power supply with different levels implies variations in internal im-

pedance. It follows, then, that a class B stage is likely to be sensitive to variations in output load resistance. In addition, biasing a device at or close to cutoff results in high sensitivity to small changes in supply voltages such as may be caused by line fluctuations. A small change in bias current or voltage can make the difference between a device being just turned on and being off.

To overcome this, a stage may be operated at a point between class A and class B, or class AB. Usually the bias point and load are selected such that, at low levels, the stage operates a little above the toe of the transfer curve, so that for small signals it operates as a class A stage, since output current flows during the entire cycle. As signal level increases the stage is cut off during part of the cycle.

Class AB is that condition of operation in which output current flows for less than 360° but more than 180° of the input cycle. In fact, the most common practice allows current flow during about 235°.

Under small signal conditions the stage offers all the advantages of class A operation, with the added advantage of reduced dissipation, while at high levels it allows high power outputs without excessive dissipation problems, although it is not as good in this respect as true class A.

This means that since the amplifier operates at low levels most of the time, it also operates in class A most of the time, with few of the disadvantages.

The power supply must still be capable of delivering varying currents without changing output voltage, but the variations are less severe than with class B.

And although somewhat sensitive to load variations, it is less severe than class B. Unfortunately, it is at its worse under high signal levels.

With transistor circuits there is the possibility of some switching distortion when devices turn off and on, but with modern devices and appropriate circuitry this is not only inaudible but won't even show up on instruments.

All in all, an excellent way of getting the best of both worlds.

In The Interests Of Completeness

Reference was made earlier to class B₁, B₂, AB₁, and AB₂. Strictly speaking, the number suffixes refer to conditions which only apply to tube cir-

cuits. Ordinarily, a tube's grid is only driven in the positive direction to the point of zero volts. A positive voltage on the grid would result in grid current, with grid overheating and distortion. However, when driven from a low impedance source capable of some power output, it is possible to drive the grid into the positive region, with a resulting increase in power output. The suffix "2" is used to indicate this condition while "1" indicates that no grid current flows.

There is no counterpart to this operating condition with bi-polar transistors, but the possibility exists for operating junction FETs and MOS-FETs of the depletion type in such a way that input voltage swings past the zero point. I haven't seen any audio power circuits in which this is done, but there seems no reason why it could not, with suitable devices.

It is normal for grid current to be drawn in class C tube circuits.

Class C is that condition in which output current is drawn during considerably less than 180° of the cycle.

Obviously, considerable distortion is generated, and this mode of operation is limited to RF and other fixed frequency circuits which can be tuned to the fundamental, thus removing the distortion components. Its main advantage is the extremely high efficiency possible. While it has no real use in audio work, I've included the reference for the sake of completeness.

Class D is another mode of operation, which does not really refer to operating points, but has a long audio history. In class D operation the device is operated in such a way as to be completely on or off. In other words, it is a switching mode. Although it applies to linear application, it also, in a sense, forms a bridge between analog and digital operation, and requires separate treatment.

But don't let anyone tell you that some particular class of operation is first class and all others second.

Just t'aint so!

If you liked this article, please circle Reader Service Card number 45. If you didn't, circle number 46.

dbx Noise Reduction

Overshadowed by Dolby despite its theoretical superiority, the dbx noise reduction system now seems poised to take the hi-fi market by storm. Peter Green expands our headroom.

UNTIL NOW it has been impossible to listen to music at home with anything like the quality of the original. However much you spend on your hi-fi, however low the distortion figures, however carefully you care for your records and however diligently you clean your tape heads, you cannot get away from the twin evils of surface noise and restricted dynamic range.

Surface noise is caused by the limited quality of the recording medium itself. Imperfections and inhomogeneity in the particles that make up the tape coating generate the familiar hissing we know and hate; the roughness of the vinyl surfaces of record grooves produces its share of hissing and pops. Surface noise also affects dynamic range. During a live performance it is possible for sound pressure levels to momentarily hit 120 dB during music transients; however, background noise levels in the audience can easily range from 30 to 50 dB and so this simplistic treatment indicates that live music has a perceived dynamic range of about 70 to 90 dB. Unfortunately a good cassette recorder has a dynamic range of only about 45 dB, while a conventional vinyl record is not much better at 55 dB. Recording engineers have to compress the signal by a factor of 2:1 so that the loudest passages are below the level that causes tape saturation or distortion, and the quietest passages are above the level of tape hiss or record surface noise (see Fig. 1). This squeezing of the signal into a restricted dynamic range makes the music sound flat, unexciting and unrealistic. You know it's a recording.

D Versus d

The noise reduction system that established a virtual monopoly in the world hi-fi

market of the seventies was Dolby B, a system that reduced high frequency noise (the most objectionable kind) by boosting high frequencies on recording and attenuating them on playback, thus also reducing the noise added in the recording process.

dbx decided to tackle the other problem — restricted dynamic range. Since sounds have to be compressed to be recorded on tape or disc, a system that allowed 1:2 expansion on playback would recreate the range of the original performance (Fig. 2). This idea is quite old but difficult to apply, because the expander and compressor must track each other (be exactly complementary), especially on transients — this in turn requires accurate detection of the signal. The difficulties in this and the way the dbx overcame them are described later, but the important point is that when the recorded signal is expanded the tape noise drops below the level of audibility. dbx have killed two birds with one stone, together with an assortment of sacred cows; for example, they recommend that you use chromium dioxide rather than metal tapes, because it's pointless to pay extra money for an improvement of 2 to 3 dB when the system itself is giving you an extra 30 dB across the whole frequency range.

Paths Of Glory

Fig. 3 shows the block diagram of a Type II dbx noise reduction system for domestic use (the Type I system has certain differences in the turnover frequencies of the filters to suit professional situations). The encoder and decoder each have two paths — the signal and detection paths.

The music signal to be recorded first goes through a band pass filter to remove unwanted out-of-band components. Type II values are 30 Hz to 100 kHz, Type I are 22 Hz to 27 kHz. The lower limit is there to prevent subsonic noise from underground trains, traffic vibrations and the like from being recorded; the upper

If you liked this article, please circle Reader Service Card number 47. If you didn't, circle number 48.

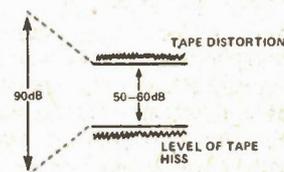


Fig. 1 When recording tapes or discs, engineers monitor the signal and turn the level up or down ('gain riding') to avoid distortion or hiss. This compression greatly reduces the dynamic range to an absolute maximum of about 60 dB.

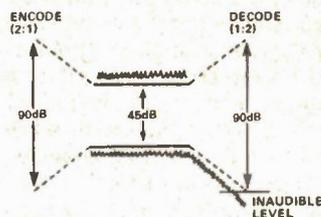


Fig. 2 By introducing 2:1 compression on recording, then accurately and automatically reversing the process on playback, the dbx noise reduction system reclaims the original dynamic range. As a bonus, tape hiss becomes inaudible.

limit prevents pick-up of CB and other interference. The Type I value is much lower because studios often have very long leads which are more susceptible to pick-up. The signal passes through a pre-emphasis network that boosts high frequencies and helps to overcome tape modulation noise (which is caused by uneven magnetisation due to tape inconsistency), and into the voltage-controlled amplifier. The VCA is linear in dB with control voltage to make things simpler later on; it compresses the signal by a 2:1 ratio.

The output of the VCA is passed to the tape recorder, and also into the detector section. The first stage is a band pass filter which has a slope of 18 dB/octave above 10 kHz, so that the detector 'takes

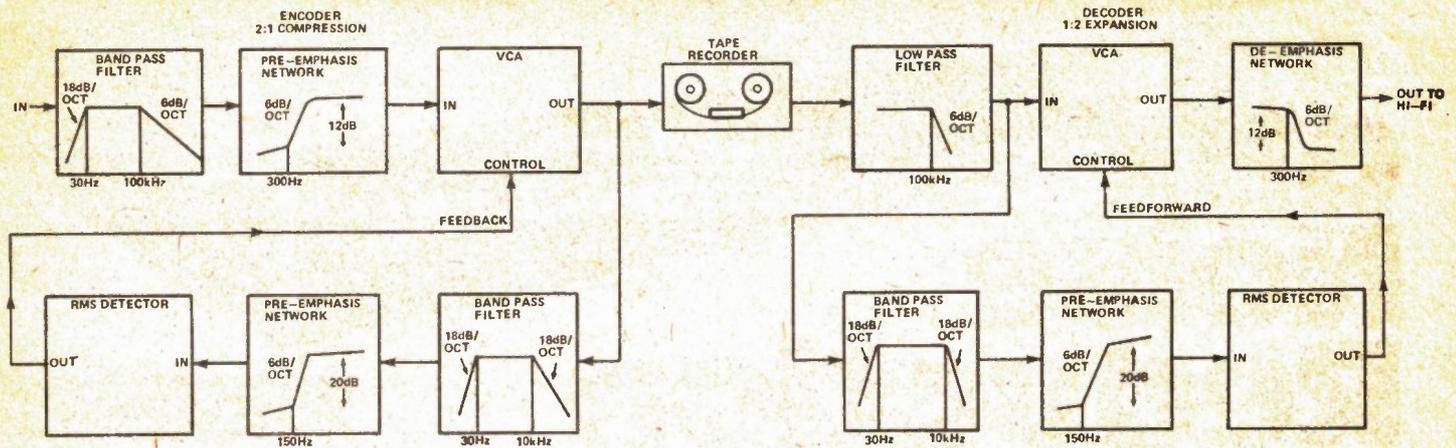


Fig. 3 Block diagram of the Type II dbx noise reduction system.

less notice' of high frequencies. Next comes another pre-emphasis network, this time to increase the compression of the signal at high frequencies and avoid the possibility that the pre-emphasis in the signal path will cause high frequency tape saturation. The RMS detector converts the AC signal into a DC voltage proportional to the level in dB; since the VCA also follows this law the whole system is linear in dB.

Mirror, Mirror

The encoder is a compressor with negative feedback; the higher the signal level the greater the gain reduction. The decoder must be a mirror image to give the correct tracking and recovery of the original performance, so it is configured as a feedforward system acting as a 1:2 expander. The importance of this is that if the tape recorder is considered to be 'transparent' the VCA control voltage in the decoder is being derived from exactly the same signal as that for the encoder VCA. The detector path in the decoder is identical to the one already described — band pass filter, pre-emphasis network, RMS detector — and so the control signals will also be identical (to within component tolerances). The decoder VCA has its control polarity reversed and gives a complementary gain change to that of the encoder; the de-emphasis network reverses the effect of the encoder pre-emphasis to restore a flat overall frequency response. It's interesting to note that this flat system response is due solely to the mirror-image nature of the signal processing — the frequency responses of encoder and decoder are complementary, but not flat.

Because a high value of loop gain (40 dB) is employed in the decoder, a low pass filter is needed at the input to prevent high-frequency oscillation caused by capacitive coupling. This keeps the system stable.

RMS detectors have been used because tape recorders aren't perfect, or

'transparent' — they introduce huge amounts of phase shift. This is not noticeable to the ear, but the effect of passing a 1V peak-to-peak square wave through a 90° phase shift filter is shown in Fig. 4; cheaper and simpler detectors such as peak or averaging types would not give identical outputs for the two waveforms and the mirror-imaging would be lost. An RMS detector is the only one that will give the same output level for both.

Silence Is Golden

If anyone feels that the working of the system is hard to understand, rest assured that a practical demonstration isn't. A recent dbx press showing started with a hiss comparison using blank unencoded tape, first with no noise reduction, then Dolby B, Dolby C and finally dbx. Hiss was still significant with the two Dolby systems, although the improvement was noticeable — but when the dbx cut in, nothing could be heard except the gasps of amazement from hardened journalists. No hiss whatsoever! Listening to extracts from discs and tapes was a revelation; for the first time in my life I could shut my eyes and believe the orchestra was really there. I

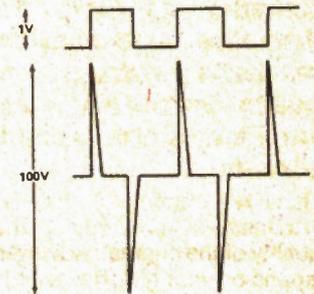


Fig. 4 Phase shift can have dramatic effects on the shape of waveforms!

heard musicians fingering their instruments, I heard someone on the record sniff, and the music appeared out of a silent background — It was real!

Naturally the impact dbx has on the market will depend on how many encoded discs and tapes they can release, and how quickly. But several major cassette deck manufacturers (eg Technics, Teac, Yamaha, Marantz) are fitting dbx along side Dolby in some of their models, and Dolby must be thinking hard about their next move.

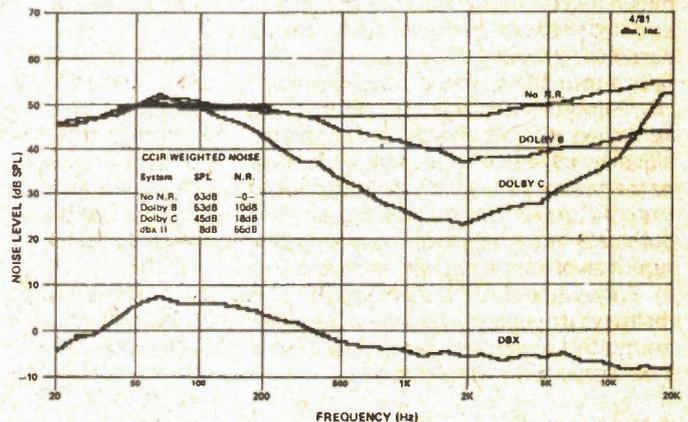


Fig. 5 A comparison graph of noise reduction systems, issued by dbx.

SW Aerials

The traditional long wire receiving aerial for short wave enthusiasts is cheap and easy to set up. These are alternatives, though

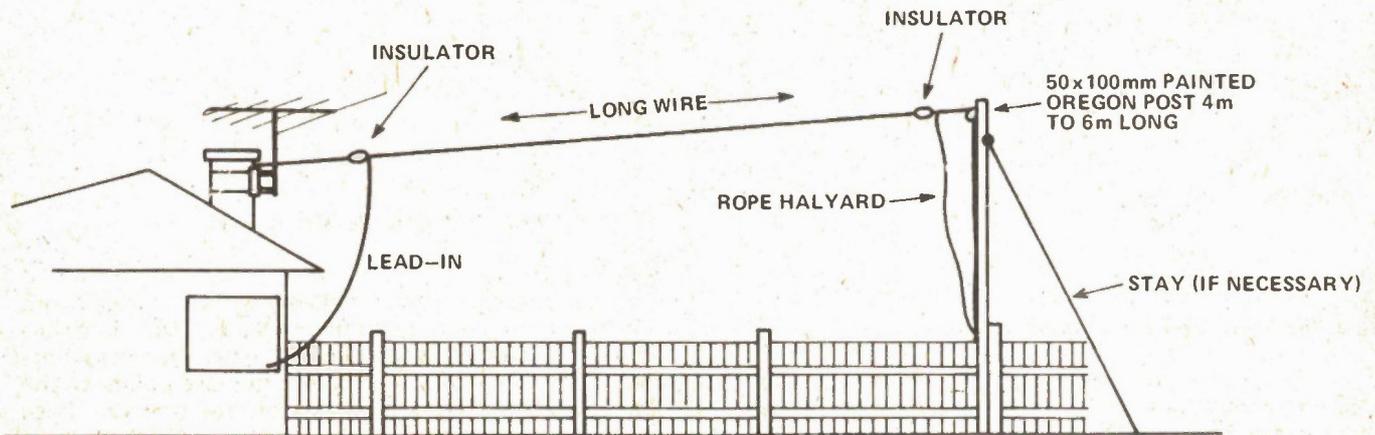


Fig. 1. Cheap and relatively simple — the long wire aerial.

SALES OF GOOD QUALITY 'general coverage' receivers with tuning ranges that cover the HF spectrum from 3 MHz to 30 MHz have boomed in recent years, bringing about an upsurge of interest in shortwave listening.

The price of receivers with good 'slow' tuning rates, dial readout to 5 kHz or better, excellent sensitivity and selectivity as well as good stability has decreased to the point where many enthusiasts can afford a 'communications quality' receiver.

However there remains a problem with aerials to suit such wide frequency coverage.

When Does Long Mean Long?

No discussion or description of wide coverage receiving aerials is complete without mention of the ubiquitous 'long wire'. The time-honoured long wire is simply what it says — any 'random' length of wire that it is possible to erect in a given space. Theoretically it is 'long' when its length is one wavelength or more at the lowest frequency of interest.

No matter, modern receivers are sufficiently sensitive that they only need a whisker of an aerial to pull in plenty of stations at good strength. It's for the weak ones that you need the big aerial.

A typical long wire installation is illustrated in Fig. 1. The actual height and length depend entirely on your circumstances. A piece of 50mm by 100 mm post is painted and bolted to a fence post or other support, as far from your receiver installation as you can reasonably manage. A pulley, obtainable at almost any hardware store, is fixed to the top and a loop of good quality hemp rope threaded through it, before erection.

An egg or strain insulator is attached to one end of the aerial which is also tied. The other end of the aerial is erected near the receiver installation. An insulator is also attached at this end and the lead-in taken down from it to the receiver installation. The aerial is then supported from this end by tying it off to a chimney, as illustrated.

Having one end of the aerial higher than the other is of little consequence. It'll still work!

The lead-in should be taken in such that it clears the house guttering and may be fed through a ventilator opening or over a window sill — whatever is convenient. Avoid running it for any distance clamped to a wall or parallel to metal guttering, pipes, or wiring. The more direct the better.

Once your long wire is up, you're ready to go! The end of the lead-in can simply be attached directly to the aerial terminal of your receiver.

'Vee Have Ways of Tuning In'

A wideband 'inverted-vee' style of aerial is illustrated in Fig. 2. This works extremely well across the range from about 5 MHz up to 30 MHz and uses ordinary TV ribbon for a feedline. However, a balun or an aerial tuner is necessary. A balun is simple but an aerial tuner will give better results.

Good signals will be picked up by this aerial right down to 2 MHz but at these low frequencies there's no substitute for size and different aerials, designed to operate in these regions, usually provide better performance.

Beggars can't be choosers though, in many circumstances!

Construction is quite simple. Again, a 4m or 6m length of 50 × 100 mm post, painted, is erected against a suitable support — shown here as the side of a house. A fence or garage is just as good.

If you can attach a length of aluminum pipe to a chimney mount or to your house gable — well and good. Just get the centre up as high as you reasonably can.

Each leg of the inverted-vee should be six metres long. However, they can be shorter — whatever you can fit, but the performance at low frequencies suffers.

Say It With Ribbon

The TV ribbon is connected where the opposite legs of the aerial join at the apex. Support the ribbon with standard screw-in TV ribbon insulator standoffs.

Each leg should be individually tensioned with the

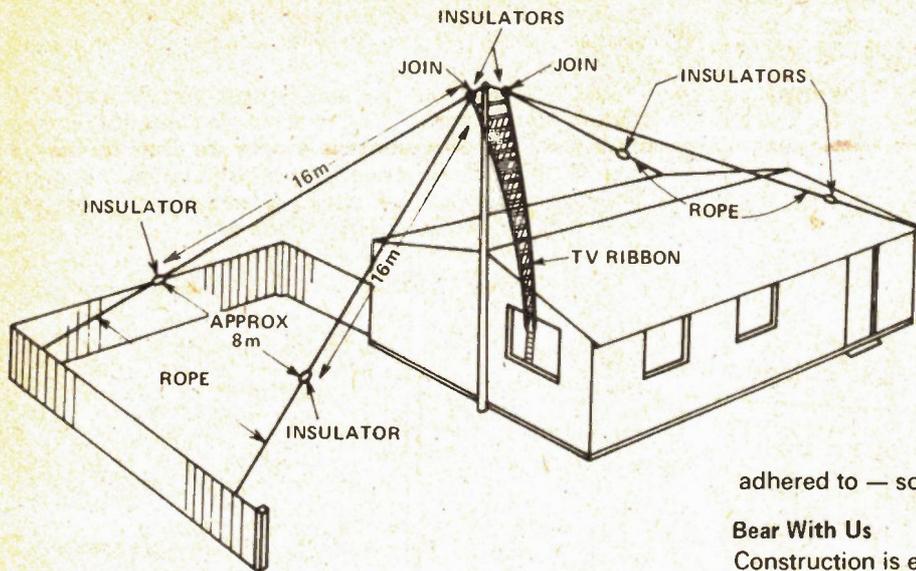


Fig. 2. The 'inverted-vee' aerial (wideband version)

rope strainers indicated in Fig. 2. Large screw-eyes, obtainable from most hardware stores, screwed into the supports, as illustrated, serve as excellent anchor points and allow the rope to be tightened using an appropriate slip knot (a round turn and two half half-hitches is excellent).

Balun and aerial tuner construction, whichever you choose to suit the inverted-vee aerial, will be described in a future article.

Straight Up

The familiar groundplane aerial, much used in commercial VHF two-way communications systems as base-station aerials becomes somewhat cumbersome at the frequencies that interest hams and shortwave listeners, although they are manageable above 14 MHz.

Loaded verticals, short verticals and other forms of the vertical aerial are popular for a variety of reasons, one good one being they have a low impedance, unbalanced feedpoint which suits most receivers on the market today.

If the *actual* ground is utilised as the ground plane for a HF groundplane aerial, a series of vertical elements can be connected in parallel at the feedpoint to provide a wideband vertical aerial system — which can give an excellent account of itself.

Such an aerial is illustrated in Fig. 3

Five elements, of different lengths, are arranged in a fan supported from a rope bearer. They are all brought down to a termination which is supported on the top of a piece of pipe which has been driven into the ground.

The joining of the bottom of all the elements at the terminal provides the feedpoint connection. The centre conductor of the 50 ohm coaxial feedline connects to this point and the outer conductor, or braid, of the coax connects to the earth via the pipe supporting the termination.

Details of the termination are shown in Fig. 4. The use of a coax socket is recommended as it is a simple matter to waterproof a coax connector; however, an alternative method is indicated. Waterproofing of the coax plug and cable will ensure that it has a long useful life. The aerial dimensions indicated in Fig.3 need not be strictly

adhered to — some latitude is possible.

Bear With Us

Construction is easy if you follow this procedure: lay out the bearer rope first. Insert the insulator ties at intervals of two or three metres as indicated. Attach the insulators that go at the top of each element to these points on the bearer ropes using short lengths of rope or wire. These will have to be subsequently adjusted, so don't tie the insulators on permanently yet.

Next, lay out all the elements, using the lengths as a guide and allow at least one metre at the termination end of each wire so that they can be individually tightened from the termination and when the aerial is erected.

Hoist the bearer rope into position and adjust the termination ends of the elements so that they come together with the termination insulator about 300 mm above the ground.

Drive the pipe into the ground below this point. Finish everything off as illustrated in Fig. 4. If using a coax socket for the coax connection, mount it on a small aluminum or galvanised steel plate which is mounted to the pipe via a long bolt passed through the pipe, as illustrated.

If you wish, the coax may be buried. However it is advisable to pass it through some flexible plastic conduit and bury the whole assembly. This will prevent damage to the cable (from enthusiastic or ignorant gardeners, dogs, small brothers etc) as well as reducing moisture seepage.

If you want the ultimate in performance, a series of ground wires can be buried about 200-300 mm below the soil surface radiating out from the pipe for a distance of six to ten metres. They should all be connected together at the centre and bonded to the pipe.

However, keeping the area surrounding the pipe well-watered should satisfy most requirements.

Biconical Monopole

Yes I know it sounds funny — looks funny too (except to the dyed-in-the-wool enthusiast!) but this aerial really performs as is attested by the fact that many professional and military receiving installations throughout the world use them.

The biconical aerial is mentioned in all the classic textbooks — so I won't go into it here. Suffice to say that it will readily cover a 4:1 bandwidth and has a low impedance, unbalanced feed. Low frequency performance is reduced of course but it still works sufficiently well to provide reasonable signals well below the low frequency design limit.

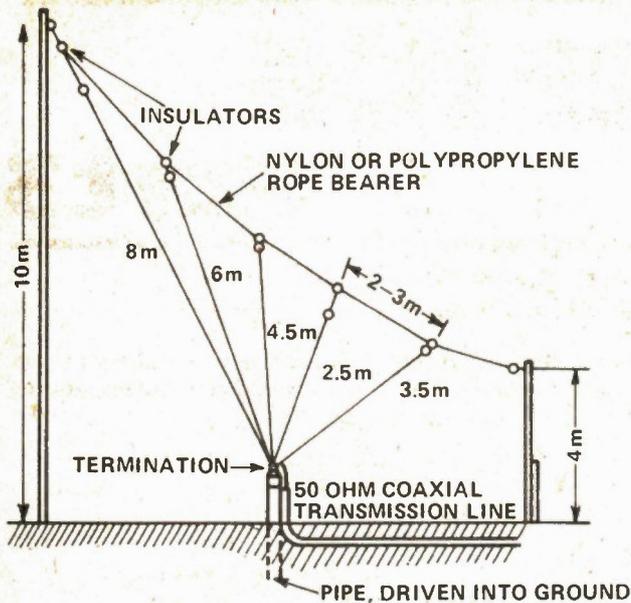


Fig. 3. A broadband version of the HF groundplane aerial. Four Guys And A Pole

A biconical monopole suitable for home-construction (for the enthusiastic!) is illustrated in Fig. 5. A central pole has two cross-arms located low down around which is passed a length of rope. Twelve wires run from the top termination to the bottom termination. All wires being connected together at the termination points. The four wires which pass over the ends of the cross-arms are arranged to act as guys so that the whole assembly is self-supporting.

to support the eight wires not used as the guys. Simply tie them with short lengths of wire to the rope to secure them, after tensioning.

All the wires should be joined together at the top and bottom terminations. The bottom termination is the feedpoint. An arrangement similar to that in Fig. 4 should be used to connect the coax feedline. A good ground stake should be used, or better still a ground radial system, as previously described.

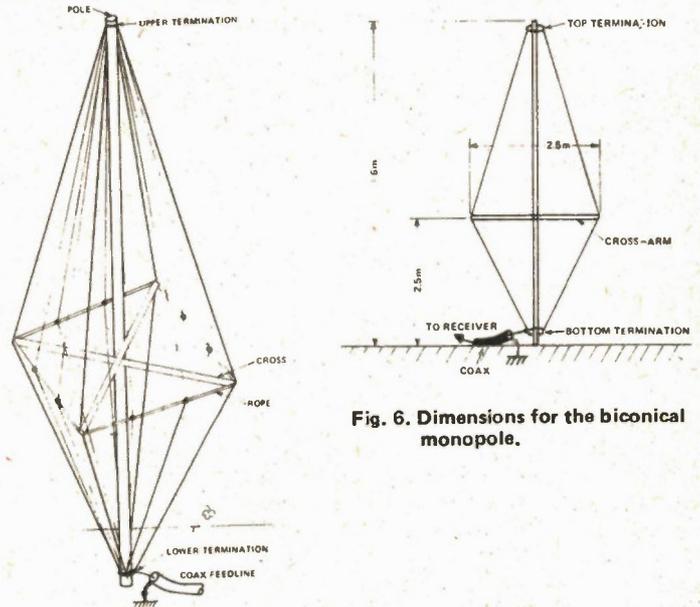


Fig. 6. Dimensions for the biconical monopole.

Fig. 5. A biconical monopole aerial.

Insulator Hints

The aerials described call for the use of insulators at various critical points to insulate the aerial elements from any support or tension rope.

There are two types generally available, the 'egg insulator' and the 'strain' insulator — both illustrated in Fig. 7. Using them is very simple. However, the rope, or aerial wire must be firmly secured where it ties on to the insulator.

Get Knotted

Where heavy, standard wire is used, simply wrapping the wire around itself a number of times is usually sufficient. If flexible hookup wire, is used then it will have to be knotted to be properly secured. Usually a number of half-hitches following several turns through the insulator eye are sufficient.

Nylon and propylene rope, while cheap and water repellent, deteriorate under the ultra-violet light from the sun and weaken considerably with time. Frequent inspection will indicate when replacement is necessary. Both types creep considerably under strain and the tension will have to be adjusted periodically, but this is only a small chore.

Continued on page 74

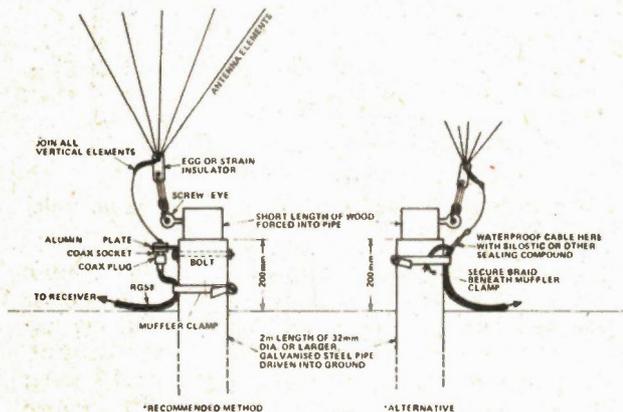


Fig. 4. Two methods of terminating the broadband ground-plane.

The most practical height for the central pole is about six metres, although if you can manage something higher, so much the better. The cross-arms are located about 40% of the pole height above the ground. Each cross-arm is about 40% of the pole height long.

Dimensions are given in Fig. 6 for a biconical monopole that will cover the 7 to 30 MHz range.

Specific construction details are left up to the individual constructor. However, the following points should be noted.

Tying And Tensioning

All the wires should be insulated from the pole and cross-arms. wooden cross-arms are recommended (paint them though). Nylon or polypropylene rope is recommended to go around between the ends of the cross-arms

Into Linear ICs

Part 3

This month, Ian Sinclair looks at the most popular of the linear IC's, the 741 op amp.

THE 741 IS GOING TO BE our introduction to linear ICs. It would be difficult to choose any other chip, because the 741 is probably the most frequently used of all linear ICs. It can come with a variety of letter codings (LM, MC, CA, NE and others), but as long as these letters are followed by the number 741, it's the same chip. It's also found in a variety of packages, but the one we shall use is the DIL 8-pin one, which is the most convenient one for our purposes.

The 741 is classed as an operational amplifier, meaning that it's a direct-coupled amplifier with a very large voltage gain — 100 000 times or more — and the usual two inputs to which signals or feedback can be connected.

The pinout for the 8-pin package is shown in Fig. 3.1. Note that not all of the pins are connected internally, and two of the pins that are connected are seldom used — we'll show later how and when they are used. Like most operational amplifiers, the 741 is intended for dual +ve and -ve power supplies, but the circuit designs can nearly always be adapted for a normal +ve and 0V type of supply as we shall see.

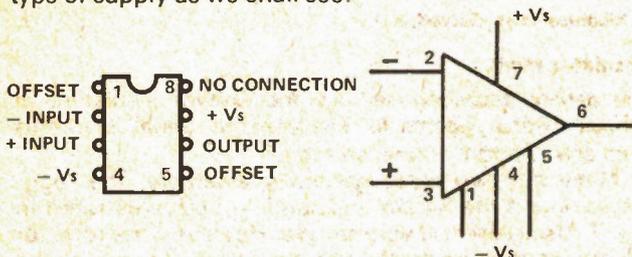


Fig. 3.1 The pin-out diagram of the 741 showing the chip appearance and the circuit symbol.

CIRCUITS AND MORE CIRCUITS

Now for some circuits. Fig. 3.2 shows what is called a voltage follower. The - (minus) input of the 741 is connected directly to the output through a resistor R₁, with no other components in the way, so that there is 100% feedback of bias and signal voltages. The + (plus) input is grounded through another resistor R₂, and is used as the signal input.

What does this do? There's no voltage gain, to start with. The signal voltage out is exactly equal, as far as we can measure, to the signal voltage in, which at first sight doesn't seem too encouraging. There is, however, a huge difference between the input and the output resistances. Remember what that's about? Any electronic device behaves as if it had a resistance at its input and another resistance at its output. When we connect these devices (transistors, ICs or whatever) together, these resistances form potential dividers, reducing the amount of signal which can be passed from one device to the next, as illustrated in Fig. 3.3. An ideal amplifier

would have a very high input resistance and a very low output resistance. This way we could connect any source

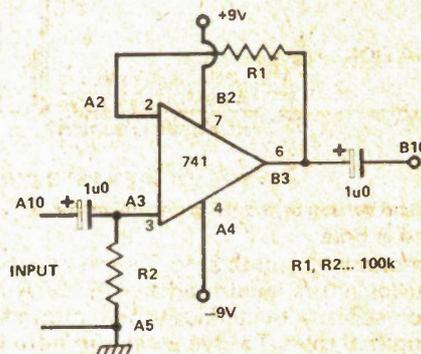


Fig. 3.2 The voltage follower circuit using dual power supplies.

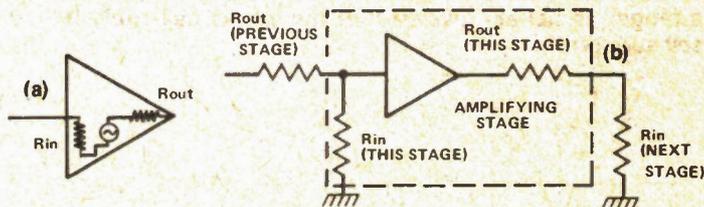


Fig. 3.3 Internal resistances (a) and how they act as potential dividers (b) for the signal.

of signal (tape, disc, microphone, radio . . .) to the input with no loss of signal, and in the same way have no loss of signal at the output even if we connected a very low resistance (such as a loudspeaker) to the output. Sometimes we prefer a lower input resistance for other reasons, but these are the rules for ensuring the greatest possible transfer of signal from one stage to the next.

The circuit of Fig. 3.2 certainly has the correct resistance values, very high at the input and very low at the output, so that the lack of gain isn't always a disadvantage. We can, for example, connect a very high resistance crystal pickup to the input and a low-resistance magnetic earpiece to the output and get a detectable signal at the output. If we connected the pickup directly to the earpiece, we don't hear a thing. This isn't because of a low signal from the pickup — crystal pickups can produce a volt or more of signal — but because of mis-match. The very high resistance of the crystal pickup is connected to the very low resistance of the magnetic earpiece, and the signal is simply divided out of existence! The 741 circuit of Fig. 3.2 is called a voltage follower, and it's a useful headphone amplifier. You can connect its input almost anywhere in an amplifier circuit without affecting the signal voltage

(why? Because of the high resistance) and that's not something you can risk with headphones. If you're going to use the voltage follower in this way, though, it's advisable to use a 0μ 1 coupling capacitor at the input so that the 741 is not affected by any bias voltage at the place where it's connected. In addition, stick to battery-operated equipment until you have a lot of experience in servicing — you don't get a second chance where there are line voltages around.

BIASED TOWARDS COMPONENTS

Fig. 3.4 shows another version of this circuit, re-drawn this time so that a single supply of 18 V can be used. You can see that this needs more components because the bias on the + input has to be set at a voltage midway between the positive and the zero supply lines. In this circuit, equal value resistors R3 and R4 set the midway voltage to which the + input is returned. The - input is biased by feedback as before, but the input and output have to be capacitor coupled because of the bias voltages.

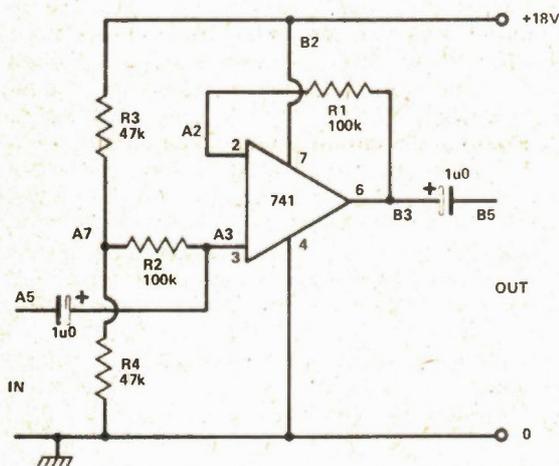


Fig. 3.4 The single-supply version of the circuit of Fig. 3.2.

A simple way to demonstrate the high input resistance goes like this. Connect an LED and a 2K2 resistor in series to the board as shown in Fig. 3.5: note the two possible connections according to whether you've built the dual or the single power supply version. Now, with no signal of any sort into the 741, the LED should not light, because the output voltage of the 741 is the same as the voltage at the cathode of the LED. Now touch the input of the 741 circuit with one finger and the +9V supply with another finger — what happens? Could the resistance between your fingers possible supply the LED directly (Fig. 3.6)? This 741 circuit is the basis for countless circuits which detect small voltages; circuits such as moisture detectors, "lie" detectors, continuity testers and so on.

We needn't, of course, use 100% feedback for our voltage amplifier. Fig. 3.7 shows a circuit which feeds back only a fraction of the output signal. Using a dual voltage supply, this is easily arranged by connecting a potential divider from the output to ground and taking the - input to the output of the potential divider. This kind of circuit is called a follower-with-gain. It has the same high input resistance as the simple voltage follower, but a voltage gain which is greater than one. The value of voltage gain is given by the ratio:

$$\frac{R1 + R2}{R2}$$

$$\frac{47 + 15}{15}$$

so that if, for example, $R1 = 47K$ and $R2 = 15K$, then the gain is

which is 4.13, as near 4 as makes no difference. The single voltage version of this circuit isn't nearly so simple. The resistor R2 can't be connected directly to ground without disturbing the bias on the + input, so that an isolating capacitor is needed. The usual pair of resistors to set half-supply-voltage, and the coupling capacitors to avoid shorting out the bias will also be needed.

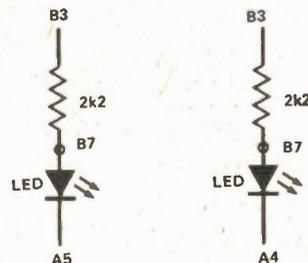


Fig. 3.5 Using an LED voltage detector (a) for the circuit of Fig. 3.2, (b) for the circuit of Fig. 3.4 R2 should be 1M in this circuit when the LED is being used as a detector.

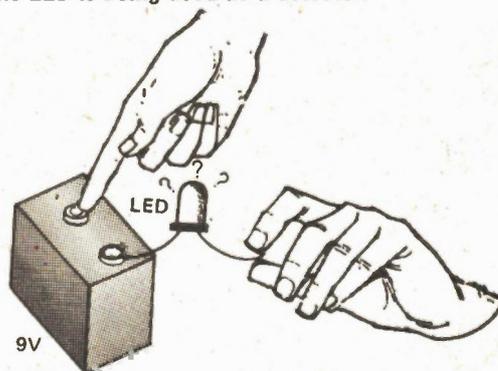


Fig. 3.6 Can enough current pass through your fingers to light an LED?

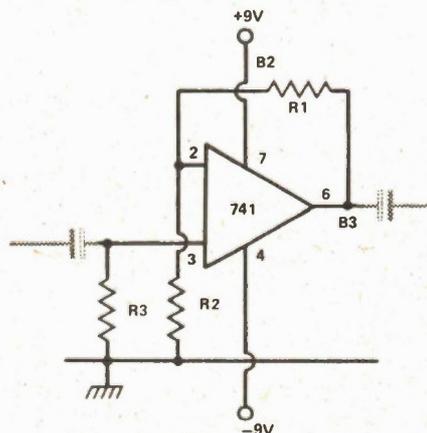


Fig. 3.7 The follower-with-gain. The (dotted) capacitors will be needed if the circuit is to be connected to any points which are not at ground voltage.

GAIN

The gain which this circuit can have makes it much more useful. It can, for example, be used to amplify the signal at a detector diode to form a modern version of the old-fashioned crystal set, as shown in Fig. 3.9. It's also an excellent pre-amplifier circuit, giving a moderate gain along with high input resistance and low output resistance. The output will drive magnetic earpieces quite happily, though the low-resistance earphones which are

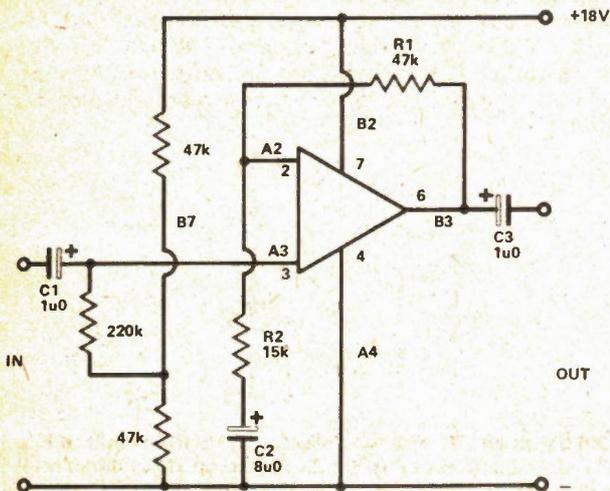


Fig. 3.8 Single-supply version of the follower-with-gain. C2 is needed to prevent the voltage at A from being reduced by the potential divider circuit, R1, R2.

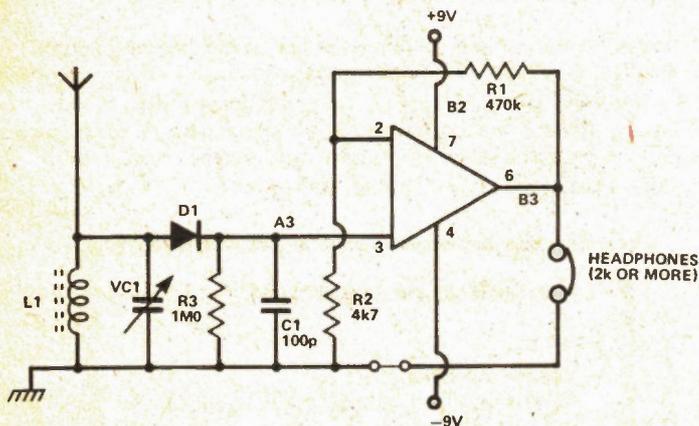


Fig. 3.9 A simple radio circuit, using the high gain of the 741 to amplify the feeble signals from the diode detector. D1 must be a germanium diode such as 1N36.

used along with stereo receivers usually need a bit of resistance connected in series if they are not to overload the 741. For the same reason, low resistance loudspeakers (4R to 15R) should not be used, though the old "transistor radio" 80R loudspeakers will work quite nicely.

Now for the next trick. This time, instead of using the + input for signals, we'll use the - input. Yes, I know that we take the feedback to this input as well, but we can get around that, as we'll see. The circuit of an inverting amplifier, as this type is called, which uses dual power supplies is shown in Fig. 3.10. As usual, the use of two separate supplies makes the circuitry simple, with the + input connected through a resistor to ground.

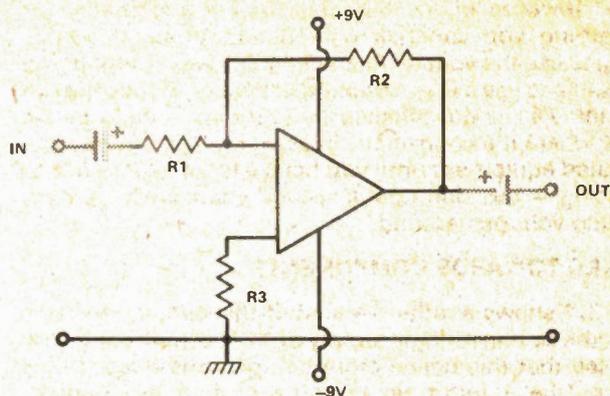


Fig. 3.10 The basic inverter-amplifier circuit. The value of R3 should be chosen so as to equal R1. Capacitors, shown dotted, should be used if the input or output is connected to points which are not at ground voltage.

This circuit is different in a number of ways. For one thing, we find that if we connect our signal directly to the - input, the input resistance is as near as we can measure, zero! It's so near zero in fact that the - input is often called a virtual ground - there's zero resistance to ground for signals at this point. We can add some resistance, however, in the shape of R1, and when we do the voltage gain of the circuit is easy to calculate - it's just $R2/R1$. The output resistance is low, the input resistance is R1, and the output signals are inverted compared to the input signals.

How can we try this one out? One way is to use it with a signal source which has a low resistance. We can, for example, use a small loudspeaker as a microphone. Fig. 3.11 shows a suitable circuit, with a magnetic earpiece used at the output, which can be used as a remote listening device - not everyone knows that a loudspeaker can double as a microphone.

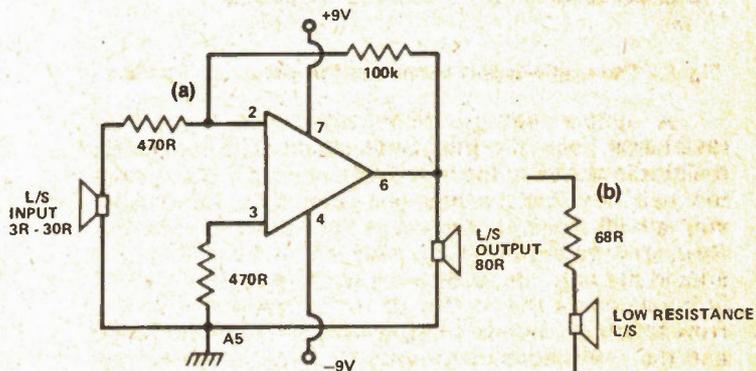


Fig. 3.11 An eavesdropper circuit. (a) The loudspeaker at the input can be of high or low resistance, but the loudspeaker at the output can be a high resistance type. (b) shows how a lower resistance loudspeaker can be used at the output.

As usual, the circuit is a bit more complicated when a single power supply is used, and coupling capacitors have to be connected to prevent the bias from being shorted out. Fig. 3.12 shows the single-supply version of the circuit of Fig. 3.11.

FOR OUR NEXT TRICK . . .

These circuits are basic circuits - they illustrate with only a few components what a 741 can do. By adding more components we can end up with a lot of useful

project ideas, and that's the next step. One such circuit is illustrated in Fig. 3.13. This one is an overload compressing amplifier; a boon if you use a microphone live or for tape recording. All microphones give a much greater output when you're close to them than when you're a few feet away, so if you set the gain of an amplifier to be just right when you're three feet from the mike, it's horribly overloaded and distorted when you come closer. The compressor circuit has a variable gain which corrects this situation — when the signals are small, the circuit has a large gain; when the signals are large the gain drops. It's like having a very smart operator at the volume control, but with the additional advantage of being automatic.

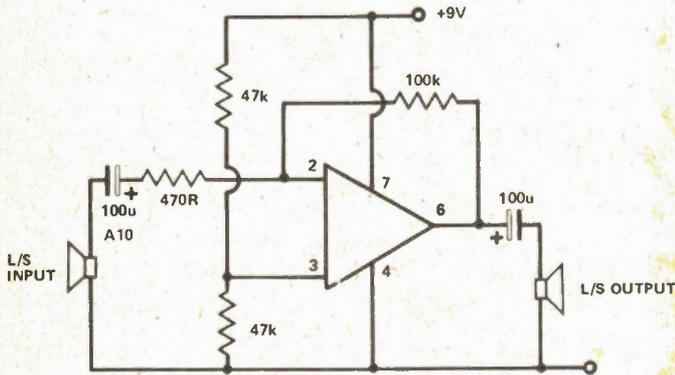


Fig. 3.12 A single-voltage supply version of the circuit of Fig. 3.11.

How does it work? The circuit (Fig. 3.13) is basically an inverting amplifier but the feedback is through a pair of diodes, D1 and D2. Now, as you'll recall, diodes conduct one way only, so that to ensure that both halves of a signal voltage will be fed back, we have to use two diodes connected back-to-back. Even when the anode of a diode is positive to the cathode, however, a diode does not conduct until there's enough voltage across it, about 0.15 V for a germanium diode, and 0.5 V for a silicon diode. Once the diode starts to conduct, what's more, it doesn't obey Ohm's law, or anything like it. There's no fixed single value of resistance for a diode, the value of resistance changes as the current through the diodes changes, becoming smaller when there's a lot of current through the diodes, and large when the diodes are almost cut off.

COMPRESSION

How does this achieve compression? Well, if the input signal is very small, the amplified signal at the output may be too small to make the diodes conduct, in which case there's no feedback and the circuit operates at full gain. When a larger input signal happens along, the diodes start to conduct, and their resistances act as a negative feedback resistor, reducing the gain of the amplifier. Still larger input signals make the diode resistance lower, causing more feedback and less gain. In the circuit which is shown, the gain for a 1 mV signal is about 20 times (output 20 mV), but the gain for a 1 V signal is about 0.6 times (output 500mV). One thousand times the original input signal has caused only 25 times the output signal— that's compression!

If you want to use this in a microphone circuit, you'll have to experiment with the best place to connect the compressor — either between the mike and the pre-amp,


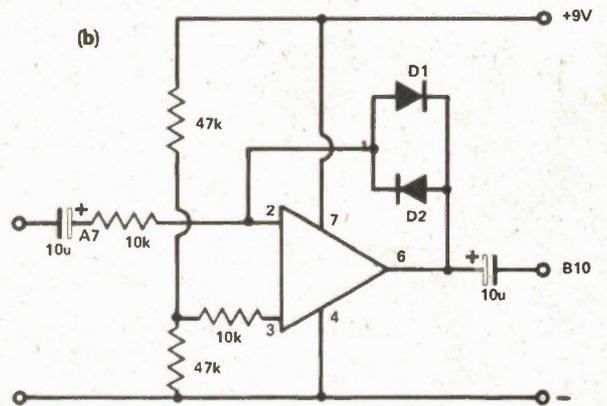


Fig. 3.13 The diode compressor circuit (a) dual voltage supply version, (b) single voltage supply version.

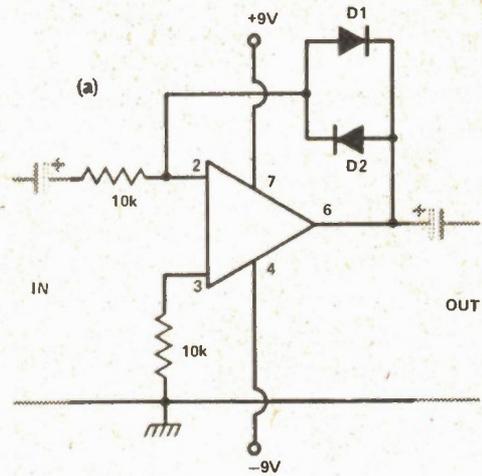or between the first stage of the pre-amp and the second. Remember to use coupling capacitors if you're connecting to anywhere which has a bias voltage, and don't take risks with line-operated equipment.



To All ETI Readers. . .

Listen up here.

When sending letters to ETI to inquire about articles or projects, it is extremely important that these letters be accompanied by self stamped and addressed envelopes. The importance of this is in that we won't answer them if they're not. Having to dig up and address envelopes for a whole raft of letters takes a fair bit of time, and slows down replies for everyone. This is most unfair for readers who *do* enclose envelopes.

Please help us help you and keep our trash baskets empty.

(If this wasn't getting to a problem, we could have had a cartoon in this space.)



150W MOSFET POWER AMP

- 1% Matched Pair HITACHI MOSFET.
- 1% Metal Film Resistors.
- High Quality WIMA Capacitors.
- Gold Plated P.C. Board.
- THD at 150W into 8 Ohm Less Than 0.0015% at 1Khz.
- Freq. Response from 1Hz - 100Khz.
- Operates on \pm 45 to 55 V D.C.

Kit \$119.50 each \$199.50/2

HITACHI MOSFET 2SK134, 2SJ49
\$14.95 each - 2 or more \$12.95 each

Send cheque, money order plus 5% for postage and handling. (no charge for orders over \$100.00). Ontario residents add 7% P.S.T. Visa and Master Card accepted: Send card No., expiry date and signature to:

AUDIOVISION
578 Marlee Ave.
(Just one block West of Glencairn Subway)
Toronto, Ont. M6B 3J5
Tel: (416) 781-3263

SHARP POCKET COMPUTER — PC 1211
— Programs in BASIC
— 24 character alphanumeric display
— 1424 steps, 26 memories
— Reservable and definable keys
— Optional cassette interface to store programs or data
— 1 year warranty, extensiv documentation (3 manuals)
Only..... \$269.00



CE-122 PRINTER & CASSETTE INTERFACE

For Above model only \$179.95

Memorex 5 1/4" Diskettes	10 for \$49.00
C-10 Cassette tapes	\$1.00 ea.
C-20 Cassette tapes	\$1.25 ea.
Cassette boxes	4 for \$1.00
Disk Storage Box holds 50-60 disks	\$39.95

BOOKS

PET Personal Computer Guide	\$18.95
Apple II User's Guide	\$18.75
PET Basic	\$16.90
All about Telephones	\$7.95

DYNA CHARGER

For charging NIC/CAD Batteries \$19.95
Recharges up to four batteries at a time

We also carry Commodore & Atari computers, video recorders, telephones, calculators, plus many other innovative products. Write for our **FREE CATALOGUE** or come in and see us.

Send Money Order, Charge, Master Charge. Include expiry date, card number, bank name and signature. Add 5% for shipping (excess refunded). Ontario residents add 7% sales tax. All prices subject to change.

ELECTRONICS 2001

5529 Yonge St. (just south of Finch)
Willowdale, Ontario M2N 5S3
(416) 223-8400

COMPUTERS • VIDEO • MICRO ELECTRONICS

Circle No. 21 on Reader Service Card.

WHEN YOU NEED...

HAND HELD DESOLDERING TOOLS

AS196



SILVERSTAT SOLDERPULLT

Special purpose SOLDERPULLT for low static work stations. Deluxe features. Static conductive construction reduces sensitive component damage.

US340

MICRO TIPPED



UNIVERSAL SOLDERPULLT

Compact manual loading tool. Easy one hand operation. Adjustable three position loading stroke. Low mass plunger, rapid vacuum impulse, negligible recoil.

- Low Static Potential
- Designed for MOS-LSI semi-conductor devices.
- Equipped with 1/8" I.D. no-stick Teflon Tip.
- Self cleaning shaft cleans every time unit is loaded.

You Need EDSYN INC.

For information on this, and other Edsyn items, complete this coupon and mail to:

Name _____

Address _____

City _____ Prov. _____

Postal Code _____

len finkler limited
80 Alexdon Road, Downsview, Ontario M3J 2B4




Circle No. 15 on Reader Service Card.

CORRECTION

GLADSTONE ELECTRONICS
January 1982 issue, page 30.

Price of 8K ROM/2K RAM Black & White ATOM was listed as \$479.95 — should have been \$399.00.

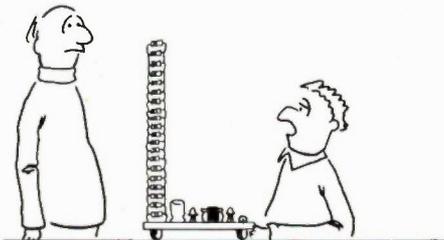We apologise for any inconvenience caused.



I didn't have a 1 ohm resistor, but I had twenty 20 ohm resistors...

SPECIAL IC SOCKET SOLDER TAIL

8 pin	.09
14 pin	.12
16 pin	.14
18 pin	.20
20 pin	.24
22 pin	.25
24 pin	.29
28 pin	.34
40 pin	.51

OK MACHINE & TOOL

Battery Wrap BW-2630
Regular \$27.95 — Special \$23.95

AP PRODUCTS

Ace 200K Solderless Board
Regular \$29.95 Special \$24.95

HOBBY BLOX

Starter Pack IC
Regular \$8.95 Special \$7.50

DISCRETE COMPONENTS

Regular \$9.25 Special \$7.25

OFFER GOOD UNTIL MAR 15/82

ASK FOR YOUR FREE CATALOG. PHONE ORDERS: (418) 839-8367 Send you cheque, M.O., VISA or C.O.D., NO Shipping charge. Minimum order: \$5.00 Quebec residents add 8% P.S.T.

SELCO ELECTRONIQUE


CASE POSTALE 2036
ST-ROUJALD
QUEBEC, G6W-5M3

Circle No. 8 on Reader Service Card.

Fail-Safe


The insulators illustrated are available in porcelain, nylon and glass. The nylon type egg insulator is usually the least expensive — but they do have one drawback. After some time in use, the tension of the wire causes the nylon to creep or remould itself and the wire literally pulls itself through the insulator. This may cause the insulator to fail completely. It isn't so much of a disaster however as the aerial wire and support rope are looped through one another and the aerial won't fall down — an replacement will obviate any problems here.

Good luck and good listening!

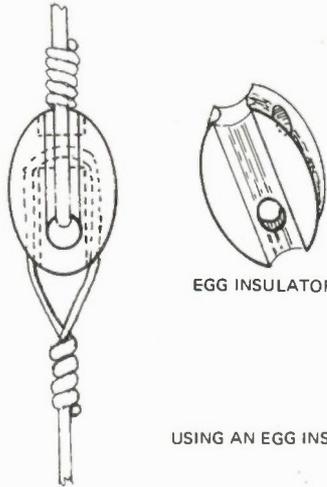

EGG INSULATOR

USING AN EGG INSULATOR

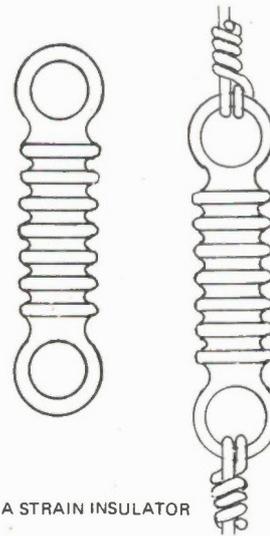

USING A STRAIN INSULATOR

Fig. 7. Two types of aerial insulator and how to attach them.



About these Editorial Inquiries. . .

If you wish to write us to ask a question about one of our projects or features, your letter *must* be accompanied by a self stamped and addressed envelope or we will not be able to answer it.

Please, help us to help you. . .

HAMEG
OSCILLOSCOPE HM 203


The new HM203 is a 20MHz bandwidth general-purpose Dual Trace Oscilloscope. The **stable sweep triggering** (to 30MHz) and the relatively **high measuring accuracy** ($\pm 3\%$) are particularly impressive. The useful display area is approximately 8 x 10cm. With the aid of the **electronic stabilization** of all operating voltages and the thermally favorable arrangement of the drift-sensitive components, an **outstanding display stability** is obtained. The brightness and display definition of the cathode-ray tube are excellent.

For further information on scopes or probes call or write:



We service all makes of Oscilloscopes:
TEKTRONIX • HEWLETT-PACKARD •
GOULD • ETC.
From coast to coast. Call us next time.

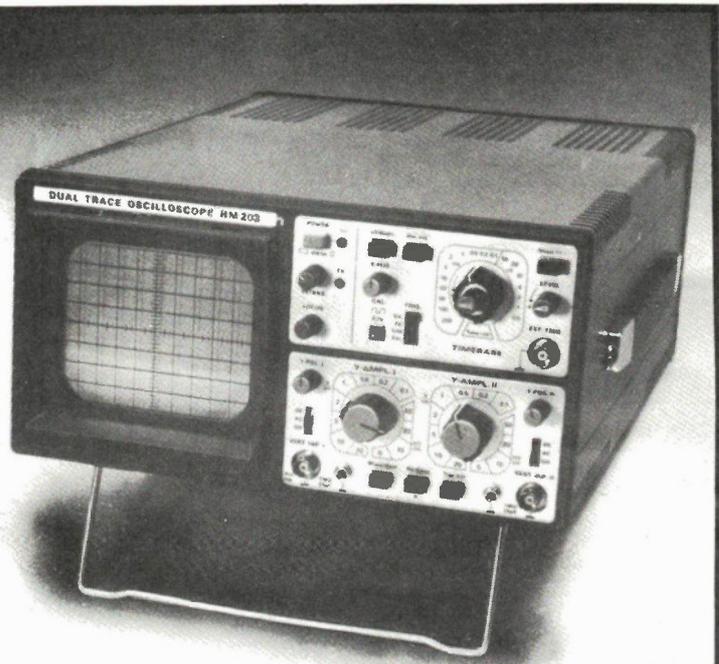980 Alness St., Unit 35, Downsview,
Ontario (416) 661-5585 M3J 2S2



LIST
\$760


- Bandwidth DC-20MHz
- Dual Trace Oscilloscope
- 8 cm x 10 cm Display
- Triggering up to 30MHz

the circuitry and battery pack make a fairly tight fit in the case.


The unit is very easy to use. Simply connect the output to an audio power amplifier/speaker combination, adjust RV2 (null) for zero output tone, then connect a voice or music input signal and see how the sound can be 'bent' using the frequency and mix controls. Level control RV1 is simply adjusted to give

good sensitivity without amplitude limiting (clipping).

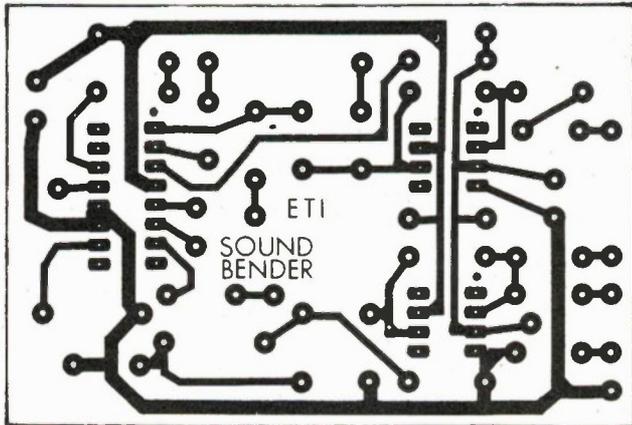To use the unit as a simple audio generator, turn the input level control down and set the mix control (RV4) to give a 'modulation only' output, then adjust null control RV2 to give the desired output signal amplitude. RV3 then acts as the frequency control and SW1 gives selection of either sine or triangle output waveforms.



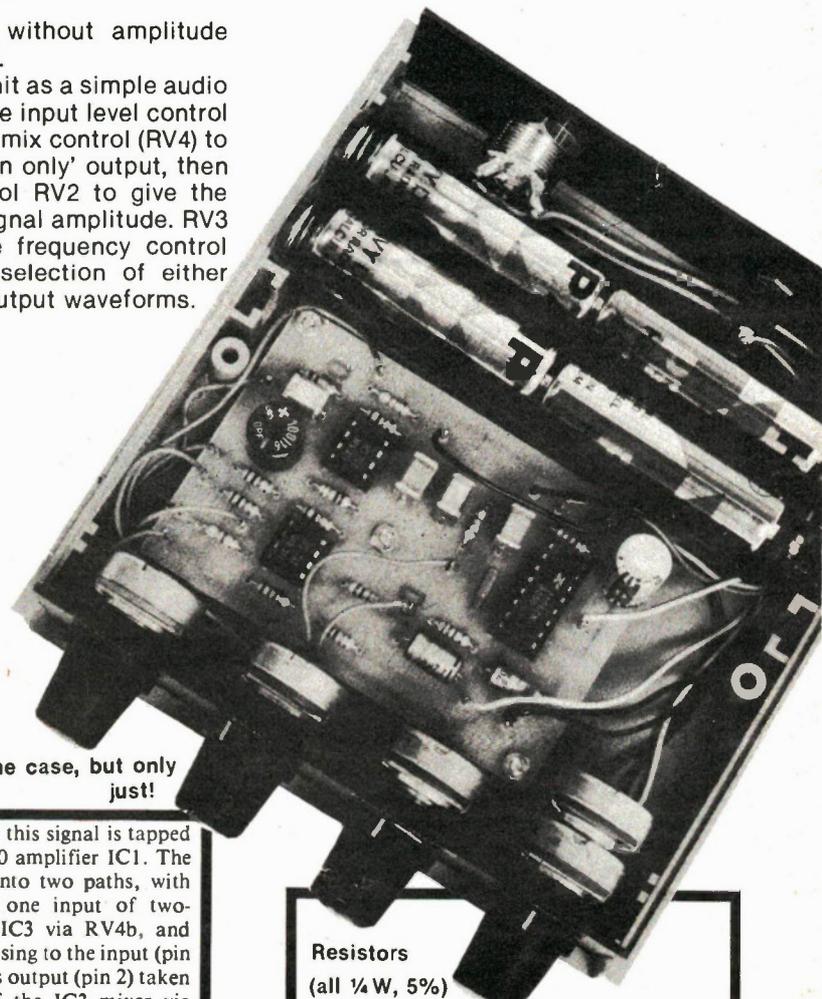Everything does fit in the case, but only just!



HOW IT WORKS


The heart of this unit is IC2, an XR2206 function generator chip that incorporates a wide-range sine/triangle waveform generator and a precision four-quadrant multiplier within a single package. The output of the waveform generator is internally connected to one input of the multiplier, and the other input of the multiplier is accessible at pin 1: the output is available at pin 2.

In our application, the generator can produce either sine or symmetrical-triangle waveforms, depending on the setting of SW1, and its frequency (determined by C4-R7-RV3) can be varied over the range 3 Hz to 5 kHz via RV3. The pin 1 input of the multiplier is biased by RV2, which is normally adjusted to balance the multiplier so that it produces zero output when zero signal input is applied to pin 1.

The audio input signal is applied across

RV1 and a fraction of this signal is tapped off and applied to X10 amplifier IC1. The output of IC1 splits into two paths, with one path passing to one input of two-channel audio mixer IC3 via RV4b, and with the other path passing to the input (pin 1) of IC2, which has its output (pin 2) taken to the other input of the IC3 mixer via RV4a. Note that mix controls RV4a and RV4b are connected in opposite directions so that they control the mixing action in 'pan pot' fashion, giving a final output from IC3 that ranges from 'all original signal' to 'all modulated signal' in the extreme settings of RV4. The output amplitude of IC3 is divided by 10 (by R12-R13), so that the final output signal has an amplitude roughly equal to that of the input signal feeding IC1, thereby giving the Sound Bender a good overall signal-to-noise ratio.

Fig. 2 Component overlay.

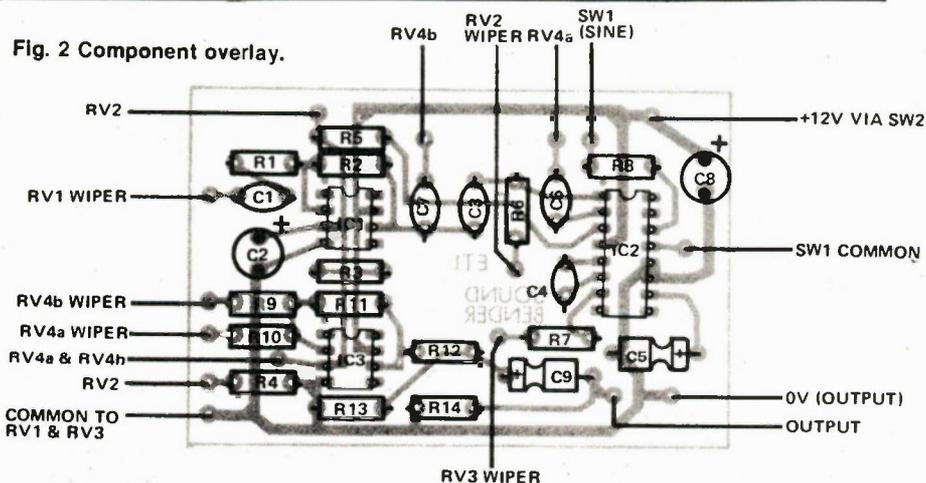

Resistors
(all 1/4 W, 5%)

- R1 100k
- R2,9,10,11 1M
- R3,12,14 10k
- R4 4k7
- R5,6 47k
- R7 2k2
- R8 220R

Potentiometers

- RV1 10k linear
- RV2 4k7 linear
- RV3 2M2 linear
- RV4 100k dual linear

Capacitors

- C1 220n polycarbonate
- C2 100u 16V PCB electrolytic
- C3,6,7 470n polycarbonate
- C4 100n ceramic
- C5 10u 25V axial electrolytic
- C8 470u 16V PCB electrolytic
- C9 4u7 16V axial electrolytic

Semiconductors

- IC1,3 741
- IC2 XR2206

Miscellaneous

- SW1,2 SPDT miniature toggle
- SK1,2 phono sockets
- PCB battery holders (two off).

PARTS LIST

ATOMic POWER

Continued from page 31

to learn on, the VIC is a lot more "user friendly". On the other hand, it's a lot more limiting once you get going, too. If you're planning to get into more sophisticated computer applications, like word processing, record management, freaky graphics, and so on, the ATOM will take you further. Suitably ambiguous, I hope.

At the time of this writing, the basic black-and-white ATOM was going for \$525.00 Canadian. In addition to this, you'll need a TV, a power supply and a cassette recorder. And coffee. Lot's of coffee. It's really hard to get to sleep when you've got one of these things to play with.

(As in the case of the VIC, we were so impressed with the ATOM we had for review that we ended up buying our review sample. It has occurred to us, however, that we have gotten ourselves into a bit of a box in doing this, as, in future, if we review a computer and don't decide to buy it, it will seem that we're not too impressed with it. In fact, it may very well be the case that we simply don't need another machine with these particular capabilities (it really is starting to look like a computer store around here). As such, while we may purchase review samples in the future, this is the last time we plan to mention it.)

EXPANSION AND SOFTWARE

The optional extras available for the ATOM are very extensive: this is probably because Acorn as a company have a history in industrial control. We did not see or try any of these so we can't comment on them. However if this is an important consideration, we suggest you contact Torch.

Some options that will be of interest immediately are colour, serial printer interface and I/O ports.

There is also a 32K memory expansion board which fits inside the ATOM's case. We did not look at all the software but there are some very interesting business and word processing packages.


BRIEF SPECIFICATIONS

- 12K RAM
- 12K ROM
- High Resolution Graphics (256x192)
- Built-in Speaker
- Built-in Modulator

Last month we incorrectly said that Torch were the manufacturers of the ATOM, in fact they are the Canadian Distributors.

ETI

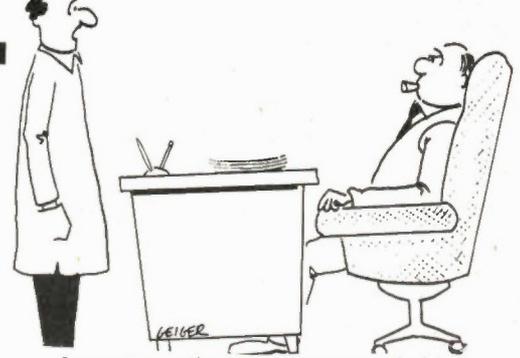If you liked this article, please circle Reader Service Card number 53. If you didn't, circle number 54.



Several months ago, we succeeded in building a full-blown computer on a chip the size of a pinhead. We've spent the last few months looking for it.

Aaron-Gavin


Equalizers • LED Meters • Mixers **KITS**

\$\$\$\$ DUTY FREE \$\$\$\$ INTRODUCTION OFFER

That's right! — We pick up the bill for both DUTY and FEDERAL TAX.

We are making this fantastic offer to determine the potential of doing business directly in CANADA. So... take us up on this limited offer. A copy of this ad must be with your order.

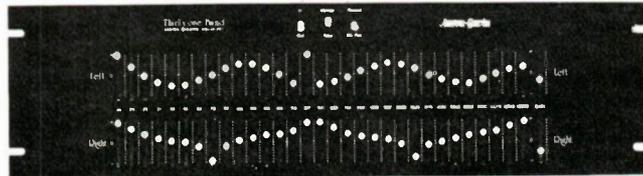Featuring this month — 31 Band Stereo EQ (1/3-octave)



FEATURES: Linear Circuit, Follower Filter Circuit, Regulated Power, +15dB Boost and Cut on EVERY BAND, 13V usec Slew Rate.

BENEFITS: Distortion/Noise: -80dB, NO Snap-On, NO Rainbow Effect, NO Band to Band Phase Cancellation. Truly built to PROFESSIONAL STANDARDS — by you or us.

STYLE: Rack or Cabinet FREQ. 16-16KHz or 20-20KHz Black or Silver Finish

GRAPHIC EQUALIZERS

Mfg.	Kit	Model
\$690.	\$328.	31 BAND Stereo EQ
230.	119.	11 BAND Stereo EQ
\$490.	\$235.	21 BAND Stereo EQ
280.	149.	11 BAND Stereo EQ

W/MIC, MIXER, LED PEAK INDICATORS, DUAL MASTER GAIN CONTROL AND MORE.

LED METERS

Mfg.	Kit	Model
\$229.	\$ 84.	20/40S:
40 LED Stereo Meter W/3 color range display, rectangle leds, -71dB to +26dB W/only 3dB separation.		
\$149.	\$ 69.	20/40R:
40 LED Stereo Meter W/1 color range display, Round Leds, -71 to +26dB W/only 3dB Separation.		

SINGLE CHANNEL MONO VERSIONS AVAILABLE IN ALL OF THE ABOVE, (20% less).

Order with this ad or send for full product information and specifications to: AARON-GAVIN, 123 South McClay Street, Unit F, Santa Ana, California 92701, phone 714/957-8710.

In addition to kits and finished goods, we also manufacture Rack Mount Front Panels and Rear Covers, Wood Cabinet Panels and rear covers, Printed Circuit Boards, Potentiometers (sliders), transformers, Mylar Capacitors (1% to 10% tolerance). We also distribute RAM, ROM, EPROM, LS and TTL components.

NEW KIT PRODUCTS AVAILABLE SOON! 40 LED per Band SPECTRUM ANALYZER with 1 1/2dB Separation from -77 to +26dB. POWER AMPS. 80 to 800 Watts Stereo. Modular Studio MIXER, in multiples of 2 to whatever number of channels desired.

NOTE: No company in this magazine can beat our prices on components even WITH Duty and Federal Taxes.

WANTED! — FACTORY REPRESENTATIVE AND DISTRIBUTORS

THE

MODE
ELECTRONICS

Skeet Shoot!

ELECTRONIC GAME KIT



challenges alertness

Your friends will enjoy testing their alertness and reaction time. You can take pleasure in combining capacitors, resistors and integrated circuits so that a "bird" is seen to move across the sportsman's path in a series of lights. If the weapon is "fired" at the right moment to "lead the target" across the LED, a hit is recorded for all to see on a seven-segment display.

It seems easy, but this kit produces the most unpredictable random speeds of movement across the sequence of lights—as random as any succession of real birds flushed by hunting dogs... or the most elaborate machines propelling clay pigeons. A real challenge to alertness and the ability to judge speed!

Mode's inexpensive kits demonstrate many of the capacities of electronic components, while resulting in useful or entertaining products. Get a Mode Skeet Shoot Kit at your Mode Dealer, and pick up a few of these other fine Mode Kits:

Mode kits for many useful and entertaining purposes.

- | | |
|---------------------------------------|-----------------------------------|
| 1. Automatic Headlight Reminder | 19. Tone Generator |
| 2. Battery Operated Fluorescent Light | 20. 5 Transistor 1 Watt Amplifier |
| 3. Bug Shoo | 22. Xenon Strobe |
| 4. Code Oscillator | 23. 3 Channel Color Organ |
| 5. Crystal Radio | 24. Loudmouth Siren |
| 7. Curiosity Box II | 25. Roulette Wheel |
| 8. Dally Lighter | 26. Electronic Sheet Game |
| 9. Decision Maker | 27. Electronic Dice |
| 10. Fish Caller | 28. Super Roulette |
| 11. Hi Power 12V DC Flasher | 29. FM Mini Broadcaster |
| 12. Photo Electric Night Light | 31. Electronic Shoot Out |
| 15. 0-20V Power Supply | 32. Road Runner Sound Effects |
| 16. Single Channel Color Organ | 33. Love-O-Meter |
| 17. Electronic Siren | 34. Soldering Iron Kit |
| 18. Shimmer Strobe Light | 35. Audio Power Watt Meter |
| | 36. Steady Hand Game |
| | 37. Decision Maker D.C. |











MODE
ELECTRONICS

HEAD OFFICE

1777 ELLICE AVE. WINNIPEG, MANITOBA
R3H 0W5 PH: (204) 786-3133

BRANCH LOCATION

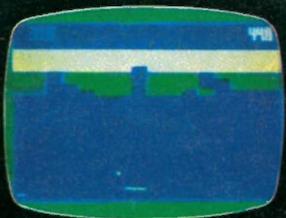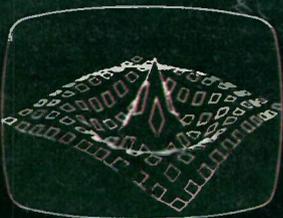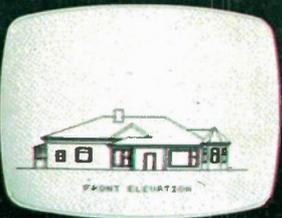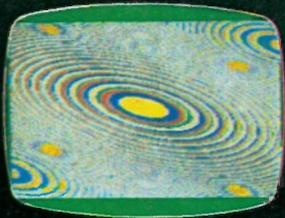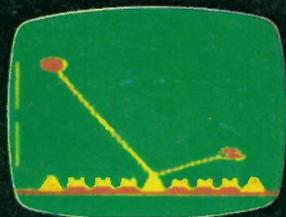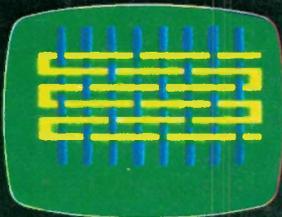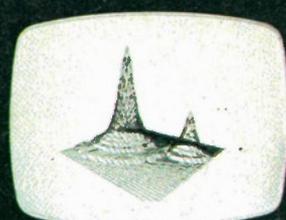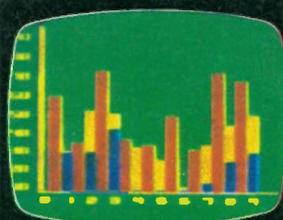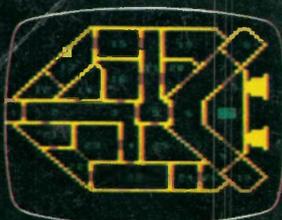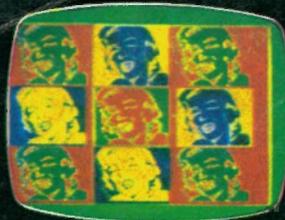88 HORNER AVE. TORONTO, ONTARIO
M8Z 5Y3 PH: (416) 252-4838



CHOOSE ATOM POWER

At work or play - everything you need in a personal computer

The Atom is a machine to be used. Every day, day after day. It's a full function machine - check the specification against others. It's rugged, easy to operate built to last and features a full-size typewriter keyboard.

Just look at some of the features!


- More hardware support than any other microcomputer
- Superfast BASIC includes symbolic Macro Assembler
- High resolution and comprehensive graphics ideal for games programmers and players
- Designed in Britain
- Software available for games, education, math, graphs, business, word processing, etc.
- Other languages: Pascal, FORTH, LISP
- I/O port for control of external devices
- Built-in loudspeaker
- Cassette interface
- Full service/repair facility
- Users club

Optional Extras

- Network facility with Econet
- Disk
- Printer connection
- Add-in cards include 32K memory, analogue to digital, viewdata VDU, disk controller, daisywheel printer, plus many, many more!
- Power supply

FREE MANUAL

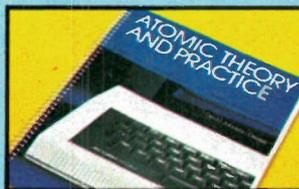The Atom's highly acclaimed manual comes free with every Atom and leaves nothing out. In just a while you'll be completely at ease with your new machine! Within hours you'll be writing your own programs.



ATOM SOFTWARE is designed and produced by Acomsoft, a division of Acorn Computers, Trust the manufacturer to get the very best from its own product. Current software includes word processing, maths packs over 30 games, database, Forth and business packages.



Dealer Enquiries Welcome

ATOM 12k RAM, 12k ROM

\$525.00

(Black and White)

\$599.00

(Colour)



Order direct from the Canadian Distributors

Mail Order to:

Torch International Computers (Canada) Ltd., Suite 212, 7240 Woodbine Avenue, Markham, Ontario, L3R 1A4.

Or Call (416) 490-8622

Name

Address

Total amt. encl. () Cheque () Money order

Charge to () Visa () Mastercard () American Express

Card No.

Expiry

Ontario Residents add 7% P.S.

Qty.	Item	Price
	Atom 12K RAM, 12K ROM (Black and White)	\$525
	Atom 12k RAM, 12k ROM (Colour)	\$599
	Power Supply	\$35

Delivery will be made by courier service where possible