

Electronics Today

\$3.25
MAY 1985

October 1985

Canada's Magazine for Electronics & Computing Enthusiasts

Oscilloscopes

What's new on the market

A Guide To Transformers

Simplified specs

Audio Mixer Project

For the home studio

Error Correction in RAM

Increase reliability

Crystal Radio

Reverse hi-tech



Digital
Scoreboard

BEST Computers

Made in Canada with pride. IBM PC & XT Compatible



Monitor not included. IBM registered trade mark of IBM Canada Ltd.

BEST MK II

Two 360K DS,DD disk drives, Serial and Parallel Ports, Real Time Clock, Phoenix BIOS, uses 8088 processor — full specifications given below.

\$1595⁰⁰

Other Configurations:

With 640K RAM	... \$1695
With 10 Meg Hard Drive/1 Floppy/256K	... \$2495
With 10 Meg Hard Drive/1 Floppy/640K	... \$2595
With 20 Meg Hard Drive/1 Floppy/256K	... \$2795
With 20 Meg Hard Drive/1 Floppy/640K	... \$2895

The FAST BEST MK III

As BEST MK II plus speed selectable: 4.77 and 8MHz (most software will run on the higher speed), uses 8088-2 processor.

\$1895⁰⁰

Other Configurations:

With 640K RAM	... \$1995
With 10 Meg Hard Drive/1 Floppy/256K	... \$2795
With 10 Meg Hard Drive/1 Floppy/640K	... \$2895
With 20 Meg Hard Drive/1 Floppy/256K	... \$3095
With 20 Meg Hard Drive/1 Floppy/640K	... \$3195

SUPER-FAST BEST MK IV

As BEST MK III plus TRUE 16-Bit machine, 8086-2 processor, IBM compatible 8-Bit I/O channel bus, even faster than MK III due to 16-Bit architecture.

\$2500⁰⁰

Other Configurations:

With 640K RAM	... \$2595
With 10 Meg Hard Drive/1 Floppy/256K	... \$3395
With 10 Meg Hard Drive/1 Floppy/640K	... \$3495
With 20 Meg Hard Drive/1 Floppy/256K	... \$3695
With 20 Meg Hard Drive/1 Floppy/640K	... \$3795

Features common to all the above systems:

- Superb IBM PC & XT Compatibility
- Canadian Made
- 256K RAM Standard minimum (uses 41256K RAM chips)
- Expandable on board to 640K RAM
- Parallel Port (for printer)
- Serial Port (for communications)
- Real Time Clock/Calendar (with Battery Backup)
- Presocketed for optional co-processor — such as 8087 Math Processor
- IBM Compatible Keyboard
- Reset Switch
- Phoenix BIOS as used in many major brand IBM compatible systems.
- 150 Watt Power Supply which will handle a Hard Drive without upgrade.
- 7 Slots
- Flip top case
- 2 Slimline DS,DD 5 1/4", 360K Disk Drives
- Colour Video (RGB & Composite) Board or Hi-Res Monochrome Card (customer choice)
- Disk Controller Board

Warranty

We have such confidence in the time tested reliability of the BEST that we offer a 300-day warranty, way above the industry standard.

Please Note: Don't be put off by our spectacularly low price; this is due to the fact we do not deal with middlemen and our volume buying power of parts. All BESTs are manufactured in Canada to the highest quality standards using prime, guaranteed components by our sister company. All systems are pretested (burnt-in) for about 48 hours before shipping. Hundreds of happy customers report excellent reliability and compatibility.

EXCELTRONIX

319 College Street, Toronto, Ont. M5T 1S2

(416) 921-8941. Order line only 1-800-268-3798

Ottawa, 217 Bank Street (613) 230-9000

Visa, Mastercard and American Express accepted.

EXCELTRONIX

Long Distance Order line only:
1-800-268-3798

319 College Street, Toronto, Ont, M5T 1S2 (416) 921-8941

217 Bank Street, Ottawa, (613) 230-9000 Mall order Enquiries (416) 252-5285

We guarantee you the combination of BEST Prices & Service in Canada!

APPLE COMPATIBLE DISK DRIVES

Now also available for Apple IIc

Famous
Multiflex
Disk
Drive



\$199.00 1 year full warranty

Features:

• Apple compatible • Attractively packaged • Professionally built and tested • Canadian Made. We believe that Multiflex put out more drives in the last year than all other Canadian manufacturers combined.

IBM compatible Disk Drives

SA455 DS,DD, 360K with warranty **\$169.00**

Hard Disk Drives

10 MEG Seagate, drive and hard disk controller. This controller can handle up to two 10 MEG hard drives.

LOWEST PRICE OF \$895.00

Quantity Discounts Available

Seg 20 MEG. with controller **\$1195.00**
Cables (for 10 or 20 MEG) **\$38.00**

Zenith Monitors

BEST SELLER ZVM 122A • 12" diagonal screen • non-glare amber display • composite input • 25 lines x 40/80 characters **\$135.00**

BEST SELLER ZVM 123A • 12" diagonal screen • non-glare green display • composite input • 25 lines x 40/80 characters **\$125.00**

ZVM 133 • 13" diagonal screen • RGB input • 25 lines x 80 characters • 640 x 240 pixels green screen only switch • 16 colours including PC brown **\$749.00**

Peripherals for your Apple

Z80 **\$ 43.00**
80 x 24 Video Card with Soft Switch **\$ 67.00**
16K RAM Card **\$ 43.00**
128K RAM Card with 128K Parallel Card with Cable **\$ 99.00**
Serial Card **\$ 59.00**
Apple Programmer **\$ 69.00**
Apple Programmer **\$ 65.00**

Multiflex 300 Baud Modem

For your Apple (Super compatibility) **\$159.00**

POWER TYPE LETTER QUALITY \$599.00
• 18 CPS bidirectional logic seeking.
• 96 Petal Wheel

IBM COMPATIBLE KEYBOARDS

Cherry **\$135.00**
Maxiswitch **\$135.00**

New from Star Micronics SG-10 Printer

• Dual Mode - NLQ/draft standard (NLQ = near letter quality) • 120 CPS and 20% faster throughput • Bidirectional logic/seeking • 2K buffer (expandable to 6K with optional buffer interface) • 100% IBM PC or Star standard control codes-switch selected • Friction and tractor standard • full 1 year warranty • 10" wide carriage • Standard parallel interface (serial optional) **\$399.00**

SG-15 same as SG-10

Except with 15" carriage and standard 16K buffer **\$599.00**
Radix — \$995.00 5R-15 \$995.00

Star Micronics Gemini 10X 1 year warranty

• 120 c.p.s., • 816 characters print buffer, option 4K or 8K • standard parallel optional RS232C • tractor & friction feed. **Super Special \$299.00**

(Time limited offer)



IBM Compatible "BEST" Peripheral Boards.

Colour Graphics Video Board Composite and RGB output **\$179.00**
Monochrome Hi-Res Video Board (TTL output) **\$179.00**
Parallel/Game Port Board (cable extra) **\$ 69.00**
Quanta Board
Parallel/Game Port, 2 x Serial Ports and Real Time Clock/Calendar with Battery Backup. Cables extra **\$159.00**
EPROM Programmer **\$ 99.00**
EPROM Programmer with ZIF Socket Adapter **\$159.00**

New Floppy Controller

Handles up to 4 DS, DD Drives
Parallel, Real Time Clock/Calendar, 2 Serial Ports **\$199.00**
Real Time Clock software included - cables extra.

High Quality AMP IC Sockets

8, 14, 16, 18, 20, 24, 28 and 40

1.5 cents per pin
Quantity discounts available

Bypass Capacitors

0.1 uF, 50V **.13¢**
100 pieces **\$9.00**

Fans

New 3in fan **\$12.95**
New 4in fan **\$13.95**

We have the best prices on 74LSXX TTL Series e.g:

74LS-00, 02, 04, 08, 10, 32 at **29¢ each**
74LS-138, 139, 158, 175 at **69¢ each**
74LS-244, 245, 273 at **\$1.19 each**

MEMORY Untouchable Prices! Guaranteed Prime Stock

Dynamic RAMs

4116 1x16k (150ns) **\$ 0.75**
4164 1x64k (150ns) **\$ 1.10**
4164's (150ns). Set of 9 **\$ 9.50**
41256 1x256k (150ns) **\$ 5.95**
41256 (150ns). Set of 9 **\$49.95**

Static RAM

2114L 4x1k 200ns **\$ 2.25**
6514 4x1k CMOS 450ns **\$ 1.20**
6116 8x2k 150ns **\$ 4.95**
2016 8x2k 150ns **\$ 3.99**
6264 8x8k 150ns **\$14.95**

EPROMS

2716 450ns 8x2k **\$ 5.50**
2716 300ns 8x2k **\$ 6.50**
2732 450ns 8x4k **\$ 3.75**
2732 250ns 8x4k - SPECIAL **\$ 3.75**
2764 300ns 8x8k **\$ 4.75**
27128 350ns 8x16k **\$ 6.95**

Limited Special

8088 **\$ 4.95**

Intel Parts Special Parts for your IBM & Apple Compatibles

8087-2 (High Speed) **\$219.00**
8087 **\$189.00**
8088 **\$ 7.90**
8237A-5 **\$ 8.90**
8250 **\$ 9.89**
8253A-5 **\$ 5.89**
8255A-5 **\$ 4.89**
8259A **\$ 4.95**
8284A **\$ 5.95**
8288 **\$ 9.75**
NEC765/8272 Equiv. **\$ 8.95**
74LS322 **\$ 5.95**
62 Pin Card Edge Connectors **\$ 2.19**
5 Pin Din Connector **\$ 0.99**
100ns Delay Line **\$ 5.89**
6502 CPU **\$ 5.45**
Z80A CPU **\$ 4.50**
68A45 CRT cont. **\$ 9.75**
TMS99532 FSK Modem **\$17.95**
Set of 8088, 8255A-5, 8237A-5, 8288, 8284, 8253A-5, 8259A **\$48.00**



The BEST PENTRAM 256K RAM

(as illustrated)
Real Time Clock,
Parallel Serial and
Game Port **\$299.00**

BEST IBM Compatible Modem

• Plugs into motherboard
• Excellent Hayes compatibility
• Auto Dial, Auto Answer, Direct-connect 300 Baud **\$179** 300/1200Baud **\$379**

BEST 512K RAM Boards

With 512K RAM **\$229.00**
With 64K RAM **\$149.00**



Our Cover

The Hameg HM208 digital storage scope, taken as the camera fell over the table edge; it was provided courtesy of BSC Electronics and photographed by Bill Markwick.



Audit Bureau of Circulations

Electronics Today is Published by:
Moorshead Publications Ltd. (12 times a year)
 Suite 601, 25 Overlea Blvd.
 Toronto, Ont. M4H 1B1
 (416) 423-3262

Editor: **William Markwick**
 Editorial Assistant: **Edward Zapletal**
 Director of Production: **Erik Blomkwist**
 Creative Manager: **Ann Rodrigues Maia**
 Production: **Douglas Goddard**
Naznin Sunderji
Sandra Hemburrow
 Circulation Manager: **Lisa Salvatori**
 Account Manager: **Marlene Dempster**
 Advertising (Que.) **John McGown & Associates**
 (514) 735-5191
 Advertising (B.C.) **(604) 688-5914**

Publisher: H.W. Moorshead; Executive Vice-President: V.K. Marskell; Vice-President - Sales: A. Wheeler; General Manager: S. Harrison; Controller: B. Shankman; Accounts: P. Dunphy; Reader Services: M. Greenan, H. Brooks, R. Cree, L. Robson, N. Jones; Advertising Services: A. LeBrocq.

Newsstand Distribution:
 Master Media, Oakville, Ontario

Subscriptions:
 \$19.95 (one year), \$34.95 (two years). Please specify if subscription is new or a renewal.

Outside Canada (US Dollars) U.S. add \$3.00 per year.
 Other countries add \$5.00 per year.

Postal Information:
 Second Class Mail Registration No. 3955. Mailing address for subscription orders, undeliverable copies and change of address notice is: Electronics Today, Suite 601, 25 Overlea Blvd., Toronto, Ontario, M4H 1B1

Printed by Heritage Press Ltd., Mississauga
 ISSN 07038984.

Moorshead Publications also publishes Computing Now!, Computers in Education, and Software Now!.

Advertisers' Index


Active Components Sales Corp.	41
BCS Electronics Ltd.	69
Budgetron Inc.	11
Computer Parts Galore	36,37
Computique	41
Dacor	43
Daetron	33
Duncan Instruments	11
Electronic Book Club	67
Exceltronix	2, 3
Hitachi	61
IBM	44
Information Unlimited	65
Kaientai Electronics Merchants Ltd.	70
K.B. Electronics	44
Len Finkler & Co.	31
McGraw-Hill	5, 29
Metermaster	62
Nicologix	32
Orion Electronic Supplies Inc.	44
Patron Components Inc.	70
Phillips Electronics	30
RCC Electronics	71
Soltech Industries Inc.	10
Sunix Inc.	6
Surplustronics	35
Tektronix Canada Inc.	72
The Software Link, Inc.	12
Universal Cross Assemblers	6
Varah Direct	7

Electronics Today

October 1985

Vol. 9 No. 10

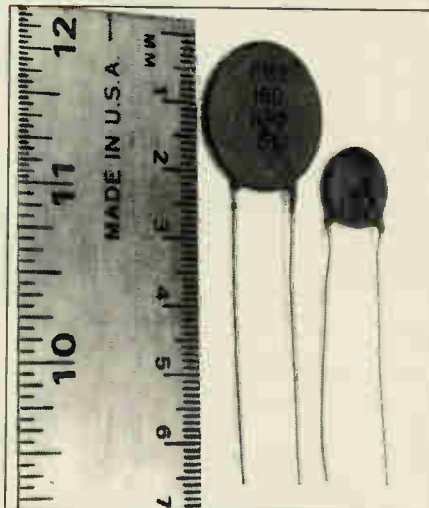Canada's Magazine for Electronics & Computing Enthusiasts



Electronics from the Start p.9



Oscilloscopes p. 39

Features

Error Correction in RAM	14
What's New In Oscilloscopes	34
A Guide To Transformers	38

Projects

Digital Scoreboard	22
Crystal Radio	50
Audio Mixer	54

Series

For Your Information	6
Computing Today: Z80 Part 5	8
Designer's Notebook: Transistor Summary	60
Electronics From The Start	9

Columns and Information

Software	47	Subscriptions	46
Electronics Today Next Month	16	Product Mart	53
Computing Now! This Month	16	Books	20
Software Now! This Month	17	Computing Books	46
Order Form	45		

MASTER THE NEW ELECTRONICS WITH MCGRAW-HILL'S

Contemporary Electronics Series

The fast, easy and low cost way to meet the challenges of today's electronic innovations. A unique learning series that's as innovative as the circuitry it explains, as fascinating as the experiments you build and explore.


From digital logic to the latest 32-bit microprocessor, the McGraw-Hill Contemporary Electronics Series puts you into the electronic picture one easy step at a time. Fifteen unique Concept Modules, sent to you one every 4-6 weeks, give you a handle on subjects like optoelectronics, robotics, integrated circuits, lasers, fiber optics and more.

Each Concept Module goes right to the heart of the matter. You waste no time on extraneous material or outdated history. It's a fast, efficient, and lively learning experience... a non-traditional approach to the most modern of subject matter.

Unique Interactive Instruction

With each module, you receive a McGraw-Hill Action Audio Cassette. Each tape is a dynamic discussion that drives home the key facts about the subject. Your learning

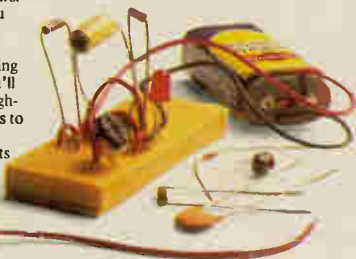With your first module, you get this solderless breadboarding system. You'll use it throughout the series to build electronic circuits and bring concepts to life.



experience is reinforced through interaction with vividly illustrated text, audio cassettes, and actual electronic experiments. Indexed binders preserve backup material, notes, and tapes for convenient referral.



wants an update in contemporary circuits... a

Perform Experiments in Contemporary Electronics

Throughout your series, laboratory experiments reinforce every significant point. This essential experience... dynamic, hands-on demonstrations of theory in practice... will help you master principles that apply all the way up to tomorrow's latest VLSI (Very Large Scale Integrated) circuitry.

In your very first module, you'll use integrated circuits to build a digital oscillator, verifying its operation with a light emitting diode (LED). You'll learn to identify passive and active components, understand concepts common to all electronic circuits.

For Anyone Interested in Electronics

The Contemporary Electronics Series is designed for anyone from hobbyist to professional. It's for you if you're looking for new fields of interest... if you're a teacher who

manager or supervisor in an electronics plant... a doctor, an engineer, a chemist who finds electronics playing an increasingly important role in your work. It's even for electronics engineers or technicians who feel their training needs freshening up. It's the quickest, most convenient, probably least expensive way to do it. And the only one that gives you hands-on experience.

15-Day No-Risk Trial


To order your first module without risk, send the postage-paid card today. Examine it for 15 days under the terms of the order form and see how the Contemporary Electronics Series gets you into today's electronics. If card has been used, write us for ordering information.



McGraw-Hill
Continuing Education Center
330 Progress Avenue
Scarborough, Ontario M1P 2Z5

For Your Information

Surge Protector

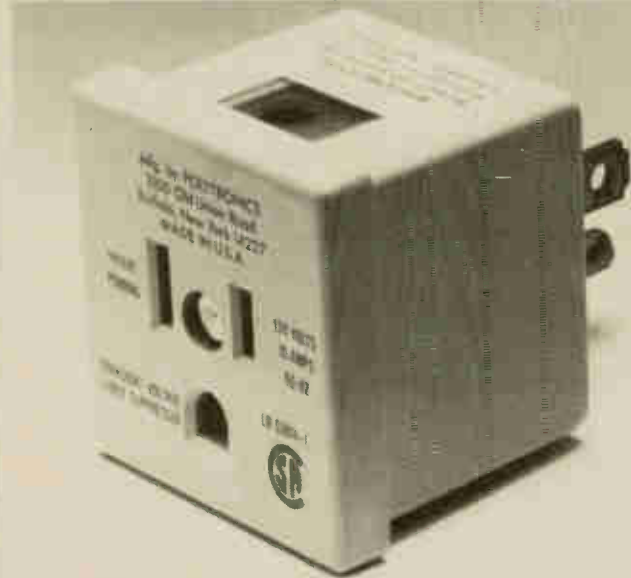


A varistor in a tiny low-cost plugpack protects computers and other electronic equipment from high-voltage spikes that come down the powerline. Low-power spikes are absorbed harmlessly; larger ones may burn out the varistor, protecting the equipment downline. A light indicates

whether the workings are still okay or not. The printing by the indicator window says 'If it's red, go ahead. If it's black, send it back.' The window was green. From Len Finkler and Co., 80 Alexdon Road, Downsview, Ontario M3J 2B4, (416) 630-9103.

Circle No. 43 on Reader Service Card

RF Patch Cords

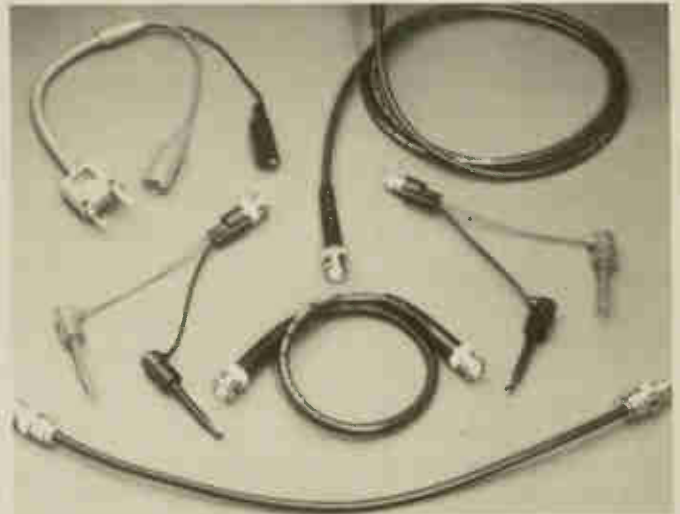

A new line of RF Patch Cords in a wide range of connector styles, including mini-hook grippers, dual stacking banana plugs, alligator clips and BNC connectors has been introduced by the E.F. Johnson Co. Components Division. They're available with more than a dozen termination configurations

with three cable types and cable lengths from 12 inches to five feet. All of the various cords are available off-the-shelf so you can leave them on-the-floor. Contact Lenbrook Electronics, Unit 1, 111 Esna Park Drive, Markham, Ontario L3R 1H2, (416) 477-7722.

Circle No. 44 on Reader Service Card

continued on page 31

NEW LOW PRICES

THE AFFORDABLE XT COMPATIBLE

HIGHEST QUALITY, RELIABILITY AND COMPATIBILITY (ALL MAJOR BOARDS MADE IN JAPAN)

STANDARD SYSTEM NOW ONLY **\$1,195**

- 256K XT System Board, w/o BIOS
- Two DSDD Disk Drives
- Controller Card
- Colour Graphic Card
- Case, Keyboard, Heavy Duty Power Supply
- Box of Nashua Diskettes FREE

90 DAY WARRANTY



DEALER INQUIRIES INVITED

PRO 25M HARD DRIVE SYSTEM NOW ONLY **\$2,295**

- 256K XT System Board, w/o BIOS
- One DSDD Disk Drive
- Controller Card
- Colour Graphic Card
- One Seagate 25MB Hard Disk Drive with Controller
- Case, Keyboard Heavy Duty Power Supply
- Box of Nashua Diskettes FREE

Options with purchase of above system only	Special	Regular
A) 384K (Installed) Multifunction Card	\$239.00	\$275.00
B) Monochrome Graphic and Printer Card	195.00	229.00
C) NEC RGB Colour Monitor, 1216 DFA	450.00	495.00
D) Zenith Monochrome TTL Monitor, ZVM 124	169.00	189.00
E) Roland NLQ Printer, 1111A	409.00	429.00
F) 512K RAM Card	168.00	195.00

SPECIAL OF THE MONTH: SEAGATE HARD DISK DRIVES COMPLETE WITH CONTROLLER AND CABLES
10MB, ST212.....\$995.00 25MB, ST225.....\$1,295.00

Mail orders cheque, money order, visa, MasterCard accepted. \$5.00 for shipping and handling. Ontario residents add 1% P.S.T.

SUNIX INC.
(Formerly Audiovision)

578 MARLEE AVE. (At Glencairn Subway) Toronto, Ontario M6B 3J5
Tel: (416) 761-3283
In Dallas, USA: (214) 935-1842



CROSS-8 MAYBE THE ONLY DEVELOPMENT SOFTWARE YOU'LL EVER NEED

- Table based 8 bit cross-assembler
- Tables/Source files included for:

1802	6502	8048	COP400
3870	6801	8051	Z8
	6805	8085	Z80
- Modify/Create tables for most 8 bit micros
Create your own instruction sets
- INTEL, MOTOROLA, TEKTRONIX output formats
- Use with any EPROM programmer
- 36 page manual, full instructions
- Available in the following disk formats:
 - 5" IBM-PC PC/MS-DOS 2.0 or greater, compatibles
 - 5" APPLE II+/IIe CP/M-80 (Softcard), compatibles
 - 8" SSSD CP/M-80 (Z80 only)

\$99⁹⁵ US \$129⁹⁵ CDN

Credit card orders: Include card no., name on card, expiry date, signature. Nova Scotia residents add 10% sales tax.



UNIVERSAL CROSS-ASSEMBLERS
P.O. BOX 384 BEDFORD NOVA SCOTIA
B4A 2X3 CANADA

Copyright

All material is subject to worldwide copyright protection. All PCB patterns are copyright and no company can sell boards to our design without our permission.

Liability

While every effort has been made to ensure that all constructional projects referred to in this magazine will operate as indicated efficiently and properly and that all necessary components are available, no responsibility whatsoever is accepted in respect of the failure for any reason at all of the project to operate efficiently or at all whether due to any fault in the design or otherwise and no responsibility is accepted for the failure to obtain component parts in respect of any such project. Further no responsibility is accepted in respect of any injury or damage caused by any fault in design of any such project as aforesaid.

Editorial Queries

Written queries can only be answered when accompanied by a self-addressed, stamped envelope. These must relate to recent articles and not involve the staff in any research. Mark such letter Electronics Today Query. *We cannot answer telephone queries.*

Binders

Binders made especially for Electronics Today (ETI) are available for \$9.75 including postage and handling. Ontario residents please add provincial sales tax.

Back Issues and Photocopies

Previous issues of Electronics Today Canada are available direct from our office for \$4.00 each; please specify by month, not by feature you require. See order card for issue available.

We can supply photocopies of any article published in Electronics Today Canada; the charge is \$2.00 per article, regardless of length. Please specify both issue and article.

Component Notation and Units

We normally specify components using an international standard. Many readers will be unfamiliar with this but it's simple, less likely to lead to error and will be widely used everywhere sooner or later. Electronics Today has opted for sooner!

Firstly decimal points are dropped and substituted with the multiplier: thus 4.7uF is written 4u7. Capacitors also use the multiplier nano (one nanofarad is 1000pF). Thus 0.1 uF is 100nF, 5600pF is 5n6. Other examples are 5.6pF = 5p6 and 0.5pF = 0p5.

Resistors are treated similarly: 1.8Mohms is 1M8, 56kohms is the same, 4.7kohms is 4k7, 100ohms is 100R and 5.6ohms is 5R6.

PCB Suppliers

ETI magazine does NOT supply PCBs or kits but we do issue manufacturing permits for companies to manufacture boards and kits to our designs. Contact the following companies when ordering boards.

Please note we do not keep track of what is available from who so please don't contact us for information PCBs and kits. Similarly do not ask PCB suppliers for help with projects.

K.S.K. Associates, P.O. Box 266, Milton, Ont. L9T 4N9.

B—C—D Electronics, P.O. Box 6326, Stn. F., Hamilton, Ont. L9C 6L9.

Wentworth Electronics, R.R. No. 1 Waterdown, Ont. L0R 2H0.

Danocinths Inc., P.O. Box 261, Westland MI 48185 USA.

Arkon Electronics Ltd., 409 Queen Street W., Toronto, Ont., M5V 2A5.

Spectrum Electronics, 14 Knightswood Crescent, Brantford, Ontario N3R 7E6.


IT'S PACKED & READY

OUR NEW CATALOGUE IS:

- ★ PACKED with over 2000 top-grade, fully spec'd components
- ★ READY to ship to you

FREE!

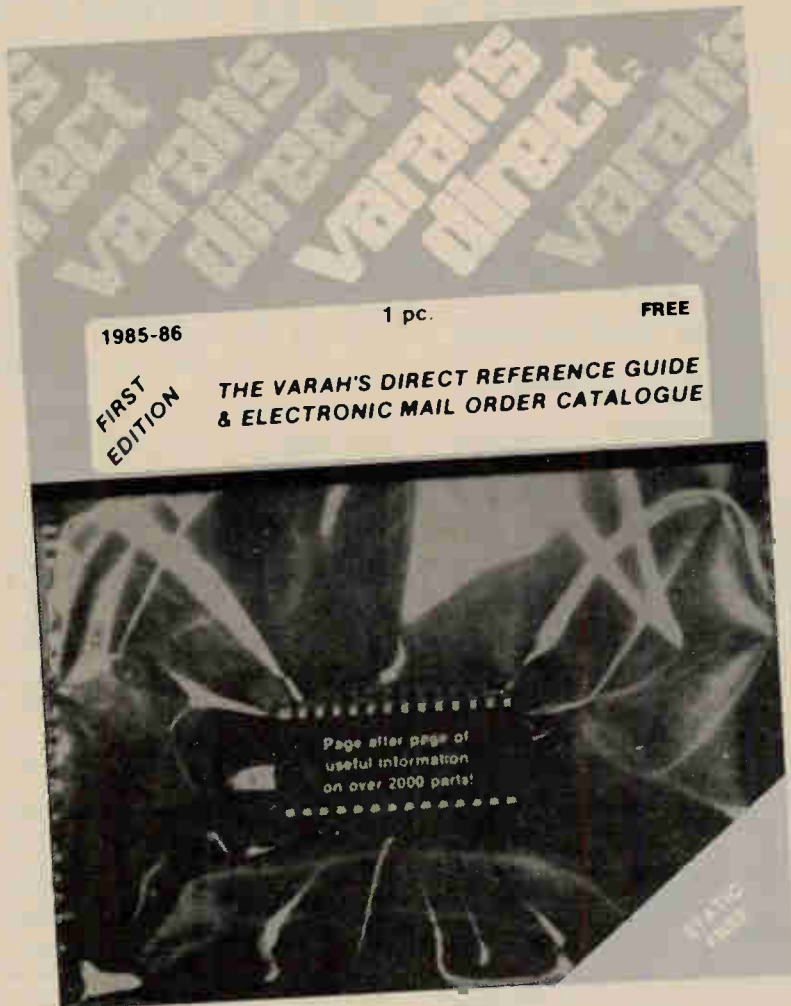Respond to this ETI ad and get yours free!



Not just a product listing, it's a fully referenced guide giving you operating specs, pin-outs, and dimensions for each part.

Everything you need to build your project:

- semiconductors
- cabinetry
- resistors
- connectors
- power supplies
- capacitors
- test equipment
- PCB Supplies
- literature

AND MUCH MORE in the Varah's Direct Reference Guide & Electronic Mail Order Catalogue



Locations:

Vancouver
Edmonton
Calgary
Winnipeg
Oakville
Nepean

Write:

Varah's Direct
504 Iroquois Shore Road
Oakville, Ontario
L6H 3K4
(please include your return postal code)

Circle:

The reader service number for this ad
Or Call:
(416) 842-8833
Monday to Friday
8:00 - 5:00, E.S.T.

Electronics Today October 1985

Circle No. 5 on Reader Service Card

7

CONNECTING LEADS

Fig. 1 A simple diagram of the internal construction of a capacitor.


Fig. 2 Some common capacitors. From front to back: a polyester, two tantalum beads, two metalized ceramics, two ceramic disc types, and two mylar film capacitors.

Electronics Today October 1985

9

Electronics From the Start

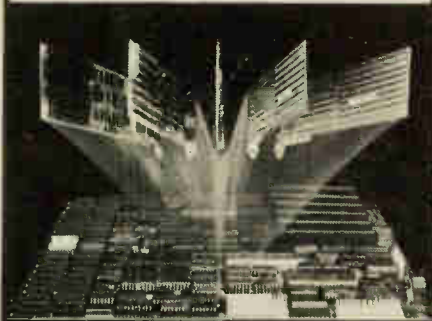**INTRODUCING:
THE NEW STANDARD
FOR IBM PC/XT
COMPATIBILITY**
The ACS-1000 Super Computer



- 1 Megabyte On-Board Memory
- Built-in Disk Controller
 - up to 4 Floppies
 - SASI Hard Disk Interface
- 54 KB User Definable ROM
- Switchable: 4.77 or 8 MHz
- Built-in Multifunction Board
 - Parallel Printer Port
 - 2 Serial Ports
 - Time-of-day Clock

**Seize Control of Your
Hardware Destiny**

If you are using board level microcomputers you can have greater power, versatility and reliability by using the ACS-1000 single board SuperComputer.

The ACS-1000 is compatible with both software and hardware designed for the IBM PC/XT. It even has the same mounting holes and the same power supply connections. The difference is that the ACS-1000 offers a much higher level of integration and costs less than \$600 when ordered in quantity.

Save your Expansion Slots for true expansion. Disk Controllers, I/O ports and extensive memory are already built-in, simplifying production and freeing the 6 expansion slots to take on specialized work of your process control, CAD/CAM or office automation applications. There's even a special port for a low cost piggyback modem.

See for yourself. We are offering a system evaluation kit for \$995.00. The 256K system includes bios, documentation, and an XT compatible power supply.

Special introductory offer on peripherals and chips.

Shugart SA 455 Floppy Drives **\$185.00**,
IBM Compatible cases **\$80.00**, 130 Watt
Power Supplies **\$220.00**, Keyboard
\$200.00, Chips 64K **\$3.00**, 256K **\$14.00**.

To order call 604-888-2606 or write:
Soltech Industries Inc.
9274 - 194th Street
Surrey, B.C. V3T 4W2

2uF, and usual working voltages go up to 600V. Like resistors, capacitors have a specified tolerance which indicates how accurate their marked values are. Paper capacitors usually have tolerances of $\pm 20\%$. Both the value and the tolerance are marked on the device's body in numerical figures.

Metallized paper capacitors use an evaporated metal film as the conductor instead of aluminum foil. The metallic film is deposited onto a former by a sputtering process. This is a technique whereby a cathode in a gas discharge tube is slowly disintegrated by bombarding it with positive ions. When this process is used to deposit metal film on an object, the object is placed near the cathode which is made of the metal to be deposited, and the tube is then evacuated to a low pressure (1 to 0.01mmHg). An anode potential of 1kV to 20 kV is then applied and the process begins.

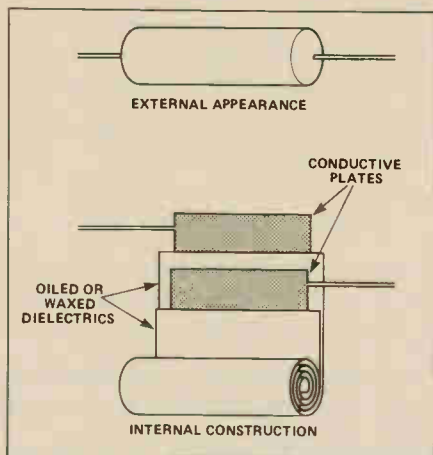


Fig. 3 This shows how the dielectric and conductive plates in the capacitor are rolled for packaging.

Mica capacitors come in a range of values from about 5pF to 50nF. As we mentioned earlier, high capacitance values are not made with mica due to the high cost.

Just as resistors are affected by their operating temperature and rated with a temperature coefficient, so are capacitors. The temperature coefficient for the average 10pF mica cap is +75ppm per degree Celsius.

Ceramic

Fig. 5 shows two low voltage miniature ceramic disc capacitors. As you might have guessed, these capacitors utilize ceramic dielectrics. These are standard general purpose low power devices and are usually available in values between 0uF01 and 1uF47. The tolerance of these components is in the order of +80%-20% and they have a working voltage of 12V. The next size up has a working voltage of 500V.

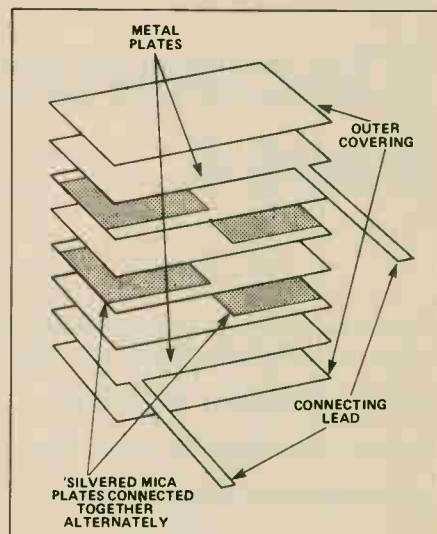


Fig. 4 A graphic illustration of the innards of a mica capacitor.

High voltage (500V) ceramic capacitors are made in exactly the same way as their low power brothers, except they're larger. The differences between the two types is determined by the type and dimension of the dielectric used.

Ceramic capacitors are made with dielectrics of three different values of relative permittivity. Very compact ceramic caps use high permittivity dielectrics of values up to 1200. These are however very sensitive to temperature. Medium permittivity types have negative temperature coefficients and are

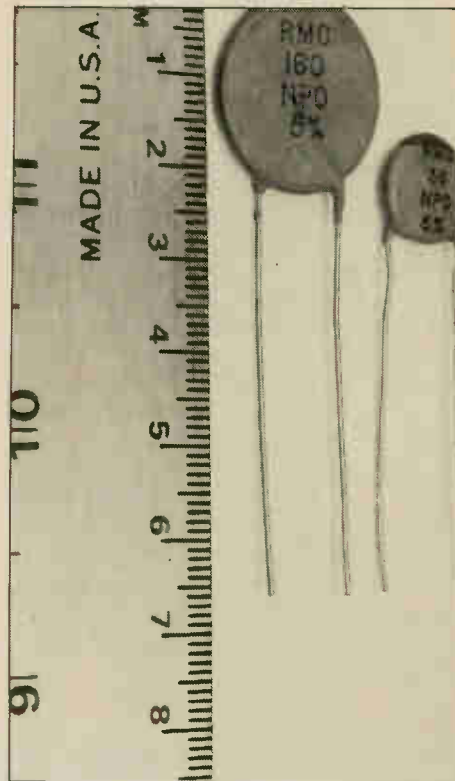


Fig. 5 Two large high voltage ceramic disc caps.

employed as temperature correcting components. Low permittivity dielectrics have a very good frequency response but a low working voltage.

Just as the mica capacitor had its conductors formed by metallization, so can ceramic components. A range of capacitances from 1pF to 22000pF is manufactured, with tolerances ranging from $\pm 0pF25$ to -20% — $+80\%$. Five different temperature coefficient ranges are made according to the

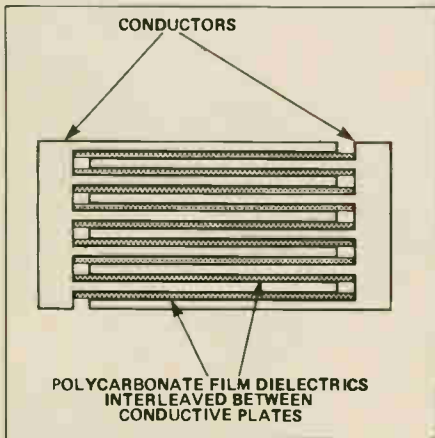


Fig. 6 This shows the internal construction of a polycarbonate capacitor.

resistance values. The coloured blend on the top of each capacitor denotes the temperature coefficient. These values are given in Table 2. Capacitors of this type are generally rated at 100VDC.

Plastics

Plastic capacitors form a major component group with dielectrics fabricated from films of polystyrene, polycarbonate, and polypropylene.

A very large range of capacitances is available, running as high as 100000pF. Of course, as capacitance increases, so does the physical size of the component. A 100000pF polystyrene cap has a body 22mm long and 17mm in diameter. Like almost all plastic capacitors, this type is made by winding the dielectric and the

Table 2

Capacitor	Temperature coefficient	Colour band
1.8 to 18pF	Zero	Black
22pF to 150pF	-150ppm°C ⁻¹	Orange
180pF to 330pF	-750ppm°C ⁻¹	Violet
390pF to 4700pF	(medium permittivity)	Yellow
10,000 to 22,000pF	(high permittivity)	Green

conductors into a roll which is then sealed into a tubular or flat package.

Typically, polystyrene capacitors possess temperature coefficients in the area of -160 ± 80 ppm per degree Celsius and have very low losses. This means that they are very good at holding their charge.

Other polystyrene capacitors are manufactured to very close tolerances, often as low as $\pm 1\%$.

Miniature polycarbonate capacitors measuring about 10mm x 10mm x 5mm are very suitable for PCB and breadboard mounting because of their small size and parallel leads. These components range in value from 0uF001 to 1uF x10% or x5%, with a temperature coefficient of 65ppm per degree Celsius. The maximum working voltage is between 120V to 400VDC,

DUNCAN INSTRUMENTS LTD.
ELECTRONIC INSTRUMENT SPECIALISTS
121 MILVAN DRIVE, TORONTO, ONTARIO M9L 1Z8
TEL. (416) 742-4448 - TELEX: 065-27271

OSCILLOSCOPE

MODEL 6022 20 MHz DUAL TRACE

The model 6022 oscilloscope meets the needs of the modern technician at a most realistic price. A built-in component tester enables problem components to be eliminated, thus saving valuable service time.

FEATURES
DC - 20 MHz (-3 dB)
5 mV vertical sensitivity
built-in component tester
140mm PDA tube with internal graticule
X-Y-Z operation
dual 1:1, 10:1 probes supplied.

\$635.00 FST incl. Ontario residents add 7% PST.

Circle No. 7 on Reader Service Card

DEALERS/OEMS
Add Value to Your IBM™
Build Your Own PC/XT COMPATIBLE

**CPS-1130M 130 WATT
SIDE SWITCHING
POWER SUPPLY**

- Direct Replacement for IBM™ 63.5 Watt
- CSA PENDING

XT COMPATIBLE MOTHER BOARD

NEW
UNITECH K-150L KEYBOARD

"IBM SELECTRIC TYPEWRITER compatible Layout"
IBM is a registered Trademark of IBM Canada Ltd.

DELTA TECHNOLOGIES

IBM™ PERIPHERAL CARDS

- FLOPPY DRIVE CONTROLLER
- MONOGRAPHICS/W PARALLEL
- COLOUR GRAPHIC • SERIAL
- PARALLEL 256/512K RAM
- 384K MULTIFUNCTION
- JOYSTICK • MONOCHROME

IN HOUSE TECHNICAL SUPPORT 90 DAY WARRANTY ON ALL PRODUCTS

BUDGETRON INC.
IMPORTER
DISTRIBUTOR

1320 Shawson Drive, Unit 1, Mississauga, Ontario, Canada L4W 1C3
Telephone (416) 673-7800 TELEX 06-968080

Circle No. 8 on Reader Service Card



Networking Raised to a Greater Power

Advanced Technology. With it, IBM tripled the speed of the PC and increased its memory capacity five-fold. Nowhere is this increase in computing power more important than in networking situations. If the AT's technological advances have prompted you to look into a multi-user network, you owe it to yourself to take a closer look at MultiLink Advanced™ . . . a unique multi-tasking, multi-user networking system that runs programs under PC-DOS 3.0.

Eight Workstations for the Price of an AT. MultiLink Advanced™ represents the next generation in networking systems for IBM microcomputers. The system enables terminals, connected to a single AT, to emulate IBM-PC's having up to 448K of RAM (The PC-Shadow™ terminal, shown above, even has a PC look-alike, as well as work-alike keyboard and display).

This means that instead of spending \$3,000 per workstation for a PC with a Kilobuck "Network Interface Board," you can use inexpensive terminals . . . eight of which cost less than an IBM AT. Even if you need only one workstation connected to your AT, you'll realize significant savings.

MultiLink Advanced™ . . . Instant Access to All of Your Resources. Central to most multi-user situations is the need to coordinate a variety of printers. With what's been described by *PC-Tech Journal* as ". . . by far, the best print spooler for the IBM PC." MultiLink Advanced™ gives users the option to print either at their workstations, or at a central location. In addition, programs and files can be shared by multiple users locally or through use of a modem. Just think of it . . . having remote access to an AT with a lightweight terminal modem.

Although designed to take advantage of the AT, MultiLink Advanced™ runs on all versions of PC-DOS, except 1.0, and certain implementations of MS-DOS. A wide range of leading programs are supported which include WordStar, dBASE III, Multimate, and Lotus 1-2-3.

Get the Advanced Story Today. Call The Software Link Today for complete details and the dealer nearest you. MultiLink Advanced™ is immediately available at the suggested retail price of \$745 and comes with a money-back guarantee. VISA, MC, AMEX accepted.

MultiLink™ ADVANCED



THE SOFTWARE LINK, INC.

400 Esna Park Drive, Suite 18, Toronto (Markham), Ont. L3R 3K2

CALL: 416/477-5480

Dealer Inquiries Invited

IBM PC, AT, & PC-DOS are trademarks of IBM Corp. MS-DOS, WordStar, dBASE III, Lotus 1-2-3, and Multimate are trademarks of Microsoft Corp., MicroPro, Ashton-Tate, Lotus Development Corp., & Multimate International, respectively.

MultiLink Advanced™ & PC-Shadow™ are trademarks of The Software Link, Inc.

Capacitor Colour Codes

Colour	First Figure	Second Figure	Multiplier	Tolerance
Black	0	0		Black = 20%
Brown	1	1	$\times 10^1$	White = 10%
Red	2	2	$\times 10^2$	Green = 5%
Orange	3	3	$\times 10^3$	Black 20%
Yellow	4	4	$\times 10^4$	White 10%
Green	5	5	$\times 10^5$	Green 5%
Blue	6	6	$\times 10^6$	
Violet	7	7	$\times 10^7$	
Grey	8	8	$\times 10^8$	
White	9	9	$\times 10^9$	

according to capacitance. These components are multi-layer devices constructed as in Fig. 6.

Self-Help

These, like many plastic film capacitors possess *self-healing* properties. This means that if the dielectric breaks down in any place, the capacitor will not be useless, but in many cases will function better than ever.

A small number of pin-holes, thin areas or air pockets in the plastic films, and these are all potential areas of breakdown. When breakdown occurs, the thin metal conductors are evaporated from around the point of breakdown. This leaves a metal free (insulated) region, and presto, we are left with a good capacitor again. As the conductive plates are made from very thin metal only a small amount of energy is used in self-healing.

During the manufacturing process, capacitors are *cleared* by subjecting them to very high voltages. This ensures that all potential breakdowns are actually *made* to happen and the capacitors are forced to self-heal at voltages higher than those to which they would be normally subjected. The healing process is graphically illustrated in Fig. 7.

Metallized polyester film capacitors are components that use polyethylene terephthalate (PETP) dielectrics that have conductive plates metallized upon them.

Polyester capacitors have a wide operating temperature range (-40 to 100 degrees Celsius), and are typically available in values from 0uF01 to 2uF2 $\pm 10\%$ to $\pm 20\%$ with an average temperature coefficient of about 300ppm per degree Celsius.

Some polyester capacitors have their values marked on them, but others have a banded colour code system similar to that used on resistors (Fig. 8).

The final type of capacitor to be discussed is the mylar film type which is a general purpose plastic capacitor available in values from 0uF001 to 0uF22 $\pm 10\%$ with a working voltage of 100VDC. *To be continued.*

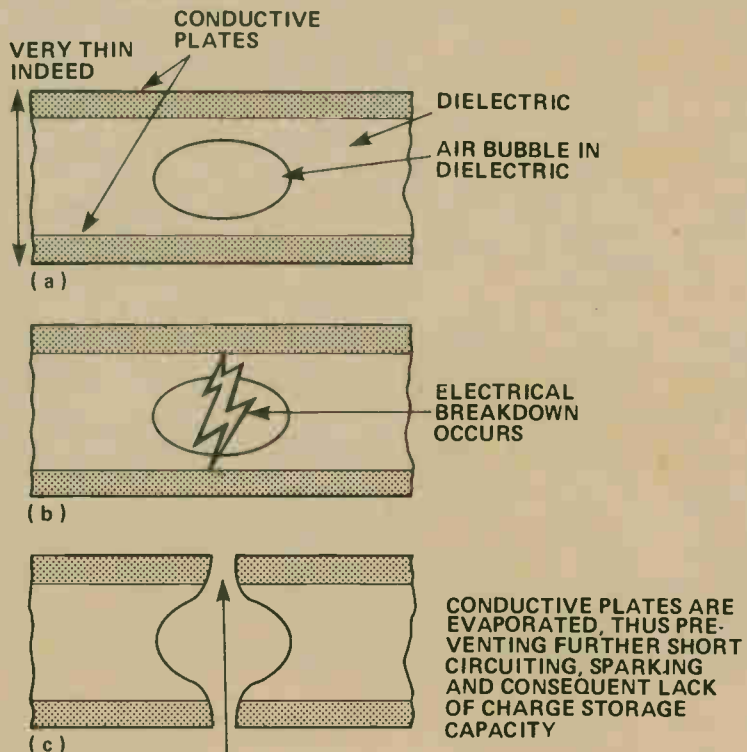


Fig. 7 A graphic representation of how a self-healing capacitor organizes itself after an electrical breakdown, so that normal functioning continues.


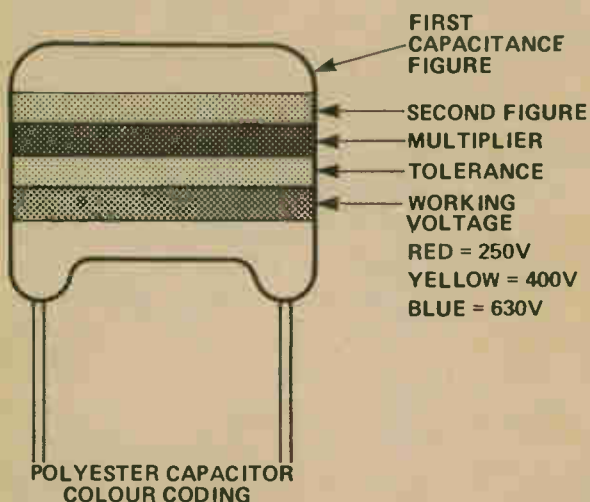


Fig. 8 A close-up diagram of the colour coding system used for many capacitors.

Error Correction in RAM

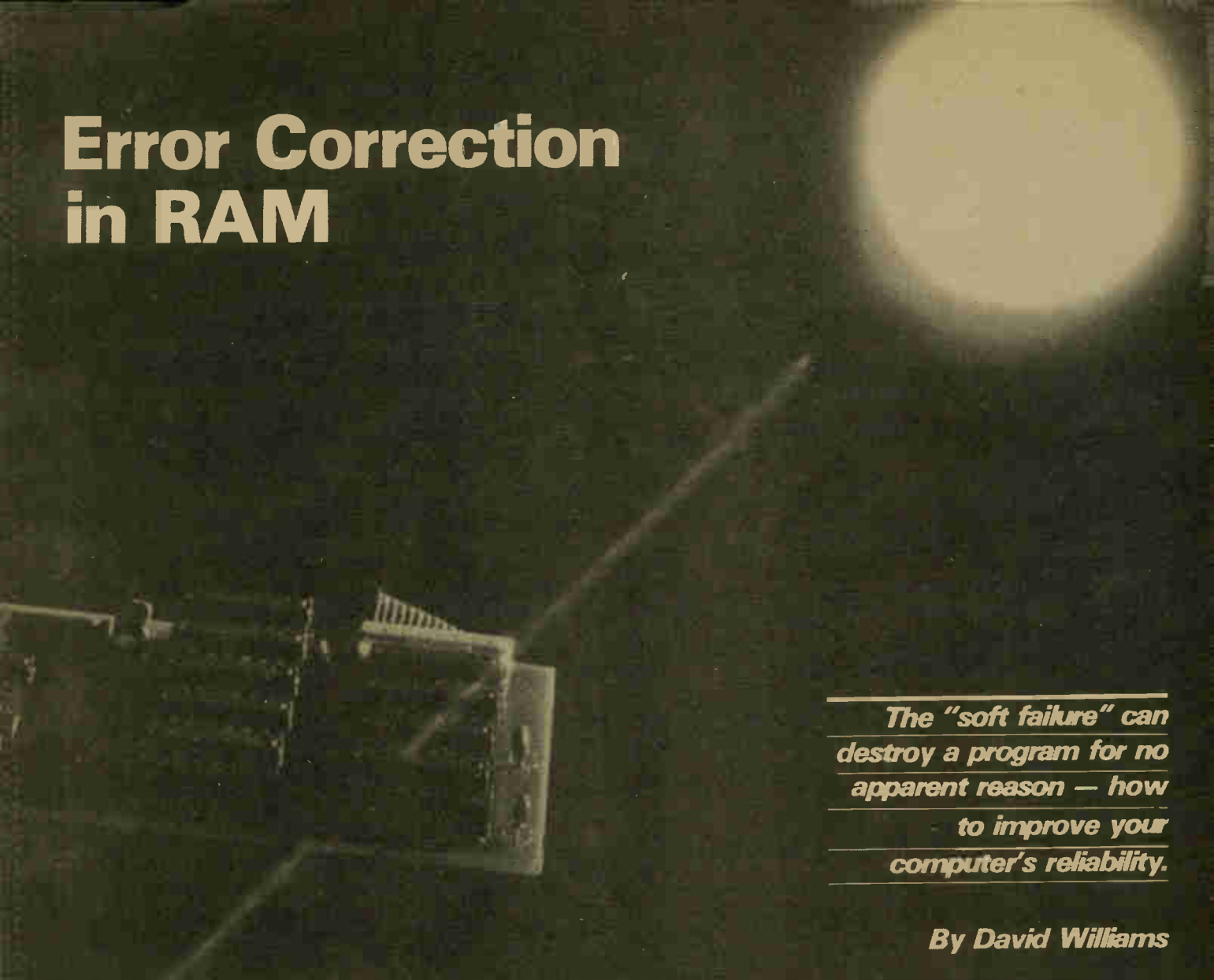

*The "soft failure" can
destroy a program for no
apparent reason — how
to improve your
computer's reliability.*

By David Williams

USERS OF microcomputers frequently suspect that their machines "make mistakes". Errors occur which seem not to be due to faulty hardware, illogical software or inaccurate data. A program which has run perfectly a thousand times suddenly goes wrong. All attempts to reproduce the problem, in order to locate and fix it, fail. After misbehaving once, the system behaves perfectly until, a long time later, a totally different problem makes a one-time appearance. These events are rare, occurring on average only once in hundreds or thousands of hours of microcomputer operation. Most of them are usually dismissed as being due to human errors or to faulty operations of components, such as disk drives, which are known not to be completely reliable. Since they are so rare, they are seldom thought of as serious problems. When they occur, the user simply re-boots the system and starts over.

But there are exceptions. Operators of computer Bulletin Board Systems

(BBSs), for example, often leave their machines running unattended for very long periods of time. Anything which causes a system crash can inconvenience all the BBS's users until the operator discovers the situation and re-boots the system. BBS operators sometimes find that these crashes have happened at times when the even cannot be explained by a human or disk error. Many BBSs spend most of their time waiting for the phone to ring. If a crash occurs during one of these waiting periods (and many such crashes have actually been observed), its cause cannot be a human or disk malfunction.

What Happens

Some of these events cause recognizable error conditions. The computer may report a "Syntax Error" in a BASIC program. Listing the program shows that one of its lines has been somehow converted to nonsense, although the previous proper operation of the program shows that the

line must initially have been correct. Many crashes, although they have not been accompanied by simple "Syntax Error" messages, have also been discovered to be due to changes in the contents of the computer's memory. Re-booting the system usually clears these problems, so they cannot be ascribed to permanent failures of the memory hardware.

These spontaneous changes in the contents of RAM are often described as "soft failures", to distinguish them from "hard failures" in which RAM fails permanently. Soft failures have no perceptible long-term effects on the computer hardware. A memory chip which has undergone a soft failure works just as well afterwards as it did before.

Deeper Causes

There are several known causes of soft failures. Some of them are incipient hard failures, in which the hardware works unreliably before (maybe) failing altogether. Bad or overheated IC chips,

Electronics Today October 1985

poor solder connections and broken PCB tracks can all cause apparent soft failures. Some people prefer to call these "intermittent hard failures". Describe them however you wish; their effect is similar to all other soft failures except that when they occur, they tend to be more frequent and predictable than those which are produced by other causes.

Some soft failures originate outside the computer. Bad electrical or electro-magnetic "noise" can sometimes make a microcomputer memory misbehave. The noise can come from voltage spikes on the A.C. power line, or from electro-magnetic fields generated by nearby equipment.

Perhaps the most mystifying soft failures are those which are caused by ionizing radiation. If, for example, a heavy radioactive nucleus decays in the vicinity of a memory chip, it may cause an "alpha particle" to pass through the chip. This is a charged particle, actually a helium nucleus, which is surrounded by an intense electrostatic field. As it passes through the material of the chip, this field can move electrons from their normal positions. These electron movements can be sufficient to "flip" a memory cell from the state which holds the digit "1" to the "0" state, or vice versa. Thus the information in the memory is corrupted.

Radioactive decay is not the only source of ionizing radiation. Cosmic rays, atomic nuclei which have accelerated to extremely high energies by various astronomical processes, are common in space. When they enter the earth's atmosphere, they usually collide with air molecules, producing large numbers of "secondary cosmic rays" which are particles with lower energies than the "primaries". By the time sea-level is reached, there are few particles with sufficient energy to cause RAM soft failures, so events from this cause are relatively rare at low altitudes. However, at elevated locations and especially in spacecraft, soft failures due to cosmic rays can be much more troublesome, requiring special precautions to eliminate their effects.

Battling the Problem

The method which is normally used on spacecraft to minimize the effects of soft errors is to employ hardware redundancy. Wherever possible, three independent computers work in parallel. Their operations are frequently compared, and, if one of them is found to be in a different state from the other two, it is deemed to have suffered a soft failure. The memory of this one computer is then re-loaded with the contents of one of the others, so that the computer is restored to the presumed error-free condition.

This method of working in bureaucratic triplicate is very effective. If the

comparisons among the computers are done sufficiently frequently, the overwhelming majority of errors can be eliminated. Only very rarely will events occur, such as all three computers being found in different states, which would require computation to be restarted from scratch. For most of us with our feet on the ground, the idea of using three computers to do the work of one is ruled out by economics. Usually, we just have to put up with occasional soft failures, using our human intelligence to detect them and to prevent their effects from becoming too large. However, there are occasions, especially when a computer spends long periods of time during which the contents of its memory should not change, when sufficient redundancy can be built into a single computer to allow errors to be detected and corrected. A BBS which is waiting for a phone call is an ideal system on which to do this. The rest of this article describes a method which I have used, with the help of some other system operators, to detect and correct soft errors in waiting BBSs.

Double Checksumming

Checksums are common means for detecting errors in information. For example, if two computers are exchanging information over a telephone line, they may transmit and receive the information in "blocks" of, typically, a few hundred bytes. During the transmission of a block, both computers calculate the sum of all the numbers contained in the bytes. The transmitting computer sums them as transmitted, and the receiving computer as it receives them. At the end of the block, the machines compare the two sums. Of course they should be identical. If so, the machines proceed to the next block. If the checksums are different, an error must have occurred during the transmission. In this case, the same block is sent again. Using checksums, quite accurate transmission of information is possible even over noisy phone lines which would otherwise produce many errors.

Checksums are a form of redundancy. Some extra information (the checksum comparisons) is transmitted over the phone lines, and can be used to detect errors in a transmission. By using a greater amount of redundancy, it is possible not only to detect errors but to correct them without requiring retransmission of the entire block. One method of doing this is to use a "double checksum".

The following little BASIC routine illustrates how a checksum and double checksum are calculated:

```
100 CHECKSUM = 0
110 DBLCHKSUM = 0
120 FOR INDEX = FIRST TO LAST
```

```
130 CHECKSUM = CHECKSUM
+ ITEM(INDEX)
140 DBLCHKSUM = DBLCHKSUM +
CHECKSUM
150 NEXT INDEX
```

The difference between this and a simple checksum calculation consists of the inclusion of the quantity DBLCHKSUM. After each ITEM is added to CHECKSUM, the current value of CHECKSUM is added to DBLCHKSUM. Whereas CHECKSUM ends up by containing the simple sum of the various ITEMS, DBLCHKSUM ends up with the sum of the last ITEM, plus twice the second-last ITEM, plus three times the third-last ITEM, and so on back to the first item.

Suppose that this is used in a data-transmission scheme and that, at the end of a block, the sending computer transmits its values of CHECKSUM and DBLCHKSUM to the receiving computer. The receiving machine finds that its own value of CHECKSUM is four more than the value which the sending computer calculated and that its own DBLCHKSUM is twelve greater than the sending machine's value. Obviously (unless several errors occurred), the third-last ITEM must have been garbled during transmission, and can be fixed by the receiving computer by subtracting four from the value it received. Mission accomplished! No more error!

The possibility that several errors have occurred can usually be distinguished from a single error. If only one byte is wrong, the difference between the two computers' values for CHECKSUM will be no more than 255, the largest possible error in a single byte. Dividing the difference between the two DBLCHKSUMs by the difference between the CHECKSUMs will produce an integer in the correct range, to point to an ITEM between the first and last, inclusive. Correcting this ITEM by the CHECKSUM difference will produce a number which is also in the range zero to 255, to be a valid content of a byte.

If any of these conditions is not met, the receiving computer should conclude that several errors must have occurred, and should then signal the transmitting machine to resend the block. Thus, although the system is not perfectly reliable (there is no such thing as a perfectly reliable information system), in the vast majority of cases it can be made to behave correctly, fixing one-byte errors quickly, and demanding re-transmission when multi-byte errors have occurred.

Double-Checksumming Memory

Checksums can be used in circumstances other than data transmission by

telephone. Any sequence of numbers can be used to generate a checksum and double checksum. If there is reason to suspect that the numbers may be corrupted, the checksum and double checksum can be used to detect and correct any error. This is the method which I have used to find and fix RAM soft failures in waiting BBS computers. When the machine enters the waiting state, almost all of its RAM is scanned by a routine which calculates a checksum and double checksum of the numbers the RAM contains. The checksum and double checksum are stored. At frequent intervals during the waiting state, the same area of RAM is scanned again. If the new values of the checksum or double checksum differ from the stored ones, the system attempts to find and fix a one-byte error. If, however, it finds that the discrepancies cannot be accounted for by an error in a single byte, it calls another routine which automatically re-boots the entire system from disk.

It is not possible, in a practical system, to include all of the computer's RAM in the scanned area. There are some bytes which are frequently changed during the normal operation of the machine, even in a waiting state. If these bytes were scanned, the changes in them would be in-

terpreted as soft failures, so the system would wrongly try to "fix" them. The small area of RAM in which the checksum and double checksum are calculated and stored must also be left out of the scanned area, since these operations would cause discrepancies for the next scan. Nevertheless, in the system I have implemented, more than 98% of the RAM is scanned, reducing the probability of a fatal soft failure by a factor of about fifty.

Machine Language

There are difficulties involved in writing a routine in BASIC to calculate a checksum and double checksum of the contents of memory. Such a routine would be very slow, taking several minutes to scan the RAM. Also, it would be difficult to make the scan exclude the RAM in which the checksum variables are calculated and stored by BASIC while still including the variables belonging to the main BBS program, which should be protected from soft failures. For these reasons and others, I decided to use machine language for the routine which calculates the checksums and corrects any errors.

In fact, in my system, the entire "wait for a phone call" program is in machine language and resides in an

EPROM. During the waiting state, the BASIC interpreter is not used at all. The machine is extremely insensitive to any changes in RAM, so soft failures are very unlikely to cause a crash. The program in EPROM alternates between two routines. For approximately one minute, one of these routines examines an input line for a signal which would indicate that the phone is ringing. If this signal is received, the routine branches back to BASIC and the main BBS program takes over. Otherwise, at the end of each minute, the memory-checking routine is called. This scans most of the RAM and responds to any errors, as described above. At the end of the memory check, the system goes back to the first routine. If the phone rings during the memory check, the caller has to wait until it is complete. This is not a significant problem, since the entire check takes less than two seconds at machine-language speed. The only circumstance in which a user would have to wait for a longer period is if the memory check shows a re-boot from disk to be necessary. This involves several minutes during which time the phone will not be answered. However, this is far preferable to the probable alternative: a complete crash of the BBS.

NEXT MONTH IN Electronics Today

Tools For Electronics

It's difficult to strip wire with a pair of scissors, even if we've all had to do it that way. A look at various tools and accessories that make life on the testbench a lot easier.

Build a Signal Generator

Using one of the readily available function generator chips, you can have a versatile sine-square-triangle unit for pennies. Well, a lot of pennies.

Direct Inject Box

Not what you think. It lets you match most electronic music instruments or gadgets to any mixer, deck or amplifier that might otherwise give you a hard time about impedances or levels.



For Subscription or Advertising Information Call (416) 423-3262

The Hardware

The memory-checking EPROMS have been installed in three identical microcomputers, aged but reliable Commodore PETs. Prior to this installation, the ROMs in these machines had already been modified in several ways to make them more suitable for running BBSs. For example, after power failures or if various error conditions occur, the modified operating systems in these machines cause the BBS to be automatically re-booted from disk and put online.

The machine language source code shown in the listing is, of course, specific to computers which use the 6502 microprocessor or other very closely related chips. Since many readers will not be interested in these particular machines, I do not intend to dwell on the details of the coding here. I should point out, however, that I have removed almost all coding which would work only on a PET. The original program, for example, contains Commodore-specific coding which prints a message on the screen if the memory-checker finds and corrects a one-byte error. This coding is not shown in the listing, so the program as printed will not indicate to its user that it has done a one-byte correction. The only coding

left in the listing which would not work on all types of 6502 machine is the jump to address \$C436 in line 960. In a normal PET, this jump would cause the machine to clear the stack and then to drop into direct mode with an "Out of Memory Error" message. (The fact that the stack is cleared explains why I have not troubled to ensure that this jump is made at any particular stack level.) The modified operating systems in the PETs which have actually been used with this routine do more. The exit to direct mode is automatically followed by a re-boot from disk. This is the route which is followed if the memory-checker finds a situation which indicates that more than one byte of RAM needs correction.

Results

The memory-checking EPROMs have been installed in the three BBS PETs for practical reasons. Like the other modified ROMs in the computers, they are intended to reduce the number of system crashes. They are not primarily intended to provide information to myself or to anyone else. If a one-byte error is corrected, a message appears on the screen which can be seen by anyone who happens to be present. However, in normal BBS operation,

this message soon scrolls off the screen and is permanently lost. If nobody is around when an error is automatically fixed, nobody ever knows about the event. Likewise, a re-boot from disk can pass unnoticed unless someone happens accidentally to observe it.

In their primary purpose, the EPROMs seem to be very successful. In approximately ten thousand machine-hours since they were installed, there have been no crashes of the systems in which they are fitted. Previous experience suggests that several crashes would have occurred in that much time without the modified ROMS.

Observed Events

On approximately twenty occasions, the computers have been observed to make corrections to their memories. Three of these occasions involved re-boots from disk; the remainder showed the screen message as single-byte errors were fixed. During the waiting state, a substantial portion of a BBS computer's memory does not contain useful information, so some of these corrections were probably made to errors which would not have proved fatal if they had been left unfixed. Nevertheless, the observed events support

This Month in

Computing! NOW!

Software Now!

Printers

A survey of what's available in the enormous printer market. Check out the best box for your hardcopy.

PC Time Bomb

A timer program for the PC: make the world's most expensive alarm clock.

Mac Fractals

A program to print fractals on the Macintosh. Fractals are, er, sort of imaginary complex numbers, and, ah... Well, it makes beautiful graphics.

MEX for CP/M

A modem executive program for CP/M that works like Modem-7 or other telecommunications packages, but adds lots of features.

Programming Languages

A look at the various languages available for the microcomputer: BASIC, LOGO, Pascal, Forth, etc.

Reviews

Turbo Pascal, ProDesign II, Da Vinci Graphics, Think Fast, Paper Clip and other applications and games software.

dBase II

How to debug dBase II to make it better suited to your needs, plus a dBase II programmer's guide.

For Subscription or Advertising Information Call (416) 423-3262

the idea that several crashes would have occurred if the error-fixing EPROMs had not been fitted.

The events which have observed have not occurred equally often in the three computers. One computer has not displayed any memory fixes. Four events have been observed in a second machine, including two of the three re-boots from disk. All of the remaining events, eighty percent of the total, have involved the third computer.

<pre> 100 *=\$7000 110 wkspc=\$20 120 permspc=\$83e9 130 ptr=\$5e 140 flg=\$83e8 150 quot=\$60 160 lopg=2 170 hipg=\$7f 180 erout=\$c436 200 strt lda #lopg 210 sta ptr+1 220 lda #0 230 sta ptr 240 tay 250 ldx #7 260 11 sta wkspc,x 270 dex 280 bpl 11 290 12 lda (ptr),y 300 clc 310 adc wkspc 320 sta wkspc 330 bcc p2 340 inc wkspc+1 350 bne p1 360 inc wkspc+2 370 p1 clc 390 p2 adc wkspc+3 400 sta wkspc+3 410 lda wkspc+1 420 adc wkspc+4 430 sta wkspc+4 440 lda wkspc+2 450 adc wkspc+5 460 sta wkspc+5 470 bcc p3 480 inc wkspc+6 490 bne p3 500 inc wkspc+7 510 p3 iny 520 bne 12 530 inc ptr+1 540 lda ptr+1 542 cmp #hipg+1 </pre>	<pre> 545 bne 12 550 ldx flg 560 beq p4 570 ldx #7 580 13 lda wkspc,x 590 sta permspc,x 600 dex 610 bpl 13 620 lda #0 630 sta flg 640 rts 650 p4 ldx #7 660 14 lda wkspc,x 670 cmp permspc,x 680 bne p5 690 dex 700 bpl 14 710 rts 720 p5 sec 730 ldx #0 740 ldy #8 750 15 lda permspc,x 760 sbc wkspc,x 770 sta wkspc,x 780 inx 790 dey 800 bne 15 810 lda wkspc 820 beq erex 830 pha 840 lda wkspc+1 850 cmp wkspc+2 860 bne erex 870 cmp wkspc+6 880 bne erex 890 cmp wkspc+7 900 bne erex 910 pha 920 cmp #\$ff 930 beq p6 940 cmp #0 950 beq p7 960 erex jmp erout 970 p6 ldx #7 980 16 lda #\$ff 990 eor wkspc,x 1000 sta wkspc,x 1010 dex 1020 bpl 16 1030 inc wkspc 1040 lda #0 1050 p7 sta quot 1060 sta quot+1 1070 ldx #24 1080 stx wkspc+1 </pre>	<pre> 1090 17 clc 1100 ldx #0 1110 ldy #5 1120 18 rol wkspc+3,x 1130 inx 1140 dey 1150 bne 18 1160 bcs erex 1170 lda wkspc+6 1180 sec 1190 sbc wkspc 1200 tax 1210 lda wkspc+7 1220 sbc #0 1230 bcc p8 1240 stx wkspc+6 1250 sta wkspc+7 1260 p8 rol quot 1270 rol quot+1 1280 bcs erex 1290 dec wkspc+1 1300 bne 17 1310 lda wkspc+6 1320 ora wkspc+7 1330 bne erex 1340 sec 1350 lda ptr 1360 sbc quot 1370 sta ptr 1380 lda ptr+1 1390 sbc quot+1 1400 cmp #hipg+1 1410 bcs erex 1415 cmp #lopg 1420 bcc erex 1430 sta ptr+1 1440 pla 1450 tax 1460 pla 1470 ldy #0 1480 clc 1490 adc (ptr),y 1500 pha 1510 txa 1520 adc #0 1530 bne erex 1540 pla 1550 sta (ptr),y 1560 rts </pre>
--	---	--

continued on page 33

BABANI BOOKS

Imported from England and exclusively available in Canada from Moorshead Publications.

BP53: PRACTICAL ELECTRONICS CALCULATIONS AND FORMULAE \$11.75
A book that bridges the gap between complicated technical theory and the 'cut and try' method. A good reference book.

BP136: 25 SIMPLE INDOOR AND WINDOW AERIALS \$6.65
People living in apartments who would like to improve short-wave listening can benefit from these instructions on optimising the indoor aerial.

BP147: AN INTRODUCTION TO 6502 MACHINE CODE \$7.75
The popular 6502 microprocessor is used in many home computers, this is a guide to beginning assembly language.

BP150: AN INTRO. TO PROGRAMMING THE SINCLAIR QL \$7.75
Helps the reader make the best use of the Sinclair QL's almost unlimited range of features. Complements the manufacturer's handbook.

BP225: A PRACTICAL INTRODUCTION TO DIGITAL ICs \$6.65
This book deals mainly with TTL type chips such as the 7400 series. Simple projects and a complete practical construction of a Logic Test Circuit Set are included as well as details for a more complicated Digital Counter Timer project.

BP130: MICRO INTERFACING CIRCUITS - BOOK 1 \$8.55
Aimed at those who have some previous knowledge of electronics, but not necessarily an extensive one, the basis of the book is to help the individual understand the principles of interfacing circuits to microprocessor equipment.

BP131: MICRO INTERFACING CIRCUITS - BOOK 2 \$8.55
Intended to carry on from Book 1, this book deals with practical applications beyond the parallel and serial interface "Real world" interfacing such as sound and speech generators, temperature and optical sensors, and motor controls are discussed using practical circuit descriptions.

BP111: AUDIO \$13.25
This one is ideal for readers who want to really get into sound. A wide range of material is covered from analysis of the sound wave, mechanisms of hearing, room acoustics, microphones and loudspeakers, amplifiers, and magnetic disc recording.


BP82: ELECTRONIC PROJECTS USING SOLAR CELLS \$7.75
A collection of simple circuits which have applications in and around the home using the energy of the sun to power them. The book deals with practical solar power supplies including voltage doubler and tripler circuits, as well as a number of projects.

BP156: AN INTRODUCTION TO QL MACHINE CODE \$7.75
The powerful Sinclair QL microcomputer has some outstanding capabilities in terms of its internal structure. With a 32-bit architecture, the QL has a large address range, advanced instructions which include multiplication and division. These features give the budding machine code programmer a good start at advanced programming methods. This book assumes no previous knowledge of either the 68000 or machine code programming.

BP47: MOBILE DISCOTHEQUE HANDBOOK \$5.25
Divided into six parts, this book covers such areas of mobile "disco" as Basic Electricity, Audio, Ancillary Equipment, Cables and Plugs, Loudspeakers, and Lighting. All the information has been considerably sub-divided for quick and easy reference.

BP59: SECOND BOOK OF CMOS IC PROJECTS \$7.75
This book carries on from its predecessor and provides a further selection of useful circuits, mainly of a simple nature the book will be well within the capabilities of the beginner and more advanced constructor.

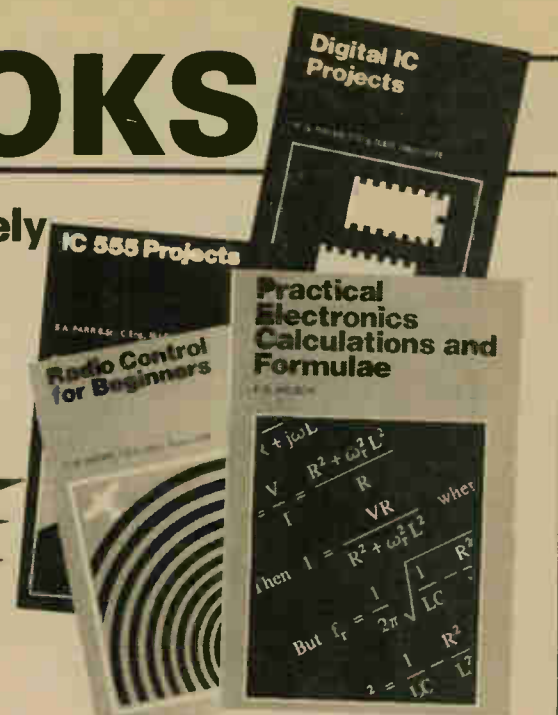BP32: HOW TO BUILD YOUR OWN METAL & TREASURE LOCATORS \$7.75
Several fascinating applications with complete electronic and practical details on the simple, and inexpensive construction of Heterodyne Metal Locators.



ELECTRONIC THEORY

ELEMENTS OF ELECTRONICS - AN ON-GOING SERIES

- F.A. WILSON, C.G.I.A., C.Eng.
- 8P62: BOOK 1. The Simple Electronic Circuit and Components \$11.70
 - BP63: BOOK 2. Alternating Current Theory \$ 8.55
 - BP64: BOOK 3. Semiconductor Technology \$18.55
 - BP77: BOOK 4. Microprocessing Systems And Circuits \$11.70
 - BP89: BOOK 5. Communication \$11.70

The aim of this series of books can be stated quite simply - it is to provide an inexpensive introduction to modern electronics so that the reader will start on the right road by thoroughly understanding the fundamental principles involved.

Although written especially for readers with no more than ordinary arithmetical skills, the use of mathematics is not avoided, and all the mathematics required is taught as the reader progresses.

Each book is a complete treatise of a particular branch of the subject and, therefore, can be used on its own with one proviso: that the later books do not duplicate material from their predecessors, thus a working knowledge of the subjects covered by the earlier books is assumed.

BOOK 1. This book contains all the fundamental theory necessary to lead to a full understanding of the simple electronic circuit and its main components.

BOOK 2. This book continues with alternating current theory without which there can be no comprehension of speech music, radio television or even the electricity utilities.

BOOK 3. Follows on semiconductor technology, leading up to transistors and integrated circuits.

BOOK 4. A complete description of the internal workings of microprocessor.

BOOK 5. A book covering the whole communication scene.

PROJECTS

BP48: ELECTRONIC PROJECTS FOR BEGINNERS \$ 7.75
F.G. RAYER, T.Eng.(CEI), Assoc.IERE

Another book written by the very experienced author - Mr F.G. Rayer - and in it the newcomer to electronics will find a wide range of easily made projects. Also, there are a considerable number of actual component and wiring layouts, to aid the beginner.

Furthermore, a number of projects have been arranged so that they can be constructed without any need for soldering and thus avoid the need for a soldering iron.

Also, many of the later projects can be built along the lines as those in the 'No Soldering' section so this may considerably increase the scope of projects which the newcomer can build and use.

BP37: 50 PROJECTS USING RELAYS, SCRs & TRIACS \$ 7.75
F.G. RAYER, T.Eng.(CEI), Assoc.IERE

Relays, silicon controlled rectifiers (SCRs) and bidirectional triodes (TRIACs) have a wide range of applications in electronics today. This book gives tried and practical working circuits which should present the minimum of difficulty for the enthusiast to construct. In most of the circuits there is a wide latitude in component values and types allowing easy modification of circuits or ready adaptation of them to individual needs.

BP221: 28 TESTED TRANSISTOR PROJECTS \$5.00
R. TORRENS

Mr Richard Torrens is a well experienced electronics development engineer and has designed, developed, built and tested the many useful and interesting circuits included in this book. The projects themselves can be split down into simpler building blocks, which are shown separated by boxes in the circuits for ease of description, and also to enable any reader who wishes to combine boxes from different projects to realise ideas of his own.

BP71: ELECTRONIC HOUSEHOLD PROJECTS \$ 7.20
R. A. PENFOLD

Some of the most useful and popular electronic construction projects are those that can be used in or around the home. The circuits range from such things as 2 Tone Door Buzzer, Intercom, through Smoke or Gas Detectors to Baby and Freezer Alarms.

BP73: REMOTE CONTROL PROJECTS \$ 8.10
OWEN BISHOP

This book is aimed primarily at the electronics enthusiast who wishes to experiment with remote control. Full explanations have been given so that the reader can fully understand how the circuits work and can more easily see how to modify them for other purposes depending on personal requirements. Not only are radio control systems considered but also infra red, visible light and ultrasonic systems as are the use of Logic ICs and Pulse position modulation etc.

BP90: AUDIO PROJECTS \$ 7.60
F.G. RAYER

Covers in detail the construction of a wide range of audio projects. The text has been divided into pre-amplifiers and mixers, power amplifiers, tone controls and matching and miscellaneous projects.

BP74: ELECTRONIC MUSIC PROJECTS \$ 7.20
R.A. PENFOLD

Although one of the more recent branches of amateur electronics, electronic music has now become extremely popular and there are many projects which fall into this category. The purpose of this book is to provide the constructor with a number of practical circuits for the less complex items of electronic music equipment including such things as a Fuzz Box, Waa-Waa Pedal, Sustain Unit, Reverberation and Phaser Units, Tremolo Generator etc.

BP44: IC 555 PROJECTS \$ 7.75
E.A. PARR, B.Sc., C.Eng., M.I.E.E.

Every so often a device appears that is so useful that one wonders how life went on before without it. The 555 timer is such a device. Included in this book are Basic and General Circuits, Motor Car and Model Railway Circuits, Alarms and Noise Makers as well as a section on the 556, 558 and 559 timers.

BABANI BOOKS

BP49: POPULAR ELECTRONIC PROJECTS \$7.75

R.A. PENFOLD
Includes a collection of the most popular types of circuits and projects which, we feel sure, will provide a number of designs to interest most electronics constructors. The projects selected cover a very wide range and are divided into four basic types: Radio Projects, Audio Projects, Household Projects and Test Equipment

BP94: ELECTRONIC PROJECTS FOR CARS AND BOATS \$7.60

R.A. PENFOLD
Projects, fifteen in all, which use a 12V supply are the basis of this book. Included are projects on Windscreen Wiper Control, Courtesy Light Delay, Battery Monitor, Cassette Power Supply, Lights Timer, Vehicle Immobiliser, Gas and Smoke Alarm, Depth Warning and Shaver Inverter

BP95: MODEL RAILWAY PROJECTS \$7.60

Electronic projects for model railways are fairly recent and have made possible an amazing degree of realism. The projects covered include controllers, signals and sound effects stripboard layouts are provided for each project

BP93: ELECTRONIC TIMER PROJECTS \$7.60

F.G. RAYER
Windscreen wiper delay, darkroom timer and metronome projects are included. Some of the more complex circuits are made up from simpler sub-circuits which are dealt with individually

BP113: 30 Solderless Breadboard Projects-Book 2 \$8.85

R.A. Penfold
A companion to BP107. Describes a variety of projects that can be built on plug-in breadboards using CMOS logic IC's. Each project contains a schematic, parts list and operational notes.

BP104: Electronic Science Projects \$8.85

Owen Bishop
Contains 12 electronic projects with a strong scientific flavour. Includes Simple Colour Temperature Meter, Infra-Red Laser, Electronic clock regulated by a resonating spring, a Scope with a solid state display, pH meter and electrocardiograph.

BP110: HOW TO GET YOUR ELECTRONIC PROJECTS WORKING \$7.60

R.A. PENFOLD
We have all built circuits from magazines and books only to find that they did not work correctly, or at all, when first switched on. The aim of this book is to help the reader overcome just these problems by indicating how and where to start looking for many of the common faults that can occur when building up projects

BP84: DIGITAL IC PROJECTS \$7.60

F.G. RAYER, T.Eng.(CEI), Assoc.IERE
This book contains both simple and more advanced projects and it is hoped that these will be found of help to the reader developing a knowledge of the workings of digital circuits. To help the newcomer to the hobby the author has included a number of board layouts and wiring diagrams. Also the more ambitious projects can be built and tested section by section and this should help avoid or correct faults that could otherwise be troublesome. An ideal book for both beginner and more advanced enthusiast alike

BP67: COUNTER DRIVER AND NUMERAL DISPLAY PROJECTS \$7.05

F.G. RAYER, T.Eng.(CEI), Assoc. IERE
Numeral indicating devices have come very much to the forefront in recent years and will, undoubtedly, find increasing applications in all sorts of equipment. With present day integrated circuits, it is easy to count, divide and display numerically the electrical pulses obtained from a great range of driver circuits

In this book many applications and projects using various types of numeral displays, popular counter and driver IC's etc. are considered.

BP99: MINI - MATRIX BOARD PROJECTS \$7.60

R.A. PENFOLD
Twenty useful projects which can all be built on a 24 x 10 hole matrix board with copper strips. Includes Doorbuzzer, Low-voltage Alarm, AM Radio, Signal Generator, Projector Timer, Guitar Headphone Amp, Transistor Checker and more

BP103: MULTI-CIRCUIT BOARD PROJECTS \$7.60

R.A. PENFOLD
This book allows the reader to build 21 fairly simple electronic projects, all of which may be constructed on the same printed circuit board. Wherever possible, the same components have been used in each design so that with a relatively small number of components and hence low cost, it is possible to make any one of the projects or by re-using the components and P.C.B. all of the projects

BP107: 30 SOLDERLESS BREADBOARD PROJECTS - BOOK 1 \$8.85

R.A. PENFOLD
A "Solderless Breadboard" is simply a special board on which electronic circuits can be built and tested. The components used are just plugged in and unplugged as desired. The 30 projects featured in this book have been specially designed to be built on a "Verobloc" breadboard. Wherever possible the components used are common to several projects, hence with only a modest number of reasonably inexpensive components it is possible to build, in turn, every project shown

BP106: MODERN OP-AMP PROJECTS \$7.60

R.A. PENFOLD
Features a wide range of constructional projects which make use of op-amps including low-noise, low distortion, ultra-high input impedance, high slew-rate and high output current types

CIRCUITS

How to Design Electronic Projects

BP127 \$8.95
Although information on standard circuit blocks is available, there is less information on combing these circuit parts together. This title does just that. Practical examples are used and each is analysed to show what each does and how to apply this to other designs.

Audio Amplifier Construction

BP122 \$8.95
A wide circuits is given, from low noise microphone and tape head preamps to a 100W MOSFET type. There is also the circuit for 12V bridge amp giving 18W. Circuit board or strip-board layout are included. Most of the circuits are well within the capabilities for even those with limited experience

BP80: POPULAR ELECTRONIC CIRCUITS - BOOK 1 \$7.75

R.A. PENFOLD
Another book by the very popular author, Mr. R.A. Penfold, who has designed and developed a large number of various circuits. These are grouped under the following general headings: Audio Circuits, Radio Circuits, Test Gear Circuits, Music Project Circuits, Household Project Circuits and Miscellaneous Circuits

BP98: POPULAR ELECTRONIC CIRCUITS, BOOK 2 \$8.85

R.A. PENFOLD
70 plus circuits based on modern components aimed at those with some experience

BP39: 50 (FET) FIELD EFFECT TRANSISTOR PROJECTS \$6.75

F.G. RAYER, T.Eng.(CEI), Assoc.IERE
Field effect transistors (FETs) find application in a wide variety of circuits. The projects described here include radio frequency amplifiers and converters, test equipment and receiver aids, tuners, receivers, mixers and tone controls, as well as various miscellaneous devices which are useful in the home

This book contains something of particular interest for every class of enthusiast - short wave listener, radio amateur, experimenter or audio devotee

BP87: SIMPLE L.E.D. CIRCUITS \$5.40

R.N. SOAR
Since it first appeared in 1977, Mr. R.N. Soar's book has proved very popular. The author has developed a further range of circuits and these are included in Book 2. Projects include a Transistor Tester, Various Voltage Regulators, Testers and so on

BP24: 50 PROJECTS USING IC 741 \$6.75

A unique book containing 52 different projects that can be simply constructed using the 741 op amp and a few components. Originally published in Germany, this book will be an valuable asset to any hobbyist

BP88: HOW TO USE OP AMPS \$8.85

E.A. PARR
A designer's guide covering several op amps, serving as a source book of circuits and a reference book for design calculations. The approach has been made as non-mathematical as possible

BP65: SINGLE IC PROJECTS \$6.05

R.A. PENFOLD
There is now a vast range of ICs available to the amateur market, the majority of which are not necessarily designed for use in a single application and can offer unlimited possibilities. All the projects contained in this book are simple to construct and are based on a single IC. A few projects employ one or two transistors in addition to an IC but in most cases the IC is the only active device used

223: 50 PROJECTS USING IC CA3130 \$5.00

R.A. PENFOLD
In this book, the author has designed and developed a number of interesting and useful projects which are divided into five general categories: I - Audio Projects II - R.F. Projects III - Test Equipment IV - Household Projects V - Miscellaneous Projects

BP117: PRACTICAL ELECTRONIC BUILDING BLOCKS BOOK 1 \$7.60

Virtually any electronic circuit will be found to consist of a number of distinct stages when analysed. Some circuits inevitably have unusual stages using specialised circuitry, but in most cases circuits are built up from building blocks of standard types

This book is designed to aid electronics enthusiasts who like to experiment with circuits and produce their own projects rather than simply follow published project designs

The circuits for a number of useful building blocks are included in this book. Where relevant, details of how to change the parameters of each circuit are given so that they can easily be modified to suit individual requirements

BP102: THE 6809 COMPANION \$7.60

Written for machine language programmers who want to expand their knowledge of microprocessors. Outlines history, architecture, addressing modes, and the instruction set of the 6809 microprocessor. The book also covers such topics as converting programs from the 6800, program style, and specifics of 6809 hardware and software availability

BP118: PRACTICAL ELECTRONIC BUILDING BLOCKS - Book 2 \$7.60

R.A. PENFOLD
This sequel to BP117 is written to help the reader create and experiment with his own circuits by combining standard type circuit building blocks. Circuits concerned with generating signals were covered in Book 1, this one deals with processing signals. Amplifiers and filters account for most of the book but comparators, Schmitt triggers and other circuits are covered

BP24: 50 PROJECTS USING IC741 \$6.75

RUDI & UWE REDMER
This book, originally published in Germany by TOPP, has achieved phenomenal sales on the Continent and Babani decided, in view of the fact that the integrated circuit used in this book is inexpensive to buy, to make this unique book available to the English speaking reader. Translated from the original German with copious notes, data and circuitry, a "must" for everyone whatever their interest in electronics

BP83: VMOS PROJECTS \$7.70

R.A. PENFOLD
Although modern bipolar power transistors give excellent results in a wide range of applications, they are not without their drawbacks or limitations. This book will primarily be concerned with VMOS power FETs although power MOSFETs will be dealt with in the chapter on audio circuits. A number of varied and interesting projects are covered under the main headings of: Audio Circuits, Sound Generator Circuits, DC Control Circuits and Signal Control Circuits

RADIO AND COMMUNICATIONS

BP96: CB PROJECTS \$7.60

R.A. PENFOLD
Projects include speech processor, aerial booster, cordless mike, aerial and harmonic filters, field strength meter, power supply, CB receiver and more

BP222: SOLID STATE SHORT WAVE RECEIVER FOR BEGINNERS \$47.60

R.A. PENFOLD
In this book, R.A. Penfold has designed and developed several modern solid state short wave receiver circuits that will give a fairly high level of performance, despite the fact that they use only relatively few and inexpensive components

BP91: AN INTRODUCTION TO RADIO DXing \$7.60

This book is divided into two main sections: one to amateur band reception, the other to broadcast bands. Advice is given to suitable equipment and techniques. A number of related constructional projects are described

BP105: AERIAL PROJECTS \$7.60

R.A. PENFOLD
The subject of aerials is vast but in this book the author has considered practical designs including active, loop and ferrite aerials, which give good performances and are reasonably simple and inexpensive to build. The complex theory and math of aerial design are avoided

OTHER PUBLISHERS

PH121: HARDWARE INTERFACING WITH THE TRS-80
J. UFFENBECK (1983) \$19.45
 TRS-80 Model I and Model III owners now have a book to help them understand how to use their personal computers to monitor and control electronics interfaces between the computer and the home or industrial environment. Contains 14 hands-on experiments using BASIC.

SB22026 POLISHING YOUR APPLE® \$7.45
 Clearly written, highly practical, concise assembly of all procedures needed for writing, disk-filing, and printing programs with an Apple II. Positively ends your searches through endless manuals to find the routine you need! Should be in the hands of every new Apple user, regardless of experience level. Ideal for Apple classrooms too!

A BEGINNER'S GUIDE TO COMPUTERS AND MICROPROCESSORS — WITH PROJECTS.

TAB No. 1015: \$14.45
 Here's plain English introduction to the world of microcomputers — it's capabilities, parts and functions — and how you can use one. Numerous projects demonstrate operating principles and lead to the construction of an actual working computer capable of performing many useful functions.

TAB1370: A MASTER HANDBOOK OF IC CIRCUITS \$21.95
 A circuit for every occasion. You'll find all the circuits you're looking for in this 532 page volume. The 932 circuits are broken down according to specific functions and in six categories. It's literally a cornucopia of ideas, projects, and designs that you can build now.

TAB1544: ELECTRONIC PROJECTS FOR PHOTOGRAPHERS \$21.95

This book gives you needed tips on the principles of electronics and building techniques, hints on how to set up a work area, and much more. Build all kinds of practical accessories for your camera, studio, or darkroom with this helpful guide.

SB22361: INTRODUCING THE APPLE MACINTOSH \$20.95

A wealth of information on hardware, software etc for the Mac. Included are such topics as making your desktop more efficient, improving your productivity with the Mac, getting the most from your mouse, how the 68000 microprocessor works and much, much more.

PH131: ZAP! POW! BOOM! ARCADE GAMES FOR THE VIC 20

T. HARTNELL & M. RAMSHAW (1983) \$17.45
 Move through the maze eating dots with MAZEMAN. Sail through space zapping the ASTROIDS. Outshoot the fastest draw in town GUNFIGHT. Owners of the VIC 20 can now play these games — and more — simply by following the programs outlined in this handy guide.

THE BASIC COOKBOOK. TAB No. 1055: \$10.45

BASIC is a surprisingly powerful language... if you understand it completely. This book picks up where most manufacturers' documentation gives up. With it, any computer owner can develop programs to make the most out of his or her machine.

HANDBOOK OF MICROPROCESSOR APPLICATIONS TAB No. 1203 \$16.45

Highly recommended reading for those who are interested in microprocessors as a means of accomplishing a specific task. The author discusses two individual microprocessors, the 1802 and the 6800, and how they can be put to use in real world applications.

MICROPROCESSOR INTERFACING HANDBOOK: A/D & D/A TAB No. 1271 \$16.45

A useful handbook for computerists interested in using their machine in linear applications. Topics discussed include voltage references, op-amps for data conversion, analogue switching and multiplexing and more.

HOW TO BUILD YOUR OWN WORKING MICROCOMPUTER TAB No. 1200 \$16.45

An excellent reference or how-to manual on building your own microcomputer. All aspects of hardware and software are developed as well as many practical circuits.

PH180: 1984 CANADIAN BUSINESS GUIDE TO MICROCOMPUTERS K. DORRICO \$11.95

Written by the managing director of Deloitte, Haskins & Sells, a Canadian partnership of public accountants and other professional advisors to management, this book is one of the most complete comprehensive guides to microcomputers available. Starting with a general overview of microcomputers and their business applications, the author helps you assess your computer needs, compares and evaluates computer systems and application packages, and gives you tips on "doing it right". A must for anyone thinking of purchasing a microcomputer for business.

COMPUTER PROGRAMS IN BASIC AB01 \$15.45

A catalogue of over 1,600 fully indexed BASIC computer programs with applications in Business, Math, Games and more. This book lists available software, what it does, where to get it, and how to adapt it to your machine.

PH217: BASIC COMPUTER PROGRAMMING FOR KIDS P. CASSIDY & J. CLOSE \$16.45

Fully illustrated with photographs and drawings, this book teaches the reader the history of computers and computing and gently introduces binary mathematics and the basic theory of how computers work. Written in an easy, conversational tone.

PH51: PASCAL FOR THE APPLE IAIN MacCALLUM \$34.20

A step-by-step introduction to Pascal for Apple II and Apple II Plus users. The package of text and software diskette provides readers with worthwhile and interesting programs which can be run immediately and the results studied. Includes over 200 exercises with full solutions. Book/Disk Package.

PH52: APPLE GRAPHICS GAMES PAUL COLLETTA \$40.95

Contains 10 arcade-style games written especially for Apple II, including Spider, Piano, Pairs and Poker, as well as education, math, and designing games. Book/Disk Package.

PH53: START WITH BASIC FOR THE COMMODORE VIC 20 D. MONRO \$33.45

This book/cassette package shows the reader how easy it really is to create programs using the full capacity of the machine. Includes helpful exercises and step-by-step instructions to put the full power of the VIC 20 at the user's fingertips. Book/Cassette Package.

SB21822: ENHANCING YOUR APPLE® II — VOLUME 1 D. LANCASTER \$25.50

Who but Mother Nature or Don Lancaster could successfully enhance an Apple? YOU can, with help from Volume 1 in Don's newest series for Sams. Among other things, you'll learn (1) to mix text, LORES, and HIREX together anywhere on the screen in any combination, (2) how to make a new-wire modification that will open up whole new worlds of 3-D graphics and other special effects, plus (3) a fast and easy way to tear apart and understand somebody else's machine-language program. Other goodies abound!

PH106: PROGRAMMING TIPS AND TECHNIQUES FOR THE APPLE II J. CAMPBELL (1983) \$23.45

An advanced exploration of the intricacies of structures programming. Further develops the skills necessary to solve programming problems. Special chapter on sound and graphics which discusses both high and low resolution graphics for the Apple II.

HB131: THE BEGINNER'S GUIDE TO BUYING A PERSONAL COMPUTER \$6.45

Written for the potentially interested computer buyer, in non-technical language, this affordable book explains the terminology of personal computers, the problems and variables to be discussed and discovered while making that initial buying decision. The book does not make recommendations, but does present a great deal of information about the range of hardware available from the largest personal computing manufacturers. Readers discover the meaning and impact of screen displays, tape cassette storage and disk storage, graphics and resolution, and much more. Comparison charts clearly define standard and optional features of all the current mass market personal computers.

DESIGNING MICROCOMPUTER SYSTEMS HB18: \$18.95

This book provides both hobbyists and electronic engineers with the background information necessary to build microcomputer systems. It discusses the hardware aspects of microcomputer systems. Timing devices are provided to explain sequences of operations in detail. Then, the book goes on to describe three of the most popular microcomputer families, the Intel 8080 Zilog Z-80, and Motorola 6800. Also covered are designs of interfaces for peripheral devices, and information of building microcomputer systems from kits.

S100 BUS HANDBOOK HB19: \$26.00

Here is a comprehensive book that exclusively discusses S-100 bus computer systems and how they are organized. The book covers computer fundamentals, basic electronics, and the parts of the computer. Individual chapters discuss the CPU, memory, input/output, bulk-memory devices, and specialized peripheral controllers. It explains all the operating details of commonly available S-100 systems. Schematic drawings.

110 THYRISTOR PROJECTS USING SCRs AND TRIACS MARSTON HB22 \$13.45

A grab bag of challenging and useful semiconductor projects for the hobbyist, experimenter, and student. The project range from simple burglar, fire, and water level alarms to sophisticated power control devices for electric tools and trains. Integrated circuits are incorporated wherever their use reduces project costs.

PH104: ACCOUNTANT'S BASIC PROGRAMMING FOR THE APPLE II A PARKER & J. STEWART (1983) \$20.45

Shows the reader how to program the Apple II to perform a variety of accounting functions, such as payroll, accounts payable, accounts receivable, tax, inventory, customer statements, and more.

HOW TO PROFIT FROM YOUR PERSONAL COMPUTER: PROFESSIONAL, BUSINESS, AND HOME APPLICATIONS LEWIS HB01 \$18.95

Describes the uses of personal computers in common business applications, such as accounting managing, inventory, sorting mailing lists, and many others. The discussion includes terms, notations, and techniques commonly used by programmer's. A full glossary of terms.

AN INTRODUCTION TO MICROPROCESSORS EXPERIMENTS IN DIGITAL TECHNOLOGY HB07 \$18.95

A "learn by doing" guide to the use of integrated circuits provides a foundation for the underlying hardware actions of programming statements. Emphasis is placed on how digital circuitry compares with analog circuitry. Begins with the simplest gates and timers, then introduces the fundamental parts of ICs, detailing the benefits and pitfalls of major IC families, and continues with coverage of the ultimate in integrated complexity — the microprocessor.

MICROCOMPUTERS AND THE 3 R'S DOERR HB09 \$16.45

This book educates educators, on the various ways computers, especially microcomputers, can be used in the classroom. It describes microcomputers, how to organize a computer-based program, the five instructional application types (with examples from subjects such as the hard sciences, life sciences, English, history, and government), and resources listings of today's products. The book includes preprogrammed examples to start up a microcomputer program, while chapters on resources and products direct the reader to useful additional information. All programs are written in the BASIC language.

HB107: GRAPHICS COOKBOOK FOR THE APPLE WADSWORTH HB107 \$15.95

Learn how to use your Apple II to "paint" shapes, objects, and letters in low-resolution graphics. The author provides a library of microcomputer graphics including such multicolored illustrations as robots and flying saucers, trees, sailboats, and colourful picture backgrounds. Contains complete annotated Applesoft BASIC programs to draw all the pictures described in the book as well as suggestions for improving programming techniques.

HB116: THE BASIC CONVERSIONS HANDBOOK FOR APPLEII, TRS-80™, and PET™ USERS BRAIN BANK \$14.50

A complete guide to converting Apple II and PET programs to TRS-80, TRS-80 and PET programs to Apple II, and TRS-80 and Apple II programs to PET. Equivalent commands are listed for TRS-80 BASIC (Model I, Level II), Applesoft BASIC and PET BASIC, as well as variations for TRS-80 Model III and Apple Integer BASIC. Also describes variations in graphics capabilities.

SARGON: A COMPUTER CHESS PROGRAM SPRACKLEN HB12 \$27.50

"I must rate this chess program an excellent buy for anyone who loves the game." Kilobaud

Here is the computer chess program that won first place in the first chess tournament at the 1978 West Coast Computer Faire. It is written in Z-80 assembly language, using the TDL macro assembler. It comes complete with block diagram and sample printouts.

BASIC COMPUTER PROGRAMS FOR BUSINESS: STERNBERG (Vol. 1) HB13 \$21.50

A must for small businesses utilizing micros as well as for entrepreneurs, volume provides a wealth of practical business applications. Each program is documented with a description of its functions and operation, a listing in BASIC, a symbol table, sample data, and one or more samples.

AUDIO AND VIDEO INTERFERENCE CURES KAHANER HB21 \$8.95

A practical work about interference causes and cures that affect TV, radio, hi-fi, CB, and other devices. Provides all the information needed to stop interference. Schematic wiring diagrams of filters for all types of receivers and transmitters are included. Also, it supplies simple filter diagrams to eliminate radio and TV interference caused by noisy home appliances, neon lights, motors, etc.

PH107: APPLE LOGO PRIMER G. BITTER & N. WATSON (1983) \$19.95

A pictorial starter book that will make LOGO easy for anyone. Includes easy to follow examples and reference tables. Also included is a workshop outline for teachers and leaders who want to train others.

SB22047: 26 BASIC PROGRAMS FOR YOUR MICRO \$17.45

Features 26 previously unpublished, simple-to-complex games you can run on almost any brand of microcomputer as long as you have enough RAM on board. Most take between 500 and 5000 bytes, with the highest taking 13K. Conversion charts that let you key them into your Radio Shack, TRS-80, Apple II, Timex/Sinclair 1000 (ZX81), Spectrum, Atari, or PET are included. Also features notes on program techniques and structures.

Large Digital Scoreboard

Do your achievements go unnoticed? Build this big, bright display board and make sure that everyone knows the score.

By Ken Wood

THIS SCOREBOARD has been designed for use in a gymnasium or other large area and uses regular light bulbs to provide a large, bright display easily visible from a distance. The scores or other numerical information are normally entered from thumbwheel switches but the system could also be adapted to accept data from a microcomputer. The basic model has a four digit display which could be used to show a two-digit score for each of two teams, but the number of digits can easily be increased to suit other applications.

The Circuit

The heart of this project is a digit driver module. This uses a 7447A, BCD to seven segment decoder, to drive a digit composed of regular 15W decorator light bulbs via seven triacs. The BCD information is fed serially through a shift register, and used to drive the display.

One module is used per digit in the display, and they are chained together so that they form a long shift register of four bits per digit. The control logic is isolated from the 120V line by an opto-isolator module at the start of the chain, and only one of these is needed for the display.

Third module is a power supply. This provides two separate 5V supplies, one for the circuitry in the display drivers and the other for circuitry isolated from the 120V supply by the opto-isolator module. The supplies shown only offer up to 100mA, so for displays with lots of digits a different regulator may be needed.

Finally there is a controller module. This takes data from up to four thumbwheel switches and turns it into a serial stream to send to the display drivers. It also takes 120V zero crossing pulses from the power supply and uses them to time the serial transmission. This allows the display to be updated while the displays are off at the zero crossing point of the AC cycle.

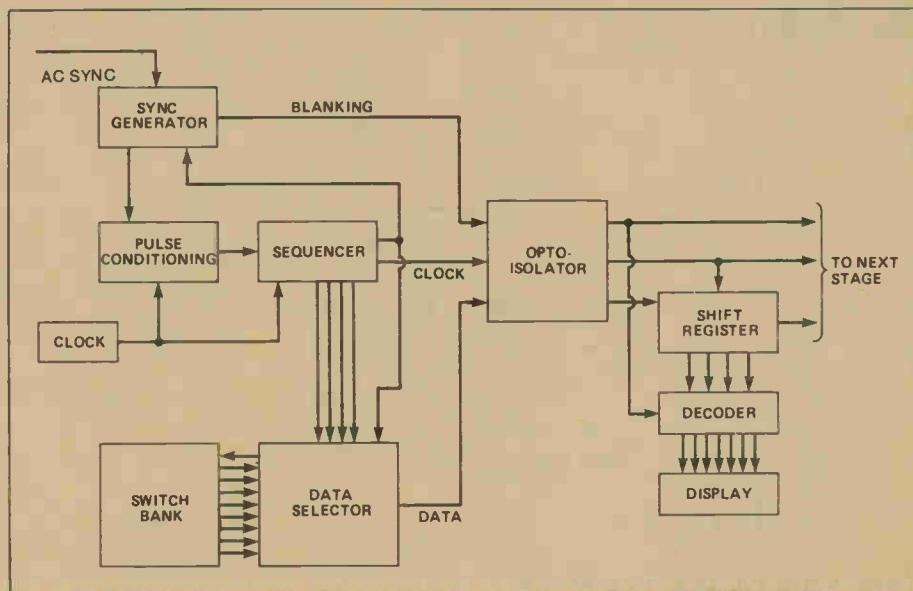


Fig. 1 Block diagram of the complete system.

How it Works

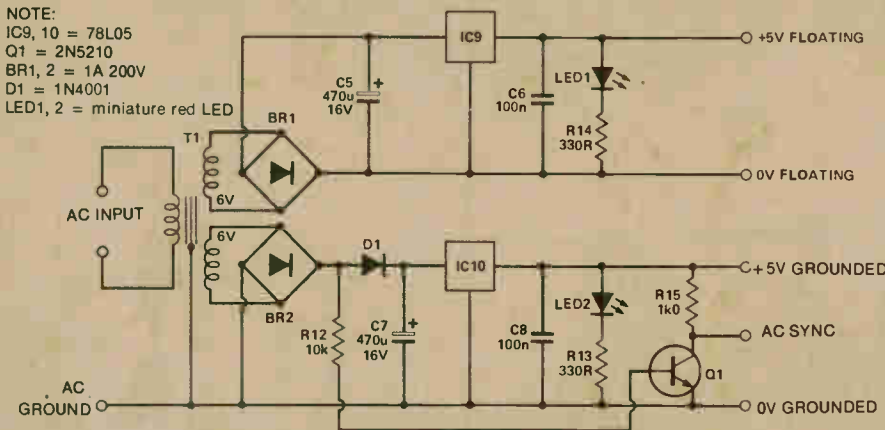


Fig. 2 Circuit diagram of the power supply. Note the use of separate grounded and floating +5v supplies. The controller operates from the grounded supply.

The power supply is in two sections, each of which has a bridge rectifier and a smoothing capacitor followed by a voltage regulator (ICs 9 and 10). C6 and C8 cut out any high frequency spikes and protect the regulators from oscillation. Each section is also fitted with an LED and current limiting resistor as a visual check of operation.

The section that supplies power to the control electronics has its 0V connected to ground as a safety precaution, and also provides AC sync pulses to the controller module. The bridge rectifier BR2 is isolated from the smoothing capacitor with a diode D1, so full wave rectified AC waveform ap-

pears at the junction between D1 and R12. This is fed to TR1, which is driven hard on for all but the brief interval when the waveform is at less than 0.7V, 100 times a second.

The AC sync pulses are not necessarily at the zero crossing point of the AC because of the phase shifts that can occur through the transformer. To overcome this, they are fed into a monostable IC1a which is trimmed so that its output is truly at the AC zero crossing point. This is fed into a second monostable whose output is gated with the controller blanking output to hold the triacs off for a period into the AC half cy-

cle. This achieves the dimming function.

IC2a, 2b, and 3a produce a square wave clock at about 50KHz. It is also used to control the operation of the remainder of the module.

IC4a, 4b, and 6a produce a pulse lasting for exactly one clock period at each AC crossing. This is used to reset IC7, a four bit counter. The counter controls IC8, an eight input multiplexer, to sequence through the bit inputs from the thumbwheel switches. Output D from the counter selects one switch bank or the other via IC2d.

When the counter reaches 15 the carry output goes high and the counter is inhibited via IC2e. This means that after each AC zero crossing, the data bits from the thumbwheel switches appear in turn at the serial data output and via IC2f and 5c at the shift data output to the digit drivers.

The beginning and end of this sequence is detected by IC3b which produces an envelope signal while data is coming out of the controller. The signal is made available to an external controller via IC6, and also gates the shift data and shift clock outputs to the digit drivers. It is also fed into the blanking signal so that, even with a very short period set for the monostable IC1b, the triacs cannot come on while data is being transmitted.

The three control signals connected to the digit drivers are fed through an opto-isolator circuit to prevent any AC potentials from reaching the control circuits, thereby making the unit completely safe for connection to a home computer for example.

Each of the three channels is identical, so reference will be made to one channel only. An emitter-follower transistor Q2 drives the LED in the opto-isolator IC11. The opto-isolator transistor, biased by R19 to improve its high frequency response, is buffered by a Schmitt trigger (IC14a and R25), and a final output buffer IC14b drives the output.

IC15 is a four bit shift register, which converts the serial data to parallel at its outputs. The fourth output passes serial data on to the next driver module in the chain, thus with four digit drivers each gets its new data after sixteen clocks. The parallel BCD data is decoded by IC16 to form the segment drive to each of seven triacs.

The blanking signal drives Q5 which switches off the outputs of IC16, preventing the possibility of a digit being displayed while the shifting process goes on and allowing the display to be dimmed.

continued on next page

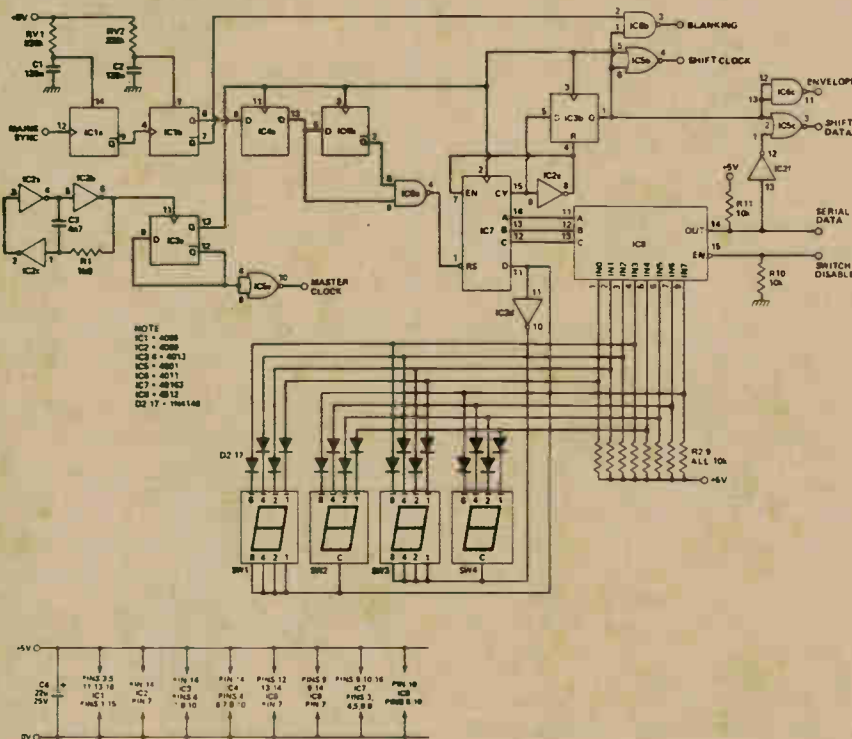


Fig. 3 Circuit details for the controller.


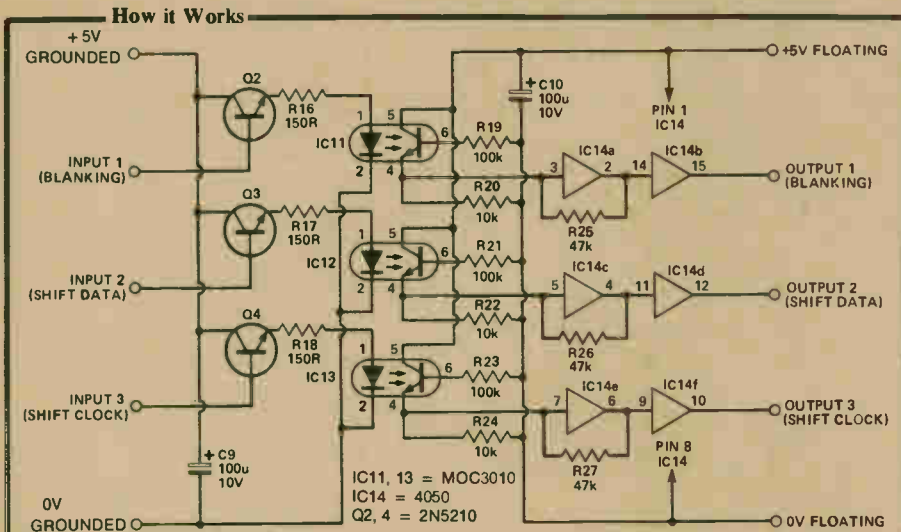


Fig. 4 Circuit of the optoisolator module.

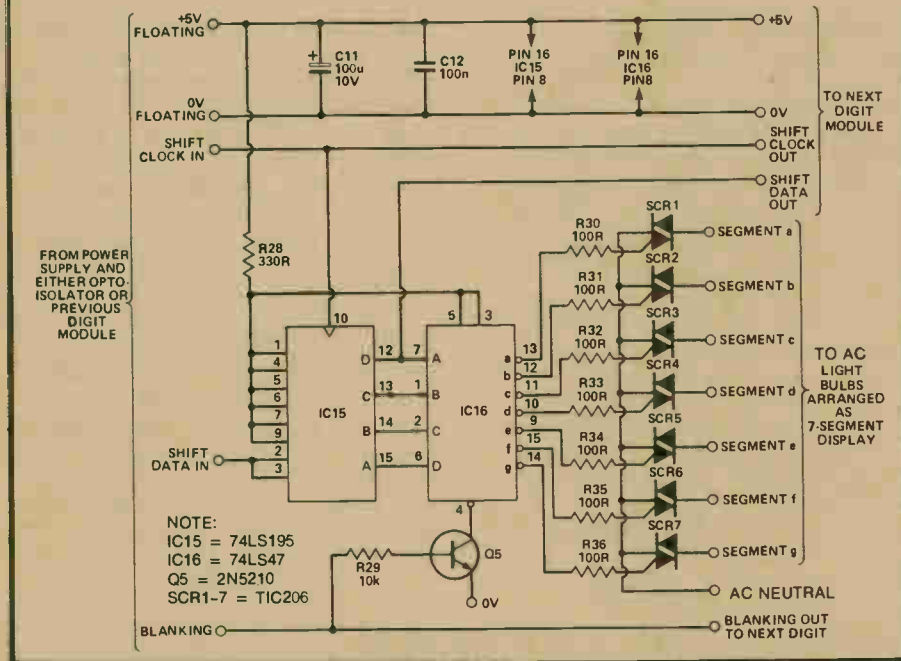

NOTE:
IC15 = 74LS195
IC16 = 74LS47
Q5 = 2N5210
SCR1-7 = TIC206

The controller also provides connections so that the display can be driven by a special purpose external controller, or by a simple I/O port on a home computer. In the case of a display with more than four digits, this is probably the easiest way to enter data and the circuitry for the thumbwheel switches can be omitted.

Construction

The box should be built first, and this is probably the trickiest part. It's not possible to give exact details and dimensions because these will vary according to the size of the digits and the number required. Fig. 6 shows the arrangement used in the prototype and this should be used only as a guide.

The circuit boards are all single sided except for the controller which is double sided. The leads of the components on the

controller board are used to bridge between tracks on each side of the board; components should be soldered on the top side as well as the bottom. Unfortunately this rules out sockets for the ICs.

Printed circuit board pins are used for the flying lead connections to the power supply (except the 120V into the transformer), the isolator module, and the display drivers. In the case of the display drivers, no flying leads are used for the triac-to-lamp connections. The pins should be installed first, followed by the wire links, the resistors, capacitors, and the semiconductors. Be careful with the ICs, some are CMOS types. Leave the power supply, transformer, and triacs for the time being.

The triacs on the digit driver modules are mounted with a small heatsink sandwiched between them and the board. This

CASE AND CONTROL PANEL

- D2-17 1N4148
- FS1 panel-mounting fuse holder and 3A fuselink
- LP1 panel-mounting mains neon
- SK1 7-pin DIN socket or other multipole connector to choice
- SW1-4 BCD ten position thumbwheel switch with true and inverse outputs
- SW5 DPST toggle or other mains on-off switch

15W light bulbs, lampholders as required; wood, brackets, etc. for enclosure; coloured filter for front of display; small aluminum panel for the controls and nuts and bolts to mount; cable ties or spiral wrap or similar, stand-off pillars, nuts and bolts for mounting PCB's; ribbon cable, writing etc. The thumbwheel switches are available from Electro Sonic, 1100 Gordon Baker Rd., Downsview, Ontario (416) 494-1555.

POWER SUPPLY

Resistors

(all 1/4W 5%)

- R12 10k
- R13,14 330R
- R15 1k

Capacitors

- C5,7 470u 16V radial electrolytic
- C6,8 100n 5% polycarbonate

Semiconductors

- IC9,10 78L05
- Q1 2N5210
- D1 1N4001
- BR1,2 1A, 200V (General Inst.)
- LED1,2 miniature red LED

Miscellaneous

- T1 6-0-6V, 500mA mains transformer, chassis mounting PCB; 1mm terminal pins; ground tag; nuts and bolts for mounting transformer. The bridge rectifiers are available from Active Components.

is a length of aluminum strip, details are given in Fig. 9. The heatsink also provides the extra two mounting points for the board. Each triac is bolted to the board through the heatsink with a mica washer and bushing to insulate the tab. Silicone grease should be used between the tab and the aluminum to improve heat transfer.

Two of the pins on each triac are bent down to pass through the board, while the centre pin is bent up for a flying lead connection to the lamps. Only after the triac-heatsink assembly has been completed should the triacs be soldered to the board.

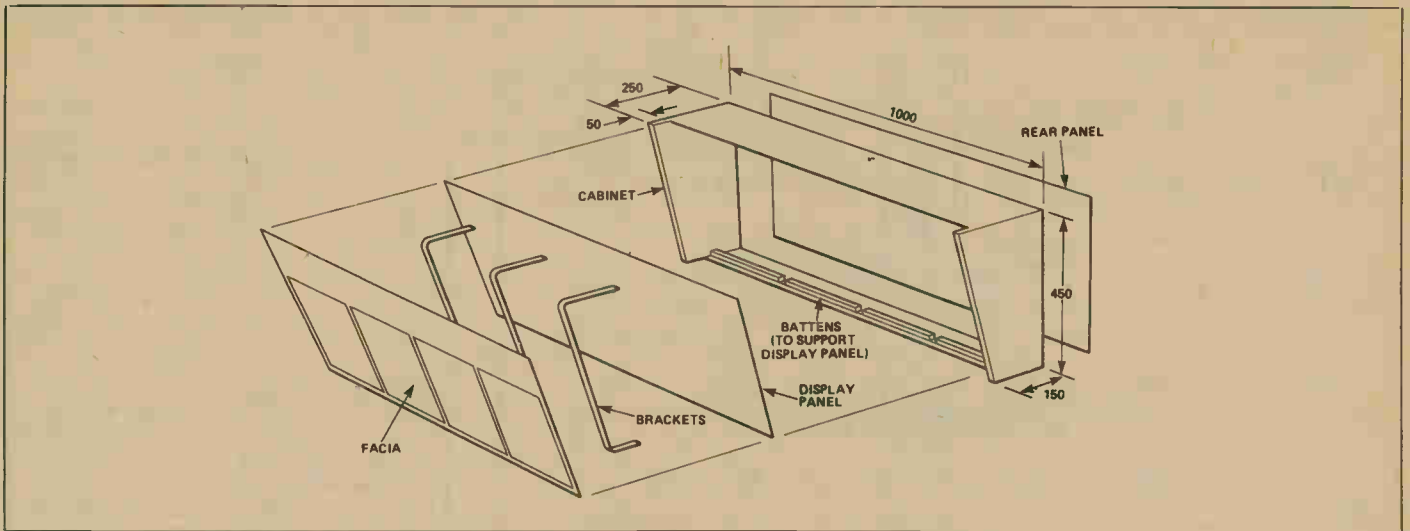


Fig. 6 Details of the cabinet used for the prototype.

The bulb sockets can be mounted on a wooden panel which is also used as the chassis for the PCBs. Mount the PCBs with standoff pillars and keep the interwiring neat by using spiral wrap around the cables. Make sure suitable cable is used for the AC supply to the lamps, between the lamps and triacs, and the returns from the digit driver boards.

The supply, return, and ground wires have been taken to a central supply point rather than chaining them from point to point. This includes the power supply module as well as each display. Remember that quite a bit of AC voltage and current is present throughout much of the wiring; wire it for safety.

The diodes associated with the thumbwheel switches are integral with the switches themselves, and the arrangement shown uses the inverse data outputs. If the

switches used do not have inverse outputs, turn all the diodes around, swap the common connections for the two pairs of digits and alter the pull-up resistors on the controller module so that they pull down to 0V. If a display of less than four digits is required, simply omit switches and diodes starting with SW1, then SW2, etc.

Any convenient connector can be used for the outlet to the external controller. A seven pin DIN socket has been used in the prototype. The external controller can interrogate the thumbwheel switches by intercepting the serial data and control signals. It can inject data in place of the switch data by driving the switch disable input to a logic 1 (3.7V+), at which point the output of IC8 goes high impedance and can be driven externally.

If the switch inputs are never going to be used, the controller module may be

dedicated to external control by omitting IC4,7, and 8, as well as R2 to R9. The copper track on the component side of the board leading to IC3 pin 1 should be cut (close to the IC only) and a wire link soldered between the pad of IC8 pin 15 and IC5 pin 2. This allows the external controller to generate the envelope signal. IC6 pins 5 and 6, and IC3 pins 4 and 5 must be wired to 0V to protect their CMOS inputs.

Setting Up and Use

Boot up the power supply with its outputs disconnected, if all is well, the LEDs should light to show that something is getting through. Check that both outputs are producing 5V.

Very little intermediate checking can be done on the rest of the circuitry so be careful while poking around the digit


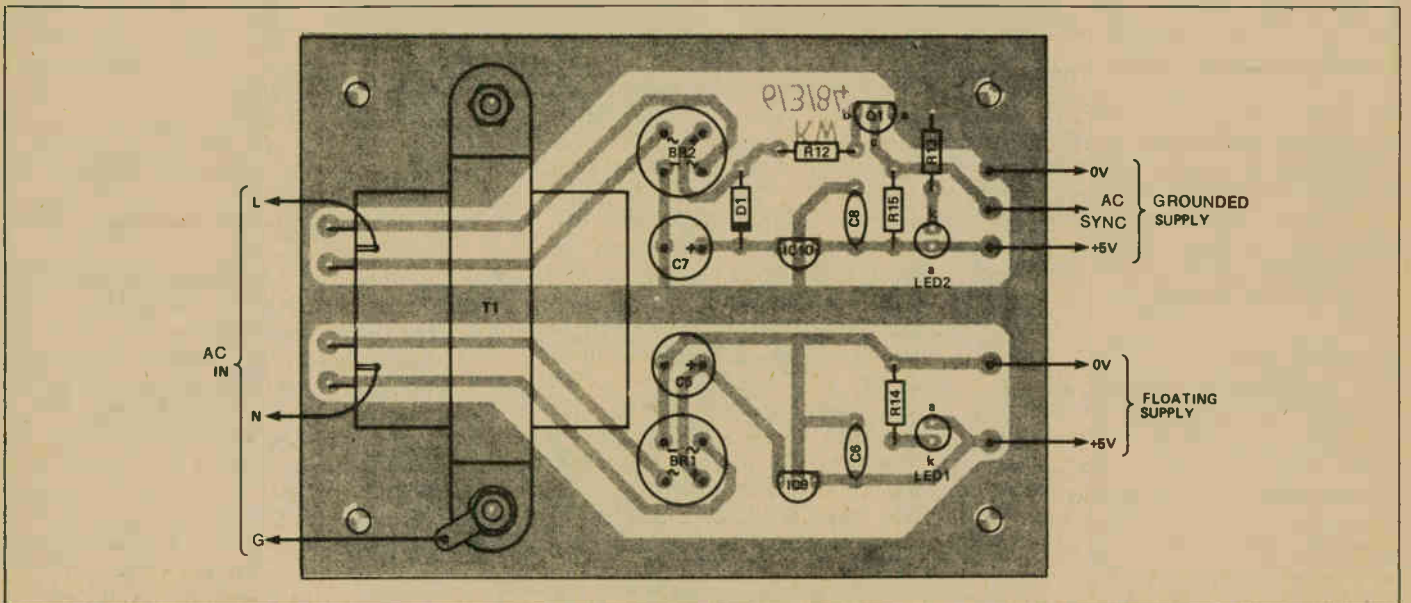


Fig. 7 Component overlay of the power supply board. Note the ground connection to the frame of the transformer and the AC connections taken directly to the transformer, not to the PCB.

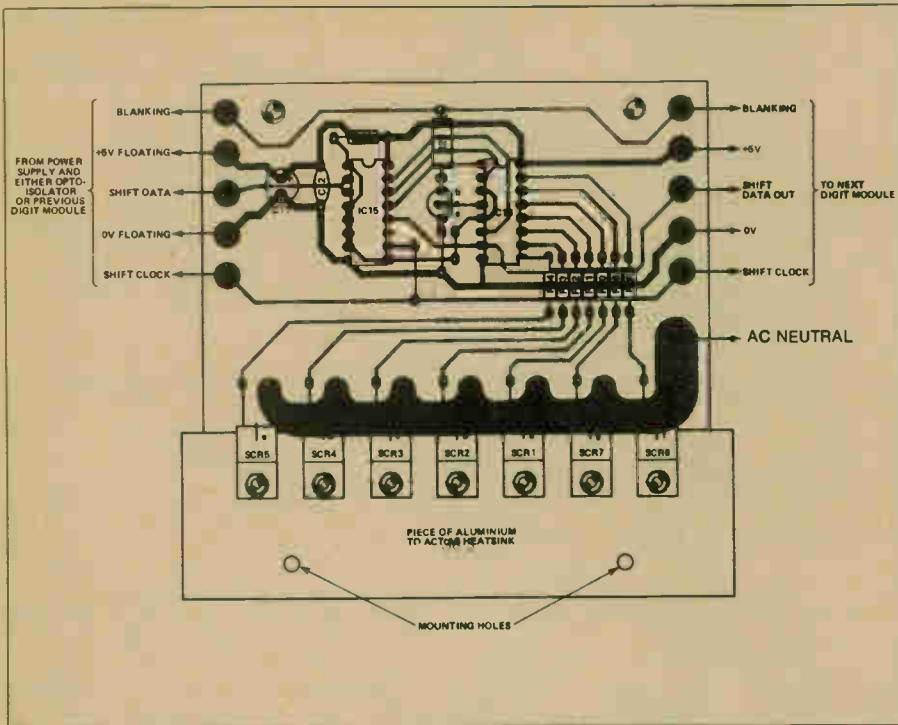

DIGIT DRIVER MODULE

Resistors

(all 1/4 W 5%)

R28	330R
R29	10k
R30-36	100R

Capacitors

C11	100u 10V radial electrolytic
C12	100n polycarbonate

Semiconductors

Q5	2N5210
IC15	74LS195
IC16	74LS47
SCR1-7	TIC206

Miscellaneous

PCB; 1mm terminal pins; nuts and bolts, mica washers and insulating bushes for triacs; heatsink (see text); IC sockets if desired — 2 off 16 pin DIL.

Fig. 8 Component overlay of a digit driver board. The lamp connections are made directly to the centre pins of the triacs.

driver areas as these are ripe with AC voltages.

Make the set-up adjustments with a single bulb plugged in somewhere, and arrange for the display to show all 8s. Set RV1 on the controller module fully anticlockwise and RV2 fully clockwise. Switch the unit on and the lamp should be at full brightness. Using an insulated screwdriver so that AC hum does not affect adjustments, slowly turn RV1 clockwise until the lamp suddenly goes dim, and stop there. Now turn RV2 anticlockwise and the lamp should increase in brightness. The lamp may now be set to the desired operating brightness.

If the display is to be run at full brightness, either because you need that much light or because you want to keep RF interference to a minimum, continue to turn RV2 anticlockwise until the lamp suddenly goes out then turn it back to the point where the lamp comes on again.

The display is now ready for use, so switch off and install all the lamps. Keep a few spare triacs on hand as well because when bulbs blow they tend to take the triac with them. Running the display at a reduced brightness should help a little.

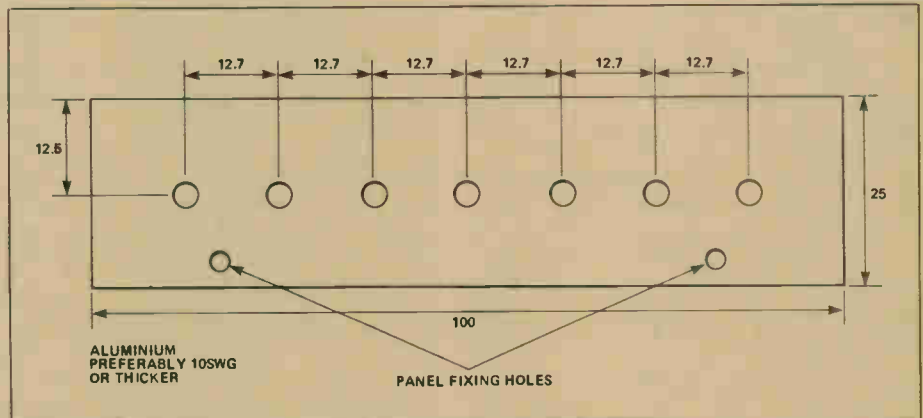


Fig. 9 Drilling details of the heatsink for the digit driver board.

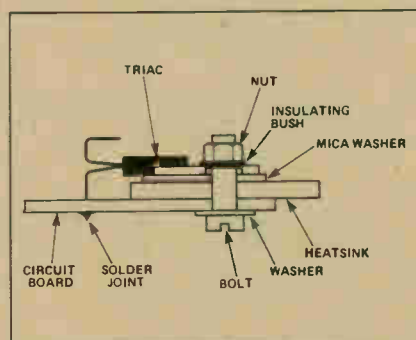


Fig. 10 Mounting arrangements for the triacs.

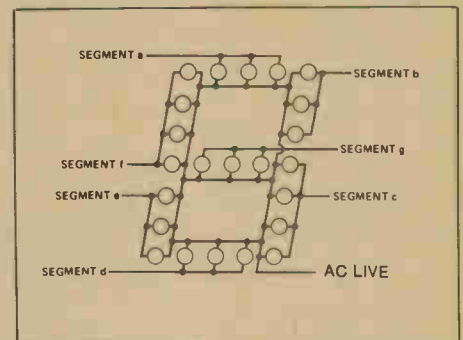


Fig. 11 How the lamps are connected to form a seven segment display.

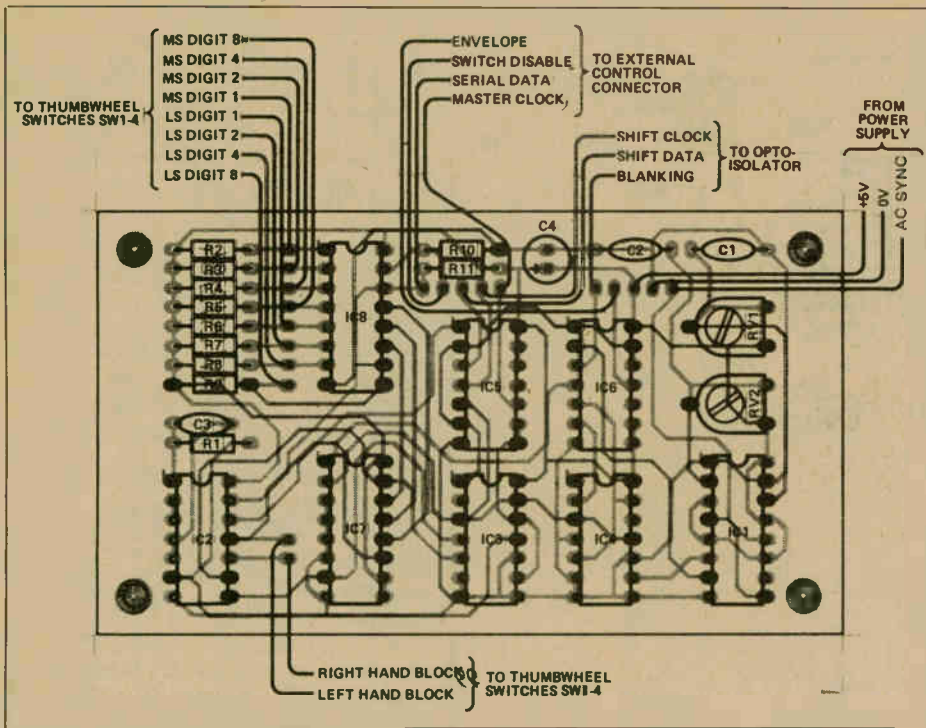


Fig. 12 Component overlay of the controller board.

CONTROLLER MODULE

Resistors

(all 1/4 W 5%)

R1	1k8
R2-11	10k
RV1,2	220k miniature horizontal preset

Capacitors

C1, 2	120n 5% polycarbonate
C3	4n7 5% polycarbonate
C4	22u 25V radial electrolytic

Semiconductors

IC1	4098
IC2	4069
IC3,4	4013
IC5	4001
IC6	4011
IC7	40163
IC8	4512

Miscellaneous

PCB

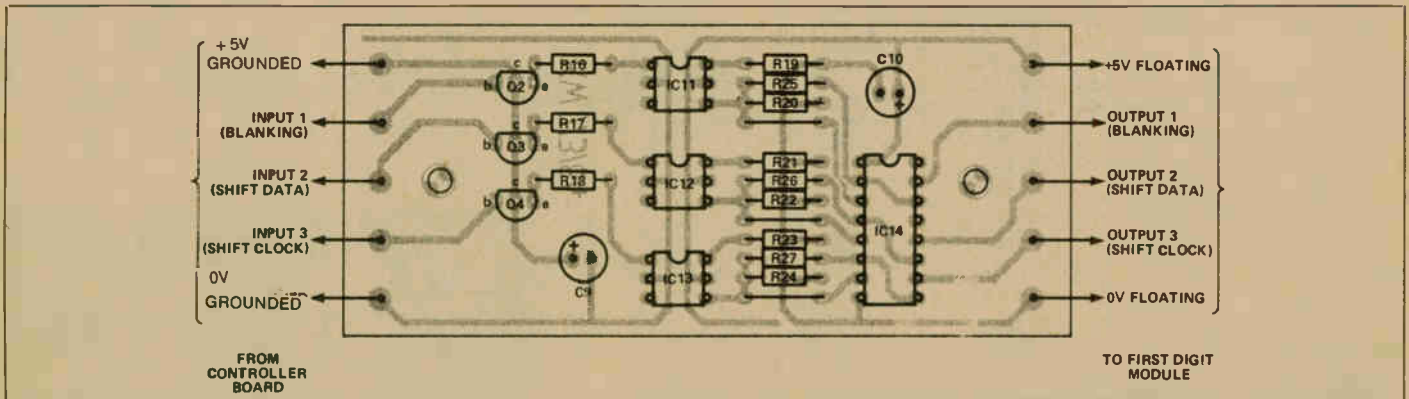


Fig. 13 Component overlay of the optoisolator board.

ISOLATOR MODULE

Resistors

(all 1/4 W 5%)

R16-18	150R
R19,21,23	100k
R20,22,24	10k
R25-27	47k

Capacitors

C9,10	100u 10V radial electrolytic
-------	-------	------------------------------

Semiconductors

Q2-4	2N5210
IC11-13	MOC3010 opto-isolator.
IC14	4050

Miscellaneous

PCB; 1mm terminal pins; IC socket if desired — 1 off 16 pin DIL



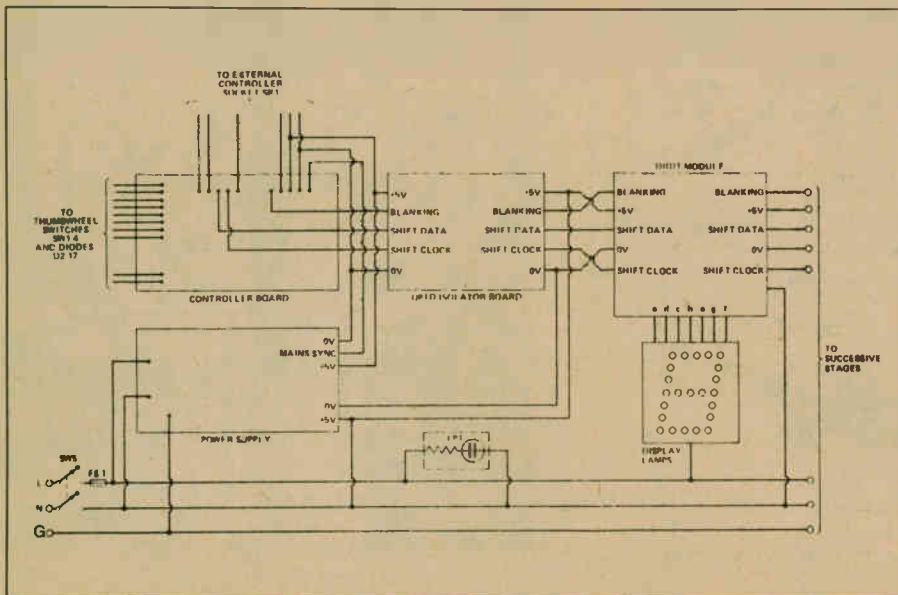
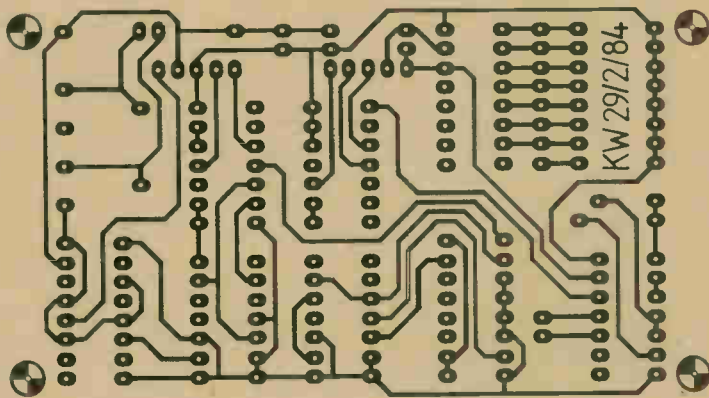



Fig. 14 Interconnection of the boards.

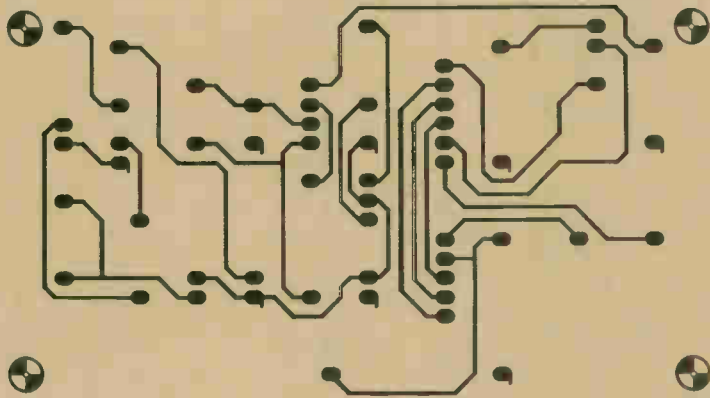

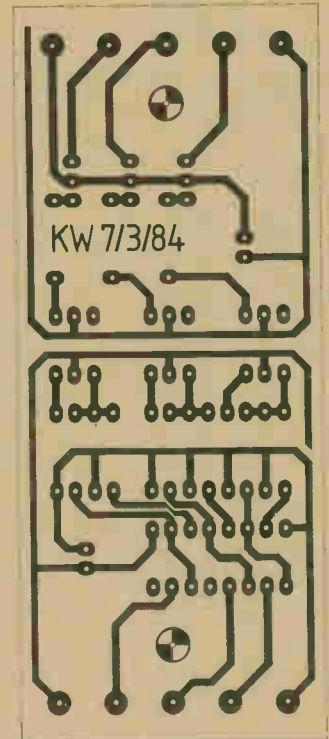
The top and bottom patterns for the scoreboard controller module.



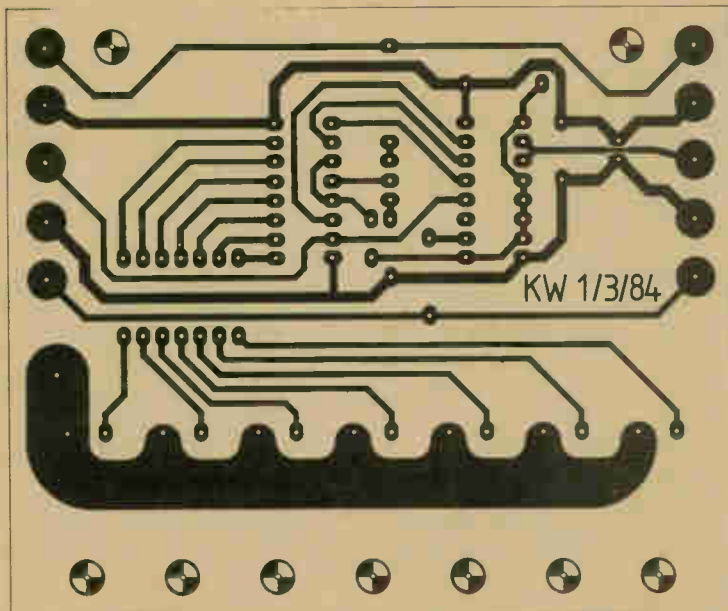The pattern for the scoreboard opto-isolator module.



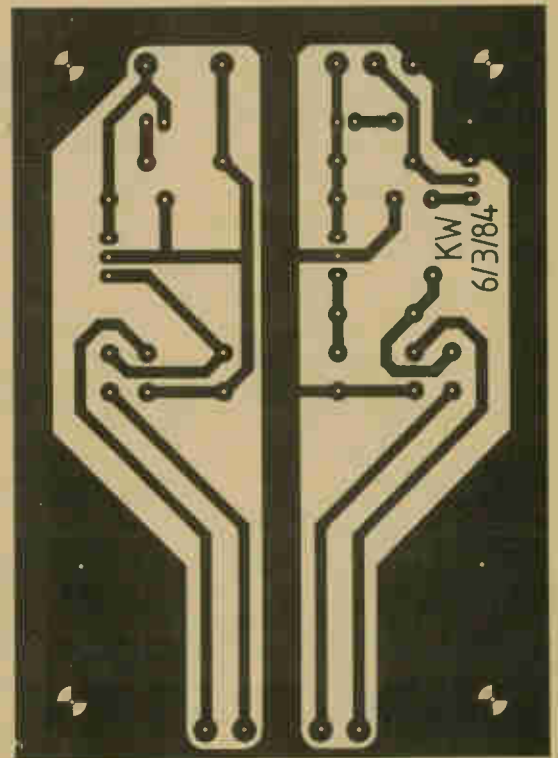The digit driver board pattern for the scoreboard



The power supply board pattern for the scoreboard.

Train for the Fastest Growing Job Skill in North America

Only NRI teaches you to service and repair all computers as you build your own 16-bit IBM-compatible micro

As computers move into offices and homes by the millions, the demand for trained computer service technicians surges forward. The Department of Labor estimates that computer service jobs will actually *double* in the next ten years—a faster growth than any other occupation.

Total System Training

As an NRI student, you'll get total hands-on training as you actually build your own Sanyo MBC-550 series computer from the keyboard up. Only a person who knows *all* the underlying fundamentals can cope with *all* the significant brands of computers. And as an NRI graduate, you'll possess the up-to-the-minute combination of theory and practical experience that will lead you to success on the job.

You learn at your own convenience, in your own home, at your own comfortable pace. Without classroom pressures, without rigid night-school schedules, without wasted time. Your own personal NRI instructor and NRI's complete technical staff will answer your questions, give you guidance and special help whenever you may need it.

The Exciting Sanyo 16-bit IBM-compatible Computer—Yours To Keep

Critics hail the new Sanyo as the "most intriguing" of all the IBM-PC compatible computers. It uses the same 8088 microprocessor as the IBM-PC and the MS/DOS operating system. So, you'll be able to choose thousands of off-the-shelf software programs to run on your completed Sanyo.

As you build the Sanyo from the keyboard up, you'll perform demonstrations and experiments that will give you a total mastery of computer operations and servicing techniques. You'll do programming in BASIC language. You'll prepare interfaces for peripherals such as printers and joysticks. Using utility programs, you'll check out 8088 functioning. NRI's easy step-by-step directions will guide you all the way right into one of today's fastest growing fields as a computer service technician. And the entire



NRI is the only home study school that trains you as you assemble a top-brand micro-computer. After building your own logic probe, you'll assemble the "intelligent" keyboard...


Your NRI course includes a Sanyo 16-bit microcomputer with 128K RAM, monitor, double-density/ double-sided disk drive, and "Intelligent" Keyboard; The NRI Discovery Lab[®], Teaching Circuit Design and Operations; a Digital Multimeter; Bundled Spread Sheet and Word Processing Software Worth over \$1000 at Retail—and More.

system, including all the bundled software and extensive data manuals, is yours to keep as part of your training.

100-Page Free Catalog Tells More

Send the postage-paid reply card today for NRI's big 100-page color catalog, which gives you all the facts about NRI training in Microcomputers, Robotics, Data Communications, TV/Video/Audio Servicing, and other growing high-tech career fields. If the card is missing write to NRI at the address below.

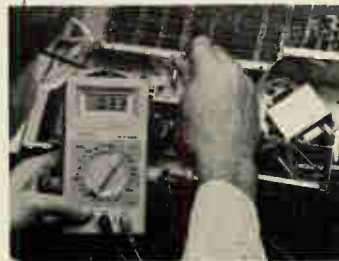... then install the computer power supply, checking all the circuits and connections with NRI's Digital Multimeter. From there you'll move on to install the disk drive and monitor.



NRI SCHOOLS
McGraw-Hill Continuing Education Center

330 Progress Avenue
Scarborough, Ontario M1P 2Z5
or telephone 416-293-8787

We'll give you tomorrow.

IBM is a Registered Trademark of International Business Machine Corporation.

“For a wide choice in LF generators...”



... Philips offers value, convenience and versatility.”

“You won’t match the choice Philips gives you in LF instruments. Whatever your application, one of these signal sources is sure to give the right combination of functions – at a competitive price!

From low-cost RC and function generators, ideal for general-purpose requirements or teaching work, right up to the most sophisticated function generators or

synthesizers with microprocessor control and full interfacing capability for use in R&D and industry, you can choose from no less than ten different models.

And don’t forget: Philips backs-up every product with full service and technical support. So you get maximum benefit from your investment. Find out more about Philips’ unbeatable choice in LF instruments from:

PHILIPS ELECTRONICS LTD.
S&I Div.,
Test & Measuring Group,
601 Milner Avenue,
Scarborough, Ontario,
M1B 1M8
Tel. (416) 292-5161
Montreal – (514) 342-9180
Ottawa – (613) 237-3131.”




**Test &
Measurement**

Circle No. 9 on Reader Service Card

PHILIPS

Compact Fibre Optics

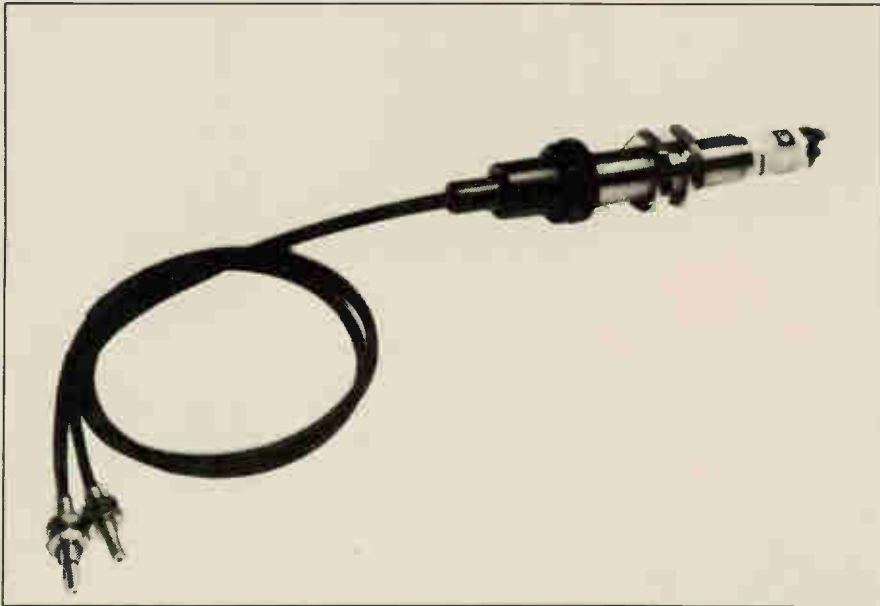

Electro Corporation has announced a new line of Photo-Trol pulsed LED photoelectric switches for target detection in industrial applications. The control head is 1/2 inch in diameter and the optical diameter of the fibres only .040 inch. No electrical energy is present in the head or cable, making them ideal for hazardous loca-

tions. Models are available in through-beam, retro-reflective or proximity modes. They're stocked by Atlas Electronics, with branches in Montreal, Ottawa, Toronto, Winnipeg, Calgary, Vancouver and Tuktoyuktuk; their head office is 50 Wingold Avenue, Toronto, ONTario M6B 1P7, (416) 789-7761. Circle No. 45 on Reader Service Card

Zentronics, 8 Tilbury Court, Brampton, is now distributing United Chemi-con aluminum electrolytic capacitors. UCC have a broad base of capacitors ranging from general purpose, tantalum replacement, power supply, high CV and computer grade. They're at (416) 451-9600
Circle No. 46 on Reader Service Card

The president of Apple Computer, John Scully, announced recently that the company would "open up" the architecture of the IIc and Macintosh to third-party vendors. This would encourage hardware and software developers to come up with expansions for both machines. The IIc, in particular, could use more memory and the ability to run CP/M.

Miniature TV

Zenith Electronics has introduced its most portable television set ever, the black-and-white model BT044S, weighing only two pounds and sporting a four-inch diagonal screen. It's said to fit easily into a briefcase, purse, totebag or palm, and has UHF/VHF 69 channel capability. It runs on household AC, your 12V car battery, or four alkaline C cells. It also has a jack for signals from a VCR or video camera, making it an ideal field monitor. From Zenith dealers.

Circle No. 47 on Reader Service Card

ComputerLand Canada Inc., Canada's largest computer retailer with 63 stores, has introduced a national, toll-free hotline to answer customers' software questions. The hotline, offering bilingual service, is available for the duration of each maintenance contract purchased, or for up to 30 days with each software purchase. Good stuff. Few things must be as frustrating as spending a bundle on software that doesn't seem to do what you want.

Circle No. 48 on Reader Service Card



LENLINE

High Performance Tool Kits for the Electronic Pro on the Go

PICK THE KIT THAT FITS YOUR NEEDS.

You can't beat LENLINE for top quality, durability and value in travelling tool kits. Choose from 8 standard kits (just 2 of them shown here)—or design your own with a customized tool assortment.

Quality tools for a wide range of on-site installation, repair and service tasks are thoughtfully organized in cases of legendary PLATT toughness and excellence. Send for complete full-colour catalogue today.



TC200/TC200M COMPACT SOFT-SIDE

55 basic tools needed for most on-site jobs housed in a handy, handsome, easy-to-tote zippered case of padded vinyl. 29 tool pockets, inc. one for your favourite tester. Metric version available.



TC400 DELUXE HARDSIDE SUPERKIT

Tough ABS thermoplastic case by PLATT, deep enough to hold an extra pallet for additional tools. Comes with a versatile assortment of tools to handle virtually every task you'll encounter in the field.



2 FREE CATALOGUES

GET THE WHOLE KIT & CABOODLE

YES: Send me your Full-colour LENLINE Electronic Tool Kit Catalogue PLUS complete catalogue of LENLINE tools, parts and accessories.

Name _____

Company _____

Address _____

City/Prov. _____

P/Code _____ Phone () _____



MAIL TODAY TO:
Len Finkler & Co.
80 Alexdon Rd.,
Downsview, Ont. M3J 2B4
OR PHONE CUSTOMER SERVICE
(416) 630-9103

LF-02

According to the joint program of Statistics Canada and the Electrical and Electronic Manufacturers Association of Canada, shipments for May totalled \$12.7 million. Exports were \$498 million, up about 9 percent from a year ago, and imports were \$1041 million, also up slightly. There were 108,000 people employed in the industry, up .8 percent over last year. In other words, no drastic changes so far.

Other facts: the electrical energy made available up until April was 147,072 gigawatt/hours. The top three imports were semiconductors, parts of semiconductors, and tape decks.

Prices: compared to 1971, major appliances are 2 1/2 times more expensive, radio and TVs twice as expensive, small appliances twice, and lighting fixtures 3 1/2 times.

The Lexicon 1200C mentioned in the last issue is used for the compression or expansion of the running time of video and audio program material, allowing split-second timing adjustments without editing. We omitted the fact that Lexicon products are available from Deltech Communications Equipment Inc., 300 Steelcase Road, Unit 11, Markham, Ontario L3R 2W2 (416) 649-2674.


Circle No. 49 on Reader Service Card

100 and 1000 Years Ago in Electronics Today



October, 1885: "Can the many readers of Electronics Today really justify to their compatriots the usefulness of the endless hours of diversion provided by coils of wire and battery jars filled with peculiar liquids? While we, the staff, enjoy these pastimes as well, we must answer in the negative. It would appear that the invention of electricity will not prove of use to society, and regretfully must be ranked with other idle fantasies, such as the flying machine or the transmission of animated photographs through the ether."

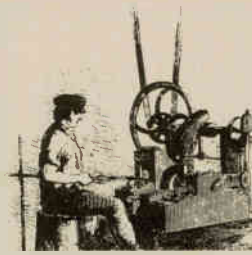"While the staff of Electronics Today makes every effort to ensure accuracy, things occasionally do go wrong. The printed circuit for last month's Electrical Health Stimulator and Perspiration Suppressor was accidentally omitted and appears in this issue along with apologies for those inconvenienced."




"Work is progressing in Southern California towards the miniaturizing of relays. The relay, at present an unwieldy coil and frame, can be used as the most basic form of 'memory', since it 'remembers' its electrical state until power is interrupted. Researchers claim that the relay could be made as small as six inches to a side, and dozens of them mounted in a framework no larger than the average living room, giving a 'memory' capability of hundreds of states. At present, we find this concept to be unrealistic; aside from having no conceivable use, it can no doubt be shown that miniaturization to this extent is simply not physically possible."



October, 985: "Verily, ye Len Fynkler and Company have presented a new machine Tool, yclept ye OK-11 Wirewrap Tool from OK Induftries. Cleverly yclad in black ABS Plaftik, ye compact Tool is defigned for ye Production and ye R&D, handling Wire from 22 to 34 AWG. Much Time will be saved over ye previous way of fastening ye Wire with ye blow of an Axe."

"In sooth, ye Goblins do wreke Havok in ye Nyght in our Office; yea, ye Printed Circuit for Ye Electrified Broadword inddeed was omitted from laft Month. It appeareth this Ifufe wyth Apologia moft profufe."

"Ye alchemifts do difturb ye Brain and quicken ye Temper: verily, they do infit that ye entyre Drawbrydge could be ufed for a 'Memory' in that it doth 'remember' one of ye two State, forsooth, ye 'up' or 'one', and ye 'down' or 'zero'. Ye Drawbrydges are to be 'miniaturised', God a-willyng, and mounted in ye 'Memory Banks' to keep afresh ye 'Data'. Suche Foolery and wafting of Tyme doth bode ille for ye Induftry."

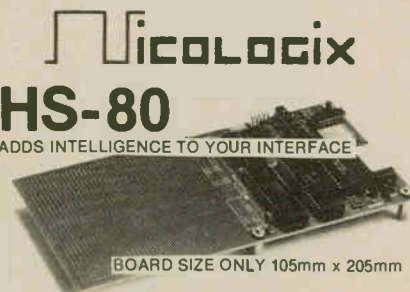

NICOLOGIX
HS-80
ADDS INTELLIGENCE TO YOUR INTERFACE

BOARD SIZE ONLY 105mm x 205mm

Save Time and Money

This low cost general purpose controller that is designed to tailor microcomputer applications ranging from teaching aids in basic microprocessor theory to sophisticated dedicated controllers. The board is already being implemented in schools and universities and is an ideal aid for both hobbyists and professionals alike.

SYSTEM FEATURES: Z80-CPU based • Z80-PIO provides two 8-bit parallel programmable ports • 8 decoded output port strobes • fully buffered user data bus • capability for an NMI driven Real Time Clock (NMI driven by second on board clock) • capability of multi-tasking using the MTHS-80 Operating System • Revision 1.1 is expandable to 8K of RAM and 16K of EPROM • 5 VDC operation, plenty of proto-typing space and more!

PRICES:

HS-80 Bare Board Revision 1.1	(\$21.95)
HS-80 Hardware Manual	(\$ 5.95)
MTHS-80 Operating System Rev 2.0 on 2732A	(\$29.95)
MTHS-80 Operating System Manual	(\$ 9.95)

Note: prices subject to change without notice.

POSTAGE AND HANDLING: add \$2.00 for the first item, \$1.50 each additional item. Ontario residents please add 7% PST.

Mail to NICOLOGIX, P.O. Box 976, Streetsville, Ontario, L5M 2C5. Make cheque or money order payable to NICOLOGIX.

Also available at Exceltronix Inc., 319 College Street, Toronto, Ontario, M5T 1S2.

PC ATE

Ate what? If you have an IBM PC or HP 150, you can build yourself an Automated Test Equipment setup with Hewlett-Packard's new PC Instruments test modules. The interface card and software allow the computer to control and display test results from up to 15 of the stackable modules. Modules available so far are: a digitizing scope, a multimeter, a function generator, a universal counter, a digital I/O interface, multiplexer, a D/A converter, and a relay actuator. Contact Hewlett-Packard (Canada) Ltd., 6877 Goreway Drive, Mississauga, Ontario L4V 1M8, (416) 678-9430.


Circle No. 51 on Reader Service Card



DMM Temperature Module

Instant temperature measurements are possible with the Fluke 80TK thermocouple converter. It has an output of 1mV per degree, giving a direct readout on any 3 1/2 digit multimeter having a 10 megohm or greater input impedance. Various probes are available for different applications, giving a range in total of -40 to 927 degrees C. Powered by a 9V battery, the converter is switchable from Celsius to Fahrenheit. From Allan Crawford Associates, Test and Measurement Division, 5835 Coopers Ave., Mississauga, Ontario L4Z 1Y2, (416) 890-2010.

Circle No. 50 on Reader Service Card

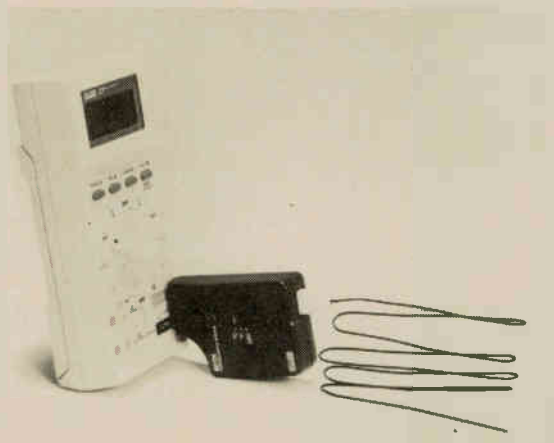

All three machines are in the Toronto area, at low altitude, so few cosmic ray induced soft failures are to be expected in any of them. In other respects, however, the computers' environments differ substantially. They are in three separate buildings. The machine on which no memory corrections have been observed is supplied with A.C. power through a commercially manufactured filter which, according to its maker, removes virtually all spikes and other forms of noise from the A.C. waveform. In contrast, the computer in which the most errors have been observed is surrounded by many other items of electrical equipment and, until recently, was supplied with "raw" A.C. without any filtering. Interestingly, no memory corrections have been seen on this machine in the most recent 1,000 hours or so of operating time. This corresponds roughly with the fact that an

A.C. spike filter has recently been installed in its power line. The machine which has twice re-booted its BBS from disk is one which is suspected by its owner of having some kind of intermittent hardware problem. If this is the case, it is not surprising that the errors it produces tend to be of the multi-byte variety.

Conclusions

Any conclusions which are drawn from these observations must be very tentative. They may not apply to types of computer other than the PET, nor in other geographical locations, particularly places at high altitude.

It does appear that the most frequent cause of memory soft failures in our BBS computers has probably been electrical noise. The difference in the error rates between the most and least error-prone computers is far greater than might

reasonably be ascribed to chance, and the only difference between them which seems to be a likely cause is the "dirtiness" of their electrical supplies.

The double-checksum technique of finding and fixing memory soft failures has been effective under the real-life conditions I have described. Its inclusion into other suitable systems is probably desirable.

The author is grateful to David and Richard Bradley and to Patrick Cole, the owners and operators of the Bradley Brothers' BBS, for having participated in this investigation. The BBBBs may be contacted, in Toronto, at (416) 487-5833. The BBS which the author operates is not a publicly accessible system.

DOES YOUR DIGITAL CAPACITANCE METER DO THIS?

FULL 4 DIGIT 0.5 INCH LCD DISPLAY COMPLETELY AUTORANGING WITH 10 RANGE MANUAL CAPABILITY

AND THIS

RANGE OF 0.0 pF to 1 FARAD (999.9 mF)
0.5% BASIC ACCURACY UP TO 100 uF

AND THIS

READS DIELECTRIC ABSORPTION

AND THIS

EXTENDED PSEUDO 5 DIGIT
RESOLUTION ON SOME RANGES ONLY

AND THIS


ABILITY TO ZERO LARGE CAPACITANCE
VALUES UP TO 99.99 uF

AND THIS

CALCULATES TRUE CAPACITANCE
IF CAPACITOR IS LEAKY

AND THIS

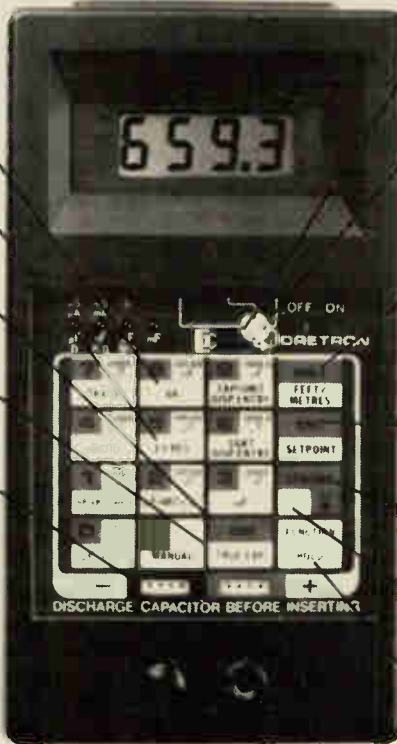DIODE CLAMP AND FUSED
PROTECTED INPUT.
DISCHARGE RESISTOR IN OFF
POSITION AT TERMINAL INPUTS.
POWERED BY 9V BATTERY



AND THIS

IDENTIFIES TRANSISTORS (NPN, PNP)
AND THEIR LEADS (E, B, C, ETC.)

AND THIS

TESTS ZENER DIODES AND RECTIFIERS.
UP TO 20V ZENER WITH AC ADAPTOR,
ZENER VOLTAGE WITH 9V BATTERY
DEPENDS ON ITS CONDITION

AND THIS

AUTOMATICALLY CALCULATES LENGTHS
OF CABLES IN FEET, METRES, MILES,
KILOMETRES (THEORETICAL RANGE
OF 9,999 MILES)

AND THIS

ABILITY TO SORT CAPACITORS IN
MANY DIFFERENT MODES

AND THIS

ABILITY TO READ LEAKY CAPACITANCE
(INSULATION RESISTANCE OR CURRENT)

AND THIS

CALCULATES TIME CONSTANTS WITH
USER DEFINED RESISTANCE VALUES

AND THIS

HOLD FUNCTION FREEZES DISPLAY

ONE YEAR PARTS & LABOUR WARRANTY

FOR ONLY THIS

\$149.95



MODEL
MC300

Approx. Size
7" x 4" x 1 1/4"

DAETRON
935 THE QUEENSWAY
BOX 641
TORONTO ONTARIO M8Z 5Y9
(416) 255-9701

DEALER ENQUIRIES INVITED

MADE IN CANADA

PLEASE SEND ME _____ (QUANTITY) MC300(s) @ \$149.95 \$ _____

CARRYING CASE \$19.95 \$ _____

AC ADAPTOR \$11.00 \$ _____

ONTARIO RESIDENTS ADD 7% PST \$ _____

SHIPPING AND HANDLING @ 4.45 per instrument \$ _____

TOTAL \$ _____

I ENCLOSE CHEQUE MONEY ORDER BILL MY VISA

VISA CARD NO. _____


EXPIRY DATE _____ SIGNATURE _____

NAME _____

ADDRESS _____

CITY _____ PROV. _____ POSTAL CODE _____

Oscilloscopes

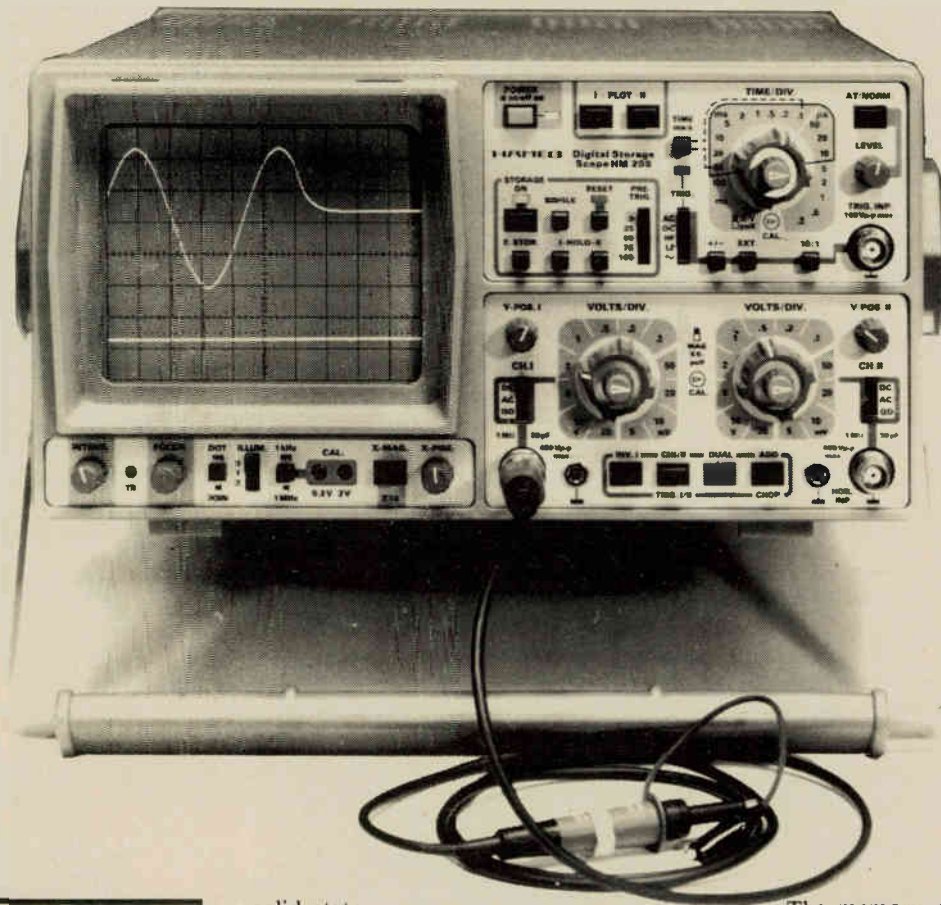

A look at oscilloscopes and the various features provided by low-cost solid-state technology.

By Bill Markwick

AS THIS article was first taking shape, I was doing some testing with my 1970s vintage storage oscilloscope. It was the high-tech of its time, being stuffed with all sorts of discrete transistors, and featuring an analog storage capability in the CRT. This worked by flooding the phosphor coating with electrons to keep the display refreshed, allowing storage of signals, or accumulated signals, for hours. It did its job all right, but the sensitive coating eventually burned a bit, especially with bright, repetitive signals; there's now the hazy ghost of a sine wave on top of anything else you happen to be looking at. It also suffers from spreading ("blooming") of the trace if you turn the intensity up too high. In addition, it cost a king's ransom and generates a remarkable amount of heat for something that's

solid-state.

The advent of low-cost digital and analog electronics has changed all that. Although discrete transistors are still used quite a bit for optimizing various characteristics, ICs are a natural for such functions as triggering circuits, and reduce power consumption in the bargain. A/D converters and inexpensive memories have replaced the analog phosphor as a storage device; not only do they eliminate the analog bugs, but they allow you to store waveforms in memories for later comparisons. On the scope on our cover, for instance, both the 1KHz pulse train and the 60Hz electrical noise were being displayed from the digital memories.

Circle No. 52 on Reader Service Card

Hameg HM 208

The oscilloscope on the cover, photographed as seen by someone who's nodding out on the testbench, is a dual trace, 20MHz storage scope with a 20MHz digitizing rate. This means that you can capture signals from extremely low frequencies to 20MHz, or 10MHz with both traces being stored. The Roll mode allows the scope to function as a chart recorder, with the signal running from right to left with continuous trace.

The memory consists of a 4096 by 8-bit block, divided into storage for channels 1 and 2, plus two backup memories of 1024 points each. The two backups can be used as a single, doubling the resolution to 2048 points.

Other features include four pre-triggering settings to allow the trace to start ahead of a particular event, X-Y operation with storage to display very low frequency transfer curves, Lissajous figures, etc., and an output for sending the stored waveforms to a chart recorder. Vertical sensitivity is 5mV/cm to 20V/cm.

The HM208 costs \$2750, FST included, from BCS Electronics, 980 Alness St., Unit 7, Downsview, Ontario M3J 2S2, (416) 661-5585.

Circle No. 53 on Reader Service Card

Duncan 6022

A general purpose 20MHz scope is the Duncan 6022, featuring dual traces, 5mV/cm sensitivity, a post-deflection-accelerator tube for linearity, and a built-in component tester. This latter item is no end of use to the troubleshooter, particularly if you come across a doubtful semiconductor; it consists of a 9VAC supply current-limited to 2mA. The AC is ap-

continued on page 42

SURPLUSTRONICS

we will not be undersold



8088 Computer Systems

\$995

- Includes:
 - 8088 motherboard
 - High quality legal Bios
 - One DS,DS 360K Drive
 - Power Supply with Fan
 - Keyboard
 - Flip-Top case
 - Disk Controller
 - With plenty of spare slots
- All you need for complete System is Video Board
 Colours: **\$159.00**
 Mono **\$159.00**

\$339

8088 motherboard with 256K (expandable on board to 640K) Fully assembled and tested with legal Bios, Flow soldered provision for 8087.

256K Memory

41256 (150nS) **\$ 4.95**
 Set of 9 **\$43.95**

64K Memory

4164 (150nS) **\$9.95**

IBM Compatible Keyboards

(Keytronics Serial Output), no housing **\$59.95**

IBM Style Case

Flip-Top 8 slot **\$75.00**

IBM Compatible Switching Power Supply, 130W, with Fan **\$136.00**

Set of 8088, 8255A-5, 8237A-5, 8288, 8284, 8253A-5, 8259A **\$45.00**

IBM Peripheral Cards

Colour Video Board **\$159.00**

Floppy Controller **\$ 99.00**

Floppy Controller with RS232 **\$139.00**

Floppy Controller with clock/RS232 **\$149.00**

Parallel and Game Port Card **\$ 59.00**
 Cable and connector extra

Peripheral Interface Card **\$119.00**
 Includes two serial ports, parallel port, game port and provision for (but not including) real time clock

Clock/Calendar Option **\$ 29.00**
 With battery backup.

256K & Multifunction Board.
 Includes: Serial port, parallel port, game port, provision for optional real time clock/calendar and socketed for up to 256K RAM. With 64K RAM **\$149.00**

512K Board. Socketed for 512K including:

64K RAM **\$119.00**

IBM Compatible Disk Drives **\$159.95**
 Brand New, fresh from factory. Shugart SA455 40 track, double sided double density Slimline. We have ordered 10,000 from Shugart - that is why we can pass the savings on to you.

IBM Compatible Keyboards
 Maxiswitch **\$135.00**
 Cherry **\$ 99.00**

IBM Style Case



Flip-Top, 8 Slot **\$75.00**
 With 150W Power Supply **\$219.00**

Disk Drives for IBM Computers

Shugart/Panasonic, 5 1/4" slimline, DD, DS 360K, 40 track **\$159.95**

Printers

Gemini 10X **\$299.00**
 Gemini SG10 **\$379.00**
 Gemini Daisy Wheel PowerType **\$599.00**
 18 cps, Bi-Directional.

Monitors

Zenith ZVM123 Green and ZVM122 Amber **\$129.00**

Complete 6502 System

- Assembled and fully tested (flow soldered)
- 64K, 80 x 24 video with soft-switch, floppy controller.
- System comes with blank EPROM's on board, does come with any proprietary software or Basic **\$199.00**

Complete System

• 6502 board (as illustrated above) with case, keyboard and power supply **\$399.00**

Complete System

• Using 6502 board above in IBM style flip-top case, using powerful 75 watt power supply with fan, programmable serial keyboard adaptor, IBM style keyboard **\$499.00**

As above with one built in disk drive **\$399.00**

As above with two drives **\$749.00**

6502 Power Supply

For 6502 Case, CSA Approved 5V, 5A, +12V 2.5A, -5V 0.5A, -12V 0.5A **\$69.00**

Keccc Power Supply

5V 5A +12V 2.8A, +12V 2A -12V 0.5A. Open Frame

\$58.95



6502 Style Case



With Numeric Keyboard **\$129.00**

Panasonic Printers

Open Frame **\$29.95**

Ideal for experimenters

IBM Style Power Supply

130W +5V 13A -5V 0.5V +12V 4.5A, -12V 0.5A **\$145.00**

Power Bars with Surge Protectors

..... **\$49.95**

Plug In Surge Suppressor

..... **\$11.95**

Apple Cards

Assembled flow-soldered/cleaned and 100% tested
 16K RAM Card **\$ 39.00**
 80 x 24 video card **\$ 59.95**
 Z80A Card **\$ 39.00**
 Parallel Printer Card (cables extra) **\$ 29.00**
 128K RAM Card with 128K **\$ 85.00**
 EPROM Programmer with Software (programs 2716 2732 2732A 2764) **\$ 63.00**
 8" Floppy Controller Final Sale
 - As is **\$ 39.00**

Modem Bargain!

Apple Compatible plug-in Autoanswer Autodial Touch Tone or Pulse Dial. Excellent for use with most Bulletin Boards. 300 Baud. Final Sale as is **\$39.95**

Apple Compatible Disk Drives

5-1/4" **\$175.00**

Apple Compatible Modem

EXCELLENT HAYES MICROMODEM COMPATIBILITY



Plugs into your Apple or compatible computer, Direct connect, 300 Baud, Autodial, Autoanswer, Touch Tone/Pulse Dial, complete with documentation.

\$139.95

Hayes is a registered trade name.

Mail Orders add \$5.00 minimum for shipping & handling. Ontario residents add 7% P.S.T. Visa, Mastercard and American Express cards accepted: send card number, expiry date, name of bank and signature. Send certified cheque or money order, do not send cash. All prices on this page are final sale. No warranty, No returns, No refunds but HUGE savings. Warranties available at extra cost.

Surplustronics, 310 College Street, Toronto, Ontario, M5T 1S3

**More lines to serve you better
 (416) 960-1350**

COMPUTER
PARTS GALORE INC.
 316 College St.
 Toronto, Ontario M5T 1S3

Toll Free Orders Only
1-800-387-1385
 Order Checking (416)925-8291
 Technical Data (416)925-1105

APPLE IIe®
DETACHED NUMERIC KEYBOARD
\$99.00



For those of you who would like to put your IIE in another case we have a high quality 100% plug in compatible Matrix keyboard with all IIE keys plus the highly desirable numeric keypad for quick entry of numeric data \$99.00

ASCII KEYBOARDS




Now, we have a new keyboard, micro controlled with 3 levels of pre-coded functions for Basic, CPM etc. and at the same old price as before.
 Function Keyboard, Numeric \$89.95
 Function Keyboard, Standard \$79.95

SOLID ABS CASE
NUMERIC
\$59.95



SOLDERLESS BREADBOARD

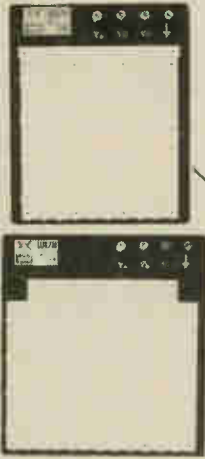


Solderless prototyping boards are the best way to quickly breadboard up a circuit. The holes are made especially for IC's, resistors, and other small parts with 22-28 gage wire leads, takes WW pins too.

- WB-106 \$42.95
- 3 IC strips, 5 power strips
- 4 Binding posts, Aluminum plate
- WB-104-3 \$29.95
- 2 IC strips, 1 power strip
- 2 Binding posts, aluminum plate
- WB-108 \$59.95
- 4 IC strips, 7 power strips
- 4 Binding posts, aluminum plate
- WB-104 \$33.95
- 2 IC strips, 4 power strips
- 2 Binding posts, aluminum plate.



MOTHER BOARD

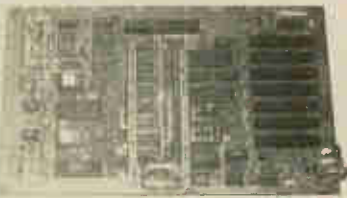


100% IIE® Compatible, for those of you who wish to build a clone of the very popular APPLE IIE®. This board is a reverse engineered copy of the IIE® and is 100% compatible. We have the motherboard and the custom ICs only. All other parts are widely sold. The custom ICs are workalike chips that do not infringe any copyrights. The software for operating the board must be obtained elsewhere as we do not have it for sale. When we say 100% we mean it.
 A very good buy at \$49.95
 Custom IC set(2) \$49.95
 Keyboard encoder (AY3-3600) \$14.95
 Character generator, U/LC \$14.95

IIE® ABS PLASTIC CASE
\$59.95



This case is made to fit the Mother Board listed here for making IIE® clones and it makes a very nice looking copy. There is just enough difference to avoid design infringement. The case also has no brand names or other marks on it \$59.95
 A good buy at

IIE® MATRIX KEYBOARD
\$79.95

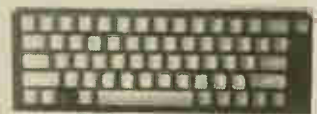

This keyboard fits the above case and has 100% clone compatibility, it will allow operation of all IIE® commands. Another bargain at \$79.95



This is a high quality Hall Effect keyboard made by Microswitch of Canada for AES data and now bought by us for 10% of the \$169.00 that AES paid for them in 10,000 lots. They are a very good word processing keyboard with both serial and parallel data outputs for use with APPLE and IBM type systems and come complete with a ribbon cable connector and complete pin-out. \$24.95

WIRED CARDS

- | | |
|------------------------|---|
| 16K \$ 45.00 | Applext 128K . \$140.00 |
| 128K no IC \$ 34.95 | Sprite gr. \$ 69.95 |
| 128K OK . . . \$ 55.00 | TMS9918A IC . . \$ 18.95 |
| 128 64K . . . \$ 99.00 | NICE PRINT . . . \$119.00 |
| 128K 128K . \$150.00 | 80 Column . . . \$ 65.00 |
| MC3242 IC \$ 12.00 | 80 Col. Sofsw . \$ 69.00 |
| DISC \$ 45.00 | Gripper \$ 50.00 |
| Z-80 \$ 45.00 | Grip cable . . . \$ 19.95 |
| Appcard . \$150.00 | Extended 80 Col. for IIE . . . \$129.00 |


NEW LOW BARE PCB PRICES*

- GROUP 1 \$7.00 each
- Real time clock
 - Rana 4 drive
 - 9 V Music
 - Disc Controller
 - Disc Controller (Shamrock)
 - PIA card
 - EPROM
 - WILD CARD
 - SAM TALKS
 - COMMUNICATIONS
- GROUP 2 \$9.00 each
- Gripper
 - 80 Column
 - 80 Column Soft Switch
 - Z-80
 - RGB
 - Sprite graphics
 - APPLACARD 128K ADD ON
- GROUP 3 \$11.00 each
- SSM MODEM
 - PARAT EPROM PROG
 - 16K
 - 128K
- All boards come with a parts list and placement diagram. We have all the parts of the PCB's just ask for them.
 *Prices so low we require payment with order

MEMORY FLASH

- | | |
|---------------------------|---------------|
| 64K-200Ns DRAM | \$1.25 |
| 64K-150Ns DRAM | \$1.00 |
| 256K-150Ns DRAM | CALL |
- Prime stock, limited quantity.

IBM POWER SUPPLY

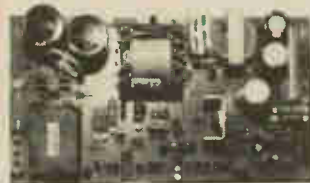

One of the nicest open frame IBM type switching power supplies we have ever seen. Came from the defunct NCR IBM compatible, runs the whole thing, has +5V-7A, +12V-3A, -5, -12-¼A. A very good unit for starter system. Will not run hard disc system. A real steal at \$49.95

SWITCHING POWER SUPPLY



Another great bargain from PARTS GALORE, A small power supply switching style that give +5v-4A; ±12v 1A and -5v (adjustable) on a compact 4x8" open frame PCB. Cost Northern Telecom \$50.00 when they bought 5000 pieces. We got em when a subcontractor went belly up for 10% of that price and we are selling em for

\$18.95 NEW IN BOX TESTED
 AC power cable (3 Wire) for above \$2.50

KEYTRONICS

PROGRAMMABLE KEYBOARD
 An excellent ASCII Keyboard, fully Apple Compatible. Full size with numeric and fully programmable key switches with full data **49.95**

POWER SUPPLY
CSA APPROVED

Our Famous "BLACK BEAUTY" power supply, now reduced in price but not in quality. Our ratings are 5V-5A, 12V-2.5A; 5A-12V A, 12V-12A for real **\$79.95**

OUR 6502 BOARD

Now only \$29.95 still with all the versatility of the original and a full 8 slots.



APPLE® DETACHED KEYBOARD \$159.00



The excellent MARK-II Apple detached keyboard using serial data (IBM) format. Price depends on Apple PCB \$159.00

GREAT DEAL

THE GREAT DEAL CARRIES ON FOREVER AND GETS BETTER
 Our proven 6502 motherboard plus a numeric case plus a black beauty power supply plus a numeric function keyboard plus any 4 bare pcb for \$225.00

CONNECTORS



DB SERIES

- | | |
|-------------------------|--------|
| DB 25 M solder | \$1.95 |
| DB 25 F solder | \$1.95 |
| DB 25 M IDC Flat cable | \$3.95 |
| DB 25 F IDC Flat cable | \$5.95 |
| DB 25 M Right angle PCB | \$4.95 |
| DB 25 F Right angle PCB | \$4.95 |
| DB 25 Shell | \$1.00 |
| DB 15 M solder | \$1.95 |
| DB 15 F solder | \$1.95 |
| DB 15 F IDC flat cable | \$3.95 |
| DB 15 M right angle PCB | \$3.95 |
| DB 15 F right angle PCB | \$2.95 |
| DB 15 Shell | \$1.00 |
| DB 9 M solder | \$1.75 |
| DB 9 F solder | \$1.75 |
| DB 9 M right angle PCB | \$2.50 |
| DB 9 F right angle PCB | \$2.50 |
| DB 9 Shell | \$0.75 |

DRIVE CONNECTORS

- | | |
|----------------------------|--------|
| 50 Pin Edge C 8" drive | \$5.95 |
| 40 Pin Edge C | \$4.95 |
| 34 Pin Edge C 5-1/4" drive | \$5.95 |
| 20 Pin Edge C Hard drive | \$4.95 |
| 34 Pin Fem header 17 x 2 | \$3.50 |
| 26 Pin Fem header 13 x 2 | \$3.00 |
| 20 Pin Fem header 10 x 2 | \$2.00 |

ASSORTED SEMI-CONDUCTORS AND OTHER STUFF

- | | |
|----------------------------|-----------|
| (A) RED LEOS/SIML | 10/\$1.00 |
| (B) GREEN LEOS/SIML | 8/\$1.00 |
| (C) AMBER LED/SIML | 8/\$1.00 |
| (D) PIN PHOTOIOODES | |
| INFRA RED | 2/\$1.00 |
| (E) PHOTO TRANSISTOR | |
| NPN VISIBLE | 2/\$1.00 |
| (F) LOR LIGHT DEP RESISTOR | \$1.00 |

NICADS 8.4V 7" D" 4A.H CELLS

A single cell battery with 8.4V and 4A.H capacity. Perfect for portable equipment. Price depends on quantity. \$14.95

COMPUTER PARTS GALORE INC.
316 College St.
Toronto, Ontario M5T 1S3

Toll Free Orders Only
1-800-387-1385
Order Checking (416)925-8291
Technical Data (416)925-1105

MAIL ORDERS We accept VISA, MC, AMEX, credit cards. Money orders, cheques (2 week wait) are also OK. Minimum packing and handling fee \$5.00 or 5% whichever is larger. The only COD we use is via CANPAR (Add \$4.00 COD fee) or motor freight. We do not use postal COD at all. All Ont. res. add 7%. All prices are subject to change without notice. Returns are subject to a 20% restocking charge.

CHERRY SWITCH IBM KEYBOARD

At last a good low cost keyboard for the IBM PC, XT or compatible machine. Uses capacitive keys, has a 'very good feel', and has TYPEWRITER LAYOUT for easy wordprocessing at the very low price of **\$119.00.**


MBE-XT AN IBM* XT Compatible 8 Slot Motherboard

MBE-XT BARE PCB WITH MANUAL AND SCHEMATICS.
\$49.95

LAZY BOARD

What is your time worth?? We have had a bunch of MBE XT boards stuffed and wave soldered so you can save all that time soldering them up. All you need are the IC's memory and BIOS and you are set to go **149.00**

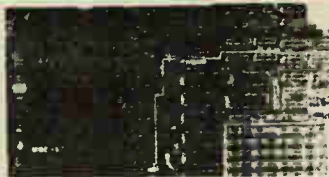FULLY WIRED AND TESTED WITH 64K ON BOARD WITH MEGABIOS AND MANUAL \$325.00



- 8086 16 Bit Microprocessor
- 8087 Math Processor Optional
- Up to 256K Dram on Board
- Has Digital Delay Line for Error Free Memory Refresh
- 4 DMA and Timer Channels
- 64K/128K Eproms Jumper Selectable
- Will run any Compatible BASIC
- IBM Power Plug Compatible
- Same PCB size as IBM XT
- Runs PC DOS and CPM 86
- Compatible BIOS in stock

KEYTRONICS 5150



Yes the famous KEYTRONICS 5150 IBM* compatible keyboard. MADE IN USA. We bought a bunch and can sell them for only **\$119.00**

We also have some Taiwan copies that are quite good and all are checked for only **\$99.00**

And lastly we have some Taiwan copies of the famous KEYTRONICS 5151 keyboard with all the same enhanced features for only **\$139.00**

512k MEMORY KIT

RAM DEAL RAM DEAL RAM DEAL RAM DEAL RAM DEAL This is a real deal. All the parts for a 512K IBM* memory card, including the card and all the RAM and sockets and other small parts. This would normally sell for around \$279.00 or more. Now for a short time we can offer this kit for only **\$139.95**

IBM BARE PCB

- (A) Color Graphics (Parsyst) **\$27.95**
- (B) Monochrome graphics **\$24.95**
- (C) Disc controller **\$17.95**
- (D) Disc controller + Printer **\$24.95**
- (E) Disc controller + Game **\$24.95**
- (F) IO + 2 i/o clock etc. **\$24.95**
- (G) Multifunction card 11 function **\$24.95**
- (H) AST SIXPACK COPY **\$34.95**
- (I) Parallel printer **\$17.95**
- (J) RS-232 card **\$17.95**
- (K) Simple modem card **\$17.95**
- (L) Disc for above **\$ 8.00**
- (M) 512K card **\$24.95**

- (N) 256K short card **\$19.95**
- (O) IBM 6" extender for service **\$19.95**
- (P) WW Proto, full sized with DB9 & DB25 footprints **\$24.95**
- (Q) WW Memory proto, full sized with 256K (1Meg) memory laid out on one end with DB9, DB25 footprint **\$29.95**
- (R) 512K Mapping PROM **\$ 4.95**
- (S) Multifunction PROMS(2) **\$24.95**
- (T) 2732 for color graphic **\$10.00**

All cards come with a detailed parts list and placement drawing, we also have all parts needed for them

MBE-XT

MBE XT Motherboard, wave soldered with no IC's at all with manual and schematics **\$149.00**

As above with 64K BIOS tested with all IC's and fully burned in, 8 Slots **\$325.00**

BASIC SYSTEM MBE XT A & T with 256K with one 360K drive & controller with power supply, hinged lid case and MEGA BIOS **\$895.00**

MBE XT SYSTEM + The fully loaded MBE XT system with 256K on board, BIOS, Cherry keyboard, color graphics, 2.360K DSDD Drives with controller and serial parallel ports, calendar, clock and many more small features fully tested ready to go **\$1395.00**

If you want a wave soldered board to save you the soldering time, LAZY kit **\$169.95**

MONOLITHIC CAPS

MONOLITHIC CERAMIC CAPS
We bought 100,000 of em dirt cheap they are very good quality 63V 02 lead spacing. Now only 10c ea.
50 pcs **\$ 5.00**
100 pcs **\$ 9.00**
1000 pcs **\$85.00**
more? ask!

IBM CASE

We have the nicest case of all the various competing cases, ask any friend who has bought someone else's case and then has seen ours. The lid is hinged with pushbutton access. The back is cut for 8 XT slots and it comes with all the case back inserts for cards, card guides, blind disc filler plates, standoffs, feet, screws, all for **\$79.95**. Please specify back or side cutout for power supply.



We also have an IBM 8 Slot/6502 Board dual duty case for making IBM look-a-like 6502 systems **\$79.95**

MEGABOARD CASE, similar to the above. Fits the MEGABOARD exactly for back power supply **\$99.00**

SWITCHING POWER SUPPLY


110V, 60Hz with Fan and two rear switched outlets.

These power supplies fit our cases.
130 WATT +5V-14A; +12V-4.2A; ±12V-1/2A
Back Switch **\$149.00**
Side Switch **\$159.00**



8" DRIVE SWITCHING POWER SUPPLY

\$39.95

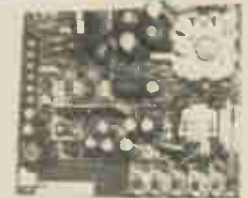

The greatest 8" Drive supply we have ever found. Has 24V-2.2A 5V-3A and -12V-17A. All you need for a dual 8" Drive system. A switching power supply by ASTEC **\$39.95**

PARTS, PARTS, PARTS, PARTS, PARTS

Hard to get parts for your IBM compatible (8088) systems and peripherals

- 8088 CPU **\$7.95**
- 8087 Math Processor **\$219.00**
- 8237A 5 Prog DMA Cntrl **\$8.95**
- 8250 Serial Port **\$9.95**
- 8253A 5 Prog Interval timer **\$5.95**
- 8255A-5 P I A **\$4.95**
- 8259A Prog Interrupt Cntrl **\$4.95**
- 8284A ADC clock gen & driver **\$5.95**
- 8288 Bus Controller **\$9.95**
- 8272 Floppy Disk Controller **\$9.95**
- NEC 765 Floppy Disk Controller (equivalent to 8272) **\$9.95**
- Set of 8088 8255A 5, 8237A 5, 8288, 8284 8253A 5 and 8259A **\$55.00**
- 22716 **\$3.49**
- 22732 **\$3.95**
- 22764 **\$4.95**

LS for IBM Systems

- 02 **\$0.39**
- 04 **\$0.39**
- 08 **\$0.39**
- 10 **\$0.45**
- 20 **\$0.45**
- 27 **\$0.45**
- 30 **\$0.45**
- 32 **\$0.80**
- 74 **\$0.50**
- 138 **\$0.70**
- 158 **\$0.75**
- 175 **\$0.80**
- 243 **\$1.20**
- 244 **\$1.25**
- 245 **\$1.50**
- 273 **\$1.50**
- 322A **\$6.00**
- 323 **\$3.50**
- 373 **\$1.40**
- 374 **\$1.40**
- 377 **\$1.25**
- 670 **\$1.75**
- 7407 TTL **\$1.00**

Hard to get parts for your 6502 Systems and Apple Compatible Peripherals.

- 6502 CPU **\$ 5.50**
- 6845 CRT controller **\$ 9.50**
- 68A45 CRT controller **\$ 9.95**
- Z80A CPU (4 MHz) **\$ 4.99**
- MC3242 **\$11.95**
- 74LS367 **\$ 62**
- 74LS259 **\$ 1.39**
- 74LS161 **\$ 99**
- 74S74 **\$ 82**
- 74S174 **\$ 1.70**
- 74LS323 **\$ 4.55**
- 74LS324 **\$ 4.55**
- Card edge connector (50 pin) **\$ 2.49**
- RCA jack PC mount **\$ 69**
- 6 pin power square connector **\$ 99**
- Pinno jack (small) **\$ 99**
- MPSA 13 trans **\$ 55**
- 2N3904 trans **\$ 19**
- 2N3906 trans **\$ 27**
- MPSU51 trans **\$ 79**
- 2N4258 transistor or equiv **\$ 69**
- 1K SIP 10 pin **\$ 69**
- 1K SIP 8 pin **\$ 69**
- 10K SIP 10 pin **\$ 75**
- 4 pos dip sw **\$ 95**
- 20 pin female header for disk drive **\$ 1.79**
- 20 pin male **\$ 1.69**
- 50 pf trim cap **\$.89**
- 220 ohm trimpot **\$ 69**
- 20 conductor ribbon cable **\$ 89.11**

DELAY LINES

- 100ns delay line **\$5.00**
- 7ns delay line **\$13.95**
- 62 pin edge con (high quality) **\$1.89**
- 5 pin Din conn **\$1.25**
- Power conn **\$1.25**
- Dip switch 8 pos **\$2.49**
- 4.7k x 6 sip **\$.69**
- 4.7k x 8 pin sip **\$.69**
- 8.2k or 10k 16 pin Resistor or network **\$.99**
- 330ohm x 8 network **\$1.10**
- Small speaker **\$1.99**
- 1 uF 50V high quality bypass capacitors **\$.10**
- Trimcap **\$.99**
- 34 pin card edge con for your floppy controller **\$5.95**

S SERIES

- S00 **\$0.75**
- S02 **\$0.75**
- S04 **\$0.75**
- S07 **\$0.75**
- S08 **\$0.75**
- S74 **\$0.85**
- S138 **\$1.75**
- S157 **\$1.85**
- S158 **\$1.85**
- S374 **\$3.25**

MISC

- 75477 **\$1.25**

WE'VE GOT EM!

5-1/4" HALF SIZE DRIVES! FOR IBM PC, TI PC, XEROX 820



- Shugart/Panasonic 1/2 sizes SA455-3AEC **\$169.00**
- TEAC (A Cadillac Drive) 1/2 size FD55B **\$169.00**
- 40 Track per side 48 TPI
- Double-sided, double density
- Same as SA455
- Latest head & drive technology
- Fast access time

QUME

Yes we have the same QUME drives that IBM uses in their IBM-XT system. 40 track, 1/2 height, double sided, double density. The exact ones you need to upgrade your old system or build your clone system up to the max. These are brand new drives that are from QUME's own inventory. They are absolutely perfect, at a perfect price of **\$135.00**

A Guide to Transformers

Some theory and some rules of thumb for getting acquainted with power and audio transformers.

By Bill Markwick

THE TRANSFORMER is usually just one of those black boxes that you don't have to think about much; it sits in your chassis supplying power or changing signal levels to suit the circuit. Once in a while, however, you may decide to build a project or do a replacement and you can't find the exact model you need.

There are enormous numbers and types of transformers for various purposes; we'll be looking at the two largest categories: power and audio transformers. Here's a brief guide to transformer operation and specifications.

Basics

Transformers are usually classed as step-up or step-down. This refers to the *output voltage* compared to the *input voltage*. This applies both to power transformers, and in a more roundabout way, to impedance-matching transformers as well. How the transformer changes the input voltage isn't too complicated, although like anything else, you can make it as complex as you want (we'll stick to finding basic parameters for replacement or simple design).

Imagine a coil of wire suspended in the air. Or you can imagine Brooke Shields or Robert Redford holding it up. Your choice. Now we apply a direct current through it; this creates a magnetic field around the wire. Nonbelievers may hold a compass near it and see the deflection. Unfortunately for those in need of lots of magnetism, you can't get a whole lot out of an air-core. To increase the available magnetic energy, the coil is wound on a *ferromagnetic core*. *My italic key is stuck!* Sorry. As I was saying. You can demonstrate this by winding some wire around a screwdriver shaft and applying an amp or so; the shaft will become magnetized enough to pick up paper clips. Borrow your neighbour's screwdriver if you try this, because it stays magnetized and will drive you crazy later picking up nails and things when you don't want it to.

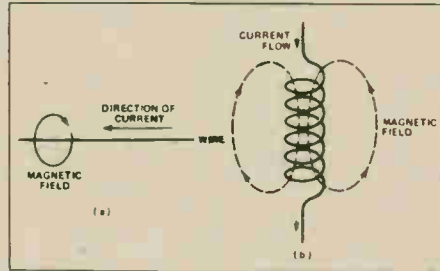


Fig. 1. If an electric current is passed through a coil of wire, a magnetic field is generated; in effect, an electromagnet.

Like all good things, though, there's a catch. First, there's a limit to how much magnetism the metal will store; this depends largely upon the material selected. As the applied current increases, so does the magnetic field until it reaches the limit called *saturation*; after this point is reached, increasing the current causes no further increase in magnetism. This effect is very important when it comes to selecting an audio transformer for low-distortion power applications. A further disadvantage to the metal core is *hysteresis* (pronounced hister-eesis). This effect happens because the field in the ferromagnetic core lags slightly behind the energizing current it it's AC; if the delay is significant, energy is wasted heating up the core. Unless you plan to design your own windings, you won't be bothered much by this; hysteresis effects are minimized by the cleverness of transformer manufacturers.

The energy stored in a coil can be substantial. For instance, you'll often see a reverse-biased diode across the winding of a relay coil. The purpose of this diode is to absorb the energy stored in the coil

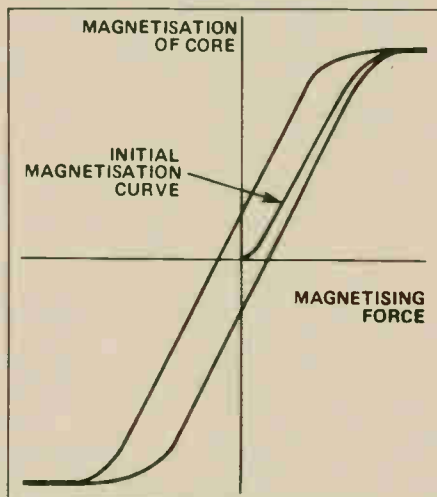


Fig. 2. The hysteresis effect caused by the lag between the magnetising force and the actual magnetism in the core.

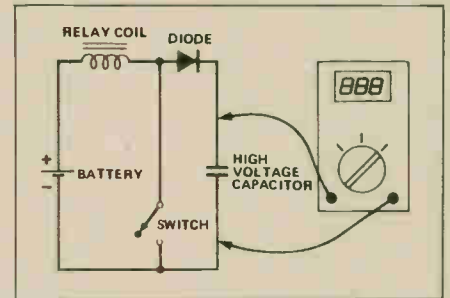


Fig. 3. An experiment to observe the storage of inductive energy in the coil of a relay; the induced voltage can be higher than the battery voltage.

when the driving circuit is switched off. Otherwise, a good-sized reverse voltage is produced, causing an unwanted spike which can feed into signal lines or even damage any transistors driving the relay.

This can be shown by the circuit in Fig. 3. If the switch is turned on and then off, the induced current in the coil will flow through the diode into the capacitor and charge it up above the battery voltage. With a suitable choice of relay (or other coil) and capacitor, much higher voltage can be induced into the capacitor than was originally applied to the coil.

Two Coils

If two coils are wound on the same core, the surge of voltage and current generated as in Fig. 3 will be generated in both coils, because the magnetic field is around both coils. You could connect the power switch and relay to one coil and the diode/capacitor to the other and meter the energy being transferred from one coil to another. This effect is called *mutual inductance* and is the principle of the transformer.

The transfer of energy between coils isn't perfect; there's always some loss, some of it due to the fact that the magnetic field generated doesn't overlap the coils perfectly. This effect is often minimized by designers by specifying *bifilar* winding. In this type of transformer, the wires for both coils are applied together rather than winding one coil, then the other. This increases the coupling between coils.

Power Transformers

They come in two basic types: the E-core and the toroidal. Fig. 4 shows the more common E-core, so-called because its magnetic core is put together from stampings in the shape of Es and Is; this allows the windings to be done easily on rotary machinery. You've noticed that these cores are made up of thin sheets or

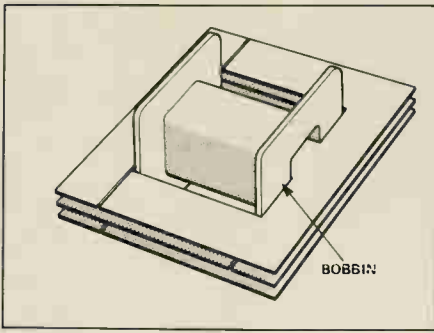


Fig. 4. E and I shaped core leaves on a plastic bobbin.

laminations; the reason is to reduce losses from eddy currents. Just as a coil can induce currents in another coil, current may be induced in the core itself, creating heat and wasting energy. The laminations break up these eddies and reduce them to a fraction of what they would be in solid cores.

The second type of transformer is the toroid; the coils are wound on a donut-shaped core which is itself wound from a strip of magnetic material (Fig. 5). The lack of corners reduces stray fields, and the aligned grain of the rolled iron strip makes it easier to magnetize. This makes them smaller and lighter for a given

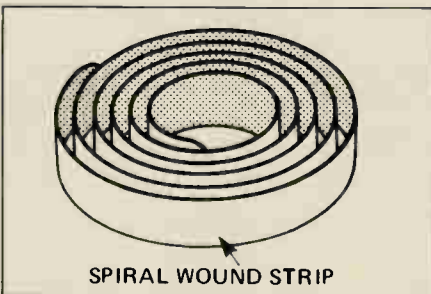


Fig. 5 The core of toroidal transformer is made from a wound strip of magnetic material.

power than the E-cores; in addition, the symmetrical shape reduces the external hum field, important in audio or test equipment.

Power Parameters

Now we come (finally) to the actual characteristics that concern you if you're looking for a new or replacement power transformer. The first one is the voltage step-up or step-down, directly determined by the *turns ratio*. If you have 500 turns on the input (primary) side, and 100 turns on the output (secondary) side, then the turns ratio is 5:1 and the output voltage will be equal to the input divided by five. As we've mentioned often in these pages, transformer voltage ratings are specified, for example, as either 12VCT (Volts Centre Tapped) or 6-0-6; both mean the same thing and both are RMS voltage ratings.

Electronics Today October 1985

The next problem is to determine the current rating. This is a bit more complex, because it depends entirely on the sort of load the transformer will be driving. If the load is a resistor, which is possible but used less often, you can take the ratings at face value: if you need 1 amp at 25VAC across your resistor, you specify a 1 amp, 25V transformer. However, the majority of applications call for conversion of the output to DC using one of the many methods available. The method of rectification determines the ratings of the transformer. Onward:

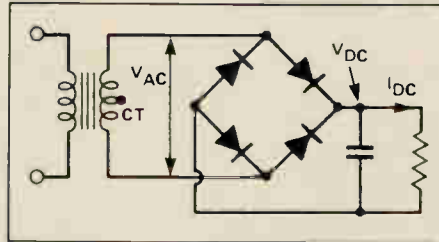


Fig. 6. The conventional full wave rectifier discussed in the text; 0.68 ohm resistor was added between the diodes and the capacitor for monitoring the charging current.

Figure 6 shows the typical full wave bridge with a capacitor input, used for the majority of rectifier circuits because it uses the available secondary energy in the most efficient way. First, we work backwards from the desired DC voltage. Let's say that you want a 35VDC supply. The secondary AC voltage for a no-load condition is:

$$VAC = VDC \times .707$$

The capacitor is charged to the peak value of the AC sine wave, which happens to be 1.414, or root 2, times the RMS

value; working backwards to find the secondary AC produces the .707 factor. This neglects the voltage drop across the diodes, and gives us a no-load secondary voltage of about 25VDC.

The problem here is that the transformer output voltage will sag somewhat under load, and the diode voltage drop increases a bit with current; the diode drop is especially important in lower voltage supplies. Here's another rule-of-thumb which takes these factors (and others) into account, and is taken from a nifty chart in a catalogue available from the L.H. Frost Co. (see the list at the end):

$$VAC = 0.8(VDC + 2)$$

Now we find that our secondary voltage under load works out to 29.6VAC. Huh? This seems a bit high compared to the original estimate of 25.

The reason for this is that the current drawn from the transformer is non-sinusoidal. Let's go over the setup so far. I tested a full wave capacitive rectifier as shown in Figure 6; the only difference was the insertion of a 0.68 ohm resistor between the rectifier and the capacitor in order to scope the capacitor charging current. The transformer was a 25 volt, 150mA unit, the capacitor was 2200uF, and the load resistor was 460 ohms, giving a load current of 76mA. Note that the transformer voltage rating applies only at the full load current into a resistor; it will rise a bit under lighter loads. Spec sheets usually give you the range of output voltages you can expect under different load conditions.

At 76mA, the secondary voltage metered as 29.5VAC and the capacitor

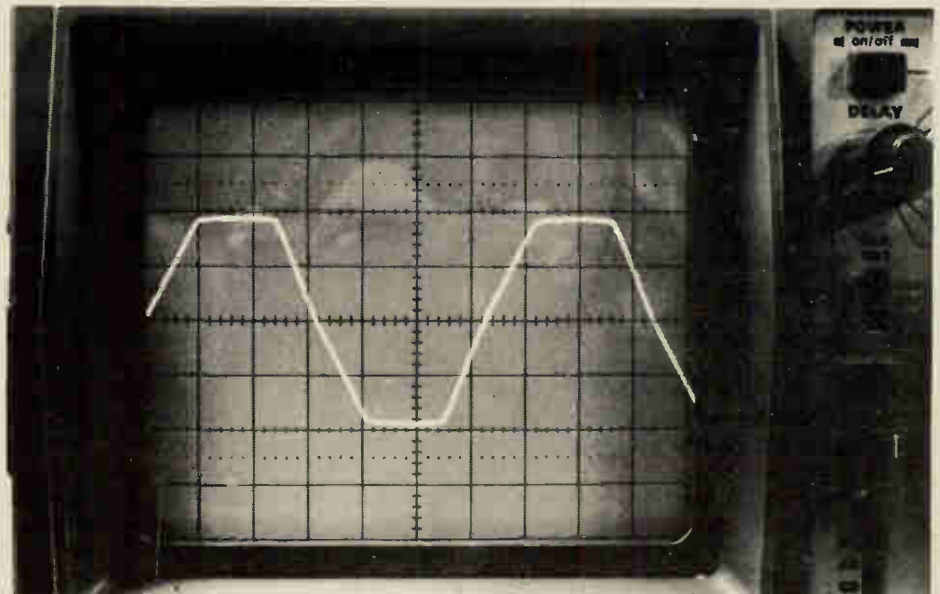


Fig. 7. The secondary AC voltage of the transformer under load; the rush of charging current into the capacitor flattens the peaks.

voltage was 35VDC. If you multiply the 29.5 by 1.414 to find the expected peak, you get about 42 volts instead of the measured 35. The reason for the discrepancy here can be seen from the photograph in Fig. 7. The peaks of the sine wave are clearly flattened; this is the point where the rising voltage from the secondary exceeds the stored capacitor voltage, the diodes turn on, and the capacitor draws a large current as it charges up again.

In the photo in Figure 8, the scope has been placed across the 0.68 ohm resistor to monitor the charging current. Since the scope was set at 100mV/div, the peak voltage is about 280mV, and therefore the peak charging current is about 410mA, considerably higher than the transformer's rated continuous value of 150mA. Note that each positive-going peak corresponds to one of the peaks of the AC waveform from the secondary.

It's this non-sinusoidal waveform out of the secondary that throws things into a cocked hat. Voltmeters, either digital or analog, respond to the average value of the applied waveform. This value is then increased artificially, either by the digital circuitry or the analog meter face, to show you what the RMS value would be if the input were a pure sine wave. Unless your meter says "True RMS" on it, this will be the case, and the reason that the volts don't seem to match up where they should.

Check out the peak value of the waveform in Figure 7; at 20V/div, the peak value is about 38 volts. After hazarding the journey through the rectifier diodes and the 0.68, our rectified and smoothed peak voltage is now 35V, agreeing with the rule of thumb from the good folks at L.H. Frost.

Here are two more handy equations for the circuit in Figure 6:

$$IAC = 1.8 \times IDC$$

$$VA = 1.4 \times (\text{watts} + 2IDC)$$

The Mysterious VA

The "watts" mentioned above is just the DC volts times the DC load amperes, but you may have noticed that transformers are rated using the VA (volt-ampere). The essential difference is that the VA implies the possibility of phase shift between the current and the voltage. In a purely resistive circuit with an AC signal, the current changes are exactly in step with the voltage changes, as you'd expect. In a circuit containing inductance, such as a transformer/rectifier, the current can happen at a different part of the cycle than the voltage; in other words, you can't multiply volts times amps to get watts because the volts and amps don't occur together. VA is not true power, but an indication of the volts and amps needed under reactive conditions.

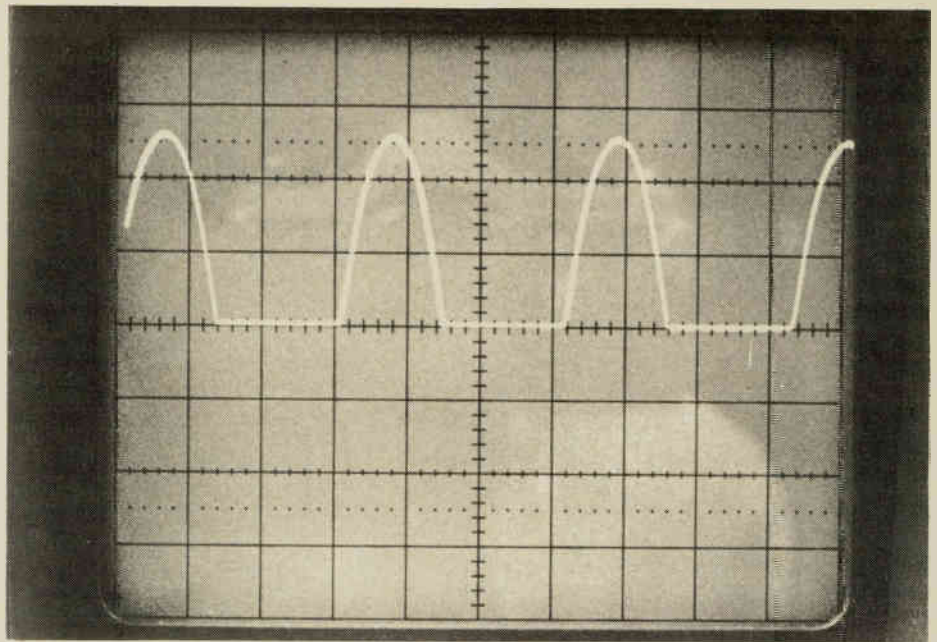


Fig. 8. The bursts of charging current as the diodes switch on can be seen by putting the scope leads across a resistor in series with the capacitor.

The VA rating has to be considerably higher than you'd expect in order to allow for peculiarities such as the sudden bursts of current as the diodes switch in and out of conduction. In our test circuit, the resistor dissipates 2.66 watts, and the VA rating works out to about 4VA.

Taps

Most commercially available transformers have a centre tap. If you're concocting a power supply from scratch, you probably wondered about the choice between a full-wave (Figure 6) and a centre-tapped (Figure 9). Simple: if you're building a low voltage supply, perhaps less than five volts, the voltage drop across the diodes becomes a significant part of things. By specifying the CT type, you only need two diodes and the transformer VA rating can be reduced a bit. However, it isn't quite as efficient as the full wave because the secondary isn't fully utilized; only half of it works at a time. Because of this, the VA rating will have to be fractionally higher than the full wave version. Remember that the voltage rating must be twice as high as the full wave type; our 25V transformer in the example would have to be a 50VCT, or 25-0-25.

The main use for the centre tap is in producing the familiar supply with lots of names: symmetrical, bipolar, or split. These put out both positive and negative voltages for use with op amps, power amps, etc. They're really just a variation on the full wave of Figure 6; the output is simply split in the middle by calling the centre tap zero-volts or ground. The beginner may be confused into thinking that there are two different kinds of electricity, positive and negative, but it's not so; it's all in how you designate it. If we

used two series capacitors in Figure 6 and connected the centre tap to their mid-point, we'd have plus-and-minus 17.5V instead of 35V. If we move the ground connection to the bottom capacitor's negative, and call that "ground", then we now have a supply with 17.5 and 35 volts. It's all in the labels. Our rules of thumb from Figure 6 still apply to the split version.

Audios, amigo

I won't go into immense detail on the audio transformer because they're largely out of favour these days. At one time they were used all over the place, especially in microphone inputs because they furnished voltage gain, and in those days gain stages cost a lot of money (no gain without pain). Now that we have all kinds of complex circuits integrated onto chips for next to nothing, the transformer has been relegated to providing balanced lines in professional audio, and even then they're being replaced with differential amplifiers.

The idea of the balanced line is simple: because the transformer will transmit only those voltages which appear across its primary, it rejects signals which appear

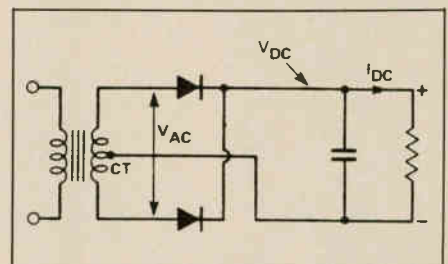


Fig. 9. The centre-tapped full wave version of the supply shown in Fig. 6.

equally on both primary terminals ("common mode signals"). Microphone and output lines are usually twisted pairs running into a transformer, and since the lead is symmetrical, noise and hum are induced on both wires with equal phase and voltages, and they get cancelled out by the transformer. The pair also has a grounded shield or braid, which is why some audio cables have three wires instead of the expected two. Good audio transformers may reject low-frequency common-mode signals by as much as 75 dB or more. High-frequency interference tends to jump from the primary into the secondary via the inevitable stray capacitance; this can be reduced by looking for a transformer with an electrostatic shield between primary and secondary. This shield is connected to ground via the chassis.

In selecting a microphone transformer, the turns ratio and impedance ratio are important; the turns ratio squared gives the impedance ratio. For example, a transformer with a 1:10 turns ratio will step up the voltage by 10 and the impedance by 100. If you drive the transformer primary with a 250 ohm microphone, the impedance looking into the secondary is 25,000 ohms.

Impedance matching is important with an audio transformer, particularly on

professional equipment. If serious mismatches occur, the most likely result will be either poor low-frequency response (source too large or load too low) or a boost in the high end (source too low or load too large). However, there's some elbow room if you can't find the exact model that you need. The general rule for fudging trannies is: select a model that has the turns ratio that you need (mike trans almost always have 10 to 20dB in gain, a turns ratio spread of 3.2 to 10). Check the impedance specs; the primary should be *more* than the driving load, and the secondary should be *less* than the secondary load.

An example: a PA amp requires a replacement transformer. Microphones are mostly 150 ohm low impedance types, and the secondary feeds a transistor amp with about 40k input impedance.

Thumbing through a Hammond catalogue turns up the 809, a broadcast-quality transformer with a 200 ohm primary and 10,000 ohm secondary. A nice bit of luck; if the impedances don't turn out to match this closely, you can always mismatch by 100 percent, or even more (who said that?). The 809 has an impedance ratio of 1:50. Taking the square root gives the turns ratio, or 7.07. The voltage gain in dB is: $20 \log 7.07 = 17\text{dB}$

This should be fine as is, but check the frequency response anyway. If you find a boost in the treble, it may be necessary to load the secondary with a resistor sub box until you find a value that smooths it out. Will the 17dB of voltage gain overload the input amp during use? Maybe. It all depends on the circuit; if you know the original equipment transformer gain, you should try to stay within 3 or 4dB of the original.

I'm out of room already, and I didn't even get to audio output transformers or autotransformers or tuned types. There's an excuse for another article in an upcoming issue. ■

For further information, catalogues, etc., contact:

Hammond Engineering,
394 Edinburgh Rd.,
Guelph, Ontario N1H 1E5,
(519) 822-2960


L.H. Frost Limited,
1130-Eighth Line,
Oakville, Ontario L6H 2R4,
(416) 844-6681

ILP toroidal types:
EDG Electronic Distributors,
3950 Chesswood Dr.,
Downsview, Ontario M3J 2W6,
(416) 636-9404

NEW 1986 CATALOG

CIRCLE READER SERVICE NO. FOR FREE COPY

THIS MONTH'S SPECIALS

Memories  **D-RAMS**

4116	16K	1.59
4164	64K 150ns	2.39
4164	64K 200ns	1.99
41256	256K 150ns	9.39


EPROMS


2732A	4K x 8 300ns	32K	5.99
2764	8K x 8 300ns	64K	5.99
27128	16K x 8 300ns	128K	10.79
27256	32K x 8 250ns	256K	18.49


STATIC RAMS

5516-25L	2K x 8 250ns	16K	5.09
6116-25L	2K x 8 250ns	16K	5.09

ALL NEW CURRENT PRODUCTION PRODUCTS

 TEXAS INSTRUMENTS




 MOTOROLA

 Advanced Micro Devices

FULL LINE OF MICROPROCESSORS AVAILABLE

WE ALSO STOCK...

- Books • Breadboard & Accessories
- Capacitors • Chemicals • Connectors
- Crystals • Plugs & Jacks • Fans
- Enclosures • Filters • Fuses • Heat Shrink Tubing • Heat Sinks • Kits
- Knobs • Peripherals • Probes • Oplo
- PCB Products • Potentiometers ...

USA
P.O. BOX 9100
WESTBOROUGH, MASS
1-800-343-0874

Active

CANADA
5651 FERRIER ST.
MONTREAL, QUEBEC
1-800-361-5884

MAIL ORDERS
SHIPPED WITHIN
24 HOURS

OUR ELECTRONIC
COMPONENTS
CENTER

CURRENT DATE
CODE PRODUCTS
VOLUMES • UNITS

SELF SERVE STORES LOCATED NEAR YOU. JUST CALL...

WESTBOROUGH, MASS.
366-9684

OTTAWA, ONT.
728-7900

EDMONTON, ALTA.
438-5888

BELLEVUE, WASH.
881-8191

TORONTO, ONT.
977-7692

CALGARY, ALTA.
235-5300

MONTREAL, QUEBEC
731-7441/256-7538

DOWNSVIEW, ONT.
630-0400

VANCOUVER, B.C.
438-3321

Circle No. 19 on Reader Service Card

PROFESSIONAL BASIC™

Powerful Yet Affordable

\$139.00

"marvelous" Jerry Pournelle - BYTE

Use 640k (e.g. 250 x 250 array)

Dynamic Syntax Checking

19 Debugging Windows

Run PC BASICA Programs

OPTIONAL: 8087/80287 Support — \$70.00

M

Morgan Computing Co., Inc.

(514) 485-2100

Distributed in Canada exclusively by:

COMPUTIQUE


5875 Cavendish Blvd. Suite 104

Montreal, Quebec H4W 2X9

plied through the component via banana jacks on the front panel, and goes to the scope's vertical and horizontal circuits. A good diode, for instance, will display a straight line (no conduction) up to about 600mV, where the trace will angle sharply to show increasing current under the forward bias conditions.

Other features include TV sync and sync separator circuits for optimum triggering of the sweep during TV testing. It comes with dual probes that can be set to 1:1 or 10:1. Price is \$654.50 from Duncan Instruments, 121 Milvan Drive, Toronto, Ontario M9L 1Z8, (416) 742-4448.

Circle No. 54 on Reader Service Card

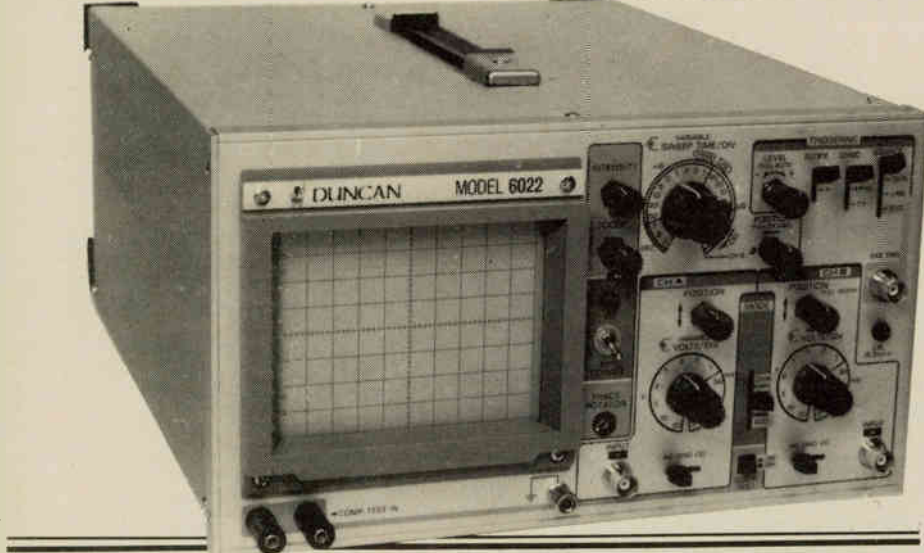

Duncan 3015

Also from Duncan Instruments (see model 6022 above) is the model 3015 Dual Trace Portable. Easy portability is the dream function for field servicing, and the 3015 fills the bill by running from 90 to 260 VAC power lines from 48 to 440Hz, NiCads with internal recharger, and DC from 11 to 30V. It has 15MHz bandwidth, a 3.8 inch CRT, 2mV/div vertical sensitivity and a comprehensive trigger amp, making it just about ideal for taking your show on the road. The price is \$951.50.



tions links such as GPIB and RS232. Signal averaging can be used to salvage the signal from noisy environments. Others in the family include the 2230 and 2240, with various extra features such as increased bandwidth, glitch capture to 2nS, and a controllable cursor for on-screen measurements. Contact the Marketing Communications Department, Tektronix Canada Inc., PO Box 6500, Barrie, Ontario L4M 4V3, (705) 737-2700.

Circle No. 56 on Reader Service Card

B&K 1596

The B&K Model 1596 is a quad input scope. Remember quad sound? Edsels? Nothing to do with it. The 1596 can parade four waveforms, just the ticket for analyzing data circuits. The vertical sensitivity is 500uV/div up to 70MHz, and 5mV/div at 150MHz. There's also a Dual function in which the A sweep and B sweep operate independently; two signals can be viewed with different sweep times, a fairly unusual feature. At 7.4kg the




Circle No. 57 on Reader Service Card

Model 1596 is suitable for either bench or field use. List price is \$4555.85. Contact Atlas Electronics, with sales offices in Montreal, Ottawa, Winnipeg, Calgary and Vancouver, or the head office at 50 Wingold Avenue, Toronto, Ontario M6B 1P7, (416) 789-7761.

Hitachi V-1100A

The Hitachi V-1100A's primary feature is cursoring capability and a digital multimeter display on the CRT. Moving the cursor dots between two points on the display is not only a super-convenient way to measure waveforms, but it eliminates guesswork and errors. The 1100A's CRT displays scope setting information, cursor locations and values, DVM values, and programmable text (8 lines of 30 characters each).

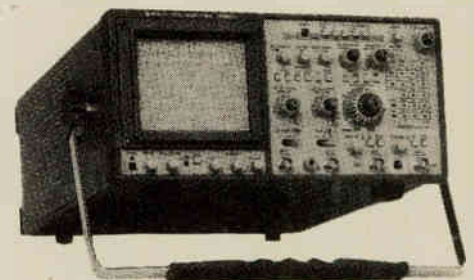Vertical sensitivity is 5mV/div (1mV/div with x5 control) and the bandwidth is 100MHz; the CRT is a 6-inch. The cursor measurement facility has a resolution of .01V/div; list price is \$3978 including FST. Contact their offices in Nepean (Ont.), St Laurent (Que.), Calgary, or the head office: Hitachi Denshi, Ltd., (Canada), 65 Melford Drive, Scarborough, Ontario M1B 2G6, (416) 299-5900.




Circle No. 58 on Reader Service Card

Leader 5825

The Leader LBO 5825 is yet another digital storage scope. If you haven't used a storage scope yet, and wonder why there are so many around these days, upgrading to a storage is like going from a slide rule to a computer. The 5825 is a 35MHz real time scope, or 500kHz in dual channel storage mode. There are memories for each channel; the memory permits four waveforms on two channels to be stored


Electronics Today October 1985

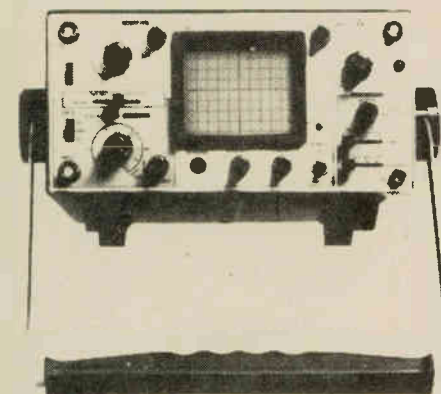

Circle No. 55 on Reader Service Card

Tektronix 2220

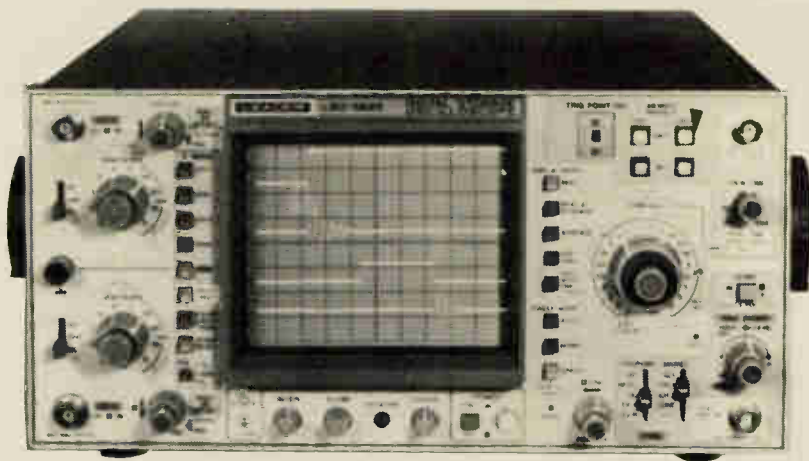The Tek 2220 is one of a new family of scopes combining both storage functions and portability. It has 60MHz bandwidth, which should be adequate for checking your Silvertone guitar amp, TV-pre-post triggering, glitch capture to 100nS, an analog output, and optional communica-



and displayed simultaneously, and if a waveform in the Real Mode is included, six waveforms may be displayed. A battery backup holds the memories for up to two weeks with the power off. List price is

Circle No. 60 on Reader Service Card

\$4995 from Omnitronix, 2410 Dunwin Drive, Unit 4, Mississauga, Ontario L5L 1J9, (416) 828-6221, or 8100F Trans-Canada Highway, St. Laurent, Quebec H4S 1M5, (514) 337-9500.



Gould 1425

Another advantage from the proliferation of microchips is the ability to have your scope converse with a computer for the analysis or control of whatever's under test. Several of the scopes listed above have outputs for interfacing, and the Gould 1425 is no exception. It's a dual trace, 20MHz storage scope that offers on-screen measurement of time and voltage via cursors and an alphanumeric readout; data can be read to and from an external computer via an RS232/RS423

serial interface. The interface can also drive a plotter for copying of the trace. The optional Type 125 waveform processor keypad allows waveforms to be stored, magnified, attenuated, transferred, averaged, filtered, etc. The 1425 lists at \$4204, taxes extra. From Allan Crawford Associates, Electronic Instruments and Systems Division, 5835 Coopers Ave., Mississauga, Ontario L4Z 1Y2, (416) 890-2010. ■

Circle No. 59 on Reader Service Card

write:

**NATIONAL
ELECTRONICS**

Box 6883

Stn. Q

TORONTO, CANADA, M4T 2N5

NON*

1498

8088

COMPUTER

SPECIAL FREE TRIAL

*** LIMITED TIME OFFER**

FULLY COMPATIBLE
256K MEMORY
8 EXPANSION SLOTS
8 ROMS OK
8087 OK
MEGA - BIOS
TWO SLIM DRIVES 360K DS/MS
COLOUR VIDEO
DISK CONTROLLER
130 WATT SUPPLY
KEYBOARD
FLIP-TOP CASE

\$34.95

Timex Software \$3.75 each

Autor The Gator • Allen Spaceship • American Shootout • Blackjack • Basic Course 1 • Basic Course 2 • Backgammon • Crown Specter • Constellation • Chess 16K • Capitalization Master • Flashcard • Games Pack • Games Pack 1K • Games Pack 2K • Galactic Commando • Grimm's Fairy Tales • 80 Hours Around Europe • Inheritance • Invaders • Inventory Control • Krakit • Movie-Hangman • Marine Rescue • Mixed Game Bag 1 • Mixed Game Bag 2 • Money Analyzer • Protector • Planet of Fear • Program of Days • Portfolio Analysis • Power Pack • Punctuation Master • Personal Finance Planner • Pop Star • Run The Country • Real Estate Investment Analysis • Ram Runner • Slots • Super Math • Stock Market Game • Supermaze • Statistics • Tic Tac Toe 3D • Tiny Logo • Time Machine • Top Secret • Trackdown in the Old West • The Budgeter • The Chequebook Manager • The Cube Game • The Challenger • The Flight Simulator • The Gambler • The Home Improvement Planner • The Loan/Mortgage Amortizer • The List Manager • The Organizer • The Puzzler • The Stock Option Analyzer • VU-File • VU-Calc • ZX Chess 1K • ZX Chess 2K • ZX Chess 1 Enhanced • ZX Bug • Zombies • ZOR • The Business Pack I • The Business Pack II.

ORION
5XT IBM XT
COMPATIBLE

~~\$1495.00~~
\$1395.00

Includes:

• 256K Memory • 8 Expansion Slots • One 360K DS/DD Disk Drive • Parallel Port • 135 Watt Power Supply • Choice of Colour or Monochrome • Card • Serial Port • Game Port • Clock

Lotus 1-2-3™
Flight Simulator,
d Base II
™ Super Calc, Visi
Calc and others.

IBM Compatible Boards

- 1F01 256K Multifunction (S/P/C) - OK \$175.00
- 1F02 384K Multifunction (S/P/C/G) - OK \$249.00
- 1F03 256K RAM Ver 11 - OK \$ 89.00
- 1F03 512K RAM Ver II - OK \$135.00
- 1F05 Color Graphic (2-Layers) \$159.00
- 1F06 Monochrome \$159.00
- 1F07 Mono-Graphic with printer port \$239.00
- 1F08 Multi I/O (S/P/C/G/FDC) \$245.00
- 1F09 I/O 11 + (S/P/C/G) \$149.00
- 1F11 Parallel Printer (Cable extra) \$ 39.00
- 1F12 Serial - RS232C \$ 59.00
- 1F13 Game \$ 35.00
- 1F14 Floppy Drive Controller + Cable \$ 99.00
- Disk Drive for IBM \$165.00

IBM Hard Disk Drives

100M External \$ 995.00 10M Internal \$ 995.00
w/power supply \$ 995.00 20M Internal \$1395.00

Diskettes (Box of 10) Lifetime Warranty

Datatech SS/DD \$15.95
Datatech DS/DD \$19.95
No Name Box of 10 \$12.50
Orion Dark Letters Diskettes SS/DD \$ 14.95
Orion Dark Letters Diskettes DS/DD \$17.50

Complete System for \$699.00

4164 RAM **99c ea.**
Quantity - 50

• 6502 Micro processor • 48K memory • Disk drive
• Disk controller card • Upper/lower case • Hi-res Amber monitor • Colour graphics • Numeric Function Key • 90 day warranty.

Orion Electronic Supplies Inc.
40 Lancaster Street West
Kitchener, Ont. N2H 4S9
(519) 576-9902

Discover a new line of IBM Personal Computer Software



Note: These IBM Personal Computer Software Products are not available in Quebec.

IBM is a registered trademark of International Business Machines Corporation. IBM Canada, a related company, is a registered user.

From as low as

\$24.99

Personally Developed IBM Software programs with value in mind

Choose from

- Business applications
- Entertainment ■ Education
- Programming ■ Productivity
- 58 programs in all

■ PLUS Special Value Packages to save you even more money!

Call IBM Canada Ltd. today for your

FREE CATALOGUE

While quantities last.

1-800-387-6100

Circle No. 13 on Reader Service Card

We Import Direct and We Service What We Sell
BEST QUALITY INSTRUMENTS AT LOWEST COST!
Why Pay More? . . . Just a Few Examples:



DMM 601
3½ dig. 0.25% acc.
0.1 mV - 1000 VDC
0.1 uA - 2 A AC/DC
0.1 mV - 750 VAC
0.1 ohm - 20 M ohms
Safety test leads incl.

\$63.90

Dmm 6010 (same as 601) except: max. 10 A AC/DC

\$69.50

Synthesized R.F. Generator SD 1003



8-512 (Model SD1004 MAX 1060 MHz) AM .O-90% FM In 10-30-100KHz steps. Output attenuation in 10dB steps with Vernier Fine Control. Price 30-40% below "Industry Standard" prices at \$3,600.00

OSCILLOSCOPE 33330

- 2 Chan.
20MHz bandwidth
Built-in components tester
5 mV vert. sensitivity
Special Price \$495.00
In areas not served by distributors.
Probes extra.



Precision Analog Multimeter Model 5050E

• Input resistance, 10M Ω /DC
• 43 measuring ranges

• AC/DC current max. 12A

Introductory Price **\$67.50**



Model 605 RF Generator

100KHz - 70 mHz
On fundamentals

Introductory price **\$183.00**

Authorized Distributor:

Waterloo Electronics Supply Co. In. 219 Hartwood Ave., Waterloo, Ont. 745-9421.

Mall Orders: Visa, Certified Cheque, Money Order or C.O.D.'s F.O.B. Oakville, Ontario residents add 7% P.S.T.

KB ELECTRONICS
355 Iroquois Shore Rd., Oakville, Ont. L6H 1M3
(416) 842-6888 Telex 06-9823 (KBEL OKVL)

The Electronics Today Electrivia Contest Results

AND THE the grand winnah of our July/August contest is... Bill Markwick, editor of Electronics Today!!! Well, thank you, thank you, I know I'll enjoy this computer for many years to come... what? I can't? Why not? What contest rules? Okay, okay, I'll draw again. This time, the winner is:

Terry Wong
118th Avenue Edmonton, Alberta

Our congratulations on your new computer.

Here are the correct answers. Since the contest was finally decided by a draw, we marked as liberally as we possibly could without being unfair to those who had gone to a lot of effort researching the questions. There were over 200 entries with correct answers.

1. The relationship between sound intensity and distance is governed by the Inverse Square Law, or the reciprocal of D squared. It doesn't matter what unit you select for measuring the sound; it falls off inversely with the square of the distance. A lot of readers got sidetracked onto the measurement units for intensity, using decibels and the Weber-Fechner law and so forth.

Inverse-square was the magic word.

2. The common-base equivalent of Beta (current gain) is Alpha, or HFB, or Ic/Ie. We also accepted other mathematical equivalents or the Greek character for Alpha.

3. False. The Wheatstone bridge, named after Charles Wheatstone, was developed by Samuel Christie in 1833. Some readers wrote False because we forgot the "Sir" in Charles' name. We gave it to you anyway.

4. The oscilloscope figures resulting from similar signals applied to horizontal and vertical inputs are called Lissajous patterns. Some readers put only special cases, such as the circle or the ellipse. We were generous.

5. True. The turns ratio of a transformer is indeed equal to the root of the impedance ratio.

6. The Bel, the log of a power ratio, was named after Alexander Graham Bell. We also accepted the decibel or dB.

7. The voltage gain of an analog buffer is one, or unity, or zero dB. A lot of entrants put "close to one", which we accepted because it's generally true, but we didn't accept "zero" unless you mentioned decibels.

8. An asynchronous counter is also known as a ripple, or serial, counter. We were liberal on this one, accepting such entries as "ring counter", even though it's a special case of the ripple counter.

9. The algebra used in logic was named after George Boole, 1815-1864. We had to turn down the several "Boolean algebra" entries on the grounds that the question wasn't read closely.

10. True. Maximum power is transferred when the source and load resistances are equal.

Many thanks to the nearly 1,000 readers who entered the contest. We'll have another one coming up in a future issue.

Moorshead Publications Order Form

Subscriptions:

Please complete reverse side of order form to start or renew a subscription.

Back Issues: \$4.00 each; Ontario residents add 7% sales tax.
Please circle issues desired.

1977	February					July
1978	April	May	September	November	December	
1979	February		March	April	May	July
	August		September	October	November	
1980	January	February	May	June	November	December
1981	January	February	March	April	June	July
	August	September	October	November	December	
1982	January		March	April	May	June
	July	August	September	October	November	December
1983	January	February	March	April	May	June
	August	September	October	November	December	
1984	January	February	March	April	May	June
	July	August	October	November	December	
1985	January	February	March	April	May	June
	July		August		September	

On the following items please add \$1.00 for postage and handling plus 7% Ontario provincial sales tax.

Special Publications:

ITEM	QTY	AMOUNT
Hobby Projects \$3.95	\$
Electronic Circuit Design \$3.95	\$
Projects Book No. 2 \$3.95	\$
Personal Computer Guide \$3.95	\$
50 Top Projects \$4.95	\$
Your First Computer \$3.95	\$
Computers in Small Business \$3.95	\$

Binders: Electronics Today; Computing Now!
 Moorshead Publications
\$9.75 each plus 7% P.S.T.

BOOKSHELF ORDER FORM

Code (e.g. BP12)	Title (Short-form is O.K.)	Price
.....	\$
.....	\$
.....	\$
.....	\$
.....	\$

SOFTWARE ORDER FORM

.....	\$
.....	\$
.....	\$
Sub Total	\$
Tax (Ontario Residents)	\$
Postage	\$
Total Enclosed	\$

Orders from the Bookshelf are tax exempt. Please add \$1.00 for postage. Remember to put your name and address on reverse side. See over for mailing details.

Do you currently subscribe to Electronics Today Yes No Computing Now! Yes No Computers in Education Yes No Software Now Yes No

BE SURE OF YOUR ISSUE EACH MONTH. SUBSCRIBE TODAY.



BOOKS, BACK ISSUES, SPECIAL PUBLICATIONS, BINDERS — SEE OVER

Moorshead Publications

Suite 601, Overlea Blvd., Toronto, Ontario M4H 1B1.

MERCHANDISE ORDER Please fill out form overleaf

SUBSCRIPTIONS: NEW SUBSCRIPTION RENEWAL

Electronics Today

One year (12 issues) **\$19.95** Two years (24 issues) **\$34.95.**

Computing Now!

One year (12 issues) **\$22.95** Two years (24 issues) **\$37.95**

Computers in Education

One year (10 issues) **\$25.00** Two years (20 issues) **\$45.00**

Software Now!

One year (12 issues) **\$19.95** Two years (24 issues) **\$34.95**

For U.S. please add \$3.00 per year other countries add \$5 per year

NAME _____

ADDRESS _____

TOWN/CITY _____ PROVINCE/STATE _____

CODE _____ DATE _____

POSTAL CODE _____

Cheque enclosed **DO NOT** send cash

Mastercard Account No. _____

Visa Account No. _____

American Express Account No. _____

Expiry Date _____

Signature _____

THE ELECTRONICS TODAY RADIO DISGUISER/MAGAZINE BINDER



When you're on a secret surveillance mission, you can't very well stick your walkie-talkie up to your ear and send a report when you're surrounded by bikers. The Electronics Today Radio Disguiser/Magazine Binder lets you look real cool while you talk to headquarters.

When you get home, you can then use it to store 12 issues of Electronics Today without cutting or punching. Available with Moorshead Publications or Electronics Today imprint (please specify).

You'll be the best-read, best-disguised surveillance officer in the district, and your magazines copies will be organized for easy future reference. Oh, yes, one more thing. When you're on a stake-out, don't forget to take off your hat.

Binders are \$9.75 each; Ontario residents please add 7% sales tax. Send to:

**Binder,
Moorshead Publications,
Suite 601, 25 Overlea Blvd.,
Toronto, Ontario M4H 1B1**

ALMOST FREE SOFTWARE

OFFER

Moorshead Publications

Almost Free Software

Almost Free Software (CP/M) #1

Almost Free Software #1, #2 and #3 are for CP/M and are available in a variety of formats: Apple // + CP/M, 8 inch SSSD*, Access Matrix, Morrow Micro Decision, Superbrain, Xerox/Cromemco*, Epson QX-10VD, Sanyo MBC 1000, Nelma Persona, Kaypro II, Osborne and double densities, Televideo, DEC VT-180, Casio FP-1000, Zorba.

Modem 7. Allows you to communicate with any CP/M based system and download files. Complete details were in Computing Now! November 1983.

PACMAN. You can actually play PACMAN without graphics, and it works pretty fast.

FORTH. A complete up-to-date version of FIG FORTH, complete with its own internal DOS.

DUU. The ultimate disk utility allowing you to recover accidentally erased disk files, fix gorged files, rebuild and modify your system. A real gem.

D. A sorted directory program that tells you how big your files are and how much space is left on the disk.

USQ/SQ. Lets you compress and uncompress files. You can pack about 40% more stuff on a disk with this system.

Finance. A fairly sophisticated financial package written in easily understandable, modifiable Microsoft BASIC.

BADLIM. Ever had to throw out a disk with a single bad sector? This isolates bad sectors into an invisible file, making the rest of the disk useable.


DISK. Allows you to move whole masses of files from disk to disk without having to do every one by hand, you can also view and erase files with little typing.

QUEST. A "Dungeons and Dragons" type game.

STOCKS. This is a complete stock management program in BASIC.

SEE. Also known as TYPE17, will TYPE any file, squeezed for not allowing you to keep documents in compressed form while still being able to read them.

**Order as AFS #1,
and specify system**

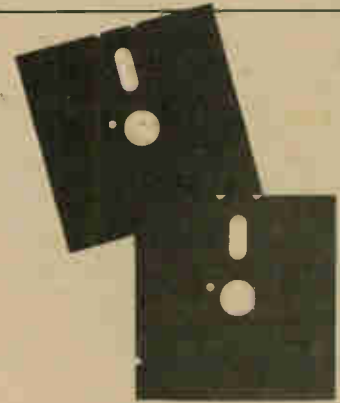

\$19.95 each

Except for 8" disks and those with two disks which are marked with an asterisk (*) above which are:

\$22.95

*single density formats require two disks. The package cost for these formats is \$22.95.

Almost Free Software (CP/M) #2

BISHOW The ultimate file typer, BISHOW version 3.1 will type squeezed or unsqueezed files and allow you to type files which are in libraries (see LU, below). However, it also pages in both directions, so if you miss something, you can back up and see it again.

LU Every CP/M file takes up unnecessary overhead. If you want to store lots of ata in a small space, you'll want LU, the library utility. It permits any number of individual files to be stored in one big file and cracked apart again.

MORTGAGE This is a very fancy mortgage amortization program which will produce a variety of amortization tables.

NSBASIC Large disk BASIC packages, such as MBASIC, are great . . . and very expensive. This one, however, is free . . . and every bit as powerful as many commercial programs. It's compatible with North Star BASIC, so you'll have no problem finding a manual for it.

RACQUEL Everyone should have one printer picture in their disk collection.

Z80ASM This is a complete assembler package which uses true Zilog Z80 mnemonics. It has a rich vocabulary of pseudo-ops and will allow you to use the full power of your Z80 based machine . . . much of which can't be handled by ASM or MAC.

VFILE Easily the ultimate disk utility. VFILE shows you a full screen presentation of what's on your disk and allows you to mass move and delete files using a two dimensional cursor. It has heaps of features, a built-in help file and works extremely fast.

ROMAN This is a silly little program which figures out Roman numerals for you. However, silly programs are so much fun . . .

CATCHUM If you like the fast pace and incredible realism of Pacman, you'll go quietly insane over Catchum . . . which plays basically the same game using ASCII characters. Watch little "C"'s gobble periods while you try to avoid the delay "A's" . . . it's a scream.

**Order as AFS #2
and specify system**

\$19.95 each

Except for 8" disks and those with two disks which are marked with an asterisk (*) above which are:

\$22.95

*single density formats require two disks. The package cost for these formats is \$22.95.



Almost Free Software (CP/M)#3

OIL. This is an interesting simulation of the workings of the oil industry. It can be approached as either a game or a fairly sophisticated model.

CHESS. This program really does play a mean game of chess. It has an on-screen display of the board, a choice of colours and selectable levels of look ahead.

DEBUG. The DDT debugger is good but this offers heaps of facilities that DDT can't and does symbolic debugging... it's almost like being able to step, trace and disassemble through your source listing.

DU87. The older DUU program does have some limitations. The version overcomes them all and adds some valuable capacities. It will adapt itself to any system. You can search map and dump disk sectors or files. It's invaluable in recovering damaged files too.


ELIZA. This classic program is a micro computer head shrinker... it runs under MBASIC, and with very little imagination, you will be able to believe that you are conversing with a real psychiatrist.

LADDER. This is... this program is weird. It's Donkey Kong in ASCII. It's fast, bizarre and good for hours of eye strain.

QUIKKEY. Programmable function keys allow you to hit one key to issue a multicharacter command. This tiny utility allows you to define as many functions as you want using infrequently used control codes and to change them at any time... even from within another program.

RESOURCE. While a debugger will allow you to disassemble small bits of code easily enough, only a true text based disassembler can take a COM file and make source out of it again. This is one of the best ones available.

Order as AFS #3
and specify system

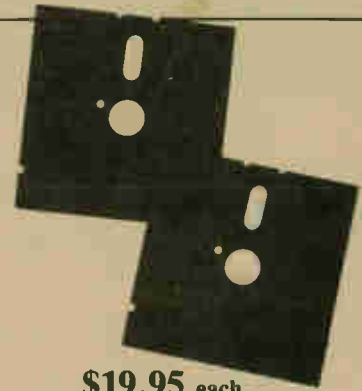

\$19.95 each

Except for 8" disks and those with two disks which are marked with an asterisk (*) above which are:

\$22.95

*single density formats require two disks. The package cost for these formats is \$22.95.

Almost Free Apple DOS Software

Almost Free Apple DOS Software#1

While CP/M is a wonderful thing in its own right, the Apple computer can also, and usually does, operate under DOS. For this reason, there's a multitude of programs available for it. Below, we offer a mini-multitude of our own.

The following programs will operate on any Apple //+, //e, //c, or true compatible operating under DOS 3.3. Apple users operating only under ProDOS may have to make alterations to some programs.

Picture Coder: All Apple HiRes pictures take up 36 sectors in their binary form. This program creates a textfile of a program in memory, squeezing out the zero bytes, that can later be EXECd into memory. The textfile often takes up less room on the disk.

DNA Tutorial: Operating under Integer BASIC, this program might appeal to 'clone' owners. In actuality, though, it's an interactive low-res graphics tutorial of DNA in its inherent forms. And you thought your Apple was only good for games...

Toad: Speaking of games, this program is an Applesoft BASIC implementation of 'Frogger' that can be controlled with either a joystick or the keyboard. The user's high scores are saved to disk.

Function Plotter: A fairly extensive Applesoft BASIC program that takes any inputted function and plots it on the HiRes Screen.

Data Disk Formatter: Apple DOS disks need not be bootable to be useful. This binary program formats a disk without setting DOS on the tracks, conserving useful disk space.

BASIC Trace: A program for the advanced Applesoft programmer, this file, when EXECd, displays the hexadecimal locations of each Applesoft line number of a program in memory.

Gemini Utility: A word processor pre-boot for Gemini printer users, this BASIC program initialises the printer's font or pitch before you boot your word processor.

Payments: This BASIC program allows you to keep track of payments and credits to and from up to 100 accounts on a single disk. A sample account is included.

Databox: A small but useful database program in Applesoft BASIC. Sample files are included to get you started.

Nullspace Invaders: A quick BASIC HiRes game testing coordination and judgement as you manipulate a monolith through mysterious gates.

Fine Print: The majority of this software has been obtained from on-line public access sources, and is therefore believed to be in the public domain. Any remaining programs were written in-house. The prices of the disks defer the cost of collecting the programs, debugging them, reproducing and mailing them, plus the cost of the media they're supplied on. The software itself is offered without charge.

Moorshead Publications warrants that the software is readable, and if there are any defects in the medium, we will replace it free of charge. While considerable efforts has been made to ensure that the programs have been thoroughly debugged, we are unable to assist you in adapting them for your own applications.


Order as AFAD #1
and specify system

Each disk is

\$19.95

or, as an introductory offer you
can order all three for

\$39.95

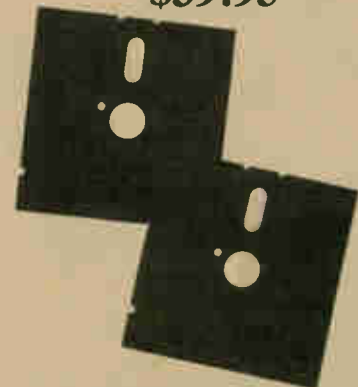

Software Services Moorshead Publications

25 Overlea Boulevard, Suite 601, Toronto, Ontario M4H 1B1
Electronics Today October 1985

Almost Free Apple DOS Software . . . #2

Amort: A monthly amortization program that calculates monthly payments to an inputted figure, calculates principle, interest on every balance, and prints out the resulting chart.

Voiceprint: An unusual program that uses the HiRes screen to sample sounds inputted through the cassette jacks at the back of your Apple. Sampling rate and other variables can be controlled, and two sounds may be compared side-by-side.

Calc NOW! Written in BASIC, this spreadsheet program is somewhat slower than VisiCalc, but still offers the power you expect from a spreadsheet. With sample files.

Cavern Crusader: A mix of BASIC and binary programming, winning this HiRes game is difficult, to say the least. For every wave of aliens shot in the cavern, there's always a meaner bunch in the wings.

Newcout: With source file. This binary program replaces the I/O hooks in the Apple with its own so you can operate your Apple through the HiRes screen. Comes with a character set.

Charset Editor: A utility to help you create your own character sets to use with Newcout.


Calendar: A BASIC utility useful for finding a particular day of any inputted month and year, or for printing out any given year.

LCLODR: With source. This binary utility BLOADs any given file into the 16K language card space at \$D000. The source is useful in showing how to use DOS commands through assembly language.

Cristo Rey: An animated HiRes BASIC program showing Cristo Rey by moonlight. For apartment-bound romantics.

ATOT: That's an acronym for 'Applesoft to Text'. EXEC this textfile to produce a textfile of your program.

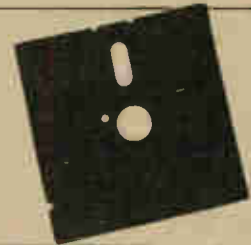Applesoft Deflator: This program takes a textfile made by ATOT and squeezes it, replacing PRINT statements with '?' and removing unnecessary spaces from the listing.



Order as AFAD #2
and specify system

Each disk is
\$19.95

or, as an introductory offer you
can order all three for

\$39.95

Almost Free PC Software

Almost Free PC Software . . . #1

Our Almost Free Software disks, volumes one through three, for systems running CP/M have been so thunderingly popular that we have assembled a volume for IBM PC users. The considerably greater power of a sixteen bit system, coupled with its larger capacity disk drives, have enabled us to offer a collection of programs that will knock the socks off virtually any sentient life form booting the disk. Be warned... wear sandals when you unwrap this thing.

This software will run superbly on genuine IBM PC's and compatible systems.

PC-WRITE While not quite Wordstar for nothing, this package comes extremely close to equalling the power of commercial word processors costing five or six bills. It has full screen editing, cursor movement with the cursor mover keypad, help screens and all the features of the expensive trolls.

SOLFE This is a small BASIC program that plays baroque music. While it has little practical use, it's just a kick to tootle with. It's also a fabulous tutorial on how to use BASICA's sound statements.

PC-TALK Telecommunications packages for the IBM PC are typically intricate, powerful and huge. This one is no exception. It has menus for everything and allows full control of all its parameters, even the really silly ones. It does file transfers in both ASCII dump and MODEM7/XMODEM protocols and comes with... get this... 119424 bytes of documentation.

SD This sorted directory program produces displays which are a lot more readable than those spewed out by typing DIR. It's essential to the continued maintenance of civilization as we know it.

FORTH This is a small FORTH in Microsoft BASIC. It's good if you want to get used to the ideas and concepts of FORTH... you can build on the primitives integral with the language.

LIFE This is an implementation of the classic ecology game written in 8088 assembler. While you may grow tired of watching the cells chewing on each other, in time the source will provide you with a powerful example of how to write code.

MAGDALEN This is another BASIC music program. We couldn't decide which of the two we've included here was the best trip, so we wound up putting them both on the disk. Ah... the joys of double sided drives.

CASHACC This is a fairly sophisticated cash acquisition and limited accounting package written in BASIC. It isn't exactly BPI, but it's a lot less expensive and suitable for use in most small business applications.

DATAFILE This is a simple data base manager written in... yes, trusty Microsoft BASIC.

UNWS Wordstar has this unusual propensity for setting the high order bits on some of the characters in the files it creates. Looks pretty weird when you try to do something other than Wordstar the file, doesn't it... Here's a utility to strip the bits and "unWordstar" the text. The assembler source for this one is provided.

HOST2 This is a package including the BASIC source and a DOC file to allow users with SmartModems to access their PC's remotely. It's a hacker's delight.

The disk also includes various support and documentation files needed to run the software.

We can provide the Almost Free PC Software Disk volume one on either one standard double sided disk or on two single sided ones.

Order as AFPC #1
and specify system.

Only
\$19.95
or **\$22.95**
for two single sided disks.




Moorshead Publications warrants that the software will be readable. If defects in the medium prevent this, we will replace your disk at no cost. While we have made every effort to assure that these programs are completely debugged, we are unable to assist you in adapting them for your application.

Natural Crystal Radio

A crystal radio is the simplest form of radio, and an interesting experiment for both beginners and experts.

By R.A. Penfold

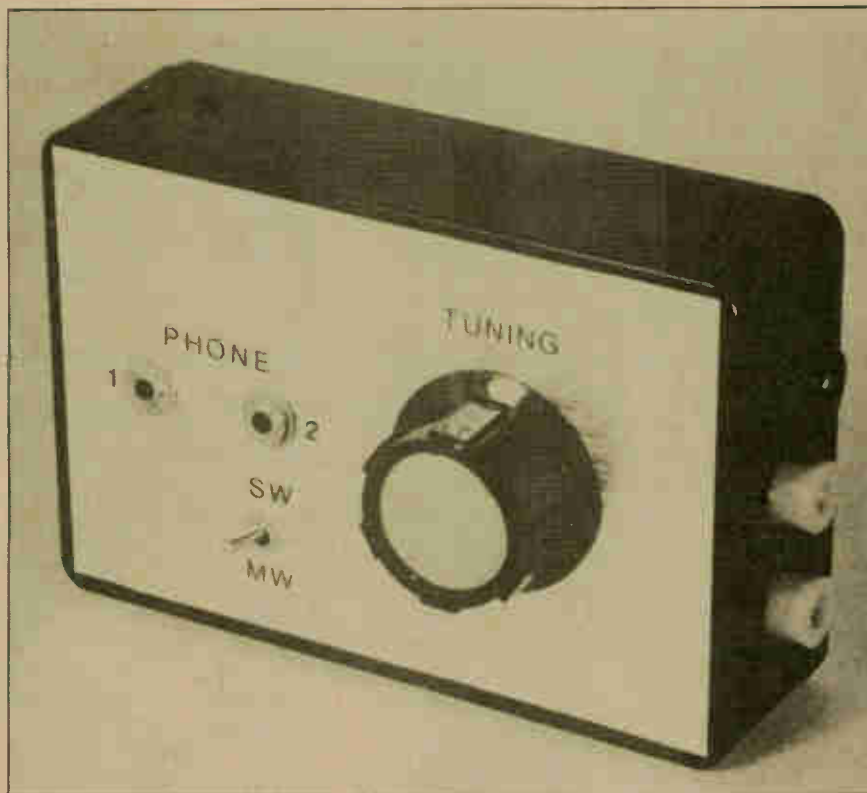

WHEN WRITING an article about a radio receiver it is normal to start by extolling the virtues of the new miracle design, but such an approach is really not appropriate for a crystal set. By any standards the level of performance provided by a crystal set is pretty mediocre, and one could reasonably ask why bother to build one? Even in these days of high technology, crystal receivers remain quite popular among electronics enthusiasts and there are a number of reasons for this:

- 1) Very inexpensive to build.
- 2) The most simple type of radio that will work.
- 3) Zero running costs as no power is required.

4) No setting up or any form of adjustment required once completed.

5) Easy enough for even a complete beginner to construct.

There are a couple of disadvantages apart from the general lack of performance. One is merely that there is only sufficient output to drive a sensitive earphone or headphones, and loudspeaker operation is out of the question. The second is that ordinary ferrite or telescopic aerials provide an inadequate signal level, and a so called *longwire* aerial is needed. This is not such a major drawback as one might think, since the aerial can just be a few meters of ordinary hook-up wire strung between two supports outdoors. A sophisticated installation with insulators and masts is not required.

This crystal set is a fairly conventional design which covers two wavebands. These are the normal medium wave broadcast band, and short wave bands from about 4.5 to 12MHz.

Circuit Operation

The simplicity of a crystal set is readily apparent from the circuit diagram of Fig. 1. There are only seven components plus the input and output sockets. SK2 is the normal aerial socket, and a reasonably efficient aerial wire will give output levels of a few hundred millivolts peak to peak or more on strong signals. Although the signal levels are quite respectable, the output impedance is quite high and the available current is therefore quite low. It is for this reason that a low impedance load such as a loudspeaker can't be driven from a crystal set, and it is not even possi-

ble to use low impedance headphones successfully.

The signals provided by the aerial are at high frequencies, and the audio signal is amplitude modulated on to each signal. Fig. 2 helps to explain the amplitude modulation and demodulation process. The waveform of Fig. 2a represents an unmodulated carrier wave, and here there is no variation in the strength of the signal with each half cycle having the same peak voltage. In Fig. 2b the carrier wave has been modulated by a lower frequency squarewave, and the signal switches between two levels in sympathy with the modulation signal. In practice the modulation signal is the audio signal that is to be transmitted, and it would normally be a complex speech or music waveform. However, whatever the waveform the system works precisely the same way, with the amplitude of the carrier wave being varied in sympathy with that of the audio modulation signal.

A crystal set has to perform two basic functions in order to recover the audio signal modulated onto the required transmission. First it must select the required signal from the multitude of signals provided by the aerial, which picks up transmissions on all bands from long waves through to VHF bands. Then it must demodulate that signal to recover the audio signal it contains.

The filtering is provided by C1 and L2 which form a parallel tuned circuit. This type of circuit has an infinite impedance at its resonant frequency, with the impedance falling as the signal frequency is varied either side of resonance. In practice the impedance does not reach infinity at resonance due to imperfections in the components (leakage in C1 and resistance through L2), but a very high impedance is still achieved. The impedance falls rapidly on either side of resonance. This gives the desired band-pass filtering with transmissions at the resonant frequency being unaffected by the tuned circuits while transmissions at other frequencies are virtually short circuited to ground.

The value of L2 and C1 enable the tuned circuit to be tuned over the medium waveband by varying the value of C1. For short wave reception L1 is switched into circuit by closing S1, and the inductance in the circuit is then the parallel inductance of L1 and L2 (approx. 4.6uH). This boosts the resonant frequency so that it covers the desired short wave broadcast bands.

Demodulation

Having selected the signal we want, the next step is to demodulate it. If you look at Fig. 2b you will see that the average signal level does not vary in sympathy with the strength of the audio signal, but

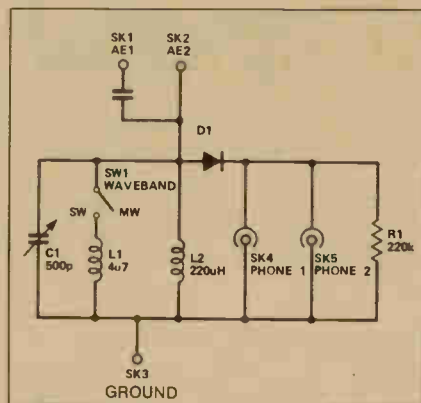


Fig. 1 The circuit: only seven components.

is always zero as the negative half cycles cancel out the positive ones. If one set of half cycles is removed as in Fig. 2c, the situation is then different, and the average signal level is proportional to the modulating signal. All that is required to recover the original signal is a simple lowpass filter to remove the radio frequency signal and leave a DC output voltage equal to the average input potential. This gives the waveform in Fig. 2d. Although the demodulated signal is a varying DC type rather than a true AC signal, this is of no real consequence, and the sound from the earphone is the same either way. A capacitor could be placed in series with output to convert the signal to an AC type, but this would not give any practical advantage and is not done here.

The filter is a C-R smoothing circuit. Although the capacitor may seem to be absent, the unit is designed to feed into a crystal earphone, and this provides a capacitance of a few nF which gives the smoothing. R1 prevents the charge on the

smoothing capacitance from simply charging to the peak input voltage and remaining there, by providing a discharge path. Two output sockets are provided, and the unit can drive two earphones if required. The unit will also operate with high impedance (about 4000 ohms) headphones. However, with these R1 should be replaced with a capacitor of about 4n7 in value as magnetic headphones provide a DC path but no significant capacitance.

Removing one set of half cycles is easy enough, and can be achieved by processing the signal with a diode (D1 in this circuit). A diode passes current in one direction, but blocks any significant current flow in the opposite direction, and gives exactly the action we need here. Unfortunately, practical diodes are less than perfect, and silicon types do not conduct in the forward direction unless a voltage of about 0V5 or more is applied to them. This level would not be achieved on many stations, resulting in many signals giving no output at all, and severe distortion plus loss of volume on the strongest signals. This is overcome by using the older type of germanium diode. These are inferior to silicon types in most respects, but have a much better forward conduction characteristic which makes them vastly superior for this application.

Selectivity

An obvious problem with a crystal set is that of obtaining a strong enough signal to give good volume. A less obvious one is that of sorting out one transmission from the rest once an adequate aerial signal has been obtained. The problem is partly due to the broad response of the filtering provided by the tuned circuit. In fact, in isolation the tuned circuit would give adequate selectivity for a simple receiver in most cases. The tuned circuit is not in isolation though, and it is damped by the signal extracted to drive the demodulator and earphone. The output impedance of the aerial often has an even greater damping effect, and making the aerial longer tends to reduce its output impedance and give reduced selectivity from the receiver. This is unfortunate as it means that using a good aerial to obtain decent volume can result in poor selectivity with two or more stations being received simultaneously.

Where possible it is best to connect the aerial to SK2 and obtain maximum volume, but if lack of selectivity is a problem it is better to use SK1 instead. C2 then gives a loose coupling into the tuned circuit which gives improved selectivity at the expense of slightly reduced volume. A ground can be connected to SK3 and this will give improved signal strengths.

Construction

With so few components there is no need for a printed circuit board and the com-

PARTS LIST

Resistors	
R1	220k 0.25W 5%
Capacitors	
C1	500pF Variable
C2	27pF ceramic plate
L1	4.7uH RF choke
L2	220uH RF choke
Semiconductors	
D1	1N34 or 1N60 germanium diode
Miscellaneous	
SK1,2,3	4mm sockets
SK4,5	3.5mm jack sockets
SW1	SPST sub-miniature toggle switch
Case about 120 x 80 x 35mm; control knob; crystal earphone with 3.5mm plug; connecting wire, solder, aerial wire, etc.	

ponents can be connected directly to the sockets and controls. Try to stick as close as possible to the layout shown in Fig. 3 and the photograph.

The major concern during soldering of the components is making sure not to damage D1, the germanium diode. Use heat shunts on each of the leadout wires when completing this step and be quick with the iron.

Aerial and Ground

Without a reasonable aerial the unit will not function at all. The minimum requirement for good results is about 10 meters of wire strung indoors, around a picture or window frame. If possible, 20 or 30 meters of wire strung up outdoors should be used. In any case the wire should be high enough from the ground so as not to interfere with anyone's neck! Proper aerial wire can be obtained but ordinary PVC covered multistrand connecting wire will work just fine.

A ground connection is not essential, but can give a substantial improvement in results. All that is needed is a rod or pipe about one half to one meter in length pushed into the ground, and connected to SK3 via a lead which should be no longer than is absolutely necessary. It would not be a good idea to make a connection to the AC ground as this could be dangerous.

In Use

It is probably best to try the medium waveband first (SW1 open) as in most areas there is normally a good selection of strong medium wave stations. With even a modest aerial and no ground connection there should be several stations received at good volume, and using a good aerial plus a ground there should be a dozen or so receivable after dark. When using either tuning range, if a lack of selectivity proves to be a problem, try connecting the aerial to SK1 instead of SK2.

Results on the short wave bands are less predictable, and stations can come through loud and clear one minute, only to disappear the next. A lot of patience is required when listening on these bands, but some interesting stations can be picked up. ■

Fig. 3 No PCB! All the components are soldered to each other. Tin the joints to ensure good connections, but beware of damaging the heat-sensitive germanium diode.


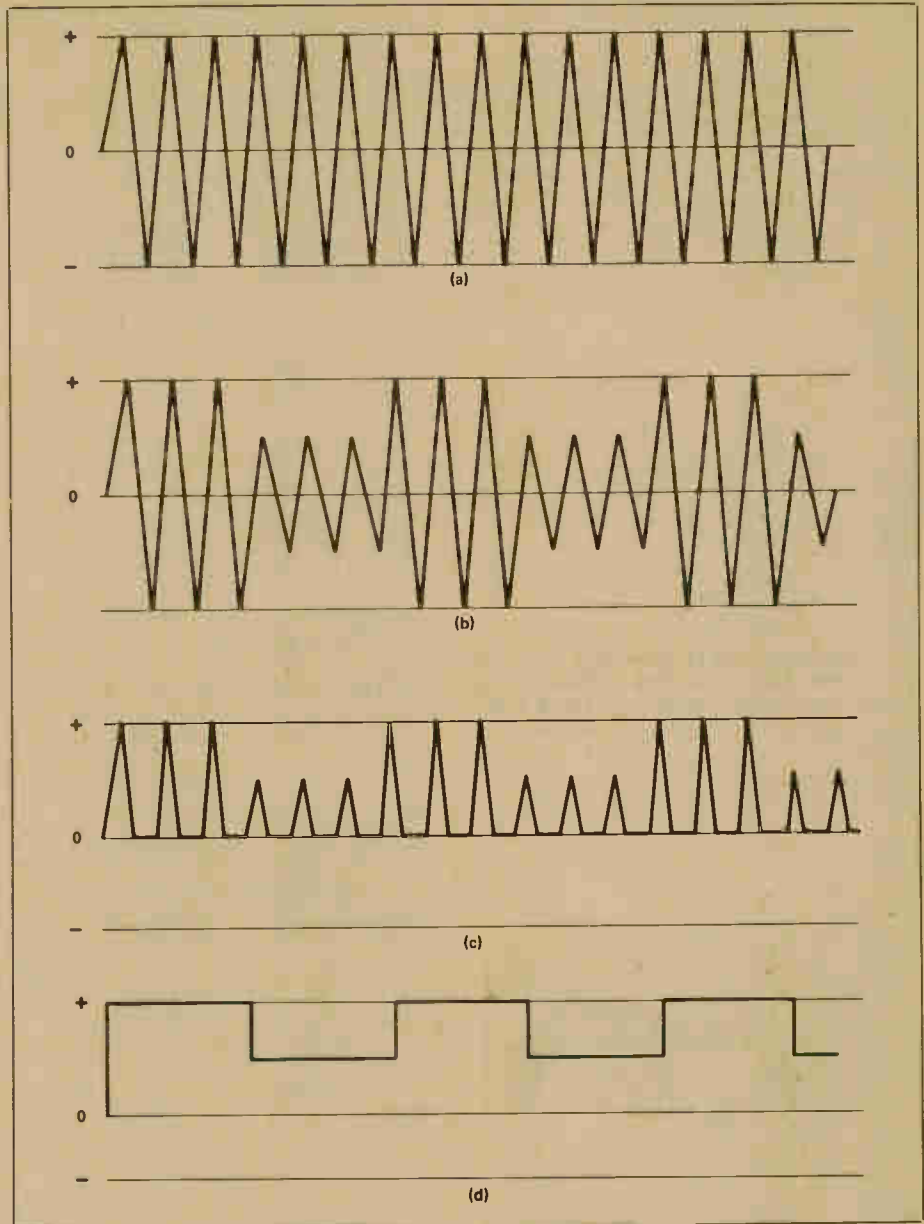


Fig. 2 A series of waveforms illustrating the processes through which the aerial signals go through: a) an unmodulated carrier b) a carrier modulated by a square wave c) the negative set of half cycles removed d) a low pass filter removes the carrier wave and leaves the square wave.

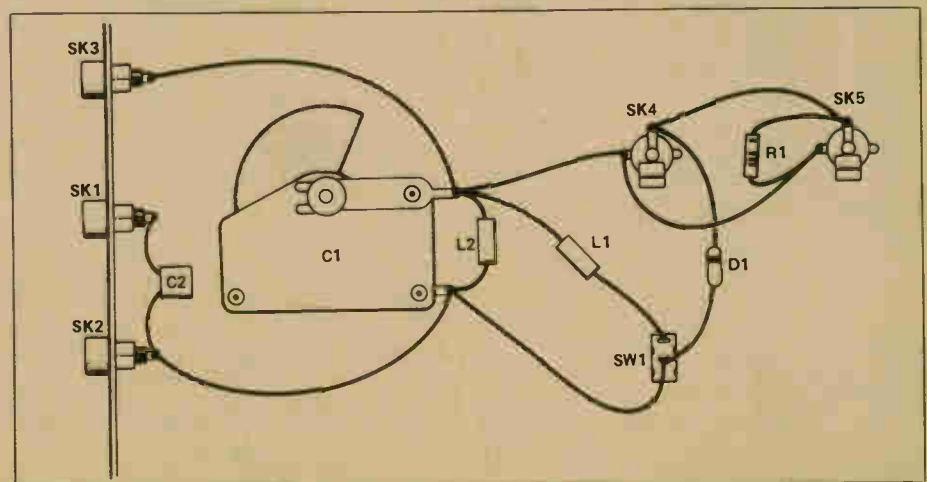

Product Mart *Where Buyers Find Sellers*

25 TESTED low cost plans regulated power supplies, electronic locks, alarms, lie detectors, testers, electronic jewelry, etc., \$6.50. Kits & parts available also. TRS-80 I/O interface plans \$15.00. Send to **J.B. ELECTRONICS**, Box 122, Delson, P.Q. J0L 1G0.

TECHNICAL BOOKS. Metalworking, woodworking, electronics, plans, science. Large catalogue \$1.00. **ERIC KEATS & COMPANY**, P.O. Box 796, Station A, Scarborough, Ontario, M1K 5C8.


HOBBIT ELECTRONIQUE

**WE DON'T SELL COMPUTERS.
WE JUST SELL THE PARTS!**

Send your name and address along with \$1.00 to: 7454 Langelier, St. Leonard Montreal, Que. H1S 3A7.
Tel: (514) 259-5581.

Projects Book No. 2
100 pages

\$3.95

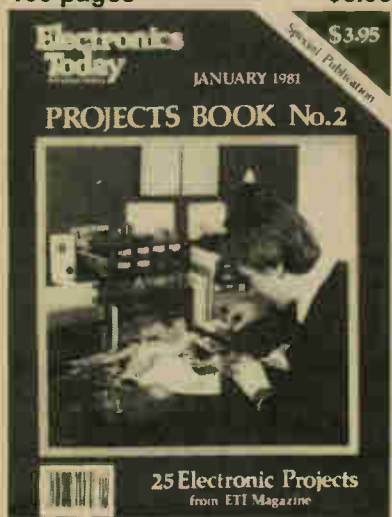

Twenty-five of the best projects from recent issues including the High Performance Series 4000 Amplifier (including Preamp and Power Supply), Rumble Filter, Dynamic Noise Filter, Logic Probe, Cable Tester, Function Generator, Rain Alarm, Digital Tacho, Two Octave Organ, Light Chaser, Shutter Speed Timer, Ni-Cad Charger and more. First published January 1981.

ORDER TODAY FROM

Moorthead Publications, 25 Overlea Boulevard
Toronto, Ont. M4H 1B1 (416) 423-3262
Postage and Handling Included.
Credit Card payment accepted

MPF III Apple IIe Compatible \$1395.00 64K Slim Drive, Z80 Printer Card, 80 Columns Amber or Green Monitor, Shipping \$10.00. Send SASS for catalog. **RAITRONIC'S**, 6650 Ross St., Vancouver, B.C. V5X 4B2.

ULTRASONIC transducers. 40KHz piezoelectric transducers as used in the PIP10 module. \$9.95 (+7% Ontario residents) for a transmit and receive pair. Add \$2.00 for Instructions and postage: **EYE ELECTRONICS CORP.**, Box 13100, Kanata, Ontario. K2K 1X3.

FAST CLEARANCE: Your price is mine!!! Complete S-100 computer: 21 slots Z80 2 serials 2 parallels; IQ-120 terminal; IDS-440 printer; Lobo-Shugart SS-8" drives. Many programs and CP/M. More details: (418) 688-8387, 2260 Masson, Sillery, Quebec, G1T 1M8.

EXCITING scientific and electronic devices you can build. Many fascinating plans and kits available. Catalogue \$2.00. Mail order only. **DUKER ENTERPRISES** 8307-160 Street, Edmonton, Alberta T5R 2H2.

LINE negatives/positives for all your projects. Write today for prices and discount rates. Also drafting aids. **ADB Graphics**, P.O. Box 203, Delta, B.C. V4K 3N6.

HARDWARE/software product design and prototyping. Mainframe communication interfacing and protocol conversion. **THE LISMA COMPUTER CORPORATION**, 4865 Sheppard Ave., East, Scarborough, Ontario M1S 3V8 (416) 297-0297.

TS2068 or Spectrum compatible disk drive controller card. Uses Shugart SA455 or compatible drive. 160 KB per disk, 2K DOS on EPROM \$119.95 **LARKEN ELECTRONICS**, R.R. #2, Navan, Ontario K4B 1H9.

ACTIVE Crossoner Modules (Stereo). Frequencies to your specs. PCB All Parts and Plans Included. Requires 20-35v supply three way \$129.95. Two way \$99.95. Subwoofer \$99.95. Residents add 5% PST. Send stamp for information or money order/certified cheque to: **SOUND REINFORCEMENT**, Box 7604, Saskatoon, Sask, S7K 4R4.

FOR \$10 per kit \$2 handling, receive free flyer and any of the following. #1: 1000 asst'd pcs choke — capacitor — resistor — transistor — hardware — etc. #2: 200 asst'd ceramic — #3: 100 asst'd silver mica — #4: 100 asst'd mylar — #5: 50 asst'd tantalum — #6: 50 asst'd electrolytic — #7: 50 asst'd feed-through — #8: 50 asst'd metallic silver mica (Elmenco) #9: 25 asst'd variable — #10: 100 asst'd 5MM L.E.D. — #11: 100 asst'd I/c sockets — #12: 6 AA nicad batteries — #13: 15 PL-259 connectors — #14: 10 UG88 connectors — #15: 10 asst'd Lorlin switch. All new material. Unconditional guarantee. **SURPLUS ELECTRO QUEBEC**, 2264 Montee Gagnon, Blainville, Quebec J7E 4H5.

**DO SMALL
ADVERTISEMENTS
ATTRACT ATTENTION?
WELL, THIS ONE DID!**

WHERE BUYERS FIND SELLERS

For more information Call:
(416) 423-3262

**Now - Motion Detection
With Your Computer**

ULTRASONIC module PIP10 connects to your computer to detect motion. Up to 7 Metre range, 12V, 10MA, LED motion indicator. Module size 6.5/4.5/2cms contains transmitter, receiver and doppler shift detector. Booklet tells how to connect module to computer, how to construct a full alarm system etc. Assembled and tested module \$29.50. Ontario residents add 7% **EYE ELECTRONICS CORP.**, Box 13100, Kanata, Ontario K2K 1X3.

J&J ELECTRONICS LTD., Box 1437E, Winnipeg Manitoba R3C 2Z4. Surplus and Semiconductor Specialists. Do you get our bargain flyer? Send \$1.00 to receive the current literature and specials and to be placed on the mailing list for future publications.

Low Cost Audio Mixer

This modular mixer is not super-fi, but it is inexpensive, portable, and so versatile you can use any source.

By John Linsley Hood

THE UNIT described here was designed and built as a control console containing the necessary electronics, and fader pots, so that an operator could mix in various voices with programme material from other sources such as: disc, radio, or tape, to produce a final stereo cassette tape.

The general layout is versatile enough for the actual inputs to be modified for other types. I will show some of the other input circuits which may be slotted in, in place of, or in addition to, the existing layouts.

One general requirement for mixer consoles such as these is the provision of a reasonable quality stereo headphone monitor facility, allowing the control engineer to hear just what is being put on to tape. The unit has been designed to be operable from a battery DC supply. It could be used as a fully portable 'studio'

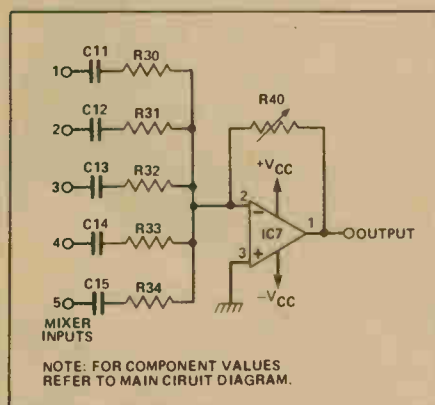


Fig. 1 The central circuit of a virtual ground mixer.

in conjunction with a suitable battery operated cassette recorder.

No VU metering system has been provided since it is assumed that the recorder used will have this facility.

Basic Layout

The circuitry is organized around the virtual ground mixer layout shown in Fig. 1, which can be hooked up easily around an IC op-amp and allows as many inputs as one wishes to be combined together into a common signal (only five are shown).

This is a very powerful technique for mixing inputs, and has the great benefit that there is no leakage back from one input into another, since the inverting input of IC1 in this layout really does look like a ground point to the incoming signals. This also implies that the input impedance of the circuit is determined by the values chosen for each input resistor, R30, R31, etc.

The overall gain of the stage is determined, for any one input channel, by the ratio of R40:Rin (Rin = input resistor). If R40 is variable (As in Fig. 1, but not in the main circuit diagram), the gain of all the input channels may be reduced or increased simultaneously.

The various inputs to this mixer stage are obtained from input stages of the types described below.

Line Input Stage

In the simplest case, where a signal is obtained from a radio or tape recorder having a line output socket (300-700mV @ low impedance), all that is required is a simple slider pot connected as shown in Fig. 2. On the other hand, if it is known that the unit may be used with signal sources having outputs conforming to the DIN standard, in which the output is arranged to provide 1mV for each 1K of load impedance, the alternative arrangement of Fig. 3 is possible.

This is quite a versatile system, and can be used with any input source where a flat frequency response is all that is needed, and where the input signal level will not exceed more than about 0.5V RMS.

Microphone Input Stage

This uses an identical circuit layout to that of Fig. 3, but with the values of R55 and

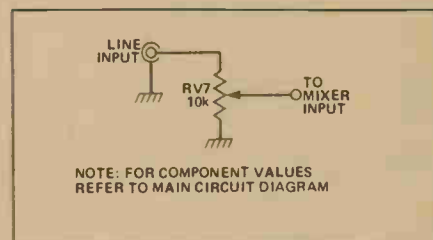


Fig. 2 A mono line input arrangement.

R56 changed to R11 and R16 in Fig. 4 to give a higher gain. The reason for this being that the expected output signal level from the mic may be only 2-3mV. The input impedance is also made switchable between 100k and 4k7 (R1 and SW1 in Fig. 4) to suit either crystal or dynamic (moving coil) microphones. Electret mics with a built-in FET buffer output could be used equally well with either.

Turntable PU Inputs

This facility was not required on the prototype, but there is no difficulty in modifying the op-amp input stage to provide the required gain and frequency response characteristics. The circuit for this is shown in Fig. 5. Since we're not aiming at the 'ultimate-fi' in this unit, a conventional series feedback layout, as used in 99.9% of domestic hi-fi amplifiers, will be adequate.

The op-amp output resistors in the DIN, mic, and RIAA stages (R57, R21, and R62 respectively), are included to prevent changes in the loading of the op-amp, due to the setting of the output gain controls which would alter the frequency response characteristically of the gain stage.

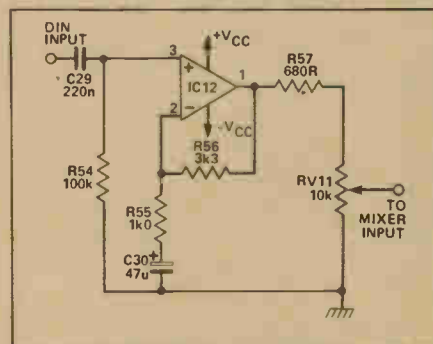


Fig. 3 A DIN input stage.

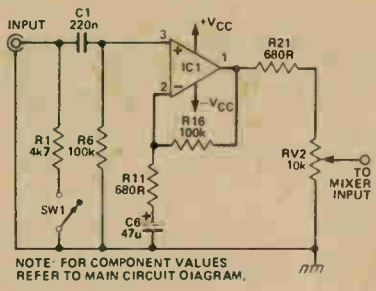


Fig. 4 Mic input stage.

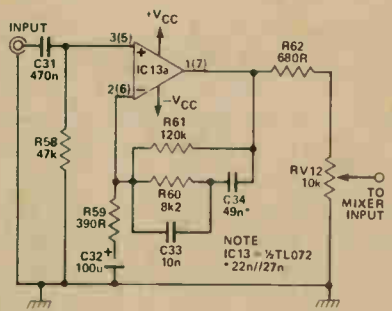


Fig. 5 Optional RIAA input stage.

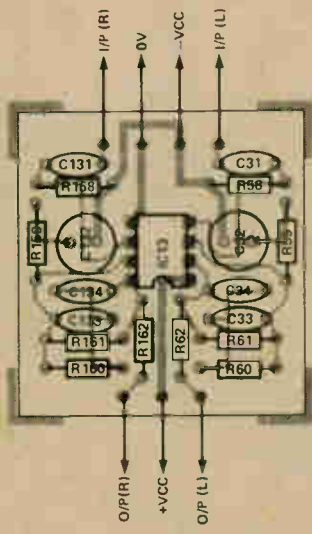


Fig. 6 PCB overlay for the RIAA stage.

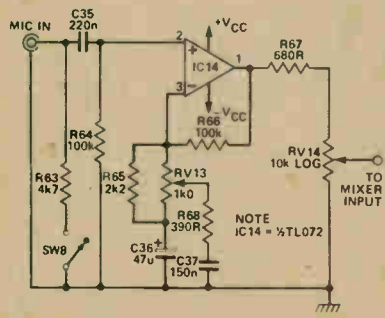


Fig. 7 Optional treble-lift mic input.

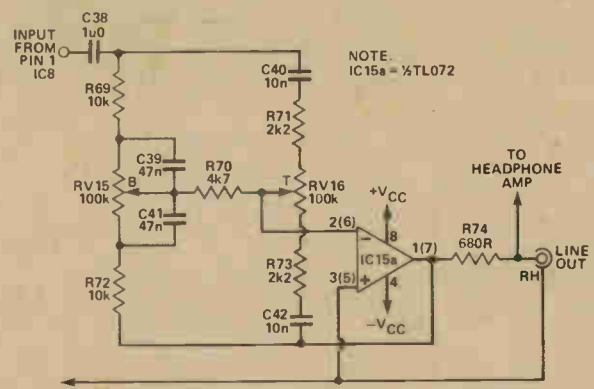


Fig. 8 Optional bass and treble lift/cut tone control stage.


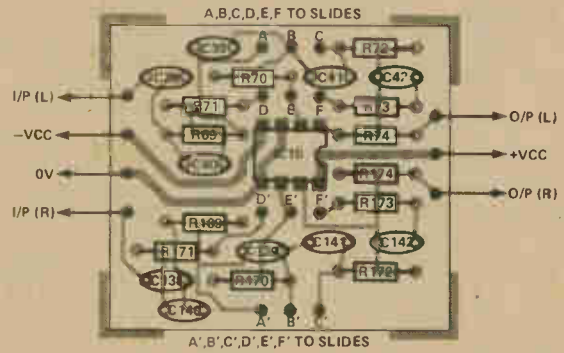


Fig. 9 PCB overlay for optional tone control stage (stereo).

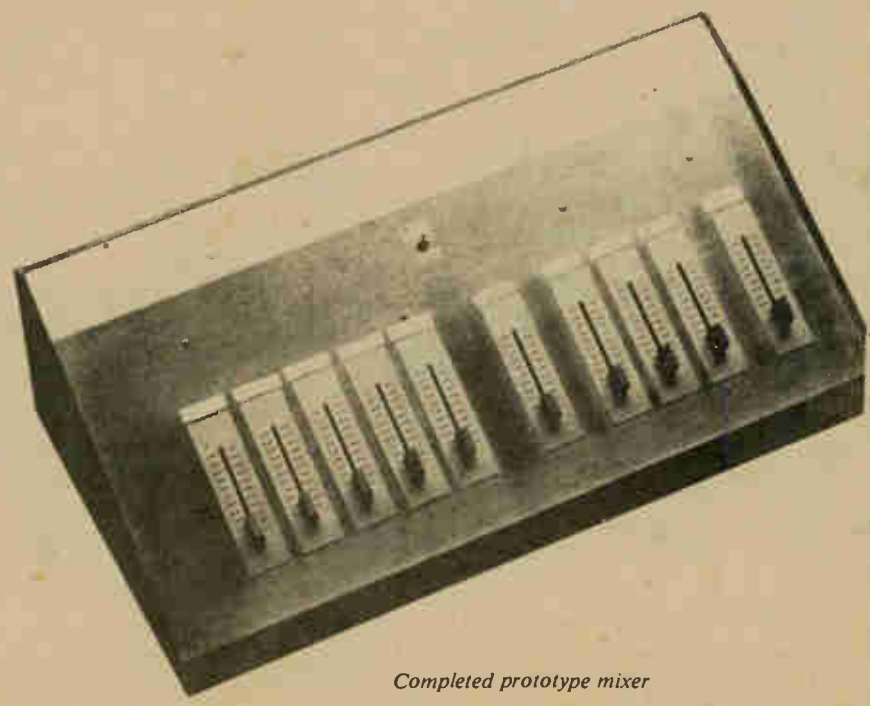

Completed prototype mixer

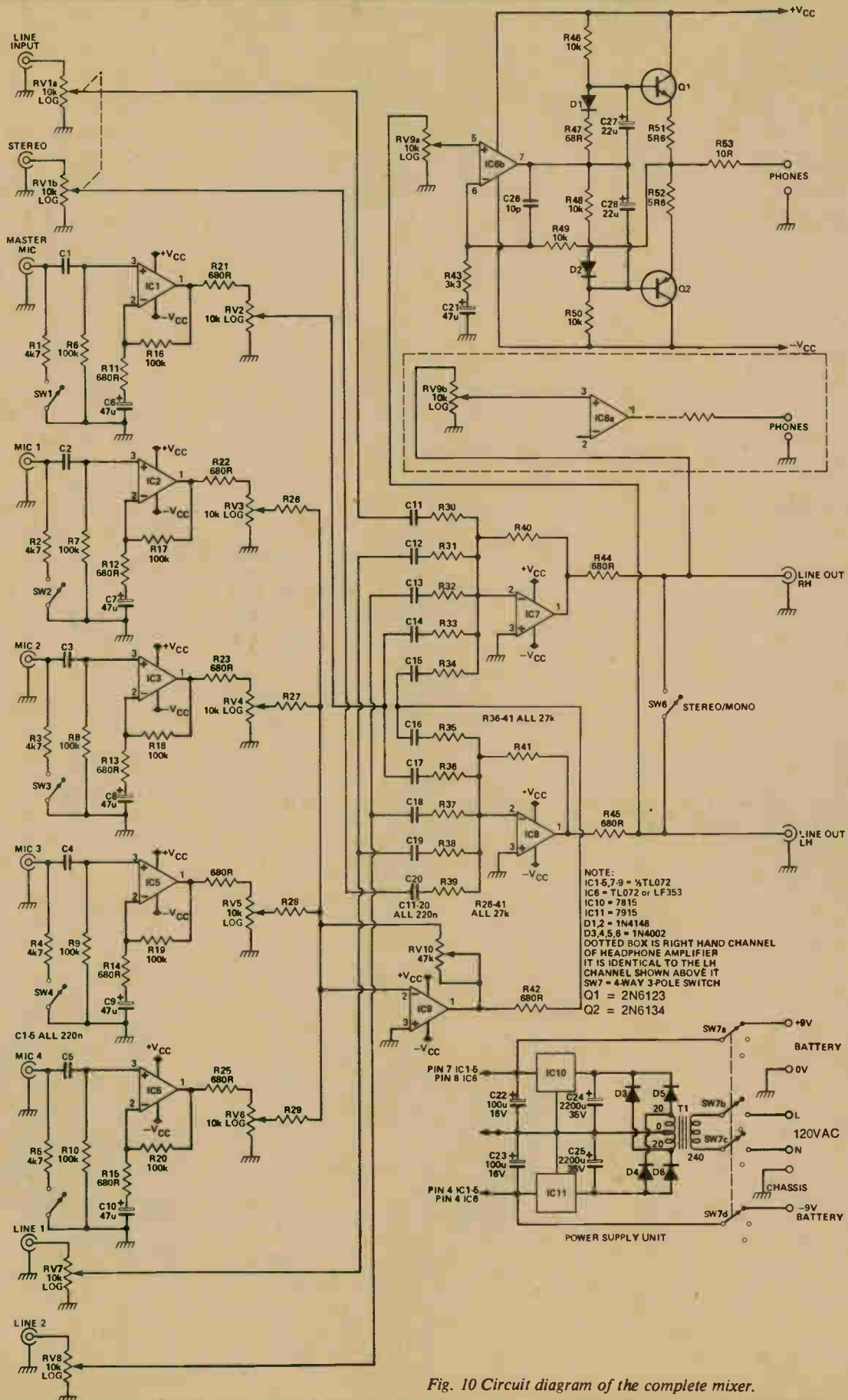


Fig. 10 Circuit diagram of the complete mixer.

Headphone Output Stage

This is fairly conventional, and again uses an op-amp as the gain block, to which some muscle power is added by the transistors Q1 and Q2. These are biased into class A by the diode/resistor network R46-R50, D1 and D2. A small capacitor, C26, is connected across the op-amp to ensure HF stability. Several pairs of headphones can be connected in parallel across the output, provided that the isolating resistors (R53) are taken separately to each output jack. This will ensure that there are no problems if phones of dissimilar type of impedance are used. (Fig. 10)

AC Power Supply

Although the mixer unit can be used quite satisfactorily on a pair of 9V batteries, batteries are expensive and it is probable that it will be powered from 120V on most occasions. A very simple dual power supply, with a couple of voltage regulator ICs, was used on the prototype, as shown in Fig. 10.

Complete System

The circuit for the whole unit is shown in Fig 10 and fitted into a shallow sloping fronted box, approximately 19 inches long, as shown in the photograph.


Since the specification to which this unit was built called for a stereo line input, as well as a pair of mono line inputs, a ganged 10k slider pot was used for RV1, while single slider units were employed for RV7 and RV8. The four main mic inputs are controlled individually by slider pots RV3 to RV6, with a master fader, RV10, controlling their overall level so that it can faded down if, for example, a voice-over commentary is to be superimposed from the master mic.

A dual-gang slider pot, RV9, is used to control the volume level of the headphone outputs. Finally, an overriding stereo/mono control is provided by SW6, which simply parallels the two L and R outputs. In general, however, the unit is used in the stereo mode, with a stereo signal from the line input, over which the (mono) mic input voices appear on 'centre stage'.

No tone control facilities were required for the unit as it appears here, but subsequently a microphone input treble lift facility was added, to give greater clarity to voices. This was done as shown in Fig. 7. The unit can completely replace the mic input shown in Fig. 4.

A more formal bass/treble-lift/cut tone control stage could be added, at pin 1 of ICs 7 and 8 in Fig. 10. The tone control circuit is shown in Fig. 8.

Fig. 11 Overlays for the mixer and PSU boards.

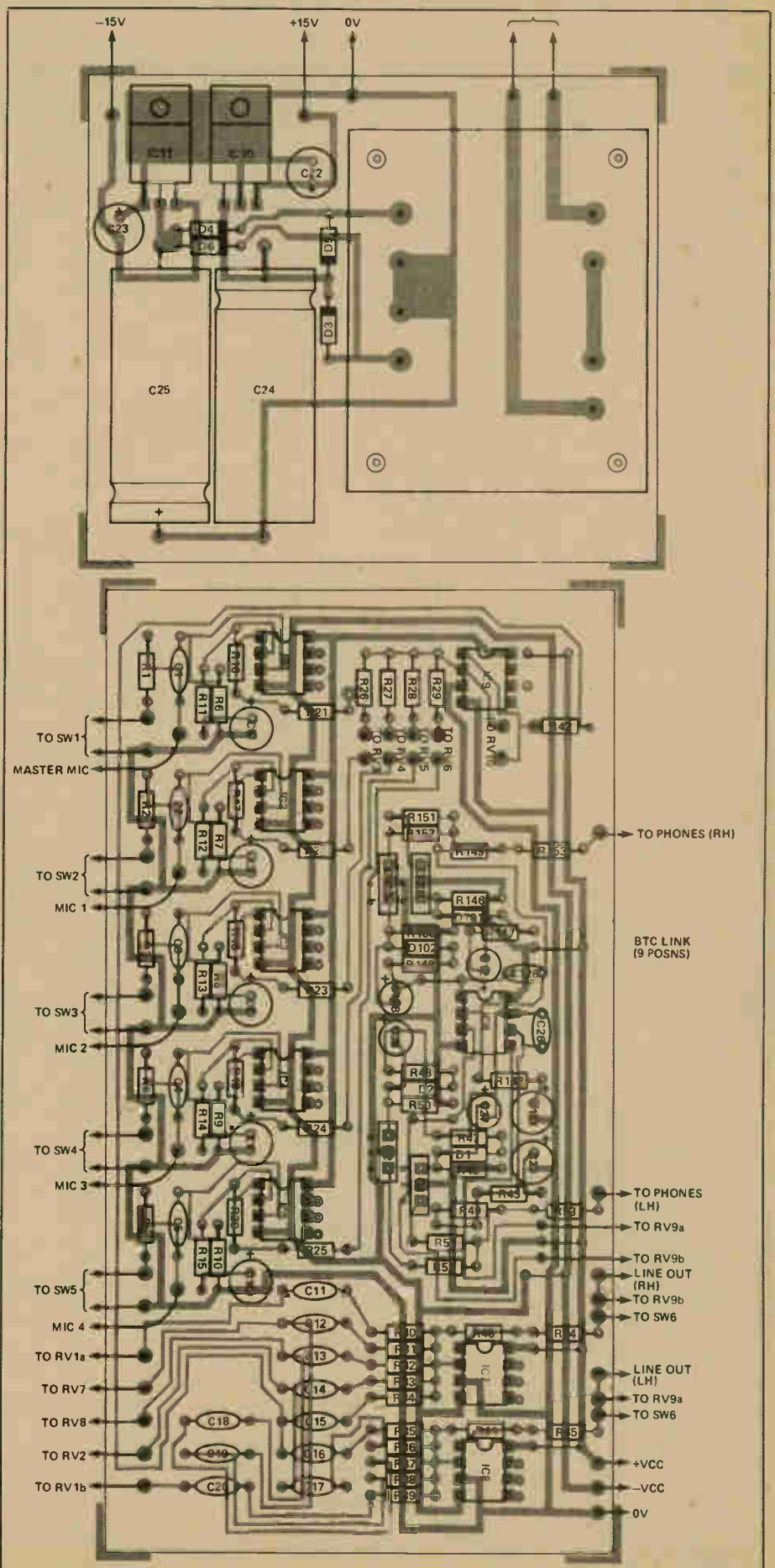

PARTS LIST

MAIN BOARD

Resistors

(all 1/2 watt unless stated)

R1,2,3,4	4k7
R6,7,8,9,10,16,17	100k
18,29,20	
R11,12,13,14,15	680R
21,22,23,24,25,42,44,45	
R26,27,28,29,30	27k
31,32,33,34,35,36	
37,38,39,40,41	
R43	3k3
R46,49,50	10k
R47,28	68R
R51,52	5R6 W/W
R53	10R/W/W
RV1,9	10k log ganged sliders
RV2,3,4,5,6,7,8	10k log single sliders
RV10	47k single slider

Capacitors

C1,2,3,4,5,11,12,13,14	47u 16V
15,16,17,18,19,20	electrolytic
C6,7,8,9,10,21	100u 16V
C22,23	electrolytic
C24,25	2200u 40V electrolytic
C26	10p
C27,28	22u 16V electrolytic

Semiconductors

IC1-6,8,9	TL072/LF353
IC10	7815
IC11	7915
Q1	2N6123/2N5296
Q2	2N6134/2N6109
D1,2	1N4148
D3,4,5,6	1N4002

Miscellaneous

SW1,2,3,4,5,6	SPST switches
SW7	3 pole, 4 way switch
Standard jack sockets (13 for main board configuration); 9V battery clips (x2); 20-0-20 20VA transformer, TR1; 19" shielded cabinet.	

(Note: R43-53, C21, 26-28, Q1-2, D1-2 have corresponding components for the right-hand headphone amplifier. They are marked R143-153, C121, 126-128, Q101-102, D101-102 on the overlay diagram).

OPTIONAL BOARD

Resistors

(all 1/2 watt)	
R54,64,66	100k
R55	1k0
R56	3k3
R57,62,67,74,75	680R
76,79,80	
R58	47k
R59,68	390R
R61	120k

R63,70	4k7
R65,71,73	2k2
R69,72	10k
R77,78,81,82	27k
RV11,12,13	10k log sliders
RV13	1k0 slider
RV15,16	100k sliders
RV18	47k ganged slider

Capacitors

C29,35,45,46	220n
C30,36	47u 16V
C31,43,44	electrolytic
	470n
C32	100u 16V
C33,40,42	electrolytic
	10n
C34	49n (22/27n)
C37	150n
C38	1u0 ceramic
C39,41	47n

Semiconductors

IC12-16	TL072/LF353
---------	-------------

Miscellaneous

Standard jack sockets are required.

(Note: R58-62, RV12 and C31-34 have corresponding components on the second channel of the RIAA equaliser board. They are numbered R158-162. RV112 and C131-134 on the component overlay. Likewise for components R69-74, RV15-16 and C38-42 whose second channel equivalents on the tone control board are marked R169-174, RV115-116 and C138-142).

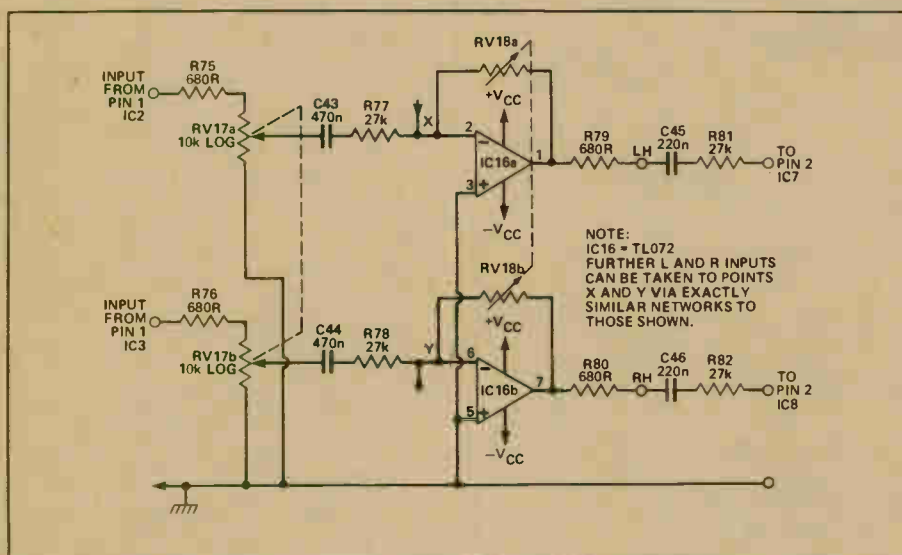


Fig. 12 Single stereo mic input arrangement using two mono input stages.

Full Stereo System


It is very easy to organize this layout to provide more stereo input channels than the one stereo line input on the prototype.

This is done by taking each pair of inputs, say those from IC2 and IC3 (Fig. 10) and routing them to a pair of master fader stages, IC16a and IC16b, as shown in Fig. 12, and from there to ICs 7 and 8, as before.


The prototype unit was designed around TL071s or their higher specification equivalents, LF351. To enable the addition of extra facilities with relative ease, we have designed the board using TL072s (LF353s) exclusively. Pads for the unused halves of the op-amps can be found on the main PCB.

And As We Go To Press...

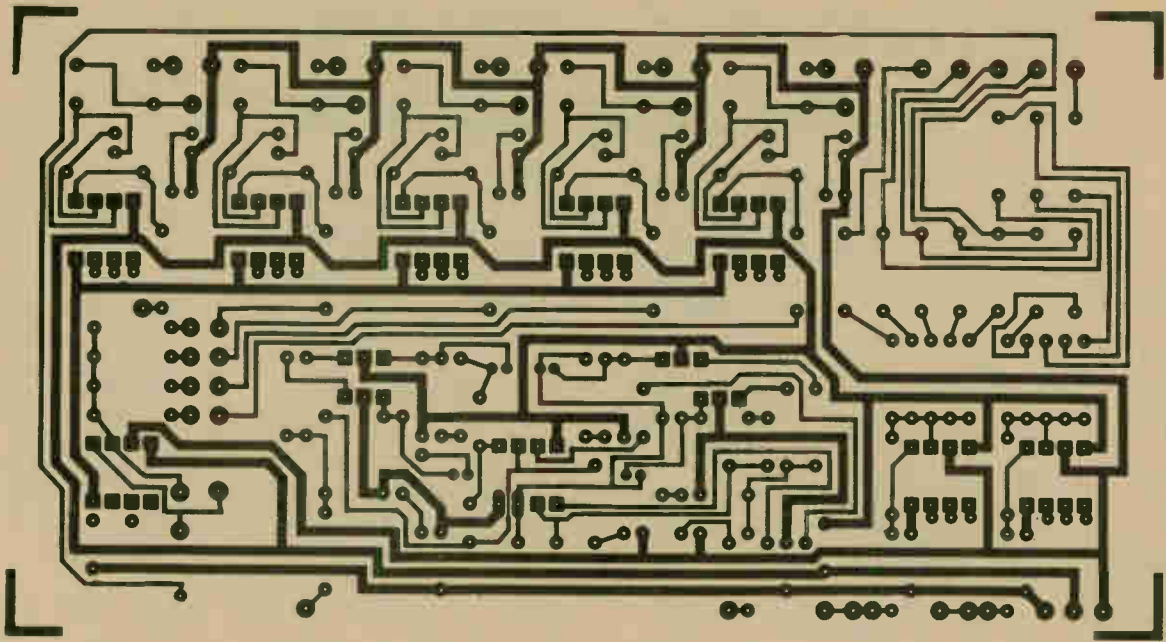
In Fig. 6, overlay for the RIAA stage, the board is incorrectly shown from the foil side. The PCB artwork itself is shown correctly.



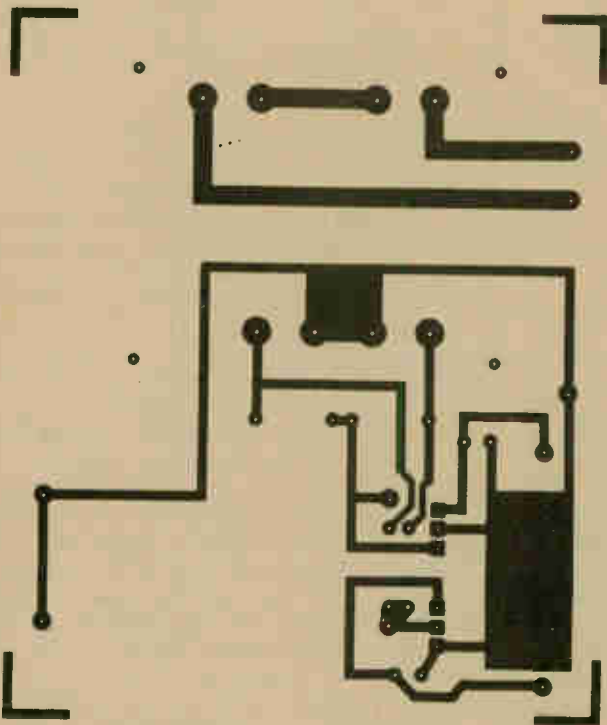
The pattern for the main board of the audio mixer.



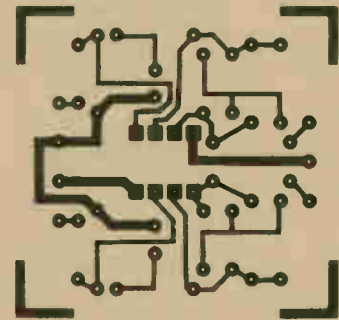The power supply board for the audio mixer.



The audio mixer RIAA input stage board

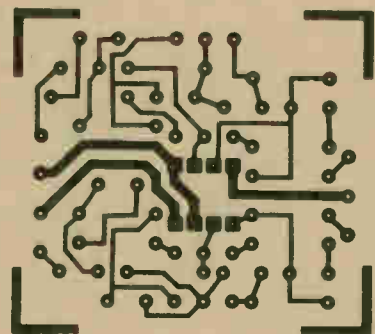

The optional tone control board for the audio mixer.

Designer's Notebook: Transistor Summary

A look at the several types of transistors available and the applications to which they are best suited.

By John Linsley Hood

AS A WORKING electronics engineer I tend to look unsympathetically at the propaganda of the *back to tubes* brigade. The enormous scope for circuit design now available to the electronics set is due entirely to the wealth of devices at our disposal. Of course, you have to know what devices are available and how to use them properly so that they perform up to specs, and it is also necessary to know their individual strengths and weaknesses so that you always use the most appropriate device for the job at hand. There are several types to choose from, so let's take a look.

Small Signal Junction Transistors

These exist as small metal cans or blobs of moulded plastic with three (or sometimes four) leads, as shown in Fig. 1. There isn't much difference these days between the longevity and reliability of plastic and metal can encapsulations, especially since the can is often just a receptacle into which epoxy resin has been poured to hold the silicon chip in place. Metal can types, especially those which are hermetically sealed, are usually far more expensive than plastic moulded types.

The chip inside the encapsulation will normally be of either the planar or the epitaxial planar type, both of which are shown in Fig. 2. Epitaxial (or epitaxial base) types have an additional thin layer of a different type of silicon grown on the chip by vapour phase techniques before the other diffusions have been made. They are cheaper and generally work better than other types and are therefore the most commonly used.

Typical power dissipations for small signal plastic transistors range from about 250 to 650 milliwatts. Metal can types typically handle from 300-1000mW dissipation. It's a good practice to keep dissipations down to about half of the rated maximum.

Small signal NPN and PNP transistors can generally be regarded as the *workhorses* in the small circuit field. They

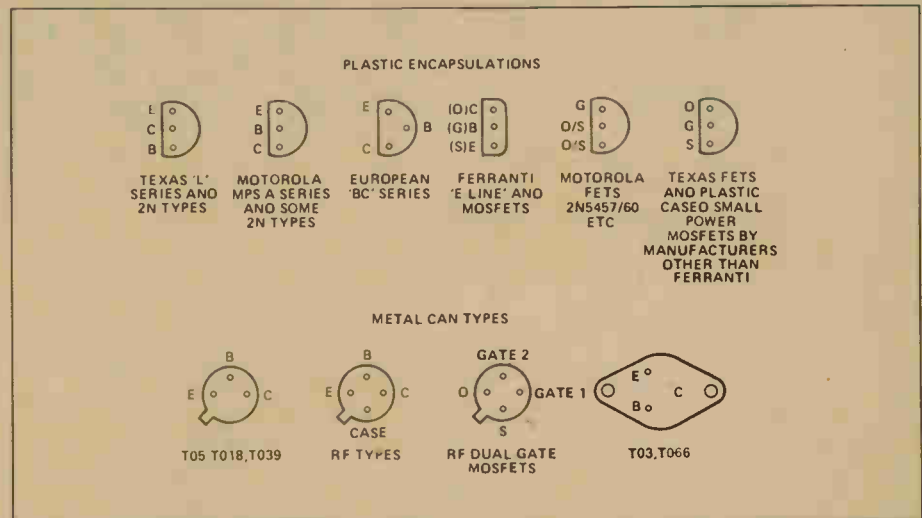


Fig. 1 Common transistor connection arrangements.

are easy to use, inexpensive, reasonably difficult to damage, and will work well when used within their limits. Certain types are particularly suited for use in very low-noise, low impedance applications. Because they can be used in complementary symmetry arrangements, some very crafty circuit layouts are possible. The circuit symbols for these devices are shown in Fig. 3a.

Darlington Transistors

These consist of a pair of small signal transistors coupled together in one case. They are available in NPN and PNP types and the circuit symbol for the NPN type is shown in Fig. 3b, with my own preferred symbol shown in Fig. 3c. They are similar to other junction transistors except that they have current gains of between 20000 and 50000 and relatively high input impedance. Typical input impedances would be from 100k to 250k for output currents of between 2 and 10mA, which is the range over which they work best. The Motorola MPSA-12/14 (NPN) and the MPSA-62/64 (PNP) are good examples. Inevitably they are more expensive than standard single transistors.

Junction Field Effect Devices

These were the original high impedance transistor types and are represented in circuit diagrams by the symbols shown in Fig. 3d. Their physical construction is shown in Fig. 4

They differ from junction bipolar transistors in that their input terminal, the gate, is normally non-conducting. In fact, it is a reverse biased junction diode, and the only current which will flow is the normal reverse leakage current of such a diode. Typical input impedances for good quality devices of this type range from ten thousand to a million megohms.

Contrary to popular belief, these devices will not normally be damaged by static charges any more than any other small signal diode would be, so they don't need special care in use. They're used in instances where high input impedances are needed, and where the cost of using a junction FET is justified - they are about five times the cost of an equivalent bipolar device. The better types are also less noisy in high impedance circuitry than bipolar devices but you need to choose carefully because some of the cheaper junction FETs are not very good in this respect.

★★★★★ **FIVE** ★★★★★
STAR PERFORMANCE
FROM



**DIGITAL + ANALOG
STORAGE SCOPES**

Whether recording lightning strikes,
crash impact data or heartbeats,
these digital and analog storage
scopes will capture them all.



**HIGH PERFORMANCE
CRT READOUT DISPLAY**

If top of the line is what you demand,
these outperformers will top your list
with features such as cursors, DVM,
programmable on screen text, etc.



**VIDEO WAVEFORM +
VECTOR MONITORS**

In the studio or on location,
the versatility and performance
of these instruments will steal the show.



**PERFORMANCE PROVEN
GENERAL PURPOSE**

From 20 MHz to 100 MHz
Hitachi's price/performance
combination is second to none.



TOUGH MINI SCOPES

These rugged ultra-portables
will take it, wherever the job
takes them.



Call us for Performance Proven Electronics

 **Hitachi Denshi, Ltd. (Canada)**

Head Office:
65 Melford Drive
Scarborough, Ontario M18 2G6
Tel: (416) 299-5900
Toll Free: 1-800-268-3597
FAX: 1-416-299-0450
Tlx: 06525324

Ottawa Office:
159 Colonade Road, Unit 3
Nepean, Ontario K2E 7J4
Tel: (613) 727-3930
FAX: 613-727-3955
Tlx: 053-4533

Eastern Office:
8096 Poute Trans Canadienne
St. Laurent, Quebec H4S 1M5
Tel: (514) 332-6687
FAX: 1-514-1664
Tlx: 05824768

Western Office:
3433-12th Street N.E.
Calgary, Alberta T2E 6S6
Tel: (403) 276-8505
FAX: 403-250-1634
Tlx: 03825861

OSCILLOSCOPES!

The Best Buys Available

Model 65601
Dual Trace Bench/Portable Scope




\$ 695.00
Probes & FST
included

Featuring at no extra cost 'The Component Tester'

- 20 MHz (-3dB) Bandwidth
- 6" CRT Display
- Fully Automatic Triggering
- Trace Rotator
- 5 mV Vertical Sensitivity
- HF Rejection

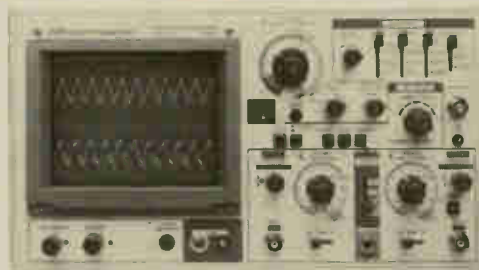Model 65635
Dual Trace Bench/Portable Scope



\$ 895.00
Probes & FST
included

- 35 MHz (-3dB) Bandwidth
- Delayed Sweep (selectable)
- Single Sweep (selectable)
- 6" CRT Display
- 1 mV Optimal Sensitivity
- X-Y or X-Y-Z Operation
- 120V AC Line Operation
- x5 Sweep Magnifier

MULTIMETERS!

Go for Quality --- Go for The Best Value

Models 78020, 78021, 78022

- AUTO ZERO
- AUTO POLARITY
- 3½ DIGIT LCD
- FULL OVERLOAD PROTECTION ON ALL RANGES
- RECESSED - SAFETY DESIGNED INPUT TERMINALS

- Supplied with:
- 28 Page Operating and Maintenance Manual
 - Calibration Certificate Traceable to NRC
 - Schematic with complete Parts Listing
 - Safety Test Leads
 - One-year Warranty



\$139.00*

- ◆ ±0.1% DC
- ◆ 2000 hrs Bat. life



\$ 99.00*

- ◆ ±0.25% DC
- ◆ 10 Amps AC+DC
- ◆ 200 hrs Bat. life



\$ 89.00*

- ◆ ±0.25% DC
- ◆ 200 hrs Bat. life

* F.S.T. incl.

Metermaster

A Div. of R.H. NICHOLS CO. LTD.

Head Office: 80 Vinyl Court
Woodbridge, Ontario L4L 4A3



5% Discount for Cash
plus Student Discount 5% on all products.
Certified Cheque, or Money Order
DEALER INQUIRIES INVITED

All prices F.O.B.
Woodbridge, Ontario
subject to change without
notice. P.S.T. extra
where applicable

Circle No. 21 on Reader Service Card

TORONTO (416) 741-9381 • MONTREAL (514) 337-0425 • EDMONTON (403) 432-7746 • OTTAWA (613) 727-3974

VANCOUVER (604) 937-3622 • SARNIA (519) 542-1201

Electronics Today October 1985

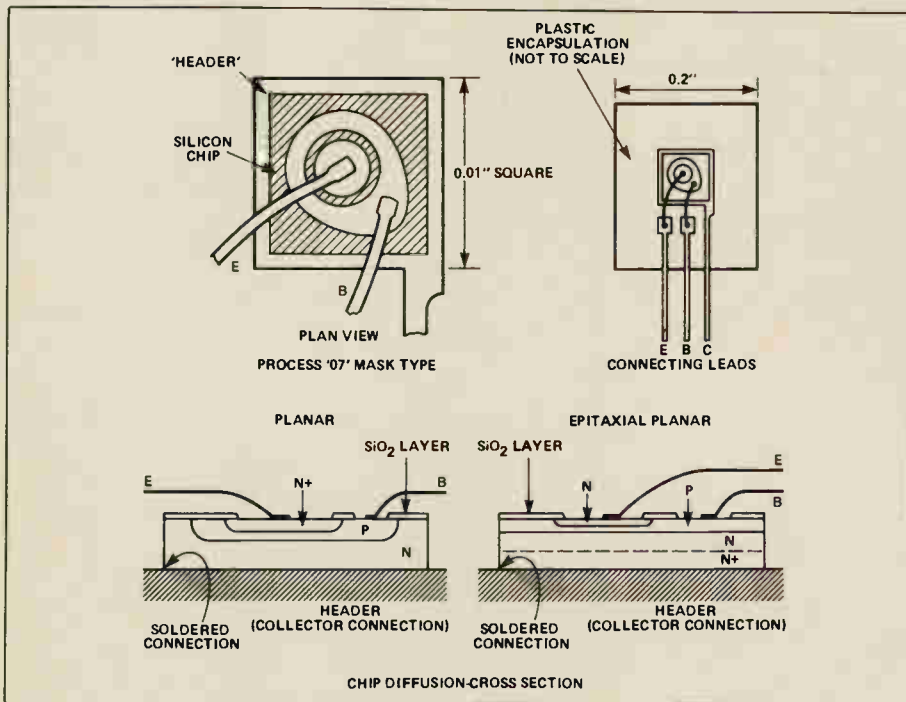


Fig. 2 The construction of a typical small-signal, plastic encapsulated transistor.

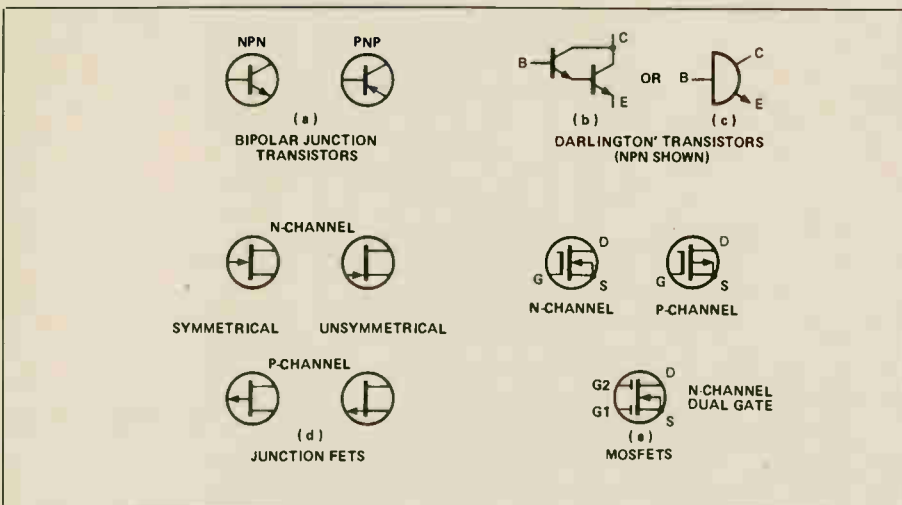


Fig. 3. Transistor circuit symbols.

Junction FETs also make good RF amplifier devices at frequencies up to about 300MHz, and can offer very low noise in this application. In circuitry, they will tend to have a lower stage gain than bipolar device, unless a very high impedance output load is employed which usually means an active load of some kind. They have a very flat drain current/drain voltage characteristic which makes them good at rejecting HT line ripple effects, and also allows them to be used as nearly ideal constant current sources.

The chip construction of a junction FET is shown in Fig. 5. The chip acts as a thin conducting layer of P-type or N-type silicon (germanium is almost never used

except in special cases), into which a depletion layer will expand, narrowing and finally cutting off the undepleted layer through which current may flow as the reverse bias potential applied to the gate is increased. Junction FETs are usually, though not always, symmetrical, so source and drain may be interchanged.

Small Signal MOSFETs

These devices, sometimes also known as insulated gate field effect transistors or IGFETs (MOSFET stands for Metal Oxide Silicon FET), have the general construction shown, for the wafer, in Fig. 6a. They work on the principle that if a charge (i.e., a voltage) is applied to an insulating layer, a charge of the opposite type will be attracted to the other face, as shown in Fig. 6b.

If that other face happens to lie in the body of a slice of high impedance (low impurity, or intrinsic) silicon, then current will flow in that charge layer. If the insulating layer is very thin, only a few volts need be applied to the gate in order to make current flow through the charge layer. The layer, which can be less than a micron thick, is usually made by oxidizing the outer face of the silicon slice, so that a metal layer can be deposited on it without making contact. It is normally capable of withstanding an applied voltage of some 20 or 30 volts only, and can be damaged by static charges or careless handling.

In order to make these devices a little less fragile in normal day to day use, it is customary to incorporate on the chip a couple of back-to-back zener diodes across the gate-source connections. This reduces the input impedance to perhaps a million megohms. It is possible to get unprotected MOSFETs which have a higher input impedance, but these need careful handling.

The most common variety of small signal MOSFET is the dual gate type shown in Fig. 7. This was specifically designed as a device for RF amplification and mixing in radio and TV tuners, and is

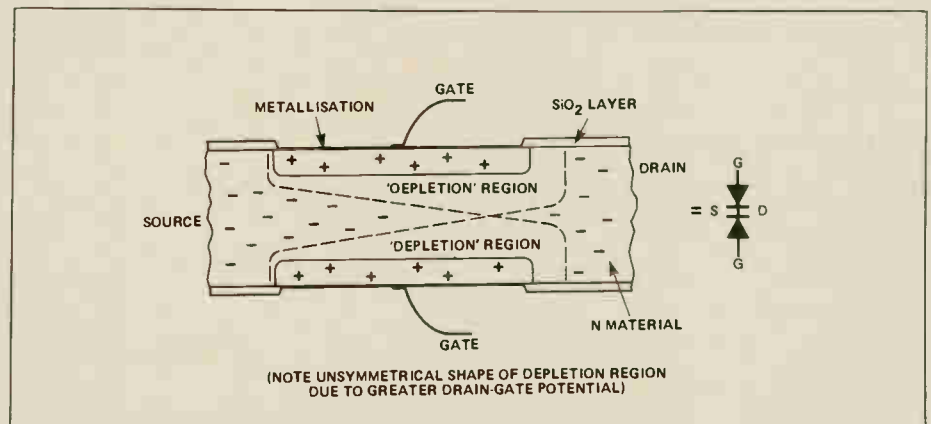


Fig. 4 Cross-sectional view of an N-channel FET, showing the depletion regions which result when the device is just biased to cut-off.

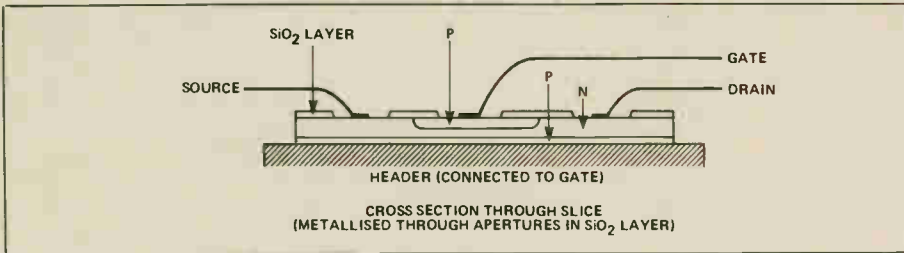


Fig. 5 Cross-sectional view of an N-channel small signal junction FET.

useable up to a few hundred megahertz. The second gate can be used to screen the input signal from the output signal on the drain, permitting stable RF amplification. In this application, it acts in a similar way to the screened-grid or RF pentode type tube. The circuit symbol for these transistors appear in Fig. 3c.

All of these MOSFETs require a forward voltage applied to the gate electrode to cause them to conduct. This will be positive in the case of N-channel MOSFET (operating on a positive DC supply line) and negative in the case of the less common P-channel types. Small signal devices of this type will typically have a mutual conductance or G_m of a

few milliamps per volt. This allows a simple calculation of stage gain from:

$$\text{Gain} = G_m \times R_L$$

where R_L is the effective load impedance.

Recently, small signal versions of the T-MOS type of power MOSFET have been introduced. These have a slightly different type of chip construction to the

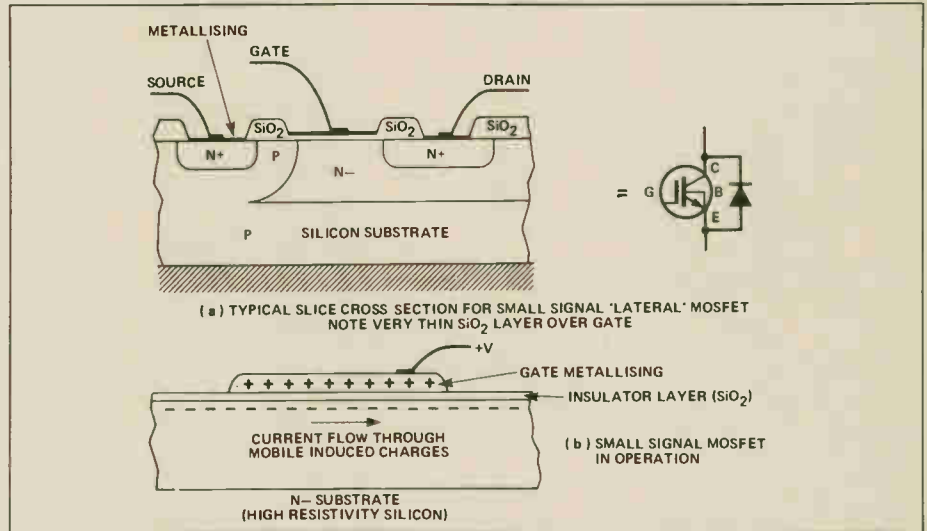


Fig. 6 Cross-sectional views showing the construction and operation of a MOSFET.

	TYPICAL INPUT IMPEDANCE	TYPICAL STAGE GAIN	OUTPUT IMPEDANCE (COMMON EMITTER)	TYPICAL MAXIMUM WORKING FREQUENCY	NOISE FIGURE (dB) (MINIMUM)	TYPICAL (MAX) WORKING VOLTAGE	TYPICAL (MAX) WORKING CURRENT	COMMENTS
SMALL SIGNAL JUNCTION TRANSISTORS	0.5-20k	40-200	200k +	300MHz	1dB	150V	500mA	NOT VERY LINEAR WITHOUT NFB
SMALL SIGNAL DARLINGTON TRANSISTORS	250k	100-500	200k	100MHz	6dB	40V	1A	TEMPERATURE SENSITIVE
JUNCTION FETS	$10^{11}R$	10-30	10M	400MHz	2.5dB	30V	15mA	LINEAR
DUAL-GATE MOSFETS	$10^{12}R$	50-100	500k	500MHz	2dB	20V	20mA	CAN BE DAMAGED BY STATIC CHARGES
SMALL POWER MOSFETS	$10^{12}R$	50-200	250k	500MHz	6dB	100V	1A	CAN BE DAMAGED BY STATIC CHARGES- VERY LINEAR
POWER TRANSISTORS (NPN)	10-200R	10-30	5k	40MHz	N/A	400V	25A	CAN SUFFER FROM 'HOLE' STORAGE EFFECTS
POWER TRANSISTORS (PNP)	10-200R	10-30	5k	10MHz	N/A	100V	15A	SOMEWHAT SLUGGISH & SUFFER FROM 'HOLE' STORAGE
POWER DARLINGTONS	20k	50 +	5k	4MHz	N/A	120V	15A	SLUGGISH AND SUFFER FROM 'HOLE' STORAGE
POWER MOSFETS	100M +	50 +	10k	500MHz	POOR	750V	10A	HIGH INPUT CAPACITANCE-PRONE TO OSCILLATE IF NOT PREVENTED
POWER FETS	10M +	10 +	5k	100MHz	N/A	?	?	HIGH OPERATING CURRENT REQUIRED

Table 1 A comparison of the characteristics of different transistor types.

normal small signal MOSFET, shown in Fig. 8. Their big advantage is that they can withstand drain voltages of up to about 100V, whereas the average dual-gate device or small signal junction FET can only cope with some 20-30V.

By comparison with bipolar tran-

Bipolar Junction Power Transistors

These are heavier duty versions of the small signal transistors we have already come across, and range in current handling capacity from an ampere or so for some of the small plastic encapsulated

Power junction transistors are available in NPN and PNP types, just like small signal devices, but the PNP versions tend to be a bit slower in action and a bit less burst-proof than the NPN ones. You should beware of assuming that because they are complementary in characteristics they can be treated as identical. A nice comment I once heard was that "NPN and PNP transistors are as similar as a man and a woman of the same height and weight".

The transition frequency of a power transistor, that is, the frequency at which the current gain falls to unity, will usually lie within the range of 4-20MHz, which is considerably lower than the transition frequency of a typical small signal device which would probably be between 100 and 400MHz. In addition to being more sluggish than small signal types, power transistors also have lower current gains. Whereas a small signal junction transistor has a typical current gain of 100-500, a power device might have a current gain of only 15-80, with the lower values usually being found at higher collector currents.

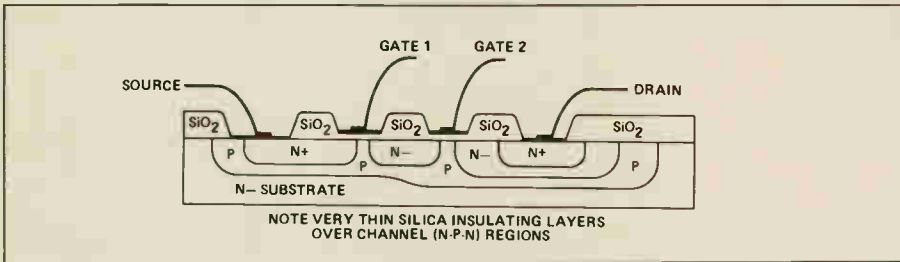


Fig. 7 Cross-sectional view of a dual-gate MOSFET.

sistors, MOSFETs are much more linear in their characteristics and do not suffer from operational problems such as thermal runaway and hole storage. The absence of this latter defect makes small signal T MOS devices considerably better than bipolar junction devices when used in the class A stages of audio amplifiers.

The circuit symbol used for the T MOS device is the same as that used for other MOSFETs except that they are only available in single gate versions.

The normal operating characteristics of the various small signal transistors are shown in Table 1, and a group of curves showing their input voltage/output current characteristics are in Fig. 9.

types with a metal cooling tag to 400 amperes in the case of some of the big industrial devices.

Permitted dissipations, with adequate heat-sinking, range from one to many hundreds of watts, and maximum collector voltages can be up to 500-1000 volts in specialized types, with 60-150V being more common in easily found devices such as the 2N3055 or 2N3442.

There isn't a big difference in price between the plastic encapsulated types and the hermetically sealed TO66 or TO3 versions, so for DIY projects where you aren't buying a lot of power transistors, the metal can versions may be preferable. They are certainly easier to cool.

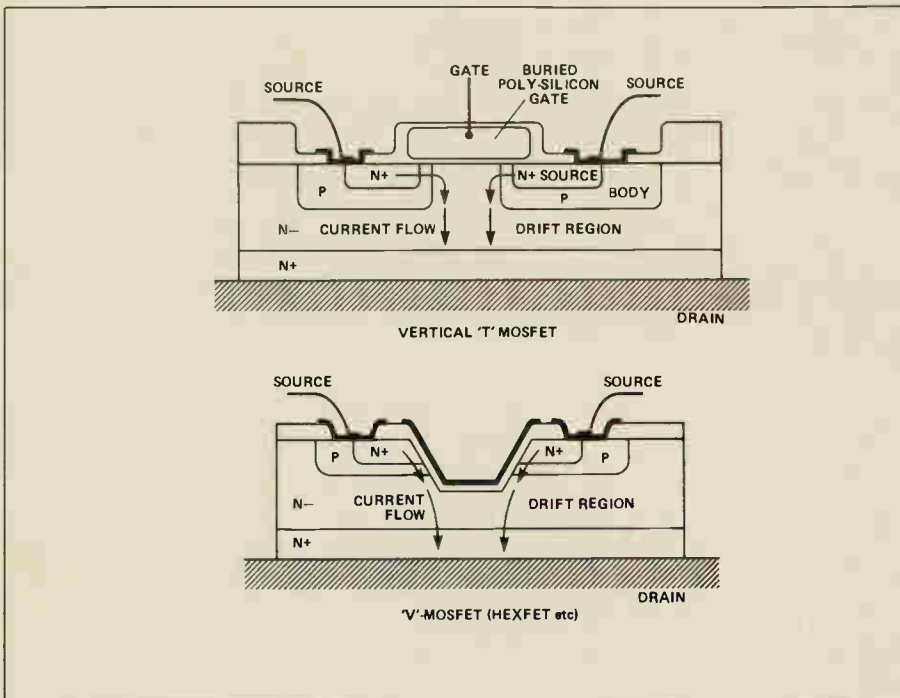


Fig. 8 Cross-sectional views of MOSFETs.

AMAZING SCIENTIFIC and ELECTRONIC DEVICES

LASER DEVICES

- LC5 BURNING CUTTING CO2 LASER \$20.00
- RUB3 RUBY LASER RAY PISTOL 20.00
- LRG3 IR LASER RIFLE/PISTOL 10.00
- LGU3 VISIBLE RED LASER RIFLE 10.00
- LBT1 - LIGHT BEAM COMMUNICATOR 10.00
- LHC2 BEGINNER simulated VISIBLE LASER 5.00

SCIENTIFIC & ELECT

- TCL3 SOLID STATE TESLA COIL 35KV 6.00
- BTC3 250 THOUSAND VOLT TESLA COIL 9.00
- BTC5 1.5 MILLION VOLT TESLA COIL 15.00
- GRA1 - GRAVITY GENERATOR 10.00
- IOG3 ION RAY FORCE FIELD GUN 8.00
- PTG1 - PLASMA TORNADO GENERATOR 10.00

ULTRASONIC ACCOUSTICAL

- PPF1 PHASOR PAIN FIELD GENERATOR 15.00
- PS3 PHASOR SHOCK WAVE PISTOL 7.00
- IPG5 POCKET PAIN FIELD GENERATOR 7.00
- RAT2 RAT AND PEST ELIMINATOR 6.00
- HT9 HIGH FREQ. LISTENING DEVICE 8.00

SECURITY & PROTECTION

- STG1 - STUN AND PARALYZING GUN 7.00
- PPG1 PHASOR PROPERTY GUARD 15.00
- MFT1 MINI VOICE XMTR 2-3 MILE 7.00
- INF1 INFINITY TRANSMITTER 15.00
- PSW3 PHASOR BURNING STUN WAND 7.00
- ITMI INTIMIDATOR PLASMA GUN 10.00

WE STOCK ALL PARTS NECESSARY FOR CONSTRUCTION OF THE ABOVE PROJECTS

• CATALOG CONTAINING HUNDREDS MORE OF ALL NEW AMAZING and FASCINATING PLANS. EASY TO BUILD KITS AND ASSEMBLED ITEMS \$1.00. CATALOG INCLUDED FREE WITH ANY OF THE ABOVE PROJECT PLANS. SEND CASH, CHECK, MO, VISA, MC IN US FUNDS.

INFORMATION UNLIMITED

P.O. Box 716, DEPT. ET, AMHERST, NH 03031

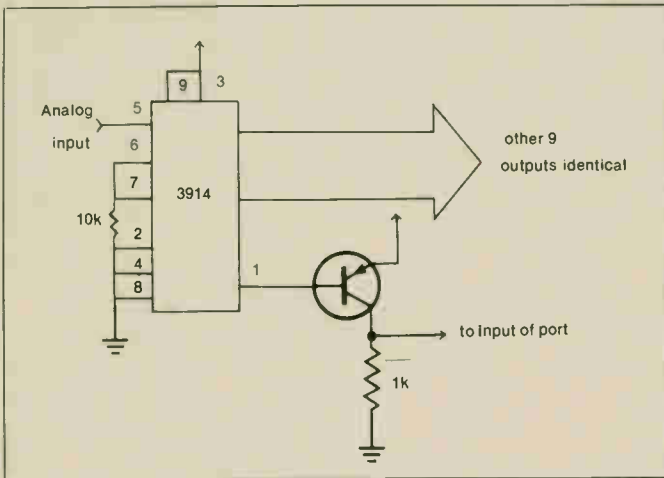


Fig. 5 Converting analog to digital using the LM3914.

Inputs without the PIO

Although the PIO is quite handy with limited I/O ports it can get quite expensive when more input ports are needed. Fig. 6 shows a 74LS245 tristate buffer connected to the CPU as an input port. This circuit uses a 74LS138 3 to 8 line multiplexer to decode the address bus. Only the upper 128 I/O address space is decoded leaving 128 address locations available for other I/O activity. The address of the input port is decoded to be 80H. Seven more input ports can be connected with corresponding addresses from 81H to 87H.

Output Devices and the CPU

Perhaps the simplest output device to be connected to the CPU is an LED or lamp. Fig. 7 shows the schematics for connecting led's and lamps, and in some cases a driver transistor is needed depending on the load. Selecting the proper base resistor to drive the transistor into satura-

tion will eliminate the need for a heat sink in most applications. The software is straight forward, a low at the output turns on the LED and a high turns it off.

Seven segment displays allow us to display numbers and various letters and patterns with only seven outputs. Fig. 8 shows the connection of two seven segment displays to a PIO. While this method might be sufficient for two displays, another method must be employed for 3 or more displays. This method calls for multiplexing the displays.

In this method each display is lit up one at a time over and over again. This is done fast enough so the human eye does not notice. Fig. 9 shows the schematic for connecting 8 seven segment display units; one output port is used to drive the seven segments and another port is used to turn on the individual displays.

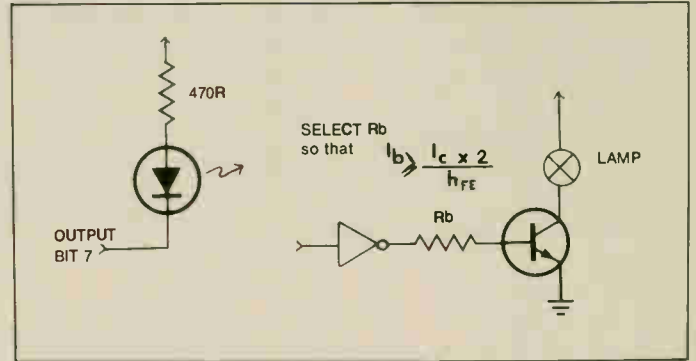


Fig. 7 Connecting LEDs and lamps to the PIO.

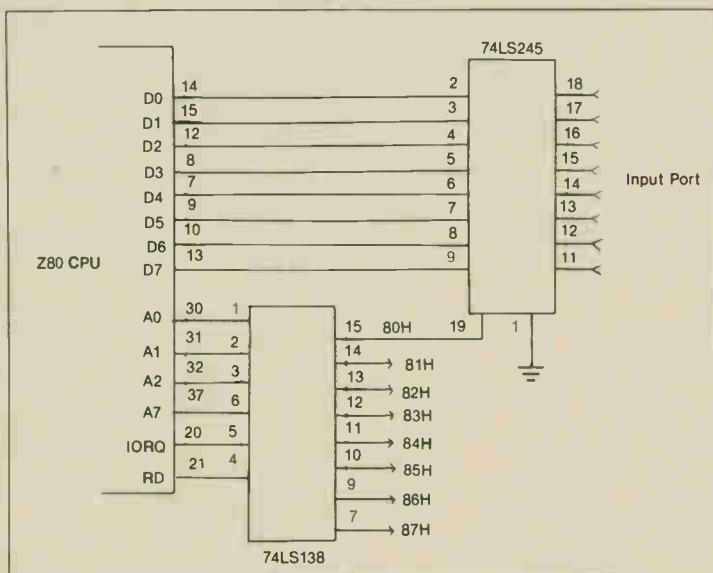


Fig. 6 A 74LS245 used as an input port.


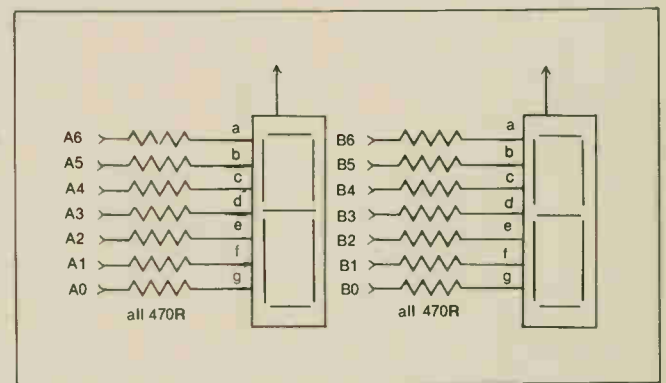


Fig. 8 Connecting two common anode displays to the PIO.

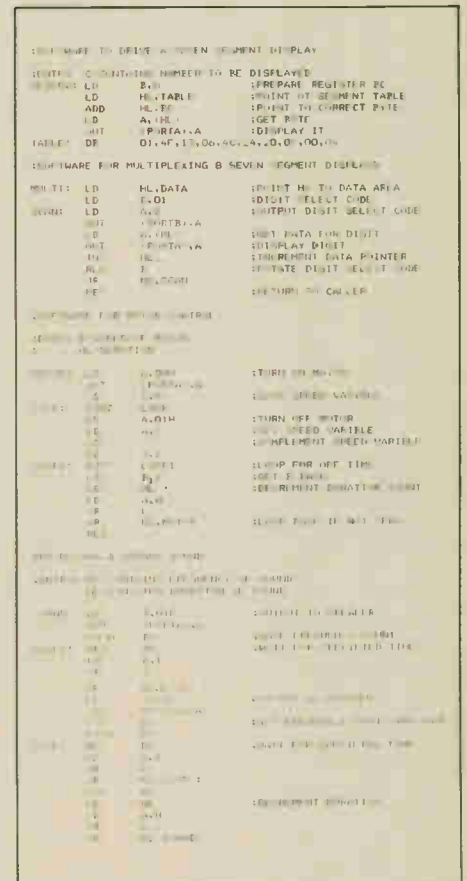

ELECTRONICS BOOK CLUB

Keep In Step With the Future . . . Become a Part of the Fascinating World of Technology!


- High-Tech How-To
- Space Age Projects
- Digital Electronics
- Artificial Intelligence
- Robotics
- Computers
- Telecommunications
- *And much more!*

Select 5 Books for Only \$2⁹⁵


(Values to \$109.75)



1277
List \$21.95

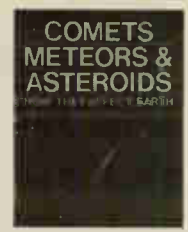


1905P
List \$12.95 paper

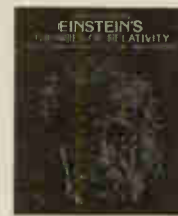

1505P
List \$11.50 paper



1650
List \$19.95

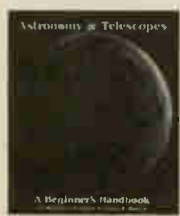

1419P
List \$14.95 paper



1183
List \$16.95



1449
List \$19.95




1672
List \$18.95



1199
List \$21.95



1632P
List \$11.95 paper

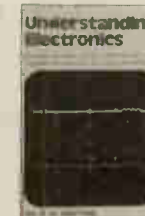

1113
List \$12.95



1671P
List \$16.95 paper




1673
List \$13.95



1211P
List \$12.95 paper



1013
List \$14.95

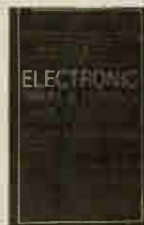


1625P
List \$13.95 paper



1465
List \$16.95




1996
List \$18.95

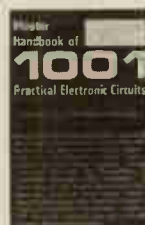

800P
List \$19.50 paper



1909
List \$21.95

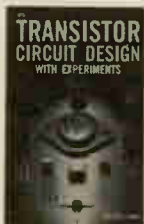

1875
List \$21.95



1536
List \$14.95



1474P
List \$12.95 paper



1539P
List \$15.95 paper



1765
List \$21.95



1825
List \$15.95

FREE:
"The Handbook of Electronic Safety Procedures"
A \$17.95 Value!



FREE When You Join Now

7 very good reasons to join the Electronics Book Club

- **Big Savings.** Save 20% to 75% on books sure to increase your electronics know-how
- **No Risk Guarantee.** All books returnable within 10 days without obligation
- **Club News Bulletins.** All about current selections—mains, alternates, extras—plus bonus offers. Comes 13 times a year with hundreds of up-to-the-minute titles to pick from
- **Automatic Order.** Do nothing, and the Main selection will be shipped automatically! But . . . if you want an Alternate selection—or no books at all—we'll follow the instructions you give on the reply form provided with every News Bulletin
- **Bonus Books.** Immediately get Dividend Certificates with every book purchased and qualify for big discounts of 60% to 80%.
- **Extra Bonuses.** Take advantage of added-value promotions, plus special discounts
- **Exceptional Quality.** All books are first-rate publisher's editions selected by our Editorial Board and filled with useful up-to-the-minute information.

Electronics Today October 1985

ELECTRONICS BOOK CLUB

P.O. Box 10,
Blue Ridge Summit, PA 17214

Please accept my membership in the Electronics Book Club and send the 5 volumes circled below, plus my FREE copy of *The Handbook of Electronic Safety Procedures* (#1420H), billing me \$2.95 plus shipping and handling charges. (Payable in U.S. dollars.) If not satisfied, I may return the books within ten days without obligation and have my membership canceled. I agree to purchase 4 or more books at regular Club prices (plus shipping/handling) during the next 12 months, and may resign any time thereafter.

800P 1013 1113 1183 1199 1211P 1277 1419P 1449
1465 1474P 1505P 1536 1539P 1625P 1632P 1650
1671P 1672 1673 1765 1825 1875 1905P 1909 1996

Name _____
Address _____
City _____
State _____ Zip _____ Phone _____

Valid for new members only. Foreign applicants will receive ordering instructions. Canada must remit in U.S. currency. This order subject to acceptance by the Electronics Book Club.

ETY-1085

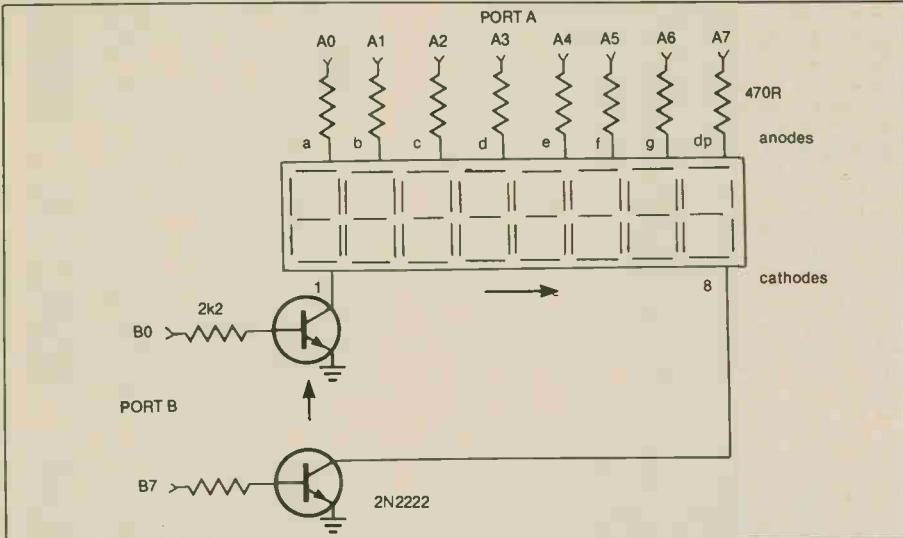


Fig. 9 Multiplexing 8 seven-segment LED displays.

```

; *****
; 100 SAMPLES-INPUT
;
; FOR THE FOLLOWING EXAMPLES IT IS ASSUMED
; INPUT PORT ADDRESS FBH
; OUTPUT PORT ADDRESS F9H
; *****
; - PUSH BUTTON INPUT
PBIN:  IN    A,(FBH)      ;READ INPUT PORT
      AND   B0H         ;MASK OFF BITS 0-6
      JP    Z,PBON      ;JUMP TO PBON IF BUTTON PRESSED
      JP    NZ,PBOFF    ;JUMP TO PBOFF IF BUTTON NOT PRESSED

; --PUSH BUTTON INPUT WITH DEROUNCER SOFTWARE
PBIN2: IN    A,(FBH)     ;READ INPUT PORT
      AND   B0H         ;MASK OFF BITS 0-6
      PUSH AF          ;SAVE REGISTER A
      CALL  DELAY       ;WAIT FOR 20MS
      POP  AF          ;RESTORE REGISTER A
      LD   B,A         ;SAVE IN REGISTER B
      IN   A,(FBH)     ;READ INPUT PORT
      AND   B0H         ;MASK OFF UNWANTED BITS
      CP   B           ;CHECK TO SEE IF SAME AS BEFORE
      JR   NZ,PBIN2    ;NO-GO BACK AND READ PORT AGAIN
      CP   A           ;SET FLAG FOR REGISTER A AGAIN
      JP   Z,PBON      ;JUMP TO PBON IF BUTTON PRESSED
      JP   PBOFF      ;JUMP TO PBOFF IF NOT PRESSED

; - ROUTINE TO SCAN AN 8 X 8 KEYPAD
; OUTPUT FROM ROUTINE- REGISTER A FFH NO KEY PRESSED
; OTHERWISE KEY CAP NUMBER
KEYPAD: LD   B,FEH     ;PRESET COLUMN SCAN REGISTER
      LD   C,FFH     ;KEY CAP COUNTER
      MOV  DI,A,B     ;OUTPUT COLUMN SCAN REGISTER
      OUT  (F9H),A    ;INPUT DATA FROM THAT COLUMN
      IN   A,(FB)    ;COMPARE FOR KEY PRESSED
      CP   0FFH      ;YES- GET KEY CAP NUMBER
      JR   NZ,GETKEY ;NO- GET KEY CAP NUMBER
      RL  B          ;ROTATE COLUMN SCAN REGISTER LEFT
      JP  C,CSCAN    ;CARRY RESET IF ALL COLUMNS SCANNED
      RET           ;RETURN TO CALLER REGISTER A CONTAINS FF

GETKEY: INC  C       ;INCREMENT COLUMN COUNTER
      RL  B         ;ROTATE COLUMN SCAN REGISTER LEFT
      JP  C,GETKEY  ;STOP UNTIL COLUMN NUMBER FOUND
      SL  C         ;MULTIPLY C BY B
      SL  C
      GETROW: INC  C ;INCREMENT KEY CAP COUNTER
      RL  CA        ;ROTATE ROW REGISTER LEFT
      JP  C,GETROW  ;CARRY RESET WHEN ROW NUMBER FOUND
      DEC C         ;ADJUST KEY CAP COUNT TO 0-63 RANGE
      RET

; - ROUTINE TO INPUT FROM A POTENTIOMETER
POT:  LD   B,0       ;ZERO TIMER COUNT
      LD   A,00H    ;TRIGGER TIMER
      OUT  (F9H),A
      LD   A,B0H
      OUT  (F9H),A
      LD   IN   A,(FBH) ;READ TIMER STATUS
      AND  B0H
      TR   Z,TIMOUT ;TIME OUT IF INPUT ZERO
      INC  B         ;INCREMENT TIMER COUNT
      JR   NZ,LOOP
      TIMOUT: RET   ;RETURN TO CALLER B-CONTAINS DIGITAL
              ;EQUIVALENT OF POTENTIOMETER POSITION

; - SUCCESSIVE APPROXIMATION METHOD OF A-D CONVERSION
RADC: LD   B,000H   ;TRIAL BIT REGISTER
      XOR  A        ;CLEAR A REGISTER
      RADC1: OR   B  ;SET TRIAL BIT IN A
      OUT  (F9H),A ;OUTPUT ON DAC
      LD   C,A      ;SAVE DAC OUTPUT
      IN   A,(FBH) ;TEST COMPARATOR INPUT
      AND  000H    ;MASK OFF OTHER BITS
      LD   A,C      ;RETURN DAC OUTPUT
      JR   NZ,RADC ;KEEP BIT ON IF INPUT G.T. REFERENCE
      XOR  B        ;TURN BIT OFF
      RADC:  RL  B  ;SHIFT TRIAL BIT RIGHT
      JR   NC,RADC1 ;CARRY SET IF CALCULATION DONE
      RET          ;RETURN TO CALLER- REG A-DIGITAL EQUIV.
    
```

THANKS ETI

Your readers' response to our Hameg-BCS sale for the German made HM-203-5 was so overwhelming, we sold out our entire stock before September 30th. We are therefore extending a raincheck to all those who were unable to have this scope from stock. We at BCS regret this shortage as our policy is never knowingly to advertise what is not immediately available.

Until October 31/85
Hameg Model HM 203-5,
complete with switch-
able probes and 2 year
parts & labour warranty

\$675⁰⁰ FST included
PST extra

FOB Downsview, Ontario (shipping extra)




980 Alness St. Unit 7,
Downsview, Ontario
M3J 2S2
(416) 661-5585
TELEX 065-28169

Mon.-Fri. 8 am - 5 pm
Saturday: 10 am - 1 pm

HAMEG

HM 208

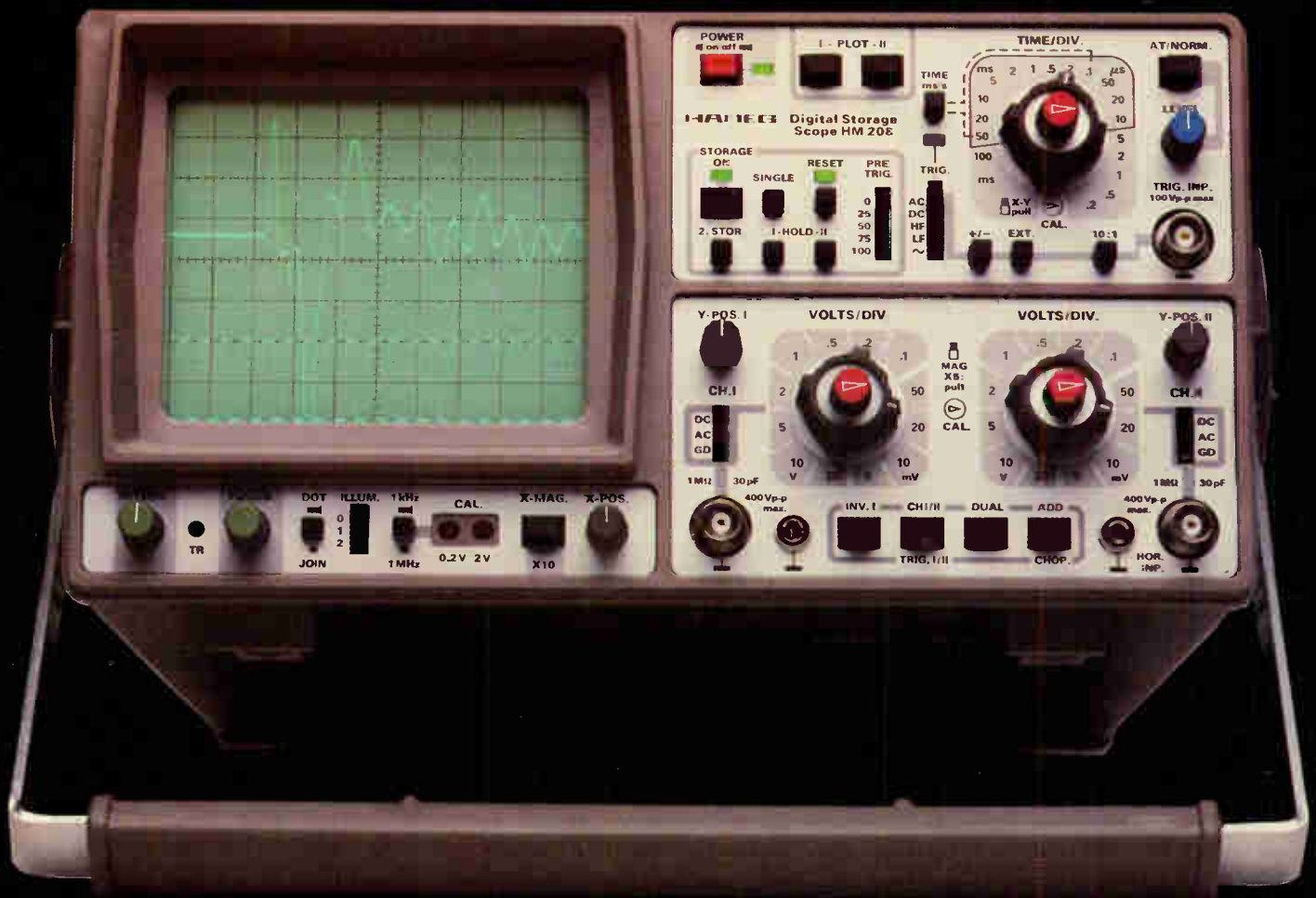

The High Performance
Digital Storage Oscilloscope
at an Economical Price!

20MHz Two Channel Oscilloscope
or as a digital storage oscilloscope with
20MHz in One Channel Operation and
2 x 10MHz in Two Channel Use.
2 Switchable x1 - x10 Probes included

\$2700 FST*
included

*F.O.B. Downsview: Price subject to change

BCS
ELECTRONICS
LIMITED

980 Alness St. Unit 7,
Downsview, Ontario
M3J 2S2
(416) 661-5585
TELEX 005-28169
Mon.-Fri. 8 am - 5 pm
Saturday: 10 am - 1 pm

PATRON COMPONENTS INC.

Stock Distributor of Memories I.C. (U.S.A./Japan),
All New Parts. Min. 1000 pcs.

RAM/EPROM:

- 16K DRAM (4116) from \$0.50 EPROM (2716) \$2.45
- 64K DRAM (4164) from \$1.10 EPROM (2764) \$3.15
- 128K DRAM (4128) from \$8.05 EPROM (27128) \$3.95
- 256K DRAM (41256) from \$5.45
- EPROM (27256) \$11.85
- 16K SRAM (6116,2016) from \$2.10
- 64K SRAM (6264,5565) from \$6.70

T.T.L.:

(74LS00 etc.) from \$0.17

4000 CMOS:

(CD4001 etc.) from \$0.17

LINEAR:

LM324 etc.) from \$0.21

MICROPROCESSOR:

8088 Kit set (8088, 8253, 8237, 8284, 8288, 8259, 8255)
from \$33.10 per set

Please call for other 8000 series MPU/O.E.M. price and delivery.

IBM* PC/XT EXPANSION PRODUCTS

Main Board 8 Slot (OK)	\$199.00
Main Board 8 slot (256K)	\$250.00
Colour Graphic Card	\$ 99.00
Multifunction Card (OK)	\$ 99.00
Multifunction Card (384K)	\$149.00
512K RAM CARD (OK)	\$ 95.00
765 Controller Card	\$ 69.00
130 WATT Power Supply	\$129.00
Monochrome Card	\$ 89.00
Monochrome Graphic Card	\$129.00
NEW-TECH Keyboard (for IBM)	\$ 69.00
JA551-2/5 (Disk Drive for IBM)	\$129.00
Asuka F.D.D. (for Apple** 2)	\$129.00
KEYTRONICS 5151 Keyboard (for IBM)	\$170.00

Quantity under 10 pcs. e.a. Please add 5% extra.

XT COMPATIBLE COMPUTER \$1050.00

includes: 256K 8088 XT (Japan) mother board, Colour graphic card
two 360K DS/DD disk drive, Controller card, Case, keyboard, 130
with power supply.

*A Registered Trademark of IBM Canada Ltd.

**A Registered Trademark of Apple Canada Ltd.

Price subject to final confirmation. Please call for details.

MAIL ORDERS:

For quantities under 1000 pcs, please add 25% extra from above
price plus postage and provincial tax.

We can ship C.O.D. freight collect for larger quantities.

4002 Sheppard Ave. E., Suite 506,
Agincourt Commercial Centre,
Scarborough, Ontario, M1S 1S6 Canada
Tel: (416) 299-7731 FAX: 416-298-4569
Telex: 065-25256

K.E.M.

HIGH SPEED EPROM PROGRAMMER ---- \$175.00

FROM 2716 UP TO 27256. ALL ROUND TYPES. ONE TOUCH OPERATION
INCLUDING 'A' AND 'CMOS' VERSIONS.


(EXAMPLE)

2784 --- 30 SEC
27256 --- 120 SEC

I/F CARD FOR **APPLE** OR **IBM**

UP TO 256!

IBM I/F CARD →

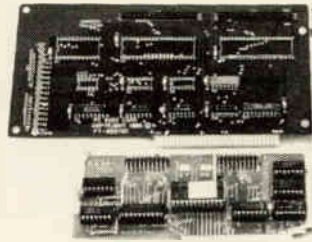


APPLE I/F CARD →

UV LAMP WITH HOLDER -- \$26.98

FOR Photosensitive PCB Exposing
or UV-EPROM Erasing.

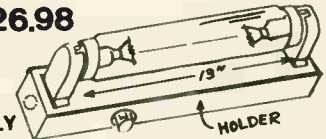When you order, please let us
know which type, exposing
or erasing.




HIGH SPEED 10MIN ONLY

ROBOTICS TRAINING I/O "ODEN" ----- \$149.00

INCLUDES STEPPING MOTOR DRIVER, SPEAKER OUTPUT,
8 BIT LED DISPLAYS, PHOTO-, THERMAL-, SOUND-SENSORS,
MANUAL DATA ENTRY SWITCHES, RELAYS.

I/F CARD ----- FOR **APPLE** OR **IBM**

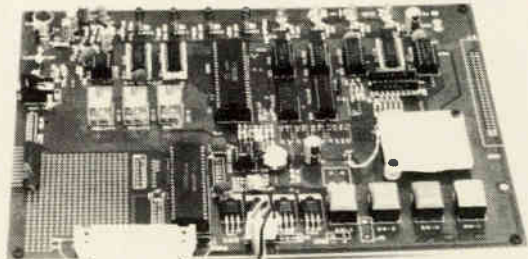DC MOTOR CONTROLLER & ULTRA SONIC RADAR UNIT(OPTION)




JUST CHANGE YOUR I/F CARD. YOU CAN SWITCH TO IBM OR APPLE.

EXTRA I/F CARD FOR 'PROGRAMMER' OR 'ODEN' ----- \$69.00

STEPPING MOTORS & DRIVERS (ASK FOR DETAIL)

MOTORS (SEVERAL MODELS)	TORQUE RANGE	280g-cm --- 20Kg-cm
	PRICE RANGE	\$16.00 --- \$165.00
DRIVERS		\$65.00 --- \$169.00

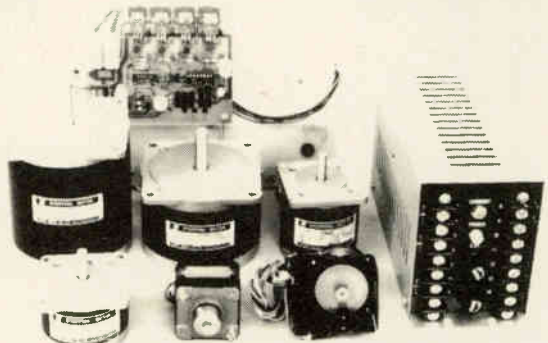

PLUS \$5.00 FOR SHIPPING. PLUS PROV. TAX WHERE APPLICABLE.
PLUS CANADA POST COB FEE IF REQUESTED.
PRICES & SPECIFICATIONS ARE SUBJECT TO CHANGE WITHOUT NOTICE.

KEM (KAIENTAI) Electronics Ltd.

879 EAST HASTINGS STREET, VANCOUVER, B.C. V5K 4W4
PHONE (604) 251-1514

MEGURO/RCC - MORE FOR YOUR INSTRUMENT DOLLAR



'SCOPE for 100 MHz

The MO-1255 100 MHz 'scope features 3-channels and 6 traces. Has alternate sweep, 6-inch rectangular high luminance internally calibrated CRT, wide dynamic range and 2-channel X-Y operation.

Control logistics make this unit exceptionally easy to operate. Has TV sync. separator circuit and 20 MHz bandwidth limiter.



LOGIC ANALYZER - 16 channel

The MLA-3300 combines timing analyzer, state analyzer and signature analyzer in one. Has 16-channel input and 100 ns resolution at 10 MHz. Portable, battery or AC operation, low power

LCD display. Comparative acquisitions are easy with 256 bit/channel acquisition and reference memories. Menu operated



DIGITAL STORAGE 'SCOPE 2 MHz sampling

MSA-1270 features 2-channels, each with 2 kiloword 8-bit A/D converter for high density, high speed, dual phenomena monitoring. Has trigger level marker display, pre and post trigger functions, and

simply switches to a 20 MHz oscilloscope. Simultaneous hard copy recording possible with external trigger.



SPECTRUM ANALYZER 1-300 MHz

The MSA-4901 spectrum analyzer covers 1 to 300 MHz with a logarithmic-scaled frequency domain and vertical axis. TV scanning mode permits CATV and VHF TV bands measurements for field

strength and terminal levels. Calibration mode at -30 dBm and 20 MHz. LCD centre-frequency display.

meguro

RCC ELECTRONICS

310 JUDSON ROAD, UNIT 6, TORONTO M8Z 5T6. (416) 252-5094

Montreal: 6600 Trans Canada Highway, Suite 750, Pointe Claire, Quebec, H9R 4S2, Telephone: (514) 694-6080, Telex: 05-821762

Vancouver: 119-255 West 1st Street, Unit 3, North Vancouver, B.C., V7M 3G8, Telephone: (604) 985-4065, Telex: 04-352841

Circle No. 28 on Reader Service Card



THE WORLD'S MOST POPULAR PORTABLES GO DIGITAL!

Now Tektronix gives you three new choices in digital storage oscilloscopes. They build on the high-value, high-performance standards that Tektronix is famous for. And they set some standards of their own – in performance, price and ease of use.

The new Tek 2430 features 150 MHz bandwidth, a 100 Ms/s digitizing rate and dual channel acquisition. It's a powerful combination that lets you digitize, view and store high bandwidth and complex signals. Also offering 8-bit vertical resolution, 1K record length per channel and a 0.01% crystal-controlled timebase, the 2430 is an advanced measurement package with many sophisticated capabilities including 2 ns glitch capture.

With its simple menu format and familiar front panel controls, you can put the 2430 right to work in one application after another – from applied research to product design to the automated production line.

If it's economy you want, for performance that's best in its class, the new Tek 2230 and 2220 offer solid features at exceptional prices. Included: storage and non-storage bandwidths of 100 MHz in the 2230 and 60 MHz in the 2220. Sampling at 20 Ms/s with 8-bit vertical resolution. Plus 4K record length with save reference memory and expansion, compression, and positioning of save reference waveforms.

Both scopes offer optional

GPIB or RS-232-C interfaces, with 26K of battery-backed reference memory included in 2230 options. All of this in scopes that are easy to use and affordable!

Contact the Tektronix office or sales representative nearest you for complete details. Each scope is backed by Tek's 3-year warranty, plus excellent documentation, training programs and outstanding service support – worldwide.

Copyright © 1985, Tektronix, Inc. All Rights Reserved.

Features	2430	2230	2220
Maximum Sampling Rate	100 MS/s	20 MS/s	20 MS/s
Equivalent Time Bandwidth	150 MHz	100 MHz	60 MHz
Interface	Standard	GPIB/RS-232-C	GPIB/RS-232-C
	Fully Programmable	Optional (Talker/Listener)	Optional (Talker/Listener)
Record Length	1K/CH	4K/1K Selectable	4K
Peak Detect	Yes (2 ns)	Yes (100 ns)	Yes (100 ns)
Signal Averaging	Yes	Yes	(repetitive sampling)
X-Y Storage Bandwidth	150 MHz	100 MHz	60 MHz
Pre/Post Triggering	Yes/Select	Yes/Select	Yes
Cursor Measurements	ΔT , $1/\Delta T$, ΔV , dB, slope, %	ΔT , $1/\Delta T$, ΔV	No
CRT Readout	Yes	Yes	No
Save on Delta	Yes	No	No
Self Calibration	Yes	No	No
Front Panel Setting Recall	Yes	No	No
Warranty	3-Year	3-Year	3-Year

Vancouver – (604) 438-4321
Toronto – (416) 675-3865
Calgary – (403) 250-7583
Ottawa – (613) 225-2850

Edmonton – (403) 434-9466
Montreal – (514) 697-5340
Winnipeg – (204) 632-4447
Halifax (902) 469-9476

Tektronix Canada Inc.
P.O. Box 6500 Barrie,
Ontario. L4M 4V3
(705) 737-2700

Tektronix
COMMITTED TO EXCELLENCE

Circle No. 29 on Reader Service Card