

# Electronics Today

\$3.75  
MM70924

August 1986

Canada's Magazine for Electronics & Computing Enthusiasts

## Home Computer Control


Remote control lights, motors and coffee

### Digital Frequency Doubler


Two cycles for the price of one

### Radio Shadows

Clandestine shortwaves

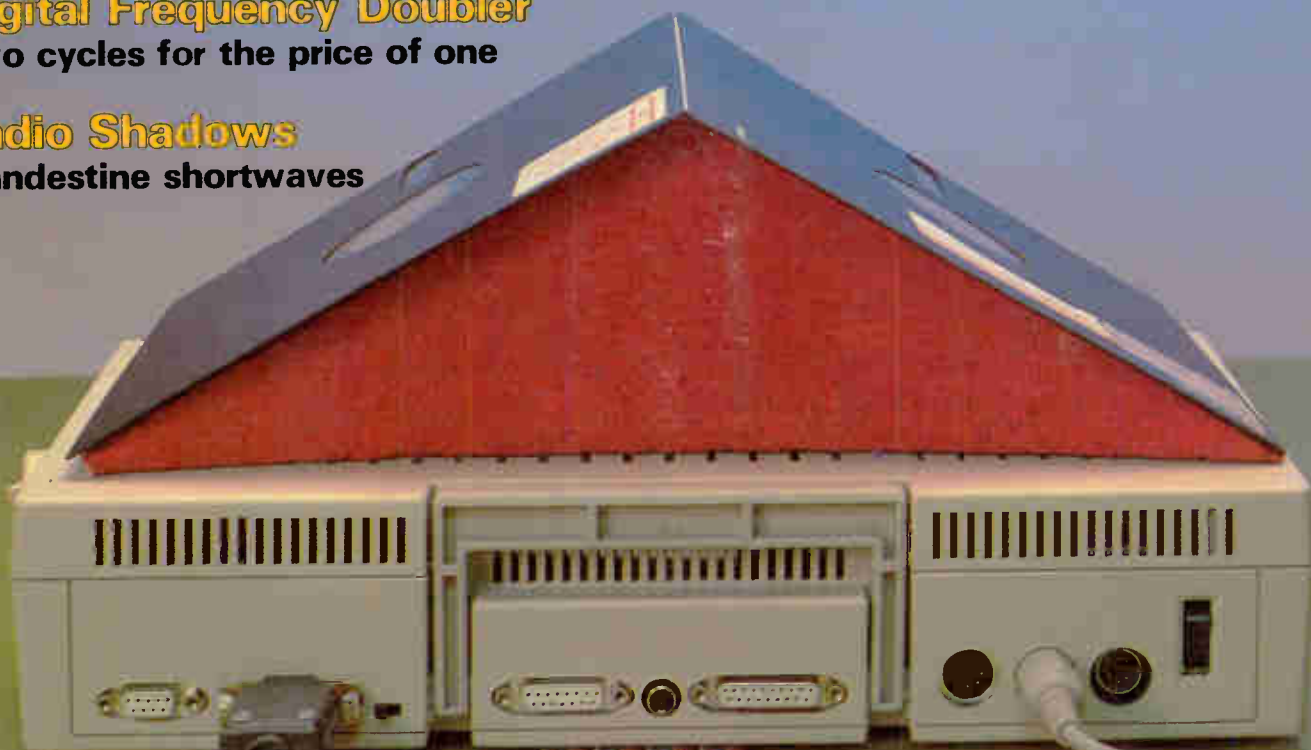


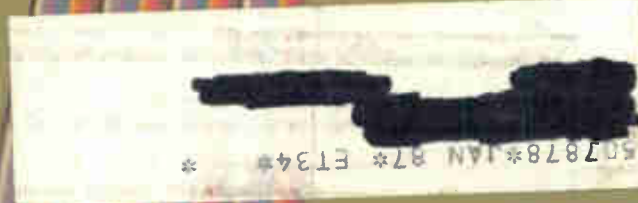**Audio Signal Tracer**  
Troubleshoot with sound


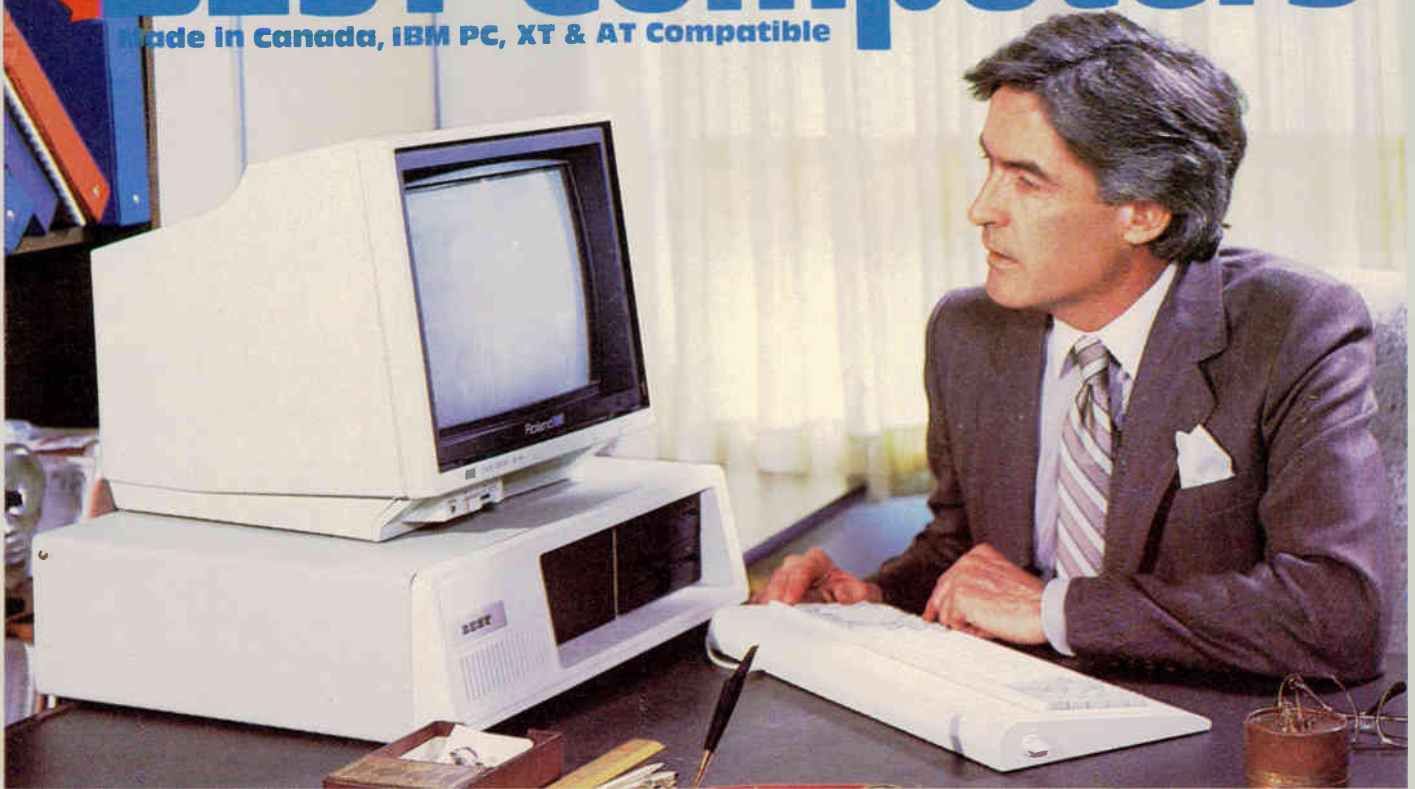
# BEST Computers

Made in Canada, IBM PC, XT & AT Compatible



Monitor not included. IBM, IBM PC, IBM XT and IBM AT are registered trademarks of IBM Canada Ltd.

## Features common to BEST MK II, MK III & MK IV

- Superb IBM PC & XT Compatibility
- Canadian Made
- 256K RAM Standard minimum (uses 41256K RAM chips)
- Expandable on board to 640K RAM
- Parallel Port (for printer)
- Serial Port (for communications)
- Real Time Clock/Calendar (with Battery Backup)
- Presocketed for optional co-processor — such as 8087 Math Processor
- IBM Compatible Keyboard
- Reset Switch
- Phoenix BIOS as used in many major brand IBM compatible systems.
- 150 Watt Power Supply which will handle a Hard Drive without upgrade.
- 7 Slots
- Flip top case
- 2 Slimline DS,DD 5 1/4", 360K Disk Drives
- Colour Video (RGB & Composite) Board or Hi-Res Monochrome Card (customer choice)
- Disk Controller Board

### Warranty

We have such confidence in the time tested reliability of the BEST that we offer a ten (10) month warranty which is way above the industry standard. On-site service plan available at extra cost Nation-wide through 3M of Canada Ltd.

### BEST MK II. Regular \$1695. This Month:

Two 350K DS,DD disk drives, Serial and Parallel Ports, Real Time Clock, Phoenix BIOS, uses 8088 processor — full specifications given above.

# \$1595<sup>00</sup>

TEN MONTHS WARRANTY

#### Other Configurations:

With 640K RAM ..... \$1695  
 With 10 Meg Hard Drive/1 Floppy/256K ... \$2495  
 With 10 Meg Hard Drive/1 Floppy/640K ... \$2595  
 With 20 Meg Hard Drive/1 Floppy/256K ... \$2795  
 With 20 Meg Hard Drive/1 Floppy/640K ... \$2895

4.77/8MHz  
DUAL  
SPEED

### The FAST BEST MK III

As BEST MK II plus speed selectable: 4.77 and 8MHz (most software will run on the higher speed), uses 8088-2 processor.

# \$1895<sup>00</sup>

TEN MONTHS WARRANTY

#### Other Configurations:

With 640K RAM ..... \$1995  
 With 10 Meg Hard Drive/1 Floppy/256K ... \$2795  
 With 10 Meg Hard Drive/1 Floppy/640K ... \$2895  
 With 20 Meg Hard Drive/1 Floppy/256K ... \$2895  
 With 20 Meg Hard Drive/1 Floppy/640K ... \$2995

SPECIAL

### SUPER-FAST BEST MK IV

As BEST MK III plus TRUE 16-Bit machine, 8086-2 processor, IBM compatible 8-Bit I/O channel bus, even faster than MK III due to 16-Bit architecture. With 256K standard.

REGULAR \$2400  

# \$2095<sup>00</sup>

TEN MONTHS WARRANTY

#### Other Configurations:

With 640K RAM ..... \$2195  
 With 20 Meg Hard Drive/1 Floppy/640K ... \$3195  
 The BEST Mk IV Main board processes data approx. 2.1 times faster than the IBM PC/XT or BEST Mk II.

IBM  
AT  
Compatible

### AVT-286

Superb IBM AT compatibility, 640K RAM, Two 5.25 in disk drives (one high density 1.2 Megabyte, one standard 360K), serial and parallel ports high quality keyboard, keyboard lock and status monitor.

# \$3495<sup>00</sup>

TEN MONTHS WARRANTY

With 20 Megabyte fast stepping Hard Disk and Controller:

# \$4950<sup>00</sup>

40 Megabyte systems also available at reasonable prices.

# Exceltronix

319 College Street, Toronto, Ont. M5T 1S2

(416) 921-8941. Order line only 1-800-268-3798

Ottawa, 217 Bank Street (613) 230-9000

Visa, Mastercard and American Express accepted



## Spectacular Gang EPROM Programmer & Emulator



Totally self-contained (has its own display, entry keypad and power supply).

Based on the Z-8 microprocessor.

Can program up to 8 EPROM simultaneously (anywhere from one to 8 EPROMs at the same time with the information in its own memory or master EPROM).

The Gang Programmer can handle a wide selection of EPROMs: 2716, 2732, 2732A, P2732A, 2532, 2764, 27128, 27128A and optionally upgradeable to handle 27256, 27512, 2758 and 2724.

Complete package with EPROM Emulator, 8 ZIF sockets, Gang Programmer with 16Kx8 of RAM and RS232. **\$995.00**

Gang EPROM Programmer with 8 ZIF sockets, 16Kx8 RAM and RS232, without Emulator. **\$695.00**

EMPROM Programmer with only one ZIF socket, 16Kx8 RAM and RS232, without Emulator. Able to do all the functions describe but can handle only one EPROM at a time. **\$499.00**

## Zenith Monitors

### NEW

#### ZVM1220A

12in. diagonal screen - non-glare amber display • composite input • 25 lines x 40/80 characters

**\$135.00**

### NEW

#### ZVM1230A

12in. diagonal screen • non-glare green display • composite input • 25 lines x 40/80 characters

**\$135.00**

**NEW ZVM 1240** • 12" diagonal screen • glare amber display • PC monochrome input (TTL) • 25 lines x 80 characters • 720 x 350 pixels • IBM PC & compatibles

**\$229.00**

## EPROM PROGRAMMER (IBM COMPATIBLE)

### MAIN EPROM PROGRAMMER CARD (WITH SOFTWARE)

With 2 standard EPROM sockets **\$ 99.00**

### EPROM PROGRAMMER WITH ZIF SOCKETS (WITH SOFTWARE)

With one 24-pin ZIF socket and one 28-pin ZIF socket with provision for serial port **\$139.00**


### EXTERNAL CARD

Ready to plug into the main EPROM Card (includes one 24-pin and 28-pin ZIF socket and cable). Saves you from opening the computer each time you want to program your EPROMS **\$ 69.00**

### SERIAL OPTION

For your main EPROM programmer. Provides you with a second RS232 serial port **\$ 49.00**

## NEW PC KEYBOARD

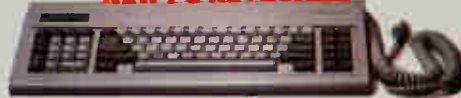

Maxiswitch AT/XT keyboard **\$129.00**

## Colour Monitor

TVM Model MD-3A 14 inch  
• Multi-Display Amber/Green/Full Colour  
• Compatible with PC/XT/AT using RGBI TTL level  
• 640x400 interlace  
• One Year Warranty  
**Only \$599.00**

• Epson Compatible • Supports both IBM and Apple systems • Centronics Parallel Interface • Both Draft and Near Letter Quality (NLQ) modes

### SC1200

• 120 cps draft quality  
• 24 cps NLQ  
• NLQ available in all print sizes  
• 11 inch carriage  
• Pin and friction feeds  
• One Year Warranty

**\$329.00**

### SC1500 \$499.00

• 180 cps draft quality  
• 36 cps NLQ  
• 3k Buffer

### SC5500 \$699.00

• 15 inch carriage  
• 3K Buffer

## MEMORY & PARTS

Untouchable Prices!  
Guaranteed Prime Stock  
Call for large quantities prices.

### Dynamic RAMs

4116 1x16k (150ns)	\$ 0.75
4164 1x64k (150ns)	\$ 2.49
4164's (150ns). Set of 9	\$21.95
41256 1x256k (150ns)	\$ 5.99
41256 (150ns). Set of 9	\$49.00

### Static RAM

2114L 4x1k 200ns	\$ 2.25
6514 4x1k CMOS 450ns	\$ 1.20
6116 8x2k 150ns	\$ 4.95
2016 8x2k 150ns	\$ 3.99
6264 8x8k 150ns	\$ 7.95

### EPROMS

2716 300ns 8x2k	\$ 6.50
2732A 250ns 8x4k	\$ 6.99
2764A 300ns 8x8k	\$ 5.99
27128 350ns 8x16k	\$ 6.95

Commonly used parts for your IBM compatible (8088) systems and peripherals.

Only prime quality parts sold.

Quantity Discounts Available.

8088 CPU	\$10.99
8087 Math Processor	\$219.00
8237A-5 Prog. DMA Cntrl.	\$8.90
8250 Serial Port	\$12.99
8253A-5 Prog. Interval timer	\$5.89

8255A-5 P.I.A.	\$4.89
8259A Prog. Interrupt Cntrl.	\$4.95
8284A ADC clock gen & driver	\$5.95
8288 Bus Controller	\$8.95
8272 Floppy Disk Controller	\$8.95
NEC 765 Floppy Disk Controller (equivalent to 8272)	\$8.95
8086 CPU	\$13.50
Set of 8088, 8255A-5, 8237A-5, 8288, 8284, 8253A-5 and 8259A	\$43.95
100ns delay line	\$4.95
7ns delay line	\$12.45
62 pin edge con (high quality)	\$1.79
5 pin Din conn	\$ .99
Power conn	\$1.25
Dip switch 8 pos	\$1.75
4.7k x 6 sip	\$ .39
4.7k x 8 pin sip	\$ .44
8.2k or 10k 16 pin Resistor	\$ .99
33ohm x 8 network	\$ .99
Small speaker	\$1.99
Trimcap	\$ .99
34 pin card edge con.	\$5.85
74LS322	\$5.49
74LS629	\$3.30
74LS670	\$1.70
74LS280	\$3.19
74LS125	\$ .60
74S157	\$1.59
74LS244	\$1.20
74LS245	\$1.39
74LS273	\$1.18
75477	\$1.19

We now carry a wide selection of 80286 parts at most competitive prices.

## BEST MODEM

The BEST modem is a smart 1200/300 direct connect modem. It can either be a stand-alone unit in which case it requires a small wall adaptor, or it plugs in one of the IBM slots. When used as a stand-alone unit, the modem looks like a Hayes 1200 Smart Modem, that is, it emulates the same instruction set. When it is used in the IBM, it looks like an intelligent serial communications port which also supports a super-set of the Hayes instruction set.

The modem supports auto-dial, auto-answer, and auto-speed select directly from software control. The modem also has a speaker so that aural monitoring of the call is possible. There are also LED monitors so that the state of the modem can always be known. These LEDs are: Modem Ready, Auto-Answer enabled, Carrier Detected, Transmitting, Receiving, Data Set ready.

Software packages such as Crosstalk, PC-talk and Hayes' Smartcom II also will run with this modem.




300/1200 Baud **\$249.00**

300/1200 Baud, Stand-Alone Unit, Attractively Packaged **\$299.00**

## Call or Write for our Full Colour Catalogue

Our Spring 1986 catalogue gives full specifications on our IBM AT and XT compatibles, AVT-286, MK II, MK III and MK IV computers plus detailed specifications, with prices on our other products, made or distributed by us.

## Copial Printers

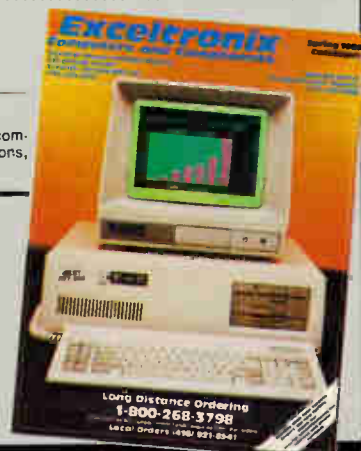

319 College Street, Toronto, Ont. M5T 1S2

(416) 921-8941. Order line only 1-800-268-3798

Ottawa, 217 Bank Street (613) 230-9000

Visa, Mastercard and American Express accepted.

# Exceltronix

# Toronto Computing Centre Inc.

Formerly Surplustronics

## 8088 Computer Systems with 90 day Warranty



**From \$995**

Includes:

- 8088 motherboard
- High quality legal Bios
- One DS,DS 360K Drive
- Power Supply with Fan
- Keyboard
- Flip-Top case
- Disk Controller
- With plenty of spare slots
- All you need for complete System is Video Board

8088 motherboard with 256K (expandable on board to 640K) Fully assembled and tested with Phoenix Bios, Flow soldered provision for 8087.

**\$339**

AT Compatible Motherboard call for Best Price.

### 256K Memory

41256 (150nS) ..... \$ 4.99  
Set of 9 ..... **\$44.00**

### 64K Memory

4164 (150nS) ..... **\$1.99**

Set of 8088, 8255A-5, 8237A-5, 8288, 8284, 8253A-5, 8259A ..... **\$45.00**

### IBM Compatible Keyboards



Taiwanese 5151 style keyboard ..... **\$137.00**  
Keytronics 5151 keyboard ..... **\$179.00**  
Taiwanese 5150 style keyboard ..... **\$ 97.00**  
Keytronics 5150 keyboard ..... **\$149.00**  
Maxiswitch Super Keyboard. Switch selectable between XT and AT compatibility ..... **\$139.00**

### IBM Peripheral Cards

Colour Video Board ..... **\$124.00**  
Monochrome Video Board ..... **\$159.00**  
Floppy Controller with RS232 ..... **\$139.00**  
Floppy Controller ..... **\$ 99.00**  
Modem 300 Baud ..... **\$179.00**  
Multifunction Floppy Board ..... **\$199.00**  
Multi I/O card with cables ..... **\$175.00**  
384 MF-FL ..... **\$289.00**  
384 MF W-OK ..... **\$155.00**  
Parallel and Game Port Card ..... **\$ 59.00**  
Cable and connector extra.

## Hard Drives Half-height, with Controller and Cables 20 Meg Seagate ..... **\$699.00**

### Disk Drives for your IBM or Compatible

JU455 Shugart/Panasonic 5.25in. Silent DS/DD, 360K ..... **\$149.00**  
JU475 Shugart/Panasonic 5.25 in. Silent AT Compatible 1.2Meg. .... **\$199.00**

### Monitors

Zenith ZVM1230 Green and ZVM1220 Amber ..... **\$135.00**  
Tatung, TTL, Hi-Res, 22MHz ..... **\$199.00**  
Tatung Colour Switchable to green or amber ..... **\$649.00**  
JIL 14in, composite RGB and NTSC ..... **\$549.00**

### Complete 6502 Board

- Assembled and fully tested (flow soldered)
- 64K, 80 x 24 video with soft-switch, floppy controller.
- System comes with blank EPROM's on board, does not come with any proprietary software or Basic ..... **\$239.00**

### Complete System

- Using 6502 board above in IBM style flip-top case, using powerful 75 watt power supply with fan, programmable serial keyboard adaptor, IBM style keyboard
- As above with one built in disk drive ..... **\$699.00**
- As above with two drives ..... **\$879.00**

## Power Supplies

Apple II + Compatible. CSA approved  
5V 5A, 12V 2.5A, -5V, 0.5A, -12V 0.5A ..... **\$69.00**  
IBM Compatible. Hydro approved  
150W 5V 15A, 12V 5.5A, -5V & -12V 0.5A ..... **\$137.00**  
As above. CSA approved  
150W 5V 15A, 12V 5.5A, -5V & -12V 0.5A ..... **\$137.00**

### Panasonic Printers — Sale

Open Frame ..... **\$29.95**  
Ideal for experimenters. No warranty.

### Printers

Copal SC550001  
180 cps, 132 column ..... **\$699.00**  
Copal SC1500T  
180 cps, 80 column ..... **\$499.00**  
Copal SC1200L  
120 cps 80 column ..... **\$329.00**

Peripheral Interface Card ..... **\$159.00**  
Includes two serial ports, parallel port, game port and provision for (but not including) real time clock.  
Clock/Calendar Option ..... **\$ 29.00**  
With battery backup.  
256K & Multifunction Board.  
Includes: Serial port, parallel port, game port, provision for optional real time clock/calendar and socketed for up to 256K RAM.  
With 64K RAM ..... **\$149.00**  
With 256K RAM ..... **\$299.00**  
512K Board. Socketed for 512K including:  
64K RAM ..... **\$149.00**

**We carry a wide selection of  
PC and AT Peripheral Cards.**

## Apple Compatible Boards Clearance Sale

Canadian Made, Flow Soldered, Super Quality. Boards fully socketed with all components except IC's and software.

80 column with hardware for softswitch ..... **\$29.00**  
Super Serial Card ..... **\$29.00**  
Parallel Card ..... **\$18.00**  
Z80/64K ..... **\$29.00**  
Deluxe Modem ..... **\$59.00**

As above but with all IC's except EPROMS and software.

80 column with hardware for softswitch ..... **\$49.00**  
Super Serial Card ..... **\$49.00**  
Parallel Card ..... **\$29.00**  
Z80/64K ..... **\$69.00**  
Deluxe Modem ..... **\$109.00**

All above boards come with schematics and component layout.

## Apple Compatible Cards

Assembled, flow soldered/cleaned and 100% tested  
16K RAM ..... **\$37.00**  
Z80A Card ..... **\$44.00**  
128K (with 128K RAM) ..... **\$79.00**  
EPROM Programmer with software ..... **\$79.00**  
(programs 2716, 2732, 2732A, 2764)  
Floppy Controller ..... **\$45.00**  
Prototyping Board ..... **\$14.95**

### Modem Bargain!


Apple Compatible plug-in Autoanswer, Autodial, Touch Tone or Pulse Dial. Excellent for use with most Bulletin Boards. 300 Baud. Final Sale as is ..... **\$39.95**

### Apple Compatible Slimline

Disk Drives 5-1/4" ..... **\$159.00**

## IBM Style Case Suitable for 8088 or Apple Boards

**\$75.00**

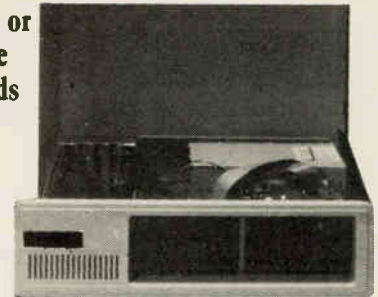

As above but no fronts and slightly scratched ..... **\$19.95**  
As above with fronts and slightly scratched ..... **\$29.95**  
These items final sale.

**AT Style Case ..... \$169.00**

Mail Orders add \$7.50 minimum for shipping & handling. Ontario residents add 7% P.S.T. Visa, Mastercard and American Express cards accepted: send card number, expiry date, name of bank and signature. Send certified cheque or money order, do not send cash. All prices on this page are final sale. No warranty, No returns, No refunds but HUGE savings. Warranties available at extra cost.

More lines  
to serve you better **(416) 960-1350**

**Toronto Computing Centre Inc. 310 College Street, Toronto, Ontario M5T 1S3**





## Our Cover

It's a house, see, made from a Laser computer with 8" floppy disks as the roof. It illustrates our Home Computer Control article, page 28, and was concocted and photographed by Bill Markwick and Ed Zapletal.

Electronics Today is Published by:  
**Moorshead Publications Ltd.**  
 (12 times a year)  
 1300 Don Mills Road,  
 Don Mills, Toronto, Ont. M3B 3M8  
 (416) 445-5600

Editor: **William Markwick**  
 Assistant Editor: **Edward Zapletal**  
 Director of Production: **Erik Blomkwist**  
 Production Manager: **Douglas Goddard**  
 Production: **Naznin Sunderji**  
**Dolph Loeb**  
 Circulation Manager: **Lisa Salvatori**  
 Advertising Account Manager: **Marlene Dempster**

**Publisher:** H.W. Moorshead; **Executive Vice-President:** V.K. Marskell; **Vice-President - Sales:** A. Wheeler; **General Manager:** S. Harrison; **Controller:** B. Shankman; **Accounts:** P. Dunphy; **Reader Services:** M. Greenan, R. Amann, R. Cree, L. Robson, N. Jones; **Advertising Services:** H. Brooks; **Advertising Telemarketing:** W. Fleet, K. Crockford.

Newsstand Distribution:  
 Master Media, Oakville, Ontario

Subscriptions:  
 \$22.95 (one year), \$37.95 (two years). Please specify if subscription is new or a renewal.

Outside Canada (US Dollars) U.S.A. add \$3.00 per year. Other countries add \$5.00 per year.

Postal Information:  
 Second Class Mail Registration No. 3955. Mailing address for subscription orders, undeliverable copies and change of address notice is:  
 Electronics Today, 1300 Don Mills Rd., Toronto, Ontario, M3B 3M8

Printed by Heritage Press Ltd., Mississauga  
 ISSN 07038984.

Moorshead Publications also publishes Computing Now!, Computers in Education, and Pets Magazine.

Circulation Independently Audited  
 by MURPHY and MURPHY  
 Chartered Accountants.

## Advertisers' Index

All-Crystal Displays	60
BCS Electronics Ltd.	34, 58, 63
Brunelle Instruments Inc.	10, 26
Budgetron Inc.	30
BV Engineering	60
Cardinal Industrial Electronics Ltd.	8
Compukits	8
Computer Parts Galore	10, 31
Daetron	39
Electronic Control Systems	40
Exceltronix	2, 3
Kaientai Electronic Merchants Ltd.	11, 37
KB Electronics	37
Lasco Montreal Inc.	11
McGraw Hill	25
Meints-Shuster	40
ORI Industries	10
Orion Electronic Supplies Inc.	10
Raitronic's Ltd.	8
Solen Inc.	33
Soltech Industries Inc.	61
Sunix Inc.	33
The Software Link Inc.	64
Toronto Computing Centre	4
Varah's Direct	7, 10

For Advertising Information  
 Call 445-5600


# Electronics Today

August 1986  
 Vol. 11 No. 8

Canada's Magazine for Electronics & Computing Enthusiasts



Computer Control page 28.

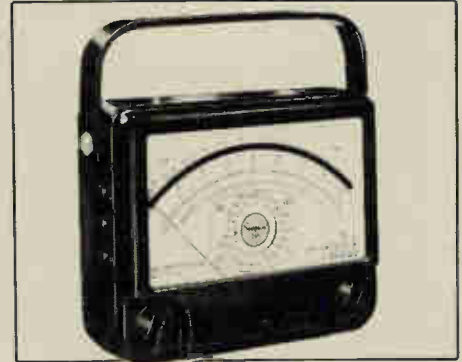

The Multimeter page 41.

## Features

Home Computer Control	28
The Multimeter	41
Radio Shadows	57

## Projects

Audio Signal Tracer	12
Versatile Power Supply	18
Digital Frequency Doubler	35
Interval Timer	44

## Product Review

Laser 128 Computer	9
--------------------	---

## Series

For Your Information	6
Designer's Notebook: Programmable Controllers	22
Beginner's Bench: Digital Basics	49

## Columns and Information

Marketplace	10	Order Form	45
Books	15	Binders	46
Circuit Ideas	38	Subscriptions	46
Product Mart	45	Software	54

# For Your Information

## The Editor's Corner

By Bill Markwick

Hello again. Welcome to a new column, an idea that just sort of happened as a result of all the little bits and pieces of musings and ramblings that I put in the For Your Information section. I decided to get them all together and give them their own space because they didn't fit too well anywhere else. It gives me a chance to comment on all sorts of irrelevant things and gives the reader the chance to ignore them all at once.

Take MS-DOS compatibles, for instance. Why are they so expensive? A famous-name two-drive unit with 256K and a monitor can cost you \$4500, and an AT work-alike may be in the neighbourhood of \$8000. For what? They aren't upgrades of the original, rather cumbersome IBM design; they aren't much faster or better.

Compare these units with what you could get for the price of an XT compatible: a good used car (or a new car at AT prices), a roomful of elegant furniture or a houseful of reasonable stuff, or five or six colour TVs. Are you into woodworking? For the price of a PC or XT, you could get yourself

a fine quality table saw, an 8-inch Swiss jointer, a bandsaw, a drill press, every portable power tool you've ever wanted, plus enough left over to buy some rare woods to get you going.

For the price of an AT or compatible you could build a concrete block garage to put it all in.

If you think I'm being unfair to the corporations, consider the IBM-compatible computers built in Canada by the smaller companies. At the moment you can get a two-drive 256K with a monitor and printer for \$1895. And yes, they do work; after all, everybody uses the same Intel-based system anyway.

I suppose it's all because people have become used to paying exorbitant prices for computers, just as they're conditioned to mufflers that fall off every two years.

Next gripe: the dreadful quality of Canadian electrical wiring equipment sold to the homeowner for new installations or rewiring. Not even the shoddiest of third-world importers use the sort of junk you're forced to buy from hardware stores and electrical sup-

pliers.

Those outlet boxes! What fool designed them? And the approved wiring methods make me wonder why every second house doesn't burn down: uninsulated ground wires, rinky-dink outlets and switches with terminals a hair's-breadth from the box, and mounting tabs that make it virtually impossible to mount the box solidly to wood or wallboard.

My 100-amp service panel accepts 24 circuits, but there isn't provision for 24 ground wires. There are no wire guides or clamps, something you need because the neutral connections are to a common buss at the bottom. What a mess. Why have a service panel at all? Borrow the idea of the ring main, where a high-current cable loops through the house and each outlet box has its own fuse or breaker. Much more sensible.

I'll bet that if we really knew the exact cause of electrical fires, those twist-on wire nuts would be involved to a great extent. Would you accept a computer or stereo that had wire nuts inside? What ever happened to terminal blocks?

The authorities insist on a system with a safety ground, and rightly so. Yet you can still buy any number of 2-wire extension cords, and now they come with one pin larger than the other for polarizing. What a mish mash. We seem to be at the mercy of an arbitrary system that changes at random. And why are some kitchen appliances grounded while others are not? Toasters and kettles are not double-insulated, but rarely have a ground pin.

I can hear the electrical distributors screaming already: the equipment is very inexpensive and does the job if installed properly. And so it does. But installing it properly would try the patience of a saint, and there are no options anywhere at any price. If you imported a sensible system such as the British type, or designed one yourself using the best of the components available to electronics people, you couldn't get it approved by the authorities because it isn't in the books.

Those doing domestic power wiring should have some higher-quality equipment available to them as an alternative.

## Mini-review: The Portasol Butane Soldering Iron



The incredibly talented hands in the photograph belong to the editor, who has just soldered three 16-gauge wires together using the Portasol Portable Soldering Iron. It's completely cordless, being powered by butane gas, the same stuff you use for lighters. In the cap (foreground) is a flint wheel lighter which ignites the gas after you thumb the on-off valve forward; the flame goes out in seconds, leaving a catalytic element to heat the tip flamelessly.

The black band at the rear of the unit is a flow valve which will adjust the tip heat over a range equivalent to 10-60 watts. This means an adjustment range suitable for any soldering from delicate PCBs to big hairy power wires.

The unit started instantly, every time, and even better is the fact that the catalytic element will restart if it's still hot; this means that you can shut off the gas flow between solder joints and it will come

on again without the flint. The operating time is up to one hour, depending on how high you set the flow. The lowest settings seemed fine for most electronic work. The supplied tip is a general-purpose nickel type; other sizes are available.

Besides the convenience of complete portability, other advantages include the elimination of leakage currents and magnetic effects; no grounding is necessary. Minor drawbacks: the list price is a wee

bit high at \$49.95, and the gas flow is a bit erratic at low settings, particularly when the fuel is getting low.

This unit is the best thing to happen to soldering since they invented flux. They'll have a hard time getting the review model away from us. From Varah's Direct, with locations in Vancouver, Edmonton, Calgary, Winnipeg and Nepean, or contact them at 504 Iroquois Shore Rd., Oakville, Ontario L6H 3K4, (416) 842-8833.

Circle No. 69 on Reader Service Card

The Stag ZL30A is dedicated logic programmer combining operational simplicity with speed. It supports an extensive range of programmable logic devices, including PAL(TM), IFL, EPLD and GAL(TM). Built-in ZIF sockets are provided for use with 20, 24, and 28-pin devices and the Stag ZL30A will accept optional adaptor modules for devices in alternative packaging styles. This unique device is the first of its kind to cater not only to 40-pin DIL devices, but also the latest SO, WSO, PLCC and LCC packages for surface mounting.

Linda Belli, Duncan Instruments Ltd., 121 Milvan Dr., Toronto, Ontario M9L 1Z8. (416) 742-4448 Telex 065-27271.

Circle No. 61 on Reader Service Card

#### Copyright

All material is subject to worldwide copyright protection. All PCB patterns are copyright and no company can sell boards to our design without our permission.

#### Liability

While every effort has been made to ensure that all constructional projects referred to in this magazine will operate as indicated efficiently and properly and that all necessary components are available, no responsibility whatsoever is accepted in respect of the failure for any reason at all of the project to operate efficiently or at all whether due to any fault in the design or otherwise and no responsibility is accepted for the failure to obtain component parts in respect of any such project. Further no responsibility is accepted in respect of any injury or damage caused by any fault in design of any such project as aforesaid.

#### Editorial Queries

Written queries can only be answered when accompanied by a self-addressed, stamped envelope. These must relate to recent articles and not involve the staff in any research. Mark such letter Electronics Today Query. We cannot answer telephone queries.

#### Binders

Binders made especially for Electronics Today (ETI) are available for \$9.75 including postage and handling. Ontario residents please add provincial sales tax.

#### Back Issues and Photocopies

Previous issues of Electronics Today Canada are available direct from our office for \$4.00 each; please specify by month, not by feature you require. See order card for issue available.

We can supply photocopies of any article published in Electronics Today Canada; the charge is \$2.00 per article, regardless of length. Please specify both issue and article.

#### Component Notation and Units

We normally specify components using an international standard. Many readers will be unfamiliar with this but it's simple, less likely to lead to error and will be widely used everywhere sooner or later. Electronics Today has opted for sooner!

Firstly decimal points are dropped and substituted with the multiplier: thus 4.7uF is written 4u7. Capacitors also use the multiplier nano (one nanofarad is 1000pF). Thus 0.1 uF is 100nF, 5600pF is 5n6. Other examples are 5.6pF = 5p6 and 0.5pF = 0p5.

Resistors are treated similarly: 1.8Mohms is 1M8, 56kohms is the same, 4.7kohms is 4k7, 100ohms is 100R and 5.6ohms is 5R6.

#### PCB Suppliers

ETI magazine does NOT supply PCBs or kits but we do issue manufacturing permits for companies to manufacture boards and kits to our designs. Contact the following companies when ordering boards.

Please note we do not keep track of what is available from who so please don't contact us for information PCBs and kits. Similarly do not ask PCB suppliers for help with projects. K.S.K. Associates, P.O. Box 266, Milton, Ont. L9T 4N9.

B—C—D Electronics, P.O. Box 6326, Stn. F., Hamilton, Ont. L9C 6L9.

Wentworth Electronics, R.R. No. 1 Waterdown, Ont. L0R 2H0.

Danocinths Inc., P.O. Box 261, Westland MI 48185 USA.

Arkon Electronics Ltd., 409 Queen Street W., Toronto, Ont., M5V 2A5.

Spectrum Electronics, 14 Knightswood Crescent, Brantford, Ontario N3R 7E6.

# Varah's direct™

introduces

## PORTASOL

The cordless, butane soldering iron!

- pocket size
- static free
- lightweight
- re-fill 15 seconds
- adjustable heat
- replaceable tips
- 400° C tip temp.
- 60 watt equivalence

PORTASOL extends the limits of soldering. Armed with PORTASOL — unhindered by a power cord or the need for an electrical outlet — professionals or hobbyists can make short work of many soldering tasks.

The PORTASOL runs off ordinary butane which is available at any corner store at a cost of less than 5¢ per refill. Butane is held in a reservoir inside the iron and a patented catalytic converter provides the heating at the tip. There's no flame during soldering. It's that simple. It's that safe!

Under normal usage, each charge of butane lasts up to 1 hour. Refilling takes seconds and is identical to filling a cigarette lighter. That's how convenient the PORTASOL is.


PORTASOL comes complete with a protective cap and a handy clip so it can be carried like a pen in your pocket. The cap includes a flint for igniting the iron.

PORTASOL — This useful tool is now offered to you by Varah's Direct. It comes with a full 1 year guarantee. ORDER YOURS TODAY!

**PORTASOL (Stk # 68570) \$49.95**  
**Replacement tip (Stk # 68572) \$14.95**



Actual Size

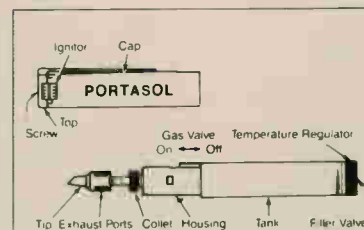

# Varah's direct

**OUTLETS:**  
Vancouver  
Edmonton  
Calgary  
Winnipeg  
Oakville  
Nepean

**WRITE:**  
Varah's Direct: 504  
Iroquois Shore Rd.  
Oakville, Ontario  
L6H 3K4  
(please include  
your postal code)

**CIRCLE:**  
Reader Service  
No. for this ad  
**OR CALL:**  
(416) 842-8833  
Mon. to Fri.  
8:00-6:00 E.S.T.



Member, Canadian  
Direct Marketing  
Association





# CARDINAL

INDUSTRIAL ELECTRONICS LTD.

Serving Industry, OEM and Educational needs since 1967

We stock 263 product lines, such as:

Siemens AMP Hammond Sola  
Amphenol Molex Microswitch  
SGS semiconductor Fluke  
Belden Rockwell Patlon Dynatem  
POTter & Brumfield Ferranti Edukit  
B & K-Precision Hitachi Vector  
Schroff Alpha Wire.

and many others. CARDINAL's new catalogue available - \$10.00. Visa/Master Card or Purchase Order. 1280 pages. Order from **CARDINAL CATALOGUE**, Box 12000, Edmonton, Alberta, T5J 2P4 (403) 483-6266. Branches in Calgary (403) 259-6817, Saskatoon (306) 934-3443.

Circle No. 5 on Reader Service Card



# DataPerfect

A Division of RAITRONICS LTD.

## AT STARTER KIT

512K MEMORY (1MB)  
8 SLOTS  
1.2 Mb FLOPPY / HO CARD  
COLOR GRAPHIC CARD  
KEYBOARD  
BATTERY BACKED CLOCK

**\$2895.00**

## XT STARTER KIT

256K MEMORY (640 M/B)  
8 SLOTS  
1 DRIVE (360K)  
COLOR GRAPHIC CARD  
KEYBOARD

**\$795.00**

## FULLY HAYES COMPATIBLE

300/1200 SMART MODEM  
AUTO DIAL/AUTO ANSWER  
AUTO SPEED SELECTION  
SPEAKER/VOLUME CONTROL  
RS232 CABLE

**\$199.00**



1 year warranty

## XT™ PORTABLE CASE

PRICE INCLUDES  
CASE, FULL SIZE  
KEYBOARD,  
9" MONITOR,  
135 WATT P.S.

**\$650.00**



## APPLE IIe COMPATIBLE

128K MEMORY

**\$439.00**

TERMS: M/C, VISA,  
M.O., C.O.D.

Add 5% Shipping  
\$2.00 Handling

207 WEST 6th AVE.  
Vancouver, B.C. CANADA V5Y 1K7

**604-875-0207**

Circle No. 6 on Reader Service Card



DAVE WONG Pres

# ASSEMBLE YOUR OWN PC & SAVE \$\$\$

## COMPLETE AT SYSTEM:

Dual Speed (6/8MHz), 80286 CPU (80287 Optional), 6 16-bit & 2 8-bit I/O Slots, RAM Expandable to 1M, Clock, Phoenix BIOS, CGA, 1.2Mb Disk Drive, Hard Disk Controller, Printer & Serial Ports, 192-watt Power Supply, 5160 Keyboard, Case, Assembled, Tested, 1-Year Warranty  
..... **\$2899.00**

## AT COMPONENTS:

**AT MOTHERBOARDS**  
Dual Speed (6/8MHz), 80286 CPU (80287 Optional), 6 16-bit & 2 8-bit Slots, Expandable to 1Mb, Clock, Phoenix BIOS, OK ..... **\$1299.00**

**FLOPPY-HARD DISK CONTROLLER**  
IBM AT-Compatible, 360K/1.2M Floppy & Hard Disks ..... **\$599.00**

**2.5Mb MULTI-FUNCTION CARD**  
2.5Mb RAM Expansion, Printer, 2 Serial Ports, OK **\$329.00**

**PARALLEL & SERIAL PORTS CARDS** ..... **\$125.00**

**KEYBOARD:** 5160-type AT Keyboard ..... **\$125.00**  
POWER SUPPLY: 192-watt Side Switch ..... **\$239.00**  
CASE: IBM AT-style Sliding Case ..... **\$139.00**

**DRIVES:**  
1.2Mb 1/2-Height Floppy Disk Drive ..... **\$269.00**  
CDC WREN HARD DISK, Voice Coil, Park/Lock Head, Ultra Fast Access (20ms), 20Mb Capacity ..... **\$1199.00**  
30Mb Capacity ..... **\$1499.00**  
30Mb Capacity ..... **\$1899.00**  
80Mb Capacity ..... **\$2599.00**



## XT SYSTEMS:

**COMPLETE STARTER KIT:**  
4.77MHz, 8088 MPU (8087 Optional), Phoenix BIOS, Hardware Reset, 8 IBM-comp. I/O Slots, 256K RAM Expandable to 640K, Panasonic or Mitsubishi Disk Drive, Printer Port, Color Graphics Adapter, 135-watt CSA Approved Power Supply, 5150 Keyboard, Flip-top Steel Case ..... **\$899.00**

**COMPLETE PRO XT KIT:**  
4.77MHz, 8088 MPU (8087 Optional), Phoenix BIOS, Hardware Reset, 8 Expansion Slots, 640K RAM, Color Graphics Adapter, 2 Panasonic or Mitsubishi Disk Drives, Printer, Serial & Joystick Ports, Clock/Calendar, 135-watt CSA Approved Power Supply, 5150 Keyboard, Flip-top Case ..... **\$1199.00**

**COMPLETE TURBO XT KIT:**  
Dual Speed (4.77/8MHz), 8088-2 MPU (8087 Optional), 640K RAM, Phoenix BIOS, Hardware Reset, 8 Slots, Printer, Serial & Joystick Ports, Clock, Color Graphics Adapter, 2 Panasonic or Mitsubishi Disk Drives, 135-watt CSA Approved Power Supply, 5150 Keyboard, Flip-top Case ..... **\$1249.00**

## XT COMPONENTS

**MOTHERBOARDS:**  
XT: 640K Board, Phoenix BIOS, Hardware Reset, OK ..... **\$259.00**  
TURBO: 4.77/8MHz, Phoenix BIOS, Reset, OK ..... **\$325.00**

**VIDEO ADAPTERS:**  
MONOCHROME GRAPHICS ADAPTER  
Hercules-Comp., Printer Port, Runs Lotus ..... **\$139.00**  
COLOR GRAPHICS ADAPTER  
IBM-Comp., Composite (Mono & Colour) & RGB Outputs ..... **\$115.00**  
DUAL MODE GRAPHICS ADAPTER  
Genoa Spectrum-Comp., Monochrome/Colour Graphics ..... **\$329.00**  
ENHANCED GRAPHICS ADAPTER  
100% EGA-Compatible, 256K Video RAM, Flicker-free ..... **\$549.00**

**EXPANSION CARDS:**  
DISK DRIVE CONTROLLER w/Cable ..... **\$ 59.00**  
384K MULTI-FUNCTION CARD - OK 384k RAM Expansion, Printer, Serial & Game Ports, Clock, Ram Disk & Print Spooler Software, OK ..... **\$159.00**  
MULTI-FUNCTION DISK I/O Disk Controller, Printer, Serial (2nd Optional) & Game Ports, Clock, Ramdisk & Printer Spooler ..... **\$ 39.00**  
PARALLEL PRINTER ADAPTER ..... **\$ 55.00**  
SERIAL COMMUNICATION ADAPTER ..... **\$ 99.00**  
5151 Keyboard w/Cursor Pad ..... **\$139.00**  
5151 Keyboard ..... **\$149.00**  
POWER SUPPLY: CSA Approved 135-watt ..... **\$ 59.00**  
CASES: Flip-top Steel Case, Side Switch

**DRIVES:**  
Panasonic or Mitsubishi 360K, DS/DD 5 1/4" Disk Drive ..... **\$189.00**  
20Mb SEAGATE Hard Disk w/WDC Controller ..... **\$799.00**  
MODEM: External 1200 Baud, Hayes-Compatible ..... **\$299.00**

**MONITORS:**  
12" DUAL MODE SMART MONOCHROME TTL/RGB compatible ..... **\$185.00**  
14" RGB MONITOR, 0.39 Dot Pitch, Green/Amber Modes ..... **\$529.00**

## GUARANTEE:

- Latest Technology
- Min. 48hr. Burn-in
- Tested Before Shipping
- Prompt Service
- Warranty: 90 Days Parts/Kits  
1-Year Systems

**ORDER NOW TOLL FREE: 1-800-663-KITS**

**BUY WHERE DEALERS & SMART BUYERS BUY**

Circle No. 7 on Reader Service Card

## CompuKits

4320 Fraser St.  
VANCOUVER B.C. V5V 4G3  
(604) 879-9288





# Laser 128 Computer

**Put the features of a IIe into a IIc case, add some ports and stir.**

By Bill Markwick



THE LASER 128 consists of the functional equivalent of an Apple IIe inside a case that's obviously been designed by taking a IIc package and adding a numeric keypad. The single included disk drive is a slot on the right hand side. The power supply lives in a small external box; it has adequate output to power the computer plus options such as another added drive.

The Laser is certainly comprehensive; aside from the 128K of memory, BASIC in ROM, and IIe cursor and function keys, it has a back panel that will be the envy of every Apple owner because it holds a mouse port, a parallel printer output, RGB/composite video outputs, an external drive connector, a port for an external modem, a serial printer port and one expansion slot. To add ports with an Apple II or compatible, you had to move half your desk, pry it open, and add a printed circuit card that had to have a suitable cable connector on it. With the Laser it's all there on the back for you.

Hackers may object to the single expansion slot, but after a II was outfitted with what you'd consider standard equipment, it usually only had one slot left over. Besides, Laser makes an expansion box with two advantages: you get two external slots and your PCB doesn't hang out in space unprotected.

The tiny disk space available on the Apple system (about 140K with DOS, about 125K with CP/M) means that you'll want a second drive for sure. The optional second drive (\$207) is in a half-height plastic box, and it plugs into the back panel via its included cable, no muss, no fuss.

Other interesting features include a volume control (and earphone jack) for the internal squeaker (bless 'em!), a switch to convert the keyboard to the Dvorak format and a built-in 80-column card with a front panel switch. The volume control was worth its weight in gold, but there was no keyboard overlay mentioned for the Dvorak switch. I sup-

pose you could always scramble the keys and fool your friends, for a while anyway. The 40/80 column switch seemed a bit pointless; DOS boots in 40, CP/M boots in 80 and the switch didn't do much. You could convert DOS to 80 by typing PR3, just like on the real thing.

The ten function keys were preprogrammed with control keys, like CTRL-C, and if there was a way to reprogram them to something more useful, I couldn't find it. There were some handy functions available from the keys on either side of the space bar, though, such as being able to do a warm boot without typing PR6, or calling up the port configuration tables from ROM (a neat feature).

The computer arrived with two disks. On one of them was a DOS demonstration disk, one of those dig-these-graphics types (and the double-res graphics are very good indeed), and I suppose you could use its HELLO to copy DOS to other disks. The manual is quiet when it comes to DOS functions, probably for copyright reasons. The other disk contained a flavor of CP/M from Applied Engineering, called CP/AM. It seemed to be functionally identical to the Digital Research original, at least as far as syntax. The supplied version was a 44K type, and contained a COM file which allowed you to make a 60K type.

The CP/M was a bit problematical. While the Applied Engineering type booted every time and did what it said it would, it had a fair amount of trouble with programs which had run successfully on an Apple II compatible with a Z80 card. WordStar in particular. It refused to load via CP/AM, and insisted on having the Digital Research CP/M version loaded first. This created another problem: on powering up with 'real' CP/M, the disk would run and then stop, with no video happening. Nudging CTRL-RESET would then bring up the sign-on.

Although WordStar would then run, it refused to exit nicely, hanging the computer every time on quitting.

To be fair about the CP/M problem: some of our programs were patched to run properly on our compatibles, so there's a gray area when it comes to saying anything definite about the Laser's Z80 capabilities. Most of our small CP/M disk utilities ran without a glitch. Still, greenhorn users will be utterly baffled, especially since the included documentation for CP/M just ain't there at all, except for a short 'readme' file.

The manual is written in a silly have-a-nice-day style that gets in the way of information, what little there is. Typical example, reproduced exactly: 'When you trun on your computer, for the first split second the microprocessor is completely confused!' Uh-huh. I trunned it on and it sure got the Z80 confused.

To sum up: the Laser is loaded, jam-packed with features and ports. You won't have to go on a hunt for auxiliary printed circuit cards and connectors. It's probably the most comprehensive Apple-compatible going.

On the down side is the fact that it costs \$789.95. With two drives (essential), the price is now \$1000. Since the sun has set on Apple DOS and CP/M, you'll have to be a real fan to invest in a compatible these days: IBM PC compatibles are turning up at the same price, with 256K and a vastly better disk operating system. Users will also have to know their stuff, or else be willing to spend some time on the phone finding out matters of syntax and so forth.

*The Laser 128 is available from:  
ABAC Electronic Enterprises,  
PO Box 662,  
Thunder Bay, Ontario P7C 4W6,  
(807) 623-6111*

# MARKET PLACE

## IBM COMPATIBLE COMPUTERS

**\* BEST PRICES \***

**ORION 5XT 640K TURBO MOTHER BOARD \$849.00**  
100% IBM Compatible


### IBM Compatible Boards

- 1F02 384K Multifunction (S/P/C/G)OK \$175.00
- 1F03 384K RAM Ver 11 OK \$ 89.00
- 1F03 512K RAM Ver 11 OK \$ 99.95
- 1F05 Color Graphic \$119.00
- 1F06 Monochrome \$119.00
- 1F07 Mono-Graphic with printer port \$175.00
- 1F09 10 + 11 + (S/P/C/G) \$115.00
- 1F11 Parallel Printer (Cable extra) \$ 35.95
- 1F12 Serial — RS232C \$ 49.95
- 1F13 Game \$ 29.95
- 1F14 Floppy Drive Controller + Cable \$ 85.95
- 360K DS/DD Disk Drive \$149.00
- XT Compatible Mother Board OK \$225.95

### Hard Disk Drives

	Prices
10M External w/power supply	\$799.00
10M Internal	\$795.00
20M External	\$799.00
20M Internal	\$1099.00
DISKETTES (Box of 10) LIFETIME WARRANTY	
Orion SS/DD	\$ 14.95
7mm DS/DD	\$ 17.50
Outboard S/DD	\$ 15.95
Datamax DS/DD	\$ 19.95
Outboard S/DD	\$ 15.95
(Box of 10)	\$ 12.50
Non-Name DS/DD	\$ 12.50

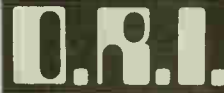**ORION ELECTRONIC SUPPLIES INC.**  
40 Lancaster St. W., Kitchener (519) 576-9902



**WE ARE NEW**

**WE HAVE**

- Integrated Circuits
- Micro-processors
- Test Equipment
- Capacitors
- Connectors
- Resistors
- Boards
- Kits

**OUR GOAL SERVICE LOW PRICES**

We want to work with you - so let us know what you want - if we don't have it, we'll look for it.

**O.R.I. INDUSTRIES**

1889 Silverberry Crescent  
Mississauga, Ontario  
L5J 1C8 (416) 822-3590

**Return this coupon for FREE Catalogue and Discount coupon towards first Mail Order.**

## Triplett Model 60 VOM



- 28 Ranges - to 1000 Volts DC or AC; 5 Ohm-meter Ranges to 10 Meg Ohms.
- Diode overload protection and 3 F arrangement.
- 3 year warranty.

Special \$219.00  
Regular \$269.00

Add \$3.00 transaction PST extra.

• Quality + Price + Service = **BRUNELLE**



**Brunelle Instruments Inc.**

73-6th Range South  
Saint Elie D'orford, Quebec, J0B 2S0  
Tel: 1-819-569-1408 Telex: 05-836266


## WAREHOUSE SALE

With this coupon

**\$2.00 worth of Free Parts**

AT OUR HUGE SURPLUS WAREHOUSE  
Monday-Saturday 10:00 am — 5:00 pm at  
20 Beverly Street, Toronto

416-977-0520

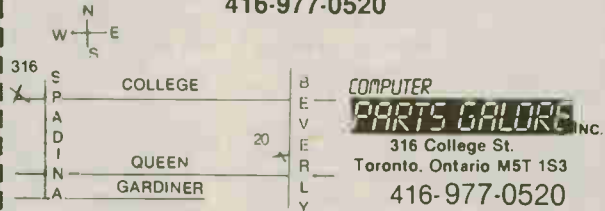

WE HAVE THOUSANDS OF ITEMS FOR SALE. ALL KINDS, OF POWER SUPPLIES AND CONNECTORS, ETC ETC. ALL THE SAMPLES WE HAVE LEFT OVER FROM THE APPLE CLONE ERA. ALL THE DEFECTIVE GOODS THAT WE DO NOT WANT TO REPAIR ALL AT LOW LOW PRICES FOR THE HOBBYIST.

## GET YOURS FREE WITH THIS COUPON!

Send us this coupon today and receive your 1986 Varah's Direct Reference Guide & Mail Order Catalogue at no charge!

Not just a price listing, this is a fully referenced book which supplies pin-outs, electrical specs, and dimensions on over 2500 items from our multi-million dollar industrial inventory.

Varah's Direct has everything to meet your electronic needs. For the best in electronic components. WRITE, CIRCLE or CALL (see below)!

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

POSTAL CODE \_\_\_\_\_ PHONE \_\_\_\_\_



• DON'T MISS OUR AD IN EACH E.T. ISSUE - SEE PAGE 7 FOR DETAILS!

WRITE: Varah's Direct  
504 Iroquois Shore Rd.  
Oakville, Ont., L6H 3K4.

CIRCLE: The Reader  
Service Number for  
page 7.

CALL: (416) 842-8833  
Monday to Friday,  
8:00 - 6:00, E.S.T.

LOCATIONS: Vancouver,  
Edmonton, Calgary,  
Winnipeg, Oakville, Nepean.



# MARKET PLACE

**WHY PAY MORE?... to support the middle man**  
**WHY NOT PAY LESS?... buy direct from the importer... WE CAN OFFER...**

## System I

- Choice of Colour or Monochrome Display Card
- 640K
- 8088 Main Board with 8 Slots
- 512K Ram on Board
- 360K Half Height Floppy Disc Drive with Controller Card
- 135 Watt Power Supply with Side Switch
- Cabinet that can House 4 Half Drives

for only **\$899.00**

## System II

- As System I but with...
- Full 640K Ram on Board
- Two 360K Half Height Floppy Disc Drives
- System Clock with Battery Back Up
- Two RS-232 Serial Ports
- Parallel Printer Port
- Game Port

for only **\$1199.00**

- 90 Day Manufacturer's Warranty
- 300 Day Warranty available.

We have many configurations, parts and peripherals to offer you.

Why not send for our free brochure..... **We promise to look after you.**

Mail Order Certified cheques or money order only — No cash please. Add \$15.00 for shipping and handling. Quebec residents please add 9% PST. FST included in prices. All prices are subject to change without notice.



**LASCO Montreal Inc.** established importers of electronics since 1976  
 785 Plymouth, T.M.R., Quebec, Canada. H4P 1B3 (514) 341-4222

## Computing Now! Microcomputer Directory

Finding the hardware or software one wants for one's microcomputer applications is very often an exercise in finding out what exists. Following this, one must locate what one has chosen, often through a labyrinth of dealers and suppliers. Conventional magazine directories and surveys can help with all of this... somewhat... but to date a comprehensive useable directory of what's available in Canada has yet to be published.

Most directories are constructed so as to be easy to compile. This one has been designed to be easy to use. Rather than selecting arbitrary categories, the items in the directory will be classified by system and within each system, in a tree structure dividing them into subclassifications.

This will result in a large directory with a lot of duplication in it. However, it will be a reference highly valued by its readers because of its resulting ease of use. It will be the essential reference work for anyone involved in microcomputers, from single system end users to small and mid-sized businesses. For advertising information contact Denis Kelly at (416) 445-5600 immediately

Cover Date: September 1986



## K.E.M. Stepping Motors & Stepping Motor Drivers

Offered by K.E.M. Electronics for industrial robotics engineers and advanced computer hobbyists.



**Motors** (from mini size to giant)  
 Torque range . . . . . 280g.cm to 30,000 g.cm (25oz. inch to 2700oz. inch)  
 Price range . . . . . **\$18.50 to \$298.00**

**Motor drivers**  
 Full line-up. Educational model to intelligent models for industrial applications. Price range . . . . . **\$68.00 to \$545.00**

please ask for stepping motor catalog

### Special introduction K.E.M. original items for new pupils of Robotics

Stepping motor training and evaluation KIT: stepping motor, driver, demonstration software for Apple II and manuals . . . . . **\$98.00**

Robotics Training I/O "ODEN" for Apple or IBM: Stepping motor driver, sound output/input, 4ch-8bit A/D, right/thermal sensors, 3 Relays output manual data entry switches, LED indicators and I/F card . . . **\$185.00**  
 \$5.00 for shipping. Plus P.S. Tax for B.C. residents. Plus C.O.D. fee if required.

## K.E.M. Electronics Ltd.

Mail: Box 69126 Station (K), Vancouver, B.C. V5K 4W4  
 Office: 879E. Hastings St., Vancouver, B.C. Tel: (604) 251-1514

# Audio Signal Tracer

*As an inexpensive alternative to the scope, this unit makes the troubleshooting of audio circuits a little less tedious.*

*By Michael Tooley and David Whitfield*

THE AUDIO SIGNAL tracer described here is a self-contained variable gain audio amplifier which provides sufficient amplification to allow even the lowest level signals to be traced. It can be operated from any convenient DC supply in the 9V to 20V range, and it features its own monitor speaker.

## Circuit Description

The signal tracer is designed around a fixed gain integrated circuit audio amplifier: the LM380. It's an audio power amp featuring short circuit protection and internal thermal limiting. The gain of the amplifier is fixed at 34dB over a bandwidth of 100kHz, i.e. the gain never falls below 25 at any frequency up to 100kHz. The LM380 operates over a wide range of supply voltages, automatically setting the quiescent output voltage to half of the supply voltage. The input resistance of 150k minimizes the need for any input buffer stages, and an output power of up to 2.5W RMS is available into an 8 ohm load when operated with suitable heatsink and power supply.

The internal circuit for the LM380 is shown in Fig. 1. The three centre pins on either side should be connected to ground; this is intended to allow copper heatsink fins to be soldered to these pins for high power operation. The heatsinking can alternatively be provided by a suitable printed circuit layout with a minimum of 40 square centimeters of 2 ounce copper foil area connected to these pins.

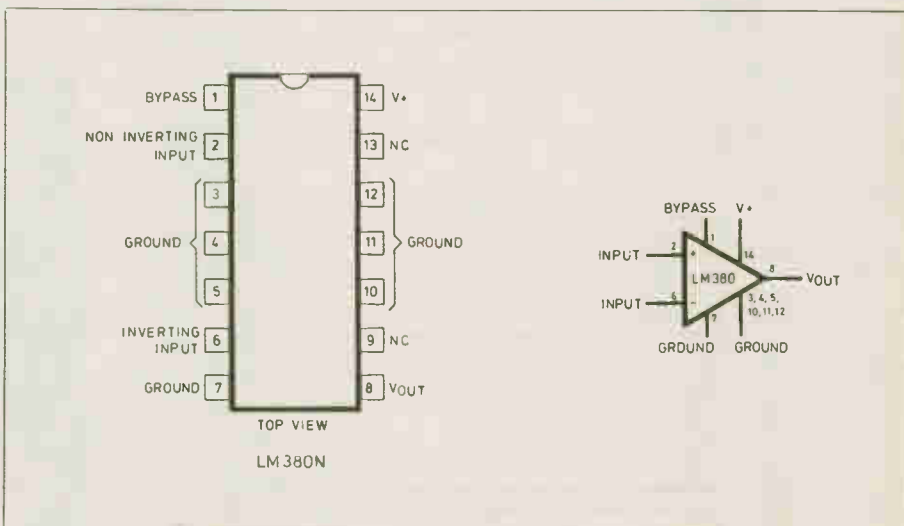


Fig. 1 The LM380N pin connections.

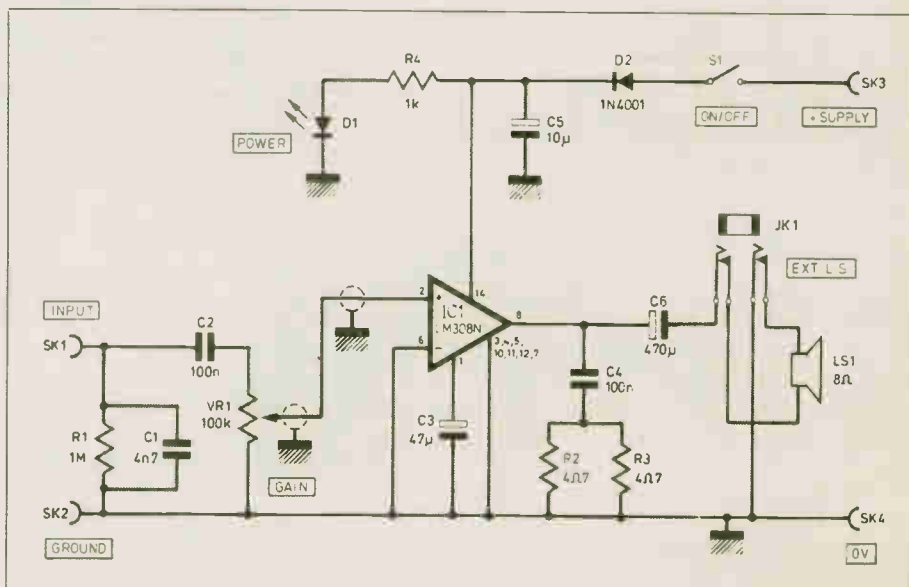


Fig. 2 The circuit diagram of the Audio Signal Tracer.



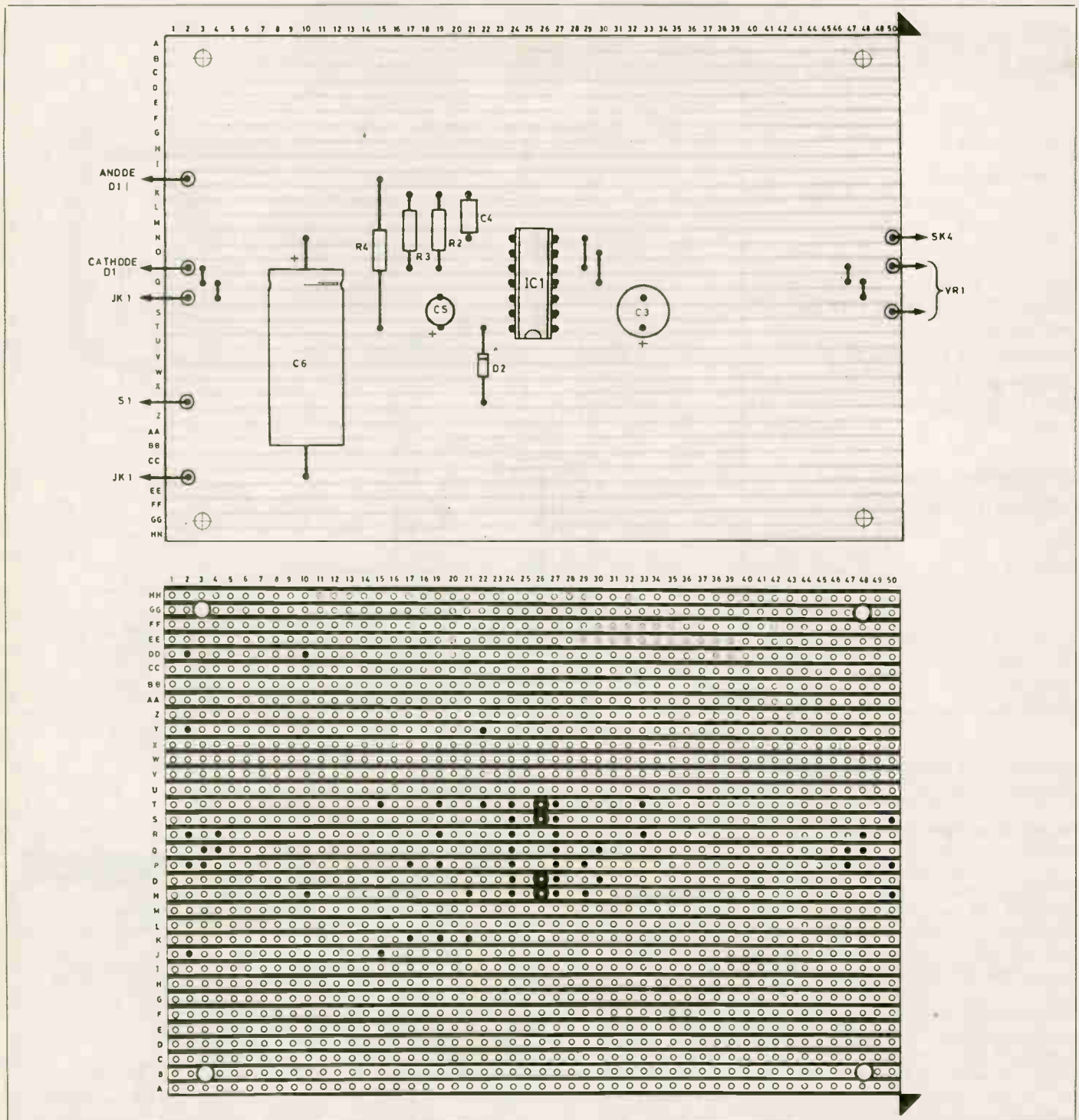


Fig. 3 The component layout (top) and breadboard for the AST.

The circuit diagram for the complete signal tracer is shown in Fig. 2. The input signal from SK1 is AC coupled to the non-inverting input of IC1 via C2. The gain of the tracer is set by VR1, and C3 provides the necessary bypass. The output from IC1 is coupled to the loudspeaker via C6. AC coupling is necessary because the no-signal output of the amplifier is automatically set to half of the supply voltage.

JK1 is a switched jack socket which allows an external loudspeaker to be used in place of the integral monitor, LS1. This is fairly useful if the tracer is being used simply as an audio amplifier, rather than a tracer. The series network formed by C4 and R2/R3 prevents oscillation of the amplifier, which may otherwise occur under some load conditions. The unit is protected against incorrect supply polarity by D2, while S1 and D1 provide power

supply switching and indicator functions respectively.

### Construction

Any suitable case which is capable of comfortably housing the perfboard and speaker can be used.

No special sequence is necessary in mounting the components; just take care in making sure that polarized components are oriented properly. The IC should be

## Parts List

### Resistors

All 0.25W 5%

R1 ..... 1M  
R2,3 ..... 4R7  
R4 ..... 1k

### Potentiometer

VR1 ..... 100k linear pot.

### Capacitors

C1 ..... 4n7 polyester 250V  
C2 ..... 100n polyester 250V  
C3 ..... 47u 25V electro.  
C4 ..... 100n polyester  
C5 ..... 10u 25V electro.  
C6 ..... 470u 25V electro.

### Semiconductors

D1 ..... 0.2" LED and panel holder  
D2 ..... 1N4001  
IC1 ..... LM380N

### Miscellaneous

LS1 ..... 2.5" 8 ohm speaker  
SK1 ..... 4mm terminal (red)  
SK2 ..... 4mm terminal (black)  
SK3 ..... 4mm socket (red)  
SK4 ..... 4mm socket (black)  
JK1 ..... switched standard jack socket  
S1 ..... SPST toggle switch

Knob with pointer; case; 0.1" breadboard, 5" x 3.75" and mounting hardware; 8 terminal pins.

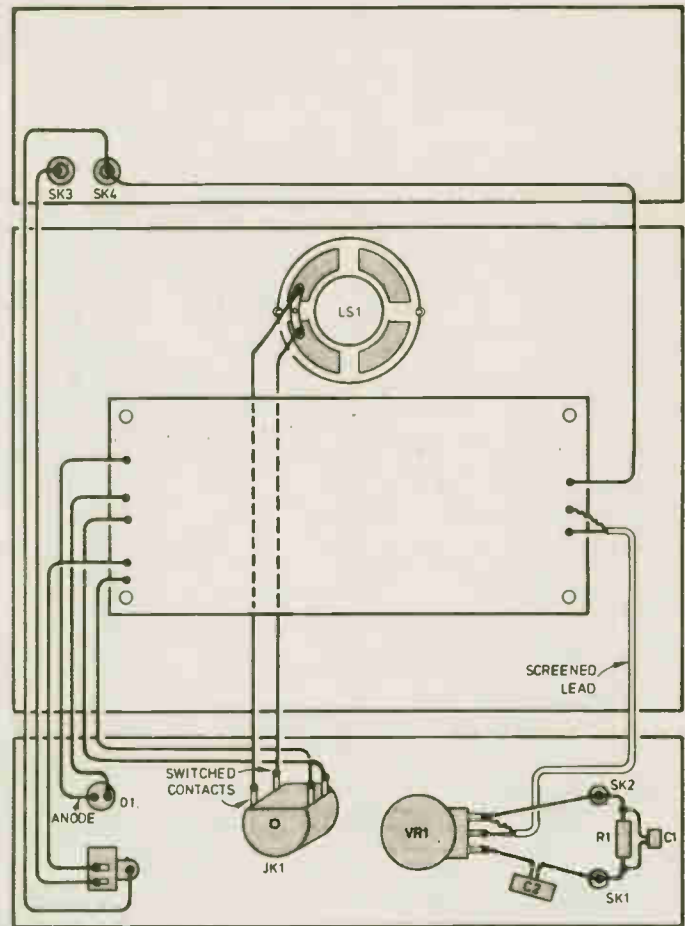


Fig. 4 Overall wiring diagram of the tracer.

mounted with a heatsink only if prolonged operation at high power levels is expected, and no heatsink is required if you're only using the small internal speaker.

The main circuit board should be mounted giving adequate clearance to both LS1 and the front panel mounting components. The remaining components (SK3 and SK4) should be mounted on the rear panel in any convenient position.

## Using The Tracer

The first check on the completed tester is to measure the supply current when the unit is connected to a DC supply of between 9V and 20V. With the gain setting at the minimum position, the current should be between 20mA and 50mA, and D1 should be illuminated. If there is no current, check the polarity of D2, and the power supply wiring. Any significantly higher current should be investigated before proceeding.

As the gain is increased, a low hum may become audible, particularly if a finger is placed on SK1. This indicates that all is well, and the tester is ready for use. The maximum output power available in use will depend on the impedance of the speaker, and on the power supply voltage.

To use the tester, a screened test lead with a 4mm plug at one end and insulated crocodile clip at the other will be required. The unit should produce a clearly audible output from signals as small as 1mV RMS.

To troubleshoot a circuit, a suitable audio signal is required, usually from a tuner, tapedeck or signal generator. The tracer can be used to follow the signal from the source (where the signal may be very low) through the various stages to the output. The change in setting of the gain control to keep the output approximately the same will give some idea of the gain of the various stages under test. This should allow the location of any change of signal, loss of gain, gain or distortion to be identified.

It must be stressed that the audio signal tracer is intended for use on transistorized equipment. *Under no circumstances should it be connected to full 120V AC potential.* ■

## Electronics Today

Offers advertisers the opportunity to increase their sales and profits in the electronic field. Over \$200 million is spent annually for both electronics and micro-computer products by Electronics Today readers.

For advertising information  
Call (416) 445-5600



NEW & REVISED

# BABANI BOOKS

Imported from England and exclusively available in Canada from Moorshead Publications.



**BP53: PRACTICAL ELECTRONICS CALCULATIONS AND FORMULAE** \$11.75  
A book that bridges the gap between complicated technical theory and the 'cut and try' method. A good reference book.

**BP136: 25 SIMPLE INDOOR AND WINDOW AERIALS** \$6.65  
People living in apartments who would like to improve short-wave listening can benefit from these instructions on optimising the indoor aerial.

**BP147: AN INTRODUCTION TO 6502 MACHINE CODE** \$7.75  
The popular 6502 microprocessor is used in many home computers, this is a guide to beginning assembly language.

**BP150: AN INTRO. TO PROGRAMMING THE SINCLAIR QL** \$7.75  
Helps the reader make the best use of the Sinclair QL's almost unlimited range of features. Complements the manufacturer's handbook.

**BP225: A PRACTICAL INTRODUCTION TO DIGITAL ICs** \$6.65  
This book deals mainly with TTL type chips such as the 7400 series. Simple projects and a complete practical construction of a Logic Test Circuit Set are included as well as details for a more complicated Digital Counter Timer project.

**BP130: MICRO INTERFACING CIRCUITS - BOOK 1** \$8.55  
Aimed at those who have some previous knowledge of electronics, but not necessarily an extensive one, the basis of the book is to help the individual understand the principles of interfacing circuits to microprocessor equipment.

**BP131: MICRO INTERFACING CIRCUITS - BOOK 2** \$8.55  
Intended to carry on from Book 1, this book deals with practical applications beyond the parallel and serial interface. "Real world" interfacing such as sound and speech generators, temperature and optical sensors, and motor controls are discussed using practical circuit descriptions.

**BP111: AUDIO** \$13.25  
This one is ideal for readers who want to really get into sound. A wide range of material is covered from analysis of the sound wave, mechanisms of hearing, room acoustics, microphones and loudspeakers, amplifiers, and magnetic disc recording.

**BP141: LINEAR IC EQUIVALENTS AND PIN CONNECTIONS ADRIAN MICHAELS** \$21.95  
Find equivalents and cross-references for both popular and unusual integrated circuits. Shows details of functions, manufacturer, country of origin, pinouts, etc.; includes National, Motorola, Fairchild, Harris, Motorola, Intersil, Philips, ADC, AMD, SGS, Teledyne, and many other European, American, and Japanese brands.

**BP156: AN INTRODUCTION TO QL MACHINE CODE** \$7.75  
The powerful Sinclair QL microcomputer has some outstanding capabilities in terms of its internal structure. With a 32-bit architecture, the QL has a large address range, advanced instructions which include multiplication and division. These features give the budding machine code programmer a good start at advanced programming methods. This book assumes no previous knowledge of either the 68008 or machine code programming.

**BP47: MOBILE DISCOTHEQUE HANDBOOK** \$5.25  
Divided into six parts, this book covers such areas of mobile "disco" as Basic Electricity, Audio, Ancillary Equipment, Cables and Plugs, Loudspeakers, and Lighting. All the information has been considerably sub-divided for quick and easy reference.

**BP59: SECOND BOOK OF CMOS IC PROJECTS** \$7.75  
This book carries on from its predecessor and provides a further selection of useful circuits, mainly of a simple nature. The book will be well within the capabilities of the beginner and more advanced constructor.

**BP32: HOW TO BUILD YOUR OWN METAL & TREASURE LOCATORS** \$7.75  
Several fascinating applications with complete electronic and practical details on the simple, and inexpensive construction of Heterodyne Metal Locators.

## ELECTRONIC THEORY

**ELEMENTS OF ELECTRONICS - AN ON-GOING SERIES F.A. WILSON, C.G.I.A., C.Eng.**

**BP62: BOOK 1. The Simple Electronic Circuit and Components** \$11.70

**BP63: BOOK 2. Alternating Current Theory** \$ 8.55

**BP64: BOOK 3. Semiconductor Technology** \$18.55

**BP77: BOOK 4. Microprocessing Systems And Circuits** \$11.70

**BP89: BOOK 5. Communication** \$11.70

The aim of this series of books can be stated quite simply - it is to provide an inexpensive introduction to modern electronics so that the reader will start on the right road by thoroughly understanding the fundamental principles involved.

Although written especially for readers with no more than ordinary arithmetical skills, the use of mathematics is not avoided, and all the mathematics required is taught as the reader progresses.

Each book is a complete treatise of a particular branch of the subject and, therefore, can be used on its own with one proviso, that the later books do not duplicate material from their predecessors, thus a working knowledge of the subjects covered by the earlier books is assumed.

**BOOK 1** This book contains all the fundamental theory necessary to lead to a full understanding of the simple electronic circuit and its main components.

**BOOK 2** This book continues with alternating current theory without which there can be no comprehension of speech, music, radio, television or even the electricity utilities.

**BOOK 3** Follows on semiconductor technology, leading up to transistors and integrated circuits.

**BOOK 4** A complete description of the internal workings of microprocessor.

**BOOK 5** A book covering the whole communication scene.

## PROJECTS

**BP48: ELECTRONIC PROJECTS FOR BEGINNERS** \$ 7.75  
**F.G. RAYER, T.Eng.(CEI), Assoc.IERE**  
Another book written by the very experienced author - Mr F.G. Rayer - and in it the newcomer to electronics will find a wide range of easily made projects. Also there are a considerable number of actual component and wiring layouts to aid the beginner.

Furthermore, a number of projects have been arranged so that they can be constructed without any need for soldering and thus avoid the need for a soldering iron.

Also, many of the later projects can be built along the lines as those in the 'No Soldering' section so this may considerably increase the scope of projects which the newcomer can build and use.

**BP37: 50 PROJECTS USING RELAYS, SCR'S & TRIACS** \$ 7.75  
**F.G. RAYER, T.Eng.(CEI), Assoc.IERE**

Relays, silicon controlled rectifiers (SCR's) and bidirectional triacs (TRIAC's) have a wide range of applications in electronics today. This book gives tried and practical working circuits which should present the minimum of difficulty for the enthusiast to construct. In most of the circuits there is a wide latitude in component values and types allowing easy modification of circuits or ready adaptation of them to individual needs.

**BP221: 28 TESTED TRANSISTOR PROJECTS** \$5.00  
**R. TORRENS**

Mr Richard Torrens is a well experienced electronics development engineer and has designed, developed, built and tested the many useful and interesting circuits included in this book. The projects themselves can be split down into simpler building blocks which are shown separated by boxes in the circuits for ease of description, and also to enable any reader who wishes to combine boxes from different projects to realise ideas of his own.

**BP71: ELECTRONIC HOUSEHOLD PROJECTS** \$ 7.20  
**R. A. PENFOLD**

Some of the most useful and popular electronic construction projects are those that can be used in or around the home. The circuits range from such things as '2 Tone Door Buzzer', Intercom, through Smoke or Gas Detectors to Baby and Freezer Alarms.

**BP73: REMOTE CONTROL PROJECTS** \$ 8.10  
**OWEN BISHOP**

This book is aimed primarily at the electronics enthusiast who wishes to experiment with remote control. Full explanations have been given so that the reader can fully understand how the circuits work and can more easily see how to modify them for other purposes depending on personal requirements. Not only are radio control systems considered but also infra red, visible light and ultrasonic systems as are the use of Logic IC's and Pulse position modulation etc.

**BP90: AUDIO PROJECTS** \$ 7.60  
**F.G. RAYER**

Covers in detail the construction of a wide range of audio projects. The text has been divided into preamplifiers and mixers, power amplifiers, tone controls and matching and miscellaneous projects.

**BP 174: MORE ADVANCED ELECTRONIC MUSIC PROJECTS** \$19.95

Complementing Book BP74, "Electronic Music Projects", BP174 provides more advanced projects, such as a flanger, a phaser, mini-chorus and ring modulators, percussion synthesis, etc. Each project has an introduction, circuit diagram and constructional notes.

**BP74: ELECTRONIC MUSIC PROJECTS** \$ 7.20  
**R.A. PENFOLD**


Although one of the more recent branches of amateur electronics, electronic music has now become extremely popular and there are many projects which fall into this category. The purpose of this book is to provide the constructor with a number of practical circuits for the less complex items of electronic music equipment, including such things as a Fuzz Box, Waa-Waa Pedal, Sustain Unit, Reverberation and Phaser Units, Tremelo Generator etc.

**BP4: IC 555 PROJECTS** \$ 7.75  
**E.A. PARR, B.Sc., C.Eng., M.I.E.E.**

Every so often a device appears that is so useful that one wonders how life went on before without it. The 555 timer is such a device. Included in this book are Basic and General Circuits, Motor Car and Model Railway Circuits, Alarms and Noise Makers as well as a section on the 556, 558 and 559 timers.

**BP82: ELECTRONIC PROJECTS USING SOLAR CELLS** \$ 7.75

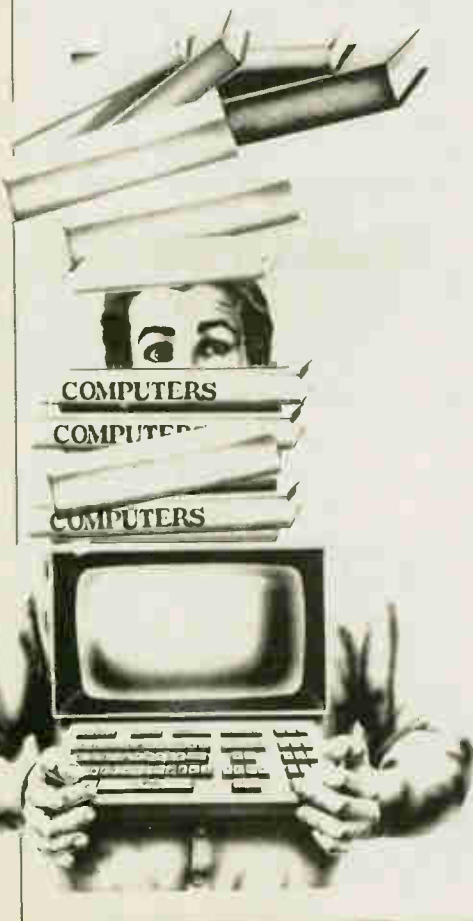A collection of simple circuits which have applications in and around the home using the energy of the sun to power them. The book deals with practical solar power supplies including voltage doubler and tripler circuits, as well as a number of projects.



# BABANI BOOKS

## BP49: POPULAR ELECTRONIC PROJECTS \$7.75 R.A. PENFOLD

Includes a collection of the most popular types of circuits and projects which, we feel sure, will provide a number of designs to interest most electronics constructors. The projects selected cover a very wide range and are divided into four basic types: Radio Projects, Audio Projects, Household Projects and Test Equipment

## BP94: ELECTRONIC PROJECTS FOR CARS AND BOATS \$7.60 R.A. PENFOLD

Projects, fifteen in all, which use a 12V supply are the basis of this book. Included are projects on Windscreen Wiper Control, Courtesy Light Delay, Battery Monitor, Cassette Power Supply, Lights Timer, Vehicle Immobiliser, Gas and Smoke Alarm, Depth Warning and Shaver Inverter

## BP95: MODEL RAILWAY PROJECTS \$7.60

Electronic projects for model railways are fairly recent and have made possible an amazing degree of realism. The projects covered include controllers, signals and sound effects. Striped layouts are provided for each project

## BP93: ELECTRONIC TIMER PROJECTS \$7.60 F.G. RAYER

Windscreen wiper delay, darkroom timer and metronome projects are included. Some of the more complex circuits are made up from simpler sub-circuits which are dealt with individually

## BP113: 30 Solderless Breadboard Projects-Book 2 \$8.85 R.A. Penfold

A companion to BP107. Describes a variety of projects that can be built on plug-in breadboards using CMOS logic IC's. Each project contains a schematic, parts list and operational notes.

## BP104: Electronic Science Projects \$8.85 Owen Bishop

Contains 12 electronic projects with a strong scientific flavour. Includes Simple Colour Temperature Meter, Infra-Red Laser, Electronic clock regulated by a resonating spring, a Scope with a solid state display, pH meter and electrocardiograph

## BP110: HOW TO GET YOUR ELECTRONIC PROJECTS WORKING \$7.60 R.A. PENFOLD

We have all built circuits from magazines and books only to find that they did not work correctly, or at all, when first switched on. The aim of this book is to help the reader overcome just these problems by indicating how and where to start looking for many of the common faults that can occur when building up projects

## BP84: DIGITAL IC PROJECTS \$7.60 F.G. RAYER, T.Eng.(CEI), Assoc.IERE

This book contains both simple and more advanced projects and it is hoped that these will be found of help to the reader developing a knowledge of the workings of digital circuits. To help the newcomer to the hobby the author has included a number of board layouts and wiring diagrams. Also the more ambitious projects can be built and tested section by section and this should help avoid or correct faults that could otherwise be troublesome. An ideal book for both beginner and more advanced enthusiast alike

## BP67: COUNTER DRIVER AND NUMERAL DISPLAY PROJECTS \$7.05 F.G. RAYER, T.Eng.(CEI), Assoc. IERE

Numeral indicating devices have come very much to the forefront in recent years and will, undoubtedly, find increasing applications in all sorts of equipment. With present day integrated circuits, it is easy to count, divide and display numerically the electrical pulses obtained from a great range of driver circuits

In this book many applications and projects using various types of numeral displays, popular counter and driver IC's etc. are considered

## BP99: MINI-MATRIX BOARD PROJECTS \$7.60 R.A. PENFOLD

Twenty useful projects which can all be built on a 24 x 10 hole matrix board with copper strips. Includes Doorbuzzer, Low voltage Alarm, AM Radio, Signal Generator, Projector Timer, Guitar Headphone Amp, Transistor Checker and more

## BP103: MULTI-CIRCUIT BOARD PROJECTS \$7.60 R.A. PENFOLD

This book allows the reader to build 21 fairly simple electronic projects, all of which may be constructed on the same printed circuit board. Wherever possible, the same components have been used in each design so that with a relatively small number of components and hence low cost, it is possible to make any one of the projects or by re-using the components and P.C.B. all of the projects

## BP107: 30 SOLDERLESS BREADBOARD PROJECTS - BOOK 1 \$8.85 R.A. PENFOLD

A "Solderless Breadboard" is simply a special board on which electronic circuits can be built and tested. The components used are just plugged in and unplugged as desired. The 30 projects featured in this book have been specially designed to be built on a "Verobloc" breadboard. Wherever possible the components used are common to several projects, hence with only a modest number of reasonably inexpensive components it is possible to build, in turn, every project shown

## BP106: MODERN OP-AMP PROJECTS \$7.60 R.A. PENFOLD

Features a wide range of constructional projects which make use of op-amps including low-noise, low distortion, ultra high input impedance, high slew-rate and high output current types

## CIRCUITS

### How to Design Electronic Projects

**BP127 \$8.95**  
Although information on standard circuit blocks is available, there is less information on combing these circuit parts together. This title does just that. Practical examples are used and each is analysed to show what each does and how to apply this to other designs

### Audio Amplifier Construction

**BP122 \$8.95**  
A wide circuits is given, from low noise microphone and tape head preamps to a 100W MOSFET type. There is also the circuit for 12V bridge amp giving 18W. Circuit board or strip-board layout are included. Most of the circuits are well within the capabilities for even those with limited experience

## BP80: POPULAR ELECTRONIC CIRCUITS - BOOK 1 \$7.75 R.A. PENFOLD

Another book by the very popular author Mr. R.A. Penfold, who has designed and developed a large number of various circuits. These are grouped under the following general headings, Audio Circuits, Radio Circuits, Test Gear Circuits, Music Project Circuits, Household Project Circuits and Miscellaneous Circuits

## BP98: POPULAR ELECTRONIC CIRCUITS, BOOK 2 \$8.85 R.A. PENFOLD

70 plus circuits based on modern components aimed at those with some experience

## BP39: 50 (FET) FIELD EFFECT TRANSISTOR PROJECTS \$6.75 F.G. RAYER, T.Eng.(CEI), Assoc.IERE

Field effect transistors (FETs) find application in a wide variety of circuits. The projects described here include radio frequency amplifiers and converters, test equipment and receiver aids, tuners, receivers, mixers and tone controls, as well as various miscellaneous devices which are useful in the home

This book contains something of particular interest for every class of enthusiast - short wave listener, radio amateur, experimenter or audio devotee

## BP162: COUNTING ON QL ABACUS

This book is designed to introduce the beginner to the use of spreadsheets in general and Abacus on the Sinclair QL in particular. It assumes no previous experience in computing or spreadsheets. Practical examples show the calculations for domestic, small business and technical applications

## BP87: SIMPLE L.E.D. CIRCUITS \$5.40 R.N. SOAR

Since it first appeared in 1977, Mr R.N. Soar's book has proved very popular. The author has developed a further range of circuits and these are included in Book 2. Projects include a Transistor Tester, Various Voltage Regulators, Testers and so on

## BP24: 50 PROJECTS USING IC 741 \$6.75 RUDI & UWE REDMER

A unique book containing 50 projects that can be simply constructed using an op amp and a few components. Originally published in Germany, this book will be an valuable asset to any hobbyist

## BP88: HOW TO USE OP AMPS \$8.85 E.A. PARR

A designer's guide covering several op amps serving as a source book of circuits and a reference book for design calculations. The approach has been made as non-mathematical as possible

## BP65: SINGLE IC PROJECTS \$6.05 R.A. PENFOLD

There is now a vast range of ICs available to the amateur market, the majority of which are not necessarily designed for use in a single application and can offer unlimited possibilities. All the projects contained in this book are simple to construct and are based on a single IC. A few projects employ one or two transistors in addition to an IC but in most cases the IC is the only active device used

## 223: 50 PROJECTS USING IC CA3130 \$5.00 R.A. PENFOLD

In this book, the author has designed and developed a number of interesting and useful projects which are divided into five general categories I - Audio Projects II - RF Projects III - Test Equipment IV - Household Projects V - Miscellaneous Projects

## BP117: PRACTICAL ELECTRONIC BUILDING BLOCKS BOOK 1 \$7.60

Virtually any electronic circuit will be found to consist of a number of distinct stages when analysed. Some circuits inevitably have unusual stages using specialised circuitry, but in most cases circuits are built up from building blocks of standard types

This book is designed to aid electronics enthusiasts who like to experiment with circuits and produce their own projects rather than simply follow published project designs

The circuits for a number of useful building blocks are included in this book. Where relevant, details of how to change the parameters of each circuit are given so that they can easily be modified to suit individual requirements

## BP102: THE 6809 COMPANION \$7.60

Written for machine language programmers who want to expand their knowledge of microprocessors. Outlines history, architecture, addressing modes, and the instruction set of the 6809 microprocessor. The book also covers such topics as converting programs from the 6800, program style, and specifics of 6809 hardware and software availability

## BP118: PRACTICAL ELECTRONIC BUILDING BLOCKS - Book 2 \$7.60 R.A. PENFOLD

This sequel to BP117 is written to help the reader create and experiment with his own circuits by combining standard type circuit building blocks. Circuits concerned with generating signals were covered in Book 1, this one deals with processing signals. Amplifiers and filters account for most of the book but comparators, Schmitt triggers and other circuits are covered

## BP24: 50 PROJECTS USING IC741 \$6.75 RUDI & UWE REDMER

This book, originally published in Germany by TOPP, has achieved phenomenal sales on the Continent and Babani decided, in view of the fact that the integrated circuit used in this book is inexpensive to buy, to make this unique book available to the English speaking reader. Translated from the original German with copious notes, data and circuitry, a "must" for everyone whatever their interest in electronics

## BP83: VMOS PROJECTS \$7.70 R.A. PENFOLD

Although modern bipolar power transistors give excellent results in a wide range of applications, they are not without their drawbacks or limitations. This book will primarily be concerned with VMOS power FETs although power MOSFETs will be dealt with in the chapter on audio circuits. A number of varied and interesting projects are covered under the main headings of Audio Circuits, Sound Generator Circuits, DC Control Circuits and Signal Control Circuits

## RADIO AND COMMUNICATIONS

## BP96: CB PROJECTS \$7.60 R.A. PENFOLD

Projects include speech processor, aerial booster, cordless mike, aerial and harmonic filters, field strength meter, power supply, CB receiver and more

## BP222: SOLID STATE SHORT WAVE RECEIVER FOR BEGINNERS \$47.60 R.A. PENFOLD

In this book, R.A. Penfold has designed and developed several modern solid state short wave receiver circuits that will give a fairly high level of performance, despite the fact that they use only relatively few and inexpensive components

## BP117: AN INTRODUCTION TO COMPUTER COMMUNICATIONS

Connecting up an ordinary home computer to the telephone system via a modem opens up a new world of possibilities, talking to other computers, databases, networks, radio links, etc. An explanation of basic principles and practicalities in simple terms

## BP91: AN INTRODUCTION TO RADIO DXing \$7.60

This book is divided into two main sections one to amateur band reception, the other to broadcast bands. Advice is given to suitable equipment and techniques. A number of related constructional projects are described

## BP105: AERIAL PROJECTS \$7.60 R.A. PENFOLD

The subject of aeriels is vast but in this book the author has considered practical designs including active, loop and ferrite aeriels, which give good performances and are reasonably simple and inexpensive to build. The complex theory and math of aerial design are avoided



# OTHER PUBLISHERS

**PH121: HARDWARE INTERFACING WITH THE TRS-80**  
**J. UFFENBECK (1983) \$19.45**  
 TRS-80 Model I and Model III users now have a book to help them understand their personal computers to monitor and interface between the computer and the industrial environment. Contains 14 hands-on experiments using BASIC.

**SB22026 POLISHING YOUR APPLE® \$7.45**  
 Clearly written, highly practical, concise assembly of all procedures needed for writing, disk-filing, and printing programs with an Apple II. Positively ends your searches through endless manuals to find the routine you need! Should be in the hands of every new Apple user, regardless of experience level. Ideal for Apple classrooms too!

**A BEGINNER'S GUIDE TO COMPUTERS AND MICROPROCESSORS — WITH PROJECTS.**  
**TAB No. 1015: \$14.45**  
 Here's plain English introduction to the world of microcomputers — its capabilities, parts and functions — and how you can use one. Numerous projects demonstrate operating principles and lead to the construction of an actual working computer capable of performing many useful functions.

**TAB1370: A MASTER HANDBOOK OF IC CIRCUITS \$21.95**  
 A circuit for every occasion. You'll find all the circuits you're looking for in this \$21.95 book. The 932 circuits are broken down into 12 functional categories and in six categories. It's a cornucopia of ideas, projects, and designs that you can build now.

**TAB1544: ELECTRONIC PROJECTS FOR PHOTOGRAPHERS \$21.95**  
 This book gives you needed tips on the principles of electronics and building techniques. It shows how to set up a work area, and much more. Includes hands of practical accessories for your studio, or darkroom with this helpful guide.

**SB22361: INTRODUCING THE APPLE MACINTOSH \$20.95**  
 A wealth of information on hardware, software etc. for the Mac. Included are such topics as making your desktop more efficient, improving your productivity with the Mac, getting the most from your mouse, how the 68000 microprocessor works and much, much more.

**PH131: ZAP! POW! BOOM! ARCADE GAMES FOR THE VIC 20**  
**T. HARTNELL & M. RAMSHAW (1983) \$17.45**  
 Move through the maze eating dots with MAZEMAN. Sail through space zapping the ASTEROIDS. Outshoot the fastest draw in town CUNFIGHT. Owners of the VIC 20 can now play these games — and more — simply by following the programs outlined in this handy guide.

**THE BASIC COOKBOOK.**  
**TAB No. 1055: \$10.45**  
 BASIC is a surprisingly powerful language. If you understand it completely. This book, picks up where most manufacturers' documentation gives up. With it, any computer owner can develop programs to make the most out of his or her machine.

**HANDBOOK OF MICROPROCESSOR APPLICATIONS**  
**TAB No. 1203 \$16.45**  
 Highly recommended reading for those who are interested in microprocessors as a means of accomplishing a specific task. The author discusses individual microprocessors, the 1802 and 1801, and how they can be put to use in real world applications.

**MICROPROCESSOR INTERFACING HANDBOOK: A/D & D/A**  
**TAB No. 1271 \$16.45**  
 A useful handbook for computer users interested in using their machine in linear applications. Topics discussed include voltage reference, data conversion, analogue switching and much more.

**HOW TO BUILD YOUR OWN WORKING MICROCOMPUTER**  
**TAB No. 1200 \$16.45**  
 An excellent reference or how-to book for building your own microcomputer. Hardware and software are developed as well as many practical circuits.

**PH180: 1984 CANADIAN BUSINESS GUIDE TO MICRO-COMPUTERS**  
**K. DORRICOTT \$11.95**  
 Written by the managing director of Deloitte, Haskins & Sells, a Canadian partnership of public accountants and other professional advisors to management, this book is one of the most complete comprehensive guides to microcomputers available. Starting with a general overview of microcomputers and their business applications, the author helps you assess your computer needs, compares and evaluates computer systems and application packages, and gives you tips on "doing it right". A must for anyone thinking of purchasing a microcomputer for business.

**COMPUTER PROGRAMS IN BASIC**  
**AB01 \$15.45**  
 A catalogue of over 1,600 fully indexed BASIC computer programs with applications in Business, Math, Games and more. This book lists available software, what it does, where to get it, and how to adapt it to your machine.

**PH217: BASIC COMPUTER PROGRAMMING FOR KIDS**  
**P. CASSIDY & J. CLOSE \$16.45**  
 Fully illustrated with photos and drawings, this book teaches the reader how to use computers and computing and gently introduces mathematics and the basic theory of computer work. Written in an easy conversational tone.

**PH51: PASCAL FOR THE APPLE**  
**IAIN MACCALLUM \$34.20**  
 A step-by-step introduction to Pascal for Apple II and Apple II Plus users. The package of text and software diskette provides readers with worthwhile and interesting programs which can be run immediately and the results studied. Includes over 200 exercises with full solutions. Book/Disk Package.

**PH52: APPLE GRAPHICS GAMES**  
**PAUL COLLETTA \$40.95**  
 Contains 10 arcade style games written especially for Apple II, including Spider, Piano Pairs and Poker, as well as education, math, and designing games. Book/Disk Package.

**PH57: START WITH BASIC FOR THE COMMODORE VIC 20**  
**D. MONROE \$33.45**  
 This book/cassette package shows the reader how easy it really is to create programs using the full capacity of the machine. Includes helpful exercises and step-by-step instructions to put the full power of the VIC 20 at the user's fingertips. Book/Cassette Package.

**SB21822: ENHANCING YOUR APPLE® II — VOLUME 1**  
**D. LANCASTER \$25.50**  
 Who but Mother Nature or Don Lancaster could successfully enhance an Apple? YOU can, with help from Volume 1 in Don's newest series for Sams. Among other things you'll learn (1) to mix text, I/O, and HIRE together anywhere on the screen in any combination, (2) how to make a new-wire modification that will open up whole new worlds of 3-D graphics and other special effects, plus (3) a fast and easy way to tear apart and understand somebody else's machine-language program. Other goodies abound!

**PH106: PROGRAMMING TIPS AND TECHNIQUES FOR THE APPLE II**  
**J. CAMPBELL (1983) \$23.45**  
 An advanced exploration of the intricacies of structures programming. Further develops the skills necessary to solve programming problems. Special chapter on sound and graphics which discusses both high and low resolution graphics for the Apple II.

**HB131: THE BEGINNER'S GUIDE TO BUYING A PERSONAL COMPUTER \$6.45**  
 Written for the potentially interested computer buyer, in non-technical language, this affordable book explains the terminology of personal computers, the problems and variables to be discussed and discovered while making that initial buying decision. The book does not make recommendations, but does present a great deal of information about the range of hardware available from the largest personal computing manufacturers. Readers discover the meaning and impact of screen displays, tape cassette storage and disk storage, graphics and resolution, and much more. Comparison charts clearly define standard and optional features of all the current mass market personal computers.

**DESIGNING MICROCOMPUTER SYSTEMS**  
**HB18: \$18.95**  
**POOCH AND CHATTERGY**

This book provides both hobbyists and electronic engineers with the background information necessary to build microcomputer systems. It discusses the hardware aspects of microcomputer systems. Timing devices are provided to explain sequences of operations in detail. Then the book goes on to describe three of the most popular microcomputer families, the Intel 8080 Zilog Z-80, and Motorola 6800. Also covered are designs of interfaces for peripheral devices, and information of building microcomputer systems from kits.

**S100 BUS HANDBOOK**  
**HB19: \$26.00**  
**BURSKY**

Here is a comprehensive book that exclusively discusses S-100 bus computer systems and how they are organized. The book covers computer fundamentals, basic electronics, and the parts of the computer. Individual chapters discuss the CPU, memory, input/output, bulk-memory devices, and specialized peripheral controllers. It explains all the operating details of commonly available S-100 systems. Schematic drawings.

**110 THYRISTOR PROJECTS USING SCRs AND TRIACS**  
**MARSTON \$13.45**  
**HB22**

A grab bag of challenging and useful semiconductor projects for the hobbyist, experimenter, and student. The project range from simple burglar, fire, and water level alarms to sophisticated power control devices for electric tools and trans. Integrated circuits are incorporated wherever their use reduces project costs.

**PH104: ACCOUNTANT'S BASIC PROGRAMMING FOR THE APPLE II**  
**A PARKER & J. STEWART (1983) \$20.45**  
 Shows the reader how to program the Apple II to perform a variety of accounting functions, such as payroll, accounts payable, accounts receivable, tax, inventory customer statements, and more.

**HOW TO PROFIT FROM YOUR PERSONAL COMPUTER: PROFESSIONAL, BUSINESS, AND HOME APPLICATIONS**  
**LEWIS \$18.95**  
**HB01**

Describes the uses of personal computers in common business applications, such as accounting, managing, inventory, sorting mailing lists and many others. The discussion includes terms, notations, and techniques commonly used by programmers. A full glossary of terms.

**AN INTRODUCTION TO MICROPROCESSORS EXPERIMENTS IN DIGITAL TECHNOLOGY**  
**HB07 \$18.95**  
**SMITH**

A "learn by doing" guide to the use of integrated circuits provides a foundation for the underlying hardware actions of programming statements. Emphasis is placed on how digital circuitry compares with analog circuitry. Begins with the simplest gates and timers, then introduces the fundamental parts of ICs, detailing the benefits and pitfalls of major IC families, and continues with coverage of the ultimate in integrated complexity — the microprocessor.

**MICROCOMPUTERS AND THE 3 R'S**  
**DOERR \$16.45**  
**HB09**

This book educates educators, on the various ways computers especially microcomputers, can be used in the classroom. It describes microcomputers, how to organize a computer-based program, the five instructional application types (with examples from subjects such as the hard sciences, life sciences, English, history, and government), and resources listings of today's products. The book includes preprogrammed examples to start up a microcomputer program, while chapters on resources and products direct the reader to useful additional information. All programs are written in the BASIC language.

**HB107: GRAPHICS COOKBOOK FOR THE APPLE WADSWORTH \$15.95**  
**HB107**

Learn how to use your Apple II to "paint" shapes, objects, and letters in low-resolution graphics. The author provides a library of microcomputer graphics including such multicolored illustrations as robots and flying saucers, trees, sailboats, and colourful picture backgrounds. Contains complete annotated Apple-II BASIC programs to draw all the pictures described in the book as well as suggestions for improving programming techniques.

**HB116: THE BASIC CONVERSIONS HANDBOOK FOR APPLIEM, TRS-80TM, and PETM USERS**  
**BRAIN BANK \$14.50**

A complete guide to converting Apple II and PET programs to TRS-80, TRS-80 and PET programs to Apple II, and TRS-80 and Apple II programs to PET. Equivalent commands are listed for TRS-80 BASIC (Model I, Level II), Applesoft BASIC and PET BASIC as well as variations for TRS-80 Model III and Apple Integer BASIC. Also describes variations in graphics capabilities.

**SARGON: A COMPUTER CHESS PROGRAM**  
**SPRACKLEN \$27.50**  
**HB12**

"I must rate this chess program an excellent buy for anyone who loves the game." Kilobaud  
 Here is the computer chess program that won first place in the first chess tournament at the 1978 West Coast Computer Faire. It is written in Z-80 assembly language using the TDI macro assembler. It comes complete with block diagram and sample printouts.

**BASIC COMPUTER PROGRAMS FOR BUSINESS: STERNBERG (Vol. 1)**  
**HB13 \$21.50**

A must for small businesses utilizing micros as well as for entrepreneurs, volume provides a wealth of practical business applications. Each program is documented with a description of its functions and operation, a listing in BASIC, a symbol table, sample data, and one or more samples.

**AUDIO AND VIDEO INTERFERENCE CURES**  
**KAHANER \$8.95**  
**HB21**

A practical work about interference causes and cures that affect TV, radio, hi-fi, CB and other devices. Provides all the information needed to eliminate interference. Schematics wiring diagrams of filter types of receivers and transmitters are included. Also supplies simple filter diagrams to eliminate TV interference caused by noisy home appliances, on lights, motors, etc.

**PH107: APPLE LOGO PRIMER**  
**G. BITTER & N. WATSON (1983) \$19.95**

A pictorial starter book that will make LOGO easy for anyone. Includes easy to follow examples and reference tables. Also included is a workshop outline for teachers and leaders who want to train others.

**SB22047: 26 BASIC PROGRAMS FOR YOUR MICRO \$17.45**

Features 26 previously unpublished, simple-to-complex games you can run on almost any brand of microcomputer as long as you have enough RAM on board. Most take between 500 and 5000 bytes, with the highest taking 13K. Conversion charts that let you key them into your Radio Shack, TRS-80, Apple II, Timex/Sinclair 1000 (ZX81), Spectrum, Atari, or PET are included. Also features notes on program techniques and structures.

# Versatile PSU

**A regulated variable voltage supply with constant current for charging Ni-cads or powering your projects.**

By M.P. Horsey

THE HIGH COST of any power supply unit is due mainly to the transformer and the need for protection from high AC voltages in the form of fuses, switches, neon indicators, and a substantial case. It is helpful, therefore, to make any power unit as versatile as possible. The unit to be described provides a regulated variable voltage output from 1.2V to 15V and a constant current output, suitable for charging a wide range of nickel-cadmium cells.

## Control

The voltage is controlled with a variable resistor linked with an integrated circuit, and regulation is sufficiently accurate to allow a scale to be marked, without the need for a built-in voltmeter.

The constant current required is set via a rotary switch. The settings are as follows:

Setting 1. Regulated voltage output.

Setting 2. Constant current 8mA (for charging 9V batteries & AAA cells).

Setting 3. Constant current 45mA (for charging AA cells).

Setting 4. Constant current 80mA

Setting 5. Constant current 150mA (for charging C cells).

Setting 6. Constant current 320mA (for charging D cells).

## Automatic Voltage Regulation

Regulator circuits can be designed which automatically compensate for a changing current, and therefore provide a true regulated voltage. Such circuits can now be obtained in the form of miniature integrated circuits, such as the chip which forms the heart of this project, the LM317T.

This IC provides a possible regulated voltage range from 1.2V to 37V, at up to 1.2A. It is fully protected from short circuits, and includes thermal shutdown which automatically reduces the current if the IC becomes too hot. The basic regulated voltage circuit is shown in Fig. 1.

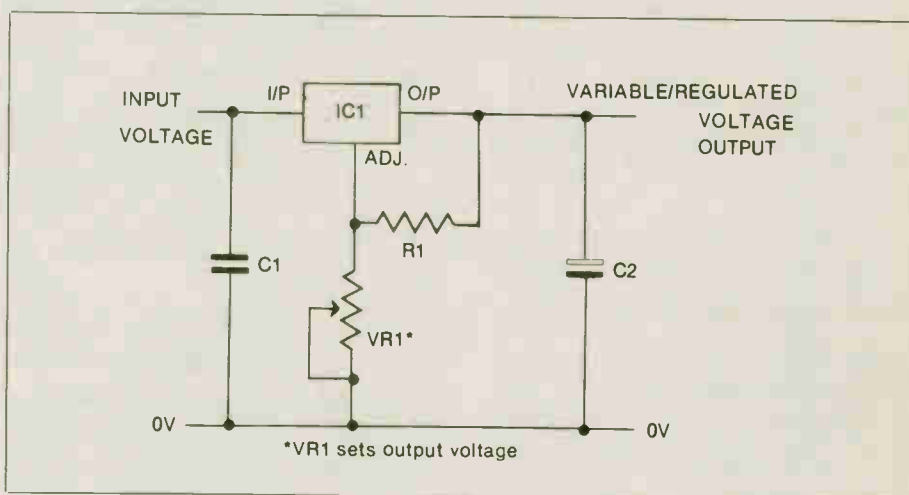


Fig. 1 Basic regulated voltage circuit.

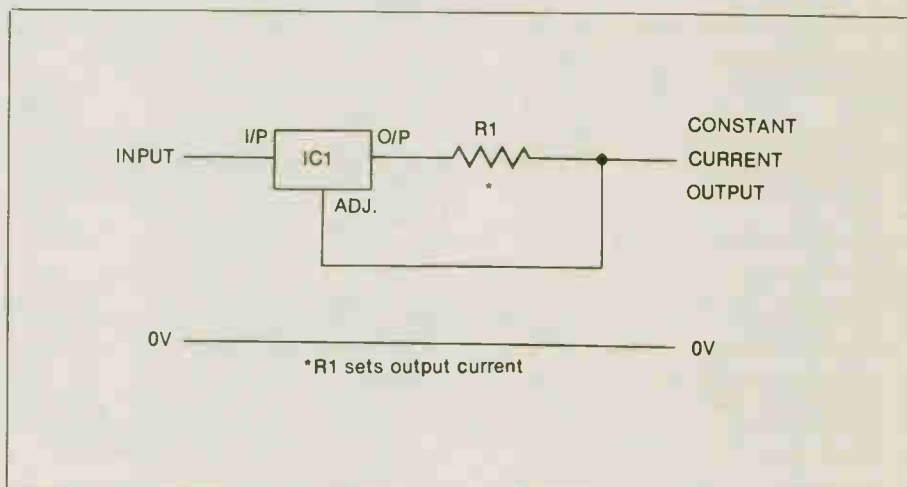


Fig. 2 Constant current regulation is determined by R1.

## Automatic Current Regulation

The same IC may also be wired to produce a constant current which is determined by a single resistor. The following formula may be used to calculate the size of the resistor required:

$$\text{Output current} = 1.25/R$$

(where R is the value of the resistor)

Thus, if a current of 45mA is required, the resistor needed will have a value of 27 ohms as shown in Fig. 2.

The figures quoted for voltage and current regulation assume ideal conditions but actual values will depend on the type of heat sink used, and the voltage drop across the IC.



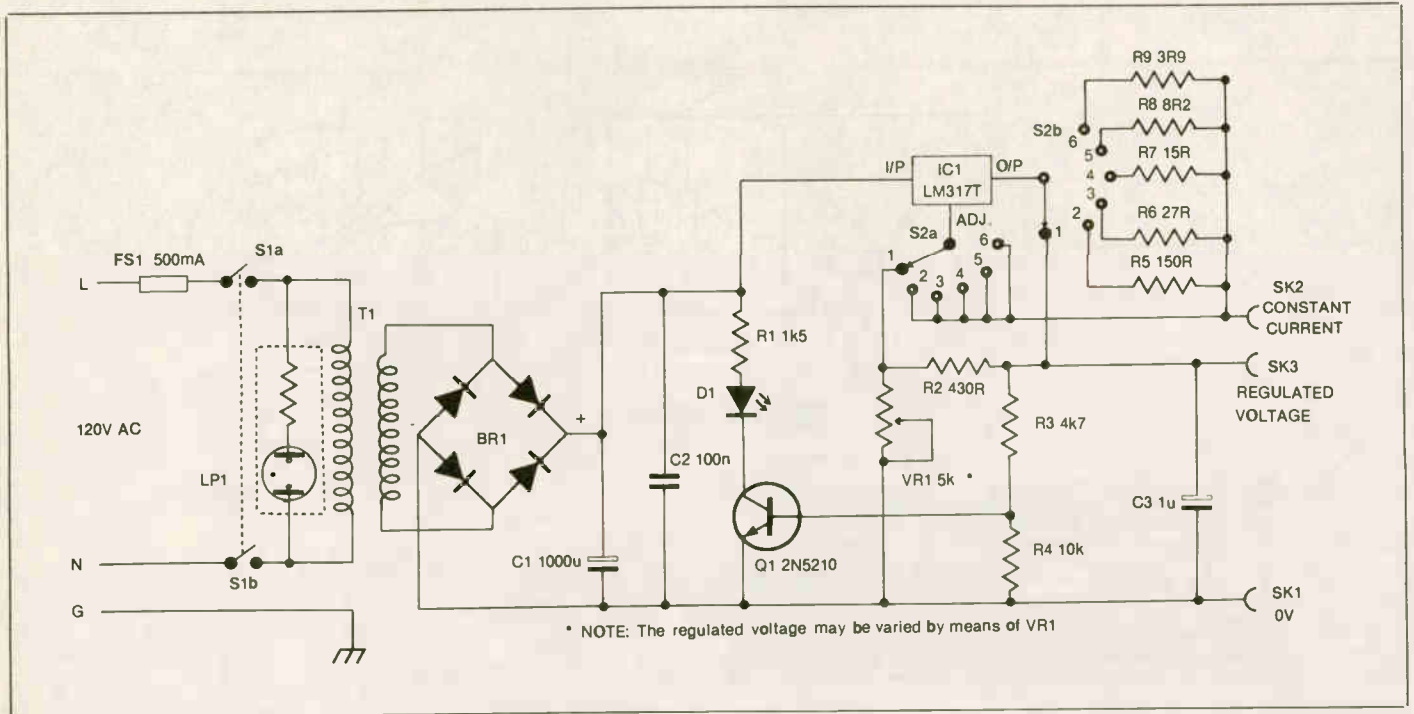


Fig. 3 Complete circuit diagram for the unit.

### Circuit Description

In this project a conventional transformer circuit is employed, with transformer T1 stepping down the 120V AC to 12V AC. Four silicon diodes (contained in a bridge rectifier), are used to rectify the AC into DC, and capacitors C1 and C2 provide smoothing of the supply. The positive supply is fed into the IC, the output of which is fed via switch S2, either into one of the current control resistors, or to the regulated voltage output. This allows VR1 to control the voltage when S2 is in position 1.

Voltage regulation is sufficiently accurate to allow calibration of VR1, which removes the need for a built-in voltmeter. However, without a voltmeter, there is no indication if a short circuit is connected across the output. An LED indicator is therefore included, with components R3, R4, Q1 and R1.

Under normal conditions, enough current will flow into the base of transistor Q1 to turn it on, and the LED will light as current flows through limiting resistor R1 to ground via the transistor. If a short circuit occurs the voltage at the junction between R3 and R4 will fall, causing the LED to switch off.

Such a short circuit will not harm the IC, or any other part of the power unit. However, it is essential to be aware of this condition, in case damage is caused to whatever is connected to the power unit. Note that the LED does not function when the unit is set to constant current, since a virtual short circuit is normal in this application.

If switch S2 is set to position 2, the adjust pin is connected directly to the constant current output. The IC output is also connected to the constant current output, but via resistor R5. Thus a circuit similar to that shown in Fig. 2 is created, the 150 ohm value of R5 fixing the output current to 8.3 mA.

The other positions of switch S2 work in a similar manner providing a variety of output current options.

### Construction

The majority of components are housed on a piece of stripboard measuring 70mm by 40mm. This is large enough to allow four holes to be drilled for mounting purposes.

Begin by marking out the stripboard, shown in Fig. 4, including the positions of the breaks. Strictly speaking, only one break is necessary on track F. It was considered necessary, however, to isolate the AC supply as much as possible; hence the other break. If the stripboard is to be mounted with metal screws, make additional breaks to isolate them from the circuit.

The regulator IC (IC1) is positioned in order to allow a heatsink to be fitted. The prototype used a strip of aluminium measuring 19cm by 5cm, and shaped in order to avoid other components. Alternatively, IC1 may be bolted to the case, if it's made of metal. Note, however, that the metal tag on the IC is connected internally to the output pin. It is essential to electrically isolate the tag, if it is bolted to the case.

The LED is connected via flexible wires. Be sure to use wires capable of carrying up to 2A for the AC input. The wires linking the rotary switch with the stripboard must have the lowest possible resistance, if good load regulation is to be achieved. Therefore, keep the wires as short as possible, and reasonably thick.

Resistors R5 and R9 are soldered to the rotary switch contacts. A piece of flexible wire is used to join their opposite ends together with the other tags of the switch as shown. The constant current output is also taken from this connection. Finally, link variable resistor VR1 with the stripboard, and solder in the regulated voltage output, and zero output wires. Check the stripboard for bridged tracks, dry joints, etc. Check also that the AC supply is fully isolated from the DC side of the circuit.

It may be easier to test the circuit before the stripboard is mounted in the case. (See 'Testing').

Almost any sturdy case may be used. Ensure that there is sufficient space for the transformer, and allow enough clearance for the potentiometer, switches, etc. The prototype unit was housed in a case with sloping front.

If ventilation holes are not provided, begin by drilling some, especially near the heatsink. However, ensure that small children are not able to make contact with AC connections inside. Any metal parts of the case must be properly grounded (i.e. connected to the AC ground), as must the transformer.

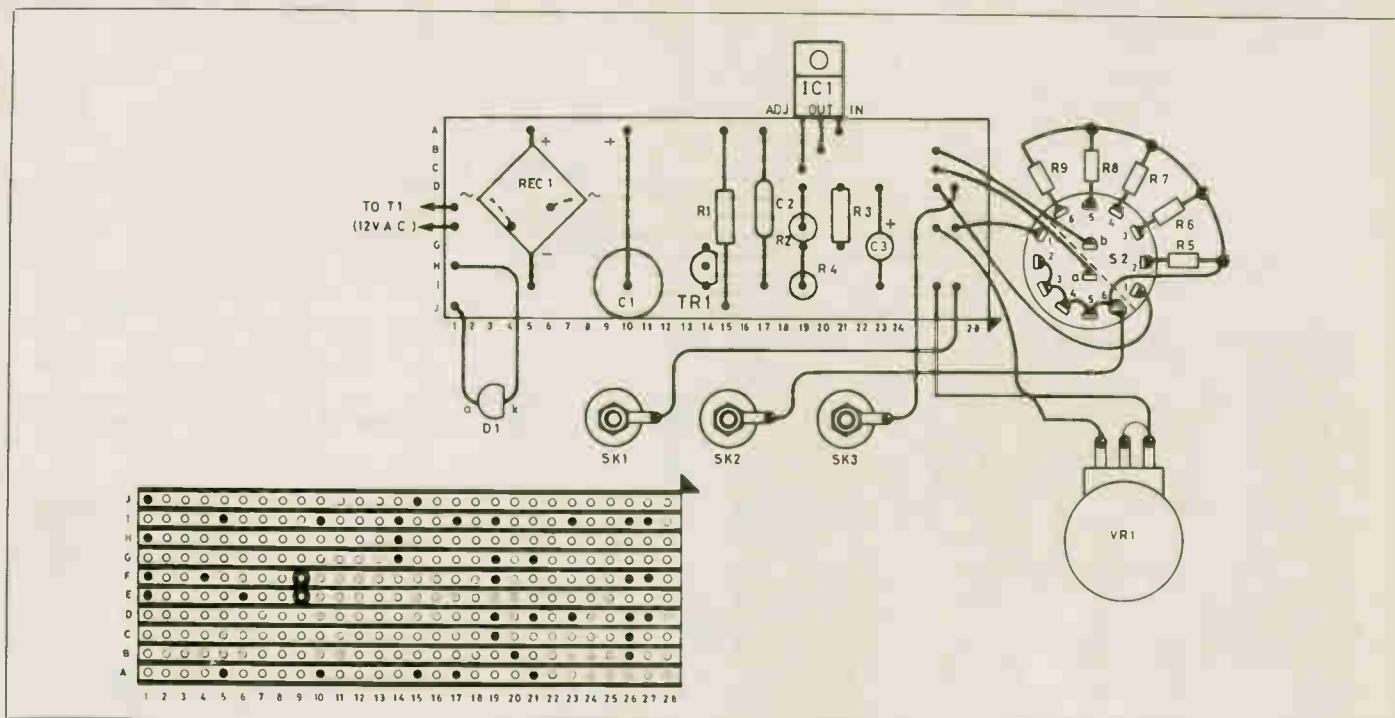


Fig. 4 Component layout.

### Parts List

#### Resistors

(All resistors 5% 1/4W unless noted otherwise)

R1	.....	1k5
R2	.....	.430R
R3	.....	.4k7
R4	.....	10k
R5	.....	150R
R6	.....	.27R
R7	.....	15R
R8	.....	8.2R (1/2W)
R9	.....	3.9R (1/2W)

#### Potentiometers

VR1 ..... k linear

#### Capacitors

C1	.....	1000uF 25V elect.
C2	.....	100n polyester
C3	.....	1uF 50V elect.

#### Semiconductors

BR1	.....	2A, 50V bridge rectifier
Q1	.....	2N5210 (npn)
IC1	.....	LM317T variable regulator IC
D1	.....	0.2" LED

#### Miscellaneous

LP1 - AC neon indicator with integral resistor; T1 - 20VA, 12VAC power transformer, 1.6A output; S1 - DPST toggle switch; S2 - 2 pole, 6-way rotary; fuse holder and 500mA fuse; knobs (2); terminals (2 red, 1 black); case to suit; heat-sink; 13A plug; stripboard (40mm x 70mm); AC cable; screws etc.

### Testing

The circuit may be tested at this stage if a suitable AC or DC supply is available (a 9V battery will suffice). Alternatively, testing may be carried out when the transformer and associated circuitry is installed and working.

Connect the AC (on the stripboard) to the supply. Set the rotary switch S2 to position 1 (fully counter-clockwise — if wired correctly).

The LED should light. If it does not, use a voltmeter to find out if there is a voltage across it. If a reading of several volts is obtained, the LED is probably connected the wrong way around.

Use the voltmeter to test the regulated output voltage. It should be possible to vary this voltage, using VR1, from 1.2V to a little less than the input voltage. If no reading is obtained, connect the voltmeter across tracks A and I, and establish that the rectifier is working properly. Check the voltage on the output (centre) pin of IC1. If this is satisfactory, there may be a wiring fault at switch S2. Note that for a regulated voltage output, the rotary switch should connect track B to track D, and track C to track F.

### Final Checks

**WARNING:** These checks will quickly run down a battery, if in use as a temporary power supply.

If all is well, short circuit the regulated voltage output. The LED should go out. The short circuit current should range from 2A to 3A, quickly falling to about 1A. This may be tested if an ammeter with an FSD of about 5A is available.

Finally, connect an ammeter set to 1A FSD to the constant current output. Turn the rotary switch to position 2. The LED should turn off, and the ammeter should show a small reading, which when set to a smaller scale, indicates about 8mA. Check that the other positions of S2 produce the correct current readings.

### Calibration

Calibration of VR1 must be accomplished with the aid of a voltmeter. The scale must be marked by hand, at 1V or 5V intervals. Switch S2 may be marked with the current options outlined earlier, not forgetting that setting 1 is reserved for regulated voltage operation. ■

## Electronics Today

Each year Electronics Today delivers thousands of sales leads processed through our Reader Service Card Program. These sales leads are qualified with name, address and title of respondent.

For advertising information call

(416) 445-5600



THE BOOK OF

# Computer Music



MIDI may be the most significant advance in music technology since the discovery of sound. However, if you can't understand what it's capable of... or can't comprehend the cacaphony of manufacturers' claims that surround it... it might as well have been a new revolution in food processors.


We understand MIDI better than anyone. We're comfortable with both the computers in all their confusing technological glory and with the music that makes them all worth while. If you read the **Book of Computer Music** you'll understand MIDI too.

And you'll realize that it's as magnificent a trip as everyone says it is.

Whether you're an amateur musician with a cassette deck and a keyboard, a working performer or a studio artist, the **Book of Computer Music** will turn you onto MIDI as no other reference work can. By the time you hit the back cover you'll be wholly comfortable with system exclusives, tracks, MIDI messages, FM synthesis, through boxes and all the other mystifying technological mind games that accompany this powerful new musical instrument.

You'll be able to play MIDI as easily as you play keyboards for guitar... or flute or violin or percussion or nose harp... right now.

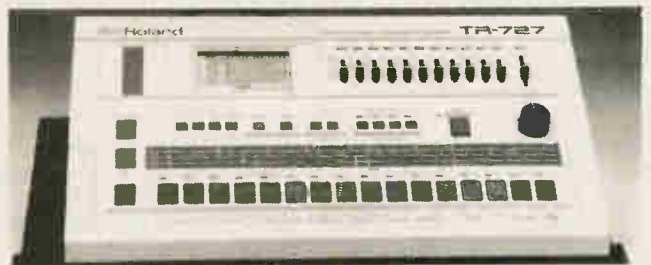Included in the **Book of Computer Music** are articles about



The Yamaha DX-7 • The IVL Pitch Rider • Personal Composer • The Yamaha RX-21 • Total Music for the Macintosh • The Yamaha CX5M Music Computer • The Akai AX-60 • The Roland GR Instruments • Computers For Musicians • The Roland SDE 2500 MIDI effects system • The Yamaha DX-100 • The Nexus FM Drawing Board • The Akai S612 Sampler • Building a MIDI Through Box • The Roland Alpha Juno • DX-7 Voice Editing • Writing Your Own MIDI Software.

Plus a complete introduction to MIDI in a number of in depth, easy to understand articles that won't leave you feeling like your head got lost in the Twilight Zone.

**Give us five bucks... we'll make you smart**  
**Actually, we only want**

**\$4.95**

plus 7% music tax for Ontario residents and \$1.00 for postage.

The **Book of Computer Music** is available now!

To order your copy, please send \$4.95 (plus \$1.00 postage and 7% Ontario sales tax) to

**The Book of Computer Music**  
 1300 Don Mills Road,  
 Don Mills, Toronto, Ontario M3B 3M8  
 or phone us at (416) 445-5600

NAME \_\_\_\_\_  
 ADDRESS \_\_\_\_\_  
 TOWN/CITY \_\_\_\_\_ PROVINCE/STATE \_\_\_\_\_  
 POSTAL CODE \_\_\_\_\_ DATE \_\_\_\_\_  
 Cheque enclosed DO NOT send cash  
 Mastercard Account No. \_\_\_\_\_  
 Visa Account No. \_\_\_\_\_  
 American Express Account No. \_\_\_\_\_  
 Expiry Date \_\_\_\_\_  
 Signature \_\_\_\_\_

**Moorshead Publications, Subscription Department,**  
 1300 Don Mills Road, Toronto, Ontario M3B 3M8 (416) 445-5600

# Designer's Notebook

## Programmable Logic Controllers

**The programmable controller is a miniature computer for industrial control; a look at the basics of how they work.**

By Peter Ihnat and Lew Pogson



SINCE the successful development of the digital computer there has been a steady increase in the application of digital principles and devices in industrial electronics. The reason for this is that digital implementation is efficient, reliable, flexible and, in many cases, cheaper than existing analogue equipment. Couple this with the ability to interconnect digital equipment in the plant with the central computer back at the office and you have a factory which is efficient and economical to run; all stages of production can be easily monitored, and new orders or changes to existing orders can be rapidly passed on to the plant.

lathe, machining into shape, drilling appropriate holes and then putting it onto a conveyor to travel to the anodizing area. This is where the industrial control system comes into the picture; it must provide precise coordination of the individual tasks for the overall system to function.

Controllers can be divided into two general categories: sequential and combinatorial. Sequential controllers are for processes which require that certain operations be performed in a specific order. Combinatorial controllers, on the other hand, perform operations without regard to the order. The machining of a metal piece as described above is an example of a sequential process needing sequential control, a bit like filling a bottle and then putting the cap on: it has to be done in that order.

An example of a combinatorial process is the placing of labels on the front and back of a cardboard carton; it doesn't matter in which order this is done. In industry, the majority of control problems are sequential but in practice all processes, whether inherently sequential or not, are performed sequentially. This generally reduces setup costs and results in a well-ordered system.

Early controllers used multicontact relays which were interconnected to perform various functions. Control switches such as start, stop, override, etc. operated the relay coils. The contacts they switched operated indicator lamps, motors, solenoids and other relay coils. With the introduction of digital logic to industry, design and implementation of these controllers were greatly simplified. Let's examine some simple ideas in the development of digital controllers.

A closed relay contact represents the TRUE or logic 1 state and the open contact FALSE or logic 0. Fig. 1 shows some basic relay contact connections and their equivalent logic functions.

Fig. 1a shows the AND function: there will be continuity between points 1

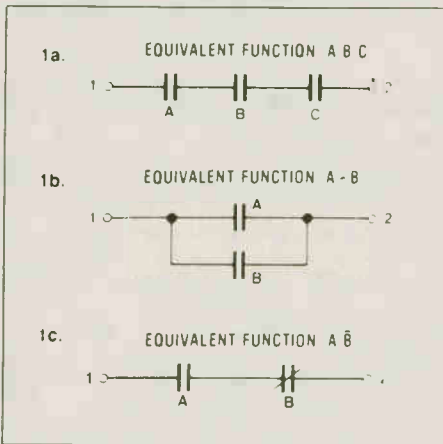


Fig. 1. Equivalent logic functions for some simple relay contact connections.

### Industrial Control

Most industrial processes require several operations to produce the required output. Some or all of the following could be involved: manufacturing, machining, assembling, packaging, finishing and transporting. But on closer examination it becomes obvious that each of these operations is composed of other operations.

For example, to machine a particular metal piece may involve loading it into a

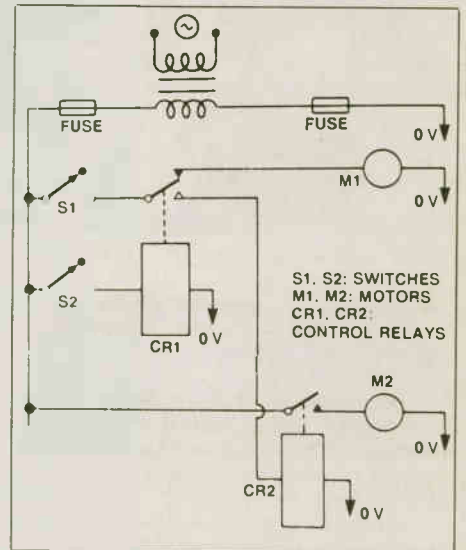


Fig. 2a. Example of a simple controller.

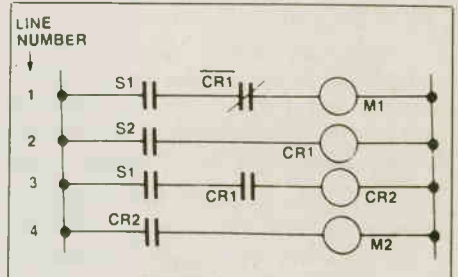


Fig. 2b. Relay ladder diagram for Figure 2a.

Electronics Today would like to indulge in an experiment. This article was typeset from a manuscript using a word processor, typesetting software and a laser printer. It should be interesting to see how the digitally created characters fare against the usual phototypesetting.



and 2 only if contacts A AND B AND C are closed. This will occur if the coils which operate contacts A, B and C are all energized.

The OR function is shown in Fig. 1b and results in continuity if contact A OR B (OR both) are closed. Once again this implies that any of the coils which operates contacts A or B is energized (or both are).

Fig. 1c is basically the same as 1b except that continuity is realized if contact A's coil is energized and B's coil is not (in other words, B is a normally closed contact which opens when its coil is energized).

To give a more practical example, refer to Fig. 2. Figure 2a shows two motors, M1 and M2, connected to switches S1, S2 and control relays CR1 and CR2. Operation is as follows: Motor M1 is energized if S1 is ON and S2 is OFF. Motor M2 is energized via relays CR1 and CR2 only if S1 AND S2 are both ON.

Figure 2b shows the equivalent "circuit diagram" which is more commonly known as the RELAY LADDER DIAGRAM. The supply transformer usually has fuses in each secondary lead which then extend vertically to form boundary lines for the diagram. The following conventions are used:

- \* the supply transformer and its fuses are usually not shown
- \* switches, relay contacts and other input devices are placed on the left of the diagram.
- \* relay coils, lights, motors and other output devices are placed on the right of the diagram.
- \* output devices are shown in the order they are energized during normal sequence of operations. This enables the operation sequence to be easily listed by traversing the ladder diagram line by line.

The actual controller is hard wired by interconnecting banks of relays in accordance with the ladder diagram and then connecting switches, motors, lamps, etc. to it.

There are several techniques for designing the sequential controller, given a request in the form of word statements, specifications or manufacturing statements. Most are rather involved and require state diagrams, transition tables and minimization techniques and, as mentioned previously, are outside the scope of this article. For very simple cases the "common sense" approach usually works and basically is a way of producing a relay ladder diagram line by line as one goes through a machine cycle. This is the method we'll use later when showing examples of P.C. programming.

### Application of Solid-state Logic

Originally, the relay ladder diagrams were implemented as implied: racks of relays hard wired to each other, to switches, indicator lights, motors and whatever else needed controlling. You can probably see the major

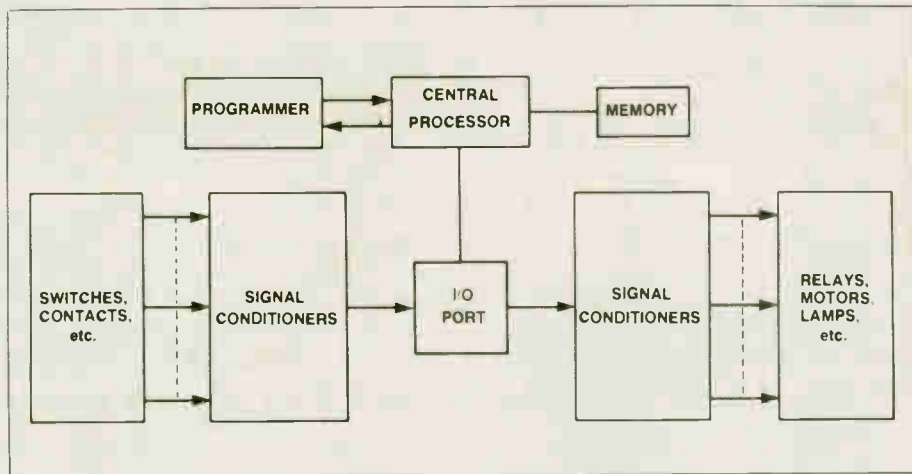


Fig. 3a. Block diagram of a programmable controller setup.

disadvantage of such a system. Any changes required to the control system meant physically changing relays and rewiring the new section, a costly and time-consuming operation.

So it seems quite logical ('scuse the pun) that the next step in the evolution of controllers was to use solid-state digital logic to replace many conventional relay panels. The advantages were higher reliability, lower cost, smaller size, higher speed, increased flexibility and compatibility with computers.

The transition to digital logic was straightforward since, as we saw in Figure 1, the various lines in a ladder diagram can be written as Boolean equations. The design process involves converting the control requirements to Boolean form, performing any simplifications, choosing the components to perform the logic decision-making and selecting the proper interfacing devices to match the circuitry to the outside world.

Solid-state logic components are classified into four categories: input interfacing, logic gates, output interfacing and accessory components. Each component is a transistorized, plug-in module able to perform one function. Groups of these plug into a base which allows interconnections to be made between the modules. Diagrammatically, the relay ladder diagram is replaced by a logic diagram which uses appropriate logic symbols for the different functions.

### Programmable Controllers

Even though solid-state logic controllers were simpler to construct than an equivalent relay panel, they were still designed and built for a specific operation or process. The cost of making changes to the circuit was still quite high. In the late 1960s a new type of controller emerged from the automotive industry's need for more flexible control on the factory floor. The programmable con-

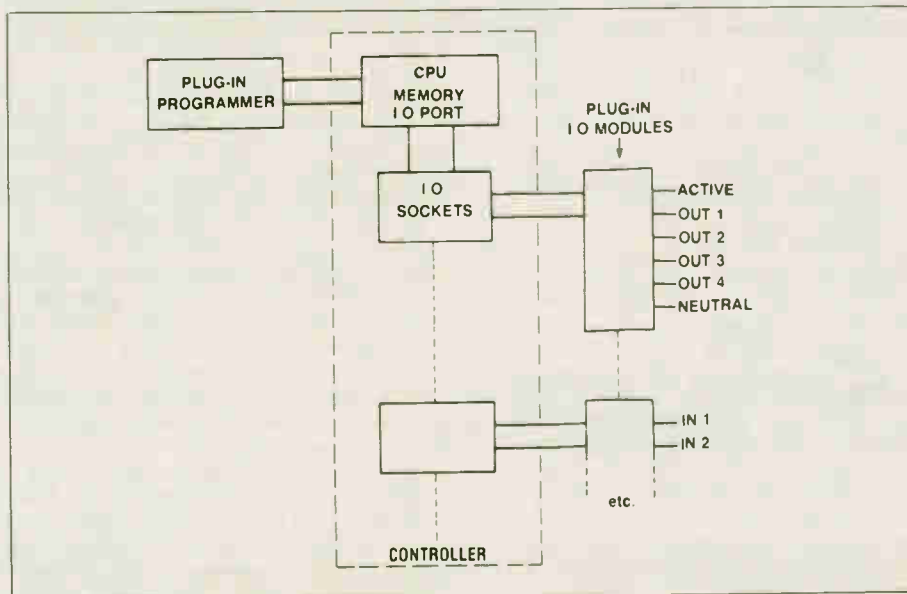


Fig. 3b. A typical P.C. used in practice.

## Subscribe now to Computing Now!

Computing Now! is from the publishers of Computers in Education and Electronics Today and offers full coverage of what's happening in Canadian microcomputing. Get the most out of your micro with:



### Listings!

From the CP/M to MS DOS; programs for business use or just for fun.

### Reviews!

The newest computers, the latest peripherals. Software, book reviews, and interesting gadgetry.

### Programming!

Articles and discussions on how to solve those programming bottlenecks.

### Systems!

If you're looking for a business system, you'll find information that lets you find the most efficient, most economical equipment for your needs.

### Subscribe now:

\$14.95 for one year (12 issues) or \$27.95 for two years (24 issues).

(Time Limited Offer)

# Computing Now!

1300 Don Mills Road,  
Don Mills,  
Toronto, Ontario  
M3B 3M8  
Telephone (416) 445-5600

## Designer's Notebook

troller revolutionized industrial control by being able to have its operation specified by a program.

The transition to using the new controllers was aided by using a programming language already understood by the plant electrician and engineer (relay ladder diagrams).

These days, controllers can replace everything from simple relay circuits to sophisticated process control equipment and, in addition, have new capabilities such as being able to accept analogue inputs, provide analogue outputs and carry out closed loop control. Other invaluable features include the ability to communicate with other P.C.s and with computers over long distances and under adverse conditions with or without separate intelligent data handling equipment.

It's probably not hard to guess that the introduction of P.C.s had something to do with the microprocessor revolution. Basically, a P.C. is a robust microprocessor-based unit which uses memory to store instructions specified in a simple ladder logic programming language. When running, it monitors the conditions of its inputs to provide outputs by implementing logic, sequencing, timing, counting and arithmetic functions.

### Architecture

Fig. 3a shows the block diagram of a typical P.C. The important sections are the CPU/memory, the programmer and the I/O modules (signal conditioners). These may all be contained in the one unit or, for added flexibility, may be available as separate units. In the latter case, the CPU/memory unit usually includes panels of sockets for the I/O modules to be plugged in. This allows any combination of inputs and outputs to be set up (only limited by maximum number possible for that particular P.C.). Let's look at each section in turn to better appreciate the operation of a P.C.

#### 1) CPU

The CPU is actually the "brains" behind the controller. In many P.C.s it is a standard microprocessor such as the Z80A, 6502 or 6800 (some manufacturers, though, use chips specially designed for logic decision making). With only a few exceptions, all the CPUs are either 8- or 16-bit devices.

The CPU, memory and I/O port form the heart of the unit. THE programmer and signal conditioners are usually external units which are simply plugged in as required. Figure 3b shows the arrangement of a typical unit used in practice. The programmer and I/O modules are discussed in the next two sections.

The controller has two modes of operation: PROGRAM and RUN, usually selected by a slide switch or, in some cases, a key-operated switch, making the unit tamper-proof. Programs are entered whilst in PROGRAM mode, which also offers a complete range of editing facilities (we all make mistakes). These include inserting and

deleting entries, finding a particular entry, changing parameters of timers and counters etc. Once programmed, it's possible to test the operation by plugging in a test panel made up of switches and indicator lights and going through all input combinations.

Alternatively, most P.C.s implement the "force" function. This allows the operator to force inputs and outputs ON and OFF under software control whether or not there are any inputs or outputs actually connected. Its main use, though, is to aid in troubleshooting.

Once programmed and checked, the unit is simply left in RUN mode to control the equipment it becomes part of. Obviously, there will be times when power failures will occur and, as every computer buff knows, static RAM loses all its information if this happens.

The problem is overcome in P.C.s by three methods. Firstly, internal static RAM always has battery backup. This, however, is not usually a permanent arrangement. It is used when the program is first loaded and de-bugged. If all is well, the program is then copied into EPROMs, which plug into the CPU unit. This provides the permanency required by the controller. If any changes are required, these are made in RAM and copied into the EPROMs after erasing the original program.

The third and latest development is to use EEPROMs (Electrically Erasable PROMs) to hold the program. These don't need a UV source for erasing old information and allow changes to be made relatively quickly.

In RUN mode, the CPU performs a number of functions. Firstly, it scans the inputs and loads their status (1 for ON, 0 for OFF) into a temporary store. Also in this store are the outputs: the results of the Boolean, arithmetic and other operations. These are output to their appropriate output modules. Next, the CPU traverses the stored program line by line and logically or arithmetically combines inputs and outputs as specified by the program to produce new outputs, which are placed in the temporary store. The cycle then repeats.

Other functions which the P.C. implements are timers, counters, master control relays, drum controllers, etc. These are all implemented in software and, as mentioned before, will not be treated here in any depth.

#### 2) The programmer

There are basically two types of programmers available with P.C.s: handheld programmers and video programmers. The cheapest is the handheld programmer and is most often used with small P.C.s. Its appearance is similar to that of a calculator and has a display (LED or more recently, LCD) and a sealed keyboard to stand harsh industrial conditions (see Fig. 4a). It is plugged into the controller either directly (that is, it physically mounts into a recessed area on the controller) or via a cable of some sort.



# NEW!

# Satellite Communications Training from NRI!

Move into commercial satellite communications and home satellite TV with NRI's latest training breakthrough

Explore Every Aspect of Satellite Transmission and Reception As You Assemble, Install, and Train With the Complete TVRO System Included in Your Course

With today's satellite technology a call to Paris is as clear and as easy to make as a call next door . . . executives use video conferencing to "meet" without leaving their offices . . . simultaneously, a billion people witness a single event (a soccer game, an inauguration, a benefit rock concert) . . . and scientists explore the mysteries of outer space without leaving their labs.

These amazing applications of satellite technology have opened up opportunities for the technician trained to install, maintain, troubleshoot, and repair satellite communications equipment.

## Home Satellite TV is Just at the Start of Its Explosive Future

In suburban backyards and alongside country farmhouses, home satellite TV systems are springing up all across the country.

Already there are over a million TVRO (Television Receive-Only) systems in place in North America, and experts predict that by 1990, a remarkable 60% of all homes will have a satellite dish.

## New Jobs, New Careers for the Trained Technician

NRI's new training prepares you to fill the increasing need for satellite communications technicians.

As an NRI-trained technician, you can concentrate on consumer-oriented TVRO equipment or use your NRI training to build a career servicing the larger commercial or military equipment used to transmit and receive voice, data, and video signals.

## NRI Brings Satellite Technology Down to Earth

Only NRI has the resources and the skills necessary to transform today's most sophisticated technology into understandable, step-by-step training.



NRI trains you thoroughly in basic electronics, communications, and television principles. Using the remarkable NRI Discovery Lab<sup>®</sup> and your digital multimeter, you perform critical experiments, tests, and measurements. Then, using your NRI Antenna Applications and Design Lab, you assemble and test various types of antennas and matching sections.

You then concentrate on both commercial and consumer satellite earth station equipment, putting theory to practice as you assemble and install the complete satellite antenna system included in your course.

## Your Home Satellite TV System Brings Theory to Life!

Your Wilson TVRO system comes complete with 5' parabolic dish antenna system, low-noise amplifier (LNA), down converter, receiver, low-loss coaxial cable, and even a permanent polar mount.

By training with an actual TVRO system, you'll come to understand first-hand the function and operation of a satellite earth station. And once completed, your TVRO system will provide the best

television entertainment available—direct from the satellite to your home.

## Train the Uniquely Successful NRI Way

It's hands-on training, at home . . . designed around the latest state-of-the-art equipment. You discover by doing . . . and you do it at your own pace.

And built into your NRI training is the enormous experience of our development specialists and instructors, whose training skills and personal guidance are available to you on a one-to-one basis.

## Make Your Move Into the Future Today! Send for Your FREE NRI Catalog

Only NRI can train you at home for an exciting and rewarding career as a satellite communications technician. But now is the time to act. Return the post-paid card to us today. You will receive your 100-page NRI School of Electronics catalog free. It details our training methods and materials and our more than 70 years of successful innovation in hands-on career training. (If the card is missing, write to us at the address below.)

**NRI** SCHOOLS

McGraw-Hill Continuing Education Center  
330 Progress Avenue  
Scarborough, Ontario M1P 2Z5  
or telephone 416-293-8787

We'll give you tomorrow.



All Equipment Included With Your Training.

Some controllers have built-in programmers but in many cases this is not required. The reason is that once the controller is programmed and fitted beside the equipment it controls, the programmer is of no further direct use. It can, however, be carried by the plant engineer and plugged into a controller to modify the program, monitor inputs, outputs, internal timers, counters or even change variables or conditions of inputs and outputs while the controller is running.

Note that if numerous controllers are used on the plant and if all are identical, then only two or three programmers need be purchased. This reduces the overall cost of the system since not all controllers will require programmers simultaneously once commissioned.

The most sophisticated method of programming and fault-finding is by use of a video programming unit. These may be standard intelligent VDUs or may be a small VDU built into a small unit which has special keys in place of the regular keyboard (see Figure 4b). This type of programmer draws ladder diagrams on the screen as the controller is programmed and if a hard copy is required, a printer can be connected to the system.

When troubleshooting or placed in RUN mode, controller operation can easily

be monitored since paths and coils which are energized are shown by thicker lines (intensification of light on a VDU or double lines in printouts). Figure 4c gives an example of a typical printout. Of course, this type of programmer is much more expensive than the other.

#### c) I/O modules

These modules provide the link between the controller and the outside world. The equipment connected to a P.C. will almost certainly require different operating voltages. In fact in practice, most outputs will need to control much higher voltages and currents than the controller will supply. Inputs may also be high voltage ac an/or dc signals. In all cases, isolation from the controller circuitry is required. This is achieved easily by means of opto-couplers, but sometimes in the case of outputs relays are used. Fig. 5a gives some examples of I/O modules.

Smaller P.C.s have a small number of inputs and outputs which come built-in. These are isolated internally and can operate devices rated up to 240VAC. Extra terminals are provided on the I/O strip (similar to a terminal strip) to which an external power supply can be connected for powering each particular device (see Figure 5b).

The outputs and inputs are usually grouped in pairs or fours so that different

voltages can be applied to each group. Larger P.C.s simply provide panels of sockets into which input and output modules are plugged. Each module provides four inputs or outputs, each with an individual indicator lamp, fuse and opto-isolator. This provides the greatest flexibility since:

\* only the number of I/O modules actually required need be purchased (plus spares).

\* a blown module can be easily swapped without switching off the entire system.

\* number of I/Os can be increased up to the limit of the machine by using expansion modules which hold extra I/O modules.

Typical inputs to a P.C. include pushbuttons, limit switches, sensors, flow switches, controllers, thumbwheels, LDRs and other optical devices, vacuum switches. Some outputs are solenoid coils, motor starter coils, indicator lights, alarm circuits, etc.

#### Overall Advantages

1. Size: A P.C. can be housed in an enclosure which is substantially smaller than that required for its relay counterpart.
2. Reliability: The P.C. has no moving mechanical parts to wear out and fail. With

## When Accuracy Counts... You Can Count On Us... Since 1977

### THE BRUNELLE Commander SERIES

#### Model 2200 - Digital Capacitance Meter



The Digital Capacitance Meter you've been waiting for... at the price you've been hoping for!

#### Featuring

- Reading Rate: 0.5 seconds
- Overrange Indication: indication of "1"
- Test Voltage: 3.2 volts peak maximum "+" input terminal voltage is always higher than "-" input terminal
- Power Requirement: 9V battery
- Battery Life: Up to 200 hours typical with Alkaline. Up to 100 hours typical with Zinc-carbon.
- Accessories Supplied: Test Lead (1) spare fuse (1), instruction manual (1) 9V Battery (Zinc-carbon).

**\$99.95**  
FST Included

#### Model 4060 - Digital Multimeter



The Multimeter you've been waiting for... at the price you've been hoping for.

#### Featuring:

- Handheld 7-function, 35 ranges with 200 uA, AC and DC, Hi-low ohms diode check.
- Built-in transistor test function.
- Overload protection, 2 amp fuse protects all meter ranges.
- Safety designed input jacks and test leads, tilt stand for bench use. Easy external battery access.
- Calibration certificate traceable to NRC supplied with meter.
- 1 year parts/labour guarantee.

**\$89.95**  
FST Included

• Quality + Price + Service = **BRUNELLE**



**Brunelle Instruments Inc.**  
73-6th Range South  
Saint Elie D'orford, Quebec, J0B 2S0  
Tel: 1-819-569-1408 Telex: 05-836266

Mail Order: Certified Cheque, Money Order, COD's FOB  
St-Elie, Quebec Residents add 9% P.S.T.

OR

**CALL COLLECT: 1-819-569-1408**



electronic systems, most failures occur during manufacture and testing.

3. Flexibility: The P.C. is ideally suited for control systems whose control schemes may be revised later. Changing a hand-wired relay system often requires long downtimes and high labour costs. By contrast, changing the control system in a P.C. most often only requires the changes to be entered with the programmer.

4. Ease of installation: With a P.C. minimal panel wiring is required for installation in the plant.

5. Simple programming: Most P.C.s are designed to be programmed in ladder logic, a language normally understood by the users.

6. Faultfinding: Faultfinding is relatively easy with the use of ladder diagrams and input/output module indicators.

7. Hostile environment: P.C.s are specifically designed to operate in industrial environments; e.g., a typical operating temperature range could be 0-60 degrees C.

8. Cost: Overall costs of P.C. schemes are less than relay schemes.

9. Range of P.C.s available: Nearly 40 manufacturers in the USA alone produce P.C.s. They vary in size from eight I/Os to 4096!

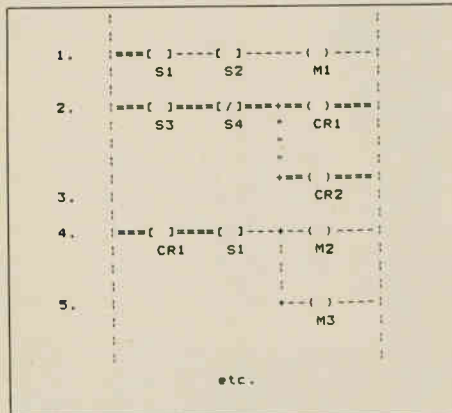


Fig. 4c. Example of a P.C. printout.

Normally open contacts (NO)  $\text{||}$   
 Normally closed contacts (NC)  $\text{||/}$   
 outputs  $\text{()}$   
 active path  $\text{=====}$   
 inactive path  $\text{- - - - -}$

### Programming Example

Just to complete the discussion of P.C.s, let's look at some very, very simple programming examples.

Example 1: Refer to the example given in Figures 2a and 2b. Since the relay ladder diagram is already given, the controller can be programmed without further simplification. Using a typical programming language we obtain:

```
START X1
AND NOT CR1
OUT Y1
START X2
OUT CR1
START X1
AND CR1
```

```
OUT CR2
START CR2
OUT Y2
END.
```

Note that START begins each new line of the program. Inputs and outputs can be represented by X and Y and control relays by CR.

When switches S1, S2 and motors M1 and M2 are connected to the P.C. they connect to I/O terminals X1, X2, Y1 and Y2, respectively. Finally, an ENTER button is usually pressed after each line of programming. Simple! Saves interconnecting relays.

Example 2: Refer to Fig. 4c.

```
START X1      OUT CR2
AND X2        START CR1
OUT Y1        AND X1
START X3      OUT Y2
AND NOT X4    OUT Y3
OUT CR1       END.
```

Example 3: Assume we have a room with two doors and one light in the middle of the ceiling. Each door has a switch which operates as follows: the light can be switched ON and OFF by either switch. For example, the light can be switched ON when you enter door 1 and switched OFF as you leave door 2. The same applied if you reenter via door 1 or door 2.

Those of you into logic will recognize this as the EXCLUSIVE-OR function. If we start with both switches in the UP position, the light will be OFF. If the room is entered via either door and the switch operated, the light will come ON.

In this condition, one switch will be in the UP position and the other DOWN. When leaving, to put the light OFF, either both switches will be in the DOWN position or both will be UP (depending on which door is used). To put this into digital form, let's call the switches X1 and X2 and the light Y1.


If a switch is put in the UP position then it is represented by barX1 (or barX2). If in the down position, then it becomes X1 (or X2, depending on which switch we're talking about).

For the light to come on, we can deduce from the previous paragraph that one switch must be DOWN and the other UP. If both are UP or DOWN then the light will be OFF. In other words:

$$\text{light ON} = X1.X2 + \bar{X1}.\bar{X2}.$$

This is read as "the light will be ON if X1 is DOWN AND X2 is UP OR X1 is UP AND X2 is DOWN". The ladder diagram and program are:
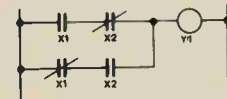
```
START X1      OR MEMORY
AND NOT X2    OUT Y1
START NOT X1  END.
AND X2
```



Note how two lines are started to give the two parallel paths. When the second path is started, the first is stored in memory (like a stack) since it wasn't completed. The OR MEMORY instruction ORs the current line with the stored line. ■

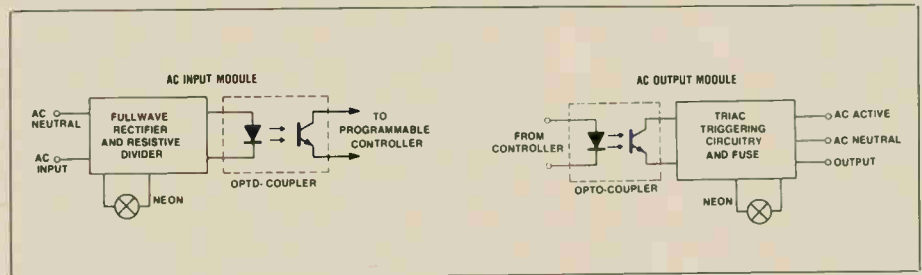


Fig. 5a. Block diagrams of typical I/O modules.

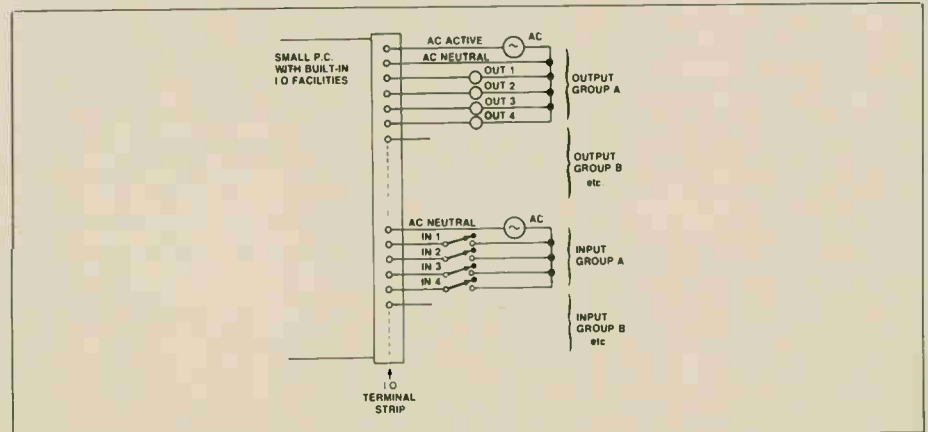


Fig. 5b. Example of I/O connections for a small P.C.

# Home Computer Control

---

*Controlling the home with the computer, that is. Dust off the micro and put it to work.*

---

*By Bill Markwick*

ONCE you get bored with the video games, or if you think a few hours a week with a word processor lets the computer go to waste, you can always get more out of your micro by adapting it to home control. The micro is a natural for this; it can monitor the state of its ports with the appropriate software and then activate other ports via an interface. It can wake you up, turn on the light, start the coffee, keep an eye out for burglars, run the heating system and take the dog out for its morning walk. Well, perhaps I exaggerate a bit...

## The Micro

Any micro with inputs and outputs will do, of course, if you want to build a system from scratch, but in that case you either need a large reference work or you don't need me at all. In most cases, the best route to follow is to look into the available commercial interface units; this saves you from reinventing the wheel. After all, the majority of electronics involved is simply mating I/O ports to sensors or relays. Mind you, this might be fun, and there's an idea for a future ET project. Hmmm.

The reason that most commercial suppliers specify particular computers is not that they work better, but that the equipment can be standardized for the I/O connections and the software can be made compatible. For this reason you'll generally find that home control systems are designed for popular micros such as the Apple, C64, Mac or IBM.

The job of the micro in all this is straightforward enough. Under control of the supplied software, the computer, timed by its own clock, sends out signals at predetermined intervals to start or stop some particular household function. In the more elaborate systems, feedback is used so that the computer has some idea what's going on and doesn't just blindly start up the power saw when you're sitting on it (not a good example, I know).

## Transmission

There are two basic types of transmission, one-way and two-way. The two-way may also be known as a feedback or full-duplex system. The two methods are further divided by the method of getting the signal in or out; the two most popular systems are hard-wiring and RF remote control via power lines.

The one-way system is appealing because of its simplicity and low cost. The computer counts down to a specific time like a smart alarm clock, and then makes a particular port line go high or low. The interface translates this into an on or off code which is picked up by an appliance controller, either by direct dedicated wiring or by decoding a digital signal sent over a common carrier. The disadvantage to the one-way system is that the computer is largely in the dark as to the state of the loads connected to it; it never finds out whether the furnace actually did bring the temperature up or not.

The two-way system is a bit more involved, but it begins to bring a bit of in-

telligence into things. The user can now install more sophisticated sensors, letting the computer know whether some desired function has actually happened or not. In some cases, only a simple yes/no is required, and in others a wide-range analog signal may have to be sampled and converted to a digital value which the computer can read, initiating action or not under control of the software.

## A One-Way System

X-10 Home Controls was formerly known as BSR X-10, and claims to be the leading manufacturer of home control units. Besides the X-10 systems which they market, they also make equipment for other companies such as the Radio Shack 'Plug 'n Power' and Sears; the private-label units are compatible with the X-10.

X-10 makes a computer interface called







the 'Powerhouse', consisting of a small panel with eight switches, an interface cable, and software on a disk. At present the system is available for the Commodore 64 and the Apple IIc/e computers; by the fall of this year they'll have systems for the Macintosh and the IBM PC. The appeal of the Powerhouse system is the simplicity of installation; no special wiring of the house is required. The switch unit consists of a microprocessor (an 80C48) with the necessary ROM and RAM and a 100-hour battery backup. Information from the software is read out of the computer via the RS232C port, processed, and converted to a high frequency signal which can be impressed on the power wiring. Although they didn't give exact figures on the frequency, most RF remote systems use a signal between 100kHz and 200kHz.

Electronics Today August 1986

The low power used (in the milliwatt range) means that the signal is unlikely to cause any interference with domestic electronic equipment, and the signal is unlikely to survive outside the house wiring, though it's theoretically possible that some interaction could happen if your next-door neighbour has an X-10.

At each location where you'd like to control an AC appliance, you install an X-10 module. For simple on-off or dimming functions, this consists of a box that plugs in between the outlet and the appliance. The RF signal is decoded by a demultiplexer, and the box performs its function whenever it sees its preset code. The modules can run incandescent lamps, small motors and so on.

If you want a small, self-contained system, the control centre of the Radio Shack version has 16 pushbuttons to control 16 modules, and presently lists at \$49.95 plus \$29.95 for each module. If you'd prefer computer control, allowing you to add more complex timing and graphic displays, the Powerhouse can control up to 256 modules and display their state on a graphic representation of the house which appears on your computer monitor. There are also eight pushbuttons for instant manual control. The control unit, software and interface cable is under \$200 in Canada.

Aside from the convenience of having the lights come on and the coffee perking in the morning, the units are ideal for timing all the lights in the house if you're away. Imagine a computer glitch that makes all the lights in the house go on and off at random every two seconds - that should confuse burglars.

In the works is a setback thermostat

that can be controlled by the X-10, and a telephone responder which will allow you to phone home and issue commands to the computer. If a burglar is in the house while you're in Tasmania, you can at least get the coffee perking for him.

### Going The Other Way

The X-10's function is to send signals to a module to control some function. If you'd like a simple system that works the other way, the PCI Sentry from Precision Controls Inc. is a receiver unit which can monitor up to 99 remote sensors. The remote sensors apply their RF signal to the power line in much the same way as the X-10 (but in the opposite direction).

Each transmitter in the system has a two-wire connection to detect the closure of any type of sensing switch, DIP switches to set the desired code, and a standard wall plug (similar to an AC adapter plugpack). When the sensing contacts close, the preset code is detected by the receiver which flashes the number of the transmitter on its front panel display. A relay is also provided on the receiver for activating various bells and whistles.

Two models are available: the Model 100 accepts up to 99 transmitters, and the Model 10 accepts up to nine. In addition, Call Buttons are available for paging the central receiver.

The company also supplies a range of 400 types of switches for monitoring pressure, immersion, air and liquid flow, voltage, noise, etc. The manufacturer claims that their 'random phase digital circuitry' is not affected by noise on the power lines and will not interfere with other equipment.



Fig. 1. The Powerhouse computer interface controls up to 256 appliance modules with a signal sent over the power wires.

## Sensors

If you're concocting your own computer monitoring system, either for the home or industrial applications, much of the work of designing the interface is already done for you by the Sensatrol system. It consists of a small control box with eight differential-input voltage-monitoring inputs and eight control outputs.

Connection to the computer is made via an RS232C port, and the controller responds to commands in BASIC, making

it compatible with any micro. When BASIC sends it a PRINT statement, an input line is selected, read at two samples per second, and the result transmitted back. The manufacturers claim that it has the resolution of '4 1/2 digits' or '40,000 sample points'. This is slightly better than the resolution you'd get from a 15-bit A/D converter (which uses 32,768 sample points per measurement), and should be more than adequate for the majority of uses. The resolution for measuring AC or

DC sensor signals is 100uV, and accuracy is 0.01 percent for DC and 0.1 percent for AC. Audio signals, for instance, can be sampled over a 66dB range.

When the software decides that something should be done, one or more of the seven outputs can be activated, controlling just about anything via 3-amp relays or optoisolated 3-amp DC power controls. Sensors are available for measuring just about everything: temperature, pressure, light, noise, humidity, flow rates, electrical signals of all types, etc.

Although the Sensatrol requires special wiring, it has the advantage that only an RS232 link is needed between the unit and the computer, and multiple control units can be connected to the same wire. Each control responds only to its own presettable code. This allows you to place the control units in locations that will minimize the amount of sensor wiring required.

In Fig. 4, traffic noise has been monitored with a microphone preamp and a Sensatrol. A Radio Shack Model 100 portable computer recorded the readings under control of custom-written software. As you can see, the vertical axis has been converted to logarithmic form (decibels) by the software. Other measurements which were recorded with the same system included inside/outside temperature, humidity, light levels, windspeed, etc.

## Butler In a Box

For those of you who are irritated by synthesized voices coming from less-than-useful gadgets, Simon the Electronic Butler at least has a purpose. It can store up to 15 numbers; a voice-recognition circuit will then make it control a particular light or appliance when it hears a number, and it can also recognize up to four different voices. It can also speak short phrases, such as a request for identification, and best of all: the voice is a real prerecorded one rather than synthetic.

Simon consists of a 64K computer with most of the processing done by software rather than expensive dedicated chips. It can be voice-activated as described, controlled by switches on a concealed front panel, or programmed with an automatic timer. Other features include an infrared intrusion alarm (which can be turned off when it hears the right identification) and a telephone speaker-phone function. The Canadian price tag is \$2195.

Although Simon might appear to be an expensive frivolous toy, but the usefulness for the handicapped shouldn't be underestimated. Monsanto Canada presented one to the Ontario March of Dimes, whose director said that Simon 'could help a disabled person lead a more nearly normal life'.

**EXCLUSIVE CANADIAN DISTRIBUTOR**


**UNITECH KEYBOARDS**  
Use West German CHERRY® Mechanical Contact Switch

**BUDGETRON INC.**  
IMPORTER DISTRIBUTOR  
Mississauga, Ontario, Canada

---

### K-151 KEYBOARD

AT Layout For IBM™ PC/AT And Compatibles




- Large size Return, Shift and Control Keys
- Sturdy Metal Base
- Large "+" Key on Separate Numeric Pad

---

**NEW**

### K-155 KEYBOARD

Intelligent Built-in Auto Switch To Run IBM™ PC/XT, PC/AT and Compatibles




- Additional Cursor Pad
- 10 Wide Function Keys
- 95 Keys
- New Ergonomic Design
- Versatile Keyboard

---

### K-150L KEYBOARD

IBM™ Selectric Layout For Easy Word Processing



- Additional Enter Key
- Direct Replacement for IBM™ PC XT
- The Most Cost Effective and Reliable Keyboard

**BUDGETRON**  
IMPORTER DISTRIBUTOR **INC.**

1320 Shawson Drive, Unit 1, Mississauga, Ont. L4W 1C3

**Tel: 416-673-7800 Tlx: 06-968080 FAX: 416-673-2679**

\*IBM is a registered trademark of IBM Canada Ltd.



**KEYBOARDS**

- (A) 5150 Style, 83 Keys, Std Layout, uses the long lasting Cherry Sw, IBM® Comp. . . . . \$109.00
- (B) 5151 Style, 105 Keys, Keytronic 5151 layout, Cherry Sw. IBM® Compatible . . . . . \$139.95
- (C) 5160 Style, AT® compatible, with 83 keys by Cherry, 5150 layout . . . . . \$159.95
- (D) 5161 Style, AT com, but 5151 layout . . . . . \$189.95
- (E) AES DATA Keyboard, Par ASCII and Serial but not IBM. Runs Apples® very good general use ASCII keyboard . . . . . \$ 24.95
- (F) APPLE NUMERIC BASIC FUNCTION, II+ . . . . . \$ 69.95
- (G) APPLE STANDAR BASIC FUNCTION, II+ . . . . . \$ 69.95
- (H) APPLE DETACHED II+, NUMERIC FUNC. . . . . \$149.95
- (I) FOX 2001 Internal keyboard, Iie . . . . . \$ 69.95
- (J) FOX 2001 External keyboard, Iie . . . . . \$139.95

**POWER SUPPLIES**

- (A) 150 Watt, Back/Side Switch, with +5v-15Amp, +12V-5.5Amp, -5,12V-½Amp, A good quality, hydro approved unit. . . . . \$139.95
- (B) 150 Watt, CSA approved unit, for the very highest system reliability, +5v-15Amp +12v-5.5Amp, -5,12V-½ Amp, Side Sw . . . . . \$159.95
- (C) APPLE II+, or FOX 2001 Iie, power supply, +5v-5Amp, +12v-2.5Amp, -5, 12V-½Amp Very high quality . . . . . \$ 79.95
- (D) OPEN FRAME Northern Telecom switcher as widely sold, +5v-4A, ± 12V-1Amp and -5 at 1 Amp, very good deal . . . . . \$ 18.95  
Power cord for (D) above . . . . . \$ 3.50
- (E) IBM OPEN FRAME, came from the defunct NCR compatible, +5v-7Amp, +12v-3Amp, -5, 12v-½ Amp, runs the whole thing . . . . . \$ 59.95

**V-20 CHIP**

You may have heard of the NEC V-20 chip. It is an upgraded 8088 that can run programs up to 50% faster (depending on code). It also can run 8080 code, allowing it to be used for 8080 development. Especially good for Video when using code using it's features. A hot and hard to get CHIP at (5 Mhz) . . . . . \$24.95  
Faster version runs at 8 Mhz . . . . . \$44.95

**SOFTWARE**

- Copywrite . . . . . \$59.95
- Disc Explorer . . . . . \$84.95
- Zero Disc . . . . . \$84.95
- Turbo lightnin . . . . . \$99.95
- Turbo Graphics . . . . . \$54.95
- Sidekick . . . . . \$89.95
- Turbo Pascal . . . . . \$69.95
- Turbo Tutor . . . . . \$34.95
- Turbo Toolbox . . . . . \$59.95
- Turbo Gamworks . . . . . \$64.95
- Raspberry**
- Canadian Tax . . . . . \$59.95
- Microsoft Word . . . . . \$389.00
- Word Perfect . . . . . \$389.00
- PC MOUSE . . . . . \$245.00
- Microsoft Mouse . . . . . \$229.00
- D BASE III . . . . . \$389.00
- D BASE III+ . . . . . \$575.00
- Framework . . . . . \$389.00
- Crosstalk . . . . . \$189.00
- ASCII Express . . . . . \$215.00
- Norton Utilities . . . . . \$109.00

**CABLES**

- Disc Drive cable (3 Con & twist) \$12.95
- IBM Parallel printer cable . . . . . \$14.95
- IBM serial printer cable . . . . . \$14.95
- IBM 6" Keyboard extension (curly) . . . . . \$ 9.95

**Toll Free Orders Only**  
**1-800-387-1385**  
(416) 928-2161

**CASES**

**XT® CASE WITH AT® LOOK**

- (A) Standard 8 slot hinged case XT® case. Fits side or back power supply (Specify) Has much heavier metal than competitors for stability, takes 1-4 ½ sized drives and fits very well . . . . . \$79.95
- (B) Same as above, but the front looks like an AT case, with switch for KB and LEDs on front (picture) . . . . . \$89.95
- (C) ABS numeric case for II+ . . . . . \$49.95
- (D) ABS case for FOX 2001 . . . . . \$49.95
- (E) Hard drive box, holds 1 full sized or two ½ sized hard drives, good for portable tape backups as well 40 Watt power supply for the above . . . . . \$59.95  
60 Watt power supply for the above . . . . . \$79.95

**QUME DRIVES**

- (A) Yes we have the drives that IBM bought for their own use, complete with the IBM® logo right on them. Brand new DS/DD ½ Height drives . . . . . \$129.00
- (B) Panasonic drives, very quiet, as above but no logo, DS/DD ½ Height . . . . . \$165.00
- (C) Toshiba drives, noiser than above, but cheaper, no logo, DS/DD ½ Height . . . . . \$159.00
- (D) Seagate 20 Meg hard drive with Controller, ½ height . . . . . \$699.00
- (E) Seagate 20 meg drum only . . . . . \$549.00
- (F) Controller only . . . . . \$169.00

**GRAY SCALE ADAPTER**

As you know the IBM colour graphics card does not look very good on a monochrome monitor. This is because often two colors look the same on monochrome so you cannot read red print on a blue background or some such. This little gray scale proportionately scales each color into a different intensity allowing easy viewing on amber, green or white monitors. We sell it as a kit for only (with cable) . . . . . \$19.95  
or wired and tested (with cable) . . . . . \$24.95

**BOOKS**

- Running MS DOS . . . . . \$26.95
- PC DOS & MS DOS . . . . . \$25.95
- Everyman's Data Base Primer . . . . . \$28.75
- Advanced Programmers Guild . . . . . \$38.00
- Using Turbo Pascal . . . . . \$28.80
- Variations in "C" . . . . . \$27.50
- Lotus guild to Learning 123 . . . . . \$28.95
- Intr to Turbo Pascal . . . . . \$21.00
- 1,2,3 Financial Macros . . . . . \$25.95
- 1,2,3 Macro Library . . . . . \$25.95
- MS-DOS Users Guide . . . . . \$26.50
- Your IBM PC . . . . . \$27.10
- Programming in "C" . . . . . \$36.10
- Beneath Apple DOS . . . . . \$28.70
- Apple Works . . . . . \$18.00
- The Lotus Guide to Learning Symphony . . . . . \$32.15
- IBM PC Users ref man . . . . . \$32.95
- Apple Iie Tech ref man . . . . . \$32.95

**MODEMS**

- GVC INTERNAL 300/1200 . . . . . \$325.00
- GVC EXTERNAL 300/1200 . . . . . \$325.00
- SMARTMODEM 300 . . . . . \$249.00
- SMARTMODEM 1200 . . . . . \$649.00
- SMARTMODEM 2400 . . . . . \$995.00

\* Note: The terms, IBM, XT, AT, PC are registered trademarks of International Business Inc.

**WIRED CARDS FOR IBM®**

- (A) 384K RAM card, ¾ size for 384K of 64K DRAM. Wired and tested with OK . . . . . \$ 79.95  
Bare PCB and assembly data . . . . . \$ 19.95
- (B) 576K RAM card, ¼ size for 576K of 256K DRAM. Wired and tested with OK . . . . . \$ 59.95  
Bare PCB and assembly data . . . . . \$ 14.95
- (C) KRAM card, a clone of the JRAM-2 card for 2 MBYTE of 256K DRAM. Runs all software 100% compatible, W & T with OK . . . . . \$169.95  
Bare PCB and assembly data . . . . . \$ 34.95
- (D) COLOR GRAPHICS, A PERSYST clone, runs all software and our one has grey scale O/P & color comp and TTL RGB, W & T . . . . . \$125.00
- (E) MONO GRAPHICS, A hercules clone, runs all software and has parallel centronics printer as well, W & T . . . . . \$139.95  
Bare PCB and assembly data . . . . . \$ 24.95
- (F) 384K/MULTIFUNCTION card, exact copy of AST SIXPACK, Ser, Par, Clock, Cal, Game I/O with software and ports, W & T, OK. . . . . \$169.95  
Bare PCB and assembly data . . . . . \$ 24.95
- (G) DISC CONTROLLER, runs 1-4 drives has newest 9216 data separator with cables wired and tested . . . . . \$ 59.95  
Bare PCB and assembly data . . . . . \$ 12.95
- (H) DISC + I/O Card, A very nice new card with disc controller plus AST sixpack on board without any RAM. Ideal for the new 640K motherboards, Ser, Par, Clock, Cal, Game, software and ports, W & T . . . . . \$189.95
- (I) 10+2, An AST SIXPACK with no RAM, has Ser, Par, Clock, Cal, Game and software and ports, W & T . . . . . \$129.95  
Bare PCB and assembly data . . . . . \$ 19.95
- (J) PRINTER, Centronics, Std parallel printer, ¼ size, W & T . . . . . \$ 49.95  
Bare PCB and assembly data . . . . . \$ 12.95
- (K) SERIAL, std serial card, two ports ½ sized, W & T . . . . . \$ 44.95  
Bare PCB and assembly data . . . . . \$ 12.95
- (L) CLOCK/Calendar, A ¼ sized card for these two functions, with battery . . . . . \$ 49.95  
Bare PCB and assembly data . . . . . \$ 12.95
- (M) GAME, card, A ¼ sized card with 2 std game ports on it, W & T . . . . . \$ 39.95  
Bare PCB and assembly data . . . . . \$ 12.95
- (N) EXTENDER, and 6" extender board for easy access for service . . . . . \$ 14.95
- (O) PROTOTYPE, full sized with all WW area and a DB25, DB9 footprint . . . . . \$ 24.95
- (P) RAM/PROTOTYPE, Full size with 256K/1M RAM area for 64K/256K DRAM at end with DB25 and DB9 footprint . . . . . \$ 29.95

**KRAM SOFTWARE**

A complete manual of operation with application notes, theory and schematic. Includes a disk of software for IBM Disk use. . . . . \$19.95  
Manual & Diskette . . . . . \$19.95

**PRINTERS**

- ROLAND
- PR1212A . . . . . \$575.00
- PR1011 . . . . . \$375.00
- PR2022 . . . . . \$645.00
- OLYMPIA
- NP . . . . . \$475.00
- RO . . . . . \$545.00

**IBM COMPATIBLE SYSTEMS**



**XT ...\$829.00**

What a deal, the nicest systems of all at the lowest price for good merchandise. The basic system has the following. For \$829.00

- 640K Motherboard
- 1 DS/DD 360K ½ Ht.DD
- 1-4 DD Controller
- Keyboard
- Colour Graphics Card
- Free software
- 256K RAM on board
- 8 XT slots
- Flip top case
- 150 Watt power supply
- All cabling & 24 hr. Test and burn-in

To upgrade the system to your choice please select from these options.

- Monochrome graphics card Add \$ 69.00
- Ser/Par/game/clock/calendar . . . . . Add \$125.00
- Printer card . . . . . Add \$ 45.00
- Serial card . . . . . Add \$ 49.00
- Second drive . . . . . Add \$150.00
- KRAM CARD, OK . . . . . Add \$179.00

**640K XT MOTHERBOARDS**

We now have several types of 640K motherboards with all the standard attributes of the "REAL" thing as well as some new ones. All have 8 XT slots, XT size, and 8087 socket and have 100% compatibility. The extra features are the use of 256K RAM to get 640K on the mother board plus the new desirable "TURBO" feature. The "TURBO" has two speeds, the basic 4.77 and either 6.67 or 8.00 Mhz. The 6.77 uses the -3 or standard 8000 chip set and RAM, the 8.00 needs the -2 high speed version. The speed advantage is the ratio of 6.67/4.77 = 1.39 or 39% faster and 8.00/4.77 = 1.67 or 67% faster, all other things being equal. Of course timing loops will be changed so that any real time output will be faster by the ratio unless the loop is fixed. The largest saving is in CAD programs with a lot of number crunching, smallest savings are disc intensive programs.

- SME-XT, wired with OK 3 hr burn-in . . . . . \$199.00
- SME-XT, wired with no IC's at all . . . . . \$ 99.00
- SME-XT, bare pcb, book parts list \$ 34.95

- TURBO 6.67 MHZ VERSION
- SME-XT A Wired, 3 Hr burn in, OK . . . . . \$229.00
- SME-XT A Wired, no IC's at all . . . . . \$129.00
- SME-XT A Bare PCB, book, parts list . . . . . \$ 39.00

- TURBO 8.00 MHZ VERSION
- SME-XT B, wired, 3 hr burn in, OK . . . . . \$249.00
- SME-XT B, wired, no IC's at all . . . . . \$139.00

All boards come with book and parts list, the wired with OK have BIOS included.

**APPLE WIRED CARDS**

- Applec card \$149.00
- 80 Column \$ 59.00
- 80 Column with soft switch \$ 69.00
- Grappler . . . . . \$ 49.00
- Cable above . . . . . \$ 19.95
- 16K . . . . . \$ 39.95
- 128K(OK) . . . . . \$ 55.00
- 128K(64) . . . . . \$ 99.00
- 128K(128K) \$149.00
- Drive Cont. . . . . \$ 49.95
- Z-80 . . . . . \$ 45.00

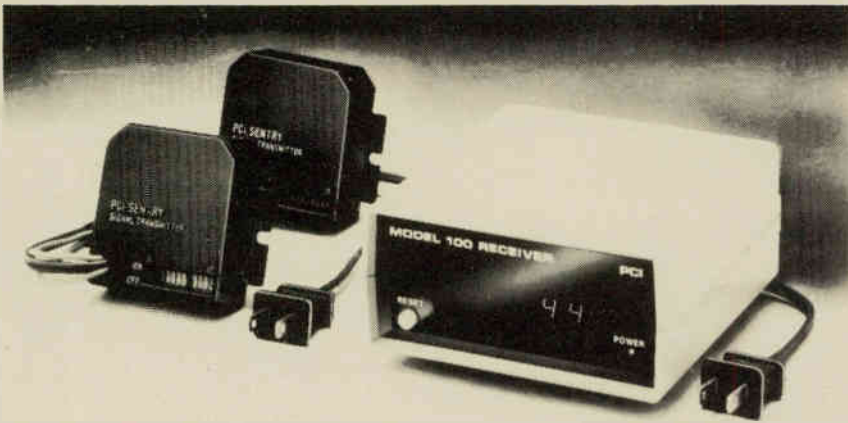


Fig. 2. The PCI Sentry is a receiver that monitors up to 99 remote transmitters for monitoring levels, flow, pressure, etc.

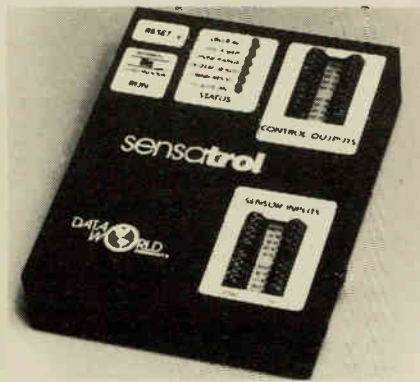


Fig. 3. The Sensatrol can accept up to eight analog inputs and outputs for sophisticated monitoring of sensors.

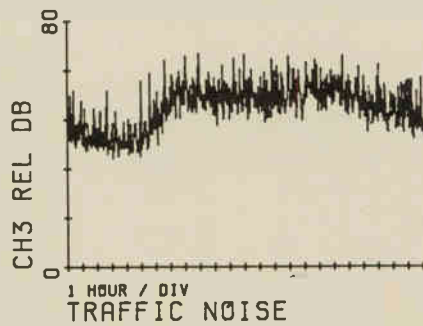


Fig. 4. Traffic noise was monitored with a mike preamp, a Sensatrol and a portable computer.

## HVAC

Heating, ventilating and air conditioning is a natural area for computer control, particularly with home systems, whose simple thermostats don't do an awful lot for energy conservation. The Hitek 3000 is a computer-controlled energy management for residential and commercial use. It uses a microprocessor for optimizing temperature, duty cycle and setback functions. The unit replaces the existing thermostat.

An EEPROM retains the heating/cooling program indefinitely in case of a power failure. The manufacturer claims savings of up to 25 percent on residential installations.

## TomorrowHouse

The TomorrowHouse system consists of a printed circuit board in a box which can mount anywhere in the house. It communicates with your micro via an RS232C link, and will display a graphic representation of the floor plan along with a readout of the state of the various things it's controlling. These include eight zones of HVAC, various dampers and registers, a



Fig. 5. Simon, the Electronic Butler with its creator, Gus Searcy.

theft-fire-smoke security system, exit lighting, up to 256 individual lights and appliances, the sprinkler system and more.

The unit has voice synthesis and can do wake-up calls, memos, etc. The program-

mable microprocessor board has a capacity of 128 SPDT relays, 22 digital channels (expandable), 29 analog inputs (also expandable), a realtime clock, battery backup and even an X-10 controller.

While the unit may run in the \$2000 area, it's said that the energy management functions will make the unit pay for itself (that's a lot of energy). Lights can come on and off when you're away, and the unit can phone for help should unforeseen things go wrong.

Not a bad gadget to have, and par-

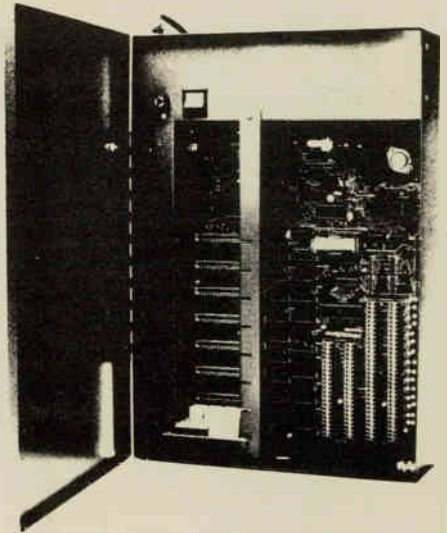


Fig. 6. The TomorrowHouse PCB in its mounting case.

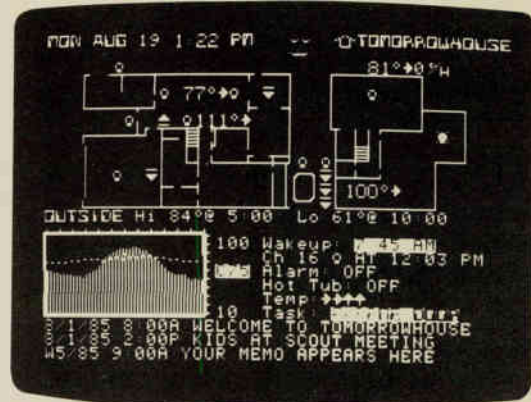


Fig. 7. A graphic display from the TomorrowHouse on a home computer.

ticularly appealing to those of us too lazy to go upstairs to turn out the closet light.

The drawback to any of the home controllers is the number of sensors you have to install, even if a lot of them can use the power lines. The TomorrowHouse, for instance, is not supposed to turn on the sprinklers during or just after a rain because it monitors soil moisture. This means a widget buried in the lawn with wires coming back to the controller. In fact, a lot of wires have to come back to the controller.



There's yet another drawback to a machine that runs everything in and around the house for you. If it decides that the sprinklers should come on because the soil is too dry, say, it removes a small chore from your life that really wasn't unpleasant. In fact, if something *really* unpleasant has to be done, standing around the back yard sweeping the hose back and forth is good for hours of very enjoyable goofing off.

And you should learn to turn off lights when you're done with them. All these systems remove something from life that shouldn't be removed...

But enough philosophy. Think how much fun one of these electronic servants could be! ■

**Powerhouse:**

*X-10 Home Controls, Inc.,  
1200 Aerowood Drive, Unit 20,  
Mississauga, Ontario L4W 2S7,  
(416) 624-4446.*

Circle No. 30 on Reader Service Card.

**PCI Sentry:**

*Precision Controls Inc.,  
14 Doty Road,  
Haskell, NJ 07420  
(201) 835-5000.*

Circle No. 31 on Reader Service Card.

**Sources:**

**Sensatrol:**

*Data World Products,  
P.O. Box 33,  
Francestown, NH 03043  
(603) 588-3746*

Circle No. 32 on Reader Service Card.

**Simon:**

*Evolution Technology,  
1155 Appleby Line,  
Burlington, Ontario L7N 3J9,  
(416) 335-4422.*

Circle No. 33 on Reader Service Card.

**Hitek 3000:**

*Servamatic Systems Inc.,  
PO Box 5114,  
2610 Crow Canyon Rd.,  
San Ramon, CA 94583,  
(415) 676-5456.*

Circle No. 34 on Reader Service Card.

**TomorrowHouse:**

*TomorrowHouse Systems Inc.,  
Suite 10,  
8291 West Minster Hwy.,  
Richmond, BC V6X 1A7,  
(604) 736-1258.*

Circle No. 35 on Reader Service Card.

**DID YOU RECEIVE  
YOUR COPY?**



This catalogue is a comprehensive description of our Almost Free Software Volumes I through VII.

If you would like a copy of this catalogue, please circle the Reader Service Card Number or mail your request to:

**Moorshead Publications  
Software Services  
1300 Don Mills Road  
Toronto, Ontario  
M3B 3M8**

Circle No. 25 on Reader Service Card

**always a head ahead**



**the innovators**

**DYNAUDIO LOUDSPEAKER  
COMPONENTS FEATURE**

- PHA cones •
- Very High Power Hexacoils •
- Magnesium Diecast Baskets •
  - Tuned Cavity Tweeter •
  - and Mid-Range Units
- Vented Centre Magnets •

**ALSO AVAILABLE**

Computer Aided Design for Enclosures and Crossovers  
Metalized Polypropylene Capacitors  
Perfect Lay Winding Inductors  
Speaker and Crossover Parts

WRITE OR PHONE FOR MORE INFORMATION  
FREE CATALOGUE AVAILABLE



**SOLEN INC**  
5940 Bergevin  
Brossard, Québec J4Z 1Z2  
(514) 656-2759

Circle No. 11 on Reader Service Card

**8088 SYSTEM \$699.00**

(Major Boards made in Japan)

- 256K Memory ● One DSDD Disk Drive
- Controller Card
- Flip-Top Case and Keyboard
- Heavy Duty Power Supply ● 180 Day Warranty

(All you need for complete system is Video Card and Monitor)



**COMPLETE 640K SYSTEM \$1250.00**

- Two DSDD Disk Drive ● Controller Card
- Colour Graphic Card or Monochrome Display Card
- Real Time Clock ● Serial, Parallel and Game Ports
- Flip-Top Case and Keyboard ● Heavy Duty Power Supply ● 180 Day Warranty

(All you need to get the system ready to use is a Monitor)

**MAIL ORDER:** Cheque, Money Order, Certified Cheque plus \$20.00 for shipping and handling. Ontario residents add 7% P.S.T. (Prices subject to change without notice).



576 MARLEE AVE. (At Glencairn Subway) Toronto, Ontario M6B 3J5  
Tel: (416) 781-3263  
In Calgary, (403) 239-1813

Circle No. 12 on Reader Service Card

**SMT Training Kit**



Design engineers and electronics technicians take note: a Surface Mount Technology training kit is now available for those who wish to keep up with the latest in component mounting technology.

The SMT2000 kit from the Vector Electronic Company of California will get you off to a good

hands-on start in SMT. Included in the kit is: over 575 SMT devices, various prototyping boards, component attachment and interconnection materials, and a comprehensive 50-page manual containing the names and telephone numbers of manufacturers and suppliers of SMT products. The

Canadian price of the kit is \$591.60

For more information on availability contact: Electro Sonic Inc., 1100 Gordon Baker Rd., Willowdale Ontario M2H 3B3. (416) 494-1555.

Circle No. 54 on Reader Service Card

The Institute of Electrical and Electronic Engineers have announced that Electronicom 87, the Canadian high-tech exhibition, will be held at the Metro Toronto Convention Centre September 28-30, 1987. The 1986 exhibition, originally scheduled for December, 1986, has been cancelled. For more information, contact the show manager at the Canadian Region, IEEE, 1450 Don Mills Rd., Don Mills, Ontario M3B 2X7, (416) 445-6641.

The Canadian government has removed the import duty from computer parts, parts of computer peripherals or accessories, hybrid transistors, linear audio amplifiers rated at less than 20 milliwatts and some other semiconductors. We have to wonder about that 20mW figure; even a 741 op amp can manage 50mW.

CanTel Inc. has introduced a data service that will allow cellular telephone customers to send or receive computer data using a mobile or transportable telephone. Data communication while travelling is made possible by automatic correction techniques to eliminate transmission errors due to radio noise or radio signal hand-off between cells. Transmission rate is initially 300 baud, with a 1200-baud service to be introduced in late 1986.

**PROBES & TEST/LEAD CLEARANCE**

Model Number	Description	Regular Price	Sale* Price
1P20	X1 Probe, 20 MHz 1.5m Long	<del>\$21.05</del>	<b>\$17.95</b>
P100	X10 Probe, 100 MHz 1.5m Long	<del>\$24.95</del>	<b>\$19.95</b>
2P150	X10 Probe, 150 MHz 2.0m Long	<del>\$26.82</del>	<b>\$18.95</b>
TL 1000	Meter Test Leads	<del>\$13.13</del>	<b>\$10.95</b>
126074	BNC-Banana Patch Cord 1.0m Long	<del>\$12.17</del>	<b>\$ 9.95</b>
126083	BNC-CROC Patch Cord, 1.5m Long	<del>\$10.74</del>	<b>\$ 8.95</b>

Prices valid on current stock only. Some quantities are limited. Sale ends June 30th 1986.

Your Canadian Coline Sales and Stocking Source.

Please add \$2 for shipping and handling. Ontario residents please add 7% P.S.T.




980 Alness St. Unit 7, Downsview, Ontario, M3J 2S2 (416) 661-5585 TELEX 065-28169

Store Hours:  
Monday to Friday 8:00 am to 5:00 pm.  
Saturday: 10:00 am to 1:00 pm.

Circle No. 26 on Reader Service Card

**New Display Drivers**

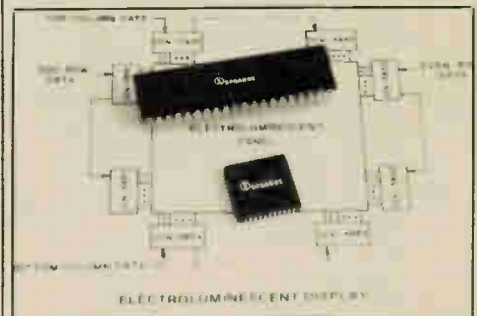

The UCN-5851A/EP and UCN-5852A/EP display row drivers from Sprague Electric combine a 32-bit shift register with 225V, 120mA DMOS sink drivers. These high voltage, thin-film electro-luminescent (TFEL) drivers make it possible to economically replace bulky, heavy, and expensive CRTs with flat-panel displays such as plasma, vacuum fluorescent, and electro-luminescent types.

A logic supply voltage range of 4.5V to 15V is possible, and in addition, these TFELs are suitable for use with piezoelectric elements, PGD, and other high voltage applications.

For more detailed information contact Sprague's Technical Literature Service at 41 Hampden Rd., P.O. Box 9102, Mansfield, MA 02048-9102.

Circle No. 55 on Reader Service Card



# Digital Frequency Doubler

## Digital Frequency Doubler

*Easily double your clock frequencies or have a TTL signal and its double without dividing down.*

*By N. Hancock*

DOUBLING A CLOCK frequency can be very convenient in digital circuits when synchronizing two parts or two system components particularly when its not feasible to divide the clock down. Simply doubling the frequency of your clock can save the hassle of redesigning. For applications where a high clock frequency or multiples of a frequency are required, this project is ideal.

A maximum output frequency of 10MHz is possible when the input is a 5MHz TTL level signal with a 50% duty cycle. To achieve this frequency range, high speed comparators (TL710s) are triggered by the rising and falling edges of the input waveform, when they pass the threshold levels.

The level of the thresholds not only determines the mark-to-space ratio of the output waveform as in Fig. 1, but also ensures even spacing of the pulses. Therefore, if the incoming signal does not comply to TTL constraints (approx. 0V-5V) the waveform will not pass the threshold levels at points for which they were set. The resulting output pulses will have irregular width and spacing.

At high frequencies the frequency doubler can actually improve the quality of TTL pulses by virtue of the resistor and capacitor combination on the input. This combination not only slews the leading and trailing edges of the incoming signal, but also filters out any spikes and ringing on it. Therefore the comparators cannot be inadvertently triggered by those glitches.

The output from the comparators is fed directly into a TTL gate and providing that there is no mismatch with the load, the output pulses from the TTL gate will be clean of ringing and spikes.

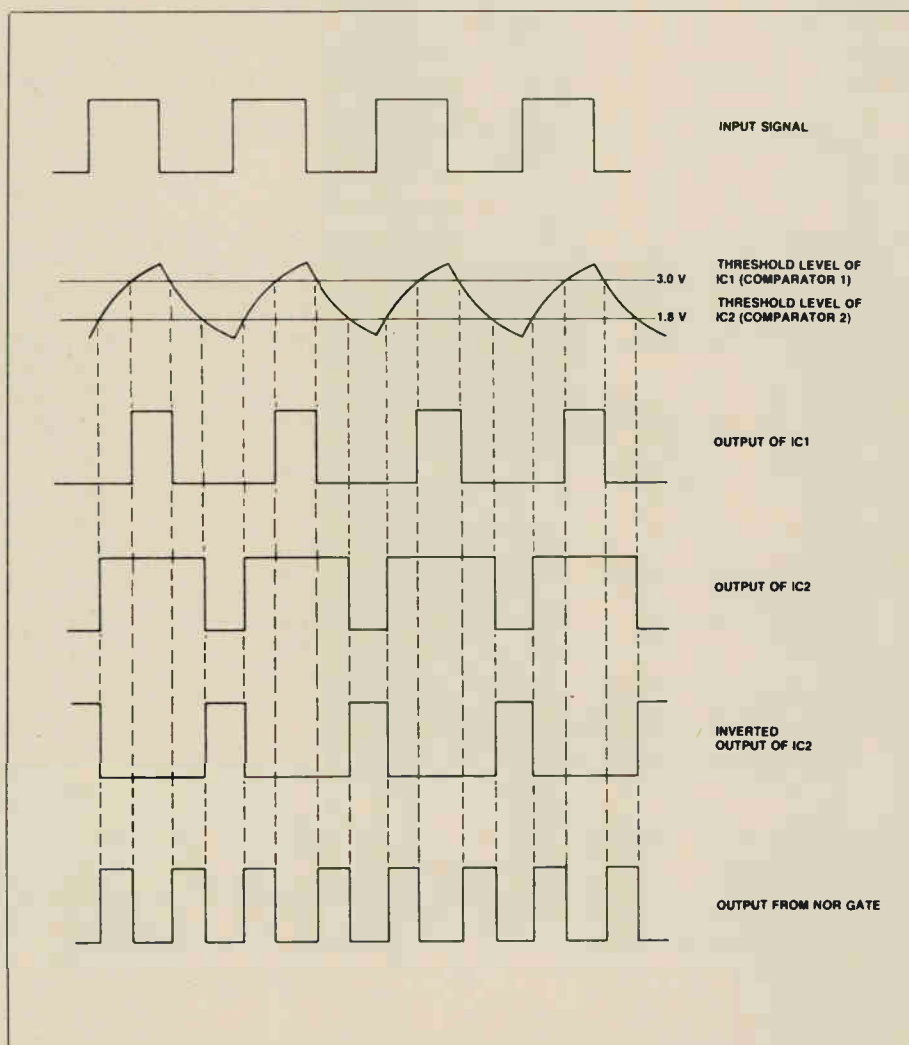


Fig. 1 The progression of the input signal through the circuit, showing how its double is derived.

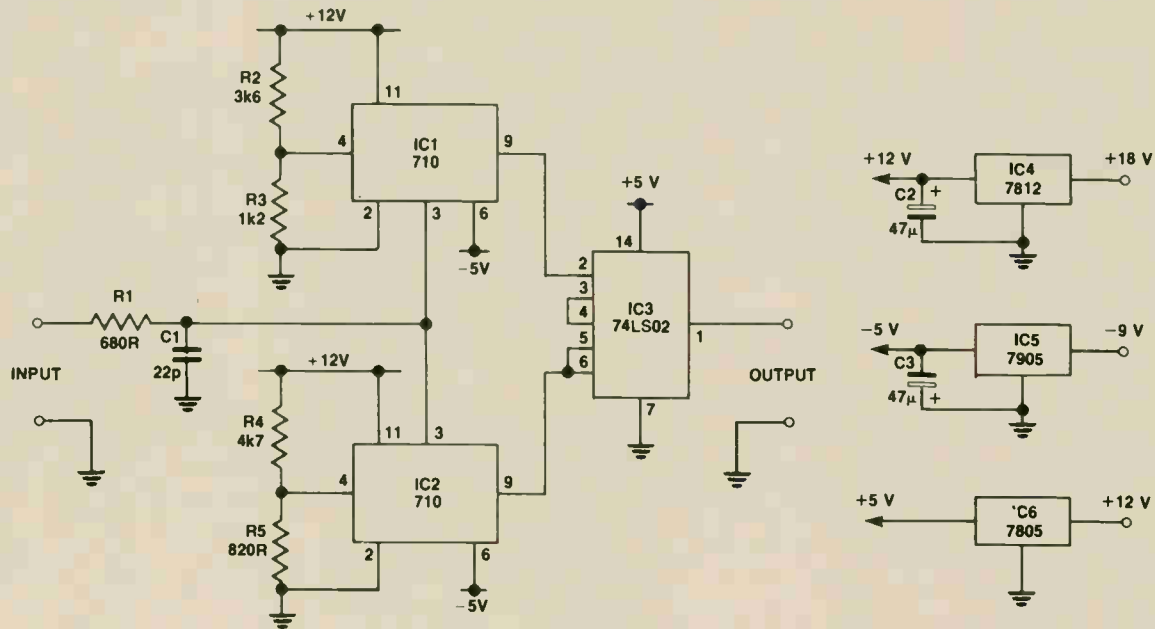


Fig. 2 The circuit diagram of the unit.

## Construction

Start by soldering in the wire link which is located near the middle of the board. Next, solder in the capacitors and resistors, and watch for the polarity of the electrolytics. Also, avoid excessive heating of R2, R3, R4, and R5 as this may cause their values to drift.

The voltage regulators can now be soldered in; check their orientation with the parts overlay. The rest of the ICs can be inserted at this stage taking the same precautions as before.

Begin the wiring connections with the battery clips. The black lead which connects the single 9V battery is soldered to one of the middle poles of the switch. The end pole is connected to the -9V input on the PCB. The red lead is soldered into the ground point next to R5. Take the remaining two battery clips and solder the red lead from one to the black lead of the other. Be sure to insulate the joint connecting the two wires or there'll be trouble. The unconnected red lead is then soldered on to the other middle pole of the switch, and the end pole to the 18V input of the PCB. The black lead from this pair of clips is connected to the ground point next to IC3.

The wires connecting the RCA sockets to the PCB can now be soldered in. First connect the input socket and the signal ground lead to their respective pads on the PCB, making these leads as short as possible. These wires should also be twisted together to reduce the chance of undesirable effects at high frequencies such as losses and crosstalk. The output RCA socket has its central terminal connected to the output pad on the PCB with

a short length of wire. The ground terminal of the output socket is connected to the ground terminal of the input socket by a short length of wire.

## Testing

First check the circuit board for dry joints and solder bridges. If it looks satisfactory, connect the three 9V batteries and switch it on. Before connecting up, check that the output from the voltage regulators IC4, IC5, and IC6 are within 100mV of their rated values which are 12, -5, and 5 volts respectively. If they are not, double check for shorts in the vicinity of the voltage rails.

If you do not get a satisfactory waveform out of the doubler check that the voltage level on pin 4 of IC1 is close to 3V. Also, check that pin 4 of IC2 has a voltage level close to 1.8V. These levels are critical because they set the threshold level of the comparators. The comparator limits can also be affected by DC offset of the incoming signal, so check that the incoming signal is pure AC.

## How It Works

The combination of R1 and C1 is used to slew the leading and trailing edge of the incoming square wave, making the rise and fall times longer. The resulting waveform goes to the non-inverting inputs of the differential comparators IC1 and IC2. R2 and R3 are connected to the inverting input of IC1 and set the upper threshold. The lower threshold is set by the combination of R4 and R5 connected to the inverting input of IC2. The output from IC2 is then inverted to make the mark-to-space ratio compatible with the output of IC1. Fig. 1 shows the relationship between the threshold settings and the resulting output waveforms from the comparators.

To combine the outputs from the two comparators, the waveforms are put through IC3 which is a quad NOR gate, thus giving twice the input frequency. The upper input frequency gives a mark-to-space ratio of close to 1:1. As the input frequency decreases, so too does the mark-to-space ratio. This is because the pulse width is set by the risetime of the waveform going into the comparators. Since the risetime is dependent on the value of C1, the mark-to-space ratio at lower frequencies can be increased by increasing the value of C1. However, this will limit the bandwidth of the doubler as high frequencies will be filtered out.

IC4 and IC5 are the 12V and -5V regulators respectively. These regulators provide accurate voltage levels, which are critical for setting the comparator thresholds. Capacitors C2 and C3 are used to decouple the voltage supply lines and thus remove any noise on the waveforms. IC6 is a 5V regulator and provides the voltage supply to IC3.

**Product Mart**  
**Classified Call**  
**(416) 445-5600**



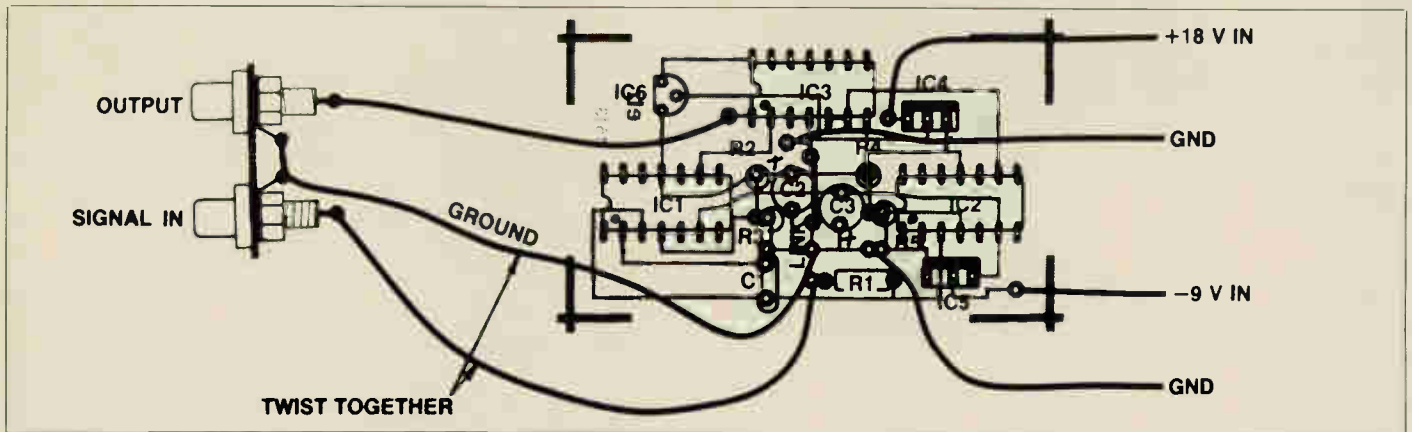


Fig. 3 The parts overlay for the frequency doubler.

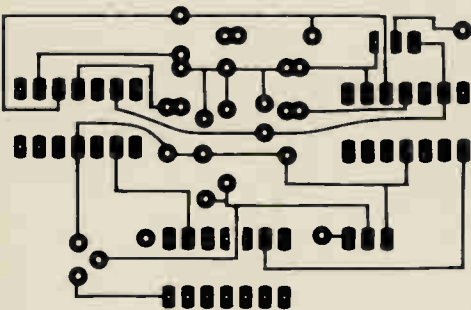


Fig. 4 The frequency doubler printed circuit artwork.

**Parts List**

**Resistors**

All 1/4W metal film, 1%

- R1 ..... 680R
- R2 ..... 3k6
- R3 ..... 1k2
- R4 ..... 4k7
- R5 ..... 820R

**Capacitors**

- C1 ..... 22p ceramic
- C2,3 ..... 47u 16V electro.

**Semiconductors**

- IC1,2 ..... 710 comparator
- IC3 ..... 74LS02 hex NOR gate
- IC4 ..... 7812
- IC5 ..... 7905
- IC6 ..... 7805 100mA

**Miscellaneous**

PC board; -3 x 9V batteries and clips; hookup wire; case to suit; 2 x RCA sockets; DPDT switch.

# K.E.M.

K.E.M. special Express Prototype Plate-thru P.C. Board service.

**In only 36 hours!**



**Price example**

- 4" x 5" with 200 holes Plate-Thru PC Board
- \*5 working days service ..... **\$145.00**/for 2 pcs.
- \*36 hour service ..... **\$290.00**/for 2 pcs.


Please ask for detailed price quotation list.

**K.E.M. Electronics. Ltd**

Mail to: Box 69126 Station (K), Vancouver, B.C. V5K 4W4  
Office: 879 E. Hastings St., Vancouver, B.C. Tel: (604) 251-1514

Circle No. 13 on Reader Service Card

# AFFORDABLE

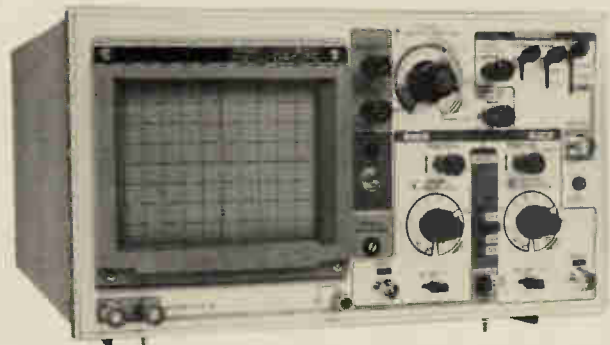

**DUAL TRACE OSCILLOSCOPE**

Here's exceptional value at a budget price! This 20 mHz dual trace scope has a built-in component tester ideal for troubleshooting solid state circuits and components with no circuit power, and features 6" high luminence CRT, TV sync measurement for vertical & horizontal circuitry, sensitivity 1 mV/div.

Model 33330 dimensions:

6.4" x 11.5" x 14".

**\$525.**

All for an incredible price of

Set of 1:1/10:1 switchable probes \$59.

35 and 45 mHz scopes also available.

Order by phone or mail. Visa, money order, certified cheque or C.O.D. accepted. Add \$15. for shipping and handling. Ontario residents add 7% PST.

# KB ELECTRONICS

355 Iroquois Shore Road, Oakville, Ont. L6H 1M3  
(416) 842-6888 Telex: 06-982396 (KBEL OKVL)

Circle No. 14 on Reader Service Card

## Multi-Channel Electronic Signal Switching.


By A. Armstrong & L. Buzzard.

THIS CIRCUIT demonstrates the use of electronically latched switching of up to 8 signals. It is intended for use in home audio systems. Unlike many electronically latched systems, it can be made to remember which position it was in when last used. Indicator driving is no problem either.

The NAND gates shown in the first figure are arranged so that, as any switch is pressed, the outputs of the latches take up the binary number corresponding to the switch pressed. Five-input NAND gates are needed for eight way switching, so one can either use 4068s and connect the extra inputs to logic 1, or five-input gates can be constructed from inverters and diodes as shown in the lower figure. In this case, the only pull-up resistors required will be the ones directly connected to the gates, a total of six instead of eight.

This scheme can be carried out using one hex inverter rather than six 4068s, but it is untidy with all those diodes hanging on the board. If you only want four way switching, two triple, three-input gates can be used, leaving two gates spare. A 4052 would then be used to switch both channels of the stereo source.

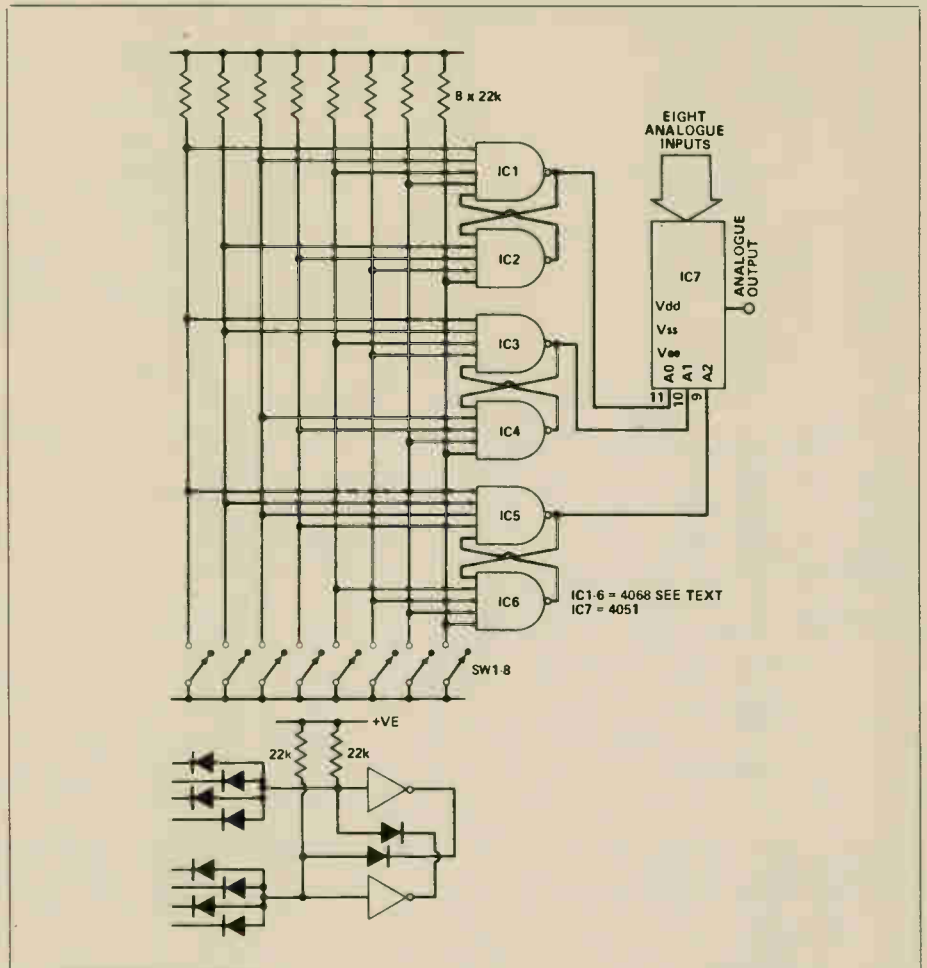Only one 4051 is shown in the diagram here, but in practice three would be used, with the address lines in parallel. Two of them would switch the signal and the third the indicator LEDs. It is quite safe to put 5mA through this type of



device, so the common input/output pin is connected to +7.5V via about 1k2 and the LEDs are connected to the switched terminals. Then one LED will illuminate at a time, corresponding with the channel selected.

Battery backup can easily be added.


The positive connections to all the CMOS gates and pullup resistors should be connected to the battery supply, but nothing else should be. The only thing to remember is that it is possible to change the state of the latch while only the battery supply is present.

## Light Operated Oscillator

By J. Short

THE FIRST half of the circuit is a light operated latch comprising the light dependant resistor, R1 and the thyristor, CSR1. R1 has a resistance of approximately 100M until it is exposed to light when the resistance will fall to about 100R. When this occurs CSR1 will fire and provide current to the second half of the circuit.

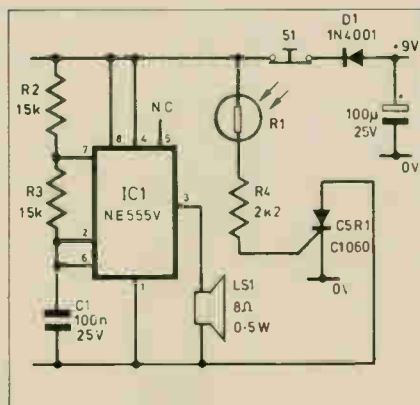When CSR1 fires, a low pitch noise is emitted from LS1 which is driven from the 555 timer, IC1. Once the tone is activated, it will continue until the circuit is reset via S1.



## Electronics Today

Each year Electronics Today delivers thousands of sales leads processed through our Reader Service Card Program. These sales leads are qualified with name, address and title of respondent.

For advertising information call

(416) 445-5600



**EPROM Markers**



A line of five new computer-printable EPROM labels are available from W.H. Brady Inc.

Two sizes are available in B-652 polyimide material, designed to withstand virtually all processes that PC boards are subjected to including heat, soldering, and solvents.


In addition, two other sizes are available in B-637 polyvinyl-flouride material which is smear-resistant, and self-extinguishing.

The fifth new EPROM configuration is made from B-619 polyester, making it resistant to solvents and smudging while offering high resolution and temperature performance (22°C to 172°C).

For further information contact: Peter Kaminski, W.H. Brady Inc., 10 Marmac Dr., Rexdale Ontario M9W 1E6. (416) 675-2112.

Circle No. 59 on Reader Service Card

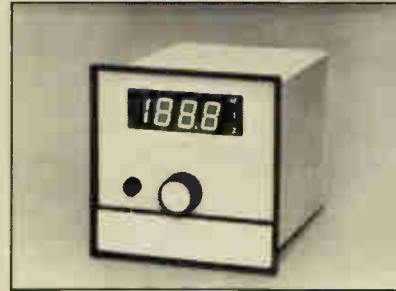**Canadian Temperature/ Process Controller**



The model TC1 temperature/process controller is a Canadian designed and manufactured unit from Marcland Instrument Services.

The TC1 has an accuracy of  $\pm 0.25\%$  and is easily modified to on-off, time proportional, high limit, low limit, and Fahrenheit or Celsius operation. A second setpoint can be changed from tracking to process, to high limit or low

limit by jumpers.

A unique feature is the front panel 'range change' whereby any new range can be chosen from 0-100% of span while still keeping the  $\pm 0.25\%$  accuracy.

For more information contact Bob Crooks or Brian McGee at Marcland Instrument Services Inc., 156 St. Denis, St. Lambert, Quebec, J4P 2G2. (514) 866-4607.

Circle No. 57 on Reader Service Card

**DOES YOUR DIGITAL CAPACITANCE METER DO THIS?**

FULL 4 DIGIT 0.5 INCH LCD DISPLAY COMPLETELY AUTORANGING WITH 10 RANGE MANUAL CAPABILITY

**AND THIS**

RANGE OF 0.0 pF to 1 FARAD (999.9 mF)  
0.5% BASIC ACCURACY UP TO 100 uF

**AND THIS**

READS DIELECTRIC ABSORPTION

**AND THIS**

EXTENDED PSEUDO 5 DIGIT  
RESOLUTION ON SOME RANGES ONLY

**AND THIS**

ABILITY TO ZERO LARGE CAPACITANCE  
VALUES UP TO 99.99 uF

**AND THIS**

CALCULATES TRUE CAPACITANCE  
IF CAPACITOR IS LEAKY

**AND THIS**

DIODE CLAMP AND FUSED  
PROTECTED INPUT.  
DISCHARGE RESISTOR IN OFF  
POSITION AT TERMINAL INPUTS.  
POWERED BY 9V BATTERY



**AND THIS**

IDENTIFIES TRANSISTORS (NPN, PNP)  
AND THEIR LEADS (E, B, C, ETC.)

**AND THIS**

TESTS ZENER DIODES AND RECTIFIERS.  
UP TO 20V ZENER WITH AC ADAPTOR,  
ZENER VOLTAGE WITH 9V BATTERY  
DEPENDS ON ITS CONDITION

**AND THIS**

AUTOMATICALLY CALCULATES LENGTHS  
OF CABLES IN FEET, METRES, MILES,  
KILOMETRES (THEORETICAL RANGE  
OF 9,999 MILES)

**AND THIS**

ABILITY TO SORT CAPACITORS IN  
MANY DIFFERENT MODES

**AND THIS**

ABILITY TO READ LEAKY CAPACITANCE  
(INSULATION RESISTANCE OR CURRENT)

**AND THIS**

CALCULATES TIME CONSTANTS WITH  
USER DEFINED RESISTANCE VALUES

**AND THIS**

HOLD FUNCTION FREEZES DISPLAY

**ONE YEAR PARTS & LABOUR WARRANTY**

**FOR ONLY THIS**



Circle No. 22 on Reader Service Card

MADE IN CANADA

**MODEL MC300**

Approx. Size  
7" x 4" x 1 3/4"


**DAETRON**

A DIVISION OF BERGERON  
TECHNOLOGIES INC.  
7686 KIMBEL STREET  
UNIT 5  
MISSISSAUGA, ONT.  
L5S 1E9  
(416) 676-1600

DEALER ENQUIRIES INVITED

PLEASE SEND ME

____ (QUANTITY) MC300(s) @	\$169.95	\$ _____
CARRYING CASE	\$19.95	\$ _____
AC ADAPTOR	\$11.00	\$ _____
ONTARIO RESIDENTS ADD 7% PST		\$ _____
SHIPPING AND HANDLING @ 5.00 per instrument		\$ _____
<input type="checkbox"/> I ENCLOSE CHEQUE <input type="checkbox"/> MONEY ORDER <input type="checkbox"/> VISA <input type="checkbox"/> MASTERCARD		\$ _____
<input type="checkbox"/> CARD NO. _____		
EXPIRY DATE _____	SIGNATURE _____	
NAME _____		
ADDRESS _____		
CITY _____	PROV. _____	POSTAL CODE _____

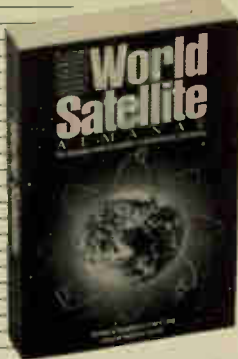


# 1985 World Satellite Almanac

## \$56.95

more than 500 pages  
over 350 maps,  
charts & tables

NOW... ALL THE WORLD'S SATELLITES ILLUSTRATED, FOOTPRINTED, INDEXED AND ANALYZED IN ONE AUTHORITATIVE SOURCE.

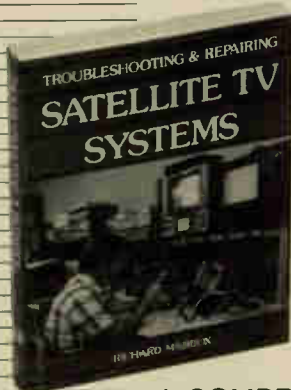**Technical Data  
Never Before Seen in Print**



# Troubleshooting & Repairing Satellite TV Systems

## \$27.95

400 pages  
351 Illustrations

A COMPREHENSIVE SERVICING GUIDE ON SATELLITE SYSTEMS FOR PROFESSIONAL TECHNICIANS AND OWNERS.

**Schematics and Repair  
Tips on 43 Different  
Model Devices**

## Meints-Shuster

400 BOUL. ROGER PILON  
DOLLARD-DES-ORMEAUX  
QUEBEC CANADA H9G 2K2



**YES!** please send me:

\_\_\_\_\_ copies of the 1985 World Satellite Almanac  
\_\_\_\_\_ copies of the Troubleshooting & Repairing  
Satellite TV Systems

NAME \_\_\_\_\_ POSITION \_\_\_\_\_

COMPANY \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ PROV. \_\_\_\_\_ POSTAL CODE \_\_\_\_\_

AMOUNT ENCLOSED \$ \_\_\_\_\_ (ADD \$3.00/BOOK FOR SHIPPING)  
MAKE CHEQUE OR MONEY ORDER (CDN. FUNDS) PAYABLE TO:

## Meints-Shuster

400 BOUL. ROGER PILON,  
DOLLARD-DES-ORMEAUX  
QUEBEC CANADA H9G 2K2 ALLOW 3 WEEKS FOR DELIVERY

**SORRY  
UNABLE TO BILL**

Continued from page 34

## For Your Information

### Tool Source

What should you be looking for in good quality tools for electronics applications? According to Hi-Tech Tools of Canada Ltd., the following is a good guideline.

In cutters, the steel is everything, but this is often difficult to determine, however, the following features are more easily identified:

- a box-joint or precision screw joint
- soft, well cushioned handle for comfort
- jaws which meet first at the tip, then close completely as pressure is applied
- a mat, dull or black finish to eliminate glare
- an internal spring or leaf spring

Gripping pliers are designed primarily around the joint. These tools are often subjected to twisting and flexing, and only a well made box-joint is going to hold the gripping tips in alignment for a long service life and precision work. Also look for the following:

- soft, well cushioned handle
- mat, dull or black finish
- an internal or leaf spring

In tweezers, the range of qualities is much greater: ranging from low carbon steel, nickel plated models for a couple of dollars, to very high precision exotic alloy types costing anywhere from \$50 to \$80. Most users, however, would be well served by Stainless Steel, anti-magnetic, anti-acid types in the \$10 to \$20 range.

If you're interested in what's available from Hi-Tech Tools, you can contact: R. Kirkwood, Hi-Tech Tools Canada Ltd., 2175 Dunwin Dr., Unit 6, Mississauga, Ontario L5L 1X2. (416) 828-0068

Circle No. 53 on Reader Service Card


Continued on page 43

Pacific Bell is testing a system in Danville, California, that will enable users to transmit five data and two voice channels simultaneously over standard telephone twisted-pair wiring. Called Project Victoria, the service uses an encoder on the subscriber's premises and a decoder at the central office; the decoder separates the signals and routes them to the proper circuits. One of the five channels offers data transmission at 9600 bps, while the other four operate at up to 1200 bps. The service is expected to be in commercial operation by 1987.
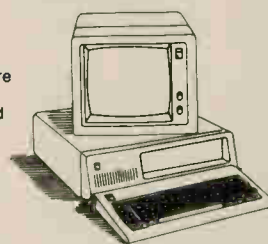
### PC/XT Compatible ECS1-PC/XT\*


Special  
**\$899.00**

- 8088 processor
- optional Intel 8087
- numeric coprocessor
- 256K memory
- double sided double density disk drive
- detachable keyboard
- colour graphic board
- 150 watt power supply
- support PC software
- 180 day warranty
- 8 slot Mother board



### TTL Flat Screen Monitor

**\$199.00**

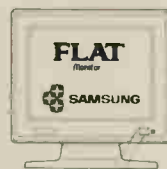

Mouse —  
**\$149.00**



### AT\* Compatible

**\$1995.00**

- 512K memory
  - 1 1.2M drive
  - Colour card
  - Keyboard
  - 200 watt power supply
- \*IBM is a registered trademark of International Business Machines.

### XT/PC MAIN PERIPHERAL

Enhance Graphic Card	\$595.00
Mother Board 8 Slot	\$249.00
Color Graphic Card	\$139.00
Multifunction	\$149.00
Monochrome Card	\$139.00
Monochrome Graphic	\$175.00
Game Port	\$ 49.00
RS232 Card	\$ 59.00
Parallel Interface	\$ 59.00
Disc Controller Card	\$ 89.00
Case	\$ 69.00
Keyboard (Cherry)	\$ 99.00
Power Supply 130 Watts	\$139.00
Printer Cable	\$ 25.00
RS232 Cable	\$ 25.00
Disk Drive Cable	\$ 15.00
Moving Message Board	\$495.00
TTL and CMOF test Card	\$ 99.00
150 Watt Power Supply	\$149.00
Modem 1200 B	\$299.00
Network Card	\$595.00



### ELECTRONIC CONTROL SYSTEMS

1590 Matheson Boulevard, Suite 1 & 2 Mississauga, Ontario L4W 1J1  
(416) 625-8036 Hours — Mon. to Fri. 10-6. Sat. 10-2



# The Multimeter

*The VOM has not been outmoded—  
it's a basic, versatile meter for  
the testbench.*

*By James W. Essex*

IN MY early days of radio, I met an engineer who was enraptured with a multimeter he'd just bought because it had a '20,000 ohms per volt' movement. This was well before vacuum-tube-voltmeters were common. I'd just learned about capacitance, inductance and transformers in those early days. The 'ohms-per-volt' posed a great mystery. What were they? By the expression on his face, I could tell that the expression was important to him. Several VOMs and many years later, my appreciation for this figure of merit of a multimeter has grown, and like that broadcast engineer of long ago, I've learned to appreciate it more.

Consider your own experience. No doubt you have thought, like most, that you needed a VTVM to read the Automatic Gain Control or Automatic Volume Control circuits, and may have been surprised to learn that a good volt-ohmmeter can exceed the input impedance of a VTVM, at least on the higher ranges. Yet, there's some feeling today that the ascendancy of the VTVM (or its solid-state equivalent) has tended to outmode the universal VOM by the accompanying glitzed-up advertising and flashing digital readouts. Not so. I learned that the old-fashioned VOM is still the best, despite those who argue that the sweep-needle with inherent parallax leaves much to be desired, or that they don't understand what ohms-per-volt means as a figure of merit. There's still much to recommend the regular VOM over the VTVM, and it's not all because of price or portability.


## Portability

On portability, and nothing could be more portable than the VOM with its built-in battery, it's perhaps significant that a line of VTVMs features a battery pack, perhaps an admission that the necessity to plug in the early VTVMs left something to be desired. In any case, especially if you're just entering electronics, buying a piece of test equipment

would be much easier if the demands on it weren't so great. Unlike some trades like 'water divining', where all you need is a willow branch, an electrical tester requires reliability and utility, every time. It's not enough, as with a water search, to note

the bending of a tree branch (experts generally agree that you'll find water underground most anyplace anyway).

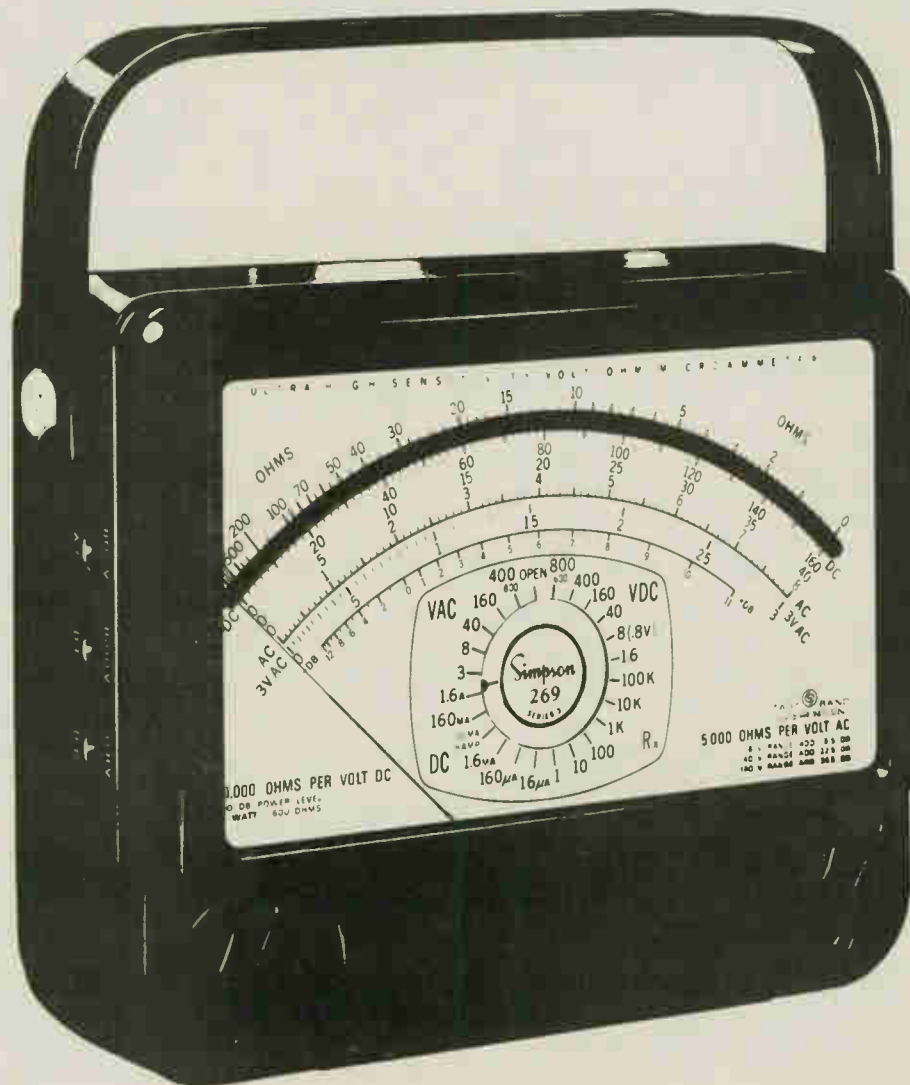With the low impedance found in today's transistor circuits, the concern for a high impedance instrument has all but



disappeared. This makes the VOM a coveted tester. And neither do you have to go to the more expensive meters to get high sensitivity with accuracy. Like the water underground, there are volts and amps everywhere to be found, and there's a multitude of electronic equipment to suit every style and price. But how well you can interpret observed results is important, and there are many pitfalls.

## Commercial VOMs

Generally, the VOMs available today have particular merits to meet buyer's requirements, and your own demands will determine which one to buy. Basically, there are features common to each: portability, easy-to-read scales, and a minimum price for a reasonable degree of accuracy.

It's interesting to note that the sensitivity of the VOM is equal to or better than the VTVM on the higher ranges, according to the manufacturer of the Model 269, Bach-Simpson. Further, the current sensitivity is extremely good; the 269, for example, allows evaluation of DC current as small as a fraction of one microampere. As far as I'm aware, no other portable has approached this current sensitivity, even in high-priced non-portable lab meters.

Even the mini 'cheap' versions of the VOM now appear regularly in the most unusual situations. I'm constantly surprised to find equipment in the over-\$40,000 category being serviced with the aid of one of those minis pulled surreptitiously from a pocket or briefcase. Perhaps the moral here is that for all their complications, circuits reduce to volts, amps and ohms, and a good basic multimeter can do the job of testing.

## Looking Inside

Inside the Bach-Simpson 269, for example, we find a simplified DC meter movement with a full-scale-deflection of 10uA. This is considerably more sensitive than the inexpensive variety, but it will serve to illustrate. In series with the meter coil is a string of resistors; the input switch can connect the input to any point in the resistor chain, allowing the sensitivity to be varied. In this case, the resistors are chosen to allow full-scale-deflection on the following DC voltage ranges: 1.6, 8, 40, 160, 400 and 1600 volts. Another resistor in an external probe allows measuring to 4kV.

The input resistance of the meter consists of the resistance of the meter coil (20k) plus any series resistors in the chain. On the lowest, most sensitive range, this consists of 20k plus the 140k, a resistance of 160k for an input of 1.6V.

To allow larger voltages to be measured, we introduce another resistor into the chain; the 8V range adds a 640k to the 160k for a total of 800k.

You can see that the internal resistance is 100k ohms for every volt on the range switch: 800k for 8V, 4M for 40V, etc. This is what the manufacturer means by a sensitivity rating of '100,000 ohms/volt'. The ohms-per-volt does not refer to the input voltage, but to the voltage on the range switch.

For measuring AC, the meter is now in a rectifier bridge configuration. The added two-diode bridge and its calibration resistors reduces the basic sensitivity to 5k ohms/volt. Basically, the meter circuit is the same as for DC. The input resistance of the unit is found by multiplying 5,000 times the number of volts that will give FSD: 40,000k for 8V, 4M for 800V, etc.

have to be 100 times the source or even more.

## Isolation

Another advantage to the VOM over the line-powered VTVM is the absence of grounding problems. If both the test circuit and the meter have their common leads connected to ground, it's possible to create a short circuit: you can blow fuses if the test circuit is powered up, or you can have resistors read zero ohms if the ground circuit gets in the way. The self-contained VOM skirts this problem.

The natural isolation of the VOM also means that the ungrounded common lead isn't likely to short out any delicate tran-

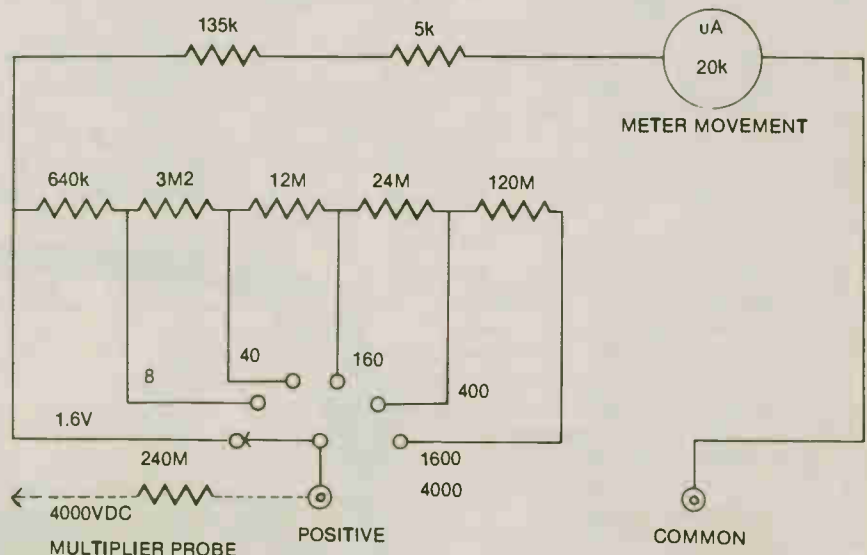


Fig. 1. A simplified DC voltmeter circuit.

## Loading

Since the VOM is a *passive* device (its movement is powered by the circuit under test), we have to take into account the current that it draws, and whether or not this will cause erroneous readings.

An important fact becomes obvious: the unusually high resistance presented by a VOM on its higher ranges means the loading effect will probably be negligible. On the 40VDC range, for instance, the Model 269 has an input resistance of 4M, and 16M on the 160V range. This latter figure is as high as the best of VTVMs, which usually have a 10M input resistance. The disadvantage is that we lose sensitivity as we increase the input resistance. Still, many measurements can be made on the 40V scale, which has an acceptably high resistance of 4M.

A good rule of thumb for general testing is that the load should be at least ten times higher than the source. The 4M figure means that we can measure circuits up to 400k in resistance without causing unacceptable errors. Of course, if you want lab-quality accuracy, the load will

sistor stages, blowing out components and causing additional trouble.

## Ohms

To implement an ohms range, a battery is inserted in series with the meter. When the test probes are placed across a resistor, current flows and deflects the meter; the internal resistors and the meter scale are calibrated to read out the value of the unknown resistor.

In checking transistors, the ohmmeter of your VOM is indispensable, for it readily indicates shorts, opens and even polarity in doubtful areas. This may sound archaic, but according to one of the largest manufacturers of solid state equipment, this is exactly how they troubleshoot on their assembly lines.

By placing the appropriate test probe of your ohmmeter onto the matching polarity of a transistor under test and reading the resistance, you can easily tell which is the P and which is the N of a base, besides testing for obvious opens or shorts. With an NPN, the positive terminal of your VOM connected to the base gives a



**Disturbance Recorder**



No, this doesn't keep track of barking dogs or screaming children, but it does keep watch over your precious power supply lines.

The AP-904 from Kuwano Electrical Instruments is a diagnostic tool which monitors and records various disturbances on AC and DC power lines by measuring each item per 10 millisecond or half wave cycle interval.


In addition, the unit incorporates an 8-channel event recorder capable of measuring a

pulse width of 1 microsecond to 1000 microseconds. In the event that a change in input voltage is detected, the AP-904 prints out the channel number and status of event, together with the time of occurrence.

Mr. Henry Taub, RCC Electronics Ltd., 310 Judson St, Unit 6, Toronto, Ontario M8Z 5T6. (416) 252-5094.

Circle No. 50 on Reader Service Card

**Automated Calibration Software**

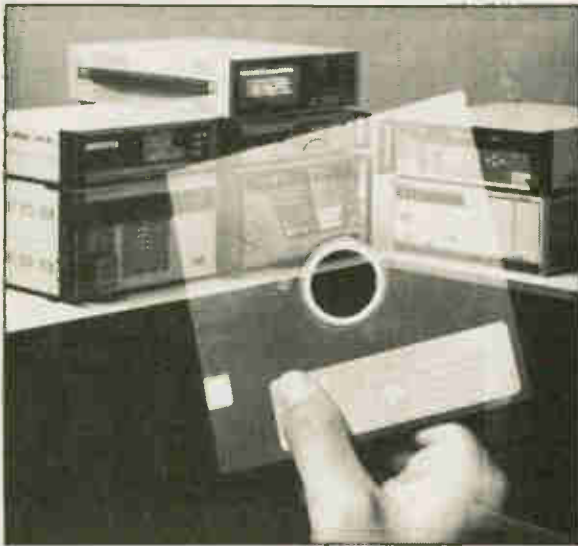

The versatile 7411A 'Calibration-at-a-Keystroke' software package from Fluke permits a modular approach to automating calibration and management functions of major electronic instrumentation equipment.

It can be used with a wide variety of calibration instruments, such as the Fluke 1722A instrument controller, in several system configurations. The complete calibration procedure can be automatically controlled using IEEE-488 based meters and scopes.

The 7411A software automates data management and report requirements, saving time and elimi-

nating errors. It also reduces cost per calibration and increases throughput to improve productivity. A Calibration History Management feature manages your data base and generates reports, such as instrument recalls, in addition to listing procedures and test results. The 7411A package is available in Canada for under \$2000.

For more information contact: Mrs. Rose Monk; Allan Crawford Associates Ltd., Test and Measurement Division, 5835 Coopers Ave., Mississauga, Ontario L4Z 1Y2. (416) 890-2010

Circle No. 51 on Reader Service Card

**AM Stereo Signal Generator**



The LSG 245 AM Stereo Signal Generator from Leader Instruments provides a wide variety of modulation and output conditions, and is an ideal source for sensitivity, separation, selectivity, distortion and other tests on Motorola C-QUAM-type AM Stereo systems.


All parameters are entered by front panel pushbuttons and are verified by LED displays. In addition, up to 100 sets of user defined test conditions can be stored and recalled enabling measurements to

be made rapidly and without error. For those who have fully automated production facilities, QA and service environments, a rear panel connector allows remote control of all front panel functions (except on/off). An optional GPIB interface is also available.

Omnitronix Ltd., 2410 Dunwin Dr., Unit 4, Mississauga, Ontario L5L 1J9. (416) 828-6221.

Circle No. 52 on Reader Service Card

**Technical Ceramic Dielectrics**

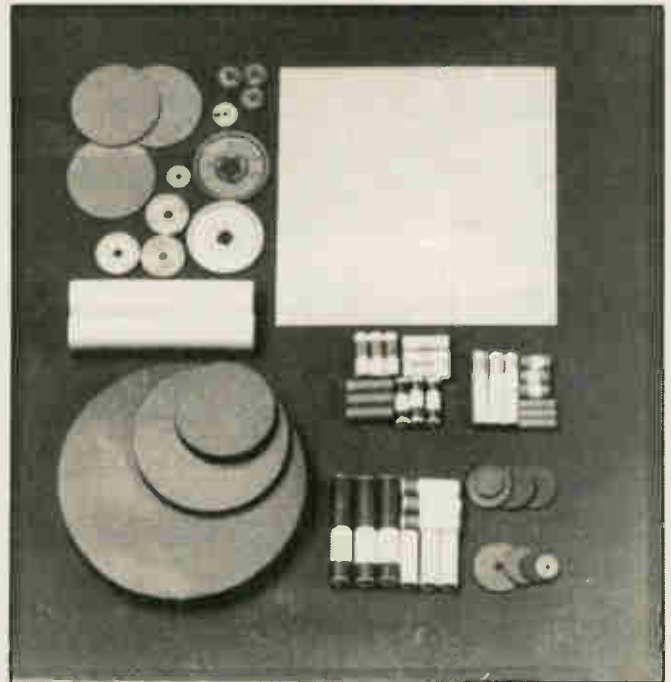

A source for technical ceramic dielectrics is Tusonix Inc., manufacturers of fixed, variable ceramic capacitors, and EMI filters.

The dielectrics are available in a variety of shapes, sizes, and formulations, including extruded, pressed, and cast. Ceramic formulations developed over a 50 year

period are available in more than 100,000 variations in capacitance values up to 1 mFd, and up to 40 kV voltage ratings.

Tusonix Inc., P.O. Box 37144, Tucson, AZ 85740-7144. (602) 744-0400

Circle No. 56 on Reader Service Card

# Interval Timer

**An inexpensive timer with many useful applications featuring intervals from 30 seconds to 15 minutes.**

By C.J. Bowes



THERE ARE NUMEROUS occasions when it's useful to have some sort of timer which emits a signal at regular intervals. The circuit described here has been designed to fulfil this function in a versatile way, by providing a range of switched time intervals between 30 seconds and 15 minutes. The duration of the output tone can be varied so that a range of signals between a short burst and long tone can be obtained.

## Circuit Description

The circuit diagram of the unit is shown in Fig. 1. The heart of the circuit is a 555 timer (IC1) which is connected as an astable multivibrator.

In this configuration the output of the IC swings from V+ to ground for a period T2 after a time interval T1, as shown in Fig. 2. The duration of both T1 and T2 are determined by the values of the resistors RA and RB (Fig. 3).

T1 is calculated using the formula:

$$T1 = 0.7 \times (RA + RB) \times C$$

(Where T=time in seconds, RA, RB= values in ohms, and C= value of the capacitor in Farads). T2 is obtained in a similar manner from the formula:

$$T2 = 0.7 \times RB \times C$$

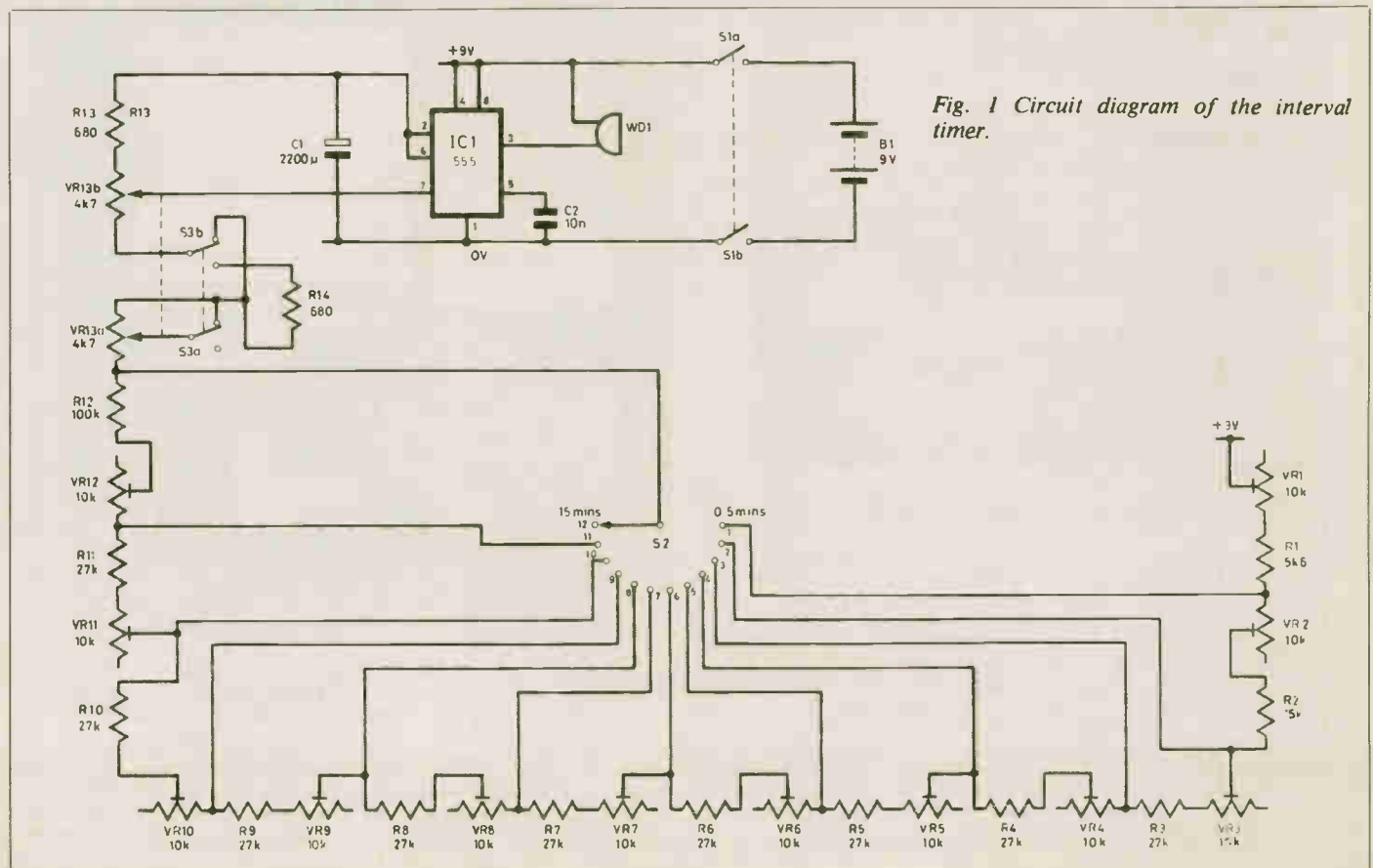


Fig. 1 Circuit diagram of the interval timer.



# Product Mart *Where Buyers Find Sellers*

**TV GENIE** channel 14 transmitter \$99.95. Cable TV Descrambling Techniques. 56 pages. \$13.95. Amazing see-in-the-dark Infra-Red night viewer kit \$295. Catalogs \$1. **CROSLEY(J)**, Box 173, Montreal, Canada H3X 3T4.

**LUSCIOUS** surprise pack of electronic parts \$6.00. 100% money back guarantee! Catalog 2-34¢ stamps. **MP2 SCIENTIFIC**, 33255 S. Fraserway, Suite 472, P.O. Box 8000, Abbotsford, B.C. V2S 6H1. BC residents please add 7% Sales Tax.

### 6502 MICROCONTROLLER

**THE 6502** for your projects. 2 or 8k static ram, 2, 4, 8, 16, or 32K EPROM, 3 6522 VIA's, 1 or 2 Mhz clock, 65C02 hardware Compatible, small 8" x 4.5", **AGGA ELECTRONICS** a Division of RTP, P.O. Box 1848, Kelowna, BC, Canada, V1Y 8P2. Bare PCB with doc. \$44.95. BC Orders add 7% PST. U.S. orders add \$2.00 shipping.

**APPLE COMPUTER MUSIC PRODUCTS**. Complete synthesizer system available in kit form: 61 note keyboard kit, enclosed in wood case with interface card for \$299.00, (Bare keyboard for \$95.00); assembled synthesizer cards with software for \$349.00; midi card for Apple or Commodore for \$159.00. Call Collect 1-416-475-1263 for free catalogue. Visa/Mastercharge. **CLASSIC ORGAN**, 300 Don Park Rd., Unit 12 Markham, Ontario L3R 3A1.

**LED..LED...LED...** Always in stock for immediate delivery by return mail. (5mm diffused) Red. \$0.10 - Green \$0.12 - Yellow \$0.12 - Amber \$0.14 - Orange \$0.14 - 2 pcs Holder \$0.4. Minimum order 100 each. Add \$2. for postage. Free sample and selection guide on your letterhead. To **SURPLUS ELECTRO QUEBEC**, 2264 Montee Gagnon, Blainville, P.Q. J7E 4H5.

**J&J ELECTRONICS LTD.**, Box 1437E, Winnipeg Manitoba R3C 2Z4. Surplus and Semiconductor Specialists. Do you get our bargain flyer? Send \$1.00 to receive the current literature and specials and to be placed on the mailing list for future publications.

**ELECTRONIC SURPLUS INDUSTRIES LIMITED**, we sell used industrial/military test instruments, including oscilloscopes by HP Tektronix, Philips; Signal generators, meters, components, tubes, etc. 1191 Lawrence Avenue West, Toronto, Ontario M6A 1E2 416-787-1837.

## PRODUCT MART

WHERE BUYERS  
FIND SELLERS

For more information Call:

(416) 445-5600

## Electronics Today Order Form

### Subscriptions:

Please complete reverse side to start or renew a subscription.

**Back Issues:** \$4.00 each; Ontario residents add 7% sales tax. Please circle issues desired.

1977	1978	1979	1980	1981
Feb. July	May Sept. Nov. Dec.	Feb. April May July Aug. Sept. Oct. Nov.	Jan. May June Nov. Dec.	Jan. Feb. March April June July Aug. Sept. Oct. Nov. Dec.
1982	1983	1984	1985	1986
Jan. March April May June July Aug. Oct.	Jan. Feb. March April Aug. Sept. Nov. Dec.	Jan. Feb. March April May June July Aug. Sept. Oct. Nov. Dec.	Jan. Feb. March April May June July Sept. Dec.	Jan. Feb. March April May

**Binders:**  Moorshead Publications  
\$9.75 each plus 7% P.S.T.

## SPECIAL PUBLICATIONS

ITEM	QTY	AMOUNT
Book of Computer Music \$4.95	.....	\$ .....
Project Book No. 2 \$3.95	.....	\$ .....
50 Top Project \$4.95	.....	\$ .....
Your First Computer \$3.95	.....	\$ .....
Computers in Small Business \$3.95	.....	\$ .....

## BOOKSHELF — Order Form

Code (e.g. BP12)	Title (Short-form is O.K.)	Price
.....	.....	\$ .....
.....	.....	\$ .....
.....	.....	\$ .....
.....	.....	\$ .....
.....	.....	\$ .....

## SOFTWARE — Order Form

.....	\$ .....
.....	\$ .....
.....	\$ .....

Sub Total \$ .....


Tax (Ontario Residents) \$ .....

Postage \$1.00 .....

Total Enclosed \$ .....

Orders from the Bookshelf are tax exempt. Please add \$1.00 for postage. Remember to put your name and address on reverse side. See over for mailing details. Specials and Software add 7% PST.
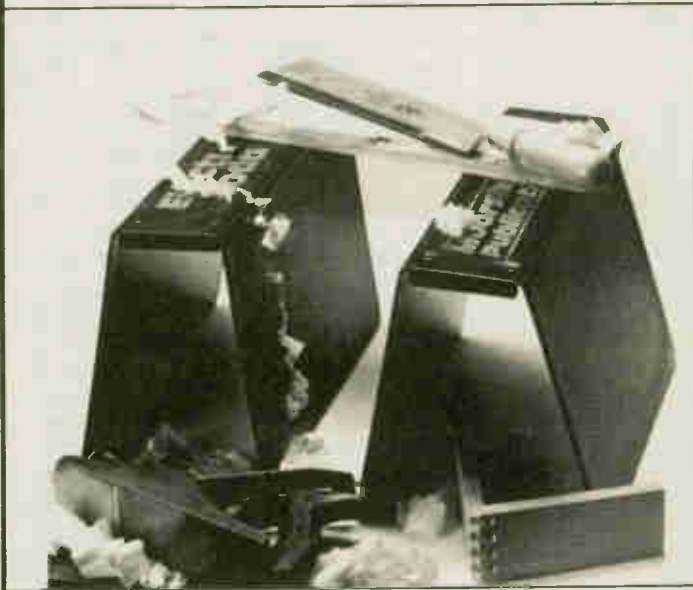
## THE ELECTRONICS TODAY SAWHORSE/MAGAZINE BINDER!



FOR THE first time, you can organize your workshop and saw boards at the same time! With one binder, you can hold boards up at an angle! With two binders, you can support your boards horizontally while you're making a bookcase!


These binders are made from vinyl and feature a special spring rod arrangement to hold up to 12 issues, neatly spaced, without cutting or punching. The binders and the magazines inside open easily and lay flat for easy reference or photocopying.

Of course, with any combination tool, some compromises are inevitable. The easy-open feature of our binders means that they're a bit wiggly as sawhorses, and what you can't see in the photograph is that the board had to be stuck to the binders with masking tape. Other than that, they work almost flawlessly, as long as the wood doesn't weigh over three ounces.

To order this amazing combination tool, send \$9.75 for each binder (Ontario residents add 7% sales tax, which works out to 68 cents each) to:

**Binders**  
**Moorshead Publications**  
 1300 Don Mills Road  
 Don Mills, Ontario  
 M3B 3M8

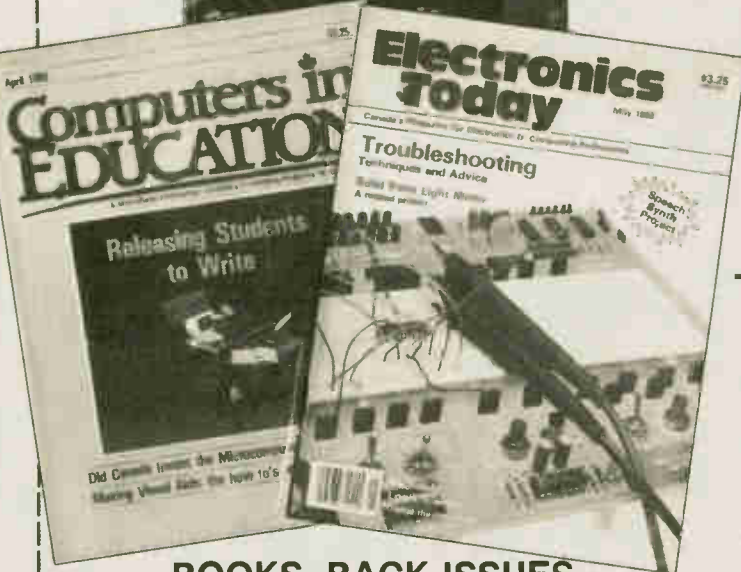**BE SURE OF YOUR ISSUE EACH MONTH. SUBSCRIBE TODAY.**



**BOOKS, BACK ISSUES,  
 SPECIAL PUBLICATIONS, BINDERS  
 — SEE OVER**

### Moorshead Publications

1300 Don Mills Rd., Don Mills, Toronto, Ont. M3B 3M8

**MERCHANDISE ORDER**  Please fill out form overleaf

**SUBSCRIPTIONS:**  NEW SUBSCRIPTION  RENEWAL

**Electronics Today**

One year (12 issues) \$22.95  Two years (24 issues) \$37.95

**Computing Now!** (Special Time-Limited Rate)

One year (12 issues) \$14.95  Two years (24 issues) \$27.95

**Computers in Education**

One year (10 issues) \$25.00  Two years (20 issues) \$45.00

**Outside Canada (US Dollars)**

For U.S. please add \$3.00 per year  other countries add \$5 per year

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

TOWN/CITY \_\_\_\_\_ PROVINCE/STATE \_\_\_\_\_

CODE \_\_\_\_\_ DATE \_\_\_\_\_

POSTAL CODE \_\_\_\_\_

Cheque enclosed DO NOT send cash

Mastercard Account No. \_\_\_\_\_

Visa Account No. \_\_\_\_\_

American Express Account No. \_\_\_\_\_

Expiry Date \_\_\_\_\_

Signature \_\_\_\_\_



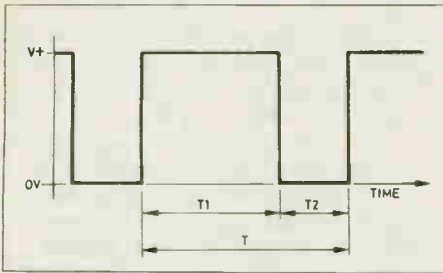


Fig. 2 Timing diagram for the circuit.

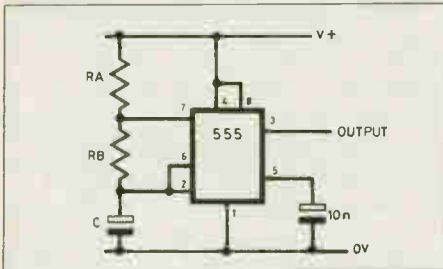


Fig. 3 The basis of the Timer circuit.

By splitting the value of RA into several smaller values it is possible to produce a circuit in which a single switch can be used to select a series of different values for T1. This has been exploited in this circuit, so that RA is in fact made up of a series of fixed and variable resistors (VR1-VR12 and R1-R12) which are wired as a chain.

The proportion of the chain used as RA is selected by the position of the wiper of the time selector switch, S2. This determines T1, which is the interval between the output tones. The length of the tone corresponds to T2 and is calculated from the second formula given above. This is set by the total resistance of VR13 and R13. R13 is chosen to give a minimum tone duration of about one second.

If the two timing formulae are combined we see that the total time for the sequence (T in Fig. 2) is found from the formula:

$$T = 0.7 \times (RA + (2 \times RB)) \times C$$

RB is the value which is adjusted to increase or decrease the duration of the tone. It is therefore necessary to alter the value of RA by twice the alteration in the value of RB if adjustment of the duration of tone burst is not to alter the duration between tones.

This is achieved by making VR13 a dual gang 'stereo' potentiometer, connected so that its wiper forms the junction of RA and RB and is connected to pin 7 of IC1.

The second half of the stereo control is connected in series with the resistor string (RA) to double the changes in value of RB. Switch S3 is included so that the duration of the tone can be either included in or excluded from the time between tone bursts.

In the inclusive position the interval set by S2 runs from the start of one burst of tone until the beginning of the next. In the exclusive position the interval selected by S2 runs from the end of one burst until the start of the next. The longer time period is achieved by placing the whole 5k of VR13a and R14 in series with the resistor chain.

### Construction

Construction of the unit is reasonably straightforward as the great majority of the components are mounted on the PCB as shown in Fig. 4. The remainder of the components are mounted on the removable lid of the case, with the exception of the buzzer. The one used in the prototype is rather large in comparison with the depth of the case, so it is mounted inside the box and protrudes through the lid (Fig. 5).

The PCB pattern shown in Fig. 4 should be transferred to a suitable board, etched and drilled in the normal way. The components should then be inserted in the appropriate positions and soldered, starting with the smallest components. After the soldering has been completed, trim off any excess wire.

### Switch Wiring

The wires required for making connections between the PCB and the other components can be soldered into place. It is advisable to use ribbon cable for the con-

nections between S2 and the PCB. The board should then be thoroughly inspected for solder bridges between tracks.

Once the PCB has been completed and checked it should be inserted into the case and a suitable position found for the piezo element you selected. This component is mounted in the case and may protrude through the lid if necessary.

When a suitable position has been found, the position of the component should be marked on the case lid and an appropriately sized hole cut out, preferably with a hole-cutter. The positions of the remaining components can be marked on the case lid and suitable holes cut or drilled.

Rub-on lettering should be applied to the exterior of the case. The only component requiring careful positioning of the lettering is S2, which is the interval time selector switch. A convenient method to locate the lettering for S2 is to mount the switch temporarily in its correct position and rotate the spindle to its farthest anticlockwise position.

The knob is then fitted with its pointer in the appropriate position. A fine pencil spot should be marked on the case directly below the pointer. This marks the location of the first legend.

The switch is then rotated to its next position and the process repeated until all twelve positions have been marked. A small rub-on spot can then be applied to cover the pencil spot and the appropriate

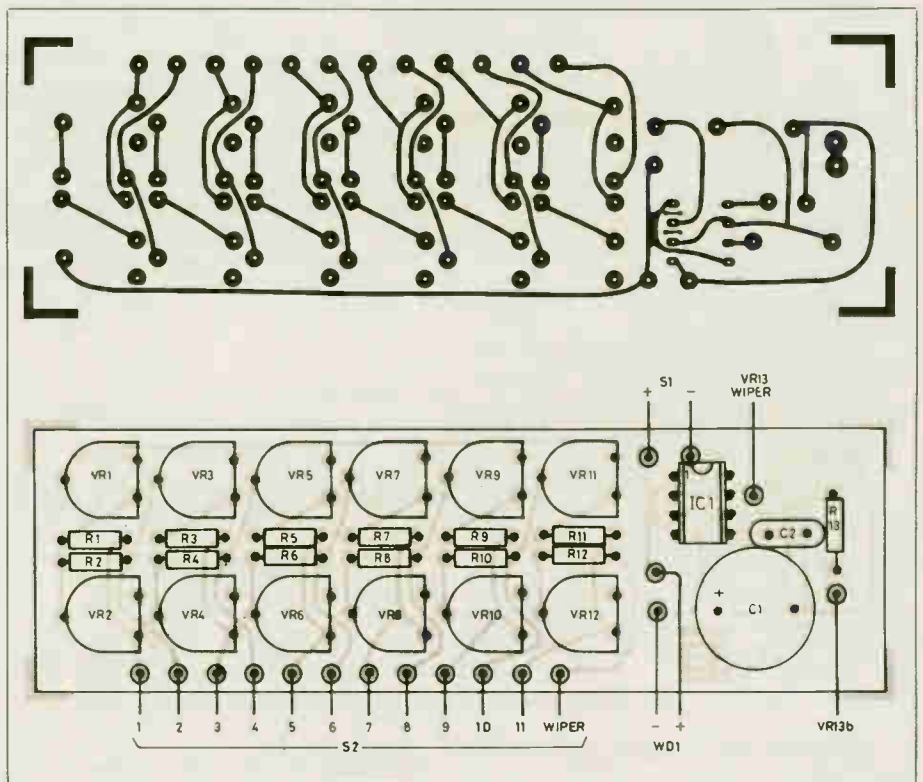


Fig. 4 The PCB (top), and the parts overlay, shown actual size.

lettering applied to complete the legend. With the components specified, the intervals will be as shown in Table 1:

Table 1: Timing intervals.

Switch Position	Interval
1	30 sec
2	1 min
3	2 min
4	3 min
5	4 min
6	5 min
7	6 min
8	7 min
9	8 min
10	9 min
11	10 min
12	15 min

Once applied, the lettering should be protected by several layers of spray-on clear lacquer.

When the case is dry, the components can be mounted onto the lid, cutting down the spindles of the rotary components as required. Both S1 and VR1 should be rotated to their fully anti-clockwise position so that the knobs can be placed in position and correctly lined up before tightening the securing screws.

The wiring between the panel-mounted components and the PCB should be completed, as should the connection between the battery connector and S1. All solder joints should then be thoroughly inspected before connecting the battery and testing the circuit.

### Testing and Calibration

To test the unit the controls should be set as follows:

- S1 On
- S2 Position 1 (Fully Anti-clock.)
- S3 Inclusive
- VR1 Minimum (Fully Anti-clock.)

After a short stabilizing period, the circuit should start emitting a short tone burst at about 30 second intervals. The intervals between the output tones should be identical but will not necessarily be accurate since the system will not have been calibrated.

VR13 should then be rotated to check that the duration of the tone is increased but that the interval between the start of one tone and the start of the next remains the same, irrespective of the setting of VR13. When S3 is placed in the exclusive position the interval between the end of one tone and the start of the next should remain constant irrespective of the setting of VR13.

Calibration of the unit is, unfortunately, a little tedious but, if done carefully and methodically, worth the effort involved. The unit should be switched on with

S2 at position 1, S3 at the inclusive setting and VR13 set to give minimum tone duration. A stop-watch should be used to time the interval from the end of one tone to the end of the next. VR1 is then adjusted until this interval is correct.

Once the first time interval is correctly set, S2 can be rotated to the next position and VR2 adjusted until the correct interval is obtained. This process is repeated until all the presets have been correctly ad-

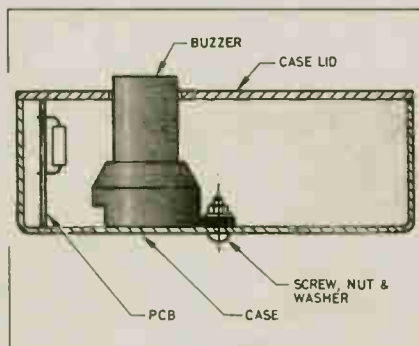


Fig. 5 Buzzer and PCB mounting details.

justed. If the correct time interval cannot be obtained by adjusting the appropriate preset, then the associated fixed-value resistor should be substituted by one with a different value.

To increase the time period, the value of the fixed resistor should be increased, and to decrease the time period the value should be decreased. Once the unit has been calibrated, the buzzer can be mounted in position, the PCB placed in the correct location and the lid attached. Care should be taken to ensure that the preset potentiometers are not disturbed during this process.

### In Use

Operation of the unit is simple and straightforward but it must be remembered that there will be a longer delay than that selected between switching on the unit and the production of the first tone.

This is caused by the need for the circuit to settle down and can be overcome by switching to the lowest time interval and waiting for the first tone to be produced before commencing to use the timer as part of an activity. ■

### Parts List

#### Resistors

R1	.....	5k6
R2	.....	15k
R3 to R11	.....	27k
R12	.....	100k
R13, R14	.....	680R
All	1/4W	5%

#### Potentiometers

VR1 to VR12	.....	10k skeleton preset, horiz. mnt
VR13	.....	Dual ganged 4k7 linear rotary

#### Capacitors

C1	.....	2200u, 16V electro. radial
C2	.....	10n ceramic disc

#### Semiconductors

IC1	.....	555 Timer
-----	-------	-----------

#### Miscellaneous

B1	.....	.9V battery
S1	.....	DPST min. rocker
S2	.....	single-pole, 12-way rotary wafer switch
S3	.....	DPDT min. rocker
WD1	.....	Piezoelectric transducer, single tone.

case, 115mm x 95mm x 37mm internal dimensions.

## Product Mart Classified

Turn unneeded  
goods into cash

Sound like a real challenge? It doesn't have to be. Not when you employ low-cost Product Mart advertising to sell the things you no longer need. Classified works for you by putting your selling information in the hands of people who are ready to buy. Call today for assistance in wording and placing your advertisement for maximum response.

Call (416) 445-5600




---

---

# Beginner's Bench, Part 4:

---

---

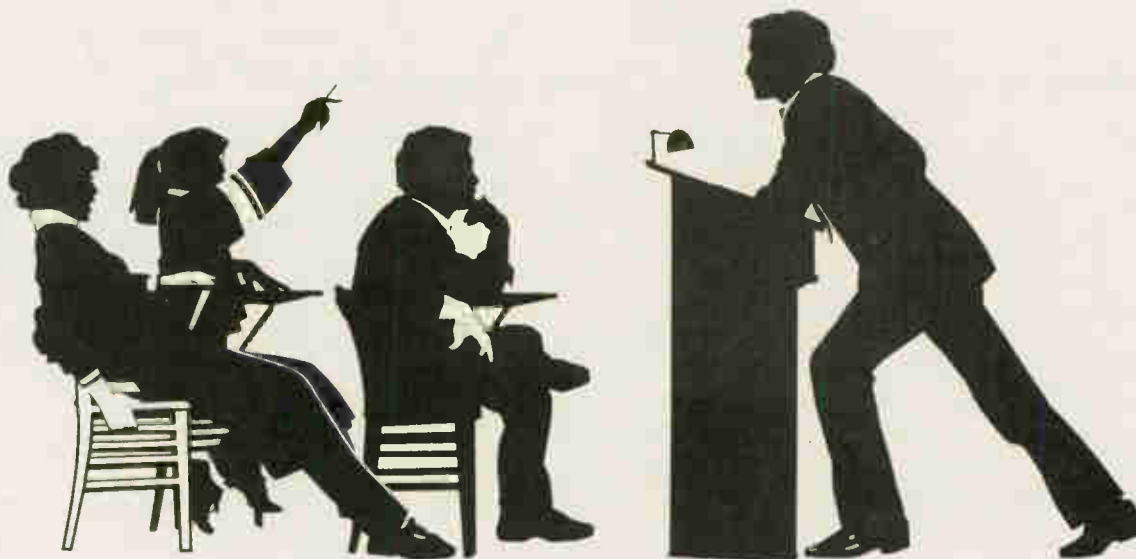

---

***An introduction to the hardware involved in processing basic digital logic.***

---

***By Michael Tooley and David Whitfield***

DIGITAL signals are very different from their analog counterparts. A digital signal does not change its signal slowly, nor does it vary freely over a range of levels. When the voltage level of a digital signal is not rapidly changing, it remains steady at one of only two possible levels or states. Any transition between these states occurs very rapidly (typically a fraction of a microsecond).

The two possible states for digital signals are commonly referred to as low/high, off/on, false/true or 0/1. Conventionally, these binary states are defined so that high/on/true/1 refers to a higher (more positive) voltage level while low/off/false/0 refers to a lower voltage level. This is known as *positive logic*. In *negative logic* the two states are simply reversed. To keep things as simple as possible, we will just refer to 0 and 1 to describe the binary logic states. Further, all our circuits will be positive logic.

The majority of circuits are designed so that 0 is represented by a voltage level near zero and 1 is represented by a voltage near the power supply level. In Fig. 3, the output remains near zero until the input circuit voltage exceeds a certain threshold voltage, at which point the output rapidly changes state from 0 to 1. This characteristic is in marked contrast with that associated with a conventional linear device shown in Fig. 4.

### **Digital Advantages**

Digital circuits offer a number of important advantages over their analog counterparts. In an analog system changes in component values due to the effects of ageing and temperature can have a marked effect on circuit performance and considerable care must be taken to ensure that such changes are compensated for. Applications requiring high precision are particularly troublesome in this respect.

Digital systems, on the other hand, use straightforward switching techniques and are very much less susceptible to individual component changes.

Another significant advantage of digital circuits is their inherent immunity to noise and interfering signals. With analog circuitry this is a particular nuisance when signals are very small and are thus easily contaminated by noise. Digital signals, however, have a very large amplitude and thus can be made relatively impervious to noise. The voltage levels used to denote the 0 and 1 states are separated by a 'forbidden region' in which no valid signal can exist.

### **Logic Families**

As part of the development of digital integrated circuits, a number of standard logic families have emerged. The importance of the concept of standard logic families cannot be over-stated. The basic

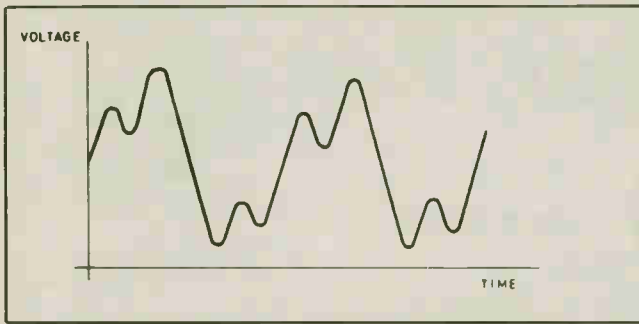


Fig. 1. Representative analog signal waveform.

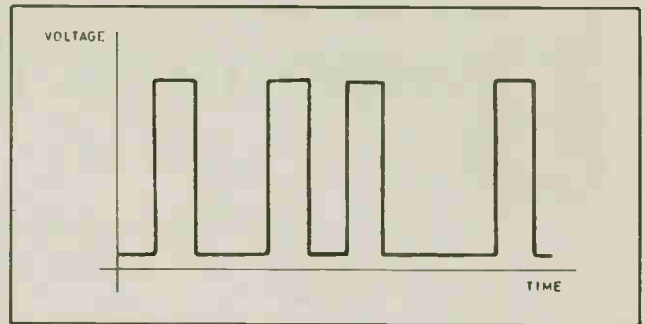


Fig. 2. Representative digital signal waveform.

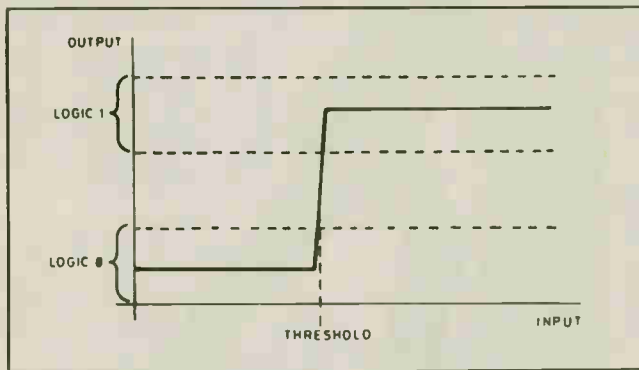


Fig. 3. Transfer characteristic for a typical logic device.

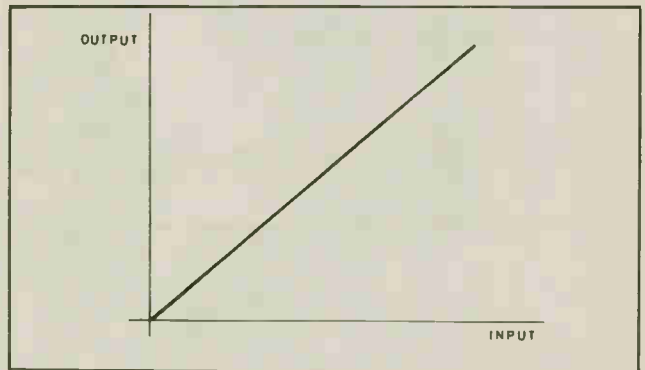


Fig. 4. Transfer characteristic for a conventional linear device.

gate in each range gives the name to the complete family of devices and determines the operational characteristics of the complete family. In this way, the designer is freed from the problem of checking that the logic levels between gates are compatible; the logic levels, power supply requirements, and general rules for dealing with such points as unused inputs are common to all devices in a particular logic family. This then allows the designer to concentrate on the functional design of his circuit and, once the basic rules are understood, greatly simplifies his overall task.

Over the years a number of different logic families have become available, but in the light of developments in technology many have become obsolete and have virtually dropped out of use. The main logic families to have emerged are listed below:

- Diode transistor logic (DTL)
- Transistor resistor logic (TRL)
- Resistor transistor logic (RTL)
- Direct coupled transistor logic (DCTL)
- Transistor transistor logic (TTL)
- Emitter Coupled logic (ECL)
- Complementary metal oxide semiconductor logic (CMOS)
- N-channel metal oxide semiconductor (NMOS)
- P-channel metal oxide semiconductor (PMOS)

Each of the logic families listed has its own special characteristics which may make it appropriate for particular applications. ECL, for instance, is extremely fast but consumes considerable power. In current practice, the two most commonly used logic families are TTL and CMOS.

At this point it is worthwhile stressing that the theory of digital logic is the same for all logic families. The difference between the various families is confined to the practical aspects of implementing circuits: power supply voltages, logic levels, power consumption, etc. A clear understanding of the theory of logic circuits is an essential prerequisite to the successful design of real digital circuitry, regardless of the logic family employed.

### The 7400 Family

Of all the families to emerge, TTL has earned by far the greatest popularity among designers of general purpose digital circuitry. The family is very commonly available at reasonable cost and in a variety of sub-families which offer significant advantages over the original standard family.

The internal circuit of a basic TTL gate is shown in Fig. 5. Readers should note the distinctive multi-emitter transistor which is associated with the input stage of TTL gates.

Standard TTL devices require a single-

rail power supply which provides a well regulated voltage of plus 5V. A typical TTL power supply using a monolithic three-terminal regulator is shown in Fig. 6.

The commonest TTL family is known as the 7400 series. Each IC in the series has a four or five digit number starting with 74. Examples are 7407, 74107, and 74207. These three devices are quite different from each other; the 7407 is an 'open collector hex buffer', the 74107 is a 'dual J-K bistable', and the 74207 is a '1k-bit RAM'.

Manufacturers add various prefix and suffix letters to indicate the origin and packaging of devices. The SN7407N, for example, is a 7407 gate manufactured by Texas Instruments and packaged in a 14-pin dual-inline-package (DIP). Readers should note that ICs of the same number will always have the same function regardless of the suffix or prefix.

The basic voltage characteristic for a TTL gate is shown in Fig. 7. As can be seen, there is a range of input voltages for which the output will be indeterminate. This simply means that any output produced by an input in this region cannot be predicted in terms of logic levels (0 or 1). Although possibly surprising, this is quite common in digital circuits and does not contradict the theory. A logic 0 is defined as a level of less than 0.8V while a logic 1



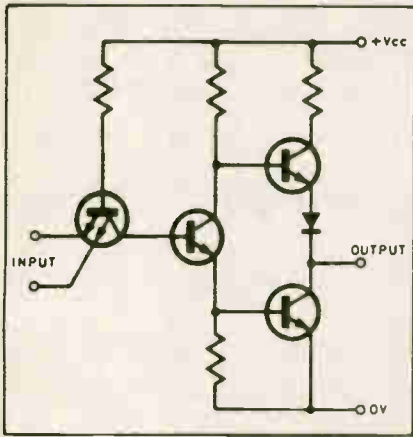


Fig. 5. Internal circuitry of a basic TTL gate.

is defined as a level greater than 2.4V (i.e., between 2.4V and the 5V power supply rail).

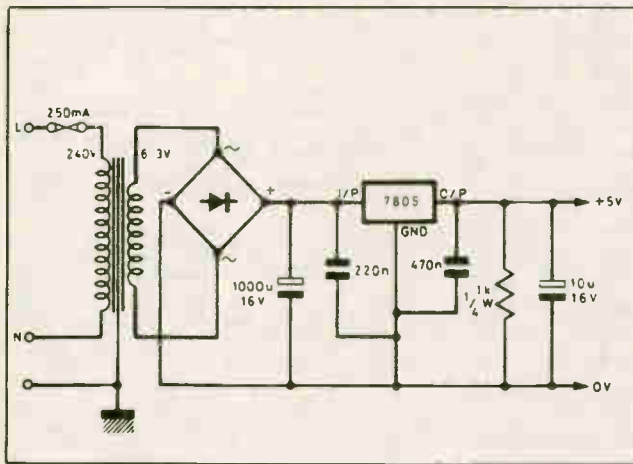


Fig. 6. A typical TTL power supply.

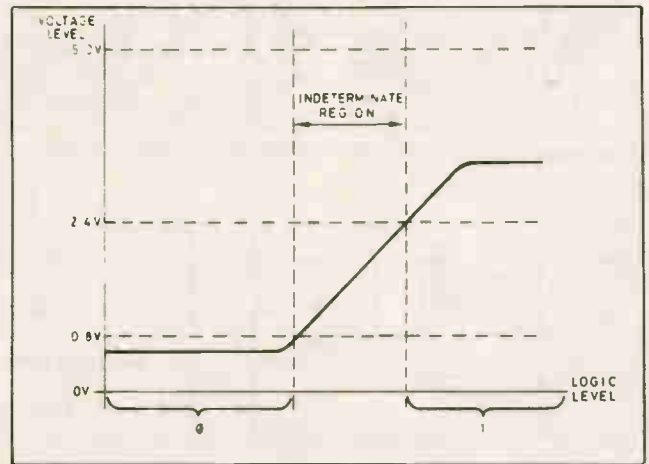


Fig. 7. Voltage characteristic for a TTL gate.

## Buffers

The simplest of all active devices is the buffer. This device has only one input and one output, and its logical output is the same as its logical input. Readers can be excused for wondering what the purpose of such an apparently redundant device might be.

Buffers are in fact quite useful and there are a number of situations in which they can be invaluable. The point to note is that although the input and output voltages of the buffer might be identical, the currents present can be very different. The output current can be greater than the input ('current gain'). In this way, buffers can be used to interface logic circuits to circuitry that requires so much current that the normal logic levels cannot be maintained by standard logic devices. Another less obvious application of buffers is concerned with regularizing and

standardizing the signals, in terms of logic levels, which are presented to or derived from logic circuits.

When drawing logic circuits, the symbol used to prevent a buffer is shown in Fig. 8. In logic diagrams it is normal to show the input on the left hand side and the output on the right. Thus, in most logic circuits the progress of a signal is left to right across the page. It is worth illustrating two of the rules which must be obeyed when connecting logic elements together (see Fig. 9). Whereas a single output can drive a number of inputs, a single input cannot be connected to more than one output. To put this more simply, circuits cannot be expected to behave properly if several outputs are directly linked together.

The 7407 is a typical example of a TTL buffer. This device actually comprises six separate inverters contained within the same 14-pin DIP package. The pin connections for the 7407 hex buffer are

output. This circle indicates inversion; the gate complements the input signal. Inverters share the same electrical properties as buffers with regard to current drain and thus can also be used in similar applications. If two inverters are connected together as shown in Fig. 13, called series, tandem or cascade connecting, the result will be the same thing as a non-inverting buffer.

The 7404 is a typical example of a TTL inverting buffer. This device is actually six buffers in one package.

## Truth Tables

The logical function of any given gate arrangement can be accurately defined using a 'truth table'. Such a table consists simply of lines representing all possible input states together with a column representing the logical state of the output. Fig. 15 and Fig. 16 show the truth tables for a buffer and an inverter. For both of these gates, there is only one input which can exist in

shown in Fig. 10. For a 14-pin DIP, the conventional supply connections are ground (0V) on pin 7 and 5V on pin 14.

## Inverters

An inverter, or inverting buffer, has only one input and output. Inverters are used to generate the logical opposite or 'complement' of a logic signal. The inverse of a 0 is 1 and vice versa.

The action of an inverter can be illustrated using the simple relay circuit shown in Fig. 11. When the logic input is at a 0 level, no current flows in the relay coil and the contacts remain in the state shown, producing an output of 1. When the logical input is 1, the relay contacts change over and the output becomes 0.

The symbol for an inverter is shown in Fig. 12. Note that it is almost identical to that shown earlier for a buffer with the addition of a small circle shown on the

one of two possible states. Thus the truth table consists of simply two columns: input (X) and output (Y).

## Fan-in and Fan-out

As mentioned earlier, the output of a TTL gate may be connected to the inputs of several other logic gates. The drive

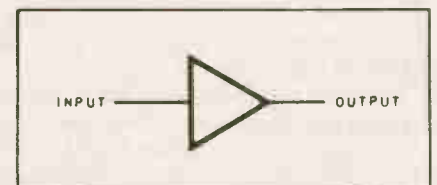


Fig. 8. Symbol for a buffer.

capability of a gate is known as its fan-out, and is usually expressed as the number of standard input loads which can be driven by the gate. For most TTL gates

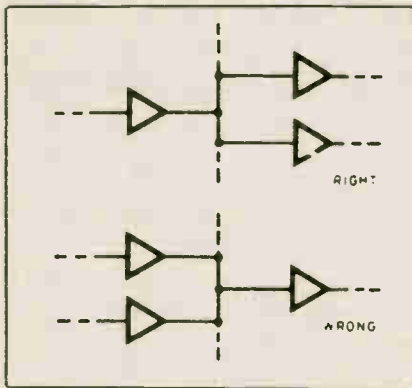


Fig. 9. Rules for connecting logic circuits.

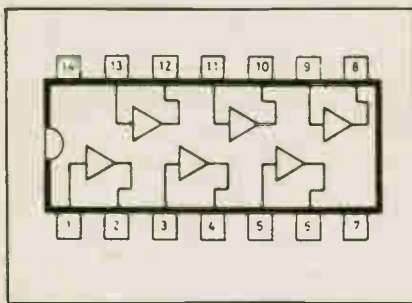


Fig. 10. Pin connector for a 7407 'hex' buffer.

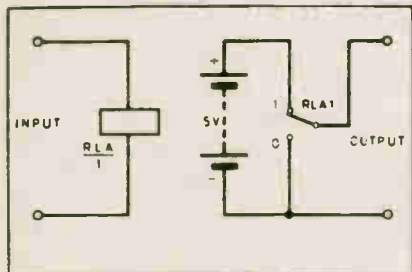


Fig. 11. Relay analogy for an inverter.

the fan-out is ten; one output can drive up to ten inputs.

The fan-in of a gate indicates its loading effect on a gate output, and is normally expressed as the number of standard inputs (loads) that it represents. The fan-in for most logic gates is therefore simply one for each available input.

**TTL I/O Currents**

The limits on fan-out are caused by the currents which must flow to hold the input of a gate at logic 0 and at logic 1. In TTL, the logic 0 currents usually predominate in determining fan-out. A standard gate input requires 1.6mA to flow between the input and common (0V). Thus, to support a fan-out of 10, the gate must be capable of 'sinking' a total current of 16mA. In the logic 1 state, the cur-

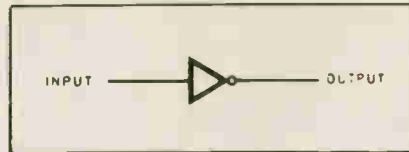


Fig. 12. Symbol for an inverter.

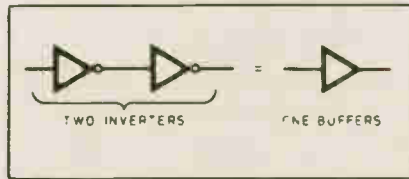


Fig. 13. Inverters connected in tandem.

rent flow is in the opposite direction and is considerably smaller. Standard TTL outputs are typically able to source 400uA while each input typically requires 40uA in the logic 1 state.

**Driving LEDs**

Light-emitting-diodes (LEDs) are commonly used as indicators in digital circuits. A typical LED requires about 10mA in order to provide a reasonably bright display. There are several methods of

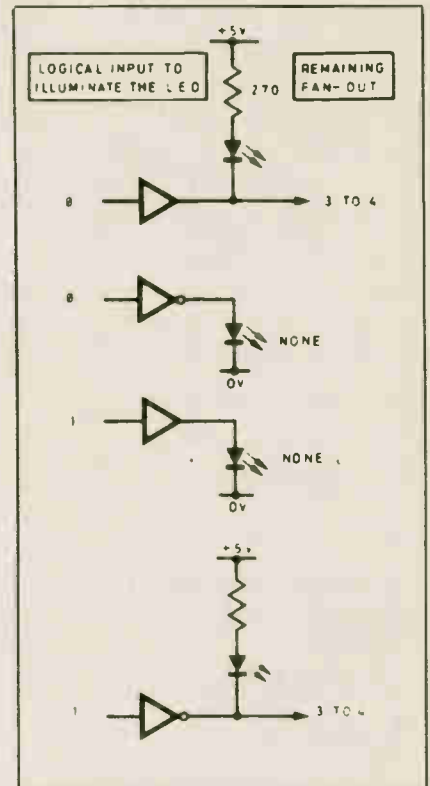


Fig. 16. Techniques for driving an LED.

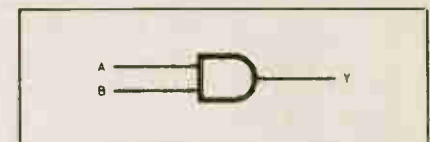


Fig. 17. Symbol for a two-input AND.

INPUT X	OUTPUT Y
0	0
1	1

Fig. 14. Truth table for a buffer.

INPUT X	OUTPUT Y
0	1
1	0

Fig. 15. Truth table for an inverter.

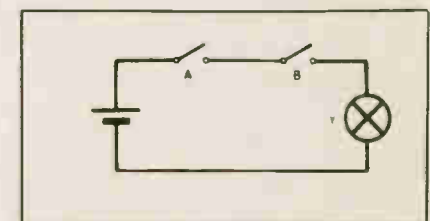


Fig. 18. Switch equivalent for a two-input AND gate.

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

Fig. 19. Truth table for a two-input AND gate.

driving an LED directly from a TTL inverter or buffer. The actual method chosen depends on whether the diode is to be illuminated for a gate output of 0 or 1 and whether the gate is required to drive any other logic gates in addition to the diode. The various techniques are shown in Fig. 17 together with the logic input/output states required to illuminate the LED and the fan-out remaining to drive other gates.



## Two-Input AND

The symbol for a two-input AND gate is shown in Fig. 18. In order to obtain a logic 1 output from this gate both inputs must be at a logic 1. Any other input combination will produce a logic 0 output. The operation of the gate can best be understood by drawing a simple 'switch equivalent' circuit like that shown in Fig. 19. In this circuit, a closed switch represents a logic 1 while an open switch represents a logic 0. In order for the lamp Y to light, both switch A and switch B must be closed. Thus a logic 1 is only obtained when both inputs are at a logic 1.

The truth table for a two-input AND gate is shown in Fig. 20. Note that, since there are two inputs and each input can exist in one of two possible states, there are four possible input combinations. To keep things neat we have arranged these in ascending order following a binary counting sequence where A is considered to be the most significant binary digit (bit).

The 7408 is a typical example of a two-input TTL AND gate. The device comprises four gates (a 'quad' gate) housed in the same DIP package.

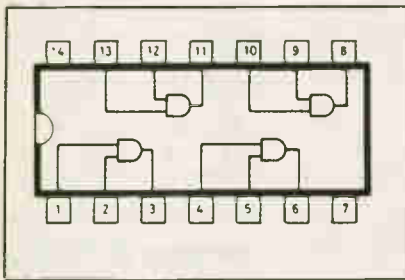


Fig. 20. Pin connections for a 7408 'quad' two-input AND gate.

## Two-Input OR

The symbol for a two-input OR gate is shown in Fig. 21. In order to obtain a logic 1 output from this gate, any one, or more, of its inputs must be at a logic 1. Putting

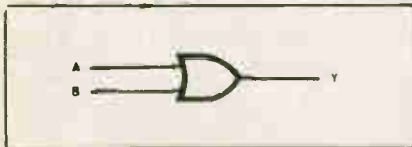


Fig. 21. Symbol for a two-input OR gate.

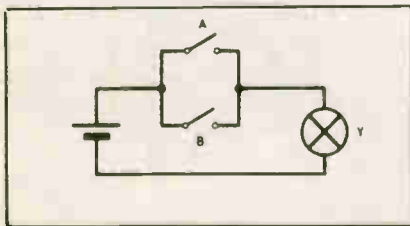


Fig. 22. Switch equivalent for a two input OR gate.

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

Fig. 23. Truth table for a two-input OR gate.

this another way, a logic 0 will only be obtained if both inputs are at logic 0. The 'switch equivalent' of the two-input OR gate is shown in Fig. 23. The lamp will light when either switch A or switch B (or both) are closed. The truth table is shown in Fig. 24. Again, since there are two inputs, there are four possible input connections.

## Two-Input NAND

The symbol for a two-input NAND is shown in Fig. 26. The output of this device is a logical complement to that produced by the two-input AND gate. The

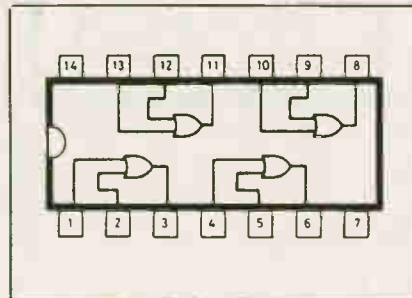


Fig. 24. Pin connections for a 7432 'quad' two-input OR gate.

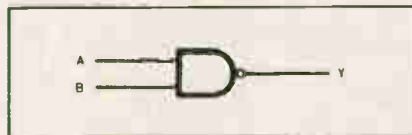


Fig. 25. Symbol for a two-input NAND gate.

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

Fig. 26. Truth table for a two-input NAND gate.

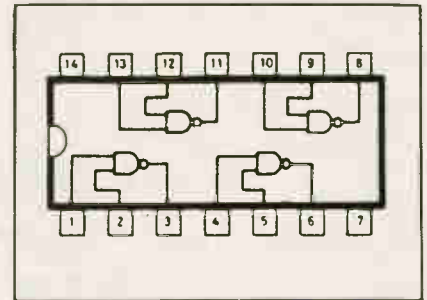


Fig. 27. Pin connectors for a 7400 'quad' two-input NAND gate.

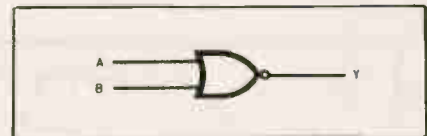


Fig. 28. Symbol for a two-input NOR gate.

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

Fig. 29. Truth table for a two-input NOR gate.

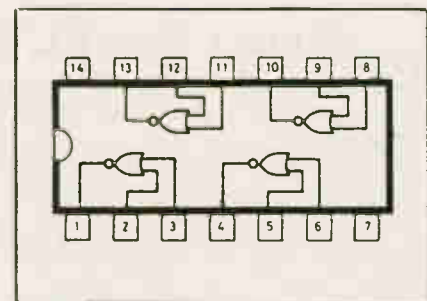


Fig. 30. Pin connections for a 7402 'quad' two-input NOR gate.

name stands for NOT-AND (and inverted AND). The truth table is shown in Fig. 27. Readers should compare this with that shown for the two-input AND.


## Two-Input NOR

The symbol for a two-input NOR gate is shown in Fig. 29. The output is the complement of the two-input OR gate; the name stands for NOT-OR (an inverted OR). The truth table is shown in Fig. 30.

# Three Almost Free for the IBM PC and

This month we really smoked the modem, listening to the wail of carriers long into the night to download the software for these three... count 'em... almost free software disks. There are two here for the IBM PC and one for the Apple Macintosh. All of them are crammed with the cream of the public domain. There are games, utilities, serious things... there was almost a computerized horoscope generator, but it got bumped by the helicopter game.

If you've encountered almost free software before, you may notice that there are fewer titles on these disks than there were on some of our earlier volumes. There is just as much software here... all the disks are within a few kilobytes

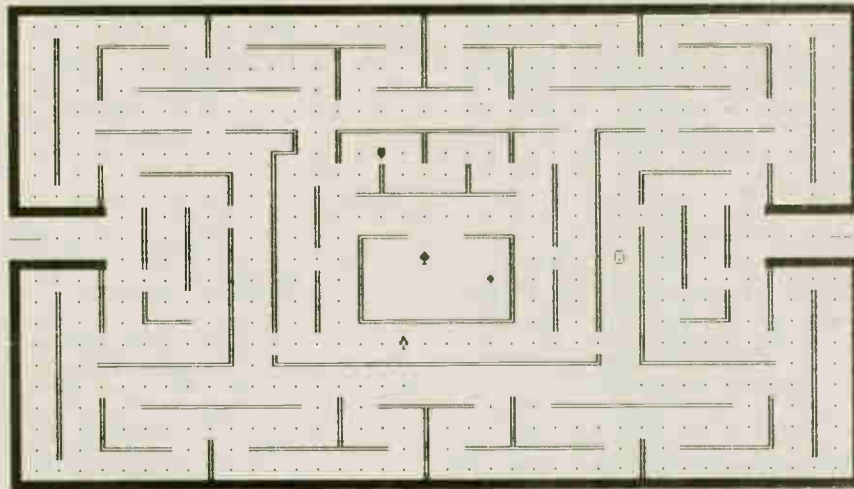

dots 453



P A C - G I R L Al J. Jiménez, Sep 26, 1982

## Almost Free PC Software Volume 11

**Pac Girl** is, predictably, a variation on the almost mythical Pacman game. This one moves like a greased cat on a skating rink, with all the speed and generally strange behaviour of the arcade version.

**Menu** allows one to set up a menu driver, tree structured operating environment that's a great deal friendlier and more manageable than is DOS. It's ideal for creating interactive systems for non-technical users.

**Z80MU** is one of the most brilliant bits of software we've ever encountered... free or not. It actually emulates a Z80 based computer running CP/M on the PC with no additional hardware... you don't even need a V20. It will run almost all CP/M software, including the old favourites like WordStar and dBase. However, it has features that CP/M never had... and even MS-DOS lacks.


**SERIO** is the assembler file from the July edition of Computing Now! that implements an interrupt driven terminal in higher level languages, such as C. It's also suitable for use with compiled BASIC. MASM is required to use this code.

**Breakdown** is a very peculiar program... it takes meaningful text, analyses it and generates meaningless... but very profound sounding... prose from it. It's fabulous in offices for creating reports if you're wondering if anyone really bothers to read your stuff.

**XMODEM** is a C language implementation of the XMODEM file transfer protocol, from the July edition of Computing Now!. It can be integrated into other programs to allow one easy access to telecommunications facilities. This code requires SERIO.. above... and version three Lattice C.

**GRABIT** is the screen grab program from the July Computing Now! It will make a useable text file from the contents of one's screen at the touch of a key. This code requires MASM.


Available for only  
**\$19.95**

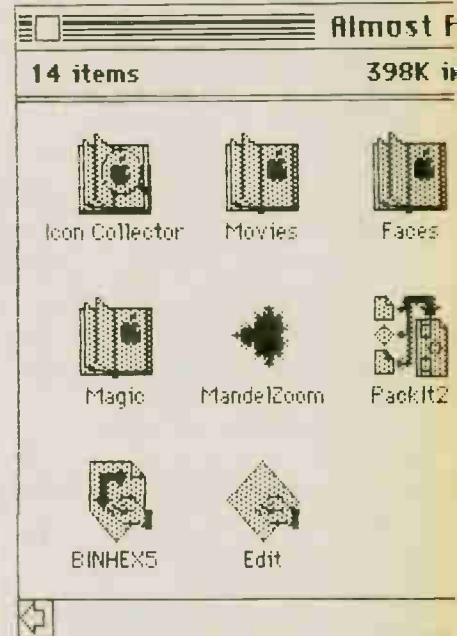
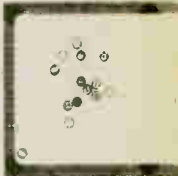
## Almost Free Macintosh

**Icon Collector** is a peculiar little program that allows you and use them in other things. It's a surprising amount

**Billiard Parlor** is worth the cost of the disk all by itself play most of the usual variations of pool and billia. unspeakable realism. It's wholly spectacular.



**MandelZoom** is the nicest Macintosh fractal generator thing considering the nature of the Mac's floating poi

**Red Ryder**. This is the latest version of this program... c dant rumours of bugs. This one runs perfectly, imp facilities, macros and enough toggles and menus to ke

**PackIt2**...not to be confused with regular PackIt... downloaded from bulletin boards. It's pretty well esse

**BINHEX5** is a file manipulation utility which allows M; Red Ryder.

**Edit** is the most sophisticated text editor available for tl to edit documents in multiple windows. It produces cl things.


Available  
**\$23.**

# e Software Disks
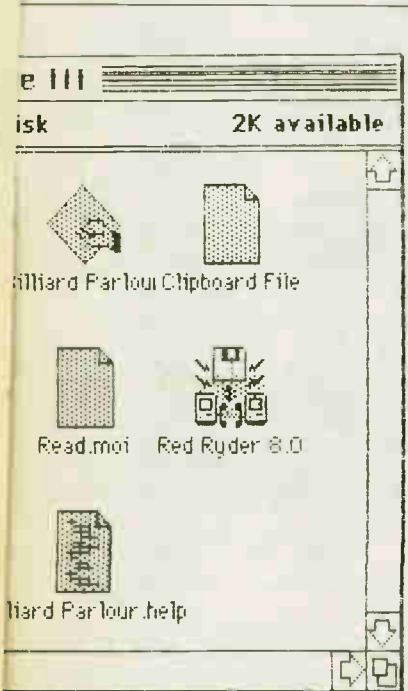
## he Apple Macintosh

of being full. However, these applications are more sophisticated than some of the earlier programs, and, as such, are bigger.

We've had quite a few requests to put the source files from some of the programs we've run in Computing Now! on these disks and, as such, these volumes contain several C and assembler programs. In actual terms, these take up only a few K of code, but they'll save you a lot of typing if you want to play with them.



### Software Volume IV

o locate icons in applications, swipe 'em, store 'em  
fun considering how pointless it sounds.

It's a glorious simulation of a billiard table. It will  
, and simulates the movement of the balls with



've come across. It's extremely fast... a remarkable  
library.


, at least, the latest one to be released without atten-  
menting a sophisticated terminal with download  
o your modem in stitches for a month.

will compress and uncompress P2T libraries... as  
tial if you're into telecommunications.

o files to be sent over a modem... another adjunct to

e Mac. Operating similar to MacWrite, it allows one  
an text files for use with a compiler, among other

for only  
95

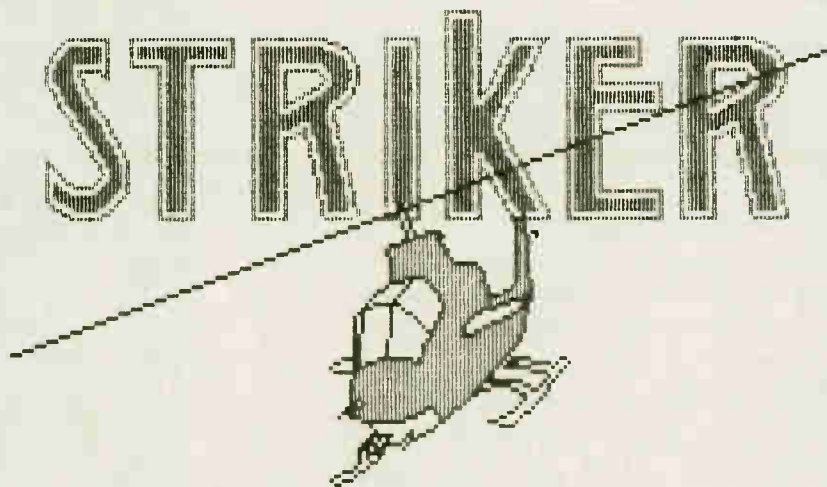

### Almost Free PC Software Volume 12

**CV** is a small utility to change the volume names on disks. Most humans never think to specify this when creating disks and, thereafter, it's usually unalterable. This is about six hundred bytes of salvation.

**Breakout Box** is an assembly language program that hides in memory and shows you what your serial ports are doing. It's the most invaluable thing going to solve your serial printer or modem glitches.

**Icon Maker** allows you to generate sophisticated bit mapped images with relative painlessness. It's easy to use and extremely colourful, producing data that can be incorporated into other programs.

**Shell** is another DOS menu program. This one is very fast, free of snow, and offers one access to virtually all the DOS features that one might want.

**Striker** is an experience. It's a brilliantly written helicopter game in the style of Choplifter, complete with professional high resolution graphics and running spies. This is one of the best public domain games we've ever encountered.

**Ramset** is a RAM expansion program from the July edition of Computing Now!. It allows one to have memory beyond the six hundred and forty kilobyte limit of the PC and to get around the long memory check time associated with lots of RAM.

**TRAP** is the high resolution Gemini patch program from the May edition of Computing Now!. It makes the Gemini 10x suitable for use with Personal Composer, but is easily modified to fix most bit mapped printing problems. This code requires MASM.

Available for only

**\$19.95**

plus seven percent Ontario disk tax

from

**Moorshead Publications**

**1300 Don Mills Road**

**Toronto, Ontario**

**M3B 3M8**

or you can order by phone and frustrate Canada Post. Call

**1 (416) 445-5600**

Fine print: All of this software was either written by ourselves or collected from public access bulletin boards, and is believed to be in the public domain. All of it has been tested and appears to be functional. However, we cannot assist you in modifying it to suit your individual applications.

We warrant that your disks will be readable. The post office, however, doesn't even warrant that they'll reach you without claw marks. If you are unable to read your disks, please contact us for a prompt free replacement.



# NEXT MONTH IN **Electronics Today**

## **Build Your Own Multimeter!**

Sure, you can buy one on the cheap, but think of the prestige of building one. Besides, it's packed with features.

## **Circuit Special!**

Our annual summer crop of all sorts of circuit schematics. Thinking caps on and soldering irons at the ready.

## **Marine Security System!**

While you read Electronics Today on your yacht, this system watches out for leaks, fumes and things that go bump in the bilge.



# This Month in

## **Computing! NOW!**

### **Amiga Survey**

We take a look at what's available in peripherals and software for the Commodore Amiga.

### **Build a PC**

Build your own PC clone using the Canadian-built Fullhouse motherboard.

### **Hot PC Video Cards**

No, they don't have scantily-clad women on them, but they will cause a certain amount of excitement with your PC's video.

### **Fast Fractals**

More fractals for the PC - in less time.



For Subscription or Advertising Information  
Call (416) 445-5600

# Radio Shadows

---

***Radio's shadow voices, practising an art dating back to WWII, but as contemporary as today's headlines.***

---

**By Gerry L. Dexter**

THEY speak of violence. They demand change. They call for revolution. They are quite unlike anything you can hear on an ordinary AM or FM dial. They are radio's shadow voices from secret stations.

Wherever there is a sore spot or an open wound on the world globe, there is usually at least one clandestine radio station doing its best to add fuel to the flames. These secret voices take several forms, some of which are more secret than others. The classic clandestine broadcaster is one which is run by a rebel group and operates in or near the territory of the government which it seeks to overthrow. The broadcasts are usually made from facilities which can be quickly knocked down and moved to another hidden location in the event government soldiers get too close. In other situations anti-government stations may be operated from more distant but still secret locations and be backed by groups not directly involved in the revolution. Often as not, no in-progress revolution is underway; the broadcasts may simply be seeking to stir up a population and help create conditions conducive to revolution.

Sometimes unfriendly neighboring governments get involved, either by providing aid to an existing opposition group, or working through a 'front' group the government has created for this purpose. In still other cases, the opposing government may simply run the stations on the sly and make no announcements about a backing organization, even denying any knowledge of the broadcasts.

Other opposition groups don't actually operate their own secret radio stations. Instead, they produce programs which are then carried by stations in countries which are sympathetic to that group's aims.

## **Black Clandestines**

Although the technique was much used in World War II and the Vietnam War, the so-called 'black' clandestine is a rarity today. A black clandestine is operated by

the government it speaks out against. But the tone of those broadcasts is less anti-government, and the object is to spread misinformation and to pull listeners away from the more strident opposition voice.

There are probably more clandestine broadcasters of all types on the air today than at anytime in the past decade, each pitching its own version of the truth. Most of these stations operate on shortwave frequencies and many of them can be picked up by listeners in North America, assuming ownership of a quality receiver and some patience. Others are difficult if not impossible to hear, since they are on the air for local and regional audiences at times and on frequencies which are not propagationally effective for a North American audience.

Here is an overview of the current clandestine broadcasting picture, worldwide.

## **Africa**

Clandestine broadcasters dot the African continent from the shores of the Mediterranean south to South Africa. In Libya, Colonel Khadafi has had a hand in several thinly veiled broadcast efforts, opposing at various times the governments of the Sudan, Lebanon and Egypt. He is believed to have been behind the brief appearance in the spring of 1985 of 'The Voice of Vengeance', which called on Arabs living in the Maghreb area to kill their Jewish neighbours and confiscate their property. At the moment, Libya continues to operate 'Radio Chad', (formerly Radio Bardai) which opposes the current government of Chad. In the winter months, this station can be heard to sign off at 3:30PM EST on 6,009kHz.

The Eritrean Popular Liberation Front, which seeks independence for the Ethiopian state of Eritrea and is backed in that effort by Somalia, operates the 'Voice of the Broad Masses of Eritrea'. It makes only rare appearances here, at 11PM to 12:30AM EST on a widely varying fre-

quency between 9,930 and 9,985 kHz. The station operates from rebel-held territory and also broadcasts the programs of the group seeking independence from the Ethiopian state of Tigre ('Voice of the Tigre Revolution'). Somalia adds its two cents worth by turning over transmitter time on the government-owned Radio Mogadishu to the 'Voice of the Eritrean Popular Revolution'.

Ethiopia returns Somalia's fire with 'Radio Halgan', supposedly operated by the United Voices of the Somali Opposition, carried over official Ethiopian government transmitters. This airs at noon on 9,595 kHz.

The current ruler of the Sudan are the target of broadcasts by 'Radio SPLA' operated by the Sudan People's Liberation Army and Sudan People's Liberation Organization. The broadcasts, originally hosted by Libya until a coup brought in a government more to Khadafi's liking, originally sought independence for the southern Sudan. The current broadcasts, believed to be coming from Egypt, now call for a total change in the Sudan.

Jonas Savimbi's UNITA opposition force in Angola runs 'La Voz de la Resistencia do Galo Negro' (Voice of the Resistance of the Black Cockerel), heard occasionally in Portuguese from 11:30PM on 4,972. Another Angolan opposition voice is 'La Voz de Verdade' (the Voice of Truth). Long thought to be a second UNITA station, that theory was recently denied by a US representative of UNITA. The station can often be heard signing on at 10PM on 4,950kHz. A third station, 'Cubanos en Africa' broadcasts on a sporadic basis to Cuban troops stationed in Africa, usually from midnight EST on 6,045. All three stations are believed to broadcast from the Transvaal area of South Africa, probably with the knowledge and support of that government.

Zimbabwe is the target of another South African-based clandestine, 'Radio

Truth', which is on the air in English nightly at 11:30PM on 5,015 and can be heard here fairly well under the right propagation conditions. The Zimbabwe government is building a high-power foreign service to combat what it terms 'anti-Zimbabwe propaganda' coming from Radio Truth.

In turn, South Africa is the target of the African National Congress and its 'Radio Freedom' program which is aired at various times over government-owned stations in Tanzania, Algeria and Ethiopia. Pretoria's hold on Southwest Africa (Namibia) is the reason for the 'Voice of Namibia' produced by the Southwest Africa People's Organization (SWAPO) and carried over sympathetic broadcasters in Angola, Tanzania, the Congo and Algeria.

### The Middle East

In the near and middle east, Khomeini's Iran has dissident broadcasts coming at it from every political angle. The communists are deeply into the game with the 'Voice of the Fedai's' which broadcasts on behalf of the Feda'lyan-e-Iran, airing broadcasts from noon to 12:45 and 4 to 4:45AM on 3,941 and 4,680. The 'Na-

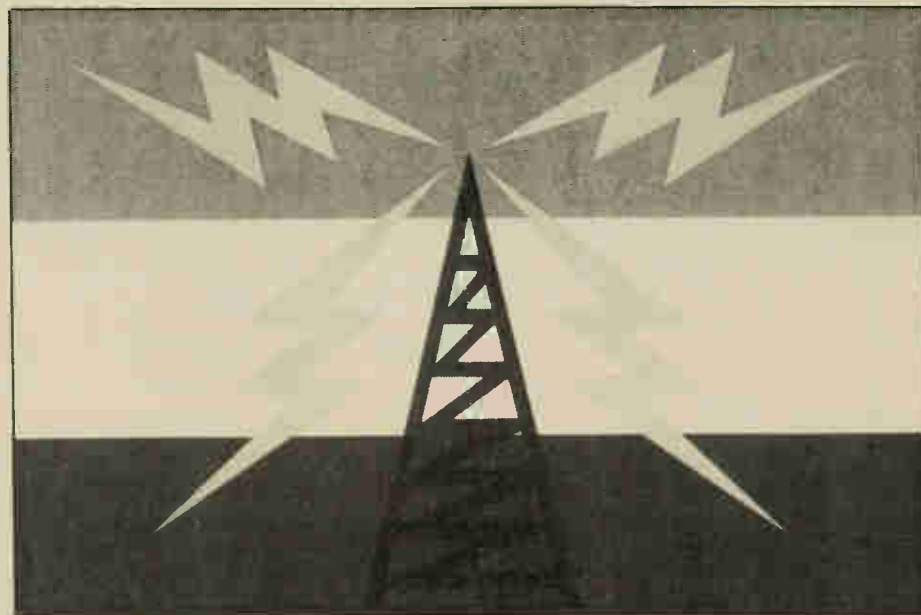


Fig. 1. A QSL card acknowledging reception of "Radio Vatan", a station operated by a group called "The Free People of Iran".

tional Voice of Iran', supported by the Iranian Tudeh (communist) party has been on the air since well before Khomeini came to power. It broadcasts from Baku

in the USSR at 12:30 to 1:15PM and 2:30 to 3PM on 5,915 and 6,025. 'Radio Iran Toilers', another communist outlet, is carried over Radio Afghanistan at 9:30PM on 7,200.

Komala, the Kurdistan division of the Iranian Communist Party runs the 'Voice of the Iranian Revolution' at 10:15 to 11:15AM and 9:30 to 11:30AM on frequencies between 6,366-6,383 and 6,420-6,440 as well as 7,245-7,300. Still another is the 'Voice of the Iranian Communist Party' at 10:15-11:15AM and 12:30 to 1:30PM around 4,500 and 6,500.

Anti-Khomeini opposition broadcasts are also aired by supporters of former Prime Minister Bakhtiar with 'Radio Iran' at 9 and 10PM, 8AM and 1:30PM on 3,360, 7,170, 9,400, 9,584, 11,640, 11,750, and 15,650. Several anti-Iranian stations appear to have merged into 'Radio Nejat-e-Iran' under the flag of the National Resistance Movement. This station can be quite widely heard at 11:30 to 1:30PM and 10:30PM to 12:30AM on 9,027 and 15,555 and is believed to come from Egypt. 'The Voice of Iranian Kurdistan' seeks independence for that region of Iran and is backed by the Kurdish Democratic Party. Still another is the 'Free Voice of Iran' at 10-11PM and 10:30-11AM, broadcasting over Iraqi transmitters on 3,367, 7,180, 9,585, and 11,765.

In contrast, Iraq is the target of only two known clandestine stations, the 'Voice of Iraqi Kurdistan' which wants independence for the Kurdish areas of Iraq and is a pro-Soviet outlet believed to be operating from Baku. The other, the 'Voice of the Iraqi Revolution', is pro-Syrian and thought to operate from Syria or the USSR.

## LOGIC PROBES FOR LOGICAL PEOPLE

CHOOSE THE PERFORMANCE YOU NEED FROM THE NUMBER ONE CANADIAN SOURCE FOR PROBES AND TEST LEADS

SPECIFICATION	PROBE LP10A	PROBE LP25	PROBE LP50	PULSER PR41	PULSER PG-1K
Frequency	17MHz	25MHz	50MHz	0.5/400Hz	1000Hz
Pulse Width	30nS	30nS	20nS	10uS	2uS
Input Limits	200V AC/DC	200V AC/DC	40V		
Fused Input	No	No	Yes		
TTL Levels 1/0	2.3/0.8	2.3/0.8	2.0/0.8		
CMOS Levels 1/0	70%/30%	70%/30%	70%/30%		
Input Impedance	1M	1M	1M/20pf		
Readout Display	3-led	3-led	7 segment		
Pulse Memory	Yes	Yes	No		
Tone Generator	No	Yes	No		
Illuminated Tip	No	No	Yes		
Replaceable tip	No	No	Yes	No	Yes
Output Cur.(max)				100mA	400mA
Variable pulse rate				No	1-50 pps
Single pulse				No	Yes
SYNC Input				Yes	No
Price*	\$33.00	\$71.50	\$203.50	\$82.50	\$181.00

PROBES AND PULSERS COMPATIBLE WITH TTL AND CMOS

\*Includes F.S.T. Add \$2.00 for shipping. Ontario orders add 7%  
BCS Store Hours:  
Mon-Fri 8 to 5, Sat. 10 to 1.

VISA & MASTERCARD accepted



980 Alness St. Unit 7,  
Downsview Ontario  
M3J 2S2 (416) 661-5585  
TELEX 065-28169



Turkey is the target of two of the longest-running clandestine outlets, both run by the Turkish Communist Party with transmitters in East Germany and Romania. 'The Voice of the Turkish Communist Party' is most likely heard at 11PM, midnight, 7, 8 and 11AM, noon, 3 and 4PM on 9,585. 'Bizim Radio' (Our Radio) airs at 9 and 10PM, 1, 2, 9 and 10AM and 1PM on 9,585.

Afghanistan's occupation by the Soviet Union is attacked by the 'Voice of Unity' (formerly the Voice of the United Muslim Fighters of Afghanistan), airing at 10:30AM on 15,050, 11,630 and 15,555. The 'Voice of Free Afghanistan' is believed to be operated by the Society for the Protection of Human Dignity and Freedom, based in Paris. Studios are in Pakistan near the Afghan border. Low power transmitters are said to operate from within Afghanistan with program tapes smuggled into the country.

### China

Mainland China is the focus of a group of unusual clandestines believed to be operated by the Soviet Union. By making use of short (5 to 10 minute) broadcasts on no set schedule, the operators try to portray the stations as being operated by dissidents within China itself, dissidents who dare not stay on the air for very long for fear of being tracked down. Among these are the 'Contingent of Proletarian Freedom Fighters', 'Radio Spark', 'The Voice of the People's Liberation Army', and 'The Central People's Broadcasting Station'. The latter uses the same name as China's main domestic network and the counterfeit CPBS uses news items from the real broadcaster, altering them to fit its own needs. All of these stations broadcast periodically between 4 and 8AM on such frequencies as 7,184, 7,525 and 9,267. Another, 'Radio Ba Yi' (Radio August First) has a more consistent schedule, 4 to 7AM on 12,120. All are believed to transmit from the Vladivostok area.

### Southeast Asia

Burma, Malaysia and Thailand are or have been subject to clandestine stations operated by the communist parties of the respective countries. The 'Voice of the Thai People' is believed inactive at the moment as is the 'Voice of the Burmese People', recently located and closed by the Rangoon government. 'The Voice of Malaysian Democracy' is on from 7:15 to 8:30AM on 6,700 and 8,998.

Kampuchea's occupation by Vietnam is berated by the 'Voice of the National Army of Democratic Kampuchea', believed to be in or near the Laotian border. This should be most easily heard around 5AM on 5,199. 'The Voice of Democratic Kam-



Fig. 2. Commander "Rigoberto", Jorge Salazar Regional Command, Matagalpa.



Fig. 3. A Mujahedeen colleague holding an RFK transmitter.

puchea' operates over the transmitters of Radio Beijing and will be most easily heard between 8 and 9AM on 5,250, 11,675 or 15,130. Both stations are operations of the Party for Democratic Kampuchea, the Khmer Rouge.

The factions led by Son Sann and former leader Prince Sihanouk share program time on a fairly new station operating on 6,325 from around 5AM. Recent reports state that the US helped to fund this station.


The two Koreas officially agreed some time ago not to use radio broadcasts to propagandize each other. Unofficially that very thing has been going on for

years. South Korea operates 'The Echo of Hope', which can be heard in the early morning hours on 3,985. North Korea has 'The Voice of Salvation', formerly the Voice of the Revolutionary Party for Reunification, which can be tuned early mornings on 4,117. A year ago, Pyongyang added a second station, 'Echo of the Public' which is on from 6AM on 5,885.

### Central America

The radio war is at its hottest in Central America and the Caribbean. The US government's Radio Marti service is neither the first nor the most recent of the

## LIQUID CRYSTAL DISPLAYS

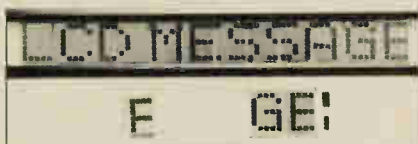

- Large 45x57mm character size 5x7 Dot Matrix LCD single digit display unit, built-in driver with memory, Serial Data Input/Output, can be cascaded into row configuration, available in various colours. . . \$19.95
- Programmable LCD moving message display board . . . . . \$399.00



- Standard and custom design LCD's available with fast lead time for prototype and production runs. Our engineering facility provides technical support to interface LCD's into your products.

For more information please call or write:

### ALL-CRYSTAL DISPLAYS

237 Lauzon Road, Windsor, Ontario, N8S 3L7

Tel: (519) 948-7225 Telex: 064-77624 WND

**FREE**

CATALOG AND APPLICATIONS GUIDE

## AFFORDABLE ENGINEERING SOFTWARE

PCDOS • MSDOS • CP/M • TRDOS

PDP — Plotter Driver Program For multi and single pen plotters	\$72.95
XFER — Transfer Function Synthesis Transfer functions ↔ Electronic circuits	\$72.95
TEKCALC — Scientific Calculator Program Screen graphics/Statistics/Programmable	\$72.95
COMCALC — Communications Design Spreadsheet Communications budget calculator	\$72.95
RIGHTWRITER — Report Proofreader Program Version 2 — Applies 2 200 rules of English	\$97.95

ACNAP — AC Network Analysis	\$72.95
DCNAP — DC Network Analysis	\$72.95
SPP — Signal Processing Program	\$72.95
PLOTPRO — Scientific Graph Printing	\$72.95
PCPLOT — High Resolution Graphics	\$72.95
LOCIPRO — Root Locus Analysis	\$72.95
ACTFIL — Active Filter Design	\$72.95
STAP — Static Thermal Analysis	\$72.95
MATRIC MAGIC — Matrix Manipulation	\$72.95

**BV** Engineering  
Professional Software



2200 Business Way, Suite 207, Riverside, CA 92501 U.S.A.  
(714) 781-0252 All price U.S. \$ include S&H

## Radio Shadows

anti-Castro programs being beamed to Cuba. A number of Miami-based groups have or are currently operating unlicensed transmitters. These include 'La Voz de Alpha 66', operated by the Alpha 66 group, which has half hour broadcasts three nights a week at 8PM on 6,666. 'Radio Antiorcha Martiana' (Torch of Marti) is aired at the same hour on 7,080, run by the Marti Insurreccional Movement.

Ex-Castroite Huber Matos, who spent two decades in Cuban jails, founded Cuba Independiente y Democratica a few years ago and the organization's 'La Voz del CID - Radio Camilo Cienfuegos' broadcasts are heard at good strength from an unknown site somewhere in Central America or the Caribbean. Another, more recent and mysterious station is 'Radio Caiman' (meaning 'alligator' or 'clever man') which runs at 6AM and 7PM; 9,960 in the morning, 7,470 in the evening. The station is very professional sounding and does not announce any backing, although a group calling itself 'Pro Libertad de Cuba' claims to operate the station. Anti-Castro groups contacted by this writer claim no knowledge of such a group.

The most famous clandestine today is probably Radio Venceremos, operated by the FMLN, the El Salvador guerilla movement. Venceremos operates from Morazan Department in rebel-held territory. Some of its programs recently have called upon listeners to supply suggestions about potential targets for sabotage or assassination. The station is well heard in North America on 6,565 variable at 7 and 9PM. Also in this frequency range is a black clandestine, also calling itself 'Radio Venceremos' but apparently being run by the Duarte government. 'Radio Farabundo Marti' is the station of the FMLN's Popular Liberation Forces and claims to be located in Chaltanango Department. Its broadcasts are less extensive than those of Venceremos, though it is scheduled on 6,740 at 7PM.

The various Nicaraguan contra groups have their own opposition voices too. 'Radio Quince (15) de Septiembre' is the main outlet of the Nicaraguan Democratic Force (FDN) which receives financial support for the broadcasts from the CIA. It is best heard from 11PM on frequencies such as 5,500, 5,555, 5,565, and 5,580. The various Indian opposition groups working under the MISURA Political Commission operate 'Radio Miskut' on a periodic basis around 8 or 9PM on 6,965 or 5,740. The ARDE group, once a main element of the opposition under the charismatic Eden Pastora, say that their 'Voz de Sandino' will return to the air. It formerly used 6,215 at various times during the evening. 'La Voz de la UNO' is the newest entry and apparently speaks on

behalf of the recently-organized umbrella group 'The United Nicaraguan Opposition'. It operates at 9PM on 5,039 and frequently relays the other clandestine stations.

Matching Radio Caiman in the level of mystery surrounding the broadcasts is 'Radio Monimbo', which beams an anti-Nicaraguan, anti-Cuban message at 7 and 9PM on 6,230. It too, is professionally produced, takes a relaxed approach in its programs and puts out very strong signals. It makes no mention on the air of any sponsoring organization.

Activity in South America is more often in the form of a rebel group taking brief control of a legitimate broadcaster in order to broadcast a brief message - at gunpoint. Peru's Shining Path guerillas make frequent use of this technique.

### Others

Algerian radio carries 'La Voz de la Resistencia Chilena' daily at 7PM on 9,510, 9,640, 9,640, 15,215 or 17,745. Radio Moscow carries a program called 'Radio Magallanes' (Magellan) for a quarter of an hour each evening, beamed at the Chilean dictatorship.


The Council for the Liberation of Surinam airs a half hour daily program over the facilities of La Voz del CID at 3:30AM on 9,940.

In addition to all this activity, there are other voices appealing for the overthrow of Khadaffi, the Palestine Liberation Organization produces the 'Voice of Palestine' which is carried on some middle eastern and African stations, and Tamil separatists of Sri Lanka are operating a limited power 'Voice of Tamil Eelam'. Recent years have also seen clandestine broadcasts aimed at Haiti, Mozambique and East Timor.

No matter what the political coloration of a clandestine and its backers, these stations play an important and sometimes vital role in achieving the ends they seek. They provide information (or disinformation), they can be morale builders, they can sow discontent. Sometimes they fail and slink away, gone forever. Sometimes they win and march into the capital with the army. Either way, the secret voices play a serious game, unconcerned with things like commercials and Top-40 play lists. Readers who own shortwave radios can tune in on many of these radio shows and, at the least, get a vicarious earful of the unending war on the airwaves. ■

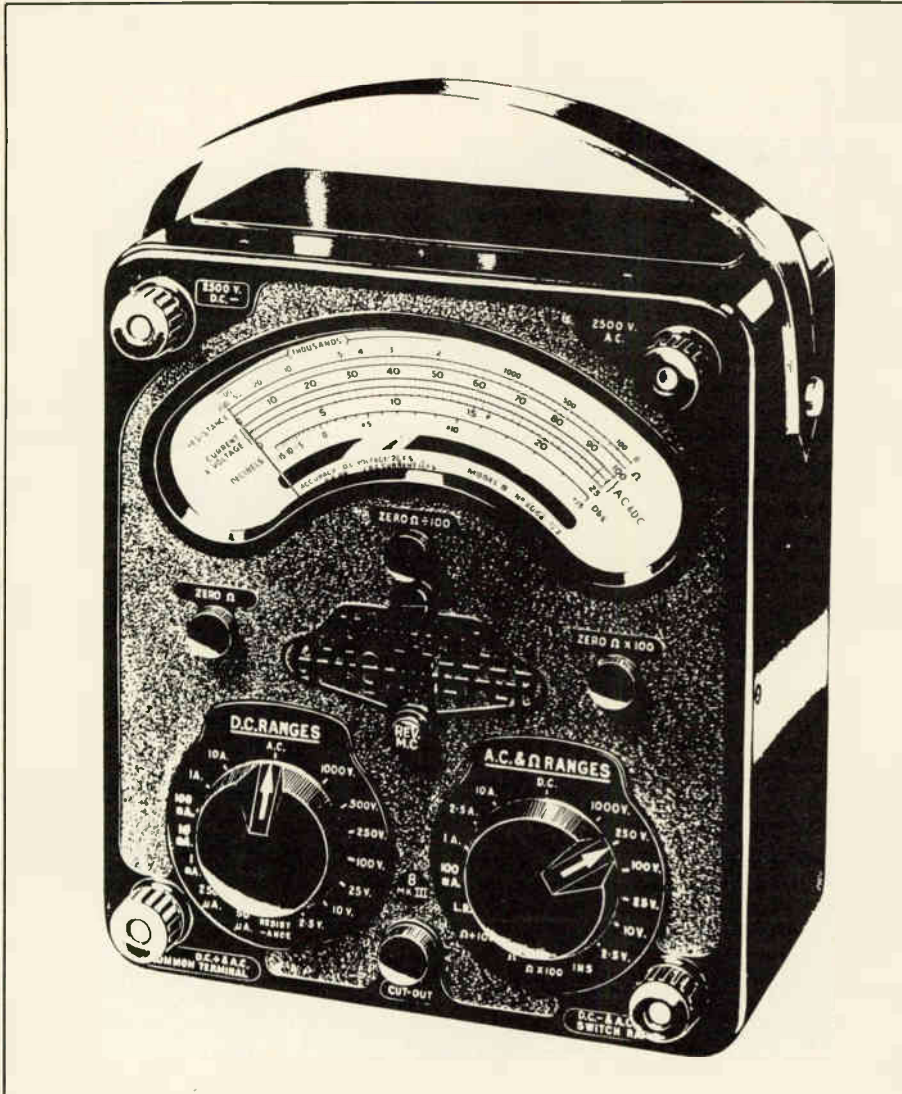**PRODUCT MART  
CLASSIFIED  
CALL (416) 445-5600**





resistance reading when you move the negative lead to the collector and emitter in turn.

It's worth noting that not all VOMs have the same lead polarity on the ohms setting. To determine polarity, switch to a high ohms range and place the leads across a good diode. If you don't get a reading, reverse the leads. Once you get a resistance reading, the negative lead will be the one connected to the cathode (usually a coloured band on one end of the diode).

It's also worth noting, when doing diode or transistor tests, that the ohms reading depends very much on the characteristics of the meters. Two different ohmmeters may give different readings from the same diode. This is due to a characteristic of any solid-state junction; the voltage across it varies non-linearly with the current through it, so its ohms reading will depend on the amount of current available from the meter circuitry.

### Lastly...

There are some special features that you might consider when shopping for a VOM. While all of them will usually read DC current, only a few read AC current, and this might be a feature you could use. Some will read resistance divided by 100, an unusual feature good for checking low-ohms resistors. Some have a mirrored scale to prevent parallax errors (reading the needle's position from the side introduces a small error). Overload protection is important; some inexpensive meters have none (or just a series resistor), some have diodes across the meter which will conduct and shunt the movement during an overload, and some, such as the Avometer, have a cutout button that pops out on overloads.

With all these features and the more obvious advantages, not to mention the low cost, the old-fashioned VOM is pretty hard to beat. ■

## ET-286 Plus HyperSpeed SuperComputer

As artificial intelligence and expert systems become more the rule than the exception in personal computer software, and as office automation takes on larger and larger tasks, superior machines will emerge with attributes that support **faster speed, massive memory and more extensive storage**. Naturally, the drive to communicate will also stimulate a variety of **networking applications**.

In the OEM Marketplace, just such a superior machine already exists: The **ET-286 plus**. The ET-286 plus pushes back the envelope in personal computer performance without sacrificing compatibility with more conservative products. The ET-286 plus is an IBM AT compatible singleboard computer from SOLTECH INDUSTRIES INC., designed for the most demanding applications in networking, office automation, CAD/CAM and high performance workstations. The ET-286 plus conforms to both the software and hardware compatibility requirements of the AT. It has the same form/fit characteristics, 6 full expansion slots, 2 PC/XT expansion slots, matching keyboard and power supply connectors **plus** high speed and high performance characteristics that set it apart from IBM and all the rest.

**It isn't enough to be merely compatible... be the best**

- 6/8/10 MHz 1 Wait State
- 6MHz 0 Wait State
- 12.5MHz Architecture
- 4 Meg On-Board Memory
- 6 Full AT Expansion Slots
- 2 PC/XT Expansion Slots
- 3 Serial Ports (Switchable)
  - RS-232
  - RS-422
- 2 Centronics Parallel Ports
- Built-In Clock/Calendar
- IBM AT Compatible BIOS

Also available: the standard for IBM PC/XT Compatibility, The ACS-1000 Super Computer.

- 1 Megabyte On-Board Memory
- Built-in Disk Controller
  - up to 4 Floppies
- 54 KB User Definable ROM
- Switchable: 4.77 or 8 MHZ
- Built-in Multifunction Board
  - Parallel Printer Port
  - 2 Serial Ports
  - Time-of-day Clock

### Seize Control of Your Hardware Destiny

If you are using board level microcomputers you can have greater power, versatility and reliability by using ET-286 plus or the ACS-1000 Singleboard Supercomputers. These products have been designed for the serious OEM.

To order or for more details call

604-888-2606 or write  
**Soltech Industries Inc.**  
 9274 - 194th Street  
 Surrey, B.C. V3T 4W2



**ANNOUNCING**

# Computers in EDUCATION **86**

**Hands-on Show and Conference**

**Arts Crafts Hobbies Building  
Exhibition Place, Toronto  
October 23rd, 24th, and 25th, 1986  
Thursday and Friday 10:00 - 9:00  
Saturday 10:00 - 5:00**


- A professional show for Canadian educators emphasising personal hands-on evaluation of educational software.
- A huge number of programs covering the entire educational spectrum will be available for private examination in the Computer Lab Facility.
- Computer Lab Facility will comprise over 100 educational microcomputers for unpressured personal testing of either the software or hardware.
- Demonstrations of the latest educational hardware.
- Wide range of classroom-orientated peripherals on show.
- Full programme of educational computing seminars.

**For Exhibitor Information contact:  
Arthur Nagels  
1300 Don Mills Road, Don Mills, Ontario, M3B 3M8  
(416) 445-5600**

# HAMEG 20MHz
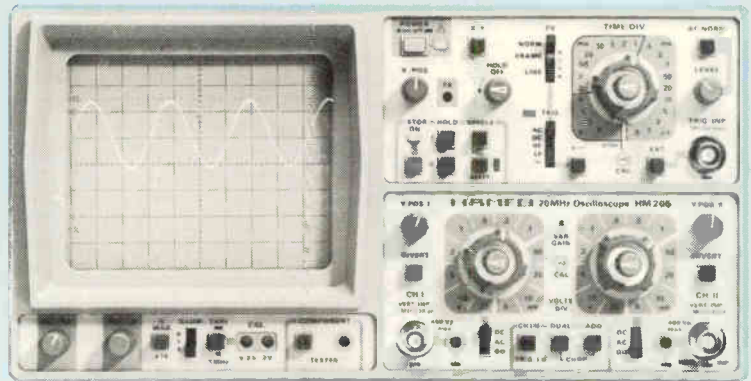
## Digital Oscilloscope

In addition to providing the impressive features of a well-designed 20 MHz real-time oscilloscope, the new HM 205 permits storage and display of slow-occurring signals and events (from 50 sec to 0.1 msec). None of the usual problems associated with long-persistence screens, such as trace flicker, streaking, and relatively short view time (max. 10 sec in Single-Shot mode) due to unavoidable loss of brightness, are present in the HM205.



**HM205 LIST \$1250**

**HM8001 WITH HM8037 & HM8027 MODULAR SYSTEM**


**DISTORTION METER  
&  
AUDIO GENERATOR**

Ideally suited to fit under either of these Oscilloscopes and other Hameg Models

## Analog Oscilloscope

The HM 203 Vertical Amplifiers incorporate variable gain controls and maximum input sensitivity is 2MV/cm over the full band width. Triggering up to 40 MHz is possible along with LINE, HF, DC and TV Sync. The instrument also has a component test built in.

**HM 203-5 LIST \$770**

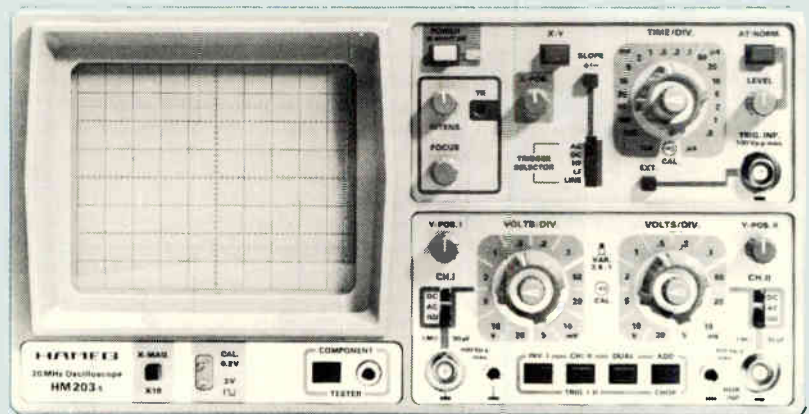

Complete audio distortion measurements are now economically possible with the new **BCS-DATE\***. Our **DATE\*** system is a low cost 4 unit system from 5HZ to 50KHZ. Probes and our H980 interconnecting cable set are also included.

**HM 203 DATE\***

**\$1895.00**  
COMPLETE

**HM 205 DATE\***

**\$2395.00**  
COMPLETE



980 Alness St. Unit 7,  
Downsview, Ontario.  
M3J 2S2  
(416) 861-5585  
TELEX 065-28169  
Mon-Fri 8-5 pm, Sat 10 am-1 pm

\*Distortion, Audio Test Equipment



# To Over 30,000 Installations, MultiLink<sup>®</sup> MEANS Multi-User.

At over 30,000 sites, as many as one-quarter of a million users tap into the power of MultiLink<sup>®</sup> Advanced everyday.

Since 1981, they've come to rely on our multi-tasking, multi-user system for compatibility with their favorite software, and the ability to share disks, files, printers, and programs in a *true* PC-DOS environment.

From the largest of the Fortune 500 to the smallest in small business, MultiLink<sup>®</sup> has provided a cost-effective multi-user solution that's available from no one else.

**MultiLink<sup>®</sup> Means Cost-Effective Timesharing on a PC.** MultiLink<sup>®</sup> Advanced utilizes the principle of timesharing by sharing a central PC's peripherals, files, and processor time among nine users. Up to eight inexpensive terminals can be connected to a single non-dedicated IBM PC, XT, AT or 100% compatible using standard RS-232 ports. Each terminal effectively emulates a PC having up to 512K RAM.

PC-Shadow<sup>™</sup> Workstations shown below, even have an AT look-alike, as well as work-alike, keyboard, display, and serial port. In addition, password-protected remote access via modem can be made with either dumb terminals or PCs running our terminal emulation software.

**MultiLink<sup>®</sup> Means PC-DOS Compatibility with a Software-Driven System.** Lotus 1-2-3, Symphony, WordStar, dBASE III, & Multimate are just a sampling of the wide variety of PC-DOS software that's fully compatible.

Our software-driven system is also IBM NETBIOS compatible, so programs that are written for IBM's Token Ring will run on our multi-user system, as well.

**MultiLink<sup>®</sup> Means Multi-User to Leading Computer Publications.** Whether you read *PC Magazine*, "MultiLink<sup>®</sup> Advanced delivers on...convenience, speed, and flexibility," or *InfoWorld*, "If you want a low-cost multiuser system with up to eight terminals, MultiLink<sup>®</sup> Advanced is worth a serious look," it becomes clear that MultiLink<sup>®</sup> Advanced is a formidable contender in the multi-user marketplace.

**See What MultiLink<sup>®</sup> Can Mean to You.** Learn, firsthand, how our multi-user system can benefit your company. Call The Software Link TODAY for complete information and the authorized dealer nearest you. MultiLink<sup>®</sup> Advanced is \$745 and comes with a money-back guarantee.

MultiLink<sup>®</sup> is a registered trademark of The Software Link, Inc. MultiLink<sup>®</sup> Advanced & PC-Shadow<sup>™</sup> are trademarks of The Software Link, Inc. IBM PC, XT, AT, PC-DOS, Token Ring, & NETBIOS are trademarks of IBM Corp. WordStar, dBASE III, Multimate Lotus 1-2-3 & Symphony are trademarks of MicroPro, Ashton-Tate, Multimate International & Lotus Development Corp., respectively.

# MultiLink<sup>®</sup> ADVANCED



THE SOFTWARE LINK, INC.

250 Cochrane Drive, Suite 12 Markham, Ontario L3R 6B7

CALL: 416/477-5480

Dealer Inquiries Invited

Circle No. 21 on Reader Service Card

