

HOW TO STOP THE HOWL

Amateur Wireless And Electrics

Vol. III. No. 58.

SATURDAY, JULY 14, 1923

Price 3d.

PRINCIPAL CONTENTS

A NOVEL NOTE
MAGNIFIER

INDOOR EARTHS AND
THE LAW

MAKING A VARIABLE
GRID LEAK

HOW THE MICRO-
PHONE AMPLIFIER
WORKS

WORKSHOP HINTS

SIMPLE TESTS FOR
CONDENSERS


POSITION AND DIREC-
TION FINDING

ON YOUR WAVE-
LENGTH

EXPERT REPLIES TO
READERS' QUESTIONS

WELL ILLUSTRATED

Registered at G.P.O. as a Newspaper

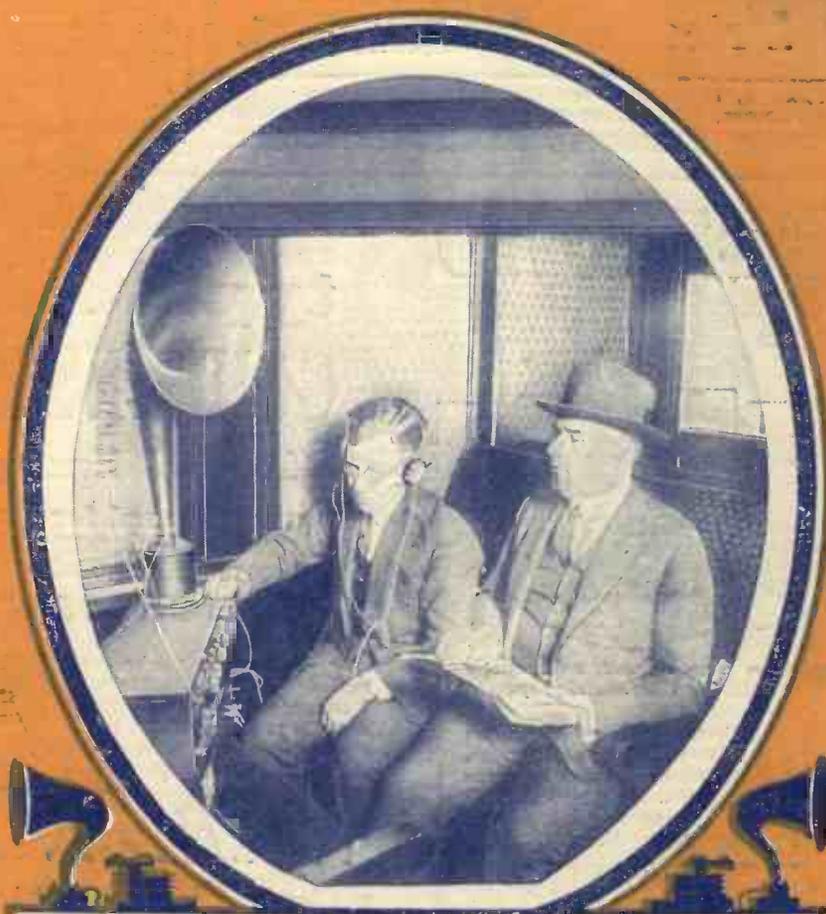

WIRELESS ON LONG-DISTANCE TRAINS

Many Experiments are being carried out with a view to the installation of receiving sets on passenger trains.

ECONOMIC ELECTRIC LTD.

Branch and Works: TWICKENHAM

NEW "XTRAUDION" VALVE SENSATIONAL DATA!

Name of Valve.	Amplification Factor.	Internal Resistance in ohms.
V24 (Ediswan), No. 3828	6.3	192,000
V24 (Ediswan), No. 3794	8.2	290,000
V24 (M.O.V. 1190)	5.0	70,300
Métal R	11.5	73,200
A bad (cheap) French R	4.4	1,362,000
Ora 6122	8.2	376,000
Ora 6220	7.3	568,000
"XTRAUDION"	12.0	90,700
M.O. valve, R4944	10.5	93,700
R4B (G.E.Co.), No. 248	13.8	84,200
B.T.H. "A" (28880)	6.9	130,000

The above table is an extract from "THE RADIO EXPERIMENTERS HANDBOOK," Part II, by Philip R. Coursey, B.Sc. (Eng.), and needs no comment from us; suffice to say that the "XTRAUDION" takes only 4 amperes at four volts and requires an anode potential of 30-75 volts.

Price 15/-

Good Detector

Excellent Oscillator

Unequaled Amplifier

Head Office: 10, FITZROY SQUARE, LONDON, W.1

40-Page Wireless List, Post Free, 4d.

Showrooms: 303, EUSTON ROAD, N.W.1

4,000 OHMS PER PAIR

BONTONE PHONES Britain's Best

**Marvellous Efficiency—
: Marvellous Price :
16/6**

per pair, plus 1/- extra for postage.

Manufactured entirely in our works, Goswell Road and City Road, under mass production, hence the quality and price.

Guarantee.—We agree to return cash in full if not satisfied, and returned to us undamaged within 7 days.

We specialize in the manufacture of Precision Tools, stamped and turned parts, in large quantities. Send us your enquiries.

We are experts in the production of Magnets of all shapes and from Tungsten or Chrome steels.

SPECIFICATION

Case.—Best hard Aluminium, solid drawn and accurately finished.

Magnets.—Latest type horseshoe pattern of finest Tungsten Steel, resulting in strong and permanent magnets.

Core Pieces.—Finest quality of special soft iron, with fibre insulating checks.

Wire.—Each earpiece is wound with best English high conductivity copper wire to 2,000 ohms by special machines.

Diaphragms.—Made from selected Iron, perfectly flat to ensure perfect tone.

Spacing Washers.—Special thin hard brass to obtain correct distance for perfect results.

Ear Caps.—Solid ebonite of ample size, best finish and correctly proportioned.

Insulation.—This is a particular feature and receives careful attention, finest materials only being used.

Head Bands.—Made from best quality Spring Steel, copper-plated, oxidized, and relieved, giving beautiful finish.

Testing.—Every earpiece is tested thoroughly, during and after assembly.

Finish and Workmanship.—Of the best possible throughout.

Assembly.—By skilled labour under expert supervision.

B. D. & Co.


(Edward A. Boynton)

ADMIRALTY AND WAR OFFICE CONTRACTORS.

Works: 167-173, Goswell Road, E.C.1.
1-9, Goswell Place, E.C.1.
361-363, City Road, E.C.1.

Offices: 173, Goswell Road, E.C.1.
Telephone: Clerkenwell 6238.

OUR IMPROVED

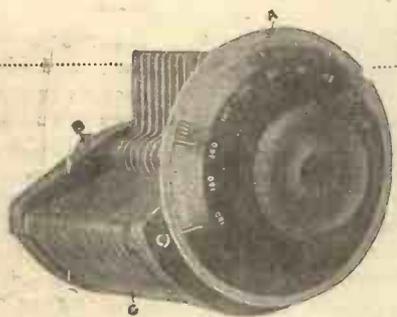

type All. CONDENSER

—for Panel Mounting—

- SPECIAL FEATURES:**

 - A. Aluminium Screening Disc, which besides enhancing the appearance of the Dial as it lies flush with the Panel, prevents the hand of the operator producing capacity.
 - B. Metal to metal adjustable bearings, of which we were the originators, as applied to Condensers.
 - C. 22 Gauge hard Aluminium Vanes.

Complete in every respect, and exactly as illustrated, to the following specification—

Rotary, Air Dielectric, 22 Gauge Aluminium Vanes, Metal to Metal Adjustable Bearings. Spacing between plates sufficient for pressure up to 1,000 volts. Engraved Ebonite Dial. Is suitable for mounting on any panel up to 1/8" thick by drilling 3 holes. Supplied with screws for fixing.

PLATES.	PRICES:
57 ...	'001 ... 10/-
29 ...	'0005 ... 8/6
19 ...	'0003 ... 6/9
13 ...	'0002 ... 5/6

Postage and Packing: 1, 1/-; 2, 1/3; 3, 1/6.
If more than 3, kindly include ample for packing and carriage.

Don't allow our low prices to prejudice you. They are no criterion whatever of the value we offer. Our motto is QUALITY FIRST, and every Condenser carries our money-back guarantee.

—is unsurpassed for workmanship, quality of materials employed, efficiency and PRICE, which, by the way, has NOT been INCREASED.

TESTIMONIAL—ONE OF HUNDREDS:—
Gentlemen,
23a, Old Bond Street, W.1.

With reference to the Condenser '001 which you supplied to our order yesterday. This was fitted to an H.P.R. Tuner and amplifier last night with the most satisfactory results. The tuning of the Paris concerts has been made infinitely easier. We consider your instrument the most wonderful value and a model of what workmanship should be. You can make any use of this letter you like.

All originals can be inspected.
Yours truly, A. O. FRENCH BREWSTER.

WARNING!

Don't buy shoddy sets of Condenser parts which are well nigh impossible of assembly, or half assembled Condensers, which are merely thrown together.—BUY OURS. We specialise in Condensers. Complete in every respect and exactly as illustrated.

FALLONS

Prompt Delivery.

THE CONDENSER PEOPLE, Cash with Order.

230a, HERMITAGE ROAD, LONDON, N.4.
Finsbury Park, near the Manor House.

FALLON CONDENSER MFG. CO., LTD., Makers of Half the World's Variable Condensers.

Amateur Wireless

and Electrics

Vol. III, No. 58

July 14, 1923

Stop that Howling!

THERE are times when one's set commences to howl with a perseverance worthy of a better object, and with such ferocity that one is driven to profanity. Weird cat-calls, shrieks of agony, and all the moans of a soul in torment emanate from headphones or loud-speaker. One wonders sometimes how so small an instrument can produce such a volume of discordance.

Re-radiation or Oscillation

On the commencement of the howl tap the finger on the aerial terminal to test whether the howling is due to re-radiation or oscillation, for if that should be the case you will be reproducing your own trouble in the receivers of other people up to a half or three-quarters of a mile away. If oscillation is present a distinct "plop" will be heard in the phones as your finger touches the terminal, followed by another click as your finger is removed.

The remedy in this case is so simple that one wonders why offenders continue to inflict such unnecessary trouble on other people: the reaction coupling is too tight—loosen it. If this does not check the

howling, perhaps your filaments are too hot: turn them down until the interference ceases.

Another Reason for Howling

But the fact that your set is howling need not necessarily mean that it is

To the amateur whose set seems particularly prone to howl this article is specially addressed. Systematic searching for the trouble will always result in its discovery and elimination, and the best system of trouble-hunting to work upon is here explained.

radiating and causing trouble to other people. The cause of the howl may be due to certain parts of the set reacting together and causing internal oscillation. Therefore if on testing for reaction in the manner described above, no "plop" is heard and the set is howling continuously, you can be pretty certain that the trouble is due to inter-reaction between some of the internal parts of the set.

Connections



First of all examine the external connections and see that all are firmly made and that the aerial and earth leads are not running too close together or parallel. Then go over the internal wiring and make sure that no two wires are too close or running parallel where not well insulated, especially the connections to the grids of the valves. Try the effect of removing or substituting the grid-leak, particularly if the detecting valve is a new one, or if you are using a different one from that with which you usually listen-in. It often happens that the grid-leak is unsuitable in such a case.

Lastly, the valve you are using may have become "soft" or gassed by excessive plate voltage, and the latter is causing the trouble. Besides turning down the filaments, try reducing the H.T. voltage.

When "Fading" Occurs

"Fading" is another annoying fault that sometimes occurs in a valve set, and the worst of it is that it generally happens at a critical moment when you are enjoying a certain item or piece of music.

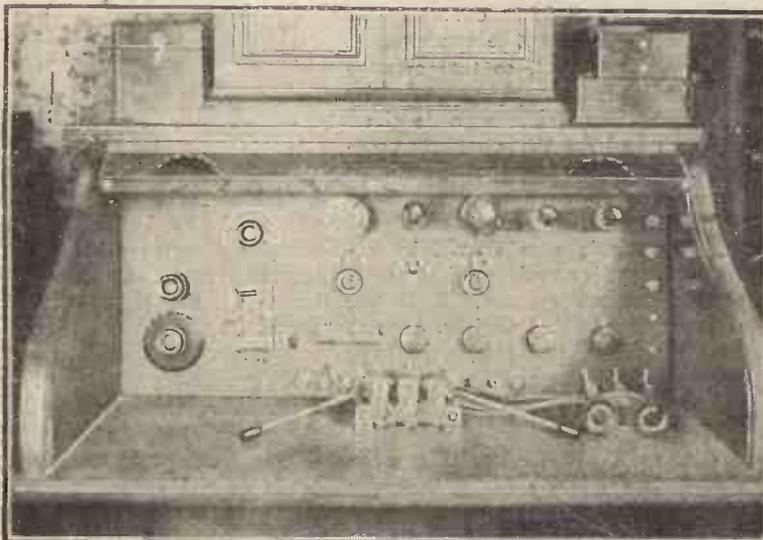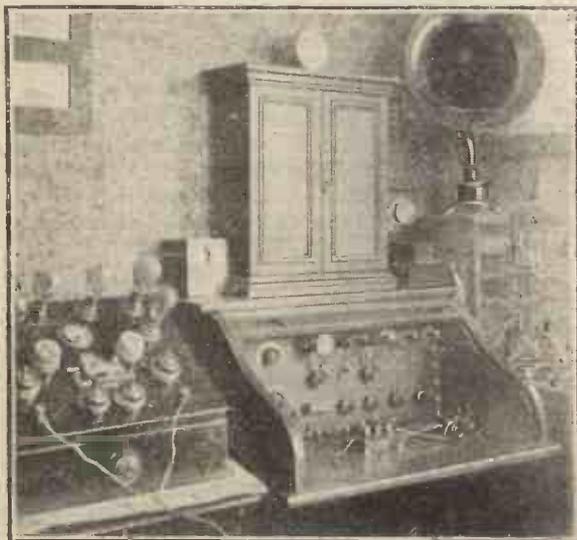An Amateur Receiving Set in a Roll-top Desk



How a receiving set can be conveniently mounted in a roll-top desk is shown in the above photographs, which depict a station built by Mr. F. Worrall, of Bolton. The illustration on the left shows the whole receiving station and that on the

right is a near view of the panel. The receiver is a 4-valve set, so arranged that either one, two, three or four valves may be used. A switch is provided to use either direct or loose coupling, and another to remove the reactance connections.

The circumstances by which fading occurs are more often than not beyond the control of the amateur. Sometimes it is due to some peculiarity in the formation of the earth, which causes the wireless waves to be occasionally deflected from their direct course. Again, it may be due to another transmitting station which is sending on a wavelength nearly the same as, or a direct multiple of, that of the station you wish to hear. When this happens the waves of the two stations become jumbled together and alternately get in and out of step with one another, causing beats that occur at regular intervals. If these beats occur rapidly they cause the receiving set to howl, or they may alternately cause the signals to increase and decrease, so producing the phenomenon of fading.

Here again the grid leak may be at fault, and this portion of the set should be overhauled as mentioned above. Test the two batteries also, as a battery that is running down may cause irregular signal strength, though it is more likely to give rise to a gradual fading away of signals until there is dead silence. If this is the case a few minutes rest will often allow the batteries to recuperate a little and provide another short spell of entertainment, when the same thing will be repeated.

Small Details that Count

Do not forget that more troubles are likely to develop from the neglect of small details than from any really radical fault in the set. Loose leads account for a great many of the little odds and ends that are constantly cropping up to annoy you. All sorts of troubles can be traced to loose connections—crackling noises, "frying," lack of signals or loss of strength, or even fading if the loose connection is moving about very slightly.

Keep your set clean. A considerable amount of leakage may occur over the surface of a panel if it is covered with dust. Moisture, too, is apt to condense on the surface of the panel, so that cleanliness in this respect is amply rewarded by increased efficiency. Don't forget to clean the valve legs and the valve sockets occasionally. The thin coating of rust or oxide which is wont to form on them can have a considerable bearing on your signal strength. Terminals also should be examined at frequent intervals, so that clean, tight connections are assured. Switches, especially of the "knife" variety, require even more attention, and should be kept as clean and bright as possible.

Look to Your Batteries

A word about the batteries. Keep the surface of both spotlessly clean, in order to minimise the risk of leakage. This will be rather difficult in the case of the L.T. accumulator, owing to the tendency of the acid to creep, and of the gassing that takes place when the cells are charged. But keep the surface of your accumulator as clean as possible. Another point to


remember is to keep the acid solution in the battery up to its required level—quarter of an inch above the surface of the plates—adding clean distilled water to make up for evaporation.

Then periodically the cells should be cleaned out and refilled with fresh acid of the correct purity and specific gravity. This job is generally left to the electrician,

and should be done every six months or so, and more often if the sediment that collects on the bottoms of the cells shows any likelihood of touching the plates.

By keeping the foregoing hints in mind, and following them, the amateur can rest assured that he is helping his set to attain that purity of reception which is, or should be, the aim of every one of us. A. J. B.

Making a Variable Grid Leak

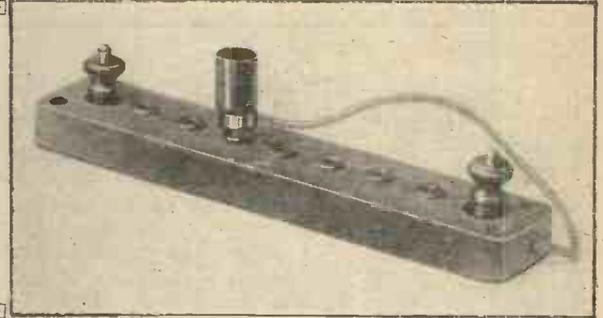

Variable Grid Leak.

TWO odd strips of ebonite or fibre, two terminals, seven contact studs, a short piece of flex wire, a few lines drawn with a pen, an old wander plug and six small screws are all that is required to construct a very efficient

each hole with the exception of the space between the last two holes (see Fig. 1). Each contact stud is drilled down through the centre as shown in section at Fig. 3, and the wander plug is made to fit tightly into these holes. A small washer made from several thicknesses of soft tin foil is placed under the shoulder of each contact stud to ensure good contact with the ink line, and the studs are then screwed firmly in position.

The holes in the second strip should be large enough to slip over the terminals and studs. Before attaching the terminals slip on the top strip, place both strips in the vice, and drill a hole in the right-hand end, as shown by Fig. 4, large enough to take the flexible wire. Take off the top strip, attach the left-hand terminal in the same manner as the contact studs, secure the bared end of the short piece of flexible wire under the shoulder of the isolated terminal on the right, and fit the wander plug to the opposite end. The top strip may now be permanently screwed down. If there are no taps and dies available, small wood screws may be used if holes are first drilled in the bottom strip. The instrument should now be nicely trimmed up round the edges with a file and some emery-cloth, and if necessary the space between each strip can be sealed up with paraffin-wax. The general arrangement of the device is clearly indicated in Fig. 5.

It will be seen that different values can be obtained by altering the position of the wander plug, and the advantage of such an arrangement should be readily appreciated by experimenters. The correct value of the leak in a rectifying circuit is a very critical factor, and dabbling with separate leaks made up in a haphazard way is a tedious job necessitating many connections and disconnections. This trouble can be obviated by means of a few simple adjustments if a variable leak is used, and properly constructed the one described will be satisfactory in every way. O. J. R.

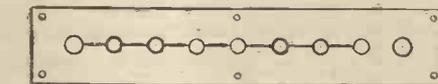


Fig. 1.—The Leak Line.



Fig. 2.—Ebonite Mount.



Fig. 3.—Plug.



Fig. 4.—Ends of Ebonite Strips.

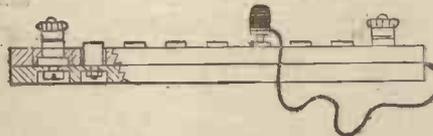


Fig. 5.—The Complete Leak shown in Part Section.

variable grid leak. Reckoning the value of the indian ink lines and the wander plug as nil (the latter being retrieved from a disused high-tension battery), the cost of the remaining materials should not exceed 1s. 6d.

Two strips of 3/16-in. sheet ebonite, preferably matted, each 5 in. long and about 1 in. wide, are marked off and drilled as shown in Figs. 1 and 2 respectively. The instrument shown in the photograph is made of red vulcanised fibre, but this is purely a matter of taste. The two end holes in one strip are drilled for two small terminals, the other seven holes being provided for the contact studs. All holes are well recessed underneath to accommodate the nuts. An indian ink line is drawn along the top surface of the strip between

150 Receiving Circuits in Diagram and Picture

Fig. 21.—A simple reaction circuit, which must not be used on broadcast wavelengths. If L2 is coupled sufficiently closely to L1, the magnified oscillations in the plate circuit will be passed into the aerial circuit, and from there through the valve, resulting in still further increases in plate current. A variable condenser of about .0002 microfarads may be placed across the reaction coil L2.

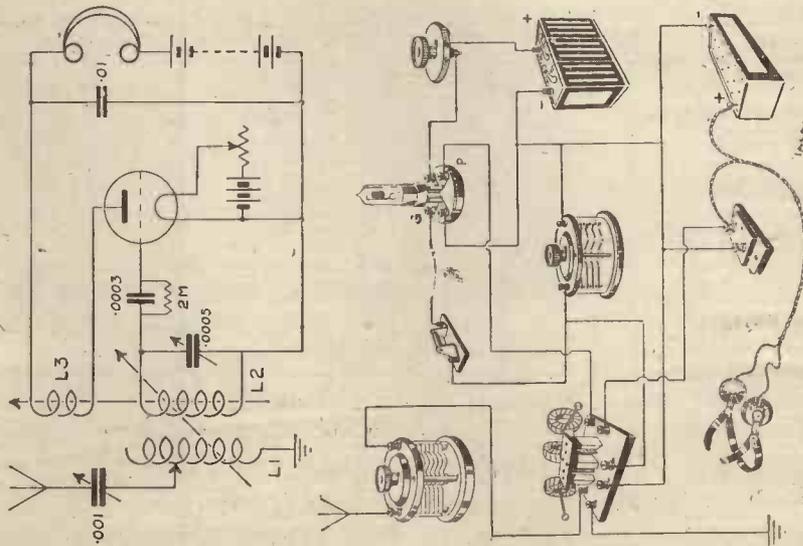
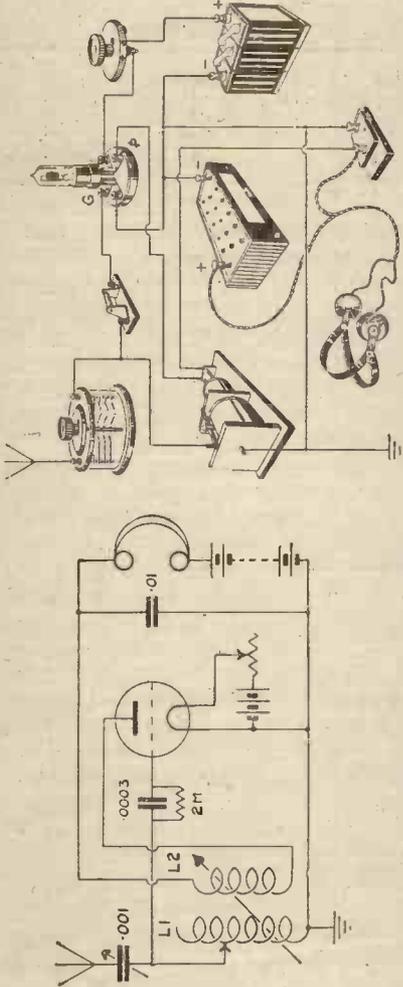


Fig. 22.—Similar to Fig. 21, but a three-coil tuning system is shown. This circuit may be used on broadcast wavelengths provided L1 and L2 are spaced well apart to prevent the reaction coil L3 energising the aerial coil.

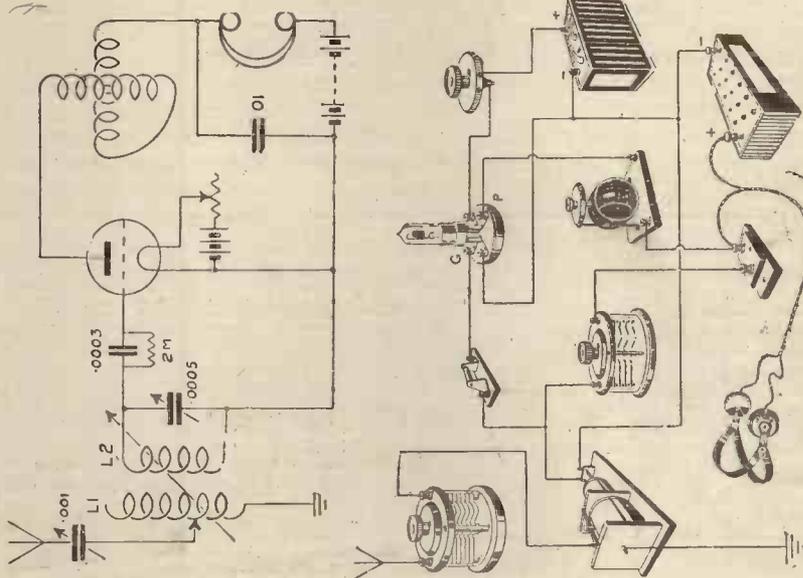


Fig. 23.—A very efficient regenerative circuit for short-waves. The variometer in the plate circuit, if tuned to the frequency of the incoming oscillations, will set the whole system oscillating. If this circuit is used for broadcasting, the variometer should be slightly mistuned.

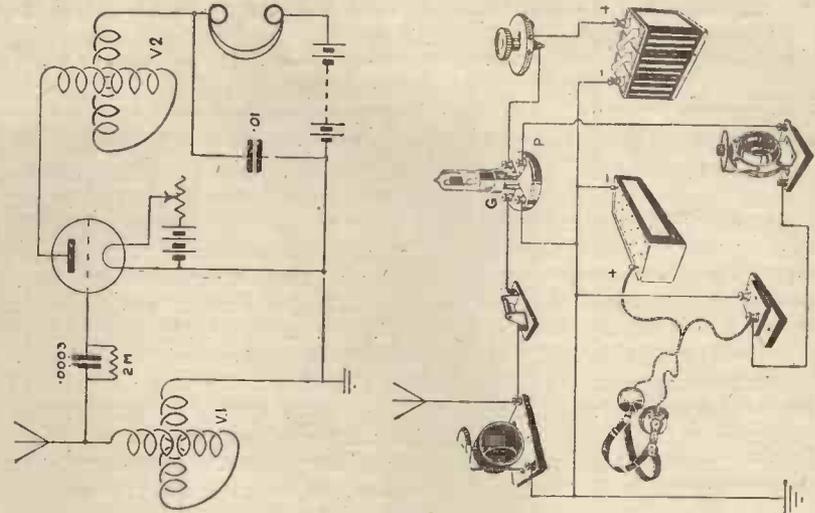


Fig. 24.—In this circuit, two variometers V1 and V2 are used. As this circuit will energise the aerial when the grid and plate circuits are in tune, it should not be used on broadcast wavelengths.

A Transmission Board or Chart

AN IDEA FOR WIRELESS CLUBS

WE reproduce on this page an original idea for a chart showing at a glance all the well-known broadcasting transmissions (according to British Summer Time). It has been drafted by Mr. A. H. Clifton, and readers will recognise its value at a glance. Merely by running the eye down a vertical column it is possible to see exactly those stations that are transmitting at any given hour on any evening of the week. Thus the experimenter, sitting down to his set at 9.45 on Monday evening, observes by a momentary glance that all the British Broadcasting Company's stations are at work; that The Hague and Radiola will last well into the next hour; that Radio-Riviera will be on for fifteen minutes (but can he hear it?); and that Prague is on, but it is doubtful when it closes down.

We should like to reproduce this chart from time to time in AMATEUR WIRELESS; but there are technical difficulties in the way of making the periodical alterations, however slight they might be, and it is

thought that wireless clubs would like to have a chart of this kind available at their meetings, and that many wireless manufacturers and dealers would welcome it as a show-window attraction. In the majority of cases it would be sufficient if a chart for just one evening were exhibited. At any meeting of a wireless society a request by the president would certainly result in a member volunteering to attend a quarter of an hour before the usual meeting time for the purpose of bringing the broadcasting chart up to date, a matter of no difficulty whatever if only a one-evening chart were in question.

Every reader will have his own idea as to the most practical form in which to construct the chart. The names of the stations need to be set out perfectly clearly; the individual names will not vary, but occasionally one may drop out or a new one be inserted. The problem is to arrive at a form of chart that can be quickly brought up to date. Personally we incline to one of two ideas in this con-

nection. In the first place we should work in half-hours instead of in hours; that is, each vertical column or unit space would be half an hour, so that the reading for the evening would be as follows:

TUESDAY

5.0—5.30
5.30—6.0
6.0—6.30
6.30—7.0
7.0—7.30
7.30—8.0
8.0—8.30
8.30—9.0
9.0—9.30
9.30—10.0
10.0—10.30
10.30—11.0
11.0—11.30
11.30—12.0

If the whole chart were contained in a tray, each half-hour space could consist of a square block of wood—white on one side and black on the other. The black would represent transmissions and the white "nothing doing." By means of a steel point any block could be picked out and reversed. A better idea would be to attach narrow mouldings (picture moulding fashion) horizontally across the board, and on these narrow mouldings to hang S-shaped-pieces of thin metal, painted black

(Continued on page 54)

HOURS OF BROADCASTING TRANSMISSIONS. B.S.T.

STATION.	SUNDAY.	MONDAY.	TUESDAY.	WEDNESDAY.	THURSDAY.	FRIDAY.	SATURDAY.
	2-3 3-4 4-5 5-6 6-7 7-8 8-9 9-10 10-11	5-6 6-7 7-8 8-9 9-10 10-11	5-6 6-7 7-8 8-9 9-10 10-11	5-6 6-7 7-8 8-9 9-10 10-11	5-6 6-7 7-8 8-9 9-10 10-11	5-6 6-7 7-8 8-9 9-10 10-11	5-6 6-7 7-8 8-9 9-10 10-11
GREAT BRITAIN.							
LONDON. 2LO. 369.							
NEWCASTLE 5NO. 400							
MANCHESTER 2ZY. 385							
BIRMINGHAM. 5IT. 425							
GLASGOW. 5SC 415							
CARDIFF. 5WA 353.							
BELGIUM.							
BRUSSELS. 1100							
HOLLAND.							
THE HAGUE. PC.GG. 1050							
- PC.UU.							
- PC.KK.							
YMUIDEN. PC.M.M.							
AMSTERDAM. PAS.							
FRANCE.							
RADIOLA. S.F.R. 1780							
PARIS. F.L. 2600							
RADIO-RIVIERA (NICE) 460							
Ecole. S. DES P.T. 450							
GERMANY.							
CZECHO-SLOVAKIA, SWITZ. UMC							
BERLIN. L.P. 2800							
PRAGUE. PRG. 4500							
GENEVA. H.B. 1200							

The Microphone Amplifier

AND HOW IT WORKS

It is well known that at the present stage in the development of wireless it is almost impossible to use more than three stages of low-frequency amplification without producing distortion. Moreover, there are times when three stages will not give sufficient volume of sound. It was for use in cases like this that the Brown micro-

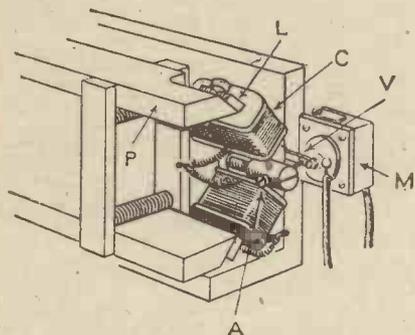


Fig. 2.—Details of Parts of Amplifier.

phone amplifier was developed. This instrument magnifies without distorting, and can thus be used in conjunction with a three-valve L.F. amplifier without producing any disturbing noises. Normally the addition of this amplifier is equal to two extra note-magnifiers. Another advantage is that the microphone amplifier is more economical in operation than an equivalent two-valve set.

Working Principle

An ordinary microphone consists of two

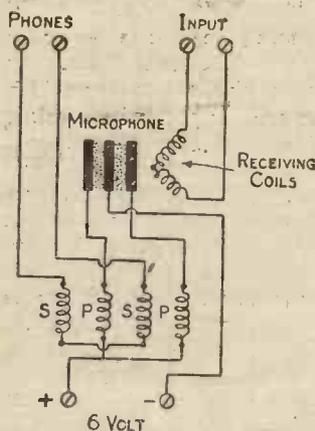


Fig. 3.—Circuit Diagram.

discs, between which are placed loosely-packed carbon granules. When one speaks air waves are produced which strike the front disc and cause it to vibrate. Thus the carbon granules are sometimes compressed and at other times the pressure is released. It will be apparent from this that when they are compressed the resistance is much less and more current will flow in the micro-

phone circuit. On the other hand, when the pressure is released the resistance will be greater, and consequently less current will flow.

The principle of operation of the Brown amplifier is that magnetic means are employed to actuate the microphone instead of air waves, as when speech is transmitted. The general arrangement of the apparatus will be seen from the photograph, Fig. 1. Fig. 2 shows the positions of the components in detail. P is a permanent magnet, at the side of which are built up the coils C on laminated cores L. A is an adjusting screw to prevent the vibrating reed V from sticking to the magnet. One end of the reed is rigidly attached to the centre disc of the microphone M.

The Circuit

The circuit diagram is shown in Fig. 3. The terminals marked input are connected to the phone or output terminals of a valve or good crystal set. The receiving coils have a resistance of the order of 2,000 ohms. The microphone has three discs, of which the centre one is rigidly attached to the vibrating reed (not shown in circuit diagram). A six-volt accumulator is connected across the middle disc and each of the outside ones, both of which are connected in series with the primary of an open-core transformer, marked P. It will be seen that these are in parallel. The secondaries S are connected in series and placed across the output terminals, to which phones or a loud-speaker may be attached.

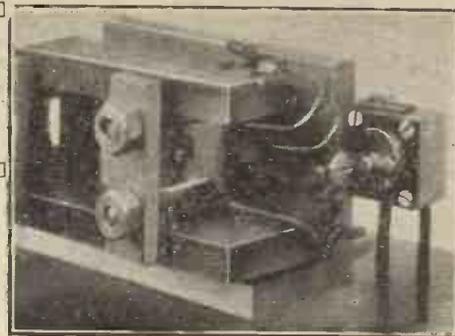


Fig. 1.—The Microphone Amplifier.

When a fluctuating current flows through the receiving coils the vibrating reed will cause the centre disc to move also, thus causing a difference in resistance on each side of the microphone. The result of this is that a variation of potential will be caused in one primary, with very little current variation. In the other primary there will be a large current variation and little difference in potential. These coils are connected in parallel, and as they are supplied from a common battery the total watts in each circuit will be the same. But as the secondaries are in series a difference of both current and potential will be induced in them by the primaries, and therefore a step-up or amplifying effect is obtained.

Transformers

The two transformers are mounted on the base of the instrument, together with a small condenser, not shown in Fig. 3. It is claimed that this amplifier is more economical in operation than a two-valve note magnifier, which it will replace. It is not guaranteed to work with a crystal set in the ordinary way, but will if reasonably loud signals are received in the first place. S.

Simple Tests for Condensers

THAT most indispensable of wireless instruments, the condenser, whether of the fixed or variable type; should invariably be tested for good insulation before being put into use in a receiving circuit.

The apparatus required for the tests are a flashlamp bulb, a battery to light it, and a telephone receiver.

For the first test connect condenser, bulb, battery and phone all in series. If a variable condenser is being tested, swing the moving plates a complete half turn backwards and forwards.


If the bulb does not light up it may safely be concluded that there are no unwanted metallic contacts bridging the positive and negative sections of the condenser.

The second and third tests—for the quality of the dielectric itself—will con-

cern the fixed type of condenser only. In the case of the moving plate variable condenser the dielectric is, of course, air.

Touch the two contacts of the condenser with the terminals of the battery, thus putting the two momentarily in series; the plates of the condenser should now be holding a charge, and this can be verified by joining up the telephone receiver in series with the condenser. If everything is as it should be a click will be heard in the phone at the moment of contact.

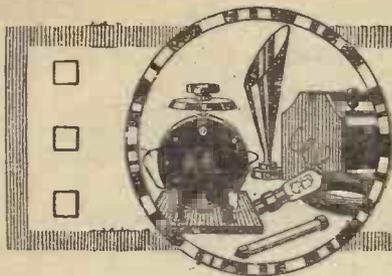
The final and most severe test is to charge up the condenser as described above, but instead of testing with the receiver immediately, let an hour elapse before so doing. If at the end of that time the charge is still there, as proved by the phone, the condenser may be passed as satisfactory. A. P.



A PAGE OF ODDS-AND-ENDS

Aerials Attached to Trees

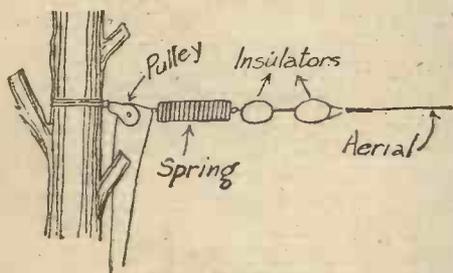AN aerial attached to a tree which sways in the wind is likely to be a source of trouble unless means are taken to over-



Method of Attaching Aerial to Tree.

come, as much as possible, the movement and strain.

The way in which this can be done is shown in the accompanying illustration.

The spring should be strong, and it should be difficult to stretch it more than an inch or so by pulling with the hands. It must be thoroughly greased or oiled frequently to keep it from rusting.

The end of the aerial nearest the house can be brought to a pulley secured to a chimney or wall. A. W. X.

A Cheap Lead-in Tube

THE materials required for making the above will be one piece of glass tube about $\frac{3}{8}$ in. diameter (the cost should not exceed 3d.) and one piece of rubber tubing to fit fairly tightly inside the glass tube. It should be about 4 in. longer than the glass. Before putting the rubber in place it should be given two good coats of shellac varnish. The rubber, when in the tube, should be left 2 in. clear on each side, and when the lead-in wire is inserted the tube should be filled up at each side with rubber stopping as used for cycle tyres. Putty could be used. The projecting ends of the tube should finally receive a good coat of varnish. A. P.

A New H.T. Battery

IN No. 6 of AMATEUR WIRELESS, p. 109, is described a high-tension battery composed of thirty small Daniell gravity-type cells, the containers being test tubes 6 in. long by 1 in. diameter. This battery would be quite satisfactory in use, the only objections being that it is rather messy and not very portable. To overcome these difficulties the writer devised the following modifications.

The test tube has the usual copper sulphate crystals at the bottom with an insulated copper wire running up to the top

of the tube, but instead of putting water in, the tube is half-filled with fine sawdust made thoroughly damp with a solution of copper sulphate in water.


The zinc strip is then put in, resting lightly on the sawdust and running up the side of the tube, which is filled to the top with sawdust dampened as before, but this time with a solution of zinc sulphate in water. The strength of either solution is unimportant.

The advantages of a cell made in this way over the more usual type are obvious, as by pouring a small quantity of melted pitch or paraffin-wax over the top of the sawdust an absolutely dry battery is obtained, with no loss of voltage. When the cells go "dead" it is an easy matter to pour a small quantity on to the sawdust, A. E. G.

Plug-in Basket Coils

A SIMPLE and inexpensive method of fixing basket coils to the usual standard plug-in coil holders is shown in the diagram.

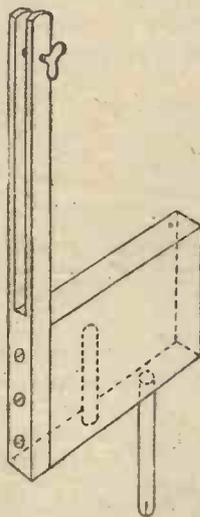A piece of $\frac{1}{2}$ -in. ebonite rod is sawn down the middle to a depth of $3\frac{1}{2}$ in., a small wing nut and bolt being screwed




Plug-in Basket-coil Holder.

through a hole $\frac{3}{4}$ in. from the top. The bottom portion of the rod is filed flat and screwed into a single coil holder as shown. A few of these will enable a set of basket coils to be used as easily as the more costly plug-in coil. C. C. B.

An Efficient Change-over Switch

THE chief difficulty in making a change-over switch is the question of inserting the switch arms in the knob. The dis-

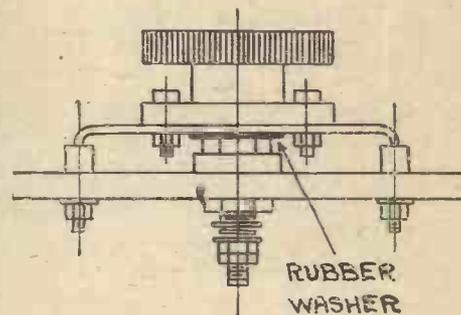advantage of the ordinary ebonite knob is that the boss on the under side is too small in diameter, and for the amateur who is not in a position to make his own knob



Efficient Change-over Switch.

specially the following method will suffice: The switch arms should be bolted to a piece of ebonite about $1\frac{1}{2}$ in. by 1 in. by $\frac{3}{4}$ in. The size can be varied to suit the requirements of the maker.

The ebonite should be drilled in the centre to suit the centre spindle, and can be attached to the knob with about four small screws. The nut on the under side also keeps the ebonite in position.

The accompanying sketch and this description give all the information the reader will require. AMATEUR.


Keeping Accumulators Filled

NOW that the hot weather is here amateurs will have to take extra care in seeing that the level of the acid in their accumulators is up to the mark on the case. The liquid soon evaporates, and if left in that condition the battery will soon deteriorate. Only distilled water should be used for this purpose, unless one lives in the country, when clean rain water may be used. Distilled water can be obtained from any chemist. See that it is kept in a clean bottle and well corked. D.

Making Holes in Ebonite


TO make holes in ebonite without a drill may seem difficult, but wonders may be done with a red-hot knitting needle. A hole any size can be made in a moment and the ebonite does not suffer in any way, that is, it does not crack or char.

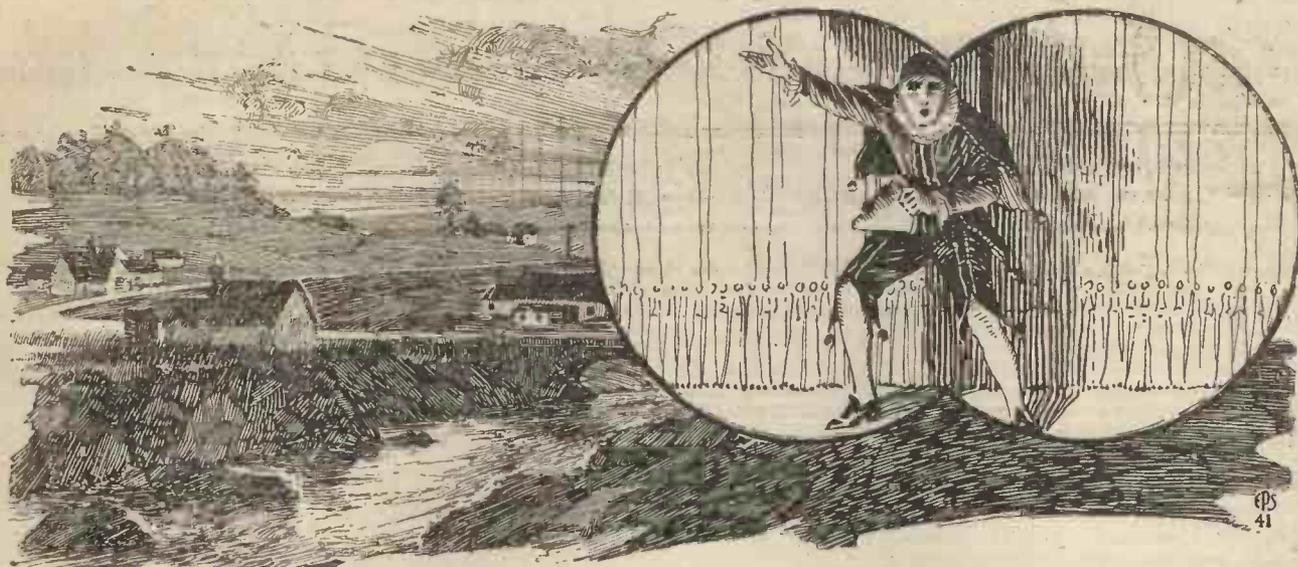To tap such a hole, just use a screw of the requisite size whilst the ebonite is still warm. To repair holes in ebonite, plug in a piece of scrap roughly shaped and push down with a warm iron. An almost invisible repair results if the work is carefully carried out. I. S.



Distance lends enchantment

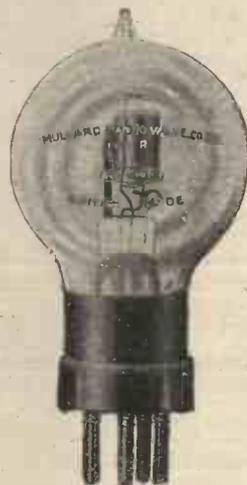THE power to see your opera in the summer evening sky, as you sink back in your easy chair, is a fascination possible to you when the opera glasses of your wireless receiver are




MULLARD
SUPERIOR
WIRELESS
VALVES.

*Reduced price of the Mullard "R"
Valve 15/-*

Mullard

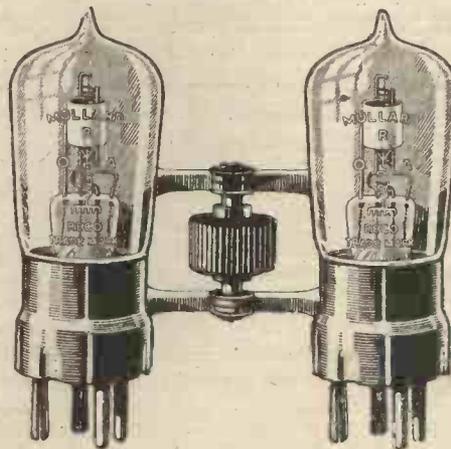Obtainable from all high-class electricians, wireless dealers, &c.



Works right — from the start

If your present Set—whether home constructed or bought—is not giving you the satisfactory service you should expect, scrap it and start with the Peto-Scott Unit System.

This well proved and thoroughly reliable standardised Unit System was first designed nearly two years ago, and has since rendered splendid service to thousands of keen wireless enthusiasts all over the country.

When you start with the Peto-Scott System you know your set will work right from the very start. You can now commence with a 3-unit Crystal Receiver, which will enable you to add high-frequency and note-magnifier Valves whenever you wish *without discarding a single piece of apparatus.*

Send Ed. now for 24 page illustrated Booklet describing the whole System.

PETO-SCOTT CO., Ltd., 3, Wellington St., Strand, W.C.2
64, High Holborn, W.C.1

Branch:
3, Wellington St., Strand, W.C.2
Demonstration Lounges:
39, High Holborn, W.C.1



Price List of Units for home construction

No. 1. Tuner Unit	27/6
No. 2. Condenser Unit	42/-
No. 3. H.F. Amp. Unit	13/6
No. 4. Detector Unit	17/6
No. 5. L.F. Amp. Unit	33/6
No. 6. Crystal Detector Unit	15/6
No. 7. "Reactode" Unit	28/6
Cabinets for 1, 3, 4, 5, 6 and 7	3/6
for No. 2	7/-

Postage gd. per Unit extra, but paid over £2

Dependable Radio Service

	£	s.	d.
AERIAL WIRE, 7/22 bare copper, stranded, 100 ft.	2	6	
INSULATORS, Reel 1½d., Egg 3d., Shell...			6
VARIOMETERS, silk wound, fitted with ebonite dial knob...	4	6	
CRYSTAL RECEIVING SET, variometer tuning	10	0	
" " " " (unassembled)	7	0	
CRYSTAL DETECTORS, on ebonite base, 3/- and:	2	0	
" (glass covered)	3	6	
OOJAH BASKET COILS, set of 7 (150-4,000 metres)	5	0	
" SLAB " " 8 (150-26,000 ")	7	6	
BASKET COILS, our Special Line, set of 6 (170-3,500 metres)	2	6	
COIL HOLDERS, 3-Way } Extraordinary Value	8	6	
" " 2 " }	6	6	
INTERVALVE TRANSFORMERS, not rubbish, 12/-, 12/6, 16	6		
VALVES, Soft, Dutch, ideal for detecting	10	6	
" Hard " " amplification	11	6	
AMPLION LOUD SPEAKERS ... upwards from	2	12	6
VARIABLE CONDENSERS. For Panel Mounting. In Celluloid Case.			
.001	12/6	15/-	
.0005	10/6	13/-	
.0003	9/6	11/-	
HEADPHONES.			
"SIDPE" 4,000 ohms, £1 0 0	8,000 ohms, £1 2 6		
"BRITISH" 4,000 ohms, £1 0 0	8,000 ohms, £1 2 6		
"BRUNET" 4,000 ohms, £1 2 6	PIVAL ... £1 2 6		

The WATERLOO ELECTRIC Co. 129, WATERLOO Rd., LONDON, S.E.1.

(HOP. 5649.)
Closed on Thursdays, 1 p.m. Sat. 9 p.m. Other nights 8 p.m.
CATALOGUES FREE.

To Radio Dealers

Write for Special Dealer
PRICE LIST
showing
standard assortment.

CONDENSITE CELORON

STANDARD RADIO PANEL

You need a radio panel and you want it immediately. But you go to a dealer expecting delay while your panel is cut. He, however, hands you a Condensite Celoron Radio Panel, cut and ready to carry home. All this in a few seconds.

- ☐ This isn't fiction. You can now get Celoron Radio Panels cut in standard sizes. No longer will you wait and pay extra cost for panel being cut from sheet stock.
- ☐ Select the size you need for your set. Should your radio dealer not have them in stock, ask him to order for you. Or write us direct, designating by number the size you need.
- ☐ Condensite Celoron has long been used in connection with electrical and radio work because of its high insulating qualities, high dielectric strength and low dielectric losses. It is easily worked, machined, drilled and tapped, and will engrave evenly without feathering. It is made in one grade of quality, THE BEST.

DIAMOND FIBRE COY., LTD.

HIGH ROAD, SOUTH TOTTENHAM, LONDON, N.15. Telephone: TOTTENHAM 2261
IN CANADA:—THE DIAMOND FIBRE CO., OF CANADA, LTD., TORONTO

TO THE TRADE

Send Your Inquiries to
LONDON METAL WAREHOUSES, LTD.,

- FOR
BRASS RODS, TUBES, SHEETS, ANGLES, etc.
COPPER SHEETS, FOIL, WIRE, etc.
- ENAMELLED COPPER WIRE; RESISTANCE WIRE.
BRASS SCREWS, NUTS, AND WASHERS.
ALUMINIUM, BRONZE, etc.
- CASTINGS IN ALL NON-FERROUS METALS.
ALUMINIUM AND GUNMETAL PULLEYS.

Foundry and Warehouse:

Hill St., Pockock St., Blackfriars Rd., S.E.2.

Telephones:
HOP 1913 & 6196

Telegrams:
"STEBRAWARE, SEDIST, LONDON."

BEHOLD!!!

V BEST COMPONENTS

V BEST PRICES

HAVING ALREADY SECURED the Manchester Business for Components at the right price we have decided to give Amateurs in all parts of the world an opportunity to get them at "V BEST" prices. We have organised a Mail Department, and can offer all the following goods ex stock.

AERIAL WIRE, 7/22's Hard drawn bare copper	per 100 ft.	2/5
AERIAL WIRE, 7/22's Hard drawn enamelled	per 100 ft.	3/9
AERIAL INSULATORS, REEL, each 2d., 2 for 3d.	STRAINER	each -/3
AERIAL INSULATORS, EGG, each 2d., 2 for 4d.	SHELL	each -/4
AERIAL PULLEYS, 2 1/2" Galvanised	each	-/6
BATTERIES, FLASH LAMP, 4-volt (Make your own H.T.), each 5d.	per doz.	4/8
CONDENSER TAPS, Fixed or moving	per doz.	-/4
CONDENSER SPACERS, Accurate small, per doz. 3d., large, per doz.	each	-/5
CONDENSER SCALES, IVORINE, Engraved, not printed	each	1/3
CONDENSER DIALS, EBONITE, Engraved, beautiful finish	each	-/5
CONDENSER SPINDLES, SQUARE Section, screwed, 2 BA, Vernier to .0005, each 4d.; .00075 and .001	each	-/3
CONDENSER ADJUSTABLE PIVOTS	each	-/14
CONDENSER TOP BUSH with flange	each	-/10
CONDENSER TOPS AND BOTTOMS, Drilled for standard fittings	each	-/2
CONDENSER, Fluted Knob and Dial combined, Beautiful finish	each	-/2
CRYSTAL CUPS, 3 Fixing screws	each	-/6
CRYSTAL DETECTORS, Mounted on Ebonite, Adjustable in every way	per doz.	-/9
CONTACT STUDS, 1/2" x 1/2" with nut and washer	per lb.	-/6
CONTACT STOPS, 1/2" x 1/2" with nut and washer	each	1/3
CORE WIRE, Soft Iron	each	7/6
COIL MOUNTING PLUGS, Universal fitting	per lb.	3/6
DUCONS, While they last	per lb.	2/6
EBONITE, Don't buy loaded ebonite. Get maximum area for minimum weight (cut to size)	per lb.	2/6
EBONITE, Manufacturer's scrap pieces in 1 lb. parcels	per lb.	1/4
EARTH CLIPS, Fix on water pipe, Adjustable to any size	per sheet	-/3
FOLI COPPER, per sheet 4d. FOLI TIN	each	2/6
FILAMENT RESISTANCES, A real piece of apparatus	each	-/10
FILAMENT RESISTANCE, EBONITE DIALS, engraved	each	1/9
FILAMENT RESISTANCE, SCALE, engraved ivoryine	each	-/3
FORMERS, PIRTOED, for Honeycomb coils	each	-/4
INDUCTANCE TUBES, Specially impregnated, 12" long 3" to 4" diam.	each	-/5
INDUCTANCE TUBES, Specially impregnated 12" long 4"	each	-/7
INDUCTANCE TUBES, Specially impregnated 12" long 5" to 6"	each	-/4
INDUCTANCE SLIDERS with spring and plunger	each	-/10
INDUCTANCE SLIDER ROD, 1 1/2" drilled	each	1/1
INSULATORS LEAD-IN, Sturdy Ebonite, Terminals each end 6"	each	-/2
INSULATORS LEAD-IN, Sturdy Ebonite, Terminals each end 12"	per yd.	-/3
IVORINE TABLETS, Black on White or White on Black, Engraved, A nice job. AERIAL, EARTH, PEONES, ETC.	per sq. ft.	-/4
INSULATING SLEEVING	each	-/1
INSTRUMENT WIRES, A huge stock of specially purchased wire in all coverings. Perfect. At bargain prices. Send 1d. stamp for price list.	each	-/2
INSULATING SILK SHEET	each	-/2
KNOB, EBONITE, Blind bushed 2 BA. One quality only—THE BEST	per doz.	1/6, 2/-, 2/6
MICA, Pure Ruby, Pieces 2 1/2" x 2 1/2"	per doz.	2/6
NUTS, Brass, Hexagon, 2, 3 and 4 BA, per doz. 3d., 5 and 6 BA, per doz.	per doz.	2/6
RESISTANCE WIRE for Filament resistances	per doz.	2/6
ROUND LOCKING NUTS 2 BA brass	each	1/8
SCREWED BRASS ROD, 12" lengths 2 BA, each 3d., 4 BA	each 1d., per doz.	-/3
SHELLAC Flake	per pkt.	-/6
SWITCH ARMS, 4 LEAF, Splendid Knob, Hefty bush, beautifully polished, with nuts and spring washer	each	1/3
TERMINALS, not Tintacks. Standard pattern according to size	per doz.	1/6, 2/-, 2/6
TERMINALS, Telephone	per doz.	2/6
TERMINALS, Telephone, wood screw	per doz.	2/6
WASHERS, BRASS, 2 to 6 BA	per doz.	1/8
WASHERS, COPPER SPRING	each 1d., per doz.	-/3
VALVE SOCKETS with nut and washer	each	-/1
VALVE PINS with nut and washer	each	-/4
VALVE HOLDERS with 8 nuts and 4 washers	each	-/10

ON THE STRENGTH of the above prices you have doubtless already decided to send us your order. But perhaps you want some scientific components also. Then take our advice—Buy the Best, don't be "PENNY WISE, POUND FOOLISH." We Supply—

SCIENTIFIC COMPONENTS

CRYSTALS (J. L. Cartwright and Co.'s), Carborundum, Copper, Pyrites, Galena, Borate, Iron Pyrites, Silicon, Manganese	per box	-/6
CRYSTALS, Best Hertzite or Zincite	per box	1/-
CRYSTALS, WOOD'S METAL	per box	-/6
FIXED CONDENSERS (J. L. Cartwright and Co.'s)	each	2/-
GRID LEAKS (J. L. Cartwright and Co.'s) 1, 2, 3, 4, or 5 meg.	each	2/-
HEADPHONES, Western Electric, 4,000 ohms	per set	32/-
HEADPHONES, Western Electric while they last, 8,000 ohms	per set	32/-
HEADPHONES, Special French, very sensitive	per set	15/-
LOUD SPEAKERS, Western Electric, 4,000 ohms	each	60/-
TRANSFORMERS, High Frequency Plug-In Type (J. L. Cartwright and Co.'s) double groove, No. 1, 3500 6/6; No. 2, 5500 7/-; No. 3, 9800 7/6; No. 4, 14000 8/-; No. 5, 2000 8/6; No. 6, 3500 9/-; No. 7, 10,000 10/6	each	21/-
TRANSFORMERS, Low Frequency (J. L. Cartwright and Co.'s)	each	12/-
TRANSFORMERS, Telephone (J. L. Cartwright and Co.'s), while they last	each	15/-
VALVES, Ediswan A. R. Type	each	17/6
VALVES, Marconi Osram R. type	each	9/6
VALVES, DUTCH	each	9/6

HUGE CASH WITH ORDER. Money back if not entirely satisfied. Please remit ample stocks postage, any balance returned. ADVICE FREE

VICTOR BEST CO.
THE COMPONENT KING
Dept. A
24, London Road
MANCHESTER

Tel. No. City 9242

(Opposite London Road Station)

HULLO EVERYBODY

VARIABLE CONDENSERS

COMPLETELY ASSEMBLED WITH EBONITE END AS SHOWN IN SKETCH.



		ASSEMBLED BUT WITH EBONITE ENDS.	
•001	8/-	•001	6/6
•00075	6/9	•00075	5/6
•0005	5/11	•0005	4/6
•0003	4/11	•0003	3/6
•0002	3/11	•0002	2/6
•0001	3/8	•0001	2/3
Vernier	3/3	Vernier	1/9

Pair of ebonite drilled cords to fit yourself on above 1/- extra

NOT A BAG OF PARTS. NOTE.—Postal Charges 9d. per set, otherwise not executed.

To callers 1d. in the 1/- discount off condensers.

Variometer on ebonite, W. 250/750 metres, internally wound. Very fine. Sell at sight, 17/11.
Fixed Condensers (from .0002 to .006), 9d., 10d., 1/-, 1/6.
Ebonite Dials (with knob 0.1807; 1/4 and 1/6.
Turned Ebonite Valve Holders, 8 nuts, 1/-.
Fil. Resistance, 1/8, 1/10, 2/3.
Fil. Resistance, 7 ohms, 3/6.
French "R" Valves, 9/6.
Moulded Valve Holders with nuts, 9d.
Perikou Crystal Detectors, glass, 2 crystals, 1/4, 1/6 and 2/8.
Glass Dustproof high-class Detector (whisker), 3/-.
Contact Studs and Nuts, doz. 4d.
Valve Pins, doz. 7d.
2 BA Nuts, 3 doz. 7d., 1/10 gross.
4, 5, 6 BA Nuts, 3 doz. 6d., 1/6 gross.
Terminals, special offer with nut, 4 for 3d.
Valve Legs and Nuts, 1d. each, 9d. doz.
Valve Legs with shoulder, 2 for 2d., 1/- doz.
Switch Arms, very good, 8d., 10d., 1/3.
Twin Flex, 4 yds. 7d., 12 yds. 1/7.
Genuine (Shaw's) Hertzite, 9d., 1/-, 1/3.
100,000 ohm Resistance, 2/3.
T.M.C. Phones, 4,000 ohms BBC, 22/6.
Grid Leak and Condenser, .0003, 2/-.
Coil Holders, 3-way on ebonite, 6/- and 6/6.
15 v. HT Batteries, 2 plugs, 2/3d.
30 v. HT Batteries, 2 plugs, 4/1d.
36 v. HT Batteries, 2 plugs, 4/6d.
100 feet 7/22 Aerial wire, 4 Insulators, the lot 2/6.
Real Ebonite Knobs, 2 BA Bush, 3d.

Marconi R valves, latest type, 45-60 v., 14/11.
Brunet 4,000 ohm genuine 1st quality Headphones, 17/11.
German-6,000 ohm Headphones, extra loud, 15/11.
H.T. Batteries, 2 Wander plugs, 66 volt, 8/-.
H.T. Batteries, 2 Wander plugs, 60 volt, 8/-.
Aerial Wire, 7/22 per 100 feet, 2/3d. and 2/1d.
Rotax Accumulators, 4 v. 40 amp., 15/6.
Phone Cords, double, extra long, 10d.
5-1 Intervolve L.F. Transformers, 11/6.
Wound Coils, 6 x 3, Turns 180, W.L. 1,100, 1/6.
Wound Coils, 12 x 4, Turns 400, W.L. 3,800, 2/6.
Variometers, very good value, 250/750, 3/5.
Crystal Detectors (whisker), extra value, 1/1 and 1/3.
Large Telephone Terminals, 2 B.A. with nut and washer, 2 for 3d.
Terminals, all kinds, with nuts and washers, 4 for 5d.
Basket Coils (6 in set) up to 3,000 metres, well made and efficient, 2/2.
1 Switch Arm, 12 Contact studs and nuts, the lot 1/-.
Sleeving, takes 18-gauge wire, 3 yards for 1/-.
Insulating Hooks, 3 for 3d., 1/- doz.
D.P.D.T. Switch, compact high class article, 2/3d.
4 yards Copper 18 gauge connecting wire, 2d.
6 yards Bell wire, 2d.
6 yards Bell wire, D.C.C., I.R., 3d.
Radio Instruments, Ltd., L.F. Intervolve, 25/-.
Special Prices Radio Clubs.

IN STOCK.—Mullard Ora, Cossor, Ediswan Valves and Crystals of every description.

Everything you want for your set.

Please note that a special discount 1d. in the 1/- is given off many articles in the windows where not marked NETT. This must save you a large sum, as in any case profits are reduced to a minimum.

We want your business by post, but MUST have postal charges as follows:

Up to 10/- 2d. in the 1/- (or any part).
Up to 20/- 1 1/2d. in the 1/- (or any part).
Over 20/- carriage paid. (Condensers excluded).

M. RAYMOND
27, LISLE STREET, W.C.2.

Right opposite DALY'S Gallery Door.

Open 9-8. Saturdays 9-6. Sundays 11-2. Phone: Ger. 4637.



for 45/-

A splendid opportunity for you to test the joys of wireless without worry and at the minimum expense.

You can have delivered to your house, the aerial erected, a

T.M.C. 3-Valve Set Complete with Loud Speaker,

installed and left working for the small outlay of 45/-.

Every week a competent wireless engineer will call, take away the old battery and replace it with a fresh one. At the end of one month, or at any subsequent time, you have the option of purchasing the set outright, or we will arrange to maintain it, inspect it and look after it in every way for a further 45/- per month, or at any time you can terminate the arrangement.

Write to-day for full particulars of this offer and the name of the nearest T. M. C. dealer.

TMC
Wireless

FULL ENJOYMENT—NO TROUBLE
The TELEPHONE MANUFACTURING CO., LTD.
London Showrooms: 68, Newman St., Oxford St., W.1
Phone—Museum 5181.

[E.P.S.]

99

EDISWAN VALVES




COMPACT,
ECONOMICAL,
RELIABLE

REDUCED PRICE

TYPE "R"

15/-

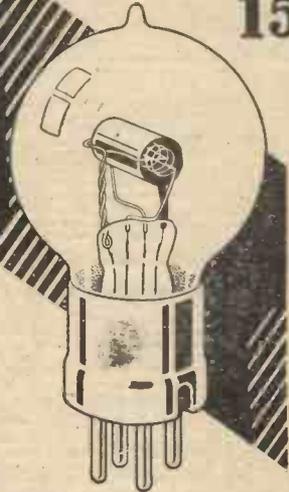

SENSITIVE,
SILENT,
ROBUST

TYPE "A.R."

15/-

Ediswans Easily Score

Actual performance has proved beyond all question the superiority of the Edison Valve for Wireless work. Every day adds to its reputation.

One Satisfied User says:

"Since using Edison Valves with only one on an ordinary circuit, I have received quite distinctly and strongly the following stations, and can pick them up at any time (judging by admitting) proving it is not freak reception. 2LO, 2ZY, 51T, 5WA, 5SC, 5NO, Radiola, Ecole Supérieure, F. L. Croydon, and local amateurs. My aerial is none too good, being a twin 26 ft. high, 30 ft. long. I have tested Edison Valves against many other makes and have no hesitation whatever in stating that for loud signals with the minimum of strain on the accumulator, EDISWANS EASILY SCORE.
(Signed) A. J. S. R., Brighton, May 15th, 1923."

We have had unique experience in the development and manufacture of the Thermionic Valve. The first experiments in connection with the investigation of the "Edison Effect" on which the working of a valve depends were carried out at our Ponders End Works by Prof. J. A. Fleming, who was the Company's Scientific adviser.

Also manufacturers of complete Receiving Sets, Accessories and H.T. and L.T. Batteries. Dealers should write at once for particulars on terms. Descriptive leaflets free on request.

FREE ON REQUEST. Illustrated Booklet entitled "The Thermionic Valve—its origin and development."

The EDISON SWAN ELECTRIC Co. Ltd.

Contractors to H.M. Admiralty, War Office, Royal Air Force,
123/5, QUEEN VICTORIA STREET, E.C.4
and 71, VICTORIA STREET, S.W.1.

Works: Ponders End, Middlesex.
Branches in all Principal Towns.



On Your Wavelength!

A New Valve I MENTIONED a short time ago in these notes that we were likely ere long to see some rather startling developments in receiving valves, and now something quite new is announced from America. This is the C-299, made by the Cunningham Company, of San Francisco. There are two ways of making a valve economical in its requirements. Either you can reduce the voltage or you can design it to work upon a very small current consumption. In some an attempt has been made to do both; the Mullard L.F. Ora A., for example, take .2 ampere at 1.5 volts, whilst the American WD-11 uses .25 ampere at 1.1 volts. To my mind the most sensible solution is to whittle away the current needs and not to bother too much about the E.M.F. One can easily obtain high potentials; that is only a matter of wiring dry cells in series. Look at your high-tension battery, which, despite its small size, may give from 30 to 100 volts. Current, however, is a different matter altogether. When it comes to supplying from a quarter of an ampere upwards no primary batteries are of any use, since their output is not sufficiently steady, and we must perforce use the expensive, cumbrous accumulator, whose acid electrolyte makes it anything but a desirable article of drawing-room furniture. There are probably few dry cells that will supply even .25 ampere for more than a short period without becoming wobbly and causing the valve to play weird pranks. The C-299 asks for nothing like so much. It is content with the almost incredible ration of .06 ampere!

What it Can Do The E.M.F. that it needs is just under $4\frac{1}{2}$ volts, which is, of course, easily obtainable from three dry cells wired in series. Now an ordinary bell battery will supply the 60 milli-amperes called for with the utmost ease. In fact, it will do a great deal more. You can use two of these valves for long periods on end from the trio of series-connected cells. Even a four-valve set can be worked from them, provided that you are careful to switch off during the three-minute and longer intervals in order to give the cells a chance of recuperating. Valves of this type should make an immense difference to the progress of wireless as a general hobby, for with them even those who live in remote country places can use valve sets with the greatest ease. Gone is the heavy messy accumulator, gone the need for constant recharging. In its place you have the clean dry

cell which can be bought anywhere, and replaced when it runs out for a trifling sum. The price of the new valve is most reasonable. It sells at \$6.50, which at the present rate of exchange (4.62 dollars to the pound) works out at, roughly, 28s. Even with an *ad valorem* duty of 33 $\frac{1}{3}$ per cent. its British price would be, only 37s. 4d., which compares very favourably with those of our own dull-emitters. Let us hope either that one of our valve makers will produce something as good—and as cheap!—or that some enterprising firm will import the C-299 and put it on the market here. I hear that the "A.W." valve man hopes to obtain some of these new "toobs" and to report upon their performances shortly.

Sunday Programmes

Though I have refrained from referring to the matter, since 2LO's staff seemed to be hard enough worked as it was, the Sunday programmes have always struck me as a blot on the B.B.C.'s escutcheon. On the one day in the week on which leisure allows nearly every wireless man in the country to use his set we used to have a wretched little programme not starting until 8.30 and ending after only one and a half hours. The first indications that an improvement was contemplated was when, instead of the usual rather meagre fare, we had the Russian Balalaika (I hope that's spelt right!) Orchestra. Then came the announcement that we were to have an afternoon entertainment from 3 o'clock until 5. This is exactly what is needed, and if only arrangements could be made on the lines of experiment that have recently been carried out for simultaneous broadcasting from all stations between these times, so as to give owners of small sets in the provinces a fair chance, I venture to predict that the popularity of wireless would increase by leaps and bounds.

No Pleasing 'Em

Mr. Burrows was quite pathetic the other night when he told us his little tale of woe. It seems that he and his staff are being peppered at times by the carping and bitter-tongued critic. "Instead of the old time Uncle Arthur," he said, "I received the other day a letter addressed to 'The Foreman, The London Gas Works, 2, Savoy Hill'!" I would not change places with him or any of his accomplices for anything in the wide world. They think out something new and put it on after spending considerable time and trouble in arranging the necessary preliminaries. Next morning's post brings

a variety of letters. Ninety per cent. are delighted; seven per cent. express opinions that are neither one thing nor another; the remainder indulge in remarks of the most caustic nature, and even prevail upon their M.P.'s to ask silly questions in the House! No programme can consist of items that please everyone, but there will always be a good deal that is to the taste of all listeners-in.

Damping

Most of us are rather prone to adopt amplification devices whose efficiency if unchecked is little short of phenomenal. I refer chiefly to the tuned plate. Have you ever tried to use two or three of these in series, even with the aid of a potentiometer? If you have you will have realised the feeling of impotence of the ancient Irishman who endeavoured to drive to market three pigs who each had widely different ideas as to the direction in which they wished to go. As he expressed it subsequently, "the devil himself was in 'em." That, to put it mildly, is how I could refer to tuned-anodes. The only way to control the beasts is to use damping plates, or to insert series resistances as has been described by other writers in the pages of AMATEUR WIRELESS. This is all very well at first sight, but it means that you are losing on the swings what you gain on the roundabouts. For one H.F. valve give me the tuned-anode every time. Thereafter I would hark back, old-fashioned though you may deem me, to the good old transformer.

A Confession

I am going to lay bare the secrets of my soul. Before broadcasting started I had no soul for good music. The frowsy locks of professional musicians of the male sex were to my eyes like a red rag to a bull's; they were effeminate-looking creatures, and the fact that one saw them as they played was enough to stifle any stirrings of the soul produced by their strains. Now, thanks to wireless, I find that I really like classical music. The splendid talks given by Major Bavin and Mr. Percy Scholes have helped me and thousands of others to realise something of what are in the compositions of the great masters. I hope that 2LO and other stations will continue to give us Wagner, Gounod, Chopin, Tschaikovsky and Chaminade, and will not be led by any clamour from a few disgruntled souls to fill their performances with laments about "Coal Black Mammies" and things of that kind. THERMION.



RULES.—Please write distinctly and keep to the point. We reply promptly by post. Please give all necessary details. Ask one question at a time to ensure a prompt reply. Always send stamped addressed envelope and Coupon (p. 55).

Making a Multiple-secondary Transformer.
 Q.—I wish to make a transformer to work on a 240-volt circuit to give voltages of 30, 25, 15, 12, 8, 6, 4 and 2. Kindly give constructional details and quantities of wire required. (N. F. G. London, W.).

A.—Unfortunately two of the most important facts essential in the design of any

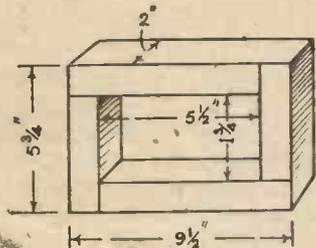


Fig. 1.—Transformer Core.

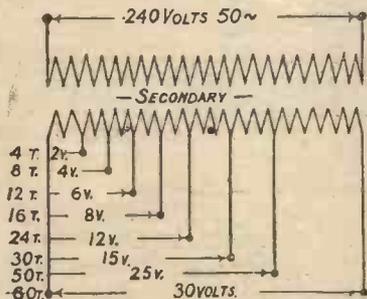


Fig. 2.—Details of Transformer.

transformer have been omitted from this enquiry, namely, the frequency of the primary supply volts, and the current output required from the secondary. The following data are therefore calculated on the assumption that the primary windings of the transformer will be supplied with 250 volts at the most general frequency of 50 cycles per second. If this is not correct, the whole of the windings will need modification in consequence, since other things being equal, the number of turns on a transformer winding are inversely proportional to the frequency of the circuit. Also it will be assumed for purposes of calculation that an output of half a kilowatt will be sufficient from any of the secondary windings. The general design of the transformer will be of the core type, on the lines laid down in "Auto-transformer Design" (A. H. Avery) and as per Fig. 1, which gives the principal dimensions of the "Stalloy" iron-core built up of laminated strips of No. 28 s.w.g. thickness. The sectional area of this core is 4 sq. in., and the working flux density about 56,500 lines per sq. in. These factors enable the number of primary turns to be calculated from the

formula: $\text{Turns} = \frac{\text{Volts} \times 10^8}{\text{Total flux} \times 4.44 \times \text{frequency}}$
 giving a total of 480 turns, or approximately two turns per volt. Since the output on the secondary is to be 500 watts, the input for the primary will be slightly greater owing to inevitable iron and copper losses. A 90 percent efficiency would be a fair figure for an instrument of this-size, therefore the total

input when the secondary is fully loaded will be: $500 \times \frac{100}{90} = 555$ watts, and the current

will be watts divided by volts = $\frac{555}{240} = 2.31$ amperes. Working at a current density of 1,500 amperes per sq. in. the nearest size of wire will be No. 18 s.w.g. d.c.c. copper. Having settled the primary windings the secondaries are very simply calculated, since their turns are proportional to the volts required and their gauges to the current they will have to carry. As stated above, the primary windings indicate a "constant" of 2 turns per volt, and the same applies to the secondary windings which are cut by the same magnetic flux. Therefore the respective number of turns on the individual secondary windings will be as follows:


2 volts	= constant	2 × 2 = 4	turns
4 "	"	2 × 4 = 8	"
6 "	"	2 × 6 = 12	"
8 "	"	2 × 8 = 16	"
12 "	"	2 × 12 = 24	"
15 "	"	2 × 15 = 30	"
25 "	"	2 × 25 = 50	"
30 "	"	2 × 30 = 60	"

With the same output from any of the secondary windings, namely, 500 watts, the current will vary inversely as the pressure, and the respective currents associated with these various voltages will be:

Watts.	Volts.	Amperes.	
500 ÷ 2 =	250	= 1 in.	by 0.16 in. copper strip
500 ÷ 4 =	125.0	= 1 in.	by 0.08 in.
500 ÷ 6 =	83.3	= 1 in.	by 0.05 in.
500 ÷ 8 =	62.5	= 1 in.	by 0.04 in.
500 ÷ 12 =	41.6	= 1 in.	by 0.03 in.
500 ÷ 15 =	33.3	= No. 8 s.w.g.	
500 ÷ 25 =	16.6	= No. 10 s.w.g.	
500 ÷ 30 =	16.6	= No. 11 s.w.g.	

A summary of the above winding data will be found in the winding diagram (Fig. 2).—Q.

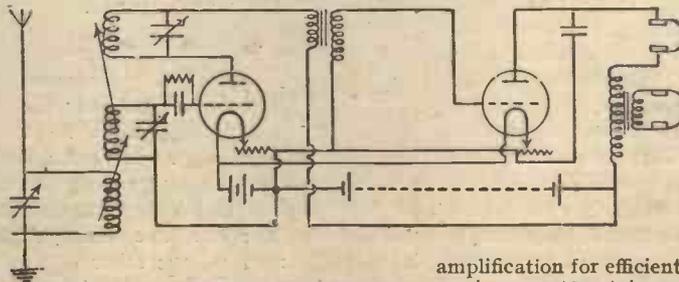Q.—Can you give me a circuit diagram for a two-valve (detector and L.F.) receiver using a loose-coupler and tuned reactance arranged so that high-resistance and low-resistance



Two-valve Circuit (1 Det. and 1 L.F.) for use with High and Low Resistance Phones.

phones can be used at the same time?—D. M. (Bournemouth).

A.—The circuit shown will meet your requirements. The condenser across the reactance should be a small one, not more than .0003 microfarad. It may be found necessary to put a .002 microfarad fixed condenser across the primary of the transformer and results may also be improved by putting a large con-

denser across the H.T., although this is not essential. The high-resistance phones are shown in series with the primary of the telephone transformer.—R.

Condenser Across "I.P." and "O.P."

Q.—Is a fixed condenser necessary across the primary of a low-frequency transformer?—I. G. H. (Manchester).

A.—The primary of the first low-frequency transformer should be shunted by a fixed condenser of about .002 microfarad, although sometimes this condenser may be omitted without detriment to signal strength, owing to the capacity between successive turns of the primary winding acting as a condenser bypassing any high-frequency currents which may be flowing in the circuit. When more than one stage of low-frequency amplification is used, only the primary of the first transformer need be shunted by a condenser, although condensers across the other transformers will assist in stabilising the low-frequency circuits when there is a tendency to howl.—B.

Insulating Guy Wires.

Q.—When using a small aerial with guy wires, is it necessary to break the latter up by means of insulators, and if this is done will it affect signal strength appreciably?—J. K. (Earls Court).

A.—When using a high unscreened aerial it is certainly advisable to put two insulators in each guy wire. If this is not done energy will be picked up by the wire and conducted straight to earth instead of flowing through the aerial and the relatively high impedance of the set. With a low aerial which is probably already screened the improvement will not be as great.—R.

Broadcast Receiver

Q.—I am about to purchase a broadcast receiver, and would like your opinion as to the best type to buy. I wish to receive all the broadcast stations.—NOVICE (Bury St. Edmunds).


A.—You will need a receiver having at least one stage of high-frequency amplification, a valve detector, and two stages of low-frequency

amplification for efficient reception. Also your receiver must contain variable reaction of some kind, preferably coupled to the tuned-anode coil or high-frequency transformer between the high-frequency valve and the detector. This is a most important point, as without reaction you will probably not hear more than two or three of the broadcast stations. Study the advertisements and arrange for a demonstration of a receiver which has variable reaction.—B.

Workshop Hints: Some Improvised Tools

ALTHOUGH there are hundreds of people engaged in making wireless apparatus for experimental purposes at the present time, there are only a few, comparatively speaking, who are fortunate enough to have a complete set of necessary tools or a handsomely-equipped workshop. With a little care, however, many commonplace tools can be made to perform the same work as those of a more intricate variety. Three simple makeshift methods are described below, and there are many others that will suggest themselves to the ingenious worker.

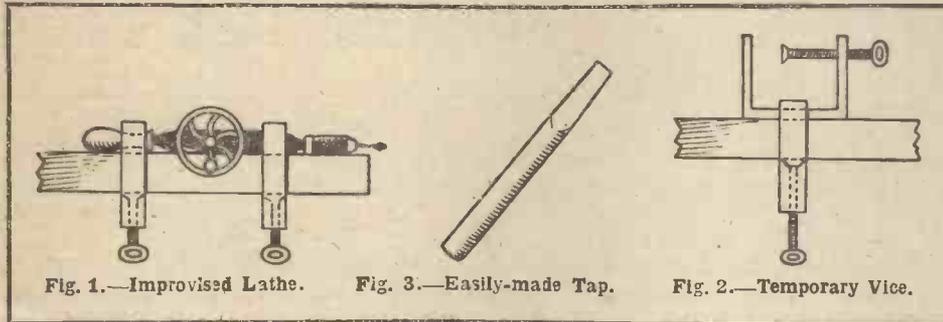Obtain two ordinary clamps, such as are included in framework sets, and with these clamp the drill to the bench in the manner shown in Fig. 1. With assistance to supply the necessary power to the drill both hands are left free to hold and steady the material being worked.



Temporary Vice

Using the same two clamps mentioned above as at Fig. 2, a vice of no mean utility can be rigged up in a few minutes. To prevent any risk of scratching or such damage the work should be held between two pieces of fibre or wood material.

Easily-made Taps

Taps for lightly tapping ebonite panels, condenser tops, etc., can be made very quickly by getting a steel bolt of the same gauge as the rod to be used and filing off the thread on four sides, as in Fig. 3. For use in a hand drill the head may be cut off and the end filed to fit the chuck.

F. T. W. D.

A Makeshift Lathe

An ordinary hand or breast drill can, in some cases, make quite a good lathe for small work such as panels when used in the following manner.

A Few Components




"Lattikone" Inductance Coil.



A Neat Transformer (G. Z. Auckland & Son, London).



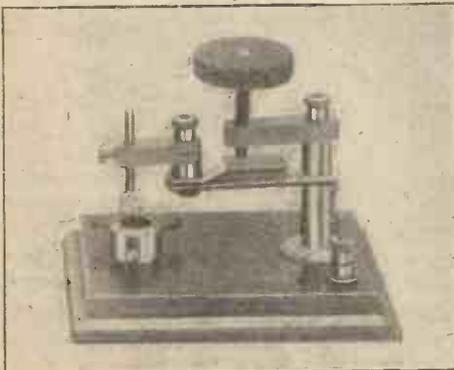
Plug-in H.F. Transformer (Grafton Electric Co., London).




Auckland Crystal Detector.



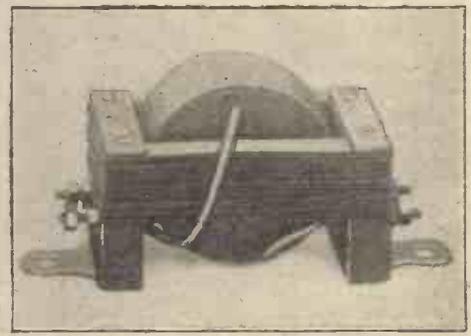Tapped H.F. Transformer (H. W. Sullivan, Ltd., London).



Auckland L.F. Transformer.

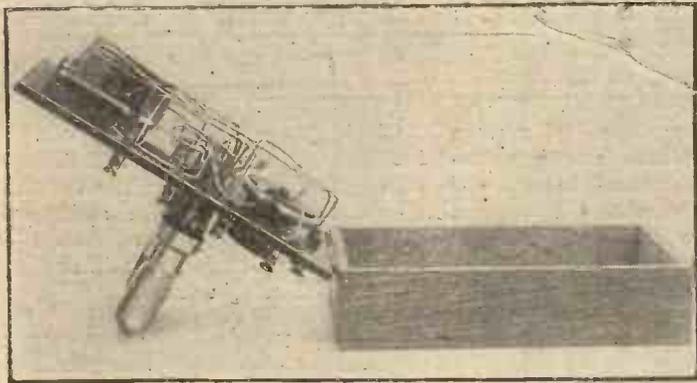

Photograph of Instrument with Panel Raised.

THE great point about the AMATEUR WIRELESS ideal unit set, which was fully described in Nos. 25 to 28 and 30, and some modifications in Nos. 46 to 49, is that one can make all kinds of additions to it and try a variety of fresh designs with the minimum of trouble. One system of amplification or rectification can be tried most easily against another. A further point is that if the panels are hinged to their cabinets it is possible, by substituting flex leads for the brass coupling rods, actually to work the set with one or more units open, so that resistances, grid leaks, condensers and so on can be changed whilst reception is going on and the improvement (or the reverse) duly noted.

Since the original set was made up and described a good many additions have been made to it, some of which will be described in this and succeeding articles; the present instalment deals with a novel type of note-magnifying unit which was constructed early in the year. It has now been in use for a long time, and it has proved so



Photograph of Complete Magnifier.

satisfactory that it is employed in preference to any other for the reception of telephonic transmissions. After a long series of tests made with low-frequency transformers of nearly every well-known make, I realised that there is no such thing as a perfect iron-cored transformer. For all ordinary purposes they are good enough; they will bring in both speech and music sufficiently well to give real pleasure; but should you set yourself, as I have done, the task of producing a considerable volume of sound without a sign of distortion or harshness at any time, with the entire elimination of all that is throaty or "gramophony," you will come to admit that when more than one stage of low-frequency amplification is used transformers, no matter how you shunt them with resistances or supply

A NOVEL NOTE

An Addition to the "Amateur Wireless" Ideal Unit Set

Amplification Systems

Resistance-capacity amplification is used a good deal on the high-frequency side of sets for long-wave work, but it has not so far become popular in this country for audio-frequency magnification. The principle is the same for whichever pur-

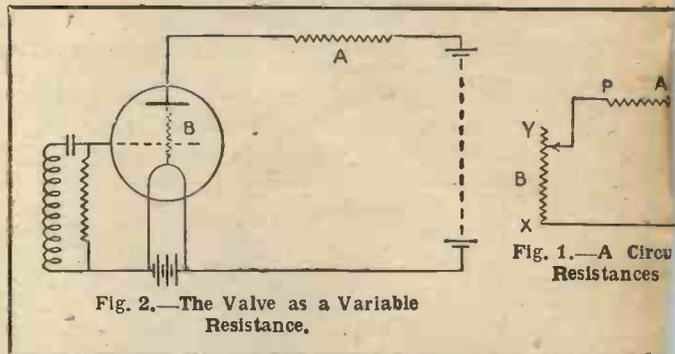


Fig. 2.—The Valve as a Variable Resistance.

Fig. 1.—A Circuit Resistances

pose it is employed. If we place two resistances in series in a circuit (Fig. 1), one variable and the other fixed, and adjust the movable one (B) so that the two are exactly equal, there will be a total potential drop across the circuit which is evenly distributed throughout. If we regard the resistance of the rest of the circuit as zero then the voltage drop will be equally divided between the two resistances; that is, the drop across A will be exactly equal to that across B. Now let us reduce the resistance of B by moving the sliding contact. The total voltage drop in the circuit remains unaltered, but its parts are different. The drop across B is decreased, whilst that across A becomes greater.

Modern Theory


In accordance with modern theory, current flows from the negative pole of the battery to the positive through the circuit. When the resistances are equal the potential difference between the points X and Y, Fig. 2, is the same as that between P and Q. If, however, we reduce the resistance of B the difference of potential between X and Y is less than that between P and Q.

Now in the valve, so long as the lead-in is not attached we have a constant resistance (Fig. 2) in the anode circuit be-

E-MAGNIFIER



By
R. W. Hallows

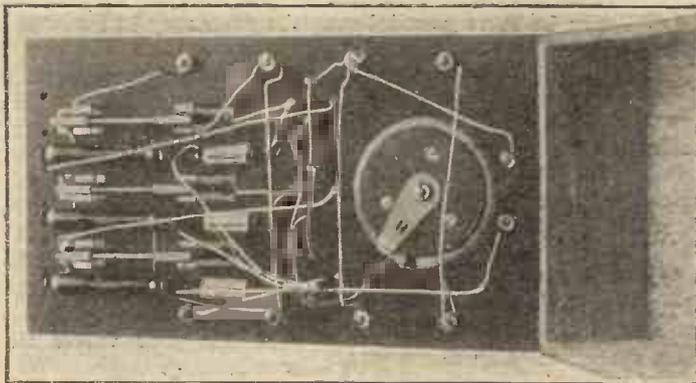

Photograph of Underside of Panel.

tween the filament and the plate. Place a millimeter in the plate circuit when the filament battery is not switched on.

Nothing at all is registered. Now switch on. Immediately the needle indicates a steady current of perhaps 1 milli-ampere. If your H.T. battery is of 60 volts, this by

transferred to the grid of the note-magnifier NM by way of the condenser. These will control the plate circuit of the second valve, producing in it still larger variations of current than those which occur in the first.

At first sight you might be disposed to regard the capacity of the grid condenser C as a printer's error. A capacity of .005 microfarad for a grid condenser sounds terrific when we remember that that of the rectifying valve is but .0003 microfarad. The value is correct. The grid of the rectifying valve has to deal with radio-frequency impulses, which pass easily through a tiny condenser. When rectified and slowed down to audio-frequency the impulses require a far bigger capacity if they are to have a free passage. A condenser of .0003 microfarad would not pass them at all.

fication than the two which they have superseded, but, as has been said, there is no comparison between the two in the matter of quality.

Wiring

Fig. 4 shows the wiring of the unit, which is not really very complicated. Those who intend to make it up are not advised to begin straight away by laying out and drilling the panel. The values of the condensers, of the grid leak and of the resistances are rather critical. Those given in the drawing work well with the D.E.R. valve, for which they were designed, but they will probably not suit many other valves.

The best method is to make a bench "hook-up," as shown in Fig. 5, beginning with one valve and adding others one by one.

Not a penny need be spent on ready-made apparatus. The resistances can be made from strips of cartridge paper thoroughly soaked in indian ink and allowed to dry. If they are made rather large to

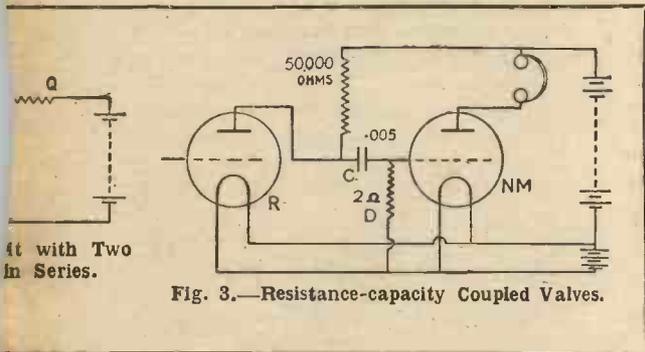


Fig. 3.—Resistance-capacity Coupled Valves.

Ohm's law shows that the resistance is 60,000 ohms. Now attach the lead-in and tune in a strong signal. You will see the pointer of the millimeter making small movements. The current is varying. It cannot do so unless the resistance alters. The grid controls the plate circuit by making tiny alterations in the resistance. We may therefore regard the valve itself as a variable resistance corresponding to B in Fig. 1. Thus if the resistance of the valve is lessened by a positive potential or the grid the potential drop between filament and plate will fall, and that across the fixed resistance A will rise. If B is reduced there will be an increase in the flow of current through A.

Resistance-capacity-coupled note-magnifiers do not give valve for valve such amplification as is obtainable by the use of transformers, for we cannot contrive with them such a big step-up in voltage as is provided by the transformer with a winding ratio of 1 to 3 or even 1 to 5. Actually, a resistance-capacity-coupled valve has about 75 per cent. of the efficiency of a transformer-coupled valve as regards volume of sound. For this reason the panel designed to replace two low-frequency transformer units was made with three resistance-coupled valves. Its three valves give slightly greater ampli-

Valve Coupling

Fig. 3 shows how to make use of this for the purpose of coupling two valves. The condenser C serves as a barrier to prevent a steady positive potential from the high-tension battery from reaching the grid; it also acts as a by-pass for oscillating impulses. The grid leak D allows a steady potential to arrive on the grid from the low-tension battery. As the internal resistance of the rectifying valve R is varied by its grid, varying potentials of relatively considerable magnitude will be

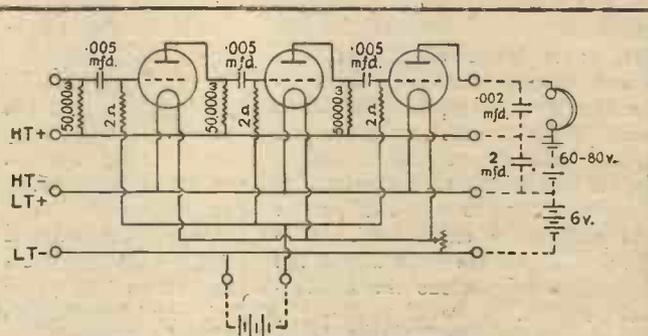


Fig. 4.—Circuit Diagram of Note-magnifier.

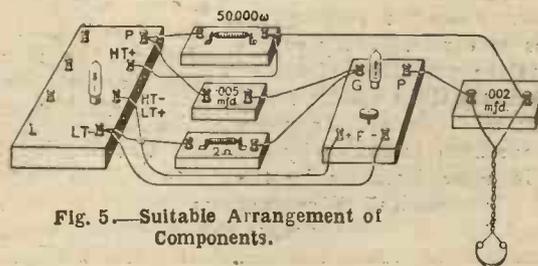


Fig. 5.—Suitable Arrangement of Components.

begin with they can be gradually reduced with a pair of scissors whilst the set is in operation, until the best value is found. The grid leaks may be mere pencil lines on paper, the proper size being found by trial.

Condensers

The condensers can be made up quite easily from copper foil and ruby mica .002 in. thick. Instructions for doing this will be found in the "Work" Handbook "Wireless Telephony and Telegraphy," price 1s. 6d. Two foils with an overlap of 2 in. by 1 in. will give a capacity of .001 microfarad, and each additional foil will increase the capacity by this amount. Condensers of capacities ranging from .003 to .007 microfarad can thus be made up and tried out.

If the condensers are too small, speech will be faint and indistinct. If they are too large a curious effect will be observed. When current is switched on an interval of perhaps as much as a dozen seconds will occur before anything is heard. This is due to the charging up of the condensers.

The extra grid cells needed will usually be provided by one pocket flash-lamp battery attached to the terminals at the lower end of the panel; some valves, however,

will require a good deal more than this for proper working to be obtained.

Once the correct values have been found the parts may be mounted upon a panel of the same size as those used for other units in the set. There is only one point that calls for attention, and that is in the filament rheostat. High-temperature valves pass an amount of current ranging from .4 ampere (Ora, Xtraudion, Cossor) to .75 ampere (R, Ediswan, V24). Three in parallel will thus need from 1.2 to 2.25 amperes, which is a good deal for one rheostat to carry. Be sure, therefore, that you obtain one capable of taking the current that your valves will need without over-heating.

Operation

In use the unit will be found to act excellently. The filament current is rather critical, but otherwise there is no special difficulty on short waves. When, however, one deals with very long waves the unit may be found liable to oscillate. This can be overcome quite easily by reducing the filament current. If any one of the three valves shows a tendency to oscillate on short waves, the value of its grid leak is not quite correct. A little thickening or reducing of the pencil-line grid leak will usually set matters right. R. W. H.

right of inspection. As regards the gas itself (as distinct from the pipes, etc.), the ownership of such gas passes from the company to the occupier automatically as it flows through the meter. Neither the house-pipes nor the gas that they contain, therefore, belong to the gas company. The latter in effect are merely licensed or allowed by the landlord or tenant to use the pipes for the sole purpose of passing gas from their outside mains into the house for the use of the occupier.

In the absence, therefore, of any distinct agreement made with the gas company regarding the use of the inside supply pipes as an earth, the company would appear to have no legal power to object. To support any claim to do so they would have first to prove either that damage had been actually caused to their property (that is, to the meter, outside mains, and the gas they contain), or else that there was reasonable cause to fear such damage. It is extremely unlikely that any court would grant an injunction based on either of these grounds.

The Landlord's Legal Position

The position of the landlord is rather different. If the aerial should be struck by lightning there is always a possibility of damage if the only earth is inside the house. In these circumstances it is perhaps reasonable that a landlord should ask for an indemnity against such damage. This risk will, of course, be covered at a very small premium by any insurance company.

The Safe Way

The safest course is undoubtedly to use an "outside" earth wherever possible, together with a switch to connect the down lead directly to earth whenever the receiving set is out of use. With such an arrangement there is absolutely no risk of damage from lightning. D. L.

Indoor "Earths" and the Liability for Damage

By a Barrister-at-Law

IT is a common practice when there is difficulty in getting convenient access to an "outside" earth to make use of the nearest gas or water supply pipe as a substitute. If there is a choice, a water-pipe is preferable for many reasons. In the first place, it is made of lead and a soldered connection presents little difficulty. In the next place, all the joints in the total length of pipe-line are metal to metal, and therefore of low resistance. Gas-pipes, on the other hand, are usually made of wrought iron, to which it is more difficult to solder the earth lead. Also any joints that occur are generally filled with red-lead, which lessens the conductivity of the system.

Gas-pipe Earth Dangers

At the same time there is a widespread feeling of "nervousness" regarding the use of gas-pipes as earths. Many people are fearful as to the possibility of fire or explosion, particularly if the outside aerial should be struck by lightning. In many cases tenants have been forbidden by the landlord, and in some instances by the inspectors of gas companies, to connect their wireless sets to the gas-supply pipes.

There is practically no ground for such excessive precaution. In the ordinary way the voltages and currents picked up by any

receiving aerial are exceedingly minute, and represent an absolutely negligible amount of energy. There is no possibility of "sparking" or fire arising from such currents.

In the very remote contingency of the aerial being struck by lightning, it is difficult to say precisely what effects might follow. The first tendency would be for the charge to spread itself uniformly over the entire pipe system. This would reduce the voltage, and the charge could then gradually leak away without causing any damage. On the other hand, the charge might jump from the gas-piping through the first available discharge path to earth. This would probably create a heavy spark or flame discharge which might burn or damage any woodwork in the vicinity, but it could not ignite or explode the gas in the pipes. Coal gas only becomes explosive when it is mixed with air. In fact, it cannot even burn until brought into contact with the atmosphere.


The Gas Company's Legal Position

As regards the power of a gas company to forbid the use of such earths, it may be of interest to set out the legal position.

Usually the house service-pipes leading from the meter are landlord's fixtures, over which, however, the gas company has a

An Improved Slider

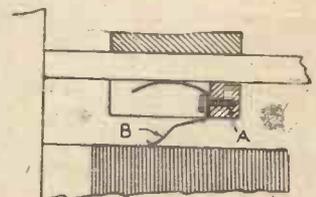AN improvement on the ordinary round slider is shown in the accompanying illustration. A block of fibre or ebonite is cut to fit the square brass rod. In this groove is fitted a small block A,



Improved Type of Slider.

to which is attached the contact spring B. No special measurements are given. The sides should be milled so that a firm grip is obtained. It is important that the spring should be bent up at the right angle at the point of contact. W. J.

:: Progress and Invention ::

Clip-in Resistance

AN improved form of clip-in resistance, such as used for grid leaks, is shown in Patent No. 198,189/23 (W. Ede, E. W. Scammell, and S. H. van Abbott, all of Birmingham). The resistance is formed by a thread of cotton or other suitable material, impregnated with a solution of copper sulphate. Alternatively any other

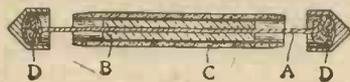


FIG. 1




FIG. 2

Figs. 1 and 2.—Longitudinal and Cross Sections of Clip-in Resistance (No. 198,189/23).

conducting and non-polarising liquid can be used. In Figs. 1 and 2, A is the thread of cotton, enclosed in a glass tube B. This is in turn placed in a slightly longer vulcanite tube C. The ends of the cotton are placed in small pads of cotton D, which are also impregnated, and make contact with the copper caps.

A Radiogoniometer

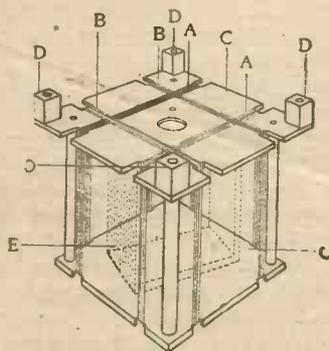THE object of the invention described in Patent No. 198,425/23 (L. G. Preston, C.B., C. E. Horton, B.A., and G. W. Harris, A.M.I.E.E., all of H.M. Signal School, Portsmouth) is to improve the electrical efficiency and simplify the construc-




Details of Radiogoniometer (No. 198,425,23).

tion of radiogoniometers. Two field coils A and B, having their axes at right angles, are each wound in two sections, proportioned and spaced so as to give an even magnetic field. The plates C are made of insulating material, notched to receive the fixed-coil windings. Small pillars D are provided, so that the instrument can be fixed to a panel. The movable search coil E is mounted on a rotatable spindle, to which may be attached a pointer.

A Simple Coil-holder

IN Patent No. 198,589/23 (A. W. Knight, of Peckham) is shown a simple and improved form of coil-holder. The general arrangement is clear from the figure. A is a piece of ebonite fixed rigidly to a base and provided with sockets for the ordinary plug-in slab, honeycomb or lattice-wound coils. Through this ebonite is placed a brass rod B, to which is attached another block, as shown. Over this rod is fixed a movable tube C, to the end of which is fixed a third block. Coils are placed in the sockets provided, and the coupling altered by turning the knobs D and E. A spring and lock-nut are provided to keep

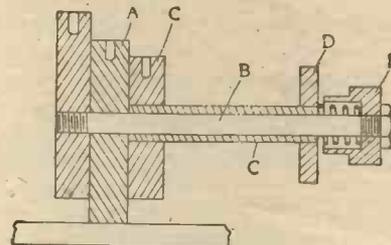the pieces of ebonite in close contact. In order that the axes of the coils may be in a



Coil-holder (No. 198,589/23).

straight line the blocks can be made in steps to accommodate various coils.

Talks, Tests & Telephony

EXPERIMENTAL transmissions are still going strong in spite of the fact that enthusiasts are almost compelled to wait until eleven pip emma each night before they can commence operations. It has been said that the operators of these stations sit up all night and sleep all day; but this is a libel. One cannot help sympathising, however, when each station closes down at about twelve-thirty with: "Well, old man, I am closing down early; going to have an early night to-night."

It appears strange that these stations do not devote a little attention to working on very low power, on, say, 175 metres. In most instances communication could be established between one and another over short distances with exceedingly low power. Some months back I heard 2XR and 5TR working together. The distance between them is something like eight miles or so, and 5TR was using a power of only 2 watts at the time. I do not think that this power would interfere with listeners-in on 300 metres or over unless the listener is a very near neighbour. If this scheme were adopted a great deal of work could be done during broadcasting hours on these short waves and low powers without interfering with the amusement of broadcast listeners-in. Anyway, it could be tried, and if a "broadcast-catcher" objected, he is bound to be a near neighbour and no doubt a satisfactory agreement could be arrived at.

2KT of Wanstead has now developed enormous strength in his signals. Since he has raised his aerial a matter of 15 ft. or so the strength is almost doubled.

2NM of Caterham is also doing well. Reports of reception of him have been received from the North and Midlands, and he appears to work quite easily with

French amateurs. He evidently is quite at home with the "Beers"!

A station which has also increased its lung power by alterations to his aerial is 5DT of Forest Hill. I believe that his aerial mast is 75 ft. higher. Loud-speaker reception of his speech with two valves is possible fifteen miles away.

2MC of Westcliff on short waves is also good. His gramophone music is extremely well modulated and pleasant to listen to twenty-three miles away on two valves.

2PX has during the last week or so been indulging in duplex telephony, and has demonstrated the possibilities of this quite effectively. It was not many months back that this stunt was thought impracticable, but now it seems to be well on the way to universal adoption, as many other stations have also given it a trial.

2OM and 5CP are still going as strong as ever. When these two stations get going they make things quite lively in their corner of the ether.

On the whole the work being done by the stations I mention and many others is very creditable, and tends to show that the enthusiasm of their owners remains unabated. The list of amateur transmitters is rapidly becoming larger, and it is understood that we are now well down the alphabet in the six series. The amateur-transmitter movement is one which has come to stay and which has got to be reckoned with in the future.

CRITICUS.

In all letters to advertisers please mention "Amateur Wireless."

About the Accumulator

THERE are two types of electric cell, the primary cell and the secondary cell, or storage cell. In a simple primary battery consisting of a zinc rod and a copper plate immersed in sulphuric acid, the energy generated when the zinc dissolves in sulphuric acid appears as electrical energy. This is shown by connecting a voltmeter between the zinc and the copper plate. This type of cell is not particularly efficient, for after a minute or so the copper plate is covered with bubbles and the current ceases to flow. This phenomenon is known as polarisation.

The same thing happens if we electrolyse water with one Daniell cell (E.M.F. 1.07 volts). The current passes for a moment or two, then it stops, and nothing will induce it to flow, except the addition of a second Daniell cell. The water is decomposed into its constituents, namely, oxygen and hydrogen.

The Gas Battery

If in this experiment the cells be quickly replaced by a voltmeter it is found that the bubbles of oxygen and hydrogen that have not detached themselves disappear, and a momentary current flows in the opposite direction with a maximum E.M.F. of 1.47 volts.

This is termed the back E.M.F. of polarisation, and explains why it is impossible to electrolyse water with only one Daniell cell. The back E.M.F. of polarisation of water is greater than the electrolysing E.M.F.

The accumulator is based upon this principle. The first accumulator was Grove's gas battery.

Many workers set themselves the task of improving the gas battery, and among the most successful was Planté. He used lead electrodes, as he found that the gases liberated combined with the electrodes.

Forming

The anode he found was coloured brown with lead peroxide and the cathode was covered with grey spongy lead. This cell had an E.M.F. of 2 volts and was superior to the Grove gas battery in many respects. Planté found that by repeatedly charging and recharging his cell the active material could be made to extend right through the plate. But this was a tedious process.

Faure found that this tedious process of formation could be reduced to about twenty-four hours by filling a lead grid with active material. The anode he filled with a paste of red lead and sulphuric acid, the cathode with a mixture of litharge and sulphuric acid. Then by passing a current through the cell for about twenty-four hours the plates were formed. When the cell is fully charged the anode is brown and the cathode is grey, and the

E.M.F. is about 2.2 volts. When the cell is discharged both plates become coated with lead sulphate.

The electrolyte of an accumulator is a good conductor of electricity, therefore the internal resistance is extremely small, in fact, in the neighbourhood of 0.01 ohm. It is obvious that when an accumulator is short-circuited a very large current will flow. From Ohm's law:

$$C = \frac{E}{R}$$

If the voltage be 2 volts and the in-

ternal resistance 0.01 ohm, then the current (C) will be 200 amperes.


If 200 amperes are being taken out of an accumulator in a very short space of time the chemical action will be so violent that the plates will buckle.

If the instructions which are printed on the side of every accumulator are adhered to, and special precautions are taken against short-circuits, and the voltage per cell is not allowed to fall below 1.8 volts per cell, the accumulator will last for several years. N. C. S.

Around the Showrooms

"Sterling" Units

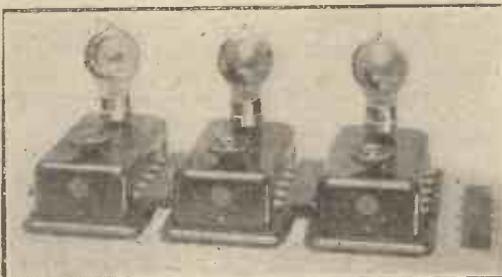ONE of the neatest series of units on the market at present is that made by the Sterling Telephone and Electric Co., Ltd., of 210-212, Tottenham Court Road, W.1. Three of these units are shown in the photo. Five terminals are provided on each side for making connections. A num-



Three Sterling Units.

ber of units can be connected in cascade by means of connections, one of which is shown on the extreme right. The metal sockets in this connector are fixed on a rocker, so that it does not matter if the units are not exactly level. The low-frequency units are made with one, two, or three valves. Detectors and high-frequency units will be placed on the market as soon as possible. Each unit is mounted on a hardwood base, complete with polished black metal cover.

Another New Filament Resistance

A filament resistance called the "Filafone" has fitted underneath the usual contact arm (it is a rotary resistance) another one which acts as a switch to cut out an amplifier and change the phone connections. This second arm, insulated from the first, extends further on one side of the spindle than on the other. The two ends make contact on two concentric split rings, like a commutator.

The connections are changed when the resistance is turned to the off position. Electro Devices, of Victoria Road, Oulton Broad, Lowestoft, make these instruments.

Lids that Make Shelves


Some neat two-, three- and five-valve cabinet sets are being made by the British Radio-Wireless Manufacturing Co., Ltd., of Electric House, Ship Yard, 116, Wardour Street, W.1. Unlike the majority of cabinet sets, the panel is horizontal and is enclosed by a lid, the two halves of which swing down to form shelves to hold batteries, etc., when the cabinet is open. Although primarily intended for broadcast reception, these receivers can be wired to cover any required wavelength range. This firm also manufactures "O-Solowd" crystal, a new specimen of the fused-galena family.

Four Phones in One

A device called the "Procophone," supplied by Spencer's Stores, Mason's Avenue, Coleman Street, E.C., consists of a tube, over the ends of which are clamped a pair of phones, provided with four pairs of ear tubes, as used in medical stethoscopes. If desired eight pairs may be used, and thus a number of persons can listen with only one pair of ordinary phones.

The Peto-Scott Company's Address.—

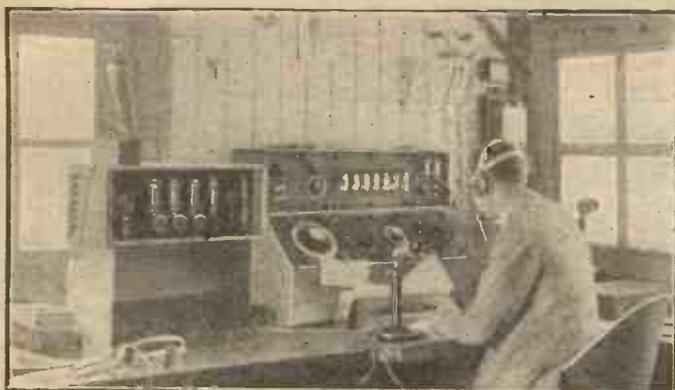Many thousands of our readers know that the address of the Peto-Scott Co., Ltd., is 64, High Holborn, London, W.C.1. That is where their head office is situated. There was a misprint in their advertisement in our issue of last week, but fortunately AMATEUR WIRELESS readers are so familiar with the address of this company that few, if any, letters went astray.



Direction Finding and Receiving Apparatus at Croydon Aerodrome.

AS was shown in the previous articles on this subject, two outstanding characteristics are to be observed in connection with loop aerials. These are: (1) When the plane of the aerial is in line with, or at right-angles to, the direction of the transmitting station, maximum or zero signals respectively will be received. (2) Whilst it is possible, with an ordinary frame aerial, to ascertain the minimum, or zero, position within one degree of accuracy, an error of ten degrees might easily be involved in finding the maximum position.

Two Systems Compared

This latter characteristic is not necessarily a disadvantageous one in all cases. In an ordinary ground direction-finding station, for instance, where silence can be maintained in the operating-room through the agency of sound-proof doors, etc., excellent results can be obtained by using the minimum method. This is only so, of course, when the important thing is to get "bearings" and there is no need to read the actual message which the signals convey.

Under certain conditions, however, it is not possible to eliminate external noises; for example, on board aircraft. Other examples (of more direct interest to certain amateurs, no doubt) would be: when the operating-room happens to be situated next to the nursery, or when there is no available means of holding up neighbouring traffic (trains, buses, trams, etc.) at critical moments. Also, apart altogether from the desire to be able to get accurate bearings, most amateurs will dislike having to miss a portion of the message whilst taking a bearing at the minimum point.

Maximum Device

These difficulties are surmounted by means of a special device which combines all the advantages of maximum strength of signals with maximum sensitivity. This device consists of two loop aerials fixed at right-angles to one another, as illustrated diagrammatically in Fig. 1. Suppose that these two coils are joined in series, the loose extremity of each being connected up to a receiver in the usual way. Suppose also that we adjust the

Position and Direction Finding :: IV.—The Maximum Method

position of the joined coils so that the portion CD is pointing towards the transmitting station X, that is, so that its plane is in line with the transmitter. CD is now in a position to receive

maximum signals from X. AB, on the other hand, should be picking up no signals from X, since its plane is at right-angles to the direction of the latter. Therefore, if we suddenly switched AB out of the circuit (automatically connecting up both ends of CD to the receiver as we did so), there should be no alteration in the strength of signals

connected to one another. Reference to Fig. 2 will make this clear. AB and CD are two coils of wire, both of which are connected to a double-pole switch, as illustrated. If a current is passed through the coil AB in the direction indicated by the arrow, it will flow *down* through the coil CD (as shown by the left arrow) when the switch is in the left-hand position, and *up* through the coil CD (as shown by the right arrow) when the switch is in the right-hand position.

Or, again, if two currents were flowing simultaneously in, say, an upward direction through both coils they would oppose one another when the switch is put in the first position, and assist one another when the switch is thrown into the latter position. The same would happen, of course, in a reverse order, if the two currents flowed in opposite directions through the coils in the first instance, that is, upwards in AB and downwards in CD. The thing to note in either case is that the resultant current flowing in the circuit will be represented by the sum of the individual currents in the one instance, and by their difference in the other. This effect can be utilised to great advantage in the maximum method.

Difficulties

Instead, therefore, of joining the two aerials directly in series, as shown in Fig. 1, we must have some means for reversing them similar to that shown in Fig. 2. With such a system it would be a simple matter accurately to determine the direction of a transmitting station, once the approximate maximum position of the coil CD had been found.

This introduces another difficulty. If we could be sure that the loudest signals were being received on this coil alone in the first instance, the matter would be quite easy. But we might actually be receiving on AB, whilst CD remained at right-angles to the transmitter, in which case the resultant bearing would be 90 degrees out! Even when more turns of wire are used in one aerial coil than in the other it is by no means a simple matter, in practice, to distinguish between two "maximums," apart from the inconvenience of such an arrangement.

It is necessary, therefore, to commence operations by excluding the coil AB from the circuit while the approximate maximum position of CD is being found. When this is done, and not before, AB is brought into the circuit. If AB is now picking up any energy this will be manifested by the increase or decrease in the strength of the signals being received. If

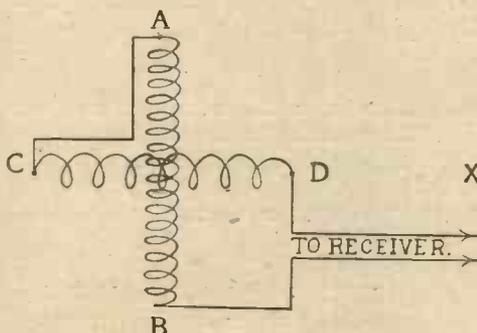


Fig. 1.—Arrangement of Loop Aerials for Maximum Method.

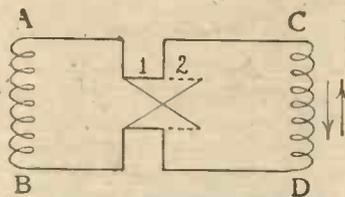


Fig. 2.—Diagram Explaining Variation in Signal Strength.

heard in the telephones. This, then, would be one way of telling whether CD is in the exact maximum position with respect to X or not. If there is any change of signal strength on switching AB out of the circuit, CD cannot be in the exact maximum position. If the plane of CD is not exactly in line with the direction of X, either of two things may happen when AB is switched out of circuit: signals will get weaker or stronger.

Advantages of Maximum Method

This is an important point which needs to be understood clearly before the advantages of this system can be fully appreciated. The nature of the variation in signal strength will depend on the manner in which the two coils are con-

the alteration in strength is very slight it may not be detected at once. By throwing the reversing switch backwards and forwards, however, even the smallest difference will be detected as the energy in the coil AB is alternately added to and subtracted from the energy in the coil CD.

AERIAL NAVIGATOR.

(To be continued)



2 L O

2 L O has evidently been thoroughly put on his mettle by the heckling of the Press and the questions asked in the House of Commons. He is passing through yet another stage, from which he will no doubt emerge with honours. Don't forget to send your postcard and state the kind of programme you like. Everyone cannot get exactly what he wants, but the majority will be satisfied. Tastes vary greatly, but the Englishman has as a rule good taste, so take heart and don't forget your postcard. There is no doubt but that the quality of the programmes issuing from that station is improving as time goes on. It is obvious, however, that jazz tunes are not so well suited to broadcasting at present as the more classical material.

The announcer at 2 L O on June 30 referred to the dance items as "spasms." According to my dictionary the word spasms means "a convulsive and involuntary muscular contraction, a sudden or convulsive act, movement, etc., a violent and generally fruitless effort"! Well—I ask you?

On June 29 Mlle. Lenglen made a delightful little speech from 2 L O. I wonder how many readers noted how the personality of that famous tennis champion was wafted over the ether? To me it seemed that the lady was actually in the room; probably it reminded our ex-service men of their *parlez-vous* with many French damsels concerning many things. When she laid stress on the correct pronunciation of her name, I felt truly sorry for the gallant announcer, but nevertheless I believe that he enjoyed the joke against himself as well as any of us. I was inclined to be antagonistic to another talk encroaching on the musical items, but when she had finished I found that I had enjoyed the talk and the spirit of France conveyed with it!

CRITICUS.

Proposed Society of Transmitting Licence Holders

A MEETING of the transmitting-licence holders in the London area is to be held at King's College, Strand, at 6 p.m. on July 20 to discuss the formation of a society of transmitting-licence holders in the London area.

BELL-SYSTEM telephone engineers have discovered that there are a particularly large number of "blinds spots" in New York. For instance, W E A F can be heard only very faintly in northern New York. The explanation offered is that the natural wavelength of the office buildings, which are largely constructed of steel, intervening is 500 metres, this being the wavelength of the station referred to, and on this account absorption takes place.

We hear on good authority that a number of "reaction fiends" are ruining the wireless concerts in Sefton Park district, Liverpool. Those responsible are certainly not "wireless amateurs," as a local paper states.

A crime for which the wireless amateur is held responsible is the stealing of telephone apparatus from call-boxes. The Post Office state that they are "not prepared to quote figures" as to the number stolen.

Mr. J. T. C. Moore-Brabazon, M.P., has written to the *Times* concerning the wreck of the *Trevessa*, urging that the Board of Trade should insist on lifeboats, as well as the mother ship, being fitted with wireless apparatus.

It is rumoured that what is to be the most powerful broadcasting station in the world is being erected secretly in Detroit (U.S.A.). Mr. Henry Ford, of car fame, is said to be responsible for the building of the station, and that he will use it in his campaign for the presidency of the U.S.A. next year.

A new system of secret telephony is being tested by Bell-system telephone engineers in America over a 30-mile stretch of water between Los Angeles and Catalina Island. The device used confuses the conversation at one end and puts it into order at the other.

A party of M.P.'s visited 2 L O, and inspected the studios and plant on Thursday, July 5. All expressed a very high opinion of the value of broadcasting. One member, also a member of a County Education Committee, discussed with a B.B.C. representative the probable cost of fitting schools with loud-speakers.

The high-power wireless station to be erected at Hillmorton, as we announced last week, is to be the British end of the Imperial wireless chain. Constructional work will be started in about a month's time. Masts 820 ft. high are to be erected for the aerial.

The report of the Marconi International Marine Communication Co., Ltd., just issued, states that the gross revenue for 1922 amounts to £1,103,970 15s. 5d., as compared with £1,084,460 6s. 8d. for the preceding year. The net profit amounts to £171,848 4s. 2d. This is an increase as compared with 1921, due in part to additional business consequent upon the return of ships to commission after the period of great depression in the shipping trade and also to economies in the methods of working and control.

The Aberdeen and Bournemouth stations are progressing "as fast as an icebreaker through a floe of ice," as a B.B.C. official put it.

On Friday, July 13, 2 L O has arranged a novel competition for listeners-in. Three B.B.C. officials will commit a "crime," and a description will be broadcast from 2 L O. All listeners-in within a radius of 40 miles from London will be able to participate, and have the chance of winning one of three prizes. The "criminals" will most likely escape in cars, and listeners will be required to furnish a description of the car and the occupants.

Mr. Tyrwhitt Drake, F.Z.S., one of the very few people who own a private zoo, will speak on his wild animals from 2 L O on July 13.

THE "WORK" HANDBOOK
WIRELESS TELEGRAPHY AND
TELEPHONY

TELLS YOU HOW "wireless" works, and how to make a complete range of crystal and valve receiving apparatus.

IT IS ONLY EIGHTEENPENCE,

But it is the Best Yet!

CASSRELL & COMPANY, LIMITED, LA BELLE SAUVAGE,
LONDON, E.C.4.



Crystals and the Loud-speaker

SIR,—With regard to crystal reception, I should like to say that I can receive 2 L O on a home-made loud-speaker using a crystal set. My aerial (which is a twin 50-ft. and only 25 ft. in height) is very badly screened by a tree. As I am situated about twelve miles from 2 L O, I consider these results good. I should also like to add that I can get 2 L O on the phones using an iron bedstead as an aerial and also an indoor aerial 15 ft. long.—F. M. (Ealing).

SIR,—We beg to inform you that we have carried out experiments as per your article on page 908, using the "Unisector" crystal circuit in conjunction with the "Maxsig" crystal. The experiments were certainly very successful in reproducing speech and music on a loud-speaker. This was quite clear at 10 ft. away from the apparatus. We are pleased also to add that we have tested nearly every crystal and crystal circuit that is known, but this is by far the best. The loud-speaker used was our new "Ultra," which we intend placing on the market shortly.—EDWARD E. ROSEN AND CO. (London).

A Reader's Opinion

SIR,—I feel it my duty to tell you how much I appreciate AMATEUR WIRELESS and also the exceedingly prompt manner in which you supply technical information.

I am a reader of several wireless publications, but I can truthfully say that in no case have I had such prompt and courteous attention to my inquiries as you have given me.—A. S. (Dornoch).

American Valves

SIR,—Allow me to take exception to the remarks on the above in Mr. J. Hartley Reynold's article on "Dull-emitter Valves" in No. 56 AMATEUR WIRELESS. This sentence: "The most satisfactory dull emitter made up to the present is the WD11," is certainly very sweeping and misleading. I propose to describe two others made by the Radio Corporation of America, or rather marketed by them and made by the G.E.C.

The first is the UV199, only recently placed on the market. This valve operates on 60 milliamperes (.06 amperes) filament current, and can be operated from an ordinary flash-lamp battery. The wattage is .18 or 3/50 of the energy used by the standard R valve. In spite

of this the valve gives better results than the UV201.

The filament, which is extremely fine, is known as the XL tungsten filament, and has all the advantages of the coated filament, and the strength and long life of the tungsten type. A curious feature of this valve is that if operated at too high a temperature it becomes inoperative, but by operating at the rated voltage of 4½ volts it again becomes normal. The length of time required is proportional to the time misused and the operation is carried out with the plate current off. Although the UV199 is an ideal valve for many purposes, it cannot compete as an amplifier with the powerful UV201, which takes 5 volts at .25 ampere, and has an electron emission five times that of UV201. This is not accomplished at the expense of a high temperature, it being much lower than the UV201. The high degree of vacuum, coupled with the electron emission already described, make it ideal for power amplification. Although I have made extensive inquiries, I cannot find any agent in this country.

In case any of your readers would like to make inquiries, the name and address of an American firm of retailers are The Sunbeam Electric Co., 71, Third Avenue, New York. The prices of the valves are UV201, \$6.25; UV199, \$6.25.—D. P. (Sheffield).

The Price of Parts

SIR,—We have read with interest the letter from W. J. E. (Hornsey) in your issue of June 30, and as retailers perhaps you will allow us a few remarks.

The letter raises several questions which are of interest to retailer and buyer alike. There always will be two classes of traders: those who are out to make a large profit at the first opportunity, without a thought for the future, and those who are satisfied with a small profit and hope for repeat business with their customers.

It seems unfortunate that so many retailers with little or no knowledge of wireless have taken up the selling of parts and accessories, as many, by their lack of knowledge both of the buying and selling side of the business, have driven local people to make their purchases away from their own local shops.

With regard to the great divergence of prices, though "300 per cent." profits may be asked by some retailers, no one is forced to buy from them. The buying public should also remember that there are

tremendous differences in the quality of wireless goods on the market.—RADIO STORES (Epsom).

[We have received several other letters of a similar nature to the above.—ED.]

Repair Your Own Valve

SIR,—Having accidentally burnt out an X-traudion valve and which I could not mend by the usual method as the distance between the ends of the broken filament was about ½ in., I solved the problem in another way. I heated the glass near both filament supports with a small blowlamp so that it softened, and the air pressure then pushed the legs closer together. Then I put 6 volts across the filament and welded it together. The valve has been used on the H.F. panel constantly for three months since the repair.—C. M. (Great Yarmouth).

Broadcasting and the Retailer

BELOW we give some points from a letter addressed to Captain Lewis, of the British Broadcasting Company, Ltd., by Mr. C. J. Close, manager of Harrod's wireless department. The letter refers to the alteration in the time of the afternoon broadcasting from 5 P.M. to 5.30 P.M., and Mr. Close says:

"Before the change, when the children's hour commenced at 5 P.M., those who desired to get an impression of what broadcasting was really like were usually advised that 'five o'clock was a good time.' Now the programme does not commence until 5.30 P.M., and the microphone is occupied by voices which may or may not be suitable for broadcasting."

Mr. Close continues: "I fully understand that you have many opinions with which to contend, but both your good selves and those of us who are interested in the sale of wireless apparatus must realise that unless the opportunity is available of giving really popular demonstrations during business hours we shall suffer financially. I therefore ask your company to consider seriously reverting to the original time of 5 P.M.; and also please let us have the 'Uncles' with their jolly talk to the kiddies."

ANNOUNCEMENTS

"Amateur Wireless and Electrics." Edited by Bernard E. Jones. Price Threepence. Published on Thursdays and bearing the date of Saturday immediately following. It will be sent post free to any part of the world—3 months, 4s. 6d.; 6 months, 8s. 9d.; 12 months, 17s. 6d. Postal Orders, Post Office Orders, or Cheques should be made payable to the Proprietors, Cassell & Co., Ltd.

General Correspondence is to be brief and written on one side of the paper only. All sketches and drawings to be on separate sheets.

Contributions are always welcome, will be promptly considered, and if used will be paid for.

Queries should be addressed to the Editor, and the conditions printed at the head of "Our Information Bureau" should be closely observed.

Communications should be addressed, according to their nature, to The Editor, The Advertisement Manager, or The Publisher, "Amateur Wireless," La Belle Sauvage, London, E.C.4.



Some of these transmissions are commercial or official. Wavelengths and times are liable to alteration without notice. The times given are according to British Summer Time.

London B.B.C. Station (2 L O), 369 metres. Weekdays, 11.30 a.m. to 12.30 p.m., concert; 5.30 p.m. to 6 p.m., women's half-hour; 6 p.m. to 7.30 p.m., children's stories and concert; 8 p.m. to 11 p.m., concert and news. Sundays, 3 p.m. to 5 p.m., concert; 8.30 p.m. to 10.30 p.m., concert and news.

Manchester B.B.C. Station (2 Z Y), 385 metres. Weekdays, 3.30 p.m. to 4.30 p.m., concert; 5.30 p.m. to 6 p.m., women's half-hour; 6 p.m. to 6.45 p.m., children's hour; 6.50 p.m. to 7 p.m., talk on "Current Events," etc.; 7.20 p.m. to 7.45 p.m., concert and news, etc.; 8.15 p.m. to 10.25 p.m., concert, news, men's hour, weather forecast, etc. Sundays, 8.30 p.m. to 10.25 p.m., concert and news, etc.

Birmingham B.B.C. Station (5 I T), 420 metres. Weekdays, 3.30 p.m. to 4.30 p.m., concert; 5.30 p.m. to 6 p.m., women's half-hour; 6 p.m. to 6.45 p.m., children's hour; 7.30 p.m. to 8.15 p.m., concert and news, etc.; 8.45 p.m. to 10.30 p.m., concert, news, men's hour, weather forecast, etc. Sundays, 8.30 p.m. to 10.30 p.m., concert and news, etc.

Newcastle B.B.C. Station (5 N O), 400 metres. Weekdays, 3.30 p.m. to 4.30 p.m., concert; 5.30 p.m. to 6 p.m., women's half-hour; 6 p.m. to 6.45 p.m., children's hour; 8 p.m. to 11 p.m., concert, news, men's hour, weather forecast, etc. Sundays, 8.30 p.m. to 11 p.m., concert and news, etc.

Cardiff B.B.C. Station (5 W A), 353 metres. Weekdays, 5.30 p.m. to 6 p.m., women's half-hour; 6 p.m. to 6.45 p.m., children's hour; 7 p.m. to 8 p.m., concert and news; 8.30 p.m. to 10.5 p.m., concert, news, weather forecast, etc. Sundays, 8.30 p.m. to 11 p.m., concert and news.

Glasgow B.B.C. Station (5 S C), 415 metres. Weekdays, 3.30 p.m. to 4.30 p.m., concert; 5 p.m. to 5.30 p.m., women's half-hour; 5.30 p.m. to 6 p.m., children's hour; 8.15 p.m. to 10.45 p.m., concert, news, men's hour, weather forecast, etc. Sundays, 8.30 p.m. to 10.45 p.m., concert and news, etc.

Croydon (G E D), 900 metres. Daily. **Eiffel Tower (F L), 2,600 metres.** Daily, 5.40 a.m. and 11.15 a.m., weather forecast; 3.30 p.m., Stock Exchange news; 6.20 p.m. to 7 p.m., concert, and 10.10 p.m., weather forecast.

The Hague (P C G G), 1,050 metres. Sundays, 4 p.m. to 6 p.m., concert. Mondays, 9.40 p.m. to 10.40 p.m., concert. Thursdays, 9.40 p.m. to 10.40 p.m., concert.

Paris Concerts Radiola (S F R), 1,786 metres. Daily, 12.45 p.m. to 1.45 p.m., concert and news; 5.5 p.m. to 6.15 p.m., concert; 8.45 p.m. to 10.30 p.m., concert; also concert from 2 p.m. to 3 p.m. on Sundays.

Rome (I C D), 3,200 metres. Daily, 11 a.m. **Königswusterhausen (L P), 2,800 metres.** Daily, 8 a.m. to 9 a.m., Stock Exchange news; 12 noon to 1.30 p.m., Stock Exchange news; 5 p.m. to 6.30 p.m., Stock Exchange news.

Amsterdam (P C A), 1,800 metres. Daily, 2.20 p.m.

Haren (O P V H), 900 metres. Daily weather report on 1,100 metres at 1 p.m. and 5.50 p.m.

Ecole Supérieure des Postes et Télégraphes, 450 metres. Tuesdays and Thursdays, 7.45 p.m. to 10 p.m., concert. Saturdays, 2.30 p.m. to 7.30 p.m., educative lectures and concert. Daily, at 11 a.m., 5.5 p.m., and 9.10 p.m., news and concert.

"A TRANSMISSION BOARD OR CHART" (cont. from p. 36.)

and white respectively on the reverse sides (see the detail illustration). These could be changed in a moment exactly as required.

An amateur might possibly feel it worth his while to construct a chart for his own use. Once he had taken his time to produce a list of the names of the stations of a good readable size, he could draw in the thick black lines, and the occasional alterations required could be made by adding lines or by cutting out lines by means of white paper pasted on; but probably he would regard the affair as not worth the trouble involved, and we should be rather inclined to agree with him; in the case of a club meeting the objection would not apply. In any case, we present the idea for exactly what it is worth.

An Interesting County Court Action

A CASE of considerable importance to users of receiving sets came before Judge Crawford at Southend County Court on Friday, July 6. According to the report in the *Daily News*, a Westcliff electrician, Henry Lee, sued Albert Bird, a wholesale tobacconist, for the value of a receiving set he had installed.

It bore, it transpired, no British Broadcasting Company stamp, and counsel for the defendant argued that the set in the absence of this stamp was useless. If used by the defendant he would be guilty of a misdemeanour.

In evidence Mr. Bird said that he told Mr. Lee this, and was advised to take out an experimenter's licence. "When I got the form," said Mr. Bird, "I saw I had to certify that I wanted the licence for some scientific object or an object of general public utility. I could not conscientiously sign that."

His Honour agreed that had he signed he would have perpetrated a fraud. He said he supposed Mr. Bird knew about as much of the science of wireless as a newly-born babe, and would have had a lot of difficulty in persuading anyone that he had an object of public utility in view. Without the "B.B.C." stamp the set was useless, and therefore, as plaintiff had failed in his contract, he could not recover.

On the understanding that Mr. Bird would return the set, judgment was given for him with costs.

The Mullard Radio Valve Company, of Nightingale Lane, Balham, S.W.12, have notified us that the Mullard R valve is now selling at 15s. (fifteen shillings), instead of at 17s. 6d. as previously.

A Great Domestic Number is this week's issue of "Work" (price 3d.), containing special articles on "Making Wooden Stair-ros," "Distemping a Room," and "Making Living-room Furniture: The Chairs." Many other subjects are treated.

WIRELESS IN PARLIAMENT



(From Our Own Correspondent)

ASKED in the House of Commons last week by Sir Harry Brittain whether he had received any complaints as to the efficiency of the present system of broadcasting, the Postmaster-General said he had received very few complaints. The whole question of broadcasting was, of course, being considered by a committee appointed by his predecessor in April last.

In answer to Mr. D. G. Somerville, the Postmaster-General said he understood that the committee, although alive to the urgency of the matter, could not yet say when they would be able to present their report.

Replying to Mr. Frank Gray, Sir L. Worthington-Evans said there was no censorship of news transmitted from this country. The only official bulletin transmitted from the Leafield wireless station was that prepared by the Foreign Office. Press messages were also forwarded from the station on behalf of the correspondents of Canadian, American and Indian newspapers, as well as to ships at sea. They all bore specific addresses and were dealt with entirely as private telegrams.

In answer to a number of questions, Sir L. Worthington-Evans said he hoped to lay the agreement with the Marconi Company as to the licence for the Empire wireless chain on the table of the House as soon as it was completed, but he could not undertake that an opportunity for discussion would arise before it became operative. The company at present held no licence covering wireless communication with any countries outside Europe except the United States and Canada. The licence which was now under negotiation with the company would cover the erection of stations in Great Britain only, and would not be exclusive. It was not proposed to give the Marconi Company a monopoly of wireless communication within the Empire. The proposed licence would certainly contain no provisions precluding the Government or other companies from establishing similar wireless communications.

Sir L. Worthington-Evans informed Sir Burton Chadwick that the capital expenditure in connection with the Post Office wireless stations was approximately as follows:

Leafield	£115,000
Cairo	136,000
Northolt	43,000
Stonehaven	31,000

Buying Ebonite.—In the advertisement of P. H. Boys and Co., of 187, Goswell Road, London, E.C.1, appearing in our June 30 issue, the thickness of ebonite was given as "3/6"—a very obvious printer's error (oh, those printers!)—for "3/16" in.

WIRELESS BY WIRELESS EXPERTS. *The Best and Cheapest in the City.*

GOODS OF RELIABILITY and Made to Standard.

Aerial Wire, hard drawn 7/22's copper, 2s. 4d.; by post, 3s.
 Condenser Bushes, top, 1d. each, 11d. per doz.
 Do., bottom, 1d. each, 9d. per doz.
 Crystal Detectors, good value, ordinary type, 1s. 3½d.
 Do., enclosed in glass tube, 2s. 6d., 2s. 3d., 1s. 11d.
 Crystals, Hertzite, Zincite, Permanite and Talite, 9d. each in box.
 Bornite and Carborundum, 4d. each in box.
 Mixed Crystals, 6 different kinds, 9d. a box.
 Condenser Vanes, fixed or moving, per doz., 3½d.
 Condenser Scales, 0 to 180, each, 3½d.
 Condenser Spindles, all sizes, from 1½d. each.
 Contact Studs, with nuts and washers, 5d. per doz.
 Crystal Cups, 2 screw, 1d. each.
 Do., 4 screw, 2d. each.
 Dry Batteries, 4½ volts, 3d. each, 2s. 9d. doz.
 Variometers, complete with knob, 3s. 6d.

TRY OUR FAMOUS 'PHONES ON THE MONEY BACK PRINCIPLE at 16/6 Per pair

Ebonite, cut to any size, per lb., 3s. 6d.
 Ebonite Knobs, 2 B.A., each, 1½d., 3d., and 4d.
 Filament Resistances, velvet action, fine value, 2s. each.
 Do., engraved dials, 2s. 11d. each.
 Real Gold Cat's Whiskers, each, 2d.
 Do., per doz., 1s. 8d.
 Silver Cat's Whiskers, 1d. each, 9d. per doz.
 Perikon Detector, 2s. 3d. each, including crystal.
 Nuts, 2 B.A., 2½d. per doz.
 Do., 4, 5, 6 and 8 B.A., 2d. per doz.
 Telephone Terminals, with nuts and washer, 1½d. each, 1s. 4d. doz.

WE PREFER YOU TO CALL, BUT YOU CAN SEND FOR GOODS WITH CONFIDENCE. NO SUBSTITUTIONS

W.O. Terminals, with nuts and washer, 2d. each, 1s. 9d. doz.
 Terminals, with nuts and washer, 1d., 1½d. and 2d. each.
 Stops, with nuts, 7d. per doz.
 Slider Rod, brass, 13 in. long by ¼ sq., drilled, each, 3½d.
 Slider Knob, 2d. each.
 Screwed Rod, 2 B.A., 12 in. long, each, 3d.
 Do., 4 B.A., 12 in. long, each, 2½d.
 Leading-in Wire, rubber insulated, 1½d. per yd.
 Insulators, white reel, 1½d. each, 1s. 4d. doz.
 Do., white egg, 2d. each, 1s. 9d. doz.
 Valve Legs, nut and washer, 1d. each.
 Do., nut and washer, 10d. per doz.
 Valve Pins, nut and washer, 1d. each, 9d. doz.
 Plunger Springs, complete, 1d. each.
 Washers, 4 B.A., 1d. per doz.
 Do., 2 B.A., 1½d. per doz.
 All Ebonite Burndept 2-Way Coil Holders, 6s. 6d. each.
 Do., 3-way, 7s. 6d. each.
 Single Coil Holders, 1s. 4d. each.
 Transformers, tested and guaranteed, 15s. 6d.

LONDON WIRELESS CO., 113-114, FENCHURCH STREET,
(Corner Billiter Street, opposite Fenchurch Street Station).

Open 9 till 7.30. Saturdays, 9 till 2.30.

TRADE SUPPLIED.

Please enclose ample postage, balance refunded.

ELECTRONITE

THE FAMOUS CRYSTAL which, when used in conjunction with our TORDINODIUM WIRE, gives WONDERFUL RESULTS

VERSE No. 9
 She lay supine within the cup
 He loved her at first sight,
 Vowed he'd never give her up,
 His own Electronite.

In box with Contact Wire

1/6 Postage 2d.



Trade Supplied.

234, HIGH HOLBORN, LONDON, W.C.1.

Sole agents for Scotland: London Radio Stores, 37, Jamaica Street, Glasgow.

The Ideal
INSULATING VARNISH
HARDICOL
SHELLAC INSULATING
VARNISH CEMENT

Guaranteed made from pure shellac.
 A saturated solution in the cold.
 Perfect for all insulation work :: ::

Inquiries invited from the Trade.

6d. and 1/- Bottles. Also in bulk.

HARDICOL IS OBTAINABLE FROM THE USUAL DEALERS AND THE MAKERS:

A. F. Harding & Co. Ltd., Exmouth St., Stepney, E.




YOU



Want Us.

Why? Because We

MANUFACTURE

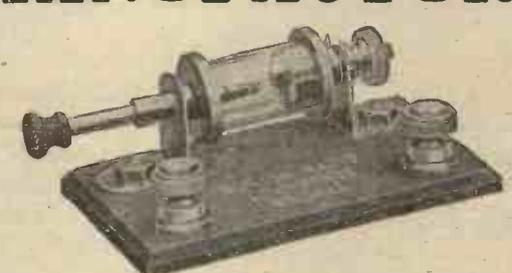

Send your inquiries for
 ALUMINIUM VANES,
 TERMINALS,
 CONTACT STUDS,
 AERIAL WIRES,
 SCREWED RODS,
 etc. etc.



MESSRS.
C. F. & H. BURTON,
 Progress Works,
 Bernard Street,
 WALSALL.

Phone 510.

Amateur Wireless

COUPON
 Available until Saturday,
 July 21, 1923.

APOLOGY to DISTURBED LISTENERS - IN

OWING to the huge demand for the "Autoveyors" Three Electrode Variable Condenser, it has been found impossible promptly to execute all the orders that have been received. Autoveyors Ltd., beg to apologise for the delay and to assure their customers that special efforts are being made to increase output and to expedite delivery at once.

The tremendous popularity of 3-E.V.C.

Three Electrode Variable Capacity Bridge Condenser
The Only Complete Absorber of Disturbances

is due to the fact that it eliminates all the interference and confusion that now spoils your reception—Static, Atmospheric, Morse, or interruptions by transmitting stations other than that to which you are tuned. In coast towns, where improperly regulated spark transmission by ships at sea reduces the ether to chaos, the 3-E.V.C. is quite indispensable. It is being demonstrated in use at Autoveyors' Showrooms daily.

British Patent 17703/22

Mfd.	Price.	Over-all Dimensions.
.0005	30/-	7 in. x 4 1/2 in. x 3 in.
*.001	40/-	7 in. x 4 1/2 in. x 4 in.

* Capacity essential for interference elimination.

All orders are being executed in strict rotation. To secure early delivery, place your order at once with any reputable dealer, or direct, with remittance, with—

AUTOVEYORS Ltd


(3-E.V.C. Dept.)

Radio Engineers and Contractors

84 VICTORIA STREET, LONDON, S.W. 1

Write for General Catalogue—

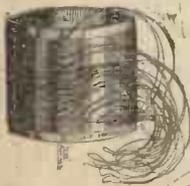the most comprehensive list in the Wireless Trade—3d. post free.



WOUND FORMERS, 3 1/2 x 4, with 10 single turns and 10 tappings of 10 turns	each	2 6
20 CONTACT STUDS with nuts	...	10
2 LAMINATED SWITCH ARMS	...	2 0
SET OF DETECTOR PARTS with Crystal	...	1 3
4 TERMINALS with nuts	...	6
8 x 6 1/2 EBONITE PANEL ready drilled	...	2 0

Postage 5

WITH A PAIR OF PHONES AND AERIAL, THIS MAKES ONE OF THE CHEAPEST & MOST EFFICIENT RECEIVING SETS FOR BROADCASTING 9 6

SCIENTIFIC BASKET COILS for all broadcasting, with circuits and calibrations per set, 2/6, postage 3d.

47 D.S.C. WIRE FOR REWINDING PHONES, per 1/2 oz. bobbin, 1/- each, postage 2d.


.001 .002 .003 FIXED CONDENSERS, 1/- each, postage 2d.

BROADCAST COILS per pair 1/3 postage 2d.

MARK 3 TERMINALS with nuts, 1/6 per doz.

SOMETHING NEW! .001 VARIABLE CONDENSER, highly finished, and very compact, total depth 1 in. ideal for base or panel mounting, guaranteed full capacity. A beautiful instrument ... each 10/6 Postage 3d.

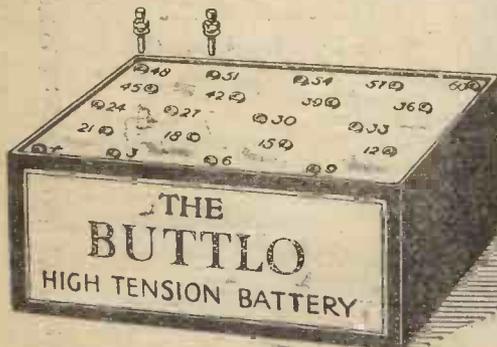SCIENTIFIC SUPPLY CO., 8 and 12, Newington Causeway, S.E.1. Phone: HOP 477.



15 volt	...	3/-
30 "	...	6/6
36 "	...	7/-
60 "	...	13/9
75 "	...	16/-
108 "	...	22/10

All sent postage free for CASH WITH ORDER

Send for fully illustrated List Post Free 4d.

H. D. BUTLER & CO., LTD.,
222, Gt. Dover Street, Borough, S.E.1.

Telephone No. : HOR. 3029.

(Over Barclay's Bank, opposite St. George's Church.)



Listen in with the Fellows

Handphone which has been specially designed for ladies. It has no headband to catch or tear the hair. Beautifully finished, very comfortable to use and wound to 4,000 ohms.

HANDPHONE

15/3 each.

Inclusive of all taxes.

Postage 1/-

He will use Fellows Headphones with two earpieces in light die cast non-ringing metal and wound to 4,000 ohms.

HEADPHONE

21/6 per pair.

Inclusive of all Taxes.

Postage 1/-

All Fellows Radio Instruments are British made throughout and guaranteed.

FELLOWS MAGNETO Co., Ltd.,
LONDON, N.W.10

Telephone :
WILLESDEN, 1560-1

Telegrams :
"QUIXMAG," PHONE, LONDON



For they are jolly good Fellows

CLUB DOINGS (continued from page 56)

Southampton and District Radio Society.

Hon. Sec.—P. SAWYER, 55, Waterloo Road, Southampton.

At the meeting of the above society held on June 14 Mr. Bateman gave a lecture on the "Fluelling Circuit," and successfully received broadcasting on an indoor aerial.

A very interesting discussion was opened by Dr. McDougall in connection with the persistent crackling disturbances which for some weeks have been seriously interfering with the reception of broad-

casting, and various theories were advanced as to the cause and origin of the annoyance.

A party of members recently paid a visit to the R.M.S. *Majestic*, by kind permission of the local manager of the White Star Line, and spent a very interesting and instructive time inspecting the wireless apparatus.

Leeds and District Amateur Wireless Society.

Hon. Sec.—D. E. PETTIGREW, 37, Mexborough Avenue, Chapeltown Road, Leeds.

At the 37th general meeting Mr. H. F. Yardley lectured on "Some Experiences with the Non-radiating Receivers." The lecturer described the difficulties that beset the manufacturer of radio receivers for broadcast traffic, and closely considered the stringent tests as conducted by the G.P.O. with regard to aerial excitation in autodyne receivers. He also spoke about the relative efficiencies of various intervalve H.F. couplings having magnetic regeneration. The need of tuned-anode coupling with magnetic retroaction included at that point was advocated. Mr. Yardley described a three-valve set using a H.F. valve coupled in the above manner to a cumulative rectifying valve, following upon which was a stage of L.F. amplification. The set was demonstrated using a 4-ft. frame and Western power equipment. The lecturer described many very interesting cases of good and bad reception in different parts of the country. As regards Leeds, it is now generally approved that the city is "in clover" as regards broadcast reception, there being very little jamming and no difficulty as regards picking up any of the B.B.C. stations on two- or three-valve sets.

Hall Green Radio Society.

Hon. Sec.—F. C. RUSHTON, Robin Hood Lane, Hall Green, Birmingham.

RECENTLY the society had a most instructive and interesting gathering, the occasion being the visit of Mr. F. H. Amis, engineer-in-charge of the Birmingham Broadcasting Station. Mr. Amis gave a most interesting account of the broadcasting station, outlining the apparatus in use there from the studio to the aerial, and explaining that less power was used when loud singing was transmitted as against the spoken voice. Great interest was manifested in the lecturer's explanation of the difficulties now experienced in broadcasting from Witton and the improvement which was likely to result when a removal could be effected to the centre of city.

Tottenham Wireless Society.

Hon. Sec.—S. J. GLYDE, 137, Winchelsea Road, Bruce Grove, Tottenham, N.17.
ON June 20 Mr. T. Vickery gave an interesting lecture on "Grid Leaks, Fixed Condensers, and Coils."

The lecturer demonstrated several types of leaks and tested their resistances on his megger. The method of building condensers was then shown, followed by detailed instruction in coil winding. Coils in all stages of completion were passed round, and the lecturer gave a practical demonstration of their manufacture. Mr. A. G. Tucker then gave the formula for calculating the inductance of coils.

On June 23 a party visited a ship station. The operator kindly explained his set—a ½ kw. rotary spark transmitter and crystal receiver. The members were greatly interested to hear the ranges over which communication had been established.

Radio Society of Highgate.

Hon. Sec.—J. F. STANLEY, 49, Cholmeley Park, Highgate, N.6.

ON June 22 a lecture entitled "Why Oscillatory Circuits Oscillate" was given by Mr. J. F. Stanley. By means of various mechanical analogies it was shown that the properties of inertia and elasticity are essential for the production of any kind of oscillatory or wave motion. The meaning of these two properties was carefully explained in a simple manner, and mathematics were studiously avoided. The properties of inductance and capacity were then explained, and it was shown that inductance corresponds to electrical inertia, while capacity corresponds to electrical elasticity. A combination of inductance and capacity is therefore capable of sustaining electrical oscillation, and the lecturer explained how the rate and duration of a free oscillation in such a circuit can be controlled and calculated.

Burnley and District Radio Society.

Hon. Sec.—W. H. THORNTON, 16, Bridge Street, Burnley.

THE above society held their usual fortnightly meeting on June 21, when the members heard a lecture on "The Care of Accumulators" by Mr. F. Drinkwater, of the Hart Accumulator Company.

The lecturer explained in detail the many and varied causes of trouble likely to be encountered when accumulators are carelessly handled. The many explanations were attentively received by those present.

South Dorset Radio Club.

Hon. Sec.—E. B. CARTWRIGHT, 18, Newberry Terrace, Weymouth.

THE first of a series of lectures on wireless and allied subjects drew a large attendance of members on June 5, when Capt. Hobs (2OY) discoursed on "The Practical Application of Theory."

The company subsequently "listened-in" on a fine two-valve set made by one of the members.

DO YOUR OWN SIGNWRITING

No Knowledge of Painting Required

Send for Transfer Letter Catalogues, Samples and Instructions, P.O. 1/-, to actual manufacturers.

Transfers of every description in stock and manufactured to special order.

The London Transfer Manufacturing Co.,
28-30, Paternoster Row, London, E.C.4.

Telegrams: DECALCO CENT LONDON. Telephone: CITY 9481

SPENCER'S STORES

4-5, MASON'S AVENUE, BASINGHALL STREET, LONDON, E.C.2
Telephone: LONDON WALL, 2292

Mounted Single Coil Holders, allow unlimited movement, 1/6 each. 1/9 post free.

Genuine Morse Keys, perfect balance, 3/- each. 3/6 post free.

Sole Agents for J. R. Crystal.

SEND FOR FREE LIST

The "PERFECT" HYDROMETER



A battery tester of precision and outstanding merit. The most reliable instrument of its kind on the market. No one who uses an accumulator should be without one; for it not only tells you when your battery is run down but shows you at a glance how much charge is left. Heavy rubber bulb and nozzle; Hydrometer scaled to indicate "full," "half" and "empty" (charge), as well as specific gravity of Electrolyte. The price is, for the first time, within the means of everyone.

3/9 each, complete, post free.



G.P.O. Detectors.


(Galvanometers.)

Three terminals, full coil and ½ shunt.

Perfect condition, **13/6** each. Post free.

(worth 50/-)

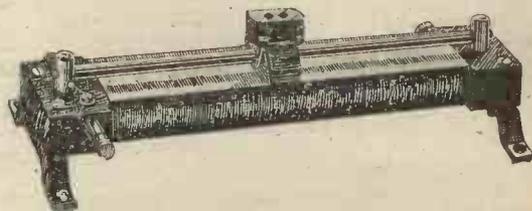Cloth cases for above, with leather shoulder strap, 1/- each.



POTENTIOMETERS

On slate bed (Army type)

Resistances 100, 500 and 600 ohms. Supplied on wooden base, if required, without extra charge.

Price for any resistance:

10/- each, post free

(worth 30/-)

INSULATORS, porcelain, green, glazed, egg shape.

ACCUMULATORS, 16-100 amp. hours.

WHOLESALE ONLY.

Guarantee.

Should you not be delighted with your purchase and return the goods within seven days we undertake to refund the money without any question.

SPECIAL TERMS TO DEALERS.

TRAVELLERS WANTED.

'Phone: Central 9182

The C. P. Co., Ltd.,
12/13, Miles Lane, Monument, LONDON, E.C.4.

EVERYTHING FOR WIRELESS

YOU WANT **BEST VALUE FOR MONEY**
 WE GIVE **BEST VALUE FOR LESS MONEY**

WE SELL SINGLE ARTICLES AT WHOLESALE PRICES TO THE PUBLIC.

- ERICSSON E.V. TYPE (Small Ear)
 Ebonite, Continental ... 15/6
- SIDPE HEADPHONES, 4,000 ohms,
 our price ... 13/6
- THOMSON.HOUSTON HEADPHONES
 (French) 4,000 ohms, our price ... 16/9
- FAMOUS N. & K. HEADPHONES,
 our price ... 15/-
- BRUNET HEADPHONES, 4,000 ohms,
 our price ... 17/6

This Week's "Snip"
BARBION HEADPHONES
 British make, Stamped B.B.C.
 4,000 ohms ... 14/6
 Every pair Guaranteed

Guarantee given with all Headphones
 CRYSTAL DETECTORS, best quality, each 1/-
 AERIAL WIRE, 7/22 bare copper, per
 100 ft. coil ... 1/11

Special Offer

VARIOMETERS, for General Broadcasting. To obtain tuning perfection with Crystal & Valve Sets 3/6



- SWITCH ARMS, best quality ... each 6d.
- GALVANISED PULLEYS, hook end, each 4d.
- HERTZITE CRYSTAL ... 6d., 9d. & 1/-
- TALITE CRYSTAL ... 6d., 9d. & 1/-
- TERMINALS, complete with nuts and washers ... 1d. each, 11d. doz.
- SOLID GOLD CAT'S WHISKERS, 2d. each 1/6 doz.
- SOLID SILVER CAT'S WHISKERS, 1d. each, 8d. doz.

MAKE YOUR OWN WIRELESS SETS
 All parts complete with oak base-board and sides ... each 8/6

All prices quoted net.

Please send sufficient stamps to cover postage.

CITY: (our only entrance) **JOHN BRAHAM WEST END:**
200, Bishopgate, E.C.2. (Next Door to "Dirty Dick's.")
 Telephone: London Wall 4094.
 NOTE: We have no connection with the Jewellers next door.


OPEN SATURDAY ALL DAY.

23, New Street, St. Martin's Lane, W.C.2.
 Telephone: Gerrard 6183.

AMATEUR CONSTRUCTORS!

We supply everything

This tuner has been tested and found very efficient as A.T.I or Anode Tuner for the new S.T.100 Circuit.

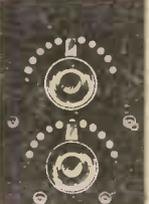Tapped inductances are far in advance of any other tuning, providing the tappings are correctly arranged. Our tuning Inductances are wound on specially impregnated 4" tubes with 26 s.w.g. double cotton-covered copper wire in the following ratio: 10 sections of 10 turns each, and 10 sections of 1 turn each. This winding will tune from 200 to 1,000 metres. Price 3/6.

Ebonite panels for the tapped inductances 7" x 5" x 3/16", drilled for 2 sets of 11 each contact studs and terminals, complete with 22 studs, 2 switch arms, complete, 2 phone, earth and aerial terminals and blue print of connections. Price 7/-. Polished Mahogany sloping front Cabinet for above panel. Price 6/-. The Coil and Panel make a most efficient tuner for Crystal or Valve.

H. F. Resistance Coupling, 50,000 to 100,000 ohms, cartridge type, with brass clips ... 1/6.

Phone: Clerkenwell 4454. **P. H. BOYS & CO.** 187, Goswell Rd, London, E.C.1. *Electrical and Wireless Engineers.*

To those interested in **CONTINENTAL HEADPHONES**

write to:—
RICHBORO M'F'G CO.,
 11-11a, RICHBOROUGH ROAD, CRICKLEWOOD, N.W.2.
 Phone: 5112 HAMPSTEAD.

DO YOU READ PRACTICAL BOOKS?

See Cassell's List of Technical, Practical and Money-saving Books. A postcard will ensure your receiving it.

CASSELL & Co., La Belle Sauvage, LONDON, E.C.4.

THAT BOOK YOU WANT ON WIRELESS OR ANY OTHER TECHNICAL SUBJECT

Foyles have it or will quickly obtain it. 1,000,000 Vols. (Second-hand and New) on Technical and every other conceivable subject in stock. Books sent on approval. Write for Catalogues (free) mentioning requirements. Books Purchased.

FOYLES, 121, Charing Cross Rd., London.

BEGINNER'S GUIDE TO WIRELESS

Explains in plain, everyday language, everything you wish to know about Wireless Telegraphy.

HOW TO ERECT, CONNECT, AND MAKE

the apparatus required, and full instructions for making coils, tuners, and complete valve and crystal sets. Instructions and diagrams for a two-valve receiver are alone worth four times cost of the book. 112 pages, price 1/- post free.

SAXON RADIO CO. (Dept 12) South Shore, BLACKPOOL

NO OTHER CRYSTAL CAN EQUAL OUR NEW AND GENUINE "HERTZITE"

FOR BROADCAST RECEPTION

SIMPLE TO USE NO BATTERY REQUIRED

Price with Detector, 4/6 post free

Sample Specimens, 1/6


Liberal Terms to the Trade and Prompt Delivery

RUSSELL & SHAW

38, Great James Street, Bedford Row, W.C.1.

The little loud speaker with the big voice!

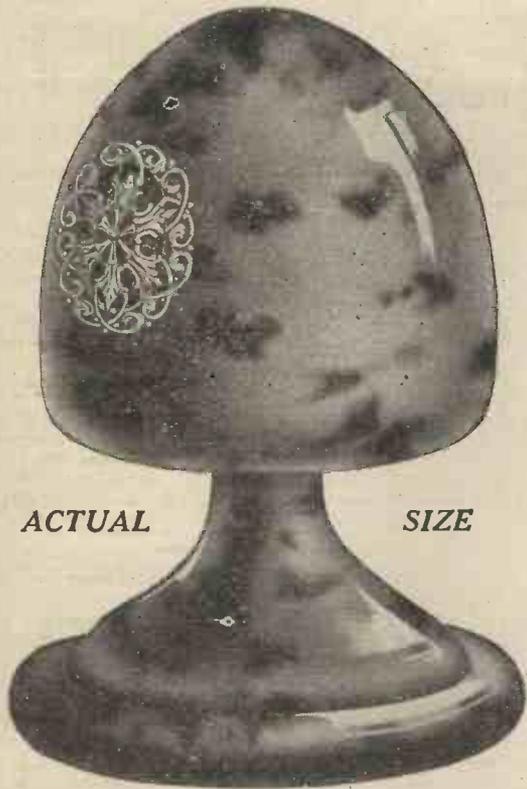NO LARGER THAN A WINEGLASS
BUT WONDERFUL TO HEAR



THIS wonderful little Loud Speaker surprises everyone. Standing only 4" high, and being in itself an ornament, resembling a small tortoiseshell vase, it floods the room with beautiful melody. No distortion. No vibratory noises. Sound is dispersed in all directions and spoken words are heard with wonderful clearness. Can be fitted to any receiving set in a few seconds. Simple and strongly made.

DEMONSTRATIONS DURING BROADCASTING
From 11.30 to 12.30 and 5.30 p.m. to 10 p.m.

The MAGNORA SUPER LOUD SPEAKER

POST 42/- FREE
ADJUSTABLE DIAPHRAGM

Complete with four feet of flex, and terminal leads. Obtainable in 3 types:—4,000 ohms, 2,000 ohms, and 120 ohms.

NOTE.—The Magnora is only for use with receiving sets which will operate an ordinary loud speaker. It cannot be used with Crystal Sets or Single Valve Sets. People who have heard it used with one detector and two amplifying valves have been amazed at the quality and volume of the tone.

C. HERING, Telephone Engineer
Washington House, 41, Conduit Street, Regent Street, W.

ELECTRADIX RADIOS

IMMEDIATE DELIVERY FROM OUR HUGE STOCKS

Everything from a Wavemeter to an Earth Clip. The best equipped City depot.

WAVEMETERS, all types, 100 to 10,000 metres
Govt. calibrated. Limited number, special prices

COME AND SEE US
9, COLONIAL AVENUE is first opening
on left in the Minories, near Aldgate Station,
Metropolitan Railway.

LESLIE DIXON & CO.,
9, COLONIAL AVENUE, MINORIES, E.1

.. ACCUMULATORS ..

BRAND NEW	
4 VOLTS, 40 A. H. (Ignition) -	18/-
4 " 60 " " -	21/6
6 " 40 " " -	27/-
6 " 60 " " -	32/3

CARRIAGE PAID
DUTTONS (Southport) Ltd.
Mariboro Road, SOUTHPORT

ADVERTISEMENT INSTRUCTIONS for "Amateur Wireless" are accepted up to first post on Friday morning for following week's issue, providing space is available.

PREPAID ADVERTISEMENTS.

Pickett's Cabinets. They're good value, 1s. 6d. each; highly polished. Write for lists, Manufacturers, Albion Road, Bexleyheath, S.E. 16r
Variometer Formers, specially hardened, 12 pairs, 6s. Special quotations larger quantities.—Pinn, 21, Amersham Road, S.E.14.
Agents Wanted.—Electricians, etc., to collect burnt-out wireless valves for repair. Good commission.—Apply Minson and Goman, 60, Churchfield Road, Acton, W.3. 11s
Frame Aerials.—Prov. patent; folds and unfolds in one second; wires always in position; made in oak, and packed in box, 21/- post free. Write for list.—Beresford, manufacturer, Stoke-on-Trent. 14s
Your Burnt-out Phones re-wound in 3 days; up to 1,000w., 5/-; 2,000w., 6/-; 4,000w., 7/6. Best work and quickest service.—Harrison, 289, Weston Street, Southwark, S.E.1. 18r
Variometers.—Highly efficient, 5/- each. Post paid.—Haskard, 53, Burton Street, Nottingham. 13s
Morse Instructor.—Teaches by ear, gives signals anywhere, any speed, repeats as desired, durable, cannot go wrong. Goes easily into pocket, not electrical. "Shipping World" says, "distinctly novel, should be invaluable." 7/6, post free.—The Standard Engineering Tools Co., Ltd., 25, Laurence Pountney Lane, London, E.C.4. 12s
Agent wanted for Patent Wireless Speciality. Sole selling rights in the various broadcasting centres throughout the country. Also agent to handle exporting rights.—The Harrison Manufacturing Co., 35, Paradise Street, Birmingham.
Radiocite Crystal.—Mr. Blake, A.M.I.E.E., writing in the Daily Mail, says: "It is wonderful stuff." "Sensitive practically all over." Obtainable at all Malone Radio Depots. Post free, 2/4.—West End Depot, 17, Piccadilly Arcade; City Depot, 7, Hart Street, Mark Lane, E.C.3. 16s
3-Valve Low-Frequency Amplifier for sale; mounted in cabinet and guaranteed perfect. Cost £16; will accept £8.—Woolmer, 34, Studley Rd., Luton, Beds. 18s
Great Wireless Discovery!—The New "Tut-Tut" Amplifying Detector. Always set; fool proof. The detector which requires no adjustment; obtains louder and clearer reception; post free, 3/—Patentees, D.W.S., 241, Park Rd., Aston, Birmingham. Agents wanted in all towns. 12s

YOU CAN "LISTEN IN"

WITHOUT ERECTING AN AERIAL

by fitting to your electric bell-push

The "BELRADIO" Adaptor

(Patent Appn. No. 10208)

Can be fixed instantly and used in any room where electric bells are fitted. No current used. No condenser required. Does not interfere with use of bells. Of special service to occupants of flats.

PRICE 2/6 EACH

WITH DIRECTIONS FOR USE


Obtainable from Wireless Dealers or Wholesale from

JOHN MACLENNAN & CO

115 NEWGATE ST., 166 INGRAM ST.,
LONDON, E.C.1. GLASGOW

"CATSEY" CRYSTAL DETECTOR

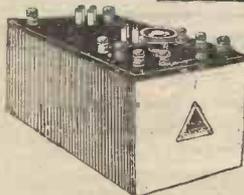Ever-set and ready. Smallest, Loudest, Latest. Complete with holder 1/6 Post Free. APAIL, 37, Red Lion St., LONDON, W.C.2. AGENTS WANTED



ADD H.F. TO YOUR SET and bring in the distant stations. H.F. is the most efficient form of amplification. It will give you power, range, and selectivity far beyond the present capacity of your set. And the Radiax System enables you to use safe Reactance. Radiax H.F. Unit in parts 18/6, complete £6.6. Co. denser for tuning anode parts 11/6, complete £14.6. H.F. Transformers or anode coils from 5/6. Variable Reactance coils 10/-. Any set needing alteration will be altered at 1/6. H.F. terminals put in by us at a cost of 10/6. Reaction terminals also required 13/6.



WE SATISFY YOU

Send 3d. stamps for our Catalogue of long and short range sets, Unit Systems and all components.
RADIAX LTD.,
21, Radio House, Percy St., Tottenham Ct. Rd., London, W.1. Tel.: Museum 409.

Ask "A.W." for.....
.....List of Technical Books

Complete Wireless Sets Supplied on Deferred Payments to suit your own pocket

We have completed the organization of our Hire Purchase Department and it is now possible for the public to obtain complete Wireless Sets without unduly disturbing capital.

Our terms are of the simplest form. For instance, should you decide to install a

BURNDEPT "ETHOPHONE V"

(one of the finest instruments on the market), it is only necessary to

PAY £10 11s. 0d. DOWN

and the balance at the rate of

£2 12s. 9d. PER MONTH

This is arrived at as follows:—

PRICE OF BURNDEPT "ETHOPHONE V"

in oak cabinet, including 4 Marconi Osram Valves, High Tension Battery and full instructions **£39 18 0**

ADD 5% interest **£ 2 0 0**

„ Insurance **6 0**

£42 4 0

FIRST PAYMENT OF $\frac{1}{3}$ COST **£10 11 0**

BALANCE **£31 13 0**

Payable in 12 monthly instalments of **£2 12s. 9d.**

All sets and accessories mentioned in our Catalogue can be purchased under this simple arrangement, providing the total value is not less than £25.

WRITE TO US, STATING YOUR REQUIREMENTS OR FOR FURTHER INFORMATION.

Have YOU had your Free Accumulator?

IF NOT—


DO IT NOW!

All that is necessary is to make up an order of £5 or over from any of the items advertised below and we will include a

6 Volt, 40 Amp.

FULLER Block Type ACCUMULATOR

VALUE - **£2 8s. 9d.**

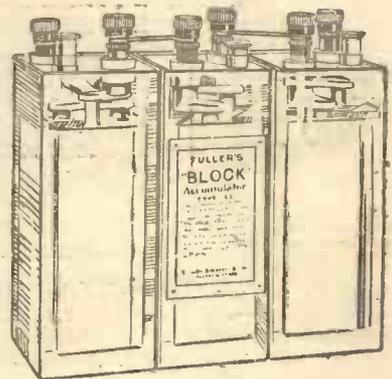

SEND FOR OUR ILLUSTRATED CATALOGUE

Select Your Goods from the Following List:

ACCUMULATORS: (For prices see our Catalogue, post free on application).

HELLESEN BATTERIES: 25 volt, 4/-; 36 volt, 8/6; 60 volt, 14/-.

McCLELLAND VARIOMETERS, 27/6 each.

COIL HOLDERS: The finest quality on the market, 25/- each.

"VIOLINA" LOUD-SPEAKERS: £5 5s. each.

VARIABLE GRID LEAK: "The Microgrid," 4/6 each.

VARIABLE CONDENSERS:

Best quality .0005 mfd. 18/6. .001 mfd. 24/6

Second quality .0005 " 14/- .001 " 17/6

Third quality .0005 " 8/- .001 " 12/6

RHEOSTATS: Circular pattern, 4/- each.

"Microswitch," 6/6 "

TRANSFORMERS: Intervalve and Telephone (Ratio 5-1).

In Iron cases. The most efficient instrument on the market, 25/- each.

Also the following items from our Catalogue:

UNIT SYSTEM. SETS OF PARTS, VALVE HOLDERS, AERIAL WIRE, LEAD-IN TUBES, TERMINALS.

THE CITY ACCUMULATOR CO.

79, MARK LANE, LONDON, E.C.3.

Phone: AVENUE 1316

10, RUPERT STREET, COVENTRY STREET, W.1.

Phone: GERRARD 3063

Agents (where the free Accumulators may also be obtained):

LANCASHIRE & CHESHIRE:

Henry Hollingdrake & Son, Ltd., Princes Street, Stockport.

S. WALES: South Wales Wireless Installation Co., Ltd., 18, West Bute Street, Cardiff, and at Cambrian Road, Newport.

YORKSHIRE (West Riding): Messrs. H. Wadsworth Sellers & Co., Standard Bldgs., Leeds.

GLOUCESTERSHIRE, SOMERSET & WILTS:

Bristol Wireless Co., 52, Cotham Hill, Bristol.

LEICESTERSHIRE:

Walter Rowe, Ltd., Eldon House, 97, London Road, Leicester.


FRANCE: 33, Rue d'Hautville, Paris.

AUSTRALIA: 4, Teakle Street, Summer Hill, Sydney.

IMPORTANT NOTICE.—Our Showrooms and Works will be closed during the whole of August Bank Holiday Week, August 6th to 11th inclusive.

Links in a chain— Lissen Components that Matter

RADIO FREQUENCY

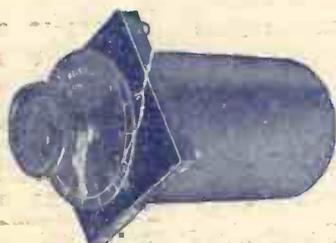

1st Stage—Use the LISSEN REGENERATIVE-REACTANCE (P. PATENT)—CUTS OUT 2 LO and brings in the other Broadcasting and Continental Stations—SO SENSITIVE that under many conditions aerial and earth connections may be dispensed with. Range 150 to 4,000 metres—REGENERATION OVER THE WHOLE RANGE WITHOUT A BREAK—tune with a LISSEN VERNIER CONDENSER (designed for fine tuning in H.F. circuits, barely 1" diameter, price 12/6). LISSEN ONE HOLE FIXING—no switch to connect—no soldering—

Price £2 12s. 6d. complete.

1st or 2nd Stage—LISSEN REACTANCE (P. PATENT)—amplifies the loudest of signals to a high degree—adds great range and power—where aerial reaction is employed, tune with a Lissen Vernier—it is entirely self-tuned if aerial reaction is not used. Range, 150 to 600 metres. 27/6. 150 to 10,000 metres, 32/6. No switch to connect—no complications—LISSEN ONE HOLE FIXING.



INDUCTANCE

LISSEN TUNER—Its efficiency is in the unique LISSEN multi-winding—its convenience is in the design—its price makes it undesirable to wind your own—dead end loss eliminated—11-point switch already mounted and connected—no taps to solder—no switch to connect—panel or table mounting—also makes a very highly efficient ANODE COIL—LISSEN ONE HOLE FIXING—range 150 to 4,000 metres when used with a .0005 condenser (preferably use a LISSEN MICA VARIABLE CONDENSER, price 17/6)—combines greatest inductance with lowest H.F. resistance and least distributed capacity—length 4", diameter 4"—goes compactly into any set—

Price 22/6

CAPACITY

LISSEN MICA VARIABLE CONDENSER—maximum capacity .0006. Losses in condensers taking place through faulty materials or BAD WORKMANSHIP reduce signal strength—a condenser increases in efficiency as these losses are reduced. THE LISSEN MICA VARIABLE CONDENSER is made so that these losses shall be the minimum possible. Panel or table mounting by slight ingenious alteration—tuning over 360 degrees of scale—small changes of capacity for a given moment of the scale on the lower readings—diameter 3½", depth 1"—LISSEN ONE HOLE FIXING ...

Price 17/6



CRITICAL VALVE CONTROL

LISSENSTAT—the new device for perfect filament control—utilises the critical tuning characteristics of the Detector Valve—each H.F. Valve and the Detector Valve should have LISSENSTAT control—gives greatly improved control of fine detection, so absolutely essential in tuning-in on long distance reception. The ordinary rheostat sets up noises in your detector valve without your knowing it. The LISSENSTAT gives smooth, finely graduated, noiseless control. Permits getting on the very spot necessary for perfect reception. Saves your valves and its own cost many times over, because with the LISSENSTAT it is impossible suddenly to throw a heavy current on to the delicate valve filament. It has an off position. LISSEN ONE HOLE FIXING

Price 7/6

Any Good Radio Dealer will show you these—if he cannot, take no substitute. Send direct to Factory. Post Free and Goods will be immediately despatched.

DEALERS.—Please order a few days ahead—orders executed direct, and charged for through any factor whose name and address is given. Alternatively, ask your factor or send direct.

AUDIO FREQUENCY



LISSEN TYPE T1 L.F. TRANSFORMER—MAKES A WHISPER LOUD—the only transformer that has a coil which matches average valve impedance—should be used in every good receiver immediately after the detector valve—every turn of its expensive coil is wound by patent process.

Price 30/-

LISSEN TYPE T2 TRANSFORMER—where LISSEN Type T1 is not used throughout use the LISSEN Type T2—it is not essential that the primary of transformers for 2nd and 3rd stages of L.F. should have such high impedance value as is required of the transformer following the detector valve ...

Price 25/-

SHORTLY TO BE INTRODUCED

LISSENAGON (P. Patent) air-wound, super efficient, plug-in coil—see the air space through it.

LISSEN APPARATUS—
Well Thought Out, Then Well Made.

LISSEN COMPANY

16-20 Woodger Road, Goldhawk Road
Shepherd's Bush, London, W.12

Phone: 1072 Hammersmith

N.B.—Close to Goldhawk Road (Met.) Station, Shepherd's Bush (Central London), or Hammersmith Tube. Buses 11 and 32.