

THE FRAME AERIAL AND SELECTIVITY

Amateur Wireless

And Electrics

Every Thursday 3^d

Vol. XII. No. 300

Saturday, March 10, 1928



COIL THREE

THREE UNIQUE FEATURES

250-2000 METRES

NO COIL CHANGING

DIRECT PICK-UP ELIMINATED

TWO of a kind



—each supreme in
it's class. Designed to
meet varying needs,
these two Loud
Speakers are iden-
tical in the sheer
value-for-money
they represent.
A factor which
distinguishes every
product bearing the
name—



Brown

Adv. S. G. Brown, Ltd., Western Avenue, North Acton, London. W.3.

CA 1923



Prize Winning LOW LOSS FORMER

Be sure to specify Becol original Low
Loss Former used in sets that have taken
1st, 2nd, 3rd and 4th prizes and gold
medal. Packed in carton 3", 4", 6"
lengths up to 36" lengths.

THE LATEST
Apply for particulars of 4 and
6 new design contact formers
with bases.

BECOL

Registered Trade Mark.


New Standard sizes
in 3 finishes, guar-
anteed panels made
by the Ebonite
Experts.



THE BRITISH EBONITE COMPANY, LTD.
HANWELL, LONDON, W.7.

Advertisers Appreciate Mention of "A.W." with Your Order

PERFORMANCE

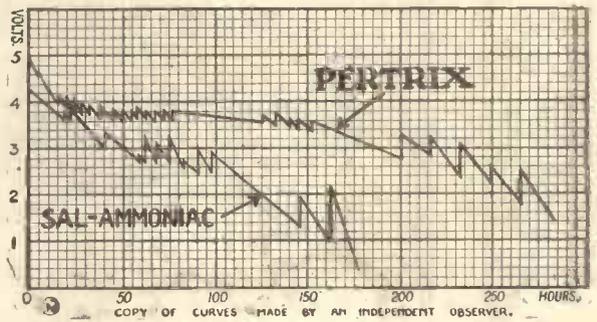

THE CURVE SHOWS THE DIFFERENCE BETWEEN A "PERTRIX"
PATENT LONG LIFE DRY BATTERY AND A GOOD QUALITY
SAL-AMMONIAC BATTERY. BOTH BATTERIES WERE OF THE
SAME DIMENSIONS, AND BOTH WERE DISCHARGED WITH A
CURRENT OF 5-6 MILLIAMPERES UNDER AVERAGE BROAD-
CASTING CONDITIONS, I.E. 5 TO 6 HOURS EVERY NIGHT
WITH OCCASIONAL LONGER PERIODS OF DISCHARGE. THE
VOLTAGE DROP ON EACH BATTERY, AFTER ONE AMPERE
HOUR HAD BEEN TAKEN OUT, WAS FOUND TO BE
SAL-AMMONIAC, 77.7% VOLTAGE DROP.
"PERTRIX," ONLY 32% VOLTAGE DROP!

DOES NOT THIS PROVE THAT OUR CLAIM THAT THE

PERTRIX PATENT

LONG LIFE DRY BATTERY IS "THE BATTERY WITHOUT
A RIVAL" IS JUSTIFIABLE?

A.F.A. ACCUMULATORS LTD. (Pertrix Dept.)
120 TOTTENHAM COURT ROAD, W.1

MARCONIPHONE

YOU GET MORE FROM


TRANSFORMERS AND CHOKES

In components, as in receivers, leadership falls naturally to Marconiphone. It is the vastness of this organisation, the continued research, that gives to Marconiphone components their technical advantage—and to you, finer, more finished results than you ever enjoyed before.


The Marconiphone "Ideal" Transformer is, to all intents and purposes, distortionless throughout the musical range. It is larger and heavier than any other transformer on account of the quantity of highest grade material used in its construction. Rigorously tested at every stage of manufacture, every "Ideal" is guaranteed to conform to the individual curve supplied with each instrument.

Supplied in four ratios, 2.7 to 1, 4 to 1, 6 to 1, 8 to 1, 25/- each.

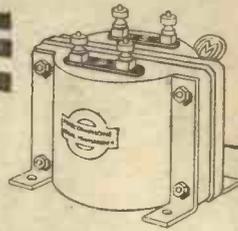
THE MARCONIPHONE COMPANY, LIMITED, (Dept. P), 210-212 Tottenham Court Road, London, W.1.



Marconiphone "Ideal" L.F. Transformer.

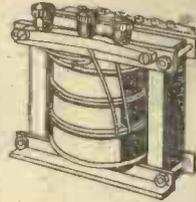


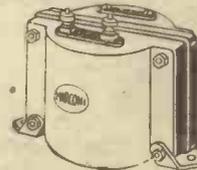Marconiphone Power Transformers. Model "A" for use with the U.S. rectifying valve, 35/-. Models "C" and "D" for use with Marconi K.L.X Valves, providing an "all-mains drive," 37/6.



Marconiphone "Ideal" L.F. Choke. Design similar to "Ideal" Transformer. Suitable for choke-coupling, H.T. Supply Unit and filter circuit, 21/-.

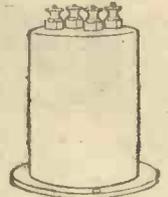Marconiphone "Ideal" Supersonic Transformer. Provides a happy blend of selectivity and good quality amplification. Designed for intermediate frequency stages of Super-Hi receivers, and is tuned to 6,500 metres, 20/-.



Marconiphone H.F. Choke. Inductance 100,000 microhenries resistance 700 ohms. Very efficient on wave-lengths up to 4,000 metres. 10/6.

There is a complete range of Marconiphone Transformers and Chokes for every purpose. Send now mentioning "Amateur Wireless" for publication No. 453.



BS75.

The CHLORIDE ELECTRIC STORAGE Co., Ltd.,

have such keen appreciation of the efficiency and reliability of

CLIX FITMENTS

THAT THEY RECOMMEND CLIX PARALLEL PLUGS EXCLUSIVELY FOR USE WITH THEIR FAMOUS EXIDE BATTERIES

Look for the CLIX COUNTER SHOWCASE at your dealers.

It contains the famous CLIX fitments—everything you need to ensure simple, safe connection. You can equip your set with CLIX for a few pence and save the possibility of endless trouble through faulty contacts.

LECTRO LINX, LTD., 254 Vauxhall Bridge Road, S.W.1.

Telegrams: "Trolinx, Churlon."

Telephone: Victoria 5120.


THE CARBORUNDUM R.C.C. UNIT

The Carborundum R.C.C. Unit gives remarkably pure reproduction when used in the recently developed popular circuits embodying R.C. Coupling.

Before building your Set, send for full details of this wonderful R.C.C. Unit, which is now recognised as the only perfect form of R.C. Coupling.

WRITE FOR FREE BOOK OF WIRING DIAGRAMS

8/6

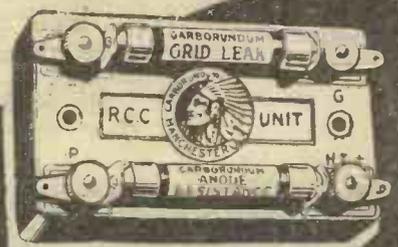


THE CARBORUNDUM CO. LTD. MANCHESTER.

FERRANTI

If you have direct current Supply in your home
DISPENSE WITH H.T. BATTERIES
 and build an Eliminator with Ferranti Components

DIAGRAM :—

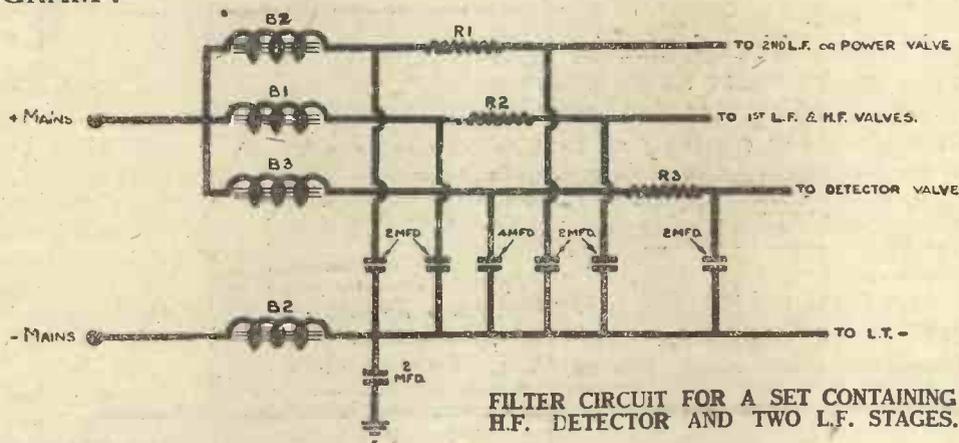

FILTER CIRCUIT FOR A SET CONTAINING H.F. DETECTOR AND TWO L.F. STAGES.

PARTS REQUIRED

	PRICE
1 Choke Type B1 : : : :	£1 1 0
2 Chokes Type B2 : : @ 21/- :	2 2 0
1 Choke Type B3 : : : :	14 0
8 Condensers 2 mfd each Type C1 @ 8/-	3 4 0
*3 Resistances : : : @ 5/-	15 0
1 Baseboard } 7 Terminals } : : : say	5 0
Wire	
	£8 1 0

* Prices of Resistances vary between 5/- and 10/- each according to value

DELIVERY FROM STOCK

An eliminator built to this specification is free from hum and motor-boating, and when used on a 230 volts supply will give an output of 200 volts 100 milliamps. If further information is required, such as the values of the resistances, this will be furnished on application, stating the valves used and the mains voltage.

FERRANTI LTD. HOLLINWOOD LANCASHIRE

Mention of "Amateur Wireless" to Advertisers will Ensure Prompt Attention

Amateur Wireless

and Electricians

The Leading Radio Weekly for the Constructor, Listener
and Experimenter

Vol. XII. No. 300

Edited by BERNARD E. JONES
Technical Editor: J. H. REYNER, B.Sc.(Hons.), A.M.I.E.E.

MARCH 10, 1928

The "Q'-Coil Three"—"The Night Fighters"—"Approved" Dealers, Please!—
Wireless in Spain—Who is it?—The "School Five"

The "Q'-Coil Three"

THE first "Q"-coil receiver which has been built is fully described and illustrated in this issue. Readers of Mr. Reyner's article on the "Q"-coil will turn to page 388 with interest. The receiver incorporates just an ordinary straightforward three-valve circuit, consisting of three stages—detector and two L.F.—these being R.C. and transformer coupled. The result is an efficient and selective loud-speaker receiver, which requires no coil changing whatever!



Wireless has played quite a prominent part in the winter sports at St. Moritz. Our photograph shows the Blatthaller giant loud-speaker "installed" on a structure on a snow-covered slope.

"The Night Fighters"

DID you like Cecil Lewis's *The Pursuit*, which we heard some time ago? It seemed to be well received, for the B.B.C. received over a thousand letters—mostly appreciative—after the broadcast. We are being given "more" in *The Night Fighters*, a second play in the new "technique" by Mr. Lewis. It will be broadcast from 5GB on March 24 and from 2LO and other stations two days later.

"Approved" Dealers, Please!

THE Radio Society of Great Britain and the Wireless League have jointly declared war on the "shady" wireless dealer and "shoddy" set repairer. They have instituted an "approval" board, which will approve or disapprove of dealers. Approved dealers will receive a sign to that effect. Those not approved and those who do not submit themselves for approval will be, presumably, boycotted. If they succeed the Society and the League will have done us all a service.

Wireless in Spain

IN Spain a company known as Transradio Espanola has been formed with a subscribed capital of 4 million pesetas. As it is really a

collaboration of the three big concerns, Marconi, Telefunken, and the Spanish Radio-Elctrica—which holds the patents of the French company Compagnie Generale de Telegraphie Sans Fil—Spanish broadcasting should soon brighten up.

Who Is It?

WITH reference to our last week's paragraph on the subject of who is it who decides who shall and who shall not broadcast, it was interesting to hear of a Parliamentary discussion on the point. It was raised by the case of an osteopath who was not allowed to speak. The P.M.G. said he was not officially aware of the

matter and did not propose to interfere with the discretion of the Corporation. Mr. Macquisten, who raised the point, said: "I wish you to interfere with their indiscretion!"

A Continental Squabble

THERE is trouble brewing between the two Bordeaux stations, the cause being that the authorities of the official station want the old Radio Sud-Ouest closed down. While this station was undergoing repairs recently the Bordeaux Mayor ordered the electric current supply to be cut off. The director of the Radio Sud-Ouest is

threatening to take the case into the courts.

Talking to China

GERMANY is now in regular communication with China by means of the Nauen AGW and AGJ stations. AGW works with a power of 400 kilowatts on 18,000 metres, and is used for the night traffic only. AGJ, the 15 kw. 40-metre transmitter, being used during daylight.

The "School Five"

DESIGNED to meet the needs of schools, the "School Five," to be described in our next issue, embodies all the latest developments, such as a screened-grid valve, astatic tuning coils, and a powerful resistance-capacity coupled L.F. amplifier. Apart from its special appeal to schools, we feel sure that many "old boys" will find the "School Five" of great interest. A push-pull L.F. amplifier, giving great volume without over-loading, using ordinary L.F. or small power valves, will interest those who have only a moderate H.T. supply available.

PRINCIPAL CONTENTS

Current Topics ..	371	Practical Odds and Ends	384
Television—The Problem of the Distant Image	372	The Frame Aerial and Selectivity	385
The "2-Wave-2"	373	Switch On or Off from Anywhere	386
Harnessing Lightning to Break up Atoms ..	375	Without Fear or Favour	387
For the Newcomer ..	376	The "Q'-Coil Three"	388
On Your Wavelength ..	381	Letters to the Editor ..	392
An Easily-made Cone Loud-speaker ..	383	"A.W." Tests of Apparatus	394
		Our Information Bureau	396

Pages 385-392 are missing.

TELEVISION—The Problem of the Distant Image


By
T. THORNE BAKER
F.R.P.S., F.INST.P.

A TELEVISION transmitter breaks up the image of the person or subject or screen into thousands of small parts. Each part is of a different brightness, according as it comes on the skin, or hair, or dark coat or pupil of the eye, and so on. The photo-electric cell, which "sees" these different amounts of brightness, converts them into electricity, in which form they can be transmitted over lines, or by wireless.

The first problem "at the other end" is to take up this rapid string of electric signals—amplitude variations or frequency changes, whatever they may be—and to turn them back into light. We might well imagine two cameras, one in Berlin focused upon a building (the image of which is thrown upon the focusing screen) and the other in London, set up, but with no lens—only an electric wire running from it to the camera in Berlin; the focusing screen of the camera in London has the image thrown upon it of the building standing before the first camera.

Except that the focusing screen is dispensed with, and that the eye sees the image without it, this wonderful feat of distance vision has, as we know, been accomplished by Baird across the Atlantic, and by Ives and Alexanderson over considerable distances on land in America.

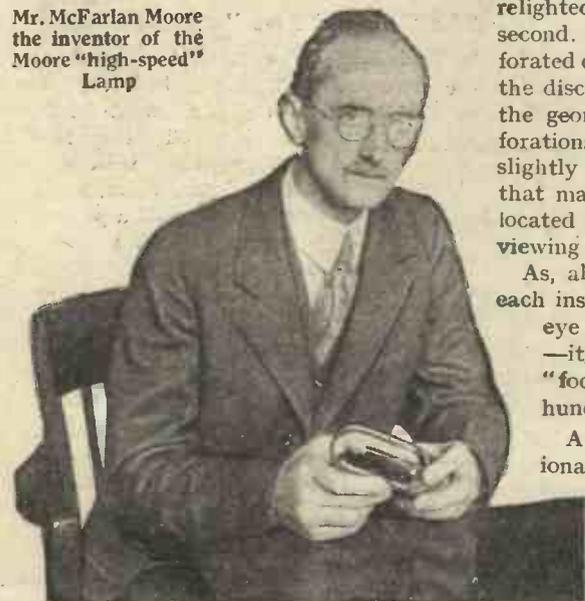Mr. McFarlan Moore
the inventor of the
Moore "high-speed"
Lamp



Electricity to Light

The reconversion of the signals transmitted from the sending to the receiving instrument into light to form the replica image may be likened to the process so often seen in electric street signs. We, perhaps, watch one lamp after another, automatically switched on, following some pre-arranged pattern, until we see a complete image—possibly a face, a motor-car, a bottle pouring wine into a glass, and so on. Indeed, the day will come when actual television scenes are broadcast in the streets by these luminous signs controlled from distant television transmitters—just as cinematograph pictures are projected in busy thoroughfares to-day.

High Speed

Baird uses one lamp only, which is relighted, as it were, thousands of times a second. The eye watches it through a perforated disc, which is revolving in step with the disc of the transmitter. By means of the geometrical arrangement of the perforations one appears to see the lamp in a slightly different position each instant, so that many times a second it seems to be located at every single spot on a given viewing area.

As, also, its brightness is controlled at each instant by the incoming signals, the eye sees a living luminous image—it watches the image on the "focusing" screen of that other camera hundreds of miles away.

A lecture experiment I show occasionally to demonstrate the television cycle is seen in the diagram. A photo-electric cell (on the left) is coupled up in series with a suitable neon lamp and a

battery of 230 to 270 volts. As soon as the light of an electric lamp (E) is shone on the cell (K) the neon lamp (N) glows. If the lamp is brought nearer to, or made to recede from, the cell, so the light emitted by the neon lamp increases or diminishes.

Dr. Alexanderson, of the General Electric Company in America, uses what amounts to a mosaic of tiny lamps, and Dr. Ives has employed one large rectangular lamp, 2 ft. by 2 ft. 6 in., which can be illuminated at any instant in any one of 2,500 different local patches or small areas. The latter can be viewed by a theatre full of people.

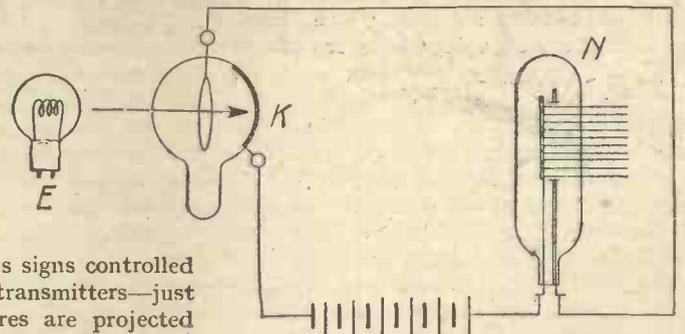


Diagram showing a Television Receiving Cycle

To describe how the complex type of viewing apparatus is operated, however, one must understand something of the most difficult part (mechanically) of the television problem, viz., synchronising the moving parts of the sending and receiving apparatus. The methods in present use will form the subject of the next article.

Readers who may have heard the weekly relays of operatic performances carried out by Radio Toulouse (France) from the local Theatre de la Capitole, may be interested to know that this station is the only European station which effects these transmissions by wireless link. As the French Posts and Telegraph Authorities have refused to place a landline at the disposal of the studio, Radio Toulouse has installed a short-wave equipment in the theatre; the signals are picked up by the 3-kilowatt transmitter at the Villa Schmidt and rebroadcast on 391 metres in the usual manner.

The 2-WAVE 2

Designed and Built by the "A.W." Technical Staff

"LONDON and Daventry calling," is a phrase which has an especial significance to the designer of wireless receivers. In that seemingly simple statement lies a difficulty peculiar to European listeners. For, whereas London, and for that matter, any other main B.B.C. station, transmits

In this up-to-date little two-valver, the change from the short wavelength band to the long waves, is simply a matter of pressing the small auxiliary knob attached to the reaction dial. There is no need to open the lid of the cabinet, delve into the interior and, at the risk of damaging the wiring of the set, perform the somewhat tedious operation of changing tuning coils.

In fact, we can truthfully say that the "2-Wave 2" is a set for the "ordinary listener," and as such, it has received very careful consideration in design to ensure the greatest possible simplicity of operation and maintenance.

The general lines on which the "2-Wave 2" has been assembled, can be gathered from an examination of the illustrations and reduced reproduction of the special full-size blueprint (which is available, price 1s., from this office). There are three panel controls, consisting of: (1) the tuning dial on the right; (2) the reaction coil dial and wave-changing knob on the left; and (3) the master rheostat in the centre controlling the filament supply to both valves.


At the back of the receiver are two small ebonite terminal panels, one for the loud-speaker and the other for the aerial and earth wires. An ingenious battery plug is situated between the two terminal strips, and this

AMATEUR WIRELESS receivers in the past. Briefly, the circuit is a detector with magnetic reaction, followed by one stage of transformer-coupled L.F. amplification. Upon analysis, we find the following points of interest. The tuning coil can be arranged to give a variable degree of selectivity, due to the provision of two aerial "taps" on the Wearite tuner. No difficulty should be encountered in separating the local station from, say, Daventry 5GB with one or other of these taps.

A .0005-microfarad variable condenser, in conjunction with this tuner, covers the complete broadcast band of 300 to 500 metres and allows a considerable wavelength range in the neighbourhood of 1,600 metres.

Sensitive valve rectification is provided for by the inclusion of a .0003-microfarad grid condenser and 2-megohm grid leak. This grid leak is connected between the grid of the detector valve and L.T. +.

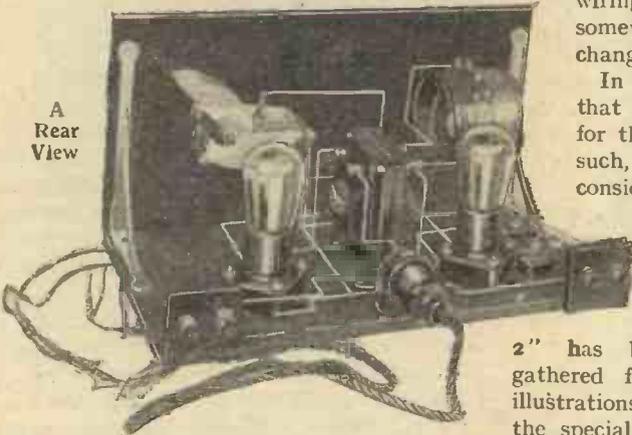
Simplification of construction seemed to us to warrant the use of magnetic reaction, especially so, since this system is readily




A Rear View

on a short wavelength, Daventry 5XX has, owing to the wide circle of listeners catered for, to transmit on the comparatively long wavelength of 1,600 metres.

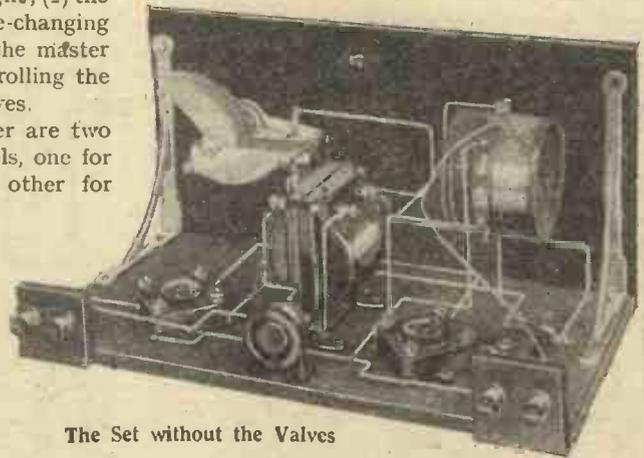The majority of experienced wireless amateurs will say that to overcome the difficulty of these widely separated wavelengths, it is only necessary to change the coils. But what of the non-technical members of the family who neither know, nor possibly care, anything about tuning coils and their relation to wavelengths? It is for these listeners that the "2-Wave 2" should have a special appeal.



The Set without the Valves

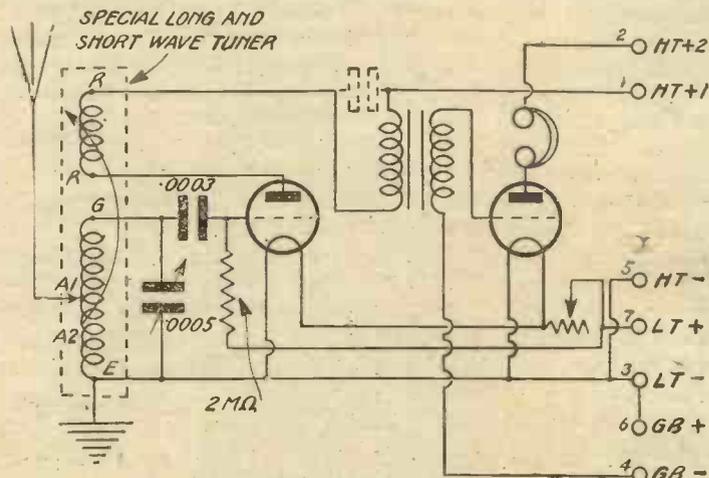

The Circuit Diagram

considerably simplifies the connecting up of the various battery leads.


From a theoretical standpoint the "2-Wave 2" offers no startling novelty, although the simple circuit used has proved its worth in many

available with the Wearite reaction tuner. Because of this form of reaction, it is necessary to connect a small condenser across the primary of the L.F. transformer in order to by-pass the H.F. currents flowing through the reaction coil. If the L.F. transformer specified is used by the reader, there is no need for a separate condenser, because a suitable capacity has been incorporated inside the iron casing, by the makers. If an alternative make of transformer is incorporated, on no account omit

THE "2-WAVE 2" (Continued from preceding page)

to shunt the primary winding with a .0005-microfarad condenser, otherwise erratic reaction effects will follow.

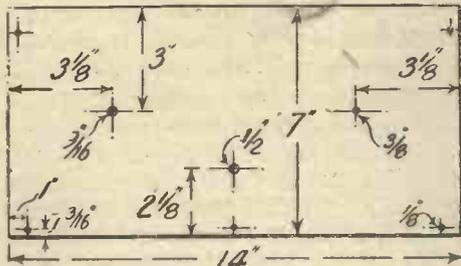In a two-valve arrangement, where the maximum results possible are required, it is important that the second valve be given an adequate H.T. supply. Thus two H.T. plus tapings are indicated in the circuit



Details of Panel

diagram, H.T.+1 giving a comparatively low H.T. to the detector valve, say 60 volts, and H.T.+2, at least 100 volts to the L.F. amplifying valve. The master rheostat in the L.T.+ lead effectively controls the filament current of both valves. Grid

To build this receiver the following components should be obtained:—

Ebonite or bakelite panel, 14 in. by 7 in. by 1/4 in. (Becol, Raymond, Ebonart, Pertinax).

.0005-microfarad variable condenser (Utility, Igranic, Burndept).

W.G. tuner (Wearite).

Panel - mounting rheostat (Benjamin, Igranic, Lissen).

.0003-microfarad fixed condenser with series clip (Dubilier, Igranic, T.C.C., Graham-Farish, Lissen).

2-megohm grid leak (Dubilier, Igranic, Graham-Farish, Lissen).

Two valve-holders (Benjamin, Wearite, Lissen).

Low-frequency transformer (Ferranti, type A.F.3, R.I. and Varley, Lissen).

Two pieces of ebonite or bakelite, 2 in. by 2 in. by 1/4 in. (Becol, Ebonart, Pertinax).

Four terminals, marked: Aerial, Earth, L.S.—, L.S.+ (Belling-Lee, Eelex, Igranic).

Wiring

In a simple receiver, such as the "2-wave 2," wiring is a very straight forward business, especially so if the point-to-point connections shown on the blueprint are carefully followed. Once again we feel it



The complete "2-Wave 2"


necessary to warn readers of the special insulated clip on the Dubilier grid condenser which, if ignored, has the effect of "shorting" the accumulator through the tuning coil. The L.T.+ connection of the grid leak is, of course, insulated from the tuning-coil side of the grid condenser by means of this clip which, incidentally, obviates the necessity of a separate grid leak holder. The grid side of the grid condenser is, of course, common to the grid side of the grid leak.

Three of the soldering tags on the battery plug are "shorted" by means of a single length of wire, namely the H.T.—, L.T.— and G.B.+ 3, 5 and 6. The other four soldering tags are soldered to wires leading to the various components. The battery ends of the seven-way battery cord terminate in small aluminium tags engraved with the battery abbreviation, say G.B.—, and underneath is the corresponding number, in this case number 4. Thus the grid-bias terminal of the L.F. transformer is wired to soldering tag No. 4 and, of course, the other end of the cable marked G.B.— is taken to the grid-bias battery. The numbers on the soldering tags are very clearly indicated, not only on the plug itself, but also in the draughtsman's representation shown by the blueprint.

The aerial terminal has soldered to it a suitable length of rubber-covered flex, terminating in a small spade tag, the latter being clamped under terminal A1 or A2, on the Wearite tuner.

Before inserting the valves and connecting up the batteries, loud-speaker and so on, it is a wise plan to compare the connections made in the receiver with those shown in the blueprint. Then suitable valves, such as are advised in our special

(Continued on page 404)

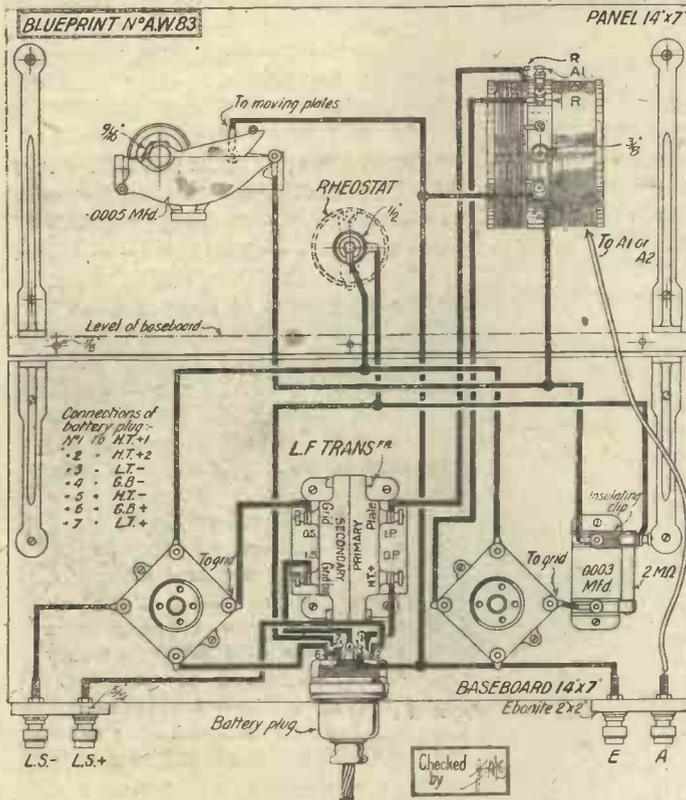

The Wiring Diagram, Blueprint available, price 1/-

bias for the L.F. valve is also provided for. It should be noted that the seven battery terminals indicated in the circuit diagram and numbered, are actually soldering tags on the special battery plug. As the connections on this plug are numbered, as shown in the blueprint, there is no possibility of a wrong connection being made.

fitting is simplified.

The baseboard components, that is, the two valve-holders, combined grid-leak and condenser and L.F. transformer are then disposed as indicated. The assembly is completed by the fitting of the two terminal strips and baseboard section of the battery plug.

HARNESSING LIGHTNING


By DR. ALFRED GRADENWITZ

TO BREAK UP ATOMS

THOSE tourists who last summer happened to visit Lugano and thence to ascend to Monte Generoso, that beautiful mountain peak towering to a height of 1,800 metres (about 5,950 ft.) and dominating the whole of the Lombardian Plain, there witnessed a strange spectacle. Workmen were busy installing what to all intents and purposes was a huge antenna system, nearly 800 metres long, carried by a cable connecting the terminal points of the bow-shaped ridge. One of the familiar hotels had been temporarily closed down and was given over to a party of physicists whose instruments were aligned on the terrace; large posters indicated the danger connected with any contact with those wires, and an enormous placard announced that the whole was not as one might have been inclined to think, a gigantic broadcasting station, but an "experimental plant for investigating extreme atmospheric high tension."

Who had been converting this celebrated belvedere into a temporary physical laboratory? The three young physicists living and working at this lofty height, when

The "Lead-In" on the Mountain Side

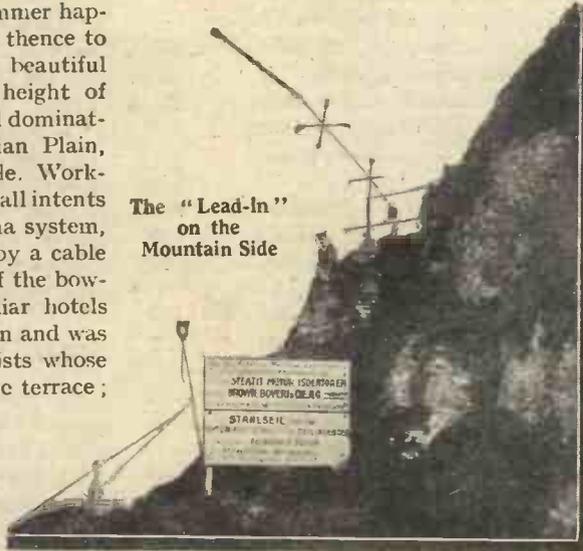

those fundamental particles which, until not very long ago, were considered indivisible and indestructible. That a further sub-division of atoms is possible, and that it points a way to the *transmutation of elements*, vainly attempted by the alchemists of old, has, of course, been shown by radio-active phenomena, and was first demonstrated by Rutherford, the celebrated British physicist.

Breaking up such a solid union as the atom, of course, entails the expenditure of extraordinary amounts of energy. Even those first results on a small scale were only possible by setting up a bombardment with alpha particles—those positively-charged helium atoms racing through space at enormous rates (up to 30,000 kilometres per second).

Now, as radium, so far resorted to to break up atoms, is only available in in-


finitesimal quantities, the effects possible were rather modest. Actual progress, it was felt, could only be hoped for, if there was a means of producing those bombarding particles in some other way, viz., by applying extreme high tensions to a tube where a high vacuum had been produced. In fact, as pointed out by these three physicists, past experience and theoretical considerations both went to show that forthcoming results would far exceed all that had hitherto been achieved.

How should, however, these extreme tensions be produced? One million volts

has, of course, often been obtained, and nearly two millions has been obtained by American engineers. This, however, seems to be the upper limit, as difficulties in exceeding this figure are very great, leaving no prospect of further advance.

This is why the three physicists of Monte Generoso, following Franklin's example, made up their minds to draw upon atmospheric electricity—that perpetual source of energy which during a thunderstorm yields huge tensions.

It may be said that Franklin's classical kite experiment has been duplicated from time to time. However, accidents discouraged any further attempt along these lines. In fact, not before modern thunderstorm research called for quantitative measurement was this problem resumed, the damage due to storms in connection with long-distance transmission plants resulting in an accurate investigation of the nature and progressive variation of thunderstorm fields. Special thunderstorm stations were at some places erected in

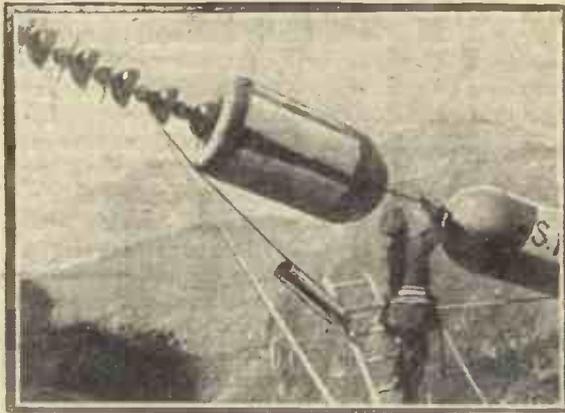

Fixing the Monte Generoso Antenna System

asked to solve the riddle, would give more or less indefinite replies.

The writer has had the good fortune of attending a recent sitting of the German Physical Society, where Dr. F. Lange, assistant at Prof. Nernst's Physical Institute of Berlin University, delivered a brief address on those most interesting experiments carried on by himself in co-operation with A. Brasch and C. Urban, and which in the course of the summer are to be resumed.

The actual aim of these experiments is nothing less than the *breaking up of atoms*—



A Spark from the Clouds—4.5 Metres Long

order to elucidate the influence of storms on high-tension lines.

Messrs. Lange, Brasch, and Urban did not think it advisable to use kites or balloons for carrying the wire system destined to collect atmospheric electricity, as such a primitive arrangement would have been subject to squalls, jeopardising the experimenter's safety and making any

(Continued on page 398)

For the Newcomer to Wireless: How Current Travels Through a Wire

I WONDER if you can explain how an electric current passes from one end of a wire to another? I can understand water flowing through a tube, but it is a little difficult to realise how an electric current makes its way through a solid wire.

First of all we had better try to see what this solid wire is made of.

Copper isn't it, as a rule?

Yes, but copper, like all other substances, is not exactly what it seems. To the eye it appears to be continuous and firmly knit, though actually it isn't.

How is that?

If we could see copper as it really is, we should find that it consists of a mass of tiny atoms, each of which is like a solar system in miniature.

Planets revolving round a central sun?

Just so. In each atom the "sun" is the nucleus which has a positive electrical charge. The planets are the far tinier electrons which are negative, electrical charges. Ordinarily the atom

is perfectly balanced, the positive and negative electrical charges being exactly equal.

Can the balance be upset?

Yes. Some of the electrons are not very closely bound to the system. They may easily travel from it to another. If an atom loses one electron its positive charge exceeds the negative and it is then known as a positive ion. Similarly, if it collects an extra electron it has a small negative charge.

Then what is an electric current?

An electric current is a flow of electrons. Let us see what happens when one electron is delivered at the negative terminal of a battery to a wire running to the positive. This electron charges into the nearest atom in the wire. Such is the force of its impact that an electron is knocked out of its orbit and goes crashing into a second atom, where the process is repeated. This happens all down the length of the wire, the net result being that whereas one electron went in from the negative terminal, one electron is shot out to the positive.

Then the one that comes out is not the one that goes in?

No, the original electron may take quite a long time to travel down the wire, but for every electron that goes in an electron is ejected and the process is so rapid that a current passes through a wire almost at the speed of light.

I suppose that a good many electrons are needed to heat the filament of a valve? several hundreds a second, I mean.

It is generally taken that the number of electrons passing a point in a wire through which an ampere of current is flowing is 8,700,000,000,000,000 in every second. Modern dull-emitter valves generally require only one-tenth of an ampere of current, so that to arrive at the number of electrons rushing through one of their filaments in each second of time you have only to knock off one nought from that figure. This is about 400,000,000 times as great as the entire human population of the world. You will understand now how it is that a thin wire gets hot when all these electrons are bustling through it.

THE "SCHOOL FIVE"

SOME NOTES ON NEXT WEEK'S BIG SET

THE "School Five," which is to be illustrated and described next week in AMATEUR WIRELESS, is the result of a considerable amount of inquiry to ascertain the wireless needs of schools.


The "School Five" is no ordinary wireless receiver, and although its particular application to school use is emphasised it must not be overlooked that it is of general interest also.

First of all, we found that what was wanted by schools was a multi-valve receiver capable of bringing in a selection of foreign programmes at very loud loud-speaker strength with unimpeachable purity of reproduction. It was also evident that the operation of the receiver had to be fairly simple and that its initial cost and subsequent running costs, although not so important as in an individual listener's case, still had to be considered.

The three essentials of a good school receiver—sensitivity and purity with volume—cannot be obtained with less than four valves; and here it should be noted that two of the valves in the "School Five" are paralleled power valves. So that actually there are four valve stages in the "School Five," arranged in the following

order: High-frequency amplifier, detector, and two low-frequency amplifiers.

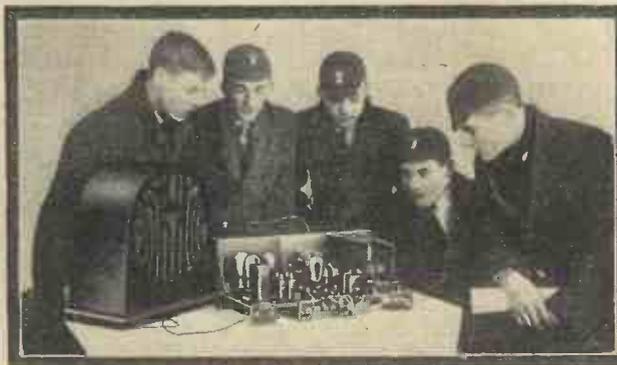Adequate sensitivity has been ensured by the incorporation of a screened-grid valve and astatically-wound plug-in coils. The two L.F. amplifying valves are



resistance-capacity coupled, a system of coupling which is now coming into its own for pure reproduction.

The combined amplification of the screened-grid H.F. valve, the detector, and the two resistance-capacity coupled L.F. valves results in a very big signal voltage being applied to the last stage, and to prevent overloading, two "super-power" valves are therefore "paralleled." In this way greater volume, without

any sense of "strain," is easily obtainable.

For such a sensitive receiver the "School Five" is unusually simple in its operation. The main control is a slow-motion dial in the centre of the panel, and on either side of this are the two subsidiary controls. One is a unique and, at the same time, extremely satisfactory reaction control, and the other what we can call a "resonator," which in plain language is simply a rough tuning control.

In its constructional aspect the "School Five" is again "something different." The completed wiring looks extraordinarily simple, because the straggling battery wires usually appearing on the baseboard are taken to a sub-panel wiring system. The screening of the screened-grid H.F. valve has also been simplified

by the use of special astatic coils.

Our message to schools is a very practical one—just this: "Build the 'School Five,' specially designed for school use and have the satisfaction of knowing that the school has a set to be really proud of."

In order to avoid interference with Warsaw and Hilversum, the Basle station has reduced its wavelength to 1,000 metres.



**Valves with the wonderful
Mullard P.M. Filament**

Powerful valves that fill any receiver with new life; lasting valves that maintain improved results long after a thousand hours' use; generous valves that give amazing volume and range due to the unequalled, tough, master filament they possess... the wonderful Mullard P.M. Filament; found **ONLY** in Mullard P.M. Valves.

Mullard
THE · MASTER · VALVE

Advertisers Appreciate Mention of "A.W." with Your Order

WIRELESS MAGAZINE

for March, is now on sale 1/-

A few items from the big contents list:

CONSTRUCTIONAL

The Music Charmer. A three-valver which can be built for £3 10 0, only 27 connections, enclosed batteries, loud-speaker reception from many British and Continental Stations. One tuning control—*Moving-coil Loud-speaker*—*D.C. Mains Eliminator for H.T. and L.T.*—*The Trapped Three-four*, incorporating special wavetrap—*All-the-world Five*, using two screened-grid valves—Full-size Blueprints at half-price.

GENERAL

G. K. Chesterton's exclusive article, "Give us Controversial Broadcasts"—The New "Q" Coils, details of a revolutionary development—The Cost of Running a Set from the Mains—A Chat on Receiver Lay-out—What to Hear on the Short Waves—Novelties and New Apparatus—Matched Impedances by Capt. H. J. Round, etc. etc.



Get a copy from your
newsagent or bookstall
T-O-D-A-Y

Does the Power Station keep your set going?

Does it supply you with music as well as light and other home comforts?

With the Met-Vick 5 Mains Set this is now possible. It is just plugged into a lamp socket or wall plug and switched on, like any other Electric Appliance, and all the little annoyances of accumulators that *will* run down, and H.T. batteries that cost so much and last such a short time, trouble you no more.

Inherently better than a battery operated set, the reproduction is so near perfection that to ask for more is hypercritical. Selectivity and range are outstanding features, and the controls, while quite simple to use, do respond to that little extra skill of the sympathetic operator which is so delightful.

With the Met-Vick 5, it is at last possible to obtain a wireless receiving set which will always give the satisfaction that only comes from really brilliant performance, and which will remain a constant source of pleasure and interest to all who hear it.

Ask your dealer for a copy of Brochure 7117/9, or write to the makers.

Those who are content with the alternative programme of their Local and Daventry Stations, but who desire the advantage of Mains operation, cannot do better than obtain the Met-Vick 3 Mains Set fully described in List 7117/10.

MET-VICK


VALVES, COMPONENTS & SETS

*



*

*

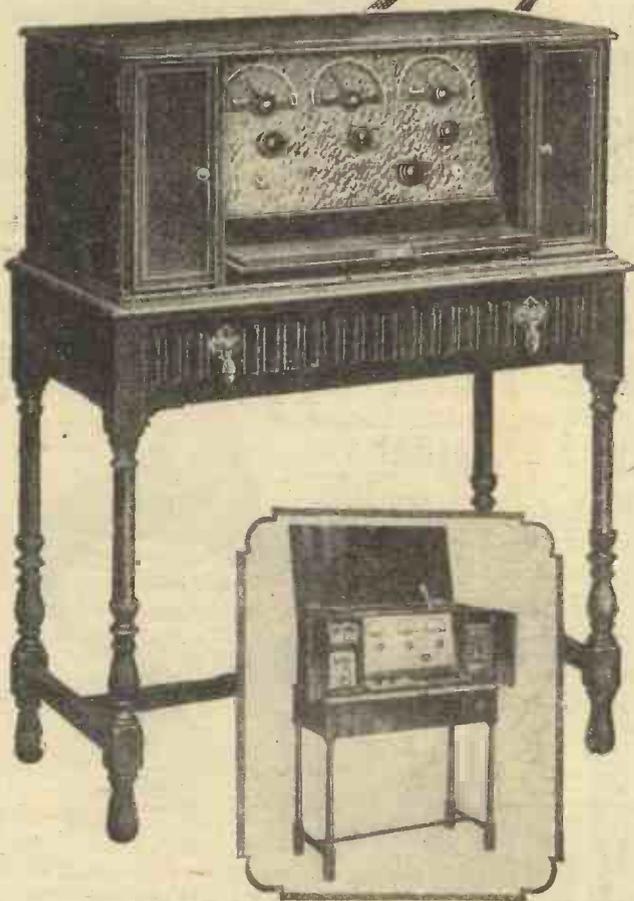METRO-VICK SUPPLIES, 155 CHARING CROSS ROAD, LONDON, W.C.2



POWER

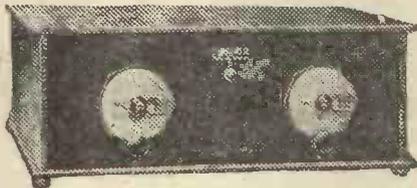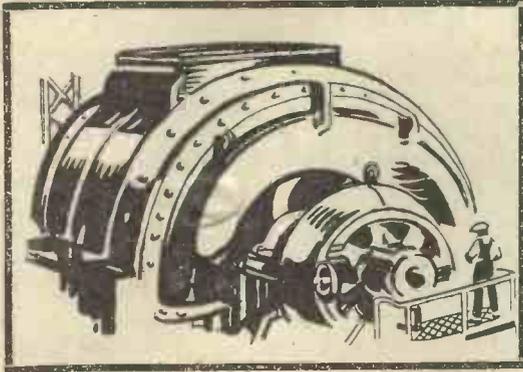

FOR YOUR COSSOR "MELODY MAKER"


CONSTANT—ECONOMICAL—SAFE

The T.C.C. book shows you how. Shows you in clear simple language how easy it is for you to build your own H.T. Eliminator. Step by step! here a diagram—there a photograph. You can't go wrong the T.C.C. way, and the Eliminator you build is a definitely efficient instrument that puts an end to Battery expense and trouble.

The T.C.C. book is free—of course. Write for it to-day and

GET YOUR POWER FROM THE SWITCH

T.C.C. CONDENSERS

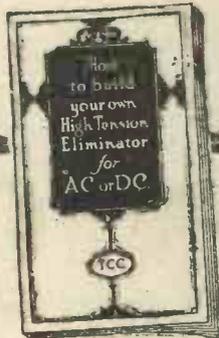

WRITE FOR THIS

FREE BOOK TODAY

Advr. Telegraph Condenser Co. Wales Farm Rd. N. Acton. London W.3.



1962

To Ensure Speedy Delivery, Mention "A.W." to Advertisers

MAKE YOUR OWN CONE SPEAKER

The New Wonder "Nightingale" CONE UNIT

Exactly as fitted to our Cabinet Cone Speaker.

Guaranteed to give results equal to the most expensive Loud-speakers yet made.

Full constructional details with each Unit.

GRAMOPHONE ATTACHMENT

Reduced from 32/6 to 15/- solely as an advertisement for the famous Bullphone Nightingale Loud-speakers. Cobalt Magnet guaranteed for all time.


With 4-inch Diaphragm.

Instantly converts your own Gramophone into a full power Loud-speaker, giving a wealth of pure undistorted volume which must be heard to be believed.



15/- each

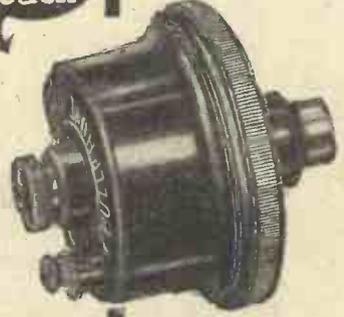SATISFACTION GUARANTEED or money refunded!



AS FITTED TO OUR £6 POST HORN

BUY ON EASY TERMS

10/- Secures this Speaker

5/- Secures this Speaker

The Nightingale "DE LUXE"

57/6 cash, or 5/- deposit and 12 monthly payments of 5/-.

21 in. high with 14 in. Bell. Mahogany finished, with plated arm & stand.



NIGHTINGALE CONCERT SUPREME SUPER

Guaranteed free from metallic resonance.

63/- cash, or EASY TERMS, 10/- deposit and 12 monthly payments of 5/-.

Send Deposit NOW!

Obtainable from your Local Dealer or direct from:—

BULLPHONE LIMITED

38, HOLYWELL LANE, LONDON E.C.2.

NIGHTINGALE SPEAKERS

On Your Wavelength!

A Revelation

WHAT Captain Eckersley would call the service area of 5GB—that is to say, the region in which dependable reception is possible with simple apparatus—is very queerly shaped. On the south coast, for example, in the neighbourhood of Brighton, signal strength is never very good, whilst fading is the rule rather than the exception. A friend of mine who lives down there found it hard to believe all the tales that I told him about the huge signal strength that I obtain from 5GB and the complete absence of fading.

A Difference

The other day, however, he helped to instal a little set—just a rectifier and two note-magnifiers—in a house situated in the Thames Valley. To his great surprise, he found 5GB what he describes as a "terrific" signal. Having seen the set working properly, he motored back to his own home and promptly tuned in 5GB with an efficient H.F. stage, a rectifier, and two note-mags., just to compare reception in the two localities. He found the transmission fading violently, whilst the quality, even during the loud periods, left a good deal to be desired. I am glad, however, of one thing. My friend now believes me when I tell him that it takes a good set in my locality to cut out 5GB and to cut in Berlin Witzleben. There are a good many problems in connection with high-power transmission on the medium waves that still leave us guessing, and no one really knows why a signal should be steady and powerful at forty-five miles, but weak and wavering at less than double that distance.

A Listeners' Strike!

I hear that in America there is a strong movement for listeners to down knobs as a protest against reception conditions over there. It appears that the U.S.A. Radio Act, despite all the care that has been expended upon it, is not being strictly enforced. Under its provisions both the power of stations and the times at which they may broadcast are very strictly limited, and it is laid down that any station which errs and strays even by a fraction of a metre from its allotted wavelength shall suffer all kinds of pains and penalties. One gathers that there is a tendency to evade the Act by boosting up the aerial watts, stretching the permitted broadcasting hours and wandering a metre or so up or down in order to avoid heterodynes—which always means producing others.

What Good?

The underlying idea of the listeners' strike is splendid; but, somehow, I don't

quite see what good it could do. If only broadcasting stations could be provided with a meter which would indicate the number of receiving valves in use in their areas at any time, such a turning over of earthing switches would give their directors a nasty shock. But as things are they have no means of knowing whether what they send out is being taken in or not.

As You Were!

I gave recently a schedule of days and times for ANH, the Dutch colonial station at Bandoeng in Java. The very day after I had written the lines that contained it the post brought me a further letter from Bandoeng containing an entirely revised scheme. Here it is. Every Monday ANE broadcasts from 12.40 to 2.40 p.m. G.M.T., using a wavelength of 15.93 metres. Also, on Tuesday and Thursday ANE is at work, and his hours are from 4.40 to 6.40 p.m. and his wavelength 31.93 metres. ANH is now transmitting regularly only on Saturdays between 12.40 and 2.40 p.m., his wavelength being 17 metres, as before.

ANE's longer wave transmission comes in very well with the bigger short-wave coils, which usually tune from about 25 to 70 metres with a .00025-microfarad variable condenser. You can take his 31.93-metre transmission as a reference point near the lower end of the calibration curve, whilst KDKA, on 62.5 metres, comes in well up the curve. Other useful checking stations, since they are both crystal controlled, are 2XAD, on 21.96 metres, and 2XAF, on 32.77 metres.

A New Short-wave Giant

Probably before these lines appear in print many readers who use short-wave sets will have picked up a new short-wave transmission of great power. This is 3XL, who is shortly to get to work with 30 kilowatts behind him on a wavelength of 59.96 metres. Since 2XAD and 2XAF use only about 10 kilowatts we should expect fine signals from 3XL. One can never say what power KDKA is employing, since the station is always experimenting—that's what it is there for—and the output varies from time to time. It is always, however, pretty useful, for signal strength is generally good.

KDKA

If you gave up KDKA in disgust some time ago owing to the queer distortion which used to accompany his transmission, you will be well advised to give him another trial, for he is now using a different system, and on most nights his quality is extraordinarily good. KDKA is also one of the easiest of the short-wave stations to receive owing to his comparatively high

wavelength. Even with a not very efficient set, capacity effects and their attendant evils do not, as a rule, manifest themselves very strongly until one drops down to about 40 metres or below. It is, in fact, quite possible to receive KDKA successfully with a 6-V-2 set designed for broadcast reception and not intended for work on the short waves.

A Dance Band Moves

Those who are fond of dance music will be grieved to read that Mr. Sidney Firman with his band is about to leave 2LO. It is understood that he intends to devote his attentions to the production of a novel theatrical revue, the setting of which is to be a broadcasting studio. He is sure to be very popular when he takes his revue on tour, for he has made many friends all over the country during his career as a broadcaster. But if we must say farewell to Mr. Firman, it is good news to hear that his place is to be taken by another star in the jazz firmament, Mr. Jack Payne. Just as Mr. Firman is about to strike a new note in revue, so Mr. Jack Payne promises us a new note in broadcast dance music. He intends to avoid the frequent repetition of popular tunes and to devote a good deal of time to the fresher and lesser known tunes.

The Young Idea

I spent an interesting, if somewhat strenuous, couple of hours the other night in giving a lecture on wireless at one of our public schools. There was no doubt about the keenness of the audience on wireless, for many of them had come armed with notebooks and pencils, which they plied assiduously, and heaps of them, when question time came round, were ready with sensible, though sometimes rather formidable questions to exercise what your THERMION is pleased to call his brain. I had rather a dreadful moment when I went in a quarter of an hour or so before the show started just to see that the demonstration sets were working properly. With one of them I tuned in 5GB and obtained splendid reception—for about ten seconds. Then came a horrid silence.

A Hectic Time

Trying to recall hastily all that I had ever read or written on the subject of rapid fault-finding, I started in with a sinking heart to locate the trouble. More by good luck than by good judgment, I was able to do this just in the nick of time. As a matter of fact, it was not in my apparatus at all. A six-volt accumulator had been provided for me, and I had hitched my L.T. leads on to it without examining it very carefully. One of the strap connections between its cells was loose, and as

On Your Wavelength! (continued)

the terminal was dirty, a slight movement had resulted in a complete cutting off of filament amps.

Huizen

The news that the Dutch Huizen transmitter, owing to interference from Scheveningen-Haven, has adopted the wavelength of 340.9 metres (that of the Petit Parisien) for all transmissions until 5.40 p.m., in a sense is somewhat disconcerting; as it is, that portion of the wave band is already fairly crowded, and the advent of a 5-kilowatt transmission in that region is rather inclined to wipe out our reception of more distant programmes, such as those we can receive from Barcelona, Posen, or even, for the matter of that, Prague.

A Pity

On top of this news from Holland, also comes the information that if the new medium wavelength is found satisfactory, Huizen will either entirely adopt it or seek one in the neighbourhood of 350 metres. If this does actually take place, I am afraid that the wipe-out effect will be even greater, at that time during the main evening hours when it is already difficult to pick up many stations in this portion of the wave band free of heterodyne or other interference. Personally, I cannot see that the congestion existing in the ether has been much reduced since the advent of the Geneva Bureau. Either this central authority of the Union of Broadcasters has executive powers or it has not; if it does possess any, why not exercise them? If it does not—well . . .

An Eye to the Future

I expect that many of my readers who have read these notes week after week are often wondering what the latest development is likely to be in receiver design. Quite rightly, many of them argue that we seem to have reached that stage when the various "dynes" have the field to themselves. The matter of most importance, however, in the near future will be selectivity of receivers, for with the advent of the regional scheme many receivers which are already obsolete will require a certain amount of attention in this respect. Already many readers have, no doubt, had a certain amount of forewarning in this respect, since the erection of the new masts at Daventry Experimental, 5GB, have resulted in a considerably increased signal strength to many listeners, which has in certain cases resulted in a certain amount of jamming when the receiver is not fitted with a wavetramp or otherwise rendered selective.

Australian Short-wave Transmissions

Short-wave enthusiasts have now another station to listen to, and one on which they

can test their sets for real DX, in 3LO (Melbourne, Australia). The usual 3LO station is well known to most wireless enthusiasts as the sister station to London, as it were, on the Continent of Australia. Apparently a short-wave transmission has been inaugurated on a wavelength of 32 metres in addition to the normal service on the usual broadcasting band.

I was playing round last Sunday with a short-wave superhet arrangement, very similar to the admirable "Short-wave Super Six," described in *AMATEUR WIRELESS* a few weeks back, and I was surprised to hear, good and strong, a clock striking five, followed by the announcement: "This is 3LO, Melbourne, transmitting on 32 metres. It is just 5 o'clock. We are continuing our programme by transmitting . . ."

Excellent Reception

I thought at first that I could not have heard aright, but I sat on him for a little time to confirm the matter. He was subject to high-speed fading, and was rather broken up and, indeed, at times was almost unrecognisable. To my joy, he repeated his call at frequent intervals, and I was soon left with no doubt that he was really Melbourne, Australia. Gradually conditions improved, and the reception became excellent, although I was not able to get him as well as 2FC. Shortly afterwards, he amused us by giving results of the Ilford by-election; subsequently, he recounted some of Hinkler's adventures since landing in Australia. I do not know what the power of this station is, but it was certainly an interesting experience, and all the more pleasing since it was totally unexpected. I am asking the Editor to find out some more about this station, and no doubt, as information becomes available, he will publish it for the benefit of other readers. (Correspondence relating to this station appears on page 392.—ED.)

The X-ray Sleuth

An X-ray photographer to whom I was chatting the other day told me of a rather amusing application of his art to wireless. A friend of his, a great wireless enthusiast and one who knew a good deal about the subject, was the possessor of one of those wireless receivers that are guaranteed for a certain length of time so long as the panel seal is not broken. Now, this instrument developed a fault. At least, the cause of the poor reception was tracked down by a process of elimination to the "innards" of the receiver.

Although quite sure in his own mind that the receiver was at fault, the photo-

grapher's friend was loth to investigate further because of the seal. Then the bright idea occurred to him of having an X-ray photograph of the receiver taken. When, subsequently, he examined a photographic negative showing an X-ray interior of the box of tricks he was able to see that one wire was severed, being just "held" by the cotton covering of the wire.

A Wizard

This is not the end of the story, for when he returned the receiver to the makers he informed them that if they broke the seal they would find a certain wire disconnected, but he omitted to mention how he knew this was so! He says that his reputation as a wireless expert went up very considerably in the estimation of the wireless firm concerned when, on opening the box, they found that his diagnosis was correct.

Where We Lead

One might have thought, from articles and correspondence appearing recently in some of the lay papers, that America had things more or less her own way as regards television. Such, however, is most emphatically not the case. The Americans themselves admit that our own countryman, Mr. J. L. Baird, is streets ahead of anybody else in this coming department of wireless, and that what he has already accomplished puts completely in the shade anything that has been done on the far side of the Atlantic. Mr. Baird does not do a great deal of talking about his work; in fact, we often hear very little about him for quite long periods on end. But he goes steadily forward. The time may not be very far distant when the television will do its work as well, at any rate, as did the wireless loud-speaker at the beginning of the broadcasting era. Once that stage is reached it will be but a short time before something like perfection is in sight.

More Radioese

You know my loathing of the jargon used by a certain section of wireless enthusiasts. So far, it seems to have been confined chiefly to wireless transmissions and to the cryptic letters or postcards that one occasionally receives from very young hands. The other day, though, I got rather a shock when a friend sent me on a letter that he had received in reply to an inquiry addressed to a wireless company.

"Dear Sir," it began, "We duly received your favour of the 17th ult. We feel sure that our — transformer is exactly the component that you are looking for, O.M. . . ." Ye gods! Fancy calling a man "Dear Sir" at one moment and "Old Man" the next! I need hardly say that my friend did *not* purchase the transformer.

THERMION.

NEXT WEEK:
FURTHER NOTES ON THE
"Q" COIL THREE

An Easily-Made Cone Loud-speaker

By J. H. REYNER

PROBABLY the most popular type of loud-speaker in use at the present time is the cone. A glance at the window of any wireless dealer will reveal numerous examples of the type; some decorative and costly; others inexpensive, yet similar in design.

In this article constructional details are given of a simple, but effective, cone speaker, utilising a form of magnetic unit known as the balanced armature. The balanced armature is recognised as a very efficient type of unit and is employed in some of the best-known cone speakers.

The Balanced Armature

The majority of readers have, at some time or other, examined an electro-magnetic unit, in which a reed, attached to a cone, is caused to vibrate due to its proximity to the electro-magnet through which pulsating currents from an amplifier are flowing.

The system utilised in the balanced-armature unit is somewhat different; here a soft iron tongue is suspended between two sets of magnets at either end. The tongue takes up its position exactly between the magnets and unless a pulsating current is flowing in the magnetic windings, there will be no resulting force tending to move it. Consequently on the arrival of a pulsating force, the tongue, which is attached to a diaphragm, or other means of producing sound waves, is free to move in both directions and is consequently caused to rock from side to side of the mean position. Hence the motion transmitted to the cone approximates more closely to a true sine wave than is the case with the previously mentioned magnetic unit.

The unit utilised in this cone speaker is the Ideal unit marketed by Messrs. F. A. Hughes and has a number of interesting points in its design which merit attention. One of the most displeasing qualities of any loud-speaker is its tendency to resonate at certain audible frequencies. Precautions have been taken in this unit to avoid any appreciable resonance of the vibrating armature by damping the movement with Sorbo rubber.

The general effect of such damping is illustrated in the diagram. The full line curve illustrates an undamped resonance, whilst the dotted curve shows the effect of damping the vibrator movement. Although the overall strength of reproduction may be

less, the reproduction is more pleasing, whilst there is less tendency for the tones to become jumbled.

The Design

No attempt has been made to design an elaborate speaker. It was thought that the reader would appreciate a simple, although efficient, construction.

The cone is essentially free-edged, in that it is supported at the periphery at one point only: in order to obtain the best possible reproduction, some form of baffle


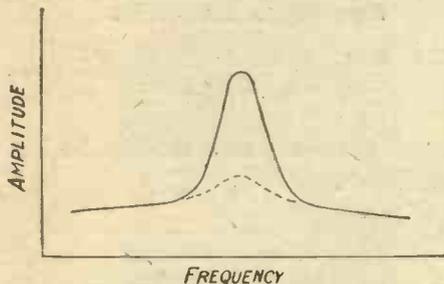


Diagram showing effect of damping

should be used consisting either of an enclosing cabinet or expanse of wood.

The Cone

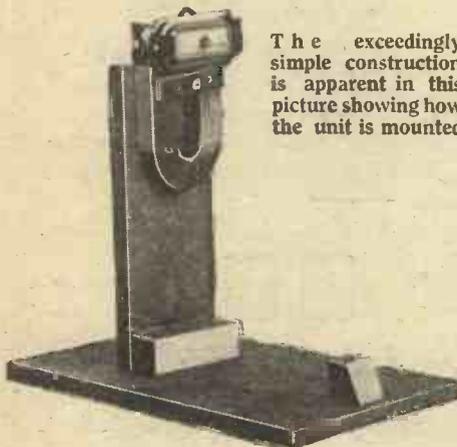Nineteen-inch diameter, Six-Sixty paper marketed by the Electron Valve Co., is utilised for making the cone. This part of the construction presents no difficulty whatsoever, as full instructions are given with each sheet of cone paper supplied. Seccotine or glue may be used in sticking the paper together.



The exceedingly simple construction is apparent in this picture showing how the unit is mounted

Since the cone is essentially free-edged some means of preventing distortion of the shape has to be provided. It was finally decided to cut out a thin piece of cardboard the same diameter as the cone and stick this round the edge. This is placed round the edge of the cone and, if necessary, a number of fairly light books are placed at various intervals on the top of the cardboard until the glue has had sufficient time to dry.

Mounting the Magnetic Unit

We must next consider a suitable method of mounting the balanced-armature unit in the correct position for attaching to the centre of the cone. The support may be a strip of wood mounted in the manner shown in the photographs. The magnetic unit is securely held by passing a screw through a small ebonite clamping piece.

A small piece of wood, with one side bevelled, is screwed on to the end of the baseboard behind the cone and serves to make the whole assembly rigid.


Assembly

The instrument may now be assembled. Unscrew the first nut on the operating spindle of the balanced armature, and remove the brass discs which are not required. With the Six-Sixty cone paper, will be found two metal centre pieces. Place one of these on the spindle, then the cone and finally fit the second disc and screw the whole up tight with the nut.


Now assemble the unit on its stand and adjust the height till the bottom of the cone just rests on the baseboard. Fit the bevelled block behind the cone and fix it in position. A screw through the cone into the block then completes the assembly.

The results obtained with this speaker are remarkably good; it will give surprising volume with quite a small input.

A new day and night wireless telegraphy service has been installed for the use of shipping by the Belgian Government at the Antwerp transmitting station OSA. Captains of ships desiring the services of a doctor address their telegrams *Radio-medical anvers Radio* and the letters SVH (*Sauvegarde de la vie Humaine*), to which priority is given. No charge is made for these messages, which can be transmitted in the French, Flemish, or the English languages. Official medical advice promptly follows all requests received from sea-going craft.

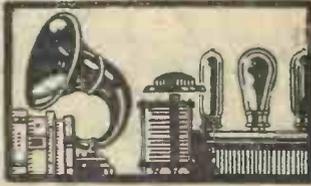


PRACTICAL ODDS & ENDS

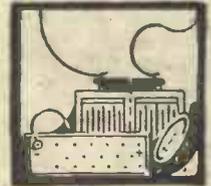

Adjustable "Fixed" Condenser

THE condenser shown in the sketch is of the fixed type, with mica di-electric, but variable capacity is obtained by means of compression applied to the two plates. Two springy brass foils each about 2 in. long by 1 in. wide are cut out as shown, and a $\frac{3}{8}$ in. hole is drilled through the centre of each, the centre being measured between the shoulder of the tag and the opposite end. The mica sheet is about $1\frac{3}{4}$ in. long by $1\frac{1}{4}$ in wide, this also being drilled $\frac{3}{8}$ in. through the centre. It is then secured to the lower foil by means of shellac varnish, the usual hot flat-iron method being employed.

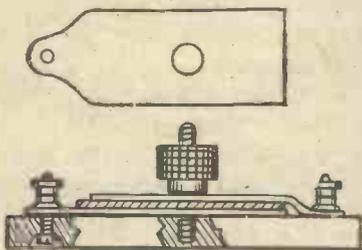A suitable ebonite base is marked off from the foils and drilled through each end of a line with the centre to take two small terminals. In the exact centre a 2B.A. tapping hole is drilled and threaded (with a plug tap) to take one end of a $1\frac{1}{2}$ in. length of 2B.A. screwed brass rod which is screwed hard down in the ebonite to form



An Adjustable "fixed" Condenser

a stud. A small ebonite knob is then drilled through and tapped 2B.A., so that it fits nicely over the end. The lower foil with the mica is slipped over the stud, and the tag secured firmly under one of the terminals. The other foil is slightly bent at the tag and secured in the same way. Care is taken to see that the edges of the central holes are well separated from the stud, and that the upper foil is just separated from the mica. The ebonite knob is now run down the stud, and by adjusting this the distance between the foils—and hence the capacity—can be carried between maximum when the foil is hard down on the mica, and minimum when the top foil is allowed to spring back to its normal position.

O. J. R.

Keeping Files Clean


FILES used for work on ebonite are apt to become quickly clogged with ebonite dust, and the cutting surface thus rendered

ineffective. This trouble is easily obviated if the file is frequently rubbed over with chalk during use. This enables the file to throw off the ebonite dust, which will not adhere to the chalked surface of the file.

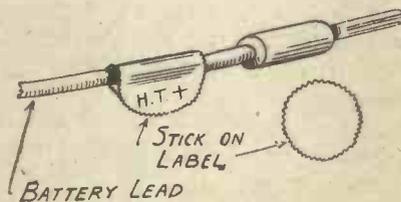H. B.

Battery Tags

OF all the methods of labelling battery tags, surely it is easiest to do so with the ordinary little paper stick or tab!



Paper Tags for Battery Leads


They take no time to put on, and they last for a surprisingly long time.

H. B.

For Users of Leclanché H.T. Batteries

WHEN a leclanché battery of some 80 or 100 cells is in use, some clean and rapid method of refilling becomes a necessity.

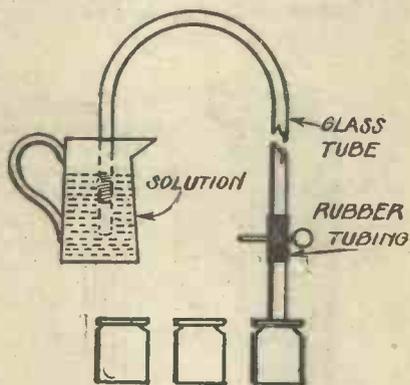A 2-ft. length of $\frac{1}{4}$ -in. glass tubing is bent to shape in a gas flame, and a fountain-pen filler attached, as shown in the drawing, by an inch or so of rubber tubing. A pinch-cock or Mohr's clamp is then slipped over the rubber. The syphon is started by filling the glass tube with the solution. The Mohr's clamp allows the flow to start or cuts it off immediately.



For Rapid Wet Battery Charging

The syphon can also be easily adapted for drawing off the old solution.

A. E. H.

Scraping Flex Leads


DO not scrape the covering off the ends of flex leads over a receiver when wiring up. The reason for this caution is obvious, although it may not occur to many. There is always a danger of a fine strand of wire dropping off unseen during the process, and it is not a good policy to have fine pieces of copper wire near the components or wiring. There is a danger of even such minute factors causing trouble in the nature of short circuits.

B. R.

A Simple Frame aerial Socket

A SIMPLE socket which may be attached to the cabinet of a receiver, or alternatively to the edge of a table or ledge, may be made from a curtain-rod adaptor, as shown in the drawing.

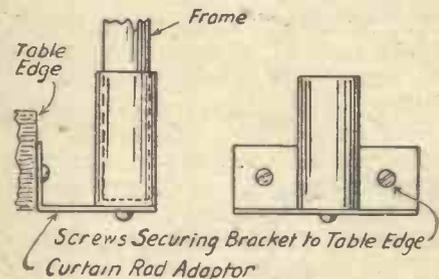It is only necessary to secure the adaptor in any desired position where the frame is to be used. The frame itself is then



A Frame-aerial Support

dropped into the socket, as shown, and revolved round until the best position for reception from the required station is found. If the frame support should not fit the socket it is only necessary to turn the end down to a corresponding diameter.

C. B.

Self-contained Receivers

A POINT worthy of note is that there is a danger in the case of all enclosed receivers, of no ventilation being allowed to enable the sulphuric fumes arising from the batteries to escape. If this is the case, it will be found that these fumes are detrimental to the component parts of the actual receiver, especially the metal elements. It is best, if possible, to well separate the batteries from the receiver by means of a definite partition. Some means of ventilation also should be provided for in the battery compartment.

R. D.



**SAVE
MUCH
SPENDING**

**BY
TIMELY
MENDING
WITH**



FLUXITE
it simplifies soldering

All Hardware and Ironmongery Stores sell FLUXITE in tins, price 8d., 1/4 and 2/8. Another use for Fluxite—Hardening Tools and cast Hardening. Ask for leaflets on improved methods.

**FLUXITE
SOLDERING
SET** -complete
7/6
or LAMP only
2/6



FLUXITE LTD.
(Dept. 326)
Rotherhithe, S.E.16



**Results
which astonish
and delight**

Are you entirely pleased with your present valves, or with the performance of your receiver? Perfect valves will not, of course, ensure perfect reproduction. There are other links. When all is said and done, however, good reception depends to a greater extent upon the valves than upon any other factor. If your set is operating on 2 volts, we say deliberately and advisedly that, unless you are using the B.T.H. Nickel Filament Valves you are not getting the best results of which your set is capable. Try them to-day, you will be astonished and delighted at the improved reception. There are three types, as follows:—

B. 210H <i>R.C. and H.F.</i>	B. 210L <i>General Purpose.</i>	B. 215P <i>Power.</i>
Fil. Volts 2	Fil. Volts 2	Fil. Volts 2
Fil. Amps. . . . 0.10	Fil. Amps. . . . 0.10	Fil. Amps. . . . 0.15
Max. H.T. V. 150	Max. H.T. V. 120	Max. H.T. V. 120
10s. 6d.	10s. 6d.	12s. 6d.

The above prices are applicable in Gt. Britain and N. Ireland only

B.T.H. NICKEL FILAMENT VALVES

B.T.H. NICKEL FILAMENT VALVES



**NICKEL FILAMENT
VALVES**

Made at the Mazda Lamp Works, Rugby.

Your Dealer holds adequate stocks

The British Thomson-Houston Co. Ltd

2903

ASTOUNDING

results are obtained from circuits embodying our L.F. Transformers, which are British made throughout.

The "RADIOGRAND"

is a component of the very highest quality, typical of a firm that has specialised in one particular instrument and achieved a reputation for outstanding excellence. Though moderately priced, design, materials and workmanship are such that these Transformers stand unrivalled for general efficiency.

12/6 RATIOS
5-1 & 3-1.



If unable to obtain, write
TELSEN ELECTRIC CO., LTD.
Head Office and Works; 207 Aston Road, Birmingham



"ACE" 8/6
Ratios 5-1 and 3-1.

This is a smaller instrument built to give first-class results, yet of a size and weight that render it particularly suited for Portable Sets where compactness is an essential feature.



Your dealer will supply on 14 days' free trial.


Every Instrument guaranteed 12 months.

"A.W." TESTS OF APPARATUS

Conducted by our Technical Editor, J. H. REYNER, B.Sc. (Hons.), A.M.I.E.E.

Tayloradio H.F. Choke

THE increased use of high-frequency chokes in not only the H.F., but also the L.F. circuits of wireless receivers, in order to avoid difficulties which arise from the presence of unwanted H.F. currents, has led to numerous samples of this component being placed on the market. It is often essential to the good working of the set that the H.F. choke function efficiently over the wave band covered by the tuning circuit of the receiver.

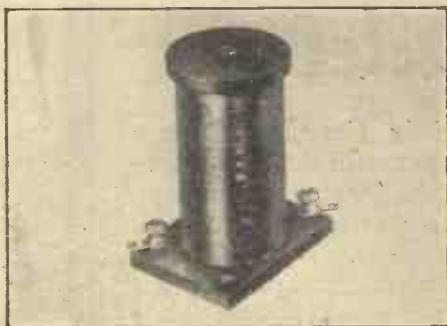

Tayloradio H.F. Choke

In view of this, we always give H.F. chokes a severe test, a special method of testing having been devised which shows up at once any defects in a choke, and it is only by the maintenance of a high standard of this nature that satisfactory performance reports can be given. The Tayloradio choke is clearly an attempt to minimise to the utmost that bugbear of designers—self-capacity. The winding is placed on a skeleton former consisting of five slotted ebonite rods. The winding is in eight sections, wound with fine-gauge enamelled wire, and the whole is enclosed in a glass tube to protect the windings from damage and dust.

On test, the choke functioned satisfactorily down to below 100 metres, and operated reasonably well on Daventry. There were indications, however, that the choking action was deteriorating in this region, and we should like to see a few more turns on the winding. The component, indeed, does not deserve to be handicapped by any such suspicion, for it is well constructed and reasonable in price.

It is produced by W. W. Taylor of 36 Furnival Street, E.C.4.

Ediswan Battery Lead

THE Edison Swan Electric Co., Ltd., of Ponders End, have recently put on the market the battery cord which they supply with their One-Der set. This has two L.T. tappings, plus and minus, and two H.T. +

tappings, the H.T.— being common with the L.T.—. The L.T. leads finish in a plug, this being done to minimise the risk of wrong connections.

The resistances of the L.T. leads in series was found to be .1 ohm, which is quite satisfactory. The leads are provided with clear indicating tabs, and should prove useful.

Pertinax Panel Material

THE popularity of the modern "American" type of panel has given rise to the production of a large number of panel materials, some good and others not so good.

The Pertinax panel, which has been submitted for test by G. L. Scott & Co., Ltd., of 69 Fleet Street, E.C.4, is made of compressed bakelite paper. This is good not only as regards insulation (which is the most important factor, except in special circumstances), but also as regards losses at high frequency.

The material works well and has an attractive finish, and it should prove a useful substitute for the more usual ebonite.

L.S.A. Dry Batteries

ONE of the most important features of the original Leclanché battery was its marked recuperative powers. The L.S.A. batteries, marketed by Messrs. Thompson & Co., of 1 and 3 Old Swan



L.S.A. Dry Batteries

Lane, E.C.4, are made at the original Leclanché works in Switzerland, and are claimed to possess this recuperative power to a high degree.


A number of batteries of this type were recently tested in our laboratories. One, of the usual small size, placed on a discharge of 6 milliamps, gave a life of over 2,000 milliamp-hours. A similar battery placed on a 6-milliamp discharge for short periods and allowed to recover in the

interim (the average use being five hours per day) is still working at the present time, having already lasted over 3,000 milliamp-hours.

These batteries thus appear to fulfil the claims of long life made for them, provided, of course, that they are discharged at a rate within the capacity of the particular size of cell.

Loriometer Potentiometer

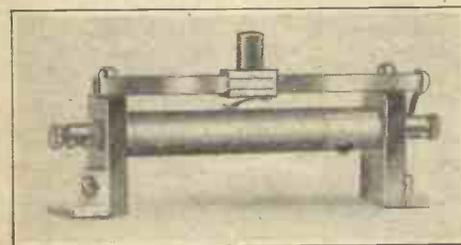LORIOSTAT resistances are well known to readers of AMATEUR WIRELESS, and it is with pleasure that we welcome the Loriometer, a potentiometer by the same manufacturer, A. W. Stapleton, of 19a



Loriometer Potentiometer

Lorrimore Buildings, Lorrimore Street, S.E.17.

This has a winding of fine-gauge resistance wire wound on a small barrel, contact being made by a slider running on a square metal rod running parallel with the barrel. The motion so obtained is very smooth and is electrically silent.

A particular point about potentiometers is that they should have a high resistance, for they are constantly across the battery, in some instances even when the set is switched off. There is thus a constant drain on the L.T. battery, and the higher the resistance of the potentiometer winding, the less will be this drain.

The sample tested had a resistance of 1,240 ohms, which is very good for so compact an instrument. We can recommend this to readers.

That birds have a short-wave transmitter and receiver located in their brains, to which is due that sense of direction and migratory instinct which has so long been a puzzle of naturalists and, in fact, all scientists, is the remarkable theory that has been put forward by M. Georges Lakhowsky, of Brussels. In conjunction with this cell is a conducting liquid which is both an oscillator and resonator of very short waves. So the carrier pigeon, for instance, makes use of wireless waves without knowing it.

WEARITE **WRIGHT & WEAIRE, Ltd.**
 740, HIGH ROAD,
 TOTTENHAM, N.17
COMPONENTS

NOTICE!

Having established a reputation as makers of all types of highest-grade Inductance Coils, and in particular, those used in published circuits, we have extended our plant and can give prompt deliveries. We would specially draw attention to our make of coils suitable for such circuits as the

- "Melody Maker" - - - - - 8/6 each
 - "Mullard Master" B.B.C. - - - 5/6 "
 - " " " 5XX - - - - - 8/6 "
- W.G.2 Tuner as used in the "Two-wave Two" described in this issue. Price 15/-.

THE NEW "Q" COIL as described in this issue.


- Selection 4
- Coils B.B.C. - - - - - 24/6 pair
 - " 5XX - - - - - 16/- "
 - Bases - - - - - 2/6 "

Paxolin panels drilled for all circuits at an additional charge of 6d.

EVERY COIL CARRIES OUR GUARANTEE OF EFFICIENCY



THE BURTON PANEL RHEOSTAT

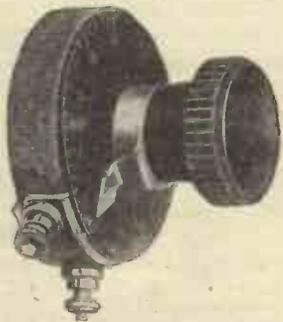

Panel Mounting
 Rheostat, 6, 10,
 15, 30 ohms,

2/3
 complete

C. F. & H. BURTON,
 Progress Works,
 BERNARD STREET,
WALSALL

Phone 560



EXPERT CHOICE
confirms the efficiency
of the new
BURNDEPT Condensers



Burndept Variable Condensers are used in the following

"Amateur Wireless" Sets:

- "LOUD-SPEAKER SPECIAL ONE"**
 Feb. 18th issue.
- "RIDLEY SHORT-WAVE THREE"**
 Feb. 25th issue.
- "SELECTUS THREE"**
 March 3rd issue.
- "THE Q COIL THREE"**
 See page 388 of this week's issue.

THE new Burndept Variable Condensers have received an enthusiastic welcome from experts everywhere. In all types of sets, the insulated spindle, insulated end-plates and metal earth shield of these Condensers have definitely been the means of eliminating hand-capacity and securing increased signal strength. Try them in your set and see what a difference they make! These robustly constructed condensers are made in two types:—


"Log Law"—for H.F. and closed circuits—as used in the Burndept "Screened Four"—.0003 mfd., 15/-; .0005 mfd., 15/6, without dial or knob—Printed Wave-Length Scales (150-3,000 metres) 1/6 per set.

"Square Law"—for capacity reaction and short-wave sets—used in Admiralty sets built by Burndept—.00007 and .0002, 13/6


Full particulars on request.

BURNDEPT

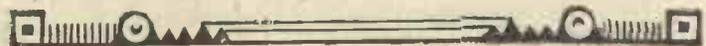
Offices: **BLACKHEATH, LONDON, S.E.3**
 London Showrooms: 15 Bedford Street, Strand, W.C.2



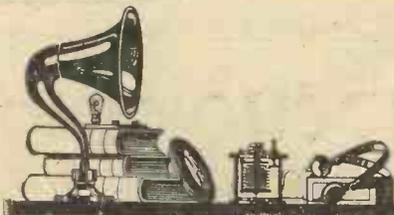You will Help Yourself and Help Us by Mentioning "A.W." to Advertisers



OUR INFORMATION BUREAU

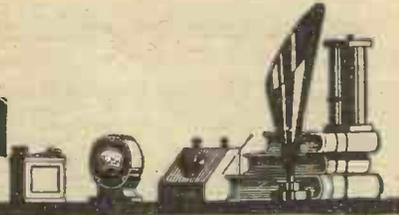

RULES.—Please write distinctly and keep to the point. We reply promptly by post. Please give all necessary details. Ask one question at a time to ensure a prompt reply, and please put sketches, layouts, diagrams, etc., on separate sheets containing your name and address. See announcement below.

Cutting Out H.F. Valve.

Q.—I wish to cut out the H.F. valve in my set, which consists of one stage of neutralised H.F., detector, and one L.F. Is there any simple and efficient means of accomplishing this without drastic alterations to the wiring of the set?—T. K. (London).

A.—If you switch off the filament current from the H.F. valve and then throw the neutralising condenser out of adjustment, you will be able to use only two valves. In this way no switch or switches are introduced and no alteration to the wiring of the H.F. circuit is necessary.—I. C.

Loud-speaker Distortion.

Q.—I experience distortion in reproduction from my loud-speaker, and although I have tested all the components, adjusted H.T., L.T., and G.B. to the best of my ability, distortion is still apparent on loud passages of music.—F. D. (Newcastle).

A.—You are advised to connect a milliammeter in the plate circuit of your last valve and then adjust your H.T. and grid-bias voltages until the M/a needle remains stationary. If distortion persists, even when the needle is stationary, then it is possible that you are saturating the loud-speaker, and we sug-

gest that you interpose a choke-filter circuit between the receiver and the loud-speaker. In this way the direct current from the H.T. battery will not pass through the loud-speaker

When Asking Technical Queries

PLEASE write briefly and to the point

A Fee of One Shilling (postal order or postage stamps) must accompany each question and also a stamped, addressed envelope and the coupon which will be found on the last page.

Rough sketches and circuit diagrams can be provided, but it will be necessary to charge a special fee (which will be quoted upon request) for detail layouts and designs.

windings and the latter will be able to deal more effectively with the signal current.—C. B.

Lead-in Insulators.

Q.—I notice that most lead-in insulators con-

sist of a tube of ebonite through which a brass rod is passed, the latter being the means of conducting the electrical energy through from the aerial to the receiver. Why is it that glass or other insulating materials are not used, as these appear to be insulators, i.e., have a greater resistance to the passage of electrical currents, than ebonite?—H. A. (Bury).

A.—When considering the design of such accessories, it is essential to bear in mind the fact that one is dealing with oscillatory currents. An insulator that has a high resistance to direct currents may also have a high dielectric constant which will create a very large capacity to earth. This, in itself, will be the means of by-passing much of the signal energy to earth, and the aerial losses will be far greater than would be the case were ordinary ebonite used. Ebonite has a mean S.I.C. value of about 2.5, whilst glass has a value of approximately 8. Air has an S.I.C. value of 1, and if it were possible to pass a lead-in wire through an air space into a receiving or transmitting station and at the same time keep the lead-in from swaying, this would be an almost ideal arrangement. Ebonite is used because it is cheap, has a low S.I.C. value, and usually affords adequate insulation for the electrical impulses picked up by an aerial.—L. C.

CHIEF EVENTS OF THE WEEK

- LONDON AND DAVENTRY (5XX)**
- Mar. 11 Military Band Concert. Belgian national programme.
 - " 12 Programme S.B. from Cologne.
 - " 13 *The Land of Heart's Desire*, by W. B. Yeats.
 - " 14 *Joseph and his Brethren*, an opera in three acts by Mehul.
 - " 15 *College Days*, a programme of students' songs from the Scottish Students' Song Book.
 - " 16 National Symphony Concert, relayed from the People's Palace, Mile End.
 - " 17 Running commentary on the Rugby International, England v. Scotland, relayed from Twickenham.
- DAVENTRY (5GB)**
- Mar. 11 Albert Sandler
 - " 12 *Joseph and his Brethren*, an opera in three acts by Mehul.
 - " 13 Programme from Cologne.
 - " 14 Two Comic Operas from Birmingham: *Breaking the Spell*, by Offenbach; *The Policeman's Serenade*, by Alfred Reynolds.
- CARDIFF**
- Mar. 15 The Second Concert (thirtieth season) of the Newport Choral Society.
- MANCHESTER**
- Mar. 13 "Down to the Sea in Ships," some glimpses of life on board an ocean-going merchantman.
 - " 15 Hallé concert from the Free Trade Hall, Manchester.
 - " 17 A Gilbert and Sullivan programme.
- GLASGOW**
- Mar. 17 A concert by the Caledonian Strathspey and Reel Society.
- ABERDEEN**
- Mar. 15 Concert relayed from the Music Hall
- BELFAST**
- Mar. 15 Comedy and light opera programme.
 - " 17 *Saint Patrick*, a narrative play.


OUR BLUE-PRINT SERVICE!

Constructors of receivers described in this journal should make full use of our Blueprint Service and avoid all risk of failure.




Model 6. Indicator and Slow Motion Dial. Price 3/9

Provides a means for recording stations received in two small windows. Practically no metal parts, thus eliminating capacity. The main moulded gear meshing, with a small gear gives a positive drive, and no backlash to a silky movement. The useful reduction ratio of 12-1. Fits all condensers.

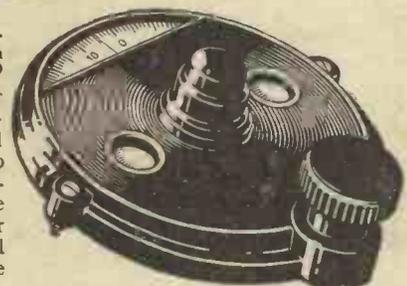

Model 7. (below) Seven way Battery Connector. Price 10/6

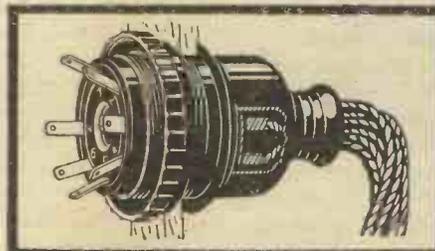The new and best way of grouping H.T., L.T., and G.B. leads together. Plug in—instant reception; withdraw plug— all batteries disconnected. Each lead is lettered and numbered at three points, so that it is impossible to wire or fit connector wrongly. Complete in best insulation Moulding, with leads ready for fixing to batteries. Dispenses with all unsightly terminals and loose ends.



THE ABOVE COMPONENTS ARE USED IN THE SET DESCRIBED IN THIS ISSUE

HARLIE BROS.

BALHAM ROAD, LOWER EDMONTON, N.9


'Phone : Tottenham 3446

BROADCAST TELEPHONY

(Broadcasting stations classified by country and in order of wavelengths).

Metres	Kilo-cycles	Station and Call Sign	Power Kw.	Metres	Kilo-cycles	Station and Call Sign	Power Kw.	Metres	Kilo-cycles	Station and Call Sign	Power Kw.
GREAT BRITAIN											
24	12,500	Chelmsford		273	1,098	Limoges (PTT)	0.5	400	750	Cork (SCK)	1.5
252.1	1,190	*Bradford (2LS)	0.2	275	1,090	Bordeaux (PTT)	1.0	407	737	Naples (Napoli)	1.5
272.7	1,100	*Sheffield (6FL)	0.2	276	1,085	Rennes	0.5	452	663	Rome (Roma)	3.0
275.2	1,090	*Nottingham		278	1,079.	Grenoble (Poste des Alpes, PTT)	1.5	550	545	Milan	
277.8	1,080	*Leeds (2LS)	0.2	287.9	1,042	Lille (Poste du Nord, PTT)	0.7			(Vigentino)	7.0
288.5	1,040	*Edinburgh		289.3	1,038	Radio Lyon	1.5	309.2	970	Zagreb (Agram)	1.25
294.1	1,020	*Stoke-on-Trent	0.2	297	1,010	Radio Agen	0.5	460	652	Belgrade (testing)	0.25
294.1	1,020	*Swansea (SSX)	0.2	300	1,000	Algiers (PTT)	2	LITHUANIA			
294.1	1,020	*Dundee (2DE)	0.2	302	993	Radio Vitus (Paris)	1.0	2,000	150	Kovno	
297	1,070	*Hull (6KH)	0.2	305.1	980	Casablanca (Morocco)	1.5	LUXEMBURG			
306.1	980	*Everpool (6LV)	0.2	309	970	Marseille (PTT)	0.5	217.4	1,380	Radio (Luxemburg)	
312.5	960	Belfast (2BE)	1.5	340.9	880	Le Petit Parisien, Paris	0.5	NORWAY			
326.1	920	Newcastle (5NO)	1.5	345	867	Rabat (PTT)	1.0	30	9,994	Bergen (testing)	
353	850	*Bournemouth		370	811	Radio LL, Paris	1.0	370.4	810	Bergen	1.0
361.4	830	Cardiff (5WA)	1.5	391	767	Toulouse		423	709	Notodden	0.7
384.6	780	London (2LO)	3.0	400	750	Mont de Marsan	3.0	434.8	600	Fredrikstad	1.1
400	750	Manchester		458	655	Paris (Ecole Sup., PTT)	3.0	448	670	Rjukan	1.5
405.4	740	*Plymouth (5PY)	0.2	477.7	628	Lyons (PTT)	1.0	461.5	650	Oslo	1.5
491.8	610	Glasgow (5SC)	1.2	1,080	277	Strasbourg (testing)		524	572	Forsgrund	1.0
500	600	Davenport EX		1,750	271	Radio Paris	3.0	566	530	Hamar	0.7
1,604	187	Aberdeen (2BD)	1.5	1,850	154	Radio Carthage (Tunis)	2	POLAND			
		Davenport (5XX)	25.0	2,650	113	Eiffel Tower (FL)	8.0	270.3	1,110	Lemberg (under construction)	10.0
AUSTRIA											
254.2	1,190	Linz (under construction)	0.5	37.65	7,966	Doberitz	3.0	344	870	Posen (Poznan)	1.3
272.7	1,100	Klagenfurt	1.5	204.1	7,170	Kaiserslautern	0.5	422	711	Cattowitz	10.0
277.8	1,080	Salzburg		236.2	1,270	Stettin	0.75	435	689	Wilno	1.5
294.1	1,020	Innsbruck	0.5	241.9	1,240	Muenster	1.5	566	530	Cracow	1.5
357.1	840	Graz	0.5	250	1,200	Gleitwitz	0.7	1,111	270	Warsaw (Varschava)	10.0
517.2	580	Vienna (Rosenhugel)	10.0	252.1	1,190	Dresden	0.75	ROUMANIA			
577	520	Vienna (Wien)	0.75	252.1	1,190	Cassel	0.7	187.4		Bucharest	2.0
BELGIUM											
508.5	590	Brussels (Radio-Belgique)	1.5	254.2	1,180	Kiel	0.7	675	444	Moscow (Popoff)	10.0
CZECHO-SLOVAKIA											
300	1,000	Bratislava	0.5	272.7	1,100	Danzig	0.75	1,000	300	Leningrad	10.0
348.9	860	Prague (Praha)	5.0	272.7	1,100	Breme	0.75	1,450	209	Moscow	
443	676	Brunn (Brno)	3.0	283	1,060	Cologne	4.0	1,700	176	Kharkov	4.0
1,870	266	Kosice (testing)	5	297	1,010	Hanover	0.7	SPAIN			
DENMARK											
337	890	Copenhagen (Kjobenhavn)	2.0	303	990	Nurnberg	4.0	310	967	Oviedo (EAJ10)	0.1
1,153.8	260	Kalundborg	7.0	322.6	930	Breslau	4.0	323.9	926	Almeria (EAJ18)	1.0
ESTHONIA											
408	735	Reval (Tallinn)	2.2	330	908	Koenigsberg	4.0	335	895	San Sebastian (EAJ8)	1.0
FINLAND											
375.9	798	Helsingfors (Helsinki)	1.8	365.8	820	Leipzig	4.0	335	895	Cartagena (EAJ16)	0.5
1,530		Jabits (testing shortly)	20	379.7	790	Stuttgart	4.0	344.8	870	Barcelona (EAJ1)	1.5
FRANCE											
37	8,108	Vitus (Paris)	2.0	396	757	Hamburg	4.0	375	800	Madrid (EAJ7)	3.0
39.5		Lyon (PTT)	10.0	400	750	Aachen	0.75	400	750	Madrid (Radio Espana, EAJ2)	1.0
61	4,018	Radio LL (Paris)	1.0	428.6	700	Frankfurt-Main	25.0	400	750	Bilbao (EAJ9)	0.5
158	1,899	Beziers	0.6	470	638	Langenberg	4.0	400	750	Cadiz (EAJ3)	0.5
200	1,500	Biarritz	0.25	483.9	620	Berlin	4.0	405	741	Salamanca (EAJ22)	0.55
230	1,304	Ste Etienne	0.25	535.7	560	Munich	4.0	434.5	600	Seville (EAJ5)	2.0
240	1,240	Nice	0.5	566	530	Augsburg	0.5	462	649	Barcelona (EAJ13)	2.0
237	1,205	Bordeaux (Radio Sud-Ouest)	2.0	577	520	Freiburg	0.75	260.9	1,150	Malmö	1.0
252.1	1,190	Montpellier	0.5	1,250	240	Koenigswusterhausen-Zeesen	40.0	476.7	720	Goteborg	8.0
257	1,170	Juan-les-Pins	0.5	1,800	167	Norddeich (KAV)	10.0	454.5	660	Stockholm	1.5
259	1,160	Toulouse		30.2	9,934	Hilversum (PCJJ)	25.0	515.6	550	Sundsvall	1.0
268	1,119	Strasbourg (SGF)	0.3	340.9	880	Huizen (until 5.40 p.m.)	4	720	416	Ostersund	2.0
				1,069	280	Hilversum (ANRO)	5.0	1,200	250	Boden	2.0
				1,950	153	Huizen	4	1,320	227	Motala	30.0
				1,950	154	Scheveningen-haven	2.5	SWITZERLAND			
				555.6	540	Budapest	3.0	411	730	Berne	1.5
				HUNGARY				588	510	Zurich	0.6
				ICELAND				680	441	Lausanne	0.6
				192		Akureyri	1.5	760	395	Geneva	0.5
				333.3	900	Reikjavik	1.0	1,000	300	Basle	0.25
				IRISH FREE STATE				1,230	243	Stamboul	7.0
				319.1	940	Dublin (2RN)	1.5	1,800	167	Angora (testing)	7.0

Standing room only!

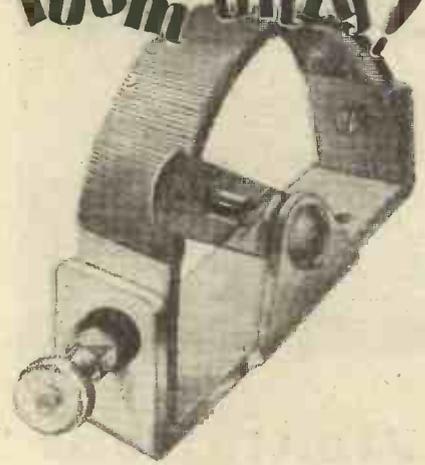

Your baseboard may be crowded. But there's room for the "Peerless Varistor." It stands up, prominent, easy to get at, but clear of complicated wiring.

Wound with finest quality resistance wire and fitted with a Phosphor-bronze adjustable arm that once set to the resistance for your valves, stays set.

Terminals are fitted in convenient positions. Five different styles—3, 6, 10, 15 and 20 ohms.

From all good dealers or direct.

Then fit PEERLESS VARISTOR

1/3

THE BEDFORD ELECTRICAL & RADIO CO., LIMITED
22 Campbell Rd., Bedford.

LONDON: 21 Bartlett's Bldgs., Holborn Circus, E.C.4.
GLASGOW: 113 St. Vincent Street, C.2.

MYSTERY WIRELESS SOS

WHEN the Italian steamship *Alcantara* was sunk with her crew of twenty-two, as the result of the collision with the Russian sailing ship *Tovarisch*, the Russian Captain sent out SOS signals. Soon afterwards the *Baron Douglas* came alongside and was informed of the disaster. As the Russian ship was in no danger the *Baron Douglas* went away, presumably in order to render assistance to the *Alcantara*. Of course, the *Tovarisch* received a number of other wireless messages asking the reason for the signals of distress. It was at this point that a disastrous confusion arose, for the Russian Captain gave the "SOS Clear" signal, although, as he

afterwards explained, this was only meant for his ship, but apparently other ships in his vicinity understood him to mean that there was no need for any assistance at all. Later the Russian Captain says he sent a message giving the place of the collision and stating that men of the *Alcantara* might be in the water.

Fortunately such occurrences as the above are very infrequent. Those who go down to the sea in ships have in wireless communication an ally that rarely lets them down.

"A.W." Solves Your Wireless Problems

"HARNESSING LIGHTNING TO BREAK UP ATOMS"

(Continued from page 375)



Plantations and Panels.

5. The last lap in the long journey.

NOW comes the last lap in the journey of the rubber which is to become a Resiston Panel. The long, thin sheets of pure rubber are now ready for ever to leave the land of their birth. The native tree tapper would see little resemblance in one of these sheets to the milky fluid he knew, but he would be more amazed to see what strength and what beauty is given to this self-same latex when, finally, it becomes a Resiston Panel.

Only the pick of the rubber ever finds its way to the Resiston factory. That is why Resiston has such sheer strength. Such lustrous beauty. Such perfect insulation. Why its colour is permanent. Why its dielectric constant is so low. If you want your Set to have the finest panel that ever was made, you will fit a Resiston Panel.

Resiston Panels come in 13 stock sizes in black and Mahogany-grained. From 6 in. x 9 in. in black, 3/5, to 8 in. x 30 in. Mahogany-grained 19/-.

RESISTON
PANELS

"24 hours Cut Panel Service"

Advt. American Hard Rubber Co., Ltd., 12a, Fore St., E. C.

2009

continuous work well-nigh impossible.

The most suitable place for thunderstorm investigation would have been the tropics. However, for obvious reasons, the three experimenters had to be content with a less distant place, viz., Monte Generoso, near Lugano, in Southern Switzerland, which of all those in Central Europe, by the particular frequency and intensity of its thunderstorms, is the most suitable. Moreover, the precipitous slopes of that mountain made it particularly suitable for the installation of antennae spanning a valley.

Voltage and Current

Preliminary tests—current and tension readings during several thunderstorms (made with a small experimental plant)—showed that only storms located immediately above the peak could supply the required energy. Whereas in normal weather the antenna tension was 3,000 volts, with a current intensity of 10.7 milliamperes, it would, during thunderstorms, rise to 600,000 volts, the current intensity, as gauged from the number of sparks per second and the capacity of the antenna, being of the order of several milliamperes. However, insulation losses in connection with these tests were considerable.

The comprehensive antenna system above referred to was therefore designed, comprising a network of large-meshed, pointed wire, 100 metres long by 4 metres wide, which at 80 metres high was suspended by a carrying cable traversing in a span of 760 metres the space between the extreme points of the ridge. Inasmuch as insulation against very high tensions, of course, raised difficulties of no common nature, and a magnitude never before faced in connection with any power plant previously installed, the co-operation of Messrs. Brown, Boveri & Co., of Mannheim, was gladly accepted. This firm supplied free of charge their steatite foot motor insulations, of which chains of 30 were provided at each end, thus affording sufficient insulation against 2.5 to 3 million volts continuous current. One-half of the carrying cable served as a discharging cable, carrying the electric charges on the antenna network to the measuring instruments installed below the place where the cable was least distant from the ground.

Corona Losses

Another problem to be solved was guarding against corona losses in the cable leading from the network to the measuring instruments. Hollow metal cylinders with very thin walls and decreasing diameters were therefore provided, surrounding the cable and touching each other like the components of a string of pearls. In fact, these cylinders proved extremely mobile and

behaved like a continuous tube surrounding the cable. A cable section 150 metres long was thus protected, beginning with a diameter of 5 cms. and progressively increasing to a terminal diameter of 75 cms. A static instrument was used to read the tension, while the distance of a spark gap at the same time allowed the actual minimum tension to be gauged.

All observations were made in a lightning-proof metal-coated cabin, whence the spark gap was controlled by means of a lever, the upper end of which could be approached towards the last corona protector. The maximum spark-gap distance was 4.5 metres, which was readily traversed, the sequence of sparks during thunderstorms being about one per second and remarkably constant. The minimum tension corresponding to 4.5 metres was found to be 1.7 million volts.

The installation not being completed before the end of August, there was only one chance of taking readings during an actual thunderstorm, when the tension of nearly 2 million volts being measured, the plant was shown to work well.

Further Experiments

There will be no difficulty in increasing the dimensions of the present installation and greater effects will be obtained. In fact, a thunderstorm field in such an arrangement is bound to yield the highest tensions obtainable.

Experiments will therefore be resumed this spring, it being believed that tensions actually sufficing for the breaking up of atoms may be then obtained.

At the same time, the experimenters have availed themselves of the past winter to design discharge tubes suitable for extreme tensions and which are to be used in connection with the forthcoming definite tests.

The Emergency Committee for Assisting Scientific Research (known as the *Notgemeinschaft der deutschen Wissenschaft*), an institution specially founded with the intention of promoting scientific work under present difficult economic conditions in Germany, supplied the means of undertaking these remarkable tests. The steel cable was supplied free of charge by the Cable Industry Co., Ltd., of Mannheim.

The United States National Air Transport Company have inaugurated a radio beacon service to guide planes flying over the air-mail route between New York and Chicago.

The Funktechnische Verein, Blumen-thalstr., of 19 Berlin W.57, is asking German radio enthusiasts to send in any old apparatus they can spare for the club members to hook up into sets for blind people too poor to buy sets for themselves.

CLEARTRON

VALVES sell on Merit

Users of Cleartron Valves expect from them a standard of reception second to none—and they are not disappointed. Although Cleartron Valves are inexpensive, they give reproduction of a strength and quality unsurpassed by any valve, irrespective of its price. Try them, prove their value, and economy.

ORDER FROM YOUR DEALER or, in case of difficulty, order direct (page 3d.) from

Sales Dept.,
CLEARTRON (1927) LTD.
21, Cumberland Street, Birmingham



FOR POWER
AND R.C.C.
AMPLIFN.

GENERAL PURPOSE


Valve.	Filament Volts	Filament Amps.	Impedance Ohms.	Amplification Factors.
CT10	3.8	0.1	15,000	7.5
CT10*	3.8	0.1	8,000	3.8
CT15	1.8-2.0	0.15	18,000	7.5
CT15*	2.0	0.3	5,000	3.5
CT215H†	2.0	0.15	100,000	45
CT25	5.0	0.25	10,000	9
CT25B†	5.0	0.25	20,000	20
CT25*	5.0	0.5	4,000	5

Power Valves are Marked*. Valve marked † are Special Valves for resonance capacity amplification.

SOLE DISTRIBUTORS IN GREATER LONDON
Selfridge & Co., Ltd., Oxford Street; Bon Marche, Brixton; Jones Bros., Bolsover; Quin & Ardens, Brixton; John Barrow, Finchley; Pratts, Peckham; Hollous, Peckham; Barratt, Clapham; Wm. Whiteley, Ltd., Westbourne Grove.

PROVINCIAL DISTRIBUTORS
Aberdare, Bucker & Phillips; Alderney, C. I. B. Martin; Ashburn, J. C. Lee & Son; Ayr, Alexander Stores; Birmingham, Radio Maintenance Service; H. F. Smith, Green & Co., Porter; Brighton, Rbl. Needham, Ltd.; Bradford, Passingham (Bradford), Ltd.; Bath, Maxims; Burnham-on-Sea, A. Trott; Boissover, S. J. Lambert; Bristol, Thomas & Stinchcombe; Brynmawr, Premier Wireless Co., W. A. Davies; Bishopscloke, G. Fryer; Bizleswade, L. Collins; Barrow-in-Furness, S. T. Whitaker; Barnley, E. Lawson; Byfleet, A. L. Kemp; Cardiff, A. Hide and Sons, Morris & Co.; Colwyn Bay, Carter & Hunt; Coventry, J. Bradbury; Cudford, A. L. Simper; Cowes, I.O.W., F. E. Dimisey; Chesham, J. Mead; Oswestry, Cycle Wireless Depot; Derby, Derby Wireless Co.; Darwen, Wraye Brothers; Eastleigh, A. E. Amos; Emsworth, T. Lee; Enfield, Wash, H. T. Mc. Farlane; Falkirk, Alexander Stores; Farnborough, H. T. Farley; Faversham, Wool; Fleetwood, Radio Service; Glasgow, London Radio Stores; Greenock, H. Russell & Co.; Giltach Gceh, W. T. Rees; Harrow, T. J. Lynch; Gt. Yarmouth, Donald Nobbs, Smith's Radio Stores; Grimsby, A. Allman; Hastings, C. P. Abraham; Belfast, Rtt. Patterson & Sons, Ltd.; Dublin, The Briscoe Importing Co., Ltd.; Huntingdon, Thurston & Thurston; Ipswich, S. Wilson; Jarvis Brook, C. C. Davis; Leeds, C. J. Hardy & Co., Ltd., London Radio Co., Ltd., F. Feldman; Liverpool, G. H. Lee & Co., Ltd., L. A. Wireless; Liversedge, Co-op. Society, Ltd.; Llanrha-ddedd, R. Owen; Luton, Wholesale Battery Co.; Lincoln, S. Woodhead; Lydney, L. Hughes; Letchworth, Elwood & Shaw; Leicester, Scientific Wireless Stores, Wathes & Co., Ltd., Birmingham Cycle Co.; Manchester, Themex Radio Co., J. E. Hulme, Universal Elec. Supply Co. (Manchester), Ltd.; Margate, T. Joyce; Middleton Junction, T. Ashton; Motherwell, Glasgow Cycle Co.; Northampton, Brice and Sons, Munin Brothers; Northwich, S. Ashworth; Nunston, H. Parker; Newbury, Edwards & Godding; Osett, P. Kitson; Paisley, J. Bryce & Co.; Peterborough, Thomsons, Ltd.; Penzance, Cornish Camera Co.; Peck, A. E. Ostick; Penzance, Thos. Matthews; Rea, A. B. Bull, Ltd., O. J. Lewis; Redcliffe, Thos. Holt; Rotherham, Shearid; Redditch, J. Dyer & Son; Ruabon, A. L. Roberts; St. Albans, A. J. Dorrell, Ltd.; Sheffield, Cole Brothers, E. A. Bezzard; Stockport and Bolton, Universal Elec. Supply Co. (Manchester), Ltd.; Sunderland, Jameson, Tennant's Wireless Co.; Swindon, G. Skinner; Sturminster Newton, A. B. Hallett; Stourbridge, L. Harold; Stafford, Radio Stores; Swansea, Milward & Son, Macowards; Torquay, J. Truran; Totnes, Ballwin's Garage; Walton, Trewins; Windsor, (Sleys); Worthing, W. Barker & Sons; Whitehaven, J. H. Borrindale; Workington, J. Wilkinson; Walsley, Chestnut Wireless Co.; Walsell, F. R. C. Bein; Ystad Mynach, Gwyn's Garage; Wolverhampton, H. Lloyd.

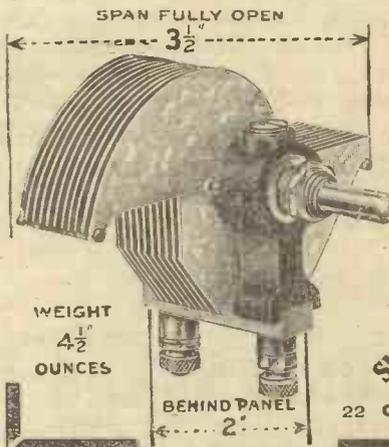PROVINCIAL RETAILERS ARE INVITED TO WRITE AT ONCE FOR LIBERAL TERMS



FORMO
"1928"
LOG CONDENSER
00035 **5/-** 0005
Absolutely the
SMALLEST, LIGHTEST, and most EFFICIENT
22 CRICKLEWOOD LANE, N.W.2
Phone: Hampstead, 1787

EELEX
TREBLE-DUTY TERMINALS
are a combination of W.O. and pillar terminals, with numerous improvements incorporated, and will hold securely, spade, plug, pin, eyes, and just bare wires in any position. Terminal parts are standard EELEX fittings, and can be used for other purposes. 36 varieties of indicating tops, and also 6 colours.
Write today for List J.A7 which contains details of all the Eelex Radio parts to:
J. J. EASTICK & SONS
EELEX HOUSE
118 Bunhill Row, Moorgate Street
London, E.C.1
Terminal T2LC 4d. each. With Plain Top 3d. each (T2LN)

Readers should note

that the special transformer recommended for the "Q" Coil Three described in this issue is the POWQUIP Orchestral Transformer. The matchless ORCHESTRAL Model Transformer (as illustrated) stands foremost amongst other makes on the market. It reproduces without the slightest suspicion of distortion. Each instrument comprising the orchestra is most clearly defined. Weight 42 oz. Height 2 1/2 in. Width 3 1/2 in. Depth 2 1/2 in. Price **22/6**



Write to the address below for full particulars

This Paper recommends the
- POWQUIP -
ORCHESTRAL TRANSFORMER
for the
"Q" - COIL THREE

THE POWER EQUIPMENT COMPANY LTD. Kingsbury Works, The Hyde, Hendon, N.W.9

OTHER POWQUIP TRANSFORMERS

It can be safely claimed that the STANDARD Model Transformer (illustrated here) has positively no equal at the price. Recently designed, its amplification and tone have benefited to the extent of 25 per cent. Weight 12 oz. Height 3 1/2 in. Width 2 1/2 in. Depth 1 1/2 in. Price **10/6**

This Popular Manchester Model embodies all the features of the Standard type, but is larger and of heavier design. Its amplification is exceptionally good, whilst clearness of speech and tone is remarkable. Weight 14 oz. Height 3 1/2 in. Width 2 1/2 in. Depth 2 1/2 in. Price **12/6**



Make certain it is POWQUIP

RADIOGRAMS



ON March 11, the B.B.C. stations and the most important Continental studios will broadcast a programme of compositions by Belgian musicians.

On the occasion of the second annual banquet of the Company of Master Mariners, which takes place at the Mansion House on March 21, the B.B.C. proposes to relay to 2LO and 5XX the speeches made by the Prince of Wales and the Prime Minister, Mr. Stanley Baldwin.

On March 27, Sir Henry Wood will go to Bristol to conduct a symphony concert which will be relayed to the Cardiff station. The orchestra will consist of the station orchestra and the Bristol Symphony Orchestra, the soloists being Miss Flora Woodman and Mr. Maurice Cole.

For the evening of March 21, the London studio promises a Sullivan concert, to which will contribute the Wireless Chorus, supported by the 2LO Wireless Orchestra. John Ansell will be the conductor. Selections from *Patience*, *The Yeoman of the Guard*, and *The Mikado* will be included in the programme.

A new series of light programmes, entitled "Noises Off," comprising an entirely novel method of presenting vaudeville, will be given by Cardiff on March 24. The entertainment includes a sketch, *The Painters*, songs at the piano, a new vocal act, and Jacque Thomas in "Cymric Comedy Cameos."

Cecil Lewis, who thrilled many listeners

with his cinematographic radio-view *Pursuit* some weeks ago, has written a new play, entitled *The Night Fighters*. It is to be broadcast for the first time from 5GB on March 24.

Sir Oliver Lodge will give his second half-hour talk on "Scientists I Have Known" from 5GB on March 22.

For the production of the musical comedy *The Gipsy Princess*, to be broadcast from 2LO, 5GB, and other stations on March 8, a particularly strong cast has been engaged. It will include Murri Moncrieff (as Niblo, the cabaret manager), Maggie Teyte, Robert Chingell, Miriam Ferris, Dorothy Monkman, Leslie Sarony, Ewart Scott, Paul England, Eric Derwent, and Frank Denton.

On March 17 (St. Patrick's Day) Belfast will give the first performance of a new play, entitled *St. Patrick*, a narrative of the life of Ireland's saint, written by F. K. Fahy. The second part of the programme consists of Irish variety and will be shared by Glasgow. The evening will conclude with a relay of a carillon from St. Patrick's Cathedral, at Armagh.

The centenary of the birth of the famous Norwegian dramatist, Henrik Ibsen, is to be commemorated by the Belfast station by a broadcast of his *Peer Gynt*, with Irene Rooke and Robert Speaight in the leading rôles.

According to the latest statistics, Japan now possesses 500,000 registered broadcast

listeners, of which 340,000 listen to the Tokio station, 99,000 to Osaka, and 41,000 to Nagoya.


Under the call letters EATH, the Radio Laboratory of the Electro-Technical Institute of Vienna regularly broadcasts gramophone records every Monday and Thursday at 9.30 p.m. G.M.T. simultaneously on 37 and 620 metres. In the near future experiments will be carried out in the transmission of pictures.

Within a few months Rumania will possess another broadcasting station, for the wireless telegraphy transmitter at Temesvar is being converted to radio telephony. Experiments have been carried out recently between 3 and 7 p.m. G.M.T. on a wavelength of 2,800 metres with a power of some two kilowatts. For the purposes of tests, gramophone records are broadcast, all announcements being made in the Rumanian, Hungarian, German, French, and English languages.

The Italian State Railways have equipped fourteen of their main stations throughout the country with wireless receivers so that they may receive broadcast time signals. Since the adoption of this scheme considerable improvement has been made in the running of the trains to advertised schedules.

Some original prizes are offered for a competition organised by the Eiffel Tower broadcasting station; they include three flats, small bachelor apartments of three rooms, rent free, for a period of three years. The idea is a novel one, and it is expected that the number of entries will constitute a record.

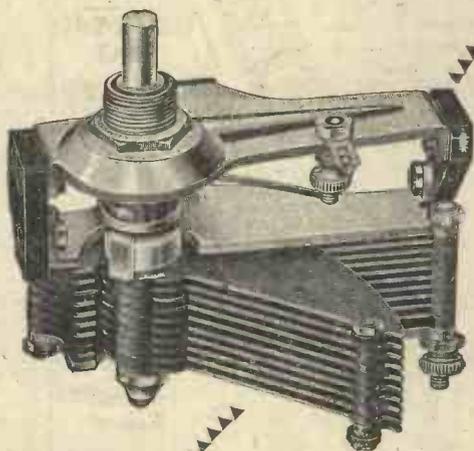In planning their afternoon talks for the next few weeks, the Scottish stations have considered their rural women listeners in particular. A number of talks on "Women's Part in Village Life" have been arranged for Wednesday afternoons.



"UTILITY" S.L.F. CONDENSERS —with Aluminium or Brass Vanes

Embodying all the unique features of our popular Low Loss Square Law Condensers—ball bearing spindles, Low Loss characteristics, and strict attention to detail.

A Condenser you can depend on for correct proportional frequency reading with a given inductance—and a compact-size job, too. Prices include 4" Knobs and Dials. Our "Utility" Micro Dial—tuning ratio 70 to 1—is fitted to the Vernier pattern

Whenever you are requiring a Condenser, study the "Utility" List—you may have one with pleasure on request—before making a purchase. Low-Loss, Neutrodyne, Logarithmic Condensers for all purposes—and all guaranteed!

Obtainable from your local dealer or direct from the makers:—

WILKINS & WRIGHT LTD., "Utility" Works, Kenyon St., Birmingham.

PRICES—ALUMINIUM

Cap.	Ref. No.	Price	Price with Vernier
.0005	W174	9/6	15/-
.0003	W175	8/6	14/-
.0002	W176	7/6	13/-

BRASS

.0005	W177	11/6	17/-
.0003	W178	10/6	16/-
.0002	W179	10/-	15/6

A WONDERFUL 3-VALVE LOUD-SPEAKER SET

The Saxon 3-Valve Loud-speaker Set is the finest 3-valve set that money can buy. Very few 4-valve sets can equal the performance of the SAXON 3, either for purity, volume, range or selectivity. 48 stations at our Works (more than half at good loud-speaker strength), Daventry on loud-speaker 1,200 miles away, 20 stations in Devonshire, 35 in Torquay, and over 20 stations on loud-speaker in the Orkney Islands have actually been received.

All latest improvements are incorporated—no coils are required, as the new SAXON all-wave tuner covers all wave-lengths from 200 to 2,000 metres by merely turning a knob.

Easily built by any beginner in two hours. All panels are drilled, and most of the components assembled ready for wiring. No soldering required. 24-page instruction book and wiring diagram 3d. post free.

SAXON RADIO Co. (Dept. A.W.), South Shore, BLACKPOOL.



OAK OR MAHOGANY CABINET SPEAKER

The Whiteley Boneham oak or mahogany cabinet speakers are designed to give true utterance to the broadcast instrument or voice. The cone unit embodied in these speakers entirely eliminates rattle and distortion.

Price £3

The range of Whiteley Boneham Speakers include:

- Patent All Bakelite Cabinet model £4 4s.
- Junior Model 20 in. x 10 in. x 4 in. £2 10s.

The W.B. ANTI-PHONIC VALVE HOLDER


A valve holder that ensures perfect freedom from vibratory noises and valve shocks and losses. The valve holder that Cosmor applied for the "Melody Maker."

At the popular price of **1/9**



WHITELEY BONEHAM & CO., LTD., Nottingham Rd., Mansfield, Notts.

PARMEKO High output smoothing chokes

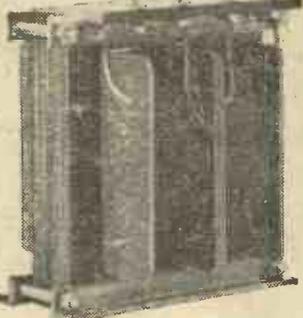

These chokes are designed for working in conjunction with our large Eliminator Transformers.

Wound in two halves so that half may be used in each leg of the smoothing circuit if desired. The windings are of heavy gauge wire and the choke will safely carry 100 milliamps without saturation. Price **£2**

Large power transformers

specially designed for driving Moving Coil Speakers, large output Eliminators and Amplifiers.

These large Parmeko Transformers are very strong and robust, extremely efficient, and have a low no-load current. A Terminal panel is provided so that all connections can be conveniently taken. Suitable for directly screwing down to a board. Price **£3:10s.**

We manufacture Transformers to give any voltage and output and for all purposes. We shall be pleased to quote you for any type of Transformer, Choke or Rectifying Apparatus.

PARTRIDGE & MEE LTD.
12, Belvoir Street, LEICESTER

MAGNAVOX

NOTICE

MAGNAVOX Dynamic Speaker Units (moving-coil) are manufactured under the following patents:

BRITISH PATENTS	AMERICAN PATENTS
No. 197,836, May 24, 1923	No. 1,051,113, Jan. 21, 1913
Others pending.	" 1,088,283, Feb. 24, 1914
Foreign Patents issued and pending.	" 1,266,988, May 21, 1918
	" 1,444,524, Feb. 6, 1923
	" 1,448,279, Mar. 13, 1923
	" 1,524,349, Jan. 13, 1925
	" 1,579,392, April 6, 1926
	" 1,582,417, April 27, 1926

Others applied for and pending.

Purchasers of these Units through our exclusive Sales Representatives: **The ROTHERMEL CORPORATION, LIMITED, 24-26 Maddox Street, London, W.1,** are advised that they will be fully protected against any infringement actions.

WARNING

The Magnavox Company serves notice that infringers of the above British patent—manufacturers of moving-coil speakers assembled or unassembled embodying any exclusive Magnavox features—will be vigorously prosecuted.

THE MAGNAVOX COMPANY
OAKLAND, CALIFORNIA, U.S.A.

Better reception with less trouble

The NEW "HOVEY" Patent COLLAPSIBLE Spiral Aerial

Take Wireless with you Everywhere

The vagaries of the English climate will never interfere with your reception once you fit a H"OV" EY AERIAL. The sales of H"OV" EY Aerials are going up by thousands through the recommendations of delighted users who had splendid TROUBLE-FREE RECEPTION throughout the recent storms.

YOU CAN FORGET GALES AND STORMS IF YOU FIT A H"OV" EY

All good dealers sell H"OV" EY Aerials. Order locally or send direct to the manufacturers.

THE HOVEY AERIAL CO.
10, Red Lion Passage, LONDON, W.C.1



2/6

OTHER POPULAR TYPES
5/6
H"OV" EY Super Flat
Size 12 ft. x 4 1/2 in.

2/6
H"OV" EY Standard Round
Indoor Size 12 ft. x 2 1/2 in. diameter

THE FRAME AERIAL AND SELECTIVITY

(Continued from page 385)

Model
No. 55

FIRST CLASS
IN
QUALITY
FIRST CLASS
IN
APPEARANCE

—so we labelled it "Blue Spot"
The "Ideal" Blue Spot Filter Cone loud-speaker is a beautiful piece of workmanship and is made in a handsome old bronze finish in a high decorative design, and the reproduction that it gives is an absolute revelation to those who have not heard the "Ideal" Filter Cone. There is an absolute absence of those false resonances and blurrings which are usually associated with a cone-type loud-speaker; this is achieved owing to the very special construction of the Filter Cone. This model is equipped with a special adjustable driving unit, so that if necessary 90 volts H.T. can be used.

Ask your Radio dealer to demonstrate the "Ideal" Filter Cone in comparison with any other cone loud-speaker whatever its price, then you will decide that there is no need to pay more than the price of the "Ideal" Filter Cone.

£3 3s. 0d.

ASK FOR THE

BLUE SPOT
FILTER
CONE SPEAKER

In case of difficulty in obtaining, write direct to—

F. A. HUGHES & Co., Ltd.
204-206, Great Portland St., W.1

Telephone: Museum 8630 (3 lines).
Telegrams: Distancing, Westlo, London.
Manchester Office: 185 Princess Street.
Telephone: City 3320.

When the frame is placed "broadside on" to the transmitter in this way, it is said to be in the position of minimum or zero response.

On the other hand, if the frame is swung about the side AB as pivot, so that it occupies the dotted-line position, the direction of the wave-front being as before, then the largest possible number of lines of magnetic force thread through the windings, consequently the induced voltage across the windings reaches a "peak" value and signal strength will be loudest.

In this case when the windings are arranged end on towards the transmitter, the frame is said to be in the position of maximum pick up.

The variation of signal strength at intermediate positions, i.e., as the frame is gradually swung from the position AC shown in plan in Fig. 2 to the position A' C', and so on round the circle, is shown shaded in the so-called polar diagram of Fig. 3.

Maximum Pick-up

It will be seen that there are two positions of maximum pick-up, one when the frame lies along the line A' C', and another when it has turned through an angle of 180 degrees. Similarly there are two "minimum" positions, one along the line AC and the other 180 degrees later. The two minimum points coincide in the centre of the polar diagram.

So far we have considered the action of the magnetic flux only, and we have seen that it affords a sufficient clue as to why signal strength should be loudest in one position of the frame and zero in another.

If we also take into account the action of the electric field it will be found to be quite consistent with the results given by the magnetic field. In the minimum or full-line position shown in Fig. 1, both the uprights AB and CD act as miniature elevated aerials so far as pick-up is concerned.

They are both situated at the same distance from the transmitter and they will, therefore, both pick up the same amount of energy, the induced voltages being in phase. All the vertical windings are, however, in series with each other, so that upwardly directed voltages induced in AB occur simultaneously with upwardly directed voltages in CD. These mutually counter-balance each other and so have a zero or minimum resultant effect in the receiver.

It must, however, be borne in mind that these voltages exist, and if they are given a chance to manifest their presence they will do so. Meanwhile theoretically we must consider them as in a state of balance.

Maximum Position

In the maximum or dotted-line position

of Fig. 1, the vertical sides AB and C'D' are no longer equidistant from the transmitter. Accordingly the induced voltages, due to the electric component of the received waves being slightly out of phase, have a net resultant value. This produces a voltage across the windings, which co-operates with that due to the magnetic field to create maximum signal strength in the receiver.

Consider, however, what happens when the two sides of the frame are connected to the grid and filament of a receiving valve as shown in Fig. 4. In the first place any signal response in the receiver must be due to the voltage existing across the condenser c, i.e., across the two ends of the frame aerial.

As we have seen, in the minimum or zero position, the induced voltages due to the electric field are mutually in opposition and should, therefore, balance out. Accordingly there should be no signals in the receiver.

Leakage Paths

The introduction of the valve, however, opens out several possible leakage paths from the frame to earth for the "balanced" voltages existing in the frame. In the first place there is the capacity between the accumulator and earth, then there is the capacity between grid and filament, and finally that between the grid and plate, all shown in dotted lines.

In all probability the capacity between the accumulator and earth will be a path of less impedance than the others. Accordingly some of the charge due to the electric pick-up on the lower plates of the condenser c leaks away to earth at a greater rate than the charge on the upper plates. This sets up a voltage difference across the condenser which destroys the theoretical balance of the minimum position. As a result signals appear where none should be heard.

In direction-finding equipment it is essential to secure a high degree of accuracy; a small auxiliary condenser may be inserted across the grid of the amplifier to earth, and be adjusted to balance the capacity between the accumulator and earth.

In this way the leakage paths from each side of the tuning condenser c are made equal, so that the residual or signal voltage reflects the clear-cut directional response of the frame.

As a further precaution a secondary coupling may be inserted between the frame and the amplifier input. The centre point on the frame windings can then be directly earthed, so that currents due to the so-called "vertical" effect of the aerial are not transferred through the valve to the telephones.

In the arrangement shown in Fig. 5,

the centre point of the frame winding is earthed at c to eliminate the vertical or direct pick-up effect, whilst the input between the grid and filament is across only half the frame windings, i.e., between the point c and terminal d.

A balancing condenser n is inserted between the plate and the upper terminal a of the frame as shown. This stabilises the valve by neutralising the effect of the interelectrode capacities indicated in Fig. 4. With such an arrangement the directional effect of a frame aerial can be made clear-cut and its selective action is increased accordingly.

M. A. L.

ELLEN TERRY'S WIRELESS BIRTHDAY

ON the eightieth anniversary of her birthday, Dame Ellen Terry was able to listen-in on a portable wireless receiver—sent down to her by the B.B.C.—to an hour's broadcast tribute to her greatness as an actress. In this way she shared a birthday hour with all the millions of her admirers who are also wireless listeners.

The "world's greetings" were spoken through the microphone at 2LO by Sir Johnston Forbes-Robertson. As it was considered inadvisable for Dame Ellen Terry to use her voice to reply to these

greetings, Miss Edith Craig read the message for her mother. "I am very grateful for this lovely posy of words you have sent me for my birthday. I am very grateful to everyone who has thought of me to-day."

In her peaceful surroundings at Watlington, Kent, this frail old lady was thus able to conjure up voices of the past through the medium of broadcasting.

Under the call-sign OHK2, the Radio Austria Company of Vienna has installed a short-wave transmitter in that city. Tests are now being carried out on a wavelength of 70 metres.

LOEWE RADIO

The Famous
LOEWE
High Vacuum
Resistances
and
LOEWE
High Vacuum
Block Condensers



Should be installed in every wireless receiving set.
They are
Free from atmospheric influences.
Moisture and dust-proof.
Free from losses.
Fully guaranteed.
Delivery from stock.
Ask for illustrated leaflet.
LOEWE RADIO COMPANY LIMITED,
4, Fountainay Road, Tottenham, London, N.15.
Telephone: Tottenham 2076.

GIGANTIC SUCCESS OF THE REDUCED PRICES P. R. VALVES

FINEST LONDON MADE

L.F., H.F., R.C. & DETECTOR in 2 & 4 VOLTS

NOW ONLY OLD PRICE 8/6

3/6

TRADE ENQUIRIES INVITED



THEY WILL SAVE YOU POUNDS

NO BETTER CAN BE BOUGHT ANYWHERE

THE WORLD'S BEST VALVE
THE WORLD'S BEST VALUE

P.R. SUPER DULL EMITTER VALVES challenge comparison with ANY OTHER VALVE ON THE MARKET. Don't imagine for one moment that they are rubbish—such as bankrupt stocks or foreign valves. On the contrary, they are the latest product of one of the finest equipped factories in London. Years of experiment and research are behind every P.R. VALVE, and before leaving the Works every valve passes the most exhaustive tests. Experimenters can have every confidence in P.R. VALVES. It was only by the lucky discovery of new elements and new methods of manufacture that the P.R. VALVE at 3/6 became an established fact. Hitherto it had been sold at 8/6. THE NEW PRICE BRINGS A GOOD VALVE WITHIN THE REACH OF EVERYBODY.

Tell us what your circuit is. We can help you to select the right valve. Remember that R.C. Valves require at least 110 volts and can take more with advantage.

Type	Fil. Vts.	Fil. Amp.	Imp. Ohms.	Amp. Fac.	M/C	
PR 1	2	.06	35,000	15	.4	H.F.
PR 2	2	.06	25,000	12	.43	Det.
PR 3	2	.06	18,000	8	.44	L.F.
PR 4	2	.06	120,000	40	.33	R.C.
PR 5	2	.15	40,000	20	.5	H.F.
PR 6	2	.15	30,000	15	.5	Det.
PR 7	2	.15	12,000	6	.5	L.F.
PR 8	4	.06	23,000	15	.65	H.F.
PR 9	4	.06	19,000	9.5	.5	Det.
PR10	4	.06	11,000	6	.55	L.F.
PR11	4	.06	120,000	40	.33	R.C.
Power Valves	2V.	.20	6,000	5	.82	P.
	4V.	.15	4,000	4	1.0	P.

7/6 Each. Post and Packing 4d.

3/6

Post and Packing 4d.

- 2 VALVES FOR 6/9
Post and packing 6d.
- 3 VALVES FOR 10/-
Post and packing 6d.
- 4 VALVES FOR 13/-
Post and packing 9d.

THEY CAN'T BE BEATEN

Phone your order: CENTRAL 0181
Pay the Postman C.O.D.
WRITE, PHONE OR CALL.

Sets of Valves made up to any requirements.
MATCHED VALVES for intermediate stages
specially selected 1/- per set extra.

OUR GUARANTEE

All valves despatched by return of post under guarantee of Money Back in Full if not satisfied. All valves are carefully packed and breakages replaced.

P. R. VALVES

Dept. 27, (Opposite Post Office Tube)
17 PATERNOSTER SQUARE,
NEWGATE STREET, LONDON, E.C.4

TUNEWELL COILS

Again specially recommended in this issue

PRICES:

25,	35,	50,	75	each	1/6
30,	40,	60,	100,	"	1/8
125,	150,	2/3	175	2/6	
200,	225,	2/9	250	3/3	

Centre tapped, 9d. each extra
Double " 1/- " "

We can specially recommend Tunewells to give maximum efficiency when used as an alternative to Special Coils, in Cossor Melody Maker and Mullard Master Three Circuits

MAKERS:

TURNER & CO., 54 Station Road, London, N.11

For Perfect RECEPTION

Patent Pending
No. 31135127.

Make a Cone Loud-speaker of wonderful tone and volume with this handsome ready-for-use FABRIC CONE at small cost. No cutting or sticking needed. The scientifically made H"OV"EV RIDGED Cone is supplied ready for fitting. Gives equally good results on small and high powered sets. Handsome Metallic Finish, Gold, Silver or Bronze. Height of peak 4 in., Diam. 12 1/2 in. Unequaled for fidelity and volume. Do not accept worthless imitations. Get the genuine H"OV"EV. Order TO-DAY from your dealer or direct from

The H"OV"EV SEAMLESS FABRIC RIDGED CONE

RIDGED CONE COMPANY, LTD.,
10, Red Lion Passage, London, W.C.1



THE "2-WAVE 2"

(Continued from page 374)

valve table, can be inserted and the various batteries connected up.

Tuning is a very simple process, and in the initial tests this should be done with

2-volt Valves for the "2-wave 2"		
Make	Detector	L.F.
B.T.H.	B210L	B215P
Cosmos	SP16/G	SP18/RR
Cossor	210HF	Stentor 2
Ediswan	HF210	PV2
Marconi	DEL210	DEP { 215 240
Mullard	PM1HF	PM { 2 252
Osram	DEL210	DEP { 215 240
Six-Sixty. ...	SS210HF	SS215P

the reaction dial set at zero, and the small auxiliary wave-changing knob pushed in. Then with the rheostat turned on, it should be possible to tune in the local station without difficulty, and when this has been done, the reaction dial can be "advanced" until the volume is sufficient. Minor adjustments of H.T. and grid bias com-

plete the preliminary tests. If the receiver is to be used by non-technical listeners the dial reading for the local station and Daventry 5XX should be calibrated and then all that will have to be done on subsequent occasions, is to set the dials at the pre-determined positions and push in the knob on the reaction for high waves dial, or pull it out for low waves.

"Amateur Wireless and Electricians." Price Threepence. Published on Thursdays and bearing the date of Saturday immediately following. Post free to any part of the world: 3 months, 4s. 6d.; 6 months, 8s. 9d.; 12 months, 17s. 6d. Postal Orders, Post Office Orders, or Cheques should be made payable to "Bernard Jones Publications, Ltd."

General Correspondence is to be brief and written on one side of the paper only. All sketches and drawings to be on separate sheets. Contributions are always welcome, will be promptly considered, and if used will be paid for. Queries should be addressed to the Editor, and the conditions printed at the head of "Our Information Bureau" should be closely observed. Communications should be addressed, according to their nature, to The Editor, The Advertisement Manager, or the Publisher, "Amateur Wireless," 58-61 Fetter Lane, London, E.C.4.

COMPLETE SETS, LOUD SPEAKERS COMPONENTS, Etc.

Supplied for all circuits, including the Mullard Master 3, Cossor Melody Maker, also the new circuits featured in this issue.

EVERYTHING WIRELESS ON EASY PAYMENT TERMS

Send list of requirements, and best monthly terms will be quoted by return.

THE P.D.P. CO., LTD. (Dept. A.W.)
41, GREAT TOWER STREET, LONDON, E.C.3

C.D.M.

IMPORTANT REDUCTIONS

C.D.M. COMPONENTS ARE NOT SWORN AT BY THEIR USERS. THEY ARE SWORN BY AS BEING THE BEST VALUE FOR MONEY COMPONENTS OBTAINABLE.

WELL KNOWN SET MANUFACTURERS ARE USING THESE COMPONENTS IN THEIR PRODUCTS WITH COMPLETE SATISFACTION—YOU SHOULD ALSO INCORPORATE C.D.M. FIXED CONDENSERS, FIXED CONDENSERS AND GRID LEAK COMBINED, ALSO C.D.M. H.F. CHOKES IN ALL YOUR SETS.

BY TEST - THE BEST!



Patent No. 275803

Fixed Condensers .00005 to .002 .. 1/8 each.
.0025 to .006 .. 2/-
Combined Condenser and Grid Leak 2/-
H.F. Chokes, 4/- and 5/-. The 4/- type is clip-in pattern.

WATCH FOR OTHER COMPONENTS NOW BEING DESIGNED

Send for Catalogue of our guaranteed products.

If your dealer does not stock, write direct to the sole manufacturer:

C. D. MELHUISH
8 GT. SUTTON STREET, GOSWELL ROAD
E.C.1

Phone: Clerkenwell 7494

SURE-A-LITE
the better battery

Sure-a-lite cells are larger than those in other H.T. batteries. Therefore Sure-a-lite give greater efficiency, unequalled recuperating powers, long life and silent working.

We make no attempt to cut our prices; you get full value for money from Sure-a-lite batteries and you will continue to do so.

The new Sure-a-lite batteries are now on sale. They incorporate a grid-bias battery and are supplied sealed and with a deep dust-proof cover.

Rely on the battery experts—and ask your radio dealer—he knows!

SURE-A-LITE

BRINGS MOST IN — GIVES MOST OUT
REGISTERED TRADE MARK

"Supra" 66 volt 7/11
100 volt 14/3
"Giant" 60 volt 10/5
100 volt 17/6

These incorporate Grid Bias tapped every 1 1/2 v. up to 0 v.



THE BATTERY COMPANY,
92 HURST STREET,
BIRMINGHAM

LISENIN

PRE-SET RESISTOR
(REGISTERED DESIGN)

Specified by the designer of the MELODY MAKER. Made with the maximum capacity of 5, 7, 10, 30 and 50 ohms. 5 ohms suitable for all COSSOR valves for MELODY MAKER.



1/9 each
Postage 2d.

Refuse substitutes
COSSOR MELODY MAKER
cells wound to specification 6/- each; Formers only 2/-.
Postage 4d.

POSITIVE GRIP TERMINALS
Plugs and Sockets complete 41d.
Spade Ends 4d.
Wander Plugs (as used in the Melody Maker) ... 2d.

Obtainable of your dealer. If he cannot supply give us his name, but refuse substitutes
THE LISEIN WIRELESS CO.,
1 EDGWARE ROAD, LONDON, W.2



TAYLORADIO

H. F. CHOKE

4/6 Designed and built for the utmost efficiency. Functions perfectly on all wavelengths. Maximum air space, minimum losses. Please send for list
W. W. TAYLOR, 33 Furnival St., E.C.4

DIGBY'S CABINETS

Write for New 16-page Catalogue

Please note new address: Phone: Clissold 5453.
F. DIGBY, 9 THE OVAL, HACKNEY ROAD, LONDON, E.2.

WIRELESS IN PARLIAMENT



From Our Own Correspondent

MR. MACQUISTEN asked the Postmaster-General whether the British Broadcasting Corporation was authorised to exercise discrimination between representatives of the medical profession and other practitioners who did not belong to that profession.

Sir W. Mitchell-Thomson said that the British Broadcasting Corporation was entirely responsible for the selection of the persons engaged to broadcast talks or lectures, and he did not propose to interfere with the Corporation's discretion in this matter.

Television

Mr. Malone inquired whether the Postmaster-General was taking any steps to keep in touch with recent developments in television, and whether he had considered the application of existing radio legislation to this invention.

Sir W. Mitchell-Thomson said that the answer to both parts of the question was in the affirmative. His technical advisers considered that television was still only in the experimental stage.

P.O. Certificates

Mr. Briant asked the Postmaster-General if he would state under what regulation, if any, a natural-born British subject was not eligible for the Post Office certificate of proficiency in radio telegraphy, and why the fact of being the son of an allied alien debarred him from the occupation of wireless operator in British ships.

Sir W. Mitchell-Thomson replied that the International Radio-telegraph Regulations prescribed that a person employed as a wireless operator in a ship must hold a certificate issued by the Government to which the ship was subject. It had been the general rule in this country since 1919 that such a certificate should be issued only to a natural-born British subject whose father was also a natural-born British subject. This rule was made after consultation with all the Government Departments concerned, and was considered necessary in view of the special character of the duties of an operator.

Ripault's Self-regenerative H.T. Battery.—In our test report in No. 298 on this battery we gave the name of the makers as the Ripault's Engineering Co. We have been advised, however, that Ripaults, Ltd., is the correct name. In the title we also omitted the words "self-regenerative." The recuperative qualities of the battery are, as we pointed out, a prominent feature.

BRITAIN'S "FAVOURITE 2"
66 "FAVOURITE 3"

No. 1 LIST OF COMPONENTS

Ormond .0005 and .00025 Log Mid-line Condensers, 12/- and 13/- each; 7-ohm Panel Rheostats, 2/-; 3 B.R. Valve-holders at 1/8; 2 Single Coil-holders; .0003 Fixed and Series Clip and Dubilier 2-meg. Leak, 5/-; H.F. Choke 5/-; R.C. Dubilier Unit, 7/-; R.I. Transformer, 25/-; 7 Terminals at 9d. (5/3); 2 Strips 4 by 2.

Total **81/6**. Sent post free for **74/6** nett
16 by 8 PANELS, BEST GRADE "A," 3/11 nett.
16 x 8 x 10" AMERICAN CABINETS (OAK), HINGED LID AND BASEBOARD. SPECIAL PRICE WITH ABOVE KIT OF PARTS ONLY, 15/- NETT. Post 1/- for cabinet.

2nd SELECTION FOR ABOVE

Two Log Mid-line Condensers, with S.M. Dials. Panel Rheostat, 7-ohm. 3 Anti-microphonic Valve-holders. 2 Single Coil Stands. 1 Lissen .0003, with Grid Leak and Series Clip. 1 H.F. Choke. Lissen R.C. Unit. L.F. Transformer (R.I. & Varley). 2 Strips 4 by 2. 7 Terminals, with Name Tabs.

POST FREE **59/6**

SEE CABINETS, ETC., ABOVE

LISSEN IMPORTANT.

Valve-Holders, 1/-; Fixed Con., 1/-, 1/6; Leaks, 1/-; Switches, 1/6, 2/6; Latest 2-way Cam Vernier, 4/6; Rheostats, 2/6; B.B., 1/6; Lissenola, 13/6; L.F. Transformers, 8/6; 100 v. H.T., 12/11; 60 v. H.T., 7/11; Coils, 60X, 6/4; 250 X, 9/9.

We stock Igranite, Climax, Ever Ready, Heleson, Siemens, Formo Ferranti, Wearie, Ormond, J.B. Benjamin, Lotus, Mullard, Dubilier, Lissen, Lewcos, Utility, Magnum, Peto-Scott, Peerless, Burndey, Eye, Marconi, McMichael, Cosmos, Carborundum, R.I. Varley, Gambrell, Brown's Sterling, Amplicon—in fact, everything it is possible to stock.

BULLPHONE UNITS 15/- EACH

DARIO VALVES
(Genuine Radio Micro)
Best in the World.
BIVOLT 2-v. 05. 7/6;
Loud Speaker Valve 10/9;
R.C. .05 1.8, 7/6; 3.5
.05, 7/6; Loud Speaker
Valve, 10/9; 3.5 R.C. .07,
7/6. Post 6d. each.

DR. NESPER
Adjustable
PHONES ... **10/6**

LOUD
SPEAKER
UNIT ... **10/6**

DE LUXE
PHONES ... **7/11**

CALLERS

Please make out your list for orders over 20/- if requiring component parts for any set, and we will give you a fixed inclusive price.

WE ARE OPEN


ALL DAY SATURDAY
ALL DAY THURSDAY
ALL DAY EVERY DAY
Hours 9 a.m. to 8 p.m.
Sat. 9 a.m. to 9 p.m.
Sunday morning 11-1

EXTRAORDINARY OFFER

D. and 2 L.F. Circuit

Illustration shows the assembled set.

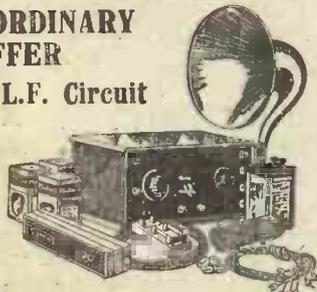For Local, 5 GB, 5 XX, and Continental Stations.



PARTS FOR ABOVE SET

2-Valve Components - 35/-
3-Valve Components - 42/-

Baseboard, wire, screws free.

OAK CABINET 14" x 7" and Panel 13/6

Ditto " 12" x 8" and Panel 12/6

H.T. Batteries, 100 v., 8/11

D.E. Valves, 5/11, 6/11; Power, 7/11

2-volt L.T., 4/6, 5/6, 8/6

Loud Speakers, 15/11 Coils, 1/- and 2/- each

These prices are to purchasers of the

Kit of Parts ONLY.

We supply the parts. You can make it in

2 hours; Wiring Diagram Free with parts. Carriage, extra.

BRITAIN'S "FAVOURITE 2"
Don't worry about paying on the weekly system—
TRY OUR CASH PRICE!

Ebonite Panel. 0005 Ormond S.L.F. and S.M. Dial, Igranite 5 ohms, 2-way geared with 4 Terminals, long handle, 2 Lotus Valve Holders, .0003 and series clip, 2 meg. Leak, B.T.H. or R.I. and Varley L.F. Transformer, .0005 Fixed, Strip 4 x 2, 8 marked Terminals, G.B. Clips, 2 Wander Plugs, Square Wire.

THE ABOVE LOT net cash post free - 45/-
With Lissen L.F. or Telsen "Ace" - 37/6

HANDSOME AMERICAN TYPE CABINET with baseboard, hinged lid all parts are enclosed. List Price 13/11. MAHOGANY POLISHED OR OAK.

YOU CAN BUY FOR 7/11 with 45/- Kit.
YOU CAN BUY FOR 8/11 with 37/6 Kit.
2/- extra if Cabinet to go by post or rail.

MUSIC CHARMER KIT (W.M.)

See Free Gift at Bottom
.0005 Raymond Condenser (AS USED IN SET), 7/6; 7 ohm. Panel Rheostat .0001 Reaction (Ormond) 4/-; Single Coil Holder, 8d.; .0003 Fixed 2-meg. Leak and Series Clip, 3/-; 3 Anti-Microphonic Valve Holders, 5/3; R.C.C. Unit, 7/-; L.F. Transformer (Igranite), 16/-; H.F. Choke (Burne-Jones), 7/6.

Nett Total 52/11

FREE WITH ABOVE Terminal Strip, 7 Marked Terminals, Ebonite Tube, Wander Plugs, Spade Tags, Rubber Flex and Pointer, and Oak Panel, 16 x 8. Carriage 1/-.

GABINETS

Large stocks of really useful cabinets kept or made to order. Solid oak, American type, hinged lid, baseboard.

- 12 x 8 x 0 ... 11/6
- 14 x 7 x 9 ... 13/11
- 16 x 8 x 9 ... 16/11
- 18 x 8 x 9 ... 19/11
- 20 x 8 x 9 ... 22/6
- 21 x 7 x 9 ... 25/-
- 24 x 7 x 9 ... 27/6

Carriage 1/6

IT IS IMPOSSIBLE TO ADVERTISE ALL THE WIRELESS PARTS NOW ON SALE, BUT IF YOU WANT THEM

RAYMOND'S FIRST I

BE SURE YOU VISIT THE Bargain Window. New 100 page Catalogue. Profusely illustrated. Price 1/- Post FREE (allowed off first 10/- order).

COSSOR, MULLARD, COSMOS, B.T.H., EDISWAN, and SIX-SIXTY valves stocked.

MULLARD MASTER THREE

No solder—only 20 wires to connect. COMPLETE SET OF COMPONENTS. 2 Term strips 2 1/2 x 2, Lewcos Base, 2 J.B. condensers, Climax H.F. choke, Master Three Coil, 3 Pye Valve Holders, Magnum Brackets, 4 Terminals, Spade Terminals, Wander Plugs, Bulgin Switch, R.I. Unit, R.I.L.F. Transformer, Mullard .0003, 2 meg. Leak, Flex, Screws, &c.

And Three Mullard P.M. Valves
ABOVE KIT £6 17 6

FREE GRID BIAS, 9 VOLTS
100 VOLT H.T. (BRITISH)
with above ALUMINIUM PANEL, 18" x 7"

Handsome Oak Cabinet for Master Three, 15/11 with kit of parts, carriage 2/-.

SET OF THE SEASON.

COSSOR MELODY MAKER

Components for same as specified.

Blue Print **£4 10 0 KIT Free**
2 Ormond .0005; 2 Do. S.M. Dials; 6 T.C.C. Condensers, .001, .002, two .003, .0001, 2 mfd.; 2 Grid Lk. Clips, B.B.; 1 Var. B.B. Rheostat; 3 Dubilier Leaks, 25, 3, 4 meg.; 3 Lotus V.H.; 1 Ferranti A.F.; 2 Panel Switches; 1 Cossor Melody Wound Coil; Terminals, Name Tabs, Glazite, 9-v. Grid Bias, Screws, etc.

NOTE.

Drilled High-grade 21 x 7 Polished Panel, with Radion Strip, FREE with above kit.

NOTE.

Handsome American Cabinets hinged lid with baseboard for 16/11 with above kit only. Or in mahogany 20/-, carriage extra.

COSSOR VALVES FOR ABOVE.

210 D	410 HF	610 HF
210 RC	410 RC	610 RC
210 P	410 P	610 P

10/8 EACH
10/6 EACH
12/8 EACH

EDISWAN NEW THREESOME

List of Components.

Three Coupling Units, Tubular Fixed Condenser, Multi-flex Cable and Plug, .0003 Variable with S.M. Dial, 2-way Geared Holder, Wire, Red and Black Flex.

The lot post free 42/- nett.

EBONITE PANEL 2/6 The two with above 5 Ply Baseboard kit only
Ediswan Valves, 10/6; Power, 12/6 each.

K. RAYMOND

27 & 28a, LISLE STREET, LONDON, W.O.2

Come to Leicester Square Tube.

IMPORTANT.—This address is at the back of Daly's Theatre.

Be sure it is Raymond's. Phone; Gerrard 4637

WE ARE OPEN: ALL DAY SATURDAY

ALL DAY THURSDAY, ALL DAY EVERY DAY
Hours 9 a.m. to 8 p.m. Sunday 11 to 1. Sat. 9 a.m. to 9 p.m.

A FOOL-PROOF VALVE HOLDER at last!



No mistakes with the TRIX Anti-microphonic Valve Holder! The guiding groove and red anode indicator prevent all possibility of error when inserting the valve. Moulded throughout in genuine bakelite; positive stop top and bottom and ample, but not excessive movement. It is absolutely the best to be obtained at the price.

Another excellent model is the TRIX Red Leg Rigid Valve Holder with its Red Indicating Anode Socket and terminals for easy connection.



Price 1/- each. TESTED COMPONENTS
ERIC J. LEVER (TRIX), LTD.
 33 CLERKENWELL GREEN, E.C.1
 Telephone: Clerkenwell 3014/5

THE FAMOUS


DIX-ONEMETER

Still leads the way
A £10 Tester for 55/-



Anode Converters, 400 volts, £4 10s. Charging Valve Bargains, B.T.H., Cossor, etc., A.C. to D.C. 50 milliamps at 200 volts to 1,200 volts, cost 35/-, Sale 8/6, guaranteed Switches, 250 volts, 6d. 8-way Lucas for Phone or Speaker circuits, 3/6. S.K. Amplifier Micro. Units, 2,000 ohms, 13/-. Buttons, 2/-. Western Electric Loud Speakers, 15/-. Violins, 25/-. Sullivan Headphones, 3/-. Single Phone, 1/6. Rubber Ear Pads, 4d. per pair. Gramo Pick-ups, 21/-. Gyroscopes, 15/-. Mains Smoothing Chokes, 1/-. 2-mid. Condensers, 2/6. Remote Relays, 10/-. Pear-Pushes, 6d. Sterling 1-valve Amplifiers, 22/6. 2-v. T.B. Amplifiers, 32/6. Inert Fuller, 1/3 cells, 1/-. Thermo A.C. Meters 250 m/a, 15/-. 4-range B21 Testers, A.C. or D.C. 200 m/a, 4 amps, 6 v., 120 v., 40/-. Large Steel Horseshoe Magnets for Coil Speakers, 3/6. Bargain Sale of Transmitters and Receivers, 1 to 6 Valves now on. Send 4d. for our Sept. edition of illus. catalogue. It will save £4.

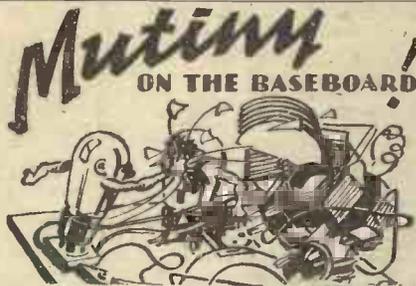ELECTRADIX RADIOS
 218 Upper Thames Street, E.C.4



When your set gets out of hand, take the one vital step that ensures the perfect balance so necessary to secure harmonious, distortionless reception—fit a Sifam Meter and tune with your eyes on the dial. FREE leaflet "Distortion" from—(Dept. A), S.I.F.A.M., 10a Page Street, Westminster, S.W.1



The WHITELINE VALVE HOLDER

"Mechanically and electrically perfect."



Bowyer-Lowe 2/3

TAYLEX WET H.T. BATTERIES

New Prices: Jars 1/3. Sacs 1/2. Zincs 11d. Sample doz. (18 volts) complete with bands and electrolyte 4/3, post 9d. Sample unit 6d. 16 page booklet free. Bargain list free. **AMPLIFIERS: 1 VALVE 19/-, 2 VALVE 30/-, 2 VALVE ALL-STATION SET 24.**
A. TAYLOR, 57 Studley Road, Stockwell, LONDON

WORTH WRITING FOR

THE Fuller Accumulator Co. (1926), Ltd., of Woodland Works, Chadwell Heath, Essex, have sent us a selection of leaflets and booklets dealing with their accumulators. The company makes various types for house, train, and automobile lighting, or general purposes, and also for wireless. Various types of cells—Leclanché, etc., are also made.

The Edison Swan Electric Co., of 123-125 Queen Victoria Street, E.C.4, have issued a new price list of motor-car lamp bulbs. We have also received from this firm an interesting accumulator catalogue.

TRADE NOTES

THE London Electric Wire Co. and Smiths, Ltd., held their third annual dance at the Whitehall Rooms, Hotel Metropole, on February 17. Over 200 employees and friends attended the function.

Philips Lamps, Ltd., announce that as from March 1 the price of their H.T. supply unit for D.C. mains (type 508) will be reduced from £5 to £3 17s. 6d.

Wembley Wireless Society Meeting

ON February 17, Mr. J. H. Reyner gave a talk on the new tuning coil which he has evolved.

Many members asked questions; this led on to various topics of an extremely interesting nature, and all were able to follow Mr. Reyner's very lucid explanations. Mr. Reyner then went on to describe a simple set which can be attached to the ordinary broadcast receiver in order to bring in the various American and Continental short-wave stations. Judging by the number of members who were seen busy with pencil and paper, this proved to be a very fascinating topic.

The meeting closed with a hearty vote of thanks to Mr. Reyner.

The "Ridley Short-wave Three"

IN their advertisement, which appeared in the issue in which this receiver was described (No. 298), Burndep Wireless, Ltd., stated that a 250,000-ohm resistance was required. A 30,000-ohm resistance was, of course, actually used. Burndep's price for this is 8s. 6d. In the bottom line of the coil chart for the receiver a typographical error occurred. Coils 25 and 15 are stated to cover the 25- to 150-metres wave band. This should read 75 to 150 metres.

In the news bulletin the other night it was announced that Metropolitan Vickers, Ltd., and Ferranti, Ltd., are sharing the contract, amounting to over a quarter million pounds, for the new Scottish electrification scheme. The Ferranti Co.'s share is thirteen transformers each weighing over 95 tons! Congratulations to the firms that have secured this big contract.

BLUEPRINTS

Full-size Blueprints, each one being a photographic contact print, from the draughtsman's original design, and produced on stout paper, are now available of the following sets.

	No.	Price.	Post free
ONE-VALVE SETS			
Alpha One*	W.M.26	1 0	2 3
Reinartz Plug-in One-valver	A.W. 46	1 0	1 0
The Dynaflex (One-valver)	A.W. 60	1 0	1 0
Constant-coupled One	A.W. 65	1 0	1 0
Long Range Hartley One	W.M.54	1 0	1 0
Economy One	A.W. 71	1 0	1 0
Loud-speaker Special One	A.W. 78	1 0	1 0
TWO-VALVE SETS			
All-wave Two-valver	A.W. 15	1 0	1 0
Empire Short-wave Two	A.W. 28	1 0	1 0
"Next-step" Receiver	A.W. 34	1 0	1 0
Girdle Two*	W.M.30	2 0	1 0
Centre-tap Two	A.W. 42	1 0	1 0
Mains-fed Two	W.M.37	1 0	1 0
The Rover Two	A.W. 53	1 0	1 0
British Broadcast Two	W.M.44	1 0	1 0
General Purpose Two	A.W. 55	1 0	1 0
The "Yule" Two	A.W. 59	1 0	1 0
The 30s. Two-valver	A.W. 61	1 0	1 0
Economical Two	A.W. 66	1 0	1 0
Two-programme Two	W.M.56	1 0	1 0
Britain's "Favourite Two" and copy of "A.W."	A.W. 74	0 4	1 0
Home and Abroad Two	A.W. 77	1 0	1 0
Two-wave Two	A.W. 83	1 0	1 0
THREE-VALVE SETS			
Purity Three-valver	A.W. 35	1 0	1 0
A Modern Tuned-anode Three	A.W. 33	1 0	1 0
A "Mains" Three-valver	W.M.34	1 0	1 0
Screened-grid Three	W.M.21	1 0	1 0
"Simpler Wireless" Special Three-valver	A.W. 44	1 0	1 0
"Home Station" Three	A.W. 45	1 0	1 0
The "Economy" Three	A.W. 48	1 0	1 0
Five-guinea Three	W.M.29	1 0	1 0
Dominions Short-wave Three	W.M.39	1 0	1 0
Short-wave Three	A.W. 50	1 0	1 0
The Ether Searcher Three	A.W. 52	1 0	1 0
Three Continent Three	A.W. 54	1 0	1 0
Tuned-anode Three for the Mains (D.C.)	W.M.43	1 0	1 0
The Standard Three	A.W. 56	1 0	1 0
Straight-line Three	A.W. 60	1 0	1 0
Screened-grid Short-waver	W.M.51	1 0	1 0
Hartley DX Three	A.W. 63	1 0	1 0
Metropolitan Three	W.M.48	1 0	1 0
Everyday Three	W.M.52	1 0	1 0
Britain's "Favourite Three" and copy of "A.W."	A.W. 72	0 4	1 0
Broadcast Three	A.W. 76	1 0	1 0
Music Charming	W.M.60	1 0	1 0
Ridley Short-wave Three	A.W. 80	1 0	1 0
Selectus Three	A.W. 81	1 0	1 0
"Q" Coil Three	A.W. 84	1 0	1 0
THREE-FOUR-VALVE SETS			
A Tuned-anode Three-four	A.W. 49	1 0	1 0
Concord Three-four	W.M.45	1 0	1 0
Trapped Three-four	W.M.61	1 0	1 0
FOUR-VALVE SETS			
Revelation Four	W.M.24	1 0	1 0
"A.W." Gramo Radio	A.W. 40	1 0	1 0
All-purpose Four	A.W. 43	1 0	1 0
All-wave Roberts Four and copy of "A.W."	A.W. 47	0 7	1 0
C.T. Four	A.W. 58	1 0	1 0
Simplicity Four	W.M.49	1 0	1 0
Astral Four	W.M.53	1 0	1 0
"Simpler Wireless" Four	A.W. 70	1 0	1 0
FIVE-VALVE SETS			
Exhibition Five	W.M.33	1 0	1 0
Phoenix Five	W.M.42	1 0	1 0
1928 Five	W.M.46	1 0	1 0
All-the-world Five	W.M.63	1 0	1 0
SIX-VALVE SETS			
Nomad Six	W.M.31	1 0	1 0
Short-wave Super-six	A.W. 67	1 0	1 0
SEVEN-VALVE SETS			
Simpladyne Seven (Super-het.)	W.M.22	1 0	1 0
AMPLIFIERS			
Two-valve D.C. Mains Amplifier	W.M.16	1 0	1 0
Range Extender (H.F. Amplifying Unit)	W.M.38	1 0	1 0
True-tone Amplifier	W.M.47	1 0	1 0
Utility Two-valve Amplifier	A.W. 68	1 0	1 0
One-valve L.F. Amplifier	A.W. 79	1 0	1 0
Screened-grid H.F. One	A.W. 75	1 0	1 0
An "Add-on" H.F. Unit	A.W. 82	1 0	1 0
PORTABLE SETS			
Springtime Portable (Two-valver)	W.M.12	1 0	1 0
Counterside Four	W.M.17	1 0	1 0
Motorists' Portable Four-valver	A.W. 14	1 0	1 0
Handy Three	W.M.27	1 0	1 0
Holiday Portable (three-valver)	A.W. 32	1 0	1 0
Club Portable (three-valver)	A.W. 30	1 0	1 0
CRYSTAL SETS			
Crystal Set for the R.C. Enthusiast	W.M.13	0	0
Two-programme Crystal Set	W.M.25	0	0
Half-Hour Crystal Set	W.M.28	0	0
Centre-tap Crystal Set	W.M.50	0	0
Super Crystal Receiver	A.W. 64	0	0
MISCELLANEOUS			
Made-to-measure Wave-trap	A.W. 19	0	0
Volume Control Unit	W.M.40	0	0
Battery Eliminator for A.C. Mains	W.M.41	1	1
Battery Eliminator for D.C. Mains	W.M.59	1	1
"Simpler Wireless" Rectifying Unit	A.W. 62	1	1
A.C. Mains Adaptor (for any "Simpler Wireless" Set)	W.M.57	1	1
H.T. Supply from A.C. Mains	A.W. 73	1	1
Cone Loud-speaker	W.M.55	1	1
Moving-coil Loud-speaker	W.M.58	1	1
* With a copy of "Wireless Magazine" complete.			

Send a Postal Order to-day to BLUEPRINT SERVICE AMATEUR WIRELESS 59-61 Fetter Lane London, E.C.



"ONE GOOD TURN
DESERVES ANOTHER"

N.C.C.384.



MIS GOOD DEED

"DECKOREM" RADIO STATION LOG

LOG THE CALL SIGN, WAVELENGTH, NAME AND DIAL SETTINGS OF THE WORLD'S RADIO STATIONS

A. F. BULGIN & CO.
Radio Manufacturers
9008 CURSTON STREET,
CHANCERY LANE, LONDON, E.C.4

RADIO PANELS

7x 6,	1/3
8x 6,	2/1
10x 8,	2/4
10x 9,	3/-
12x 10,	4/-
14x 7,	2/2
16x 8,	3/2
18x 7,	3/2



9x 6,	1/7
11x 8,	2/3
12x 8,	2/6
12x 9,	2/10
14x 10,	3/5
16x 9,	3/6
21x 7,	3/7
24x 7,	4/-

1/2 in. thick,
Post Free.

Money-back guarantee that each and all Panels are free from surface leakage. Megger test Infinity.

CROXSONIA CO., 10 South St., Moorgate, E.C.2


Phone: Clerkenwell 7853

Agents: John Henry Smith, 139 Anlaby Road, Hull.
L. H. Helyar, 82 Chamberlin Road, Norwich.
A. Stredwick & Co., 27 The Market, Chatham.
Boynnton & Co., Ltd., 34 Bradford Street, Birmingham.

THE LORIOSTAT

For perfect filament control.

1 way	2/-
2 "	3/9
3 "	5/6
4 "	7/3
5 "	9/-
6 "	10/9

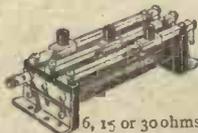

6, 15 or 30 ohms

As used in numerous "Amateur Wireless" receivers

A multiple unit superseding the fixed Resistor. Can be used in any circuit to perfectly and independently control any number of valves. For downright efficiency use a LORIOSTAT in your set.

A. W. STAPLETON

19a, Lorrimore Buildings, Lorrimore Street,
Walworth, S.E.17 Phone: Rodney 3869

REPAIRS—TWELVE MONTHS GUARANTEE—accompanies all our repairs. Any make of L.F. Transformer, Loud-speaker or Headphones. Repaired and despatched within 48 hours. 4/- Post Free. Terms to Trade

SERVICE DEPT.:
TRANSFORMER REPAIR COMPANY
214 HIGH ST. COLLIER'S WOOD, LONDON: S.W. 19

The right place for the
Watmel
H.F. CHOKE

Double-silk covered wire cross-wound in four balanced sections, giving low capacity, constant impedance, small external field. Windings fully protected. Mounted on Bakelite base n.p. terminals. Greatly improves the Cosor "Melody Maker" when connected in place of wire No. 28. Also when used in "S. 20 Express" and other circuits.

Write for particulars stating requirements for coil drive loud-speakers.

WATMEL WIRELESS CO., LTD.
Imperial Works, High Street, Edgware, Middlesex

"SWITCH ON AND OFF FROM ANYWHERE"

(Continued from page 386)

by the relay is in the neighbourhood of .2 ampere.

The relay having been constructed and wired up as shown in Fig. 1, the counter-weight is adjusted so that the copper contacts are just lifted clear of the cups when the armature is not attracted to the magnet. The armature is gently raised with one finger, and the copper contacts adjusted until they just reach the bottom of the cups and a bolt is inserted through the baseboard to act as a stop for the rocker. A similar stop is fixed to prevent the undue movement of the rocker in an upward direction.

These adjustments having been made, the effect of switching on the current from the local battery may be tried. The rocker should tilt smartly. If it fails to tilt, the armature is too far away from the magnets, and the screw on the contact post must be tightened up to push the armature towards the magnets. This adjustment may necessitate the readjustment of the rocker contacts, but this is easily accomplished. This operating satisfactorily, the cups in the ebonite may be filled with clean dry mercury. Closing the switch, the lamp beneath the switch will light up, the armature will be attracted to the electro-magnets of the bell movement, and the rocker will tilt, plunging the copper contacts into the mercury cups and completing the H.T. and L.T. circuits, thus putting the set into operation.

It will be noticed from Fig. 5 that both the H.T. and the L.T. circuits are broken where they are connected together. This obviates the danger of burning out the valves through a wrong connection, such as might occur if both poles of the H.T. battery were connected to the relay. In conclusion, it might be mentioned that the relay constructed by the writer has given entire satisfaction.

You cannot afford
NOT to buy

VOLTRON VALVES

VOLTRON Co., Ltd., Ponders End

"TROMBA" THE WET H.T.

Small Capacity Large Capacity
SACS 1/4 ZINCS 5d. doz. SACS 2/3 ZINCS 10d. doz.

JARS for either size 1/2 doz. Postage extra.
90 v. for 2 valves 18/6, 125 v. for 5 valves 38/7.
Any voltage to order. NO EXTRAS. CARRIAGE PAID.
1/2d. brings booklet, 6d. a cell 1/- full range of samples.

TROMBA ELECTRICAL CO. (Dept. D.)
13 High Road, Kilburn, N.W.6. Phone: Maida Vale 1669

EASY TERMS

Send Particulars of your Requirement to
THE WOOLLRIDGE RADIO Co. LTD.
RADIO COMPONENTS DEPT.
17 & 22 LISLE ST.
W.C.2

PREPAID ADVERTISEMENTS.

Advertisements under this head are charged **THREEPENCE PER WORD**, minimum charge **THREE SHILLINGS.**

DEPOSIT SYSTEM

As the Publishers cannot accept responsibility for the bona fides of advertisers in this publication, they have introduced a system of deposit which it is recommended should be adopted by readers when dealing with persons with whom they are unacquainted. It is here explained.

Intending purchasers should forward to the Publishers the amount of the purchase money of the article advertised. This will be acknowledged to both the Depositor and the Vendor, whose names and addresses must necessarily be given. The Deposit is retained until advice is received of the completion of the purchase, or of the article having been returned to and accepted by the Vendor. In addition to the amount of the Deposit, a Fee of 6d. for sums of £1 and under, and 1s. for amounts in excess of £1, to cover postage, etc., must be remitted at the same time. In cases of persons not resident within the United Kingdom, double fees are charged.

The amount of the Deposit and Fee must be remitted by Postal Order or Registered Letter (Cheques cannot be accepted), addressed to

"AMATEUR WIRELESS,"
ADVERTISEMENT DEPARTMENT,
58/61, FETTER LANE, LONDON, E.C.4

HOME BATTERY CHARGERS for alternating or direct current Charges both high and low tension Accumulators. Prices from 30/- Send for illustrated list. Runbsken Magneto Works, Ardwick, Manchester, or 240 Deansgate; London, 39 Victoria Street, S.W.1.

PERTINAX PANELS

SUPER BAKELITE BOARD

PRICES:

	Nat.	Col.
UNBREAKABLE UNFADEABLE		
7x14	4/4	5/3
7x18	5/4	6/4
7x21	6/3	7/6
8x12	4/2	5/-
8x20	6/8	8/3
8x26	8/8	11/-
8x30	10/6	12/2
	3/16" Thick.	
7/12	3/2	4/-
	1/8" Thick.	

Made in the following colours—natural brown, black walnut and mahogany. Natural brown 1d. per square inch. Other surfaces 1d. per square inch. Send postal order to GEO. L. SCOTT & CO., LTD., 69 Fleet Street, London, E.C.4. Money back if not satisfied.

D-XELLENT!

DX COILS

From 1/- DX COILS, LTD., London, E.8

EASY PAYMENTS

We specialise in the supply of All Wireless Goods (Components, Sets and Accessories of any make) on the Easy Payment system—10% down—balance spread over 10 months.

EFFICIENT SERVICE
Send list of requirements to—
LONDON RADIO SUPPLY CO.,
11 OAT LANE, LONDON, E.C.2 Telephone: City 1977

A.C. Mains Problems **D.C. Mains Problems**

Comprehensive Four Catalogue price

A. W. KNIGHT & CO., LTD.
180 Tower Bridge Road, LONDON, S.E.1

THE LITTLE CELLS THAT SATISFY

Eton Primary H.T. Battery, Pl Porous Pot Cells, S1 and S2 Sac Cells. All complete for assembly.

1-cell	6-cell	12-cell	20-cell
Pl 6d.	3/3	5/9	14/-
S1 6d.	3/-	5/3	12/-
S2 4d.	2/6	3/10	9/3

Send 1/2d. stamp for booklet giving full particulars to—
THE ETON GLASS BATTERY CO.
46 ST. MARY'S ROAD - LEYTON - E.10

Amateur Wireless


Available until Saturday,
MAR. 17th, 1928

NO MORE JACK TROUBLES

Now you can eliminate the old, messy soldering troubles when fixing jacks and switches. The famous Lotus Jacks and Switches are being made with terminals instead of soldering tags. The terminal makes as good a permanent connection as the most expert soldering job.

Lotus Jacks and Switches are made of finest bakelite, with nickel silver springs and pure silver contacts. To establish reliable connections in any set you make, choose Lotus Jacks and Switches. They occupy the minimum space—only 1 1/4 in. behind the panel.

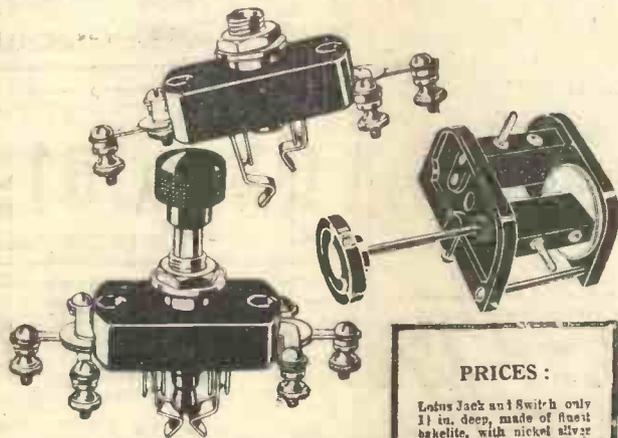The Lotus Coil-holder holds the heaviest coil in position. The moving block cannot fall. Prevents fading away of volume. Vernier movement reduces speed of moving-coil block by eight times. For left or right hand.



LOTUS JACKS · SWITCHES · PLUGS

Made by the makers of the famous Lotus Remote Control and the Lotus Buoyancy Valve Holder

PRICES :
 Lotus Jack and Switch only 1 1/2 in. deep, made of finest bakelite, with nickel silver springs and pure silver contacts. With terminals. Jack No. 3, 2/6; others from 2/- to 3/-. Jack Switch No. 8, 4/-; others from 2/6.
 Lotus Jack Plug. Spring sleeve fitting supplied. Can be used with any jack. Bakelite mouldings, nickel-plated brass parts. Price 2/-.
 Lotus Coil-holder, 2-wire, for outside panel mounting, 7/-; 3-way, 12/6. For inside baseboard mounting, with 6-in. handle, 8/-; 3-way, 12/6.

GARNETT, WHITELEY & Co., Ltd.
 Broadgreen Road, Liverpool

Lewcos Coils for all modern circuits

We are now making Coils for the **MASTER THREE.** Details upon request.

Patent No 277876.

Supplied in the following types:

- Split Primary Transformer.
- Split Secondary Transformers.
- Reinartz Transformer.
- Split Secondary Tapped Primary.
- Aerial Coil.



Binocular Coils are the latest Lewcos development in six-pin Coils. They are interchangeable with the popular types and can be used in a standard Lewcos Screen, although for use in multi-stage receivers they are sufficiently fieldless without screening. All dealers can obtain them for you. Full particulars and prices gladly sent on request.

THE LONDON ELECTRIC WIRE CO. & SMITHS, LTD.,
 Playhouse Yard, Golden Lane, London, E.C.1.


LEWCOS

(Regd. Trade Mark)

Binocular Coils

Mention of "Amateur Wireless" to Advertisers will Ensure Prompt Attention

YOUR FRIENDS WILL CONGRATULATE YOU!

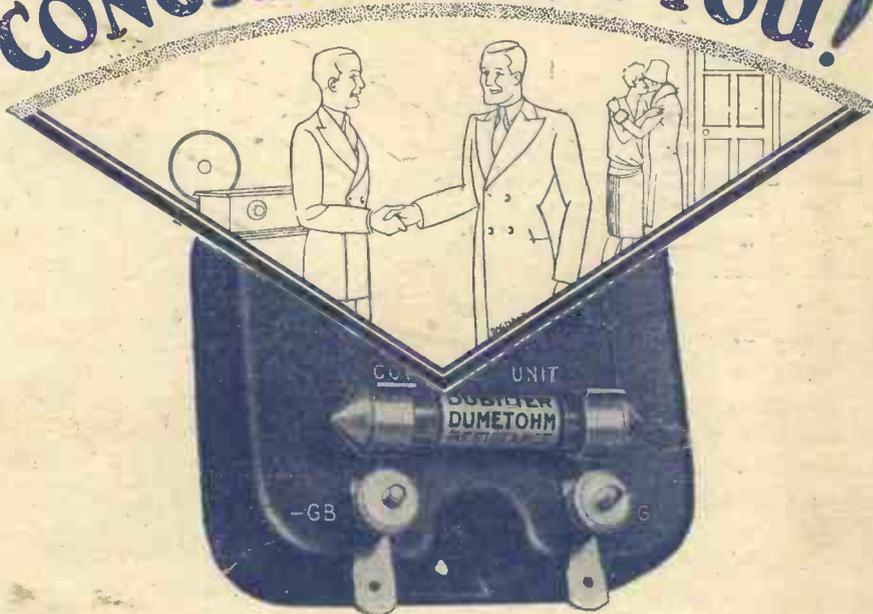

—on the improved performance of your set; on its remarkably increased clarity of reception with yet sufficient volume: meanwhile they might wonder at the cause. They would be astonished if you told them—that it was due to your having fitted a Dubilier R.C. Coupling Unit to your set.

Some may tell you they have tried Resistance Capacity Coupling as the recommended means of obtaining purer amplification, but with a disappointing decrease in volume. Yet the fault lies not in the method—mostly it emanates from the various components in the set having been carelessly selected.



Thousands are now being delighted by the purer reproduction, combined with adequate volume, which their sets have given since they installed the Dubilier R.C. Coupling Unit—proof enough of the supremacy of the Dumetohm for R.C. Coupling.

The Dubilier R.C. Unit will take Dumetohms of various values to suit your particular requirements, an advantage second only to that of price; for this efficient component costs no more than 7/-.



Advt. of The Dubilier Condenser Company (1925), Ltd., Ducon Works, North Acton, London, W.3. © 125

Specified for "A.W." Circuits in this issue.

Dubilier R.C. Coupling Unit. Complete with 2 "Dumetohms." Price 7/-



Dubilier Mica Condenser. Type 610. .0002 mfd., each 2/6 .0003 mfd., each 2/6



"Dumetohm" 2-megohm. Each 2/6

Whatever circuit you follow and whether the set you build is for the purpose of pleasure or experiment, remember

"Dubilier Built is Better Built"