

THE COMING SUPER-HET—AND WHAT YOU WILL FIND IN IT

Amateur Wireless

and
Radiovision

PRACTICAL
SHORT-WAVE
HINTS & TIPS



Every
Thursday

3^d

Vol. XXI. No. 541

Saturday, October 22, 1932

TO-DAY'S BEST AERIAL?

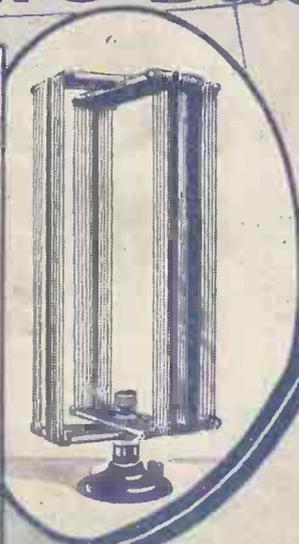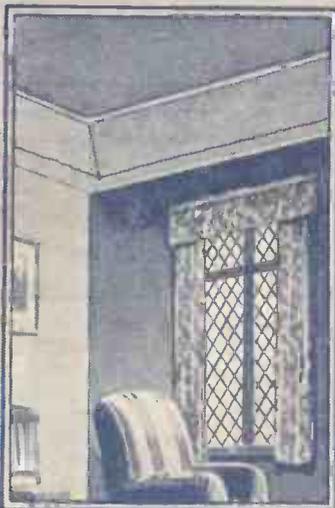

*In the
Supplement:*


The
A·B·C
of

DETECTION AND AMPLIFICATION

AND
MANY
STAR
FEATURES

Registered at the G.P.O. as a Newspaper

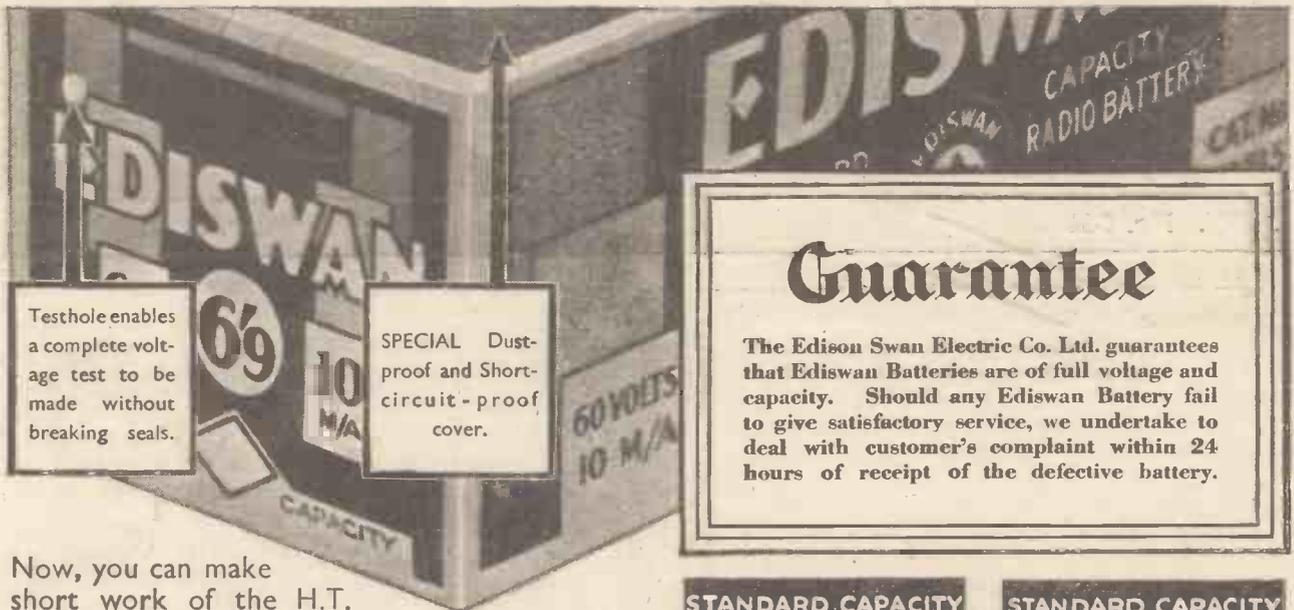**"MAINTAIN THE HIGH STANDARD
that CHARACTERISES ALL EDISWAN
PRODUCTS" —** *says the "Wireless World," reporting on the
performance of Ediswan H.T. Batteries.*



Now, you can make short work of the H.T. problem. This tribute from the "Wireless World"—the "blue book" of the radio enthusiast—is all that is needed to confirm the absolute reliability of Ediswan H.T. batteries. Every Ediswan battery is now **GUARANTEED** against failure to give absolutely satisfactory service. Every single cell has to pass numerous tests before it leaves the factory. Special precautions are taken to ensure perfect insulation between cells. Never before has there been a battery which you could try with greater confidence, with such positive assurance that you will get long life and good service.

All good radio dealers sell . . .

EDISWAN **Guaranteed**
RADIO H.T. BATTERIES

THE EDISON SWAN ELECTRIC CO. LTD.



PONDERS END, MIDDLESEX

B.175

STANDARD CAPACITY
60 6'9
VOLTS

STANDARD CAPACITY
120 13'
VOLTS

9 v. grid bias **1/-** **108** v. grid bias **12/-** incorporating **12/-** Standard Capacity. Where the anode current required does not exceed 10 M/a these batteries will give highly satisfactory service. If super-power valves are used, the super-capacity type should be used. **Super Capacity.** These batteries have twice the capacity of the standard type and, owing to their large reserve of power, last nearly three times as long when used as replacements to standard capacity batteries.

Send for your **FREE** copy of "How to get the most out of your H.T. Battery." Full of useful data, hints and tips.

To Ensure Speedy Delivery, Mention "A.W." to Advertisers



A NEW SET OR A RENEWED SET at a fraction of the cost

Perhaps your radio reception is on the downward path. Fewer stations; less volume; worse tone. Your set is not to blame. Your set is as up-to-date to-day as it was a year ago. It's your valves; they are not pulling their weight. Renew your set throughout with Tungram Valves. Make it as good, or even better than when you bought it, or built it. More stations; increased volume; perfect tone. But it must be Tungram! For this reason; Tungram Valves are the most efficient that modern science has so far produced. Tungram Valves are used by 61 British set manufacturers. But they cost very much less than the price you're used to paying. You cannot get Tungram quality in any other valve, even by paying twice the Tungram price! Insist on Tungram. Don't be put off. Go to a Tungram dealer; take nothing but Tungram!

RENEW YOUR SET WITH

TUNGSRAM


If in difficulty write for literature and for the name and address of your nearest Tungram dealer to:
Tungram Electric Lamp Works (Gt. Britain) Ltd., Radio Dept., S.T. 4, Commerce House, 72, Oxford Street, London, W.1.

BARIUM VALVES

You will Help Yourself and Help Us by Mentioning "A.W." to Advertisers

The most
marvellous
home constructor
set ever
produced!

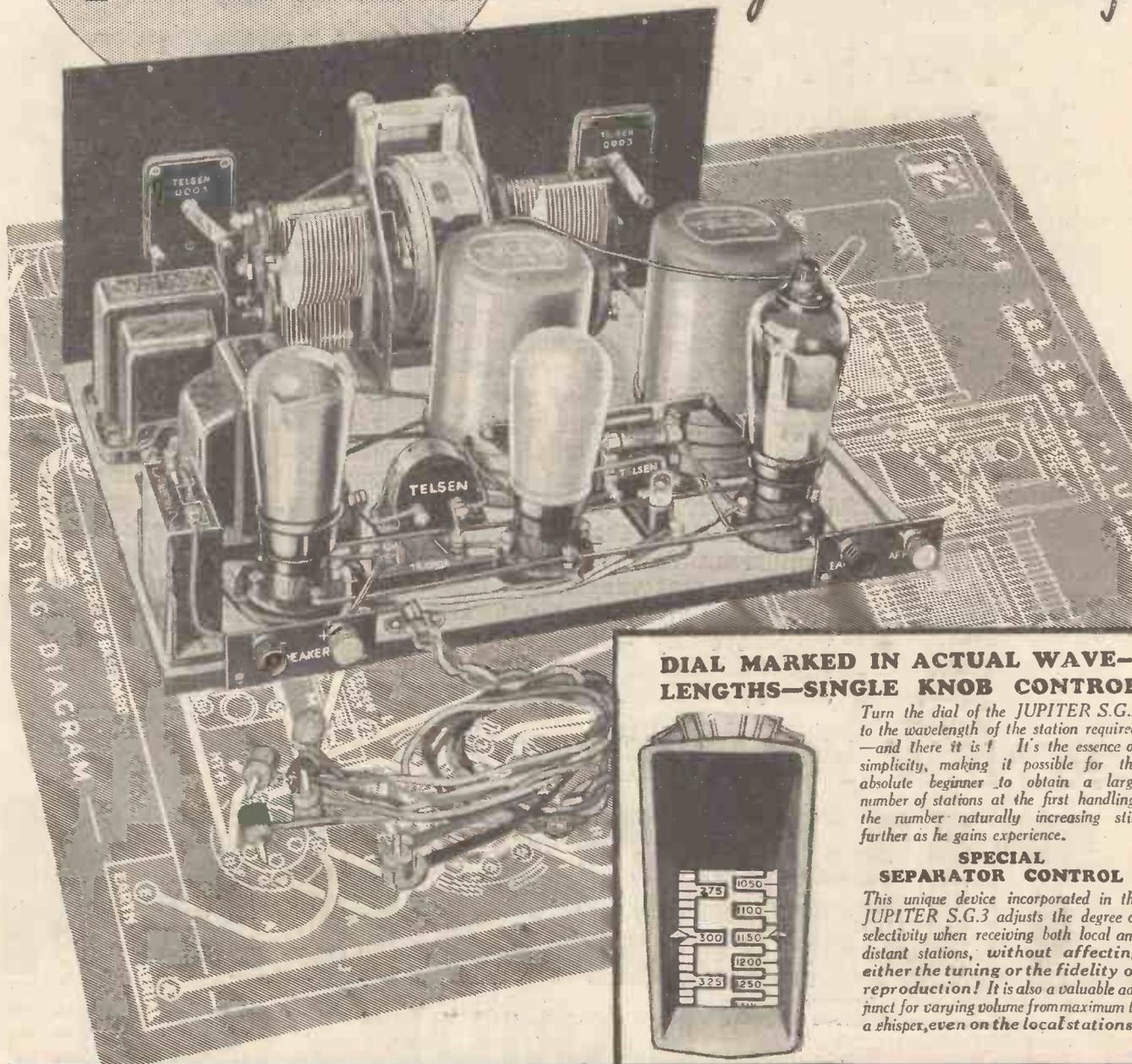Super-selective!
TELSEN
Single knob tuning!




DIAL MARKED IN ACTUAL WAVELENGTHS—SINGLE KNOB CONTROL

Turn the dial of the JUPITER S.G.3 to the wavelength of the station required—and there it is! It's the essence of simplicity, making it possible for the absolute beginner to obtain a large number of stations at the first handling, the number naturally increasing still further as he gains experience.

SPECIAL SEPARATOR CONTROL

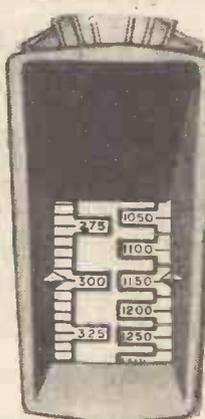This unique device incorporated in the JUPITER S.G.3 adjusts the degree of selectivity when receiving both local and distant stations, without affecting either the tuning or the fidelity of reproduction! It is also a valuable adjunct for varying volume from maximum to a whisper, even on the local stations!



MAKE SURE YOU GET YOUR

ANNOUNCEMENT OF THE TELSEN ELECTRIC CO., LTD. ASTON, BIRMINGHAM

Mention of "Amateur Wireless" to Advertisers will Ensure Prompt Attention

Hyper-sensitive!! Ultra-modern!!!

JUPITER S.G.3.

Dial marked in wavelengths! Special Separator Control!

Full size 1/- Blueprint given FREE with the TELSEN RADIOMAG No. 3.

Never before has it been possible for the ordinary home constructor to build so powerful a 3-valve receiver as the Telsen JUPITER S.G.3! For never before has such amazing power, such tremendous range and such superlative selectivity been attained with the use of only standard components! Child's play to build, child's play to operate, it is beyond

question the most *sensational home constructor set ever produced*. Yet it is not a "Kit" set, but purely a circuit design using specified components—some of which you may already have and will not therefore need to buy!

In keeping with the highest modern practice, the Telsen JUPITER S.G.3. incorporates Ganged Condensers, Ganged Coils, a Tuning Dial calibrated in wavelengths, and Matched Output, the brilliant circuit arrangement providing for absolute control of selectivity, with entire prevention of L.F. oscillation. The revolutionary 10-1 Coupling Unit specified gives an L.F. stage gain equal to that of a *two-stage* amplifier, ensuring (in conjunction with the special low loss coils) an overall amplification never hitherto approached in any receiver of its type.

Yet you can build it yourself—in an evening—with the aid of the full size 1/- Blueprint and complete constructional details contained in the Telsen Radiomag No. 3. PRICE 6d. Get your copy NOW!



3 full size 1/- Blueprints given FREE with the new TELSEN RADIOMAG

The Telsen Radiomag No. 3 tells you how to build the very latest types of receivers—how to modernise and improve your existing set—how to rectify little faults—how to get the best out of radio in every way. Get your copy now—price 6d. of all radio dealers and newsagents.

TELSSEN

RADIO COMPONENTS

TELSSEN RADIOMAG No. 3

ANNOUNCEMENT, OF THE TELSEN ELECTRIC CO. LTD., ASTON, BIRMINGHAM

Advertisers Appreciate Mention of "A.W." with Your Order

**Change over now to
POWER from the MAINS**



**Economise with
BETTER RADIO**

Dry batteries, to give the necessary power for modern valves, are expensive and last but a few months. Power from the mains with an "ATLAS" Unit costs less than a shilling a year and lasts for ever.

The wonderful new "ATLAS" A.C.300 gives, for the first time, three alternative outputs and supplies H.T., L.T., and G.B. for all sets up to five valves. £6 10s., or 10s. down. Ask your dealer for a demonstration and insist on "ATLAS," winners of the Olympia Ballots in 1930 and 1931. WESTINGHOUSE RECTIFIERS, Guaranteed 12 months.

**10/-
DOWN
AND BALANCE
IN EASY
MONTHLY
PAYMENTS**



A.C.244. H.T. for 3-4 Valve Sets from A.C. Mains. 59/6 Cash.



D.C.15/25. H.T. for 3-4 Valve Sets. from D.C. Mains. 39/6 Cash.

**CLARKE'S
"ATLAS"
MAINS UNITS**

H. CLARKE & CO. (M/CR), LTD., Patricroft, MANCHESTER
London Office: BUSH HOUSE, W.C.2.
Scottish Distributors: The G. E. S. Co., Ltd., 38 Oswald Street, Glasgow.

-POST NOW!

Messrs. H. CLARKE & CO. (M/CR), Ltd., George Street, Patricroft, Manchester.

Please send me folder describing the complete range of "ATLAS" Mains Units and Components.

NAME (in Capitals).....

ADDRESS.....


29/22/10.

**A BETTER ACCUMULATOR—
BASED ON A NEW PRINCIPLE**



Type E.L.S.7
60 a/h capacity
Price 12/6

Type E.L.M.4
45 a/h capacity
Price 8/-

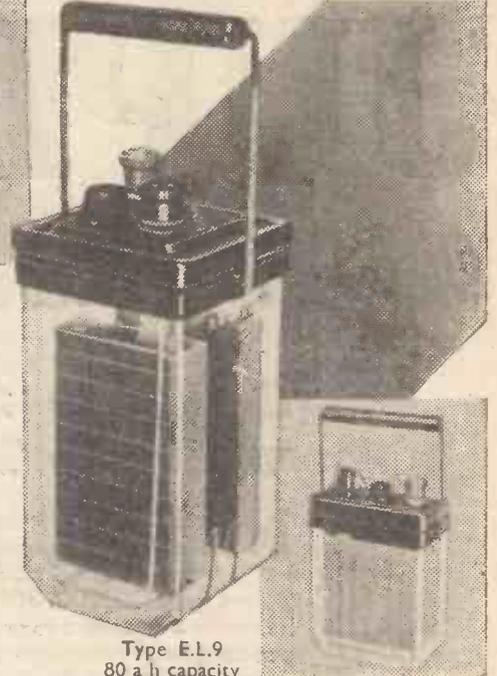

Type E.L.9
80 a/h capacity
Price 12/3

yet you pay no more for it

"Balanced capacity"—an entirely new development in accumulator design—is the outcome of three years' ceaseless research in the Ediswan laboratories. Briefly it means that positive and negative elements are in accurate electrical balance making very rapid charge and very slow discharge rates equally practicable without damage to the elements. Careful tests show that the new Ediswan accumulator outlasts every other accumulator of similar capacity.

Outside as well as inside, the new Ediswan accumulator is a tribute to the quality of Ediswan workmanship. The glass containers are British made with moulded ebonite lids, screwed vents, non-corrodible and non-interchangeable connectors and a carrier which fits beneath a moulded projection of the glass container. In the E.L.S. types a "grease-cup" on pillar prevents "acid-creep". . . . See them at your radio dealer's.

**EDISWAN
EXTRA LIFE
ACCUMULATORS**



THE EDISON SWAN ELECTRIC CO. LTD.
155 CHARING CROSS ROAD, LONDON, W.C.2

B.183

To Ensure Speedy Delivery, Mention "A.W." to Advertisers

AMAZING DISCOVERY

98% RADIO SETS "DOWN" IN EFFICIENCY THROUGH FAULTY GRID LEAKS OR MICA CONDENSERS!

A RECENT analysis of Kit sets and Home Constructor Receivers reveals the astounding fact that 98% were considerably 'down' in efficiency through faulty Grid Leaks or Mica Condensers. These tests were carried out by one of the foremost Radio Engineers in the Country on sets which the owners thought were working satisfactorily.

The above facts were brought to the notice of TELSEN Engineers who immediately commenced intensive research and experimental work to discover the causes. Every known make of Grid Leak and Mica Condenser was tested and examined in conjunction with all types of Receivers.

Invaluable information and new data were obtained from these investigations among which were startling revelations concerning the rapid deterioration and consequent loss of efficiency in these components.

The new TELSEN Grid Leaks and Mica Condensers are the direct outcome of this

amazing discovery. They have been designed on entirely new lines and embody the new



TELSEN FIXED MICA CONDENSER (Shown with Grid Leak Clips removed).


principles formulated by the Telsens Radio Engineers to overcome the numerous faults



Two views of the TELSEN GRID LEAK.

disclosed and to attain permanent efficiency.

TRY THIS SIMPLE TEST

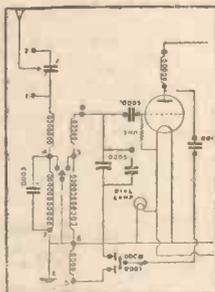

Tune in a station at the top of the medium wavelength band—say the Northern Regional. Note the signal level. Now connect a Telsens Mica Condenser (up to .0003 mfd. in value) across the aerial tuning condenser. Decrease the value of the

tuning condenser until the same station is heard, and it will be found that the signal strength is equal to that previously obtained, proving that the Telsens Mica Condenser has an efficiency comparable with that of the variable air condenser, the most efficient type of condenser used in radio broadcast reception.

The new TELSEN Grid Leaks and Mica Condensers set a world's standard in lasting efficiency.

IT'S THE 'LASTING EFFICIENCY' THAT COUNTS



TELSEN FIXED MICA CONDENSER (Complete with Grid Leak Clips & Grid Leak)

WE HEAR

That well over a quarter of a million radio components are produced every day in the new Telsens Works (the largest and best equipped radio organisation in the world, employing in the neighbourhood of 8,000 workpeople)—and that even this record output is only barely sufficient to meet the enormous and still rapidly increasing demand for these popularly priced quality components.

★ ★ ★

That enormous numbers of home constructors are fitting the new Telsens Drum Drive and Ganged Condenser Assembly, whose single knob operated tuning scale, calibrated in actual wavelengths, makes station logging literally as easy as A.B.C.

★ ★ ★

That the new Telsens Telornor (illuminated variable ratio slow-motion Disc Drive, whose handsome silver oxidised escutcheon plate permits of the very effective grouping of all controls) gives home-built sets the dignity and beauty of line of expensive commercial radio receivers.

★ ★ ★

That home constructors everywhere are thrilled with the performance of the sensational new Telsens JUPITER S.G.3 and AJAX 3 receivers, and that free 1/- blueprints and constructional details of these amazing sets are given with the Telsens Radiomag No. 3, price 6d.

Announcement of The Telsens Electric Co., Ltd., Aston, Birmingham.

Mention of "Amateur Wireless" to Advertisers will Ensure Prompt Attention

A BATTERY SET BECOMES A BETTER SET WHEN ELECTRIFIED WITH REGENTONE



An all-electric receiver is constant in efficiency of output, because the supply of power never varies.

If you have a battery set or a battery kit set, why not enjoy the advantages of All-electric Radio in the cheapest way possible? Join up a REGENTONE Mains Unit in the same manner as a dry battery, connect to the electric supply socket, and your set becomes permanently powered by the mains at a cost not exceeding 6d. per month. Regentone mains units cost from 39/6, or 8/- down.

6 STAR FEATURES COMMON TO ALL REGENTONE MAINS UNITS

- ★ Seven voltage tapings.
- ★ Line voltage output regulator.
- ★ Solid drawn steel case.
- ★ High capacity smoothing.
- ★ One efficiency only.
- ★ Price determines current output.



THE SYMBOL OF INDIVIDUAL CRAFTSMANSHIP

REGENTONE LTD., Regentone House, 21 Bartlett's Buildings, E.C.4


Telephone: Central 8745 (5 lines)

Irish Free State Distributors: Kelly & Shiel, Ltd., 47 Fleet Street, Dublin

Advertisers Appreciate Mention of "A.W." with Your Order

Micromesh

A MODERN VALVE WITH NEW PRINCIPLES

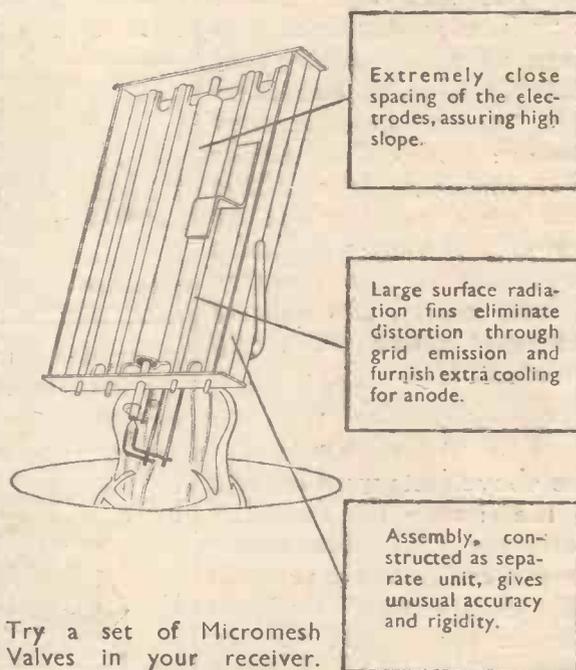

Try a set of Micromesh Valves in your receiver. Note the vast improvement in crispness of tone and clarity of reproduction. Micromesh—the modern Valve—gives perfect reception from every station.

Type H.L.A.1 Detector.
List Price, 13/6.

Type P.A.1 Power Output.
List Price 17/6.

Type R.1 Indirectly
Heated Full-wave Rectifier.
List Price 12/6.

Type R.2 Indirectly
Heated Full-wave Rectifier.
List Price 15/-.

Write for leaflet containing full details of Micromesh valves.

Standard Telephones  and Cables Limited

Radio Merchandise Dept., St. Chad's Place, 364 Gray's Inn Road,
London, W.C.1.

Telephone: Terminus 6255.

TELSEN

MANSBRIDGE AND MICA

CONDENSERS

THE 100% PERFECT CONDENSERS



TELSEN TAG CONDENSERS

Of extremely compact and sturdy construction. May be mounted on either insulated or metal panels by utilising the two baseboard screw holes in the neatly designed moulded casing. The tags enable the condensers to be connected to any other components, either directly or by soldering. H.F. losses are negligible.

In capacities of .0001 mfd. to .002 mfd. **6d.**



TELSEN 'MICA' CONDENSERS

Represent an important advance in technique: H.F. losses have been practically eliminated, even in the larger capacities. Enclosed in a very attractive moulded case, adaptable to flat and vertical mounting. Grid-leak clips, which may be mounted in series or in shunt, are supplied at no extra charge, with capacities of .0001, .0002, and .0003 mfd.

In capacities of .0001 mfd. to .002 mfd. **1/-**
Also .006 mfd. 1/3



TELSEN PRE-SET CONDENSERS


Very low minimum capacity, giving a wide range of selectivity adjustment when used in the aerial circuit. Substantially made, easily adjusted and provided with locking ring. High insulation and low loss.

In maximum capacities of .0001 mfd. to .002 mfd. **1/6**


TELSEN MANSBRIDGE TYPE CONDENSERS

Made by the most advanced processes from the finest materials, triple sealed and guaranteed non-inductive, and subjected during manufacture to stringent tests up to Admiralty and Post Office standards. Offered in two types—the capacities from .01 to 2 mfd. in bakelite cases and in blocks of 4, 6 and 8 mfd. in metal cases with soldering tags.

Cap mfd.	500 volt test	Cap mfd.	500 volt test
.01	1/6	.25	2/-
.04	1/9	.5	2/3
.1	1/9	1	2/3
		2	3/-

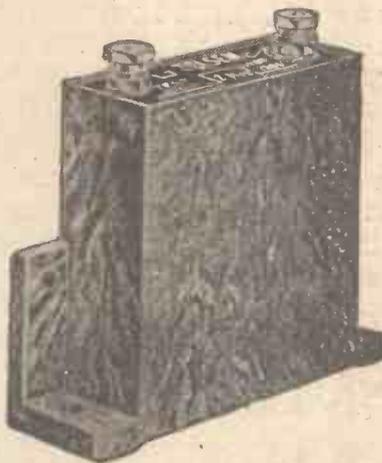

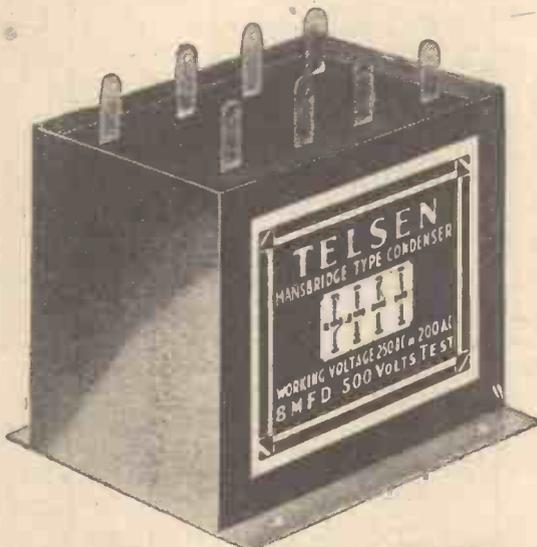THEY SET A WORLD'S STANDARD IN LASTING EFFICIENCY



TELSEN MANSBRIDGE BLOCK CONDENSERS

Contained in metal cases with fixing holes. Like all Telsens Mansbridge Condensers, they are triple sealed and guaranteed non-inductive, being tested during manufacture to Admiralty and Post Office standards. Made in three types, each having total capacities of 4, 6 and 8 mfd., each type being divided into 2-mfd. sections, so that several arrangements of capacity may be obtained. Soldering tags provided for each section.

Cap. mfd.	500 volt test	1,000 volt test
4	5/6	9/6
6	8/-	14/6
8	10/6	

TELSEN
RADIO COMPONENTS

IT'S THE 'LASTING EFFICIENCY' THAT COUNTS

ANNOUNCEMENT OF THE TELSEN ELECTRIC CO., LTD ASTON BIRMINGHAM

Mention of "Amateur Wireless" to Advertisers will Ensure Prompt Attention


TRUE TONE CONTROL

WHAT IS SELECTIVE TONE AMPLIFICATION

Selective tone amplification is the method of tone control made possible by Multitone. By turning a knob you can AMPLIFY low tones, middle tones, or high tones, just as you wish. NO OTHER TONE CONTROL CAN DO THIS.

If the tone of your present set is not all it might be, you can easily substitute the Multitone Transformer for your existing L.F. transformer or add it to the Resistance Capacity Coupling. If you are not a constructor, your dealer will do this for you.

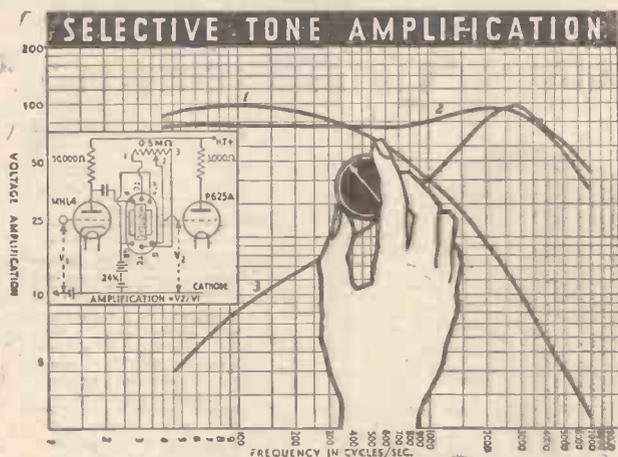Ask for it at any reliable dealer's: if you have any difficulty write to us direct.



By changing the setting of a Potentiometer, the response-curve of the Multitone Transformer is progressively altered from a falling (1), through a level (2), to a rising (3) characteristic. The limiting responses and an intermediate level-response are shown by these curves. When the response is level the transformer ratio is 4:1. True Two-way Tone Control is immediately at your disposal on any set. In use all that is necessary is to turn the Potentiometer until the desired overall response is obtained.



Any good Potentiometer exceeding 0.5 megohms can be used with the Tone Control Transformer, but the best results are obtained with the Multitone Graded Potentiometer (price 3s. 6d.) which has been specially designed for this purpose.

17/6

Our Booklet on Tone Control will be sent post free on receipt of a postcard.

MULTITONE

TONE CONTROL L.F. TRANSFORMER

Multitone Electric Co., Ltd.
95/98, White Lion St., London, N.1. Phone: North 5063

GANGED CONDENSERS AT THEIR BEST

British Radiophone ganged Condensers are used by discerning amateurs and Set-designers in preference to all others because of their extreme accuracy—the trimmers being first adjusted, our guarantee is for a maximum error of $\frac{1}{2}$ m.m.f. $\pm \frac{1}{2}$ per cent., whichever is the greater.

This unequalled precision is achieved by virtue of sound mechanical construction which maintains the electrical characteristics at fixed values under the most exacting conditions.


Built up from sheet steel and treated with a special anti-corrosive medium, the cases resist all tendency to distort or rust—an important factor where high and lasting accuracy is concerned.

The rotor bearings are designed so that any endwise movement of the spindles is effectively prevented and smooth, silent action is ensured during rotation.

PRICES:

- 2-Gang Condenser, 15/-; Dustproof Metal Cover, 2/6
- 3-Gang Condenser, 25/-; Dustproof Metal Cover, 3/-
- 4-Gang Condenser, 30/-; Dustproof Metal Cover, 3/6
- Escutcheon and Drum Drive Assemblies with Pilot Lamp Attachments, 8/6.
- Escutcheon and Disc Drive with Pilot Lamp Attachment, 5/-.

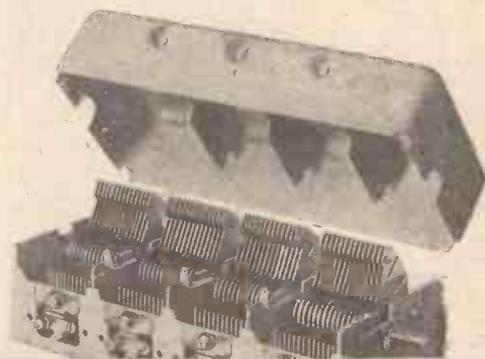Send for full particulars of British Radiophone Components including Gramophone Pick-up, Volume Controls, Q.M.B. Switches and the new Band Pass Radiopak.



RADIOPHONE GANGED CONDENSERS

THE BRITISH RADIOPHONE LTD., Aldwych House, Aldwych, W.C.2.

You will Help Yourself and Help Us by Mentioning "A.W." to Advertisers

FOR EVERY SET — there's a PILOT AUTHOR KIT

CASH — C.O.D. — or H.P.

EVERYTHING RADIO
IMMEDIATE DELIVERY—
CASH, C.O.D. or H.P.

CARRIAGE PAID TO YOUR DOOR

COSSOR MELODY MAKER MODEL 334 with Metallised Variable-mu S.G. and Detector Valves, Power Valve and Cabinet. Cash Price, £6/7/6. Balance in 11 monthly payments of 11/10. **Send 10/- only**

LISSEN "SKYSCRAPER 3." Chassis model with (Lissen) S.G., Detector and Pentode valves. Cash Price £4/9/6. Carriage paid. **Send 8/3 only**
Balance in 11 monthly payments of 8/3.

LISSEN SKYSCRAPER 3. Cabinet model. Complete with Lissen speaker and Lissen S.G., Detector and Pentode valves. Cash Price £6/5/0. Carriage Paid. Balance in 11 monthly payments of 11/6. **Send 11/6 only**

SLEKTUN SCOUT S.G.3. S.G., Detector and Power. Pilot Author Kit "A" (less valves and cabinet). Cash or C.O.D., £3/19/6. Carriage Paid. Balance in 11 monthly payments of 7/3. **Send 7/3 only**

W.B. PERMANENT-MAGNET MOVING-COIL SPEAKER P.M.2. With 3-ratio input transformer. Cash Price £4/5/0. Carriage Paid. Balance in 11 monthly payments of 7/10. **With 7/9 order**

R & A "VICTOR" PERMANENT-MAGNET MOVING-COIL SPEAKER DE LUXE. With 6-ratio input transformer and protecting grille. Cash Price £3/10/0. Carriage Paid. Balance in 11 monthly payments of 6/5. **With 6/5 order**

EPOCH "20 C" PERMANENT MAGNET MOVING-COIL SPEAKER. (New Edition). With 5-ratio input transformer. Cash Price £1/15/0. Carriage Paid. Balance in 6 monthly payments of 6/6. **Send 6/6 only**

BLUE SPOT SPEAKER UNIT AND CHASSIS. TYPE 100U. Cash Price £1/12/6. Carriage Paid. Balance in 6 monthly payments of 5/2. **Send 5/2 only**

BLUE SPOT UNIT AND CHASSIS TYPE 99 P.P.M. Including matched Transformer. Cash Price £2/19/6. Balance in 11 monthly payments of 5/6. **Send 5/6 only**

ATLAS ELIMINATOR. Type A.C.244. Three tappings. S.G., detector and power. Output: 120 volts at 20 m/a. Cash Price £2/19/6. Carriage Paid. Balance in 11 monthly payments of 5/6. **Send 5/6 only**

EKCO H.T. UNIT. Type A.C.25. For multi-valve sets requiring up to 25 m/a. 3 tappings, S.G., detector and 120/150 volts: For A.C. mains. Cash price, £3/17/6. Balance in 11 monthly payments of 7/-. **With 7/- order**

EKCO A.C.12 H.T. ELIMINATOR for A.C. mains. Tapped S.G. 80 v. 120/150 v. at 12 m/a. Cash Price £2/15/0. Balance in 11 monthly payments of 5/-. **Send 5/0 only**

GARRARD INDUCTION GRAMOPHONE MOTOR. For A.C. mains. Model 202. Mounted on 12-inch nickel motor plate with fully automatic electric starting and stopping switch. Cash Price £2/10/0. Carriage Paid. Balance in 11 monthly payments of 4/7. **Send 4/7 only**

ROLA PERMANENT MAGNET MOVING-COIL SPEAKER F.6. With universal tapped input transformer. Cash Price £2/9/6. Carriage Paid. Balance in 11 monthly payments of 4/6. **Send 4/6 only**

RADIO FOR THE MILLION "STATION MASTER 3" (Model A). With valves and cabinet for battery use. Cash Price £5/11/0. Carriage Paid. Balance in 11 monthly payments of 10/2. **Send 10/2 only**

WIZARD

KIT "A" 76/-
As described in Sept. 17 issue. Author Kit of specified parts, including ready-drilled panel, less valves and cabinet. **CASH OR C.O.D. CARRIAGE PAID**
Or 12 monthly payments of 7/-

Specified Valves £1 : 12 : 3
Peto-Scott Special Cabinet £1 : 0 : 0

KIT "B" As Kit "A" above, with valves, but less cabinet. **Cash or C.O.D. £5-8-3**
Carriage Paid. Or 12 monthly payments of 40/-

KIT "C" As Kit "A" above but complete with valves and cabinet. Cash or C.O.D., Carriage paid, £6/8/3. Or 12 monthly payments of 11/10.

THE QUALITY 30/- TWO PILOT ALTERNATIVE KIT

KIT "A" 30/-
Editor's Kit of recommended parts containing Ready Drilled Ply Panel, less Valves, Speaker and Cabinet. **CASH OR C.O.D. CARRIAGE PAID**
Set of Specified Valves 15/9
Oak Cabinet to Specification 10/6

IMPORTANT Parts, Kits, Miscellaneous Components, Finished Receivers or Accessories for Cash, C.O.D. or H.P. on our own system of Easy Payments. Send us a list of your wants. We will quote you by return C.O.D. orders value over 10/- sent carriage and post charges paid.

PETO-SCOTT WALNUT CABINET SPEAKER

FITTED TO CHOICE BLUE SPOT 100U or Peto-Scott P.M. Moving Coil SPEAKER.
In handsome Walnut cabinet with contrasting Walnut inlaid veneers. Hand French polished. Carefully designed of specially chosen wood to provide the perfect acoustic conditions necessary for the correct rendition of the upper and lower musical frequencies. Eminently suitable for 3 or 4-valve receivers. **CASH or C.O.D. 47/6**
or by 12 monthly payments of 4/6.

IF THE MAKERS CAN DELIVER — PETO-SCOTT WILL SUPPLY IMMEDIATELY

PETO-SCOTT CO. LTD. 77 City Rd. London, E.C.1. Telephone: Clerkenwell 19406/7
West End Showrooms: 62 High Holborn, London, W.C.2. Telephone: Holborn 3248
Dear Sirs, Please send me CASH/C.O.D./H.P. for which I enclose £..... d. CASH/H.P. Deposit. Also send your FREE 1933 Radio Catalogue.
NAME
ADDRESS
A.W. 22/10/32.

Buy by Post — it's Quicker

1933 WALNUT ADAPTAGRAM

Convert your Set to a Radiogram with this beautiful inlaid Walnut Cabinet. Supplied with vignette front as illustrated and motor board, ready to take your own Set, Gramophone Motor and Pick-up. Panel 18 in. by 8 1/2 in. Base-board, 14 in.; Speaker compartment, 17 in. by 19 1/2 in.; overall dimensions, 38 1/2 in. high, 21 1/2 in. wide, 15 1/2 in. deep. Generous accommodation for batteries or mains equipment. Fitted with back. Baffle Board 3/8 extra if required. Model "A" Cash or C.O.D. Easy Terms: 12 monthly payments of 5/9. Carriage and packing 2/6 extra. **63/-**



MODEL "B" with Garrard Double Spring Motor and B.T.H. Combined Pick-up and Volume Control. Cash or C.O.D. 6 guineas, or 12 monthly payments of 12/-. Carriage Paid. **6 GNS.**
MODEL "C" with Collaro Electric Gramophone Unit complete with Pick-up and Volume Control. Cash or C.O.D. 7 guineas or 12 monthly payments of 13/9. Carriage Paid. **7 GNS.**

BUILT LIKE A FINE PIANO

PILOT BAND-PASS UNIT

Whether your set is Mains or Battery operated, the **PILOT BAND-PASS UNIT** cuts out programme interference effectively and sharpens tuning to needle-point selectivity. It is simple to attach and can be operated by anyone without technical knowledge. No valves or extras required. **CASH or C.O.D. 25/-**
Or 6 monthly payments of 4/6

Instantly converts any Set to Band-pass Tuning with Needle-sharp Selectivity.



STOP PRESS OFFERS

W.B. PERMANENT-MAGNET MOVING-COIL SPEAKER. Type PM4. Complete with transformer. Cash Price £2/2/0. Carriage Paid. Balance in 7 monthly payments of 5/9. **Send 5/9 only**

1932 KELSEY SHORT WAVE ADAPTOR. Tunes in the Short Wave Stations on your existing Set. Cash or C.O.D. Carriage Paid, £1/19/6. Balance in 7 monthly payments of 5/3. **Send 5/3 only**

READY RADIO KENDALL-PRICE S.G.4. S.G., Detector, L.F. and Power. Complete kit less valves and cabinet. Cash Price £4/6/6. Carriage Paid. Balance in 11 monthly payments of 8/-. **Send 8/- only**

UNIVOLT ELECTRIC UNIT. Standard unit with Univolt pick-up, automatic start-and-stop, for A.C. mains, 110/250 v. Cash Price £5/15/6. Carriage Paid. Balance in 11 monthly payments of 10/6. **Send 10/6 only**

GARRARD AUTOMATIC RECORD CHANGER for A.C. mains. Mounted on unit plate complete ready for fitting in position, including Garrard pick-up and tone-arm. Cash Price £10/0/0. Carriage Paid. Balance in 11 monthly payments of 18/6. **Send 18/6 only**

Don't Forget to Mention "A.W." to Advertisers

Here's the Set for YOU!

SLEKTUN



A Triumph of
Simple Construction

SCOUT S.G.3


Amazing Reception 40-50 STATIONS

Kit includes

- ★ The famous Slektun Super Transformer.
- ★ Slektun Dual Range Coils.
- ★ Cydon Ganged Condenser with Sector Vision Escutcheon.
- ★ T.C.C. Fixed Condensers.
- W.B. Valve Holders and Switches.
- ★ Ready Drilled Panel and Terminal Strip of "Permol" non-discolorable Ebonite.
- ★ Baseboard Assembly covered with "Konductite" metallic screening material.
- ★ All necessary screws, terminals, connecting wire, wander plugs and flex.

Complete Kit
of Parts

84/-

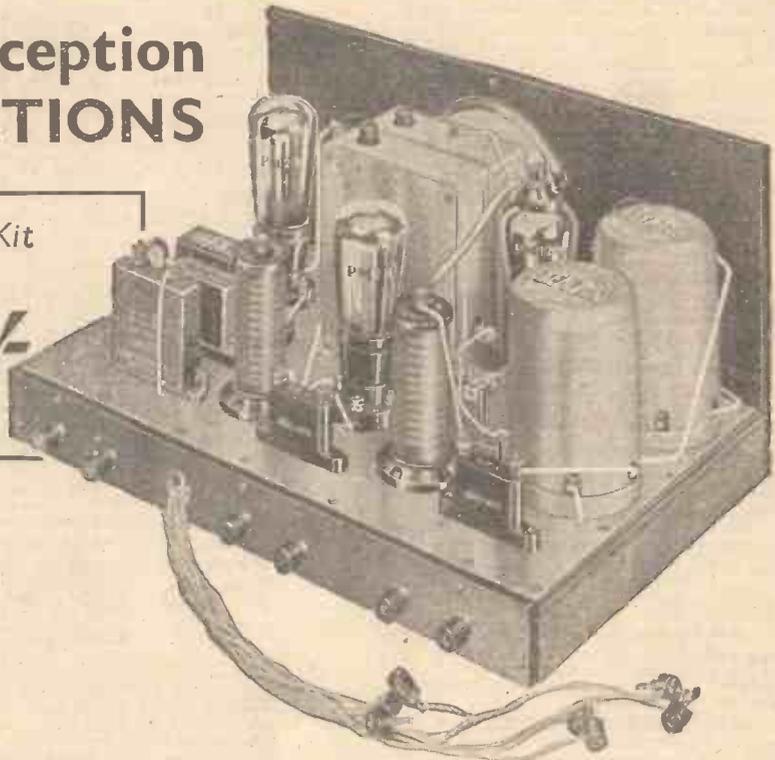

FREE Blueprint and Construction Book

The book of the Scout S.G.3 is the most comprehensive Radio Set Construction book ever printed. Ask your dealer or write for a FREE copy.

This super set has been designed so that the amateur can build as good a receiver as the radio engineer. All you have to do is to put it together. Every component has been carefully chosen for easy construction and perfect results. Amazing range and selectivity are obtained, and powerful, distortionless performance is assured by the use of Slektun Dual Range Coils and the Slektun Super Transformer. 40-50 stations can be tuned in at full loud-speaker strength—including even Fécamp, a station almost impossible to get with most receivers.

The entire set can be built in an evening by anyone—at very moderate cost. Ask your dealer or write for the FREE Constructional Book.

SLEKTUN

QUALITY COMPONENTS

SLEKTUN PRODUCTS, LTD.
21 Douglas Street, Westminster, S.W.1

To Ensure Speedy Delivery, Mention "A.W." to Advertisers

Use this Coupon

To SLEKTUN PRODUCTS, LTD.
21 Douglas Street, Westminster, S.W.1

Please send me the FREE illustrated Book of the Scout S.G.3, together with the full-size Blue Print. I enclose 1½d. stamp to cover cost of postage

Name.....

Address.....

A.W.5

National



**BRITAIN'S LEADING RADIO WEEKLY
FOR CONSTRUCTOR, LISTENER & EXPERIMENTER**

EDITOR:
BERNARD E. JONES.

TECHNICAL EDITOR:
J. H. REYNER. B.Sc. AM.I.E.E.

RESEARCH CONSULTANT:
W. JAMES.

ASSISTANT EDITOR:
H. CORBISHLEY.

NEWS & GOSSIP OF THE WEEK

OUR NEW "SUPER"

THIS week we announce the introduction of an amazing new super-het—a worthy successor to the "Century Super" which broke all records for home constructor sets. The new "Century Super" has been designed by three of the most popular set designers in the country—W. James, Percy W. Harris and Rutherford-Wilkins. An introduction to the set is given on page 837 and next week's issue will be a bumper number, giving the full story of the construction.

EVERYBODY CAN BUILD IT

SO that everyone will have an opportunity of making up this new super-het, next week's bumper number will contain a profusely illustrated constructional guide. There will be a pictorial diagram of the set and a full-size layout and wiring guide.

You can start building the new "Century Super" without even having to buy a blueprint. Make sure of next week's issue. You cannot afford to miss it!

HENRY HALL'S BAND

ON October 24 Henry Hall's Band is to undergo a change. Three members of the present band are leaving and three newcomers are to take their places. Harry Robins, the versatile drummer and xylophonist, is leaving to take up stage work again, and Henry Hall is now trying to decide which of three "possibles" shall take Robins' place. Another vacancy is caused by the departure of Mr. Denahey, the tenor saxophone player. Additional "pep" will be obtained by including a trumpeter, Mr. A. Williams, in place of the oboe. The new

IN THIS ISSUE

Features You Should Not Miss

TO-DAY'S BEST AERIAL.
The new CENTURY SUPER. W. James and Percy W. Harris discuss this amazing new set.

HOW YOU CAN STOP INTERFERENCE.
A GOOD BATTERY-OPERATED POWER AMPLIFIER.

ANOTHER FINE EIGHT-PAGE SUPPLEMENT FOR THE BEGINNER

sax. player, Mr. J. Halsall, comes from Billy Cotton's popular band.

OTHER DANCE BANDS CHANGING

THIS is the season of change in the dance-band world. We hear that Roy Fox is forming a new band and that his present band at the Monseigneur will be led by the pianist. At the Dorchester there is talk of the Blue Lyres being changed, but nothing is yet decided.

BOY OBOIST IN VAUDEVILLE

THE boy oboist, Dick Matthews, who has just left the B.B.C. Dance Band owing to the difficulty of scoring numbers specially for his instrument, will appear from time to time as deputy for oboe players in various B.B.C. orchestras. He will also appear before the microphone on November 7 in a vaudeville show.

MOBILE VAN FOR BELFAST

THE B.B.C. is getting right down to the new Belfast high-power station. The famous mobile test van is on the way to Belfast to seek out the most suitable site. As we have mentioned before, it is proposed to build the new station about fifteen miles south-west of the city. This will make it somewhere in the vicinity of Mount Divis, which is 1,500 feet above sea level. We think the power will be between 50 and 70 kilowatts.

The Post Office pirate tracking vans are now touring the country, and here one of them is seen with its direction-finding receivers at work outside a row of houses, while a Post Office Inspector examines listeners' licences



NEXT WEEK : THE "NEW CENTURY SUPER"—YOU CAN'T AFFORD TO MISS IT !

NEWS · & · GOSSIP · OF THE · WEEK

—Continued

INSTALLING THE NEW ORGAN

NEXT month the B.B.C. will be installing the large organ specially built for the Concert Studio at Broadcasting House. There will be a movable console on the stage. A very interesting point will be the remote console fitted up in another studio, to allow the organist to hear what his playing sounds like through a loud-speaker.

AN AERIAL BLOWN DOWN

THERE is one of the tallest wooden masts in the world at Breslau, the latest station in the German Regional scheme. This carries a vertical aerial—or, at least, it did until recently, when heavy storms during the last ten days caused extensive damage to the wooden tower! This explains why Breslau, although a 60-kilowatt, has been a weaker signal of late. It is working with a temporary aerial.

A BUSY PLAYWRIGHT

MR. L. DU GARDE PEACH is very active in the service of broadcasting at present. In addition to the script of one of the "star" programmes of B.B.C. birthday week, *Communications—1922-1932*, he has written a new radio play, *Nor' West*. This mystery of the sea is to be, according to the Productions Director's forecast, a close rival of the same author's *The Marie Celeste*, which has been heard several times by listeners. *Nor' West* will be heard by Regional listeners on October 24 and National listeners on October 23.

TOURING THE TWENTY-TWO

ONE of the features of the "Tour of Broadcasting House" programme, which is to be given in birthday week, on

In The Beginners' Supplement NEXT WEEK

STEP-BY-STEP BUILDING THE "NEW CENTURY SUPER." In addition to a full-size blackprint of the layout of the new set there will be two pages of illustrated details on how to build the new set.

ADDING A THIRD VALVE. Another practical article in the "Build As You Learn" series by Percy W. Harris.

WHAT THE VALVE IS. J. H. Reyner and the Staff of "A.W." continue the Elementary Wireless Course for Beginners.

MAKING ANY AERIAL SELECTIVE. A special supplement article of interest to all listeners.

WHAT YOU MUST KNOW ABOUT ACCUMULATORS. Practical advice on the proper upkeep of the low-tension battery that heats the valve filaments. Of great value to all battery set owners.

November 14, to be exact, will be a revue specially written by Henrik Ege. In this will be a cast of twenty-two people, one in each of the twenty-two studios of Broadcasting House. The revue will call for amazing dexterity on the part of the producers at the Dramatic Control panel in manipulating cue-lights and potentiometers to "fade in" and "fade out" one studio after another in proper sequence.

EX-ANNOUNCER'S NEW ROLE

A FORMER B.B.C. announcer, the Hon. David Tennant, will broadcast a reading of the seventeenth-century religious poetry on October 30. Mr. Tennant was heard

anonymously in the closing item of the "Good-bye, Savoy Hill" programme recently, being wrongly assumed by a number of people to be the Director-General, Sir John Reith, or alternatively, Sir Charles Cargendale!

TELEVISION RECEIVERS

A NOTHER television receiver has now been delivered to the B.B.C. by the Baird people. This is being used by the engineers. As soon as the third machine arrives it will be installed in the Press Listening Room. We shall have to re-name this room the "Stop, Look and Listen" room!

MIKES ANCIENT AND MODERN

ALTHOUGH at Broadcasting House there are microphones of every conceivable type, it was recently brought home to the B.B.C. that some of the microphones in provincial centres are getting rusty. At Edinburgh, during a recent attempt to record a programme, it was found that the microphones were giving at least 25 per cent background hiss, some of them being four or five years old. The order has now gone forth that every studio is to have the latest microphones, as at London.

ANOTHER GAP FILLED

When School Broadcasts End

WHEN the present school broadcasting term ends at Christmas the B.B.C. will fill the gap that now frequently occurs between the hours of three and four in the afternoon. Light music, of the cinema-organ and café-orchestra type, will be the main fare in this new hour. We shall then have continuous broadcasting from 12 mid-day until 12 midnight. Slowly we seem to be catching up to the American idea, which is to start with early morning physical jerks and go on until midnight, or later, without a single break.

TELEVISION MANNEQUIN PARADE

ON October 28 the B.B.C. will stage its first mannequin parade for television purposes. Dresses and gowns by the leading *modistes* will be displayed but no names will be mentioned. Later we hear there will be a television broadcast of a greyhound. Physical culture experts are also billed.

IMPROVING RELATIONS

THE other afternoon Mr. Fred Bates, the N.B.C. liaison official in this country, had the pleasant task of introducing Mr. Warwick Deeping, the novelist, to American listeners, via a B.B.C. studio and the transatlantic phone. By the way, Mr. Bates is out to improve relations between the B.B.C. and the N.B.C. He ought to know his job, having been associated with the Dawes and Young Commissions.

MISSING THEIR CUE!

Bad Luck in the Talks Department

NO one can say the B.B.C. Talks Department has had a lot of luck lately. First there was the Vernon Bartlett misunderstanding, when Mr. Bartlett turned up at the studio in Geneva at 10 p.m., when he was wanted for relaying by the B.B.C. at 9.20 p.m. Then Professor Cornford's talk had to be read by an announcer, owing to a hold-up on the line up from Cambridge. And now J. B. Priestley has had his talk delayed owing to the mislaying at the studio of his manuscript.

THE LATEST IN ALARMS!



This burglar alarm is switched on by a photo cell-device which can work in the dark. The grammo-radio side of the apparatus is switched on, the receiver of a telephone is lifted off its hook and the record rings up the police! At the same time a powerful light is switched on and the camera at the left takes a "snap" of the eavesdropper

SPECIAL ENLARGED NUMBER NEXT WEEK

The Editor Talks about his Splendid Supplement, his New-style Full-size Print and, chiefly, about the "A.W." "NEW CENTURY SUPER"


FOR many weeks past we have been presenting a supplement with each issue of AMATEUR WIRELESS—undoubtedly the most successful and the best appreciated series of supplements ever issued with any wireless periodical. Next week's issue of "A.W." will contain a further supplement, stronger than ever in the quality of its contents: (Turn, in due course, to the last page of this week's AMATEUR WIRELESS supplement, and see what we promise.)

A SPECIAL NUMBER

But will you make particular note, too, that next week's AMATEUR WIRELESS will contain many extra pages and include not only the supplement, but a full-size blackprint of a remarkable set, and the issue in itself will be outstanding, both in interest and in the number and variety of its pages. It will be a special number, very largely devoted to a special subject, the "New Century Super," a successor to a set that made radio history: The "Century Super" in AMATEUR WIRELESS last year, and its companion set, the "Super 60" in the *Wireless Magazine*, were the most successful home-constructor sets of recent years, and have set a fashion in super-hets which is reflected in the manufactured receivers of to-day. There is no need to remind you that the original "Century Super" was a success on the grand scale, and I predict that the "New Century Super" which will see the light next week, will repeat it. Mr. W. James designed last year's great set. This year, Mr. W. James—known to everybody as a designer of exceptional merit; Mr. Percy W. Harris—a famous radio personality with whom every reader is familiar; and Mr. S. Rutherford Wilkins—in charge of "A.W."s Construction Dept. and a keen radio technician; all three have collaborated in the design of the "New Century Super." It is a collaboration of radio giants, ensuring that in the soundness of its design and technique, in the complete way in which it fills the bill, and in the practical and workmanlike style in which the details of the set have been managed,

the "New Century Super" has no equal. It stands alone. The collaborators have given of their best and the result is something of which they and AMATEUR WIRELESS and its readers can all be proud. Mr. W. James talks of this set on another page in this present issue, and all I need do is briefly to tabulate some, but by no means all, of its advantages: **Selectivity**, given by the aerial input filter. **Sensitivity**,

set next week, and shall present with every copy—stitched in so it cannot accidentally fall out and be omitted—a Full-size Blackprint of the "New Century Super," an absolutely full-size layout plan just as good in every way as a blueprint, but grey-black, and for that reason all the more readable. The issue will contain constructional details, specification, circuit diagram, etc., etc., and particular care is

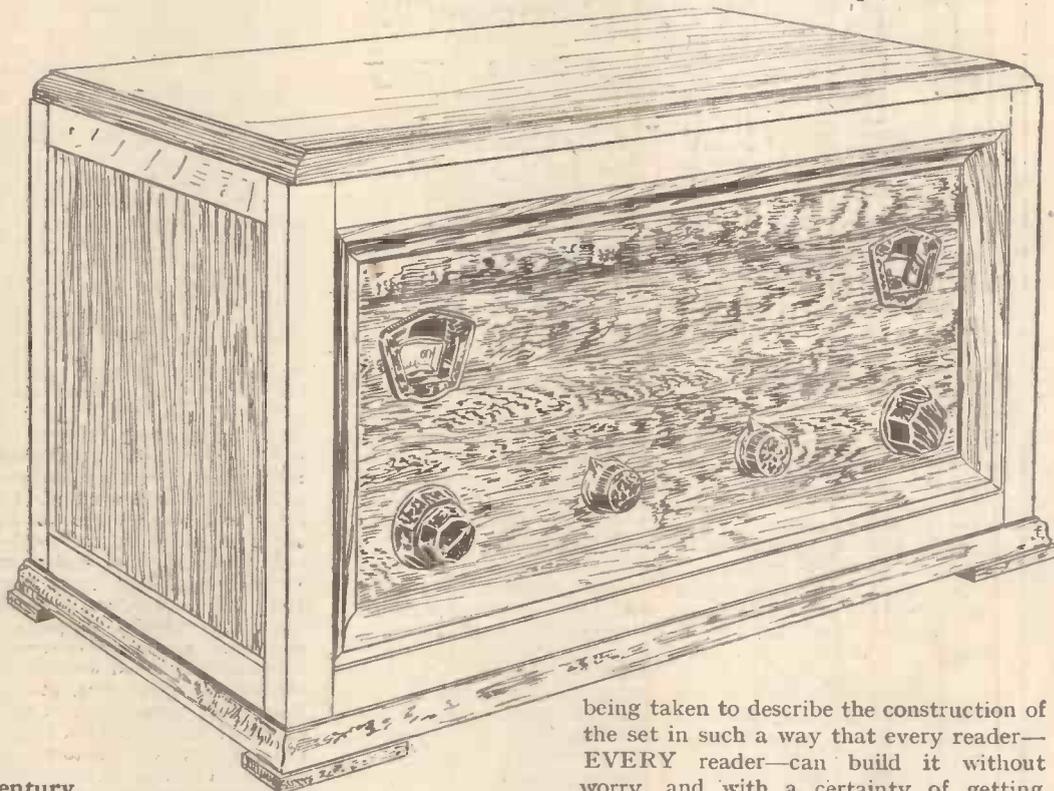

by a screened-grid first detector. **Great magnification**, with **distortionless volume control**, given by the variable- μ intermediate frequency valves.

There is **very small H.T. consumption**, with **large output**. There is **freedom from interference**; there is **power**; there is **marked simplicity of control**; there is **good quality** and, what every reader wants, there are **just as many stations as you will ever want to get**. And what about the cost? Extremely moderate, particularly in relation to what you get for the money.

FULL DETAILS NEXT WEEK

We shall describe this absolutely modern

being taken to describe the construction of the set in such a way that every reader—EVERY reader—can build it without worry, and with a certainty of getting results. Well-informed wireless men know what the super-het can do and are eagerly awaiting this new version, but beginners, for whom the word "super-het" may have quite unnecessary terrors, can take it from me that with our instructions before them they can build with ease and operate with pleasure the "New Century Super" and obtain from it in all certainty the most wonderful service.

My advice! There will be a big run upon next week's issue of AMATEUR WIRELESS, so will you immediately, please, order your copy. Failing this, be sure to get your copy first thing next Thursday morning, or you run a considerable risk of being disappointed.—THE EDITOR.

A Special Number, complete with our "Wireless Made Easy" Supplement, and Full-size Blackprint, on Sale Next Thursday, October 27, at our Usual Price, 3d.

HINTS AND TIPS ON SHORT-WAVE WORK

Useful information of particular interest to the short-wave enthusiast

H.F. AMPLIFICATION ON SHORT WAVES

It has been generally accepted that a screen-grid H.F. stage in a short-wave receiver is purely a passenger and of little material advantage.

While admitting that the amplification gained at these high frequencies is only slight, there are numerous definite

reasons why a screen-grid stage should never be omitted if the maximum sensitivity is required with ease of control. After experimenting a considerable time with an S.G.3 short-wave receiver, an appreciable gain was obtained on wavelengths down to as low as 18 metres.

A theoretical circuit, Fig. 1, shows that the arrangement is quite usual and does not call for any comment. It is in this case the components, etc., that account for the unusual efficiency. As is only to be expected, the most important components are the screen-grid valve and the high-frequency choke. The maximum amplification was obtained when using a moderately low impedance screen-grid valve, such as the Cossor 220SG, together with a choke such as the Lewcos. It is important that the impedance of the screen-grid valve should not exceed 200,000 ohms, and at this figure to have a mutual conductance as high as possible.

It cannot be too strongly emphasised that the H.F. choke must be of the highest efficiency possible to obtain any appreciable amplification on wavelengths of 25 metres and under. The selectivity of a normal short-wave receiver is particularly good when a screen-grid stage is added; as the load on the detector circuit is decreased, the selectivity is inclined to be too great for normal working, so that care must be taken to flatten the tuning as far as possible.

Between the screen-grid and the detector stages is the coupling condenser *ci*. This should have a capacity of .0005 microfarad and be taken directly to the fixed plates of the tuning condenser in the detector stage. If a tapping or a coupling coil has formerly been used, these should be disregarded.

An efficient air-space con-

slight modification on the following lines should be made to the aerial circuit.

Firstly, remove the aerial from the top of the coil and connect to a tapping on the coil by means of a short length of single flex and a crocodile clip. Secondly, replace the fixed condenser in series with the aerial with a variable air-space condenser having a maximum capacity of .0001 microfarad. Thirdly, should the aerial coil be of commercial design, it is more than probable that this is wound with a covered wire or has the windings totally enclosed. In such cases the circuit should be slightly altered in the following way.

Wind about two or three turns of 20 s.w.g. d.c.c. wire tightly around the windings already on the coil. Join one end of this primary winding directly to earth, the other side being taken to the small variable condenser in series with the aerial lead-in wire.

In some cases it may be beneficial not to connect the primary coil directly to the secondary coil, but to couple this in the following manner. Remove the earth connection from your receiver and join this to one end of the primary winding, the other end being taken to the aerial pre-set condenser.

On wavelengths under 20 metres, aerial damping is even more troublesome, and in many cases the previous suggestions will not completely overcome this trouble. When working on such low wavelengths, it has been found by experiment that an aerial having a total length of 15 to 18 ft. is ample to supply maximum efficiency. At the same time, the aerial condenser should not have a maximum capacity exceeding 50 micro-microfarads, with a low minimum of approximately 1 micro-microfarad. Incidentally, below 20 metres, it is nearly always an advantage to omit the earth connection should this go directly to a water pipe or a similar type of earth. A much more satisfactory arrangement is to use a counterpoise earth of a similar length to the aerial employed.

INCREASING THE CLARITY OF WEAK SIGNALS

The reproduction with a short-wave receiver is usually very pleasant and mellow, particularly on the really short waves round about 20 metres.

While this may be satisfactory on a powerful station giving a musical programme, imagine what will happen with a powerful station broadcasting news, etc. The pitch of the speech will be so low that the majority of the news will be unintelligible and it will be necessary to incorporate a simple control so that some of the predominating bass notes can be reduced or removed altogether. A simple control is shown in Fig. 2; this consists of a .25-henry choke with a variable resistance of 25,000 ohms. Although this control is very effective, the regulation is sufficiently smooth to permit an easy variation of the pitch to be obtained.

A low-consumption pentode, such as the Mazda Pen220, is particularly useful in the output stage, as not only is the volume greatly increased, but at the same time the pitch is raised to a great extent.

One does not consider the use of a moderately high impedance triode in the output stage. With a 120-volt H.T. battery and 1½-volt grid bias, a valve such as the Cossor 210Det will give a considerably higher output than a small pentode or power valve; but only when listening to a weak station and using headphones. A signal that can hardly be heard with an ordinary power valve is usually

receivable at fair strength with a detector valve in the output stage. If such a valve is not at hand, a screen-grid valve can be used quite easily. It is not usually appreciated that the standard screen-grid valve is very flexible and can be used in nearly any position in the receiver. It will take the place of the power valve by merely plugging this in and omitting to make any contact to the screw terminal at the top of the bulb. When used in this way the actual anode is not required and the screening grid is used in its place. The effect of this is to reduce the impedance to about 7,000 or 8,000 ohms, and as the slope is usually about 1.5 milliampere per volt, it is then turned into a really useful L.F. valve.

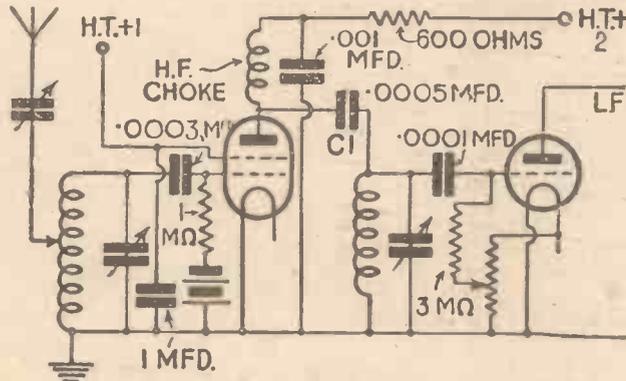


Fig. 1. A good short-wave circuit in which a screen-grid valve is used

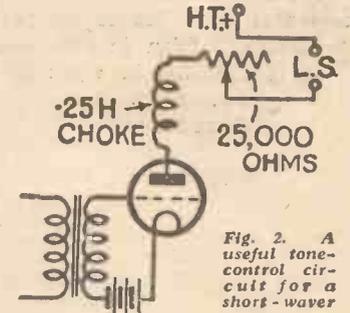


Fig. 2. A useful tone-control circuit for a short-waver

denser should always be used in series with the aerial to minimise damping, one having a maximum capacity of .000075 microfarad or .0001 microfarad will usually be found quite suitable.


To anyone who has handled an S.G.3 short-wave receiver the ease of control can readily be appreciated. The reaction is set a little below the maximum point and can be left in such a position while searching for a station, being adjusted to regulate the volume when the station has been correctly tuned in. The normal detector circuit compares very badly with such a receiver as the sensitivity is mainly dependent on the smoothness of the reaction control, while the receiver is usually oscillating or on the verge of oscillation when searching for stations.

AERIAL DAMPING

An aerial having a length of between 50 and 60 ft. is fairly average and usually is quite satisfactory when used with a standard broadcast receiver. On short waves, however, such an aerial, unless due precautions are taken, would so heavily damp the grid circuit that the receiver would probably refuse to oscillate.

The use of two aerials is not always convenient, so in such circumstances

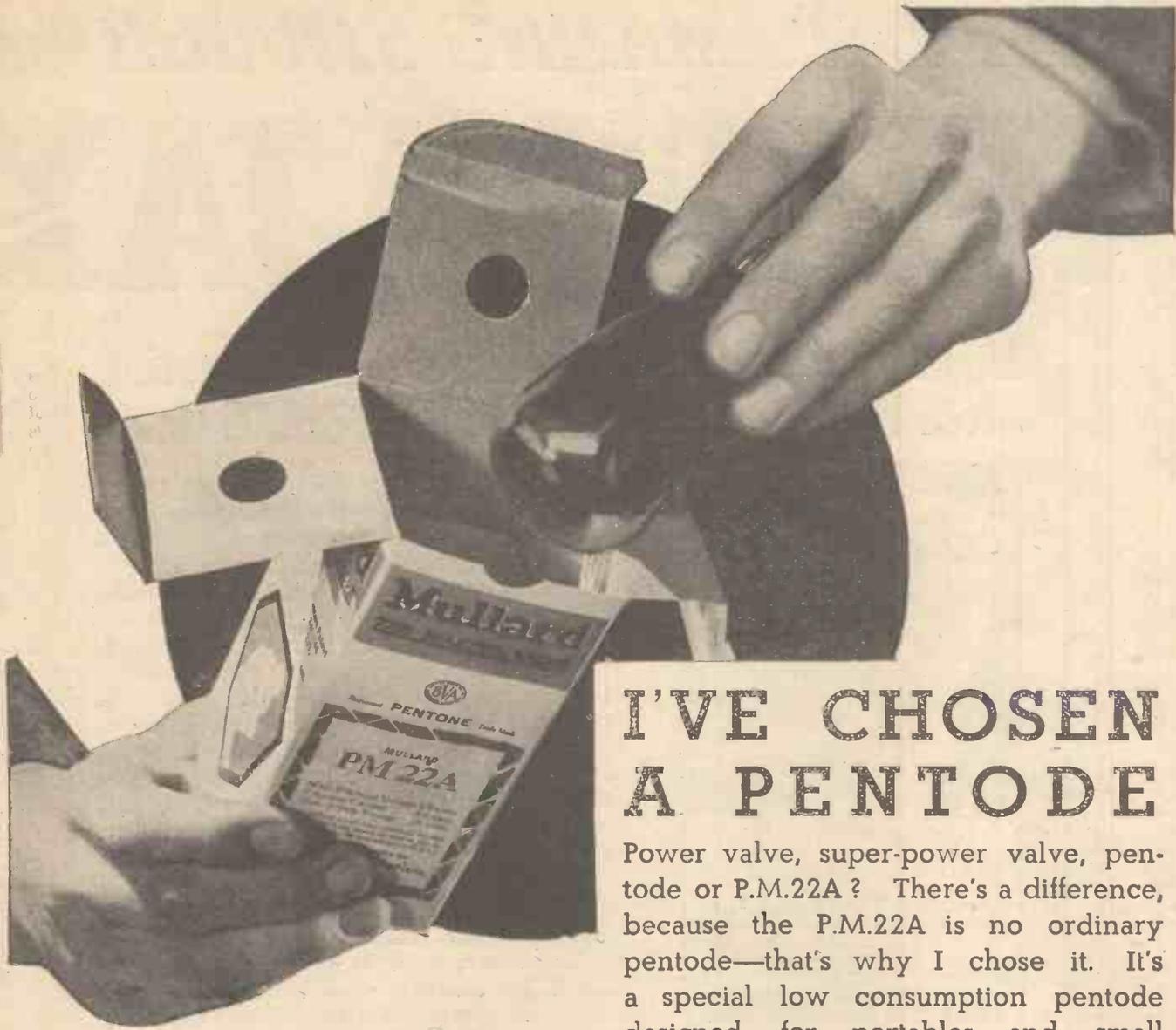THE "NEW CENTURY SUPER"
See page 837 for news of outstanding interest to you.



I'VE CHOSEN A PENTODE

Power valve, super-power valve, pentode or P.M.22A? There's a difference, because the P.M.22A is no ordinary pentode—that's why I chose it. It's a special low consumption pentode designed for portables and small battery sets: it works off an ordinary 100 volt high tension battery and only uses $4\frac{1}{2}$ milliamps: it's the pentode you can use without draining your batteries.

PRICE 17/6

MADE IN ENGLAND.

The valves specified for the "Amateur Wireless push pull Amplifier" described in this issue are: (1) Mullard P.M.1HL and (2) Mullard P.M.22A.

PM 22A

Mullard

THE · MASTER · VALVE

Advt. The Mullard Wireless Service Co., Ltd., Mullard House, Charing Cross Road, London, W.C.2

ARKS

Please Mention "A.W." When Corresponding with Advertisers

THE MOST AMAZING 'STRAIGHT 3'

TELSEN AJAX

Build it to-night with the full size 1/- Blueprint given FREE with the TELSEN RADIOMAG No. 3



3

full size 1/- Blueprints given FREE with the TELSEN RADIOMAG

The Telsens Radiomag is the finest radio sixpennyworth ever offered. In simple language, clearly illustrated by photographs and diagrams, and complete with 3 full size 1/- Blueprints, it tells you how to build the latest types of receivers... how to modernise your present set... how to rectify little faults... how to get the best out of radio in every way! Get your copy now—price 6d. from all radio dealers and newsagents.

NOT a "Kit" set which you have to buy complete—but simply a brilliant new circuit design using certain specified Telsens Components (some of which you may already have!)—that's the amazing new Telsens AJAX 3! It's the receiver countless home constructors have waited for—a receiver which is as inexpensive to build, as economical to run and as simple to operate as only a "straight three" can be, yet which is capable of such tremendous range and power, such razor-sharp selectivity and such superb reproduction that it literally sets an entirely new standard of performance for receivers of its type! Yet its construction has been so simplified that you can build it *easily* in an evening... even if you are an absolute novice! You simply can't go wrong, for not only is a *full-size* Blueprint given FREE with the TELSEN RADIOMAG No. 3, but every stage in its construction is explained by carefully worded instructions and clearly understandable illustrations. Get your copy of the TELSEN RADIOMAG now—and build the AJAX 3 this evening!

TELSEN

RADIO COMPONENTS

Make sure you get your TELSEN RADIOMAG N°3.

ANNOUNCEMENT OF THE TELSEN ELECTRIC CO., LTD., ASTON, BIRMINGHAM

Mention of "Amateur Wireless" to Advertisers will Ensure Prompt Attention

RECEIVER EVER DESIGNED....!


3

Gives 'screened grid' brilliance combined with 'straight 3' economy!

The total cost of
Telsen Matched Com-
ponents for building
the AJAX 3 is

61/6

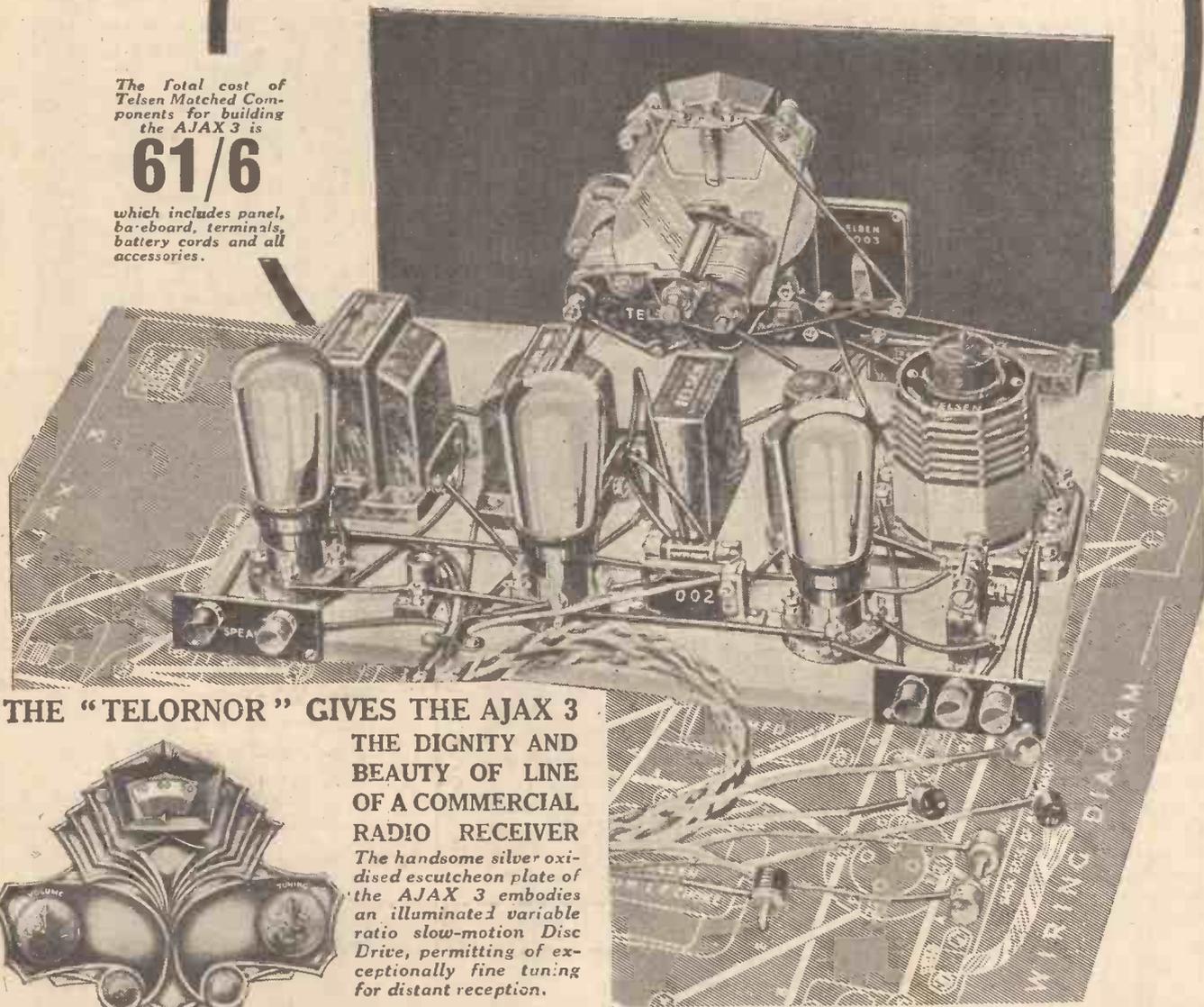
which includes panel,
ba-board, terminals,
battery cords and all
accessories.



THE "TELORNOR" GIVES THE AJAX 3

THE DIGNITY AND
BEAUTY OF LINE
OF A COMMERCIAL
RADIO RECEIVER

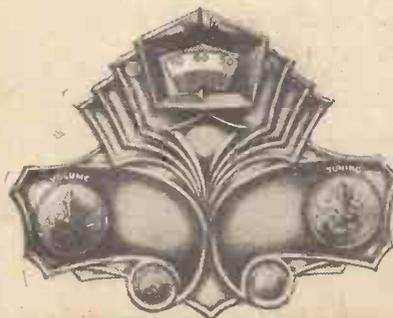The handsome silver oxidised escutcheon plate of the AJAX 3 embodies an illuminated variable ratio slow-motion Disc Drive, permitting of exceptionally fine tuning for distant reception.



Make sure you get your TELSEN RADIOMAG N°3.

ANNOUNCEMENT OF THE TELSEN ELECTRIC CO., LTD., ASTON, BIRMINGHAM

To Ensure Speedy Delivery, Mention "A.W." to Advertisers

Trawlers,
liners, tramps
... all alike
trust to



MARCONI VALVES

NOTHING can be more desolate than the sea. Nowhere do men feel more utterly alone. And in the old days (the 'good old days'?) sailors were utterly alone. Vessels burnt and men starved and went down and no-one ever knew. The sea is no less terrible today—but sailors are safer. In twenty odd years wireless has saved innumerable lives. And what are the valves that serve trawler, liner and tramp alike? They are Marconi valves—When lives depend on a valve they choose Marconi.

MARCONI D.C. MAINS VALVES

Marconi D.C. valves are standardised by many leading set manufacturers on account of their unequalled economy and durability and consistently high efficiency. The range includes a type for every possible purpose,

each one fitted with the standard Marconi heater requiring only 0.25 Amp. at 16 Volts, giving a total power consumption of only about 60 Watts for the whole set.

We show here the curve for Marconi VDS, the new high-conductance Variable-mu type. Note how the amplification decreases evenly and smoothly with rising grid bias, and the enormous reserves of sensitivity, all under perfect control.


MARCONI D.C. MAINS VALVES

- DSB Screen Grid (Single Stage) ... 19/
- DS Screen Grid (Multi Stage) ... 19/
- VDS Variable-Mu 19/
- DH General Purpose 13/6
- DL L.F. and Power 15/
- DPT Power Pentode 20/

WHAT IS THE PURPOSE? —

WE HAVE THE VALVE!

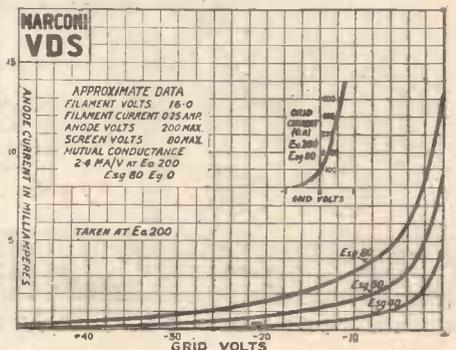Ask your local dealer or write direct to The Marconiphone Company, Radio House, Tottenham Court Road, London, W.1, for the Marconi Valve Folder which gives curves, facts and figures for all types of valves.



Advertisers Appreciate Mention of "A.W." with Your Order

On Your Wavelength!

THE LONG AND SHORT OF IT

IT is a great pity, I think, that so many set and component manufacturers label their wave-change switches "Long" and "Short," or simply "L" and "S." Already this is causing a certain amount of confusion amongst the uninitiated, and matters are likely to become a good deal worse when genuine short-wave wireless achieves the popularity that is sure to come its way as soon as the Empire broadcasting station gets into its stride. Not a few listeners of the kind that know little about the workings of wireless have come to me puzzled over this "Short" wave business. "My set," said one of these, "is supposed to receive the short waves, for the switch is so marked. I keep on reading about the wonders of short-wave transmissions, but I am told that I cannot tune them in with this set. Can you tell me why?" You see the kind of thing I mean. There is absolutely no excuse for the misuse of the term "short," for it is an accepted practice to call wavelengths below 100 metres, short; those between 100 and 1,000 metres, medium; and the remainder above 1,000 metres, long.

OTHER INSTANCES

THIS, though, is not the only case in which unhappily chosen names lead to confusion. Before the advent of the mains receiving set, it was customary to call the detector valve the rectifier. In the older wireless books and in early issues of *AMATEUR WIRELESS* and *Wireless Magazine* you will find this done as often as not. Then came the all-electric A.C. set with either a metal or a valve rectifier, whose purpose was, of course, to iron A.C. out into D.C. Most writers then saw the wisdom of calling this apparatus the rectifier and of using the term detector for the valve whose function is to convert H.F. into L.F. in the strictly wireless department of the set. We do, though, still continue to talk about this valve as the rectifier, which is a pity. Another unfortunate name is that of the condenser, which does not condense. And don't you hate the word "network," which occupies such a prominent place in the more high-brow type of wireless article? It is largely used to

describe systems of chokes and condensers, and anything less like a network than these I cannot imagine.

THE WORST OF ALL

THE outstanding case of confusion, not only in wireless alone, but in electricity as a whole, is that of the flow of current. Before anything was known about electrons, it was believed that current flowed from the positive terminal of a battery through an outside conductor back to the negative terminal. We know nowadays that a current travels in precisely the opposite direction and consists of an actual movement of electrons. It is impossible to obtain a grasp of the principles of, say, the wireless valve unless you realise that current does flow in this way. But all the old rules, many of which are still in use, for finding the polarity of electro-magnets and so on, postulate a current flow in a direction precisely opposite to that which actually occurs. These things badly require straightening out.

DUBLIN CALLING

YOU have no doubt observed that the Dublin station is often much more easily received than he was a short time ago. This is because the new big transmitter—situated, I think, at Moydown—is being brought into operation. So far as I can make out, he is not yet using full power or anything like it. When he really gets to work, the new Dublin station will be putting out 100 whole kilowatts, and the transmitting apparatus is arranged so that there will be no difficulty about increasing the power to double this amount if required. Dublin's wavelength of 413 metres is a pretty good one for distance-getting, and I prophesy that it won't be long before we find the Irish station showing a pretty hefty wipe-out in this country.

A PEEP AHEAD

ACTUALLY, before so very many months have passed there will be a super-power station on nearly every available channel between 413 and 550 metres. Munich is going up to 60 kilo-

watts and Vienna probably to 100. The new Berlin station will be a big fellow and I believe that Belgrade contemplates a big increase. As Brussels, Florence, Prague, the North Regional, Langenberg, Beromuenster, Rome, Stockholm, and Dublin are now all in the super-power class, you will see, if you examine the lists, that this means that every channel, except those used for groups of common-wave stations, will be occupied by a really big noise. Don't forget that there are quite a number of Russians preparing to lift up 50- or 100-kilowatt voices within the limits of the same band of wavelengths. The need for selectivity will become more and more evident.


STRANGE SECRETY

MY two morning papers for the day on which this note is written both tell me that the Post Office anti-pirate campaign has just been launched. One of them, though, speaks of G.P.O. vans as cunningly disguised and throws out hints about frame aerials made to look like step-ladders! (Help!) The second paper publishes a picture of one of these vans which is so cunningly disguised as to look exactly like . . . a Post Office detector van. In fact, both its back and its sides are plastered with placards warning pirates and asking whether *your* set is licensed. On the top of the van is something that looks suspiciously like a dummy frame aerial. I am all for fair and above-board methods in the campaign, and I am sure that nothing makes pirates stampede to the Post Office like the sight of an obvious G.P.O. van.

THE LOST TALK

SOMETHING that never happened before since broadcasting began occurred in the National programmes the other night. Listeners were kept waiting for fifteen whole minutes for a talk which in the end couldn't be given at all. Mr. J. B. Priestley was billed to give the first of a series of talks to "an unnamed listener." At the appointed time an announcer asked us to wait a few moments as the manuscript had been mislaid. And then for a quarter of an hour there followed the most impressive silence—one only wished that they could have turned the microphone on to the people who were engaged in making the search. It appears that, in accordance with the B.B.C.'s weird rule, Mr. Priestley's manuscript had been submitted for approval. It had been dealt with by some official who had left it under a pile of papers on his desk. Well, well, these little things will happen. But why on earth didn't somebody have the *nous* to turn on the gramophone during those fifteen minutes instead of leaving us in silence? If there isn't a gramophone available at Broadcasting House for use in emergencies of this kind, all I can say is that there ought to be.

PERSONALITIES OF THE WEEK'S PROGRAMMES

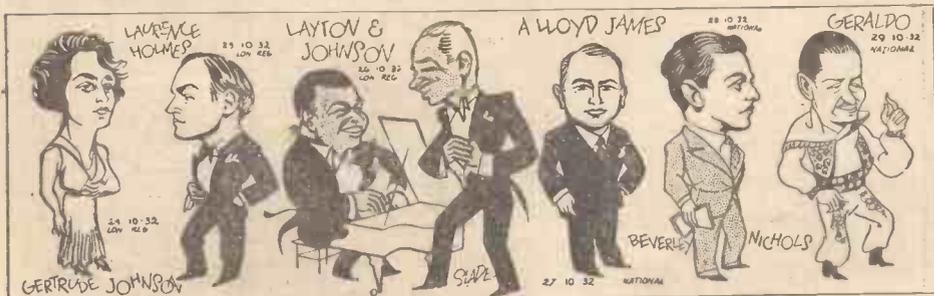

On Your Wavelength! (continued)

AN OUT-OF-THE-WAY FAULT

I HAD a breakdown with a battery set the other night that would have taken a bit of tracing if I hadn't had measuring instruments available for the purpose. The set simply became absolutely silent, and a careful examination of its wiring or stringent tests of its components would have disclosed no fault whatever. Actually, I was able to track down the defect in quick time, and I certainly couldn't have done so if I didn't make a habit of having always an ammeter in the low-tension leads and a milliammeter in the high-tension leads of the set. As both instruments showed zero readings, it was clear that this was an L.T. fault. A simple test proved that it wasn't located inside the set, and as the battery was known to be right up to the mark there was only one place left—the L.T. leads. These looked perfectly good, but there proved to be a complete disconnection in one of them. When the outer cotton covering of the wire was removed, it was found that there was a hole inside the rubber insulation which had allowed acid fumes from the battery to reach the fine stranded wires. These had been eaten away by corrosion until the lead gave out.

WATCH VALVE HOLDERS

AS a matter of fact, the most fruitful source of trouble in both battery and mains sets is, so far as my experience goes, that apparently harmless component, the valve holder. I don't know how many instances I have come across in the last twelve months of sets reduced to silence by "dud" valve holders. Over and over again I have dealt with sets which have been working perfectly for a long time, but refused to function at all when switched on one evening. It was quite clear that no part of the internals of the set had been touched; yet an examination disclosed a broken valve-holder contact. This kind of fault, unless you are expecting it when you come to examine a broken-down set, is not at all easy to track down. It may lead even the expert to burst into tears and fling handfuls of hair on to the carpet. The golden rule is always to use, not the terminals, but the *sockets* of valve holders when you are testing a set.

NOT SURPRISING

THERE is still far too much broadcasting of "National" items by Regional stations. It is not surprising, in view of the amount of this kind of thing that is done, that some Continental countries ask why on earth the B.B.C. wants nine separate wavelengths if it broadcasts the same items on all or most of them. When you come to think of it, the position is ridiculous. It is absolutely certain that nobody who can hear the London Regional is unable to tune in 5XX. What is the sense of giving the listener, not alternative programmes, but alternative

wavelengths for the same programme? In any case, it seems to happen pretty frequently that the Regionals are all sending out the same item. Looking at to-day's Midland Regional programme, for instance, I find that at midday it is "giving" this item to the London Regional, the North Regional, and the Scottish Regional. At 1.15 p.m., it is "taking" a concert from the North Regional, which is also taken by the London Regional and the Scottish Regional. At 2 p.m., the Scottish Studio Orchestra supplies the programmes of all Regional stations. From 2.40 p.m. to 3 p.m. the same station does the schools programme for all, and at 10.35 p.m. every station in the country, Regionals and Nationals alike, is sending out the same dance music. Is this kind of thing good enough?

PENNY WISE . . .

A PROPOS of a recent paragraph on long-lived valves, a correspondent makes the point that it is not always wise to run a valve to the very last limit. He cites his own experience with a valve which, after four years' useful service, began to show signs of decrepitude. The symptoms took the form of an occasional "crash" not unlike a strong atmospheric—though he tested this possibility by disconnecting the aerial. At all events, one evening the set suddenly went "dead." For a few seconds he thought the failure was due to a temporary breakdown at the transmitter, until an unmistakable whiff of burnt insulation made him spring for the set and switch off. It was found afterwards that the grid of the ancient valve had collapsed on to the filament.

TEN MILLION VOLTS

PRESSURES of this order are now being produced artificially at the G.E.C. laboratory in Pittsfield. The voltage is built up gradually and

then discharged in the form of a lightning discharge, which, for the fraction of a second it lasts, develops twice as much power as all the generating stations in the United States combined. The flash produced by a 10,000,000-volt discharge will easily split a large wooden post, and will fuse a tube of sand into a solid glasslike substance; similar, in fact, to the so-called thunderbolts or fulgurites found in nature. A close study of these artificial flashes tends to show that ordinary lightning is not an oscillating discharge, as was once thought, but a series of direct-current pulses repeated at short intervals.

D.C. MAINS VARIATIONS

I WONDER how many people realise the very large variations in voltage which may take place on an electric-light main. Just recently, I had to look at a D.C. mains set belonging to a friend of mine on which I found two of the valves defective. One had lost its emission entirely and the other had gone one better and blown up. I repaired this set and adjusted it on my own D.C. supply, which I make myself, and it was quite O.K. When I took it round to his house to install it, I found that the current through the valves, which were all run in series in the usual way, was appreciably greater than I expected; and investigation showed that the voltage on his supply instead of being 250, was actually over 270!

Now, by law, the supply companies are allowed a variation of + or - 4 per cent. Therefore, a 250-volt supply is allowed a 10-volt rise or drop, so that the voltage may be anything from 240 volts to 260; but in the case in question the percentage rise was nearer 10 per cent. than 4 per cent., and I had to provide my friend with a special resistance which he used during the day and cut out during the evening, for I found that at night time, when the lighting load came on, the voltage dropped to a respectable value.

WORTH INVESTIGATION

ON the other hand, of course, one may have a voltage correct during the daytime, in which case it may be 10 to 20 volts down at night, which will give poorer results. I believe it is worth while checking one's mains voltage occasionally, just to make sure that everything is O.K. Theoretically, you should be able to claim on the supply company, and if you have been wise enough to advise the company that you are operating a wireless set from your supply and have obtained their consent, then the company is liable for any damage which may result from fluctuation in the mains voltage over and above the stipulated 4 per cent. The "if" is a big one, because I have never yet met anybody who fulfilled his own contract and advised the supply company that he proposed to use a wireless set or any other apparatus. THERMION.

EUROPEAN BROADCASTERS TURIN

273-7 metres (1,096 kilocycles), 7 kilowatts. 578 miles from London. Relayed by Milan, Genoa, and Florence. Transmits at intervals from 7.15 a.m. Main programme starts at 6 p.m. Announcements in



Italian, the call being "Radio Milano e Torino," when the relays are made from Milan. Closes down with a Fascisti hymn and the Italian National Anthem.

OVER
75%

of the Units sold
in Gt. Britain to-day

ARE
EKCO



All models are similar in external appearance
Size 9" x 5" x 3 1/2"

Prices from
39/6
or by Easy Payments

1. Whatever your Set—there is an EKCO Unit for it.
2. Made to fit inside all portables—contact plugs recessed.
3. Connections a few seconds' work, and contact certain.
4. Patent bridge plugs make voltage variation simple.
5. High, Medium or Low voltage variation.
6. High or Low voltage output as desired.
7. Silent in operation—no hum.
8. Impossible to damage the D.C. Unit by short-circuit.
9. Westinghouse *Permanent Metal Rectification*.
10. Low running costs.
11. All Units conform to I.E.E. Regulations and Recommendations.
12. Extremely handsome appearance. Solid drawn steel case with an artistic oxidised copper finish.
13. Components and construction of the highest quality.
14. Made by the pioneers and specialists of ALL-ELECTRIC RADIO—we lead, others copy.
15. Easiest of Easy Payment Terms available.
16. Guaranteed for one year.

Every two seconds an EKCO Mains Unit is completely manufactured and sold.

To E. K. GOLE, LTD., (Dept. K.24).
Ekco Works, Southend-on-Sea.
Please send me illustrated FREE literature of EKCO All-Electric Radio.


Name

Address

EKCO
ELECTRIC POWER UNITS

Don't Forget to Say That You Saw it in "A.W."

TELSEN SCREENED TUNING COILS

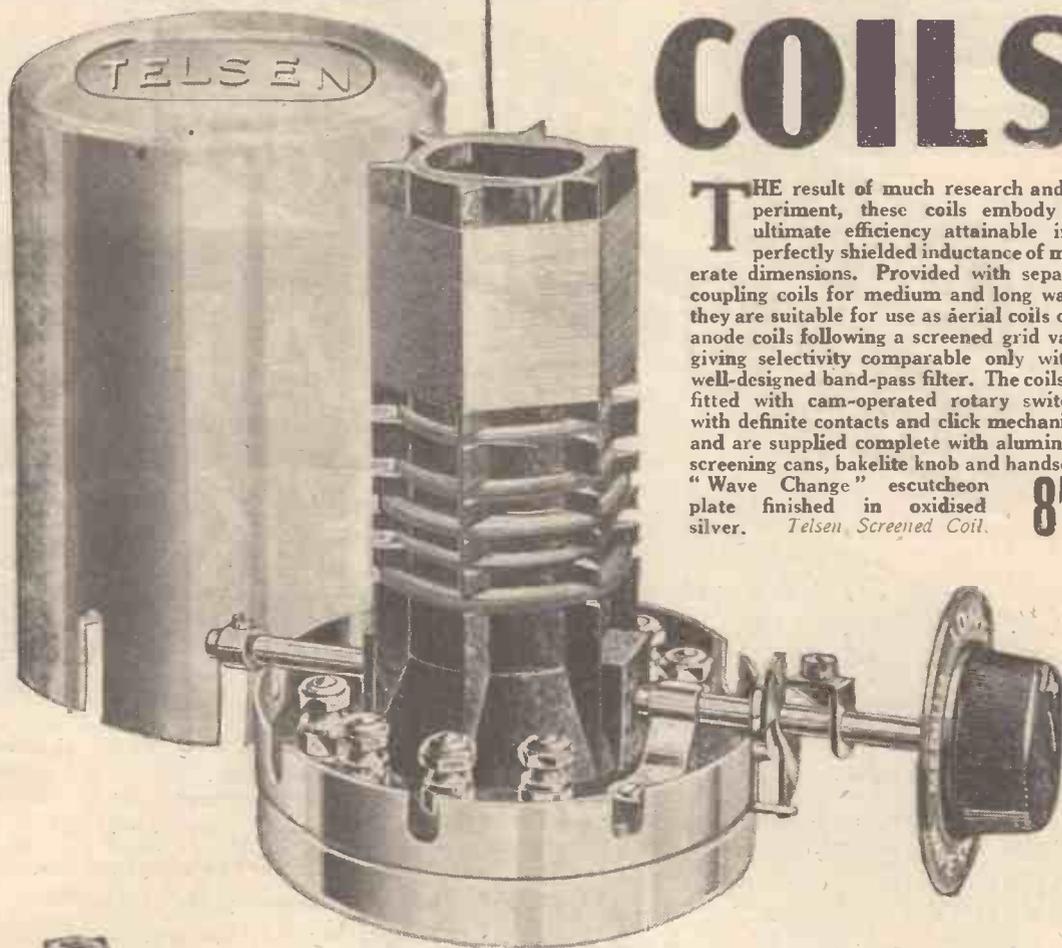

THE result of much research and experiment, these coils embody the ultimate efficiency attainable in a perfectly shielded inductance of moderate dimensions. Provided with separate coupling coils for medium and long waves, they are suitable for use as aerial coils or as anode coils following a screened grid valve, giving selectivity comparable only with a well-designed band-pass filter. The coils are fitted with cam-operated rotary switches with definite contacts and click mechanism, and are supplied complete with aluminium screening cans, bakelite knob and handsome "Wave Change" escutcheon plate finished in oxidised silver. *Telsen Screened Coil.* **8'6**



*Triple Matched
Screened Coils*
25/6

*Twin Matched
Screened Coils*
17/-

Full instructions are supplied with every Telsen Screened Tuning Coil, showing you the alternative methods of mounting the coils, either singly or in twin-matched or triple-matched form, as required.

TELSEN

RADIO COMPONENTS

BUY A COPY OF THE TELSEN RADIOMAG - PRICE 6d.

ANNOUNCEMENT OF THE TELSEN ELECTRIC CO., LTD., ASTON, BIRMINGHAM

Don't Forget to Say That You Saw it in "A.W."



USING THE SCREEN-GRID AS A DETECTOR

Our Technical Editor gives practical information of the conditions under which it is necessary to operate a screen-grid valve when used as a detector

DESPITE the fact that the screen-grid valve is becoming very popular as a detector, particularly in mains-operated receivers, there seems to be little definite information as to the best conditions under which the valve should be used. The advantages of the valve are an increased sensitivity over the ordinary three-electrode valve and a considerable reduction in the damping which the valve introduces into

volts, a series of tests were made with a screen-grid detector resistance—coupled to a valve voltmeter, as shown in Fig. 1. The value of the anode resistance was of the order of 20,000 to 50,000 ohms, but the actual value was varied for each reading until the voltage actually on the anode of the valve was 100. With the anode voltage kept constant in this way it is quite easy to select the optimum screen voltage and then to find the value of anode

able grid swing, and if this has to be done, the screen voltage must be increased. This involves a sacrifice of sensitivity and the designer must make his own compromise between ability to handle a strong signal without overloading and sensitivity to weaker signals.

Fig. 3 shows the variation between the L.F. output and the H.F. input, for two different values of screen voltage. The curve with the higher screen voltage will be seen to be less sensitive than the other, but it remains straight for a longer distance and will actually give out more volts on the L.F. side before it overloads.

The screen-grid valve may be used quite


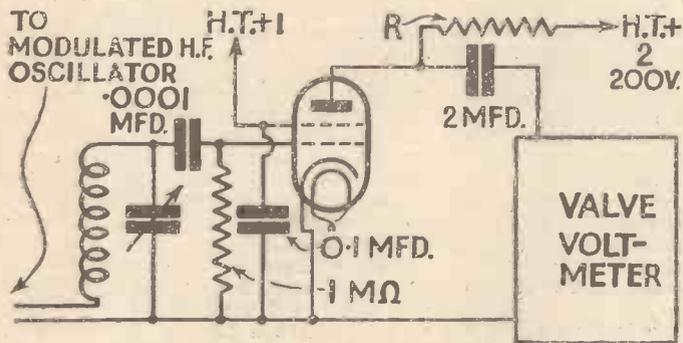


Fig. 1. A typical screen-grid detector circuit using cumulative grid rectification. The anode resistance should be 20,000 to 50,000


Fig. 2. Best results are usually obtained with somewhat lower screen voltages than usual, 30 to 50-volts being the average

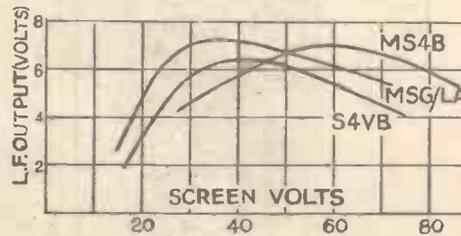

the tuned circuit just preceding it. Consequently this circuit not only tunes more sharply, giving better selectivity, but it also develops more voltage for a given signal, so that the increase in sensitivity is further enhanced.

A Sensitive Arrangement

The most sensitive method of using a screen-grid detector is as an ordinary grid rectifier. For this purpose the customary condenser and leak should be inserted in the grid lead and these can have values of .0001 microfarad and 1 megohm respectively. The operation of the detector, however, depends very largely upon the proper adjustment of the screen voltage. There will be found to be one particular voltage at which the signal strength is greatest and the actual value of this

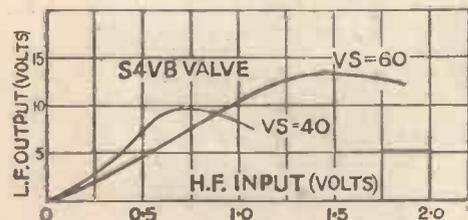

voltage depends very largely on the operating conditions. It is proposed in this article to give some idea of the manner in which the efficiency may vary.

Firstly, regarding this question of screen


resistance which will give these operating conditions.

Fig. 2 illustrates the variation of output voltage for a constant input. The voltage shown is the actual low-frequency voltage developed across the resistance R and it will be seen to reach a maximum at one particular value of screen voltage. The maximum is not sharply defined, however, so that an alteration of 10 volts either way will not make any material difference to the results.

The S4VB and MSG/LA require a much smaller screen voltage than usual in order to give good detector characteristics, while

Fig. 3. (left) Increasing the screen voltage beyond the best value causes the sensitivity to fall off but gives greater freedom from overloading

Fig. 4. (right) A typical anode-bend detector circuit. Owing to a reflex action in this circuit the rectification is practically linear

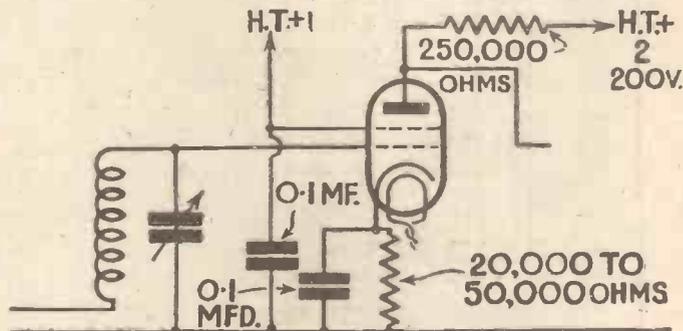

the MS4B operates well as a detector under its normal amplifying conditions.

Where there is no danger of overloading it is best to choose the optimum value of screen voltage. In many cases, however, it will be necessary to handle a consider-

ably increased anode current flows successfully as an anode-bend detector although there is not much advantage in this procedure. With A.C. valves, however one of the big bugbears of the anode-bend detector is removed. Fig. 4 shows an anode-bend rectifier circuit with the customary self-biased arrangement. Under ordinary conditions the anode-bend rectifier obeys a square law, so that if the input is doubled the output goes up four times, and this, of course, introduces distortion.

With the arrangement shown, however, the arrival of a signal causes the anode current to increase, due to the rectifier action. This increased anode current flows

through the bias resistance and increases the bias. The effect of this is to prevent the anode current from increasing as much as it would have done, and, in fact, the relation between the output voltage

(Continued on page 870)

THREE EMINENT EXPERTS DESIGN— THE NEW CENTURY SUPER



W. JAMES on THE MOST MODERN SET OF TO-DAY

A GOOD super-heterodyne receiver must be selective and also able to bring in stations with the least possible interference. Much, therefore, depends upon the first tuned circuit.

If this is of poor design, the chances are that, although the tuning is sharp enough, there are interferences which may tend to spoil the reception of certain stations. Tests prove that the best results are obtained when an input filter is used. This should have two circuits, and the usual ganging difficulty may be avoided by fitting a two-gang tuning condenser having, besides the main adjusting knob, a trimming control. There will then be no difficulty in tuning accurately, and in the "New Century Super" this has been carried into effect.

It is advisable to have in the aerial wire to the first circuit a pre-set condenser and to adjust this according to the size of the aerial and the locality. When near a local station the condenser may be set at a value below the maximum in order to reduce the input. A screen-grid valve makes an excellent first detector when fitted with a grid condenser and leak. The stability of the circuit is better than when a bi-grid or a three-electrode valve is fitted. There is, in fact, a marked all-round improvement. It is easy to adjust the valve, and the extra cost is more than compensated for.

A separate oscillator has proved to be better than the other arrangement in which the first detector works as an oscillator as well. For simplicity, the oscillator is best tuned with a separate condenser, but the oscillator coil can easily be coupled to the input filter coils, one switch knob controlling the three coils. This helps in making a neat layout, and the complications of gang tuning these circuits are avoided.

The tuning of the oscillator is always sharp, and so it is necessary to use a good slow-motion type tuning condenser. Accuracy here is important for the logging of stations. Thus it will be seen that, although the coils are controlled by a ganged switch, the condensers are not ganged, so that exact tuning may be obtained. The tuning of the "New Century Super" is very sharp, as it must be in these days for good results, but yet it is not tricky and not difficult.

The next important point is the method of controlling volume. When the second detector and output circuits are fixed, as is usually the case, the volume control actually varies the input to the detector. It works in the high-frequency circuit, and many attempts have been made to combine

PERCY W. HARRIS on SUPER THRILLS with the SUPER-HET

THIS article will, I am sure, be read by many readers of AMATEUR WIRELESS who, so far have neither built nor operated a super-heterodyne receiver. They are for this reason, in a very enviable position, for they have a great deal of pleasure coming to them!

It is easy to understand why the "super" has not achieved the same measure of popularity as the "straight" set. Until recently it could justifiably be said that this type of receiver was complicated and expensive to build, whatever the results might be. Those of us who have collaborated in the production of the "New Century Super" have, we hope, changed all this.

Modern valves are so good and modern "straight" circuits so efficient that you might easily fall into the error of assuming that nowadays a "super" is not worth building. Don't you believe it! A 7 H.P. car will take you from London to Cornwall in a day, but it is much more comfortable to go there in a Rolls-Royce. And one of the first things that can be said about the super-heterodyne is that it is the Rolls-Royce of Radio.

I have had many thrills with super-heterodynes. I remember one evening, a brand new super-het. was delivered to my room on the 13th floor of the Hotel Pennsylvania in New York. Five minutes after I had connected it up a wire fell into the "innards" of the set and blew eight brand new and perfectly good valves in one vivid flash. All the usual wireless shops being closed, I scoured New York and finally succeeded at half-past nine at night in buying eight substitutes from a United Cigar Store on Lower Broadway. I then set up until about two o'clock in the morning picking up station after station, all over the United States, even as far west as California.

That was an 8-valve set and every valve took a quarter of an ampere filament current. Our new "Super" has far fewer valves, takes far less current and is infinitely more efficient.

The charm of the "Super" which in our new design has been so simplified as to make it as easy to build and operate as a "straight" set is its immense reserve of power, the clear-cut supply of good quality reproduction free of background noises, and the fact that there is plenty of sensitivity to spare, when with an ordinary set the station you want would have faded down to inaudibility. The many faults which "supers" have had in the past, have been eliminated in our latest design and the co-operation of the component manufacturers



The production of the "New Century Super" is the result of the combined efforts of the three experts whose portraits are shown above: they are, W. JAMES (top), PERCY W. HARRIS (centre), and S. RUTHERFORD WILKINS.

**YOU CAN BE SURE OF THE
"NEW CENTURY."**

(Continued on page 875)

FULL DETAILS OF THE "NEW CENTURY SUPER" NEXT WEEK

OUR BROADCAST CRITIC

on VAUDEVILLE



TOMMY HANDLEY
who made a welcome reappearance last week

I HAPPENED to hear the second broadcast of *The White Blackbird* and found that it contained some clever characterisation, and also some very good playing. I thought William, played by Patrick Price, very well done. After the play was over I left the set on to hear an orchestral concert by Section D of the Orchestra. I was greatly entertained to find the microphone had also been left on, evidently by mistake. Some extraordinary sounds were emanating from the studio. One of the cellists had a good practice of some passage that was apparently worrying him. Then someone said: "I am now going to make a test." If that was not Dr. Boulton then I do not know his voice when I hear it.

Unfortunately someone found out that the microphone was on and we did not hear the test. Instead the announcer apologised for the delay. The concert began with Weber's *Der Freischütz*. I wish the B.B.C. would not translate those words by "The Marksman." Why not "The Freeshooter"? Much better translation.

I did not linger long. The horns so massacred the opening passage that I switched into the Regional. I listened to the London Singers whose singing I should have liked better had they been dead in tune. They were not so bad as the B.B.C. horns, but they were not quite up to their usual standard. As I have thus criticised them, I should add, in fairness, that their rhythm was beyond reproach.

There was a fine bass-baritone on the other night—William Heughan. I do not remember having heard him before. He sang absolutely in tune, which I always appreciate. The only complaint I have is that I only heard one word in four. However, that is a matter I put before him to correct for another time. A voice like his is really worth hearing.

GOOD VAUDEVILLE

I wonder what you thought of *House-Party*. Like all these extravaganzas it required one's patience in places. I can quite imagine that anyone coming into a room, switching on and listening to it might be inclined to switch off again immediately. I find the only way is to give each broadcast a chance unless someone sings or plays out of tune. Then I think there is only one thing to be done. I always do it.

There were two sets of impersonations in the Saturday evening vaudeville—one good and the other not so bad, putting it generously. The good one was given by

something worth saying with him. Comedians who rely on what they say, and not on how they say it, are worth a dozen of the other kind. The Spotless One was well up to form the other night. I hope he will come again soon.

There was an exceedingly funny turn in the Monday night vaudeville. In the programme a certain Mrs. Pullpleasure was advertised to play violin solos. Knowing what some of these violin solos in vaudeville can be, I was about to switch off for a while when something she said made me think she was trying to pull pleasure out of pulling my leg. I am glad I did not switch off because she was really brilliant. Having indignantly denied that she ever intended to play the violin, she proceeded to give a lecture on museums which was one of the funniest things I have heard for a long time. If you did not hear her, look out for her again. Surely you will not forget her name (or "nom-de-studio") Mrs. Pullpleasure!

Jeanne de Casalis was good as the friend visiting someone in a nursing home who had recently undergone an operation for appendicitis. I had a similar operation a few years ago. All I can say is that if "Mrs. Feather" had visited me and said half what she said to that friend of hers I should not be writing these notes. She frightened the poor soul into sneezing (with its attendant risks of bursting stitches) in a thoroughly typical way. "Mrs. Feather" is not so far from real life after all. I know one or two people who correspond to her!

Tommy Handley on encyclopedias was good. How he varies! It is with every respect to him that I say that. Sometimes I cannot laugh at him; sometimes I cannot do anything else. Anyhow, I congratulate him on saying a few really funny things the other night.

Did you hear the New English Singers? They took the Personal Hour on Sunday afternoon. As they are new—at least I suppose that is true, as I have not heard them before—I think it quite fair to prophesy concerning them. When they are a little more together, and a wee bit more evenly balanced, they will be one of the radio successes. The quality is there. Just a little better ensemble and they will be beyond reproach.

WHITAKER-WILSON.

PROGRAMME POINTERS

It is impossible not to make comparisons and to draw distinctions between those singers whose diction is beyond reproach and those whose diction demands reproach. The variation is so marked that I feel I must point to it. It is literally a fact that in some instances it is practically an impossibility to miss a word even if one is not listening intently. It is also a fact that in other cases—no matter how carefully one listens—a word here and there is all one can understand. I heard a singer recently of whom I was unable to write an acceptable criticism not merely because I could not hear her words, but because I had not the faintest idea what language she was supposed to be singing. I am not exaggerating. If an ordinary audition fails to separate the sheep from the goats, would it not be possible to use the Blattnerphone and make the singer listen to his—or more often her—performances? I believe that the Blattnerphone is not used for music in the ordinary way, but I imagine some sort of result might be obtained. Until some singers are made to realise how bad they are in this respect—and how good some others are—we shall not get much further. Good singing might be described as putting your words so vividly before your audience that they cannot miss them, and making a pleasant noise while you do it!

HAVE you ever been called on to provide some local club or function with loud-speaker gear so that public address announcements can be made, or so that gramophone records can be reproduced through loudspeakers?

This little assistance in social matters cannot easily be given with an ordinary set. The power output is not sufficient. What you need is a special power amplifier for the job, but here a snag crops up.

Most power amplifiers are greedy. They take so much high-tension that any possibility of working them from dry batteries is ruled out of the question. That means that either you have to get a mains unit suitable for the local supply, or else the amplifier be worked from high-tension accumulators. The B.B.C. nearly always works its power amplifiers from H.T. accumulators, but then the B.B.C. has a van to carry them about!

You will find their lack of portability a disadvantage. Moreover, they will probably have to be bought specially for the job, which makes the simple fitting up of loud-speaker gear for perhaps only one occasion so expensive a matter that the hon. sec. of the function will probably wish that the social committee had not asked for loud-speakers!

If you make up a really suitable and economical amplifier for this kind of work you will find that it has dozens of other uses. It is a good gramophone amplifier where more than usual power is needed. It can be used for out-of-doors speakers, provided the speakers themselves are fitted with directional baffles or of the horn type

FOR PLAYING YOUR GRAMOPHONE



The A.W. B.A.T. POWER AMP

PENTODES IN
PUSH-PULL!



to make the most use of the sound output.

WHY IT IS ECONOMICAL

The reason why this amplifier is so particularly economical, although giving a useful power output, is that its output stage consists of two pentodes in push-pull. The new pentodes are very economical, and if suitably biased the total H.T. consumption of this amplifier can be kept down to well under 10-milliampères. The steady D.C. is between 7 to 8 milliampères only.

You might think that the use of pentodes would mean a number of special and probably expensive components such as pentode input and output transformers, complicated decoupling arrangements and so on.

You have only to look at the photographs of the amplifier to see that there are no expensive components. The amplifier can be made up from parts, many of which the average keen wireless man will have

in his spare parts box.

The photographs show that there are no special pentode input and output transformers, and you will have to glance at the circuit diagram to see how these components

For the many occasions when you want a loud-speaker this useful big volume but economical amplifier and is so economical in high-tension consumption

have been dispensed with and how an ordinary L.F. transformer, a choke, and a few resistances and condensers have been made to take their place.

THE CIRCUIT—IT'S SIMPLE

The first valve of the amplifier is an ordinary triode, and in the grid circuit of this is the input volume control ganged up with the main on-off switch.

COMPONENTS YOU WILL NEED

CONDENSERS, FIXED

- 3—2-microfarad condensers (Lissen, Telsen, Dubilier, Wilburn, Ferranti, Formo, T.C.C.).
- 1—.005-microfarad fixed condenser (Lissen, Telsen, Dubilier, Formo, T.C.C.).

CHOKES, LOW-FREQUENCY

- 1—Centre-tapped output choke (Lissen, Telsen).

RESISTANCES, FIXED

- 2— $\frac{1}{2}$ -megohm wire-end grid leaks (Lissen, Dubilier).
- 1—20,000-ohm spaghetti resistance (Lewcos Lissen, Telsen, Sovereign, Bulgin).

POTENTIOMETER


- 1—250,000-ohm potentiometer combined with switch (Bulgin type VS20).

HOLDERS, VALVE

- 1—4-pin and 2 5-pin valve holders (Telsen, Lissen, W.B., Igranic).

TRANSFORMER, LOW-FREQUENCY

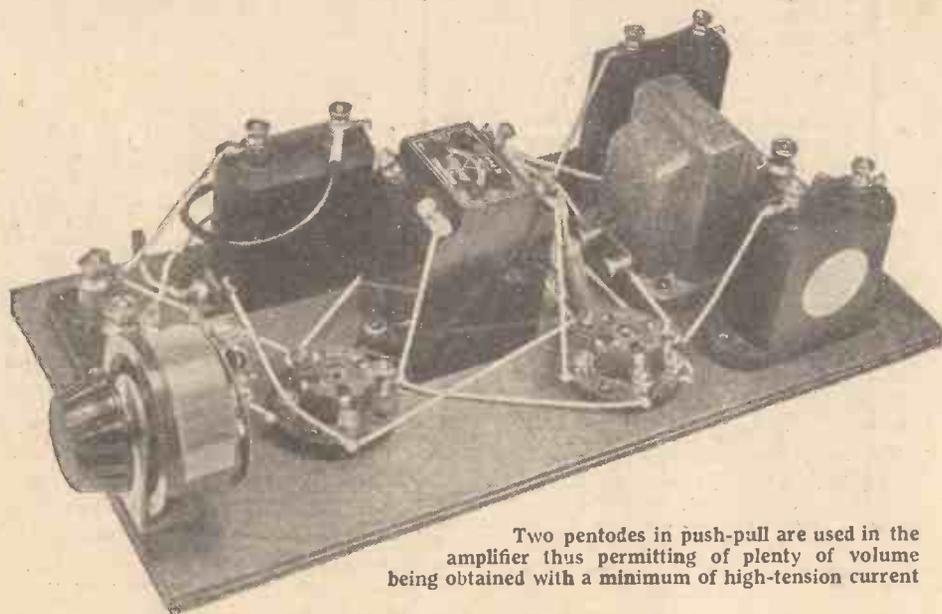- 1—Low-frequency transformer (Varley Nicore II, Lissen, Telsen, Igranic, Ferranti, Sovereign, R.I., Lewcos).



Two pentodes in push-pull are used in the amplifier thus permitting of plenty of volume being obtained with a minimum of high-tension current

ELECTRICALLY OR PUBLIC ADDRESS

BATTERY-OPERATED
AMPLIFIER

USES VERY
LITTLE H.T.



It dispenses with the usual tapped primary pentode output transformer. In this way it saves cost.

A choke and condenser system is used in place of a pentode output transformer. The choke is connected between the two anodes of the pentodes. The centre tapping of this choke is taken to the main H.T. tapping. Connected to each end of the choke is a 2-mfd. fixed condenser. The other sides of the condensers are taken to the loud-speaker output terminals and across these terminals

Two quarter-megohm leaks in series are connected across the G.B.—and grid terminals of the transformer—, that is across the whole secondary winding. The grid bias to the pentodes is applied to the join point of these two leads.

The screening grids of the pentodes are taken direct to a separate H.T. tapping so that they can be adjusted to be as economical as possible. This separate H.T. tapping could have been dispensed with and the screening grid voltage

obtained through a dropping resistance connected to the main H.T. tap. This would have necessitated further decoupling, however; would have made independent adjustment of the screening grid

voltage impossible, and would also have put up the cost. A single flex lead is cheaper than a dropping resistance and decoupling condenser!

NOVEL OUTPUT IDEA

The second novel scheme in the amplifier is the output arrangement.

is shunted a .005-mfd. fixed condenser for tone correction. In this ingenious way, you see, an ordinary tapped choke is used as the pentode output and the two 2-mfd. condensers pass the audio-frequency output to the speaker.

Constructionally, the amplifier is just as simple and ingenious as its circuit layout. The fact that it is cheap to build can be seen from an examination of the components list.

This gives details of the transformer, centre-tapped choke, ganged volume control and switch and the other parts needed for the amplifier. It also gives recommended accessories in the way of H.T. and L.T. supply, and speaker.

When ordering the components you will be well advised to get also a copy of the full-size blueprint which has been prepared in connection with this amplifier. It costs only one shilling post free, and can be obtained from the Blueprint Department, AMATEUR WIRELESS, 58-61 Fetter Lane, London, E.C.4.

A reduced reproduction of this print is given on page 852. This is to scale and so you can gauge the positions of the

peaker amplifier of more than usual power output, will do the trick. It uses pentodes in push-pull action that it can be worked from dry batteries.

its ends connected to the grids of the push-pull valves. In a circuit of this description there is no need to have the stabilising resistances which are sometimes put in each grid lead to cut out parasitic oscillation.


A novel scheme is the way in which the centre tap to the secondary of this transformer has been arranged so that bias can be applied to the grids.

D TO BUILD THE AMPLIFIER

- SUNDRIES**
Connecting wire and sleeving (Lewcos, Quickwyre, Jiffilinx).
Four yards thin flex (Lewcodex).
7—Wander plugs marked H.T.—, H.T.+1, H.T.+2, H.T.+3, G.B.—, G.B.—1, G.B.—2, (Belling-Lee, Clix, Eelex).
2—Spade terminals marked L.T.—, L.T.+ (Belling Lee, Clix, Eelex).
Small bracket (Wearite).
Baseboard, 12 in. by 6 in. (Peto-Scott, Camco).
2—Terminal blocks (Lissen, Telsen).

ACCESSORIES

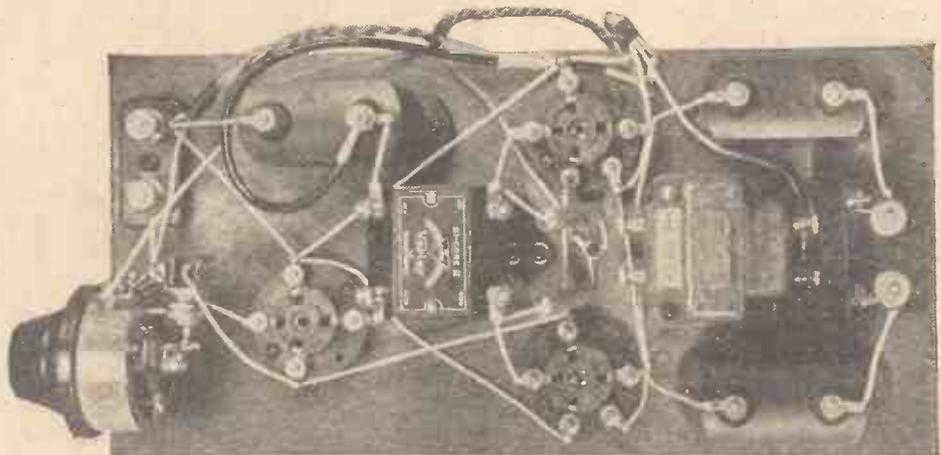- BATTERIES**
120-volt high-tension battery (Lissen, Drydex, Fuller, Ever Ready).
9-volt grid-bias battery (Lissen, Drydex, Fuller, Ever Ready).
Accumulator (Lissen, Exide, Fuller, Ever Ready).
LOUD-SPEAKER
Loud-speaker (Rola, Lissen, H.M.V., Blus Spot, W.B., Epoch, Celestion).




This plan view shows the simple construction of the amplifier, with all the components mounted on a baseboard

AN AMPLIFIER TO PLAY YOUR GRAMOPHONE ELECTRICALLY *(Continued)*

parts on the small plywood baseboard; but, of course, it is much easier to work with a full-size print and plot the mounting positions direct.

HOW TO BUILD IT

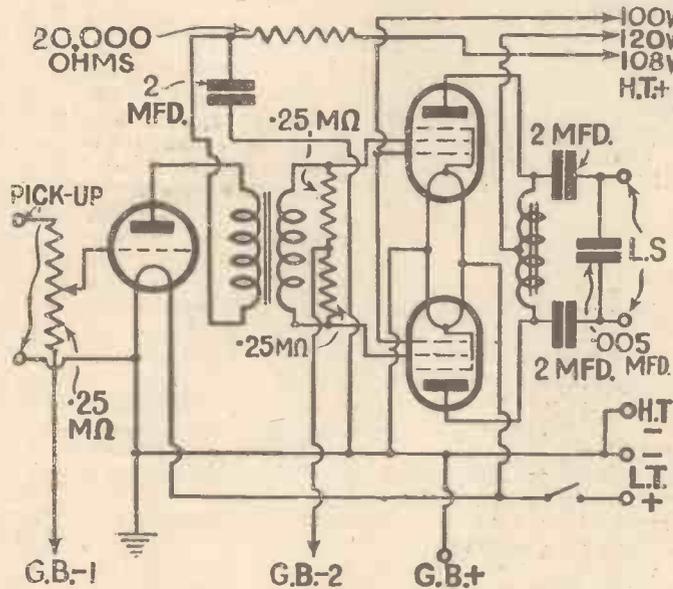All the parts are mounted on the 12 in. by 6 in. baseboard. There is no panel.



Although this amplifier has pentodes in push-pull, the circuit is quite simple. The input transformer has quarter-megohm leaks across the secondary, to avoid the necessity for a special tapped secondary transformer, and the output is taken through a choke and double condenser arrangement, so that no tapped output transformer is needed. These are factors which make the amplifier cheap to build.

Two terminal blocks are fitted, one at each end for the input and output leads. The three groups of battery flexes are taken direct from the various components on the baseboard. The parts are arranged in a logical order and more or less as you see them represented symbolically in the theoretical circuit diagram.

The ganged volume control and switch is mounted at one end of the baseboard close to the input terminals. The first valve of the amplifier is right at the back of the volume control, and at the side of this holder is its decoupling condenser and spaghetti resistance. The transformer which is used in the special way as a pentode input transformer is about in the centre of the baseboard.

The valve holders are arranged one on each side of the transformer, thus still further keeping the amplifier layout like the circuit diagram. A tapped choke is between them, near the other end of the baseboard, and the output condensers are arranged one on each side of the choke.

When you start the wiring, you will see that the two quarter-megohm leaks, by means of which a centre tap is obtained on the secondary of the transformer, are connected with their lower ends wired together under a spade tag. This is the tap of the grid bias lead which biases the pentode grids.

NO SOLDERING NEEDED

The amplifier is shown wired up on the point-to-point system, but as the leads are so direct it is possible to carry out most of the wiring without soldering. The only points where soldering is advisable are on the contacts of the ganged switch mounted on the volume control.

This control is mounted on an L-shaped aluminium bracket. The bracket must be screwed to the baseboard before the potentiometer is clamped to it.

The eight battery flexes are taken direct from the various components on the baseboard and when wander plugs and spade tags have been attached they can be twisted and held in groups by small pieces of adhesive tape at the ends of the twists.

CHOOSING THE ACCESSORIES

If you have wired up the amplifier correctly it should be all ready for working directly the batteries are connected up and the valves plugged in. Suitable batteries can be chosen from the accessory section of the components list, but quite likely you will test the amplifier out with the ordinary batteries of your set. Suitable valves

tapping on the choke) is taken to 120-volts. The anode lead from the first L.F. valve of the amplifier (which is connected to the 20,000-ohms decoupling resistance) is taken to the 108-volt point. The screening grids of the pentodes are given 100 volts.

GIVING IT BIAS

This bias on the first valve should not be too much. Probably 1½-volts will be sufficient with the average valve of the PM1HL type specified. The bias leads to the pentodes should be taken to about 4½ volts negative on the battery, as the valves of the PM22A class, working with 120-volts H.T. and 100-volts on the screening grid, not more than 4½-volts negative bias is generally needed.


Once you have adjusted the voltages correctly, the amplifier needs no further attention. As the volume control is turned up from the minimum position the amplifier is switched on and then the input is applied through the volume control.

If you find it necessary to alter the speaker output arrangements or to vary

SUITABLE TWO-VOLT VALVES FOR THE AMPLIFIER

	L.F.	Output (2)
Mullard ...	PM1HL	PM22A
Marconi ...	HL2	PT2
Osram ...	HL2	PT2
Mazda ...	HL210	Pen 220
Cossor ...	210HL	220 HPT
Six-Sixty ...	210HL	*SS230PP
Lissen ...	HL210	PT225
Triotron ...	SD2	*P215
Tungram ...	L210	*PP230
E T A ...	BY1814	—
Fotos ...	BC18	*BD100

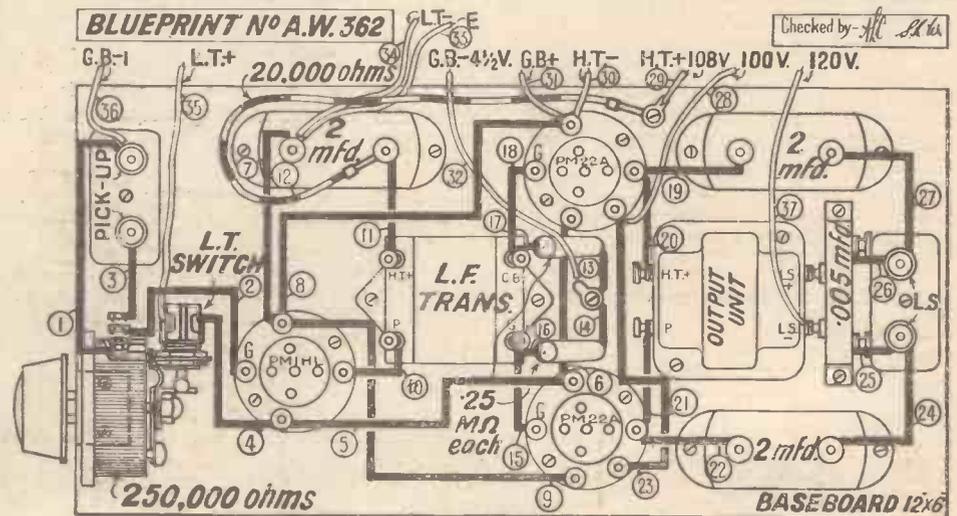Pentodes marked * are not low consumption.



A reduced reproduction of the layout and wiring blueprint. A full-size print is obtainable from these offices, price 1/-

are shown in the valve table, these being battery-type 2-volters of well-known make.

If the amplifier is worked from a 120-volt power type battery, then the main H.T. lead (the one going to the centre

the grid bias, switch the amplifier off first.

The amplifier can be seen this week in the Radio Department of Messrs. Selfridge and Co., Ltd., Oxford Street, London, W.1.

HOW STUDIO SOUNDS
ARE PRODUCED



The Twang of a Bow String



Test your radio reproduction by noticing how the twang of a guitar and the twang of a bow (produced in the studio by plucking elastic) sound. Does your set give you that gradual fading away of the reverberations, or is the sound quickly cut off so that it seems to have no tail to it? It is the tail of the twang that tells the tale of the studio. Best reproduction is built up of detail, and purity in your high tension current is absolutely necessary if you desire to have *detailed* reproduction.

No current is purer than the current of a Lissen Battery—no current is longer lasting—none flows so smoothly, none so noiselessly. Ask firmly by name for a Lissen High Tension Battery—every radio dealer sells it.



LISSEN^{H.T.} BATTERY

an exclusive process makes it last longest and provide a pure high tension current that gives realism to your radio—always

Please Mention "A.W." When Corresponding with Advertisers



HOW YOU CAN STOP INTERFERENCE

KENNETH ULLYETT describes some simple cures for man-made static. These can be effected on your set, and are the result of Post Office experiments in reducing interference

THE Post Office engineers checked up nearly ten thousand cases of interference last year and as a result of this experience they claim to have cures for practically every variety of man-made static.

If you are seriously troubled with local interference of this kind you can, of course, get the assistance of the Post Office experts by writing to the B.B.C. or direct to the Post Office. Before doing so, however, you will find it worth while trying a number of simple ideas for cutting out interference,

checked by some simple alteration to the aerial system.

H.F. Interference

H.F. interference is most troublesome and a more frequent source of trouble, to which about 90 per cent. of the cases of H.F. interference are attributed arises from the passage of H.F. strays into the mains wiring. The H.F. voltage imposed on the house wiring in this way may be only a few microamps, but if the aerial is anywhere near the mains wiring (or if the set is mains driven and the mains leads, therefore, run close to the set wiring) the interference can be considerable. The microvolts of interfering H.F. induced in this way can have the same effect as the field strength of a local transmitter!

The first step is to cut out any possibility of high-frequency interference getting to the set via the mains wires. If you have the electric light then you will be able to fit a simple filter, but if the electric light is only in a neighbour's house, then it will be necessary to get his permission to fit a filter.

The simplest filter for a direct current mains supply is shown by the theoretical circuit diagram, Fig. 1. It is easy to arrange. Take two 2-microfarad condensers of a voltage rating at least double that of the mains supply and connect them in series across the mains wiring of the house, as close to the meter as possible. The join point of the two condensers should be connected to earth and this earth connection should preferably be a short, direct one to the earth and not the earthing connection which is generally a part of the mains wiring. The Post Office engineers fit 600 microhenry chokes in series with each mains lead in bad cases of interference.

When you have stopped stray H.F. currents getting to the set through the mains wiring you can then start at the other end of the set and prevent induction of interference by the aerial.

There are bad cases where fitting a

counterpose earth (a series of insulated wires) in place of a proper earth connection does not affect a cure and the Post Office are making use of a simple way of cutting out man-made static induced through the aerial.

You can quite easily try this scheme. Lead covered copper wire as used for external mains wiring should be used for the aerial. There is no need to use the heaviest gauge lead-covered wire.

This should be strung up like ordinary aerial wire, and you should, of course, keep the direction of the aerial at right angles to any possible source of interference. The aerial should not run parallel with

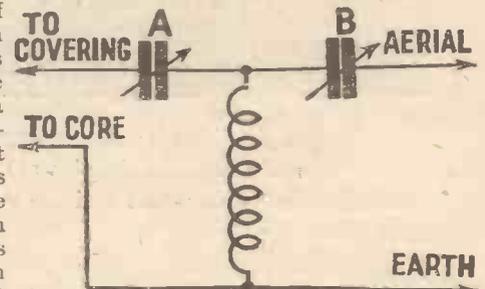


Fig. 2. A filter circuit which is put between the sheathed aerial and the set. A is the tuning condenser and B the coupler

tramway cables or power lines, for instance.

A Special Type of Aerial

Now for connecting up the special aerial to the aerial and earth terminals of the set. There are two ways of making use of the lead-covered aerial, these being shown by Figs. 3 and 4. Fig. 3 gives the better result, but it requires an additional tuned circuit which is shown separately by Fig. 2. The aerial of lead covered wire is brought close to the set, being carefully insulated all the way. The aerial terminal is connected to the core, while the earth terminal of the set is connected to the lead sheathing. No other earth is needed.

(Continued at foot of page 858)

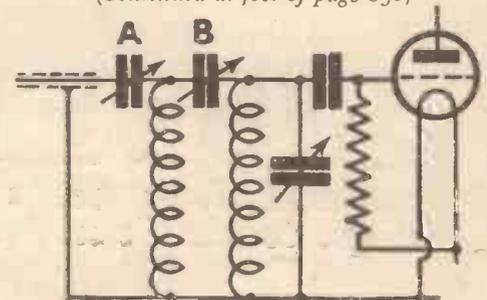


Fig. 3. A complete circuit using the sheathed aerial and the filter shown by Fig. 2



This shows one of the special sheathed aerials in part section. The covering of the wire is used as an earth and the centre core as the aerial

not at source (for the source is often difficult to trace) but on your own set.

These schemes for reducing local interference are based on the Post Office experiments and you will thus have a good idea of whether it is possible to cut out the interference by simple alterations to the

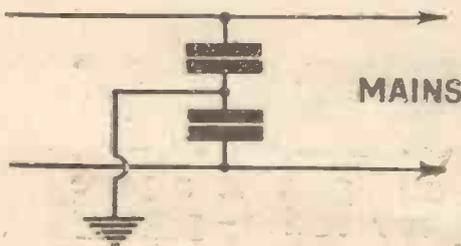


Fig. 1. A simple filter circuit to by-pass H.F. interference on electric light wires. The centre connection between the two condensers is earthed

H. T. Current $1\frac{1}{2}^D$ per week

for less than

20 MILLIAMP OUTPUT **27¹/₆** D.C. MODEL "A"



FROM THE FOUR TYPES OF LISSEN ELIMINATORS MENTIONED ON THIS PAGE YOU CAN CHOOSE ONE WHICH EXACTLY SUITS YOUR SET.

Low first cost is practically your only outlay because the cost of running a Lissen Eliminator is so small that your meter will hardly register the current it takes. No current from any eliminator is smoother or more silent than the current of a Lissen Eliminator. No eliminator output is more constant, none is so free from hum. Every Lissen Eliminator will deliver—

Yours for
5/-
DOWN

20 mA Output in perpetuity—

sufficient H.T. current to feed the largest receiver, with the biggest power valves you are ever likely to use.

Large smoothing chokes—big condensers—no chance of motor-boating. Decoupling arrangements incorporated in every eliminator—you connect the Lissen Eliminator almost as you would an H.T. battery. Everything has been thought out for you—you simply put the eliminator in. Lissen have made eliminators safe by totally enclosing all the current-carrying parts in high-grade insulating material—see also the thickly insulated "cab-tyre" flex.

EASY TO CHOOSE

The type you want is easy to choose. Your dealer will help you, or write direct to factory.

EASY TO BUY

Every Lissen Eliminator is available for a small initial payment and easy gradual purchase terms.

D.C. MODEL "A"

100/110, or 200/250 volts. Cash price 27/6. Or 5/- down and 5 monthly payments of 5/6.

D.C. MODEL "B"

100/110, or 200/250 volts. Cash price 39/6. Or 5/- down and 8 monthly payments of 5/-.

A.C. MODEL "A"

100/110, or 200/250 volts. Cash price 60/-. Or 5/- down and 10 monthly payments of 6/6.

A.C. MODEL "B"

100/110 or 200/250 volts. Cash price 75/-. Or 5/- down and 10 monthly payments of 8/-.

LISSEN A.C. OR D.C. ELIMINATORS

You will Help Yourself and Help Us by Mentioning "A.W." to Advertisers

ALL ENGLAND NOW

The ONLY set employing metallised Screened Grid Valve, High Mu Detector and Economy Power Pentode



KIT INCLUDING METALLISED SCREENED-GRID, HIGH-MU. DETECTOR & ECONOMY POWER PENTODE VALVES


89/6

There never has been the equal of this set within the range of the home constructor—this new Lissen Skyscraper is the only one on the market that you can build yourself, employing Metallised Screen Grid, High Mu Detector and Economy Power Pentode Valves. No factory—however well-equipped—can build a better receiver. No manufacturer, however large, can produce a receiver whose results will surpass those you will get from the Lissen Skyscraper you build yourself. It is the only battery set that can deliver such power—yet the H.T. current consumption is far less than that of the average commercially designed 3-valve set.

Yet the Lissen Skyscraper is made simple for you to build. Elaborate care has been taken to ensure your success by giving—in the Skyscraper Constructional Chart—such detailed instructions and such profuse illustrations that everybody, with no technical knowledge or skill at all, can build it quickly and with complete certainty of success.

**THE MOST SUCCESSFUL SET EVER BUILT!
THE MOST SUCCESSFUL CHART EVER PUBLISHED!**

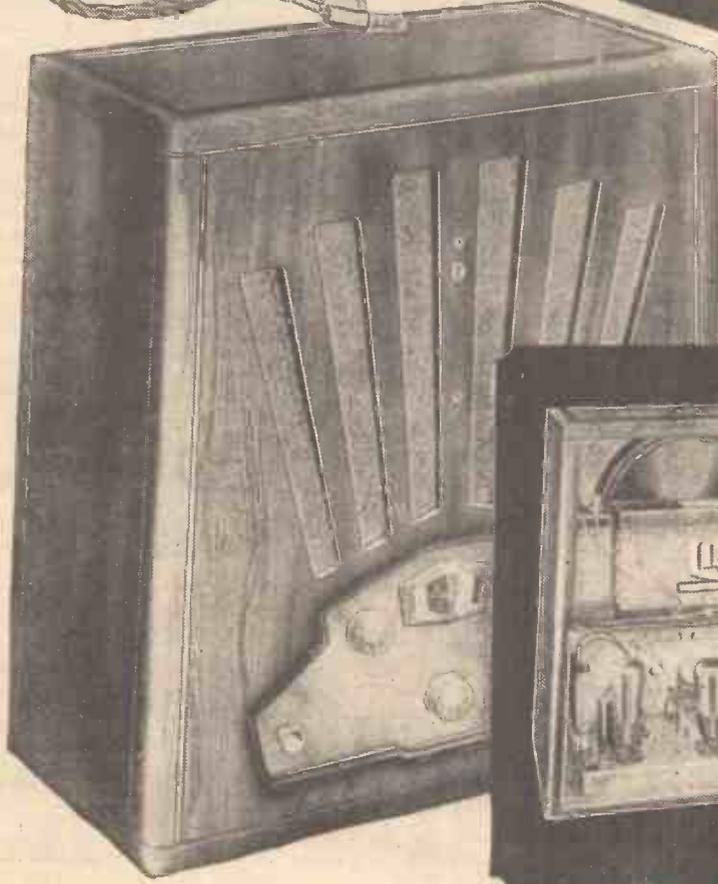You buy the Lissen Skyscraper Kit complete with valves—a Lissen Metallised S.G., a High-Mu Detector, and a Lissen Economy Power Pentode Valve—and the price is only 89/6. Or you can buy the Lissen Walnut Console Skyscraper Cabinet and Loudspeaker combined as illustrated.



It holds all batteries, and accumulator and loudspeaker as well. It makes everything self-contained. A special Pentode Matched Balanced-armature Loudspeaker of great power is supplied with the cabinet and the price of the Skyscraper Kit complete with valves and this cabinet and loudspeaker is only £6 5s.

COMPLETE WITH WALNUT CABINET AND LOUDSPEAKER

£6 5s

Mention of "Amateur Wireless" to Advertisers will Ensure Prompt Attention

BUILDING THE SKYSCRAPER

GREAT LISSEN CONSTRUCTIONAL

CHART

Free!



TELLS EXACTLY WHAT TO DO WITH EVERY SINGLE NUT AND SCREW

COMPLETE WITH 89 1/6 VALVES

COUPON


To LISSEN LTD., Dept. A.W.7, Worple Road, ISLEWORTH, Mddx.

Please send me Name.....
FREE copy of your 1/- Skyscraper Chart Address.....

..... A.W.7

Don't Forget to Say That You Saw it in "A.W."

THE CONCERTS AT BROADCASTING HOUSE

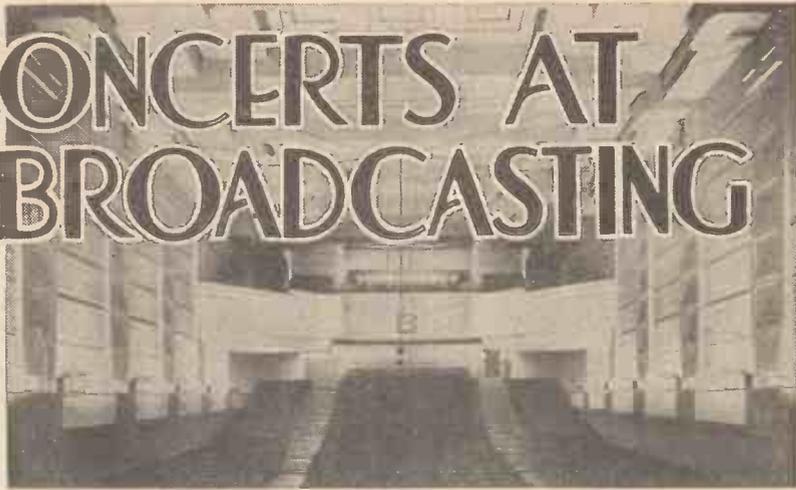

I HAVE a B.B.C. announcement before me to the effect that on Saturday, October 15, a Chamber Music Concert was to be given in the Concert Hall at Broadcasting House. It is the first public concert in the new building. Tickets could be had at prices varying from 7s. 6d. down to 2s. The players were the members of the Catterall Quartet and the programme comprised favourite quartets by Haydn, Mozart, and Schubert. John Coates also sang two groups of English songs, one Elizabethan and the other modern.

I had a good look round the concert hall at Broadcasting House a few days ago. Undoubtedly, it is very suitable for chamber concerts.

Its shape is irregular. It is much broader at the balcony end than at the stage end. The fixed platform is quite narrow, but there is an extension which will accommodate the B.B.C. Symphony Orchestra. None too comfortably, I imagine, but it can be done. The lighting arrangements are a feature of the hall. They can be seen at the side in the accompanying picture, and consist of rather quaint glass panels in which powerful lights are placed.

The hall—at least, when empty—is singularly peaceful. I went into it with a member of the B.B.C., and we remarked how extraordinarily restful the effect was. The seating accommodation is for 538 people in addition to the full orchestra.

On the western wall, directly under the lights, are six friezes of which the carvings

are of classical scenes representing poetry, dancing, a ball game of some kind, a foot race, a sacrifice, and music. The poetry scene shows the winged horse Pegasus unsealing the spring of Poetry. He is rather like your old rocking horse, but the scene is not amiss. The ball scene rather intrigued me. Odysseus is represented watching Nausicaa and some companions playing ball. All I can say is that they will never catch the ball in their present attitudes. It couldn't be done!

The foot race represents Milanion conquering Atalanta. I don't wonder. Atalanta sadly needs training.

In the course of my work I meet many musicians and hear a good deal of opinion. The times are hard for musicians and everyone is complaining—at least, those who earn their living largely on the concert platform—that the B.B.C. is strangling them inch by inch. Whether that is quite true or not I am not prepared to say. On the other hand, I think I see the point of view. Nowadays if you are to be anybody in the musical world you must work for the B.B.C. Precious little else is being done.

Musicians complain that the B.B.C. calmly goes on its way, retaining those who have been fortunate enough to gain admit-

tance within those marble halls. It is being said that the outsider stands no chance. Others say that they are asked to broadcast once in two years and are paid four guineas for the privilege.

It is obvious that the B.B.C. cannot employ the entire musical profession.

Broadcasting certainly caused a deep depression in the music teaching world. Bad times generally, of course, did not tend to improve matters. A teacher with a large practice told me he had lost over two hundred a year owing to pupils having given up learning. I told him I did not wish to depress him, but I thought that figure might be doubled because of those pupils who *would* have come to him, but who did not.

I do not think it fair to put all the blame on the B.B.C. On the other hand, I sincerely hope that Broadcasting House will continue to do everything possible to relieve the situation, which is undoubtedly grave. Perhaps the day will come when the B.B.C. will hold out a helping hand by going to the other extreme and "commandeering" all concerts throughout the country. It might be possible in that case to offer employment. On the other hand, it might not. Still, there it is. Broadcasting House is running a concert, probably the first of a series. You can buy tickets and go if you wish or you can stay at home and hear it that way.

WHITAKER-WILSON.

"HOW YOU CAN STOP INTERFERENCE"

(Continued from page 854)

In the scheme of connections shown by Fig. 4 the aerial is connected through a



Another type of sheathed aerial wire with part of the covering removed to show the arrangement of the core

with the coil or coils in the set. The condenser A should be an ordinary .0005 tuning condenser and the condenser B can be a pre-set with a maximum value of .0003 microfarad.

When first setting up this aerial arrangement, unscrew the pre-set condenser, so that there is the least possible coupling between the aerial and the set. In all probability the addition of this special filter circuit will alter the dial readings on the set by a few degrees.

The connection scheme shown by Fig. 4 is easier to work as there is no independent tuning. The lead sheathing is connected direct to the earth terminal of the set (the normal earth being disconnected) and the core of the wire is taken through a .0003-microfarad compression condenser to the aerial terminal.

coupled circuit. The coil of this should be an ordinary dual-range coil to match up

If your set does not use screened coils, then you will probably find it necessary to

fit screening cans on these, or to line the set cabinet with metal foil, in order to cut out direction induction by the coil.

Using Reaction

The special aerial system shown may entail a slight loss of sensitivity, but this can usually be counteracted by increasing reaction. This can safely be done as there

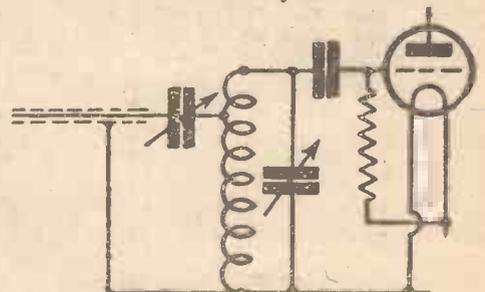




Fig. 4.—A simple way of using a sheathed aerial without an intermediary filter circuit. The core of the aerial wire is taken through a coupling condenser to the grid circuit of the first valve

will be a noiseless background free from interference.

IGRANIC QUALITY COMPONENTS

The quality of your reproduction depends upon the quality of your components. You can be certain of both if you use Igranic components. Nothing is left to chance in the designing, construction, and finishing of this Igranic T.24B Transformer. The primary inductance of this transformer is high, permitting a high amplification of bass notes, whilst at the same time reproducing faithfully all notes over the whole scale of musical frequencies. Supplied in two ratios 3 : 1 and 5 : 1.

Price **5/6**

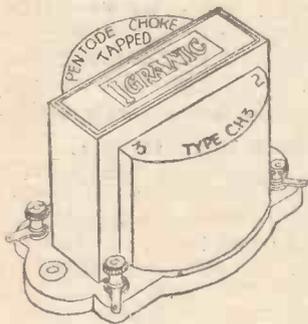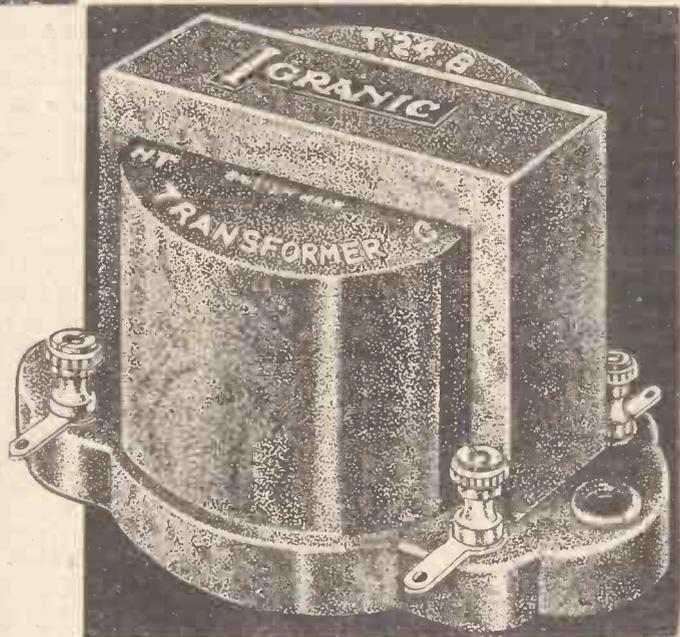

PENTODE TAPPED CHOKE

The Igranic Pentode Choke is designed so that the impedance of various types of loud-speakers may be matched to that of the pentode valves whilst keeping the inherent self capacity of the choke at a minimum.

Price **10/6**



TAPPED 'C.C.' OUTPUT UNIT

Invaluable for receivers employing a power output valve. It prevents demagnetisation and makes possible a closer adjustment of loud-speaker movement. Designed to pass a maximum current of 30 milliamps.

Price **12/6**

Write to-day for fully illustrated Catalogue No. D. 170 of complete new range of Igranic Quality Components.
Igranic Electric Co., Ltd., 149, Queen Victoria Street, London, E.C.4

**IGRANIC
COMPONENTS WILL
BE THE MAKING
OF YOUR SET.**



SEND FOR THE 1932 CATALOGUE

Please Mention "A.W." When Corresponding with Advertisers



A Curious Fault

SIR,—I think the following experience may be of interest to some of your less experienced readers. I was recently asked to examine a well-known manufactured battery set mounted on a metal chassis.

The on-off switch was constructed of a brass rod threaded into an ebonite bush with the contact point threaded on the other end. Through constant use this rod had worked down the ebonite bush until it came into contact with the contact point and consequently, owing to the metal chassis being earthed, the whole lot was shorting; the switch got very hot and the L.T. flex melted. It was very difficult to detect where the shorting was occurring because the actual point was hidden by the ebonite bush.—B.J.D. (Bristol).

Collecting the Volts

SIR,—With reference to Thermion's recent note "Collecting the Volts" ("On Your Wavelength") I thought, perhaps, the following would interest you.

I am employed on the mains department of an electricity supply undertaking and we had a report come in that the metal cover of a pit in the pavement was "alive."

Upon investigating this, we found that the shock was only obtained if one touched the omnibus that pulled up in the vicinity. In this case the shock was considerable and quite a loud "crack" could be heard as the contact was being made. The situation of the occurrence was at the foot of Crouch Hill, Hornsey, N.8.

L. H. L. (London, N.).

A Grid-leak Point

SIR,—Being a wireless constructor I naturally take a keen interest in components. I have always been in favour of having the wire soldered on to grid-leaks ready for wiring into circuits but there is one point manufacturers seem to have overlooked, namely, that the grid-leaks are not supplied with insulating sleeving for protection against short circuits when the points of connection are far apart. The extra sleeving would not cost much and would certainly save the "rending of hair" when one finds that the grid-leaks have caused a valve to burn-out through the bare wire touching a wire at high potential.

F. N. B. (Stratford).

What Our Readers Think

The Editor does not necessarily agree with the views expressed by readers and does not accept responsibility for the letters published. Letters cannot be published which do not bear the sender's full name and address



Power Limitation

SIR,—I was much interested in Thermion's recent remarks on the question of high-powered broadcasting stations. I entirely agree with him that the best thing the Madrid Conference could do would be to limit all stations to a power of 10 k.w.

In this district interference from foreign stations at night is almost intolerable. Even the most expensive S.G.3's (commercial sets, as well as home constructed) sometimes have difficulty in separating Mühlacker from London Regional; and this, not because of the power of the Regional station, but because of the colossal power of Mühlacker.

Every medium-wave British station suffers very badly here from fading, and really the only satisfactory reception that can be obtained is from Daventry National.

J. G. D. (Southwold, Suffolk).

Accumulator Charging Methods

SIR,—I am glad to see from articles in **AMATEUR WIRELESS** that you are doing your best to enable your readers to obtain satisfaction from their low-tension accumulators. This is a great deal more than the average so-called charging station does. I have seen batteries returned in the most disgusting condition; terminals corroded, the tops of cells awash with acid spray, and very often short of distilled water. I have seen cells practically ruined through charging at too high a rate, and being filled with acid of the wrong specific gravity.

H. K. A. G. (Battle).

Faulty Components

SIR,—I read with much interest Thermion's caustic comments upon American sets and valves, and particularly his query on page 494, "Can you beat it." In view of his invitation I feel myself justified in troubling you with this letter.

Whilst I hold no brief whatsoever for American manufacturers, I am of the opinion that some of our English manufacturers have but little to pride themselves on, unless of course my experience is an exception.

In November last I decided to build the "A.W." Britain's Super, and to that end purchased a kit of parts. In due course I assembled the kit and found trouble at

The Editor invites letters from readers on all interesting radio subjects. For the most interesting letter published each week a general-purpose valve or other component to the same value will be given.

once. I eventually traced it to two sources, a faulty coil and a gang condenser. These components were returned and exchanged. The set then worked, but not at all satisfactorily, particularly the band-pass coil. I took this off the baseboard and found that one of the wires underneath was to all intents and purposes broken. With the aid of solder I repaired it. Some little time later it went wrong again, and eventually I returned it to the makers who replaced it with a new one within a few days. From the commencement of working of the set I had trouble with one of the valves—intermittent silence. It was eventually traced to the screen-grid valve of a well-known make, and I was informed by one of their representatives that on test there was nothing wrong with it, and I was also given the gratuitous information that it was as good as the day it left the factory. I replaced it in the set, and still the same trouble occurred. I bought a new valve and the trouble ceased. I subsequently sent the valve to the makers, and was then informed that on test at their London depot it was found that the filament was sagging, and would have to go to the works for a further test. After an interval of many days a new valve was sent. I am still wondering what will be the next defect, but at present the set is functioning satisfactorily.


C. H. (London).

The True Road to Radio (Ferranti, Ltd., 5s. net).—This is the title of a comprehensive book, the third edition of which has just been published by Ferranti, Ltd. In its 245 pages it deals in an interesting way with the technical side of wireless, giving facts and figures in connection with H.F. and L.F. amplification, detection, rejectors, power output, mains supply systems, and the design of radio circuits. It is a handsome production, being well bound, printed on art paper, and profusely illustrated. In this third edition, a number of alterations have been made, a good deal of information about band-pass circuits has been included, and the section dealing with H.T. supply units has been extended to include the latest type of valve rectifiers and details of automatic grid bias arrangements. Copies of "The True Road to Radio" can be obtained, price 5s. from Messrs. Ferranti, Ltd., Hollinwood, Lancs.

The new wing of the National Museum of Wales, Cardiff, will be opened on October 25 by Prince George. The proceedings will be relayed on the West Regional wavelength. They will also be relayed to the North Regional transmitter for the benefit of listeners in North Wales.

TELSEN LOGARITHMIC CONDENSERS


and DRUM-DRIVE

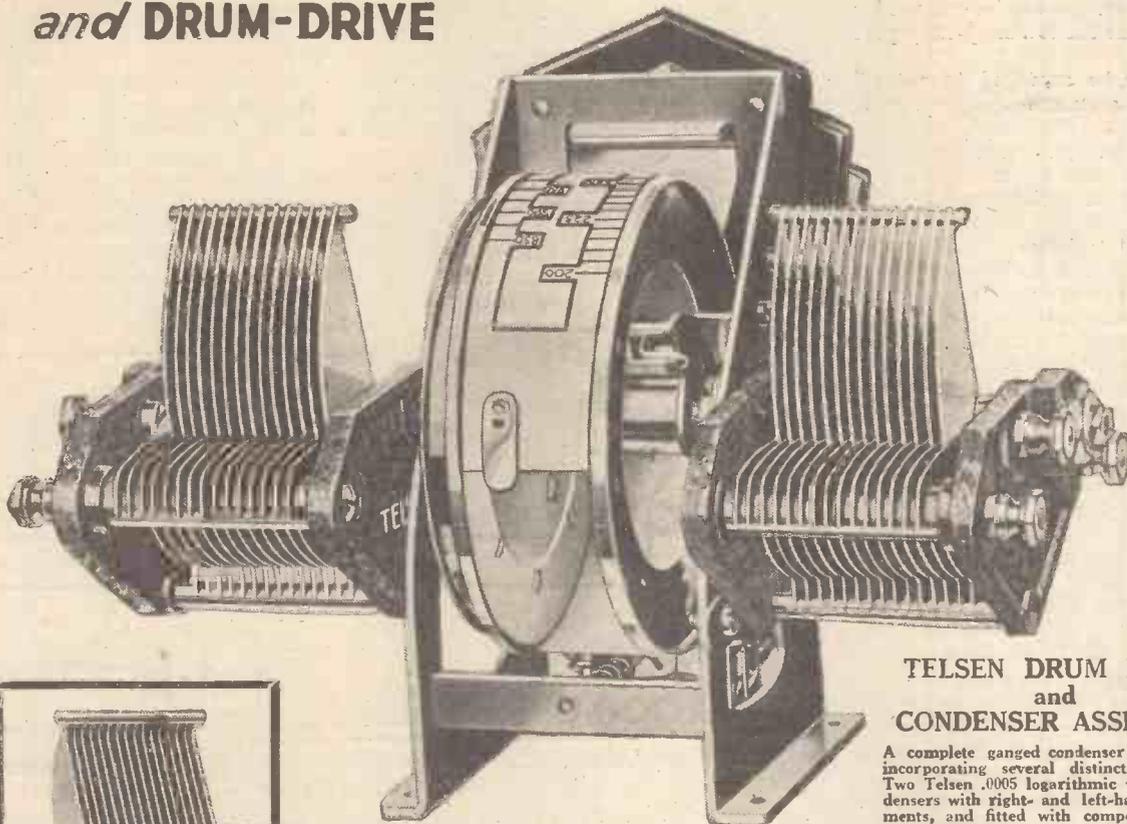

TELSEN DRUM DRIVE and CONDENSER ASSEMBLY

A complete ganged condenser tuning unit incorporating several distinctive features. Two Telsen .0005 logarithmic variable condensers with right- and left-handed movements, and fitted with compensators, are mounted and ganged together through a rigidly constructed drum-drive control. Mounted on the same spindle axis as the main tuning drive is a trimmer, giving a swinging movement of about 20 degrees to the stator vanes of the right-hand variable condenser, enabling perfect matching of the condensers to be maintained throughout the tuning range. Two scales are supplied, one marked in wavelengths and one in graduations from 0-100. The scale is illuminated and is easily removable when it is desired to fit one of special calibration. The escutcheon is handsomely finished in oxidised silver, with knobs of the push-on type. Provision is made for panel and baseboard mounting; full instructions for mounting, together with a double-ended spanner for fitting the variable condensers, are included with every unit.

17/6

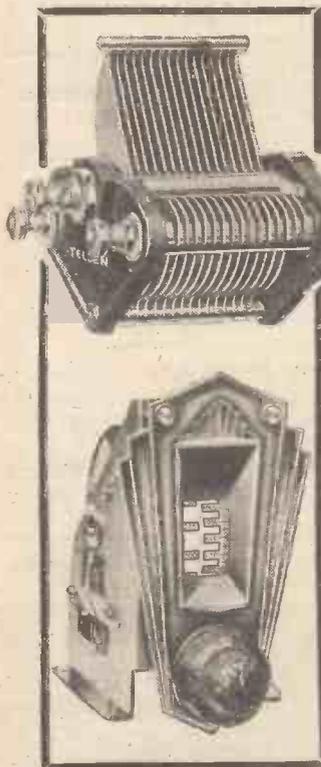

TELSEN LOGARITHMIC CONDENSERS

The frame is braced by three solid pillars, and the vanes clamped at three points, making distortion impossible. The rotor is also built into a rigid unit, the vanes being held at both ends. Generous bearings obviate backlash or end-plate. Models with left-hand and right-hand movements respectively incorporate a compensator (max. cap. 60 micro-microhenrys).

Cap. .00025	4/6
Cap. .00035	4/6
Cap. .0005	4/6
Cap. .0005	(left-hand movement with trimmer)	5/-
Cap. .0005	(right-hand movement with trimmer)	5/-

TELSEN DRUM DRIVE

Embodies numerous refinements, including a cord drive, arranged to reduce wear to a minimum and to prevent over-run, and a rocking stator trimmer, which gives a variation of 20 degrees, and visual indication of setting. For use with Telsen screened coils, an extra scale, marked in wavelengths, is supplied free. Illustration shows escutcheon, handsomely finished in oxidised silver. 8/6

TELSEN
RADIO COMPONENTS

BUY A COPY OF THE TELSEN RADIOMAG - PRICE 6d.

ANNOUNCEMENT OF THE TELSEN ELECTRIC CO., LTD., ASTON, BIRMINGHAM
To Ensure Speedy Delivery, Mention "A.W." to Advertisers

IN MY WIRELESS DEN

WEEKLY HINTS—

CONSTRUCTIONAL



& THEORETICAL

BY W. JAMES

CUTTING OUT WHISTLE

A GOOD deal of the mush and high-pitched whistles heard when tuning to some distant stations can be cut out by including a filter in the low-frequency part of the set.

The filter may be arranged to cut off notes of above a certain frequency and it therefore clarifies the results. With sharp tuning circuits there is, of course, a cutting of the higher notes, but the results are not the same as when a satisfactory filter is used.

The filter ought to be connected to the detector circuit, for then the low-frequency amplifier or power stage will not have to handle the high notes unnecessarily. There is no sense in connecting the filter to the power stage, in the loud-speaker circuit, for instance, if it is possible to connect it to the detector and so avoid having the power valve deal with the unwanted signals. It is possible that the mush and interference will fully load the power stage, even though the wanted signal is relatively weak, but this cannot happen when the filter is joined to the detector. Many sets would be all the better for the addition of a filter, and if this is a good one the quality of the reception as judged by listening to the local stations, will not be affected.

WATCH THE ANODE CURRENT

WHEN a power valve having a good slope is used it is necessary to adjust the grid bias very carefully. The reason is that the anode current is varied by a large amount with a small change in the bias.

If you tested by listening only, you might easily use too little bias, with the result that the anode current would be more than necessary. The best method is, of course, to use a milliammeter in the plate circuit of the power valve. You can then increase the bias, noting the plate current and the quality until the most effective results are obtained.

The life of a dry battery falls rapidly if the current is increased, and it is therefore advisable to adjust the set to take the smallest current consistent with results. If the power valve is over or under biased the maximum results will not be obtained.

It is better to use a little too much bias than too little, for then the anode current will be below normal and the high-tension battery will have a longer life. Very often the quality and volume are not appreciably affected by using a little more than the theoretically best bias and as this leads to economy in working the rule should be to use as much bias as possible.


This advice has often been given, I know, but I have met numerous cases where excessive expenditure on H.T. batteries has been due to the use of too little bias.

GETTING "FREE" BIAS

IS it worth while fitting a "free" bias circuit to a battery set?

This question is often asked. It is well known that resistances and condensers are used in mains sets to provide the bias for the grids of the valves, and this is why, I suppose, people ask whether it is worth applying these circuits to sets run from batteries.

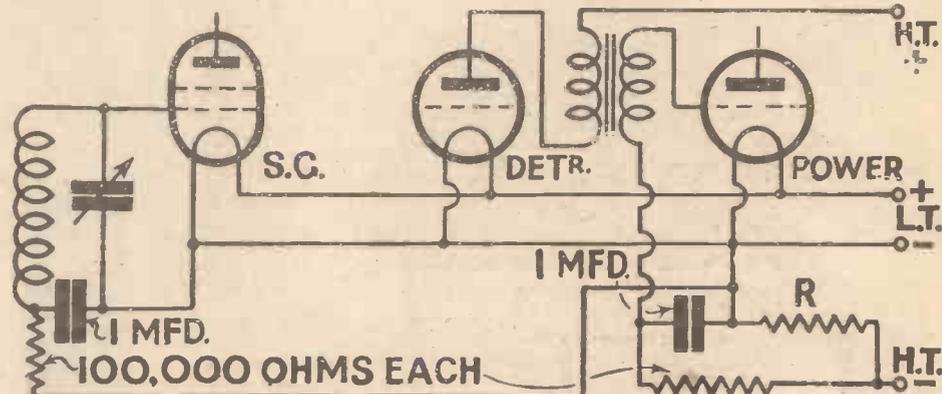The object is first to save the cost of the grid battery that is normally used. There is also a second object, which is to avoid the trouble of looking after the grid battery, and finally it is thought that the "free" bias automatically adjusts itself to the valve and high tension.



This is a typical three-valve circuit in which automatic bias is applied by means of voltage-dropping resistances

Now, while grid batteries can be obtained for a shilling or two and are reliable components, there is not much to be gained by going over to the "free" bias scheme. This may be quite costly if there are two or three bias circuits, as resistances, decoupling resistances and condensers are needed. Further, the bias is not "free."

If the voltage across the high-tension supply is normally 120 and the maximum bias required is 10, the effective high-tension is 110 volts. The loss in high tension combined with the cost probably make the scheme *not* attractive, but those who like to try these things will find the circuit shown above useful.

This shows bias for the screen-grid valve and the power valve. There are two decoupling resistances of 100,000 ohms each and two condensers of 1 microfarad each. Resistance R is joined between the negative side of the low tension and the negative high tension. Its value may be found by dividing the total bias required by the total current.

For instance, if the power valve needs 10 volts bias and the total current is 15 milliamperes, the resistance is 666 ohms, or, say, 650 ohms. If the screen-grid valve is to have a bias of 1 volt the tap must be made at one-tenth of the resistance from

the low-tension end and two resistances could be connected if desired.

IN A SUPER-HET

THERE is nearly always a component in the anode circuit of a detector for passing high-frequency currents from the anode to the filament.

In many sets a by-pass condenser alone is used. But in a super-heterodyne set, something more is often necessary for the best results. A high-frequency choking coil is often used with one or two condensers. This choking coil may be rather different from the type used in ordinary sets, for the reason that the wavelength of the high-frequency currents is higher.

Many chokes are satisfactory only over the normal broadcast band, but in a *super* the wavelength to which the circuits of the intermediate frequency amplifiers are tuned is above this band. The result is that a special choke is often necessary.

Given a good choke and a by-pass condenser in the anode circuit of the second detector, several advantages are obtained. First, the operation of the detector is

improved. Secondly, whistles are avoided, and thirdly, high-frequency currents are kept out of the power valve. It therefore pays to use the right parts here and they cost no more than unsuitable components.

IS IT MICROPHONIC?

IT is sometimes rather difficult to stop microphonic noises in a self-contained set, particularly when the parts are very close together.

You might try changing valves and so on, only to discover that the trouble remains. In some cases the only cure is to mount the part of the set carrying the valves upon rubber. The difficulty is that often the loud-speaker sets the whole cabinet vibrating, and these vibrations are transmitted to the valves, tuning condenser, and other parts.

If, therefore, the chassis is mounted upon rubber the vibrations will not pass from the cabinet to the chassis. It has been found in many bad cases that mounting upon rubber improves the results.

The sides of the cabinet may sometimes be stiffened with good results and a piece of wood jambed between the sides is usually effective.

20 M.A. ONE VARIABLE
AT 0-120v. and 3 fixed
120v. 75v. 90v. and 120v.

45/-

FOR A.C. MAINS
 200 - 250 volts

All Models Incorporate:
 WIRE WOUND RESISTANCES,
 DOUBLE CHOKES & WESTING-
 HOUSE METAL RECTIFIERS

MODEL
 A.C.1

E
L
I
M
I
N
A
T
O
R



ALL BAKELITE CASE

OTHER MODELS
 WITH BATTERY
 CHARGER

A.C.2. Same as A.C.1, but with Trickle Charger ... **60/-**

A.C.3. 150 v. 30 m.A., 4 v. Raw A.C. ... **60/-**

A.C.4. Same as A.C.3, but with Trickle Charger ... **75/-**

A.C.5. 200 v. 40 m.A., 4 v. Raw A.C. ... **65/-**


D.C. 25 M.A. OUTPUT
3 TAPPINGS, 75v. 90v. and 120v. 22 1/6

D.C.2. 140 v. 35 m.A. One Variable, Three Fixed ... **35/-**

THE NIGHTINGALE PARALLEL FEED TRANSFORMER UNIT

The results obtainable from this Transformer Unit will astound you when compared with any other of double the price. It has a greater primary inductance (150 henries) than any other nickel alloy core transformer in general use, and reproduces with perfect realism all frequencies from those of the bass drum to the highest overtones of the violin. Incorporating 35,000-ohm wire-wound resistance and non-inductive coupling condenser, which are mounted in the base of the unit.

10/-

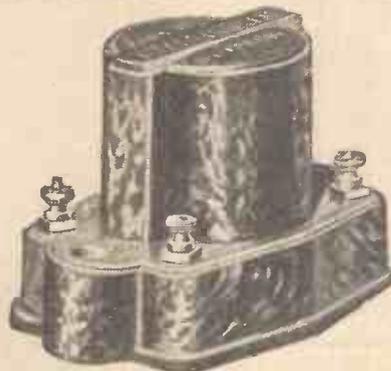

BULLPHONE RADIO

NEW NORTH ROAD, BARKINGSIDE, ESSEX. Telephone: CHIGWELL 162

Advertisers Appreciate Mention of "A.W." with Your Order



SETS OF THE SEASON

The METEOR THREE KIT

THIS is a kit set that will delight the heart of the true experimental constructor. It is a set bristling with good points. It gives a wide range of ordinary broadcast programmes with relatively simple operation, while offering plenty of scope for more spectacular efforts by the seasoned amateur.

This Meteor is a screen-grid, detector, power combination with the great attraction of all-wave tuning. Medium and long waves are covered by two well-designed dual-range coils, which are interchangeable with two special short-wave coils for below 100 metres.

My tests, which I must confess have interested me for several evenings, confirm an early impression that this is a "hot" three, capable of really astounding feats of station-getting and separation. Midnight oil has yielded a fine crop of American

THE METEOR-THREE IN BRIEF

Makers.—Ready Radio Ltd.

Price.—£8 17s. 6d. This includes the kit of parts, the valves, the walnut cabinet, and the fitted moving-coil loud-speaker. A less expensive kit is model B, available price £5 7s. 6d., without the speaker.

Circuit.—All-wave three-valver, the medium and long waves covered with dual-range coils and the short waves with interchangeable coils. Screen-grid coupled to detector by a variable differential system.

Power Supply.—Batteries, for which there is ample room inside the cabinet.

Type.—Kit set with metal-chassis assembly, providing simplified wiring and high efficiency.

Remarks.—An outstanding kit set, especially recommended to amateurs who delight in getting the last ounce out of three valves. Good quality from the moving coil.

stations on the short waves, in addition to hosts of Continental amateurs and such short-wave relays as Zeesen, Rome, Paris, and Moscow.

My test model of the Meteor was a ready-assembled set in an attractive console cabinet, with permanent-magnet moving-coil loud-speaker. The aim has been to give battery users really good quality

at a reasonable price. I am confident the makers have succeeded in their aim.

The circuit makes more of three valves than the average amateur would think possible. A fine system of variable selectivity has been adopted, with a panel-mounted knob giving a ready control over this very important aspect of modern reception. As the designers rightly remark, a fixed degree of selectivity is not always the best practice with a three-valver, since conditions vary so much, not only with locality, but with the time of reception.

With the variable selectivity device on this set you can be sure of getting as much out of the high-frequency amplification as the conditions at any given time will permit, and you will have the great satisfaction of knowing that, though the volume may be cut down for the separation of two particularly difficult adjacent stations, it can be brought right up to scratch for many other stations.

Selectivity with Range

Anybody can make a three-valver selective, but it takes a good designer to effect the best possible compromise between selectivity and range. That is what the designers have done with this set. Even if it were a normal broadcast set I should say it is outstanding. When you remember that good short-wave reception is also provided you have to admit that the Meteor is a great achievement.

Aerial coupling is quite normal, the aerial being taken through a .0004-microfarad pre-set type of condenser to the grid end of the aerial coil. It is in the high-frequency coupling that the real development has been done. Here we find a differential type of condenser of .0001 microfarad acting as the variable coupling for energy transfer from the anode of the screen-grid to the grid of the detector.

Reaction is applied to the grid-tuning winding in the detector circuit by means of the usual coil and condenser across the anode circuit. Transformer coupling follows the detector, with a 20,000 ohms resistance in series with the primary instead of a high-frequency choke.


Such is the basic circuit. It has been interpreted in the most modern way by the use of a metal chassis, the assembly of which is made clear by a wealth of photographs in the instruction booklet. The fixing of the two tuning condensers, selectivity condenser, reaction condenser and two switches, one for battery on-off and the other for the dual-range coils used for broadcast reception, is very simple to understand, and so is the assembly of the two tuning coil bases, valve holders

and other small parts on the metal chassis.

The wiring, as with all these modern metal-chassis sets, is simplified by earthing to the metal chassis all parts common to earth.

This set is worth a good batch of valves, such as the Mullard combination chosen by the makers. The screen-grid is one of the latest high-efficiency metallised types, PM12A, the detector is a PM2DX, and for the power valve you have a choice of a PM2 small power valve or a PM22 pentode.

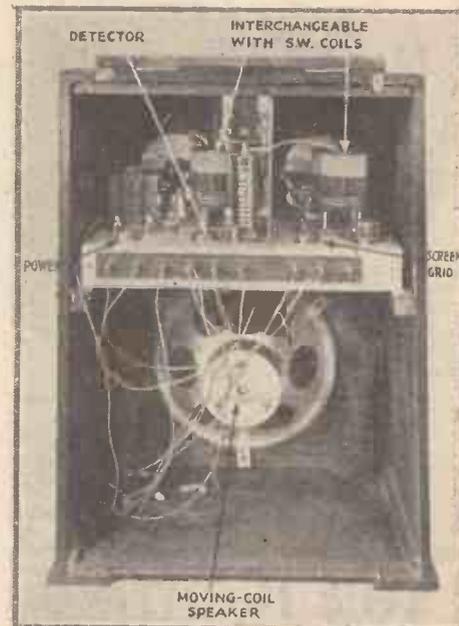When you operate this Meteor set you appreciate the designers' point about not using a gang condenser for tuning. Weak stations that are entirely missed with badly-ganged constructor sets come in at



The Meteor Three is metal-chassis built and most of the wiring is underneath the base

full blast on the Meteor, simply because they are accurately tuned in.

I soon became accustomed to the controls, I almost, but not quite, got Mühlacker clear of London Regional. Certainly Scottish Regional was clear, and so was Langenberg of North Regional.

One of the remarkable features of the Meteor is the way foreign stations come in at full strength during daylight. I got Prague, Langenberg, Rome, both Brussels, and Fécamp at great strength during an afternoon test.

On the short waves, with the special coils, you soon appreciate the smoothness of the reaction—essential for short-wave success. The screen-grid valve certainly pulls its weight all round the dial.

SET TESTER.

Read what J. H. REYNER says about FILT!



J. H. Reyner, B.Sc., A.C.G.I., D.I.C.;
A.M.I.E.E., M.Inst.R.E., Consulting
Radio Engineer. The well-known
designer of many famous sets described in
the foremost wireless publications.

THE FURZEHILL LABORATORIES,
BOREHAM WOOD,
HERTS.

TELEPHONE: ELSTREE 130.
RAILWAY STATION, ELSTREE (L.M.S.)

J. H. REYNER,
B.Sc., A.C.G.I., D.I.C., A.M.I.E.E., M.Inst.R.E.
CONSULTING RADIO ENGINEER.

24th September 1932.

JHR/LW.

Messrs. Graham Farish Ltd.
Masons Hill,
Bromley,
Kent.

Dear Sirs,

I have been much interested in the Filt Percolative Earth which you have submitted for test. The importance of a good earth connection is often overlooked, although attention to this point is repaid by improved signal strength and less liability to interference from external sources, particularly with Mains receivers.

A low electrical resistance is the first essential, and you appear to have gone to the root of the matter by providing an earth bowl filled with chemicals which firstly attract the moisture from the surrounding soil and then saturate it with salts of high electrical conductivity.

My tests indicate that the device is both simple and effective and that the earth resistance is definitely lower than is obtained by the usual methods.

I imagine that in the majority of cases the installation of the Filt Earth will give a definite improvement in results.

Yours faithfully,
J. H. Reyner

Why YOU should fit a FILT

Efficient earthing is vital to good reception. Without it you cannot obtain the power, purity or volume of which your set is capable.

Filt is the most efficient scientific earthing system ever invented. As soon as the copper receptacle is buried, the wonderful chemical it contains begins to spread through the soil, making a permanent highly conductive area to a depth of several feet, ensuring perfect earthing in any climate.

Get a FILT to-day. It may put right faults that you thought could only be remedied by expensive new valves or parts.



GRAHAM FARISH FILT PERCOLATIVE EARTH

Obtainable from your radio dealer or post free from the sole manufacturers,

Graham Farish Ltd.
203 Masons Hill, Bromley, Kent




Mention of "Amateur Wireless" to Advertisers will Ensure Prompt Attention

WIE TEST FOR YOU

A weekly review of new components and tests of apparatus conducted by J. H. Reyner, B.Sc., A.M.I.E.E.

NEW PEAK CONDENSER

WE have received for test and review this week a 4-microfarad 800 volt D.C. working Peak condenser, manufactured by Messrs. Wilburn & Co. This condenser forms an addition to the range of Peak condensers placed on the market some months ago, and of which, as readers will recall, we recently tested two samples. The external construction of this condenser is similar to its predecessors in that it is housed in a grey finished metal can provided with extensions at the base to

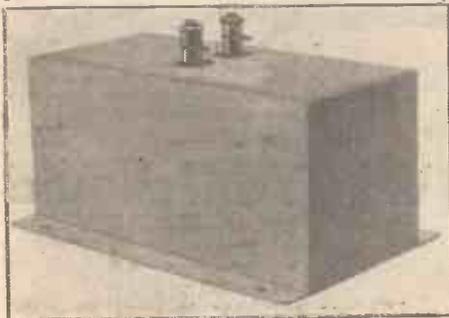

One of the new Peak condensers. A test on a 4-mfd. 800-volt test job is described.

facilitate baseboard mounting. For the external connections to the condenser, terminals and soldering tags are provided, these being located at the top of the condenser.

On test the measured capacity of the condenser was 3.96 microfarads, which figure is in very good agreement with the rated value. The insulation resistance was also excellent, this being too high to obtain any accurate measurement, both before and after a full voltage run.


This condenser appears to be quite satisfactory in use and it can be recommended.

FORMO MULTI-COUPLER

WE have tested this week one of the new Formo Multi-couplers. Essentially this consists of a parallel-feed low-frequency transformer, along with the necessary coupling condenser and resistances. A very small transformer is employed, the core being of a special high-permeability iron. The primary inductance of the transformer with no direct current in circuit—that is, under working conditions—is over 100 henries. The overall resistance of the anode resistance is 50,000 ohms and it is tapped at 30,000 ohms from the anode end, thus allowing the best results to be obtained with valves of various impedances. The connections from the components in

the coupler are all brought out to separate terminals, thus enabling various methods of connection to be employed. For example, the transformer may be parallel fed in the usual way, or it may be auto-coupled, so obtaining a variation of the effective step-up ratio. The coupler is housed in a metal can and mounted on a small moulded bakelite base, the eight terminals being arranged thereon.

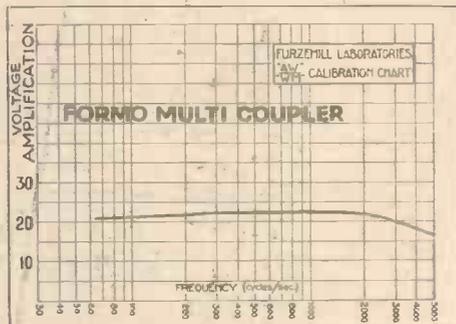The coupler was tested using the normal parallel-feed system, and an HL type of valve, such as would normally be employed in the detector stage, was used. The effective amplification of the transformer can be seen plotted against the frequency on the accompanying chart. It will be seen from the curve that a very good overall



This curve shows the effective amplification of the Formo Multi-coupler plotted against frequency

response is obtained from 64 cycles up to about 3,000 cycles. The component is very well made and can be recommended.


ELECTONE PROGRAMME SELECTOR

AN interesting device which we have received for review is the Electone Programme Selector. This is a device for automatically switching on the receiver at a predetermined time. It consists of a spring-driven clock mechanism having fixed to the hour spindle a wiper which moves over the studs arranged behind the clock-face. Around the periphery of the face are also 24 small holes corresponding to the studs behind.

The device is connected in series with the filament or mains supply of the receiver. In order to switch on the receiver with the device in circuit it is necessary to insert one of the small spring pins provided in the appropriate hole. When the wiper attached to the hour hand makes contact with the stud, a circuit is completed through the metal pin and the

framework of the clock. The contact will remain made for one half-hour after which the wiper will leave the stud and the receiver will be switched off unless further pins have been inserted in adjacent holes. Six of these pins are provided, thus giving a three-hour programme stretch.

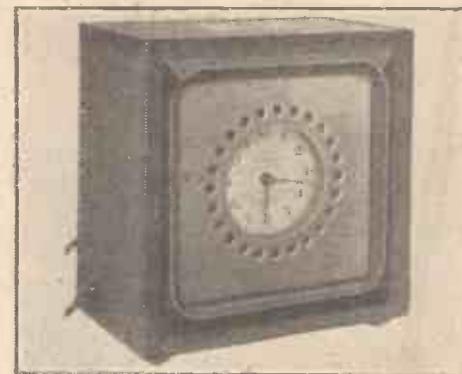We tested the action of the switch both in the filament circuit of battery-driven sets and in the mains lead to all electric sets. The contact was effective and the make and break quite satisfactory. A special fibre cover is placed over the face of the clock for mains working to minimise



An automatic switch—the Electone

risk of shock, but even so it is recommended that any alterations in the setting should not be made with the set switched on.

The Children's Hour is taking its part in the Worcester County Week by giving a "Worcestershire Corner" on October 22.

As the series of plays, "Summer Laughter," ended for this year with the passing of summer time, a new series, under the general title of "Burlesque," will take their place in West Regional programmes for the autumn and winter months, beginning on October 21.

A new series of anonymous talks will be given for West Regional listeners under the title of "My Job and Why I Like It." The first of these, on October 22, will be given by a village craftsman.

A school concert given by the boys of Dean Close School, Cheltenham, will be heard on October 24. The school choir will be assisted by an orchestra composed mainly of students.

The fourth instalment of "Vignettes of Variety" is entitled *Playbills*, and will be heard on October 25 from the Birmingham studios.


Harold Samuel, the famous Bach player, is the artist at the symphony concert to be given by the City of Birmingham Orchestra on October 27.

TELSEN H.F. CHOKES



TELSEN STANDARD H.F. CHOKE

Covering the entire broadcast band, and occupying only the minimum of baseboard space, the Telsen Standard H.F. Choke has proved deservedly popular ever since its introduction. With an inductance of 150,000 microhenries, a resistance of 400 ohms, and an extremely low self capacity, it is highly suitable for use in reaction circuits, and is constantly being specified in this respect by the leading set designers.

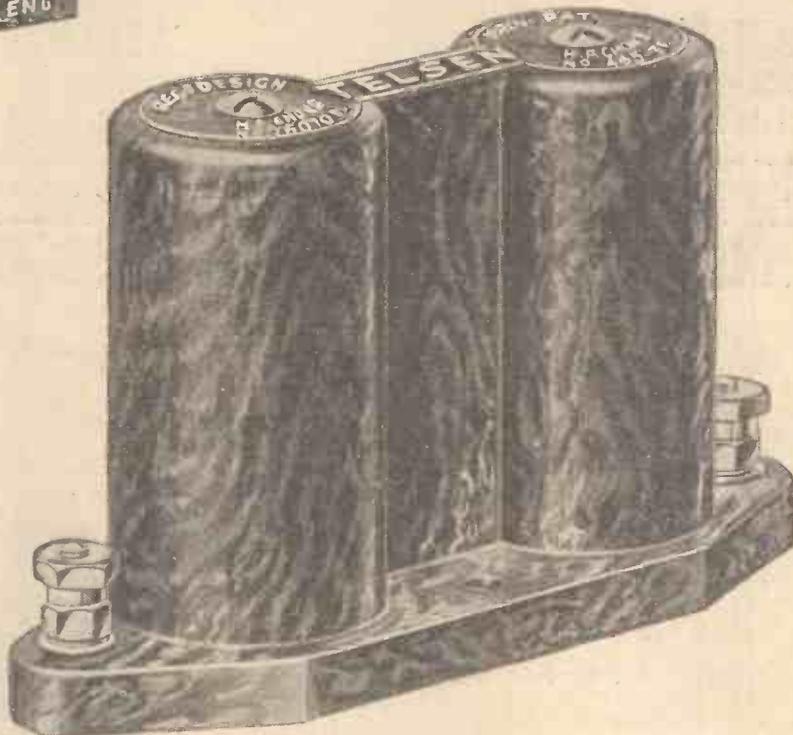

TELSEN BINOCULAR H.F. CHOKE

In H.F. amplification, the performance of a choke is of supreme importance. Where the very highest efficiency is the primary requisite, the Telsen Binocular H.F. Choke is the inevitable choice. It has a high inductance of 250,000 microhenries, with a very low self-capacity and a practically negligible external field (due to its binocular formation). It is from every point of view the ideal choke—and where high-class circuits are concerned, definitely the essential choke.



TELSEN

RADIO COMPONENTS

BUY A COPY OF THE TELSEN RADIOMAG - PRICE 6d.

ANNOUNCEMENT OF THE TELSEN ELECTRIC CO., LTD., ASTON, BIRMINGHAM

Don't Forget to Say That You Saw it in "A.W."

CHEAPER BLUE SPOT SPEAKERS

ALL set users will be interested to know that some big price reductions have been made in connection with Blue Spot speakers, and the value now offered is notable.

Three popular Blue Spot speakers are shown in the accompanying group, these including the well-known 100U inductor type speaker, which now costs 32s. 6d. in chassis form, the popular 31K cabinet speaker, which is of solid oak and which uses the 66K unit; also the 66KC, which

is a standard Blue Spot chassis fitted with the 66K unit.

The 31K speaker complete costs only 31s. 6d., while the 66KC chassis job costs only 19s. 9d. The 66K unit alone costs only 15s., without chassis, which is excellent value. The 66R unit is of larger construction and is a high-quality unit for fitting to any solidly constructed chassis, such as the Blue Spot Major. The 66R unit cost 35s.

Full details of these speakers and units,



Three of the popular Blue Spot speakers, including the 66KC speaker and the 31K cabinet speaker, both of which are fitted with the 66K unit, and the 100U chassis job

of the Blue Spot permanent-magnet speakers and the Blue Spot pick-up, can be obtained free on mention of "A.W." from the British Blue Spot Co., Ltd., Blue Spot House, 94-96 Rosoman Street, Rosebery Avenue, E.C.1.

A HALF-HOUR thrill will be broadcast Regionally on November 4, and Nationally on November 3. Entitled "The Other Room," it is taken from a short story by Don Marquis. The production is by Howard Rose, who has also adapted the play for the microphone.

Ballet music associated with the dancing of Anna Pavlova will be broadcast in the Regional programme on October 29. This will be the second concert of a similar nature conducted by Walford Hyden, who was first Pavlova's rehearsal-accompanist.

Readers in the Burton-on-Trent district should note that an Amateur Radio Society has been formed and new members are welcomed. Information can be obtained from the hon. sec., Mr. W. A. Mead, Addiscombe, Branstone Road, Burton-on-Trent.

Radio telephone transmitting apparatus is being fitted up in the Traffic Department of Edinburgh Police Headquarters by way of experiment. Tests (the first of their kind in Scotland) are shortly to be carried out by sending messages to be picked up by a specially equipped patrol car as it traverses the city, and the possibilities of the innovation as a means of running criminals to earth are being closely watched by other police authorities in Scotland.

YOU NEED A MOVING-COIL SPEAKER

You will never get the realism and quality that is there to get until you get a modern moving-coil speaker. You need the "Mansfield" permanent-magnet moving-coil speaker—W.B.'s latest and famous P.M.4. It gives true and brilliant reproduction from any 2 or 3 valve set. Price 42/- complete. Write now for the free art booklet "Speaking of Speakers."

PIONEERS & LEADERS

ALWAYS



TELSEN L.F. TRANSFORMERS COUPLING UNITS and OUTPUT CHOKES

TELSEN "RADIOGRAND" L.F. TRANSFORMERS

Typical of all that is finest in British Radio craftsmanship. Designed in accordance with recent research, constructed on the soundest engineering principles and tested rigorously for immaculate performance and enduring efficiency.

Ratio 3-1 **7/6**
Ratio 5-1

TELSEN "RADIOGRAND" (Ratio 1.75-1) TRANSFORMER

For use in high-class receivers employing two stages of L.F. amplification. When used following an L.F. stage employing choke or resistance coupling, it gives ample volume with remarkable re- **10/6** production.

TELSEN "RADIOGRAND" (Ratio 7-1) TRANSFORMER

Gives extra high amplification on receivers employing only one stage of L.F. amplification. Not recommended for use with two L.F. stages, as overloading is likely to **10/6** occur.

TELSEN POWER PENTODE OUTPUT CHOKE

For mains operated pentodes taking an anode current of up to 40 m.a. Serves both to prevent direct current passing through the speaker and to match the speaker to the pentode valve, with the choice of three ratios—1-1, 1.3-1, 1.7-1. Used with a 1-mfd. condenser it gives a great increase **10/6** in both quality and volume.

TELSEN TAPPED PENTODE OUTPUT CHOKE

For mains and battery operated pentodes taking an anode current of up to 20 m.a. The single tapping provides (by reversing) ratios of 1-1, 1.6-1, 2.5-1, ensuring perfect matching under widely varying conditions. Also suitable for matching a low-impedance speaker with an ordinary power valve, a 1-mfd. coupling condenser being recommended for this purpose. **7/6**

TELSEN INTERVALVE L.F. COUPLING CHOKES

Primarily designed for use as coupling chokes but may be used in any circuit carrying not more than the stipulated maximum current. The 100H type is for H. or H.L. type valves and the 40H for L. types.

Rating.	Normal Current.	Max. Current.
40 H.	5 m.a.	10 m.a.
100 H.	3 m.a.	8 m.a.

5/-

TELSEN OUTPUT CHOKE



Designed for use with power or super-power valves taking an anode current of up to 40 m.a., this output filter provides an ideal response curve under all conditions. For use with a condenser of not less than **7/-** 1 mfd. capacity.

THE TELSEN "ACE"

The Telsen "Ace" is eminently suitable for Receivers where highest efficiency is required at low cost and where space is limited. As its characteristic curve will show, it gives a performance equal to that of the most costly transformers.


Ratio 3-1
Ratio 5-1

5/6

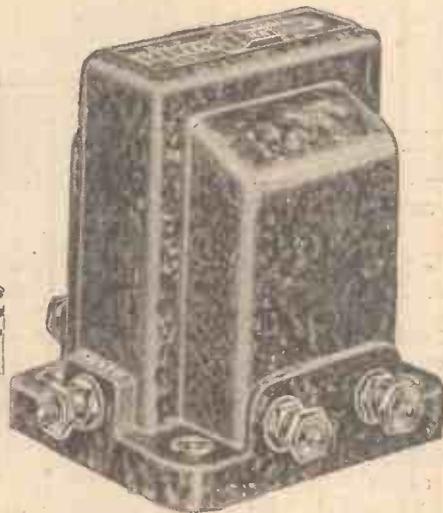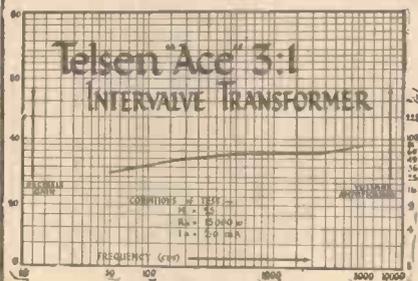

TELSEN 10-1 INTERVALVE COUPLING UNIT

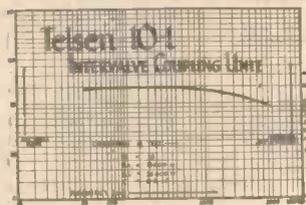
A filter-fed transformer using a high permeability nickel alloy core, securing a 10-1 voltage step-up while preserving an exceptionally good frequency characteristic. The response is compensated in the higher frequencies for use with a pentode valve giving an amplification greater than anything previously achieved, equal to two ordinary L.F. stages but with better quality of reproduction.



12/6

TELSEN 1-1 INTERVALVE COUPLING UNIT

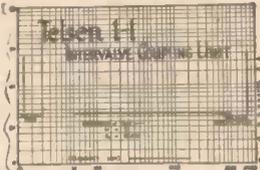A modern development of the deservedly popular R.C. unit incorporating a low pass filter feed in its anode circuit, thus preventing "motor-boating," "threshold howl" and other instability due to common couplings in eliminator and battery circuits. Used with an H.L. type valve it gives an amplification of about 20 and a perfect frequency response on a negligible consumption of H.T. current. **7/6**



TELSEN MULTI-RATIO OUTPUT TRANSFORMER

For use with moving-coil speakers, having a low-impedance speech coil winding, and suitable for anode currents of up to 40 m.a. Three ratios—9-1, 15-1, 22.5-1—allow for correct matching of speakers of **10/6** widely varying characteristics.

TELSEN OUTPUT TRANSFORMER (Ratio 1-1)

For connecting the speaker to the output stage, using a triode valve. Avoids saturation by isolating the D.C. from the speaker windings. Also keeps H.T. voltage from the speaker and its lead, which is especially important where a D.C. eliminator is being used. Suitable for anode currents of up **10/6** to 40 m.a.

TELSEN

RADIO COMPONENTS.

BUY A COPY OF THE TELSEN RADIOMAG - PRICE 6d.

ANNOUNCEMENT OF THE TELSEN ELECTRIC CO., LTD., ASTON, BIRMINGHAM.

Mention of "Amateur Wireless" to Advertisers will Ensure Prompt Attention

"USING THE SCREEN-GRID AS A DETECTOR"

(Continued from page 847)

and the input is tolerably a straight line, giving distortionless rectification. The operating conditions here are that with no signal the anode current shall be quite small (0.1 milliamp. in the present tests), and this condition is obtained by

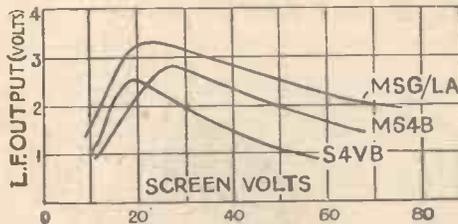


Fig. 5. The optimum screen voltage is more critical with the anode-bend-circuit and is also distinctly lower

suitable adjustment of the self-biasing resistance. If this is done the actual value of anode resistance is not at all critical, the usual value being about 250,000 ohms. Once again there is an optimum anode voltage and this is quite different from that for the grid rectifier. It is in fact only about half as great and is rather more sharply defined. However, much the same state of affairs occurs as with the grid rectifier, viz.: that with the optimum screen voltage the detector overloads too easily, and it is necessary to sacrifice some of the efficiency in order to obtain satisfactory handling capacity.

The curves, Fig. 5, show the L.F. output in terms of screen voltage with a constant H.F. input to a screen-grid valve used as an anode rectifier. Comparison of these figures with those of Fig. 2 will show that the sensitivity is only about one half that of the same valve used as a grid rectifier.

An industrial relay from the depot in Derby of a firm of well-known motor manufacturers is to be given next week. Engines made by this firm were used very largely during the Great War for heavy aeroplanes and cars. The talk will be given by Mr. A. F. Sidgreaves.

DOES YOURS RATTLE ?

About once a year it will pay you to tighten up all the small screws in the actuating mechanism of a moving-iron type speaker.



The vibration in an ordinary speaker unit is considerable and if there are any slack clamping screws they will in time set up the rattle

GIANT LOUD-SPEAKERS ON TOUR

HUGE loud-speaker equipment nearly 200 times as powerful as the speaker on the average set featured in the tour of the "Daily Mirror Eight" around the coastal resorts of England and Wales.

The travelling loud-speaker gear was designed and supplied by Messrs. Tannoy Products and the speaker van accompanying the tour was fitted up with a



The giant loud-speaker van fitted with the Tannoy equipment

250-watt amplifier. All the power for the operation of this big public-address plant was obtained from a motor-generator on the van. Banks of power valves provided the huge output to the loud-speakers on the roof.

B.B.C. type microphone arrangements were used in conjunction with the special amplifiers designed by Tannoy Products and announcements were made through the loud-speaker equipment in just the same way as an ordinary broadcast. The van is shown by the photograph above.

SIMPSONS ELECTRIC TURNTABLE



PRICE
39/6

Outstanding features :

1. Only 2 1/2 in. deep.
2. Sizes 10 in. and 12 in.
3. Superb finish.
4. 50 cycles, 100/150 and 200/250 volts A.C.
5. Costs less than 1d. per week.
6. Nothing to go wrong.
7. Correct speed of 78 revs. per minute.

The famous Simpson's Electric Turntable can be fitted in any Gramophone at little cost and no trouble. Starts and stops at the touch of the finger. Ask your dealer for particulars and demonstration. If any difficulty write for free illustrated leaflet.

SIMPSONS ELECTRICALS LTD.,
Grange Road, Leyton, London, E.10



This OSBORN RADIO CABINET

Made by Craftsmen for Particular People

Model No. 227. Beautifully designed Radio-gramophone Cabinet, 3 ft. 4 in. high by 2 ft. 2 in. wide by 1 ft. 6 in. deep. Space for speaker, 24 in. by 16 in. Accommodation for set and any type of gramophone motor, 24 in. by 12 1/2 in. high. Baffle behind fret, 24 in. by 16 in. Special Silk Fabric included.

PRICES

- Machined ready to assemble: Oak, £3-0-0; Mahogany, £3-5-0; Walnut, £3-15-0. Assembled ready to polish: Oak, £4-0-0; Mahogany, £4-5-0; Walnut, £4-15-0. Assembled and polished: Oak, £5-0-0; Mahogany, £5-15-0; Walnut, £6-10-0. All models carriage paid.

STANDS 117 and 118 BLOCK "S"

Scottish National Radio Exhibition, Edinburgh, Waverley Market, October 12-22.

Write for Beautifully Illustrated FREE Catalogue of Latest Models, post free.
CHAS. A. OSBORN, Dept. A.W., The Regent Works, Arlington Street, London, N.1. Telephone Clerkenwell 5095.
And at 21 Essex Road, Islington, N.1. Telephone: Clerkenwell 8634.

British Made



YOU WANT PERFECTION ? FOR SHORT WAVES

Then use the original BECOL EBONITE LOW-LOSS FORMER, tested before despatch and reliable. Prices Low. Look for Trade Mark. Efficiency Tells.

INTERESTING.—Send 6d. (post free) for UP-TO-DATE HANDBOOK of Tuning Coils for Circuits, Dual Range, Band Pass and Super-het, fully illustrated with data.

THE BRITISH EBONITE CO. LTD. HANWELL LONDON, W.7


IS YOUR LOUD-SPEAKER WORTHY OF YOUR SET ?

Read all about Modern Loud-speakers in the **BIG SUPPLEMENT** in the **WIRELESS MAGAZINE NOVEMBER ISSUE**

On Sale Friday, Oct. 21, of all Book-stalls and Newsagents

148 PAGES, USUAL PRICE 1/-

Comparisons

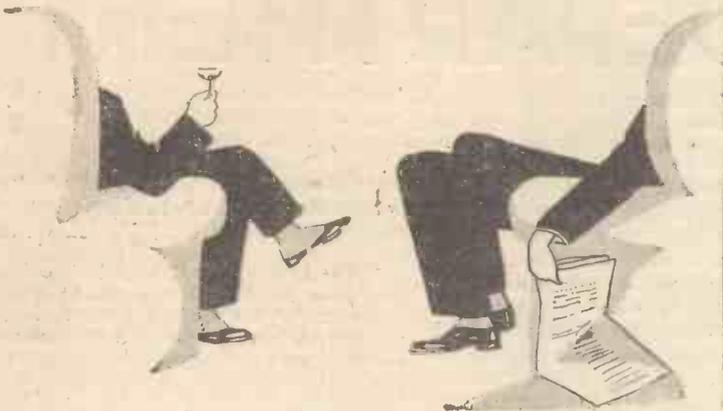

The R. & A. 'Challenger' is a Permanent-magnet Moving-coil Reproducer, of which the *Wireless World* states:—

"Performance . . . is such that it merits discussion from an absolute standpoint and without regard to the very reasonable price asked . . . overall sensitivity slightly better than average of its class . . . the reproduction in the bass below 100 cycles quite definitely above average . . . full-bodied bass without boom . . . speech natural . . . balance in music exceptionally good."

Complete with 3-ratio Ferranti Transformer.

35/-



Holdens

"Comparisons are odious. We frequently assess faulty values without reference to the perfect, by which, after all, only true comparisons can be made.

"You, for example, until to-night, thought your Loud-speaker was quite good, but my 'CHALLENGER,' although not perfect, certainly represents the 'best yet.'"


"Yes, I must admit your argument, and

although I bow to your judgment when you say the 'Challenger' is not perfect, it certainly seems so to me. I must say I have now heard speech and music reproduced as I have never before thought possible, but such reproduction is beyond my purse."

"Nonsense! An R. & A. 'Challenger' will cost you a modest 35/-."

REPRODUCERS & AMPLIFIERS LTD., WOLVERHAMPTON

30% Price Reduction

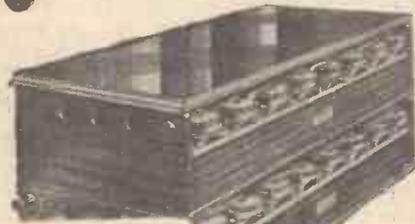

Leclanché PERMANENT H.T. BATTERY

Self Charging

STANDARD


We provide personal attention and show even Bigger savings on your battery expense. Install the Standard which lasts for years, because it recharges itself when the set is shut down. This PERMANENT saving is enjoyed by thousands of enthusiasts. Ample level current brings in difficult stations without background. Eventual replacements merely a matter of changing cartridges at a few pence each. Such great promise deserves your investigation. DO IT NOW.

STANDARD BOOKLET POST FREE Popular Type Battery for Ordinary Sets

Any Voltage Any Capacity Model H5, No. 3 size, 12,500 milli-amp capacity, 120 volts, 84 cells. Price, complete without trays 37/8 Tray containers extra if required. Other capacities, 2,000 to 25,000 milliamps.

5/- Down STANDARD BATTERY CO., Dept. A.W. 184-188 Shaftesbury Avenue, London, W.C.2

FUSE HOLDERS AND FUSES

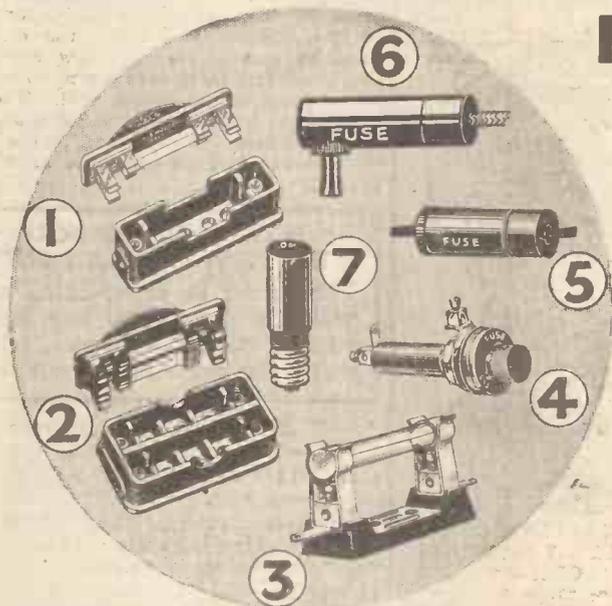

- 1 SINGLE SAFETY BASEBOARD FUSE-HOLDER. Fuse carried on lid, making shocks impossible. Complete with 1 amp. fuse 1/6
- 2 TWIN SAFETY BASEBOARD FUSE-HOLDER. Fuses carried on lid, rendering shocks impossible. Complete with two 1 amp. fuses. 2/6
- 3 SINGLE OPEN FUSE-HOLDER. With 1 amp. fuse 9d.
- 4 PANEL FUSE-HOLDER. For panel mounting. With 1 amp. fuse . . . 1/6
- 5 FLEX FUSE-HOLDER. With 1 amp. fuse . . . 1/-
- 6 WANDERFUSE. With 150 m.a. fuse 1/-
- 7 "SCRUFUSE," Not bulb, not cartridge, yet both! . . . 6d.

SPARE FUSES, LONG FUSE. 60, 150, 250, 500, 750 m.a., 1, 2, or 3 amp. SHORT FUSE (for wanderfuse only), 60, 150, and 500 m.a. All ratings and sizes 6d. each. Each rating a different colour (avoiding possibility of error.)

Ratings:—(Black) 60 m.a. (Red) 150 m.a. (Brown) 250 m.a. (Yellow) 500 m.a. (Green) 750 m.a.


BELLING-LEE

Advert. of Belling & Lee, Ltd., Cambridge Arterial Road, Enfield, Middlesex

Dealers will fit other ratings in any of these holders at the time of purchase.

You will Help Yourself and Help Us By Mentioning "A.W." to Advertisers

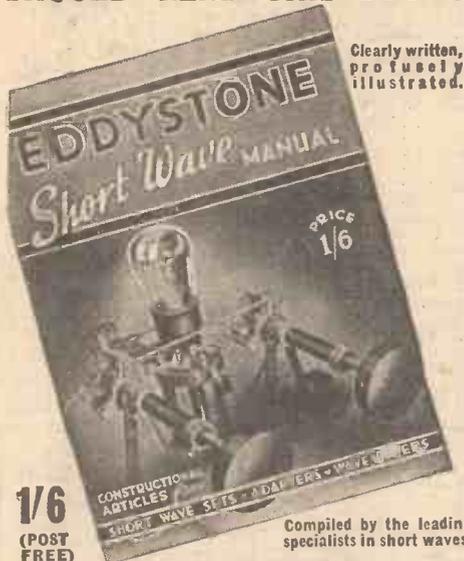• EVERYONE
INTERESTED IN **SHORT WAVES**
SHOULD READ THIS BOOK!



Clearly written,
profusely
illustrated.

1/6
(POST
FREE)

Compiled by the leading
specialists in short waves.


• "The Eddystone Short-wave Manual" includes fully illustrated constructional articles for building 2-, 3-, and 4-valve short-wave receivers, a 1-valve superhet. S.W. converter, a 1-valve S.W. adaptor, a dynatron and heterodyne wavemeter, and a 7-metre ultra S.W. converter. List and cost of parts given in detail for each set. Articles on short waves, short-wave tuning, S.W. condensers, trouble locating, etc. Ask your Radio Dealer for this splendid book.



STRATTON & Co. Ltd.
Bromsgrove St.,
Birmingham
Eddystone Service
Depot 184 Charing
Cross Rd., W.C.2.

EDDYSTONE
— SHORT-WAVE —
MANUAL

CLIX
CHEAPEST PERFECT CONTACT

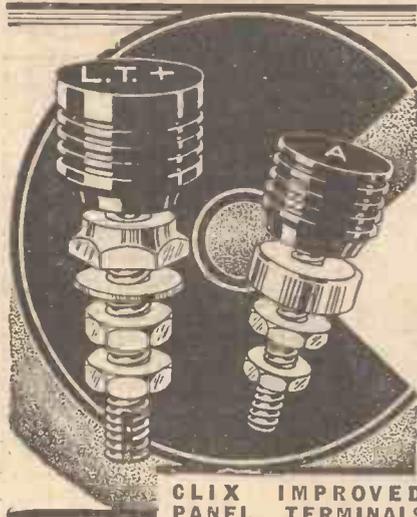

**CLIX IMPROVED
PANEL TERMINALS
FOR CONSTRUCTORS**

From the "T. & R. Bulletin"
(Official organ of the Radio Society
of Great Britain)

"What we particularly like about this is the fact that the body is provided with a hexagon shoulder so that it can be held with a spanner while the nuts behind are made tight."

CLIX terminals are more robust; completely insulated, non-removable heads. Red or black. Full range of easily read markings.

Prices:
Type B, with hexagonal shoulder

4d.

Type A - **2d.**

Order 'A' free.

LECTRO LINX, LTD., 254 Vauxhall Bridge Rd., S.W.1

OUR QUERY DEPARTMENT?

The attention of readers is directed to the rules printed below. Replies are sent by post, only a selection of queries of general interest are printed here.

Patent Royalties

SIR,—I understand all wireless receivers made are subject to royalties, but I have never seen it fully explained. Does one have to pay royalties on any set made up from the designs which appear from time to time in the pages of your journal, whether made for personal use or for the use of friends? Furthermore, if one has an existing receiver and uses the components of this set, with other new parts, to make up a later design of receiver, is it essential that royalty be paid on the new set? I should appreciate as much information as possible on the subject.

S. Y. J. (Bucks.).

Quite a number of the wireless patents that originally existed and for which royalty had to be paid have now lapsed. It is, therefore, possible to build up wireless receivers which do not make use of existing patents. Royalty cannot be demanded for such sets. The question as to which patents are still in existence, however, is one which cannot be dealt with briefly. If you have a set upon which royalty has already been paid and you want to modernise the receiver without increasing the number of valves, then no further royalty is payable provided you do not infringe fresh patents in altering your set. If you build up sets for sale among your friends and you infringe different firms' patents, then you are liable for royalty on the patents you make use of. These royalties, usually, are payable to the Marconi Co., who share them with the numerous firms who belong to the patent pool. The whole question of what royalty is payable on sets made for sale will be made clear by the Marconi Co., to whom you are advised to write for particulars.

**THE SET FOR YOU
THE NEW CENTURY SUPER**
The latest in super-hets., a set which will get you any station you want. Pictorial guide, full-size wiring plan and full details next week.

Electrolytic Condensers

SIR,—In replying to a querist in **AMATEUR WIRELESS**, September 17, 1932, you stated that "wet electrolytic condensers should be mounted in a horizontal position with the vent holes at the top." Do you not mean that the condensers should be placed in a vertical position as otherwise it is not possible to have the vent holes at the top? Furthermore, you say "it is not advisable to use electrolytic condensers on the rectifier side of the smoothing-circuit choke." I am using one in such a position and there are millions of sets in the States so fitted. I can see where the error occurred in regard to the fitting of the electrolytic condenser, but I cannot reconcile your statement concerning where the condenser should not be fitted, when my

own knowledge tells me that electrolytic condensers can be used on the rectifier side of the smoothing circuit. L. W. (M/c)..

The statement that "electrolytic condensers should be fitted in a horizontal position" is incorrect. If the vent-holes are to be at the top, the condensers themselves must necessarily be fitted in a vertical position. As regards the advice that "it is not advisable to place electrolytic condensers on the rectifier side of the smoothing-circuit choke," this advice is particularly sound. The current from the rectifier, before reaching the smoothing choke, still possesses some of its A.C. qualities, i.e., an A.C. ripple of double the frequency of the supply, and this ripple in the current is sufficient to cause a fairly large leakage of current across an electrolytic condenser if arranged on the rectifier side of the choke. After the current has been smoothed by passing through the high-inductive smoothing choke, very little leakage will occur across such a condenser when arranged on the receiver side of the smoothing choke. Quite apart from this, the A.C. ripple on the rectifier side of the choke is likely to damage electrolytic condensers; this applies more to dry electrolytic condensers than to the wet type. We are aware that in many American sets the electrolytic condensers are placed on both sides of the smoothing-circuit choke.

Reference to the leaflets supplied by British manufacturers with electrolytic condensers substantiate our advice.

An hour's vaudeville for West Regional listeners will be given on November 4.

Ghosts will be abroad in the Belfast studio on Hallow-e'en (October 31)! A special play has been selected for this evening called *The Ghost of Gillhall*, a tale of old Ireland by Patrick Riddell.

A third edition of Mungo Dewar's revue with a naval flavour, *Eight Bells*, will form part of the programme from Belfast on November 4.

WHEN SUBMITTING QUERIES

Please write concisely, giving essential particulars. A Fee of One Shilling (postal order), a stamped addressed envelope, and the coupon on the last page must accompany all letters. The following points should be noted.

Not more than two questions should be sent with any one letter.

The designing of apparatus or receivers cannot be undertaken.

Modifications of a straightforward nature can be made to blueprints, but we reserve to ourselves the right to determine the extent of an alteration to come within the scope of a query. Modifications to proprietary receivers and designs published by contemporary journals cannot be undertaken.

Readers' sets and components cannot be tested at this office. Readers desiring specific information upon any problem should not ask for it to be published in a forthcoming issue, as only queries of general interest are published and these only at our discretion. Queries cannot be answered by telephone or personally.

Readers ordering blueprints and requiring technical information in addition, should address a separate letter to the Query Department and conform with the rules.

CONVERT YOUR RADIO TO A RADIO-GRAM
without cabinet or mounting



BY ATTACHING UNIVOLT TO YOUR PRESENT SET

Connected in an instant, Univolt reproduces electrically all records through your Radio with full, clear, beautiful volume . . . giving the performance of an expensive Badk-gramophone at the least possible cost. Absolutely self-contained. Solid walnut-grained bakelite Case. Silent and uniform, running free from Radio interference. No overheating. Minimum Current Consumption. Speed Control (70 to 90 r.p.m.). Invisible On-off Switch. Flex and Adaptor. Univolt Super Pick-up with perfect tracking, swivel Head, Weight-adjustable Arm, and a sensitivity and frequency response hitherto never attained. Square Law Volume Control. Automatic Start and Stop. Univolt is needed in every home where there is Radio.

FULLY GUARANTEED 2 YEARS

Standard Unit For A.C. Mains. **5¹/₂G** As described above, complete with pick-up equipment. **5¹/₂S.**

C.O.D. IMMEDIATE DELIVERY

Universal Model for A.C. and D.C. Mains 15/- Extra.

The Gramophone Needle Problem Solved
The Goldring Automatic Needle Cup delivers ONE Needle between finger and thumb at a touch. Holds 200, with outside container for used needles. Never falls in action, cannot spill or prick fingers. Beautiful plated or bronze finish. Available as table model or to sink into playing-desk. **5/-**

ANDREWS TRADING CO.,
13, ST. ALBANS VILLAS, HIGHGATE ROAD
LONDON, N.W.5. Telephone: Gulliver 5136.



39¹/₆

MOVING COIL PERM-MAG-SPEAKER

" . . . the finest permanent magnet moving coil speaker the industry has yet produced."
AMPLION (1932) LTD. 82/84 ROSOMAN STREET, LONDON, E.C.1. CLERK. 5440-1

PLAYER'S



Smokers make doubly sure by getting **Quality and Quantity** in the Cigarettes



10 for 6^D
20 for 11¹/₂^D

NCC 1038

SEE THAT YOUR A.C. MAINS SET INCORPORATES

A

WESTINGHOUSE

METAL RECTIFIER

WHY? Because it is the only rectifier to combine long life with high efficiency, so as to ensure a steady and lasting high-tension supply.

THE WESTINGHOUSE BRAKE & SAXBY SIGNAL CO., LTD., York Road, King's Cross, LONDON, N.1.

Mention of "Amateur Wireless" to Advertisers will Ensure Prompt Attention

P.P.M. 19



47/6
INCLUDING TRANSFORMER

There has been every year a steady improvement in the transmission and reception of Broadcast programmes—greater range, finer selectivity has placed more and better programmes within the reach of listeners. It has, however, been left to Celestion to supply the all-important link in the chain of Broadcasting—the loud-speaker—for the loud-speaker must take the responsibility of reproducing music and speech with life-like fidelity.

Celestion's latest achievement, the P.P.M. 19, exercises this duty with remarkable success, the tonal quality and sensitivity being amazing. Hear this wonderful speaker at your local dealer's.

Price **47/6** Including transformer.

CELESTION

The Very Soul of Music

Celestion Ltd., London Road, KINGSTON-ON-THAMES
London Showrooms: 106 Victoria Street, S.W.1

POSTCARD RADIO LITERATURE

GET THESE CATALOGUES FREE

Here "Observer" reviews the latest booklets and folders issued by well-known manufacturers. If you want copies of any or all of them FREE OF CHARGE, just send a postcard giving the index numbers of the catalogues required (shown at the end of each paragraph) to "Postcard Radio Literature," "AMATEUR WIRELESS," 58/61, Fetter Lane, E.C.4. "Observer" will see that you get all the literature you desire. Please write your name and address in block letters.

A Radiogram Conversion

THE Univolt electric unit—a combined gramophone motor, pick-up, volume control, and selfstop—is described in a new folder just sent me. A Junior model of the unit is available without the pick-up equipment and in either case it is possible, for a small extra charge, to have a universal motor fitted for A.C. and D.C. operation. The Univolt unit is a complete radiogram adaptor. **861**

The Antinodal Idea

R.I. Ltd. have sent me details of the R.I. Antinodal Short-wave Converter—the A.C. edition. It is claimed that this is the only A.C. short-wave converter that can be connected externally to an A.C.-operated set without removing the valves or altering the wiring. It enables you to bring in the short-wave stations from 18 to 80 metres. Altogether a good idea and fully described in the folder, a copy of which you can have free. **862**

The R. & A.'s

Until I received the new R. & A. folder I did not know that there were so many speakers in the range. The "Challenger," a permanent-magnet, moving-coil handling 3 watts A.C. without distortion, and having a cadmium-plated, 15 per cent. forged cobalt steel magnet, is one of the many R. & A.'s that looks like being a popular favourite. The biggest of the family is the R. & A. Victor, a big permanent-magnet speaker. **863**

Tone Control

The Multitone system of tone control is described in the new Multitone booklet. It gives circuits showing how to use this novel tone control transformer, together with curves which show what happens when the control is affected. If you want to fit a tone control to your set, then get this book. **864**

Give It a Cabinet

A fine cabinet to house the Osram Music Magnet is made by the Vibranti people and described in a newly issued sheet. It is only one of the many Vibranti cabinets and I advise you to write through my free catalogue service for details of the right "box" for your set.—OBSERVER. **865**

USED IN THE B.B.C. STUDIOS

THE HOWE BROADCASTING HOUSE BAFFLE

If you have not heard a loud-speaker fitted with a Howe Box Baffle, you cannot know how good reception can be. This simple and inexpensive addition to your set, which any novice can fit at home without alt. at on to the set itself, is the solution of the resonance problem, the cause of unpleasant "boominess" and distortion.

The Howe Box Baffle Kit, which can be fitted into your existing cabinet, costs 20/-, including royalty, or with a Knockdown Cabinet, 30/-, or the Baffle assembled complete in Cabinet, prices on application.

Send P.C. for full details to:—

F. McNEILL & CO. LTD.
(Radio Dept. H), Lambs Passage, Bunhill Row, E.C.1

ELECTRADIX

"Hang it! I've just got my accumulator charged and now the H.T. Battery has faded out!"

Now, if he had a Brown's 2 volt H.T. Superseder, which gives 80 volts D.C., the wireless would have been on that night. These £3.15s. boons and blessing are now only



37/6
from us.

1,000 other bargains in our OCTOBER SALE LIST.

ELECTRADIX RADIOS,
218, Upper Thames Street, London, E.C.4.

PROTECT YOUR VALVES FROM ACCIDENTAL SHORT-CIRCUITING



3/- EACH
Post Free
Complete
with Fuse
Bulb

BY FITTING THE "BUSCO" FUSE SWITCH

All "BUSCO" Switches have self-cleaning contacts and "Set Cracking" is safeguarded through the Vice-like Grip at Contact Points.

BUSEY & Co. Ltd. Price 5/-, BIRMINGHAM

DESIGNS FOR APPARATUS FOR ANY RADIO PURPOSE, INCLUDING TRANSMISSION, OVERSEAS ENQUIRIES INVITED; ANY APPARATUS SUPPLIED. CONSTRUCTIONAL WORK UNDERTAKEN.

We undertake to solve your Problems, including obtaining Amateur Transmitting Licence. Whatever your difficulty, write us. Charges: 3/- per query, four or more, 2/6 each, with diagrams.

Radio Technical Agency, (Dept. A.W.), 2, Westgate Chambers, Newport, Mon.

BROADCASTING STATIONS

Broadcasting Stations classified in order of wavelengths. For the purpose of better comparison, the power indicated is that of the carrier wave.

Kilo-Metres cycles	Station and Call Sign	Power (Kw.)	Kilo-Metres cycles	Station and Call Sign	Power (Kw.)	Kilo-Metres cycles	Station and Call Sign	Power (Kw.)
19.737 15,200	Zeesen (DJB)	8.0	288.5 1,040	Bournemouth	1.0	409.8 640	Tartu	0.5
25.4 11,810	Rome (2RO)	15.0	288.5 1,049	Plymouth	0.12	472.4 635	Langenberg	60.0
25.53 11,751	Chelmsford (G5SW)	10.0	288.5 1,049	Scottish National	50.0	480 625	North-Regional	50.0
31.25 9,598	Lisbon (CTIAA)	2.0	288.5 1,049	Swansea	0.12	488.6 614	Prague	120.0
31.51 9,520	Skamleback	0.5	291 1,031	Tampere	1.0	495.8 605	Tondheim	1.2
31.38 9,560	Zeesen (DJA)	8.0	291 1,031	Viipuri	13.0	500.8 599	Florence (Firenze)	20.0
32.26 9,300	Rabat	0.5	293 1,022	Kosice	2.5	508.5 590	Astrakhan (RV35)	10.0
40.3 7,464	Radio Nations	20.0	293.7 1,021.5	Limoges (PTT)	1.0	509.3 589	Brussels (No. 1)	15.0
43.75 6,865	Vitus/Paris	0.3	296.1 1,013	Hilversum	20.0	518.1 579	Vienna	15.0
50.0 6,000	Moscow	20.0	298.8 1,004	Tallinn	11.0	also testing on 1,254 m. from 7 p.m. (Mon., Wed., Sat.)		
58 5,172	Prague	0.5	301.5 995	North National	50.0	525.4 571	Riga	15.0
198.5 1,510	Riga (test)	16.0	304.9 984	Bordeaux (PTT)	18.0	527 569.8	Palermo	3.0
203.6 1,473	Seraing	0.2	306.8 978	Zagreb (Agram)	0.75	532.9 563	Munich	1.5
206 1,460	Antwerp	0.4	307.1 976.6	Falun	0.5	541.5 551	Sundsvall	10.0
208.5 1,438.5	Budapest (2)	3.0	308.4 972.6	Vitus-Paris	1.0	550 545	Budapest (1)	18.5
210 1,430	Magyarovar	1.5	309.9 968	Cardiff	1.0	550.7 536	Kaiserslautern	1.5
211.3 1,420	Newcastle	1.0	312.8 955.6	Genoa (Genova)	10.0	557.7 530	Augsburg	0.3
214.3 1,400	Aberdeen	1.0	315 950	Marseilles	1.6	564.4 521.5	Wilmot	18.0
214.3 1,400	Warsaw (2)	1.9	318.9 941	Naples (Napoli)	1.5	569.9 511	Hanover	0.3
215.6 1,319	Brussels (Conf)	0.25	318.8 941	Soňa (Rodoň Radio)	1.0	569.1 527	Grenoble (PTT)	2.0
217.1 1,382	Königsberg	0.9	319.7 936	Dresden	0.25	569.3 527	Freiburg	0.25
218 1,373	Salzburg	0.5	321.9 928	Göteborg	10.0	574.7 523	Ljubljana	5.2
220.1 1,362.0	Béziers	0.5	322.5 923	Breslau	00.0	575 494	Oufa (RV22)	10.0
222.9 1,344.6	Cork (DCK)	1.2	325 923	Poste Parisien	60.0	678.7 447	Lausanne	0.6
225.2 1,331.7	Fécamp	10.0	328.2 914	Poste Parisien	60.0	710.4 413	Moscow (RV2)	20.0
227.4 1,319	Flensburg	1.5	331.4 906	Milan	50.0	748 408	Ostersund	0.6
230.6 1,301	Malmö	1.2	335 896	Poznan	1.9	759.5 395	Geneva	1.25
231.1 1,299	R. Wallonia	0.3	337.8 888	Brussels (No. 2)	15.0	848.7 353.5	Rostov (Don)	20.0
233.4 1,282	Kiel	0.25	342.1 877	Brunn (Brno)	35.0	882 340	Saratov	20.0
235 1,283	Loz	2.2	345.2 869	Strasbourg (PTT)	11.5	937.5 320	Kharkov (RV4)	20.0
235.5 1,271	Kristiansand	0.5	348 860	Barcelona (EAJ1)	8.0	967.7 310	Alma Ata	10.0
237.2 1,265	Bordeaux	0.5	351 855.5	Leningrad (RV20)	20.0	1,000 300	Leningrad	100.0
238 1,260	Nîmes	0.5	352.1 852	Graz	7.0	1,034.5 290	Kiev	100.0
238.9 1,256	Nürnberg	2.0	355.8 843	London Regional	50.0	1,071.2 280	Tiflis (RV7)	100.0
239 1,255	Binche	0.3	360.5 832	Mühlacker	60.0	1,074.4 256	Schevninge-Haven	10.0
240.1 1,249	Stavanger	0.5	363.4 825.5	Algiers (PTT)	10.0	1,085 277	Oslo	60.0
241.3 1,243	Liege (Exp.)	0.2	366.2 819	Seville (EA15)	1.5	1,107 271	Minsk (RV10)	35.0
242 1,238	Belfast	1.0	369.3 819	Fredriksstad	0.7	1,117.4 268.5	Moscow Popoff	40.0
244.1 1,229	Basle	0.5	368.1 815	Bolzano	1.0	1,133.8 260	Kalundborg	7.5
245.0 1,220	Berne	0.5	368.5 814	Helsinki	13.2	1,170 236	Tashkent	25.0
245.0 1,220	Cassel	0.25	369.3 812.1	Radio LL (Paris)	1.0	1,190.5 232	Luxemburg	100.0
245.9 1,220	Linz	0.5	372.2 806	Hamburg	1.5	1,209 250	Istanbul	5.0
247.7 1,211	Trieste	10.0	376.4 797	Scottish Regional	50.0	1,209 250	Reykjavik	21.0
249 1,205	Prague (Strasnice)	5.0	380.7 788	Lvov	10.0	1,229.5 244	Boden	0.6
249.7 1,201.3	Juan-les-Pins	1.0	385 779	Radio Toulouse	60.0	1,252.6 239.5	Vienna Exp.	8.0
250 1,200	Radio Schaarbeek	0.3	385 779	Stalino (RV20)	10.0	1,290 238	Bakou	35.0
252.3 1,180	Barcelona (EAJ15)	6.0	388.5 772	Archangel	10.0	1,304 230	Moscow (Trades Unions)	165.0
253.4 1,184	Gleiwitz	5.0	389.6 770	Frankfurt-a-m.	1.5	1,318 222.5	Notala	30.0
255 1,175	Toulouse (PTT)	1.0	394 761	Bucharest	12.0	1,380 217.4	Novosibirsk (RV6)	100.0
256.7 1,168	Hörby	10.0	398.9 752	Midland Regional	25.0	1,411.8 212.5	Warsaw	120.0
259.3 1,157	Leipzig	2.0	403 743	Sittens	25.0	1,445.7 207.5	Eiffel Tower	13.5
261.6 1,147	London National	50.0	408 734	Katowice	12.0	1,481.5 202.5	Moscow RV1	500.0
263.8 1,137	Moravska-Ostrava	11.0	413.8 725	Athlone (tests)	0.0	1,538 195	Ankara	7.0
265.8 1,238.5	Lille (PTT)	1.3	413.8 725	Dublin	12.0	1,554.4 193	Daventry (Nat.)	30.0
266.7 1,234.4	Bremen	0.3	416.4 720.5	Radio Maroc (Rabat)	2.5	1,600 187.5	Irkutsk (RV14)	10.0
266.8 1,234.5	Valencia	8.0	419 716	Berlin	1.5	1,620 185	Norddeich KVA	10.0
270 1,111	Bar	20.0	423.4 707	Madrid (Espana)	2.0	1,634.9 183.5	Zeesen	60.0
271 1,107	Cointe-Liege	0.3	424.3 707	Madrid (EAJ7)	2.0	1,725 174	Radio Paris	75.0
271.4 1,105	Rennes	1.3	431 695	Belgrade	2.8	1,796 167	Lahti	54.0
273.7 1,096	Turin (Torino)	7.0	431 696	Pareda (tests)	1.5	1,875 160	Huizen	8.5
276.5 1,085	Heilsberg	60.0	435.4 689	Stockholm	55.0	1,910.8 157	Sverdlovsk (RV38)	20.0
279.5 1,073.2	Bratislava	14.0	441.2 680	Rome (Roma)	60.0	1,935 155	Kaunas	7.0
281 1,067	Copenhagen	0.75	447.1 671	Paris (PTT)	7.0	2,625 119	Königswusterhausen (press)	20.0
282.2 1,063	Lisbon (CTIAA)	2.0	453.2 662	Danzig	0.5	2,650 113	Eiffel Tower	15.0
283 1,058	Innsbruck	0.5	453.2 663	Klagenfurt	0.5	2,900 103.5	Königswusterhausen (press)	15.0
283.6 1,058	Berlin (E)	0.5	455 659	Radio Agen	0.5	4,000 75	Königswusterhausen (press)	15.0
283.6 1,058	Magdeburg	0.5	459.4 653	Beromuenster	00.0			
283.6 1,058	Stettin	0.5	456.8 557	San Sebastiaun (EAJ8)	0.0			
286 1,049	Montpellier	0.8	465.8 644	Lyons (PTT)	1.6			
287.1 1,045	Radio Lyons	10.0						

"THE 'NEW CENTURY SUPER'"

(Continued from page 848)

The Most Modern Set of To-day

an adequate range of control and negligible distortion.

Fortunately, there are now available variable-mu screen-grid valves, and it is only necessary to adjust their grid-bias in order to vary the amplification over a wide range. With two stages of intermediate-frequency amplification the maximum magnification is enormous, but by adjusting the control it is possible to cut this down to very little.

Actually, the total current can be kept at a reasonable figure by using the right valves. A pentode output valve, for example, will handle a signal of the desired strength for relatively little high-tension. This type of valve has been proved to have a good life, and may be used with confidence. You must be careful not to break the plate circuit before switching off, but apart from this there are no snags.

A good deal of work has gone into the production of this new super-heterodyne receiver, working from batteries, and tests have shown that it has a remarkable performance. It is naturally much better than the original "A.W." "Century Super," and I feel that it will meet the needs of a large number of readers.

W. JAMES.

Super Thrills with the Super-hat

in producing just what is required to complete the picture, has still further simplified our task.

Of course, we have not beaten Mother Nature completely. We have not been able to introduce a correction device which will change opera to jazz, or talks to music, and we have no thunder-storm eliminator, but I think you will agree that all the things you look for in a good set have been properly attended to.

PERCY W. HARRIS.

New Times Sales Co.

EST. 1924



EVERYTHING CARRIAGE PAID

- PETO-SCOTT 1933 WALNUT ADAPTGRAM.**
Cash or C.O.D., 63/-, or 12 monthly payments of 5/9.
- LISSEN SKYSCRAPER S.G.3 CHASSIS KIT.**
Cash or C.O.D., 89/6, or 12 monthly payments of 8/3.
- LISSEN SKYSCRAPER S.G.3 COMPLETE KIT.**
Cash or C.O.D., 146/5/-, or 12 monthly payments of 11/6.
- COSSOR MELODY MAKER MODEL 334.**
Cash or C.O.D., 48/7/6, First payment, 10/-; balance 11 monthly payments of 11/10.
- COSSOR MELODY MAKER MODEL 335.**
Cash or C.O.D., 49/17/6, First payment, 10/-; balance 11 monthly payments of 14/10.
- SLEKTUN SCOUT S.G.3 CHASSIS KIT.**
Cash or C.O.D., 43/19/6, or 12 monthly payments of 7/1.
- STATION MASTER 3 CHASSIS KIT.**
Cash or C.O.D., 45/11/-, or 12 monthly payments of 10/2.
- RENDALL-PRICE S.G.4 CHASSIS KIT.**
Cash or C.O.D., 44/6/6, or 12 monthly payments of 5/-.
- READY RADIO 303 COMPLETE KIT.**
Cash or C.O.D., 48/17/6, or 12 monthly payments of 12/7.
- OSRAM MUSIC MAGNET COMPLETE KIT.**
Cash or C.O.D., 49/9/-, First payment, 15/-, balance in 11 monthly payments of 12/6.
- BLUE SPOT SPEAKER TYPE 100U.**
Cash or C.O.D., 41/12/6, or 12 monthly payments of 3/2.
- BLUE SPOT 50 P.M.**
Cash or C.O.D., 42/19/6, or 12 monthly payments of 5/6.
- ROLA PERMANENT-MAGNET MOVING-COIL SPEAKER TYPE F.6.**
Cash or C.O.D., 42/9/6, or 12 monthly payments of 4/6.
- EPOCH 20C PERMANENT-MAGNET MOVING-COIL SPEAKER.**
Cash or C.O.D., 41/15/-, or 8 monthly payments of 6/6.
- W.B. PERMANENT-MAGNET MOVING-COIL SPEAKER TYPE P.M.2.**
Cash or C.O.D., 49/5/-, or 8 monthly payments of 7/9.
- W.B. PERMANENT-MAGNET MOVING-COIL SPEAKER TYPE P.M.4.**
Cash or C.O.D., 42/2/-, or 8 monthly payments of 5/9.
- R. & A. VICTOR PERMANENT-MAGNET MOVING-COIL SPEAKER DE LUXE.**
Cash or C.O.D., 43/10/-, or 12 monthly payments of 6/5.
- R. & A. BANTAM PERMANENT-MAGNET MOVING-COIL SPEAKER.**
Cash or C.O.D., 41/7/6, or 6 monthly payments of 5/-.
- ATLAS ELIMINATOR TYPE A.C. 244.**
Cash or C.O.D., 42/19/6, or 12 monthly payments of 5/8.
- EKO H.T. ELIMINATOR A.C.12.**
Cash or C.O.D., 42/15/-, or 12 monthly payments of 5/-.
- EKO H.T. UNIT TYPE A.C.25.**
Cash or C.O.D., 43/17/6, or 12 monthly payments of 7/-.
- GARRARD INDUCTION MOTOR MODEL 232.**
Cash or C.O.D., 42/10/-, or 12 monthly payments of 4/7.

Miscellaneous Components, Accessories, etc., etc., supplied CASH, C.O.D., or H.P. on our own Private System of Easy Payments.

Any items advertised in this journal sent C.O.D. If value over 10/- sent all C.O.D. charges paid.

To NEW TIMES SALES CO., 56 Ludgate Hill, London, E.C.4. Telephone: Central 2716

Please send me (a) Your 1933 Catalogue

(b) for which I enclose first payment of £.....

Name


Address

SAFEST FOR EASY TERMS

Send FIRST PAYMENT with order and ensure PROMPT DELIVERY



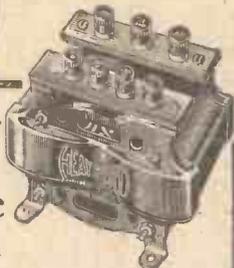Make your Receiver All-Electric for 12s. 6d.



If you already have a Mains Unit for your H.T. supply, you can make your receiver All-electric by scrapping your battery valves and accumulator, and fitting A.C. valves instead. All you need then is a Heyberd Mains Transformer, giving 4 volts, to operate your A.C. valves from the Mains.

HEYBERD MODEL 723 L.T. TRANSFORMER. Secondary output: 2+2 volts 3 amps. Price 12/6
Mains Transformers of all types are given in the Heyberd 1933 Catalogue and Handbook.



Post Coupon
for Heyberd handbook on Mains Working
I enclose 3d stamps for New Handbook of Mains Equipment. Packed with Technical Tips, Service Hints and diagrams

Mr. _____
Address _____

F.C. HEYBERD & Co.,
10 FINSBURY STREET, LONDON, E.C.2
One minute from Moorgate Stn

THE SCOTTISH SHOW

THE Scottish National Radio Exhibition which is being held in the Waverley Market, Edinburgh, closes this Saturday, October 22. Readers who have not yet taken advantage of this opportunity to see the latest wireless goods displayed in this popular centre of Edinburgh are strongly advised to do so. An accompanying list shows that at the Scottish National Show are represented not only the leading radio firms in Scotland, but manufacturers of National repute.

The Exhibition is organised under the auspices of the Radio Manufacturers' Association and the B.B.C. has an exhibit of outstanding interest. This is a model studio from which programmes which would normally be put on in the Scottish Broadcasting House in Queen Street, Edinburgh, are staged every day at the Exhibition.

The admission is 6d. and special arrangements have been made for those going to

LIST OF EXHIBITORS THIRD SCOTTISH NATIONAL RADIO EXHIBITION, WAVERLEY MARKET, EDINBURGH

- | | |
|-------------------------------------------|--------------------------------------------|
| Peter H. Ronaldson | Spensers (Scotland), Ltd. |
| Thomson & Brown Bros., Ltd. | Jenners, Princes Street, Edinburgh, Ltd. |
| Ultra Electric, Ltd. | D. & G. Innes |
| L. McMichael, Ltd. | National Accumulator Co., Ltd. |
| The British Radiophone, Ltd. | A. G. Cossor, Ltd. |
| A. Borland | The British Broadcasting Corporation |
| Edinburgh Rubber Co. | A. H. Baird |
| Partridge, Wilson & Co. | Michael Black, Ltd. |
| Allied Music Traders, Ltd. | T. T. Young & Co. |
| R. S. Macrae | The General Electric Co., Ltd. |
| John Ritchie & Co. | Fychon, Ltd. |
| Oldham & Son, Ltd. | Murphy Radio, Ltd. |
| Wood & Cairns, Ltd. | James Robertson |
| H. Clarke & Co. (Manchester), Ltd. | Kenwell Radio, Ltd. |
| Ionia, Ltd. | Gilbert Ashton & Co. |
| Robt. B. Donaldson | Radio Gramophone Development Co., Ltd. |
| H. C. Rawson (Sheffield and London), Ltd. | Electrical and Radio Products (1931), Ltd. |
| E. K. Cole | Henry Tatton & Son |
| Chloride Electrical Storage Co. Ltd. | Caledonian Wireless Colleges, Ltd. |
| The Edison Swan Electric Co., Ltd. | Baxendale & Co., Ltd. |
| Philips Lamps, Ltd. | Simpsons Electricals, Ltd. |
| Chas. A. Osborn | The Glycinate Supply Co. (1922), Ltd. |
| The Marconiphone Co., Ltd. | Stenibae (Cabinets), Ltd. |
| Irranic Electric Co., Ltd. | Siemens Electric Lamps and Supplies, Ltd. |
| Roberts Radio | Mullard Wireless Service Co., Ltd. |
| Epoch Radio Manufacturing Co., Ltd. | Ever Ready Co. (G.B.), Ltd. |
| Radiovision, Ltd. | |

the Show to obtain vouchers entitling their holders to travel from any station in Scotland to Edinburgh at single fare for the double journey. Particulars of this scheme and any other details in connection with the Scottish National Show can be obtained at the Organisers' Office, 6-7 Waverley Market, Edinburgh.

TURN TO PAGE 837

The set of the century—the "New Century Super"!

"Amateur Wireless and Radiovision." Price Threepence. Published on Thursdays and bearing the date of Saturday immediately following. Post free to any part of the world: 3 months, 4s. 6d.; 6 months, 8s. 9d.; 12 months, 17s. 6d. Postal Orders, Post Office Orders, or Cheques should be made payable to "Bernard Jones Publications, Ltd."

General Correspondence is to be brief and written on one side of the paper only. All sketches and drawings to be on separate sheets. Contributions are always welcome, will be promptly considered, and if used will be paid for. Communications should be addressed, according to their nature, to The Editor, The Advertisement Manager, or The Publisher, "Amateur Wireless," 58-61 Fetter Lane, London, E.C.4

QUICK EASY PAYMENT SERVICE

We supply all good quality Radio Receivers, and Accessories on deferred terms. Large stocks are carried and orders are executed promptly. Price List free on request

MANUFACTURERS' KITS

NEW LISSEN "SKY-SCRAPER" KIT, including Valves. This is an outstanding Kit, and we can strongly recommend it. Cash price, 8/3
And 11 monthly payments of 8/3.

NEW TELSEN AJAX 3. Complete Set of parts for Det.; 2 L.F. Receiver, less Valves. Cash Price, £3/1/6.
And 11 monthly payments of 5/8.

READY RADIO "METEOR" S.G.3 KIT, including cabinet, valves, and moving coil unit. Cash Price, £3/17/6.
And 11 monthly payments of 16/8. This Receiver also tunes to Ultra-short Waves.

READY RADIO 303 KIT. Cabinet Model, including moving-coil unit and valves. Cash Price, £6/17/5.
And 11 monthly payments of 12/9.

ACCESSORIES

NEW R. & A. "VICTOR" PERMANENT MAGNET MOVING-COIL REPRODUCER DE-LUXE. One of the finest Moving Coil Units available. With 6-ratio Transformer and Cadmium plated Grill. Cash Price, £3/10/-.
And 11 monthly payments of 6/5.

NEW ORMOND PERM. MAGNET MOVING-COIL L.S. UNIT. (just released) Cash Price £1/13/6.
And 7 monthly payments of 5/4.

ATLAS ELIMINATOR, A.C.244. 3 H.T. Tappings. 20 M/A output. Cash Price, £2/13/3.
And 11 monthly payments of 5/6.

NEW R. & A. "CHALLENGER" PERM. MAGNET MOVING-COIL UNIT. Cash Price, £1/15/-.
And 6 monthly payments of 5/8.

NEW EPOCH 20c PERMANENT MAGNET MOVING-COIL UNIT. Cash Price, £1/15/-.
And 6 monthly payments of 5/7.

NEW BLUE SPOT 99 P.M. MOVING-COIL UNIT. Cash Price, £2/19/6.
And 11 monthly payments of 5/6.

BLUE SPOT 100U. INDUCTOR UNIT. Cash Price, £1/12/3.
And 6 monthly payments of 5/2.

All above carriage paid.

To avoid delay, will customers kindly send first payment with order.

Goods ordered C.O.D. are dispatched by return of post. All Post charges paid by us.

The LONDON RADIO SUPPLY COMPANY ESTD 1925
11, Oat Lane, Noble St., LONDON, E.C.2
Phone NATIONAL 1977



Hear the difference now? That's what a "TONAX" does for you. Only three minutes to fit and every trace of chatter, "buzz" and rattles gone. Reproduction is clean and you'll find those "foreigners" come in louder & clearer.

TONAX IMPROVED CONE ADAPTOR

From most dealers or Post and Packing Free for 1s. 2d. P.O.

Money returned if not satisfied.

Write Dept. "A."

GARRATT STORES, 193 GARRATT LANE, WANDSWORTH, S.W.18.

REPAIRS to Loudspeakers 4/-. Blue Spots 5/-. Transformers 4/-. Moving Coils, etc. quoted for. Prompt Service. 12 months guarantee. Trade Invited. Streatham 6818. Loud-speaker Repair Co., 2 SHIPKA ROAD, Balham, London

OUR LISTENING POST

By JAY COOTE

RECEPTION conditions, generally, during the past week have vastly improved and I have been able to register the reappearance of a number of transmissions which, although constituting nightly logs last winter, had entirely faded away during the spring and summer months. Amongst these are Reykjavik, Ljubljana, and Riga. The first named was well received on several nights, and in particular at the end of the week, as it keeps up its broadcast of dance music on Saturdays until midnight, which corresponds to our 1 a.m. G.M.T. In addition, I picked up on two evenings what appeared to be test transmissions from Rostov-Don (U.S.S.R.) on 848.7 metres. From a 4-kilowatt, according to reports, it has developed into a high-power station and, notwithstanding its distance from London, was clearly heard between 9.45 and 10.15 p.m. G.M.T. The studio, similar to most of the Russians, possesses both a man and woman announcer.

The Power Goes Up

If Hilversum on 296.1 metres is one of your favourite stations, its increased power during the evening will have been welcome. The new 20-kilowatt transmitter does not work during the daytime. In addition to the extra power, the station has been equipped with an ultra-modern vertical aerial some 148 metres high. Personally, I am very pleased that the A.V.R.O. and V.A.R.A. broadcasts now occupy the lower channel for a further three months.

Beromuenster and Sottens now appear in my log with three stars against them as reliable stations to which to turn on any evening. Moreover, the Berne, Basle, and Zurich studios, in order to give their listeners an insight into foreign programmes, have decided to carry out relays at regular intervals. Curiously enough, it was through Beromuenster I heard the best relay of the opera *Faust* as performed at Paris on October 8. Both Ecole Supérieure and the Eiffel Tower, which took it, were poor transmissions.

Berlin on Short Waves

This reference to relays also reminds me that Berlin has been carrying out tests on short waves with Buenos Aires as a preliminary to an interchange of programmes. They will take place on Tuesdays and Fridays between 10 and 11 p.m. G.M.T. It will also be possible to hear them through Zeesen on 31.38 metres as well as through most of the German stations on the broadcast band.

Whether it is possible to pick up broadcasts from the experimental station at Craiunelu on 2,000 metres I cannot say, but freak reception also, exists on the longish waves, and it might be worth your while to make a search for this Rumanian station. Its power is 1 kilowatt and its duty that of providing field measurements to assist in finding a suitable site for the high-power transmitter which Budapest intends to install.

A correspondent recently wrote to me that on a wavelength between 1,800 and 2,000 metres he had heard a call, "Hallo! Hallo! Vitajé," but failed to trace it. Should you hear this at any time, bear in mind that the official call-letters allotted to Radio Paris are F8AJ, or in French (phonetically) *Eff-wit-ah-ehay*, and consequently this was a test by the Radio Paris transmitter.

But here is a puzzle. Has anybody heard a call on about 439 metres, in possibly Spanish or Portuguese, which sounded something like *Radio Maveeko*? I am told that it was picked up in the early hours of the morning, and it does not tally with the name of any existing station in Europe.



When you throw away an old H.T. Battery, you throw away voltage you cannot use. You are wasting money.


The Lively 'O' H.T. Accumulator stops waste—definitely! From the moment it is charged, up to the time it needs recharging, it is full of power-giving life—full of powerful energy—full of punch! No self-discharge—no leakage—its "Air-Spaced" cells are leakage-proof. The Lively 'O' H.T. Accumulator gives you constant voltage. Smooth, silent current—power that never varies. Isn't that the kind of H.T. supply you've always wanted? Your dealer stocks the Lively 'O' H.T. Accumulator.

Oldham & Son Ltd., Denton, Manchester. Estd. 1865, and at London, Glasgow, Belfast & Dublin

TWO TYPES

Standard 10 volt unit capacity 2,750 milliamps - **5/6**

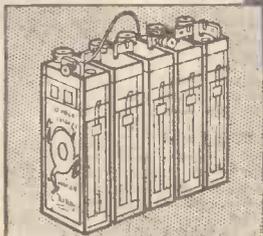Extra large capacity 5,500 milliamps (10 volt unit) - **6/9**



The Lively 'O' H.T. ACCUMULATOR

PREPAID ADVERTISEMENTS

Advertisements under this head are charged THREEPENCE PER WORD, minimum charge THREE SHILLINGS. DEPOSIT SYSTEM. As the publishers cannot accept responsibility for the bona fides of advertisers in this publication, they have introduced a system of deposit which it is recommended should be adopted by readers when dealing with persons with whom they are unacquainted.

The amount of the Deposit and Fee must be remitted by Postal Order or Registered Letter (Cheques cannot be accepted), addressed to "AMATEUR WIRELESS," ADVERTISEMENT DEPARTMENT, 58/61 FETTER LANE, LONDON, E.C.4.

RYALL'S RADIO, 33 Chancery Lane, London, W.C.2. New, surplus, and tested used radio components at very reasonable prices. Write for free list or inspect our display personally. We purchase approved goods for cash, or accept same in part payment for new only.

A BETTER OPPORTUNITY awaits you in Radio and Sound Picture Engineering! Intensely practical, fascinating home-study courses, whole or part time. Valuable introductions. Prospectus free.—Radio Training Institute, Union Buildings, St. John Street, Newcastle-on-Tyne, 1.

THE RADIO INDUSTRY.—During the past twenty years I have placed nine hundred students in good permanent posts. I have devised a Home Study course, followed, if desired, by two weeks practical training. Prospectus free.—H. F. Yardley, M.I.R.E., A.I.E.E., Northern Counties Wireless School, Preston.

SUPPLY YOUR FRIENDS with Anything Wireless. Join our Club and get 20-25 per cent. discount. Stamp for particulars.—Radio Supplies, 337 North Road, Darlington, Durham.

"A.W. BATTERY-OPERATED POWER AMPLIFIER."—Author's Kit. Special 7-day cash offer. Exchanges. C.O.D. H.P. lists free.—Melford Radio, Holmes Avenue, Hove.

OAK CABINETS, beautifully finished, hinged lid, 14 in. by 7 in. by 10 in., 7/6; 16 in. by 7 in. or 8 in., and 18 in. by 7 in. by 10 in., 8/-. Baseboards, 9d., carriage paid. Refused unsatisfied. Hundreds sold. Other sizes made. Panels, etc., supplied. Send for list of cabinet required. Speaker cabinets from 5/6. Stand cabinets, 30/-. Radio-Gram., 37/- State nearest station.—Gibson, Cabinet Maker, 99 Burnley Road, Alnsdale, Lancs.

COMPLETE KITS for the "Quality 30/- Two," or separate components supplied on special terms; also Speakers, Batteries, Mains Units; cash or C.O.D.—Highbury Supply Stores, 44 Highbury Hill, N.5.

ARE YOU CONTEMPLATING BUILDING A NEW SET? Save time, trouble, and risk by having it built for you; any specified set constructed, installed, and guaranteed for the price of components only. No extras; easy terms arranged.—Radio Construction, 204 Doyle Gardens, London, N.W.10. Phone: Willesden 5593.

EXPONENTIAL METAL HORNS for cabinets. Clearing huge stock, all types. Prices from 2/6 each.—Bowley, Gramophone Manufacturers, Mossbury Road, Clapham Junction, London.

SUPPLY YOUR FRIENDS' wireless requirements and make money. Particulars from "Wireless," 76 Wiverton Road, London, S.E.26.

BANKRUPT BARGAINS.—List free with 3-valve diagram. Three-valve Kit, 22/6; S.T. 300 Kit, 42/-; Century Super, 75/-; Wizard, 50/- Any kit supplied. If you have some modern parts on hand and require new goods, write for my exchange offer. Air-spaced .0005 S.M., 3/6. Mica .0005, 10d. Dual Coils, 3/6. Fixed, 5d. Leaks, 5d. Transformers from 2/9. Panels from 2/3. H.F. Chokes from 1/-. Millgate Speaker Units, 2/6. Triotron, 8/6. Magnavox D.C. M.C., 25/-. Millgate D.C. M.C., 18/6. P.M. type M.C., 22/6. D.C. Eliminators from 16/6. Get my price for any kit or set. Quotations per return. Anything wireless.—Butlin, 143b Preston Road, Brighton.

KNOWLEDGE SAVES MONEY.—You can't read all wireless papers or all makers' catalogues. You can read "Wireless Notes" each month. It gives a complete review of the month's radio press, telling which sets to build. Also frank criticism of commercial components and sets and an absolutely unique information service. Particulars from Capt. Robinson, Langmead, Pirbright, Woking.

47/8.—Met.-Vick A.C. eliminators, guaranteed new, with U.U.60/250 Mazda valve, manufacturers' surplus. Suitable for Screen-grid 3- or 4-valve Sets; output 40 m.a., 200 volts, automatic bias, 4 volts 4 amps. A.C., early stage and S.G. tapping; carriage paid. C.O.D. or cash with order; send for list of other unused bargains.—Seekamp, 46 Farringdon Street, E.C.4.

30/.—B.T.H. R.K. moving-coil speakers, guaranteed new, unused manufacturers' surplus; original price 6 guineas; these are highly sensitive and have a wonderful response to high and low notes, will handle heavy outputs. Available for 6 volts, 100 volts, 200 volts D.C. A.C. models, £2/10.—Ask for list of other unused bargains; carriage paid, C.O.D. or cash with order.—Seekamp, 46 Farringdon Street, E.C.4.

£5/10!—Power Pentode Two Edison A.C. mains receiver, listed at £12/10, guaranteed brand new, complete with new Mazda valves, A.C./H.L., A.C./PEN, and U.U.60/250 rectifier valve, a modern receiver with a high output, suitable for operating a moving-coil speaker on radio or gramophone; carriage paid, cash with order, or C.O.D.—Seekamp, 46 Farringdon Street, E.C.4.

AGENTS WANTED to sell Private Christmas Cards. Sample Book Free. Good Commission.—Apply, Denton Ltd., Dept. D118, Accrington.

SPECIFIED KITS AND COMPONENTS etc. at special discounts. Write Childs, 29 Moray Road, London, N.4.

"UNIVERSAL" RADIO BARGAINS.—Valves from 3/11. Screen-grid, 8/11. Dual Coils, 2/-. Speaker Units, 2/11. Premier Transformers, 2/8. Volt Meters, 2/11. S.T.300 Coils, 5/11 pair. Chokes, 1/-. Accumulators, 2/9. Slow-motion Dials, 1/3. Variable Condensers, 1/6. Fixed, 5d. Leaks, 5d. Diffs., 1/6. Valve Holders, 4d. Ebonite Panels from 2/6. UNIVERSAL All-wave Tuners, get more stations at greater volume; Paris as loud as your local, 5/6, post free, including blueprint. Print separate, 2d. Thousands of other radio bargains. Lists free. Get our quotation for any Component, Kit, or Set.—"Universal," 20 Victoria Road, Peckham, S.E.15.

ENGINEERS.—Sit down and think this over. We believe that our 200-page handbook, "Engineering Opportunities" will show you the way to well-paid, permanent and progressive employment. In any case, the handbook costs nothing, and it will at least show you various surprising possibilities about which at present you know nothing. Can you, as any man, who cares a hoot about his future, afford to allow this opportunity for a worth-while job to pass unheeded. Think it over. Can you? We want you to read "Engineering Opportunities." Among other things it gives details of all recognised examinations (A.M.Inst.C.E., A.M.I.Mech.E., I.E.E., G.P.O., etc.), outlines modern Home-study Courses in all branches of Civil, Mech., Elec., Motor, Radio, Aero and Talkie Engineering, and explains the unique advantages of our Employment Department. The book is quite free. Send a post-card for your copy NOW. We promise that it will be a moment of your time well spent.—The British Institute of Engineering Technology, 100 Shakespeare House, 29-31 Oxford Street, London, W.1.

RADIO.—Special discount home constructors.—Write, Page, 42 Moray Road, London, N.4.

GILBERT INDUSTRIES offer following guaranteed bargains, all post paid. Healyberd Chokes, type 757, 50h 150 ma., new and boxed, 15/-; Tapped 2-ratio pentode chokes, heavy, 6/-; 20h 10 ma. eliminator chokes 3/6; 3-gang 0.0005 by Polar, end vane trimmers and continuous slow-motion drive 9/-. Polymet 8-mfd. 435v. working voltage electrolytics 4/-. Special mains transformer, input 210, 230, 250, output 2v. 4 amp. C.T., 4v. 2 amp., 325-0-325 at 85 ma, 15/-.—Gilbert Industries, 519 London Road, Westcliff-on-Sea.

THE "TONIC" keeps any make 2-volt Accumulator fully charged at home. Electric mains unnecessary. Ideal for remote places. 7/- each, postage 9d. Particulars, copies of testimonials, etc., with pleasure.—Williams, Netherend, Cradley, Birmingham.

1933 RADIO SETS, Kits, Speakers, Components. Your old Radio equipment taken in part payment. Top prices allowed. Coupons accepted.—Rad-Auto-Gram Co., Tulketh Street, Southampton.

THE REPRODOME.—Improves your speaker 100 per cent. Ensures mellow tone. Easy to make. Blueprint, full instructions 1/3.—Reprodome, 145 High Holborn, W.C.1.

CHARGE YOUR H.T. FROM YOUR L.T. AT HOME.—Combination trickle. Charges efficiently 1 to 12. H.T. 10-volt accumulators, 10/6. Postage 6d. Diagram only, 1/6.—R. Fox, 188 Camberwell Grove, S.E.5.

SPECIAL OFFER OF T.O.C. CONDENSERS.—Brand New Bankrupt-stock. 2 mfd., 500v. A.C. test, 1/9; Blocks 2x2x2x1 mfd., 500v. D.C. test, 6/3. Reduction for quantities. Lists of others.—Pepper, Wakegreen Road, Birmingham.

2/6. A TIT-BIT FOR YOUR SET.—Complete kit with instructions for building efficient "Long Distance" mains aerial. Improved reception on any receiver. Plugs into lamp-holder.—Unlonwave Radio Co., Devonport Road, London, W.12.

WIRELESS YOUR HOUSE NOW.—Inclusive charge covering switching, flex and speaker, 12/- per room. State distance to be covered. Surplus stock quality cone speakers, etc., makes this remarkable offer possible.—City Radio Surplus Supplies, 14 Cursitor Street, London, E.C.4.

RADIO AT LESS THAN COST! Kits and Components. Send list of requirements. 20-80 per cent. saving guaranteed now. "This Week's Special" comprising limited stock, quality components below cost (Dubilier, Burndet, etc.): L.F. Transformers, 1/3; Binocular H.F. Chokes, 6d.; Speaker Units, 1/11; variable condensers (.0003, .0005), 10d.; Fixed Condensers, Valve Holders, 3d.; Grid Leaks, 4d.; 3-pole Switches, 11d.; Valves, guaranteed, 2/11; P.M.M.C. Speakers, 22/6; Kits (with diagrams), 3-valve S.G., 18/6; 3-valve, 10/6. Special selected "A.W." kits at greatly reduced prices carefully compiled from surplus stocks, and specified components where necessary. "Full price results" guaranteed. "Wizard" Kit for 48/-. With valves and cabinet, 77/6. "30/- Two" for 19/6. With valves and cabinet, 37/6. Any goods sent C.O.D.—City Radio Surplus Supplies (Dept. A.W.), 14 Cursitor Street, London, E.C.4.

The ACME of CRAFTSMANSHIP High Grade RADIO GRAMOPHONE CABINET of exclusive modern design, with record wells, handmade and polished, on Queen Anne legs. Figured Oak, Figured Walnut, or Figured Mahogany, Remarkable Values. Illustrated Catalogue Free. Cabinets made to order a speciality. GILBERT Cabinet Maker, SWINDON Estimates Free. Estd. 1886.



FULL-SIZE BLUEPRINTS

When ordering, please send Postal Order, NOT STAMPS.

CRYSTAL SET (6d.) 1931 Crystal Set .. AW308 ONE-VALVE SETS (1s. each) Easy to Build One .. AW304 Short-wave One-valver .. AW327 B.B.C. One-valver .. AW344 Portable Short-wave One .. AW354

TWO-VALVE SETS (1s. each) Two Star 2 (D, Pen) .. AW315 25/- Two (D, Trans) .. AW330 Ten-Station Two (D, Trans) .. AW336 Inexpensive A.C. 2 (D, Trans) .. AW346 Midget Two (D, RC) .. AW348 Mascot Two (D, Trans) .. AW353 Ideal Regional 2 (D, Trans) .. AW357 Quality 30s. Two (D, Trans) .. AW361 Music Lover's Two (D, Trans) .. WM260 New Economy Two (D, Trans) .. WM265 Family Two (D, Trans) .. WM278 Screen-grid Two (SG, Trans) .. WM289 Economy A.C. Two (D, Trans) .. WM286 A Two for 7 Metres (D, Trans) .. WM295 New-style Radiogram (D, Trans) .. WM299

THREE-VALVE SETS (1s. each) 1932 Ether Searcher (SG, D, Pen) .. AW325 New Favourite Three (D, RC, Trans) .. AW334 Home-Lover's All-electric 3 (SG, D, Trans) .. AW335 P.W.H. ("Mascot") D, RC, Trans .. AW337 Home-Lover's Battery 3 (SG, D, Trans) .. AW341 £8 Radiogram (SG, D, Trans) .. AW343 New Regional Three (D, RC, Trans) .. AW349 World-Ranger Short-wave Three (D, RC, Trans) .. AW355 Wizard (SG, D, Trans) .. AW360 Ether Marshal (SG, D, Trans) .. WM247 Five-advantage Three (D, RC, Trans) .. WM257 Everybody's A.C. Radiogram (SG, D, Trans) .. WM258 Double Band-pass Three (SG, D, Trans) .. WM259 Everybody's A.C. Radiogram (with automatic G.B.) .. WM262 New Economy Three (SG, D, Trans) .. WM263 New Plug-in Coil Three (D, 2 Trans) .. WM270 Transportable Three (SG, D, Trans) .. WM271 Multi-Mag-Three (D, 2 Trans) .. WM285 Percy Harris A.C. Radiogram (D, RC, Trans) .. WM294 Prosperity Three for Batteries (SG, D, Trans) .. WM296 Prosperity Three for A.C. Mains .. WM297 Prosperity Three for D.C. Mains .. WM298

FOUR-VALVE SETS (1s. 6d. each) Four Star 4 (SG, D, RC, Trans) .. AW318 Advance Four (2 SG, Trans) .. AW356 Your Home Radiogram, (SG, D, RC, Trans) .. AW358 Brookman's Three-plus-one (SG, D, RC, Trans) .. WM233 Ether Rover (SG, D, RC, Trans) .. WM266 Quadradyne (2 SG, D, Pen) .. WM273 Double Band-pass Four (SG, D, RC, Trans) .. WM274 Everybody's Radiogram, (SG, D, RC, Trans) .. WM276 A.C. Quadradyne (2 SG, D, Pen) .. WM279 Ideal A.C. Home Super (Super-list) .. WM290 Gold Coaster (A.C. Short-waver) .. WM292 Triple-tune Four (2 SG, D, Trans) .. WM293 Calibrator (SG, D, RC, Trans) .. WM300

FIVE-VALVE SETS (1s. 6d. each) James Short-wave Super (Super-het) .. AW328 Simple Super (Super-het) .. AW340 Ideal Home Super (Super-het) .. WM280 Easytune 60 (Super-het) .. WM284

SIX-VALVE SETS (1s. 6d. each) Century Super (Super-het) .. AW287 A.C. "Century Super" (Super-het) .. AW295 "Mains Unit (1/-) .. AW295A Super 60 (Super-het) .. WM229 Super 60 (with Wearite base) .. WM249 Super 60 (with Lewcos base) .. WM251 1932 Super 60 (Super-het) .. WM269 1932 A.C. Super 60 (A.C. Super-het) .. WM272

SEVEN-VALVE SETS (1s. 6d. each) Super Senior (Super-het) .. WM256 Super Senior (Wearite base and Lewcos coils) .. WM261

PORTABLES (1s. 6d. each) Hiker's Two (D, Trans) (1/-) .. AW345 General-purpose Portable (SG, D, RC, Trans) .. AW351 Town and Country Four (SG, D, RC, Trans) .. WM282 Everybody's Portable (5-valve super-het) .. WM291

AMPLIFIERS (1s. each) Universal Push-pull Amplifier .. AW300 "A.W." Record Player (LF, Push-pull) .. AW319 The Battery-operated Amplifier .. AW362 Quality Amplifier (DC), 1/6 .. WM264 A-P-A (Power, Amplifier for A.C. Mains) .. WM275

MISCELLANEOUS (1s. each) Short-wave Plug-in Adaptor (6d.) .. AW326 Short-wave Super-het Adaptor (6d.) .. AW329 Ether Searcher Radio-gramophone Motor Board .. AW333 "A.W." Short-wave Adaptor .. AW339 "Mascot" Mains Unit .. AW350 "A.W." Trickle Charger .. AW352 Add-on Band-pass Unit .. AW359 Copies of the "Wireless Magazine" and of "Amateur Wireless" containing descriptions of most of these sets can be obtained at 1s. 3d. and 4d. respectively, post free. Index letters "A.W." refer to "Amateur Wireless" sets and "W.M." to "Wireless Magazine." Address letters:

Amateur Wireless Blueprints Dept., 58-61 Fetter Lane London, E.C.4

RADIO SUPPLIES Send your list of Radio needs for our quotation. Kits, Parts, Sets, etc. Everything in Radio stocked. Prompt delivery; seven days' approval. Catalogue free. Taylex and Standard Wet H.T. replacements stocked. A. TAYLOR, 67 STUDLEY ROAD, STOCKWELL, LONDON

Amateur Wireless INFORMATION BUREAU COUPON Available until Saturday OCTOBER 29, 1932 FEE 1/-

**SAVE MONEY
ON RADIO COSTS!**



Buy Pertrix Dry Batteries and Accumulators for efficient service and long life. Pertrix Patent Dry Batteries with their remarkable recuperative powers give a life that is amazing in its length. The secret is in the patent construction and the high quality of the materials used, and it is this that makes Pertrix such an economical proposition.

Pertrix Accumulators with their robust construction and patent Kaptive Karrier give unending trouble-free service.

The world's most economical Batteries

PERTRIX



DRY BATTERIES & ACCUMULATORS



Advt. of Britannia Batteries Ltd., 233, Shaftesbury Avenue, London, W.C.2.
Telephone: Temple Bar 7971 (5 lines). Works: Redditch (Worcs.).
Branches: Manchester, Glasgow, Bristol and Dublin.

The Star

CONFIRMS OUR CLAIMS

“The British Blue Spot loud-speaker 100D is one of the few loud-speakers to challenge the higher-class moving-coil reproducer. It is definitely better than the usual low-priced moving-coil in sensitiveness and in range. It will reproduce frequencies as low as 50 and yet give a beautiful quality to the higher notes and preserve a natural speech. At 52s. 6d. it is exceptionally good value.”

Extract from "The Star" Saturday October 8th issue.

DON'T be tempted to buy "cheap" moving-coil speakers which by their very nature and price cannot guarantee you LASTING satisfaction. 100D (or in unit form mounted to chassis 100U, price 32/6) guarantees you perfect reproduction of all programmes with every item clear and true to life.

There are other advantages which *no* moving-coil speaker can offer. 100D can be used with normal or Pentode valves without the addition of a matching transformer. 100D is sensitive even to small inputs and is therefore equally efficient with battery and all-mains receivers.

Get a demonstration at your dealers or send to-day for catalogue A.W.54S. and get full particulars.

BRITISH MADE

100D 52/6
IN OAK



BLUE SPOT RECEIVERS


The most modern of all and wonderful performers. Send for particulars (catalogue No. A.W.54R.) of the Blue Spot Battery Four and All Mains Five.

THE BRITISH BLUE SPOT CO., LTD.
Blue Spot House, 94-96 Rosoman Street,
Rosebery Avenue, London, E.C.1
Telephone: Clerkenwell 5370
Distributors for Northern Ireland, Scotland and Wales: H. C. RAWSON (Sheffield and London), Ltd., 100, London Road, Sheffield; 22, St. Mary's Parsonage, Manchester; 41-46 High Bridge, Newcastle; 37, 38, 39, Clyde Place, Glasgow.



Don't Forget to Say That You Saw it in "A.W."

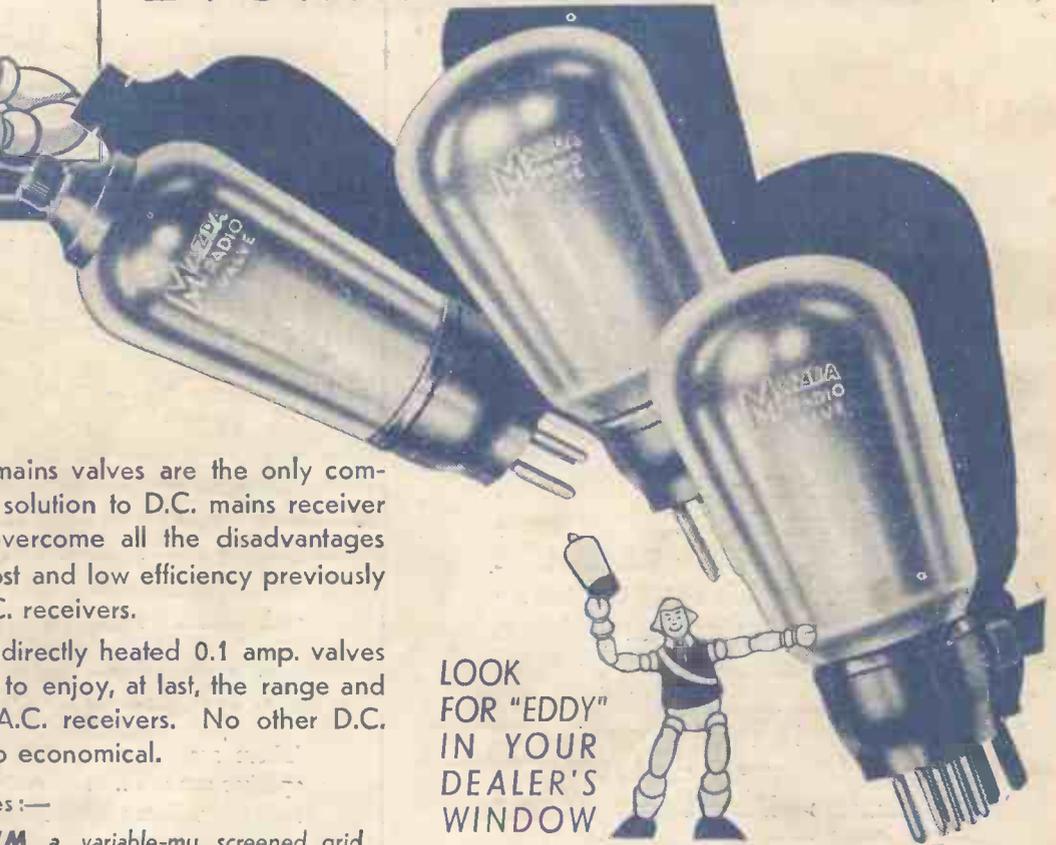FACTS YOU SHOULD KNOW ABOUT THE MAZDA D.C. MAINS RANGE . . .



The Mazda D.C. mains valves are the only completely satisfactory solution to D.C. mains receiver operation. They overcome all the disadvantages of high running cost and low efficiency previously associated with D.C. receivers.

The new Mazda indirectly heated 0.1 amp. valves enable D.C. users to enjoy, at last, the range and quality given by A.C. receivers. No other D.C. mains valves are so economical.

The Range comprises:—

THE DC 2/SGVM a variable-mu screened grid valve giving results fully equal to its A.C. counterpart.

THE DC 2/SG is for those who wish to use an ordinary screened grid valve.

THE DC 3/HL for the detector stage.

THE DC 2/P or DC 2/Pen for the output stage.

Full details of these and other useful Mazda types will be found in the Mazda catalogue, sent FREE on request.

Mazda valves are fitted by all the leading receiver manufacturers. All good radio dealers stock them.

LOOK FOR "EDDY" IN YOUR DEALER'S WINDOW



The amazing
MAZDA
THE
BRITISH
VALVES

EDISWAN RADIO

100% BRITISH—Designed by British Engineers

The Edison Swan Electric Co. Ltd.



155 Charging Cross Rd. London. W.C.2

Mazda Radio Valves are manufactured in Great Britain for

The British Thomson-Houston Co. Ltd., London and Rugby.

V.205