

Amateur Wireless.  
March 4, 1933

**METAL DETECTORS INSTEAD OF VALVES!**

**NEW METHODS OF CUTTING OUT NOISES**

# Amateur Wireless

and  
Radiovision

**A.B.C.  
of the PENTODE  
in BEGINNER'S SECTION**

Every  
Wednesday  
**3<sup>d</sup>**

Vol. XXII. No. 560

Saturday, March 4, 1933

*The* **A.C. MAINS**  
**MELODY**  
**RANGER**



*Special Article—*  
**NEW**  
**VALVES**  
**FOR 1933**

Registered at the G.P.O. as a newspaper



**A BRILLIANT SUCCESS**

**The Lewcos**  
REGD

**POTENTIOMETERS**

have attained such a high degree of success that they are recognised by experts as the standard of efficiency by which all others are judged. We shall be pleased to send descriptive leaflets, Ref. R. 79 & 81, of these outstanding technical improvements which are moderately priced at 3/- to 9/-.

A Lewcos 50,000 ohm Potentiometer (Price 3/6) and a Type M.C.H.F. Choke (Price 2/6) are specified together with 6 yards of Lewcoflex and Connecting Wire for the A.C. "Melody Ranger."



The London Electric Wire Company and Smiths Ltd.  
Church Road - - - Leyton - - - London, E.10

**WEARITE COMPONENTS**

A Guide to Standard Wearite Components for the "Melody Ranger" and other sets. This book contains full data on all the components used in the "Melody Ranger" and other sets.

**This WEARITE BOOK No. 2 A.I. WILL HELP YOU SEND FOR IT TODAY**

**BEFORE** you start "shopping" for your "Melody Ranger", or for any set, have this booklet, the A.I. beside you. Resistances, chokes, volume controls, mains transformers, switches, etc., they are all there—illustrated with full data—get your copy now.

# HERE'S The WEARITE H.F.O.

—nothing else will do for your 'A.C. MELODY RANGER'



THE Wearite H.F. Choke is the result of much patient research. It is designed and built to cover from 10—2,000 metres without resonance peaks. Because of this, because of the name behind it, the designer of the "A.C. Melody Ranger" uses exclusively the H.F.O.

High frequency instability was the greatest difficulty to be overcome. The designer of the "A.C. Melody Ranger" tested and tested, and only the Wearite H.F.O. proved efficient. Don't jeopardise the quality and performance of your set, play for safety, use the designer's choice, the Wearite H.F.O. — — **PRICE 6/6**

**WEARITE**  
Regd Trade Mark

**WRIGHT & WEAIRE Limited,**  
740, HIGH ROAD, TOTTENHAM, N.17.  
Telephone: TOTTENHAM 3847/8/9

You will Help Yourself and Help Us by Mentioning "A.W." to Advertisers



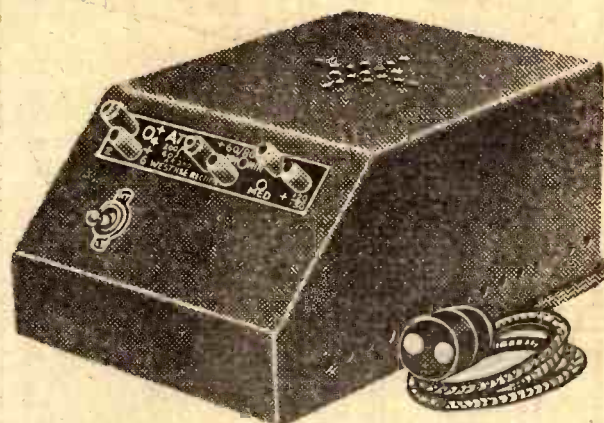
# "ATLAS" MAKE THE ONLY UNITS

suitable for the  
**JAMES "PUSH-PUSH 3"**



**"ATLAS" LATEST  
NEW "Q.P."  
MAINS UNITS  
for  
"Q.P.P."  
RECEIVERS**



**"ATLAS"** are first again with their new "Q.P."

Units specially designed for "Quiescent Push-Pull" and "Class B" Amplification. In these circuits the anode current varies widely according to the signal strength. But the voltage must remain quite steady, regardless of the current passed in order to prevent distortion. The ordinary unit is quite unsuited because its voltage varies with every fluctuation of output current. "ATLAS" "Q.P." Units have specially designed smoothing, voltage regulation and provision for pentode matching and are the only units specified by the author of the "PUSH-PUSH 3." They give an average output of 12 m/A at 150 v., but peak loads of up to 20 m/A are passed without appreciable voltage drop.

<b>MODEL D.Q.P.,</b> for D.C. Mains, H.T. only.	<b>MODEL Q.P.24,</b> for A.C. Mains, H.T. only.	<b>MODEL Q.P.26</b> for A.C. Mains, H.T and L.T. Trickle Charger.
<b>45/-</b> or down.	<b>72/6</b> or down.	<b>£5</b> or down.

**"CLARKE'S  
ATLAS"**

**FIRST AGAIN!**

Messrs. H. Clarke & Co. (M/cr.), Ltd.,  
George St., Patricroft, Manchester.  
Please send me full details of the new  
"ATLAS" "Q.P." UNITS.

Name .....

Address .....

29/4/3

Post coupon to-day for full details and, if your dealer cannot demonstrate, write direct to

**H. CLARKE & CO. (M/CR), LTD., PATRICROFT,  
MANCHESTER.**

London : Bush House, W.C.2.

Glasgow : G.E.S. Co., Ltd., 38 Oswald Street.



# WHY Buy a new set? ETA VALVES make your old set like new!

These are not times to disregard economies. Other valves may cost more than ETA valves but they give you no more for your money.

**FREE** Ask for the ETA "Comparative Table" No. 14a showing which ETA valves to use in place of your old ones.

Technical advice gladly given. Write to THE ELECTRICAL TRADING ASSOCIATION, Aldwych House, Aldwych, W.C.2.

Scottish Agents: Radiovision Ltd. 233, St. Vincent St., Glasgow, C.2.

AMERICAN SETS  
There are ETA  
valves for all  
types of American  
Sets

PRICES FROM

5'6

# ETA

THE INTERNATIONAL VALVE


As low in price as a really good valve can be

## Get a HET for Your Set!
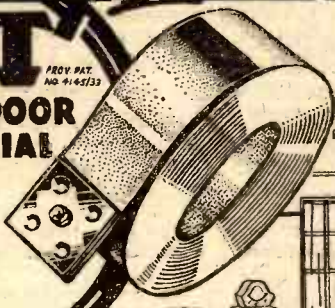
# HET

AMALGAMATED METAL INDOOR AERIAL

Away with unsightly wires. Get greater selectivity, more stations and more volume with the neat and elegant "HET" Indoor Aerial. Just fix this adhesive aerial round the picture rail. It has the appearance of a frieze. It looks as good as it is—better than any other aerial.



BRITISH MADE

In gold or silver finish. From all radio dealers or direct from

UNIVOLT ELECTRIC LTD.  
Balfour House,  
Finsbury Pavement, E.C.2.

## NEW SPEAKER CABINET VALUE



Wonderful results are obtained with units housed in the Camco "Dominion" speaker cabinet—and what a remarkable saving on price. Front 12/6. See it at our showrooms open 9.15 to 5.45 (Sat. 12.30) and send coupon for FREE Camco Cabinet Catalogue. CARRINGTON MFG. CO. LTD.

12/6


Showrooms:  
24 Hatton Garden, LONDON, E.C.1.  
Phone: Holborn 8902  
Works: S. Croydon.



Post in 1d. envelope.

NAME .....  
ADDRESS .....  
18AW .....
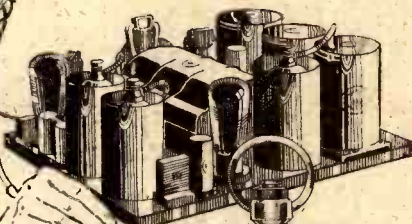
## The DOCTOR of RADIO WILL END YOUR RADIO TROUBLES



Whatever trouble may develop in your radio, the "All-in-One" Radiometer will quickly point to the cause. The "All-in-One" Radiometer is the doctor of radio and instantly diagnoses the reason for any radio trouble. There is no other instrument in the world like it. Ask to see it demonstrated at your radio dealer's or electrician's. If any difficulty, send P.O. direct to PIFCO LTD., High Street, MANCHESTER, or 150 Charing Cross Road, London, W.C.2.



PIFCO  
**ALL IN ONE**  
RADIOMETER

De Luxe Model Above is shown  
or all types of radio. Price Model for  
£2:2:0 Battery Sets  
only. Price 12/6

British Made



## YOU WANT PERFECTION? FOR SHORT WAVES

Then use the original BECOL EBONITE LOW-LOSS FORMER, tested before despatch and reliable.

Prices Low. Look for Trade Mark. Efficiency Tells.

INTERESTING.—Send 6d. (post free) for UP-TO-DATE HANDBOOK of Tuning Coils for Circuits, Dual Range, Band Pass and Super-het, fully illustrated with data.

THE BRITISH EBONITE CO. LTD. HANWELL LONDON, W.7

## 7 DAYS FREE APPROVAL!

H.T. BATTERY ELIMINATORS

2 Years Guarantee BRITISH THROUGHOUT

All A.C. Models incorporate Westinghouse rectifiers and most use 20mfd. condensers

D.C. MODEL

15/-

Send for literature to actual manufacturers.

V.M.C. RADIO COMPANY,  
Mail Order Dept.  
198 Goswell Road, London, E.C.1

A.C. MODEL

30/-

An "Amateur Wireless" Handbook

## THE HOW AND WHY OF RADIO

By ALAN HUNTER

2/6 net

Of all Newsagents and Booksellers, 2/6 post free, from "Amateur Wireless," 58, 61, Fetter Lane, London, E.C.4.

Don't Forget to Say That You Saw it in "A.W."



# PETO-SCOTT

# RADIO BY MAIL

## MELODY RANGER

### PILOT AUTHOR KITS—Exact to Specification

#### A.C. MODEL DESCRIBED THIS WEEK KIT "A"

CASH or C.O.D.  
Carriage Paid.

**£7-7-0**

Author Kit of First Specified Parts for SET PORTION ONLY, including Ready Drilled Panel, Set Baseboard and Screening Foil, but less Valves, Cabinet, Power Pack and Speaker.  
Or 12 monthly payments of 13/6.

#### POWER PACK

CASH or C.O.D.  
Carriage Paid.

**£3-6-6**

Author Kit of First Specified Parts, for Power Pack only including special shelf and baffle but excluding rectifier valve and speaker.  
Or 12 monthly payments of 6/1.

Set of 5 specified Valves .. .. £3 13 6  
Peto-Scott Console Cabinet in oak (less shelf and Baffle) .. .. £1 5 0

#### COMPLETE KIT

Includes all First Specified Components for SET and POWER PACK, including Valves and Cabinet as above (less Speaker).  
Or £2/12/0 deposit and 11 monthly payments of 28/-.

CASH or C.O.D.  
Carriage Paid.

**£15-12-0**

Specified W.B. P.M.4 Speaker £2 2 0 Cash or C.O.D., or add 3/10 to each of the 12 monthly payments.

#### BATTERY MODEL KIT "A"

Author Kit, comprising all FIRST SPECIFIED components, including Ready Drilled engine-turned Aluminum Panel as listed, but less valves and cabinet. Cash or C.O.D. £8/6/0.

**11/6**

Balance in 11 monthly payments of 11/6.  
Set of 4 Specified Valves - £1-19-3

#### "MELODY RANGER" RADIOGRAM

Convert your "Melody Ranger" into a Radiogram by building it into a 1933 ADAPTGRAM, illustrated in "Amateur Wireless," page 285, Feb. 18th issue.

MODEL "A" (Cabinet only). Cash or £3 5 6 C.O.D. Carriage paid.

or 8/3 deposit and 11 monthly payments of 5/9

MODEL "B" With Garrard Motor and B.T.H. Pick-up. Cash or £6 6 0 C.O.D. Carriage Paid

or 12 monthly payments of 12/-

## PILOT Q.P.P. CONVERSION KIT

CONTAINS: 1 Q.P.P. Transformer; 1 Q.P.P. Output Choke; 4 Non-Inductive Resistances; 1 Potentiometer; 2 Mansbridge Condensers; 2 Valve Holders; 1 Tone Compensating Condenser; 1 H.F. Choke; G.B. Plugs; Wires, Screws, Flex, etc.: Complete with FULL-SIZE working diagrams and copious instructional notes.

If GUARDIAN Milliammeter required with Kit, add 10/- to cash price, or 1/5 to Kit "A," or 11d. to Kit "B" monthly payments.

Every purchaser of the PILOT Q.P.P. Conversion Kit is assured of our FULL TECHNICAL ASSISTANCE.

#### KIT "A"

CASH or C.O.D.  
Carriage Paid

**42/6**

or 8 monthly payments of 6/1

#### KIT "B"

but with 2 Pentode Valves, Cash or C.O.D.

£3/17/6, or 12 monthly payments of 7/-.

Set of 2 Valves (separately), £1/15/0.

## JAMES PUSH-PUSH THREE

COMPLETE WITH LISSEN COILS AND UTILITY CONDENSERS AS SPECIFIED

### PILOT AUTHOR KIT

EXACT TO SPECIFICATION

#### KIT "A"

CASH or C.O.D.,  
Carriage Paid

**£5'9'0**

Author Kit of specified parts, including ready-drilled panel, but less valves and cabinet.

Or 12 monthly payments of ... **10/-**

#### KIT "B"

As Kit "A" with valves, less cabinet. Cash or C.O.D., Carriage Paid, £3/7/6.

Or 12 monthly payments of ... **15/4**

#### KIT "C"

As Kit "A" complete with valves and cabinet. Cash or C.O.D., Carriage Paid, £9/4/6.

Or 12 monthly payments of ... **17/-**

Set of 4 Specified Valves ... **£2 18 6**

### PILOT ECONOMY KIT

OFFICIALLY APPROVED BY THE EDITOR  
See Page 327 last week's issue.

#### KIT "A"

Full complement of parts including ready-drilled Panel, but less Valves and Cabinet. Cash or C.O.D. Carriage Paid.

**88/-**

Or EASIWAY

**8/-**

12 monthly payments of

Set of 4 Specified Valves ... **£2 18 6**

#### KIT "B"

As Kit "A" with Valves, but less Cabinet. Cash or C.O.D., Carriage Paid, ... £7/6/6

or 12 monthly payments of **13/6**

#### KIT "C"

Complete Economy Kit, with Valves and Cabinet. Cash or C.O.D. Carriage Paid ... £8/3/6

or 12 monthly payments of **15/-**

### EVERYTHING RADIO

IMMEDIATE DELIVERY  
CASH, C.O.D. or H.P.

CARRIAGE PAID TO YOUR DOOR

#### SPECIAL BARGAIN BLUE SPOT 100U

OUR  
**19/6**  
PRICE

Speaker and Chassis. For high or low-powered sets. List Price £1/12/6.  
[Cash or C.O.D. Post Paid.]

### QUIESCENT PUSH-PULL ACCESSORIES

CASH—C.O.D. or  
EASYWAY

CELESTION Q.P.P. 19a MOVING-COIL SPEAKER with input transformer. Cash or C.O.D. Carriage Paid, £2/10/0.

Balance in 11 monthly payments of 4/7. only  
W.B. PM4 Q.P.P. MOVING-COIL SPEAKER with input transformer. Cash or C.O.D. Carriage Paid, £2/2/0.

Balance in 7 monthly payments of 5/9. only  
ROLA Q.P.P. MOVING-COIL SPEAKER with input transformer. Cash or C.O.D. Carriage Paid, £2/9/6.

Balance in 11 monthly payments of 4/6. only  
ATLAS Q.P.P. (A.C.) H.T. ELIMINATOR. Specially designed for Quiescent Push-Pull Output. Cash or C.O.D. Carriage Paid, £3/12/6.

Balance in 11 monthly payments of 6/10. only

#### GUARDIAN MILLIAMMETER

Specially designed for Q.P.P. Panel type 10/-; Pocket type 7/6. Dial diameter 2 in.



**GUARDIAN  
METER**

PETO-SCOTT (GUARANTEED)  
Q.P.P. Intervalve Transformer 9:1 .. .. 12/6  
Q.P.P. Output Choke 1:1, 2:1, 3:1 .. .. 9/-  
R.I.  
"C" Type Q.P.P. Multi-Ratio Choke D.Y.35 .. .. 12/6  
"Q" Type Q.P.P. Transformer D.Y.23 8:1 .. .. 16/6  
VARLEY  
D.P.36 Q.P.P. Input Transformer 9:1 .. .. 17/6  
D.P.38 Q.P.P. Output Transformer 3:1 and 50:1 .. .. 16/6  
Above Q.P.P. Transformer prices include Royalty 1/8.

LISSEN "SKYSCRAPER 3." Chassis model with (Lissen) S.G., Detector and Pentode valves. Cash Price, £4/9/6. Carriage Paid.

Balance in 11 monthly payments of 8/3. only

LISSEN "ZALMA." Kit "A." For building the "Melody Ranger." Complete kit less valves and cabinet. Cash Price, Carriage Paid, £5/5/0.

Balance in 11 monthly payments of 9/6. only

TELSEN ASTRALA 3. Complete Kit of Parts with Blueprint and Instructions, but less valves and cabinet. Cash Price, Carriage Paid, £1/19/6.

Balance in 7 monthly payments of 5/6. only

ATLAS ELIMINATOR. Type A.C.244. Three tapings. S.G., Detector and Power. Output: 120 volts at 20 m.A. Cash Price £2/19/6. Carriage Paid.

Balance in 11 monthly payments of 5/6. only

PETO-SCOTT CO. LTD., 77, City Road, London, E.C.1.  
Tel.: Clerkenwell 9406/7  
West End Showrooms: 62 High Holborn, London, W.C.2.  
Tel. Holborn 3948

Dear Sirs, Please send me CASH/C.O.D./H.P. ....

for which I enclose £.....d.

CASH/H.P. Deposit.

NAME .....

ADDRESS .....

A.W. 4/3/33

Send 3d. Postage for 3 PILOT RADIO ENVELOPES  
and full-size BLUEPRINTS—FREE.

**CASH, C.O.D. or EASIWAY**

Please Mention "A.W." When Corresponding with Advertisers



# The ZALMA KIT OF THE "MELODY RANGER" BATTERY MODEL

**BOXED COMPLETE  
TO THE  
LAST SCREW!**



**LISSEN STAND BEHIND IT!**

For the first time a kit of parts for a technical journal circuit, produced in its entirety by a single radio firm—for the first time a kit set "test reported" by the technical designer—for the first time a kit of parts every one of which has been made in the same factory, matched and balanced, tested and re-tested to meet the demands of the circuit. Lissen have produced this kit of parts for the "Amateur Wireless" "Melody Ranger"—with every screw, every wire, every terminal packed in an attractive carton and branded with the name Zalma—with Lissen standing behind it.

This Zalma Kit has been distributed by Lissen to the radio dealers of the country. You do not have to pay cash—you can get it on the easiest of easy terms from your own dealer.

**THE ZALMA KIT INCLUDES THE LISSEN UNIVERSAL 4 WAVE-RANGE COILS** specified by Mr. Rutherford Wilkins

The Lissen Universal 4 Wave-range Coils specified for the "Melody Ranger" CANNOT BE IMITATED OR DUPLICATED SUCCESSFULLY. It is of UTMOST IMPORTANCE that constructors should realise this and BUY ONLY A KIT OF PARTS WHICH INCLUDES THE GENUINE LISSEN COILS.

A Special Zalma Blueprint of the "A.W." "Melody Ranger" is yours for the asking—either from your dealer or by posting COUPON below.

**FREE  
ZALMA  
BLUEPRINT**

**ON EASY  
PAYMENT  
TERMS**

**KIT  
'A'**

**WITHOUT VALVES**

**£5.5**

Or 13/- deposit and 12 monthly payments of 9/-.  
KIT "A" includes every part required to build the set, except valves.

**KIT  
'B'**

**COMPLETE WITH VALVES**

**£6.15.9**

Or 15/- deposit and 12 monthly payments of 11/9.  
INCLUDING VALVES—absolutely complete kit, with Lissen Metallised S.G. Valve S.G.215, Two Lissen Valves Type L.2, and Lissen Power Valve P.220.

**ZALMA**  
TEST REPORTED  
KITS

MADE BY LISSEN LTD.,  
WORPLE RD ISLEWORTH MIDDLESEX

**COUPON**

To Lissen, Limited, "Zalma" Dept. 5, Worpole Road, Isleworth, Middlesex.  
Please send me FREE your Zalma Blueprint of the "A.W." "Melody Ranger."

Name.....

Address.....

Mention of "Amateur Wireless" to Advertisers will Ensure Prompt Attention





## BRITAIN'S LEADING RADIO WEEKLY FOR CONSTRUCTOR, LISTENER & EXPERIMENTER

EDITOR:  
**BERNARD E. JONES.**

TECHNICAL EDITOR:  
**J. H. REYNER, B.Sc. AM.I.E.E.**

RESEARCH CONSULTANT:  
**W. JAMES.**

ASSISTANT EDITOR:  
**H. CORBISHLEY.**

### NEWS & GOSSIP OF THE WEEK

#### A "MELODY RANGER" FOR THE MAINS

##### No Battery Bothers

OUR sensational "Melody Ranger," the first practical set to tune from 12 to 2,000 metres, has won an immense circle of friends. It truly has an amazing performance. The battery-driven version has been presented in "A.W." and has proved itself in thousands of readers' homes. Now we describe a "Melody Ranger" for the mains! This is an even better set than its battery brother. The mains valves give more "punch." And, of course, if you build this set you put an end to battery bothers.

#### TOWARDS THE "PLAN DE LUCERNE"

AT the time of going to press the B.B.C. delegates have not returned from the meeting at Brussels of the International Broadcasting Union where, it will be recalled, plans have been under discussion for an alteration to the present Prague Plan of wavelength distribution. So far the engineers have not

disclosed the nature and extent of the proposed changes. What has been settled is the date for the full-dress meeting of the various administrations at Lucerne. This has now been fixed for May 18. From that meeting we may expect to emerge the new Plan de Lucerne.

#### B.B.C. GOING ALL HOLLYWOOD!

IF Eric Maschwitz has his way when he takes over the directorship of the new Department for Light Entertainment in April, some of the more amiable attributes of Hollywood will soon be introduced into the vaudeville programmes. For example, Mr. Maschwitz has strong views on the necessity for "putting artistes across," as they say in Hollywood. He estimates that his time will be equally divided between the three tasks of finding new stars, in "making" them, and in supervising programmes in which they appear.

#### MAKING THEM SNAPPY!

MR. MASCHWITZ intends to have a topical variety show at least once a fortnight, in which there will be room for any visiting artistes of interest to listeners and for

#### Also in this Issue—

##### FEATURES YOU SHOULD NOT MISS

Metal Rectifiers Instead of Valves!

More About the "James Push-push (Q.P.P.) Three"

New Methods of Cutting Out Noises

New Valves for 1933

The "A.C. Mains Melody Ranger."

AND SPECIAL SECTION FOR BEGINNERS—"WIRELESS MADE EASY"

anyone who is "in the news." In this enterprise he will be ably assisted by Mr. John Macdonnell, whose work in the one-time highly popular "surprise" items will be recalled with pleasure by many readers.

#### BOAT RACE PREPARATIONS

WHAT might turn out to be the most amusing "SOS" signal every broadcast is foreshadowed as a dark possibility owing to the fitting of larger batteries to the launch *Magician*, used for the Boat Race commentary on April 1 this year.

It seems that a larger transmitting power is desirable but the extra batteries needed to provide this increased power may make the boat rather unseaworthy. Last year, owing to the weight on board, the launch could only with difficulty keep up with the crews. Other sports broadcasts which will be worth hearing are Mr. Allison's talk on March 11, in which he will deal with the F.A. semi-finals which take place on March 18, and his talk on April 22 about the Cup Final to be played on April 29. On March 4, Mr. F. T. Bidlake, President of the Road Records Association and a Vice-President of the Cyclist's Touring Club, will talk on "Speed Cycling." Mr. Bidlake is a former holder of the fifty-mile, hundred-mile, twelve-hour and twenty-four-hour tricycle records and still retains the last-named record, which he put up in 1893. On March 18, Mr. H. M. Abrahams, the old Cambridge Blue, will give an eye-witness account of the Oxford v. Cambridge sports.



#### HUNTING for NOISE!

The Paris police have declared war on street noises, and this electrical apparatus is being used in public thoroughfares to check the average noise level

**NEXT WEEK: A BATTERY-OPERATED RADIO-GRAM—By PERCY W. HARRIS**



## [NEWS &amp; GOSSIP OF THE WEEK]—Continued

## BETTER DERBY COMMENTARY

FOR the broadcast commentary on the Derby this year the B.B.C. has secured a place in the Grand Tier. This means that the commentators will be able to speak without interruption, from which they frequently suffered in their former position in the Press Stand.

## EXTENDING THE EMPIRE SERVICE

AS mentioned last week, the B.B.C. proposes to extend the Indian zone programme one hour each side of the present schedule. This takes effect on April 2. The gap between the two African zone programmes between 8 and 8.30 is also being filled, so that there will now be a continuous programme to South and West Africa from 6 to 10.30 p.m. By the way, as British Summer Time comes into force on April 9 the Empire listeners to Daventry after that date will notice an apparent error of one hour in the chimes of Big Ben. This will, for a time, be explained by the Empire announcers.

## AFRICA SPEAKS I

WE have previously mentioned in these notes the B.B.C.'s desire to exchange programmes with other parts of the Empire, as a sort of *quid pro quo* for the Daventry transmissions of the British programme to overseas listeners. The first of these new programmes will be given by the B.B.C. on March 6, when a descriptive commentary will be relayed from Table Mountain, South Africa. Lord Clarendon, who was the first chairman of the present corporation, and who is now Governor-General of South Africa, will inaugurate the broadcast.

## BIG MUSIC HALL PROGRAMME COMING

ON March 11 the B.B.C. will put over another of its star music-hall programmes. Included in the cast are many famous names, such as Laddie Cliff and Phylliss Monkman, the New Trix Sisters, Marie Lloyd, jun., George Lacy, Gus Elen, Leslie Sarony and Mussi—a new "golden-voiced" tenor who is half Scotch and half Italian.

## BOOKING THEM UP IN ADVANCE

TAKING a leaf from the book of the music-hall people the B.B.C. is now making long-term engagements with vaudeville artistes. The New Trix Sisters, for example, and Clapham and Dwyer now have engagements booked with the B.B.C. up to the end of the year. This is in the nature of a safeguard on the part of the B.B.C., which naturally wishes to ensure an adequate supply of artistes in the future.

## MUSICAL PILGRIM'S PROGRESS

KEEN amateur students of music will be glad to hear that Mr. J. D. N. Rorke has now definitely fixed up a contract with the B.B.C. for a series of twelve talks on a "Musical Pilgrim's Progress." Mr. Rorke has the Walford Davies microphone manner, charmingly intimate and highly informative.

## PLYMOUTH GOES DOWN

AS from February 25 the Plymouth relay on the 288.5-metre B.B.C. National common wavelength ceased to function and all Plymouth listeners transferred to the new and more powerful relay on 218.5 metres. Local listeners have had plenty of time to adapt their sets for the shorter wavelength, which is at present an unappropriated international channel.

## A Q.P.P. FOUR-VALVER

THOSE who are interested in the construction of a powerful yet inexpensive battery-operated four-valve radio gramophone with a Q.P.P. output stage should make a point of looking at the "Words and Music" Radiogram de Luxe, of which the construction is fully described in the March issue of *Wireless Magazine* (1s.). On test the set has picked up more than seventy-five stations—all at "mains" volume!

## AN ORGAN "O.B."

THE B.B.C. "O.B." engineers are continuing to take outside organ broadcasts from various London centres, and the popular St. Stephen's relays are continuing. Many men who may give recitals on the B.B.C.'s new organ have been heard in this way, including (last week) Francis W. Sutton, the well-known organist.

## HOW RADIO PETS HELP

MOST radio stations have their pet animals, though few can be put to such good use as the animals at a certain South African broadcasting station. There they have two cats, one named Blackie and the other Amy Johnson, and a fox terrier dog. These animals are said to chase the rats from the studio when these massive rodents appear and frighten the artistes!

## MORE FLESH AND BLOOD

FOLLOWING complaints about the programmes sent out on the Canadian zone wavelengths of the Empire service, the B.B.C. has decided to introduce more "flesh and blood" in place of the canned music and Blattnerphone tapes that have so far served as the main fare of this zone's transmissions. The reason for so much second-hand stuff in the Canadian programmes is, of course, that they are broadcast in the middle of our night, when most self-respecting artistes are in bed. Still, the B.B.C. Orchestra is to forego its beauty sleep on the night of March 22-23, when it will broadcast to Canada from 1 to 2 a.m. Quintets and other musical combinations are also being fixed for this period.

## RUGGER INTERNATIONAL BROADCASTS

THAT highly popular commentator Mr. H. B. Wakelam will be heard during the running commentaries on the Rugger internationals between England and Scotland at Murrayfield, Edinburgh, on March 18; and between England and Wales from Ravenhill Park, Belfast, on March 11.


## THE B.B.C. FILMED

MICROPHONE personalities play their part in a film entitled *King's English*, which goes on tour shortly. The film was made by British Instructional Films, Ltd., and the B.B.C. co-operated. The theme is the adventures of a news item which starts its history in the office of a news agency and travels to a newspaper office and to Broadcasting House. The news is read by people in various parts of the country in their own particular dialects, and finally we see the Chief Announcer at the microphone, reading the same item. Mr. A. Lloyd James and M. Stephan also appear in the film. If cinema audiences find no moral in *King's English* it should, at any rate, entertain them!

## NO ADVERTISING!

FOURTEEN DAYS' SUNSHINE is a new musical play now being completed by Henrik Ege and Norman Hackforth for broadcasting on March 20 (National) and March 21 (Regional)—a John Watt production. The play revolves around the people who meet on board a liner for one of those much-heralded pleasure cruises, but the critics may spare themselves their usual delightful pursuit of looking for a subtle advertisement of some renowned shipping line which will betray the B.B.C. moral turpitude. There will be no advertising. Which is a reminder that one of the best-known vaudeville artistes in the B.B.C.'s "bills" recently broadcast a skit telling of his projected attempt to swim the Channel at the widest point, and in the course of the skit he was asked how he expected to get across. "At the end of a tow line hitched on to the —," he said, naming a transatlantic liner. Within a few hours the B.B.C. received a request from a competing shipping company for a similar advertisement of one of their boats.

## HOME MOVIES BECOME TALKIES!

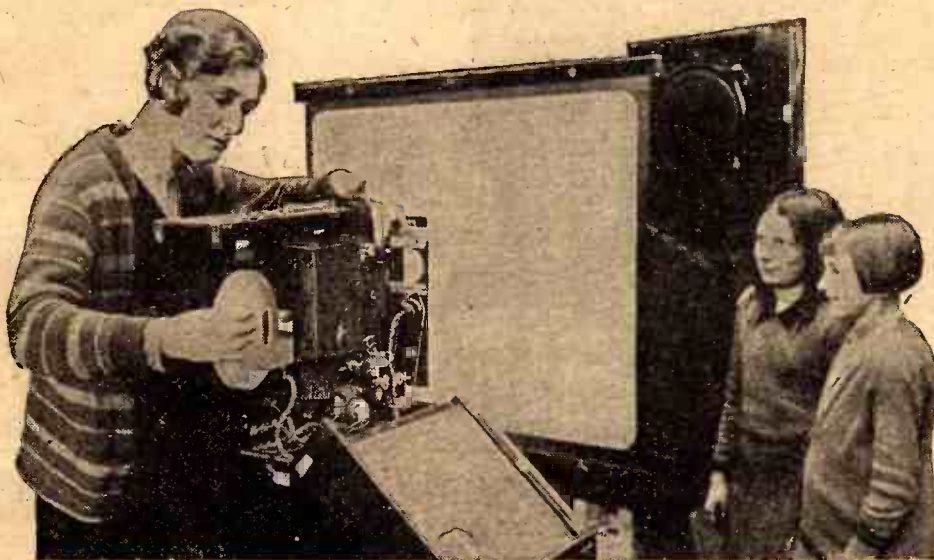

Thanks to radio-type L.F. amplification in conjunction with a photo-cell, home movies now need be no longer silent. This complete home-talkie outfit was a feature at the British Industries Fair. The sound-on-film system is used



# NEW VALVES FOR 1933

During the ensuing year there is likely to be a considerable amount of valve development and the probable trend of this is briefly reviewed below

**B**EHIND the doors of their laboratories designers are hard at work on the production of new sets for next August.

Their ideas revolve round automatic volume control, quiescent push-pull, Class B, tone compensation and other innovations which

screen-grid, pentode, or indirectly-heated valves were in their day?


So far as can be ascertained up to the moment, nothing like this is likely to appear, but there are a number of new types which may be described as developments of existing standard valves, introduced to perform functions which experience has found to be useful.

The user of battery sets will find the most interesting steps forward in the output stage. A very old friend, the original push-pull circuit, in fact, has been revived under the title of "quiescent push-pull," sometimes called "push-push." For this no new valves are necessary, an advantage lying in the use of the existing small, high-efficiency pentodes, which have the essential virtue of giving a large output—about 1 watt maximum—for a moderate input grid swing, and can thus be loaded directly from the detector though a suitable inter-valve transformer.

The second development is known as "Class B," and again, although not new, it is rendered possible by improved valve and transformer technique. Here the distinguishing feature is that the grid voltage is swung past zero into positive, and there are two variations. In the first, one may use a pair of small power valves biased to the bottom bend; in the second, valve

non-microphonicity and other important general properties.

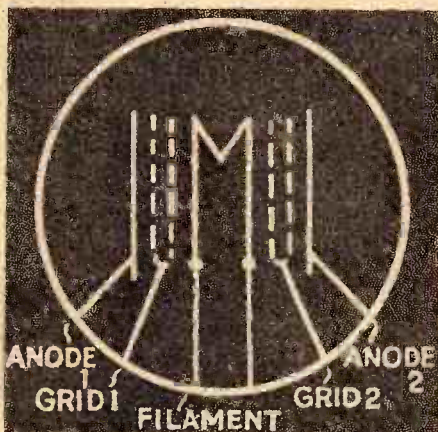In the mains classes there are many changes. We shall see a number of high-frequency pentodes with variable- $\mu$  characteristics, which bid fair to replace screen-




The Class B output battery valve, with two sets of electrodes in one bulb. This is designed to work with positive voltage on the grids

will take receivers for 1933-4 a step nearer perfection.


Improvements in coils, condensers, transformers, volume controls, switches and each and every component are carefully tested and approved as contributions towards a better product.

And dominating the scene is the valve manufacturer with the new valves.

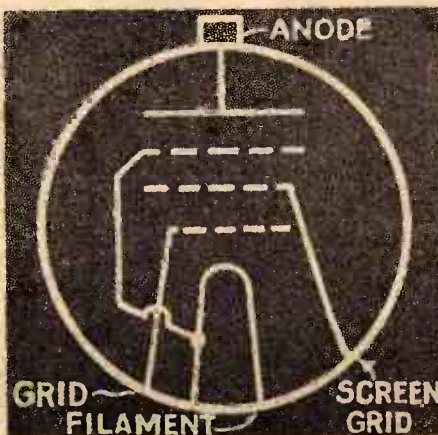What are they going to give us? Shall we see anything revolutionary, such as the



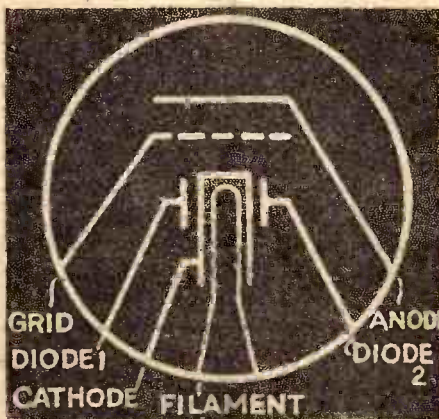
The H.F. pentode, which will look exactly the same as a screen-grid valve so far as outside appearance and connections are concerned, but has an extra internal grid



The double-diode triode, consisting of an ordinary triode with two small extra anodes placed close to the cathode and brought out to additional pins. This valve will need a new seven-pin base

makers are introducing a special double valve having two sets of electrodes in one bulb. This valve will have two grids in each anode, connected to act as one, so that with a small grid bias the anode current will be only a milliampere or two.

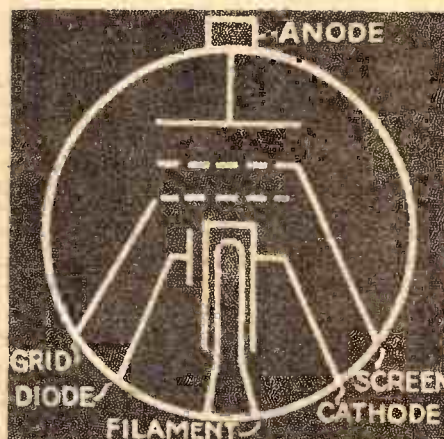
So far, there are no indications of other battery valve novelties, although one or two makers are effecting improvements in



The single-diode tetrode, which is a low-magnification screen-grid valve with an additional small anode close to the cathode

grid valves in a year or two, if we can take American progress as an example. Then the double-diode-triode makes its bow, with a rival in the single diode-tetrode. These are both primarily for use in the second detector position of superhets, although they can, of course, be applied to "straight" sets as well. Which of the two will emerge triumphant, or whether yet another novelty will displace

(Continued on next page)

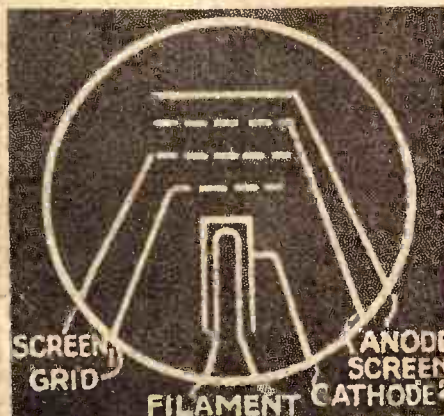

The type 59 pentode, popular in America, which can be used in three quite different ways according to the manner in which the grids are connected



# A NEW RADIO-GRAM BY PERCY W. HARRIS

First details of a new receiver to be described next week

**S**IMPLICITY, sensitivity, selectivity and quality—you can talk as much as you like about a receiver and cover up the real facts about it in a maze of words, but these four qualities, these "Big Four" are the requirements of to-day. The simplicity, too, must be genuine. It must come from real design and not merely from the omission of controls which ought to be there if the set is to be made to work properly.

Now sets, and indeed circuits, vary considerably in selectivity, and it is just as well to face facts at once. Broadly speaking and other things being equal, the selectivity of a receiver varies with the number of tuned circuits employed. Observe my remark, "other things being equal." I mention this because there are many two-circuit receivers more selective than those using three tuned circuits, and we may get trouble if we do not provide proper screening from direct pick-up coming on to the detector coil without troubling to go through the previous tuned circuit.

Yet very sharp tuning with comparatively few tuned circuits can be obtained if we combine good coil design with a very loose coupling. Loose coupling involves a certain loss of signal strength, but with the modern screen-grid valve and

particularly with proper and scientifically applied reaction, this loss can be made up in a satisfactory manner.

## Sharp Tuning and Quality

In the past the trouble with very sharp tuning in simple circuits has been the loss of quality, and up to a very few years ago this loss of quality was accepted as an inevitable accompaniment to very sharp tuning. With the introduction of band-pass tuning, however, high selectivity without loss of quality—or rather with a retention of quality sufficient for good reception—was obtained, but this led to further complications with tuning, and in the case of a simple screen-grid set it involved three tuning condensers which must either be separately tuned (which is a great nuisance) or ganged very accurately (which is expensive).

Thanks to the discoveries of Dr. James Robinson, with whom I worked on this problem extensively for some time, it has now been shown (and *after* demonstrations, theoretical proof given!) that the loss of high notes which was associated with very sharp tuning, can not only be remedied by suitable design of the low-frequency end of the receiver, but also that the additional selectivity brought about by the so-called sideband cutting

is *not* lost again when the tone is corrected.

Before Dr. Robinson announced his discoveries in this regard, it was universally held that it was useless to take a very sharply tuned circuit so as to obtain the necessary selectivity regardless of quality and then correct the quality in the audio end, because, it was said (all kinds of proofs being as usual given) that the interference which had been reduced or cut out by the high selectivity would be brought back again if the audio quality were properly corrected. You have no idea how many important people in the radio world went on record with this opinion and wish now that they had never said it!

## A "Quality" Radio-Gram

In my new radio-gramophone, which I shall describe next week in these pages, I can give you the "big four" referred to at the beginning, and by using the tone correction method in place of band-passing, I have been able to dispense with a complete tuned circuit and its associated expense. The tone correction method adopted is such that you can adjust the quality to suit your own ear or your loud-speaker; the selectivity is adjustable over a wide range, tuning has all the advantages of a one-knob control, with the precision and accuracy of separate tuning, while the overall cost is such that you will be surprised such a "quality" radio-gramophone can be produced for so low a figure. It is, of course, a radio-gramophone, and it is arranged for battery operation—the method which, at the present time at least, meets with the requirements of the great majority of listeners. That is all I can tell you at the moment. I assure you that you will not be disappointed!

## "NEW VALVES FOR 1933"

(Continued from preceding page)

both, will probably be seen in the future.

Limitations in the range of grid bias obtainable from the diode of these valves in automatic-volume-control circuits is leading to a reduction of the grid bias in variable-mu screen grids and pentodes. Now they operate at  $-1$  to  $-40$  volts, but we shall see a change, in some cases to  $-30$ , and to  $-15$  in others. Thus, a far more effective control of fading is achieved.

It is possible that we shall see rises in conductance in certain cases, but nothing very much; in fact, the trend of the last few months has been to introduce lower

conductances than the peak values reached a year ago.

Output mains valves are not likely to alter to any extent. The popular indirectly-heated pentode will be modified and rated up to 250 volts screen instead of the present 200, with a consequent theoretical increase in output.

In the D.C. classes we can expect very much the same introductions, as for A.C. operation, with the possible addition of new pentodes and Class B valves designed for maximum output at 180 volts. This will enable the D.C. set to compete effectively with the larger A.C. models, in spite of the limited voltage available from D.C. mains. It is conceivable that we may get

a valve like the American 59, which is in essence a pentode with the "earthed" grid brought out to an additional terminal. This valve can be used in three ways: firstly, with the earthed and screen grids connected to anode, as a simple triode power valve; secondly, as a pentode; and thirdly, with the three grids connected together to form one control grid, Class B becomes possible, giving an astonishing increase in output.

Here, for the moment, we must end our prophecies of what the valve makers have in store, and you will agree that even if there is nothing more to come there is enough to promise some very interesting new circuits for 1933.

**A** VERY important point, which is very rarely given any consideration in a short-wave receiver, is having the correct L/C ratio to obtain maximum efficiency.

It is usual to use a coil of approximately the correct inductance to cover as wide a wave-range as possible, and if the results are reasonably satisfactory and the stations picked up without very much difficulty, it is assumed the coil is correct. When down below 50 metres, the lower the capacity that is used—that is, the smaller the condenser—and the larger the coil, the better should be the amplification. For example, using a .00025-microfarad tuning condenser with a 180-degree dial and a six-turn plug-in coil, a 50-metre station would come in at approximately 120 degrees, with perhaps fair strength.

If the inductance of the coil was increased and a 9-turn coil used, the condenser would have to be of lower capacity, and the dial reading would most probably be in the region of 30 or 40 degrees. You would find that this arrangement where C (that is, the capacity) is fairly low and L (that is, the inductance) is as high as possible, the ratio of L/C is more correct and the efficiency is greatly increased. So remember, in future, to use the largest coil you

## SHORT-WAVE NOTES

By "SHORT-WAVER"

possibly can and always try to tune your station in at the bottom end of the tuning scale.

Some very interesting experiments have been carried out on the common or garden "earth" and some surprising results were obtained. When an earth consisting of a copper plate was buried in normal dry soil, the efficiency increased over 1,000 per cent. when the ground was liberally watered. With a short-wave set the question of the earth connection is of vital importance, and it certainly pays to make quite sure that your earth is of as low resistance as possible.

During the past week the English amateurs have been very lively, and during Sunday morning twenty or thirty of them were "on the air," coming in on the loud-speaker. Heterodyning was very bad, but, even so, it was very amusing listening to some of these

enthusiasts putting over a really powerful signal when using only a few watts. I strongly advise you to tune in next Sunday morning about 11 or 12, on the 40-metre band and hear a few for yourself; but, please, don't oscillate—there is enough interference already.

I cannot possibly provide a wiring plan for the simple single valve circuits which I give, but I would be only too glad to give any help, should it be required, or should there be any queries regarding values, or components, etc.


The conditions during the last week have not been at all good. W3XAL is definitely deteriorating; but, what is worse, the schedule is not at all reliable. On one or two afternoons, instead of beginning at 1 o'clock, it has been a little after 3 p.m. before the first programme was sent out.

I understand that experimental broadcasts on Sundays have now been stopped, so if you wish to hear any Americans on Sunday afternoons you must rely on the 13.92-metre W8XK until about 3 o'clock and the 19-metre relay from 3 p.m. onwards. As the days are getting very much longer, the low wavelength stations come in much later in the day, and stations under 20 metres can be picked up as late as 7 o'clock in the evening.


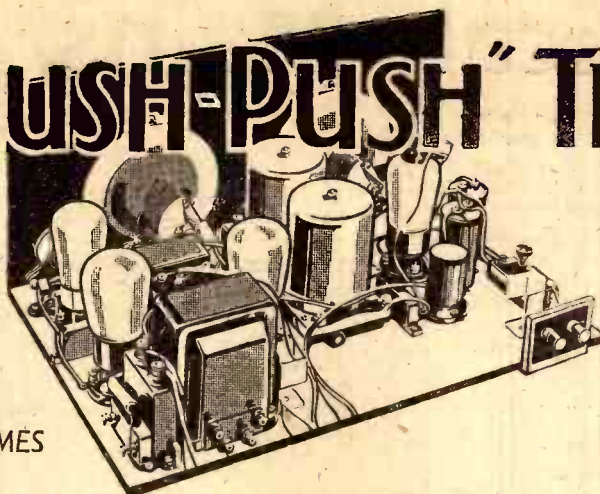
# USING The JAMES "PUSH-PUSH" THREE

Here are the operating instructions for the Quiescent Push-pull Set of which constructional details were given in last week's issue



BY  
W. JAMES

**EXPERIENCE** shows that the most satisfactory and economical set for all-round use is one having a high-frequency stage, a detector and a power stage.

With this type of set the selectivity is usually good enough to allow the worthwhile stations to be received with the minimum of interference. But those who must use batteries have always, until now, had to put up with rather poor volume.

With a Q.P.P. output stage the performance is entirely changed. Much more volume is obtained and this seems to add life to the set.

## Good Quality

The quality, too, seems to be much better than from standard sets, chiefly because a more satisfying output is obtained. Added to these advantages of the Q.P.P. system is the further one that the standing (no signal) current is very small and the average current during an evening's work is less than the average current of a single valve used in the ordinary way.

You do not get everything for nothing, however, as more volts must be applied to

the power stage. There is no difficulty about this, however, as with a sensitive detector and coupling transformer combination the necessary magnification is easily obtained.

This receiver may, therefore, be said to put up the same performance as other sets having a single high-frequency stage as regards both selectivity and sensitivity. It surpasses other sets in the volume and the quality of the output.

In this respect it can be said to give practically as much sound output as the usual mains set having a pentode output stage. There is, in fact, a remarkable difference in the results between a set as described and another having just the ordinary power stage.

The difference really is much greater than you might think possible and when it is remembered that the average current from the high-tension battery is less than

the normal for one power valve you will realise how worth while the Q.P.P. system is.

A variable-mu screen-grid valve must be fitted in the first stage of the set. The bias for this valve is obtained through the volume-control potentiometer connected to the grid-bias battery and the

wander plug joined to the flex from the potentiometer should be plugged into the negative end of the grid battery. There is a switch in the circuit and when the control is turned off the potentiometer circuit is broken.

## Proper Adjustment

I like a high-frequency stage with a variable-mu screen-grid valve as the amount of the amplification can be controlled so easily. A further point is that the anode current is reduced as the magnification is brought down, with the result that the minimum of high-tension current is taken when listening to strong stations.

Associated with this part of the circuit is a pre-set condenser and reaction. There is great scope here for those little adjustments which enable one to obtain exceptional results. The effective selectivity can be improved, for example, by reducing the capacity of the pre-set condenser, by lowering the amplification provided by the valve by turning back the volume control and by using reaction.

Good separation of stations can easily be obtained by careful tuning and I always think that this part of a circuit is very interesting because of the fine adjustments that are possible.


It should be remembered that if the reaction is adjusted to the point where the tuned-grid circuit is practically oscillating, increasing the volume control will have the effect of taking the circuit a little further away from the oscillating point.

## Suitable Valves

If, on the other hand, the volume control is turned back a little, the tendency will be for the tuned-grid circuit to go nearer the oscillating point. This is because the impedance of the screen-grid valve increases when the volume control is turned back and is reduced when the control is turned up.

A good valve for the detector stage is one of the HL series, having an impedance of the order of 20,000 ohms. It is advisable to give the anode of this valve all the volts available and it was partly for this reason that the anode de-coupling resistance was

(Continued on page 401)

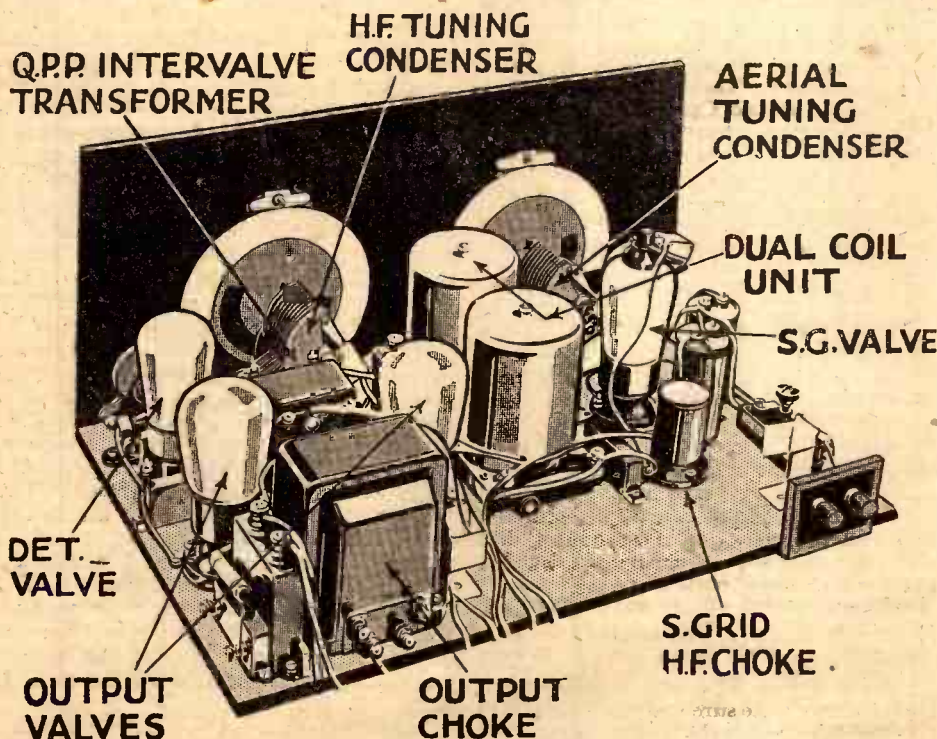

This lettered pictorial diagram of the "James Push-push (Q.P.P.) Three" will make the explanation given in the text easily understandable

**NEXT WEEK: A BATTERY-OPERATED RADIO-GRAM BY PERCY W. HARRIS**



# Practical Mains Working— for Beginners (Part 2)

**L**AST week we saw why you cannot use "raw" alternating current to operate the electric supplies in your set and how, simply by changing the valve holders and making one or two connections in the set, we can take our supply of low-tension current from the mains, provided, of course, we use a special form of valve.

I have already mentioned that these indirectly-heated valves are much more efficient and the question, therefore, arises as to which types we should use in a simple set consisting of a detector and two low-frequency stages.

We cannot do better than to use the mains equivalent of the "H.L." type of valve for the first two valves. For the output a great deal will depend upon our high-tension supply, for output valves can be exceedingly "greedy."

No particular pains are taken to make mains output valves especially economical, because these valves are invariably operated from mains high-tension units. We must, however, take into account the maximum efficient output from our mains high-tension unit when choosing our output valve.

While it is extremely unusual, there is no theoretical reason why the high-tension supply of a mains valve should not be provided by dry batteries, but of course this is a very extravagant way of doing it, in view of the high consumption of mains valves.

## Choosing Your Valves

Let us look over the valve makers' lists and see what we can find. The detector valve and the first low-frequency valve together will take about five milliamperes, provided the low-frequency valve is properly biased (I am assuming for this the maximum plate voltage is about 150). For the output valve you can choose one of the mains power or mains super-power types. The high-tension consumption of these valves varies considerably among different makes, but a typical mains power valve I have in mind, correctly biased, takes about 15 or 16 milliamperes, and in the same make the super-power valve for mains working at the same voltage takes about twice that.


We come now to a very interesting point. Designers of A.C. mains sets for home construction invariably make them complete with mains-driven supply for both low tension and high tension. Many people who have been running battery sets and desire to go in for mains operation scrap their existing battery set and with it a perfectly efficient high-tension mains unit, so as to build the new receiver complete from tip to toe. I want to emphasise here there is no need whatever, when you want to go in for mains operation in the most economical way, for you to scrap a good high-tension mains unit.

There are many small high-tension units in use designed to give 20 to 30 milliamperes at 120 volts. If you choose for your receiver two "H.L." mains-type indirectly heated valves for detector and first low-frequency stage and an economical mains power valve (not mains super-power

valve) for your output, the total consumption at 120 volts will not exceed that which your mains unit will give.

It is unusual in these days to design a mains set with a detector and two low-frequency valves, the most frequently adopted plan being to use a high-frequency stage, a detector, and one low-frequency stage. When you use a high-frequency stage you get an additional tuned circuit, which adds to the selectivity.

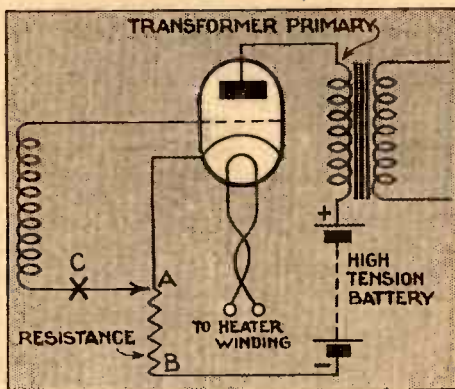If, however, you use two tuned circuits prior to the detector and follow this by two low-frequency stages, a very high selectivity is obtainable, as I have shown in the "Mascot" receiver, which is quite capable of being turned into a mains-driven receiver along the lines we are now discussing. Indeed, I have worked one so converted for a long time in my laboratory.



Grid bias is applied to a mains valve by inserting a resistance between the cathode and high-tension negative, part of the high-tension voltage being used for the grid-bias voltage in this way

I also published in *Wireless Magazine* last year a mains-driven radio gramophone using a detector and two low-frequency stages, the detector being preceded by a band-pass arrangement and two tuned circuits.

## Good De-coupling Needed

There is another very important point in all such conversion schemes as that we are discussing. Owing to the very much higher efficiency of the mains valves, there is a great tendency for unwanted feed-back to occur and it is absolutely essential in such conversions not only to use adequate detector decoupling (that already described for the "Build As You Learn" detector and two low-frequency set is adequate), but also a choke and condenser output, which I did not include in the battery set.

You will now be asking about grid bias. Mains sets do not include grid-bias batteries, because everyone wants to get everything from the mains. There is, however, no reason why one should not operate a mains set with a grid-bias battery, and actually it is the cheapest and most efficient way to do it.

This statement may come as a surprise to many, but you will see my point if you

consider the facts for a moment. A 9-volt grid-bias battery, which is adequate for such a conversion set as we have described, costs but a few pence, and as the current drained from it is infinitesimally small, it will last for the best part of a year.

"Automatic" grid bias, which I shall describe in detail next week, requires a wire-wound resistance for each valve to which grid bias must be applied, together with at least a 1-microfarad condenser.

To give the very best results and avoid distortion grid-circuit decoupling must be used, and this calls for one more resistance and one more condenser in each stage. This grid decoupling is often omitted, but without it, theoretically at least, results as good as that obtainable with an 8-volt or 9-volt grid-bias battery are unobtainable. It will thus be seen that the total cost of fitting automatic grid bias is bound to be appreciably higher than that of a grid-bias battery.

## Remember Ohm's Law!

Before we come to next week's lesson I want you to think over the fundamental principle upon which automatic grid bias is based. You know that according to Ohm's Law voltage, current, and resistance are related to one another. To send a certain current through a resistance requires a certain voltage. If we insert a resistance in the plate circuit of a valve, there is what we call a "voltage drop," through it.

Take for example a valve circuit consisting of the valve itself, the primary of a transformer, a high-tension battery, and a resistance, this last being connected to the cathode or emitting surface of an indirectly-heated mains valve.

So far as the grid circuit is concerned, we will assume that there are voltages being applied to the grid, and changes of voltage, therefore, occur across the transformer and are passed on to the next valve. Notice that every bit of plate current of this valve passes through not only the transformer, but also this special resistance joined to the cathode. I want you to note particularly the two points marked A and B.

Now if the bottom end of the grid circuit is joined to A or directly to the cathode, the grid bias will be just nil. If we insert a grid-bias battery at the point marked C we can, of course, make any grid bias we like.


As the whole of the plate current of the valve is passing through the resistance R, there must be a voltage drop across this resistance.

The path of the current through the valve with this resistance is such that A is the positive end and B the negative end, therefore B will be more negative than A. This being so, let us transfer the bottom end of the grid circuit from A or the cathode to B.

What will be the result? Think it out and you will see that the grid now becomes negatively biased, the amount of negative bias being dependent upon the strength of the plate current. PERCY W. HARRIS.



**ALL MAINS BY ALL MEANS  
—BUT BE SURE OF THE VALVES**

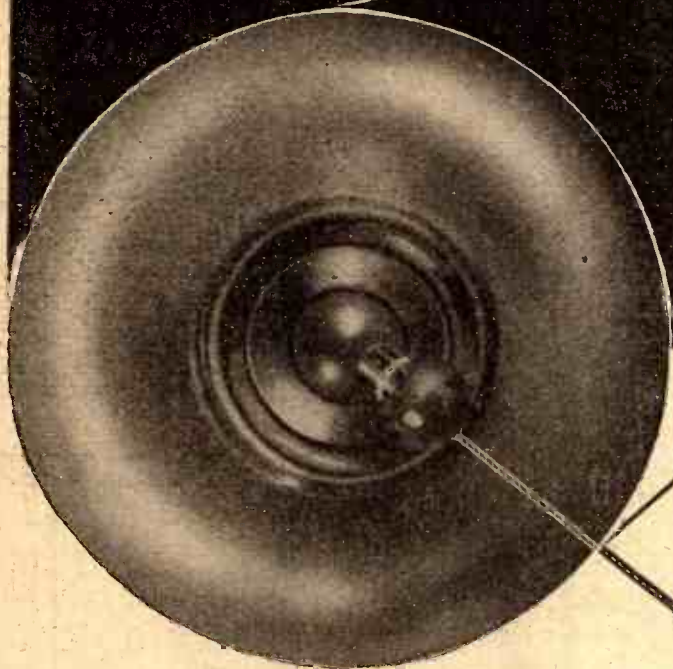

**DW2**  
**DW3**

The switch means no more than an introduction to the valves. It's no use flogging it. Forget about the switch. It is the valves which matter. They must be Mullard if the switch is to mean more to you than simply "mains."

Change to Mullard Mains Valves. Switch over from ordinary reception to Mullard reception. Be content only with better radio—with the best radio.

Two Mullard rectifiers, the D.W.2. and D.W.3. Two rectifiers whose reliability and performance show how advanced Mullard valve production has become. The D.W.2. for outputs up to 60 mA at 250 volts, and the D.W.3. for outputs up to 120 mA at 350 volts.

Switch over to Mullard Mains Valves—and hear the difference.

Mullard Valves specified for the A.C. version of the "Melody Ranger" described in this issue are: 1-VM 4V. 1-904V. 1-354V. 1-104V. 1-D.W.2 Rectifier.

MADE IN ENGLAND

ASK T.S.D. Whenever you want advice about your set or about your valves—ask T.S.D.—Mullard Technical Service Department—always at your service. You're under no obligation whatsoever. We help ourselves by helping you. When writing, whether your problem is big or small, give every detail, and address your envelope to—T.S.D., Ref. B.G.F., The Mullard Wireless Service Co., Ltd., Mullard House, Charing Cross Road, London, W.C.2.

**Mullard**  
**THE • MASTER • VALVE**

The Mullard Wireless Service Co., Ltd., Mullard House, Charing Cross Road, London; W.C.2

You will Help Yourself and Help Us by Mentioning "A.W." to Advertisers

Arks






# Get Original Tone

Tone is radio's severest Test. When everything else about your set has lost its novelty, tone remains, day after day, year in, year out—doesn't it pay you over and over again to be right at the start? Get the fullest benefit of Columbia's latest radio development—ORIGINAL Tone—clear, brilliant, almost startling in its actuality.

Attractively presented in polished walnut, the four-valve mains model shown here has met with an amazing popularity. Test its superiority in the actual reception conditions of your own home. It will tell its own story! The coupon will bring you fullest particulars.

USE THE COLUMBIA DEALER SERVICE.  
Expert advice on local radio conditions and  
service after sales

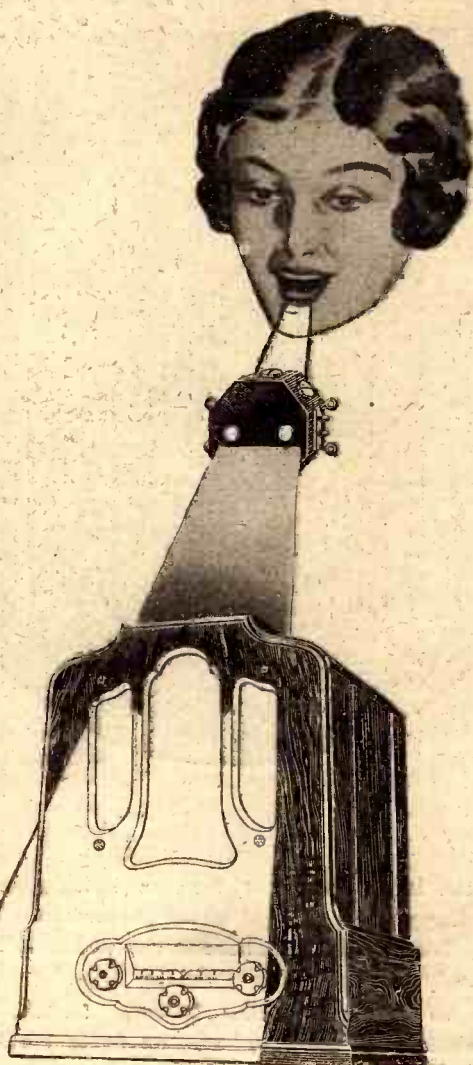All-Electric Four  
**16** gns. cash (A.C. or D.C.)  
or delivered on first payment of  
**£1 13s.**



## Columbia ALL-ELECTRIC FOUR



### CUT OUT AND POST TO-DAY!

Please send me fullest particulars of Columbia Model 355. (Write in block capitals).

NAME .....

ADDRESS .....

A.W. 4/2/33

Cut this out and post in an unsealed envelope bearing 1d. stamp to 5—Columbia, 98, Clerkenwell Road, E.C.1.

Advertisers Appreciate Mention of "A.W." with Your Order



# On Your Wavelength!

## SIGHT AND SOUND

**I** SUPPOSE nine people out of ten would say, off hand, that the eye is more sensitive in action than the ear, though in point of fact, the truth lies the other way round. It is not easy to make a direct comparison, because the two organs react to very different impulses, but it has been calculated that the average ear will respond to an energy-impact equal to that of the light from a candle eight miles away—which is more than twice the distance at which the same candle could be seen by the naked eye through perfectly transparent air. Yet, in spite of having so sensitive a "threshold," the ear is noticeably tolerant of certain forms of distortion, which is a lucky dispensation of providence for set-designers, who have quite enough problems to contend with as things are.

## FILLING IN THE GAPS

**F**OR instance, the ear will often fill in notes that do not really exist, particularly at the upper and lower ends of the scale—whereby some loud-speakers get credited with more good marks than they actually deserve. On the other hand, the range of human hearing is known to be definitely inferior to that of certain animals who can hear sounds both above and below our own limits of audibility. This is probably part of the price we have to pay for the privilege of speech, which makes so keen a demand upon the ear for interpretations that it completely monopolises some of the aural nerves, and so in course of time has put them out of action for any wider purpose.

## THE FACTOR OF SAFETY

**I**N photography the lens of a camera has a diaphragm which is adjusted according to the value of the light, and the control knobs at the broadcasting studio are handled with the same object applied to sound. In both cases the pick-up range is adjusted to cope with the largest sound or light, and the weak tones have to take care of themselves. The incorrect rendering of extreme volumes is not really a distortion, however, so long as the different values are reproduced in correct relation to one another. A good factor of safety in the receiver, in the shape of plenty of H.T., correct grid bias, good transformers and power valves, will take care of this.

## REFLEX SETS

**I**N the early days of broadcasting the horrible sounds that emanated from some loud-speakers gave the whole game a bad name, and the cause of the distortions was invariably a reflex circuit. Reflex sets have been (rightly) out of popularity for some years and are probably unknown to very young wireless

constructors. The most popular form of reflex circuit was the H.F.-detector-r.L.F. type, in which the first valve was used for both H.F. and L.F. amplification. In the light of present practice, the use of such circuits for loud-speaker reproduction seems absurd. But, on the other hand, the small loud-speakers available then would probably not have done justice to anything better.

## LIKE THE POOR—

**T**HERE is one type of distortion that will always be with us, and, indeed, is highly desirable. However good loud-speakers and amplifiers become we shall always have amplitude distortion. Consider the terrific differences in the volumes of steam syrens, gun fire, and whispers; these differences might be expressed in values of hundreds of decibels. But in gramophone disc recording the volume range is about 25 decibels from the weakest to the loudest recorded sounds. Loud sounds are limited by the permissible width of the cut on the record and weak sounds are masked by needle scratch. Volume range is similarly reduced in broadcasting, but not quite to such a small range. In the reproduction of sounds in small rooms the reduction of volume range is essential, but in public address and cinema reproduction the extension of the present range is being sought.

## DIRECTIONAL AERIALS

**T**HE Empire broadcast transmitter uses different aerials for sending to various zones, and this recalls the fact that directional aerials were used by the B.B.C. in early days—for reception. The first American broadcast relay was accomplished with the aid of Beveridge aerials, 500 yards or so long, pointing away from the direction of the American station, KDKA. The first successful broadcast was made with the receiver installed at Biggin Hill aerodrome,

Kent, and the aerial stretched from a hut across a main road to a field, where it was continued in a straight line at a height of only about ten feet from the ground. One stormy night the aerial fell down across wires supplying lighting to the aerodrome, making physical and verbal sparks fly.

Years before this, however, the Beveridge aerial had been used by an amateur in this country for the first reception of messages from American amateur transmitting stations. An American amateur came over specially to do the job, the "hams" over there believing that our men hadn't the receivers or necessary knowledge. Nevertheless, many messages were picked up by British amateurs with much less elaborate receiving sets or aerials. This happened only about twelve years ago! And now almost everyone has tuned in to telephony from America, while the morse messages of American amateur transmitters can be picked up by anyone with a short-wave receiver and a knowledge of the code.

## NO TROUBLE REALLY

**S**OME readers tell me that they find H.T. accumulators rather a nuisance but I am inclined to think that those who do so have themselves to blame, as a rule. If you want to avoid trouble with an accumulator H.T.B., make a contract with a reliable charging station to call for it, say, once every six weeks, and stipulate that their attentions shall include topping up the cells with distilled water and greasing the connections. If you make such an arrangement, your battery never becomes more than half run down and it is always kept in excellent order. It is no more trouble than a dry battery, you don't suffer from falling voltage, and you are never troubled by noisiness. Don't forget too, that when your positives begin to show signs of wearing out you can have the battery replated usually for less than half the cost of a new one. Treat your accumulator H.T.B. well and it won't give you any bother.

## PERSONALITIES IN THE WEEK'S PROGRAMMES





## On Your Wavelength! (continued)

### SHATTERING GLASSES

**A** GOOD many correspondents, I see, have been rather puzzled over the breaking of ornaments, glass lampshades, and so on when their loud-speakers were in action. The reason why this happens is simply that the fundamental frequency of the object in question is emitted strongly by the loud-speaker. The ornament, or whatever it may be, responds, and if this particular note is a long one the vibrations build up to such magnitude that it flies to pieces. Caruso was very fond of giving one demonstration of the power and the exact pitch of his voice. He would pick up a wineglass and flip it with his finger nail to ascertain its resonant frequency. Then he would sing the note into the glass, beginning very softly and letting the sound grow louder and louder. Presently the glass flew into fragments.

### A PUZZLING CASE

**T**HOUGH the actual shattering of treasured possessions by the loud-speaker is rare, one often does come across something in a room with a strong tendency to vibrate whenever its resonant frequency occurs. Some people hardly notice the effect of the "zizz" so produced, but to most of us it is quite distressing. I remember, some years ago, suffering from a resonance of this kind which took days to track down. I had installed the instrument with great pride, but its performances were ruined by a horrible response which seemed to come from one corner of the room. Everything that could possibly be responsible in or near that corner was removed at one time or another, but still the nuisance continued. Eventually I did track down the cause. It was a loose glass in a picture frame, and the noise was not coming from that corner at all in reality; it seemed to do so because of an echo effect.

### ORDERS ARE ORDERS

**T**HE Japanese, I observe with some interest, have been ordered by their Government to refrain from listening to any broadcast transmissions save those which emanate from their home stations. One of these, by the way, has the call-sign JOAK. And did you know that there was a Russian station RED? The purpose of this amazing decree is apparently to protect the Japanese from being contaminated by propaganda from outside, but I am rather wondering how the Government proposes to enforce it. Japanese wireless men are probably just as enthusiastic DX-ers on both the waves and the wavelets as we are, and I fear that it may be a case of that is an order—that was. Doubtless, though, there are conscientious citizens who will obey it to the full. I only hope that they will not mark their disapproval of the goings on of those who do listen to foreign stations in the traditional Japanese manner. Over there, I understand, the strongest hint you

can give a fellow that his conduct is not pleasing to you is to go and commit harakiri on his doorstep!

### USING VARIABLE-MU'S

**A** GOOD many people, I find, don't know how to get the best out of the wonderful variable-mu valves responsible for the high-frequency amplification in their receiving sets. One of this valve's queer little ways is that the more you increase the negative grid bias, the smaller is its response to an unwanted signal upon a wavelength close to that of the wanted station. Suppose, now, that you are trying to separate the giant Breslau from its equally powerful next-door neighbour the Poste Parisien. Here is the proper way to set about the business. With the volume control at about the midway position and reaction almost, if not quite, at zero, tune in Breslau as nearly as you can. There is almost certain to be distinct interference from the French station. Now turn back the volume control (which has the effect of increasing the negative grid bias) until the Poste Parisien disappears. By this time, Breslau will have become in all probability nothing better than a small faint bleat. This is where reaction comes in. Work up Breslau's strength by careful use of the reaction knob, turn the volume control if necessary still further towards the minimum position, and you will be able to bring him in without any interference at all from Paris. The degree of selectivity obtainable by working the volume control against the reaction control is astonishing with variable-mu's.

### "JUMPERSPHERICS"

**I** HAVE made in my time most of my own wireless bits and pieces, not even excluding low-frequency transformers and a loud-speaker. But until the other day I don't think that I had ever manufactured my own atmospherics. Now I can claim to have done that; and quite a useful crop of tearings and crashings, too. I had been at work for some time in the lab., and after a very chilly start the day warmed up considerably—so considerably that the pullover I was

wearing was clearly no longer required. I peeled it off, standing, as I did so, quite close to the down lead of an indoor aerial whilst a biggish set was at work. You just ought to have heard the atmospherics that resulted! You know how a woolly crackles when you pull it off over your head; if you do so in the dark you can often see quite a display of sparks. Each of these little discharges produced its own "jumperspheric," and the response from the loud-speaker was truly magnificent.

### THE PENDULUM SWINGS

**T**HE coming of both simple Q.P.P. and Class B looks like bringing about a very peculiar position in the world of wireless. For the past year or two mains sets have had it all their own way in the matters of quality and volume, and the battery set has had to follow a good long way behind. The ambition of every battery-set user has been to possess a mains receiver. But it now seems to me that the battery set may actually be a better performer than the mains set, chiefly on account of the dead silent background. Running costs will, of course, remain higher for battery sets than for mains sets; but, owing to the small amount of H.T. current consumed by the former under the new conditions, they will not be very serious. A strong point about the battery set is that you can use it anywhere. Further, there is always the problem of the freak voltages and the freak frequencies in A.C. that are still found in so many parts of this country of ours. And as for D.C.—well, this is sometimes so rough that it is an exceedingly difficult matter to obtain even respectable reproduction. I foresee a huge business this year in both constructors' and ready-made battery sets.

### TREATING 'EM ROUGH

**I**T is amazing to find what the modern set will stand in the way of rough treatment. It doesn't receive it purposely, but accidents will happen even in the best regulated families. The other day my plan for returning a set that had been lent to me for test purposes came sadly unstuck. I rather pride myself on the care that I take about returning such apparatus. Having packed it up snugly, I drove it down to the station, selected the trustiest of porters, and saw it safely installed in the carriage. Arrived in London, I hailed a porter, asking him to put the set into a taxi and telling him to handle it with the utmost care. He picked it up as if it had been made of the finest glass and walked delicately towards the waiting taxi. Then his feet, somehow, got tangled up, and next instant the set had dropped flat on its face with the most resounding of crashes on the cold, hard platform. Almost in tears, I conveyed it to its makers and watched its unpacking. Except for one small scratch on the cabinet, it was in perfect order!


THERMION.

Have you tried fitting one of the new variable resistances or potentiometers combined with a cut-out switch? The cut-out switch can be used as shown to



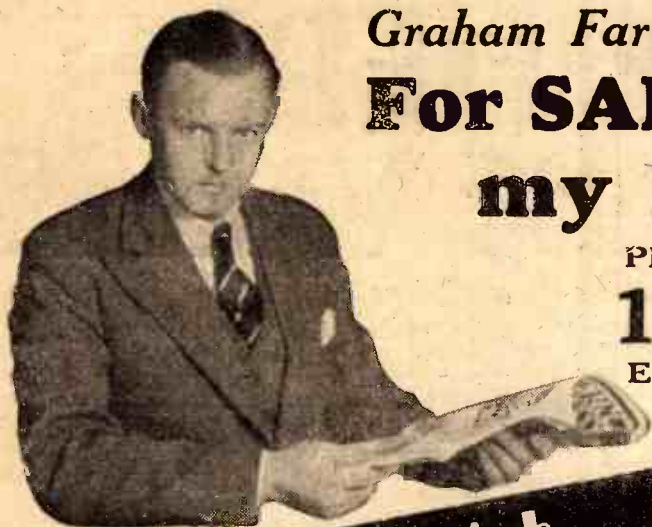disconnect a tone control from the circuit. Or, in the case of variable-mu valves, it is handy to disconnect the potentiometer which supplies the variable-mu bias





Graham Farish says:

## For SAFETY'S SAKE fit my NEW OHMITES

PRICE  
**1/6**  
EACH

Because they will carry far more than their stated load. They readily handle those strong 'surges' from the mains and not being wire-wound they are not liable to corrosion, neither can they create hum. My NEW OHMITES put reliability in a set where it is most needed. For your peace of mind fit my NEW OHMITES and forget them.


SAFE MAXIMUM CURRENT CARRYING CAPACITY OF "OHMITES."

100° F. Temperature rise.			
Ohms	Milliamps	Ohms	Milliamps
100,000	3.5	10,000	12
80,000	4.24	5,000	20.25
60,000	5	4,000	24
50,000	5.5	3,000	29
40,000	6	2,000	35
30,000	6.75	1,000	40
20,000	8	Other values pro rata.	

Heavy Duty type approximately double the above ratings.  
Price 2/3

Every wireless enthusiast should have a copy of the Graham Farish "Component Book" and also a free copy of the "Instant Station Tuning Chart." Send a Postcard request for these by return.

Graham Farish  
**OHMITE**  
RESISTANCES

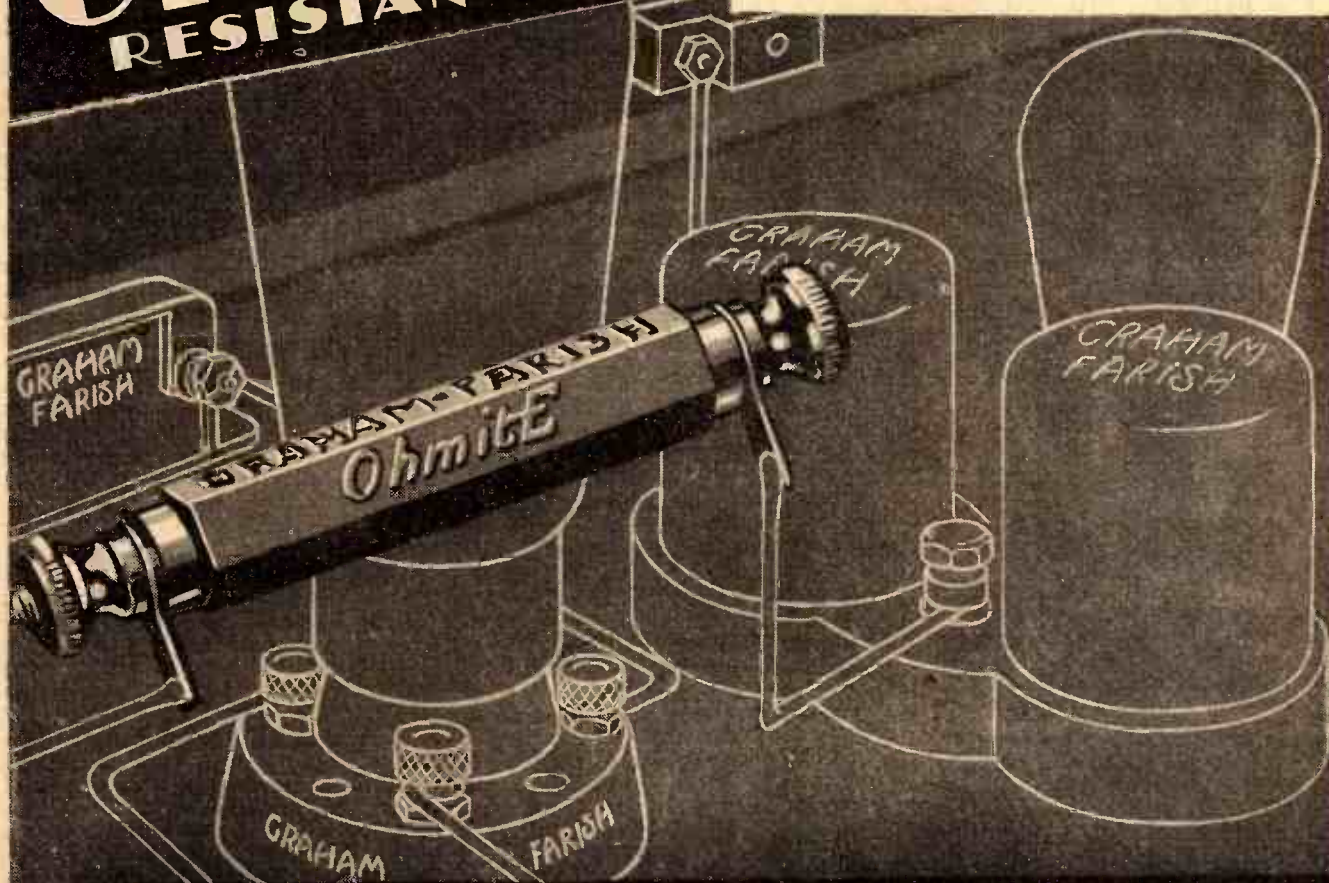

# GRAHAM FARISH COMPONENTS

MAISON HILL, BROMLEY, KENT. EXPORT OFFICE: 11/12, FENCHURCH STREET, E.C.3.

Advertisers Appreciate Mention of "A.W." with Your Order



# METAL RECTIFIERS INSTEAD OF VALVES


*A new type of detector based upon the principles of the metal rectifier is now available which under certain*

*conditions, can replace the valve. In this article J. H. Reyner describes the device and explains its uses.*

A COMPONENT which may have a considerable influence on the design of wireless sets next season is just making its appearance and will shortly be available to the public. This is the metal detector which, as its name implies, is a metal rectifier specially suitable for high-frequency currents.

The ordinary metal rectifier is now a very familiar product in A.C. sets. It consists, as most readers know, of a series of discs made of copper. One side of the disc is treated in a furnace so that it becomes coated with a film of oxide, and it is then found that if two such discs are placed in contact the arrangement will only conduct current in one direction. If the voltage is reversed the amount of current which flows is less than one-thousandth of the original current.

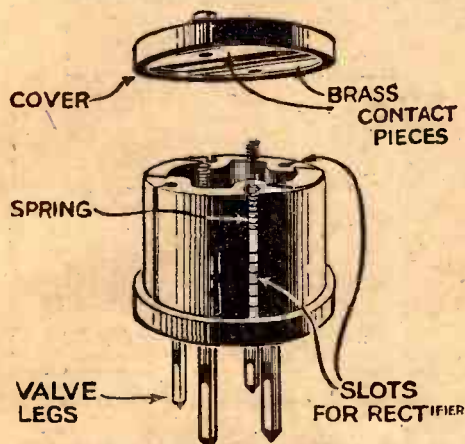The ordinary rectifier is built up by using



This sketch shows the construction of the new rectifier. The rectifying units are contained in slotted holes and are held in contact by means of a light spring

a series of discs of this sort mounted up in a pile. In order to preserve an intimate contact between one disc and the next, small washers of lead are included between the individual discs and the whole is clamped up under pressure, forming a very solid and robust unit.

Apart from the main use of this type of rectifier small units have been used for some time for instruments. These rectifiers enable an ordinary D.C. moving-coil meter to be used on alternating current measurements and tests have shown that the rectification is satisfactory up to frequencies of 5,000 and 6,000 cycles per second. Beyond this point, however, the efficiency begins to fall off somewhat rapidly and any attempt to use the

ordinary rectifier at radio frequencies is unsuccessful.

The reason for this is that the capacity of the rectifier, as a whole, is too large, and we have in effect a small capacity shunted across the terminals. Now the rectifier has a certain resistance, several hundred ohms in actual fact, and at high frequencies the impedance of the self-capacity is considerably less than the actual resistance of the rectifier.

The result is that the currents prefer to go through the self-capacity and therefore do not pass through the rectifier at all. Consequently there is no D.C. voltage produced and the rectifier simply does not function.


## The New Rectifier

Following this line of research the Westinghouse Laboratories evolved a form of metal rectifier in which the discs were considerably reduced in size. Instead of a diameter of  $\frac{3}{4}$  inch or more, these discs are now made only  $\frac{1}{8}$  inch diameter. The thickness of the lead spacers between the discs is also increased which again reduces the capacity between the discs and by mounting the discs in this way it is possible to obtain a rectifier which operates satisfactorily on frequencies of a million a second and more. This, of course, is not the whole story, but it indicates the two principal points of difference between the "Westector," as it is called, and the ordinary metal rectifier.

This form of rectifier can be made up either as an ordinary single-wave rectifier or as a double-wave or bridge rectifier. In the former case the rectifier is very similar to the ordinary crystal detector. Its use is the same in that it is connected in series with the telephones or a suitable resistance or transformer, across the tuned circuit. It then operates in much the same way, but it has the important advantage over the crystal that it is constant in its operation and is not thrown out of adjustment by vibration or similar happenings. There is, in fact, no adjustment for the best point. It is always working at full efficiency.

It is just as easy, however, to arrange double-wave rectification with this device. A suitable circuit is shown by the diagram in which a centre-tapped circuit is used. Alternate half-waves are rectified by the top and bottom rectifiers in turn, and this system has important advantages. One of the big difficulties with the ordinary detector, whether it be metal or valve, is that of disposing of the radio-frequency currents after they have been rectified.

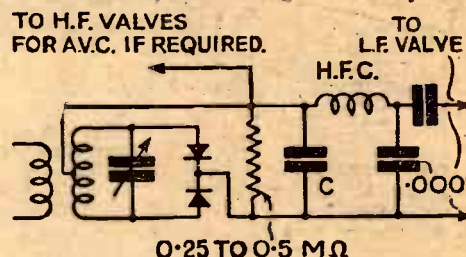At the rectifier the process of detection separates out the low-frequency modulation from the high-frequency carrier, and the radio-frequency currents are no longer required. We must provide an easy path for these currents, as otherwise they will



Typical metal detector circuit: both halves of the wave are used

leak through into the low-frequency stages and cause distortion or tendency to self-oscillation.

## Unwanted H.F.

Now this unwanted high-frequency current is rather similar to the ripple which is obtained in a mains eliminator. Following the rectifier we place a reservoir condenser, and the pulses of rectified alternating current which come through the rectifier charge up this condenser, which thus acquires a more or less steady voltage with only a small ripple on the top. Without the reservoir condenser the ripple would be much larger.

We can use exactly the same procedure here at radio frequencies. We use a small reservoir condenser following the rectifier, as shown at c in the diagram. This absorbs the high-frequency ripple to a very large extent and in many cases no further filtering is necessary. Even if a little high-frequency is still left it is only necessary to use a small and inexpensive high-frequency choke with a .0001 by-pass condenser to eliminate the high-frequency current almost entirely.

There are numerous other applications of this detector. One of the most important is that it may be used to provide voltage for automatic volume control quite easily, its connection in this case being somewhat similar to that of the ordinary diode valve, but it is, of course, considerably cheaper, not only in first cost, but also in running.

The damping introduced into the circuit by the use of this detector is, of course, appreciably greater than that of the ordinary detector, due to its comparatively low resistance. This same objection, however, applies to the diode detector which is becoming so popular.



# CUTTING OUT NOISES

This helpful article gives some new methods of eliminating noises which are heard in a set as a result of stray H.F. and mains interference

the mains end of the wiring. First you can try putting large fixed condensers across the mains leads to the set as shown in Fig. 1. The centre point of the condensers is taken to earth.

This is quite a good hint as, in many cases, you will find it an advantage to disconnect the earth wire from the set itself (using a counterpoise or a shielded aerial arrangement, as will be described later) and the earth wire can then be connected to the join point of the condensers. 2-microfarad condensers capable of standing to voltage surges on the mains should be used and the condenser arrangement must be connected on the set side of the fuses so that if there is a breakdown the mains side of the wiring won't be affected.

An arrangement which is particularly effective on direct current supplies is shown by Fig. 2, where an additional smoothing choke is placed in one side of the mains wiring (the earth side if one side of the mains is earthed) and a 2-microfarad condenser is connected between the other mains lead and earth. Or you can use the choke in conjunction with the split condenser arrangement shown by Fig. 1.

This often makes a great difference to mains ripple which is so troublesome on D.C. supplies. Post Office engineers who have tested D.C. supplies, find the following is the maximum allowable ripple in a 200-volt D.C. supply at various frequencies under various reception conditions.

Reception Conditions	Frequency of Ripple in Supply		
	50	300	600
Silent periods	96	62	150
Normal speech	96	138	150
Soft music passages	107	150	150
Loud passages	128	150	150

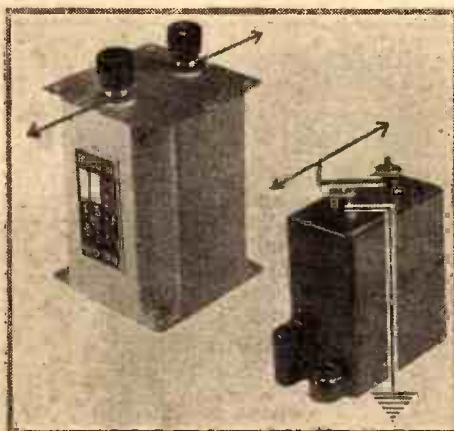


Fig. 2.—A choke and condenser filter circuit which is of especial value in D.C. supplies. A choke can be used in both mains leads if necessary, and the split condenser arrangement of Fig. 1 added



Flashing Signs—a bug-bear of reception.

STRAY noises come into a set, no matter whether it is mains or battery driven, as the result of external high-frequency interference.

Battery sets can be affected by H.F. or

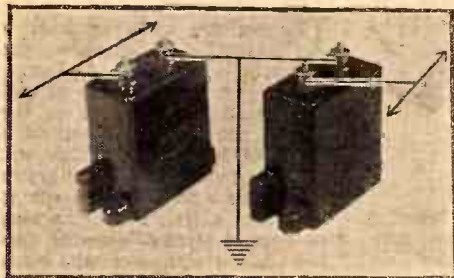


Fig. 1.—A simple split condenser arrangement which can be inserted in a mains supply to filter out stray H.F. A centre-tapped condenser can be used in the same way

even L.F. disturbances on adjacent power cable wiring running close to the set or aerial. Mains sets, of course, are much more liable to pick up this interference.

When a set starts humming or crackling—and the fault is found to be due not to any bad connection in the set itself—external sources of interference (neon signs, motors and so on) mustn't be blamed until you have made sure that you have done everything to cut out interference at the set end.

A mains supply to a set forms a workable aerial and it is often on this section of the wiring, rather than on the aerial itself, that stray H.F. is induced into the set. This applies to H.F. or L.F. strays in the wiring as a result of power cable deficiencies, and to neon sign, clicking contact and motor interference which is induced on the lines.

The first step is to filter out the H.F. at

Voltage surges cause trouble in mains-driven sets and on a bad supply may even cause the breakdown of condensers in the smoothing circuits. A series resistance can be used to reduce the overall mains voltage but a simpler plan is to run a lamp in parallel with the wiring to the actual plug point of the set. In

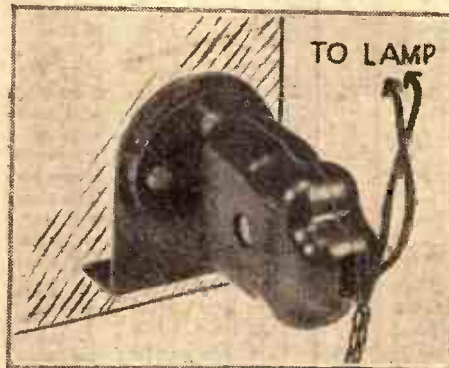


Fig. 3.—With certain badly-regulated supplies it is an advantage to run a lamp in parallel with the set to minimise voltage surges. A reading lamp may be used, or a small bulb can be wired as a pilot light

certain cases the easier path provided by the lamp filament has the effect of absorbing surges. The scheme need not be wasteful as a small high-voltage lamp can

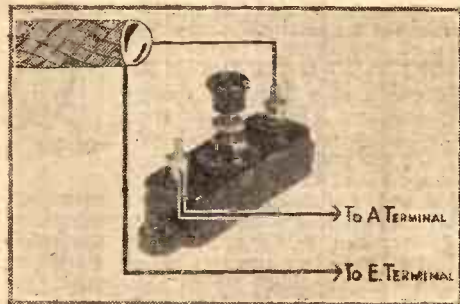


Fig. 4.—These are the connections for a shielded aerial arrangement to cut down interference at the H.F. end of the set. The outer casing of the shielded wire is connected to the earth terminal. No actual earth wire is used. This special wire is now obtainable in this country

be used as a pilot light, or an ordinary bulb used in a reading lamp. (Fig. 3).

Shielded aeriels are used by Post Office engineers in extreme cases of interference, where the induction is caused by the aerial. Until recently, the special shielded wire needed for an effective arrangement like this has only been available on the Continent. Now, shielded lead-in wire, suitable for the job, is made by one British firm.

The aerial wire passes down a core of insulators over which a flexible metal covering is woven. A length of this wire should be used as an aerial. The centre wire is connected through a preset condenser to the aerial terminal on the set as shown in Fig. 4.


(Continued at foot of next page)



# That Radio Dodge
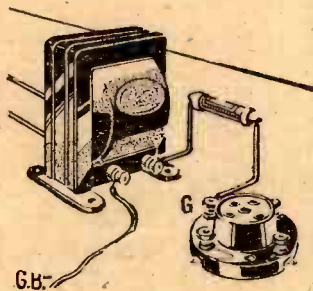
## PREVENTING H.F. STRAYS

IF you put a grid leak of about  $\frac{1}{4}$  megohm between the grid terminal of a low-frequency transformer and the grid of the L.F. or power valve following the detec-



tor (in place of the direct wire connection) you can often cut out instability. This is almost as effective in some cases as putting an H.F. choke in the primary winding of the transformer. The self-capacity of the transformer disperses the stray H.F. currents and they are prevented from entering the low-frequency stage by the resistance in the grid circuit. The tone is not affected by putting the leak in this position, though it is, of course, if the leak is placed across the secondary winding.

## MOUNTING A CONDENSER

IF you have a three-hole fixing condenser, but have lost the template, here is a method for finding the position for the fixing holes. First drill the spindle hole and one fixing hole. The position of this can generally be estimated fairly accurately. Then fill the other two mounting stubs with vaseline. Mount the condenser with one screw and


screw it tightly. This will pull the other two stubs tight to the panel. When the condenser is removed, two grease rings will indicate the position of the other two holes.

## TERMINAL BUSHES

NOW that chassis-type sets are in great demand. A good way of making your own is as follows. Cut a piece of ebonite tube to fit over the terminal shank, having a bore just larger than the shank, and about  $\frac{1}{4}$  in. long. Plunge this in boiling water for a few moments, fit over the shank and screw home as quickly as possible. The ebonite will be rendered quite soft by the heat and the ends will splay out, effectively insulating the terminal.
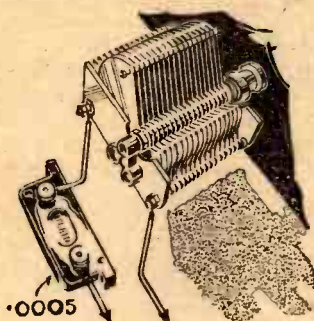
## FOR SHORT WAVES

IF you have a broadcast-band set which you want to convert for short-wave operation, it is generally advisable to have short-wave condensers for the tuning




controls. These have a lower maximum capacity, but owing to the characteristics of the short-wave circuit they cover the full tuning range and are much easier to operate than the ordinary

.0005-microfarad tuning condensers. If your set conversion is only a temporary one, though, you needn't scrap the .0005's. Just put a fixed condenser of .0005 microfarad in series with each tuning condenser. This will cut down the maximum capacity and make it much easier to tune the outfit on the short waves.
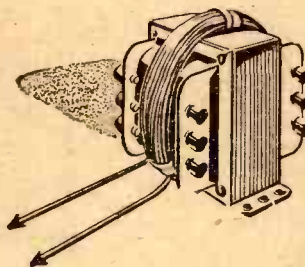
## LIGHTING A PILOT BULB


IN a mains set you can often get a suitable low-tension supply for a dial lamp even if there is no low-tension winding on the mains transformer. An external low-tension winding can be fitted by just winding a hank of wire outside the transformer. If the transformer is not shielded there will be an external field which will create a sufficient voltage for the dial lamp. Fairly stout wire of about 24 gauge should be used and the number of turns depends on the primary winding of the transformer and the distance between the primary and this



additional secondary winding. Start off with a dozen turns bunched closely together and wind on more if necessary until the pilot lamp (3.5-volt screw-in type) gives a sufficient light.
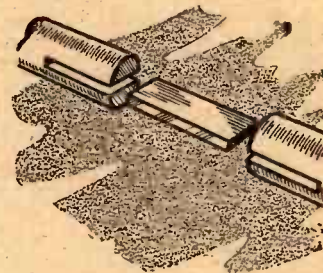
## SLIPPING COIL SWITCHES

GANGED coil switches sometimes slip if not coupled firmly together. Then one set of coil contacts remains open while the others are closed. If the



coupling link between rotary switches consists only of a tubular piece with grub screws, a slip may occur unless the screws are tight. A good plan is to fit a positive link as shown in the accompanying sketch. File slots in the ends of both coil-switch rods and cut a flat piece of sheet brass to fit in the slots as a link piece.

## MICROPHONIC VALVES

IF you are suffering from a "pongy" detector valve, the following is a simple but effective cure. Just stick a piece of well masticated chewing-gum on the top of the valve and embed a piece of lead in it. This will damp out vibration almost before it has time to start, except in very bad cases. Plasticine may be used in place of chewing gum but Chatterton's compound is not recommended. It has to be applied hot and the heat of the iron is liable to break the bulb.

## "CUTTING OUT NOISES"

(Continued from preceding page)

The outer covering of the shielded wire is taken to the earth terminal of the set and the normal earth is disconnected. No actual earth should be used, but if the set is mains driven, an additional precaution can be effected by taking the earth wire to the split condenser arrangement of Fig. 1.

It is worth while taking a little trouble to filter out stray H.F. in the mains supply. Post Office experts state that the high-frequency potential imposed on house wiring in this way may be only a few microvolts, but the interference experienced can be as strong as the signal received from a 50-kilowatt transmitter, 30 miles away!

Other means of inducing interference aren't so direct. For instance, experience shows that motor interference rarely

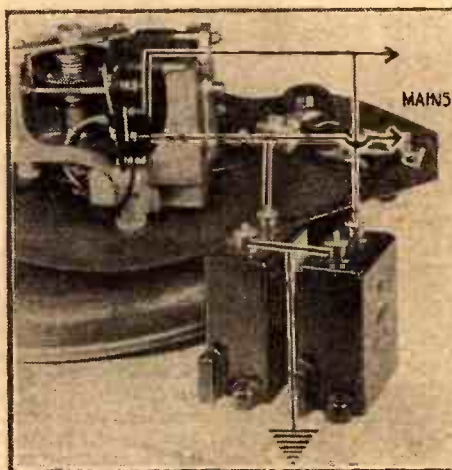


Fig. 5.—A split condenser arrangement can be connected across the terminals of a "noisy" motor to reduce the H.F. interference.

extends to a greater distance than 200 yards. This has the advantage that if you suspect a noisy motor of causing interference with your reception you can generally trace the motor and the owner. A split condenser arrangement across the input to the motor terminals, as shown by Fig. 5, is generally successful.

The City of Birmingham Orchestra will be heard twice on March 25, relayed from the Town Hall. In the afternoon their Children's Concert includes Elgar's Second "Wand of Youth" series and in the evening there is a plebiscite concert under the direction of Leslie Heward.

In the Peto-Scott announcement in last week's issue, the price of the Pilot Structakit for the "James Push-Push Three" was incorrectly given as 10s. 6d. This should have read 6s. 6d.



# OUR BROADCAST CRITIC

## ON AN EVENING RECITAL



LAURI KENNEDY

I APPRECIATE the value of hearing something beautiful last thing at night. I have always imagined I understood what made Chopin write nocturnes, and have always enjoyed going to Queen's Hall for an evening symphony concert, even though the train journey home has often spoilt the effect. When I hear something really artistic last thing at night in my own home the effect has always been the same; a contemplation of wireless as a great psychological power.

One night (during the present week of writing) Evelyn Scotney and Lauri Kennedy gave a joint recital. I do not remember having enjoyed anything more for a considerable time. Miss Scotney's voice possesses all the qualities requisite for perfect radio transmission. I would rather hear her than anyone who I can call to mind at the moment. It is a big thing to say, because there are so many that are good, but I say it because I honestly think it.

Miss Scotney was wise to choose good but lightish songs. Her voice was so clear, and tonally beautiful, that I found myself wishing I could write down a list of all the songs and arias which appeal to me—the list would be rather lengthy, I fear—and “make” her sing them all. That thought came to me as she sang *Solveig's Song*, which I never heard sung as she sang it. Having thus extolled her undoubted great qualities (those of a perfect soprano voice coupled to considerable power of interpretation) I am going to say one other thing—and quite frankly. *Her diction is not good enough.* Only one word in four came through the other night. Now, in case she (or anyone else) might be inclined to suggest that the fault lay in my set, or the transmission, or both, I point out that less than an hour previously, I heard a vaudeville artiste, who would not pretend to have a tenth of Miss Scotney's tone, sing three songs of the vaudeville type. Her words were absolutely distinct. If I need to add anything further on this subject, so far as Miss Scotney is concerned, it would be to tell her that, although I knew the words of *Solveig's Song* I could not hear them. I want her to remedy this one fault. When she does so, she will be the perfect wireless soprano.

Lauri Kennedy's playing always appeals to me. He has often given me pleasure at Queen's Hall when he has had some fragmentary melody as a solo in a symphony. His tone in Kreisler's arrangement of Dvorak's *Indian Lament* seemed to suit my loud-speaker extraordinarily well. I should like to hear him play a

'cello concerto in one of the Sunday night symphony concerts. Will somebody ask him to do so?

Variety, I have come to the conclusion, must be divided into three distinct classes. They are Vaudeville, Boredeville, and Funeraudeville. We had a Boredeville on Thursday night. It would have been a Funeraudeville had not Alec Shaw and Gillie Potter saved it between them. Alec Shaw imitated the songs of the birds in such a way as to beat the birds at their own game. The nightingale at the end of this amazing recital was absolutely to life. The good Gillie gave us a splendid satire as a judge trying a case of an offender against the Shops Closing Act. Some of it was very smart.

As I have said, they saved the show which, otherwise, was more than a little boring. The Hulbert Bros. not appearing, Harry Tate came instead. All I will do is to quote his funniest lines. Mr. Tate told somebody to go to the post office with a label and tell them to tie a parcel to it. That made me laugh so much that I nearly missed the other. A man was described as coming up the stairs two at a time. Mr. Tate asked why. What do you think the reason was? (I can scarcely write the words

### PROGRAMME POINTERS

More than one concert has been spoilt recently by its programme containing both classical music and ultra-modern music. It seems to me that, as ultra-modern music has broken away so definitely from music written in the classic and romantic periods, the change of thought is too virile to be artistic. Programme-making is a psychological activity at the best of times; it is not merely “contrast at all costs.” This refers as much to chamber-music concerts as it does to symphony concerts. To listen to music of the dissonant type requires an effort not everyone is inclined to make, especially those who are devotees of the classical Masters. As broadcasting is so universal it should express its catholicity of taste by giving everything, but only in a suitable position. It is one thing to give everything over a period; it is another to mix everything up together.

for laughing, even now). *It was because it was quicker than coming one at a time.* There now. Isn't that a scream?

Huntley Wright's songs were what one would expect from him. Quite enjoyable, but the first one had ten verses too many.

The Eden Phillpotts play *The Point of View* had good points about it, certainly, but the dialogue was rather heavy-going and I regret to say I found my attention wandering. For some reason “entirely out of our control” (I quote the Announcer) the second play *The Carrier Pigeon*, by the same author, was not performed. The revival of the play about salesmanship, which took its place, is one I should not criticise, I think. It was obviously rushed on at the last moment. I imagine without rehearsal.

Schnabel's playing of the *Emperor* Concerto of Beethoven created the usual deep impression. Those who have followed him know what to expect. Another point about that concert was Adrian Boult's handling of Mozart's *Jupiter* Symphony. One or two musicians have told me how much they enjoyed it. I agree.

### A Popular Series

The series of historical entertainments called “As It Might Have Been” ought to be popular—at least, to those who are remotely interested in history. I did not hear the first of them, but I enjoyed the second. The year 1783 was a good one to choose because so many interesting people were living in London about that time, such as Dr. Burney, Sir Joshua Reynolds, Dr. Johnson, Horace Walpole and Nathaniel Wraxhall. Incidentally, I recognised the voice of Ronald Simpson in the last-named part. It was amusing and also not a little instructive, to be reminded that an overture of “Mr.” Haydn was being performed for the first time in England, and that the new “forte-piano” had recently taken the place of the usual harpsichord. To hear Mozart regarded as a very modern type of composer was another good point. I have always held the opinion that real characters are far more interesting in plays or shows of this sort than fictitious characters. Within reason, we cannot have too many historical subjects treated, so long as they are accurately treated. There was not much wrong with the facts in this show. I look forward to the next.

WHITAKER-WILSON.



# The A.C. MAINS MELODY RAN



**DESIGNED BY  
S. RUTHERFORD WILKINS**


of our wonder set is bound to be very popular with all those who are on an A.C. supply, for the all-electric model illustrated in these pages does away with the high-tension, the low-tension and even the grid-bias batteries.

## SIMPLE ALTERATIONS

In effect, the alterations to the original set as first described are simple enough, if you understand the essential differences between a battery-operated set and one that derives its power from the electric-light supply.

As Mr. Percy W. Harris is explaining in his new series of articles on Practical Mains Working, the really big difference

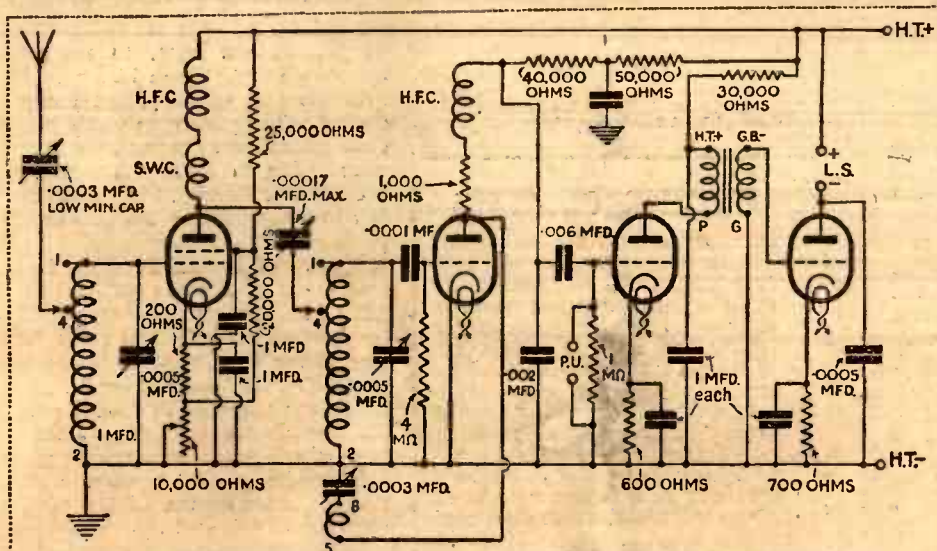**N**OW you can build a "Melody Ranger" that not only has all the wonderful attributes of the all-wave set first described in **AMATEUR WIRELESS** dated January 28, 1933, but that can be worked entirely from the A.C. mains. This latest version




This is the circuit of the actual receiver which incorporates indirectly-heated valves. Details of the separate rectifier unit will be given next week

HERE IS THE MAINS MODEL OF THE FAMOUS  
"MELODY RANGER" — THE SET WHICH COVERS  
FOUR WAVEBANDS AT THE TOUCH OF A SWITCH  
AND MARKS SUCH AN ADVANCE IN DESIGN

is in the arrangement of the filament and the high-tension negative side of the circuits. Instead of the negative side of the anode supply.

the filaments forming the earth connection of the grid circuits, we make use of the cathodes of indirectly-heated valves. These cathodes in mains valves do, in fact, correspond in connection to the negative side of the ordinary battery filaments.

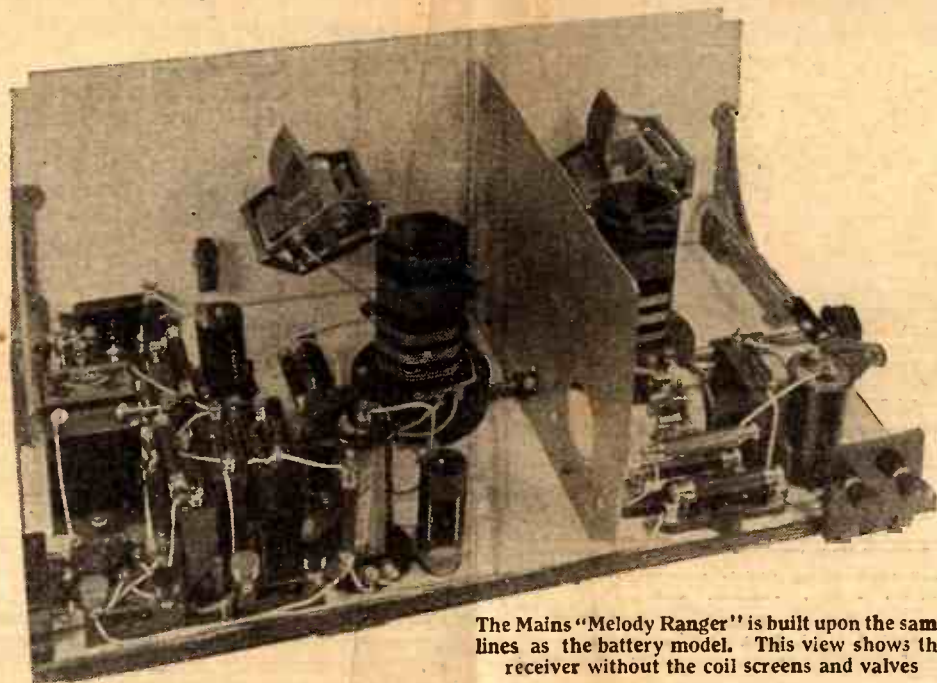The first alteration is therefore to use valve holders that will take the five-pin mains valves in place of the holders



The Mains "Melody Ranger" is built upon the same lines as the battery model. This view shows the receiver without the coil screens and valves

originally used for the four-pin battery valves. The work of altering the original "Melody Ranger" is mostly in the re-wiring of the valve holders, as shown by the blueprint and other illustrations.

## GRID BIAS

One point of special importance is that in a mains set grid bias is obtained in an indirect way from the high-tension supply and not from an entirely separate source of voltage as in a battery set.

To obtain this grid-bias voltage we insert bias resistors between the cathodes

the low - frequency - amplifying valves.

The detector grid leak is connected to the cathode and this in turn is connected to earth. An A.C.-mains detector works at zero grid volts for efficient detection, and in this differs from the battery valve that needs a slight positive bias.

In the electrified version of the "Melody Ranger" only the last two valves have the bias resistors, as the detector does not need one and the variable- $\mu$  high-frequency valve has a variable negative bias applied by means of a potentiometer network across the high-tension supply.

WITH THE "MELODY RANGER" YOU CAN LISTEN TO THE WO



# RANGER

## 12 TO 2,000 METRES AT THE TOUCH OF A SWITCH

We should explain that this negative bias on the variable- $\mu$  is actually obtained by producing a progressive change in the positive bias on the cathode of this valve. This comes to the same thing as providing a negative bias on the control grid.

The values are so chosen that although a variable negative bias is, in effect, obtained from the control grid, the voltage on the screening grid of this valve is constant.

### CIRCUIT MODIFICATIONS

Apart from the changeover from battery to mains valve holders, there are one or two other necessary circuit alterations in the original "Melody Ranger." There is, for example, a .0005-microfarad fixed condenser connected between the anode of the output valve and earth. This improves the smoothness of the reaction.

Adequate de-coupling is probably the most important circuit feature of any mains set and in the revised "Melody Ranger" this important business has received very careful attention. You will note that the detector anode circuit is now de-coupled with a 50,000-ohm resistance and a 2-microfarad fixed condenser.

So much for the chief alterations to the original set as first described for battery operation. In addition to these alterations, which are, of course, designed to eliminate the grid-bias battery and the accumulator, we must consider the high-tension supply.

So far as the external accessories are concerned we have to provide the apparatus for the elimination of the high-tension battery. The high-tension voltage, most of which is for the anode supplies, but part of which, by means of the bias resistors, is for the grid bias of the valves, is obtained from the A.C. mains by a valve rectifier.

We shall describe this unit in detail next week. For the present all we need explain is that between the mains supply and the rectifier is a mains transformer. The primary of this is connected to the mains and there are three secondaries.

One is for the filament supply of the rectifying valve and the second is for the filament heating of the indirectly-heated valves in the set. The third is for the high-tension voltage.

Between the rectifier and the output terminals of the unit there is a smoothing circuit, which consists of a choke with electrolytic condensers. There is another condenser to eliminate what is known as modulation hum.

### THE UNIT'S OUTPUT

This unit supplies the set with a maximum output of about 250 volts at 40 milliamperes, which means there is ample power in hand required for the valves actually in the all-electric version of the "Melody Ranger."

Taking a general view of the new "Melody Ranger," it is, of course, clear that with the indirectly-heated mains



The "Melody Ranger" is a handsome instrument, designed to give the greatest efficiency. The lower part of the cabinet contains the actual receiver, and the loud speaker and mains unit are in a separate compartment above.




# A 12-2,000 METRE SET—MAINS OPERATED (Continued from preceding page)

valves the overall performance is superior to the battery version. In what exact manner this superiority is shown in practice may not be clear to all readers.

For one thing, the sensitivity to weak signals is greater. Stations that are almost inaudible on the battery version may come in at good strength on this all-electric version. This applies especially on the short waves, where the extra amplification of the mains valves is heard to very great advantage.

Another way in which this mains-operated "Melody Ranger" scores is in the greater power output. There is about 750 milliwatts undistorted power handed on by the fully loaded power valve to the moving-coil loud-speaker. This, with the specified speaker, corresponds to very considerable volume.

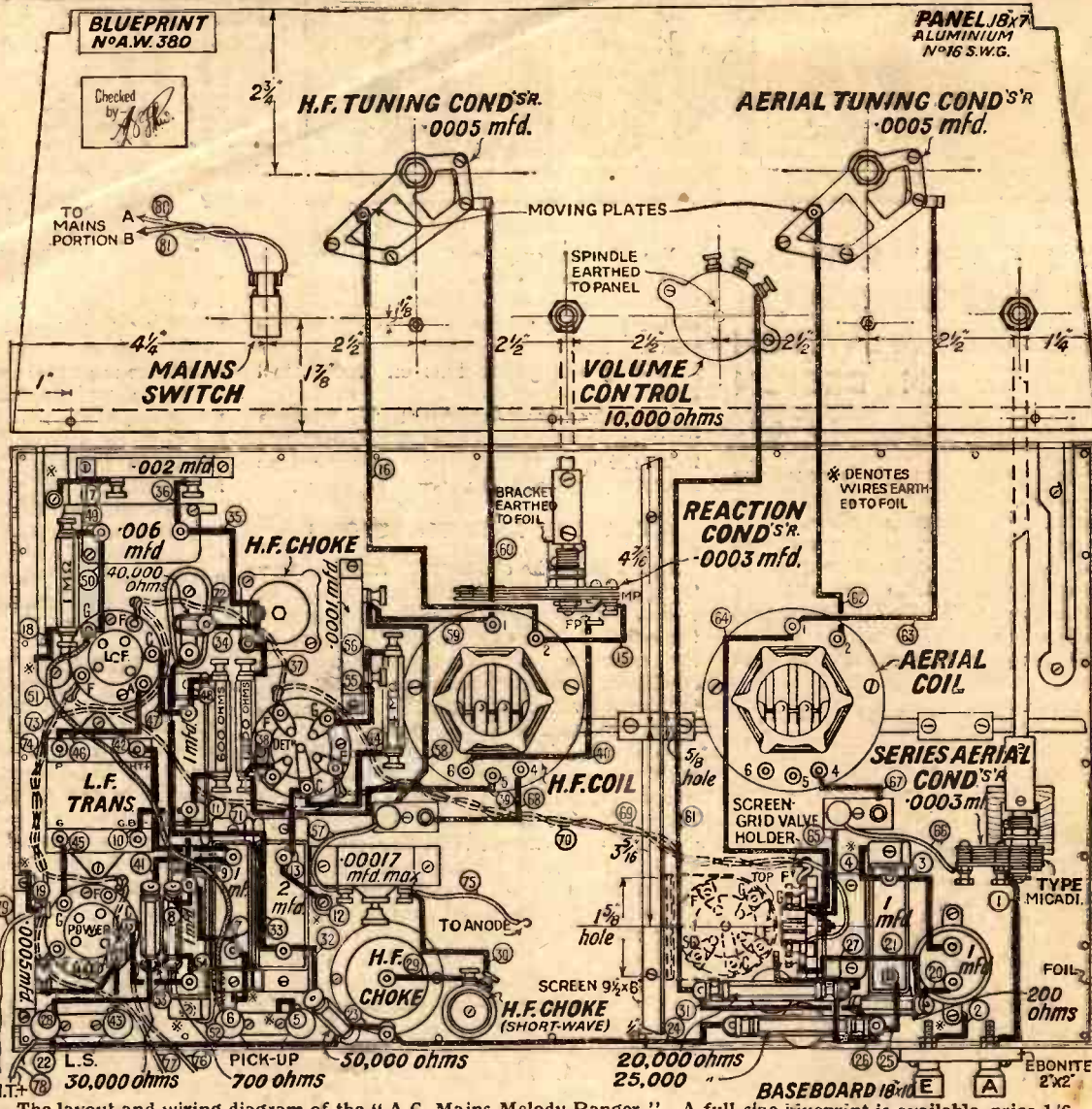As a fairly economical power valve has been fitted the overall running cost of the "Melody Ranger" when worked from the mains is very low indeed. The total power taken from the mains is between 20 and 25 watts, which is less than a single electric-light bulb.



## DETAILS OF THE MAINS UNIT NEXT WEEK

The layout and wiring diagram of the "A.C. Mains Melody Ranger." A full-size blueprint is available, price 1/6

### COMPONENTS REQUIRED FOR THE "A.C. MAINS MELODY RANGER"

#### CHOKES, HIGH-FREQUENCY

- 1—H.F. choke (Wearite, type H.F.O., Lewcos, or Ready Radio).
- 1—H.F. choke (Slektun standard, Graham Farish, type LMS, Lissen astatic, Lewcos, Ready Radio, Goltone, Varley, Tunewell, Climax, R.I., Wearite).
- 1—Short-wave H.F. choke (Igranite type CHORT, Wearite, Goltone, Slektun).

#### COILS

- Two special coils complete with two couplers and extension rods (Lissen).

#### CONDENSERS, FIXED

- 1—.0001-mfd. fixed condenser (Lissen, Dubilier, T.C.C., Telsen, Graham Farish, Goltone).
- 1—.002-mfd. fixed condenser (Lissen, Dubilier, T.C.C., Telsen, Graham Farish, Goltone).
- 1—.0005-mfd. fixed condenser (Lissen, Dubilier, T.C.C., Telsen, Graham Farish, Goltone).
- 1—.008-mfd. fixed condenser (Lissen, Dubilier, T.C.C., Telsen, Graham Farish, Goltone).
- 4—1-mfd. fixed condensers (Telsen, Dubilier, Lissen, T.C.C., Goltone, Igranite).
- 1—1-mfd. fixed condenser (Dubilier, type 9200, T.C.C., Telsen, Igranite).
- 1—2-mfd. fixed condenser (Telsen, Lissen, Dubilier, T.C.C., Igranite, Ready Radio, Goltone).

#### CONDENSERS, VARIABLE

- 2—.0005 tuning condensers (J.B. type JL6, Polar No. 3 with phosphor bronze balls, Utility).
- 1—.0008-mfd. series aerial condenser (Ready Radio special low minimum type Micadi).
- 1—.0003-mfd. reaction condenser (Ready Radio, type Micadlog).
- 1—.00017-mfd. pre-set condenser (Lissen, Ready Radio, Sovereign, Goltone).

#### DIALS

- 2—Slow-motion (Igranite, Indigraph type VINIL, Utility type W181).

#### HOLDERS, RESISTANCE

- 1—Vertical mounting holder (Graham Farish).
- 2—Horizontal mounting holders (Graham Farish).

#### HOLDERS, VALVE

- 1—Low-loss screen-grid 5-pin valve holder (Ready Radio, type SG short-wave, or Eddystone).
- 1—Low-loss 5-pin valve holder (Ready Radio, type short-wave baseboard, or Eddystone).
- 2—5-pin valve holders (Ready Radio standard, Lissen, Tunewell, Telsen, Igranite, W.B., Graham Farish, Lotus, Goltone).

#### PANEL AND BASEBOARD

- Aluminium panel, drilled and cut to specification, 18 in. by 7 in. (Peto-Scott or Ready Radio).  
Baseboard covered with foil, 18 in. by 10 in. (Peto-Scott or Ready Radio).  
Aluminium screen, drilled to specification, 9½ in. by 6 in. (Peto-Scott or Ready Radio).

#### RESISTANCES, FIXED

- One 200, one 600, one 700, one 1,000, one 20,000, one 25,000, one 30,000, one 40,000, one 50,000, one 1-megohm, one 4-megohm fixed resistances (Graham Farish type Ohmite, Ede, Dubilier, Goltone, Claude Lyons).

#### SUNDRIES

- Pair of panel brackets (Peto-Scott, Bulgin, Burton).  
Complete extension equipment and mounting brackets (Ready Radio).  
Four yards thin flex (Lewcoflex, Goltone).  
Connecting wire and sleeving (Lewcos).  
Piece of ebonite 2 in. by 2 in. (Becol).  
Two coil tap mounts complete (Peto-Scott, Bulgin), or four ¼-in. sockets (Belling-Lee); piece of ebonite 2 in. by ½ in. (Becol).

Knob for volume control (Bulgin, type K6).

Two terminal blocks (Telsen, Lissen).  
1 foot single screened cable (Lewcos).

#### SWITCH

- 1—Mains on-off toggle switch (Bulgin, type S80, Claude Lyons, Igranite, Tunewell, Utility, Ormond).

#### TERMINALS

- 2—Terminals, marked Aerial, Earth (Belling-Lee, type R, Eelex, Bulgin).

#### TRANSFORMER

- 1—Low-frequency (Varley Nichoke II, Lissen, R.I. Di-Feed, Telsen, Multitone, Bulgin, Slektun, Ferranti, Tunewell, Wearite, Lewcos).

#### VOLUME CONTROL

- 10,000-ohm variable resistance (Bulgin type VC32, Watmel type T1, Varley, Lewcos, Tunewell, Ready Radio, Sovereign).

#### MAINS PORTION

- 1—Mains transformer (Heayberd, type MR).
- 1—Smoothing choke (Tunewell type S70/50, Wearite, Igranite, R.I., Ferranti).
- 1—4-pin valve holder (Ready Radio, Lissen, Telsen, Igranite, W.B., Graham Farish, Lotus, Goltone).
- 2—4-mfd. electrolytic condensers (Dubilier, T.C.C.).
- 1—1-0.1-mfd. fixed condenser (Dubilier, type BE31.L, T.C.C.).
- 1—Twin fuse holder and fuses (Bulgin, type F9).

Length of mains flex (Lewcos).

#### ACCESSORIES

- Cabinet (Peto-Scott) with loud-speaker chassis (Myers-Hunt, Camco).  
Loud-speaker (W.B., type PM4 chassis model, Rola, type F5PM1, Atlas, R. & A., Celestion Epoch).  
Earth (Graham Farish "Filt").  
Aerial (Electron).



# "The LISSEN COILS ARE THE HEART OF THE MELODY RANGER"

*Says Amateur Wireless*



**EXTRACT FROM  
AMATEUR WIRELESS  
4<sup>TH</sup> FEBRUARY 1933**

The following is an extract from "Amateur Wireless," 4th February, 1933:—"In the 'Melody Ranger' . . . there is the outstanding feature . . . of a four-range coil. This coil is indeed the heart of the 'Melody Ranger' circuit, and accounts for the wonderful range of stations that has been logged during our tests all round the country. . . . The very wide wavelength range enables many stations normally outside the range of sets to be tuned in at full strength . . . the coil is a great engineering triumph."

The first successful all-wave receiver—the "Amateur Wireless" MELODY RANGER. The first time it has been found possible to combine all-wave ranges from 12 to 2,000 metres in a single coil—and Lissen have done it! Short-wave work is tricky work—minute stray capacities, relatively small masses of material such as knobs of solder, have an altogether disproportionate effect upon the tuning efficiency of the coil. Switching is extremely difficult to arrange—the medium- and long-wave windings have unexpected effects upon the short-wave coil. You would be surprised if you knew how many times this Lissen "Melody Ranger" Coil has been backward and forward between the "Amateur Wireless" laboratory and the Lissen physicist. It definitely could not have been produced at all except for this close co-operation between the "Amateur Wireless" designers and the unrivalled facilities of the Lissen organisation.

No matter how you intend to buy the parts for your "Melody Ranger"—as a complete kit or part by part, for cash or by easy payments—YOU MUST, FOR YOUR OWN SAKE AND IN FAIRNESS TO A FINE SET, INSIST UPON THE GENUINE LISSEN "MELODY RANGER" COILS. Look for the name Lissen on every coil if you want satisfaction from the set.

**THERE IS  
AND CAN BE  
NO  
SUBSTITUTE  
FOR THIS  
COIL**

**PRICE  
15/-  
EACH**

**LISSEN**  
UNIVERSAL

**4-WAVE-RANGE COIL**

LISSEN LTD., WORPLE ROAD, ISLEWORTH, MIDDLESEX

To Ensure Speedy Delivery, Mention "A.W." to Advertisers



# What Our Readers Think



*The Editor does not necessarily agree with the views expressed by readers and does not accept responsibility for the letters published. Letters cannot be published which do not bear the sender's full name and address*



## A Switch Point

SIR,—With reference to L. N. R.'s letter in the issue of AMATEUR WIRELESS dated February 4 under "Watch that Switch," an experience of mine may be of interest to your readers.

Switching my set on a short time ago I failed to get any signals from it; as the set had worked the previous day I was rather at a loss to know what had happened. To cut a long story short, everything was tested and proved O.K. and a test proved that the valves were receiving the necessary current. What, then, was wrong?

When switched over to the long waves a thin, distorted signal could be heard, but on the medium waves, nothing.

The coils used have push-pull switches for the wavechange. I took the coils out and adjusted the nuts, which act as stops on the push-pull switch and, replacing the coils, switched on and found that results had improved, but were still far from satisfactory. It took some time to adjust the nuts so that results were satisfactory and even now, if the switches are touched while the set is working a crackling noise can be heard in the loud-speaker.

C. A. B. (Reading).

## Balanced-armature v Moving-coil

SIR,—You publish in your issue dated February 4 a letter from "G. E. F." (Sheffield) headed "Balanced-armature v Moving-coil," which we have read with considerable amazement and not a little amusement.

Would this gentleman be so good as to enlighten us on the points enumerated below.—

(a) How does he know when his balanced-armature speakers are reproducing frequencies of 50 and 5,000 cycles?

(b) Has the output from these speakers been plotted on a decibel scale? If so, its publication would be interesting.

(c) What type of amplifier does G. E. F. use? Has it a linear output from 0 to 5,000 cycles, and if so what proof is there of this?

(d) Does your correspondent suggest that the same type of amplifier is equally suitable for the operation of both balanced-armature and moving-coil speakers?

It is, of course, quite unnecessary at this stage to go very deeply into the construction and characteristics of both types of loud-speakers or into the fundamentals of design which render it a mechanical impossibility for a balanced-armature

speaker to reproduce frequencies which are quite within the normal range of a properly designed moving-coil.

We should be very grateful if your correspondent could find time to reply to the queries set out herewith as it appears that he is at present suffering from some form of aural delusion.

RADIO SERVICE LABORATORIES  
(London, N.W.).

## B.B.C. Response Tests

SIR,—With your correspondent "J. E.", I hope the recent response tests of the B.B.C. will be repeated.

I, unfortunately, missed them, but think they were most welcome and much overdue.

A query to the B.B.C. brought a reply to the effect that they were unable to say "whether the transmission would be repeated but the matter would receive careful consideration."

I could have wished the B.B.C. had chosen a happier phrase knowing that in business, at any rate, it means the end of the deal. Still, we will live in hope that it may be considered important that we should receive the quality the B.B.C. are at great pains and expense to turn out. I wonder what percentage of listeners have any notion of their reproduction below 150 cycles?

A. W. F. (Newcastle-on-Tyne).

## Appreciation

SIR,—I have now been a reader of AMATEUR WIRELESS for seven months and, believe me, sir, I have certainly improved my radio knowledge from it.

I honestly say there is not another wireless book like it on the market for the price. It certainly is worth its "3d. double."

S. A. C. (Ramsgate).

## B.B.C. Pronunciation

SIR,—May I add a word of correction and advice to our friend W. T. (Godrer Craig)? He accuses the B.B.C. announcers of incorrect pronunciation, whereas their's is absolutely correct. W. T. is apparently Welsh. He pronounces Welsh place-names in Welsh. English announcers pronounce them in English.

How does W. T. pronounce "Paris"—Par-iss or Par-ee? The former is correct in English, whilst the latter is correct in French.

H. R. (Manchester).

The Editor invites letters from readers on all interesting radio subjects. For the most interesting letter published each week a general-purpose valve or other component to the same value will be given.

## The "Melody Ranger"

SIR,—I was one of the fortunate winners of a kit of components for the "Melody Ranger" in your recent competition and have now built it and given it a good test.

First, I think Messrs. Peto-Scott deserve a word of praise for the kit I received, complete in every respect down to the smallest screw and exact to your specification and beautifully packed.

Now about the set. I think the easiest way to express my opinion is to say that it is all that you claim it to be and does all that you say it will do.

I live in a badly shielded district and have only a poor indoor aerial, but it gets the stations, and on all wavelengths—Americans on the short waves, with Lisbon, Moscow, Zeesen, amateurs and others, and all worthwhile ones on the medium and long waves.

I think great praise is due both to the designers of the circuit and the coils. I have built all sorts of sets in my time, from crystal up to the "Century Super," and am really surprised at the strength and selectivity of this straight four-valver.

G. L. C. (London, W.).

## IF YOU ARE A NEW READER

EVERY issue of AMATEUR WIRELESS contains a wealth of information and new readers will be interested to have details of helpful practical and constructional articles which have appeared in the past few issues.

They cover a wide range of helpful information, from hints on speakers to the construction of an amplifier on the new "Q.P.P." principle! For instance, a simple L.F. amplifier incorporating the quiescent push-pull system was described in "A.W." No. 557, and in the previous week's issue, No. 556, the theoretical side of Q.P.P. was dealt with in an authoritative article. Short-wave working is even yet a closed book to many listeners who do not realise what they are missing by not taking advantage of below 100-metre reception. There is a special short-wave supplement in "A.W." No. 556, and in this Mr. Percy W. Harris describes practical short-wave working for beginners. You will find this a really helpful guide to short-wave reception.

Of more general interest are the novel power supply ideas given in "A.W." No. 554. These apply to batteries and mains, and will interest you no matter what kind of set you have.

All the issues of "A.W." referred to can be obtained, price 4d. post free, from the Publishing Department, AMATEUR WIRELESS, 58-61 Fetter Lane, London, E.C.4.



# BUILD WITH YOUR OWN HANDS

## THIS BETTER SET

## SAVE POUNDS

## SUCCESS A CERTAINTY

YOU ARE TOLD  
EXACTLY WHAT TO  
DO WITH EVERY  
SINGLE NUT  
& SCREW

**89½**  
INCLUDING  
VALVES

GET YOUR  
**FREE COPY**  
OF MOST SUCCESSFUL  
**CHART**  
EVER PUBLISHED  
enabling you to build  
MOST SUCCESSFUL  
**SET EVER  
BUILT!**

THE ONLY KIT YOU  
CAN BUILD YOURSELF  
EMPLOYING METALLISED  
S.G. HIGH-MU DETECTOR  
AND ECONOMY POWER  
PENTODE VALVES

NEVER before was there such a set within the reach of the home constructor. Never before such power from a battery set. Never before so many enthusiastic letters from constructors or so much talk about any radio set as this Lissen "Skyscraper" Kit has elicited. 50-60-70 loud-speaker stations—everybody who builds a "Skyscraper" gets results like that! Lissen have published a 1/- Constructional Chart, giving the most detailed instructions ever printed for the building of a wireless set. You can't go wrong—every part, every wire, every terminal is identified by photographs. Everybody, without any technical knowledge or skill, can safely and with COMPLETE CERTAINTY OF SUCCESS undertake to build this most modern of radio receivers from the instructions given and the parts Lissen have supplied.

This new Lissen "SKYSCRAPER" Kit Set is the only one on the market that you can build yourself employing a Metallised Screened Grid Valve, High Mu Detector and Economy Power Pentode. Around these three valves Lissen have designed a home constructor's kit the equal of which there has never been before. Why be satisfied with whispering foreign stations when you can BUILD WITH YOUR OWN HANDS this Lissen "SKYSCRAPER" that will bring in loudly and clearly distant stations in a profusion that will add largely to your enjoyment of radio?

## YOURS FOR ONLY 8½ DOWN

To-day you can buy the LISSEN "SKYSCRAPER" KIT on Gradual Payment Terms.

"Skyscraper" Chassis Kit, complete with Valves, CASH PRICE, 89/6. Or 8/6 down and twelve monthly payments of 7/6.

"Skyscraper" Kit complete with Walnut Cabinet and in-built Loud-speaker, as illustrated, £5 5s. cash. Or 11/6 down and twelve monthly payments of 19/6.

You can get the Lissen "Skyscraper" Chart FREE from any radio dealer, or by posting the COUPON below direct to factory.

COMPLETE IN CABINET  
WITH LOUDSPEAKER **£65** or 11/6 DOWN  
& twelve monthly  
payments of 10/6

### COUPON

To Lissen, Ltd., Publicity Dept. A.W.33, Worple Road, Isleworth, Middlesex.

Please send me FREE copy of your 1/- Skyscraper Chart.

Name.....

Address.....

# LISSEN "SKYSCRAPER" KIT 3

Mention of "Amateur Wireless" to Advertisers will Ensure Prompt Attention



## SETS of the SEASON

# EKCO RG 23 RADIO-GRAMOPHONE

IT would be difficult at the present time to point out a better value-for-money proposition in radio-gramophones than the Ekco RG23, which I have just had the great pleasure of testing.

Some instruments, from the word go, as you might say, impress one with their essentially sound performance. Such an instrument is this Ekco RG23, a three-valve radio-gramophone with so many excellent features, I hardly know where to begin in recounting them.

Perhaps you, as a potential radio-gramophone buyer, would prefer to know something of the general specification. If you have come across the admirable M23 table console set you will have a very fair idea of what the RG23 can do, because this radio-gramophone is designed around the chassis of the M23 radio set.

### Effective Three-valves

The chassis in question is a fine nucleus for a radio-gramophone, since it has one of the most effective three-valve combinations available. There is a screen-grid high-frequency valve, a detector, and a pentode

power output valve, all obtaining their high-tension supply from the A.C. mains via a Westinghouse metal rectifier.

In addition to all the controls found on the M23 set, the RG23 radio-gramophone has a separate volume control for the gramophone side, and a radio-gramophone switch fitted concentrically around the volume control.

The same permanent-magnet moving-coil loud-speaker is used in the radio-gramophone as in the radio set. I mention this because you may have heard the M23 in action and from that you can judge the quality from the radio-gramophone. As a matter of fact the quality is better with the radio-gramophone, for the rather obvious reason that the bass-note response has a better chance to show itself behind the ample baffle of the walnut cabinet.

I think most readers would like the style of the cabinet, which, for so inexpensive an instrument, has a quiet dignity of line and finish that agreeably surprised me. The cabinet wood is polished, I understand, by a new process. Certainly the satin-like finish is well done.

When you lift the lid of the cabinet you find the turntable of the electric gramophone motor and to one side the gramophone pick-up.

The front of the cabinet is taken up with the main controls mounted above the grille or fret for the moving-coil loud-speaker. There is the usual tuning escutcheon, well lighted when the set is switched on, with a scale clearly marked in medium and long wavelengths.

The tuning is done with a neat concentric arrangement of two knobs, a main tuning knob working a two-gang condenser and a centre trimmer knob putting the finishing touch on the accuracy of the tuning when the wavelength is radically changed from one part of the scale to another. What I mean is that you do not necessarily have to touch the trimmer every time you alter the main tuning. When you do, the operation is definitely in the nature of a refinement to the tuning and, as such is, of course, very valuable under present ether conditions.

What I particularly like about the controls is the provision of an input volume control on the left and a reaction control on the right. With these two controls worked in harmony the selectivity is definitely above the average, because you can reduce the overall input and magnify with the reaction the station you want to the exclusion of those you do not want.

Just below the tuning knob is a lever for changing over from medium to long waves,



and that completes the layout of the controls on the front of the cabinet. On the right-hand side, looking from the front is the combined gramo-radio switch and pick-up volume control. On the left is the mains on-off switch.

At the back we find a variety of connections, for such accessories as an additional

### BRIEF SPECIFICATION

Makers: E. K. Cole, Ltd.


Price: 28 guineas.

Power Supply: A.C. mains (D.C. model available at 2 guineas extra).

Power Consumption: 60 watts with gramophone motor in action.

Type: Pedestal radio-gramophone.

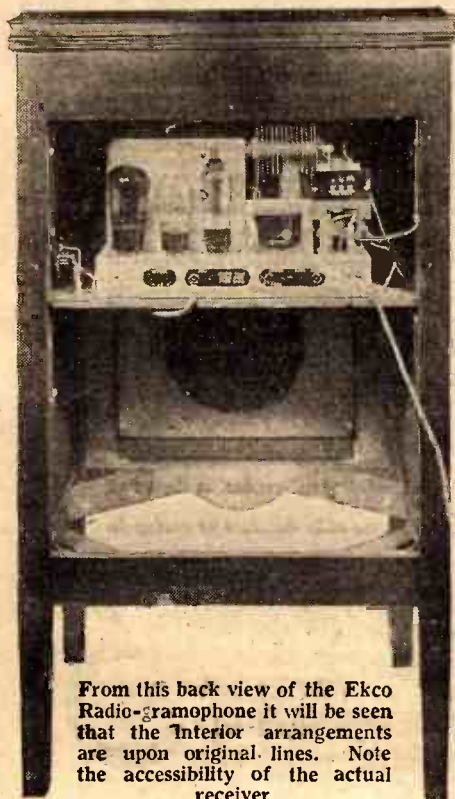Remarks: A really good radio-gramophone, giving pleasing quality of reproduction and a wide selection of programmes with quite straightforward operation.



From this back view of the Ekco Radio-gramophone it will be seen that the interior arrangements are upon original lines. Note the accessibility of the actual receiver

speaker and for the connection of the aerial and the earth. You do not have to use an aerial for the reception of the powerful locals or for the majority of the more powerful foreigners as there is an internal earth wire and as a further alternative the mains aerial can be used.

My first test was with the gramophone. I may say at once that I was more than satisfied with the overall tone obtained, at both loud and soft volumes. The bass has a pleasing depth and there is ample top-note response to retain the definition without introducing objectionable needle scratch.

At about the half-way position of the gramophone switch you can get enough volume for dancing in the average-sized room. At maximum setting of the volume there is slight overload.

Selectivity, if the input volume and reaction controls are properly used, is amazingly good for two tuned circuits. I was able to hear Mühlacker practically clear of London by reducing the input almost to zero and increasing reaction up to maximum. On long waves our old favourite, Radio Paris, is decisively clear of Daventry.

SET TESTER.



# QUIESCENT PUSH PULL KIT

**Mains Results  
from Battery Sets**

**DOUBLE OUTPUT**

**ALL-ELECTRIC VOLUME  
MOVING-COIL QUALITY  
50% H.T. SAVED**

**Save Pounds—Build it Yourself**

## PILOT GUARDIAN Q.P.P. 4-VALVE KIT

**FREE CONSTRUCTIONAL  
CHART SHOWS YOU HOW**

**S**TEP by step and wire for wire—you simply cannot go wrong. Success comes right from the start. **FULL-SIZE DIAGRAM** accompanied by the most detailed instructions. Every component, wire and terminal clearly identified. Without any technical knowledge you can build this amazing Kit Set with this straightforward Chart. Remember the Guardian Q.P.P. Set is the only one on the market that you can build yourself employing Screened-Grid and Quiescent Push-pull—the greatest advance in Battery Receiver design for years. This wonderful 1/- Chart is yours **FREE**. Fill in the Coupon **NOW**.



**B**UILD this latest Kit Set yourself and Save Pounds. Q.P.P. is the last word in Radio—first to be commercialised for the Home Constructor by Peto-Scott—Pioneers in Kits of Parts since 1919. Never before has such all-electric volume and moving-coil quality with screened-grid selectivity and range been possible with low priced small capacity H.T. Batteries.

**KIT "A"  
SEND ONLY**

**7/6**

Balance in 11 monthly payments of 7/3

**KIT 'A'**  
Complete Kit of Parts including ready-drilled panel but less valves, cabinet and meter. CASH or C.O.D. Carriage Paid.  
**£3.19.6** or 7/6 Deposit and 11 monthly payments of 7/3

**KIT 'B'**  
As KIT 'A', but with Valves, less cabinet and meter. CASH or C.O.D. Carriage Paid.  
**£6.18.0** or 12 monthly payments of 12/6

For GUARDIAN Meter, add 10/- to cash prices, or 11d. to each monthly payment.

PETO-SCOTT Oak Table Cabinet - 15/-

PETO-SCOTT Oak Console Cabinet 25/-

**We originated KITS OF PARTS in 1919**

**PETO-SCOTT CO. LTD. 77 CITY ROAD, LONDON, E.C.1.**

Dear Sirs,  
Please send me C.O.D./CASH/H.P. Guardian Q.P.P. Kit A with/without Guardian Meter. Kit B with/without Guardian Meter.  
for which I enclose £.....s.....d. CASH/H.P./DEPOSIT.  
**FREE CONSTRUCTIONAL CHART.**  
\*Strike out what does not apply.

NAME.....  
ADDRESS.....  
A.W. 4/3/33



**POST COUPON  
TO-DAY**

**OBTAINABLE ONLY DIRECT FROM PETO-SCOTT—CASH—C.O.D.—H.P.**

Don't Forget to Say That You Saw it in "A.W."






*A weekly review of new components and tests of apparatus conducted by J. H. Reyner, B.Sc., A.M.I.E.E.*
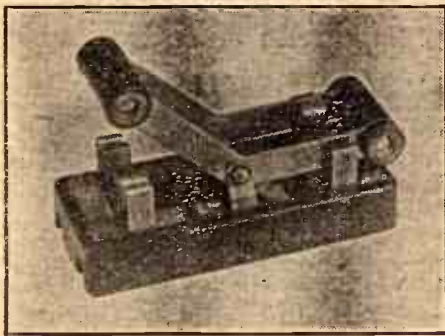
#### W.B. SAFETY SWITCH

WE have received for test a new type of double-pole double-throw switch which is intended for use as an aerial earthing switch. It is generally similar to the normal type of double-throw double-pole switch, but has two pairs of contacting arms instead of the usual one pair. These arms are arranged in the form of a wide V and thus the change over from one position to the other is accomplished by a movement of about 30 degrees only instead of the more usual 180 degrees. In this way a rapid



A handy double-pole double-throw switch made by W.B.

change in position is possible. The switch is built up on a small bakelite base measuring some 3 in. by 1½ in., the whole making a neat assembly. This switch is made by Messrs. Whiteley Boneham & Co., and retails at 1s.

#### HANDY SOLDER

AN interesting type of solder which we have tested recently is that made by Messrs. Andrew Findley of Glasgow, under the name of "Sme." This solder is in paste form and in order to use it, it is only necessary to coat the two surfaces to be joined with the paste and then to apply heat in any convenient way. We have found the material quite effective, several joints being made by means of it, and in every case the result was entirely satisfactory. This solder should prove a boon to those who are not experts with the soldering iron and even in certain circumstances to those who are.

The solder is retailed in small collapsible tubes costing 7½d. each, but it can also be obtained in 1-lb. tins, if desired.

#### EARL SPEAKERS


A NEW permanent-magnet loud-speaker which we have tested recently is that known as the "Earl" and made by Electric

clocks & Radio, Ltd. The speaker employs an E-shaped permanent magnet bolted to the back of the chassis which also carries the input transformer and the diaphragm. The diaphragm is of the moulded type and is mounted in an original fashion in that it is not rigidly fixed at the outer edge, but is



The Earl permanent-magnet moving-coil speaker, a performance curve of which is shown below

held lightly between the chassis and some thick felt pads which are also used to prevent rattling against the baffle. It is claimed that this method of arranging the diaphragm causes an increase in the response at the upper frequencies and as can be seen from the response curve reproduced herewith, the results obtained at around 5,000 cycles are appreciably above normal. The bass response also is good,

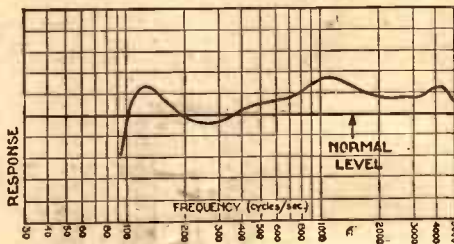

This curve of the Earl permanent-magnet speaker shows that there is a good overall response

there being actually a slight peak in the neighbourhood of 120 cycles. On actual signals the reproduction was good, the overall tone being very pleasant.

The input transformer provided has two ratios giving impedances at 512 cycles of 5,700 and 10,400 ohms respectively.


This speaker can be recommended.

#### YOUR SET ON THE SHORT WAVES

A BIG thing about short-wave reception, which many enthusiasts overlook is the fact that you don't need a special receiver to pick up the stations below 100 metres.

Useful short-wave converters and modulated oscillators are made by J. J. Eastick & Sons, and with an Eelex converter it is possible to use practically any broadcast band set on the short waves.

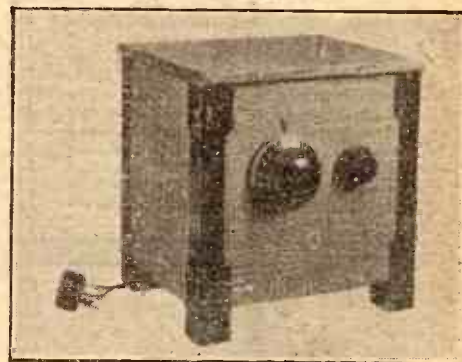One of the standard Eelex converters is shown by the accompanying photograph. It does not matter whether you have a mains or battery-driven set. There is a suitable converter available. The Duplex types can, in fact, be used either with a



An Eelex short-wave converter

mains or battery outfit. One- and two-valve models are made, and the chassis of the Duplex battery and mains types are available separately for building into an existing receiver.

Connecting one of these Eelex converters to an existing broadcast receiver takes only a few minutes. The aerial is disconnected from the set and joined to the aerial socket on the converter. From another socket which is marked "Output," a short lead is taken to the aerial terminal on a broadcast set.


The Duplex coils used have a two-range position covering 15-30 and 30-60 metres.

A handy booklet describing the whole range of Eelex converts can be obtained free on mention of "A.W." from Messrs. J. J. Eastick & Sons, Eelex House, 118 Bunhill Row, E.C. This book also gives an abridged list of short-wave stations, with their wavelengths and working times.

LET "A.W." SOLVE YOUR  
WIRELESS PROBLEMS



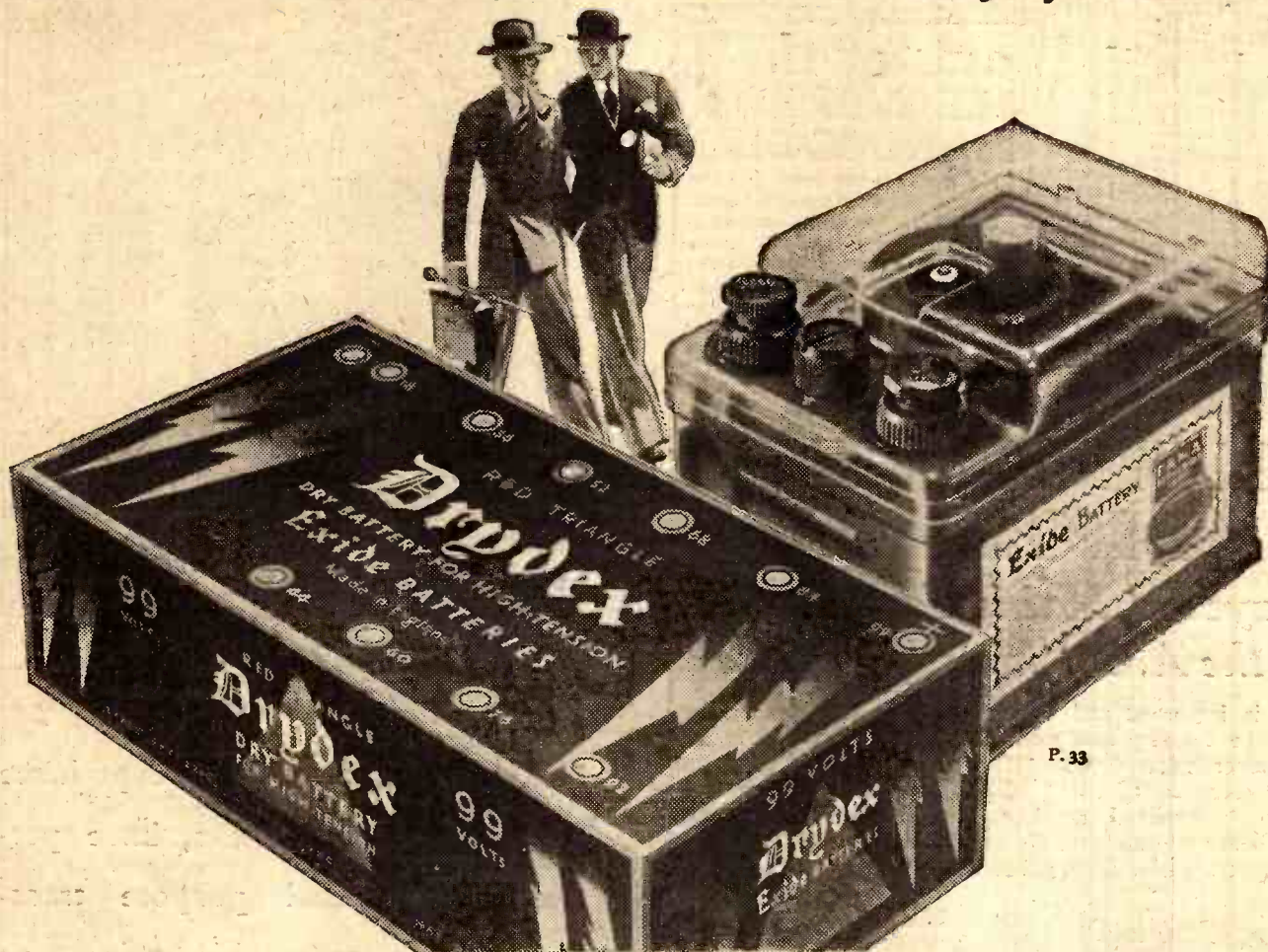**"STAMBOUL?** *Why, we get Stamboul on our portable when we like since we've had Exide and Drydex Batteries. Wonderfully clear, too."*



P. 33

EXIDE AND DRYDEX FOR FAMOUS SETS

	For L.T.	For H.T.
Burgoyne Portable Five	Exide LCJ4 11/6	Drydex H.1025 10/-
Columbia 380 Portable		
Super Het	" JZ3 14/-	" H.1056 12/-
K.B. 156 Portable	" JWX5 11/6	" H.1022 18/6
McMichael Duplex Four		
(SC)	" LBJ4 12/6	" H.1048 16/6
Pye "Q"	" LCA4 14/-	" H.1039 17/6

There is an Exide and Drydex Battery for every set  
The prices do not apply in the Irish Free State

# Exide AND Drydex

## BATTERIES FOR WIRELESS


Exide Batteries for wireless low tension and high tension. Drydex Dry Batteries for wireless high tension and grid bias. Also for torches, cycle lamps and bells.

Obtainable from Exide Service Stations and all reputable dealers

EXIDE BATTERIES, EXIDE WORKS, CLIFTON JUNCTION, NEAR MANCHESTER. BRANCHES: LONDON, MANCHESTER, BIRMINGHAM, BRISTOL, GLASGOW, DUBLIN, BELFAST

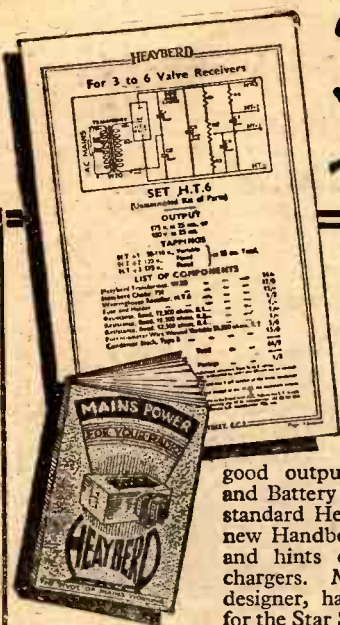Mention of "Amateur Wireless" to Advertisers will Ensure Prompt Attention





Take a leaf—


## out of the HEAYBERD HANDBOOK!

No matter what your problem in mains working—Heayberd, the mains specialists, can help you. Mains Units, with really good outputs, Mains Transformers, Chokes and Battery Chargers. The complete range of standard Heayberd apparatus is detailed in the new Handbook, together with circuit diagrams and hints on constructing mains units and chargers. Mr. Wilkins, the "Melody Ranger" designer, has chosen a Heayberd transformer for the Star Set of AMATEUR WIRELESS.

## EXCLUSIVELY SPECIFIED
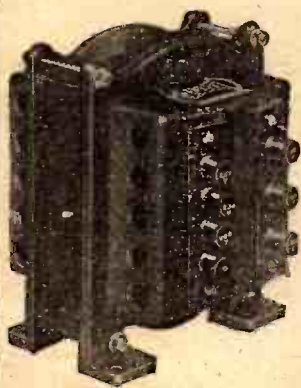
### Heayberd Mains Transformer for the A.C. "Melody Ranger"

For this important and popular receiver the components had to be the very best possible. That is why the mains transformer selected was HEAYBERD. Constructed to the specification of the "Melody Ranger" designer and exclusively specified by him for this famous receiver. What better testimony to the excellence and high standard of Heayberd Mains Components?



#### HEAYBERD TYPE "M.R." TRANSFORMER

Secondary Outputs :

230 + 230 v.	40 m/a.
2 + 2 v.	1 amp.
2 + 2 v.	4 amps.

PRICE .. .. 25/-

Guaranteed 12 months

Constructed by craftsmen from finest quality materials and thoroughly tested. Windings protected by special metal end-plates. Insulated screw-on terminals fitted. Extremely good voltage regulation, negligible temperature rise.



MONARCH OF THE MAINS.

10 FINSBURY ST., LONDON, E.C.2  
One Minute from Moorgate Station.

#### POST COUPON.


I enclose 3d. stamps for Handbook, "Mains Power for Your Radio," packed with hints, tips and 17 circuit diagrams on mains working.

Mr. ....

Address .....

..... A.W.

F. C. HEAYBERD & CO.

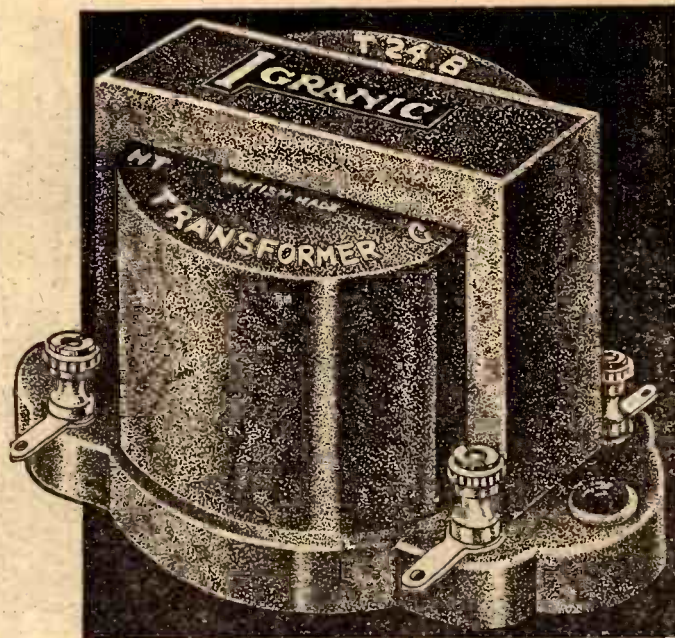

"I do not know what the life of a transformer is supposed to be, but this one has been in constant use for 7 years and has given about 10,000 hours' actual performance and is still going strong."

J.A.L., Liverpool. Extract from letter.

Igranic, with their long experience of wireless construction, have perfected a general purpose transformer at a reasonable price—you can be certain that it is the best of its kind. The Igranic T24B Transformer reproduces over the whole scale of musical frequencies. Ratios 3 — 1 and 5 — 1. Price 5/6.

Write to-day for fully-illustrated Catalogue No. D.184 of complete new range of Igranic Quality Components.

Igranic Electric Co., Ltd.,  
149 Queen Victoria Street, London, E.C.4

**IGRANIC COMPONENTS WILL BE THE MAKING OF YOUR SET**

CVS—56

Mention of "Amateur Wireless" to Advertisers will Ensure Prompt Attention



# WIRELESS MADE EASY

## SECTION

### Why Metal is Used for Modern Sets

ONE of the most obvious tendencies in set design, whether in the amateur field or in the factory, is the use of metal instead of wood and ebonite for the baseboard and panel respectively.

A natural question arises: *Why should we use metal?* The answer forms the subject of this little article.

If you, as a beginner, care to look back two or three years, you will find that *nearly all the older designs of sets made use almost exclusively of an ebonite panel and a wooden baseboard.*

#### The Modern Set's Layout

On comparing the sets of yesterday with those of the present time, you will notice that the outstanding feature of the modern set is the apparent simplicity of the baseboard layout.

In fact, except for a very few wires, you might think the modern set was almost devoid of inter-component connections! Actually it is not. Indeed, there are far more circuit complications in present-day sets than in sets of even two years ago.

#### Metal Acts as a Shield

The bulk of the connections are carried out below the chassis, as the main framework of the modern set is called. In effect, the low-frequency components are shielded from the super-structure components carrying the high-frequency current, such as the tuning coils and tuning condensers.

*It is this necessity for shielding that really accounts for the lavish use of metal in the modern set.*

Whereas sets of the early days had little if any real high-frequency amplification, the modern set depends for its success on a large measure of real high-frequency signal gain before the detector stage is reached.

#### How the Screen-grid Valve Altered Design

As soon as it was found possible to obtain really effective high-frequency amplification—namely, at the inception of the screen-grid valve—the whole

*technique of radio set design had to be altered.*

To-day nearly every set has its high-frequency amplifying valve, and in some way or other the grid circuit of the screen-grid valve is shielded from the anode circuit. The maximum amplification is now obtained without instability due to inter-action between these two circuits.

#### "Canned" Coils

Shielding can be done in many ways. In most home constructor sets, for example, where the practical limitations of blueprint presentation to some ex-

with some metal shielding material, often with a metal partition erected on the baseboard to afford further screening between one circuit and another.

#### The Metal Chassis

In factory-built sets the metal chassis is now practically standard. This consists of a metal deck on the top of which are fitted the usual tuning components and perhaps one or two others.

Below the deck are mounted the smaller parts, mostly of the low-frequency amplifier. It is underneath the

#### THIS WEEK: THE ABC OF THE PENTODE

By J. H. Reyner

#### TWO KINDS OF AMPLIFICATION Specially for Beginners

#### Avoiding "Hand-capacity" Effects

Apart from this all-important business of shielding the tuning circuits one from another, the use of metal is now very frequently decided upon for other reasons.

For example, in the now famous "Melody Ranger" four-valve set described in *AMATEUR WIRELESS* recently, a metal panel is used to reduce what is known as "hand-capacity" effects.

By earthing the panel, the approach of your hand, which is also partially earthed through your body, does not upset the tuning, and you are thus able to make critical adjustments.

This is of great value on the short-wave ranges of the set, where the slightest change in the condenser's capacity means a big change in the wavelength of the tuning circuit.


Another very practical advantage of metal for the set is the elimination of many of the connecting wires that would normally have to be taken over fairly devious routes.

As the metal is earthed, all component terminals that are connected to earth can be connected to the nearest point on the metal chassis—panel or baseboard—instead of being inter-connected by leads.

This saving of connections is of special value in the high-frequency side of the set. The elimination of earthed wires running parallel or near to high-frequency leads brings about a great increase in the overall stability.

Although the panel and baseboard layout is by no means finished, especially in amateur designs, it certainly looks as though metal will play an increasingly important part in the designs of the future.

### THE SIMPLEST METAL SCREENING

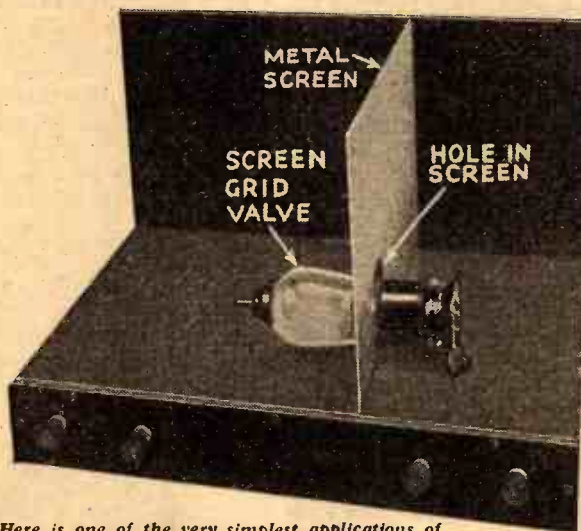

*Here is one of the very simplest applications of metal to an amateur layout. You will see that a metal partition is erected between one end of the screen-grid valve and the other, the idea being to shield the grid tuning circuit of this valve from the anode circuit and thus prevent inter-action. Usually with this type of metal shielding there would also be a metal lining for the baseboard and possibly the panel would be not of ebonite but of metal.*

tent dictate design policy, you will usually find the shielding done by means of metal "cans" round each of the tuning coils, with a gang condenser consisting of separate tuning condenser units shielded one from the other by a metal casing.

In simpler sets, where the coils are not screened, it is usual to line the baseboard with metal foil and to use a panel backed

chassis that most of the wiring is done.

The variable controls are easily mounted on brackets fitted to the metal chassis, so that their spindles can project through the cabinet into which the chassis is placed.

In some sets the tuning spindle is connected by a cord-drive to the tuning knob on the front or top of the cabinet.

ANOTHER SECTION FOR BEGINNERS NEXT WEEK



## ELEMENTARY WIRELESS COURSE

## THE A.B.C. OF THE PENTODE

**What is a pentode?**

It is a special form of output valve having a much higher sensitivity than the ordinary valve.

**What do you mean by sensitivity?**

Our object in the output valve is to obtain a large change in the anode current, to obtain which we apply a voltage between the grid and filament. A sensitive valve is one that gives us the anode current change we want with a very small applied voltage.

**What sort of voltages do we want?**

An ordinary triode output valve will give an output of approximately half a watt with a voltage change on the grid of about 36 volts. We should put 18 volts grid bias on the valve and then apply a signal which changes the voltages periodically from 0 to -36.

**What is a triode?**

An ordinary valve having three electrodes, the filament, the grid and the anode or plate.

**I remember now. Then a triode wants about 36 volts on the grid?**

Not necessarily. Sometimes we are content with a smaller power output than this which we can obtain with a grid change of only 9 or 10. I chose the output of half a watt for purposes of comparison, and as I said, the ordinary battery triode will require a total grid change of about 36 volts to give this output.

**Will a pentode need less?**

Distinctly so. With a pentode we can obtain an output of half a watt, under the same conditions of high-tension voltage, with a total grid swing of only 9 volts. That is, we should put  $4\frac{1}{2}$  volts bias on and cause the grid voltage to vary between 0 and -9.

**Then the pentode is four times as sensitive?**

In this particular case, yes. Generally speaking, a pentode is several times as sensitive as a triode in that it will give the same watts output for a much smaller voltage applied to the grid.

**What do you mean by "watts output"?**

I told you last week that the object of our output valve was to produce power. The unit of power is the *watt*, and it is customary to rate the power valves in terms of the watts output which they will give.

**Can you give me some example?**

I told you last week that with a loud-speaker of 2,000 ohms resistance, a current change of 10 milliamps would produce quite a good signal. This will



This week J. H. REYNER and the "Amateur Wireless" Staff help beginners to understand the pentode valve, which is a specialised type of power valve having five electrodes

actually correspond to a power of 0.2 watts, that is, one-fifth of a watt. We arrive at this in the following way:

The voltage developed across the loud-speaker is given by the product of the current and the resistance. We have 2,000 ohms and 10 milliamps, which gives us  $2000 \times 10/1000 = 20$  volts.

The power is the product of the voltage and the current, so that we multiply this voltage of 20 by the current, which gives us  $20 \times 10/1000 = 0.2$ .

**But if one-fifth of a watt is a good signal why do we want half a watt?**

To deal with the loud passages. On strong signals the power goes up very rapidly, and on some of the mains sets to-day a power output of 2 watts on the strong signals is nothing unusual. On ordinary normal volume, however, the power is only about one-fifth or one-quarter of a watt.

**You still have not told me what a pentode is.**

You have hardly given me a chance! However, you remember I told you that for high-frequency amplification we could obtain a greater magnification by using a screen-grid valve. The pentode is a form of screen-grid valve specially suitable for low-frequency amplification.

**I am afraid that does not convey much to me.**

Let us hark back to the screen-grid valve a moment. When we were

discussing that valve, I told you that we could not increase the amplification from an ordinary valve beyond a certain limit.

The sensitivity is increased by placing the grid wires closer together, but after a time this acts like a barrier between the filament and the anode, and prevents any anode current from flowing.

To overcome this difficulty we place another grid just outside the ordinary grid and place a fairly high positive voltage on this outer grid. The result is that the screening effect of the ordinary grid is neutralised and the electrons are pulled out of the filament as they should be and flow across the gap through the anode unhindered.

**I remember now. You can get amplification factors of several hundred?**

That is so. The amplification factor of the valve can be increased much beyond the point at which an ordinary triode would become useless, and we use this fact to make valves specially suitable for giving large amplification.

**Then is this a pentode?**


Not yet; actually it is a *tetrode*, because we have now four electrodes inside the bulb instead of the usual three.

**How many has a pentode?**

Five. Hence the name. It sounds very complicated, perhaps, but with modern valve construction it is quite easy to make robust valves having five or even more electrodes inside.

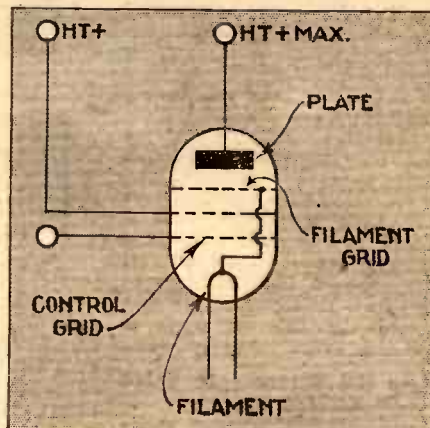**Why do we require so many electrodes?**

The story is rather interesting. With the screen-grid valve, the anode current variations are quite small, because we are dealing with only small signals. If



Here is the circuit symbol for a pentode power valve. Note that there are three grids and that one of them is connected to the filament. The remaining two have external connections, one being the usual grid and the other a screening grid connected to a point on the high-tension battery



the anode current changes by a large amount, however, as it will do in an output valve, we find that under certain conditions the electrons from the filament refuse to stay at the anode, but bounce off again and return to the screen grid.

To prevent this we insert still another grid just inside the anode. This is connected inside the valve to the filament, and its effect is to keep the electrons on the anode, once they have got there.


*It sounds very complicated to me.*

It is not simple, but in ordinary practice the why and wherefore does not arise. A pentode behaves in much the same way as an ordinary valve, but it has a much increased sensitivity.

To obtain this increased performance we have to insert a screen grid in between the normal grid and the anode, and this has to be connected to a suitable point on the high-tension battery. Actually there is still another "suppressor" grid inside the valve, but as far as the actual user is concerned it can be forgotten.

*Is a pentode used like an ordinary valve?*

Yes. The connections to the pins on

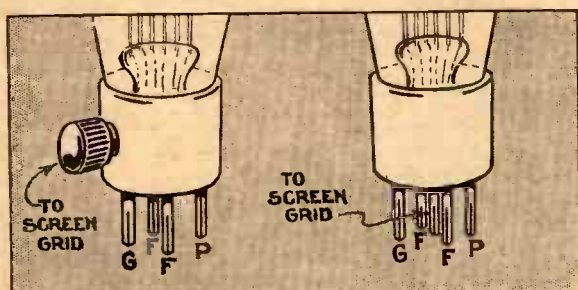

Two types of valve base used for pentode power valves. That on the left has a terminal on the side for the screening grid connection to the high-tension battery. On the right is a five-pin valve base, which does away with the terminal on the side and fits into a five-pin valve holder

the cap are the same as usual. There are the two filament pins, the grid pin and the anode pin in the customary positions, while the extra grid is connected to a side terminal on the side of the cap.


Sometimes, in order to do away with any loose leads, use is made of a fifth pin situated in the centre of the base. This particular form of base is used for certain types of valve specially designed to operate from the electric-light mains instead of batteries, and it can be conveniently applied to the pentode. In this case the centre pin is connected to the screen or priming grid.

*Where did you say this extra grid is connected?*

Simply to the high-tension battery. With a screen-grid valve we connect it to a point about 60 or 80 volts positive, but with the pentode we connect it to the full voltage, that is, 120 to 150 volts with the ordinary battery set.

*Do we still need an output transformer?*

It is still necessary to use a loud-

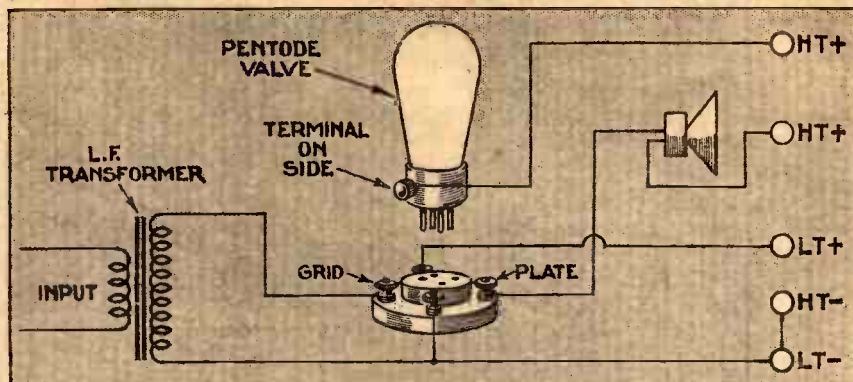

Skeleton circuit layout for a pentode power valve. Note that the terminal on the side of the base is taken to a tapping on the high-tension battery. Apart from this the circuit is quite normal, though in most well-designed sets there are tone-compensating components

speaker having the correct impedance for the particular valve if the reproduction is to be satisfactory, and although a speaker can be included directly in the anode circuit it is preferable as a general rule to use an output transformer as mentioned last week.

As with ordinary valves, the manufacturers quote the optimum loud-speaker impedance for the particular pentode, and by choosing a suitable ratio on the output transformer, the loud-speaker may be matched up correctly.

*Apart from its greater sensitivity, is the pentode just as good as an ordinary valve?*

If it is properly used, it is superior in every way. One important advantage is that it has a greater efficiency. Remember that our valve is taking a steady anode current of, say, 10

milliamps. If the H.T. battery is 150 volts, this is equal to a power of 1½ watts.

With a triode the maximum undistorted output of speech or music which we could obtain would be about 300 milliwatts, that is, 0.3 watts, which gives an efficiency of only 20 per cent. With a pentode operating under the same conditions we could obtain about 500 milliwatts corresponding to an efficiency of 33 per cent. Thus we make much more effective use of our batteries.

*Why should that be so?*

It is a matter of the valve characteristics. If we wish the anode current to be a faithful copy of the grid voltage the characteristics must be "straight." In practice it never is so and distortion is introduced.

With the ordinary valve the characteristic curves in the same direction all the time so that after the grid swing

increases our distortion gets worse and worse. With a pentode, on the other hand, the characteristic turns first one way and then the other, so that although some distortion is present, it is appreciably less and we are able to obtain more power from the valve.

*Is a pentode always used nowadays?*

No. For one thing it is more expensive while there are certain difficulties in getting it properly matched to the loud-speaker.

The impedance of the average loud-speaker is not constant but increases with frequency. With a triode this does not matter, because after a certain point the power output is constant, however large the impedance in the anode circuit.

With a pentode, however, there is no such limit, and the power output continues to increase as long as we make the impedance larger.

*What effect does this have?*

The upper frequencies are accentuated and the reproduction sounds shrill and harsh unless we take special steps to overcome the trouble.

*Can you get over the difficulty then?*

Yes. We place a condenser across the loud-speaker. At low frequencies (deep notes) this has no effect, but in the treble registers it has a two-fold effect.

First of all it reduces the effective impedance of the loud-speaker so that the power obtained from the valve is not so much. Secondly it shunts some of the current so that it does not all go through the loud-speaker, some of the current flowing through the condenser instead.

The net result is that the accentuation of the upper frequencies is checked and the reproduction once more sounds balanced and normal.

*Then is this scheme quite successful?*

Quite, and by the aid of a simple corrector of this sort we are able to obtain as good quality as with the triode, with the added advantages of extra sensitivity and better efficiency.

**NEXT WEEK : The Super-het**



# Two Kinds of Amplification!

Many beginners will welcome this simple explanation given in question-and-answer form of the real difference between high- and low-frequency amplification

*Tell me something about the difference between high- and low-frequency amplification.*

For a start, do you know what we mean by high-frequency amplification and low-frequency amplification?

*Well, I know that high-frequency amplification comes before the detector and low-frequency after it. Exactly what "high" and "low" mean, though, I do not know.*

Many listeners use these two words without really knowing what the difference between them is. Actually the broad division between high-frequency amplification before detection and low-frequency amplification after detection, though easy to understand, is not exactly accurate.

## Before the Detector

For, as a matter of fact, the signal you amplify before detection contains not only the high-frequency but also the low-frequency current.

After the detector, when the high-frequency current is bypassed to earth because it is no longer wanted to "carry" the low-frequency current, this low-frequency current is alone amplified.

*What beats me is why you have to amplify both before and after the detector. Wouldn't it be just as well to amplify at one end of the set—the high or the low?*

That is a commonly-asked question. There are many good reasons why we cannot do all the amplification either before or after the detector.

## Limitations of the Detector

Let us try to show you the most important reasons. Firstly, there is the detector, which suffers from two limitations.

For one thing it cannot work efficiently unless a certain minimum voltage is applied to the grid circuit. This means that unless you can amplify the signal before detection only the

powerful locals will be properly detected and the signals from foreign countries, which should be treated even better than the robust locals to make up for the long distance they have come, would be very poorly handled by the detector.

Secondly, the detector valve normally does not give much power output. It is true that the power-grid detector with its high anode voltage and low impedance gives more power output than in say the average three-valve, but even so this power output is small compared with the output obtained from a valve specially designed for giving power.

*Why must the detector give a large power output?*

In practice it does not have to do so, though the final process before the loud-speaker must be a power change. That is to say the loud-speaker works on a power change, and this is provided by varying the power supply.

*Couldn't the detector be used to vary that?*

No, because the impedance of the power valve is too high to provide sufficient current changes to work the loud-speaker efficiently.

## Separate Valve for Power

It is, in fact, essential to separate the functions of detection and power handling. We have to use two valves, one for the detection and the other, called the power valve, to translate voltage changes into power changes to work the loud-speaker.

*So that disposes of my simple little plan to do all the amplification before detection! Well, here's another point. Why not do all the amplification after the detector?*

We have already explained that this is not possible because the detector cannot work efficiently unless a certain minimum voltage is applied to the grid circuit.

*Sorry! I had forgotten that very important point. Tell me, though, is this the only reason for using amplification before detection?*

No, as a matter of fact it is not. We certainly need amplification before detection when tuning in fairly weak signals, but there are to-day so many strong signals, even from abroad, that on that score alone we might even dispense with high-frequency amplification.

## Don't Forget Selectivity

There is a much more important reason now for having high-frequency amplification, and that is for selectivity.

*How can high-frequency amplification possibly be connected with selectivity?*

Very intimately! Selectivity consists in passing the signal through a series of tuned circuits, each of which tends to differentiate more markedly between the wanted signal and all other signals that are not wanted.

In going through these tuning circuits the signal loses some of its original energy. It is necessary to "boost up" the signal between each of the tuning circuits, otherwise the signal arriving at the detector, even if it were moderately powerful when it first impinged on the aerial, would be too weak to operate the detector efficiently.

## Easy Sets to Operate

That explains why, in a set that is at once easy to operate and selective in its tuning, you usually find at least two stages of high-frequency amplification.

In simpler sets the selectivity is obtained partly by tuned circuits and partly by means of reaction.

It is quite easy to make a three-valve selective if you know how to operate reaction properly, but for non-technical listeners there is much to be said for a set that gets all its amplification by means of valves

and all its selectivity by means of tuned circuits.

*So that you have really advanced good reasons why both high- and low-frequency amplification are necessary in a good set?*

We think so. Let us briefly summarise these reasons. Firstly, low-frequency amplification is needed because we have eventually to work the loud-speaker with a varying low-frequency current, which we cannot obtain at sufficient amplitude from the anode circuit of a detector valve.

Secondly, we need high-frequency amplification because the detector will not work properly with a very weak input, and because even strong signals lose energy in passing through the several tuned circuits now needed to give adequate selectivity for modern conditions. A.H.


## YOUR LOUD-SPEAKER

**W**HAT type of loud-speaker do you use? There are many types but probably there are only two in common use to-day. One is the moving-iron, also called the balanced-armature, and the other is the moving-coil.

Cheap speakers usually employ the moving-iron principle, which enables a good response of the middle and top frequencies to be obtained and provides a good volume output from a fairly small input.

The only real deficiency of the moving-iron is its lack of bass-note reproduction. With small sets this is not really a great drawback, because at the volume output of such sets the intensity of the low-note output would be small anyway.

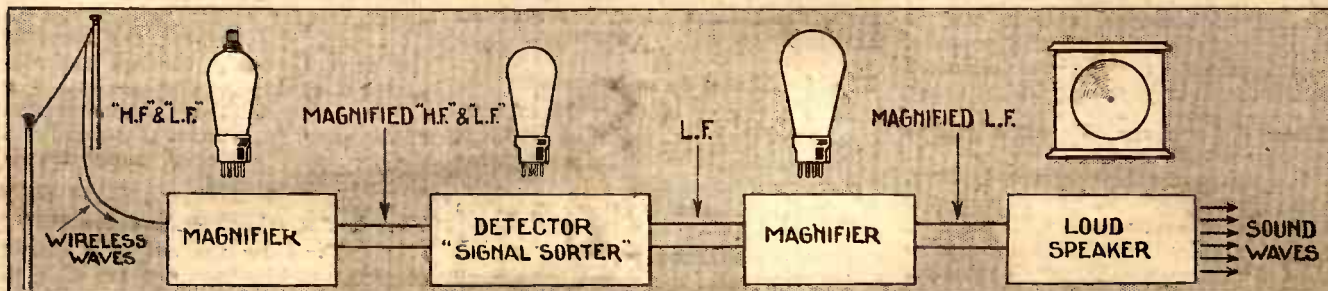
The moving-coil loud-speaker is now available in cheap chassis form, with a permanent-magnet instead of a field magnet that in the old days always had to be energised by some external means, such as the electric-light mains or an accumulator.



A simple diagrammatic sequence showing the stages in the process of reception at which high- and low-frequency amplification are introduced. It will be seen that before detection the wireless-wave energy consists of both high- and low-frequency amplification and that after detection there is only low-frequency current, the high-frequency current having been filtered out by the detector


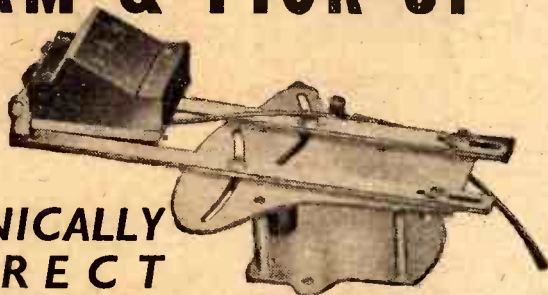
# PERFECT TRACKING WITH THE SIMPSON ARM & PICK-UP



## TECHNICALLY CORRECT MECHANICALLY PERFECT!

A Simpson Straight Track Arm and Pick-up is the only instrument which will give you perfect gramophone reproduction through your radio set. Here are a few points which show that the Simpson has no equal in value at the price:—

- |   |                             |
|---|-----------------------------|
| 1. Record wear minimised.                             | 4. Life of records doubled. |
| 2. 100% Straight Track ensured.                       | 5. Tone natural and pure.   |
| 3. Needle scratch eliminated.                         | 6. Fits any gramophone.     |
| 7. A scientifically designed and produced instrument. |                             |
| 8. Incorporates Automatic Stop.                       |                             |

Consider these points in comparison with others and your choice of the Simpson will be fully justified.

# 32/6

Fill in coupon below for the Free Booklet describing this Pick-up and Arm.

## COMPLETE

# SIMPSON'S SYNCHRONOUS MOTOR & TURNTABLE!

## CONSTANT SPEED

## NOTHING TO WIND

## 2½" DEEP



No winding the Simpson Synchronous Motor and Turntable, a flick of the finger starts or stops it, and with an almost negligible electricity consumption revolves at a constant speed of 78 (correct speed) with perfect silence. Consider the following points when purchasing an electric gramophone motor and see why the Simpson is supreme:—

- |                               |  |
|-------------------------------|--|
| 1. Only 2½ in. deep.          | 5. Sizes 10 in. and 12 in.               |
| 2. Nothing to go wrong.       | 6. Costs less than ½d. per week to run.  |
| 3. Fits any gramophone.       | 7. Goes by itself.                       |
| 4. Takes five minutes to fix. | 8. Constant speed of 78 (correct speed). |

Buy yours to-day! It is amazing value, and can be obtained from all good retailers for 39/6.

# 39/6

Fill in coupon below for your Free copy of booklet describing this motor.

## COMPLETE

# FREE

SIMPSON'S ELECTRICALS, LTD.,  
Grange Road, Leyton, London, E.10

To interested readers of "Amateur Wireless" we shall be pleased to send our illustrated Folder containing all technical details on receipt of completed coupon.

NAME.....

ADDRESS.....

# THERE'S MONEY IN THIS FASCINATING WORK!



Any  
Intelligent  
Man or Woman  
CAN  
MAKE THESE  
AND  
MAKE  
MONEY

HERE'S fascinating work which any intelligent man or woman can do! Free from all drudgery, it is at once an absorbing Hobby and a MONEY-MAKING SPARE-TIME BUSINESS!

This work is in connection with the Wireless and Electrical Industry—a business which everybody knows is going ahead by leaps and bounds. And as it enlarges so does your scope for earning still bigger profits enlarge with it.

## NO PREVIOUS KNOWLEDGE IS NECESSARY

No expensive plant or machinery is required. Just a few simple hand tools and presses are all you need. A start can be made on your kitchen table and the work is so simple that even the family can help you.

## PROFITS GUARANTEED!

If necessary, we will take sufficient of your output to guarantee you a weekly profit, provided your work reaches the required standard, which is easily attainable. AND we will train you FREE as long as required.

## FREE PARTICULARS HOW TO START

Do not let an opportunity like this pass by. Write at once for FREE PARTICULARS, telling you how you can start RIGHT AWAY to turn your spare hours into Golden Hours of Profit and Pleasure! Here is a way to defeat the bogey of Depression and to lift yourself to better times!

ONE  
MAN  
EARNED  
£960  
IN  
SPARE  
TIME

Send this COUPON TO-DAY

To Mr. V. ENGLAND-RICHARDS,  
THE ENGLAND-RICHARDS CO.,  
LTD., 1225, King's Lynn, Norfolk.

Please send me Free Particulars of how to start the Money-Making Business you describe and PROOF of how others are making money. I enclose 2d. stamp for postage.

Print your name and address boldly in capital letters on a plain sheet of paper and pin this coupon to it.

"Amateur Wireless," 4/3/33.

FOR  
EXTRA  
CASH



## PIONEERS &amp; LEADERS



ALWAYS

The Sensational  
'MANSFIELD'

**PERMANENT MAGNET  
MOVING-COIL SPEAKER**  
is SPECIFIED for the  
**MELODY RANGER** and  
the **FURY FOUR** because

THE revolutionary 'Mansfield' Magnetic System gives greater power from a smaller magnet. It has made possible in a moderate priced moving-coil speaker a performance at least equal to very high priced instruments. The magnetic flux is concentrated where the work is done and there is no loss of magnetism. The magnet is 30 per cent. more efficient than good cobalt steel of same weight and 10 per cent. more efficient than chrome steel of three times the weight. Write for leaflets, then HEAR it at your dealers—you will be AMAZED.

'Mansfield' Senior - - - 42/-  
(including tapped transformer)

Handsome Oak Cabinet to suit, 25/-.

Advert. of

**WHITELEY ELECTRICAL RADIO CO., LTD.,**  
Dept. A., RADIO WORKS, MANSFIELD, NOTTS.  
E. W. G.

## FULLER

## 120 Volt H.T. Accumulator

Accumulators are best for H.T. power, because of the continuous supply of smooth, silent current they provide for the smallest and largest of sets. We can supply 120-volt banks of H.T. Accumulators, 6,500 m.a.-hour capacity, carriage paid for 7/6 deposit and 12 monthly payments of 7/6, or £4 1s. cash. Send for your set now and be free from battery trouble and mains hum. During the past two years we have supplied hundreds of these units to satisfied customers.



120-volt unit

**LESLIES RADIO SERVICE,**  
9 SPRINGFIELD PARK CRESCENT - CATFORD, S.E.6  
Phone: Hither Green 1585 or LESLIE PLACE, FALKIRK

## 2/9 VALVES 3/6

Each **BRITISH MADE—POST FREE** Each  
210 H.F. Simply tell us your Set and we 230 Super Power.  
210 L.F. will supply the correct B.H. And also the  
210 Det. Valve. All our valves are famous 220 S.G.  
220 P. fully tested. at 4/- each!

MONEY RETURNED IF NOT SATISFIED. Send to-day to:—  
The B.H. Valve Co., 8 Station Road, Finsbury Park,  
London, N.4. Phone - Archway 3119: Trade Enquiries Invited

In My  
Wireless  
Den

Weekly Notes: Theoretical and Practical

## PENTODES AND TONE

IT is usual to connect a resistance and condenser across the output circuit of a pentode for the purpose of reducing the relative strength of the higher notes.

Some people say for bringing up the bass, but in actual fact you cut off some of the higher notes. If you increase the capacity of the condenser the higher notes are further reduced.

The same effect is brought about by lowering the value of the resistance. If the resistance be short circuited, leaving only the condenser across the circuit, the higher notes may be cut off entirely.

The best practice is to proportion the resistance and condenser to suit the valve and the loud-speaker. Usual values are .015 microfarad and 15,000 ohms, but it is surprising what a wide range of valves may be tried and be found to work satisfactorily.

The chief thing to bear in mind is that the condenser must be capable of standing up to high voltages, actually several times the normal high-tension. Many a user has found to his cost that the condenser may break down if it is not well made.

## THESE ELECTROLYTICS

ELECTROLYTIC condensers have been employed in sets for a period long enough for us to state that they are satisfactory and economical.

There are the two types, the wet or aqueous and the dry. Both are useful and have relative advantages.

In the dry type there are many patterns of various voltage ratings and capacities. One example is rated at 50 microfarads, 12 volts; there are other of 8 microfarads, 200 volts, and so on. The chief point is to choose the pattern which will always withstand the voltages developed in the circuit.

These voltages are not always so small as they may seem. There are sometimes surge voltages. In mains sets the valves heat up slowly and, therefore, take a few seconds to arrive at their normal working state. Meanwhile the condensers may be subjected to much more than the steady working voltage which we know exists while the set is running. These points must be taken into account when choosing condensers, or breakdowns may occur.

## DETECTOR WORKING

A DETECTOR valve having a resistance in its anode circuit should usually be given the maximum voltage available.

There will be a drop in voltage across the resistance and the actual voltage at

the anode of the valve will be less than the total by the amount of the drop.

Thus if the anode circuit resistance is 20,000 ohms, and the current is 2 milliamperes, the voltage drop is 40. Now with a battery voltage of 120, the anode will have a voltage of 80.

This is usually about right. Sometimes the current is heavier when the drop is greater, or the resistance may be more than the value assured.

It is necessary to add the decoupling resistance to the anode resistance proper, when one is used as in a resistance fed transformer circuit.

If the anode voltage is too low the valve will not handle a normal signal without distorting it, and the output suffers as well. A valve may be a more sensitive detector when the anode voltage is low, but it cannot deal with such large inputs as when the voltage is higher.

## ATLAS Q.P.P. MAINS UNIT


MAINS units for use with quiescent-push-pull receivers are now being manufactured by H. Clarke & Co. (Manchester), Ltd. Several models are available, and a typical unit of the Q.P.P. range is shown by the accompanying photograph. The model Q.P.24 is for 200-250-volt A.C. mains, and has three H.T. tappings. The



The new Atlas Q.P.24 mains unit, specially designed for Q.P.P. receivers

average output is 150 volts at 12 milliamperes, but peak outputs up to 20 milliamperes are passed without any appreciable voltage drop, owing to the extremely fine voltage regulation. The cash price of the Q.P.24 is £3 12 s. 6d. The Q.P.26 unit has a similar specification to the Q.P.24, but is fitted with a trickle charger with an output of .5 amperes. The cash price of this model is £5. A D.C. mains unit for Q.P.P. receivers is available, and this is the model D.Q.P., the cash price of which is £2 5s. It gives the same output as the Q.P.24 unit. Easy-payment terms are available for all these units, and full details can be obtained free on mention of "A.W." from Messrs. H. Clarke & Co. (Manchester), Ltd., George Street, Patricroft, Manchester.



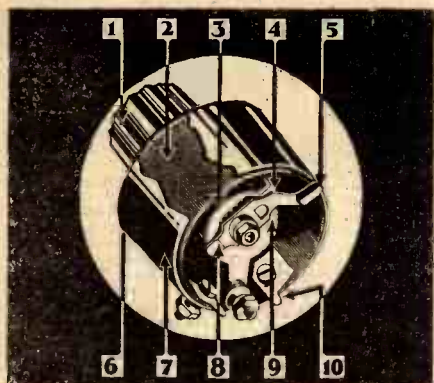

# Specified FOR THE JAMES PUSH-PUSH THREE

TYPE 2  
With  
MAINS  
SWITCH  
Price

WATMEL 50,000 ohm  
POTENTIOMETER

8/6

This resistance meets with requirements for a volume control which will have an equal variation of volume for the rotation of the knob. This is specially important for the control of the grid bias of the new Variable-Mu Valves. The carrying capacity of the type specified is 15 milliamperes. Our policy this year is to specialise in Potentiometers and Volume Controls of all types. You can, therefore, be certain when purchasing a Watmel Potentiometer, that you are obtaining the very best from a firm that is concentrating on this type of component.

## NOTE THE POINTS:—

1. Polished Pointer Knob.
2. Wire-wound Former. (N.B.—The resistance is wire, NOT compound with wire contacts, and is specially wound on a tapered former.
3. Insulating bush to insulate spindle from panel.
4. Positive Stop.
5. Contact finger—Phosphor Bronze.
6. The hole fixing—brass bearing bush resulting in perfect bearing.
7. Bakelite case protects winding.
8. Back self-cleaning contact.
9. Large contact plate.
10. Stops at end of wiring.

This resistance is specially wound on a tapered former which gives a perfect square-law reading. This is the first resistance of its kind.

If you have any difficulty in obtaining Watmel Components write direct to us and your order will be executed within 24 hours. Write for catalogue.

We are at the B.I.F., STAND 61, "Hall of Music."



Watmel Wireless Co., Ltd., Imperial Works - High Street - Edgware  
Telephone: Edgware 0323

## "THE JAMES 'PUSH-PUSH' (Q.P.P.) THREE"

(Continued from page 373)

kept down to the fairly low value of 5,000 ohms. The high-tension lead from the anode circuit of this valve is marked H.T.4 and should be taken to about 120 volts.

In the output circuit two pentodes are used. The smaller pentodes are satisfactory.

A bias of from 7.5 to 9 volts is needed and it should be noted that the bias is much larger than is normal for these valves as used in the ordinary way. The object is to reduce the standing current (no signal) to a small value, such as 2-3 milliamperes, for the pair of valves. The anode circuit is joined through H.T.+4 to the highest voltage of the battery, about 120 volts.

There are now the two pentode screen leads to be connected and one should be taken to the tap below the maximum, such as 115 volts. The others can also be taken to this tap for the time being. Tap H.T.+1, for the screen of the screen-grid valve, should be taken to the maximum allowable voltage for the type of valve, such as 80 volts.

### SUITABLE VALVES FOR JAMES "PUSH-PUSH (Q.P.P.) THREE"

Make	H.F.	Detector	Output
Mullard	PM12V	PM1HL	(2) PM22A
Cossor ..	220VSG	HL210	PT220
Marconi	VS2	HL2	PT2
Osram ..	VS2	HL2	PT2
Mazda ..	S215VM	HL2	Pen220
Six Sixty	SS215VSG	SS210HL	SS230PT
Lissen	SG215V	HL210	PT225
Micromesh	—	HLB1	PenB1
Triotron	—	SD2	P215
Tungsram	—	PD220	PP230
Eta ..	—	BY1814	—

The adjustments are really quite easy and can be made quickly. A moving-coil loud-speaker is recommended.

You cannot go far wrong as the components and the circuit are specially arranged, but the setting of the bias and the screen voltages have to be carried out by the user. In many cases the two pentode screens can have the same voltage as the two valves will normally be near enough alike to give the desired results.

Incidentally, larger pentodes than those recommended can be used, but the bias must be increased to reduce the standing current for the pair of valves to from 3 to 4 milliamperes and the output transformer must suit them.

### A Meter for 12 to 2,000 Metres

It should be noted that in the components for the "Meter for 12—2,000 Metres," described last week, the values of the two large condensers were given incorrectly. These should be .01 mfd. as shown on the blueprint, and not .25 mfd. as stated.

In the Wilkins & Wright announcement of "A.W." for February 25, the variable condensers specified for the "James Push-push (Q.P.P.) Three" were incorrectly shown. The correct Utility condensers for this set are the disc-drive type W318 (price 13s. complete) as specified by W. James.

Easy Terms

FIRST IN 1924  
FOREMOST TO-DAY

MELODY RANGER

Easibilt KIT

WITH LISSEN COILS

COMPLETE KIT OF TESTED AND MATCHED PARTS, including the specified set of LISSEN COILS and ready drilled engine turned Aluminium panel, but less valves and cabinet. CASH or C.O.D. Carriage Paid, £5/5/0. Balance in 11 monthly payments of 9/6. See "A.W." page 225, Feb. 4th, 1933, for full details.

ROLA Q.P.P. P.M. MOVING-COIL SPEAKER. With Input Transformer. Cash or C.O.D. Carriage Paid, £2/9/6. Balance in 11 monthly payments of 4/6. CELESTION Q.P.P. 19A MOVING-COIL SPEAKER. With Input Transformer. Cash or C.O.D. Carriage Paid, £2/10/- Balance in 11 monthly payments of 4/7.

SEND 2/6 Just pay further 2/6 on delivery and balance in 5 monthly payments of 5/6. For NEW PETO-SCOTT GUARDIAN Q.P.P. MOVING-COIL SPEAKER with input transformer. Cash or C.O.D. Carriage paid, 29/6.

SONOCHORDE SN. Q.P.P. MOVING-COIL SPEAKER. With Input Transformer. Cash or C.O.D. Carriage Paid, £3/7/6. Balance in 11 monthly payments of 6/3. W.B. PM4 Q.P.P. MOVING-COIL SPEAKER. With Input Transformer. Cash or C.O.D. Carriage Paid, £2/2/-.

Balance in 7 monthly payments of 5/9. ATLAS Q.P.P. (A.C.) H.T. ELIMINATOR. Specially designed for Quiescent Push-Pull Output. Cash or C.O.D. Carriage paid, £3/12/6. Balance in 11 monthly payments of 6/10. LISSEN "SKYSCRAPER 3." Chassis model with (Lissen) S.G. Detector and Pentode valves. Cash price, £4/9/6. Carriage paid.

Balance in 11 monthly payments of 8/3. LISSEN "SKYSCRAPER 3" KIT, with Lissen valves, Walnut Console Cabinet, and special Balanced Loud-speaker. Cash price, £6/5/0. Carriage paid.

Balance in 11 monthly payments of 11/6. TELSEN ASTRALA 3. Complete Kit of Parts with Blueprint and Instructions, but less valves and cabinet. Cash Price, £1/19/6. Carriage Paid. Balance in 7 monthly payments of 5/6.

SPEAKERS, ACCESSORIES, KITS or PART KITS. Cash, C.O.D., H.P. Carriage paid to your home. Orders value over 10/- sent carriage paid or C.O.D. charges paid.

SEND FOR LATEST LISTS FREE.

ATLAS ELIMINATOR. Type A.C.244. Three tappings, S.G., detector and power. Output: 120 volts at 20 m/a. Cash Price, £2/10/6. Carriage Paid.

Balance in 11 monthly payments of 5/6. BLUE SPOT UNIT AND CHASSIS. Type 99 P.M. Including matched transformer. Cash Price £2/19/6. Carriage Paid.

Balance in 11 monthly payments of 5/6. ROLA PERMANENT-MAGNET MOVING-COIL SPEAKER F.6. With Universal tapped input transformer. Cash Price, £2/8/6. Carriage Paid. Balance in 11 monthly payments of 4/6.

TO NEW TIMES SALES CO. 56 Ludgate Hill, London, E.C.4.

Please send me..... for which I enclose £ s. d. Cash/Deposit

Name .....

Address .....

A.W.4/3/33

EVERYTHING CARRIAGE PAID



## H.T.

INVESTMENT or EXPENSE?

## Battery that Lasts Years

WRITE FOR FREE BOOKLET AND  
FIGURE OUT WHAT YOU CAN SAVE

"I have been using my Standard Battery three years. It is trouble free, always ready and speaks for itself. What more can one require?" (R. H., Stoke-on-Trent.)

Here's another testimonial giving facts beyond dispute. You WILL save money by installing STANDARD H.T. once for all. You WILL get better reception. The STANDARD battery recharges itself when the set is shut down, being a special adaptation of the famous Leclanché principle—and it is PERMANENT because the eventual replacement is merely a matter of changing cartridges (which you do yourself) at 3d. each. We sell direct in order to Guarantee your satisfaction.

Send a postcard for our Free Booklet. It shows how to end battery expense and make it a permanent investment. Do it now, before you forget.

## Model H.5

## 126 VOLT STANDARD BATTERY

No. 3 size. 84 cells, 12,500 milliamp capacity.

Cash Price **37/8** or delivered on 1st payment of **5/4**

STANDARD BATTERY Co., Dept. A.W.  
184-188 Shaftesbury Avenue, London, W.C.2



## "REPAIRS? SEND THEM TO ME"

When the repair has been O.K'd by me, you can be sure your component is as good as new. All repairs are laboratory tested and guaranteed for 12 months. Any make of speaker unit, Transformer or Pickup 4/-; Blue Spots 5/-; Moving Coils from 5/-; Address your repairs to: REPAIR DEPT. A. WEEDON POWER LINE RADIO CO., 186, EARLHAM GROVE, LONDON, E.7; (Phone, Maryland 4344)

## RADIO SUPPLIES

Send your list of Radio needs for our quotation. Kits, Parts, Sets, etc. Everything in Radio stocked. Prompt delivery; seven days' approval. Catalogue free. Taylex and Standard Wet H.T. replacements stocked.

A. TAYLOR, 67 STUDLEY ROAD, STOCKWELL, LONDON.

LET "A.W." SOLVE YOUR  
WIRELESS PROBLEMS.

## BROADCASTING STATIONS

Broadcasting Stations classified in order of wavelengths. For the purpose of better comparison, the power indicated is that of the carrier wave.

Kilo-	Station and	Power	Kilo-	Station and	Power	Kilo-	Station and	Power
Metres	Call Sign	(Kw.)	Metres	Call Sign	(Kw.)	Metres	Call Sign	(Kw.)
13.97 21,470	Daventry (GSH)	15.0	283	1,058	Innsbruck	0.5	472	635.6
16.88 17,770	Daventry (GSG)	15.0	283	1,058	Berlin (E)	0.5	472.4	635
19.737 15,200	Zeesen (DJB)	8.0	283	1,058	Magdeburg	0.5	480	625
19.82 15,140	Daventry (GSF)	15.0	283	1,058	Stettin	0.5	483	621.1
25.28 11,865	Daventry (GSE)	20.0	284.8	1,053	Radio Lyons	1.0		
25.4 11,810	Rome (2RO)	15.0	286	1,049	Montpellier	0.8	488.6	614
25.53 11,750	Daventry (GSD)	20.0	288.5	1,040	Bournemouth	1.0	495.8	605
81.20 9,615	Lisbon (CTIAA)	2.0	288.5	1,040	Plymouth	0.12	501.7	598
31.3 9,585	Daventry (GSC)	20.0	288.5	1,040	Scottish National	50.0	509	590
31.31 9,580	Radio Nations	20.0	291	1,031	Vilpuri	13.0	509.3	589
31.38 9,560	Zeesen (DJA)	8.0	293	1,022	Kosice	2.5	518.7	578.4
31.51 9,520	Skamleback	0.5	293.7	1,021.5	Limoges (PTT)	0.7	525.4	571
31.55 9,510	Daventry (GSB)	20.0	296.1	1,013	Huizen	20.0	532.9	563
32.26 9,300	Rabat	0.5	298.8	1,004	Tallin	11.0	537.6	558
40.3 7,464	Radio Nations	20.0	301.5	995	North National	50.0	541.5	554
43.75 6,865	Vitus/Paris	0.3	304.3	986	Bordeaux (PTT)	13.0	550.5	545
45.38 6,611	Moscow	12.0	306.8	978	Zagreb (Agram)	0.75	555.5	542
49.4 6,070	Vienna (UOR2)	2.0	307.5	975.8	Falun	0.5	559.7	536
49.59 6,050	Daventry (GSA)	20.0	308.3	972.9	Vitus (Paris)	1.0	559.7	536
49.83 6,020	Zeesen (DJC)	10.0	309.9	968	Cardiff	1.0	564.4	531.5
50.0 6,000	Moscow	20.0	312.8	959	Cracow	1.5	564.8	531.1
52 5,769	Prague	0.5	313.9	955.6	Genoa (Genova)	10.0	565	531
207.3 1,477	Sersing	0.2	315.8	950	Marselles	1.6	566	530
207.5 1,445	Pez	3.0	318.8	941	Naples (Napoli)	1.5	573.2	523.3
209.7 1,430.4	Magyarovar	3.0	318.8	941	Sofia (RodnoRadio)	1.0	574.7	522
211.3 1,420	Newcastle	1.0	319.7	936	Dresden	0.25	587.1	511
211.3 1,420	Antwerp	0.4	321.9	932	Goteborg	10.0	680	442
214.3 1,400	Aberdeen	1.0	325	925	Breslau	60.0	719.4	416.6
214.3 1,400	Warsaw (2)	1.9	328.2	914	Poste Parisien	60.0	746.2	402
216 1,391	Chateaufort (EL)	2.0	331.6	904	Milan Vigentino	20.0	759.5	395
217.1 1,382	Konigsberg	0.9	332.2	902.9	Poznan	15.0		
217.1 1,382	Brussels (Conf.)	0.25	338.2	887	Brussels (No. 2)	15.0	779.2	385
218 1,373	Salzburg	0.5	341.7	878	Brunn (Brno)	35.0		
218.5 1,373	Plymouth	0.2	345.2	869	Strasbourg (PTT)	11.5	825	363.6
219.6 1,366	Blinche	0.3	348.6	860.5	Barcelona (EAI)	8.0	833	360.1
220 1,363.7	Beziers	0.5	351.8	853	Leningrad (RV70)	15.0	845	355
223.2 1,344	Swedish Relays	1.2	352.1	852	Graz	7.0	848.7	353.4
224.4 1,337	Cork (6CK)	1.0	355.8	843	London Regional	50.0	887.3	340
225.9 1,328	Fecamp	10.0	360.5	832	Muhlacker	60.0	895	350
227.4 1,319	Flensburg	0.5	363.6	825	Algiers (PTT)	16.0	937.5	320
230.6 1,301	Malmö	1.2	365.5	820.7	Bergen	1.0	967.9	310
231.8 1,294	Kiel	0.25	367.2	817	Frederikstad	0.7	1,000	300
232 1,285	Liege (Wallone)	0.3	368.1	815	Bolzano	1.0	1,034.5	290
233.4 1,285	Lodz	2.2	368.1	815	Helsinki	1.5	1,043	287.6
236 1,270.9	Kristiansand	0.5	369	813	Seville (EAI5)	1.5	1,071.4	280
236.4 1,269	Bordeaux (S.O.)	3.0	370.1	810	Radio LL (Paris)	0.8		
237.2 1,265	Nîmes	1.0	372.2	806	Hamburg	1.5	1,075	279
238.9 1,256	Nurnberg	2.0	376.4	797	Scottish Regional	50.0	1,107	271
240.1 1,249	Stavanger	0.5	381.7	788	Lvov	16.0	1,153.8	260
241.3 1,243	Liege	0.3	385	779	Radio Toulouse	60.0	1,170	256
242 1,238	Belfast	1.0	385	779	Stalino (RV26)	10.0	1,190.5	252
244.1 1,229	Basle	0.5	389.6	770	Leipzig	75.0	1,200	250
245.9 1,220	Berne	0.5	392	768	Archangel (RV36)	10.0	1,200	250
245.9 1,220	Cassel	0.25	394	761	Bucharest	12.0	1,239.7	242
245.9 1,220	Linz	0.5	398.9	752	Midland Regional	25.0	1,252.6	239.5
245.9 1,220	Swansea	0.12	403.8	743	Sottens	25.0	1,260.5	238
247.7 1,211	Trieste	10.0	408.7	734	Katowice	12.0	1,304	230
249.5 1,202.6	Juan-les-Pins	1.0	413.8	725	Athlone	60	1,354.4	221.5
250 1,200	Prague (Strasnice)	5.0	416.4	720.5	Radio Maroc		1,380	217.4
250 1,200	Radio Schaebeek	0.3			(Rabat)	6.0		
252.9 1,186	Barcelona (EAI15)	6.0	419.5	715	Berlin	1.5	1,411.8	212.5
253.4 1,184	Gleiwitz	5.0	424.2	709	Madrid (Españ)	2.0	1,445.7	207.5
255.1 1,176	Toulouse (PTT)	0.7	424.2	709	Madrid (EAI7)	3.0	1,481	202.5
256.7 1,168	Horbj	10.0	424.3	707	Moscow (RV39)	10.0	1,538	195
259.3 1,157	Frankfurt-a-M.	17.0	430.4	697	Belgrade	2.8	1,554.4	193
259.3 1,157	Trèves	2.0	431	696	Pareda (CTIGL)	1.5	1,620	185
261.6 1,147	London National	50.0	435.4	689	Makhatch-Kala	100.0	1,634.9	183.5
263.8 1,137	Moravska-Ostrava	11.0	435.4	689	Stockholm	55.0	1,685.3	178
265.7 1,129	Lille (PTT)	1.3	441.2	690	Rome (Roma)	60.0	1,725	174
267.1 1,123	Valencia	8.0	447.1	671	Paris (PTT)	7.0	1,796	167
267.8 1,120	Nyiregyhaza	6.0	447.1	671	Danzig	0.5	1,875	160
268.3 1,118.9	Bremen	0.3	449.7	667	Madona	15.0	1,920	156
269.4 1,112	Bari	20.0	450	666.5	Odessa (RW37)	20.0	1,935	155
271 1,107	Colte-Liege	0.3	451.8	664	Madona	25.0	2,000	150
271.5 1,105	Rennes	1.3	453.2	662	Klagenfurt	0.5	2,625	119
273.7 1,096	Turin (Torino)	7.0	453.2	662	Agén	0.5		
276.5 1,085	Hellsberg	60.0	453.8	661.3	Milan-Siziano	50.0		
279.7 1,072.4	Bratislava	14.0	455.9	658	San Sebastian (EAI8)	3.0	2,650	113
281 1,067	Copenhagen	0.75	459	653	Beromuenster	60.0	2,900	103.5
282.1 1,064	Lisbon (CTIAA)	2.0	465.8	644	Lyons (PTT)	1.6		

FREE

WE WILL CONVERT YOUR  
EXISTING SET TO Q.P.P. FREE

## To "AMATEUR WIRELESS" READERS

FREE collection and delivery within 10 miles radius of Charing Cross. Country orders carriage paid one way, providing customers purchase from us necessary components including valves.

We also invite inquiries for the repair and modernising of all makes of receivers, including home-constructed sets. Customers' sets of parts built up at low cost.

SEND ALL INQUIRIES TO SERVICE DEPARTMENT.

Send for Full Details To-day

## PILOT REPAIR SERVICE

Proprietors: PETO-SCOTT CO. LTD.

77 CITY ROAD, LONDON, E.C.1

West End Showrooms: 62 High Holborn, London, W.C.1



POST CARD

# POSTCARD

## RADIO LITERATURE

**GET THESE CATALOGUES FREE**  
Here "Observer" reviews the latest booklets and folders issued by well-known manufacturers. If you want copies of any or all of them FREE OF CHARGE, just send a postcard giving the index numbers of the catalogues required (shown at the end of each paragraph) to "Postcard Radio Literature," "AMATEUR WIRELESS," 58/61, Fetter Lane, E.C.4. "Observer" will see that you get all the literature you desire. Please write your name and address in block letters.

### Melotone Speaker Kit

If you think that any improvement is possible in the mounting and baffle of your speaker, then write through my free Catalogue Service for a folder describing the Melotone speaker kit. This is a padded type baffle having several advantages and enabling a speaker to be provided with an effective baffle area. **954**

### Rola Moving-coils

Rola dual-balanced pairs of speakers are described in the latest Rola folder. There is an impression that balanced pairs of speakers are expensive but this is discounted by the fact that two matched F5 speakers, complete with transformer, cost only £2 16s. 6d. the pair. The Rola pairs of speakers are supplied in specially matched groups, only one input transformer being necessary for each pair. **955**

### Bulgin Kits

Two layouts have just been sent me by Bulgin. One is of the Simple Two-three battery driven kit and the other the Drive-all A.C. box universal unit. Both the receiver and the eliminator are made up mainly with well-known Bulgin components. The layouts give lists of components and wiring instructions. **956**

OBSERVER.

### INFORMATION BUREAU

Will every querist please observe the following revised rules.

Please write concisely, giving essential particulars. A fee of one shilling postal order (not stamps), a stamped, addressed envelope and the coupon on the last page must accompany all queries.

Not more than two questions should be sent at any time.

The designing of apparatus or receivers cannot be undertaken.

Slight modifications of a straightforward nature only can be made to blueprints. For more serious alterations the minimum charge is 2/6.

Blueprints supplied by us will be charged for in addition, but of course, readers may send their own blueprints for alteration.

Modifications to proprietary receivers and designs published by contemporary journals cannot be undertaken. Readers sets and components cannot be tested by us. Queries cannot be answered by telephone or personally. Readers ordering blueprints and requiring technical information in addition should address a separate letter to the Query Department and should see that their remittance covers the price of the Blueprint and the amount of the Query fee.

We do not answer queries in cases where the fee is omitted.

Queries should be addressed to the Query Department, "Amateur Wireless," 58/61, Fetter Lane, London, E.C.4.



During the last eight years we have supplied many thousands of readers of "Amateur Wireless" with their radio requirements. Our aim has always been to give our customers complete satisfaction, and our advice on all radio matters is at their disposal.

### THE BEST KITS

**LISSEN "SKYSCRAPER" KIT,** With order  
including valves. Cash Price **5/-**  
£4/9/6.  
And 11 monthly payments of 8/6.

As above, but including high-class polished Cabinet and Loud-speaker. Cash Price £6/5/-, or 10/- with order and 11 monthly payments of 11/6.

**NEW LISSEN ZALMA (MELODY RANGER).** Complete kit of parts, less valves. Cash Price £5/5/-, order With **7/6**  
And 11 monthly payments of 9/6.

**KIT "B."**—As above but including Valves. Cash Price £6/15/-, order With **10/-**  
And 11 monthly payments of 12/6.

### QUIESCENT PUSH-PULL

By converting your battery set to Q.P.P. it becomes equal to a first-class all-mains receiver at a lower cost of H.T. than before

**R.I. PUSH-PULL INPUT TRANSFORMER and R.I. P.P. OUTPUT CHOKE,** With order  
complete with 2 Mazda pentode valves. List Price **5/10**  
£3/4/-.  
And 11 monthly payments of 5/10.

We shall be pleased to send you a quotation for any radio goods you may require. Price List free.

To avoid delay, will customers kindly send first payment with order.

### LOUD SPEAKER UNITS

**NEW CELESTION REETONE DUAL-MATCHED L.S. UNITS.** Complete with input transformer. Capable of magnificent reproduction. Vastly better than single L.S. unit. Cash Price **5/-**  
And 11 monthly payments of 8/-.

**BLUE SPOT 99 P.M. MOVING-COIL UNIT.** Cash Price **5/-**  
And 11 monthly payments of 5/6.

**NEW R. & A. "VICTOR" PERMANENT MAGNET MOVING-COIL REPRODUCER DE LUXE.** With 6-ratio transformer and cadmium-plated grill. Cash Price **6/5**  
And 11 monthly payments of 6/5.

### ACCESSORIES

**EXIDE W.H. HIGH-TENSION ACCUMULATORS** (120 volts, 5,000 M/A). The cheapest and best high-tension supply where mains are not available. Cash Price **7/-**  
And 11 monthly payments of 7/-.

**ATLAS ELIMINATOR A.C.244.** Three H.T. tappings, 20 M/A output. Cash Price **5/-**  
And 11 monthly payments of 5/6.

**SET OF THREE NEW VALVES:** Mazda, Cossor, or Mullard. 1 S.G., 1 detector, and 1 power. Cash Price **5/2**  
And 6 monthly payments of 5/2.

All goods delivered carriage paid to your door.

The **LONDON RADIO SUPPLY COMPANY**  
**11, OAT LANE · LONDON · E.C.2**  
Established 1925 Phone National 1971

# Q.P.P. doubles the volume!

This new system of doubling your output is fully explained in "Wireless Magazine," March. Constructional details of five Q.P.P. units are also given.

There are also details for building the A.C. Quality Gem, by W. James, and over 50 other features in this splendid issue. Get your copy to-day. Price 1/-.

# WIRELESS MAGAZINE

MARCH



## PREPAID ADVERTISEMENTS

Advertisements under this head are charged  
THREEPENCE PER WORD, minimum charge  
THREE SHILLINGS. DEPOSIT SYSTEM.

As the publishers cannot accept responsibility for the bona fides of advertisers in this publication, they have introduced a system of deposit which it is recommended should be adopted by readers when dealing with persons with whom they are unacquainted.

The amount of the Deposit and Fee must be remitted by Postal Order or Registered Letter (Cheques cannot be accepted) addressed to

"AMATEUR WIRELESS" ADVERTISEMENT DEPARTMENT,  
58/61 FETTER LANE, LONDON, E.C.4

**NEW EDITION RELIABILITY WIRELESS GUIDE.**—Describes on page 23 Stupendous free gift.

**NEW EDITION RELIABILITY WIRELESS GUIDE.**—Complete Constructor's Encyclopedia detailing principal advertised components. Traders supplied.

**NEW EDITION RELIABILITY WIRELESS GUIDE.**—Incorporating Station Log sent post free.—J. H. Taylor and Co., 8 Radio House, Macaulay St., Huddersfield.

**B.T.H. R.K. MOVING-COIL SPEAKERS.** Guaranteed new, unused. Manufacturers' surplus. Original price, 6 guineas. Highly sensitive and wonderful tone response. Will handle up to 10 watts output. Available for 6 v., 100 v., 200 v., 30/-; Also A.C. models, £2/10/-. Carriage paid, C.O.D. or cash with order. Send for list of other unused bargains.—Seekamp, 46 Farringdon Street, London, E.C.4.

**WIRELESS AS A CAREER.**—Whether you are engaged in the Radio Industry, and wish to improve yourself, or if you wish to obtain employment in this profession, we can help you. Our students are engaged in responsible positions in the majority of the large wireless firms in England. Booklet describing Home-study Course, post free.—Northern Counties Wireless School, Preston.

**THE IMPROVED "TONIC"** self-generating trickle-charger kit keeps 2-volt accumulators fully charged. Electric mains and charging stations unnecessary. Ideal for remote places, 7/- each, postage 9d. Particulars, testimonials, with pleasure.—Williams, Netherend, Cradley, Birmingham.

**PATENTS**—Trade Marks, "Advice Handbook" free.—B. T. King, Regd. Patent Agent, 140a Queen Victoria Street, London.

**QUIESCENT PUSH-PULL.**—Revolutionise your present Battery Receiver by replacing existing output valve with quiescent push-pull. Full moving-coil output (1½ watts). Current only 6 milliamps. Complete conversion kit, including 2 pentodes, specially matched transformers (push-pull), milliammeter and all necessary resistances, condensers, etc., £3 9s. Send for lists and diagrams.—Woods Radio, Holcombe Brook, near Bury.

**CABINETS.**—We can supply Brand New Complete Gramophones, London-made Cabinets, at less than the cost of Cabinets. Ideal for converting to Radio-Grams. £3 models to choose from, £2/6 to £10. Illustrated list free.—Radleys Ltd., Canal Road, Bradford.

**"UNIVERSAL" RADIO BARGAINS.** Manufacturers' surplus. Igranite Universal Mains Transformers, 8/11. Igranite 6-1 L.F. transformers, 4/11. Lamplugh P.M. moving-coil speakers, Junior (List 29/6), 18/6. Senior (List 42/-), 23/6. Ready Radio 303 Kits, 23/-. Meteor 5 G.G. Kits, 33/-. Six Sixty Units, 2/9. Pye 32 or 20 Hy Chokes, 5/6. A.B. Valves, L.F., H.F., or Power, 2/9 each. Super, 3/6. Screen-grid, 6/3. Disc Chokes, 1/-. Switches, 6d. Sprung Valve-holders, 5d. Leaks, 5d. Var. Condensers, 1/11; fixed, 6d. Millgate Pick-ups, 5/11. Transformers, 2/9. Pre-sets, 11d. Diffs, 1/7. Dual Coils, 2/6. Q.P.P. Transformers in stock. Telsen full range components and ASTRAL 3 Kits in stock. "MELODY RANGER" Kits and components at right prices. All the goods we offer are brand new, guaranteed and in original cartons. Thousands of Radio bargains. Lists with Blue Prints FREE!—"UNIVERSAL", 20 Victoria Road, Peckham, S.E.15 (back of Tower Cinema).

**"A MINIT TO TIN-IT" SOLDERING FLUX** dissolved in water makes soldering easy. "TIN-IT" solders all metals except aluminium. P.O. 6d. for 2 ozs. sent post free. Money returned if not satisfied. Sample post free. Write for post free Price List of soldering components, and copper wires, insulating materials.—Cooper & Warr, Ltd., 86 Duke Street, St. Helens, Lancs.

**FAMOUS FOR MAIL ORDER BARGAINS.**—Receivers, Speakers, Valves, Components, etc. Stamp for Quotation.—Simmons Radio Supplies, 9 Ilfracombe Avenue, South-end-on-sea.

**VALVES!**—Used, but emission passable. Filament continuity guaranteed. P.M.I.L.F. and P.M.G. 6d. each, post 2d.; 3 for 1/6 post free. P.625, 1/6 each, post 3d.; P.M.168.G., 2/- each, post 3d. Below.

**FOR EXTENSION TO KITCHEN OR NURSERY.**—Horn type Loud-speakers. Take little power to drive. Perfect order, 1/6 each, post 6d.—10 West Crescent, St. Annes-on-sea.

**INVENTORS' POCKET-BOOK.**—How to patent. Invaluable aid to selling your ideas. Expert advice. Copies free.—Edwin O. Axe, A.I.M.E., 27 Chancery Lane, London.

**MORE PART-EXCHANGE RECEIVER BARGAINS** for disposal. State approximate requirements for quotation.—Coutts, Wireless Engineers, Horley.

**REPAIRS** to Loud-speakers, transformers and headphones, 4/- each; Blue Spots or Wufas, 5/-; mains eliminators, etc., quoted for; prompt service; satisfaction guaranteed; terms to trade.—Loud-Speaker Repair Co., 2 Shipka Road, Balham, London. Streatham 6618.

**TURN YOUR WIRELESS KNOWLEDGE INTO CASH** with our assistance. In every district there is an opportunity for ambitious men and women to earn up to £300 a year.—Write for proof to England-Richards, Ltd., (IV), King's Lynn, Norfolk.

**ENGINEERS.**—Let's go into this together. All we ask is the chance to prove to you that you can earn £300, £400, £500 per year, and more. Other men are doing it and you can do the same. The first thing to do is to send for our FREE Handbook, "ENGINEERING OPPORTUNITIES." This 250-page book contains details of B.Sc., A.M.I.C.E., A.M.I.Mech.E., I.E.E., A.M.I.A.E., M.I.M.T., G.P.O., etc. Exams., outlines Home-study Courses in all branches of Civil, Mech., Elec., Motor, Aero, Wireless, and "Talkie" Engineering and explains the advantages of our unique Employment Department. Our offer means a lot to you, we urge you not to neglect it. Send for your copy of our Handbook to-day, FREE of any charge.—British Institute of Engineering Technology, 109 Shakespeare House, 29-31 Oxford Street, London.

**PENTODES, 10/6; H.F., Det., L.F., 4/6; Power, 5/6.** Best French manufacture.—Service Charging Station, Fairmead Avenue, Westcliff.

**WANTED.**—Sound discarded Components. Send list and prices.—Below.

**"NORTHERN STAR" VALVES.**—2 volt Det., H.F., 3/6; Power, 4/-.—R. Wigfield, Furlong Road, Goldthorpe, Yorks.

**A NEW SCIENTIFIC INVENTION.**—Chemico Efficient Earthing Device. You will hear more about this wonderful patent which gets the very best out of a set. Obtainable only from the sole manufacturers, British Wireless Components, Alker Street, Chorley, Lancs. Post free, 2/-.

**AMERICA NIGHTLY!**—All-wave Tuner, 20-2,000 metres, reaction incorporated, 6/-.—Evans, 77 Jermyn Street, London.

**BANKRUPT BARGAINS.**—List free with 3-valve diagram. S.T.300 Kit, 40/-. S.T. 400, 50/-. Formo Economy 3, 22/6. Cruiser 4-Wave 3, 32/6. Straight 3, 22/6. Any kit supplied. Eliminators, M.C. Speakers, Valves, all smaller parts at very keen prices. R. for M. Set in Camco Cabinet, 50/-. Spencer new 1½-guinea Portable, £6/10/-. Mains Sets cheap. Modern components taken in part exchange. Lissen Skyscraper Kit, as new, 50/-. Butlin, 143b Preston Road, Brighton. Phone: Preston 4030.

**OSRAM 4-VALVE MUSIC MAGNET, 1932, £5/10/-**—Lissen Skyscraper, £2/10/-; Bakers Permag moving-coil speaker, £1/10/-; all working well.—Burgess, 20 Woodstock Road, Oxford.

**"Amateur Wireless and Radiovision."** Price Threepence. Published on Wednesdays and bearing the date of Saturday immediately following. Post free to any part of the world: 3 months, 4s. 6d.; 6 months, 8s. 9d.; 12 months, 17s. 6d. Postal Orders, Post Office Orders, or Cheques should be made payable to "Bernard Jones Publications, Ltd."

General Correspondence is to be brief and written on one side of the paper only. All sketches and drawings to be on separate sheets. Contributions are always welcome, will be promptly considered, and if used will be paid for. Communications should be addressed, according to their nature, to The Editor, The Advertisement Manager, or The Publisher, "Amateur Wireless," 58-61 Fetter Lane, London, E.C.4.


**BELLING-LEE**  
FOR EVERY RADIO CONNECTION  
Cambridge Arterial Road, Enfield, Mdx.

**WALNUT or BLACK**

AND A PRICE REDUCTION

"R" and "B" Type terminals and terminal mounts now made in Black or Walnut Bakelite.

The Terminal Mount is reduced from 6d. to 6d.



**TAYLEX WET H.T. BATTERIES**  
Give long service, improved volume and tone. Very economical. Replacements for Taylex or Standard batteries at low prices details post free. Also Bargain List, Radio Kits and parts at lowest prices.  
A. TAYLOR, 57 STUDLEY ROAD, STOCKWELL, LONDON

## FULL-SIZE BLUEPRINTS

When ordering, please send Postal Order, NOT STAMPS. Quote the Blueprint number shown below; not the number of the issue.

## CRYSTAL SET (6d.)

1531 Crystal Set .. .. . AW308

## ONE-VALVE SETS (1s. each)

Easy to Build One .. .. . AW304  
B.B.C. One-valver .. .. . AW344  
Portable Short-wave One .. .. . AW354

## TWO-VALVE SETS (1s. each)

Ten-Station Two (D, Trans) .. .. . AW336  
Inexpensive A.C.2 (D, Trans) .. .. . AW346  
Mascot Two (D, Trans) .. .. . AW353  
Ideal Regional 2 (D, Trans) .. .. . AW357  
Quality 30s. Two (D, Trans) .. .. . AW361  
Ether Music Two (B, Trans) .. .. . AW364  
Clarion-voice 2 (SG, D, Pen) .. .. . AW371  
Home Station A.C. 2 (D, Pen) .. .. . AW374  
B.B.C. National Two (D, Trans.) .. .. . AW377  
New Economy Two (D, Trans) .. .. . WM265  
Family Two (D, Trans) .. .. . WM278  
Economy A.C. Two (D, Trans) .. .. . WM286  
Screen-grid Two (SG, Trans) .. .. . WM289  
A Two for 7 Metres (D, Trans) .. .. . WM295  
New-style Radiogram (D, Trans) .. .. . WM299  
A.C. Quality Gem (D, Trans) .. .. . WM312

## THREE-VALVE SETS (1s. each)

New Favourite Three (D, RC, Trans) .. .. . AW334  
Home-Lover's All-electric 3 (SG, D, Trans) .. .. . AW335  
Home-Lover's Battery 3 (SG, D, Trans) .. .. . AW341  
£8 Radiogram (D, RC, Trans) .. .. . AW343  
New Regional Three (D, RC, Trans) .. .. . AW349  
World-Ranger Short-wave Three (D, RC, Trans) .. .. . AW355  
Wizard (SG, D, Trans) .. .. . AW360  
£2 2s. Family Three (D, 2 Trans) .. .. . AW368  
Build As You Learn Three .. .. . AW366  
Build As You Learn SG 3 (SG, D, Trans) .. .. . AW372  
James Push-Push Three (SG, D, Q.P.P.) .. .. . AW378  
Everybody's A.C. Radiogram (with automatic G.B.) .. .. . WM262  
New Economy Three (SG, D, Trans) .. .. . WM263  
New Plug-in Coil Three (D, 2 Trans) .. .. . WM270  
Transportable Three (SG, D, Trans) .. .. . WM271  
Multi-mag Three (D, 2 Trans) .. .. . WM288  
Percy Harris A.C. Radiogram (D, RC, Trans) .. .. . WM294  
Prosperity Three for Batteries (SG, D, Trans) .. .. . WM296  
1933 Economy S.G. Three (SG, D, Trans) .. .. . WM306  
Harris Ethergram (SG, D, Trans) .. .. . WM308  
A.C. Calibrator (SG, D, Trans) .. .. . WM309  
Narrow-pass Three (SG, D, Trans) .. .. . WM314

## FOUR-VALVE SETS (1s. 6d. each)

65/- Four (SG, D, RC, Trans) .. .. . AW370  
Melody Ranger (SG, D, RC, Trans) with copy of "A.W." .. .. . AW375  
"A.C. Melody Ranger" (SG, D, RC, Trans) .. .. . AW380  
Quadradyne (2 SG, D, Pen) .. .. . WM273  
Economy Radiogram (SG, D, RC, Trans) .. .. . WM276  
A.C. Quadradyne (2 SG, D, Pen) .. .. . WM279  
Ideal A.C. Home Super (Super-het) .. .. . WM290  
Gold Coaster (A.C. Short-wave) .. .. . WM292  
Triple-tune Four (2 SG, D, Trans) .. .. . WM293  
Calibrator (SG, D, RC, Trans) .. .. . WM300  
Table Quad (SG, D, RC, Trans) .. .. . WM303  
"Words and Music" Radiogram (2SG, D, Trans) .. .. . WM307  
Home Short-wave (SG, D, RC, Trans) .. .. . WM311  
"Words and Music" Radiogram de Luxe (SG, D, RC, Q.P.P.) .. .. . WM307a  
Empire Short-wave (SG, D, RC, Trans) .. .. . WM314

## FIVE-VALVE SETS (1s. 6d. each)

James Short-wave Super (Super-het) .. .. . AW328  
Simple Super (Super-het) .. .. . AW340

## SIX-VALVE SETS (1s. 6d. each)

New Century Super (Super-het) with copy of "A.W." .. .. . AW363  
New A.C. Century Super (A.C. super-het) .. .. . AW365  
1932 Super 60 (Super-het) .. .. . WM269  
1932 A.C. Super 60 (A.C. Super-het) .. .. . WM272  
Ideal Home Super (Super-het) .. .. . WM280  
Easytune 60 (Super-het) .. .. . WM284

## SEVEN-VALVE SETS (1s. 6d. each)

Super Senior (Super-het) .. .. . WM256  
Seventy-Seven Super (A.C. Super-het) .. .. . WM350

## PORTABLES (1s. 6d. each)

General-purpose Portable (SG, D, RC, Trans) .. .. . AW351  
Town and Country Four (SG, D, RC, Trans) .. .. . WM282  
Everybody's Portable (5-valve super-het) .. .. . WM291

## AMPLIFIERS (1s. each)

A.W.'s Push-push Amplifier .. .. . AW376  
Universal Push-pull Amplifier .. .. . AW300  
"A.W." Record Player (LF, Push-pull) .. .. . AW319  
Battery-operated Amplifier .. .. . AW362  
"Q.P.P." Output Circuits .. .. . WM315

## MISCELLANEOUS (1s. each)

"Mascot" Mains Unit .. .. . AW350  
"A.W." Trickle Charger .. .. . AW352  
Add-on Band-pass Unit .. .. . AW359  
Short-wave Adaptor for New Century Super .. .. . AW367  
Band-pass H.F. Unit (1/-) .. .. . AW373  
"W.M." Linen Diaphragm Loud-speaker .. .. . WM243  
Short-wave Director (6d.) (wavemeter) .. .. . WM285  
Voltage Regulator .. .. . WM287  
A.C. Mains Unit .. .. . WM310  
A-P-A (Power Amplifier for A.C. Mains) .. .. . WM275  
A-P-A Radio Unit (SG, D.) .. .. . WM281  
Economy Gramophone Amplifier .. .. . WM277

Copies of the "Wireless Magazine" and of "Amateur Wireless" containing descriptions of most of these sets can be obtained at 1s. 3d. and 6d. respectively, post free. Index letters "A.W." refer to "Amateur Wireless" sets and "W.M." to "Wireless Magazine". Address letters:

Amateur Wireless Blueprints Dept., 58-61 Fetter Lane, London, E.C.4

**Amateur Wireless**  
FEE 1/-

**INFORMATION BUREAU  
COUPON**  
Available until Saturday  
MARCH 11, 1933



# SELFRIDGE'S

## FAMOUS BASEMENT Wireless Dept.

Offer a quantity of  
Second-hand and Re-conditioned  
Radio Receivers and Gramophones  
including such makes as

- ★ COLUMBIA
- ★ H.M.V.
- ★ PHILIPS
- ★ G.E.C.
- ★ CLIMAX

All Offered at Bargain Prices

—and all covered by a 12 month's guarantee against faulty work-  
manship or materials.

Personal shoppers only:

Selfridge & Co. Ltd., Oxford Street, London, W.1



"We're Fluxite and Solder—  
the reliable pair:  
Famous for soldering—  
known everywhere!"

Carry US with you—  
as well as your SET.  
If things go wrong—  
no cause for regret!"

See that Fluxite and Solder are always by you—in the  
house—garage—workshop—anywhere where simple, speedy  
soldering is needed.

ALL MECHANICS WILL HAVE  
**FLUXITE**  
IT SIMPLIFIES ALL SOLDERING

All Ironmongers sell Fluxite in tins: 4d., 8d., 1s. 4d. and  
2s. 8d. Ask to see the **FLUXITE POCKET SOLDERING  
SET**—complete with full instructions—7s. 6d. Ask also for  
our leaflet on **HARDENING STEEL** with Fluxite.  
**FLUXITE LTD.** (Dept. 326). ROTHERHITHE, S.E. 16.

**FOR ALL REPAIRS!**




# You'll be amazed! at their long life

## PERTRIX

TRADE MARK

### H.T. BATTERIES

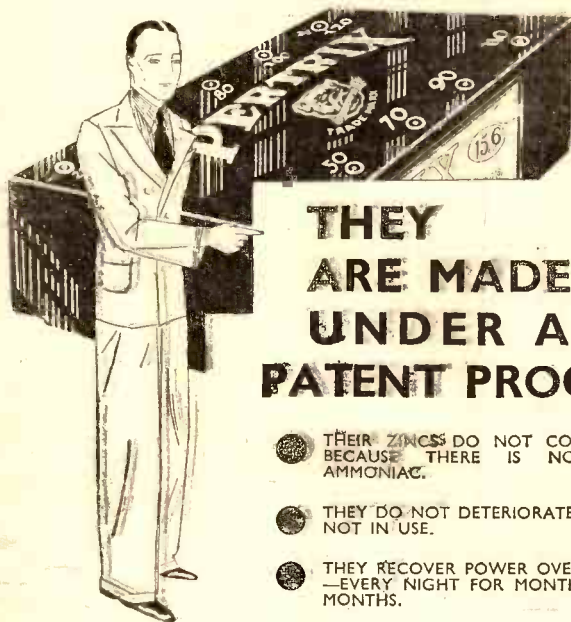

## THEY ARE MADE UNDER A PATENT PROCESS


- THEIR ZINCS DO NOT CORRODE:  
BECAUSE THERE IS NO SAL-  
AMMONIAC.
- THEY DO NOT DETERIORATE WHEN  
NOT IN USE.
- THEY RECOVER POWER OVERNIGHT  
—EVERY NIGHT FOR MONTHS AND  
MONTHS.
- THEY GIVE CLEANER CURRENT AND  
HIGHER VOLTAGE FOR A LONGER  
TIME.
- They are superior in every way to the  
common sal-ammoniac battery. For  
long, trouble-free service and clear radio  
rendering, the patent Pertrix is obviously  
the only high-tension battery a dis-  
criminating person will use.

COMPLETE THE  
EQUIPMENT with

## PERTRIX

TRADE MARK

ACCUMULATORS

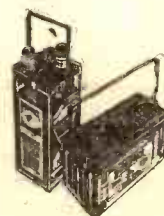

## BRITANNIA

## BATTERIES LTD

Pertrix Accumulators are built on clean  
engineering lines; the glass boxes are  
solidly cast; the plates are massive; they  
have heavy lugs, fool-proof terminals  
and a permanent carrying handle known  
as the "Kaptive Karrier." See them at  
your Pertrix Dealers.

233 Shaftesbury Avenue, London, W.C.2.

Works: Redditch.

Depots at Belfast, Birmingham, Bristol, Glasgow, Leeds, Manchester, Newcastle,  
and Dublin.

Mention of "Amateur Wireless" to Advertisers will Ensure Prompt Attention



EVERYTHING **The S.E.C.** ELECTRICAL  
your guarantee

**EFFICIENCY** WITH

**ECONOMY** IN

**QUIESCENT PUSH-PULL CIRCUITS**



**TWO OSRAM  
L.P.2 VALVES**

PRICE **17/6** Per Pair



#### CHARACTERISTICS

Filament Volts ... 2.0 max.  
Filament current ... 0.2 amps.  
Amplification Factor ... 15  
Impedance ... 3,900 ohms.  
Mutual conductance ... 3.85 m.a. volt  
Price 8/9 each

## OSRAM L.P.2

### THE ECONOMY OUTPUT VALVE

- 1** The OSRAM L.P.2 is the ideal Triode for use in Q.P.P. circuits owing to its high amplification factor and high slope, which means sensitivity and large power output.
- 2** Using 150 volts H.T. Battery, the working characteristics give maximum efficiency with any standard type of Q.P.P. output transformer.
- 3** Very low quiescent H.T. current of only 2.0 m.a. per pair of valves ensures minimum running costs.
- 4** The Triode characteristics are ideal for moving coil or moving iron loud speakers.
- 5** Low valve costs mean saving in initial outlay.

**Osram**  
2 VOLT BATTERY  
**Valves**

MADE IN  
ENGLAND  
SOLD BY ALL  
WIRELESS  
DEALERS

**EXTRA QUALITY  
WITHOUT EXTRA COST**

Advt. of The General Electric Co., Ltd., Magazine House, Kingsway, London, W.C.2.