

**SIMPLE but ASTONISHING EXPERIMENTS with a CATHODE-RAY TUBE**

# Amateur Wireless

3<sup>d</sup>  
Every  
Wednesday

and  
Radiovision

**WHEN TO LISTEN  
on the SHORT WAVES**

**HIGH SPOTS IN  
THE PROGRAMMES**


**CHRISTMAS SHORT  
STORY**

**MYSTERY AT  
BISAMBERG**

## SHORT CUTS to SUCCESS in SET BUILDING

*and*  
**ASSEMBLING  
the 1934 CENTURY  
SUPER**

Special Article  
by Percy Harris

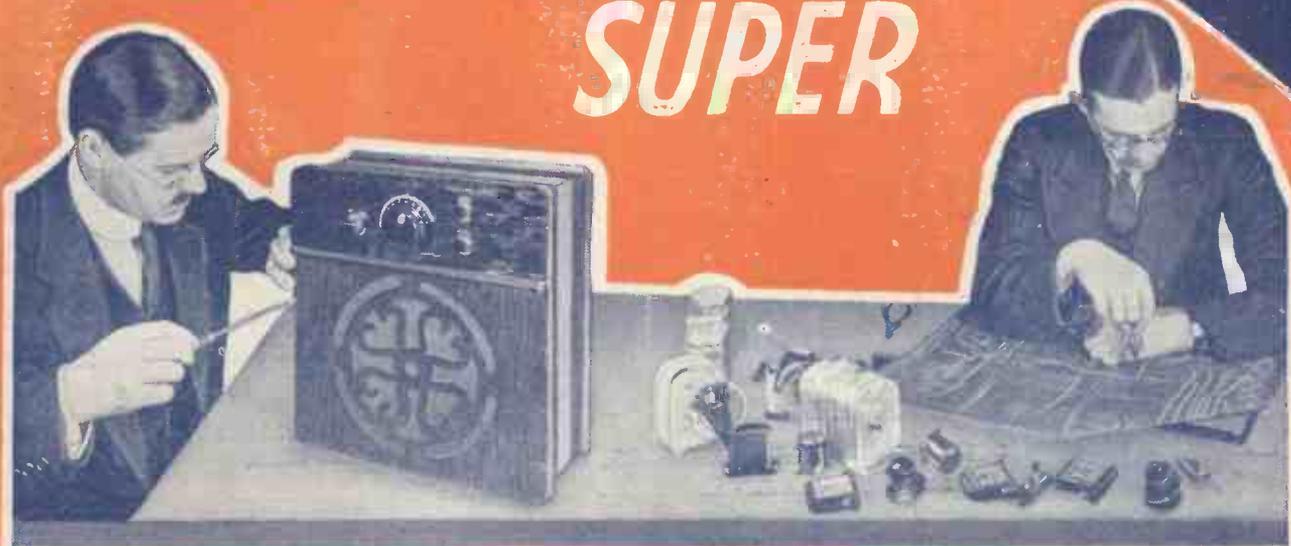


EVERYTHING **The G.E.C.** ELECTRICAL

# A "SUPERHET" SIX

unique in selectivity

range getting properties and

PURE TONE POWER

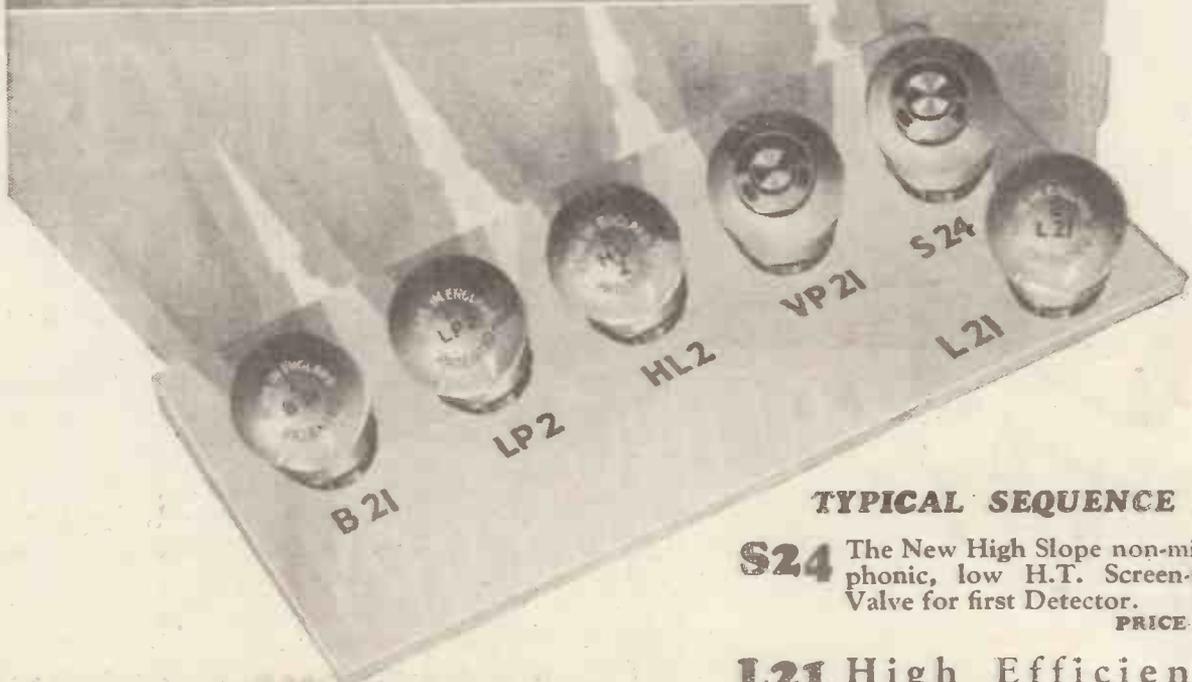

### TYPICAL SEQUENCE

**S24** The New High Slope non-microphonic, low H.T. Screen-Grid Valve for first Detector. **PRICE 15/6**

**L21** High Efficiency oscillator **PRICE 7/-**

**VP21** High Efficiency Variable mu. high frequency pentode. **PRICE 15/6**

**HL2** The non-microphonic Detector for sensitivity and Silent Background. **PRICE 7/-**

**LP2** Power driver for Class B. **PRICE 8/9**

**B21** The New Double Triode "Class B" valve for Great Volume with pure tone. **PRICE 14/-**

**Osram**  
2 VOLT BATTERY  
**Valves**

WRITE for the OSRAM VALVEGUIDE (1933-4 Edition) sent post free.

MADE IN ENGLAND

SOLD BY ALL RADIO DEALERS

**Longer life**

---

**unwavering power**

---

**greater selectivity**

---

from the



**WIRELESS  
BATTERIES  
AND ACCUMULATORS**

**MADE TO POWER  
YOUR SET PRECISELY!**

**IF YOURS IS A BEETHOVEN PORT. S.G. 4**

you need Ever Ready Batteries—H.T./108 Pop; G.B./9 v. Winner; L.T./2178 B—all made specially for it. If not, simply ask your dealer for the Ever Ready List, showing all popular makes with their special Ever Ready batteries. Your set will be powered perfectly by its appropriate Ever Ready batteries.

THE EVER READY CO. (GREAT BRITAIN) LTD.,  
HERCULES PLACE, HOLLOWAY, LONDON, N.7



**Give yourself a  
USEFUL PRESENT  
this Xmas** 

A HANDY outfit for the handy man, invaluable for 101 jobs in the Garage, the Home, the Workshop, and for the Wireless Constructor. Being small and adaptable it is the solution of innumerable problems.

The outfit comprises 16 tools for Slotting, Sawing, Scraping, Slitting, Filing—a Screw-driver, also—all of the finest tungsten steel, complete with patented holder in a neat metal case.



**COMPLETE  
5/-  
OUTFIT**

A few illustrations of the many uses of the 4S TOOL

Obtainable from usual suppliers

Sole Manufacturers

E4S8

**JAMES NEILL & CO. (SHEFFIELD) LTD.,  
COMPOSITE STEEL WORKS, SHEFFIELD, 11**

# What's happening now in AFRICA

## Build with your own hands a set on which you can hear the news and views of all the world DIRECT!

At last the day of All-World Radio has arrived, and you can build with your own hands the first receiver to give you not only England and Europe, but America and Australia direct. The Lissen All-Wave All-World Skyscraper 4 tunes from 12 to 2,100 metres. It gives you all the ordinary British and Continental programmes you can desire, and in addition stations all over the world which broadcast news and views and entertainment on the Short and Ultra Short wavelengths. These Short Wave stations are receivable on this Lissen All-Wave All-World Skyscraper at truly amazing ranges—Melbourne, Australia, at almost 12,000 miles, Johannesburg at 6,000 miles, Sydney, Australia, at 12,000, Pittsburg, Pennsylvania at 4,000 miles—these and many more of which the ordinary listener cannot hear even a whisper.

**CHASSIS KIT  
COMPLETE WITH  
FOUR VALVES  
£5.12.6**

And remember you get these stations through Double Balanced Pentode Output giving brilliant reproduction on a Moving Coil Speaker—as much power as a Mains Set from ordinary high-tension batteries



## ULTRA-SHORT-SHORT MEDIUM & LONG WAVES

Lissen have made this All-Wave All-World radio available to Home Constructors first, because it brings back the thrill of conquest to hear America and Australia direct on a set you have built yourself. It makes you an enthusiast to realise what a wonderful thing you have created!

And when you see the Great Free Chart of the All-Wave All-World "Skyscraper" 4, which tells you how to build it and how to work it and why it gives such marvellous results, you will agree at once that it will be wise of you to build for yourself rather than buy a factory assembled receiver which cannot give you these new and intriguing short-wave stations.

The FREE CHART simplifies everything; there are pictures of every part, with every wire numbered, every hole lettered, every terminal identified. YOU CAN'T GO WRONG! But get the Chart and see for yourself—then build the Lissen All-Wave All-World "Skyscraper" 4, the SET THAT SPANS THE WORLD!


THE SET  
THAT  
SPANS  
THE  
WORLD



To LISSEN, LTD., Publicity Dept., ISLEWORTH.  
Please send me FREE copy of All-Wave All-World "Skyscraper" Chart.  
Name .....  
Address .....  
A.W.2034

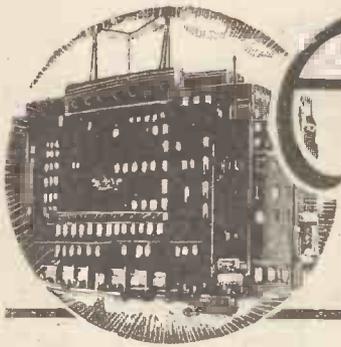**GREAT  
CHART  
FREE  
POST THIS  
COUPON!**





# Amateur Wireless

AND RADIOVISION



Britain's Leading Radio Weekly for Constructor, Listener and Experimenter

Editor: D. SISSON RELPH      Radiovision Editor: H. CORBISHLEY      Editor-in-Chief: BERNARD E. JONES      Technical Editor: J. H. REYNER, B.Sc.(Hons.), A.M.I.E.E.      Assistant Editor: ALAN HUNTER  
 Research Consultants: W. JAMES and PERCY W. HARRIS, M.Inst.Rad.E.

Published by BERNARD JONES PUBLICATIONS, LTD., 58-61 Fetter Lane, London, E.C.4. Telephone: Central 4341 (four lines). Telegrams: "Beejapee, Fleet, London." Subscription post paid to any part of the world: 3 months, 4s. 6d.; 6 months, 8s. 9d.; 12 months, 17s. 6d. Published on Wednesdays and dated for the following Saturday

## News from Broadcasting House

By Our Special Commissioner

### Phyllis Makes Good

DANCE-BAND fans, please note: our Phyllis, whose surname is Robbins, has passed from her probationary period with Henry Hall. She has emerged from her broadcasting trials with great credit.

We may expect Phyllis to become as much a fixture with Henry Hall's band as the tireless Les Allen, the official male vocalist.



Phyllis Robbins

### Christmas Dance Music

HENRY tells me that over the Christmas period of broadcasting he intends to cater for the masses and not for the high-temperature enthusiasts.

We shall hear all the popular hits of the day during Henry's Christmas Day date, from 10.30 to 12 p.m., and from 9.20 to 10.30 on Boxing Day.

"Push back the chairs and roll up the carpet," will be Henry's Christmas inducement for you all to dance.

### Don't Mis-tune

"SOME of the wavelength changes under the Lucerne Plan are so small," said an engineer to me at Broadcasting House, "that perhaps some listeners will be tempted to make up any loss of volume by turning the volume control instead of re-tuning the set."

"Please tell them not to do this horrid thing. If they don't re-tune, however little it may be, they are bound to get a backwash from a foreign station." Well, I have told you—so don't blame me.

### Old Station, New Site

SORRY, but I must shatter any fond hopes Midland Regional listeners may be entertaining about their new 50-kilowatt transmitter at Droitwich.

It will not be a new station, after all. Just

a redundant medium-wave National with its wavelength changed. It may be London, or North or West National.

No need for desolation. These stations are still right up to date, or will be when the engineers have re-erected them.

### Songs from the Shows

FOR his first programme in the new "Songs from the Shows" series, I gather from John Watt that he will deal with famous Adelphi shows.

He is trying to get W. H. Berry to take part. If he succeeds the show is certain to be a great success.

### Four Nervous Young Men

CAN you imagine what they were nervous about? Nothing less than an announcing audition at Broadcasting House. Truly a nerve-wracking experience.

Huddled in studio 3D, each had to speak from a copy of a three-years-old news bulletin. The "inquest" was held under the auspices of Colonel Dawnay and Mr. Lloyd James, with the Blattnerphone remorselessly recording every slip of the tongue.

Don't jump to the conclusion that fresh announcers are imminent at London. Mr. Marriott, the new arrival, is doing well, but the B.B.C. always likes to have a few tested and approved applicants up its capacious sleeve.

### B.B.C.'s Recording Plans

MORE and better Blattnerphone recording will be done at Broadcasting House. They have also decided to do more recording on the new treated-gelatin process. It is cheap and quick—no mean merits for broadcasting work.

Of course, the normal soft-wax recordings are still unbeatable for sheer quality, but they take time—and are somewhat expensive.

### Special Recording Department

THAT the B.B.C. attaches a growing importance to its recording work is proved



W. H. Berry

### This Week's "Specials"

When to Listen on the Short Waves.	Page
A helpful article by J. Godchaux Abrahams ...	1093
Building the 1934 Century Super.	
"The Experimenters" continue their instructions for rebuilding a famous set ...	1094
We Test for You	
J. H. Reyner reviews some interesting new apparatus ...	1102
Radio Christmas—1999 A.D.	
A short story by Derek England	1103
Dodging Constructional Difficulties	
Short cuts to success explained by Percy W. Harris ...	1104
Amateur Television	
Interesting experiments with cathode-ray tube ...	1108

by the recent appointment of a senior engineer as Engineer-in-Charge Recording.

It is hoped to develop a band of semi-specialists for this recording work, which entails records of rehearsals and records for Empire broadcasting.

### At Maida Vale

IN spite of the fact that the new Maida Vale premises are a good ten minutes walk from the nearest tube station, the B.B.C. has taken them over for several years. Perhaps they will institute a private bus service to convey artists backwards and forwards from Broadcasting House?

Meanwhile, the notion I put forward last week about a vaudeville studio gathers favour. There is no hurry at the moment, though, with

Special Christmas Programme Feature Next Week



Eric Maschwitz

the St. George's Hall on lease until next Autumn.

**Eric Hits Back**

WE radio columnists were taken into Eric Maschwitz's confidence to-day. He had us all nice and snug in one of the listening rooms at Broadcasting House, where he very ably defended all he has done.

He told us he was not going to drop the "In Town To-night" series, and that the "First Time Here" series was being only temporarily suspended.

He has bright ideas to liven up the Saturday teatime hour. In the New Year we shall have a "Tea Mixture" series—with a star to sponsor the numbers while we rattle the teacups and slog into the cake.

**For Studio Audiences**

ERIC made out a very sound case for the studio audience, I thought. He pointed out that there was a difference only of degree, not of principle, between the studio audiences and those in St. George's Hall.

Whereas the studio audience consisted all too often of "forty frightened people," the

**Hint from America**

IN thus placing the emphasis on the programme rather than on the artist, our B.B.C. Light Entertainment department is taking the hint from a very widespread practice in American broadcasting.

On the other hand, the Americans are learning a thing or two from us. Recently they have been taking broadcasts from the Carnegie and other halls, just to give listeners that "No. 10 Studio" effect we have striven so long to impart into our programmes. If that isn't a compliment, what is?

**Are Studios Wasted?**

MORE and more the tendency is for broadcasting to be done from halls instead of from studios. The other night, for instance, the Theatre Orchestra played its programme from St. George's Hall.

The effect at the loud-speaker was undoubtedly superior to any studio performance the orchestra has done to date.

It makes one wonder whether all that talk about exact reverberation periods in the Broadcasting House studios was not just a trifle over-done.

**Radio Gossip of the Week**

**Rejecting Static**

DO you appreciate the difficulty of testing a receiver in the neighbourhood of static interference such as is radiated from the electric signs of Piccadilly Circus? If you do, then you will be surprised to know that at the Radio Centre in Haymarket a radio receiver on test can reproduce programme signals without a trace of static interference. The manager has installed a Rejectostatic unit. He claims that good reception is possible on any make of set.

**Strasbourg Off the Air**

IN anticipation of any mystified knob-twiddlers who, on tuning their sets between December 13-16, fail to pick up Radio Strasbourg, may we inform them that the station will be off the air from G.M.T. 13.15 on the former, until 16.00 on the latter date, to permit the engineers to make essential alterations to the plant? On December 17 you should note an improvement in signals.

week, we take it that many enthusiasts must stay up all night to pick up North and South American transmissions, and we wonder whether towards 5 a.m. they think of turning to some of the European transmitters. If they do, they will hear Prague's famous cock-crow, which is now being imitated and even embellished by the new opening signal put out by the Latvian stations to awaken the sleepy heads and drag them out of bed for the daily physical jerks.

Tune in to Madona or Riga and enjoy the short farmyard "song scena" which acts as a prelude to the early morning gymnastic course. Whether it is an effective alarm or not we cannot say, but at least it is a novelty for the town dweller.

**For Constructors**

PERCY W. HARRIS has always been a friend of the amateur constructor. This week he proves how closely in touch he is with constructors' needs by his article in our centre pages.

He goes right into the heart of things, passing on tips that he has learned himself in the hard school of experience. You, too, can benefit from these tips—and thereby improve your wireless reception.

**Century Super 1934**

ALTHOUGH too early yet to give readers' comments on our 1934 Century Super indications strongly point to its enthusiastic reception by a large number of amateurs.

The new version has the great merit of using up nearly all the old parts, involving the constructor in the minimum of extra expense to bring the original model right up to date.

**Self-adjusting Volume Control**

OUR self-appointed task of cleaning up wireless nomenclature started with the system known for short as "A.V.C." or automatic volume control. We prefer to call it self-adjusting volume control, and so, apparently, do many of our readers.

**Ready for Christmas?**

In a wireless sense, we mean? You must have a good set if you are to make the most of all the fine programmes being prepared by the B.B.C. Why not build a new "A.W." set? There's still time!

**From the B.B.C. Year Book . . .**

YOUR licence costs you ten shillings a year. How much of it goes into broadcasting? The B.B.C.'s Year Book for 1934 reveals this and other mysteries. In 1932 the total amount left for the B.B.C. after Post Office and Treasury percentages had been deducted was 4s. 7d. per licence. Added to this amount was 1s. 3d. per licence for publication profits.

You will be interested to know that of the gross revenue of 5s. 10d. per licence no less than 2s. 6½d. was spent on programmes—half the total revenue.

Let us should think that the "higher-ups" of broadcasting are overpaid, note that governors' fees amounted to only ¼d. per licence.

In the basement of Broadcasting House there is a restaurant. Contrary to rumours, the building is not licensed for the sale of alcoholic beverages, but this does

not affect the patronage of the restaurant.

The S.O.S. service has taken a definite place in the social life of the community. It is not always effective, but the number of successes is quite high. A year's total S.O.S.'s of 542 for illness produced 304 successful answers.

In September, 1933, the Recorded Programme Library comprised 25,000 records. These had been accumulated, carded, and filed within six months. Two copies of each record are kept, one for rehearsal and one for transmission.

Eventually the B.B.C. hopes its Empire broadcasting will enable programmes to be exchanged between the British Isles and the Dominions and Colonies overseas. Australia may send us an Empire programme in 1934.

more free-and-easy attitude of the audience in St. George's Hall lent just the right atmosphere to the broadcasts.

**Starring Special Features**

PERHAPS the most significant development of broadcast light entertainment foreshadowed by Eric Maschwitz is the emphasis on feature programmes instead of on individual stars.

For example, following up the undoubted success of the "Café Colette" feature, the New Year will herald in a Tyrolean Band, compèred by two personalities to be known as Hans and Franz, who will cross-talk in broken English

Betty Joel, the only woman radio designer, with the KB666 receiver, for which she designed the cabinet



Percy W. Harris

J. GODCHAUX ABRAHAMS Tells You—

# When to Listen on the Short Waves


CONDITIONS during the past few weeks have been somewhat mixed inasmuch as although certain nights have proved exceptionally favourable for the reception of short waves from distant transmitters, on others any attempt to pick up broadcasts, even from some of the nearer and more powerful stations, has brought much disappointment.

Apparently we have struck another period of "sun spots," which, according to previous observations, have a very adverse effect on wireless transmission in general, and on the higher frequencies in particular. However, as these conditions are not of a lasting character, but change from day to day, the unfavourable results on one evening should not deter the experimenter from making another attempt on the following day or night.
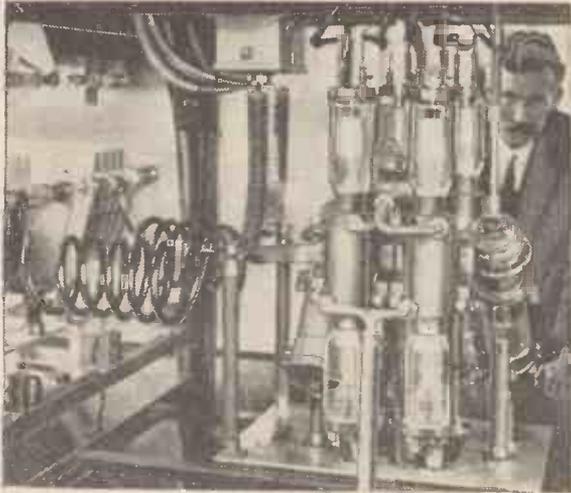
## New Transmission Schedules

As we have now reached the "short day" period of the year, most broadcasting stations have now advertised their new schedules and it will be useful to make a note of them as but few changes are likely to be made until the Spring. Some alterations have been made in the "timings" of the European stations.

Poste Colonial (Paris Pontoise) is now on the air on 19.68 metres from G.M.T. 13.00-16.00; on 25.20 metres from 16.15-19.15, and again from 20.00-23.00. For the later transmissions, namely from 23.15-02.00 and from 03.00-05.00,



A close-up view of the 60-kilowatt valves used for the Canadian service at Rugby

the 25.60-metre channel is used. As it frequently happens that the Poste Colonial takes from the Ecole Supérieure (P.T.T.) studio any relays of operatic performances or events of national or international interest, it is good to know that when these occur between 20.00 and 23.00 G.M.T. they are simultaneously broadcast on 25.20 and 25.60 metres.

With the bringing into operation of the new Budapest-Csepel 150-kilowatt transmitter, the Hungarian authorities have decided to give a

short-wave relay of the programmes for the benefit of their nationals overseas. The broadcasts will be carried out by HAT, Szekesfehervar, which is testing at present on 43.86 metres (night) and on 21.92 metres (day).

Reports have been notified of reception in the United Kingdom of HJ4ABB, Radio Manizales, Columbia, on 42 metres. Two transmissions appear to be made weekly which, translated into G.M.T., represent 01.00-03.00. (Thursdays), 04.00-05.00 and 20.00-22.00 (Sundays). Announcements are made in both Spanish and English, the opening and interval signal consisting of a gramophone record ("Just a Giglo").

Another South American station which has now cropped up is HC2RL, of Guayaquil, Ecuador, on 45.42 metres (6,605 kilocycles). It has been picked up on Thursdays between G.M.T. 03.00-04.00.


Should you hear a Spanish transmission on a wavelength slightly above that of HVJ, Vatican (50.26 metres), you may log it as HJ2BA, Tunja (Columbia), of which the call incorporates the slogan: *La Voz del Pais*. The frequency is 5,952 kilocycles (50.4 metres). Broadcasts are irregular, but have been heard between midnight and 03.00 G.M.T. Be careful, however, that you do not mistake this station for EAJ25, Radio Club of Barcelona, which is now regularly working; on Saturdays between G.M.T. 20.30 and 21.30.

Of the Mexican broadcasters the "star" to-day is XETE, operated by the Ericsson Telephone Company at Mexico City, on 31.23 metres (9,600 kilocycles) between 19.30 and 22.00, and again from 23.30-00.00 G.M.T. Here we have a woman announcer giving out details of the programmes in both Spanish and English.

There appears to be no interval signal, but the station closes down with the playing of one of Rudolf Friml's most popular songs, "*L'Amour, Toujours l'Amour*." Although this short-waver mostly gives its own programme, occasionally it carries out a relay from the studio of XETR, also at Mexico City.

Mention has frequently been made of YV1BC, Caracas, but less is heard of its competitor YV3BC, Las Barrancas, near the same city and which also broadcasts nightly on 31.55 metres (9,510 kilocycles). You might, however, make a note of the fact that this station transmits a special wireless entertainment on the eleventh of each month, specially destined to listeners in the U.S.A. The time is G.M.T. 02.30-05.00.

This transmitter has also been heard

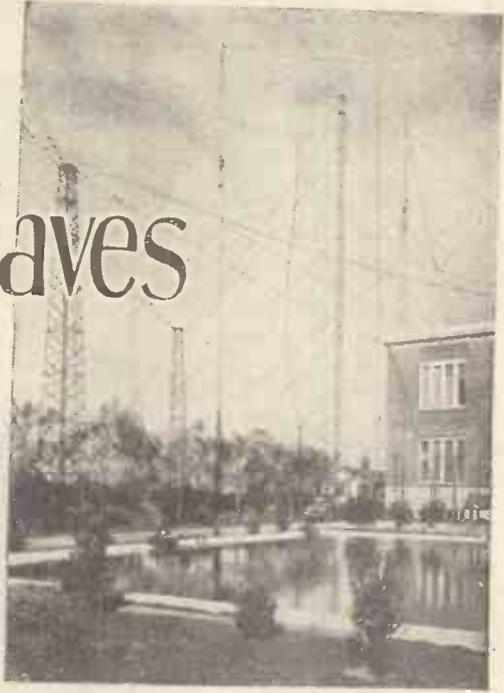

A fine group of aerials at the Monte Grande (Buenos Aires) commercial station, well-known for its short-wave activities

experimenting on 49.34 metres (6,080 kilocycles) and on 48.91 metres (6,134 kilocycles). The call usually incorporates the words: "Radio Difusoria Venezolana."

Slight alterations have again been made in the schedules of some North American stations. W8XAL, Cincinnati, now in possession of its new 10-kilowatt transmitter, works on 49.5 metres (6,060 kilocycles) in three "bursts," namely, from 11.00-15.30; 18.30-20.30 and 23.00-06.30 G.M.T.

W2XE, Wayne (N.J.) which broadcasts the Columbia programmes of the WABC, New York, studio, continues to operate on three different frequencies: 15,270 kilocycles (19.646 metres); 11,830 kilocycles (25.36 metres); and 6,120 kilocycles (49.02 metres), for which the times are respectively G.M.T. 16.00-19.00; 20.00-22.00 and 23.00-03.00 daily.

Another short-waver of the Columbia system, W3XAU, which relays WCAU, Philadelphia, works alternately on two channels 9,590 kilocycles (31.28 metres) daily from G.M.T. 16.00-22.00 and on 6,060 kilocycles (49.5 metres) from 01.00-05.00.

## Popular Canadian Station


Of the Canadians, VE9JR, relaying CJRX Winnipeg, is one of the most popular. A search for this station is facilitated by the fact that it is on the air from 14.30-03.00 daily, except Saturdays and Sundays. The actual times are G.M.T. 14.30-15.30; 16.00-16.35; 19.00-19.15; 20.15-20.35 and from midnight to 03.00. On Saturdays, in addition to the first two broadcasts, it operates between 17.45-18.15 and from midnight to 03.30 (Sunday morning); the Sunday transmission would be heard in the British Isles between G.M.T. 02.00-03.00.

Finally, if distance is no object, you might try for J1AA, Tokyo on 30.40 metres (9,862 kilocycles); it would be picked up between G.M.T. 09.30-12.40. The 38.07- and 19.36-metre channels usually given for this station are used for commercial purposes *only*. It would be worth while trying for this broadcast of Japanese entertainments direct; on a recent occasion they were relayed by Zeesen and fed to all the German transmitters.

## Building the

## 1934 Century Super

By The Experimenters

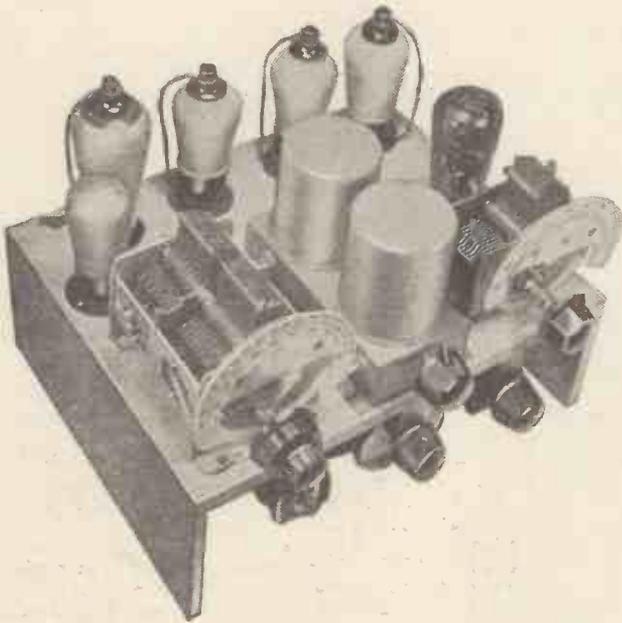

The completed 1934 Century Super, which takes advantage of the latest super-het technique

This week "The Experimenters" continue their instructions for building the 1934 Century Super, preliminary details of which appeared last week

LAST week we tried, in a simple way, to tell you what we thought of the 1934 Century Super—what it can do, why it can do it, and why you simply must make it. Whether you already have a super-het of some kind or you are going in for your first home-built set is immaterial.

If you are already using a super-het more than a few months old, it is almost certain to be obsolete after January 15, when the Lucerne Plan comes into action. Have you realised that the wavelength of London Regional will be 342 metres? Where is the most congested part of the waveband on your own set? It is almost bound to be between 340 and 350 metres. But things won't be so bad as they seem if your set is capable of dealing with the changing conditions.

#### Superlative Claims

Most of you will think twice about scrapping £10 or £12 worth of perfectly good components to build a new set—even if you can find one to build that you know will do the job. So many sets for the home constructor are claimed to give amazing selectivity and superlative quality that one is rather inclined to become sceptical and to overlook a really good set that lives up to any moderate claims made for it.

Being experimenters by nature, we have gone into the job of redesigning the Century

from the set-builder's point of view. We are making a lot of claims, but we are going to back them up by giving definite figures from which you will be able to judge the performance for yourselves. You see, we are not "sprucing"—we want to make you believe what we know—the 1934 Century Super will be the set of the year.

There are one or two little points that we want to explain before we tell you how to build the set. We can visualise so many of our readers taking up their copy of "A.W." and criticising the illustrations of the new set.

From experience we know that from nearly half of them the first words will be: "Another chassis set, why can't they use plain baseboards?" Why aren't chassis more popular? They are easier to handle than a baseboard—after you have got over the initial prejudice. All manufacturers use chassis—so does the knowing amateur if he wants his set to have that professional look about it.

The worst job with a chassis is the cutting of the holes for the valve holders, but this is because many of you don't go the right way about it. Some, or rather most, of you may not be blessed with too many small tools suitable for radio, but nearly everyone will have a brace and bit in the old tool chest.

Mark out all the holes on the chassis where the valve holders should go and churn these out with a 1-inch bit. You will find that the holes can be made very cleanly without any trouble. Use a fretsaw if you like, but we couldn't cut round holes this way.

Fix the valve holders first; this will give you a guide to the position of the other components. Leave the variable condensers and the band-pass coil unit until last, otherwise the chassis won't lay on flat when you are trying to screw on underneath the fixed condensers and whatnots. Scratch a line across the centre of the chassis; you will then be able to get the correct positions more easily.

Firstly, fix the brackets that hold the oscillator coil, volume control, and push-pull

switch. The oscillator coil must be in the middle, otherwise it will upset other components, but the other two brackets are not so important. Just arrange them on either side to look neat and tidy.

Then screw down the fixed condensers; there are eleven of them. This may sound a lot, but you can get at them without taking the skin off your knuckles.

Now about the whistle filters. There are two types you can use, the variable Kinva in the anode circuit of the L2DD or the Bulgin type LF26 in the loud-speaker circuit. If you have made any alterations to the layout you will most probably have to use the Bulgin owing to lack of space. How this filter is fitted can be seen on the next page.

#### Using a Whistle Filter

To go off the rails for a moment, any old set that suffers from whistles can be improved out of all recognition by using a whistle filter in the loud-speaker circuit. This Bulgin filter, by the way, is about the only type that can be added without taking the set out of its cabinet to make alterations.

Be careful how you fix the valve holders to carry the intermediate-frequency coils; this may sound Irish, but we do mean valve holders. If these holders are too low the coil cans will touch the bottom of the cabinet, and if too high, the cans will touch the valve pins, with dire results. Obtain the correct positions with the coils in the holders, and mark with a sharp edge.


That's about all for the underside of the chassis. The low-frequency transformer will almost fit itself; just see that the H.T. and P terminals face the back of the chassis, then fix with woodscrews.

All the fixed resistances are held in place by the wiring, so that there is no need to worry about these. We chose Ohmites because they are supplied with terminals—and you don't like soldering, do you?


Actually, this set can be built on the dining-room table—if the rest of the family will let you. There are no awkward jobs to do.

Now turn the chassis over. It is quite bare on top except for the six valve holders. The Wearite band-pass unit should be screwed down exactly in the middle, over the top of the line we told you to scratch. Screw it down about 1/4 in. from the front, otherwise when you get the set in the cabinet the knob will stick out through the front about 1/2 in. It doesn't look at all nice that way.

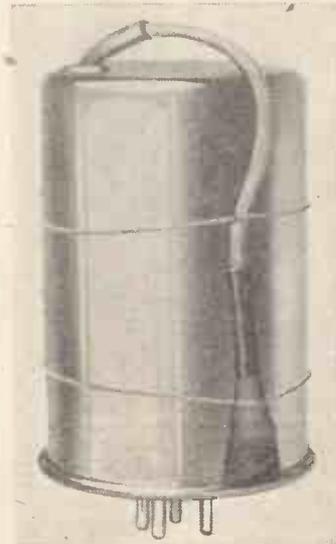Fix the double-gang condenser on the left-hand side of the coil unit and the single condenser on the right-hand side. The exact



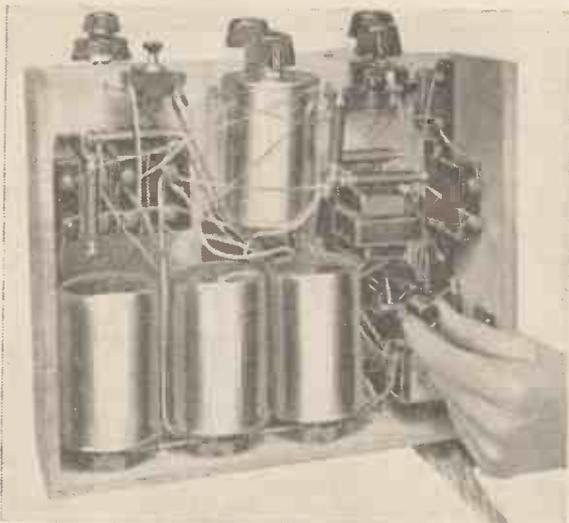How the pigtail on an old coil can be strapped to the side of the can out of the way



Note the compact arrangement of the parts on the underside of the chassis

positions are not important, but we suggest you line up the knobs with those of the push-pull switch and volume control.

Except for a few oddments, that completes the fixing of the components. The first oddment is the drilling of the holes for the metal-covered wire. Drill these holes from the top down through the chassis. We emphasise this point because we tried to drill them from the underneath and almost went through the valve holders.

Then drill two holes down the left-hand side of the two-gang condenser and one on the left-hand side of the single condenser. That's everything. The 1.5-volt grid-bias battery is fixed after all the wiring has been completed.

Like most people, we are a trifle lazy, so we always start on the easy wires first, although it's the wrong way about.

**Follow the Layout**

We started off by wiring up the band-pass coil, but the safest way is to follow the layout guide and go by numbers, so you won't miss any wires.

By the way, the Editor has arranged to supply a full-size blueprint of the set for 1s. 6d., post paid. Just send your application to AMATEUR WIRELESS Blueprint Dept., 58-61 Fetter Lane, E.C.4, and mention No. A.W.413.

A vital point is to earth the metal-covered wires which go through the chassis. If these wires are badly earthed they will cause crackles and perhaps a noisy background. See that the wires holding the Ohmites are as short as possible and quite taut otherwise the resistances might take a short walk and probably come into contact with something they shouldn't.

When you have put on the last wire and checked up with the blueprint, connect up the six- and four-way cables. You can please yourself how you use the various colours; you can make your own colour scheme.

On the four-way cable fix two wander plugs, marked H.T.+ and H.T.—. Follow the colours through and connect H.T.— to one side of the switch, and H.T.+ to the 2-microfarad fixed condenser. The two remaining cables are for the loud-speaker. Connect one to the anode of the Pen220A and the other to the 2-microfarad condenser. There is already the H.T.+ tapping on this condenser, so fix both of the connections very tightly, otherwise they may come off.

The six-way cable is not so easily disposed of; that's why

we left it till last—laziness coming out again. First join up two cables to two spade terminals marked L.T.+ and L.T.—. Take the L.T.— wire to the push-pull switch (it doesn't matter which point you use) and the L.T.+ wire to the filament leg of the oscillator valve holder. That leaves two spare points on the switch. Join one to the common side of the four fixed condensers—they are all lined up like soldiers—the last point being reserved for G.B.+.

That leaves you with G.B.—, G.B.—1, and G.B.—2. G.B.— goes to one side of a 1-microfarad fixed condenser. G.B.—1 is for the L2DD, and is connected to a grid leak, you can see it on the left, by the side of the whistle filter. G.B.—2 is easy; take it straight to the G.B.— terminal on the low-frequency transformer. Then fix the 1.5-volt bias battery and take two connections to the fixed condenser and the Ohmite, and the whole set is completed.

Now for the big moment—testing. You will want a high-tension battery of 120 volts (capable of giving about 20 milliamperes), a 16-volt grid-bias battery, and a 2-volt accumulator—the bigger the better. Unlike the original Century Super the voltages are distributed internally by means of resistances, so plug the two high-tension tapings into the negative and 120-volt sockets.

Join up the accumulator and then think about the grid-bias battery. G.B.— goes into the 1.5-volt socket; this is for the oscillator valve. Plug G.B.—1 into the 3-volt socket to apply bias to the triode section of the L2DD and finally apply 10.5 volts to G.B.—2 for the Pen220A.

By the way, don't get worried about the Mazda L2DD. It is only a normal low-frequency amplifying valve with two diode anodes in the same bulb. The idea is for one diode to act as a detector; the second is to provide the self-adjusting volume control voltage and the triode to boost the output from the detector diode. That's how we use the three-in-one valve.

When the intermediate-frequency coils are plugged in, make sure that they are a tight fit. To make quite sure, open the pins a little.

Some thousands of volt-milliammeters are sold every year, so it is not too much to assume that many of you will have some means of testing high-tension voltage and anode currents. If the set has been wired according to the blueprint and your high-tension supply is up to scratch you should be able to obtain approximately the following readings:—


Between the chassis and the anode of the oscillator valve, 115 volts. If you don't get this voltage, see that you have the right resistance in the anode of the oscillator valve; it should be 15,000 ohms. Go through the whole set and just check the anode voltages without any valves in circuit.

**Making Sure of Connections**

This will let you know whether or not your multi-way cables have been wired up correctly and that the fixed resistances are all in the right positions. The anodes of the first detector valve and those of the two intermediate-frequency valves are at the tops of the bulbs, so between this point and the chassis you should get a reading of 120 volts. The same applies to the anode of the Pen220A and to the auxiliary grid.

Don't forget to check the screen voltage of the two intermediate-frequency valves. This should be about 75 or 80 volts.

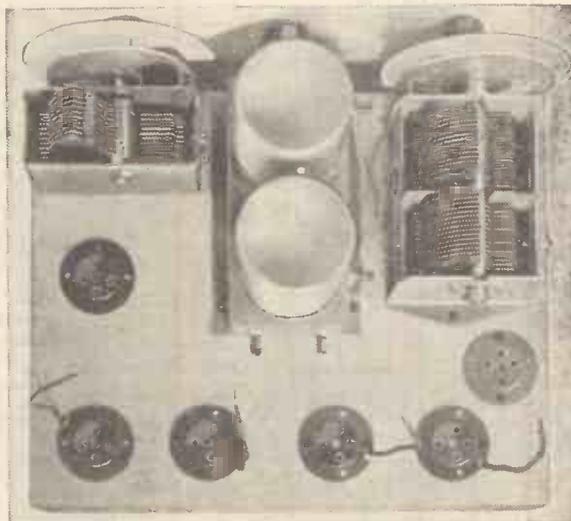It should be safe to insert the six valves at this point. The oscillator comes just behind the two-gang condenser on the left-hand side—it is a Mullard PM2DX. Just behind this is the first detector, a Mullard PM12A. In the centre of the chassis are the two intermediate-




The layout of the top of the chassis is particularly neat and clean as this plan view proves


frequency valves, both Cossor 220VS's. On the extreme right is the high-light of the set, the Mazda L2DD. The final valve is a Mazda Pen220A. All the valves, with the exception of the pentode, are metallised.

It is hardly worth-while saying much about operating, but in case of accidents, here are just a few hints. Pull out the main switch which connects up the low-tension, high-tension, and grid-bias batteries, and you will hear a gentle rustle in the loud-speaker. Tune the set in the usual way, but a little more slowly, for remember that the selectivity is in the order of 9 kilocycles.

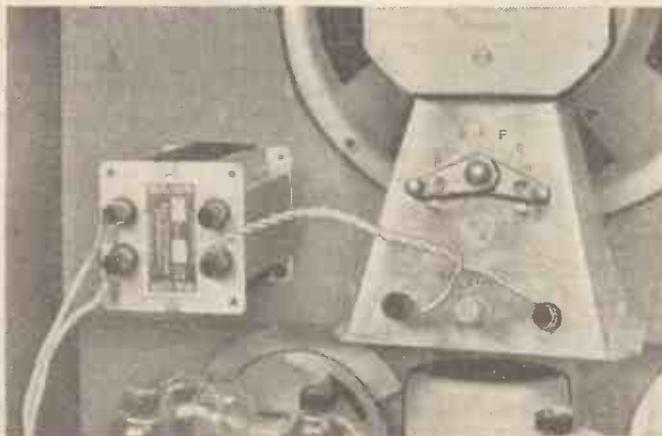In actual practice, this means that two stations which have a minimum separation of 9 kilocycles can be heard without mutual interference. To give an example, the London Regional station uses a



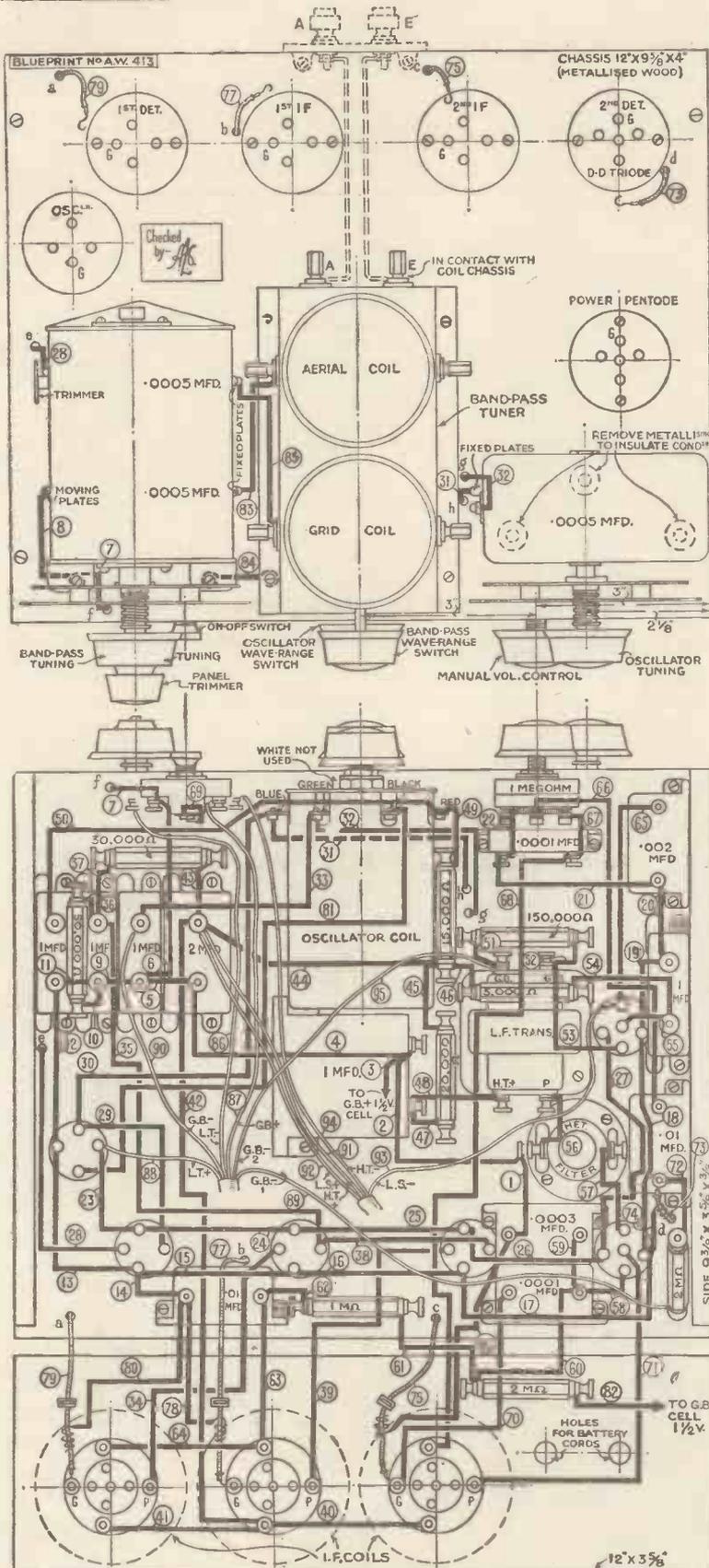How the Bulgin whistle filter can be screwed to the cabinet alongside the loud-speaker



This layout and wiring guide is reproduced at one-third scale. If desired a full-size blueprint can be obtained for 1s. 6d., post paid. Application should be made to "Amateur Wireless" 58/61 Fetter Lane, London, E.C.4.

frequency of 843 kilocycles, while Graz uses 852, a difference of 9 kilocycles. There should be no need for you to write to us to find out whether this set will be sufficiently selective for your aunt or any of your other relatives to cut out, say, Daventry, at ten miles, for you may rest assured that the Century Super will eliminate the local station in a degree or so, within a matter of a mile or two.

**HERE IS A LIST OF THE COMPONENTS NEEDED for "THE EXPERIMENTERS" 1934 CENTURY SUPER**

- CHASSIS**  
 \*1—Peto-Scott Metaplex, 12 in. by 9 3/8 in. by 4 in.
- COILS**  
 \*1—Wearite band-pass unit, type G.N.2.  
 1—Wearite oscillator, type Oz.
- CONDENSERS, FIXED**  
 \*2—Graham Farish .0001-microfarad (or Lissen, Telsen).  
 1—Graham Farish .0002-microfarad (or Lissen, Telsen).  
 \*1—Graham Farish .002-microfarad (or Lissen, Telsen).  
 \*2—Graham Farish .01-microfarad (or Lissen, Telsen).  
 5—T.C.C. 1-microfarad (or Graham Farish, Lissen).  
 \*1—T.C.C. 2-microfarad (or Graham Farish, Lissen).
- CONDENSERS, VARIABLE**  
 \*1—J.B. .0005-microfarad, type Nugan A.L.  
 \*1—British Radiophone two-gang, .0005-microfarad, type 458A.
- HOLDERS, VALVE**  
 \*4—Clix four-pin, chassis mounting.  
 \*2—Clix five-pin, chassis mounting.  
 3—W.B. four-pin, type Midget, (or Graham Farish).
- PLUGS, TERMINALS, ETC.**  
 6—Belling-Lee wander plugs, marked G.B.—1, G.B.—2, G.B.—3, G.B.—4, H.T.—, H.T.—+ (or Clix, Ealex).  
 2—Belling-Lee spade terminals, marked L.T.—, L.T.—+ (or Clix, Ealex).
- RESISTANCES, FIXED**  
 \*2—Graham Farish 5,000-ohm, type Ohmite (or Lissen, Telsen).  
 1—Graham Farish 15,000-ohm, type Ohmite (or Lissen, Telsen).  
 1—Graham Farish 20,000-ohm, type Ohmite (or Lissen, Telsen).  
 \*1—Graham Farish 30,000-ohm, type Ohmite (or Lissen, Telsen).  
 \*1—Graham Farish 50,000-ohm, type Ohmite (or Lissen, Telsen).
- \* Asterisks indicate parts needed for the new set which were not used in the original Century Super
- SUITABLE VALVES**
- | Make    | Oscillator | 1st Detector | Intermediate-Frequency (2) | 2nd Detector | Power    |
|---------|------------|--------------|----------------------------|--------------|----------|
| Mullard | PM2DX†     | PM12A†       | PM12M                      | —            | PM22     |
| Cossor  | 210Det     | 215SG        | 220VS†                     | —            | 220PT    |
| Mazda   | L2         | 215SG        | S215VM                     | L2DD†        | Pen220A† |
| Osram   | L21        | S23          | VS24                       | —            | PT2      |
| Marconi | L21        | S23          | VS24                       | —            | PT2      |
| Hivac   | D210       | SG210        | VS210                      | —            | Z220     |
| Lissen  | —          | SG215        | SG210                      | —            | PT240    |
| Tungram | L210       | S210         | —                          | —            | PP230    |
- †Valves used in "A.W." tests. All metallised except power.
- RESISTANCE, VARIABLE**  
 \*1—Igranic 1-megohm, type Megostat.
- SUNDRIES**  
 \*3—British Radiogram 2-in. metal mounting brackets.  
 \*1—Bulgin four-way battery cord.  
 \*1—Bulgin six-way battery cord.  
 \*1—Siemens 1.5-volt cell.  
 \*Connecting wire and sleeving (Lewcos).  
 \*3 ft. screened sleeving (Lewcos).  
 \*1—J.B. escutcheon.
- SWITCH**  
 \*1—Telsen four-point, type W153.
- TRANSFORMERS, INTERMEDIATE-FREQUENCY**  
 3—Wearite, type OT1.
- TRANSFORMER, LOW-FREQUENCY**  
 1—Lissen, type Hypernik (or Graham Farish, Telsen Ace).
- WHISTLE FILTER**  
 \*1—Kinva, type B (or Bulgin, type LF26).
- ACCESSORIES**
- BATTERIES**  
 2—Lissen 60-volt high-tension, type super power LN2005 (or Drydex, Ever Ready).  
 1—Lissen 16-volt grid-bias (or Drydex, Ever Ready).  
 1—Lissen 2-volt 40-ampere-hour accumulator (or Fuller, Ever Ready).
- EARTH**  
 1—Filt earth connector.
- LOUD-SPEAKER**  
 1—Blue Spot 45 P.M. (or W.B. type PM4A, Igranic, Rola with pentode transformer).

When you tune in a weak station you will notice a slight time lag of a fraction of a second. This is the self-adjusting volume control getting going.

Another point is the band-pass coil. This is of the latest type, and it causes the dial readings to be a shade out as compared with the oscillator. This is due to our retaining the old oscillator coil. We didn't think that it was worth another 18s. 6d., just to make these dial readings agree, but if you disagree with us you can change the coil if you like.

**Advantages of Self-adjusting Volume Control**

We haven't said much about the self-adjusting volume control and what it means to you. Imagine listening to a Continental station; a good example is Fécamp. Every few moments or so you have to jump up from a comfortable armchair to adjust the volume because of fading—one moment the volume is almost blowing your head off, and the next moment it is practically inaudible. A little of this soon spoils the programme.

With the self-adjusting volume control you vary the volume by means of the manual control to an agreeable level, and leave it. All variations are taken up automatically. During an evening the self-adjusting volume control can increase the entertainment value of foreign stations by as much as 50 per cent.

Finally, the variable whistle filter. This is simplicity itself. In the filter is a round metal core. If you want to cut off some high-pitched whistles, push the core in as far as it will go.

That's all. You've got the whole Christmas holidays in front of you. Make a good job of the 1934 Century Super!

**EFFICIENCY**

**UNIFORMITY**

**LONG LIFE**



You can appreciably improve the performance of your All-Electric Receiver, especially if it is two or three years old, by fitting the correct types of Cossor Mains Valves. Due to their advanced design and their famous Mica Bridge Construction, Cossor Mains Valves possess remarkable efficiency, uniformity and long life. Your dealer will tell you the types you need to make your Set like new again.



# COSSOR

## A.C. and D.C. MAINS VALVES

COSSOR A.C. MAINS VALVES (4 Volt Indirectly Heated Cathodes)

Type	Purpose	Impedance	Amp. Factor	Mut. Con. m.a./v.	Price
*†M.S.G.-H.A.	Super H.F. Amp'n	500,000	1,000	2.0	17/6
*41 M.S.G.	Super H.F. Amp'n	400,000	1,000	2.5	17/6
*†M.S.G.-L.A.	Super H.F. Amp'n	200,000	750	3.75	17/6
*†M.V.S.G.	Variable Mu S.G.	200,000	—	2.5	17/6
**M.S./PEN.-A	H.F. Pentode	—	—	4.0	17/6
*†M.S./PEN.	H.F. Pentode	—	—	2.8	17/6
*†M.V.S./PEN.	Variable Mu H.F. Pentode	—	—	2.2	17/6
*41 M.D.G.	Bigrid	40,000	10	.25	19/-
**D.D./PEN.	A.V.C. (Detector and L.F. Amp.)	—	—	2.7	20/-
**D.D.T.	A.V.C. (do.)	17,000	41	2.4	15/6
41 M.R.C.	R.C.C. or Det.	19,500	50	2.6	14/-
*41 M.H.	Detector	18,000	72	4.0	13/6
41 M.H.F.	H.F. or Det.	14,500	41	2.8	14/-
*41 M.H.L.	Det. or H.F.	11,500	52	4.5	13/6
41 M.L.F.	Low Frequency	7,900	15	1.9	14/-
41 M.P.	Normal Power	2,500	18.7	7.5	14/-
41 M.X.P.	Extra Power	1,500	11.2	7.5	16/6
*M.P./PEN.	Pen. Power Output	—	—	3.5	18/6
*P.T. 41B	Pen. Power Output	—	—	2.25	22/6
*P.T. 41	Pen. Power Output	—	—	3.0	18/6

COSSOR D.C. MAINS VALVES (16 Volt 0.25 amp. Indirectly Heated Cathodes)

Type	Purpose	Impedance	Amp. Factor	Mut. Con. m.a./v.	Price
*†D.V.S.G.-	Variable Mu S.G.	—	—	2.5	17/6
*D.H.L.	Detector	13,000	58	4.5	13/6
D.P.	Power Output	2,800	17	6.0	15/-
D.P./PEN.	Power Pentode	—	—	3.5	18/6
*D.S./PEN.	H.F. Pentode	—	—	3.0	17/6
*D.V.S./PEN.	Variable-Mu H.F. Pentode	—	—	3.0	17/6
**D.D.T.16	Double Diode Triode (A.V.C.)	16,000	40	2.5	15/6

\*Supplied with Plain or Metallised Bulbs. \*\*Stocked with Metallised Bulb only. † Characteristics measured at -1.5 Grid Volts. ‡ Directly heated filaments. Prices in this List do not apply in I.F.S.

**FREE!**

**72 PAGE WIRELESS BOOK**

From cover to cover this new Cossor 72-page Wireless Book is packed full of useful and interesting information — latest circuits — explanations of technical terms — list of broadcasting stations, etc. Send at once for free copy. Please use the coupon.

To A. C. COSSOR LTD., Middy Dept., Highbury Grove, London, N.5  
Please send me free of charge, a copy of the Cossor 72-page Wireless Book.

Name .....

Address .....

B.V.33 A.W. 16/12/33 .....

# A RADIO EXPERT FOR



The SHERLOCK HOLMES of RADIO

# 12/6

## Answers every Radio question!



The "All-in-One" Radiometer is sold at all good radio shops.

Issued by PIFCO LTD., High Street, Manchester and 150, Charing Cross Road, London, W.C.2.

The "All-in-One" Radiometer solves every radio problem, traces any trouble and ensures 100% reception at all times from any battery-operated radio set. Yet it costs only 12s. 6d. Isn't that a very small price to pay for such service? There's no instrument in the world at anywhere near the price which makes all the tests the "All-in-One" Radiometer makes. You can't afford to be without one—it will save you pounds a year.

# PIFCO ALL IN ONE RADIOMETER

© R.5

YOU CANNOT BUY A BETTER VALVE..... NO MATTER WHAT YOU PAY



Insist on, and see you get genuine TRIOTRON VALVES... Definitely better, yet they cost less! Write our Technical Dept. for advice on all Radio matters.

# TRIOTRON VALVES

To TRIOTRON RADIO CO., LTD.

Triotron House, Bloomsbury St., LONDON, W.C.1.

I enclose 2d. stamp. Please send your Big New Catalogue and Radio Guide, to:—

Name .....

Address .....

Use sealed envelope 1½d. stamp.

A.W.3

Post this Coupon FOR YOUR

## FREE GIFT



## Smoke

# PLAYER'S AIRMAN MIXTURE

## The finest mixture

## at 10<sup>D</sup> per oz

ALSO PLAYER'S 'AIRMAN' NAVY CUT DE LUXE AT 11<sup>D</sup> PER OZ.

P.A.32

# On Your Wavelength!

By Thermion

### The Five-bob Battery

NOT long ago a correspondent told me of a wonder battery, a 120-volter, that he and others were buying for the sum of five shillings. He reported that his present one had been working a three-valve set—screen-grid, detector, and small power valve—for ten weeks at not less than seven hours a day and wasn't half done yet.

I hoped to go across to see what the real voltage of the battery was after ten weeks, but, unfortunately, my free times and his didn't fit in; so it couldn't be managed.

However, I found out from him where the battery could be obtained, and a couple of days before these notes were written I blued five bob on one, which is now undergoing a laboratory test. This test consists in running it for four hours a day through a fixed resistance that gives an initial load of 10 milliamperes. I will report week by week what its doings are.

### What the Voltmeter Says

WHEN it arrived the five-bob battery showed an E.M.F., as taken with a high-resistance laboratory voltmeter, of 122.7 volts when under no load. Immediately it was placed under a load of 10 milliamperes this fell to 121.6 volts.

At the end of its first four-hour run the reading was 111.8 volts. A drop of all but 10 volts during its first four hours of service doesn't seem to point to a very long life.

Just before I began to write this morning it was brought into action once more. It had picked up somewhat during its twenty-hour rest, for the reading was 118.0 volts.

At the end of half an hour this had fallen to 112.2 volts and when its work for the day was done the voltmeter showed 109.0 volts. Remember that this is under the most favourable conditions possible; almost constant temperature and a full twenty hours' rest between working periods.

### Wireless Peace in France

FRANCE'S long-promised regulations against man-made interference have at last become law. But it is one thing to make wireless regulations and another—particularly in France—to enforce them. On paper the law is excellent, since at first sight it compels

users of any apparatus whatever that is found capable of radiation to have it rendered innocuous.

There are, though, a good many exceptions, and once any law contains loopholes it is weakened from the very start. It is to be hoped that some good will come of this piece of legislation. Its results will be watched with great interest by the authorities in our own country, who are thinking of bringing in legislation on the same lines.

Don't ask me when this happy event will take place. At present matters are in the exploring - every - avenue - and - leaving - no - stone - unturned - in - order - to - find - a - formula stage.

### New Wireless Word

MEANTIME, the French have coined an entirely new wireless word, which will probably be borrowed by us in course of time. To render electrical apparatus non-radiating by means of suitable appliances is, when you come to think of it, a rather cumbersome expression, but it is about the best that we can do at the moment.

The French call it quite simply anti-parasitising, or deparasitising. Neat and effective, I think.

### Thrilling Broadcast

SELDOM have I listened to a more exciting broadcast than the running commentary on the Harvey-Petersen fight. It was extraordinarily well done, for the commentator never let his own excitement run away with him, as sometimes happens.

Through him we were able to follow the whole course of the fight in the most vivid way and to share the final thrill. Something, though, went wrong when the assistant commentator tried to make use of the microphone, for then such distortion occurred that his words were barely intelligible.

Probably the mike was wrongly placed, a matter which will doubtless receive attention on future occasions.

### Who Took the Alternative?

IT was rather sad that the alternative to the big fight was one of those political talks. I felt quite sorry for the talker, for I couldn't help wondering just how many of the six million receiving sets in use were tuned to the wavelengths allotted to him.

I am afraid that the counter-attraction must have been too strong for him to have had much of an audience.

### Budapest Excels

BUDAPEST'S new 120-kilowatt transmitter is now in full operation and the station's programmes are magnificently received in this country. I was quite sure that they would be, for the old 18-kilowatt transmitter was pretty good after dark, and for some weeks prior to the opening of the new giant I had been listening to test transmissions, some on reduced and some on full power.

By the way, amongst the most attractive broadcast items from the Continent are the tzigane concerts which Budapest relays about three times a week. If you are not already familiar with them, you have a splendid chance now of discovering for yourself just how good they are.


### Idea for "The Experimenters"

IF "The Experimenters" want a new field for investigation, here's an idea for them. There is no doubt that our present standard intermediate frequencies in super-heterodynes of 110 and 126 kilocycles are not too satisfactory, for, unless rather elaborate filtering circuits are used, second-channel interference is apt to be a nuisance.



Henry Hall playing over a piece of music with the St. Dunstan's Dance Orchestra, which has been invited by the Prince of Wales to take part in a Christmas Party at York House
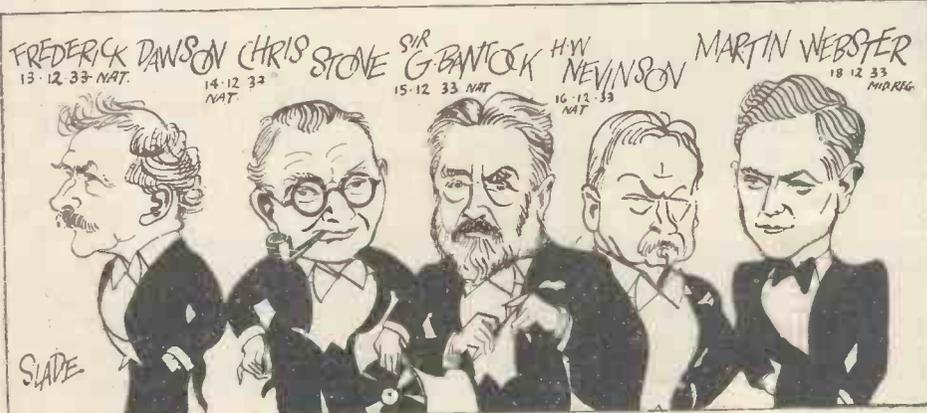
## Listen to These Broadcasters - - - - - By Slade



Can a better frequency be found? I think that quite possibly it can. The whole problem is to find a frequency so high that second channels, when they do occur, will fall outside the limits of the medium wave-band; yet it must not be high enough to spoil the performances of the set when operating on the long waves.

A frequency in the neighbourhood of 300 might be well worth investigating, and I know

that one or two firms of manufacturers are ready to make up intermediate-frequency transformers tuned to any required frequency. What about it, "Experimenters"?

### Don't Worry About Wavelengths

ARTICLES which have appeared in certain of the lay papers may have dealt something of a blow to Christmas wireless sales by suggesting quite erroneously that sets bought or made now will be more or less out of date when the new wavelengths come into force on January 15.

I know quite a few people who thought of putting off purchases for a month or two until I explained the position to them. The new order of things will not make the slightest difference to present receiving sets, except that the station-name tuning dials will not give accurate indications. But, as they never do, I don't see that that matters very much.

Some firms are arranging to supply corrected dials at a nominal price, whilst others, as a temporary measure, are giving free to owners of their sets printed slips showing the approximate readings of stations under the new scheme. In any case, it will probably be midsummer before stations have settled down to their wavelengths, and the wise man will wait till then before changing his dial.

### Station-list Suggestion

HERE'S an idea for a very simple method of dealing with the situation after January 15. Make a list in two columns, one headed "Stations" and the other "Tuning Position." In the first column write in the biggest and best European stations, or those that you normally receive, in their new wavelength order. In the second, show the position of the pointer needed to bring them in under the Lucerne Plan.

Thus the London Regional, which drops from 356 metres to 342.1 metres, would probably appear in column 2 as "Between Brussels No. 2 and Strasbourg." Similarly for Langenberg column 2 might show "Just below Beromünster," and for Heilsberg "Between the Scottish National and Hilversum."

A list of this kind won't take long to compile and, once you have made it, tuning will be simplicity itself. Further, you can always keep it up to date by making any necessary alterations from time to time.

### Radiograms at Christmas

AT Christmas time the radiogram can be pressed into service as a provider of all kinds of fun. A large variety of special records has been prepared for the purpose. One of these contains extracts from a score of classical airs and the game is to see who can correctly name the greatest number with their compositors. Identifying every-

day noises is another good one and there is a really exciting race game on records. Forts and comic fortune-telling also figure, and if you have a taste for astrology there are predictions by a well-known expert.

By the way, if you want a really funny record there is an old one that I can strongly recommend, if you don't already know it. This is "Laughing Gas," and if it doesn't make you laugh—the second side, anyhow—I am prepared to eat it.

### Wireless Fan's Elbow!

IS mine the first case of radio's very own disease?

Many other trades, professions, and hobbies have ailments peculiar to themselves, but so far wireless has appeared to be innocent. Well, here's what happened to me. For years I have been in the habit when sitting at the controls of leaning hard on my left elbow. It began to be painful and eventually developed a kind of bunion which called for treatment by the family medicine man.

Just in case you would like to know, he called it an olecranon bursitis. To disarm criticism at the outset, let me state emphatically that it was caused by putting down the elbow, and *not* by lifting it.

### Tip for Terminals

IT is extraordinarily difficult, as you have probably found, to screw down the round milled nuts supplied with certain components so that they really *are* tight. Or perhaps I should say so that they remain tight. If you want your connections to stay put, as no doubt you do, here's a tip worth remembering.

Provide yourself with a dozen or two full-thickness hexagon nuts in both 4B.A. and 6B.A. sizes, scrap the round nuts, and use these instead for your connections. Turn them down with a box spanner and you

needn't have any fear of their working loose.

It is really worth while to do this when you are building a set, for I suppose that more than half the faults that can plague the constructor are due to screwed-

down connections that have come partially or completely unstuck.

### Adding Punch to Filaments

A FRIEND whose knowledge of wireless is, to say the least of it, sketchy, wrote for my advice on a little problem the other day. He didn't seem, he said, to be getting enough punch out of his set, so he proposed to add some by substituting a 4-volt accumulator for his present 2-volter.

Didn't I think it was a good idea? My reply was that the suggested punch would unquestionably be a knock-out blow, with five valves taking the count.

### Wireless Eliminators

NOWADAYS the term eliminator is usually applied to the gadget which supplies us with high tension from the mains, though whether it is the dry-cell battery which is supposed to be "eliminated"—or the hum from the mains—is a matter of some doubt.

In the early days I remember the same word was used to describe either a rejector circuit, or a couple of balanced crystals, or some similar arrangement for cutting-out atmospheric and other "parasitical" disturbances, and in this respect I think the name was well chosen.

### Kerr Cell's History


THE Kerr cell, though quite an up-to-date refinement in television, is based on a discovery which dates back to 1886, when it was found that a polarised ray of light could be "depolarised" by passing it through carbon bisulphide under the influence of an electric field. The stronger the field, the more illumination gets through, and vice versa, so that the arrangement acts as a very convenient form of light "control."

Actually the carbon bisulphide converts the plane-polarised light into an elliptically-polarised ray. As the applied signals get stronger, the ellipse becomes more nearly a circle, in which condition the maximum amount of light gets through on to the viewing screen. Another striking instance of a scientific "dug out" coming back to active service!
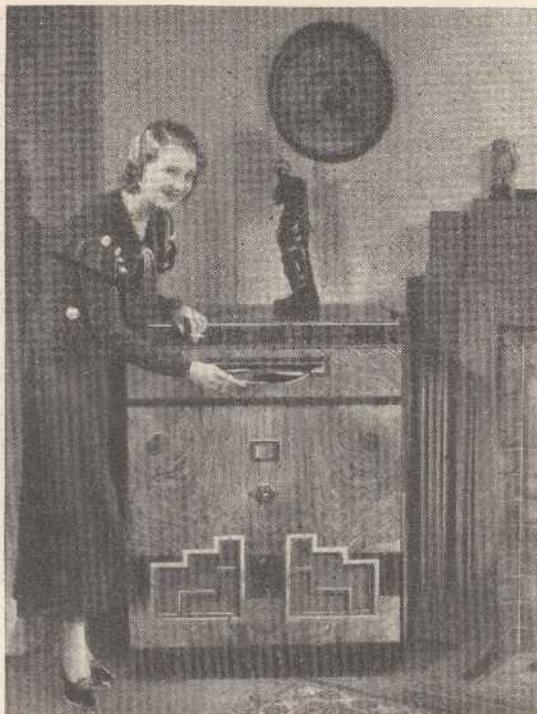
### Mystery of Valve Life

MOST people find that two pairs of boots used alternately will outlast two single pairs worn out in succession. I am not quite sure why this should be so, but apparently the same rule applies to valves.

A friend of mine assured me the other day that his set of valves had lasted for four years, and were still going strong. Of course I know very well that some valves put up a very good show—particularly the battery-driven variety which, as a rule, seem to enjoy greater longevity than those on the mains. All the same, one must expect a serious falling-off in performance after four years, and I was proceeding to advise him to replace them at once when he "spiked my guns" by explaining that he had invested in a "duplicate" set of valves from the beginning, and had changed them over regularly once a week ever since.



### New Automatic Record Changer

is very original as it overcomes many of the defects which at the moment appear to be inherent in other types of changer. The Collaro unit costs £6 17s. 6d. in chassis form or £8 17s. 6d. as a table model.

Collaro claim that to play gramophone records with their equipment is as easy as posting a letter and very similar in operation. The gramophone record is simply pushed through an opening in the front of the cabinet, the changer completing the job and rejecting the record after it has been played through.

The salient features of this invention are that it would convert any radio set into an automatic radiogram; it will play 9-in., 10-in., and 12-in. records mixed up in any order; the lid of the cabinet need never be opened for either record or needle changing; and there are no controls to operate.

At the moment, it is only available for A.C. mains.

FOR the amateur to make his own radio gramophone with an automatic record changer does seem to be rather an ambitious project. The trouble appears to be not so much in the design, but in the cost of the automatic record-changing equipment.

We are pleased to record that a new automatic changer has been developed and finally marketed by Collaro, Ltd. This idea

# Programme Items for Your Entertainment



Enjoying radio at a pre-Christmas party with the Marcomphone 274 radiogram

Wednesday, December 13

**NATIONAL.**—Symphony concert relayed from Queen's Hall.

**London Regional.**—"On the House," a Radiovaria programme by Godfrey M. Hayes and F. Keston Clarke. The cast includes the Three Ginxs.

**Midland Regional.**—Rushden Temperance Band conducted by Thomas Young; Eddie Robinson will entertain with Lancashire sketches. The Ross-on-Wye Orpheus Society concert.

**West Regional.**—"The Exile," a Welsh concert. Christmas music by the University of Bristol Madrigal Singers. Pianoforte solos by D. E. Pitcher.

**North Regional.**—Orchestral and choral.

**Scottish Regional.**—The Falkirk Octet Party,

## International Relay on Christmas Eve

**PURSuing** its motto "Nation Shall Speak Peace Unto Nation," the B.B.C. has arranged a very interesting international broadcast for Christmas Eve.

Taking part in this special programme, which will be broadcast from the Nationals at 8 p.m., will be studios in New York and London, as well as the famous bells of Bethlehem and a service from Winchester Cathedral.

At present the exact make-up of the programme is being kept a secret, and the B.B.C. does not intend to enlighten listeners until Christmas Eve actually arrives. The element of surprise will certainly add to the interest of this broadcast.

Considerable technical skill will be needed to make the broadcast a real success. The various points in England, in America, and Jerusalem, will all be linked to the Control Room at Broadcasting House.

directed by John Trapp. The Falkirk Trades Band conducted by John Faulds.

**Belfast.**—Symphony concert relayed from London. The Mayfair Glee Singers in the afternoon.

Thursday, December 14

**National.**—Recital of Albert Roussel's music.

**London Regional.**—*By Royal Appointment*, a revue. Producer, C. Denis Freeman; B.B.C. Theatre Orchestra and revue chorus, conducted by Mark H. Lubbock.

**Midland Regional.**—*Cards on the Table*, a one-act comedy by Vernon Sylvaine. Cheltenham Spa Octet directed by Arthur Cole. Part of Handel's *Messiah* by the Nottingham Philharmonic Society, with London Symphony Orchestra, conducted by Sir Hamilton Harty.

**West Regional.**—*Mid-summer Morning*, a one-act play by A. O. Roberts; action takes place on the summit of Snowden. Also *Y Mynydd (The Mountain)*; all items of this programme will deal with the mountain.

**North Regional.**—A relay of variety from the Grand Theatre, Blackburn. *The Messiah*; first party by the Halifax Choral Society and the second party by the North Staffordshire district Choral Society.

**Scottish Regional.**—Vocal and instrumental recital.

**Belfast.**—Recital of music for harp, flute and violoncello.

Friday, December 15

**National.**—*The Path of Glory*, a war play in which both sides are determined to lose for economical reasons. Producer, Lance Sieveking.

**London Regional.**—Chamber concert (No. 5) from Concert Hall, Broadcasting House.

**Midland Regional.**—Midland Composers, Gustav Holst (No. 19).

**West Regional.**—Orchestral concert.

**North Regional.**—Microphone Tour No. 1.

**Scottish Regional.**—John MacArthur Quintet; Juliette McLean will take part. Peeblesshire Shepherds Annual Dinner—you can expect some good stories.

Saturday, December 16

**National.**—Special variety programme—Alexander and Mose, Sandy Rowan and Florence Oldham.

**London Regional.**—*The Path of Glory*.

**Midland Regional.**—A carol concert by the City of Birmingham Choir; Stuart Robertson, soloist.

**West Regional.**—*The Messiah*, parts 1 and 2, relayed from the Colston Hall, Bristol.

**North Regional.**—Light instrumental recital.

**Scottish Regional.**—Variety programme—Tommy Morgan, Denis Emons (light songs), Nora K. Mitchell (Scottish humour) and Tommy Yorke (comedian) are taking part.

**Belfast.**—*Between Two Stools*, an Ulster Comedy by J. H. McIlveen.

Sunday, December 17

**National.**—Choral programme by Wireless Singers. Viola recital by William Primrose.

**London Regional.**—Service from St. Andrew's Presbyterian Church, Eastbourne. Mozart pianoforte concerto by Myra Hess, in orchestral concert.

**Midland Regional.**—Midland composers, Basil Harwood (No. 20). Relay from the Church of the Messiah, Birmingham.

**West Regional.**—Carol Service from the Royal Naval College, Dartmouth. Choir entirely of cadets, officers and masters.

**North Regional.**—B.B.C. Orchestra, conductor Adrian Boult.

**Belfast.**—Oratorio, Mendelssohn's *Elijah* (Part II).

Monday, December 18

**National.**—*A Christmas Carol*, full-size presentation lasting over an hour. Seymour Hicks as Scrooge.

**London Regional.**—Police band concert.

**Midland Regional.**—*Daylight Robbery*, a burlesque by the Melluish Brothers; producer, Martyn Webster.

**West Regional.**—Last of the "Let's Do a Play" series. Scenery and lighting will be the topic.

**North Regional.**—Police band concert from London.

**Scottish Regional.**—Bonnybridge and District Prize Silver Band.

**Belfast.**—Orchestral concert.

Tuesday, December 19

**National.**—Chamber music.

**London Regional.**—*A Christmas Carol*.

**Midland Regional.**—A band concert.

**West Regional.**—Swansea Orpheus Choral and Orchestral Society's first concert of the season. *A Christmas Gambol*, by Richard Gwinnet, an eighteenth century comedy.

**North Regional.**—Pantomime rehearsal of Laidler's *Cinderella*; short relay from Theatre Royal, Leeds. Harold Bradbury, tenor.

**Scottish Regional.**—"Scotland To-day and To-morrow"; John Highton, who gave the first broadcast of the series, will sum up. The Heather Sextet and a short Handel recital by W. Watt Jupp.

**Belfast.**—Orchestral concert.

## High Spots of Xmas Broadcasts

**THIS** year the B.B.C. is making special efforts to give listeners a really first-class series of Christmas radio broadcasts. No effort has been spared to provide suitable fare for the festive season.

Perhaps the biggest high spot of the Christmas broadcasts will be the pantomime of *Sindbad the Sailor*, an old-time affair with an excellent cast as announced last week. On the Nationals this panto will first take the air at 7.45 p.m.

In that night's appeal, Mr. Lloyd George will speak on behalf of that very deserving cause, the Wireless for the Blind fund.

A programme of Gilbert and Sullivan will be another high spot of Christmas Day.


Henry Hall will conclude the Christmas Day broadcasting by supplying you with plenty of dance music—specially chosen so that you can dance to the strains of the loud-speaker.

On the Regional wavelength there will be "Hey Ho the Holly"—a goodly mixture of literature and music for the slightly higher-brows.



Myra Hess

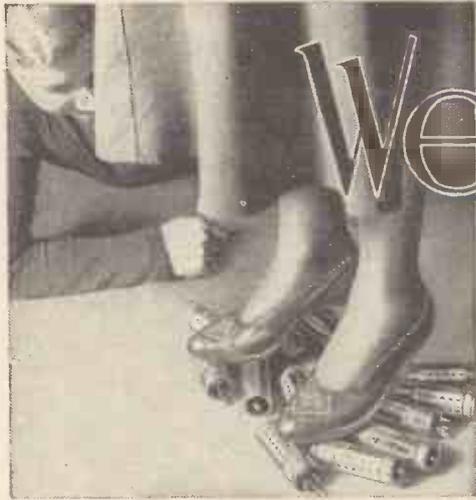Conducted by J. H. Reyner, B.Sc., A.M.I.E.E.




Demonstrating the strength of Catkin valves

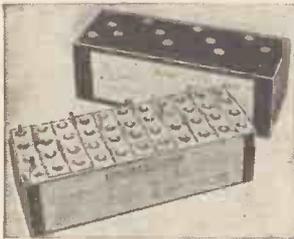**NONFADE SECTIONAL HIGH-TENSION BATTERY**

**I**N this new type of high-tension battery each cell is replaceable in the event of its developing a high internal resistance. The individual cells are quite normal in appearance, being contained in small zinc cans, and when assembled in a battery are insulated from each other.


The batteries are supplied unassembled, but the process of assembling and connecting up is



A 66-volt Nonfade high-tension battery

extremely simple and such that anyone can undertake it. The battery may be obtained in three sizes—66 volts, 108 volts, and 126 volts. The refill cells are available with different coloured filling compound, thus enabling the user to be quite certain which portion of the battery has been renewed at any time.

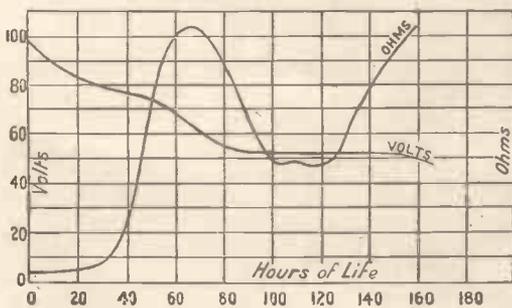**Test Results.**—The battery tested was a 66-volt size, but the results have been plotted on the basis of 100 volts, as is our usual practice. The chart accompanying this report shows the variation



Performance curve of the Nonfade 66-volt battery

# We Test for You

of voltage and internal resistance over the working life of the battery. It will be seen that the voltage drops somewhat rapidly at first, but thereafter somewhat more slowly until the cut-off point, which occurs after about 160 hours of life.

The internal resistance is initially fairly low, but then rises very rapidly, dropping again till the cut-off point, where a very rapid rise occurs. The milliampere-hour capacity of the battery was approximately 1,200, which is just up to standard.


Blue Spot loud-speaker of fairly recent design.

On the chassis are mounted the driver transformer and the various terminals for grid-bias, accumulator and high-tension battery in addition to the seven-pin valve holder. There is also provided a tone-control switch and plug for use of an extension loud-speaker.

No output choke or transformer is provided as some of the Blue Spot loud-speakers are already arranged for class-B opera-

generally satisfactory in use.

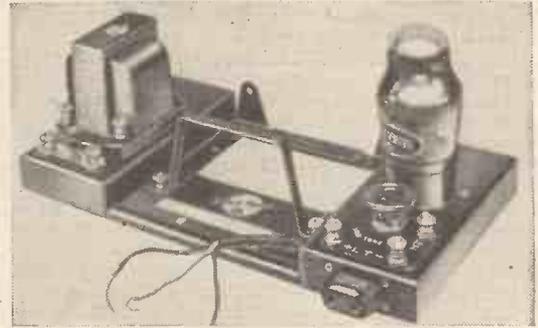When an extension loud-speaker is used, care should be taken to ensure that the resultant load imposed by the two loud-speakers is in parallel on the output valve is



Blue Spot class-B adaptor unit

**Test Methods Explained**

**High-tension Batteries**

**T**HERE are many methods of testing high-tension batteries, but for present purposes obviously the best is that which tests the battery under conditions which approximate to actual practice.

Of the two methods in general use, one puts a constant load on the battery and allows it to discharge continuously, while the other loads the battery for eight-hour periods with sixteen-hour rest periods between. The last method is the one employed for the tests published in these columns.

The method, then, is to select a portion of the battery under test, and having measured the voltage with no load, to connect across it a such known resistance that the current is 9 milliamperes in the case of the standard-capacity battery, and 18 and 27 milliamperes respec-

tively for double and triple sizes.

The initial value of 9 milliamperes is chosen because the average discharge current over the life of the battery is then approximately 7 milliamperes, the rated current for single-capacity size. The same argument applies for the other sizes.

The internal resistance and load voltage of the battery are measured during each eight-hour discharge period, and the results reduced to the standard of a 100-volt battery are plotted in the form of a curve which shows at a glance the behaviour of the battery. The end of the useful life is assumed to have been reached when the voltage has dropped to 50, at which point it is found that the internal resistance has usually reached a value in the neighbourhood of 1,000 ohms.

correct or distortion and lack of sensitivity may result.

Makers: British Blue Spot Co., Ltd. Price: £1 9s. 6d. and £1 17s. (including output choke).

**ERIE TUBULAR CONDENSERS**

**T**HE new Erie tubular condensers are made up in small lengths of paxolin tube approximately 3/8 in. in length, which is about the same as the well-known Erie composition-type resistances. These condensers are available in almost any value, the smaller sizes having a diameter of 5/32 in. and the larger values slightly more. They are provided with approximately 1 3/4 in. of thin copper wire to enable them to be wired easily direct into circuit. They are all tested at 1,500 volts D.C.


**Test Results.**—The four samples tested were rated at .0002, .0003, .0005 and .01 microfarad. The measured capacities

In order to facilitate testing for dud cells a small gadget is supplied which consists simply of a flash-lamp bulb fitted in a small holder. Makers: Nonfade Battery Works. Price: 66 volts, 5s. 6d.; 100 volts, 7s. 6d.; 126 volts, 9s. 6d.

tion. In the event of a loud-speaker being used which is not so arranged, a special output choke is available for fitting to the chassis, the extra cost being quite small.

The circuit of the adaptor is suitable for all types of class-B valve, including those requiring a small amount of grid bias; in fact, the adaptor is quite universal and can be used in most circumstances.

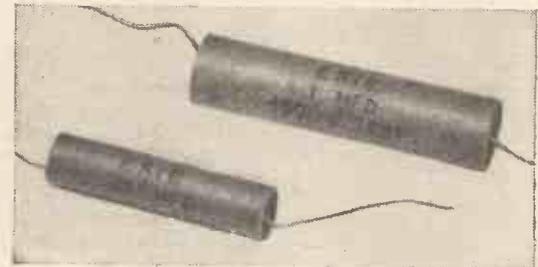**Test Results.**—The adaptor was tested under the maker's specified conditions with both biased and unbiased class-B valves and it was found to be



Two Erie tubular fixed condensers

were found to be .00023, .00028, .00047 and .011 microfarad, which values are in fair agreement with those given by the makers. No sign of leakage was found when the condensers were tested on 500 volts. Makers: Radio Resistor Co. Price: .0001-.0006 microfarad 1s.; .01 microfarad 1s. 3d.; .02-.25 microfarad 1s. 6d.

**BLUE SPOT CLASS-B ADAPTOR**

**T**HIS new Blue Spot adaptor has been designed especially for use with Blue Spot loud-speakers. It is built up on a metal chassis which provides space and fixing lugs for mounting any

# Radio Christmas-1999 A.D.



DEREK ENGLAND Peeps Into the Future

COME with me to this Christmas party (yes, we've been given a couple of invitations) and see how radio has changed social habits.

1999 A.D.!

It's late on Christmas Eve, and being dark you can't see the outline of our host's house clearly; but it strikes you as futurist, though not cubist, as was the "modern" style in 1933. By 1999 we have become thoroughly practical again, for cubes are so uncomfortable!

We are the first to arrive, so there's plenty of time to look round before the cocktails are handed out:

It still looks like Christmas, although it's 1999!

Although the room is deserted, the lights are not switched off. You notice that there are no electric-light bulbs, for the light comes from rows of tubes built into the walls and ceiling, somewhat like the neon-gas advertising signs we used to know sixty-six years ago.

"I've just had this Raylite installed," explains the host, "as everybody else in the road has it, and my wife would insist."

He continues, and explains. The natural daylight comes from the incandescent gas in the tubes. The electricity is never switched off, for there is a photocell control by the windows which turns the light up brighter as daylight fades so that the room is always constantly brilliantly lit.

Radio must take a big place in the modern villa, and just as you're wondering where the set is, the proud houseowner continues:

"This Raylite gas, y'know, old man, is the stuff they discovered ten years ago for radio . . . you know, the stuff on which they project the pictures."

You don't know, of course, and a blank look conveys as much.

He turns to a dial and very slowly one end of the room glows a vivid white. The effect is electrical. You could not say that the light was on the wall, nor from which direction it was coming. It is simply that this part of the room is ten times as brilliantly lit as the daylight part.

Built into the wall is a little panel with a dial like an automatic telephone. He refers to a directory card for the number and dials it. Then the magic happens.

The brilliantly lit part of the room takes shape and parts become darker. Figures can be seen moving about in the brilliant glow, and within five seconds you can see that a man and a woman are doing a vaudeville act at the end of the room. If there were not a slight lack of solidity you would be quite sure that they were in the room, for the speech and music are absolutely natural; but although they are pictures standing out in stereoscopic relief, you can see that they are not quite the living thing.

"Surely," says our host, "you have seen this before? Why, it's almost as old as loud-speakers!"

Another blank look, which compels him to explain.

The Raylite gas fills one end of the room and the television pictures received by the radio set which we have not yet seen is projected on to the vapour which, although invisible, causes a life-size three-dimensional picture to be built up in natural colour.

There's nothing for it but to make a clean breast of matters. Sorry, we've been out of touch with radio for many years; too busy, and all that. Our host is condescendingly sympathetic, but the other guests are drifting in and Christmas, 1999, is near at hand. The party is beginning.

The life of the party is the radio. Our host dials number after number of the telephone-like wall panel. The vaudeville act fades out and for a moment everything is dark. A shot rings out and a torchlight (don't be scared, it isn't real!) breaks the darkness. A figure steals along a parapet which looks surprisingly real, although you know by now that it is only a gas glow.

No need to ask what it is. A radio thriller is being broadcast with a hundred per cent. thrill conveyed by the lifelike television.

The crook disappears and gives place on the gas screen to the curtain of a vast stage. Radio opera. A plump contralto paces to the edge of the stage just in front of your feet and sings an aria written two hundred years ago.

The contralto fades in favour of a German-looking announcer as a fresh number is dialled. Then come a costume play, some dancers, a comedian, more vaudeville. . . .

This amazing kaleidoscope is too vivid to be real, but it is more concentrated entertainment than you ever saw on the stage or cinema years ago in 1933.

Our Christmas party is gay, but four hours of this radio tour of Europe is too much.

Somebody gets up and dials "O." The vision vanishes. It's time for the kiddies to have their bonbons, and while this is going on we can buttonhole one of the Bright Young Things and get a few technical facts.

"You don't know about Raylite, International Broadcasting, microwaves, wired wireless. . . ."

That does strike a resonant chord. There was wired wireless even in 1933 and American experts in the Bell Telephone Laboratories had put out radio programmes on electric-light wires.

"Is that how broadcasting is done now?"

"Picture broadcasting, yes. When all the governments got together about ten years ago and formed an International Broadcasting Control, we thought it was high time that ordinary picture broadcasting for home programmes was taken off the ether. There were two million stations, programmes and commercial, all wanting wavelengths. As, by then, every house had electric light, the obvious thing was to impress the radio high-frequency waves on the electric-light wires."

"So real wireless is only used by Government stations, ships and . . ."

"Ships? My dear fellow, there aren't any ships these days big enough to have radio. The only boats of any size are the tenders which take out supplies to the floating aircraft platforms in the North Sea and in mid-Pacific and mid-Atlantic. All the air liners use wireless on about 250 kilocycles (that's about what you used to call 1,200 metres, in the old days when wireless was measured in wavelengths) and the International Government stations use microwaves only a few inches long. Their transmissions are secret, you see."

"What's happened to the B.B.C.?"

"Surely, my dear chap, you don't remember the old B.B.C. days? Why, it must be over twenty years ago that the American entertainment industry swamped this country and when there was such a war between broad-


casting and the cinema kings that we gave up the idea of allowing any one company to broadcast. All the programmes you saw at the party to-night came from the International stations, some in this country, and some from European divisions—what you used to call France and Germany, before we did away with nationalism."

The glow came on again at the end of the room and out of nowhere came the sound of bells, pealing in Christmas Day, 1999. Our party was almost at an end, so we take one more look at the miraculous radio artists moving about in the gas glow. Just one more question.

"All this comes by radio on the electric-light wires?"

"Yes."

"And you still call it wireless!"

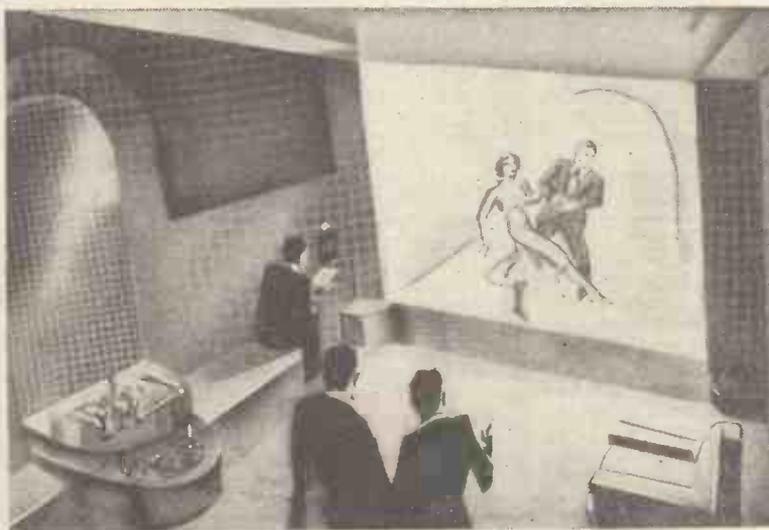

The brilliantly lit part of the room takes shape and parts become darker. Figures can be seen moving about in the brilliant glow . . . .

It is good for us set designers every now and again to spend a little time watching other people build sets! I say this in all seriousness because one has only to peruse some set-construction articles to realise that the writers thereof have very few points of contact with the average man.

A mere statement that this or that should be done is of little use if the task in question is beyond the ordinary man's ability, or the set is one requiring the use of tools which are not generally to hand.

Here are a few hints and tips about matters which I find from personal experience give difficulty in home construction. Very few, if any, of the hints are new, but I am giving them just because they appear to be little known. More commonly, it is assumed that the reader knows them, for which reason they have been left for a long period unexplained.

**BASEBOARD-ASSEMBLED COMPONENTS**

Baseboards nowadays are practically standardised in seven-ply wood 3/8-in. thick. This means that for the attachment of most baseboard-mounting components you can standardise on 3/8-in. wood screws and be sure that they will not go right through the back of the baseboard into the table on which you are assembling the set. (1)

There are, however, a few cases of components where very thick lugs are used. Transformers, for example, are nowadays generally made with bakelite cases and the lugs are usually about 1/2-in. thick. (2) A good supply of both 3/8- and 5/8-in. screws should therefore be kept on hand as one or other of these will be suitable for practically every component which you screw to the baseboard.


So far as the screws themselves are concerned these can be either brass, with round heads, or black japanned iron, with round heads. Avoid like the plague any thin brass screws, for plywood is quite hard and in a large number of cases while you are screwing down your component—"snick," the screw will break, leaving itself broken off flush with the baseboard in such a way as to be very difficult to remove. This will prevent your attaching the component exactly where you wanted it to be and may spoil your layout.

**JAPANNED STEEL SCREWS**

Personally I nearly always use black japanned steel screws which can be obtained from any ironmonger's and are quite cheap. They do not break off in normal use and they have the great advantage that if you magnetise your screwdriver it will pick them out of awkward corners of the set!

Sometimes you will find a component in which the holes in the fixing lugs are actually larger than the heads of the screws you are accustomed to use. Some manufacturers are still very silly and careless about these things and do not realise the trouble they give.

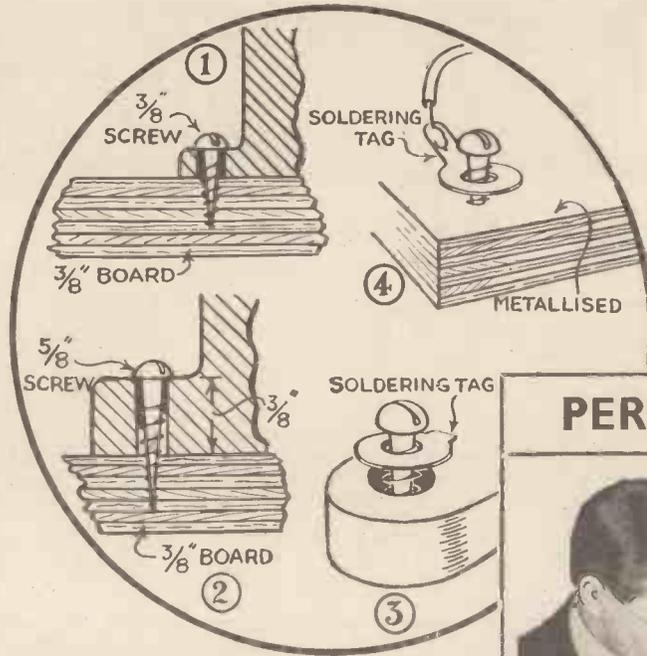Instead of trying to get a screw with a large enough head to hold it down (a difficult matter because large screws usually have long shanks which will go right through the baseboard)



look round in your scrap box and see if you can find an old soldering lug, nip off the tongue of this and you will have a washer with a hole in the centre which will take your ordinary round-headed screw, the washer itself being bigger than the hole in the component that you want to secure. (3)

In a large number of designs nowadays you will have either a metal-foil covered baseboard or else one which has been sprayed with metal and gives a similar conducting surface. This surface is joined to earth and you may want to make a number of connections to it. To copper foil you can make a soldered connection, and to some of the metallised baseboards, but you cannot do this to aluminium foil, which does not solder in the ordinary way.

In any case soldering to the metal foil is a messy business and you will find it a much better way to take a 3/8-in. screw, slip it through a soldering lug and screw it down to the baseboard, bending the soldering lug upwards at an angle. You can now solder this neatly and conveniently. The surface underneath the screw pressed against the metal baseboard will give you just as perfect a connection as you can desire. (4)

Never try to use a screw which is a tight fit, in a bakelite moulding. Ten to one the screw shank (which is slightly conical in many cases) will force its way into the hole and quite likely split off the lug and ruin the component. You have no idea how many home-built sets I have looked at which have had damaged components through such treatment.

Some home constructors, who do not mind within reason what they spend on components, seem frightened to lay out a few pence on one or two packets of screws. Half-a-crown's worth of wood screws of various sizes chosen at the local ironmonger's will serve for all the sets you are likely to want to make for several years.

**PANEL-MOUNTING COMPONENTS**


Most panel-mounting components require

the panel hole to be 3/4-in. diameter and as most people have such a drill, making these holes does not present much difficulty. There are, nevertheless, a few components which are secured by making a fairly large hole, inserting the threaded shank of the component, and screwing on a collar which fits into the hole of the panel. I hate these components myself, but a few still exist that require a hole to be made much bigger than 3/4 in.


The best plan, I find, is to make a 1/2-in. hole first of all, then widen it out with a reamer, which should be of sufficient diameter to clear a hole up to 3/4-in. diameter. You can get one of these from a tool shop very reasonably, and its use is preferable to buying larger drills,

**PERCY W. HARRIS Gives S**

**Dodging D**

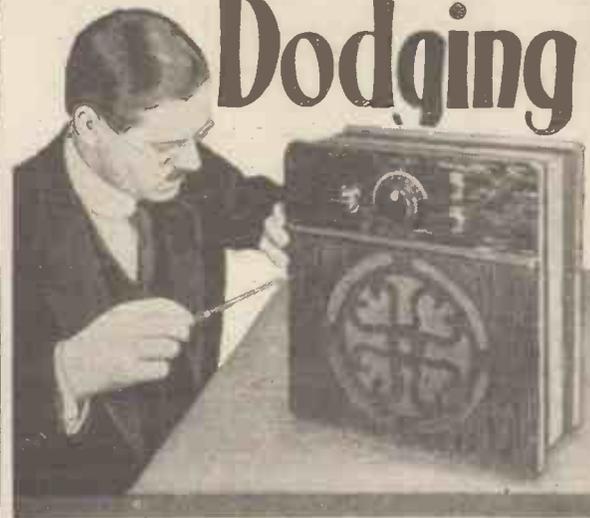


**Short Cuts to Succ**

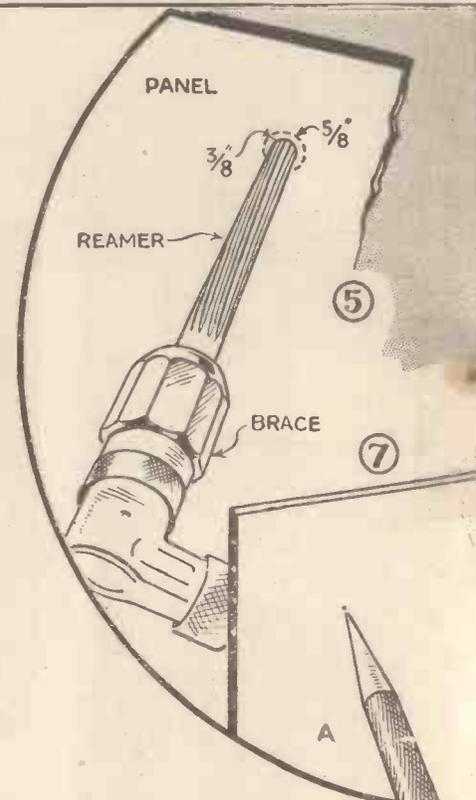

as you can make the holes to exactly the size you want by trial and error. (5)

One still finds some panel-mounting components (such as potentiometers, reaction condensers and the like) the spindle of which is "live" or joined to one of the terminals. This is bad design and a relic of the days when all panels were insulating. Take, for example, a differential reaction condenser. This component has three terminals, one joined to the moving plates and generally taken to the plate of the valve, a second which goes to the reaction winding and a third which goes to earth.

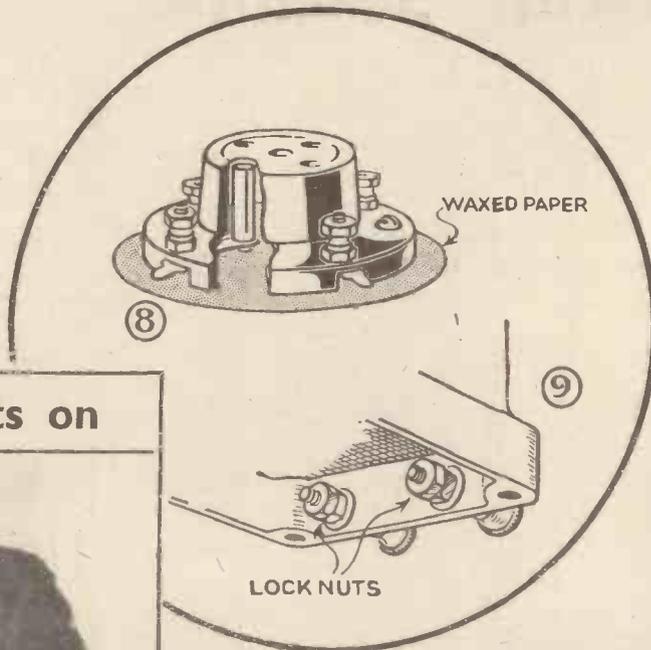If, as occasionally happens, the moving plates are in electrical contact with the fixing bush, and if a metal or metal faced panel is



small drill— $\frac{1}{8}$  in. at the largest—making sure the positions are correct and then using these drill holes as a guide for the larger drills. (7)

Furthermore, if you have a polished mahogany or walnut panel and you mark it out on the back it is greatly preferable to drill your holes through with small drills first and then to turn the panel over with its back on the table, afterwards drilling from the front. This will preserve the front surface from many scratches it would otherwise get and will prevent its breaking away in splinters as sometimes happens when you are drilling from the back.

By the way, whatever kind of panel you are drilling, metal, ebonite or wood, lay it face downwards on at least half a dozen sheets of newspaper before drilling and make sure the table underneath is quite flat and not likely to be damaged by your drills.

Set Builders Some Hints on

Difficulties in Set Construction



Successful Set Building

used, then anything joined to the moving plates will go straight to the metal panel, which is almost invariably earthed.

Sometimes you find potentiometers with the spindle attached to the moving contact and again if these are used on a conducting panel faults through short-circuits may arise.

If you must use one of these components and your panel is conducting you should bore your hole larger than otherwise would be the case and slip over the spindle an insulating collar


to keep it from coming in contact with the panel. These insulating rings and collars are supplied with some components and can be obtained from several manufacturers through your dealer. (6)

sure the table underneath is quite flat and not likely to be damaged by your drills.

SECURING PANEL TO BASEBOARD

Securing the panel perfectly to the baseboard seems to give many constructors difficulty, but there should be no trouble if on the back of the panel and along its bottom edge you draw a line equal to the thickness of the baseboard and drill three holes, one at each end and one at the exact centre, so that the holes will come half way down the edge of the baseboard when the panel is held upright against it. The holes drilled should be only just big enough to take the wood screws you are going to use, and then if you take a perfectly flat table and place the baseboard on it and hold the panel vertically in front there will be no difficulty in screwing the centre screw into position.

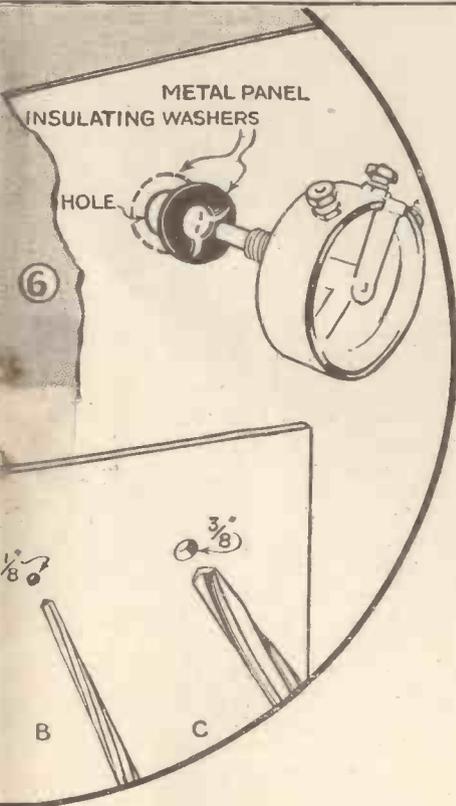This will clamp the panel upright against the front edge of the baseboard. The two end screws can then be inserted and screwed up tight. Unless there are very heavy components on the panel, brackets are seldom necessary nowadays.



SYMMETRY

Perhaps the commonest of all faults in home construction is a lack of symmetry either in the placing of panel components or the use of knobs. Most published designs have a symmetrical layout and most home constructors start off with the intention of adhering to this, but by the time the set is finished there is often just sufficient difference in level between two components, equally spaced on each side of the central knob, to spoil the balance.

I have looked into a number of cases of panels which have "gone wrong" for this reason and have almost invariably found that the trouble has been inaccurate drilling. The panel has been carefully marked out and a pencil cross or other mark made where the drill must go, but the home constructor has usually been in such a hurry that the drill has shifted sideways by  $\frac{1}{8}$  in. or so without his noticing it.

Now most panel holes are rather large— $\frac{3}{8}$  in. in diameter is a frequently used size—and it is by no means easy to place the point of a  $\frac{3}{8}$ -in. drill on a small mark and keep it there. The best thing to do, and the practice I invariably follow myself when drilling panels, is first of all to mark out the positions accurately, secondly to drill each hole with quite a

VALVE HOLDERS

A number of valve holders on the market are so made that if one presses a valve firmly into the socket the central springy portion bears downwards and either the pins of the valve or the metal springs of the anti-microphonic mountings come into contact with the baseboard. This does not matter if it is a wooden baseboard, but if it is either metallised or metal-covered the batteries will be short-circuited.

Two or three pieces of wax paper cut to the shape of the underside of the valve socket will prevent this and will be quite invisible when the valve holders are screwed down. (8)

LOOSE TERMINALS

One final tip. If when finally screwing down your connections you find a terminal on any component is loose and turns round and round, disconnect the other wires, remove the component from the baseboard and put this matter right at once. It is usually due to the screw on which the terminal runs not being locked tightly by a nut. (9)

# Broadcasting Stations

Wavelengths are brought up to date week by week. For the purpose of better comparison, the power indicated is that of the carrier wave.

Kilo-Metres cycles	Station and Call Sign	Country	Power (Kw.)	Kilo-Metres cycles	Station and Call Sign	Country	Power (Kw.)
16.86 17,790	Daventry (GSG) ...	Great Britain	20.0	307.6	975 Vitus-Paris	France	1.0
19.56 15,330	Schenectady (W2XAD)	United States	20.0	309.9	968 Tchernigov	U.S.S.R.	10.0
19.68 15,234	Paris (Coloniale) ...	France	15.0	309.9	968 West Regional	Great Britain	50.0
19.73 15,200	Zeesen (DJB) ...	Germany	8.0	312.5	960 Genoa	Italy	10.0
20.20 11,905	Paris (Coloniale) ...	France	15.0	312.8	959 Craow	Poland	2.0
25.28 11,865	Daventry (GSE) ...	Great Britain	20.0	315.8	950 Marseilles	France	1.6
25.4 11,810	Rome (ZRO) ...	Italy	15.0	318.8	941 Sofia (Rodno Radio)	Bulgaria	5
25.51 11,760	Zeesen (DJB) ...	Germany	8.0	318.8	941 Dresden	Germany	2.5
25.53 11,750	Daventry (GSD) ...	Great Britain	20.0	319.5	939 Niles	Italy	1.3
25.57 11,730	Huizen (PHI) ...	Holland	40.0	321.9	932 Göteborg	Sweden	10.0
25.63 11,705	Paris (Coloniale) ...	France	15.0	325	923 Breslau	Germany	60.0
30.0 10,000	Madrid (EAQ) ...	Spain	20.0	325.2	914 Poste Parisien	France	60.0
31.25 9,598	Lisbon (CTIAA) ...	Portugal	2.0	332.2	903 Milan (Siziano)	Italy	50.0
31.3 9,585	Daventry (GSC) ...	Great Britain	20.0	334.4	897 Poznan	Poland	2.0
31.38 9,560	Zeesen (DJA) ...	Germany	8.0	338.2	887 Brussels (No. 2)	Belgium	15.0
31.55 9,510	Daventry (GSB) ...	Great Britain	20.0	342.1	877 Brunn (Brno)	Czechoslovakia	32.0
31.6 9,490	Poznan (SR1) ...	Poland	1.0	345.2	869 Strasbourg (PTT)	France	11.5
37.33 8,036	Rabat (CNR) ...	Morocco	6.0	348.8	859.2 Leningrad	U.S.S.R.	100.0
38.47 7,799	Radio Nations (HBP)	Switzerland	20.0	349.6	850 Barcelona (EAJ1)	Spain	8.0
42.92 6,990	Oslo (LCL) ...	Norway	0.5	352.1	853 Graz	Austria	7.0
45.38 6,610	Moscow	U.S.S.R.	10.0	355.9	842 London Regional	Great Britain	50.0
46.69 6,425	Boundbrook (W3XL)	United States	1.0	360.6	832 Stuttgart (temp)	Germany	1.5
48.86 6,140	Pittsburgh (W8XK)	United States	40.0	363.6	825 Algers (PTT)	North Africa	13.0
48.94 6,130	Mexico (XETE)	Mexico	6.0	364.1	824 Bergen	Norway	1.0
49.02 6,120	Wayne (W2XE) ...	United States	1.0	365.6	818 Fredriksstad	Norway	0.7
49.18 6,110	Chicago (W9XE) ...	United States	5.0	368.1	815 Bolzano	Italy	1.0
49.18 6,110	Boundbrook N.J. (W3XL)	United States	18.0	368.1	815 Helsinki	Finland	13.2
49.4 6,073	Skanlebaek (OXV)	Denmark	5	370.1	810 Seville (EAJS)	Spain	1.5
49.5 6,060	Nairobi (VO7LO) ...	Kenya Colony	5	372.2	806 Hamburg	Germany	0.8
49.55 6,055	Vienna (UOR2) ...	Austria	5	376.4	797 Scottish Regional	Great Britain	50.0
49.59 6,050	Daventry (GSA) ...	Great Britain	20.0	380.7	788 Lwow	Poland	16.0
49.83 6,020	Zeesen (DJC) ...	Germany	10.0	385.1	779 Radio Toulouse	France	8.0
50.0 6,000	Moscow (RNE)	U.S.S.R.	20.0	385.1	779 Stalino	U.S.S.R.	10.0
50.26 5,969	Vatican (HVJ) ...	Italy	10.0	389.6	770 Leipzig	Germany	150.0
202.2 1,483	Tarragona (EAJ33)	Spain	2.5	394.2	761 Bucharest	Roumania	12.0
203 1,478	Bilbao	Spain	2.5	398.9	752 Midland Regional	Great Britain	25.0
204 1,470	Seraing	Belgium	3	403	743 Sottens	Switzerland	25.0
204.7 1,465.4	Liege (Exp.)	Belgium	3.5	408.7	734 Katowice	Poland	12.0
207.4 1,446	Verviers	Belgium	2.5	413	725 Athlone	Irish Free State	80.0
209.8 1,429	Miskolcz	Hungary	1.25	416.4	720.5 Rabat	Morocco	6.0
209.8 1,429	Magyarovar	Hungary	1.2	419.9	716 Berlin	Germany	1.5
209.8 1,429	Pecs	Hungary	1.2	424.3	707 Madrid (EAJ7)	Spain	3.0
211.3 1,420	Newcastle	Great Britain	1.0	424.3	707 Moscow (ROZ)	U.S.S.R.	100.0
214.3 1,400	Aberdeen	Great Britain	1.0	431	696 Belgrade	Yugoslavia	2.8
215 1,395	Liege (Reg)	Belgium	0.35	436	689 Stockholm	Sweden	55.0
215.6 1,391	Chatelneau (EL)	Belgium	2	441.2	680 Rome (Roma)	Italy	60.0
217.1 1,382	Konigsberg	Germany	5	447.1	671 Paris (PTT)	France	7.0
217.1 1,382	Dublin	Irish Free State	1.2	447.1	671 Danzig	Danzig	5
218.5 1,373	Salzburg	Austria	1.5	451.8	664.1 Madona	Latvia	15.0
218.5 1,373	Plymouth	Great Britain	2	451.8	664 Agen	France	2
220 1,365	Beziere	France	1.0	452.8	663 Milan (Vigentino)	Italy	4.0
220 1,365	Turin (2)	Italy	1.0	453.2	662 Odessa (RDH)	U.S.S.R.	15.0
222.1 1,351	Binche	Belgium	2	453.2	662 Klagenfurt	Austria	5
223.5 1,342	Antwerp	Belgium	4	456.6	657 San Sebastian	Spain	5.0
224.4 1,337	Cork (6CK) ...	Irish Free State	1.2	459.4	653 Beromunster	Switzerland	60.0
225.9 1,327.3	Fecamp	France	10.0	465.8	644 Lyons (PTT)	France	15.0
227.4 1,319	Bremen	Germany	1.5	472.4	635 Langenberg	Germany	60.0
227.4 1,319	Flensburg	Germany	5	480	625 North Regional	Great Britain	50.0
227.4 1,319	Hanover	Germany	1.5	488.6	614 Prague	Czechoslovakia	120.0
230.6 1,301	Malmö	Sweden	1.25	495.8	605 Trondheim	Norway	1.0
232.4 1,295	Kiel	Germany	2.5	501.7	598 Florence	Italy	20.0
232.8 1,289	Wallonia (Binche)	Belgium	3	501.7	598 Gorki	U.S.S.R.	10.0
235 1,283	Lodz	Poland	2.2	508.5	590 Astrakhan	U.S.S.R.	20.0
235.9 1,271.5	Bordeaux (S.O.)	France	3.0	509.3	589 Brussels (No. 1)	Belgium	15.0
237.8 1,261.3	Nimes	France	1.0	518.1	579 Vienna	Austria	100.0
238.9 1,256	Nurnberg	Germany	2.0	525.3	571 Riga	Latvia	15.0
240.6 1,247	Stavanger	Norway	5	532.9	563 Munich	Germany	1.5
242.3 1,238	Belfast	North Ireland	1.0	539.8	555.7 Palermo	Italy	10.0
242.7 1,236	Liege	Belgium	3	542	554 Sundsvall	Sweden	3.5
244.1 1,229	Basle	Switzerland	5	550.5	540 Budapest (1)	Hungary	10.0
245.9 1,220	Linz	Austria	5	555.5	540 Wilno	Poland	120.0
247.7 1,211	Trieste	Italy	10.0	559.7	536 Tamper	Finland	22.0
250.1 1,199.7	Juan-les-Pins	France	1.0	559.7	536 Kaiserslautern	Germany	1.5
251.5 1,193	Barcelona (EAJ15)	Spain	1.0	559.7	536 Augsburg	Germany	2.5
253 1,185	Gleiwitz	Germany	5.0	565.5	530.5 Freiberg i/B	Germany	0.25
255.1 1,176	Toulouse (PTT)	France	7.0	569.3	527 Grenoble (PTT)	France	3.0
257.3 1,166	Horby	Sweden	10.0	577.3	519.6 Ljubljana	Yugoslavia	7.5
259.3 1,157	Treves (Trier)	Germany	2.3	582.6	515 Tartu	Estonia	5
259.3 1,157	Frankfurt-A-M	Germany	17.0	690	434.7 Oulu	Finland	1.2
259.3 1,157	Cassel	Germany	0.5	746.2	402 Moscow (RMO)	U.S.S.R.	20.0
261.6 1,147	London National	Great Britain	50.0	747.2	401.5 Ostersond	Norway	0.6
261.6 1,147	West National	Great Britain	50.0	760	395 Geneva	Switzerland	1.25
263.8 1,137	Moravska-Ostrava	Czechoslovakia	11.0	833	360.5 Heston Airport	Great Britain	50.5
265.7 1,129	Lille (PTT)	France	1.3	844.8	355 Budapest (2)	Hungary	3.0
267.4 1,122	Nyiregyhaza	Hungary	6.3	1,000	300 Moscow (ROZ)	U.S.S.R.	100.0
267.6 1,121	Valencia	Spain	3.0	1,071.4	280 Tiflis	U.S.S.R.	35.0
269.8 1,112	Bari	Italy	20.0	1,083	277 Oslo	Norway	60.0
271.5 1,105	Rennes (PTT)	France	1.3	1,105	275 Minsk (RMG)	U.S.S.R.	35.0
274 1,095	Turin (Torino)	Italy	7.0	1,115	269 Moscow (Popoff)	U.S.S.R.	40.0
276.5 1,085	Heilsberg	Germany	75.0	1,137	263.8 Monte Ceneri	Switzerland	15.0
279.5 1,073	Bratislava	Czechoslovakia	14.0	1,153.8	260 Kalundborg	Denmark	30.0
281.2 1,067	Copenhagen	Denmark	75	1,190.5	252 Luxembourg	Gd. Duchy of Lux	200.0
282.2 1,063	Lisbon (Tests)	Portugal	20.0	1,200	250 Istanbul	Turkey	5.0
283.6 1,058	Innsbruck	Austria	5	1,200	230 Reykjavik	Iceland	21.0
283.6 1,058	Berlin (E)	Germany	5	1,255	239 Vienne (Exp.)	Austria	3.0
283.6 1,058	Magdeburg	Germany	5	1,276.3	235 Tunis	Tunisia	7.5
283.6 1,058	Stettin	Germany	5	1,304	230.1 Leningrad	U.S.S.R.	100.0
285.1 1,052	Radio Lyons	France	1.0	1,348	222.5 Motala	Sweden	30.0
286 1,049	Montpellier	France	9	1,411.8	212.5 Warsaw	Poland	120.0
288.5 1,040	Bournemouth	Great Britain	10.0	1,445.8	207.5 Eiffel Tower	France	13.0
288.5 1,040	Scottish National	Great Britain	50.0	1,481	202.6 Moscow (RTC)	U.S.S.R.	500.0
291 1,031	Vilpuri	Finland	13.2	1,554.4	193 Daventry National	Great Britain	30.0
293 1,022	Kosice	Czechoslovakia	2.5	1,634.9	183.5 Zeesen	Germany	60.0
293.7 1,021	Limoges (PTT)	France	7.0	1,721.1	174 Radio Paris	France	75.0
296.1 1,013	Hilversum	Holland	20.0	1,796	167 Lahti	Finland	54.0
298.8 1,004	Tallinn	Estonia	11.0	1,875	160 Kootwijk	Holland	50.0
298.8 1,004	Salonika	Greece	1.5	1,875	160 Moscow (RCZ)	U.S.S.R.	100.0
301.5 995	North National	Great Britain	50.0	1,875	160 Brasov (tests)	Roumania	20.0
304 986	Bordeaux (PTT)	France	13.0	1,935	155 Kaunas	Lithuania	7.0

## Re-grouping Europe's Transmitters

By JAY COOTE

FOR purposes of economy, on the Continent a considerable amount of reorganisation is taking place with a view to the re-grouping of transmitters. The method used is somewhat different to the National and Regional principle adopted by the B.B.C., but its eventual aim is the provision of alternative programmes for a greater number of listeners. Some little time ago, Italy achieved this object by forming a Northern and Southern group, with mutual interchange of programmes, and to facilitate at Milan and Turin the reception of the Rome and Naples entertainments, installed, or rather "revived," small transmitters in each city.

### Three German Networks

Germany now, with a similar end in view, has formed three networks, namely, *Nord, West and Süd-West Gruppe*, which include respectively:—  
 (1) Berlin, Magdeburg, Stettin, Hamburg, Hanover, Flensburg, Kiel, Bremen, Königsberg, Heilsberg, and Danzig.  
 (2) Frankfurt, Trier, Cassel, Cologne (Langenberg), Stuttgart, and Freiburg.  
 (3) Munich, Nurnberg, Kaiserslautern, Augsburg, Leipzig, Dresden, Breslau, and Gleiwitz.

In future, therefore, from that country, apart from the special entertainments broadcast from the *Deutschlandsender* (Königswusterhausen), we shall only get three different programmes, as the transmissions in each group will go out on the S.B. system.

On the other hand, the authorities have realised that with the recent electioneering addresses, their nationals have had a surfeit of political speeches and have now deserved some compensation.

It will be found in a greater percentage of musical programmes (with official pronouncements and tubthumping cut down to a minimum) and especially in somewhat prolonged broadcasting hours. Later entertainments are also now given by Längenberg, Frankfurt and Mühlacker.

Austria is the third country to attempt a reorganisation of a similar character. Possibly this will not take place before January 15, and may coincide with the wavelength alterations.

### Two New Relay Stations

Two more relays are to be erected, at Leoben and Villach, to increase the areas of respectively Klagenfurt and Linz. Leoben lies about eighty miles to the south-west of Vienna; Villach is situated in Carinthia near the Italian frontier. Linz, Klagenfurt and the new Vorarlberg (Brégenz) station will work as one group; Graz, Salzburg and Villach as another.

Some alterations will be made when, on January 15, the Lucerne Plan comes into operation. Vienna will operate on 506.8 metres, Graz on 338.6 metres, Salzburg on 222.6 metres, and Innsbruck will take over a new channel borrowed from the shipping band, namely, 578 metres. Linz, Klagenfurt, and Bregenz will work on 231.8 metres.

From Vienna, in any case in January, there is a treat in store for us; it is the production of a new comic opera, *Giudella*, by Lehar, in which Richard Tauber will play the principal part. The performance will be relayed to the Austrian broadcasters and, it is hoped, will also be taken by the principal Continental stations.



## WHEN THE AUDIENCE APPLAUDS

**THERE IS A SUDDEN DRAIN OF  
30 MILLIAMPS OR MORE ON  
YOUR HIGH TENSION BATTERY**

In modern Transient Load receivers, current consumption depends upon the "noise-value" of the programme; and when suddenly a thousand pairs of hands crash out the approbation of the audience, a heavy drain is thrown on your high-tension battery. This studio applause may take 30 milliamps or more of current, and an ordinary H.T. battery simply cannot stand up to such a drain—the voltage drops off alarmingly and immediately you lose all the advantages of your modern Class "B" and Q.P.P. output.

The  
Voltage  
of a

Now the cells of a Lissen Battery stand up to ANY sudden drain; they give the required current without volt drop. The big oxygen content of the Lissen cells reduces internal resistance so that the battery can respond instantly to any demand. And all the time the current flow is smooth and silent, giving distortionless reproduction at a volume which really justifies the claim "Mains power from battery sets."

**LISSEN BATTERY**  
stands up to ANY sudden drain!

# AMATEUR TELEVISION

SPECIAL SECTION FOR EXPERIMENTERS — CONDUCTED BY H. CORBISHLEY.

## Your Wireless Set and the Cathode-ray Tube

Here is a number of interesting experiments which can be made with your wireless set and the cathode-ray tube. Most useful information can be obtained and the tube will reveal all the good and bad qualities of your receiver

THE owner of a cathode-ray tube will, no doubt, welcome a change from television experimenting during the Christmas holidays, and the suggestions given in this article will form the basis of an interesting demonstration of the other uses to which the tube may be put. One or two simple circuits will be required for some of

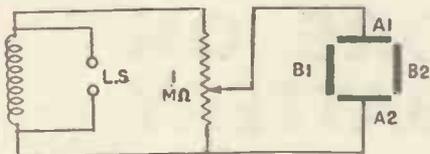


Fig. 1.—Connection of plates across loud-speaker for observation of acoustic wave-form. B1 and B2 plates are connected to the time base

the effects shown, but without going to any trouble the tube can be made to show some striking phenomena when applied to an ordinary radio receiver.

The deflector plates will draw no current from the circuit to which they are connected, and hence will not upset the

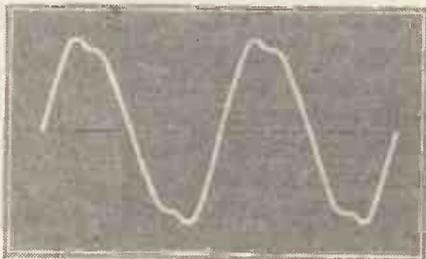


Fig. 2.—Typical wave-form of sustained pure note

operating conditions of the receiver when they are connected between any two points in it. On the other hand, the potential applied to the plates may be too high for a reasonable deflection and a high-resistance potentiometer is sometimes desirable to control the voltage applied to the deflectors.

With an anode voltage of 600 on the tube a good deflection would be given by 50 volts on the plates, and this figure should be borne in mind when the tube is connected

to the receiver. It is always comforting to think that the tube will not be damaged by excessive voltage applied to the deflector plates, the only effect being that of forcing the beam off the screen.

The simplest effect to study is the audio frequency wave-form applied to the loud-speaker, and for this a single linear time base will be required, constructed according to the article in the issue of October 28, page 774. The vertical deflector plates are connected directly across the loud-speaker transformer secondary terminals, and the voltage will usually be found sufficient to give a good deflection. If it is too high, a 1-megohm potentiometer may be connected across the plates as shown in the circuit of Fig. 1.

Since the frequency of the notes from the speaker is continually varying, it will seldom happen that the wave remains stationary on the screen, but the speed of the time base can be adjusted to give a stable well-defined wave for the greater part of the time. When a single note is sounded in the middle of an orchestral piece the wave-form of the instrument will stand out like the example in Fig. 2.

### Checking a Radiogram

If a radio-gram is available, a constant frequency record can be used to give a steady wave-form, and this can be used to check the constancy of the gramophone-motor. A wavering motor, or an irregularity in the turntable rotation will cause the wave-form to oscillate slowly backwards and forwards across the screen. Incidentally a constant-frequency record is invaluable for checking distortion in audio-frequency stages in a receiver. The deflector plates can be arranged by means of

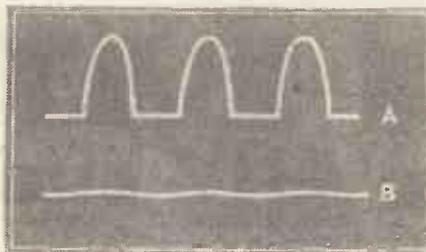


Fig. 4.—Effect of smoothing condenser in rectifier circuit

a change-over switch to record the wave in the first L.F. circuit and compare it with the wave at the speaker terminals.

If a constant-frequency record is not

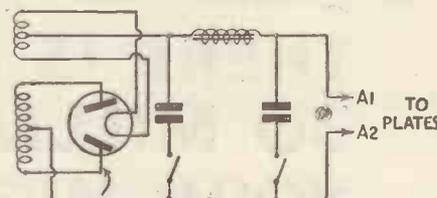


Fig. 3.—Rectifier circuit arranged to show half-wave rectification and effect of smoothing

available, a good effect can be obtained by disconnecting the set from the aerial and increasing the reaction until it howls. With careful adjustment a low growl can be obtained which will record easily with the time base running at a moderate speed.


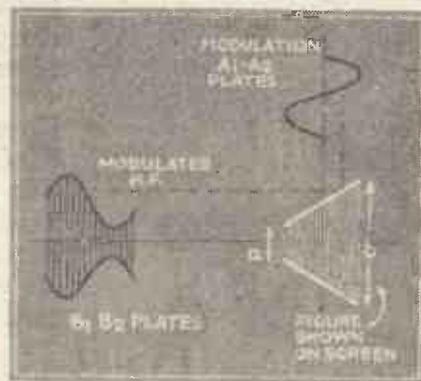


Fig. 5.—Showing figure produced by modulated H.F. on the plates

With sets employing battery bias, it is an easy matter to show the effects of over bias on the amplifying valve, and to see how, in extreme cases, the valve will rectify the audio-frequency signal. It is advisable to disconnect the speaker during these experiments to avoid distracting the attention of the audience by the dreadful sounds emitted.

Continued on page 1110

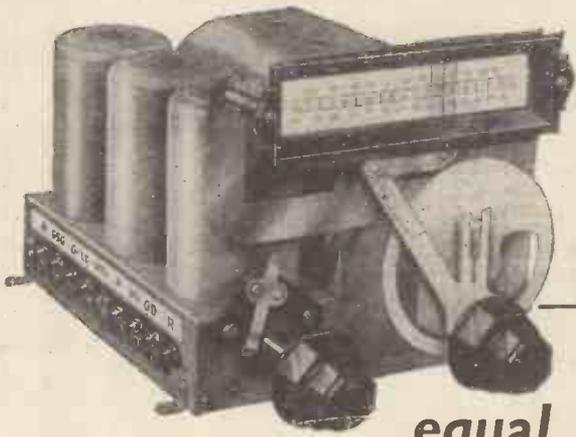

# Free Blueprint!

## THE REMARKABLE LINACORE

### 3-valve circuit equal to a Superhet


By sending this coupon NOW you will receive free a blueprint of an ideal battery model "LINACORE" circuit which from 3 valves will give you results equal to a "Superhet." Enclose 2d. only for postage.



For battery receivers type BPB  
(as illustrated)
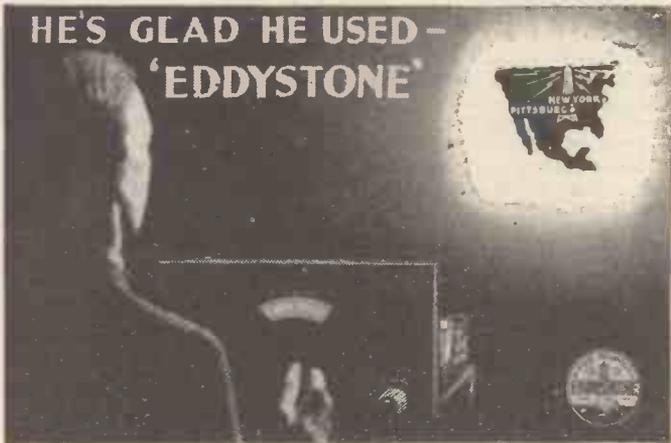
# 69/6

To: Jackson Bros. (London) Ltd., 72 St. Thomas' St., London, S.E.1  
Please send Free blueprint. I enclose 2d. in stamps for postage.  
NAME \_\_\_\_\_ ADDRESS \_\_\_\_\_  
A.W.



### HE'S GLAD HE USED - 'EDDYSTONE'

#### CORRECT DESIGN -ALWAYS TELLS

"EDDYSTONE" short-wave components are designed by short-wave engineers. Here is one of the "EDDYSTONE" S.W. valveholder designs, fundamentally and basically sound for its purpose. That is why it has minimum self-capacity, one piece no noise metal sockets, special Frequentite insulating ring (see note at side) and loss reducing pillar mounting.

SOLE MANUFACTURERS:-  
STRATTON & CO., LTD., BROMSGROVE STREET, BIRMINGHAM.  
LONDON SERVICE DEPOT:-  
WEBBS RADIO STORES, 14 SOHO STREET, OXFORD STREET, W.1.


## EDDYSTONE

SHORT-WAVE COMPONENTS
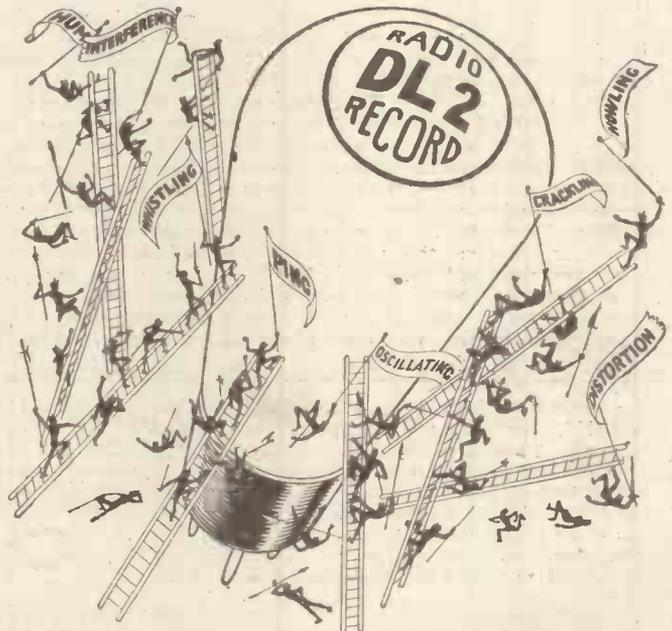
#### "EDDYSTONE" FREQUENTITE SHORT WAVE VALVEHOLDER

Frequentite is a new material which is far superior to all present insulators for ultra-short-wave work. Its characteristics are only excelled by fused quartz. Technical details on request.

No. 949, 4-pin ... 1/5  
No. 950, 5-pin ... 1/8



### Keep away PARASITIC NOISES

Are you troubled with whistling, crackling, howling, etc.? The Radio Record D.L.2 (battery operated) really non-microphonic Detector Valve will act like a tonic to your set and eliminate these interferences. Obtain one to-day from your nearest dealer; you will be amazed at the difference of your reception! Complete range of Radio Record 2 volt and A.C. Valves of guaranteed quality.

Prices from  
**3/9**

RECORD RADIO LTD.  
Eldon Street House, Eldon Street, E.C.

Amateur Television—Cont. from page 1108

Speaking of rectifying, it is surprising how little the functions of the reservoir and smoothing condensers in a mains unit are appreciated, and the cathode-ray tube shows their use in a very striking way.

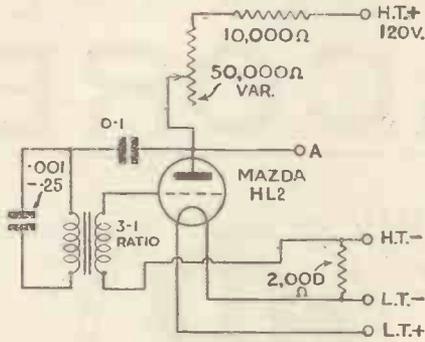


Fig. 6.—Circuit of simple audio-frequency oscillator for experiments with wave-forms

To obtain the best effect the rectifier should be modified to half wave by disconnecting one anode terminal of the normal full-wave rectifier. The set should be disconnected so that the rectifier is on no-load, and the deflector plates should be connected directly across the H.T. terminals through a potentiometer (Fig. 3). Disconnect both condensers at the points marked X, X and switch on. The wave-form of a half-wave rectified voltage will appear on the screen, but considerably displaced from the centre. This is because the D.C. component of the voltage is permanently pushing the beam off centre. The movement can be controlled, however, by connecting a bias battery in series with the opposite plate and adjusting its value until the wave appears as Fig. 4 (a).

Now reconnect the reservoir condenser and the result will be as Fig. 4 (b). The voltage will be practically free from ripple. In that case what is the use of the smoothing choke and second condenser? The answer is given at once on putting a load on the rectifier. As soon as the set is reconnected the reservoir-condenser loses its charge and the humped wave reappears. The addition of the choke and the second condenser will once more restore the voltage to the approximate straight line of Fig 4 (b).

An interesting effect, but one slightly more difficult to obtain, is that of the figure produced by the application of

modulated radio-frequency to the deflector plates. If the radio input is applied to the plates with the beam deflected by the time base, the ordinary modulated carrier wave can be seen if the voltage is sufficiently high to produce a good deflection. A better plan is to dispense with the time base and connect one pair of plates across the audio frequency and the other across the modulated radio frequency. The resulting figure on the screen will be a sort of irregular triangle with a blunt apex if the modulation does not reach 100 per cent. The reason for the figure is seen from the details of Fig. 5, which show the effect of each wave on the beam and the resulting deflection.

As said above, this picture is difficult to obtain on an ordinary receiver, but with a modulated oscillator it can easily be produced and the depth of modulation measured by comparing the heights marked a and b in the figure. (If the modulation is linear the coefficient of modulation is  $\frac{b-a}{a}$  measured from the figure.)

An audio-frequency oscillator for experi-

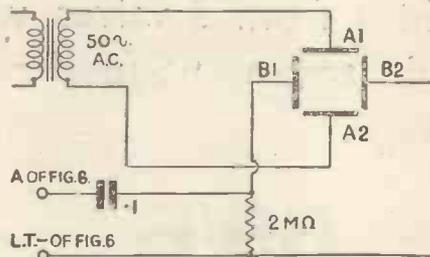


Fig. 7.—Connections for making patterns with the oscillator of Fig. 6

ments in wave form can be simply constructed from the stock components found in most experimental workshops. The theoretical circuit is shown in Fig. 6 and with the values shown the frequency can be varied from 100 to 5,000 cycles per second, but this depends on the type of transformer used to couple the anode and grid circuits. With an old Ferranti 3-to-1 transformer inverted the figures quoted were obtained with three different values of tuning condenser ranging from .001 to .25 microfarad. However, the circuit is bound to oscillate if the transformer is connected round the right way and the values of the components can be left to

the taste and sense of the constructor.

Using a 50-cycle mains supply for one pair of deflector plates and with the oscillator connected across the other pair,

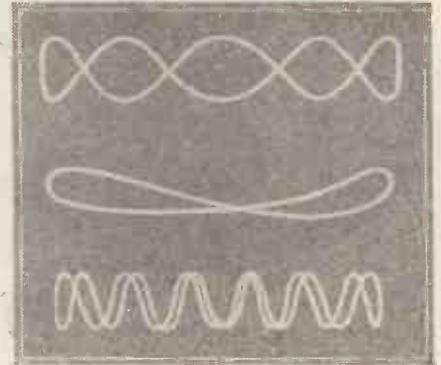


Fig. 8.—Patterns made by the oscillator of Fig. 6 used with a 50-cycle A.C. supply on the other pair of plates

a variety of beautiful patterns can be obtained which will delight the "lay" members of any audience.

The circuit of Fig. 7 shows the connections for producing the patterns, and Fig. 8 gives an indication of some of the simplest forms produced.

### Small Motors and Scanning Disc Speed

QUITE small motors, such as are used for model purposes, are often used with success for driving scanning discs, but sometimes it happens that the power of the motor is just a little less than is required to keep the disc running at the full speed of 750 revolutions per minute. In such cases there is an effective dodge that can be resorted to slightly to reduce the amount of power which is necessary. This consists of reducing the size of the disc by cutting round the periphery with a pair of scissors. An appreciable amount can be trimmed off without in any way impairing the disc and usually it will be found that the slight reduction of weight and lessened air friction will be just sufficient to enable the motor to do its work. Of course if the power of the motor is very much below the standard this procedure may not be effective, but generally it will make up for a lack of from 25 to 50 revolutions per minute.

IS the wireless earth as important as it used to be? Many listeners are asking that question. They have found by experience that the modern set seems to work just as well without an earth as with one.

They tell us they can get as many foreign stations using just the aerial and no earth, as they can get when an earth is carefully installed and connected up; that the strength of the foreigners is just as good without an earth as with one; that mains hum is no less and no more apparent with an earth than without.

#### The Great Earth Fallacy

So, say these listeners, what about this great earth fallacy? Why continue to say the earth is important?

These are knotty questions. Yet there is a catch in them. Do you spot it? Possibly not. The catch is that in mentioning these earths of doubtful virtue our correspondents do not give any details of the type of connection used.

All too frequently we find that, when a reader complains he can detect no difference with or without an earth lead on his set, only

## Your Earth Connection

a very poor earth has been installed—a gas-pipe connection, a water tank that does not lead to anywhere in the earth, or a feebly buried spike or tube.

You may take it that if an earth makes no difference at all to your set, it is a bad earth. That is axiomatic—except, of course, with frame aerial sets, such as portables.

If you take pains with your earth you will find that its connection will improve your reception, no matter how powerful it may be. The theory of the earth is not easy to understand, but you can take it that when you make a good low-resistance contact with earth, you are virtually making an electrical image of your aerial.

The earth, never forget, is just a part of the aerial-earth system, up and down which wireless signals oscillate. If there is no earth connection you are making things difficult for those wireless waves, which have to make do with whatever substitute they can find as an earth. The chassis of the set may make a sort of capacity earth; in fact, often when you imagine that your set is working entirely without an earth the metal part of the set is actually acting as one.

#### Manifold Good Effects

The good effects of a well-installed earth are manifold. You get cleaner signals, more stable working, less background noise from the mains and, in short-wave sets, infinitely easier tuning and reaction control.

So just remember this about the wireless earth: if its connection to the set makes no difference to your reception, it is probably a bad earth. Your remedy is obvious—put in a solid plate or one of the new "Chemical" earths and solder the stranded earth wire to it, or make a really low-loss connection with stout wire to a main water pipe. J. B.

# 'Ferrocart' — a triumph of precision



Made under license from the patents, Hans Vogt

- Ferrocart coils are the outcome of years of ceaseless experiment and research.
- They are the most accurate coils ever made, accurate to a degree never before attained.
- Built to the highest standard of engineering precision, every coil is thoroughly tested and guaranteed.
- Insist on Ferrocart coils—the coils made by Colvern.
- Full details of Ferrocart coils are given in our Radio list No. 12. Send now for a copy—it's absolutely free of charge.

**COLVERN LIMITED, ROMFORD, ESSEX**  
London Wholesale Department: 150 KING'S CROSS ROAD, W.C.1

# COLVERN

British Made



## YOU WANT PERFECTION ? FOR SHORT WAVES ■

Then use the original **BECOL EBONITE LOW-LOSS FORMER**, tested before despatch and reliable. Prices Low. Look for Trade Mark. Efficiency Tells.

**INTERESTING.**—Send 6d. (post free) for 3rd Edition of **UP-TO-DATE HANDBOOK** of Tuning Coils for Circuits, Dual Range, Band Pass and Super-het, fully illustrated with data.

**THE BRITISH EBONITE CO. LTD.** HANWELL, LONDON, W.7

## MAKE YOUR OWN WIRELESS ENCYCLOPEDIA FOR 3/3!

Readers can be supplied at a very low price with a perfect reading case and self-binder in one. The insertion of the issue into the self-binder is a matter of simplicity; the issues in their self-binder open perfectly flat at every page; no fastening devices are visible from the outside; the issues can be put in the self-binder either before or after they are read, and once they are in they become part of a book.

Each case will hold twenty-six issues.

"Amateur Wireless" volumes run from the first issue in January to the last issue in June, and from the first in July to the last in December. When applying, indicate whether for the last twenty-six copies issued or otherwise.

This self-binding case sent, packed and post free, for 3/3. A limited number only available; send for yours to-day.


**AMATEUR WIRELESS, 58/61, FETTER LANE, E.C.4**
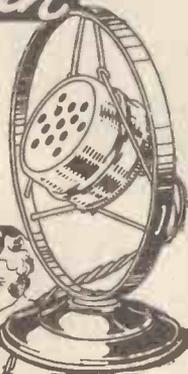
## Endless Xmas Fun



Be Your Own B.B.C. with the super scientific **HOME MIKE**

Your friends and family can become radio artists. Songs—Music—Charades, etc; never a dull moment for young and old



Complete in itself. Just connect to set. No alterations and no extras to buy.

Free Pamphlet "A" with instructions and many suggestions to add to your gaiety; sent with every Home Mike

**HOME MIKE**, de Luxe Model, Giving extreme sensitivity and maximum volume **17/6**

Post Free Junior Model, 12/6. Post Free, or either model sent C.O.D. on receipt of a post card. Don't delay if wanted for Christmas

See interesting article on p. 961, also our adol. on p.1030, Dec 2 A.W. **SCIENTIFIC SUPPLY STORES (Wireless) LTD.** Dept. "A.W.," 126 Newington Causeway, Southwark, London, S.E. (Hop 4177)

## A Modernistic Cabinet



This cabinet is undoubtedly the finest value obtainable, made as it is by cabinet constructors with years of experience. In selected walnut veneer and supported on black polished feet. Makes a most acceptable Xmas Gift.

**36/-** complete with baseboard 22" x 10"

Order now or write for Free Catalogue.

**DAVENTRY**



Carrington Mfg. Co. Ltd., 24 Hatton Garden, London, E.C.1. Works: S. Croydon Holborn 8202

Post in 1/2 d. envelope

Name.....  
Address.....  
..... 36 A.W.

To Ensure Speedy Delivery, Mention "A.W." to Advertisers

Sets of the Season Tested

# Lissen A.C. Three-valver


It is unusual for kit receivers to include so many refinements that are usually associated only with higher-priced sets. The Lissen All-electric Three is a three-valve receiver (not counting the full-wave rectifying valve). It consists of a variable-mu screen-grid high-frequency stage, a steep-slope detector and a pentode output valve having an amplification factor of 70. It is, of course, built on a steel chassis, with all of the major components completely screened.

The receiver is full of useful refinements,

provision has been made for an external loud-speaker.


The receiver can be operated without any external aerial at all. The wander plug attached to the lead coming through the chassis immediately above the three aerial sockets, marked A1, A2 and A3, should be inserted into the socket from which the best results are obtained. Lissen's recommend that up to distances not exceeding ten miles from a broadcasting station, A3 should be used, or A2 up to 40 miles, leaving A1 to give fairly flat tuning when a long way from the station.

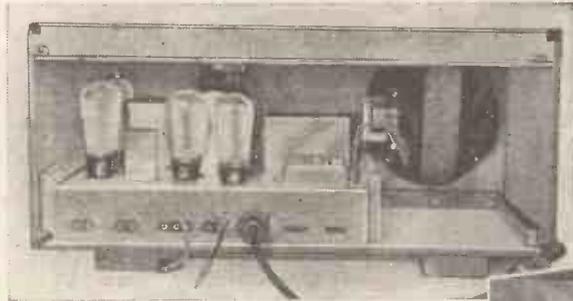The receiver is very simple to operate as the tuning scale is calibrated in wavelengths, varying between 200 and 550 metres and 825 to 2,000 metres. For those who are not used to this method of marking, the approximate positions for the regional stations are clearly marked.



Two views of the Lissen A.C. three-valver reported on this week

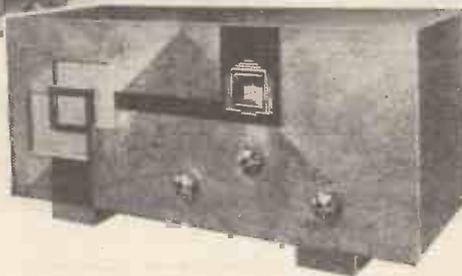such as three aerial tappings to give adequate selectivity under all conditions. Two alternative sockets are provided for a tone control, giving high- or low-note emphasis. There are six alternative sockets for A.C. voltage, making the receiver suitable for any voltage between 100 and 125, 200 or 250 volts. Of course,



### Brief Specification

Makers : Lissen, Ltd.

Model : A.C. Three, type LN8039.

Price : £10 10s.

Valve Combination : High-frequency amplifier, AC/SGV; three-electrode detector, AC/HL; pentode output, PT425; and full-wave valve rectifier, U650.

Type : Table model, suitable for A.C. mains, any voltage between 100 and 125, or 200 and 250 volts.

Remarks : An ideal set for the home constructor which, when completed, has a very professional look.

When this receiver was tested on a 25-ft. aerial, twenty miles from London, the daylight range was really remarkable. Huizen, Radio Paris, Zeesen and Daventry could all be tuned-in at full loud-speaker strength without mutual interference, while later in the day Warsaw, Motala, Kalundborg and several Russian stations were picked up.

On the medium waves thirty or forty stations could be tuned-in without touching the volume control and we feel sure that if the set were tuned carefully most of the powerful Continental stations could be received at will.

The reproduction is extremely good. Of course, the moving-coil loud-speaker (which was carefully matched to the pentode) had a lot to do with this. When the receiver is used with a gramophone pick-up, the volume is sufficient to fill a very large room. Perhaps that is why Lissens recommend that you use one of their needle-armature pick-ups.

This is one of the few sets that is entirely free from hum; even with one's ear in front of

## VIVID REALITY from YOUR set

Your set this Christmas can give reproduction more vivid and lifelike than you ever thought possible. The unique features of these W.B. Speakers (fully protected by patents) place them in a different class from all other moving-coil reproducers ● The 'Microloode,' giving perfect matching to the set, brings an evenness of response obtainable in no other way ● The 'Mansfield' magnetic system brings sensitivity, crisp attack and clear, brilliant top notes ● Hear one at your dealers and realise how good YOUR radio might be if you gave your set a fair chance! The improvement will AMAZE you!



PM 4A



### MICROLOODE Models

PM 6	-	-	-	-	-	32/6
PM 4A	-	-	-	-	-	42/-
PM 2A	-	-	-	-	-	79/6
PM 1A	-	-	-	-	-	120/-

Handsome cabinets are also available. Write for the W.B. folder.

## 'MICROLOODE' MOVING-COIL SPEAKERS

Whiteley Electrical Radio Co., Ltd., Dept. A, Radio Works, Mansfield, Notts.

Sole Agents in Scotland : Radiovision Ltd., 233 St. Vincent Street, Glasgow, C.2.

Sole Agents in I.F.S. : Kelly and Shiel, Ltd., 47 Fleet Street, Dublin

the loud-speaker there is hardly any trace of ripple. It is supplied with a heavily insulated mains cable with a twin plug, making it suitable for a light or power socket.

Two .5-ampere fuses are fitted to this plug—so that should you have a mishap and blow your fuses they are very easily replaced. Compactness is a very desirable feature and the size of the walnut cabinet that houses this receiver is only 22 in. long by 10½ in. high by 9 in. deep.

A combination of good design and highly efficient valves makes this receiver one to be remembered.

**Special Foreign Programmes**

To the Editor, "Amateur Wireless."

SIR,—I have some information that will interest your readers. The Westinghouse stations KDKA and W8XX (48.86 metres) at Pittsburg are now putting over every week (at present at 5.15-6 a.m. G.M.T.), on Mondays, a programme of notes, tips, etc., arranged by the International Dx'ers Alliance and dedicated to us and our brother clubs.

I am also able to say that a special transmission will be put over from the Radio Strasbourg PTT station at 7-8.30 a.m. on December 30, on their wavelength of 345 metres (11.5 kilowatts power). I am enclosing a copy of the programme.

A programme will be put over from WRUF (830 kilocycles, 5 kilowatts), Gainesville Florida on December 14, at 7 a.m. G.M.T.

RICHARD S. RAWLES.  
(I.D.A. Publicity Director.)

Newport, I. of W.

**Programme Dedicated to I.D.A.**

December 30, 1933.

7-8.30 a.m. G.M.T. Orchestra Radio Strasbourg

Direction: Maurice de Villars

- 1. March, "Stars and Stripes" ... Sousa
  - 2. "Salut d'Amour" ... Elgar
  - 3. "Air d'Caron" (Solo, M. Gillig) ... Lully
  - 4. Air from *The Marriage of Figaro* (Solo, Mme. Ines Maujean) ... Mozart
  - 5. Overture *William Tell* ... Rossini
  - 6. Duet, "La petite mariee" (Mme. Maujean, M. Gillig) ... Lecocq
  - 7. Prelude d'En'acte, *Cavalleria Rusticana* ... Mascagni
  - 8. Duet, "La fille de Mme. Angot" (Mmes. Maujean, Jeanne Wild) ... Lecocq
  - 9. Prelude, *The Deluge* ... Saint Saëns
  - 10. Air, "Rose Marie" (Solo, Jeanne Wild) ... Fritzl
  - 11. "Scenes Alsaciennes" ... Massenet
  - 12. Air d'Vilga, "La Veuve Togens" (Solo, Jeanne Wild) ... Lehar
  - 13. March, "La pere da Victoire" ... Ganne
- From Radio Strasbourg (PTT), 345 metres (11.5 kilowatts), on December 30, 1933, 7-8.30 a.m.

**Self-adjusting Volume Control**

IN the issue of AMATEUR WIRELESS dated November 18, "The Experimenters" described some experiments with a Mazda L2DD in a short-wave set. The circuit published with the article showed a .0003-microfarad condenser connected across the diode instead of from anode to filament. As this condenser connected across the diode reduces the voltage across the A.V.C. diode to one-quarter, as well as introducing a large fixed capacity across the primary of the intermediate-frequency transformer, it will materially reduce the performance of the receiver. This alteration is brought to our notice by the Mazda valve works, whose original circuit "The Experimenters" followed.


**R. & A. Alpha Loud-speaker**

WITH reference to the test report on the R. & A. Alpha loud-speaker that appeared on page 1026 of our December 2 issue we are asked by the makers to point out that the purpose of the sub-assembly carrying the diaphragm and speech coil is that distortion of the outer chassis, which carries the magnet and transformer only, in no wise affects the location of the speech coil in the gap, as is the case where the periphery of the cone is fixed to the same member as in ordinary types.

Good reproduction is obtained even when only a medium size of baffle is available.

How's this for **CHRISTMAS?** **Double capacity accumulator**

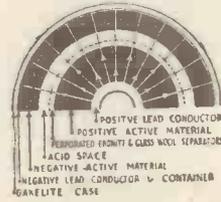
Besides huge amp. hour capacity, a plate-less accumulator (1) holds full charge when inactive (2) will not sulphate (3) is far more durable (4) is clean and good-looking. This new principle in electrical storage entirely replaces the old type.



Alongside is a half section of the new cell, in plan. In the old type, current largely concentrated round the good-conducting but inert grids, causing uneven charging. Now plates are gone—and circular formation forces the current to pass through every particle of paste in its passage from central positive to outer negative. Absence of grids also reduces waste weight and space. What a sensible Christmas present!



*and hand lamp too!*

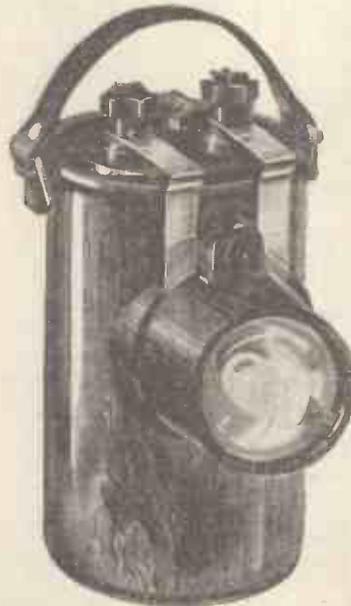

A further idea for Christmas is the beautiful lamp attachment for the Block plate-less L.T. cell. Fitted in a moment, it gives a really powerful beam, and will serve you for months on one charge. Made of coloured bakelite to match the accumulator; chromium plated metal parts.

PRICES L.T. cell, 80. a.h., 2 v. 11/6. Lamp fitting with switch and bulb, 10/6— or complete with L.T. cell, 21/-

**"Half the bulk" H.T. accumulators**

The double capacity of Block cells provides H.T. accumulators which, though of standard capacity, are only half the bulk! This portability disposes for ever of the only point in favour of constantly expensive dry batteries (the falling voltage of which, in any case, ruins reception). Demand has swamped supply for the moment, but we are catching up! PRICES 60v. unit in bakelite casket with handle, 5,000 m.a.h. 37/6. 30v. 21/-



Block Batteries Limited, By-Pass Road, Barking, Essex

Programme Criticisms by WHITAKER-WILSON

# Without Fear or Favour

## Average Listener says—


"What's Contemporary Music? According to my dictionary, the word contemporary means 'in our time.' I've been trying to apply that to the concerts of contemporary music from Broadcasting House on Friday nights.

"Does the B.B.C. mean to tell me the hyper-modern stuff really represents the best of the music written in our time?"

"Perhaps if I went to Portland Place and watched them playing, I might appreciate some of it; but on the wireless it is more than I can stand.

"I'm only an average listener, and I'm anxious to learn, but I must say I don't think I shall ever get to like anything quite so ugly.

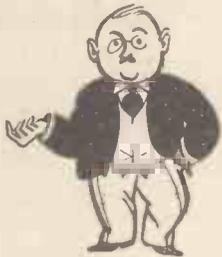"What is the point of it, anyway. I thought music was always supposed to be beautiful?"



### Monday

THERE is not much point in comparing or contrasting one dance band with another. Most of us have our likes and dislikes regarding them.

I listened to two excellent bands to-night. One was Carroll Gibbons and the Savoy

Orpheans, and the other Sydney Kyte and the Piccadilly band. I enjoyed both. I admired both. All I offer in the way of criticism is that there was too much similarity in the tunes. There also might be a limit to variations on one theme. If it is not "Since I met Yew," it is "If I had only met Yew," or "When first I met Yew," "If I had never met Yew." It is always Yew, anyhow.

Those fellows at the Radio Manufacturers' Association dinner had a good deal to say to each other. At all events, they kept us waiting for half an hour for the cabaret show.

Very good when it did come, though. Rex Evans made an excellent compère. He is one of the few who have grasped the principles of that delicate art.

While I think of it, Ivy St. Helier ought to be heard more often. Her imitation of an American woman trying to order *déjeuner* in a French hotel was one of the cleverest things I have heard for a long time.

John Tilley addressed that shareholders' meeting again. Excellent, of course, but I think it is the third time I have heard it. It may have been the Prince's first. If so, I am sure His Royal Highness enjoyed it.

### Tuesday

*Follies of the Air* (for the second time of asking) ought now to have established the show as a type in broadcasting. Davy Burnaby manages to infuse the Folly style into everything he does. As it is a distinct style nothing more need be said. Good enough.

It is quite possible to overdo regular features even in a ninety-hour week, but these trans-

missions of Students' Songs will stand a fair amount of repetition. It is certainly one excuse for the existence of the Wireless Male Voice Chorus, which seems to have improved a good deal lately.

### Wednesday

Henry Hall was broadcasting when I came into the house this afternoon. Another performance of "Don't Blame Me!" Henry, old man, I have never blamed you. I swear it. I couldn't do such a thing. So don't plead with me like that so often. Even now, I am typing with tears in my eyes.

Cortot said nothing new about the C-major Beethoven piano concerto, but what is there new to say about it? They all play it much the same.

Adrian Boult did manage to put a new construction on Mendelssohn's *Midsummer Night's Dream* overture. I want to hear him do it like that again—only in the summer, when I can listen in the garden.

### Thursday


I hear *Scots Wha Hae*—on St. Andrew's Night—thrilled Scottish listeners. I can understand it. I wished I could have understood it.

### Friday

I listened to *Red Tabs* with a copy of the manuscript before me. Val Gielgud once told me he thought it was not really a good play. Well, he's wrong. It is a good play because it drives home an interesting theme and isn't misty anywhere.

## The famous

# BRITISH GENERAL

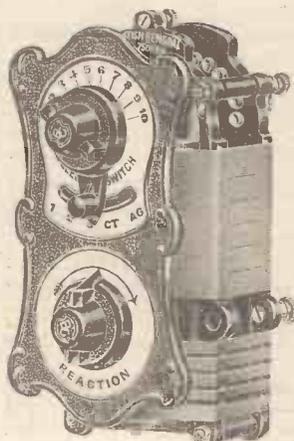

## TUNING UNIT

NOW REDUCED TO  
**10/6**

Increased demand and enlarged turnover enable us to offer this popular tuning unit at this remarkable price. Cuts out ordinary coils and covers all wave lengths from 200 to 2,000 metres. Easy to fix, simple tuning. Free wiring diagrams supplied.

From all dealers or direct

**BRITISH GENERAL  
MANUFACTURING Co. LTD.  
Brockley Works, London, S.E.4**

## Indispensable to Every Owner of a Radio Set!

INTENDED for the Listener who wants to know how his wireless set works, this Course takes the reader in easy stages through all the processes of wireless reception, from the aerial to the loud-speaker. Written by J. H. Reyner in collaboration with the technical staff of "Amateur Wireless," the authors have successfully avoided text-book style, yet every line in the book is technically accurate. The unique illustrations are a remarkable feature and constitute the finest series of explanatory diagrams ever included in any volume on the subject.

**3/6**  
Stocked by all Booksellers, or 3/10 post free from the publishers.



"Amateur Wireless,"  
58-61 Fetter Lane, London, E.C.4

**GET  
YOUR  
COPY  
NOW!**

# MORE STATIONS

are every day crowding each other and making clear reception almost impossible. Don't put up with that annoying background that

interferes with the complete enjoyment of your set. A Pix fixed in your aerial will reduce interference to a minimum on any set, because it sharpens tuning to a knife edge. You will be pleasantly surprised at the number of new stations you can hear clearly. Send us 2/- P.O., try it on your set for a week, if you are not completely satisfied with the result return it to us for full refund.




The British Pix Co., Ltd.  
Southwark Street, S.E.1.

**2/- FIX A PIX FOR BETTER RADIO**

WITH HANDY HOLDER 2/6

## YOUR SET CRACKLES...

Save it before it's silenced

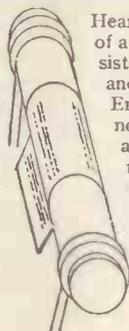

Hear it? Crackle—the death rattle of a dying resistance. Old type resistances can't help disintegrating and quickly going phut. So fit Eries. They have the lowest noise level of any Radio Resistance. It will pay you to scrap those two or three old grid leaks and spaghetts in your set and to replace with ERIE. Just notice the difference. Your dealer carries all values. Notice our Kit assortments on his counter.

**1/ PER WATT IMPREGNATED RESISTORS**

ERIE RESISTORS are specified for the BRITISH RADIOPHONE "MATCHED PERFECTION 7"

Write for new Colour Code Chart, FREE!

**RADIO RESISTOR CO.**

1, Golden Square, Piccadilly, London, W.1

The worst point about it is that its story may have been true. One of the best in this series of revivals.

The singer in the Casani Club Orchestra has asked us not to blame him, either. Blame Eric instead. He gets most of the kicks just now.

### Saturday

The third of the *In Town To-night* transmissions was a decided improvement on the other two.

I was sorry I could not get that Chinese gentleman's name down—the one who walked and cycled twenty thousand miles. I wanted to ask him to let me go back with him. With a good portable I could write these notes just the same.

How did you enjoy Mr. Forsythe's band? I thought it so different from most others I have heard as to be quite refreshing. Or is it that I am tired of the others?

Not that I have anything against Jack Hylton's. Smart lot. Even so, my conclusion was that "If You Were the Only Girl in the World" was the best tune he played. There is some real music in it. If you don't think so, don't blame me!

Did you hear the talk about that film coming over here—the lynching business, I mean. The



An impression of Carrell Gibbons

speaker who defended it talked rubbish. We are far too morbid as it is.

If there were a public execution in Hyde Park to-morrow I don't believe there would be standing room at ten guineas a ticket. Just as well the B.B.C. allowed such a discussion. If the Home Secretary heard it—I hope he did—he should know what to do.

### Sunday

I listened to Bach's *Ein' Feste Burg* because I like the tune of its chorale. A very dignified performance.

### Our Christmas Cover

Our portrait of His Majesty the King appealed to all our readers. Here is an extract from a letter written by C. H. Hopwood, M.B., Ch.B., of Calstock, Cornwall, to a member of our staff:—  
"Congratulate the Editor on his cover—it has caused great comment here."



PETO-SCOTT sends his Xmas Greetings to all readers of "Amateur Wireless" and best wishes for a Happy and Prosperous New Year. PETO-SCOTT have the interests of all their customers at heart and the full staff between now and Xmas is working day and night on the execution of orders.

All CASH or C.O.D. ORDERS RECEIVED UP TO TUESDAY, DEC. 19th, are guaranteed for delivery by XMAS, or notified otherwise by return of Post. SEND YOUR ORDER NOW.

## PILOT AUTHOR KITS

### 1934 CENTURY SUPER

**KIT "A"** Author's Kit of first specified parts, including Peto-Scott Metaplex chassis, but less valves, cabinet and speaker.

CASH or C.O.D. £8/16/6 Or 12 monthly payments of 16/- Carriage Paid

**KIT "B."**—As Kit "A" but with valves only. CASH or C.O.D. Carriage Paid, £13/2/0.

SEND ONLY 24/- Balance in 11 monthly payments of 24/-.

**KIT "C."**—As Kit "A" but with valves and Peto-Scott Universal Consolelet with baffle baseboard assembly. CASH or C.O.D. Carr. Paid, £14/8/6. Balance in 11 monthly payments of 26/3. Blue Spot 45 P.M. Speaker, if required, £2/5/0, or add 4/3 to each monthly payment.

KIT-BITS	£	s.	d.
1 Peto Scott METAPLEX Chassis	...	3	0
1 Wearite Bandpass Unit, Type G.N.2	...	1	1
1 Wearite Oscillator Coil (Type G.2)	...	10	6
1 J.B. .0005 mfd. Condenser, Type Nugang A.1	...	17	6
1 British Radiophone 2-gang Variable Condenser, .0005 mfd., Type 458A	...	1	1
3 Wearite, type C.T.I. Intermediate-frequency Transformers	...	1	11
1 Lissen "Hypernik" L.F. Transformer	...	12	6
1 Set Specified Valves	...	4	5
1 Peto Scott Specified Cabinet, complete with Baffle-Baseboard Assembly	...	1	4

### 5-GUINEA S.G. 3

**KIT "A"** Author's Kit of first specified parts, including Metaplex Baseboard, with all necessary wire, screws and flex, but less Valves, Cabinet and Speaker.

CASH or C.O.D. £2/2/0 Or 12 monthly payments of 4/- Carriage Paid

**KIT "B."**—As for Kit "A" but with Valves as specified. CASH or C.O.D. Carriage Paid, £3/13/3. Or send only 6/9. Balance in 11 monthly payments of 6/9.

**KIT "C."**—As for Kit "A" but with Valves and specified Peto-Scott "Compact" Cabinet and Speaker. CASH or C.O.D. Carriage Paid, £4/12/9. Or Send only 8/6. Balance in 11 monthly payments of 8/6.

## PETO-SCOTT PERMANENT MAGNET MOVING-COIL SPEAKER

Complete with input transformer. Send only 2/6; balance in 5 monthly payments of 4/3. Cash or C.O.D. Carriage paid, 19/6.

Class "B" Model Cash or C.O.D. Carriage Paid £1/2/6 or 2/6 down and 6 monthly payments of 4/-.


YOURS FOR **2/6**

## XMAS ORDER COUPON

PETO-SCOTT Co., Ltd., 77, City Rd., London, E.C.1  
Telephone: Clerkenwell 9406/7.  
West End Showrooms: 92 Elyk Habour, London, W.C.1.  
Telephone: Holborn 3218.

Dear Sirs,  
(a) Please send me.....  
(b) I enclose Cash/Deposit.....  
NAME.....  
ADDRESS.....

A.W. 16/12/33.

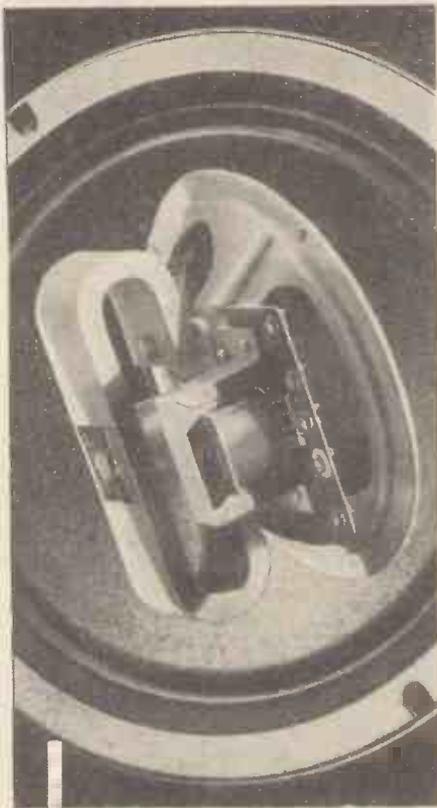

## It must be MAGNAVOX

There is always a demand for a de-luxe speaker, and it is that demand which the Magnavox P.M. "Senior" Model at £3.3.0 so completely fills.

Based on the unique Magnavox experience of 22 years' standing it is—only naturally—the finest P.M. speaker obtainable.

The same exclusive qualities are found in the P.M. "Standard" Model—perfection in a smaller speaker—and this costs 37/6; both models, of course, being fitted with universal transformers, for Class "B," etc.


You can buy cheaper speakers, but if you are to feel really confident and happy about your purchase there can be no alternative—it MUST be MAGNAVOX.

"SENIOR" MODEL  
£3 . 3 . 0

"STANDARD" MODEL  
£1 . 17 . 6
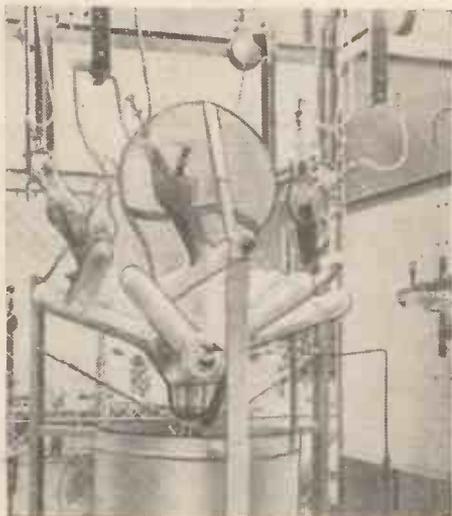
# BENJAMIN

The Benjamin Electric Ltd., Tariff Rd., Tottenham, N.17



## Mystery at Bisamberg

NEAR Vienna is Bisamberg, now "on the map," etherically speaking, because it is the site of the new high-power Austrian broadcasting station. So far so good. Being a keen DX'er, and therefore greatly interested in anything connected with foreign stations, I eagerly waited for the photographs to arrive showing what this new ether giant was really like.

Came the photograph you see here. With it the cryptic caption: "An interior view of a section of the works." What do you know about that? I give you three guesses at the nature of the monstrous-looking piece of work you see in the foreground.

In fact you can have as many guesses as I did. To me it was something rather horrible. A hatefully shaped glass "God of the Machine." Look at its bulbous head, its sinuous tentacles, its quite disgusting outgrowths! Horrible, eh?

But personal feelings had to be ruthlessly suppressed. This was a first-class mystery. Austria, I always imagined, was a long way this side idolatory. Yet nothing less than a radio idol appeared to answer the question: what is it?

Feeling pretty grim, I went out with my mystery, determined to solve it, or forever deny myself reception of Bisamberg. Indeed, I felt that with such a monster in the building it could be only a matter of time before it got the upper hand, and then heaven help the poor unprotected engineers!

My first effort was not very helpful. A technically minded friend took one look at the photograph and said: "Well, what's the joke?" I assured him it was no joke, but he only laughed, the fool.

On to Broadcasting House. First official took one look at it and exclaimed: "Really, I never thought you were interested in deep-sea fishing."

Visibly weaker, I sent in my card to an engineer I knew slightly. "Have you ever come across anything like this before?" showing him the photograph. He yelled. "No, and I hope I never shall," he answered. "Gee, fancy that at Brookman's Park!"

So in desperation I consulted a Very High Authority. He wrote as follows: "The thing you take to be an idol or deep-sea monster is really only a mercury-vapour rectifier, or rather a bank of rectifiers. No, we don't use such things over here, but we shall have a tank rectifier at Droitwich."

I tell you this because you may see this photograph elsewhere. And a heartless editor may see fit to append the photographer's caption: "An interior view of a section of the works."

And that may keep you awake at night, as it did me  
O. H.

**THE SUPREME VALVE**  
but at **ECONOMY** prices  
THE PLUMP NOTE: "Impudence!  
My volume has NOTHING to do with  
Christmas pudding! It was entirely  
developed, at small cost, in a Tung-  
ram symphonic valve!"



**OLD SETS RE-VITALISED BY  
TUNGSRAM'S NEW SYMPHONIC  
VALVES**



New life from your old set—without change of circuit! This Christmas—re-vitalise your set with Tungram Symphonic Valves! Specially designed, after months of research, to improve the volume, quality and sensitivity of old A.C. sets! Inexpensive, too!

**THE SYMPHONIC A.C. RANGE INCLUDES**


- Symphonic Screen Grid AS 4120
- Symphonic VIM Screen Grid AS 4125
- Symphonic H.F. Pentode HP 4100
- Symphonic VIM H.F. Pentode HP 4105
- Symphonic Detector AP 4101
- Symphonic Multi Grid Output APP 4120

Ask your Dealer or write our Technical Dept.

# TUNGSRAM
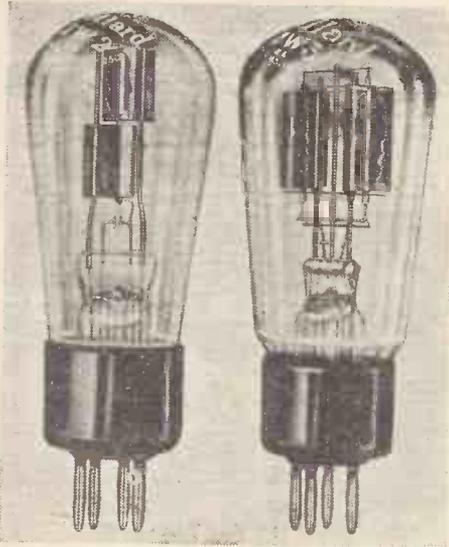
## BARIUM VALVES

Tungram Electric Lamp Works (Gl. Brit.) Ltd, 72 Oxford St., W.1  
TAS/TU



(Left) Mullard IW2 indirectly-heated rectifier and (right) the IW3

### New Rectifiers

**DIRECTLY-HEATED** valves for receiving circuits went out of fashion many years ago. Why hasn't the directly-heated rectifying valve followed suit? It is well known that in an A.C. mains set the emission from the rectifying valve begins almost instantly, causing strain on the fixed condensers and other components.

To overcome this defect, delayed-action switches and other rather unnecessary gadgets of a similar nature were introduced. The Mullard Company have now released some indirectly-heated rectifying valves which take approximately the same length of time before they begin emitting as do normal indirectly-heated receiving valves.

This immediately overcomes the trouble of voltage surges, removes the strain on the fixed condensers and obviates the use of delayed switching.

From tests we have made these valves appear to be entirely satisfactory and, in fact, a distinct improvement over the old directly-heated type. The hum level is distinctly lower.

As the cathode of these valves is connected internally, they are suitable for replacement in practically any type of set where a directly-heated valve is at present in use. The IW2 will undoubtedly be the most popular valve. A 4-volt heater at 1.2 amperes and with 250-0-250 volts r.m.s. will give 60 milliamperes. The IW3 gives 120 milliamperes with 350-0-350 volt r.m.s.

A special valve is the IW2A, designed to give almost perfect voltage regulation. This has a 4-volt heater, but at the current of 2.4 amperes, and will give 60 milliamperes with 250-0-250 volts r.m.s.

### More Dial Alterations

**T**O enable users of H.M.V. and Columbia receivers to sort out the stations during the Lucerne Plan changes, special cards are being prepared by these companies.

These cards consist of a replica of the present station dial and a sketch of a dial based on the Lucerne Plan.

The card, which will be available free of charge from the dealer from whom the instrument was purchased, is only intended as a temporary measure. Later, when wavelength conditions may be considered to have settled down once more, new tuning-dial strips will be issued at a nominal charge.

# MAINS INTERFERENCE



## SUPPRESSED

with the

# T.C.C. CONDENSER ANTI-INTERFERENCE UNIT

**NOISY** mains, motors, generators and other electrical apparatus need no longer spoil your reception. In nine cases out of ten interference of this type can be reduced to a reasonable minimum by fitting a T.C.C. Anti-Interference Unit at the house side of your main switch. In other cases it can be entirely suppressed.

Bad cases of interference from electrical apparatus may need individual attention and suppression at source, but whenever the remedy is "two condensers across the mains and centre point earthed" this unit provides an efficient and handy solution.

★ **NOTE**: — 'Atmospherics' are not mains noises.

PRICE COMPLETE **10/6**

Supplied complete with instructions

THE TELEGRAPH CONDENSER CO. LTD.  
WALES FARM RD., N: ACTON, W:3:

# "Old hands" use DUBILIER Condensers

The new range of Dubilier Condensers marks the greatest advancement in Condenser design and more than maintains Dubilier's established position as the foremost manufacturers of the highest quality products at the lowest possible prices. It would pay you to be more familiar with the latest developments in condenser design. The new Dubilier booklet tells you all there is to know. Write for your free copy.



# DUBILIER ★ CONDENSERS

DUBILIER CONDENSER CO. (1925) LTD., DUCON WORKS, VICTORIA ROAD, NORTH ACTON, W.3

**Ensures Trouble-free Radio in Every Home—  
RADIO UPKEEP AND REPAIRS FOR AMATEURS**

By ALFRED T. WITTS, A.M.I.E.E.

Keep your set up to the highest pitch of perfection—this new book for every radio listener shows you exactly how to deal with all types of breakdowns and imperfections in your set and its components.

Do not hesitate—order to-day. 5/- from a bookseller or 5/5 direct from the publishers. A p.c. brings full details.

## PITMAN

Parker Street, Kingsway, London, W.C.2.

### Sets That Set A Standard.—I

## The 1927 Ether Searcher

EVERY now and then a set is designed, built and published—and from the first day of its appearance before the wireless public its success is assured. Some sets are like that.

Looking back over the years AMATEUR WIRELESS has been designing and publishing wireless sets for constructors this truism about sets in general is once more emphasised.

Some sets, in this long vista of designs of every conceivable type, stand out head and shoulders above all others. It would seem that certain sets are pre-destined to set the standard for their year.

### Back to the Year 1927

It is a far cry back to the year 1927. In November of that year the very first Ether Searcher set was designed. Alan Hunter did it, but even he would probably willingly admit that he had no thought of producing the standard type of set for that year.

Yet records prove that the first Ether Searcher was the set of the year 1927-8. Many hundreds of blueprints were sold, and dozens of letters poured into the editorial offices, all bearing witness to the success of this Ether Searcher.

Looking back on that set, we realise how useless it would be for present-day conditions. It had quite an elementary circuit, consisting of a detector valve with reaction, followed by a resistance-capacity-coupled stage, followed by a transformer-coupled power valve. No pentodes or screen-grid valves in those days!

Plug-in coils were used for tuning and reaction. The aerial was coupled to the grid-tuning coil of the detector by a small fixed condenser—even the pre-set type of condenser had not arrived.

Yet this simple set undoubtedly set a fashion in detector circuits; in circuits consisting of a detector and resistance-transformer coupling. It so happened that just that combination of valves gave enough volume to bring up foreigners to full loud-speaker strength, but not enough to overload the power valve.

### Purity of Reproduction

Much of the purity of the resistance-capacity cum-transformer-coupled sequence, which succeeded the two-transformer sequence that had previously held sway was no doubt due to the avoidance of overloading.

Whatever the causes of its success, the first Ether Searcher set a standard. Down through the ensuing years there have been different Ether Searchers, improved Ether Searchers, in fact Ether Searchers so different from the original model as seemingly to have very little relation to it.

Yet all Ether Searchers have had this in common: they have set a standard for their year. The New Year of 1934 approaches and with it, well, another Ether Searcher—naturally. Be patient. It is coming soon.

Constructors of chassis sets will be interested in the new valve holders manufactured by Ferranti, Ltd. They are available in four-pin, five-pin and seven-pin types, and are provided with soldering tags so constructed that the flux cannot run into the sockets.

An error occurred in the last sentence of the test report on the Ready Radio E.M. Plus 4 kit published on page 1083 of the last issue. It should have read: "... it will give results comparable to many commercial receivers at a much higher price."

**A USEFUL XMAS GIFT**

THE HANDYMAN...  
MOTORIST...  
WIRELESS CONSTRUCTOR...  
ENGINEER...  
MODEL MAKER...  
**ALL NEED THE SOLON**



Electric soldering with the "Solon" supersedes the old-fashioned methods. It gives cleaner, stronger joints; it is quicker, cheaper, simpler. Plug in to any lamp-holder, switch on and in four minutes the Solon is ready for continuous use.

**SOLON**  
ELECTRIC SOLDERING IRON

**7/6** FOR ALL STANDARD VOLTAGES. If unable to obtain, send us the name of your nearest dealer.

W. T. HENLEY'S TELEGRAPH WORKS CO. LTD.  
DEPT. T.H.14, HOLBORN VIADUCT LONDON, E.C.1  
BRITISH THROUGHOUT

**Postcard Radio Literature**

Here "Observer" reviews the latest booklets and folders issued by well-known manufacturers. If you want copies of any or all of them **FREE OF CHARGE**, just send a postcard giving the index numbers of the catalogues required (shown at the end of each paragraph) to "Postcard Radio Literature," AMATEUR WIRELESS, 58 61 Fetter Lane, E.C.4. "Observer" will see that you get all the literature you desire. Please write your name and address in block letters.

**Special Cone Construction**

**L** OUD-SPEAKERS to suit all requirements are manufactured by Nuvolon Electric, Ltd., and descriptions of all these loud-speakers are contained in a new list. An interesting point to note is the construction of the cones. A 14-lb. weight can be placed on the top of the speech coil without doing any harm to it. **110**

**Car Radio Folder**

Are you one of the more fortunate who own a car? If you are then you should write for this folder of car radio. The distributors of these sets are the Arvin Electric Co. One set is priced at £12 12s., being complete with suppressors for spark-plugs and distributor, remote control and loud-speaker. The output is 2.75 watts. **111**

**Coscor Accessories**

A new Coscor folder catalogue is devoted to radio accessories, including extension loud-speakers, pick-ups, high-tension batteries and accumulators. **112**

**Every Constructor Requirement**

Almost anything the constructor requires is contained in a comprehensive catalogue published by J. H. Taylor. It contains 120 pages of information, with a six-page section of bargains ranging in price from 3d. to 5s. It is impossible to list every component manufactured, but this firm can supply any materials advertised by the leading manufacturers. Truly a useful list to have on hand. **113**

**Notes and Jottings**

**E** VERY radio dealer should have a copy of the 1934 edition of *The Wireless and Gramophone Trader Year Book* (5s. 6d., post paid). This is the tenth successive year of publication and the issue just published contains many new and important features. The page size has been doubled and it is much more convenient in its new form for reference purposes.


Full o' Power batteries, manufactured by Siemens Electric Lamps and Supplies, Ltd., now include two double-capacity batteries to fit the cabinets of the new Coscor receivers.

From the land of skyscrapers and tall stories comes yet another "true" tale. An eminent American professor had a very brainy idea. He trained a powerful telescope upon Venus. The light that was received was then projected on to a photoelectric cell. This caused a current flow from the photoelectric cell sufficient to be fed into a powerful amplifier. It is said that the sound that issued from the loud-speaker was comparable with oriental music. Perhaps "unearthly" would be a better definition.

*A Complete Range* **ROTARY SWITCHES**



LIST No. 585

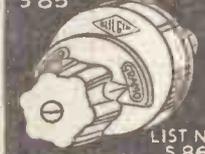

LIST No. 586



LIST No. 584



LIST No. 5110



**ON-OFF TYPE**  
The finest snap action switch obtainable. Fitted with phosphor bronze cleaning action springs and bakelite indicating plate. Black, Walnut, or Mahogany finish. Price **1/6**  
List No. S. 85.

**RADIOGRAM TYPE**  
Quick action, single-pole change-over switch, with radiogram indicating plate. Black, Walnut, or Mahogany finish. Price **1/9**  
List No. S. 86.

**THREE-POINT SWITCH**  
A quick-action wavechange switch specially made to match our popular models S. 85 and S. 86. Complete with bakelite indicating plate, engraved "Medium" and "Long." Black, Mahogany, or Walnut finish. Price **2/-**  
List No. S. 84.

**DOUBLE-POLE CHANGE OVER**  
For complete control of any receiver, Bakelite nameplate engraved "Radio," "Off," "Gramo," and on the reverse side "Short," "Off," "Long." All terminal connections. Price **2/6**  
List No. S. 110.

SEND FOR 60-PAGE CATALOGUE No. 153 "A". Enclose 2d. Postage

**A. F. BULGIN & Co.**  
Abbey Road, Barking

London Showrooms 9, 10, 11  
Coursier St., Chancery Lane, E.C.4.

**FIXED IN ONE MINUTE**  
THIS BRITISH-MADE  
**ULTRA-MODERN AERIAL ELIMINATOR**



(A) RED WIRE TO AERIAL TERMINAL  
(B) BLACK TO EARTH TERMINAL

TO OUTSIDE EARTH

**SIR AMBROSE FLEMING, F.R.S., says:-**  
"I always feel that there is a constant need for some invention, however small, which may add something to the question of avoiding interference and improving reception."

**MAKES AERIALS UNNECESSARY. IDEAL FOR FLATS, ETC. INTERFERENCE REDUCED. SELECTIVITY IMPROVED. IN SHORT—A PROVED SUCCESS AND INVALUABLE. 2/- for Battery or A.C. Wireless Receivers. 2/6 for D.C. Mains.**  
(Postage 2d. England, Scotland, Wales)

Send crossed P/O's:-  
**BRITISH & EXPORT P. LTD.,**  
Sales Dept., 28/9 Wheatheaf House, Carmelite Street, London, E.C.4

LET "A.W." SOLVE YOUR WIRELESS PROBLEM

**Why not broadcast YOURSELF?**

**SEASON'S GREATEST NOVELTY. HOME MICROPHONE.** You speak in one room—voice comes over radio in another. Easy to connect—fits any set—no extras required. Just connect, press button and speak. Causes endless fun at parties. Complete with 16 ft. flex and full instructions. Post Free 5/6.  
Full Novelty & Joke List Free.  
**D. J. HUNTER**  
304 Edgware Rd., London, W.2

**RADIO SUPPLIES**  
Send your list of Radio needs for our quotation. Kits, Parts, sets, etc. Everything in Radio stocked. Prompt delivery, seven days' approval. Catalogue free. Taylor and Standard Wet H.T. replacements stocked.  
**A. TAYLOR, 9 GROVE ROAD, BALHAM, S.W.12.**

**FIT A FILT**

PRICE **2/6**  
REFILLS 1/6

**PREPAID ADVERTISEMENTS**

Advertisements under this head are charged **THREEPENCE PER WORD**, minimum charge **THREE SHILLINGS. DEPOSIT SYSTEM.** As the publishers cannot accept responsibility for the bona fides of advertisers in this publication, they have introduced a system of deposit which it is recommended should be adopted by readers when dealing with persons with whom they are unacquainted. It is here explained. The amount of the Deposit and Fee must be remitted by Postal Order or Registered Letter (Cheques cannot be accepted), addressed to "Amateur Wireless," Advertisement Department, 58/61 Fetter Lane, London, E.C.4.

**PATENTS.**—Trade Marks, "Advice Handbook" free.—B. T. King, Regd. Patent Agent, 146a Queen Victoria Street, London.

**REPAIRS** to Loud-speakers, Transformers, and Head-phones. 4/- each; Blue Spots, 5/-. Moving Coils a speciality. Cones fitted, Eliminators and Sets quoted for. Satisfaction guaranteed. Prompt service. Inquiries invited. Terms to trade.—Loud-speaker Repair Service, 5 Balham Grove, London, S.W.12. Battersea 1321.

**CHARGING WITHOUT MAINS**—Thousands are charging their own accumulators, why don't you? "Tonic" trickle-charger kits keep 2-volt accumulators fully charged. Ideal for remote districts. From 7/-, postage 9d. Full particulars, stamp.—Williams, Netherend, Cradley, Nr. Birmingham.

**GRAMOPHONES**, Radiograms, Motors, Arms, Pick-ups, Loud-speakers, Horns, Springs, Needles, Repairs, cheapest.—Catalogue, Regentem, 120 Old Street, London, E.C.1.

**INSTRUMENT AND RESISTANCE WIRES.** Transformer and Choke Stampings. Insulation. Lists free.—Lumen Electric Co., Scarisbrick Avenue, Litherland, Liverpool, 21.

**TELEVISION APPARATUS.**—We specialise in all components, Discs, Neons, Lenses, Motors, etc. Illustrated List Free.—Sanders, 4 Grays Inn Road, London, W.C.1.

**"UNIVERSAL" RADIO BARGAINS.**—Iron-cored dual coils, 3/3. Ready Radio 303 kits, 17/6; with cabinet and M.C. speaker, 35/-. Silver Ghost M.C. speakers—get our price. Sinclair M.C. speakers, 15/11. Blue Spot 100 U's, 14/11. D.X. screened coils, 2/11. S.T.500 kits, in sealed cartons, 69/6. Class-B drivers and chokes, 5/11. H.M.V. screened chokes, 10d. Dario super transformers, 3/6. Lotus transformers, 2/11. Six-pin coil formers and cans, 1/-. Record valves, 3/3. Variable condensers, 1/11. Fixed and leaks, 5d. Full range Lissen components, kits, and sets at right prices. Thousands of other astounding bargains. Stamp for our huge bargains lists and prints.—"Universal," 20 Victoria Road, Peckham, S.E.15. New Cross 4933. Stockists Milnes H.T. units and spares.

**CHARGE YOUR BATTERIES WITH SERADEX BATTERY CHARGERS.** Illustrated catalogue for stamp. Models from 22/15/0.

**SERADEX RESISTORS**, as specified by leading designers. Fitted wire ends. Grid leaks, 6d.; 1/2-watt type, 6d.; 1 1/2-watt type, 8d. Full range of lists for stamp.

**CATALOGUES OF SERADEX MAINS EQUIPMENT**, Television Accessories, etc., for stamp.—575 Moseley Road, Birmingham.

**REVOLUTION IN H.T. BATTERY CONSTRUCTION.**—The Nonfade Sectional H.T. Battery (prov. patent), the home-constructor's dry battery, has arrived. No scrapping for small defects. Each cell can be tested with cell tester supplied free with battery. When battery runs out, send for Nonfade Cells and rebuild at home: result, new battery at two-thirds cost. Price: 66 volts, 5/8; 108 volts, 7/6; 126 volts, 9/6; Pye portable, 11/6. Refills when required, 3/8, 6/-, 8/8, 9/6. Nonfade Chemical Earth, 1/-. All post free.—Nonfade Works, Haselbury, Crewkerne.

**ANY RADIO SET, Kit, or Gramophone Part** at bottom price or H.P. Catalogues free.—A. W. Burt, 185 High Street, Deptford, S.E.8.

**WANTED.**—Good Modern Wireless Parts, Sets, Eliminators, Meters, Valves, Speakers, etc. Spot cash waiting. Send or bring. We pay more than any other dealer. Open 9-8.—University Radio, 142 Drummond Street, Euston, N.W.1.

**WANTED.**—Rotary Converter, second hand. D.C.240 to A.C. 232/245.—Dixon, 12 Waldegrave Park, Twickenham.

**INFORMATION BUREAU**

Will every querist please observe the following revised rules.

Please write concisely, giving essential particulars. A fee of one shilling postal order (not stamps), a stamped, addressed envelope and the coupon on the last page must accompany all queries. Not more than two questions should be sent at any time.

Slight modifications of a straightforward nature only can be made to blueprints. For more serious alterations the minimum charge is 2/6.

Blueprints supplied by us will be charged for in addition, but of course, readers may send their own blueprints for alteration.

Modifications to proprietary receivers and designs published by contemporary journals cannot be undertaken. Readers' sets and components cannot be tested by us. Queries cannot be answered by telephone or personally. Readers ordering blueprints and requiring technical information in addition should address a separate letter to the Query Department.

We do not answer queries in cases where the fee is omitted.

Queries should be addressed to the Query Department, "Amateur Wireless," 58/61, Fetter Lane, London, E.C.4.

**LET US QUOTE FOR "A.W." SPECIFIED COMPONENTS.** Eliminators, Speakers, anything radio. S.T.500 components. Keenest prices, guaranteed goods.—Childs', Radio Factors, 29 Moray Road, London, N.4.

**INVENTOR'S POCKET-BOOK.**—How to patent. Invaluable aid to selling your ideas. Expert advice. Copies free.—Edwin O. Axe, A.I.M.E., 27 Chancery Lane, London.

**5-GUINEA S.G.3 KIT** with Valves, Compact Consolelette Speaker Cabinet, Batteries, etc., 24/4/0. Class-B-Four Kits, 22/10/0; S.T.500 Guaranteed Kits, 23/19/6; Etherdyne Super Kits, 26/5/0. Keenest prices quoted for Radio Requirements. Old Sets taken in part exchange for 1934 models.—Servwell Wireless Supplies, 64 Prestbury Road, London, E.7.

**HUNDREDS REAL UP-TO-DATE BARGAINS.**—Clear cheap. List.—Simmons, 9 Ilfracombe Avenue, Southend-on-Sea.

**180 ACCUMULATOR CHARGERS**, 1/2 amp., 2-6 volts, in ventilated metal case with mains flex (Westinghouse rectifiers) 7 days' trial, 13/11, postage 6d. 1 1/2 amp., 21/-—W. Arden Agency, Wollaston, Wellingborough.

**MAINS TRANSFORMERS REWOUND.**—Prompt service, satisfaction guaranteed. Prices on request.—The Sturdy Electric Co., Wesley Terrace, Dipton, Newcastle-on-Tyne.

**N.P. BATTERY CHARGERS** for A.C. Mains; trade lists free.

**N.P. MAKE CHARGERS** to suit requirements; send for prices; we are the lowest in the trade.

**N.P. ADVISE** on all matters of Battery Charging with diagrams and instructions.

**N.P. have** a few slightly used travellers' models, bargains for cash; trial 7 days; satisfaction or cash refunded.

**N.P. send** trade lists and photographs of battery chargers, from 62/6 to £17 10s., suitable for large stations.—Nash Products, Ltd. (Dept. A.W.), Stechford, Birmingham 9.

**NEW AND USED RADIO COMPONENTS.**—Cheap for cash.—Arlin, 44 Ranelagh Road, Westminster, S.W.1.

**FEED YOUR WIRELESS** with Fuilers H.T. Accumulators 120 volts, 6,500 milliamperes. Delivered free on first payment of 7/8. Lists free.—Leslie's Radio, Catford, London.

**OAK CABINETS**, good finish, hinged lid, all sizes to clear from 7/6 C.P. Radio Catalogue, 1/-.—Gibson, 99 Burnley Road, Alnsdale, Lancs.

**SUPER "DIRECTOTONE" KIT BARGAINS.**—Remarkable offers to home constructors. All parts guaranteed. Every component carefully tested. Straight 2-valve kit, 14/6. Straight 3, 17/6. S.G.3, employing 2 H.F. stages, 24/6. Also the new S.T.500, 66/6. All carriage paid, cash or C.O.D. Large quantities of radio parts at revolutionary prices! 2d. stamp brings lists of these with particulars of our Special December Snip!—The Direct Trading Company, 65-66 York Terrace, Baker Street, N.W.1.

**LOUD-SPEAKERS, TRANSFORMERS.**—Any make promptly and efficiently repaired, 3/6. Satisfaction guaranteed.—Breeze, Clapper House, Morden, Kent.

**"A.W." SPECIFIED TELEVISION DISC RECEIVER.**—Baseboard mounted, wired, tested, £3.—Bennett, Jesmond, Redstone Copse, Redhill.

**SAVE MONEY: SPECIAL CHRISTMAS OFFERS** from Melford. Author kit specialists. S.T.500, 78/- to £5 5s.; 3, 29/6. Lists free.—5 Queen's Place, Hove.

**UNIT.**—Blue Spot, nearly new, cost 25/-; sent C.O.D. 7/6, or near offer. Post card.—Davis, 54 Southcote Road, Bournemouth.

**TELEVISION CONSTRUCTORS' GUIDE**, 1/3.—Illustrated catalogue free. Notes 1d.—Goodman Television, 16 Highbury Terrace N.5. (Nr. Highbury Station).

**SPECIAL OFFER IN ACHROMATIC LENSES** for television: 2 in., 11/6; 1 1/2 in., 10/-; 1 1/4 in., used, 6/6. Kits of mirror drums, £1. Stamp list.—Cooks, 83 New Oxford Street, W.C.1.

**BANKRUPT BARGAINS.**—List free with 3-v. diagram. S.T.300 kit, 35/-; S.T.400 kit, 45/-; S.T.500, 52/6. Class-B Burgoyne sets complete, listed 26/10/-, my price 24/17/6. Lumophon D.C. and A.C. Mains Sets in stock. Lumophon Class-B 4-v. S.G., complete, £6. D.C. Eliminators from 12/-; A.C. from 28/6. P.M. M.C. Speakers from 12/6. Triotron Valves from 3/6. All S.T. parts in stock. Southern Radio Class-B Drivers and Chokes, 4/6. Stal, 5/6. Latest B.G. Tuners, 7/-. Formo 3-gang units with 2-gang, list 33/6, my price 16/6. Formo Bandpass in cabinet, P.M. M.C., 25/-. Triotron ditto, 20/-. Millgate S.T. Coils, 4/6. Amplion, 5/6. 0005 Wavenaster S.M., 3/6. Pick-ups from 6/9. Large stock of various goods at very keen prices. One only Brownie Battery Superseder, secondhand, 20/-. Part exchange. Any kit or Set supplied. Let me know what you require and what you have.—Butlin, 143B Preston Road, Brighton. Phone: Preston 4030.

Any Amplion, Blue Spot, Baker, Celestion, Epoch, Ferranti, Grampian, Igranic, Lamplugh, Magnavox, Ormond, R. & A., Rola, Sonochorde, or W.B. Speaker supplied.

Send 5/- only

and pay balance by monthly instalments. No references. Entirely private and confidential.

KITS, PARTS, SETS, ELECTRIC CLOCKS, ON EASY TERMS,

Send for catalogue and state requirements to

**TURNADGE & PARTNERS LTD.,**  
110, Fleet Street, London, E.C.4.

**FULL-SIZE BLUEPRINTS**

When ordering, please send Postal Order, NOT STAMPS. Quote the Blueprint number shown below; not the number of this issue.

**CRYSTAL SET (6d.)**

1931 Crystal Set . . . . . AW308

**ONE-VALVE SETS (1s. each)**

B.B.C. One-valver . . . . . AW387  
Portable Short-wave One . . . . . AW354

**TWO-VALVE SETS (1s. each)**

Clarion-voice 2 (SG Det, Pen) . . . . . AW371  
Home Station A.C. 2 (D, Pen) . . . . . AW374  
B.B.C. National Two (D, Trans) . . . . . AW377  
Melody Ranger Two (D, Trans) . . . . . AW388  
Full-volume 2 (SG Det, Pen) . . . . . AW392  
"A.W." Iron-core Two (D, Trans) . . . . . AW395  
"A.W." Iron-core Two with Q.P.P. . . . . AW396  
Consolectric Two (D, Pen) . . . . . AW403  
Screen-grid Two (SG Det, Trans) . . . . . WM289  
A Two for 7 Metres (D, Trans) . . . . . WM295  
New-style Radiogram (D, Trans) . . . . . WM299  
A.C. Quality Gem (D, Trans) . . . . . WM312

**THREE-VALVE SETS (1s. each)**

James Push-push Three (SG, D, Q.P.P.) (1/6) . . . . . AW378  
Everybody's Home Radiogram (SG, D, Trans) . . . . . AW381  
Home-lover's New All-electric 3 for A.C. mains (SG, D, Trans) . . . . . AW383  
Our Up-to-the-minute Three (SG, Westector, L.F. Trans) . . . . . AW384  
Class-B Three (D, Trans, Class B) . . . . . AW386  
S.S.3 (A.C.) (SG, SG Det, Pen) . . . . . AW390  
"Up-to-the-minute Three" with Class B, 1/6. . . . . AW384B  
New Britain's Favourite Three (D, L.F, Class B) . . . . . AW394  
A.C. Triodyne (SG, D, Pen) . . . . . AW399  
Home-built Coil Three (SG, D, Trans) . . . . . AW404  
Fan and Family Three (D, 2LF) . . . . . AW410  
£5. 5s. S.G.3 (SG, D, Trans) . . . . . AW412  
1933 Economy S.G. Three (SG, D, Trans) . . . . . WM306  
Harris Ethergram (SG, D, Pen) . . . . . WM308  
A.C. Calibrator (SG, D, Pen) . . . . . WM309  
Narrow-pass Three (SG, SG Det, Pen) . . . . . WM314  
£6 6s. Radiogram (D, RC, Trans) . . . . . WM318  
Simple-tune Three (SG, SG Det, Pen) . . . . . WM327  
Tyers Iron-core Three (SG, SG Det, Pen) . . . . . WM330  
I.C.B. Three (D, L.F, Class B) . . . . . WM333  
Economy Pentode Three (S.G, D, Pen) . . . . . WM337  
Three-range Three (SG, D, Pen) . . . . . WM336  
Simplicity A.C. Radiogram (SG, D, Pen) . . . . . WM338  
Duo-tune Three (SG, D, Pen) . . . . . WM341

**FOUR-VALVE SETS (1s. 6d. each)**

Melody Ranger (SG, D, RC, Trans) with copy of "A.W." 4d. postage . . . . . AW375  
"A.C. Melody Ranger" (SG, D, RC, Trans) . . . . . AW380  
Signpost Four (SG, D, L.F, Class B) . . . . . AW398  
"A.W." Ideal Four (2SG, D, Pen) . . . . . AW402

Copies of the "Wireless Magazine" and of "Amateur Wireless" containing descriptions of most of these sets can be obtained at 1s. 3d. and 4d. respectively, post free. Index letters "A.W." refer to "Amateur Wireless" sets and "W.M." to "Wireless Magazine". Address letters:

Amateur Wireless Blueprints Dept., 58-61 Fetter Lane, London, E.C.4

**HOME BROADCASTER**



Why not be your own Announcer and give your voice a microphone opportunity.

OUR NEW LESDIX NO. 11 SUPER MICROPHONE in bakelite case is a marvel for speech and music reproduce 5/6

tion on your radio set. For hand or stand. ONLY Can be used with any radio set for home broadcasting. Your Christmas would be incomplete without one. 5/6 only. GET OUR LATEST SALES LIST "A."

**LESDIX SERVICE CHARGERS A.C.—D.C.**



We have 25 models to offer and our prices are low for special requirements. Three popular sizes are the AC109A for 36 cells, the AC106 for 108 cells, and the Lesdix Super Six for 200 cells.

Write for "CHARGER" Leaflet "A"



**ELECTRADIX RADIOS**,  
218 Upper Thames Street, London, E.C.4  
Telephone City 0191

**STATION HETERODYNING**

CUT OUT WHISTLES, SIDEBAND SPLASH,

**WITH THE 'KINVA' FILTER**

Three highly developed types, for use in Detector or L.F. Anode of any Set. Type A.3 Super Filter, 3,500 cut-off, 13/6. Types 'D' 2-Range, or 'B' variable 7/6. Complete with Instructions. (Lists Free.)

**POSTLETHWAITE BROS.,**  
(Dept. D), Kinver, Stourbridge

# G.E.C. H.T.

**SUPER INSULATED CELLS**  
**Long Life • Purity and Power**  
**GUARANTEED CAPACITY**

**120 volt**  
**144,000 milliwatt hours**  
**GUARANTEED**

**PRICES :**  
60v : 5 6. 99v : 9 -. 108v : 10/-. 120v : 11/-.  
150v : 14/-. 60v Triple Capacity : 12/-.  
120

*A Reminder*  
SEE THAT YOU  
HAVE PLENTY OF  
**G.E.C. H.T.**  
THIS CHRISTMAS



MADE IN  
ENGLAND

Sold by all  
Wireless Dealers

**BETTER RESULTS THIS CHRISTMAS WITH G.E.C. H.T.**

Advt. of The General Electric Co. Ltd., Magnet House, Kingsway, London, W.C.2

# 3 GREAT SAVINGS

## 1 SAVE MONEY

**19s. 7d. IN THE £.**  
Obtain H.T. for your Radio from one of the NEW AND IMPROVED EKCO UNITS and you save 19s. 7d. in the £. Sound design and utmost efficiency enable running costs to be reduced to 1/- per year.\*

\* Based on 3 hours daily use of an average 3-valve set.



## 2 SAVE TIME

**NO MORE ACCUMULATOR CHARGING.** Use an EKCO Combined Power Unit, which not only gives H.T. but keeps your accumulator fully charged.

## 3 SAVE TROUBLE

**NO MORE BATTERIES.** Connect the suitable EKCO Power Unit in place of the battery, plug into the electric light and switch on—that's all! No alterations to set, valves or wiring. Silent in operation; outstanding in performance.

*The latest EKCO Power Units are housed in attractive all-insulated bakelite cases. Size 9" x 5" x 3 3/8". Ask your dealer for literature or post coupon below!*

PRICES FROM  
**37'6**  
or by Easy Payments.

# EKCO

RADIO POWER UNITS

To: E. K. COLE, Ltd. (Dept. K.13) Ekco Works, Southend-on-Sea  
Please send me full details of Ekco Radio Power Units.

Name .....

Address .....