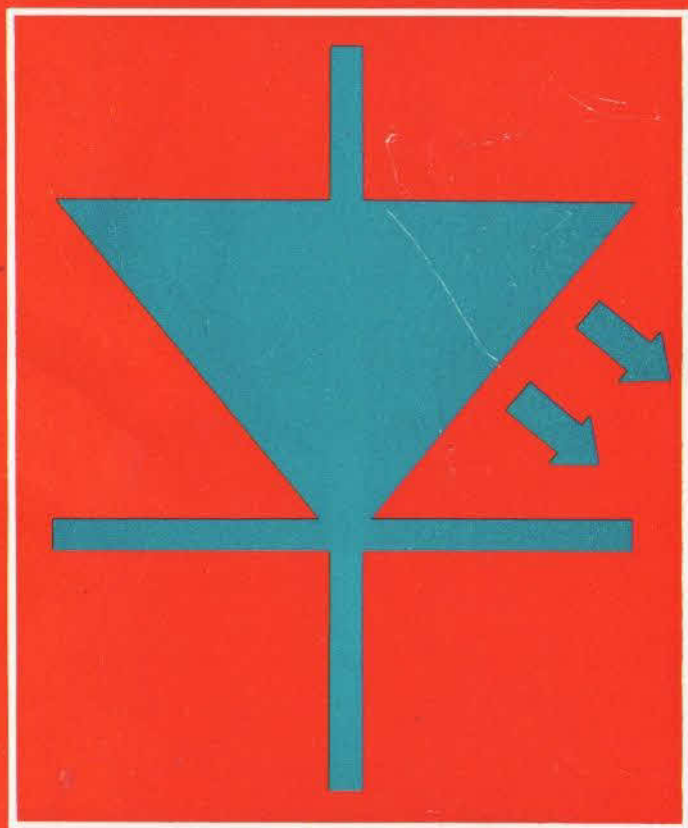


50 Simple L.E.D. Circuits Book 2

R. N. SOAR



Although every care has been taken with the preparation of this book, the publishers or author will not be held responsible in any way for any errors that might occur.

©1981 BERNARD BABANI (publishing) LTD

First Published -- June 1981

British Library Cataloguing in Publication Data

Soar, R.N.

50 simple L.E.D. circuits -- Book 2

1. Light emitting diodes -- Amateurs' manual

I. Title

621.3815'3043 TK9965

ISBN 0 85934 062 7

CONTENTS

Circuit No.		Page
1	LED Test Circuit	1
2	Diode Tester.	2
3	Improved Diode Tester.	5
4	"Heads or Tails" Circuit	5
5	Unijunction LED Flasher	5
6	Portable Television Battery Monitor	8
7	Car Voltage Probe	9
8	Logic Level "1" Detector	10
9	Improved Logic Probe	10
10	Opto Isolator	12
11	Low Voltage Stabiliser	13
12	Numbers Toy	14
13	SCR Tester.	15
14	NPN Transistor Tester	17
15	1½ Volt Cell Tester	18
16	Numeral "1" Display	19
17	Matching LEDs for Brilliance.	21
18	Using LEDs on AC.	22
19	The "2-LED" LED	23
20	"Magic Boxes"	23
21	3-Colour LED.	25
22	2/3 Colour LED	26
23	Super "Magic Boxes"	28
24	AND Gate	28
25	NAND Gate	29
26	OR Gate	30
27	Exclusive OR Gate.	31
28	NOR Gate	32
29	Rectifier Tester.	33
30	Simple Rectifier Test	34
31	Simple Changeover Circuit	35
32	2-Colour Changeover Circuit	36
33	ZN414 IC Supply	37
34	Simple "Snap" Indicator.	37
35	Stable 1mA Current Source.	40

Circuit No.		Page
36	Simple 3 Digit Display	40
37	Current Flow Indicator.	42
38	Improved "6" Display for CA 7-Segment Display . . .	44
39	Simple Ni-Cad Recharger	44
40	555 LED Flasher.	45
41	Flashing Seconds Display	45
42	Simple Signalling Device	48
43	Precision Voltage Reference	48
44	Fuse Tester	48
45	Simple Timer	51
46	Flourescent Indicator Device Filament Tester	52
47	Magnet Operated LED	54
48	Variable Capacitor Tester	54
49	LM3909 Flasher	56
50	LED "Line of Light"	57

INTRODUCTION

This book is the result of further experiments and tests carried out after the publication of my book No. BP42 "50 Simple LED Circuits" by Bernard Babani (publishing) Ltd. in 1977. As a result certain ideas have had to be modified.

It was stated in my first book that the longer lead of the LED is the cathode, this was the case with every LED tested. However, since the publication of that book, LEDs appeared which have the longer lead connected to the *Anode*, this is against the usual convention that the cathode of a diode is identified, but it seems that at least one major manufacturer produces LEDs with a longer anode lead.

This means that LEDs must always be checked for polarity before being soldered into circuit (see Circuit 1).

Red LEDs seem to be much more robust than green or yellow ones. Several of the original green LEDs used failed after several months for no apparent reason. LEDs can be destroyed by excessive current or a relatively low reverse voltage but the green LEDs failed in circuits where neither cause was possible. The reason for this sudden failure remains unknown. The lifetime of a LED is predicted as many years with a very gradual reduction in light output over the period. No red LED has failed in this way. LEDs can be used on low voltage A C but there is a possibility that the LED could be destroyed by the reverse voltage, a silicon rectifier should be connected to protect the LED, as described later.

Many of the circuits are shown as powered by 3 volt or 9 volt batteries, batteries are expensive, but at least this means that the circuits are perfectly safe for anyone to experiment with. However, one or two circuits are clearly marked as being not suitable for beginners.

ABBREVIATIONS USED

A	Anode
AC	Alternating Current
CA	Common Anode
CC	Common Cathode
DC	Direct Current
DPDT	Double Pole Double Throw Switch (Two circuit changeover switch)
G	Gate
K	Cathode
LED	Light Emitting Diode
SCR	Silicon Controlled Rectifier (Thyristor)
SPST	Single Pole Single Throw Switch (ON/OFF)

CIRCUIT 1

LED Test Circuit


This is a simple circuit to determine the polarity of a LED.

The longer lead of the LED should always be connected as shown. At switch position 1, if the LED glows the longer lead is the ANODE. At switch position 2, if the the LED glows the longer lead is the CATHODE. See Circuit 1.


If the LED does not glow in position 1 or 2 it is faulty but check carefully that the two LED leads are not touching and causing a short circuit.

If you are testing a large number of surplus or "bargain price" LED's you may get weird results. One Green LED was found which glowed brightly in one direction (anode positive) but also glowed dimly but distinctly in *reverse*. You might come across a LED which glows equally brightly in either

Circuit 1

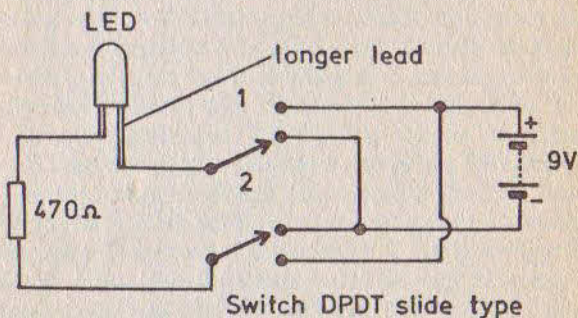

Circuit 1b

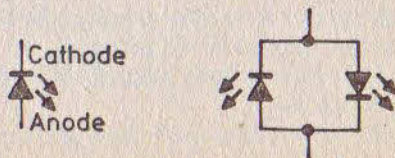

direction, this is a "twin" LED as shown in Circuit 1b, i.e. two LEDs connected in Inverse Parallel, or a LED which glows Red in one direction and Green in the other (see later Circuits).

The resistor value shown is 470Ω this makes the tester suitable for any colour LED, if Red LEDs only are tested the value can be $1k\Omega$ or $2.2k\Omega$ this will still give quite a bright glow but will reduce the current drawn from the battery.

The switch is a miniature D P D T slide type details of the several ways in which the D P D T slide switch can be used are given later.

CIRCUIT 2

Diode Tester

Power rectifiers can be tested easily with a LED and a 3 volt battery but signal diodes such as the 0A91 are intended to pass only a small current and might be damaged. This circuit uses a low current to test the diode, the test current is amplified by a transistor and the transistor turns the LED on. The test current through the diode is about 1mA. The transistor is a 2N697, this is a general purpose type available at low cost and is used in several other circuits in the book. Any transistor which is described as "similar to the 2N697" is perfectly suitable.

If the diode under test is connected as shown the LED will glow if the diode is functional. The diode should also be tested in the reverse direction and if the diode is functional the LED will not glow. A diode which is functional conducts in one direction, forward bias — anode positive, and does *not* conduct in the reverse direction, reverse bias — anode negative. If the diode conducts in both directions it is short circuit, if it conducts in neither direction it is open circuit. A short circuit or open circuit diode is useless.

If the diode appears to be open circuit make certain that it is actually connected into the circuit properly.

The cathode of a signal diode is usually indicated by a ring next to the cathode lead.

If you remove diodes from old broken radios you may find that the cathode end is coloured red.

Germanium signal diodes are numbered 0A91, 0A90,

0A81 etc. diodes of American or Japanese origin have type numbers 1N60 etc. For further details on signal diodes and their uses see Book No. BP36 50 Circuits using Germanium, Silicon and Zener Diodes, published by Bernard Babani (publishing) Ltd. Tr1 the 2N697 is functioning as a current amplifier.

Germanium diodes are not perfect rectifiers they do pass a small current in the reverse direction, this reverse current when amplified may be sufficient to cause the LED to glow very dimly, this does not mean that the diode is faulty it is quite normal.

Sometimes the anode and cathode of a diode are indicated as A and K.

