

THE No1 MONTHLY FOR THE ELECTRONICS & MUSIC HOBBYIST

# ELECTRONICS & MUSIC MAKER

PROJECTS, FEATURES, NEWS & REVIEWS  
IN ELECTRONICS & ELECTRO~MUSIC

JULY 1981  
65p

**ALPHADAC 16**  
MULTI-CONTROL OF  
MONO SYNTHESISERS  
FROM ONE KEYBOARD

**THE SYNWAVE  
SYNTHESISER**  
AN EXCITING PROJECT  
FOR CREATING SEA  
EFFECTS


**CAR DIGITAL PETROL  
GAUGE**  
NUMERICAL READOUT &  
WARNING INDICATION

PLUS

- \* EXCLUSIVE PPG WAVE 2  
SYNTHESISER REVIEW
- \* NASCOM 1 MICROMUSIC
- \* DUNCAN MACKAY FEATURE
- \* ATARI MUSIC COMPOSER



**TWO  
SPECIAL  
OFFERS!!**

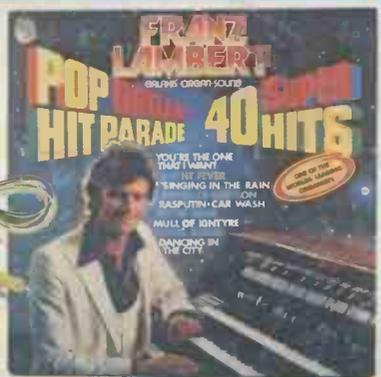

HOME \* WORKSHOP \* VEHICLE \* EDUCATION \* COMPUTING \* ELECTRO~MUSIC

## THE VIDEO GENIE SYSTEM

Ideal for small businesses, schools, colleges, homes, etc. Suitable for the experienced, inexperienced, hobbyist, teacher, etc.

EXTENDED GUARANTEE BY COMPCARE

16K  
£279  
+ VAT

● 16K user RAM plus extended 12K Microsoft BASIC in ROM ● Fully TRS-80 Level II software compatible ● Huge range of software already available ● Self contained, PSU, UHF modulator, and cassette ● Simply plugs into video monitor or UHF TV ● Full expansion to disks and printer ● Absolutely complete — just fit into mains plug.

EG3000 Series

WITH NEW EXTRA KEYS!

## YOUR ZX80 IS NOW NO LONGER REDUNDANT

EXTENDED GUARANTEE BY COMPCARE

Upgrade your ZX80 to the full animated graphics of the ZX81. (No screen flicker). For only £12.95 + VAT, in kit form. Works only in conjunction with new 8K ROM from Sinclair (not included).

## WE ARE NOW STOCKING THE AUTOSTART APPLE II AT REDUCED PRICES



EXTENDED GUARANTEE BY COMPCARE

16K £549  
32K £579  
48K £599  
+ VAT

**Getting Started** APPLE II is faster, smaller, and more powerful than its predecessors. And it's more fun to use too because of built-in features like:  
● BASIC — The Language that Makes Programming Fun.  
● High-Resolution Graphics (in a 54,000-Point Array) for Finely-Detailed Displays. ● Sound Capability that Brings Programs to Life. ● Hand Controls for Games and Other Human-Input Applications. ● Internal Memory Capacity of 48K Bytes of RAM, 12K Bytes of ROM; for Big-System Performance in a Small Package. ● Eight Accessory Expansion Slots to let the System Grow With Your Needs.  
You don't need to be an expert to enjoy APPLE II. It is a complete, ready-to-run computer. Just connect it to a video display and start using programs (or writing your own) the first day. You'll find that its tutorial manuals help you make it your own personal problem solver.

## INTRODUCING THE NEW & EXCITING TRS80 MODEL III



EXTENDED GUARANTEE BY COMPCARE

16K £559 + VAT    32K £589 + VAT    48K £619 + VAT

The Radio Shack TRS-80™ Model III is a ROM-based computer system consisting of:  
● A 12-inch screen to display results and other information  
● A 65-key console keyboard for inputting programs and data to the Computer  
● A Z-80 Microprocessor, the "brains" of the system  
● A Real-Time Clock  
● Read Only Memory (ROM) containing the Model III BASIC Language (fully compatible with most Model I BASIC programs)  
● Random Access Memory (RAM) for storage of programs and data while the Computer is on (amount is expandable from "16K" to "48K", optional extra)  
● A Cassette Interface for long-term storage of programs and data (requires a separate cassette recorder, optional/extra)  
● A Printer Interface for hard-copy output of programs and data (requires a separate line printer, optional/extra)  
● Expansion area for upgrading to a disk-based system (optional/extra)  
● Expansion area for an RS-232-C serial communications interface (optional/extra)  
All these components are contained in a single moulded case, and all are powered via one power cord.

EUROPE'S FASTEST SELLING ONE BOARD COMPUTER

# COMPUKIT UK101

★ 6502 based system — best value for money on the market. ★ Powerful 8K Basic — Fastest around ★ Full Qwerty Keyboard ★ 4K RAM Expandable to 8K on board. ★ Power supply and RF Modulator on board. ★ No Extras needed — Plug-in and go ★ Kansas City Tape Interface on board. ★ Free Sampler Tape including powerful Disassembler and Monitor with each Kit. ★ If you want to learn about Micros, but didn't know which machine to buy then this is the machine for you.



Build, Understand and Program your own Computer for only a small outlay.

NEW MONITOR IN ROM available separately £22 + VAT  
Revised BASIC 3 ROM — contains cure for GARBAGE collection routine — allows correct use of STRING ARRAYS. Suitable for CompuKit or Superboard £7.50 + VAT.

FOR THE COMPUKIT — Assembler Editor £14.90    Screen Editor Tape £1.90

GAME PACKS — 1). Four Games £5.00    2). Four Games £5.00    3). Three Games 8K only £5.00  
Super Space Invaders (8K) £6.50    Space Invaders £5.00    Chequers £3.00    Realtime Clock £3.00  
Case for CompuKit £29.50    40 pin Expansion Jumper Cable £8.50    All Prices exclusive VAT

NEW ISSUE COMPUKIT WITH ALL THE FEATURES THAT MADE IT THE MOST PROFESSIONAL COMPUTER KIT ON THE MARKET. Now WITH FREE NEW EXTENDED MONITOR (a saving of £22), which includes Flashing Cursor, Screen Editing, & Save Data on Tape.

KIT ONLY £149 + VAT

Fully Assembled — £199 + VAT

DEALER ENQUIRIES INVITED

4K Upgrade Kit  
£15.90 + VAT

## NEW REDUCED PRICES

16K £449 } VAT  
32K £499 }  
RRP £795 for 32K



**The PEDIGREE PETS** Very popular for home & business use 8K Microsoft Basic in ROM 8K Pet 32K & 16K with new improved keyboard. All with green screen  
Cassette Deck £55 extra    Full range of software available  
Interface PET IEEE — Centronics Parallel  
Decoded £77.00 + VAT


## SPECIAL SCOOP GET YOURSELF A NEW MX80 PRINTER AND SAVE A FORTUNE

only £299 + VAT

Interface Cards for Apple, Pet, TRS80, Nascom and CompuKit — RS232 Interface Cards not necessary for parallel. £49 + VAT  
Full TRS80/Genie Graphics including cables. Ready to go. **EX-STOCK.**



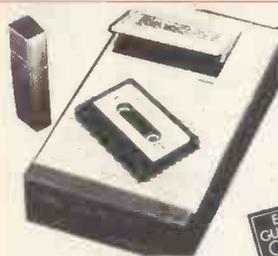Now Available Fiction Feed Option £49 + VAT



NOW AVAILABLE PANASONIC KX-T1520 AUTOMATIC ANSWERING SYSTEM £190 + VAT

## LOW COST TELEPHONE ANSWERING MACHINE

only £99.95 + VAT

Microprocessor controlled answering machine. Plug into your phone line. Records any phone call messages. Remote bleeper enables you to listen to your messages from anywhere in the world. Uses standard cassettes. Comes complete with mains adaptor, microphone, remote bleeper, base unit, cassette with 30 sample pre-recorded messages.

## HITACHI PROFESSIONAL MONITORS



9" — £129 £99.95  
12" — £199 £149

● Reliability Solid state circuitry using an IC and silicon transistors ensures high reliability. ● 500 lines horizontal resolution Horizontal resolution in excess of 500 lines is achieved in picture center. ● Stable picture Even played back pictures of VTR can be displayed without jittering. ● Looping video input Video input can be looped through with built-in termination switch. ● External sync operation (available as option for U and C types) ● Compact construction Two monitors are mountable side by side in a standard 19-inch rack.

## TEAC DISK DRIVES



EXTENDED GUARANTEE BY COMPCARE

● TEAC FD-50A has 40 tracks giving 125K Bytes unformatted single density capacity.  
● The FD-50A can be used in double density recording mode.  
● The FD-50A is Shugart SA400 interface compatible.  
● Directly compatible with Tandy TRS80 expansion interface.  
● Also interfaces with Video Genie, SWTP, TRS80, North Star Horizon, Superbrain, Nascom, etc. etc.  
● Address selection for Daisy chaining up to 4 Disks.  
● Disks plus power supply housed in an attractive grey case.

40 TRACK Single Disk Drive £225 + VAT    Double Disk Drive £389 + VAT

77 TRACK Single Disk Drive £299 + VAT    Double Disk Drive £499 + VAT



SHARP PC1211 £79.90 + VAT

COMPUTER POWER THAT ONCE FILLED A ROOM CAN NOW BE CARRIED IN YOUR POCKET!  
● Programs in BASIC ● "QWERTY" Alphabetical Keyboard ● 1.9K Random Access Memory ● Long Battery Life.



"Europe's Largest Discount Personal Computer Stores"

Delivery is added at cost. Please make cheques and postal orders payable to **COMP SHOP LTD.**, or phone your order quoting **BARCLAYCARD, ACCESS, DINERS CLUB** or **AMERICAN EXPRESS** number.

### MAIL ORDER AND SHOP:

14 Station Road, New Barnet, Hertfordshire, EN5 1QW (Close to New Barnet BR Station — Moorgate Line).  
Telephone: 01-441 2922 (Sales) 01-449 6596    Telex: 298755 TELCOM G

**OPEN (BARNET) — 10am - 7pm — Monday to Saturday**

### NEW WEST END SHOWROOM:

311 Edgware Road, London W2. Telephone: 01-262 0387  
**OPEN (LONDON) — 10am - 6pm — Monday to Saturday**


★ IRELAND: 80 Marlborough Street, Dublin 1. Telephone: Dublin 749933

★ COMP SHOP USA, 1348 East Edinger, Santa Ana, California, Zip Code 92705.  
Telephone: 0101 714 5472526

CREDIT FACILITIES ARRANGED — send S.A.E. for application form.

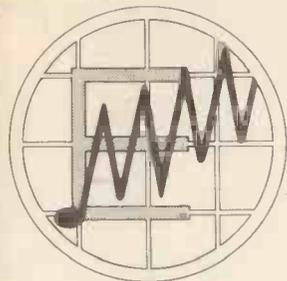TELEPHONE SALES  
OPEN 24 hrs. 7 days a week  
01-449 6596





# ELECTRONICS & MUSIC MAKER

July 1981

100 Pages for the Electronics and Music Hobbyist!

**Editor**

Mike Beecher

**Art Editor**

Peter Blackmore

**Production Manager**

Brian Searle

**Editorial Secretary**

Sue Forster

**Technical Illustrators**

John Dudley

David Stacey

Roy Smith

**Photography**

Ian James

**Consultants**

**Projects**

Robert Penfold

**Circuit Design**

Chris Lare

**Electro-Music**

Vince S. Hill

David Ellis

**Microprocessors**

Peter Kershaw

**Music Synthesis**

Tim Souster

**Studio Recording**

Mark Andrews

**Education**

Steve Leverett

**Hi-Fi**

Jeff Macaulay

**TV & Video**

Andy Emmerson

**Stage Equipment**

Ben Duncan

**Organ Electronics**

Ken Lenton-Smith

**Guitar Electronics**

Adrian Legg

**Percussion Electronics**

Warren Cann

**Electronics News**

Mark Space

**Book Reviews**

Nigel Fawcett

**Microcomputers**

Graham Knight

**Software**

Graham Daubney

**Course Writers**

Norman Butler

Graham Hall

**Technical Lab**

Bob Kirsch

Dave Goodman

**Studio Technician**

Glenn Rogers

**Editorial Offices**

282 London Road  
Westcliff-on-Sea  
Essex SS0 7JG  
Tel: (0702) 338878

**Advertisement Manager**

Terry Day

**Classified Manager**

Dennis Hill

**Advertisement Offices**

Electronics & Music Maker  
Hillcroft House  
16 The Avenue  
Highams Park  
London E4 9LD  
Tel: 01-527 3376

**Published by**

Maplin Publications  
282 London Road  
Westcliff-on-Sea  
Essex SS0 7JG  
Tel: (0702) 338878

**Distributed by**

Cemas Limited  
24 Bridge Street  
St Ives  
Huntingdon  
Cambridgeshire PE17 4EG  
Tel: (0480) 63942

**Printed by**

Eden Fisher (Southend) Limited

**Typeset by**

Quillset Typesetting

**Subscriptions**

Rates for 12 issues:  
UK & Overseas Surface: £9.90  
Europe: £11.64  
Airmail: £25.20

**Special Offers (Overseas)**

LP — extra 56p on price  
Cassette — extra 19p on price

**Copyright**

All material is subject to world wide Copyright protection, and reproduction or imitation in whole or part is expressly forbidden. All reasonable care is taken to ensure accuracy in preparation of the magazine but Maplin Publications cannot be held legally responsible for its contents. Where errors occur corrections will be published as soon as possible afterwards. All prices and data contained in advertisements are as ascertained to be correct at the time of going to press. Permission to reproduce printed circuit board layouts commercially or marketing of kits must be sought from the Publisher.  
© Copyright 1981 Maplin Publications.

## CONTENTS

### ELECTRONICS

	Page
Alphadac 16 Synthesiser Controller .....	8
Synwave Percussion/Trigger Effects Unit .....	20
Starting Point .....	<i>Robert Penfold</i> 25
Car Cassette Power Supply .....	26
Matinée Organ Part 5 .....	30
Circuit Maker .....	40
Car Digital Petrol Gauge .....	<i>Michael Kennedy</i> 43

### COMPUTING

Micromusic: Notate your Nascom ....	<i>Don Finlay</i> 46
Atari Music Composer Cartridge .....	48
Basically Basic .....	<i>Graham Hall</i> 52
Using Microprocessors .....	<i>Peter Kershaw</i> 54

### ELECTRO-MUSIC

Hot-Wiring your Guitar .....	<i>Adrian Legg</i> 57
Duncan Mackay: Going Solo .....	58
PPG Wave 2 Synthesiser Review .....	62
Electronic Music Techniques .....	<i>Lawrence Casserley</i> 66
Sound on Stage .....	<i>Ben Duncan</i> 68
Working with Video .....	<i>Andy Emmerson</i> 70
Wersi Pianostar Review .....	72
Organ Talk .....	<i>Ken Lenton-smith</i> 74
Hi-Fi .....	<i>Jeff Macaulay</i> 76
Advanced Music Synthesis .....	<i>Dave Bristow</i> 78

### NEWS

America .....	<i>Ian Waugh</i> 80
Record Review: Kraftwerk .....	82
Book Reviews .....	84
Industry Profile: Wersi Electronics .....	86
New Products .....	90
Events .....	92
Special Offers .....	92
E&MM Subscriptions .....	6
Next Month .....	94
E&MM Cassettes .....	94
Classified .....	95
E&MM T-Shirts .....	96
Advertisers Index .....	96

## ETI VOCODER



COMPLETE KIT ONLY £195 + VAT!

Features as a construction article in Electronics Today International this design enables a vocoder of great versatility and high intelligibility to be built for an amazingly low price. 14 channels are used to achieve its high intelligibility, each channel having its own level control. There are two input amplifiers, one for speech either from microphone or a high level source e.g. mixer or cassette deck and one for external excitation (the substitution signal) from either high or low level sources. Each amplifier has its own level control and a rather special type of tone control giving varying degrees of bass boost with treble cut or treble boost with bass cut. The level of the speech and excitation signals are monitored by LED PPM meters with 10 lights - 7 green and 3 red which indicate the level at 3dB steps. There are three internal sources of excitation - a noise generator and two pulse generators of variable frequency and pulse width. Any of the internal sources and the external source can be mixed together. There is a voiced/unvoiced detector which substitutes noise for the excitation signal at the points in speech where the vocal chord derived sounds of the speaker are substituted for by the unvoiced sounds of sibilants, etc. There is a slow rate control which smooths out the changes in spectral balance and amplitude enabling a change of the speech into singing or chanting and other special effects. A foot switch is provided to permit a complete freeze in spectral balance and amplitude whenever required. An LED on this indicates when the freeze is in operation.

An output mixer allows mixing of the speech, external excitation and vocoder output. The majority of the components fit into the large analysis/synthesis board with the rest on 8 much smaller boards with the controls and sockets mounted on them for ease of construction. Connectors are used for the small amount of wiring between the boards.

The kit includes fully finished metalwork, professional quality components (all resistors 2% metal oxide), nuts, bolts, etc - even a 13A plug!

## TRANSCENDENT 2000 SINGLE BOARD

Designed by consultant Tim Orr (formerly synthesiser designer for EMS Ltd.) and featured as a constructional article in ETI, this live performance synthesiser is a 3 octave instrument transposable 2 octaves up or down giving sweep control, a noise generator and an ADSR envelope shaper. There is also a slow oscillator, a new pitch detector, ADSR repeat, sample and hold, and special circuitry with precision components to ensure tuning stability amongst its many features.

The kit includes fully finished metalwork, fully assembled solid teak cabinet, filter sweep pedal, professional quality components (all resistors either 2% metal oxide or ½% metal film), and it really is complete - right down to the last nut and bolt and last piece of wire! There is even a 13A plug in the kit - you need buy absolutely no more parts before plugging in and making great music! Virtually all the components are on the one professional quality fibreglass PCB printed with component locations. All the controls mount directly on the main board, all connections to the board are made with connector plugs and construction is so simple it can be built in a few evenings by almost anyone capable of neat soldering! When finished you will possess a synthesiser comparable in performance and quality with ready-built units selling for many times the price.

Comprehensive handbook supplied with all complete kits! This fully describes construction and tells you how to set up your synthesiser with nothing more elaborate than a multi-meter and a pair of ears!

COMPLETE KIT ONLY £168.50 + VAT!



Cabinet size 24.6" x

## CHROMATHEQUE 5000 5 CHANNEL LIGHTING

This versatile system featured as a constructional article in ELECTRONICS TODAY INTERNATIONAL has 5 frequency channels with individual level controls on each channel. Control of the lights is comprehensive to say the least. You can run the unit as a straightforward sound-to-light or have it strobe all the lights at a speed dependent upon music level or front panel control or use the internal digital circuitry which produces some superb random and sequencing effects. Each channel handles up to 500W and as the kit is a single board design wiring is minimal and construction very straightforward. Kit includes fully finished metalwork, fibreglass PCB controls, wire etc. - Complete right down to the last nut and bolt!



### MANY MORE KITS AND ORDERING INFORMATION ON PAGE 42

All projects on this page can be purchased as separate packs, e.g. PCBs, components sets, hardware sets, etc. See our free catalogue for full details and prices.

## POWERTRAN ELECTRONICS

PORTWAY INDUSTRIAL ESTATE  
ANDOVER, HANTS SP10 3WW

ANDOVER  
(STD 0264) 64455

# POWER

## DJ90 STEREO MIXER as being featured in Electronics Today International - July issue!

COMPLETE KIT ONLY £97.50 + VAT!

This versatile new mixer, shown fitted to our console, has 2 stereo inputs for magnetic cartridges, a stereo auxiliary (e.g. cassette or jingle machine) input and a microphone input. The decks can be automatically panned either fast or slow and all 3 music inputs can be mixed with slider controls. There is a 5-section graphics equaliser and a beat-lift control. Also there is a voice-over unit (ducking) and an override button for interrupt announcements. The microphone input can be modulated at a variable rate to produce 'growl' effects and there is monitoring of any music input (pre-fade listen) via the stereo headphone socket and a pair of LED PPMs. The kit includes fully finished metalwork fibreglass, PCBs, controls, wire etc. - complete down to the last nut and bolt! The console is shown fitted with two 19" panel units - a Chromatheque 5000 lighting controller and an SP2-200 stereo 100W/channel power amplifier. For a 200W/channel system two SP2-200s could be fitted.

Power supply for mixer with screening metal box £9.90+VAT. Console complete with switch panel, lid feet and carrying handles £69.50+VAT. BSR P256 - their latest belt-drive disco turntable £29.90+VAT.



# POWERTRAN

**SP2-200 2-CHANNEL 100 WATT AMPLIFIER** COMPLETE KIT ONLY £64.90 + VAT!



The power amplifier section of the MPA 200 has proved not only very economical but very rugged and reliable too. This new design uses 2 of these amplifier sections powered by separate power supplies fed from a common toroidal transformer. Input sensitivity is 775mV. Power output is 100 rms into 8 ohm from both channels simultaneously. The kit includes fully finished metalwork, fibreglass PCBs, controls, wire, etc. - complete down to the last nut and bolt!

## TRANSCENDENT 2000 MULTI VOICE SYNTHESIZER COMPLETE KIT



Cabinet size 36.3" x

## SYNTHESISER



15.7" x 4.8" (rear) 3.4" (front)

## 1024 COMPOSER



COMPLETE KIT ONLY £89.50 + VAT!

Programmed from a synthesiser, our latest design to be featured in Electronics Today International, the 1024 COMPOSER controls the synth. with a sequence of up to 1024 notes or a large number of shorter sequences e.g. 64 of 16 notes all with programmable note length. In addition a rest or series of rests can be entered. It is mains powered but an automatically trickle charged Nickel-Cadmium battery, supplying the memory, preserves the program after switch off. The kit includes fully finished metalwork, fibreglass PCB, controls, wire etc. - complete down to the last nut and bolt!

# POWERTRAN

## EFFECTS SYSTEM COMPLETE KIT ONLY £49.50 + VAT!



## BLACK HOLE CHORALIZER COMPLETE KIT ONLY £49.80 + VAT! (single delay line system)



De Luxe version (dual delay line system) also available for £59.80 + VAT

Cabinet size 10.0" x 8.5" x 2.5" (rear) 1.8" (front)

The BLACK HOLE designed by Tim Orr, is a powerful new musical effects device for processing both natural and electronic instruments, offering genuine VIBRATO (pitch modulation) and a CHORUS mode which gives a "spacey" feel to the sound achieved by delaying the input signal and mixing it back with the original. Notches (HOLES), introduced in the frequency response, move up and down as the time delay is modulated by the chorus sweep generator. An optional double chorus mode allows exciting antiphase effects to be added. The device is floor standing with foot switch controls, LED effect selection indicators, has variable sensitivity, has high signal/noise ratio obtained by an audio compander and is mains powered — no batteries to change! Like all our kits everything is provided including a highly superior, rugged steel, beautifully finished enclosure.

# POWERTRAN

## 200 100 WATT (rms into 8 ohm) MIXER/AMPLIFIER

COMPLETE KIT ONLY £49.90 + VAT!



Featured as a constructional article in ETI, the MPA 200 is an exceptionally low priced — but professionally finished — general purpose high power amplifier. It features an adaptable input mixer which accepts a wide range of sources such as a microphone, guitar, etc. There are wide range tone controls and a master volume control. Mechanically the MPA 200 is simplicity itself with minimal wiring needed making construction very straightforward.

The kit includes fully finished metalwork, fibreglass PCBs, controls, wire, etc. — complete down to the last nut and bolt.

## TRANSCENDENT DPX DIGITAL SYNTHESISER COMPLETE KIT ONLY £299 + VAT



5.0" x 5.0" (rear) 3.3" (front)

The Transcendent DPX is a really versatile 5 octave keyboard instrument. There are two audio outputs which can be used simultaneously. On the first there is a beautiful harpsichord or reed sound — fully polyphonic, i.e. you can play chords with as many notes as you like. On the second output there is a wide range of different voices, still fully polyphonic. It can be a straightforward piano as a honky tonk piano or even a mixture of the two! Alternatively you can play strings over the whole range of the keyboard or brass over the whole range of the keyboard or should you prefer — strings on the top of the keyboard and brass as the lower end (the keyboard is electronically split after the first two octaves) or vice-versa or even a combination of strings and brass sounds simultaneously. And on all voices you can switch in circuitry to make the keyboard touch sensitive! The harder you press down a key the louder it sounds — just like an acoustic piano. The digitally controlled multiplexed system makes practical touch sensitivity with the complex dynamics law necessary for a high degree of realism. There is a master volume and tone control, a separate control for the brass sounds and also a vibrato circuit with variable depth control together with a variable delay control so that the vibrator comes in only after waiting a short time after the note is struck for even more realistic string sounds.

To add interest to the sounds and make them more natural there is a chorus/ensemble unit which is a complex phasing system using CCD (charge coupled device) analogue delay lines. The overall effect of this is similar to that of several acoustic instruments playing the same piece of music. The ensemble circuitry can be switched in with either strong or mid effects. As the system is based on digital circuitry data can be easily taken to and from a computer (for storing and playing back accompaniments with or without pitch or key change, computer composing, etc., etc.).

Although the DPX is an advanced design using a very large amount of circuitry, much of it very sophisticated, the kit is mechanically extremely simple with excellent access to all the circuit boards which interconnect with multiway connectors, just four of which are removed to separate the keyboard circuitry and the panel circuitry from the main circuitry in the cabinet.

The kit includes fully finished metalwork, solid teak cabinet, professional quality components (all resistors 2% metal oxide), nuts, bolts, etc., even a 13A plug!

Plugs to 24 tracks, we

# TEAC Portastudio M-144




At last, affordable multitrack for every musician. TEAC's new Portastudio combines a mixer and multitrack tape recorder in one compact unit. The solenoid, cassette transport runs at twice normal speed and with the built in Dolby system produces remarkable sound fidelity. Precision heads enable four tracks to be recorded with full sel-sync and ping-pong facility. The mixer section accepts any signal with bass, treble, echo send and pan on each channel. These are switched from laying tracks to performing mixdown. The simplified monitoring allows you to listen to the mix you are recording, plus the tracks already on tape. Use the powerful internal headphone amplifier or an external speaker/amp system. Track bouncing, signal processing, memory rewind and varispeed are more facilities that put this remarkable unit on par with what you will get from systems costing many times the price. Just plug in a microphone and a pair of cans and you have your own four track demo setup. You make the music, Portastudio does the rest. Full details on request.

**£539**

£579 including mike and cans

specialise in professional audio equipment from major manufacturers. Call us with your system requirements. Our business is helping you with yours.

## Comp-Cards

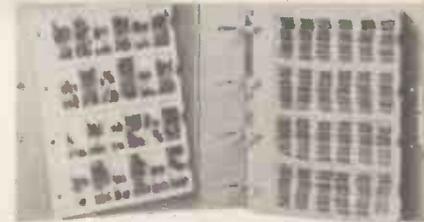

FILE **£6.50** TRAY **£1.20**

A new concept in neat and efficient parts storage. File your small components in these vacuum formed trays, each with 24 compartments, with see through, snap-on lids. The modified ring binder takes up to 7 cards - that's 168 orderly locations in the size of a book. Ideal for servicing, constructors and research work.




## Accessit

A unique range of add-on signal processors for PA or studio use. As reviewed in this magazine.

- Compressor **£31.97** Variable threshold and speed give scope for effects
- Parametric **£31.97** Low and high band, tunable equaliser design
- Booster **£33.12** Four way line amplifier solves all matching problems
- Companer **£34.27** Up to 30dB of noise reduction for semi-pro recorders
- Reverb **£33.12** Custom spring and variable EQ ensure a natural sound
- Power Supply **£28.52** Mains operated, will power up to four Accessit units
- RacKit **£19.55** Mounts three Accessit units to standard 19in rack


Send for the new data folder including specification cards, application notes, review reprints and details of the 21 day free trial offer.

## £35.95 Microchip Orchestra

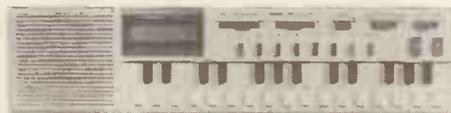

The revolutionary musical instrument that turns you into an instant musician. Order the Casio VL-Tone now, and try it out at no obligation for 14 days.

## Books

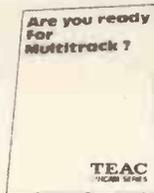

"Are you ready for Multitrack?" explains recording techniques from sound on sound through to eight track, with many pages about the equipment to use.

**60p**


## "The Multitrack Primer"

from TEAC is a practical guide to setting up a home studio with many tips on wiring, acoustics, mike placement etc. The book is packed with superb illustrations. The best guide around by far.

**£3.50**


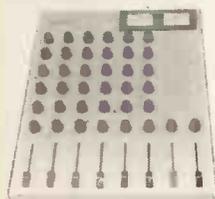
## SECK £108.33 Professional Mixer in Kit Form



£152.25 ASSEMBLED

A six input stereo mixer featuring wide range gain, treble, bass, echo, foldback and pan on each channel. For compact PA, keyboards, stage monitoring or recording, the ultra slim design is at home anywhere.



All prices shown are inclusive of postage and VAT. You can order by phone using Visa or Access Cards, or drop in and see us! Export enquiries welcome.

Please send me a free copy of your 32-page catalogue.


Name \_\_\_\_\_

Address \_\_\_\_\_

E&MM/7

turnkey

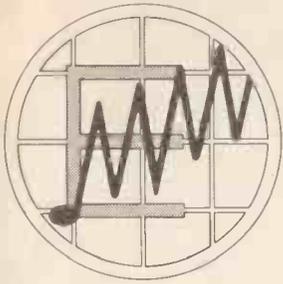8 East Barnet Road, New Barnet, Herts EN4 8RW Tel: 01-440 9221



# ELECTRONICS & MUSIC MAKER

## Monophonic Goes Polyphonic!

by Mike Beecher, Editor  
Electronics & Music Maker.



panies had ensured their products would be able to interface with other instruments through the provision of control voltage and trigger inputs and

outputs. Unfortunately, one main difference in this interfacing came with Yamaha and Korg (also EMS), who did not choose, for good reasons, the one volt per octave relationship for CVs and also used differing trigger thresholds. This can be overcome, however, by using linear and logarithmic converters, so the possibility of linking up mono synthesisers of all kinds has existed for some time.

Now we can offer a very cheap way of producing sophisticated polyphonic music through our Alphadac 16 project. An enormous number of control possibilities come from its microprocessor and EPROM and it points to the direction that new musical instruments are taking, from the

Casio VL-Tone to the PPG Wave 2 and the Yamaha GS-1.

The electronic drum machine can now be micro-controlled and even the new guitar synthesisers from Roland employ the concept that polyphonic outputs are another step forward.

Joining this polyphonic band come the home computers that have a strong selling potential simply from their music-making qualities.

The Atari 400 and 800 are the latest home computer additions and offer four-part polyphony from a plug-in cartridge.

Now, perhaps we have (besides electronic project construction!) a different theme for the TV, video and computer in our home — Let's Make Music!

## Readers Letters

Dear Editor,  
I really liked reading your first issue of Electronics & Music Maker and found it one of the best magazines on the market. I really wish that in one of your future issues you will include a circuit of a colour analyser which is used in colour photographic printing. I am sure many readers would be interested to build one.

I. Calleja  
Ta'Xbiez, Malta

What do other readers think?

Dear Sirs,  
Having just finished the first, excellent, issue of E&MM, I'd like to seek some advice from the experts — you!  
I'm thinking of starting a synth-based band along the lines of G. Numan, John Foxx, New Musik, and I'd like advice on which synth to go for.  
Money is a big problem — something in the range up to £200 would be ideal. Any ideas?

David Daniells  
Chesterfield, Derby

*play; but if you only want to be able to play relatively simple lead lines, and produce a wide range of sounds, then this may be just right for you. The WASP would suit the Gary Numan, John Foxx school of synthesists, but wouldn't be too good for the Wakemans, Emersons and Moraz's of this world. Incidentally, EDP, the manufacturers of the WASP have recently introduced a proper keyboard version.*

*Next up, you could try getting hold of an ARP Axse, or a Kitten (made by Octave Electronics), these are very similar instruments, and fall within your price bracket (if you shop around, or go for second hand), but they are only single oscillator instruments, and consequently are not so versatile. If I were in your position I would definitely go for a Moog Prodigy, which sells for under £250.00. This really is a monophonic synthesiser with a good history behind it (I understand that it recently became the world's best selling synthesiser ever), and the more recent versions of the Prodigy have control voltage and gate interface sockets on the rear panel, thus enabling the system to be expanded at a later date. The only drawback of the Prodigy is its lack of a noise generator for making 'natural' and percussive effects.*

*If you really want to sound like Gary Numan/New Musik for £200 then I would suggest a second WASP at £80, and a phase tone MT 30 for around £80, and a phase or chorus pedal. The Casiotone can then be used to give a synth string sound, and the monophonic for the lead lines; but if you are hoping to make a long term investment, then the Prodigy is a better bet, and you can get a string machine or a poly synth later.*

Dave Crombie

Dear Editor,

I require a mono play and recording and bias circuit for a reel-to-reel deck taken from a (fairly) ancient HMV 2206. The heads are in good condition, so are the mechanics but the valves are, unfortunately, dead. I intend to use it for effects as detailed in your fabulous magazine, so I only need reasonable quality since I'm not going to use it for music recordings etc. Thanks.

J. R. Walker  
Norwich, Norfolk

Any ideas?

Dear Sir,

I would appreciate it if you would answer the following questions: How can I adapt the circuit of the Workshop Power Supply unit in the April issue of E&MM, to enable the unit to give out 0-24 volts at up to 5 amps. Secondly, what changes need to be made to component values? Also could you detail what the new setting up procedure would be?

Finally, can I use the same meter, or do I need to use one with a lower internal resistance?

K. L. Hall, Liverpool

*It is not possible for the circuit to handle 5 amps at 25 volts in its present form, because TR1's power rating would be exceeded under short-circuit conditions. The only way to correct this would involve the use of two transistors in parallel (with emitter resistors) which would preclude the use of the Maplin PCB. If this is done D1 to D4, FS3, T1 should be updated to 5A types, and R1 changed to 0R1 (use two 0R22 3W*

*wirewound in parallel).*

*The setting-up procedure is not affected, except that the maximum current should be set at 5 amps. The same meter may be used, but it must of course be scaled to read up to 5 amps, not 2.5.*

*A more practical solution would be to build two power supplies! This would enable you to set up split rail supplies, in addition to the application you have in mind.*

Dear Editor,

Thank you for a most interesting magazine which I have read from the start. I have a particular interest in the Matinee Organ, for which I have already placed an order and I am looking forward with great anticipation to receiving the kit. With regard to your Vero Board Project 2, this looks good for an audio probe, but I have noticed that there is no connection between Pin 1 of IC1 and C5 and I would suggest that there should be 4 link wires and not 3 as is quoted in your text. I also note that in the photograph there is an LED shown — what for pray?

D. S. Upton  
Powys, Mid-Wales

*Yes, it would appear that you are correct and there is a link wire missing from the Vero Project 2 board. This should be added between D-12 and F-12 on the Veroboard, although as C5 is only needed as a precaution against instability, the unit may well function properly without this wire. The mysterious LED visible in the heading photograph is due to the fact that the 'Metronome' and 'Test Amplifier' photographs were accidentally transposed.*

Dear Sir,  
Please could you inform me what keyboards Stevie Wonder uses and their approximate prices. Also I soon hope to be starting a two-piece soul group and would like some advice on what keyboard/synthesizer to purchase.  
I'm writing this letter after picking up your mag by chance and I can tell you now you've just picked up a regular reader. Thanking you in advance.

Paul Williams  
London E3

After a great deal of research we've managed to track down a list of Stevie Wonder's keyboards, the ones he used on his last tour. Approximate prices are in brackets. Yamaha CS 80 (£3,500), Fairlight CM1 (£13,000), Steinway 7' grand piano, Hohner D6 Clavinet (£400), Fender Rhodes Suitcase 73 (£1,000). He has a host of other instruments dotted around his American homes including a Yamaha CX-1, which used to cost a staggering £50,000.

With regard to your enquiry as to which keyboards/synthesizers you should buy, we hope to be doing a special feature in a forthcoming issue dealing specifically with this subject, so keep your eyes peeled.

The Roland JP8 should be on sale at the end of May for around £2,500, though prices haven't as yet been fixed due to fluctuations in the exchange rates.

Dave Crombie

Dear Editor,  
Having just received my third issue of E&MM I, like so many others, must congratulate you on a superb magazine, designed for the every-day enthusiast for whom electronics has been a realm of wonder in the past.  
However, I feel it is my duty to request that you ensure total safety to your ama-

teur constructors who will undoubtedly build many of your projects.

From experience I have found that the amateur builder will also be the person who will want to construct for as little cost as possible. With this in mind I would like to draw your attention to Figure 12 of May issue Page 24. The wiring to the mains fuse is such that, should an unshielded fuse carrier be used, with mains switched on at the unit it is possible to be in contact with the supply before the fuse link has been fully inserted. The fuse connections should be reversed.

As the production manager for an electronics company I have to be very aware of the fact that the general public do not always switch off units before checking fuses.

R. D. Baker  
Weston Super Mare, Avon

Your comments with regard to the safety aspect of mains powered equipment are noted and Maplin Electronic Supplies are taking appropriate action to correct the error.

Dear Sirs,

You have certainly set a very high standard and maintenance of this, which I am certain, will ensure a long and successful life for this new publication.

It occurs to me that you may have some sort of advisory service.

I am trying to get information on a Compton Melotone organ which I have recently acquired. This appears to be a 'vintage' instrument and is of the electrostatic tone wheel sound generation type. I assume that the instrument is no longer in production and if I could obtain the circuit diagrams and any other technical information it would assist me in the renovation of the instrument. I have attempted to contact Compton but they appear to have moved from their original premises

and have amalgamated into Compton Mirfield.

P. Davies  
Kirton Lindsey, Lincolnshire

We were fortunate in enlisting the help of Mr. W.F., one of the parents of the electrostatic organ. He started work in 1928 with Leslie Bourn, inventor of the Compton Melotone, and was his assistant for many years. Mr. Davies received a circuit diagram and helpful letter from W.F. which should enable him to renovate the Melotone.

J. & J. Makins of Rochdale bought the Compton Company from the Official Receiver and continued to make electrostatic organs until turning to other methods some six months ago.

Dear Sir,

Let me start off by congratulating you on a superb new magazine that brings my two main hobbies together under one cover.

Yes, you have probably guessed, I have a problem, one that has oft caused me sleepless nights, one I hope you will be able to help me with, or at least point me in the right direction. Let me explain.

I have a Commodore Pet computer, which I can get to play four part music. Four part harmony can be very limiting, so without changing my whole system, I can think of only one way of increasing the number of ports. By recording four ports on to one track of a reel-to-reel, and then recording additional ports on to another track. My problem is 'sync'. How can I record on to the second track at exactly the right place, so that when replaying both tracks together they sound right?

I would be most grateful if you could either help me or put me in touch with someone who could.

I look forward to all subsequent issues of E&MM.

Thanking you in sleepless anticipation,  
B. N. Bidgood  
London

Synchronization isn't possible unless you're going from one tape recorder to another with a sync track recorded on a non-music track. I'd suggest that you investigate the Micro Technology Unlimited Instrument Synthesis Software Package (obtainable for £30 plus VAT from IJJ Design Ltd, 37 London Road, Marlborough, Wilts SN8 2AA), which, with two D/A boards, will offer stereo synthesis, the 'voices' being distributed between the left and right channels. E&MM will be reviewing this shortly if you'd care to wait before committing yourself!  
Dr David Ellis

Dear Sir,

Being a musician and a computer enthusiast at the same time, I'm looking for a device rather like the add-on device for the Casio FX 501-502P. That is, a device that when attached to a micro (ZX-81) produces a monophonic instrument, when given the frequency. Is it possible to hand that over to one of your experts in hope of some design rising to the surface?

D. Parvaz  
Henley-on-Thames

Here's an idea for someone to take up — we'll publish the first suitable design submitted.

Dear Sir,

I thought I would just write a short note regarding your new magazine.

Last September my wife and I decided to take up organ playing (from scratch). We bought a fairly cheap model in case we tired of it. Now we have taken it seriously we would like to up role the organ. Your D-I-Y organ seems to fill the bill admirably. In fact, I enjoy the whole magazine. Good luck with it.

R. A. Clarke  
Melton Mowbray, Leics

Dear Editor,  
Having seen the first few issues of E&MM I must say that the magazine is superb. I am eagerly awaiting publication of Alpha-dac 16. I would like to offer a few suggestions of future issue content.

(1) An interview/equipment review on Tangerine Dream — surely the most important and impressive live performance totally electronic progressive band of the decade.

(2) A feature reviewing amateurs own electronic studios — perhaps with photographs.

(3) One of the major problems with home built synthesis equipment is insurance — the finished product would be extremely expensive to replace with commercially made equipment if stolen and insurance companies require written valuations when dealing with equipment worth over £200 to £300. Would it be possible to produce an official E&MM equipment valuation as a service?

W. J. Philips  
Solihull, W. Midlands

Our interviews over the year will certainly try to cover interesting groups or composers who make a valuable contribution to electronic music and from the onset we have welcomed possible features on 'unknown' musicians who have a good studio set-up.

Insuring musical equipment, especially custom-built items, can be expensive and is best left to specialist insurance agencies. Try Entertainment & Leisure (Insurance) Services, PO Box 64, Harrogate, North Yorks, HG2 9ND.

Dear Sir,

I want to commend you on your wonderful magazine. As a student of music in the '30's in Paris I met some of the pioneers of electronic music and became interested in the aspects of 'aperiodic' sounds. When I returned to London in 1935, with some 'radio fiends', we would get some old TRF sets and overload the speakers, producing 'motor boating'. Along with some Theremin type instruments we would produce some very variable sounds. I would add that the results were far more interesting than 'Mr X'. In order to attract musicians to embrace electronic instruments, we will need something more than a singular, monophonic score. Even the old percussion, acoustical efforts of the West African drummers with a trio of kalingas produced a bigger variety of sound, and the kalingas certainly produced a larger 'melodic' effort, one part even producing hyper-phygian melodic structures. Certainly in the case of folk music we expect diatonic form plus primary chords, but this is 1981, not very far off from the 21st century!

I. J. Gordon  
London

Dear All at E&MM,

Without exaggeration, your new magazine is causing me great problems, for since the first issue work here seems to have come to a standstill, the fact of the matter is that once picked up, no one can put it down, and that includes myself. Congratulations, it's a winner.

The Sound Revival Centre  
Corsham, Wilts

Dear Sir,

The first four copies of E&MM have been superb, keep up the good work. I have built the Syntom and it has some quite amazing sounds.

I would like to see a project for an AC adaptor with three 9 volt outlets or perhaps one 18 volt outlet as well. This would be useful for controlling three or four effects pedals.

K. Wild  
Birmingham

The idea of a battery eliminator for effects pedals has arisen before, but we feel that the extra wiring from power source to effect may cause problems in a 'live performance' environment. However, as we plan several more percussion/trigger effects boxes, a suitable design may be forthcoming.

# SUBSCRIBE!

to ELECTRONICS & MUSIC MAKER —  
the No.1 Monthly for the Electronics and  
Music Hobbyist

For 12 issues:

UK and overseas surface .....£9.90

Europe .....£11.64

Airmail (excluding Europe).....£25.20

Overseas payments including Republic of Eire should be covered by Bankers draft in pounds sterling.

Subscriptions normally commence from the current issue of E&MM.  
Back copies can be obtained from E&MM at £1 each inc. postage.

\* Binders will be available shortly \*

E&MM Subscriptions Dept., Maplin Publications  
282 London Road, Westcliff-on-Sea, Essex SS0 7JG

E&MM Subscriptions Dept., Maplin Publications, 282 London Road, Westcliff-on-Sea, Essex SS0 7JG.

Please send me the next 12 issues of Electronics & Music Maker. I enclose a cheque/postal order\* for £9.90/£11.64/£25.20\* made payable to Electronics & Music Maker.

\*DELETE AS APPROPRIATE

PLEASE PRINT

Name .....

Address .....

E&MM7/81

# Good guitars are grown, not made.



Of course, it does help to have advanced construction facilities and some of the finest craftsmen in the world.

But like the great traditional luthiers, we attach unusual importance to the selection and curing of the finest 'soundwoods' available. Such timbers behave as living materials which continue maturing and mellowing even after the guitar is made. The wisdom of working with their natural qualities is the wisdom of Yamaha craftsmen.

Play a Yamaha at your local music store. You'll hear the difference that extra care can make.



musical instruments  **YAMAHA**

Mount Avenue, Bletchley, Milton Keynes MK1 1SE.  
Telephone 0908 71771

# ALPHADAC 16



## SYNTHESISER CONTROLLER

by Charles Blakey and Ken Hitchmough  
Digisound Limited

This low-cost micro-based system provides almost unlimited control possibilities for up to 16 monophonic synthesisers played in real time from one keyboard.

Since the introduction of the first voltage controlled synthesiser in the mid-Sixties two major aspects have concerned designers. The first being a polyphonic capability which was realised about ten years later and has since proliferated, although many have a restricted voicing capability. Secondly, and equally important, the ability to achieve real time control over such a versatile instrument without detracting from its capabilities. Recent reviews in E&MM reveal the cost range of such instruments. 'Alphadac 16' is a micro-processor based system which achieves both of these aims with extensive provision for extending the real time control features. Particular advantages are the ease of fitting to most existing synthesisers coupled with the ability of the current control program to greatly enhance the playing capabilities of equipment which only have one or two voices.

### General Description

'Alphadac 16' is a multi-option system providing computer management of synthesisers having exponential voltage control response, that is most synthesisers, over a five octave range and up to sixteen voices. It is the versatility of the project which gives it an air of complexity but in reality getting the unit up and running only requires an ability for fine soldering and the use of a voltmeter to calibrate the control voltages. There is only one constraint, namely, that the unit


works in conjunction with a digitally encoded keyboard but a suitable encoder is readily available which can be retro-fitted to the majority of popular keyboards. The digital encoder is low in cost and takes the place of the conventional keyboard interface with its resistive divider, sample and hold circuits and gate/trigger generators.

Let us look at two main options. Firstly we recognise that many keyboard players will not wish to get involved in computer programming and also a full computer option will be bulkier and more expensive. So 'Alphadac 16' will operate from a built and tested Controller Card produced by Tangerine Computer Systems and which simply goes into Slot 1 of Alphadac's motherboard. Programs for synthesiser control are provided in EPROMs (permanent memory which may be reprogrammed to incorporate future additions) and the selection of a particular effect is achieved using a sixteen key control pad which may be incorporated into the keyboard case or housed in a separate box adjacent to the keyboard. A single LED provides the necessary communication between the computer and the user. That is all there is to it — in this configuration one does not need to know anything about the operation or programming of computers but at the same time it

allows those who so desire to become familiar with micro-processors and could act as a stepping stone to bigger things. 'Alphadac 16' will also operate from a minimum configuration Microtan 65 and Tanex, also produced by Tangerine Computer Systems. Again the keyboard control can be in EPROM and program selection uses the same control pad mentioned above. There are, however, two important differences. First the communication for the latter will be via a video display and, secondly, the Microtan and Tanex may be expanded to give the user the opportunity to write other synthesiser control programs. We can already hear some of you saying 'can Alphadac be used with my present computer?' Well, first the good news, none of the programs for Alphadac use TANBUG (Tangerine's monitor) and so it would be relatively easy to convert the programs to any 6502 based computer such as Apple, Pet, Superboard, Atari and so on. Difficulty may arise, however, in configuring the input/output port to accept the control pad and keyboard signals.

Each control voltage output from Alphadac uses a separate Digital to Analogue converter. At first sight this may seem rather extravagant but it greatly simplifies user programming. More important though is that it allows

more compact programs so that several keyboard routines can operate simultaneously and this makes the additional cost well worth while. Six slots are provided on the motherboard and four of these are designated for the D to A converters. Each PCB for the latter contains four D to A converters, portamento selected by computer control on each channel, and four gate generators with LED drivers to indicate which gates are on. The actual number of D to A converters installed will be equal to the number of voices (VCOs, etc.) available, for example if you have three voices then only one PCB need be installed together with three Digital to Analogue converters on this PCB. Others may be added later, if required, up to a maximum of sixteen. We also realise that perhaps only a few users will want to fully expand the system to sixteen voices but the design of the motherboard and the front panel is such that we can install other types of controller into any spare slots. This approach keeps expansion costs low. The control voltage and gate signal for each voice is available from a miniature jack socket on the front panel and also from DIL sockets on the motherboard. We have aimed at giving the user as much flexibility as possible without significantly adding to the cost. For example, as already indicated, each control

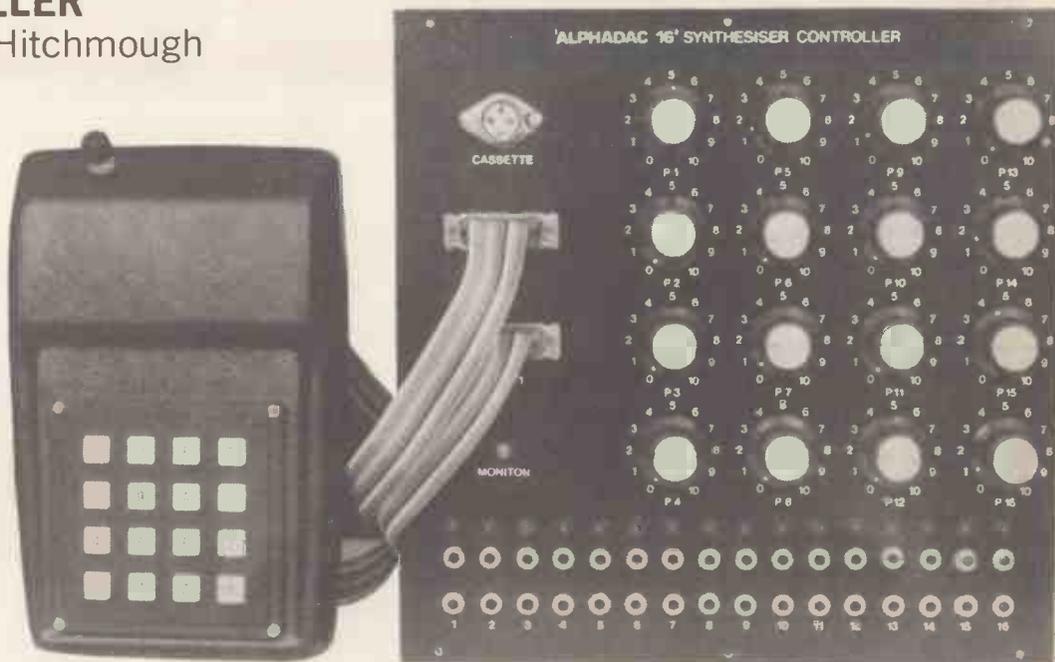

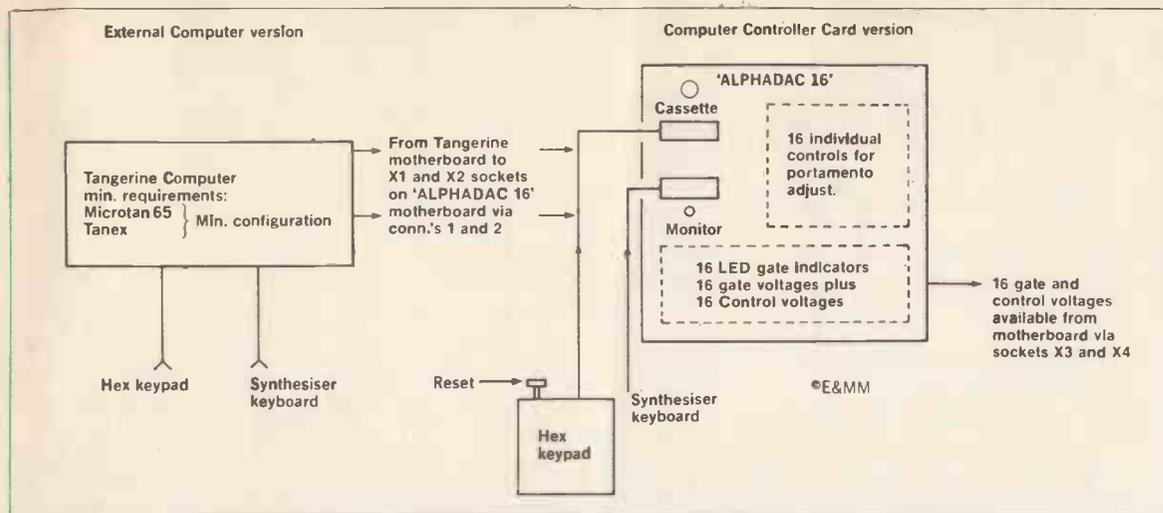


Figure 1. Basic arrangement of 'ALPHADAC 16' with internal computer controller or with external computer.

voltage has its own manual portamento adjustment. Typically, however, we would expect the controller to operate with up to four voices which can be user patched so as to take full advantage of the sound capabilities of the synthesiser and for additional voices to use pre-patched voices. The system will therefore be extended later with an intermediate controller having facility for master control over portamento and all of the other features normally found in polyphonic synthesisers.

Another option is packaging. The block diagram of Figure 1 represents 'Alphadac 16' mount-

ed behind a 9 x 9 inch panel so as to fit in with a range of modular synthesisers. The motherboard and other PCBs could equally well be incorporated into a standard racking system or housed in some other type of portable case.

At the time of publication Alphadac comes complete with a set of keyboard routines in EPROM, called DIGI-1. First of all it is a polyphonic keyboard controller. DIGI-1 can assign control voltages and gates with intelligence, that is, it remembers the keys pressed down on the previous scan and will assign the key to the same voice and avoid note jumping. The memory of

keys pressed remains up to the time when the output channel has to be used for another key because you have run out of voices. But polyphonic control is a trivial application for a micro-processor and one can get a better feel for the available power from the short summary below of other programs incorporated into DIGI-1.

**a. Tune.** Sends the same control voltage plus gate signal to all channels to allow tuning of oscillators and other setting up.

**b. Keyboard Split.** If selected will split the keyboard at any point determined by the first key you press on the keyboard after selection. Choice of whether top or bottom portion of synthesiser is to be the polyphonic section. The monophonic side may even be used to control a separate synthesiser or a voltage controlled module such as a VCO to obtain special effects.

**c. Select Portamento.** If the keyboard has been split then portamento may be independently selected for the monophonic and polyphonic sections. The degree of portamento on each voice is manually adjusted.

**d. Transpose.** Notes may be transposed up or down and at pre-selected intervals; tones, octaves or any semitone interval up to fifteen semitones. Again independent transpose on either side of a split keyboard is possible.

**5. Arpeggiation.** Arpeggiation in up or down or hold modes. Staccato and legato modes. Speed up and slow down. These routines are, of course, for the monophonic section but are very effective even with one or two voices and can act as a simple sequencer.

Remember that these facilities are brought into effect by use of the control pad which becomes a supplementary keyboard to bring the effects into play at any time. Furthermore all of the effects (not

TUNE obviously) can be in use simultaneously.

Some of the above routines could be achieved by a skilled player using multi-track recording techniques but others are impossible to play manually. So what the micro-processor does is to give a new power to the synthesiser, even one with limited voices, and it begins to combine the voice capabilities of a synthesiser with the playability associated with modern electronic organs.

DIGI-1 occupies just an eighth (or a sixteenth by using larger EPROMs) of the EPROM storage area on the Tangerine Controller Card and so ample room for expansion exists. For a four voice controller the cost is about £50 per voice but thereafter each additional voice will be around £15 and a whole new set of programmes put into the existing EPROM somewhat less than the latter figure. The relatively high initial cost is therefore recovered later by savings in expensive additions such as sequencers and other hardware needed to simulate the software capabilities of the 'Alphadac 16'.

## Circuit

No wiring is required between individual PCBs since they are connected together via a motherboard, illustrated in Figure 2, using 64-way DIN plug and sockets. Slot 1 is for the Tangerine Controller Card, Slot 2 for the interface card, and Slots 3, 4, 5 and 6 are identical, accepting a quad D to A converter PCB. DIL sockets X1 and X2 allow the Controller Card to be replaced by the Microtan 65/Tanex combination which connect to these sockets via the 15-way sockets mounted on the front panel. DIL sockets X3 and X4 are connected to the sixteen available control voltages and sixteen gate signals to facilitate connection of the Alphadac to future extensions. The only other components on the motherboard are inputs for the power supplies, which are  $\pm 15V$  and  $+5V$ ; the decoupling capacitors C1, C2 and C3; and the common emitter driver for the monitor LED, D1, which is built around TR1, R1 and R2.

A simplified block diagram of the Controller Card is shown in Figure 3. This unit is supplied ready built and tested and fully socketed for easy expansion. The only component that may have to be soldered in later is a crystal for the serial input. The Controller Card has the following facilities: 6502 CPU (supplied); 8K RAM area using 2114's (1K supplied); 8 EPROM area using 2716's al-

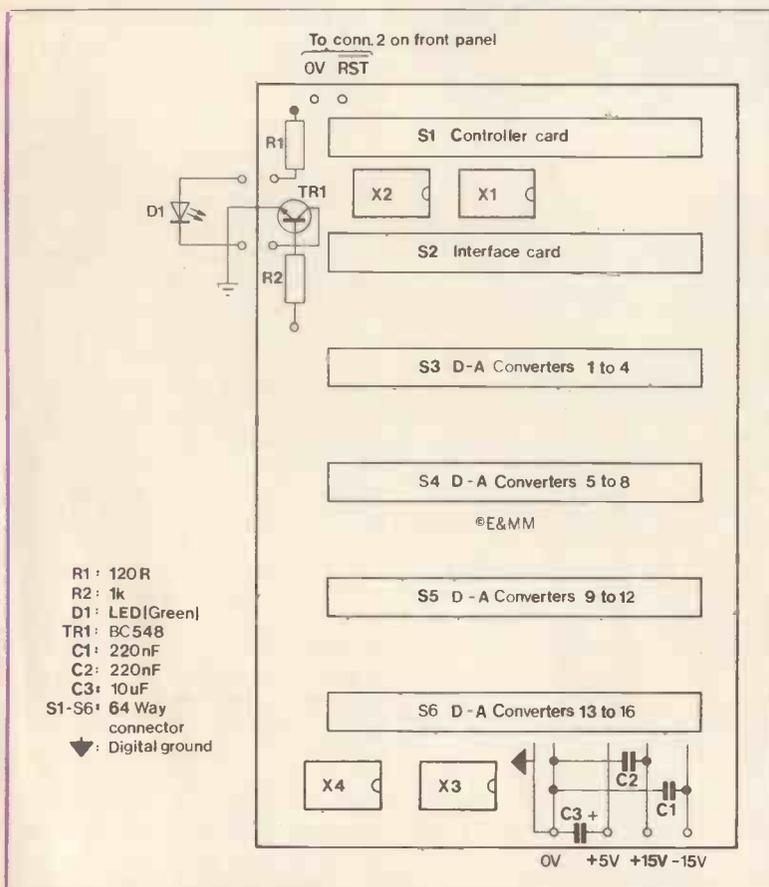


Figure 2. 'ALPHADAC 16' Motherboard.

though this may be expanded to 16K by using 2732's and changing a link on the PCB (2K EPROM supplied as DIGI-1); two 6522 VIA I/O ports (one required and supplied); a cassette interface; and a 6551 serial input.

Slot 2 accommodates the Interface Card whose circuit is illustrated in Figure 4. In reality this is only part of the inter-facing required, the remainder is on the quad D to A converter PCBs. The part on the latter will, however, be required with any computer and splitting the interface up in this way keeps the motherboard bus versatile so that it may be used to accommodate other types of control card in Slots 3 to 6. The nine inputs (don't worry since two have been ANDed together) to the 8-input NAND gate, IC2, are the most important since they are the six address bits (A4 to A9); the R/W; the Input/Output (I/O) line; and  $\phi 2$  from the microprocessor. The combination of these inputs provides a valid WRITE (actually inverted to suit subsequent hardware) signal to allow the keyboard information data bits, D0 to D6 to be converted to analogue outputs for controlling the synthesiser. D0 to D5 are the code bits representing the keys while D6 is a KEY-DOWN signal for the gate information. Bit D7 is a user generated signal to signify that portamento is required. Address bits A2 and A3 determine which of the four possible quad DAC cards are to be addressed while A0 and A1 determine which of the four DAC's, gates and portamentos are selected on the card determined by A2 and A3. These four address bits are simply buffered on the interface card. Likewise the data bits D0 to D7 are buffered. It should be observed that D7 is inverted and the reason for this will be apparent later.

Turning now to the circuit for the quad DAC board, as shown in Figure 5. From the interface card A2, A3 and  $\bar{W}$  go to one half of a dual 1 of 4 decoder (IC1a, 74LS139). With the microprocessor program the first address is the highest, that is, A2 and A3 both at logic '1's' and so naturally the last address will be a '0' + '0'. When IC1a is enabled by the  $\bar{W}$  signal going low it will respond to the A2 and A3 address bits and if both are high then pin 7 will go low. Notice that pin 7, and the other three outputs are connected to a DIL switch marked S1 to S4. With S1 closed the remaining logic on the quad DAC board is enabled whenever A2 and A3 are both high. The switch is not entirely necessary since we could have inserted a wire link in place of S1 for the quad DAC which goes into Slot 3 and provides the out-

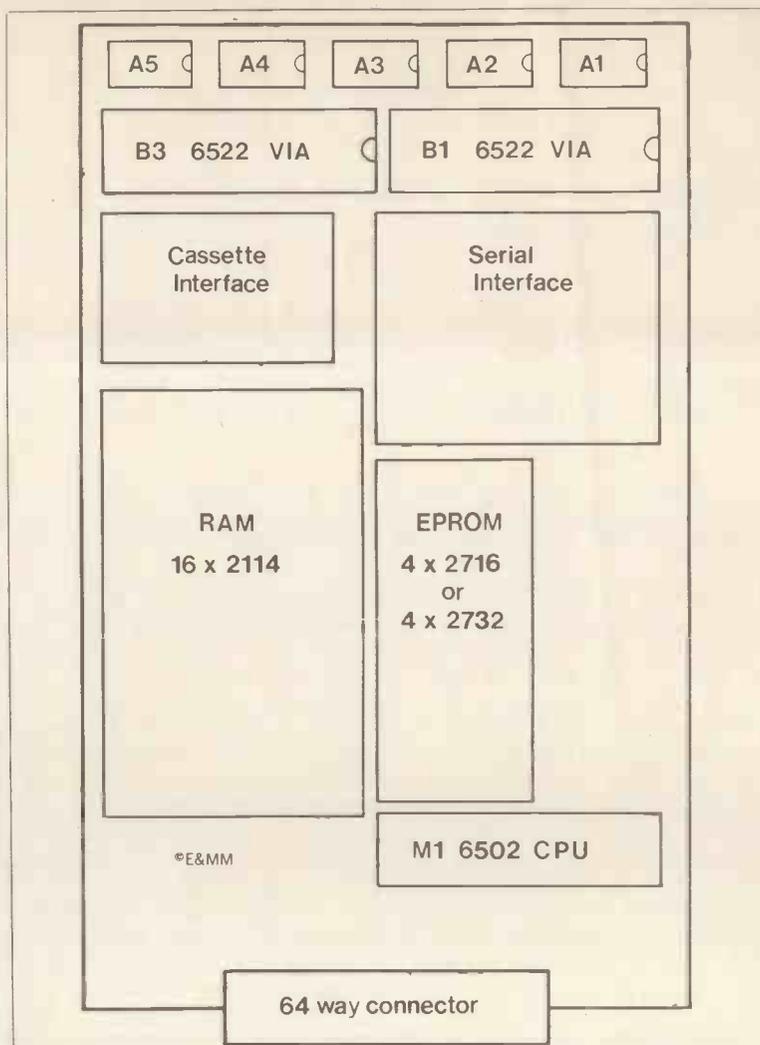


Figure 3. Simplified arrangement of controller card produced by Tangerine Computer Systems.

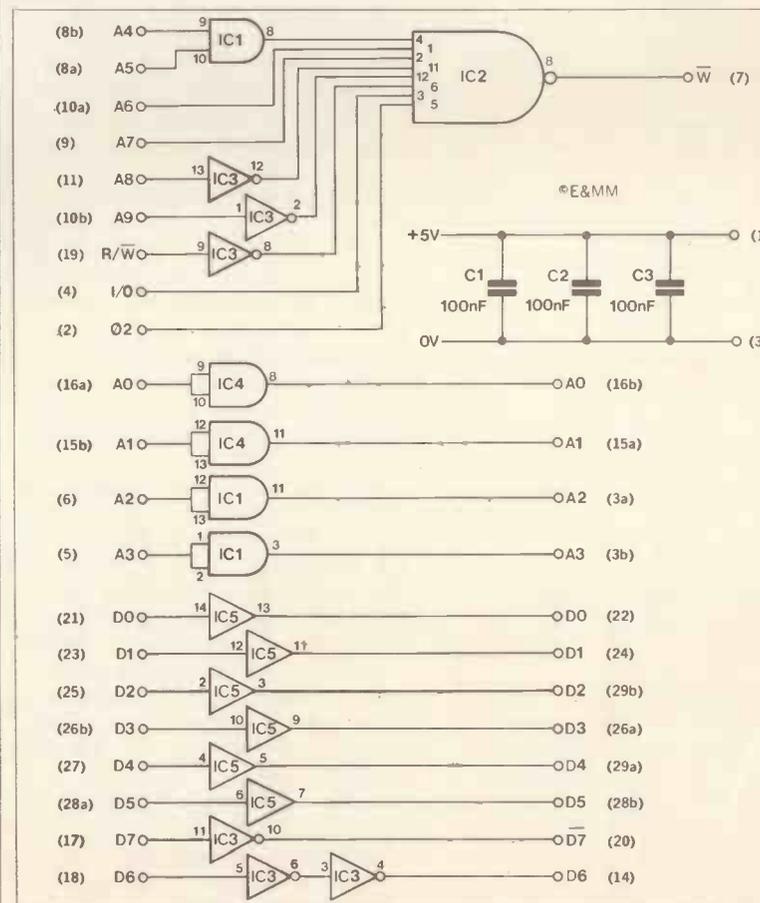


Figure 4. 'ALPHADAC 16' Interface Card.

puts for the first four voices. The switch is nevertheless useful for calibration and enables any quad DAC to go into Slots 3 to 6 by closing S1 to S4 respectively.

The ENABLE from IC1a (the exit side of S1 to S4) goes to both IC1b and IC2. IC1b operates in a similar manner to IC1a, namely with A0 and A1 high pin 9 goes low and this connects with IC3 which is the D to A converter for Channel 1. The four D to A converters are ZN428E-8's which are microprocessor compatible such that when their ENABLE line (pin 4) goes low the converter is transparent to the data bits (D0 to D5 in our case) at the appropriate inputs. Conversely when the ENABLE goes high the data bits are latched into the converter. Thus apart from converting the data bits into an analogue voltage the ZN428E-8 also acts as a perfect sample and hold — the output voltage will remain constant for an unlimited period until either the ENABLE goes low again and new data is presented or until the power is switched off! The ZN428E-8 also has an internal voltage reference from pin 7 and for IC3 this is connected to the voltage reference input at pin 6. R1 connected to the +5V supply produces the necessary reference current while C12 is a stabilising and decoupling capacitor. The same reference voltage used for IC3 is also connected to pin 6 of the other D to A converters, IC7, 9 and 11, which saves power as well as providing excellent gain tracking between the four converters. Apart from this voltage reference aspect all four D to A converters are the same and so we will just describe the first which is built around IC3, IC4, IC5a and IC6a. The ZN428E-8 is an 8-bit (256 increments) device although we are only using the lowest six bits (64 increments) and thus the nominal maximum output from pin 5 of IC3 will be 0V64, or 10mV for each bit increment. Now to achieve a 1V/octave relationship we require each step to increase by 1V/12 (semitones) = 83.33mV and so pin 5 of IC3 is connected to IC4 arranged as a non-inverting amplifier whose gain is precisely adjustable around the nominal gain of 8.3 by the use of the multitrurn trimmer RV1. Trimmer RV2 is used to cancel out the small amount of offset in IC4 while C13 acts as a low pass filter sufficient to remove glitches arising from the D to A converter. It will be apparent that by altering the values of R2, R3 and perhaps RV1 the gain may be altered to suit relationships other than 1V/octave. RV3, C14 and voltage follower IC6a provide a portamento


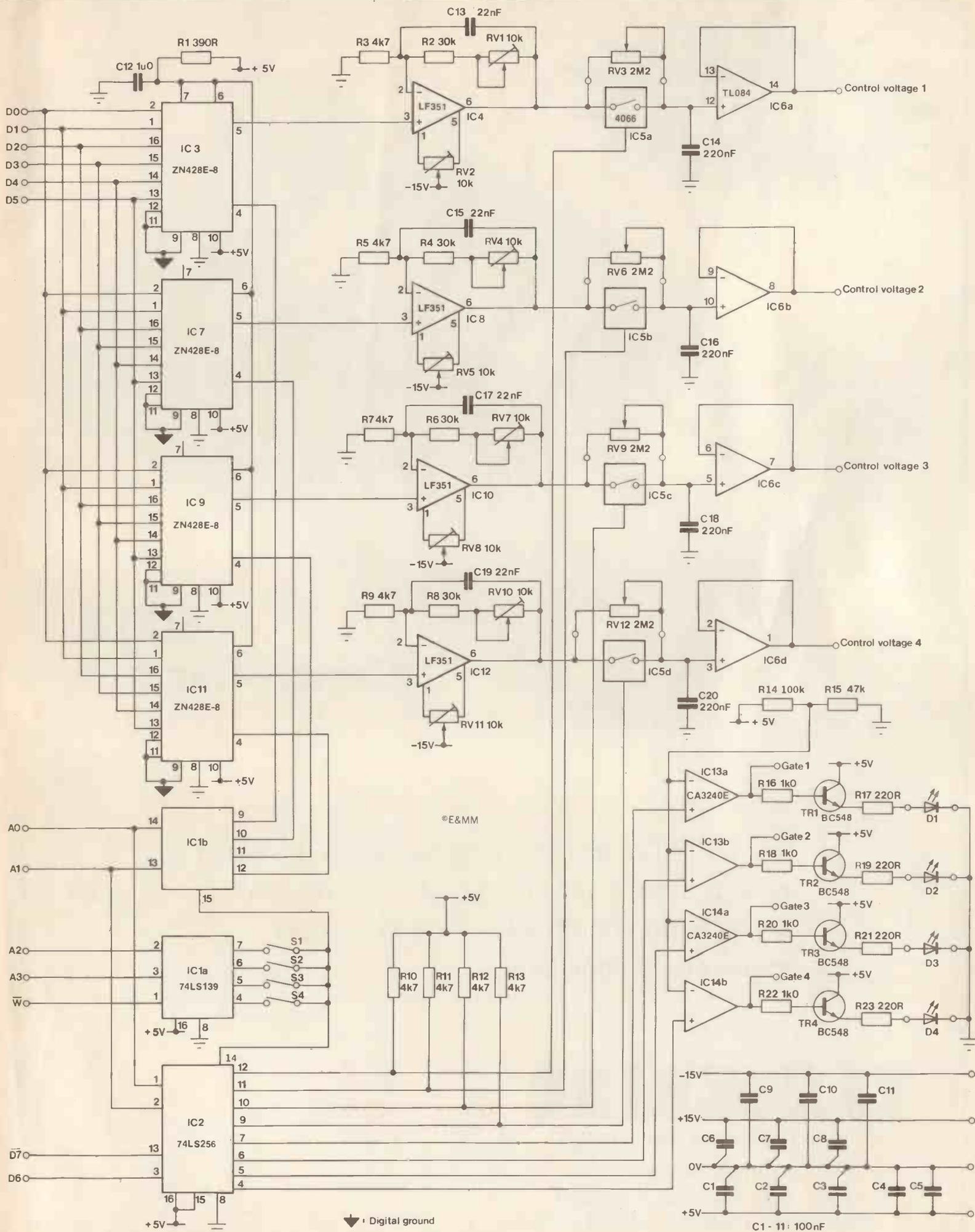


Figure 5. 'ALPHADAC 16' Quad DAC board.

**NEW!**

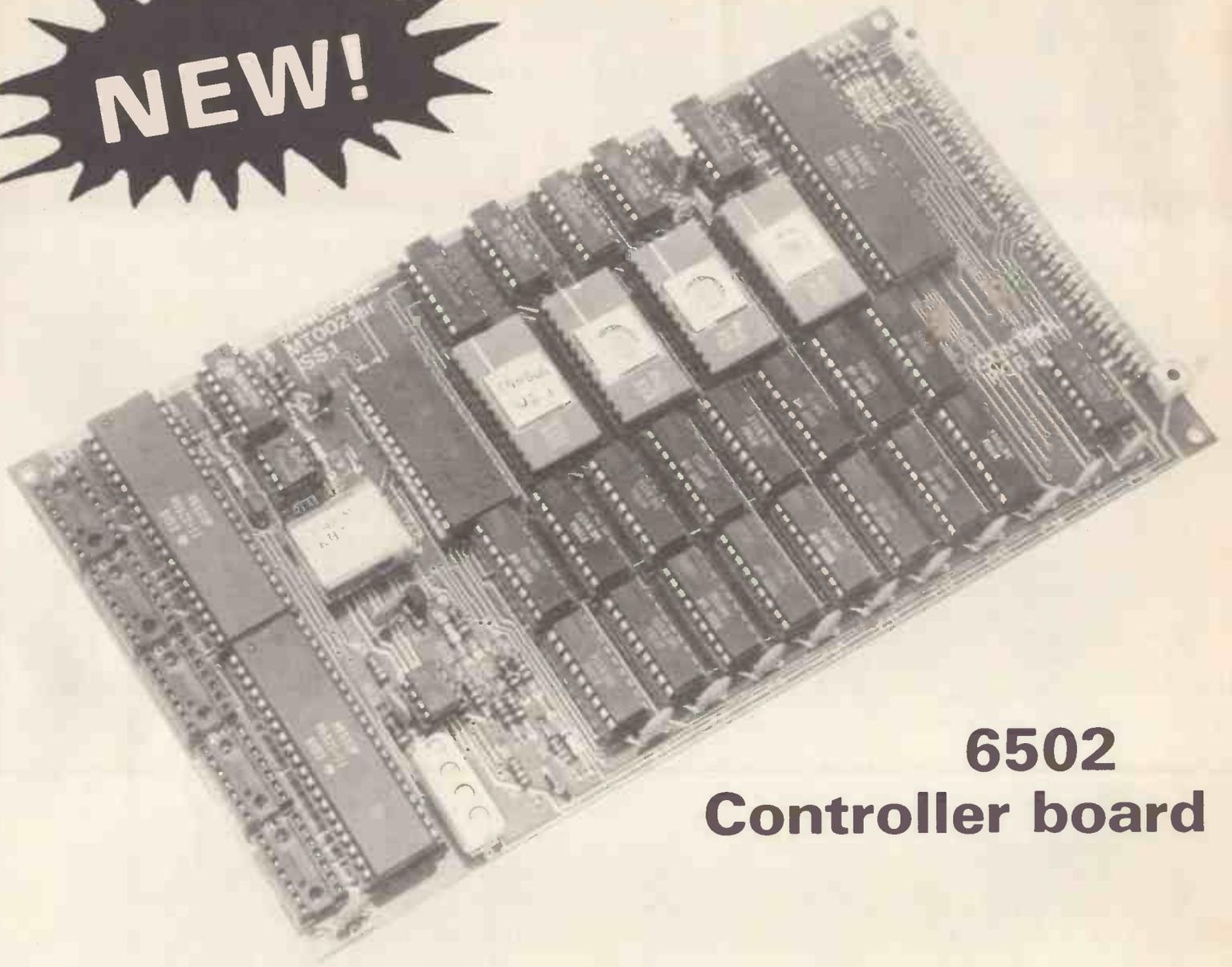

## **6502 Controller board**

The 6502 Controller board has been designed to meet the needs of the O.E.M., but may also be considered by the serious enthusiast and laboratory engineers/technicians.

# **TANGERINE**

COMPUTER SYSTEMS LIMITED

Forehill Works

Forehill, Ely, Cambs., England

Telephone: (0353) 3633

Fully expanded, the 6502 Controller board can provide 16K RAM, 32 I/O lines with handshake, serial I/O port and a cassette interface.

The architecture is identical to the Microtan/TANEX combination, enabling TANBUG V2.3, X Bug and Microsoft BASIC to be used. Furthermore, the O.E.M. can develop software on a Microtan System and transfer the firmwave to the controller board with confidence.

## SPECIFICATION

<b>CPU</b>	<b>6502 (1, 2 or 3 MHz versions)</b>
<b>Clock</b>	<b>crystal controlled</b>
<b>RAM</b>	<b>1K to 8K Bytes Static</b>
<b>ROM</b>	<b>2716 or 2732 up to 16K</b>
<b>Parallel I/O</b>	<b>One or Two VIA type 6522 providing up to 32 I/O lines with handshake and 4 sixteen bit counter timers</b>
<b>Serial I/O</b>	<b>RS232 Software selectable baud rates</b>
<b>Cassette I/O</b>	<b>Software controlled</b>
<b>Expansion</b>	<b>32K ROM BOARD, TAN RAM, PARALLEL I/O CARD, SERIAL I/O CARD, HI-RES GRAPHICS</b>
<b>Price:</b>	<b>from £60.00 to £120 (includes TANBUG) ex VAT</b>

*For further information call PAUL KAUFMAN on (0353) 3633, 5326, 61460 or simply clip coupon and return.*

Please send me full information on the NEW 6502 CONTROLLER BOARD.

Name: .....

Address .....

.....

E&MM7

Please enclose 12p stamp — Thank You

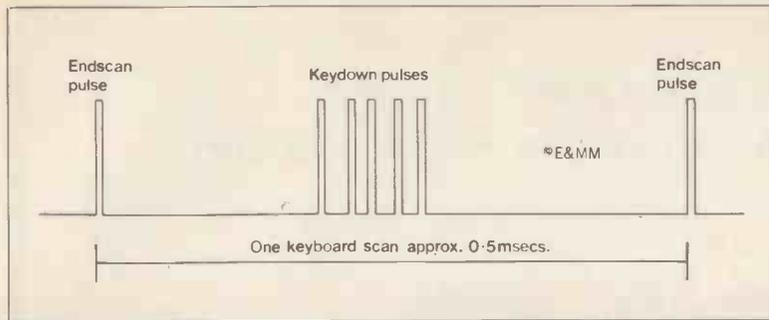


Figure 6. Example of outputs from digitally encoded keyboard.

circuit, i.e., by increasing the resistance of RV3 then C14 will take longer to reach the full voltage and so the rate of glide between notes will increase. A computer controlled facility is provided by IC5a, a voltage controlled switch. When the switch is closed then RV3 is by-passed and no glide will occur since C14 will charge up rapidly. When the switch is opened by the computer then the note will glide at a rate determined by the manual setting of RV3. The control voltage from channel 1 of the Alphadac which connects to the VCO, VCF, etc. is available from the output of IC6a.

Back to the logic circuitry. The ENABLE from IC1a also connects to IC2 (74LS256) which is a dual 4-bit addressable latch. When its ENABLE (pin 14) goes low the outputs will change to the logic status on the data inputs, D6 (gate control) at pin 3 and D7 at pin 13. The outputs that change are, however, governed by the same address lines, A0 and A1, used for the D to A converters. When the ENABLE goes high the data is latched within the IC in much the same way as discussed for the ZN428E-8. You will recall that we inverted D7 on the interface card and the reason is simply

that the computer outputs a logic '1' when portamento is selected. If this '1' were to pass through IC2 to IC5 then it would put the switch in the ON state and cancel the glide. Since this is the opposite to what we require then we simply invert D7. Resistors R10 to R13 on the portamento lines are pull-ups to ensure correct interfacing between the TTL IC2 and CMOS IC5. Gates are also set by a logic '1' on data bit D6. The gate outputs from IC2 go to a comparator (IC13 and IC14) which will go high on receipt of the logic '1' signal from IC2. The comparator reference voltage is set by R14 and R15. A gate output of about 4V5 comes direct from IC13 and IC14 and is fully short-circuit protected. Provision is made on the PCB board for operating ICs 13 and 14 from the +15V supply so as to give gate voltages of about +13V which suits many other synthesisers. Each gate output is connected to an LED, D1 to D4, via transistor drivers TR1 to TR4 so as to provide a visual indication of the channels which are in use.

Well, that is the hardware side

of 'Alphadac 16' but its operation primarily depends on the keyboard electronics, a control pad made up of sixteen keys arranged as a 4 X 4 matrix, and above all on the software called DIGI-1 contained in an EPROM. The keyboard controller, whose electronics cost about £10, consists of two clock driven 8-bit scanners (CD4724's) which examine the keyboard, arranged as an 8x8 matrix, in a sequential manner. Each key up to a practical maximum of 63 therefore has a precisely defined 6-bit code, which is our data bits D0 to D5 discussed above. The scanners are driven by a clock which may be stopped (inhibited) under computer control. Each time a key is found down by the scanner other logic elements output a KEYDOWN pulse which tells the computer to store the value for the key and then carry on doing something else until it receives another instruction. When the scanner completes one scan of 64 steps an ENDSCAN pulse is produced. The computer recognises this pulse as ENDSCAN since the data lines

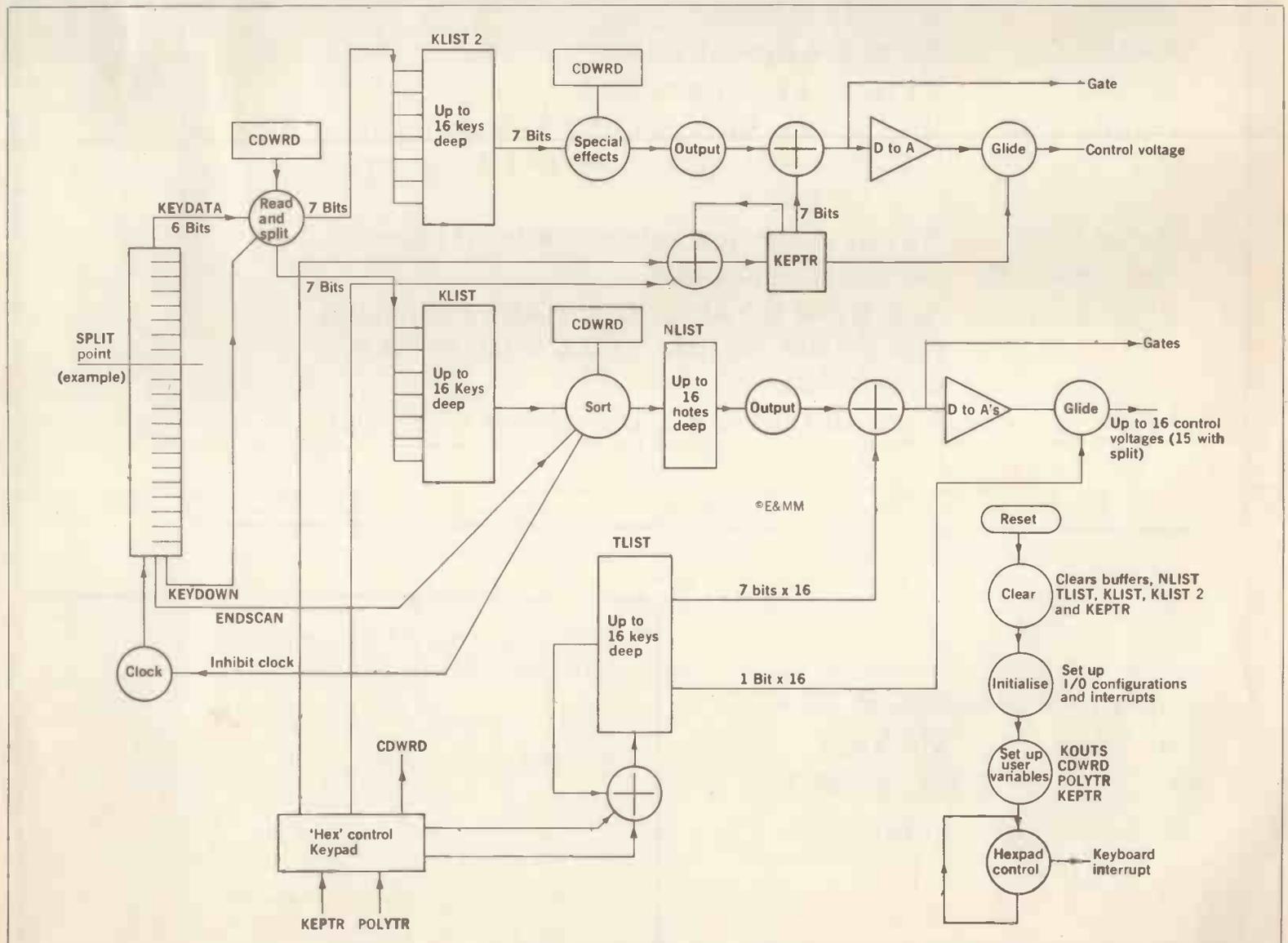


Figure 7. Block diagram of DIGI-1 program.

are at zero when it occurs (this is what limits us to 63 keys since zero is an invalid key response). It is a very short pulse but the computer now goes into a routine to decode all of the KEYDOWN pulses it received during the scan and during this time the keyboard scanning stops — but only for such a very short time that it has no aural effect. If we were to hold down, say, five keys then the various strobe pulses going to the computer would look like Figure 6.


Figure 7 is a block diagram to assist in understanding the operation of the computer program. Since the keyboard is counting upwards the data for keys found pressed are entered into a key list (KLIST) in ascending order. We do, however, have an option to split (SPLIT) the keyboard at any point into a monophonic portion and a polyphonic portion and in these circumstances the computer enters data from the mono section into KLIST2 while the poly side goes to KLIST. This housekeeping task is taken care of by CODEWORD (CDWRD). ENDSCAN initiates a SORT routine to put current valid data into NLIST. At the end of each scan data in NLIST is compared with that in KLIST to determine if a note (or notes) stored in NLIST, with or without gates set, has re-appeared in KLIST. If this is the case then it sets on the gate flag and rubs out the key code from KLIST. If a note present on a previous scan is no longer in KLIST the gate flag is removed. This routine assures that notes do not jump about from output to output as they do with simpler algorithms, or many hardware designs, and that they are all re-assigned to the same channel until such times as limited resources, namely, synthesiser voices, causes the channel to be used for another key. The routine also allows correct operation of ADSR's since once the gate flag is removed from NLIST the note will go into its release cycle. NLIST is filled up in sequence so that all notes played, assuming they are all different, find a slot in NLIST until it becomes full. It will be obvious, however, that the maximum number of notes in NLIST should not exceed the number of synthesiser voices otherwise missed notes will occur. Once keys are allocated to NLIST they are erased from KLIST so that the latter only contains information on keys that have just been pressed or were not able to find a home last time due to insufficient space. When a new note does appear in KLIST the routine looks at NLIST to find a space and it does so by choosing the first non-

allocated space, for example, one where the gate flag is removed. All of this action: comparing KLIST with NLIST; updating NLIST; removing data from KLIST; and outputting data from NLIST to the hardware takes a matter of microseconds and so the scanner is soon running again looking for new keyboard information.

KLIST and NLIST relate to the 16 channel polyphonic keyboard and additional facilities in the program allow us to transpose notes up or down in real time by pressing keys on the control pad. The transpose interval is pre-selected at start up (it can be altered in under two seconds by resetting and entering a new transpose value) and may be any interval from one to fifteen semitones per press of the control key. The transpose value is held in TLIST and is added to the NLIST value prior to outputting the data to the digital to analogue converter. Remember though, the keyboard is restricted to six data bits or a little over five octaves and so if we add an octave transpose to the five octave data bit then some funny things will begin to happen and you will likely have a low note and the data bits will spill over and set the glide (portamento) on and perhaps take the gate off. Similar strange things are likely to happen when transposing down from a low note. It is relatively simple to alter the software to prevent this but in practice you should know what note you are on before doing a realtime transpose and so the strange effects should only happen when you want them to and we feel sure that some users will put it to good use. Lastly, for the polyphonic mode, another control key allows selection of portamento as described in the section dealing with the quad DAC card.

If SPLIT is selected then one less output is available from the polyphonic side — you only have fifteen left. Also in this event channel 1 output is always allocated for the monophonic side of the keyboard and so the output of NLIST starts at channel 2. The monophonic side of the split point obviously does not require any sophisticated allocation routines and so the monophonic data from the keyboard goes to KLIST2. The monophonic side does, however, still retain portamento select, and transpose, via the data stored in KEPTR, and these are independently controllable, that is, one may transpose up or down both or either of the polyphonic channels and each by different amounts.

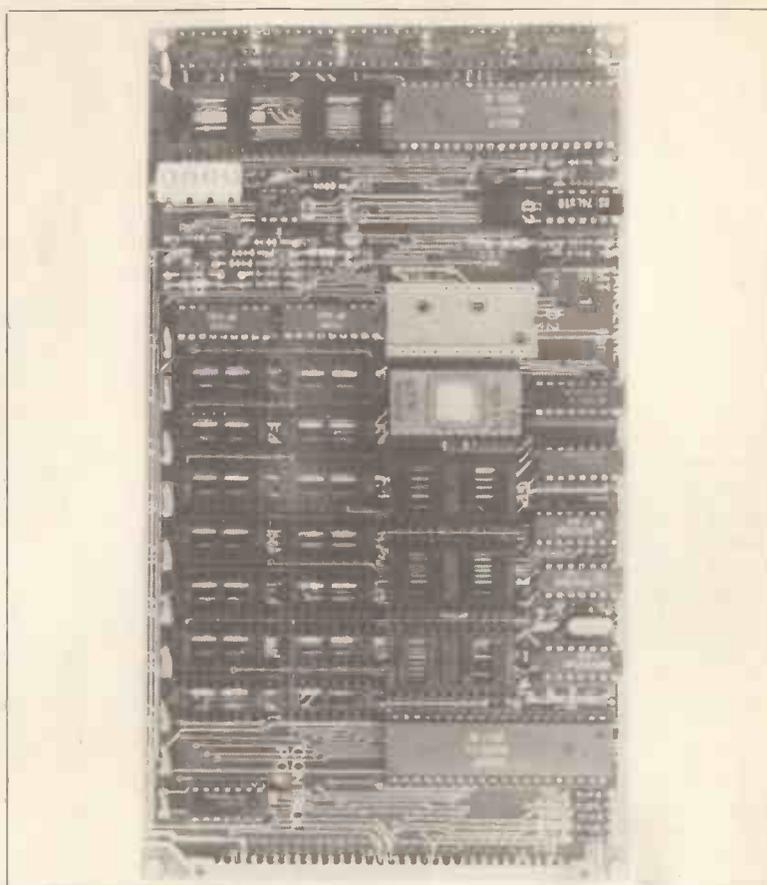DIGI-1 also contains some SPECIAL EFFECTS for the monophonic channel which may be initialised on start-up of the




Tangergine Computer Systems Controller Card.

system. These effects are described in the section dealing with the use of the Alphadac 16.
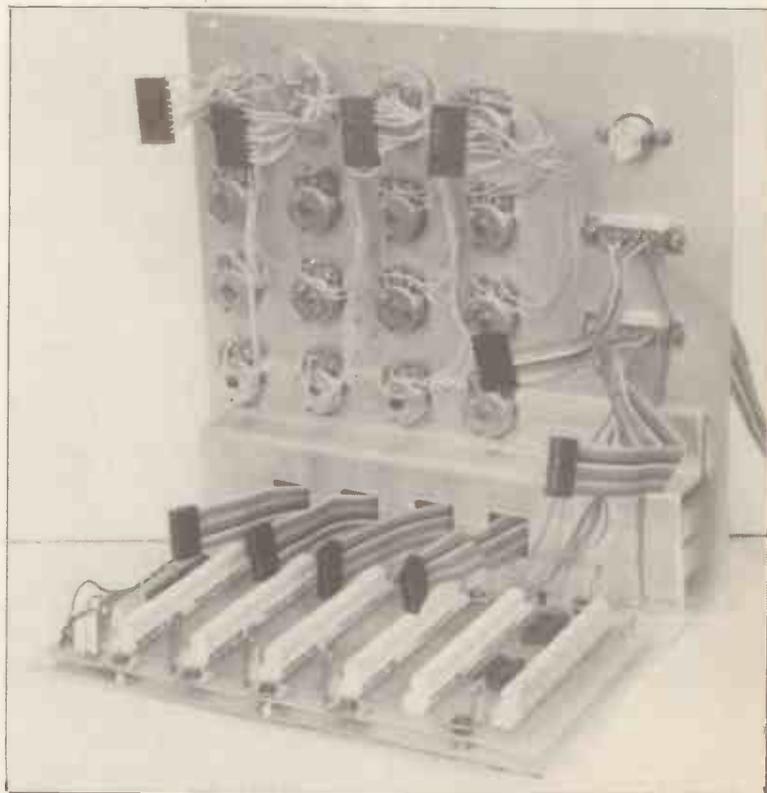
## Construction

These construction notes assume that 'Alphadac 16' is panel mounted, as illustrated, although alterations to suit other methods should be obvious. Like-

wise to avoid confusion on connection listings only those relating to the installation of the Controller Card version are given. For those wishing to use the recommended external computer then additional construction information is available from Digisound Limited. All PCBs for this project have component overlays printed on



Motherboard and front panel wiring.

and so component placement is not shown here. Special care should be taken with orientation of ICs and the DIN connectors but again these are clearly marked on the PCBs.

Start by installing the components on the quad DAC card (PCB 80-C3) since the completed PCB is required for positioning purposes in the next stage. All links are marked and normally can be made with bare solid wire, such as 1/0.6mm, although insulated wire should be used where "INS. LINK" appears. IMPORTANT: THERE ARE TWO LINKS MARKED INSIDE BOXES, ONE IS MARKED "SP. LINK" AND IS THE LINK TO BE USED FOR A NOMINAL 5 VOLT GATE OUTPUT. THE OTHER IS MARKED "HIGH G LINK" AND IS TO BE MADE ONLY WHEN A NOMINAL +15 VOLT GATE IS REQUIRED IN WHICH CASE "SP. LINK" MUST NOT BE MADE. FAILURE TO OBSERVE THIS MAY RESULT IN COSTLY DAMAGE. Carefully check the foil side of the PCB after construction for excess solder or solder splashes which may make unwanted connections — this is normal practice with any project.

Next install the components on the motherboard PCB (PCB 80-C1) and if you are only going to be using four voices in the immediate future then install: the wire links; DIN sockets in Slots 1, 2, 3 and 4 (4 is for ease of calibrating); the components R1, R2, C1 to C3 and TR1; the power connector PCB plug. Next solder wires to: points marked RST and 0V near Slot 1 which are long enough to reach to CONN. 2 on panel; to points marked LED+ and LED 0V long enough to reach the monitor LED; and finally to point marked SKT A1, P11 which has to reach to socket A1 on the Controller Card. After cropping the leads from the underside of the PCB and making the usual check on soldering we are now ready to bolt the PCB to the mounting bracket at points adjacent to Slots 1, 4 and 6 and using nuts as spacers. Plastic nuts and bolts are used at Slots 4 and 6 on the PCB edge nearest the panel to remove the possibility of shorting out a PCB track. First, however, install 'L' brackets at either side of Slots 3 and 5 (plastic bolts at PCB panel edge) with their uprights towards the power supply input. Their precise location can be adjusted later but these brackets will be in front of the component side of the 80-C3 PCBs when the latter are installed in their slots. The PCB can now be put on to the six mounting bolts and spacers and the 'L' brackets installed for Slots 1 and 3. For the Controller Card in Slot 1 the mounting bracket is a

PIN 1 Channel 2 LED	PIN 6 Channel 4 C.V.	PIN 11 Channel 4 gate
PIN 2 Channel 1 LED	PIN 7 Channel 2 C.V.	PIN 12 Channel 2 gate
PIN 3 0V line	PIN 8 Not used	PIN 13 Channel 3 LED
PIN 4 Channel 1 gate	PIN 9 Channel 1 C.V.	PIN 14 Channel 4 LED
PIN 5 Channel 3 gate	PIN 10 Channel 3 C.V.	

Table 1

PIN 1 P1, input	PIN 5 P2, output	PIN 9 P4, output
PIN 2 P1, output	PIN 6 P3, input	PIN 10 Not used
PIN 3 Not used	PIN 7 P3, output	
PIN 4 P2, input	PIN 8 P4, input	

*Input and output refer to the side of the voltage controlled switch, IC5*

Table 2

PIN NO.	KEYPAD 15-WAY CABLE AND CONN. 2 15-WAY SOCKET	CONN. 2 15-WAY SOCKET TO 14 PIN HEADER TO A2 ON CONTROLLER CARD
1	N.C.	N.C.
2	C1	C1
3	C2	C2
4	C3	C3
5	C4	C4
6	R1	R1
7	N.C.	N.C.
8	N.C.	N.C.
9	R2	R2
10	R3	R3
11	R4	R4
12	N.C.	N.C.
13	N.C.	N.C.
14	0V	N.C.
15	RST	N/A

Table 3

PIN NO.	KEYBOARD CONTROLLER AND CONN. 1 15-WAY	14 PIN DIL HEADER FROM CONN. 1 TO A1 ON CONTROLLER CARD
1	D0	+5V
2	D1	D0
3	D2	D1
4	D3	D2
5	D4	D3
6	D5	D4
7	N.C.	0V
8	N.C.	0V
9	N.C.	D5
10	0V	N.C.
11	N.C.	TO R2 ON MOTHERBOARD
12	INHIBIT	INHIBIT
13	STROBE	STROBE
14	N.C.	+5V
15	+5V	N/A

Table 4

shorter type and its upright should face the non-component side of the PCB. In this instance the PCB is secured with a plastic nut and bolt with another nut as an insulating spacer between the bracket and the PCB.

The DIL socket X5 on the quad DAC board for Slot 3, the first four voices, now connects with the first four sets of LEDs and pairs of jack sockets on the front panel. The 0V line from X5 is used for the ground connection to the LEDs (short lead) and the ground connection of the jack sockets. The jack socket just below the LED should be assigned to the gate output voltage. A length of ribbon cable is used to connect between the X5 DIL header and the panel components. This 13-way cable should be long enough so that the quad DAC card can operate from

Slot 3 or Slot 4, but do not make it excessively long. The length can be gauged by offering up the motherboard bracket to the panel with the quad DAC in place. The X5 connections are shown in Table 1.

If more than one DAC card is fitted then the connections between X5 and the panel can be made the exact length for Slots 4 onwards. When all of the connections to the panel have been made then thread the DIL headers through the appropriate holes in the mounting bracket and join the latter to the panel using two or more of the bottom row of potentiometers. For the first quad DAC potentiometers P1 to P4 (equivalent to RV3, 6, 9 and 12 respectively on the circuit diagram) are now wired up to the Molex socket which connects to

the DAC card as in Table 2.

Again by temporarily installing the DAC into its slot the wire lengths can be accurately gauged but for the DAC in Slot 3 the wires must be long enough for the DAC to be used in Slot 4. Viewing the potentiometers from the rear and their connections facing upwards the wiper and right hand connection are connected to one wire and the left hand connection to the other wire.

Now make up the control keypad. This may either be installed in the keyboard case or in a separate housing as illustrated. The housing shown allows space for expansion. The keypad should be located close to the bottom lip of this case and by turning the keypad over the hole positions can be marked and then drilled. A slot will have to be cut into the case to allow connections from the keypad to pass through and this is best done by drilling a row of holes of 5 to 6mm. diameter and cutting out the excess plastic between the holes — do this carefully since it is difficult to play keyboards with a bandaged hand! A hole is also required at the rear of the case to accept a 15-way cable. The photographs show the use of flat cable but most constructors will find it more convenient to use round cable. The RESET button is mounted on the top slope of the case at the rear about 20mm. in from the left edge so that it does not interfere with the internal clips. A 6.5mm (or ¼ inch) hole is required for this push-button switch. Finally the case should be fitted with four rubber feet at its extreme corners to prevent it slipping around when in use. The keypad connects to the 15-way socket, CONN. 2, on the panel and the connections are listed in Table 3.

The R and C numbers in Table 3 refer to the markings on the keypad used. Do not cut short any unused wires on the 15-way cable since they will be required at a later date.

If the keypad is installed into the keyboard case then the simplest technique is to also install a 15-way socket as well and to connect up with CONN. 2 using a length of 15-way cable terminated at each end with 15-way plugs.

Now install CONN. 1 which goes to the keyboard controller using 15-way miniature D connectors as above. The sockets are installed on the keyboard and the Alphadac panel and the connections are made using a short connecting lead with a plug at both ends. Behind the panel, CONN. 1 connects with socket A1 of the Controller Card using a 14-pin DIL header. The connections

are shown in Table 4.

Next install the monitor LED and connect the remaining wires on the motherboard. The wire at the end of R2 on PCB goes to pin 11 of the DIL header for the A1 socket of the Controller Card, as listed above. The wire at the end of R1 (LED+) goes to the long lead of the monitor LED and that from TR1 collector (LED 0V) to the short lead. The 0V and RST wires near Slot 1 go to CONN. 1 connector as listed earlier in order to connect up with the RESET push button switch.


Finally, install the components on the Interface PCB (PCB 80-2). After inserting the DIGI-1 EPROM into socket F2 of the Controller Card we are now ready to go. Install the Controller Card in Slot 1; the Interface Card in Slot 2; and one quad DAC Card into Slot 4 for the calibration step with switch S2 on and the other switches off. Join up the Molex connector from P1 to P4 to the DAC Card and also the DIL header for channels 1 to 4 to socket X5 on the DAC. Power supplies required are  $\pm 15V$  and  $+5V$  and the 0V lines for both supplies should be commoned together. Life will be simpler if both power supplies are turned on from the same mains switch but if not then it is good practice to switch the  $+5V$  supply on first followed by the  $\pm 15V$  supplies. Likewise the latter should be switched off first followed by the  $+5V$  supply.

## Operating and Calibrating the Alphadac 16

After switching on the power the first step is to press the RESET button associated with the control pad. With a computer operated system the video would ask four questions and expect the appropriate responses. These are:

**A. VOICES?** That is how many synthesiser voices are you going to use? Press key 1 to F which equals 1 to 15 while pressing key 0 at this time indicates that you have sixteen voices.

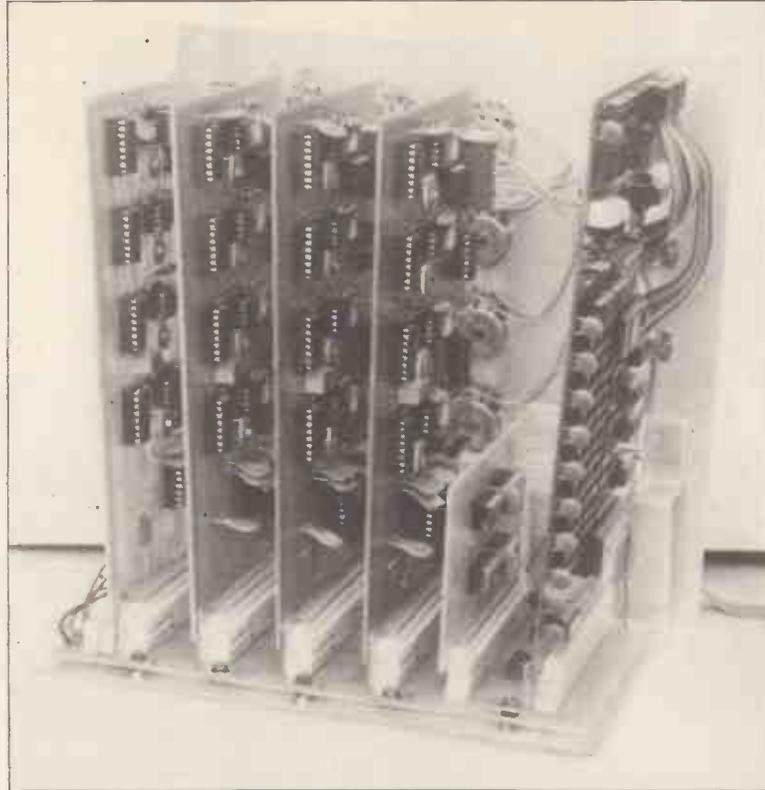**B. CDWRD?** At this stage a CDWRD of 0 or 1 should be entered. Key 1 will indicate that you will require a top split, that is the top section of the keyboard will be used for the monophonic section with a high note priority and its output always going to channel 1 with the bottom portion of the keyboard being polyphonic with up to fifteen more available channels. Pressing key 0 gives a bottom split, the monophonic channel being at the lower portion of the keyboard. Note that the response to this question is preparing the computer for a subsequent control pad response.



Complete synthesiser controller with 4 DACs and Tangerine Card.

In other words you are only informing the computer that when you do select split (see later) it will be top or bottom and until such times as this additional command is given the keyboard will respond solely in the polyphonic mode. In fact CDWRD is more powerful than this and does allow you to enter into various keyboard routines immediately from this start up stage. For simplicity, however, will we stick with the 0 and 1 response to CDWRD and further details of the use of this function are provided with the programme listing.

**C. POLYTR?** Enter the transpose value for the polyphonic channels. Pressing keys 1 to F equal transpose values of 1 to 15 semitones, so for example key C will result in an octave transpose. As with split described above, the transpose will only take place in response to a subsequent control pad response so as to be able to effect the transpose in real time, but you are deciding beforehand the effect you will obtain.

**D. KEPTR?** Enter transpose value that may be required for the monophonic channel. The key values are the same as for POLYTR but note that the monophonic portion of the keyboard (if required) can have a different transpose value.

The computer then expects you to press any button on the keypad to start, so do it now.

Starting up with the Controller Card is just as easy. Press the RESET button at which time the monitor LED will be extinguished and remain off. Then press the

control pad keys as though you were responding to the four questions listed above and then press any other key to start. On completion the monitor LED will now flash slowly and it will stay in this condition except when arpeggiation routines are in use at which time it will flash on and off at the arpeggiation rate.

Suppose then we wish to set up for four voices, top split and octave transposes on both polyphonic and monophonic channels. Just press RESET followed by control pad keys 4-1-C-C-C (the last C being the start command). The whole procedure takes less than two seconds. If a mistake is made during setting up, or the monitor LED stops flashing (perhaps a short power failure) or you wish to change the program then press RESET followed by the required keys on the control pad.

Calibration is also straightforward except that close packing of the PCBs restricts access to the quad DACs. In the construction we have recommended installing Slot 4 even though no more than four voices are installed initially. The first DAC is therefore put into Slot 4 as described earlier and using a small screwdriver or trimming tool there is now sufficient space to access the trimmers on the DAC Card. Remember switch S2 should be on and the others off when it is in this Slot. Turn power on, press RESET and press control keys 4-1-C-C-C in sequence. To be sure, now press key 0 on the control pad and adjust trimmers RV2, RV5, RV8

and RV11 so that the output from the respective ICs is exactly zero. The voltage can be measured at the Molex plug on the PCB by connecting up to the appropriate P 'input' as listed earlier, e.g., P2 input at pin 4 of the Molex connector will allow the offset of IC8 to be trimmed out using RV5. Now measure the control voltages from the jack sockets for channels 1 to 4 and use trimmers RV1, RV4, RV7 and RV10 respectively to obtain the required 1V/octave relationship. The initial voltage may be a millivolt or two from zero due to the small offset in IC6 but this should be ignored — trying to trim it out with the presets used above will make matters worse. Calibrate each channel in turn using the following procedure. Press control pad key 4 twice and adjust the appropriate multiturn trimmer to give exactly 2 volts. Press key 4 again and adjust trimmer, if necessary, to obtain exactly 3 volts. Next press key 5 which takes you back to 2 volts and keep pressing keys in the sequence 4-5-4-5... until the values obtained are as close to 2 and 3 volts as you can make them. Pressing key 0 puts you back to zero and repeated pressing of key 4 (up to five times) takes you up in octave steps and so allows you to obtain the best linear response by using the trimmers.

## Using the 'Alphadac 16'

There are a large number of effects available in the DIGI-1 program and they should be treated as an aid to playing and not taking full command of the synthesiser. In other words they increase the scope for experimentation to achieve some novel effects. This using section therefore lists the function of the sixteen keys on the control pad.

**KEY 0.** This is the CLEAR key. It clears all values entered from the keyboard or control pad and can be used at any time if you find yourself in an awkward situation. It does not affect the original program values — only pressing RESET and entering new values can do that.

**KEY 1. TUNE.** This key outputs the same key code to all channels and puts the gate on. It therefore allows all oscillators to be tuned exactly to each other. Pressing key 0 when tuning is complete puts the keyboard and control pad back into your control.

**KEY 2. PORTAMENTO.** Sets glide on all polyphonic channels. If glide is off then pressing the key puts it on while if it is already on then pressing key 2 will turn it off. This key will not affect channel 1

if split is in operation.

**KEY 3. PORTAMENTO.** Operates as key 2 but only on channel 1 when split keyboard is in use.

**KEY 4. (POLY) TRANSPOSE UP.** Pressing this key will transpose the polyphonic voices up by the interval selected at start-up. It does not affect channel 1 if split is in operation.

**KEY 5. (POLY) TRANSPOSE DOWN.** As key 4 but the polyphonic section is transposed down by the selected interval. Note that the control pad may be used like a second keyboard and the keys may be pressed in time with the music to give, for example, instantaneous transposition of any part of the music. Remember the strange effects that may occur if you transpose outside of the five octave range of the control bits. To put the keyboard into some other tune range still requires the normal octave shift facility found on most synthesisers.

**KEY 6. (MONO) TRANSPOSE UP.** As key 4 but operates on channel 1 if keyboard split is in use.

**KEY 7. (MONO) TRANSPOSE DOWN.** As key 5 but operates on channel 1 in split mode.

**KEY 8. SELECT SPLIT POINT.** After key 8 on the control pad has been pressed then the first key pressed on the keyboard becomes the split point, that is, the point where the keyboard changes from monophonic to polyphonic. Whether the monophonic section is at the top or bottom portion of the keyboard depends on the program value entered at start-up, as discussed earlier. If you find that the split point is not quite in the right position when you come to play the music then simply press key 0, press key 8 and then press the new note on the keyboard where you require the split to occur. You can, of course, always do a RESET and split the keyboard the other way round. Pressing key 8 again while in the split mode will make the keyboard revert back to polyphonic operation without having to clear other values you may be using.

With the split mode plus the

ability to independently select portamento, transpose up and transpose down on each side in real time the playing possibilities become exciting. For example, with a bottom split (key 0 during setting up) channel 1 may be set to a bass guitar sound to accompany yourself on the polyphonic channels. The possibilities are, however, endless since you could also select top split and by transposing the top monophonic section down and the bottom polyphonic section up you would be able to play the bass line with your right hand! Much of the fun comes from experimenting with the effects yourself and learning their musical possibilities but, as other examples, the monophonic channel could be used to control another 1V/octave synthesiser or you may use it to control a separate low frequency VCO (or other voltage controlled module) to obtain dynamic control of modulation and so on.

**KEY 9.** This key puts you into the arpeggiation mode in the mono-

phonic section of a split keyboard. Up to 16 keys may be held down in this mode and the computer will play each one in turn.

**KEY A.** Selects UP or DOWN arpeggiation. If the computer is reading up the scale then pressing the key will cause it to read down or vice versa.

**KEY B.** Pressing this key causes the arpeggiation to reverse direction automatically at the end of each scan of the keys being held down.

**KEY C.** Selects staccato or legato mode of arpeggiation. Again if you are in the staccato mode then pressing the key puts you into legato or vice versa.

**KEY D.** Increases the rate of arpeggiation each time the key is pressed.

**KEY E.** Decreases the rate of arpeggiation each time the key is pressed. When in the arpeggiation routine the monitor LED flashes at the arpeggiation rate.

**KEY F.** This key will turn the arpeggiation into a sequence which will continue to play even when all keys are released and so

## PARTS LIST — MOTHERBOARD (4 VOICES)

Resistors — ¼W 5% carbon film

R1 120R  
R2 1k0

Capacitors

C1,2 220nF polyester (Plessey Minibox) (2 off)  
C3 10uF 25V tantalum electrolytic

Semiconductors

TR1 BC548  
D1 SEL1710Y (5mm yellow LED)

Miscellaneous

64-way A/B DIN sockets (4 off)  
PCB 80-C1  
Sundry mounting hardware

## PARTS LIST — 'ALPHADAC' INTERFACE CARD

Capacitors

C1,2,3 100nF ceramic disc (3 off)

Semiconductors

IC1,4 74LS08 (2 off)  
IC2 74LS30  
IC3 74LS04  
IC5 74LS365

Miscellaneous

14 pin DIL sockets (4 off)  
16 pin DIL socket  
64-way A/B DIN plug  
PCB 80-C2

## PARTS LIST — ADDITIONAL ITEMS FOR 'ALPHADAC 16'

TANGERINE 'CONTROLLER CARD' or 'MICROTAN 65'/'TANEX'

Hex. Keypad. 4 x 4 matrix

Optional case for above. West Hyde VDU PR4.

Push to make switch

15-way miniature-D plugs (2 off)

15-way miniature-D sockets (2 off)

3.5mm jack sockets (8 off)

Panel, mounting bracket, miscellaneous hardware. (for four voices)

## PARTS LIST FOR QUAD DIGITAL TO ANALOGUE CONVERTER BOARD

Resistors — ¼W 1% metal film

R1 390R  
R2,4,6,8 30k (4 off)  
R3,5,7,9 4k7 (4 off)

Resistors — ¼W 5% carbon film

R10,11,12,13 4k7  
R14 100k  
R15 47k  
R16,18,20,22 1k0 (4 off)  
R17,19,21,23 220R (4 off)

Capacitors

C1,2,3,4,5,6,7,8,9,10,11 100nF ceramic disc (11 off)  
C12 1uF MKH polyester  
C13,15,17,19 22nF polyester (Plessey Minibox) (4 off)  
C14,16,18,20 220nF polyester (Plessey Minibox) (4 off)

Potentiometers

RV1,4,7,10 10k, 25 turn cermet (Spectrol 64Y) (4 off)  
RV2,5,8,11 10k cermet (Egen 482H20) (4 off)  
RV3,6,9,12 2M2 log. potentiometers (4 off)


Semiconductors

IC1 74LS139  
IC2 74LS256  
IC3,7,9,11 ZN428E-8 (4 off)  
IC4,8,10,12 LF351N (4 off)  
IC5 CD4066B  
IC6 TL084CN  
IC13,14 CA3240E (2 off)  
TR1,2,3,4 BC548 (4 off)  
D1,2,3,4 SEL2110R and clips (3mm red LED) (4 off)

Miscellaneous

Switch, S1 to S4 4-pole SPST lateral DIL (4 off)  
8-pin DIL sockets (4 off)  
14-pin DIL sockets (5 off)  
16-pin DIL sockets (6 off)  
14-pin DIL header  
10-way 0.1 inch Molex connector (plug, cover and pins)  
64-way A/B DIN plug  
PCB 80-C3

A complete set of parts for a 4-voice controller card version of 'Alphadac 16' as described above, is £193.50 plus VAT. Parts for control of an additional four voices is £50.44 plus VAT. These are available from Digisound Ltd, 13, The Brooklands, Wrea Green, Preston, Lancs. PR4 2NQ. Tel: 0772 683138. Both sets exclude single connecting wire, solder and the four control knobs — the latter being a user choice to match other equipment. It does include the programs in EPROM, keypad, panel, nuts and bolts, special wire (15-way cable and strip type), connectors and DIL sockets, PCBs and all electronic components.

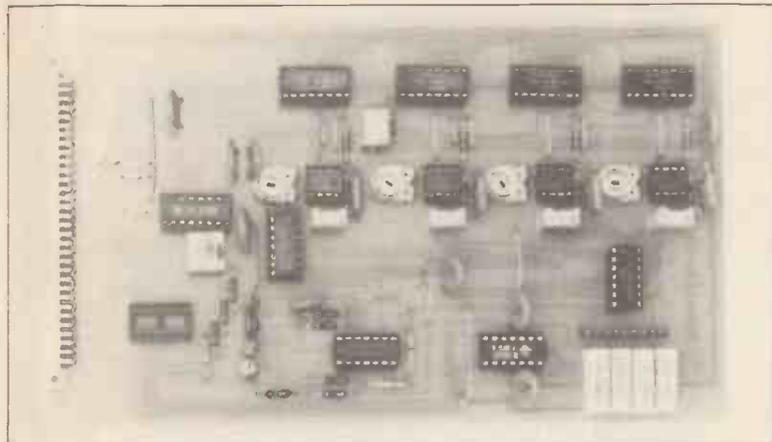


Alphadac 16 Quad DAC board.

provide an automatic accompaniment. One precaution has to be observed, namely, that the notes selected have to be released from the top of the keyboard downwards. This is quite easy to do. But the effect does not end there since pressing any other single key will now take the place of the lowest note that was originally pressed and all of the notes could be replaced by another sequence. Press key F again to stop this mode or key O to clear. Remember also that transpose and glide are still available while in the arpeggiation routines.

It is routines such as the arpeggiation techniques which add playability to the synthesiser even when only one or two voices are available. For example, pressing keys 9 and A and holding down a chord in the monophonic section will almost sound like a chord if the scanning rate is fast enough — press key D successively to increase the rate. Another effect could be obtained by connecting channel 2 output

(on the polyphonic side) to a second control input on the arpeggiation oscillator (channel 1 monophonic portion) and with this patch pressing one key on the polyphonic side will effect a transpose at various intervals available on the latter portion. It is all good fun but it also has many musical possibilities as well and remember if you get in a muddle while learning then just press key O and start again.

Having run out of keys this seems a suitable stage at present to conclude the DIGI-1 program. In later versions, which will be exchanged for DIGI-1 at a small cost, we propose to keep to one control pad and have an external switch which will effectively double its capacity. Likewise other routines such as sequencing will be following on. There is, however, a great deal of music to be made with DIGI-1 and it is best to get to know this program thoroughly now so that you will be able to make the best use of later additions. E&MM

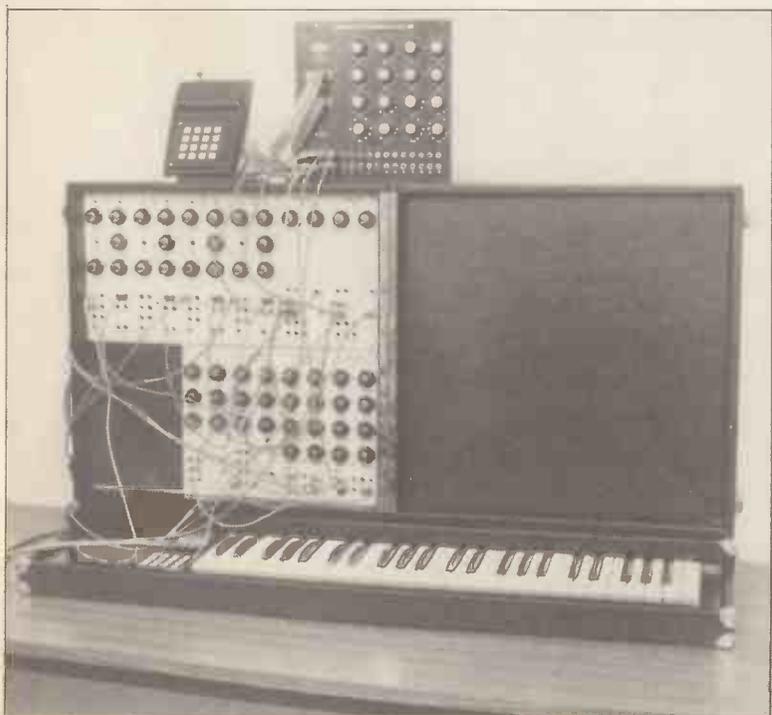

A complete 4-voice synthesiser controlled by Alphadac 16.

# 'ALPHADAC 16'

## FIRST U.K. OFF-THE-SHELF MICROPROCESSOR CONTROLLER FOR SYNTHESISERS

- The intelligent method of achieving polyphonic control
- Up to sixteen voice capability
- DIGI-1 program also includes routines for tune; keyboard split; portamento select; transpose and several arpeggiation techniques.
- Effects operate in real time and in any combination
- Great when used with one or two voices and magic with three or more
- Major expansion capability which will give greater value for money than stand alone sequencers and other hardware add-ons
- More playing power for skilled and unskilled keyboardists
- Suitable for all synths. having exponential control. Keyboard controller easily retro-fitted to most instruments

\* *DIGI-1 now occupies full 2k EPROM with addition of two sequencer programs*

Only available from Digisound Limited

Send 2 x 14p stamps for pricing information and advice on 'ALPHADAC 16' options; for DIGISOUND 80 modular synthesiser; for special ELECTROMUSIC ICs; and for TANGERINE COMPUTER SYSTEMS parts which we are proud to add to our range of products stocked. Fast and personal service with technical back-up.



**DIGISOUND LIMITED,**

13 THE BROOKLANDS, WREA GREEN,  
PRESTON, LANCS. PR4 2NQ

Tel: 0772 683138 (MAIL ORDER ONLY)

(MAIL ORDER — VISITORS BY APPOINTMENT)

# SYNWAVE

- \* Sounds from swirling sea to cymbal and wood block
- \* Easy to build and play
- \* Dual trigger operation - percussive/external trigger
- \* Touch sensitive

Design - Mike Beecher  
Development - Robert Penfold

The Synwave continues our series of small projects that produce sounds for use in electro-music by percussive control. The minimum number of controls have been selected to give a wide range of 'sea-wave' sounds. In addition, different settings of the controls will produce wind, cymbal and woodblock sounds.

Like the 'Syntom' project featured in our April issue, the unit can be triggered by tapping the case or by striking a drum (on which the Synwave is mounted). These projects are also ideal for triggering from an external source (e.g. a sequencer synthesiser or micro) and thus a second mode of operation can be from an electronic trigger using a positive-going edge of about 7 to 15 volts in amplitude. Interaction of the two modes of use is possible so that complex rhythms can be made from a steady 'external triggered' beat mixed with hand or drum taps providing syncopation.

The four controls are Volume (with on/off switch), for setting output level; Decay - adjusts the time it takes for the sound to die away; Pitch - sets the frequency range of noise from low to high; 'Q' - a resonance control that narrows and highlights the pitch range selected.

## Circuit

The block diagram of Figure 1 shows the general arrangement used in the Synwave. An envelope shaper can be operated by either

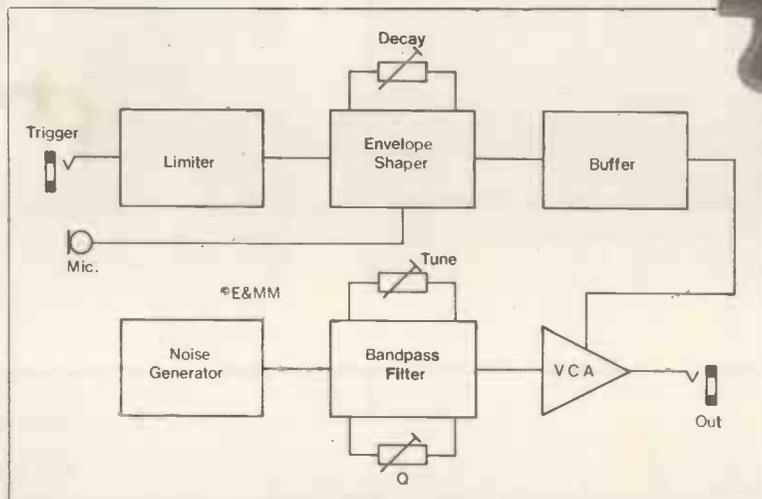


Figure 1. Block diagram of the Synwave.

an internal microphone or an external trigger signal, or both. The envelope shaper has a fast attack and slow decay, with the latter being adjustable from less than 100ms to about 5 seconds. The output of the envelope shaper is fed to the control input of a voltage controlled amplifier (VCA) via buffer stage.

A simple noise generator feeds a bandpass filter which in turn feeds the input of the VCA. The bandpass filter is tunable from a few hundred hertz to more than 10kHz, and therefore gives considerable control over the sound produced by the unit. The bandwidth of the filter can be varied from a very broad response to a very sharp peaky response by means of the Q control, and again, this permits the output sound of the unit to be varied greatly.

If we now consider the full circuit diagram of the Synwave (Figure 2); C1, R1, D1, D2, and R2 process the trigger signal so that on its rising (positive) edge a brief positive pulse of about 7 volts in amplitude is supplied to the base of TR1. TR1 and TR2 form a Darlington pair emitter follower the brief input pulse to TR1. R3 and RV1 provide a discharge path for C2, and the setting of RV1 determines the discharge time of C2 (and therefore the length of the output signal).

If crystal microphone X1 is subjected to strong vibrations it will give an output level of several volts peak to peak, and positive going output half cycles will result in C2 being rapidly charged. The output signal level and hence the charge produced on C2 depends on how hard the unit or the drum

to which it is attached is struck, and this gives a degree of touch sensitivity.

The signal across C2 must be only lightly loaded or the decay time will be greatly shortened by the charge current leaked away through the loading circuit. TR3 is therefore used as an emitter follower buffer stage which couples the output from C2 to the control input of the VCA. The VCA uses a CA3080 transconductance amplifier, and it gives a level of gain that is proportional to the control voltage. The output signal thus rises rapidly to its peak level, and then decays relatively slowly, in sympathy with the envelope voltage across C2. The output of the VCA is coupled to the output socket by way of volume control RV2. Dual balanced supplies are required by the VCA circuitry and a central 0V rail is effectively produced by R10, R11 and C5.

TR5 is used as the noise generator and R18 applies a reverse bias to its base-emitter junction. This junction behaves rather like a Zener diode and like a Zener diode produces noise spikes. This arrangement is preferable to using a Zener diode though, as it gives a higher output at audio frequencies. The high frequency output of the noise generator is


PARTS COST  
GUIDE  
£12.25



excessive, and so C11 is used to give high frequency attenuation to correct this.

A twin T filter is used as the basis of the bandpass filter, but as a twin T network gives a notch at its centre frequency rather than a peak, the filter network is connected to give negative feedback over a common emitter amplifier. This amplifier features TR4 in a conventional configuration. TR4's emitter circuitry enables a certain amount of negative feedback to be applied to the amplifier and the amount of feedback is controlled by RV4 at or near the lower track connection there is little or no feedback; giving the circuit a high Q value and a narrow, peaky response. Moving the wiper of RV4 towards the upper end of its track gives increased feedback and a consequent reduction in Q together with a broader, flatter response.

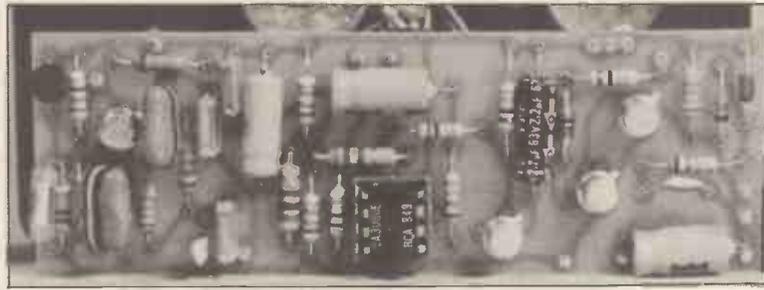RV3 is part of the twin T network, and varying the setting of this component alters the centre frequency of the filter. Ideally all three resistive elements in the filter should be varied when tuning the filter, but this is not really



Completed circuit board.

practical. This simple system works quite well though, and the only minor drawback is that the Q of the filter varies somewhat with changes in the setting of the pitch control. At some settings of RV3 it may be found that setting RV4 for a very high Q causes the filter to oscillate at its centre frequency. If desired, this can be avoided by adding a resistor of about 150 ohms in value between the positive terminal of C9 and the upper track connection of RV4. However, as this would limit maximum Q available, especially at the highest and lowest pitch control settings, it would reduce the effectiveness of the unit and is not really worth while.

C13 is needed to prevent the filter becoming unstable due to

stray high frequency feedback. C4 couples the output of the filter to the input of the VCA. The current consumption of the circuit is only about 1.5mA., or a little higher than this when it is triggered.


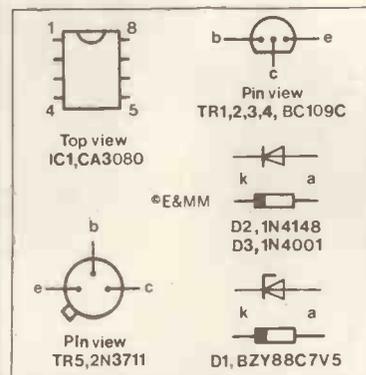


Figure 2. The circuit diagram of the Synwave.

## Construction Details

Except for C9 all the resistors, capacitors, and semiconductors are fitted onto a printed circuit board. Fit the semiconductors last, and make quite sure that the electrolytic capacitors and semiconductors are connected the right way round. The printed circuit board fits into the mounting rails of the specified case, but this leaves insufficient room for leads to be taken around the board to the controls, battery clip, microphone, and sockets. This makes it necessary to fit Veropins to the board at the points where it connects to these components, or if preferred, these leads can simply be soldered direct to the copper tracks. Details of the printed circuit board are provided in Figure 3.

The removable lid of the case is used as the rear panel in this application, and the two sockets are mounted on this panel. The front panel is drilled to take the four potentiometers and the microphone is mounted on the right side of the case (as viewed from the front). The microphone is

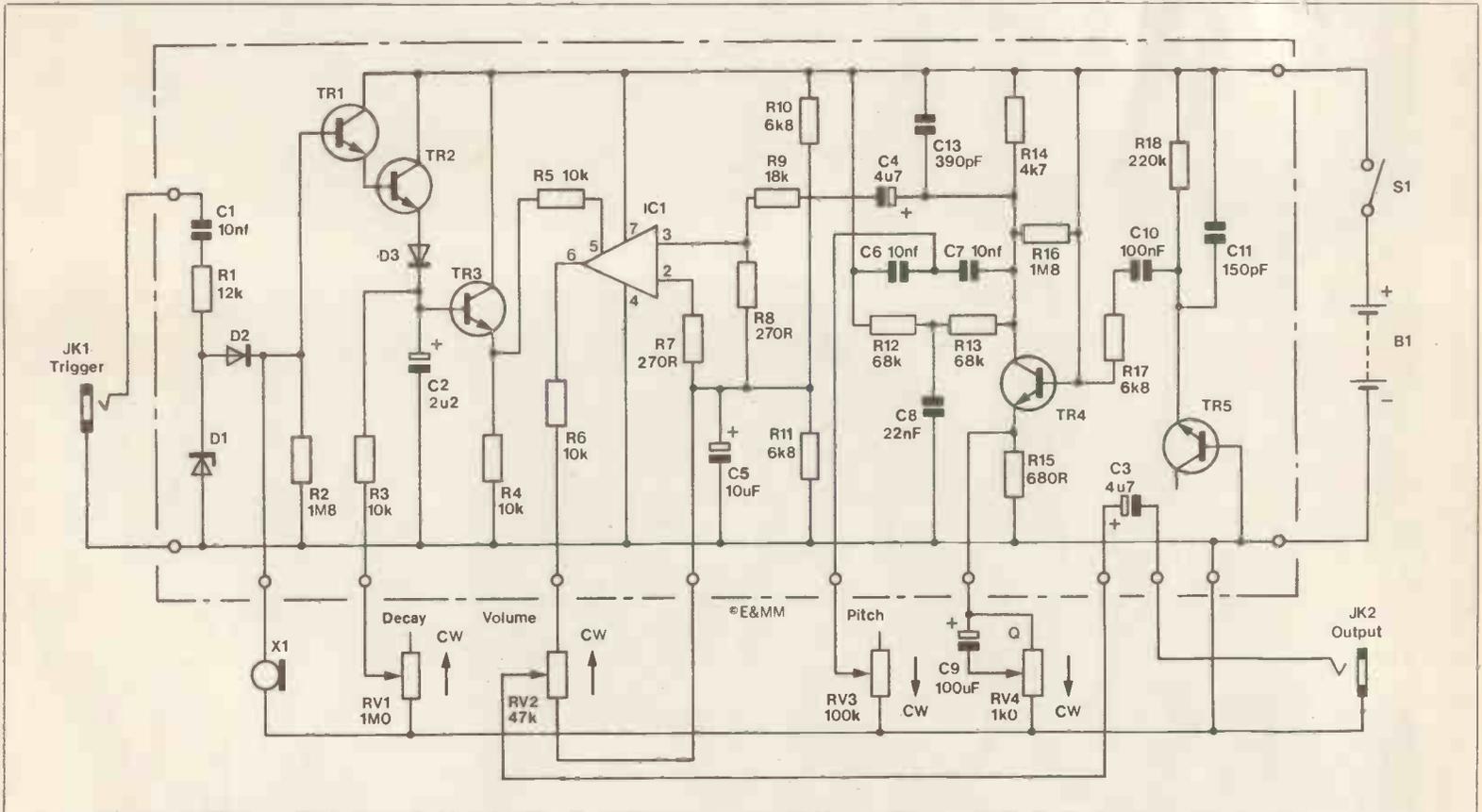

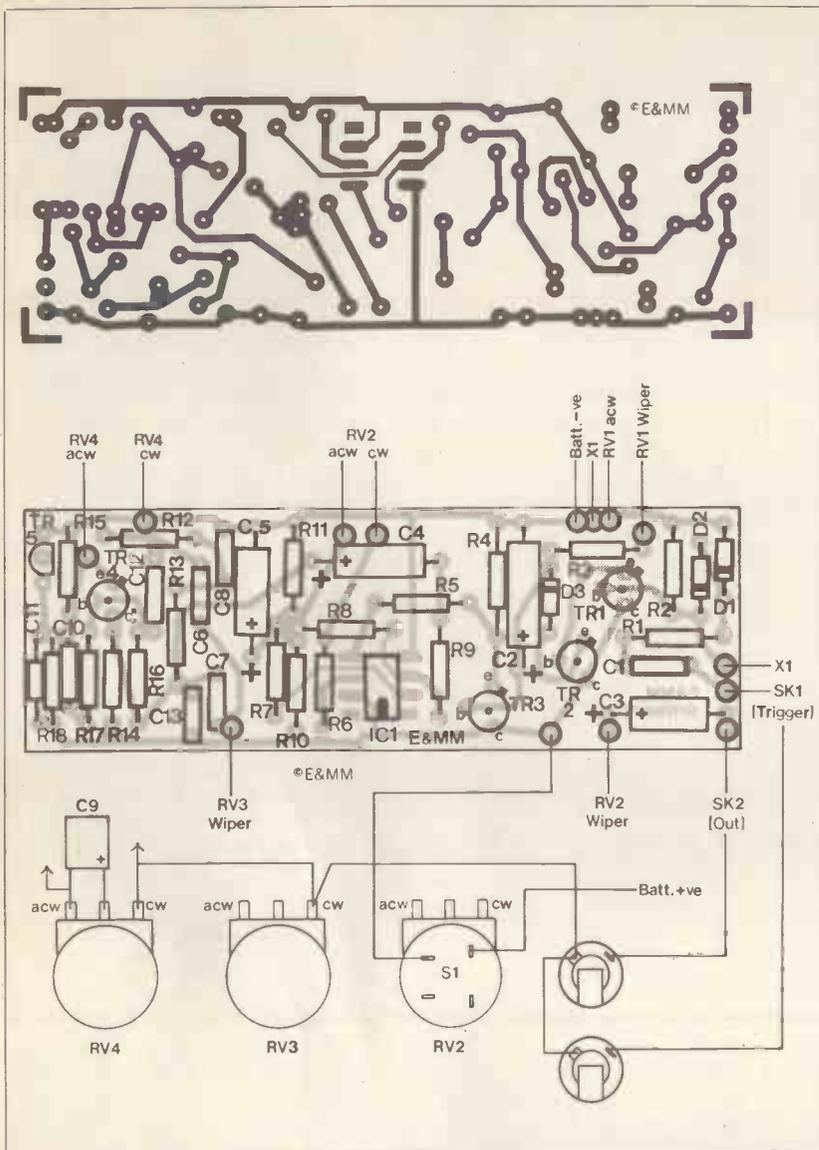


Figure 3. PCB track, component layout and wiring details.


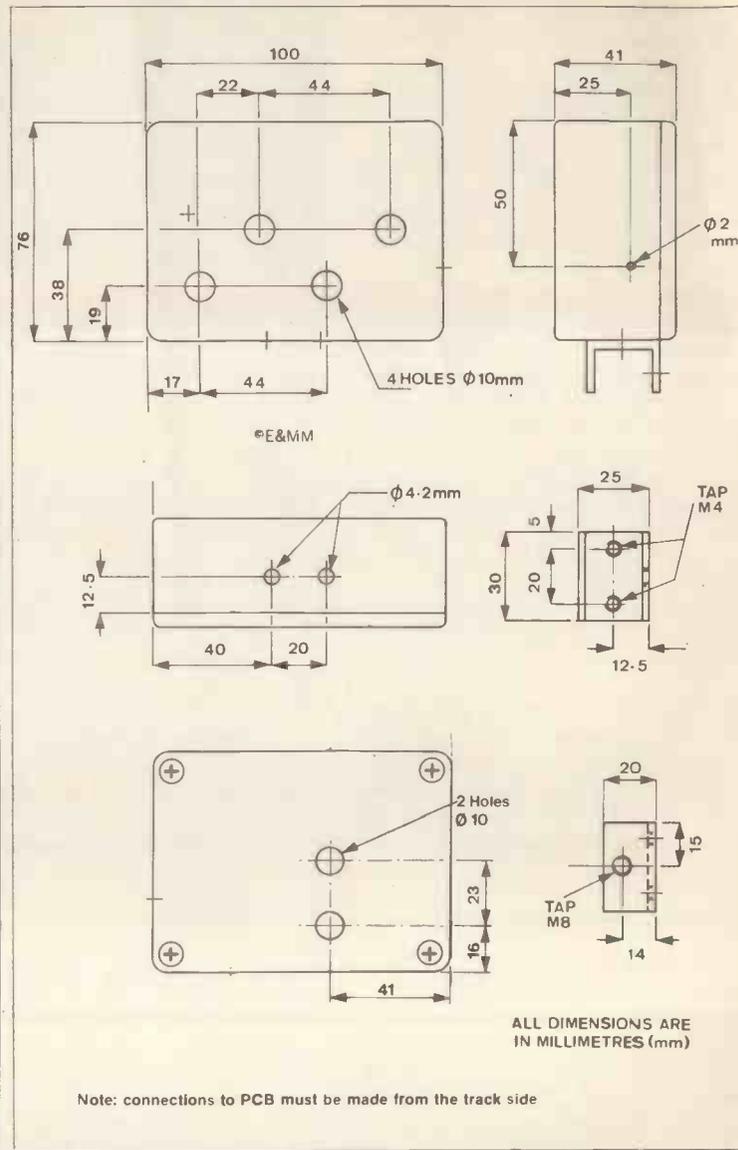


Figure 4. Case and bracket construction.

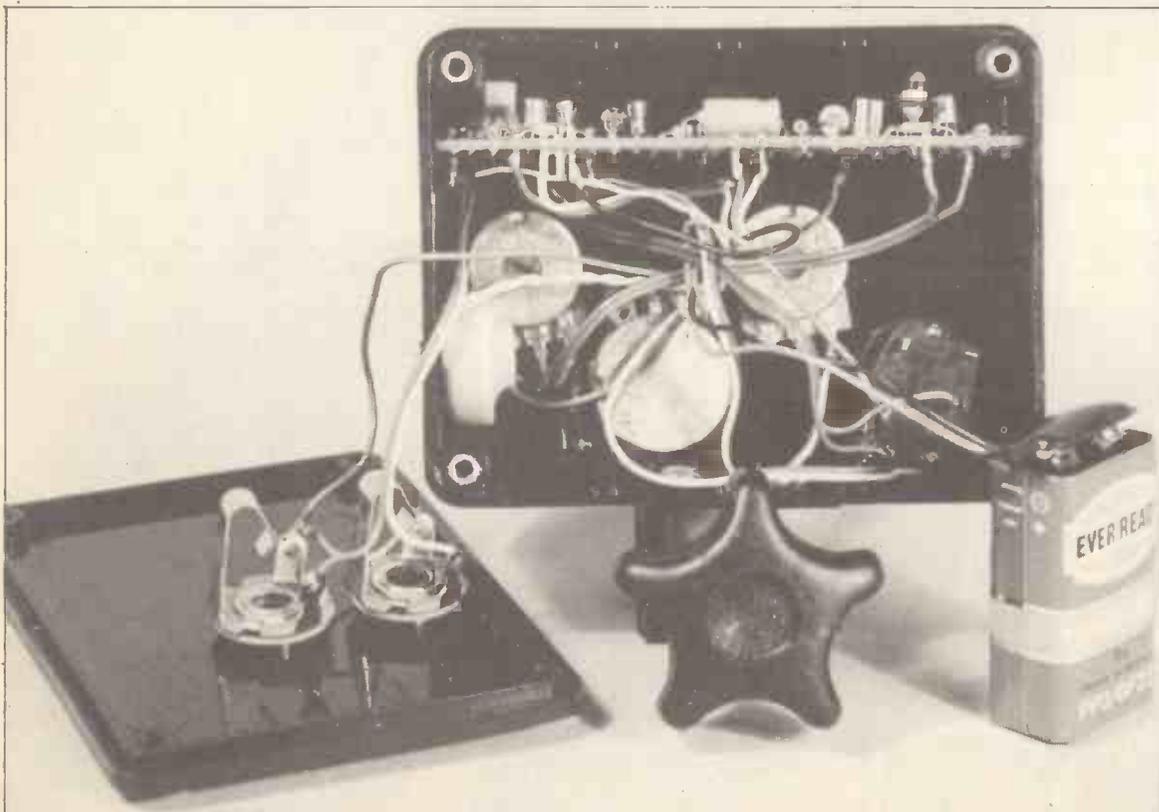

Synwave with wiring completed and PCB board inserted in case.

actually a crystal earphone having the earpip unscrewed. The small screw at the rear of the earphone is removed, and this is then used to fix the earphone to the case. Figure 4, shows the drilling of the case, and it is advisable to follow this as accurately as possible since there is not a great deal of excess space inside the case and it might otherwise be found that all the parts cannot be fitted into the case.

Next C9 is connected to RV4 and the other wiring to the off-board components is completed. Figure 3 gives details of all this wiring. The printed circuit board fits into the upper set of mounting rails in the case with the component side uppermost. The battery fits vertically into the case in the space between the two sockets and the microphone. A piece of foam material can be glued to the rear panel of the case to keep the battery firmly in place.

If the Synwave is to be fitted onto a drum it is necessary to fit the unit with a mounting bracket. This can consist of a piece of

25mm aluminium channel section which is fixed to the case using a couple of 6mm M4 bolts. A large bolt is used to clamp the Synwave onto the drum, and the bracket is drilled and threaded on one side to take this bolt. A handwheel bolt is ideal for use in this application, but an ordinary type can be used of course. It is advisable to fit a small pad of rubber on the part of the bracket opposite the mounting bolt as this will help to prevent the rim of the drum from becoming scratched when the Synwave is fitted in place.

To complete your project use our smart brushed aluminium panel with electric blue legend and sticky back as shown.

## Testing and Use

Connect the Synwave to an amplifier via SK2 and switch on with the Volume control set to midway. Set Decay to maximum, Pitch to minimum and Q to midway. Give the unit a sharp tap or use a suitable trigger signal (applied to SK1) and a 'seawave' should be heard.

Using short Decay and high Pitch and Q, the woodblock sound can be obtained. Cymbal effects require high Pitch and Q with slightly longer Decay.

## PARTS LIST

Resistors — all 1/2 watt 5% unless specified

R1	12k	2 off	(M12K)
R2,16	1M8 (10%)	4 off	(M1M8)
R3,4,5,6	10k	2 off	(M10K)
R7,8	270R	2 off	(M270R)
R9	18k	2 off	(M18K)
R10, 11,17	6k8	3 off	(M6K8)
R12,13	68k	2 off	(M68K)
R14	4k7		(M4K7)
R15	680R		(M680R)
R18	220k		(M220K)
RV1	1M lin. pot.		(FW08J)
RV2	47k log. pot. with switch		(FW65V)
RV3	100k lin. pot.		(FW05F)
RV4	1k lin. pot.		(FW00A)

### Capacitors

C1	10n ceramic plate		(WX77J)
C2	2u2 63V axial electrolytic		(FB15R)
C3,4	4u7 63V axial electrolytic	2 off	(FB18U)
C5	10u 25V axial electrolytic		(FB22Y)
C6,7	4n7 polycarbonate	2 off	(WW26D)
C8	10n polycarbonate		(WW29G)
C9	100u 10V PC electrolytic		(FF10L)
C10,12	100n polyester	2 off	(BX76H)


C11	150p polystyrene		(BX29G)
C13	390p ceramic plate		(WX63T)
<b>Semiconductors</b>			
IC1	CA3080, 8-pin, DIL		(YH58N)
TR1,2,3,4	BC109C	4 off	(QB33L)
TR5	2N3711		(QR34M)
D1	BZY88C7V5		(QH11M)
D2	1N4148		(QL80B)
D3	1N4001		(QL73Q)

### Miscellaneous

X1	Crystal earpiece		(LB25C)
SK1,2	Mono jack socket (open type) 2 off		(HF91Y)
	Case MB2		(LH21X)
	Handwheel bolt		(YL23A)
	M4 6mm bolts		(BF33L)
	Printed circuit board		(GA35Q)
	PP3 connector		(HF28F)
	PP3 battery		
B1	1mm Veropins		(FL23A)
	Knobs	4 off	(YG40T)
	Knob cap blue		(QY01B)
	Knob cap grey		(QY03D)
	Knob cap red		(QY04E)
	Knob cap yellow		(QY06G)
	Front panel		(BX99H)

In addition, the Q control can put the filter into oscillation and Pitch will then vary the frequency. Of course, this effect may not be desirable, especially as the volume increases substantially, and is simply removed by reducing the Q control or inserting a resistor as mentioned earlier.

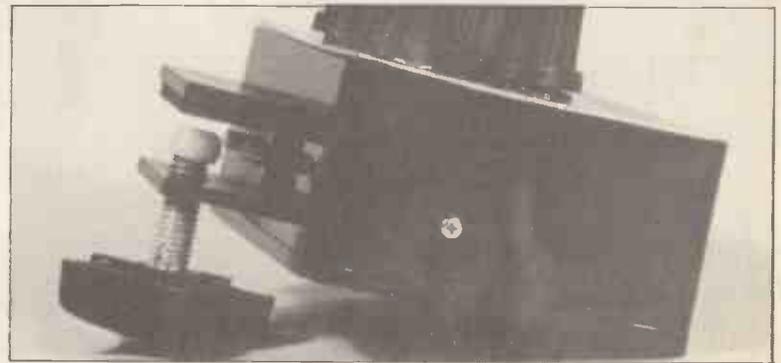A little experimentation with the controls will soon give an idea of the wide range of useful effects that can be produced. **E&MM**



Synwave external view with bracket.

### 3 CHANNEL SOUND/LIGHT CHASER

LB31000SLC £32.70



A high performance sound to light system which automatically switches to a chase when the music ceases. Super sensitive with an anti-interference circuit. The unit will operate from practically any amp and control up to 1,000W/channel. 5Hz to 70K. Controls: bass / mid / treble / master sensitivity / chase speed.

### 3 CHANNEL SOUND/LIGHT

LB31000SL £22.70



All the advantages of the SLC without chase. Controls: bass/mid/treble/master sensitivity.

### 2/4/8 CHANNEL CHASER

LB81000LC £28.00



An all logic chaser system for use with up to 8 channels at 1,000W each. Facilities include foot-switch trigger and module cascading (16, 24, 32 channel, etc.), chase speed and re-cycle delay.

### 4 CHANNEL SEQUENCER

LB41000LS £19.20



A 4 channel sequence generator for banks of lamps up to 1,000W per channel. Two speed controls, cross effect to provide settings between seconds and rapid burst.

### LBP42

£17.20

A four channel mixer and tone stage for mics, guitars, etc. Can be used with any LB amps. Set of pots £2.74.

### 3 CHANNEL DIMMERS

LB31000LD £16.20



Power dimmer units for the theatre / stage applications up to 1,000W per channel, with on board suppressing. The unit is also available without rotary pots for use with sliders — LB31000LD (no pots) £15.00. Sliders 75p each.

### STEREO DISCO MIXER/PREAMP

LBPA3 £33.70

M — Magnetic  
C — Ceramic



All the requirements of a stereo disco preamp on one board, left and right deck mixers/tones controls/mic mixer/tones/mic auto fade over decks/and P.F.L. The unit can be used with either LB100/150/250. Full set of pots — £8.63

### 3-WAY ACTIVE CROSSOVER

LBAC01 £17.90



Bass/mid/treble active crossover with stage booster! Available with crossover points of 200 or 300Hz, and 2K or 3KHz (please specify) LBPSU1 supply for LBAC01 (1 or 2).

LBPSU1 £7.20

### MINI MODULES

Ingeniously designed mini pre-amplifier building blocks for use in music and PA applications. You choose the type and number of units you require for your particular system and mount each module via its control direct onto your panel.  
LBMM1 Pre-amp for mics, guitars etc. LBMM2 Mixer for up to 6 LBMM1 2 3 4 5 LBMM3 Bass boost cut for either LBMM1 2 3 4 5 LBMM4 Mid-boost cut for either LBMM1 2 3 4 5 LBMM5 Treble boost cut for either LBMM1 2 3 4 5 LBPSU1 15V supply for up to 12 modules LBPSU2 15V regulated for up to 50 modules MM1 £4.50, MM2 £5.20, MM3 £5.70, MM4 £5.70, MMS £5.70, PSU1 £7.20, RPSU £14.50. Discount on MM1 2 3 4 5 10 to 24 20% 25 - 30%



### ROPE LIGHTS/DRIVER

LB41000LC-S £24.20



A four channel chaser up to 1,000W per channel, with a sound trigger facility. The music input signal modulates the speed of the chase giving an excellent sound/light effect. The unit will control up to 10 ropes with chase speed and trigger level control.

4 colour Ropes  
Red/yellow/green/blue  
6-metre length  
ROPE LIGHTS £45.40

### POWER AMPLIFIERS

Tough dealing power amps for use in sound systems. Open/short circuit protection and fused. Heavy gauge heatsinks and rugged o/p devices (all operate down to 4 ohms).

25W RMS	100W RMS	150W RMS	250W RMS
20Hz to 60K	5Hz to 25K	5Hz to 25K	5Hz to 25K
0.07% THD	0.1% THD	0.1% THD	0.1% THD
96DB S/N	110DB S/N	110DB S/N	110DB S/N
LB25	LB100	LB150	LB250
£11.20	£19.70	£29.20	£43.50

Note all models are available with either 500mV or 775mV sensitivity. Please state when ordering.

### POWER AMP POWER SUPPLIES

LB25PS	LB100PS	LB150PS	LB250PS
£11.20	£16.20	£19.00	£26.50
P/P £1.20	P/P £1.40	P/P £1.70	

### FOR GUITARS P.A. & DISCO



PIEZO HORNS £5.75 P/P 50p

### CELESTION LOUDSPEAKERS (ALL STANDARD CONE 8 OHMS)

G10-50	G12-65	G12-100	G15-100
(10in 50W)	(12in 65W)	(12in 100W)	(15in 100W)
£14.70	£20.70	£26.45	£36.45
P/P £1.70	P/P £1.70	P/P £1.70	P/P £2.00

Each module is manufactured from the highest quality components, fully tested, supplied with a connection and circuit diagram and guaranteed for twelve months. All prices shown are VAT inclusive. Please include 50p post packing except where individually stated. To mail order send cheque P.O. registered cash or Access number C.O.D. service £1 extra. For the new Autumn catalogue send 50p (full spec shown). Please note this company has no connection with LB Electronics of Hillingdon.



## L & B ELECTRONIC MODULES

PROFESSIONAL ENGINEERING BY PROFESSIONALS

45 Wortley Road, Croydon, Surrey CRO 3EB. Tel: 01-689 4138 DEPT. E&MM/7



# Starting Point

by Robert Penfold

PARTS COST  
GUIDE  
£6.10

## Voltage Regulators

As we have already seen in this series, a 9V battery has an output voltage that is nominally 9 volts but which is likely to vary between about 9.5 volts and 7.5 volts in practice, as the battery voltage tends to fall as the battery becomes exhausted. In many applications the fact that the supply voltage falls by about 2 volts during the working life of the battery is of little or no real consequence but there are occasions when a stable supply voltage is essential.

We have also seen how the voltage provided by a power source can vary due to variations in the load current, and the consequent voltage drop due to the internal resistance of the power source. Once again, this lack of voltage stability is often of little or no significance but sometimes it can cause malfunctions in circuits.

This month we shall consider some simple voltage regulator circuits and devices and the use of ordinary silicon diodes as voltage regulators will be considered first.

## Diode Regulators

In last month's article we saw how the current flowing through a silicon diode is practically zero until the forward bias reaches about 0.6 volts, and how only a very small increase in the bias voltage is then sufficient to produce a very high current flow (see Figure 3 of Starting Point Part 4). This characteristic enables a diode to be used in a simple voltage regulator circuit of the type shown in Figure 1.

Here D1 is forward biased from the input supply via R1, and a little over 0.6 volts (say nominally 0.65 volts) is developed across D1 and fed to the output. If the input voltage rises for some reason, the current flowing through R1 and D1 rises, causing D1 to conduct more heavily. This effective reduction in the resistance of D1 prevents the voltage developed across this component from more than marginally increasing, and most of the increased input voltage is developed across R1. If the input voltage should decrease for some reason, less current flows through R1 and D1, and D1 conducts less heavily. This effective increase in the resistance of D1 results in the

output voltage only decreasing marginally, with most of the decrease in the input voltage being reflected in the voltage drop across R1.

This stabilising effect also operates if the output current varies. A higher output current flow tends to tap-off some of the current that would otherwise have passed through D1, and its resistance therefore increases. This rise in resistance largely compensates for the decrease in load resistance at the output (bearing in mind that D1 and this load resistance are connected in parallel), and little change in output voltage results. If the output current is reduced, D1's resistance decreases and the output voltage remains virtually constant.


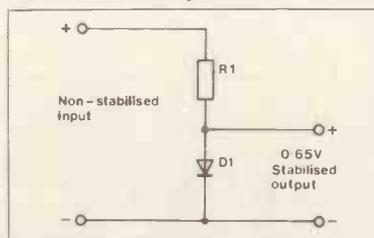


Figure 1. Silicon diode used in a simple shunt stabiliser circuit.

This type of regulator is known as a "shunt" regulator, and certain conditions must be met if it is to function effectively. Obviously the input voltage must be higher than the required output voltage. In fact the minimum input voltage must be high enough to give a current flow through R1 and D1 that is at least as high as the maximum output current that is required. If this is not the case, it is likely that R1 and the load will form a potential divider that takes the output voltage below the threshold voltage of D1, rendering D1 ineffective.

The required value for R1 is calculated using Ohm's Law, after first deducting 0.65 volts from the minimum expected input voltage to find the minimum expected voltage across R1. The maximum acceptable value for R1 is then equal to this voltage divided by the maximum output current required. A lower value is acceptable of course but this would make the current consumption of the circuit much higher than is really necessary if the value used was to be well below the calculated maximum acceptable value.

An obvious drawback to using

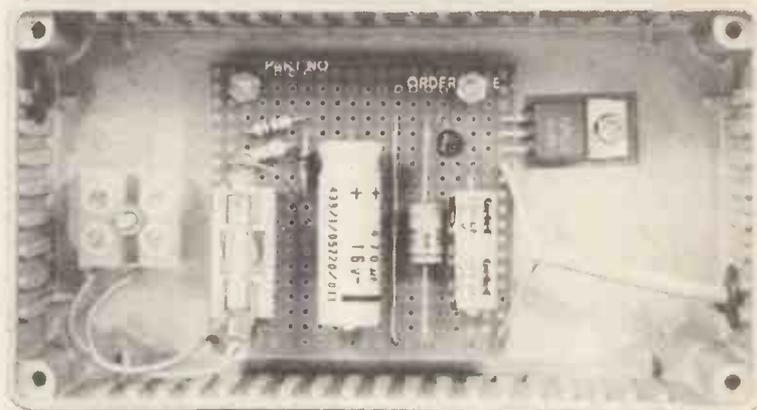

Car Cassette Power Supply.

a voltage regulator of the type shown in Figure 1 is that only a single output voltage of 0.65 volts is available; this is far too low to be of any use in most applications. One way of achieving higher and additional output voltages is to connect diodes in series, as shown in the circuit of Figure 2. This type of circuit operates in the same way as the basic circuit of Figure 1 but the threshold voltage of the series network of diodes is equal to the sum of the threshold voltages in the network. Thus in the circuit of Figure 2 there are three diodes, and the nominal output voltage is  $3 \times 0.65$  volts, or 1.95 volts in other words.

Of course, this type of circuit is

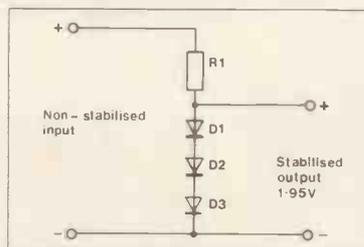


Figure 2. Example of a multiple diode shunt stabiliser circuit.

still rather limited with regard to the maximum output voltage that can be attained, since an impractically large number of diodes would be needed in order to achieve output potentials of more than about 3 volts.

## Amplified Diode

A transistor can be used in a simple low voltage shunt regulator using the arrangement shown in Figure 3, which is usually termed an "amplified diode" arrangement. The transistor used must be a silicon type and not germanium.

As we discovered last month, a silicon transistor does not conduct between its emitter and collector terminals until a forward

bias of about 0.6 volts is applied to its base-emitter junction. The base-emitter bias voltage only needs to exceed this threshold level slightly in order to make the device conduct heavily between the emitter and collector terminals.

If we assume that R2 and R3 have the same value, then about 1.2 volts will be needed at the collector of TR1 before this device begins to conduct, since R2 and R3 provide half the collector potential to the base of TR1. A slightly higher collector voltage is sufficient to bias the device hard into conduction, giving the "avalanche" effect needed to give stabilisation of the output voltage.

With R2 and R3 at the same value the nominal output voltage is 1.3 volts, but this can be reduced by making R2 lower in value, the minimum voltage available being 0.65 volts with R2 at zero. TR1 is then effectively being used as a silicon diode regulator. Higher voltages can be obtained by making R2 higher in value so that a higher collector voltage is needed before the base terminal is brought to the 0.6 volt

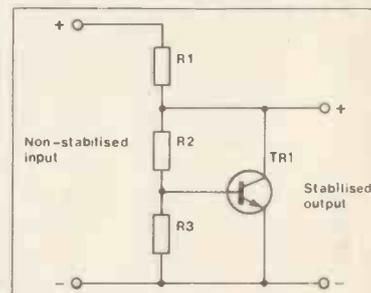


Figure 3. An 'amplified diode' regulator circuit using an NPN transistor.

threshold level. However, the higher the output voltage is made, the less efficient the circuit becomes and this type of circuit is not normally used if an output voltage of more than about 3 or 4 volts is required.

## Zener Diodes

Higher output voltages can be obtained using a special type of diode known as a "Zener" diode. This is used in exactly the same way as a silicon diode or an amplified diode, as can be seen from the circuit of Figure 4 (which also shows the circuit symbol for a Zener diode).

Note that the Zener diode is connected with the opposite polarity to a silicon diode employed as a shunt regulator. As a Zener diode is basically just an ordinary silicon diode, it will give an output voltage of only about 0.65 volts if it is connected with the wrong polarity. In the circuit of Figure 4 the Zener is reverse biased, but it will still conduct as the input voltage will exceed the reverse breakdown voltage of the component. At this breakdown voltage the resistance of the device suddenly drops from a figure of typically many hundreds of megohms to just a few tens of ohms, giving the avalanche effect and the required stabilisation of the output voltage.

Normal silicon diodes usually have quite high reverse breakdown voltages and the exact breakdown voltage will vary considerably from one device to another, it will even vary considerably between two devices of the same type. Zener diodes are designed to breakdown at relatively low voltages, and are marked with a value that indicates the breakdown voltage, usually with a tolerance of 5% on

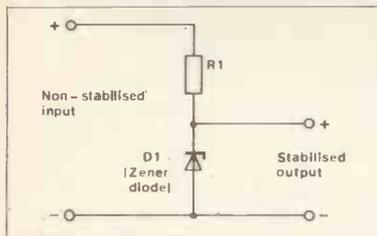


Figure 4. Zener diode shunt regulator circuit.

this figure. As the voltage developed across a Zener diode varies slightly with changes in the current passing through the device, the Zener voltage is usually specified at a certain current (5mA for instance, in the case of the popular BZY88 series of Zener diodes). The voltage developed across lower voltage Zeners (i.e. 5.6 volts and less) tends to vary significantly with changes in the current passing through the device, and these are not really suitable for use in circuits where a very high degree of stabilisation is required.

Zener diodes are available with operating voltages of between about 2.7 volts and 60 volts or so. Due to the lack of Zeners

having operating voltages below about 2.7 volts there is little alternative to using an amplified diode or silicon diodes when such a voltage is required. Even at potentials of around 3 volts, where suitable Zeners are available, it is more common for silicon diodes or an amplified diode to be used as the latter are more efficient in general.

## Series Regulators

A serious drawback of the shunt regulator in many applications is the fact that they have a constant current consumption that is at least as high as the maximum output current required. The regulator thus consumes a high current even if only a fairly modest output current is needed for the majority of the time, a high output current being required only occasionally and intermittently. This can lead to an unnecessarily short battery life in battery powered equipment and can result in the generation of substantial amounts of heat in medium and high power circuits.

This problem can be overcome by the use of a series regulator. As the name implies, this is connected in series with the load rather than in parallel with it and has a resistance which is self-adjusting to give a voltage drop that maintains the output voltage at the required level. Thus a perfect series regulator would not consume any current as the input current would be the same as that required by the circuit fed from the output of the unit. Practical series regulators do not quite achieve this, but usually have a current consumption marginally above that required by the load.

Figure 5 shows the simplest series regulator configuration. R1, D1 form a straightforward shunt regulator of the type described earlier, but the output is taken via a transistor which is connected in series with the load. TR1 is used in what is generally called the "emitter follower" mode but is sometimes given the alternative name of "common collector" mode.

TR1 does not provide any voltage gain from the input at its base to the output at its emitter, there is in fact a small voltage drop of about 0.6 volts or so from the base to the emitter (assuming a silicon device is used); this being the base to emitter voltage needed to bias the device into conduction. The output is therefore stabilised at about 0.65 volts below the operating voltage of D1.

Although TR1 provides no voltage amplification, it does of course give current amplification and only a small base

current will be drawn by the shunt regulator even if a substantial output current is taken from TR1's emitter terminal. For example, if TR1 has a current gain of one hundred and the shunt regulator can provide an output current of 1mA, an output current of 100mA could be drawn from the emitter of TR1 before the 1mA output capability

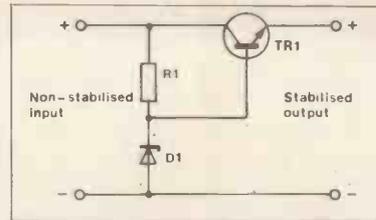


Figure 5. Simple series regulator using an emitter follower stage.

of the shunt regulator became exceeded and the output voltage dropped significantly. The circuit would then consume a current equal to the output current drawn from the unit, plus the 1mA required by the shunt regulator section of the unit. A shunt regulator with no series element would need to have a continuous current drain of at least 100mA.

Where very high output cur-

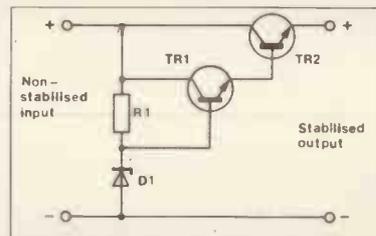


Figure 6. Series regulator using a Darlington pair.

rents are required (a few hundred milliamps or more) it is quite common for the circuit configuration of Figure 6 to be employed. This is basically the same as the arrangement of Figure 5, but the output of the emitter follower stage is fed to the input of a second emitter follower. The two transistors form what is called a "Darlington Pair", and together they effectively form a single transistor having a current gain equal to the product of the current gain of the two devices. This enables high output

currents to be obtained with good regulation and only a low current through shunt regulator part of the circuit.

## Car Cassette Power Supply

The construction project for this month is a simple voltage regulator circuit that enables a cassette recorder or radio which requires a 6V supply to be powered from a 12V car battery. This method of powering a radio or cassette unit that is to be used in a car or boat eliminates the need to buy expensive batteries which tend to be short-lived, especially in the case of cassette units. The unit can easily be modified to give an output potential of 7.5 or 9 volts if required, as will be explained in detail later.

In this application, where a well stabilised output is not required (bearing in mind that the voltage provided by a battery varies considerably during its life-span), it may seem that a voltage dropper resistor in series with the supply is all that is required. This is not in fact the case. The voltage dropped across this series resistor would depend on the supply current, as we know from Ohm's Law, but the supply current is an unpredictable quantity and may well vary considerably from one instant to the next. A voltage regulator circuit is therefore required.

The circuit diagram of the car cassette power supply unit is shown in Figure 7. R1, D2 form a shunt stabiliser circuit having a nominal output potential of 7.5 volts. Zener diodes tend to give the output voltage that contains small, rapid, and random changes in voltage. This "noise" is obviously undesirable and is smoothed out by C2.

TR1 is the emitter follower buffer stage, and this is a Darlington device (i.e. two transistors connected as a Darlington pair and contained in a single package). The emitter of TR1 connects to the output by way of R2, which forms part of a simple current limiting circuit. The pur-

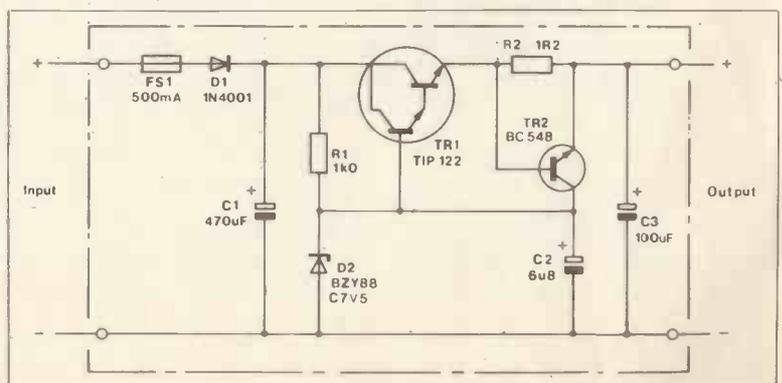


Figure 7. Circuit diagram of the car cassette power supply.



**SIMPLY AHEAD**  
and staying there



**ELECTRONICS LTD.**

The range grows bigger &  
bigger & bigger... **BETTER...**

**New Profile Amplifiers - Two New Series**



HY120

**MOSFET**

**CHOOSE AN I.L.P. MOSFET POWER AMP** when it is advantageous to have a faster slew rate, lower distortion at higher frequencies, enhanced thermal stability, the ability to work with complex loads without difficulty and complete absence of cross-over distortion. I.L.P.'s

exclusive encapsulation technique within fully adequate heatsinks has been taken a stage further with specially developed computer-verified 'New Profile' extrusions. These ensure optimum operating efficiency from our new MOSFETS, and are easier to mount. Connection is via five pins on the underside. **I.L.P. MOSFETS ARE IDENTICAL IN PERFORMANCE TO THE COSTLIEST AMPLIFIERS IN THIS EXCITING NEW CATEGORY BUT ARE ONLY A FRACTION OF PRICES CHARGED ELSEWHERE.**

Model	Output Power RMS	Distortion Typical at 1KHz	Slew Rate	Rise Time	Signal/Noise Ratio DIN AUDIO	Price & VAT
MOS120	60W into 4-8Ω	0.005%	20V/μs	3μs	100dB	£25.88 + £3.88
MOS200	120W into 4-8Ω	0.005%	20V/μs	3μs	100dB	£33.46 + £5.02



HY60


**BIPOLAR**

(Standard O-P Transistors)

**CHOOSE AN I.L.P. BIPOLAR POWER AMP** where power and price are first consideration while maintaining optimum performance with hi-fi quality and wide choice of models. From domestic hi-fi to disco and P.A., for instrument amplification, there is


an I.L.P. Bipolar to fill the bill, and as with our new Mosfets, we have encapsulated Bipolars within our New Profile extrusions with their computer-verified thermal efficiency and improved mounting shoulders. Connections are simple, via five pins on the underside and with our newest pre-amps and power supply units, it becomes easier than ever to have a system layout housed the way you want it.

Model	Output Power RMS	Distortion Typical at 1KHz	Slew Rate	Rise Time	Signal/Noise Ratio DIN AUDIO	Price & VAT
HY30	15W into 4-8Ω	0.015%	15V/μs	5μs	100dB	£7.29 + £1.09
HY60	30W into 4-8Ω	0.015%	15V/μs	5μs	100dB	£8.33 + £1.25
HY120	60W into 4-8Ω	0.01%	15V/μs	5μs	100dB	£17.48 + £2.62
HY200	120W into 4-8Ω	0.01%	15V/μs	5μs	100dB	£21.21 + £3.18
HY400	240W into 4Ω	0.01%	15V/μs	5μs	100dB	£31.83 + £4.77

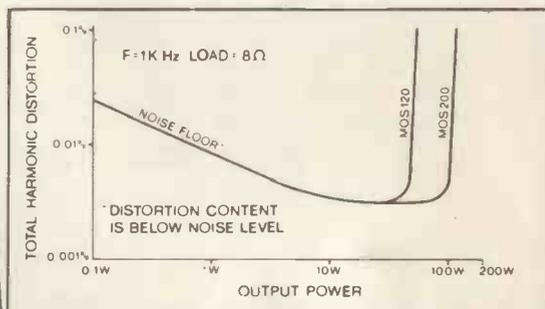

Load impedance both models 4Ω-∞ Input impedance both models 100KΩ  
Input sensitivity both models 500mV Frequency response both models 15Hz-100KHz - 3dB


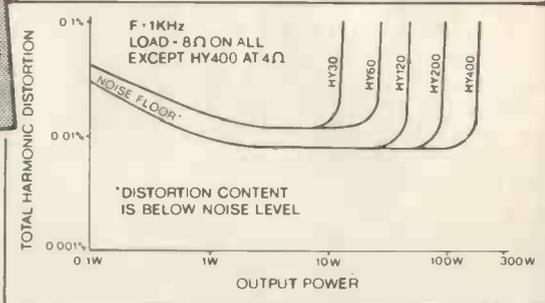
**I.L.P. POWER AMPS ARE ENCAPSULATED FOR THERMAL STABILITY AND LONGER LIFE**



Load impedance all models 4Ω-∞ Input impedance all models 100KΩ  
Input sensitivity all models 500mV Frequency response all models 15Hz-50KHz - 3dB

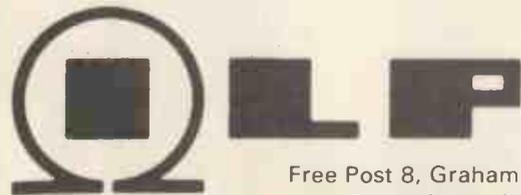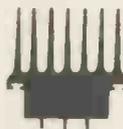**THE NEW PROFILE EXTRUSIONS**

The introduction of standard heatsink extrusion for all I.L.P. power amplifiers achieves many advantages:- Research shows they provide optimum thermal dissipation and stability. Slotted shoulders allow easy mounting; standardisation enables us to keep our prices competitive. Surfaces are matt black, anodised for higher thermal conductivity. Extrusions vary in size according to module number.



Electronics Ltd

Free Post 8, Graham Bell House,  
Roper Close, Canterbury

To: I.L.P. ELECTRONICS LTD, CANTERBURY CT2 7EP

Please supply .....

Total purchase price £ .....

I enclose Cheque  Postal Orders  International Money Order

Please debit my Access/Barclaycard Account No. ....

NAME .....

ADDRESS .....

Signature .....

DEPT. E&MM8

**ALL U.K. ORDERS  
DESPATCHED  
POST FREE**

pose of this circuit is to limit the maximum output current of the unit to a safe level in the event of a short circuit or serious overload at the output.

If the output current is about 0.5 amp or less, the voltage developed across R2 will only be about 0.6 volts (1.2 ohms x 0.5 amps = 0.6 volts), and TR2 will therefore have no significant effect on the circuit as this voltage is insufficient to bias it into conduction. There will be a small voltage drop across R2 that will reduce the output voltage when high supply currents are being drawn, but this voltage drop is not high enough to be of any consequence; this is something that happens with batteries as well due to their internal resistance.

If the current drawn from the unit should go much above 500mA the voltage developed across R2 will be sufficient to switch on TR2. This then tends to tap off some of the current through R1, sending it to the negative supply rail through the load connected across the output. This tends to pull the base terminal of TR1 lower in voltage, and thus reduces the output voltage as well. This gives the required current limiting action and, even with a short circuit across the output, an output current of only about 550mA would flow since TR2 would reduce the output voltage to practically zero.

FS1 protects the unit against damage if a short circuit should occur across the non-stabilised input for some reason. D1 simply protects the unit by blocking the supply if the input should be inadvertently connected with the wrong polarity. The 12 volt supply of a car is often polluted with a fair amount of electrical noise, these noise spikes are smoothed out by C1, C3 so that they do not appear at the output.

## Output Voltage

The output voltage of the unit under low-load conditions is equal to the 7.5 volts across D2 minus about 1.3 volts (0.65 volts x 2) dropped between the base and emitter of TR1, i.e. about 6.2 volts. This drops to a little under 6 volts under high-load conditions, this range of voltages is similar to those provided by 6 volt dry batteries under similar conditions.

If an output voltage of 7.5 volts is needed, this can be accomplished by changing D2 for a 9.1 volt component (a BZY88C9V1). For a 9 volt output D2 can be changed to a 10 volt Zener (a BZY88C10V). Although this will give an output voltage which is slightly less than that provided by

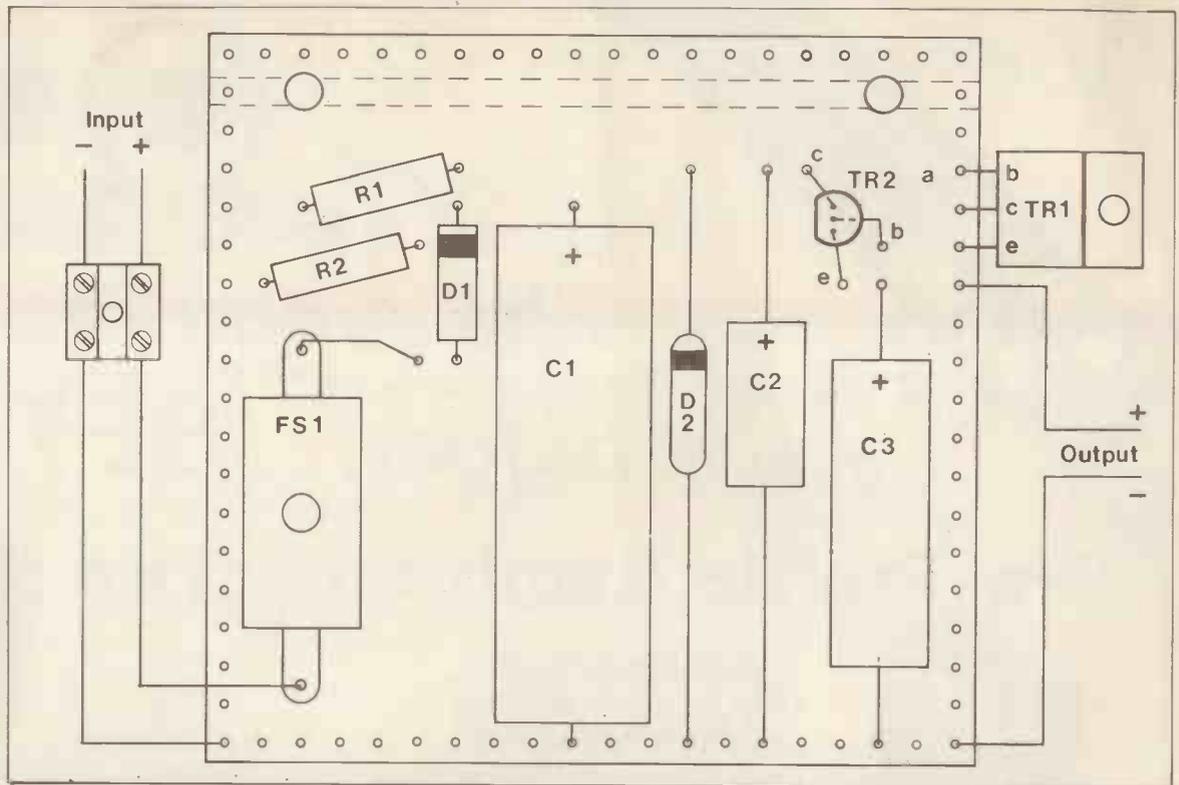


Figure 8. Veroboard layout for the car cassette power supply.

new, 9 volt, dry batteries, the output potential of about 8.7 volts is still well within acceptable limits.

## Construction

The suggested component layout is shown in Figure 8 and is based on a 0.1in. matrix Veroboard which has 19 copper strips by 20 holes. No cutting of the Verotrack is required. Construction of the board is carried out in the usual way but note that FS1 is mounted in a chassis mounting fuseholder; the latter is fitted on the component panel using a short M3 or 6BA bolt and fixing nut.

Under some circumstances TR1 has to dissipate a few watts of power, and the consequent heat generated will destroy the device unless some heatsinking is provided to enable it to lose this heat in the surrounding air at a suitably fast rate. A simple way of providing the necessary heatsinking is to build the unit in a metal case, then bolt TR1 to the case so that it acts as the heatsink. The prototype is housed in a diecast aluminium box (Maplin type DCM5004) but any metal case of similar dimensions (120 x 65 x 40mm) should be suitable.

In order to find the correct position for the mounting hole for TR1, first mount the completed component panel on the base panel of the case using M3 or 6BA fixings with 6.35mm spacers over the bolts in order to keep the connections on the underside of the board out of contact with the metal case. The leadout wires of

## PARTS LIST

### Resistors

R1	1k, ½ watt 5%	(M1K0)
R2	1R2, ½ watt 5%	(S1R2)

### Capacitors

C1	470u, 25V, axial	(FB73Q)
C2	6u8, 63V, axial	(FB21X)
C3	100u, 25V, axial	(FB49D)

### Semiconductors

TR1	TIP122	(WQ73Q)
TR2	BC548	(QB73Q)
D1	1N4001	(QL73Q)
D2	BZY88C7V5 (see text)	(QH11M)

### Miscellaneous

	Box, type DCM5004	(LH71N)
	Veroboard 0.1in. matrix	(FL08J)
FS1	500mA, 20mm, quick-blow	(WR02C)
	20mm, chassis-mounting fuseholder	(RX49D)
	Connector block	(HF01B)
	Insulating set for TR1	(WR23A)
	Power plug of appropriate type	
	Wire	(BL09K)
	Bolt 6BA, 1 inch	(BF07H)
	Nut 6BA	(BF18U)
	Spacer 6BA, ¼ inch	(FW34M)
	Grommet small	(FW59P)

TR1 are then carefully formed so that the metal pad on the underside of the component fits flat against the base panel of the case. The position of the mounting hole is then marked using TR1 as a template. The component panel is then removed so that the mounting hole for TR1 can be drilled safely.

One end of the case is drilled to take the input lead and the other end drilled to take the output lead. The input lead is taken to the component panel by way of a two-way terminal block. These blocks are normally only sold in twelve-way strips, it is therefore necessary to cut a two-way block from one of these using a modelling knife. The terminal



block is mounted on the base panel of the case beside the component panel using a 25mm 6BA or M3 bolt and matching fixing nut.

The output lead is terminated in a power plug of the type appropriate to the equipment to be supplied by the unit, be careful to connect the plug with the correct polarity. Normally the outer connector is negative and the inner connector is positive but it would be advisable to check this point with the operating manual for the equipment used with the unit, if this is possible.

When finally fitting the component panel and TR1 into place, TR1 should be fitted with an insulation set so that its heat-tab (which connects internally to its collector terminal) is electrically isolated from the case). The insulating set consists of a mica washer, which is placed between TR1 and the case, and a plastic bush which fits over the mounting bolt and into the fixing hole of TR1 so that the bolt is insulated from TR1.

As the case is electrically isolated from the supply circuit, and assuming that any exposed metalwork on the equipment supplied by the unit is also electrically isolated (which is invariably the case), the unit is suitable for use with both negative and positive earth systems.

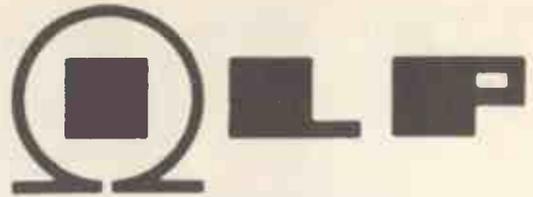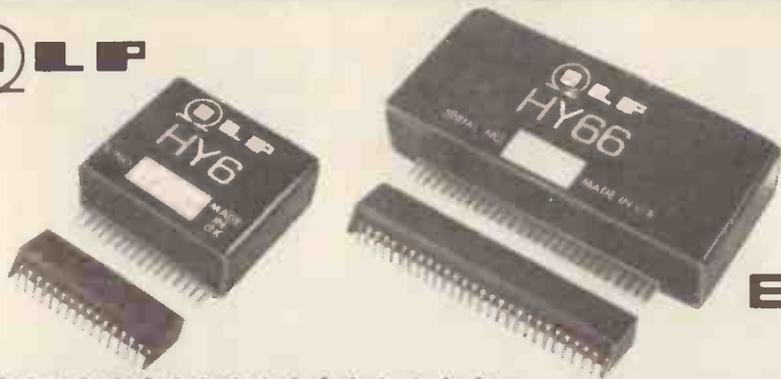The quiescent current consumption of the unit is only a few milliamps. This is not sufficient to warrant the fitting of an on/off switch or disconnecting the unit when it is not in use. E&MM



ELECTRONICS LTD.

## NEW PRE-AMPS

HY6 (mono) and HY66 (stereo) are new to I.L.P.'s range of advanced audio modules. Their improved characteristics and styling ensure their being compatible with all I.L.P. power-amps both MOSFET and BIPOLAR, giving you chance to get the best possible reproduction from your equipment. HY6 and HY66 pre-amps are protected against short circuit and wrong polarity. Full assembly instructions are provided. Mounting boards are available as below.

Sizes - HY6 - 45 x 20 x 40 mm. HY66 - 90 x 20 x 40 mm. Active Tone Control circuits provide  $\pm 12$ dB cut and boost. Inputs Sensitivity - Mag. PU. - 3mV; Mic - selectable 1-12mV; All others 100mV. Tape O/P - 100mV; Main O/P - 500mV; Frequency response - D.C. to 100KHz - 3dB.


HY6 mono £6.44 + 97p VAT Connectors included

HY66 stereo £12.19 + £1.83 VAT Connectors included

B6 Mounting Board for one HY6 78p + 12p VAT

B66 Mounting Board for one HY66 99p + 15p VAT

COMPATIBLE WITH ALL I.L.P. MODULES

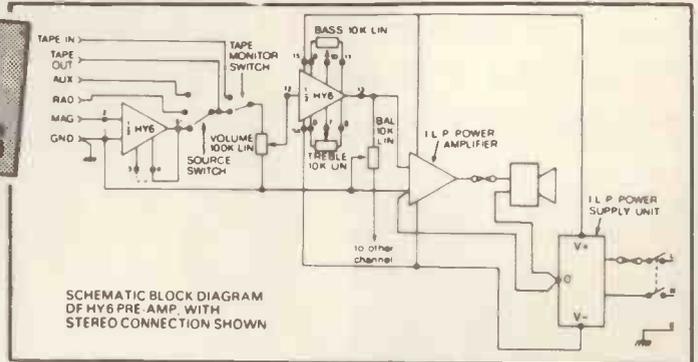

- DISTORTION TYPICALLY 0.005%
- S/N RATIO - 90dB (Mag. P.U. - 68 dB)
- 38 dB overload margin on Mag. P.U.

- LATEST DESIGN HIGH QUALITY CONNECTORS
- ONLY POTS, SWITCHES AND PLUGS/SOCKETS NEED ADDING
- NEEDS ONLY UNREGULATED POWER SUPPLY  $\pm 15$  to  $\pm 60$ v

NO QUIBBLE  
5 YEAR GUARANTEE  
7-DAY DESPATCH  
ON ALL ORDERS  
BRITISH DESIGN &  
MANUFACTURE  
FREEPOST SERVICE



PSU

IN A RANGE OF 11 MODELS USING LATEST TOROIDAL TRANSFORMERS

## NEW POWER SUPPLY UNITS

1971-1980  
TEN YEARS OF PLANNED  
PROGRESS

Of the eleven power supply units which comprise our current range, nine have toroidal transformers made in our own factory. Thus these I.L.P. power supply units are space-saving, more efficient and their better overall design helps enormously when assembly building. All models in the range are compatible with all I.L.P. amps and pre-amps with types to match whatever I.L.P. power amps you choose.

When, in 1971, Ian L. Potts founded his now world-famous company, he saw the need for a different and more rational approach to exploiting to the full, the potential that lay in modular construction. New thinking was badly needed. The result was a range of modules revolutionary in concept. The rightness of this new thinking is shown by the size of the company today, its new factory, its vast exports, its acceptance by constructors as the modules to build with. The range grows bigger and better. Exciting new lines (in no way conflicting with existing ones) are well past drawing board stage. This is why I.L.P. are simply ahead and staying there.

- PSU30  $\pm 15$ V at 100mA to drive up to 12 x HY6 or 6 x HY66 £4.50 + 0.68p VAT
- THE FOLLOWING WILL ALSO DRIVE I.L.P. PRE-AMPS
- PSU36 for use with 1 or 2 HY30's £8.10 + £1.22 VAT
- ALL THE FOLLOWING USE TOROIDAL TRANSFORMERS
- PSU50 for use with 1 or 2 HY60's £10.94 + £1.64 VAT
- PSU60 for use with 1 HY120 £13.04 + £1.96 VAT
- PSU65 for use with 1 MOS120 £13.32 + £2.00 VAT
- PSU70 for use with 1 or 2 HY120's £15.92 + £2.39 VAT
- PSU75 for use with 1 or 2 MOS120 £16.20 + £2.43 VAT
- PSU90 for use with 1 HY200 £16.20 + £2.43 VAT
- PSU95 for use with 1 MOS200 £16.32 + £2.45 VAT
- PSU180 for use with 1 HY400 or 2 HY200 £21.34 + £3.20 VAT
- PSU185 for use with 1 or 2 MOS200 £21.46 + £3.22 VAT

BRITAIN'S FOREMOST QUALITY MODULE SUPPLIERS

### ★ Freepost facility

When ordering or writing about I.L.P. products, you do not need to stamp the envelope. Mark it FREEPOST plus the code shown in the address below. We pay the postage for you.

★ TO ORDER Send cheque or money order payable to I.L.P. Electronics Ltd and crossed. Or pay by ACCESS or BARCLAYCARD. Cash payments must be in registered envelope; if C.O.D. payment is wanted, please add £1.00 to TOTAL value of order.

To: I.L.P. ELECTRONICS LTD, CANTERBURY CT2 7EP

Please supply .....

Total purchase price £ .....

I enclose Cheque  Postal Orders  International Money Order

Please debit my Access/Barclaycard Account No. ....

NAME .....

ADDRESS .....

Signature .....

DEPT. E&MM8



Electronics Ltd

Free Post 8, Graham Bell House,  
Roper Close, Canterbury

ALL U.K. ORDERS  
DESPATCHED  
POST FREE

# THE MATINÉE ORGAN

A complete electronic organ to build at low cost

## PART 5: Cabinet construction; lower manual and rhythm generator circuits

If you wish to make your own cabinet, cutting details and requirements are given in Table 6. Construction details are shown in Figure 36. Fix the swell pedal to the baseboard before starting to put the panels together. The cabinet can now be completed except for the top and the back. The ready-made cabinet comes complete with a roll-top that runs in plastic guide slots fitted into routed out slots in the cabinet sides. The roll-top and guide slots are available separately for those who wish to make their own cabinet but since few constructors have access to routing machinery, it is not easy to fit and we have not shown details in the construction drawing.

If you use the guide slots you will need to cut off the forked end 465mm from the closed end and let them into the sides of the cabinet. Also, the dropped front of the top will need to be shortened. Alternatively, another inner side-piece could be fitted, on whose edge the roll-top would run and in this case it will be necessary to widen the whole cabinet slightly. However, if you feel the roll-top is essential, we strongly recommend using the ready-made cabinet.

### Fixing the Organ in the Cabinet

Install the trim and housing around the swell pedal, then fix the pedalboard and bolt the loudspeaker to the baffle board. If making your own cabinet, this is a suitable time to fit the grille cloth. Remove the transformer fixing bolts and place the PSU module in position on the base. Mark the four holes and drill through the base using a 4mm or 5/32in. drill. Note that these are the only four fixings that are not provided in the ready-made cabinet due to variations in the transformer frame size.

Screw down the terminal block as shown in Figure 12. Fix the P-clip to the 3-core mains cable and screw down near the terminal block. Fix the reverb spring-line, using the rubber couplings, either to T-nuts fitted in the ready-made cabinet or as shown in Figure 36.

Place the keyboard roughly in position. Remove the screws supplied with the keyboard assembly from where they are fitted in the top of the keyboard cheek mounting supports. Placing the keyboard cheeks in position now determines the exact position for the keyboard. Carefully remove the cheeks, screw down the keyboard and refit the cheeks screwing down from above. Hinge up the top keyboard and remove the screws in the frame. Place the keyboard separator in position and screw up.

Push the mains switch into the pre-cut hole in the side cheek and carefully reconnect the wires. Fix the metalwork (supplied with cabinet kit), as shown in Figure 37. The screws into the sides of the cabinet should not be tightened to allow for adjustment when the PCB and front panel are in position.

Since describing the main PCB construction in Part 3 we have discovered that it is much easier to put the drawbars to-

gether before soldering the slide pot to the PCB. Put the M3 bolts through the frame after placing one of the special 4BA washers under the head of the bolt through the slot as shown in Figure 38. Hold the unit upside-down and place four of the special washers on each bolt; then place the slide pot upside-down over the bolts, align and screw up. Now solder the whole assembly to the main PCB.

Snap the latchbuttons onto the latchswitches. S16, 24 and 33 are red, S22, 23, 34 and 35 are grey, S26 and 27 are white and the remainder are black. Cut the shafts of the rotary pots to 22mm long. Bolt the PCB onto the metalwork, then pull the covers off the rocker tablets S17 to 21 to enable the front panel to be fitted.

Fit the LED holders to the front panel then snap the LEDs into the clips from behind. The red LED fits in the 'Downbeat' hole and the green LED in 'Tempo'. Push the drawbars fully back, then fit the front panel and bolt up to the metalwork. Carefully re-align the metalwork frame then remove the front panel and PCB and tighten up the end screws.

Re-fix the main PCB and reconnect all the cables. Bolt the headphone socket to the front

panel, then refit the front panel. Replace the covers on the rocker tablets. S17 and 18 are grey, S19 is orange and S20 and 21 are red. Push the three knobs onto the shafts of the rotary pots. Double-check that all plugs and sockets are correctly connected. If using the ready-made cabinet kit, fit the roll-top as described in the instructions supplied with the kit. Fix the top and the back to the cabinet. The Matinée organ is now completed.

### Lower Manual Circuits

Figure 39 is the circuit diagram of the lower manual. In Part 4 we described the circuits around the lower manual M108 and this is now continued. There are eight signal outputs from the M108, all connected to quad op-amps IC5 and 6 that are used to raise the signal levels. The footages are connected through CMOS switches, IC8 and 10 to the appropriate flute and string fil-



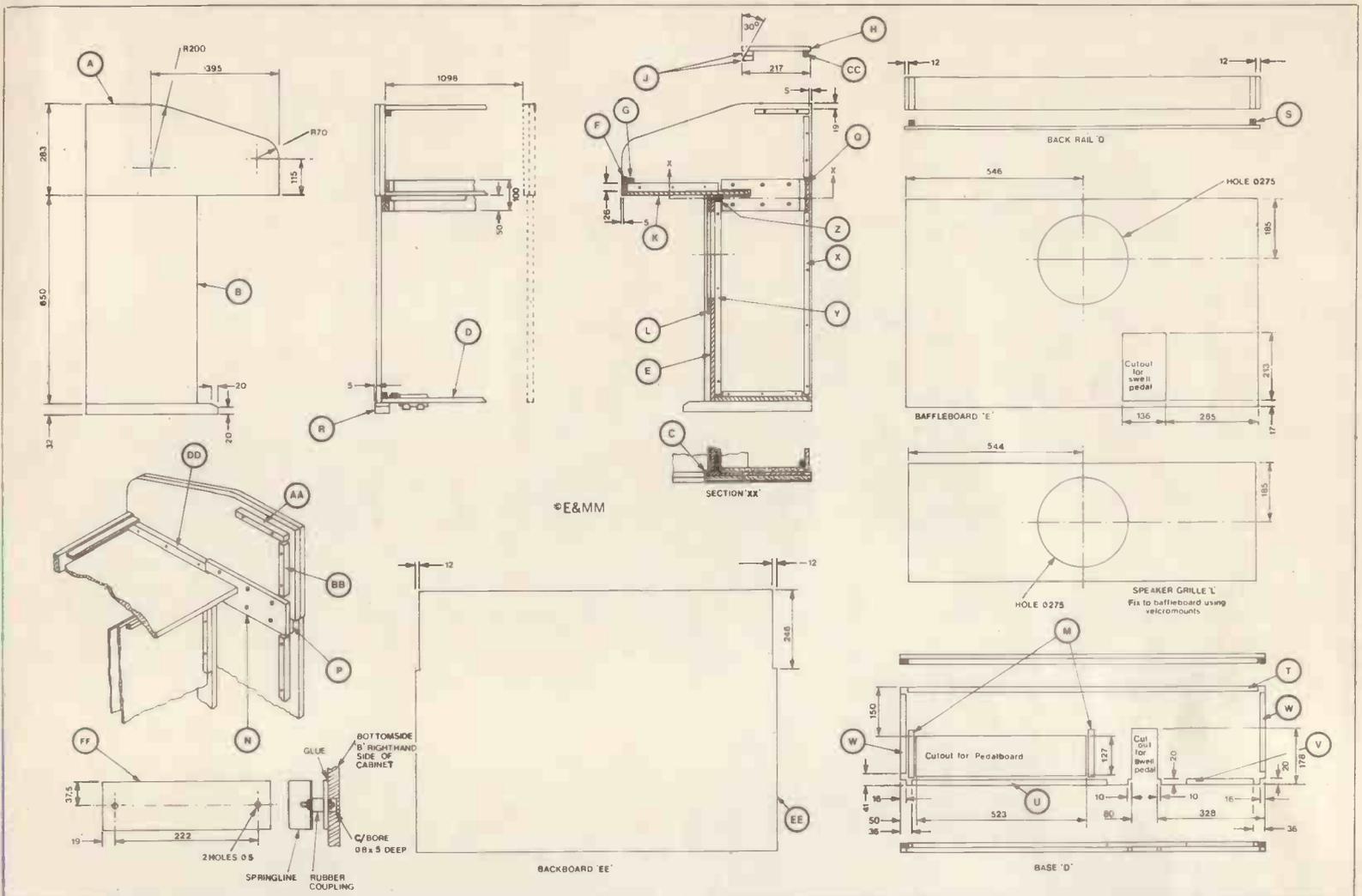


Figure 36. Cabinet construction details.

Part	Name	Material	Size (mm)	Qty
A	Topside	15mm Chipboard	595 x 283	4
B	Bottomside	15mm Chipboard	650 x 340	2
C	Thickening Strip	15mm Chipboard	650 x 50	2
D	Base	15mm Chipboard	1122 x 305	1
E	Baffle Board'	15mm Chipboard	1092 x 650	1
F	Front Rail (1)	15mm Chipboard	1098 x 56	1
G	Front Rail (2)	15mm Chipboard	1098 x 22	1
H	Top	15mm Chipboard	1098 x 220	1
J	Top Front Runner	15mm Chipboard	1098 x 35	2
K	Keyboard Shelf	12mm Chipboard	1098 x 380	1
L	Speaker Grille	6mm Plywood	1088 x 370	1
M	Pedalboard Spacer	6mm Plywood	150 x 20	2
N	Side Joint	12mm Plywood	267 x 100	2
P	Side Thickening Strip	12mm Plywood	267 x 50	2
Q	Back Rail	15mm Plywood	1098 x 100	1
R	Foot	Hardwood	405 x 32 x 43	2
S	Batten	18mm Square	100	2
T	Batten	18mm Square	1080	1
U	Batten	18mm Square	600	1
V	Batten	18mm Square	205	1
W	Batten	18mm Square	244	2
X	Batten	18mm Square	579	2
Y	Batten	18mm Square	626	2
Z	Batten	18mm Square	1050	1
AA	Batten	18mm Square	172	2
BB	Batten	18mm Square	190	2
CC	Batten	18mm Square	1056	1
DD	Batten	18mm x 26mm	285	2
EE	Backboard	3mm Hardboard	1122 x 814	1
FF	Springline Mount	6mm Plywood	260 x 75	1

Table 6. Cabinet Cutting List.

ters. These each have two inputs mixed together in the manual mode, except for 8-foot from IC4 pin 5 which does not require the CMOS switch. In automatic mode, the footages from the upper half of the keyboard (IC4 pins 16, 17 and 18) are cut off by the CMOS switches, and IC4 pins 3, 4, 5 and 6 now become four notes of an 8-

foot chord when one key is pressed in one of the two lower octaves of the keyboard.

The 16-foot and 4-foot from the lower half of the keyboard are disconnected from their filters and the four notes of the chord are combined in R84, 85 and 86 and mixed together in IC9. The output of IC9 in automatic mode

### MISCELLANEOUS PARTS LIST FOR CABINET

Front panel		(XY94C)
Metalwork mounting kit		(XY95D)
Spring clip	4 off	(BF15R)
End cheek set		(XY96E)
Keyboard separator		(XY97F)
Swell pedal housing and trim		(XY98G)
Rubber coupling	2 off	(FB98G)
Self-tapper No. 8 x 1/2 in.		
(for fixing metalwork to cabinet)	4 off	(BF69A)
Bolt 4BA 1 in. (for PCB mounting)	8 off	(BF04E)
Spacer 4BA 1/4 in. (for PCB mounting)	8 off	(FW31J)
Nut 4BA (for PCB mounting)	8 off	(BF17T)
Panel screw 4BA 1/2 in. (for metalwork)	8 off	(BF14Q)
Bolt 2BA 1 in. (for speaker)	4 off	(BF01B)
Nut 2BA (for speaker)	4 off	(BF16S)
Bolt M4 25mm (for swell pedal and pedalboard)	8 off	(BF50E)
Nut M4 (for swell pedal and pedalboard)	8 off	(BF57M)
Self-tapper No. 4 x 3/8 in. (for swell pedal housing)	6 off	(BF65V)
Wood screw No. 10 x 1 in. (for fixing frame to shelf)	4 off	—
P-Clip 1/4 in.		(LR45Y)
Velcromount	4 off	(HB21X)
Music stand		(XG01B)
Roll top		(XY99H)
Roll top guides (pair)		(XG00A)

*Note: The above parts are only required if you are constructing your own cabinet. The cabinet kit (XY93B) supplied by Maplin Electronic Supplies Ltd. is complete and no other parts are required if this is used.*

is connected through a CMOS switch into the 8-foot string and 8-foot flute filters. The note on the original 8-foot line is mixed with the other three notes at the input to the 8-foot string and 8-foot flute filters.

In the manual mode the lower manual circuits are much the same as for the upper manual.

The 4-foot flute filter is built around IC11a, 8-foot flute around IC11b, 16-foot flute around IC11d, 4-foot string around IC12 and 8-foot string around IC13. In the manual mode the outputs of the flute filters are connected through the mixer IC11c to the flute VCA, IC15. The 8-foot string filter is connected to its VCA

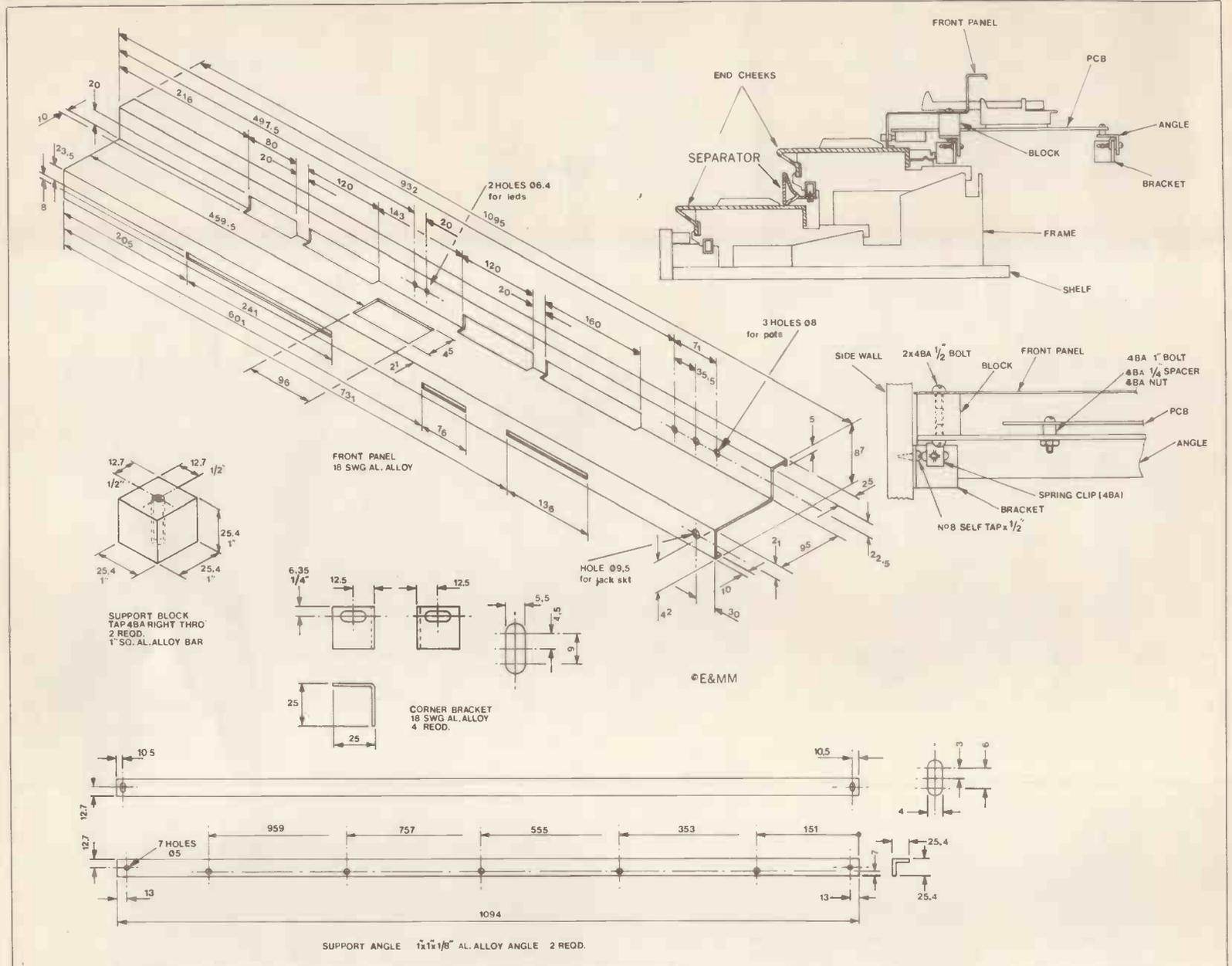


Figure 37. Metalwork.

IC14b and the 4-foot string filter is connected to its VCA, IC14a. In the automatic mode the 4-foot string VCA becomes the counter-melody VCA and the 8-foot string VCA becomes the vamp VCA when the vamp button is pressed.

In the manual mode all three VCAs are controlled by the flute envelope shaper (TR5 and 6 and associated circuitry) which is itself controlled by KPS. If memory is pressed, the KPS signal is overridden by an earth on the cathode of D53 which pulls TR5 on permanently and the last keys pressed sound indefinitely. When the vamp button is pressed, all three VCAs are controlled from the vamp envelope shaper TR9 and 10. However, the vamp only plays when keys are pressed and the rhythm unit is switched on.

When KPS is high (all keys released), both the vamp and counter-melody envelope shapers are inhibited to prevent pulses from the rhythm generator trig-

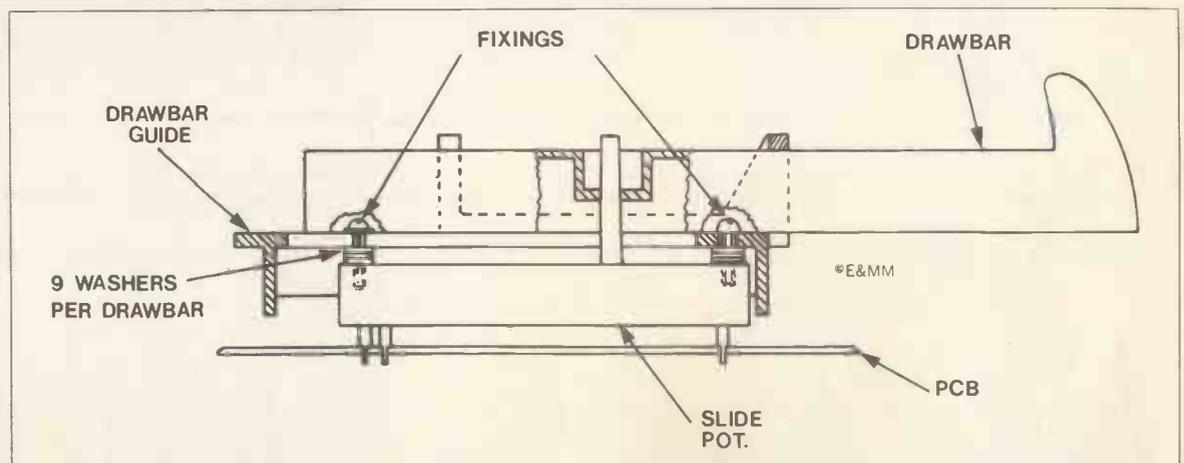


Figure 38. Drawbar assembly.


gering them. When KPS goes low or memory button is pressed, the bias is removed from D55 and 66 and the pulses from the rhythm generator are now able to trigger the envelope shapers.

With the "auto" button pressed, the flute envelope shaper is still controlled by KPS as is the 8-foot string envelope

shaper. However, the 4-foot string VCA is now controlled from the counter-melody envelope shaper, TR7 and 8. The counter-melody is generated from the four notes of the chord produced by IC4. These are switched through to the mixing resistors R69 to 72 by IC7 under control individually of four outputs from the rhythm unit.

From the mixing resistors, the counter-melody is fed to the 4-foot string filter and thence to the 4-foot string VCA.

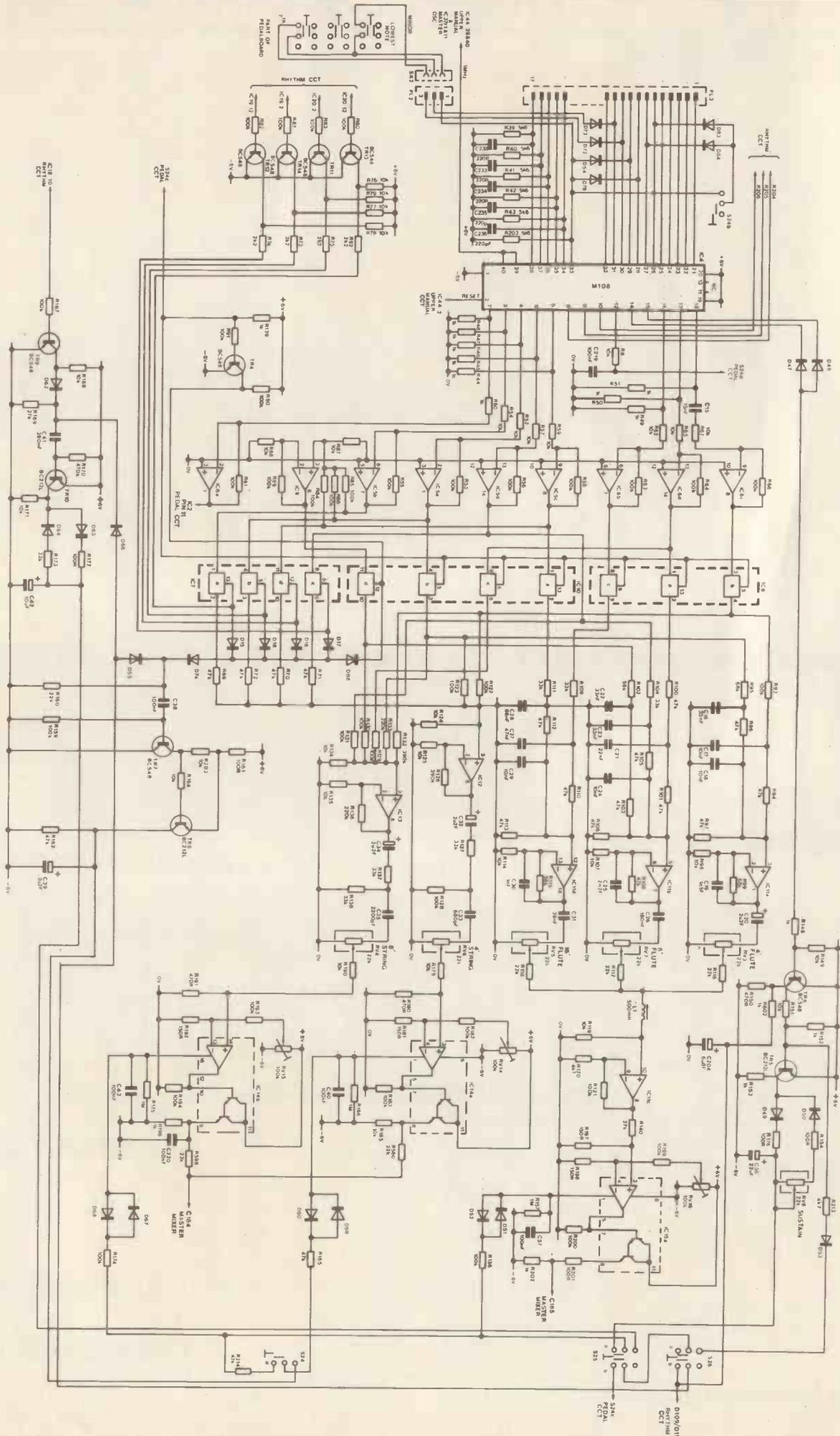If the auto and vamp buttons are both pressed, the flutes and 8-foot string VCAs come under control of the vamp envelope shaper whilst the 4-foot string remains under the control of the counter-



IC4 = M108  
 IC5,6,11 = 3403  
 IC7,8,10 = 4016BE  
 IC9,12,13 = uA741C  
 IC14,15 = LM13600N  
 ALL DIODES 1N4148

NB: +6V to  
 PIN 4 IC5,6,11  
 PIN 7 IC9,12,13  
 PIN 14 IC7,8,10  
 \*6V to  
 PIN 4 IC9,12,13  
 PIN 7 IC7,8,10  
 PIN 11 IC5,6,11

Figure 39. Circuit diagram of the lower manual.

## TRANSISTORS

AC107	25	BC107C	12	BC174	15	BC550	14	BD201	80	BF164	50	BFR62	24	MPSA06	20
AC125	30	BC108	10	BC175	35	BC556	14	BD202	80	BF165	50	BFR79	28	MPSA55	20
AC126	22	BC108A	11	BC177	14	BC557	13	BD201/202	M/P	BF167	24	BFR80	28	MPSA56	20
AC127	22	BC108B	11	BC178	14	BC558	13	M/P	1.70	BF173	24	BFW10	55	ND120	18
AC128	20	BC108C	12	BC179	14	BC559	14	BD203	80	BF176	36	BFX29	25	OC19	85
AC128K	37	BC109	10	BC180	12	BCY30	80	BD204	80	BF177	24	BFX30	30	OC20	1.85
AC132	26	BC109A	11	BC181	10	BCY31	80	BD203/204	M/P	BF178	25	BFX84	24	OC22	1.50
AC141	26	BC109B	11	BC182	10	BCY32	85	M/P	1.70	BF179	30	BFX85	26	OC23	1.50
AC141K	40	BC109C	12	BC182L	10	BCY33	80	BD205	80	BF180	30	BFX86	26	OC24	1.35
AC142	26	BC113	16	BC183	10	BCY34	80	BD206	80	BF181	30	BFX87	26	OC25	1.00
AC142K	40	BC114	17	BC183L	10	BCY70	14	BD207	80	BF182	30	BFX88	26	OC26	1.00
AC176	24	BC115	18	BC184	10	BCY71	15	BD208	80	BF183	30	BFX89	55	OC28	90
AC176K	40	BC116	19	BC184L	10	BCY72	15	BD222	47	BF184	22	BFY50	50	OC29	95
AC187	25	BC116A	20	BC186	15	BCZ10	70	BD225	47	BF185	22	BFY51	20	OC35	90
AC187K	40	BC117	20	BC187	18	BCZ11	70	BD232	85	BF186	26	BFY52	20	OC36	90
AC188	40	BC118	17	BC207	11	BCZ12	70	BD233	65	BF187	26	BFY53	20	OC41	20
AC188K	40	BC119	25	BC208	11	BD106	50	BD234	55	BF188	32	BFY90	80	OC42	22
ACY17	50	BC120	35	BC209	12	BD115	50	BD235	55	BF194	10	BIP19	38	OC44	24
ACY18	50	BC125	25	BC212	10	BD116	50	BD236	58	BF195	12	BIP20	38	OC45	20
ACY19	50	BC126	30	BC212L	10	BD121	50	BD237	65	BF196	12	BIP19/20	38	OC70	24
ACY20	50	BC132	18	BC213	10	BD123	65	BD238	65	BF197	12	M/P	80	OC71	15
ACY21	50	BC134	18	BC213L	10	BD124	75	BD239A	50	BF198	15	BRY39	39	OC72	24
ACY22	50	BC135	18	BC214	10	BD131	35	BD240A	50	BF199	16	BSX19	20	OC74	26
AD130	75	BC136	20	BC214L	10	BD132	35	BD239A/240A	1.00	BF200	30	BSX20	20	OC75	30
AD140	70	BC137	20	BC225	26	BD131/132	M/P	BF222	90	BF222	90	BSX21	21	TC76	35
AD142	85	BC138	28	BC226	36	BD139	38	BD240	45	BF224	20	BSY95	13	OC77	50
AD143	85	BC139	32	BC237	13	BD133	40	BD241	45	BF240	13	BSY95A	13	OC79	40
AD149	70	BC140	25	BC238	14	BD135	35	BD242	45	BF241	18	BU105	1.60	OC81	22
AD161	40	BC141	28	BC239	15	BD136	35	BD243	45	BF242	28	BU105/	OC81D	24	
AD162	40	BC142	25	BC251	15	BD137	35	BDY11	1.30	BF257	30	O2	OC82	24	
AD161/162	80	BC143	25	BC251A	16	BD138	36	BDY17	1.80	BF259	35	BU204	1.40	OC82D	30
M/P	80	BC144	46	BC300	30	BD139	38	BDY55	1.40	BF263	60	BU205	1.40	OC83	26
AF114	50	BC145	49	BC301	28	BD139/140	M/P	BF263	60	BF270	36	BU208	1.90	OC84	38
AF115	50	BC146	49	BC302	29	M/P	80	BF115	2.0	BF271	31	GP300	02	OC140	80
AF117	50	BC148	09	BC303	28	BD155	60	BF117	50	BF273	36	MJ480	95	OC169	80
AF118	65	BC149	09	BC304	28	BD175	60	BF118	75	BF274	38	MJ481	1.05	OC171	80
AF124	50	BC151	22	BC307	13	BD176	60	BF119	75	BF275	38	MJ490	95	OC200	46
AF125	50	BC152	20	BC327	12	BD177	68	BF120	50	BF336	34	MJ491	1.15	OC201	95
AF126	50	BC153	25	BC328	13	BD178	68	BF121	50	BF337	34	MJ2955	90	OC202	1.20
AF127	50	BC154	19	BC337	13	BD179	75	BF122	50	BF338	38	MJE340	55	OC203	85
AF139	38	BC157	10	BC338	13	BD180	75	BF123	60	BF339	38	MJE370	55	OC204	90
AF239	42	BC158	10	BC384	14	BD185	68	BF127	60	BF371	26	MJE370	55	OC205	1.15
AL102	1.90	BC159	10	BC400	30	BD186	68	BF152	25	BF457	37	MJE371	60	OC208B	2.50
AL103	1.80	BC160	26	BC441	30	BD187	75	BF153	25	BF458	37	MJE370	55	OC209	2.60
AS26	50	BC161	38	BC460	32	BD188	75	BF154	22	BF459	38	MJE251	65	OC210B	2.60
AS28	50	BC167	11	BC461	32	BD189	78	BF155	35	BF494	30	MJE2955	90	OC211	29
AS29	50	BC168	10	BC477	20	BD190	78	BF156	28	BF495	28	MJE3055	65	OC212	30
AU104	1.90	BC169	10	BC478	20	BD195	90	BF157	28	BF496	28	MJE3440	52	OC213	30
AU110	1.90	BC169C	11	BC479	20	BD196	90	BF158	28	BF497	24	MP8113	52	OC214	55
AU113	1.90	BC170	09	BC479	20	BD197	95	BF159	28	BF498	25	MPF102	60	OC215	42
BC107	10	BC171	09	BC479	20	BD198	95	BF160	28	BF499	25	MPF104	35	OC216	44
BC107A	11	BC172	09	BC479	20	BD199	95	BF161	24	BF500	25	MPF105	35	OC217	38
BC107B	11	BC173	09	BC479	20	BD200	99	BF163	30	BF502	25	MPSA05	20	OC218	40

TIP308	42	2N708	14	2N2904	24	2N3823	60
TIP30C	44	2N711	30	2N2904A	26	(FET)	60
TIP31	38	2N717	30	2N2905	24	2N3903	12
TIP31A	40	2N718	25	2N2905A	26	2N3904	12
TIP31B	42	2N718A	50	2N2906	18	2N3905	12
TIP31C	44	2N726	29	2N2906A	20	2N3906	12
TIP32	38	2N727	29	2N2907	20	2N4058	12
TIP32A	40	2N743	20	2N2907A	22	2N4059	14
TIP32B	42	2N744	20	2N2923	15	2N4060	14
TIP32C	44	2N914	20	2N2824	15	2N4061	12
TIP41C	44	2N918	30	2N2825	15	2N4062	12
TIP42A	44	2N929	20	2N2826	10	2N4220	20
TIP42B	46	2N936	40	2N2926G	10	2N4220	20
TIP42C	48	2N1131	24	2N2926H	09	(FET)	35
TIP2955	60	2N1132	24	2N2926J	09	(FET)	35
TIP3055	50	2N1302	25	2N2926K	09	(FET)	35
TIS43	22	2N1303	28	2N3011	20	2N4282	28
TIS90	24	2N1305	28	2N3012	20	2N4283	28
TIS91	22	2N1306	35	2N3013	20	2N4284	28
TIS92	22	2N1307	35	2N3014	20	2N4285	28
UT46	20	2N1308	40	2N3015	20	2N4286	28
ZTX107	10	2N1309	40	2N3016	20	2N4287	28
ZTX108	10	2N1599	35	2N3017	20	2N4288	28
ZTX109	10	2N1613	28	2N3018	20	2N4289	28
ZTX300	12	2N1711	30	2N3019	20	2N4290	28
ZTX301	12	2N1889	45	2N3020	20	2N4291	28
ZTX302	16	2N1890	45	2N3021	20	2N4292	28
ZTX303	16	2N1893	40	2N3022	20	2N4293	28
ZTX304	20	2N1894	40	2N3023	20	2N4294	28
ZTX305	15	2N1895	40	2N3024	20	2N4295	28
ZTX501	12	2N1932	38	2N3025	20	(FET)	60
ZTX502	12	2N1933	38	2N3026	20	2N4923	65
ZTX503	12	2N1934	38	2N3027	20	2N5135	10
ZTX504	12	2N2117	25	2N3028	20	2N5136	10
ZTX505	12	2N2118	25	2N3029	20	2N5137	10
ZTX511	25	2N218A	28	2N3030	20	2N5138	10
ZTX520	25	2N219	28	2N3031	20	2N5139	10
ZTX530	25	2N219A	28	2N3032	20	2N5142	14
ZN388	36	2N2220	20	2N3033	20	2N5194	56
ZN388A	56	2N2220	20	2N3034	20	2N5245	40
ZN404	20	2N2221	20	2N3035	20	2N5246	40
ZN404A	24	2N2221A	22	2N3036	20	2N5294	50
ZN524	50	2N2222	20	2N3037	20	2N5295	50
ZN527	50	2N2222A	20	2N3038	20	2N5448	12
ZN598	40	2N2368	18	2N3039	20	2N5449	12
ZN599	46	2N2369	14	2N3040	20	2N5457	12
ZN696	24	2N2369A	14	2N3041	20	2N5458	12
ZN697	24	2N2411	25	2N3042	20	2N5459	12
ZN698	30	2N2412	25	2N3043	20	(FET)	32
ZN699	32	2N2646	47	2N3044	20	2N5459	12
ZN706	10	2N2711	22	2N3045	20	2N5459	12
ZN706A	12	2N2712	22	2N3046	20	2N5459	12
ZN707	48	2N2714	22	2N3047	20	2N5459	12

## DIODES

AA119	08	BB104	30	BY176	75	OA79	10
AA120	08	BAX13	07	BY206	30	OA81	10
AA129	09	BAX16	08	BY210	600	OA85	10
AA130	09	BY100	22	BY210	45	OA90	07
AA131	15	BY101	22	BY211	45	OA91	07
AA132	15	BY105	22	BY212	40	OA95	07
BA100	10	BY114	22	BY213	40	OA182	13
BA102	20	BY124	22	BY216	41	OA200	08
BA144	09	BY126	11	BY217	36	OA202	08
BA148	15	BY127	12	BY218	36	IN344	07
BA154	12	BY128	16	BY219	36	IN60	06
BA155	14	BY130	17	OA5	60	IN914	04
BA156	14	BY133	21	OA10	35	IN916	05
BA173	15	BY156	08	OA47	38	IN4148	04
BA248	16	BY164	51	OA70	08	IS44	05

## 74 LS SERIES TTL

# - new extended 1981 range

<b>AL30A</b> <b>10w R.M.S.</b> <b>AUDIO AMPLIFIER MODULES</b>  <b>£4.16</b>	<b>AL60</b> <b>25w R.M.S.</b> <b>AUDIO AMPLIFIER MODULE</b> <b>25 Watts RMS</b>  <b>£5.15</b>	<b>SPM120</b> <b>STABILISED POWER SUPPLIES</b> <b>SPM120/45</b> <b>SMP120/55</b> <b>SMP120/65</b>  <b>£6.38</b>	<b>AL80</b> <b>35w R.M.S.</b> <b>AUDIO AMPLIFIER MODULE</b>  <b>£8.07</b>
<b>S450</b> <b>STEREO FM TUNER</b> <b>Fitted with phase lock-loop</b>  <b>£25.56</b>	<b>Stereo 30</b> <b>COMPLETE AUDIO CHASSIS</b>  <b>7+7w R.M.S.</b> <b>£21.09</b>	<b>GE100 Mk2.</b> <b>10 CHANNEL MONOGRAPHIC EQUALISER</b>  <b>£23.00</b>	<b>AL120</b> <b>50w R.M.S.</b> <b>AUDIO AMPLIFIER</b> <b>(With integral heat sink and short-circuit protection).</b>  <b>£13.14</b>
<b>AL250</b> <b>125w R.M.S.</b> <b>POWER AMPLIFIER</b>  <b>£19.60</b>	<b>SPM80</b> <b>STABILISED POWER SUPPLY</b>  <b>£4.84</b>	<b>VPS30</b> <b>REGULATED VARIABLE STABILISED POWER SUPPLY</b>  <b>£7.60</b>	<b>MONO PRE-AMPLIFIERS</b> <b>MM 100. Supply voltage 40-65v inputs: Tape, Mag P.U. Microphone Max output 500mv.</b> <b>£12.43</b> <b>MM 100G. Supply voltage 40-65v inputs: 2 Guitars. Microphones Max output 500mv.</b> <b>£12.43</b>
<b>PA100</b> <b>STEREO PRE-AMPLIFIER</b>  <b>£17.65</b>	<b>STA5. 5 watts per channel Stereo Amplifier. Kit consisting of: 2xAL20 amplifiers, 1xPA 12 pre-amplifier, 1xPS12 power supply, 1x2036 transformer and necessary wiring diagram</b> <b>£19.52</b> <b>STA10. 10 watts per channel Stereo Amplifier. Kit consisting of: 2xAL30 amplifiers, 1xPA12 pre-amplifier, 1xPS 12 power supply, 1x2036 transformer and necessary wiring diagrams.</b> <b>£20.63</b> <b>STA15. 15 watts per channel Stereo Amplifier. Kit consisting of: 2xAL60 amplifiers, 1xPA100 pre-amplifier, 1xSPM80 power supply, 1x2034 transformer, 2xcoupling capacitors for 8 ohms 470mfd 30v and necessary wiring diagram.</b> <b>£36.76</b> <b>STA25. 25 watts per channel Stereo Amplifier. Kit consisting of: 2xAL60 amplifiers, 1xPA200 pre-amplifier, 1xSPM120/45 power supply, 1x2040 transformer, coupling capacitors for 8 ohms 470 mfd 45v, 1xreservoir capacitor 2200mfd 100v and necessary wiring diagram.</b> <b>£40.50</b> <b>STA35. 35 watts per channel Stereo Amplifier. Kit consisting of: 2xAL60 amplifiers, 1xPA200 pre-amplifier, 1x2035 transformer, 2xcoupling capacitors 470mfd at 50v for 8 ohms, 1xreservoir capacitor 2200mfd 100v and necessary wiring diagram.</b> <b>£45.76</b> <b>STA50. 50 watts per channel Stereo Amplifier. Kit consisting of: 2xAL120 amplifiers, 1xPA200 pre-amplifier, 1x2041 transformer, 2xcoupling capacitors 1000mfd 63v, 1xSPM 120/65, 1xreservoir capacitor 3300mfd 100v and necessary wiring diagram.</b> <b>£59.89</b>	<b>STA100. 100 watts per channel Stereo Amplifier. Kit consisting of: 2xAL250 amplifiers, 1xPA200 pre-amplifier, 2xSPM 120/65 power supplies, 2x2041 transformers, 2xcoupling capacitors 1000mfd 100v and necessary wiring diagram.</b> <b>£84.68</b>	<b>HARDWARE IN PACKS OF 25</b> <b>839 08A 1" Bolt 0.70</b> <b>840 08A 1/2" Bolt 0.40</b> <b>842 28A 1" Bolt 0.35</b> <b>843 28A 1/2" Bolt 0.30</b> <b>844 28A 1/4" Bolt 0.32</b> <b>845 48A 1" Bolt 0.28</b> <b>846 48A 1/2" Bolt 0.20</b> <b>847 48A 1/4" Bolt 0.18</b> <b>848 68A 1" Bolt 0.24</b> <b>849 68A 1/2" Bolt 0.18</b> <b>850 68A 1/4" Bolt 0.20</b> <b>851 08A Solder Tags 0.20</b> <b>852 28A Solder Tags 0.16</b> <b>853 48A Solder Tags 0.14</b> <b>854 68A Solder Tags 0.12</b> <b>855 08A Full Nut 0.12</b> <b>856 28A Full Nut 0.26</b> <b>857 48A Full Nut 0.18</b> <b>858 68A Full Nut 0.18</b> <b>859 08A Washer 0.12</b> <b>860 28A Washer 0.09</b> <b>861 48A Washer 0.09</b> <b>862 68A Washer 0.09</b> <b>FUSE HOLDERS</b> <b>506 20mm Chassis Fuse Holder 0.14</b> <b>507 1 1/2" Chassis Fuse Holder 0.14</b> <b>508 1 1/4" Car in line Fuse Holder 0.12</b> <b>509 20mm Panel Fuse Holder 0.26</b> <b>510 1 1/4" Panel Fuse Holder 0.32</b> <b>FUSES:</b> <b>Quick Blow 20mm:</b> <b>611 150mA 0.06</b> <b>612 250MA 0.06</b> <b>613 500MA 0.06</b> <b>614 800MA 0.07</b> <b>615 1 Amp. 0.06</b> <b>616 1.5 Amp 0.07</b> <b>617 2.0 Amp 0.06</b> <b>618 2.5 Amp 0.06</b> <b>619 3.0 Amp 0.07</b> <b>620 3.15 Amp 0.06</b> <b>621 5.0 Amp 0.06</b> <b>Semi Delay: 20mm</b> <b>622 100MA 0.07</b> <b>623 250MA 0.07</b> <b>624 500MA 0.07</b> <b>625 1 Amp 0.07</b> <b>626 1.5 Amp 0.07</b> <b>627 2 Amp 0.07</b> <b>628 2.5 Amp 0.07</b> <b>629 3.15 Amp 0.07</b> <b>630 5.0 Amp 0.07</b> <b>Quick Blow: 1 1/4"</b> <b>631 250MA 0.06</b> <b>632 500MA 0.06</b> <b>634 800MA 0.06</b> <b>635 1 Amp 0.06</b> <b>636 1.5 Amp 0.06</b> <b>637 2.0 Amp 0.06</b> <b>638 2.5 Amp 0.06</b> <b>639 3 Amp 0.06</b> <b>641 4 Amp 0.06</b> <b>642 5 Amp 0.06</b>

### Stabilised Power Supply Kit

Variable from 2-30 volts and 0-2 Amps

## VPS30



**Kit includes:**  
 1 - VPS30 Module.  
 1 - 25 volt 2 Amp transformer.  
 1 - 0-50v 2" Panel Meter.  
 1 - 0-2 Amp 2" Panel Meter.  
 1 - 470 ohm wirewound potentiometer.  
 1 - 4K7 ohm wirewound potentiometer.

**Wiring Diagram Included.**

**KIT £20 + VAT**

### PS12 POWER SUPPLY MODULE

Power supply for AL20A-30A, PA12, S450 etc.

Input A.C. Voltage 15-20V  
 Output D.C. Voltage 22-30V approx. (Dependent upon input.)  
 Output Current 800mA maximum.  
 Dimensions 60x43x26mm.



**£1.65**

### PA12 STEREO PRE-AMPLIFIER



**£8.55**

### MPA30 MAGNETIC CARTRIDGE PRE-AMPLIFIER



**£3.27**

### BP124 SIREN ALARM MODULE

American Police screamer powered from any 12 volt supply into 4 or 8 ohm speaker. Ideal for car burglar alarm, freezer break-down, and other security purposes.



**ONLY £3.85 5 WATTS -**

Transformers are not included with power supplies.  
 SPM 120 Range also require reservoir and output capacitors.

BP124. 5 watt 12v max. - Siren Alarm Module. <b>£3.85</b>	2041. 2 amp 0-55v-65v. Suit: SPM120/55, SPM120/65v. <b>3.46</b>
GE100MK11. 10 channel mono-graphic equaliser, complete with sliders and knobs. <b>£23.00</b>	2039. 1 amp 0-20v. Suit Stereo 30. <b>£3.50</b>
VPS30. Variable regulated stabilised power supply 2-30v 0-2 amps <b>£7.60</b>	2043. 150mA 15-0-15v. Suit: SG30. <b>£1.60</b>
PS250. Consists - 1 capacitor & 4 diodes for constructing unregulated power supply for AL250 to 125 watts <b>2.90</b>	

#### ACCESSORIES

139. Teak Cabinet. Suit: Stereo 30, 320x235x81mm. <b>£7.00</b>
140. Teak Cabinet. Suit: STA15, 425x290x95mm. <b>£9.50</b>
FP100. Front Panel for PA100 & PA200. <b>£1.80</b>
BP100. Back Panel for PA100 & PA200. <b>£1.60</b>
GE100FP. Front Panel for one GE100MK11. <b>£1.75</b>
2240. Kit of parts including Teak Cabinet, Chassis, Sockets and Knobs etc. (To house STA15 Amplifier). <b>£19.95</b>

Full data sheets are available FREE on request, please enclose a S.A.E.

Access and Barclaycards accepted — just telephone our Orderline — Ware (STD 0920) 3182.  
 All prices exclude VAT, add 50p postage per order. Terms: C.W.O., cheques. **STOP! PRESS!**  
 Postal Orders payable to Bi-Pak at address below.

# BI-PAK

## SEMICONDUCTORS

Dept. EMM 7 P.O. BOX 6, WARE, HERTS.  
 Tel: Ware (STD 0920) 3442. Telex: 817861.  
 Giro No. 3887006.  
 Visit our shop at: 3, Baldock St, Ware, Herts.

### CB ACCESSORIES

105 Adjustable Aerial Gutter Mount	£3.00
106 CB Mobile Antenna	£9.50
1340 Mobile or CB Mike 600 ohms	£4.98
1341 Mobile or CB Mike 250 ohms	£6.00
1715 PL 259 Plug	£0.40
1716 SO239 Socket 4 hole fixing	£0.38
1717 SO239 Socket single hole fixing	£0.40
1718 PL259 Double Ended Female Coupler	£0.40
1719 NC555 Reducer for PL259 (Small)	£0.16
1720 NC556 Reducer for PL259 (Large)	£0.16
1721 M359 Right Angle Coupler PL259 SO239	£0.75
1722 M358 T Connector Female-Male-Female	£0.85
1723 NC563 Inline Coupler PL259 x 2	£0.60
1724 BNC15 50 ohm standard plug	£0.64
1725 BNC1502 Chassis mounting socket	£0.76
1726 BNC1503 Chassis mounting socket single hole fixing	£0.70
1727 BNC1520 BNC male to SO239 female	£0.85
1728 BNC1521 BNC female to PL259 male	£0.85

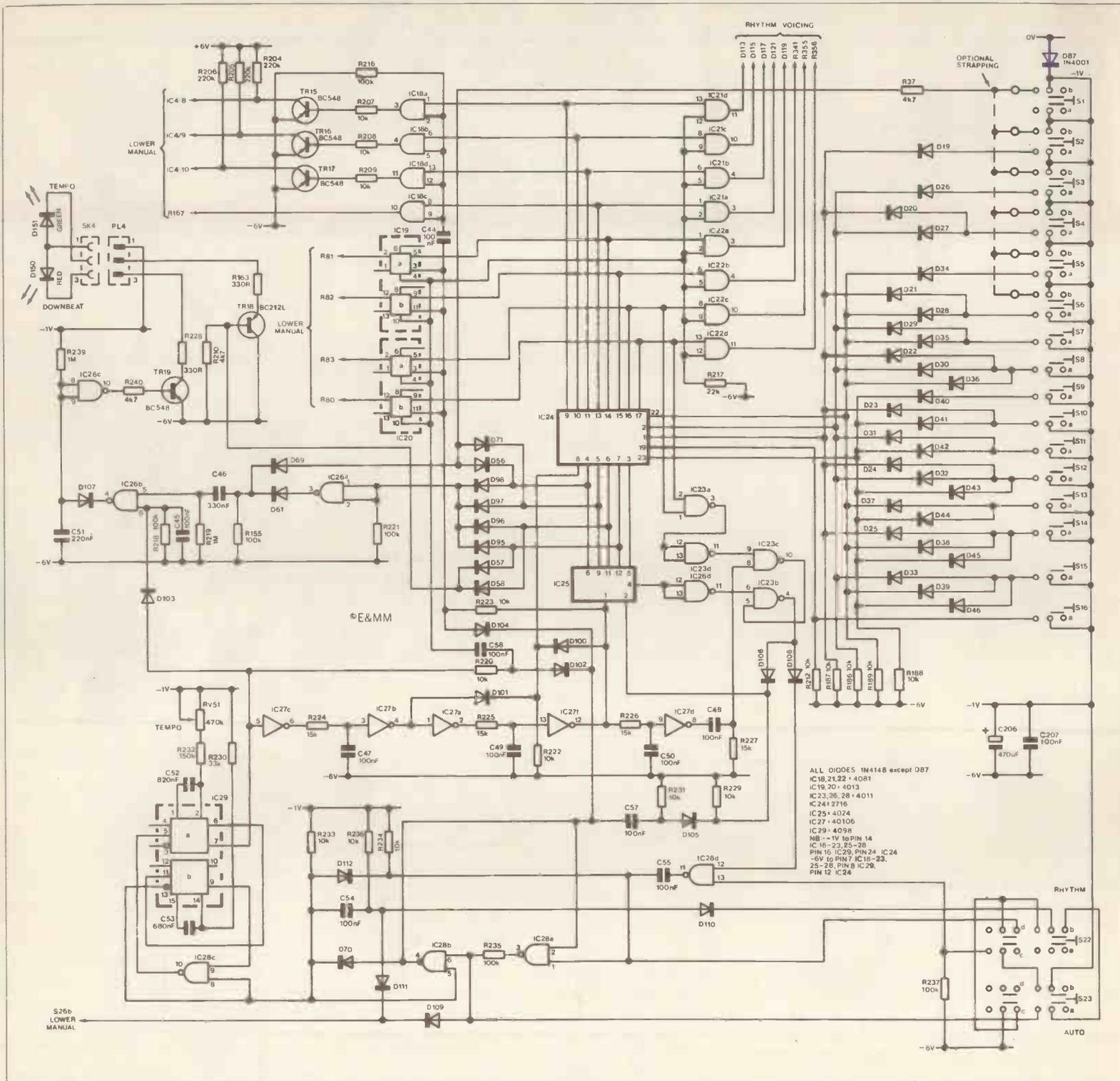


Figure 40. Circuit diagram of the rhythm unit.

melody envelope shaper. The vamp envelope shaper is triggered by positive-going pulses from the rhythm unit. These pulses turn TR9 on and C41 charges through R169. Whilst C41 is charging, TR10 is turned on. When the input pulse is not present, TR9 turns off, C41 discharges through D62 and then TR10 turns off. Thus we now have a pulse at the junction of D63 and 64 of the length we require and at the required level. C42 now determines the attack and decay of the envelope in the same way as the other envelope shapers we have described previously. The rhythm unit has four of its

outputs connected via R80 to 83 to TR11 to 14 which act as level shifters and inverters. When a negative-going pulse occurs on one or more of these lines, the transistor turns on and drives the appropriate CMOS switch in IC7 which connects one or more of the notes of the automatic chord through to the countermelody VCA. At the same time, any pulse is also fed through D15 to 18 and D74 to trigger the envelope shaper. The resultant positive-going pulse turns TR7 on during the charge time of C38 and the collector of TR7 going low turns on TR8 which charges C39. When

the pulse goes off, C39 discharges via R162 which sets the discharge time. This envelope shaper is a high speed version of the others in the organ, designed to respond to rapid input control signals, retriggering each time. As the rhythm generator can be used in manual mode, the countermelody must be inhibited when auto is not selected and this is achieved by preventing the cathodes of D15 to 18 from going high which stops the CMOS switches in IC7 from turning on. The 'auto/manual' switch S24 when in auto mode presents a -6V level to the junction of R91, 139. In the manual mode, this -6V is

not present and R139 pulls the junction of R91, 139 to +6V which turns on the CMOS switches in IC8 and 10a, b and c. This also turns on TR4, via R91 which turns off IC10d and this turns the automatic chord lines off. The collector TR4 being low provides the -6V that allows D88 to conduct and turn off the countermelody also. **Rhythm Unit Circuits** The circuit diagram of the rhythm unit is shown in Figure 40. All the rhythms consist of two bars of up to 32 counts total and


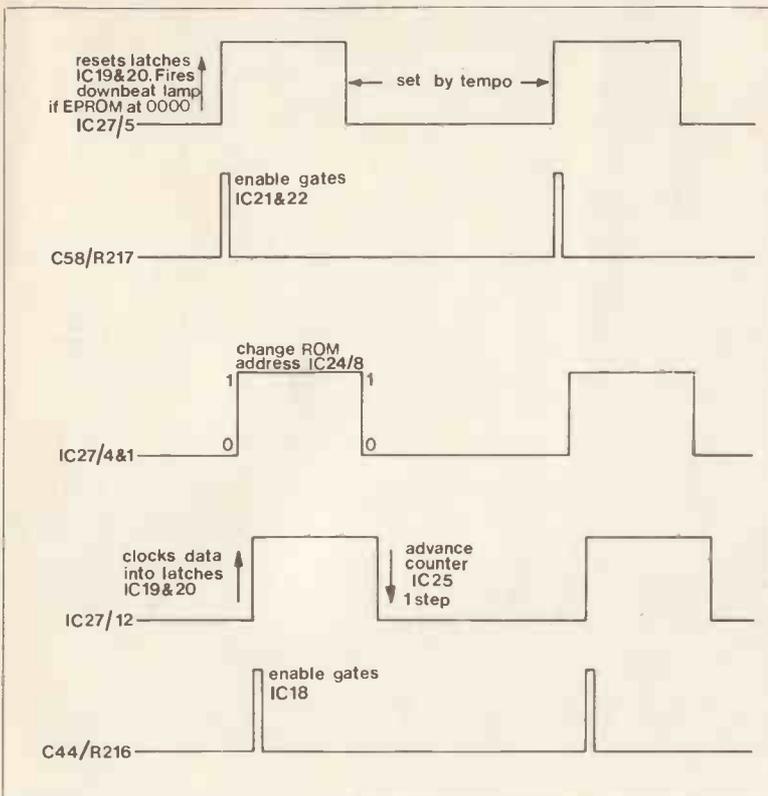


Figure 41. Rhythm unit timing chart.

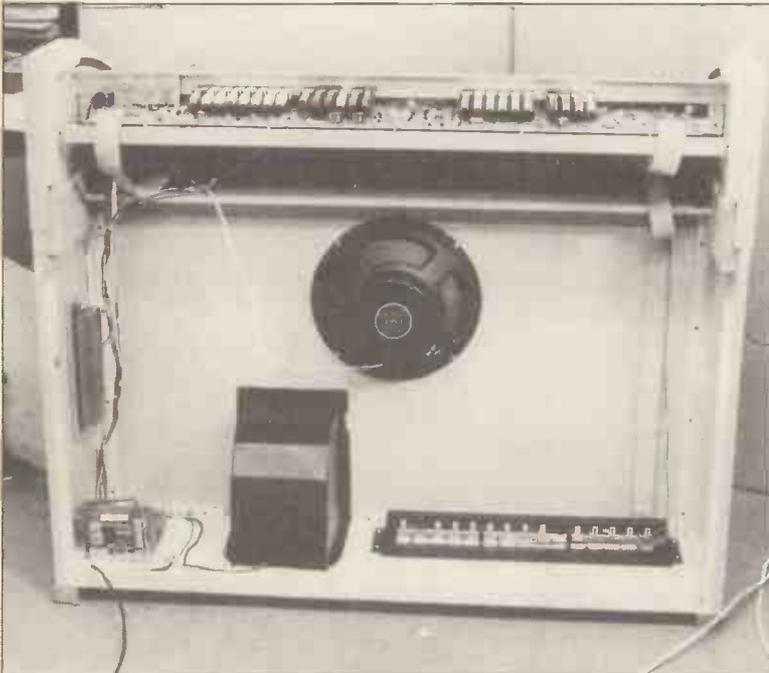

Rear view of cabinet with parts installed.

at each count, any of the 16 outputs can be enabled. Four of these outputs provide a continuous level until changed (countermelody), whilst the remainder simply provide a pulse at the appropriate time. The information is stored in a pre-programmed 16K EPROM. As the EPROM has only 8 output lines, for each count the EPROM is addressed twice.

IC29 is a dual monostable that provides the clock pulses from which the rhythm generator is timed. The timing consists of a fixed duration high period set by C53 and R230 and a variable duration low period set by C53 and R232 and the tempo control

RV51. The output is from pin 7. IC27 provides high impedance points to allow the timing circuit to function correctly.

Referring to Figure 41, positive transitions of the clock pulse first enable all the gates in IC21 and 22 during the charge time of C58, thus transferring the information standing on the outputs of the EPROM to the outputs of the gates. Second, they reset the four countermelody latches IC19 and 20 and third, enable IC26b which we shall describe later.

The leading edges are also inverted by IC27c, a Schmitt trigger, and delayed by R224 and C47 to allow time for the above

operations to take place. After the delay, IC27b further inverts the signal and the positive levels are applied to IC24 pin 8. This is the least significant address line of the EPROM and allows the second set of 8 bits to be made available at the outputs of the EPROM.

By this time all the gates in IC21 and 22 have been disabled and the positive-going transition at IC27b output has been inverted by IC27a. The signal is now delayed by R225 and C49 and inverted again by IC27f. This positive-going transition enables all the gates in IC18 during the charge time of C44 and clocks the four latches in IC19 and 20. This is also connected to the input of IC25, a 7-stage ripple counter.

The positive-going pulse at the output of IC27f is delayed by R226 and C50 and inverted by IC27d. It is turned into a pulse by R227 and C48 and applied to IC23 pin 8. When the clock goes negative, the least significant address line of the EPROM returns low and this negative transition steps IC25 which moves the EPROM to its next address ready for the next positive-going clock pulse.

IC25 addresses the five next least significant address lines for each of the 32 possible counts. The four next address lines are directly coded from the rhythm selection switches via the diode matrix D19 to 46. These lines are normally held low by R186 to 189, but go high via the diodes when selected. S16 switches the most significant address line to select the second set of 15 rhythms.

Two methods are needed to reset the counter to count one (count one is the downbeat of the first bar, bearing in mind that there are two bars in each rhythm) so that a rhythm can be any length to generate unusual time signatures such as 5/4 time. A reset always occurs if the counter reaches maximum and for rhythms requiring fewer steps a non-valid output option (short and long cymbals together) is coded. This corresponds to pins 16 and 17 of the EPROM being high simultaneously.

Thus the output of IC23a goes low, is inverted by IC23d and applied to IC23c, the other input of which is only high for a short period after the counter has returned the least significant address low and moved the counter to the next EPROM address. So, if a reset is required after count 24, for example, the non-valid output option must be coded in count 25. This all happens very quickly, whilst the delay set by the tempo control occurs and ensures that the next beat is the downbeat.

If the output of IC23c goes low or pin 4 of IC25 goes high, thus indicating the end of 32 counts, then after an inversion by IC26d, the output of IC23b goes high and resets IC25 via D106 and IC28d is enabled.

When S22, the rhythm start/stop switch is pressed, S22B connects a low level via S23C normal, to the cathode of D110 which pulls the junction of R236 and C54 low. The pulse produced by C54 charging pulls pins 5 and 8 of IC28 low, resetting the clock and causing the start/stop latch IC28a and b to change over giving a high on pin 4. This removes the -6V that has been inhibiting the output gates and latches via D102 and 104 and allows the rhythms to sound. It also resets the counter IC25, so that rhythms always start on the downbeat of the first bar.

If S22 is released and S23, the auto start/stop switch is pressed, the -6V is removed from IC28 pins 5 and 8 as before. This allows the clock to run, but as pin 6 of IC28 is held high by KPS from IC4, the start/stop latch remains at stop. When a key on the lower manual is pressed, KPS goes low and the start/stop latch changes over. The pulse produced by C54 in this case, ensures that the clock starts in the right phase.

When the keys are released, KPS goes high which allows the high from R236 via D110 to turn the start/stop latch off. This ensures that the rhythm starts on the downbeat of the first bar when a key is pressed, stops when released, yet allows the tempo and downbeat lamps to flash even when the rhythm is not sounding, so that the tempo may be set prior to playing.

If S22 and S23 are both pressed, the rhythm starts when you press a key, but does not stop when the keys are released until a pulse via C55 from IC28d pulses IC28 pin 1 low and sets the start/stop latch to stop. This occurs at the end of the second bar as previously described.

The downbeat and tempo LEDs are controlled by the output from the counter IC25. The downbeat LED always flashes on the first count. The second flash occurs halfway through the count (except for 5/4 time) which can be either 24 or 32 counts. For unusual time signatures the second flash does not occur in the right place but we considered this was relatively unimportant compared with the facility of being able to generate unusual time signatures. The second flash therefore occurs at count 13 or count 17. This is selected by the strapping behind the first six rhythm switches S1 to 6. The unit

## LOWER MANUAL PARTS LIST

Resistors - all 5% 1/2W carbon unless specified

R8,52,54,57,59,62, 65,67,76-79,87,88, 98,107,114,119, 124,125,134,135, 149, 151,164,168, 171,179,185,190, 202,283	10k	32 off	(M10K)
R39-43,203	5k6	6 off	(M5K6)
R44-51,60,139,148, 152,153,196,602	1k	15 off	(M1K)
R53,55,56,58,61, 63,64,66,80-86, 89-91,93,121-123, 128-131,156,159, 167,174,182,183, 193,194,199,200	100k	36 off	(M100K)
R69-72,94,96,97, 100,101,103,105, 106,108,110,112, 113,162,165,214	47k	19 off	(M47K)
R73-75,92	2k2	4 off	(M2K2)
R95,99	68k	2 off	(M68K)
R102,115	56k	2 off	(M56K)
R104,109,111,127, 137,138,173	33k	7 off	(M33K)
R116-118,160,560, 598	22k	6 off	(M22K)
R120,213	390k	2 off	(M390K)
R133,136	220k	2 off	(M220K)
R140,169	27k	2 off	(M27K)
R150,180,191	470R	3 off	(M470R)
R154,161,172,176, 201	100R	5 off	(M100R)
R157,166,175	1M	3 off	(M1M)
R170	470k		(M470K)
R181,192,197,198	150R	4 off	(M150R)
RV3-7	Drawbar white, 22k lin	5 off	(BR42V)
RV8	Drawbar blue, 22k lin		(BR98G)
RV14-16	Hor S-min preset 100k	3 off	(WR61R)

Capacitors

C15	15nF polyester		(BX71N)
C16,22,23	33nF polyester	3 off	(BX73Q)
C17,18,24,29	10nF polyester	4 off	(BX70M)
C19	1n5 polycarbonate		(WW23A)
C20,32,34,39	2u2 63V axial, elect.	4 off	(FB15R)
C21	22nF polyester		(BX72P)
C25	2n2 polycarbonate		(WW24B)
C26	180nF polycarbonate		(WW44X)
C27	47nF polyester		(BX74R)
C28	68nF polyester		(BX75S)
C30	1nF polycarbonate		(WW22Y)
C31	39nF polycarbonate		(WW36P)
C33	680pF ceramic		(WX66W)
C35	2n2 polystyrene		(BX30H)
C36	22uF 10V axial, elect.		(FB29G)
C37,40,43	100nF polyester	3 off	(BX76H)
C38	100nF polycarbonate		(WW41U)
C41	390nF polycarbonate		(WW48C)
C42	10uF 25V axial, elect.		(FB22Y)
C204	6u8 40V axial, elect.		(FB20W)
C219,220	100nF disc, ceramic	2 off	(BX03D)
C232-236	220pF ceramic	5 off	(WX60Q)

Semiconductors

D15-18,47-55,59,60, 62-64,66-68,72-74, 78,83,84,88	1N4148	28 off	(QL80B)
TR4,6,7,9,11-14	BC548	8 off	(QB73Q)
TR5,8,10	BC212L	3 off	(QB60Q)
IC4	M108		(YY90X)
IC5,6,11	3403	3 off	(QH51F)
IC7,8,10	4016BE	3 off	(QX08J)
IC9,12,13	uA741C	3 off	(QL22Y)
IC14,15	LM13600	2 off	(YH64U)

Miscellaneous

L1	Choke, 500mH 40R		(HX24B)
S25,26	Latchswitch, 2-pole	2 off	(FH67X)
PL2	Minicon latch plug, 3-way		(BX96E)
PL3	Minicon plug, 17-way		(BH64U)
SK2	Minicon latch housing, 3-way		(BX97F)
SK3/SKB	Jumper cable, 17-way		(BX98G)
	Minicon terminal	3 off	(YW25C)
	DIL socket, 40-pin		(HQ38R)
	Veropin 2141	2 off	(FL21X)

## RHYTHM UNIT PARTS LIST

Resistors - all 5% 1/2W carbon unless specified

R37,210,240	4k7	3 off	(M4K7)
R155,216,218,221, 235,237	100k	6 off	(M100K)
R163,228	330R	2 off	(M330R)
R186-189,207-209, 212,220,222,223, 229,231,233,234, 236	10k	16 off	(M10K)
R204-206	220k	3 off	(M220K)
R217	22k		(M22K)
R219,239	1M	2 off	(M1M)
R224-227	15k	4 off	(M15K)
R230	33k		(M33K)
R232	150K		(M150K)
RV51	Pot lin 470k		(FW07H)

Capacitors


C44,45,47-50,54, 55,57,58	100nF polycarbonate	10 off	(WW41U)
C46	330nF polycarbonate		(WW47B)
C51	220nF polycarbonate		(WW45Y)
C52	820nF polycarbonate		(WW52G)
C53	680nF polycarbonate		(WW51F)
C206	470uF 6.3V axial, elect.		(FB70M)
C207	100nF disc, ceramic		(BX03D)

Semiconductors

D19-46,56-58,61, 69-71,95-98, 100-112	1N4148	52 off	(QL80B)
D87	1N4001		(QL73Q)
D150	LED Red		(WL27E)
D151	LED Green		(WL28F)
TR15-17,19	BC548	4 off	(QB73Q)
TR18	BC212L		(QB60Q)
IC18,21,22	4081BE	3 off	(QW48C)
IC19,20	4013BE	2 off	(QX07H)
IC23,26,28	4011BE	3 off	(QX05F)
IC24	2716/M2		(QY15R)
IC25	4024BE		(QX13P)
IC27	40106BE		(QW64U)
IC29	4098BE		(QX29G)

Miscellaneous

S1-16	Latchswitch, 2-pole	16 off	(FH67X)
S22,23	Latchswitch, 4-pole	2 off	(FH68Y)
PL4	Minicon latch plug, 3-way		(BX96E)
SK4	Minicon latch housing, 3-way		(BX97F)
	Minicon terminal	3 off	(YW25C)
	LED clip, clear	2 off	(YH54J)
	DIL socket, 24-pin		(BL20W)
	Veropin 2141	6 off	(FL21X)

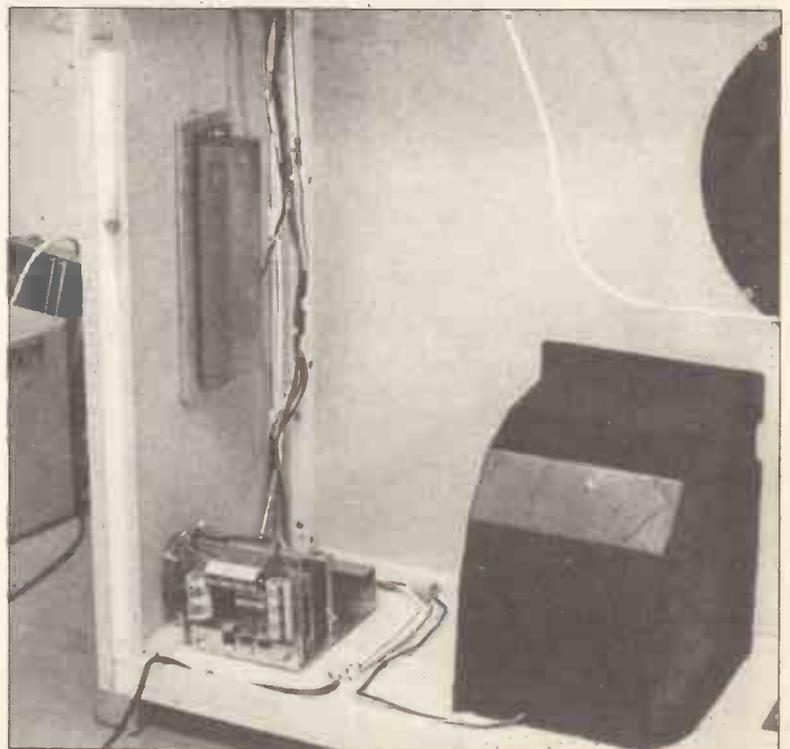

Mounting of springline and power unit.

is set for 32 counts if no connection is made and for 24 counts if a connection is made.

The count is decoded by D95 to 98 for the 32 count rhythms and D56 and 71 for the 24 count rhythms. The seventeenth count is pins 6, 9, 11 and 12 of IC25 going low together, which allows the input of IC26a to go low via R221. Pin 3 of IC26 now goes high, thus pulsing the input of IC26b high. If this corresponds with a high on pin 6 of IC26, pin 4 goes low thus removing the high from the input of IC26c which produces a high that turns on TR19 via R240 and this turns on D150 via R228. The length of this flash is determined by the charge time of C51 and R239.

The thirteenth count is pins 6 and 9 of IC25 going high simultaneously which means that the cathodes of D56 and 71 are allowed to go high via R37 and the 24-count strap. This positive-going transition is connected via D69 to C46 as in the previous case. In this case, however, the discharge time for C46 exceeds the maximum length of time possible between counts 13 and 17 and thus the flash that would have occurred at count 17 is inhibited.

The tempo LED, D151, is triggered by pins 11 and 12 of IC25 going low together, thus allowing the cathodes of D27 and 28 to be

pulled low via R210, thus turning on TR18 which causes the green LED to flash via R163.

The four latches in IC19 and 20 hold the counter melody information for each count of the rhythm. IC18c provides the vamp output to the vamp envelope shaper and IC18a, b and d provides the outputs to control the bass codes of the M108. TR15 to 17 act as inverters and level shifters. The M108 recognises this negative logic 3-bit code and internally latches it and produces a bass note and bass envelope trigger pulse TDB. The automatic bass output from IC4 pin 7 is amplified by IC6a and fed to IC2 pin 11 (see Figure 34).

Since all the CMOS in the rhythm unit is designed to run at +5V relative to -6V it is necessary to generate a -1V rail (which effectively becomes +5V). This is achieved by feeding the 0V through D87 which drops about 1V. This rail is smoothed by C206 and 207.

In the final part, next month, we shall describe the rhythm generator voicing, the audio mixing stages, the wah, rotor sound, reverb and power amp circuits to conclude the circuit descriptions. We shall also list any amendments and errors that have occurred in the series and give some playing instructions. **E&MM**

## SPECIAL PARTS FOR PROJECTS IN THIS MAGAZINE

The following items shown in parts lists in this issue of Electronics and Music Maker are not listed in the current Maplin Catalogue, but are available from Maplin Electronic Supplies Ltd at the following prices:—

BX96E	Minicon latched plug 3-way .....	20p
BX97F	Minicon latched housing 3-way .....	9p
BX98G	Jumper cable 17-way .....	£2.95
BX99H	Synwave front panel .....	£1.10
FB98G	Rubber coupling .....	60p
GA35Q	Synwave PCB .....	95p
QY15R	2716/M2 .....	£10.50
XG00A	Roll-top guides (pair) .....	£2.50
XG01B	Music stand .....	£4.00
XH53H	Matinée component identification schedule .....	40p
XY86T	Matinée main PCB .....	£50.00*
XY91Y	Matinée organ kit .....	£299.95■
XY93B	Matinée cabinet kit .....	£99.50†
XY94C	Matinée front panel .....	£17.95*
XY95D	Matinée metalwork mounting kit .....	£8.50*
XY96E	End cheeks (set of 4) .....	£6.75
XY97F	Keyboard separator .....	£1.80*
XY98G	Swell pedal housing and trim .....	£3.75
XY99H	Roll-top .....	£19.50*

\*These items are too large to be sent through the ordinary inland mail and they will therefore be despatched by carrier. Please add £6 towards the cost of carriage to any order containing one or more of these items.

†Carriage is charged extra on this item; please add £20 to your order.

■Carriage is charged extra on this item; please add £15 to your order.

Send orders to:


Maplin Electronic Supplies Ltd.,  
P.O. Box 3, Rayleigh, Essex.

**MAPLIN**

Having trouble containing yourself?

Then why not  
**BOX CLEVER**  
with one of our

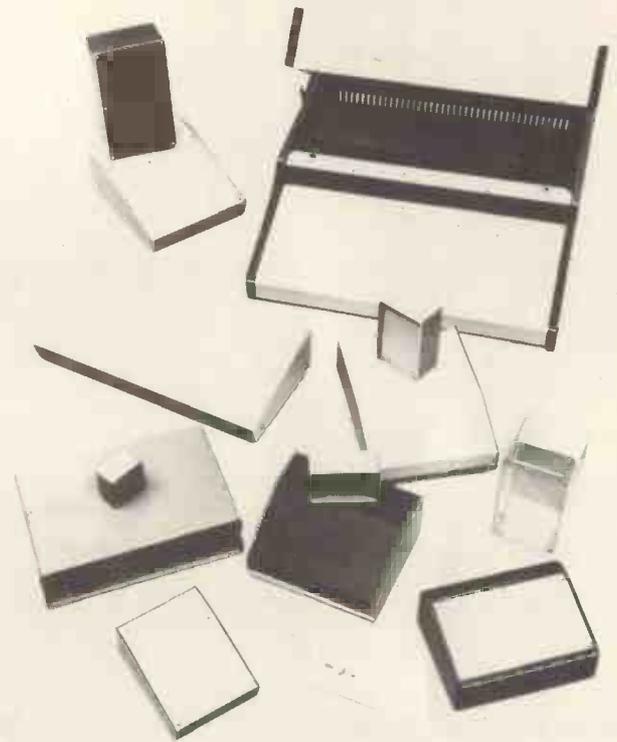**STANDARD or CUSTOMISED  
BIMENCLOSURES**



**Instrument Cases**  
Small ABS Desk Consoles  
Low Profile Keyboard Consoles  
Easy Access Hinged Lid Consoles  
Diecast and ABS Multi-Purpose Boxes  
All Metal or Genuine Wood Panelled Consoles

**BIMCASES**  
**BIMBOXES**  
**BIMCONSOLES**

**FOR PROFESSIONAL QUALITY  
AT REALISTIC PRICES**

**BOSS**  
**INDUSTRIAL MOULDINGS LTD**

2 Herne Hill Rd, London SE24 0AU, England  
Telephone 01-737 2383 Telex 919693  
Cables & Telegrams: LITZEN LONDON SE24

E&MM/7

# CIRCUIT MAKER

Readers contributions can be an original feature or constructional article describing electronic or electro-musical equipment which is ideally a complete building block that will


aid the circuitmaker. All ideas and circuits presented for publication should have been proved before submission and should include a circuit diagram and explanatory text.

## Logic Power-Up Resets

It is often necessary to ensure that a logic circuit powers up in some predetermined state, and simple circuits can be added to achieve this. Indeed, on many occasions the reset circuit can be designed around spare gates in the main circuit.


The most simple circuit holds any reset lines high for a period after power is applied, after which the resets are taken low (a). The circuit is based around a Schmitt trigger, which generates a clean switching signal from a slowly rising, or noisy, input signal. In this case a slowly rising voltage is obtained from an RC network, connected directly to the gate inputs and the supply rail. As power is applied the voltage on the capacitor starts to rise until the threshold of the trigger is reached, at which point the gate output goes low. This inversion is simply due to the fact that most logic Schmitt triggers are derivations of the traditional gates, in this case an inverter.

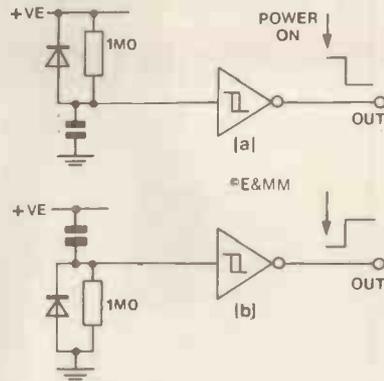This circuit may be improved with the addition of a diode as shown. Without the diode the capacitor may not discharge during a short power



supply break, and thus a reset would not be generated. The diode allows the capacitor to discharge to the power rail as it collapses, and thus a reset will always be generated if the power drops long or low enough to corrupt the logic states.

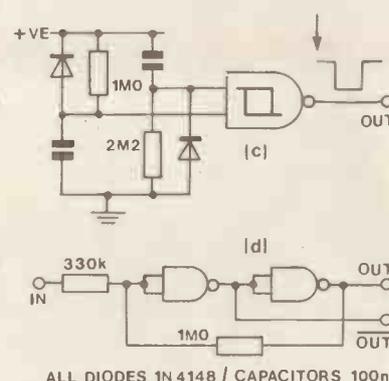A reset of the opposite sense (from low to high as for TTL) can be obtained by transposing the resistor and capacitor (b). In this case however the diode is essential, preventing the destruction of the gate at power down, since without the diode the gate input would be taken to -5 volts due to charge stored on the capacitor. The



ALL DIODES 1N4148 / CAPACITORS 100n

diode also provides response to momentary power collapses.

Some reset circumstances, particularly with shift registers, require that a proper high-low-high clock sequence is generated, perhaps to strobe a load input. This can be obtained by combining the two above reset circuits (c). In this case the type (a) RC network should have the lower time constant. At power up, one gate input is high, the other low. The NAND output is thus high. Both capacitors start to charge, but the integrator (type (a)) reaches the threshold of its input first, thus both inputs are high,

and the output drops. As the other network charges, the other input to the gate falls, and hence the output returns to the high state where it remains.

If a proper Schmitt trigger is unavailable (often no other use will be found for the rest of the Schmitt gates in a package), a discrete trigger can be made from any two inverting gates, including NAND, NOR or simple inverters. These should be connected in series, with a positive feedback resistor connected as (d). This resistor provides a current flow to help 'snap' the trigger over quickly once it starts to change state referred to as hysteresis action. These form of triggers do have advantages over their single gate counterparts. Firstly, both polarities of reset are available without need for further inverters, and secondly, the degree of positive feedback, and hence the threshold voltage, can be chosen simply by altering the feedback resistor.

In the circuits shown the values are chosen for CMOS logic, making use of the high gate input impedances. The circuits may be used for TTL, but it is necessary to reduce the values of all the resistors to 1k and increase the capacitors accordingly.

## Syntom Trigger Input

The Syntom drum synthesiser, described in the April '81 issue of E&M, is a very versatile instrument capable of producing a wide range of useful effects. In its original form, however, the unit can only be triggered by way of the internal microphone, no trigger input for use with a synthesiser being provided.

Fortunately, it is quite easy to add a trigger input to the Syntom, and a simple method for doing this is given here. The trigger signal must be a positive pulse between 3 and 15 volts in amplitude, and have a duration of a few milliseconds or more.

Figure 1 shows the small additional circuit required to provide the trigger input. TR2 has its collector and emitter terminals connected across the input of the main Syntom circuit and effectively feeds a small, negative pulse to this input if it is switched on briefly. Due to the high gain of the amplifier at the input of the Syntom, this small input pulse is sufficient to send the output of IC1 fully positive, and thus activate the envelope shaper and other circuits (see Figure 1 of the original article).

TR2 will in fact be switched on if a positive input pulse of adequate amplitude is applied to JK2. C5 ensures that TR2 is only pulsed on briefly regardless how long the input pulse may happen to be. R30 is a current

limiting resistor which protects the base-emitter junction of TR2.

### Construction

As there is very little excess space inside the Syntom unit, it is strongly recommended that the method of construction described here is followed precisely or it may be found that the additional components cannot be accommodated inside the unit.

Start by mounting the input jack on the rear panel in the position shown in Figure 2. Note that with the addition of this socket there is not enough space for the battery to fit horizontally across the rear of the unit so it must be fitted vertically into the case, as close to the microphone as possible.

The other components are mounted on a small piece of 0.1in. matrix Veroboard which measures 5 strips by 7 holes. The component layout is shown in Figure 3. There are no breaks in any of the copper strips and the leadout wires of TR2 should be trimmed quite short so that the component panel is as compact as possible.

A Veropin or a short piece of thick, non-insulated wire is soldered to the board at the point where it must connect to JK1. When this pin or wire is soldered to the appropriate tag of JK1, it should be found that the board is held firmly in place. Be careful to


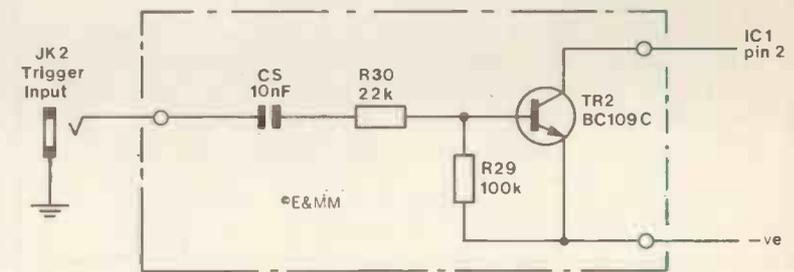


Figure 1

position the board where it will not come into contact with the jack plug when inserted into JK1.

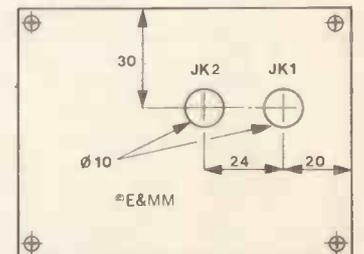The other two leads from the component panel are then wired in place; these can conveniently connect to the Syntom printed circuit board at the two pins which connect to X1 but be careful to connect the leads the right way round. After connecting the earthing lead from JK1 to JK2, as shown in Figure 3, the unit is ready for testing and use.



All dimensions in millimetres

Figure 2

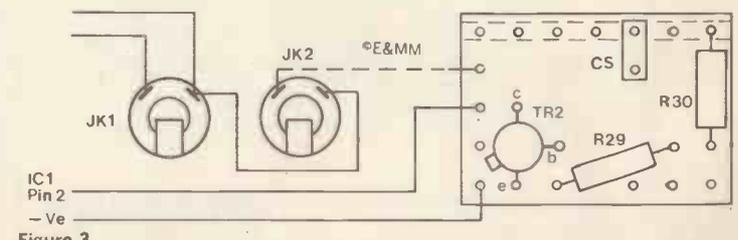


Figure 3

# Audio Cassette auto-cue

Ray James, Hayes, Middlesex

One of the main disadvantages of music on cassette instead of record is the difficulty encountered when trying to find a particular track. It would therefore be useful to be able to select a required track and then wind/re-wind to it, the tape stopping automatically at the required position.

One method of doing this is to code information onto the tape between tracks and detect these codes during winding. This involves complicated modifications to the cassette mechanism and is impractical for the home constructor.

Another method, which forms the basis of this design, is to use the tape counter on the cassette deck as a reference and index all the tracks on the tape. A required track can then be found by setting the counter value of that track on a set of switches and comparing this value with the tape counter during a fast wind, stopping the wind when the numbers are equal.

The circuit design here was intended as an add-on for the JVC/Tandberg cassette cassette mechanism although it could be employed with any mechanism provided that a stop solenoid is available. Furthermore, the provision of an electronic counter and display to replace the mechanical counter means that construction becomes much easier because a sloping window for the original counter is not required; indeed a very attractive unit could be made by locating the counter in the meter area.

The circuit (shown below) works by counting the pulses derived from the reed switch on the mechanism. The number of pulses is divided by 6 using IC2 and fed to a three-digit bcd counter (IC3,4,5). The output from this counter is compared with the settings on a bcd switch when they are equal, the a=b output of the comparator goes high and energises the stop solenoid by means of

the Darlington transistor. A three digit display is connected to the counter; this consists of three 74LS47 decoder drivers and three common anode displays.

The direction of the counter is determined by the logic level on the up/down line, which in turn depends on the operational key pressed. Obviously an up count is required for play and fast wind, this corresponds to a logic low and is achieved by connecting two reed switches in parallel, one on each key. In addition, the automatic function is disabled simply by switching off the drive to the stop solenoid if required.


The accuracy of the system is adequate to cue most album tracks, an error of 0.4 inch of tape being typical, this equates to a mere 250ms.

### Operation

The tape should be rewound and the counter reset by pressing the reset switch which zeros the counter.

The tape is wound onto any required points and the counter reading noted for future use. When this is done any number may be set on the bcd switches and wind or rewind pressed accordingly. Naturally if the direction chosen is wrong the tape will wind to the end without automatically stopping.

NOTE: Some readers may not be familiar with the 'bus' type of drawing used in the diagram. Diagrams for logic circuits such as this generally have large numbers of wires all following the same path, and to simplify the drawing they are all drawn as a single line, with an accompanying label to state how many wires are in the line. It is convention to mark all pins with the wire name or number at both ends, though in many circumstances the bus structure is quite clear in itself. For example in the diagram IC4 pin 2 is indicated as going to IC7 pin 12 by virtue of their relative positions.

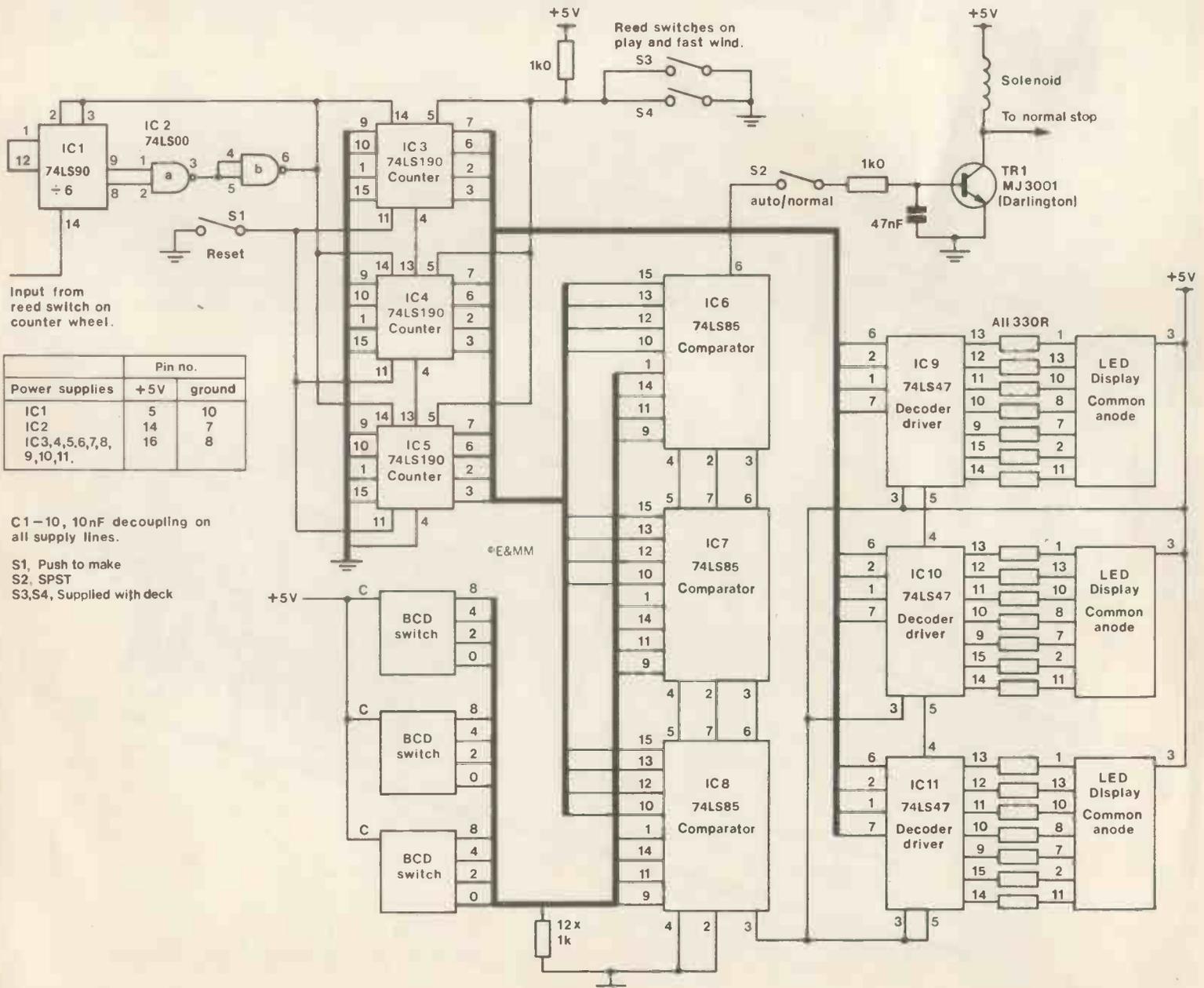

	Pin no.	
Power supplies	+5V	ground
IC1	5	10
IC2	14	7
IC3,4,5,6,7,8,9,10,11.	16	8

C1-10, 10nF decoupling on all supply lines.

S1, Push to make  
S2, SPST  
S3,S4, Supplied with deck

**EXPANDABLE  
POLYPHONIC  
SYNTHESISER**



Cabinet size 31.1" x 19.6" x 7.6" rear 3.4" front

**COMPLETE KIT  
ONLY**

**£320.00 + VAT!**  
(single voice)

Plug in extra  
Voices — Kit price £52 + VAT  
(£48 — + VAT if ordered with kit)

# TRANSCENDENT POLYSYNTH

By brilliant design work and the use of high technology components the Polysynth brings to the reach of the home constructor a machine whose versatility and range of sounds is matched only by ready built equipment costing thousands of pounds. Designed by synthesiser expert Tim Orr and being featured in Electronics Today International, this latest addition to the famous Transcendent family is a 4 octave (transposable over 7½ octaves) polyphonic synthesiser with internally up to 4 voices making it possible to play simultaneously up to 4 notes. Whereas conventional synthesisers handle only one at a time.

The basic instrument is supplied with 1 voice and up to 3 more may be plugged in. A further 4 voices may be added by connecting to an expander unit, the metalwork and woodwork of which is designed for side by side matching with the main instrument. Each voice is a complete synthesiser in itself with 2 VCOs, 2 ADSRS, a VCA and a VCF (requiring only control voltages and a power supply, the voice boards are also suitable for modular systems). One of these voices is automatically allocated to a key as it is operated. There are separate tuning controls for each VCO of each voice. All other controls are common to all the voices for ease of control and to ensure consistency between the voices.

Although very advanced electronics the kit is mechanically very simple with minimal wiring, most of which is with ribbon cable connectors. All controls are PCB mounted and the voice boards fit with PCB mounted plugs and sockets. The kit includes fully finished metalwork, solid teak cabinet, professional quality components (resistors 2%, metal oxide or metal film of 0.5% and 0.1%), nuts, bolts, etc.

main instrument. Each voice is a complete synthesiser in itself with 2 VCOs, 2 ADSRS, a VCA and a VCF (requiring only control voltages and a power supply, the voice boards are also suitable for modular systems). One of these voices is automatically allocated to a key as it is operated. There are separate tuning controls for each VCO of each voice. All other controls are common to all the voices for ease of control and to ensure consistency between the voices.

Although very advanced electronics the kit is mechanically very simple with minimal wiring, most of which is with ribbon cable connectors. All controls are PCB mounted and the voice boards fit with PCB mounted plugs and sockets. The kit includes fully finished metalwork, solid teak cabinet, professional quality components (resistors 2%, metal oxide or metal film of 0.5% and 0.1%), nuts, bolts, etc.

**Kit also available as separate packs**

Pack	Price
POLY 15 Pots, switches, diodes, Cs for VOICE PCB	£4.80
POLY 16 PCB for plug in voice	£8.20
POLY 17 Rs, Cs, presets, connectors for one voice	£16.30
POLY 18 IC's, IC skts, diodes for one voice	£27.50
POLY 19 Transformer 0-120-240, 17-0-17, 0-7.7	£6.30
POLY 20 Pitch bend control	£3.90
POLY 21 Misc parts e.g. jack sockets, knobs, mains switch etc.	£13.00
POLY 22 Ribbon cable, ribbon cable connectors, mains cable	£8.45
POLY 23 Fully finished metalwork and fixing parts	£25.60
POLY 24 Solid teak cabinet	£25.80
POLY 25 Construction manual	£1.50
Total cost for individually purchased packs for single voice instrument	£355.15
Special kit for 4 voice expander kit including connectors	£295.00

Pack	Price
POLY 1 Pair of PCB's for multiplex cct. K.B. contacts	£9.50
POLY 2 IC's IC sockets, Rs, Cs, for multiplex cct.	£8.20
POLY 3 Superior quality keyboard	£32.25
POLY 4 Contacts and bus bars	£12.00
POLY 5 Double sided plated through PCB for digital control and pitch/gate generator cct.	£17.25
POLY 6 Rs, Cs, heat sink for fitting to Pack 5	£10.50
POLY 7 IC's IC sockets, diodes for fitting to Pack 5	£31.30
POLY 8 Double sided mother board (for plug-in voices)	£18.90
POLY 9 Rs, Cs, connectors for mother board	£14.10
POLY 10 IC's IC sockets, Trs, heat sinks for mother board	£13.10
POLY 11 PCB for master controls (left of section marked VOICES)	£18.80
POLY 12 IC's IC sockets, diodes, Trs, Rs, Cs for master control PCB	£9.30
POLY 13 Pots, Switches for master control board	£11.80
POLY 14 PCB for VOICE controls	£11.80
	£6.80

ADSR IC CEM 3310 ..... £4.00  
VCO IC CEM 3340 ..... £6.00

ICs and details of all packs in our **FREE CATALOGUE**

**ALL PRICES VAT EXCLUSIVE**

Quote E&MM on all enquiries  
SECURICOR DELIVERY: For this optional service (U.K. mainland only) add £2.50 (VAT inclusive) per kit.  
SALES COUNTER: If you prefer to collect your kit from the factory call at Sales Counter Open 9 a.m. — 12 noon, 1—4.30 p.m. Monday-Thursday.

**MANY MORE KITS ON PAGES 2 & 3**  
**POWERTRAN**  
ANDOVER (0264) 64455

**PRICE STABILITY:** Order with confidence. Irrespective of any price changes we will honour all prices in this advertisement until August 31 1981 if this month's advertisement in Electronics & Music Maker is quoted with your order. Errors and VAT rate changes excluded.

**EXPORT ORDERS:** No VAT. Postage charged at actual cost plus £1.00 handling and postal documentation.

**U.K. ORDERS:** Subject to 15%\* surcharge for VAT. No charge is made for carriage, \*or at current rate if changed.

**OUR CATALOGUE IS FREE! WRITE OR PHONE NOW!**  
**POWERTRAN ELECTRONICS, Portway Industrial Estate, Andover, Hants SP10 3WW**

Please send me the following kits.....  
I enclose cheque/postal orders for.....  
Name..... Address.....

# CAR DIGITAL PETROL GAUGE

by Michael Kennedy

Get an accurate indication of petrol in your tank down to the last drops

**PARTS COST GUIDE**  
£14.50

'The needle's in the red again. Not to worry, it's not right anyway — at least a gallon left.' Two miles later, 'Blast! Out of petrol. The gauge says empty too!' Famous quotes of the average motorist. From these two comments it is apparent that the only relevant part of the average petrol gauge is the low zone. So to satisfy this requirement we feature a useful fuel indicator with digital readout and critical level indication.

The unit, in fact, gives a digital display of the percentage amount of fuel remaining, a full tank representing 100% and producing a readout of 9 until 10% of the fuel has been used at which point

the display changes to 8. Thus there is a 10% safety factor built into the gauge. When the indicator goes to 0 (i.e. you're down to 10% fuel), two red LEDs start to flash warning you it is time to buy more fuel. When both the display and the LEDs extinguish, the tank is virtually empty and you've got your last chance to get to a garage!

## Circuit

The circuit diagram for the petrol gauge is shown in Figure 1. The input voltage for the circuit is

derived from the car's petrol tank sensor which, in conjunction with R4, forms a potential divider producing virtually 0 volts with a full tank and about 5 volts when the tank is empty. To divide this input range into the ten divisions required, the National LM3914N bargraph IC is used. This IC contains a buffer input stage, a potential divider chain, comparators, and a precise 1.2 volt reference source.

The outputs of the LM3914N are capable of sinking the current and voltage applied to them and thus act as zero voltage switches.

To encode the outputs of IC1 into signals capable of being displayed on a common anode, seven segment display they are passed through a diode matrix (D1 to D47).

Each segment of a seven segment display is given a code letter, as shown in Figure 2, which also contains a table detailing which segments must be lit to produce each of the ten digits. Where a tick is shown in this table, a diode must be connected between the appropriate IC output and the segment required. Each segment is therefore given a bus-


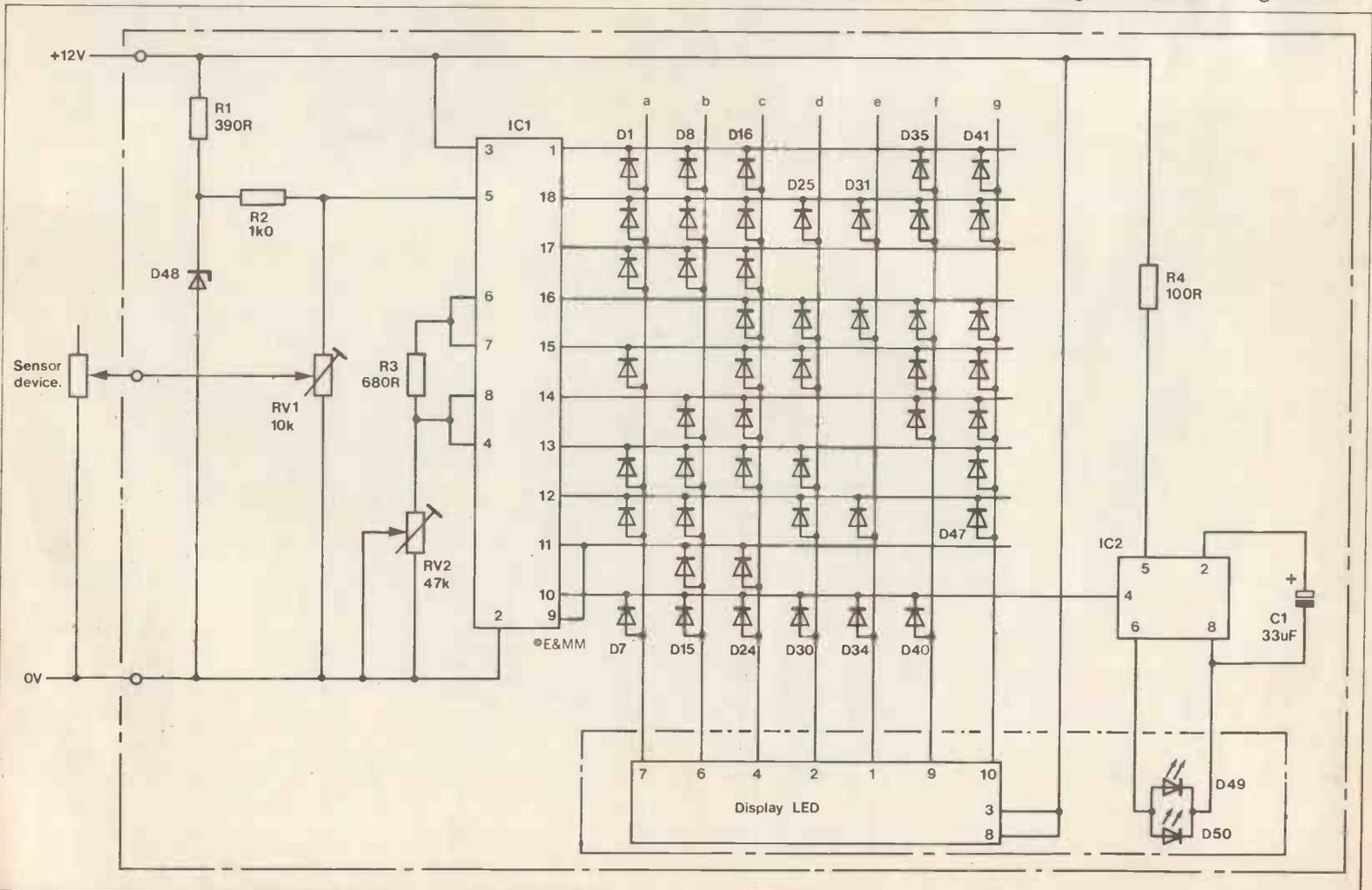


Figure 1. Circuit diagram for digital petrol gauge.

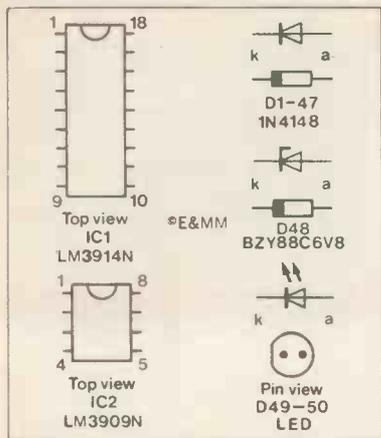

bar to which the diode anodes are connected, the diode cathodes going to the appropriate output pin bus-bars.

The output from IC1 pin 10 also goes to the 0 volt pin of IC2. IC2 is the National LM3909N LED flasher device which, when enabled, flashes the two LEDs to give the low level warning.

The input level from the sensor can be adjusted by means of RV1, while RV2 sets the internal voltage reference of IC1. Adjustment of these two components is dealt with later. R3 and D48 stabilise the supply to the sensor circuits so that variations in the supply voltage do not cause changes in the number displayed by the unit. It is not necessary to stabilise the supply to IC1 as its internal circuits provide any necessary stabilisation.

### Construction

Most of the components are fitted onto a 0.1in. pitch Veroboard panel measuring 24 strips by 50 holes. This is a standard size in which the board is sold. Figure 3 shows the component layout of this board. The two mounting holes are 3.3mm in diameter.

The seven segment display and the two LED indicators are

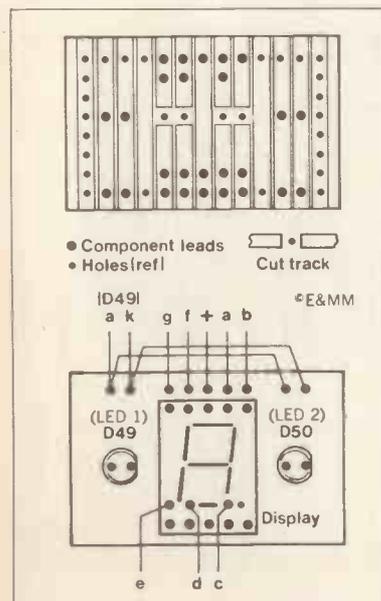


Figure 4. Display board details.


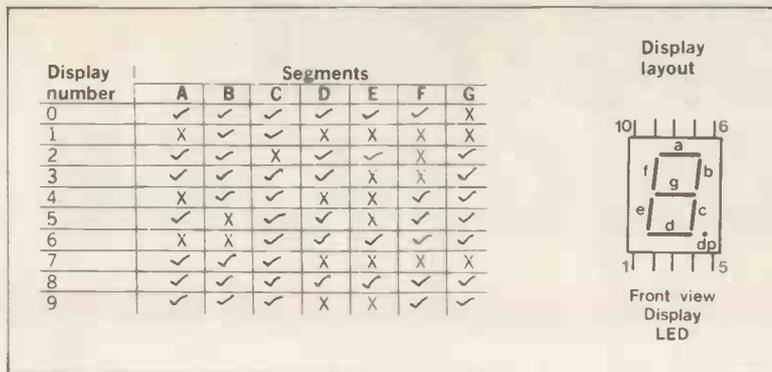


Figure 2. Display segment connection.

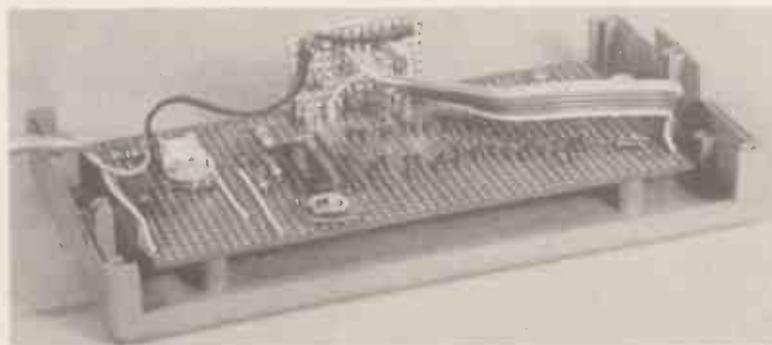

Component board and display board mounting.

mounted on a separate, smaller board, shown in Figure 4. Veropin pins are fitted to this board at the points where it connects to the main panel. A couple of extra pins are fitted to the board and these are soldered to two matching pins fitted on the main board, so that the display panel is mounted at right angles to the main board. The diagrams and interior photograph of the unit should clarify the method of mounting and eliminate any problems that may arise.

Ribbon cable can be used to wire the two boards together and will give a neat finish. However, ordinary connecting wire can be used if preferred.

The specified Verocase makes a convenient housing for the project since the main component board will fit onto the front pair of mounting pillars of this case, using the mounting screws provided with the case. The front panel of the case requires a rectangular display window to be cut out at the appropriate place. This cut-out can be made by

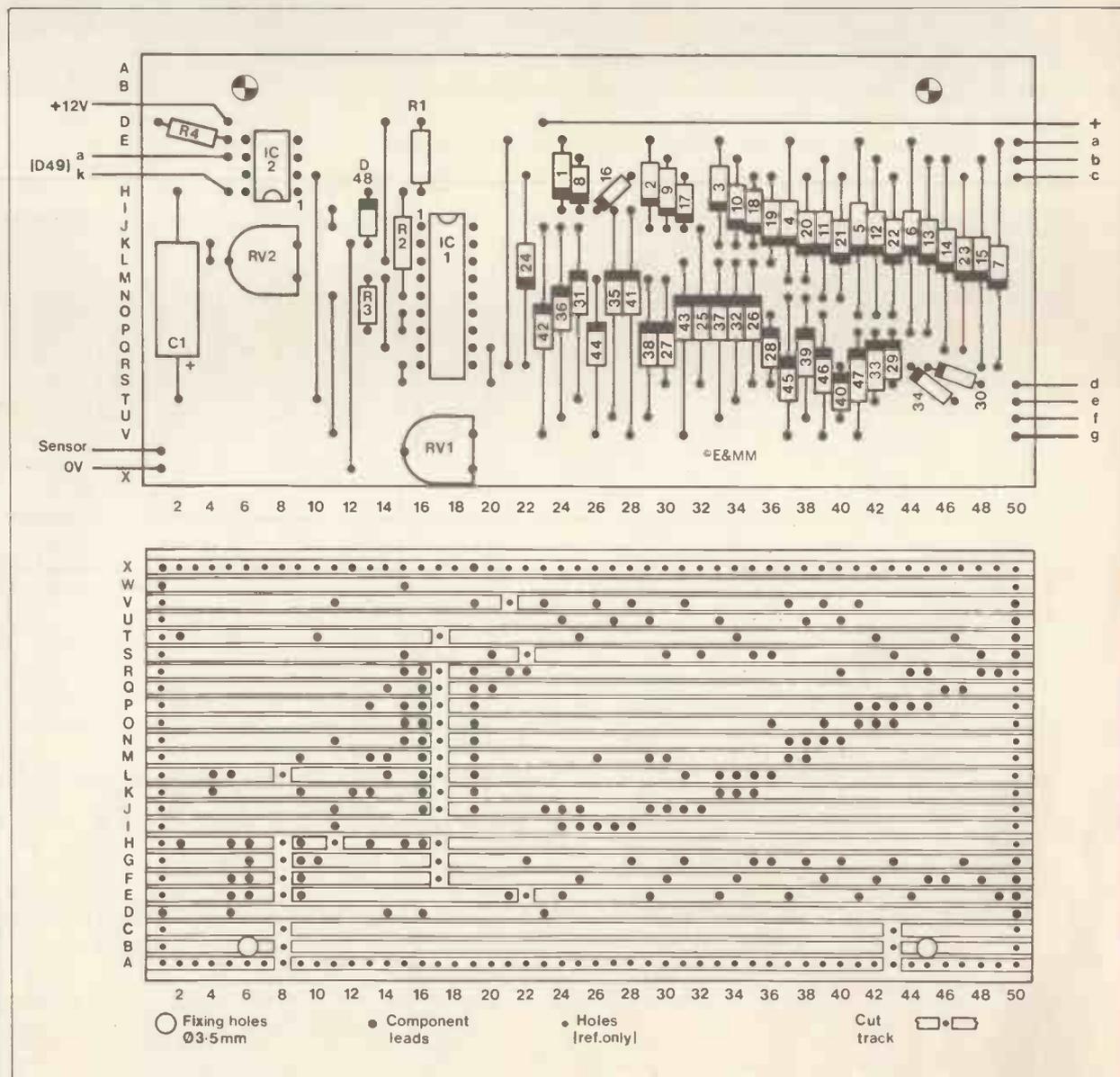


Figure 3. Wiring details and main board layout.




# Micromusic

A series that focuses on using the popular microcomputers for making music.

## Notate Your Nascom

### How to play tunes without any extra hardware except an audio amplifier and speaker

by Don Finlay

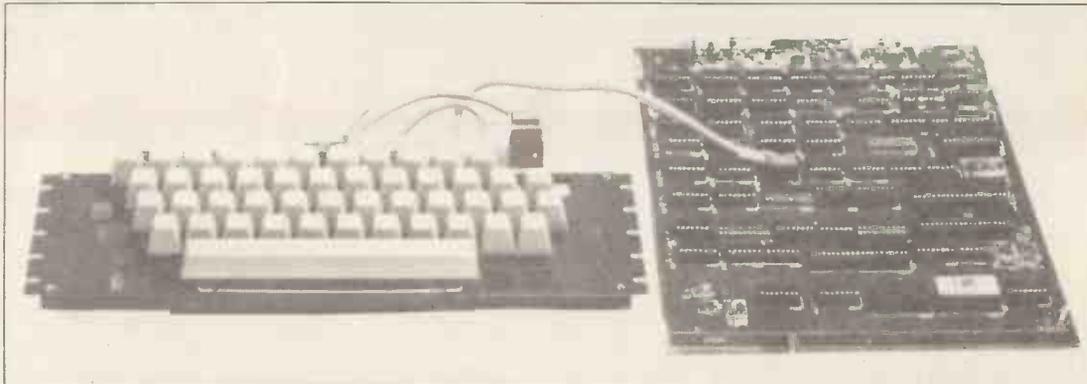

Programming in machine code is difficult, so they say. But why do I find it so addictive? Once I start to work out a problem, it occupies my mind in every spare moment. It is like the challenge of a good puzzle, but much more satisfying because the solution is useful and leads on to other things. After building a Nascom 1, I spent a great deal of time in devising programs for playing tunes with controllable waveforms, using a little extra hardware. Even on Christmas Day, I was sitting down with a pencil and paper in a few odd moments!

This Nascom is being developed to control equipment in the Electronic Music Studio of The City University, where music students are given experience in recording and compositional techniques. It has 32K memory; a 16-channel analogue output board to 12-bit precision; 2K Tiny BASIC (surprisingly useful for controlling the analogue output board); ZEAP assembler; V&T Electronics cassette deck, about to be installed; and a PIO board on order. One of the things we hope to do soon is 'place' sounds accurately in a multi-speaker environment, using the analogue board to control a bank of VCA's. There are many other ways we could use the equipment, the main difficulty being to find enough time and manpower to build and develop hardware, and write software.

Although some personal computers have an optional tune-playing routine using a squarewave signal from just one line of an output port, I have never seen one for the Nascom. When the Scamp was launched, several years ago, I collected some information on a music program for a hand-held 'toy' which was demonstrated. It completely flummoxed me at the time, as there was far too much jargon for a beginner to take in at the meeting (what were these 'flags' they kept talking about?) and the music program wasn't explained. Yet it is the only simple tune program I have managed to acquire.

Probably this will cause a flood of letters from readers saying I haven't done a proper search, and these routines are available all over the place, for any system. If so, I'm sure E&MM will be pleased to publicise them!

Here, then, is my method of playing tunes on a Nascom 1, devised in some more spare moments (over Easter!) before assembly. It goes without saying that machine code is essential, for both speed and timing. There is plenty of room even in the 4K version, as the playing routine occupies only 54 (hex) bytes, and tunes can be fitted into the remaining RAM taking only 2 bytes per note.

The playing routine, as shown in the listing, starts at 0E00. It may be better to move it to 0F00, making room for a longer tune sequence from 0C50; I didn't use this because the ZEAP assembler uses 0F00 onwards, making the task a little easier than my earlier efforts, which were all hand-assembled. If this move is made, the two CALL instruction bytes at 0F1D and 0F30 must be changed from 0E to 0F. All other jumps are relative, so need no alteration. The £ sign in the listing indicates that the number which follows is hex, as required by ZEAP. Most assemblers use a following H, but one soon gets used to this alternative. I have omitted the line numbers which ZEAP incorporates, and typed the listing by hand as I wasn't able to get the use of a printer at the time of writing this article.

Anyone who wants just to use the routine can type in the second column of the listing at the addresses indicated in the first column. Then a 'tune table' needs entering at 0C50. A sample tune is shown in Table 1; this has slight relevance to an event due to take place in July. The tune table consists of pairs of bytes, the first in each pair being a duration code and the second one a note frequency code.

Also needed, of course, is connection to an audio amplifier, earpiece or headphones. The program produces identical squarewaves on all lines of Port 4, so any one of these may be connected through a volume control (a 5-volt squarewave is a very large signal) to the amplifier or high-impedance 'phones.

Finally, the program will run when executed from 0E00, and return to the Nascom monitor afterwards.

Usually people like to write their own tunes, so the codes for notes and their durations have to be looked up from Table 2. The duration is entered

0E00	3E0F	LD A,£0F	;	EXECUTION ADDRESS
0E02	D306	OUT (06),A	;	SET PIO FOR OUTPUT
0E04	21500C	LD HL,£0C50	;	START OF TUNE TABLE
0E07	1E00	LD E,00	;	
0E09	56	LD D,(HL)	;	DURATION INTO DE
0E0A	7A	LD A,D	;	
0E0B	FEFF	CP £FF	;	TEST FOR END CODE
0E0D	CA8602	JP Z,£0286	;	IF SO, GO TO MONITOR
0E10	23	INC HL	;	
0E11	4E	LD C,(HL)	;	HALF-PERIOD INTO C
0E12	7E	LD A,(HL)	;	ALSO INTO A
0E13	FE00	CP 00	;	TEST FOR PAUSE CODE
0E15	282E	JR Z,PAUSE	;	IF SO, JUMP
0E17	3EFF	LD A,£FF	;	
0E19	D304	OUT (04),A	; 7	SET OUTPUT HIGH
0E1B	CD3C0E	CALL DELAY	; 11	
0E1E	00	NOP	; 17	START OF 47-CYCLE
0E1F	00	NOP	; 4	BALANCING DELAY
0E20	00	NOP	; 4	
0E21	00	NOP	; 4	
0E22	00	NOP	; 4	
0E23	00	NOP	; 4	
0E24	00	NOP	; 4	
0E25	00	NOP	; 4	
0E26	00	NOP	; 4	
0E27	00	NOP	; 4	
0E28	3E00	LD A,00	; 7	END OF DELAY
0E2A	3E00	LD A,00	; 7	
0E2C	D304	OUT (04),A	; 11	SET OUTPUT LOW
0E2E	CD3C0E	CALL DELAY	; 17	
0E31	EB	EX DE,HL	; 4	DURATION INTO HL
0E32	ED42	SBC HL,BC	; 15	SUBTRACT HALF-PERIOD
0E34	EB	EX DE,HL	; 4	STORE DURATION
0E35	3802	JR C,NXTNTE	; 12(7)	NEW NOTE
0E37	18DE	JR CYCLE	; 12	TEST TAKES 47 CYCLES
0E39	23	INC HL	;	POINT TO NEXT DURATION
0E3A	18CB	JR DURATN	;	
0E3C	7E	LD A,(HL)	; 7	
0E3D	0601	LD B,1	; 7	OUTER LOOP
0E3F	10FE	DJNZ LOOP1	; 8(13)	INNER LOOP
0E41	3D	DEC A	; 4	
0E42	20F9	JR NZ LOOP2	; 12(7)	LOOP OF 31
0E44	C9	RET	; 10	
0E45	1B	DEC DE	; 6	
0E46	7B	LD A,E	; 4	
0E47	B2	OR D	; 4	
0E48	00	NOP	; 4	START OF 36-CYCLE DELAY
0E49	00	NOP	; 4	
0E4A	00	NOP	; 4	
0E4B	00	NOP	; 4	
0E4C	00	NOP	; 4	
0E4D	00	NOP	; 4	
0E4E	00	NOP	; 4	
0E4F	00	NOP	; 4	
0E50	00	NOP	; 4	END OF DELAY
0E51	20F2	JR NZ,PAUSE	; 12(7)	TOTAL 62
0E53	18E4	JR NXTNTE	;	

Listing of tune-playing routine for a Nascom 1. Figures in the remarks column show the number of cycles taken by the instructions.

first. Values given are approximate, since the duration varies with the note for unavoidable reasons explained later. I have shown the values I used in

the sample tune; those at the left form a basis for notes formed of minim, crotchet, quaver, semiquaver and demi-semiquaver, for instance, with

their dotted versions at the right. The first note in the sample tune has 30, indicating a duration of about 3/8 second, and 59, indicating the note F above middle C.

OC50	30	59	10	5F	30	6A	10	5F
OC58	20	59	20	4F	20	46	10	59
OC60	10	00	20	42	20	46	20	4F
OC68	20	59	20	5F	20	6A	20	5F
OC70	20	78	30	59	10	5F	30	6A
OC78	10	5F	20	59	20	4F	20	46
OC80	20	34	10	3A	30	46	30	4F
OC88	1Q	46	80	59	FF			

Table 1. Coding of a sample tune. Each note is coded by one byte for duration, followed by one for frequency. The end is signalled by FF.

### There's Method In It

For those who would like to know how the program was devised, here is my approach.

We start by assuming that a squarewave signal is required, i.e. the line is set high and low for equal times alternately. This uses the OUT instruction in a Nascom system. To get the required frequency, we must arrange to have a controlled time delay between the OUT's. In the absence of an external timer chip and interrupt system, this has to be done by software loops, requiring knowledge of how long each instruction takes. The OUT instruction itself takes 11 cycles of clock frequency, or 5 1/2 microseconds.

At this stage, where we start to look at Z80 instructions, it is necessary to be aware of the range of instructions, what they will do, and the timing. I have found a Zilog booklet, giving the instructions in condensed form, immensely helpful here, but the manufacturers' programming manual gives more detail, as do several books on Z80 programming. One strange-looking instruction which is very useful is seen at address 0E3F of the listing: DJNZ LOOP1. This decrements the B register and gives a jump if not zero. The mnemonic doesn't obviously relate to the B register - you just have to know this. The jump would take 13 cycles, but no jump, i.e. program continues, takes only 8.

To get a variable delay, we enter a number into a register and subtract 1 at regular intervals. When the result is zero, the delay is ended. So the B register is often used for this purpose. As it turns out in this case, it is better to use it as an inner timing loop with the main count-down in an outer loop, because if we increment the number initially loaded into B we get an extra 13 cycles of delay, whereas using any other register would take longer. The outer loop here counts down using the accumulator, which is loaded first with the frequency code.

Since the delay is proportional to this code, good resolution and accurate frequency generation require it to be as large a number as possible. Hence we try to use FF hex, or 255 decimal, or near to it, for the longest half-cycle period, which is at the lowest frequency we are to use. (256 is possible, but we reserve the maximum code of 00 to indicate a pause. Why does 00 give a maximum delay? I leave the reader to spot this.) My note table was chosen to span three octaves up from C at 130.8Hz, which has a corresponding periodic time of 7645 microseconds. If we now

divide 7645 by 255 we get the length of time to be occupied by the counting loop. A greater length means the divisor is reduced, spoiling the resolution; but a smaller length means we can't get the full period at the lowest frequency. So 7645/255 is in fact a minimum, and it comes to almost exactly 30. We should aim, then, at getting a counting loop as near as possible to 30 microseconds per cycle; but since these will be used twice in every cycle in the countdown, we need 30 'T cycles' (Z80 clock cycles) in each half-period, with the Nascom 1's 2-MHz clock.

The loop shown between addresses 0E3D and 0E42 takes 31 cycles, as can be seen by adding the four cycle lengths for these instructions. The DJNZ line is a little luxury which enables a single change in the previous line to slow down the tune, although it also reduces the pitch. I found this very useful in checking my sample tune, which I loaded with one or two errors; changing 0E3E from 1 to 3 made it play more slowly, and I was able to spot the errors more easily. This change added 26 cycles to the delay loop.


Loading A at the beginning of DELAY, and returning from the sub-routine, take an extra 7 and 10 cycles respectively, so the total delay is 17 + 31\*n cycles, where n is the note frequency code.

Having got the note sounding, we need a method of deciding when to end it. One possible method is to decrement a counter by 1 after each cycle, but this would mean a different delay code for each note frequency, and would be very trying to enter. The Scamp system I mentioned earlier did this, in order to shorten and simplify a ROM program in a device not intended for flexibility.

There is a simple alternative. Each cycle lasts for 31\*n microseconds, ignoring a small (we hope) extra time for loads and tests which we will check later. So let us subtract n from the duration code after every cycle; we have then subtracted effectively the length of the cycle from the code, measured in 31-microsecond units. The duration code must then be simply the number of 31-microsecond periods required. Since we need a large number, to get notes of about a second in length, the duration code is made the high-order byte 'd' in a 16-bit number with low-order byte zero. Then d\*256\*31 is the duration in microseconds. For example, 30 hex gives 380928, or 0.38 second. Duration is loaded into the Z80's register pair DE at programme steps 0E07 to 0E09.

The subtraction routine is done at TEST. To do a 16-bit subtraction, we must use the HL pair - but this is also used as a pointer to the tune table and we have to save its previous contents. What a beautiful instruction EX DE, HL turns out to be! It not only gets DE into HL but saves the pointer in DE until we are ready to swap back. It couldn't be more tailor-made for the job. All this takes 47 cycles, however, so we waste 47 cycles in the first half-cycle to preserve our squarewave, although we needn't really do so as square-waves aren't all that interesting.

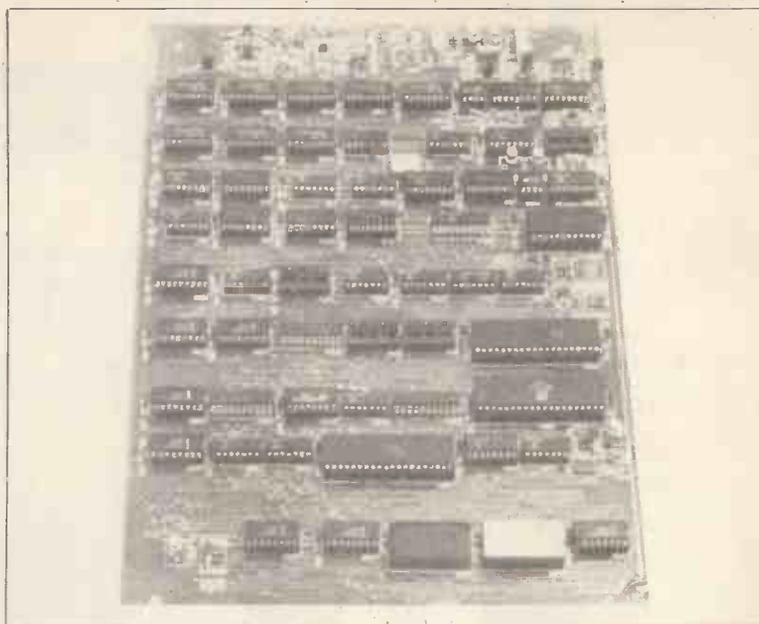The true half-cycle time can be calculated now, allowing for 35 cycles



Nascom 1 microprocessor board.

NOTE	CODE	NAT	#
	b		
C	1B		
B	1F	1D	
A	23	21	1F
G	28	26	23
F	2B	2B	28
E	31	2E	
D	37	34	31
C	3A	3A	37
B	42	3E	
A	4A	46	42
G	54	4F	4A
F		59	54
E	64	5F	
D	71	6A	64
C		78	71
B	87	7F	
A	98	8F	87
G	AB	A1	98
F		B5	AB
E	CB	C0	
D	E5	D8	CB
C		F3	E5
PAUSE	00		

DURATIONS (APPROXIMATE)			
80	1 sec	CO	1 1/2 sec
40	1/2	60	3/4
20	1/4	30	3/8
10	1/8	18	3/16
08	1/16	0C	3/32
FF	'END OF TUNE' CODE		

Table 2. Composer's aid: note codes are shown against standard musical notation, and a possible set of duration codes is given. Pause is signalled by 00 in the note code position, and end of tune by FF in the duration code position, in the tune table.

to output high or low and call delay; 47 for test or balance; and delay itself, 17 + 31\*n. The total is 99 + 31\*n, giving a full-period time of 99 + 31\*n microseconds. The required values of n for the different frequencies are calculated from equating this formula to the period time. The result is about 3 less than the number of 31-microseconds loops in the period, and leads to the values in Table 2.

Pauses are as important in music as sounds. To simplify coding, it is best to use the same duration code for a pause as for a note. Since every subtraction in the note routine corresponds to n\*31 microseconds, we need a 31-microsecond loop in PAUSE, i.e. 62 T-cycles, and count this down by ordinary decrements instead of subtractions. Note another quirk of the Z80: decrementing DE

doesn't set any flags, so we have to test for zero by ORing D and E.

We can now check the inaccuracies caused by the load and test parts of the cycle. At the top of the musical scale, we have a large number of cycles in a given duration, so the duration is extended more than at the bottom by the fixed 99 microseconds per cycle. Taking extremes: top C, with duration 30 hex for example, will have INT (48\*256/27) cycles, i.e. 455 cycles, each of which takes 99 + 27\*31 = 936 microseconds, giving a total duration of 425880 microseconds. Bottom C, on the other hand, with the same duration, will have only 50 cycles of 7632 microseconds, giving a total of 381600 microseconds, which is about 10% less. The error is not noticeable for most purposes; if it proves to be, it is still easier to make a small adjustment to a duration code than to have a different one for every note.

For convenience in a first approach, I have classified code 30 as giving 3/8 second in the duration table. This is slightly low compared with the figures I have just shown, but is within about 2% at the bottom end of the range.

### Next?

Finally, we may be stimulated into thinking how to alter and improve things. Can we alter speed without altering pitch? At step 0E32, the duration code is decremented. We could decrement faster by repeating this instruction, more than once if wanted, and this would speed the playing. I haven't tried it because it means reassembling the following program. And inserting a counting loop round this instruction slows the basic program. We could also write a program to multiply or divide all the duration codes in the tune table. We could experiment with pulse waveforms. We could have a sequence table, which plays several tunes or parts of tunes in the order specified. We could interact with BASIC to make loading even easier, generate random sequences, or compose. And so it goes on. Is anyone else hooked?

E&MM

# Micromusic

## Atari Music Composer Cartridge

The Atari Music Composer is a plug-in ROM for use with Atari computer systems. The cartridge can be used with either the 400 or the 800 personal computer, and in both cases it replaces the BASIC cartridge. Facilities for saving your compositions enable both disk-based and cassette-based systems to be used, and obviously the amount of memory the system has governs the length of your composition.

Our cartridge was tested on the Atari 800 with 48K of memory, providing the facility to store up to 13,880 notes. The number of notes available for composing, with a given memory capacity, is as follows:

48K: 13,880 These figures were obtained  
32K: 9,784 after the disk operating  
16K: 1,592 system had been loaded

The 21-page manual provided is in four parts: a general description, a sample session, a description of the music file structure and a quick reference guide. The manual assumes you have some musical knowledge, but not that you are used to using a keyboard. Each keyboard entry is explained step by step. This, combined with printed examples of computer responses and screen displays, means that anyone unfamiliar with keyboards should have very little problem. Although a difficult item to write a manual for, we felt that the description of the various functions and commands left much to be desired.

### Choosing the Menu

The programs contained in the ROM are menu driven. In other words, you are given a list of options to choose from. This, in most cases, leads to a further sub-menu, from which parameters can be set. When the cartridge is inserted into the machine you immediately enter the main menu. This lists the sub-menus (Figure 1). The options available are outlined below:

**EDIT MUSIC.** This leads to a sub-menu (Figure 2), the first item of

which is PHRASE. This resembles a phrase in music, in that it groups notes into sections. However, unlike a musical phrase, it does not denote accents or context, but rather enables you to move sections of music around in your arrangement. There are 9 different phrases available.

**METER.** This sets the time signature, which defaults to 4/4 unless told otherwise. Since there are no accents available this is of limited use, but combined with another function, CHECK MEASURES, it becomes impossible to exit from a bar that does not contain the correct number of notes.

**KEY SIG.** You can write in any key by simply typing the number of #'s or b's needed. Accidentals may also be written in as they occur.

**TEMPO.** This is programmable between 1 and 9, 1 being the fastest.

Having set these parameters it is now possible to proceed and write the first phrase. Two musical staves are displayed on the screen - the treble and bass clefs. This is because there is a choice of pitch which ranges over 3 octaves.

For the purposes of writing you are provided with a cursor, which may be moved horizontally back and forth. Thus enabling you to delete or insert

notes in the required position. Also displayed are: an indication of the phrase you are in, the bar number, the number of notes free, and an entry prompt. An example of how easy it is to enter notes is given in Figure 3.

After setting the measure of bar number, the notes are entered as follows: the first letter is the note required N, F or S will denote natural flat or sharp respectively. Then you need the octave numbers. 3 to 6 are valid, and after one note has been entered you stay in that octave unless you specify otherwise. Next is the length of note required, which ranges from W for a 'whole' note or breve, down to T for a 32nd note or demi-semi quaver. Lastly, if the note is tied or dotted you must type in T or . respectively. Rests are entered as R, plus desired length.

As each note is entered the notes of that measure are played, which is a help if you are composing, but can be a hindrance if you are simply entering notes from sheet music. Once composition of the phrases is complete, you can proceed to the ARRANGE MENU.

**ARRANGE MENU.** The first thing asked for is which of the 4 voices you wish to arrange. After entering the relevant number you are presented


with the heading ARRANGE VOICE (plus the number you entered) and a list of line numbers from 1 to 20 on the left hand side of the screen (Figure 4). One of these numbers is a different colour from the rest. This represents the cursor and can be moved vertically using normal cursor controls, thus allowing deletion or insertion of lines. At the bottom of the screen you are presented with a row of 8 letters: C,D,G,M,P,S,T,V. If M is selected the full ARRANGE MENU is displayed (Figure 5). The functions provided are: COUNT. This enables you to set up a loop and is used in conjunction with GOTO; DISPLAY can be used to show the notes on the screen as they are played; GOTO enables you to jump back and forth in your arrangement and can be used with COUNT for repeating passages a specified number of times; PLAY PHRASE is self explanatory, and is accompanied by a number from 1 to 9 denoting the phrase you wish to be played; STOP, as in all other menus, exits to the next menu; TRANPOSE allows you to transpose a phrase up or down, in semitone steps. Numbers from -36 to +36 are valid, but have to be used with some caution, as it is possible to transpose music out of the 3 octave range. If this happens the machine



Figure 1. Main MENU.



Figure 2. EDIT MUSIC.

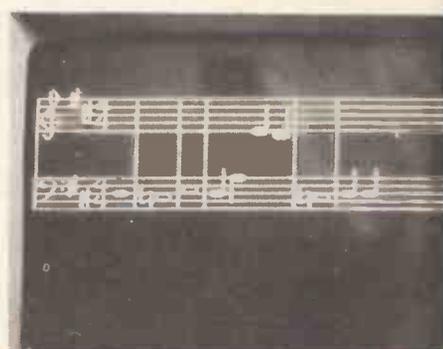

Bass Clef music.


# ELECTRONIC GAMES

## COLOUR CARTRIDGE T.V. GAME



SEMI-PROGRAMMABLE T.V. GAME  
+ 4 Cartridges + Mains Adaptor  
Normal Price £73  
NOW REDUCED TO: **£39.50** inc VAT

## DATABASE T.V. GAME

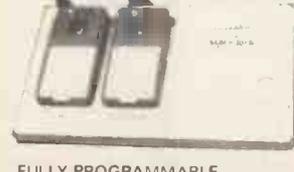


FULLY PROGRAMMABLE CARTRIDGE T.V. GAME  
14 Cartridges available  
Normal Price £87.86  
NOW REDUCED TO: **£59** inc VAT

## ATARI T.V. GAME




The most popular T.V. Game on the market with a range of over 40 cartridges including SPACE INVADERS with over 112 games on one cartridge.  
**£95.45** inc VAT

## SPACE INVADERS

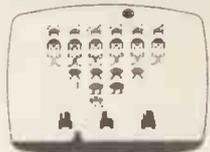

Hand-held Invaders Games available **£19.95**  
+ Invaders Cartridges available to fit  
ATARI RADOFIN ACETRONIC/PHILIPS G7000  
+ Cartridges also available for  
MATTEL/TELENG/ROWTRON/  
DATABASE/INTERTON

## CHESS COMPUTERS

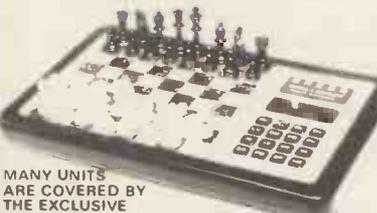

MANY UNITS ARE COVERED BY THE EXCLUSIVE SILICA SHOP 2 YEAR GUARANTEE

We carry a range of over 15 different Chess computers:  
Electronic Chess **£29.95**  
Chess Traveller **£39.95**  
Chess Challenger 7 **£79.00**  
Sensory 8 **£119.00**  
Sensory Voice **£259.00**  
**SPECIAL OFFERS:**  
VOICE CHESS CHALLENGER  
Normal Price £245 NOW **£135.00**  
SARGON 2.5/BORIS 2.5  
Normal Price £273.70 NOW **£199.95**  
All prices include V.A.T.

## TELETEXT



## ADD-ON ADAPTOR **£199** inc VAT

THE RADOFIN TELETEXT ADD-ON ADAPTOR

Plug the adaptor into the aerial socket of your colour T.V. and receive the CEEFAX and ORACLE television information services

THIS NEW MODEL INCORPORATES:

- Double height character facility
- True PAL Colour
- Meets latest BBC & IBA broadcast specifications
- Push button channel change
- Unnecessary to remove the unit to watch normal TV programmes
- Gold-plated circuit board for reliability
- New SUPERIMPOSE News Flash facility

## SPEAK & SPELL



Normal Price £49.95  
NOW REDUCED TO:

**£39.50** inc VAT

Teach your child to spell properly with this unique learning aid Fully automatic features and scoring. Additional word modules available to extend the range of words.

## ADDING MACHINE

### OLYMPIA HHP 1010

Normal Price £57.21  
NOW REDUCED TO:

**£34** inc. VAT

Uses ordinary paper  
No need to buy expensive thermal paper  
Fast add listing PRINTER CALCULATOR. 2 lines per second. 10 digit capacity  
Uses normal adding machine rolls. Battery or mains operated  
Size 9 1/4" x 4 3/4" x 2 1/2"  
(Mains adaptor extra)

## 24 TUNE ELECTRONIC DOOR BELL




Normal Price £19.70  
NOW REDUCED TO:

**£12.70** inc. VAT

Plays 24 different tunes with separate speed control and volume control. Select the most appropriate tune for your visitor, with appropriate tunes for different times of the year!

## MATTEL T.V. GAME

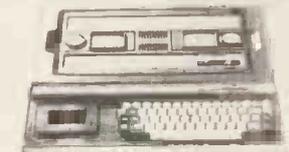

The most advanced TV game in the world 20 cartridges available Add-on KEYBOARD coming soon to convert the MATTEL to a home computer with 16K RAM. Fully expandable and programmable in Microsoft Basic. Other accessories will be available later in the year.  
**£199.95** inc VAT

## HAND HELD GAMES EARTH INVADERS



These invaders are a breed of creature hitherto unknown to man. They cannot be killed by traditional methods — they must be buried. The battle is conducted in a maze where squads of aliens chase home troops. The only way of eliminating them is by digging holes and burying them.  
**£23.95** inc. VAT

## THE OLYMPIA — POST OFFICE APPROVED TELEPHONE ANSWERING MACHINE WITH REMOTE CALL-IN BLEEPER

This telephone answering machine is manufactured by Olympia Business Machines, one of the largest Office Equipment manufacturers in the U.K. It is fully POST OFFICE APPROVED and will answer and record messages for 24 hours a day. With your remote call-in bleeper you can receive these messages by telephone wherever you are in the world. The remote call-in bleeper activates the Answer/Record Unit, which will at your command repeat messages, keep or erase them, and is activated from anywhere in the world, or on your return to your home or office. The machine can also be used for message referral, if you have an urgent appointment, but are expecting an important call. Simply record the 'phone number' and location where you can be reached. With optional extra



bleepers (£13 each) this facility can be extended to colleagues and members of the family. Using a C90 standard cassette you can record as many as 45 messages. The announcement can be up to 16 seconds long and the incoming message up to 30 seconds long. The machine is easy to install and comes with full instructions. It is easily wired to your junction box with the spade connectors provided or alternatively a jack plug can be provided to plug into a jack socket. Most important, of course, is the fact that it is fully POST OFFICE APPROVED. The price of £135 (inc. VAT) includes the machine, an extra-light remote call-in Bleeper, the microphone message tape, A/C mains adaptor. The unit is 9 3/4" x 6" x 2 1/2" and is fully guaranteed for 12 months. The telephone can be placed directly on the unit — no additional desk space is required.  
**£135** inc. VAT

## PRESTEL VIEWDATA



The ACE TELCOM VOX1000 Prestel Viewdata adaptor simply plugs into the aerial socket of your television and enables you to receive the Prestel/Viewdata service in colour or black & white.

### Features —

- Simplified controls for quick, easy operation
- Special graphics feature for high resolution
- State-of-the-art microprocessor controller
- Standard remote telephone keypad with Prestel keys 'A' - 'B'
- Auto dialler incorporated for easy Prestel acquisition
- True PAL colour encoder using reliable IC — chroma filter and delay line incorporated for minimum picture interference/maximum fidelity
- Includes convenient TV — Prestel switchbox
- Easily connected to standard home or office telephone lines
- Fully Post Office approved

**SPECIAL PRICE £228.85** inc. VAT

**FOR FREE BROCHURES — TEL: 01-301 1111**



For free illustrated brochure and reviews on our range of electronic games, please telephone 01 301 1111. Free delivery service available. To order by telephone please quote your name, address and ACCESS BARCLAYCARD number, and leave the rest to us. Post and packing Free of Charge. Express 48hr delivery service available.  
• CALLERS WELCOME. Demonstrations daily at our Sidcup shop, open from 9am-6pm Monday-Saturday (Early Closing Thursday 1pm. Late Opening Friday 6pm).  
• 2 YEAR GUARANTEE. All goods are covered by a full year's guarantee and many are further covered by our exclusive Silica Shop 2 year Guarantee.  
• MONEY BACK UNDERTAKING. If you are unsatisfied with your purchase and return it within 7 days we will give you a full refund.  
• AFTER SALES SERVICE. Available on all machines out of guarantee.  
• COMPETITIVE PRICES. We are never knowingly under-sold.  
• HELPFUL ADVICE. Available on the suitability of each machine.  
• CREDIT FACILITIES. Full credit facilities available over 12, 24 or 26 months at competitive rates of interest.  
• PART EXCHANGE SCHEME. Available on second-hand machines.  
• CREDIT CARDS WELCOME. Access Barclaycard, Diners Club, American Express.

## SILICA SHOP LIMITED

1-4 The Mews, Hatherley Road, Sidcup, Kent DA14 4DX  
Telephone: 01-301 1111 or 01-309 1111



will do the best it can; VOLUME. This is adjustable between PP and FF.

This set of instructions provides a very powerful, high level music programming language. A sample arrangement for one voice is shown below.

- 1 DISPLAY
- 2 VOLUME MF
- 3 COUNT 3
- 4 PLAY PHRASE 1
- 5 GOTO 4
- 6 TRANSPOSE 12
- 7 COUNT 12
- 8 PLAY PHRASE 2
- 9 GOTO 8

The next items on the main menu are SAVE and RETRIEVE. Upon entering the SAVE menu (Figure 6), the first thing to do is enter a file name. Having done this you will be asked WHICH? At this point the following options are open to you: save EVERYTHING, ALL PHRASES, ALL VOICES, PHRASE X (a particular phrase), VX (a particular voice). RETRIEVE offers you the same facilities.

Files saved using the Music Composer can be used from BASIC and a comprehensive breakdown of the file structure is given in the manual provided. The details are too complex to describe in a review, but basically each file is made up of four sections. Each record starts with a header byte enabling you to locate the starting point. A phrase record contains pitch and duration values for a given phrase. The voice record is the actual program for playing one of the four voices. There is also a miscellaneous information record in which the time signature, tempo and key signature are stored.

The DOS instruction in the main menu is for use with disk-based systems and when selected, returns control of the machine to the disk operating system, thus enabling use of all usual DOS commands. This command is non-destructive and on exiting the disk operating system, using option B which is RUN CARTRIDGE, you will find your composition intact.

LISTEN enables you to hear everything from the arranged programs.

## Making Music

Having explained the functions provided we shall now relate our experiences of using the cartridge. We decided to approach this review in two ways. From the point of view of users with little or no musical knowledge we thought a good test would be

Figure 3. Entering Music.

to enter sheet music and for those of you who are musically adept or more adventurous, we composed a 24-bar piece of original work.

In order to enter sheet music it is obviously necessary to identify the notes their duration, and symbols such as rests and sharps, flats, etc. With a little patience and a prompt table, those with no musical knowledge should be able to master this in a short period of time. The manual is also very useful here as it lists note durations, octave spacings and symbols.

After a quick trip to a local music shop we had our eager hands on some popular music for piano. We found the best approach was to initially number the bars and then write the code for each note immediately beneath it. At this point we assigned each of the four voices in the music to a phrase. We then typed each phrase in turn, only to realise that many sections of each phrase (the verses and choruses) were repeated and we should have

split the phrases up further and then used the ARRANGE facility to play them in the correct order. This entails more time spent on planning, but much time is saved at the keyboard and the possibility of typing errors is reduced.

Upon listening to the result it was obvious that we had made a number of errors. Some of these, such as a note in the wrong octave, were quickly located and we found the cursor controls very effective for correcting these errors. Other errors were harder to find. The answer is to take your time and get it right in the first place. Although most sheet music can be entered, the machine has difficulty in coping with some aspects, not least of which is the lack of emphasis on individual notes. This can make some music sound noticeably different. Triplets, some turns and some trills are not possible and obviously rullando, crescendo, diminuendo and glides etc. are out.

For our second test we entered a

four-part composition having phrase one as the melody line, phrase two as the first harmony, phrase three as an arpeggio rhythm and phrase four as bass. We changed things as we went along, replacing a triplet with a single note, for example, and altering notes which though musically correct, sounded slightly wrong on the computer when the four phrases were played together. This, we suspect, is because all the voices have the same timbre. CHECK MEASURES proved to be invaluable as it is easy to forget the step to the next bar when concentrating on writing the notes, and when you try to exit the error message MEASURE TOO LONG is displayed so the error may be corrected almost as soon as it is made.

## Conclusions

Considering that this is the cheapest way of generating computer music, we feel the 'Music Composer' represents outstanding value for money. The emphasis is more on fun than on serious music making though for anyone who has always wished to know something about music, but has been put off by text books and terminology, this could be a fun way to learn. As a classroom teaching aid it would definitely hold a student's attention, without too much teacher involvement. For the professional musician it promises much, but you may soon find yourself restricted by this particular composer's limitations. However it is, after all, written for a home computer system. And no doubt more sophisticated programs and peripherals will become available in due course.

We wish to thank Ingersoll Ltd. for the loan of a cartridge, and a pre-production Atari 800.

Tony Search  
Graham Daubney

E&MM



```

ARRANGE VOICE
COUNT
DISPLAY
GOTO LINE
FOR THIS MENU
PLAY PHRASE
STOP
TRANSPOSE
VOLUME
SPACE BAR TO GO ON
    
```

```

ARRANGE MENU
COUNT
DISPLAY
GOTO LINE
FOR THIS MENU
PLAY PHRASE
STOP
TRANSPOSE
VOLUME
SPACE BAR TO GO ON
    
```

```

SAVE MUSIC
EVERYTHING
ALL PHRASES
ALL VOICES
PHRASE X
VOICE X
STOP
FN?
    
```

Figure 4. ARRANGE VOICE.

Figure 5. ARRANGE MENU.

Figure 6. SAVE MUSIC.

# MAPLIN for ATARI

AUTHORISED DEALER



## The World-beating ATARI PERSONAL COMPUTERS

3 consoles available

**Atari 400 with 16K RAM (AF36P) £340**

**Atari 400 with 32K RAM (AF37S) £395**

**Atari 800 with 16K RAM (AF02C) £625**

(expandable to 48K)


All consoles when connected to a standard UK colour (or black and white) TV set can generate the most amazing graphics you've ever seen.

### Look at what you get:

- \* Background colour, plotting colour, text colour and border colour settable to any one of 16 colours with 8 levels of illuminance!
- \* Video display has upper and lower case characters with true descenders, double and quad size text and inverse video.
- \* 57-Key keyboard (touch type on Atari 400) and four function keys.
- \* Full screen editing and four-way cursor control.
- \* 29 keystroke graphics and plottable points up to 320 x 192 (160 x 96 only with 8K RAM).
- \* 40 character by 24 line display.
- \* Extended graphics control and high speed action using a DMA chip with its own character set.
- \* Player missile graphics.
- \* Four programmable sound generators can be played individually or together and each has 1785 possible sounds playable at any one of eight volume settings, for game sounds or music.
- \* Full software control of pitch, timbre and duration of notes in 4-octave range.
- \* Four joystick or paddle ports, sounds output to TV.
- \* BASIC cartridge and 10K ROM operating system and full documentation.



Atari 400 Console

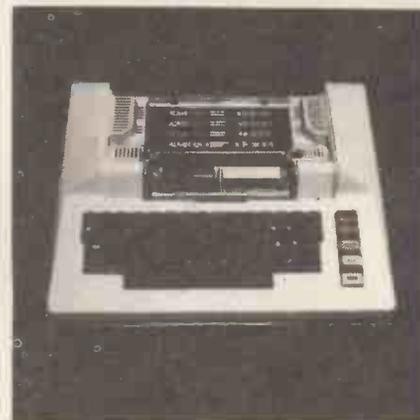

Atari 800 Console (with cover removed)

### MORE HARDWARE

Atari 410 Cassette Recorder (AF28F)	£45
Atari 810 Disk Drive (AF06G)	£325
Atari 822 40-column Thermal Printer (AF04E)	£240
Atari 850 Interface (AF29G)	£120
Joystick Controllers (AC37S)	£13.95
Paddle Controllers (AC29G)	£13.95
16K RAM Memory Module (AF08J)	£65

MUCH MORE FOR ATARI COMING SOON

### SOFTWARE

Lots and lots of amazing software for Atari available during June 1981.

- ★ Word Processor ★ VISI-CALC
- ★ ADVENTURE GAMES ★ Arcade Games
- ★ Trek Games ★ ASSEMBLER & DISASSEMBLER ★ FORTH ★ Teaching
- ★ 3D GRAPHICS ★ Character Set Generator

SEND S.A.E. NOW FOR OUR LEAFLET XH52G available JUNE

### SPECIAL PACKAGE OFFER

Disk-based system for £725!  
With Le Stick  
The Atari 400 Console  
Special 32K RAM Module  
Atari 810 Disk Drive  
Disk Operating System  
Documentation  
Interconnecting Leads  
Everything in "Look at what you get" list.  
Can any other computer on the market offer all this at anything like this price?

### VERSAWRITER

12½ x 8in. drawing board. Drawing on board is reproduced on TV via Atari with 32K RAM and Disk Drive. Closed areas may be filled in with one of 3 colours. Text may be added in any one of 4 fonts. Paint brush mode: select size of brush and paint away. Air brush mode: shade in your drawing - colour and density is up to you. Plus many more features. S.a.e. for price and further details.

# MAPLIN

Maplin Electronic Supplies Ltd  
P.O. Box 3, Rayleigh, Essex.  
Tel: Southend (0702) 552911/554155

### LE STICK

For Atari Computer or Video Game  
Replaces standard joystick, but much easier to use. Internal motion detectors sense hand movements. Large pushbutton on top of Stick. Squeeze Stick to freeze motion. A MUST for SPACE INVADERS, STAR RAIDERS & ASTEROIDS.  
ONLY £24.95 (AC45Y)

Note: Order codes shown in brackets. Prices firm until August 30th 1981 and include VAT and Postage and Packing. (Errors excluded.)

Demonstrations at our shops from June 9th 1981. See Atari at 284 London Road, Westcliff-on-Sea, Essex. Tel: (0702) 554000 and at 159-161 King St., Hammersmith W6. Tel: 01-748 0926

# BASICALLY BASIC

Graham Hall, B.Sc.

This regular series will attempt to teach BASIC to those who would like to use it for any home, business, scientific or musical application, but have no previous programming experience.

## The IF Statement

So far in this series the IF statement has been used to compare a variable with a constant to test for equality. Different actions can then be taken depending on the result of the comparison. For example, the statement:

```
20 IF C=10 THEN GOTO 50
```

Compares the contents of the variable C with the constant 10. If C contains a value of 10, program execution branches to line 50; otherwise it continues with the statement immediately following line 20. Thus a conditional branch has been made according to the value of C.

The '=' symbol in the above statement is being used as a 'relational operator' (the 'comparison relational operator'). It is one of six relational operators in BASIC. Table 1 shows the six symbols used to represent relational operations. Using these symbols with the IF THEN statement makes it possible to determine relationships such as relative size. For example, the statement:

```
20 IF C>10 THEN 50
```

Compares the contents of the variable C with the constant 10. The branch to line 50 occurs when C contains a value which is greater than 10.

The IF statement can also be used to compare two variables or two expressions. For example, the following statement compares the result of two expressions:

```
50 IF B↑2>4*A*C THEN GOTO 10
```

(NOTE: the IF statement can send program execution back to a previous line as well as ahead.)

Some versions of BASIC allow the GOTO part of the statement to be omitted so that only the line number branched to is specified. For example:

```
10 IF C=A THEN GOTO 90 is the same as:
```

```
10 IF C=A THEN 90
```

for some versions of BASIC.

IF statements can contain executable statements other than the GOTO statement. For example:

```
10 IF B↑2>4*A*C THEN PRINT "ROOTS ARE REAL"
```

(This statement could be used as part of a program dealing with 'quadratic equations'.)

**RELATIONAL OPERATOR** — a symbol used in the BASIC language to determine a relationship of relative size between:

- i) two variables,
- ii) a variable and a constant,
- iii) a variable and an expression,
- iv) an expression and a constant,
- v) two expressions.

For example, the relational operator 'less than' (<) can be used as follows:

```
10 IF A<0 THEN PRINT "NEGATIVE"
```

## Multiple Statements on a Line

Each numbered line of a BASIC program requires a minimum amount of space in computer memory. Most versions of BASIC allow you to have more than one statement on a single program line; thus saving memory space because the total number of program lines is reduced. In a line containing more than one statement, a special character called a 'separator' is used between the statements. The separator enables the computer to distinguish each new operation. The symbol used as a separator varies according to which version of BASIC is used. The most commonly used symbols are a backslash (\) or a colon (:). You should consult the relevant operator user manual to check for the correct separator.

The following program uses colons as separators:

```
10 LET X=4 : LET Y=5 : LET Z=6
20 PRINT : PRINT X*Y+Z
30 END
```

Three numbered statement lines have been saved by using more than one statement on a line. Line 10 assigns a constant to each of three variables. Line 20 outputs a blank line and then the result of an arithmetic expression involving the three variables. To make the program more readable it is a good idea to put a space each side of the colon, although space often becomes vital when fitting statements on a line and may not allow this. The computer ignores the space when it 'reads' the program.

Multi-statement lines are especially useful when used with IF statements. Earlier we saw that if the condition specified in an IF statement is not fulfilled, the program ignores that statement line and continues execution at the next numbered line. Thus, using an IF THEN multi-statement line the execution of more than one statement can depend on the result of a comparison. For example:

```
10 IF F>0 THEN PRINT "F IS POSITIVE" : GOTO 50
```

The computer will print the message and branch to line 50 if the condition 'F>0' is true, but neither will be executed if the condition is false.

As you write more BASIC programs you will find that multi-statement lines help to organise a program and increase the usefulness of the IF statement. Also the memory space saved will enable larger programs to be written using the same amount of memory. This is important when memory space is limited.

## The INPUT Statement

Already we have examined how an assignment can be made to a variable by using a LET statement: The 'data' which is to be assigned to a variable is specified when the program is typed into the computer. There are several other methods for informing the computer of the value of variables. One of them is the INPUT statement. The INPUT statement allows the computer user to assign values to variables while the program is running and to change that data each time the program is run.

Consider the following program:

```
10 LET A=3
20 LET B=4
30 PRINT A*B
40 END
```

Lines 10 and 20 use the LET statement to assign constants to the variables A and B. The variables are then operated on, and the result printed by line 30.

Now let us use the INPUT statement to assign this data when the program executes:

```
10 INPUT A,B
20 PRINT A*B
30 END
RUN
```

When the program is run it asks you to input to the terminal the values to be assigned to A and B. Your input is requested by a question mark (?) prompt. For example, when you type the RUN command the program prints: ? Program execution then stops and waits for you to type values for A and B. When more than one number is to be input each number is separated by a comma. So, to assign 3 to A and 4 to B type after the question mark prompt: 3, 4

After you type the values and the RETURN key the program will continue to run automatically, and in this example will print the result of A multiplied by B which is 12. When the program is run again different values for A and B can be specified.

If you do not type enough values for the number of variables in the program another prompt is output and so on, until a value has been typed for each vacant variable. If you type the RETURN key instead of a value in response to the prompt, BASIC assumes the value to be zero. If the input character is non-numeric it will be rejected by the computer and an error message will be output to the terminal. (The actual message displayed will depend on the version of BASIC you are using.) The computer will then output the prompt again to allow you to type in the correct input. Later in this series we will show how BASIC enables strings of characters to be input to a program.

It is good programming practice to output a message using the PRINT statement before an INPUT statement requests data. This message will remind the program user of what the INPUT is to be used for. For example, the previous program can be modified as follows:

```
10 PRINT "INSERT VALUES FOR A AND B"
20 INPUT A,B
30 PRINT A;"*";B;"=";A*B
40 END
```

Some versions of BASIC allow the INPUT statement itself to contain the reminder, if the reminder is enclosed in quotation marks. For example:

```
10 INPUT "INSERT VALUES FOR A AND B";A,B
20 PRINT A;"*";B;"=";A*B
30 END
```

The semicolon between the reminder message and the two variables causes the program to print the message and the question mark prompt on one line as follows:

```
INSERT VALUES FOR A AND B?
Your input should follow after the string and prompt. After you type the RETURN key, the answer appears on the terminal.
```

### Statement Review

The following BASIC program contains examples of BASIC statements and techniques discussed so far in this series:

```
10 REM—NUMBER GUESSING GAME
20 LET X=37 : REM—NUMBER TO BE GUESSED
30 PRINT "I'M THINKING OF A NUMBER FROM 1 TO 100"
40 PRINT "GUESS MY NUMBER"
50 INPUT "YOUR GUESS";G
60 IF G<X THEN PRINT "TRY A BIGGER NUMBER" : GOTO 50
70 IF G>X THEN PRINT "TRY A SMALLER NUMBER" : GOTO 50
80 PRINT "THAT'S RIGHT! YOU GUESSED MY NUMBER"
90 END
```

The program is composed of the following lines:

*line 10* — The REM statement allows you to insert comments into your program. All the characters following the REM statement on the same line as shown are ignored by the computer.

*line 20* — The LET statement declares the variable 'X' and assigns to it the constant 37. The colon is a 'separator' symbol which enables more than one statement to be written on a single numbered line.

*lines 30 and 40* — The two PRINT statements issue a message on the terminal.

*line 50* — The INPUT statement outputs a reminder message followed by a question mark prompt. In answer to the prompt you type a single numeric value followed by the RETURN key. This value is stored in the variable 'G' and is used later in the program.

*lines 60 and 70* — These are multi-statement comparison lines. If the comparison succeeds, a message is printed and a conditional branch is made to line 50.

*line 80* — The PRINT statement outputs the message in quotation marks to the terminal. The only way program execution can reach line 80 is if the value you type in for G is the same as the value assigned to X (because line 60 or 70 re-directs program execution back to line 50 if G is less than or greater than X respectively).

*line 90* — The END statement signifies program completion.

Later in this series we will examine automatic features of BASIC called 'functions'. Functions are built into the BASIC language in order to perform frequently needed operations. Two BASIC functions can be combined and used in the above program so that each time the program is run the program itself generates a number between 1 and 100 for the user to guess. The two functions needed are the 'RND' and 'INT' functions.

If line 20 is replaced with the new line:

```
20 LET X=INT(100*RND(1))+1
```

the value assigned to X will be different each time the program is run.

You may wish to try and modify the program so that it prints out how many guesses the user tried in order to get the correct number. Also it would be a good idea if the program repeated automatically until it receives a special 'terminator', instead of typing 'RUN' each time a number is to be guessed. For example, if you type a negative number as your guess the program will stop. The modified program will be given in next month's BASICALLY BASIC.

Mathematical Symbol	BASIC Symbol	Example	Meaning
=	=	X=Y	X is equal to Y
<	<	X<Y	X is less than Y
≤	<=or=<	X<=Y	X is less than or equal to Y
>	>	X>Y	X is greater than Y
≥	>=or=>	X>=Y	X is greater than or equal to Y
≠	<> or ><	X<> Y	X is not equal to Y

Table 1. BASIC Relational Operators and examples of their use.

# THE POWERFET AMPLIFIER



**PFA 80**  
(100W plus into 8Ω)

### Elegant Simplicity

Advances in high technology should make life simpler. A cluttered power amplifier board may well perform superbly, but its busy elaboration is an indication that its design is pushing the limit of its component technology.

There are now many first class bipolar power amps on the market. All of them are complex and consequently expensive. Any additional improvements in the areas where they are weak (e.g. H.F. distortion) can only be obtained with yet further complexity and cost.

Only a new technology can provide the sort of "quantum jump" in component performance necessary to reduce the clutter on the board, reduce the cost and make the highest fit once more affordable.

### Powerfets

So far 29 semiconductor manufacturers have invested in this new technology. Clearly powerfets are something special.

Their enormous power gains eliminate conventional drive circuitry in power amps, permitting delightfully simple designs. Their freedom from secondary breakdown and their tendency to shutdown when thermally overstressed, result in inherently stable and destruction-proof output stages, not needing protection circuitry. And perhaps best of all, their lack of charge storage make them fast and responsive, producing amplifiers of wide bandwidth and low distortion even at high frequencies.



Some day all power amps will be made this way

We sell electronic components too... at unbeatable prices. Send SAE for lists.

### PFA80/120

The PFA is perhaps the perfect realisation of the classic powerfet amp design. The superb PCB allows the use of either one or two pairs of output devices, providing easy expandability for those starting with the smaller system. (The extra output pair of the PFA120 results in lower distortion and improved efficiency, particularly into low impedance loads).


The components used in the PFA have been chosen with extreme care. The lowest noise input devices and lowest distortion gain stage devices were selected regardless of cost. 140V powerfets were chosen against the more usual 120V to give improved safety margins.

Specification	PFA80	PFA120
Bandwidth	10Hz —	100KHz± 1dB
Output Power	80W (Vs± 50V)	120W (Vs± 55V)
R.M.S. into 8Ω		
THD	≤ 0.008%	≤ 0.005%
(20Hz—20KHz)		
(KHz at rated output)	0.004% typ.	0.002% typ.
SNR		120dB
Slew Rate		>20V/μS
Gain		X22
Rin		30K
Vs max		±70V
Cost (built)	£15.95	£22.85
(kit)	£13.95	£20.85
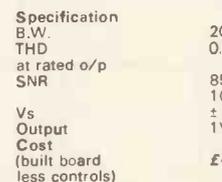
### Pre-amp PAN 20

The design is unique. Equalisation is applied after a flat gain stage, resulting in one of the best noise performances available. Superb overload figures are ensured by a front end incorporating a special gain/attenuator control (volume control to you!). The inputs are uncommitted and can be used with any combination of signal sources in the 1mV to 10V range. RIAA equalisation is provided for mag PUs and space on the board is available for different equalisations.

**PFA 120**  
(150W plus into 8Ω)  
300W INTO 4Ω)



Specification	
B.W.	20Hz-30KHz ± 1dB
THD	0.003% typ.
at rated o/p	
SNR	85dB (ref. 5mV RIAA)
	105dB (ref. 100mV flat)
Vs	± 20V
Output	1V (clips at + 20dB)
Cost (built board less controls)	£4.75 2 needed for stereo

### Power Amp PAN 1397

A high quality 20W power amp board based on the HA1397. Easily modified for bridge operation, providing high powers from low supply voltages.

Specification	
Output power RMS	20W into 8Ω at ± 22V
	20W into 4Ω at ± 19V
THD	0.02% at 1KHz 1W to 12W
SNR	90dB
Input	100mV into 50K
Cost (Built)	£5.80

## THE POWERFET SPECIALISTS

# J. W. RIMMER

Mail order only to:

148 Quarry Street, Liverpool L25 6HQ. Tel: 051 428 2651

Technical enquiries:

367 Green Lanes, London N4 1DY. Tel: 01-800 6667

# USING MICROPROCESSORS

Peter S. Kershaw B.Sc (Eng.)

The aim of this series of articles is to teach by example the basic principles of microprocessor hardware and software to the level at which the reader will be able to understand, modify and even design microprocessor-based projects.

## Part 5 A Design Example

This month we present a hardware design example. A simple car computer has been chosen, as it has most of the standard requirements of dedicated processor applications. ROM, RAM, interrupts and analogue and digital I/O. This is not intended to be a constructional project - there are many better ways of achieving the same result. The Z80 has been used only because the previous articles have been based upon it. At each stage of the design, the options available are discussed in detail.

### Specification

The first stage in any design is the specification of the required performance characteristics. These should include the facilities offered, input and output tolerances, power supplies available, etc. All facilities which may be required should be included - it is much easier to remove some than to add them later. Similarly with tolerances, it is better to err on the side of accuracy. The following is a provisional specification for the car computer:

#### Facilities and tolerances:

Instantaneous speed	(0-99 mph $\pm 2$ )
Instantaneous mpg	(0-99 mpg $\pm 5\%$ )
Average speed	(0-99 mph $\pm 2$ )
Average mpg	(0-99 mpg $\pm 5\%$ )
Total distance	(0-99 miles $\pm 1$ )
Total fuel used	(0-9.9 gallons $\pm 0.2$ )

#### Inputs:

- Magnetic induction transducer (magnet mounted on front wheel)
- Fuel flow rate transducer (proportional d.c. voltage output)
- Pushbuttons: mode set (6), system reset

#### Output:

- Seven-segment LED displays

#### Power:

- 12v DC @ 500 mA

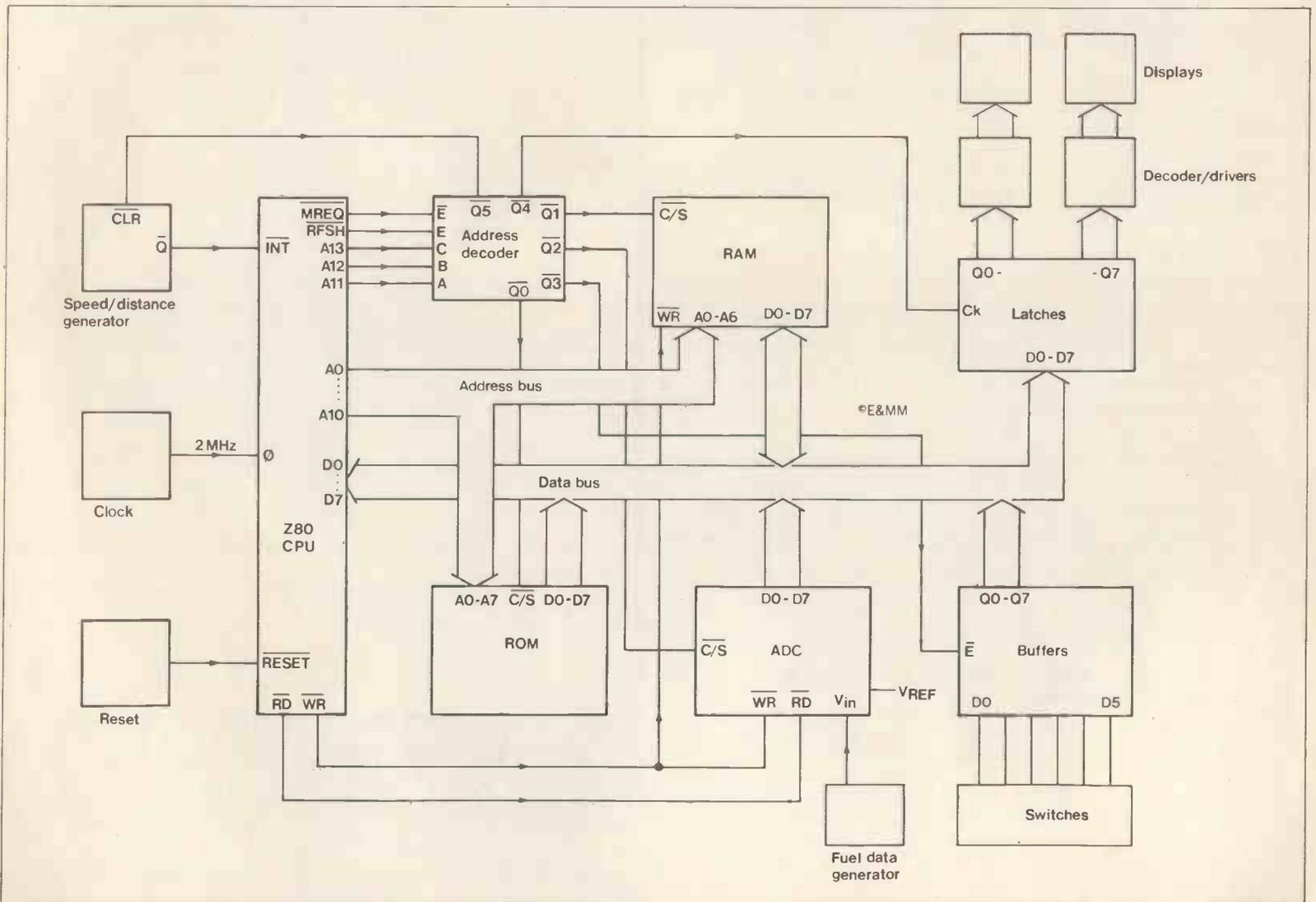


Figure 1. Car computer: block diagram.

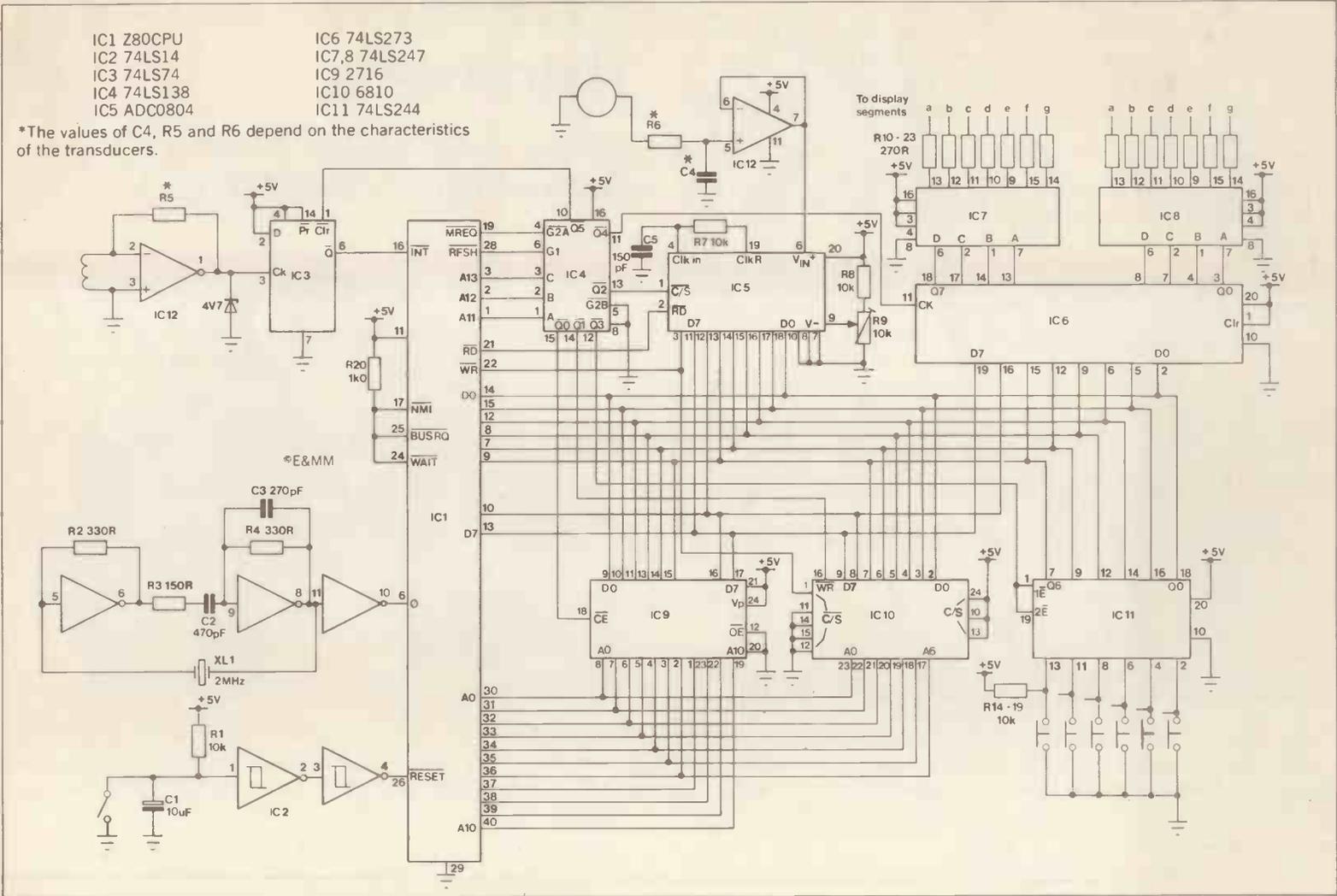


Figure 2. Car computer: complete circuit diagram.

In addition, for a real application size, weight and cost would be specified. Note that during a substantial design project these specifications may change several times as new requirements and new problems arise.

## Hardware Design

It is usual to design the hardware of a microprocessor-based project first. However, the software requirements should be borne in mind even at this stage. (In fact, it is often software requirements which determine the choice of processor).

### System Timing

One of the first things to notice is that some form of real-time reference is required to measure speed. We could use a Counter-Timer Circuit (Z80-CTC) which contains counters which may be clocked externally or from the system clock. We would then count, say, the number of wheel revolutions in one second. However, this reduces the accuracy at low speeds. For example, at 10 mph there are only 2.51 revs/second (assuming a wheel diameter of 56 cm). Alternatively, we could count the number of clock cycles between wheel revolutions. The time for one revolution varies from 39.8 ms at 99 mph to infinity at 0 mph. When stationary, in fact, the count will never be terminated, and this must be taken into account in the software.

Instead of using a CTC, we could set up a software counting loop, using the system clock as our reference. Provided the time spent computing is very small compared with the time spent counting, or the computing time is somehow compensated for, this method can be quite accurate enough. Even at maximum speed, the time per revolution (39.8 ms) is very long compared with the time required for computation (probably less than 1 ms). This timing method saves the cost of the CTC and its associated wiring.

A block diagram of the car computer is shown in Figure 1. The output from the induction coil is amplified by an op amp. This signal is then used to set a D-type flip-flop. This causes a maskable interrupt to the CPU. When the interrupt has been serviced, an address is read (or written to) which causes Q<sub>0</sub> to go low. This then clears the flip-flop, removing the interrupt.

### Memory

The amount of ROM required can only be estimated at this stage, but the smallest standard EPROM available is the 2708 (1k x 8). However, this requires +12v and -5v supplies. Thus, the 2716 (2k x 8) which runs from a single +5v supply is used. In assessing the amount of RAM required, we must remember that a stack will be required for interrupt servicing and subroutines. But the

software will be quite simple and the intermediate data storage requirement is small, so a 6810 (128 x 8) should be adequate.

### Input and Output

There are as many ways of implementing I/O as there are applications. In this instance we may choose between octal latches and buffers and LSI I/O chips. Devices like the Z80-P10 (Peripheral Input/Output) or the Intel 8255 PPI (Programmable Peripheral Interface) offer flexibility and facilities such as interrupt generation, bidirectional ports and 'handshaking'. These devices may be more expensive than TTL chips but they offer a considerable saving in space and wiring. In this application, however, we only need six input lines. These can be provided with an octal buffer (74LS244).

It is worth mentioning here that whereas most microprocessors have special support chips for I/O, displays, etc many of these devices are usable with almost any processor. Thus, even though the range of Z80 support chips is quite small there are many devices which can be used from families such as 8080 and 6800. The designer should always try to keep abreast of new developments in microprocessor support.

### Address Decoding and Control

Address lines A<sub>11</sub>, A<sub>12</sub> and A<sub>13</sub> are decoded to select particular devices. As with most microprocessor components, inputs and outputs are active low. Thus, when A<sub>12</sub> & A<sub>13</sub> are low, Q<sub>0</sub> goes low (active) and the ROM is selected. Two other signals are applied to the address decoder: MREQ and RFSH. MREQ goes low when a valid memory address is on the address bus. With the Z80, there are two circumstances where this occurs. One is where a memory location is being read or written to. The other is where a dynamic memory refresh address is being supplied. This is done automatically each time an opcode is being decoded. When a valid refresh address is present, both MREQ and RFSH go low. As we are not using dynamic RAMs, we can gate out these addresses by applying RFSH to the decoder, as shown in Figure 1.

Note that the I/O is addressed as if it were memory (i.e. it is memory-mapped). This has been done simply because the address decoding is there so no further circuitry is needed to derive the appropriate chip select signals. The Z80 does, however, generate IORQ which is similar to MREQ, but can only address 256 I/O port addresses. It can be seen that, whilst A<sub>10</sub>-A<sub>13</sub> are applied to the ROM, the RAM sees only A<sub>0</sub>-A<sub>10</sub>. This means that any address given to the RAM is independent of A<sub>11</sub>-A<sub>13</sub>. Thus, the block of RAM may be addressed starting at 0800, 0900, 0A00.... Similarly, since A<sub>11</sub> & A<sub>13</sub> are ignored entirely, the whole of memory space is repeated 4 times. A memory map (showing only the first occurrence of each device) is given in Figure 3.

For the analog-to-digital (A/D) conversion, a device has been chosen which interfaces directly to the processor bus. A fairly common and cheap alternative is to use a D/A converter and a comparator. This and other conversion techniques will be discussed in more depth in a later article.

The 7-segment displays are driven by decoder/drivers from a single 8-bit port. It would have been possible to drive each segment directly using two seven-bit ports and performing the encoding of the segments in software. However, standard 74LS273 latches cannot provide the necessary current to light the LEDs and high current devices are more expensive and impose a greater load on the data bus. The switch outputs are applied to a tri-state buffer. These will be read regularly to check for a switch closure.

**Bus Loading**

The Z80 data and address bus outputs can each drive several LSTTL inputs. The loading imposed by the devices on the bus can be found from manufacturers' data sheets. If the buses are too heavily loaded, or if they are taken off the main circuit board, they should be buffered using unidirectional or bidirectional tristate octal buffers, as required.

**Clock**

A clock frequency of 2 MHz has been chosen as it is suitable for the standard 2.5 MHz Z80 and does not place severe demands on any of the other devices. In general, the timing of memory devices and peripherals should be checked to see that they will operate correctly under the design conditions. For memory devices, the access time is particularly important. This is the time taken for valid data to be available on the output pins after the chip select becomes active, assuming a stable address.

Timing charts in the Mostek Z80 technical manual show that 1½ clock cycles are available for an opcode fetch (OCF) cycle (i.e. when reading an opcode from the ROM), and 2 clock cycles are available for a normal data read or write. These times are reduced slightly by internal delays, but clearly the standard memories with access times of 450 ns or less will be adequate with a 2 MHz clock. Ways of using fast CPUs with slow memories will be discussed at another time. An I/O cycle is half a clock cycle longer than a memory read/write. This enables MOS I/O devices (such as the Z80-P10) to operate at full speed. Thus, when working near full speed, these devices should be configured as I/O ports rather than memory-mapped.

**System Reset**

Finally, the combination of C<sub>1</sub> and R<sub>1</sub> causes the RESET pin of the CPU to be held low until the 5v supply has settled. This is called 'power on reset'. The manual reset button can be pressed at any time, causing a restart to location 0000H. If dynamic RAMs are used, the reset has to be synchronised to the clock, for which additional circuitry is required.

A complete, detailed circuit diagram is shown in Figure 2.

**Better Hardware Solutions**

For small applications such as this, single-chip microcomputers are often used. These contain a microprocessor and combinations of ROM, RAM, I/O ports and timers. The ROM is normally mask programmed by the manufacturers. This is only economically feasible for very large quantities.

If the car computer is to be left on when the car is stationary, a low power CMOS processor and liquid crystal displays would drain far less current from the car battery. For example, the Motorola MC146805E2 is a CMOS processor with:

- \* 112 bytes of on-chip RAM
- \* 16 bidirectional I/O lines
- \* Programmable timer
- \* Automatic power-on-reset
- \* On-chip oscillator

It consumes 20 mW at the full clock speed of 5 MHz (compared with 750 mW for the Z80 at 2 MHz), and less than 1 mW in its special standby mode. This device would therefore be far more suitable for an application such as this.

Some multifunctional devices are also very useful for reducing the chip count. For example, the new Mostek MK3886 'Combo Chip' contains a serial I/O port, two timers, three interrupt channels and 256 bytes of RAM. Thus, the complete processing requirement for many applications could be met simply by a Z80 CPU, a Combo Chip and a ROM.

Next month we will look at the design of hardware and software for a digital music keyboard. **E&MM**

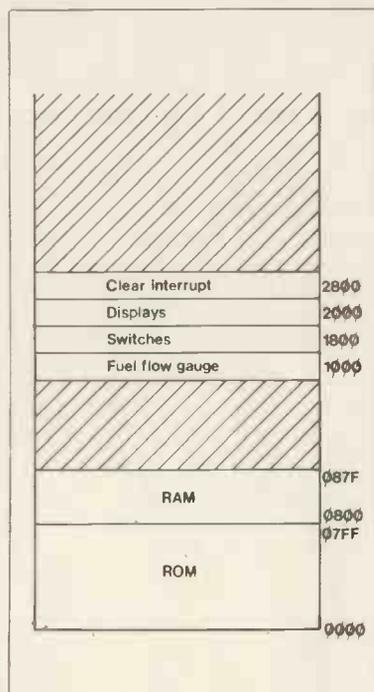


Figure 3. Memory map (not to scale).

# Two New Additions

## to the successful Studio Series from McKENZIE



Both capable of a massive power handling of 200 watts are a useful addition to any discerning DJ or Musicians Sound System.

The Studio 15-200 Bass is a 15-inch driver which can be selected with confidence for any high performance Bass application.

The Studio 12-200GP is a high power general purpose 12-inch unit developed from the already successful 125 Series which received reviews worthy of note earlier this year.

Both units are built on a new pressure die-cast aluminium chassis and have the same massive magnet system fitted with a finned aluminium heat-sink.

The power is handled by our new 75mm high temperature voice coil which is cooled by venting immediately over the winding and through the rear of the magnet assembly.

All the Studio Series have the same durable high quality stoved gold epoxy finish and have a recommended retail price of £74.00 for the Studio 15-200 Bass and £69.00 for the Studio 12-200GP.

# McKENZIE

## Acoustics Limited

ROCKLEY AVENUE  
BIRDWELL, BARNSELY, YORKSHIRE S70 5QY  
Telephone (0226) 43894

Please send me your free literature

Name.....

Address .....

E&MM/7

# Hot Wiring your GUITAR



Adrian Legg

## Series/parallel and pick-up phase reverse

Series/parallel is an alternative feature to coil tap that is included in quite a few production guitars using humbuckers, and a useful item it is too. The difference between the two is simple. Both will give the normal series coil humbucker sound in one position, but where the coil tap cuts out one of the coils, probably by one of the methods I've shown so far, the parallel setting alters the coil wiring so that effectively, instead of a humbucker, you have two single coils operating in parallel. Each coil has its own output and earth, though the pair still use the same magnetic field, and remain out of phase, so are still humcancelling. This gives a thinner, more topky sound than series, but is still not absolutely the sound of a single coil pick-up or a tapped humbucker.

The most common set-up requires a three or four conductor and shield humbucker, and an on/on DPDT switch. Where the overall phase of the pick-up is not going to be reversed after the series/parallel switch, a three conductor and shield type will do. But where phase reverse is required, then the in-phase earth end of the coils has to run via the series/parallel DPDT to an on/on DPDT cross-wired so that in reverse phase, this earth-end of the coils will become the output end. Figure 1 shows a four conductor pick-up linked to a series/parallel DPDT, and on from there to a phase reverse DPDT. This set-up can easily be extended to include a coil

tap, either partial or complete, by running a wire from terminal 6 of the series/parallel DPDT to any of the earth type taps I've shown so far.

Obviously, the most sensible one to go for in a control situation beginning to get complicated would be the tone control spare leg tap. Where phase reverse is not required, the wiring would be as in Figure 2. I use here for convenience the colour codes as used on Dimarzio and Velvet Hammer four-conductor pick-ups. The extra tap here would operate when the DPDT was set to series. Parallel would be unaffected. This gives you an interesting A-B com-


parison facility on the DPDT between parallel and tap, and the opportunity to draw your own conclusions about the relative values of the two.

The interesting point about phase reverse in conjunction with an earth-type tap, either via the series/parallel DPDT, or direct tapped from the coils link, is that phase selection determines which coil is tapped. Figure 3 shows phase reverse in conjunction with a tone control earth-type tap. In normal phase, coil 2 will be turned off, and in reverse phase, coil 1 will be turned off. In my experience, this extra range of tone is of most use on the bridge pick-up. There are taps

where this does not apply but they're for another time. Note that in Figure 3, both the black and the white wire run to the tone control, the series link is achieved from 0-9, when there is sufficient resistance to prevent the link between the coils shorting to earth. As before, from 9-10 the tap operates.

Beware when dealing with multi-conductor and shield production "custom" pick-ups. Schecter and Lawrence humbuckers for example, are normally wired for phase reverse and tap as in Figure 4, so series/parallel switching is not possible without rewiring the conductors. Others, like the earlier Dimarzio Dual Sound, were wired as in Figure 5 for series/parallel and/or tap, but not for overall phase reverse. In the latter case though, one could always tap out coil 2, and reverse phase on coil 1 only to get an out-of-phase mix with another pick-up. More about coil phase reverse later on. The reason that you cannot reverse overall pick-up phase on the latter type of three conductor and shield is simply that in reverse phase, the shield would become the output, and if that didn't simply earth out somewhere along the line, it would be horribly noisy. These Dual Sounds are wired four conductor nowadays, and the simplest way to get all the options is to rewire a humbucker with less than four conductors up to four, using a single separate shield to earth the pick-up base and hardware.

E&MM

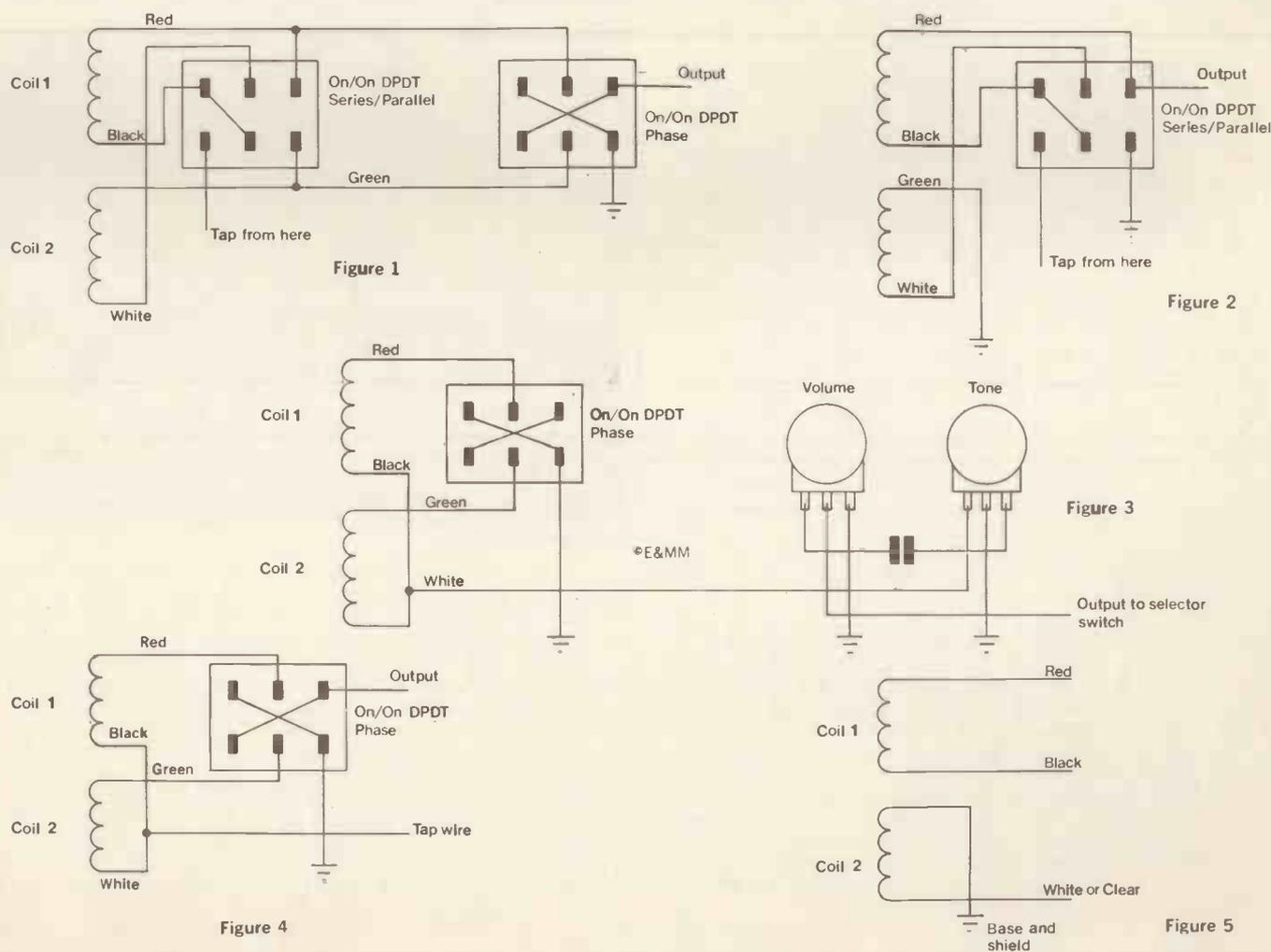

# GOING SOLO

An insight into the background and musical equipment that brought about Duncan Mackay's Electronic Music LP 'Visa'

RECORDED ON CASSETTE NO. 3



There is no lack of musical experience in the life of Duncan Mackay, for he learnt the violin from the age of three and through the encouragement of his late father, who was a Professor of Music, continued playing until he was fifteen. His father then started lecturing at the University in Port Elizabeth, South Africa and here Duncan took the LTCL and LRSM examinations on the violin.

His keyboard experience began with the church organ whilst at university and it also gave him the opportunity to play jazz three times a week (Jimmy Smith style) on an old Hammond M100 organ. He started teaching music for six months but this was something he couldn't cope with at all, so by chance he got a job as keyboard player with a jazz group from Brazil. Having worked for some time in Rio in his early twenties he then came back to work in Rhodesia and finally returned to England seven years ago, planning to join up with Ginger Baker. This association didn't work at all and he started working with John Hiseman with what was to become Collisium II.

Duncan's music making in these days brought little income until Steve Harley came along from Cockney Rebel and offered him £50 a week. He remained with Cockney Rebel until four years ago and when Rebel split up he stayed with Steve for another year as musical director. Then came the move to 10cc during which three albums were made, including 'Bloody Tourists' and 'Look Now'. During that time he still worked with Steve Harley and nearly a year ago they completed

an LP entitled 'Score'. This was quite different from his 'Visa' record, with its 'thousand-notes-a-minute', very orchestral, dramatic music and unusual time signatures.

'Score' came from Duncan wanting to do something outside of Cockney Rebel, with the title coming from the music holding all the elements of a good film sound track. It was recorded at Scorpio Studios and certainly couldn't have been recorded in his present studio, for it used numerous live percussion and keyboards. Coming just before the advent of polyphonic keyboards, the music required an enormous amount of time spent multi-tracking monophonic synthesiser tracks layer by layer and turned out to be an expensive album to produce. The album was not as big a success as it should have been, for it contained plenty of interesting ideas. Shortly after 'Score', Duncan left EMI to join a new record company, Edge Records.

## How Visa Started

Duncan took all the music he had recorded on two-track Revox to Edge management who recognised it had good potential for an album. When discussing the cost of going into an eight-track studio to make the recording, Duncan suggested that the company loaned him a mixing desk and an eight-track recorder as down payment on the album. "This enabled me to record the entire album in the studio at home using my own equipment in addition. But having spent years in recording studios where there was usually an engineer to help



Duncan Mackay.



The main mixing desk.

out, it was quite a daunting experience to begin the LP entirely on my own knowing that it had to be completed in six weeks!"

Although the mixing desk (an Allen & Heath Modular 3, 16 into 8) had limited EQ facilities, it was sufficient since most synthesisers had their sounds shaped before being direct injected into the desk. Because it had only three 'sends', extra junction boxes were made to switch these outputs to various effects boxes, without having to change jacks around.


Duncan dislikes untidy wiring in studios, and, needless to say, spent a lot of time moving the equipment around until he was satisfied. Part of the solution has been to use several

patch boxes around the room to minimise the amount of extra wiring needed. To hold the keyboards, he uses a Roland rack which although quite expensive at around £100 is ideal for angling each piece of equipment exactly as required.

He prefers to use reverberation and other effects on individual tracks, rather than at the final mix-down stage and feels that this adds greater depth and spatial effect to the stereo field. He added, 'You have to be careful not to add too much reverberation, otherwise the sound can become swamped - but it does allow you to listen carefully to your monitor mix and get a good impression of what you are building up'. We reminisced



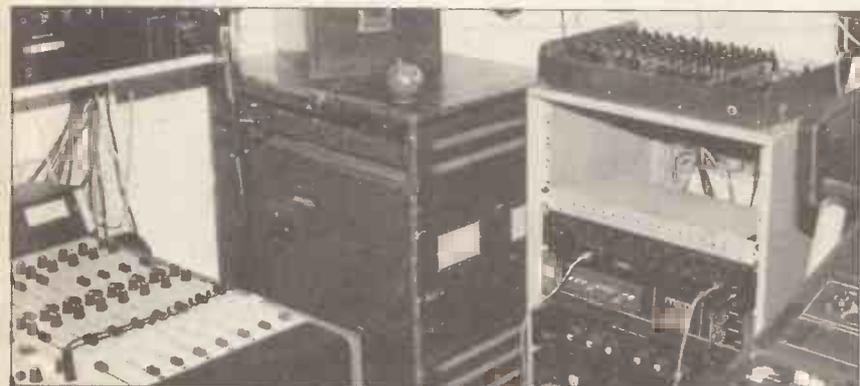The main keyboard rack with echo and drum units above.



The Hammond Leslie unit (centre).

on the difficulties of making an 8-track demo and then going into a 24-track studio to try and recreate the original version. It was obviously easier and cheaper to put the whole album together in his own purpose-built studio. "With more time available, making electronic music often brings situations when you might be changing the controls slightly and getting an effect you couldn't possibly have thought up". He remembers setting up a drum pattern on the Compu-Rhythm which by chance had some echo added and sounded so good that it was kept for the final track.



Stereo recorders and various effects units.

## Recording Equipment and Effects

The multi-track tape machine used was a Brenell Mini-8 with Vari-speed and remote control. The amps in the studio are Quad 405's fed into a pair of JBL speakers (Decade 36 3-way speakers set for flat response), although he has tucked away a pair of Auratones which he likes as additional reference speakers (even though the bass needs boosting!).

The mixing desk sits in front of what used to be an old fire-place, conveniently positioning it sufficiently away from the monitor speakers. The sound of the room is already fairly dry from the carpeting and curtains, so no special equalising was needed even at the mastering stage. Noise reduction is not used - instead the Brenell recorder receives fairly high signals that can peak into the 'red' frequently without producing distortion, thus eliminating one additional step in the chain that could affect the final sound. "The only time I like using dbx is when I am recording piano and I like to play it back without it to get a really bright penetrating 'honky-tonk' effect".

Although Duncan's Hammond is capable of giving him a great organ sound through its tone cabinet on the album, he used a Roland VK1 through a 'Sound Dimension' unit that really spreads out the sound. There are two Revox tape recorders (both A77's) and one is used for the mix-down and the other for tape echo and back-up copies. There is also a Technics M04 cassette tape machine that is useful for recording any make of tape with correct bias and equalisation and its 'search facility' helps to locate tracks quickly. For more complex echo effects there is a Yamaha E1010, Roland Space Echo RE150 and also the DC30. Each of these produces a different kind of echo along with an early solid-state Roland unit, the Digital Chorus. Other effects come from the Roland 'Sound Dimension D', a Phase Shifter - the SPH323, and a Bell Flanger - the BF20 stereo version. The Eventide Clockworks Harmoniser has pride of place next to an old Yamaha tuning scope which is very useful for tuning the Clavinet.

Echo and other effects are controlled occasionally from foot pedals and the former especially is operated from a 'push-to-make' rather than an 'on/off' switch to give more accurate echo timing. We mustn't forget Dave Simmons' Clap-Trap too which adds extra percussive sounds.

In the photographs you might also spot an instrument that excited both of us - the Roland Auto Harp, which is simply the traditional auto harp with piezo pick-ups under each string. We both agreed the sound it produces was unobtainable even from guitars and added interesting chordal and

arpeggio effects.

Duncan points out, 'It is important to listen to recordings in various environments - even the car stereo is useful for evaluating if there is too much bass and so on'. Next to his Leslie unit there is a rack of equipment from his old 10cc days and space for some Kepex noise gates which help to keep the background noise of the Clavinet down in recording.

## Onto Keyboards

Looking at the impressive array of keyboards, we started with the Hammond B3 and its accompanying Leslie unit which has a 200W Gauss bass speaker and JBL horns, 'Rarely used these days', comments Duncan 'and certainly never played as loud as it could be'. The Hammond was bought in Cape Town for £400 brand new from an old lady who had been left it in a relative's will and was first discovered ornating her living room with a table cloth over it and pictures on top!

Under the main rack is the Yamaha CS80 which provides most of the harmony and polyphonic textures on 'Visa'. This has been modified to take two extra memories and the string sounds have also been improved. A firm favourite is the Hohner Clavinet, which is sent through the Digital Chorus, helping to add a great deal of clarity to the sound. "I use the Multi-Moog quite a lot for sequencing - its touch-sensitive action helps to accent notes - and operates with the Roland system 100 sequencer. The latter's Channel A is used for note control and Channel B for filter control and rests are inserted by simply closing the filter."


On the top part of the rack is a Roland TR78 Compu-Rhythm which has its bass drum sound beefed up by a Moog Equaliser. 'I find the pad for entering rhythms impracticable, so I use the writing switch which is much more accurate, although you have to keep removing jacks for normal operation'. The drum sounds go through the Space Echo which gives further syncopation to the rhythms and these are very evident on the 'Visa' album! Throughout the LP the percussion is always intended to sound electronic - listen to the nice phased cymbal on the second track. Duncan only occasionally uses his Moog Taurus pedal for penetrating synthesiser bass: "This really comes from my time with 10cc and playing jazz in Africa when I gigged with just a drummer". His church organ experience obviously gives him an interest in playing pedals and he plans to reinstate a two-octave pedalboard with his Hammond shortly. The Yamaha CS15D shown on the top of the Hammond will have been donated since as a prize in a competition promoting 'Visa'.

## Writing the Music

During composing, the music was often written down in traditional notation, without detailing all the synthesiser and mixer settings. No physical tape editing is done as Duncan prefers to collect on a Revox numerous sounds that he experiments with, from which he will extract parts afterwards that he likes



The original Hammond B3!

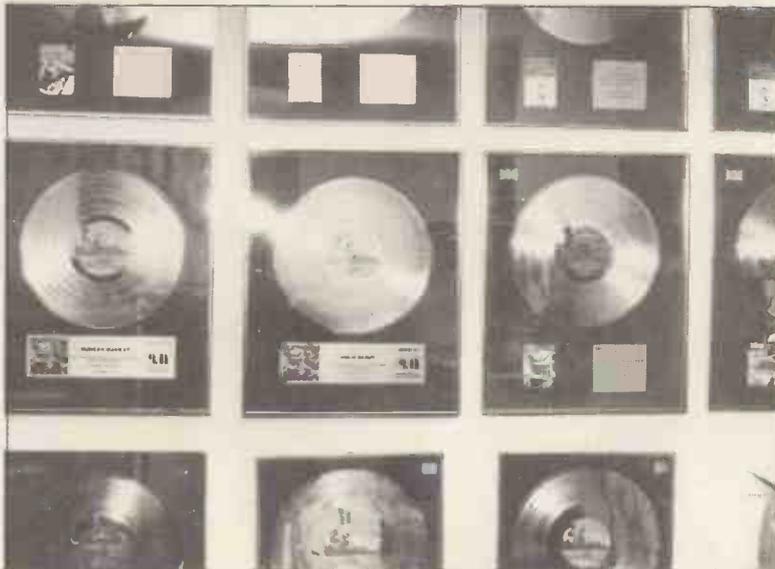

Just a few of Duncan's gold, silver and platinum disc awards.



The Brenell 8-track recorder



How to keep your cables tidy!

- in fact, that is how all of the 'Visa' pieces were written. Talking about the reasons for writing 'Visa', Duncan mentioned his initial dislike for drum machines had recently changed and prompted him to do a lot of experimenting with them. "I'm still continuing to write music in the vein of 'Score', but it's just not commercially viable at the moment. It was challenging to produce 'Visa', for everything was created in my studio from beginning to end. The excitement of composing electronic music for me came from the manipulation and interfacing of controls as well as the composing of the music and the record was intended to be pleasing and enjoyable to listen to, rather than contain exciting innovative ideas."

Its directness and catchy melodies should appeal to the whole family and points to the important developments that are taking place in providing cheaper synthesisers for everyone to play easily and have fun with.

What this album will prove to many people is that acceptable music can now be written in a good home studio set-up and should inspire the many hundreds of people who now enjoy recording their own music to continue their experiments. Surprisingly, the whole of the 'Visa' LP was recorded by simply filling the eight tracks of the recorder and mixing these down into stereo. When 'Visa' is performed at a concert, Duncan uses one other keyboard player and backing tapes.

Certainly 'Visa' is a big step for Duncan and it contains the personality of the composer through its warmth and directness, its neat and precisely organised rhythmic and melodic counterpoints. Like many electronic music composers, his next album promises to be different again. His latest release is a single which is not on the album, titled 'Sirius 3 Mark II'. It's more in the dance vein and shows yet another side of his composing. Meanwhile, he continues to compose film sound tracks, jingles, play most of the music for Kate Bush and looks forward to plenty of solo dates this year.

Mike Beecher

E&MM

You can listen to Duncan playing his studio keyboards on our E&MM Demo Cassette No. 3.



We are also offering his 'Visa' LP to E&MM readers for only £3.49 inc. post, packing and VAT. Send your cheque to 'Maplin Publications', 282, London Road, Westcliff-on-Sea, Essex, SSO 7JG.

TTLs by Texas	74367	100p	4024	50p	93 SERIES	74S SERIES	74S114	120p			
7400	11p	4025	20p	9301	160p	74500	60p	74S124	300p		
74500	60p	74390	200p	9302	175p	74504	60p	74S132	160p		
7401	12p	74393	200p	9308	316p	74505	75p	74S133	225p		
7402	12p	74490	225p	9310	275p	74508	75p	74S138	225p		
7403	14p			9311	275p	74510	60p	74S139	225p		
7404	14p			9312	160p	74520	60p	74S157	250p		
7405	18p			9314	165p	74530	60p	74S163	300p		
7406	30p	J4LS SERIES	4034	200p	9316	225p	74532	90p	74S174	250p	
7407	30p	74LS00	14p	110p	9321	225p	74537	90p	74S175	320p	
7408	17p	74LS02	14p	4036	9322	150p	74564	60p	75S194	350p	
7409	19p	74LS03	18p	4039	9334	380p	74574	80p	74S241	450p	
7410	19p	74LS04	18p	4040	9368	250p	74585	300p	74S250	70p	
7411	24p	74LS05	22p	4041	80p	9370	300p	74586	180p	74S373	500p
7412	20p	74LS08	22p	4042	80p	9374	200p	745112	120p	74S374	500p
7413	30p	74LS09	21p	4043	90p						
7414	40p	74LS10	20p	4044	90p						
7414	40p	74LS11	40p	4046	110p						
7416	90p	74LS14	40p	4047	100p						
7417	27p	74LS14	50p	4048	55p						
7420	17p	74LS20	20p	4049	45p						
7421	40p	74LS21	40p	4050	45p						
7422	22p	74LS27	38p	4051	80p						
7423	34p	74LS30	20p	4052	80p						
7425	30p	74LS32	20p	4053	80p						
7426	40p	74LS37	30p	4054	150p						
7427	34p	74LS38	38p	4055	125p						
7428	38p	74LS42	70p	4056	135p						
7430	17p	74LS47	60p	4059	600p						
7432	40p	74LS51	24p	4060	15p						
7433	40p	74LS55	30p	4063	120p						
7437	35p	74LS73	50p	4066	50p						
7438	35p	74LS74	27p	4067	450p						
7440	10p	74LS75	36p	4068	27p						
7441	10p	74LS76	45p	4069	30p						
7442A	60p	74LS76	45p	4070	30p						
7443	112p	74LS85	80p	4071	25p						
7444	112p	74LS86	40p	4072	25p						
7445	100p	74LS90	40p	4073	25p						
7446A	93p	74LS92	70p	4075	25p						
7447A	93p	74LS93	50p	4076	17p						
7448	80p	74LS97	40p	4081	27p						
7450	17p	74LS107	45p	4082	27p						
7451	17p	74LS109	80p	4086	72p						
7454	17p	74LS112	40p	4089	150p						
7454	17p	74LS113	90p	4093	70p						
7460	17p	74LS114	45p	4094	80p						
7470	36p	74LS122	80p	4095	95p						
7472	30p	74LS123	60p	4096	95p						
7473	34p	74LS124	180p	4097	340p						
7474	30p	74LS125	50p	4098	120p						
7475	38p	74LS126	50p	4099	200p						
7476	38p	74LS127	50p	4100	200p						
7480	50p	74LS133	60p	4101	132p						
7481	100p	74LS136	55p	4102	180p						
7482	84p	74LS138	55p	4103	180p						
7483A	70p	74LS139	75p	4104	89p						
7484	100p	74LS145	120p	4105	120p						
7485	110p	74LS147	120p	4106	75p						
7485	110p	74LS148	175p	4107	60p						
7486	34p	74LS151	80p	4108	470p						
7489	210p	74LS153	60p	4109	100p						
7490A	30p	74LS154	200p	4110	300p						
7491	100p	74LS155	80p	4114	250p						
7492A	46p	74LS156	80p	4202	120p						
7493A	30p	74LS157	60p	4503	70p						
7494	84p	74LS158	60p	4507	55p						
7495A	30p	74LS160	90p	4508	290p						
7496	65p	74LS161	75p	4510	90p						
7497	180p	74LS162	100p	4511	80p						
74100	100p	74LS163	100p	4512	80p						
74107	34p	74LS164	90p	4514	250p						
74109	55p	74LS165	140p	4515	300p						
74116	200p	74LS166	180p	4516	110p						
74117	130p	74LS173	110p	4518	180p						
74119	210p	74LS174	100p	4520	100p						
74120	110p	74LS175	100p	4521	250p						
74121	34p	74LS181	320p	4526	108p						
74122	48p	74LS190	80p	4527	150p						
74123	80p	74LS192	80p	4528	100p						
74124	75p	74LS193	80p	4532	140p						
74126	60p	74LS194	80p	4534	20p						
74128	75p	74LS195	140p	4536	375p						
74132	60p	74LS196	120p	4538	120p						
74136	60p	74LS197	90p	4543	180p						
74137	50p	74LS221	120p	4555	320p						
74138	50p	74LS220	140p	4556	72p						
74142	200p	74LS240	200p	4560	120p						
74145	90p	74LS242	120p	4569	250p						
74147	120p	74LS243	120p	4572	40p						
74148	100p	74LS244	120p	4583	110p						
74150	130p	74LS245	150p	4584	75p						
74151A	70p	74LS247	100p	4585	150p						
74153	70p	74LS251	140p	4724	250p						
74154	90p	74LS253	90p	40097	90p						
74155	90p	74LS257	90p	14411	700p						
74156	90p	74LS258	160p	14412	1100p						
74157	50p	74LS259	160p	14433	1100p						
74159	120p	74LS265	100p	14500	700p						
74160	70p	74LS273	170p	14599	290p						
74161	70p	74LS279	90p								
74162	70p	74LS283	90p								
74163	70p	74LS298	160p								
74164	90p	74LS323	250p								
74165	90p	74LS324	200p								
74166	90p	74LS348	200p								
74167	200p	74LS365	48p								
74170	240p	74LS367	70p								
74172	450p	74LS368	100p								
74173	120p	74LS373	120p								
74174	90p	74LS374	120p								
74175	85p	74LS375	120p								
74176	90p	74LS377	160p								
74177	90p	74LS378	140p								
74178	160p	74LS390	120p								
74180	93p	74LS393	120p								
74181	80p	74LS399	200p								
74182	90p	74LS445	140p								
74184A	150p	74LS670	200p								
74185	150p										
74186	500p										
74188	325p										
74190	120p	4000 SERIES									
74191	120p	4000	15p								
74192	100p	4001	22p								
74193	100p	4002	20p								
74194	120p	4006	95p								
74195	95p	4007	20p								
74196	95p	4008	80p								
74197	80p	4009	40p								
74198	150p	4010	50p								
74199	150p	4011	20p								
74221	160p	4012	25p								
74251	140p	4013	40p								
74259	250p	4014	84p								
74278	290p	4015	84p								
74279	110p	4016	45p								
74283	140p	4017	60p								
74284	380p	4018	89p								
74285	380p	4019	45p								
74290	150p	4020	90p								
74293	150p	4021	110p								
74298	200p	4022	100p								
74365	100p	4023	20p								

LINEAR ICs	MB3712	150p	
AY1-0212	600p	MC1310P	150p
AY1-1313	668p	MC1458	48p
AY1-1320	320p	MC1495L	350p
AY1-5050	140p	MC1496	140p
AY3-1270	840p	MC3340P	120p
AY3-8910	700p	MK50398	75p
AY3-8912	650p	ML920	775p
AY5-1224A	240p	MM55160	620p
AY5-4007D	520p	NE531	150p
CA3019	80p	NE555	20p
CA3046	70p	NE556	70p</

# INSTRUMENT REVIEW

Each month we review the latest Electro-Music Equipment — from synthesisers to sound reproduction and effects!

E&MM's special in-depth reviews look at what's new in the world of commercial music — a vital updating for both electronics designers and musicians.

## PPG Wave 2

8-Voice Polyphonic Digital Synthesiser with 8-Track Digital Sequencer



PPG have been designing and building synthesisers in Germany for several years but, to date, have not made them available elsewhere. Their range of instruments covers monophonic models through to the complex 360 Wave Computer and the company in particular specialises in digital synthesiser technology.

The Wave 2 combines new digital microprocessor circuits with accepted analogue control synthesis and thus aims to overcome the complexity often inherent in computer based systems through its analogue settings and realtime keyboard. The result is an instrument that sounds quite unlike other performance synthesisers, producing complex digital waveforms that can be filtered to produce a vast range of sounds.

### System Design

Rather than produce an instrument following the conventional sine, triangle, sawtooth and squarewave basic sound sources, PPG designed the Wave 2 with banks of waveforms that are digitally produced. They are contained in 30 'Wavetables' which are accessible through a numerical keypad linked to an LCD 80-character display.

This innovative idea solves the problem of many programmable synthesisers — their inability to show the control settings of memorised sounds. Hence, information on all controls can be displayed and through the keypad can be used to update and change the preset sounds.

There are 5 separate displays available for indicating the main panel functions, digital routing and control, oscillator tuning, analogue control settings (on a scale from 0 to maximum 63) for both channels A & B, and Sequencer/Arpeggio functions.

Each of the Wavetables contains



64 different waveforms. These are programmed at the factory and stored in part of the 24K EPROM memory making a total of 1920 in all available. The rest of the EPROM space holds the control information for sending data to and from the main 6809 microprocessor. Some Wavetables have a reasonably smooth transition through their 64 waveforms whilst others have very dramatic changes that contain strongly accentuated and very different harmonic structures — it is with these latter Wavetables that the Wave 2 makes some unique sounds.

Eight oscillators all receive the waveform control information that sets the basic waveform structure, filter and VCA action, which therefore shapes the required harmonic structure. The keyboard then takes any eight notes played and sets each oscillator's basic pitch. As soon as you change waveforms all eight voice synthesisers are reshaped identically to sound the same. Selection of the waveforms is made from the Analogue section on the left half of the front panel either manually, using the 'Partial Wave Numbers' (PWN) control or automatically, with an ADSR envelope.

All the digital information is entered with the numerical keypad and 'display select' buttons on the right half of the panel.

There are two other important design concepts on the Wave 2. First, the relatively low number of analogue controls is achieved through a triple-sharing system that lets you select the panel mode to allocate a specific routing for each set of functions. Second, the notes played on the keyboard can be stored in the 12K RAM memory of an 8-track digital recorder in numerous ways for simultaneous or individual playback.


### Live Performance

On powering the instrument, you immediately have access to a total of 100 programmable stereo sounds.


Thirty of these (and possibly more in production models) are supplied factory preset although the user can reprogram all of them if he wishes.



Wave 2 opened up.

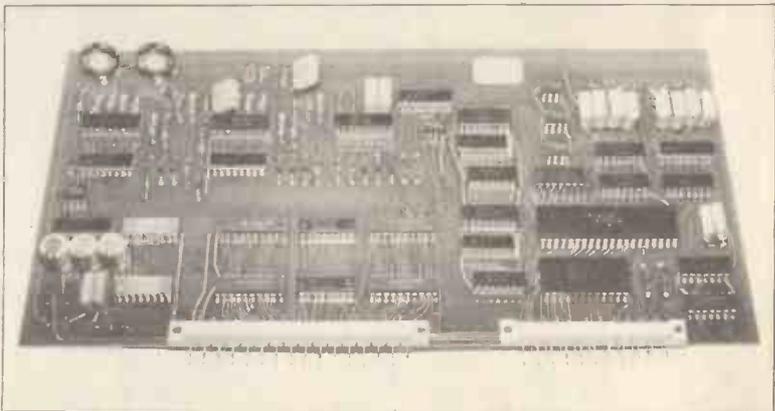

Dual oscillator, filter, VCA board.

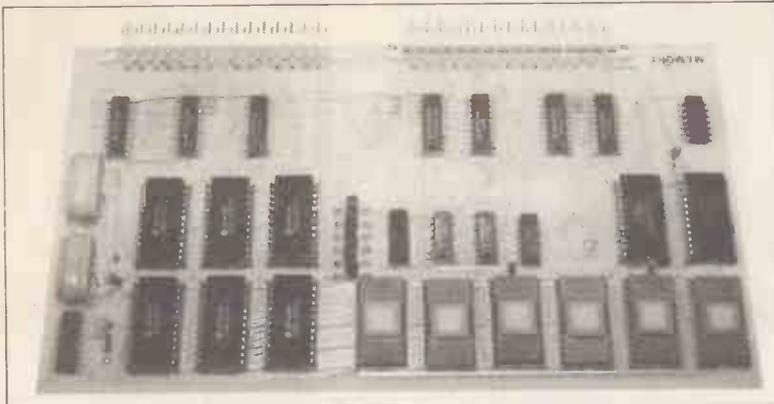

Memory board.

The Wave 2 might be considered at this stage just like another programmable polyphonic instrument with program numbers punched in on the numerical keypad. But it is also like an analogue synthesiser and if you want to change any of the settings you simply move the desired control in the analogue section. This gives great potential for continually updating sounds during performance, with memory storage at any time.

**Analogue Controls**

In the 'Multiple Function Analog Control Panel' from left to right, we start with a Master Tune for adjusting the pitch of all oscillators simultaneously  $\pm$  semitone to other instruments and a Master Volume output.

Next there are two ADSR generators: Envelope 1 and 2. In the first of the 3 panel modes, indicated by LEDs in the Panel Function section and selected from a 'Display Select'

button, Envelope 1 can be used independently for the Low Pass Filter and the PWN. Envelope 2 controls the VCA shape (or loudness). The maximum Attack time is 14 seconds with Decay and Release lasting up to 30 seconds.

Switching to second panel mode, the top controls now determine LFO parameters for setting a delay before the LFO operates, Waveform (continuously variable through triangle, sawtooth, reverse sawtooth and square wave), intensity of modulation and LFO speed.

The LFO can be selected by viewing the LCD display and inserting a '1' instead of an '0' after two code letters representing modulation of pitch, partial wave numbers, filter frequency and VCA, with LFO triggering able to give sequential running of the oscillators. What was Envelope 2 now becomes Envelope 3 and has Attack, Decay and Depth controls for EG pitch changes. Although the adjustments made in each panel mode are held whilst you set your sound up, in order to retain the complete synthesiser 'preset' you must then put it in a program from 0 to 99, using Data

Transfer, otherwise the sound will be lost on selection of another program. Data Transfers can be done in 9 different ways allowing update of certain sections of information.

Analogue panel 3 mode now assigns the original 8 controls of Envelope 1 and 2 as volume level outputs for the eight tracks of the sequencer/arpeggio digital recorder in the instrument. The LFO speed control now adjusts the sequencer master clock rate.

At first, this jumping around from one mode to another appears slightly confusing, but of course, all the information can be seen as numerical values for each setting on the LCD display. In performance, switching from one panel mode to the next is simply a touch of a button. I like this method, because you can focus on the LCD display rather than peer back and forward over numerous controls.

The output of the standard Wave 2 instrument is stereo and for each program there are outputs A and B. It can also be supplied with 8 individual outputs from its sequencer. The 'Group' button (in Display Select) chooses either or both channels and is indicated on the main display and on the two Panel Function LEDs. So you can produce two completely different sounds (based on the same Wavetable) from the same program.

Exciting possibilities come from this truly stereo programming. Selection of VCA envelopes will simulate panning from one channel to another and echo, with individual change of one channel only giving de-tune, chorus and complex tonal effects.

**Keyboard and Tuning**

Using the keyboard select modes you can specify (counting from the left) from which note the split point should be to put channel A and B on each half.

Besides the full keyboard in 8-note polyphonic mode, there are 8 other modes that give choice of oscillators on each channel, choice of the number of oscillators on each note and keyboard split. This makes utmost use of the 8-note system — you can achieve rich string effects from 4 oscillators on two monophonic notes using key split or play top solos to left hand chords just as easily.


Other uses for the keyboard (highest note played) voltage are: 'Keyboard Follow' opening the filter up the keyboard over 7 increasing amounts, loudness balance at low and high ends and particularly interesting, its control of PWN, being able to select individual waves on each note or produce whole sweeps of partials from note jumps.

Locating and modifying all information on the display is done by moving a cursor to the data e.g. SPLIT 10, and then typing a new number. There's a clear perspex spring-loaded wheel for pitch-bends (up or down 4 semitones) on the left of the keyboard that's usefully angled towards the player. I would have preferred at least an octave jump here.

Each oscillator can be adjusted in 4 'micro' steps from -1 to +2 for rich 'chorus' and de-tuning effects. A further instruction (shown on the display along with micro tuning)



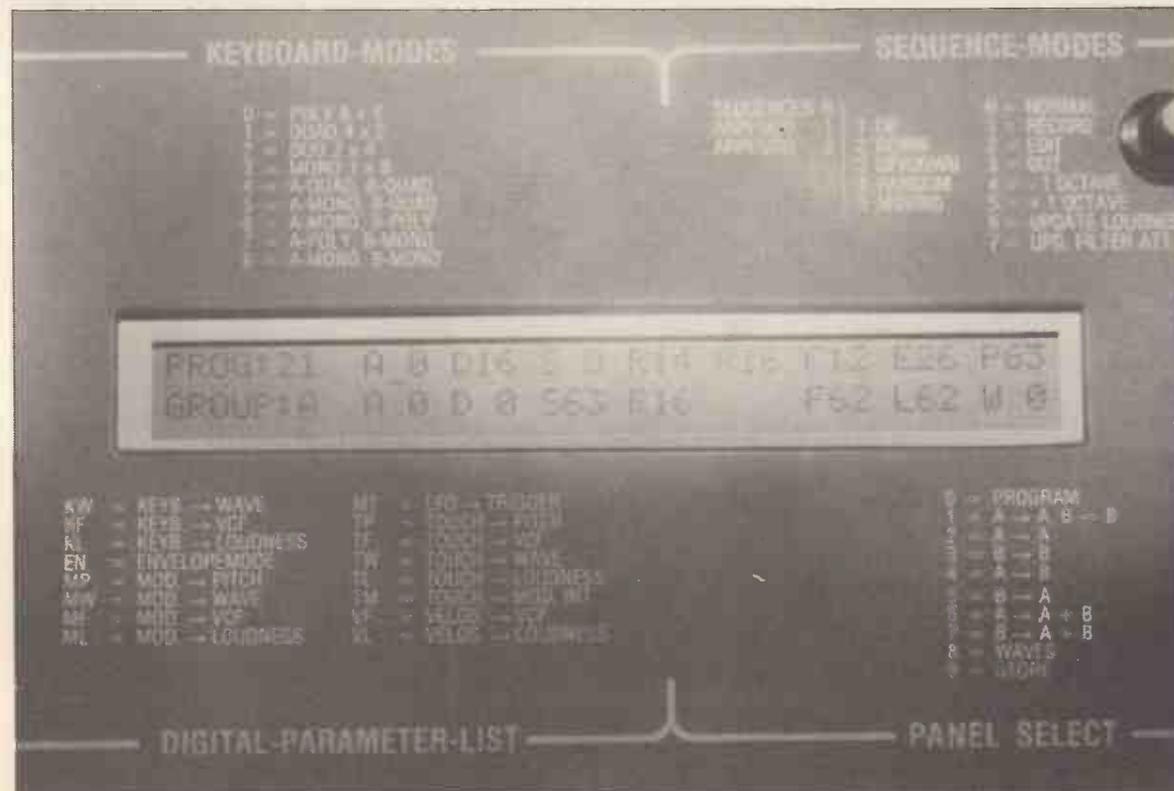Multiple Function Digital control section.



Panel Display showing Analogue control settings.



Multiple Function Analogue control section.



Rear panel sockets.

enables the pitch of individual oscillators to be stated as a number which is the semitone count from the bottom note e.g. '12' is 1 octave up, '31' is 2 octaves and a fifth up. All eight oscillators are therefore capable of wide parallel interval playing from one or more notes (Ravel 'Bolero' style!).

Two types of control from finger touch operate. First, there is the 'electric piano' kind of touch sensitivity that generates a control voltage

dependent on the velocity of a pressed key. This will open the filter or increase the volume on faster touch playing.

The second type is pressure sensitivity, the control voltage being derived from the action of a firmly pressed key. A little disappointing, in terms of mechanics, as the whole keyboard droops with the key(s) depressed (memories of the EMS Polysynth here!) yet it does its job of

altering (individually or collectively) the filter, partial wave numbers, loudness and LFO modulation intensity.

## Partials and Extras

If you play big chords on a particularly dramatic wavetable, the sound can be very dense and somewhat overpowering. This is where the ability to select one or more waveforms of a Wavetable is very useful. It's done by adjusting the 'Env. 1 Wave' control which really sets the number of waveforms heard in sequence from 1 to 64 at attack, decay, sustain (holding one waveform) and release times. Aurally, a sweep at varying speeds from one waveform to the next is heard, starting from the point set by the PWN control (e.g. 1/2-way is waveform 32). If a start is selected from say, waveform 50, then provided the ADSR carries on after 64, the table skips back to 1.

Here's another plus — the effect will convince you that echo and reverberation are present on long releases!

Every wavetable has triangle, sawtooth and pulse waveforms available as the basis of standard analogue synthesis. These occur usually at the end of the PWN sweep where waveforms are more widely separated on the control's movement. The Low Pass filter present can further modify a partial wave using its Cut-Off and Emphasis (resonance) controls.

'Test and Cancel' is an unusual facility that checks oscillators, so that if a problem should arise, the particular board can be located and 'cancelled' — ideally a safety feature to get you out of trouble on stage.

The rear panel has a data in/out socket for micro connection, control voltage in, gate in and out, headphones, sustain switch, and cassette 5-pin Din interface socket. All the program information can be dumped onto a standard mono cassette (it takes about one minute). Instruction 1 dumps the program data, 2 dumps the sequencer tracks, 3 loads from cassette and 4 will verify a dump.

## The Sequencer

The addition of an 8-track digital recorder in the Wave 2 must make it a

really attractive proposition and it can be used to record up to 10 sequences and/or arpeggio effects. A sequence can only be recorded by entering each of the eight possible layers one at a time in monophonic fashion. The big advantage here is the possibility of recording 8 melodies using completely different synthesiser sounds. Alternatively, arpeggios that rise, fall or do both on a chosen chord, have random selection or continuously moving groups of notes, and have a specified number of notes in a loop taken from your chord are easily done using a keypad instruction.

A sequence can run from 0 to 99 times (the latter makes it a continuous repeat). Further layers would be played whilst hearing previous tracks. Provided memory is available (no running indication of this on the present model), up to 10 'labelled' sequences on up to eight tracks can be recorded. Routing can be changed while the sequence is running as well as in single step mode.

Needless to say, numerous editing features and modes of operation are available, with updating of pitch, filter, waves and EG filter control at the mixdown stage possible (Panel mode 3). A total of 2000 events can be recorded and an optional expansion card will bring this up to 6000 events in all.

## Conclusion


Because the Wave 2 is micro-based and software controlled it can easily be updated. Here lies its main strength although the purchaser will want the instrument to be versatile and fully operational when he buys it.

There were one or two 'bugs' in the system that I am informed will definitely not be in the production model and, like any other powerful control processor, has to be used with some thought to achieve its full potential. Jittering can occur if you stop PWN between two waves although in practice your ear would make you move on to a complete wave. Two nice features are auto-cursor movement from one data point to the next and the LCD display has a useful control that adjusts the 'output angle' to suit your position during performance. Wave 2's sequencer would be very versatile indeed if it could record realtime polyphonic music as well as single melodies and the initial click track needs to be a 'click' and not its present 'note' which clashes with your key notes. Another interesting extra that could be implemented is to have mixer settings remembered as you adjust them during your sequence realtime playback — but of course you have to stop somewhere! As the instrument stands it presents a new concept of sound synthesis in the studio or on stage. If you don't believe me, listen to its special sounds on E&MM's Demo Cassette 3!

Mike Beecher

E&MM

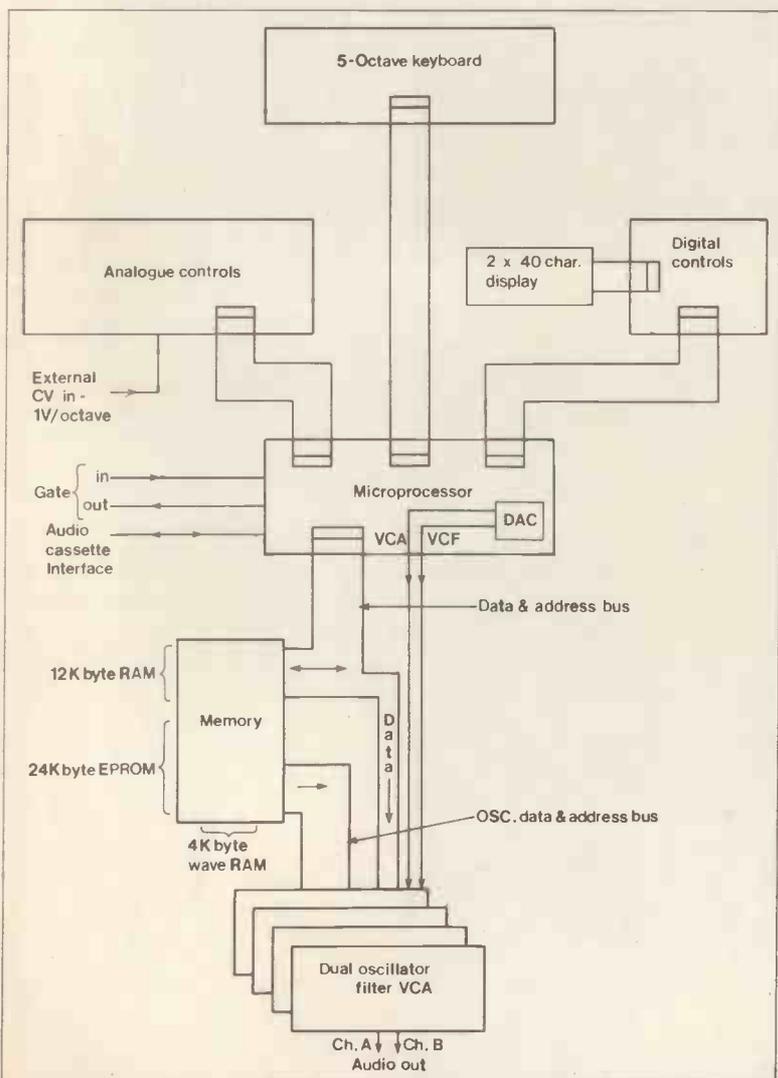The Wave 2 has been competitively priced at £3232.16 including VAT and comes in a black metal cabinet with electric blue front panel (Length 92cm, Depth 55cm, Height 17cm). It is obtainable in the UK from Desert Distributors, 6 Erskine Road, London NW3. Tel: 01-586 0357.



Block diagram PPG Wave 2.

**PRESENTING**

Products now available from  
Great Britain's leading synthesiser  
specialists



**NEW!**

**GNAT SYNTHESISER**  
R.R.P. £99.00


**WASP DELUXE**  
R.R.P. £345.00



**WASP SYNTHESISER**  
R.R.P. £199.00

**CATERPILLAR  
POLYPHONIC  
KEYBOARD**  
R.R.P.  
£149.00

**NEW!**

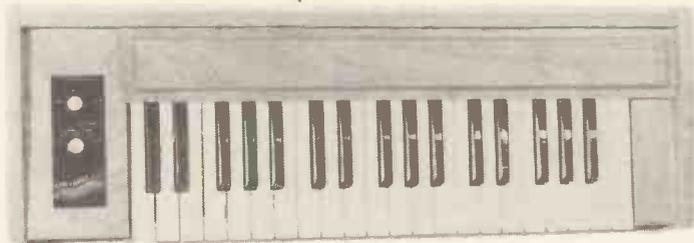

**SPIDER  
SEQUENCER**  
R.R.P. £199.00

**CATCH US IF YOU CAN!**



**ELECTRONIC DREAM  
PLANT** (OXFORD) Limited (Contact your nearest WASP dealer  
for full product details)

# Guide to Electronic Music Techniques

## Microphone techniques for 'Musique Concrete'

### Lawrence Casserley

I've already talked about how to manipulate sounds on tape and these ideas apply to any sounds that you might want to use. Now I want to talk about ways of getting the sound you want from acoustic sources.

In order to do this it is necessary to convert acoustic energy into electrical energy by means of some form of microphone. There are many different types of microphone and they can be used in many different ways.

Microphones can be divided into two broad classes - air mics and contact mics. Air mics detect variations in voltage that can then be recorded and/or manipulated electronically. There are various categories of air microphone and it is worth knowing a bit about them. First, they can be divided according to the method of energy conversion. The two you are most likely to encounter are dynamic (or moving coil) and capacitor (used to be called condenser). A dynamic mic is effectively the inverse of a speaker - a diaphragm which is moved by pressure waves in the air is attached to a coil which moves with the diaphragm in a magnetic field thereby generating current in the coil. A capacitor microphone, on the other hand, uses the diaphragm as one plate of a capacitor with a charge on it. As the diaphragm is moved by the air, the distance between the two plates changes causing a change in the voltage across the capacitor. As the capacitor must have a charge on it, and because, for technical reasons, most capacitor mics contain a pre-amp it is necessary for them to have some form of power supply, which may make their use more complicated. Apart from that, you mostly won't need to worry all that much about the different types. If you don't understand why these two approaches work you'd better bone up on basic electronic theory; there are a number of good books available and Robert Penfold's articles in E&MM will help.

A more important consideration is the polar diagram, or directional characteristic, of the microphone. The two characteristics you are most likely to encounter are omnidirectional and cardioid. An omnidirectional mic is equally sensitive to sound from all directions, while a cardioid mic has a roughly heart-shaped characteristic with a null at the rear of the mic and the most sensitive point at the front (Figure 1). This is the most commonly used directional characteristic and this type of mic will usually be the most useful to you. Generally we are concerned with recording a particular sound from a particular source and we want to direct the most sensitive point of the microphone towards it.

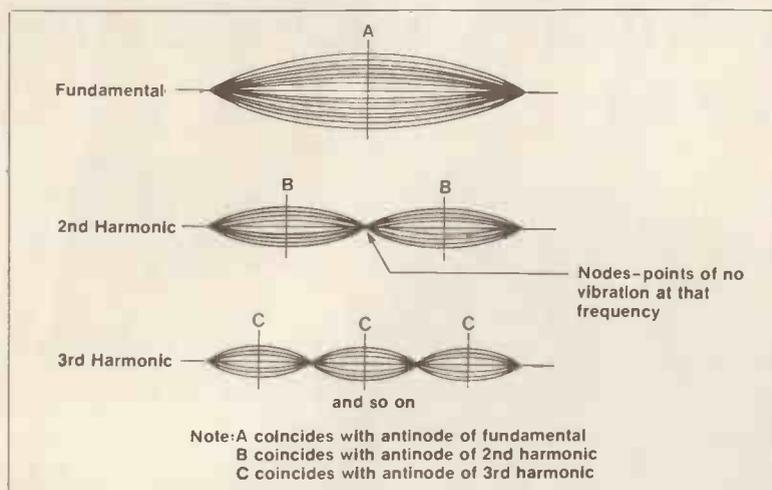


Figure 2. Modes of vibration of a string.

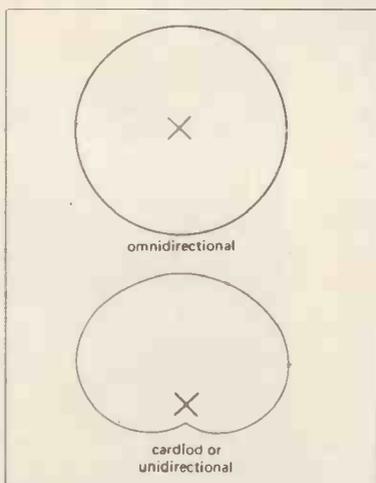


Figure 1. Microphone Polar diagrams.

Contact mics also come in different types. There are two common types. The first is not really a contact mic at all, but a magnetic pickup which senses the movement of a metal object within its magnetic field. This is the type of pickup used on electric guitars and similar instruments and can be useful for some applications provided the vibrating body is metal. Magnetic pickups are mounted close to the vibrating object whilst contact mics detect vibrations directly. The most common method for achieving this is to use a piezoelectric crystal which produces a small output voltage when stressed. The vibrations of the sound-producing object to which the mic is attached produced stresses in the crystal, thus generating a waveform analogous to the vibrations.

The other point to note about microphones is impedance. Most professional microphones are low impedance (200 ohms or less), but cheaper microphones and most contact microphones are usually of much higher impedance and some domestic tape recorders only accept high impedance mics. The most important point is to get the impedance matched or else you will get hum, noise and/or overload problems. Also, if you are using high impe-

dance mics (particularly contact mics, which sometimes have a very high impedance) keep the leads as short as possible in order to reduce hum and other interference.

Finally, before talking about what you can do with your microphones, a few comments about what microphones to use.

There are a number of mics available in what is usually called the semi-professional range. I'll first mention a couple which I have found useful for this sort of work. For a dynamic mic the AKG D190 is hard to beat for price vs. performance, giving a lot of the quality of a really professional mic for about £50. A "cheap" capacitor mic is the Calrec 652 (which I use quite a lot) which is a similar price to the D190 but, of course, you'll need a power supply, which is extra. It's worth trying some of the electret mics (a cheaper form of capacitor, usually powered by a small battery in the mic itself). There are a number of types available at various prices.

For contact mics there are various types ranging from a few pounds up to hundreds. Many of the very cheap ones are apt to fall apart unless you are extremely gentle with them, so may prove a false economy, but there are several in the £10-£20 range that are worth looking at. I use a number of Schaller mics which are really sold as acoustic guitar pickups, but can be attached to all sorts of things and they are fairly robust. Also ColourSound do a range of pickups that are worth looking into. In the more expensive range there is a new capacitor contact mic by DI Tapes Ltd. (at 107 Park Street, London, W1Y 3TA) which was designed as a piano pickup and sells for about £50. This mic is very sensitive and has a good frequency response (often a problem with the cheaper models). There is also an extensive range of contact mics by Barcus Berry at various prices. Lastly, there are all sorts of odd pickups that can be bought very cheaply on the surplus "junk" market and it is worth getting some of these to experiment with; and, don't forget, amazing things can be done with dismembered telephone receivers! (To cover myself I

must advise you not to use Telecom property!!)

### Using microphones

The one really important problem with mics is where do you put them - how close to the sound source? - which part of the source should they point at? There are no fixed rules for this - just experiment until you get the sound you want; but it will help to have some idea of the principles involved. The most important thing to realise is that a vibrating body does not vibrate in the same way all over and therefore does not produce the same sound from all parts.

Let us take a simple example; a vibrating string will have a number of modes of vibration (Figure 2) corresponding to the different harmonics; placing a mic over different parts of the string will emphasise different harmonics and, therefore, alter the timbre. Electric guitars with more than one set of pickups exploit this principle to get different tone colours. But if we have a moveable pickup or an air mic we can take the idea further by running it along the vibrating string. If we are over the middle of the string (Point A in Figure 2) all the odd harmonics, and especially the fundamental, will be emphasised and all the even harmonics will be at a nodal point and, therefore, de-emphasised. At point B, the second harmonic and its odd multiples (6, 10, 14, etc.) will be emphasised; at point C the third harmonic and its odd multiples (9, 15, 21, etc.) will be emphasised; and so on, with the fundamental getting progressively weaker as we move toward the end of the string. While other vibrating bodies tend to be more complex than a string, the same principles apply, and the best bet is to experiment by moving the mic over the surface - indeed you may want to use the filtering effect of moving the mic while you are recording.

Another matter to consider is the distance of the mic from the point of excitation (hammer striking object, bow scraping string, etc.). If the mic is very close to the point of excitation the noise made at this point will be emphasised, while if the mic is further away the characteristic resonance of the vibrating body will be emphasised.

All these points apply to both air and contact mics, but remember that contact mics, because they are actually attached to the vibrating object, may affect the way it vibrates and, therefore, the sound it makes. This should be taken into account, particularly on small or light objects, or if you are trying to get a long resonance (the extra weight of the contact mic will tend to damp out resonances more quickly).

Remember that we can use the mic as part of the whole process of making the sound we want to hear; it is not just a mechanical device, but can be used as a creative instrument - all it needs is imagination and a willingness to experiment. E&MM

# BECOME AN INSTANT MUSICIAN — NO EXPERIENCE NECESSARY


## CASIO'S REVOLUTIONARY VL-TONE As featured on "TOMORROW'S WORLD"

The success story of 1981. Hundreds sold already!

Create your own music with a VL-TONE. You combine the sound, rhythm and tempo and the VL-TONE plays it back... beautifully!
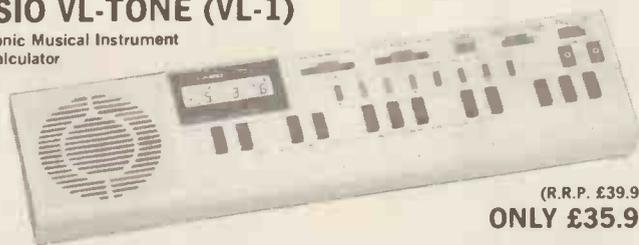
### CASIO VL-TONE (VL-1)

Electronic Musical Instrument  
and Calculator



(R.R.P. £39.95)  
**ONLY £35.95**

Thanks to Casio's V.L.S.I. circuit and revolutionary technology you can now compose and play music with one finger! It's as easy as this: First choose one of the five Preset Instrument Sounds: Piano, Violin, Flute, Guitar or Fantasy. Now enter the notes of a melody into the memory (maximum 100 notes) via the numbered keyboard.

Notes entered (or played back) are shown digitally on the liquid crystal display. Memory break-in allows you to correct any mistakes and add or delete individual notes.

You then simply press the One Key Plan key to have each note played back in sequence. Vary the tempo and duration of the keystroke to create a melody. Now you're playing the music! To add the professional touch, select one of the ten Auto Rhythm accompaniments and adjust the 19-step Tempo Control, with digital readout. Playing in time to the rhythm, record your best performance back into the memory.

The Auto Play Function lets you re-listen to the melody you have just recorded. A repeat function can give you four non-stop playbacks. Choose any of the Auto Rhythms to accompany your recording and vary the tempo and pitch of both. For a change select another instrument voice, or switch to ADSR and programme in eight digits to create your own unique sound. With over 80 million variations of Attack, Decay, Sustain level and time and Release, as well as tremolo and vibrato intensities to play around with, the only limit to your creativity is your own imagination. Manual playing, with Auto Rhythm, can also be recorded and played back. A medley of tunes can be entered up to a maximum of 100 notes.

VL-1: 29 note monophonic synthesiser with Octave Shift expanding the range to almost 5 octaves. Calculator: 4 basic calculations (+, -, X, ÷) with constants and percentage. Non-volatile memory and square roots. 8 digit display.

Facilities: LC Display of notes, including sharps, tempo and calculations. Battery saving Auto Power Off with protection of the stored melody and the pre-set ADSR data (or calculator memory total). Built-in amplifier and loudspeaker. Pitch control for tuning. Output jack for external amplifier or tape recorder. (0/p 0.5V rms).

Power supply: Four AA size batteries last approx. 12 hours playing or 4,000 hours calculating. AC adaptor, type AD 4160 costs £5.

Dimensions: 30 x 300 x 75mm (1 1/4 x 11 3/4 x 3"). Weight: 438g; 15.4oz. Complete with instruction book, Song book and soft cover.

## NEW CASIOTONE CT-202

"Son of success... the two harpsichords demonstrate the Casiotone's talent for sparkling, crystal clear tones... Even more impressive is the clav..." (Melody Maker).

### CT-202



(R.R.P. £325)  
**ONLY £275.00**

Polyphonic playing of 49 instruments over 4 octaves. 3 vibrato settings and sustain switch. 4 voice memory function with push-button selection. Pitch control (+/- 1/4 tone). Built-in amplifier and speaker (10W output). Output jack (5 kilohm, 1.4V max). Power source: AC only. Dimensions: 90 x 866 x 284mm (3 3/4 x 34 1/4 x 11 3/16) 7.15kgs (15.8lb).

#### OTHER CASIOTONES (Polyphonic)

MT-30. 22 instruments. 3 octaves. Mains/battery (RRP £115) £95.

CT-301. 14 instruments. 4 octaves. 8 x 2 rhythm accompaniments. Vibrato and delayed vibrato. Pitch control. Output jack. AC only (RRP £285) £245.

CT-401. As CT-301 but with Casio Auto Chord for one finger or auto accompaniment. Major, minor and 7 chords with bass. Sustain and hold (£345) £295.

Send 20p (postage) for our illustrated catalogue of selected CASIO, CASIOTONE and SEIKO products.

Delivery normally by return of post, subject to availability. Send your order FREEPOST, no stamp required.

Price includes VAT and P&P. Send your company order, cheque, P.O. or phone your ACCESS or BARCLAY-CARD number to.

## The latest craze sweeping the country "CUBE MANIA" — FREE OF CHARGE!


You can have this Hungarian Magic Cube (Rubik's Cube) absolutely free with any purchase from us totalling over £17.50.

Supplied only on request, at time of ordering. Offer closes 31/8/81. Subject to availability.

Invented by Prof. Rubik of the Budapest Academy of Design, this 3x3x3 array of 27 cubes starts off with each external face of 9 unit cubes in one of six colours. Although it does not come apart, any single layer of 9 cubes can be rotated about its centre, quickly confusing the colour symmetry.

Since there are 43,252,003,274,489,856,000 permutations, it may take a while to make just one face all the same colour again, and just a little longer to return it to its original pattern!

With step-by-step solution

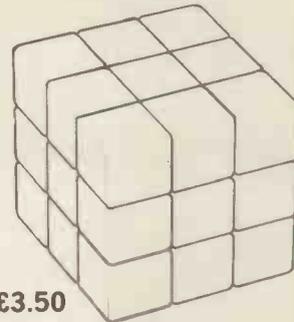

Sold separately **ONLY £3.50**

## THESE SPACE INVADERS WILL ALARM YOU

### CASIO'S MOST AMAZING WATCHES EVER

Display: Hours, minutes, seconds, am/pm, day and date. 12 or 24 hour format.

Auto Calendar: Day, date, month, year.

Alarm: 24 hour, with "On" symbol.

Hourly Chimes: Time signal every hour, on the hour. Easily switched on or off.

Professional Stopwatch: Lap times etc, from 1/100 second to 24 hours.

Dual Time: Second time zone.

Calculator: 8 digits, four functions, with constant and display symbols.

FINGER-TOUCH KEYBOARD.

DIGITAL SPACE INVADER GAME

with sound effects and scoring.

Water resistant case. Mineral glass.

CA-90: 46 x 36 x 10.55mm. Black resin

(RRP £29.95) **ONLY £24.95**

CA-901: 40.5 x 35.2 x 10.5mm. Metal

(RRP £34.95) **ONLY £29.95**

**CA 901**



### CASIO ALARM CHRONOGRAPHS

100-metre water resistant



**W150C**  
Stainless-steel case  
black resin strap  
**£25.95**



**W150**  
All stainless steel  
**£32.50**



**W100**  
All black moulded resin  
**£19.95**

All have an easily-read display of full time and calendar, with half-hourly time signals which can be switched on or off. Easy-to-use functions include: 24-hour alarm. Professional stopwatch measuring lap times, etc., to 1/100 second. Countdown alarm timer with repeater memory function. The time is always visible regardless of the display mode. One-touch selection of 12- or 24-hour format. Micro light for night viewing. ±15 seconds/month accuracy. Amazing 5-year battery life. 9.65mm thick case with mineral glass face.

### OTHER CASIO WATCHES

Sports: F5, resin £6.95. Sports Chronograph: F500, resin £9.95.

ALARM CHRONOGRAPHS. F81, resin £15.95. Melody A/C: M12, resin £19.95. M1200 S/S £29.95. LCD Analogue/digital A/C: AA81, chrome £29.95. AA82, S/S £39.95. AA81G, gold plated £49.95.

\*\*\*NEW!\*\*\*UC50W, S/S 50 metre water resistant A/C with full month calendar display with forward and reverse stepping, alarm, chimes, etc £19.95.

### CASIO CALCULATORS

\*\*\*SPECIAL OFFER. FX502P programmable with FREE MASTERPACK software kit (RRP £17.95) and 3 Rubik's Cubes **ONLY £74.95**. FA1 cassette adaptor £19.95.

Digital Space Invader game: MG880 £10.95. MG770 £12.95.

With alarm/s, calendar etc: BQ1100 Biolator £16.95.

With melody alarm/s: UC360 £19.95. UC365 £19.95. UC3000 £27.95. ML75 £17.95. ML90 £19.95. MQ1200 £19.95. ML2000 £22.95.

SCIENTIFICS: FX81 £12.95. FX100 £16.95. FX510 £19.95. Programmable: FX2700P £19.95. FX180P £19.95. FX3500P £22.95.


With clock, alarms, stopwatch, etc: FX6100 £18.95. FX7100 £24.95. FX8100 (also has calendar function) £24.95.

# TEMPUS

Dept E&MM/7, FREEPOST,  
164-167 East Road  
Cambridge CB1 1DB  
Tel: 0223 312866

# SOUND ON STAGE

Ben Duncan

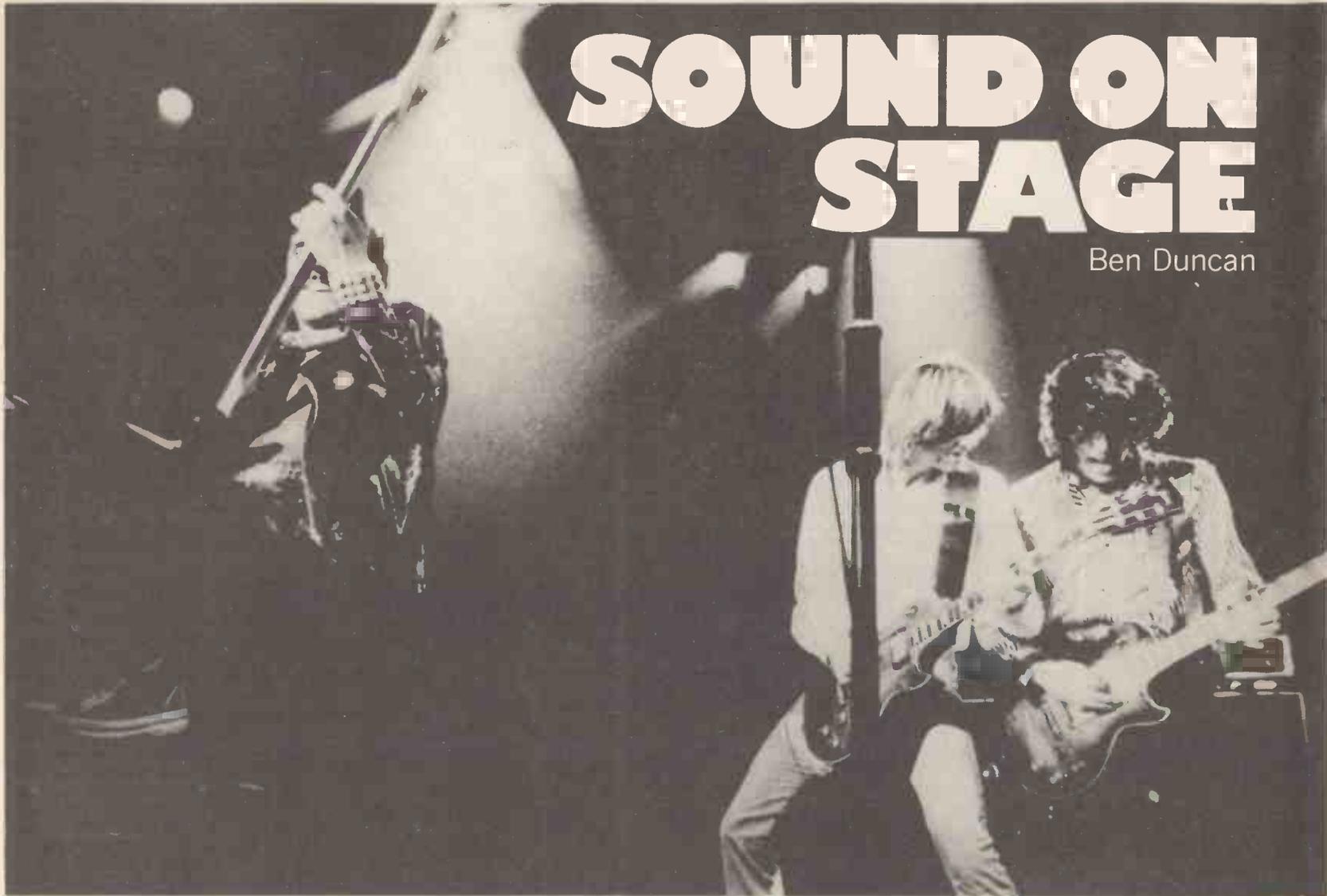

Thin Lizzy

## Power, loudness and power amplification

Regrettably, there is nothing very tangible in the relationship between amplifier power, sound level and perceived loudness; this is something many musicians are painfully aware of, after having parted with lots of cash for a casually described 'megga-wattage' which didn't live up to expectations! Broadly speaking, a tenfold increase in sound level or amplifier power corresponds to a mere doubling of loudness to our ears. Thus doubling the power of your instrument amps can be expensive yet disappointing. All other factors being equal, the increase in loudness will be very subtle indeed. But variations in the methods by which amplifier watts are measured, together with the effects of loudspeaker impedance, efficiency and dispersion pattern can all work together to make, say, a nominal '100 watts' sound impossibly loud or puzzlingly mute.

These are objective, measurable effects; others are subjective, but equally real. Colouration (the emphasis of certain frequencies) in the speakers and distortion can suggest immense loudness, whilst clean, uncoloured sound rarely seems loud enough. The general result is that amplifier watts should be taken with a generous pinch of salt; the loudness your ears perceive is always the final arbiter! When a good valve amplifier is

overdriven, it produces a distorted sound that is both immense and palatable. Apart from their ability to add ethereal ambience, emotion and warmth to the guitar, valve amplifiers of any given rating invariably seem louder than equally powerful transistor counterparts. The reason lies partially in psychoacoustics — the characteristic distortion of the valve amplifier simply sounds loud — but also in the conservative nature of valve amplifier power ratings. Additionally, the output power of any amplifier is at least doubled by gross overloading, and in good valve amplifiers, this potential extra power is musically acceptable and thus usable, whilst in transistor amplifiers, it is usually very discordant and 'ear-ripping'. As a result, a carefully chosen 30 to 100 watts of valve amplification is adequate for playing loud, raunchy music almost anywhere! It's not surprising that valve amplifiers are the quintessential sound of Rock...

In creative hands, a handful of transistor amplifiers can exhibit 'musical' overload characteristics similar to good valve amplifiers but in general, transistor amplifiers produce tinny, harsh, brittle, metallic effects when they are overdriven; they sound either crystal clear or extremely obnoxious. This doesn't mean that the

transistor amplifier is useless — merely that different techniques are needed to coax music out of it. Or, to look at it another way, the transistor amplifier suits some types of music better than the valve amp. In general, transistor amplifiers have to be played clean at levels well below overload to avoid the generation of unpleasant sounds. This means that the potential of full power isn't available, and adequate power ratings will be at least three times those indicated above for valve amplifiers, ie: 100 to 300 watts for lead guitar.

The transistor amplifier is best suited to clean styles of playing and is therefore very acceptable on bass or guitar work demanding a clinical, sterile feel, whilst the harsh, ear-ripping characteristics were well suited to the punk idiom of '76-'79. However, acceptable distortion can be introduced via FX circuits and the speakers in order to extend the versatility of the instrument and make it sound louder without discomfort. Neither type of amplifier is inherently 'the best', there are good and bad examples of each. It's only that one is better suited to your music, your skill and your guitar. In short, the best amplifier is the one you can develop a relationship with.

As a potential amplifier purchaser, listen to, or better still, try out as many

models as you can — preferably with your own guitar or bass, and bear in mind that the sound of a 'head' (separate) amp will be profoundly influenced by the speakers it's tested with, amongst other factors. It's all too easy to end up with a bland and unsympathetic beast of an amplifier simply because it was demonstrated with a particularly good guitar and speaker cabinet! Find the point(s) where the amplifier overloads, and listen to how the sound changes above and just below the overload point. Is it a useful and potentially musical sound? Or does it rip your ears and shatter windows? If you ever intend to practise with the amp at low levels, then listen to the amp at these levels. The sound may be different, but again, is it a useful sound? Above all, talk to other guitarists, and visit your local group gear shop and try different types of guitar amps with different wattage ratings.

## Speakers — an introduction

Two types of speakers are used in conjunction with electro-musical instruments. The first, akin to the hi-fi speaker, is primarily a reproducer, which aims to convert electrical waveforms into facsimile air vibration.

## Frequency


10Hz

100Hz

1000Hz

10kHz

20kHz

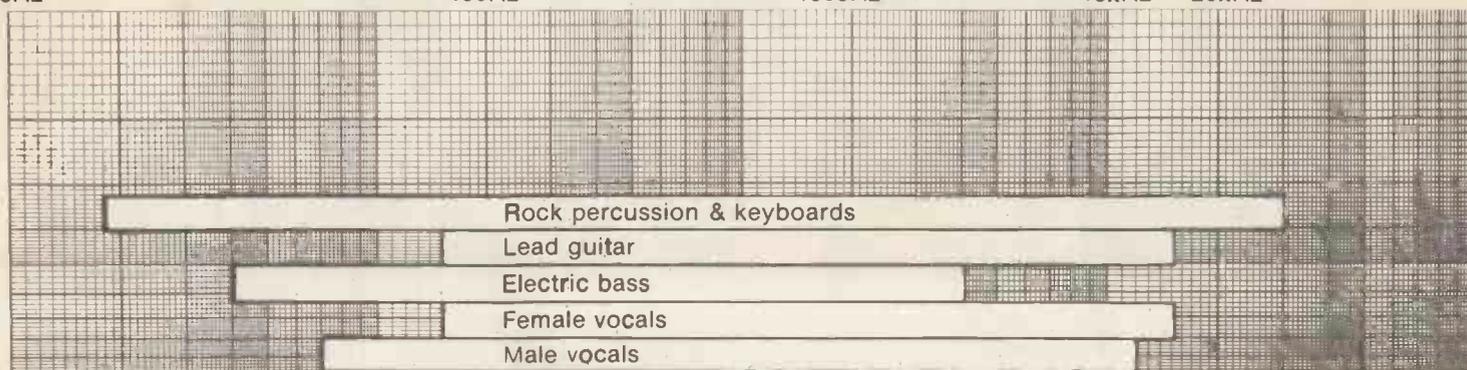

Frequency range of Rock instruments and vocals.

These 'reproduction' speakers are most useful for keyboards and are the foundation of the best PA systems. We'll look at this type of speaker later in the series, particularly as it concerns the bass player. Meanwhile, speakers intended for the guitarist and for vocals PA provide the antithesis of pure reproduction — again they are part of the instrument. Like the amplifier, the speaker can be driven hard to subtly mould the nature of a valve amp's distortion, giving a slight 'edge' to the sound for instance. In conjunction with a transistor amplifier, the speaker's distortion can be dominant at average levels, and helps to give 'roundness', 'punch' or 'bite' to an otherwise neutral sound. Some speakers feature metallic centre domes to enhance the upper harmonics of the guitar; these are best avoided with transistor amps, which tend to emphasise these harmonics naturally. Whilst the centre dome will certainly give extra bite, it will also exaggerate the tinny, metallic sound generated by the amplifier to a fatiguing degree. In this case, a speaker with a conventional paper tweeter cone is preferable.

The prime requirements for guitar and vocal speakers are an efficient mid-range response and a power capacity that's about twice that of the amplifier. The second requirement arises because guitarists invariably overload their amplifiers, and in this case, the power output will be well in excess of the amplifier's nominal rating. Hence it's a sensible and well proven rule of the thumb to allow a 100% power margin for guitar speakers. Although a modern 12 inch driver will often meet these requirements, in the past, high power drivers weren't readily available, if at all, and it was necessary to use several 12 inch or 10 inch drivers to achieve a sensible power capacity, eg: the traditional 4 x 12 cabinet. At the same time, guitarists discovered the unique musical properties of overdriving these marginally rated speakers with valve amplifiers. As a result, another school of thought has arisen — rate your speakers to match the power capacity of the amplifier, enjoy the music and pray that they don't blow up! Fortunately, this philosophy works, provided you're using the right speakers, preferably the ones that the manufacturer supplied. The secret here is essentially a case of causing the cone to produce distortion without burning out the voice coil.

Term	Definition
Head	— an amplifier discrete from the speaker cabinet.
Combo	— a combined speaker and amplifier.
Slave	— a discrete power amplifier without tone controls, usually driven with the 'line level' signal from the guitar amplifier.
Loudspeaker	known variously as a driver, a cone driver, a chassis speaker, a horn-loaded driver, etc, when the essential sound generating component is referred to.
Loudspeaker	known variously as a 'cab', cabinet, enclosure, column, direct radiator speaker, horn-loaded speaker, horn, baffle or reflex — when a complete loudspeaker system is being discussed.
Direct radiator	— also known as an <i>infinite baffle</i> , this type of speaker cabinet is the commonest to be found on stage; the driver is visible and couples directly with the air.
Column speaker	— a specialised form of direct radiator, where several drivers are arranged in a line to control the sound dispersion.
Horn-loaded loudspeaker	— also known as in various guises a horn, 'bin', 'bullet' or 'lens', the driver is usually hidden and couples with the outside air via some form of expanding tube.

Table 1. Glossary of technical terms

The overall result is that no hard and fast rules can be laid down for guitar and vocal speakers — the 4 x 12 inch, 2 x 10 inch and even 4 x 8 inch are all broadly similar and equally valid approaches. The only definite proviso is that driver(s) with a diameter greater than 12 inches will rarely provide sufficient 'top' and should be avoided; 10 inch and 12 inch speakers are the traditional choice for guitar and vocals rendition, and not without good reason! For bass, the frequency response requirements are shifted down by around two octaves. 'Top' becomes unimportant, whilst the overriding need for good low bass response governs the cabinet size. The traditional sound of the electric bass puts great emphasis on the low notes, as if to mimic its cousin, the double bass. Because the ear is insensitive to low bass, high sound levels are essential for them to become audible. In the double bass, this is achieved by the sheer size of the vibrating panels. Likewise, for the electric bass, to make the bottom notes audible, a large area of speaker cone is called for, together with a high-power amplifier. Thus the traditional 60's bass sound was usually achieved with 24, 18 or 15 inch drivers, singly, in multiples, or by horn loading, which can achieve the same results with a smaller driver, together with a number of other advantages, though at greater cost.

However, the bass has few interesting sounds to offer when the harmonics are suppressed in this manner. The bass becomes much more expressive when the harmonics

are emphasised; something that the funky bass players of the '70's extolled. To make these harmonics audible, one can simply use a mid-range speaker in conjunction with the large diameter bass speakers to boost the upper octaves, or, alternatively, use 12 inch drivers. These have a natural response which extends into the upper register of the bass but to achieve audible bass (simultaneously), a large cone area is also required — hence 4 x 12 inch drivers again, which elegantly combines good 'top end' response with an area (and hence bass response) more than equal to two 15 inch drivers. Finally, unlike the guitar, a heavily thumbed bass readily causes speaker cones to bang against their end stops. As this is potentially much more disastrous than the voice coil overheating that can occur in guitar speakers, it's good practice to rate speakers intended for electric bass at *four times* the amplifier's nominal power capacity.

For vocals, the power and frequency response requirements are much the same as the guitar speaker's. Hence 8, 10 or 12 inch speakers, used in multiples to provide adequate power handling capacity. Although a peaky, coloured response will give a useful 'pokey' vocals sound that is just about capable of cutting through wailing guitars, it may aggravate tendencies to feedback, 'howling round' before you can raise the volume control to the sound level you require. Unfortunately, this problem can only be totally avoided by using microphones and speaker systems with a flat, uncoloured response.

Nonetheless, it's wise to steer clear of exceptionally coloured vocals speakers unless you can be sure they can be wound up to workable levels in practice. Vocals speakers also profit from special enclosure techniques, again to avoid premature feedback. The traditional column speaker, although much maligned, is excellent from this point of view. Containing between four and eight 12, 10 or 8 inch speakers in a vertical array, the typical column provides a well defined and 'forward' dispersion pattern, the idea being to keep the sound away from the microphone and the ceiling, from where it's likely to be reflected back to the stage. In many respects, a well designed column speaker is the ideal vocals speaker, short of a very expensive tri-amplified, horn-loaded system. In comparison with the currently trendy scaled down (and therefore compromised) models of large scale PA rigs, a pair of good columns exhibit the fine balance of delicacy and incisive 'punchiness' that is the hallmark of good mid-range and hence a good vocals speaker. Best of all, secondhand columns are available cheaply, being ostensibly 'out of fashion'.

When choosing a speaker cabinet, remember that you will have to carry it around! Today, there is rarely any intrinsic merit in owning a huge speaker stack, unless as a heavy metallist you demand an impressive and machismo stage set up; a well designed and sensibly small speaker enclosure can be just as loud and efficient as the monsters of the '60's. Again, listen to the sound of the speaker; a good cabinet will tend to produce a useful and acceptable sound without requiring much prompting from the amplifier's tone controls. Then stand back from the cabinet and try to judge how well the sound will project from a stage. Projection is all-important — don't forget that your audience also has to hear you! In particular, the low notes have a habit of disappearing as you move away from vented (reflex loaded) bass cabinets.

For many people, loudspeakers are as much a journey of self-discovery as the music they convey. You will only find the perfect speaker when you cease to be creative. Since the speaker is a part of your instrument, it deserves to be changed and toyed with as much as your guitar and your own ideas and feelings about music.

E&amp;MM

# WORLDWIDE WITH VIDEO

## Andy Emmerson

This month we look at video discs, what they do, what they don't do, how they do it if they do it and how they will affect you.

It is easy to draw parallels between video discs and video tapes on the one hand and audio discs and tapes on the other. Some of these comparisons are valid, others are misleading. Audio discs are simpler to manufacture than tapes because the process is a relatively straightforward moulding/stamping operation as opposed to the long-winded business of recording a piece of tape, cutting it to length and assembling it inside a complex housing. The action of making a video disc is a far more expensive and precise activity than making an audio disc but it is still more straightforward than making a tape. It is also a faster process than making a tape: tapes are still made in 'real time'. In other words, if you are producing a two hour film it will take you two hours to copy the film from the master recording and additional time to finish the assembly. This time factor alone restricts the number of video cassettes that can be produced. Video discs can be produced as fast as the machine can turn them out and this should therefore make them a cheaper item to make, all other factors being equal.

Continuing our comparison, audio discs are replay-only devices, whereas with cassettes you can make your own recordings. Exactly the same applies in video - but video discs have not yet appeared in this country - we only have tapes. Whereas records outsell music cassettes this is not yet the case in video and it may never turn out that way. However, given the choice of video tape or disc, which would you choose?

The first point to appreciate is that the quality of reproduction offered by video discs and tape is not the same. Many people find the quality of reproduction of a home video recorder perfectly adequate but most would admit that broadcast TV is better. Video discs on the other hand promise pictures and sound every bit as good as broadcast TV, with the promise of full hi-fi sound (even stereo in some cases) or a selectable foreign language soundtrack. The price of video discs and their players should be less than that of tapes and video recorders, say a third or a half cheaper. All sorts of 'trick' features will be standard such as slow motion, perfect freeze frame, reverse, fast scan and random access. The contents of the disc can even be still



The Philips LaserVision (formerly VLP) video disc system, which will be launched in the UK in mid-1981. Designed for the modern home, LaserVision produces high-quality pictures and sound on any domestic colour television set. The player can simultaneously be connected to a hi-fi system for full stereo sound.

LaserVision (formerly VLP) is capable of a multitude of functions, all at the touch of a button and with no wear to the disc. These include freeze frame, varying slow motion speeds in both forward and reverse and rapid forward and reverse search, enabling any section of the disc to be found in seconds. An exciting range of disc albums will be available when LaserVision is launched, including top feature films such as *Alien*, *Star Trek - The Motion Picture* and *Saturday Night Fever*.

pictures, up to 54,000 on one side! You could put an encyclopedia on a disc and access any individual page at random in less than 15 seconds.

With all these marvellous features there must be a couple of snags. Experience in the USA has shown picture quality to be variable due to poor disc pressings, though this can obviously be cured by better quality control. One side of a disc cannot contain a complete film, so you will have to interrupt your viewing to turn over, but this is not really a problem. No, the only real drawback with these devices is that they cannot record!! This is a serious disadvantage for the majority of video enthusiasts who use their video machines to 'timeshift', that is to record a favourite programme while they are away from home or even while watching another programme. Hopefully, some of the people who read this column are interested in things more creative such as shooting their own material, but once again this is something you cannot do with videodiscs. Even if

films on video disc turn out to be as cheap as, say, £10, the cost of the special player (say £250 to £400) is likely to outweigh the attractions of the pre-recorded programmes. Some people will of course be able to afford both tape and disc machines, and market research indicates that people who are already into video (i.e. existing VCR owners) have a greater interest in owning both systems than people who don't have a VCR. On the other hand, three out of five VCR owners expressed no interest in video discs.

Later this year video disc equipment will come on to the UK market and it will be interesting to see if these predictions are fulfilled. In any case, the increased competition and awareness in video will benefit all video enthusiasts. It is extremely likely that the arrival of video discs will force down the cost of video tapes, both blank and pre-recorded, and machines may well become cheaper. The VCR manufacturers may even retaliate with a low-cost replay-only

machine!

Finally, we ought to take a quick look at how video discs work. There is (predictably) more than one format and the three formats are (also predictably) totally incompatible. So discs made for one system will not be playable on machines of other types and considering the deals which manufacturers will make to sign up exclusive material for their own system this will probably reduce your choice of programmes, more so than with tape.

The three systems are known as VHD, Laservision and Selectavision. VHD is promoted by JVC and in this country by Thorn-EMI, so it seems set to enjoy the same success as their VHS system. The records are grooveless and the actual information is recorded by laser in minute pits. These are played back by a capacitance-sensing stylus which glides over the recorded surface. The stylus is guided not by grooves but by rows of even smaller pits on either side of the programme track. The disc itself is 10.2 inches in diameter and made of high-quality, conventional PVC, like an audio disc. To prevent contamination, the record must be handled in a protective sleeve.

System two was invented by Philips and is known as the Philips/MCA/Pioneer Laservision system. In this system the recorded information exists in the form of microscopic pits on the surface of a silvered disc, twelve inches in diameter. The silvered layer has its own built-in protective plastic surface - this avoids contamination from dust and all but the deepest of scratches. The pits are scanned optically, using a miniature laser. Again, there are no grooves.

The third system, Selectavision, is the property of the American RCA organisation and unlike the other two systems will not be available in Europe for some time. It lacks several of the impressive features offered by the other two systems because it has opted for a simpler but more restrictive method of operation. Like VHD it also senses capacitance variations as an electrode passes over microscopic pits in the disc surface. But, unlike VHD, the pickup travels in a physical groove which simplifies player technology but prevents freeze framing. The disc is also 12 inches in diameter and must be protected in a special sleeve.

Over the next few months you will hear a lot of claims and counter claims about discs and their merits - use this guide to form your own opinions.

E&MM

**FREE** OUR CURRENT BARGAIN LIST WILL BE ENCLOSED WITH ALL ORDERS.

**TRANSMITTER SURVEILLANCE \***

Tiny, easily hidden but which will enable conversation to be picked up with FM radio. Can be made in a matchbox — all electronic parts and circuit. £2.30.

**RADIO MIKE \***

Ideal for discos and garden parties, allows complete freedom of movement. Play through FM radio or tuner amp. £6.90 comp. kit.

**SAFE BLOCK**

Mains quick connector will save you valuable time. Features include quick spring connectors, heavy plastic case and auto on and off switch. Complete kit. £1.95.

**LIGHT CHASER**

Gives a brilliant display — a psychedelic light show for discos, parties and pop groups. These have three modes of flashing, two chase patterns and a strobe effect. Total output power 750 watts per channel. Complete kit. Price £16. Ready made up £4 extra.

**FISH BITE INDICATOR**

Enables anglers to set up several lines then sit down and read a book. As soon as one has a bite the loudspeaker emits a shrill note. Kit. Price £4.90.

**6 WAVEBAND SHORTWAVE RADIO KIT**

Bandspread covering 13.5 to 32 metres. Based on circuit which appeared in a recent issue of Radio Constructor. Complete kit includes case materials, six transistors, and diodes, condensers, resistors, inductors, switches, etc. Nothing else to buy if you have an amplifier to connect it to or a pair of high resistance headphones. Price £11.95.

**SHORT WAVE CRYSTAL RADIO**

All the parts to make up the beginner's model. Price £2.30. Crystal earpiece 65p. High resistance headphones (gives best results) £3.75. Kit includes chassis and front but not case.

**RADIO STETHOSCOPE**

Easy to fault find — start at the aerial and work towards the speaker — when signal stops you have found the fault. Complete kit £4.95.

**INTERRUPTED BEAM**

This kit enables you to make a switch that will trigger when a steady beam of infra-red or ordinary light is broken. Main components — relay, photo transistor, resistors and caps etc. Circuit diagram but no case. Price £2.30

**OUR CAR STARTER AND CHARGER KIT** has no doubt saved many motorists from embarrassment in an emergency you can start car off mains or bring your battery up to full charge in a couple of hours. The kit comprises: 250w mains transformer, two 10 amp bridge rectifiers, start/charge switch and full instructions. You can assemble this in the evening, box it up or leave it on the shelf in the garage, whichever suits you best. Price £11.50 + £2.50 post.

**GPO HIGH GAIN AMP/SIGNAL TRACER.** In case measuring only 5 1/2" x 3 1/2" x 1 1/2" is an extremely high gain (70dB) solid state amplifier designed for use as a signal tracer on GPO cables, etc. With a radio it functions very well as a signal tracer. By connecting a simple coil to the input socket a useful mains cable tracer can be made. Runs on standard 4 1/2v battery and has input, output sockets and on-off volume control, mounted flush on the top. Many other uses include general purpose amp, cueing amp, etc. An absolute bargain at only £1.85. Suitable 80ohm earpiece 69p.

**NEW KIT THIS MONTH!**

**CB RADIO** — Listen in with our 40-channel monitor. Unique design ensures that you do not miss sender or caller. Complete kit with case and instructions only £5.99.

**8 POWERFUL BATTERY MOTORS**

For models, Meccanos, drills, remote control planes, boats etc. £2.50.

**WATERPROOF HEATING WIRE**

60 ohms per yard, this is a heating element wound on a fibre glass coil and then covered with p.v.c. Dozens of uses — around water pipes, under grow boxes in gloves and socks. 23p per metre.

**COMPONENT BOARD Ref. W0998**

This is a modern fibreglass board which contains a multitude of very useful parts, most important of which are: 35 assorted diodes and rectifiers including 4 3amp 400v types (made up in a bridge) 8 transistors type BC107 and 2 type BFY-51 electrolytic condensers. SCR ref 2N 5062, 250uf 100v DC and 100uf 25v DC and over 100 other parts including variable, fixed and wire wound resistors, electrolytic and other condensers. A real snip at £1.15.

**FRUIT MACHINE HEART.** 4 wheels with all fruits, motorised and with solenoids for stopping the wheels with a little ingenuity you can defy your friends getting the "jackpot". £9.95. + £4 carriage.

**4-CORE FLEX CABLE**

White pvc for telephone extensions, disco lights, etc. 10 metres £2, 100 metres £15. Other multicore cable in stock.

**MUGGER DETERRENT**

A high-note bleeper, push latching switch, plastic case and battery connector. Will scare away any villain and bring help. £2.50 complete kit.

**EXTRACTOR FANS — Mains Voltage**

Ex-computer, made by Woods of Colchester, ideal as blower; central heating systems, fume extraction etc. Easy fixing through panel, very powerful 2,500 rpm but quiet running. Choice of 2 sizes, 5" £5.50. 6" £6.50. post £1 per fan.

**KEYBOARD BARGAIN**

50 computer type keys, together with 5 miniature toggle switches, all mounted on a p.c.b. together with 12 i.c.'s and many transistors and other parts, in a case but the case may be cracked or otherwise damaged. £11.50 + £2 post. This is far less than the value of the switches alone. Diagram of this keyboard is included if you request it, or it is available separately. Price: £1.

\* (Not licenceable in the U.K.)

**SUPER HI-FI SPEAKER CABINETS**

Made for an expensive Hi-Fi outfit — will suit any decor. Resonance free cut-outs for 8" woofer and 4" tweeter. The front material is carved Dacron, which is thick and does not need to be stuck in and the completed unit is most pleasing. Colour black. Supplied in pairs, price £6.90 per pair (this is probably less than the original cost of one cabinet) carriage £3.50 the pair.



**Vu METER SNIP.**

Approximately 1 5/8" square, suitable for use as a recording level meter power output indicator or many similar applications. Full vision front, cover easily removable if you wish to alter the scale. Special snip price £1.00, or 10 for £9.00.




**MOTORISED DISCO SWITCH**

With 10 amp changeover switches. Multi-adjustable switches all rated at 10 amps, this would provide a magnificent display. For mains operated 8 switch model £6.25, 10 switch model £6.75, 12 switch model £7.25.

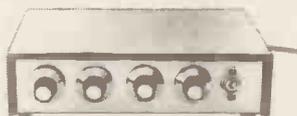**3 CHANNEL SOUND TO LIGHT KIT**

Complete kit of parts for a three-channel sound to light unit controlling over 2000 watts of lighting. Use this at home if you wish but it is plenty rugged enough for disco work. The unit is housed in an attractive two-tone metal case and has controls for each channel, and a master on/off. The audio input and output are by 1/4" sockets and three panel mounting fuse holders provide thyristor protection. A four-pin plug and socket facilitate ease of connecting lamps. Special snip price is £14.95 in kit form or £19.95 assembled and tested.



**FLOURESCENT TUBE INVERTER**

For camping — car repairing — emergency lighting from a 12v battery you can't beat fluorescent lighting. It will offer plenty of well distributed light and is economical. We offer Phillips inverter for 12" 8 watt miniature tube for only £5.25. (With tube and tube holders as well.




**THIS MONTH'S SNIP**

**1/2 PRICE CABLES!** Flat P.V.C. covered mains cables — for lighting and power installations.

SIZE	TYPE	100 Metres	CARRIAGE
1.5mm	Single	£ 3.95	£2.00
1.5mm	Flat twin	£ 6.50	£2.50
1.5mm	Flat three core & E	£ 9.85	£3.00
6mm	Single	£ 7.50	£2.50
4mm	Flat twin	£11.50	£3.50
6mm	Flat three core	£34.50	£4.50
16mm	Twin & E	£65 + £9.75	£10.00

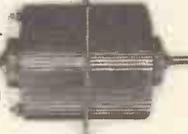**12v MOTOR BY SMITHS**

Made for use in cars, these are series wound and they become more powerful as load increases — they will in fact burn themselves out if overloaded to stopping point. Size 3 1/2" long by 3" dia. These have a good length of 1/4" spindle — price £3.45. Ditto, but double ended £4.25.



**SOLENOID WITH PLUNGER**

Mains operated £1.99  
10 — 12 volts DC operated £1.50.

**MINI-MULTI TESTER** Deluxe pocket size precision moving coil instrument, Jewelled bearings - 2000 o.p.v. mirrored scale. 11 instant range measures: DC volts 10, 50, 250, 1000. AC volts 10, 50, 250, 1000. DC amps 0 — 100 mA.



Continuity and resistance 0 - 1 meg ohms in two ranges. Complete with test prods and instruction book showing how to measure capacity and inductance as well. Unbelievable value at only £6.75 + 50p post and insurance.

**FREE** Amps range kit to enable you to read DC current from 0 - 10 amps, directly on the 0 - 10 scale. It's free if you purchase quickly, but if you already own a Mini-Tester and would like one, send £2.50.

**MULLARD UNILEX**

A mains operated 4 + 4 stereo system. Rated one of the finest performers in the stereo field this would make a wonderful gift for almost anyone. In easy to assemble modular form this should sell at about £30 — but due to a special bulk buy and an incentive for you to buy this month we offer the system complete at only £16.75 including VAT and post. **FREE GIFT** — buy this month and you will receive a pair of Goodman's elliptical 8"x5" speakers to match this amplifier.



**VENNER TIME SWITCH**

Mains operated with 20 amp switch, one on and one off per 24 hrs. repeats daily automatically correcting for the lengthening or shortening day. An expensive time switch but you can have it for only £2.95. These are new but without case, but we can supply plastic cases (base and cover) £1.75 or metal case with window £2.95. Also available is adaptor kit to convert this into a normal 24hr. time switch but with the added advantage of up to 12 on/off per 24hrs. This makes an ideal controller for the immersion heater. Price of adaptor kit is £2.30.

**DELAY SWITCH**

Mains operated — delay can be accurately set with pointers knob for periods of up to 2 1/2 hrs. 2 contacts suitable to switch 10 amps — second contact opens a few minutes after 1st contact. £1.95.



**LEVEL METER**

Size approximately 1/2" square, scaled signal and power but cover easily removable for rescaling. Sensitivity 200 uA. 75p.

**STEREO HEADPHONES**

Japanese made so very good quality. 8 ohm impedance. padded, terminating with standard 1/4" jack-plug. £2.99 Post 60p.



**BRIDGE RECTIFIER**

1 amp 400v 30p each.  
10 for £2.50. 100 for £20.00

**BURGLAR ALARM CONTROL PANEL**

Contains labelled connection block, latching relay, test switch and removable key control switch. Simplifies the whole installation, all you have to do is to take wires to pressure pads and to alarm bell. Price £7.95, with complete diagram.

**PRECISION MAINS OPERATED CLOCK**

For only £1.99. Sounds unbelievable but that's what you can have if you send your order right away. The clocks which have large clear dials were made by the famous Smiths Company for use with domestic cooker/switch, brand new and guaranteed.

**12V SUBMERSIBLE PUMP**

Just join it to your car battery, drop it into the liquid to be moved and up it comes, no messing about, no priming, etc. and you get a very good head. Suitable for water, paraffin and any non-explosive non-corrosive liquid. One use if you are a camper, make yourself a shower. Price: £8.50.

**POPULAR SNIP — STILL AVAILABLE**

And it still carries a free gift of a desoldering pump, which we are currently selling at £6.35p. The snip is perhaps the most useful breakdown parcel we have ever offered. It is a parcel of 50 nearly all different computer panels containing parts which must have cost at least £500. On these boards you will find over 300 IC's. Over 300 diodes, over 200 transistors and several thousand other parts, resistors, condensers, multi-turn pots, rectifiers, SCR, etc. etc. If you act promptly, you can have this parcel for only £8.50, which when you deduct the value of the desoldering pump, works out to just a little over 4p per panel. Surely this is a bargain you should not miss! When ordering please add £2.50 post and £1.27 VAT.



**MAINS MOTORS** Precision made as used in record players, blow heaters, etc.

Speed usually 1,400. All have ample spindle length for coupling fan blade, pulley, etc. Power depends on stack size. 5/8" stack £2.00; 3/4" stack £2.50; 7/8" stack £3.00; 1" stack £3.50; 1 1/2" stack £4.50. Add 25% to motor cost to cover postage, and then add 15% VAT.

**YOUR LAST CHANCE FOR THIS BARGAIN**

100 twist drills, regular tool shop price over £50, yours for only £11.50. With these you will be able to drill metal, wood, plastic, etc. from the tiniest holes in P.C.B. right up to about 1/4". Don't miss this snip — send your order today.

**MINI MONO AMP** on p.c.b., size 4" x 2" approx. Fitted volume control and a hole for a tone control should you require it. The amplifier has three transistors and we estimate the output to be 1 W rms. More technical data will be included with the amplifier. Brand new, perfect condition, offered at the very low price of £1.15 each, or 10 for £10.00.



**J. BULL (Electrical) Ltd.**

(Dept. EM), 34 - 36 AMERICA LANE, HAYWARDS HEATH, SUSSEX RH16 3QU.

J. BULL (Electrical) Ltd — Established 25 years. MAIL ORDER TERMS: Cash with order -- please add 60p to all orders under £10, to offset packing, etc. ACCESS & BARCLAYCARD WELCOMED. Our shop is open to callers. BULK ENQUIRIES INVITED. Telephone: Haywards Heath (0444) 54563.

# INSTRUMENT REVIEW

## THE WERSI PIANOSTAR

The Pianostar will come as quite a surprise to the many people who have built Wersi organ kits over the years. Having established a high reputation in the organ world, it is an ambitious new direction for the company to take and in many respects they have succeeded in producing an upright piano that looks and more importantly feels like the traditional acoustic piano. But what is equally important is its innovative extras that take conventional piano principles and stretch the tonal and control possibilities to make the Pianostar suitable for many modern styles as well as classical music.

All this is a lot to expect from one instrument that has refined its electronics (without the use of micro-processors) to fit a remarkably small space. From the photographs, virtually all the electronics can be seen installed on one main rack. Ribbon cables and prewired connectors have done away with all tedious wiring and, apart from the two main dual speaker systems, foot pedals and main amplifier in the base, the whole piano has little to put together.

Except for the keyboard frame, of course, which forms the heaviest and undoubtedly the most critical item for the advanced pianist. A lot of attention has gone into the correct weighting of each key and its smoothness of action. The keys are pleasing to play, although Wersi are planning to update the existing keyboard with a further improved action developed in Italy for production kits. Keys have a firm feel and at first, seem to bounce back too much and prove difficult to manipulate trills. A good playing technique can produce acceptable classical music. It is easy to move from acoustic grand piano to Pianostar and say, "I told you so - not a bit like a 'real' piano". But so much of your decision probably comes from the evaluation of whether or not it's a typical piano 'sound' and Wersi have certainly tried to get this and more. For the player, other factors are important and keyboard sensitivity, harmonic modulation and dynamics should be as critical as tonal excellence.

Dynamic range is certainly as good, if not better (lacking mechanical noise except on very low output volume setting) than an acoustic instrument. Control of keys at pp levels is adequate, although equal sensitivity from one note to the next relies on careful mechanical contact setting-up. This is much improved on the usual 'velocity sensitive' configuration by the use of two 'rest' and 'operate' bus-bars for the key contact instead of two further contacts that often move out of line after a time, producing erratic note volumes.




Pianostar S2000

### Circuit Design

The Pianostar sounds are derived from a voltage controllable high frequency oscillator operating at about 1MHz. A correction frequency is fed via a top octave synthesiser IC and 16 to 1 line multiplexer. This frequency is differentiated and rectified, with the resulting DC voltage controlling the final HF pitch output. The multiplexer selects one of the 12 TOS frequencies from the BCD 4-bit code of the Transposer, enabling the whole piano to be tuned instantly to any interval. A Pitch control matches tuning over several semitones to other instruments and Vibrato, Hawaii and Slalom all function by sending appropriate control voltages to the HF oscillator.

The HF signal is then passed to a pre-scaler section that divides the basic frequencies for the 12 notes of each octave on Channel 2. It also goes via a programmable fractional divider before another frequency divider produces the notes for Channel 1. This enables Channel 1 to be de-tuned against Channel 2 at calculated intervals up to a perfect 5th. Electronic keying of the fully polyphonic keyboard ensures clean production of all the pitches.

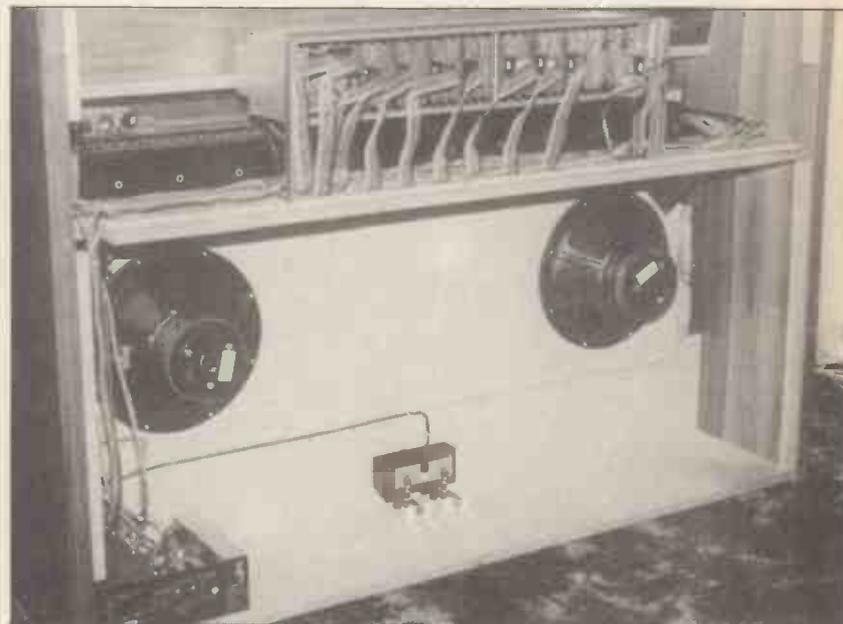Dynamic volume and envelope shaping are set at this stage, with the latter dependent upon Banjo and Sustain switches and the speed of transition of the key contact from the 'rest' bus-bar to the 'operate' bus-bar.




Back removed showing the electronics.

The critical resistor for sustain time is chosen for each key to match the 'decay' of equivalent piano strings. At this point, too, comes the control logic (through CMOS gates) for switches, sustain and pedals.

Both channels then go through their individual filter sections containing two types of circuitry. The first filter accepts the 'raw' signals produced by the keying circuits and


shapes the preset voices. The second filter produces a sine wave from keyed frequencies to make the 'Stage Piano' voice. One active filter is used on octaves 1, 2 and 3 with separate filters on the rest.

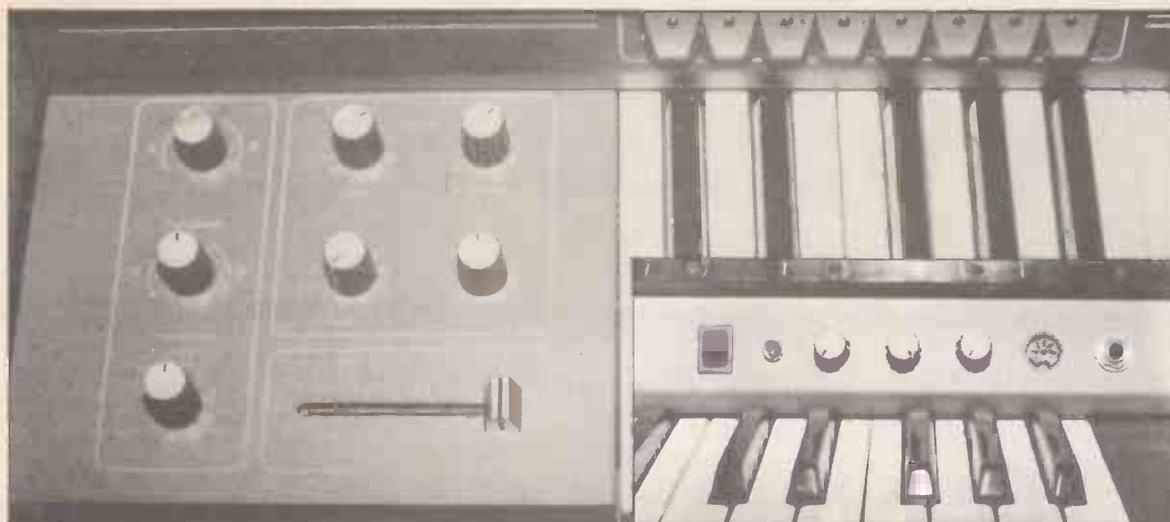The channel outputs are finally treated by separate VCFs before going to pre-amps containing volume and tone controls (also noise gates). The S2000 takes these signals to two



Left hand controls.

Right hand controls.

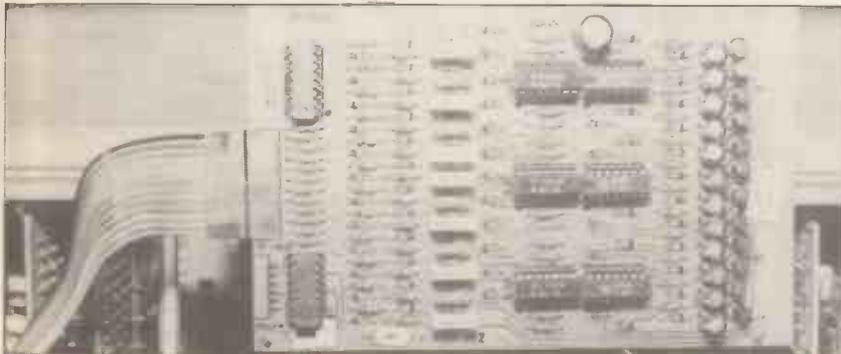

Envelope shape board taken from mounting rack.

hybrid amplifier modules and a relay is used to effect switching to headphones.

## Performance Features

Playing the Pianostar for the first time at Wersi's superb showrooms in Germany, I was immediately impressed by its stereo image received. The wide spacing of the speakers that are powered by 2 x 100 Watt amplifiers gave a surround sound stereo piano that was truly exciting. The maximum power output seemed overrated but did give enough bass to shake the ceiling at home and would be plenty for regular gigging in restaurants and hotels.

Like the best electric pianos, it uses two-oscillator tuning to achieve its harmonic modulation similar to a piano's vibrating strings. But it uniquely provides de-tuning at set degrees from a single control. Besides giving the very slight pitch differences required for de-tuning to produce the superb stereo 'chorus-like' effect, without which the notes sound dull, it also enables automatic tuning for each preset as well as interval separation of the third, fourth and fifth between the left and right channels. The potential of these larger intervals is great with solo monophonic playing, especially jazz, but its use in polyphonic music is restricted to bell-like effects and complex note clusters for the more avant-garde experimentalist.

Coupled with instant pitch transposition for putting a piece into any key - ideal for accompanying trumpets, clarinets and saxophones with music all in the same pitch - the

'Slalom' slider gives polyphonic glide down an octave and 'Hawaii', at the touch of the left foot pedal, gives that well-known semitone glide up to the note. In addition, this pedal can operate Vibrato (slow/fast, heavy or light) while the right pedal gives the expected sustain.

An interesting feature, situated with these controls at the left end of the keyboard, is filter control. A low pass filter can be modulated using its Speed control to give a continuously changing tonal effect set by Resonance, Frequency Cut-off and Amplitude (depth of modulation) controls. At slow speeds this creates deep swirling qualities associated with polyphonic synthesizers and at higher speeds produces tremolo and wah-wah, that can be made to 'bubble' at maximum Resonance and Speed. A button also selects 'Keyboard follow' for the filter, opening it up on progressively higher notes and interesting on a sequence of low to high chords for its sudden tonal changes. A combination of vibrato and filter modulation on piano tones gives some pleasant vibraphone effects.

There are eight presets that produce distinctive percussive tones: the Rock Piano is bright on top but thinner on bass; the Stage Piano is the most mellow and nearest to classical piano except in the lowest registers which tend to be lacking in bright harmonics; the Kinura has boosted high harmonics to give a great punchy and penetrating sound; Banjo is really banjo - even the action of the piano seems different (through envelope keying) - but you'll have to do strumming yourself by rapid reiteration (hard work!); Harpsichord and Cem-

ballo (the latter couples two octaves of Harpsichord) are very authentic; Honky-Tonk puts the de-tuning to maximum use (incidentally, all de-tuning is set appropriately for each preset on normal 'automatic' setting) for all pub piano enthusiasts; and Piano gives a brighter overall sound compared with Stage Piano.

During playing, it's better to stick to one preset for classical music choosing Stage Piano or Harpsichord more frequently than the rest, but for modern music the choice of tones (including mixed combinations of presets) make the instrument very satisfying to play.

Each preset button has an LED indicator built in and a similar set of buttons control Octave coupling as well as Hawaii, Vibrato and VCF.

Finally, the right hand controls provide total Volume setting for the built-in amp/speaker system or stereo headphones, Bass boost and Tape playback level, with on/off switch, 5-pin Din record/playback for stereo tape and headphone jack socket close by. The tape facility is ideal for electronic music recording and also allows you to play along with any accompaniment.

The cabinet is factory made with a well polished wood veneer finish and tasteful speaker cloth. No castors though - you have to slide its quite heavy weight on glide buttons. You'll never open the lid to see inside, for the

whole of the back's thick hardboard panel unscrews instead. The electronics construction has been well thought out, with the main rack section and the keyboard sliding out for easy access. Circuit boards with clear legends take components supplied in labelled packs and the assembly manuals have enough information for all but the most inexperienced constructor.

A portable version, the Pianostar T2000, is also available without amps and speakers. The keyboard range is reduced from seven octaves to six and the cabinet is finished in black rexine and a heavy moulded plastic material. This version measures 26 x 52 x 112 cms and comes with stand and separate pedal unit, whilst the upright model is 102 x 58 x 145 cms.

## Conclusion

Probably the best way to make a final assessment is to try the Pianostar yourself at one of Wersi's showrooms or listen to it being played by their expert German demonstrator, Hady Wolff on E&MM's Demo Cassette No. 3.

My criticisms are few - low notes tend to be a little woolly on Stage Piano, which is generally a very usable rich sound; the lowest octave with non-piano presets like Cembalo (using added low octave) is best avoided and, in any case, would not be part of the range of its original instrument. Slight transformer buzz was completely solved by reseating it in its case and the only playing problem was in avoiding transient clicks from preset buttons by switching them when keys are released (and sustain off).

The upright piano model S2000 kit represents best value at £1,273.00 (inc. VAT) with complete cabinet and built-in amplification. The portable T2000 is £1,225.00 (inc. VAT) with 5 Watt stereo monitor, headphone, and preamp outputs. Ready made prices are £2,102.00 and £2,038.00 respectively.

The instrument gives a lot of pleasure by virtue of its variety of sounds and will be an ideal complement for any lounge, be it a family living room or hotel, and a versatile electronic instrument for professional or home recording studios.

Mike Beecher

E&MM



Pianostar T2000

# Organ Talk

## FRANZ IN CONCERT

Ken Lenton-Smith

The virtuoso performer and Wersi demonstrator Franz Lambert toured the U.K. some weeks ago and I was among a party from E&MM that attended his first concert here - at the Fairfield Halls, Croydon.

Programmes were not available so I surmise that Franz changes his programme according to location and as the mood suits him. After the show at Croydon he was to perform at eight other centres and, as the Franz Lambert Fan Club tends to follow him in his travels, he may well like to leave his choice of programme wide open. Certainly, he gave his Croydon audience a very wide range of music - possibly with the accent on serious music. The audience in the Fairfield Halls appeared to be a mixture of his fans and organ lovers generally, not forgetting representatives of the Press!

The tour had been organised by Aura Sounds of Purley and the concert we attended was - with one minor criticism - a well-staged, interesting and exciting occasion. Sitting ready on stage were the Galaxy and Helios organs with the new Pianostar electric piano between them. On each side of the stage were percussion kits: timpani, gong, bells, bongos, glock and other traps occupied one side, the other having a full rhythmic kit including synth drums.

Rather unusually, the two Wersi organs were back-on to the auditorium but a large, angled mirror behind the instruments allowed the concert-goers a back view of the organist. Additionally, a remote-controlled colour TV camera was directed on the keyboard and its signal shown on eight monitors at the sides of the stage. These viewing aids gave the audience the opportunity to see the rapid changes in registration continuously taking place.

Six 100W speaker cabinets were ranged along the back of the stage and this gave more than ample volume on the louder passages and appeared to be set to accentuate the lower frequencies. It certainly did justice to the Galaxy, though the Helios lacked the same level of reverberation. I appreciate that each hall has its own acoustic characteristic, which alters with an audience in place: this was, of course, the first of a series of concerts and subsequent performances may well have seen alterations to the PA arrangements.

Franz Lambert and his percussionist, Kurt Bong, arrived on stage and the Galaxy was used to open the show with a Fanfare - of Trumpet, Voluntary flavour, with timpani. It was not possible, because of the oblique view afforded by the CCTV, to be precise about the registrations used: in any case, Wersidata was no doubt in constant use (a random access preset system fitted to these organs). Thus I can only give a general indi-



Franz Lambert

cation of the tones the organist used.

An ABBA number in rock tempo followed, mainly using third harmonic percussion, after which the tempo slowed for a 'cascading strings' melody. The Galaxy is a three-manual instrument with just about all the facilities one could wish for and, from the moment the concert began, the organist was demonstrating not only his own prowess but also the capabilities of the organ itself.

After the applause for this session had died down, a German compère addressed the audience - and here I must make a criticism. Broken English through a rather bassy, reverberated amplification system is extremely difficult to follow. He also addressed Franz Lambert in German across the stage and even a smattering of that language was no help at all. Bearing in mind that Franz plays in the USA, I would respectfully suggest that this brilliant organist speaks at least one English phrase - and possibly changes his compère when away from home! I was reminded of the occasion when I first tried out an early Wersi organ and was completely at sea because every control was labelled in German.

Returning to the performance itself, Dvorak's 'Ninth Symphony' began with synthesised strings and the well-known theme became a cor anglais solo (well-known, that is, to lovers of Hovis!). The reprise was in polyphonic brass with string accompaniment. Today's organ having become orchestral rather than solely imitative of its pipe counterpart, instruments like the Galaxy offer great scope to the more seriously-inclined musician.

in re-arranging the classics. This appears to be Franz Lambert's strong point, the Ninth Symphony being executed with exquisite expression.

'Japanese Lantern' was evocative of Geisha Girls and cherry blossom. Phased strings with 5½' tone added set the theme in rubato tempo, changing into heavy swing in organ tone for the final choruses. The location was then changed by Tchaikowsky's 'Capriccio Italien', heralded by a mournful trumpet with strings as backing against a slow bolero rhythm.

To prove to the many organists in the hall just how it should be played, 'Tico Tico' was the next offering. Franz chose to register in straight 'electronic organ tone', no doubt because from the era of Ethel Smith this is how we have always been used to hearing this famous samba. Kurt Bong also capitalised on this number with a very lively solo in the percussion department. I guess that 'Tico Tico' elated the non-players in the audience, but left the practical musicians somewhat downhearted! Despite a raging tempo, the organist's keyboard technique was faultless and breathtaking.

Cat Stevens' 'Morning Has Broken' began with chimes, which appeared to be a percussed flute mixture with odd harmonics, the tune being played by a most realistic oboe. The theme was repeated by the 'string orchestra' in a grand and expressive manner. 'Elizabethan Serenade' was registered in woody flute harmony with white noise for the accompaniment, the melody in synthesised strings.

Moving over to the Helios organ, a selection from the European Hit Parade was played with rock backing by Kurt who had also moved over to his rhythmic kit. This medley allowed liberal use of the synth drums but for the most part Franz kept his registration in organ tone.

'Flight of the Bumble Bee' was another of the organists special arrangements, combining a brilliant demonstration of the man and his instrument. Franz managed to register his organ so that an incisive and insistent bee gyrated round the hall.

A swing medley, mainly based on 'C Jam Blues' was to follow and was much in the style of Jimmy Smith - with percussed third harmonic prominent. This part of the performance modulated into 'Sweet Georgia Brown' with the solo taken on a very windy jazz flute: although there was probably too much white noise added, the effect was interesting nevertheless.

Returning to the Galaxy, Franz and his percussionist prepared to play 'If I Could Be a King', making great play of the fact that they were turning to sheet music - to the amusement of the audience. This arrangement employed brass, horn, string and harp arpeggios: the latter, and indeed many of the solo voices, are a great credit to Wersi's engineers.

'Germtlichkeit' was how the compère introduced Franz Lambert's 'Nutties Selection' (I translate this as giving a feeling of satisfaction or well-being). This part of the programme was a rock and roll romp for both performers - mostly Country & Western numbers that are well-worn but allowed the use of banjo, train whistles and plenty of corn!

Lennon and McCartney compositions, surely among the best to emerge in the last couple of decades of popular music, were used in the penultimate medley. A boisterous version of 'She Loves You' gave way to a plaintive oboe solo of 'Yesterday': that particular sound, which must be synthesiser based, is total realism on the Wersi organ. 'Michelle' was also in haunting vein, the solo being taken by trombone with a string backing. A rollicking version of 'Yellow Submarine' was followed by the breathy flute being used again for 'Hey Jude'. This selection ended as it began with 'She Loves You' - but not before Kurt had taken a drum solo lasting several minutes, lambasting everything within reach including the synth drums!

The final part of the show was another of the organist's special arrangements - 'Sabre Dance' by Khachaturian, expertly played on the Galaxy. This began with a lament played on rolling strings, then turned to Baroque organ style in counterpoint. The theme was prestissimo in organ tone with a fair amount of dissonant harmonics: the full dynamic range of the organ was brought into play and the performance can only be described as scintillating.

The audience would not let the artists leave the stage until two encores had been heard - a fast gallop, followed by a slow number on the electric piano. No doubt Franz finds it advisable to wind his audience down before it emerges into the world of reality again.

This concert was highly enjoyable, combining first class musicianship and instruments. It was also proof of the change in character of the entertainment organ in recent years into an orchestra at the fingertips.


Few organists ever achieve the expertise shown at this concert, but anyone interested in electronic music can build a Wersi organ.

Some readers may not be aware of the existence of a club that consists of organ builders, working both to their own designs and on kits. The Electronic Organ Constructor's Society is a non profit-making organisation which was founded twenty years ago. The Society holds regular meetings in London, Manchester and elsewhere and publishes *The Electronic Organ Magazine* which it circulates to a world-wide membership.


Details of membership may be obtained by sending a stamped, addressed envelope to Ralph Purdy (Membership Secretary), 11 The Avenue, Station Road, Billericay, Essex CM12 9HH.

E&amp;MM

# Create One Yourself!

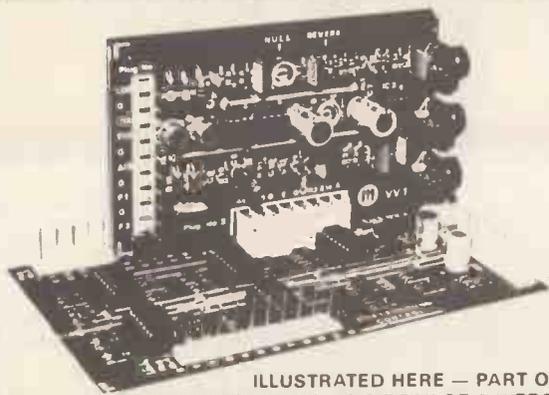

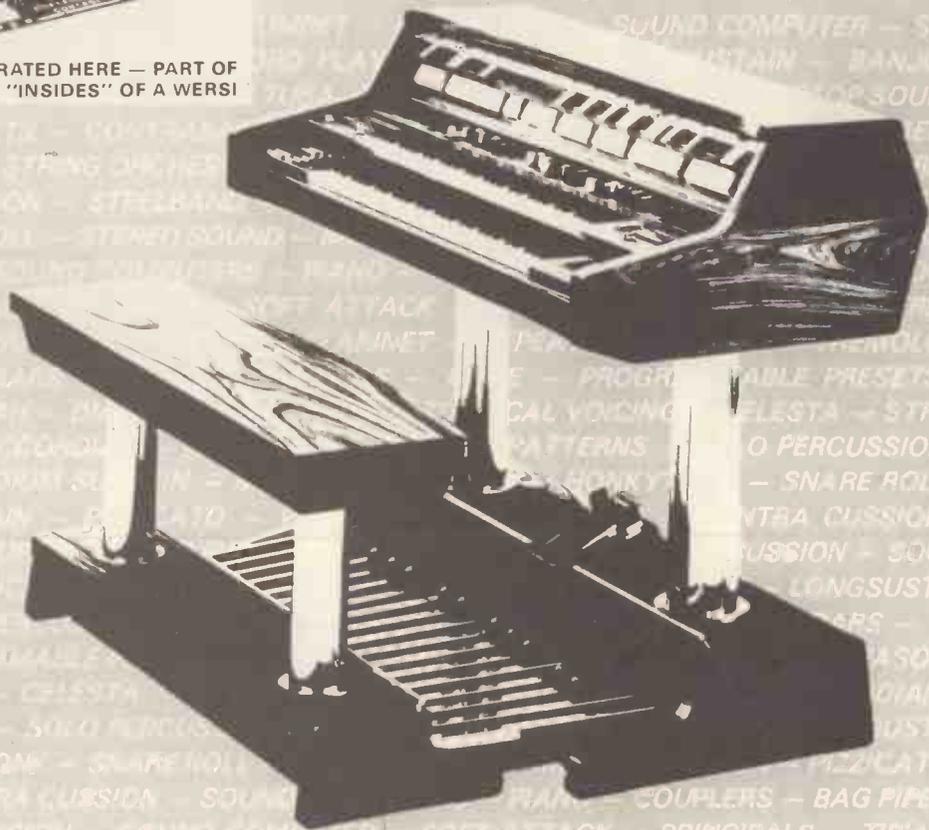ILLUSTRATED HERE — PART OF THE ELECTRONIC "INSIDES" OF A WERSI



## Aura and WERSI Show You How

Create one of Wersi's electronic organs by building it yourself from an easy to build kit. Create a perfect match in decor by picking a spinet or console in contemporary or traditional styling. Create your own personalized instrument by picking just those features that fit your playing style.

Create your own custom electronic organ by having WERSI build it for you. Create the keyboard instrument that exactly fits your needs in styling and features. Create a lifetime investment with WERSI's unique updating system which allows you to ADD new features in the future.

Want to know more about WERSI? AURA SOUNDS are the first company to successfully market WERSI Organs and kits in the U.K. Our technical telephone support service is second to none. There's a friendly welcome and free demonstration at our three showrooms. Fill in the coupon and enclose a cheque/P.O. for £1.00 payable to AURA SOUNDS

LTD. FOR IMMEDIATE ACTION TELEPHONE 01-668 9733 24 HOUR ANSWERING SERVICE, QUOTING ACCESS/BARCLAYCARD NUMBER.

AURA SOUNDS LTD.  
14-15 Royal Oak Centre, Brighton Road, Purley, Surrey.  
Tel: 01-668 9733  
17 Upper Charter Arcade, Barnsley, Yorkshire. Tel: (0226) 5248  
1729 Coventry Road, Sheldon, Birmingham. Tel: 021-707 8244

Please send me the full colour WERSI Catalogue. I enclose cheque/P.O. for £1.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

Send to Aura Sounds Ltd., 14/15 Royal Oak Centre, Brighton Road, Purley, Surrey.

E&MM/7

**WERSI AND AURA SOUNDS — THE WINNING COMBINATION**

## Something Old? Something New?

Sony have taken out a patent on a speaker system. Nothing new in that you may think but there you'd be wrong! This speaker is the first of a new generation of 'digital' speakers.

To understand how it works though, we have to understand how audio signals can be digitally encoded.

Sound consists of a pressure wave that travels in air. If a suitable transducer, a microphone, picks these signals up, its output will consist of an electrical voltage whose amplitude will rise and fall in sympathy with the pressure wave (the sound) that impinges on it. If this signal is examined on an oscilloscope, a complex ever-changing voltage level will be seen. Conventional audio equipment operates with amplified levels of this original voltage.

There is, however, another way in which this signal can be encoded. Before describing this in detail it will be as well to define just what we are trying to encode. Sound levels in a live concert can vary by a ratio of 10,000:1 in amplitude. This is known as the signal's dynamic range.

The frequency range that must be covered extends from 20Hz to 20kHz, a thousand to one ratio. Digital recording works by sampling the waveform at a very high frequency and encoding its instantaneous amplitude.

Now computers cannot count in tens like us, they only know two numbers, 0 and 1. 1 represents a high voltage level and 0 an absence of voltage.

At first sight this seems extremely limiting but in fact a computer can count quite easily with just these two levels. In our conventional number system (decimal) large numbers are represented by thousands, hundreds, tens and units, i.e. powers of ten. The computer equivalent uses powers of two (binary). For example, consider the computer number 1001100. Note that only 0 and 1 appear. The key to translating this back to a decimal number is shown below:


$2^6$	$2^5$	$2^4$	$2^3$	$2^2$	$2^1$	$2^0$
64	32	16	8	4	2	1
1	0	0	1	1	0	0

Note that the number is read from left to right and contains 1-64, no 32's or 16's, one 8, one 4, no twos and no 1's. By adding up what we have we find that the number is  $64+8+4=76$ . Notice that instead of tens, hundreds, etc. (i.e. powers of ten) each column advances by a power of two.

Our music signal has a dynamic range of 10,000:1 and to encode any of the possible levels between these limits we must be able to count up to  $2^{14}$ , 16,384. Now each of our columns contains a bit of information which is either 0 or 1, so



Jeff Macaulay

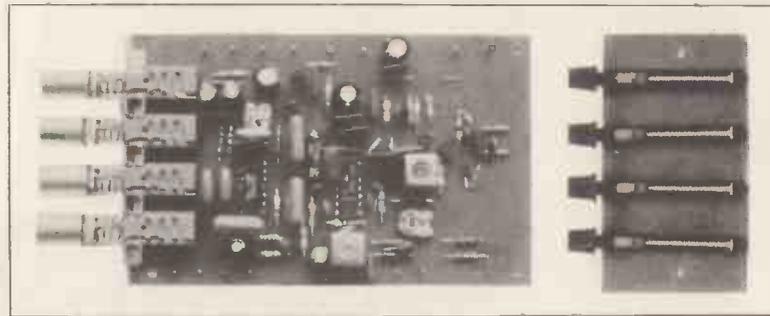

Bi-Pak FM main board and tuning panel.

we can say that each of our samples requires 16,384 bits of information. Having settled this, all that has to be established is the sampling rate.

Luckily this can be readily determined because of the work of a gentleman named Nyquist who showed that the maximum frequency that can be completely recovered when modulated on a carrier is exactly half that of the carrier. So to encode our highest frequency audio signal we need a carrier of 40kHz minimum.

Our digitally encoded signal then consists of a 14-bit binary code that changes 40,000 times per second. The most successful commercial digital recording equipment, the Soundstream, uses a 16-bit code and a sampling rate of 50kHz.

Once in digital form, the program has to be translated back to analogue in order for it to be heard, which raises the natural question 'Why bother in the first place?' The answer is simple. For a start, once the signal has been recorded in digital form, it won't deteriorate in any way. No compression is required since the full dynamic range can be accommodated; and last, but by no means least, the S/N ratio is greatly improved.

Unfortunately the problem of converting the digital code back to analogue form remains. At present this is done with D/A converter chips and the resulting signal is then recorded on a conventional analogue disc. All this brings us back to where we started with Sony's new speaker.

The innovative idea behind this system is to dispense with moving coil speakers and conventional amplifiers and replace them by compressed air drivers. Basically a tank of compressed air is fed via electro-mechanical valves to 'Horns' which vent into the listening room. There are 14 of these horns and the control for the air flow valves is obtained directly from the incoming digital 'word'.

When a logical one is applied to the valve it opens for the duration of the pulse allowing air to enter the horn. If things are arranged so that the air pressure pulse produced at the horn

connected to the most significant digit is  $2^{14}$  times stronger than that at the least significant digit, then the combined pressure valve produced by the horns will be an exact replica of the input before it was digitally converted. In other words, the whole system operates as a powerful digital to analogue converter without the need for a separate amplifier.

A fascinating idea and one which we will all no doubt hear more of in years to come. It is not altogether new though.

At the turn of the century, a mechanical amplifier using compressed air was invented, which worked on similar principles. The 'drive unit' consisted of a slotted, fixed plate with a comb which was free to slide across it. Compressed air was blown through the plate and the comb was mechanically linked to the record stylus. As the stylus moved the comb across the fixed plate, the air pressure varied in sympathy with the groove modulations producing sound. The device was coupled to an acoustic horn to provide amplification.

Commercial versions of this equipment were on sale in 1906 and for reasons that are somewhat obscure, it was named the 'Autexaphone'.

A commentator of the time reported that the sound could be heard for two or three miles in calm weather which must have meant a hefty SPL was being generated.

The analogy to an electronic amplifier can be more readily appreciated if one remembers just how these work. A conventional amplifying device modulates an external power source, a DC supply. This modulation is controlled by the input signal. Thus an amplifier functions as a copying device. In the air driven speaker, the pressurised air is analogous to the DC supply. The input signal is the mechanical movement of the comb and the output is modulated air pressure changes (sound).

### Hi-Fi, Lo-Cost

There are several ways one can acquire a decent hi-fi system. The

most obvious (and expensive) is to trail around hi-fi stores and, after listening to various combinations, part with your well earned cash. Another way, is to assemble the projects featured in this and other magazines. A third, very much underestimated method, is to assemble a stereo system from ready made modules, many of which are excellent in value and performance.

One such module I have recently come into contact with is an interesting example of this approach. Bi-Pak have established an excellent reputation over the years for the reliability and performance of their amplifier modules so it was with great interest that I received the new S453 FM tuner module.

Like it's predecessor, the S450, this module consists of two PCBs, one of which holds the guts of the tuner, and the other the four 100k multiturn presets which control the varicap tuning.


Also in common with the S450, tuning is accomplished by means of four pushbuttons. Although this means that only four FM stations can be selected, this isn't a major drawback. For those who wish to experiment it is not too difficult a problem to add further stations by using a separate switch bank.

One of the great things about this tuner is its small size, the large PCB is only 125 x 80mm. The tuning PCB is 45 x 80mm. Adding the unit to an existing installation is simple since the unit requires a supply voltage between 18-25V and has a current consumption of 45mA. In many cases a suitable supply rail will already be available and the tuner can then be run via a simple network consisting of a dropper resistor and decoupling capacitor.

So much for the mechanics. Now, how does it sound? To find out I built the module together with a simple PSU into a Verocase in which it was a fairly tight fit. After the usual debugging exercise, in my case the elimination of an earth loop, I was most impressed with the performance. While it is not the most sensitive tuner that I have ever tested, adequate stereo reception of all the major stations with good signal to noise ratio was obtained. Stereo separation was extremely good (Bi-Pak quote 30dB). What is more important though is a tuner's ability to produce a good stereo sound stage with the subtle depth of effects intact. This the tuner can do. Technically the unit employs a discrete front end with an IC limit/demodulator stage. Stereo decoding is carried out by the ubiquitous PLL IC. Stereo operation incidentally can be bypassed by fitting an external switch.

In conclusion, a fine product which can be recommended for those who wish to obtain a good tuner and are prepared to do some mechanical work themselves. The price is £19.53 exclusive of VAT and should be available during August from Bi-Pak Limited.

E&MM

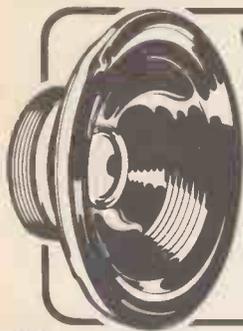

# WILMSLOW AUDIO

The firm for Speakers

EVERYTHING IN STOCK FOR THE SPEAKER CONSTRUCTOR! BAF, LONG FIBRE WOOL, FOAM, CROSSOVERS, FELT PANELS, COMPONENTS, SPEAKER STANDS & BRACKETS ETC., LARGE SELECTION OF GRILLE FABRICS (send 30p in stamps for fabric samples).

## HI-FI DRIVE UNITS



AUDAX HD12.9D25	£8.75
AUDAX HD11P25EBC	£7.50
AUDAX HD20B25H4	£14.95
AUDAX HD13D34H	£12.95
AUDAX HD24S45C	£21.95
AUDAX WFR15S	£23.95
CHARTWELL CEA205 pair	£61.25
COLES 4001	£7.65
COLES 3000	£7.65
COLES 3100	£7.95
COLES CE20000 8"	£14.95
CELESTION HF1300 II	£12.50
CELESTION HF2000	£13.60
DALESFORD D10 tweeter	£8.45
DALESFORD D10 ferrofluid	£8.95
DALESFORD D30/110	£11.95
DALESFORD D50/153	£12.95
DALESFORD D50/200	£12.25
DALESFORD D100/250	£29.95
DALESFORD D300	£35.75
DECCA London Horn	£79.95
ELAC 6NC204 6 1/2"	£7.50
ELAC 8NC298 8"	£8.95
EMI type 350, 13" x 8", 4 ohm	£9.45
EMI 14A/770, 14" x 9", 8 ohm	£19.50
ISOPHON KK8/8	£8.15
ISOPHON KK10/8	£8.45
JORDAN WATTS Module	£25.95
JORDAN WATTS Module Mk III	£28.50
JORDAN WATTS HF kit	£10.50
JORDAN 50mm unit	£31.50
JORDAN crossover pair	£31.90
KEF T27	£9.45
KEF B110	£12.25
KEF B200	£13.50
KEF B139	£27.75
KEF DN12	£9.40
KEF DN13	£6.75
LOWTHER PM6	£63.00
LOWTHER PM6 Mk I	£67.75
LOWTHER PM7	£99.00
PEERLESS K010DT	£10.95
PEERLESS DT10HFC	£10.50
PEERLESS K040MRF	£13.60
RICHARD ALLAN CG8T	£13.50
RICHARD ALLAN CG12T Super	£29.50
RICHARD ALLAN HP8B	£20.75
RICHARD ALLAN LP8B	£14.50
RICHARD ALLAN HP12B	£33.50
RICHARD ALLAN DT20	£9.95
RICHARD ALLAN DT30	£10.75
SEAS H107	£9.95
SEAS H211 ferrofluid	£10.95
SHACKMAN ES units pair	£136.00
SHACKMAN ES units with cabs. pair	£170

## PA GROUP & DISCO UNITS



CELESTION G12/50TC	£19.50
CELESTION G12/80CE	£24.50
CELESTION G12/80TC	£23.75
CELESTION G12/125CE	£42.00
CELESTION G15/100CE	£37.95
CELESTION G15/100TC	£38.50
CELESTION G18/200	£64.75
CELESTION POWERCEL 12/150	£66.00
CELESTION POWERCEL 15/250	£88.00
FANE CLASSIC 45 12"	£13.95
FANE CLASSIC 55 12"	£15.50
FANE CLASSIC 80 12"	£19.75
FANE CLASSIC 85 15"	£26.00
FANE CLASSIC 150 15"	£37.95
FANE CLASSIC 125 18"	£43.95
FANE CLASSIC 175 18"	£47.95
FANE GUITAR 80L 12"	£26.25
FANE GUITAR 80B/2 12"	£27.25
FANE DISCO 100 12"	£28.75
FANE PA85 12"	£26.75
FANE BASS 100 15"	£39.00
FANE CRESCENDO 12E 12"	£57.50
FANE CRESCENDO 15E 15"	£74.50
FANE CRESCENDO 18E 18"	£94.75
FANE COLOSSUS 15E 15"	£99.95
FANE COLOSSUS 18E 18"	£107.00
FANE J44	£6.90
FANE J73	£10.90
FANE J104	£15.95
FANE J105	£23.95
GAUSS 3181A 10" 150 watts	£115.00
GAUSS 4281 12" 300 watts	£146.00
GAUSS 4581 15" 300 watts	£162.00
GAUSS 4583A 15" 400 watts	£162.00
GAUSS 4882 18" 400 watts	£220.00
GOODMANS 8PA	£5.05
GOODMANS PP12	£22.50
GOODMANS DI12	£25.50
GOODMANS GR12	£24.95
GOODMANS 18P	£48.45
GOODMANS HIFAX 50HX	£21.85
GOODMANS HIFAX 100HX	£24.50
McKENZIE C12100GP	£24.45
McKENZIE C12100TC	£24.45
McKENZIE C12100 BASS	£24.45
McKENZIE C12125GP	£39.95
McKENZIE C12125TC	£39.95
McKENZIE GP15	£35.10
McKENZIE TC15	£35.10
McKENZIE C15 BASS	£59.60
MOTOROLA PIEZO HORN 3 1/2"	£8.50
MOTOROLA PIEZO HORN 2" x 6"	£12.25
RICHARD ALLAN HD8T	£20.25
RICHARD ALLAN HD10T	£21.75
RICHARD ALLAN HD12T	£29.75
RICHARD ALLAN HD15	£52.75
RICHARD ALLAN HD15P	£52.75
RICHARD ALLAN ATLAS 15"	£77.00
RICHARD ALLAN ATLAS 18"	£96.00

## WILMSLOW AUDIO


KITS FOR MAGAZINE DESIGNS etc.

Kits include drive units, crossovers, BAF/long fibre wool etc. for a pair of speakers

Carriage £3.95 unless otherwise stated

Practical Hi-Fi & Audio PRO9-TL including felt panels and level controls	£152.75 carriage £5.00
Hi-Fi Answers Monitor	£146.00
Hi-Fi News State of the Art	£189.00
Hi-Fi News Midline	£99.75
Hi-Fi News Miniline	£49.00
Hi-Fi News Tabor with J4 bass units	£66.00
Hi-Fi News Tabor with H4 bass units	£70.00
Hi-Fi for Pleasure Compact Monitor	£116.00
Hi-Fi for Pleasure E.C.M. including felt panels, foam etc.	£77.50 carriage £5.00
Popular Hi-Fi Jordan System 1	£125.00
Popular Hi-Fi Mini Monitor	£77.00
Popular Hi-Fi Round Sound including complete cabinet kit	£74.00
Practical Hi-Fi & Audio BSC3	£65.00
Practical Hi-Fi & Audio Monitor	£180.00
Practical Hi-Fi & Audio Triangle	£120.00
Practical Hi-Fi & Audio DBS4	£85.00 carriage £5.00
Everyday Electronics EE20	£29.50
Everyday Electronics EE70	£150.00 carriage £5.00
Wireless World T.L. KEF	£125.00
Wireless World T.L. RADFORD	£190.00

## SPEAKER KITS

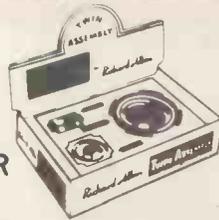

SPEAKER KITS Prices Per Pair Carriage £3.95 unless otherwise stated

COLES NIMBUS KIT mounted on baffle	£69.00
DALESFORD SYSTEM 1	£54.00
DALESFORD SYSTEM 2	£57.00
DALESFORD SYSTEM 3	£104.00
DALESFORD SYSTEM 4	£110.00
DALESFORD SYSTEM 5	£142.00
DALESFORD SYSTEM 6	£95.00
DALESFORD 'D' KIT including cabinet	£79.95
KEF Reference 104aB kit	£133.00 plus £5 carriage
KEF Cantata kit	£199.00 plus £5 carriage
LS3 Micro Monitor kit	£84.00
LOWTHER PM6 kit	£132.75
LOWTHER PM6 MK I kit	£139.95
LOWTHER PM7 kit	£199.00
RADFORD Studio 90	£181.00
RADFORD Monitor 180	£243.00
RADFORD Studio 270	£309.00
RADFORD Studio 360	£450.00
RICHARD ALLAN Tango Twin	£55.50
RICHARD ALLAN Maramba	£77.50
RICHARD ALLAN Charisma	£111.00
RICHARD ALLAN Super Triple	£102.50
RICHARD ALLAN Super Saraband II	£159.95
RICHARD ALLAN RA8 kit	£62.75
RICHARD ALLAN RA82 kit	£98.75
RICHARD ALLAN RA82L kit	£108.00
SEAS 223	£42.50
SEAS 253	£67.00
SEAS 403	£79.95
SEAS 603	£134.95
WHARFEDALE DENTON XP2 kit	£31.45
WHARFEDALE SHELTON XP2 kit	£40.40
WHARFEDALE LINTON XP2 kit	£56.20
WHARFEDALE L60 kit	£52.50
WHARFEDALE L80 kit	£72.00
WHARFEDALE L100 kit	£87.00
WHARFEDALE E50 kit	£129.00
WHARFEDALE E70 kit	£160.00
WHARFEDALE E90 kit	£249.50

WILMSLOW AUDIO BA1 sub bass amplifier/crossover kit £37.95 plus £1 carriage

Building speakers is easy with the new WILMSLOW AUDIO FLAT PACK CABINET KITS!

## CARRIAGE & INSURANCE

Tweeters/Crossovers	70p each
Speakers:	
4" to 6 1/2"	90p each
8" to 10"	£1.10 each
12", 13" x 8", 14" x 9"	£2.00 each
15"	£3.00 each
18"	£5.00 each
Speaker Kits	£3.95 pair
Mag. Design Kits	£3.95 pair

unless otherwise stated

ALL PRICES INCLUDE VAT AT 15% AND ARE CORRECT AT 1/6/81

**SWIFT**  
OF WILMSLOW  
The firm for Hi-Fi  
5 Swan Street,  
Wilmslow, Cheshire.

SEND 50P FOR 56-PAGE CATALOGUE 'CHOOSING A SPEAKER' (or price list only free of charge) Export catalogue £1 or \$3 U.S.

Tel: 0625-529599 for speaker drive units, kits, PA equipment, mail order enquiries, and all export enquiries.  
Tel: 0625-526213 for Hi-Fi equipment and complete speaker enquiries.

Lightning service on telephoned credit card orders!

**WILMSLOW**  
AUDIO  
The firm for Speakers

35/39 Church Street,  
Wilmslow, Cheshire.

# Advanced Music Synthesis

Dave Bristow

Whilst it is essential to understand the mechanics and logic of the instrument you play, the end product, making music, should be the prime consideration. There is only one way of monitoring progress to this goal, and that is by ear - so for the short time it takes to read this article, unplug the mental oscilloscopes and warm up the ears and fingers!

There is more to synthesis than good programming; the sound has to be delivered and it is this area which is often neglected by both players and manufacturers. It is easy to become infatuated with the novelty and wide variety of sounds available from synthesisers without developing their musical potential and it seems to me that manufacturers are taking too long to design and produce good keyboard-actions for otherwise good synthesisers, by which this potential can be realised.

During the course of my consultancy and demonstration work for Yamaha, I find myself at many European Trade Fairs where all makes of synths. are on show and technology rules supreme! TV displays, computer interfaces and illuminated panel indicators are surrounded by rows of faders and buttons, yet, midst all this sophistication, there will probably be a 4 (or maybe 5) octave keyboard, F to F, badly sprung, the action of which is similar to any department store chord organ!

Design began to improve with the Yamaha CS80, and the GS1 action is even better but these are the exception rather than the rule. However, despite the manufacturers' slowness to meet our needs in this area, there are still techniques which keyboard players need to develop in order to utilise fully synthesisers currently on the market, and to enable them to deliver carefully programmed sounds with maximum effect. These are: control of the various means of expression and the use of differently tuned oscillators requiring some harmonic investigation. These skills are as much part and parcel of the modern synthesists' technique, as programming and should not be overlooked, so I should like to consider them in more detail.

## Playing Technique

Most monophonic or duophonic synthesisers seem to function in such a way that any-release time set on the envelope generator controlling the VCA or VCF has to be allowed to complete before the successive note will operate according to the programmed attack time. As most of

## So it's a good programme?



Dave Bristow and Gary Luenberger at the Yamaha test studio, Japan.

many workable solo synthesiser sounds in the woodwind, reed, brass and string area require a very small release time (this is just as important to the musical nature of the sound as the gentle attack time), a playing technique needs to be developed in which each key is released before the next is depressed, even in legato playing. This way, each note will have the full benefit of the envelope programming and the front of the notes will not 'clip'. Pianists do not normally play legato in this manner and it takes some practice to develop this technique, but the rewards in the form of more authentic imitative and musical sounds are well worth the effort. Even grace notes should be played in this way - set up a brass sound on a monophonic synth. and compare normal legato playing with "every note released" legato. The difference will be very noticeable, the careful playing giving more credibility to the programme. Tapping the fingers on a table, ensuring that each one is lifted before the next one taps, will help develop this 'push and release' finger-style approach to the synthesiser keyboard and significantly broaden its musical potential.

Some polyphonic synthesisers (the ones I use are the CS80 and the new GS1) have independent pressure sensors on each key to control volume, timbre, LFO modulation etc. In order to maximise the potential of this refinement, it is necessary to develop a controlled "after pressure" in all fingers of both hands, which for most keyboard players is a novel requirement. The skill is very easily developed by resting the fingers and thumb on a firm surface (as if on the keys of a piano) and pressing each one down firmly in turn, without ever lifting them from the surface. Although this facility is only available on a few synths, the effect is very good, allowing inside or top single lines to be brought out in a

chordal movement.

Generally, introducing LFO modulation or VCO, VCF and VCO control is done via mod-wheels, pitch wheels, levers and ribbons, and foot-pedals. Competent use of these controls requires practice and thought. The 'click' of self-centring pitch wheels is not always too apparent and the fingers need to be sensitive to the position of the wheels. It is important to know the pitch span (i.e. 1 tone, 3rd interval, octave) of any pitch device, and whether it has a linear or logarithmic effect in order that musical bends can be consistent and thus make a pitch bend of a given interval instantly. The use of LFO modulation is also very important. For instance, the introduction of LFO modulation on a flute sound should have more effect on the timbre (VCF) and amplitude (VCA) than on the pitch (VCO), whereas, with a violin sound, modulation should mainly effect the pitch (VCO). Choosing the correct speed, depth and area of influence (VCO, VCF or VCA) enables LFO modulation to be carefully incorporated into programmes or introduced during playing via wheels, levers, or pedals, or pressure on the keys and will bring an instrumental performance to life, broadening its musical value.

Another area that should be explored, and is unique to synthesists, is the possibility of obtaining 2 or more notes from one key, where more than one VCO per note is provided with the instrument. This effect is of course more interesting where duophonic or polyphonic instruments are concerned and it can be rewarding to investigate the harmonic possibilities through combining specific pitches. The best interval to begin with is the fifth, this being the first different harmonic in the series. For instance, playing a major third interval with the two oscillators for each note tuned apart, will sound a major 7th chord - a minor 3rd interval will be a minor 7th.

The only note which brings in an out-of-scale 5th is B. Two note combinations of any other notes will sound interesting and give useful harmonies directly related to the root key. Playing more than two notes requires more investigation of course, but if your instrument has this facility then it should not be ignored. The relative volumes of the two oscillators is also an important factor - if one is significantly lower than the other, then there is an effect of "ghost" harmonies, not unlike the effect of harmonics on a Hammond seeming to change the mood of any given chord. This is another musical area waiting to be explored, but don't expect the instrument to produce it alone - choose the right notes, and be aware of the extra combination of notes you are producing by detuning the oscillators.

I hope that the tone of this article expresses my belief that the synthesist is more important than the synthesiser and that the correct interpretation of a sound and good playing of the keyboard is every bit as important as the logical construction of the programme. Generally, programming is considered to be part of the synthesist's job as a musician but this need not necessarily be so. Over the last eighteen months, I have been involved with the development and presentation of Yamaha's latest polyphonic synthesiser, the GS1, and in the case of this instrument, programming and playing have become completely separated. The instrument has presets (although these can be interchanged from a voice-card library system), all the programming being done at the factory. In order to present the instrument with my band at the Frankfurt Trade Fair last February, I spent some days programming suitable voices at the factory, but after this, during the shows, no alteration to the voices was possible. The result was an enforced freedom from knob twiddling and button pushing that I found totally relaxing, and this coupled with an 88-note keyboard and an action like a grand piano, enabled me to concentrate 100% on the delivery of the music - and that's what it is all about.

Programming the GS1 was, I must admit, quite an experience but one I would rather relate on another occasion, leaving you to think about your skills as a synthesiser player and performer rather than a synthesiser programmer. And I would like to ask the manufacturers generally this question: Do your synthesisers as musical instruments, have the qualities that these skills will ultimately demand?

E&M

# ELECTRONICS MUSIC & EFFECTS KITS

## AUTOWAH UNIT

Automatically gives wah or swell sounds with each guitar note played.

Kit order code = M-SET-58 £16.04

## GUITAR EFFECTS UNIT

Modulates the attack, decay and filter characteristics of a signal from most audio sources producing 8 different switchable sounds that can be further modified by manual controls.

Kit order code = M-SET-42 £14.11

## GUITAR FREQUENCY DOUBLER

Produces an output one octave higher than the input. Inputs and outputs may be mixed to give greater depth.

Kit order code = M-SET-98 £10.55

## GUITAR MULTIPROCESSOR

An extremely versatile sound processing unit capable of producing, for example, flanging, vibrato, reverb, fuzz and tremolo as well as other fascinating sounds. May be used with most electronic instruments. Some SW's not incl. in kit - see list for selection.

Kit order code = M-SET-85 £72.90

## GUITAR OVERDRIVE

Sophisticated versatile fuzz unit incl. variable controls affecting the fuzz quality whilst retaining the attack and decay, and also providing filtering.

Kit order code = M-SET-56 £19.60

## GUITAR PRACTISE AMPLIFIER

A 8 watt mains powered amplifier suitable for instrument practise or as a test gear monitor. Drives 8 or 15 ohm speakers (not incl. in kit).

Kit order code = M-SET-106 £18.72

## GUITAR SUSTAIN

Maintains the natural attack whilst extending note duration.

Kit order code = M-SET-75 £11.77

## PHASER

An automatically controlled 6 stage phasing unit with internal oscillator. Depth can be increased with extension.

Main kit code = M-SET-88 £18.34  
Extension kit = M-ADN-88 £7.31

## PHASING & VIBRATO

Includes manual and automatic control over the rate of phasing and vibrato. Capable of superb full sounds. A separate power supply is included.

Kit order code = M-SET-70 £42.85

## SMOOTH FUZZ

As the name implies!

Order code = M-SET-91 £11.68

## SPLIT-PHASE TREMOLO

The output of the internal generator is phase-split and modulated by an input signal. Output amplitudes, depth and rate are panel controlled. The effect is similar to a rotary cabinet.

Kit order code = M-SET-102 £27.55

## SWITCHED TONE TREBLE BOOST

Provides switched selection of 4 preset tonal responses.

Kit order code = M-SET-89 £10.51

## AUDIO EFFECTS UNIT

A variable siren generator that can produce British and American police sirens, Star Trek Red Alert, heart beat monitor sounds, etc.

Kit order code = M-SET-105 £12.91

## FUNNY TALKER

Incorporates a ring modulator, chopper and frequency modulator to produce fascinating sounds when used with speech and music.

Kit order code = M-SET-99 £15.43

## WIND & RAIN EFFECTS

As the name says!

Order code = M-SET-28 £9.94

## DISCOSTROBE

A 4-channel 200-watt light controller giving a choice of sequential, random or full strobe mode of operation.

Kit order code = M-SET-57 £36.52

## LIST

Send stamped addressed envelope with all U.K. requests for free list giving fuller details of PCBs, kits and other components. Overseas enquiries for list - Europe send 50p, other countries send £1.00

## All kits include custom designed printed circuit boards

### KIMBER-ALLEN KEYBOARDS

Claimed by the manufacturers to be the finest moulded plastic keyboards available. All octaves are c-c, the keys are plastic, slope fronted, spring loaded, fitted with actuators and mounted on a robust aluminium frame. 3-octave £25.50, 4-oct £32.25, 5-oct £39.50. Gold-clad contacts (1 needed for each note) type GJ (SPCO) 33p each. Type GB (2-PR N/O) 38p each.

### CHOROSYNTH

A standard keyboard version of the published Elektor 30-note chorus synthesiser with an amazing variety of sounds ranging from violin to cello and flute to clarinet amongst many others.

Kit plus keyboard & contacts = M-SET-100 £114.12

### FORMANT SYNTHESIZER

For the more advanced constructor who puts performance first. This is a very sophisticated 3-octave synthesiser with a wealth of facilities including 6 oscillators, 3 waveform converters, voltage controlled filter, 2 envelope shapers and voltage controlled amplifier. Case and hardware not included - see our lists for further details.

Kit plus keyboard & contacts = M-SET-66 £323.35

### P.E. MINISONIC SYNTHESIZER

A very versatile 3-octave portable mains operated synthesiser with 2 oscillators, voltage controlled filter, 2 envelope shapers, ring modulator, noise generator, mixer, power supply and sub-min toggle switches to select the functions. A case is excluded, but the text gives comprehensive constructional details.

Kit plus keyboard & contacts = M-SET-38 £169.69

## Prices include 15% VAT & U.K. P&P New kit make-up See below

### 128-NOTE SEQUENCER

Enables a voltage controlled synthesiser, such as the P.E. Minisonic, to automatically play pre-programmed tunes of up to 32 pitches and 128 notes long. Programs are initiated from the 4-octave keyboard and note length and rhythmic pattern are externally variable.

Kit plus keyboard & contacts = M-SET-76 £114.09

### 16-NOTE SEQUENCER

Sequences of up to 16 notes long may be pre-programmed by the panel controls and fed into most voltage-controlled synthesisers. The notes and rhythms may be changed whilst playing making it more versatile than the name would suggest.

Kit order code = M-SET-86 £60.13

### DIGITAL REVERB UNIT

A very advanced unit using sophisticated I.Q. techniques instead of noise-prone mechanical spring lines. The basic delay range of 24 to 90ms can be extended up to 450ms using the extension unit. Further delays can be obtained using more extensions.

Main kit order code = M-SET-78 £67.22  
Extension kit = M-ADN-78 £45.94

### RING MODULATOR

Compatible with the formant and most other synthesisers.

Kit order code = M-SET-87 £11.69

### WAVEFORM CONVERTER

Converts saw-tooth waveform into sinewave, mark-space sawtooth, regular triangle, or squarewave with variable mark-space. Ideally one should be used with each synthesiser oscillator.

Kit order code = M-SET-67 £20.13

*Kits originate from projects published in PE, EE and Elektor.*



Terms: C.W.O., MAIL ORDER OR COLLECTION BY APPOINTMENT

TEL.: 01-302 6184  
(MONDAY-FRIDAY)

## BASIC COMPONENT SETS

Include specially designed drilled & tinned fibreglass printed circuit boards, all necessary resistors, capacitors, semiconductors, potentiometers and transformers. They also include basic hardware such as knobs, sockets, switches, a nominal amount of wire and solder, a photocopy of the original published text, and unless otherwise stated, a robust aluminium box. Most parts may be bought separately. For fuller kit and component details see our current lists.

## RHYTHM GENERATORS

Two different kits - the control units are designed around the M252 and M253 rhythm-gen chips which produce pre-programmed switch-selectable rhythms driving 10 effects instrument generators feeding into a mixer.

12-rhythm unit = M-SET-103-258 £64.10  
15-rhythm unit = M-SET-103-252 £57.26

## 6-CHANNEL MIXER

A high specification stereo mixer with variable input impedances. Specs given in our lists. The kit excludes some SW's - see lists for selection. The extension gives two extra channels.

Main kit code = M-SET-90 £88.99  
Extension kit = M-ADN-90 £11.74

## 3-CHANNEL STEREO MIXER

Full level control on left and right of each channel, and with master output control and headphone monitor.

Kit order code = M-SET-107 £18.68

## 3-MICROPHONE STEREO MIXER

Enables stereo live recordings to be made without the hole in the middle effect. Independent control of each microphone.

Kit order code = M-SET-108 £12.31

## HEADPHONE AMPLIFIER

For use with magnetic, ceramic or crystal pick-ups, tapedeck or tuner, and for most headphones. Designed with RIAA equalisation.

Kit order code = M-SET-104 £18.10

## VOICE OPERATED FADER

For automatically reducing music volume during disco talk-over.

Kit order code = M-SET-30 £7.80

## DYNAMIC NOISE LIMITER

Very effective stereo circuit for reducing noise found in most tape recordings.

Kit order code = M-SET-97 £12.67

## DYNAMIC RANGE LIMITER

Automatically controls sound output levels.

Kit order code = M-SET-62 £9.51

## TUNING FORK

Produces 84 switch-selectable frequency-accurate tones with LED monitor displaying beat-note adjustments.

Kit order code = M-SET-46 £34.56

## TUNING INDICATOR

A simple octave frequency comparator for use with synthesisers where the full versatility of Kit 46 is not needed.

Kit order code = M-SET-69 £14.41

## PULSE GENERATOR

Produces controllable pulse widths from 100NS to 2 sec. variable frequency range of 0.1HZ to 100HZ.

Kit order code = M-SET-115 £21.45

## SIGNAL TRACER & GENERATOR

Allows audio signals to be injected into circuits under test, and for tracing their continuity. Includes frequency & level controls.

Kit order code = M-SET-109 £15.31

## WAVEFORM GENERATOR

Provides sine, square and triangular wave outputs variable between 1HZ & 100KHZ up to 10V P-P.

Kit order code = M-SET-112 £21.58

## SPEECH PROCESSOR

Improves the intelligibility of noisy or fluctuating speech signals, and ideal for inserting into P.A. or C.B. radio systems.

Kit order code = M-SET-110 £9.21

## FREQUENCY COUNTER

A 4-digit counter for 1HZ to 99HZ with 1HZ sampling rate.

Kit order code = M-SET-79 £43.30

## EXPOSURE TIMER

Controls up to 750 watts in 0.5 sec. steps up to 10 minutes, with built-in audio alarm.

Kit order code = M-SET-98 £36.44

More kits and Components are in our Lists

PHONOSONICS : Dept E&MM7 : 22 HIGH ST. : SIDCUP : KENT : DA14 6EH  
More kits and components are in our lists. Prices correct at time of press. E&OE subject to availability

# America

Ian Waugh

As promised last month, a few more goodies for the guitarist plus more info about the ultimate drummer... I didn't realise Jane Fonda played drums...

Guitarists first. MXR have an Effects Loop Selector made from die-cast aluminium which allows the guitarist to choose between two effects systems while running into a single amplifier. The unit requires no separate power unit and a circuit is included to minimise 'pop'. It can also be used to choose between speaker or amp arrangements and retails at \$25.

A similar unit is available from Roger Eddy at \$24.95. You pay your money...

The Think Tank has been working overtime at Whirlwind Music and come up with the 'ultimate' guitar lead. Called the Constrictor — known in the trade as the 'augmented cord' — it consists of 20 inches of coiled lead attached to 10 feet of straight lead. The 20 inches extends up to 10 feet, too, giving a total lead 20 feet long which should not get snarled around your feet. Made from cured neoprene cable by Belden, the Constrictor is designed to pass signals with the minimum of cable noise.

New from Stars Guitars is their Star Grinder which is a distortion unit designed for retrofit in electric guitars. A pot allows a mix between straight and distorted guitar and an optional bypass switch is available. A single 9-volt battery is required and the unit should fit most control cavities.

The HF-4 Hot Foot Active Gain Pedal from Polyfusion runs from a 9-volt battery which is activated by plugging in a cord. The volume output level is adjustable from unity (input and output signal) to 12dB (four times original power). It has a high impedance input and low impedance output. The tension on the pedal's movement is adjustable. The HF-4 sells for \$99.95 from BKL.

Fast-Fret from Kenyon is an applicator stick designed to clean and lubricate guitar strings. It is applied by rubbing the applicator along the strings. Excess can be wiped off with the cloth supplied; the solution does not harm guitar finishes and it is non-toxic.



Linn LM-1 Drum Computer.

There are literally dozens of 'small' amps on the market designed either for use in small rooms or as practice amps. Most of them will give good quality output at low levels. The latter are much more common and the Zeus model 8401 (has everyone got a computer working on new product names?) is one of many worth considering. It provides 1 watt of clean power and 2.5 watts of overdriven signal from its internal speaker. Tone and volume controls are included and the preamp can add up to 21dB of boost to the guitar's signal. The entire unit is only 7½" x 3" x 1¾", is housed in an aluminium case and is powered by 8 small batteries (an AC adapter can be used). It costs \$64.95.

For those who think nostalgia ain't what it used to be, Echoplex have re-introduced their tape echo with tubes. Their EP-6T uses the same basic circuitry as the original EP-2 but has a PCB. After many years of solid-state construction the new unit is deemed to fulfil a long-felt demand. It is available to special order (6-8 weeks) from Market Electronics.

The Peavey EQ-27 has, would you believe, 27 frequency bands each spanning ¼ octave. All 27 slide controls have centre dents and provide for +15dB boost and cut. All inputs and outputs have transient, over-voltage, and short-circuit protection. The voltage regulator protects against power variations. The unit has a bypass switch and is rack-mountable.

...Talking about drummers...

The PAiA Programmable Drum Set now has improved memory circuitry which allows the 'save' mode to hold rhythm patterns for over a year while battery life for normal operation has been extended to several hundred hours.

Right! This is it! Introducing the LM-1 from Linn Electronics. This sophisticated, yet easy to operate machine, contains actual drum sounds recorded digitally in its computer memory. It holds up to 100 drumbeats and these are programmable in real time. Drums include snare, bass, hi-hat, cabasa, tambourine, two congas, two tom-toms, cowbell, clave and hand claps. Programming features include automatic error correction, programmable dynamics, flams, rolls, build-ups, open and closed hi-hat, etc. Special timing circuitry is included to give a 'human' feel to the drumming and all time signatures are possible (including the one our drummer plays after a bottle of rye and a Pepsi). The LM-1 has versatile editing facilities and rhythm patterns can be linked together into complete song formats. All programmed parts can be retained in the memory when power is switched off and programmed data can be stored on cassette. Other features include a 13 output stereo mixer with volume, pan and separate outputs for each drum. The pitch of each drum can be individually adjusted and the unit can be used to overdub on tape and sync to almost anything. The bad news is the price —

\$5,500. Not too expensive, really, when you consider the flexibility of the unit but possibly other manufacturers will see a market here and introduce their own models. It doesn't look quite as pretty as Jane Fonda but then if looks were important our drummer would be peeling potatoes. This is certainly a unit to look at, especially for electronic music composers and enthusiasts. Warren Cann of Ultravox is reviewing this for us.

Next month we'll give guitarists' pockets a rest and see what else is going on in America.

Companies and manufacturers mentioned:

MXR Innovations, 740 Driving Park Ave., Rochester, NY 14613, also Atlantex Music Ltd, 34 Bancroft, Hitchin, Herts SG5 1LA; Roger Eddy, 1330 Miles Ave., Pacific Grove, CA 93950; Whirlwind Music Inc., P.O. Box 1075, Rochester, NY 14603; Stars Guitars, 818 Folsom St., San Francisco, CA 94107; BKL International Distributing, Box 248, Neptune, NJ 07753; Kenyon International, Box 10185, El Paso, TX 79992; Zeus Audio, 511 S. Palm Ave., Alhambra, CA 91803; Market Electronics, 38367 B Apollo Parkway, Willoughby, OH 44094; Peavey Electronics, 711 A St., Meridian, MS 39301; PAiA Electronics, 1020 W. Wilshire Blvd., Oklahoma City, OK 73116; Linn Electronics Inc., 3249 Tareco Drive, Hollywood, CA 90068. E&MM

# Everything You need from Start to Finish


To our Customers . . .

We have pleasure in presenting our new 1981 Catalogue. This contains many new stock lines and additional technical information.


In addition to standard stock lines we also specialise in obtaining non-list items. Please phone us at the Sales Desk or call at our Trade/Retail Counter if you have any queries concerning prices, non-list items or technical information.

Page	Items	65p including p&p
1.	74 Series TTL.	
2.	74LS Series Low Power TTL.	
3.	74C Series CMOS.	
4.	4000 Series CMOS.	
5.	Linear Devices.	
6.	Memories, EPROMS (MM2114N), (MM4116N), (MM2708Q), (MM2716Q)	
7.	Opto Devices —LED's, 7 Segment Displays, LDR's.	
8.	Opto Isolators/Neons/Bulbs & Holders.	
9.	Transistors.	
10.	FETs/UJT's.	
11.	Transistor Case Styles/ Transistor Pin Outs	
12.	VMOS Power FET: Voltage Regulators.	
13.	Thyristors, Triacs, Diacs.	
14.	Diodes, Bridge Rectifiers, Zener Diodes.	
15.	Electrolytic Capacitors.	
16.	Polystyrene Capacitors, Disc Ceramic Capacitors, Polyester Capacitors.	
17.	Polyester Capacitors: Trimmers, Variable Capacitors, Capacitor Clips.	
18./19.	Resistors.	
20.	Potentiometers, Presets, Wirewound (3.5W).	
21.	DIL Sockets, Header Plugs, Switches.	
22./23.	Switches, Plugs and Sockets.	
24.	Plugs and Sockets, Battery Snaps	

## TOOLS

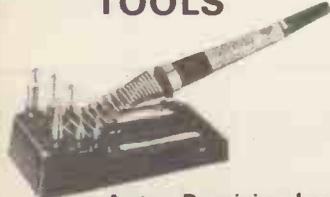

Antex Precision Irons

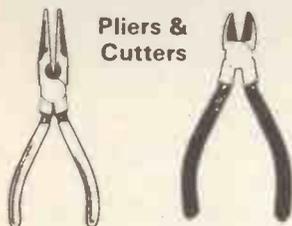

Pliers & Cutters



Electric Drills

### Reliant

A subminiature 12V electric drill suitable for general applications including drilling printed circuit boards. Full load current 1.5A. Torque 100gm cm. Speed approx. 9000rpm. Chuck has a 3/32in. capacity and drill is supplied with a collet which accepts tools with a 2.35mm shank.

**COMPLETE RANGE OF TOOLS AVAILABLE ON REQUEST — EX-STOCK**

## VEROBOARDS for circuit construction


### Laying Out



### Fitting Components



### Track Cutting

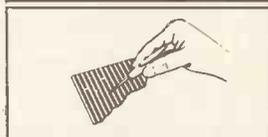

The World famous Veroboard is still considered the fastest and easiest permanent method of assembling electronic circuits. **Laying Out:** If you are constructing your circuit from a published design you will, of course, follow that layout. But if you are designing your own layout, time spent at this stage will be rewarded with a neat link-less circuit board. Lay out the circuit plan on 0.1" graph paper, being sure to allow proper spacing for components and indicating where the copper strips are to be broken. Try to keep the layout as near to the circuit diagram as possible. **Fitting Components:** Lay out the components on the plain side of the Veroboard at right angles to the copper strips, inserting the leads into the appropriate holes. Leads may be soldered directly to the copper strips using a clean low wattage soldering iron 15-25 watts. Use Vero terminal pins for taking wires from the board to external controls (displays, loudspeakers etc). **Track Cutting:** For cutting the tracks on Veroboard the Vero Spot Face Cutter is highly recommended. It is possible to use a small drill — although unless it has been ground at the right angle, it will remove a high percentage of the base board with the copper, thus weakening the board. If the drill is not exactly the right size it is possible to leave hair lines of copper which can cause shorting problems.

## BOXES POLYBOX, OCTOBOX, MINIBOX, CABINBOX, VISEBOX, TUBOX



FLIP TOP BOXES — CASE-BOX — VERO BOXES — CONTROL BOXES

## KNOBS

All Standard Fixing Hole



## TRANSFORMERS



All primaries are 240 volts AC. All secondaries are AC volts directly out of transformer.

## TEST EQUIPMENT



TEST LEADS




MULTIMETERS

DIGITAL FREQUENCY METER PFM200



## AUDIO PRODUCTS

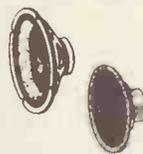

SPEAKERS



MICROPHONES

HEADPHONES 30-18K HZ



Orders to:

**STEVE'S ELECTRONICS SUPPLY COMPANY**  
15/17 CASTLE ARCADE BALCONY,  
CARDIFF CF1 2BU. Tel: 0222 41905

TRADE/RETAIL COUNTER OPEN 9.00 a.m. to 5.30 p.m. MONDAY to SATURDAY

Complete Range of Construction Publications by BABANI PRESS available. Send Now for Full Details.

# RECORD REVIEW

**Computer World**  
by Kraftwerk  
EMC 3370

Earlier this year, EMI Records (UK) signed Kraftwerk and here is their first LP release for this company, which is just in advance of the group's first UK tour since 1976.

The concept of the album is that it IS the Computer World, and its titles range from 'Computer Love' to 'Home Computer' and 'It's More Fun to Compute'.

For many people, Kraftwerk create in their music an impression of robot composers sitting rigidly at vast banks of controls. This 'robotic feel' seems to have been the group's trade mark since the No. 1 success of 'Autobahn' (single and album) in 1974 on the Vertigo label. The double album 'Kraftwerk' preceded this although it really contained more sound effects rather than pure electronics. Other records have been 'Ralf and Florian' (named after Ralf Hutter and Florian Schneider who make up the present group with Wolfgang Flur and Karl Bartos), 'Radio Activity' (1975), 'Trans-European Express' (1977) and 'The Man Machine' (1978) with the latter three on the Capitol label. Two Vertigo compilation albums may also be of interest 'Exceller 8' (1975) and the recent 'Elektrokinetik'.


This latest album has been recorded at Kraftwerk's Kling Klang Studio in Dusseldorf. At the same time, the Kling Klang studio was being modified to be transportable on tour. Giant video screens have been specially made for the visuals, but for now it's the music that remains our focal point.

The title of the main track 'Computer World' introduces a musical phrase that dominates the whole LP. In the Key of E minor here, it has the notes G-D-B-E (the diagonals indicate an upward or downward movement of pitch).

Kraftwerk don't often name on LPs the equipment they use, probably because a lot of it's custom built. No particular synthesiser sound is evident, although the sequencer controlled melodies usually have dry percussive pizzicato string tones at centre stereo, enabling a repeated echo of the sequence to be heard in syncopation at the left hand stereo position.

The only words sung on the record are on 'Computer World' and 'Computer Love'. Any other speech either comes from vocoder treated human voice as in 'It's More Fun To Compute' or as computer processed speech. The rather limited vocabulary of their speech board is evident on the opening track with the words 'address, numbers, money, people, time, travel, pre-ignition and entertainment', (perhaps they've not seen E&MM's Wordmaker yet!)

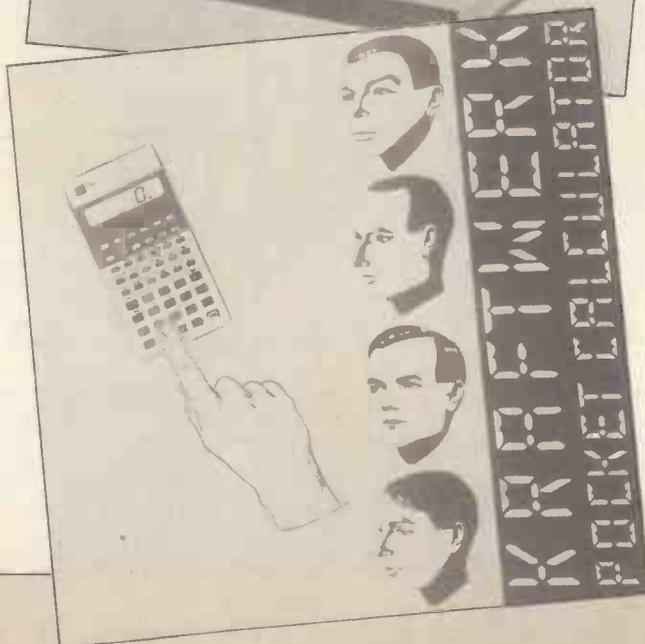Repetition plays a major part in the music of Kraftwerk and is very evident



on 'Computer World'. The use of simple harmony is another element that either attracts you through its simplicity and 'primitive' flavour or, through its lack of development and same dynamic level throughout, may not inspire you. And the question that most of the 'still inspired' listeners ask is, 'Did it really take three years to put this LP together? Surely not, so perhaps we should regard the purpose of it is to set an 'image' for the future. Certainly, computer speech and musical calculators are here to stay and the whole feeling of automated music comes from the open and simply structured pieces.

The E minor harmony of 'Computer World' has one change to G minor for the words 'Interpol and Deutsche Bank' (using the melody G/A/Bb BbA F/GND).

'Pocket Calculator' is amusing to listen to and utilises interjections from Casio and Texas calculators in between 'I'm the operator with my pocket calculator ...' Placement of sounds is not important in the music, but a dominating syncopated repeated Ab note catches attention at stereo centre whilst the bass line holds on to octave Bb's. Against the bass comes Ab harmony that often sounds like a suspended 4th chord when the melody 'Ab/C/FFAb/C/EbEb'D' appears.

'Numbers' uses one to eight count speech in various languages over



repeated random sampled notes and deep grunting bass riff. Some panning is noticeable and timed echo too. This piece runs into 'Computer World' again using instruments only except for a fade out on jumbled computer speech running at fast clock rate.

'Computer Love' has the 'Computer World' theme in G minor. This piece builds up nicely and has an interesting electronic drum rhythm. In fact, the best feature of this record in terms of electronic music is its subtle use of electronic drums — the

phased/flanged cymbal is unusual and the clarity of the 'bubbling melodies' that occasionally appear makes them effective. The simple harmony does pay off as well, with the G minor chords receiving a strong C vocal note that holds the listeners'

attention. Only one new melody appears on notes 'D/G\F\D\C\Bb/C/D/G-\D'.

'Home Computer' has the most in it for me and is cleverly put together on a 'C/Eb\Bb/Db' bass that introduces a 'Dr. Who glass harmonica' solo sound. Despite the one chord basis (C minor), the sequences are well thought out and are controlled from rising ramp waveforms. One contrasting four-note motif (Ab/Bb/Eb\D) leads to ring modulated oscillator sweeps and flanging is prominent on drums which hold the music together.

'It's more fun to compute' really shows off Kraftwerk's electronic cymbal and suitably emphasises that their music although simply built-up (using C/Eb\Bb/Db\C—C\Bb G/D\C— sustained melodies throughout C minor harmony) can be effective.

Their tour commences on June 15th in Manchester with dates all over the UK ending in London on July 3rd. We all wait to see whether Kraftwerk in person will actually appear on stage or whether as their record implies will be replaced by the 'Computer World'.

Mike Beecher  
Dave Townsend

E&amp;MM

**SUPERSALE '81**

All full spec. 2114 (450ns) £1.85, 8 of £1.65 each. P&P 35p. 2708 £2 p&p 35p. TEXAS INSTRUMENTS 2716 single rail, full spec. £4.50. 504116 (200NS) £1.75.

**PORTABLE DATA TERMINAL**  
Transdata 305 Thermal Portable Printer, built in acoustic Modern ACS11, V24 Interface, supplied fully working, £185. Weight 22lb. Carriage at cost. Leaflet SAE.

UA710DC 14 dil 22p, 6 for £1, p&p 30p. (All Full Spec)

2526 Character Generator (64 x 9 x 9) £2.95 + data & p&p 35p. MM5240 AA/J Character Generator £3.50 + data. p/p 35p.

LEAR SIEGLER dot matrix print-head, 7 needle. £19.50 p/p 50p.

ZETTLER low profile PCB relay 30mm x 36mm 4.8/6.9v d.c. 2/2.5 amps a.c. contacts. 85p p/p 35p.

**D TYPE CONNECTORS**

9 Way: sockets (solder) 55p.  
15 Way: wirewrap plugs only 75p.

50 Way: skt (wirewrap) £1.65.  
50 Way: skt £1.45, p&p 25p.

25 Way Male to Female with covers plus minimum 1 metre of cable (12 way) £4 each p/p 35p.

25 Way plug (soldercaul), 25 Way socket £1.50 each.

**COVERS**

37 Way: 90p (plastic), p&p 35p.  
9 Way (metal) 60p, 15 Way (metal) 95p, 25 Way (plastic) 85p, 37 Way reduced from 90p to 80p. 50 Way (plastic) 90p.

**DISPLAYS**

HP 5082/7414 4 digit DIL display full spec £1.50 each, p&p 35p. Large quantities POA.

LED 3 Digit DIL 55p, p&p 35p. HPS082/7650 .4" cc, left and right decimal point, high brightness (unmarked), only 50p, 12 for £5, p&p 35p.

**SUPERSAVER 1**

Ribbon Cable Headers 16 DIL Jernyn, gold-plated, with cover 45p, p&p 25p.

Ansley Header plugs. PCB mounting. 14 Way 75p, 16 Way 95p, 24 Way £1.80. (Insulation-piercing type) p/p 35p.

Ansley I/O Header plugs. 1in 26 Way 65p, 26 Way (right-angled) 85p. 40 Way £1 p/p 35p.

**SUPERSAVER 2**

Tantalum Capacitors 25 volt. 4.7 uF, 14 for £1, p&p 35p.

**SUPERSAVER 3**

PRICE SMASH FND500 .5in. LED displays, full spec 50p each, p&p 35p, large quantities POA.

**SUPERSAVER 5**

Battery eliminator 6VDC 200MA 240V AC input ideal for calculators, radio, etc., give away price 95p each. Large quantities P.O.A. p&p 35p.

**SUPERSAVER 6**

EAO KEY SWITCH oblong fascia, 25mm x 18mm (approx. 18mm hole), fixing supplied, brand new with 2 keys. £2.95 p&p 35p.

**SUPERSAVER 7**

SN74116 Dual 4 Bit latch 75p, p&p 35p.

SN74118 Arithmetic Logic Unit, 80p, p&p 35p.

SN74194 4 Bit Reg 50p p&p 35p. SN74198 8 Bit Shift Register, 75p p&p 35p.

**SUPERSAVER 8**

ITT 4cx 250b brand new full spec £7.50 each p&p 35p.

**SUPERSAVER 9**

5 digit 7 segment DIL LED .11" displays 5 for £1.50 p/p 35p.

**SUPERSAVER 10**

9-way male/female connector, ELCO 8129, 0.1 inch pitch, gold-plated PCB mounting, ideal for bussing two PCBs together. Superb value, 35p, p&p 35p.

**SUPERSAVER 11**

74LS266 50p. 74LS245 £2.40. 74LS240 £1. 74S260 35p. P&P on all above 35p.

**SUPERSAVER 12**

TMS 3128NC Static shift register, £1.50, p&p 35p.

**SUPERSAVER 14**

Recording Designs Ltd digital cassette deck, 50-100 Baud RS232 240V input. A professional superb deck. £48, p&p £2.

**SUPERSAVER 15**

5K 3/4" multiturn trim pots. PCB mounting, per box of 14 £2.50, p&p 35p.

**SUPERSAVER 16**

OPTRON OPTO SLOTTED SWITCH (Type OPB-814) £1, p&p 35p.

**SUPERSAVER 17**

VU METER 48mm x 50mm approx. overall size. Face size 50mm x 28mm approx. Brand new. £1.15 p&p 30p. (Sent at purchaser's risk).

**SUPERSAVER 18**

PCB AMP (LM380). Unused. 65mm x 95mm approx. 9-12v DC. £1.35 p&p 35p.

**SUPERSAVER 19**

10 DIGIT (Red). LED display. (1.22in digit size). With built-in driver chip and built-in lens magnifier. Data sheet supplied. Brand new. £2.50 p&p 35p.

**SUPERSAVER 20**

4 1/2in. JUMPER LEAD. 16 DIL header to 16 DIL header, 95p p&p 30p.

**SUPERSAVER 21**

2 1/2in. JUMPER LEAD. 14 DIL header. 65p p&p 30p.

**SUPERSAVER 22**

N82S126. 1024 bit programmable bipolar ROM open collector £1.25, 8 for £8, p&p 30p.

A FEW LEFT—ITT 2082 Data Modem £115 each, p&p £3. (See previous ads for technical details).

Just arrived. ICL Termpriinter terminal with keyboard. Switchable rates. 4 only. £125 + VAT.

TMS 4030, 4096 x 1 dynamic RAM, 200ns removed from PCBs. £1 each. 16 for £15, p&p 35p.

GPO LINE MATCHING TRANSFORMER. With 12V reed relay etc. removed from equipment. £1 = 40p p&p.

CAPACITOR SCOOP. 1.600uF at 10v, 160uF at 25v. Axial lead. 2 dozen for £1 = 35p p&p.

DON'T KILL YOUR EPROMS. Augat 24 Way low profile socket. Solid gold pins. A superb socket. Leave your eproms in them for programming or usage to prevent breaking off pins. Only 40p each, p&p 35p.

**LB ELECTRONICS**

11 HERCIES ROAD, HILLINGDON, MIDDX, UB10  
9LS ENGLAND

All enquiries s.a.e. please. Telephone answering machine service out of business hours. New retail premises, now open Mon, Tues, Thurs, Fri and Sat, 9.30-6.00. Lunch 1.2-1.15 weekdays. Closed all day Wednesday. We are situated just off the A40 opposite Master Brewer

UXBRIDGE 55399

All components full spec

PLEASE DO NOT ORDER  
GOODS FROM OLD  
ADVERTS

PHONE BEFORE  
ORDERING

ALL PRICES  
INCLUSIVE OF VAT



SURPLUS STOCKS PURCHASED FOR CASH

# BOOK REVIEWS


## Musical Applications of Microprocessors

by Hal Chamberlin  
Published by Hayden Book Co Inc.  
Price £14.85

Here's a book that is truly for the E&MM 'Electro-Musician' of the future. I haven't stopped reading it since I picked it up (some time ago I must confess!). Its 600 pages are packed with the most up-to-date information on making electronic music through your micro and it really does give practical examples that will give you numerous building blocks for experiment.

Although many computer music techniques have been developed since the 1960's, their widespread use in electronic music production and their possibilities of interfacing with commercial and kit synthesizers are only just being realised. This is not to say that we shall have to wait a little longer for computer music composition to become feasible for the 'ordinary' musician working with limited financial resources. In fact, the hardware is available, as this book proves, and all the reader needs in addition is an understanding of BASIC, machine code and peripheral interfacing.

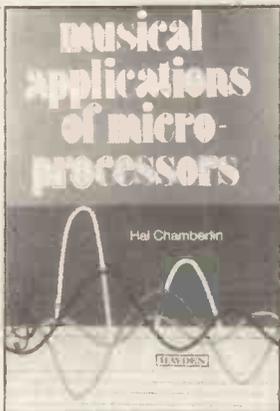The first section of the book covers background material, analogue and digital musical synthesis principles as well as introducing specific micro-systems from Z-80 to 6502. The second section deals with computer-controlled analogue synthesis and the



final part has digital synthesis and sound modification.

In particular, it teaches the reader the vital controlling and interfacing techniques needed to link your Pet, Sharp or popular micro to input/output ports and shows practical ADC and DAC circuits as well as possible keyboard matrix scanning systems. (This month's 'Alphadac 16' uses this type of application.)

The book uses minimal mathematical theory and maximum circuit examples and/or sample programs — from organ interfacing to percussion generation. Finding the answers to using the electronics is the stumbling block for many musicians and this superbly written book with accurate wave diagrams and circuits will be a tremendous help.

Mike Beecher



## The Joy of Minis and Micros

by Philip Stein and Howard Shapiro  
Published by Hayden Book Company Inc.  
Price £5.95

An odd title but a book full of constructive advice, easily digested wit and many a true word on the faults that can accompany the sort of computer destined for the consumer market.

The book is typically American in format using an abundance of clichés, puns and sheer lunatic headings to introduce each section, but it is this kind of informal approach that lends itself so well to a subject that has become over-rated and over-publicised.

At last here is a book purposely written for those who do not own a micro-computer. A book which aims to resolve the computer's usefulness or role and if necessary advise against purchasing such a unit without even an inkling of what to do with it when you have bought it.

The subjects covered are:— Do you or don't you need a mini-computer? What about main frames or micro-computers? How to pick the right mini-computer? (and it is here that such considerations as which language do you require or do you need time sharing, are considered). Hooking it up with the rest of the world (I think they mean interfacing). But what are you going to use it for? And a very brief chapter on how does it work?

It is 100 per cent devoid of any form of illustration which judging by most American books is another point in its favour. From a software point of view, there is very little unexplained, however, I must underline the fact that it is only a preliminary guide to the subject and at no point goes into deep or gory detail.

The main text is preceded by an incredible 20 verse poem, the purpose of which is quite obscure — even having read the book. Nonetheless, my advice is if you are thinking of purchasing a home computer some time in the near future then this is certainly as good a volume as any to choose in an effort to start you off in the right direction.

Nigel Fawcett

## Electronics Pocket Book

by E. A. Parr  
Published by Newnes  
Technical Books  
Price £5.60

The fourth edition of this popular reference book has been completely rewritten in an attempt to cope with an electronics technology that progresses at an astonishingly rapid rate. Since making its first appearance eighteen years ago, the book has seen the simple germanium transistor technology of those days grow into the sophisticated micro-processor chip systems of today. Indeed, one is reluctant to produce a reference book these days for fear it will be outdated before even leaving the printers' press. I must give full marks to Mr Parr for achieving considerable success in producing a book that is up to date yet retains some of the more 'old fashioned' techniques upon which the technology is still based.


In his preface, the author states the book's unchanged philosophy of 'a non-mathematical presentation of the many varied topics covered by electronics'. This I found, generally, to be so. Although no claims are made for completeness (and indeed who would be so bold as to try to write a complete book of electronics today) I found the wide range of topics covered quite surprising.

The various sections dealing with, for example, basic atomic structure, electronic components, simple circuits to more advanced computer circuits, power supplies etc., are concisely presented but perhaps, a little too brief in parts.

Nice to see Teletext and Prestel mentioned but disappointing to find no reference to glass-fibre optics as a communication means — currently being introduced by British Telecom and undoubtedly the data transmission medium of the future. The usual reference data section is included at the end of the book.

Summarising: A book of use to the student and enthusiast as well as of possible use to the designer for quick reference. However, for detailed information, reference elsewhere would be required.


Anthony M. Ball

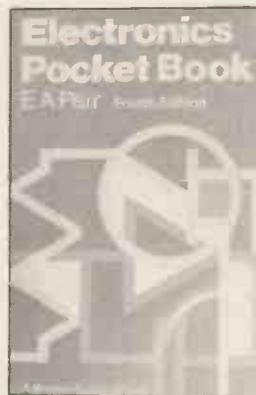
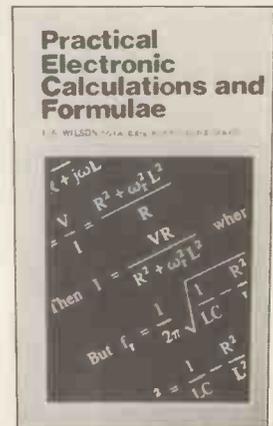
## Practical Electronic Calculations and Formulae

by F. A. Wilson  
Published by Bernard Babani  
Price £2.25

Almost invariably the books that are reviewed in the various electronic periodicals consist of project books, teach yourself books or theory books. Whether you are a newcomer to the subject, a budding amateur or even a fully fledged professional, it is virtually impossible to remember or recall all the mathematical calculations and formulae required to bring your various electronic designs to a fruitful conclusion. There are many publications that cover this aspect of electronics and




make very handsome items of support documentation to compliment the other books on your bookshelf but in my opinion F. A. Wilson's "Practical Electronic Calculations and Formulae" stands out on its own. It is an excellent book and has been compiled to suit all levels of technical knowledge. If the arithmetic involved is likely to be too advanced then maximum use has been made of tables and graphs.

It is primarily a reference book and has been divided into six sections: Units and Constants, Direct Current Circuits, Passive Components, Alternating Current Circuits, Networks and Theorems, and Measurements. You will notice that these sections follow the format applied to teach-yourself or elementary theory books on electronics.

The amateur should never feel that having to refer to books such as this is indicative of his not being able to grasp the subject fully. The fact is professionals always make good use of reference books because the more involved one becomes in electronics, the more confusing and similar the methods of calculation become.

It would be impossible for me to give a brief outline of the contents or even to precis the subjects covered within the text — it quite simply covers the lot. Every symbol, every constant, every unit of mensuration is there for those who have never quite been able to grasp those complicated formulae involving vectors, time lag and phase difference, which are so common in AC theory, this is the book for you as I have never seen a better approach to or explanation of this very difficult area.

Nigel Fawcett

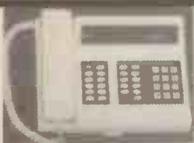

### COMPUPHONE LAMBDA 738

This is the most advanced computerised telephone on the market. It has a built in calculator, clock with seven alarms, a stop watch/timer, 28 memories to store most frequently used telephone numbers, automatic dialling of pre-programmed number, automatic re-dial with repeat dialling at short intervals until the other party answers, a one way speaker enables you to monitor the line. Push button dialling, built in telephone index and lots of other features. It is being sold in Exchange and Mart at £150.00, but we are offering it at a very special price.

£99.95 + £2.90 p&p



### PUSHBUTTON CONSO TELEPHONE

This is a superbly styled, one piece, very compact push button telephone, with last number redial facility (on pressing one button it will redial the last number you dialled). A special MUTE Button enables you to talk at your end without the other party hearing you. The electronic buzzer can be switched on or off.


£25.95 + £1.95 p&p



### HANDHELD SPACE INVADERS

A superb game, provides endless fun for children and adults alike. (WARNING - THIS GAME CAN SERIOUSLY AFFECT YOUR PASTIME). It gives you 90 seconds to hit enemy craft. The elapsed time and 4 digit score is constantly displayed. Score is decremented if you hit a friendly ship or if enemy missile penetrates your defence.

£10.95 + 75p p&p

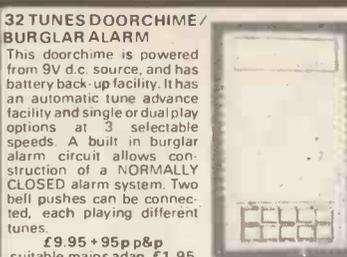

### 32 TUNES DOORCHIME/BURGLAR ALARM

This doorchime is powered from 9V d.c. source, and has battery back-up facility. It has an automatic tune advance facility and single or dual play options at 3 selectable speeds. A built in burglar alarm circuit allows construction of a NORMALLY CLOSED alarm system. Two bell pushes can be connected, each playing different tunes.

£9.95 + 95p p&p  
suitable mains adap. £1.95



### FLIP CALLER PUSHBUTTON TELEPHONE

This is a very compact beautifully designed, high technology digital telephone. It has last number re-dial facility at the touch of a button. The folding part directs the sound into a built-in microphone during use, and protects the keys when not in use.


£23.95 + £1.95 p&p

### GALAXY GAME II

This hand held computerised game unit has three different games, and allows one or two players to play at two skill levels (slow and fast). A two digit display shows the score. The 3 games are:

1. CROSS FIRE Allows you to shoot the passing space objects.
2. PASS THROUGH: The moving objects.
3. FOLLOW ME: Follow the pattern initiated by the game.

£10.95 + 75p p&p

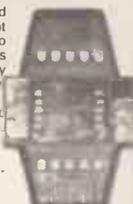

### COOKIE MONSTER ALARM CLOCK RADIO

This is an ideal gift for young children, it has a top quality wind up clock movement with sweep second hand. Wake to radio or buzzer alarm. Radio uses 4 penlite batteries and has rotary tuning and volume controls.

£10.95 + £1.25 p&p

### DUAL TIME MUSICAL ALARM CHRONOGRAPH

Continuously displays hours, mins., secs., day of the week, AM/PM indicator and alarm-on indicator - 1/10th sec. chronograph with lap time facility. Alarm plays "YELLOW ROSE OF TEXAS." Comes with a fully adjustable stainless steel matching bracelet. (Chrome colour).

£12.95 LM101 + 50p p&p



### SLIM PENDANT WATCH

This watch is beautifully designed as a slim pendant and comes complete with a 26" long neck chain. The functions include: hours, minutes, seconds, date, month and 4 year auto calendar. Comes in gold colour and is ideal for day and night wear.

£6.95 + 50p p&p



### SUPER SLIM PEN WATCH

Beautifully styled super slim stainless steel ballpoint pen (replaceable refill) combined with precision quartz timepiece normal display in hours and minutes with flashing colon, date and month and second, can be displayed by pressing a button, 4 year auto calendar. It comes in a very neat presentation case. Our price

£8.95 + 50p p&p

### DUAL TIME COUNT DOWN ALARM CHRONOGRAPH

This superb watch has all the features one would ever need. It has selectable 12/24 hr. display count down timer/ alarm, dual time zone, chronograph with lap time facility, 24 hr. alarm with 5 min. snooze facility, back light fully adjustable stainless steel bracelet and we are offering it at our incredibly low price.

£8.95 + 50p p&p



### 6 DIGIT LADY'S SNOOZE ALARM

This is a very good value for money, it has large easy to read 6 digit display and shows: hours, minutes and seconds, pressing a button it shows date, month and day of the week, the 24 hour alarm has 5 min. snooze facility. It has a fully adjustable bracelet and a backlight. (Gold colour).

£7.95 + 50p p&p



### CAR STEREO PLAYER WITH AM/FM-MPX RADIO

This compact, quality product is designed to provide you with exceptional listening pleasure. The features include: AM/FM dial-in-door, local/distance attenuator switch for better stereo reception, AM/FM indicator, FM stereo indicator. Fast forward and eject button for cassette, balance, volume and tone controls. 7 watts per channel output.

£29.95 + £1.90 p&p  
Suitable speakers £5.00 per pair + 95p p&p

### LADY'S SUGAR COATED WATCH

Lady's 9 function LCD watch. Hours, minutes, seconds, month, date, backlight, auto date/time display mode. 4 year auto calendar. This watch has an optional auto date/time display mode. In this mode, time and date is alternatively displayed every 2 seconds. (Chrome or Gold).

£5.95 + 50p p&p

### DUAL MELODY WORLD TIMER

At a touch of a button it displays time anywhere in the world, with geographical position indicated by flashing that zone on the world map. It has two line display and displays hours, minutes, month, date and day of the week, and option to display seconds instead of date. It has two alarms, a home time alarm and a world time alarm, each play different melody for approx. 30 seconds, it also has song demonstration facility.

£24.95 + 75p p&p



## GUARANTEE

All our products are guaranteed for a period of 1 year. We also offer a 10-day money back guarantee (if you are not completely satisfied with our product, then return within 10 days in same condition as you received it). All our products are fully tested before despatch.

### CAR ELECTRIC AERIAL

Add a little luxury to your car by installing this motorised car aerial. Can be installed in any car or truck with 12V supply. It is an excellent value for money and is an ideal gift.

£8.95 + £1.25 p&p

### LIGHTWEIGHT HIGH QUALITY STEREO HEADPHONES

This is a very high quality stereo headphone, to minimise the size and weight it uses samarium cobalt magnet and a sensitive polyester film vibrator unit enables very stable Hi-Fi stereo sound, with minimum distortion. The frequency range is 20-20,000Hz, impedance 32 ohms, sensitivity 98 db/mw, maximum input power 100mw, weight 40 gms (excluding cord). An adaptor is also supplied to enable use with both 3.5mm and 1/4 inch jack sockets.

£7.95 + 75p p&p



### SOUND-A-ROUND STEREO PLAYER

You can enjoy a very high quality perfect stereo wherever you go or whatever you are doing. This very high quality stereo player comes complete with a carrying case, a set of super sensitive extremely light weight headphones and a demonstration cassette. A very special feature is the "HOT LINE", this enables you to hear what is going on around you through a built in microphone. It has a socket for additional headphones.

£44.95 + £1.95 p&p  
Extra headphones £7.95 + 75p p&p

### 2-BAND HIGH QUALITY HEADPHONE RADIO

You can buy this AM/FM Headphone radio for the price of just headphones. Runs off a single PP3 battery, has a volume control and a telescopic aerial for FM waveband. The ideal gift for youngsters.

£9.95 + 95p p&p

### STAR CODE TO WALKIE TALKIES

These Walkie Talkies made by GENERAL ELECTRIC COMPANY use 49MHz AM (Crystal controlled - single channel). The other features include: STAR CODE signal key for sending morse code messages (range approx. 1/4 mile). Combination speaker/mic. (range approx. 1/4 mile). Belt clip, flexible antenna, spare battery compartment, volume control. Super-regenerative receiver circuit and operate on standard PP3 type battery. S.A.E. for details.

£23.95 + £1.95 p&p

### FLUORESCENT PORTABLE LIGHT

A very good quality battery-operated high-power fluorescent light for use in the car or for camping. Uses 8 'D' size cells and it has a socket for 12V DC input for use in the car. Power consumption is 6 watts. New circuit makes batteries last longer.

£4.95 + 95p p&p



### FM WIRELESS MICROPHONE

This high quality Electret microphone can be tuned to transmit in the range 85-95 MHz FM. It can be received on any FM receiver, the range depends on the sensitivity of the receiver. Uses one penlight battery which fits inside the microphone. Ideal for parties, discos and clubs.

£8.95 + 50p p&p

### NEWTONE WALKIE TALKIES

These impressively designed Walkie Talkies are very good value for money. These have built-in morse code button, volume control, telescopic antenna, belt clip, transmit receive indicator, 49 MHz AM crystal controlled transceiver. The effective range for morse code is approx. 1/4 mile and for speech approx. 1/2 mile. Use standard PP3 type battery.

£16.95 + £1.95 p&p

### THREE-IN-ONE FLUORESCENT

This very compact unit is a torch, a portable fluorescent light and a hazard flashing amber light, all built into one neat case. It comes complete with a shoulder strap to allow both hands to be free. Ideal for campers, hikers, and motorists. Runs on six 'C' size batteries.

£6.95 + 95p p&p



### ALCOM CORDLESS TELEPHONE

This telephone system gives you freedom from the desk, the base station connects to your telephone line, the remote hand set can be carried in own case with shoulder strap or clips to your belt. You can receive calls or make calls from within a radius of 1/4 mile from base station. The hand set has push button dialling with last number re-dial facility and has rechargeable batteries. The batteries are charged when plugged into base station. It is being sold elsewhere for £169.00, we are offering at a very low price.

£139.95 + £2.90 p&p



### QUARTZ TRAVEL ALARM CLOCK

This is a very versatile alarm clock, you can use it in the car, in the kitchen or as a desk top clock. Large (1cm character size) display makes it easy to read from a distance. It has 4 year auto calendar, backlight, AM/PM indicator and alarm on indicator.

£7.95 + 75p p&p



### SMOKE DETECTOR FIRE ALARM

Statistics show that it is not the fire that kills, it is the toxic fumes before the flames which are the killers. This early warning smoke detector can detect the fire at its early stages, and give those extra vital minutes to save life. At our offer price you could put one in each room. If you buy four, we will give you one free. Each unit comes complete with a battery. (Please note that all units are tested before despatch in case of malfunction, our liability is limited to the replacement of alarm unit).

£8.95 + 75p p&p  
(p&p for more than one unit is £1.50)



### RAPIDE REACTOLITE SUNGLASSES

These photochromic sunglasses get darker as the sun gets brighter, and are crystal clear in the shade. These are available in strong metal frames in Silver, Gold or Black colour. These come complete with a simulated leather carrying case. The suggested retail price is £12.95, but we are offering them at a very special price of £4.95 + 75p p&p. 'Sunsitive' Photochromatic sunglasses £2.95 + 75p p&p

### TALKING ALARM CLOCK/STOPWATCH

This 'SHARP' Talking Clock is a 'state-of-the-art' product. On pressing the button it announces the time. At the preset alarm time a musical alarm is played and again the time is announced. It has 5 mins. snooze facility. Also has a useful timer and speaks time elapsed every 1 min., 5 mins. or 30 mins., whichever is selected. In the stop watch mode it announces the elapsed time at preset intervals or on pressing of a button at any time. It is an ideal gift, especially useful for blind people. Overall size is 11 4x6x2 2cms.

£39.95 + £1.95 p&p



**AKHTER INSTRUMENTS LTD**  
DEPT. E&MM  
11-15 BUSH HOUSE  
HARLOW, ESSEX CM18 6NS  
TEL: 0279-414464




Phone your Barclaycard or Access Number for Immediate Despatch

# INDUSTRY PROFILE

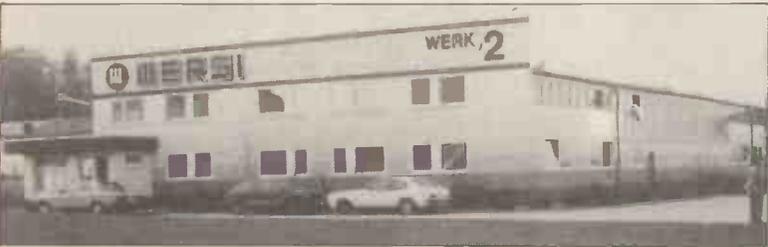
## Wersi Electronics



Wersi main showrooms, factory and offices in Halsenbach.



Wersi's large factory 2.

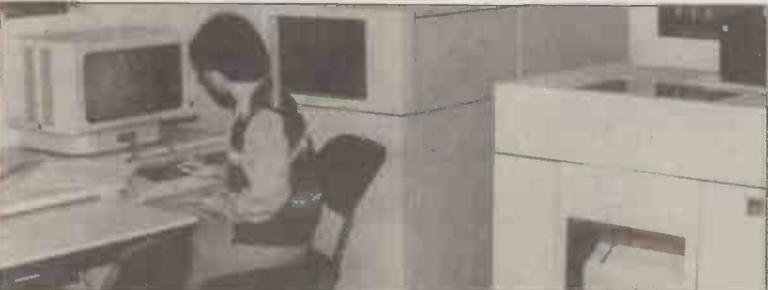

IBM computer system for administration and customers orders.

The story of the German Company of Wersi Electronics began in 1968 when the priest from St. Goars on the Rhine asked a well known young electronics expert in the town, Reinhard Franz, to repair his electronic organ. Wilhelm Franz, his older brother, quickly recognised the potential of setting up a business in the field of electronic music. They both worked intensively on the idea of developing an electronic organ with the newest technology down in the cellar of their parent's house in Werlau. Soon the first Wersi organ was made and in 1969, the Company premises were established in the small town of Halsenbach near the Lorelei Rock on the river Rhine.

Here, the team of young engineers produced electronic organs as do-it-yourself kits with easy-to-follow assembly manuals. The idea of building a home electronic organ not only appealed to the German public, but quite unintentionally from the outset brought the Wersi kits to many people who initially could not play, as well as


to the enthusiastic hobbyist and professional musician.

The last ten years have seen the continued development of the company, with a second factory built in 1974 for constructing the cabinets and larger mechanical parts. A third factory is now being erected to cope with the increased production and marketing of Wersi kits to many parts of the world.

Wersi now employs over 300 people and has nine retail outlets in the Federal Republic of Germany, nine distribution offices in Europe and the USA as well as ten worldwide representatives. In the UK, two companies provide the personal service that is needed for kit sales and after-sales advice: Aura Sounds Ltd. in Purley, Barnsley and Birmingham; Electro-Voice Sales Ltd. in Rickmansworth, Nottingham and Ipswich. In many respects, their commitment to customers is a long standing one, for the larger kits are often built over a considerable period of time.



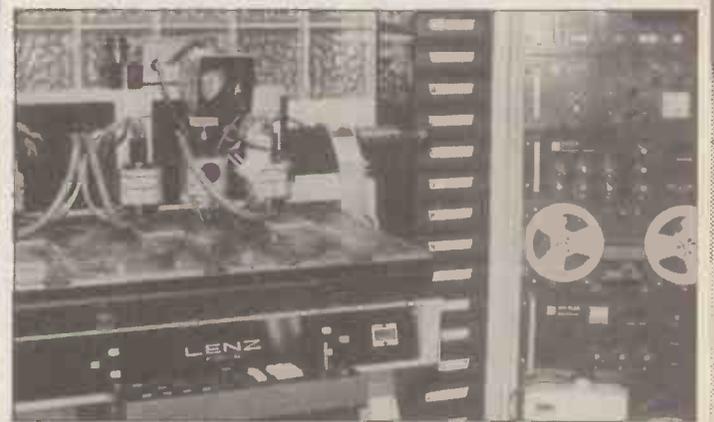Screen printed etch-resist circuit boards.



Computer controlled PCB drilling speeds production.



Legends are screen-printed by Wersi.



Plastics moulding plant with (inset) a finished item.



Factory 2 main cabinet construction areas.



Selecting suitable wood veneers for cabinets.



Preparing rexine covered cases.




Varnishing speaker cabinets.



Factory made wiring harnesses save a lot of construction time.



Putting components into labelled bags.

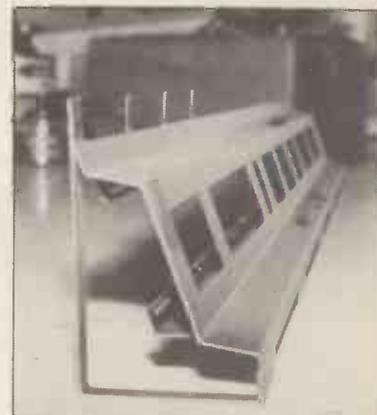

A complex metal part.



Component packing department.

For the future, Wersi plan to sell more of their kits in Africa, South America and Australia. Reinhard Franz has only just returned from promoting his products in Tokyo at the first German 'Musik Messe' in Japan, where organ kits seem to be unheard of.


Today Wersi offers a whole range of kits for electronic music making, from the portable 'Entertainer' single-manual organ at £250 to the huge 'Galaxy' organ costing £7,546. The concept of the Wersi kit is to provide modules that are built individually with little or no electronic knowledge. All the small component parts come in separate numbered packs that are referred to in the step-by-step instructions. These modules are then easily wired together through factory prepared multi-wire harnesses, thus eliminating one of the biggest chores in organ construction. Finally, nearly all of the cabinets are hand-made at their second factory in Halsenbach.

In terms of sound and materials, the Wersi organ and range of speakers, mixers and sound proces-


sors represent high quality although the proof of this was best shown to me when I visited their German showrooms and factories recently.

The friendly hospitality of the German company was more than evident during the whole of our two day visit (accompanying me was Arthur Griffiths of Aura Sounds Ltd). In the main factory we visited the drawing office, component packing departments, circuit board manufacture and despatch areas. At the second factory was the huge cabinet assembly plant and large component storage including ready-made instruments which have 'laser-assisted' component board assembly. Here too, are the research and service departments. Finally, we returned to the sales offices and showrooms.

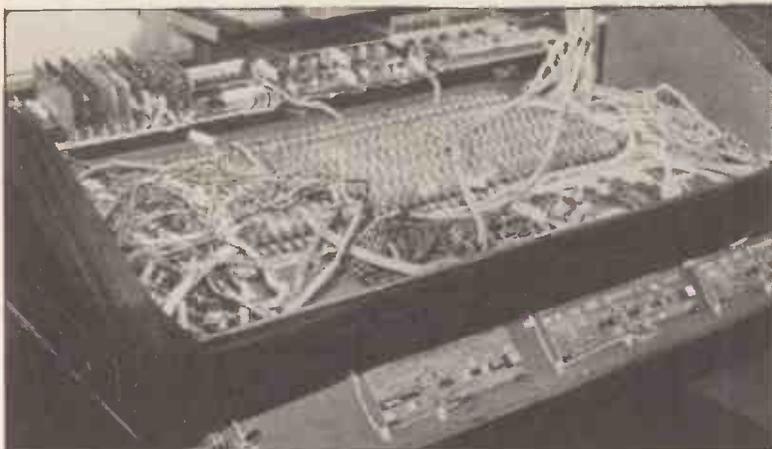
One of the most important criteria for the company's success in its attention to the supply of best quality components. All electronic and mechanical parts are tested thoroughly. Often, special grade ICs from Texas, Motorola, Phillips and others are prepared for Wersi to



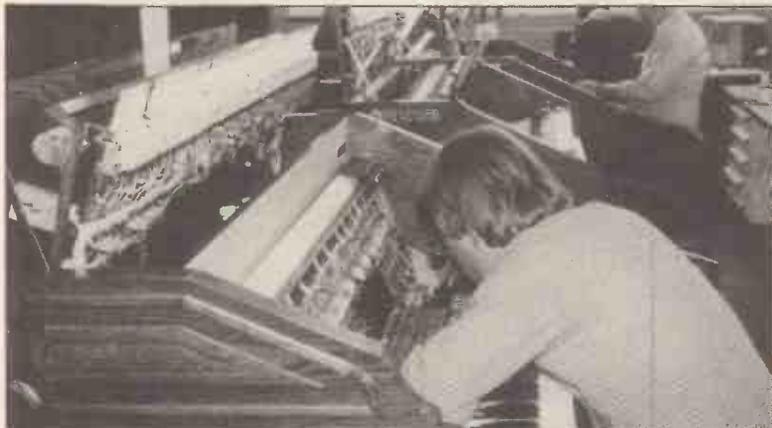A large organ kit during assembly with wiring harnesses installed.



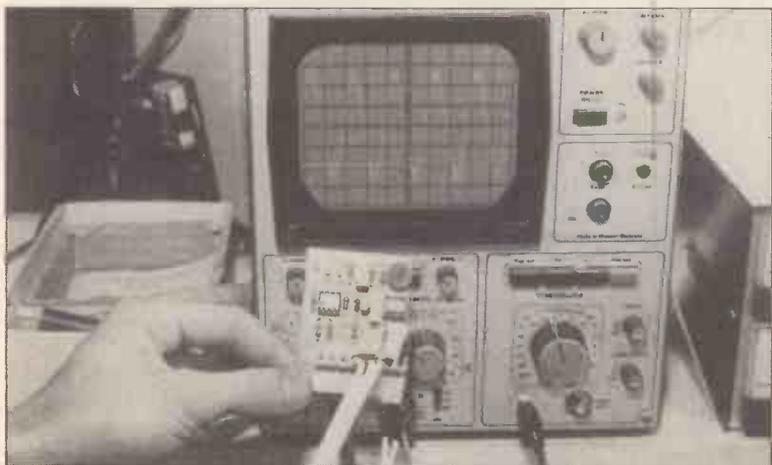Easy access to all parts makes servicing quicker.



The new Noise Gate board kit being checked.



Development boards for cymbal and side drum.



The improved keyboard mechanism for the Pianostar.

ensure that the specification of their kits is maintained.

From the start, integrated circuits were used in kit designs, one of the first chips being ITT's SHA110 device. The full organ range was restructured from the beginning of 1977, covering 1 to 3 manual concert instruments that utilise TTL, CMOS and LSI technology. In all, some 45 patents exist for the circuitry including the 'Sound Computer' which enables up to 64 registration switch settings on the organ to be electrically programmed with EAROMs (Electrically Alterable Read Only Memory) for instant recall at the touch of a button. Literally every switch and tab on the organ from sustain, delay, vibrato to Leslie speaker has a DC control voltage to enable this. Microprocessors will certainly become part of Wersi organ technology for facilitating control of rhythms, voicing and registration.

The electronic keying circuitry is also patented and produces clean sounds from multiple registration and virtual silence otherwise (better than 65dB over the whole instrument at full volume) plus variable attack and sustain — a joint development by Wersi and Texas Instruments.

Wersi's chief engineer, Wilfried Dittmar (also a classically trained organist!) and his team often produce add-on extras to the standard kits that immediately up-date the models. Recent additions include a 'breathy' flute stop with noise filter control, a stereo noise gate that shuts down outputs in between playing, a realistic metallic cymbal, improved snare-drum and the Pianostar S2000 (reviewed this month).

Features such as 13 harmonic drawbars, rhythm tempo presets, drum break emphasis, key click, arpeggios, glissandos, contracussion, multi-preset registration, polyphonic octave slide, transposition, slalomatic, full auto-accompaniment, string orchestra and electronic rotating baffle effects all help to make the Wersi organ as commercial as possible.

Wersi developments include original circuit board mounting stop tabs with self-cleaning contacts, BBD chorus and choir effects, power amps, cabinet construction allowing highest option kits to be implemented at a later date, sine (cascaded filtering) plus square and sawtooth waveforms simultaneously providing basic

sound sources, sealed pedal contacts, and MOS-LSI tone generators normally silent until pressed.

As the photographs will show, most of the organ kit main parts are produced in the Wersi factories including circuit boards, woodwork, plastics, metalwork, wiring harnesses, panel and tab legending and even the manual printing. All this attention to quality that Wersi provides comes at a price — the first 2-manual with pedals organ kit, the Cosmos, costs £1,499 and the popular Helios costs around £3,500. Still, if you buy the Galaxy ready-assembled it's £20,450! The Toccata and Classica instruments are for the church organist and the Combo portable should interest the gigging musician. Many of the instruments were ably demonstrated by Hady Wolff in the immaculate showroom, extracts of which are on E&MM's Cassette No. 3.

At the end of our tour I spoke to Horst Hoppe, the Chief Sales Manager. He stressed their need for more manufacturing and storage space and talked about their planned 400-seater auditorium for demonstration concerts as well as a second-hand organ shop. Visitors frequently come to the showrooms and concert tours in many countries are given by Franz Lambert, Kurt Prina and Jimmy Smith, with Klaus Wunderlick also a frequent Wersi performer. French assembly manuals are now complementing the German, English, Dutch versions already available.




Arthur Griffiths, Mike Beecher and Wersi Managing Director Reinhard Franz

I'll leave the last word to Herr Hoppe who commented 'Much to my own personal regret, there are no magazines similar to E&MM here in Germany. I think there should be great interest in this magazine and like E&MM, we specialise in the field of electro-music and see a great opportunity to offer kits for the layman, giving them many possibilities for enjoying their leisure hours by building their own musical instrument.'

Mike Beecher

E&MM

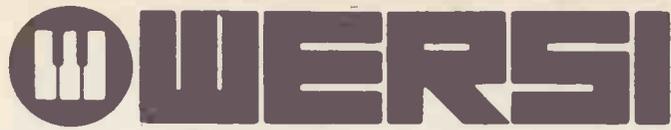

# THE CRÈME DE LA CRÈME OF ELECTRONIC ORGANS



## *Easier to own than you think!*


Believe it or not WERSI organs were designed for those who wanted to build their own organ but never conceived it possible. The WERSI concept is to make assembly an automatic step-by-step procedure. NOW even the humblest do-it-yourselfer can construct a WERSI organ — experience isn't necessary, just the desire to own an organ which is technically brilliant and is guaranteed to produce the world renowned WERSI sound.

Perhaps you have toyed with the idea but are still hesitant about taking the plunge — Electro-Voice are WERSI specialists and whilst giving you the opportunity to see, hear and play the complete range of WERSI instruments at any one of our fully equipped showrooms, we will be more than happy to discuss in full the advantages of building your own organ.

Seeing plus hearing equals believing, so, why not come along to one of our studios and meet one of our resident

demonstrators who will be delighted to demonstrate any instrument. Additionally, talk with one of our engineers who will show you one of the WERSI kit-pack systems. (Electro-Voice customers are guaranteed full after sales service plus engineering support).

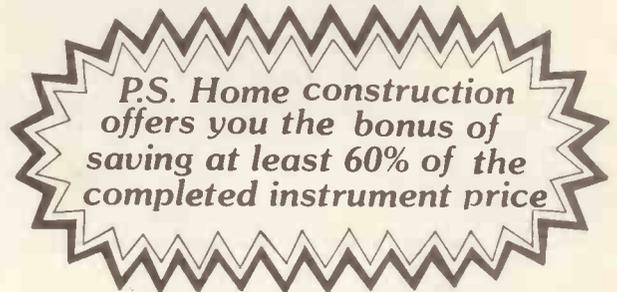WERSI . . . one of the world's most desirable instruments — easier to own than you thought!!






*the voice of WERSI!*

**Head Office & Showroom:**  
Maple Cross Industrial Estate,  
Denham Way,  
Rickmansworth, Herts.  
Tel: (Rickmansworth) 75381

**Nottingham:**  
389 Aspley Lane,  
Nottingham  
Tel: (Nottingham) 296311

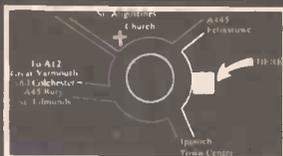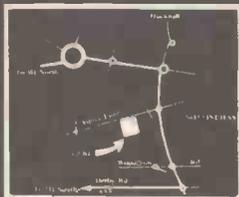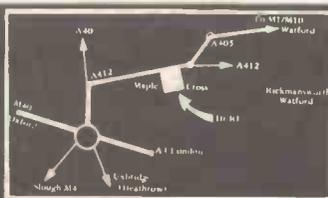**Ipswich:**  
486 Felixstowe Road,  
Ipswich, Suffolk  
Tel: (Ipswich 0473) 710051



Name .....

Address .....

.....


Tel. ....

Please send me the 104 page catalogue. I enclose £1 to cover postage and handling.

**Send to: Electro Voice, FREEPOST, Rickmansworth, Herts RD3 6FP.**

E&MM/7

# NEW PRODUCTS

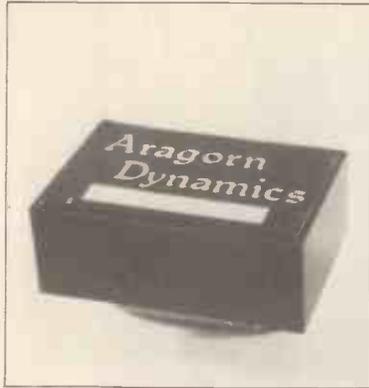


## EXPONENTIAL VOLTAGE TO FREQUENCY CONVERTER

Turner Electronics Ltd, have recently developed a voltage to frequency converter for use in applications where the requirement of a wide, stable exponential frequency range is of prime importance. The Aragorn VF01 encapsulated module also operates in a linear mode with minimal change of external components.

The proven operational frequency range lies between 0.1Hz and 200kHz with a possible maximum of 500kHz at a slightly degraded spec. Accuracy in the linear mode is better than 0.1% central to 6 decades and in the exponential mode, better than 0.1% over 5 decades. Power supply requirements are +15 volts. The module measures L 45 x W 30 x H 21mm. with 0.040 inch diameter, gold plated pins on a 0.1 inch grid pattern.

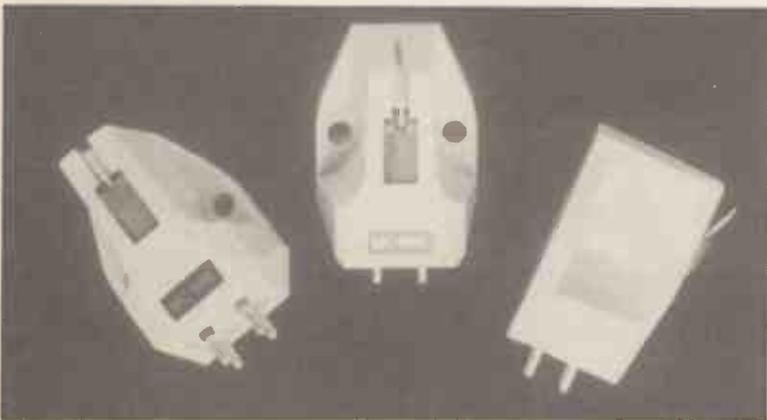For further information and prices contact:  
Turner Electronics Ltd., Unit B2, Old Barn Lane, Kenley, Surrey, CR2 5AT.



## MOVING CORAL


Coral of Japan have released a new high output, low impedance, moving coil cartridge designed as a direct replacement for moving magnet types.

Designated the MC88E, the cartridge features: Coral's one-point suspension system, a magnesium-aluminium alloy cantilever, a specially shaped armature and an output impedance of less than one twentieth of that of a moving magnet design.  
MCA88E Specification:
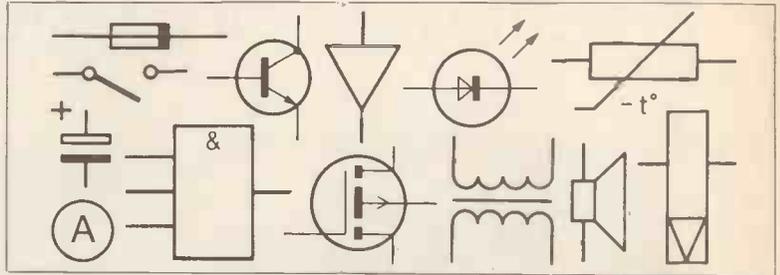
## STANDARDS FOR EDUCATION

The British Standards Institution has recently released a booklet containing 270 symbols and an A1 size wall-chart showing 160 symbols from BS3939 for use in schools and colleges.

The 20 page, A4 booklet containing the 270 selected symbols includes a page of general notes on symbols and diagrams, two examples of circuit layout, 28 general, qualifying, supplementary and unclassified symbols, 28 symbols for conductors and connecting devices, symbols for resistors, capacitors, inductors and transformers, rotating machines, transducers, measuring instruments,



relays and contact units, valves and tubes, semiconductors, logic elements etc.

The wall chart contains 160 of the more common symbols taken from the booklet. Copyright subsists in all BSI publications, but teachers and lecturers are permitted to duplicate

pages of the booklet for their own and students use within the one educational establishment.

The package (designated PD7303) costs £6.00 + VAT and is available from:  
BSI Sales Department, 101, Pentonville Road, London, N1 9ND.

## MINIATURE HANDTOOLS


Tele-Production Tools Ltd., the Westcliff based manufacturer of handtools and production aids have recently released a set of three new 'Easi-Grip' miniature handtools designed for use in electronics and fine modelling.

The set consists of miniature carbon steel side cutters, fine nosed stainless steel tweezer-pliers and a serrated stainless steel scissor (shear for cutting fine wires, boards, foil, etc).

All are fitted with ergonomically styled self-opening handles and are fingertip operated to ensure fine control and ease of operation.

The tools weigh around 40gms each and cost £3.75 each including postage, packing and VAT or £10.00 for the set of three.

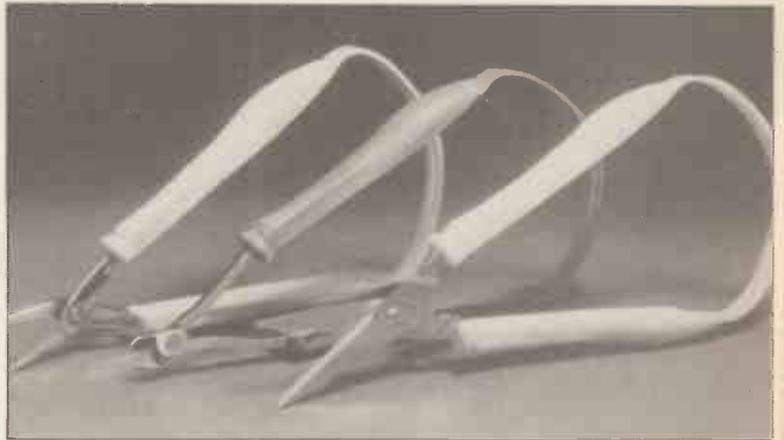Tele-Production Tools Ltd., Stiron House, Electric Avenue, Westcliff-on-Sea, Essex, SS0 9NW.



## PROFESSIONAL WHARFEDALE

Wharfedale, best known for domestic hi-fi loudspeakers, have launched their first purpose-built professional speaker, the E90 PRO.

Designed for high power, high quality PA use, the 300 Watt rating of the E90 and its hi-fi quality reproduction should ensure its welcome to night clubs, small concert halls, and discos.

The E90 PRO is suitable for amplifiers from 30 to 300 Watts with a sensitivity of 95dB per watt at one metre, and features two, 250mm computer-optimised, low-inertia, moving-coil bass drivers, two 100mm high-flux moving-coil, mid-range drivers and a 25mm compression drive horn-loaded tweeter.

Protection against misuse is provided by thermal circuit breakers which make it virtually impossible to overload the E90 PRO, and with mobile discotheque use in mind, the speaker is fitted with castors and recessed grab handles.


The price for the E90 PRO is around £495 each and the speakers will be available at hi-fi shops, music dealers and sound installation specialists throughout the UK.

For further information contact the Marketing Department, "E90 PRO" Wharfedale, Highfield Road, near Idle, Bradford, West Yorkshire. Tel. 0274 611131.


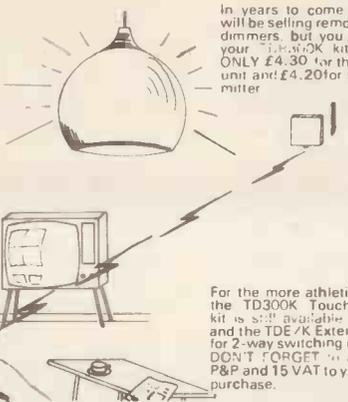
## KIT

Our new TDR300K Touch Dimmer Kit will ensure that you are. Based on our highly successful TD300K touch controlled dimmer kit, the TDR300K incorporates an infra red receiver, enabling the lamp brightness to be varied and switched on or off by touch or remotely by means of a small hand held transmitter. The complete kit, which includes easy to follow instructions will fit into a plaster depth box and the plastic front plate has no metal pads to touch, ensuring complete safety. Even a neon is included to help you locate the switch in the dark.



In years to come everyone will be selling remote control dimmers, but you can have your TDR300K kit now for **ONLY £4.30** for the dimmer unit and £4.20 for the transmitter.

For the more athletic of you the TD300K Touchdimmer kit is still available at **£6.50** and the TDE/K Extension kit for 2-way switching etc is **£2**. **DON'T FORGET** to add 50p P&P and 15 VAT to your total purchase.

## PROJECT

Whatever kind of door you have, our New Electronic Combination Lock will enable you to open it easily but make things very difficult for unwelcome visitors. The unit, which comes complete with a 10-way keypad, requires an easily remembered four digit code to be entered before the door can be opened, while the intruder has over 5,000 combinations to choose from. The code can be easily changed by means of a pre-wired plug and a momentary or latched output version can be made. The kit has even more uses in a car where it may be used to disable the ignition. Another useful feature is the Save Button. This stores the combination number, enabling the car to be used by authorised persons such as garage personnel without disclosing the code. The complete kit measures 7x6x3 cms deep and consumes a mere 40uA when not in use and will drive a 5V to 15V (750mA) solenoid or relay coil (not supplied) directly. So why not treat your door to a new lock for **ONLY £10.50** and think about all the keys you can lose or forget without ever locking yourself out (As featured in PE May '81)



## DISCO LIGHT KIT

Each unit has 4 channels (rated at 1KW at 240V per channel) which switch lamps to provide sequencing effects, controlled manually or by an optional opto isolated audio input.

### DL1000K

This kit features a bi-directional sequence, speed of sequence and frequency of direction change being variable by means of potentiometers. Incorporates meter dimming control. **£14.60**

### DLZ1000K

A lower cost version of the above featuring unidirectional channel sequence with speed variable by means of a preset pot. Outputs switched only at mains zero crossing points to reduce radio interference to minimum. **£8.00**. Optional Opto Input DLA1 **60p**



## 24-HR CLOCK APPLIANCE TIMER KIT



Switches any appliance up to 1KW on and off at preset times once per day. Kit contains: AY 5-1230 1C, 0.5" LED display, mains supply, display drivers, switches, LEDs, triac, PCBs & full instructions.

CT1000K Basic Kit **£14.90**  
CT1000KB with white box (56x131x71mm) **£17.40**  
Ready Built **£22.50**

## MINI KITS

These kits form useful subsystems which may be incorporated into larger designs or used alone. Kits include PCB short instructions and all components.

### MK1 TEMPERATURE CONTROLLER/THERMOSTAT

Uses LM3911 1C to sense temperature (80°C max) and triac to switch heater. 1kW **£4**

### MK2 SOLID STATE RELAY

Ideal for switching motors, lights, heaters, etc from logic. Opto-isolated with zero voltage switching. Supplied with triac. Select the required triac from our range. **£2.60**

### MK3 BAR/DOT DISPLAY

Displays an analogue voltage on a linear 10-element LED display as a bar or single dot. Ideal for thermometers, level indicators, etc. May be stacked to obtain 20 to 100 element displays. Requires 5-20V supply. **£4.75**

### MK4 PROPORTIONAL TEMPERATURE CONTROLLER

Based on a new zero voltage switch 1C, this kit may be wired to form a 'burns fire' power controller, enabling the temperature of an enclosure to be maintained within 0.5°C. Thermistor failure causes output to switch off. Temperature range ambient to 90°C. 3KW **£5.55**

### MK5 MAINS TIMER

Based on the ZN1034E Timer 1C this kit will switch a mains load on (or off) for a preset time from 20 minutes to 35 hours. Longer or shorter periods may be realised by minor component changes. Maximum load 1KW **£4.50**

## REMOTE CONTROL COMPONENTS & KITS



LD271 1R Emitting diode	.36	ML926 16-channel receiver	4
SFH205 Photodiode Detector	.90	latched binary outputs	1.40
SL480 1C Pulse Amp	1.70	Clip-on Plastic Reflector for 1R LEDs, increases range	.20
SL490 32 Command Encoder/transmitter	2.40		
ML922 10-channel receiver + 3 analogue outputs	4.20		

ML925 A decoder designed for model/toy control providing a 2-speed drive motor and three position latched steering system or a vehicle with momentary action steering and a third motor, eg. gun turret, winch, etc. Outputs also available for other facilities such as horn, turn indicators, headlights etc. **2.10**

To make things EVEN EASIER, we have designed several new kits:—  
MK6 — Simple Infra Red TRANSMITTER. A Pulsed infra red source which comes complete with a hand held plastic box. Requires a 9V battery. **4.20**

MK7 — Infra Red RECEIVER. Single channel, range approximately 20 ft. Mains powered with a triac output to switch loads up to 500W at 240V ac, but can be modified for use with 5 to 15V dc supplies and transistor or relay outputs. **9.00**  
"Special Price" MK6 and MK7 together. Order as RC500K. **12.50**

MK8 — Coded Infra Red TRANSMITTER. Based on the SL490, the kit includes 2 1R LEDs measures only 8x2x1.3 cms and requires a 9V (PP3) battery **5.90**

MK9 — 4 Way KEYBOARD. For use with the MK8 kit, to make a 4-channel remote control transmitter **1.90**


MK10 — 16-Way KEYBOARD. For use with the MK8 kit to generate 16 different codes for decoding by the ML928 or ML926 receiver (MK 12) Kit. **5.40**

MK11 — 10 On-Off Channel 1R RECEIVER with 3 analogue outputs 0-10V) for controlling such functions as lamp brightness, volume, tone, etc. Other functions include an on/standby output and a toggle output, which may be used for sound muting. Based on ML922 decoder 1C. Includes its own mains supply. **12.00**

MK12 — 16 Channel 1R RECEIVER. For use with the MK8 kit with 16 on/off outputs which with further interface circuitry, such as relays or triacs, will switch up to 16 items of equipment on or off remotely. Outputs may be latched or momentary, depending on whether the ML926 or ML928 is specified. Includes its own mains supply. **11.95**


MK13 — 11-Way KEYBOARD. For use with MK8 and MK11 kits. Transmits programme step + and analogue + and (3), mute normalise analogue outputs and on/standby **4.35**

## DVM THERMOMETER KIT

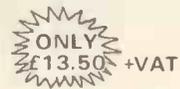
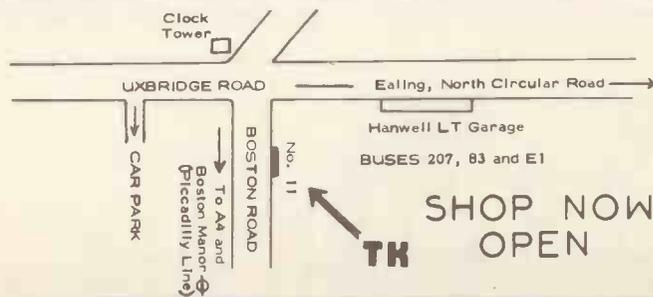
### NEW RIDICULOUS LOW PRICE FOR DVM/THERMOMETER KIT

Based on ICL7106 DVM chip and a 3 1/2 digit liquid crystal display. This kit will form the basis of a digital multi-meter - only a few additional switches and resistors required (details supplied) or make a sensitive digital thermometer (-50° to 150°C) reading to 0.1°C. The basic kit has a sensitivity for full scale of 200mV, automatic polarity and runs from a 9V PP3 battery. At this price you can use this kit in place of moving coil meters in virtually any application from bathroom scales to bicycle speedometers - the possibilities are endless.



**SHOP NOW OPEN**

ALL COMPONENTS ARE BRAND NEW AND TO SPECIFICATION ADD 50p P&P and 15% VAT TO TOTAL. OVERSEAS CUSTOMERS ADD 1.50 (Europe) £4 (elsewhere) for P&P. Send s.a.e. for price list and with all enquiries. Callers welcome 9.30-5.00 (Mon-Fri) 10.00-4.00 (Sat)



**TK Electronics**  
(EM) 11 Boston Road, London W7 3SJ. TEL. 01-579 9794/2842



## COMPONENTS

We also supply a wide range of components including INTEGRATED CIRCUITS, MINI TRANSFORMERS, CMOS, LEDs, VOLTAGE REGULATORS, DISPLAYS, VMOS POWER FETS, TRIACS, DIL IC SOCKETS etc etc.

## EVENTS

- June 15th-19th INTERNATIONAL COMMUNICATIONS, ELECT'L & ELECTRONIC COMPONENTS EXBN., Milner Park, Johannesburg, South Africa. Further information from ECL (Exhibition Agencies) Ltd, 11 Manchester Square, London W1M 5AB.
- June 18th THE TWENTIETH CENTURY ENSEMBLE - Royal College of Music Conductors - Edwin Roxburgh, Lawrence Casserley. The programme includes works for instruments plus electronics. Cristobal Halffter - Variaciones sobre la Resonancia Lineas y Puntos/de un Grito. Heinz Hollifer - Pneuma (all first UK performances). Tickets on the door.
- June 23rd-26th INTERNATIONAL WORD PROCESSING EXHIBITION Wembley Conference Centre, London. Tickets from Business Equipment Trade Ass., 8 Southampton Place, London.
- June 24th PERCUSSION & ELECTRONICS, Programme - 1. Indifferent Affair - Charles Barber. 2. First performance of new work - Nicholas Wilson. 3. A film improvisation - Mark Limbrick. 4. Study for solo snare drum - Jeffery Wilson. Venue: Royal College of Art, Kensington, London. Admission 50p. Commences 1.00 pm. Also June 26-29 as below.
- June 26th St Martins School of Art, Charing Cross Road, London.
- June 28th New Half Moon Theatre, London. Commences 8.00 p.m. Admission £1.00.
- June 29th Brady Centre, London. Commences 8.00 p.m. Admission £1.00.
- June 26th/27th/28th BROMLEY FAMILY & TRADE EXHIBITION, Norman Park, Orpington, Kent. Tickets available half price from EXPLAN, Exhibition Promoters, International House, Cray Avenue, Orpington, Kent.
- June 27th/30th NANN INTERNATIONAL MUSIC EXHIBITION - McCormick Place, Chicago, USA. Special travel arrangements may be made with British Airways (01-821 4544), Trade Fairs and Exhibition Bureau.
- June 27th-July 4th KEYBOARD AND ELECTRONIC MUSIC FESTIVAL, to be held at the London Musicians' Collective, in conjunction with the October Gallery. If you wish to participate, contribute or perform, please post tapes, videos, cassettes to: Ken Guntar, C/O October Gallery, 24 Old Gloucester St, Queen Square, London WCL. Closing date 20th May 1981.
- June 30th FLUTE & ELECTRONICS, British Music Information Centre, Stratford W1. To mark Telemann's 300th Anniversary. Simon Desorgher on Flute, Lawrence Casserley on Electronics performing Telemann Canonica Sonata for flute and electronics. Commences 7.30 p.m.
- June 30th LEEDS ELECTRONICS EXHIBITION, Dept. of Electrical & Electronic Engineering, Leeds University.
- July 8th-12th AUDIO VISUAL EQUIPMENT EXHIBITION, World Trade Centre, Singapore. Further information from Bob Hackett, European Sales Manager, ITF International, Ratcliff House, Blenheim East, Solihull, W. Midlands. Tel. 021-705-6707.
- July 15th-18th NATIONAL FESTIVAL OF MUSIC FOR YOUTH, Fairfield Hall, Croydon. Tickets £1.50 (60p under 19) at the door.
- July 19th SUSSEX MOBILE RALLY, Brighton Race Course - Trade stands dealing in all forms of electronics, including amateur radio, microprocessors, components and C.B. Entrance 50p (with free lucky draw ticket). Commences 10.30 a.m. - 6.00 p.m.
- July 29th-31st MICRO COMPUTER SHOW, Wembley Conference Centre, London. Aimed at both the hobbyist and trade. Tickets £1.50 on the day or three for £1.00 from Online Conferences Ltd, Argyle House, Joel St, Northwood Hill, Middx. (cash and S.A.E. required with order).
- Aug 29th-Sept. 5th NATIONAL HOME ELECTRONIC ORGAN FESTIVAL, Pontins Tower Beach, Prestatyn, North Wales. The programme for this residential event will include: daily concerts by "star" organists - teach-in sessions - sheet music and book sales - exhibitions and demos by leading manufacturers - synthesisers, rhythm units and rotary speakers. Accommodation from £78 for two people. Ring (07456) 2244.

We shall be pleased to publish news of forthcoming electronic and electro-music exhibitions, clubs - also special electronic music concerts.

## THIS MONTH'S SPECIAL OFFERS

Each month, Electronics & Music Maker gives special offers to its readers that represent a substantial saving on normal retail prices.

### FRANZ LAMBERT POP ORGAN HIT PARADE

If you missed Franz Lambert's concert in the UK recently, here's a chance to enjoy the superb modern style of this top organist playing the Wersi Galaxy organ.

Polished organ technique, multi-tracking and effective drums, plus numerous realistic instrumental sounds make this an impressive and most enjoyable record to listen to in widespread stereo.

Normally £4.50  
Offer Price £3.99



### TEST LEAD SET

A set of ten leads: two each of five colours, terminated at both ends with an insulated crocodile clip. Guaranteed a place in any workshop!

Normally £1.30  
Offer Price 99p



Complete this Order Form for either or both of our Special Offers. Please allow 28 days for delivery.

Overseas payments including Republic of Eire should be covered by Bankers draft in pounds sterling.

Closing date 31st July 1981 - Subject to availability.

Send this coupon and cheque/P.O. to:  
ELECTRONICS & MUSIC MAKER (Special Offers)  
282 London Road, Westcliff-on-Sea, Essex SS0 7JG.

Please send me:

Quantity	Item	Item Price £	Total £
	Test Lead Set	0.99	
	Pop Organ Hit Parade LP	3.99	

I enclose a cheque/P.O. payable to:

Electronics & Music Maker for: £.....

PLEASE PRINT

Name: Mr/Mrs/Miss .....

Address .....

E&MM7/81

All prices shown include VAT, postage and packing


BELLS & HOUSINGS-CAR ALARM-CARAVAN ALARM-CONTACTS

CONTROL PANELS-PRESSURE MATS-SIRENS-WINDOW FOIL-ETC
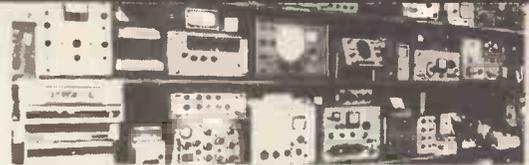
# BURGLAR ALARM EQUIPMENT FOR THE D.I.Y. MAN



4 HELSTON CLOSE, LINTON,  
BURTON ON TRENT, STAFFS. DE12 6PN  
PHONE: BURTON (0283) 761877  
24 Hour Phone Answering Service



RANK KALEE 1742 Wow & Flutter Meter.  
AIRMEC 314A Voltmeter, 300mV (FSD)-300V.  
AIRMEC Wave Analyzers types 853 & 248A.  
DERRITRON 1KW Power Amplifier with control equipment for vibration testing, etc.  
HEWLETT-PACKARD 8551B/851B Spectrum Analyser. 10MHz-40GHz.  
HEWLETT-PACKARD tuned amp & null detector.  
TF2600 Voltmeter 1mV-300V fsd.  
RADIOMETER Distortion Meter BKF6 £125.

LABGEAR T.V. PATTERN-GENERATORS 625-line cross-hatch/  
dot/grey scale £45 (£1 post).  
RANK SIGNAL STRENGTH METERS UHF Channels 20-60.  
Battery operated £30 (£1 post).

#### TELEVISION TEST EQUIPMENT

TEXSCAN VS-60B Sweep Generator, 0-1000MHz £250.  
TEXSCAN DU-88 X-Y Display units £95  
TELONIC 2003 Sweep Generator System £225.  
TELONIC 101 X-Y Display units £75  
TELONIC 1204 Sweepers 0-500MHz £150.  
TELONIC 121 X-Y Display units £95.

#### OSCILLOSCOPE SALE

SOLARTRON CD1400, D/Beam 15MHz £150.  
HEWLETT-PACKARD 1707A. 75MHz £450.  
TELEQUIPMENT D75.  
TELEQUIPMENT DM64 Storage scope.  
DYNAMCO D7100.  
HEWLETT-PACKARD 122A SB. Audio.  
AIRMEC 279. 4 Beam Display Scope.  
TEKTRONIX 581A, 545A & B, 544, 661, 515A.

#### RHODE & SCHWARZ

Selective UHF V/Meter. Bands 4 & 5. USVF. XUD Decade Synthesiser & Exciter.  
Selectomat Voltmeter USWV £450. POLYSKOPS SWOB I and II.  
UHF Sig. Gen. type SDR 0.3-1GHz £750. Modulator/Demodulator BN17950/2.  
UHF Signal Generator SCH £175. UHF Sig. Gen. type SCR. 1-1.9GHz.

#### MARCONI

TF2360R TV Transmitter Sideband Analyser.  
TM6936R UHF Converter for above.  
TF1101 RC oscillators £65.  
6951 SAUNDERS 1400-1700MHz. FM.  
TF1066B/1. 10-470MHz. AM/FM.  
TF1152A/1. Power meter. 25W. 500MHz £50.  
TF1370A RC Oscillator £135.  
TF791D Carrier Deviation Meter.

#### U.H.F. SIGNAL GENERATORS

TF1066B/2 400-555MHz. Deviation to 300KHz.  
TF1060/2 450-1250MHz.  
TF1058 1.6-4000MHz.

#### BECKMAN TURNS COUNTER DIALS

Miniature type (22mm diam). Counting up to 15 turn "Helipots".  
Brand new with mounting instructions. Only £25.00 each.

#### PRINTED CIRCUIT MOTORS

'Printed Motors Ltd' type G16M4. 60V DC. 5.5 amps. Continuous torque 140oz, in 2350 rpm. Diameter 7.5". Depth 2.5". Shaft diam. 1/8" & 3/16". Price from Printed Motors is now over £150 ea. Supplied in good, used condition, tested & guaranteed £25 each (postage £3).

#### AUDIO & RF SIGNAL GENERATORS

ADVANCE types H1, H1E, C2, SG62B, J4A.  
TAYLOR 62A (AM/FM). AVO HF134.  
AIRMEC 352 Sweep Generator.  
MARCONI TF1066B/1 (AM/FM 10-470MHz).

LABORATORY OVENS. — Gallenkamp 3 cu. ft. £145. Also Morgan Grundy 1 cu ft. £55.  
20-WAY JACK SOCKET STRIPS. 3 pole type with two normally closed contacts £25.50 each (+25p pp). Type 316 three pole plugs for above — 20p ea. (pp free).

#### DC POWER SUPPLIES

\*APT 10459/8, 12-14V @ 5 Amps £25 (£2 p.p.)  
\*APT 10459/8, 24V @ 5 Amps £25 (£2 p.p.)  
\*We can supply the above power supply at any fixed voltage between 5V and 36V at 5A £25.  
\*Mullard Dual supplies. Brand new with handbook. Pos & Neg 12V at 1A and 0.4A respectively. Dimensions 9x4x5ins. £10 + (£1 p.p.)  
\*FARNELL Current limited. Dimensions 7x5x4ins. Following types available: 13-17 Volts @ 2A £15. 27-32 Volts @ 1A £15. 5V @ 3A £15. (pp £1.50).

#### SPECIAL PURCHASE LAMBDA POWER SUPPLIES

Excellent LXS Series DC power units at less than a tenth of new price.  
The snag? — they're all 110V AC input. Prices as follows:  
5V at 24A. LXS D5 0V R. £25. (List £350).  
15V at 12A. LXS D15 R. £20. (£339).  
5V at 14A. LXS CC 5 0V. £20. (£258).  
24V at 3.1A. LCS C 24. £15. (£223).

Carriage each £2.50 extra

#### MODULATION METERS

AIRMEC 210 3-300MHz. AM/FM. £125  
RADIOMETER AFM/1 3.5-320MHz. AM/FM. £145  
RACAL 409 3-600MHz. AM/FM.

#### ROTRON INSTRUMENT COOLING FANS

\* Supplied in excellent condition, fully tested:  
\* 115V, 4.5 x 4.5 x 1.5" £4.50. 230V £5. 115V, 3 x 3 x 1.5" £4 + postage ea. 35p.

CT212 RF Signal Generators. 85KHz-32MHz £55.

#### BELL & HOWELL MICROFICHE VIEWERS

\* Type SR5. Screen size 9 x 5" — New condition £75.

#### DIGITAL MULTI-METERS

DE FOREST ELECTRONICS TYPE MM200. DC 0-1KV. AC V 0-700. DC 9.0-1A. AC 1.0-1A.  
Each in 4 ranges. Resistance 0-19.99 Mohms. 5 ranges. LED Display 1999. BRAND NEW.  
SPECIAL REDUCED PRICE OF £39, INCLUDING VAT & P.P.

## P. F. RALFE ELECTRONICS

DEPT E&MM7, 10 CHAPEL STREET, LONDON NW1  
TELEPHONE: 01-723 8753

NOTICE. All the pre-owned equipment shown has been carefully tested in our workshop and reconditioned where necessary. It is sold in first-class operational condition and most items carry our three months' guarantee. Calibration and certificates can be arranged at cost. Overseas enquiries welcome. PLEASE ADD 15% VAT TO ALL PRICES.

THE MODERN BOOK COMPANY

Britain's Largest Stockist of British & American Technical Books

All Prices incl. postage

NEW 1981 MODERN ELECTRONIC CIRCUITS REFERENCE MANUAL by Markus Price: £32.50p

1001 THINGS TO DO WITH YOUR PERSONAL COMPUTER by M. Sawusch Price: £5.75

WORLD RADIO TV HANDBOOK 35th Annual Ed. Price: £10.50p

1981 THE RADIO AMATEUR'S HANDBOOK by ARRL Price: £8.00

THE CATHODE RAY OSCILLOSCOPE & ITS USE by G. N. Patchett £4.00

UNDERSTANDING HI FI SPECIFICATIONS by J. Earl Price: £3.50p

HIGH PERFORMANCELOUDSPEAKERS by M. Colloms Price: £7.00

AUDIO IC OP-AMP APPLICATIONS by W. G. Jung Price: £5.75p

NEWNES BOOK OF VIDEO by K. G. Jackson Price: £6.50p

HOROWITZ & HILL: THE ART OF ELECTRONICS Price: £13.50p

**THE MODERN BOOK CO.**  
15-21 PRAED STREET,  
LONDON W2 1NP. TEL: 01-402 9176  
(closed Saturday 1 p.m.)

# NEXT MONTH — August Issue

on sale at your newsagent from July 12th

## SIGNAL PROCESSOR

A professional quality audio control system for theatre and group P.A. use. Features include audio limiter, LED VU meters, 3-way active crossover and balanced line output.

## HEXADRUM

A six-tone touch sensitive 'electronic bongo' drum that is an ideal electro-music instrument for education, home and studio.

## POWERCOMP

Purpose-built power supply unit for driving microprocessor peripherals.

## MODEL CAR RACE STARTER

Useful accessory for model car racing enthusiasts. Creates real race atmosphere!

## CAR AERIAL BOOSTER

Basic but functional signal booster for AM/FM reception. Ideal for fringe areas or poor signal strengths.

## IRMIN SCHMIDT ON HIS TOY PLANET

This experienced and creative composer from 'Can' group discusses his electronic music techniques used on his superb 'Toy Planet' LP.

Plus our regular articles covering Electronic, Computing and Electro-Music.



Electronics & Music Maker is the first monthly publication to produce its own cassettes that will provide a unique aural complement to the magazine. Produced in our own recording studio, these C60 cassettes will allow you to hear the sound of instruments and electro-musical effects in our projects and reviews.

### Demo Cassette No. 1 (March/April issues) contains:

1. The sounds of the Matinée Organ.
2. Musical extracts played on the Yamaha SK20 Synthesiser reviewed last month.
3. Examples of the basic waveforms and effects discussed in 'Guide to Electronic Music Techniques'.
4. Music and sound effects played on the Sharp MZ-80K Microcomputer.
5. Warren Cann demonstrates the Syntom Drum Synthesiser.
6. The PAIA8700 Computer/Controller.
7. Frankfurt Music Fair: the Yamaha GS-1, Electro-Harmonix Clockworks Controller.

**Cassette Price: £2.45 inc. VAT and p&p.**

### Demo Cassette No. 2 (May/June issues) contains:

1. Tim Souster 'feature' examples from his electronic music studio.
2. Electronic Dream Plant: Adrian Wagner plays the Wasp/Spider and some of his music.
3. Lowrey MX 1 Electronic Organ — the essential music complement to the review!
4. Apple Music System — polyphonic computer music.
5. E&MM Word Synthesiser — speech from our friends in Texas.
6. Fairlight Computer Musical Instrument

## ELECTRONICS & MUSIC MAKER DEMONSTRATION CASSETTES

review — because of its price, very few have heard this amazing instrument.

7. Sharp 'Composer' and 'Morse' programs.
8. Yamaha PS20 keyboard — a complete piece on this portable play anywhere instrument.
9. Vero projects: Radio/Metronome/Oscillator 10. Some extraordinary sounds from the creative David Vorhaus.

**Cassette Price: £1.99 inc. VAT and p&p.**

**Demo Cassette No. 3 contains from this issue:**

1. The unique sounds of the new PPG Wave 2 synthesiser.
2. Synwave sea effects and other sound possibilities.
3. Wersi Pianostar — the versatile kit instrument demonstrated by German demonstrator Hady Wolff, who also shows some of the special sounds from the Wersi organ range.
4. Musical examples of the immense possibilities from the Alphadac 16 synthesiser controller.
5. Atari's new Music Cartridge programming 4-part compositions.
6. Duncay Mackay makes creative sounds from his 'Visa' LP keyboard set-up.

Next month's issue will also list further examples for Demo Cassette No. 3.

**Cassette Price: £1.99 inc. VAT and p&p.**



Please allow 28 days for delivery

E&MM Cassettes Dept., Maplin Publications, 282 London Road, Westcliff-on-Sea, Essex SS0 7JG

Please send me the following Demonstration Cassettes:

Cassette No.	Quantity	Price	Total
Demo Cassette 1 for (March/April issues)		£2.45	
Demo Cassette 2 for (May/June issues)		£1.99	
Demo Cassette 3 for (July/August issues)		£1.99	
			£

I enclose a cheque/postal order payable to: Electronics & Music Maker  
PLEASE PRINT

Name .....

Address .....

E&MM7/81

# CLASSIFIEDS

APPOINTMENTS - SERVICES - SALES - WANTS

### STUDIO HIRE

8 TRACK STUDIO INCLUDING SYNTHESISERS, FREE TEA and a handy musician/engineer, £20 per 6-hour session. Ideal for composers, synth players etc.

For full details catch DAVE on WAT-FORD 39347.

### FOR SALE

Clef "Joana" electronic piano; 5 octave, polyphonic, touch sensitive. £55. Telephone: Marlow 3186.

All types of Kits constructed (Maplin, Wersi, etc.). Competitive prices.

For quotation Ring Newtown (0686) 28646.

### HAVE YOU SEEN THE GREEN LIST?

1000s of components (electronic, audio, musical) plus electronic items and accessories at unbelievably low prices. Ideal for the Electronics and Music Hobbyist. Send 25p for list and receive FREE RECORD SPEED INDICATOR.

MYERS (Dept EM) 14-16 Clifton Grove, Leeds LS9 6EW. M.O. only.

Unique opportunity to acquire an established work-from-home organ service operation in the S.E. Turnover £15,000 P.A. rising. Full instruction given. Details: Box No. J1, E&MM, Hillcroft House, 16 The Avenue, Highams Park, London E4 9LD.

Roland JP-4 Jupiter Synth (new) List £1,889  
 Roland RS-505 Paraphonic Synth/Strings (new) List £1,229  
 Roland MP-700 Piano c/w amplifier (used) Last list £1,586  
 Roland EP-09 Piano, self amplified (new) List £399  
 Roland Revo 250 watt reverb keyboard amp/tremolo cabinet with 18" Pioneer speaker (new) Last list £995  
 All in mint condition. Total cost over £5,500. Accept £2,600 the lot or will split for sensible offers.

KEYBOARDS, The Headrow, Leeds 1  
 Telephone (0532) 468939



## ELECTRONICS & MUSIC MAKER

### TECHNICAL EDITOR

Additional staff are needed to join our editorial team to help us produce projects, features, news and reviews that make E&MM the No. 1 monthly for the electronics and music hobbyist.

We require immediately a TECHNICAL EDITOR having practical experience of electronic project design and construction, with responsibility for preparation of submitted projects for publication.

In addition, you will work with our projects team in researching and developing new designs for E&MM.

The salary for this important position will be commensurate with age and experience.

Please write, enclosing detailed C.V. to: The Editor, 282 London Road, Westcliff-on-Sea, Essex SS0 7JG.

## CLASSIFIED ADVERTISEMENTS

Attach your copy to this form and send to:

ELECTRONICS & MUSIC MAKER, Advertisement Dept., Hillcroft House, 16, The Avenue, Highams Park, London, E49LD.

Name .....

Address .....

Remittance value.....enclosed

**SPECIAL INTRODUCTORY OFFER**  
 Only £4.00 per single column centimetre for a Semi-Display. Cheques payable to Maplin Publications.

This size Adv. 1 cm single column £4.00

This size Adv.  
 3 cm x 2 columns  
 £24.00

This size Adv.  
 2 cm single column  
 £8.00

This Adv. size  
 8 cm single column  
 £32.00


This size Adv.  
 3 cm single column  
 £12.00

This size Adv.  
 4 cm x 2 columns  
 £32.00

# CLEF ELECTRONIC MUSIC

## MASTER RHYTHM

As published in Practical Electronics

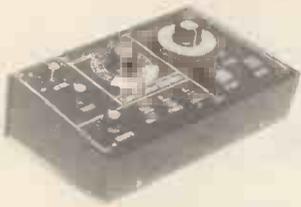

**FULLY PROGRAMMABLE  
TWENTY-FOUR PATTERNS  
EIGHT PARALLEL TRACKS  
TWELVE INSTRUMENTS  
SEQUENCE OPERATION**

Kit includes all components to build this comprehensive User Programmable Rhythm Generator in an attractive metal case with finished case, hardware and wire.

**KIT: £79 BUILT: £114**

### PIANOS

Specialists since 1972  
Stage and Domestic Types



The most advanced form of Touch Sensitive action simulating piano keyinertia by patented technique.

Four mixable voices for serious tone variation plus electronic chorus and flanger effects.

See lists for Cabinets, P.A. & Manu-  
7 1/4 Octaves £207  
7 1/2 Octaves £232

### STRINGS £174

Versatile String Synthesiser with split keyboard facility and impressive voices, 49 note organ diode keyswitch plus two-phase Chorus.

### ROTOR-CHORUS £89

Two-speed Rotor simulation plus Three Phase Chorus on a single 8" x 5" PCB. Mains PSU included.

### KEYBOARDS

Square Front with two hole actuator — easily cut.

**49 NOTE—£25; 73 NOTE—£41  
88 NOTE—£49.50**

### OUR PRICES INCLUDE VAT, CARRIAGE & INSURANCE

Please send s.a.e. for complete lists or use our telephone BARCLAYCARD service. Very competitive EXPORT rates — in Australia please contact JAYCAR in Sydney

**ALL INSTRUMENTS MAY BE SEEN IN OUR SHOWROOM**

**CLEF PRODUCTS (Electronics) LTD., Dept. M., E&MM/7  
44A BRAMHALL LANE SOUTH, BRAMHALL, STOCKPORT,  
CHESHIRE SK7 1AH. — TEL: 061-439 3297**

## LOOK TO THE FUTURE

by wearing a T-shirt with the special Electronics & Music Maker symbol.

These superior quality T-shirts have our symbol printed in white on the front, and come in red or black and S, M, L or XL sizes, price £2.75 inc. VAT & p&p. Sweatshirts are also available in the same colours and sizes, price £5.99 inc. VAT & p&p.

Overseas payments including Republic of Eire should be made by Bankers Draft in Pounds Sterling.

#### T-Shirt size guide:

S 28-34; M 34-36; L 36-40; XL 40-44

#### Sweat Shirt size guide:

S 30-34; M 36-38; L 38-42; XL 40-44

E&MM T-shirts Dept., Maplin Publications, 282 London Road, Westcliff-on-Sea.

Essex SS0 7JG. Please allow 28 days for delivery Subject to availability



Please send me:

	Red/Black	S/M/L/XL	Quantity	Price	Total
T-shirt				£2.75	
Sweatshirt				£5.99	
				£	

I enclose a cheque/postal order payable to: Electronics & Music Maker  
PLEASE PRINT

Name .....

Address .....

E&MM7/81

## ADVERTISERS INDEX

Ahktar .....	85	McKenzie .....	56
Ambit .....	45	Modern Book Co. ....	93
Aura Sounds Ltd .....	75	Phonosonics .....	79
Bi-Pak Semiconductors ...	34,35	PM Components .....	24
Boss Industrial Mouldings ...	39	T. Powell .....	Inside Back
J. Bull .....	71	Powertran .....	2,3,42
Clef Products .....	96	P. F. Ralph .....	93
Comp-Shop .....	Inside Front	J. W. Rimmer .....	53
Digisound Ltd .....	19	Rose Morris .....	76
Electronic Dream Plant .....	65	Silica Shop .....	49
Electro-Voice .....	89	Steve's Electronic Supply Co.	81
ILP .....	27,29	Tangerine .....	12,13
Kramer .....	76	Tempus .....	67
LB Electronics .....	83	Technomatic .....	61
L&B Electronics .....	33	TK Electronics .....	91
Linton Electronics .....	93	Turnkey .....	4
Maplin Electronic Supplies		Wilmslow Audio .....	77
.....	39,51	Yamaha (Kemble) .....	7
.....	Back Cover		

## CORRIGENDA

The following errors and omissions have been noted in previous issues of E&MM and are brought to your attention:

#### APRIL ISSUE

Page 30. Figure 2. R6, 7 and 8 should read R8, 6, 7.

#### MAY ISSUE

Pages 32 and 34. Test amp and Metronome pictures transposed.

Page 33 Figure 2. C5 should be connected to pin 1 of IC1 by wire link from D12 to F12.

Page 45 Figure 6. R3 should go to E1 not F1 as shown.

#### JUNE ISSUE

Page 13. Wire links shown on Wordmaker PCB have now been replaced by extra tracks on component side of PCB.


Page 64 Figure 6. C2 is shown reversed, S1 is shown reversed. Col 3, sentence beginning 'When S1 is in its normal position ...' should read: When S1 is in its normal position, the gate of TR1 is negative biased and the device presents a high resistance across its drain — source terminals.

Page 83. City of Fear and Synergy sleeve photos transposed.

Page 84 Col 3 Line 9 should be line not fine. Col 4 Line 36 should be Crotech not Growtech.
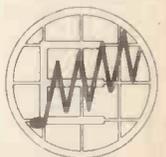
## BACK ISSUES

can be obtained from E&MM at £1 each (inc. postage)



**MARCH** Matinee Organ Pt. 1 \* Spectrum Synthesiser Pt. 1 \* Hi-Fi Sub-Bass Woofer \* Balanced line system \* Car battery monitor \* Yamaha SK20 review \* BBC Radiophonic Workshop

**APRIL** Syntom Drum Synthesiser \* Workshop Power Supply \* Car Ignition Timing Strobe \* Direct Inject Box \* Ultravox \* Paia 8700 review \* Matinee Pt. 2 \* Spectrum Pt. 2

**MAY** Noise Reduction Unit \* 6 Vero Projects \* Car Digital Rev Counter \* Lowrey MX-1 review \* Apple Music System \* Matinee Pt. 3 \* Spectrum Pt. 3

**JUNE** Wordmaker \* Guitar Tuner \* Hi-Fi/Group Mosfet amp \* Select-a-Match \* Fairlight CMI review \* David Vorhaus \* Matinee Pt. 4

# \* TEACH-IN FOR THE 80's \*

## ELECTRONICS CONSTRUCTION KITS

Electronics assembly is fast becoming the most fascinating and educational hobby for beginners of all ages. Monthly constructional projects, appear in most of the magazines in the hobbyist electronics field, with basic technical principles and symbols explained in great detail.

The sheer simplicity of these projects are a must for all beginners. Start with a hobby that could become a worthwhile career.

Our kits come complete with all parts as specified.

**\*ALL PROJECT KITS ARE SUPPLIED WITH CASES**

(except items marked \*).

All kits come complete with items; plus Texas IC sockets where required, also Veroboard connecting wire, etc.

Listed below is a selection of the many projects available.

Reprints are available at 40p extra.

### E&MM PROJECTS

Continuity Tester	ZF1	March 81	P.O.A.
Balanced Line System	ZF2	March 81	P.O.A.
Car Battery Monitor	ZF3	March 81	P.O.A.
The Syntom Drum Synthesiser	ZF4	April 81	P.O.A.
Car Ignition Timing Strobe	ZF5	April 81	P.O.A.
Direct Inject Box	ZF6	April 81	P.O.A.
Power Controller	ZF7	April 81	P.O.A.
Noise Reduction Unit	ZF8	May 81	P.O.A.
Car Digital Tachometer	ZF9	May 81	P.O.A.
Tone Generator (on Vero)	ZF10	May 81	P.O.A.
Test Amplifier (on Vero)	ZF11	May 81	P.O.A.
Metronome (on Vero)	ZF12	May 81	P.O.A.
Signal Mixer (on Vero)	ZF13	May 81	P.O.A.
Scratch Filter (on Vero)	ZF14	May 81	P.O.A.
MW Radio (on Vero)	ZF15	May 81	P.O.A.
Wordmaker Speech Synthesiser	ZF16	June 81	P.O.A.
Mosfet Amplifier	ZF17	June 81	P.O.A.
Select-A-Match	ZF18	June 81	P.O.A.
Guitar Tuner	ZF19	June 81	P.O.A.

Sound to Light	ZB127	Nov. 80	£19.00
Audio Effects Unit	ZB122	Oct 80	£12.25
Phone Call Charge Jogger	ZB121	Oct 80	£6.90
Darkroom Controller	ZB123	Oct 80	£17.25
Bicycle Alarm	ZB124	Oct 80	£9.25
Lights Failure Monitor	ZB77	Sept 80	£3.75
TTL Power Supply Unit	ZB78	Sept 80	£9.50
Duo-Deci Timer	ZB75	Sept 80	£8.50
TTL Logic Probe	ZB76	Sept 80	£3.25
Bedside Radio	ZB74	Sept 80	£14.25
Auto Lighting-Up Warning	ZB71	Aug 80	£5.65
Zener Diode Tester	ZB79	July 80	£5.00
Signal Tracer	ZB80	July 80	£5.00
General Purpose Amplifier	ZB81	July 80	£6.00
Voltage Converter	ZB82	July 80	£4.75
Autowaa	ZB83	July 80	£19.25
A.F. Signal Generator	ZB84	July 80	£20.00
Courtesy Light Delay	ZB85	July 80	£5.25
Auto Phase	ZB86	July 80	£19.25
Battery Voltage Monitor	ZB64	May 80	£4.80
Lights Warning System	ZB63	May 80	£3.60
Autofade	ZB66	May 80	£10.25
Audio Tone Generator	ZB67	May 80	£3.50
*Pre-tuned 4-Station Radio	ZB62	May 80	£14.00
Automatic Level Control	ZB60	April 80	£8.00
Cable and Pipe Locator	ZB54	March 80	£3.75

Stereo Headphone Amplifier	ZB57	March 80	£15.25
Doorbell Register	ZB58	March 80	£3.60
Kitchen Timer	ZB55	March 80	£12.75
Touch Switch	ZB56	March 80	£9.00
Micro Music Box	ZB45	Feb 80	£17.00
Simple Short Wave Receiver	ZB44	Feb 80	£18.00
Morse Practice Oscillator	ZB43	Feb 80	£6.00
Slide/Tape Synchroniser	ZB42	Feb 80	£11.50
Power Supply 3-9V	ZB47	Jan 80	£4.50
Burglar Alarm	ZB51	Dec 79	£5.00
Baby Alarm	ZB40	Nov 79	£8.50
Opto Alarm	ZB41	Nov 79	£5.00
Radio Tuner MW/LW	ZB108	Nov 79	£14.75
3-Function Generator	ZB52	Nov 79	£25.00
One Armed Bandit	ZB33	Oct 79	£21.00
Lights-on Reminder	ZB34	Oct 79	£4.60
Signal Level Indicator	ZB36	Oct 79	£4.50
Chaser Light	ZB4	Sept 79	£17.50
Lower Power Audio Amplifier	ZB3	Sept 79	£3.75
Simple Transistor Tester	ZB2	Sept 79	£5.50
Varicap MW Radio	ZB1	Sept 79	£8.50
Trailer Flasher	ZB9	Aug 79	£3.00
Electronic Tuning Fork	ZB7	Aug 79	£8.90
Power Supply 9V	ZB6	Aug 79	£3.25
Warbling Timer	ZB5	Aug 79	£6.40
Water Level Indicator	ZB111	July 79	£4.50
Darkroom Timer	ZB17	July 79	£3.50
Electronic Canary	ZB19	June 79	£4.50
Tremolo Unit	ZB18	June 79	£10.00
Electronic Dice	ZB24	May 79	£13.50
Intruder Alarm	ZB23	May 79	£23.00
Touch Bleeper	ZB27	April 79	£3.25
Transistor Tester	ZB100	April 79	£4.00
One Transistor Radio MW/LW	ZB104	March 79	£7.25
Time Delay Indicator	ZB98	March 79	£4.00
Micro Chime	ZB96	Feb 79	£12.00
Lights Reminder for Car	ZB32	Jan 79	£4.50
Headphone Enhancer	ZB101	Jan 79	£4.00
Continuity Tester	ZB115	Jan 79	£4.30
Fuzz Box	ZB106	Dec 78	£5.00
Vehicle Immobiliser	ZB110	Dec 78	£5.00
Audio Effects Oscillator	ZB109	Nov 78	£3.50
Radio MW/LW	ZB116	Oct 78	£7.00
Sound to Light	ZB112	Sept 78	£7.00
Guitar Tone Booster	ZB117	Sept 78	£5.00
A.F. Signal Generator	ZB119	Aug 78	£10.00
Weird Sound Effects Generator	ZB113	March 78	£3.50
Catch-a-Light	ZB102	March 78	£6.00
Chaser Light Display	ZB97	Feb 78	£22.00
Car System Alarm	ZB92	Feb 78	£4.50

**PERSONAL CALLERS PLEASE RING TO CHECK AVAILABILITY OF KITS  
ALL PRICES INCLUDE POST PACKING AND 15% V.A.T.**

### IONISER KIT ZD13

This negative ion generator gives you power to saturate your home or office with millions of refreshing ions. Without fans or moving parts it puts out a pleasant breeze. A pure flow of ions pours out like water from a fountain, filling your room. The result? Your air feels like fresh ocean air, pure crisp and wonderfully refreshing.

All parts PCB and full instructions £12.50. A suitable case including front panel, neon switch, etc. Available at £10.50.

**CALLERS BY APPOINTMENT ONLY**

HOURS: Mon-Fri 9.00-5.30 p.m. Sat. 9.00-4.30 p.m.

# T. POWELL

ADVANCE WORKS, 44 Wallace Road  
London N1. 01-226 1489

HOURS  
MON FRI 9 5 30 PM  
SAT 9 4 30 PM



ORDERS  
ADD 30p POST/PACKING  
ADD 15% VAT TO TOTAL

Minimum telephone Orders £5.00  
Minimum Mail Order £1.00

# MAPLIN make it easy



in  
**SOUTHEND**  
284 London Road  
Westcliff-on-Sea  
Essex  
Tel: (0702) 554000  
(Closed Mondays)



in  
**HAMMERSMITH**  
159-161 King Street  
Hammersmith  
London W6  
Tel: 01-748 0926  
(Closed Mondays)

For personal service visit one of our stores.  
Our new store at Hammersmith is conveniently situated near the end of the M4 and the North and South Circular Roads. There is excellent street parking on meters a few steps away and Hammersmith Underground Station is nearby. Call in and see us soon.



in our  
**CATALOGUE**

320 big pages packed with data and pictures of over 5,500 items

Over 100,000 copies sold already!  
Don't miss out on your copy.

On sale now in all branches  
WH Smith  price £1.

In case of difficulty check the coupon below.

**by MAIL ORDER**  
A fast service you can rely on

- \* Same day service on in-stock lines
- \* Very large percentage of our stock lines in stock
- \* All prices include VAT
- \* Large range of all the most useful components
- \* First class reply paid envelope with every order
- \* Quality components—no rejects—no re-marks
- \* Competitive prices
- \* Your money is safe with a reputable company

On price, service, stock, quality and security it makes sense now more than ever to make **MAPLIN** your first choice for components every time!

## make it easy... with MAPLIN

The **Maplin Matinée**  
Amazing value for only £229.95 plus £99.50 for cabinet if required

Easy to build, superb specification. Comparable with organs selling for up to £1,000. Full construction details in Electronics & Music Maker commencing March, 1981 issue. Back numbers available.



**MAPLIN** ELECTRONIC SUPPLIES LTD.

### Post this coupon now.

Please send me a copy of your 320 page catalogue. I enclose £1.25 (incl. 25p p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the U.K. send £1.68 or 12 International Reply Coupons.

Name \_\_\_\_\_

Address \_\_\_\_\_

All mail to: P.O. Box 3, Rayleigh, Essex SS6 8LR. Tel: Southend (0702) 554155 Sales: (0702) 552911