

electronics today

The background of the cover is a dark, starry space. A rocket with a white and red body is ascending from the bottom left towards the top center. In the bottom right, a yellow spaceship with a curved, metallic body is shown, appearing to be in a dynamic maneuver or firing. The overall aesthetic is that of a classic science fiction magazine cover from the late 1970s.

APRIL 1979

INTERNATIONAL

50p

**3080
Circuits**

**Amplifier
Module
Survey**

**Videograph
AMBUSH**

... NEWS

PROJECTS . . .

MICROPROCESSORS

ADVERTISING

CHROMATHEQUE 5000

5 CHANNEL LIGHTING EFFECTS SYSTEM

All kits are available as complete kits or as P.C.B. component sets. See page 10 for prices in FREE CATALOGUE.



This versatile system featured as a user's choice in ELECTRONICS TODAY INTERNATIONAL has five channels with individual level controls on each channel. Control of the lights is independent of the sound. The local 'mix' control for use with the mixer is a superbly rugged and sequenced effects. Each channel handles up to 500W and as the kit is a PCB design it is a superbly rugged construction. The kit includes fully featured manual and automatic 'B' controls, with a sound down to 100Hz and a high pass filter.

**COMPLETE KIT
ONLY
£49.50 + VAT!**

MPA 210

100 WATT (fits into 19") MIXER/AMPLIFIER



**COMPLETE KIT
ONLY
£48.90 + VAT!**

Required by a leading hi-fi store for its hi-fi system, the MPA 210 is a superbly rugged and sequenced general purpose rugged high power amplifier with a built-in mixer. It is a superbly rugged and sequenced general purpose rugged high power amplifier with a built-in mixer. It is a superbly rugged and sequenced general purpose rugged high power amplifier with a built-in mixer.

Kit includes fully featured manual and automatic 'B' controls, with a sound down to 100Hz and a high pass filter. Complete kit down to 100Hz and a high pass filter. Complete kit down to 100Hz and a high pass filter.

Power amp mode. £10.60 + VAT

Custom design, 100Watt, 19" format, 100Watt, 19" format. £10.50 + VAT

Parts for power supply only (caps, rectifier, fuses, F holders) £3.40 + VAT

TRANSCENDENT 2000

SINGLE BOARD SYNTHESIZER


LIVE PERFORMANCE SYNTHESIZER DESIGN BY CONSORT TIM ORR (FORMERLY SYNTHESIZER DESIGNER FOR EMS LIMITED) AND FEATURED AS A CONSTRUCTION ARTICLE IN ELECTRONICS TODAY INTERNATIONAL. TRANSCENDENT 2000 is a 2 octave instrument transposable 2 octaves up or down giving an effective 2 octave range. There is portamento, pitch bending, a VCO with shape and pitch control, a VCF with low and high pass outputs and a separate dynamic sweep control, a noise generator and an ADSR envelope shaper. There is also a slow or fast attack, a retrigger for ADSR repeat, sample and hold, and special circuitry with precision components to ensure tuning stability amongst its many features.

Kit includes fully featured manual and automatic 'B' controls, with a sound down to 100Hz and a high pass filter. Complete kit down to 100Hz and a high pass filter. Complete kit down to 100Hz and a high pass filter.

**COMPLETE KIT
ONLY
£172.00 + VAT!**

Comprehensive handbook supplied with all complete kits! The fully detailed construction and info you need to set up your synthesizer with nothing more elaborate than a multi meter and a pair of ears!

POWERTRAN

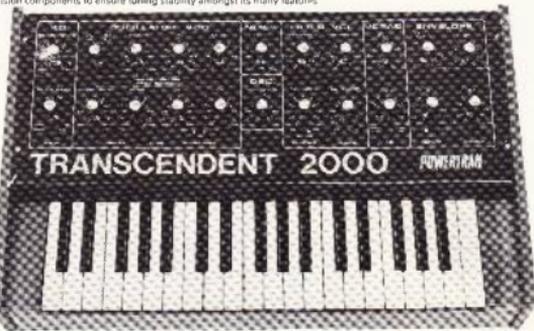

Cabinet size 24 6/8" x 15 7/8" x 4 8/8" (rear) 3 4" (front)

**ORDERING INFORMATION
AND MORE KITS ON PAGE 8**

electronics today


APRIL 1979 VOL 8 NO 4 INTERNATIONAL



To Boldly Go . . . p61



Beats Crossroads . . . p27

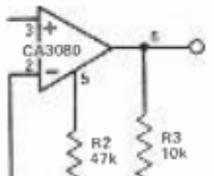

How To Use It! . . . p70

FEATURES

- NEWS DIGEST **9** Did you know
- POWER AMP SURVEY **19** Power to the people
- Gm REVISED **37** New life for an old idea
- DATA SHEET **52** C survey
- READERS DESIGNS **54** Your designs built
- TEN 308D CIRCUITS **70** It does more than you think
- MICROFILE **80** A floppy pet
- TECH TIPS **103** Circuits from you to you

PROJECTS

- VIDEOGRAPH **27** Sound to light on your telly
- CLICK ELIMINATOR **41** Clean up your records
- AMBUSH **61** The new space game with sounds
- WIND SPEED INDICATOR **85** Get the wind up this unit
- GUITAR EFFECTS UNIT **97** We think we've found a new one for you
- PCB FOIL PATTERNS **110** All in one place now

INFORMATION

- BOOK SERVICE **25** You name it, we have a book on it
- HOBBY ELECTRONICS PREVIEW **35** On its way to you
- ETI PRINTS **49** For DIY PCB's
- MARKET PLACE **58** Can you beat these prices?
- ETI SPECIALS **69** Specially for you
- COMPUTING TODAY **83** On its own now
- NEXT MONTH IN ETI **90** What we've got for May

EDITORIAL AND ADVERTISEMENT OFFICE
25 27 Oxford Street London W1R 1RF Telephone 01 434 1781/2 Telex 8811896

INTERNATIONAL EDITIONS

- AUSTRALIA Collyn Rivers
Publisher
Les Bell
Acting Editor
- Holland Anton Kriegerman
Editor-in-Chief
- CANADA Steve Bradwood
Editor
Graham Videman
Assistant Editor
- GERMANY Udo Witting
Editor

- Ron Harris B Sc Editor
- Rick Maybury Ian Graham B Sc Henry Budgett Editorial Assistants
- Diego M Rincon Art Director
- Pete Howells Production Editor
- Paul Edwards Tony Strakas Technical Illustrators
- Ray Marston Project Editor
- John Friggeraid Project Engineer
- Steve Ramsahadoo Project Development
- Margaret Hewitt Administration
- Alen Carlton (Managed) Kim Hamlin Reader Services
- Bren Goodwin Tim Salmer Advertising
- Christopher Surgenor (Manager) David Sinfeld Joy Cheshire Halma Di Lallo Editorial Director
- Halvor Moorhead



ABC


PUBLISHED BY Modnags Ltd 25 27 Oxford Street
DISTRIBUTED BY Argus Distribution Ltd (British Isles)
Gordon & Gorch Ltd (Overseas)
PRINTED BY OB Limited Colchester

Electronics Today International is normally published on the first Friday of the month prior to the cover date

COPYRIGHT All material is subject to world wide Copyright protection. All reasonable care is taken in the preparation of the magazine to ensure accuracy but ETI cannot be held responsible for it legally. Where errors do occur a correction will be published as soon as possible afterwards.

POWERTRAN



PSI 4002 STUDIO MODEL

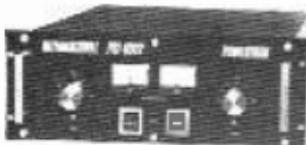

Overall size 17.2 x 17.2 x 8.2

COMPLETE KIT ONLY €196.90 + VAT

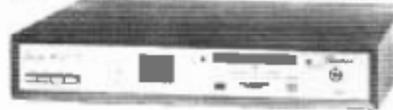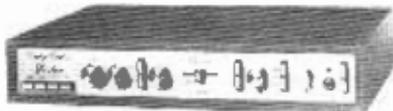READ THE REVIEW
IN SOUND INTERNATIONAL DEC. '78!



T20 + 20 20W STEREO AMPLIFIER €33.10 + VAT

This kit based on a design published in Practical Wireless uses a single or paired circuit board and offers a very low cost, state of the art kit on all the normal frequencies. It is built to meet the 4.33 mhz + 100khz tolerance of 200 kHZ per channel.

POWERTRAN SFMT TUNER €35.90 + VAT

This is a simple low cost design which can be modified to meet any of the normal frequencies. It is built to meet the 4.33 mhz + 100khz tolerance of 200 kHZ per channel. The kit is built to meet the 4.33 mhz + 100khz tolerance of 200 kHZ per channel.

WWW TUNER €47.70 + VAT

This is a simple low cost design which can be modified to meet any of the normal frequencies. It is built to meet the 4.33 mhz + 100khz tolerance of 200 kHZ per channel. The kit is built to meet the 4.33 mhz + 100khz tolerance of 200 kHZ per channel.

COMPLETE KITS. On completion of the kit, the amplifier will be ready to use. It is built to meet the 4.33 mhz + 100khz tolerance of 200 kHZ per channel.

All of the kits shown in this page are available as separate products except the Power 4002 ST. It is built to meet the 4.33 mhz + 100khz tolerance of 200 kHZ per channel.

PRICE STABILITY. The price of the kits is stable and will not increase. It is built to meet the 4.33 mhz + 100khz tolerance of 200 kHZ per channel.

EXPORT ORDERS. No VAT. Foreign charges are extra. It is built to meet the 4.33 mhz + 100khz tolerance of 200 kHZ per channel.

SECURITY. The kits are built to meet the 4.33 mhz + 100khz tolerance of 200 kHZ per channel.

SALES DELIVERY. The kits are built to meet the 4.33 mhz + 100khz tolerance of 200 kHZ per channel.

FOR ELECTRONIC KITS OF DISTINCTION

200+ 200 watt AMPLIFIER

As featured in Electronics Today International

400W rms continuous — 800W peak!

0.03% THD at FULL power!

PLUS all the following features too!

- Each channel is a very independent 100 watt stereo channel
- Impedance matched to the speaker
- Ultra low frequency noise in the audio path
- Professional quality components
- Easy to build
- All the normal features of a high quality amplifier

DE LUXE EASY TO BUILD LINSLEY HOOD 75W STEREO AMPLIFIER €99.30 + VAT


This is a simple low cost design which can be modified to meet any of the normal frequencies. It is built to meet the 4.33 mhz + 100khz tolerance of 200 kHZ per channel.

WIRELESS WORLD FM TUNER €70.20 + VAT

This is a simple low cost design which can be modified to meet any of the normal frequencies. It is built to meet the 4.33 mhz + 100khz tolerance of 200 kHZ per channel.

LINSLEY-HOOD CASSETTE DECK €79.60 + VAT

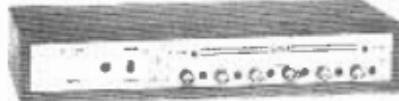This is a simple low cost design which can be modified to meet any of the normal frequencies. It is built to meet the 4.33 mhz + 100khz tolerance of 200 kHZ per channel.



OUR CATALOGUE IS FREE! WRITE OR PHONE NOW!

POWERTRAN ELECTRONICS

PORTWAY INDUSTRIAL ESTATE
ANDOVER HANTS SP10 3NN

ANDOVER
(STD 0264) 84455

news digest.....



COME UP AND SEE ME

A new model of the far flung pocket bleeper will be keeping athletes on their toes at the Moscow Olympics.

Multitone's new RB111 receiver uses a combination of single digit numerical display with a choice of eight audible codes to convey more information than any other long range receiver on the market.

The receiver also has a memory. In a meeting far in distance where direct sound would be unusable, call information can be stored and recalled after the meeting.


Ten remote control units will be used in Moscow to send out

messages and all information can be displayed on a monitor or printed out.

Each remote controller has a conventional pad of ten keys for entering numerical information and four keys enabling one of four call codes to be selected.

Additionally, a deafening alert call can be sent to a group of receivers. Another group of keys allows calls to be transferred automatically to any other designated receiver. There are also batteries check and out of range warning buttons. Multitone Electronic Company Ltd, 10 28 Ludlow Street, London N1 7JF.


GLOW BAR

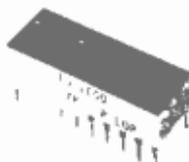

The new RGB 1800 from Hitronix is a red 10 element linear bar display in a compact long 20 pin DIL package. Individual addressable anodes and cathode and intensity colour coding for displays uniformly are featured. At 20 mA typical

minimum intensities for display and element are 5 and 0.5 mcd respectively. Suggested applications include solid state meters and positional indicators. Details from Hitronix Inc, 25 Churchgate Hitchin, Herts, SG1 5JN.

CALL FOR ANALYSIS?

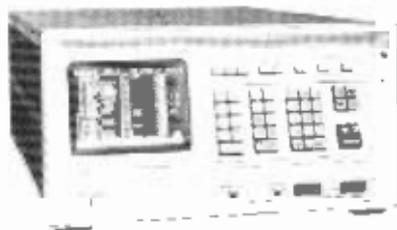

Hewlett Packard's new HP-3779 is a microprocessor based instrument for checking multiplexed telephone equipment. The scope-size unit replaces two large racks of test gear and automatically displays its results in minutes rather than days.

Over forty different measurements from gain to intelligible cross-talk and local alarms can be assembled into a test sequence defined by the user.

The results are displayed in tabular form on the instrument's own CRT. The information can be fed to a computer or printer through an integral IEEE 488 (HP-IB) digital interface.

The analyzer is produced in two models — the 3779A for the 3779B Europe and the 3779B for Bell system users. Further details from Hewlett Packard Ltd, King Street Lane, Winsors, Worthingham, Berkshire RG11 5AR.

TELETEXT — A LOAD OF RUBBISH ...

THE most irritating aspect of teletext from the viewer's standpoint is trying to decipher the occasional sentence or word on a page that may look like this example. This week's premium bond winner is "1311". The above statement emphasizes a need for a device which could eliminate these annoying factors usually raised by multipath reception problems. A new large scale integrated circuit developed by Toshiba and NHK has proved successful in attenuating 'ghosts' of up to 27 dB delay by a reduction of up to 30 dB.

The principal method of circuit operation is as follows: The circuit examines the ordinarily stable intervals between equalising pulses in the composite video required to determine the presence of ghost images. They would actually appear as smaller trailing pulses. Through multiplexing and analog memory techniques, voltages accurately derived from the amplitude and amount of delay of the ghost pulses are applied to vary the gain on each of the 64 MOSFET weighting circuits fed in parallel

with a sample of the video signal. These outputs of the weighting circuits in turn feed 64 CCD delay lines each having a pre-determined delay time. The outputs of the delay lines are added and then applied as negative feedback to the composite video signal in a form having sufficient amplitude and delay to cancel the ghosts.

Do not however expect to see this ghost eliminator available just yet. It is still many months from the full production. GERALD CHEVIN

AND ALSO ...

An enterprising American TV station has finally decided to write a software package allowing American teletext to link up with British Videotext.

What is believed to be the first US attempt to interface the two systems, station KSL-TV (Salt Lake City) hopes to use the combination of the two systems to store and edit incoming US international wire copy in its General Automation 16 440 computer.

WATFORD ELECTRONICS

33/35 CARDIFF ROAD, WATFORD, HERTS, ENGLAND
MAIL ORDER, CALLERS WELCOME.
Tel. Watford 3881/9

ALL DEVICES BRAND NEW FULL SPEC. AND FULLY GUARANTEED. CASH ON DELIVERY. RETURNS OF POST. TERMS OF BUSINESS: CASH ON DELIVERY. FOR OR BANKERS: 28 GREAT NORTH STREET, WATFORD, HERTS. INSTITUTIONS: OFFICIAL OFFICERS ACCEPTED. TRADE AND EXPORT INQUIRY WELCOME. P.P.S. ADD 20p TO ALL ORDERS UNDER £10. OVERSEAS ORDERS: POSTAGE AT COST. AIR SURFACE. SEND 50p TO 23p FOR OUR CATALOGUE

VAT 1968 orders on V.A.T. Apply rates to U.K. customers only. United States orders at prices plus excise duties at 10%. Please add 2 1/2% by airpost insured. A 1% rate add 10 1/2%.

1968 (Residence) orders on V.A.T. 1968 orders on V.A.T. are exempted under Watford's Central District. Watford's Unincorporated 1968. Watford's High Street. Watford's High Street. Watford's High Street. Watford's High Street.

RESISTORS 1/2W 1/4W 1/8W 1/16W 1/32W 1/64W 1/128W 1/256W 1/512W 1/1024W 1/2048W 1/4096W 1/8192W 1/16384W 1/32768W 1/65536W 1/131072W 1/262144W 1/524288W 1/1048576W 1/2097152W 1/4194304W 1/8388608W 1/16777216W 1/33554432W 1/67108864W 1/134217728W 1/268435456W 1/536870912W 1/1073741824W 1/2147483648W 1/4294967296W 1/8589934592W 1/17179869184W 1/34359738368W 1/68719476736W 1/137438953472W 1/274877906944W 1/549755813888W 1/1099511627776W 1/2199023255552W 1/4398046511104W 1/8796093022208W 1/17592186044416W 1/35184372088832W 1/70368744177664W 1/140737488355328W 1/281474976710656W 1/562949953421312W 1/1125899906842624W 1/2251799813685248W 1/4503599627370496W 1/9007199254740992W 1/18014398509481984W 1/36028797018963968W 1/72057594037927936W 1/14411518807585584W 1/28823037615171168W 1/57646075230342336W 1/115292150460684672W 1/230584300921369344W 1/461168601842738688W 1/922337203685477376W 1/1844674407370954752W 1/3689348814741909504W 1/7378697629483819008W 1/14757395258966378016W 1/29514790517932716032W 1/59029581035865432064W 1/118059162071730864128W 1/236118324143541728256W 1/472236648287083456512W 1/944473296574166913024W 1/188894659314833226048W 1/3777893186296664521984W 1/7555786372593329043872W 1/15111572745186658087744W 1/30223145490373316175488W 1/60446290980746632350976W 1/120892581961492646701952W 1/241785163922985293403904W 1/483570327845970586807808W 1/9671406556919411736155616W 1/19342813113838823523111232W 1/38685626227677647047222464W 1/77371252455355294094444928W 1/15474250491071058188888864W 1/30948500982142116377777732W 1/6189700196428423275555544W 1/12379400392456846551111188W 1/247588007849137733111111176W 1/495176015698275466222222352W 1/990352031396550932444444704W 1/19807040627931018648888881408W 1/39614081255862037297777772816W 1/7922816251175240759555555557132W 1/15845632503550481519111111114264W 1/31691265007100963238222222228512W 1/63382530014210186466444444447024W 1/12676506002842037293333333334048W 1/25353012005684074586666666668096W 1/5070602400113680151733333333316192W 1/1014120480022760303466666666632384W 1/2028240960045520606933333333364768W 1/40564819200910401212666666666129536W 1/81129638400182082424253333333259072W 1/162259276800364164848486666666518144W 1/324518553600728329696969999991036288W 1/6490371072001456659393939999992072576W 1/129807421440029133187878789999994145152W 1/25961484288005826637575759999998291024W 1/51922968576001165337537539999996582048W 1/103845937152002330675375399999913164096W 1/2076918743040046613507537599999926328192W 1/415383748608009322701507599999952656384W 1/83076749221600186444030150999999105312768W 1/16615349843320037288806030150999999210625536W 1/332306996866400745776120603015099999942125072W 1/664613993732800149155240120603015099999984250144W 1/132922798746560029831048040120603015099999916850288W 1/26584559749312005966209608040120603015099999933700576W 1/53169119498624001193241921608040120603015099999967401152W 1/1063382389972480023664838432016080401206030150999999134802284W 1/2126764779944960047329676864032016080401206030150999999269604568W 1/42535295598899200946593536128032016080401206030150999999539209136W 1/8507059119779840018930870722560640160804012060301509999991078418272W 1/170141182395596800378617444512801280160804012060301509999992156836544W 1/340282364791193600757234889025602560160804012060301509999994313670088W 1/6805647295823872001514479681812512801280160804012060301509999998627341776W 1/13611294581647744003028957763625256025601608040120603015099999917254683552W 1/2722258963329548800605791545525128012801608040120603015099999934509371104W 1/54445179266590976001211583091090256025601608040120603015099999969018742208W 1/108890358133181952002423166218181280128016080401206030150999999138037484416W 1/21778071626636390400484633236363628012801608040120603015099999927607496832W 1/43556143253272780800969266472727256012801608040120603015099999955214993664W 1/87112286506545561600193852929292560128016080401206030150999999110429983296W 1/17422457101311123200387705858585560128016080401206030150999999220859966592W 1/3484491420262224640077541171717560128016080401206030150999999441719333184W 1/69689828405244492800155082353535560128016080401206030150999999883438666768W 1/13937965681048897600310164707070560128016080401206030150999999176687333536W 1/27875931362097795200620329414141560128016080401206030150999999353374667072W 1/557518627241955904001240658822828256012801608040120603015099999970674934144W 1/111503725443911180800248131765656556012801608040120603015099999914134868288W 1/223007450887822361600496263531313560128016080401206030150999999282697365776W 1/44601490177644472320099252666666560128016080401206030150999999565394731552W 1/892029803552889446400198505333335601280160804012060301509999991130789471104W 1/178405960710577892800397010666665601280160804012060301509999992261578942208W 1/3568119214211557856007940213333356012801608040120603015099999945231578944416W 1/713623842842311515520158804266666560128016080401206030150999999904631578948832W 1/14272476568462311515520317600933333560128016080401206030150999999180927157899664W 1/2854495313692462311515520635201866666560128016080401206030150999999361854315799328W 1/570899062738492462311515521270417333335601280160804012060301509999997237086315846752W 1/1141798125476949246231151552254082933333560128016080401206030150999999144741726315893504W 1/22835962509538994924623115155250816666665601280160804012060301509999992894834515947008W 1/4567192501907798984924623115155210163333335601280160804012060301509999995789669015994016W 1/9134385003815597979849246231151552203266666656012801608040120603015099999911479338016088032W 1/1826877000763119597979849246231151552406533333356012801608040120603015099999922958676016176064W 1/365375400152623919597979849246231151552813066666656012801608040120603015099999945917352016272128W 1/73075080030524783919597979849246231151552162613333333560128016080401206030150999999918354704016344256W 1/146150160061049567839195979798492462311515523252266666656012801608040120603015099999918354704016344256W 1/292300320012209139195979798492462311515526505333333356012801608040120603015099999936660708016388512W 1/58460064002441827839195979798492462311515521301066666656012801608040120603015099999973321416016437024W 1/116920128004883655567839195979798492462311515522602133333333560128016080401206030150999999146642832016474048W 1/23384025600976731111391959797984924623115155252042666666656012801608040120603015099999929328564016548096W 1/467680512001953422227839195979798492462311515521040853333333356012801608040120603015099999958657128016596192W 1/93536102400390684444567839195979798492462311515522081706666666560128016080401206030150999999117234136016672384W 1/18707220480078136888811391959797984924623115155241634133333333560128016080401206030150999999234468272016744768W 1/374144409601562737777227839195979798492462311515528326846666666560128016080401206030150999999468936944016889536W 1/7482888192031254755554556783919597979849246231151552166536933333333560128016080401206030150999999937873888016979072W 1/14965776384062511911111111391959797984924623115155233307386666666560128016080401206030150999999187547776017058144W 1/299315527681250238222222227839195979798492462311515526661475533333333560128016080401206030150999999375095552017116288W 1/5986310553625004764444444456783919597979849246231151552133219106666666560128016080401206030150999999750191104017132576W 1/119726211072050095288888888113919597979849246231151552266438213333333335601280160804012060301509999991500382208017165152W 1/2394524224010019057777777722783919597979849246231151552532764266666666560128016080401206030150999999300076441617170304W 1/4789048448020038115555555545567839195979798492462311515521065528533333333356012801608040120603015099999960015288320171740688W 1/957809689604007623111111111111391959797984924623115155221311170666666665601280160804012060301509999991201305760171780136W 1/19156193792080152422222222222278391959797984924623115155242622133333333335601280160804012060301509999992402611520171796272W 1/383123875840164844444444444456783919597979849246231151552852442666666665601280160804012060301509999994805223040171796272W 1/7662477516803296888888888888113919597979849246231151552170488466666666560128016080401206030150999999960104480171796272W 1/1532495503360659377777777777227839195979798492462311515523409769333333333560128016080401206030150999999192196960171796272W 1/306499100672131875555555555455678391959797984924623115155268195386666666560128016080401206030150999999384393920171796272W 1/6129982013443437511111111111113919597979849246231151552136390766666666560128016080401206030150999999768787840171796272W 1/12259964026868751111111111111111391959797984924623115155227278153333333333560128016080401206030150999999153757680171796272W 1/2451992805373751111111111111111113919597979849246231151552545563066666666560128016080401206030150999999307515360171796272W 1/4903985610747511111111111111111111391959797984924623115155210911273333333333560128016080401206030150999999614706720171796272W 1/980797122149501111111111111111111139195979798492462311515522182244666666665601280160804012060301509999991229413440171796272W 1/1961594242990011111111111111111111391959797984924623115155242448933333333335601280160804012060301509999992458826880171796272W 1/3923188485980011111111111111111111391959797984924623115155284897866666666560128016080401206030150999999491765440171796272W 1/7846376971960011111111111111111111391959797984924623115155216979533333333333560128016080401206030150999999983530880171796272W 1/15692753943920011111111111111111111391959797984924623115155233959066666666560128016080401206030150999999196761760171796272W 1/31385507887840011111111111111111111391959797984924623115155267918133333333333560128016080401206030150999999393563520171796272W 1/627710157756800111111111111111111113919597979849246231151552135836266666666560128016080401206030150999999787127040171796272W 1/12554203151376001111111111111111111139195979798492462311515522716725333333333356012801608040120603015099999915742480171796272W 1/25108406302752001111111111111111111139195979798492462311515525433456666666656012801608040120603015099999931484960171796272W 1/502168126055040011111111111111111111391959797984924623115155210866913333333333356012801608040120603015099999962969920171796272W 1/10043362521008001111111111111111111139195979798492462311515522173381866666666560128016080401206030150999999125939840171796272W 1/200867250420160011111111111111111111391959797984924623115155243576373333333333560128016080401206030150999999251879680171796272W 1/401734500840320011111111111111111111391959797984924623115155287154753333333333560128016080401206030150999999503759360171796272W 1/803469001680640011111111111111111111391959797984924623115155217430950666666665601280160804012060301509999991007518720171796272W 1/160693803361280011111111111111111111391959797984924623115155234861901333333333335601280160804012060301509999992015037440171796272W 1/32138760672256001111111111111111111139195979798492462311515526972362666666665601280160804012060301509999994030074880171796272W 1/64277521344512001111111111111111111139195979798492462311515521394472533333333335601280160804012060301509999998060149760171796272W 1/128555042688824001111111111111111111139195979798492462311515522789445066666666560128016080401206030150999999161203520171796272W 1/257110085377648001111111111111111111139195979798492462311515525578890133333333333560128016080401206030150999999322407040171796272W 1/51422017075529600111111111111111111113919597979849246231151552111577801666666666560128016080401206030150999999644814080171796272W 1/102844034151059200111111111111111111113919597979849246231151552223155601333333333333560128016080401206030150999999128962880171796272W 1/2056880683021184001111111111111111111139195979798492462311515524463112066666666656012801608040120603015099999925792560171796272W 1/411376136604236800111

ATFORD ELECTRONICS

ILP MODULES 15-240 WATTS

We are now stocking the most popular, 24" guaranteed 12-month warranty on all modules. For prices, prices & Power Supplies

HY1	Power Amp. Input - approx. peak-to-peak 200mV Output - 150W RMS, Distortion 0.1% at 1kHz	Price £8.27
HY30	Amplifier for 15 Watts into 8Ω, approx. 400mV rms continuous. Output 150W RMS, Distortion 0.1% at 1kHz	Price £8.27
HY50	4 x 400mV rms into 8Ω, approx. 400mV rms continuous. Output 150W RMS, Distortion 0.1% at 1kHz	Price £8.18
HY120	Amplifier Module - 80 Watts into 8Ω, approx. 400mV rms continuous. Output 150W RMS, Distortion 0.1% at 1kHz	Price £18.98
HY200	4 x 400mV rms into 8Ω, approx. 400mV rms continuous. Output 150W RMS, Distortion 0.1% at 1kHz	Price £27.98
HY400	80 Watts into 8Ω, approx. 400mV rms continuous. Output 150W RMS, Distortion 0.1% at 1kHz	Price £38.00

POWER SUPPLIES

100W	12V	£5.64
150W	12V	£6.18
200W	12V	£16.08
250W	12V	£18.10
300W	12V	£25.42

JACK PEGS		SOCKETS		SWITCHES		SLIP JEWEL	
1/2"	100	1/2"	100	1/2"	100	1/2"	100
3/4"	100	3/4"	100	3/4"	100	3/4"	100
1"	100	1"	100	1"	100	1"	100
1 1/2"	100	1 1/2"	100	1 1/2"	100	1 1/2"	100
2"	100	2"	100	2"	100	2"	100


CRYSTALS		VOLTAGE REGULATORS		COMPUTER HARDWARE		ALLUM BOXES	
100kHz	100	5V	100	100	100	100	100
200kHz	100	12V	100	200	100	200	100
300kHz	100	15V	100	300	100	300	100
400kHz	100	20V	100	400	100	400	100
500kHz	100	25V	100	500	100	500	100

ULTRASONIC TRANS.		DIODES		MIGHTY MINI-SWITCH	
100W	100	1N4001	100	100	100
200W	100	1N4002	100	200	100
300W	100	1N4003	100	300	100
400W	100	1N4004	100	400	100
500W	100	1N4005	100	500	100

CMOS		YOU Chip and MODULE for TV	
100	100	100	100
200	100	200	100
300	100	300	100
400	100	400	100
500	100	500	100

..... news digest

BIG SCREEN SCOPE

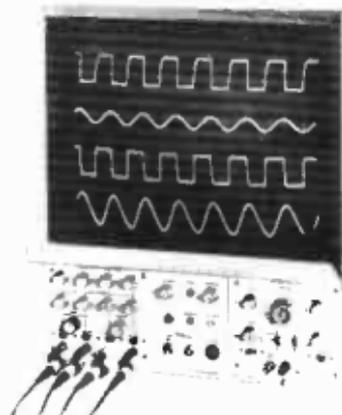

Chimeire have introduced what they believe to be the only low cost, large screen (17 inch) oscilloscope in Britain designed the BWD 1722.

The high sensitivity four channel amplifier can switch up to four traces with alternate or chopped presentation. All inputs are AC or DC coupled with independent gain and shift

controls. Trigger output is taken from channel one.

Continuously variable sensitivity, from 35 mV to 5 V per inch is provided. Auto manual, line and external triggering with a horizontal sensitivity of 100 mV to 50 V per inch are provided. The BWD 1722 sells at £1350 from Chimeire Ltd Instruments, Aptley House, Aptley Road, New Malden, Surrey

MIGHTY MINI-SWITCH



Digtran's new series of miniature push buttons are built to last. The Series 12000 Minibutton is designed for use in applications where severe environmental conditions are expected.

The switch is designed for a life of one million diene operations. It meets the shock, vibration, moisture-resistance, thermal shock, salt spray, explosion - proofing and sand and dust requirements of MIL-STD-202, a stringent specification. Eight or ten standard dial positions are available. Series 12000 is available from Digtran UK, Melbourn, Royston, Herts.

MICRO CHIMES

FROM THE INVENTORS
OF MICROPROCESSOR
MUSICAL CHIMES

New price for the
original

CHROMA- CHIME KIT

24 tune model!

Due to the fantastic
success of this product right
across the World we are able to offer it at

only **£9.95 + 75p p&p**

Comes complete with

- > TMS1000 Micro Fully prepared PCB
- > Superb cabinet All semiconductor
- > AII R's & C's Loudspeaker
- > Switches & pots Socket & Hardware
- Fully detailed kit manual

TMS 1000N - MP0027A Micro
computer chip available separately if
required. Full 24 tune spec device
supplied with data sheet and fully
guaranteed

New low price only **£4.95 inc. p&p**

(Only present 24 tune replicate currently available)

A COMPLETE KIT FOR THE NEW MICRO CHIME

This easy to
build kit includes

- TMS1000 Custom MPU Chip
- Special purpose designed case
- Fully drilled and legended PCB
- All transistors Resistors and Capacitors
- Full set of mechanical parts
- Smart fascia labels
- IC Socket and Loudspeaker
- Really Low Price!

only **£8.95 + 55p p&p**

ALL CHROMATRONICS PRODUCTS
SUPPORTED BY THE MONEY BACK GUARANTEE
PLEASE ALLOW 7-10 DAYS FOR DELIVERY

Please send me
TO: CHROMATRONICS, HEVER WAY, HAVAR, 1 & 5 FIFE, UK.
NAME _____
ADDRESS _____

I enclose cheque, PO or bill etc
or debit my ACCESS/PAID/CARD account no

Signature _____

CHROMATRONICS

..... news digest.....

DIL SWITCHES

The Series 206 DIL program
ming switches from AB
Controls has been extended to
include SPST, DPST, SPDT and
DPDT version Applications in
clock logic functions in com-
puters and test equipment.
Switches are available with two
to ten sections.

Gold plated wiping contacts
and terminals ensure long term
corrosion resistance. Further
details from AB Electronic Pro-
ducts Group Ltd, Abernnon
Vial Glamorgan CF 45 45J.



IN BEZELFD?

This new display bezel from
Vero Electronics comes with
your choice of neutral, red or
clear lens (polarised or unpo-
larised).

The bezel is positioned in a
single rectangular cut out by
four removable pegs and finally
secured by two screwed studs
which also secure the display
mounting board in the spacer-
provided. A full range of com-

patible mounting boards for
LED and LCD displays is avail-
able.

Prices range from £1.50 for a
four digit bezel with clear lens
to £2.60 for a six digit with
coloured lens. Further details
on Display Bezel AB094 from
Vero Electronics Ltd, Industrial
Estate, Chandler's Ford, East
Hampshire SO6 1ZK.



OOPS AND ALL THAT ..

**Disco Lightshow — Dec
78**

Page 46 — C14 19 24 29 34 are
shown upside down
junctions 11 R33 12 R45
T3 R51 T4 R60 T5 R68 all
should be shown going to
—12V

Page 47 — R71 1k (between
D18 and ZD5) was not
shown on the circuit dia-
gram (it is however shown
correctly on the oscilloscope
Transformer)

Page 47 — ZD6 is 5V6 not 4V7

Page 48 — (Parts list) R73 is
4K7

Page 48 — batch 3 the two
brown wires should be

shown on tag 3 not 4. On the
output terminal blocks 3
and 4 are interchanged.

**Stage Dimmer — March
79**

We omitted details of the choke
L3 from the Parts List. On our
prototype this was wound onto
a one inch square core with a 50
thou gap. The 10A version is
wound full of 16 SWG wire and
the 20A is wound full of two
parallel windings of 16 SWG.

T1 can be wound as
45:1 primary and 15:1 secondary
on Nicoid Lore 4320R/3/F7
EC if available.

STEVENSON

Electronic Components

SWITCHES

Subminiature toggle plated at 3A 250V

SPDT 85p DPDT centre off 70p
DPDT 75p DPDT centre off 90p

Standard Toggle

SPST 34p DPDT 48p

Wavechange switches

1P12W 2P6W, 3P4W or 4P2W
at 37a each



Miniature switches (non locking)

Push to make 15p Push to break 20p

POTENTIOMETERS

5K 2M2 single 25p ea 100K 2M2 horizontal
5K-2V2 stereo (dual) 75p ea or vertical preset 6p ea
5K 2M2 DP switched 60p ea

KNOBS

Ideal for use on mixers etc. Push on type
with coloured cap in red, black, green, blue,
yellow and grey.
Pop back line marked 14p each



MICROPROCESSORS

6800 670p 6870 350p 27L02 110p
8080A 525p 6850 360p 2112 175p
6810 300p AY5 +013 380p 2114 700p

REGULATORS

78L05 30p 79L05 70p LM309K 110p
78L12 30p 79L12 70p LM317 220p
78L15 30p 79L15 70p LM329K 630p
7805 60p 7905 80p LM723 35p
7812 60p 7912 80p
7815 60p 7915 80p

THYRISTORS AND TRIACS

Plastic case Thyristors Triacs

	4A	8A	12A
100V	36p	45p	62p
200V	42p	53p	68p
400V	61p	66p	86p

Plastic case Triacs Triacs

All rated at 400V

4A	70p	12A	90p	20A	185p
8A	80p	16A	95p	26A	215p

We now have an express telephone order service. We guarantee that all orders received before 5pm are shipped first class on that day. Contact our Sales Office now! Telephone 01 464 2951/5770

ORDERS
DESPATCHED
BY RETURN
POST

Quantity discounts on any mix TTL, CMOS, 74LS and Linear circuits: 25-10% 100+15%. Prices VAT inc. Please add 30p for carriage. All prices valid to 30th April 1979. Official orders welcome.

BARCLAYCARD AND ACCESS WELCOME.



TRANSISTORS

AL121 15p	BCY10 14p	2T-100 44p	27-020 16p
AD120 15p	BCY17 14p	27-030 16p	27-030 16p
AD126 16p	BCY21 15p	27-037 16p	27-037 16p
AD127 16p	BCY25 15p	27-039 16p	27-039 16p
AD128 16p	BCY26 15p	27-040 16p	27-040 16p
AD129 16p	BCY27 15p	27-041 16p	27-041 16p
AD130 16p	BCY28 15p	27-042 16p	27-042 16p
AD131 16p	BCY29 15p	27-043 16p	27-043 16p
AD132 16p	BCY30 15p	27-044 16p	27-044 16p
AD133 16p	BCY31 15p	27-045 16p	27-045 16p
AD134 16p	BCY32 15p	27-046 16p	27-046 16p
AD135 16p	BCY33 15p	27-047 16p	27-047 16p
AD136 16p	BCY34 15p	27-048 16p	27-048 16p
AD137 16p	BCY35 15p	27-049 16p	27-049 16p
AD138 16p	BCY36 15p	27-050 16p	27-050 16p
AD139 16p	BCY37 15p	27-051 16p	27-051 16p
AD140 16p	BCY38 15p	27-052 16p	27-052 16p
AD141 16p	BCY39 15p	27-053 16p	27-053 16p
AD142 16p	BCY40 15p	27-054 16p	27-054 16p
AD143 16p	BCY41 15p	27-055 16p	27-055 16p
AD144 16p	BCY42 15p	27-056 16p	27-056 16p
AD145 16p	BCY43 15p	27-057 16p	27-057 16p
AD146 16p	BCY44 15p	27-058 16p	27-058 16p
AD147 16p	BCY45 15p	27-059 16p	27-059 16p
AD148 16p	BCY46 15p	27-060 16p	27-060 16p
AD149 16p	BCY47 15p	27-061 16p	27-061 16p
AD150 16p	BCY48 15p	27-062 16p	27-062 16p
AD151 16p	BCY49 15p	27-063 16p	27-063 16p
AD152 16p	BCY50 15p	27-064 16p	27-064 16p
AD153 16p	BCY51 15p	27-065 16p	27-065 16p
AD154 16p	BCY52 15p	27-066 16p	27-066 16p
AD155 16p	BCY53 15p	27-067 16p	27-067 16p
AD156 16p	BCY54 15p	27-068 16p	27-068 16p
AD157 16p	BCY55 15p	27-069 16p	27-069 16p
AD158 16p	BCY56 15p	27-070 16p	27-070 16p
AD159 16p	BCY57 15p	27-071 16p	27-071 16p
AD160 16p	BCY58 15p	27-072 16p	27-072 16p
AD161 16p	BCY59 15p	27-073 16p	27-073 16p
AD162 16p	BCY60 15p	27-074 16p	27-074 16p
AD163 16p	BCY61 15p	27-075 16p	27-075 16p
AD164 16p	BCY62 15p	27-076 16p	27-076 16p
AD165 16p	BCY63 15p	27-077 16p	27-077 16p
AD166 16p	BCY64 15p	27-078 16p	27-078 16p
AD167 16p	BCY65 15p	27-079 16p	27-079 16p
AD168 16p	BCY66 15p	27-080 16p	27-080 16p
AD169 16p	BCY67 15p	27-081 16p	27-081 16p
AD170 16p	BCY68 15p	27-082 16p	27-082 16p
AD171 16p	BCY69 15p	27-083 16p	27-083 16p
AD172 16p	BCY70 15p	27-084 16p	27-084 16p
AD173 16p	BCY71 15p	27-085 16p	27-085 16p
AD174 16p	BCY72 15p	27-086 16p	27-086 16p
AD175 16p	BCY73 15p	27-087 16p	27-087 16p
AD176 16p	BCY74 15p	27-088 16p	27-088 16p
AD177 16p	BCY75 15p	27-089 16p	27-089 16p
AD178 16p	BCY76 15p	27-090 16p	27-090 16p
AD179 16p	BCY77 15p	27-091 16p	27-091 16p
AD180 16p	BCY78 15p	27-092 16p	27-092 16p
AD181 16p	BCY79 15p	27-093 16p	27-093 16p
AD182 16p	BCY80 15p	27-094 16p	27-094 16p
AD183 16p	BCY81 15p	27-095 16p	27-095 16p
AD184 16p	BCY82 15p	27-096 16p	27-096 16p
AD185 16p	BCY83 15p	27-097 16p	27-097 16p
AD186 16p	BCY84 15p	27-098 16p	27-098 16p
AD187 16p	BCY85 15p	27-099 16p	27-099 16p
AD188 16p	BCY86 15p	27-100 16p	27-100 16p
AD189 16p	BCY87 15p	27-101 16p	27-101 16p
AD190 16p	BCY88 15p	27-102 16p	27-102 16p
AD273 16p	BCY171 15p	27-185 16p	27-185 16p
AD274			

news digest.....

INFRARED EYES



NORBITAN have announced the introduction of two new reflective object sensors. Optrom types OPB708 and OPB709 are reflective transducers incorporating a gallium arsenide infrared emitting diode and a planar silicon phototransistor (OPB708) or photodarlington (OPB709).

With a reflective surface of shining tape 0.15 inches from the read head, typical values of

photo current are 65 mA (OPB708) and 8 mA (OPB709). An aluminium foil at the end of a tape produces typical values of 1 mA and 140 mA respectively. With an opaque reflective surface flush to the read head maximum cross-stalk currents are 100 nA (OPB708) and 250 nA (OPB709). Further details from Norbitan Optoelectronics Division, Norbitan House, Arkwright Road, Reading, Berkshire RG2 0AT.

THREE-FUNCTION TOOL

Cut the copper conductor of a wire (see strip off a length of insulation and wrap several times around a terminal) all in one operation with this bit and sleeve combination from Vero Systems (Electronics) Ltd. The three functions are performed in one rotating operation using an electric or pneumatic tool with normal output and a speed of about 3 000 RPM. Vero's Standard Pneumatic £30 V wrapping tool is suitable.

The bit and sleeve is designed to use a specific gauge of conductor and insulation diameter are available in the range 22 to 10 AWG. Low strip force Mlene wire for use with these bits and sleeves is available in six colours from Vero Systems. Cut strip and wrap tool AB965 is £8 from Vero Systems (Electronics) Ltd, 362 Spring Road, Sholing, Southampton Hampshire SO9 5QJ.



DOING TIME?

ARE you one of the select few whose calculator is doing you months in Parkhurst? Have you been ordering digital watches from the Lord Chancellor? What FTI reader is his right mind small do that?

It seems that Ministry of Justice's old phone number was similar to that of the Lord Chancellor's Prison Office. Hence the confusion.

If you still have a piece of paper with Mountaindene's old number on it, use it to patch connect 4017 back to the Lord Chancellor. If you ask not to be might give your calculator parole.

AUDIO MODULES

1 Stereo Cassette Deck N999

Complete with electronics uses Music centres 4400 circuits, tape editing, 41. Frq resp 6.3 Hz 30KHz W/O 0.15% FLUTTER 0.8 channel separation 55dB Electronic speed control, ALC, Mic and line inputs. JAPANESE manufacture requires 12 VDC. **£23.95.**



2 Preamp Amp — PSU Wumbo 11W per channel

Four rotary controls Vol, Bass, Treble, Balance, 2 x PSU for RF Board — essential, deck LM 3877 preamp IC driver, TIP 31 — TIP 32 Output Pair. Special price includes transformer. **£16.95** (October 1978, Pk).



3 AMP 041 8 watts RMS per channel amp preamp

8 watts RMS per channel amp preamp 8 watts RMS per channel amp preamp 8 watts RMS per channel amp preamp. Price complete **£6.99.**



4 AMP 020 Stereo power amp 0.5 W RMS per channel

Class AB1 TIP 14A — TIP 33A 16 Transistor circuit Fr. resp 15Hz — 18 KHz 1dB **£7.99.**



5 Matching Hi-Fi Preamplifier, four rotary controls

Vol, Bal, Treble, Bass, Tickle — 14dB Bass 14dB Treble for loudness control. **£6.99.**



RF MODULES

6 Surplus RF Board 020

Complete MW LW FM MPX Tuner uses 3 stage FET front end 2 ceramic filters 308RE 1310 Decoder AM section built around 3132E 2 stage tuning comes with 4-way switch — ferrite rod aerial. **£9.99.**



7 RF 030

Improved version of above extra gain stage, enhanced S/N ratio and 1.5 μ V sensitivity for 26dB S/N way selector switch AFC stereo mono switching — two additional inputs. **£19.95.**

8 RF 040 MW LW FM MPX varicap tuned RF board

Nov. Dec PW Dual gate MOSFET front end 2 x 1F gain stages 3.89 Deviation mute — interstation mute — MPX filters 5Tab PSU 1 μ V sensitivity and 75dB S/N ratio. AM Section also varicap tuned HA1197 excellent performance. Special price **£26.95.**

9 VT01 108 150MHz MOSFET front end 26dB gain

10.7MHz IF output. Covers 2 metres. Amateurs Aircraft etc. **£7.99.**



10 IF15 Matching IF Strip double conversion 10.7MHz 470 KHz AM NB FM Excellent performance. **£12.95.**

We have all parts in stock for the Wumbo Music Centre parts for amps, tuner, amps and music centres up to 25 watts per channel. We stock all hardware and trim to give you a professional finish. Front panels, encoders, knobs, sockets etc.

in price. Also visit our website at www.electronics-today.com for more information.

ESE RAILWAY HOUSE, HARDHAM CROSSING, PULBOROUGH, SUSSEX

INTRODUCING DUAL DRIVE MINIFLOPPY FOR PET!



DUAL MINI FLOPPY DRIVE WITH 100K PER DISK SIDE FOR TOTAL 200K ON LINE
DESIGNED FOR COMMERCIAL SPEED REQUIREMENTS
FAST LOADING SPEED

*DISKMON™ (DOS) AUTOMATICALLY REORGANIZES FREE DISK SPACE AFTER SAVE OR ERASE
*DISKMON IS RESIDENT IN ROM VIA DISK CONTROLLER BOARD PLUGGED INTO EXPANDAPET™
*DISKMON ADDS 14 COMMANDS TO BASIC INCLUDING DISK DATA FILES
*DISKMON COMMANDS SUPPORT COMMERCIAL PRINTER OFF PARALLEL PORT SUCH AS CENTRONICS 779
*FULL DISK SOFTWARE SUPPORT
*FORTRAN & PLM COMPILERS THIS JANUARY
*90 DAY MANUFACTURER'S WARRANTY ON HARDWARE READY TO USE ON DELIVERY WITH FULL INSTRUCTIONS AND UTILITY DISKETTE
*CALL OR WRITE FOR ADDITIONAL INFORMATION INITIAL QUANTITIES LIMITED
*THIS SYSTEM IS FULLY SUPPORTED BY SOFTWARE FROM THE MANUFACTURER
DELIVERY NOW
DKH841—DUAL DRIVE SYSTEM COMPLETE WITH DISKMON (316 = VAT)
DK1067—DISKMON ASSEMBLER LISTING / DOS P.O.A.
ASM789T—PET ASSEMBLER ON CASSETTE P.O.A.
ASM789D—PET ASSEMBLER ON DISKETTE (5.5 inch) P.O.A.
LWK456—AUTOLINK LINKING LOADER ON DISKETTE P.O.A.
FOR300—FORTRAN COMPILER ON DISKETTE P.O.A.
PLM400—PLM COMPILER ON DISKETTE P.O.A.
* BUSINESS PACKAGES STARTING IN 1st QUARTER 1979 *
* THIS SYSTEM REQUIRES EXPANDAPET MEMORY (MINIMUM 16K—SEE BELOW)

INTERNAL MEMORY EXPANSION FOR PET! EXPANDAPET™



INTERNAL MEMORY EXPANSION UNIT
MOUNTS EASILY INSIDE YOUR PET
EASY TO INSTALL (15 MINUTES)
USES LOW POWER DYNAMIC RAMS
90 DAY PART & LABOUR 1 YR. RAMS
30 DAY MONEY BACK GUARANTEE
MOUNTING SLOTS FOR 4 BOARDS
CALL WRITE FOR ADDITIONAL INFO
DEALER INQUIRIES INVITED

32K UNIT ALLOWS BK. OF ASSEMBLY LANGUAGE SUBROUTINES ACCESSED VIA THE USA COMMAND

OPTIONAL PLUG IN BOARDS
SERIAL I/O BOARD P.O.A.
5-100 I/O BOARD P.O.A.
4K EPROM BOARD P.O.A.

EXPANDAPET PRICES	
16K	8K PET 24K) £398 VAT
24K	8K PET 32K) £364 VAT
32K	8K PET 40K) £425 VAT

MUSIC BOX

Turns your PET into a programmable musical instrument. You can record and play up to 90 pages 16 notes per page, change tempo key etc.

£37.50 inc. VAT & P&P


T.I.S. WORKBOOKS

A set of 5 workbooks to give you a full understanding of all the ins and outs of your PET more fully than any previous manuals.

£15.95 per set, inc. P&P

Lots of software and other goodies.
Send large SAE

OHIO SCIENTIFIC SUPERBOARD II

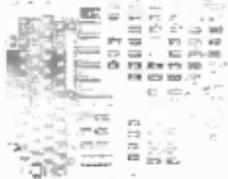

£263 plus VAT

Standard Features

- Uses the ultra powerful 6502 microprocessor
- 8K Microsoft BASIC-in-ROM
- Full feature BASIC runs faster than currently available personal computers and all 8080 based business computers
- 4K static RAM on board expandable to 8K
- All 53-key keyboard with upper-lower case and user programmability
- Kansas City standard audio cassette interface for high reliability
- Full machine code monitor and I/O utilities in ROM
- Direct access video display has 1K of dedicated memory besides 4K user memory, features upper case lower case graphics and gaming characters for an effective screen resolution of up to 256 by 256 points. Normal TV's with overscan display about 24 rows of 24 characters, without overscan up to 30 x 30 characters

Extras


- Available expander board features 24K static RAM, additional mini-floppy interface, port adapter for printer and modem and QSI48 line expansion interface
- Assembler editor and expanded machine code monitor available

Fully built and tested. Requires only 5V at 3 amps and a video monitor or TV and RF converter to be up and running.
Phone or write for catalogue, prices, full range user manuals.

LOTUS SOUND, 4 MORGAN ST., LONDON E3 5AB

Tel: 01-981-3993 Telex: 261426 Attn: Lotus Sound

NON-SUBSCRIBERS START HERE

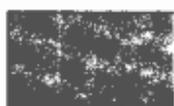

GIVE UP GO HOME AND TAKE OUT A POSTAL SUBSCRIPTION TO ETI

It can be a nuisance can't it, going from newsgent to newsgent? "Sorry square don't have it — next one should be out soon."

Although ETI is monthly, it's very rare to find it available after the first week. If it is available, the newsgent is going to be sure to cut his order for the next issue — but we're glad to say it doesn't happen very often.

Do yourself, your newsgent and us a favour. Place a regular order for ETI, your newsgent will almost certainly be delighted. If not, you can take out a postal subscription so there's nothing for you to remember — we'll do it for you.

For a subscription, send us £7.00 (£8.00 overseas) and tell us which issue you want to start with. Please make your payment (in sterling please for overseas readers) to ETI Subscriptions and keep it separate from any other services you want at the same time.

ETI Subscriptions
Map Publications
PO Box 35
Bridge Street
Hemel Hempstead
Herts

AUDIO AND TEST EQUIPMENT CENTRE

RETAIL MAIL ORDER EXPORT
ALL PRICES INCLUDE VAT



Telephone your order with Access and Telecards or send cheque with order

LONDON'S TEST GEAR CENTRE
OPEN 6 DAYS A WEEK 9 am-6 pm

SCORES — IN STOCK (UK P/P £1.50 ea)

2000 V 100 mA	87.00	EMAG RECORDS	127.00
4000 V 50 mA	124.20	100000	1734.00
Super 100 V 200 mA	225.00	100000	1734.00
Super 100 V 200 mA	225.00	100000	1734.00
Super 100 V 200 mA	225.00	100000	1734.00
PROBER 1.0 100000 0.005 7.00	5.00	100000	1734.00

LED AND LCD DIGITAL MULTIMETERS

DM200 1000 V 200 mA	89.95	DM400 1000 V 200 mA	129.95
DM250 1000 V 200 mA	99.95	DM450 1000 V 200 mA	139.95
DM300 1000 V 200 mA	109.95	DM500 1000 V 200 mA	149.95
DM350 1000 V 200 mA	119.95	DM550 1000 V 200 mA	159.95
DM400 1000 V 200 mA	129.95	DM600 1000 V 200 mA	169.95
DM450 1000 V 200 mA	139.95	DM650 1000 V 200 mA	179.95
DM500 1000 V 200 mA	149.95	DM700 1000 V 200 mA	189.95
DM550 1000 V 200 mA	159.95	DM750 1000 V 200 mA	199.95
DM600 1000 V 200 mA	169.95	DM800 1000 V 200 mA	209.95
DM650 1000 V 200 mA	179.95	DM850 1000 V 200 mA	219.95
DM700 1000 V 200 mA	189.95	DM900 1000 V 200 mA	229.95
DM750 1000 V 200 mA	199.95	DM950 1000 V 200 mA	239.95
DM800 1000 V 200 mA	209.95	DM1000 1000 V 200 mA	249.95
DM850 1000 V 200 mA	219.95		
DM900 1000 V 200 mA	229.95		
DM950 1000 V 200 mA	239.95		
DM1000 1000 V 200 mA	249.95		

MULTI-METERS — GENERAL PURPOSE & ELECTRONIC

TM11 1000 V 200 mA	129.95	TM11 1000 V 200 mA	129.95
TM21 1000 V 200 mA	139.95	TM21 1000 V 200 mA	139.95
TM31 1000 V 200 mA	149.95	TM31 1000 V 200 mA	149.95
TM41 1000 V 200 mA	159.95	TM41 1000 V 200 mA	159.95
TM51 1000 V 200 mA	169.95	TM51 1000 V 200 mA	169.95
TM61 1000 V 200 mA	179.95	TM61 1000 V 200 mA	179.95
TM71 1000 V 200 mA	189.95	TM71 1000 V 200 mA	189.95
TM81 1000 V 200 mA	199.95	TM81 1000 V 200 mA	199.95
TM91 1000 V 200 mA	209.95	TM91 1000 V 200 mA	209.95
TM1000 1000 V 200 mA	219.95	TM1000 1000 V 200 mA	219.95
TM1100 1000 V 200 mA	229.95	TM1100 1000 V 200 mA	229.95
TM1200 1000 V 200 mA	239.95	TM1200 1000 V 200 mA	239.95
TM1300 1000 V 200 mA	249.95	TM1300 1000 V 200 mA	249.95
TM1400 1000 V 200 mA	259.95	TM1400 1000 V 200 mA	259.95
TM1500 1000 V 200 mA	269.95	TM1500 1000 V 200 mA	269.95
TM1600 1000 V 200 mA	279.95	TM1600 1000 V 200 mA	279.95
TM1700 1000 V 200 mA	289.95	TM1700 1000 V 200 mA	289.95
TM1800 1000 V 200 mA	299.95	TM1800 1000 V 200 mA	299.95
TM1900 1000 V 200 mA	309.95	TM1900 1000 V 200 mA	309.95
TM2000 1000 V 200 mA	319.95	TM2000 1000 V 200 mA	319.95

GENERAL EQUIPMENT

SP100 1000 V 200 mA	129.95	SP100 1000 V 200 mA	129.95
SP200 1000 V 200 mA	139.95	SP200 1000 V 200 mA	139.95
SP300 1000 V 200 mA	149.95	SP300 1000 V 200 mA	149.95
SP400 1000 V 200 mA	159.95	SP400 1000 V 200 mA	159.95
SP500 1000 V 200 mA	169.95	SP500 1000 V 200 mA	169.95
SP600 1000 V 200 mA	179.95	SP600 1000 V 200 mA	179.95
SP700 1000 V 200 mA	189.95	SP700 1000 V 200 mA	189.95
SP800 1000 V 200 mA	199.95	SP800 1000 V 200 mA	199.95
SP900 1000 V 200 mA	209.95	SP900 1000 V 200 mA	209.95
SP1000 1000 V 200 mA	219.95	SP1000 1000 V 200 mA	219.95
SP1100 1000 V 200 mA	229.95	SP1100 1000 V 200 mA	229.95
SP1200 1000 V 200 mA	239.95	SP1200 1000 V 200 mA	239.95
SP1300 1000 V 200 mA	249.95	SP1300 1000 V 200 mA	249.95
SP1400 1000 V 200 mA	259.95	SP1400 1000 V 200 mA	259.95
SP1500 1000 V 200 mA	269.95	SP1500 1000 V 200 mA	269.95
SP1600 1000 V 200 mA	279.95	SP1600 1000 V 200 mA	279.95
SP1700 1000 V 200 mA	289.95	SP1700 1000 V 200 mA	289.95
SP1800 1000 V 200 mA	299.95	SP1800 1000 V 200 mA	299.95
SP1900 1000 V 200 mA	309.95	SP1900 1000 V 200 mA	309.95
SP2000 1000 V 200 mA	319.95	SP2000 1000 V 200 mA	319.95

GENERATORS

GE100 1000 V 200 mA	129.95	GE100 1000 V 200 mA	129.95
GE200 1000 V 200 mA	139.95	GE200 1000 V 200 mA	139.95
GE300 1000 V 200 mA	149.95	GE300 1000 V 200 mA	149.95
GE400 1000 V 200 mA	159.95	GE400 1000 V 200 mA	159.95
GE500 1000 V 200 mA	169.95	GE500 1000 V 200 mA	169.95
GE600 1000 V 200 mA	179.95	GE600 1000 V 200 mA	179.95
GE700 1000 V 200 mA	189.95	GE700 1000 V 200 mA	189.95
GE800 1000 V 200 mA	199.95	GE800 1000 V 200 mA	199.95
GE900 1000 V 200 mA	209.95	GE900 1000 V 200 mA	209.95
GE1000 1000 V 200 mA	219.95	GE1000 1000 V 200 mA	219.95
GE1100 1000 V 200 mA	229.95	GE1100 1000 V 200 mA	229.95
GE1200 1000 V 200 mA	239.95	GE1200 1000 V 200 mA	239.95
GE1300 1000 V 200 mA	249.95	GE1300 1000 V 200 mA	249.95
GE1400 1000 V 200 mA	259.95	GE1400 1000 V 200 mA	259.95
GE1500 1000 V 200 mA	269.95	GE1500 1000 V 200 mA	269.95
GE1600 1000 V 200 mA	279.95	GE1600 1000 V 200 mA	279.95
GE1700 1000 V 200 mA	289.95	GE1700 1000 V 200 mA	289.95
GE1800 1000 V 200 mA	299.95	GE1800 1000 V 200 mA	299.95
GE1900 1000 V 200 mA	309.95	GE1900 1000 V 200 mA	309.95
GE2000 1000 V 200 mA	319.95	GE2000 1000 V 200 mA	319.95

PROBES IN STOCK

PR100 1000 V 200 mA	129.95	PR100 1000 V 200 mA	129.95
PR200 1000 V 200 mA	139.95	PR200 1000 V 200 mA	139.95
PR300 1000 V 200 mA	149.95	PR300 1000 V 200 mA	149.95
PR400 1000 V 200 mA	159.95	PR400 1000 V 200 mA	159.95
PR500 1000 V 200 mA	169.95	PR500 1000 V 200 mA	169.95
PR600 1000 V 200 mA	179.95	PR600 1000 V 200 mA	179.95
PR700 1000 V 200 mA	189.95	PR700 1000 V 200 mA	189.95
PR800 1000 V 200 mA	199.95	PR800 1000 V 200 mA	199.95
PR900 1000 V 200 mA	209.95	PR900 1000 V 200 mA	209.95
PR1000 1000 V 200 mA	219.95	PR1000 1000 V 200 mA	219.95
PR1100 1000 V 200 mA	229.95	PR1100 1000 V 200 mA	229.95
PR1200 1000 V 200 mA	239.95	PR1200 1000 V 200 mA	239.95
PR1300 1000 V 200 mA	249.95	PR1300 1000 V 200 mA	249.95
PR1400 1000 V 200 mA	259.95	PR1400 1000 V 200 mA	259.95
PR1500 1000 V 200 mA	269.95	PR1500 1000 V 200 mA	269.95
PR1600 1000 V 200 mA	279.95	PR1600 1000 V 200 mA	279.95
PR1700 1000 V 200 mA	289.95	PR1700 1000 V 200 mA	289.95
PR1800 1000 V 200 mA	299.95	PR1800 1000 V 200 mA	299.95
PR1900 1000 V 200 mA	309.95	PR1900 1000 V 200 mA	309.95
PR2000 1000 V 200 mA	319.95	PR2000 1000 V 200 mA	319.95

DRILLS AND DRILL BITS

DR100 1000 V 200 mA	129.95	DR100 1000 V 200 mA	129.95
DR200 1000 V 200 mA	139.95	DR200 1000 V 200 mA	139.95
DR300 1000 V 200 mA	149.95	DR300 1000 V 200 mA	149.95
DR400 1000 V 200 mA	159.95	DR400 1000 V 200 mA	159.95
DR500 1000 V 200 mA	169.95	DR500 1000 V 200 mA	169.95
DR600 1000 V 200 mA	179.95	DR600 1000 V 200 mA	179.95
DR700 1000 V 200 mA	189.95	DR700 1000 V 200 mA	189.95
DR800 1000 V 200 mA	199.95	DR800 1000 V 200 mA	199.95
DR900 1000 V 200 mA	209.95	DR900 1000 V 200 mA	209.95
DR1000 1000 V 200 mA	219.95	DR1000 1000 V 200 mA	219.95
DR1100 1000 V 200 mA	229.95	DR1100 1000 V 200 mA	229.95
DR1200 1000 V 200 mA	239.95	DR1200 1000 V 200 mA	239.95
DR1300 1000 V 200 mA	249.95	DR1300 1000 V 200 mA	249.95
DR1400 1000 V 200 mA	259.95	DR1400 1000 V 200 mA	259.95
DR1500 1000 V 200 mA	269.95	DR1500 1000 V 200 mA	269.95
DR1600 1000 V 200 mA	279.95	DR1600 1000 V 200 mA	279.95
DR1700 1000 V 200 mA	289.95	DR1700 1000 V 200 mA	289.95
DR1800 1000 V 200 mA	299.95	DR1800 1000 V 200 mA	299.95
DR1900 1000 V 200 mA	309.95	DR1900 1000 V 200 mA	309.95
DR2000 1000 V 200 mA	319.95	DR2000 1000 V 200 mA	319.95

MICROPHONES SPEAKERS AND COMPONENTS

MC100 1000 V 200 mA	129.95	MC100 1000 V 200 mA	129.95
MC200 1000 V 200 mA	139.95	MC200 1000 V 200 mA	139.95
MC300 1000 V 200 mA	149.95	MC300 1000 V 200 mA	149.95
MC400 1000 V 200 mA	159.95	MC400 1000 V 200 mA	159.95
MC500 1000 V 200 mA	169.95	MC500 1000 V 200 mA	169.95
MC600 1000 V 200 mA	179.95	MC600 1000 V 200 mA	179.95
MC700 1000 V 200 mA	189.95	MC700 1000 V 200 mA	189.95
MC800 1000 V 200 mA	199.95	MC800 1000 V 200 mA	199.95
MC900 1000 V 200 mA	209.95	MC900 1000 V 200 mA	209.95
MC1000 1000 V 200 mA	219.95	MC1000 1000 V 200 mA	219.95
MC1100 1000 V 200 mA	229.95	MC1100 1000 V 200 mA	229.95
MC1200 1000 V 200 mA	239.95	MC1200 1000 V 200 mA	239.95
MC1300 1000 V 200 mA	249.95	MC1300 1000 V 200 mA	249.95
MC1400 1000 V 200 mA	259.95	MC1400 1000 V 200 mA	259.95
MC1500 1000 V 200 mA	269.95	MC1500 1000 V 200 mA	269.95
MC1600 1000 V 200 mA	279.95	MC1600 1000 V 200 mA	279.95
MC1700 1000 V 200 mA	289.95	MC1700 1000 V 200 mA	289.95
MC1800 1000 V 200 mA	299.95	MC1800 1000 V 200 mA	299.95
MC1900 1000 V 200 mA	309.95	MC1900 1000 V 200 mA	309.95
MC2000 1000 V 200 mA	319.95	MC2000 1000 V 200 mA	319.95


TM11

TMK500

PIEZO HORN TWEETERS

POWER AMP SURVEY

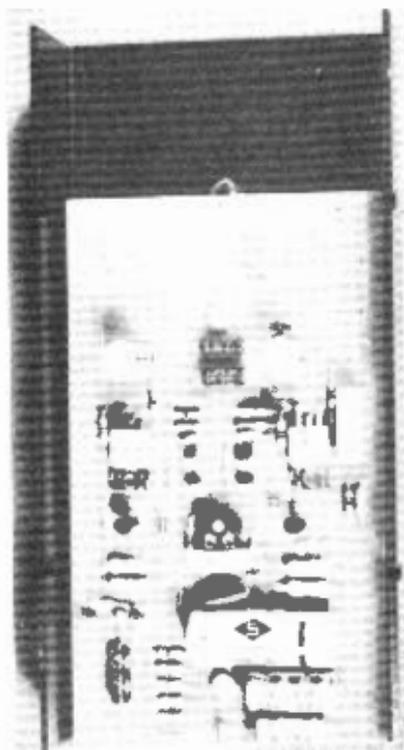The Americans would describe it as a 'crowded marketplace'. Power amplifiers appear almost daily and the resulting choice can easily lead to confusion. Ron Harris attempts an overview.



UPGRADING HI FI is a costly business using commercial units as better can somehow read dearer once over the threshold into a hi-fi euphemism. Once contracted however the improving bug is no respecter of price and pocket.

Quite commonly the malady can be caught via the cones of new loudspeakers which are crying out for more watts to drive them. The amplifier just has to go!

The Modular Connection

One method of gaining the extra power — if you re quite content with facilities etc — is to replace output stages of your present equipment with two power amplifier modules. There are certainly enough on the market to choose from.

This will certainly be cheaper and most of these modules outperform similarly priced commercial units so performance need not suffer. Since you need not necessarily have to pay for a PSU and case you don't need it must be cheaper. Very often too the existing case can be utilised to house the new boards with attendant saving in that most onerous of tasks — metalwork.

Judging by the continuing popularity of the audio projects which appear within these pages do-it-yourself hi-fi continues to abound even though building up from scratch is often no cheaper than buying commercial units. Modular construction — with most designs being pre-tested — can make this task easier and more certain.

With kit construction however there is obviously more to go wrong and this tends to mean the results are more dependent (at times!) upon the constructor than the supplying company. We have been told by several reputable kit suppliers that the greatest single reason for non functioning units is poor soldering!

Board Decision

With the large number of available kits for power amplifiers in mind we decided to exclude them from our deliberations and concentrate on modules alone. This was defined as a unit in which the amplifier is supplied completely pre-assembled in other words as a PCB which can then be utilised.

Undoubtedly there are some modules we have missed out in our scan across the adverts — and if you know of any we have missed please let us know so that as few injustices as possible are perpetrated! ▶

Advantage Points

Using these units is very straightforward. The manufacturers will have set up the amplifier already and hopefully need a few to specification. All that should remain for the purchaser to do is to connect up a PSU, some input and output sockets and a case. Music should then flow forth — suitably amplified!

One hint for wiring up a unit from modules is to keep an eye on the earthing arrangements. Insufficient attention to this can — and will — lead to monumental amplification at 50 Hz along a tube. Use a spider earth technique taking loudspeaker PSU and board earths to a common point. The Reservoir capacitors, etc. a convenient place to work upon.

Connect all the earth legs on the input phono sockets together and take out a single lead to the PCBs only. Make sure there is only a single path to signal earth as this will alleviate any loop problems which may otherwise arise.

When laying out the case, keep the transformer as far away from the amplifiers as possible and always shield it properly. Positioning the PSU board between modules and windings will ensure that some distance is maintained.


Choosing

If you're using your new unit to replace an aging or new underpowered predecessor remember that to obtain a barely perceptible increase in sound volume (3 dB) you will need to DOUBLE power output!

It is no good going from 20 W to 30 W and expecting to tick neighbours out of bed — if they could sleep through your 181.2 renderings before that extra 10 W is not going to add significantumph to your overtures. It is better to choose too high a power output for your application and be gentle with volume control than to underpower and regret it later. The correct rating depends upon the volume of the room you intend to play your music in.

Allow 25 W for the first 1000 cu ft and add 10 W per 1000 cu ft thereafter. This will yield up a minimum figure for normal listening levels with a decent reserve accounting average efficiency loudspeakers.

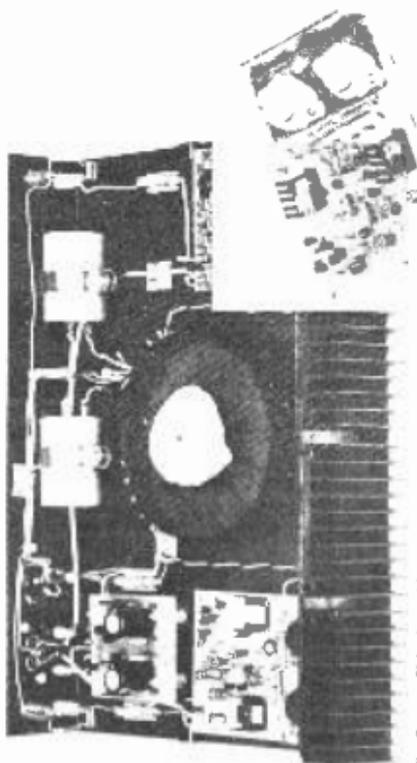If you use transmission line designs add 15 W to every 25 W of your estimate to allow for the basic inefficiency of this loading method.



The Conson Electronics amplifier system. Shown here are two CE608 modules mounted on their case along with PSU and pre-amp stabiliser board. Inset: a CE608 in detail.

What Happened?

One part of this survey led to a somewhat more materialised visit to proposed listening tests with one sample from each of you. Most manufacturers seemed unable to respond within the time required — approx. two weeks. We were left with BI PAK, Crimson and two IEP HV50c1 borrowed from a neighbour!

The idea had been to select a power output which was common to all ranges — 60W seemed reasonable and build up a unit from each suppliers' modules. This would have told us much about the sound quality, reliability and overall standard of the amplifiers.

We would have

Press On

In fairness to Magnum Audio they came upon the scheme late and were very quick indeed sending us information and a sample of their excellent instruction manuals. The scheme is not however ideal and buried yet — it is at least possible that our samples are reposing

Table A Motion

The table shown here lists some thirty odd modules ranging in power output from about three watts to well over 150W. A list of manufacturers is given at the end of the article.

All the companies produce their own power supplies to power the amplifiers and it is at least convenient to employ these where needed. One common failing of these is that the firms tend to underpower the modules in that not enough reserve is allowed for in the PSU design as for driving a single module.

At the high power end of the ranges, where cost is pretty high anyway it is worth powering each module from a separate PSU board. This reduces dynamic cross-talk where a peak on one channel drains the supply thus distorting the second channel by clipping the signal. If you use a single transformer make sure it is generously rated at least 50% above the current you expect to draw.

COMPARISON TABLE

MODEL	POWER OUTPUT	FHD (as given, load at 1kHz)	FREQUENCY RESPONSE	SIGNAL TO NOISE RATIO	DAMPING FACTOR	SENSITI- VITY (see rated output)	SETTLING TIME (BR 2- μ f)	OUTPUT PROTECTION REQUIRED	POWER SUPPLY (DC)	SIZE (mm)	PRICE INCL VAT
BI-PAK											
AL30A	10W (8R)	0.25% (5W)	50Hz 20kHz* 3dB	-	-	75 mV	4.20	NO	15V	74 x 63 x 28	£ 4.20
AL60	25W (8R)	0.1% (25W)	20Hz 30kHz* 2dB	-	-	280 mV	-	NO	30 50V	103 x 64 x 15	£ 5.11
AL80	35W (8R)	0.1% (35W)	20Hz 30kHz* 2dB	-	-	280 mV	-	NO	40 60V	103 x 64 x 15	£ 7.72
AL120	50W (8R)	0.05% (50W)	25Hz 20kHz* 1dB	-	-	500 mV	-	YES	65V	142 x 89 x 49	£ 17.90
AL250	125W (4R)	0.1% (50W)	25Hz 20kHz* 2dB	-	-	450 mV	-	YES	50 80V	-	£ 18.61
CRIMSON											
CE508	55W (8R)	All models	All models	All models	All models	All models	All models	All models	36 0 36V	All models	£ 16.40
CE1004	81W (4R)	0.01% full	20Hz 20kHz* 1/2dB	110dB	40	775 mV	20 μ S	YES	35 0 35V	80 x 120 x 25	£ 19.22
CE1008	92W (4R)	0.0035% 10W		unweighted	(50Hz)				61 0 61V		£ 23.22
CE1704	160W (4R)								61 0 61V		£ 29.12
CE1708	145W (8R)								61 0 61V		£ 31.80
ILP											
HY30	15W (8R)	0.1% (15W)	10Hz 16kHz* 3dB	75dB	-	All models	-	All models	18 0-18V	PCB mounted	£ 7.05
HY50	25W (8R)	0.04% (25W)	10Hz-45kHz* 3dB	75dB	-	500 mV	-	YES	25 0 25V	105 x 50 x 20	£ 9.20
HY120	60W (8R)	0.04% (60W)	10Hz-45kHz* 3dB	90dB	-	-	-	-	35 0 35V	114 x 50 x 85	£ 20.53
HY200	120W (8R)	0.05% (120W)	10Hz-45kHz* 3dB	96dB	-	-	-	-	45 0 45V	114 x 100 x 85	£ 30.23
HY400	240W (4R)	0.1% (240W)	10Hz-45kHz* 3dB	94dB	-	-	-	-	45 0 45V	114 x 100 x 85	£ 41.71
KINGSLEY											
ET1100	100W (4R)	0.1% (100W)	5Hz 50kHz* 0dB -3dB	100dB	20	500 mV	-	YES	40 0 40V	-	£ 18.35
MAGNUM											
CP2715	2 x 20W (8R)	0.03% (20W)	20Hz 25kHz* 3dB	106dB	-	1000 mV	20 μ S	YES	20 0 20V	130 x 102 x 32	£ 14.45
STERLING											
SOUND											
SS103	3W (8R)	0.3% (1W)	-	-	-	100 mV	-	YES	20V	-	£ 2.85
SS105	5W (4R)	0.3% (5W)	-	-	-	30 mV	-	NO	14V	82 x 50 x 25	£ 3.95
SS110	10W (4R)	0.3% (5W)	-	-	-	60 mV	-	NO	24V	82 x 50 x 25	£ 4.65
SS120	20W (4R)	0.3% (10W)	-	-	-	80 mV	-	NO	34V	82 x 50 x 25	£ 7.15
SS125	25W (8R)	0.1% (10W)	-	70dB	-	140 mV	-	NO	50V	82 x 50 x 25	£ 7.85
SS140	40W (4R)	0.05% (20W)	-	70dB	-	300 mV	-	YES	45V	125 x 80 x 25	£ 6.50
SS160	60W (8R)	0.1% (30W)	20Hz 20kHz* 3dB	70dB	-	350 mV	-	YES	50V	125 x 80 x 25	£ 8.50
SS1100	100W (4R)	0.1% (50W)	20Hz-20kHz* 3dB	70dB	-	500 mV	-	YES	70V	125 x 80 x 25	£ 10.00

securely in the cavernous bosom of the GPO and should they ever be disgorged. Audiophile will be more than pleased to follow up and complete the project.

Anyway, only slightly daunted we shall proceed with what we have and consider the two amplifiers which did arrive (and the one on loan).

Our source for the listening tests was to be a Sony EL 7 Elcaset machine which gives reel-to-reel quality of reproduction without all the time-consuming drawbacks of that medium. When you're trying to compare several pieces of equipment such luxurious convenience is not to be scorned lightly.

I could never understand why Elcaset has not done better for itself. The Sony machines in particular offer a standard of reproduction far above that which any cassette machine achieves.

The reference amplifier was a Lecson AP3 II.

AL-120 BI-PAK

This unit arrives three quarters wrapped in a black heatsink with connection being made to pads at one end which protrude beyond the edge of said heatsink. The output pair (2N3055s) are bolted to the back of the heatsink and are hard wired into the circuit.

The quality of construction was generally high and in use the AL120s gave us no trouble at all. They drove the required speakers (Celestion/KEF) with no apparent distress and gave a sound technical account of themselves.

Crimson CE608

There's not really a lot to say about Crimson Elektrik that has not been said already. Their products are well constructed, well thought out and well thought off. The CE608 is no exception.

Crimson supplied us their unit completely assembled within the superb metalwork shown in the photograph which includes a PSU and stabiliser board to run one of their pre-amp modules.

The metalwork is black and in style looks not unlike a Quad 405 power amplifier unit.

ILP HY50

Since these are completely encapsulated we can offer no real comment on constructional finish. A mere five pins protrude from the metalwork along which travels all communication between the HY50 and the world.

Three In A Testbed


Once introduced to their proper PSUs all three amplifiers functioned well and gave no real problems at all. The ILP gave a poorer hum performance than the others regardless of how we tried to wire it, so the problem must lie within the black box.

Of the three the Crimson gave what must be regarded as the best overall performance. Its sound is very clean and it possesses good attack. However the BI PAK A2120 was not far behind and loses out mainly due to a slight lack of transparency when directly compared to the CE608. It has a warmer sound overall too and one that many people may well prefer.

Alas the ILP HY50 did not produce reproduction of the same quality as the other two. The test modules are about three years old though — our new review samples not having turned up in time — so things may well have improved here. We hope to give a listen to some more



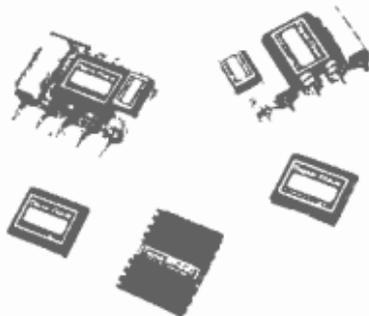BI PAKs AL-120 module, removed from its heatsink. The output pair are centrally on the reverse of the black heatsink.



The Magnum Audio range. Their power amp is shown in the centre foreground. Note that this is in fact a dual unit incorporating two amplifier circuits.

The ILP HY50. This is an encapsulated unit, and only five pins are required for connection purposes.



recent samples as soon as possible to confirm or deny this, but as it is the impression of one of a hard, gritty sound which was immediately distinguished in comparisons.

Conclusions

Well there it is. Not as complete as might have been, but very interesting (we hope) nonetheless. As for the comparisons we never got if the manufacturers agree we'll follow those up in the next few issues in Audiophile.

ETI



Left: the Sony EL-7 Elcass unit which proved the source for the listening tests. Somehow the machine has never received the attention it deserves for its performance.



Below: remind you of anything? Looking like a squashed 405 is the Crinson unit all boxed and set to go.

Suppliers

Magnum Audio Ltd
13 Hazeled Crescent
Luton
Beds
LU1 1DF

BI PAK Semiconductors
Dep: ETI
PO Box 6
Ware
Herts

Crinson Elektrik
1A Stamford Street
Leicester
LE1 6NL

Stirling Sound
37 Vauxhall Way
Shoeburyness
Essex

ILP Electronics Ltd
Graham Bell House
Roper Close
Canterbury
Kent
CT2 7EP

Kingsley TV
40/A2 Shields Road
Newcastle upon Tyne
NE5 1DR

CHROMASONIC electronics

your soundest connection in the world of components

DEPT. ETI 1, 56 FORTIS GREEN ROAD
MUSWELL HILL, LONDON N10 3NN
TELEPHONE: 01-883 3705

LOW POWER SCHOTTKY and TTL CMOS

BITS and PIECES

LOW POWER SCHOTTKY and TTL CMOS										BITS and PIECES									
1000	5	15	30	50	100	150	200	250	300	1000	10	20	30	40	50	60	70	80	90
1001	12	18	25	35	45	55	65	75	85	1002	12	18	25	35	45	55	65	75	85
1003	15	22	30	40	50	60	70	80	90	1004	15	22	30	40	50	60	70	80	90
1005	18	25	35	45	55	65	75	85	95	1006	18	25	35	45	55	65	75	85	95
1007	22	30	40	50	60	70	80	90	100	1008	22	30	40	50	60	70	80	90	100
1009	25	35	45	55	65	75	85	95	105	1009A	25	35	45	55	65	75	85	95	105
1010	30	40	50	60	70	80	90	100	110	1010A	30	40	50	60	70	80	90	100	110
1011	35	45	55	65	75	85	95	105	115	1011A	35	45	55	65	75	85	95	105	115
1012	40	50	60	70	80	90	100	110	120	1012A	40	50	60	70	80	90	100	110	120
1013	45	55	65	75	85	95	105	115	125	1013A	45	55	65	75	85	95	105	115	125
1014	50	60	70	80	90	100	110	120	130	1014A	50	60	70	80	90	100	110	120	130
1015	55	65	75	85	95	105	115	125	135	1015A	55	65	75	85	95	105	115	125	135
1016	60	70	80	90	100	110	120	130	140	1016A	60	70	80	90	100	110	120	130	140
1017	65	75	85	95	105	115	125	135	145	1017A	65	75	85	95	105	115	125	135	145
1018	70	80	90	100	110	120	130	140	150	1018A	70	80	90	100	110	120	130	140	150
1019	75	85	95	105	115	125	135	145	155	1019A	75	85	95	105	115	125	135	145	155
1020	80	90	100	110	120	130	140	150	160	1020A	80	90	100	110	120	130	140	150	160
1021	85	95	105	115	125	135	145	155	165	1021A	85	95	105	115	125	135	145	155	165
1022	90	100	110	120	130	140	150	160	170	1022A	90	100	110	120	130	140	150	160	170
1023	95	105	115	125	135	145	155	165	175	1023A	95	105	115	125	135	145	155	165	175
1024	100	110	120	130	140	150	160	170	180	1024A	100	110	120	130	140	150	160	170	180
1025	105	115	125	135	145	155	165	175	185	1025A	105	115	125	135	145	155	165	175	185
1026	110	120	130	140	150	160	170	180	190	1026A	110	120	130	140	150	160	170	180	190
1027	115	125	135	145	155	165	175	185	195	1027A	115	125	135	145	155	165	175	185	195
1028	120	130	140	150	160	170	180	190	200	1028A	120	130	140	150	160	170	180	190	200
1029	125	135	145	155	165	175	185	195	205	1029A	125	135	145	155	165	175	185	195	205
1030	130	140	150	160	170	180	190	200	210	1030A	130	140	150	160	170	180	190	200	210
1031	135	145	155	165	175	185	195	205	215	1031A	135	145	155	165	175	185	195	205	215
1032	140	150	160	170	180	190	200	210	220	1032A	140	150	160	170	180	190	200	210	220
1033	145	155	165	175	185	195	205	215	225	1033A	145	155	165	175	185	195	205	215	225
1034	150	160	170	180	190	200	210	220	230	1034A	150	160	170	180	190	200	210	220	230
1035	155	165	175	185	195	205	215	225	235	1035A	155	165	175	185	195	205	215	225	235
1036	160	170	180	190	200	210	220	230	240	1036A	160	170	180	190	200	210	220	230	240
1037	165	175	185	195	205	215	225	235	245	1037A	165	175	185	195	205	215	225	235	245
1038	170	180	190	200	210	220	230	240	250	1038A	170	180	190	200	210	220	230	240	250
1039	175	185	195	205	215	225	235	245	255	1039A	175	185	195	205	215	225	235	245	255
1040	180	190	200	210	220	230	240	250	260	1040A	180	190	200	210	220	230	240	250	260
1041	185	195	205	215	225	235	245	255	265	1041A	185	195	205	215	225	235	245	255	265
1042	190	200	210	220	230	240	250	260	270	1042A	190	200	210	220	230	240	250	260	270
1043	195	205	215	225	235	245	255	265	275	1043A	195	205	215	225	235	245	255	265	275
1044	200	210	220	230	240	250	260	270	280	1044A	200	210	220	230	240	250	260	270	280
1045	205	215	225	235	245	255	265	275	285	1045A	205	215	225	235	245	255	265	275	285
1046	210	220	230	240	250	260	270	280	290	1046A	210	220	230	240	250	260	270	280	290
1047	215	225	235	245	255	265	275	285	295	1047A	215	225	235	245	255	265	275	285	295
1048	220	230	240	250	260	270	280	290	300	1048A	220	230	240	250	260	270	280	290	300
1049	225	235	245	255	265	275	285	295	305	1049A	225	235	245	255	265	275	285	295	305
1050	230	240	250	260	270	280	290	300	310	1050A	230	240	250	260	270	280	290	300	310
1051	235	245	255	265	275	285	295	305	315	1051A	235	245	255	265	275	285	295	305	315
1052	240	250	260	270	280	290	300	310	320	1052A	240	250	260	270	280	290	300	310	320
1053	245	255	265	275	285	295	305	315	325	1053A	245	255	265	275	285	295	305	315	325
1054	250	260	270	280	290	300	310	320	330	1054A	250	260	270	280	290	300	310	320	330
1055	255	265	275	285	295	305	315	325	335	1055A	255	265	275	285	295	305	315	325	335
1056	260	270	280	290	300	310	320	330	340	1056A	260	270	280	290	300	310	320	330	340
1057	265	275	285	295	305	315	325	335	345	1057A	265	275	285	295	305	315	325	335	345
1058	270	280	290	300	310	320	330	340	350	1058A	270	280	290	300	310	320	330	340	350
1059	275	285	295	305	315	325	335	345	355	1059A	275	285	295	305	315	325	335	345	355
1060	280	290	300	310	320	330	340	350	360	1060A	280	290	300	310	320	330	340	350	360
1061	285	295	305	315	325	335	345	355	365	1061A	285	295	305	315	325	335	345	355	365
1062	290	300	310	320	330	340	350	360	370	1062A	290	300	310	320	330	340	350	360	370
1063	295	305	315	325	335	345	355	365	375	1063A	295	305	315	325	335	345	355	365	375
1064	300	310	320	330	340	350	360	370	380	1064A	300	310	320	330	340	350	360	370	380
1065	305	315	325	335	345	355	365	375	385	1065A	305	315	325	335	345	355	365	375	385
1066	310	320	330	340	350	360	370	380	390	1066A	310	320	330	340	350	360	370	380	390
1067	315	325	335	345	355	365	375	385	395	1067A	315	325	335	345	355	365	375	385	395
1068	320	330	340	350	360	370	380	390	400	1068A	320	330	340	350	360	370	380	390	400
1069	325	335	345	355	365	375	385	395	405	1069A	325	335	345	355	365	375	385	395	405
1070	330	340	350	360	370	380	390	400	410	1070A	330	340	350	360	370	380	390	400	410
1071																			

ETI BOOK SERVICE

How to order: Make cheques etc payable to ETI Book Service. Payment in sterling only please. Orders should be sent to ETI Book Service, PO Box 79, Maidenhead, Berks. All prices include P&P.

BEGINNERS

Beginners Guide to Electronics **£2.75**
Beginners Guide to Transistors **£1.75**
Electronic Measurement Techniques **£1.95**
Electronic Self-Teach **£1.40**
Beginners Guide to Integrated Circuits **£1.25**
Principles of Transistor Circuits **£1.75**
Understanding Electronic Circuits **£1.25**
Understanding Electronic Components **£1.25**
Beginners Guide to Radio Kits **£1.25**
Beginners Guide to Audio **£1.25**

COOKBOOKS

TV Typewriters Cookbook **£7.75**
CMOS Cookbook **£4.25**
Active Filters **£1.30**
IC Theory Cookbook **£7.50**
IC Top Amp Cookbook **£10.00**
Video Cookbook **£7.50**
FET Cookbook **£7.50**

APPLICATIONS

Advanced Applications for Postage Cable **£3.95**
Build Your Own Working Robot **£1.75**
Electronic and Physiological **£1.95**
Fire and Theft Security Systems **£1.95**
How To Build Probability Detectors and Meters **£1.95**
How To Build Electronic Mail **£1.25**
Linear Integrated Circuit Applications **£1.75**
Pulse and Clock Circuits Design & Applications **£1.95**
100 Electronic Alarm Projects **£1.75**
100 Semiconductor Projects for the Home **£1.25**
100 Integrated Circuit Projects for the Home **£1.25**
100 Thermostat Projects Using ICs **£1.25**
Handbook of IC Circuit Projects **£1.25**
Practical Electronic Project Building **£1.25**

TV AND HI-FI

Audio Handbooks **£1.95**
Casework for Recorders **£1.25**
Solid State Colour TV Circuits **£1.95**
Hi-Fi Loudspeakers and Loudspeaker Cables **£1.25**
How To Build Speaker Enclosures **£1.95**
Master Hi-Fi Installation **£1.25**

LOGIC

Logic Design Projects Using Standard ICs **£1.25**
Practical Digital Logic Using ICs **£1.25**
Designing With TTL Integrated Circuit Transistors **£1.25**
How To Use IC Circuit Logic Elements **£1.25**
170 CMOS Digital IC Projects for the Home Constructor **£1.25**
Understanding CMOS Integrated Circuits **£1.25**
Digital Electronic Circuits and Systems **£1.25**
MOS Digital ICs **£1.25**

COMPUTING

Microprocessors and Microcomputers **£1.25**
Microprocessors **£1.25**
Introduction to Microprocessors **£1.25**
Beginners Guide to Microprocessors **£1.25**
Beginners Basic Learning **£1.25**

OP-AMPS

Applications of Operational Amplifiers **£1.25**
100 Operational Amplifier Projects for the Home Constructor **£1.25**
Experiments With Operational Amplifier **£1.25**
Designing With Operational Amplifiers **£1.25**
Operational Amplifier Design and Applications **£1.25**
Op Amp Circuit Design & Applications **£1.25**

FIRST INSTRUMENTS

The Oscilloscope in Laboratory **£1.25**
Test Instruments for Technicians **£1.25**
Working With the Oscilloscope **£1.25**
Servicing With the Oscilloscope **£1.25**
Radio Testers and Audio Test Instruments **£1.25**

SERVICING

Electronic Troubleshooting **£1.25**
Rapid Servicing of Transistor Equipment **£1.25**
Tape Recorder Servicing Manual **£1.25**
Hi-Fi Radio Servicing Handbook **£1.25**

COMMUNICATIONS

Communication Systems: Signals & Noise **£1.25**
Digital Signal Processing: Theory & Applications **£1.25**
Electronic Communication Systems **£1.25**
Frequency Synthesis, Theory & Design **£1.25**
Principles of Communication Systems **£1.25**

THEORY

Introduction to Digital Filtering **£1.25**
Transistor Circuit Design **£1.25**
Essential Formulae for Electrical and Electronic Engineers **£1.25**
Modern Electronic Maths **£1.25**
Semiconductor Wireless Electronics **£1.25**
Fundamentals of Wireless Electronics **£1.25**
Colour Television Theory **£1.25**

REFERENCE

Transistor Tables (Includes power) **£1.25**
Electronic Engineers' Reference **£1.25**
Solid State Circuit Guide Book **£1.25**
Electronic Components **£1.25**
Electronic Diagrams **£1.25**
Indexed Guide to Modern Electronics **£1.25**
Internals and Transistor Selector **£1.25**
International FET Selector **£1.25**
Popular Valve Transmitter Techniques **£1.25**
Radio Valve and Semiconductor Dials **£1.25**
Master Transistor Integrated Circuit **£1.25**
World Radio TV Handbook 1978 **£1.25**
Radio TV and Audio Selector Reference **£1.25**
TV Technicians Bench Manual **£1.25**

MISCELLANEOUS

Integrated Electronics **£1.25**
Microelectronics **£1.25**
Practical Solid State ICs **£1.25**
Practical Electronic Projects for the Experimenter **£1.25**
Tutorial Circuit Assembly Pages **£1.25**

Fallen behind recent advances?
Just starting out?
Need a decent reference book?
ETI Book Service provides an easy
way of getting your hands
on the right title

ELECTROVALUE

FOR A GOOD DEAL BETTER THAN MOST

WE PAY POSTAGE on U.K. C.W.D. orders over £5.00 for value

WE GIVE DISCOUNTS on C.W.D. on U.K. orders over £10.00 on flat value over £10.00, 10% on flat value over £25.00.

WE GUARANTEE all goods are brand new, clean and in complete 100% fit - depends on supplier.

WE GIVE SERVICE and orders large or small - we use modern in-house storage, computer processing and double check parcelled shipments.

This month's
ELECTROVALUABLES

TOP SLIDING IRONS	75	25-30 CAMCOP 2200	200
VYNAIR	975	25-VICTORS	200
SWITCHES	50p	ROTECHMETERS	50p
LAMPS	10p	WIRE WOUNDS	20p
HEAT CLIPS	50p		
BITTERS FOODS			
	£3.55		
	£1.75		
	£6.50		
WIRE WOUNDS	20p		

WE ARE NATIONAL DISTRIBUTORS FOR



NASCOM COMPUTER KITS

MOTOROLA 6202 MICROPROCESSOR EVALUATION KIT

CATALOGUE 9

Yours for the asking - and it's FREE



TWO DEPOTS TO SERVE YOU NORTH AND SOUTH

ELECTROVALUE LTD

Head Office: Dept. ET14, 26 St. Jude's Road, Eaglefield Green, Egham, Surrey TW20 0HS. Telephone: Egham 3803. Telex: 244475.

Northwest Depot: 500 Barnage Lane, Barnage, Manchester M18 1NA (061) 432 8845

Shop hours: 10.30-4.45 (9.30-10.00) 1.0 p.m. Sat.

Clef Kits

Designed improved quality kits for Electronic Musical Instrument Construction



JOANNA 72 & 88 PIANOS
Clef Products Electronic Piano
Joanna 72 & 88 Pianos are
designed for the P.E. JOANNA which
incorporates 12 pins steps and key
levers - all in one available in
two different designs

P.E. STRING ENSEMBLE
This is a new design for the
A.J. Boothman Design for the
P.E. String Ensemble

Clef Products (Dept E T 1)
16 Mayfield Road, Bramhall, Cheshire SK7 1JU

PLEASE MENTION ETI
WHEN REPLYING
TO ADVERTS



Wilmslow Audio

THE firm for speakers!

Send 15p stamp for the world's best catalogue of Speakers, Drive Units, Kits, Crossover, etc., and discount price list.

- AUDAX ● BAKER ● BOWERS & WILKINS ●
- CASTLE ● CELESTION ● CHARTWELL ● COLES ●
- DALESFORD ● DECCA ● EMI ● EAGLE ● ELAC ●
- FANE ● GAUSS ● GOODMANS ● I.M.F. ●
- ISOPHON ● J.R. ● JORDAN WATTS ● KEF ● LEAK ●
- LOWTHER ● MCKENZIE ● MONITOR AUDIO ●
- PETRISS ● RADFORD ● RAM ● RICHARD ALLAN ●
- SEAS ● TANNAY ● V. DEUTONE ●
- WHARFEDALE ● SHACKMAN ● AUDIO MASTER ●
- TANGENT ● STAG ● YAMAHA

WILMSLOW AUDIO Dept. ETI

SWAN WORKS BANK SQUARE, WILMSLOW
CHESHIRE SK9 1HF

Discount Hi-Fi, etc. at
5 Swan Street and 10 Swan Street

TEL WILMSLOW 525559 FOR SPEAKERS
WILMSLOW 528213 FOR HI-FI

VIDEOGRAPH

Turn your colour television into a dual trace oscilloscope with this UHF colour modulator and video display generator.

THE PURCHASE of even the simplest oscilloscope is probably unjustified for most amateur electronics constructors. Other amateurs feel rightly or wrongly that their money is better spent on projects which other members of the family can appreciate!

Which ever category you belong to - or even if you are in the scope league already - Videograph will be found to be a fascinating and useful piece of equipment which will give many hours of pleasure.

Principle Of Operation

The Videograph makes use of the fact that the television screen is scanned from top to bottom every 20 mS. This is used as the effective



oscilloscope timebase, trace modulation being obtained by varying the timing between start of

each line and a fixed-length bright up-pulse.


Two complete circuits are required to produce a twin trace - and these are colour coded blue and orange respectively. These circuits are triggered by a common sync pulse generator, and further components generate an eight-stage background colour change, triggered by peak signals. There is also an internal frame-locked square wave generator which serves as a test waveform for injection into amplifiers and tape recorders.

Controls are provided for inverting one channel, freezing the background colour and switching a filter to give a relatively smooth music display.

Complete kits can be obtained from William Stuart Systems Ltd who hold the PCB copyright. They also produce a ready drilled cabinet. The heavy gauge anodised fascia plate is screen printed to improve finish and the PCBs are silk screened to aid construction.

Construction

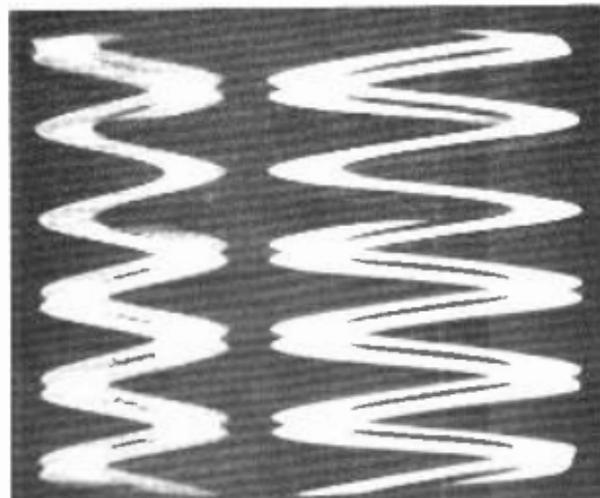Two printed circuit board assemblies are involved - one consisting of a UHF Colour Modulator and the other the



Sine wave generation with Videograph

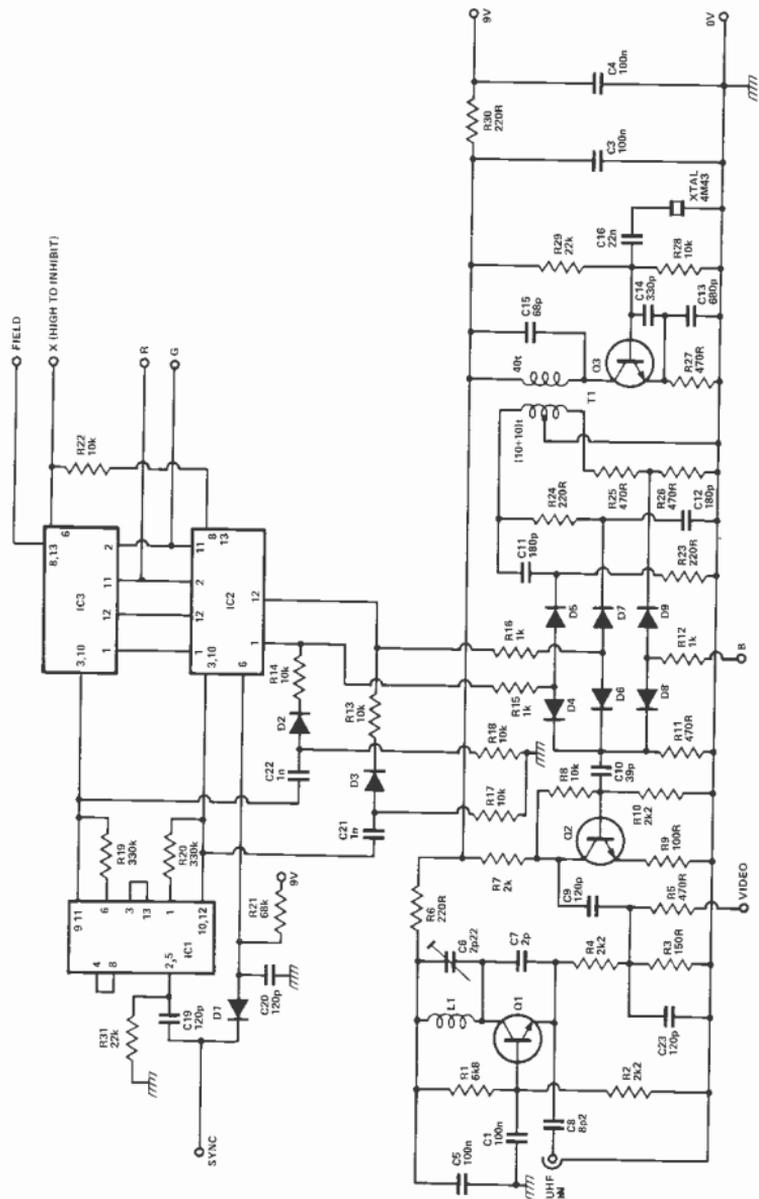


Fig 1. UHF Colour Modulator circuit diagram



A typical Videograph teletype picture

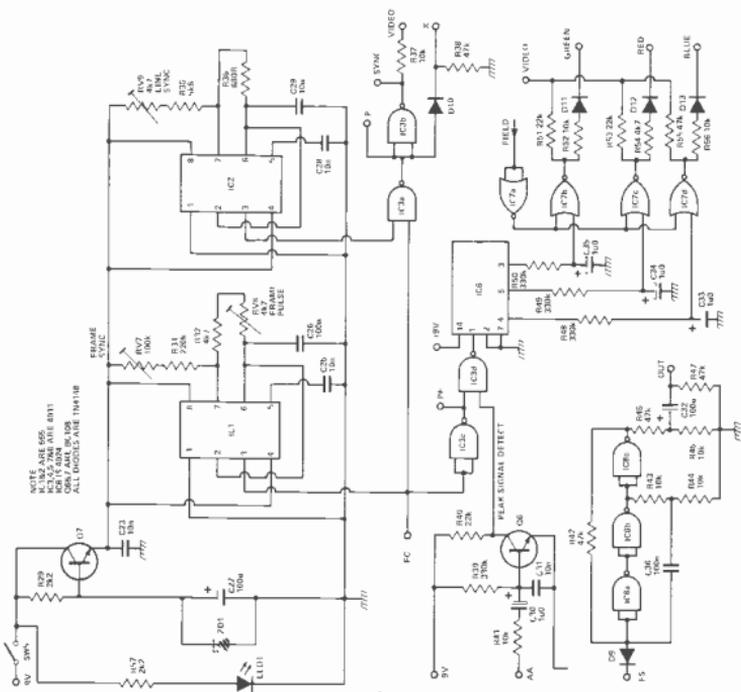


Fig. 3 Videograph generator circuit diagram

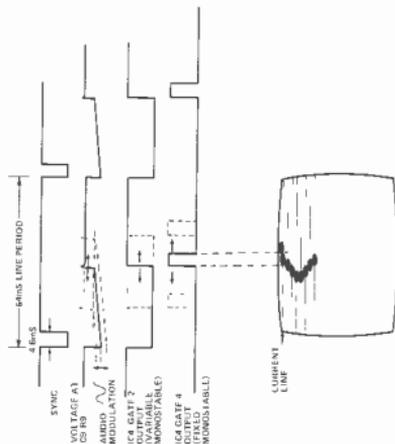


Fig. 5 Generating graphics with the Videograph.


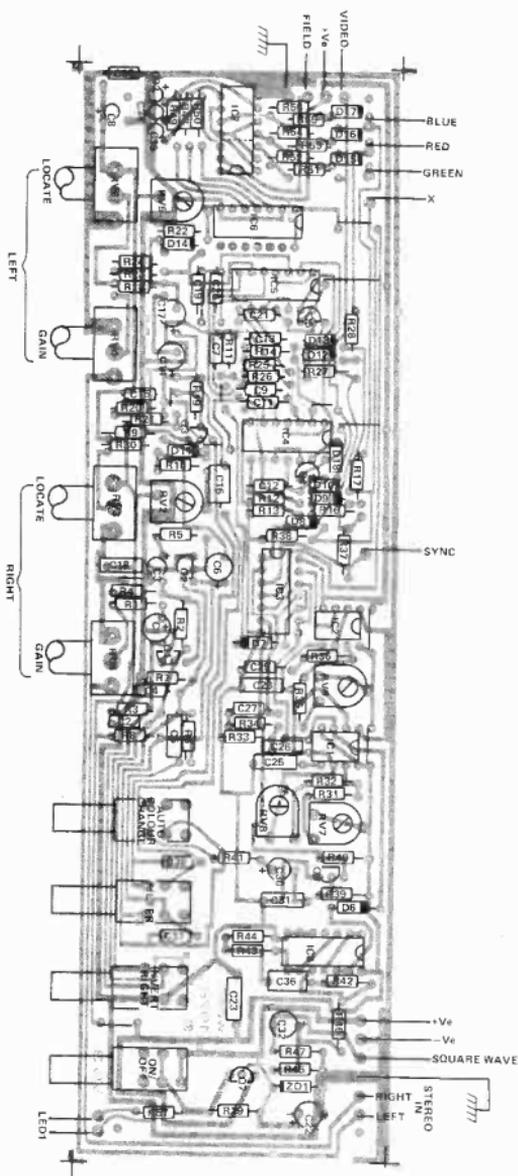


Fig. 6 Videograph generator component overlay

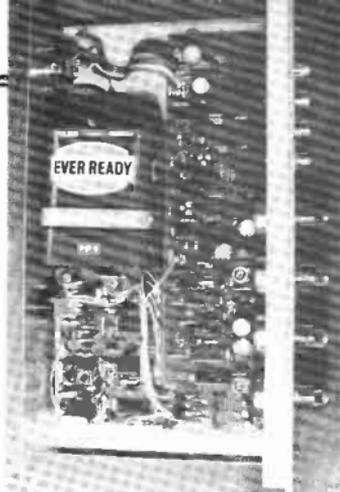

Circuit boards completed and installed in the Videograph chassis



No, it's not something from outer space!

BUYLINES

A complete kit of parts is available for this project from William Stuart Systems Ltd, Dower House, Herongate, Brentwood, Essex CM13 3SD. The PCBs remain their copyright and will be available only from them. All components are available separately, and the PCBs are normally supplied as a 'mini-kit' along with ICI-3 and ready wound coils. See advert elsewhere in this issue for prices.

pots are turned clockwise. Position both stripes centrally, then separate them using the LOCATE controls. At this stage the line sync (RV9) should be fine-adjusted to give perfect colour registration on the stripes.

IC7 may now be inserted (and the link removed!) to give the background colour change function the sequence being black, white, cyan, yellow green, mauve, blue, red.

ETI

Next
Month


Hobby Electronics

Power Supply Project



For a complete kit of parts for this project, see page 30. The kit includes a transformer, a bridge rectifier, a filter capacitor, and a voltage regulator. The kit also includes a printed circuit board (PCB) and a manual.

Electronic Doorbell

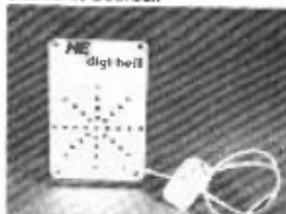

Not only is the sound great, but it also has a built-in door buzzer. The kit includes a push button, a speaker, and a transformer.

Personal communications



The messenger with the cash book is the telephone. The phone communication has become more and more personal and fun. There are many a variety of systems for communication. They are like the variety of systems for communication. They are like the variety of systems for communication.

Multimeters



The Multimeter introduced in this issue is a digital multimeter. It has a large LCD display and several control knobs. It is a very accurate and reliable instrument.

Electronic Music



The Translucent 2000 is a digital synthesizer. It has a keyboard and a digital display. It is a very accurate and reliable instrument. It is a very accurate and reliable instrument.

White Noise Effects Unit



The White Noise Effects Unit is a digital synthesizer. It has a control knob and a power switch. It is a very accurate and reliable instrument. It is a very accurate and reliable instrument.

Parking Meter Timer



The Parking Meter Timer is a digital synthesizer. It has a digital display and a coin slot. It is a very accurate and reliable instrument. It is a very accurate and reliable instrument.

Binary Numbers

The Binary Numbers are a digital synthesizer. They have a digital display and a coin slot. They are a very accurate and reliable instrument. They are a very accurate and reliable instrument.

The May issue will be on sale on April 13th

The Hobby Electronics Project Kit is available in a variety of sizes and prices.

L.P. ENTERPRISES

Room ET
313 Kingston Road, Ilford
Essex IG1 1PJ, England

From the representatives in Europe for America's leading Micro computer magazines and books, for the hobbyist, educational and professional alike, we bring you a little light browsing! Reading made a full waste. * Finance Bacon (1981 1828)

Micro 1.0 to 1.5 (complete sets)	£5.95
Micro 1.0 to 1.5 (single issues)	£2.50
Micro 1.5 to 2.0 (complete sets)	£11.95
Micro 1.5 to 2.0 (single issues)	£2.50
Micro 2.0 to 2.5 (complete sets)	£17.95
Micro 2.0 to 2.5 (single issues)	£2.50
Micro 2.5 to 3.0 (complete sets)	£23.95
Micro 2.5 to 3.0 (single issues)	£2.50
Micro 3.0 to 3.5 (complete sets)	£29.95
Micro 3.0 to 3.5 (single issues)	£2.50

8080 Programming for the Logic Designer	£2.50
8080 Programming for the Logic Designer	£2.50
8080 Programming for the Logic Designer	£2.50

Micro Computer Games	£5.50

8080 Instructional Handbook	£2.50
8080 Programming for the Logic Designer	£2.50
8080 Micro Logic Card	£1.95
8080 Micro Logic Card	£1.95

Micro Computer Games	£5.50

8080 Programming for the Logic Designer	£2.50
8080 Programming for the Logic Designer	£2.50
8080 Programming for the Logic Designer	£2.50

MAGAZINE SUBSCRIPTIONS	J.R.	Overseas
Micro 1.0 to 1.5 (3 issues)	£16.00	£17.00
Micro 1.5 to 2.0 (3 issues)	£20.00	£22.00
Micro 2.0 to 2.5 (3 issues)	£24.00	£26.00
Micro 2.5 to 3.0 (3 issues)	£28.00	£30.00
Micro 3.0 to 3.5 (3 issues)	£32.00	£34.00
Micro 1.0 to 1.5 (6 issues)	£32.00	£34.00
Micro 1.5 to 2.0 (6 issues)	£40.00	£42.00
Micro 2.0 to 2.5 (6 issues)	£48.00	£50.00
Micro 2.5 to 3.0 (6 issues)	£56.00	£58.00
Micro 3.0 to 3.5 (6 issues)	£64.00	£66.00
Micro 1.0 to 1.5 (12 issues)	£64.00	£66.00
Micro 1.5 to 2.0 (12 issues)	£80.00	£82.00
Micro 2.0 to 2.5 (12 issues)	£96.00	£98.00
Micro 2.5 to 3.0 (12 issues)	£112.00	£114.00
Micro 3.0 to 3.5 (12 issues)	£128.00	£130.00
MICRO 4502 Journal (6 issues)	£11.95	£12.95

HOW TO ORDER

Please note our prices include postage and packing but not insurance, if wanted add 12p for every £10 of books ordered. Make cheques PO's etc payable to

L.P. Enterprises.
CREDIT CARDS accepted
BARCLAYCARD VISA/ACCESS
DINERS CLUB/AMERICAN EXPRESS

Phone 01-583 1001 for Credit Card orders (24 hour service)

Send to address above
 Indicate Payment Method

All Orders must be Prepaid
 Total Enclosed £

My cheque P O I M O is enclosed in Sterling on U.K. Bank

Charge to Barclaycard/Visa/Access/Diners American Express

Credit Card No _____ Expiry Date _____

Name _____

Address _____

Signature _____

POSTCODE _____

Micro 1.0 to 1.5 (complete sets)	£5.95
Micro 1.0 to 1.5 (single issues)	£2.50
Micro 1.5 to 2.0 (complete sets)	£11.95
Micro 1.5 to 2.0 (single issues)	£2.50
Micro 2.0 to 2.5 (complete sets)	£17.95
Micro 2.0 to 2.5 (single issues)	£2.50
Micro 2.5 to 3.0 (complete sets)	£23.95
Micro 2.5 to 3.0 (single issues)	£2.50
Micro 3.0 to 3.5 (complete sets)	£29.95
Micro 3.0 to 3.5 (single issues)	£2.50

Some Common 8080 Programs	£6.50
Computer Programs that Work in BASIC	£2.50

Introduction to Personal and Business Computing	£4.95
Get to Know your Own Personal Computer	£4.95
How to Profit from your Personal Computer	£4.95
Reference Book of Personal Home Computing	£4.95
How to Buy a Personal Computer	£3.95
Understanding Microcomputers & their Applications	£3.95

Micro BASIC	£7.50
Micro BASIC	£2.50
Micro BASIC	£2.50
Micro BASIC	£2.50

Micro Computer Games	£5.50
Micro Computer Games	£5.50
Micro Computer Games	£5.50

BASIC Software Library	£11.50
Micro Computer Games	£5.50

8080 Standard Manual	£9.95
8080 Standard Manual	£9.95
8080 Standard Manual	£9.95

MAGAZINE BACK ISSUES	£1.75
Micro 1.0 to 1.5 (3 issues)	£1.75
Micro 1.5 to 2.0 (3 issues)	£1.75
Micro 2.0 to 2.5 (3 issues)	£1.75
Micro 2.5 to 3.0 (3 issues)	£1.75
Micro 3.0 to 3.5 (3 issues)	£1.75
Micro 1.0 to 1.5 (6 issues)	£1.75
Micro 1.5 to 2.0 (6 issues)	£1.75
Micro 2.0 to 2.5 (6 issues)	£1.75
Micro 2.5 to 3.0 (6 issues)	£1.75
Micro 3.0 to 3.5 (6 issues)	£1.75
Micro 1.0 to 1.5 (12 issues)	£1.75
Micro 1.5 to 2.0 (12 issues)	£1.75
Micro 2.0 to 2.5 (12 issues)	£1.75
Micro 2.5 to 3.0 (12 issues)	£1.75
Micro 3.0 to 3.5 (12 issues)	£1.75
MICRO 4502 Journal (6 issues)	£1.75

Gm REVISITED

Nothing to do with American car manufacturers Gm is in fact a throw-back from the days of valves, now finding a new lease of life with up-to-date semiconductor devices. K. T. Wilson explains . . .

MANY A LONG YEAR ago when transistors were an item which hadn't been dreamt of by science fiction writers we all used valves and we all knew the magic letters Gm. Gm stood for a quantity called mutual conductance and it measured an important feature of the valve from which we could work out how much voltage gain we could get out of a given bottle. Well, the years have passed and valves are dead for many purposes, but Gm lives and is back working for us.

It is odd that Gm should have gone out of fashion for so long because the idea of Gm is even more useful in transistor amplifier circuits than it ever was in valve circuits. Still, the idea seems to be coming back in a big way, so let's take a look at it.

Mutual conductance of any electronic device means the ratio of signal current at the output to signal voltage at the input. For a transistor this is the ratio I_c/V_{be} (the collector current and V_{be} the voltage between base and emitter). Fig 1. The squiggle above the letters means that it's AC signal voltage and currents, we're talking about not the steady bias voltages and currents.

Using Gm therefore allows us to treat not a valve or transistor as a generator of signal currents, the amount of signal current being $G_m V_{in}$. Now a current generator means a device which will deliver its current into any load, high or low. No valve or semiconductor is really like this, but for most of the uses we make of transistors, the idea of a current generator is not far from the mark.

Current Generators

If a transistor were a perfect current generator, it would have an infinite resistance at its output. That means just that a signal voltage applied between the collector and the emitter would cause no collector signal current.

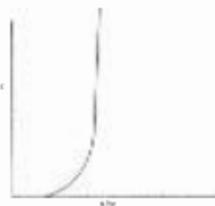


Fig 1 Mutual conductance, I_c/V_{be} for a transistor

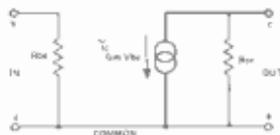


Fig 2 An equivalent circuit for a transistor

Of course, it's not quite correct, but not far from the truth. A bit of collector signal current does flow, but not as much as you'd expect, such as would flow if there were a resistor of around 40k between collector and emitter.

Now, the usefulness of all this is that it allows us to draw an equivalent circuit for a transistor. An equivalent circuit is a circuit made of simple components which behaves in just the same sort of way as some device which is in reality much more complicated. A simple equivalent circuit for a transistor is, therefore, as shown in Fig 2. It consists of a current generator which generates a signal current $G_m V_{be}$ and a resistor of about 40k in parallel. This simple circuit accounts for the size of the signal current at the output (the collector) and the output resistance between collector and emitter.

How does this help us? Quite a lot if we remember all the time that equivalent circuits are about signal currents, not about bias currents. As far as signal currents are concerned, the positive supply line of an amplifier is just as earthed as the earth line. Why? Because in the power supply there's a smoothing capacitor of several thousand microfarads connected between the +ve and -ve lines. As far as DC is concerned, this capacitor is an insulator, but for AC signals the capacitor is just a short circuit, shorting the +ve line to the -ve line. When we connect a load resistor between the collector terminal of a transistor and the positive line, then, as far as signals are concerned, the load resistor is connected between collector and emitter. Draw this into the equivalent circuit, and the result is Fig 3. Back in the old days of valves (nostalgia's corner, this!) we found the sum of these two resistors in parallel, which was

$$\frac{R_{ce} \cdot R_L}{R_{ce} + R_L}$$

and then the voltage signal out was just the current signal times this resistance (Ohm's Law still rules, OK?) $G_m V_{in}$

$$\frac{G_m R_{ce} R_L}{R_{ce} + R_L}$$

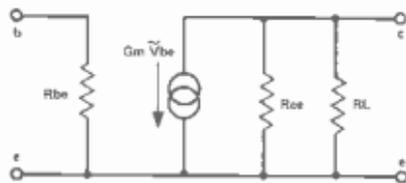


Fig 3 For AC signals, a load resistor connected between collector and positive supply behaves as if connected between collector and emitter

$$G_m = \frac{q}{kT} I_c$$

q = CHARGE CARRIED BY AN ELECTRON
 k = BOLTZMANN'S CONSTANT
 T = TEMPERATURE IN KELVIN SCALE
 I_c = STEADY (BIAS) COLLECTOR CURRENT

Simple Silicon

One of the things that makes life simpler in these days of silicon transistors is that the quantity R_{oe} (the output resistance of the transistor) is quite a large value compared to most of the load resistors we use. An output resistance (the usual symbol nowadays is h_{o}) of 40k is quite a bit larger than the 3k Ω or so we use as a load, so that most of the signal current from the transistor is through this resistor in the equivalent circuit. That simplifies the output voltage to $G_m R_L$, so that the gain of a transistor amplifier is just $G_m R_L$.

If it is as easy as that, why don't we see it in text books? The reasons are historical — we did start with silicon transistors and a transistor unlike a valve doesn't have a constant value of G_m . If we plot a graph of collector current against base voltage as in Fig 1, the result is not the nice straight line we get when we plot such a graph for a valve, or the not too crooked line we get when we plot the graph for an FET, but a very curved line indeed. This indicates that the value of G_m is not constant, but a value which changes as the current through the transistor changes. This, coupled with the rather low output resistance of the early germanium transistors seemed to spoil the fate of G_m for good.

Ebers Moll

A few years back, though, the Ebers Moll equation was noticed. You've never heard of it? You're not alone, very few text books mention it, and some mention it without explaining it. Very briefly, it's an equation which links the collector current with the V_{be} value for a transistor. In other words, it's the equation for finding G_m . Now the full equation is a fearsome looking thing full of mathematical symbols you may never have seen before. It repays close attention, though, because most of the symbols are of quantities that are pretty well constant, and only two of them vary very much. One of them is the steady bias current I_c , and the other is temperature. As it happens, temperature for the purposes of the Ebers Moll equation is measured in the Kelvin scale which starts at the absolute zero of temperature around -273°C . Room temperature is therefore around 293K (no degrees sign) in the Kelvin

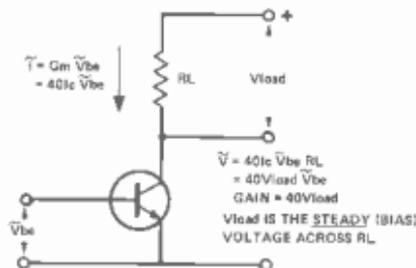


Fig 4 Transistor circuit with load resistor (R_L); G_m can be replaced by $40I_c$

scale, and a few degrees above or below doesn't make much difference to the equation.

That leaves I_c as the one thing that really affects G_m and the relationship works out at approximately

$$G_m = 40 I_c \quad (I_c \text{ in mA})$$

Put in words, that means we can take a G_m value of 40 times the steady bias collector current in milliamperes. For a bias current of 1 mA, the G_m value of a transistor is 40 mA/A. Too good to be true? Looks it, but it really does apply to any silicon transistor, apart from a few freak types.

This brings back the G_m idea in a big way, and we can forget a lot of the old formulae we once used in calculating the design of transistor amplifiers. The fact that G_m is not constant but varies with the bias current is, oddly enough, a help rather than a hindrance.

Gain

Going back to our equivalent circuit, and ignoring the large output resistance of the transistor, we can now write $40 I_c$ in place of G_m (Fig 4). This makes the gain of a transistor with load resistor R_L become $40 I_c R_L$. But I_c in this equation is the steady bias collector current, and so $I_c R_L$ must be the steady DC voltage across R_L , the load resistor. This makes calculating the gain of transistor amplifiers with resistive loads a bit easier than falling off a log. Pick a value of voltage across the load resistor, multiply by 40, and that's your value of gain!

For example, we very often design voltage amplifiers so that about half of the supply voltage is dropped across the load resistor. For a 9 V supply, that's 4.5 V. Do this, and you can expect a voltage gain of $40 \times 4.5 = 180$ times. Don't believe it? It works all right, and tests on a single transistor amplifier confirm it as a rule of thumb. You don't, of course, expect to get a gain of exactly 180 in the case we illustrate, there are all sorts of tolerances on load resistors apart from anything else, but you're never far out, that's what a rule of thumb is for.

When you couple a single transistor amplifier to another stage, of course, that's another story. You may have set the gain of the first stage to 180 times, but not all of its output signal ends up usefully at the input of the



CLICK ELIMINATOR

Part two of the Click Eliminator article, presented here, is in fact a redesign of the project leading to better performance and lower cost.

In the January issue of ETI we presented a design for a click eliminator unit. However, between that issue and the time for the February ETI — in which we were to complete the project we found several disturbing inconsistencies which would have rendered the design's repeatability doubtful—to put it mildly.

These problems mainly concerned the area around Q1, IC9 and IC10. The biasing arrangement for Q1, and its function within the circuit means that the adjustments are very very critical indeed. Our prototype operated satisfactorily, especially in its breadboarded form, but was too dependent upon too many variables for us to be happy with the project.

Taking Aim

The aim then, as now, was to present a design for a unit which would remove the clicks and scratches from damaged LPs without impairing the music material contained therein.

Operation was to be indicated by an LED, and threshold of operation was to be variable to make the Eliminator flexible in use.

However, as we said, development work has continued since initial publication, and while we felt that there was nothing wrong with the aims of the project, our method of realising them left something to be desired.

Change Of Track

Accordingly, we are presenting here an alternative design, and

recommend our readers to construct this in lieu of the design shown in Part One of the article. A comparison between both circuits will show this version to be greatly simplified, and using components which will make construction cheaper.

For example, the 570 has been replaced with a 4016, which is closed to the signal for a short period of time to blank the click signal.

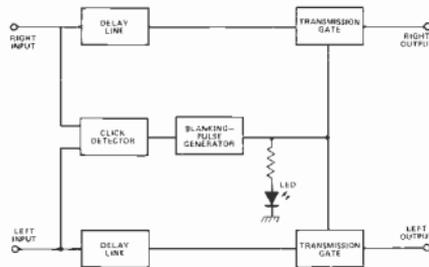


Fig 1. Basic block diagram for Click Eliminator Mk 2


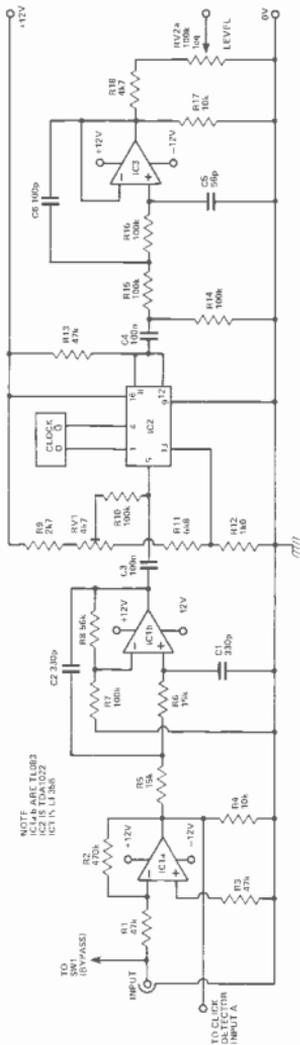


Fig. 2. Circuit diagram for the audio pre-amplifier and delay line sections of the Eliminator unit. Note that only one channel is shown, but both are identical.

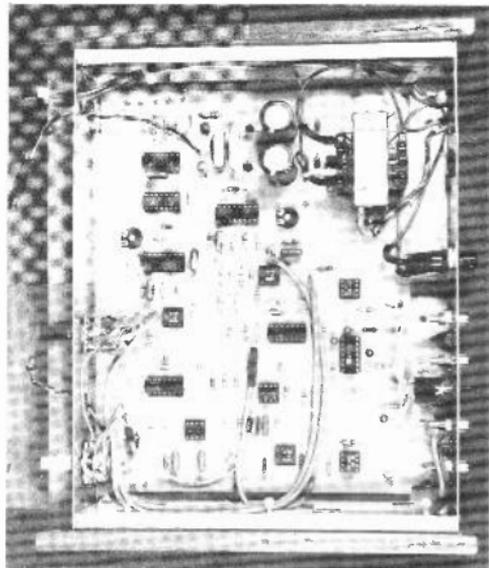

HOW IT WORKS

The full circuit of the right pre-amp and delay line block is shown in Figure 2, the left channel circuit block is identical.

The input signal from the pick-up is fed into IC1a, which is wired as a $\times 10$ inverting amplifier with an input impedance of 47k. The output of this stage is fed to the click detector (IC2). IC2 is a 741 configured as a second order low pass Butterworth filter with a turnover point of about 18 kHz. This stage also has a small amount of gain in its pass band.

The output of the Butterworth filter is fed into pin-9 of IC3, which has TDA 1022 as its input stage. IC3 is a 741 configured as an inverting amplifier. The R9-R11, R12 and R13 network at the input of the IC is used to set pin-13 at

about 1.5 volt above ground to ensure maximum dynamic range on the delay line, and to bias pin-5 into class A at minimum distortion. The delay line is clocked by synchronous and phase signals to pins 1 and 4 at a few hundred kHz, to provide a total delay of about 1 ms.

The output of the delay line is taken via C6 to another second order Butterworth filter (IC3), which removes the unwanted, high frequency, clock signals that are imposed on the audio signal by the delay line, and the cleaned up signals are then sent to the speaker blanking circuit via volume control RV2.

As the block diagrams of Fig. 1 will show, the basic remains unchanged. The incoming audio is delayed by a TDA 1022, long enough for the circuit to detect the click and generate a pulse which shuts off the transmission gate (4016) as the click arrives.

The waveforms shown in Fig. 8 give an indication of the timing of the circuit, and the manner in which the blank period is made to straddle the click signal.

Circuits and Components

Figures 2-6 show the schematic for the Click Eliminator. Figure 2 is the audio input and delay line circuit. Figure 3 shows the click detection and blanking pulse generation components. Inputs A and B come from points A and B marked on the left and right audio inputs respectively.

Circuits 5 and 7 are the output blanking (and bypass) and system clock respectively. The latter is referred in the audio circuit simply as Q and Q̄.

Construction

The unit is assembled onto a single PCB and so construction is really quite straightforward. Assemble the board carefully, remembering to fit resistors and capacitors first, and ICs last. Sockets are best used for these devices especially the high cost items. This will facilitate checking and servicing should this be needed.

The easiest place to make a mistake is in fitting the polarised components — electrolytics, diodes ICs etc so check these carefully. It is best to build up the PSU first and check this before connecting to the rest of the circuit.

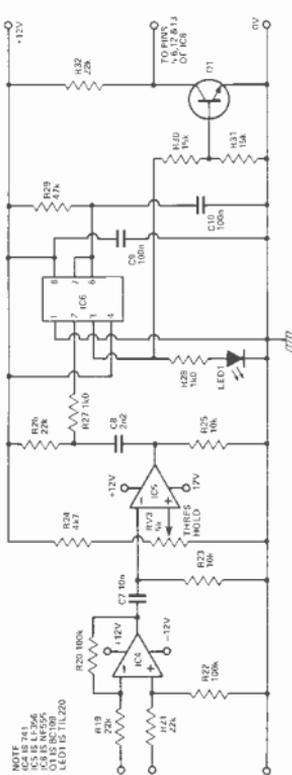


Fig. 3. Circuit of the click detector section of the Mk 2 Click Eliminator. The LED flashes to indicate operation.



Fig. 4 (a). Above: the waveform of the Click Eliminator blanking pulse straddling the click (see Fig. 4(b)). Below: the combined waveform showing the blank period inserted into the music.



HOW IT WORKS

The full circuit diagram of the click detector block, which incorporates a 'click identifier', a threshold detector and a blanking pulse generator, is shown in Figure 3. IC1, IC2 and IC3 are all 7418 7418 ICs. IC1 has a number of unique characteristics. It has fast attack and decay times, and its output is commonly 7418 7418 in high-frequency components. Also, it appears to have a stereo pick-up head as a set of recorded anti-phase signals, since it can pass either normal or inverted signals without any phase and equalise predominantly horizontal movement of the stylus. The ETI Click Eliminator uses these unique phase characteristics to provide its primary means of click identification.

Such as it takes from the outputs of the two channel pre-amplifiers (IC1), Fig. 2, and are passed to one or other of the two inputs for IC1. IC1 is configured as a differential amplifier or 'subtractor' and has a gain of about five on each input. The action of this IC is such that it amplifies the anti-phase 'click' signals, but tends to cancel the predominantly in-phase recorded signals, so that the output is really a blanked 'clicks'. This signal is passed to threshold detector IC2, which is wired as an open loop voltage comparator, with its output normally at positive saturation.

The 'threshold' level of IC2 can be adjusted and parallel to the output head of the IC2, which is wired to a 'clean' record. Then, each time that a 'click' arrives, the output of IC2 switches to negative saturation, to produce a large negative-going pulse. This pulse is used to trigger monostable IC3, which produces a narrow pulse which drives 'click indicator' LED-1, and which drives output transistor Q1 to saturate for the duration of the 5 ms pulse. The output of Q1 appears as a blanking pulse, and is fed to the click blanking circuit of Fig. 4.

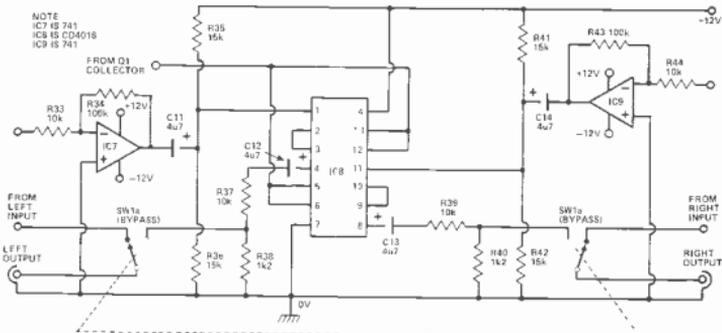


Fig 5. Click blanking circuit. Note that SW1 is the bypass switch.

HOW IT WORKS

The circuit of the click blanking block is shown in Figure 5. Circuit operation is fairly straightforward. The output of each channel is taken from the volume control (Fig 2) and is fed through a times ten inverting amplifier (IC7 or IC8), and is then passed to one half of IC9, a 4016 quad bilateral switch. In each channel, two of the 'internal' switches of the 4016 are wired in series, and are normally held on by the high control signal from the collector of Q1 (Fig 4), but turn off for 3 ms when a blanking pulse arrives from the click detector circuit. The output of each channel is then passed on to the outside world via a divide-by-ten (approx) attenuator network.

Thus, during 'clean' parts of the record the output signal from the delay line is passed through the click blanking circuit of Fig 5 via the two series-connected

The power supply is a straightforward design based on a pair of three-terminal IC regulators, which provide plus or minus twelve volt outputs. LED 2 is a panel-mounted component, which indicates the power on state.

switches of IC9 with negligible loss of gain, but in the presence of a 'click' the 4016 switches of IC9 open 1 ms before the arrival of the click and remain open for about 3 ms, thus replacing the click with an imperceptible 'blank'.

Note in the circuit that the inputs of IC9 are biased at half-supply volts to enable

the IC to pass signals with a minimum of distortion when operated from a single-rail power supply. The 4016 IC suffers from a certain amount of control-signal breakthrough, by using a times ten amplifier before the input and a divide-by-ten attenuator after the output of the IC, this breakthrough is reduced to insignificant levels relative to those of the basic audio signal.

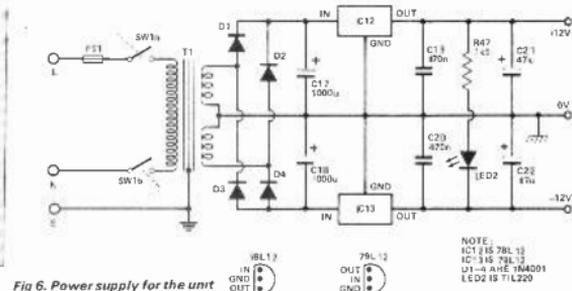


Fig 6. Power supply for the unit

Next assemble and check the audio circuitry. Make sure a signal is present at the level control RV2a and RV2b. Normally IC8 gates will be open, and so an audio output should be present at the phono sockets if all is well.

If no output is present, check the audio through to RV2, and if a signal is present here, the fault probably lies with IC6 and Q1. Disconnecting the base of Q1 will restore output if this is the case.

Over the Threshold

In use, the unit is connected between the output of a record player pick-up

and the input of a stereo amplifier. Volume control RV2 should be adjusted so that no perceptible difference occurs in audio sound levels when the bypass switch is switched in and out. Pre-sets RV1 and RV101 should be adjusted for minimum distortion on the Right and Left channels respectively. Threshold control RV3 should be adjusted, in use so that LED 1 just operates in the presence of a 'click'.


It should be noted that the relative amplitude of a click is proportional to the velocity of the record track past the pick-up head, and decreases as the head moves towards the centre of the disc, the threshold control may

consequently need occasional readjustment as the record progresses through its play.

There is no equalisation circuitry within our design, and so it cannot be used in place of the preamp in your system, it must be used in front of it instead.

When playing damaged LP's simply advance the Threshold control RV3 from its minimum setting until the click is removed. This is the correct setting.

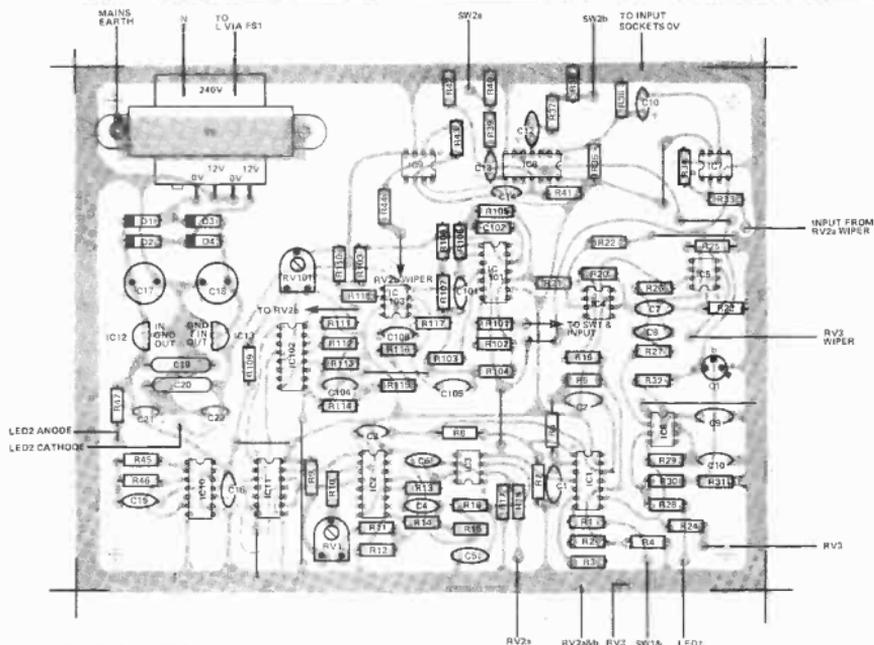LED 1 will indicate the unit operation, and if it flashes on musical peaks, chances are you have the threshold control set too high and are removing some of the signal as well.



BUYLINES

Being composed mainly of standard components, the Eliminator should pose most component shops no problems. The LF 356 is available from Watford in case of difficulty.

Fig 7. Component overlay for the Click Eliminator unit. Note that all the components bar the potentiometers mount on this PCB. The operation LED is also best front panel mounted.

PARTS LIST

RESISTORS (all ¼W 5%)

R1, 3, 13	
R2, 45	47k
R2	470k
R4, 17, 23, 25,	
33, 37, 39, 44	10k
R5, 6, 30, 31	
35, 36, 41, 42	15k
R7, 10, 14,	
15, 16, 20,	
22, 23, 34,	
43	100k
R8	56k
R9	24k
R11	6k8
R12, 27, 28	1k
R18, 24	44k
R21, 26, 32	22k
R38, 40	142
R46	180
R47	1k5
Resistors 101-118 for RH channel identical to R1-18	

POTENTIOMETERS

RV1	4k7 preset
RV2	100k log twin gang
RV3	5k Lin

CAPACITORS

C1, 2, 15	330p polystyrene
C3, 4, 9,	
10, 16	100n polyester
C5	56p ceramic
C6	100p ceramic
C7	10n polyester
C8	2n2 polyester
C11-14	47µ 25V electrolytic
C17, 18	1000µ 25V electrolytic
C19, 20	470n polyester
C21, 22	47µ 25V electrolytic

SEMICONDUCTORS

IC1	T1083
IC2	TDA1022
IC3, 5	LF 356
IC4, 7, 9	741
IC6	555
ICB	4016
IC10	4011
IC11	4013
IC12	78L12
IC13	79L12
Q1	BC 109
D1-D4	1N 4001
LED1, 2	TIL 220

MISCELLANEOUS

240/12-0-12 transformer (100mA), fuse (3A) and holder, case to suit, DPDT mains switch control knobs, PCB

TRANSAM

The exciting new TRITON Personal Computer

Basic in Rom a powerful 7k Tiny basic resident on board makes Triton unique easy to use and versatile

Graphics: 64 Graphic characters as well as full alpha numerics

Single Board Holds up to 8k of memory 4k RAM and 4k Rom supplied with 3k ROM and 2k RAM

Memory Mapping 2 mode VDU 1 D or memory mapped for animated graphics

Cassette Interface: crystal controlled Modern tape I/O with auto start stop + named file search

UHF TV Interface On board uhf modulator plugs into TV aerial socket

Comes complete with keyboard case full power supply quality through hole plated PCB full (118 page) instruction manual. A powerful 1k monitor & 2k tiny basic in Eprom All IC sockets

All components can be bought separately so you can start construction on a low budget. Full details of prices and discounts are shown in our new 1979 catalogue

EXPANSION BOARDS

Mother Board

A new 8 slot Triton motherboard is now available based on Eurobus it allows easy expansion & has its own meaty power supply

Bk Static Ram

Eurocard size 160 x 100mm Bk Static RAM fully buffered on board regulation & decoding Uses 4k (1k x 4) Static RAMs Just plugs into motherboard for memory expansion

Bk Eprom Board

Designed to take 8 x 2708 Eproms on the Triton bus Don't forget our programming service



Triton Kit £286
Motherboard Kit £50
Bk RAM Card £97
Bk EROM Card TBA and Feb.
Full details in Catalogue 30p + SAE

COMPUTER PRODUCTS NEW LOW PRICES

Part No.	Price						
1010001	18	1010002	21	1010003	25	1010004	28
1010005	18	1010006	21	1010007	25	1010008	28
1010009	18	1010010	21	1010011	25	1010012	28
1010013	18	1010014	21	1010015	25	1010016	28
1010017	18	1010018	21	1010019	25	1010020	28
1010021	18	1010022	21	1010023	25	1010024	28
1010025	18	1010026	21	1010027	25	1010028	28
1010029	18	1010030	21	1010031	25	1010032	28
1010033	18	1010034	21	1010035	25	1010036	28
1010037	18	1010038	21	1010039	25	1010040	28
1010041	18	1010042	21	1010043	25	1010044	28
1010045	18	1010046	21	1010047	25	1010048	28
1010049	18	1010050	21	1010051	25	1010052	28
1010053	18	1010054	21	1010055	25	1010056	28
1010057	18	1010058	21	1010059	25	1010060	28
1010061	18	1010062	21	1010063	25	1010064	28
1010065	18	1010066	21	1010067	25	1010068	28
1010069	18	1010070	21	1010071	25	1010072	28
1010073	18	1010074	21	1010075	25	1010076	28
1010077	18	1010078	21	1010079	25	1010080	28
1010081	18	1010082	21	1010083	25	1010084	28
1010085	18	1010086	21	1010087	25	1010088	28
1010089	18	1010090	21	1010091	25	1010092	28
1010093	18	1010094	21	1010095	25	1010096	28
1010097	18	1010098	21	1010099	25	1010100	28

MICROPROCESSORS

8080A	£6 33	8085	£23
8080	£10 00	8502	£15
780 CPU Ps	£15 80	80C86	£10
780A CPU P.	£21 00	TM59901	£30

VERO

We stock a complete range of Vero products and accessories for the Vero computer user. 5100 cards, 1 megabyte keyboard cassettes & consoles, up to 2 megabyte 100% and 2 megabyte card frames and Bk easy Dink connectors & ribbon cables - Newton open 6 axis & week



CENTRAL LONDON SHOWROOM

If you're in town, visit our showroom in Chapel Street next to Edgars Road tube station. We have Tritons on display plus a comprehensive range of components and accessories, specifically for personal computer users. Books, magazines, cables plus much more.

NEW 1979 CATALOGUE

SEND 30p + SAE

MEMORY 9 SUPPORT

SUPPORT	VOLTS	PRICE	PRICE	PRICE	PRICE	PRICE	PRICE
1011	2.2V	100	100	100	100	100	100
1012	2.2V	100	100	100	100	100	100
1013	2.2V	100	100	100	100	100	100
1100	2.2V	100	100	100	100	100	100

HOME COMPUTING

Books, Tapes, Data and Cassettes. We have a good selection, mainly on micro and personal computing with regular shipments of Byte, Dr Dobbs etc. direct from US & A. The latest Triton Software available on cassette or using Triton User Club membership is £4 per annum.

PROGRAMMER

We use the latest Data I/O Model 19 Programmer, mainly for Z80 and we offer a programming and editing service from our SHOWROOM. Fast, reliable and safe. Burn in your own firmware. Full editing and copying facilities.

TRANSAM

TRANSAM COMPONENTS LTD.
12 CHAPEL STREET
LONDON NW1
TEL: 402 8137

ETIPRINTS

ETIPRINTS are a fast new aid for producing high quality printed circuit boards. Each ETIPRINTS sheet contains a set of etch resistant rub down transfers of the printed circuit board designs for several of our projects.

ETIPRINTS are made from our original artwork ensuring a neat and accurate board. We thought ETIPRINTS were such a good idea that we have patented the system (patent numbers 1445171 and 1445172).

PARTS LIST

Shown below is the listing for the last year's ETIPRINTS

Earlier sheets are available, ring Tim Salmon for details.

003	Race Track Game Hydrator Throw Freezer Alarm	Jan 78 Jan 78 Dec 77	010	Bench Amplifier Firecracker Alarm Marker Generator LED Dice Worshipdog (2 PCBs) Stars & Dots PSU	Project Book Six	016	Star Timer XMAS Gen Wheel of Fortune	Sept 78
004	Metal Locator Mk II Ultrasonic Tx/Rx 5 Watt Stereo Amp (modified) Metronome Shutter Tama	Feb 78 Feb 78 Jan 77 Feb 78 Feb 78	011	Noise Generator General Preamp Flash Trigger Compufer Active Crossover (2 PCBs)	Project Book Six	017	Complex Sound Gen Tele Ball Extender Power Budge	Oct 78
005	Op-Amp Supply Frequency Shifter LCD Potentiometer Light Dimmer (3 times)	Mar 78	012	Disc Lightshow Stereo Simulator Dry Ice Thermometer	Project Book Six	018	RF Power Meter Proximity Switch Audio Oscillator (2)	Oct 78 Oct 78 Nov 78
006	CMOS Switched Preamp From Exclusion meters P 5 U 545 Boards twice	'Electronics' Tomorrow	013	Amplifier Module Amplifier PSU Enjolaze Enjolaze PSU	Book 5 v	019	Car Alarm (2) Wyle Temp (2) Curve Tracer	Dec 78 Dec 78 Dec 78
007	Star Trek Radio CD Ignition CCD Phaser White Line Follower	May 78 May 78 May 78 April 78	014	Sweet Game Switch Oscillator Burglar Alarm GSR Monitor	Project Book Six	020	Digital Tacho Module Digital Dot	Jan 79 Jan 79 Jan 79
008	Tank Battle Helping Hand	May 78	015	URF Detector Tough Fender (twice) Ebert's clock	July 78 July 78 Aug 78	021	Tape Slide Switch Tape Noise Limiter Light Tacho	Feb 79
009	AM/FM Radio Bridge Oscillator CMOS Stars & Dots	June 78				022	Logic Trigger Power Meter Headlight Devis (x2)	Mar 79

HOW IT WORKS



Lay down the ETIPRINT and rub over with a soft pencil until the pattern is transferred to the board. Peel off the backing sheet carefully making sure that the resist has transferred. If you've been a bit careless there's even a 'repair kit' on the sheet to correct any breaks!

BUY LINES

ORDER TODAY

Send a cheque or P O (available to FTI Magazine) to:

ETI PRINT, ETI MAGAZINE
25/27 OXFORD STREET, LONDON W1R 1RF

75p INC P & P

7400	10p	7460	12p	7413	90p	74195	50p	4055	130p	CA 3140	80p	LM 3909 N	85p	TBA 480 Q	200p
7401	10p	7470	25p	74138	100p	74196	50p	4056	120p	LF 356	80p	MC 1310 F	140p	TBA 520 Q	200p
7402	10p	7475	20p	7414	80p	74197	50p	4060	100p	LF 357	80p	MC 1312 P	180p	TBA 530 Q	200p
7403	10p	7477	25p	74142	80p	74198	100p	4066	35p	LM 271 H	25p	VC 1314 P	180p	TBA 540 Q	200p
7404	12p	7478	25p	74143	270p	74199	80p	4069	12p	LM 300 TR	170p	MC 1315 F	230p	TBA 560 Q	250p
7405	12p	7479	25p	74144	270p	74200	80p	4070	12p	LM 301 AH	30p	MC 50396	850p	TBA 580 Q	280p
7406	25p	7476	25p	74145	85p	74200	110p	4071	12p	LM 304	200p	MM 5311	380p	TBA 641 A	112
7407	25p	7480	40p	74147	100p	7451	2	4072	12p	LM 307N	65p	MM 5318	480p	TBA 700 Q	280p
7408	12p	7481	85p	74148	90p	CMOS	4081	4073	12p	LM 308 TOS	100p	NE 529 K	150p	TBA 720 Q	225p
7409	12p	7482	75p	74150	65p	4000	12p	4082	12p	LM 308 DIL	100p	NE 555	25p	TBA 750 Q	200p
7410	12p	7483	75p	74151	45p	4001	12p	4083	12p	LM 309 K	100p	NE 556	90p	TBA 800	80p
7411	15p	7484	70p	74153	70p	4006	80p	4084	12p	LM 310 D5	150p	SN 7627 B	150p	TBA 810	100p
7412	15p	7485	80p	74154	45p	4007	12p	4510	70p	LM 311 T01	32p	SAD 1124	1500p	TBA 820	100p
7413	25p	7486	50p	74155	45p	4007	14p	4511	70p	LM 312 K	40p	SN 7660 B	75p	TCA 920 Q	280p
7414	45p	499	130p	74156	45p	4009	30p	4518	65p	LM 324	70p	SN 76003 N	110p	TCA 970 D	230p
7415	25p	7490	25p	74157	45p	4011	12p	4520	65p	LM 319	80p	SN 78013 N	110p	TCA 270 B	230p
7416	25p	7491	40p	74160	55p	4012	12p	4528	80p	LM 348 N	90p	SN 76013 ND	125p	TCA 700	300p
7417	12p	7492	35p	74161	55p	4013	30p	4583	70p	LM 380	80p	SN 76023 N	110p	TCA 4800 A	450p
7418	20p	7493	70p	74162	55p	4015	30p	LINEAR		LM 381 N	90p	SN 76023 ND	125p	TDA 1008	350p
7419	20p	7495	45p	74163	55p	4016	30p	AV1 8500	450p	LM 382	90p	SN 76073 N	150p	TDA 1034	450p
7420	20p	7496	45p	74164	60p	4017	30p	CA 3039	70p	LM 391	180p	SN 7627 N	150p	TDA 7002	300p
7421	22p	7497	120p	74165	60p	4018	50p	CA 3046	60p	LM 505	25p	SN 7628 P	180p	TDA 2020	300p
7422	22p	74100	80p	74167	180p	4019	40p	CA 3045	225p	LM 709 C	40p	SN 7860 B	75p	TCA 960	120p
7423	25p	74104	40p	74170	100p	4020	50p	CA 3044	250p	LM 710 TOS	40p	TAA 300	100p	KF 320	250p
7424	12p	74105	40p	74173	80p	4023	12p	CA 3076	250p	LM 710 OIL	65p	TAA 390	190p	KR 2706	450p
7425	20p	74107	25p	74175	80p	4024	12p	CA 1080	75p	LM 723 TOS	40p	TAA 550	35p	KR 2207	450p
7426	20p	74108	25p	74176	80p	4024	40p	CA 3084	250p	LM 723 OIL	40p	TAA 570	220p	KR 2208	800p
7427	22p	74109	25p	74177	80p	4025	12p	CA 3085	85p	LM 733	120p	TAA 6618	140p	KR 2215	850p
7428	25p	74110	25p	74178	80p	4025	12p	CA 3086	85p	LM 741	20p	AA 700	350p	KR 2567	250p
7429	25p	74111	25p	74179	80p	4027	40p	CA 3088	190p	LM 748	40p	AA 730	350p	KR 4136	150p
7430	25p	74112	25p	74180	80p	4028	40p	CA 3089	190p	LM 743 N	100p	TAD 100	150p	KR 4202	150p
7431	28p	74108	100p	74181	130p	4029	50p	CA 3090/3090P	190p	LM 1458	100p	TAD 110	130p	KR 4712	150p
7432	20p	74116	75p	74182	80p	4030	30p	CA 3123 E	130p	MC 3080	75p	TBA 120 S	60p	KR 4739	150p
7433	20p	74119	75p	74183	130p	4032	80p	CA 3140	100p	LM 1900	55p	TBA 120 T	85p	ZN 114	100p
7434	45p	74120	80p	74189	120p	4033	80p	IN 2148	Driver by ITT. Texas. 100 for £1.50						
7435	40p	74121	80p	74190	120p	4034	80p	Star C	Ram 2102 1024 x 1 bit 450 nano sec £1.00 each						
7436	60p	74122	35p	74191	120p	4034	80p	21	2 250 x 4 B + 450 nano sec £2.50						
7437	60p	74123	35p	74192	120p	4034	80p	Muata	Ultrasonic Triadultrasonics 40KHz £2.00 each £3.50 pair						
7438	60p	74124	35p	74193	120p	4034	80p	As per ref no. in spec. add tax							
7439	60p	74125	35p	74194	120p	4034	80p								
7440	60p	74126	35p	74195	120p	4034	80p								
7441	60p	74127	35p	74196	120p	4034	80p								
7442	60p	74128	35p	74197	120p	4034	80p								
7443	60p	74129	35p	74198	120p	4034	80p								
7444	60p	74130	35p	74199	120p	4034	80p								
7445	60p	74131	35p	74200	120p	4034	80p								
7446	60p	74132	35p	74201	120p	4034	80p								
7447	60p	74133	35p	74202	120p	4034	80p								
7448	60p	74134	35p	74203	120p	4034	80p								
7449	60p	74135	35p	74204	120p	4034	80p								
7450	12p	74136	35p	74205	120p	4034	80p								
7451	12p	74137	35p	74206	120p	4034	80p								
7452	12p	74138	35p	74207	120p	4034	80p								
7453	12p	74139	35p	74208	120p	4034	80p								
7454	12p	74140	35p	74209	120p	4034	80p								

FANTASTIC NEW GAMES

NEW CHESS CHAMPION - 6 LEVELS

£89.50

NEW

IN COLOUR

STAR CHESS

BE FIRST with

ELECTRONIC MASTERMIND

£59.95

WITH SOUND EFFECTS

£14.90

Mastermind Ltd
27 Solihull Road, London W22 1LT
Tel: 01-898-9736

T. POWELL
209 ST PAULS ROAD, HIGHWAY CENTER, LONDON W11 2EL 01 226 1489
Retail Access - Tel: 01 226 1489

NO DISCO SYSTEM IS COMPLETE WITHOUT...

CITRONIC MM 313 MAKER

PIEZO HORNS

BULGIN OCTAL PLUGS AND SOCKETS

PROJECTORS

STARLINE 343

PLUS MANY DISCO ACCESSORIES

Roger Squire's DISCO GEAR

85.00 + A.V.

data sheet.....

IC SURVEY

THERE ARE VLR's many IC's available on the market today and new devices seem to appear daily (probably hourly). This barrage of innovations can be rather daunting, particularly to the newcomer to electronics. The following article tries to untangle some of the confusion by surveying IC technology in four groups of devices: Op Amps, audio amplifiers, multipliers, and oscillators.

Operational Amplifiers (Op Amps)

There are many different types of OP Amp and they are manufactured by several different companies. Most of these companies produce standard Op Amp devices but they put their own part number on them.

In recent years, the trend has been to develop IC's with more than one Op Amp inside. This has resulted in a range of dual and quad Op Amp packages. Texas have brought out a range of JFET Op Amps. These are pin for pin compatible with standard types, but they are different in that they have FET inputs giving them a very high input impedance.

Chart 1 shows comparative performance for several standard Op Amp types. The parameters chosen are the most important ones when selecting Op Amps.

Audio Amplifiers.

Several manufacturers produce monolithic medium power amplifiers for audio use. This makes the design of small audio

amplifier sections relatively easy. There are some pitfalls to watch out for. IC amplifiers can easily destroy themselves if the power rails are high or if insufficient heat sinking is provided. There are now quite a wide range of devices, some of which are shown in Chart 2.

Multipliers

The range of multiplier IC's has never been so large, but recently a few more have been added to the list, partly inspired by the needs of telephone companion systems. These systems produce a better signal to noise ratio over the line. Another and very common noise reducer (a special multiplier) is the Delta R chip. This unfortunately is not obtainable under license.

Oscillators

There are many oscillator IC's that can provide waveforms with periods of several hours to tens of nano seconds. For high frequencies, such there is the SM746124 at 85 MHz and the LM7475 at 100 MHz. There are TTL devices, they are not linear and are intended for use in feedback circuits. The 74124 is a well known linear VCO. Teledyne also make a wide range of VCO modules. The SM5632 and the 5288 are the same device. They are both pseudo random oscillators that is they oscillate but the waveform is so complex that the resultant output just sounds like noise. Chart 3 details the most common types.

CHART 1 OP AMP — ABRIDGED PERFORMANCE S = Single D = Dual Q = Quad

Op amp type	Input offset voltage mV	Input bias current nA	Type of input structure	Band width MHz	Slew rate V/NS	Voltage gain dB	Maximum supply voltage V	CMRR dB	Op	Comments
709	2	300	NPN	1	0.25	90	±18	90	S	Needs frequency compensation
307	2	70	NPN	1	0.25	100	±18	90	S	Internal frequency compensation
301	2	70	NPN	10	0.5	100	±18	90	S	Needs frequency compensation
741	2	80	NPN	1	0.5	106	±18	90	S	Internal frequency compensation
748	1	120	NPN	10	0.5	103	±22	90	S	A decompensated 741
308	2	1.5	NPN	3	0.5	110	±18	100	S	Low supply current drain 0.3mA Needs frequency compensation Very low differential input voltage range
318	4	150	NPN	15	50	106	±20	100	S	Very low differential input voltage range Sometimes needs frequency compensation
747	2	80	NPN	1	0.5	106	±18	90	D	Internal frequency compensation
1458	1	80	NPN	1	0.8	103	±18	90	D	Internal frequency compensation
4136	0.5	40	PNP	3	1.0	110	±18	100	D	Low noise
3900 3401	Current inputs	30	Current sinks	2.5	0.5 20	70	±18	—	Q	Current balancing amplifier
324	2	45	PNP	1	0.5	100	+30	70	Q	Ground sensing inputs Output voltage can go to ground Low power 0.5mA drain per IC
3403	2	150	PNP	1	1.2	100	+36	90	Q	Ground sensing inputs Class AB output Output voltage can go to ground Low power 3mA drain per IC
348	1	30	NPN	1	0.5	103	±18	90	Q	Low power 2.4mA drain per IC Class AB output

CHART 2 MONOLITHIC PREAMPLIFIER AND POWER AMPLIFIER SURVEY		Manufacturer	Part No.	Description	Package	Frequency Range									
Part Number	FAIRCHILD NA 739 NA 706	Tolladine	9400	LN VCO	14 pin DIL	0.2 to 85 MHz	Pulse and low data rate								
			XR2208C	LN VCO - AS + FSX	16 pin DIL	2000 1 sweep range D 0.1 Hz to 1 MHz									
MOTOROLA MC 1306	0.5 watt audio amplifier 12V operation	EXAR	KR2205C	LN VCO	16 pin DIL	7.1 sweep range up to 4MHz	Pulse and low data rate								
			KR2207C	+AM VCO	14 pin DIL	1000 1 sweep range D 0.1 Hz to 1 MHz									
			KR2208C	LN VCO	8 pin DIL	1000 1 sweep range D 0.1 Hz to 1 MHz									
NATIONAL SEMICONDUCTOR		Raytheon General Signetics	RC4151 8038 NE555	LN VCO VCO T mod Oscillator Qual 555 -ln VCO	8 pin DIL 14 pin DIL 8 pin DIL 14 pin DIL 8 pin DIL	0.1 Hz to 1 MHz 0.01 to 1 MHz Lp to 100kHz 10 ³ sweep 1MHz max	Pulse and low data rate								
LM 370 LM 371 LM 378 LM 379 LM 380 LM 381 LM 382 LM 384 LM 386 LM 387 LM 388 LM 389 LM 390 LM 1103	AGC switch amplifier Dual 2 watt amplifier Dual 4 watt amplifier Dual 5 watt amplifier 2.5 watt mono amplifier Dual low noise preamplifier Dual mono amplifier Low noise dual preamplifier 0.35 watt mixing amplifier plus npn transistor amplifier 1.0 watt low voltage amplifier Stereo preamplifier	National Semiconductor	LM3908	Led Flasher VCO + TTL Buffer	8 pin DIL	Up to 15 kHz	LED or loudspeaker drive FTL								
			LM371	Dual 2 watt amplifier	14 pin DIL	0.01 to 1 MHz		Pseudo random NOISE							
			LM378	Dual 4 watt amplifier	8 pin DIL	Lp to 100kHz			Synthesized sinewave Telephone 2 tone sinewaves						
			LM379	Dual 5 watt amplifier	14 pin DIL	Up to 200MHz				random NOISE					
			LM380	2.5 watt mono amplifier	8 pin DIL	0.01 to 1 MHz					Telephone 2 tone sinewaves				
			LM381	Dual low noise preamplifier	8 pin DIL	Up to 15 kHz						LED or loudspeaker drive FTL			
			LM382	Dual mono amplifier	14 pin DIL	0.01 to 1 MHz							Pseudo random NOISE		
			LM384	Low noise dual preamplifier	8 pin DIL	Lp to 100kHz								Synthesized sinewave Telephone 2 tone sinewaves	
			LM386	0.35 watt mixing amplifier plus npn transistor amplifier	14 pin DIL	Up to 200MHz									random NOISE
			LM387	1.0 watt low voltage amplifier	8 pin DIL	0.01 to 1 MHz									
LM388	Stereo preamplifier	14 pin DIL	Up to 15 kHz	LED or loudspeaker drive FTL											
LM389	Low noise dual preamplifier	8 pin DIL	Lp to 100kHz		Synthesized sinewave Telephone 2 tone sinewaves										
LM390	0.35 watt mixing amplifier plus npn transistor amplifier	14 pin DIL	Up to 200MHz			random NOISE									
LM1103	1.0 watt low voltage amplifier	8 pin DIL	0.01 to 1 MHz				Telephone 2 tone sinewaves								
LM1103	Stereo preamplifier	14 pin DIL	Up to 15 kHz					LED or loudspeaker drive FTL							
RAYTHEON RC 4138 CA 4739	Quad low noise op amp Low noise stereo preamplifier	Motorola	MC14412						FSK Modem 2 out of 5 tone ENCODER	16 pin DIL	16 pin DIL	For fast frequency operation - as in switches			
MC14410			DSC - 2 ^{1/2} bit det						6 pin	16 pin DIL					
SIGNETICS NE 540 NF 542	Power drive op amp Dual low noise preamp	Mo group	MC 4451						FSK - 3 ^{1/2} bit 2 ^{1/2} bit det	6 pin	16 pin DIL	For fast frequency operation - as in switches			
			MC 1451						4-programmable Osc 11 or	16 pin DIL	16 pin DIL				
RCA CA 3052 CA 3134	Stereo preamp TV sound IF and audio output 1.13 watts	†Tegostis	MC 1451						4-programmable Osc 11 or	16 pin DIL	16 pin DIL				

ABBREVIATIONS

LN - Line
VCO - Voltage Controlled Oscillator
IC - Current Controlled Oscillator

AM - Amplitude Modulation
FSK - Frequency Shift Keying
DL - Dual In Line

CHART 4 OP AMP - ABRIDGED PERFORMANCE

Op amp type	offset voltage mV	Input bias current nA	Type of input structure	Band width MHz	Slew rate V/μs	Voltage gain dB	Maximum supply voltage V	CMRR dB	Qty IC	Comments	
RC4739	2	40	PNP	3	1	110	±18	100	D	Raytheon device only Low noise audio amplifier	
uA739	1	300	NPN	10	1	86	±18	90	D	Fairchild device only Low noise audio amplifier Needs frequency compensation	
LM381	Not applicable	Not applicable	NPN	15	-	112	±20	-	D	Low noise amplifier Internally compensated	
CA3130	8	0.005	MOSFET	15	10	110	+16	90	S	Ground sensing inputs Very high input impedance Needs frequency compensation	
CA3140	8	0.010	MOSFET	4.5	9	100	+36	90	S	Ground sensing inputs Very high input impedance	
CA3160	6	0.005	MOSFET	4	10	110	+15	90	S	Ground sensing inputs Very high input impedance	
NE531 RC4531	2	400	NPN	10	35	96	±22	100	S	Very fast op amp Needs frequency compensation	
CA3080	0.4	1μg- 100	NPN	2	50	-	±18	110	S	OTA device Programmable gain Current output	
CA3094	0.4	1μg- 300	NPN	30	50	-	±12	110	S	OTA device Programmable power switch/ amplifier	
TL080	15	0.4	JFET	3	13	83	±18	70	S	JFET input op amps, with fast slew rate and wide bandwidth [TEXAS]	
TL081	15	0.4	JFET	3	13	83	±18	70	S		Pm for pin replacement for 748
TL082	15	0.4	JFET	3	13	83	±18	70	D		741
TL083	15	0.4	JFET	3	13	83	±18	70	D		1458
TL084	15	0.4	JFET	3	13	83	±18	70	D		747

Pm for pin replacement for

748

741

1458

747

324

TELEPHONE CALL TIMER Submitted by Mr A. M. Tucker of Dorchester.

TO CARRY OUT its function, which is to display the cost of individual calls, and also to keep a running total of all metered calls, the circuit must add the amount of the unit charge (at present 3p) to each register when the call commences, and subsequently at the end of each charge period. This period will vary for peak standard and cheap times, and with distance. Provision should be made for altering the settings of the counting circuits if there is a change in the Post Office charges.

Various circuits were considered, and this was considered to be as cheap to make as any for the facilities provided, as although there is a large number of ICs, the bulk are low priced.

The two sets of figures are circulated in a single shift register, the digits being interlaced, ie, the least significant figure in one register is followed by the least significant figure in the other register, and then by the next figure in the first register, and so on.

In order to be able to adjust the unit charge, and the periods available per unit, the outputs of the dividers are connected to sockets into which leads from the inputs of the resetting gates are plugged. These sockets, plus "parking places" for spare gates, can be made from IC sockets or soldercon pins in plastic supports. To prevent damage to the pins of sockets when cutting into sections, push into a piece of rigid foam plastic. The wider leads are just lengths of connecting wire. Solid core is suitable, if stranded wire is used, tin the end and check that it is thin enough to insert into the socket.

In the interests of economy, small low consumption displays have been used. If larger displays are required, it will probably be necessary to add segment drivers. The

drivers should then be supplied from the unregulated side of the supply, and S1 made a double-pole switch.

The 9-volt standby battery is essential, as otherwise the total cost register would be cleared in the event of a mains failure. In order to reduce consumption during idle time, the counters IC1 and IC2 and their associated gates, the oscillator IC21 and the display buffers and driver IC23-IC26 are switched off by S1. It is unwise to try to include other ICs, as some inputs may be high. In any case, with the oscillator off, power consumption is very low in the remaining circuits.

It may simplify the wiring of a 4001 and a 4011 are substituted for the 4069. One NOR gate can be used instead of IC20a and IC22a, and a choice of ICs is available for the other inverters.

The meter can be adapted for battery power only by including a 4518 to divide the 10 kHz oscillator frequency down to 100 Hz, and doubling the division in IC1 by shifting each flying lead one place to the right. Setting the oscillator frequency exactly can be carried out either by comparing the 100 Hz output with 50 Hz from the mains on an oscilloscope, or by varying the setting until the charges are incremented at 10 second intervals for long distance calls at peak rates.

Decoupling capacitors for pulses in the supply lines may be required. While CMOS is less exacting than TTL in this respect, 10n non inductive capacitors should be fitted across the supply pins of ICs at the end of supply lines, and across each of the more complex ICs.

A flashing LED is provided as an indication (and reminder!) that the timing circuits are operating.

ETI

HOW IT WORKS

TO commence timing a call, SW1 is switched on, and SW4 and SW5 set. When the person replies, SW2 is closed. This removes the reset from IC1 and IC2, which start counting 50Hz mains pulses. At the same time IC15 is triggered, producing a 7ms pulse which clears the single call register—the digits being selected by IC21b and IC18b.

At the termination of the pulse, Q goes low and triggers IC8b. The Q output of this IC then goes low for 7ms or until reset by IC7, which is enabled by the high Q output of IC8b, and is clocked through IC9b each time the LSB of the registers are present at Q, and Q₂ of IC11, until the output connected to IC22e goes high, when IC6b resets and inhibits IC7.

The output from IC7 is fed through IC3 to the "carry" of the adder (IC14) driving the

LSB. Three cycles of the shift registers are required to increment the registers by 1p.

SW4 and SW5 set the time available for one unit. For present Post Office rates, IC1 is preset to divide by 250, giving an output pulse every 55.1C2a divides by two, three or twelve, IC2b by three or twelve.

A pulse stretcher (R3, C3, D5) is included to ensure IC1 resets.

When the timing pulse reaches IC20d, IC8b is retriggered, clocking up another unit charge. The two sets of figures are stored in four 8 stage shift registers IC12 and IC13 and are circulated through the adder (IC14). The digits are selected for display by the driver IC11.

Clocking of these ICs and IC16 is effected by the 10k oscillator IC21a, b. The exact frequency of this is not important, but must be related to the length of the moonbeams

IC16 and IC8b.

IC13a is a buffer and the laser clocking pulse required by the shift registers is provided by IC13d.

When the call is completed, SW2 is switched to off, and the resets on IC1 and IC3 go high, stopping the count. The cost of the call remains in the register until SW3 is closed for the next call. At the end of a quarter, the "total cost" register can be cleared by pressing SW3. C3, D4, R4 provide a "power-on" reset which ensures that the flip-flops are correctly set initially, and that IC7 is not started in the middle of a charge period.

When no more calls are expected to be made for a while, SW1 is opened, dropping current consumption to a very low figure so that a battery backup can be used against mains failure.

PARTS LIST

RESISTORS all 5% 1/4W

R1, 2 14-20 1k

R3 12k

R4, 5, 10 100k

R6, 7, 9, 11, 13 1M

R8 1M5

R12 3M3

R21 22 1k5

POTENTIOMETERS

PV1 500k ± 10% trimpot

CAPACITORS

C1 2 470µ electrolytic

C3 47p ceramic

C4

C5, 7

plus various 10n ceramic decoupling capacitors

SEMICONDUCTORS

D1 4x1N4001 or 1A bridge

D2, 5 1N914 or equivalent

IC1 4046

IC2 4520

IC3 8 4062

IC4 4075

IC8 4098

IC9, 11 4022

IC8, 16, 21 4027

1µ electrolytic

1n polyester

IC9 20

IC10 4027

IC12, 13 4008

IC14 4008

IC18 4511

IC17-18 4081

IC21 4011

IC22 4069

IC23 24 4050

IC25 26 74592

IC27 LM78L13

D-type HP5082-2414

MISCELLANEOUS

100MA transformer, etc.

This new feature is open to all our readers. It exists as a showcase for projects YOU have designed and built. We pay full ETI page rates for any designs we publish. We must stress that these designs must have been built by you. To further this end, we are giving preference to those which arrive at our offices with photographs, or which can be photographed by us.

Initially a simple draft outlining the idea behind the project and what the unit can do is all that is required. Photographs should be included at this stage.

Write to 'Readers Designs,' ETI Offices, 25-27 Oxford Street, London, W1R 1RF.

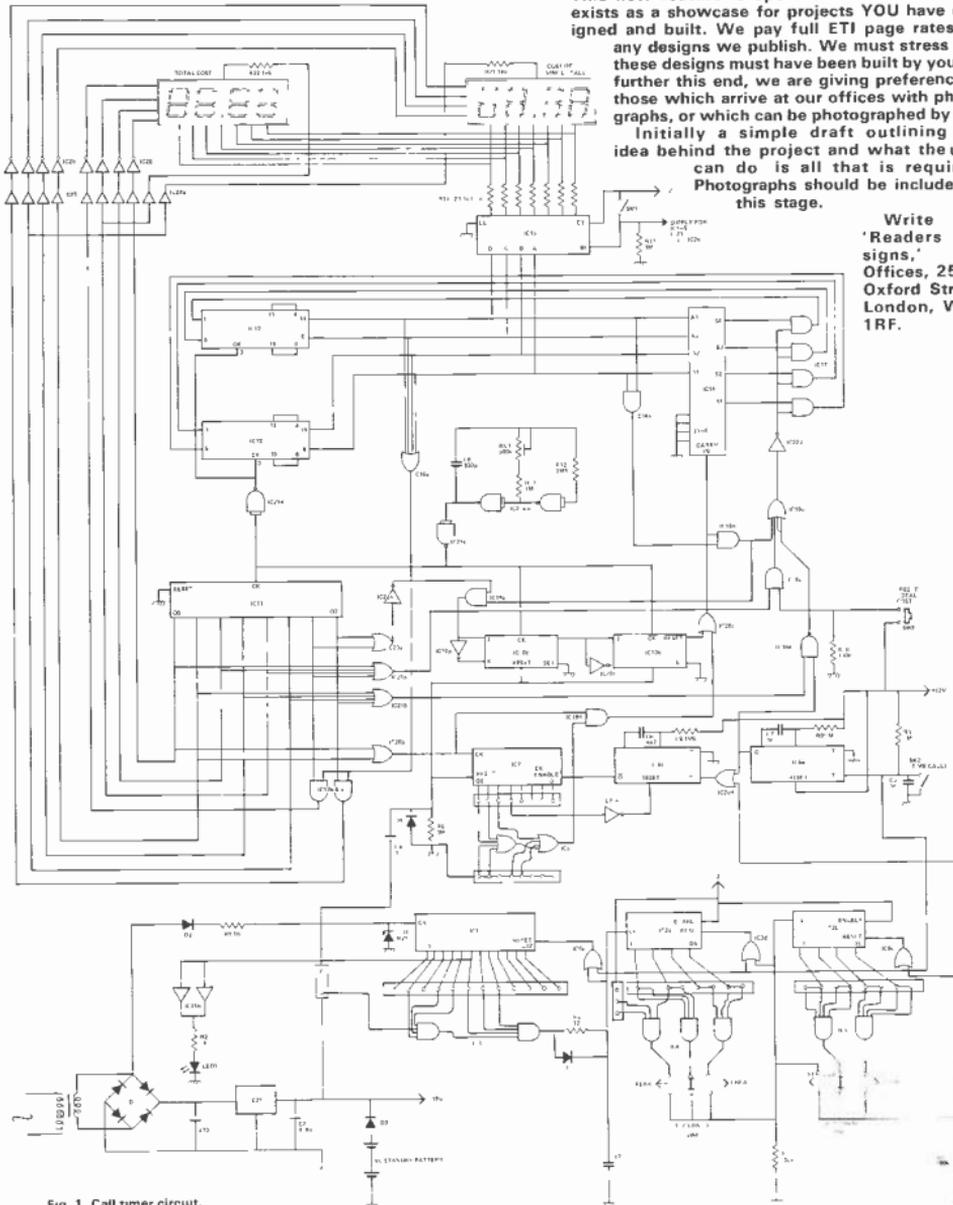


Fig. 1. Call timer circuit.

CLOCK RADIO



You probably won't believe us as we're selling the goods but we're going to tell you anyway! We have rejected eight clock radios for Marketplace, they were all cheap enough but the quality was so poor that we couldn't have lent our name to them. However, we are now able to offer a portable LCD Clock Radio to you which meets our standards.

The clock is a 12-hour one with AM/PM indicated and a back light. The radio is Medium Wave and FM with very nice quality for a small speaker — for FM there's a telescopic aerial. The alarm can be either a deep-beep type or the radio, there's also a snooze facility.

The case is sensibly rugged and is printed on the back with a World Time Zones map, a bit of a cheek really, especially as the time is relative to Japan!

We won't even mention the RRP — but just check on comparable prices — you'll find ours a bargain.

An example of this Clock Radio can be seen and examined at our Oxford Street offices.

£20.50

(Inclusive of VAT and Postage).

To:
CLOCK RADIO Offer,
ETI Magazine,
25-27 Oxford Street, London W1R 1RF

Please find enclosed my cheque PO for £20.50 (payable to ETI Magazine) for my Clock Radio.

Name

Address

Please allow 28 days for delivery

LADIES LCD WATCH



and don't you ever say we don't listen to you again! Ever since we first did a gentleman's watch, we have been dealing with a constant never-ending stream of requests for a ladies' model. Well at long last we can claim to have done something about it!

It wasn't easy bringing the sort of price on a product this good — but ETI's done it again! The watch is small enough to look good on the prettiest wrist, and accurate enough to satisfy the most fastidious. Normal display shows time of course, with both date and seconds available on a push of a button. A backlight is also included.

Battery life should be pretty in excess of a year and the bracelet is a smart stainless steel.

An example of this watch can be seen and examined at our Oxford Street offices.

£9.95

(Inclusive of VAT and Postage)

To:
Ladies LCD Watch Offer,
ETI Magazine,
25-27 Oxford Street,
London W1R 1RF

Please find enclosed my cheque PO for £9.95 (made payable to ETI Magazine) for a ladies LCD watch.

Name

Address

Please allow 18 days for delivery

DIGITAL ALARM



THIS IS THE THIRD digital alarm clock that we are offering (we regret the earlier versions are no longer available). We have sold thousands and thousands of these and our buying power enables us to offer a first rate branded product at a really excellent price.

The Hanimec HC-1100 is designed for mains operation only (240V/50Hz) with a 12-hour display, AM/PM and Alarm Set indicators incorporated in the large display. A switch on the top controls a Dim Bright display function.

Setting up both the time and alarm is simplicity itself as buttons are provided for both fast and slow setting and there's no problem about knocking these accidentally as a locking switch is provided under the clock. A 9 minute snooze switch is located at the top.

An example of this clock can be seen and examined at our Oxford Street offices.

£8.95

(Inclusive of VAT and Postage)

To:
Hanimec Alarm Offer,
ETI Magazine,
25-27 Oxford Street,
London W1R 1RF

Please find enclosed my cheque PO for £8.95 (payable to ETI Magazine) for a Hanimec Digital Alarm Clock.

Name

Address

Please allow 28 days for delivery

LCD CHRONO



We feel we've got to tell you carefully about this offer which we're introducing for the first time. Why? Because our price is so enormously lower than anywhere else you may suspect the quality.

The exact same watch is currently being offered by another magazine as a special at £24.95 — some of the discounters are selling it at £29.95, the price to ETI readers for exactly the same watch is £12.95.

The display is LCD and shows the seconds as well as the hours — and minutes — press a button and you'll get the date and the day of the week.

Press another button for a couple of seconds and you have a highly accurate stopwatch with hundredths of a second displayed and giving the time up to an hour. There is a lap time facility as well — and of course a back light.

Our Chrono comes complete with a high-grade adjustable metal strap and is fully guaranteed.

A sample of this watch can be seen and examined at our Oxford Street offices.

£12.95

(Inclusive of VAT and Postage)

To:
LCD Watch Offer
ETI Magazine
25-27 Oxford Street
London W1R 1RF

Please find enclosed my cheque/PO for £12.95 (payable to ETI) for my LCD Chrono-graph.

Name
Address

Please allow 28 days for delivery.

DIGITAL ALARM MK2



Both ETI and Hobby Electronics have sold a lot of digital alarm clocks — over 10,000 in fact — maybe that's something to do with the fact that we sell at real bargain prices. Now we can offer you a truly modern, space age model.

It includes all the facilities expected in a good design — fast, slow setting, snooze facility, etc. plus two unusual features — automatic brightness control and a weekend alarm cancel.

An example of this clock can be seen and examined at our Oxford Street offices.

£10.50

(Inclusive of VAT and Postage)

To:
DIGITAL ALARM CLOCK MK2 Offer,
ETI Magazine,
25-27 Oxford Street,
London W1R 1RF.

Please find enclosed my cheque/PO for £10.50 (payable to ETI Magazine) for my digital alarm clock.

Name
Address

Please allow 28 days for delivery.

ALARM-CHRONO LCD



Carefully this watch is being discounted elsewhere for typically £39.95 (we don't quote RRP as this is meaningless) and the watch is a Chinese copy of a very famous one in the £100 range!

- The facilities are exceptional:
- Normal hours and minutes
 - Continuous seconds or date display
 - Day of the week
 - Stopwatch with 0.1 secs resolution
 - Lap time facility with automatic return to stopwatch after 6 seconds
 - Different time zone setting with independent date/day of week settings
 - Good sleeping alarm
 - Easy time correcting on the sixth pip — press a button and it's reset to 00 seconds as long as watch is plus or minus 29 seconds.
- It comes with a full guarantee of course.

An example of this watch can be seen and examined at our Oxford Street offices.

£27.95

(Inclusive of VAT and Postage)

To:
ALARM/CHRONO LCD WATCH Offer,
ETI Magazine,
25-27 Oxford Street,
London W1R 1RF.

Please find enclosed my cheque/PO for £27.95 (payable to ETI Magazine) for my Alarm Chrono LCD watch.

Name
Address

Please allow up to 28 days for delivery.

AMBUSH



AMBUSH! is bound to rate as the most fascinating, exciting, and addictive space game of the year. It gives visual and sound effects of a space battle, and is loaded with realism. Impress your friends (and enemies) by building this unique and fascinating game.

(Photo by courtesy of 20th Century Fox)

AMBUSH! is a space game par excellence. It represents a space ship (yours) that is about to be attacked by a fleet of suicide craft. The craft can attack you on one of four randomly selected quadrants. The attacks come one at a time, at randomly selected intervals that vary between nought and five seconds. Your ship has a limited store of ammunition, and you can defend the vessel with one of four FIRE buttons. You have to hit the correct one of those buttons to stop the attack; if you hit more than one button at a time, you use up ammunition at an excessive rate.

The game continues until all the attacking craft are destroyed, or until you are wiped out. You can be wiped out by being too slow in hitting a FIRE button, by hitting the wrong FIRE button, or by running out of

ammunition through incorrect operation of the FIRE buttons. You can choose to face an attack by either ten (a DEK) or a hundred (a CENT) suicide craft; ammunition storage is automatically selected to suit the type of game chosen. A DEK game typically takes less than one minute to play. A CENT game takes several minutes.

Sound And Light

The game is loaded with audio and visual effects. On the sound side, there are individual noises to represent an attack, or the operating of FIRE weapons, and to indicate the winning or losing of a game. The level of the ATTACK sound varies with the quadrant of attack; attacks from the forward quadrant are silent, those from port or starboard are at

half volume, and those from aft are at full volume.

The visual effects are also quite impressive. The attacks are shown by an array of LED's arranged in the form of a cross with arms of varying lengths. The upper arm represents the forward attack quadrant, and comprises five orange LED's. The lower arm represents the aft attack quadrant, and comprises seven green LED's. The port and starboard arms each comprise six yellow LED's. At the centre of the cross is a red LED, representing your own ship.

The game is also provided with an ammunition level indicator, in the form of a three colour column of ten LED's, and with a two digit attack counter with seven-segment LED readouts. There are individual LED's to indicate the GAME WON and GAME LOST states.

Science Project


Ambush! is a CMOS based design of considerable technical interest, and should make an excellent educational project for schools and colleges. It uses seventeen IC's plus a couple of transistors. The IC types range from simple NAND and NOR gates to complete decade counter-decoder chips, and include flip-flops, data latches, 12-stage ripple counters, and multiplexers.

Playing The Game

Game Start. The game starts as soon as power is applied to its circuits. A game can be restarted by pressing the RESET switch.

Attacks:

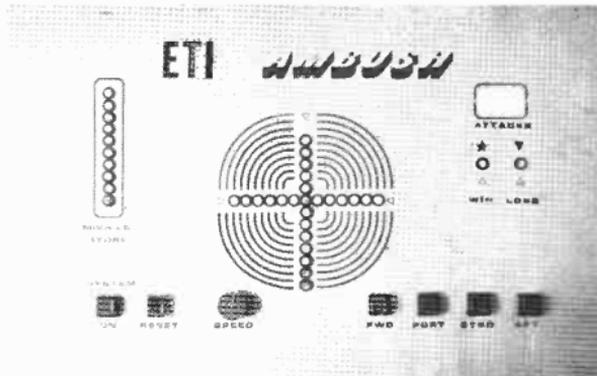- (1) The game can be set for play against either ten (a DEK) or a hundred (a CENT) attacks.
- (2) Attacks come at random intervals, variable between nought and approximately five seconds.
- (3) The quadrant of each attack is randomly selected, except for the first attack of the game, which always



comes from the aft quadrant.

(4) The speed of attack can be pre-set by the player to suit skill levels. A 'respectable' attack speed is equal to about 50 mS per LED division on the quadrant attack indicator.

(5) At 'respectable' attack speeds, the player has approximately 250 mS of attack warning on the forward quadrant, 300 mS on the port and

starboard quadrants, and 350 mS on the aft quadrant.

(6) Attacks on the aft quadrant are accompanied by a full volume staccato sound. Port and starboard attacks are at reduced volume, and those from the forward quadrant are silent.

(7) The accumulated number of attacks is registered on a 2-digit display throughout the game.

HOW IT WORKS

SIMPLIFIED BLOCK DIAGRAM OF THE AMBUSH GAME

The heart of the unit is the 'Display Matrix Driver and Logic' block, which in reality takes the form of a 4017 decade counter with ten decoded outputs. Outputs 1 to 7 of the counter are fed to the LED display matrix, and outputs 8 to 9 are selectively fed via a multiplexer to the GAME LOST indicator block and to the CLOCK DISABLE pin of the 4017. The input of the 4017 is derived from a clock generator via a gate, which in turn is controlled by a simple START-STOP (Reset-Set) bistable.

The operating sequence of the above six blocks is fairly simple. Initially, the bistable is in the STOP mode; the gate is closed, the 4017 is in the RESET state, and all LEDs in the display matrix are off. At some randomly determined time a START pulse is fed to the bistable; the gate opens, clock pulses start to reach the 4017, and LEDs are sequentially switched on in one of the arms of the display matrix. If the gate remains open, one of the selectively chosen 6-7-8 outputs of the IC eventually goes high and operates the GAME LOST indicator and disables the clock input line of the 4017.

Alternatively, the bistable can be set to the STOP mode before the game terminates by operating the appropriate FIRE switch. In this case the bistable closes the clock gate, and the 4017 reverts to the zero state. A new sequence of operations starts when another random START pulse is fed

to the input of the bistable. Note that output 1 of the 4017 is fed to the ATTACK COUNTER, so that the counter advances by one count each time the clock genera-

tor gate opens. The game ends shortly after the attack counter reaches its full (at 10 or 100) state, at which point the GAME WON indicator circuits come into operation.

The START signal to the bistable is derived from the random delay generator, which is integral with the FIRE switch circuitry. In each attack, the appropriate one of the four FIRE switches is selectively coupled to the STOP side of the



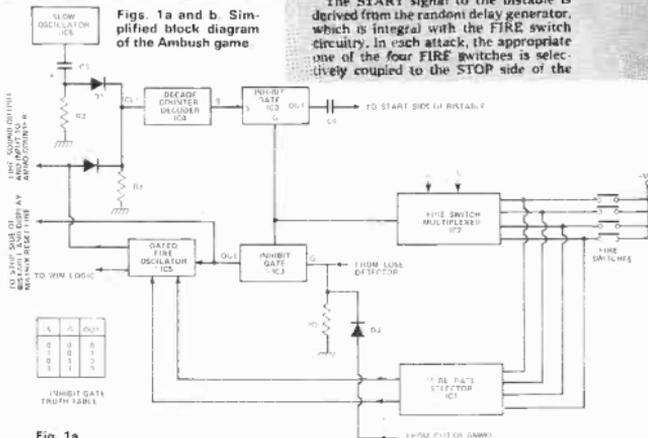


Fig. 1a

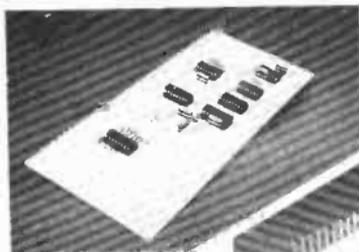

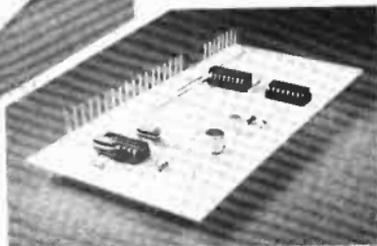(right) This board carries LED display matrix drivers, multiplexers and logic, plus audio and power connections.



(left) ICs 2 and 6-11 mounted on an Ambush PCB.

Defence

(a) The player has four FIRE buttons for defence. The buttons are marked F (forward) P (port) S (starboard) and A (aft). To stop an attack the player must press the FIRE button appropriate to the prevailing attack quadrant, before the attacking vessel reaches its target (the red LED at the centre of the display). A correct firing is accompanied by a rasping sound

No sound is produced if the wrong button is pressed.

(b) The ship has sufficient ammunition to fight off attacks only if each FIRE duration is limited to about 100 mS or less. Thus there is sufficient ammunition for about one second of continuous fire in the DEK game, and ten seconds of fire in the CENT game. The ammunition state is shown on a register throughout the game.

bistable via a multiplexer, and a simulated 'fire' sound is generated if the operator activates the correct switch; the frequency of the 'fire' sound is determined by the FIRE RATE SELECTOR circuit, and is proportional to the total number of FIRE switches pressed at any given moment.

The output of the fire sound generator is used to drive the ammunition register, which counts and gives a visual readout of the total number of cycles generated. The sound is also used to generate a latched random 'effect' code for the four multiplexers that are used in the game. These multiplexers are used for FIRE

switch selection, for LED Display Matrix line and line length selection, and to determine the audio levels of the ATTACK sounds.

The ATTACK, FIRE, WIN and LOSE sound signals are all fed to a simple two-transistor audio amplifier which drives a 40 ohm output speaker.

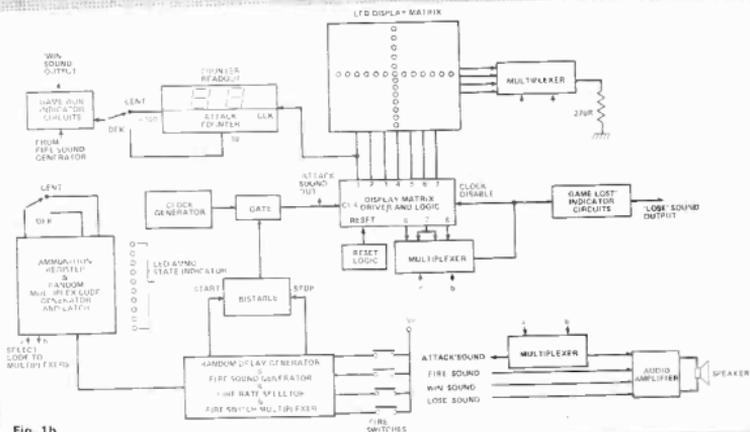


Fig 1b

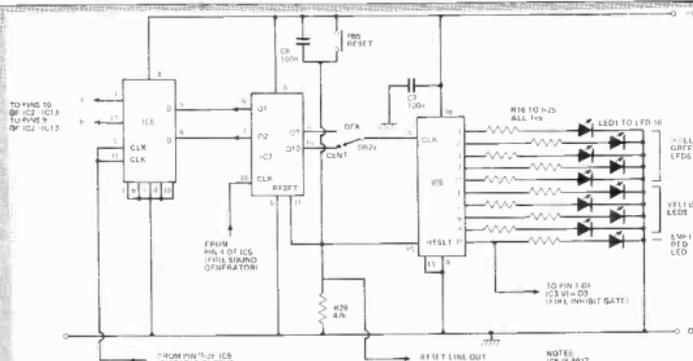


Fig. 3. Circuit diagram of ammo register, random multiplex code generator and latch with the reset line control.

HOW IT WORKS

THE AMMO REGISTER, RANDOM MULTIPLEX CODE GENERATOR AND LATCH AND RESET LINE CONTROL THIS BLOCK is relatively simple in its theory of operation. IC7 is a 4046 12-stage ripple counter, and takes its clock input from the output of the 'FIRE' sound generator. IC8 is a 4013 dual D flip-flop, which is wired as a dual data latch with its clock signal taken from the output of the bistable and its data taken from the Q1 (+2) and Q2 (+4) outputs of IC7. Thus whenever a FIRE button is pressed and then released IC7 sets randomly determined states on the data inputs of IC8; the next time that the output of the bistable goes high (as an attack begins, on receipt of the stable START command) these states are latched into the 4013 and are

pressed on to the games multiplexers as a 2-bit binary code.

IC6 is yet another 4017 decade counter with ten decoded outputs. It has its outputs fed to a vertical line of ten LED's, which act as the ammunition register. The '0' output of the 4017 goes to the top (FULL level) of the line, and the '9' output goes to the bottom (EMPTY level) of the line. The '9' output also goes to the inhibit gate controlling the 'FIRE' oscillator, preventing the oscillator from working under the 'ammo exhausted' condition. At the start of each game the counter is reset to zero, so that the line of LED's indicate the FULL state.

The clock input of the counter is taken from one of the outputs of the IC7 ripple counter via SW2a. When SW2 is set for a

DEK (ten attack) game the Q7 (+128) output is fed to the clock input of IC6, giving a clock signal of about 6.2 Hz when a single FIRE button is operated, and thus causing the register to empty in about 1.5 seconds. When SW2 is set for a CENT (hundred attack) game the Q10 (+1024) output is fed to IC6, giving a clock frequency of about 0.8 Hz from a single FIRE button, and causing the register to empty in about 11.2 seconds. Thus, to win a DEK game the average FIRE duration must be limited below 150 ms in each attack, and in the CENT game it must be limited below 112 ms.

The games main reset line is activated automatically at switch-on via CA. The line can be operated manually at any time via RESET button PB8.

red LED at the centre of the games main display matrix. This LED is normally on, but goes off when the game is lost.

IC11/1 and IC11/2 are wired as a medium-speed gated astable, which provides the 'GAME LOST' sound output via D9 and R34, and IC11/3 and IC11/4 are

wired as a low-speed gated astable, which drives a red 'GAME LOST' LED. Both astables are normally off, with their outputs low. Under the 'GAME LOST' condition both astables operate, the 'LOSE' sound is generated and the 'LOSE' LED flashes on and off.

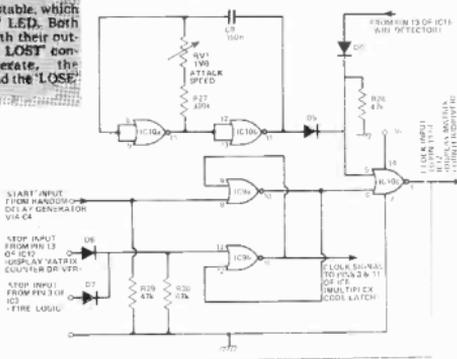
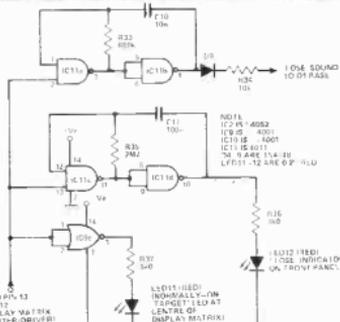


Fig. 4 (left) Display matrix counter/driver, target LED and 'LOSE' indicator.

Fig. 5 (right) Bistable, clock gen., 'ATTACK' sound multiplexer and 'GAME LOST' indicators.

new books on ELECTRONICS

INTRODUCTION TO MICROELECTRONICS,

2nd Edition

D. RODDY *Lanthead University, Ontario, Canada*

Presents a thorough treatment of the fundamental principles of microelectronics and their applications

228pp 0 08 022687 6 H US\$20 00 £10 00
1978 0 08 022688 4 F US\$10 00 £ 5 00

MICROPROCESSORS

Principles and Applications

M. J. DEBENHAM *Standard Telephone & Cables Ltd London, England*

A concise introduction to the field of microprocessors their design and uses. A wide range of actual and potential applications are described with particular consideration of future trends

150pp 0 08 024205 5 H US\$15 00 £7 50
June 1978 0 08 024207 3 F US\$ 7 50 £3 75

ELECTRONIC INVENTIONS AND DISCOVERIES

(2nd Revised and Expanded Edition of Electronic Inventions 1745-1976)

G. W. A. DUMMER *Melbourn Works, Warc, England*

This unique mini-encyclopedia provides a comprehensive source of reference and information on practically all electronic developments over almost two and a half centuries

208pp 0 08 022730 9 H US\$30 00 £15 00
1978 0 08 023223 X F US\$15 00 £ 5 00

MICROWAVES, 2nd Edition

An Introduction to Micro wave Theory and Techniques
A. J. BADENFULLER *University of Leicester, England*

Provides a theoretical development of electromagnetic wave propagation of guided waves and the material properties (together with a descriptive treatment of microwave components and measurements)

300pp 0 08 024228 6 H US\$30 00 £15 00
August 1979 0 08 024227 6 F US\$13 00 £ 6 50

Pergamon Related Journal

Free Specimen Copy Available on Request

MICROELECTRONICS AND RELIABILITY

Editor in Chief: G. W. A. DUMMER *Melbourn Works, Warc*

Published 8x monthly

Annual subscription (1979) US\$130 00

Two years (1979/80) US\$247 00

Reduced rate for individuals whose library subscribes US\$30 00

Journal prices include postage and insurance

A catalogue of these and other new and forthcoming titles in Electrical & Electronic Engineering is available from your nearest Pergamon office. All prices are subject to change without notice. Sterling prices apply to customers in the UK and Eire only.

H - Hardcover F - Flexicover



Pergamon Press

Headington Hill Hall, Oxford, OX3 0BW
Fairfax Park, Elmsford, New York 10523, USA

GREENWELD

443A Millbrook Road, Southampton
SO1 0HX Tel. (0703) 772501

All prices quoted include VAT Add 25% UK BPPC Postage. Most orders despatched on day of receipt. S&T with angles please. MINIMUM ORDER VALUE £1. Off orders accepted from schools, etc. (Minimum invoice charge £3). Export/Wholesale enquiries welcome. Wholesale list now available for bona-fide traders. Sample components always available. Prices in this advertisement valid until 30/4/79. 100+ prices are per value and may not be exact.

RESISTORS

1/4W 5% Carbon film 18 10M E24 series 1 99 15p 100 89 1p

1000+ 0 7p

1/4W 2% Metal Glaze 10R 1M E24 series 1 99 15p

1/4W 5% Carbon Film 4W 10W E12 series 1 99 3p 100+ 2 5p

1/4W 100+ 7 5p 100+ 2 5p

values under 10R and over 510K

1/4W 5% Carbon Film 4W 10W E12 series 1 99 3p 100+ 2 5p

1/4W 100+ 7 5p 100+ 2 5p

values under 10R and over 510K

1/4W 5% Carbon Film 4W 10W E12 series 1 99 3p 100+ 2 5p

1/4W 100+ 7 5p 100+ 2 5p

values under 10R and over 510K

1/4W 5% Carbon Film 4W 10W E12 series 1 99 3p 100+ 2 5p

1/4W 100+ 7 5p 100+ 2 5p

values under 10R and over 510K

PRESETS

1/4W 0 1W var. or horiz. mmg 100R

4M7 1 00 7p 100+ 4 5p 510

0 3W var. or horiz. mmg 100R 4M7

1 59 9p 100+ 6p

values under 10R and over 510K

1/4W 0 1W var. or horiz. mmg 100R

4M7 1 00 7p 100+ 4 5p 510

0 3W var. or horiz. mmg 100R 4M7

1 59 9p 100+ 6p

values under 10R and over 510K

1/4W 0 1W var. or horiz. mmg 100R

4M7 1 00 7p 100+ 4 5p 510

0 3W var. or horiz. mmg 100R 4M7

1 59 9p 100+ 6p

values under 10R and over 510K

1/4W 0 1W var. or horiz. mmg 100R

4M7 1 00 7p 100+ 4 5p 510

0 3W var. or horiz. mmg 100R 4M7

1 59 9p 100+ 6p

values under 10R and over 510K

POPULAR SEMICONDUCTORS

Type 1 99 100+

741 18p 14 5p

555 25p 18 5p

556 55p 85p

8C101 9p 7p

8C108 8p 6 5p

8C109 7p 7p

129 Red LED 1 1p 8 5p

2 Red LED 18p 10p

76C03N 180p 100p

76C13N 130p 85p

76C23N 130p 85p

76C33N 160p 100p

1N6148 2p 1 3p

1N4003 7p 2 5p

1N4007 7p 4 9p

values under 10R and over 510K

1/4W 0 1W var. or horiz. mmg 100R

4M7 1 00 7p 100+ 4 5p 510

0 3W var. or horiz. mmg 100R 4M7

1 59 9p 100+ 6p

values under 10R and over 510K

1/4W 0 1W var. or horiz. mmg 100R

4M7 1 00 7p 100+ 4 5p 510

0 3W var. or horiz. mmg 100R 4M7

1 59 9p 100+ 6p

values under 10R and over 510K

1/4W 0 1W var. or horiz. mmg 100R

4M7 1 00 7p 100+ 4 5p 510

0 3W var. or horiz. mmg 100R 4M7

1 59 9p 100+ 6p

values under 10R and over 510K

1/4W 0 1W var. or horiz. mmg 100R

4M7 1 00 7p 100+ 4 5p 510

0 3W var. or horiz. mmg 100R 4M7

1 59 9p 100+ 6p

values under 10R and over 510K

1/4W 0 1W var. or horiz. mmg 100R

4M7 1 00 7p 100+ 4 5p 510

0 3W var. or horiz. mmg 100R 4M7



1 59 9p 100+ 6p

3080 CIRCUITS

The 3080 is not a run of the mill op amp. These ten circuits from Tim Orr show you why.

The CA3080 is known as an operational transconductance amplifier, (OTA). This is a type of op amp the gain of which can be varied by use of a control current, (I_{ABC}). The device has a differential input, a control input known

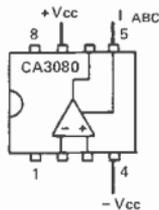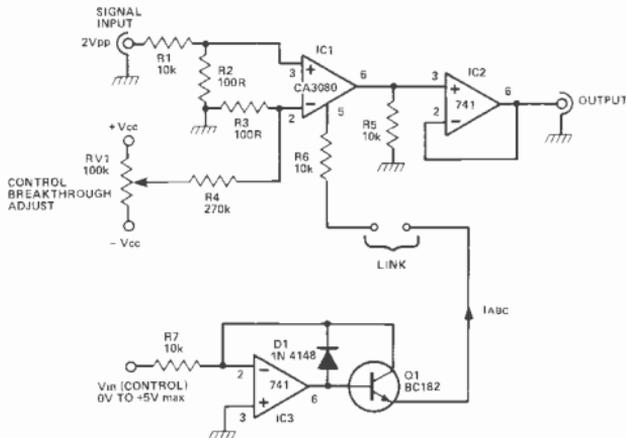
as the Amplifier bias input and a current output. It differs in many respects from conventional op amps and it is these differences that can be used to realize many useful circuit blocks.



Voltage Controlled Amplifier



The CA3080 can be used as a gain controlling device. The input signal is attenuated by R1, R2 such that a 20 mVpp signal is applied to the input terminals. If this voltage is much larger, then significant distortion will occur at the output. In fact, this distortion is put to good use in the triangle-to-sinewave converter. The gain of the circuit is controlled by the magnitude of the current I_{ABC}. This current flows into the CA3080 at pin 5, which is held at one diode voltage drop above the -V_{cc} rail. If you connect pin 5 to 0 V, then this diode will get zapped, (and so will the IC!). The maximum value of I_{ABC} permitted is 1 mA and the device is 'linear' over 4 decades of this current. That is, the gain of the CA3080 is 'linearly' proportional to the magnitude of the I_{ABC} current over a range of 0.1 μ A to 1 mA. Thus, by controlling I_{ABC}, we can control the signal level at the output. The output is a current output which has to be 'dumped' into a resistive load (R5) to produce a voltage output. The output impedance seen at IC1 pin 6 is 10k (R5), but this is 'unloaded' by the voltage follower (IC2) to produce a low output impedance. The circuit around IC3 is a precision voltage-to-current converter and this can be used to generate I_{ABC}. When Vin (control) is positive, it linearly controls the gain of the circuit. When it is negative, I_{ABC} is zero and so the gain is zero.

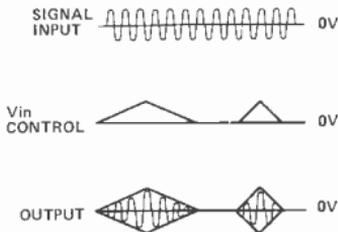This type of circuit is known by several names. It is a voltage controlled amplifier, (VCA), or an amplitude modulator, or a two





quadrant multiplier

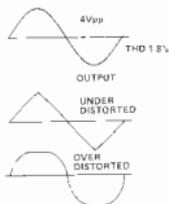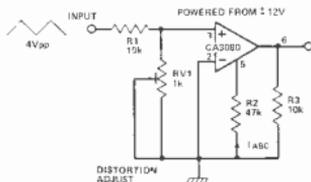One problem that occurs with the CA3080 is that of the 'input offset voltage'. This is a small voltage offset between its input terminals. When there is no signal input and the control input is varied a voltage similar to the control input will appear at the output. By adjusting RV1 it is possible to null out most of this control breakthrough.



Triangle To Sinewave Converter

By overloading the input of a CA3080 it is possible to produce a 'sinusoidal' transfer function. That is, if a triangle waveform of the correct magnitude is applied to the CA3080 input, the output will be distorted in such a way as to produce a sinewave approximation. In the circuit shown, RV1 is adjusted so that the output waveform resembles a sinewave. I tested this circuit using an automatic distortion analyser and found the sinewave distortion to be only 1.8%, mostly third harmonic distortion, which, for such a simple arrangement, seems very reasonable indeed. This could be used to produce a sinewave output from a triangle/square wave oscillator.

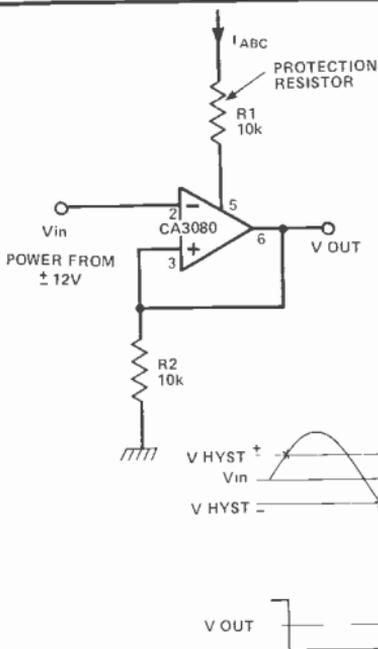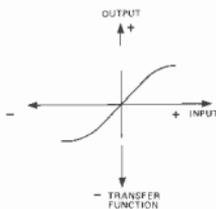

Schmitt Trigger


Most Schmitt trigger circuits prove to be very complicated when it comes to calculating the hysteresis levels. However, by using the CA 3080 these calculations are rendered trivial plus there is the added bonus of fast operation. The hysteresis levels are calculated from the simple equation.


$$V_{HYST} = -(I_{ABC} \times R2)$$

The output squarewave level is in fact equal in magnitude to the hysteresis levels. The circuit operation is as follows.

Imagine the output voltage is high. The output voltage will then be equal to $(R2 \times I_{ABC})$ which we will call $+V_{HYST}$. If V_{IN} becomes more positive than $+V_{HYST}$, the output will start to move in a negative direction, which will further accelerate the speed of the output movement. This is known as regenerative feedback and is responsible for the schmitt trigger action. The output snaps into a negative state, at a voltage equal to $-(R2 \times I_{ABC})$ which is designated as $-V_{HYST}$. Only when V_{IN} becomes more negative than $-V_{HYST}$ will the output change back to the $+V_{HYST}$ state.

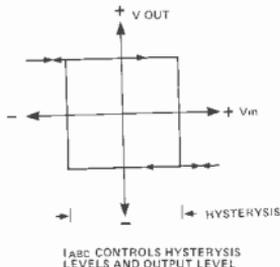The Schmitt trigger is a very useful building block for detecting two discrete voltage levels and finds many uses in circuit designs.



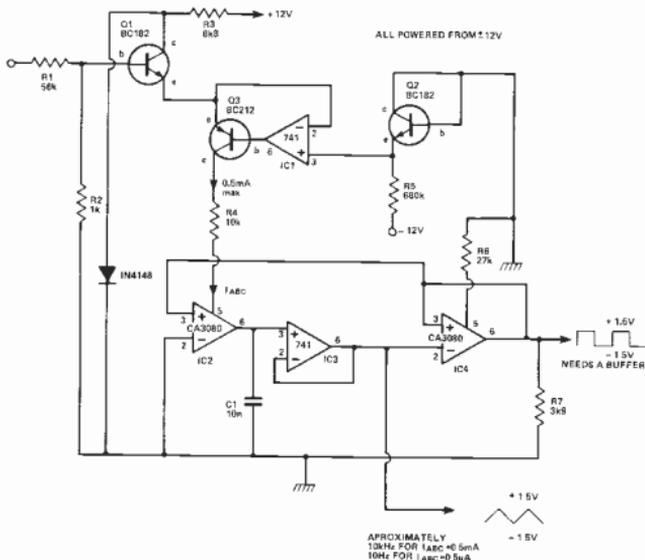


Voltage Controlled Oscillator

By using two CA3080's and some op amps it is possible to make an oscillator, the frequency of which is voltage controllable. This unit finds many applications in the field of electronic music production and test equipment. The circuit has been given a logarithmic control law, that is, the frequency of operation doubles for every volt increase in the control voltage. This makes it ideal for musical applications where linear control voltages need to be converted into musical intervals (which are logarithmically spaced) and also for audio testing where frequencies are generally measured as logarithmic functions.

IC2 is an integrator. The I_{ABC} current that drives this IC is used to either charge or discharge C1. This produces triangular waveforms which are buffered by IC3, which then drives the Schmitt trigger IC4. The hysteresis levels for this device are fixed at -1.5V, being determined by R6, R7.

The output of the schmitt is fed back in such a way as to control the direction of motion of the integrator's output. If the Schmitt output is high, then the integrator will ramp upwards and vice versa. Imagine that the integrator is ramping upwards. When the integrator's output reaches the positive hysteresis level, the Schmitt will flip into its low state, and the integrator will start to ramp downwards. When it reaches the low hysteresis level the Schmitt will flip back into its high state. Thus the integrator ramps up and down in between the two hysteresis levels. The speed at which it does this, and hence the oscillating frequency is determined by the value of I_{ABC} into IC2. The larger the current, the faster the capacitor is charged and discharged. Two outputs are produced, a triangle wave (buffered) from IC3 and a squarewave (unbuffered) from IC4. If the squarewave output is loaded then the oscillation frequency will change.


The log law generator is composed of Q1, 2, 3 and IC1. Transistors Q1 and Q2 should be matched so that their base emitter voltages (V_{be}) are the same for the same emitter current, (50uA). Matching these devices to within 5 mV is satisfactory, although unmatched pairs could be used. When matching transistors take care not to touch them with your fingers. This will heat them up and produce erroneous measurements. Transistor Q2 is used to produce a reference voltage of about -0V6 which is connected to IC1 pin 3. This op amp and

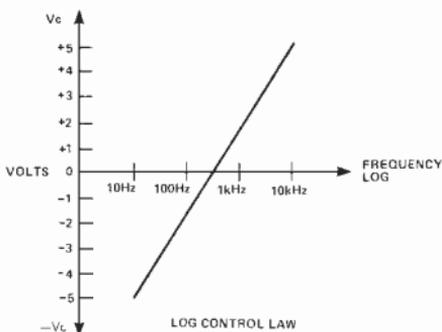

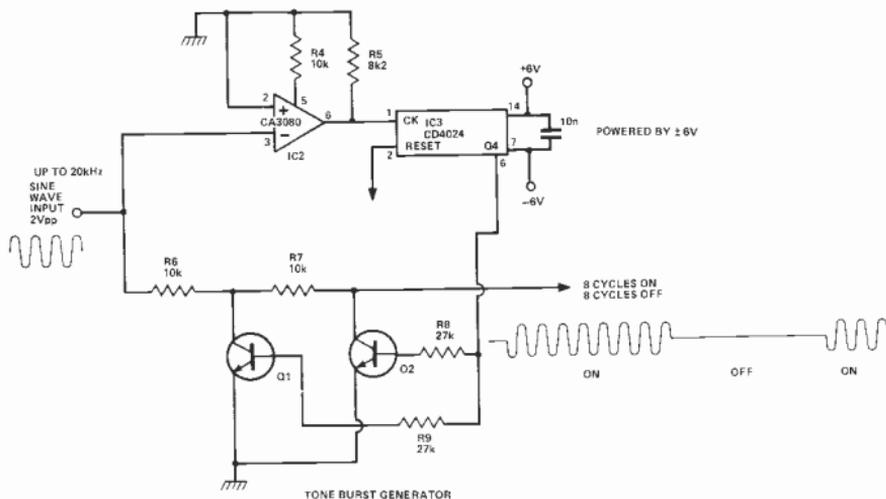Q3 is used to keep Q1 emitter at this same voltage of -0V6. The input control voltage is attenuated by R1, R2 such that a +1 V increase at the input produces a change of only +18 mV at the base of Q1. However the emitter of Q1 is fixed at -0V6, so the current through Q1 doubles. (It is a property of transistors that the collector current doubles for every 18 mV increase in V_{be}).

The emitter current of Q1 flows through Q3 and into IC2 thus controlling the oscillator frequency. It is possible to get a control range of over 1000 to 1 using this circuit. With the values shown, operation from 10 Hz to 10 kHz is achieved. Reducing C1 to 1 n will increase the maximum frequency to 100 kHz, although the waveform quality may be somewhat degraded.



Changing C1 to 1uF (non-polarized) will give a minimum frequency of 0.1 Hz.




Fast Comparator

The high slew rate of the CA3080 makes it an excellent fast voltage comparator. When pin 2, IC1 is more positive than V_{ref} the output of IC1 goes negative and vice versa. V_{ref} can be moved around so that the point at which the output changes can be varied. As long as the input sinewave level is quite large (1 V say) then the output can be made to move at very fast rates indeed. However, care must be taken to avoid overloading the inputs. If the differential input voltage exceeds 5 V, then the input stage breaks down and may cause an undesired output to occur.

One use of a fast comparator is in a tone burst generator. This device produces bursts of sinewaves, the burst starting and finishing on axis crossings of the sinusoid. The comparator is used to detect these axis crossings and to produce a square wave output which then drives a binary divider (IC3). The divider produces a 'divide by sixteen' output which is high for eight sinewave cycles and then low for the next eight. This signal is then used to gate ON and OFF the sinewave. The gate mechanism is a pair of transistors which short the sinewave to ground when the divider output is high and let it pass when the divider output is low. The resulting output is a toneburst. However, if the comparator is not very fast, then there will be a delay in generating the gate and so the tone burst will not start or finish on axis crossings. Using the circuit shown, operation up to 20 kHz is obtainable.

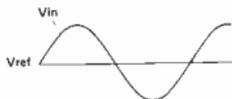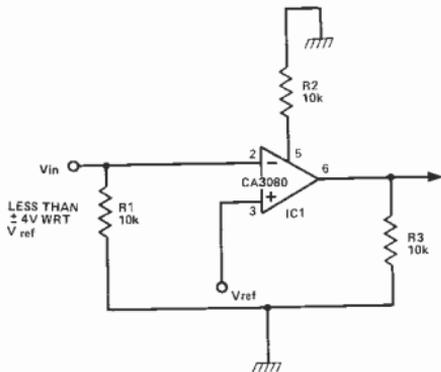

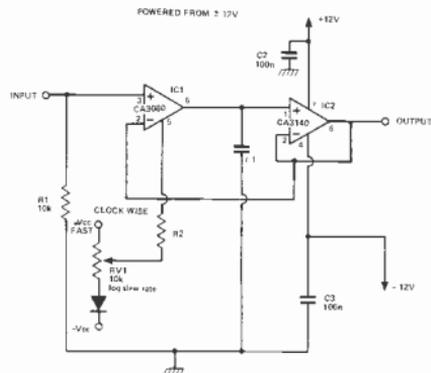

Slew Limiter


The current output of a CA3080 can be used to produce a controlled slew limiter. By connecting the output current to a capacitor, the output voltage cannot move faster than a rate given by

$$\text{slew rate} = \frac{I_{ABC} \text{ Volts per sec.}}{C_T}$$

Note that I_{ABC} determines the slew rate and as I_{ABC} is a variable then so is the slew rate. The output voltage is buffered by a voltage follower, IC2. This is a MOSFET op amp which has a very high input impedance, which is necessary to minimise the loading on C1.

When an input signal is applied to IC1 the output tries to move towards this voltage but its speed is limited by the slew rate. Thus the output produces a linear ramp which stops when it reaches the input signal level.


R2	C1	FASTEST SLEW RATE
150k	100n	1.5V/mSec
150k	10n	15V/mSec
150k	1u0	0.15V/mSec
1M5	1u0	15V/Sec

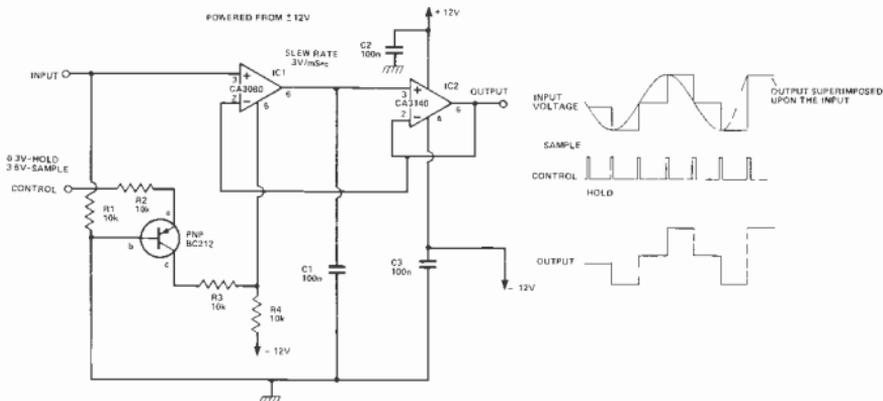

Sample And Hold

The slew limiter can be modified so that it becomes a sample and hold unit. In this circuit I_{ABC} is either hard ON (sample) or completely OFF (hold). In the sample mode, the output voltage quickly adjusts itself so that it equals the input voltage. This

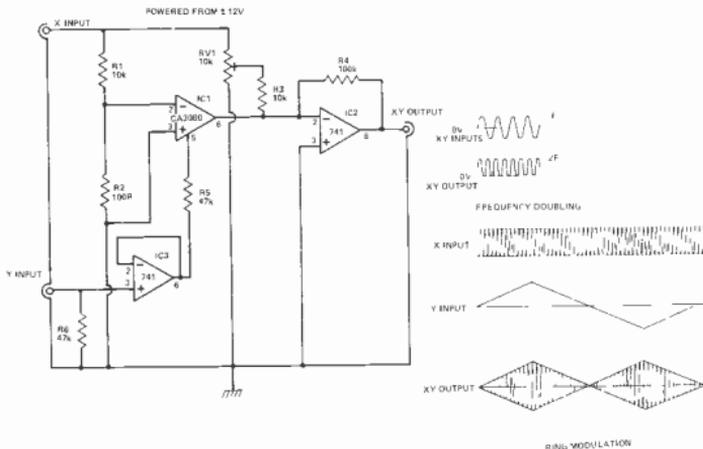enables a short sample period to be used. In the HOLD mode, I_{ABC} is zero and so the voltage on C1 should remain fixed. The circuit is in fact an analogue memory. It is used in music synthesisers (to remember the pitch), in analogue to digital converters and many other circuits.




4 Quadrant Multiplier

The CA3080 is a two quadrant multiplier but, with the addition of a few extra bits of electronics, it can be made into a four quadrant circuit. A two quadrant multiplier has two inputs, one can accept bipolar signals (the inverting or non inverting input) and one can only accept a unipolar signal, (the IABC current). However, a four quadrant multiplier can accept bipolar signals on both of its inputs which enables it to perform frequency doubling and ring modulation.

The circuit is fairly similar to that of the two quadrant multiplier described earlier except for two differences. IC3 is used to generate IABC in such a way that the Y input can go both positive and negative, thus the Y input is bipolar, when Y is at 0 V

and there is a signal on the X input the desired output ($X \times Y$) should be zero. This is achieved by adjusting RV1 so that the signal via IC1 (this is inverted) is exactly cancelled out by that via R3. Now, when Y is increased positively, a non-inverted value of X is produced at the output and, when Y is increased negatively, an inverted value of X is produced. When Y is zero, so is the output. This is known sometimes as ring modulation. If a speech signal is connected to the X input and a variable frequency oscillator to the Y input the resulting sound is that of a 'dalek'. Also, if a sine wave is connected to both the X and Y inputs, the XY product is a sine wave of twice the frequency. This is known as a frequency doubler, but it will only work with sine waves.

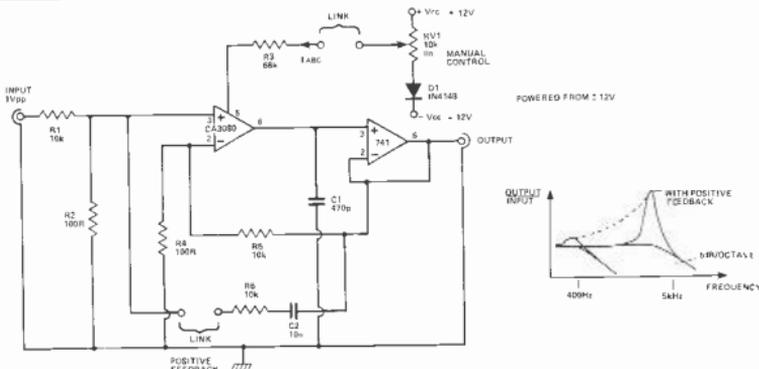

Single Pole Filter

A singlepole lowpass filter can be constructed using a CA3080 as a current controlled resistor. The filter is, in fact, just a simple RC low pass section where the R, which is controllable, is constructed out of IC1, R4, R5. Varying IABC changes the amount of current drive to C1. This would normally make the circuit a slew limiter, but because the signal level that IC1 (pins 2

and 3) handles is so small, the CA3080 works in its linear mode. This enables it to look like a variable resistor. When this resistor is varied, the break frequency of the filter also varies. By applying some positive feedback around the filter (R6, C2) it is possible to produce a peaky filter response. The peak actually increases with frequency making the circuit useful as a guitar Wah Wah unit

SERVICE TRADING CO

WHY PAY MORE?!

100% GUARANTEE! Meters Type 2000
 1/2 DC Volt 10 50 250 500 mA
 1/2 AC Volt 10 50 250 500 mA
 Dimensions 100 x 70 x 40mm Price £7.95
 Quantity 100 £750.00



TRAC

Photoconductive Tracer - 1/2 inch dia. 1000 - 100000 cycles/min
 Glass window 100 x 70 mm. Price £10.00
 Dimensions 100 x 70 x 25mm Price £10.00
 Quantity 100 £1000.00

0 to 100 MINUTES CLOCKWORK TIMER

100 x 70 x 25mm Price £1.50
 Quantity 100 £150.00

MERCURY SWITCH

100 x 70 x 25mm Price £1.50
 Quantity 100 £150.00



230 VOLT AC FAN ASSEMBLY

100 x 70 x 25mm Price £1.50
 Quantity 100 £150.00



21-WAY SELECTOR SWITCH

100 x 70 x 25mm Price £1.50
 Quantity 100 £150.00



VORTEX BLOWER AND VACUUM UNIT

100 x 70 x 25mm Price £1.50
 Quantity 100 £150.00



CENTRIFUGAL BLOWER

100 x 70 x 25mm Price £1.50
 Quantity 100 £150.00



24V DC BLOWER UNIT

100 x 70 x 25mm Price £1.50
 Quantity 100 £150.00



MINIATURE UNISELECTOR

100 x 70 x 25mm Price £1.50
 Quantity 100 £150.00



MICRO SWITCHES

100 x 70 x 25mm Price £1.50
 Quantity 100 £150.00



NEW HEAVY DUTY SOLENOID

100 x 70 x 25mm Price £1.50
 Quantity 100 £150.00



WESTON TYPE MANG WOODS 2

100 x 70 x 25mm Price £1.50
 Quantity 100 £150.00



240 V A.C. SOLENOID OPERATED FLUID VALVE

100 x 70 x 25mm Price £1.50
 Quantity 100 £150.00



INSULATION TESTERS (NEW)

100 x 70 x 25mm Price £1.50
 Quantity 100 £150.00



100 VOLTS

100 x 70 x 25mm Price £1.50
 Quantity 100 £150.00



YET ANOTHER OUTSTANDING OFFER

100 x 70 x 25mm Price £1.50
 Quantity 100 £150.00

VARIABLE VOLTAGE TRANSFORMERS

INPUT 230 V A.C. 50 Hz	
OUTPUT VARIABLE 0/250V A.C	
BRAND NEW 8V 800VA	£14.50
200V (11 Amp) Input A.C	
0.5 KVA (Max. 2 Amp)	£17.00
1 KVA (Max. 4 Amp)	£22.50
2 KVA (Max. 10 Amp)	£37.00
3 KVA (Max. 15 Amp)	£48.50
5 KVA (Max. 25 Amp)	£74.00
10 KVA (Max. 50 Amp)	£138.00
17 KVA (Max. 75 Amp)	£280.00

LY TRANSFORMERS

1/2 Amp 0-250V	£2.95	£3.24
1/2 Amp 0-250V	£2.95	£3.24
1/2 Amp 0-250V	£2.95	£3.24
1/2 Amp 0-250V	£2.95	£3.24
1/2 Amp 0-250V	£2.95	£3.24
1/2 Amp 0-250V	£2.95	£3.24
1/2 Amp 0-250V	£2.95	£3.24
1/2 Amp 0-250V	£2.95	£3.24
1/2 Amp 0-250V	£2.95	£3.24
1/2 Amp 0-250V	£2.95	£3.24

ROTARY VACUUM AIR COMPRESSOR & PUMP

100 x 70 x 25mm Price £1.50
 Quantity 100 £150.00



BLOWER / VACUUM PUMP

100 x 70 x 25mm Price £1.50
 Quantity 100 £150.00

STROBE! STROBE! STROBE!

HY-LIGHT STROBE KIT Mk. IV
 Ultra violet strobe light
 100 x 70 x 25mm Price £1.50
 Quantity 100 £150.00

ULTRA VIOLET LIGHT

100 x 70 x 25mm Price £1.50
 Quantity 100 £150.00

SQUAD LIGHT

100 x 70 x 25mm Price £1.50
 Quantity 100 £150.00

WIDE RANGE OF DISCO LIGHTING EQUIPMENT

100 x 70 x 25mm Price £1.50
 Quantity 100 £150.00

XENON FLASH GUN TUBES

100 x 70 x 25mm Price £1.50
 Quantity 100 £150.00

RELAYS

100 x 70 x 25mm Price £1.50
 Quantity 100 £150.00

SPECIAL OFFER BERCO type L RHEOSTAT

100 x 70 x 25mm Price £1.50
 Quantity 100 £150.00

FRACMO MOTOR

100 x 70 x 25mm Price £1.50
 Quantity 100 £150.00

VAT AT CURRENT RATE MUST BE ADDED TO ALL ORDERS

FOR THE TOTAL VALUE OF GOODS INCLUDING POSTAGE UNLESS OTHERWISE STATED

GEARED MOTORS

100 R.P.M. 1.15 lbs. 100.11
 100 x 70 x 25mm Price £1.50
 Quantity 100 £150.00



GEARED MOTORS

100 x 70 x 25mm Price £1.50
 Quantity 100 £150.00



FRACMO MOTOR

100 x 70 x 25mm Price £1.50
 Quantity 100 £150.00



PARVALUX MOTOR TYPE S. D. 2

100 x 70 x 25mm Price £1.50
 Quantity 100 £150.00

PARVALUX 230/250V a.c. MOTOR

100 x 70 x 25mm Price £1.50
 Quantity 100 £150.00



CITENCO

100 x 70 x 25mm Price £1.50
 Quantity 100 £150.00



REVERSIBLE MOTOR 230V A.C.

100 x 70 x 25mm Price £1.50
 Quantity 100 £150.00



12V DC GEARED MOTOR

100 x 70 x 25mm Price £1.50
 Quantity 100 £150.00



METERS (New) - 90mm DIAMETER

100 x 70 x 25mm Price £1.50
 Quantity 100 £150.00



'VENNER TYPE' ERD TIME SWITCH

100 x 70 x 25mm Price £1.50
 Quantity 100 £150.00



SANGANO WESTON TIME SWITCH

100 x 70 x 25mm Price £1.50
 Quantity 100 £150.00



REG TIMERSWITCH

100 x 70 x 25mm Price £1.50
 Quantity 100 £150.00

AC MAINS TIMER UNIT

100 x 70 x 25mm Price £1.50
 Quantity 100 £150.00



POWER RHEOSTATS

100 x 70 x 25mm Price £1.50
 Quantity 100 £150.00



FRACMO MOTOR

100 x 70 x 25mm Price £1.50
 Quantity 100 £150.00

SPECIAL OFFER BERCO type L RHEOSTAT

100 x 70 x 25mm Price £1.50
 Quantity 100 £150.00

ACCOUNT CUSTOMERS MIN. ORDER £10.00

ALL MAKE ORDERS! ALSO CALLERS AT 57 BRIDGMAN ROAD, CHISWICK, LONDON, W6 8SB. Phone 01-895 1560. Cashed Surfers. SERVICE TRADING CO. SHOWROOMS NOW OPEN AMPLE PARKING. PERSONAL CALLERS ONLY. 9 LITTLE NEWPORT STREET, LONDON, WC2H 7JZ. Tel: 01-437 0576.

microfile.....

Gary Evans looks at PLT add-ons, a Simon that's not simple and has news on superboard II.

WITH THE PLETHORA of new small computer systems appearing on the market, it's nice to see some of the old warhorses beginning to meet this onslaught by supporting the user with a broad base of hardware. Surely one of the oldest warhorses (its flock cry protest this month) and one which has to date been poorly supported by its manufacturer is the PET.

A number of companies have stepped into the void caused by lack of Commodore peripherals, everything from RS232 interfaces to PET compatible floppy drives are available but not from Commodore. The latest issue of the PET User's Club newsletter indicates that this situation is about to change.

The most exciting of the PET add-ons from Commodore is their 2040 Dual Drive Floppy Disk. Details are sketchy at present but I'll outline the spec of the 2040 as presented in the newsletter.

The drive will allow 360K bytes of data to be stored on two standard 5 1/4 in Disk drives (Shugart SA390). This is accomplished without resorting to double tracking or double density. This is achieved (we're not told exactly how) by the use of two MPUs — 6504 and 6502 — and fifteen memory ICs within the 2040.

Formatting is by the drive itself and any mini floppy disk may be used. 35 tracks with a constant density recording on each track provide 171520 bytes for user storage per disk side.

The 2040 requires only one connection to the PET — an interface cord connecting the unit to PET's IEEE port.

Just what we've been waiting for — but you'll have to wait until May and part with £799.90 for the pleasure of fitting this box of tricks next to your PET.

Good news that we don't have to wait for is a price reduction in the PET model 2001 B. The 8K machine that until now has been the only PET computer is down in price to £594.00.


The 8K machine is to be joined by a 4K machine at £496.00 and two models featuring 16K and 32K of memory. The memory used in these larger systems is dynamic, a departure from the static RAM used in the 8K and 4K versions. The 16K and 32K machines will also feature a full typewriter style keyboard in place of the calculator keyboard that was one of the most persistent criticisms of the 8K 2001 B. In order to make room for the larger keyboard the integral cassette deck has been omitted and a separate deck will have to be obtained in order to record programs.

The 4K PET is due in February, the other versions will be here in May.

The last addition to Commodore's hardware is the 2023 printer. This will replace the ill-fated 2020 printer — announced but not seen — and has to quote a significantly better quality and more efficient feed. The 2023 is due in April.

Well there we are then a range of value added PET peripherals. Let's hope that Commodore manage to meet the promised delivery dates as in the past this is the area in which Commodore have been distinctly lacking in performance.

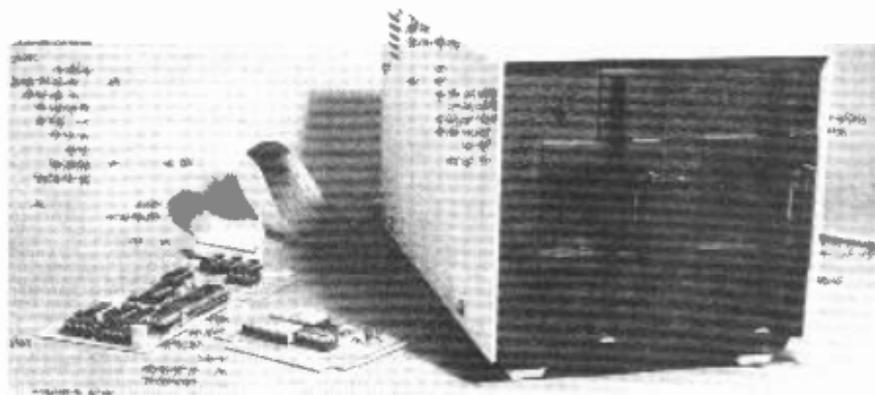If you can't wait for Commodore's floppy disk unit, this product from Computhink is available now and plugs into a PET that has been fitted with a minimum of 16K additional memory.



Toying With MPUs

At last the MPU has found its way into the toy market. Christmas saw a number of electronic games. Invicta's Mastermind being one of the most popular and the new year is seeing many more games added to the shop's shelves.

The current rage in America is a game called Simon. Presented with four buttons of different colours, the player has to remember the sequence in which the machine calls them. The sequence starts off with just two colours but rapidly extends this until the player must press the four buttons in a sequence that as it extends will eventually defeat the user.

Not very easy to explain but it's all the rage in the US and will be over here soon — you'll be able to see it for yourself then.

Super Ohio

I am assured that the long awaited Ohio Scientific's Superboard II will be available "off the shelf" within the next 45 days. Needless to say I am trying very hard to get hold of one of these boards and will report on its performance soon.

ETI

Back numbers

Not all back issues of ETI are available. Indeed more are not than are! The table below shows which copies can be obtained from our offices. Each copy costs 50p inc p&p and please mark your envelopes "Back Issues".

	1978	1977	1976	1975	1974	1973	1972
Jan				No!	No!	No!	No!
Feb				No!			No!
March		No!			No!		
April			No!	No!		No!	No!
May	No!	No!		No!		No!	No!
June	No!		No!	No!			No!
July		No!		No!			No!
Aug	No!	No!		No!		No!	No!
Sept				No!	No!	No!	No!
Oct			No!	No!	No!	No!	No!
Nov			No!	No!	No!	No!	No!
Dec			No!	No!	No!	No!	No!

Photocopies of any article from any one issue are available, and cost 50p regardless of nos. of pages. Copies of series will be charged at article rate per installment. Mark envelope "P".

**ALL INVOICES, ENQUIRIES, ETC., TO
OUR TEMPORARY ADDRESS OF
CHILTMEAD LTD
NORWOOD ROAD
READING
TELEPHONE NO. READING 65916**

15 — 240 Watts!

HY5

Preamplifier

HY5 is a 5Watt preamplifier with a frequency response of 20Hz to 20kHz. It is designed to be used as a preamplifier for a variety of audio systems. It has a high input impedance and a low output impedance. It is available in a variety of packages and is priced at £5.27 + 79p VAT P&P free.

FEATURES

- 5Watt output
- Frequency response 20Hz to 20kHz
- High input impedance
- Low output impedance

APPLICATIONS

- Pre-amplifier for audio systems

SPECIFICATIONS

- Output power: 5Watt
- Frequency response: 20Hz to 20kHz
- Input impedance: 10kΩ
- Output impedance: 100Ω

Price £5.27 + 79p VAT P&P free



HY30

15 Watts into 8Ω

HY30 is a 15Watt amplifier with a frequency response of 20Hz to 20kHz. It is designed to be used as a power amplifier for a variety of audio systems. It has a high input impedance and a low output impedance. It is available in a variety of packages and is priced at £6.22 + 79p VAT P&P free.

FEATURES

- 15Watt output
- Frequency response 20Hz to 20kHz
- High input impedance
- Low output impedance

APPLICATIONS

- Power amplifier for audio systems

SPECIFICATIONS

- Output power: 15Watt
- Frequency response: 20Hz to 20kHz
- Input impedance: 10kΩ
- Output impedance: 100Ω

Price £6.22 + 79p VAT P&P free



HY50

25 Watts into 8Ω

HY50 is a 25Watt amplifier with a frequency response of 20Hz to 20kHz. It is designed to be used as a power amplifier for a variety of audio systems. It has a high input impedance and a low output impedance. It is available in a variety of packages and is priced at £9.10 + £1.02 VAT P&P free.

FEATURES

- 25Watt output
- Frequency response 20Hz to 20kHz
- High input impedance
- Low output impedance

APPLICATIONS

- Power amplifier for audio systems

SPECIFICATIONS

- Output power: 25Watt
- Frequency response: 20Hz to 20kHz
- Input impedance: 10kΩ
- Output impedance: 100Ω

Price £9.10 + £1.02 VAT P&P free



HY120

60 Watts into 8Ω

HY120 is a 60Watt amplifier with a frequency response of 20Hz to 20kHz. It is designed to be used as a power amplifier for a variety of audio systems. It has a high input impedance and a low output impedance. It is available in a variety of packages and is priced at £15.01 + £1.52 VAT P&P free.

FEATURES

- 60Watt output
- Frequency response 20Hz to 20kHz
- High input impedance
- Low output impedance


APPLICATIONS

- Power amplifier for audio systems

SPECIFICATIONS

- Output power: 60Watt
- Frequency response: 20Hz to 20kHz
- Input impedance: 10kΩ
- Output impedance: 100Ω

Price £15.01 + £1.52 VAT P&P free

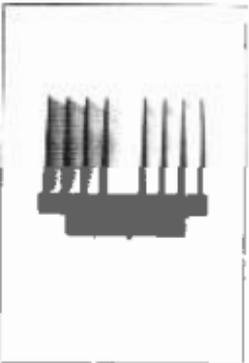

HY200

120 Watts into 8Ω

HY200 is a 120Watt amplifier with a frequency response of 20Hz to 20kHz. It is designed to be used as a power amplifier for a variety of audio systems. It has a high input impedance and a low output impedance. It is available in a variety of packages and is priced at £23.88 + £2.34 VAT P&P free.

FEATURES

- 120Watt output
- Frequency response 20Hz to 20kHz
- High input impedance
- Low output impedance

APPLICATIONS

- Power amplifier for audio systems

SPECIFICATIONS

- Output power: 120Watt
- Frequency response: 20Hz to 20kHz
- Input impedance: 10kΩ
- Output impedance: 100Ω

Price £23.88 + £2.34 VAT P&P free

HY400

240 Watts into 4Ω

HY400 is a 240Watt amplifier with a frequency response of 20Hz to 20kHz. It is designed to be used as a power amplifier for a variety of audio systems. It has a high input impedance and a low output impedance. It is available in a variety of packages and is priced at £38.81 + £3.88 VAT P&P free.

FEATURES

- 240Watt output
- Frequency response 20Hz to 20kHz
- High input impedance
- Low output impedance

APPLICATIONS

- Power amplifier for audio systems

SPECIFICATIONS

- Output power: 240Watt
- Frequency response: 20Hz to 20kHz
- Input impedance: 10kΩ
- Output impedance: 100Ω

Price £38.81 + £3.88 VAT P&P free



POWER SUPPLIES

HY400 is a 240Watt power supply with a frequency response of 20Hz to 20kHz. It is designed to be used as a power supply for a variety of audio systems. It has a high input impedance and a low output impedance. It is available in a variety of packages and is priced at £25.42 + 20p VAT.

FEATURES

- 240Watt output
- Frequency response 20Hz to 20kHz
- High input impedance
- Low output impedance

APPLICATIONS

- Power supply for audio systems

SPECIFICATIONS

- Output power: 240Watt
- Frequency response: 20Hz to 20kHz
- Input impedance: 10kΩ
- Output impedance: 100Ω

Price £25.42 + 20p VAT

TWO YEARS GUARANTEE ON ALL OF OUR PRODUCTS

I.L.P. Electronics Ltd,
Graham Bell House
Roper Close
Canterbury
Kent CT2 7EP
Tel (0227) 54778

Please Supply _____
Total Purchase Price _____
I Enclose Cheques _____ Postal Order _____ Money Order _____
Please debit my Account _____ Bank Transfer _____
Account number _____
Name & Address _____
Signature _____

computing today

WHAT'S IN THE APRIL ISSUE



NASCOM ADD ONS

The NASCOM 1 computer has been one of the most successful of the DIY computer kits on the market recently. NASCOM introduced a number of extras that allow the basic machine's potential to be considerably enhanced.

We take a look at the expansion board and RAM card as well as the TINY BASIC Nascom are now offering.

EXPANDA PET

The Commodore PET has been with us for over a year now but peripherals for the computer have been slow to appear. One of the essential devices in many applications is a floppy disk to provide a system of mass storage that is faster in operation than the tape system of the standard machine.

Next month we review the CompuThink disk drive and disk-mom operating system that will plug straight into your PET.

COMPUTER SURVEY

The number of small systems on the market has increased greatly over the past year and the choice of a machine to suit your application.

The April issue of Computing Today surveys some of the more popular small computers and presents in a clear, concise, fashion the capabilities and facilities offered by the different products.

"YOU CAN TAKE A HORSE TO WATER, BUT SELF-ILLUMINATING DISPLAYS MUST BE L.E.D." !!



"DON'T CARE 4 PAPER! MULTICOLOR BUBBLES ARE BOUNTY 4 ME - I WANT 'EM L.I.C.E." !!



AMBUSH GAME

The April issue of our sister magazine, ETI, carries a project called Ambush. Ambush is an

exciting space war game. Computing Today will carry a program that will allow those of you who don't dabble in electronics to play Ambush on your computer.

CONSUMER SHOW

The recent Winter Consumer Electronic Show in Las Vegas saw the introduction of many new MPU based products including a chess challenger that talks.

Gerald Chevin was there for Computing Today and his report appears in the April issue.



Plus all the regular features, news, softspot, hardlines and next month, a new regular letters page.

WIND METER

Here is the project all you amateur meteorologists have been waiting for. When this meter gets the wind up you'll know how fast and where it's coming from.

TRADITIONALLY THE FOUR primary elements are fire, earth, water and air. At ETI, we've designed projects concerned with the first three (temperature meters, soil moisture indicators, rain alarms) but not much for the last. The major property of the air, apart from the fact that it is necessary to support life, is the movement of the air — wind. Light winds generally aren't of terribly much significance except to meteorologists, but stronger winds can be useful as a source of power for traditional milling, for electricity generation or as a means of propulsion for sailing yachts. Stronger winds such as hurricanes, can be destructive, causing damage to life or property.

So for all the private pilots, yachtsmen, amateur meteorologists and general weather watchers who read ETI, here is a device which will tell you the wind's speed and direction, with a remote indication of both quantities. Our design is, we'd like to think, both stylish and unusual, but there are simpler methods of mechanical construction which you can follow if you wish.

The Head

The drawings along with the photos will give the general design that we used. The actual dimensions have to be left to the individual constructor as components such as the ball races and light bulbs may vary in size.

While we used a single head for both speed and direction, it may be simpler to use separate heads.

The discs we used were 1.5mm thick clear plastic with a piece of photographic film glued onto it. It may be easier to make it out of thin aluminium and cut out the slots. For the speed disc, simply drilling holes will suffice.

The most important part of the design, apart from ensuring that the discs rotate with a minimum of friction, is the shielding of the light and preventing light scatter striking a

transistor which should be dark. As can be seen from the photos and diagram, the bulbs and transistors are embedded in aluminium blocks with small holes providing a passage for the light beam.


The wiring of the head is shown in fig. 3. Note that the base lead is not used and can be cut off close to the body. Insulate the joints onto the transistors to ensure that they do not short on the aluminium blocks. The bulbs may touch the block with their outer connection but this is the 0 volt line and does no harm. In fact it provides some electrical shielding for the leads. The bulbs we used were 12V but they were bright enough on 6V giving a much longer life.

Design Features

When we started design on this project it was to have a digital

readout of wind direction with a resolution of either one or two degrees. This would also make it useful in a sailing boat to tell the wind direction relative to the heading.

Difficulties however soon became apparent. The first of these was the sensor head. The only accurate method is a digital head, probably optical. Two methods could have been used, one using a disc with a single optical track of 360 slots and an updown counter and the second using eight or nine tracks in a grey code. The first is simpler in head design but the second is less prone to error. The problem, and the reason for rejecting both, is that with such resolution, the reading would move around so much when the wind is gusty to be unreadable. What is needed is an averaging circuit which unfortunately becomes

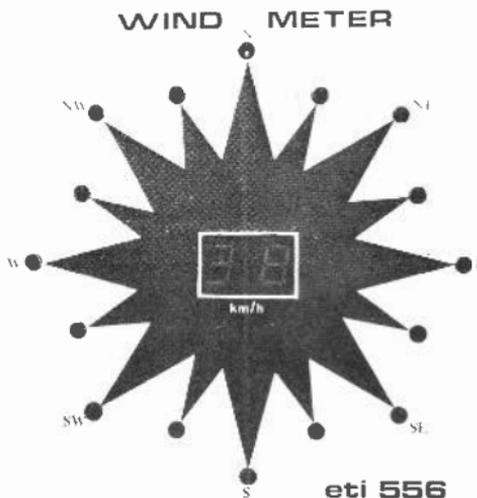

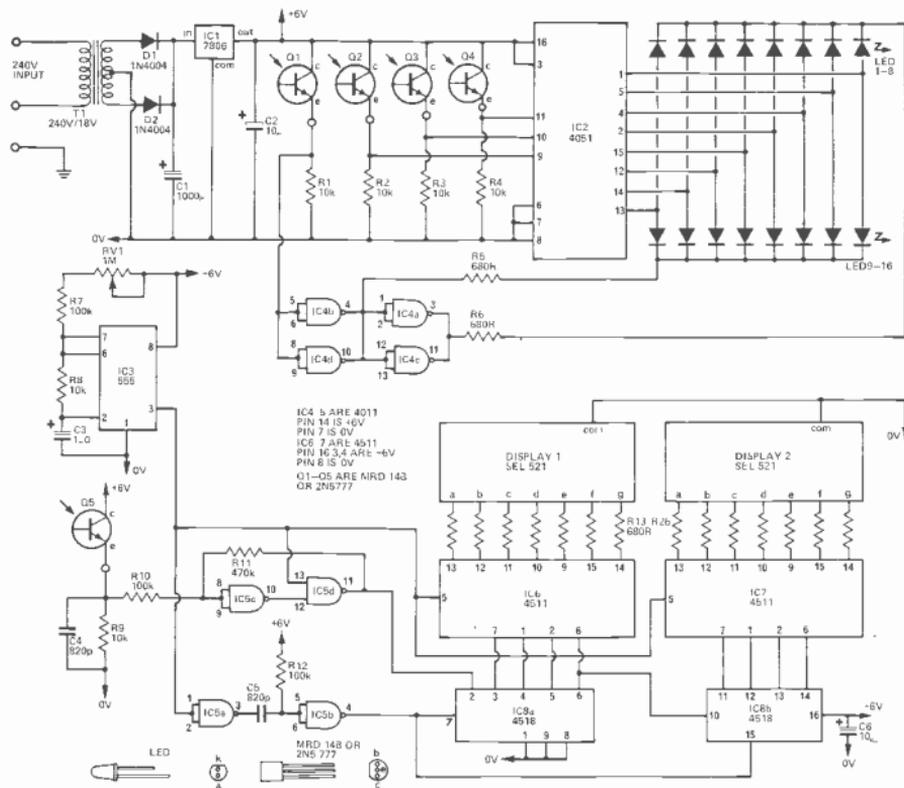


Fig. 1. Complete circuit diagram of the ET1 Wind Meter

difficult when the wind is changing from just west of north to just east of north i.e. 355 to 005. How do you average these (use a microprocessor?)

As this was intended to be a simple project we relaxed our original specification, deleting the use in a boat (we may get back to this problem). A four track 'Grey' scale allows the wind to be given to within 11° of its true heading, without the complexity of a nine track one, and the use of LEDs to give direction solves the problem of averaging as the variations can be seen and averaged by the brain.

Construction

The electronics is relatively simple provided the PCB described is used. Due to a height limitation C1 should be mounted on the rear of the board. The LEDs should be mounted about 7mm from the board with care being taken not to damage them as the leads have to be bent out slightly. The regulator also has to lie down to give clearance.

We mounted the unit behind an aluminium front panel with the LEDs protruding through holes. If this is to be done it is preferable not to solder the LEDs until after alignment with

the front panel.

The head is more difficult as some mechanical ability is necessary to ensure good results. The requirements are basically simple. A disc is to be allowed to rotate either continuously with the wind or aligning it to the wind with a bulb on one side and phototransistors on the other.

The method used by us is shown in fig 4 with the aluminium blocks providing the shielding necessary to give accurate results. As the unit will be exposed to the weather it must be made waterproof otherwise the ball races will corrode. The races used

HOW IT WORKS

Wind Direction

Wind direction is indicated by a series of 18 equally spaced LEDs around a circle. These represent the main points on the compass. These are controlled by IC2 and IC4 which are in turn controlled by the direction sensor head.

The sensor head, which is described in fig. 3, consists of a disc which has four optical tracks and four bulbs and phototransistors. The phototransistors sense either a clear disc (logical "1") or a black disc (logical "0") and thus control IC2 and IC4. The code used is special in that only one bit is changed at each location eliminating gross errors which occur with the binary code if the heads are not perfectly aligned. An example of this is going from location 7 (0111) to location 8 (1000). If this is not done simultaneously almost any location can be specified. With the grey code the same change is from 0100 to 1100. Here there can be no ambiguity as only one bit is changed. Remember these bits are not weighted similarly to binary and a lookup table must be used to decide what number (decimal) a particular code is.

The decoder, IC2, is an eight output analogue demultiplexer with the common line joined to the +3V line. When a particular 3 bit code is presented to its control inputs one of the eight outputs will be joined to the +6V line. The fourth output from the sensor head controls IC4 which gives two inverted, outputs to drive either bank of LEDs. The complete four bit code therefore specifies a particular LED to be lit. By placing the LEDs correctly around the circle the grey code is decoded.

Wind Speed


This is a simple frequency counter measuring pulses from the sensor head. The head consists of a disc with eight holes which breaks a light beam to its associated phototransistor. The output of this phototransistor is squared up by a schmitt trigger formed by IC5c and IC5d.

The counting is done by IC8a and IC8b (a dual decade counter) with IC6 and IC7 providing the store and LED drivers necessary to drive the seven segment display. Time base is provided by IC3 which gives a 7 mS wide negative pulse about every one second. We say about as it is adjustable by RV1 as individual heads will have different responses and calibration will be necessary.


This negative pulse opens the store to allow the number reached by the counters to be displayed while simultaneously stopping any further counting by disabling the schmitt trigger. On the completion of the 7mS pulse IC3a and IC3b generate a 90mS wide pulse which resets the counter IC8 to recommence the sequence.

Power Supply

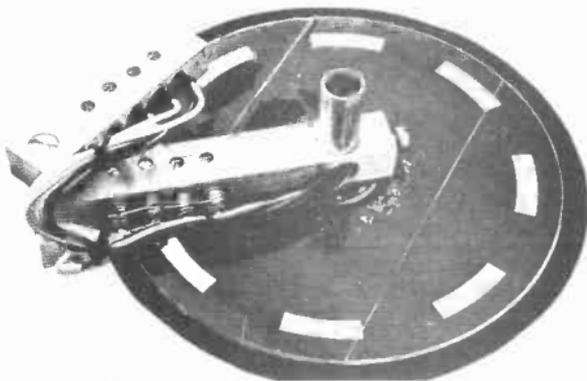This is simply a full wave rectified supply with IC1 giving a regulated +6V output. This regulation is needed to ensure that the time base (IC3) remains accurate.



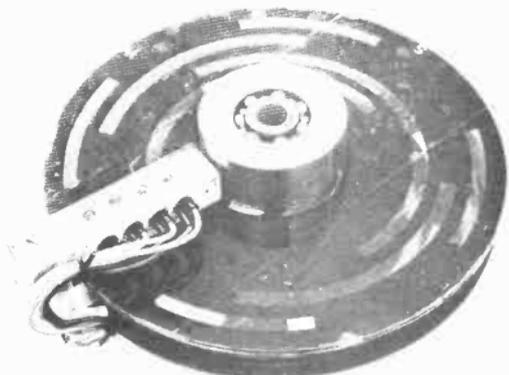Above and Below: Constructional details of the sensor head



The finished unit in use

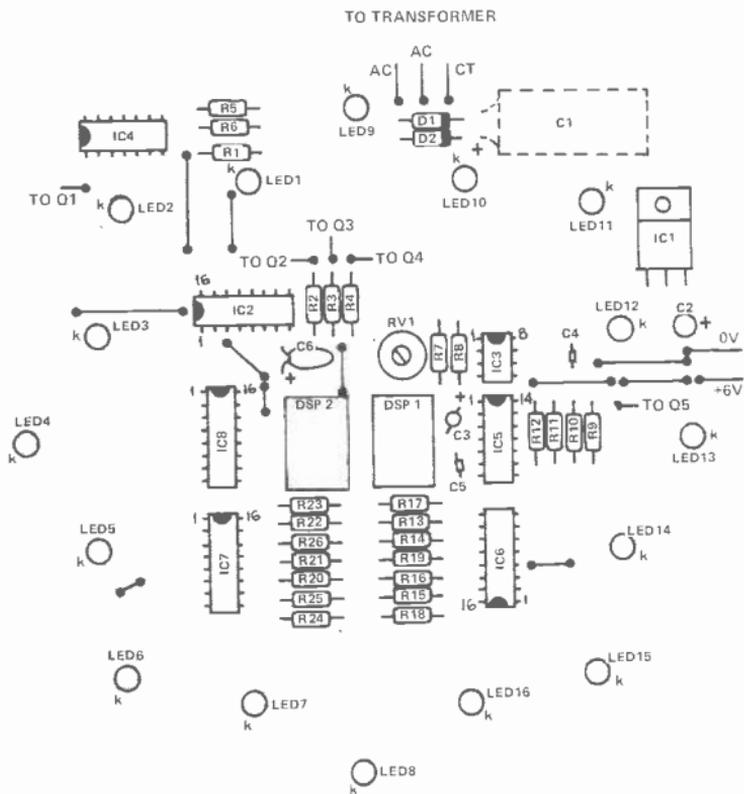


Fig. 2. Component overlay for the Wind Meter

PARTS LIST

RESISTORS (all 1/4W 1%)		SEMICONDUCTORS	
200-4.5K	10K	C1	1000p
98.5K-20K	0.60P	C2	1000p
85.1K-12K	100K	IC3	555
R11	470K	IC4, 5	4011
		IC5, 7	4011
		IC2	4016
		IC1, 6	2N5771
POTENTIOMETER		C1, 2	1N4004
RV1	1M trimmer	LED 1-16	T1, 209 or similar
		DSP 1, 2	Cermet or cathode near segment (high brightness)
CAPACITORS		VISCELLANEOUS	
C1	1000p, 16V		Four miniature 1.2V bulbs; PCB1, 240V/
C2, 6	10u, 25V		10V transformer box, head assembly
C3	1u, 25V		
C4, 5	820p ceramic		


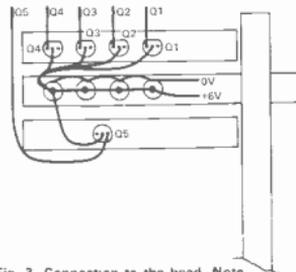


Fig. 3. Connection to the head. Note that transistor bases are not used.

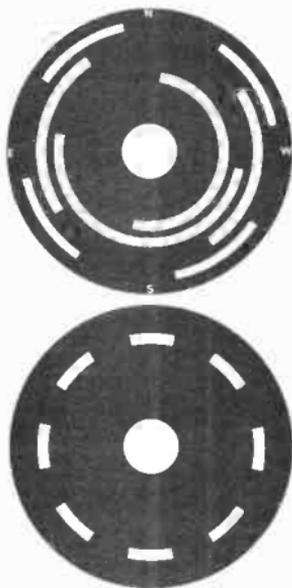

Discs used in the sensor head — 1.5 mm thick, clear plastic with photographic film glued on.

will normally have to be washed out to give low enough friction with a light spray of WD40 or similar to give some protection.

While our housing is a little ornate, it did work but the more usual half ping pong balls may be more suitable.

Calibration

Wind Speed.

The easiest method for wind speed calibration is to provide the unit with a DC supply (via the common and one of the AC inputs) and to take a drive in the car with the unit supported above the vehicle. Providing there is no wind the potentiometer should be adjusted until the reading corresponds to the speed.

Direction alignment is simply a matter of aligning the vertical rod so that it gives the correct results.

ETI

BUYLINES

The metalwork for this project we must leave to our readers, as this will be fabricated to suit individual requirements. The displays can be any type no's really, just observe polarity. Similarly with the LEDs. The photodiodes can be supplied by Marshall's.

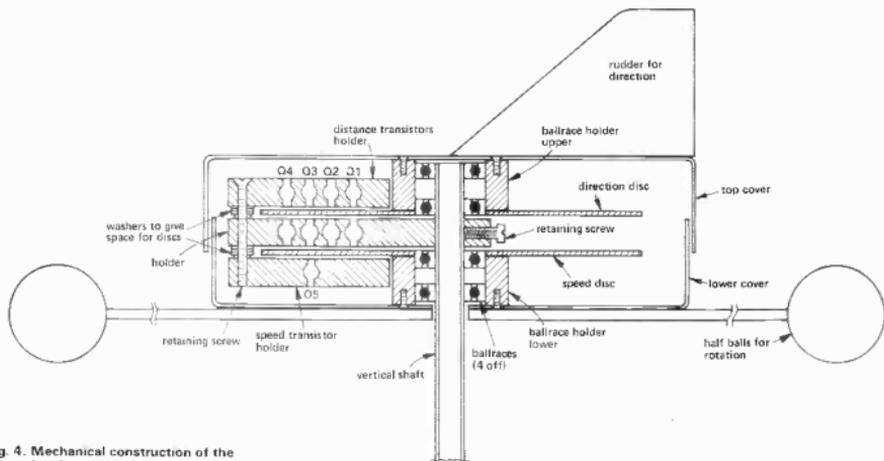


Fig. 4. Mechanical construction of the sensor head.

electronics today

international


What to look for in the May issue: On sale April 6th

START YOUR OWN ARMOURED DIVISION

Ever fancied driving your own tank across the battlefields? Or taking a Porsche around a racetrack at 140mph? Well, much as we'd like to build a Chevrolet as a project it would never go into one issue and so we offer you a fully proportional six channel radio control system for models instead.

The design offers joystick control (or switched position) and special attention has been paid to metalwork and setting up procedure. A kit of metalwork (and ready wound coils) will be available, and alignment requires nought but a simple voltmeter.

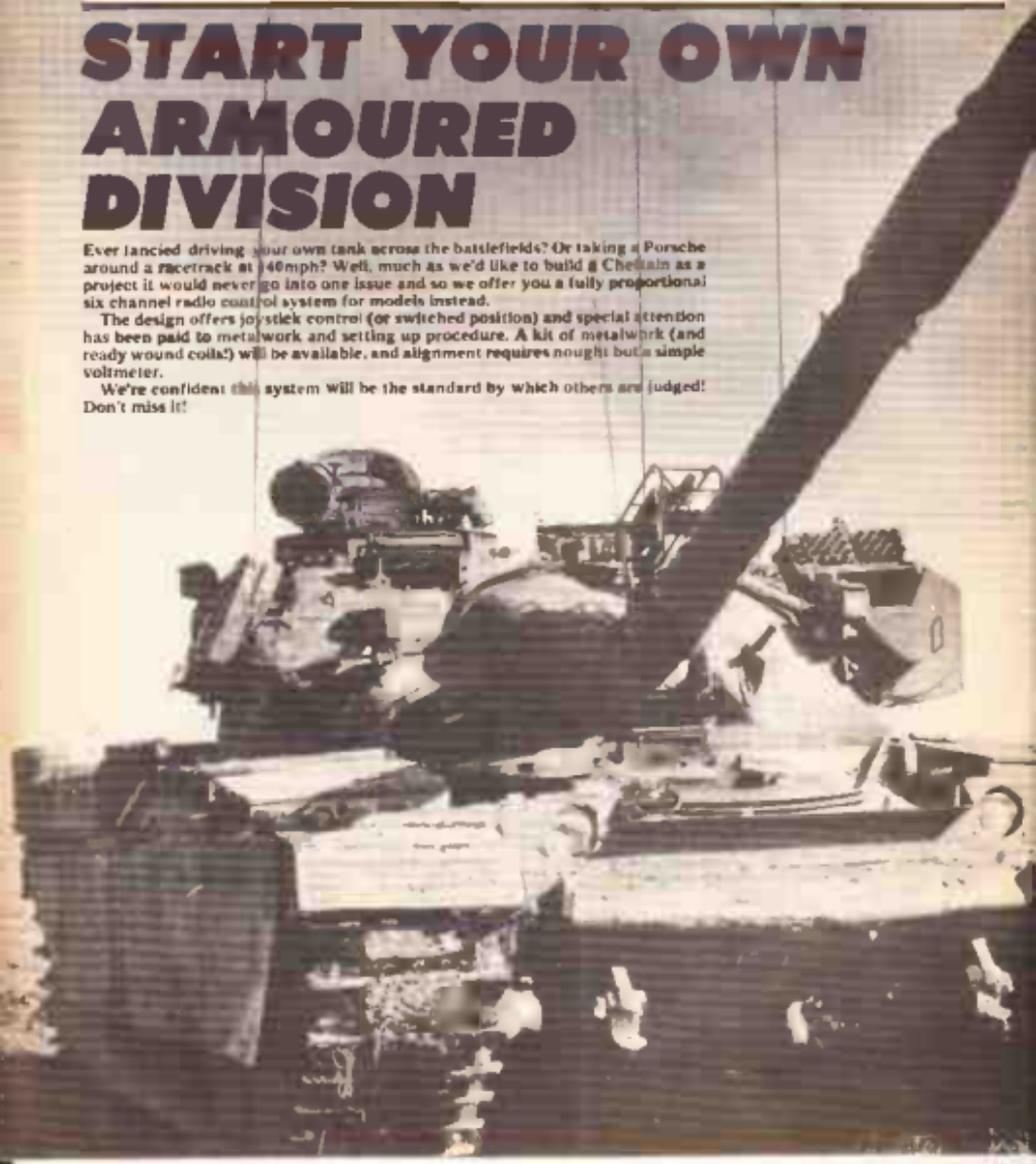We're confident this system will be the standard by which others are judged! Don't miss it!



How It Works - AM/FM

The second in our occasional series by Gordon King. This time he turns his attention to radio, and goes in and out of the ins and outs in great, easily explained, detail. Masses of circuits to illustrate the points, and a must for anyone remotely interested in the field.

SAW POINT

Its goodbye to the faithful IF strip as we know it. SAW will soon be found in TV receivers, replacing the usual array of coils and capacitors. You can expect to see and hear a lot more about them in the future, be one jump ahead and read the expose in next month's ETL P.S. SAW - Surface Acoustic Wave!

DOUBLE DICE

OK, so you've seen them before. Ours have a novel method of display decoding, switchable odds to allow adaptation for wargaming, etc. Single board construction makes life easier and overall we think its a nice one!

See what you think next month.



HEADPHONE AMPLIFIER

A project to warm the ears and please the rest of the universe. Based on a high quality Class A design, this unit provides hi-fi drive for one or more pairs of dynamic headphones, allowing you to wallow within an undisturbed sound field, and leaves everyone around free to do their own thing without having to listen to yours.



SINTEL

**SOME 74LSPTL
NOW AVAILABLE
PLEASE SEND FOR LIST**

NEW PRICES AND SOME NEW CMOS ADDITIONS

Part No.	Manufacturer	Price	Part No.	Manufacturer	Price
CMOS01	74LS01	0.84	74LS01	74LS01	1.10
CMOS02	74LS02	0.71	74LS02	74LS02	1.10
CMOS03	74LS03	1.02	74LS03	74LS03	1.10
CMOS04	74LS04	0.80	74LS04	74LS04	1.10
CMOS05	74LS05	2.00	74LS05	74LS05	1.10
CMOS06	74LS06	0.81	74LS06	74LS06	1.10
CMOS07	74LS07	1.25	74LS07	74LS07	1.10
CMOS08	74LS08	1.74	74LS08	74LS08	1.10
CMOS09	74LS09	1.06	74LS09	74LS09	1.10
CMOS10	74LS10	2.18	74LS10	74LS10	1.10
CMOS11	74LS11	0.95	74LS11	74LS11	1.10
CMOS12	74LS12	0.82	74LS12	74LS12	1.10
CMOS13	74LS13	2.78	74LS13	74LS13	1.10
CMOS14	74LS14	0.97	74LS14	74LS14	1.10
CMOS15	74LS15	0.75	74LS15	74LS15	1.10
CMOS16	74LS16	0.89	74LS16	74LS16	1.10
CMOS17	74LS17	0.88	74LS17	74LS17	1.10
CMOS18	74LS18	0.84	74LS18	74LS18	1.10
CMOS19	74LS19	0.86	74LS19	74LS19	1.10
CMOS20	74LS20	0.89	74LS20	74LS20	1.10
CMOS21	74LS21	0.86	74LS21	74LS21	1.10
CMOS22	74LS22	0.86	74LS22	74LS22	1.10
CMOS23	74LS23	0.89	74LS23	74LS23	1.10
CMOS24	74LS24	0.86	74LS24	74LS24	1.10
CMOS25	74LS25	0.89	74LS25	74LS25	1.10
CMOS26	74LS26	0.86	74LS26	74LS26	1.10

ORDERS TO SINTEL, PO BOX 75A, OXFORD
Tel: 0865-49781



VERO

OUR RANGE OF
PRODUCTS ARE NOW INDIVIDUALLY
AND ATTRACTIVELY PACKAGED

Order of goods with metal
cases for extra protection. And we want
your business! We offer systems and
components which you need to use
your computer. The quality of our
products is guaranteed. Send
for our price list today. It's free.

VERO ELECTRONICS LTD. RETAIL DEPT
Industrial Estate, Chardlers Ford, Hants. SO5 3ZR
Telephone (01263) 2151 2956

NEW LOW PRICES

56-STATION ASCII KEYBOARD

NOW IN STOCK — ASCII KEYBOARD MODEL KB756



SELF SCAN ALPHANUMERIC PANEL DISPLAY	
5 x 7 dot matrix	0 characters 8% + 2%
with character code	1% Supply with
type 2 x 1 dot matrix	100% 2% 200% 4%
0-9 0-9 ROM code	100 100 100 100
0-9 0-9 ROM code	100 100 100 100
0-9 0-9 ROM code	100 100 100 100
0-9 0-9 ROM code	100 100 100 100

SEAELECTRO PATCH BOARDS

Programme boards for switching and interconnecting input/output circuitry 11 x 20 XY matrix. Includes connection to 16 pins of micro-processor and component holding pins. (not supplied). Connections: 74 = 54 x 1

PRICE: £12.50
(mail order total £14.50)

NEW KEYTOP/ KEYSWITCH KITS

Pack of 56 keyswitches plus 56 keytops consisting of standard ASCII characters. Ideal as a base for self-build keyboards and projects.

**BRAND NEW SURPLUS
PRICE: £15.00**
(mail order total £17.20)

HAZELTINE VISUAL DISPLAY UNIT

- Teletype Compatible
- 12" Diagonal Screen
- TTY Format Keyboard
- 12 lines of 80 characters
- 64 ASCII Character Set
- 6 x 7 Dot Matrix
- Switch selectable Transmission Speeds up to 3600 baud
- Switch selectable Parity
- Standard CCITT V 24 interface



MODEL H-1000 PRICE £350 (mail order total £370)

Also available —
Model H 2000 Buffered Editing model with direct cursor addressing, dual intensity video and detachable keyboard with separate numeric and edit clusters. 27 lines of 74 characters. Price £495.00 - carriage + VAT

ELECTRONIC BROKERS LTD.
49-53 Pancras Road, London, NW1 2QB
Tel: 01 837 7781 Telex: 298694

A breadboard as big as your ideas.

EXPERIMENTER 325 £2.54

The ideal Breadboard for 1 chip circuits. Accepts 8, 14, 16 & up to 22 pin IC's. Has 100 contact points including two 40 point bus bars.

EXPERIMENTER 600 £7.88

The Breadboard for quick construction of Microprocessors and other circuits. EXP 600 has 550 contacts including two 40 point bus bars with 0.6 centres.

EXPERIMENTER 650 £4.70

Perfect for checking out Microprocessors. EXP 650 has 270 contacts including two 20 point bus bars with 0.6 centres.

EXPERIMENTER QUAD BUS STRIP £3.29

Need more bus bars? Use an EXP 4B and you have four 40 point bus strips with 8, 12 and 16 line address. Create other buses by combining EXP 4B Bus Strips.



No soldering simply plug all standard components in and out. Pick up all contacts at 0.6 centres. Breadboard and components may be used over and over again without damage.


Adaptable accepts any component without adjustment. Jumpers use 22/30 gauge solid wire in simple ways.

Mix and Match large and small components in the same circuit. Use 100 series for small and 0.3 inch DIP's 600 series for Microprocessors with 0.6 centres. Change effortlessly for other large chips.

Smallest to Biggest, remember CSC's Breadboards snap back together so you can start with a small idea and expand it to fit into as Big a Breadboard area as you like.

Easy Permanent Mounting, simply push sockets from front or side. Leads are visible. Vinyl insulate and back panel if you prefer to etch surface.

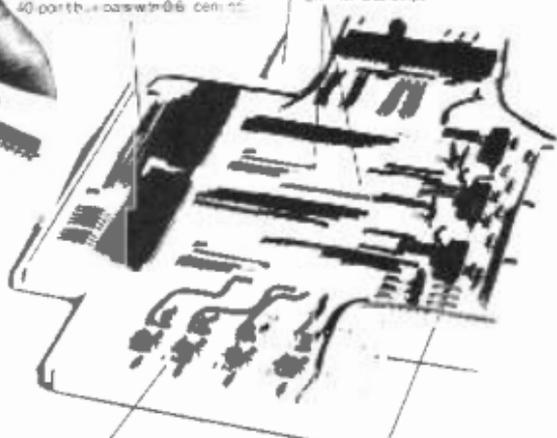Pick any project you want to build or any part of a project that you want to test or modify. Count the number of IC's you need or the project. Then simply look up the box or boxes in the Breadboard you require. You need more than two bus bars simply add the number of Quad Bus Strips. GET STARTED NOW. FOR AS LITTLE AS £2.54



EXPERIMENTER 350 £4.21

EXP 350 specifically designed for the hobbyist working with up to 3 x 14 DIP IC's. With 270 contact points including two 20 point bus bars the EXP 350 accepts a 14 pin DIP with 0.3 spacing.

Marked Contact Points transfer component by component from letter number positions on Breadboard to finished P.C. Board or Wiring Table.

Ruggedly built of an injection resistant material which withstands 100°C.

EXPERIMENTER 300 £2.29

The hobbyists' ideal Breadboard accepts 6 x 14 DIP or 5 x 16 DIP has 550 contact points including two 40 point bus bars accepts any size DIP with 0.3 spacing.

Tailor-Made Breadboards are a project realises up to 5 x 14 DIP chips and needs up to six bus bars. Which to buy? Easy from the table below select an EXP 300 plus an EXP 4B. Total cost £10.58.

	1	4	5	6	8	10	12	14	16	18	20	22	24	26	28	30	32	34	36	38	40
	1	4	5	6	8	10	12	14	16	18	20	22	24	26	28	30	32	34	36	38	40
EXP 300	£2.29	£2.29	£2.29	£2.29	£2.29	£2.29	£2.29	£2.29	£2.29	£2.29	£2.29	£2.29	£2.29	£2.29	£2.29	£2.29	£2.29	£2.29	£2.29	£2.29	£2.29
EXP 4B	£1.29	£1.29	£1.29	£1.29	£1.29	£1.29	£1.29	£1.29	£1.29	£1.29	£1.29	£1.29	£1.29	£1.29	£1.29	£1.29	£1.29	£1.29	£1.29	£1.29	£1.29
EXP 350	£4.21	£4.21	£4.21	£4.21	£4.21	£4.21	£4.21	£4.21	£4.21	£4.21	£4.21	£4.21	£4.21	£4.21	£4.21	£4.21	£4.21	£4.21	£4.21	£4.21	£4.21
EXP 600	£7.88	£7.88	£7.88	£7.88	£7.88	£7.88	£7.88	£7.88	£7.88	£7.88	£7.88	£7.88	£7.88	£7.88	£7.88	£7.88	£7.88	£7.88	£7.88	£7.88	£7.88
EXP 650	£4.70	£4.70	£4.70	£4.70	£4.70	£4.70	£4.70	£4.70	£4.70	£4.70	£4.70	£4.70	£4.70	£4.70	£4.70	£4.70	£4.70	£4.70	£4.70	£4.70	£4.70
EXP 325	£2.54	£2.54	£2.54	£2.54	£2.54	£2.54	£2.54	£2.54	£2.54	£2.54	£2.54	£2.54	£2.54	£2.54	£2.54	£2.54	£2.54	£2.54	£2.54	£2.54	£2.54
EXP 350	£4.21	£4.21	£4.21	£4.21	£4.21	£4.21	£4.21	£4.21	£4.21	£4.21	£4.21	£4.21	£4.21	£4.21	£4.21	£4.21	£4.21	£4.21	£4.21	£4.21	£4.21
EXP 600	£7.88	£7.88	£7.88	£7.88	£7.88	£7.88	£7.88	£7.88	£7.88	£7.88	£7.88	£7.88	£7.88	£7.88	£7.88	£7.88	£7.88	£7.88	£7.88	£7.88	£7.88
EXP 650	£4.70	£4.70	£4.70	£4.70	£4.70	£4.70	£4.70	£4.70	£4.70	£4.70	£4.70	£4.70	£4.70	£4.70	£4.70	£4.70	£4.70	£4.70	£4.70	£4.70	£4.70
EXP 325	£2.54	£2.54	£2.54	£2.54	£2.54	£2.54	£2.54	£2.54	£2.54	£2.54	£2.54	£2.54	£2.54	£2.54	£2.54	£2.54	£2.54	£2.54	£2.54	£2.54	£2.54

CONTINENTAL SPECIALITIES CORPORATION



Europe Africa Mid East CSC UK LTD
Shire Hill Industrial Estate Units 1 and 2
Saffron Walden Essex CB11 3AG Unit 1
Telephone Number SAFFRON WALDEN 21682
Telex 817477

TO ALL TRADERS, MAIL ORDER HOUSES
CONTACT MRS TINA KNIGHT FOR "PROFIT-PACKAGE" DETAILS

ACCESSORIES ARE ONLY AVAILABLE TO THESE CUSTOMERS WHO ARE BUYING OUR BARGAIN PACKS

Mullard

AUDIO MODULES IN BARGAIN PACKS CURRENT CATALOGUE

PRICE \$ AT OVER 25 PER PACK

SEE OUR PRICES

- 1** PACK 2 - LPT102 10w RMS output power audio amp module - 1 LPT102/2 Service amp for car stereo and auxiliary input. **OUR PRICE per £1.95**
- 2** PACK 2 - LPT103 10w RMS output power audio amp module - 1 LPT104/2 Stereo amp for magnetic, cassette and auxiliary input. **OUR PRICE per £1.95**



ACCESSORIES

Available separately, particularly music cassette tapes, including recommended test CD's, cassette tapes, cassette tapes, cassette tapes, cassette tapes. **OUR PRICE per £1.95**

Recommended test CD's, cassette tapes, cassette tapes, cassette tapes, cassette tapes. **OUR PRICE per £1.95**



20 x 20 WATT STEREO AMPLIFIER

Two channel stereo amplifier with 20W RMS output power and 20W RMS output power. Features include: 1) 20W RMS output power, 2) 20W RMS output power, 3) 20W RMS output power, 4) 20W RMS output power.

£29.90

SPECIAL OFFER FOR PERSONAL SHOPPERS ONLY

For the experienced audiophile, the 30x30 Watt Amplifier in Kit Form is a must have. It features a 30W RMS output power and 30W RMS output power. Features include: 1) 30W RMS output power, 2) 30W RMS output power, 3) 30W RMS output power, 4) 30W RMS output power.

£29.00

SPECIAL OFFER 30x30 Watt Amplifier in Kit Form with Speakers

2 Channel stereo amplifier with 30W RMS output power and 30W RMS output power. Features include: 1) 30W RMS output power, 2) 30W RMS output power, 3) 30W RMS output power, 4) 30W RMS output power.

£49.00

BUILT AND READY TO PLAY 39.00

30x30 Watt Amplifier in Kit Form with Speakers

EMI SPEAKER BARGAIN

Speaker 120 or 150mm diameter with 11" x 18" speaker with 10W RMS output power. Features include: 1) 10W RMS output power, 2) 10W RMS output power, 3) 10W RMS output power, 4) 10W RMS output power.

£14.95

BSR P200

100 Watt Stereo Amplifier with 100W RMS output power and 100W RMS output power. Features include: 1) 100W RMS output power, 2) 100W RMS output power, 3) 100W RMS output power, 4) 100W RMS output power.

£24.95

BSR P200

100 Watt Stereo Amplifier with 100W RMS output power and 100W RMS output power. Features include: 1) 100W RMS output power, 2) 100W RMS output power, 3) 100W RMS output power, 4) 100W RMS output power.

£7.75

GARRARD DECK MODEL CC 10A

Record changer with 10W RMS output power and 10W RMS output power. Features include: 1) 10W RMS output power, 2) 10W RMS output power, 3) 10W RMS output power, 4) 10W RMS output power.

£7.95

SANTO Record Changer

Record changer with 10W RMS output power and 10W RMS output power. Features include: 1) 10W RMS output power, 2) 10W RMS output power, 3) 10W RMS output power, 4) 10W RMS output power.

£7.50

100 Watt Stereo Amplifier

100 Watt Stereo Amplifier with 100W RMS output power and 100W RMS output power. Features include: 1) 100W RMS output power, 2) 100W RMS output power, 3) 100W RMS output power, 4) 100W RMS output power.

£19.95

100 Watt Stereo Amplifier

100 Watt Stereo Amplifier with 100W RMS output power and 100W RMS output power. Features include: 1) 100W RMS output power, 2) 100W RMS output power, 3) 100W RMS output power, 4) 100W RMS output power.

£19.95

100 Watt Stereo Amplifier

10+10 AMPIFIER KIT

10+10 Ampifier Kit with 10W RMS output power and 10W RMS output power. Features include: 1) 10W RMS output power, 2) 10W RMS output power, 3) 10W RMS output power, 4) 10W RMS output power.

£11.95



BARGAINS FOR PERSONAL SHOPPERS

100 Watt Stereo Amplifier with 100W RMS output power and 100W RMS output power. Features include: 1) 100W RMS output power, 2) 100W RMS output power, 3) 100W RMS output power, 4) 100W RMS output power.

£5.95

100 Watt Stereo Amplifier with 100W RMS output power and 100W RMS output power. Features include: 1) 100W RMS output power, 2) 100W RMS output power, 3) 100W RMS output power, 4) 100W RMS output power.

£6.95

100 Watt Stereo Amplifier with 100W RMS output power and 100W RMS output power. Features include: 1) 100W RMS output power, 2) 100W RMS output power, 3) 100W RMS output power, 4) 100W RMS output power.

£2.95

100 Watt Stereo Amplifier with 100W RMS output power and 100W RMS output power. Features include: 1) 100W RMS output power, 2) 100W RMS output power, 3) 100W RMS output power, 4) 100W RMS output power.

£11.95

100 Watt Stereo Amplifier with 100W RMS output power and 100W RMS output power. Features include: 1) 100W RMS output power, 2) 100W RMS output power, 3) 100W RMS output power, 4) 100W RMS output power.

£13.95

100 Watt Stereo Amplifier with 100W RMS output power and 100W RMS output power. Features include: 1) 100W RMS output power, 2) 100W RMS output power, 3) 100W RMS output power, 4) 100W RMS output power.

£3.50

100 Watt Stereo Amplifier with 100W RMS output power and 100W RMS output power. Features include: 1) 100W RMS output power, 2) 100W RMS output power, 3) 100W RMS output power, 4) 100W RMS output power.

£1.50

100 Watt Stereo Amplifier with 100W RMS output power and 100W RMS output power. Features include: 1) 100W RMS output power, 2) 100W RMS output power, 3) 100W RMS output power, 4) 100W RMS output power.

£20.00

100 Watt Stereo Amplifier with 100W RMS output power and 100W RMS output power. Features include: 1) 100W RMS output power, 2) 100W RMS output power, 3) 100W RMS output power, 4) 100W RMS output power.

£14.95

100 Watt Stereo Amplifier with 100W RMS output power and 100W RMS output power. Features include: 1) 100W RMS output power, 2) 100W RMS output power, 3) 100W RMS output power, 4) 100W RMS output power.

£41.95

100 Watt Stereo Amplifier with 100W RMS output power and 100W RMS output power. Features include: 1) 100W RMS output power, 2) 100W RMS output power, 3) 100W RMS output power, 4) 100W RMS output power.

£9.95

100 WATT MONO DISCO AMP

100 Watt Mono Disco Amp with 100W RMS output power and 100W RMS output power. Features include: 1) 100W RMS output power, 2) 100W RMS output power, 3) 100W RMS output power, 4) 100W RMS output power.

£29.95

100 Watt Mono Disco Amp with 100W RMS output power and 100W RMS output power. Features include: 1) 100W RMS output power, 2) 100W RMS output power, 3) 100W RMS output power, 4) 100W RMS output power.

£57

100 Watt Mono Disco Amp with 100W RMS output power and 100W RMS output power. Features include: 1) 100W RMS output power, 2) 100W RMS output power, 3) 100W RMS output power, 4) 100W RMS output power.

£65

100 Watt Mono Disco Amp with 100W RMS output power and 100W RMS output power. Features include: 1) 100W RMS output power, 2) 100W RMS output power, 3) 100W RMS output power, 4) 100W RMS output power.

£17.00

100 Watt Mono Disco Amp with 100W RMS output power and 100W RMS output power. Features include: 1) 100W RMS output power, 2) 100W RMS output power, 3) 100W RMS output power, 4) 100W RMS output power.

£17.00

100 Watt Mono Disco Amp with 100W RMS output power and 100W RMS output power. Features include: 1) 100W RMS output power, 2) 100W RMS output power, 3) 100W RMS output power, 4) 100W RMS output power.

£17.00

100 Watt Mono Disco Amp with 100W RMS output power and 100W RMS output power. Features include: 1) 100W RMS output power, 2) 100W RMS output power, 3) 100W RMS output power, 4) 100W RMS output power.

£17.00

100 Watt Mono Disco Amp with 100W RMS output power and 100W RMS output power. Features include: 1) 100W RMS output power, 2) 100W RMS output power, 3) 100W RMS output power, 4) 100W RMS output power.

£20.95

100 Watt Mono Disco Amp with 100W RMS output power and 100W RMS output power. Features include: 1) 100W RMS output power, 2) 100W RMS output power, 3) 100W RMS output power, 4) 100W RMS output power.

£20.95

100 Watt Mono Disco Amp with 100W RMS output power and 100W RMS output power. Features include: 1) 100W RMS output power, 2) 100W RMS output power, 3) 100W RMS output power, 4) 100W RMS output power.

£20.95



RTVC

323 EDGEWARE ROAD, LONDON W2 1JZ

211 HIGH STREET, ACTON W3 6NG

ACTON: Mon Order only. No calls. All prices include GST at 12.5%. All items subject to availability. Price correct as of 1/9 and subject to change without notice.

NOTE: Due to the high demand, please allow extra time for delivery of your order.

NOTE: Due to the high demand, please allow extra time for delivery of your order.

NOTE: Due to the high demand, please allow extra time for delivery of your order.

NOTE: Due to the high demand, please allow extra time for delivery of your order.

NOTE: Due to the high demand, please allow extra time for delivery of your order.

NOTE: Due to the high demand, please allow extra time for delivery of your order.

NOTE: Due to the high demand, please allow extra time for delivery of your order.

NOTE: Due to the high demand, please allow extra time for delivery of your order.

GUITAR EFFECTS UNIT



Our guitar effects unit isn't just a fuzz box. Use it to give you a new sound to play with.

LIKE US, YOU probably thought that one guitar effects unit was much the same as any other. After fuzz and Wah-Wah, what do you do? Well, we think we have come up with a new one - which we have christened

STRUZZ.

With this unit you can select either a conventional fuzz effect or our new struzz effect. A depth control allows you to alter the sustain rate of the effect. If the neighbours start banging the wall, you can instantly cut out the crunchy effects with a bypass switch.

Make-up

Construction should not pose any problems. It's even easier if you use our PCB. Make sure the electrolytic capacitors are put in the correct way round. As always, don't plug in the ICs until you have checked the circuit thoroughly.

Happy fuzzing and struzzing ▶

BUYLINES


The only component that may be difficult to find is the LF356 FET op-amp. Warford Electronics can supply this IC.

Smashing sound

Now you are wondering what struzz sounds like, aren't you? Well, it's a distortion of fuzz. The fundamental frequency of the input is full-wave rectified but the numerous harmonics are not. The result sounds rather like an antique piano finally succumbing to the ravages of woodworm, and collapsing. If you play the guitar (we don't) you will, no doubt, find many more musical uses for this effect than we could.

Switching between fuzz and struzz while playing produces an interesting sound. You might like to use a footswitch for this purpose.

Internal view of the effects unit

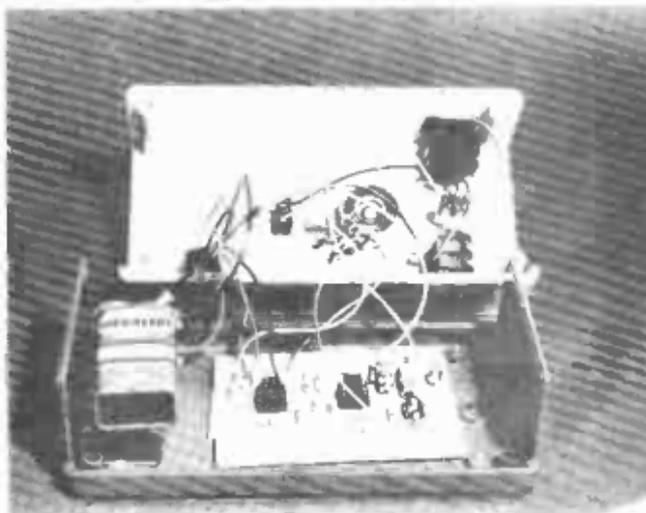

PARTS LIST

RESISTORS (All 5% 1/4W)

R1	680k
R2	5k8
R3	270R
R4, 6, 10, 11, 12	10k
R5	3k3
R7	100k
R8	33k
R9	820R
R13, 14	1k

POTENTIOMETERS

PV1	1MΩ
-----	-----

CAPACITORS

C1, 2	1µ0 electrolytic
C3	560p polystyrene

SEMICONDUCTORS

Q1	BC109
IC1	741
IC2	LF356
D1, 2	1N4148

SWITCHES

SW1	SPDT Footswitch
SW2	SPDT
SW3	DPDT

MISCELLANEOUS

Two 4-pin, mono-jack sockets
PCB
Vero-case to suit



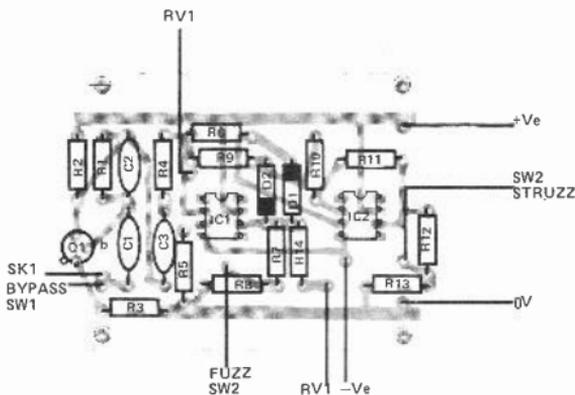


Fig. 1. (above) PCB component overlay

(Above right) Completed PCB

Fig. 2. (Below) Circuit diagram

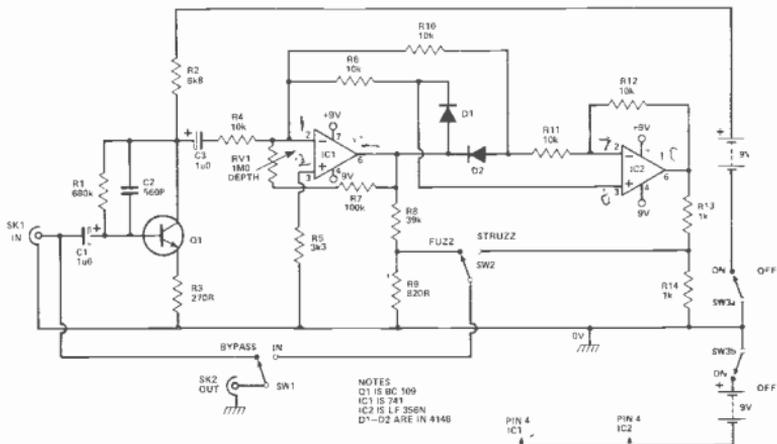

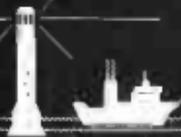

A board to plug into a NASCOM I with or without expansion which provides 84 line and black graphics characters plus reverse field graphics

Only slight modification is required to main board

Orders will be handled in strict rotation

A games program will be included
A kit is available from (mail order only)

BITS AND P.C.'s
8 Church View
Crugstone
WAKEFIELD
Tel: 261007

Cash with order £32.75 inc

LOOK!

NASCOM OWNERS

NASCOM I USERS HARDWARE

Keyboard Repeat (variable speed) **£3.50**

NoiseBox (make music) **£3.50**

SOFTWARE
Programmes for the NASCOM (can yours earn money?)

Sold on tape with documentation

S.A.E. for further details

READY-BUILT NASCOMS £190

COMPONENTS
S.A.E. & 20p, lots of goodies!

TWELECTRONICS
15 Damside St.
LANCASTER
LA1 1PD
Phone 0524-33596

SOFTY the all-in-one Development and Training Aid with Software-Firmware Copier and Programmer


- Execute programmes on TV screen by resident microprocessor. Programme halt and display contents of all internal registers at 50 break points
- Develop your firmware on TV screen with true memory mapped hex display with block shift, displacement, calculations, insertion and deletion, byte matching and other assembler functions
- Produce your firmware with high speed on board EPROM programmer, approx. 2 mins for 2708. Also handles 2704 and 2716
- Replaces monitor or debug programme
- Plus many other standard features including high speed cassette interface user programmable function keys zero insertion force socket

Universal Monitor which can be directly connected to ANY external microprocessor in system suitable for firmware development (written by resident micro and executed by external micro)

SOFTY is equivalent to Development Systems costing thousands of pounds. Yet **SOFTY** only costs you for kit and full instructions — **£99.95 + 8% VAT**, built and tested — **£145 + 8% VAT** Requires only power supply — full details on request

NASCOM 1 NOW AT THE NEW PRICE OF **£165** **FEATURES + 8% VAT**

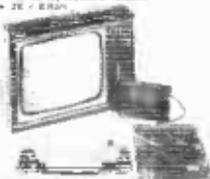- 16K or 32K monitor program in 8K chip
- Powerful Monitor 280 CHG
- 16 x 48 character display interface to the standard 84 TV
- TV display screen mapped for high speed access
- On board expansion to 2K x 8 EPROM
- On board expansion for 6000000 16K 0 Lines
- Memory may be expanded to full 90K (plus 4K saving on board)



SOFTWARE FEATURES

- 16 x 8 monitor pseudo-graphics
- 8 operating elements: single step, break, examine, modify, substitute, copy, break, stop, step, execute, tape, load, tape, dump
- Reference character addressing for hex, oct, dec, or a character through user programs
- Monitor and keyboard include a data, ASCII, walking, break, or the administration of control up to 2000 post cursor shift and memory address

Standard Features

- Uses the ultra powerful 5502 microprocessor
- 16K Monitor 280CHG in ROM
- Full feature BASIC built faster than currently available personal computers and all 5502 based business computers
- 4K video RAM on board expandable to 16K
- Full 11 key keyboard with upper/lower case and user programmability
- Keyboard only standard audio cassette interface for high reliability
- Full machine code monitor and I/O interface in ROM
- Three serial video displays, has 1K or dedicated memory (depends on user required) features upper/lower, lower case, graphics and opening characters for an effective screen resolution of up to 206 by 238 (double height) 17.5" with average density about 24 lines of 24 characters without expansion up to 30 x 30 characters

Extras

- 16K expansion board features 24K Macro RAM (with dual in-line memory interface, 10 x address for program and monitor) and 6502 8K ROM, computer module
- Assembler editor and assembler machine code monitor interface

Over 500 programs

Superboard II

Full 8K basic and 4K user RAM built and tested

£263.84

+8% VAT

Requires only 8 + 5V at 3 amps and an ASTEC Videomonitor or a TV and an ASTEC Modulator (see below)

Available during March 79

Order today with No Deposit or 0% finance to avoid shortage disappointments

ASTEC SWITCH MODE

- POWER SUPPLIES
- MONO UNIT PER 1
 - 5V 10A — £29.95
 - 5V 20A — £39.75
 - 5V 5A
 - 17V 1A — £78.90
 - 12V 1A
- full range of voltage and current



ASTEC 12" MONITOR UNCASED — £49.95 + VAT
CASED — £59.95 + VAT

Aslec Modulator UM1111 — £30
Selling — £2.50 + VAT
Aslec Modulator UM1211 — £25
Selling — £4.00 + VAT

visit our showroom and get hands on experience!
Full data on any of the above on request. All cashback costs inclusive
Please add 8% VAT unless specified Cheques and P.O.'s to

VIDEOTIME PRODUCTS
56 Queens Road, Basingstoke, Hants RG21 1RE
Tel: 0256 58417 Telex: 858747



OHIO SCIENTIFIC

Microcomputers from the world's largest
full-line manufacturer



The C2-4P Mini Floppy

20K RAM
Basic + Assembler
Personal, Games, Small
Business & Educational Disks
90K Mini Floppy Storage
Printer Interface
OS 65D V.30 Operating System

Economic expandable
systems with good disk
based software, available
now.

See your nearest
dealer for full price
list and catalogue



Abacus
Computers
Limited


62 New Cavendish Street
London W1 Tel: 01-580 8841

Mutek
Quarry Hill, Box Corsham
Wiltshire SN14 9HT
Tel: 0225-743289

Other systems available include the
C3 OEM with 32K RAM, 512K of disk storage and
BASIC as standard.

**Thames Personal
Computers**
13 Wilmot Way Camberley
Surrey Tel: 0276-27860
Linn Products
235 Drakemire Drive
Castlemilk Glasgow

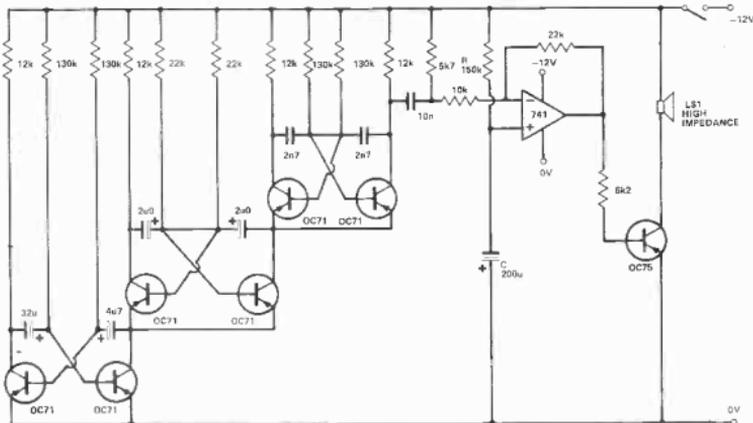G45 95Z Scotland
Tel: 041-634 3860
U Microcomputers
PO Box 24 Northwich
Cheshire CW8 1RS
Tel: 0606-75627




Gentle Clock Alarm

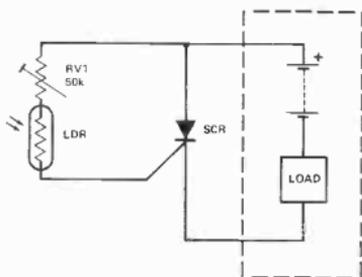I. Hill-Smith

RING! RING! BUZZ! This is DLT CLANG! PIP PIP!

There are gentler ways to wake up. This circuit provides an alarm which builds up from being inaudible to loud over about one minute. As a result you are always woken by the minimum volume required to wake you, a far more comfortable experience than the usual trauma. The three multivibrators in cascade provide a signal like the sound of a warbler telephone. As C slowly charges through R a larger fraction of the signal is amplified by the op amp producing a louder output.



X	.	00
#	3	01
4	4	02
5	5	03
1	1	04
	A	05
8	8	06
1	1	07
-	F	08
-	C	09
#	3	10
1	1	11
-	-	12
▼	A	13
gin	1	14
0	0	15
9	9	16
#	3	17
8	8	18
8	8	19
8	8	20
-	-	21
stop0		22

Calculator Radio Alarm

T. Corringham

This very simple circuit, used with a Sinclair Cambridge Programmable calculator, enables a transistor radio to be turned on after a predetermined time, (within the range of a few seconds to five months).

None of the components are critical, but the SCR should have a suf-

ficiently high voltage and current rating for the radio used.

If a transistor radio is used the SCR is connected in series with the battery, but if a cassette recorder/player is used it can be connected to the remote socket.

The LDR is placed above the left hand three digits of the display. RV1 is adjusted so that the circuit is triggered by '888' being displayed, but not by the background light only.

Using the program given, the time

in minutes of the required delay is put in and /RUN/ pressed to start the timing period.

To stop the program prematurely /+ /c /CE/ is pressed.

The calculator should be used with a mains adaptor.

The timing is accurate to within five minutes in eight hours.

If a buzzer or similar alarm is used the same circuit can be used to give an audible indication of the termination of long programs.

Tech-Tips is an ideas forum and is not aimed at the beginner. We regret we cannot answer queries on these items.

ETI is prepared to consider circuits or ideas submitted by readers for this page. All items used will be paid for. Drawings should be as clear as possible and the text should preferably be typed. Circuits must not be subject to copyright. Items for consideration should be sent to ETI, TECH-TIPS, Electronics Today International, 25-27 Oxford St., London W1R 1RF.


Keyboard/display sound converter

K. G. Reid

This circuit can be used in several modes: It can provide quantized feedback (a distinct improvement over the normal single 'bleep') from the key actions made on a calculator-type keyboard. It can be used to give a 'sound' translation of a digital display or completely replace the display when sound would be a better communication medium.

The keyboard or display information (a maximum of 16 bits with one 16-line 74150 multiplexer) is translated into a series of 16 high or low frequency tone pulses, corresponding to the high or low logic state of the 16 bits.

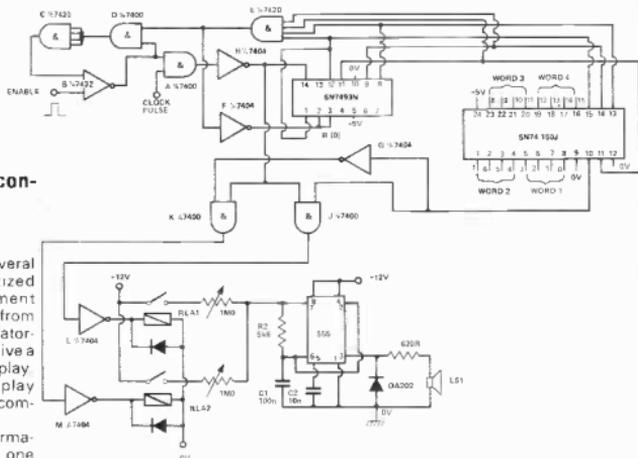The circuit illustrated was used in conjunction with a digital multimeter, requiring three 4-bit words for the digits and three additional bits for over-range, negative and decimal point. Thus, 15 lines only were required, the 16th being used for resetting.




The 15 bits are latched on to the inputs of the 74150 multiplexer. Presentation of the enable pulse results in a logic '1' appearing at the output of gate B, allowing clock pulses to pass via gates A and H to the 7493 counter. Gates B, E, D and C form a latch which remains 'set' until all 15 bits have been sampled. As each bit is sampled, the inverse state appears at the multiplexer output, opening gate


J or K and thus operating one of the two reed relays. As a count of 1111 appears from the counter, the output of F drops low, resetting the latch and counter. The operation of either relay results in a tone appearing at the loudspeaker (or earpiece), the tone frequencies being set (1.2 kHz maximum) by the 1 megohm pots. The tone pulse length is governed by the clock rate.

Digital Pulse Compressor

N. C. Hall

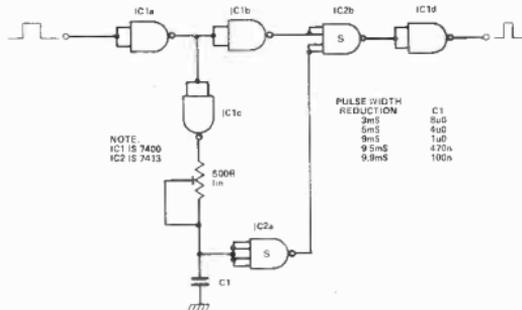Whilst constructing a digital frequency meter the author found it necessary to be able to accurately trim the width of a gate pulse. The circuit shown uses only two ICs and can reduce the width of a pulse applied at its input by up to a few milliseconds. The table shows the reduction achieved by using different values of C1.



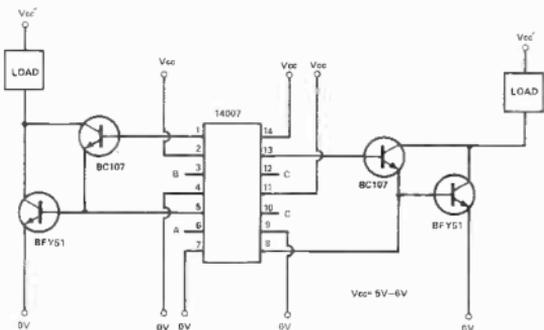

Darlington Drivers for a few pence

C. J. Ramey


This circuit offers a very efficient way of driving a pair of transistors in Darlington configuration from CMOS. The circuit in Fig 1 shows how two loads of up to 1A may be driven from a single 14007 chip with no external resistors. Using a 2N3055 in place of the BFY51 will enable loads of up to 3A to be driven at voltages limited only by the V_{ce0} of the transistors (V_{cc}).

Fig 2 shows the internal circuit of one section of the 14007. A high on

pin 6 switches the lower CMOS transistor on, holding Q2 off and sinking the leakage current of Q1. A low on pin 6 drives Q1 and switches the lower CMOS transistor off and the upper CMOS transistor on.

The result is fast switch off at low cost and efficient switch on.

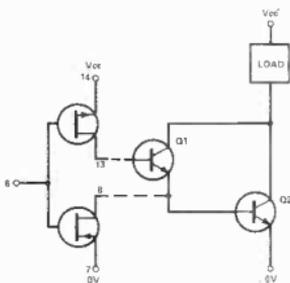
A bonus is the inverter between pins 10 and 12. Note V_{cc} should be 5-6V to prevent excessive current being drawn from the CMOS chip.



Precision Rectifying with the LM3900

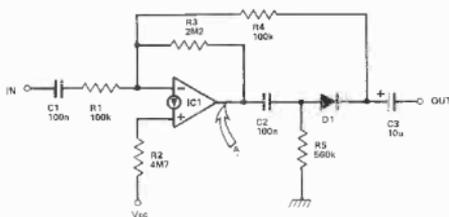A. Winsor

The LM3900 is different from most op-amps in that it is current differencing and operates from a single supply rail, which means that the inputs bias at one base-emitter voltage above ground. Hence standard techniques are not applicable as the diode would always be forward-biased. Two feedback paths are therefore provided:— R3 for DC stability, and R4 for the AC signal after C2 and R5 have filtered out the DC bias. When $R2 = 2 \times R3$ point A will be at $V_{cc}/2$, allowing the diode to be reversed at will. For large positive input returned to ground input impedance equals $R1$, and voltage gain equals $-R4/R1$ since R4 is



NOTE
IC1 IS LM3900
D1 IS ANY GENERAL PURPOSE DIODE

made very much smaller than R3. C1 and C3 are DC blocking capacitors and determine the low frequency roll-off. Component values quoted are those used on the prototype and may be altered to suit individual require-

ments. This circuit has obvious potential, especially in portable equipment where the 4 amps in one package and single supply rail yield a more compact, more convenient unit.

Here's why you should buy an I.C.E. instead of just any multimeter

- * Best Value for money
- * Used by professional engineers, D I Y enthusiasts, hobbyists, service engineers
- * World-wide proven reliability
- * Low servicing costs
- * 20K/volt sensitivity and high accuracy
- * Large mirror scale meter
- * Fully protected against overload
- * Large range of inexpensive accessories.
- * 12 month warranty, backed by a full after sales service at E B Sole U K Distributors

Prices from £16.60 —
£32.00 + VAT



I.C.E.

ELECTRONIC BROKERS LIMITED

49-53 Pancras Road, London NW1 2QB
Tel: 01-837 7781 Telex: 296694

Please send me full colour leaflet and prices on whole I.C.E. range including accessories

Name _____

Address _____

AT LAST!

The new Strathand Security Division catalogue is here! Full details of alarm circuit principals and practice

How the professionals keep burglars at bay

Including diagrams of how to wire up doors windows etc

Full price list and order form included

£1.00 inc P&P
(Refunded on orders over £10)

Telephone your Access/Barclaycard number for fast delivery

STRATHAND SECURITY

44 St Andrew's Square

Glasgow, G1

Tel. 041-552 6731/2

Callers Welcome



OSCILLOSCOPE

WITH FULL
INSTRUCTION MANUAL


FEATURES

- Response DC to 5MHz
- Sensitivity 100MV to 50V division
- Fully calibrated time base circuit and automatic blanking
- 100% solid state
- Utilising 13 transistors 1 P&T and 1 speciality time base module
- Stabilised power supplies and active sync circuits
- Rugged construction together with portability
- Inexpensive — excellent value and performance

FULL INSTRUCTION & OPERATING MANUAL

SPECIFICATIONS

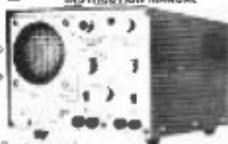Time Control 100ms to 100µs
Sweep 100ms to 10µs
Sensitivity 100mV to 50V
Input Impedance 1MΩ to 10kΩ
Input Voltage Max 100V AC
Power 100W
Dimensions 100mm x 100mm x 100mm
Weight 1kg



FROM STOCK
£83.25
Add VAT £8.66
Current price £91.91
EXPORT ADD £5.00

Also at 248 Tottenham Court Road, London, W 1
301 Edgware Road, London, W 2

Henry's
RADIO

All mail to Henry's Radio
404 Edgware Rd London W2
PHONE 01-723 1005 ENGLAND


PCB FOIL PATTERNS

GATHERED HERE are all the PCBs for this month's projects. From now on the boards will be grouped together like this in order to facilitate their use by those readers wishing to produce their own PCBs from these patterns.



All are shown foil side up, and full size. Companies wishing to produce these for sale as ready made PCBs should note that where the board carries a copyright

symbol, the designer retains that copyright to himself or his company, and that particular board may *not* be produced on a commercial basis.

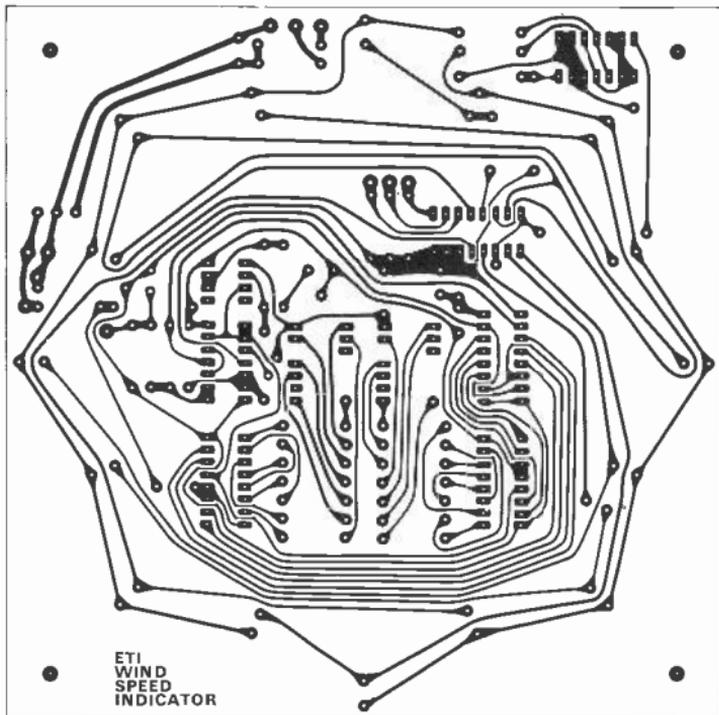These pages form the basis of our ETIPRINT sheets which are etch resistant transfers of the foil patterns designed to simplify one-off PCB production. See the ad on page 49 for further details.



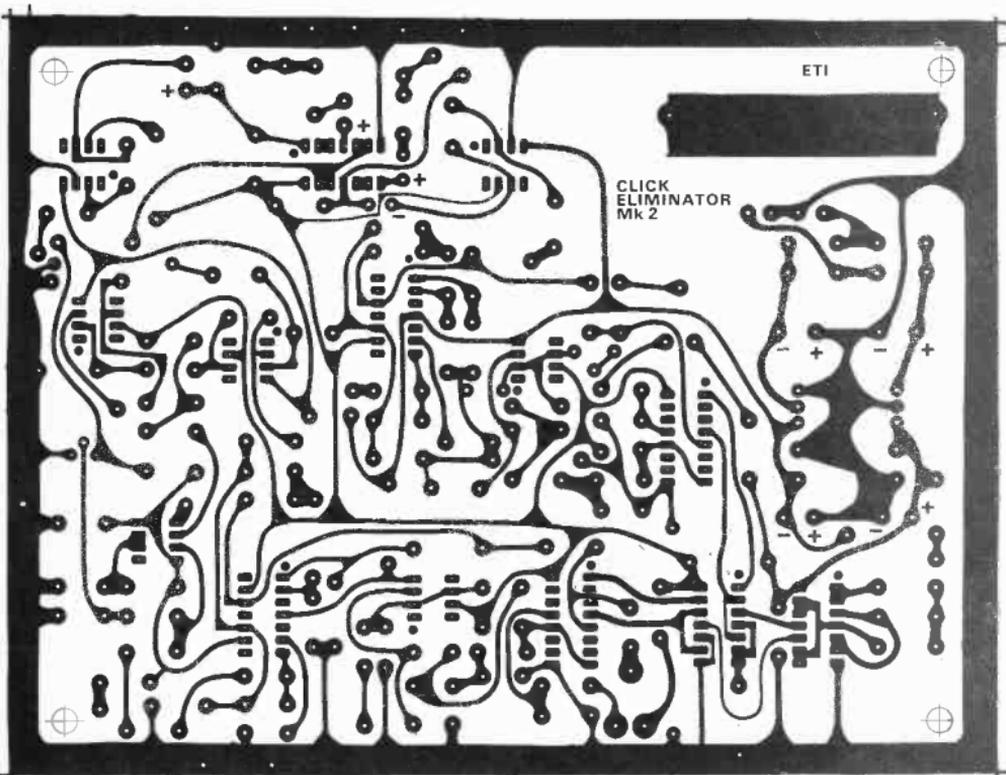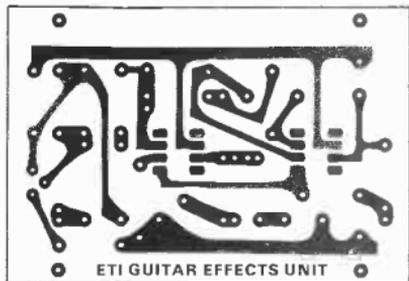Below left: Wind Speed Indicator PCB
 Below right: Click Eliminator Mk 2 board
 Right: Struzz effects unit
 All are shown full size and will form the basis of ETIPRINT
 sheet 023 which will be available shortly



INTERESTED IN HOME COMPUTING?

Start now and don't get left behind. **THE NASCOM 1** is here. Ex-stock with full technical services.

Plus the opportunity to join the fastest moving club of personal computer users enabling you to get the most out of your computer. You can **OBTAIN** and **EXCHANGE** programs and other software - many now available.

The Powerful Z80 Microprocessor
Professional Keyboard
1 Kbyte Monitor an EPROM
2 Kbyte RAM (expandable)
Audio Cassette interface
Plugs into your domestic TV
Easy construction from straightforward instructions - no drilling or special tools
Just need soldering retainer.



SAVE £60

Only **£199.00** + 8% VAT (includes p & p + insur. price)

Manuals separately: **2.95**
Z80 Programming Manual **6.90**
Z80 Technical Manual **2.95**
PIO Technical Manual **2.95**

NEW LOW PRICE
£165

Power supply suitable for NASCOM 1 **19.90**

NASCOM ADONS - Nascom improved monitor & Bug (2K) featuring - "Four times tape speed" "Direct to entry without ASCII" "Extended keyboard facility" "Additional useful subroutines" **£23.00**

Nascom Vero Case **£22.50** Nascom Music Box Kit **£9.90** (write your own tunes and play them on your Nascom)

Nascom Joy Stick Kit **£14.90** Complete with full documentation

GRAPHICS ADD ON BOARD £9.90

Complete kit to upgrade your NASCOM for graphics capability includes full documentation and demonstration program

NASCOM IMMEDIATE EXPANSION \$100 from COMP - strongly recommended

The only available \$100 motherboard kit (fully buffered) that plugs directly into your Nascom. Designed for the insertion of S100 boards (e.g. Static RAM, EPROM and discs etc.)

S100 Motherboard/Buffer **£47.50** } Motherboard comes complete with 2K Tiny Basic On cassette
(Complete kit + documentation)
Suitable 8K Static RAM Memory **£52.50** £110 (fully assembled tested and guaranteed)

ATTENTION! SAVE £90

TRS 80 & APPLE II USERS **SAVE £90** *Save £90 for only a screen on per is required*

16K UP GRADE KIT HALF NORMAL PRICE **£99** + VAT **LIFETIME GUARANTEE**

SHORT C12 CASSETTES 10 for £4.00 FOR COMPUTER PROGRAMMES

TV GAME BARGAINS TELEPLAY PROGRAMMAGE
Fully Assembled Reduced to **£24.90** + VAT **SAVE £10**

ATARI VIDEO SYSTEM

REDUCED TO **£138** + VAT

SAVE £30

PET COSTS LESS AT COMP and it's a pedigree

The No. 1 Personal Computer in the U.K.
Affordable **£499** SAVE **£50**
For the first time user and the professional check out the PET the world's most popular personal computer **8K**



OHIO SUPERBOARD II NEW FIRST IN U.K. - ON DEMO

For electronic buffs. Fully assembled and tested. Requires - 5V at 3 Amps and a video monitor or TV with RF converter to be up and running

STANDARD FEATURES
Uses the ultra powerful 6502 microprocessor
8K Microport BASIC in ROM
Full feature BASIC runs faster than current available personal computers and all 8080 based business computers
4K Static RAM on board expandable to 8K
Full 55 keyboard with upper/lower case and user programmability
Kansas City standard audio cassette interface for high reliability
Full machine code monitor and IO utilities - ROM

Direct access video display has 1K of dedicated memory (besides 4K user memory) features upper case, lower case, graphics and gaming characters for an effective screen resolution of up to 256 by 256 pixels. Normal TV's with overcan display about 24 rows of 24 characters - without overcan up to 30 x 30 characters

EXTRAS
Available expand board features 24K static RAM (additional dual in line floppy interface port adapter for printer and modem and a CDS 48 line expansion interface)
Assembled for and extended machine code monitor available
~~£280.00~~ **£249.00** + VAT *Save £20 to reserve one - call to order on delivery*

MODULATORS UHF Channel 36

Standard 6 meg band width **£2.25**
High Quality 8 meg band width **£4.90**

BULK PURCHASE VDU MONITORS

£99
£69
+ VAT



CASED AND GUARANTEED 12"

TRS 80 SOFTWARE

100 MIXED PROGRAMMES **NEW** **£49.00**
on cassette

KEY BOARD

756 GEORGE RISK

Brand new professional ASCII keyboards (USA)

Full technical details included, RRP **£60.00**

Only **£49.90**

- 8% VAT

Ready built tested and guaranteed




All prices include VAT except where shown. Orders over £5 post and packing free otherwise add 20p. Please make cheques and postal orders payable to COMP or phone your order quoting BARCLAYCARD or ACCESS number

OPEN - 10am to 7pm - Monday to Saturday
CONTINUOUS DEMONSTRATIONS





SORCERER™ COMPUTER SPEAKS YOUR LANGUAGE

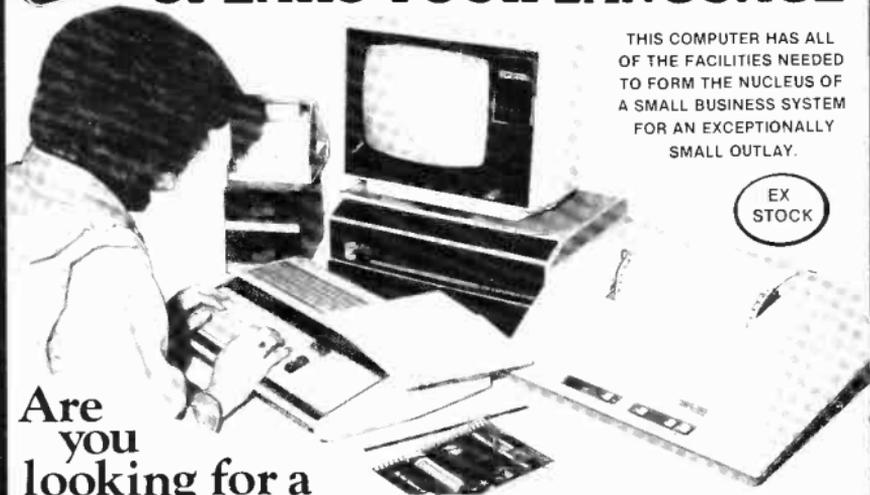

THIS COMPUTER HAS ALL OF THE FACILITIES NEEDED TO FORM THE NUCLEUS OF A SMALL BUSINESS SYSTEM FOR AN EXCEPTIONALLY SMALL OUTLAY.

EX STOCK

SEND FOR OUR SPRING '79 CATALOGUE - 0-60p

Are you looking for a PERSONAL or SMALL BUSINESS Computer? Look at these features for only **£850** - VAT

- 256 Character Graphics Set includes 128 that you can define
- Z80 Based computer
- Power-on 4K Monitor
- Excellent bit-mapped graphics (512 x 240 point resolution)
- Full 79 key dp keyboard including 16 key numeric pad (Full ASCII)
- Plug in ROM facility (e.g. 8K BASIC (supplied), Assembler/Editor, word processing etc.) so that you can change your language or utility by simply plugging in the one you want
- Serial I/O ports for cassette/RS232 etc (300 or 1200 Baud)
- Parallel I/O port for printer (Centronics Compatible)
- Z80 bus available at the rear for connection to the optional 6 slot S100 expansion box (e.g. S100 Floppy disk drives, graphics boards, extra memory etc.)

EXIDY SORCERER 32K RAM computer	£850
(Add £9 for UHF output) 16K RAM computer	£751
12" Video monitor	£69
S100 expansion box (includes 6 Slot Motherboard and power supply)	£210

DISK SYSTEM as shown
MICROPOLIS S100 disks — 315 K bytes per drive
 Drive 1 includes S100 controller
 Micropolis M DOS and BASIC software) **£649**
 Additional 315 K bytes drives (up to 4 per controller) **£349**
 Cables and regulators for 2 disk system **£41**

PRINTER as shown
ANADEX DP8000
 80 columns 112 char/sec 5 x 7 dot matrix head
 Connects to parallel or serial ports **£575**

ADDITIONAL SOFTWARE FOR SORCERER PLUS DISK SYSTEM

CP/M operating system	£145
CP/M with C BASIC (Compiler/Interpreter)	£235
FORTRAN 80	£350
COBOL 80	£490

MICROPOLIS BASIC PACKAGES FROM COMPUMAX	STOCK CONTROL (INVENTORY): PAYROLL ACCOUNTS RECEIVABLE LEDGER PERSONNEL	£99 each
---	---	-----------------

COMP COMPUTER COMPONENTS

For technical and sales literature send SAE to:
 COMP COMPUTER COMPONENTS (Exidy UK Sales),
 Freepost, 14 Station Road, New Barnet, Herts
 Tel: 01 441 2922 (Sales) 01 449 6596 Telex: 298755

TAKE ADVANTAGE OF OUR
 SHORT DELIVERY TIME

All prices exclusive of VAT

(PART OF THE COMPSHO LTD GROUP)



A quality range of British made electrical accessories plus a free to book. Do your own home electrical work with complete confidence. See our pages 129 to 134



This superorganiser - build the best working section for just over £100. Full specifications in our catalogue



A range of highly attractive LEDs is described in our catalogue. Our prices are unbeatable too!



Mobile amateur radio. TV and FM aerials, price lists, accessories are described in our catalogue



A pulse width train controller for smooth slow running plus inertia braking and acceleration. Full construction details in our catalogue




A wide range of items in common as in our catalogue. Our catalogue has all the details



ribbon cassette tape for organs. Two excellent bass guitar stops for guitarists complement. See 74 column in our catalogue



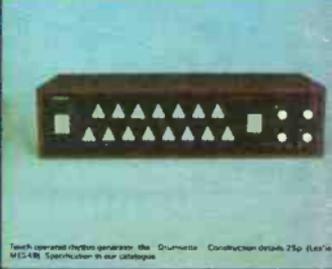The 3800 synthesizer - build it yourself at a fraction of the cost of one ready made with the specification. Full details in our catalogue



Bench operated crystal generator. Drumstick Construction details 75p (plus £1.50 VAT). Specifications in our catalogue

MAPLIN

ELECTRONIC SUPPLIES LTD
 All mail to:-
 P.O. Box 3, Rayleigh, Essex SS6 8LR.
 Telephone: Southend (0702) 554155.
 Shop 284 London Road,
 Westcliff-on-Sea, Essex.
 (Closed on Monday).
 Telephone: Southend (0702) 554155.



A superb technician lookalike in your home! All you need is our catalogue. Post the coupon now!



An attractive mains alarm clock with radio receiving section and battery back up. Components for with case only £12.95 (incl. VAT) & plus M41023 module only £8.95 (incl. VAT)



A massive new catalogue from Maplin that's more pages and better than before if you ever buy electronic components. This is the one catalog that you must not be without.

Over 280 pages - some in full colour - is a comprehensive guide to electronic components with hundreds of photographs and illustrations and complete data pages of invaluable data.

Our bi-monthly newsletters contain guaranteed prices, special offers and all the latest news from Maplin.



A 62-key ASCII keyboard with 625-line TV interface. 4-page memory and microprocessor interface. Details in our catalogue

Post this coupon now for your copy of our 1979-80 catalogue price 75p.

Please send me a copy of your 280 page catalogue as soon as it is published (8th Jan 1979). I enclose 75p but understand that if I am not completely satisfied I may return the catalogue to you within 14 days and have my 75p refunded immediately if you live outside U.K. send £1 or ten International Reply Coupons

NAME _____

ADDRESS _____
