

# electronics today

JANUARY 1978

INTERNATIONAL

58p


Take out the scratches with our



**Digital Tacho**  
**Born in Check**  
**Power Supplies**  
**Loudspeaker Principles**

**Inside:**  
**computing**  
**today no3**

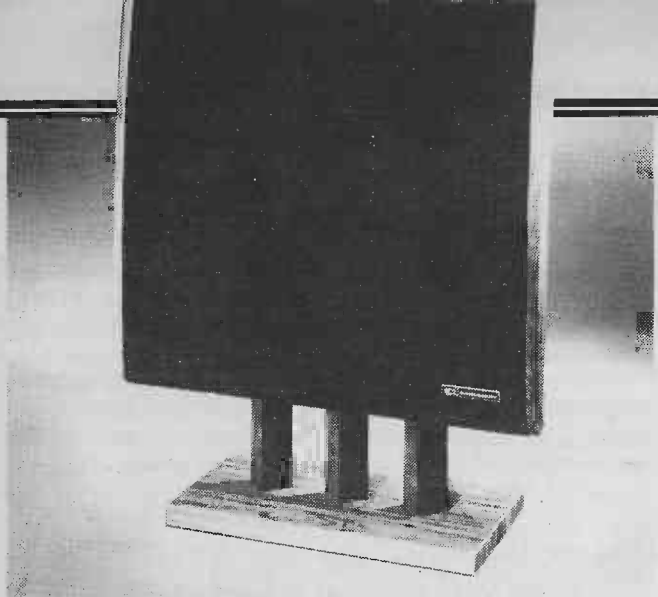... NEWS ... PROJECTS ... MICROPROCESSORS ... AUDIO ...



**The DQ10.** This design makes use of what the makers term a 'phased array'. This means that the driver units are staggered so that their effective radiator 'points' are equi-distant from the listener which eliminates the time delay distortion (phase linear?) flat baffle designs are prone to. In addition each driver is mounted on its own optimum sized baffle to minimise diffraction problems.

## Transmission Lines

This is another method of 'losing' the rear radiation of a drive unit, or making it think it is working into an infinitely long column. This is achieved by having a maze of woodwork inside the enclosure which is filled with graduated damping material. In this way total column length can be far greater than enclosure dimensions.


If the far end of the column is open then help is afforded to the bass performance in much the same way as bass reflex cabinets.

The design is usually for almost total absorption of the rear wave — and this leads to a gradual and smooth fall off in bass response due to the almost constant velocity working conditions for the cone.

Conversely to both acoustic suspension and basis reflex loading methods, transmission line methods lower the bass resonance of the drive units and hence enhance LF performance.

IMF have championed this technique for long time passing now, and as exemplified in their products transmission line bass possesses a 'solid' quantity totally different to that from the other methods. It is more extended and more realistic. Used in a large enough room there is no better way to replay the lower registers.

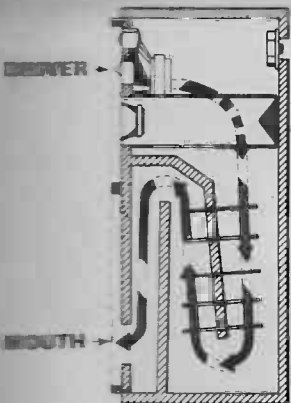Oh for a successful combination of transmission line bass and electrostatic HF!




The basic principle behind the transmission line speaker enclosure. The air from the rear of the cone gets 'lost' down the line.

**KEFs 105 linear phase design.** The upper two enclosures are rotatable to aid stereo imagery. Note the rounded edges to prevent re-radiation and the staggered drivers with respect to the listener.
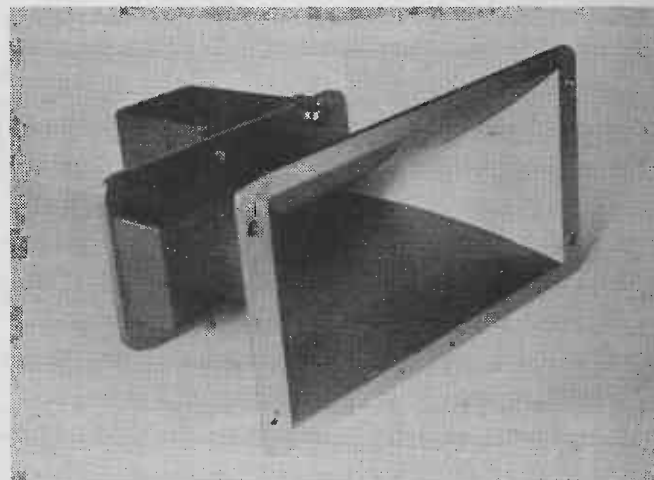
## Horn Loading

A method of designing to considerably reduce required driver excursion for a given acoustic output. The driving element is coupled to its air load by a gradually 'flaring' throat — usually exponential in cross section.


The horn converts the high pressure, low velocity sound energy present in the region of the driver into low pressure high velocity waves for propagation. The advantages of this type of loading are good damping of the driver, low distortion but a limited frequency response.



**The Decca London ribbon unit, loaded by a catenoidal horn.** The flare can be clearly seen in this photo leading down to the ribbon itself somewhere in that block at the back!

To design a single horn to cover the entire audio spectrum is a confused exercise, and one yielding impractical results for domestic use, since an exponential horn to reproduce 30 Hz has a mouth of 1.5m diameter and is some 4m long! Folding the horn back and forth within an enclosure can reduce dimensions, and the American firm Klipsch market units which employ the room walls as extensions of the horn to reach lower frequencies. Usually though, the system is used to load MF and HF units within a system.

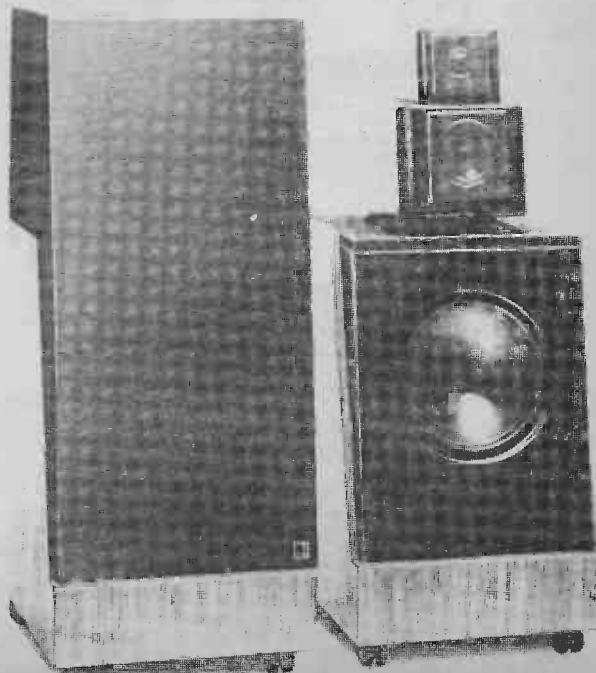Advantages of this principle are phenomenal efficiency  $\approx 10\%$  compared with  $1\%$  for bass reflex and  $0.1\%$  for transmission lines, and an attack unmatched by any other cone driver recipies. ▶





# ELECTROSTATIC


As we have seen the moving coil design suffers because the cone area is unevenly driven by the electrical music signal. The electrostatic principle, developed by both David Tombs and Peter Walker (of the Acoustical Manufacturing Company) is an attempt to produce a unit in which the entire surface of the unit is driven by the input signal.

At its most basic the design consists of two plates as shown in the diagram. The moveable plate is made to have as low a mass as possible and is so suspended that it cannot touch the fixed plate at any point in its travel. The fixed plate will usually in fact take the form of a metal 'mesh'. A high polarising voltage  $\approx 5\text{kV}$  is applied between the plates, and the audio signal superimposed on this.

An electrostatic force—such as that which holds dust on to LPs and LPs onto turntables—is thus generated between the plates and the moveable one vibrates in sympathy with variation in the input signal.

A refinement of this is the push-pull system where the moving plate is situated between two fixed meshes as shown in the drawing. The polarising voltage is DC in nature, from a very high impedance source, and is of the order of  $5\text{kV}$  once again.

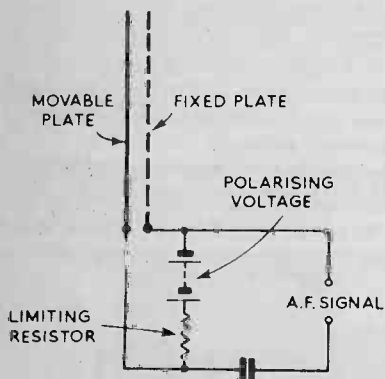The outer plates (meshes) are fed from a step-up transformer connected to load the incoming signal. This applies a high voltage electrical AC signal to these plates (the music signal) and causes the center plate to move in sympathy with this. Distortion is greatly reduced using this push-pull arrangement and can equal 0.5% in a good design.



**Scheme of operation for electrostatic loudspeakers. On the top we have the basic single ended design, and below that the commercially employed, much-improved push-pull scheme as employed by Quad and Koss amongst others.**

This system first appeared on the market many many years ago in the form of the Quad electrostatic system—which remains largely unsurpassed for lack of colouration and mid-range clarity.

The advantage of driving the plate evenly over its whole area show up as a linear frequency response—no rippling or 'break-up'—very low distortion and a good transient performance due to low driver mass.

However this system does have inherent drawbacks. Consider the Quad system as an example. It is noted for its mid-range clarity and its high frequency accuracy—but also for its lack of extreme bass and its beaming of top end signals—poor vertical dispersion.

The reason for this is its physical size. Since the push-pull radiator is by nature a dipole radiator—sound emitted both front and back, some cancellation at frequencies whose wavelength exceeds the plate dimension is inevitable.

The Quad is also very room sensitive for this same reason. Rear radiation can be dumped, but not without acoustically loading the plate—an undesirable excursion into non-linearity. At high frequencies there is low energy in the wave to absorb, and so this is easier to affect without adverse consequences on the drive plate.



KLH made a brave attempt to reach the theoretical size of plate for good bass response with their superb KLH9 full range units. These are almost exactly door sized—and you need **two** per channel! And they cost £2000 a pair. And they are probably unbeatable by any speaker on the market for sheer accuracy and delicacy. Their size endows them with a hefty bass punch too. Units to sell your soul for. (Anyone listening down there?)

## Loading Problems

Another less serious drawback is that transformer into which the electrical signal is fed. This presents an awkward load to the amplifier, and can produce some nasty effects from transistor amps.

Modern designs however—Lecson, Quad and the rest, can cope perfectly and experience no traumas when presented with the wickedly reactive termination characteristic of electrostatic speakers.

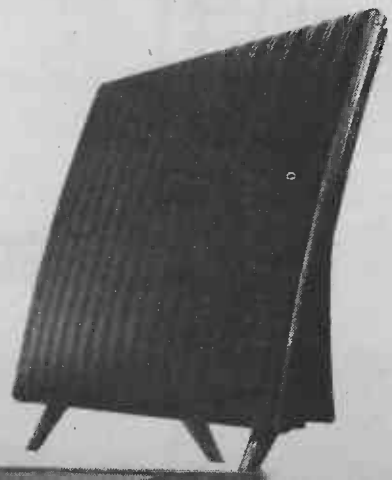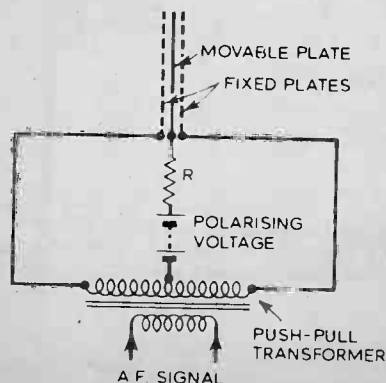Many attempts have been made to marry together electrostatic mid-high drivers with cone bass units. B&W DM70 was perhaps the first (and the best!) but not have been entirely successful. Perhaps its simply that the superior distortion and colouration properties of the electrostatics will always show up the bass units!



## ISODYNAMIC


With the release of the Stathearn 21000 speakers, and the new Wharfedale series incorporating Isodynamic tweeters, this approach is gaining ground. It certainly has a lot of promise, which we shall undoubtedly see exploited as time goes on.

The principle was pioneered by Wharfedale with their Isodynamic headphones some six years ago or so. It is really an attempt to gain the advantages of the electrostatic system, without the need for high voltages and attendant drawbacks.



A drive unit built to this principle consists of a thin sheet of mylar, or some such material, with a conductive track bonded onto it in a pattern which covers the surface in as symmetrical manner as possible. This conductor acts as the voice coil of the speaker, and when an electrical signal is passed through it it responds to nearby magnets by moving the diaphragm in sympathy.

Once again colouration is low, and driver mass small—but also once again to obtain bass means large areas, and conductors capable of handling large currents. Stathearns units are above 500Hz operators only and are transformer coupled to the input. Wharfedale employ their invention in high frequency units only.

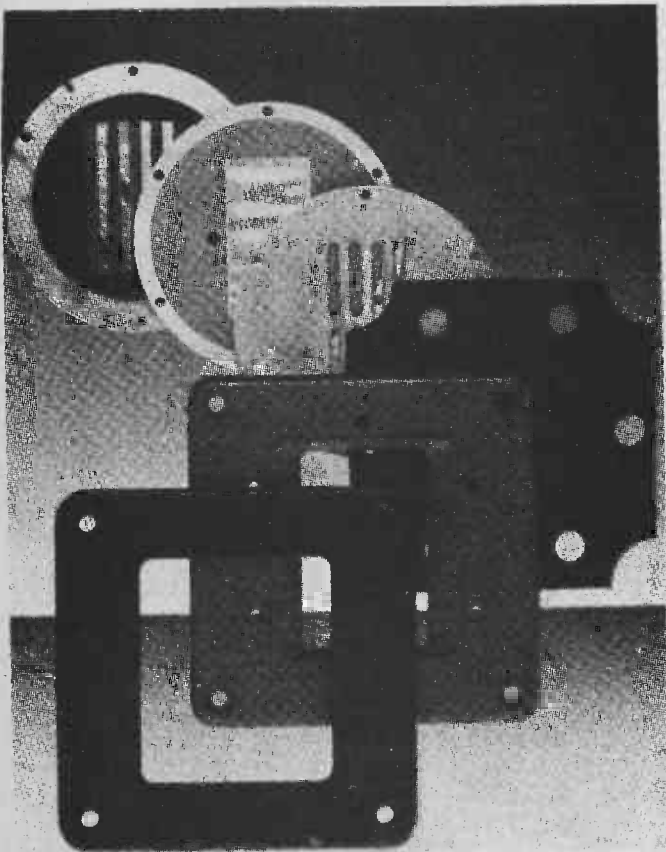
A pity—but one we might see rectified sometime in the future.



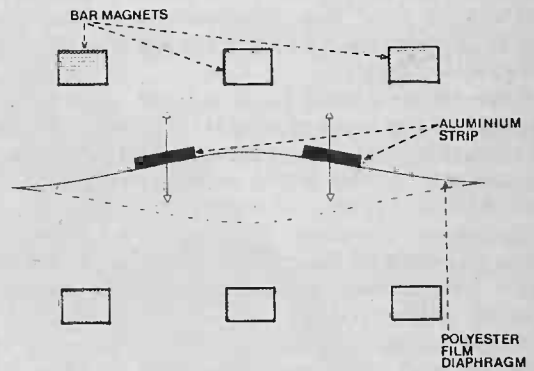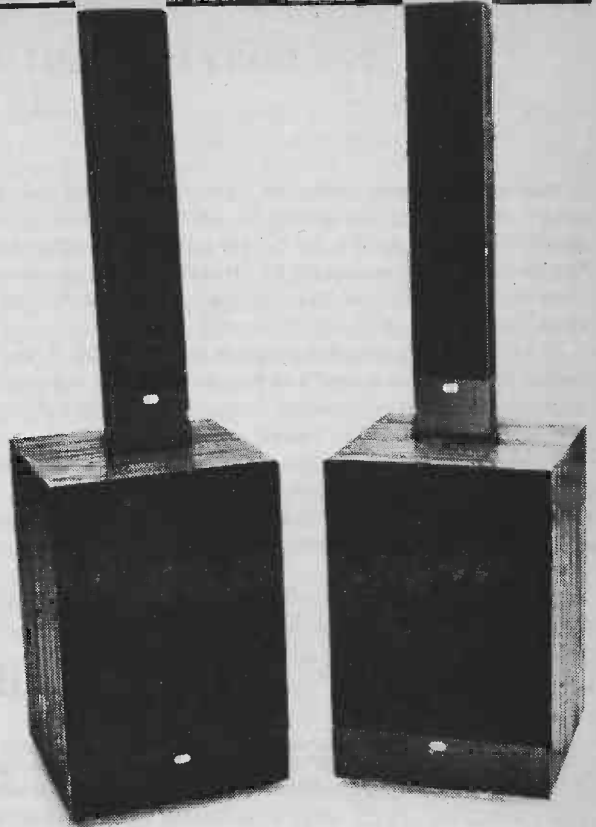Exploded view of the Wharfedale Isodynamic tweeter. The driver plane — second from the rear — uses a material 25 microns thick with an etched aluminium circuit.



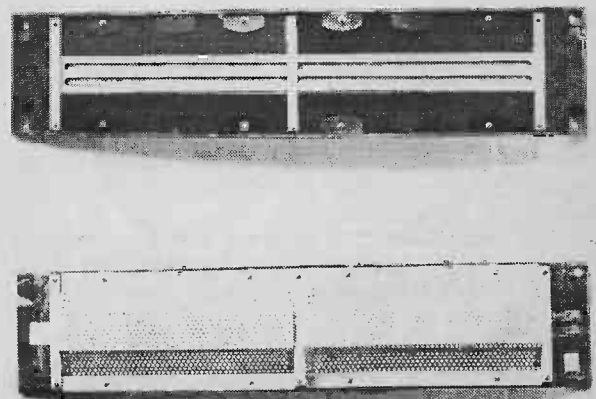The 21000 from all angles. At the top we have the full system. Below that the diagram shows the operating principle of the SLC1. The polyester diaphragm acts as the speaker cone. Below this caption two internal views of the unit. The radiating areas can be seen in the top diagram, and the lower rear view illustrates the damping material to control rear radiation.



## RIBBON


If we take the voice coil of moving coil speakers, and make this the active element, instead of the cone, we would do away with a lot of the causes of colouration in the process. Mass would be much smaller, break-up or rippling would be greatly reduced, if not eliminated and thus transient handling improved.

The ribbon loudspeaker does exactly this. A very thin metal 'ribbon' is suspended between the magnet pole faces and the signal passed through it. It will vibrate with the signal, and thus produce the sound output.

Acoustic output is low, and horn loading is usually employed to alleviate this problem.

Once again obtaining bass is a major problem, and moving coil units will take over from the ribbon as the frequency decreases.

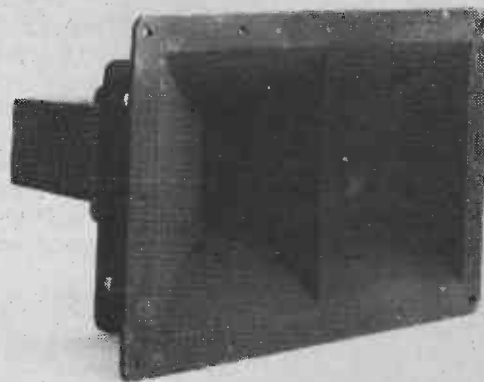Decca market an excellent example of this principle, which operates above 2.5kHz.



Decca's ribbon loudspeaker. This features a ribbon element one tenth the thickness of human hair, and is horn loaded to increase efficiency. An 'acoustic lens' can also be fitted to aid sound dispersion.

## PIEZO-ELECTRIC

In the July 1976 edition of ETI we reviewed the Motorola KN 6006A, the first piezo-electric unit to be released commercially. Since that time many commercial loudspeaker enclosures have employed piezo-electric tweeters for their total insensitivity to crossover networks, phenomenal transient response and clean subjective sound quality.

Piezo-electrics have been around in hi-fi for a long time now in the guise of crystal/ceramic cartridges. The principle of operation is based upon the fact that stress a piezo-electric crystal and a voltage proportional to the applied force is produced across its ends.

Conversely therefore if we apply a varying voltage across the ends of the crystal, mechanical deformation occurs, sympathetic to that voltage. No magnets are required, and no coil is used.

In the Motorola design two thin slices of ceramic material—lead zirconite-lead titanate in case it makes your life the fuller for knowing are epoxied onto a brass separator, and nickel electrodes deposited on to facilitate connection. In order that the discs respond correctly to the input, they are polarised in opposite senses, so that on application of a common signal one disc expands and the other contracts—acting in the same direction therefore on the air load.

### Pros . . . . .


Since the impedance curve for the unit shows a steep rise in value with falling frequency, the unit does not need a crossover to reject low frequencies.

A perfect tweeter.

Since there is no voice coil or cone the driver mass is significantly lower than an equivalent conventional speaker.

Being composed of a ceramic material heat dissipation is less of a problem also, and the Motorola can stand 35V RMS for protracted periods with no signs of distress.

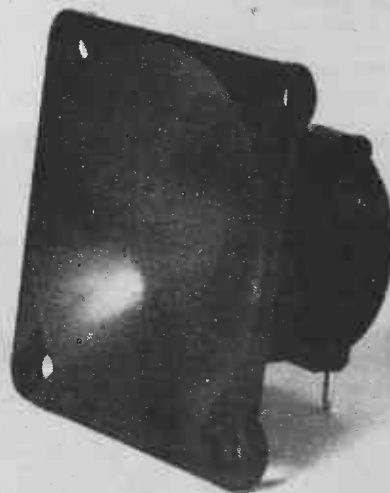Due to the nature of its impedance, it is difficult to compare efficiency with normal units, suffice it to say that 4V RMS produces 105dB at 18ins distance, and that this can be considered efficient!



Motorola's KN 6006 piezo-electric high frequency driver. The actual driver is the small section at the rear, and the horn is to increase acoustic efficiency.

### . . . . . And Cons.

Some amplifiers may not like the load any more than electrostatic units, but since these things are normally used with a good deal of attenuation and response shaping circuitry between them and the valued output stages this should not be too great a problem.

Subjectively these units have always sounded a little 'hard' to me, and never as smooth as a good dome unit like the Isophon or Celestion 2000 designs. Still personal taste and all that . . . . .

Once again acoustic efficiency is low, and horn loading is employed.

### MOTIONAL FEEDBACK

Although this perhaps only a modification of earlier systems, the performance gains at LF are such that it warrants a closer look.

Motional feedback is a form of feedback control of the driver cone in moving coil systems. The power amplifier are mounted within the enclosure, a separate amp for each drive unit, and so signal feed is from a preamplifier. The system is marketed by Philips.

The main advantage of this extra complication lies at the bottom end of the range where the output for given enclosure volume is considerably enhanced. The complication lies in the sensor fitted onto the driver.

This is mounted on a small PCB and is a ceramic acceleration sensor. This generates a signal proportional to the actual driver output, and this is compared electronically to the incoming audio. Correction is applied to remove any errors present. Cross over is carried out at small signal level, and active filters with all their inherent superiority are applied.


There is a 'slave' output which allows the enclosures to be stacked up to increase power handling and effective output.

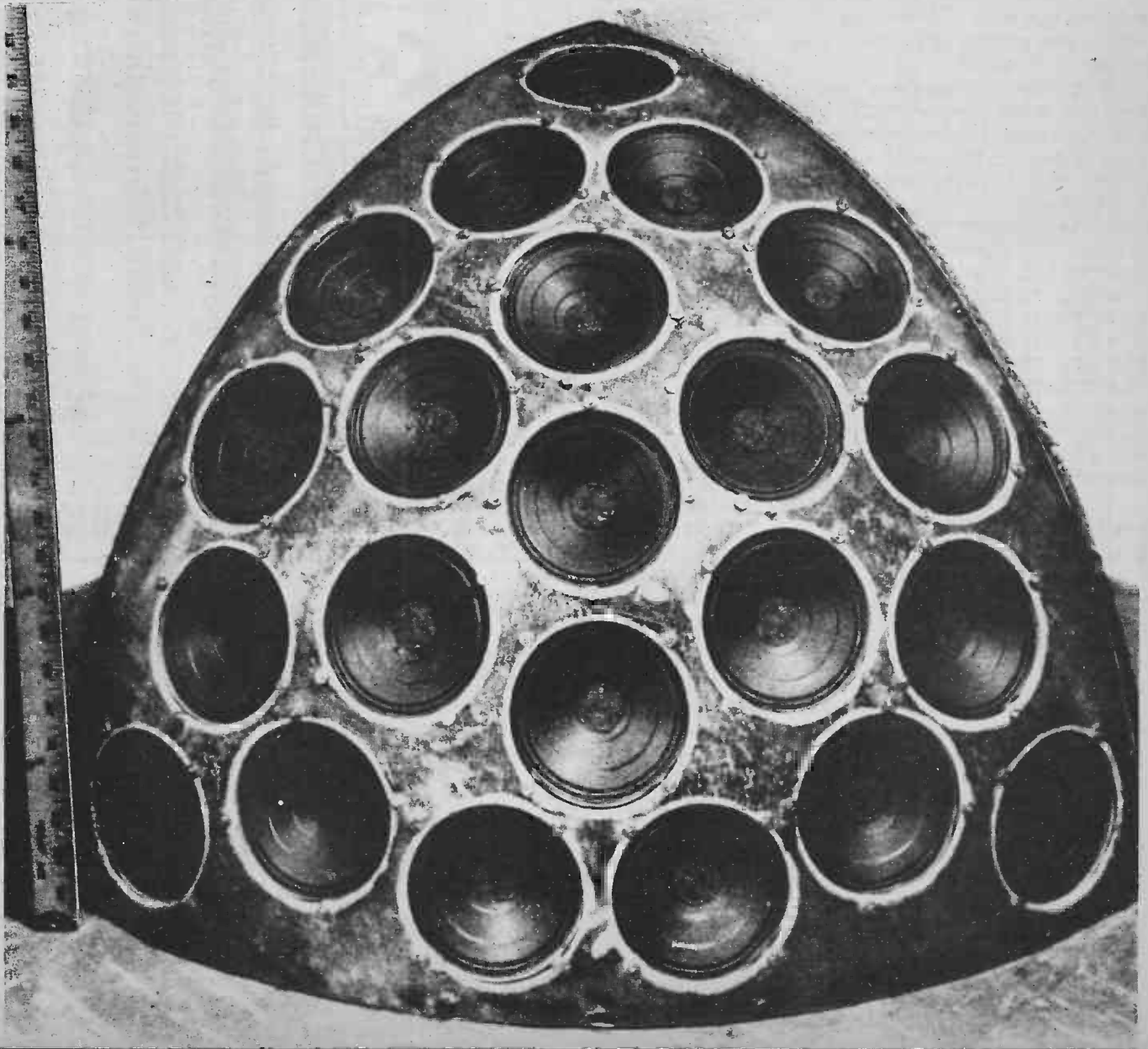**ETI**



Philips loudspeaker RH 544 Motional Feedback design. This unit incorporates a separate bass power amplifier, and a lower power amplifier for mid-high frequencies. Bass performance is exceptional for the tiny enclosure size, but other areas of output are undistinguished.

This is one-eighth of the perfect speaker! Many experts consider that elusive device to consist of a pulsating sphere operating in free field conditions. Bose built this approximation to test pulse waveform response. From here sprung the excellent Base 901 series III loudspeaker.



# CAR TACHOMETER

**We've been contemplating a digital car tacho, but have been put off by resolution and response speed problems. However this Phase Locked Loop design overcomes these quite neatly — so here it is!**

WE HAD OFTEN considered the design of a digital tacho for automobile use, but had rejected several schemes as we were unable to get both good resolution and response time — the two seemed to provide a very good demonstration of Heisenberg's Uncertainty Principle.

Consequently, we were rather pleased when Mike Pratt of SM Electronics came to us with his phase-locked loop based design which got round the problem. Would we like to do it as a project, he asked? Obviously, we said yes, and here it is.

This tacho features a fast response time, coupled with 10 Hz resolution, through the use of a phase locked loop frequency multiplier. It can be set up, by means of a single link, to work on 4, 6 or 8 cylinder motors.

## Design Features

To measure the revolutions per minute of a motor is simply a matter of counting the number of ignition pulses over a given time. With a four-cylinder, four-stroke motor there is such a pulse twice per revolution. Therefore if we count these pulses for 30 seconds we will have revs/min with a one cycle resolution. Obviously this is much too long a sample period for practical use in a motor car and some compromise has to be made.

The usual solution is to use a 100 rev resolution and a sample time of 0.3 seconds (on 4 cylinders). We considered this inadequate which is why we have not published a design until now.



In this design an oscillator is used which is phase locked to the ignition pulses except at a higher frequency (x8 for 4 cylinder) allowing a short sample time (0.375sec) with a 10 rev resolution. By using a different multiplication factor compensation for different numbers of cylinders can be made. Unfortunately with the multiplication factors used (x8, x6, x4) the sample time for 6 cylinders is not exactly the same as that used for 4 and 8 cylinder motors. Altering the ratios to x12, x8 and x6 would enable a 0.25 sample time to be used for all ranges, but this is not possible with the divider IC utilised in this design.

## Construction

Assemble the PCB with the aid of the overlay ensuring the components are

orientated correctly. The tantalum capacitors normally have a + mark indicating the positive lead, or a dot on the side. When soldering the CMOS ICs (4, 6, 7) earth the tip of the soldering iron.

Note that there is one feedthrough or link between the two sides of the board near C10

## Calibration

Initially place a link between the point 'C' and the terminal corresponding to the number of cylinders. Now with the power supply connected feed a 50 Hz signal of between 12 and 30 V into the points input using the 0 V as common. Now adjust RV1 until the display reads 1500 RPM for 4 cylinders, 1000 for 6 or 750 for an eight cylinder car. ▶



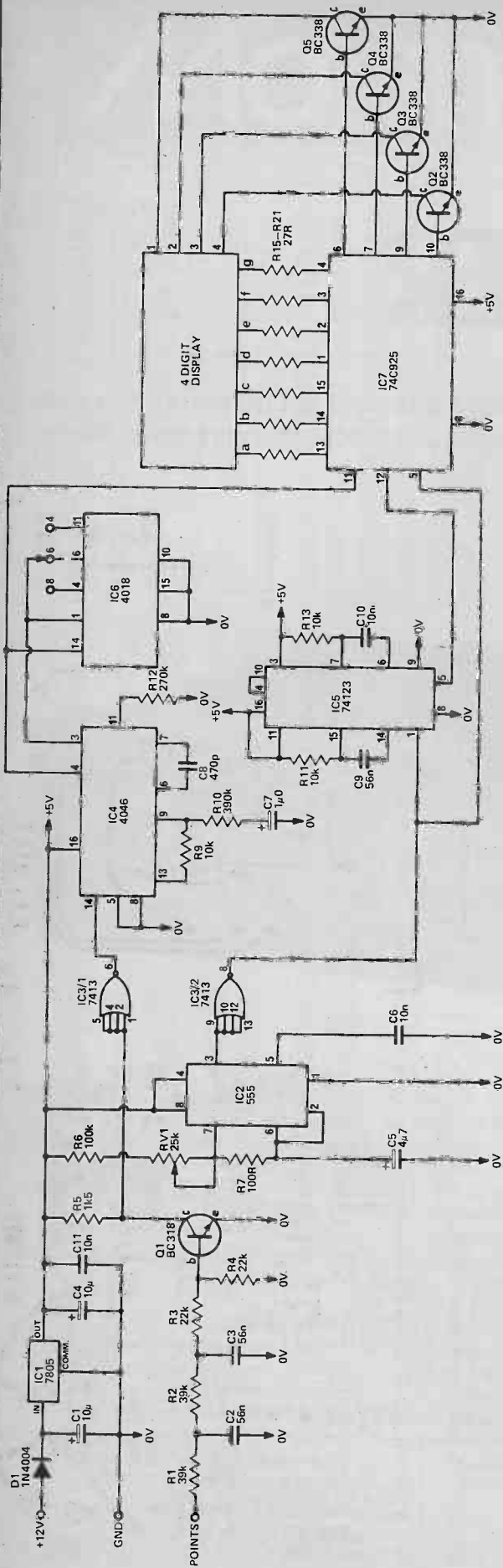


Fig. 2. Full circuit diagram for the digital car tacho unit.

## HOW IT WORKS

The output from the points of the distributor is basically a 0 to 12V square wave with a 200 volt pulse on the rising edge. A filter network, R1-R4, C2, 3 is used to remove the high voltage pulse (and points bounce) and Q1 buffers it giving a +5 to 0V output on its collector. As the filter network removes the sharp edge of the input a schmitt trigger is needed on the output of Q1 to give fast edges. IC3/1 is used for this.


The output of IC3/1 is connected to the input of the phase-locked loop IC (4046). This IC has an internal voltage controlled oscillator and its output is divided by 4, 6 or 8 by IC6 and this lower frequency is fed back to the phase-locked loop IC. The IC then compares this frequency to that at its input and adjusts the internal oscillator until it is the same. The result is a frequency which is an exact multiple of the input.

The time base is generated by IC2 (555) which has a negative output pulse, about 300  $\mu$ s wide every 375 ms (or 333 ms for 6

cylinder). This is inverted by IC3/2 and is used as the strobe pulse for the 4 digit counter IC7. This pulse also triggers the first of the monostables in IC5 which gives a 200  $\mu$ s delay before triggering the second half of IC5; this gives a 40  $\mu$ s pulse to reset IC7 back to zero.

IC7 is a 4 digit counter with a latch (store) and seven segment decoder driver. It needs four external transistors to drive the digits but the segment drivers are internal. As we need only a three digit counter, i.e. for good resolution, with the right hand permanently zero the least significant digit is connected to the second right digit, etc, with the most significant digit connected to the right hand digit. Provided one does not exceed 9990 RPM this digit will remain on 0 as intended!

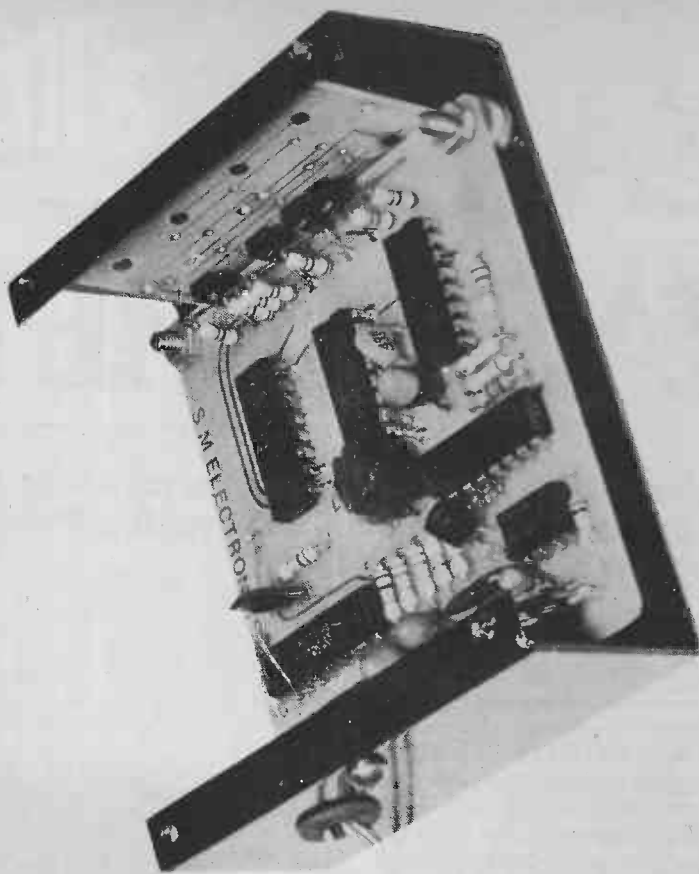The 555 timer, the TTL and the 74C925 needs a regulated +5V and IC1 provides this with D1 preventing damage due to reverse polarity inputs.





# SPECIFICATION

**Range**  
 100 to 9990 RPM  
 10 RPM  
**Resolution**  
 2.66 per second  
 3 per second  
**Reading rate**  
 4 or 8 cylinders  
 6 cylinders  
**Power supply**  
 7 to 15V @ 400mA  
**Suitable ignition systems standard**  
 CDI  
 transistor assisted  
 'it will not operate on  
 'pointless' systems

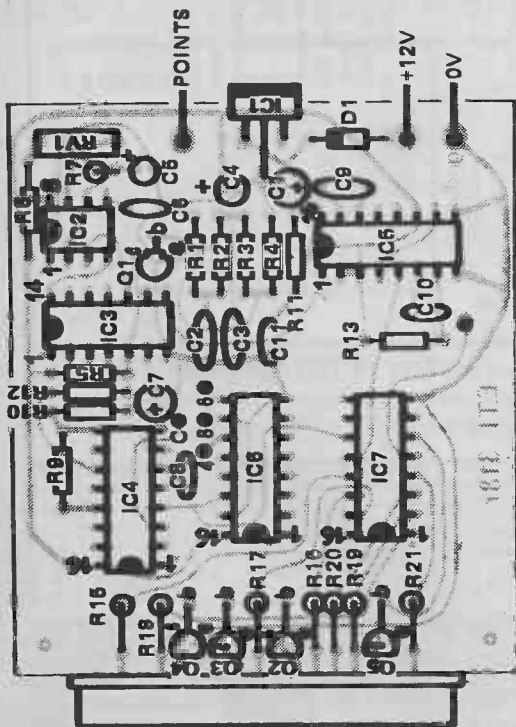


Fig. 1. The component overlay for the board. The board is double sided although only the lower surface is shown here. Note the link between the two surfaces of the board near C10.

# PARTS LIST

RESISTORS	all 1/4 W, 5%
R1,2	39k
R3,4	22k
R5	1k5
R6	100k
R7	100R
R8	not used
R9	10k
R10	390k
R11	10k
R12	270k
R13	10k
R14	not used
R15-R21	27R
POTENTIOMETER	
RV1	25k trim
CAPACITORS	
C1	10u 25V tantalum
C2,3	56n polyester
C4	10u 25V tantalum
C5	4µ 7 25V tantalum
C6	10n polyester
C7	10u 25V tantalum
C8	470p ceramic
C9	56n polyester
C10	10n polyester
C11	10n ceramic
SEMICONDUCTORS	
IC1	7805 regulator
IC2	555 timer
IC3	7413 dual schmitt
IC4	4046 PLL
IC5	74123 dual mono
IC6	4018 divide by n
IC7	74C925 4 digit counter
Q1	BC318
Q2-Q5	BC338
D1	1N4004
Display	NSB5881
MISCELLANEOUS	
PCB	Case to suit

# BUYLINES

The components employed here are all readily available from any of the major mail order companies advertising in this issue. Note that the counter is a CMOS chip, and not a standard bi-polar TTC chip. The standard component will not operate on this mode.

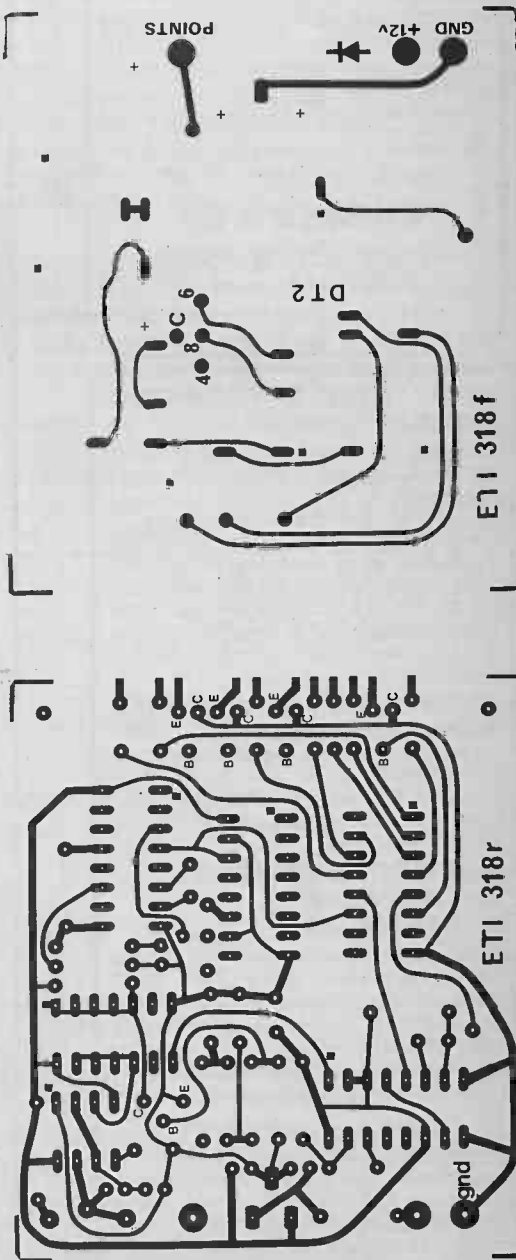


Fig. 3. PCB foil patterns shown full-size.

# POWER SUPPLIES

One more from Tim Orr. This time he takes us through a series of different methods for powering up circuits. On the way he explains the theory behind each.

THE JOB OF producing stable regulated power rails has been much simplified by the introduction (about seven years ago), of three terminal fixed voltage regulators. These devices can make the power supply design, problem relatively simple, but even so the designer must be fully aware of a lot of other important details that can cause poor results. Firstly, consider a simple unregulated power supply, fig. 1.

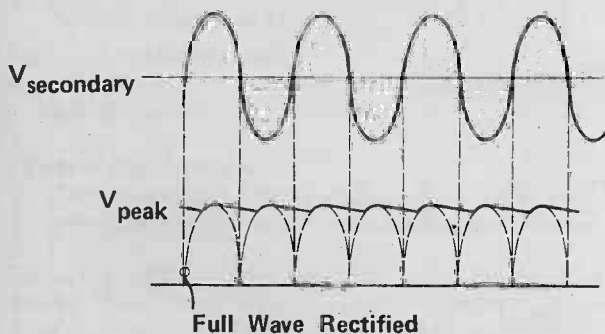


Figure 1. Below: an unregulated power supply. Above: The output (with a load resistor).


The function of a mains isolating transformer is to physically separate the user end of a piece of equipment from the 'potentially' (!) lethal mains voltage. The transformer also provides a suitable voltage which can be rectified and smoothed and connected to a voltage regulator. This is the secondary voltage of a transformer and it is measured in VRMS at a particular loading.

That is, if the transformer is rated at 15V at 10VA, then the output voltage will be 15V when the load upon the transformer secondary is 10VA (10 watts).

If the load is removed the output voltage will rise. The percentage change from load to no load is known as the TRANSFORMER REGULATION and is typically of the order of 20%.

To convert the  $V_{RMS}$  voltage to a DC voltage it must be multiplied by 1.4142. Thus a 15VRMS (loaded) transformer secondary will generate 21V2 DC when full wave rectified and smoothed, which will rise to 25V45 DC when the load is removed (assuming 20% regulation see Fig. 1).

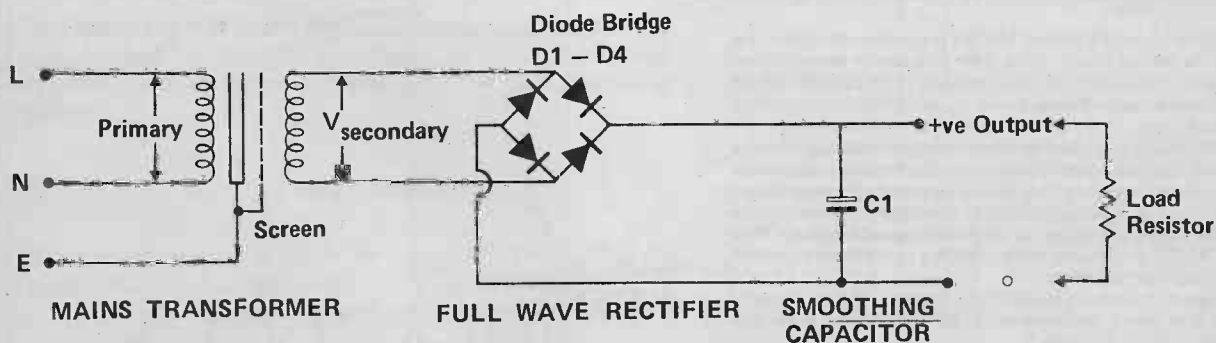Thus care has to be taken when selecting a transformer such that the smoothing capacitor working voltage is not exceeded. Also, make certain that the polarity on this capacitor is correct, they can LITERALLY explode if wired up backwards!




This piece of hardware has three sections, a step down, isolating transformer, a diode bridge and a smoothing capacitor. The transformer is driven from the mains, the voltage of which varies depending on where you live (it's 250V/RMS in Fulham). Some transformers have got a copper screen which isolates the primary winding from the secondary windings. For the purpose of safety, this should be connected to earth.

Also, for maximum safety, connect the 220/240/250 tapping to mains LIVE. Another type of mains transformer uses what is known as a split bobbin, the primary is wound on one bobbin, the secondary on another. Thus the two windings are inherently physically isolated, and so no safety screen is included. These two transformer types are generally constructed on what is known as an 'E' core; take one to bits and you will find that it is

constructed out of lots of 'E' shaped laminations. These 'E' laminations are butted into 'I' laminations, and clamped together. This butting together of the laminations can cause magnetic field problems. The wider the gap between the 'E' and 'I' laminations, the larger the magnetic field around the transformer.

The magnetic field generates a significant amount of induced hum in nearby electronics, this can be overcome by using a low leakage toroidal transformer which is constructed from circular laminations. The primary and secondary windings are wound through the centre of the toroid (see if you can imagine how). The toroidal transformer, by virtue of its 'continuous' laminations results in a low stray field and a low profile design, making it ideally suited for audio amplifier applications.

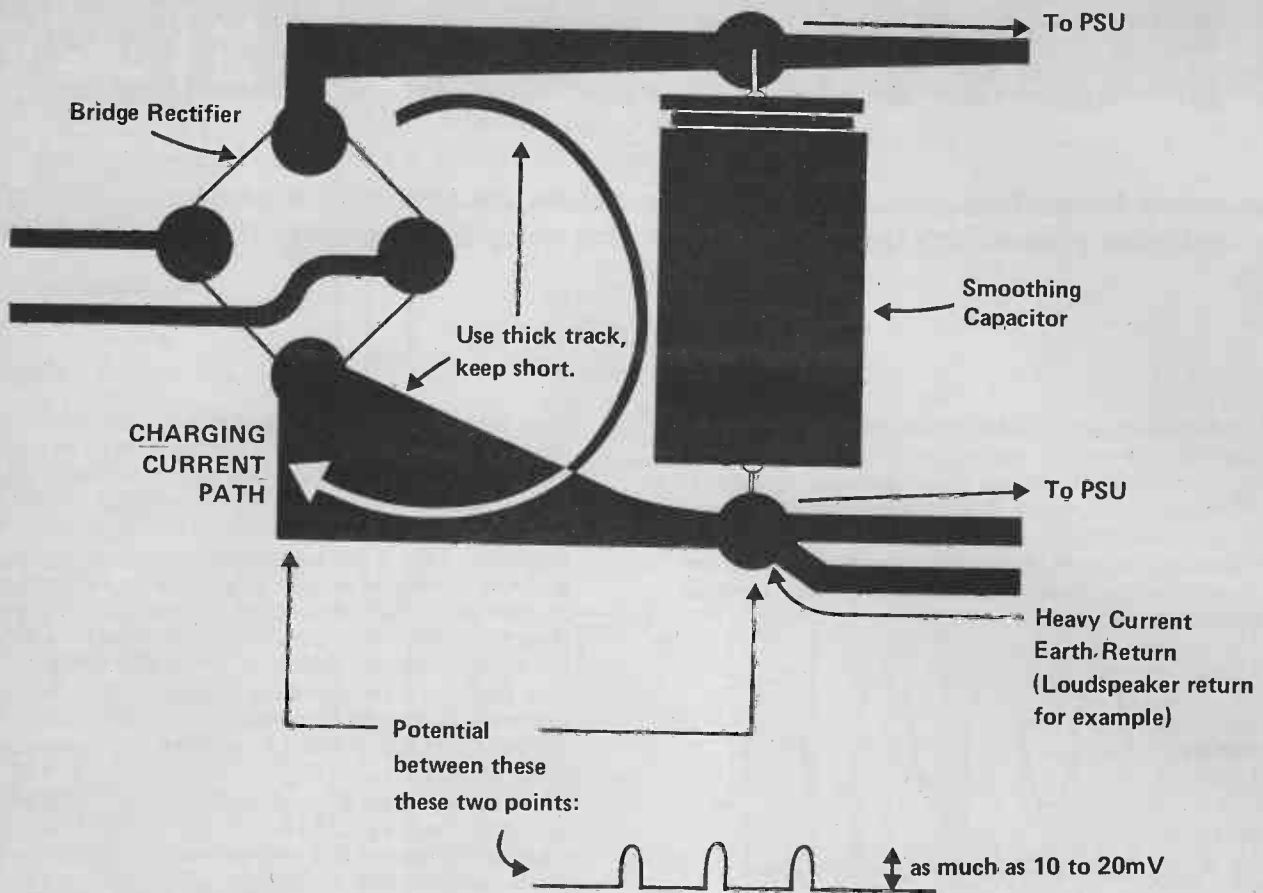


When a load is placed upon the power supply shown above, the output voltage appears as a DC voltage on top of which is a ripple voltage. This can be thought of as two separate periods, a charge period where the capacitor is charged up by the power supply and a discharge period where the load discharges the capacitor.

This charging and discharging generates a ripple voltage which has a period of 10 ms (100 Hz). A load current of 100 mA, and a 100µF capacitor will result in a ripple voltage (V<sub>pp</sub>) of about 7V.

As a rule of thumb I usually allow 1 to 1V5 maximum ripple if a voltage regulator is being used. This will generally result in an output ripple of less than 1 mV. If this ripple were to be obtained by just using a larger capacitor, then a 700,000µF-capacitor would be required!

Generally the discharge period is much longer than the charge period. This means that the transformer is only supplying power for short periods, in fact during the charge period. During these periods the smoothing capacitor is rapidly charged, and it is quite common for these current surges to exceed several amps. This can cause mains BUZZ problems when laying out printed circuit board designs for power supplies.

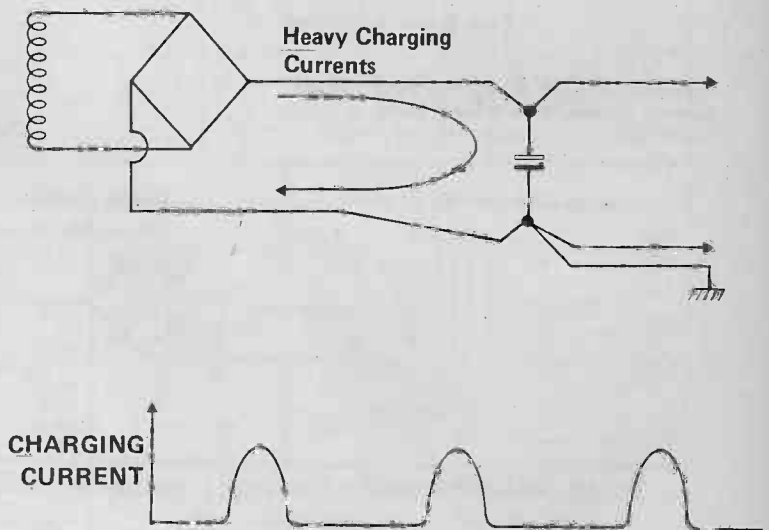The correct layout is shown below the circuit. If the current surge is 1 A and the track resistance is 20 milliohms then the voltage developed will be 20 mV<sub>pp</sub>.



## Voltage regulators

A voltage regulator takes a varying unregulated input voltage and produces a fixed regulated output voltage. There is a wide range of fixed voltage three terminal regulators to choose from, with a choice of maximum current handling, output voltage and positive or negative operation. The data sheets for these devices contain lots of seemingly complex pieces of information and so a glossary of terms is now included.

## Ripple Rejection

The ratio of the ripple voltage at the regulator input to that at the output, generally expressed in dB. Typically of the order of 60 dB (1000 to 1), that is 1 V<sub>pp</sub> of ripple at the input ends up as 1 mV<sub>pp</sub> at the output.

## Temperature Coefficient

The output voltage change for a change in regulator temperature, expressed in mV/°C.



# electronics today

JANUARY 1979 VOL 8 NO 1 **INTERNATIONAL**

## FEATURES

NEWS DIGEST	<b>7</b>	What goes on with whom and where!
LOUDSPEAKER PRINCIPLES	<b>14</b>	Cone-fident appraisal of all types!
POWER SUPPLIES	<b>27</b>	Tim Orr explains how — and why.
ELECTRONICS IN MEDICINE	<b>40</b>	A history of the electron put to use.
DATA SHEET EXPLAINED	<b>57</b>	This was your idea.
MICROFILE	<b>67</b>	Big news for micro-men.
BORIS IN CHECK	<b>81</b>	A new chess machine tested.
AUDIOPHILE	<b>87</b>	A Shure winner?
TECHNICAL MEMORANDUM	<b>91</b>	A revolutionary new concept!
TECH TIPS	<b>93</b>	Readers own ideas.

## PROJECTS

DIGITAL TACHO	<b>23</b>	Going around in the car accurately.
DIGITAL MODULE	<b>35</b>	Useful four digit design.
DIGITAL DIAL	<b>49</b>	Medium wave high quality.
LOG CONVERTOR	<b>62</b>	Turn your keyboard to use.
CLICK SUPPRESSOR	<b>73</b>	Record project!

## INFORMATION


ETI BOOK SERVICE	<b>47</b>	Fine print this.
SPECIALS FROM ETI	<b>55</b>	All our publication on show.
PANEL TRANSFERS	<b>59</b>	Finishing touch.
HOBBY ELECTRONICS	<b>61</b>	Look out for it!
BINDERS	<b>69</b>	Keep 'em looking good.
ETI PRINTS	<b>71</b>	What other way is there?
FEBRUARY PREVIEW	<b>79</b>	News of next month's ETI.
MARKETPLACE	<b>84</b>	A new LADIES' watch!
SUBSCRIPTIONS	<b>92</b>	Make it easy on yourself.
T-SHIRTS	<b>98</b>	Good cover!



Time we did this p.84



Check it out p.81

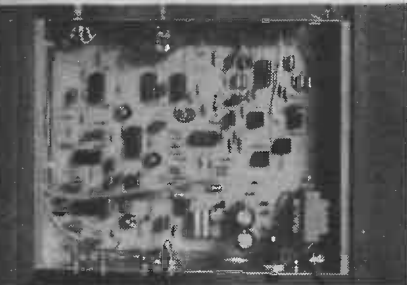

De-click de hi-fi p.73

### INTERNATIONAL EDITIONS

AUSTRALIA	Collyn Rivers Publisher Les Bell Acting Editor
Holland	Anton Kriegsman Editor-in-Chief
CANADA	Steve Braidwood Editor Graham Wideman Assistant Editor
GERMANY	Udo Wittig Editor



ABC

EDITORIAL AND ADVERTISEMENT OFFICE  
25-27 Oxford Street, London W1R 1RF. Telephone 01-434 1781/2. Telex 8811896

Halvor W. Moorshead	Editor
Ron Harris B.Sc	Assistant Editor
Gary Evans	Project Editor
Pete Howells	Production Editor
Paul Edwards	Technical Illustrator
Steve Ramsahadeo	Project Development
Margaret Hewitt	Administration
Kim Hamlin, Brenda Goodwin	Reader Services
Tim Salmon, Val Tregidgo	Advertising Manager
Mark Strathen	Provincial Advertising Manager
David Sinfield	Advertising Assistant
Joy Cheshire	

PUBLISHED BY Modmags Ltd., 25-27 Oxford Street, London W1R 1RF  
DISTRIBUTED BY Argus Distribution Ltd. (British Isles)  
Gordon & Gotch Ltd. (Overseas)  
PRINTED BY QB Limited, Colchester

Electronics Today International is normally published on the first Friday of the month prior to the cover date

COPYRIGHT: All material is subject to world wide Copyright protection. All reasonable care is taken in the preparation of the magazine to ensure accuracy but ETI cannot be held responsible for it legally. Where errors do occur a correction will be published as soon as possible afterwards.

## Input Voltage range

The range of voltages over which the regulator will function normally. For example, a 12V regulator may work from 14V5 to 30V. At 14V5 the regulator will 'drop out' and lose its regulation. Regulators generally need 2 to 2V5 in excess of their output voltage. At 30V the regulator will go 'pop' (time to buy a new one).

## Output voltage

The voltage at the output terminal with respect to ground. Generally within  $\pm 5\%$  of stated value.

## Line Regulation

The ratio of the change in the output voltage caused by a change in the input voltage, typically of the order of 0.2%.

## Load Regulation

The output voltage change for a specific change in output load current.

## Short Circuit Current

The output current when the output is shorted to ground.

## Output Noise Voltage

The RMS noise voltage measured at the regulators output, not including any ripple.

## Power Dissipation

The maximum power that the regulator can safely generate on a particular heatsink.




As a rule of thumb the regulator case should not exceed about 80°C (which is hot to touch). However, always run the device at as low a temperature as possible. It is thermal ageing that eventually kills electronic devices and for higher temperatures the ageing process is disproportionately faster.

Some applications of voltage regulators are given below.


The table below relates the secondary voltage of a transformer to the peak voltage at rated load and the off load voltage, which will be considerably higher.

TABLE ONE


V secondary at rated load	V peak at rated load	V peak off load transformer regulation 20%
5 VRMS	7V07	8V48
6 VRMS	8V48	10V18
9 VRMS	12V72	15V26
10 VRMS	14V14	16V97
12 VRMS	16V97	20V36
15 VRMS	21V21	25V45
20 VRMS	28V28	33V93
25 VRMS	35V35	42V42
30 VRMS	42V43	50V92
35 VRMS	49V50	59V40
40 VRMS	56V57	67V88

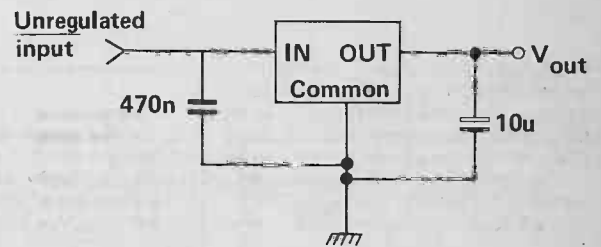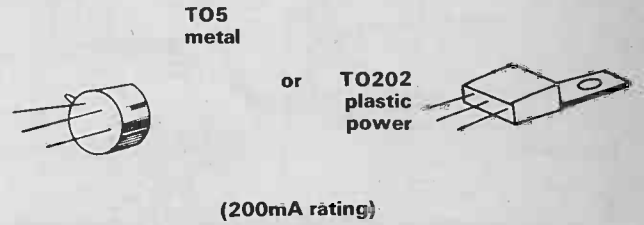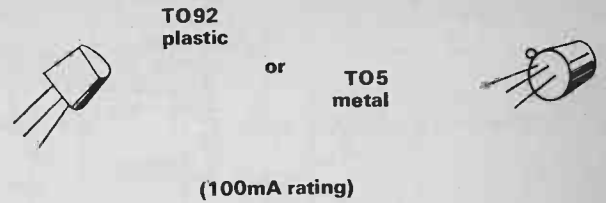

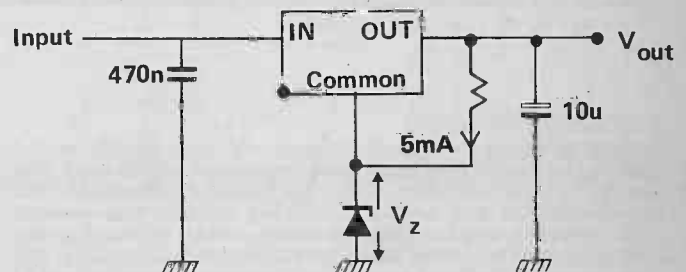
A) This circuit shows a conventional arrangement of a three terminal device. It is advisable to use a decoupling capacitor connected close to the input terminals. This prevents high frequency instability. If this capacitor is left out then regulation can sometimes be greatly reduced. The decoupling capacitor on the output helps reduce the impedance at high frequencies, where the regulator loses its performance. For best results use a tantalum capacitor.



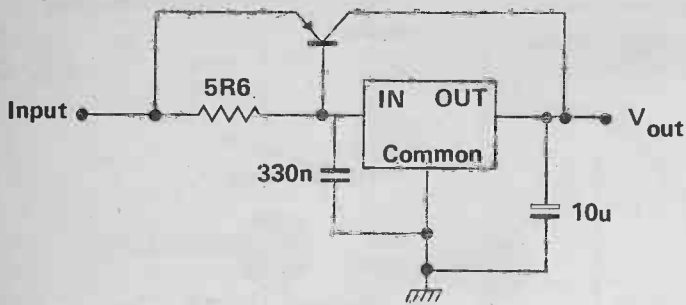B) The output voltage of a regulator can be increased by applying a voltage to the common terminal. This can be done by using a zener diode.



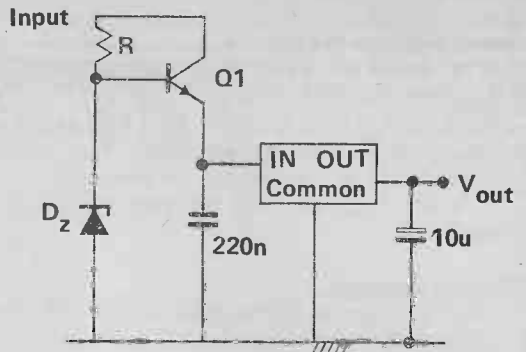C)  
The output current can be increased by using a bypass transistor. When the current flowing through the voltage regulator exceeds 100 mA (the voltage across the 5R6 being 560 mV), the bypass transistor begins to turn on. This transistor takes all currents in excess of 100 mA and yet the output still remains regulated. However a few extra components are needed to get current limiting in the transistor path.




D)  
A high voltage unregulated supply can cause problems when using regulators. It may at times exceed the maximum voltage rating of the regulator. A simple voltage regulator  $D_z$  and  $Q_1$  can be used to overcome this problem.  $D_z$  should be chosen so that it is about 6V greater than the regulator output voltage. This technique has the added advantage that the power dissipated in the regulator is less (the rest being dissipated in  $Q_1$ ), and the regulator is presented with a semiregulated voltage, so the output will have less ripple.
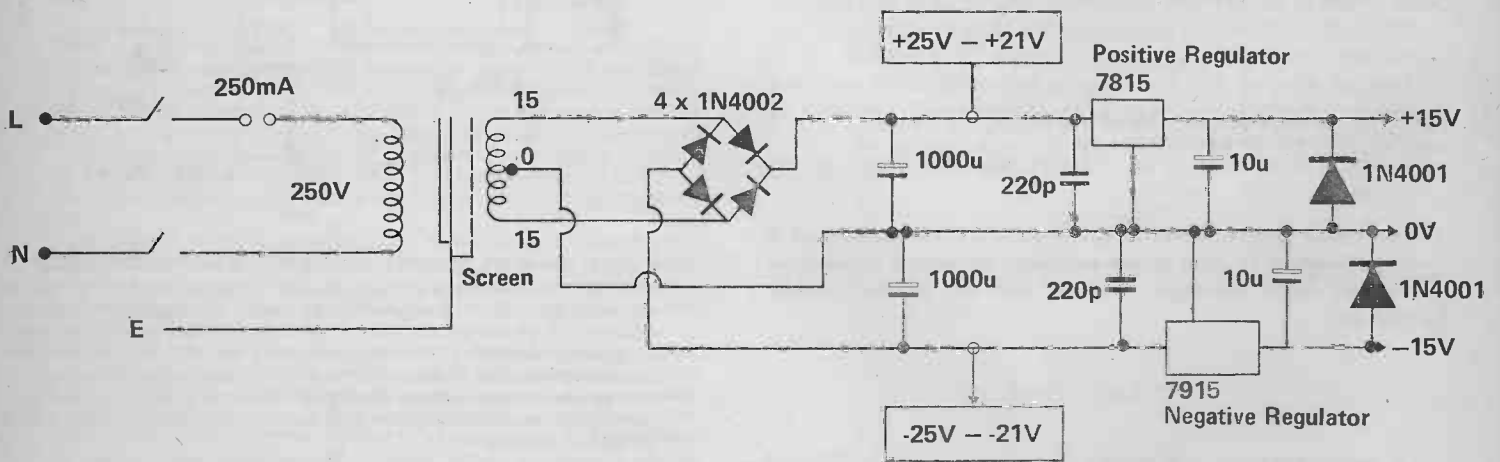
### Dual Power Supply


The circuit shows a complete regulated dual power supply. The unregulated rails are obtained from a split secondary transformer, a bridge rectifier and two smoothing capacitors. A positive and a negative regulator have been used to generate the + and - rails. These regulators should be mounted on heat sinks

and they should be insulated. The pin out of the negative regulator is different to that of the positive regulator. The two diodes at the output prevent latching up situations (on load) whereby one side starts up faster than the other and forcibly reverse biases it, preventing it from operating.


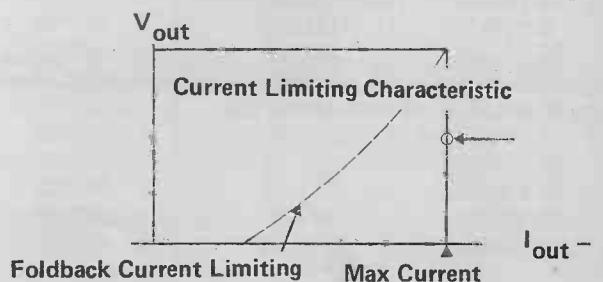
### Tracking Regulator

Instead of using a negative voltage regulator to obtain the negative rail, an op amp and a power transistor can be used. The resistor ratio,  $R_1$ ,  $R_2$  determines the negative rail voltage. The negative rail is not, however, current limited. The internal current limiting of the regulator is shown. When the load current exceeds the current limit, the output voltage drops to almost 0V. This makes the regulator short circuit protected. Another type of current protection is known as 'FOLD BACK' current limiting (shown dotted). This serves to reduce the short circuit current. These devices protect the power supply from abuse. Another type of protection device is the overvoltage clamp, which






protects the 'non-power supply electronics' from an increase in the power supply voltage. These are two terminal heavy current devices which are placed across the power supply. When the supply voltage exceeds a certain level a thyristor is triggered on and clamps the rail to ground. This is intended to pop a fuse and so disconnect the faulty power supply (which is better than replacing a £1,000 worth of IC's).

$$\text{-ve output} = -(\text{+ve output} \times R2/R1)$$

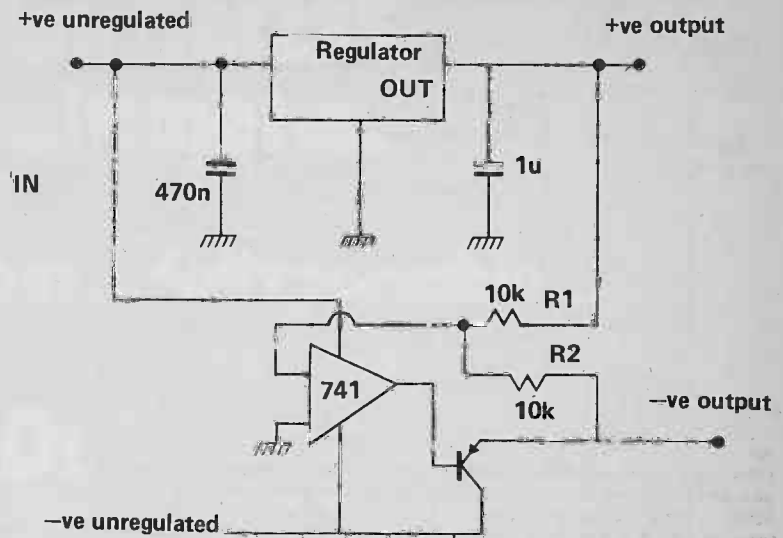
With foldback the short circuit power dissipated in the regulator is less than that with current limiting.


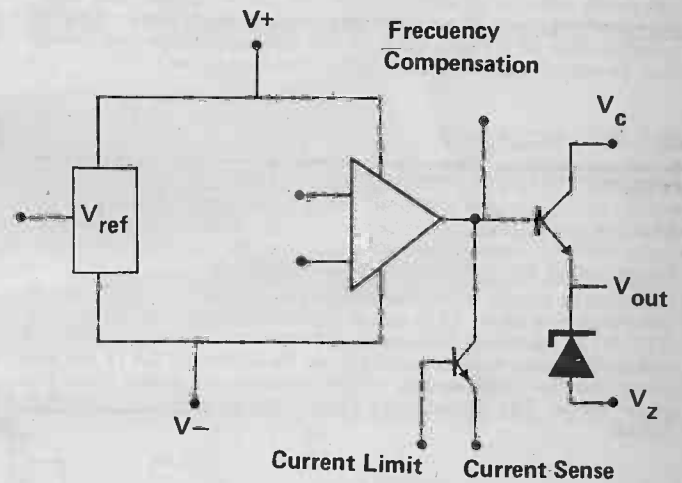
## 723 Voltage Regulator


The 723 is an industry 'standard' device. Many manufacturers produce it and the device itself is versatile. It comes in a 10 pin TO5 can or a 14 DIL pack. The device contains a precision voltage reference, with a temperature coefficient of 50ppm/°C, an error amplifier, an internal transistor capable of handling 100 mA and a current limiting mechanism. By using a few external resistors, a capacitor and maybe an external power transistor, a wide variety of regulator designs can be realised.

Left is shown the block diagram of the 723 regulator. As pinouts vary depending upon package, no pin numbers are shown.



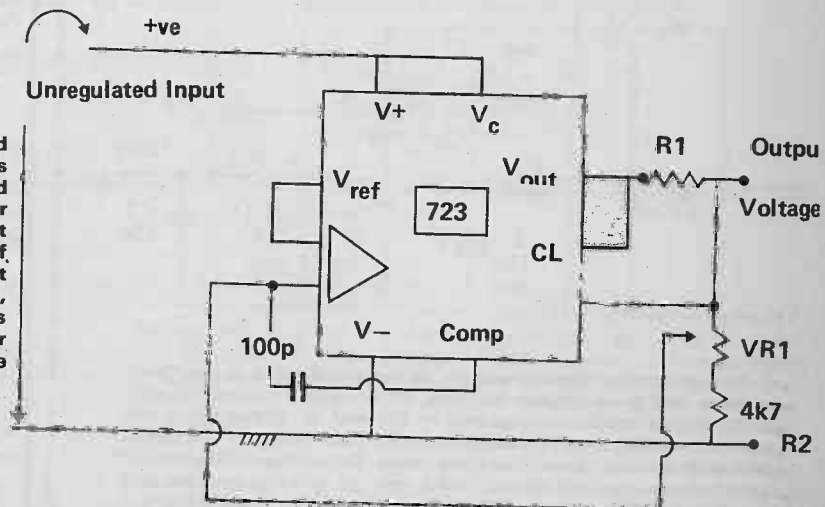
## Adjustable Positive Voltage Regulator

By using a variable feedback path (RVI), a variable regulated output voltage can be generated. The voltage reference is connected to the non-inverting input of the error amplifier and the output voltage (via RVI), to the inverting input. The error amplifier drives the output transistor and hence the output voltage is controlled by the feedback voltage from VR1. A 100pF capacitor is used to stabilise the device. R1 is used as a current limit control. When the current through R1 (the load current), exceeds 100 mA a voltage of 560 mV is set up across it. This is just about sufficient to turn on the current limiting transistor which in turn shorts out the regulating transistor, causing the output voltage to collapse towards 0V.


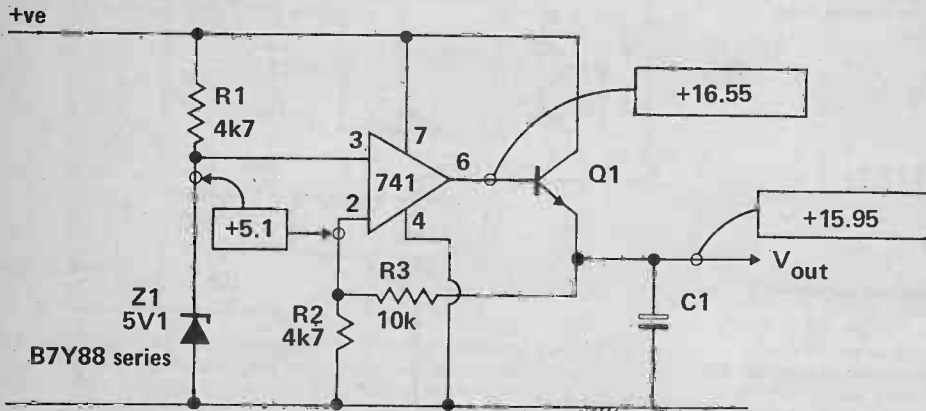
## Regulated Power Supply

Sometimes it is necessary to make a simple power supply using discrete components when a non-standard voltage is required.



Left: Circuit diagram of discrete component PSU. Voltage measurements are taken with high impedance voltmeter.

The circuit shown uses all the basic elements of a voltage regulator, that is, a reference voltage Z1, an error amplifier and a series control Transistor Q1. The zener diode, Z1 sets up a reference voltage of 5V1. This diode has a temperature coefficient of  $-1.2\text{mV}/^\circ\text{C}$  (a 5V6 zener is best at  $-0.2\text{mV}/^\circ\text{C}$ ). The resistor ratio of R3 and R2 sets the output voltage and the op amp provides the error correction (the regulation).


C1 is used to reduce the output impedance at high frequencies. The zener diode has a slope resistance of  $76\Omega$ , and so any fluctuations in the unregulated rail will be attenuated by the ratio of 76:7: 0.016

R1 4700

Therefore a 1 Vpp ripple will end up as 16 mVpp, but will be multiplied by the gain of the R3, R2 network to nearly 50mV.
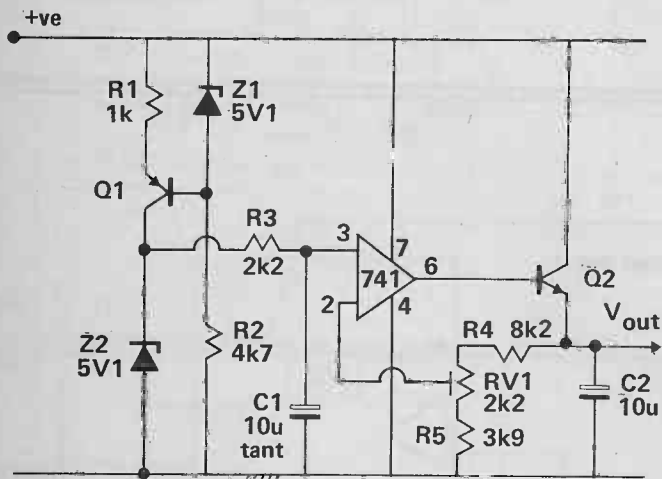
## Improved Regulated power supply

This power supply has various improvements over that shown. The reference zener Z2 is run at almost constant current by the R12, Q1 Z1 network. This makes Z2 much less sensitive to ripple and unregulated supply fluctuations. The filter R3 C1 (7 HZ low pass), further reduces any ripple voltage and noise from the zener diode. The preset VR1 allows the output voltage to be varied.



If a precision power supply is required then a precision voltage reference should be used. These can be obtained with temperature coefficients as low as  $10\text{ppm}/^\circ\text{C}$ . When using this level of stability, high stability resistors ( $\text{TC} = 10\text{ppm}/^\circ\text{C}$ ), and a low drift op amp should be used. Also, to reduce mains carried interference (mainly sharp clicks due to electric motors and thyristors turning on), a mains filter should be used. This is a passive inductor capacitor low pass filter network which attenuates high frequency spikes and clicks.

ETI

## MAINS OPERATED ELECTRONIC DIGITAL ALARM CLOCK

IMMEDIATE DELIVERY

£8.95

INCL. V.A.T. POST PAID

THREE FOR £26.00 POST FREE

ETI RECOMMEND THIS MODEL

BARCLAY ACCESS

Just phone in number

- Hanimex HC-1100
- Large Bright LED display
- White case with red display on black background
- Adjustable dim/bright control
- Silent operation, all electronic
- Space age technology L.S.I. circuitry
- Alarm and 9 minute snooze repeater
- P.M. indicator
- Hour and minute display
- Size 100mm x 130mm x 60mm high
- Fully guaranteed




**HENRY'S**  
RADIO

HENRY'S RADIO  
404 Edgware Rd. London W2  
PHONE (01)723 1008
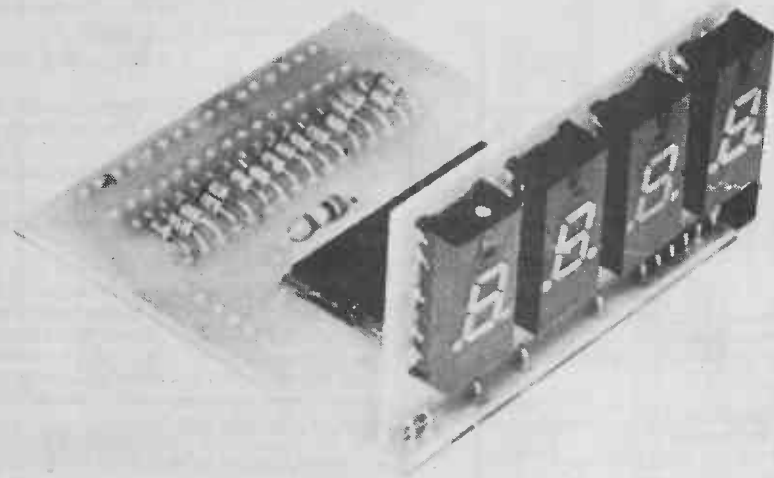
# DIGITAL MODULE

- \* 4 digit
- \* up/down counting
- \* drives LEDs directly
- \* latch
- \* presettable
- \* second register
- \* equal and zero outputs
- \* DC to 2MHz
- \* 5V operation



THE THREE DIGIT display we previously published has proved to be one of our most popular projects. We have used it in a number of projects and we know of several commercial companies using it in their own equipment.


Many people have asked us for a 4 digit version and we have been looking round at ICs available. We have chosen this Intersil device because we believe it offers the best versatility at the moment. Apart from being a 4-digit counter-latch-decoder driver needing no external components except the displays, it also is an up-down counter and can be preset to any number. In addition, it has a separate register which also can be set to any number and comparators which give outputs when the counter is equal to the register and when it is zero — all in one IC!

## Mod Build

The unit is built on two small PCBs which are connected together with short links of tinned copper wire. Be careful to orientate the IC correctly as it is expensive!

The preset system is designed to use a 4 digit BCD thumbwheel switch

Fig 1. Full circuit diagram of the counter module. The How It Works section for this is given overleaf — but as this is really a "How To Use It" section it don't matter — does it?

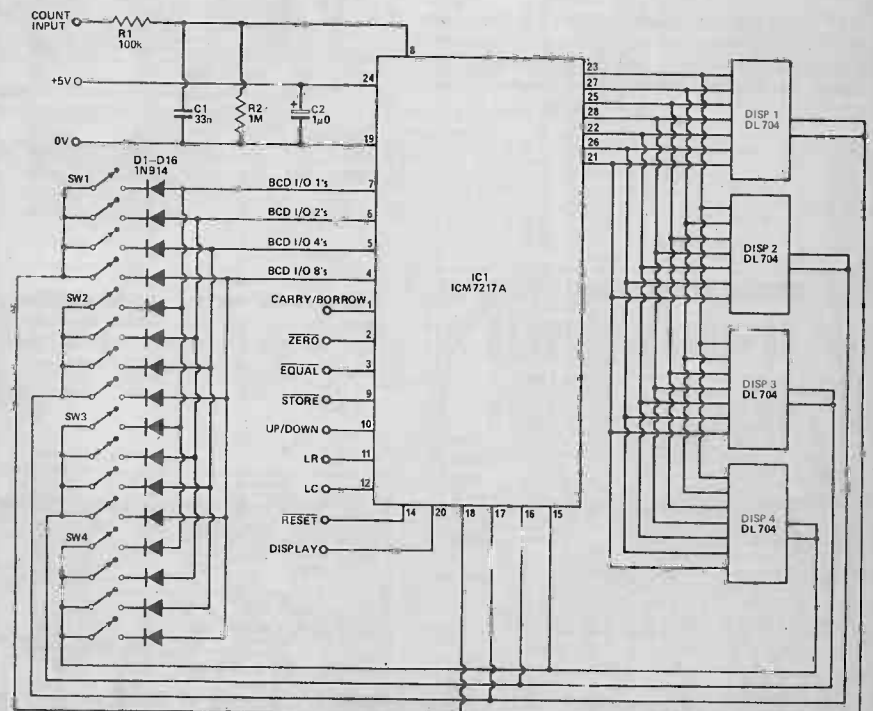

## SPECIFICATION

Number of digits	4
Readout	LED
Maximum frequency	2MHz
Input impedance	100k
Output drive	1 TTL load
Supply voltage	4.5 – 5.5V
Supply current	
low power mode	500µA
all eights	100mA



(closed = '1') but individual switches can be used if required. Input is in BCD, therefore the switches will have the weighted values 8, 4, 2 and 1. If the preset is not needed then the diodes can be left out. If a preset is needed, but always to a fixed number, links can be inserted to replace the "on" switches and the other diodes left out.

ETI

Fig. 2. The positioning of the displays and the links which must be installed before the displays.



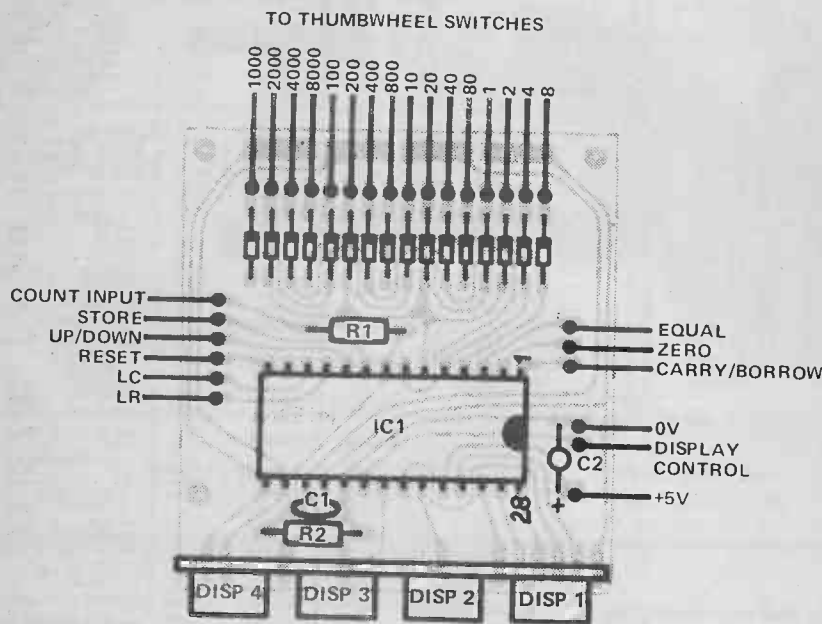
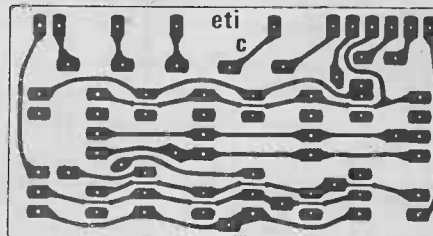


Fig. 3. The component overlay for the main board. The common connection from each of the thumbwheel switches goes to the track next to the other connections.

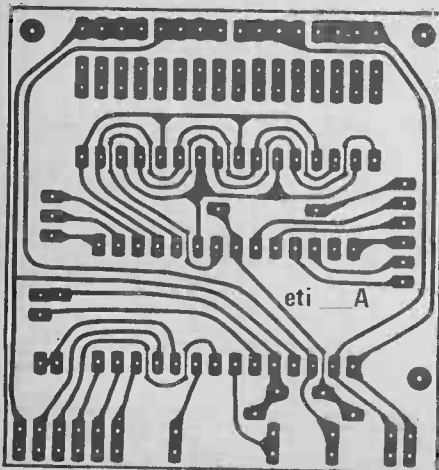

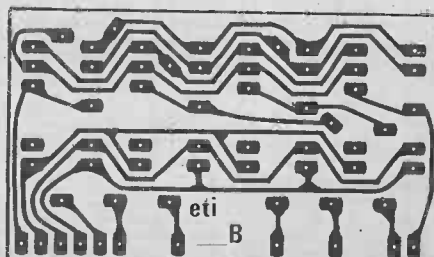Full patterns for the digital module project. Shown full size. Board C — above — is to fit high brightness displays such as employed in our digital dial project.



## HOW IT WORKS

### Count Input — Pin 8

The counter is incremented or decremented on the leading edge of this input. A schmitt trigger is provided with a 500 mV hysteresis on a 2 V trigger point. For high speed operation, or operation from a digital output, delete R2 and C1 and short out R1. Maximum frequency of operation is about 2 MHz.

### Up-Down — Pin 10

If this pin is left open or taken to +5 V the counter will be incremented by the count input. If it is taken to 0 V the counter will be decremented by the count input.

### Reset — Pin 14

If this pin is left open or taken to +5 V the counter is free to be incremented or decremented. If it is taken to 0 V the counters will be reset to zero and held there until reset is taken high again.

### Store — Pin 9

If this input is left open or taken to +5 V the latches are "closed" and the information which was in the counters at the time the store input went high will be remembered, decoded and displayed. The counters can be reset, incremented or decremented without affecting the display.

If it is taken to 0 V the counter contents will continuously be displayed for as long as this input is at 0 V. Any change in the counter contents will be shown on the display.

### Load Counter — Pin 12

This is a 3 level input. If it is left open the counter works normally. If it is taken to +5 V the counter is loaded with the BCD data which is set on the thumbwheel switches. If the latch is open, this number will also be displayed. If this input is taken to 0 V the BCD I/O pins become high impedance. If a 3 level input is to be controlled by other logic outputs they must be tristate devices.

### Load Register — Pin 11

This is also a 3 level input. If it is left open the counter works normally. If it is taken to +5 V the register is loaded with the BCD data. If taken to 0 V the circuit goes to a low power state with the multiplexing oscillator stopped, the display off and the BCD I/O pins in a high impedance state. The operation of the counter is unaffected except that there is no display.

## BUYLINES

Since this project is based entirely upon the one chip—ICM 7217A — this is all there is to cause problems! Since it appears in most peoples catalogues we cannot foresee any trouble here. Displays can be any type really — but for outdoor work use high brightness types.

# PROJECT: Digital Module

## Display Control - Pin 20

This is also a 3 level input. If it is left open, leading edge blanking occurs. If all digits are zero then all are blanked. If it is connected to +5 V the display is completely blanked irrespective of the value. If taken to 0 V all digits are ON irrespective of value.

## Scan - Pin 13

The internal multiplexing frequency is nominally 10 kHz giving a digit repetition rate of 2.5 kHz. With a 20 pF capacitor from this point to 0 V the frequency drops to 5 kHz and with 90 pF it is about 1 kHz.

## BCD I/O - Pin 4-7

This is a multiplexed data port, normally an output which can drive 1 TTL load. It becomes an input when either LC or LR is at +5 V. Pin 7 is the least significant bit.

## Digit Drives - Pins 15-18

These are used both to drive the LEDs and to provide data indicating which digit is being presented at the BCD I/O port. Pin 18 is the least significant digit.

## Zero - Pin 2

If the value of the counter is zero this output will be at 0 V.

## Equal - Pin 3

If the value of the counter is equal to the value of the register this output will be at 0 V.

## Carry/Borrow - Pin 1

When the counter goes from 9999 to 0000 or from 0000 to 9999 a 500 ns positive pulse occurs on this output. This is connected to the count input of a second unit when an eight digit display is needed.

# PARTS LIST

### RESISTORS (all 1/2W 5%)

R1 100k  
R2 1M

### CAPACITORS

C1 33n polyester  
C2 1u0 35V tantalum

### SEMICONDUCTORS

IC1 ICM 7217A  
D1-D16 1N914  
DISPLAYS DL704

# Greenbank

(Dept T1E) 92 New Chester Road,  
New Ferry  
Wirral, Merseyside. L62 5AG  
(Tel: 051-645 3391)

TERMS: VAT, C.W.O. Add VAT to all prices at 8% except where stated otherwise. Post etc.: UK 25p (+2p VAT = 27p) per order. Export: NO VAT but add 75p (Europe) and £2.50 elsewhere.  
(Polys, universities, govt. depts., etc can telephone their orders for immediate despatch on account.)

## CMOS

These cut prices for Amateur Users and Export. Note: industrial users - quantity prices available.

Mostly Motorola, RCA			
4000	15p	4051	72p
4001	17p	4052	72p
4002	17p	4053	72p
4006	£1.05	4054	£1.10
4007	18p	4055	£1.28
4008	87p	4056	£1.34
4009	50p	4057	£25.70
4010	50p	4058	£4.80
4011	18p	4059	£1.15
4012	18p	4061	£15.67
4013	42p	4062T	£10.00
4014	86p	4063	£1.09
4015	89p	4064	N/S
4016	45p	4065	N/S
4017	89p	4066	57p
4018	89p	4067	£3.80
4019	48p	4068	22p
4020	99p	4069	20p
4021	91p	4070	23p
4022	86p	4071	21p
4023	20p	4072	21p
4024	65p	4073	21p
4025	19p	4075	23p
4026	£1.80	4076	85p
4027	45p	4077	23p
4028	81p	4078	21p
4029	99p	4081	20p
4030	58p	4082	21p
4031	£2.05	4085	74p
4032	£1.00	4086	73p
4033	£1.45	4089	£1.50
4034	£1.96	4093	63p
4035	£1.11	4094	£1.90
4036	£2.45	4095	£1.05
4037	£1.00	4096	£1.95
4038	£1.08	4097	£1.00
4039	£2.45	4098	£1.10
4040	£1.05	4099	£1.45
4041	80p	4061	N/S
4042	75p	40100	£2.50
4043	94p	40101	£1.51
4044	90p	40102	£2.12
4045	£1.45	40103	£2.12
4046	£1.28	40104	£1.09
4047	87p	40105	£1.06
4048	58p	40106	61p
4049	48p	40107	88p
4050	49p	40108	£5.36
40109	£1.02	40181	£3.39
40182	£1.40	40183	£1.40
40184	£1.40	40185	£1.40
40186	£1.18	40187	£1.18
40257	£1.48	40258	£1.48
4160	£1.08	4161	£1.08
4162	£1.08	4163	£1.08
4174	£1.08	4175	99p
4176	99p	4177	99p
4194	£1.08	4195	£1.08
4408	£6.59	4409	£6.59
4410	£5.73	4411	£5.73
4412	£5.00	4413	£5.00
4431	TBA	4432	£11.32
4433	£11.32	4434	£7.93
4435	£7.93	4440	£11.58
4450	£2.57	4451	£2.57
4452	£5.00	4453	£5.00
4431	TBA	4452	£10.55
4453	£3.87	4454	£1.19
4455	£7.9p	4456	£1.14
4457	£3.86	4458	£1.14
4459	£3.69	4461	£2.18
4462	£2.42	4463	£6.54
4464	£6.54	4465	£6.54
4466	£1.59	4467	£1.59
4468	£2.38	4469	£2.38
4470	£2.57	4471	25p
4472	25p	4473	69p
4474	£2.62	4475	£3.71
4476	£5.86	4477	£5.86
4478	76p	4479	76p
4480	43p	4481	43p
4482	£1.01	4483	£1.01
4484	£2.06	4485	£2.06
4486	£1.06	4487	£1.06
4488	£1.06	4489	£1.06
4490	£1.06	4491	£1.06
4492	£1.06	4493	£1.06
4494	£1.06	4495	£1.06
4496	£1.06	4497	£1.06
4498	£1.06	4499	£1.06
4500	£5.56	4501	17p
4502	91p	4503	69p
4504	£3.71	4505	£3.71
4506	£1.06	4507	55p
4508	£2.48	4509	£2.48
4510	99p	4511	£1.38
4512	81p	4513	£1.38
4514	£2.65	4515	£2.65
74C90	£4.38	74C91	£1.10
74C92	85p	74C93	£1.04
74C94	85p	74C95	£1.04
74C96	£1.04	74C97	£1.36
74C98	£1.22	74C99	£1.73
74C100	£4.12	74C101	54p
74C102	£2.46	74C103	54p
74C104	£3.67	74C105	54p
74C106	£2.20	74C107	54p
74C108	£1.10	74C109	54p
74C110	£1.10	74C111	54p
74C112	£1.10	74C113	54p
74C380	£1.10	74C381	54p
74C382	£1.10	74C383	5

# A HISTORY OF ELECTRONICS IN MEDICINE

THE USE OF ELECTRICITY FOR medical purposes dates back to the Ancient Greeks who used the electric eel to treat various maladies. In 1759 Wesley collected case histories of the use of electricity. The first recorded use of electricity for treatment in a hospital in London was in 1767.

Not quite 200 years ago, in 1786 to be precise, Professor Luigi Galvani — an anatomist at the University of Bologna, Italy — discovered by chance that the muscles of a dead frog contracted under the influence of an electrical quantity.

He wrongly assumed that animal electricity stored within the muscle caused this to happen. It was, in fact, the result of dissimilar metals forming a primary electric cell which energised the nerves of the muscle. Volta of the University of Paris proved it and subsequently gave the world the voltaic battery, in 1800.

The contribution of these two men provided, in the simple primary cell, a workable basis for using electricity in practical ways not previously possible with the electro-static form of electricity. Galvani's work on "animal fluid" was amongst the earliest electro-medical studies. The apparatus he used was crude by today's standards — see Fig. 1.



Fig. 1. Artist's idea of Galvani experimenting with frogs' legs on the left and the Leyden jar on the right (Funk and Wagnells).

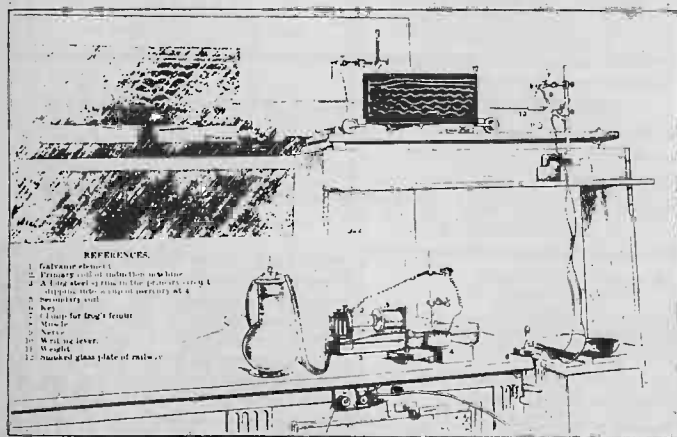


Fig. 2. Apparatus used by McKendrick to give lectures on life in motion to Royal Institution, London, audiences around 1890.

## Body Electric?

Research into physiological electric quantities gradually became more sophisticated as the 19th century passed. This development, however, had to wait for suitable experimental inventions such as the electromagnetic galvanometer which became available in its crudest form around 1830. A typical laboratory electro-medical instrumentation set-up of the 1890s is shown in Fig 2. A smoked glass plate moved steadily across the end of a mechanical pen secured to the end of a frog's leg muscle. The muscle was energised by high-voltage generated from a vibration induction coil which was energised by a chromate primary single cell of the Grenet kind. Smoked screen recorders are still in use today in some medical research measurements, blood flow parameters being one example.

The sphygmometrograph (as a pulse measuring instrument was known in that time) was originated by Marey in 1860. A later design by Verdin is shown in Fig 3. Electronic method was little used in medicine in early times, as powerful electric signal amplification was not obtainable until the beginning of the 20th century —

Electricity has long been used for medical purposes, here's the story of the past and a look into the future. By Peter Sydenham.

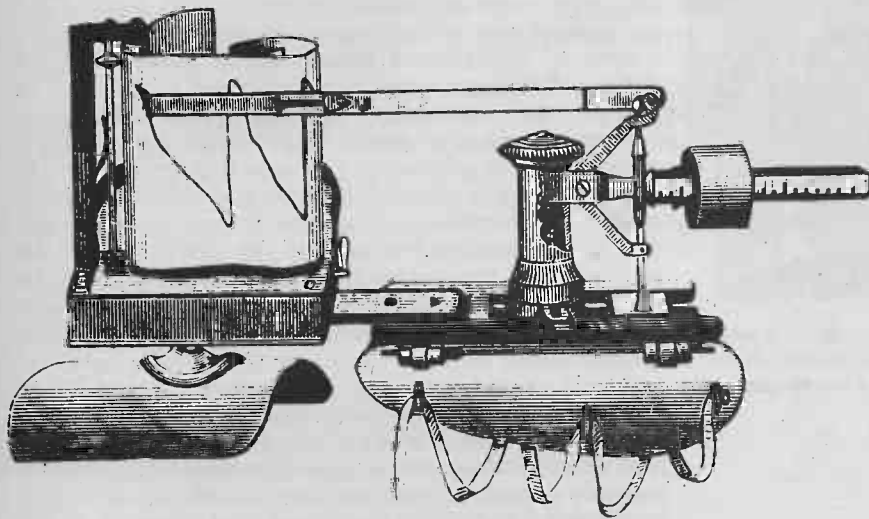


Fig. 3. Verdin's apparatus of the 1890s for recording action of the pulse.

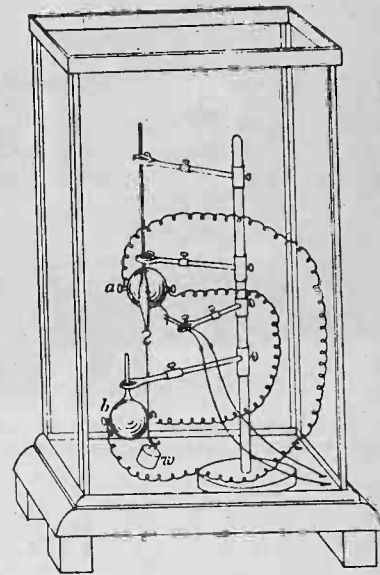


Fig. 4. Schematic of McKendrick's 1891 method for measuring heat generation in muscle.

when the thermionic valve was invented by Fleming (in 1904).

Figure 4 shows experimental equipment for measuring heat production of muscular contraction around 1880. Thermocouples, forming a thermopile, drive the crude galvanometer.

### Ion Therapy

Another aspect of medicine where electricity is used is for therapeutic treatment. Since the very early 1800s output of the various kinds of electric current generator, namely the Faraday induction coil, the galvanic chemical battery, the sinewave rotating generator and the friction statical generator have been applied to appropriate parts of the body to provide a cure for all sorts of ailments.

X-ray equipment was born in 1895 when Roentgen discovered X-rays in a chance situation using photographic plates. There is probably no case in instrument history where application was more rapid. Edison, and others, had equipment in use in hospitals within months. Figure 5 shows contemporary American X-ray plant of 1899.

Measurement and recording of heart performance also began around 1900. Professor Einthoven of Holland devised a rapid response, high sensitivity detection instrument in 1903 — the string galvanometer. Soon after this was coupled to a photographic recording system, by the Cambridge Instrument Co., to produce an electrocardiograph. The first installation of this was made in 1909. By 1945 cardiographs were available in portable form. Figure 6 shows the interior of a 1930s. Both Brothers portable electro-cardiograph invented and made in Adelaide, South Australia — possibly one of the first portable units devised anywhere. It used a loud speaker drive unit (right) to mark a rotating smoked disk.

The record was viewed by the physician using an optical magnifier. Amplification to drive the stylus from skin electrode signals was obtained by thermionic tubes.


As with all disciplines, electronic method opened the door to new accomplishments. In medical electronics it happened from the 1920s onward. Equipment for researching physiology at Oxford University, in 1949 is shown in Fig 7. The unit, advanced for its time, incorporated amplifiers, a temperature control unit, stimulators to induce responses, a time base and a cathode ray tube display unit.

Electronic equipment used in medicine has come a long way during the past 50 years. This can be seen by comparing the apparatus pictured above, which covers the 1800s to 1930s period, with modern equipment such as that used in pathological testing and nuclear medicine.

### Future

Against this background let me now suggest developments we can expect to experience over the next quarter century.

Fig. 5. Complete X-ray apparatus in use in America around 1900. Note the lack of safety devices and precautions.

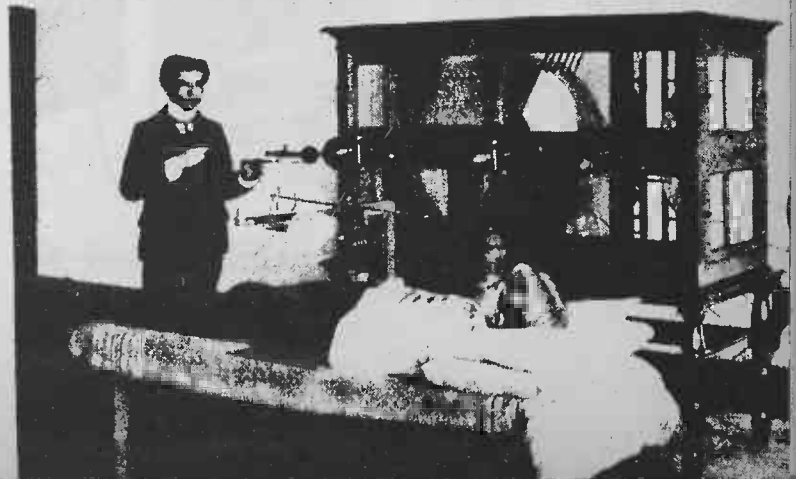



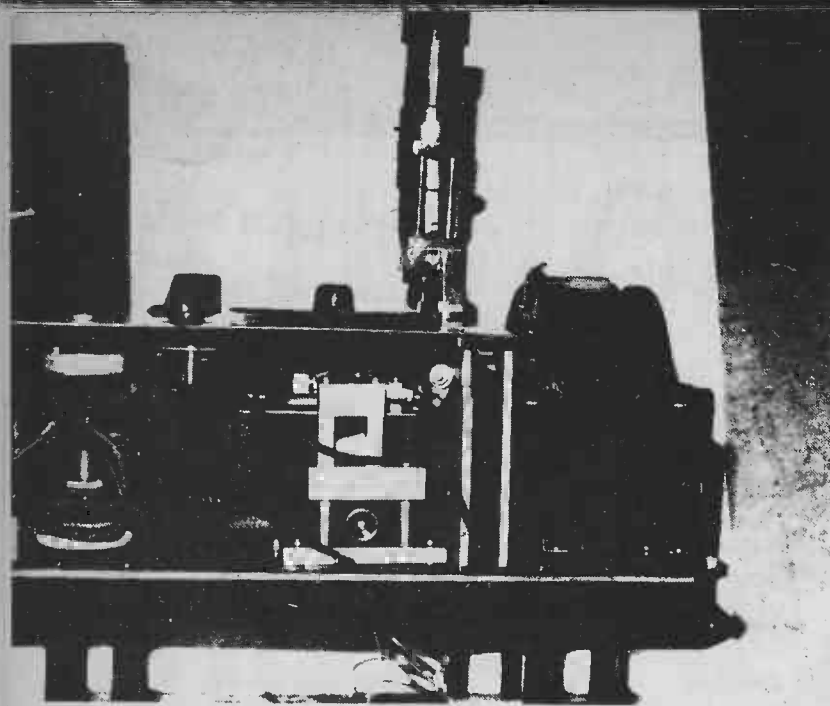


Fig. 6. Interior view of a Both portable electro-cardiograph machine made in Adelaide around 1930.

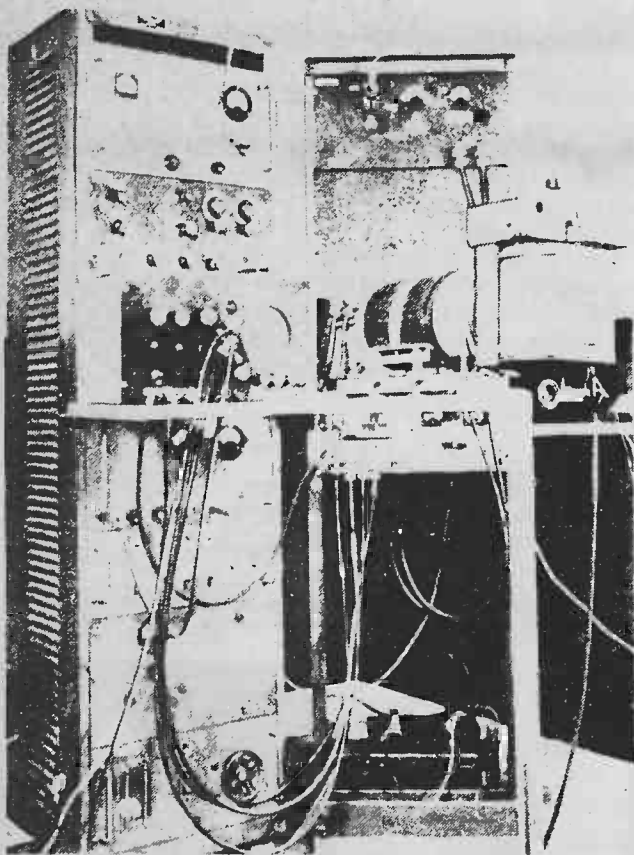


Fig. 7. E Electro-physiological research equipment used by Dickinson at Oxford University in 1949.

## Monitoring

The largest proportion of electro-medical equipment is concerned with measurement; for detection of abnormal states. At present comparatively few of the incredibly great range of medical measurements needed can be made in situ on the body and without disturbing its functions. Samples of tissue, blood, urine, etc. are removed for analysis in the pathological laboratory. This process, although performed faster today than ever before, can still take several hours before a diagnosis is available to the physician in order that he or she can decide corrective action. Analysers now exist that handle many measurements of a sample entirely automatically once the sample is loaded into the analyser. But the sample must first be extracted from the body and then be transported to the machine, processes which consume time and in some circumstances alter the sample from its original state.

It is realistic to expect the transport step to be eliminated in the future with most local clinics having their own units for analysis of samples. The next stage in progress will come about by the invention of units that measure parameters such as blood count, albumin, etc. by contact externally to a suitable vein or artery. Direct measurement like this would also provide more accurate measurement as the blood would be in its normal working state. Furthermore, it would then be possible rapidly to optimize drug dosage and to investigate changes in parameters as they happen. The concept of in-situ measurement will apply to numerous other tests.

In special cases some people have already been equipped with sensors of critical body parameters. The outputs are telemetered to a remote observer. Examples of this are in space-medicine, in fitness studies and in a few heart disease cases.

## Microbody

Considering the low-cost data processing power already available, and coupling this with inexpensive micro-miniature sensors we can expect to see developed in the future, it is possible that individuals will one day be able to obtain self-monitors that provide warning when body parameters exceed allowable limits.

Better measurements always leads to better control. As an example, respiratory tract problems, such as hay fever and asthma, are hard to combat effectively because of the lack of detailed data about each individual's characteristics in the various circumstances encountered. Not all people are allergic to the same pollens — we could benefit greatly if an easy way existed that determined the allergic pollens involved.

At present, a pollen count is usually taken by drawing the ambient air over a sticky surface for many minutes — hours sometimes. The surface is then observed with a microscope, the technician counting all pollen grains together to obtain the total pollen count. This process is now sometimes carried out using computer-controlled video TV camera systems, but the systems are still barely able to group the various kinds of pollen grain. (They are typically a micrometre in diameter or smaller — counts of a few grains per cubic metre can cause unwanted symptoms.)

A development that could help is a sensor that provides a virtually instant count of the individual kinds of pollen grain present — a real-time sampling analyser.

# news digest.....


## FLEET OF FOOT?



For all us kiddies (anyone who isn't — please leave now) this is a good idea. Those nasty sneaky MPUs have invaded our nice little game of Battleships. Based on a TMS 1000 the unit contains enough

RAM to hold the board as seen by both players, and make appropriate noises at time of defeat or victory or whatever. Nice explosion sound effects etc too. And what's more it's British designed — which

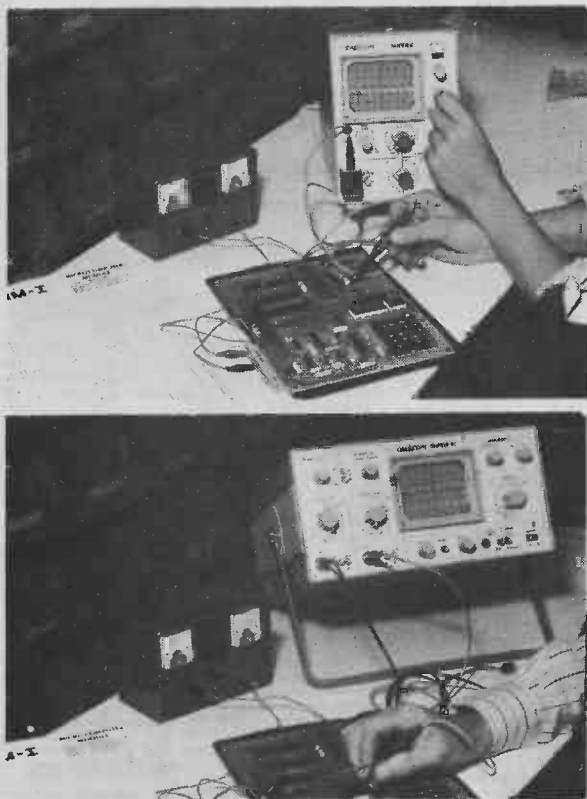is a distinct recommendation and selling well in America — which isn't. Price £29 or thereabouts. AID, 10 RATHBONE PLACE, LONDON W1P 2DN.



## NOT A TRACE OF GREED

Two new oscilloscopes for the home constructor, from the Scopex stable. Called the Calscope 6 and Calscope 10 they are probably indicative of the fact the home market is of growing importance to manufacturers. Specs. below.


**Calscope 6:** — single trace: sensitivity range 50mV to 50V per cm/in 12 ranges: Bandwidth 6MHz: time base range 1 and to 100 ms per cm. Time base triggering is claimed to be particularly good. Price £162.

**Calscope 10:** — dual trace: 10mV sensitivity: bandwidth 10MHz (displayable across full screen size): time base range 200ns to 100 ms: accuracy 3% all ranges. Price £219.

Both available from Maplin and Marshall both of whom you should know already.
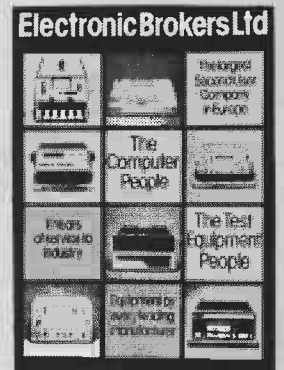
## PEDIGREE CATS

**Electronic Brokers** — superb range of second hand hardware that should interest most small firms and not a few individuals. Much new equipment is also included, and although the cost is high at £1 to private individuals companies can get it free!



Not fair this world is it? **ELECTRONIC BROKERS**, 4a PANCRAS ROAD, LONDON NW1 2GB.

**Ace Electronics** — good range of components. Poorly produced catalogue but it is free, and adequate, and contains some nice little kits amongst other things worth sending for **ACE MAILTRONIX** TOOTAL STREET, WAKEFIELD, W. YORKS.

## PUT THESE TO GOOD USE

Some new PUTs (at last), and in different packages too. The MEU21 and 2N6028 are intended for use in long internal timers and such and have low leakage (100nA max).

The MEU22 (and 2N6027) are general purpose types. All have specs of: 150nA peak point current (2N6028), low forward voltage (1V5 for 50mA  $I_{FWD}$ ) and high pulse output voltage (6V minimum) **MICRO ELECTRONICS LTD**, YORK HOUSE, EMPIRE WAY, WEMBLEY, MIDD.

With such a device the sufferer could test for the hostile situation *before* symptoms arise and take remedial action in time. Technologically such an instrument appears feasible. It is, however, cost and physical size that holds up its development and its practical everyday use at present.

A likely parallel already existing is the Coulter counter that analyses the size and number of cells in a blood sample. Blood-cell counting of several years ago required the blood to be smeared on a microscope slide and the cells counted by eye under a microscope. Today the machine makes the measurements in a few seconds by counting particles as they pass a small orifice — but it is neither portable nor inexpensive. Figure 8 shows a Coulter counter installation as used in the larger pathological laboratories.

Development of personal monitors will almost certainly pass first through a telemetry method in which a central computer processes the data, perhaps with the help of the trained physician to begin with. A direct self-contained method will then be developed in which the specific data processing requirements that have emerged from experience, are integrated into the unit.


## Sensors

The human body is a vastly complicated chemical process plant. It has sensors feeding information to the brain for central processing. In turn, the brain sends signals to actuators — the muscles which cause the body to function and to do work. Nerves are the hardwired data channels for receiving and sending control information.


Slight deficiencies in the senses of sight and hearing have been aided using instruments — spectacles and hearing aids. The latter began as acoustic horns which provided sound pressure gain without active amplification. The advent of the telephone led to amplifierless hearing aids in the 1900's which used several mouth-pieces coupled to the ear pieces (Fig 9). Then came electronic units which provided active signal gain from miniature thermionic tubes. Today we have integrated semi-conductor circuitry. We have still a way to go, however, before we are able to compensate for a failed action of the inner ear mechanism.

Vision, until very recently, was aided only by optical lens compensation. But this applies only where the eye is still largely operative as an optical-to-electrical transducer. Quite recently experiments have been reported in which a miniature video camera provides electronic signals that drive cells in the brain to provide illusion of sight. The method is still crude compared with the performance of natural process. Given time for research it seems reasonable to assume that quite compact and useful artificial eyes will soon be available for blind people. Bionic man is not so fantastic! Interestingly, once the bionic eye is developed it is an easy matter to provide greater than natural visual acuity and to offer sensitivity to other than the visible light band — infra-red for instance.

Providing electronic replacements for the sense of smell will most likely be a much later development. We know too little about the olfactory senses and have no really compact and cheap smell sensors at this time to expect great progress to occur in the near future.

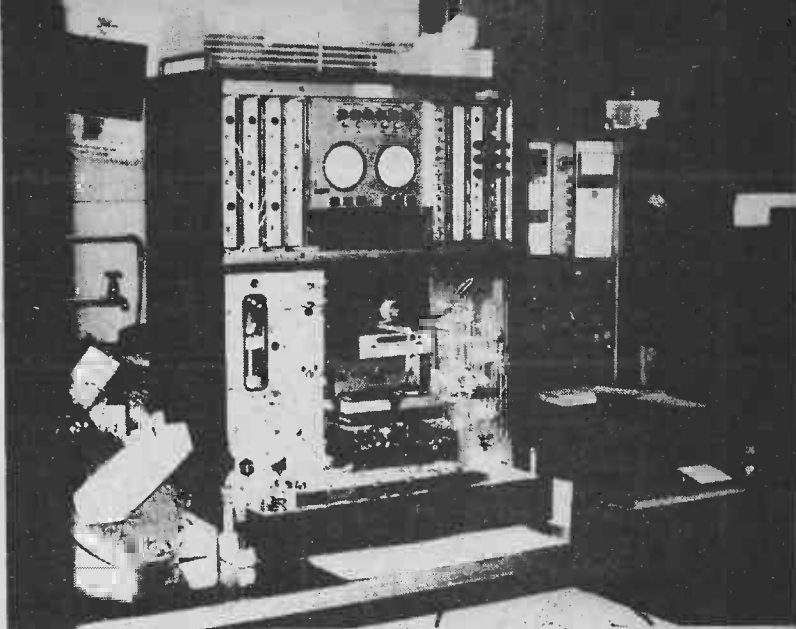

**Fig. 8. Coulter counter unit of today that analyses blood sample particles providing a printout (IMUS, Adelaide).**

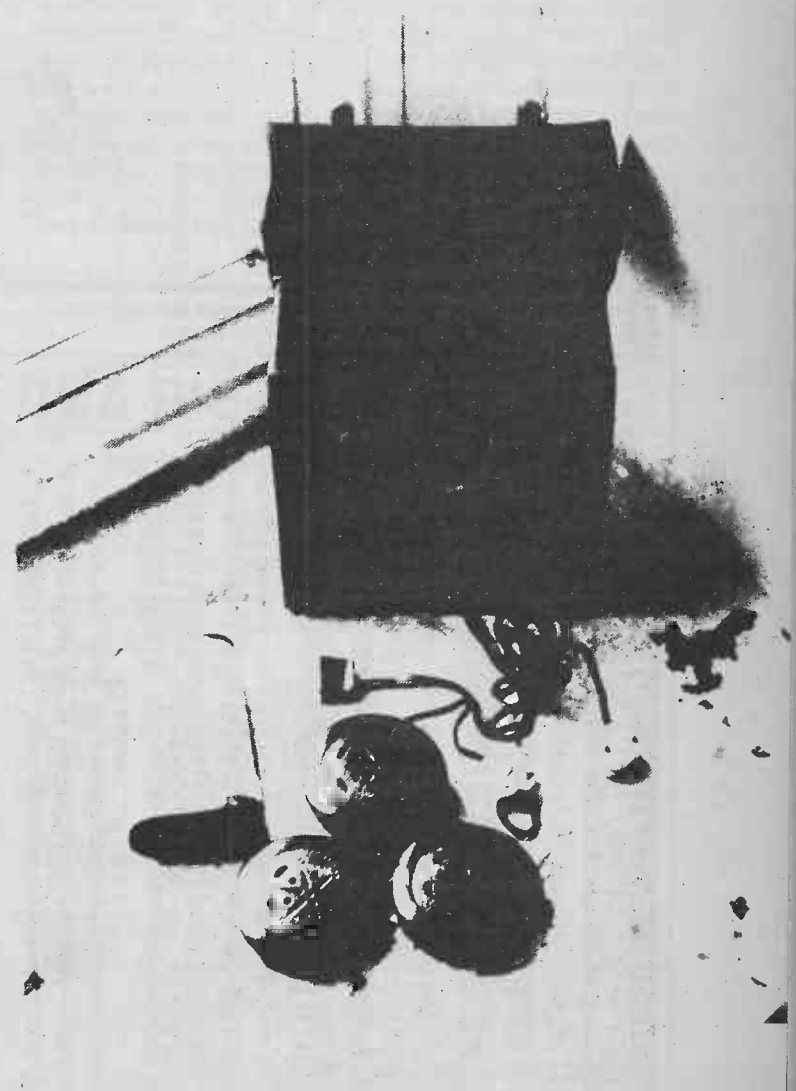

**Fig. 9. 1900's hearing aid. The three receivers, which fit into the case, provide signal to the two earpieces. No active amplifier was involved. (Birdwood Mill Museum, S.A)**

# FEATURE: Electronics in Medicine

Animals, such as dogs, possess a sense of smell vastly much more sensitive than humans. Ants track each other by a scent trail! Yet man has not yet produced small and inexpensive chemical analysers (smell is a largely chemical process) that can meet the complex sensing requirements of smell detection.

## Scanners

X-ray and nucleonic diagnostic methods have the valuable feature that certain internal structures of the body can be seen. But all such methods lack the spatial resolution we obtain by visual examination with the unaided eye or through a microscope. A nuclear radiation source set-up within the body provides a rather diffuse output picture. Resolution is improved by increasing the number of individual elements at the sensing stage. The gamma camera, for example, provides two-dimensional pictures using over thirty scintillometers connected in such a way as to provide many more picture elements. The latest development senses the body area by scanning multiple sensors thereby collecting yet more data in a given time. Sophisticated processing is then used to provide video screen outputs which contain much more useful information than ever before. Similar techniques apply to X-ray, nucleonic and ultrasonic signal transmission. Now that vastly more powerful data processing capability exists the future development will be to incorporate many more sensors of the same kind and make more effective use of three-dimensional data. Other variables, such as, say, thermal emission will also be incorporated along with systematic experience gained in the processing, all this to providing data conversion for a more meaningful measurement process.

## Surgery

Electrical methods in surgery traditionally include endoscopes with which to see into inaccessible places and cauterizing probes for sealing blood flow, cutting and destroying cells where need be. The recent introduction of the laser as a cutting tool has most valuable properties. Selection of the appropriate wavelength decides which kind of body tissue will be cut. For example, it is possible to weld the retina of the eye through the pupil without need for surgery. The radiation is only absorbed by retinal material, the pupil and fluid of the eye ball being transparent to the wavelength used.

The selective property of narrow-band radiation will enable some highly precise surgical operations in the future. An operation might go as follows: a rigid framework holds the patient fixed with respect to an x-y-z translating pulsed laser operating head. Wired to the control unit of the translator are electrodes fixed to the body. These sense when low-power sensing pulses are energising the specific part of the body required to be operated upon. The unit scans until sensing signals (operated by a non-cutting wavelength source) verify the location of the beam. Once at such a point the laser is switched to full cutting power continuing to cut as the time-multiplexed sensing signals indicate position is satisfactory.

Looking back, electro-medical apparatus has only been with us for a mere 50 years. In the last 10 years of that time we developed inexpensive and very powerful data processing methods. The next 25 years are likely to unfold regardless of aids to medicine many of which we would regard as miraculous if we heard about them today.

ETI

<b>STRUTT ELECTRICAL AND MECHANICAL ENGINEERING LTD.</b>		<b>3C, Barley Market St. Tavistock, Devon PL19 05F.</b>		<b>TAVISTOCK 5439 TELEX 45263</b>					
<b>BUY BIG AND SAVE ££££££</b>									
<p><b>Transistor 1+25+100+</b></p> <p>BC107 .09 .095 .068 BC107A/B .10 .095 .075 BC108 .09 .085 .068 BC108A/B/C .10 .095 .075 BC109 .09 .085 .068 BC109B/C .10 .095 .075 BC147A/B .12 .104 .088 BC149 .12 .104 .088 BC157A/B .13 .114 .108 BC169C .08 .073 .057 BC172B .09 .08 .076 BC177B .14 .125 .106 BC178A/B .16 .137 .115 BC187 .24 .217 .182 BC213/B .09 .08 .057 BC227 .12 .104 .088 BC238A/B .10 .081 .069 BC238C .12 .104 .088 BC238D .11 .091 .077 BC237 .11 .091 .077 BC338 .11 .095 .077 BC516/7 .23 .205 .173 BC547A/B .10 .081 .069 BC548 .11 .091 .077 BC549 .10 .081 .069 BC556 .14 .119 .101 BC557A/B .11 .091 .077 BC558 .13 .112 .094 BC559/B/C .11 .091 .077 BC570/B .17 .148 .125 BC570A/B .19 .171 .144 BC578 .15 .133 .109 BC579 .15 .133 .109 BF224 .16 .14 .118 BF241 .16 .14 .118 BF248 .21 .188 .158 BC257 .30 .273 .23 BF258 .31 .285 .24 BF337 .32 .285 .24 BF339 .16 .146 .123 BF340 .16 .142 .12 BF341 .16 .146 .123 BF342 .16 .146 .123 BF343 .15 .133 .112 BF344 .16 .146 .123 BF345 .29 .252 .221 BF346A/B .29 .252 .221 BF347 .28 .25 .211 BF350A/B .27 .237 .20 BU105 .125 .113 .955 BU106 .16 .144 .121 BU205 .133 .121 .1019 BU206 .16 .144 .1219 CU509 .42 .38 .32</p>	<p><b>Transistor 1+25+100+</b></p> <p>MU340 .74 .703 .555 MPS340E/6 .21 .182 .154 MPS341E .26 .228 .192 MPS345E .21 .182 .154 R2008B .150 .134 .1136 R2008C .127 .114 .968 TIP29 .33 .305 .258 TIP29A .36 .323 .272 TIP29B .39 .351 .296 TIP29C .43 .387 .326 TIP30 .36 .323 .272 TIP30A .38 .34 .286 TIP30B .41 .37 .312 TIP31B .43 .389 .328 TIP31C .48 .427 .36 TIP32 .40 .357 .301 TIP32B .45 .41 .346 TIP32C .50 .45 .379 TIP33C .74 .668 .563 TIP34 .65 .587 .494 TIP34A .69 .619 .522 TIP34B .75 .674 .568 TIP35B .150 .135 .138 TIP35A .148 .133 .133 TIP36B .163 .146 .125 TIP41A .54 .48 .405 TIP41B .79 .714 .502 TIP41C .54 .575 .485 TIP42A .56 .503 .397 TIP42B .61 .551 .435 TIP42C .67 .604 .477 TIP50 .14 .119 .101 TIP51 .15 .136 .115 TIP52 .25 .218 .178 TIP58 .38 .342 .288 TIP59 .26 .235 .196 TIP132 .30 .269 .227 TIP133 .21 .19 .16 TIP217 .27 .237 .20 TIP218 .36 .321 .27 TIP219 .34 .304 .256 TIP219A .30 .266 .224 TIP219B .28 .25 .211 TIP219C .39 .347 .293 TIP221 .27 .237 .20 TIP221A .21 .182 .154 TIP221B .18 .159 .134 TIP222A .35 .296 .251 TIP222B .18 .159 .134 TIP222C .34 .304 .256 TIP223A .19 .171 .144 TIP223B .29 .255 .218 TIP223C .33 .294 .248 TIP223D .35 .317 .267 TIP2906 .22 .191 .162</p>	<p><b>Transistors 1+25+100+</b></p> <p>2N205A .21 .19 .16 2N2907 .18 .159 .134 2N2907A .21 .19 .16 2N3053 .25 .222 .187 2N3055 .50 .411 .343 2N3702/3/4 .09 .079 .067 2N3705/7/9 .10 .083 .07 2N4028 .09 .071 .144 2N3820 .59 .526 .443 2N3823 .66 .594 .501 2N3903 .09 .081 .069 2N3904/5 .16 .144 .188 2N3906 .17 .148 .125 2N4036 .32 .285 .24 2N4037 .29 .262 .221 2N4058 .10 .091 .077 2N4059 .09 .077 .066 2N4060 .11 .093 .078 2N4061 .10 .091 .077 2N4062 .11 .088 .083 2N4123 .10 .067 .074 2N4124 .31 .273 .23 2N4125 .11 .095 .08 2N4126 .30 .267 .226 2N4226 .31 .273 .23 2N4229 .130 .118 .995 2N4232 .13 .114 .096 2N4233 .10 .091 .077 2N4234 .33 .298 .251 2N4235 .48 .433 .365 2N4236 .10 .091 .077 2N4237 .39 .35 .291 2N4238 .58 .52 .438 3N201 .58 .52 .438 RC403347 .92 .828 .698 RC403360 .45 .40 .34 RC403361 .47 .423 .357 RC403362 .50 .452 .381 RC403363 .59 .53 .447 RC403364 .92 .828 .698 RC403365 .77 .689 .581 RC403366 .94 .849 .716 955 .805</p>	<p><b>Transistors 1+25+100+</b></p> <p>4024B .93 .836 .704 4025A .19 .171 .144 4025B .45 .399 .336 4025C .84 .76 .64 4028A .120 .180 .912 4028B .45 .399 .336 4028C .118 .106 .896 40428 .86 .778 .656 40438 .80 .722 .608 40448 .80 .722 .608 40508 .44 .399 .336 40518 .124 .112 .944 4052A .19 .171 .144 40718 .19 .171 .144 40988 .167 .151 .1272 40998 .44 .399 .336 7040 .16 .144 .122 7401 .19 .167 .141 7401A .21 .182 .154 7403 .19 .167 .141 7404 .16 .144 .122 7405 .20 .178 .15 7406/7 .27 .239 .202 7409 .20 .178 .15 7410 .16 .144 .122 7411 .21 .19 .15 7412 .22 .195 .165 7413 .32 .288 .243 7416 .24 .216 .182 7417 .24 .216 .182 7420 .16 .144 .122 7421 .31 .285 .225 7422 .46 .416 .351 7425 .21 .19 .16 7430 .16 .144 .122 7431 .18 .155 .131 7432 .20 .18 .152 7437 .16 .144 .122 7441 .74 .665 .56 7442 .44 .392 .33 7443 .40 .355 .299 7448 .32 .285 .24 7450/1/3 .19 .167 .141 7454/50 .19 .167 .141 7470/2 .34 .30 .253 7470/4 .25 .222 .192 7476 .31 .273 .23 7480 .36 .321 .27 7481/2 .57 .513 .432 7483 .31 .273 .23 7484 .45 .40 .338 7486/90 .20 .178 .15 7491A .20 .178 .15 7492 .31 .275 .232</p>	<p><b>TTL 1+25+100+</b></p> <p>7493 .20 .178 .15 7494 .40 .355 .299 7495 .23 .205 .173 7496 .34 .307 .259 74107/9 .35 .313 .264 74118 .89 .803 .677 74122 .44 .393 .331 74123 .42 .38 .32 74130 .105 .95 .85 74135 .45 .399 .315 74137 .25 .222 .187 74145 .36 .321 .27 74150 .45 .40 .338 74151/3 .29 .258 .218 74156 .36 .321 .27 74157 .29 .258 .218 74161/3/4 .36 .321 .27 74167 .126 .114 .963 74174 .54 .488 .411 74180 .40 .355 .299 74181 .99 .893 .752 74182 .40 .355 .299 74191 .31 .279 .235</p>	<p><b>DIL Sockets 1+25+100+</b></p> <p>8 pin .13 .112 .094 14 pin .14 .125 .104 16 pin .16 .138 .116 18 pin .22 .193 .163 20 pin .23 .203 .171 22 pin .26 .224 .188 24 pin .25 .223 .196 26 pin .34 .307 .259 40 pin .49 .437 .368</p>	<p><b>Diodes</b></p> <p>8A113 .02 .016 .014 8A113C .045 .04 .034 8A113D .05 .04 .036 8A113E .05 .043 .037 8A113F .055 .046 .039 8A113G .055 .048 .04 8A113H .06 .051 .044 8A113I .06 .055 .047 8A113J .02 .015 .013 8A113K .02 .016 .014</p>	<p><b>Zeners</b></p> <p>BZ78C Series .07 .055 .047</p>	<p><b>Capacitors 1+25+100+</b></p> <p>Electrolytic 10v 220uf .075 .066 .052 25v 100uf .08 .072 .061 25v 47uf .09 .076 .066 25v 100uf .14 .124 .104 25v 100uf .27 .237 .187 50v 1.5 6.8 2.2 3.3 4.7 1.2 .106 .089 10uf 15uf .12 .107 .09 22uf .14 .121 .102 47uf .17 .147 .124</p>	<p><b>Resistors 1+25+100+</b></p> <p>Carbon Film 5% E12 1/4watt .015 .01 .009 1/2watt .02 .014 .012 1watt .05 .038 .032 Trim Pots Type 90 single turn e3 trimmer, horizontal or vert in case 10k-2M .32 .285 .24 Type 94 20 turn 4 pin pin E3 50R-1M .68 .60 .51</p>
<p><b>Bridge Rect.</b></p> <p>2A50V .38 .342 .288 2A100V .42 .38 .32 2A200V .47 .418 .352 2A400V .59 .532 .448</p>									
<p><b>LEDs</b></p> <p>TL209 .17 .152 .128 TL212-1 .21 .186 .156 TL216-1 .21 .186 .156 TL220 .16 .14 .118 TL222 .23 .207 .174 TL223 .23 .207 .174 TL232-1 .21 .186 .156</p>									
<p><b>Film Roll</b></p> <p>001 .0015 002 .15 .135 .113 003 .16 .138 .116 015 .022 .17 .152 .128</p>									
<p>VAT 8% 25p P&amp;P on orders under £10, all other orders carriage will be invoiced, to PD rates. Callers Welcome. All components new and to full spec. Send SAE for full list. We operate a mixed pricing system on semiconductors of the same group. Example: 10 X 7400, 10 X 7411, 30 X 7412, 50 X 74156 = 100 items. You will be charged the 100+ price.</p>									



# DIGITAL DIAL

**Most AM radio dials are pretty hopeless — especially portables and car radios. This application of our counter module can be a decided improvement.**

WITH MODERN RADIOS which are designed to be operated anywhere in the world, the local station call signs are no longer marked on the dial. Instead the dial is marked with frequencies making it more universal. Unfortunately the scaling on many receivers leaves a little to be desired, with many car radios lucky to have 3 or 4 markings. The use of pushbutton selection helps but when a cassette is fitted or you are out of your local area there is still the problem of knowing to what station you are tuned.

This project gives a direct readout of the station being received allowing for easy identification and selection. The display is remote from the receiver allowing it to be mounted on the dashboard for easy viewing.

## Design Features

This project is the first to employ our four digit module presented elsewhere in this issue. We will be using the module again over the next few months so don't lose track of it!

If this device is to be used outdoors i.e. in the car, it is recommended that high brightness displays, such as the Hewlett Packard HDSP 4133, be used. As these have a different pin-out a new display board is presented in this article.

The theory of operation is that we actually measure the frequency of the local oscillator in the radio and subtract the IF frequency. While we could have subtracted this using digital logic we chose to do it by resetting the display not to zero but to 9545 (10 000-455). The first 455 pulses in the timing period are then used getting to zero and in effect, only pulses after this are counted and displayed. This number can be loaded into the counter by

selecting the appropriate diodes and using the "load counter" input instead of the reset line. The only difference is that as the data is entered into the counter serially the pulse used must be longer than 4 times the internal oscillator period. Also as the LC input is a three state input it cannot be driven by conventional two-state.

## Out of Tune

We initially tried capacitive coupling onto the tuning capacitor of our portable radio (oscillator section!) but the loading detuned the set too much. We then tried a pickup coil and found enough signal with it in the correct place not to require any electrical connection to the set. With



## SPECIFICATION

Frequency range	500-1700 kHz
Accuracy	± 5 kHz
Sensor	pickup coil or direct connection
Power supply	7-20VDC @ 80mA or 240VAC
Display	4 digit LED

# PROJECT: Digital Dial



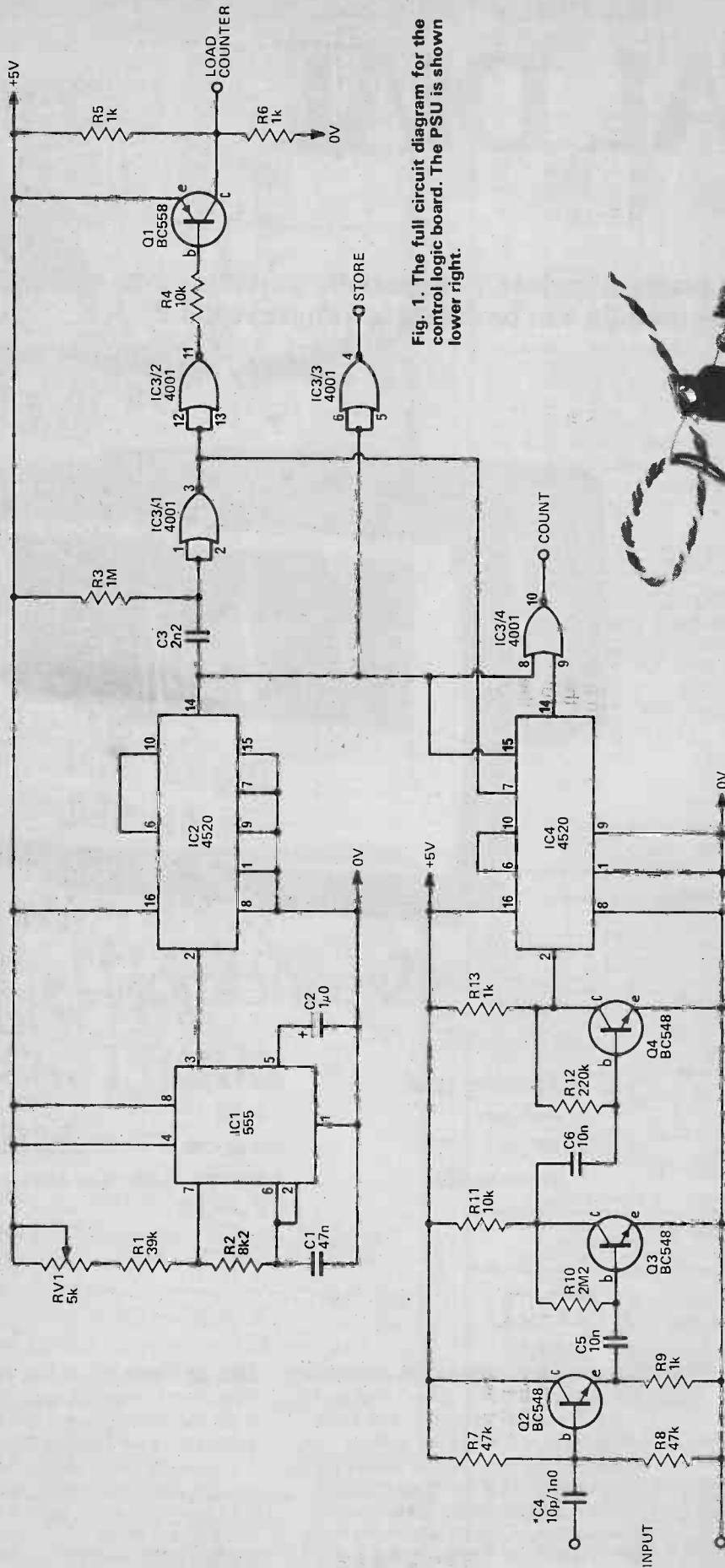


Fig. 1. The full circuit diagram for the control logic board. The PSU is shown lower right.

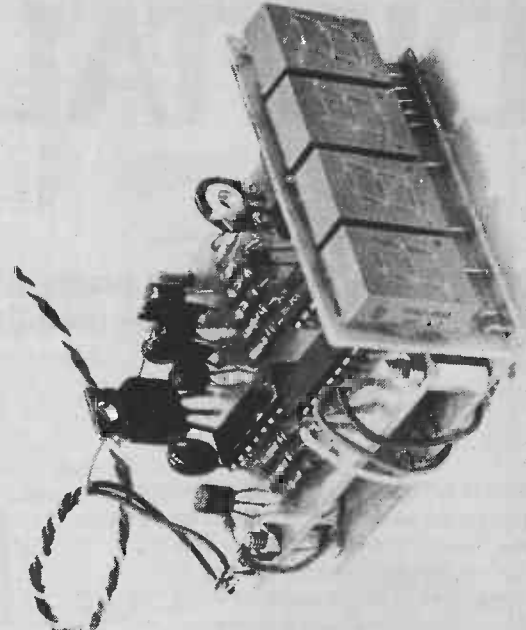

The photo to the right shows the module with the HP 5082-7663 displays. Suitable displays and their light outputs are given below.

Type	Colour	Size	Light output
HDSP 4133	yellow	10.9 mm	2100 $\mu$ Cd @ 20mA
HDSP 3733	red	10.9 mm	1800 $\mu$ Cd @ 20mA
5082-7663	yellow	10.9 mm	1500 $\mu$ Cd @ 20mA
5082-7653	red	10.9 mm	1720 $\mu$ Cd @ 20mA
DL704	red	7.6 mm	320 $\mu$ Cd @ 25mA

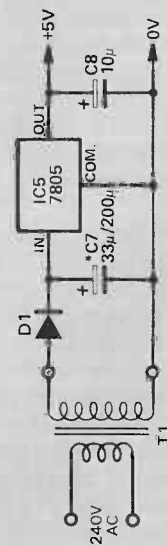

## HOW IT WORKS

A signal from the local oscillator in the tuner is picked up either by a pickup coil or by direct connection to the set. It is then amplified by Q2-Q4 to give a square wave on the collector of Q4. The gain of this amplifier is about 250 (48 dB). The frequency of this signal will vary from around 1 MHz to about 2 MHz and this signal is then frequency divided by 256 (2<sup>8</sup>) in IC4. This is used to clock the display module.

To measure the frequency we have to count the number of these pulses for 256/1000 seconds (256 because we divided the input by 256 and 1000 as we want a 1 kHz resolution). We used a 555 oscillator for the time base and its output is also divided by 256 (by IC2). This improves the stability of the time base by averaging out any short term variations in the 555 frequency.

The output of IC2 is a symmetrical square wave and when the output goes low a 1.5 ms wide pulse is generated by R3, C3 and IC3/1. This is inverted by IC3/2 which turns Q1 on for the 1.5 ms period. Two resistors are used to bias the output of Q1 to 2.5V to ensure that the three level input will work.

This pulse "loads" 9545 into the counters (in the display module). Counting now starts from this number and after 455 pulses it is passing through zero. 256 ms after the load pulse ended the output of IC2 goes high. This resets IC4 back to zero, inhibits any further clocking via IC3/4 and opens the latches via the strobe line allowing the total in the counter to be displayed. 257.5 ms later when the output of IC2 goes low again, the store is closed, the counter is once again preset to 9545 with the process starting again.

**Right: full site foil patterns for the Digital control board. Refer to the module article for details of those PCBs. Not shown here i.e. the two display boards and the third for high brightness seven segment types.**

the car radio however the coils are shielded so well that reliable operation was not possible. However it was found that we could tap onto one side of the oscillator coil without affecting the operation.

We use a NE55 as the time base with its output being divided by 128 to improve stability. However if an accuracy of  $\pm 5$  kHz is to be maintained its frequency has to be better than 1/4% and a polystyrene capacitor for C1 and 2% resistors for R1 and R2 are recommended.

### Construction

The display board should be built according to the overlay in Fig. 4 which shows which diodes are required. Note that R1, 2 and C1 are not used in the display module and a link is used in place of R1.

The control card can now be assembled and wired to the display module. The two boards are

mounted one above the other using 9.6 mm spacers. Check that these screws do not touch any tracks and insulate them if too close.

Depending on whether the unit is going to be used with a car radio or portable the values of C4 and C7 will vary. The pickup coil is made by winding about 80 turns of 0.25 mm enamelled wire onto a 25 mm long piece of 10 mm ferrite rod with the end terminated onto a twisted pair of plastic covered wires long enough to go between the radio and the position of the display. Do not use coaxial cable for this as the capacitance is too high.

The case chosen has been left to the individual with our own being from a discarded digital clock. If you use the 240 V powered version be careful with the high voltage wiring. For the 12 V version the power can come from the radio via a twisted lead (3 wires).

When connecting into a car radio, tune the set to a local station and try the pickup wire on the terminals of the tuning coils in turn until one is found which will give a reading without moving it off station.

Permanently connect to this point. With a portable radio try moving the pickup coil around the set, probably in line with the aerial coil, until the best results are obtained.

### Calibration

Place the pickup coil in position such that reliable operation is obtained and tune to a known station (preferably near the top end of the dial). Now adjust RV1 until the digital dial agrees with that station. Check then with other stations.

Alternatively feed a known signal of between 1 and 2 MHz from an oscillator into the input and adjust RV1 until it reads 455 less than that frequency.



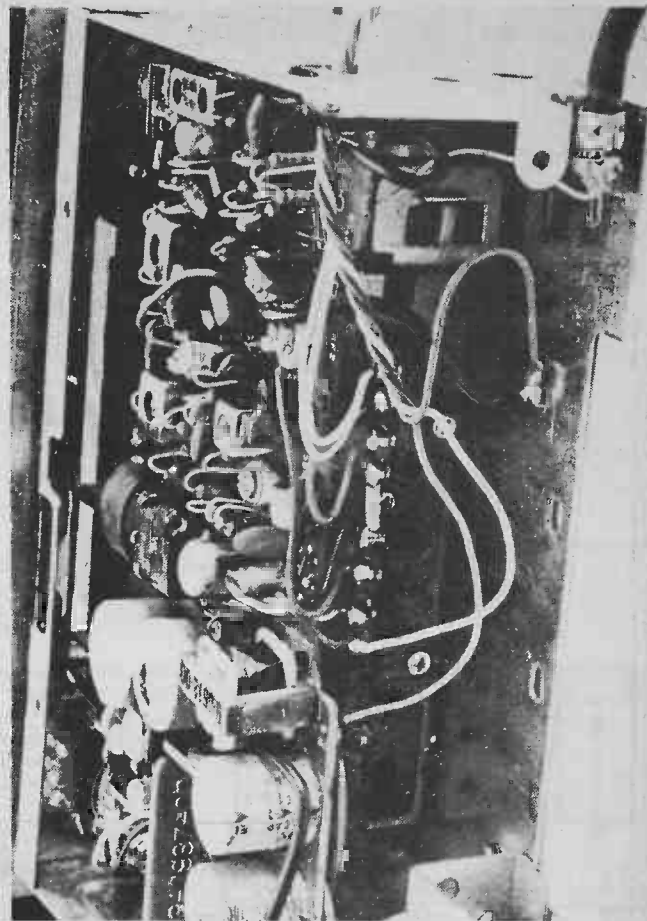


Photo showing where we tapped into the car radio.

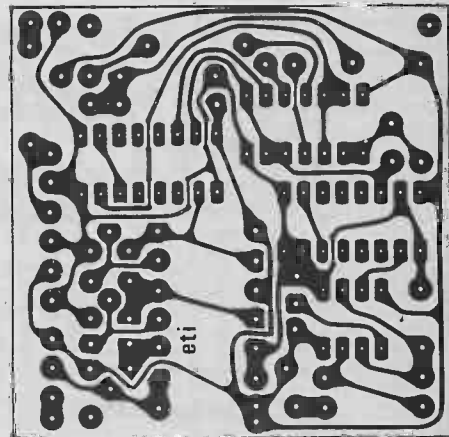

# PROJECT: Digital Dial

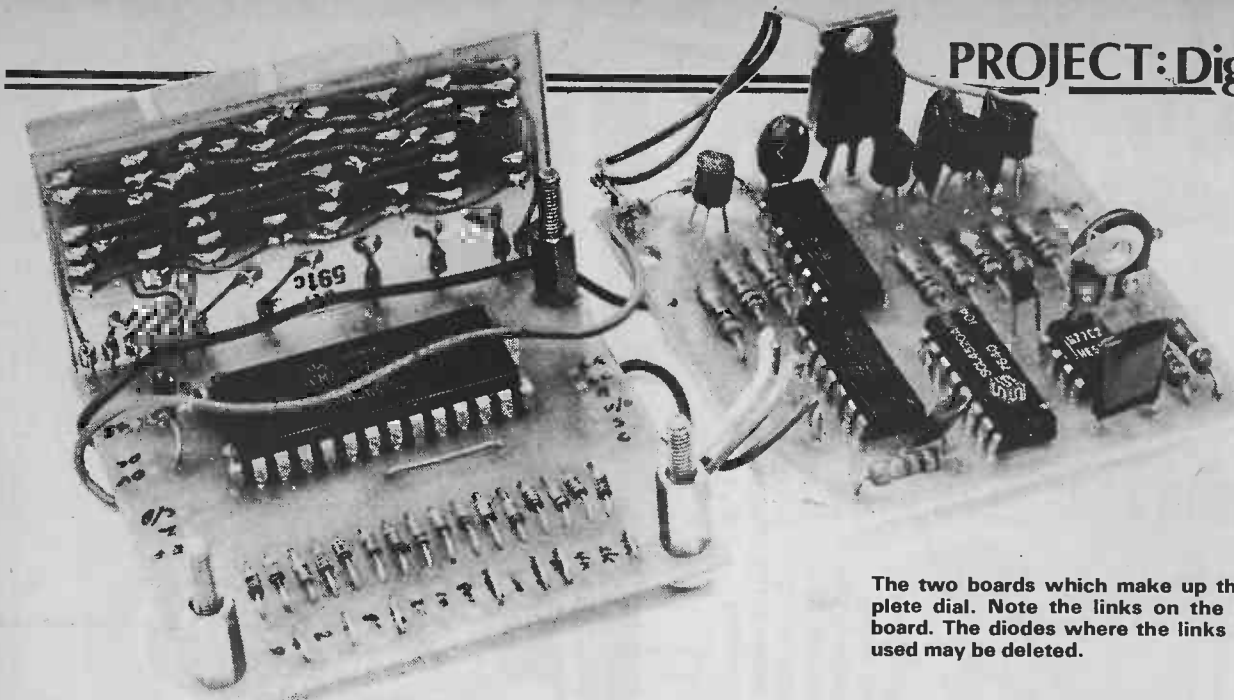

The two boards which make up the complete dial. Note the links on the display board. The diodes where the links are not used may be deleted.

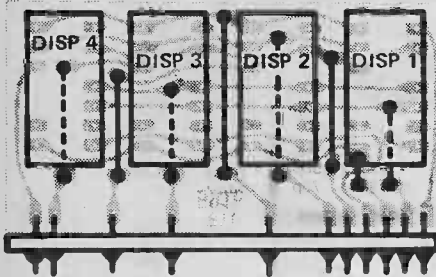


Fig 3(a) The overlay for the display board employing the high brightness displays. (b) Below that (left) the control board overlay.

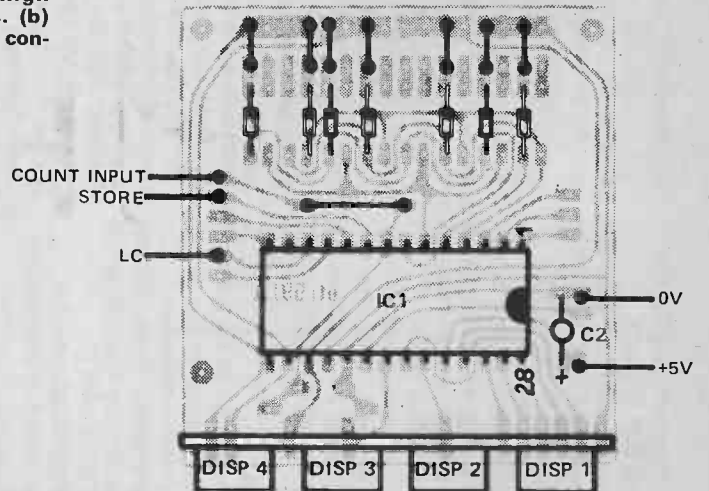
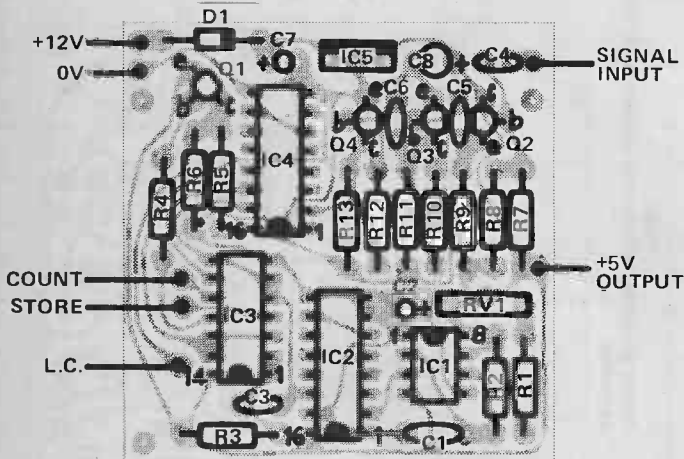


Fig. 4. The component overlay of the display module showing the diodes and links required.

## PARTS LIST

RESISTORS	all 1/2W, 5%	*C7	33u tantalum
R1	39k	C8	10u 25V electrolytic
R2	8k2	SEMICONDUCTORS	
R3	1M	IC1	555
R4, 11	10k	IC2	4520
R5, 6, 9, 13	1k	IC3	4001
R7, 8	47k	IC4	4520
R10	2M2	IC5	7805
R12	220k	Q1	BC558
POTENTIOMETER		Q2-Q4	BC548
RV1	5k trimmer	D1	1N4004
CAPACITORS		MISCELLANEOUS	
C1	47n polystyrene	*Transformer 240V-12V6, 150 mA	
C2	1u0 tantalum		
C3	2n2 polyester		
*C4	10p ceramic		
C5, 6	10n polyester		
		*For 12 V operation delete transformer.	
		For 240 V version C7 should be 220u	
		25 V. For use with pickup coil increase	
		C4 to 1n0.	

## BUYLINES

Any displays mentioned here are of course suitable and should be easily obtainable. The semiconductors are all available from Technomatic, or indeed from most other mail-order suppliers.

### Power Supply

The unit can be powered by an AC or DC voltage of between 7 and 20 volts. If an AC voltage is used the capacitor C7 should be increased to 220 u. A 240 V to 12V6, 150 mA transformer is recommended. **ETI**



# DATA SHEETS EXPLAINED

The data sheets which we publish regularly are very popular, but from time to time we receive requests for a fairly simple explanation of the terms and abbreviations which one finds in semiconductor device data sheets, and so here it is!

THE INFORMATION contained in semiconductor device data sheets is often grossly misunderstood. Great care must be taken to ensure that the exact meaning of a term or abbreviation is clear. As an example, we can quote the following conversation which actually occurred between two people who should both have known better.

A representative of a semiconductor distributor was showing data on a new power device to a lecturer. The lecturer said that the device data was wrong, since the maximum collector current was quoted as 12A and the maximum collector-emitter voltage ( $V_{CE0}$ ) as 80V; this is a power level of  $12 \times 80 = 960W$ , but the maximum permissible dissipation quoted in the data sheet is only 90W. The representative could provide no answer!

The data was, of course, perfectly correct. The problem arose because neither of the people concerned had appreciated the exact meaning of  $V_{CE0}$  which signifies the collector-emitter voltage *with the base open circuited*. Under these conditions (with zero base current) the collector current will be very small and the power dissipation in the transistor will also be quite small. Thus there is a great deal of difference between  $V_{CE}$  (the collector-emitter voltage under any conditions) and  $V_{CE0}$  (the collector-emitter voltage with the base open circuited). If still more information is required, one must look into the SOAR (Safe Operating Area) graph to ascertain the regions of the collector voltage/collector current curve where the device can be safely operated for limited or unlimited times.

This is a very simple example of the pitfalls one can encounter if one does not really understand the exact meanings of the terms and abbreviations used in data sheets. Such misunderstandings are very common, but not (we hope!) amongst the devices covered in our data sheets, since it is equally important that our readers understand the exact meanings of abbreviations used in data sheets on relatively simple devices such as ordinary diodes and transistors.

## Letter Symbols

Three of the most important symbols used in semi-conductor device data sheets are V, I and P for voltage, current and power respectively. Various subscripts are added to these three letters to indicate the electrode(s) to which the symbol is being applied and possibly certain circuit conditions. Some of the most commonly used subscripts are listed below.

A	anode
AV	average
B	base
BO	breakover
BR	breakdown
C	collector
D	drain or delay
E	emitter
F	forward
G	gate
H	holding
I	input
J	junction
K	cathode
M	peak value of a quantity
O	open circuit or output

R	reverse or repetitive
S	source, short circuit, series or shield
T	in the on state (that is, triggered)
W	working
X	specified circuit
Z	impedance

## Order of subscripts

In most cases more than one subscript is needed; the subscripts are usually placed in a definite order governed by the following rules:

The first subscript indicates the electrode at which the current or voltage is measured.

The second subscript denotes the reference terminal or circuit mode. (This subscript is often omitted if it is felt no ambiguity will arise.)

The letter O may be used as a third subscript to show that the electrode not indicated by any previous subscript is open circuited. Similarly the letter S can be used as a third subscript to show the third electrode is shorted to the reference electrode of the second subscript, whilst the letter R as a third subscript indicates that a specified resistance is connected between the third electrode and the reference electrode.

The supply voltage to a collector is indicated as  $V_{CC}$ , the second suffix being a repetition of the first in the case of supply voltages. Similarly, one often meets the symbol  $V_{DD}$  for the positive supply to a CMOS (or COS/MOS) device, this being the supply to the drain. The negative supply to CMOS devices is normally represented by the symbol  $V_{SS}$ .

It should now be clear why  $V_{CE0}$  is the steady collector emitter voltage with the base open circuited. Similarly  $I_{CER}$  is the collector cut off current with a specified resistance between the base and emitter. It is current with the base and emitter joined, since either the base or emitter can be used as the reference electrode without any change when they are joined.

The parameters of individual devices vary from one device to another of the same type number. The typical value of a parameter such as transistor current gain is often quoted in data sheets by the abbreviation 'typ' after the quantity, but minimum and maximum values are also often quoted. In economical devices no maximum and minimum values may be quoted. In the case of breakdown voltages the minimum value applicable to any device of that type number is usually quoted so that the circuit designer knows that he can apply that value of voltage without danger of the device junction breaking down.

The above discussion gives the general principles of the way in which the symbols for various parameters are chosen. It is not complete, since we have not yet covered such items as current gain of a transistor or thermal characteristics of a device. However, these and other quantities will be covered in the following tables.

## Thermal characteristics

The symbols used for the following thermal quantities apply to all types of semiconductor device.

$P_{tot}$	total power dissipated within the device
$T_{amb}$	ambient temperature
$T_c$	temperature of the case of the device
$T_j$	temperature of the junction in the semiconductor material
$T_{mb}$	temperature of the mounting base of the device ( $=T_c$ )

$T_{stg}$	storage temperature
$\theta_h$	thermal resistance of heat sink. (Units: °C/W)
$\theta_i$	contact thermal resistance between the case of the device and the heat sink
$\theta_{j-amb}$	junction to ambient thermal resistance
$\theta_{j-c}$	junction to case thermal resistance

## Symbols used mainly with diodes

$C_d$	diode capacitance with reverse bias
$C_f$	diode capacitance with forward bias
$C_j$	capacitance of the junction itself
$C_{min}$	minimum capacitance (which occurs at the rated breakdown voltage)
$C_o$	diode capacitance at zero bias
$f_{co}$	cut off frequency of a varactor diode
$I_F$	total dc forward current
$i_F$	instantaneous forward current
$I_{F(AV)}$	average forward current
$I_{FM}$	peak forward current
$I_{FRM}$	repetitive peak forward current
$I_{FSM}$	non-repetitive peak forward current occurring under surge conditions
$I_R$	continuous reverse leakage current
$i_R$	instantaneous reverse leakage current
$I_{RRM}$	repetitive peak reverse current
$I_{RSM}$	non-repetitive peak reverse current
$I_Z$	zener diode continuous operating current
$I_{ZM}$	zener diode peak current
$t_{on}$	turn on time
$t_{off}$	turn off time
$t_r$	rise time
$t_{rr}$	reverse recovery time
$t_s$	storage time
$V_F$	steady forward voltage
$v_F$	instantaneous forward voltage
$V_R$	steady reverse voltage
$v_R$	instantaneous value of the reverse voltage
$V_{RM}$	peak reverse voltage
$V_{RRM}$	repetitive peak reverse voltage
$V_{RSM}$	non-repetitive peak reverse voltage (on surges)
$V_Z$	zener diode working voltage

## Symbols used mainly with transistors

$C_{ob}$	transistor output capacitance in the grounded base circuit
$C_{oe}$	transistor output capacitance in the grounded emitter circuit
$f_T$	transition frequency or gain-bandwidth product in common emitter circuit
$h_{FE}$	current gain in the grounded emitter circuit (or in the grounded base or grounded collector circuit).
$(h_{FB})$	
$h_{FC}$	
$h_{fo}$	the increase in collector current divided by the small increase in the base current which produces it. (Small signal current gain.)
$I_B, I_C$ or $I_E$	the steady base, collector or emitter current.
$I_{B(AV)}$ $I_{C(AV)}$ or $I_{E(AV)}$	the average value of the base, collector or emitter current.
$I_{CEX}$ $I_{CM}$ , $I_{BM}$ or $I_{EM}$	collector cut-off current in a specified circuit peak value of collector, base or emitter current
$I_b, I_c$ or $I_e$	rms value of the alternating component of the current
$I_{bm}, I_{cm}$ or $I_{em}$	peak value of the alternating component of the current
$i_c, i_b$ or $i_e$	instantaneous value of the total current
$i_c, i_b$ or $i_e$	instantaneous value of the alternating component of the current
$I_{CBO}$	collector cut off current with the emitter open circuited

$I_{CBS}$ or $I_{CES}$	collector cut off current with emitter shorted to the base
$I_{CEO}$	collector cut off current with the base open circuited
$I_{CER}$	collector cut off current with a specified value of resistance between the base and the emitter
$I_{EBO}$	emitter cut off current with the collector open circuited
$V_{BE(SAT)}$	base-emitter saturation voltage
$V_{(BR)}$	breakdown voltage
$V_{BR(CBO)}$	collector to base breakdown voltage with emitter open circuited
$V_{(BR)CEO}$	collector to emitter breakdown voltage with base open circuited
$V_{CB}$	collector-base voltage
$V_{CBO}$	collector to base voltage with emitter open circuited
$V_{CC}$	collector supply voltage
$V_{CE}$	collector to emitter voltage
$V_{CEO}$	collector to emitter voltage with base open circuited
$V_{ce}$	collector to emitter rms voltage
$V_{CE(SAT)}$	collector to emitter saturation voltage
$V_{EB}$	emitter-base voltage
$V_{EBO}$	emitter-base voltage with collector open circuited
$V_{ob}$	emitter-base rms voltage

## Symbols used mainly with FETS

$I_D$	steady value of the drain current
$I_{DSS}$	steady value of the drain current with the gate connected to the source
$i_m$	peak drain current
$I_G$	steady gate current
$I_S$	steady source current
$r_{DS}$	drain to source (or channel) resistance
$V_{DS}$	steady drain to source voltage
$V_{GS}$	steady gate to source voltage

## Symbols used mainly with thyristors

$I_{FRM}$	repetitive peak forward current.
$I_{FSM}$	non-repetitive peak (surge) current
$I_{GD}$	gate current which does not trigger the device
$I_{GT}$	gate trigger current
$I_{GO}$	gate turn off current
$I_H$	holding current required to maintain conduction
$I_R$	steady reverse leakage current
$I_{RG}$	reverse gate current
$I_{RRM}$	repetitive peak reverse current
$I_{RSM}$	non-repetitive peak reverse current (in surge conditions)
$I_T$	steady anode-cathode 'ON' state current
$P_G$	gate power
$t_{gt}$	gate controlled turn-on time
$t_{gs}$	gate controlled turn-off time
$V_{(BO)}$	breakover voltage
$V_D$	continuous off state voltage
$V_{FG}$	forward gate voltage
$V_{GT}$	gate trigger voltage
$V_R$	steady reverse voltage

## Operational amplifier terms

**Bandwidth,  $\Delta f$ .** The frequency at which the gain falls by a factor of 0.7 relative to the gain at low frequencies.

**Common mode rejection ratio, CMMR.** The gain when a signal is applied to one of the inputs of the amplifier divided by the gain when the signal is applied to both the inverting and non-inverting inputs. It is usually expressed in dB.

**Frequency compensation.** An operational amplifier requires a capacitor to enable it to be used in circuits which are stable over a wide frequency range. Internally compensated operational amplifiers have this capacitor fabricated on the silicon chip, but an external capacitor must be used with other types of operational amplifier which do not contain an internal capacitor.

**Input bias current,  $I_{BIAS}$ .** The mean value of the currents at the two inputs of an operational amplifier.

**Input offset current,  $I_{OS}$ .** The difference in the two currents to the inputs of an operational amplifier. Normally much smaller than the input bias current.

**Input offset voltage,  $V_{OS}$ .** The voltage which must be applied between the two input terminals to obtain zero voltage at the output.

**Open loop voltage gain,  $A_{VOL}$ .** The amplifier gain with no feedback applied.

**Output resistance,  $R_O$ .** The small signal resistance seen at the output when the output voltage is near zero.

**Voltage regulator terms**

**Dropout voltage,  $V_{DO}$ .** When the difference between the input and output voltages falls down below the dropout voltage, the device ceases to provide regulation.

**Foldback current limiting.** In regulators with foldback current limiting, the current will 'fold back' to a fairly small value when the output is shorted.

**Line regulation.** The change in the output voltage for a specified change in the input voltage.

**Load regulation.** The change in output voltage for a change in the load current at a constant chip temperature.

**Quiescent current,  $I_Q$ .** The current taken by the regulator device when it is not delivering any output current.

**Ripple rejection.** The ratio of the peak-to-peak ripple at the input of the regulator to that at the output. Normally expressed in dB.

**Monolithic timer terms**

**Comparator input current.** The mean current flowing in the comparator input connection during a timing cycle.

**Timing capacitor,  $C_t$ .** This capacitor is normally connected between the comparator input and ground. The time taken for it to charge controls the delay time.

**Timing resistor,  $R_t$ .** This is the resistor through which the timing capacitor charges.

**Trigger current.** The current flowing in the trigger input connection, at the specified trigger voltage.

**Trigger voltage.** The voltage required at the trigger pin to initiate a timing cycle.

**Conclusions**

Data sheets must be used intelligently and with much thought. Information on the conditions under which an entry in the data sheet is applicable is often stated in small print, but is of great importance. Data should always be thoroughly studied before a device is used for the first time, only then will you be able to fully understand the potential applications of the device.

Thus  $i_c$  is the instantaneous value of the total emitter current,  $i_e$  the instantaneous value of the alternating component of the emitter current, and  $I_{E(AV)}$  the average (DC) value of the total emitter current. Other subscripts can be used in a similar way,  $I_F$  being the forward DC current with no signal,  $i_F$  the instantaneous forward current and  $I_{FM}$  the peak forward current.

ETI

# WE'RE OUT TO FINISH


## YOU OFF! Rapitape # eti PANEL TRANSFERS MOD MAGS 1977 no 1

### GOOD AND PROPER!

... or at least your projects. If there is one thing which is impossible to do at home is lettering front panels to professional standards. At least until now. If you cast your eyes right a while you'll see our new panel transfers sheet, which has been carefully designed to allow you to do exactly that.

The transfers are easily rubbed down, and the two sheet set contains a mass of lettering and -uniquely- control scales for both rotary and slider puts.

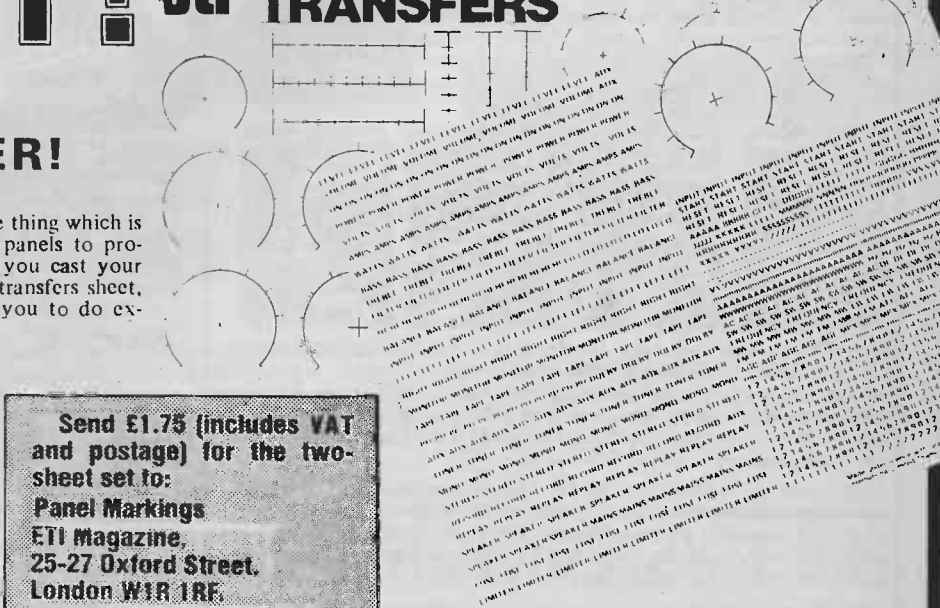Each sheet measures 180mm X 240mm and comes packed flat in a stiff cardboard envelope for protection. There should be enough for dozens of projects here - and the longer you wait the worse they'll look!




Send £1.75 (includes VAT and postage) for the two-sheet set to:  
**Panel Markings**  
**ETI Magazine,**  
**25-27 Oxford Street,**  
**London W1R 1RF.**
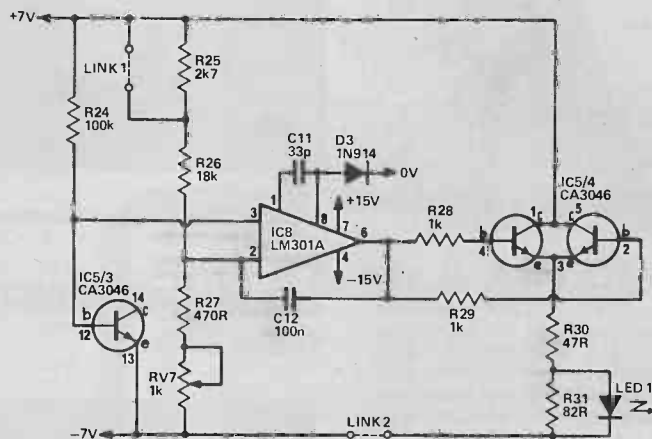
# TEMP STABILISED LOG CONVERTER

This design can be set up for either logarithmic or exponential operation and incorporates a neat heater circuit for temperature stability.

IN THE CONVENTIONAL musical scale, consecutive notes are not separated by the same frequency, but by the same ratio — the twelfth root of two. This is quite acceptable for most musical instrument manufacturers, except that in electronic music equipment it is easier to make oscillators which have an accurately linear frequency/control voltage characteristic. The keyboards of most music synthesizers give an output voltage of 1 V for each octave on the keyboard. This can easily be generated by a set of equal resistors between the contacts on each key and a voltage applied to each end (normally 5 V). However this means the oscillator is required to have an exponential frequency/control voltage response.



Below: the circuit diagram of the converter section. One channel only is shown here, the second — identical — uses the even components numbers. Above: the oven circuitry.


## Trouble

This is where the trouble usually starts. An exponential converter is normally used which relies for its operation on the relationship between current and voltage in a silicon diode or transistor. However, unless temperature stabilisation is used the oscillator will not stay in tune for very long. With this unit the transistor used is heated to around 55° C and stabilised at this temperature, eliminating the problem of thermal drift.

In the instrumentation field a lot of functions are displayed in dBs which are a logarithmic measurement. As this unit can be connected in either exp or log modes it is useful for this purpose also.

As the unit will normally be used with some other equipment, we have not described any mechanical housing.

VALUES OF UNMARKED COMPONENTS		
	LOG	EXPONENTIAL
R3	33k	390k
R5	∞	150k
R13	∞	100k
R15	22k	470k
R17	390k	33k
RV3E	LINK	200k
RV3L	200k	LINK
LINKS REQUIRED		
	A-B	A-D
	D-C	B-C

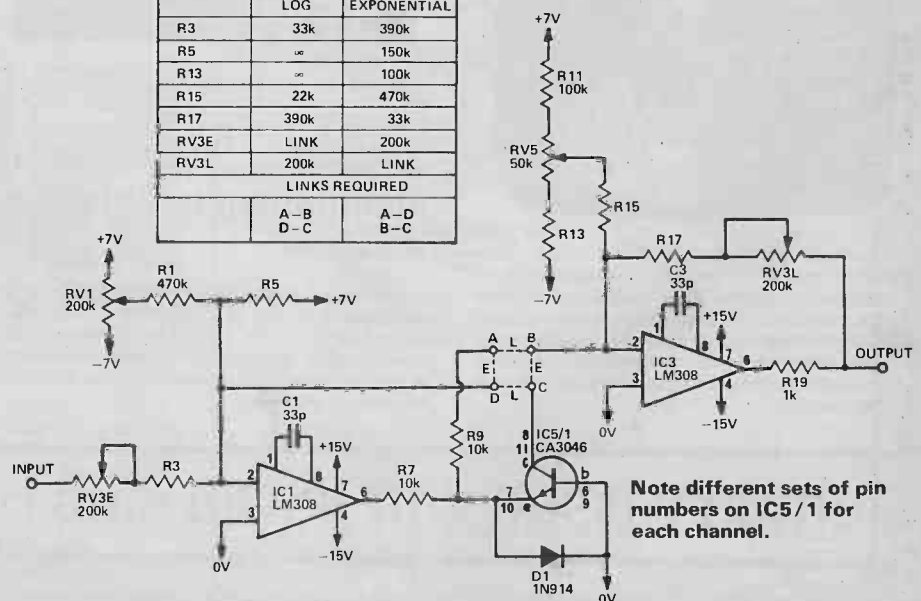


Note different sets of pin numbers on IC5/1 for each channel.



# ..... news digest.....

## PROM-IN-AID TIME

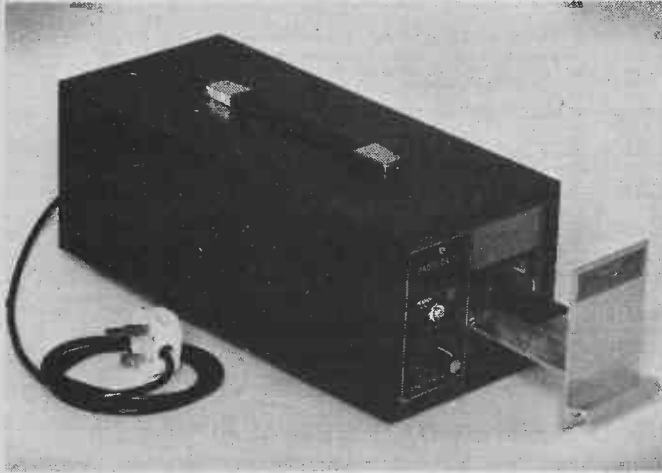

Micro-men take note. The Prombix 12 can wipe out twelve PROMs at once with variable erase time with safety interlock. Priced at £59.00 all inc. Should be of interest to

small firms and rich enthusiasts.  
GP INDUSTRIAL ELECTRONICS, SKARDON WORKS, SKARDON PLACE, NORTH HILL, PLYMOUTH PL4 8EZ.

## GETTING INTO PRINT



A low cost printer is announced by Kimberley Business Records giving a low cost printer is announced by Kimberley Business Records giving good quality output. This will allow the expansion of many home systems into the extensive field of word processing, and God help you then! A standard lever operated typewriter mechanism has been used, driven by 240V solenoids.

Designed for parallel data input with handshake control, ASCII coding is

accepted for the 88 characters available operating at a speed of 8 CAPS from a standard peripheral interface. It is supplied fully built and cased at £200 (including carriage and VAT). Alternatively as a print mechanism only, requiring all power other than 240V, case, and TTL logic to be added, the cost is £160.

KIMBERLEY BUSINESS RECORDS, 2, HARTINGTON ROAD, GOSPORT, HANTS, PO12 3AG.

# Catronics for

## SOLID STATE R.T.T.Y.

We can supply Printed Circuit Boards and components for the RTTY Video Display published by G3PLX in "Radio Communication".

This video display unit is designed to be an all-electronic replacement for a Teleprinter, and therefore does not suffer its disadvantages — bulk, unreliability and noise. The basic function is to take Murray Code — either from a Terminal Unit (on receive) or from a Keyboard — and produce a complete TV signal. This signal may be fed into a monitor or modulated and fed into the aerial of an ordinary domestic TV set. The resulting display is a page of 24 lines of up to 40 characters. It may also be used (with its keyboard) to send fully encoded Murray Code signals for transmit purposes.

Hundreds of these units have been built, with very little trouble, and the pleasures and fascination of RTTY operation are now being experienced by more and more amateurs. Listeners, too, find it very interesting to be able to read international news and other transmissions without the inconvenience of the mechanical teleprinter.

Kit price from £83.55 — send SAE for details.

Introducing the most comprehensive R.T.T.Y. TERMINAL UNIT you can, or indeed, need ever buy —

## THE CATRONICS CT100 R.T.T.Y. TERMINAL UNIT

### INPUTS for:

Audio FSK signal in  
Data in from V.D.U. (e.g. G3PLX)  
TTY Keyboard or Tape Reader

### OUTPUTS for:

V.D.U. or other TTL compatible equipment  
TTY Magnet — single or double current  
AFSK to drive Transmitter

Featuring a unique digitally controlled "Autoprint" circuit which is a superior replacement for the "Antispace" and "Autostart" facilities found on some other terminal units. The terminal will ignore most CW and phone signals but will respond to a correct RTTY signal. Tuning correctly into an RTTY signal is made simple with a single "correctly tuned" LED plus an additional "Mark frequency" indicator.

The FSK demodulator circuit utilises a special "state-of-the-art" system to give excellent performance and stability at low cost.

The teleprinter interface unit incorporates electronic "de-bounce" circuitry to eliminate spurious switching from the Keyboard.

### UNITS ARE AS FOLLOWS:

CT100. Receive only RTTY Terminal Unit housed in attractively styled metal cabinet approx 9 by 7 by 2½in., with integral mains power supply.	£71.00
CT101. Receive Unit + Hi-stability AFSK oscillator for transmission purposes.	£79.00
CT102. Receive Unit + Teleprinter interface unit.	£80.00
CT103. Complete terminal unit for reception and transmission with facilities for connection to Teleprinter	£88.00

ADD £3 for Securicor delivery

## Catronics NEW KEYBOARD KIT

Catronics Ltd. are proud to announce the introduction of the world's first modular Keyboard Kit available to the home constructor!

The printed circuit board is designed to take a maximum of 70 keys but may be assembled with a smaller number of keys for a simpler keyboard.

The board is not dedicated to any specific coding, allowing it to be used for any project whether it requires ASCII, Baudot or any other code. This makes it suitable for many projects including

### E.T.I. — System 68 MPU (54 keys)

Auto morse sender, etc.

The Keyswitches themselves are single pole push-to-make type and require no extra mechanical mounting arrangements.

A legend sheet is provided with each kit enabling the constructor to label the keys to suit individual requirements.

Catronics price: Kit for 70 station Keyboard: £29.00


Please add 50p for post and packing

All prices INCLUDE VAT at current rates  
Send SAE for FREE PRICE LIST or 45p and large (A4) 18 ½p  
SAE for copy of our Data Catalogue.

CATRONICS LTD.  
COMMUNICATIONS HOUSE  
20 WALLINGTON SQUARE  
WALLINGTON, SURREY SM6 8RG

(DEPT.  
951)

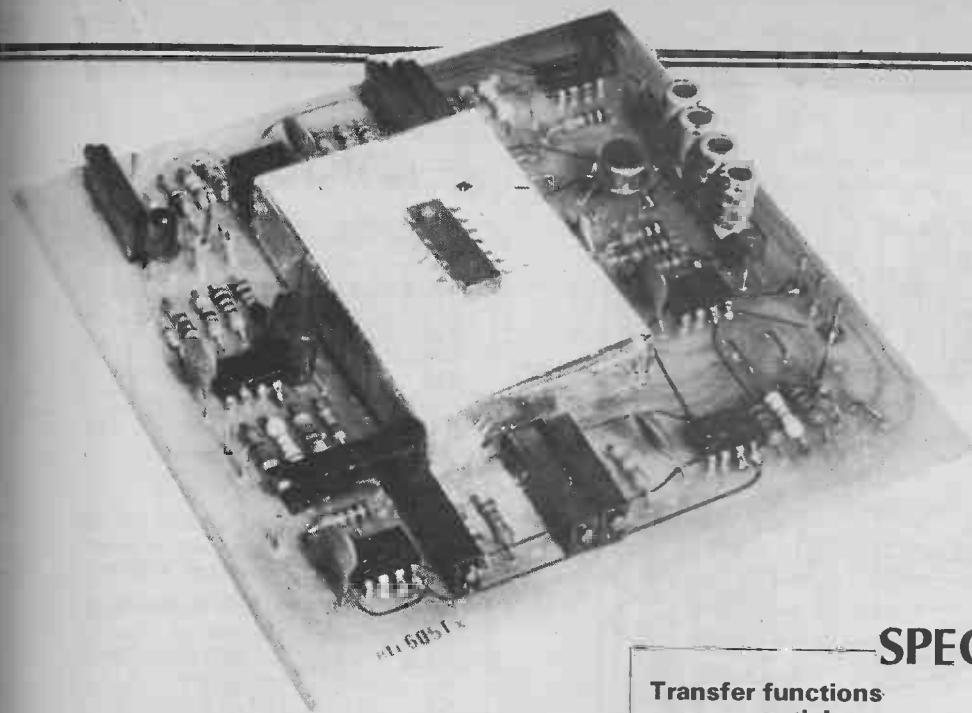Tel. 01-669 6700. Open Mon.-Fri. Also Sat. a.m.



The photo on the left shows the complete unit with the oven top removed to show IC5. Link 1 is made from a couple of valve socket pins in this prototype.

## SPECIFICATION

Transfer functions	
exponential	$V_{out} = 0.15625 \times 2V_{in}$
log.	$V_{out} = \ln(V_{in}/0.15625)/\ln 2$
Useful dynamic range	50dB or 8 octaves
Oven temperature	approx. 55°C
Warm up time	about 2 minutes
Power supply	$\pm 10$ to $\pm 15$ volts

## HOW IT WORKS

This unit relies on the fact that the collector current of a transistor is exponentially related to the base voltage.

In the log mode the collector of the transistor is linked back to the input of IC1. In this way the collector current is proportional to the input voltage and therefore the voltage on its emitter is logarithmically related to the input voltage. This voltage is then amplified and level shifted by IC3 to give the desired output.

In the exponential mode the 10k resistor R9 is linked back to the input of IC1 and the voltage on the emitter of the transistor is proportional to the input voltage; the collector current is exponentially related to the input voltage. This current is converted to a voltage by IC3.

All this works well provided the transistor is at a constant temperature. Compensation can be made by using other junctions and thermistors, however even the self-heating effect of the transistors can affect linearity. The transistors we have used are part of a transistor array IC which has three individual NPN transistors and a differential pair. We heat the chip up by dissipating heat in the differential pair while measuring the base-emitter voltage of one of the individual transistors. IC8 is used to compare this voltage to one set by the divider R25, 26, 27 and RV7. The base-emitter voltage is normally about 0.67 V at 20°C and drops about 2.2 mV per degree above this temperature. IC8 then stabilises the chip temperature to about 35°C above the temperature at which it was initially calibrated. As it warms up the current in the transistors will fall and when hot the voltage drop across R31 will be low enough that the LED will extinguish. The transistor array is housed in a polystyrene housing to conserve heat.


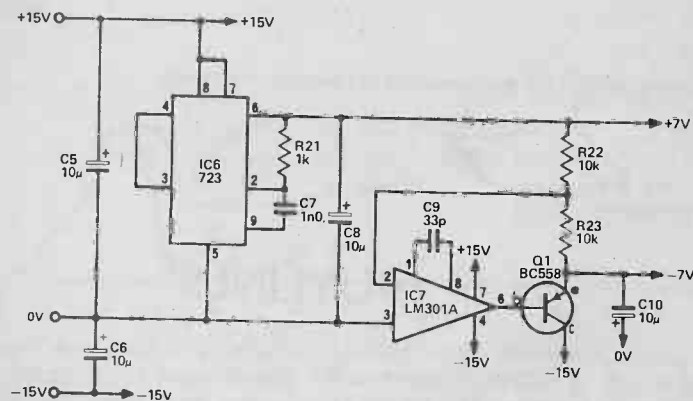


Fig. 1b. The power supply section which supplies the stable  $\pm 7$  V needed for the bias and adjustment controls.

The only difference between the assembly of this board and any other is the oven and the connections to the transistor array package. The oven is made out of two pieces of polystyrene about 55 x 35 x 12 mm. The outside of the oven should be covered with aluminium foil to help reduce heat loss. The aluminium itself should be covered with a layer of adhesive tape where the leads can touch. A piece of thick paper should be used between the oven and the pcb to insulate the tracks.
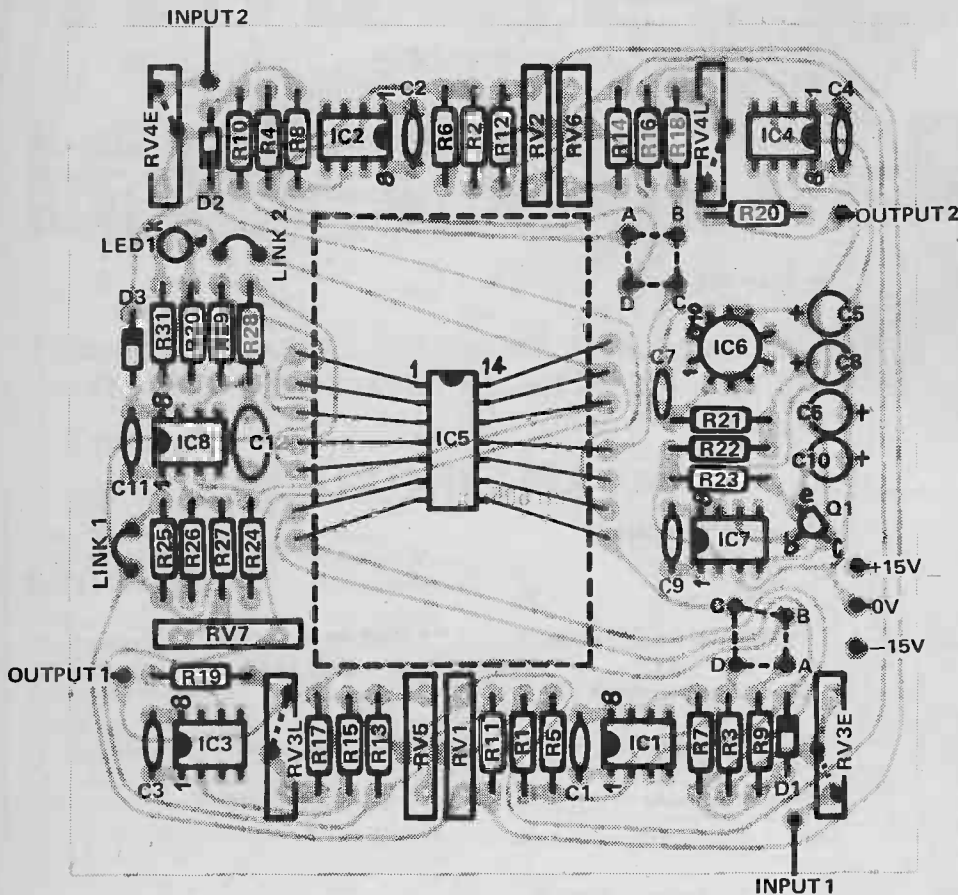
## Half Baked

The centre of the oven should be hollowed slightly to hold the IC (bend the leads out straight as shown in the photo; a hot soldering iron is the easiest method. Do not remove more than necessary. Now solder a 40 mm length of thin copper wire (a single strand of multistrand cable is best) to each pin, then with the base of the oven in position, sit the IC in the oven and connect the leads to the appropriate holes. If a small amount



Component overlay for the complete log converter project.

## PARTS LIST

RESISTORS	all 2%, 5W
R1, 2	470k
R3-R6	see table 1
R7-R10, 22, 23	10k
R11, 12, 24	100k
R13-R18	see text
R19-R21, 28, 29	1k
R25	2k7
R26	18k
R27	470R
R30	47R
R31	82R

POTENTIOMETERS	
RV1-RV4	200k multiturn trimmer
RV5, 6	50k multiturn trimmer
RV7	1k multiturn trimmer

CAPACITORS	
C1-C4	33p ceramic
C5, 6	10u 25 V electrolytic
C7	1n0 polyester
C8	10u 25 V electrolytic
C9	33p ceramic
C10	10u 25 V electrolytic
C11	33p ceramic
C12	100n polyester

SEMICONDUCTORS	
IC1-IC4	LM308
IC5	CA3046
IC6	723
IC7, 8	LM301A

Q1 BC558

D1-D3	1N914
LED	T1L 209

MISCELLANEOUS  
PCB  
Polystyrene foam for oven

## BUYLINES

The project depends upon the CA 3046 device — near equivalents will probably **not** function. The CA 3046 itself is readily available — we

found it in both the Marshalls and Stevenson catalogues when we looked for it! Initial reaction here had been that it would be difficult to obtain.

of epoxy cement is placed under the oven it will stay in position. Now fit the top of the oven and secure with a piece of adhesive tape until it has been checked out. It finally can be cemented with epoxy adhesive.

The potentiometer values chosen are a compromise between ease of adjustment and the ability to compensate different transistors. If the potentiometer does not have enough range then the series resistor will have to be varied. We have

specified 2% resistors throughout to obtain a better temperature coefficient than is possible with conventional 5% resistors. It will not help to select out of normal 5% types.

### Calibration

The equipment needed comprises an accurate digital voltmeter and a variable power supply with a fine voltage control. The + 7 V rail can be used for this with a multi-turn potentiometer.

## CALIBRATION TABLE

A	B
-3.00 V	19.5 mV
-2.00 V	39 mV
-1.00 V	78 mV
0.00 V	156 mV
+1.00 V	312 mV
+2.00 V	625 mV
+3.00 V	1.25 V
+4.00 V	2.50 V
+5.00 V	5.00 V
+6.00 V	10.00 V

This table shows the relationship between the input and output. In the exponential model A is the input with B the output while in the log mode B is the input and A the output.

## Oven Control

1. Before switching on, remove link 2 and fit link 1.
2. Switch on and monitor the voltage on the output of IC8 (pin 6).
3. Adjust RV7 until the voltage is about  $-5$  V. The potentiometer is sensitive in this area but the actual voltage is not critical.
4. Remove link 1 and fit link 2. The LED should now come on for about two minutes before slowly going out. This indicates that the oven is stable.

## Calibration of Log Mode

1. Set 0 V on the input.
2. Monitor the voltage on the junction of R7 and R9.
3. Adjust RV1 to give a negative voltage on this point. Now adjust RV1 slowly until the voltage just switches positive.
4. Set 0.15625 V in the input.
5. Adjust RV5 to give 0 V output.
6. Set 5.00 V on the input.
7. Adjust RV3 to give 5.00 V output.
8. Set 1.25 V on the input and check the output voltage. It should be 3.00 V. If it is higher go back to step 4 except adjust RV5 to give  $-0.010$  V and use RV1 to bring it back to zero. Continue with step 6, 7 and 8. If the output voltage at 1.25 V input is less than 3.00 V adjust RV5 to give  $+0.010$  V instead of  $-0.010$  V.



Continue until all three points are correct.

## Calibration of Exponential Mode

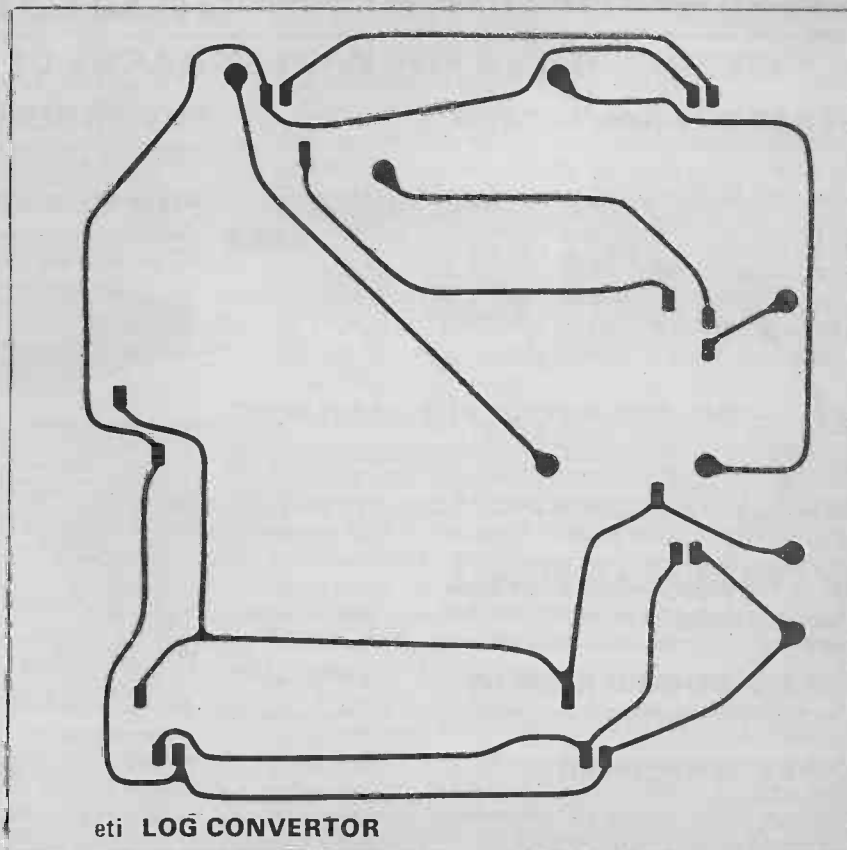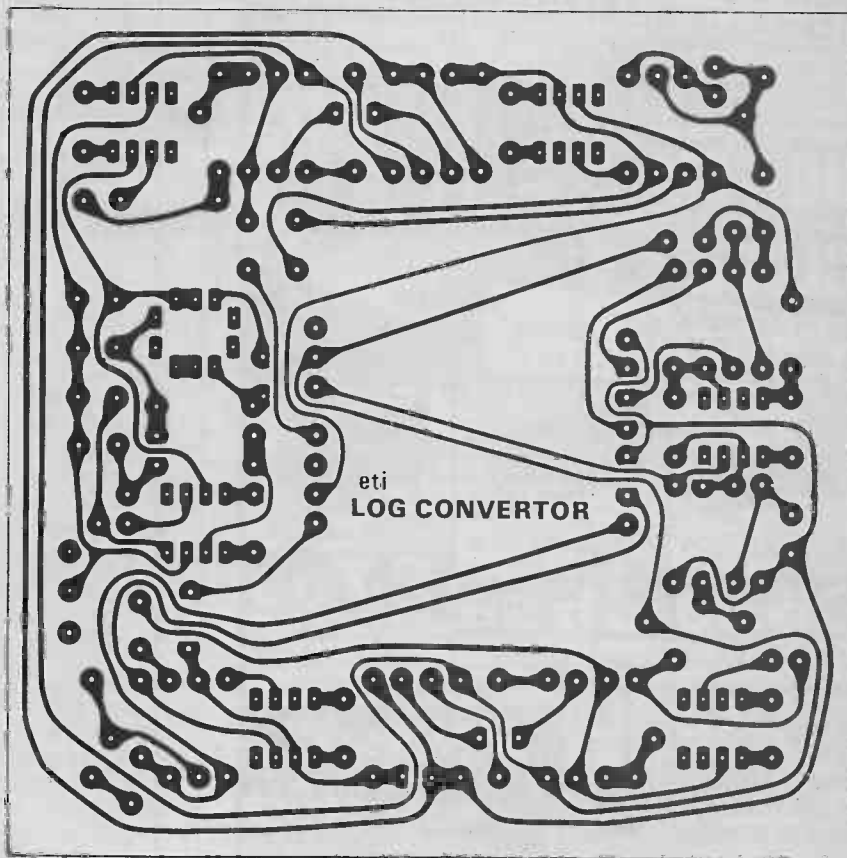1. Place a link between the junction of R7 and R9, and OV.
2. Adjust RV5 to give 0.00 V output. Remove the link.
3. With 0.00 V input, adjust RV1 to give 0.15625 V output.
4. With 5.00 V input, adjust RV3E to give +5.00 volts output.
5. Check output voltage with 3.00 V input. It should be 1.25 V.
6. If high repeat steps 1-5 except output. If low, repeat steps 1-5 except adjust RV5 to give about 10mV output.

ETI

Both sides of the PCB shown full size. On the top is the underside and the pattern beneath that is for the topside of the board.





# microfile.....

**This month dynamic Gary (mines a pint) Evans goes random, ROMs the seas as a pirate and plays strange games with a T.V., but still finds time to visit North London.**

BEING CAUGHT PIRATING software could lead to all sorts of unpleasantness—boys in blue or more likely the boys in black (the legal eagles) looking for a large fee in some test case. At any rate copying, or rather being caught copying, software that someone, somewhere is willing to protect is something to avoid. It's for this reason that the guys at Transam — they who supply kits for the Triton — suffered a few nervous twitches when they heard that someone called Dobbs on the phone and he wanted to have a few words with them.

Now the BASIC that was used in the Triton has been around for some time. When development of the computer started we realised we could not undertake to write an 8080 interpreter from scratch and we looked around for something that was "in the public domain". The listing of an interpreter that appeared in Dr. Dobbs journal seemed to us to be just the thing we wanted — had we made a dreadful mistake.

Well gentle reader (I'm an Asimov fan) as it turned out we need not have worried at all. On picking up the phone, instead of some irate, distant American voice a softspoken northerner (north of England that is) greeted the ear.

This Dobbs had nothing to do with publishing a software journal working — as it turned out — for British Rail. He wanted to order a Triton.

Relief all round — is there a Mr. Byte in the house. What the manufacturers produce today, industry uses the next day and we, the amateurs, use the day after that and what the manufacturers are producing now are 16 bit MPUs. Intel, Motorola, Zilog Texas — everybody seems to have caught the 16 bit bug.

The first small system for the Home Office to use a 16 bit beast is almost certain to be the long awaited, and much talked about, Texas machine. Just what overnight "quantum jump" in performance these 16 bit based systems are going to provide, remains to be seen — but at least we should have something with a bit more to offer in terms of throughput and facilities than the current crop of 8 bitters. At what cost penalty will become evident over the next year or so.

Dynamic RAMs are very cheap, are they not? A couple of systems in use in this country feature such devices — the TRS-80, although here any cost savings do not seem to be passed on to the end user, and the NASCOM.

The more extensive use of dynamic RAM in small systems is probably a hang over from the days when it was all anybody could do to get a dynamic memory card up and running. There is no doubt that a dynamic card

can be a real pig to fault find. So many things have to happen at exactly the right time for the system to work at all. Unless some very sophisticated diagnostic equipment is available, it could prove almost impossible to decide what is wrong.

With the current crop of dynamic RAM controllers, however, hopefully there will be so little margin for error that we shall start to see nice cheap 4K and 16K memory expansion systems.

One example of a RAM controller that seems to do it all is the Intel 8202 — I have not yet managed to get a data sheet for this device but when I do I'll let you know just what it can do. In the meantime, if any of you have played around with dynamic devices, perhaps you'll let me know how you got on.

The North London Hobby Computer Club seems to be going from strength to strength. I was at their second meeting a while back and there was standing room only in the two rooms occupied by the club for demonstrating on the PET and the Triton. A continuing program of interesting talks and demonstrations is planned and if you live in North London, is recommended that you go along to the North London Poly in the Holloway Road and see what is going on for yourself.

Mine of Information Ltd is a company that is out to contest the high prices charged for many of the American microcomputer books brought over to this country. To quote from their literature "some worthwhile books are distributed by companies with exclusive European or British rights; there is a temptation to capitalize on the monopoly by increasing prices. In these circumstances Mol has to charge its customers more than is reasonable! Mol is taking action to contest the high prices. (When the choice of books is wider there will be no need to buy from such suppliers)."

A freshing attitude, as I can think of at least one outfit which must be making a mint from a number of exclusive titles sold at a high mark up. Some increase in cost from a straight \$70 £ conversion is acceptable — to quote Mol again — "It means extra hassle and expense to bring books to Britain" — but not as much expense and hassle as some would have us believe.

I wish Mol luck in their campaign and if you would like their lists send an SAE to

Mine of Information Ltd  
1 Francis Avenue  
St. Albans  
AL3 6BL

By the way members of the North London Computer Club get 10% off the prices in the list — yet another reason to pay a visit to the club. ▶

# NEWS: Microfile

The trend in America at the moment, or at least one of the trends, is for the home computer and the TV games to meet in a sort of common ground. One example of such a product is the Bally Arcade "box". The machine features a calculator style keyboard with slot for a Bally cartridge as well as sockets into which a number of accessories can be plugged, these include the two hand controllers supplied with the basic machine.

The machine features a number of built in games including the excellent gunfight which many of you may have seen in the arcades over here. This game produces good high resolution graphics in colour as well as a repertoire of musical sounds.

By plugging a ROM cartridge into the front panel socket additional games can be played on the machine and if a BASIC cartridge is used the Arcade is converted to a computer running the familiar TINY BASIC as per the TRITON.

Z80 based, the Arcade is supported by 8k of ROM to store the resident games and 4K of RAM which acts mainly as a screen memory.

The Bally Arcade is not the only product to appear in this area. Magnavox has the "Dyssey 2" machine from Intercat and it's rumoured, Atari are ready to launch something into this market.

ETI

## LINES FROM OUR VAST STOCKS—IMMEDIATE DELIVERY

All below manufacturers' prices — all new stocks. Quantity discounts — export enquiries invited. Postage & packing 35p per order.

**CALCULATOR CHIPS** General instrument GIMT4 on anti-static foam 24 pin D.I.L. socket for use with Bowmar display £1.50 ea. Pack of 25 chips £25. 100 for £80. 500 for £350.

**BOWMAR 9 DIGIT CALCULATOR DISPLAY** with PC connector 0.2 digits. Common cathode with red bezel £1.25 ea. 10 £1.10.

**TEXAS 19** gold-plated snap key contact on gold-plated P.C. board. Size 70x80x2mm 75p ea. ORP12 light dependent resistance (Eq = RPY30). 2 for £1. 10—£4. 100—£35.

**FAIRCHILD FND10 0.15** 7 segment display. C cathode 50p. 10 for £4.50. 100 for £40.

**TBA 120A T.V. I.C.** amplifier Siemens 75p. 10—£6. 100—£50. 1000—£350.

**BECKMAN 500 kca** Triggerable clocking oscillator for use with calculator chips 5v supply with circuit £1. 10 for £8. 100 for £65.

**BURROUGHS 9 DIGIT** Panaplex calculator display 7 segment 0.25 digits. Neon type with red bezel socket and data. £2.25 ea. 10 for £20.

**ALMA PUSHBUTTON** high reliability read switches. Push to make 18x27x18mm 40p ea. 10 for £3.50. 100 for £33.

**SMITHS INDUSTRIES** Audible warning devices 6-12 volts. 2 transistors 30x10mm encapsulated 50p ea. 10 for £4. 100 for £30.

**HONEYWELL PROXIMITY DETECTOR** integral amplifier 8v D.C. £2.50 ea. 10 for £20. 100 for £175.

**OSMOR CHANGE OVER REED RELAY** 12v coil 20m/a operating current 59x17x13mm 75p ea. 10 for £5. 100 for £45. 1000 for £400.

**MAINS TRANSFORMERS** (miniature) all with 240v primary.

12v 100 m/a ..... ea. 10 100  
60x40x42 m/m ..... 95p £8 £60

12-0-12v 100 m/a 28x25x27mm ..... £1.20 £10 £80

Valve output 40 1 61x15x42 m/m ..... 75p £6 £50  
20-0-20v 100 m/a ..... 95p £8 £65

**SOLDER** (multicore type) Servical 10 metres for £1. 50 metres for £4. 100 m. £7

**RADIATION DETECTORS** Quartz Fibre Dosimeters. Pen type with clip with lens and scale 0-50R. Originally over £5. OUR PRICE 95p EACH. 10 for £8. 10 for £60. 1,000 for £500.

**CLOCKING OSCILLATOR** (Pye-Dynamics). thick film 1mHz supply 5v 19x25x6mm 85p. 10 for £7. 100 for £60.

**T.V. TUNERS** by G.E.C. U.H.F. 38 mcs size 34x23x14 £2.50 ea. 10 for £20. 100 for £175.

**T.V. SOUND TUNER KIT.** Through your F.M. tuner. Kit of parts with instructions £5.50. Ready-built, tested, £7.00.

**JOYSTICK CONTROLS.** (Ideal for TV Games. model control), sturdily constructed compact giving full 360° movement and control. Each unit fitted with 100K linear controls. Pair £4.00.

**1/4" RF LONG-MEDIUM & FM TUNER WITH MC1310 DECODER & 5-BUTTON SELECTOR SWITCHES** \* INPUT SELECTORS FOR GRAM AND TAPE \* Supplied complete with FRONT-END TUNER AND FERRITE AERIAL \* SIMPLE INTERCONNECTIONS \* Size 19x13x6cm.

**THIS QUALITY AMPLIFIER £10.95 WITH CIRCUIT**

**POWER UNIT KIT FOR ABOVE MODELS 25/28 VOLTS £2.95**

**TAPE HEADS** 1/4 track. Record Marriot XRF536 £5. XES11 erase £1.25. XRPS 18 £3.50.

**MULLARD TUNER MODULES** with data. LP1171 combined AM/FM IF strip — £3.50 \* LP1179 FM front end with AM tuning gang, used with LP1171 — £3.50 \* LP1171 and 79 pair — £5.75 \* LP1157 complete AM strip — £2.05 \* 10 pairs for £50. 100 pairs for £400.

**SEVEN DIGIT MINIATURE COUNTER** by Durant 12-24 volts D.C. 3 Watts. Size 40x25x45 551 mcs £1 each. 10 for £9. 100 for £80.

**2N3055A TO3 POWER 80 VOLT VERSION.** 10 for £2.50. 100 for £22.00. 1,000 for £200.

### TRANSISTORS BY BULLARD, TEXAS, FAIRCHILD

Price ea per	10	100	500	1,000
AC128	0.230	0.260	0.180	0.150
AD149	0.750	0.650	0.550	0.490
AD161	0.380	0.330	0.290	0.250
AD162	0.380	0.330	0.290	0.250
BC707	0.100	0.085	0.075	0.065
BC108	0.110	0.095	0.080	0.070
BC109C	0.120	0.100	0.085	0.075
BC114	0.080	0.065	0.050	0.040
BC132	0.080	0.065	0.050	0.040
BC153	0.085	0.070	0.050	0.040
BC172	0.075	0.060	0.050	0.040
BC173	0.075	0.060	0.050	0.040
BC205	0.070	0.055	0.040	0.035
BC208	0.075	0.060	0.050	0.040
BC209	0.075	0.060	0.050	0.040
BD181	0.600	0.500	0.050	0.040
BD182	0.700	0.600	0.500	0.440
BF181	0.240	0.200	0.185	0.160
BFY50	0.180	0.16	0.140	0.125
BFY51	0.180	0.160	0.140	0.125
BFY64	0.220	0.195	0.175	0.150
BFY90	0.750	0.680	0.630	0.550
BU205	1.000	0.900	0.800	0.750
BU208	1.250	1.100	1.000	0.950
BY127	0.110	0.090	0.075	0.065
BY128	0.440	0.385	0.350	0.300
LM311H	0.700	0.600	0.055	0.050
TBA25BX5	0.680	0.600	0.055	0.050

LOW PRICES EX-STOCK

**Henry's RADIO**

Buy it with Access

All mail to:  
Henry's Radio  
404 Edgware Rd  
London W2  
Phone (01) 723 1008




# TRAMPUS

SEMICONDUCTOR DISTRIBUTORS

58-60 GROVE ROAD, WINDSOR BERKS SL4 1HS  
TELEPHONE WINDSOR (07535) 54525  
ORDERS WELCOME BY POST OR TELEPHONE  
TRADE, EDUCATIONAL & EXPORT SUPPLIED



## WINTER SALE THIS MONTH TO MAKE ROOM FOR NEW MICRO MEMORY PRODUCTS WE ARE REDUCING OVERSTOCK PRODUCT.

Post & Packing free on orders over £3. Other orders please add 25p P&P. Credit orders welcome by post or phone. Normally 24 hours turnaround on ex stock product. UK add 8% VAT to prices marked \*. all other prices add 12 1/2% VAT. All priced each. Price list free send S.A.E. Data costs extra. Discounts: This month buy 10 PAKS get one free. Also 10% off 100 up TTL or CMOS. All products to makers specification.

**OPTO.** All grade 1. Big 1/2" Displays FND508 CA or CC early 90p\* 0.3" Displays 75p\* LEDs Big & Bright Red 3mm 1/2" dia 8p\* Red 5mm 2" dia 9p\* Smm Clip & Lock ring 2p\* TIL209 Red & Clip 9p\* Green or Yellow with 3 or 5mm 1/2" 19p\* Color LED no clip 16p\* MEMORIES: 10% off 8 up.

2102 RAM 450ns 88p\*  
2102 RAM 350ns E1.20p\*  
2102 RAM 250ns E1.35p\*  
2114 Static 4K RAM Easy use. No clock. 5v + Timer £26\*  
6845 PMA - MUX BUS PROM + Timer £26\*

**MICRO BUSS STOP**  
8080 CPU 1MHz £6\*  
6800 CPU/RAM 1MHz £12\*  
6846 PMA - MUX BUS PROM + Timer £26\*

6845 ACIA 1MHz £5\*  
ATS 1013 UART £4\*  
ATS 1014 UART £6\*  
8350 VID 1 Chip PDA\*  
INTERFACE: RS232C:3.  
MC1488 & 1489 90p\*  
MC6880 & 6889 £2\*  
81LS95 & 96 E1.40\*  
XTAL 1MHz £3\*

**DEVELOPMENT SETS**  
All loose packed in 1 bag.  
SET 1: 250x50 volt Ceramic Capacitors 5x 10 each 22pf to 0.1uf £5  
SET 2: Testolms full to 200MΩ 220 to 35v Total 50 Capacitors £5  
SET 3: Electrolytic 25 volt Total 80. 10 each 1/2/5/10/47/100/220. 5 each 500/1000 £5  
SET 4: 1/2 watt Resistors 5% C.F. 10 each 10 ohms to 10 meg ohm. Total 500 £5  
SET 5: Zeners 400mW Total 100. 33 volt £5  
SET 6: 100 Presets £5

**PASSIVE GEAR**  
Resistors 1/2W 5% Cf 2p Presets PR Vert 10p Type 45 Pots Log/Un 26p

**CAPACITORS** Tants 12p Ceramic 50v 5% Hi Stab 22pf to 0.1uf. 22. 47 5p

**ELECTROLYTICS** 25 volts 1/10/17/100uf All 10p (50x20) 220/470uf 30p 1000uf 25v 35p

**KNOBBS** 1/2" Dia & Trim 15p

**HEATSINKS** TO3 25p\* TO3 Large 50p\* T14 25p 105 or 1018 9p.

**YEND.** All B.I.\* & most products at normal prices as advertised  
I.e. 3/4"x5/8" 0.1" 56p\* 6"x4" OIL Board £2.25\* DALO PCB PEN. 2 nbs 70p\* 1/4 K6 FCC Eicher £1\* Copper Clad 6"x4" 60p\* PPS or PPS Chip. Pair 15p DIN Plugs. All 15p DIN Sockets. All 10p Discs Strobo Tube £5

**FULL SPEC PAKS E1**  
PAK T: Tenx/Motorola Plastic Power NPN 2amp 60v/100131 type) £1\*  
PAK A: 12xRed Leads E1\*  
PAK B: 6x741 OIL 8 E1\*  
PAK C: 4x2N 3055 E1\*  
PAK D: 12xBC109 E1\*  
PAK E: 13xBC182 E1\*  
NEW PAK D: 10xBC212 E1  
PAK F: 13x2N3704 E1\*  
PAK G: 7xBFY51 E1\*  
PAK H: 7x2N3819 E1\*  
PAK I: 10xKoaB 3/4" Dia E1  
Metal Trim (Synthesiser) E1

PAK J: 6x2N3053 E1\*  
PAK K: 50x1M4148 E1  
PAK L: 50x330 10 Volt E1  
PAK M: 4xPairs NPN/PNP 2 Amp 60 volt E1  
PAK N: 50x0A81/9 E1  
PAK O: 20xSmall Signal NPN. Similar to 109 E1  
PAK P: 50x220uf  
6.3v/10V Electrolytic E1  
PAK R: 14xBC107 E1\*  
PAK S: 14xBC108 E1\*  
PAK T: 10x1A 50v SCR E1\*  
PAK W: 40x4Electrolytics Mixed. All good E1  
PAK X: 4x555 Timer E1\*  
PAK Y: 5xDual Transistors MD7021. 6 Leads TO5 E1\*  
PAK Z: 20xPNP Small Signal 3702 Type E1  
LOOK. Plastic powder. Lo Noise. Hi Speed for Digital switching etc. Similar to BFY51 spec. 60 volt 20 watt. Bulk Pak of 100 E8\*

**TRANSISTORS**

Matching 20p*	ins Kit 10p*
AC127 17p*	BD131 37p*
AC136 10p	BD132 37p*
AC187 20p*	BD955 69p*
AC188 20p*	BD956 69p*
AD161 40p*	BFY50 16p*
AD162 40p*	BFY51 16p*
AF239 42p*	BF229 28p*
BC107 6p*	BSX20 18p*
BC108 7p*	MJE2955 E1*
BC109 8p*	MJE340 44p*
BC109C 12p*	MJE2955 75p*
BC147 15p*	MJE3055 75p*
BC148 12p	MPU131 35p*
BC149 12p	DR12(P) 49p*
BC157 15p	TIP41A 60p*
BC158 15p	TIP42A 60p*
BC159 15p	TIP2955 60p*
BC167 10p	TIP3055 50p*
BC168 11p	TIS43 55p*
BC169 12p	2N2646 39p*
BC177 18p*	2N2905 22p*
BC178 16p*	2N3706 9p*
BC179 18p*	2N3819 10p*
BC182 10p	2N3053 15p*
BC183 10p	2N3614 E1*
BC183 10p	2N3702 9p*
BC183 10p	2N3704 9p*
BC184 10p	2N3706 9p*
BC184 10p	2N3819 10p*
BC212 12p	2N3820 38p*
BC212 12p	2N3904 15p*
BC213 12p	2N3906 15p*
BC213 12p	2N9547 32p*
BC214 12p	2N3777 44p*
BC214 12p	TIL211 E2*
BC271 20p*	TIL63 E1*

**7400M SERIES TTL ALL FULL SPEC FANTASTIC PRICES**

7400	7p*	7475	44p*
7401	7p*	7476	29p*
7402	10p*	7480	35p*
7403	10p*	7481	99p*
7404	14p*	7482	99p*
7405	7p*	7483	99p*
7406	25p*	7485	99p*
7407	26p*	7486	35p*
7408	12p*	7490	29p*
7409	12p*	7491	50p*
7410	10p*	7492	33p*
7411	22p*	7493	33p*
7412	22p*	7494	69p*
7413	25p*	7495	69p*
7414	25p*	74100	99p*
7417	25p*	74107	29p*
7420	7p*	74121	27p*
7423	26p*	74123	49p*
7425	26p*	74141	95p*
7430	7p*	74157	50p*
7432	20p*	74145	85p*
7440	14p*	74147	E1.65*
7441	7p*	74152	E2*
7442	87p*	74154	E1.69*
7445	50p*	74155	80p*
7447	75p*	74156	80p*
7450	15p*	74157	50p*
7451	15p*	74164	99p*
7453	15p*	74174	99p*
7454	15p*	74176	99p*
7460	15p*	74190	E2*
7470	12p*	74193	E1*
7472	25p*	74196	E1.30*
7473	25p*		
7474	29p*		

**CMOS PUT VALUE ALL GOOD BRANDS**

4000	13p*
4001	13p*
4002	17p*
4006	E1*
4007	18p*
4008	92p*
4009	49p*
4010	56p*
4011	13p*
4012	18p*
4013	55p*
4015	93p*
4016	52p*
4017	99p*
4018	99p*
4020	99p*
4021	99p*
4022	99p*
4023	20p*
4024	76p*
4025	E1.96*
4027	55p*
4028	50p*
4029	99p*
4030	58p*
4032	99p*
4034	E2*
4035	E2.02*
4038	E1.02*
4041	86p*
4042	81p*
4043	96p*
4044	85p*
4046	E1.30*
4047	99p*
4049	52p*
4050	E1.15*
4053	E1.10*

**DIL SOCKETS** Disc 10 amp Lo Profile 400v E1\*  
8. 14 or 15 Pin 12p\*  
18 Pin 25p\*  
24 & 28 Pin 50p\*  
C106 4x 400v 40 Pin 75p\* 50p\*

**TRIACS**  
Disc 10 amp 400v E1\*  
SCR 1A 400v 50p\*  
C106 4x 400v 50p\*

**IC SUPERMARKET**

301 Op Amp	30p*
555 Timer (NE555)	26p*
556 Dual Timer	60p*
709 DIL 14	25p*
710 Comparator	40p*
723 Regulator	45p*
741C 8 Pin DIL OPA	17p*
741 Pin Op Amp	33p*
747 DIL 741	50p*
748 Op Amp	33p*
3000 Quad Op Amp	45p*
7805 1 amp 5 volt	60p*
7805 (TO3) 100mA	E1*
7808, 7812, 7815	60p*
8038 Sig Gen	E3.55*
7900 Series	E1.35*
7413 & 74023	85p*
CA3130	75p*
CA3140	80p*
CA3064	49p*
CA3065	49p*
LM200 2 1/2 amp 3-30v	E3*
LM200 Regulator	E3.50*
LM3801 1 watt amp	75p*
LM3801 Dual Preamp	E1.05*
LM3807 Quad Ramp	50p*
LM3900 Quad OPA	45p*
MC1460. 61 & 69 All	E3*
MCMS 14433 A/O	E1.05*
NE536 Fet OPA	E4*
T8017 7WAF	E1
TL071 Lo Noise 741	75p*
TL081 Fet 741	69p*
TL080 Fet 748/308	E1.49*
TL170 Dual Effect	69p*
TL170 Dual	10p*

# CLICK ELIMINATOR

**The Cat Sat On The Mat: or was there one of your favourite records on the mat? Never mind — ETI steps in to rescue your valuable vinyl from those evil clicks and pops.**

EVEN THE MOST fastidious of record collectors must have some records in his collection which during their career have picked up the odd scratch or two. Perhaps your record collection dates back to the time before you obtained that second mortgage, sold the wife or whatever, to get the latest in laser controlled fluid damped, tangential tracking phonograms, sorry record deck, and the previous system has left it's mark on these early platters.

## In The Click Of Time

However the scratches got there, they are bound to be obtrusive on any reasonably Hi-Fi set up and even if you do not qualify for the title Hi-Fi purist — someone who listens, not to the music, but to the defects, real or imagined, in the Hi-Fi chain — the clicks will detract from your enjoyment.

Enter ETI — we can help. The click suppressor described here will remove or greatly reduce the audible transient sounds — nice phrase — resulting from scratches on a record's surface.

## Design Decisions

When designing a click suppressor it is fairly obvious that we have to be able to tell the click from the cacophony as it were. Fortunately a click has several unique characteristics which set it apart from a music signal. For instance it will have very fast attack and delay times — even high frequency percussive sounds will delay slowly, although attack will be fast. A click will also be of a very short duration — again musical sounds are in general of a longer duration.

Once we have spotted our click, it is necessary to remove it. In our case we substitute a short period of silence

— subjectively unnoticeable — in place of the click.

As our click detection circuit requires a finite time in which to operate, we will also have to provide some sort of delay for the music signal within the system. Our circuit, and all the commercially available units, use a CCD delay line to provide this delay. It is the recent availability of this device that has made the click suppressor possible, or rather brought it within the financial reach of the constructor. ▶

**Next month we will be giving the full details for building and setting up the Click Eliminator**



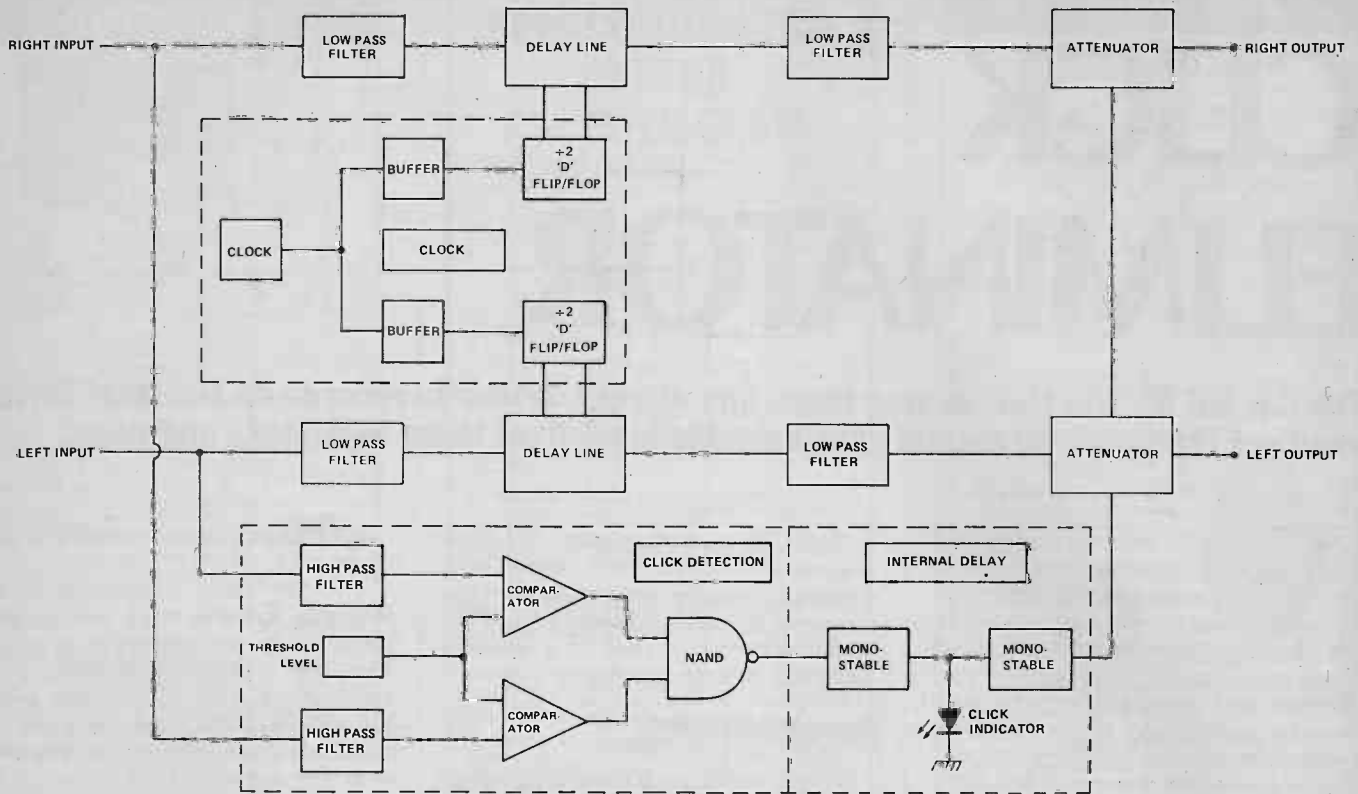


Fig. 1. Block diagram of the ETI click eliminator.

## HOW IT WORKS

Overall operation of the circuit can best be understood by reference to the block diagram shown in fig 1. The signal from each of the inputs is fed both to a delay line, with associated low pass-filters, and to the "Click Detection" block. This provides a negative going signal at its output coincident with a click appearing on either input channel.

With the click identified, the next step is to remove it without affecting the subjective quality of the program material. The circuit operates by dramatically attenuating the signal passing through the unit for a brief period of time "Either Side" of the click.

If the attenuation is large enough and it's period accurately synchronised to the occurrence of the click, the effectiveness of the unit is dramatic. The loss of program material during this blanking period which might be thought to be as objectionable as the click itself, seems to produce little subjective disturbance.

It has been shown that periods of attenuation of this nature, up to 10ms, do not unduly disturb the signal, and the 2ms or so necessary to "straddle" a click goes entirely unnoticed.

It is necessary to incorporate a delay line within the circuit as a finite time is necessary for the click detection circuits to operate. The chain of events is shown in fig 2. The click is fed to the input of the delay line and at some time later will emerge from this device where it is passed to the attenuator. Meanwhile the click has been detected and activates two 555 timers acting as monostables. The first provides a click detection indicator for the front panel. As this returns to its stable state, it triggers the second 555. It is this IC that causes the 570 IC to suppress the signal.

By careful selection of the timing components associated with the 555's, the signal is blanked during the time when the click is emerging from the delay line.

A detailed description of the various circuit blocks now follows.


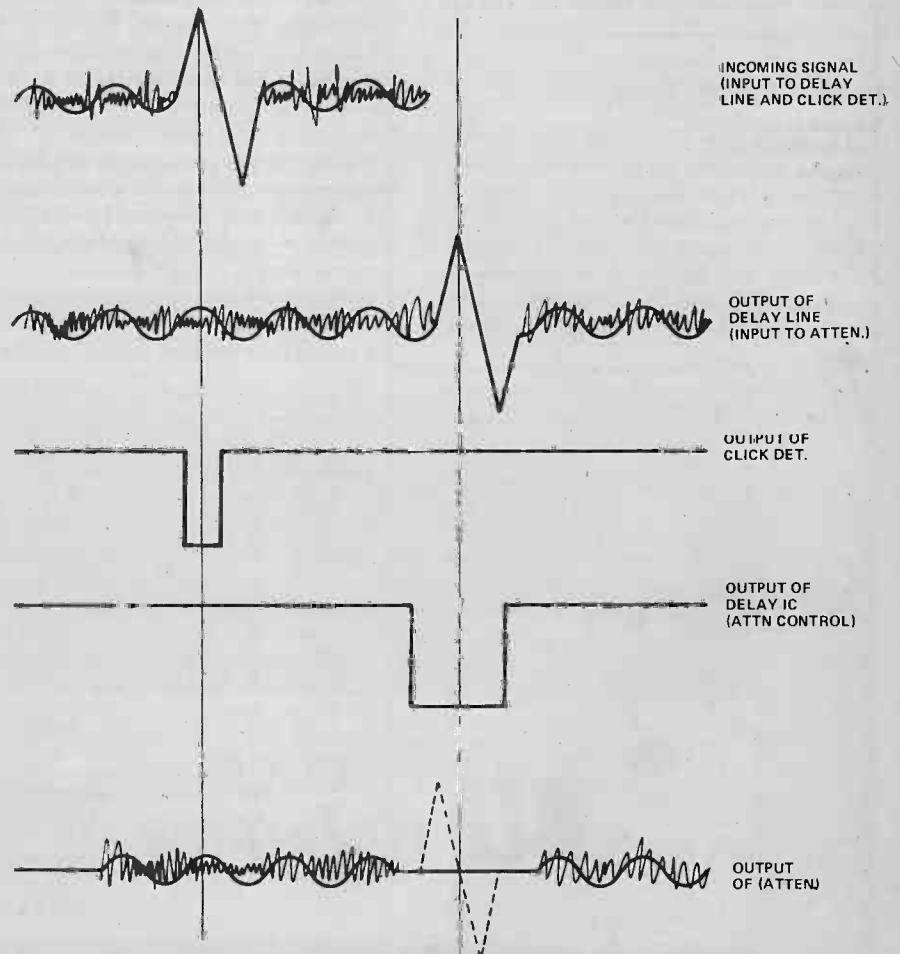


Fig. 2. Above are shown the waveforms that illustrate the action of the circuit when a click has been identified and is to be suppressed.

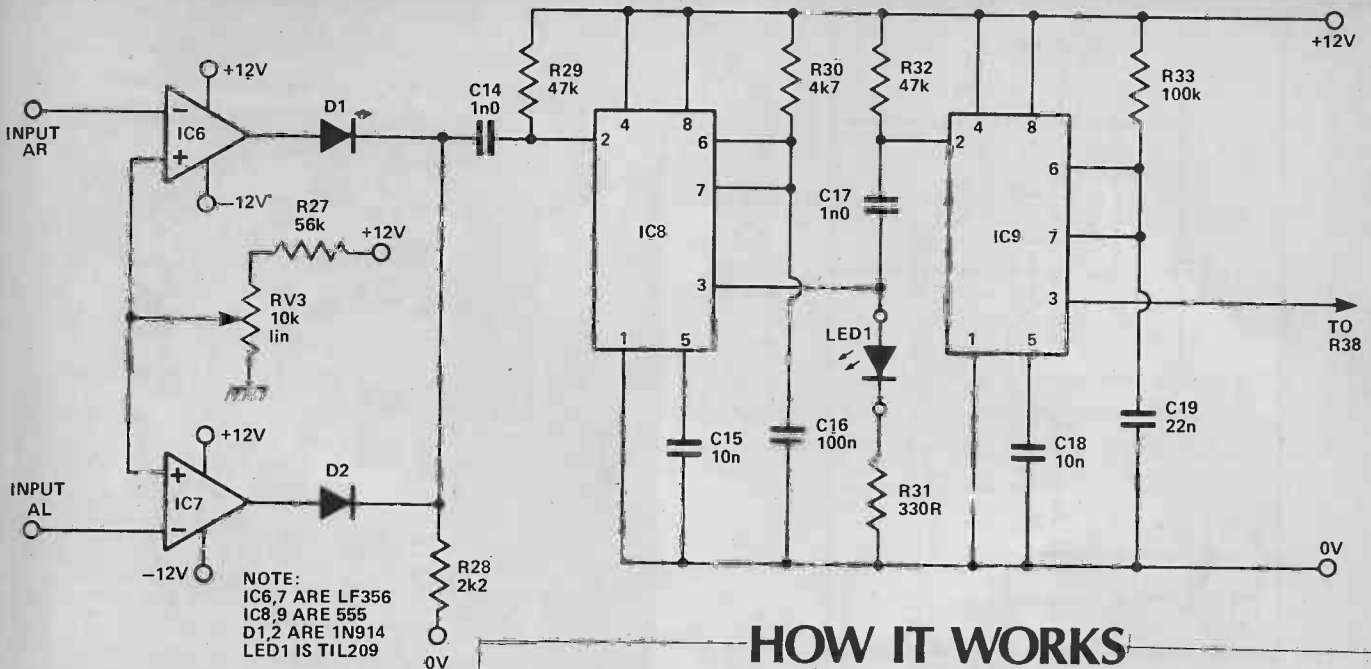

# PROJECT: Click Eliminator



## HOW IT WORKS

### CLICK DETECTOR AND ATTENUATOR CONTROL

Outputs from the low pass filters described above are passed to comparators IC6 and 7. The outputs of these IC's are usually high, but if the level at their inputs exceeds a level (set by RV3) they will go low. This control is set such that the comparator will operate only when a high amplitude click is passed to IC6 and IC7, the click being of greater amplitude than the program material.


Another unique characteristic of a click is that it will appear on both channels simultaneously. We therefore pass the outputs of the comparator IC's to the NAND gate formed by D1, D2, and R28. The junction of these components and C14 will be high unless both the comparator outputs are low. A negative going signal applied to IC8 via

C14 will trigger this IC and illuminate LED 1 the click indicator LED. After X mS the IC's output will return to its stable state and in so doing will trigger IC9. This IC controls the attenuator and will suppress the program material during its stable state.

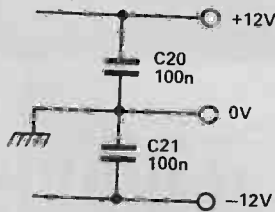
### ATTENUATOR STAGE

The attenuator is built around an NE570 dual compandor IC (see data sheet Oct 77 p.59). The inputs to the IC are at pins 14 and pin 3, the outputs — with suitable filters — are taken from pins 10 and 7. Gain control is achieved by robbing current from the NE570.

As the input to Q1 is taken high, the device will start to conduct and thus rob the NE570 of current, thus reducing the gain of the amplifier within the device. The control action is set up by RV4.




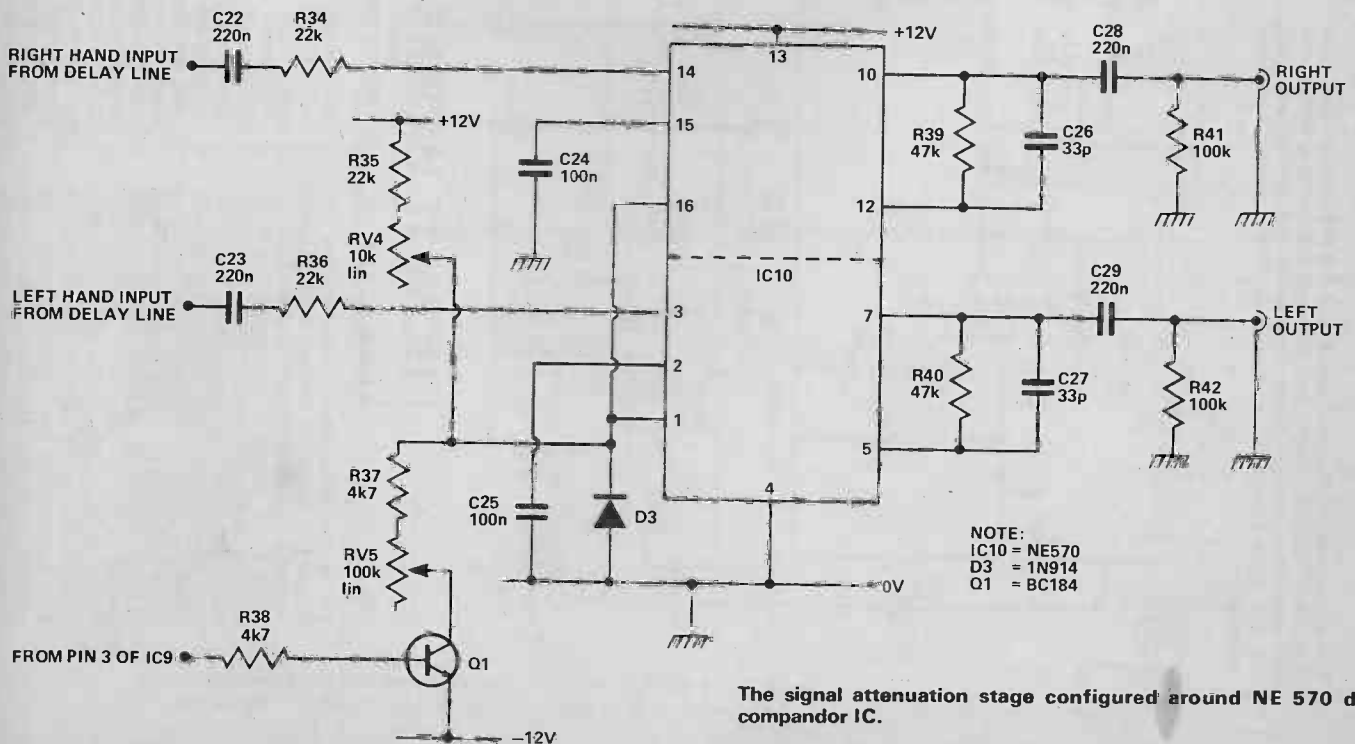Second stage of the "click detection" circuitry.



The signal attenuation stage configured around NE 570 dual compandor IC.

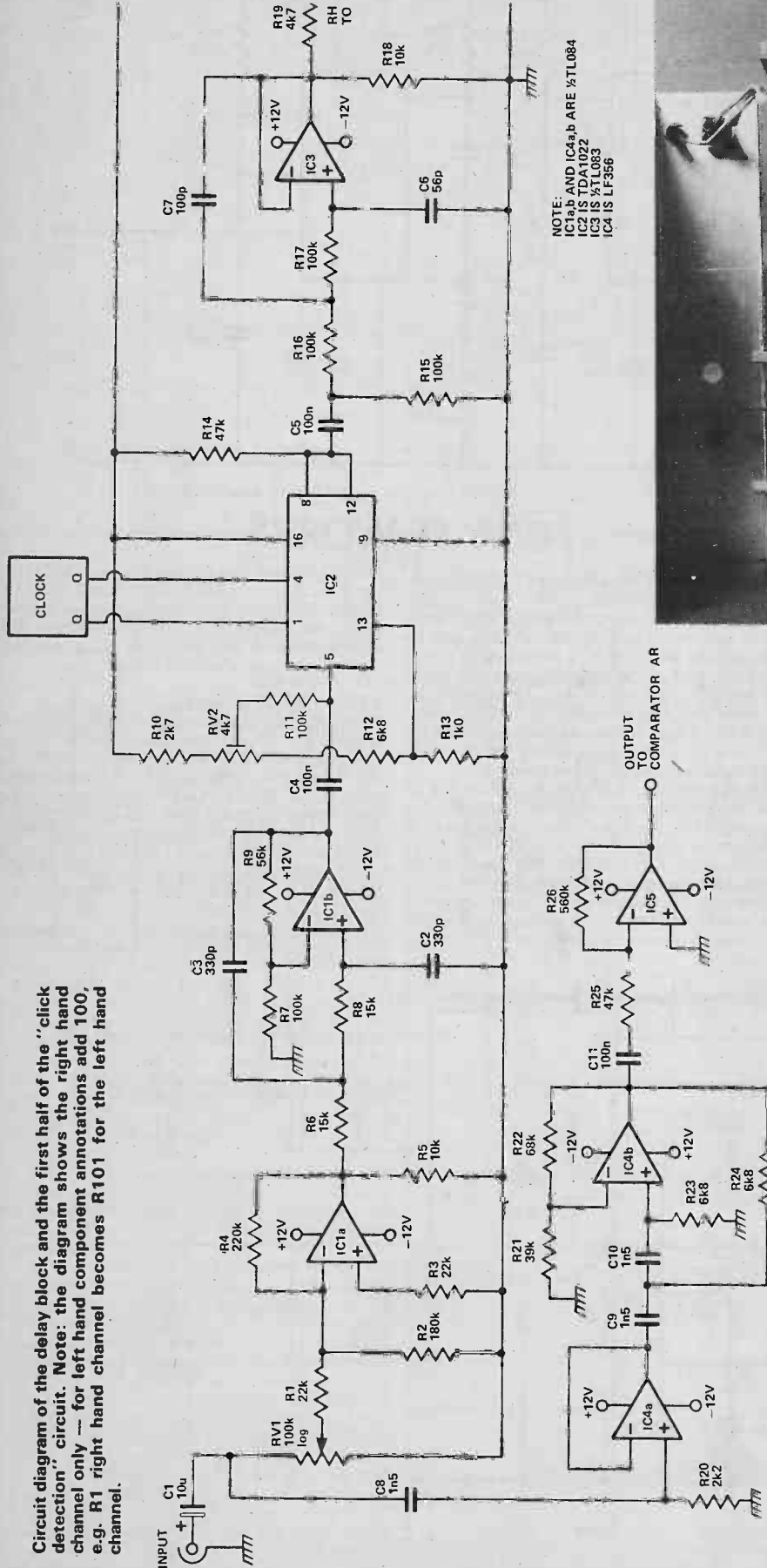Circuit diagram of the delay block and the first half of the "click detection" circuit. Note: the diagram shows the right hand channel only — for left hand component annotations add 100, e.g. R1 right hand channel becomes R101 for the left hand channel.




NOTE:  
IC1a,b AND IC4a,b ARE 1/2 TL084  
IC2 IS TDA1022  
IC3 IS 1/2 TL083  
IC4 IS LF356

## HOW IT WORKS
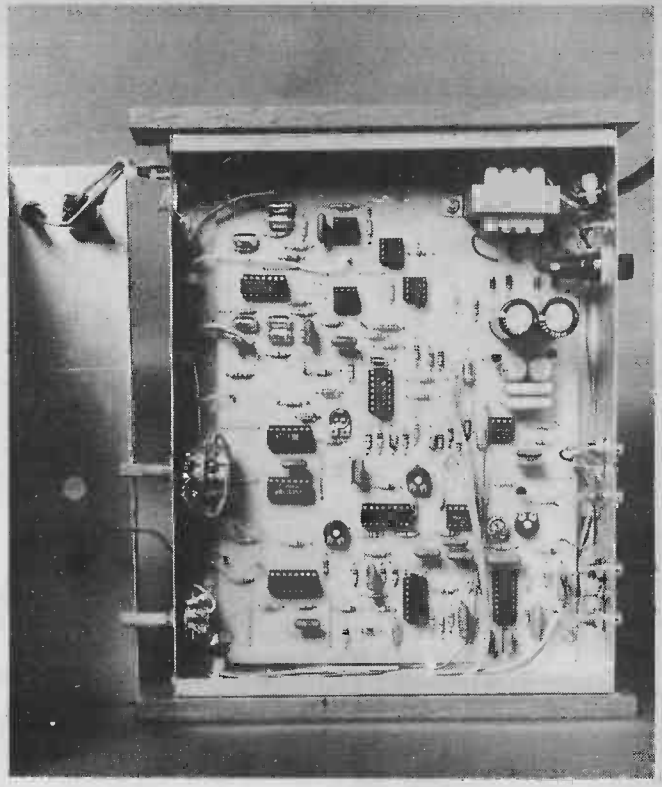
### DELAY LINE AND FIRST STAGE OF CLICK DETECTOR

The circuit block shown above forms one channel of the delay line and click detector circuitry (the other channel is identical). The input signal is first passed to IC1a, which is configured as an inverting amplifier. The output from this stage is fed to IC1b and associated components. This stage forms a second order Butterworth filter with an upper 3dB point of about 18kHz. The stage also has a small amount of gain in its pass band. This configuration ideally meets the drive requirements of the delay line, which suffers from an insertion loss, made up for by the passband gain and must have the maximum frequency applied to it limited to, in this case, the audio spectrum of frequencies. The reason for the frequency limit is that the maximum frequency fed to a delay line must not be greater than half the frequency of the

clock signal superimposed on the output that might cause HF overload in subsequent stages. The input of the delay line is pin 5, the filter section that forms the first stage of the click detector. A click has a number of unique characteristics, one of which being that it is rich in HF energy — a result of its fast attack and delay time. The effect of passing the music signal through a low pass filter will be to highlight the high energy click amongst the generally low high frequency content of normal program material. The low pass filter is once again built around a second order Butterworth stage. The signal is passed to this stage after a simple HF filter and buffer (IC4a). The output from the filter is amplified by inverting amplifier IC5 and fed to the second half of the



click detector described below.

**CLOCK AND POWER SUPPLY**

Pins 1 and 4 of the delay line must be presented with 180° out of phase wave forms. The clock signal is generated by the CMOS oscillator based around IC11a and b, which after buffering is fed to the two D type flip-flops contained within IC12. The Q and Q' outputs of this device provide the required 180° out of phase drive signals.

The power supply is a straightforward design based on two three-terminal regulators.

clock signal used in controlling the device. If this precaution is not observed, the result is severe distortion.

The clock drive circuitry is described below.

The input of the delay line is pin 5, the resistor chain R10, R11, R12, R13 and RV2 is to hold pin 13 at 1V0 above ground, this ensures maximum dynamic range in the delay line, and to bias pin 5 for class A operation which minimises distortion.

The output from the delay line is taken, via C5, to another Butterworth filter, this stage being used to remove any high frequency

- RESISTORS**
- R1, 3, 34, 35, 36, 22k
  - R2, 102, 180k
  - R4, 104, 220k
  - R5, 18, 105, 118, 10k
  - R6, 8, 106, 108, 15k
  - R7, 11, 15, 16, 17, 33, 38, 41, 42, 107, 111, 115, 116, 117, 100k
  - R9, 27, 109, 56k
  - R10, 110, 2k7
  - R12, 23, 24, 112, 123, 124, 6k8
  - R13, 44, 113, 1k0
  - R14, 19, 25, 29, 32, 39, 40, 43, 114, 119, 125, 47k
  - R20, 28, 120, 2k2
  - R21, 121, 39k
  - R22, 122, 68k
  - R26, 126, 560k
  - R30, 37, 4k7
  - R31, 330R

**POTENTIOMETERS**

- RV1 +101, 100k log gang
- RV2, 102, 4k7 min. preset
- RV3, 10k
- RV4, 6, 10k min. preset
- RV5, 100k min. preset

**CAPACITORS**

- C1, 101, 100n polyester
- C2, 3, 37, 102, 103, 330p polystyrene
- C4, 5, 11, 16, 20, 21, 24, 25, 30, 104, 105, 111, 100n polyester
- C6, 106, 56p polystyrene
- C7, 107, 100p polystyrene
- C8, 9, 10, 108, 109, 110, 1n5 polystyrene
- C12, 13, 35, 36, 47u 16V electrolytic
- C14, 17, 1n0 polystyrene
- C15, 18, 10n polyester
- C19, 22n polyester
- C22, 23, 28, 29, 220n polyester
- C26, 27, 33p polystyrene
- C31, 32, 1000u 25V electrolytic
- C33, 34, 470n polyester


**SEMICONDUCTORS**

- IC1, 4, TL084
- IC2, TDA1022
- IC3, TL083
- IC5, 6, 7, 105, LF356
- IC8, 9, 555
- IC10, NE570
- IC11, 4001
- IC12, 4013
- IC13, 78L12
- IC14, 79L12
- Q1, BC108
- D1, 2, 3, 1N914
- D4, 5, 6, 7, 1N4001
- LED1, 2, T1L209

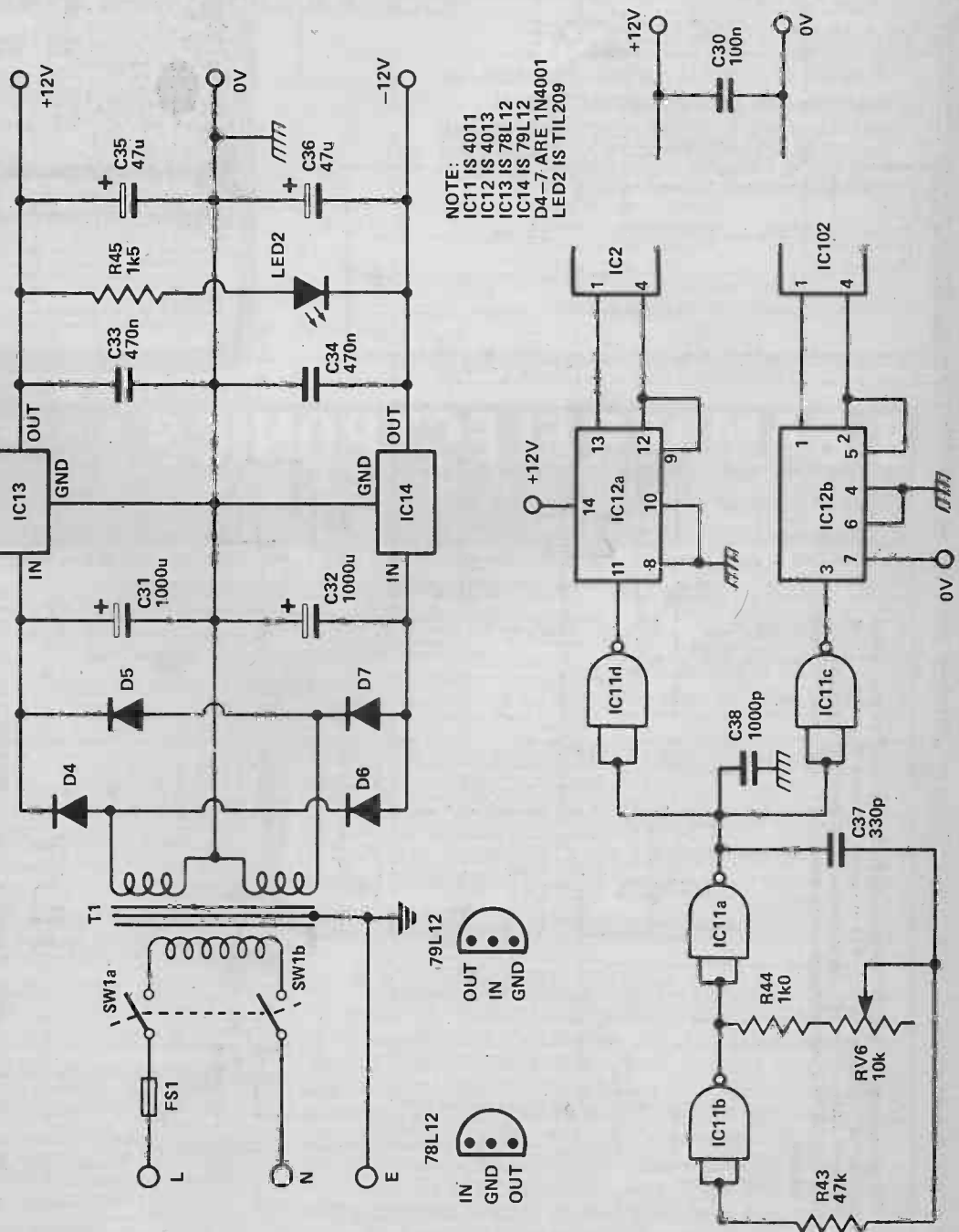
**MISCELLANEOUS**

PCB as pattern, case (Maplin B3), phono sockets, fuse (500mA) plus holder, switch (DPDT), knobs to suit, cable etc.

The power supply and delay line clock generator circuit.



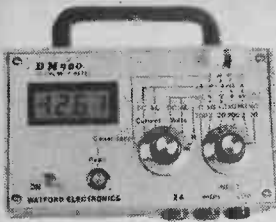NOTE:  
 IC11 IS 4011  
 IC12 IS 4013  
 IC13 IS 78L12  
 IC14 IS 79L12  
 D4-7 ARE 1N4001  
 LED2 IS T1L209



**Introducing DM900 - The DIGITAL MULTIMETER with "Hidden Capacity" - It measures Capacitance too!**

(as published in E.T.I. August 1978)  
 Away with analogue meters for some of these you may often as not use a crystal ball to make circuit measurements instead gaze into our crystal - not a ball but the 3 1/2 0.5" LIQUID CRYSTAL DISPLAY - on our amazingly accurate DMM incorporating:

- 5 AC & DC Voltage ranges; 6 resistance ranges
- 5 AC & DC Current ranges; 4 Capacitance ranges

The prototype accuracy is better than 1%

This is a unique design using the latest MOS ICs and due to the minimal current drain, is powered by one only PP3 battery. There is also a battery check facility.

The DM900 is an attractive hand-held, light weight device, built into a high impact case with carrying handle and has been ingeniously designed to simplify assembly.

Never before have all these features been offered to the electronics enthusiast in a single unit.

Complete Kit Only **£54.50\*** (p&p Insured add 80p)

Optional Extras Probes **£1.50\*** Carrying Case **£1.50\***

Calibration service charge for working Units only **£5.75.**

Ready-built and tested units only **£78.50\*** incl. Case & probes p&p 80p

Demonstration on our Shop

JACK PLUGS	SOCKETS			SWITCHES*	SLIDE 250V
Screened chrome	Plastic body	open metal	moulded with break	2A, 250V	1A DPDT 14p
2.5mm 12p	8p	8p	11p	SPST 28p	1A DPDT c/over 15p
3.5mm 15p	10p	8p	12p	DPST 34p	1/2A DPDT 13p
MONO 23p	15p	13p	20p	DPDT 38p	4 pole 2-way 24p
STEREO 31p	18p	15p	24p	4 pole on/off 54p	PUSH BUTTON Spring loaded
				SUB-MIN TOGGLE	SPST on/off 60p
				SP changeover 59p	SPDT c/over 65p
				SPST on/off 54p	DPDT 6 Tag 85p
				SPST biased 89p	MINIATURE Non Locking Push to Make Push Break 15p
				DPDT 6 tags 70p	
				DPDT centre off 79p	
				DPDT Biased 115p	
				ROTARY Make your own multiway Switch. Adjustable Stop Shifting Assembly. Accommodate up to 6 Wafers. Mains Switch DPST to fit Break Before Make Wafers. 1 pole/12 way, 2p/6 way, 3p/4 way, 4p/3 way, 6p/2 way	
				Spacer and Screen 47p	
				ROTARY (Adjustable Stop) 1 pole/2 to 12 way, 2p/2 to 6 way, 3 pole/2 to 4 way, 4 pole/2 to 3 way 41p	
				ROTARY Mains 250V AC, 4 Amp 45p	
DIN	PLUGS	SOCKETS	In Line		
2 PIN Loudspeaker 3, 4, 5 Audio	11p	7p	18p		
	13p	8p	20p		
CO-AXIAL (TV)	14p	14p	14p		
PHONO	9p	5p single	15p		
assorted colours	12p	8p double	-		
Metal screened		10p 3-way	20p		
BANANA	4mm 11p	12p	-		
2mm 10p	10p	-			
1mm 7p	7p	-			
WANDER 3 mm	8p	8p	-		
DC Type	15p	20p	-		
AC 2-pin American	15p	15p	-		

**VOLTAGE REGULATORS**

TO3 Can Type p  
 1A +ve 5V, 12V, 15V, 18V **145**  
 MVR5 or 12 **150**  
 1A -ve 5V, 12V, 15V **220**

Plastic (TO92)  
 +ve 0.1A 5V, 6V, 8V, 12V, 15V **30**

+ve 1A (TO220)  
 5V, 12V, 15V, 18V, 24V **85**

-ve 0.5A 5V, 6V, 8V, 12V, 15V **86**

-ve 1A 5V, 12V, 15V **110**

-ve 0.1A (TO92)  
 5V, 12V, 15V **60**

LM309K **135**  
 LM320-12 **105**  
 LM320-15 **165**  
 LM323K **598**  
 LM304H **240**  
 LM317H **100**  
 LM317K **350**  
 LM325N **240**  
 LM326N **240**  
 LM723 **45**

**EARPHONES**

Magnetic  
 2.5mm **18p**  
 3.5mm **18p**  
 Crystal **33p**

**ULTRASONIC TRANS-DUCERS**  
**£3.95\*** per pair

**TRANSFORMERS\*** (Mains Prim. 220-240V)

6-0.6V-100mA, 9-0.9V 75mA, 12-0-12V 100mA **95p**

8VA: 6V-5A 6V-5A; 9V-4A 9V-4A; 12V-3A 12V-3A; 15V-2.5A 15V-2.5A **195p**

12V: 4.5V-1.3A 4.5V-1.3A; 6V-1.2A 6V-1.2A; 12V-5A 12V-5A; 15V-4A 15V-4A; 20V-3A 20V-3A **220p (20p p&p)**

24VA: 6V-1.5A 6V-1.5A; 9V-1.3A 9V-1.3A; 12V-1A 12V-1A; 15V-8A 15V-8A; 20V-6A 20V-6A **290p (45p p&p)**

50VA: 6V-4A 6V-4A; 9V-2.5A 9V-2.5A; 12V-2A 12V-2A; 15V-1.5A 15V-1.5A; 20V-1.2A 20V-1.2A; 25V-1A 25V-1A; 30V-8A 30V-8A **350p (50p p&p)**

100VA: 12V-4A 12V-4A; 15V-3A 15V-3A; 20V-2.5A 20V-2.5A; 30V-1.5A 30V-1.5A; 40V-1.25A 40V-1.25A; 50V-1A 50V-1A **650p (60p p&p)**

**COMPUTER HARDWARE\***

(N.B. p&p charge to be added above our normal postal charge.)

KNOBs\* to fit 1/4" shaft  
 K1 Black Pointer type **9p**  
 K1a White Pointer type **11p**  
 K2 Slim Silvered Aluminium **12p**  
 K3 Satin Black Ribbed 22mm diam. **22p**  
 K4 Black Serrated Metal top with line indicator 35mm diam. **20p**  
 K4a As K4 but 25mm diam. **20p**  
 K5 Black Fluted, metal top & skirt, calibrated 0.9, 37mm diam. **28p**  
 K6 As K5 but with pointer on skirt **28p**  
 K7 Black Knurled, tapered, metal top & skirt. Calibrated 0.9, 30mm, **26p**  
 K7a As above but pointer on skirt **26p**  
 K8 Black or Silvered for Slider Pot **10p**  
 K12 Aluminium plastic with line indicator, 22mm diam. **16p**  
 K19 Soid Aluminium Amplifier Knob. Etch line indicator, skirted 22mm **30p**

2101 **99**  
 2102 **100**  
 2111 **175**  
 2114 **650**  
 2516 **TBA**  
 2532 **TBA**  
 2708 **650**  
 27L08 **995**  
 2716 **1650**  
 3064 **TBA**  
 4027 **180**  
 4045 **750**  
 74S188 **165**  
 74S262 **875**  
 74S287 **325**  
 74S470 **325**  
 74S475 **825**  
 81LS95 **70**  
 81LS96 **70**  
 9900 **£35**  
 9980 **TBA**  
 325 **TBA**  
 TMS6011 **TBA**  
 Z80 **TBA**

**ALUM. BOXES\***

WITH LID p  
 3x2x1" **45**  
 2 1/2x5 1/2x1 1/2" **68**  
 4x4x1 1/2" **68**  
 4x2 3/4x1 1/2" **60**  
 4x5 1/4x1 1/2" **78**  
 4x2 1/2x2" **64**  
 5x4x2" **82**  
 6x4x2" **88**  
 7x5x2 1/2" **114**  
 8x6x3" **148**  
 10x7x3" **172**  
 10x4 1/2x3" **142**  
 12x5x3" **142**  
 12x8x3" **210**

**PANEL METERS\***

FSD  
 60x46x **45**  
 35mm **35mm**  
 0-50uA **0-500uA**  
 0-100uA **0-500uA**  
 0-1mA **0-5mA**  
 0-10mA **0-50mA**  
 0-100mA **0-500mA**  
 0-1A **0-2A**  
 0-25V **0-50V AC**  
 0-300V AC **0-500V AC**  
 475p each

4 1/2x3 1/2x1 1/2  
 0-50uA **120**  
 0-100uA **100**  
 0-500uA **100**  
 0-1mA **595p each**

**HEAT SINKS\***

TO92 **8p**  
 TO5 **9p**  
 TO18 **9p**  
 TO220 **24p**  
 TO3 **24p**  
 TO66 **24p**

**CMOS\***

393	230	4018	89	4046	128	4085	74	4450	295	VDU Chip and MODULE for TV
395	218	4019	48	4047	87	4086	73	4451	295	Convert your TV into a VDU by using the new Thompson CSF TV-CRT controller chip
396	215	4020	99	4048	58	4089	150	4452	695	SF-F96364, 16 line by 64 characters text refreshment, Cursor management, Cursor management on screen. Line erasing. Compatible with any computing system.
398	276	4021	91	4049	48	4093	85	4490F	525	SF-F96364E <b>£11.75*</b>
399	230	4022	88	4050	48	4094	190	4490V	525	AV-3-10115 <b>£5.60*</b>
445	150	4023	20	4051	72	4096	105	4501	17	AY-5-1012UART <b>£4.50*</b>
447	144	4024	66	4052	72	4097	372	4502	120	1301 ROM <b>£8.20*</b>
490	180	4025	19	4053	72	4098	110	4503	69	SF80102 RAM <b>£2.05*</b>
668	182	4026	180	4054	110	4099	145	4507	55	74LS163 <b>£1.18*</b>
669	182	4027	45	4055	128	4160	109	4508	51	SN75451 <b>£1.20*</b>
670	248	4028	81	4057	2570	4161	109	4508	298	SN75452 <b>70p*</b>
		4029	99	4059	480	4162	109	4510	99	SN75454 <b>£2.25*</b>
		4030	58	4060	115	4163	109	4511	150	UHF Modulator <b>£2.50*</b>
		4031	205	4063	110	4174	110	4512	98	Complete Module <b>£136.50*</b>
4000	15	4032	100	4066	58	4175	99	4513	206	(Send 30p stamps for full technical data)
4001	17	4033	145	4067	380	4194	108	4514	265	
4002	17	4034	196	4068	22	4408	720	4515	299	
4006	105	4035	111	4069	20	4409	720	4516	125	
4007	18	4036	325	4070	32	4410	720	4517	382	
4008	87	4037	100	4071	21	4412F	1650	4518	102	
4009	50	4038	108	4072	21	4412V	1380	4519	55	
4010	18	4039	320	4073	21	4415F	795	4520	108	
4011	18	4040	105	4075	23	4415V	795	4521	188	
4012	42	4041	80	4076	85	4419	280	4522	199	
4014	86	4042	75	4077	40	4422	545	4527	152	
4015	89	4043	94	4078	21	4433	1099	4528	99	
4016	45	4044	88	4081	20	4435	825	4529	165	
4017	89	4045	145	4082	21	4440	1275	4530	85	

# .....news digest.....



**POCKET ADVANTAGE**

A wallet type machine with hold-on memory. The new TI 50 has two memories, some scientific features and will turn itself off after 15 minutes if you aren't using it. Up to 15 levels of parenthesis are allowed. There is even a 'battery low' indicator.

Available now, it will cost under £30 and be in most shops that sell this sort of thing.

**SCREEN TEST**

The UK is now Hong Kongs largest market for TV games. We absorbed 26% of their export in the field, some 523,506 items if you please, in the first eight months of this year. Germany finished second

on 22% and the USA came third with 13%.

Somewhat of a surprise, and a shame, that we take more than the States of these items. I always thought we had more taste.

**SHORTS**

● Every Ready - now called Berec - have released four rechargeable consumer batteries, in the HP2, HP11, HP7 and PP3 varieties. Chargers are also available. An undoubted reaction to the phenomenal loss of dry cell power these days.

● Fairchild are making a big fuss about having their F16K Dynamic 16K RAMs available at last. Access times vary from 150 ns to 300 ns.

● Direct drive turntables yes. But direct drive MPUs? Also yes - now. The S2000 is a new release from AMI which can drive fluorescent displays directly, with HT drive and 7-segment decoding on chip. Also on board 64 x 4 RAM and 1K ROM. Intended for low lost applications.



● Ingersoll - the tick tock people - are into electronics. They have released three TV games, three clock radios, two Door Chimes, and a portable micro cassette player. Photo shows one of their new TV games. It must be Christmas.



# BORIS IN CHECK

There are quite a few chess machines lying around the shops these days, and this one has a reputation for being one of the best. Armed with his "Best of Spassky Volume 2" Ron Harris went to check it out.

BORIS is a multi-level chess machine with the disconcerting ability to comment on its opponent's (your) moves. The level of its analysis is set by the user who determines how long BORIS may consider its reply. Thus a tyro may set the machine to minimum time to begin with, and steadily advance the machine as he improves.

## Present Arms

The presentation of the machine is excellent. The electronics consist of an F8 based system accessed by a 16 (multi-function) key array and interfaced to the outside world by a display consisting of eight alpha numeric devices. These are packed into a very smart wooden case which also holds the mains adaptor and chess pieces. A board is also provided, but is of a standard which suggests it is included out of duty rather than devotion. Alas, the chess pieces fall into this lamentable category also, but improvements are now being made by the importers, and the quality of replacements is much higher.


On the two units we were able to examine the mains adaptor terminates in a two pin American 'hi-fi' type of plug — which now fails BS of course. This is moulded into the adaptor body and makes life very awkward for the buyer. At first glance there is no way of getting mains into BORIS aside from wrapping wires around them. DANGEROUS. The importers *must* look into this very quickly. We are assured they are doing so — let us hope.

In the meanwhile I would advise purchasers to take a trip down to good ole Woolies and make off with one of their shaving adaptor plugs, into which BORIS's adaptor will neatly plug. 240V AC is a poor opening gambit in any game.
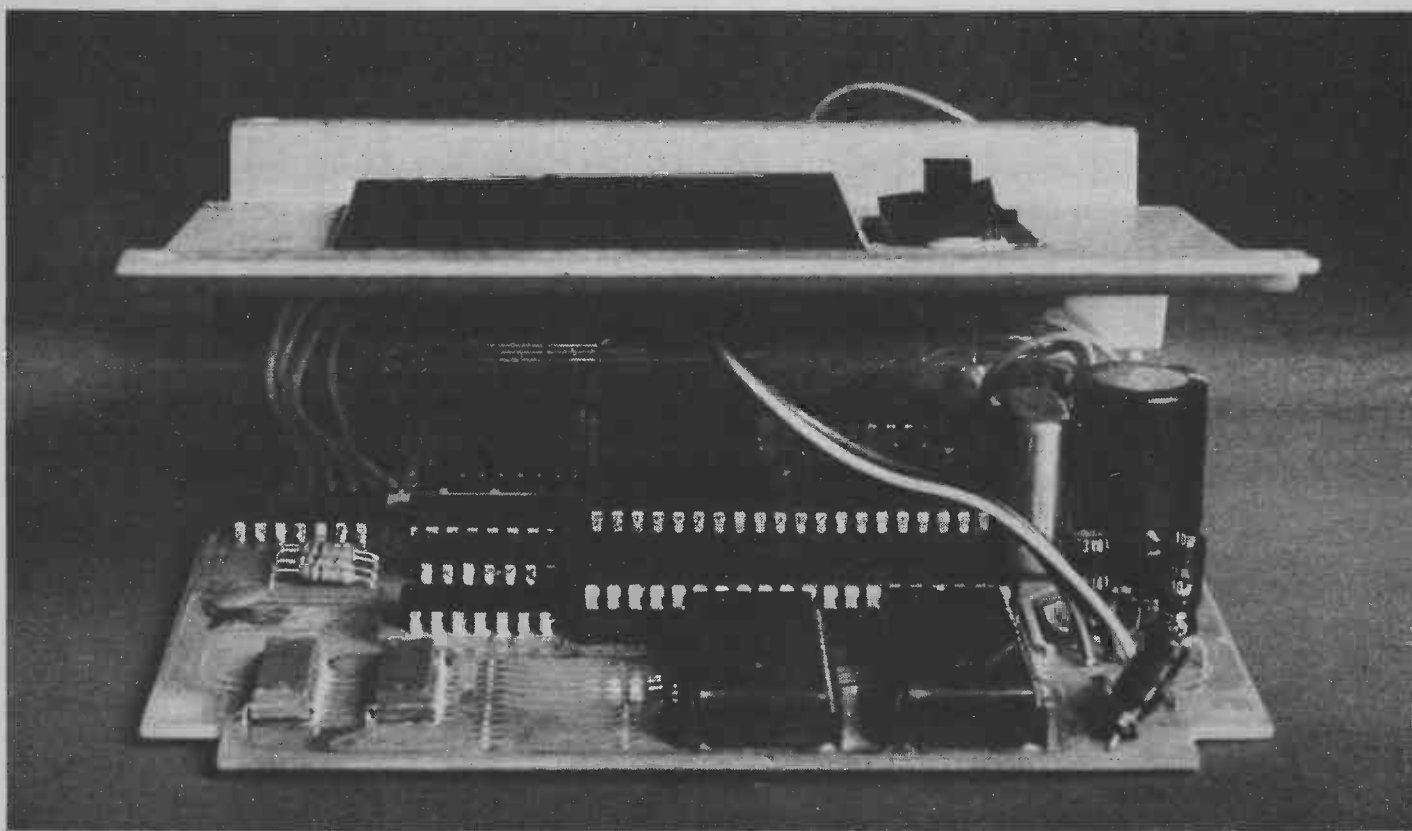
## Getting Rooked . . . and Pawned And . . .

Using this machine is both simple and interesting. The keyboard sets up your move on the display — which is also showing elapsed time — and the ENTRY key presents it to BORIS for reply.





**BORIS exposed to the world!**

Once he's thinking about, the display flashes at 1 Hz, the timer counts down the time allotted to BORIS and the various moves he's cogitating appear on the display, settling finally at time 00 seconds. The display then counts down *your* time — but there's no penalty for not playing inside the time limits you've imposed on BORIS.

If for some reason (like cheating) you wish to alter the board at any time during a game, pressing RANK displays the contents of each row of the board using a very ingenious symbols set. The keyboard now creates or destroys pieces as required. Korchnoi could have done with *that* in his armoury. This makes correcting errors very easy.

Use of the RANK key while BORIS is having a think lets you watch the pieces moving around in his head(!?). Hypnotic.

### Alpha-numeric Big Mouth

Undoubtedly the first thing to impress about BORIS has nothing to do with his chess abilities. It's his big mouth. Exactly how many comments his PROMs contains is anyone's guess — the importers Optimisation aren't saying — but we counted 47 in two evenings of chess, and I don't think we got them all!

The comments appear in the eight displays and are clocked along right to left at about 2Hz. At any position on the board the program limits BORIS to a shortlist of appropriate comments, and a 'random' choice is made amongst them — or indeed not to comment at all. Saying nothing is the most likely choice of all, which means that the sayings do not always appear and so do not become boring with repetition.

### Play It Again BORIS

Once in play BORIS is a fair match for most people. On its basic level the machine plays a good beginner's game, and will find most things you leave lying around the board. Responses differ sufficiently even at this level to make 'psyching out' difficult. The biggest drawback of BORIS's chess is his passion for exchanging pieces.

Being cowards we started at this level to see what he could do. The first comment we got was 'AWFUL' to our opening move. Frightening! From here we kept increasing the time BORIS had to think about his answers. At five minutes he was winning consistently, and at two it's a long, long struggle to get him to lie down and die!



The symbols BORIS uses to identify the chess pieces. Shown here is the back rank of the white men. The black appear upside down so you can tell which men are which. Pawns appear as triangles.

Below: BORIS in play at the computer chess championship recently. He finished second to a private program.



We're only average chess players ourselves and so passed the infernal pawn-pusher onto a club standard player to get his comments.

On the longer response times, five minutes upwards, he considered BORIS a good opponent — and of course wouldn't admit how often he'd lost! Certainly everyone who had a game against him considered BORIS entertaining — the comments really do seem appropriate at times.

For example, in the middle of a game with BORIS hard pressed and the telephone ringing — I NEED LESS NOISE appears! Coincidence but fun all the same. One move away from being checkmated and he asks READY TO RESIGN? The classic must be after losing a queen to a knight fork — WHOOPS!

## Conclusions

All in all then BORIS can be confidently recommended to anyone interested in the game of chess. It can play a good game, and entertain while doing so. It is very difficult indeed *not* to think of the machine containing an (evil) little elf — a grand master type elf — plotting against your every manoeuvre, and unleashing sarcastic comments where possible. A definite winner. **ETI**

Our thanks to Kramer and Co for their assistance in the preparation of this article — they lent us a BORIS! (They also supply to the public!)

# GREENWELD

443 Millbrook Road Southampton  
SO1 0HX Tel: (0703) 772501

All prices quoted include VAT. Add 25p UK/BFPO Postage. Most orders despatched on day of receipt. SAE with enquiries please. **MINIMUM ORDER VALUE £1.** Official orders accepted from schools, etc. (Minimum invoice charge £5). Export/Wholesale enquiries welcome. Wholesale list now available for bona-fide traders. Surplus components always wanted.

## BUY A COMPLETE RANGE OF COMPONENTS AND THESE PACKS WILL HELP YOU

- \* **SAVE ON TIME**—No delays in waiting for parts to come or shops to open!
- \* **SAVE ON MONEY** — Bulk buying means lowest prices — just compare with others!
- \* **HAVE THE RIGHT PART** — No guesswork or substitution necessary!

ALL PACKS CONTAIN FULL SPEC. BRAND NEW, MARKED DEVICES — SENT BY RETURN OF POST. VAT INCLUSIVE PRICES.

**K001** 50V ceramic plate capacitors. 5%. 10 of each value 22pF to 1000pF. Total 210. **£3.35**

**K002** Extended range, 22pF to 0.1µF. 330 values **£4.90**

**K003** Polyester capacitors, 10 each of these values: 0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1, 0.15, 0.22, 0.33, 0.47µF. 110 altogether for **£4.75**

**K004** Mylar capacitors, min 100V type. 10 each all values from 1000pF to 10,000pF. Total 130 for **£3.75**

**K009**. Extended mylar pack. Contains all values from 1000pF to 0.47µF. Total 290 capacitors to **£11.25**

**K005** Polystyrene capacitors, 10 each value from 10pF to 10,000pF. E12 Series 5% 160V. Total 370 for **£12.30**

**K006** Tantalum bead capacitors. 10 each of the following: 0.1, 0.15, 0.22, 0.33, 0.47, 0.68, 1, 2.2, 3.3, 4.7, 6.8, all 35V; 10/25, 15/16 22/16 33/10 47/6 100/3. Total 170 tants for **£14.20**

**K007** Electrolytic capacitors 25V working, small physical size. 10 each of these popular values: 1, 2.2, 4.7, 10, 22, 47, 100µF. Total 70 for **£3.50**

**K008** Extended range, as above, also including 220, 470 and 1000µF. Total 100 for **£5.90**

**K021** Miniature carbon film 5% resistors, CR25 or similar. 10 of each value from 10R to 1M, E12 series. Total 610 resistors **£6.00**

**K022** Extended range, total 850 resistors from 1R to 10M **£8.30**

**K041** Zener diodes, 400mW 5% BZY88, etc. 10 of each value from 27V to 36V, E24 series. Total 280 for **£15.30**

**K042** As above but 5 of each value **£8.70**

## STEREO AMPLIFIER CHASSIS £5.50

Complete and ready built. Controls: Bass, treble, volume/on-off, balance. 8 transistor circuit gives 2 watts per channel output. Just needs transformer and speakers for low cost stereo amp. Suitable metal cabinet (W374) **£2.00** — or buy the amp, case and transformer for **£10.00** and get DIN speaker sockets and knobs free!!

## AMPLIFIER KIT £1.75

Mono gen. purpose amp with tone and vol./on-off controls. Utilizes sim. circuitry to above amp. Output 2W into 8 ohms. Input matched for crystal cartridge. 4 transistor circuit. Simple to build on PCB provided. Can be either battery or mains operated. (For mains powered version add **£2.20** for suitable transformer). Blue vinyl covered aluminium case to suit (W372) **£1.30**.

## BC182B OFFER

Special Offer for quantity users. 1k .035 + VAT; 5k .032 + VAT. Price negotiable on 10k + approx. 80k available.

## PC ETCHING KIT MK III

Now contains 200 sq. ins. copper clad board, 1lb. Ferric Chloride, DALO etch-resist pen, abrasive cleaner, two miniature drill bits, etching dish and instructions. **£4.25**.

## EDGE CONNECTORS

Special purchase of these 0.1" pitch double-sided gold-plated connectors enables us to offer them at less than one-third of their original list price! 18 way **41p**; 21 way **47p**; 32 way **72p**; 40 way **90p**.

## THE NEW 1978-9 GREENWELD CATALOGUE

### FEATURES INCLUDE:

- \* 50p Discount Vouchers
  - \* Quantity prices for bulk buyers
  - \* Bargain List Supplement
  - \* Reply Paid Envelope
  - \* Priority Order Form
  - \* VAT inclusive prices
- Price 30p + 15p Post.

### HEAT SINK OFFER

Copper TO5 sink 17mm dia x 20mm. 10 for 40p; 100 for £3; 1,000 for £25.

### 74 SERIES PACK

Selection of boards containing many different 74 series ICs. 20 for £1; 50 for £2.20; 100 for £4.

### TMS4030 RAM

4096 bit dynamic RAM with 300ns access time; 470ns cycle time; single low capacitance high level clock i/p; Fully TTL compatible; Low power dissipation. Supplied with data **£2.75**.

### MISCELLANEOUS ICs

Supplied with data if requested. MC3302 quad comp. **120p**; 710 diff comp. (TO99) **40p**; ZN1034E precision timer **£2.25**; LM711 Dual diff comp **65p**; LM1303 dual stereo pre-amp **75p**; MC1469R voltage reg **£1.50**; UPC1025H audio **£3.50**; 575C2 audio **£2.88**; TDA2640 audio **£2.92**; TBAB10S audio **70p**; SN75110 dual line driver **70p**; MCB500 CRCC gen POA.

### SCOPELOSOPES

We have available from stock the following SCOPEX models: 4D10A — DC-10MHz; 10mV sensitivity; Stab. power supplies; Dual beam; 3% accuracy. Excellent value at **£214** inc. VAT and carriage. 4S6 — DC-6MHz; 10mV sensitivity. Ideal portable scope. Solid state circuitry. All for **£150** inc. VAT and carriage.

### RESISTOR PACK

Carbon film 5% mostly 1/4W, few 1/2W resistors. Brand new but have pre-formed leads, ideal for PC mntg. Wide range of mixed popular values at the unrepeatable price of **£2.50** per 1,000; **£11** per 5,000.

### DIN SOCKET OFFER

2 pin switched speaker socket, PC mntg; 5 pin 180° PC mntg. or chassis mntg. (clip fix). All the same price, any mix: 10 for **70p**; 25 for **£1.60**; 100 for **£5.50**.

### PUSH BUTTON SWITCH BANKS

Lots of diff. types illustrated in Bargain List No. 6 — send SAE for your copy.

### RELAYS

W847 Low profile PC mntg 10 x 33 x 20mm 6V coil, SPCO 3A contacts **93p**.  
W832 Sub. min type, 10 x 19 x 10mm 12V coil DPCO 2A contacts **£1.15**.  
W701 6V SPCO 1A contacts 20 x 30 x 25mm. Only **56p**.  
W817 11 pin plug in relay; rated 24V AC, but works well on 6V DC. Contacts 3 pole c/o rated 10A. **95p**.  
W819 12V 1250R DPCO 1A contacts. Size 29 x 22 x 18mm min. plug-in type **72p**.  
W839 50V ac (24V DC) coil. 11 pin plug-in type. 3 pole c/o 10A contacts. Only **85p**.  
W846 Open construction mains relay. 3 sets 10A c/o contacts. **£1.20**.  
Send SAE for our relay list — 84 types listed and illustrated.

### LOW COST PLASTIC BOXES

Made in high impact ABS. The lids are retained by 4 screws into brass inserts. Interior of box has PCB guide slots (except V219).

V210	80x62x40mm black	<b>58p</b>
V213	100x75x40mm black	<b>72p</b>
V216	120x100x45mm black	<b>86p</b>
V219	120x100x45mm white	<b>86p</b>

### DIODE SCOOP!!!

We have been fortunate to obtain a large quantity of untested, mostly unmarked glass silicon diodes. Testing a sample batch revealed about 70% useable devices — signal diodes, high voltage rets and zeners may all be included. These are being offered at the incredibly low price of **£1.25**/1,000 — or a bag of 2,500 for **£2.25**. Bag of 10,000 **£8**. Box of 25,000 **£17.50**. Box of 100,000 **£60**.

# audiophile .....

What would you say if we told you about a cartridge which has a totally new stylus shape, a new improved magnet structure and revolutionary two part cantilever system — and a new radically different method of controlling operating conditions? It is all true, and its been around a few months too! Ron Harris took his time getting to the V15 Mk.4 — but found it worth the wait!

IT HAS BEEN some time now since the launch of the V15 IV from Shure, and by now I hope all the fuss has died down. Never has a product been rumoured to appear for so long, and met with such polarised comment when it did. In the meanwhile since the release the cartridge has slowly gained ground, and now would appear to be highly regarded in all but the most partisan anti-moving-magnet circles.

## Changes By Design

There is a lot in this design to interest the engineer, so let's consider that aspect first. The criteria to be met were to produce a cartridge which performed as close to perfection as possible under ideal conditions, and which went some way to creating those conditions.

The ambition I applaud!

Naturally these days computer analysis of just about anything numerically expressible was undertaken — and quite right too! Everything down to body size and mass were considered, and then more models set up to attempt to blend the whole design successfully. (I don't think it would be an outrageous suggestion to make that the SME Series III was used as the optimum arm in all these cavortings.



The new features to come out of all this are a dynamic stabiliser — and it's *not* just a brush, a new cantilever assembly, a new stylus shape, and a static reduction system. In addition the effective mass of the dynamic system has been lowered significantly.

## Tipped For Shape


Shure have decided, somewhat bravely, to go it alone and produce a new stylus profile. The reason is they wanted lower distortion but without sacrifice of low wear and trackability in the process.

Any design for a stylus *must* include consideration of such factors as the actual groove itself, tip mass, manufacturing cost, record wear etc etc.

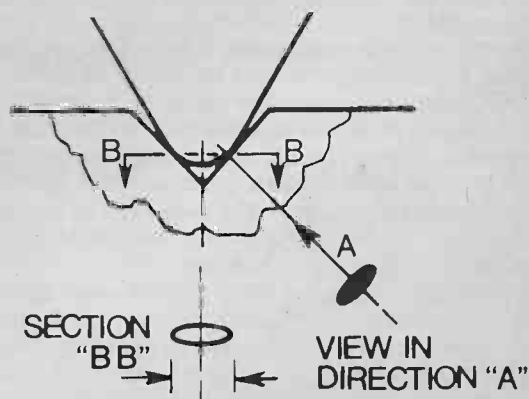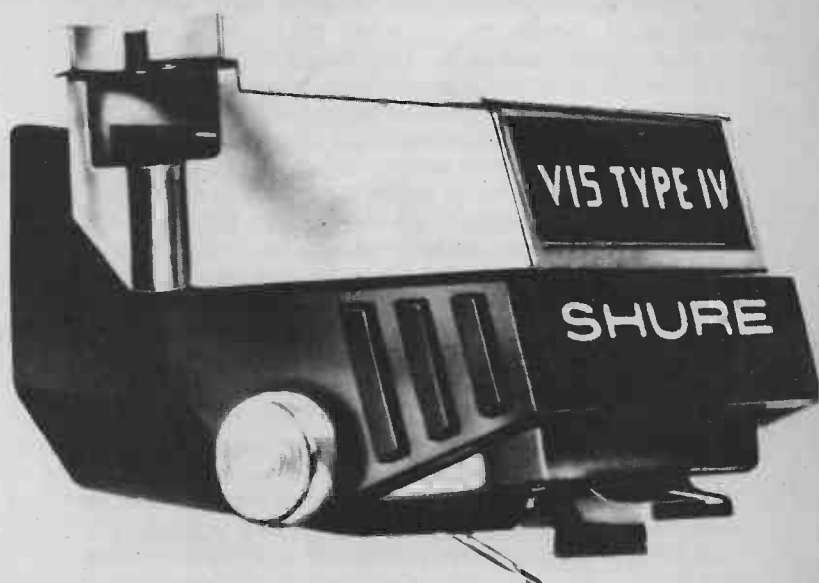As you can see from the diagram the end result of Shures endeavours is a long contact profile, basically a hyperbola from the front, termed a hyperelliptical design. Its actual contact radius is around 38 microns, while its tracing radius (parallel to groove tangent) is smaller than other types. The compromise does appear to offer advantage over other types, right enough.



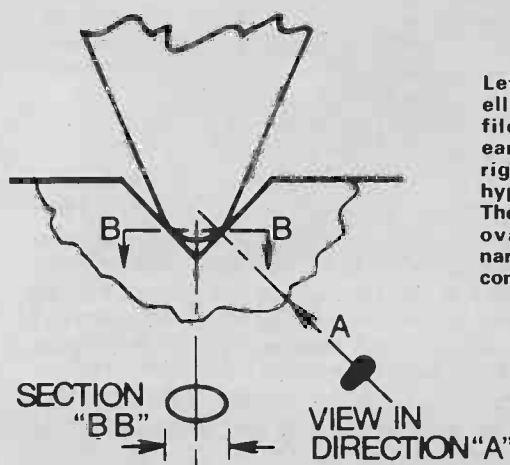Left: a conventional elliptical stylus profile, as used in the earlier V15/III, and right, the new hyperelliptical profile. The "footprint" (black oval) is longer and narrower than in the conventional profile.





## Magnetic Heart

The cantilever assembly is always the first section to come under scrutiny whenever a cartridge is to be improved, (just shows what improvements *could* be made if you ask me!) and it has not escaped this time.

After much playing with computers and trading off advantages against system requirements, Shure put themselves some prototypes together and carted them off for listening tests. Measurements, mathematical models and ears later a telescopic two element design emerged as the overall best solution, and was duly adopted.

Part of the reason for this is vibration control — presumably to suppress resonances excited by dynamic stresses — and this is assisted by an elastomer damping device. The earlier M24 featured something like this, but not so sophisticated apparently.

The magnet itself is of a new type, of lower mass but higher strength than its predecessors, allowing the cantilever unit mass as a whole to be lower. Taken together the improvements to the system are claimed to provide better high frequency tracking ability, and the shifting of the HF resonance to beyond 20 kHz.

## Brush Up On Damping

Now down to the obvious bit — which I had to do last just to keep you reading. Static on records can be blamed for most of the ills besetting disc reproduction as it now stands. It attracts dust — and holds it — leading to quicker wear of both disc and stylus and higher-replay noise.

There are umpteen devices on the market for clearing static charge, most of which resemble gas lighters. But Shure make the valid point that unless you know what polarity the charge is you're trying to clear, you've a 50-50 chance of making it worse by pumping ions at it.


Another nasty well-known to LPs of all age groups is the warp. Warps come free with most records these days and provide such delights as variation in tracking angle, mis-tracking due to effective reduction of applied tracing force and overall disruption of the ideal conditions in which cartridges like to operate.

Damping applied at the arm pivots can help with this, but represent a compromise at best. It is better to have the control as close to the tip as possible. The dynamic stabiliser is designed to do exactly that. The carbon fibre brush is mounted to ride just ahead of the stylus, and is equipped with viscous damped pivots. These are designed to absorb the shock produced by a warp, be it gradual or sudden. The optimum distance between cartridge body and record is thus preserved.

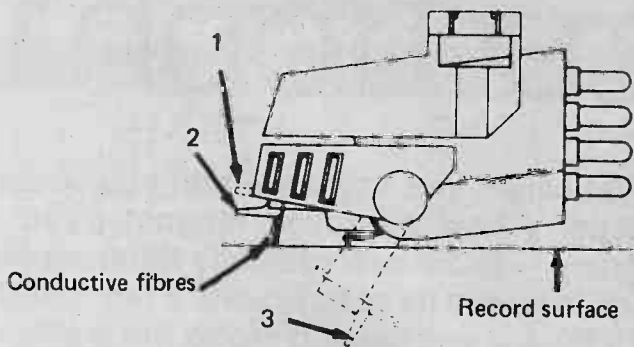
## Bristling With Pride

That brush is made up of about 10,000 carbon fibre bristles, ten of which would fit nicely into a record groove. Since it is carbon fibre it is conductive and can leak static charges to system earth since it is connected to one channel earth. Shure's research has indicated too that local static charges can increase tracking force by attracting the cartridge to the LP!


Sounds logical once someone tells you doesn't it? The brush does a good job shifting dust and muck out of the way too!



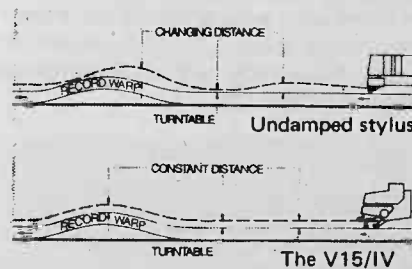The outrigger carbon-fibre brush may be set in any one of three positions: 1) in the "Up" position. 2) the dynamic stabiliser in its operating position 3) set down as a guard.



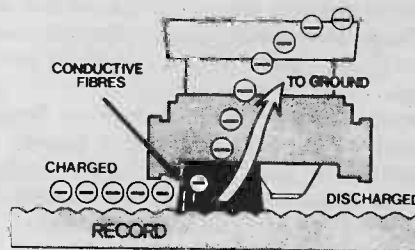
The V15 Type IV's brush with damped pivot is said to aid the tracking of warped discs by matching stylus movement more closely to the motion of the arm



The carbon-fibre brush is in continuous contact with one of the earth pins and leaks static charges to earth.
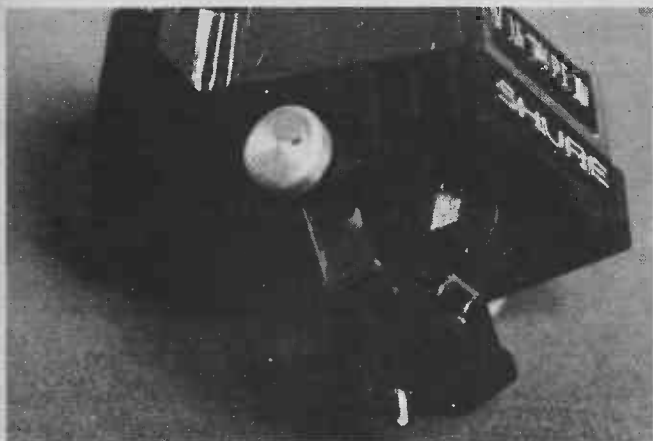
## Having A Fit

Setting up the V15 was very simple indeed. It's a shame to have to take it out of the box at all unfortunately, the packaging is superb indeed! Holding the body into the arm is done by screwing into a small metal block tapped for the bolts. Simpler than using fiddly nuts — if you'll pardon the expression — but probably more massive.



A close-up view of the stabiliser fitted to the V15 Mk-4, reposing in its guard position. The white line tells you where to line up the stylus when at play!

Because of the stabiliser, the stylus sees 0.5g less than is applied to the arm as a whole. This means that to get 1g tracking force, you set 1.5g. It can look confusing at first, and don't forget later and clip up the stabiliser, else the cantilever gets the lot!

### Tracing Class

After brief experiments, all our tests were conducted with 1g applied to the stylus, as the V15 tracked anything at this weight, regardless of how torturous we made our torture tracks. I failed to catch it out even once. Foiled again. One to Shure.

In contrast to the Mk3 the new model is sensibly specified for capacitive loading, and is apparently as insensitive to these things as it can be. Using a Sony TA-88 preamp enabled me to vary the loading while the cartridge was playing — a reviewer's delight! No adverse effects can be expected in normal use. Noise seems to be reduced too.

The stabiliser does offer real benefits as it definitely aids tracking and makes the system as a whole very tolerant of record 'flatness'. I tried the cartridge with and without pivot damping on the SME and would suggest it be used *with* damping — it somehow gains confidence that way!

### Sound Stuff?

This is the bit where I lose some 'musical' friends no doubt, because whatever anyone may have said amid the initial rash of reviews you will not find a cartridge better at information retrieval than the V15 IV. Its sound is incredibly detailed, and free from audible vices. It has a nice confidence about it altogether, and did not mis tracks — or mis anything — even once.

The sound has an overall smoothness that is perhaps its most 'nameable' feature. The bass quality is good, although I have heard better. In the mid-range and treble the sound stands forward towards the listener presenting a good stable image with all the detail you could wish for, with no trace of hardness or brightness whatsoever.

### Conclusions

So there it is — interesting and worth the wait for its appearance. Whether you like the sound of the V15 or not only you can tell, but if you're considering spending around £70 on a cartridge you'd be ill-advised to miss listening to it.

### Main Trouble

One of the most oft repeated queries to Audiophile concerns the problem of mains borne clicks and pops appearing out of loudspeakers.

Unfortunately there is no immediate overall solution. The first thing to try is to move either the hi-fi or the appliance — usually a fridge — causing the clicks to another outlet.

If this doesn't work then there are several suppressors on the market, at varying prices, to deal with the trouble. The most expensive is the QED unit at about £10. It does work in most cases, but no more so than some others.

The cheapest such unit available is probably the RS mains suppressor. Your local component stockist should be able to order this for you, and fitting it is pretty simple. Its input comes from the mains, and its output feeds the hi-fi in question.

### Otherwise

If none of this works then pretty obviously your problem is not mains borne. For radiated problems there's not much you can do except move things around. This is pretty rare though.

### Change Of Load



Above is the Sony TA88E preamp I mentioned a couple of months ago. Next month I'll be going through the circuits of this device in detail, as it represents a job done very very properly. At £699 so it should. The effect of all this engineering on the sound proved to be interesting too.

ETI

# A TECHNICAL MEMORANDUM

By Simian

DURING THE LAST FEW weeks some valuable research work has been incorporated into BSI and MIL standards, and this will greatly ease the specification of equipment. These standards help to combat a hitherto neglected environmental hazard; the users of equipment. A range of Standard Idiots (SIDs) has been defined, and these will be useful additions to any development laboratory.

## Using Standard Idiots

Standard Idiots are useful both for acceptance testing of incoming equipment, and for developing foolproof electronics. The latter is of particular value to manufacturers producing consumer goods. In general the technique of using SIDs is very simple: it consists merely of letting them come into contact with the equipment to be tested. Any flaws will be quickly shown up.

SIDs locate ergonomic faults very rapidly. It is instructive to watch them at work sometimes. If something is weak, they will break it; if no-one in their *right* minds would dry-off a poodle in a microwave oven, they will do just that.

Almost all old-style quality-control testing can be abolished. If SIDs are allowed to get at all products before they leave the factory, it will be found that only the perfect get through. This reduces the number of complaints received from users, but the cost of disposing of the rejects (in bulk) can be rather high.

## Types of Standard Idiot

Several specialist schools have been set up to train SIDs since these students are not well received at normal colleges. The coursework is intensive, and there are rigorous examinations to maintain standards. Over 600 people have received a Diploma in Idiocy (Dip. I) to date.

Many people have been found to have a natural aptitude for this work.

There are various grades of SID, ranging from the merely incompetent to those capable of sinking the Titanic, and there are many specialist fields:

(1) The 'non-technical' person (BS 91000-FOOL). This type normally panics when faced with more than two control knobs simultaneously. She (sometimes he) always mis-tunes radios, and would be hard put to it to recognise the difference between a watch and an oil refinery.

(2) Fiddler, or fidgeter (MIL-ID-99436/010). This

type is rapidly becoming an industry standard; the real world is full of them. If, for example, there is a switch controlling a lamp, the fiddler will flick it on and off for hours until either it breaks, or he spots something more exciting to play with. He will also use calculators to divide numbers by zero or to find  $\arcsin(-10)$ .

(3) The Ph.D (MIL-ID-12345/678) never reads instruction manuals. 'Of course, it's obvious that this piece of equipment works like so . . .'. It is only when clouds of blue smoke issue from a new £2,000 oscilloscope that he scuttles back to his desk to read in the unused handbook that this model is for 110V, not 240V.

Ph.Ds are often quite intelligent.

(4) Dismantler. A member of this species is guaranteed to dismember any piece of equipment which he owns or uses. However, it is very rare for the article ever to be re-assembled. (They are usually foxed by the new child-proof pill boxes).

There are a few other specialist categories: for example, the 'jonah', whose mere presence in a room is enough to make clocks stop and television sets neurotic; or the Standard Irishman with fourteen fingers.

## Disadvantages


One major problem with SIDs is that of storage when they are not in use. Obviously they cannot be left to roam freely around the lab! Normal work under these conditions is difficult. Even when they are stored in cupboards the voluble and plaintive cries of 'let me out' are disruptive.

There is another hazard which should not be overlooked: there have been a few unfortunate cases where standard idiots have been mistaken for engineers. Most of the companies where this has happened have now ceased trading.

## Conclusions

Standard idiots, in their present form, can be useful development tools, but there are associated hazards; on no account should they be left alone to amuse themselves. The new specifications are a major advance in a naturally chaotic field and standard idiots are adding a new dimension to destructive testing. This technological advance is helping to provide jobs for those people whose natural talents previously made them unemployable.

ETI

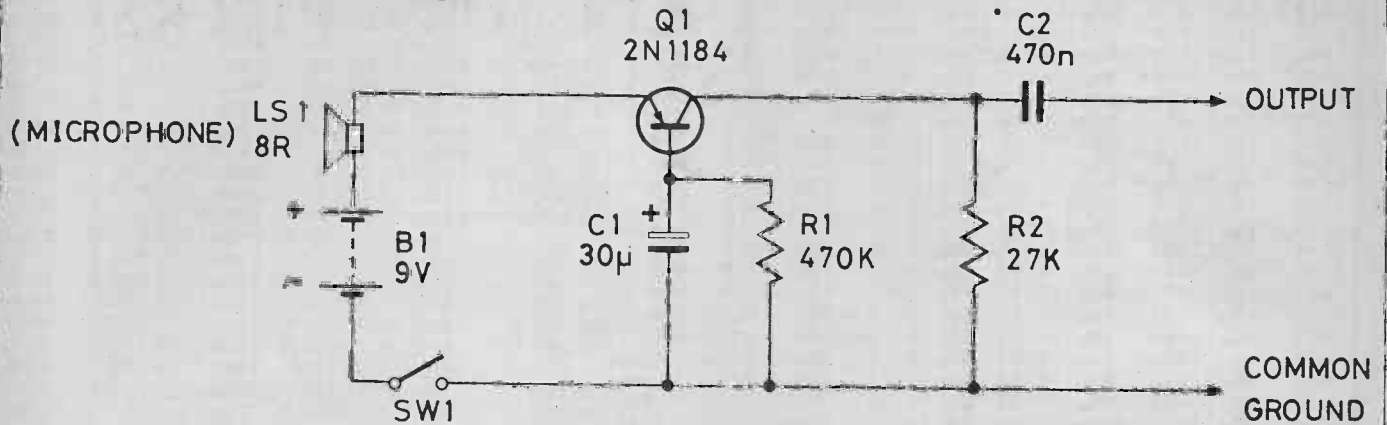

### Microphone Speaker

J. Smith

What do you do if you need a microphone in a hurry — the shops are closed and your friends are on holiday? Or you are just a little short of money? The answer is to build the following circuit from your odds and ends box. This circuit uses a small speaker as a microphone, one transistor and only four other parts, draws only about 2 mA of current from a 9 volt battery so an on/off switch is not really necessary.

The transistor shown is 2N1184 and is a PNP germanium medium power type but is not critical — try the ones you have first before buying this new type. The components too are not critical and the prototype was found to work OK with 20% variation in values. The output is high impedance and is fed into the mic input of a tape recorder or pick-up input of an amplifier.

### Speed Alarm

D. Ian

It is all too easy, during a long journey on a motorway, to allow one's speed to gradually creep beyond that point which the boys in blue take an unwelcome interest; this alarm gives an audible nudge whenever you drift over a pre-set speed.


Pulses from the distributor points (due to the ignition coil up to 400V may be developed as the points open) are passed through a current limiting resistor, rectified and clipped at 4V7. Via Q1 and the diode pump a DC voltage, which is proportional to engine revs, is presented to RV1; the sharp transfer characteristic of a CMOS gate, assisted by feedback, is used to enable the oscillator formed by the remaining half of the 4011.

At the pre-set 'speed' (revs) a non-

ignorable tone emits from the speaker, and disappears as soon as the speed drops by three or four mph.


Calibration of Ca may be conducted with an accurate pulse generator remembering that, for a four stroke engine, frequency = revs per minute times the number of cylinders divided by 120; for a car with a specification of 17½ MPH per 1000 revs, in top gear,  $f = 133\text{Hz}$  at 70 MPH, 124Hz at 65 MPH (4000 RPM and 3714 RPM). The necessary frequency should be fed to Q1 and VR1 set so that the alarm is just off. Reliable switching occurs on the prototypes with a change of only 5Hz (150 RPM), ie less than 3 MPH for the above example.

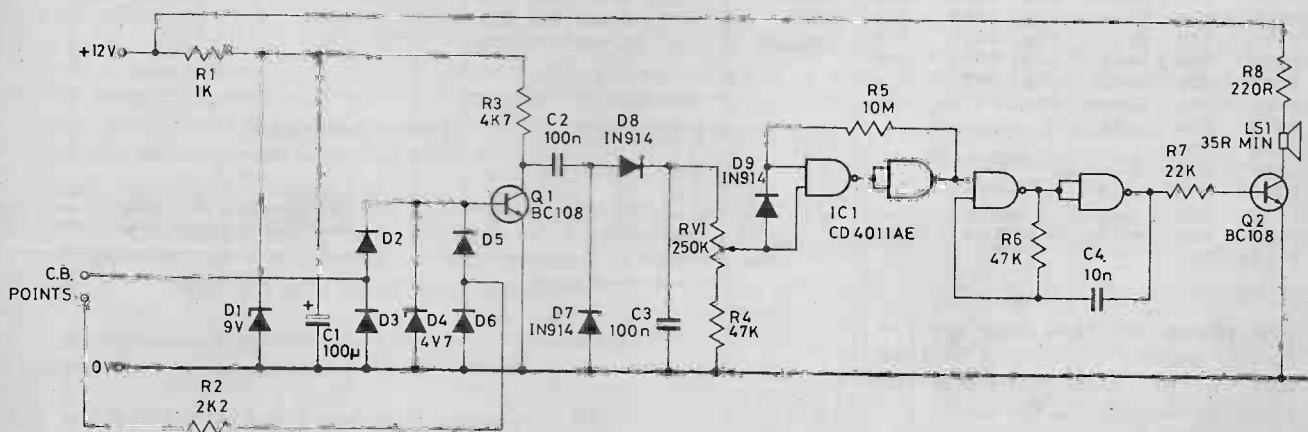Direct calibration 'on the road', while covering discrepancies due to tyre size, etc, will only be as good as the speedometer and obviously should be carried out by a passenger rather than the driver.



Tech-Tips is an ideas forum and is not aimed at the beginner. We regret we cannot answer queries on these items.

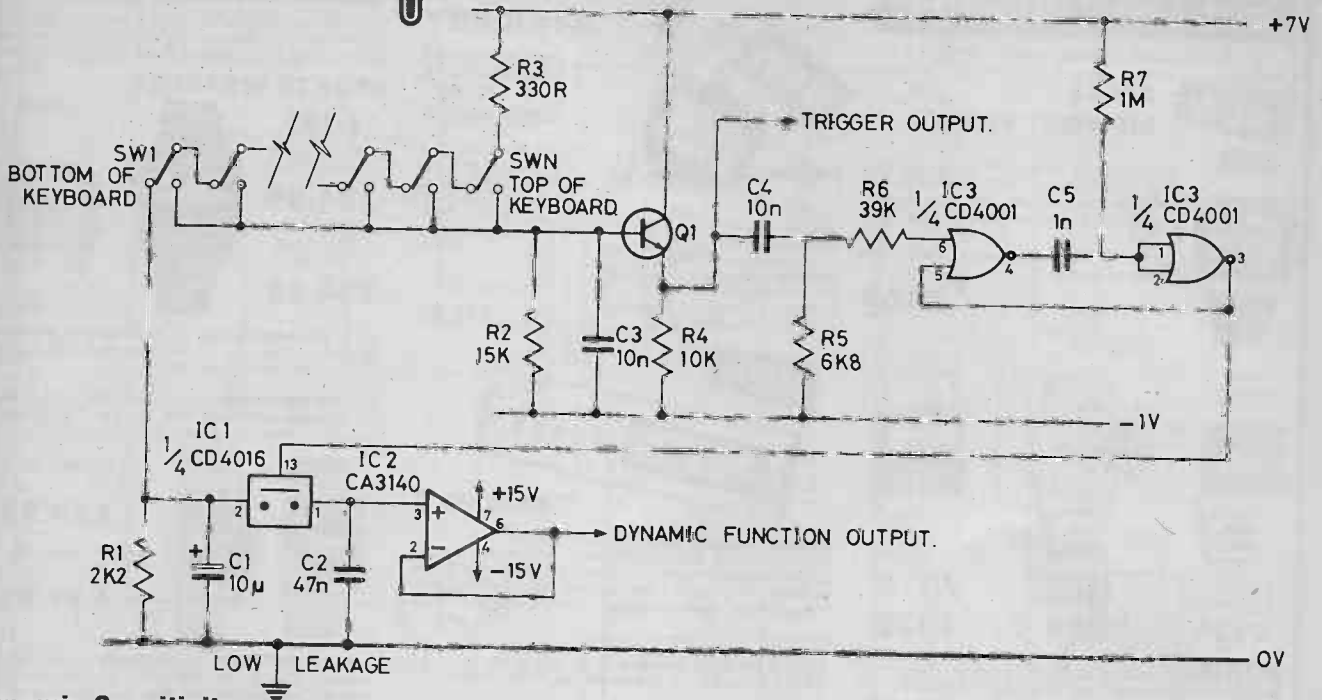ETI is prepared to consider circuits or ideas submitted by readers for this page. All items used will be paid for. Drawings should be as clear as possible and the text should preferably be typed. Circuits must not be subject to copyright. Items for consideration should be sent to ETI, TECH-TIPS, Electronics Today International, 25-27 Oxford St., London W1R 1RF.




### Dynamic Sensitivity

W. Stride

A dynamic function (touch sensitivity) greatly increases the flexibility of expression available to the player of a music synthesizer. This circuit by measuring the dynamic function by achieving the dynamic function by measuring the change over time of the keyboard switches, and hence the velocity of the key depressed.

The circuit is basically composed of three parts; firstly an RC time-constant network ( $R_1, C_1$ ) controlled by the keyboard switches, a buffer and amplifier and monostable ( $Q_1, IC_1$ ) and a sample/hold circuit ( $IC_2, C_2, IC_3$ ).

Normally  $C_1$  is kept charged up to +7 volts through the 'chain' of closed keyboard switches. When a key is depressed, the 'chain' is broken and  $C_1$  discharges through  $R_1$ . As the key is further depressed, contact is made with the trigger busbar,  $TR_1$  is turned on, and the monostable triggered. The monostable gives out a 1 millisecond pulse, which causes the analog switch ( $IC_1$ ) to close allowing  $C_2$  to charge up to the voltage on  $C_1$  at that time. After this, the voltage is stored on  $C_2$ , the output being buffered by  $IC_2$ . Since the input impedance of  $IC_3$  is  $\sim 1.5 \times 10^{12}$  ohms the delay time of  $C_2$  is very long. An output is available from the emitter of  $TR_1$  to trigger envelope shapers etc. To make sure the response is the same all over the keyboard, the distance between the gold wires on all the contact assemblies should be made the same.

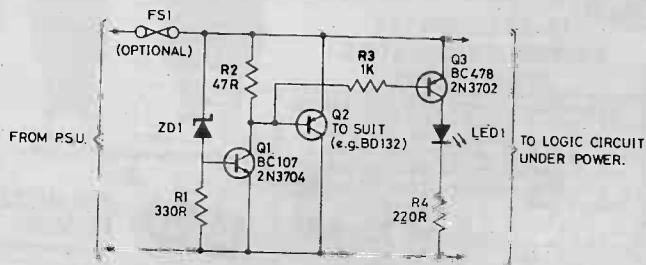

### Overvoltage Protection for 10 TTL chips.

E. Parr

With the introduction of integrated circuit voltage regulators it is very easy to make power supplies for logic circuits. Unfortunately it is only easy to blast a board of TTL by letting the voltage rise above 7V as could happen if the common line came off a regulator IC or the sense lines came off a commercial power supply.

The described circuit was designed by the author as a "last ditch" defence after a disconnected sense line allowed a commercial 5V supply to rise to 9V and blast 50 TTL chips. The circuit is simple to add onto any power supply, and it is the author's intention to build it "on board" with any future system containing more than about


Zener diode ZD1 senses the supply, and should the supply rise above 6V  $Q_1$  will turn on. In turn  $Q_2$  conducts clamping the rail.

Subsequent events depend on the source supply. It will either shut down, go into current limit or blow its supply fuse. None of these will damage the TTL chips.

The rating  $Q_2$  depends on the source supply, and whether it will be required to operate continuously in the event of failure. Its current rating obviously has to be in excess of the source supply. If the source supply is likely to sit down, LED1 should be added to indicate the circuit has operated.

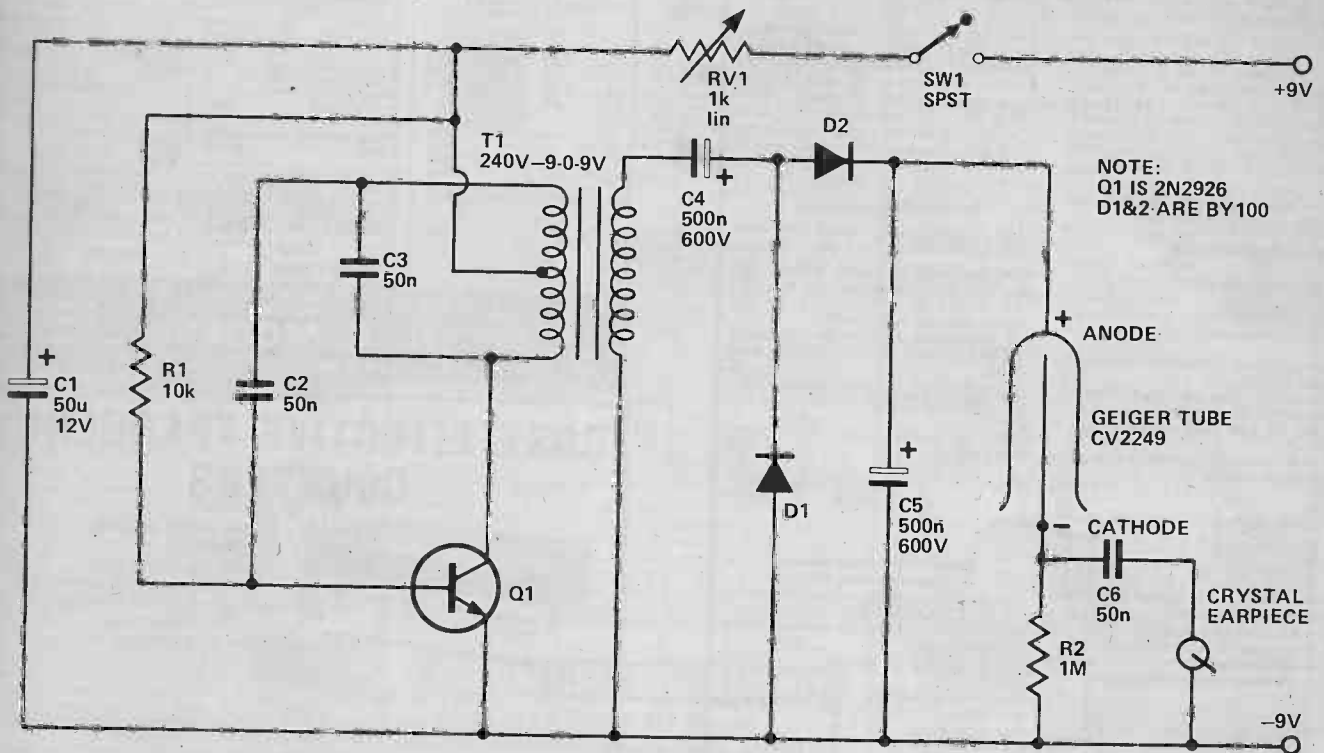The circuit will operate in approximately 500 nS space, so it will also protect the logic from transient spikes which a normal regulator would not block.






### Geiger Counter

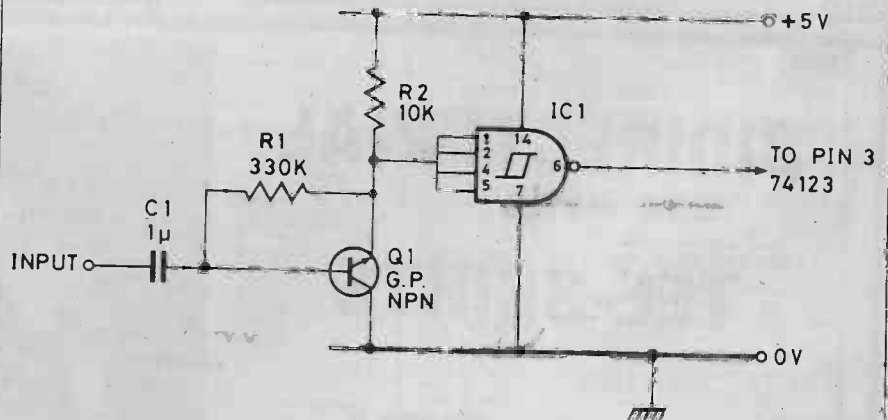A. Wheatley

Although the circuit is inexpensive and simple it is just as sensitive as many commercial devices. The important part is the geiger tube and this will probably cost about £1.90. It needs a high voltage supply which, in this case consists of Q1 and its associated components. The transformer is a low current 250V 9.0-9 and is connected in reverse. The secondary is connected into a Hartley oscillator, the base bias being provided by R1. RV1 is connected to control the voltage to the Geiger tube. A device to double the voltage is included because otherwise the voltage would still be insufficient to drive the tube. This comprises D1, D2, C4 and C5. This also rectifies it and smooths it. It is very important that C4 and especially C5 are of good quality and have low leakage. RV1 should be set so that each click heard is a nice clean one because over a certain voltage all that will be heard is a continuous buzz. The high voltage section is perfectly safe although if touched it will give a slight shock. This is unpleasant but quite harmless.



### Cuts Above

B. Houseley

The circuit here is an improved version of the original cuts encoder. If Q1 is preceded by a high impedance buffer, quite low signal levels can be accommodated successfully — and still trigger the 74123. A 74C02 or a 7402 was found to trigger only unreliably in this circuit.

# news digest.....

WHEN THE COMPUTING and Control department of Imperial College decided that they needed a logic hardware teaching lab, they were faced with several alternatives. One was to teach all the students in each year to solder and then let them loose on a handfull of TTL and CMOS chips each. This would have meant a plethora of supply problems, technicians and even minor burns.

What they opted for instead was to use — you guessed it — a computer.

The setup works roughly like this: A computer terminal is situated in the centre of the 'lab' and is surrounded by 16 benches, each provided with an oscilloscope, a signal generator and other relevant test equipment and peripherals. Each bench also has a perspex case with several dozen sockets and LEDs in it. The student goes to the central console, tells the machine which bench he wishes to use and which logic elements he requires. He then goes to the bench and sticks labels on the perspex case. Each label is printed with the relevant logic symbol. By connecting patchcords between the sockets on the 'breadboard,' the student can build up a logic network. The LEDs indicate the state of the various outputs. Each of the boards also has various 'utilities' — several clocks, a random logic output and handswitches to provide inputs.


All of these functions are provided by the computer — the sockets all lead into it's bus and it is the computer which drives the LEDs. This means that not only is there no possibility of the students damaging ICs which would then have to be replaced, but also that any component can be 'synthesised' — the department has even designed an imaginary CPU for use with the system.

The computer also calculates propagation delays — the students learn the pitfalls of race hazards in digital systems. It is even possible to simulate faulty components — as a fault-finding exercise. Another system (experimental as yet) can pretend to be linear components as well. Clearly the teaching possibilities offered by such a system are tremendous — what price blobboards now?

— Phil Cohen



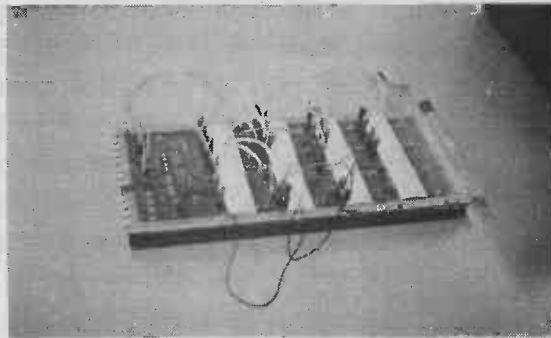Martin Cripps telling the machine what it's supposed to be!



What the students see. The wires disappear into the table — some conjuring trick!

Our thanks to Roy Francis and Martin Cripps of Imperial College for their time and trouble.

## Clearly-Precision within your grasp for only

# £79.00 +P&P

**LCD Multimeter Kit — Measures Voltage (AC/DC), Current, Resistance, Temperature\*.**

This is a compact, portable, hand-held precision instrument, accurate to within  $\frac{1}{2}\% \pm 1$  digit and giving crystal-clear readout from  $\frac{1}{2}''$  'black-on-silver' digits. It has automatic polarity indication, automatic zero, battery state indication and a shockproof case in black ABS with brushed aluminium-finish fascia plates.

We supply full instructions for easy building on a single PCB (+display). No metalworking etc. required.

### TECHNICAL SPECIFICATION

- Accuracy:  $\frac{1}{2}\% \pm 1$  digit
- DC Volts: 200mV, 2V, 20V, 200V, 1000V
- AC Volts: 200mV, 2V, 20V, 200V, 500V
- Current AC/DC: 200 $\mu$ A, 2mA, 20mA, 200mA, 2A
- Resistance: 200 $\Omega$ , 2K $\Omega$ , 20K $\Omega$ , 2M $\Omega$
- \* Temperature: 0-100°C (with sensitive external sensor supplied)
- Connectors: 4mm sockets,  $\frac{3}{4}''$  spaced; 1 red + 1 black test probe provided.
- Internal battery: PP3 type (not supplied)
- Current consumption: < 10mA.
- Transflective display
- Critical components selected for  $\pm \frac{1}{2}\%$  accuracy.

PRICE INCLUDES VAT.




## REMINDER

The DORAM Electronic Hobbies Catalogue is now available.

# FREE

Order now. Guarantee of Satisfaction. Send the coupon immediately. Your Kit will be delivered within 25 days. If you are not completely satisfied you may return your purchase within 30 days for a full refund. Doram Electronics Ltd, PO Box TR8, Leeds LS12 2UF.

 An Electrocomponents Group Company  
OFFER CLOSES 14 th February 1979.

To Doram Electronics Ltd PO Box TR8 LS12 2UF  
Please send ..... 60-632 Kit(s) at £79.95 ea. (£79.00+95p p&p)  
Please send a Hobbies Catalogue

I enclose cheque/PO for £  
I am paying via National Giro Centre Bootle Lancs to your Account Number 00/643/7257

Please debit my ACCESS Card No.

I expect delivery within 25 days

Signature .....

Name ..... (BLOCK LETTERS)

Address .....

Doram Electronics Ltd Reg 1155856

ETI 12

# LOUDSPEAKER PRINCIPLES

ON PAPER most loudspeakers look to be terrible pieces of design. Distortion averaging 1%-2% — and what's worse varying with frequency. Efficiency only rarely exceeding 1% — so that the vast majority of those carefully nurtured, 0.002% THD amplifier watts pumped in down those non-inductive £10 a metre cables turn into nice, safe, un-musical heat!

The purpose of any loudspeaker is to convert an incoming complex electrical signal into compressions and rarefactions in the air—sound waves — which can be perceived as being as close to the original signal as possible. The different methods now being used to realise this end form the basis of this article.

## What Is Left Undone

You will find references throughout this article to frequency divider — crossover — networks. Unfortunately there is too much to be said on that subject to allow a full and proper treatment of it within this article, and we shall return to it in a companion article later.

Forgive us our evasion.

Loudspeakers of whatever variety interact crucially with the surroundings they are used in — the living room, studio or whatever. When judging performance it is vital to remember this, and even moving a speaker around in a room can significantly alter performance. Some manufacturers are becoming sensitive to this themselves — notably AR — and are producing designs specially tailored to a particular location, or allowing adjustment of output to suit varied positioning (AR 10π, AR9).

Such adjustments are generally carried out within the crossover network, and alter the electrical inputs to the units to compensate for specific emphasis placed on certain frequencies — usually the bass — by the loudspeakers position.

## And What Is Not

We have concentrated on the major fundamentally different systems in commercial use today, and tried to explain how they operate what their advantages are, and what are their drawbacks. Many minor variations have been left out simply through lack of space.

Forgive us our omissions.

The types covered are:

1. Moving coil — and methods of loading
2. Electrostatic
3. Isodynamic
4. Ribbon
5. Piezo-electric
6. Motional Feedback Control

**Every hi-fi must have not one but two. Loudspeakers are perhaps the weakest link in the precarious hi-fi chain. Many methods of improving the sound we hear have been tried. Few have succeeded well enough to reach production. Ron Harris explains the innermost secrets of those that made it!**

## MOVING COIL

This system dominates the field at present, and is certain to do so for the foreseeable future. The principle is an exact reverse of the microphone principle, and takes its being from the fact that a wire carrying a current  $I$  in a magnetic field of flux density  $B$  will experience a force,  $F$ , where


$$F = B \cdot I \cdot k \quad k = \text{a const.}$$

A coil of wire carrying the audio is sited within an intense magnetic field, and is attached to a 'cone' as shown in the diagram. The cone is held in position by the edge suspension and 'spider'.

When a signal passes through the coil the force produced tries to push it out of the field in one direction or another, and this movement is transferred to the air by the movement of the cone. The suspension system provides a 'return-to-rest' force. This movement is related more or less linearly to the input as long as the coil remains within a constant field.

If it moves out, then the relationship will change, introducing non-linearity or distortion. For this reason large and powerful magnets are employed, which have as great a depth of field as possible.

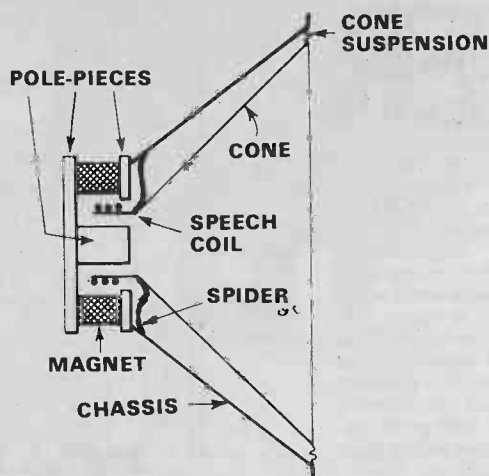Another solution is to use very long coils so that the number of turns of wire within the gap between the pole pieces remains relatively constant.




Basic schematic of moving coil loudspeaker. In practice the coil winding would be longer relative to the magnets, so that it did not move out of the field.
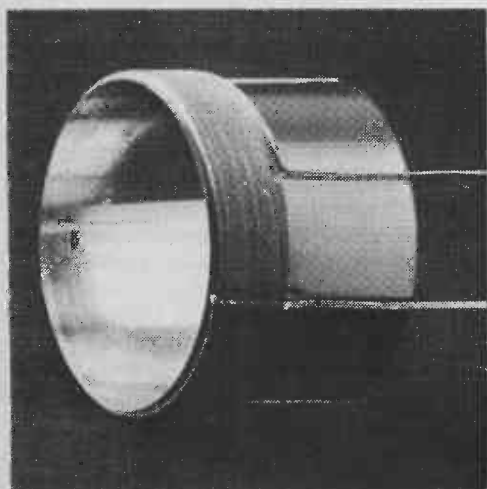
### Heated Exchange

Heat is generated in the coil and must be conducted away, usually by the magnet assemblies and chassis. AR speakers now incorporate a heat conducting fluid which is present in the gap and the coil is immersed in this. Heat conduction is thus improved and power handling raised. The fluid also acts as a damper to aid movement control.

The speaker chassis must be as rigid as possible, since the only reason the coil and cone move and it doesn't is that it weighs more! Any resonances present in the structure will act to transfer energy from the coil movement and hence distort the output.




Close-up of a voice coil. This is a machine wound unit belonging to a Bose driver. Note the winding is butted very close to the edge of the paper former, and the precise nature of the winding necessary for linearity.
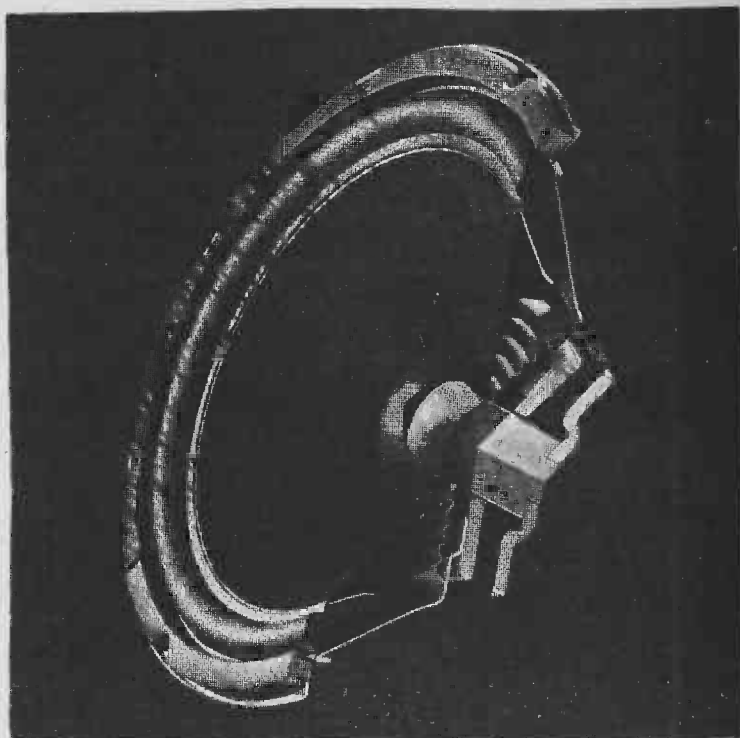
### Cone-ventional?

The greatest drawback of this system is the cone itself. This is usually either doped paper or Bexetrene — an erstwhile packing material someone fell over once! It should act as a piston to the air, with the entire surface moving together to produce the required air movement.

However, since it is driven only at the centre, unless the material is possessed of infinite rigidity(!) flexing or



Cutaway photo of a moving coil unit — in this case a Bose driver. If you look carefully you should be able to identify the voice coil, magnet assembly, spider and cone assembly.

rippling will take place — once again deviating from the input signal. The larger the cone the worse the effect as the frequency rises, since the centre driven portion may well be oscillating with a period smaller than the time taken for the energy to be transmitted through the cone material to the outside edge.

Hence the centre of the cone leads the outside by a number of cycles, all of which appear as ripples in the cone. This is the reason for dividing up the incoming electrical signal, and for employing smaller coned drive units for higher, less energetic, frequencies.

To handle the high end of the audio spectrum, dome units have almost entirely replaced the coned variety, as they spread the sound more evenly, giving a better dispersion across the listening area. Also domes can be produced smaller, and a hemispherical dome, edge driven, will tend to act more as an integral surface than a centre driven cone.

### Getting A Hangover

Since the cone has mass, and therefore inertia (Dr. Who excepted) it cannot respond instantaneously to changes in direction called for by changes in polarity of the electrical signal. This inability to get back in time is called 'overhang' and is another problem facing designers. To minimise it driver mass has to be as small as possible, while rigidity has to be as high as possible.

This has led over the years to many experiments with metal cones, mylar cones, polyester et etc etc. Anywhere other than bass units most of these have proved successful. ▶

An integral part of a moving coil loudspeaker design is the method of housing the units, and thus putting an acoustic-loading upon the actual units. A brief discussion of the various methods is thus required at this point.

### Housing Shortages

There are basically six methods of providing a home for drive units and at the same time augmenting its performance. These are:

- (i) Finite Baffle
- (ii) Acoustic Suspension (sometimes called Infinite Baffle)
- (iii) Bass Reflex
- (iv) Auxiliary Bass Radiator
- (v) Transmission Line
- (vi) Horn Loading

All of these apply primarily to moving coil units with the exception of horn loading which can be used to enhance efficiency of several types. In order then:—

### Finite Baffle

Since the vibrating cone is emitting sound waves in both directions, unless prevented the two waves will interact causing cancellation and reduction in acoustic output. The effect is reduced by placing the speaker in the centre of a large solid board to make it difficult for a compression produced in front to cancel the rarefaction produced behind the speaker.

Obviously an infinitely large piece of wood prevents this entirely, but such things don't grow on (ANY) trees(!?) and so the finite baffle is an attempt to do the best that can be done.


Once the sound wavelength approaches the baffle size destructive interference takes place and response rolls off.

This method is responsible for those hardened enthusiasts mounting their bass units flush into walls and sides of houses!

Sinclair marketed a finite baffle speaker some years ago but this seems to have ceased to be.

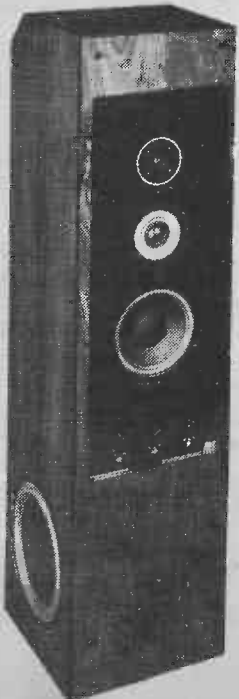
### Acoustic Suspension

Here the rear radiation from the units is (hopefully) entirely suppressed by totally enclosing the unit in a box, and radiating through a hole in that box (sounds odd when phrased like that eh?).



**The AR9. Coming from one of the 'founder' manufacturers it represents Acoustic Researches state of the art. The cabinet is treated around the baffle with absorption material to prevent diffraction and re-radiation effects that lesser enclosures suffer from. It also stands an endearing 53in high!**

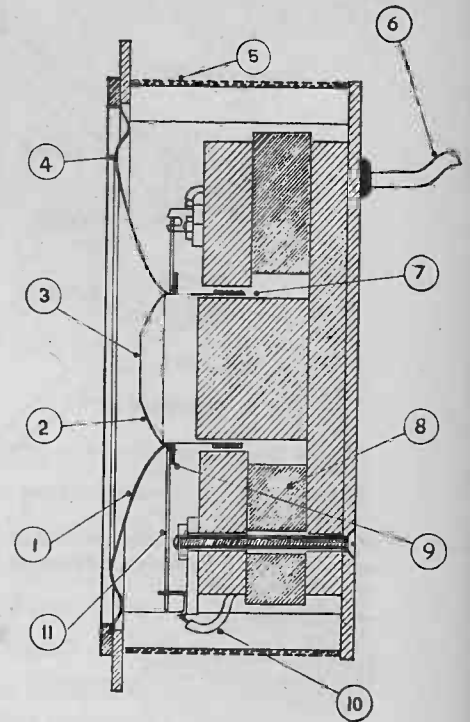**Schematic of a Jordan Watts driver module. Numbers refer to: 1. Metal cone contoured to hyperbolic law. 2. Phase correcting dome. 3. Resistive termination to dome centre. 4. Resistive termination to cone edge. 5. Acoustic damping. 6. Direct input signal cable. 7. Coil completely immersed in magnetic field. 8. High efficiency "Feroxa" magnet. 9. Resistive termination at junction of cone, coil and suspension. 10. Connections to coil via suspension. 11. Silvered beryllium copper suspension cantilevers.**



Damping of the cone movement occurs due to the compliance of the trapped air, and the suspension system now consists of both the actual cone suspension plus the air load.

In order to preserve bass response the enclosure should be fairly large and hence present a good air load allowing high levels of energy to be applied. Bass units designed for this type of loading have a high cone mass and high compliance. In addition they are generally of the long voice coil variety. The air load then applies most of the restoring force required by the design. Efficiency is reduced since the cone mass is increased and compliance (total) is low.

### Bass Reflex

The aim of this method is to raise efficiency at low frequencies and thus decrease the required enclosure size for a given bass output. This is accomplished by addition of a vent, or port, in the front panel of the enclosure. This allows a controlled movement of air between cabinet and room. The effect of careful design of vent dimensions and placement is to produce an effective addition to bass response below a certain frequency, such that the air moving out of the vent aids the air movement produced by the bass driver.

Above the operating frequency the vent has no effect on performance (they hope).

### Auxiliary Bass Radiator

Basically a variation on the above principle, but with the vent 'plugged' with a driverless unit or suspended mass. This is tuned to provide antiphase radiation in the required frequency band. Above this band the unit acts like part of the enclosure wall. Perfected and practised by Celestion, and perhaps epitomised by the Ditton 66 design.