

electronics today

OCTOBER 1978

INTERNATIONAL

45p

Television

Chess

MRM 101

RF Meter

SCRUMPI 3


Gain Control



**8 - PAGE
TECH-TIPS
SPECIAL**

... NEWS ... PROJECTS ... MICROPROCESSORS ... AUDIO ...

PROJECT: Sound Gen.

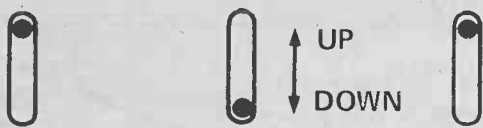

OUTPUTS
SELECTED

DOWN	DOWN	DOWN	VCO
DOWN	DOWN	UP	SLF/NOISE
DOWN	UP	DOWN	NOISE
DOWN	UP	UP	SLF/VCO
UP	DOWN	DOWN	SLF
UP	DOWN	UP	SLF/VCO/NOISE
UP	UP	DOWN	VCO/NOISE
UP	UP	UP	INHIBIT

TABLE 1


Set the leftmost mixer switch to down again and move the right hand switch up, the output from the noise generator will now be heard.

The various combinations of the oscillators and noise source


corresponding to the settings of the mixer controls are shown in Table 1.

That then is a run down of the various controls and their effects, its now up to you to put them together and hopefully make a little music.

ETI

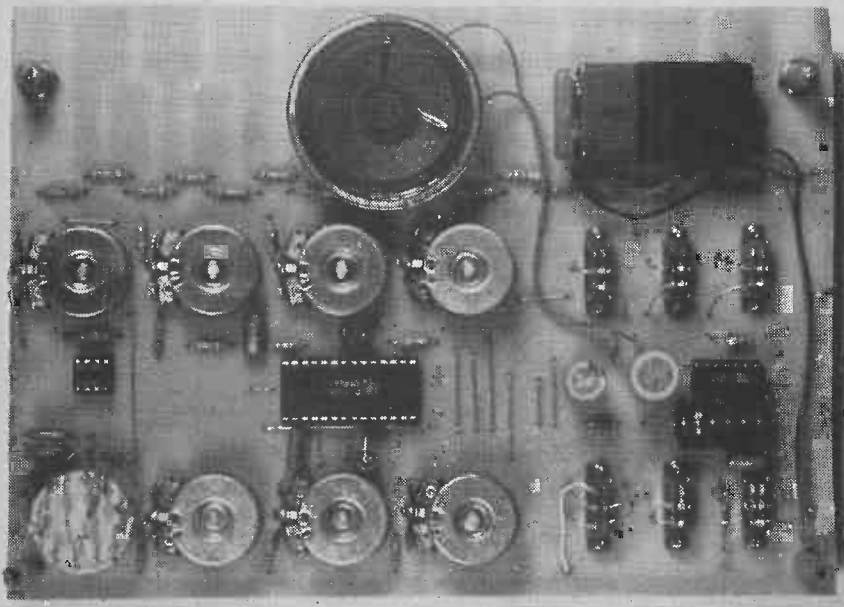

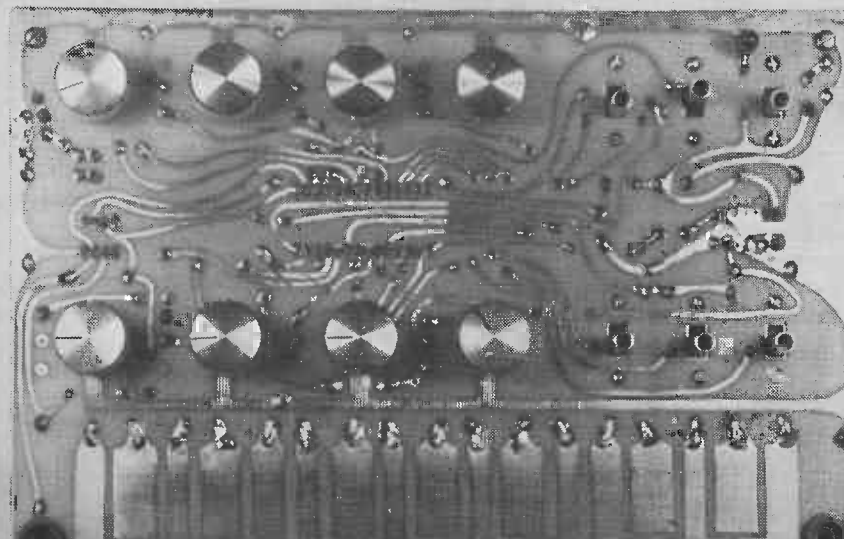Two photographs showing the PCB from above and below. Note the front panel lettering on page 17 is in error — the attack and delay designations being reversed.



UNBEATABLE PRICES ALL FULL SPEC.

741 (RCA 8DIL) 17p, 2" Red LED 8p, TIL 2098 Red 8p, LM711CH (T05 Voltage Comparator + Data) 25p, TBA810s + Data 65p, 2513 (Upper Case) £5, 1702 £2.95, TMS 3128NC (Shift Reg) 80p, 2521 (Dual 128Bit Static Shift Reg) 80p, 75S108 (TTL TO MOS Level Converter) 35p, 74150 90p, 74154 £1, 74H00 18p, 74H72 30p, 74H150 90p, 74H183 £1, CD4001 14p, CA3046 65p, CA3081 70p, 93422-DC (256x4 RAM) £2.25 (Few only), 4027 (300ns) £2, 4027L3 £2.50 (Few only), 2708 1Kx8 UVEPROM £6.50 Cannon D-Type, 15 way Plug 50p, SKT 50p, Covers 60p, 37-way Plug 80p, SKT 80p, Covers £1, Amphenol 57 Series 50-way SKT 95p, 28-way SKT 65p, 24-Way SKT 50p, RS SUBMIN Transformer 240 Input 12-0-12V 50MA (Screened) Type 196-274 £1.35, DIL SWTS 4-way 55p, 7-way 80p, P/P 10p. All inquiries s.a.e. please. Cat. s.a.e. 8x6 free with goods.

Now distributor for Mutek Products including Ides Micro Systems. In stock Video Interface board. 16 line. 64 characters. data and control inputs. video output. Ideal for Micro Processor use. With full documentation, £81, P/P plus insurance £1. Brochure available. s.a.e.

POCKET PAGER

Miniature crystal controlled FM RX Single Superhet around 30MHZ 450 KHZ IF contains various tone detectors. Ideal for modifications to 27 MHZ Radio Control OR 28MHZ Amateur Band. Complete, without 2.5v DEAC + circuit of similar type. £3.95. P&P 25p.

L. B. ELECTRONICS
43 WESTACOTT, HAYES
MIDDLESEX UB4 8AH

CALCULATORS SCIENTIFIC

TEXAS T1 25 (new LCD Sci. Stats)	£18.90
TEXAS PC100B (Printing Unit for T159 T158)	£140.00
HP & TEXAS Libraries and Accessories avail.	POA
TEXAS T1 59 (Card Progs. 980 steps of 100 Mem.) Plus Applied Statistics Module	£176.00
TEXAS T1 56 (Key Progs. 450 steps of 60 Mem.)	£60.00
TEXAS T1 57 (Key Progs. 8 Mem. up to 150 Keystrokes - 50 Prog. steps)	£26.20
TEXAS T1 45 (new updated version of T140)	£19.95
TEXAS T1 33 (spec. as T1 30 but 3 Mem.)	£13.95
TEXAS 42 M54 (10 Dig. Fin. Stat. Progr.)	
12 Mem. 32 Keystrokes	£42.95
TEXAS T1 51 (New 8 Dig. - Exp 10 Mem.)	
32 Prog. Steps Stat/Sci	£26.30
TEXAS T1 Programmer (Hexadecimal/Oct)	£46.50
TEXAS T158 (Complete with Master Module plus Applied Statistics Module)	£80.00
CBM 561 (stat. plus sci. 6 mem. V and S div. ch. sq. etc)	£54.00

SLIM-LINE CHRONOGRAPH SUMMER BARGAIN OFFER

12-function—Hrs., Min., Sec. plus fingertip control for Months, Date, Day, Stop Watch and Lap Time to 1/1000th sec

ONLY £27.50 + £1 P/P. Ins.
14-day money back offer if not fully satisfied

COMMODORE PET COMPUTER 8K bytes RAM 2001-B
(Cassette, VDU Display Unit and Keyboard built into the Pet)
ONLY £843.00

HP19C (Continuous mem. key prog printer)	£163.00
HP29C (as 19C but no printer)	£110.00
HP27 (10 mem sci. lin. stat. 8 digit + exp.)	£73.00
HP67 (card prog. 224 steps 26 mem.)	£277.00
HP97 (card prog. 224 steps print 26 mem.)	£466.50
All HP range available including NEW 'E' Range. Prices on request	
CASIO FX8000 (sci. Calc Stopwatch 5 alarms)	£27.65
CASIO FX3100 (LCO Sci-Stat / Div. Polar Rec. etc.)	£22.50
CASIO FX201P (sci. 11 mem. 127 step prog.)	
FORTRAM SYSTEM	£45.00
CASIO PROFXI (as above but card prog.)	£99.00
FREE Mains charger included	

SPECIAL OFFER

Texas T159 with PC100B £285.00

(Price includes all items as mfg specification)

GOODS FULLY GUARANTEED. PRICES EXCLUDE V.A. (ADD 8%) BUT INC. P&P CHEQUE WITH ORDER

Company, Hospital and Gov. orders accepted by phone
EXPORT ORDERS ACCEPTED
Barclaycard, Access order accepted by phone

Tel. 01-455 9855

MOUNTAINDENE LTD
22 Cowper Street, London, EC2
(Near Old St. Station) Tel. 01-455 9855

GAIN CONTROL

PART ONE

THERE ARE MANY cases in signal processing where the control of the gain is necessary. Some common examples are automatic volume controls in cassette recorders and in the IF sections of radio receivers. Also in professional audio equipment there is a whole range of compressor, expander, limiter and noise gate devices which find great use in recording and broadcast studios. Maybe you have wondered how the volume of the music drops when the DJ starts to talk and then fades up again when he stops. This process, known as voice over or "ducking," uses *voltage control of gain*.

Noise reduction systems such as dolby and dBX employ voltage controlled amplifiers. Synthesizers and sound processors obtain effects such as ring modulation, automatic panning frequency shifting, dynamic filtering, tremolo and envelope shaping also by the use of this technique.

Gaining gain

There is a wide variety of methods which can be used to obtain the gain control. This can be anything from constructing the variable gain element yourself from basic parts, to buying IC or module designed specifically to solve your particular problem. Generally the solution is some sort of compromise, because unfortunately the

problem of making high performance controlled gain cells (multipliers), is rather difficult and therefore the IC's tend to be rather expensive.



However with a bit of care a cost effective solution can usually be produced.

A good example is the AGC in a transistor radio. The transistors in the IF section have an h_{fe} that varied widely with the magnitude of their collector current. Thus, by sticking three transistors in series it is possible to vary their overall gain by about 40 dB, (x100), merely by controlling their collector currents. The AGC stops the audio output of the radio from varying as the radio reception conditions alter.

Electronic multipliers

When it is required to control the level of one signal with that of another, an electronic multiplier is used. This process is analogous to arithmetic multiplication. If input A is positive, Fig. 1, and input B is positive then the product (the output), will also be positive. If A goes negative then the product will be negative. If both A and B are negative then the product will be positive thus preserving the arithmetic rules.

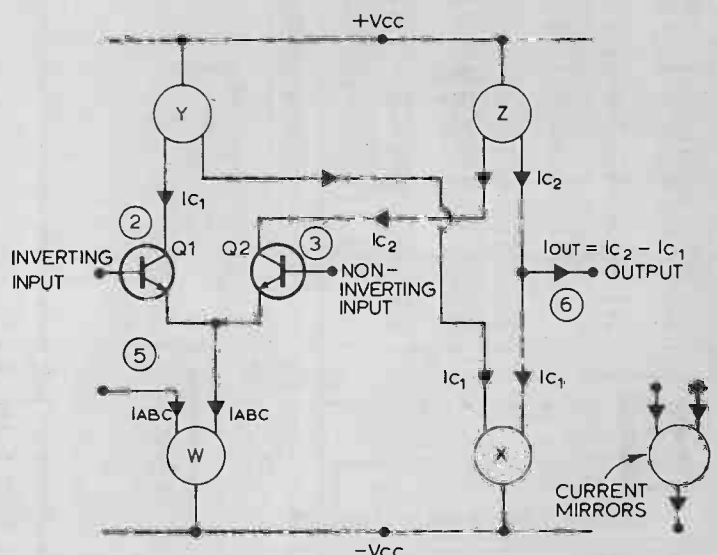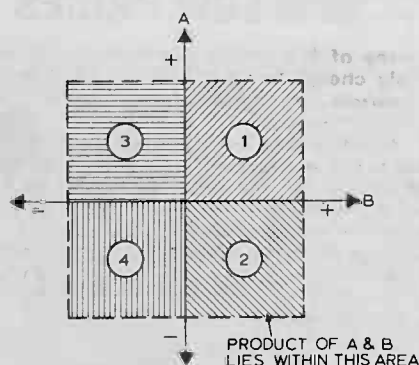If A and B are limited to be only one sign each then



Left: the principle behind electronic multipliers. The graph shows the possible outputs for a variety of combinations of input polarities.

Above: Internal workings of a CA3080, an Operational Transconductance Amplifier. Say that too fast and you'll need a new set of teeth.

Tim Orr continues his occasional series of circuits, methods and explanations with a detailed look at how gain can be controlled by another electronic signal, be it squarewave, sinewave or voice signal. This leads to some interesting circuits — from ducks to filters!

the multiplier is known as a one quadrant multiplier. That is the product can only lie in one quadrant. If A can be both +ve and -ve, and B only of one sign then the multiplier is known as a two quadrant multiplier. This is what is called an amplitude modulator. The audio signal which is bipolar is A and the control voltage is B.

If A and B can be both +ve and -ve, the product can lie anywhere in the four quadrants and hence the multiplier is known as a four quadrant multiplier. This type of device is found in frequency shifters and ring modulators.

CA3080 — An OTA!

The CA3080 is a two quadrant multiplier, or to give it its full title, it is an Operational Transconductance Amplifier. It has a differential input and a single quadrant current input known as I_{ABC} , (amplifier bias current), Fig. 2. The differential transistor pair is used to steer the I_{ABC} current between the two transistors Q2. There is a region where the input differential voltage is linearly proportional to the percentage of current steered between the two transistors. This voltage region is fairly small, being about 20 mV, but using the CA3080 in this area then a reasonably linear 2 quadrant multiplier can be obtained.


What has happened is the the I_{ABC} current has been multiplied by the input voltage. The product is the difference between the two collector currents. This difference is extracted by the use of mirrors, current mirrors that is. The current mirrors can be attached to either the +ve or the -ve supply rail.

They have two terminals, and whatever current flows into one terminal, then the same flows into the other, which is why they are called mirrors.

What we want to do is take the difference between the collector currents of Q1 and Q2, I_{C1} is reflected from mirror Y and then from mirror X and then appears at the output. I_{C2} is reflected from mirror Z and then appears at the output. The two currents are subtracted from each other and the output current is thus $(I_{C2} - I_{C1})$, which is the product of $I_{ABC} \times V_{in} \times K$, where K is a constant. Note that the I_{ABC} current is also reflected from a current mirror on the negative rail.


The CA3080 is a low cost two quadrant multiplier and can be used to perform a wide variety of multiplication functions. The linearity of the device holds true for I_{ABC} variations of over three decades. When using this device keep I_{ABC} below 0.5 mA.

VCA Using CA3046 Array

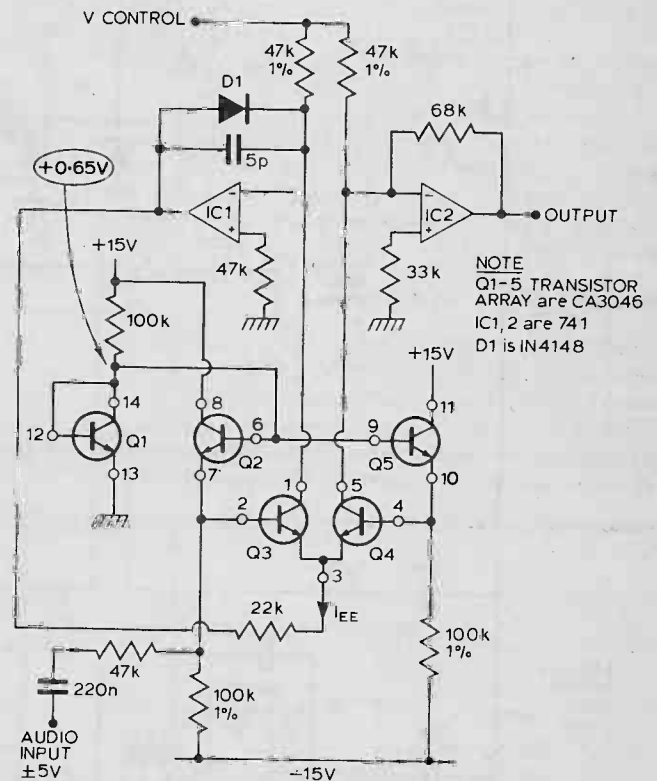

The CA3046 is an array of 5 transistors which are all well matched and relatively cheap. Qe, 4 forms the differential transistor pair, IC1 controls the current and IC2 extracts the differential output current and turns it into an output voltage. The audio input is inserted into the base of Qe but also connected to this node is the emitter of Q2. Q2 and Q5 serve to predistort the input signal, but they distort the signal the opposite way to which the multiplier distorts it. This is known as distortion cancelling, and it allows a larger signal level to be applied to the multiplier for the same percentage of distortion at the output. The larger input signal allows a higher signal to noise ratio to be obtained. Transistor Q1 is used to bias the bases of Q2, 5 to a suitable operating region.

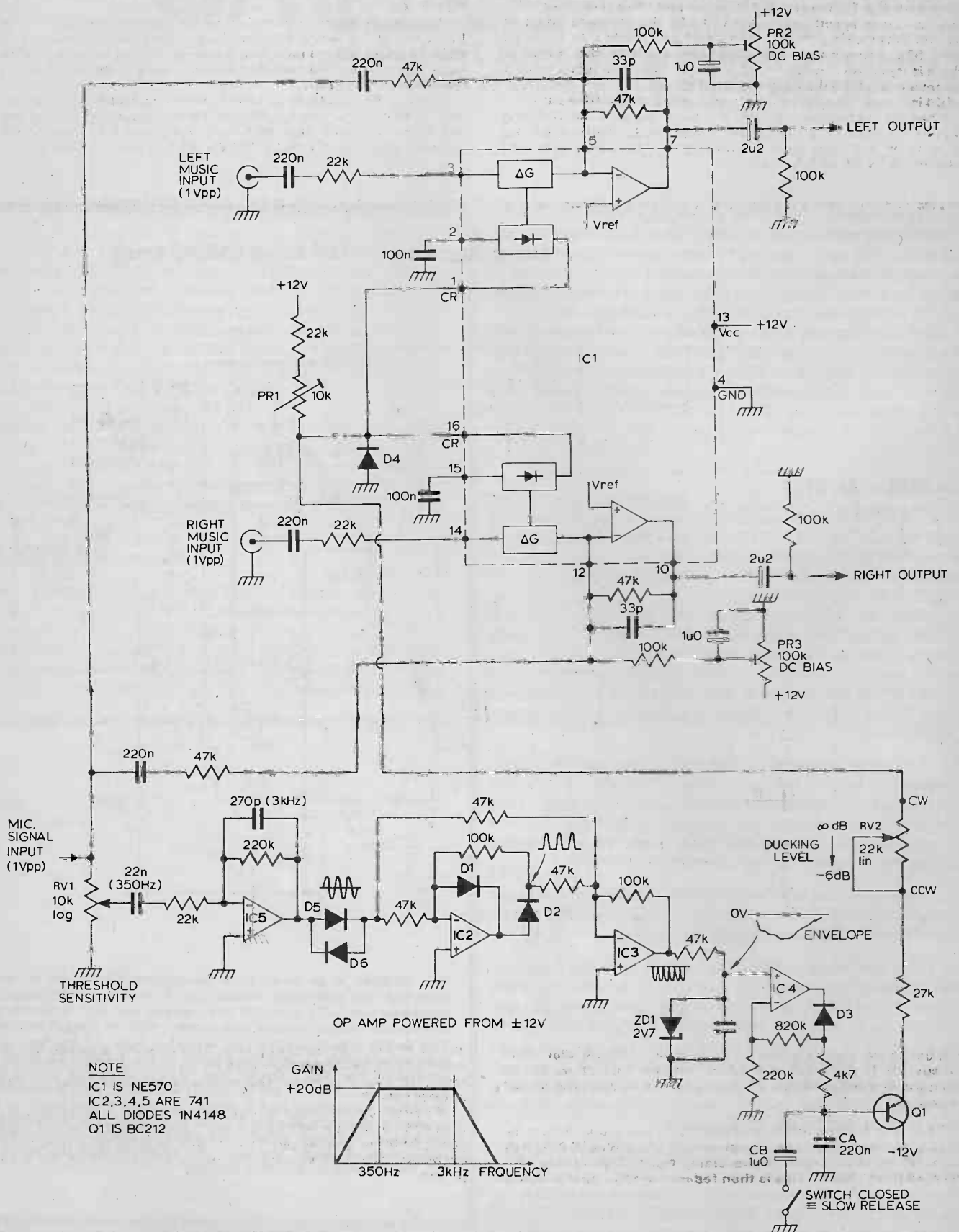Stereo Voice Over (Ducking) Circuit for Disco Unit



The circuit operation is as follows. The microphone signal comes via VR1. This pot sets the sensitivity of the circuit to the microphone signal. If it is too sensitive the unit will be 'ducking' every time the DJ breathes. IC5 is an amplifier and filter. The filter has been specifically tailored to fit the characteristics of speech, thus making the ducking unit less sensitive to spurious noise. IC2, 3 forms a precision full wave rectifier, the output of which is low pass filtered and then fed to IC4. This wave form is the envelope of the microphone input signal.


IC4 is a peak, negative going, voltage detector with a gain of x 5. When the DJ begins to speak, IC4 goes negative and in doing so pulls the base of G 1 negative. When the DJ stops speaking the base of G 1 rises back towards 0 V with a time constant determined by CA or CA + CB.

This is the release time and it controls the speed with which the faded down music comes back to full volume. G 1 is an emitter follower and its job is to rob current from the gain cells in the NE570.

This current sets the volume of the two music channels. When the base of G 1 is pulled down to the negative rail, the amount of robbed current is maximum, and when no current flows into pins 1 and 16 of the NE570 and all of it flows into g 1, then both music channels are turned off.

To set up PR1, put a large signal into the microphone channel, set RV2 so that it is a short circuit and then adjust PR1 so that the two music channels just close off. PR2 and PR3 should be adjusted so that pins 7 and 10 of the NE570 are both + 6 V.

Clever Fuzz Box

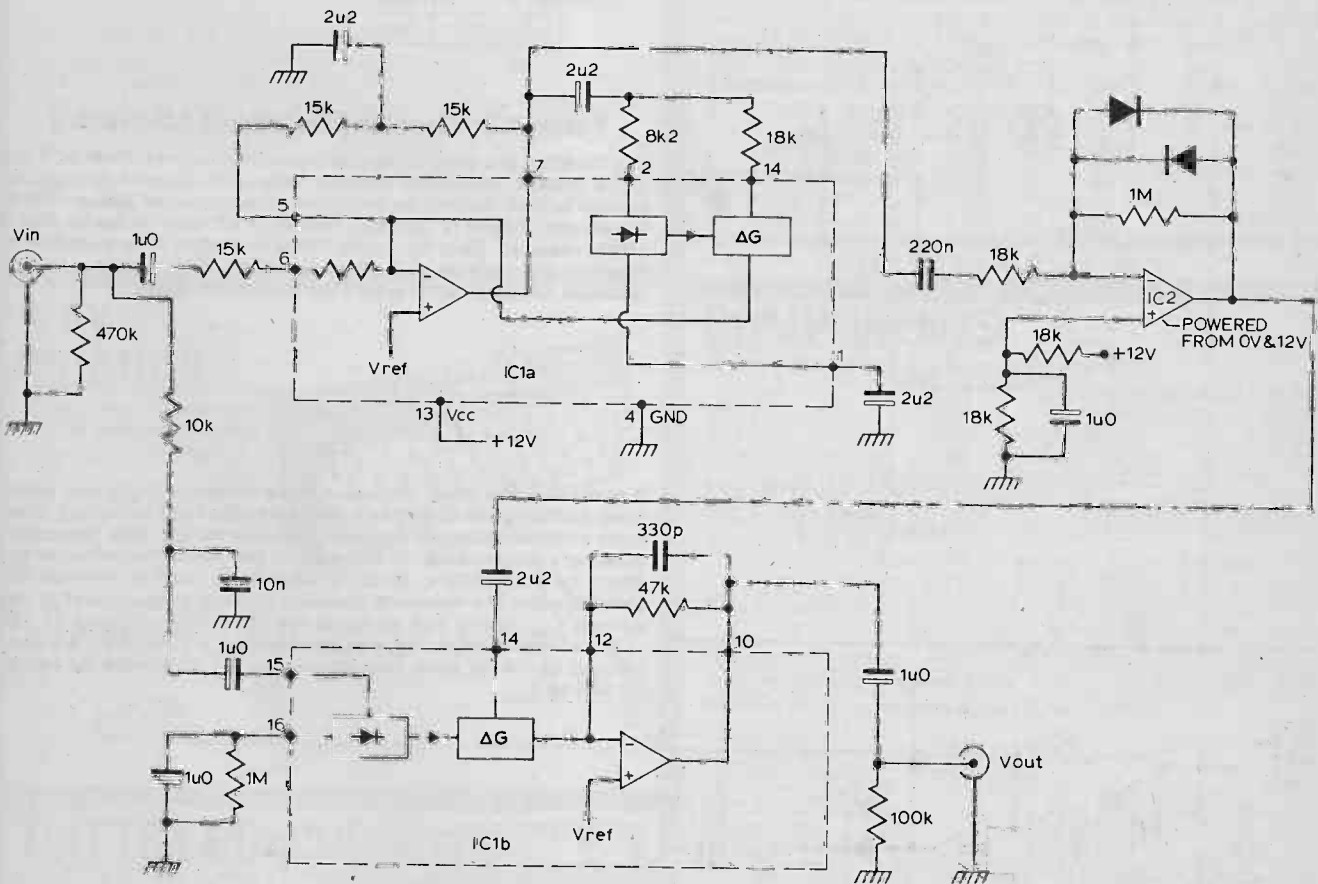

Fuzz boxes are used by guitarists to produce harmonic distortion and sustain. If you want to produce only the distortion, but to retain the original envelope of the signal then this is the circuit for you.




IC1 is a 2:1 compressor as described previously. This produces a relatively high level signal which then drives IC2, which is a x 50 amplifier with diode clamping. IC2 produces the distorted (fuzz) sound. This is then fed into the IC3 gain cell, the

output of which drives the op amp. This gain cell is driven by the rectified original signal (low pass filtered at 1k5 Hz), so that the distorted sound is given the envelope characteristics of the original sound.

If a fuzz sustain sound is required rather than a dynamic fuzz then IC3 could be modified (by the inclusion of a clamped high gain amplifier driving pin 15) so that it acts as a low level expander. This will squelch the noise at the end of the fuzz period.

Track and Hold

In this example the CA3080 is used as a current controlled switch. When the control voltage is high, I_{ABC} is maximum, (0.44 mA) and the OTA gain is maximum. The voltage at pin 2 of IC1 adjusts itself so that it is the same as that on pin 3, this being due to the 100 per cent feedback via the high input impedance voltage follower IC2. When the control voltage is 0V, I_{ABC} is zero and hence the gain of the OTA is zero. Therefore no current comes out of its output and so the voltage at the output of IC2 remains frozen (Hold mode). The maximum differential input voltage is 5 V and this must not be exceeded. The capacitor C should be selected to suit the speed of the operation.

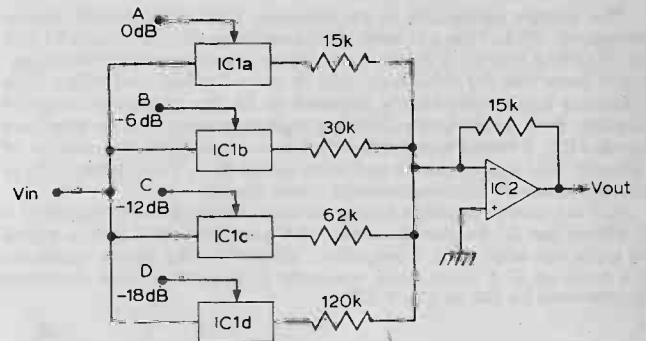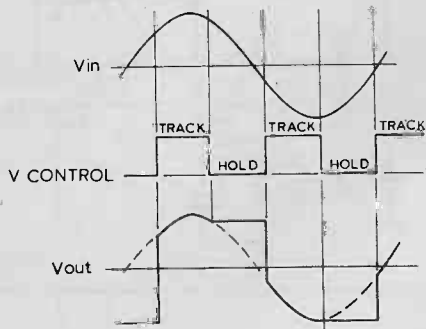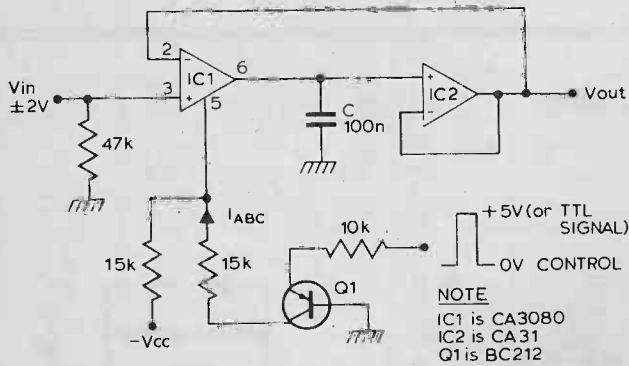

0 ≡ -6V
1 ≡ +6V

A	B	C	D	GAIN
1	0	0	0	0dB
0	1	0	0	-6dB
0	0	1	0	-12dB
0	0	0	1	-18dB

POWERED BY ±6V


NOTE
IC1 is 4016
IC2 is 741

Voltage Controlled (Switched) Attenuator

The CD4016 is a quad analogue transmission gate. That is, it is a quad voltage controlled switch. When the control is high the switch is ON, having an effective resistance of about 400R. When the control is low the switch is off and it looks like a 100M resistor. Thus by using 4016 switches it is possible to 'Switch' the voltage gain of an amplifier. The resistors in this example are selected to give 6 dB changes in gain.

Filter

A state variable filter produces three outputs: highpass, band-pass, and lowpass. It is thus a very versatile filter structure, even more so if the resonant frequency can be varied. This frequency is linearly proportional to the gain of the two integrators in the filter. Two CA3080's, (IC2, 4) have been used to provide the variable gain, the resonant frequency being proportional to the current I_{ABC} . Using 741 op amps for IC3 a control range of 100 to 1, (resonant frequency) can be obtained. If CA3140's are used instead of 741's then this range can be extended to nearly 10,000 to 1.

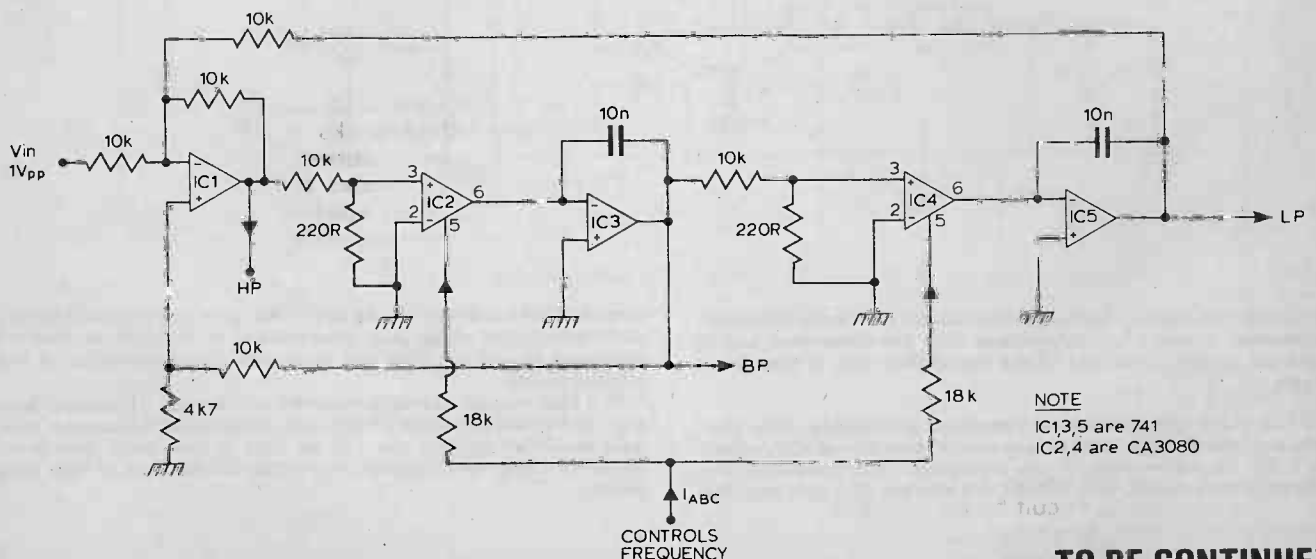

RF POWER METER

Take a load off your mind — and put a proper and useful load on your antenna — with the ETI Project Team's venture into the realms of the short and shorter wave.

THIS REFLECTOMETER design, apart from being simple, elegant and easy to construct, covers three decades — from 100 kHz to 100 MHz, and can be constructed for RF powers as low as 500 mW or up to 500 watts.

The problem for most designs for reflectometers, or "Swar" meters as they tend to be called colloquially these days, is that they generally only cover about one decade in frequency range — usually 3 to 30 MHz or, if further, have discontinuities and drastic sensitivity variations at the extreme ends of their frequency range.

Sensitivity is a problem with the commercially available instruments also. Those with the best sensitivity — 5W full scale usually — are made for the (overseas) CB market, and while they will work over most of the HF spectrum (some extending beyond that), sensitivity is insufficient if you are working with low power solid state RF circuitry or doing a deal of antenna experimentation.


Performing antenna measurements at powers of 5W or more is discourteous to say the least, especially where sustained or many consecutive measurements need to be made.

The reflectometer / RF power meter described meets the requirements of most people involved in RF measurements requiring such an instrument and where a disparate variety of facilities are required.

This project will be extremely useful to radio amateurs, servicemen involved in communications, in laboratories, etc.

Construction

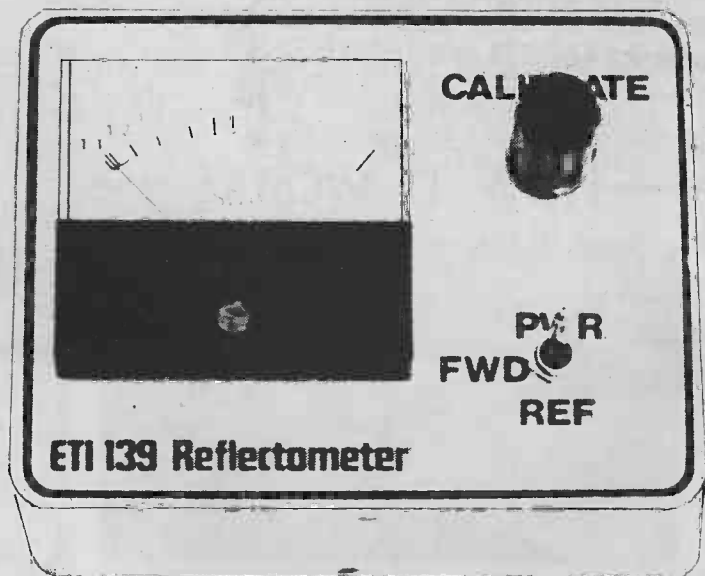Construction is very straightforward. The printed circuit design given is recommended, as variations in layout may affect performance.



All the components are mounted on the *copper side* of the PCB, which is subsequently assembled onto the coax sockets and mounting bolts.

Commence by winding the toroid current transformer secondary turns. Refer to the circuit diagram. Cut a 45 mm length of RG58, stripping back the braid and insulation as illustrated in the component overlay and photographs. This is not all that critical, but maintain as much braid as you can to reduce problems with errors creeping in at the top end of the frequency range due to discontinuities here.

Slip the toroid over the short length of coax and mount this assembly on the PCB. Position the toroid centrally and fix it in place with a small amount of pliable plastic cement compound.

Mount all the other components next. Pay particular attention to the orientation of the diodes D1, D2, D3.

The trimmer capacitor, C2, is shown as a mica compression type. Any suitable trimmer — such as the Philips film trimmers — can be used, however, the mica compression

trimmer provides a certain amount of 'vernier' adjustment.

The PCB and major components are assembled into a suitable metal box.

The completed PCB is mounted in the following way:

Once the coax sockets are mounted, and the two mounting bolts are in position, a coax plug (with cable) should be plugged into each of the sockets in order to locate the centre-conductor pins of each socket.

The PCB is then placed into position and the input/output pads soldered to the coax socket pins. Make sure that a good fillet of solder secures the pin to the PCB pad.

Two nuts on the mounting bolts, one under the PCB, one on top of the PCB, then secure the board mechanically as well as providing a ground connection. Refer to the pictures and components overlay.

Connections to the meter, pot, and switch — located on the front panel, can then be made with short lengths of hookup wire.

Calibration

A suitable RF source, a dummy load and an RF voltmeter or a known-accurate RF power meter are required for test calibration of the instrument. Any of the standard amateur texts (ARRL, RSGB handbooks etc) provide excellent construction details of dummy loads to dissipate a variety of powers. The same texts describe suitable RF

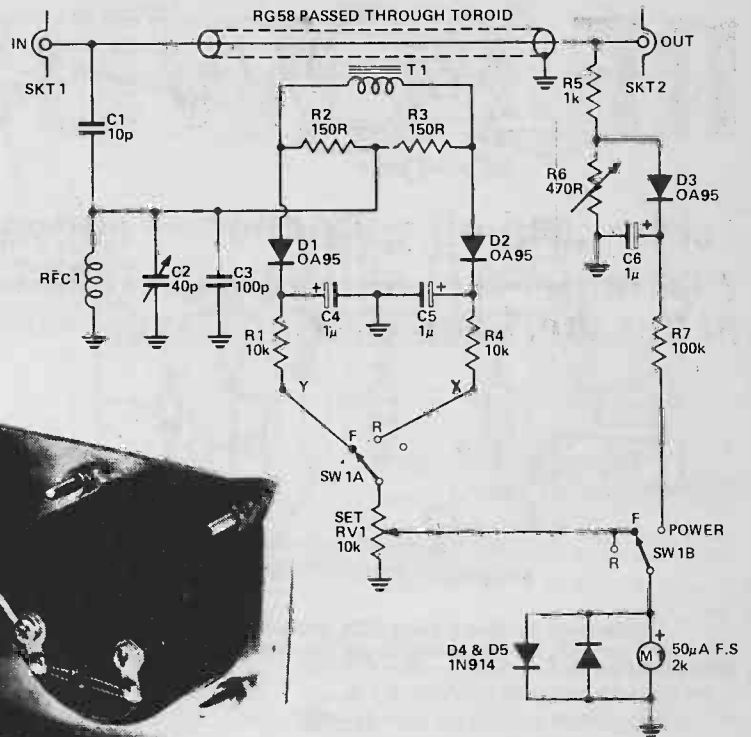
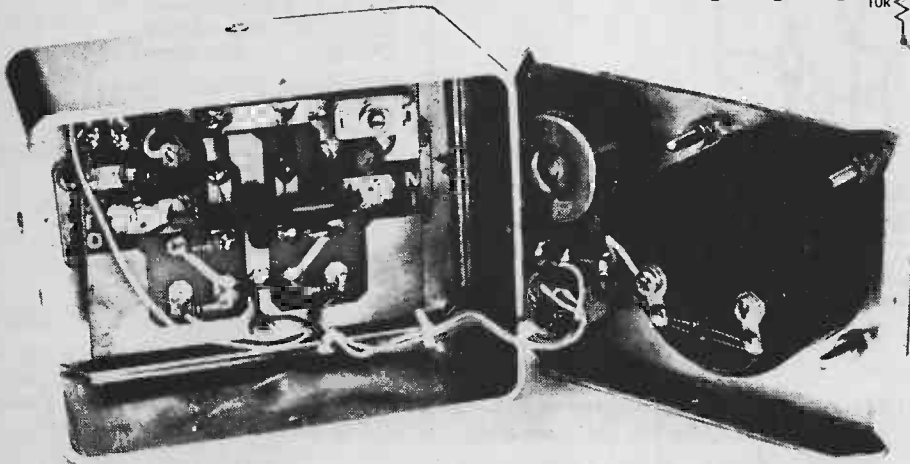


Fig.1. Circuit diagram of the SWR power meter. Note the unusual switch configuration, using a double pole three way switch.

voltmeter probes that may be used in conjunction with a multimeter.

SWR Scale

The instrument is connected between the RF source and the dummy load. Turn the sensitivity control fully anticlockwise. Switch to read forward power.

Key the RF source and slowly rotate the sensitivity control clockwise. The meter reading should increase. If it doesn't, check wiring. If it goes in reverse, you've got D1 back to front!

If all is well, advance the sensitivity control until the meter reads full scale. Switch to read reverse power. Adjust the trimmer C2 to obtain a minimum meter reading. It should go to zero; increase the sensitivity when a very low reading is reached to ensure that C2 is adjusted correctly.

This completes the adjustment of the Reflectometer section. The scale calibration can be obtained from Table 1.

The scale on the meter may be hand-lettered using Letraset or other 'rub-on' lettering. The original lettering may be painted over and the new SWR scale inserted beneath the original scale.

HOW IT WORKS

The reflectometer employs a "current transformer" having an electrostatically-shielded primary with a high-ratio secondary winding driving a low value load resistance.

A short length of coaxial cable, passed through a ferrite toroid, forms the primary with the braid connected so as to form an electrostatic shield.

The secondary of the current transformer consists of a winding around the circumference of the toroid, coupled to the magnetic component of the 'leakage' field of the short length of coax cable.

The secondary drives a centre-tapped resistive load (R2/R3) connected to a voltage sampling network (C1-C2/C3) tapped across the RF input such that sum and difference voltages will appear across the ends of the

current transformer (T1) secondary winding.

Diodes D1 and D2 rectify the sum and difference voltages from the secondary of T1, RF and audio (modulation) bypassing being provided by C4 and C5. The RF choke, RFC1, provides a low-resistance DC return for the signal rectifiers, D1 and D2.

The power measurement facility is obtained by tapping off a portion of the RF voltage on the line via R5 and R6, and rectifying this with D3. Capacitor C6 provides RF and audio (modulation) bypassing.

As the load on the rectifier is so light — R7 being 100 k and the meter being 2 k, peak power is measured.

Diodes D4 and D5 provide protection for the meter.

BUYLINES

As with all RF projects, some of the components will not be stock items with the majority of suppliers.

In case of difficulty with any of the

items Catronics at Communications House, 20 Wallington Square, Wallington, Surrey should be able to help.

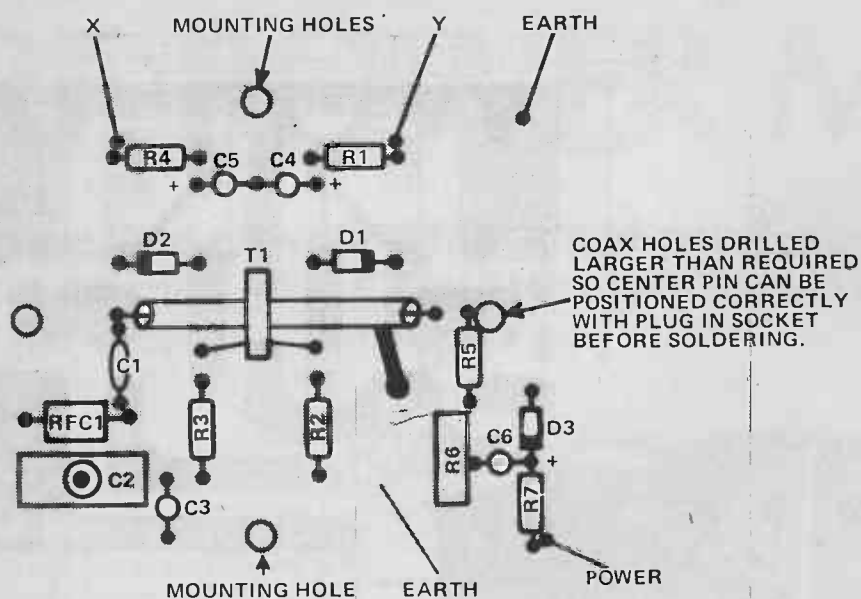


Fig. 2. Component overlay for the PCB. Note that, contrary to the usual practice, the components are mounted on the copper side of the board.

TABLE 1

SWR	Scale reading
3:1	0.5 full scale
2.5:1	0.42 full scale
2:1	0.34 full scale
1.5:1	0.2 full scale
1.2:1	0.1 full scale
1.1:1	0.05 full scale

TABLE 2

Peak Power, full scale	R2 value.
500 W	68R
200 W	2 x 33R in parallel
100 W	33R
50 W	68R
20 W	2 x 330R in parallel
10 W	330R
5 W	680R
3 W	1k + 100R in series *

*linearity suffers

Power

The circuit (Fig. 1) shows a divider network, consisting of R5 and R6, tapped across the RF on the coax line.

The lower divider resistance R6 is shown as a variable element. A

miniature deposited carbon track trimpot was used in the prototype. The low value types seem to perform quite well over a wide frequency range and one was used here for convenience. It was set so that the full-scale reading of M1

PARTS LIST

- Resistors** all 1/4W, 5%
 R1 10k
 R2,R3 150R
 R4 10k
 R5 1k
 R6 470R trimpot or fixed
 —see text
 R7 100k
- Potentiometer**
 RV1 10k/C pot
- Capacitors**
 C1 10p ceramic
 C2 40p trimmer
 C3 100p ceramic
 C4 - C6 1u solid dipped tantalum
- Semiconductors**
 D1 - D3 OA95
 D4,5 1N914
- Miscellaneous**
 RFC1 Any moulded RF choke, 1mH or more (value not critical).
 SW1 Two pole three way
- M1 50 μ A meter T.E.W. type 2k resistance.
 T1 40 turns of 35 gauge B & S enamelled wire, around circumference of Neosid toroid type 28-511-31, 12.7 mm o.d., 6.35 mm i.d., 3.18 mm thick, F14 material (see text)
- Coax sockets SO239 or other type to suit
 Case Horwood type 34/2/D (100 mm x 75 mm x 50 mm).
 PC board ETI 139
 Two 25 mm long bolts with three nuts and two lock washers each; nuts and bolts for coax sockets (if required); length of RG58 coax; 6 mm dia. sleeving; hookup wire, etc.

corresponded to a particular peak power dissipated by the dummy load (as measured with an RF voltmeter or known-accurate RF power meter).

Fixed resistors may be substituted for a trimpot, necessitating only a check of the accuracy of the full scale peak power reading. Values for particular full-scale power readings are given in Table 2.

The power scale should be calibrated to suit the individual instrument. It will be non-linear, particularly at the bottom end.

Performance

The inherent impedance of the prototype instrument was measured using a TEK 5 W dummy load and a Hewlett-Packard vector impedance voltmeter. The results are illustrated in Fig. 4.

The impedance discontinuities introduced by the prototype are well

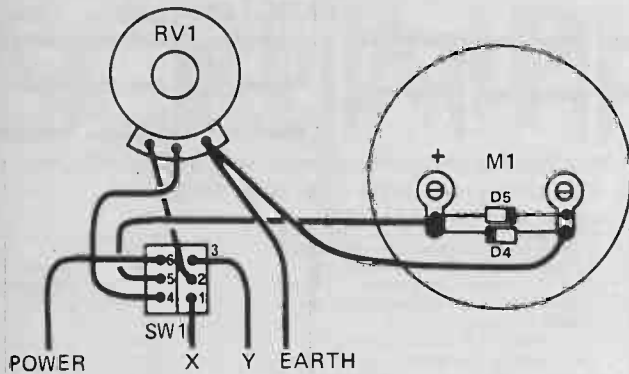


Fig. 3. The meter, sensitivity pot and switch connections. Leads X and Y go to the D2 and D1 respectively, while the lead marked 'POWER' goes to R7. Refer to Fig. 2.

inside the basic accuracy capability of the meter movement! The real part of the instrument's impedance is within 5% of the nominal 50 ohms — most of this is probably due to connectors and construction discontinuities.

The variation in the real part of the impedance is within \pm one ohm across the frequency range of the instrument, and can be essentially ignored.

The reactive (imaginary) component of the instrument's inherent impedance is negligible up to 20 MHz when it begins to become slightly capacitive.

The overall impedance decreases rapidly above 100 MHz.

Sensitivity and sensitivity bandwidth of the prototype is excellent. The half-power points of the sensitivity bandwidth of the reflectometer are at approximately 350 kHz and 25 MHz.

Full-scale deflection at 27 MHz requires 0.8 watts into 50 ohms. Mid-band sensitivity is under half a watt!

Modifications

For higher power applications, the basic sensitivity of the reflectometer can be reduced by one of several methods, or a combination.

If you are working with powers around 20 to 50 watts, R2 and R3 can be reduced to 47 ohms. For higher powers, the number of turns on the toroid can be reduced, and R2/R3 further reduced in value. As a guide, reduce the secondary of T1 to 20 turns and R2, 3 to 47 ohms.

Everything else remains unchanged. This should suit power levels of 200 watts and higher.

Other types of coax sockets can be used, such as the BNC, type N or the inexpensive Belling-Lee sockets. No modifications to the PCB are necessary, however, mounting details of the sockets and board will need to be altered to suit.

The basic reflectometer construction is so simple and inexpensive that several can be built and installed to provide remote SWR/RF-output monitoring of antenna installations.

The RF portion can be mounted at a convenient place and the reflectometer output leads X and Y taken to remote metering facilities. Power output measurement circuitry is probably superfluous in these circumstances.

Protection circuitry for transceivers and power amplifiers may be simply realised using the basic reflectometer circuit and activating protection devices by comparing the output voltages of D1 and D2.

Swept VSWR measurement can be accomplished using the basic reflectometer circuit. The differential output from D1/D2 can be used to drive the vertical axis of a CRT display (via suitable amplification), the horizontal axis being driven by the sweep voltage of a voltage-controlled signal generator. Voila! — swept VSWR measurements.

Accurate SWR measurements for

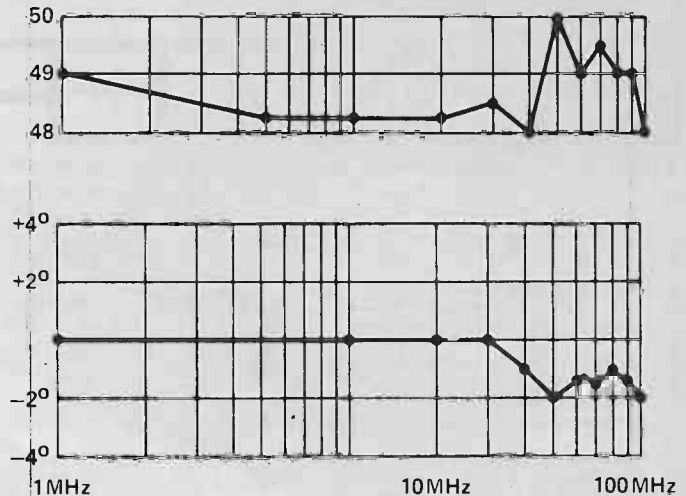


Fig. 4. Top: real or resistive component of the prototype's inherent impedance. Lower: Reactive component.

VSWR values below 2:1 can be made by driving an expanded-scale differential voltmeter circuit that measures the output difference between D1 and D2. This technique is well illustrated in reference 2.

This type of instrument is particularly useful when making VSWR performance plots of antennas over a narrow bandwidth (providing they closely match 50 ohms in the first place).

This reflectometer technique can also be used to measure power. However, the authors opted for the diode RF voltmeter method as it is somewhat more versatile, and is unaffected by the sensitivity bandwidth of the toroidal current transformer. See the two references for more details.

The sensitivity bandwidth may be shifted up in frequency by a decade or more, such that it rolls off around 1 MHz and 50 MHz, by employing a toroid for T1 of the same dimensions but made of F25 material. **ETI**

References


Whilst not the 'definitive' texts on this type of reflectometer, these two references provide good practical sources of information.

1. "Frequency Independent Directional Wattmeters"; P. G. Martin, Radio Communication (RSGB journal), July, 1972.
2. "Test Equipment for the Radio Amateur"; H. C. Gibson G8CGA, published by the RSGB, 1974.


electronics today

OCTOBER 1978 VOL 7 NO 10


INTERNATIONAL

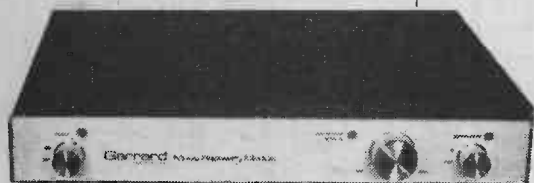

De-click box p.70

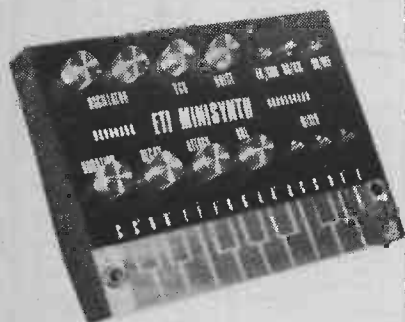

Sound project! p.17

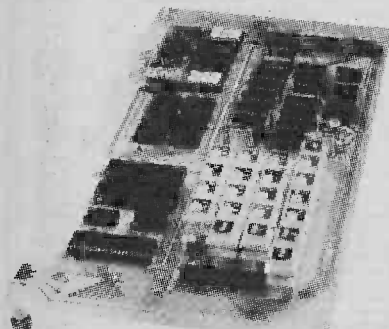

Key Issue p.35

FEATURES

NEWS DIGEST	7	News, Views and Comments
GAIN CONTROL	22	Electronic methods of controlling gain
SCRUMPI 3	35	It's a kit — it's cheap — is it good?
PIRATE RECORDINGS	45	How it's done — and undone!
DATA SHEET	61	7217-2-7227 and counting!
GARRARD MRM 101	70	De-clicking de records
MICROFILE	83	More on micros
AUDIOPHILE	87	A glass, a pre-amp and a new class . . .
ELECTRONICS TOMORROW	90	Logic of tomorrow?
TECH-TIPS SPECIAL	94	Eight pages of circuits to try

PROJECTS

COMPLEX SOUND GENERATOR	17	A cheaper way to annoy people!
RF POWER METER	30	What's watt at RF
POWER BULGE	41	Two into one <i>does</i> go
TELEVISION CHESS GAME	48	Make your move on screen
BELL EXTENDER	65	Keep it ringing the changes
PROXIMITY SWITCH	75	A bit near the mark!

INFORMATION

ETI PRINTS	29	You know it makes sense
MARKETPLACE	39	Time for a couple of offers
ETI SPECIALS	58	Make an issue(s) out of 'em
NOVEMBER PREVIEW	56	Have we a surprise for you!!!
SUBSCRIPTIONS	69	Make life easy
PANEL TRANSFERS	74	It'll rub off on you!
ETI BOOK SERVICE	81	Read <i>this</i> fine print

INTERNATIONAL EDITIONS

AUSTRALIA	Collyn Rivers Publisher Les Bell Acting Editor
Holland	Anton Kriegsman Editor-in-Chief
CANADA	Steve Braidwood Editor Graham Wideman Assistant Editor
GERMANY	Udo Wittig Editor

EDITORIAL AND ADVERTISEMENT OFFICE

25-27 Oxford Street, London W1R 1RF. Telephone 01-434 1781/2. Telex 9311896


Halvor W. Moorshead	Editor
Ron Harris B. Sc	Assistant Editor
Gary Evans	Projects Editor
Jim Perry	Specials Editor
Phil Cohen B.Sc, William King	Editorial Asslstants
John Koblanski	Project Design
Steve Ramsahadeo	Project Development
Paul Edwards	Technical Illustrator
Margaret Hewitt	Administration
Andrew Scott	Office Manager
Kim Hamlin, Bren Goodwin	Reader Services
Tim Salmon, Val Tregidgo	Advertising
Mark Strathern (Manager), Tom Moloney	

PUBLISHED BY Modmags Ltd., 25-27 Oxford Street, London W1R 1RF
 DISTRIBUTED BY Argus Distribution Ltd. (British Isles)
 Gordon & Gotch Ltd (Overseas)
 PRINTED BY QB Limited, Colchester

Electronics Today International is normally published on the first Friday of the month prior to the cover date

COPYRIGHT: All material is subject to world wide Copyright protection. All reasonable care is taken in the preparation of the magazine to ensure accuracy but ETI cannot be held responsible for it legally. Where errors do occur a correction will be published as soon as possible afterwards.

SCRUMPI 3

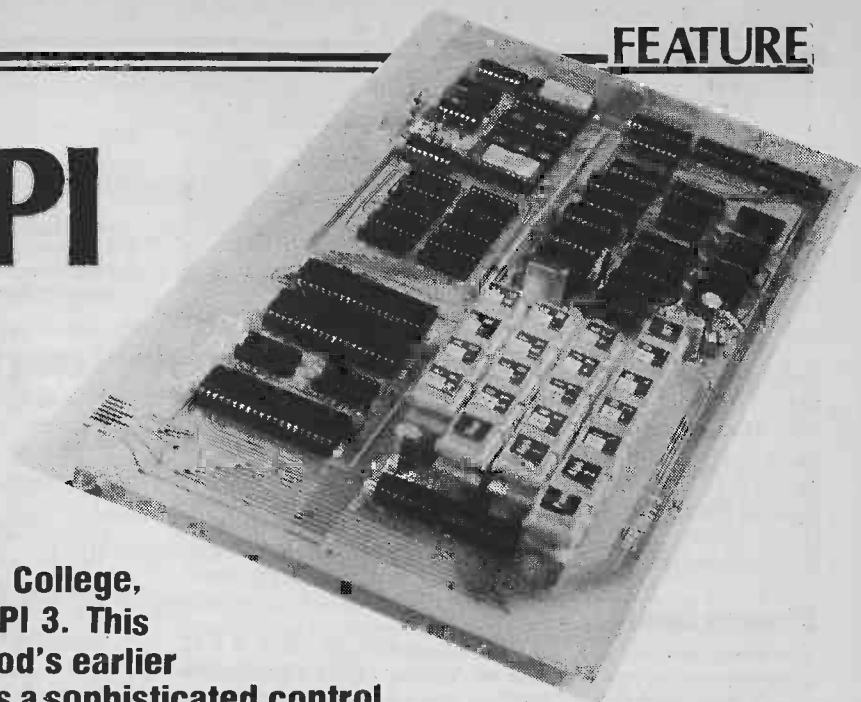

Justin A. T. Halls, of Queen Mary College, takes a look at Bywood's SCRUMPI 3. This kit is an improvement over Bywood's earlier LED switch kits but is still seen as a sophisticated control device rather than a personal computer. The kit also provides an excellent introduction to the worlds of MPUs.

Scrumpi 3 is the cheapest currently available micro-processor kit with full alphanumeric input and a VDU type display. It is the successor to the Scrumpi 1 and 2, switch and LED kits and is based on the same MPU, National Semiconductor's SC/MP. The kit also provides facilities for cassette and teletype interfaces.

Scumpi 3 is built on a 380 X 190mm printed circuit board, with plated through holes and a clearly component overlay. High quality, low profile sockets are provided for all the ICs and two 16 pin DIL sockets are provided for access to the 16 I/O ports and the UART. Access to the TTY interface is via four pins at one side of the board, while power supply lines, reset line and video signal are taken to an eight way, 0.1" edge connector. A UHF modulator is mounted on the underside of the board and provides a signal suitable for most 625 line TV sets via a standard phono socket. Data and address busses are not directly available, but test points are provided at either end of the board. Input is via a 21 key keyboard, made up of good quality switches with transparent key caps, beneath which are fitted self-adhesive labels identifying the key functions.

Three main chips are the sc/mp ii, which has the advantage over the SC/MP 1 of being faster and requiring only a single +5 V power supply, the INS8154 RAM I/O, which contains 128 bytes of memory and provides 16 individually addressable I/O ports, and the AY-5-1013 UART. Two EPROMs, protected from accidental erasure by opaque labels over the quartz windows, hold the 512 byte monitor program and 512 bytes of user accessible I/O routines. A 7MHz crystal provides a clock from which are derived the VDU control signals as well as a 3.5 MHz clock for the MPU and a 15 kHz clock for the UART. The video interface circuitry occupies nearly half the board and uses the 8675bwf character generator to provide the full 64 upper case ASCII characters in white on black or black on white, either of which may be selected as standard and which may be mixed on the screen.

Data sheets are provided for the MPU and RAM I/O chips and two handbooks provide assembly and

operating details. An SC/MP pocket instruction guide is also provided. The user has to provide a +5 V, -12 V power supply plus a 7.5V supply for the UHF modulator. It is also necessary to drill holes in the PCB to take mounting pillars if the kit is to be fitted in a case, or take legs if the kit is to be used naked. A reset switch is also needed.

Getting It All Together

Actual construction of the kit was quite straightforward, although the instruction manuals tended to be reminiscent of some car technical manuals, with instructions like 'all sockets, capacitors, resistors, diodes, links and keyswitches can be installed at this point', and the crystal and one of the ICs are never mentioned at all. One component that did cause some problems was the UHF modulator. The position of this is not marked on the board and the connections to it are not indicated. A phone call to Bywood confirmed that this does in fact fit beneath the board, the mounting pins having to be filed down to fit the holes provided. If the kit is not fitted in a case the presence of the modulator beneath the board means that legs must be fitted to enable the board to sit squarely on the table when in use.

When fitting the 21 keyswitches care must be taken as the holes for them are not too accurate and bending the pins too far to make them fit could damage the switch. Since many of the tracks run very close together, care should also be taken with the soldering and it is a good idea to leave the kit overnight after assembly and then re-checking very carefully for the presence of solder splashes or bridges.

To minimise the possibility of damage to delicate and expensive ICs and to ease trouble-shooting, the chips are inserted sequentially, checks being made at each stage to ensure that one part of the circuit works before proceeding to the next. Apart from TV synchronisation problems most of this setting up procedure was very simple, although some statements were a little misleading and a great deal of time was spent won-



The assembled Scrumpi 3 kit. The system's firmware is resident in the two EPROMs seen top left with their protective labels. The three presets we had to fit to get the video levels right can be seen bottom centre.

dering why the address decoding wasn't decoding before we found that the NWDS line had to be earthed first. It is in cases like this that a circuit diagram would have been invaluable. The use of the INV line as a test probe was very clever and useful; if the line is taken to logic 1, the screen remains the same, but if taken to logic 0 the screen inverts (i.e. black characters on a white background instead of white on black).

Pictures Galore


The video circuitry is basically quite simple, with a 7.02 MHz clock driving a series of dividers and a handful of gates. Two MM2112, 256X4 RMs hold the picture in a memory mapped display. The rest of the video circuitry simply consists of the character generator and a number of buffers.

The UHF modulator is pre-tuned to channel 36 and merely needs connecting to the aerial socket of a TV set. It can be run from the on-board +5 V line, but with some sets better resolution, especially when displaying black characters on a white background, is obtained by running the modulator from a separate supply of about 7.5 V. A simple, unregulated battery eliminator, set at 6 V (actual output about 7.5 V) is sufficient.

The Bywood errata sheet points out that some video monitors or converted TVs require a 4 V pk-pk video signal rather than the 1.5 V pk-pk signal provided by the kit, and that this can be obtained by adjusting the values of R3-R5. We had great difficulty in obtaining a stable picture and eventually had to resort to replacing the resistors with 470R presets; even now picture stability is not as good as it might be and it is continually necessary to adjust the vertical and horizontal hold controls. It is quite possible however that these difficulties are due to the use of a cheap portable TV which may well not be set up correctly. No problems have been found with these modulators in other applications.

Key Features

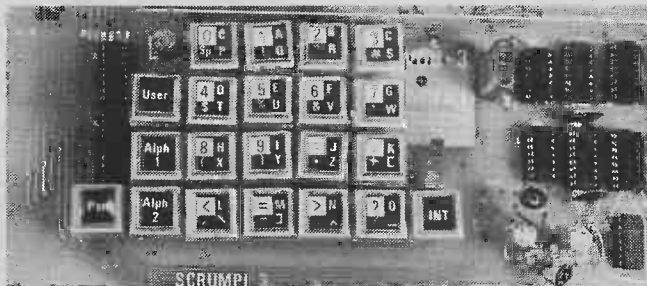Bywood have managed to squeeze all 64 upper case ASCII characters onto a 21 key keyboard. This is achieved by the use of three shift keys. One soon gets used to using the shift keys and although it would be more convenient for entering hexadecimal code if the lower case characters were 0-9 and A-F, the current layout has presumably been chosen to ease use as a general purpose teletype.



Getting In And Out

The teletype interface, supplies and receives a 20 mA current loop and is therefore compatible with many types of TTY. Control of this interface is purely by software, using the SC/MP 'flag 0' for output and 'sense B' line for input, each bit being set or sensed individually, with a delay instruction being used to set the bit rate to 110 baud or whatever rate is required. Unfortunately, details of sending and receiving routines are not supplied, although these should not prove too onerous to write.

Parallel I/O is provided for by the INS8154 RAM I/O chip which also contains the 128 bytes of RAM supplied with the kit. 16 I/O lines are available and these may be configured as two independent eight bit ports designated A and B, each of which may be specified as an input or an output port. This provides for very versatile interfacing with the outside world.

For those who prefer a serial interface however, an AY-5-1013 UART is provided. The rate at which data is output or received by the UART is determined by an external clock, this being set to sixteen times the desired baud rate. In the Scrumpi 3, the 15.625 kHz line frequency for the VDU is used, providing a baud rate of 960 (not 9600 as stated in the manual). If a more standard baud rate is desired, the internal clock can be disconnected and an external clock provided via one of the I/O sockets; 4 800 Hz will give 300 baud suitable for a cassette interface, while 1 760 Hz will give a rate of 110 baud. No details are given of how to use the UART, but these have been published in ETI (Dec. 1977).

All of these various I/O lines, except the TTY 20 mA loops, are available from two 16 pin DIL sockets. Each socket is provided with +5 V and ground connections, as well as the UART transmit and receive lines and the MPU 'sense A' line, used by SC/MP for software interrupts. In addition socket A has the eight bits of port B, reset, and the UART clock, while socket B looks after the eight bits of port A. Unfortunately the INTR line from the RAM I/O chip, which is used in handshaking routines, is not available, but it could be connected to an unused pin on one of the sockets, as could the serial input and output lines from the SC/MP which are also unavailable.

Where Its All At

The kit comes with 128 bytes of RAM (not counting the 256 bytes used by the VDU) of which 64 bytes are

Close up view of Scrumpi's keyboard. By using the various shift functions this keypad can provide a full alpha-numeric set.

available to the user for writing programs. Of the remainder, 32 bytes are available as a user stack which may also be used by some of the Scrumpi sub-routines, eight bytes are used for storing labels and eight bytes are used as a monitor permanent area, the remainder being used as monitor stacks during various command routines. This RAM occupies the area of memory from 0F80 to 0FFF (see Fig 1). The monitor PROM takes up 512 bytes from 0000 to 01FF, with 512 bytes of I/O sub-routines in PROM at 0600-07FF. Keyboard, UART, VDU and parallel I/O takes up all the space from 0C00 to 0F80. Since the SC/MP only provides direct access to the lower twelve bits of the address bus, allowing for 4K of addressability, this leaves 2K to be accounted for. On-board sockets are available for all this, divided into 2x5 12 byte PROMS (5204 or 4214) and 1K of RAM as eight 256 X 4 (2112). To expand further than this the top four bits of the address bus have to be latched at NADS time, when they appear on the data bus. However since it is assumed that very few users will want to go beyond the available 1K of RAM and 1K of PROM without the aid of an assembler, access to the control lines and buses is not provided. For testing purposes however, the buses are available at test points at either end of the board and control lines could be taken out by means of wire links from convenient points.

Controlling Your Scrumpi

The monitor contains five basic commands. Typing 'I', followed by a four digit hexadecimal address and 'INT', results in the display of the address called and the data stored there. A number of alternatives now exist. Typing in a two digit hex number followed by 'INT' will cause that number to be stored at that memory location and the address and contents of the next byte of memory are displayed. Instead of entering data you can type '=n', where n is an integer from 0-7. The lowest two characters of the address are then stored and can be used later, by typing '?n', which will calculate the offset required for a programme counter relative jump to the address labelled by n. When using '=n' or '?n' the address is not incremented and the offset provided or fresh data may be entered at that location in the normal way. To return from the data input mode to command level, you can either press reset or type '>'. Typing the command 'L' followed by 'INT' will result in the display of the eight bytes of memory holding the labels.

The command 'H', followed by a four digit hex address, produces a hexadecimal dump of the next 48 bytes from the address given, arranged as six rows of eight bytes, each row preceded by the address of the first byte in that row.

Having entered a program using 'I' command and having checked it using a hex dump we now want to run it. This is done simply by typing 'G' and the address at which the program starts, bearing in mind that the first byte of a program is always ignored. Software break-points may be inserted in a program by using an XPPC 3 instruction, exchanging the program counter for the contents of pointer register 3, which returns control to the monitor and gives a current status dump. In this the contents of the three internawcpointer registers are shown, (P3 will always point to the address of the breakpoint), as well as the contents of the accumulator, extension register and status register. In addition, the 32 bytes of user stack are also displayed. The program can be continued from where it left off by typing the command 'C'

In addition to the monitor, eight I/O subroutines are provided for use by user programs. With these data may be entered from the keyboard or written to the VDU, or messages can be displayed on the VDU. Alternatively the value in the accumulator can be displayed as a hex number (rather than as an ASCII character) with or without a trailing space, or a hex number can be read from the keyboard. Finally four bytes from the user stack may be used to display a six digit number with its sign. All of these subroutines are accessed simply by exchanging the program counter and pointer 3 and most of them are re-entable.

If additional PROMs are used to extend the monitor, they will be automatically detected by the existing monitor, which checks for a 00 at address 0200, and used directly. One additional PROM that is available from Bywood is a disassembler, which will take a machine code program and translate it back into mnemonic form, producing a full assembler style listing.

Reading It Up

The two handbooks are well and entertainingly written, starting from absolute basics and working up, so that even someone who had never heard of a microprocessor before would soon be able to use the Scrumpi. Book 1 starts with an explanation of the hexadecimal number system and proceeds to build a micro-(macro-?) processor called PC/MP (Paper and Cardboard Micro Processor) with which it explains all the happenings inside the MPU, by making you do all the internal operations yourself. In this way a deep understanding of what actually occurs within the MPU is imparted.

Having explained the workings of MPUs in general the architecture of SC/MP is considered, along with the necessary associated components such as RAMs and PROMs. Book 1 then goes on to describe the construction and use of Scrumpi 2, most of which is of little interest to the Scrumpi 3 owner, although the final section on interfacing with the outside world via UARTs and ports is of interest even if lacking in detail.

Book 2 is more concerned with Scrumpi 3 and begins by describing the rationale behind the design of this kit. Construction and testing details follow, with a circuit diagram for the VDU and a block diagram for the rest of the system. Bywood consider that 'the PCB is its own circuit diagram' and that further documentation is therefore unnecessary. Having built and tested the kit, you are taken through a series of demonstration pro- ▶

Scrumpi 3's status dump displays the current value of the SC/MP's internal registers plus a hex dump of a section of memory.

```

SCRUMPI 3 STATUS DUMP
P3 P2 P1 EX ST AC
0000 0000 0000 00 30 00
0FC8 F4 03 DC 0B 8B C4 8B 34
0FD0 FC 4A 74 8B 0F 84 87 F0
0FD8 D7 0B F4 0F 59 B6 FB D5
COMMAND ?
    
```

FEATURE: SCRUMPI 3

grams which display the full character set, write messages on the screen and demonstrate all the internal logical and arithmetic functions that are available. Here again the text is clearly written and we soon got to know how to use the majority of the various facilities that are available. Finally the memory assignments are given as well as a description of the monitor routines, I/O subroutines and the optional disassembler. At the end of the book is a glossary of technical terms, some useful addresses and data on the SC/MP II and the INS8154.

What there is of the handbook is excellent, well written and well illustrated and without too many errors. However, a great deal of information is lacking, such as any details of how to use the UART or how to configure and use the I/O ports. It would also have been nice if a few simple user programs could have been included, say for a cassette interface, handling the teletype link and maybe some mathematical routines.

Terminal Device

In general this kit succeeds in doing what it sets out to do very well indeed. It is nicely produced, fulfills its designers requirements and the distributor, Bywood Electronics, are very helpful in the event of any difficulties or problems.


The quality of the product is let down however, on two counts. The main defect lies in the lack of information supplied with the kit and this is a very serious failing. A TTY. 20 mA loop interface is provided, with no indication of how to send data to it, or how to receive data from it and with no mention of what format the data should be in. i.e. what should be supplied in the way of start, stop and parity bits. Also, no data or information is provided on the UART and even when a data sheet has been obtained, describing how to use the device, it is necessary to trace out the tracks on the PCB in order to identify the TBMT and DAV lines. Admittedly a data sheet is provided for the INS 8154, but this is only of marginal use when attempting to use the device and such a versatile chip as this deserves far more recognition in the manuals.

The other failings of the kit are relatively minor, but seem all the more unnecessary for that very reason. Things like not using the serial input and output lines from the SC/MP. The kit already has impressive I/O facilities, but why not make use of a facility that is sitting there waiting to be used. The unused INTR line from the RAM I/O chip is another case in point, since this negates a large proportion of the power of the I/O device, especially if you want to interface to devices such as A/D converters which require a certain amount of handshaking.

Once you have found out how to use them, the I/O facilities on this kit are very good, largely thanks to the versatility of the RAM I/O chip, which gives such a varied selection of I/O modes. The keyboard is not as convenient as a full QWERTY keyboard, but it is perfectly adequate for a kit that is intended for semi-dedicated applications. The 8 X 32 character TV display may seem limited in size when compared to full VDU systems, but is quite adequate for the vast majority of applications and it has even been found possible to play Conway's Game of Life on it, although this led to some rather interesting edge effects at times.

This kit is certainly a great advance over Bywood's previous, LED and switch kits and with a price tag of around £150 is certainly good value for those who are either hooked on SC/MP or who are prepared to use the full power of the kit to make it pay its way as an intelligent terminal for a larger or more powerful system.

ETI

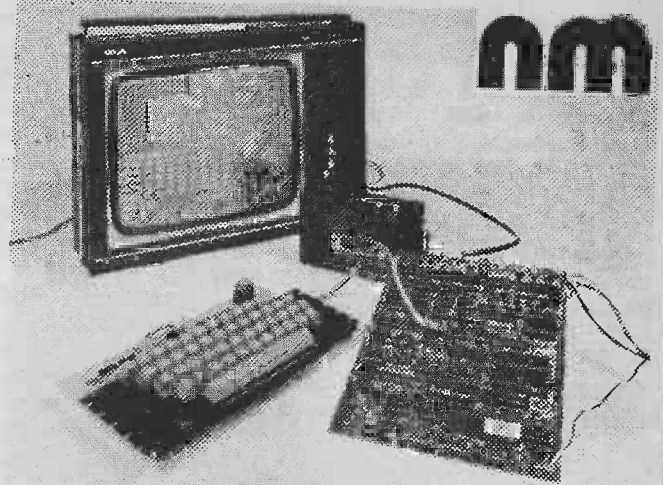

MICRO-COMPUTER for the HOBBYIST

THE ONLY **COMPLETE** MICRO-COMPUTER
AVAILABLE TO THE HOME CONSTRUCTOR

FEATURES

- ★ Supplied in kit form for self-assembly
- ★ Full documentation supplied
- ★ Fully screened double-sided plated through hole printed circuit board
- ★ Full 48 key keyboard included
- ★ 2K x 8 Ram
- ★ 1K x 8 monitor program in Eprom
- ★ Powerful Mostek Z80 CPU
- ★ 16 x 48 character display interface to std un-modified T.V.
- ★ T.V. display memory mapped for high speed access
- ★ On board expansion to 2K x 8 Eprom
- ★ On board expansion for additional 16 I/O lines
- ★ Memory may be expanded to full 60K (plus 4K existing on board)

SOFTWARE FEATURES

- ★ 1K x 8 monitor program providing
- ★ 8 operating commands, supporting Mem examine/modify, tabulate, copy, break, single step, executive, tape, load, tape dump.
- ★ Reflective monitor addressing for flexible monitor expansion through user programs
- ★ Monitor sub-routines include: — delay ASCII coding, binary to hex conversion, clr screen, scroll up, string print, cursor shift and many others.

EXPANSION

- ★ Expansion buffer board £25.00
- ★ Memory board, with decoders and all hardware except memory ICS £35.00
- ★ 4K dynamic memory ICS £36.00
- ★ 8K dynamic memory ICS £60.00
- ★ 16K dynamic memory ICS £144.00
- ★ 32K dynamic memory ICS £250.00
- ★ I/O board with decoders and all hardware except ICS £35.00
- will accept up to 3 PIOs, 1 CTC and 1 UART
- ★ S.a.e. for full expansion details

OTHER HARDWARE

- ★ 2.2A power supply for up to 4K expansion £24.50
- ★ 8A power supply for larger than 4K expansion £45.00
- ★ Expansion card frame £29.50
- ★ Programming manual £3.50
- ★ Hardware & software manuals (supplied in kit) £2.95

Add VAT at 8% on all items except manuals

Manuals
Separately
£2.95

Complete Kits
NOW IN STOCK

£197.50
+ VAT 8%
POST PAID

Sole Appointed
London
Stockists

After sales service available

HENRY'S RADIO
All mail to: Henry's Radio 404 Edgware Rd, London W2
LONDON W2: 404 '6 Edgware Road. Tel: 01-723 1008

POWER BULGE!

Astound your ears and annoy your neighbours with four times your normal sound level, courtesy of the ETI Power Bulge.

POWER AMPLIFIERS COME in all sorts of shapes and sizes, most small groups rely on 100 W types as they are widely available and relatively cheap. Even though the people next to the speakers think the sound is loud enough, the performers usually want more power. The simple solution is to buy more powerful amplifiers — but it can be a lot cheaper to buy two less powerful ones.

The 'Power Bulge' is designed to be used with two low power amplifiers, and produce not just double power but four times the power of the separate amplifiers! The reason for the apparent power gain is that the voltage finally produced at the loud speaker decides the power — and power is proportional to the square of the voltage.

Construction and Use

The prototype was built into a small Verobox. As large signals are involved screening in a metal box was not needed. The box size dictated the battery type, if you want to use a PP3 or other battery obviously a larger box will be needed.

When completed you need two power amplifiers (preferably of the same type) to use the unit. A normal stereo amplifier is ideal, if it has a tape monitor switch. A signal is taken out from the preamplifier and fed back into the power amplifier section (via the tape input if fitted). The loudspeaker is connected across the two positive speaker terminals as shown.

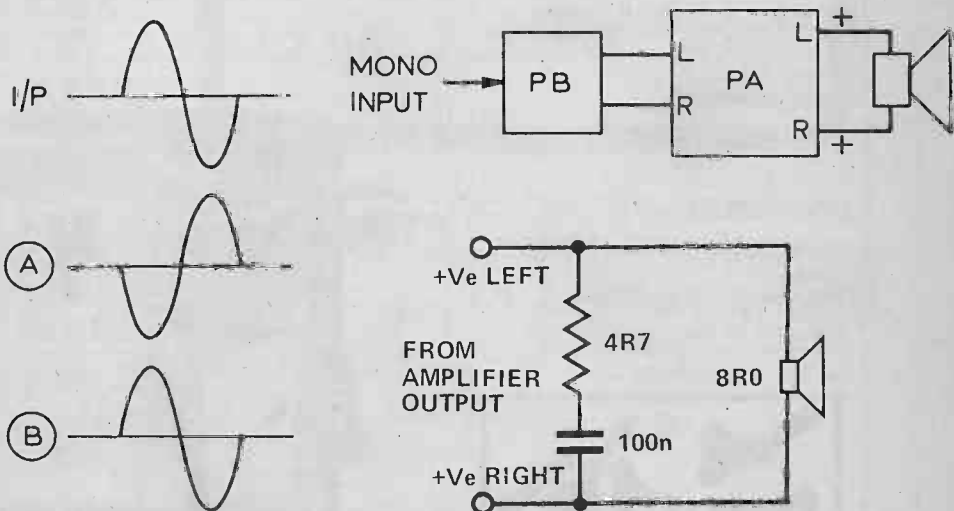


Fig 1. On the left is a diagram showing the input and output waveforms from the Power bulge, as can be seen the two outputs (A and B) are 180° out of phase with each other. Above right is how to connect the unit to any stereo amplifier, the lower circuit shows additional components suggested to stabilise the speaker load.

HOW IT WORKS

The idea of the unit is to produce two waveforms 180° out of phase. This is accomplished by Q1. The balance between the two waveforms is equalised with RV1. The three 10u capacitors are to AC couple the signal and C4 is to decouple the battery.

BUYLINES

No problems here, the case is stocked by most component outlets; the battery is available from photographic shops if not stocked by your friendly neighbourhood electronics shop.

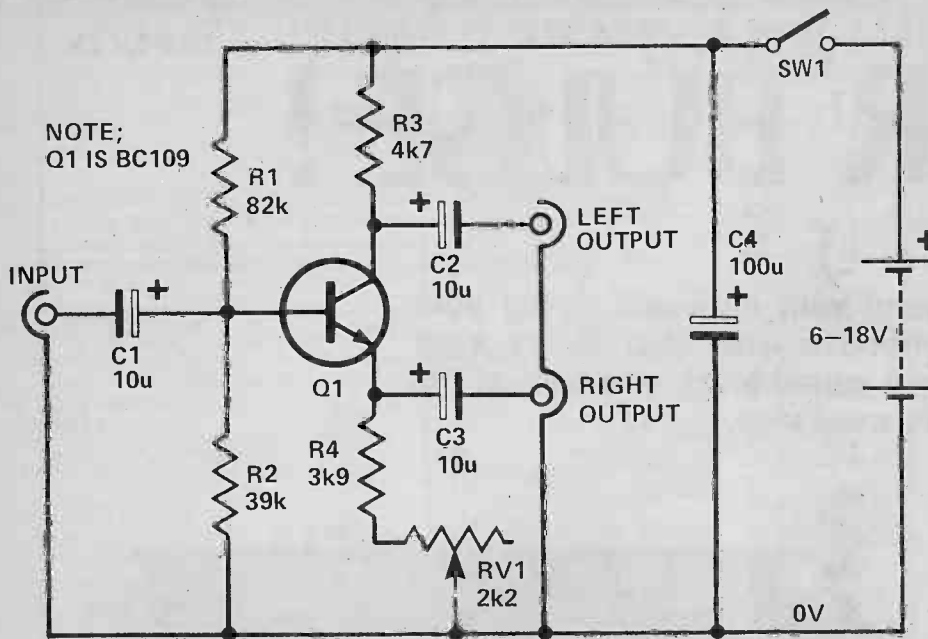


Fig. 1 Full circuit diagram

PARTS LIST

RESISTORS

R1	82k
R2	39k
R3	4k7
R4	3k9

POTENTIOMETER

RV1	2k2 preset
-----	------------

CAPACITORS


C1, 2, 3	10u 16 V electrolytic
C4	100u 25 V electrolytic

SEMICONDUCTOR

Q1	BC109
----	-------

MISCELLANEOUS

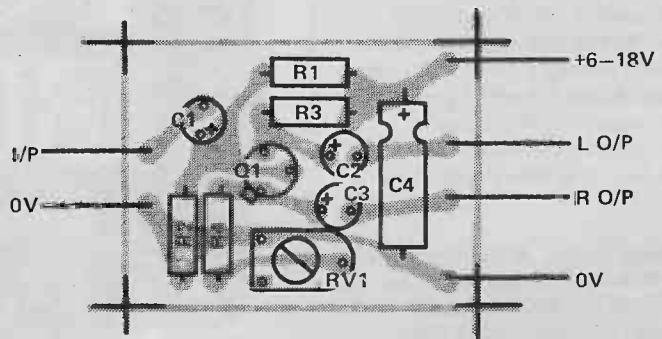PCB as pattern, case (vero 75-1413E), battery B154, switch, phono sockets.



Above is the component overlay of the complete device, below left is the PCB pattern shown full size (45 x 34mm). Neat layout of the prototypes can be seen clearly in the photograph below.



Fig. 3 PCB patterns shown full size



PIRATES AND JOLLY NOTCHES!

IT WAS ONLY a few years ago that private or 'bootleg' versions of Bob Dylan's Basement Tapes and Pink Floyd's Dark Side of the Moon, sold like the proverbial hotcakes, along with a host of others.

These recordings blatantly advertised the fact that they were pirated, and thus of illegal origin — transgressing not only performer's rights but also copyright. Many people were attracted to pirate recordings for there seemed to be something rather exciting about owning a recording which the artist did not approve. Often, the pirate recordings contained material not released on genuine recordings, or were of concert performances which often differ markedly from studio performances. Quality was almost inevitably low-fi!

Through a combination of circumstances, these bootleg recordings gradually disappeared from the market. Groups employed stewards to hunt through audiences looking for tape recorders, legal prosecutions were brought against bootleg distributors etc. Finally, high prices for low-fi killed the market.

New Track

Recently, however, the pirates have changed tack and are presenting recordings that are either made to mimic legitimate releases on well know labels or to appear like legitimate competition. For example, a recording stolen from EMI may either be packaged to look like an EMI recording, or packaged in a sleeve with an authentic-sounding company label, but not that of an authorised EMI trader. In neither case does the artist, EMI or anyone else (save the bootlegger and his outlets) receive any reward.

Those recordings that mimic legitimate releases are usually a straight, undoctored copy of the original, with slightly reduced fidelity. When released on a phony label, often the recording is altered in the transfer to disguise its origin, usually by dubbing applause or extra instruments onto the copy.

The problem arises here in that both these techniques are far harder to detect and prove as bootleg than the previous methods. The British Phonographic Industry (the UK recording industry trade association) have taken numerous court actions, with some success, resulting from pure detective work.

Self-Destruct

However, the final solution to professional piracy relies on technological aids. This can be achieved by either making the physical act of illegitimate copying technically impossible, or to make the technical detection of such copying unambiguous. Unfortunately, despite considerable efforts, little real practical headway has yet been made in either of these directions.



If record companies had their way, each disc or pre-recorded tape released and sold to the public, would self-destruct, refuse to play or produce unacceptable sounds if copying was attempted.

To date, anti-copy remains an impossible dream. Inventors still tackle the problem, the cash rewards for a workable system would be enormous. Inevitably, one red-herring scheme keeps being re-invented.

Back in 1967/68, the Beatles' Electronics Company, Apple, leaked a story about three patent applications on a new anti-copy system. Any attempt at recording a disc pressed according to this system would result in a high-pitched whistle they claimed. The idea attracted a certain amount of attention, but, in time, the patent applications were allowed to die, along with the publicity and Apple Electronics disintegrated.

Although details of the idea remain a secret, the system probably involved recording an ultrasonic carrier frequency on the disc. Thus, at any attempt to put the ▶

disc material on tape the carrier on the disc would beat with the tape recorder's ultrasonic bias signal and impress an audible signal on the tape.

In this way, two inaudible frequencies are combined to produce an audible frequency which destroys the recording attempt.

A little thought shows the snags in the system. To produce an audible beat with the very high bias frequency used on tape recorders (around 70 kHz or higher) requires that a similar signal be recorded on the disc. The studio cutting machine won't cut it, the factory pressing machines won't press it and the would-be-recordist's cartridge wouldn't reproduce it.

It is also easily filtered out at any stage of the production chain, either intentionally or otherwise, with no loss of quality, because the carrier signal is inaudible anyway. Different tape recorders have widely different bias frequencies which also defeats the system.

The drawbacks are enough to discourage further reinvention of this system and doubtless account for the demise of the Apple patents.

There is another daunting aspect to anti-copy systems. It is likely that if anyone does devise a system that will prevent the copying of a disc or tape onto existing tape recording machines, the recorder manufacturers will soon devise a defeat button or circuit to make copying possible again.

Watermarks

Anti-copy systems appear defeated for the moment. However, the concept of an indelible watermark on the recorded sound appears somewhat less fanciful.

As with anti-copy, watermark systems have gone through numerous futile reinventions. The aim is to record an inaudible identification signal along with the recorded sound. The watermark signal is inaudible to the listener when the disc or tape is played on conventional equipment, but it can be identified or decoded by special equipment.

Ultrasonic (high frequency) and infrasonic (very low frequency) watermarks have similar limitations to the anti-copy schemes. For this reason, it is essential to adopt a sledge-hammer approach to prove the origin of copied material. One such attempt, by Capital Radio who recently broadcast some previously unpublished Beatles tapes, involved putting a loud station ident ('194') over the recording every few seconds. Thus, if ever a bootleg recording is issued, its origin will be audibly stamped all over it! With the station ident so loudly intrusive there would likely to be little incentive anyway.

Notches

There is another approach which a number of recording companies are seriously considering. This is the *Audicom* system invented by Murray Crosby.

It was originally intended for collating automatically the number of times a commercial was transmitted on a radio or TV station, for accounting and statistical purposes.

The system works like this: At a frequency around 2-3 kHz, a tight notch filter with a very narrow bandwidth (around 100 Hz) bites a small chunk out of the audio spectrum. At the same time a binary code watermark signal is modulated onto an audio frequency subcarrier of the corresponding frequency and bandwidth so that it fits neatly into the window left by the notch filter. The amplitude of the subcarrier frequency is varied so that it



BSM/KH/RS/T

tracks the audio level of the surrounding programme. In this way, the coded identification signal is always submerged by the programme, but it is still recognisable by a decoder tuned to the narrow band notch frequency and designed to interpret the digital information modulated on the subcarrier.


Sounds like a great system for discs and tapes. However, several difficulties arise. If, for instance, the coded subcarrier is at such a low level, might it not be lost in noise after transmission or the copying process? This is one area which EMI, RIAA and others are investigating. Even if they get results, we are not likely to read, or hear about. Because, if the system is adopted, it would not be prudent for the record companies to indicate the level at which noise destroys the code.

Sub-Noise


One set of technical specifications indicates that when the programme audio level is zero, the subcarrier coded signal will be 55 dB below the peak level the carrier would be at peak audio programme level. When the programme audio is at peak level then the audio subcarrier in the notch will be 40 dB below the programme level. Thus, the subcarrier is always submerged by the programme but would still be detectable by a decoder tuned to the narrow band notch frequency so that the digital watermark code is recognisable by the digital decoder.

ETI


TELEVISION

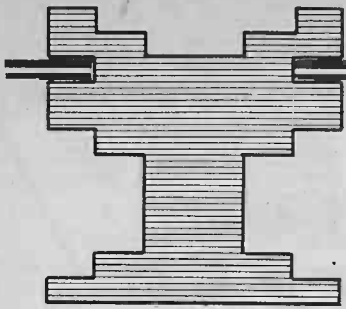


QUEEN

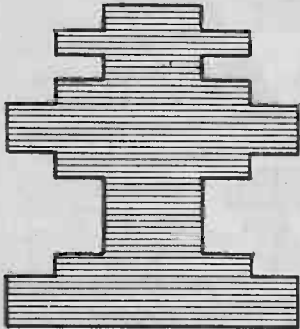


KING

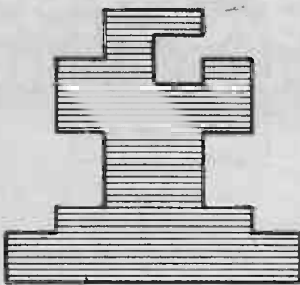

BISHOP

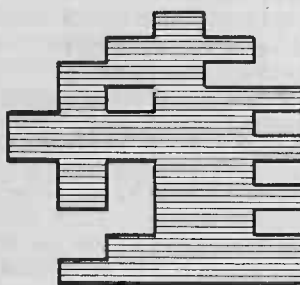

KNIGHT

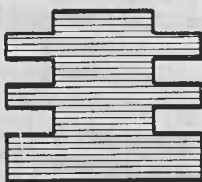

PAWN



TOLINKA IS A device which is genuinely useful to the chess-player, performing automatically all the housework of listing, analysis and filing of chess information. It is not like a TV game, nor is it one of those machines which plays chess from an internally stored programme, which is little more than chess-like solitaire.

The project is based on a SC/MP MPU, which with some RAM, ROM and various support ICs performs all the work that goes on in this chess players comfort. Don't be worried by the mention of the term MPU — to use Tolinka you won't need to think — or curse — in Hex, manipulate machine code and be generally au fait with ALUs. The machine has been designed to be both straightforward to use and to build.

Design Philosophy

Tolinka was designed with cost and availability in mind. When a function could be performed by a few, cheap readily available parts instead of one special expensive chip, the former course was taken. The chess set, for

example, appears to have been made from Lego bricks. If a character generator ROM with more bits in it had been used in conjunction with a highspeed clock, a chess set which would have met the approval of Lewis Carroll could be produced (though I suspect that gentleman would like the present one). If you have sufficient memory, then you have sufficient resolution to transmit pictures even of Raquel Welch digitally, but no intelligence would be added by this course in spite of the doubled cost — faster memories, more power, bigger box etc.

The piece design has been subjected to much consideration and choice became, in the end, a matter of taste. The intention is to represent a Staunton Chess Set without conflict of symbolism or departure from family likeness. It is true that representations are not beyond reproach and any suggestions will be welcomed.

In each square 128 bits are available, eight horizontal and sixteen vertical divisions. A border must be left around the piece —

CHESS

PART ONE

Tolinka, the name coined by Victor Korchnoi to describe this machine that can display a full chess set on the TV screen. The pieces may be moved around at will, and all the moves of a game recorded on a cassette tape for later playback and analysis. Barry Savage, the designer, describes this secret weapon of the West.

BUYLINES

A complete kit of parts for this project will be available only from Videotime Products, 56 Queens Road, Basingstoke, Hants, RG21 1REA for the all inclusive price of £109.50.

Individual parts are also to be

made available but Videotime will offer help, advice and a repair service only to readers who purchase the complete kit. Note also that software, piece design PCB pattern, etc, are subject to copyright.

partly so that identification of the square's colour may be made. So a six by thirteen grid is left. With the exception of the pawns it is thought more uniform if the pieces stand upon a level base. The major pieces are bilaterally symmetrical (both halves the same, if you must), the centre of each of the major pieces is therefore a double column.

The Facts Of Life, Or, How Little Computers Are Made


Son, it is time you were told about the birds and the bees. The creation of computers like the creation of new human beings depends upon the combination of hardware with software. Unlike humans, however, the labour involved cannot be said to be unskilled. Once Tolinka had a mother system to which it was joined by an umbilical cord of wires through which was fed power and information.

During this time of gestation Tolinka's programme was undeveloped and volatile. It was stored on cassette tape whilst the


inventor was not working on it. The instructions were entered in Tolinka's surrogate memory from a hexadecimal keyboard, because little computers do not use ASCII or high level languages which do not use memory space in the most economical way. The author did not use assembly language either because continuous conversations with an MPU in machine code soon render even this mnemonic aid superfluous.

The whole purpose of parenthood lies in teaching the offspring how to manage without parents: little birds are taught to fly alone. So Tolinka's mother system eventually generated Tolinka's software package in the form of a PROM and worked herself out of a job. The umbilical cord was severed, a separate power supply constructed, and Tolinka set up house alone in a small box instead of a 19" card frame.

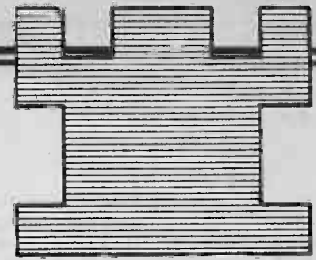
The first prototype circuit boards were made. And modified. And made again. Etc. Until a version of Tolinka was made which represented all of the most desirable features that it was possible to get into the available




ROOK

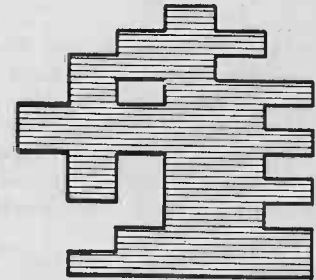


KNIGHT

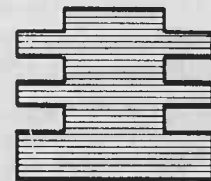

PAWN

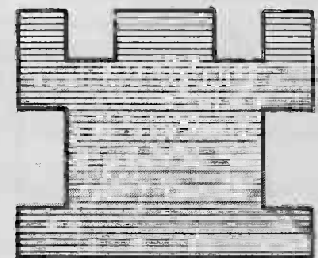

ROOK

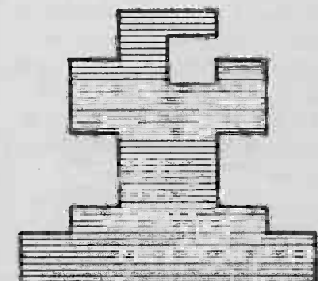

BISHOP

news digest.

for light music

These charming little blobs are Motorola's new BF900 MOSFETs, designed for use in FM tuner designs. They possess a power gain of 20 dB at 200 MHz and low capacitance. The dual gate configuration is intended for AGC operation where the first gate receives the RF while the second controls the transconductance (DC). Both gates are diode protected. Dead clever these

Hong Kong King

Some numbers to tick off on your fingers. In the first six months of the year Hong Kong exported 16 million watches (worth £77m). These break down as 61% mechanical, 29% LCD and only 10% LED and quartz analogue com-

bined. Surprising LED figures eh?

Germany developed a sudden lust for these non-tockers and their imports leapt up by 287%, putting them as the second largest consumers — behind the US and ahead of us!

blobs...
Motorola Ltd, Semiconductor Division, York House, Empire Way, Wembley, Middx.

forget who not?

You know we've quite forgotten why we used this photo at all. Now let's see something to do with TV games? Anyway the editorial desks have been bereft of nice lady photos lately — so this one appeared as an oasis amid the dusty filing trays.

P.S. Binatone the people who make the box in front — don't ask what box or in front of what or we won't



Speak to you again — claim to now taken over half the TV game market — the magic 51% in fact.



son of eti.....




The word is out. For months at ETI we've been planning a second magazine for the electronics enthusiast. Because of the intense competition in this field we've kept quiet about it but now all can be revealed.

ETI has been remarkably successful but we've never pretended that we are ideal reading for the newcomer to electronics—we have assumed that the reader is already hooked into the hobby.


Hobby Electronics will hit the newstands in just over a month and is designed as a companion to ETI—indeed it is being prepared by the same editorial team.

HE is written for the person wanting to find out about electronics—there'll be projects of course but we reckon we've got some pretty good features as well including 'Into Electronics' a major introductory series linked to the O/A level Electronics course.

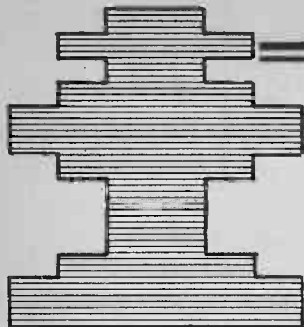In next month's ETI we'll give you a complete breakdown of the contents of No. 1. The cover shown here is of a 'dry-run' issue that has already been produced in small quantities.



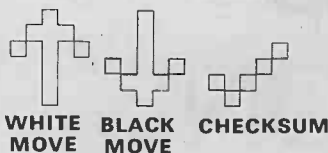The chess set and the numerals were carefully designed to ensure easy recognition without recourse to shapes that would require a high resolution character generator.



memory space. But even now there is more than one software package available and the machine which is in use by Viktor Korchnoi's team is different in certain essential respects from that which is used on the World Championship reports or on the BBC 2 late news.

Further obstetric details and examination of the parent system would form another story.

Tolinka is a Microcomputer

Tolinka is a box measuring 8" x 5" x 3" with a 12 switch keyboard, a DIN socket to interface a cassette recorder and UHF output to drive a domestic TV set.

The picture is in black and white. (Why do people keep asking if it can be done in colour? They never ask for yellow and green chessmen. Yes, it **can** be done in colour, but it isn't as experience with video games has shown that monochrome is easier on the eyes — this remark can be justified by many quotations from manufacturers. Monochrome sets also have wider bandwidth and better resolution.)

What follows is a description of how to use Tolinka — when everything else has failed you might try reading it.

When connection has been made with the TV and cassette recorder, the TV must be tuned to receive a stable picture. If there is a push button tuner, one of the buttons may be left tuned to Tolinka. The output signal Tolinka is producing is assembled from digital waveforms in a preset fashion and there are no adjustable controls. If the TV is overscanning and losing some of the picture it must be adjusted by someone who knows what he is doing. A TV which is set up correctly does not lose any intelligence, but the chessboard sits rather high in the frame and slightly right of centre so that the status information shown on the left of the board may be seen.

On switching on the pieces appear correctly set for the start of a game. On the left of the picture a two digit move number appears with an arrow indicating which player is to move. It is important to remember that Tolinka always considers the move number as having two digits. If the number is less than 10 it has a leading zero.

Making A Move

Tolinka works by moving the contents of one location in memory to another i.e. the contents of one square to another. The eight move-entry keys are divided mnemonically into two groups, kingside/queenside, and labelled both alphabetically and numerically on the standard 'alpha' chess notation system.

Moving A Piece

Four keystrokes enter a move. d2d4 is a move. b1c3 is another. When the machine has received a total of four keystrokes it will 'flash' the move on screen, moving the piece back and forth three times. This is not yet a permanent move, it is the machine inquiring about you intentions. If you are satisfied that the move which is flashing is the move you intended, the MOVE key may be pressed. Tolinka will then make the move final and update the move counter; if it was white's move the arrow will transfer to indicate black is to play next, if it was black's move the arrow will shift to white's end and the counter will increment.


The same keys are used for letters and numbers so it is important to know where you are in the entry sequence. For this reason a STROKECOUNT appears during partial entry at the bottom left of the screen and denotes the number of entry strokes Tolinka has received. If a total entry has been received the location is blank, otherwise it contains 1, 2 or 3. The machine will not accept further instructions unless a proper entry has been made: the


STROKECOUNT must be blank on pressing a function key. If the move which is flashed is not the one desired it may be overwritten by a correct entry of four keystrokes. The game does not progress until the MOVE key is pressed. This maintains integrity with the rules of chess, which state that a move is not made until one's hand has released the piece. If there is a partial entry any key may be pressed until the STROKECOUNT clears, then the correct sequence entered.

Tolinka will allow you to move anything anywhere and does not care whether you break every rule in the book, except in three special circumstances. It is never necessary to make more than one move, even when Castling, capturing en passant or Queening a pawn. Tolinka presumes that if you move your king two spaces you intend to castle, and completes the move for you. If you put a white pawn on the back rank Tolinka presumes that you want a queen instead. (Tolinka might not be right in all cases. You might want a knight or a rook to avoid stalemate. Of all the people who will use Tolinka for the rest of their chess lives, there are a few who might meet this eventuality once or even twice. To these unfortunate few we suggest you extend this apology: "Sorry, couldn't you think of it as a knight, just this once?") If a pawn is moved diagonally into a square where there is no piece to capture, Tolinka presumes and executes the en passant move.

It is not possible to beat Tolinka by fast entry. It is not necessary to wait for the flashing to stop. There is never any point in holding down any key because Tolinka is only waiting for you to let go. Keystrokes should not overlap: one finger entry prevents this. Touch typists should stick to QWERTY keyboards — Tolinka, like the calculator, is a woodpecker's tool.

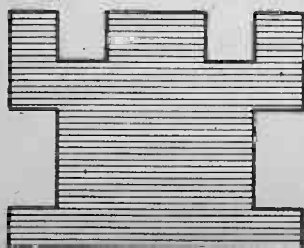Tolinka runs out of memory after black's move 62. If the game must



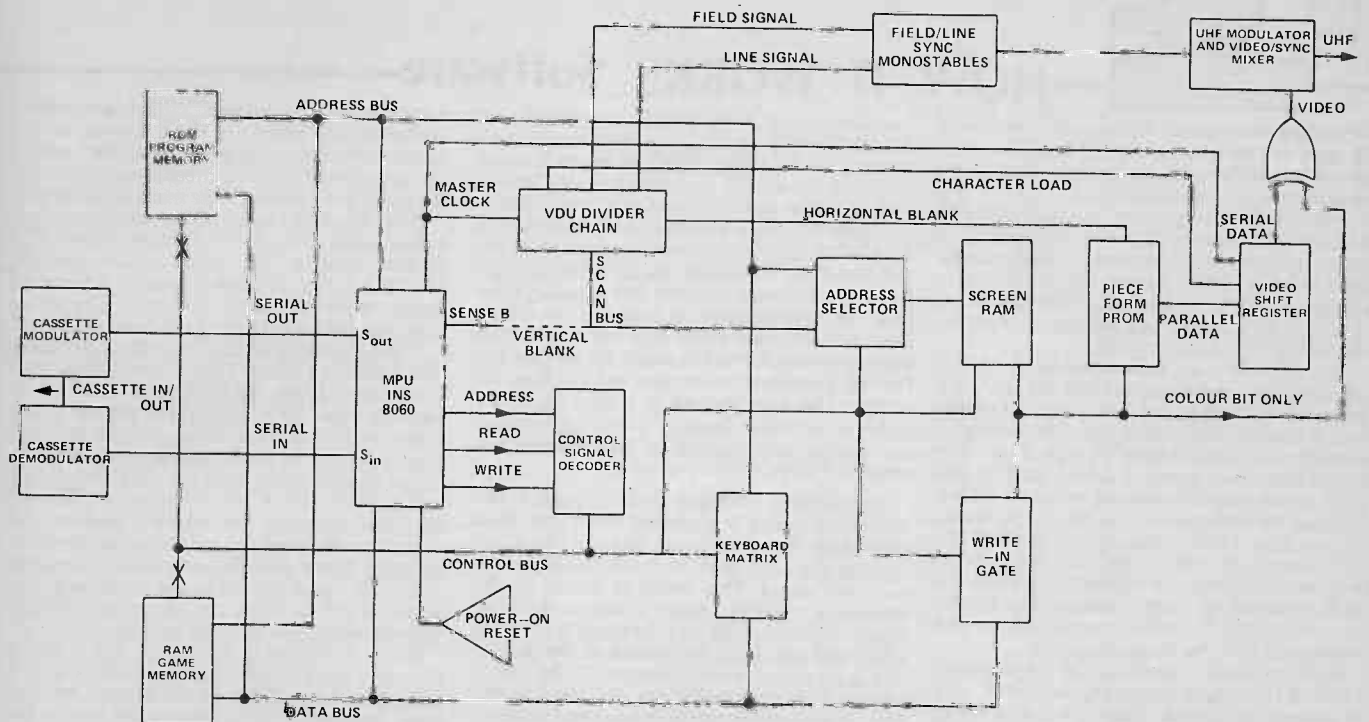

The block diagram of Tolinka. The hardware sections of the design will be described in detail next month.

be continued then it must be set up as a position — after 62 moves there are not many pieces left. Positions and Chess Problems can be set up my moving pieces without regard to the rules. There is no legal sequence of moves to the position of many chess problems anyway.

The GO TO Function

During the entry of a game the position which is current is always shown. But any other position in the game may be brought to view by pressing the GOTO key followed by a two digit move number. Do not forget the leading zero for numbers less than 10. When, for example, GOTO, 0, 9 has been keyed in the position will instantly revert to the position at white's ninth move, which will flash on screen. Remember then the flashing is interrogation, and a different move may be entered, or if the move is satisfactory the MOVE key may be pressed. Thus it is possible to step through the game, making modifications as necessary, or go instantly to any point in it.


Pressing GOTO followed by a RECALL or RECORD function key brings trouble. Tolinka identifies RECALL and RECORD with a hexadecimal number greater than 10. It therefore cannot increment the decimal counter to equal it — but will willingly spend the rest of eternity trying. The only cure is to switch off.


You see Tolinka starts again at the beginning of the game when the GOTO button is pressed and plays quickly through to reach the requested point. Note that the GOTO key doubles as zero and the MOVE key doubles as 9.

Tolinka Is A Videorecorder

There is no need to write down a game sequence. Tolinka records chess games on tape. It records them as a three second leader tone followed by a four second data burst which contains the complete contents of the game memory — up to 62 moves by each player. It follows that a single C60 cassette will hold about 500 games. That's a lot of chess!

Recording time is cheap, less than a penny a game, so it pays to keep two copies of all information and use some tape space between games to make them easy to find. If the tape recorder has a counter a written index should be made, if there is no counter then a single spoken number between games is the best system. To record on the tape a description of opponent, event, date, etc., isn't much help in finding a game in a long tape. These comments are for guidance only, and you will no doubt find your own system for using Tolinka.

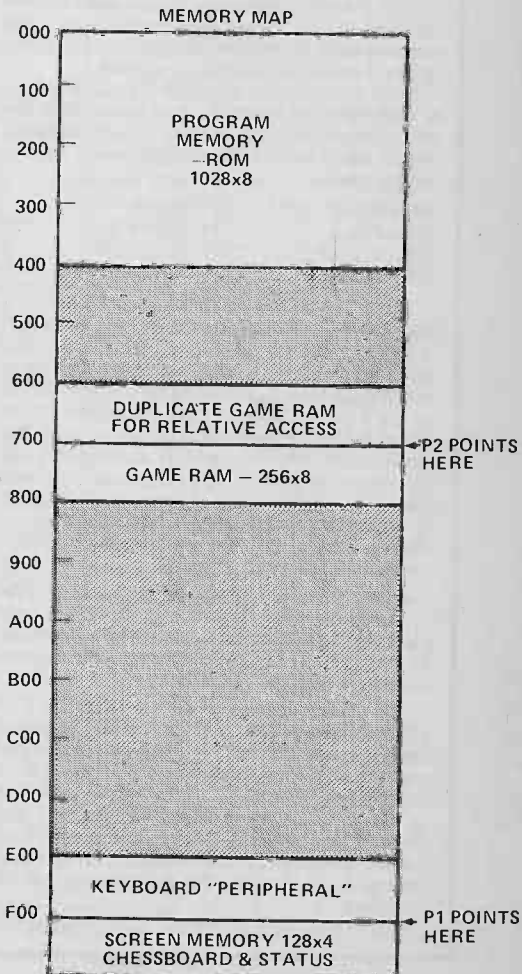

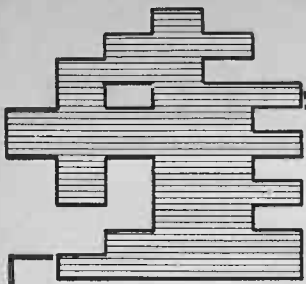

—HOW IT WORKS Software

A detailed description of the software would fill most of this issue of ETI. What follows is an outline of the various sections that go to make up the systems software.

It is not necessary to be familiar with the detailed architecture of the SC/MP MPU on which the project is based to understand what follows. Briefly, however, the SC/MP is an eight bit MPU with a set of 46 instructions covering arithmetic, logical, data transfer and miscellaneous operations.

The SC/MP has four on board 16 bit pointer registers designed PO-P3. SC/MP forms the address of the next program (data) byte it requires by adding (or subtracting) a displacement, which may be zero, from any one of these four pointers. PO is used by the MPU as the program counter while P1-P3 are assigned by the software. A Power on Reset ensures that when power is first applied the MPU starts by examining location one in program memory, the instructions here set these pointers to indicate locations in the memory field which correspond to the chessboard and the game sequence.

The pointer P3 is reserved for subroutines, while P1 is used to indicate both the chessboard and the keyboard, it being set to the boundary between them. A positive value added to this pointer will find the chessboard, a negative value the keyboard. P2 is used to indicate the game sequence.

The first routine used is called CLEARALL which clears all locations in game RAM and board RAM. Clearall is not a subroutine because it will never be needed again. Its purpose is to overwrite the 'garbage' present in RAM when power is first applied.

Next a subroutine is called. The subroutine is referred to as DEBOX. At a location in the program memory is a table of the chesspieces which have been defined according to following codes:

000 = Blank	100 = Rook
001 = Pawn	101 = Queen
010 = Knight	110 = King
011 = Bishop	111 = Not assigned

These are the lower three bits: if bit four is high then the piece is white, if it is low then it is black. DEBOX takes the pieces from the table and places them in the 64 locations making up Board. Thus the pieces will be set up for a game. The piece codes stored in the Board RAM are used in conjunction with the piece form PROM, which stores the bit patterns corresponding to the various chess pieces, an address selector and various items of hardware to generate the game display. The operation of this section will be discussed next month.

DEBOX is a subroutine because it will be called again from another part of the programme. A part of this subroutine is to set the Move Number back to '01' and the arrow to indicate white has the move.

The next subroutine to be called is EXTRACT. This examines location one in game memory and places information about the current move in temporary storage. This information includes the 'from' square, the 'to' square, the piece being moved and the piece being captured if any. The purpose of storing this information is that it should not be lost in the move flash sequence to be described.

The SCAN subroutine is now entered. A

location called KEYWORD is cleared and SCANCOUNT is set to a predetermined value. Also FLASHCOUNT is set to a value which determines the number of flashes which will be made following a Move written. Three flashes are considered enough. The SCANCOUNT determines the duration of the final byte. The serial output is placed high for three seconds to form the Leader Tone and the transmission is made. Each word does not contain eight bits but six, so an asynchronous format is made by setting the first bit in each word to zero and the final bit to one. This corresponds to a start bit and an interval between flashes. These operations are carried out regardless of whether we require a piece to flash or not.

To perform a single scan sequence the keyboard, which is matrixed from four data lines and three address lines is read, all locations at once, and the result examined for non-zero value. This result is stored in the extension register. After a delay of about seven milliseconds the keyboard is read again and the result compared to the first — this is to defeat switchbounce. If the result after the delay period is not the same as the first, or both are zero, there has been no valid keypress and control is passed back to the start of the loop. If there is still a non-zero value then the keyboard is examined one line at a time by changing the address location and adding four to the keyword on zero result, to find the row of switches which contains the valid key. When the row has been found the data is shifted out of the end of the register, adding one to the keyword for each shift, until the result is a clear register. At this point the keyword has a value unique to the individual key. Release is then awaited and debounced as before and return is made to the main programme with a keyword for processing.

When first entered the 'from' and 'to' squares will have been set to zero by the CLEARALL routine. This will mean that when the flash sequence occurs the piece corresponding to square-zero-top left hand square's rook- will be made to flash back and forth to the same square. It will thus seem as if the piece is not flashing.

The MOVE subroutine first examines the STATUS register and hands control back to the keyboard if the Strokecount does not equal zero. This is to prevent spurious moves being made. Then the serial output of the MPU is brought high briefly to record a tone on tape should the tape recorder be operating. The piece moved is examined for 'Kingship' and if it is a king the 'From' location is compared with the 'To' location for a castling situation. The castling routine is entered if necessary, the corresponding Rook being placed on the appropriate side of the King. If the piece fails the 'Kingship' test it is tested for 'Pawnhood'. If it is a pawn it is tested for a diagonal move and if there is no captured piece in a diagonal move situation an EN PASSANT move is presumed and the piece in the square adjacent to the diagonal is removed. If the pawn is moved to the final rank a Queen is substituted. A move is made by accessing the board RAM and writing a blank in the memory location corresponding to the FROM square, derived from the EXTRACT routine, and the corresponding piece

code to the TO square. The arrow which indicates the player is then moved to the opposite location and if this be white's end of the board the Move Counter is incremented. Return is then made to the main programme.

If the Keyword is GOTO the scan routine is called twice to fetch the Request Point. The DEBOX routine sets up the pieces and the MOVE routine is called until the Request Point equals the Move Counter. Control is then handed back to the keyboard.


If the Keyword is RECORD the subroutine RECORD is called. This transmits all the contents of Game RAM in serial form on to cassette tape. First a digit 9 is placed in the Cassette Status location on-screen and the final locations in Game Memory are cleared. These locations are used for FLASHCOUNT and SCANCOUNT, etc. The entire contents of Game memory are added together and complemented and the complement stored in stop bit. When the transmission is complete control is handed back to the keyboard. The Baud Rate is not conventional being approximately 460 bits per second.


If the Keyword is RECALL then a six is placed in the Cassette Status position which forms the bitcounter. When a start bit has been received, and verified after half a bit interval, a word of six bits is clocked in at the serial input, right-justified and stored in the next Game RAM location. After a complete Game reception the whole contents of game memory is added together and tested for zero result. If the total equals zero a tick is placed in the cassette status position. Compensating errors would have to be received for a transmission to pass this test and still be incorrect. Control is retained in the Recall routine after a transmission and if a tone is received at the serial input the next move in memory is made. (The Subroutine calls other subroutines DEBOX and MOVE.) If a leader tone comes along or any key is pressed control reverts to the keyboard.

If the Keyword is not a Function, then it is Move Information which is being written-in. Bit 2 of the Status register, which keeps account of whether a letter or a figure was entered last, is examined and the appropriate Letter or Figure routine is chosen. The word is processed to make its binary value equivalent to the requested rank or file on the Chessboard and stored in the Game Memory in the appropriate From or To locations which are addressed alternately. The actual form in which the word is stored bears little relationship to the letters/figures code, the top left square being 00 (base 16) and the bottom right 3F. Only six bits are necessary to define the squares of a chessboard, these being 26 in number.

As each keystroke is entered the Status register is examined and a Tally, called the Strokecount, is entered in an offboard location on the bottom left of screen memory. The strokecount informs the user of how many keystrokes have been entered. A partial move entry transfers control back to the main routine after the "Extract" sequence so that spurious moves are not flashed. A total entry passes control to before the "Extract" sequence so that the intended move is flashed for verification.

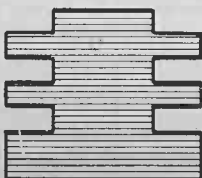The MOVE and GOTO operations will be inhibited until the appropriate entry sequence is complete.



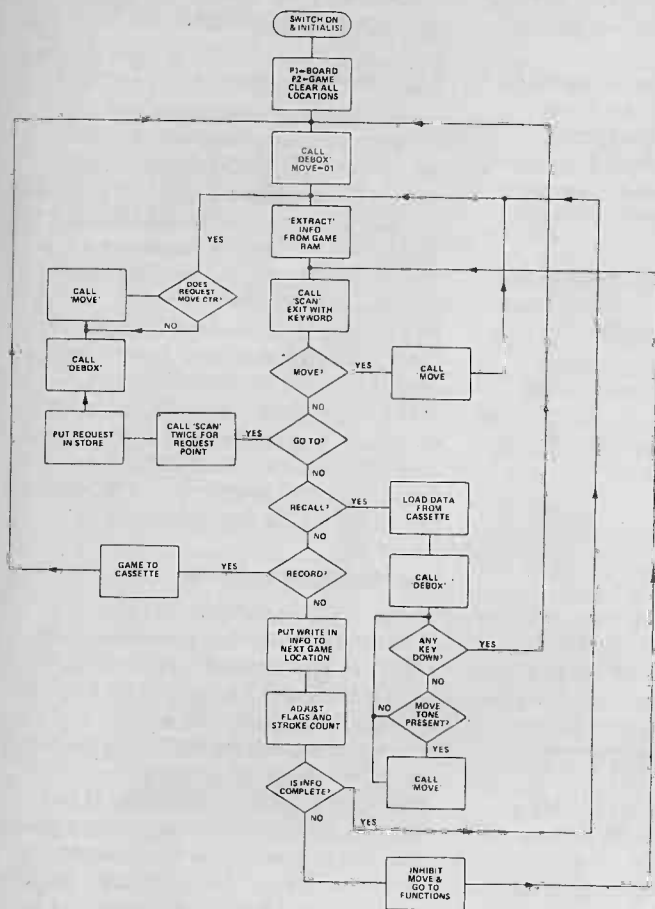

The flow chart for Tolinka's software is shown above.


The SCAN subroutine (reproduced in full below) is one section of Tolinka's software.

SCAN — SUBROUTINE

Video Interval?	06	Copy Status to Accumulator
	D420	And Immediate 20 (Check Sense B)
	9C4E	Back to Keyscan if not zero
Examine Flash	C15D	Get Flashcount from P1 + 5D
	D40F	And OF = Strip off top 4 bits
	9848	Go to keyscan if zero
Examine From/To	B95D	Decrement Flascount
	06	Copy Status to Accumulator
	D401	And 01
	9C16	Go to 'Back' if odd
'Forth'	C400	Load Immediate zero
	01	Clear Extension Register
	C2FC	Load Fromloc from P2
	01	Fromloc to Extension (Zero to Acc.)
	C980	Store zero to Fromloc at P1 (Board) Implied Address.
	C145	Get piece from P1 'Extract'
	01	Piece to Extension
	C2FD	Load Toloc from P2
	01	Toloc to Ext. Piece to Acc.
	C980	Store Piece in Toloc at P1 — Implied Address
	06	Copy Status to Accumulator
	DC01	Or Immediate 01. = Adjust From/To flag
	07	Copy Accumulator to Status
'Back'	901A	Back to Keyscan
	C145	Get piece from P1 'Extract'
	01	Piece to Extension
	C2FC	Load Toloc from P2
	01	Exchange Extension with Accumulator
	C980	Replace piece in Fromloc
	C146	Load captured piece from P1 Extract

Entry Point	01	Capture to Extension
	C2FD	Load Tloc from P2
	01	Exchange Accumulator and Extension
	C980	Restore Capture in Toloc
	06	Copy Status to Accumulator
	D4FE	Set last bit low
	07	Copy Accumulator to Status
	9004	Skip over Flascount Set.
	C407	Load 7 = Flashcount
	C95D	Store Flashcount
	C430	Load 30 = Scancount
	CAFF	Store Scancount at P2
	C400	Load zero
	C94D	Clear Keyword
	C2FF	Load Scancount
	9C03	Go to Scan if not zero
Scan Keyboard	98B0	Otherwise go to 'Video Interval?'
	BAFF	Decrement and load scancount
	C1FF	Read Allkeys
	D40F	Strip off top 4 bits
	E40F	Exclusive or OF (Any down?)
	01	Result to Extension
	8F07	Delay 7 milliseconds. (Debounce)
	C1FF	Read Allkeys
	D40F	Strip off top 4 bits
	E40F	Exclusive or OF
	50	And Extension
Adjust piece	98E5	Back to Scan if zero (No key down)
	06	Copy Status to Accumulator
	D401	Examine From/To bit
Findrow	9CBE	Make move if set (Go to 'Forth')
	C4F4	Load Rowcount
	01	Rowcounter to Extension
	C180	Read Keyboard at implied address
	D40F	Strip off top 4 bits
	E40F	Exclusive of OF
	9C12	If not zero go to Rowfound
	C14D	Load Keyword
	02	Clear carry
	F404	Add 4 to Keyword
	C94D	Restore Keyword
	01	Keyword to Extension (Rowcounter to Acc)
	03	Set Carry
	1F	Rotate Accumulator right with link
	01	Rowcounter back to extension
	C4FF	Load FF (Set all bits high)
	60	Exclusive-or Extension
	98BD	If zero No Row Found. Back to Scan
Rowfound	90E6	Otherwise back to Findrow
	1C	Shift right
	9806	If zero go to Release
	01	Switchboard to Extension
	A94D	Increment Keyword
	01	Switchboard back to Accumulator
	90F7	Jump to Rowfound
Release	C1FF	Real Allkeys
	D40F	Strip off top 4 bits
	E40F	Exclusive-or OF
	01	Result to Extension
	8F07	Delay 7 millisecond (Debounce Release)
	C1FF	Readl allkeys
	D40F	Strip off top 4 bits
	E40F	Exclusive or OF
	50	And Extension — Is any Key down?
	9CEE	Go to Release if key still pressed
	C14D	Fetch Keyword
	D40F	Strip off Top 4 bits
	01	Keyword to Extension
	3F	Exchange Pointer Register with Program Counter
		Exit from Subroutine with keyword in Extension

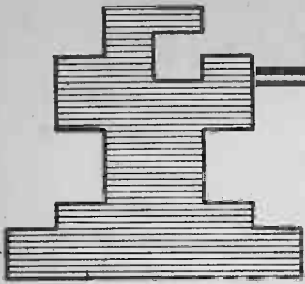(Why is the Subroutine entered in the centre? It is because jumps relative to the Program Counter may only be -128 or +127 locations and it is therefore politic to keep the main decision lines central to the block).



Recording A Game

To record a game the recorder is started in the recording mode, and then Tolinka's RECORD button is pressed. Some tape recorders have a monitor, which means one can hear what is being recorded, and some do not. During the recording time a 9 appears in the 'Cassette Status' position at the top left of the screen. When the 9 disappears recording is complete and the game resets to the opening move. The game in Tolinka's memory is not destroyed by the recording process and it may be recorded as many times as is required. The game may also be modified, other versions tried, and these be recorded as well.

If the move key is pressed whilst the tape is still recording, a tone will be recorded on tape which indicates to Tolinka that it should make a move when the tape is replayed in the RECALL mode. The tone does not contain any information other than to tell Tolinka to make the next move in its memory.

Recalling A Recorded Game

First the game to be recovered must be found on tape, by means of one of the indexing systems previously described. When the leader tone is heard the RECALL key must be pressed. The leader tone has two purposes: to overcome any noise problem leading into game data and to allow the tape recorder's internal Automatic Volume Control to stabilize. The RECALL key must be pressed **and** released during the three second continuous leader, to transfer control to the cassette recorder.

A 6 will then appear in the 'Cassette Status' position and should remain stationary for the rest of the leader, change to a running digit during the data transmission and be replaced by a tick if the game is received correctly. The tick denotes that a 'Checksum' appended at transmission time has been correctly received. A Checksum is a way of

checking data transmissions. Simply all the words in the data are added together and the total complemented. This complement is then transmitted as the last byte. When the data is added together it should total zero and the tick denotes that the contents of game memory has been totalled and does, in fact, equal zero.

If a recall is executed when there is no signal connected the machine will check in an all zero game — this is a useful way of clearing game memory. It is also the reason that zero was chosen as the checksum, so that one could be aware that memory was cleared without further checking.

If there is any symbol in the Cassette Status position it means that the Cassette has control, and move tones on tape will cause moves to be executed as they occur. It is also possible to record speech on the tape between the move tones, and explain to anyone who is willing to sit and watch how cleverly you demolished your opponent, blow by blow. Pressing any key such as MOVE or GOTO etc. causes control to revert to the keyboard and tones on tape will be ignored. The only time control may be passed to the Cassette Recorder is during the leader tone. If the Recorder is left playing and another game comes along the leader will pass control back to the keyboard. Operation of the controls is nearly foolproof and almost everyone becomes expert in ten minutes.

Reliability Of The Recording system

For absolute reliability a high quality studio recorder and data certified cassettes should be specified. In practice any recorder which works properly and a good quality audio tape will be quite all right. If possible the same recorder should be used for recording and replay because differences in motor speeds can introduce errors.

When acquaintances in pubs air their ability to read and learn new words tell you about 'dropouts' thank them admiringly. It costs little to spread happiness and they might buy you a drink. The author has never had any problem with dropouts but this may be the influence of fraternity.



Useful Example

Here is an example of use: the French Defence has been decided upon as this season's reply to e2e4 and a tape will be kept of all French Defences played. The same information will be recorded perhaps on other tapes which are chronological or event files. It only takes a few seconds to record a game and the process may be repeated at will. The French Defence tape begins with analysis from the precedent in literature: standard lines are recorded as an aid to learning the strategy. Later in the tape the actual games are listed followed by their post-mortems, in the light of hindsight. This is a powerful aid to learning.

ETI

Next month the full circuit diagram, together with Hardware How It Works and full constructional information, will be presented.

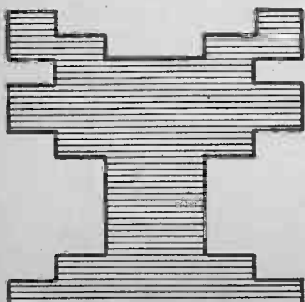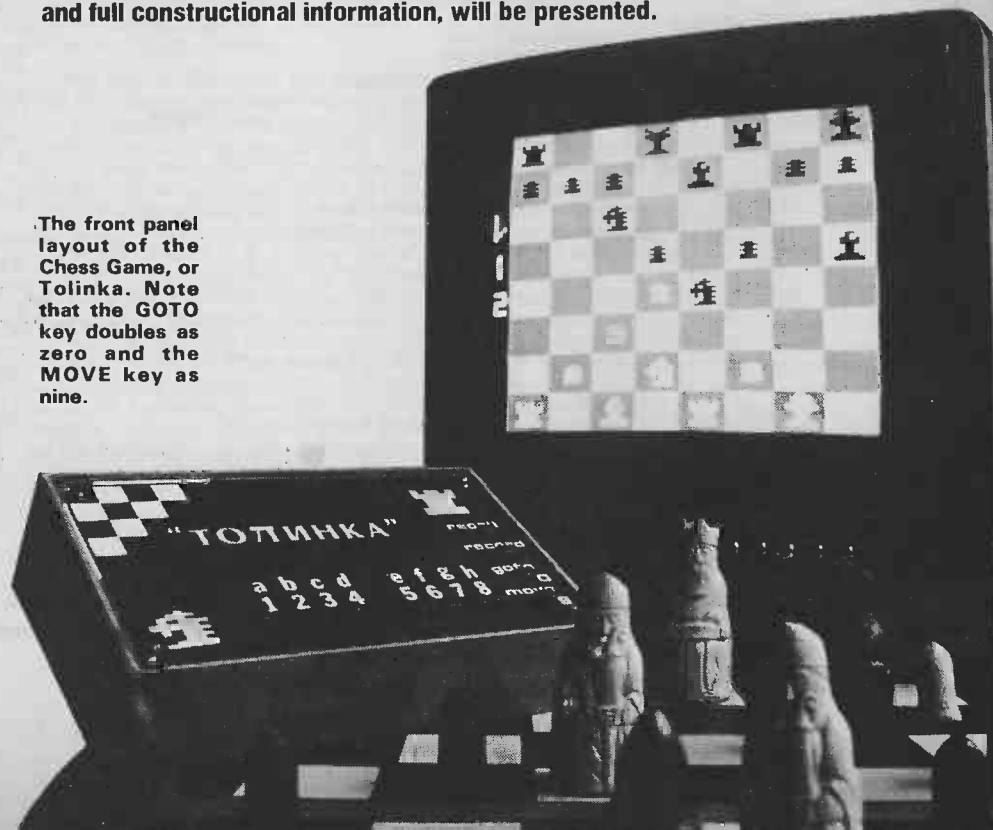The front panel layout of the Chess Game, or Tolinka. Note that the GOTO key doubles as zero and the MOVE key as nine.



data sheet

ICM 7217/7227 SERIES

INTERMIL

The ICM 7217 and ICM 7227 are four digit, presetable up/down counters with an onboard presetable register continuously compared to the counter. The ICM 7217 versions are intended for use in hardwired applications where thumbwheel switches are used for loading data and simple SPDT switches are used for chip control. The ICM 7227 versions are intended for use in processor-based systems where presetting and control functions are performed under processor control.

These circuits provide multiplexed seven segment LED display outputs, with common anode or common cathode configurations available. Digit and segment drivers are provided to directly drive displays of up to 250mm character height at a 25% duty cycle. The frequency of the onboard oscillator (and thus the multiplex frequency) may be controlled with a single capacitor, or the oscillator may be allowed to free run. Leading zeroes are blanked, and the display drivers may be disabled allowing the display to be used for other purposes. The data appearing at the seven segment and BCD outputs is latched; the content of the counter is transferred into the latches under external control by means of the Store pin.

The ICM7217/7227 (common anode) and ICM1721A/7227A (common cathode) versions are decade counters, providing a maximum count of 9999, while the ICM 7217B, 7227B (common anode) and ICM7217C/7227C (common cathode) are intended for timing purposes, providing a maximum count of 5959.

These circuits provide three main outputs; a carry/borrow output which allows for direct cascading of counters, a zero output which indicates when the count is zero, and an equal output which indicates when the count is equal to the value contained in the register. Data is multiplexed into and out of the device by means of a tri-state BCD I/O port, which acts as a high impedance input when loading, and provides a multiplexed BCD output. The carry/borrow, equal, and zero outputs, and the BCD port functioning as an output, will drive one standard TTL load.

In order to permit operation in noisy environments and to prevent multiple triggering with slowly changing inputs, the count input is provided with a Schmitt trigger.

The carry/borrow output is a positive going signal occurring typically 500nS after the positive going edge of the count input advancing the counter from 9999 to 0000 counting up and from 0000 to 9999 counting down. This output allows direct cascading of counters.

The equal output assumes a negative level when the contents of the counter and register are equal (i.e., for the duration of one period of the count input until the count is changed by a positive going edge on the count input).

The zero output assumes a negative level when the content of the counter is 0000.

The digit and segment drivers provide a decoded seven segment display system, capable of directly driving common anode LED displays at typical peak currents of 40mA per seg. This corresponds to average current of 10mA/seg with the 25% multiplex duty cycle. For the common cathode versions peak segment currents are 12.5mA, corresponding to average segment currents of 3.1mA. The display control pin controls the display output using three level logic. The pin is self-biased to a voltage approximately half way between rails which corresponds to normal operation. When this pin is connected to V+, the segments are inhibited, thus disabling the display and reducing power. When this pin is connected to V- the leading zero blanking feature is inhibited. For normal operation (display on with leading zero blanking) the pin may be left open. The display may be controlled with a 3 position SPDT switch as in the test circuits.

The BCD input/output port provides a means of transferring data into and out of the device in BCD format. The ICI 7217 versions self-multiplex data into the counter or register via thumbwheel switches in response to inputs at the load counter or load register pins, while in the ICI 7227 versions input/output control and timing must be provided externally. When functioning as outputs, the BCD I/O pins will also drive one standard TTL load.

The onboard multiplex scan oscillator has a nominal free-running frequency of 10kHz. This may be reduced by the addition of a single capacitor between the Scan pin and the positive supply, or the oscillator may be directly overdriven to about 20kHz.

FEATURES

Four decade, presetable up-down counter with parallel zero detect.

Setable register with contents continuously compared to counter.

Directly drives multiplexed seven segment common anode or common cathode LED displays.

On-board multiplex scan oscillator.


Schmitt trigger on count input.

TTL compatible BCD I/O port, carry/borrow, equal and zero outputs.

Display blank control for low power operation; quiescent power dissipation less than 5mW.


Display off control to allow use of display for other purposes.

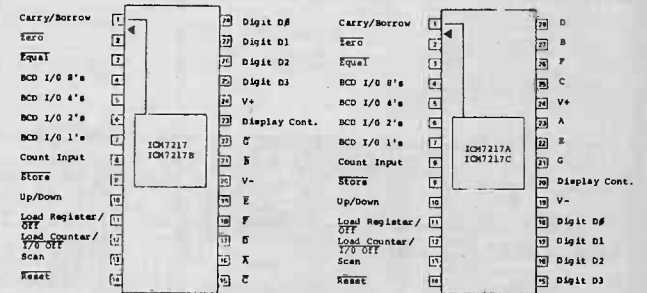7217 numbers refer to hardwired control versions of the device, while 7227 numbers refer to the processor control versions.



COMMON ANODE

COMMON CATHODE

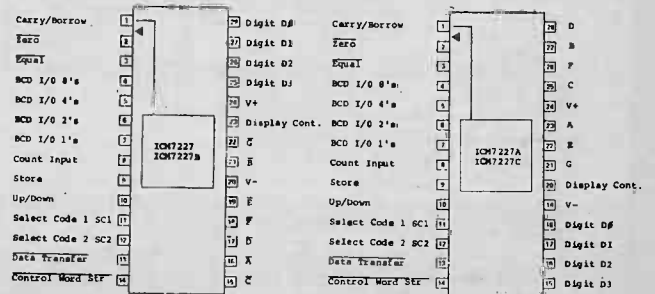

The Store pin of the 7217 will allow the output latches to be updated only if it is held low. The device will count up if the Up/Down pin is high and down if low. The Reset pin will allow normal operation when high, resetting the device when taken low. The Load Counter pin has three states. When high the counter is loaded with BCD data, when floating normal operation is selected and when the pin is low the BCD port is forced to a high impedance. The Load Register pin also has three states. High loads the register with BCD data, floating allows normal operation while low disables the display drivers. The three state Display Control disables the segment drivers when high, allows normal operation when floating and inhibits the leading zero blanking when low.


The 7227 pin configurations are somewhat different. The Data Transfer pin will allow normal operation when high, and when pulsed low will cause a transfer of data as directed by the select code set up on pins Select Code Bits 1 and 2. If these are set to 00 there will be no data transfer, 01 will latch the output data, 10 will preset the counter while 11 will preset the register. The Control Word Strobe will allow normal operation when high and when pulsed low will cause the control word set up on the Store and Up/Down pins to be written to the control latches. The Store pin will update the latches if high during CWS's active period, not allowing updates if low. The counter will count up if Up/Down is high, down if low. The display control is a three state input, blanking if low and allowing normal operation if left floating, blanking if low and allowing normal operation of left floating.

The ICM 7217/7227 series provides in one easy to interface circuit (1) a high speed four decade up/down counter with carry out and parallel zero detect (2) setable register and comparator; (3) output latches for (4) a multiplexed LED display decoder/driver system and (5) multiplexed (or directly addressed in the ICM7227) BCD outputs. These five subsystems can be used together or separately to provide a large number of circuit configurations.

A few possible applications are shown below.


TIMER DISPLAY COUNTER /

ICM7217	Common Anode	Decade/9999
ICM7217A	Common Cathode	Decade/9999
ICM7217B	Common Anode	Timer/5959
ICM7217C	Common Cathode	Timer/5959
ICM7227	Common Anode	Decade/9999
ICM7227A	Common Cathode	Decade/9999
ICM7227B	Common Anode	Timer/5959
ICM7227C	Common Cathode	Timer/5959

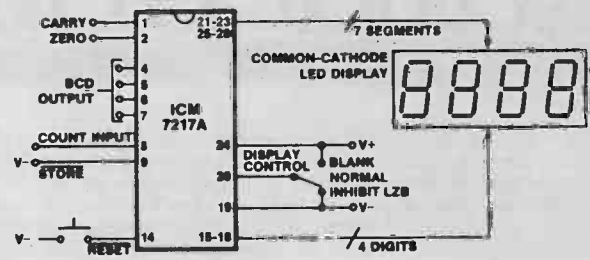

UNIT COUNTER WITH BCD OUTPUT

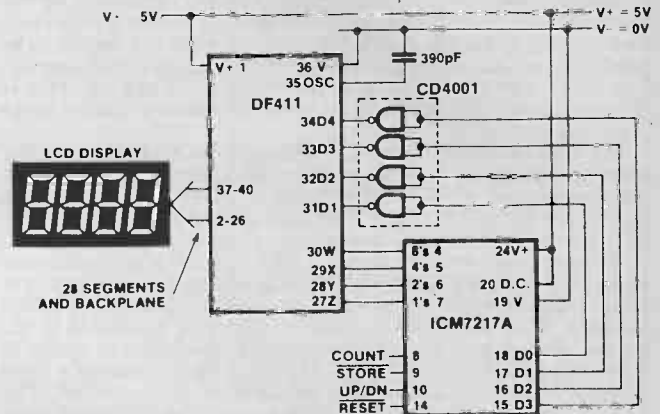The simplest application of the ICM217 is as a four digit unit counter. All that is required is an ICM7217, a power supply and a four digit display. Add a momentary switch for reset and an SPDT centre-off switch to blank the display or view leading zeroes. One more SPDT gives up/down.



LCD DISPLAY INTERFACE

The low-power operation of the ICM7217 makes an LCD interface desirable. The Siliconix DF411 four digit BCD to LCD display driver easily interfaces to the ICM7217A with one CD4000-series package to provide a total system power consumption of less than 5mW. The common-cathode devices should be used since in these versions the digit drivers are CMOS, while in the common-anode devices the digit drivers are NPN devices and will not provide full logic swing.

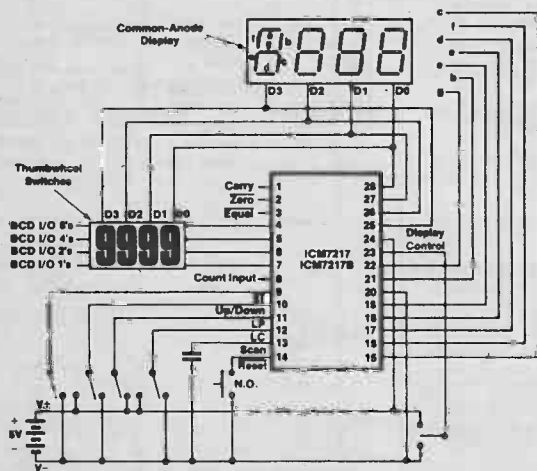


Fig. 1. The 7217 (common anode) version. The display and power connections are the same for the 7217B, 7227 and 7227B.


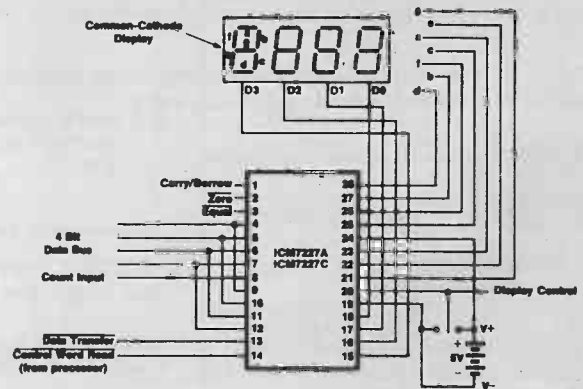
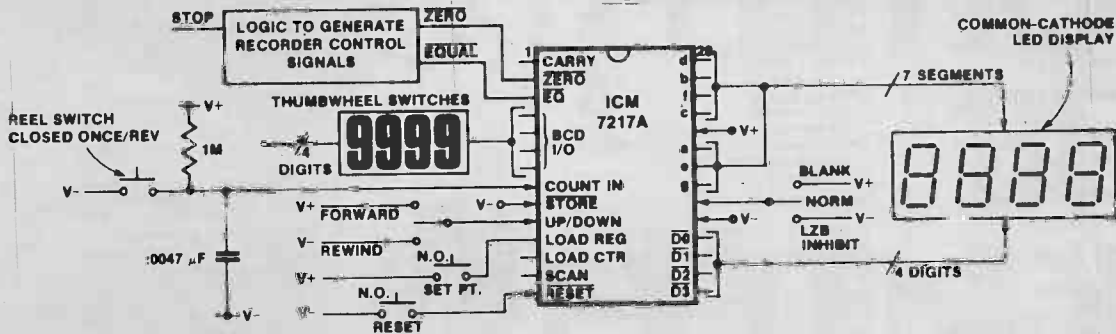


Fig. 2. The 7227A (common cathode) version. The display and power connections are the same for the 7227C, 7217A and 7217C.

PRECISION FREQUENCY COUNTER/TACHOMETER

This circuit is a simple implementation of a four digit frequency counter, using an ICM7207A to provide the one second gating window and the store and reset signals. In this configuration, the display reads hertz directly. With Pin 11 of the ICM7207A connected to V+, the gating time will be 0.1 second which will give tens of hertz in the least significant digit. For shorter gating times an ICM7207 may be used (with a 6.5536 MHz crystal), giving a 0.01 second gating with Pin 11 connected to V+ and a 0.1 second gating with Pin 11 open.

To implement a four digit tachometer, the ICM7207A with a one second gating should be used. In order to get the display to read directly in RPM, the rotational frequency of the object to be measured must be multiplied by 60 (or 600 using a 0.1 second gating for faster update). This can be done electronically using a phase-locked loop or mechanically by using a disc rotating with the object with the appropriate number of holes drilled around its edge to interrupt the light from an LED to a photo-detector.

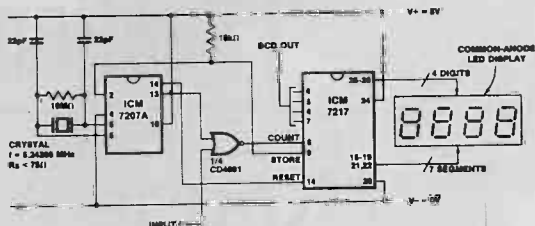

TAPE RECORDER POSITION INDICATOR/CONTROLLER
This circuit shows an application which uses the up/down counting feature of the ICM7217 to keep track of tape position on a tape recorder. This circuit is representative of the many applications of up/down counting in monitoring dimensional position.

In the tape recorder application, the preset register, equal and zero outputs can be used to control the recorder. To make the recorder stop at a particular point on the tape, the register can be set with the stop point and the equal output used to stop the recorder (either on fast forward, play or rewind).


ok WIRE WRAPPING CENTRE ok

HOBBY WRAP
Model BW 630
Battery Wire-Wrapping Tool
Complete with Bit and Sleeve.




WIRE-WRAPPING TOOL
For .025" (0.63mm) sq. post "MODIFIED" wrap, positive indexing, anti-overwrapping device.

A	For AWG 30	BW-630
B	For AWG 26-28	BW-2628
C	Bit for AWG 30	BT-30
D	Bit for AWG 26-28	BT-2628

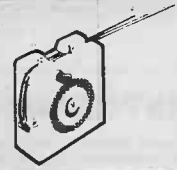

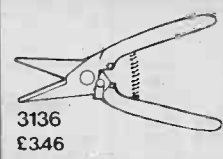
3 IN 1 WIRE DISPENSER
New wire dispenser cuts and strips three different colours of wire. Quick and easy to use pocket size. Wire Size: 30 AWG. 50 ft. Red, Blue, White Kynar insulated. £4.07




OK PLIERS AND CUTTERS
UNIVERSAL CUTTER
Cuts everything. Leather, wire, plastic, tin-plate, cardboard, Stainless steel blades. Just one of the range of high quality pliers, cutters, tweezers and screwdrivers.

DIP/IC EXTRACTOR TOOL £119
The EX-1 Extractor is ideally suited for hobby enthusiast or lab engineer. Featuring one piece spring steel construction, it will extract all LSI, MSI and SSI devices of from 8 to 24 pins. Extractor Tool EX-1.

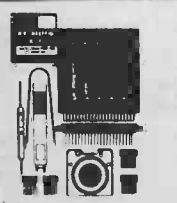
DIP/IC INSERTION TOOL WITH PIN STRAIGHTENER £2.79
INS-1416



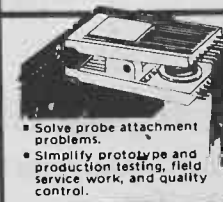WIRE-WRAPPING KIT
Contains: Hobby Wrap Tool WSU-30 M, Wire Dispenser WD-30-B, (2) 14 DIP's, (2) 16 DIP's, Hobby Board H-PCB-1, DIP/IC Insertion Tool INS-1416 and DIP/IC Extractor Tool EX-1.
Wire-Wrapping Kit WK-4B (Blue) £19.22



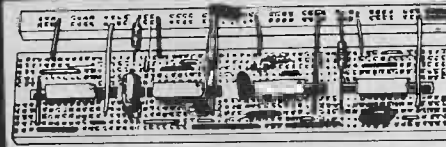IC TEST CLIPS £2.97
FOR DUAL-IN-LINE PACKAGES
Provide full access to integrated circuit DIP leads.
Remove DIP's damage free.
Available in sizes to accommodate all DIP's; TC-14 fits 14-pin DIP's etc.



FROM 80P TERMINAL AND DISTRIBUTION STRIPS
Bread boarding building blocks with universal matrices of solderless plug-in tiepoints.
Facilitate quick, solderless circuit build-up and check-out on universal .1" x .1" matrix.

- Are offered in ten configurations.
- Accept all components with leads up to .032" diameter.
- Require no special patch cards.
- Includes integral non-shorting instant mounting backing.



HOBBY WRAP TOOL
Wire-wrapping, stripping, unwrapping tool for AWG 30 on .025 (0.63mm) Square Post.
A £4.74 B £5.07

Regular Wrap	A	WSU-30
Modified Wrap	B	WSU-30M



DIP SOCKET
Dual-in-line package, 3 level wire-wrapping, phosphor bronze contact, (inlay finish pins .025 (0.63mm) sq., .100 (2.54mm) centre spacing.

14 Pin Dip Socket	14 Dip
16 Pin Dip Socket	16 Dip

RIBBON CABLE ASSEMBLY £2.92
With 14 Pin Dip Plug - 2" Long DE 14-2
With 14 Pin Dip Plug - 4" Long DE 14-4
With 14 Pin Dip Plug - 6" Long DE 14-6
With 16 Pin Dip Plug - 2" Long DE 16-2
With 16 Pin Dip Plug - 4" Long DE 16-4
With 16 Pin Dip Plug - 6" Long DE 16-6

See us at
BREAD BOARD '78
21st-25th November.
Seymour Hall, London
Stand Nos. A5-A6

OK Machine & Tool U.K. Limited
48a The Avenue, Southampton SO12 5Y
Telephone Southampton (0703) 38966 7 Telex 477222 Cablegram OKMAC

DISTRIBUTORS WANTED ***

Extend Buzby's influence with our

TELEPHONE BELL EXTENDER



MANY TIMES WHILE you're working in the garden the phone may ring and by the time it is heard, if it is at all, it is often too late to reach the phone. While the GPO will install a remote bell for you it has to be rented and for people who are hard of hearing it may not be loud enough.

This bell extender will allow you to add, without touching the phone, an external bell, buzzer or speaker anywhere it is desired. When using a horn loaded speaker the sound level is high enough to be heard over high ambient noise making it ideal for the industrial environment.

Adjustment

There are two controls to be set, these being sensitivity and volume. The volume can be set first by rotating RV1 until the tone starts then adjusting RV2 to give the desired volume. To adjust the sensitivity first tape the sensor coil to the underside of the phone and then adjust RV1 until the sound stops. Note however that it should be rotated slowly as C3 gives a delay on switch off. Check that picking up and replacing the phone does not operate

the alarm then get someone to ring you to check that the phone tone does. It may be necessary to experiment with the position of the pickup coil to get the best results.

Construction

While any construction method could be used we recommend that the PCB board be used and the overlay in Fig. 2 be followed. The pickup coil was made out of 0.125 mm enamelled wire, although the gauge is not important, with about 200 turns wound around a former about 50 mm diameter. The former can then be removed, the wires terminated in some thin plastic insulated wires (twin "bell" wire is ideal) and then the complete coil wrapped with plastic insulation tape.

We built our unit into a small plastic box using an external speaker. The unit can be mounted anywhere suitable, taking care however with the 240 V wiring. The speaker used will depend on the volume required with a larger speaker producing more sound. If a horn speaker is used a very high sound level can be produced.

If it is required only to operate a buzzer the second IC can be altered to be an on-off device by deleting C5, R5, R6, D2 and RV2 and fitting a link in place of C5.

BUYLINES

All the components used in this programme are freely available from component stores and mail order firms.

As the text points out the pick up coil is by no means critical, and most enamelled wire will do, the number of turns being adjusted to achieve a satisfactory performance.

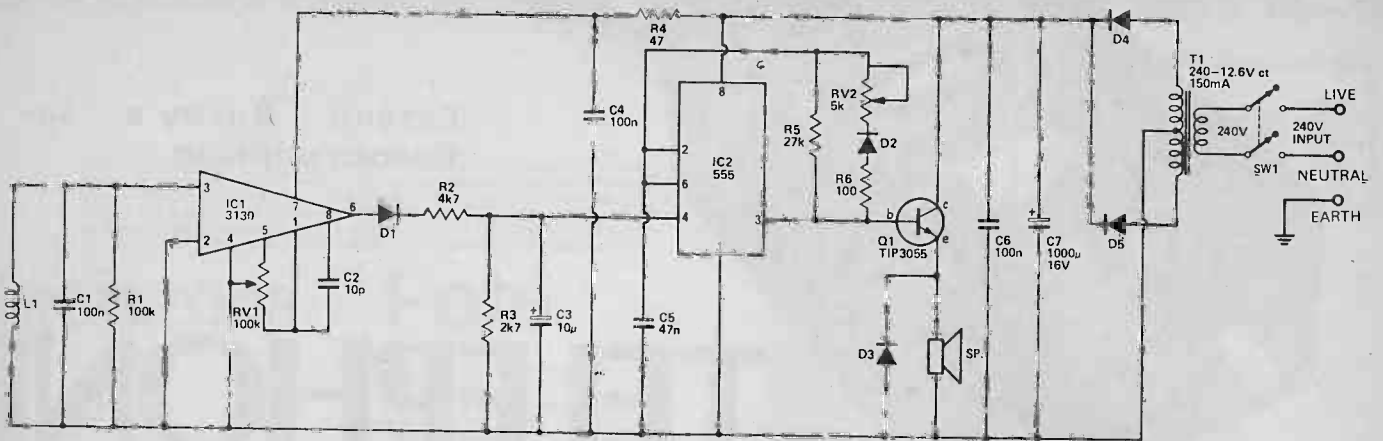


Fig. 1. Full circuit diagram of the tele bell extender.

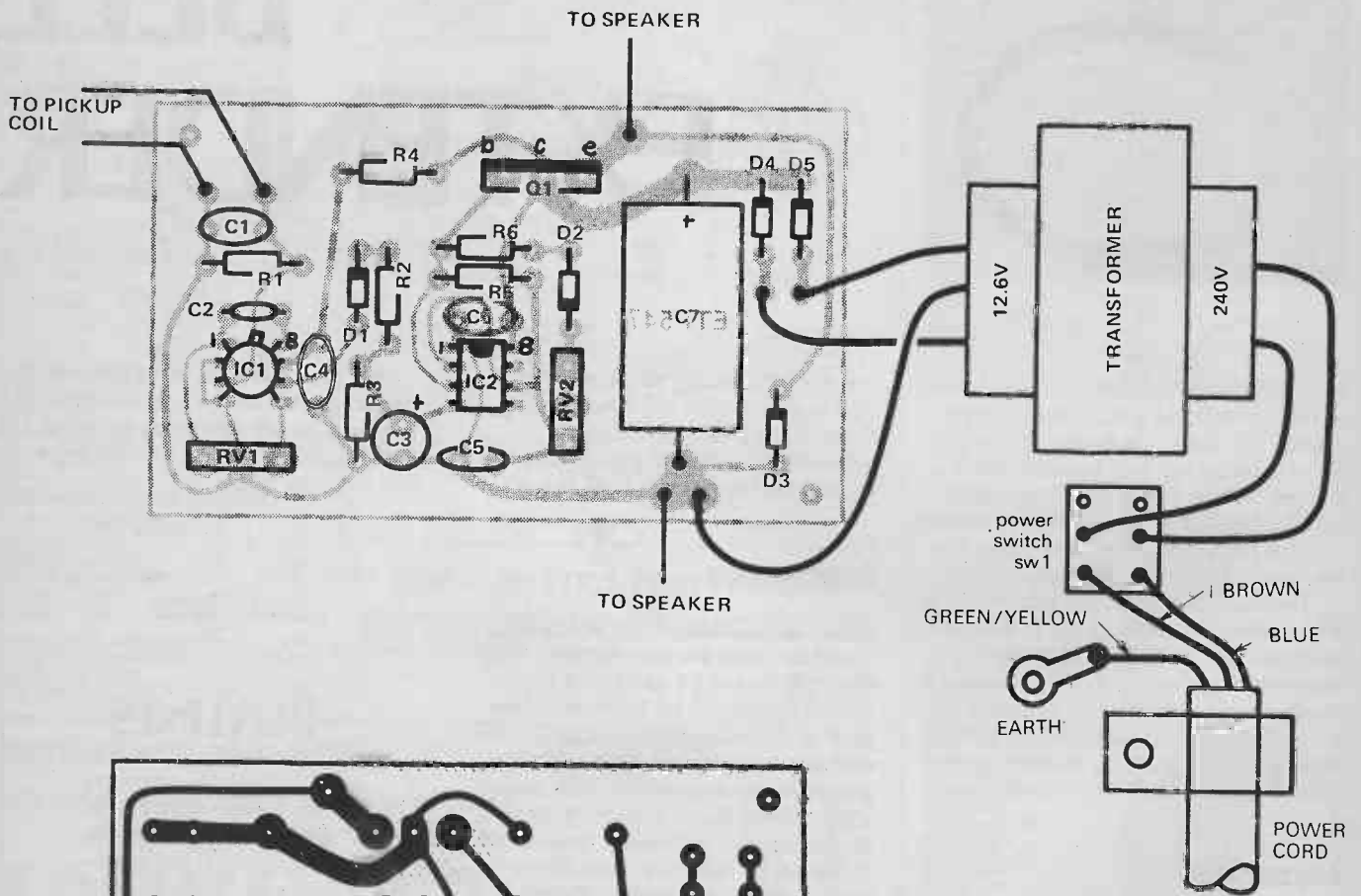


Fig. 2. (above) overlay for the extender's PCB

Fig. 3 (left) full size foil pattern for the telephone bell extender printed circuit board.

Airamco Ltd.

MICRO COMPUTER PRODUCTS

Distributors for JADE COMPUTER PRODUCTS
All products brand new with full industrial specification

	ASSEMBLED	BARE BOARD
S100 COMPUTER CARDS KIT		
Jade 8080A CPU BOARD	£122.50	£22.50
Jade Z80 CPU BOARD 2MHz		
..... £99.95	£138.75	£26.25
Jade Z80 CPU BOARD 4MHz		
..... £112.50	£149.95	£26.25
Jade Serial / Parallel I/O BOARD		
..... £93.70	£134.29	£22.50
Jade 2708/2716 EPROM BOARD		
(16x2708 or 2716) WITH 8 2708s	£82.46	£22.50
..... £97.46	£134.96	£22.50
Jade REAL TIME CLOCK BOARD		
..... £93.71	£134.96	£22.50
Problem Solvers 16K STATIC RAM 450nS	£270.00	---
16K STATIC RAM 250nS	£296.00	---
Jade 8K static RAM BOARD 450nS	£112.50	---
..... £94.50	£119.96	£19.95
Jade 8K static RAM BOARD 350nS	£104.95	£19.95
..... £127.50	£142.50	---
Jade 8K static RAM BOARD 250nS	£127.50	---
S.D. Sales "EXPANDORAM" Dynamic Memory 375nS access time 8K	£113.25	---
Memory 375nS access time 16K	£194.25	---
..... £318.75	---	---
Memory 375nS access time 32K	£746.25	---
..... £11.75	£165.00	---
VERSAFLOPPY DISK CONTROLLER (up to 4 drives 5 1/4" or 8")	£385.00	---
..... £11.75	£225.00	---
SHUGART 8" Drive	---	---
PERTEC 5 1/4" Drive	---	---

All prices in bold are constantly falling at AIRAMCO.
Phone for last minute up to date prices

Components		
2708 1024x8 EPROM	£6.99	4116 16Kx1 DRAM
2716 2048x8 EPROM (intel)	£29.90	8 for
2516 2048 x 8 EPROM	£29.90
(equivalent of above) T.I.		6821P PIA
1702 256x8 EPROM	£4.85
2104 4096x1 DRAM	£3.50	AY 51013 UART
8 for	£26.00	AY51014 UART(5V)
2107B-4 4096x1 DRAM	£3.50	AY53600 ENCODER
8 for	£26.00	8080A CPU
Note New Low Prices 16K Memory		21L02-1 450nS
		8 for
	
		21L02 250nS
		8 for
	
		2112-1 256x4 (450)
		4044 4Kx1 (450)
		4045 1Kx4 (450)

All Prices EXCLUDE VAT @ 8%.
Trade discounts on Quantity
Please add £1.00 P&P for S100 items then add VAT @ 8%.
24-hr. Ansaphone order service with ACCESS or BARCLAYCARD.
MAIL ORDER ONLY



For components please add 40p P&P, then add VAT @ 8%.
AIRAMCO LTD.
30 WITCHES LINN
ARDROSSAN
AYRSHIRE
KA22 8BR
TEL. 0294 65530

Semiconductor prices are always changing and the trend is generally downwards. So ring for latest up-to-date details.

... news

drool here



Now before we go any further this lot costs about £2,000, and is definitely pie in the sky for most of us — but its lovely all the same. For once we're gonna let someone describe their own product — take it away HP.

Called the Hewlett-Packard Model 1742A Delta Time Oscilloscope, the instrument is also available with an optional 3-1/2 digit autoranging digital multimeter which displays time in seconds, milliseconds, or microseconds. This DMM option (034 or 035) can be ordered installed initially, or added later in the field because the delta time capability is built-in the basic oscilloscope. The DMM can also be used to

measure ac and dc voltage and current as well as resistance.

In the delta time mode, the oscilloscope measures time between two events on either channel A or B, or between an event on one channel and an event on the other. Measurements of high-speed digital timing, transition times, propagation delay, and clock phasing are rapid and with greater accuracy than with traditional differential delay time base oscilloscopes.

Stable internal triggering to 100 MHz requires 1 cm vertical deflection (only 0.3 cm to 25 MHz).

Excuse us while our workbench gently weeps.

close encounters calls

There are probably only a handful of ETI readers who aren't 'Star Wars' fans and most of the staff here have seen it more than once. At the beginning of August one of our people was in North America and saw the first follow-up, 'Battlestar Galactica', made by John Dykstra, the principle effects man on 'Star Wars'.

Battlestar Galactica itself is the equivalent of a battleship and the only survivor of twelve such giant fighting ships from a sneak attack launched by the Cylons. The mission of Galactica is to gather together the human survivors of the Galaxy and to find the lost planet Earth which was colonised in the long distant past by other humans.

Like 'Star Wars', the

film is full of parables, in this case the Old Testament escape of Moses from Egypt is only thinly disguised. Throughout the film you can't help noticing the Star Wars parallels, even down to the noise made by the laser guns.

Galactica is a film you'll have to see if you get the chance — it lacks the novelty of 'Star Wars', there's no R2D2, Darth Vader or light sabres but the effects are excellent none the less.

Universal, who handle the film, have not yet decided if the film will be distributed here. It is a major, and very expensive (at \$14,000,000), pilot for a TV series. If it is shown it will not be before next spring.

PROJECT :Bell Extender

HOW IT WORKS

Inside the telephone there is a solenoid which operates a striker which hits a pair of bells to give the ring tone. When it operates there is a high magnetic field generated and we detect this field to give the indication that the bell is ringing. To do this we use a coil wire under the telephone and use an IC to detect the presence of a signal. IC1 has its offset voltage adjusted by RV1 such that a slight positive voltage is needed to make the output go high. It is used in the open loop mode as a comparator only. The capacitor C1 is used to remove the unwanted higher frequency signals.

The oscillator used to operate the speaker is simply a 555 timer with a TIP3055 to buffer the output. The frequency is determined by C5 and the volume by RV2. Changing the volume does change the frequency slightly. Oscillation can however only occur if the voltage at pin 4 is greater than 0.6V. If the output of IC1 is low, R3 ensures that pin 4 is less than this voltage. However when the bell rings the output of IC1 oscillates high and low in time with the ring tone of the bell. This lifts pin 4 high, allowing IC2 to oscillate and C3 holds pin 4 for a short time to prevent the oscillator turning on and off at the ring tone frequency.

The power supply is a simple full wave rectifier with no regulation with IC1 being decoupled further by R4 and C4. Batteries could be used but the drain is reasonably high.

PARTS LIST

RESISTORS all 1/2W 5%

R1	100k
R2	4k7
R3	2k7
R4	47R
R5	27k
R6	100R

POTENTIOMETERS

RV1	100k trim
RV2	5k trim

CAPACITORS

C1, C4	100n polyester
C2	10p ceramic
C3	10u 16V electrolytic
C5	47n polyester
C7	1000u 16V electrolytic

SEMICONDUCTORS

IC1	CA3130
IC2	NE555
Q1	TIP 3055
D1-D5	1N4001

MISCELLANEOUS

PCB as pattern
Transformer 240V — 12V 6V ct
Mains switch, 3 core flex
Box, speaker, pickup coil

SPECIAL OFFER TO E.T.I. READERS

ALARM CHRONOGRAPH WITH DUAL TIME ZONE FACILITY


In a superb stainless steel case with mineral glass face. THIS MUST BE THE ONE YOU HAVE BEEN WAITING FOR!

If you could write the specification for your own ideal watch you would probably want everything this one has. As for styling, without a close inspection nobody is going to be able to tell the difference between this watch and that world famous James Bond classic selling for £145. However, this one goes one better and has 1/100 second timing of net, lap and 1st and 2nd place times, with dual time facility.

- Constant LCD display of hours and minutes plus optional seconds or date display plus day of the week and am/pm indication.
- Perpetual calendar; day, date, month and year.
- 24 hour alarm with on/off indication.
- 1/100 second chronograph measuring net, lap and first & second place times.
- Dual time zone facility. Night light.
- Fully adjustable stainless steel bracelet.
- Stainless steel case. Mineral glass face.

This watch should not be confused with cheaper models with chrome plated cases and plastic lens. Manufactured by National Electronics, it runs a close second to Casio, Citizen and Seiko for quality and reliability, with undeniable value for money. It is fully guaranteed for 12 months, with first-class service back-up.

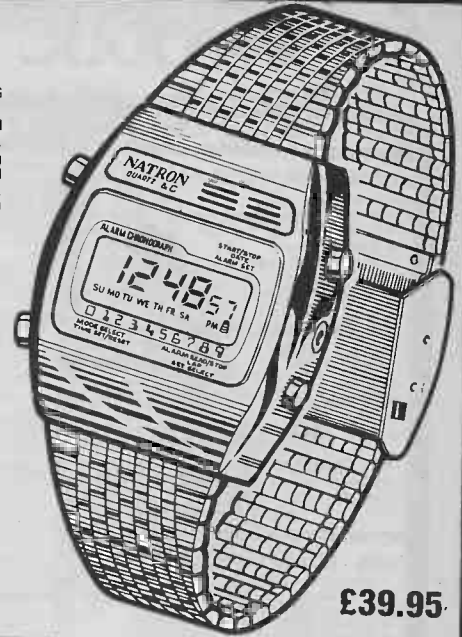The first very limited quota will be available in mid-September with another small consignment in October, so order now to avoid disappointment. We will quote you a delivery date by return of post.



£39.95

NATIONAL low cost watches (or similar)

PH-ALARM WATCH. Similar to above but without stopwatch and dual time. Chrome plated case. Plastic lens.

£29.95

PH-CHRONOGRAPH

Hrs, mins, secs. Month, date, day
1/100 sec. Net.
lap, 1st & 2nd
place. Light.

£18.50

PH-ANALOGUE

Step, motor,
sweep secs.

Day, Date £24.95



CASIO QUALITY AND VALUE SPORTS WATCHES

F-100

Left, 9.45 mm
(£29.95)

£24.95


52QS-14B

Right 8 mm
(£44.95)

£34.95



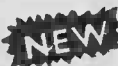Up to 25 functions. Net, lap and first and second place times to 1/100th second. F-100. Resin case and strap.
52QS-14B. S/S encased version and bracelet.
Water resistant to 2 atmospheres (66ft).



ST-24 CARD TIME

Stopwatch from 1/10 second to 10 hour, then seconds to 24 hours. Or 24 hr. clock. Net, lap, 1st & 2nd place. Two alarm/timers. Calculator. Full memory.
K% 1/2x3 1/2x2 1/2 ins.

£24.95) £19.95

CQ-81 CALCULATING ALARM CLOCK PLUS 2 ALARM/TIMERS

Two AA batteries last for 10,000 hrs (1 year) LCD 6 digit clock, large angled display. 24 alarm, also two 24 hr Alarm/Timers with countdown (one self-clearing, one repeats). Full memory, constants %, √ 1% x 2% x 5

RRP £22.95

£17.95



THE INCREDIBLE FX-8000

43 Scientific funct. 1/100th sec Stopwatch. Five Alarm/Timers, sequential (self-clearing) or repeat. 2 level parenthesis. Memory, Deg, Rad, Gra, Standard deviations. Fractions. Sexagesimal. Rect/Polar convert. LCD. 1300 hr batteries. 1/4 x 2 3/4 x 5 3/4" 2.7 oz

RRP £35.95

£29.95



AQ-1000. CALCULATING ALARM CLOCK PLUS 3-WAY STOPWATCH

Hours, minutes, seconds, am/pm, 24-hour Alarm with sign. Stopwatch: Net times, Lap times, 1st & 2nd Place times from 1/10sec to 10 hrs, with ST & LAP signs. Calculator: 4 key memory, %, √, 1 year batteries. ± 20 seconds/month. 1/4 x 2 3/4 x 4 3/4" (RRP £26.95) £21.95

SAVE £££ WITH THE MONITEL

Telephone call charge, calculator, and clock. UK model £28.95. International £38.50

Send 25p for our illustrated catalogue. Prices include VAT and P&P. Send your cheque, PO or phone your credit card no to —

FREE! SPECIAL OFFER THIS MONTH

At least two spare batteries worth up to £1.30 with every CASIO product advertised, on request with order.

WATCH BATTERIES 65p each D.I.Y. KIT 35p (with battery order).

Dept. ETI, 19/21 Fitzroy Street, Cambridge. Tel. 0223 312866

TEMPUS

GARRARD MRM 101

MUSIC RECOVERY MODULE

GORDON KING examines the new Garrard Music Recovery Module for ETI. This machine is designed to remove the transient noise created by damaged grooves on an LP. How effective is it and how does it work? Read on

THIS INTERESTING BRITISH innovation is a small, self-contained, mains-powered unit designed for connecting between the left and right outputs of a magnetic pickup and the left and right auxiliary or tuner inputs of a hi-fi amplifier. The unit processes the signals passing through it so that the disconcerting clicks produced by badly scratched records are virtually eliminated. In other words, the unit can be regarded as a record 'scratch remover'.

Basic principle of operation is fairly straightforward. The clicks are processed to form large amplitude pulses which are then applied to an electro-optical fader which, at the precise moment of the clicks, severely attenuates both audio channels, thereby exchanging the clicks for very short periods of 'silence.' Record clicks have a fast rise-time and the effective slewing-rate is determined by the primary parameters of the cartridge, which are the effective tip mass, compliance and, to some extent, the mechanical resistance or damping of the cartridge.

Provided that the attenuation is large enough, that it switches on and switches off swiftly enough just to straddle the periods of the clicks and that it is accurately synchronised to the occurrence of the clicks in the audio channels, then the effect is singularly dramatic — the loss of information during the time of the attenuation appears to be of little subjective moment.

The effect is akin to tape dropouts, but it appears to be less affected by the accompanying S/N ratio impairment of these. Experimental work has suggested that provided the period of program loss or attenuation does not exceed about 10 ms, then the result is not unduly obtrusive subjectively. The attenuation period of the MRM-101 is a trifle above 2 ms hence the 'gaps' come and go unnoticed.

Built to A Standard

The unit is built into a shallow enclosure and the front forms a brushed aluminium fascia carrying three controls and three light emitting diodes (LEDs). One control is for power on/off, another for suppressor on/off and the third provides a continuous threshold adjustment for the suppressor action. In use, this is set for the best subjective improvement in reproduction.

If the control is too far advanced music peaks as well as scratch clicks may be processed; if insufficiently advanced only very large amplitude scratch clicks will be processed. It is easy to determine the most desirable setting because one of the LEDs flashes each time a scratch is detected. Thus, when playing a record of given mutilation the control is slowly turned up until the suppressor activity LED flashes on all the significant scratches yet remains unaffected by high-frequency

music peaks. Another LED merely glows when the mains is switched on, while the third LED signifies that the suppressor mode switch is on.

The rear is equipped with 'phono' type and DIN input and output sockets, making it a simple matter to connect the unit to virtually any contemporary hi-fi amplifier. There is sufficient output to drive a power amplifier direct, but to control the volume this would need its own volume control. Not all power amplifiers are equipped with a volume control, so it is a pity that Garrard did not see fit to include an output gain control. When driving from the unit direct to our power amplifier high quality reproduction was achieved.

Operations

Operation of the unit can be appreciated from the diagram in Fig. 1. This is partly schematic and partly in *simplified* block format. With the suppressor off, the signal is directed from the output of the front-end, which is a partly equalised preamplifier composed of Q1-Q4 to the output buffer amplifier (RC4136DB), which provides the remainder of the RIAA equalisation.

Equalisation of the front-end is provided by the usual frequency-selective feedback arrangement which gives the 'bass boost' requirements of 3180 and 318 μ S. The 75 μ S. de-emphasis equalisation is provided by the 51k resistor and 1n5 capacitor in the feedback path of the output buffer. The circuit as a whole is also engineered to cater for the more recent IEC-98/4 specification corresponding to a 20 Hz additional turnover, equivalent to a time-constant of 7950 μ S.

A Gain Gained

Front-end gain is about 34dB at middle frequencies, and an extra 1.6 dB is provided by the output buffer. The circuit has some desirable aspects, including the differential input stage Q1, 2 and the 'Darlington' Q3, 4 stage which provides a high input impedance and low output impedance from Q4 emitter. Operating in the 'suppressor off' mode extremely good quality pickup signals are obtained.

The split equalisation, where the de-emphasis is provided at the output, helps to provide a high S/N ratio, and the circuit overall demonstrates an input overload threshold of about 37 dB at 1 kHz ref. 2 mV input.

Accuracy of the overall RIAA equalisation is revealed by the pen chart response in Fig. 2. This is maintained within 0.25 dB between the left and right channels over the entire spectrum. With the suppressor on the accuracy is almost the same, but our sample did exhibit a very


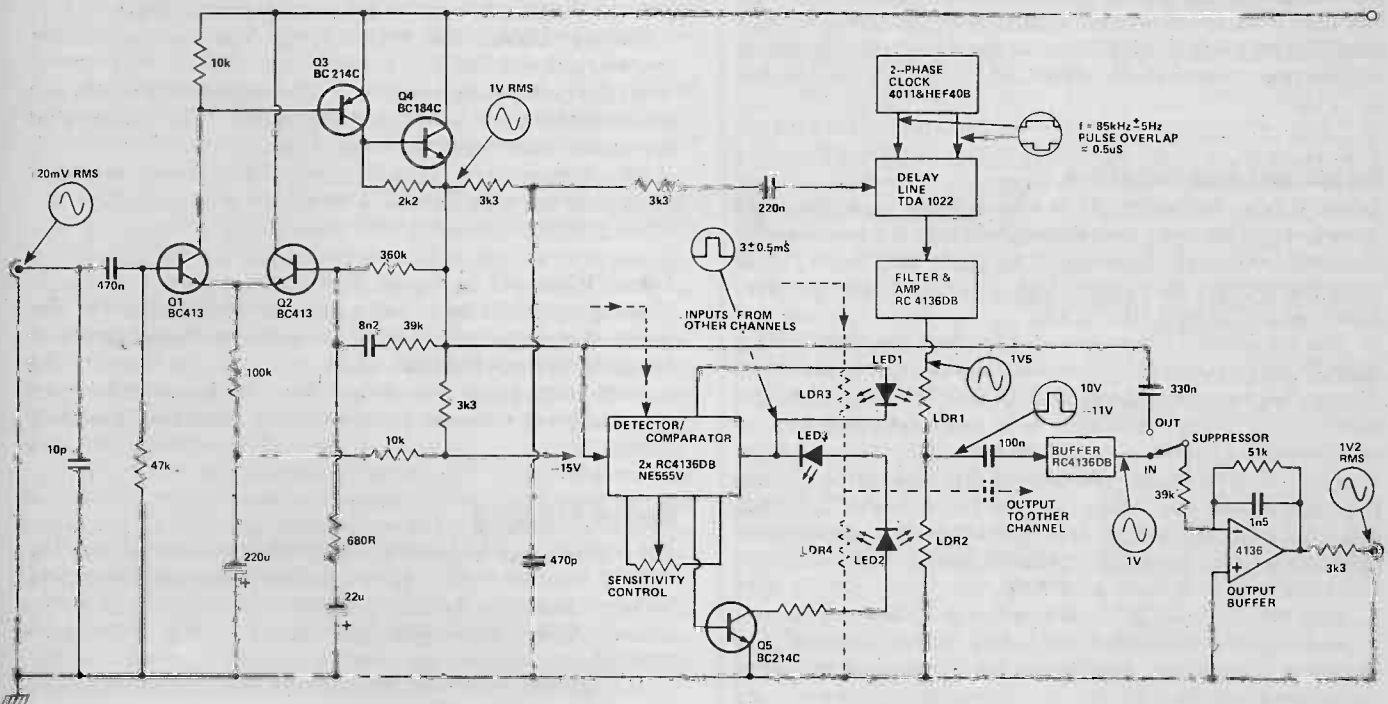


Fig. 1 (Above) The block diagram of the Garrard click eliminator MRM 101. The pickup amplification and equalisation stages were found to give a very high quality signal output. Note the use of quad op-amp 4136.

Fig. 2 (Right) RIAA equalisation curve for the unit. Channel balance was an excellent 0.25dB!

mild error round 15 kHz which was subsequently proved to be caused by a poor tolerance component. The tolerance in this area is being tightened by the manufacturer.

To the onset of peak clipping the amplifier is capable of providing an output of 9 V RMS at middle and low frequencies, with adequate reserve up to 20 kHz, resulting in an output slewing rate of round 0.15V/ μ sec., which will accommodate all disc material played on top-flight pickups. With the suppressor active the output is reduced by approximately 10 dB, but this is still more than adequate, even when driving direct to a power amplifier. The measured S/N ratio was 75 dB (CCIR/ARM weighting) ref. 7 mV RMS input.

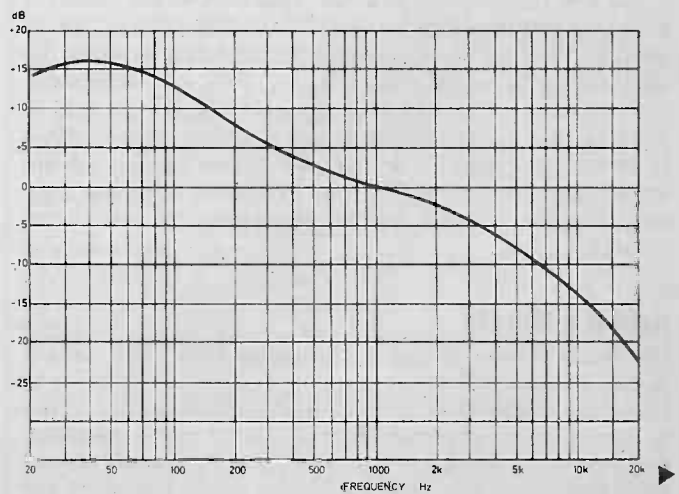

Lines of Frequency

The spectrogram in Fig. 3. gives an excellent impression of the spectra purity with a 200 Hz signal of $2V_{RMS}$ output level. Ripple components are below our measuring floor of -90 dB, and the only harmonic of significance is the 2nd at -79 dB, corresponding to 0.0112%! With the suppressor active the distortion is greater, as shown by the spectrogram in Fig. 4, again at 2V RMS output. The 2nd harmonic again predominates, but this time it is -50 dB (0.3%). The 3rd harmonic is down at -59 dB (0.112%), while all subsequent harmonics are at levels of insignificance.

The relatively high value of 2nd harmonic distortion is not disconcerting. Indeed, recent tests have suggested that a controlled amount of even-order non-linearity can, in fact, enhance rather than detract from the reproduction.

There seems to be a tendency for it to 'disguise' the heavy odd-order distortion carried by some program signal sources, including gramophone records, and that this can lead to improved auditioning of some highly specified transistor amplifiers — owing to the resulting 'valve type sound,' no doubt!

Circuitous Examination

Looking now at the circuit in Fig. 1 with the suppressor active, it will be seen that the signal from the front-end is directed two ways. One way is to delay line (TDA1022) and the other way is to the detector/comparator ($2 \times RC4136DB$ and NE555V).

The detector recognises the whole waveform of a scratch and isolates it from the peaks of the recorded music. Two monostables (one in the NE555V and the other the bipolar transistor Q5) are switched by the scratches to generate pulses of about 3 mS. duration and 10 V amplitude (shown on the diagram). These pulses are then caused to operate LEDs 1 and 2, which are optically-coupled to two pairs of light dependent resistors (LDRs). One pair relates to the right channel and the other pair to the left channel.

Just one channel is shown in the diagram.

The LDRs associated with the other channel are drawn in broken line, as also are the inputs and output of the other channel.

Each pair of LDR forms an attenuator (called a fader) and is arranged to control the level of the audio signal emanating from the delay line prior to the signal arriving at the first buffer (RC4136DB). This part of the circuit is deliberately simplified for the sake of description, but in practice the degree of attenuation amounts to some 50 dB in the audio signal channels each time a pulse occurs.

Now, since it takes a little time for the pulses fully to develop, the signals in the audio channels proper need to be delayed slightly so that the scratch pulse on the music signal arrives at the fader at exactly the same time as the pulse created by the detector and associated circuits.

Hold it a Minute

The delay is provided by a 256-stage TDA1022, which is two-phase-clocked by a pair of ICs HEF4011 and HEF40B. The clock is running at 85 kHz, and the overlap of the two associated waveforms (shown in the diagram) ensures the required delay time. The net result is that each time a scratch click occurs the audio channels are

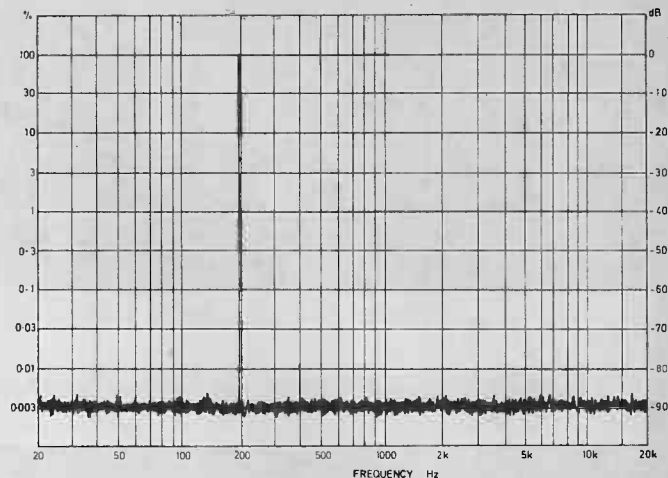


Fig. 3 Spectrogram of the 200Hz drive signal, suppressor switched out.

faded by about 50 dB for a period a shade over 2 mS.

This straddles the time of the 'real' scratch click, thereby eliminating it.

LED3 is the suppressor activity indicator on the fascia which, being in series with a fader LED, flashes in sympathy with the suppressor action.

The detector circuit includes auto and manual threshold control, while a filter in the amplifier IC, RC4136DB, following the delay line eliminates the spikes and spurious signals produced by the delay line action. It should be noted that although the maximum clipping output is less in the suppressor mode than in the direct mode, the gain of the amplifier sections remains the same in both modes.

It is thus possible to achieve A/B comparisons without level change by switching between the two modes.


House Training

The sample unit has been operating very successfully for several months under typical domestic conditions in our test hi-fi system. It certainly removes the very disconcerting staccato clicks caused by badly scratched records.

It does not, however, remove the general background noise from worn or dirty records.

Such noises occur in almost continuous manner, so advancing the threshold control to achieve a response to these noises would lead to the elimination of a substantial proportion of the music.

Operated as the designers intended, the unit constitutes a valuable item of record playing hardware which, at the probable selling price of £80 or so, would soon pay for itself, records costing what they do today.

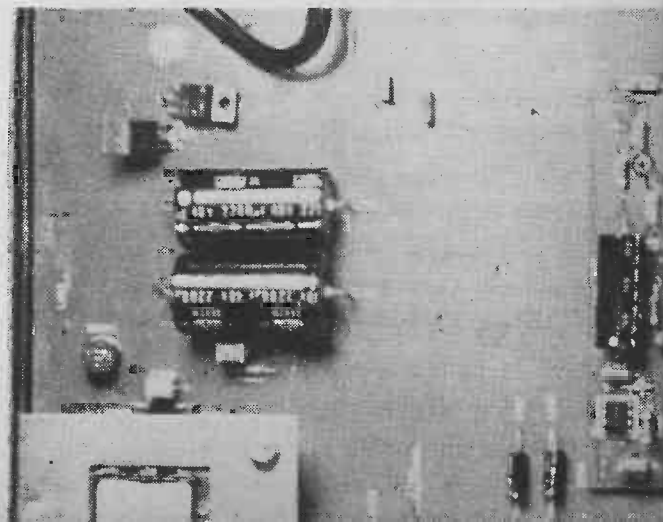

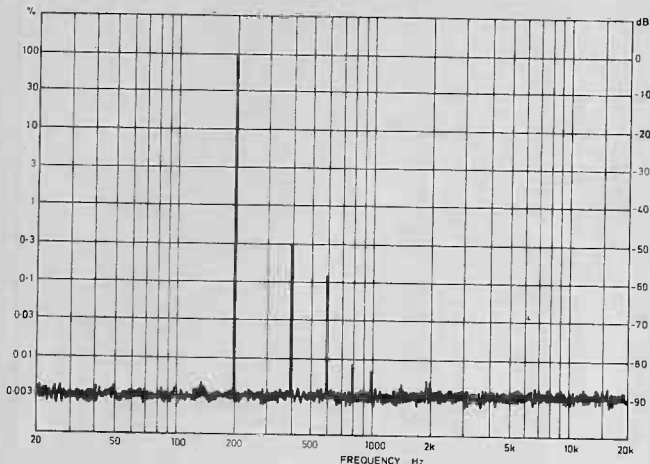


Fig. 4. Spectrogram of the 200Hz drive signal with the suppressor active.

In spite of the rise in distortion with the suppressor active, the reproduction is very satisfying provided the threshold control is not over-advanced.

In the suppressor off mode, the unit can be regarded as a top-flight RIAA-equalised preamplifier of potentially high audio output which could, if required, be connected direct to a power amplifier, thereby bypassing the circuits and tone controls of conventional preamplifiers, which are regarded by some enthusiasts as an impairment to 'musicality.'

A Cabled Reason?

Although acoustical feedback (below the howl-round threshold) is currently being blamed for one aspect of adverse auditioning of some record decks, we have recently isolated other, probably more important, causes of auditioning differences.

We have discovered that signal from the power amplifier section can get back to the high gain pickup input via a common impedance or by magnetic induction from the loud-speaker cables, for example) or electrostatic coupling somewhere.

The degree of response to the delayed spurious signals of this nature can be **as great as, if not greater than, the spurious and delayed signals attributable to mild acoustical feedback!**

Perhaps this is one reason why the 'special' loud-speaker and source cables are receiving acclaim, because the improved shielding of these cables is reducing the amount of signal back-coupling.

Anyway, during experiments with the MRM101 we found that by using this unit for disc signal amplification the degree of back-coupling was substantially reduced with respect to certain integrated power amplifiers. Food for thought, at least.

ETI

GREENWELD

443 Millbrook Road Southampton
SO1 0HX Tel: (0703) 772501

All prices quoted include VAT. Add 25p UK/BFPO Postage. Most orders despatched on day of receipt. SAE with enquiries please. **MINIMUM ORDER VALUE £1.** Official orders accepted from schools, etc. (Minimum invoice charge £5). Export/Wholesale enquiries welcome. Wholesale list now available for bona-fide traders. Surplus components always wanted.

DIODE SCOOP!!!

We have been fortunate to obtain a large quantity of untested, mostly unmarked glass silicon diodes. Testing a sample batch revealed about 70% useable devices — signal diodes, high voltage rets and zeners may all be included. These are being offered at the incredibly low price of **£1.25/1,000** — or a bag of 2,500 for **£2.25**. Bag of 10,000 **£8**. Box of 25,000 **£17.50**. Box of 100,000 **£60**.

SPECIAL SUMMER OFFERS

Audio IC's
76003N **£1.40** 76013N **£1.00**
76023N **£1.00** 76033N **£140**
LM380 **80p** TBAB10S **90p**

Linear ICs etc.
741(BDIL) **18p** BD131 **24p**
555 **25p** BD132 **28p**
1N4148 **2p** 2N3819 **18p**

TTL PANEL

52 logic ICs including 32 x 74161 (4 bit binary counter) + 16 tant bead caps, R's, C's, etc. Over £30 worth of TTL alone!! **ONLY £3.00.**

DISC CERAMIC PACK

Amazing variety of values and voltages from a few pF to 2.2uF! 3V to 3kV! 200 **£1, 500 £2.25, 1,000 £4.00.**

PC ETCHING KIT MK III

Now contains 200 sq. ins. copper clad board, 1lb. Ferric Chloride, DALO etch-resist pen, abrasive cleaner, two miniature drill bits, etching dish and instructions. **£4.25.**

EDGE CONNECTORS

Special purchase of these 0.1" pitch double-sided gold-plated connectors enables us to offer them at less than one-third of their original list price!
18 way **41p**; 21 way **47p**; 32 way **72p**; 40 way **90p**.

VERO PLASTIC BOXES

We keep a very large range of VERO products — inc. their recently introduced G range of cases, and Series II boxes. SAE for their catalogue.

TMS4030 RAM

4096 bit dynamic RAM with 300ns access time; 470ns cycle time; single low capacitance high level clock I/p; Fully TTL compatible; Low power dissipation. Supplied with data **£2.75.**

MISCELLANEOUS IC's

Supplied with data if requested. MC3302 quad comp. **120p**; 710 diff comp. (TO99) **40p**; ZN1034E precision timer **£2.25**; LM711 Dual diff comp **65p**; LM1303 dual stereo pre-amp **75p**; MC1469R voltage reg **£1.50**; UPC1025H audio **£3.50**; 575C2 audio **£2.88**; 1DA2640 audio **£2.92**; TBAB10S audio **70p**; SN75110 dual line driver **70p**; MC8500 CRCC gen POA.

EXPERIMENTERS CALCULATOR

Based on the C500 chip, this pack of parts enables the more experienced constructor to make an 8 digit 4 function calculator. The comprehensive data supplied includes full-size layout of PCB required, types of suitable display and keyboard that can be used etc. Components included in the pack are C500 calculator chip, driver IC, all components for inverter/clock circuits, R's C's etc. All for only **£3.50.**

RELAYS

W847 Low profile PC mntg 10 x 33 x 20mm 6V coil, SPCO 3A contacts **93p**.
W832 Sub. min type. 10 x 19 x 10mm 12V coil DPCO 2A contacts **£1.15**.
W701 6V SPCO 1A contacts 20 x 30 x 25mm. Only **56p**.
W817 11 pin plug in relay, rated 24V ac, but works well on 6V DC. Contacts 3 pole c/o rated 10A. **95p**.
W819 12V 1250R DPCO 1A contacts. Size 29 x 22 x 18mm min. plug-in type **72p**.
W839 50V ac (24V DC) coil. 11 pin plug-in type. 3 pole c/o 10A contacts. Only **85p**.
W846 Open construction mains relay. 3 sets 10A c/o contacts. **£1.20**.
Send SAE for our relay list — 84 types listed and illustrated.

LOW COST PLASTIC BOXES

Made in high impact ABS. The lids are retained by 4 screws into brass inserts. Interior of box has PCB guide slots (except V219).
V210 80x62x40mm black **58p**
V213 100x75x40mm black **72p**
V216 120x100x45mm black **86p**
V219 120x100x45mm white **86p**

STEREO AMPLIFIER CHASSIS £5.50

Complete and ready built. Controls Bass, treble, volume/on-off, balance. 8 transistor circuit gives 2 watts per channel output. Just needs transformer and speakers for low cost stereo amp. Suitable metal cabinet (W374) **£2.00** — or buy the amp, case and transformer for **£10.00** and get DIN speaker sockets and knobs free!

AMPLIFIER KIT £1.75

Mono gen. purpose amp with tone and vol./on-off controls. Utilizes sim. circuitry to above amp. Output 2W into 8 ohms. Input matched for crystal cartridge. 4 transistor circuit. Simple to build on PCB provided. Can be either battery or mains operated. (For mains powered version add **£2.20** for suitable transformer). Blue vinyl covered aluminium case to suit (W372) **£1.30.**

1977/8 CATALOGUE

48 BIG pages packed with over 4,000 items, many of them illustrated. Discount vouchers worth 50p. PRICE **30p + 15p** post. (Overseas send **60p** surface or **£1** airmail.) Also included is our current Bargain List. Send SAE for bargain list alone.

SIRENS


Use in cars, houses, anywhere that a powerful noise will frighten off would-be intruders. Uses 4 HP7 batts. Overall size 100x72x60mm. Only **£1.70.**

BUY A COMPLETE RANGE OF COMPONENTS AND THESE PACKS WILL HELP YOU

- * **SAVE ON TIME**—No delays in waiting for parts to come or shops to open!
- * **SAVE ON MONEY** — Bulk buying means lowest prices — just compare with others!
- * **HAVE THE RIGHT PART** — No guesswork or substitution necessary!

ALL PACKS CONTAIN FULL SPEC. BRAND NEW, MARKED DEVICES — SENT BY RETURN OF POST. VAT INCLUSIVE PRICES.

- K001** 50V ceramic plate capacitors, 5%, 10 of each value 22pF to 1000pF. Total 210. **£3.35**
- K002** Extended range, 22pF to 0.1µF, 330 values **£4.90**
- K003** Polyester capacitors, 10 each of these values 0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1, 0.15, 0.22, 0.33, 0.47µF, 110 altogether for **£4.75**
- K004** Mylar capacitors, min 100V type, 10 each all values from 1000pF to 10,000pF. Total 130 for **£3.75**
- K009** Extended mylar pack. Contains all values from 1000pF to 0.47µF. Total 290 capacitors to **£11.25**
- K005** Polystyrene capacitors, 10 each value from 10pF to 10,000pF, E12 Series 5% 160V. Total 370 for **£12.30**
- K006** Tantalum bead capacitors, 10 each of the following 0.1, 0.15, 0.22, 0.33, 0.47, 0.68, 1, 2.2, 3.3, 4.7, 6.8, all 35V; 10/25, 15/16, 22/16, 33/10, 47/6, 100/3. Total 170 tants for **£14.20**
- K007** Electrolytic capacitors 25V working, small physical size, 10 each of these popular values 1, 2.2, 4.7, 10, 22, 47, 100µF. Total 70 for **£3.50**
- K008** Extended range, as above, also including 220, 470 and 1000µF. Total 100 for **£5.90**
- K021** Miniature carbon film 5% resistors, CR25 or similar, 10 of each value from 10R to 1M, E12 series. Total 610 resistors **£6.00**
- K022** Extended range, total 850 resistors from 1R to 10M **£8.30**
- K041** Zener diodes, 400mW 5% BZY88, etc. 10 of each value from 27V to 36V, E24 series. Total 280 for **£15.30**
- K042** As above but 5 of each value **£8.70**

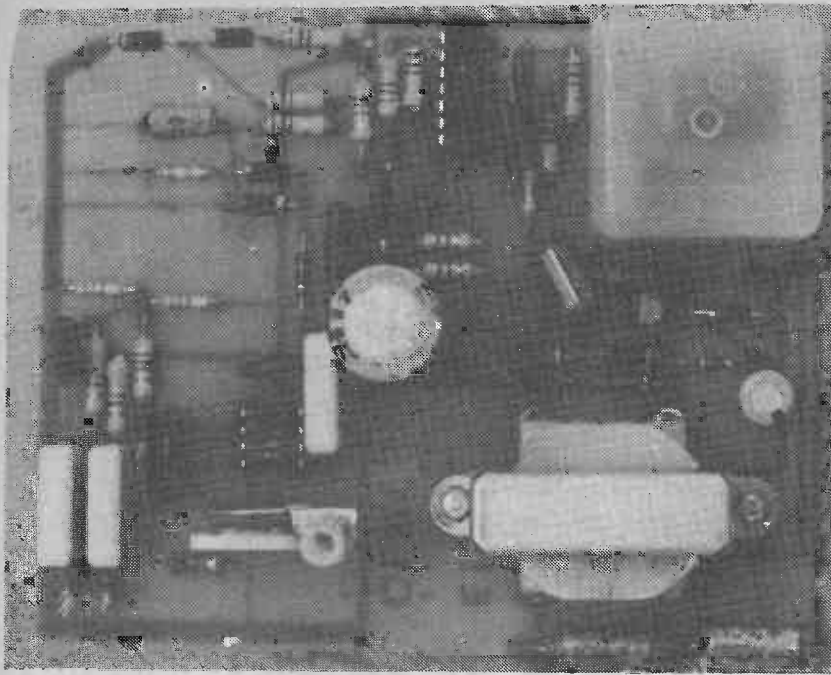

It was touch and go with ETI's project team this month during the design of this project

PROXIMITY SWITCH

ALTHOUGH THIS PROJECT may look a bit complicated for a 'mere' switch, it has some unique features, both in design and function, as will be clear from the following:

1. It is a true proximity switch. You do not have to actually touch anything to operate it.
2. There are no light beams, sound waves etc. While radio frequencies are used, switching action results solely from the capacitance of 'approaching bodies.'
3. The sensor may be some distance away from the device, and also may extend several feet in length.
4. The sensor — and, if you want to mystify your friends, the switch itself — can be completely concealed from view.
5. The switch latches ON or OFF each time it is operated. No special re-set provision is needed.
6. Since a relay is used for the actual switching, the 240V circuit and the 'electronics' are isolated from each other.

Making Magic

In our application, the 'Magic Switch' was installed so that when one walked through a doorway a light in the further room automatically went on. Also, the sensor extended close to the floor, so

that even the family dog was able to "light the way".

(Admittedly, this at first struck terror and bewilderment into the mind of the canine, but, as usual, he soon came to accept the miracle as just one more example of human omnipotence!) Other applications could well include burglar alarms etc., all of which is to say nothing of its main function, which is to impress your friends.

Construction

Use of the PCB of Fig. 4 is recommended, though three prototypes were built using different layouts, and all worked well. Note that this PCB has space for the power transformer and relay, but is left blank as far as the foil pattern for those units is concerned. This enables you to use whatever components you happen to have, or which may be available to you. You can either fill in your own foil pattern, or hard-wire the units into the circuit. Beyond this, no special comments are necessary, except to mention that it is preferable to use IC sockets. Since 240V AC will be present on-board, the unit should be housed in a suitable cabinet such as a 7-3/4" x 4-3/8" plastic utility box. An AC outlet receptacle could be mounted to the box, plus a main switch if desired.

Adjustment

The success of the project depends on the oscillator being just, but only just, within its tolerance limits, and the operating point is set by RV1 (coarse) and RV2. This adjustment is critical, but as a rule RV1 can be preset on the bench and RV2 adjusted at the time of installation. The exact operating point, and hence sensitivity, depends on the length of sensor used.

In a very few cases, RV1 needs to be more than 2k2. The easiest thing is to pad the control with a oto0 series resistor. This can easily be mounted on board and the existing track connecting RV1 to RV2 broken, the additional resistor being 'tapped in' in its place.

When you have completed wiring the switch, and have carefully checked your work, plug it in and clip a length of wire 200-300mm to the sensor input at point A. Set RV2 to mid-rotation, and adjust RV1 until you hear the relay clicking. This is an approximate adjustment, but at some nearby setting you will find that the relay clicks every time you approach the sensor wire with your hand. If you clip the sensor wire to point B you will find the circuit somewhat less sensitive; since sensitivity increases with sensor length, this is

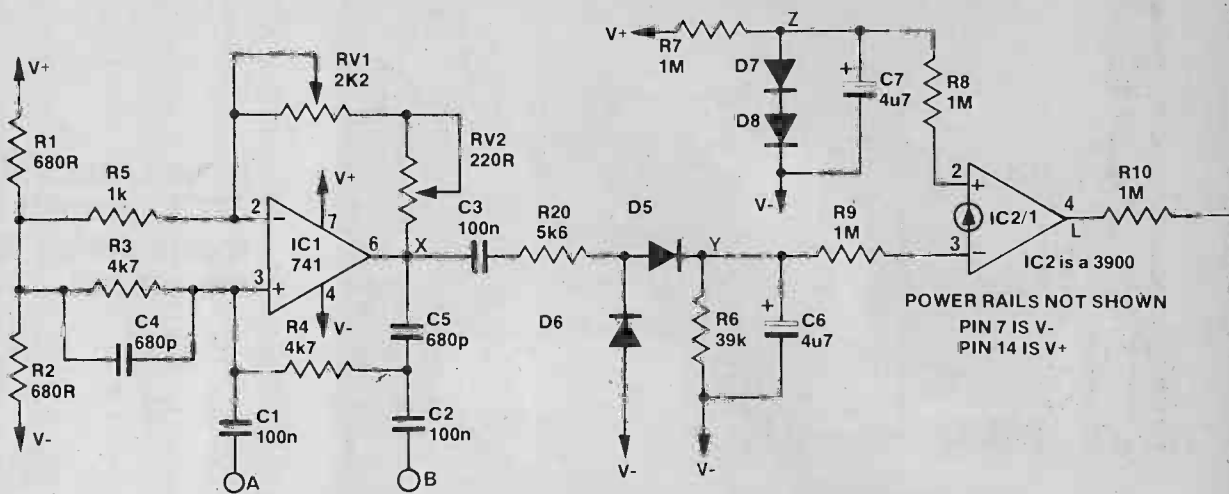


Fig. 1. Main circuit diagram of the proximity switch.

useful where long sensors are to be used.

You can trace the sequence of events using an ordinary voltmeter. Point Y, the rectified oscillator signal, should read about 3 V, and drop to 0 V every time the sensor is approached. The reference voltage can also be measured at point Z. If you have a scope, you can display the waveform at point X, and see it 'collapse' when the switch is operated. Further tracing can be done at point L (comparator output), M (shaper) and N (flipflop), which makes it easy to pinpoint problems should they arise.

Installation


This will depend on the purpose for which your 'Magic Switch' is intended, but the following hints and observations will apply.

1. Aluminium foil strip (30mm wide) makes a good sensor. It can be 3m or even longer, and is easy to conceal behind vinyl decorator tape, wallpaper, tile etc. If the switch is to be some distance away from the sensor, a length of wire can be used to connect it, but this will add to the effective length.
2. The longer the sensor is the more sensitive the switch will be, and you will find the provision of two inputs helpful. While it is true that you do not have to actually touch the switch to operate it, long sensors and

HOW IT WORKS

IC1 is a standard LM741 Op Amp configured as an oscillator operating at a supersonic frequency. The circuit is adjusted so that it is 'on the edge', and the capacitance effect of a body approaching its sensor causes it to "drop out." The rectified signal is fed to section 1 of IC2 (an LM3900 quad 'current differencing' amplifier) where it is compared with a reference voltage obtained from the R7-D7-D8 network. When the oscillator drops out, the signal voltage falls below the reference level, causing the comparator to produce a pulse at its output. This is 'squared up' by section 2 of IC2 to positively trigger a flipflop, composed of sections 3 and 4, and the output of this is used to operate a relay via driver Q2.

Because the relay draws enough current to cause a change in supply volts every time it is ON, and this would de-stabilise the oscillator, a simple voltage regulator of the series pass transistor type is used. This works like an emitter follower, in which the circuit as a whole is the load. The emitter of Q2 tracks the base, which is clamped by a zener diode to 15 V. In addition we reap the advantage of 'capacity multiplication,' since C11 smooths any ripple etc. present in the base supply. Though C11 is small, the filtering effect is impressed on the output, and in practice the value of the capacitor is multiplied by the gain on the transistor.

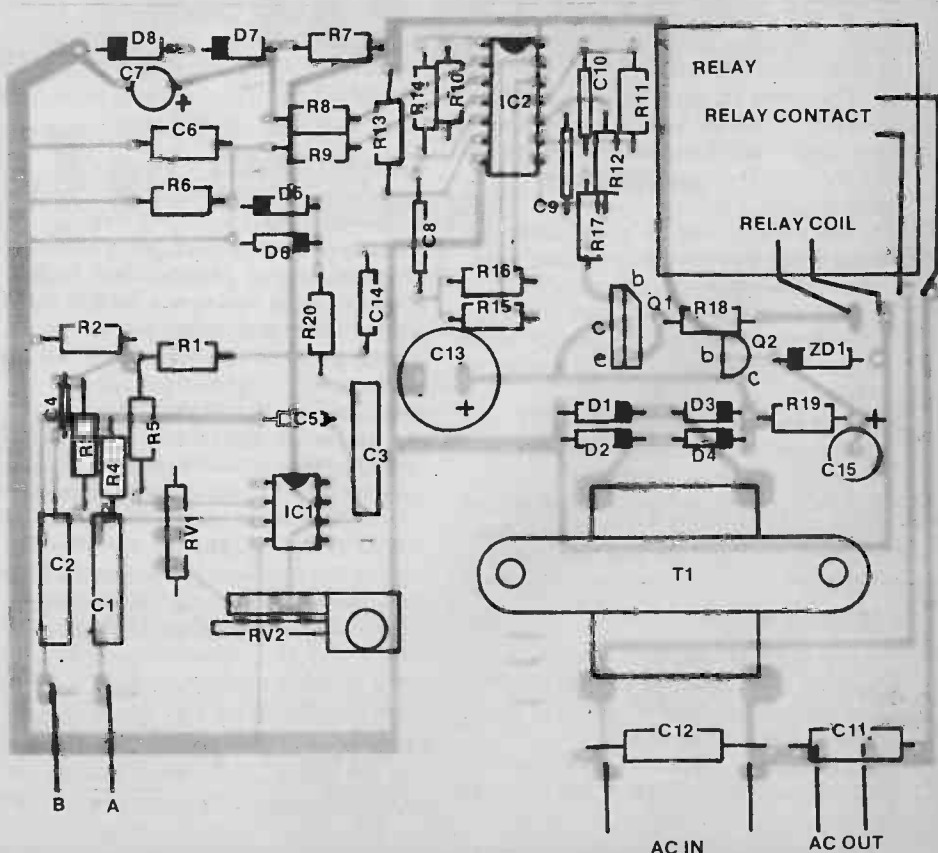

PROJECT: Proximity Switch

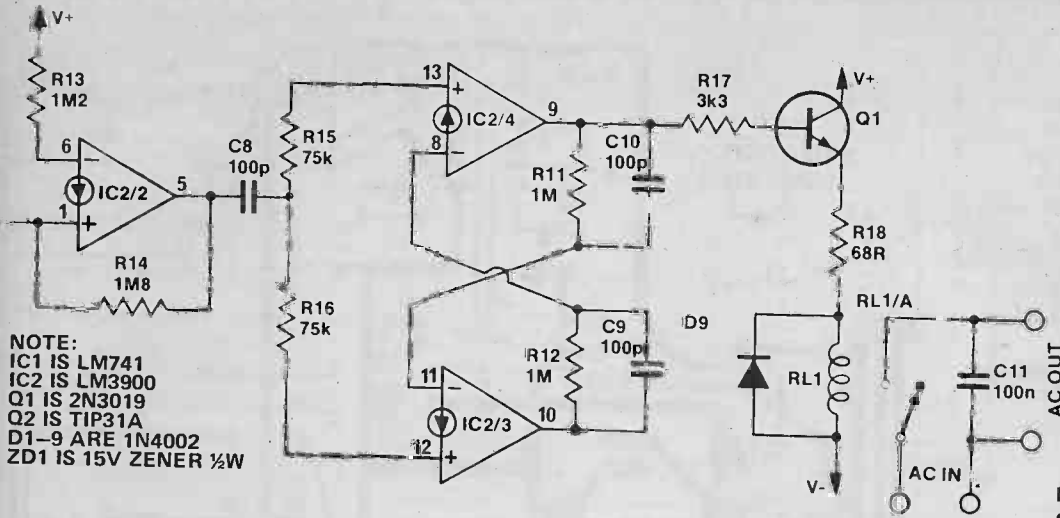


Fig. 3. (Below) Circuit diagram of the switch's power supply.

PARTS LIST

RESISTORS

1/4 W 5% unless stated

R1,2	680R
R3,4	4k7
R5	1k0
R6	39k
R7,12	1M0
R13	1M2
R14	1M8
R15,16	75k
R17	3k3
R18	68R 1/2 W
R19	470R
R20	5k6

CAPACITORS

C1,2,3,11,12	100n	polyester
C4,5	680p	polystyrene
C6,7	4u7 16V	electrolytic
C8,9,10	100p	polystyrene
C13	1000u 16V	electrolytic
C14	68n	polyester
C15	47u 16V	electrolytic

Note C11 and C12 should be rated at 400 V

SEMICONDUCTORS


IC1	741
IC2	3900
Q1	2N3019
Q2	TIP31A
D1-9	1N4002
Z1	15 V 400 mW

TRANSFORMER

T1	240 V / 12 V 300mA
----	--------------------

MISCELLANEOUS

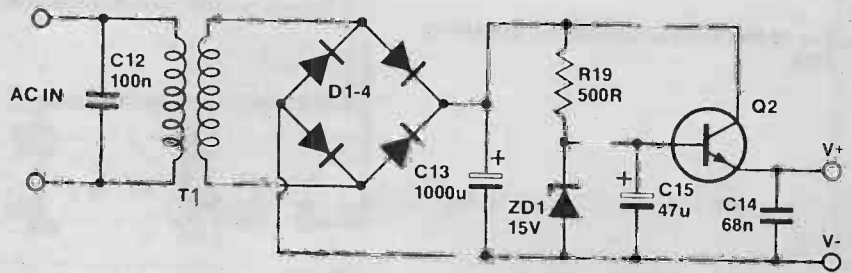PCB as pattern, Relay (10-30mA, 15 V or less), case to suit, sensor, etc.



BUYLINES

All of the parts used in this project should be available from most of the advertisers in this issue. Make sure the 100n capacitors C11 and C12 are adequately rated at 400V.

The case should be earthed if it is metal as 240V is present on board. Our prototype, however, was built into a plastic box.

extreme sensitivity can raise problems. If, for instance, the switch is made sensitive out to 1m from the sensor, merely walking around will probably cause it to switch on and off erratically. This is due to local capacitance-field effects and not to any shortcoming in the switch itself, and therefore makes it desirable to operate with more limited sensitivity.

3. If operation is erratic, it will usually help to connect circuit (-) to a true ground (waterpipe etc.) In most cases, however, this is not necessary.

4. The switch can be directly connected to any metal object (e.g., filing cabinet) you might wish to protect. Likewise, it can be used to operate any external circuit, such as

an alarm. As a protection device, the 'Magic Switch' will baffle any intruder, if not psych him out completely.

Interference

The 'Magic Switch' is relatively immune to interference such as mains surges, field disturbances etc. About the only time trouble may possibly arise is when the switch is run off the same 240V circuit as is used to power some inductive load, e.g., a refrigerator. The reason is that every time the inductive device is switched on, a large transient voltage is developed on the AC line (chiefly across the 1 ohm resistance of the

Fig. 2. Overlay for the proximity switch PCB (left).

PROJECT: Proximity Switch

main fuse). If your room lights dim every time the 'fridge goes into action, you will appreciate the magnitude of this type of surge. Experience has shown that the 'Magic Switch' can cope with most things — SCR dimmers, tape recorders, vacuum cleaners, to name but three which we have operated off the same 240V line — but in a few cases special precautions are necessary. Mains surge suppressors may be fitted, but generally it is simplest just to run the 'Magic Switch' off a different AC circuit.

ETI

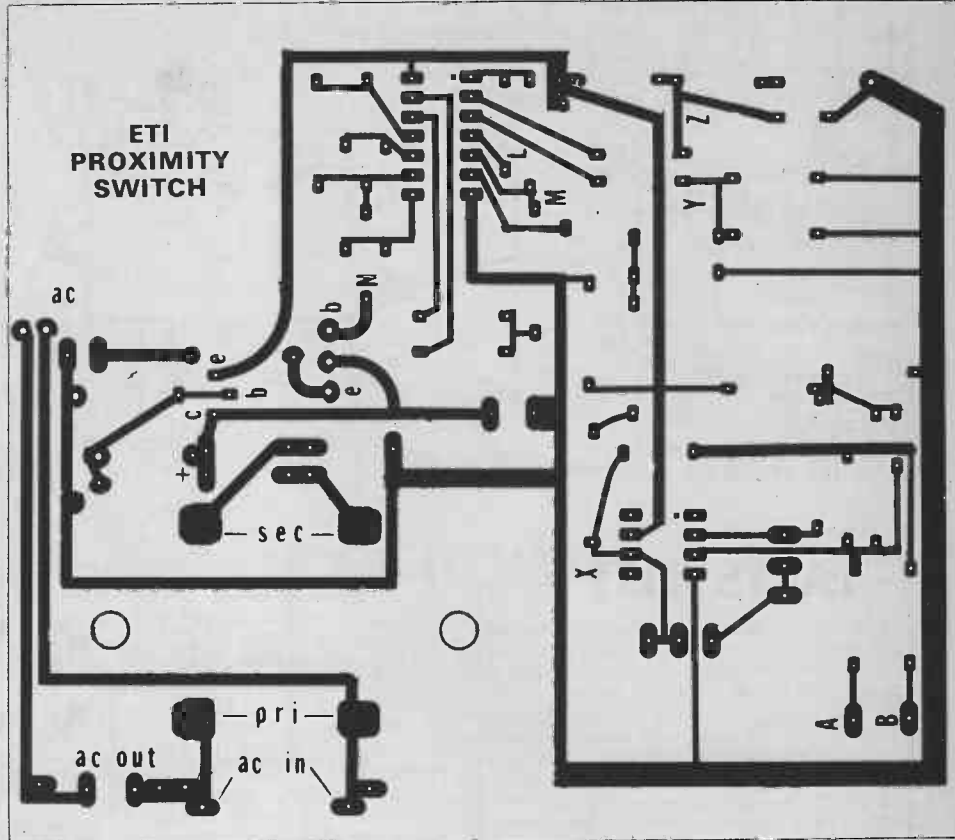


Fig. 4. Full size foil pattern for the switch's PCB.

DORAM

SEE THE RANGE OF BOOKS IN THE NEW DORAM HOBBIES CATALOGUE.



Doram Electronics Ltd
PO Box TR8, Leeds LS12 2UF

Please send my FREE Hobbies Catalogue.
I enclose 25p contribution to p. & p. (AVAILABLE LATE SEPT)

Name.....
Address.....

DORAM Doram Electronics Ltd
PO Box TR8, Leeds LS12 2UF


Overseas customers (except for N. Ireland)—60p including despatch by Air (or all-up post).

ET16

ALMARC & VECTOR GRAPHIC

"Nobody Does It Better"

INTRODUCING THE VECTOR 1 COMPUTER

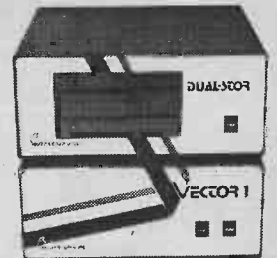

- S-100 BUS
- HIGH QUALITY
- LOW PRICE

Whatever your application Vector Graphic and Almarc have the answer. Mainframes, Memory, I/O Boards, Disk Systems, Processors, and the unmatched High Resolution Graphics board. Send for our catalogue today.

OTHER PRODUCTS:

Solid State Music, including 8k Static Ram Board, £98.95.

ALSO:

Cromenco, North Star, Dynabyte, and, our best product, "Service".

Write for details to:

ALMARC DATA SYSTEMS LTD.
29 CHESTERFIELD DRIVE
BURTON JOYCE, NOTTINGHAM
TEL. 0602 248565

microfile.....

Go north young man they said and Gary Evans did this month to see Liverpool's new Personal Computing store.

TAKING LIFE, LIMB and day return ticket in hand, I headed North this month. The carrot that induced this seemingly irrational behaviour was the fact that a new computer store was to open in Liverpool, which for those of you whose sense of direction is as bad as mine, is north of London.

Microdigital is Liverpool's first Computing Store and, as far as I know only the second shop in the country to sell a broad range of low cost computing equipment (the other being the Byte Shop). The range of items Microdigital will sell you is indeed large, everything from that dreadful MPU door-chime, through video games and chess machines to PETs and APPLES taking in the MK14 and NASCOM1 on the way. The reason for this wide range, which includes items that many of us would not associate with personal computing, back to the door-chime, is quite straightforward. The aim is to hook people with these items that can be considered impulse purchases in the hope that when installed in the family home they will promote the idea that the computer does have a place in the home.

The site of the shop, like the items stocked, has also been chosen with care. The site is not what would be considered prime by the likes of Dixons, being situated in the business area of the city. The idea behind siting Microdigital here was again to do with hooking potential customers, but here the potential victims are the City Gents of Liverpool. A shop in the "jean jungle" that now

Gary Evans, to photography what Cyril Smith is to the world of ballet, took this photo of Liverpool's new computing store on its opening day.



forms the heart of Liverpool would not have exposed the shops name to this market. The site in Brunswick Street will mean that many of the aforesaid business men will not be able to avoid the name of Microdigital and it is the hope of the company that some of them may even walk through the door. Don't get the idea that the shop is too far from the centre of the city, it's just a few moments walk away so those interested in the novelty value of the shop will still make the trip as well as the already converted Computer Hobbyist.

The staff at Microdigital will offer advice and as one of them comes from a background as an accountant, it should mean that the advice given will be formed with an appreciation of the businessman's needs. The shop will also sell a wide variety of literature and software to enable the best use to be made of the different hardware packages available.

The firm's range of systems is detailed in their catalogue and an SAE to them should secure a copy of same. Better still, why not call in and pick one up in person, you'll probably find chatting to the staff very helpful.

**Microdigital
25 Brunswick Street
Liverpool 2**

Disk-O-Spec

Floppy disk drives will probably be one of the items that will fall in price considerably over the next year, they have to. The cost of producing a drive will fall as the volumes demanded by the world markets increase, after all if you want a handmade cassette deck expect to pay the earth for it, buy 100,000 and the price comes down to a reasonable figure. As we see the price come down we'll also see more people offering hardware/software packages to enable you to hook the drive up to your particular breed of machine. At the present floppies for even the most popular of machines are hard to find, but I've heard of a couple of people who might be able to help.

James Clarke and Co Ltd are interested in developing a 512K or 1.2M drive which they see as having some additional memory and, of course, an operating system. They are interested in hearing from anyone who might be interested in such a product.

The other company, Ocean Electronics, have a single card controller for the Shugart SA400, suitable for interfacing this drive to the PET (the company can also offer controllers for 6800 and 8080 based systems).

The card is expected to sell for £120, and with the SA400 at around £225, this seems like an attractive package.

The companies can be reached at the addresses shown below.

James Clarke and Co
7 All Saints Passage
Cambridge
CB2 3LS

and **Ocean Electronics**
3 Pavillion Parade
Brighton
BN2 1RA

digest..

watch reaction

Once more into the breach . . . and all that stuff. Why is it that buying anything these days turns into a battle between salesman and (intended) victim? Are there nought but sharks lurking on the far side of the counters? Are all the good men honest and true working for ETI? (ouch).

Forgive the outpourings of despair gentle reader but there really are times when we do wonder. With apologies to all the excellent retail outlets in the trade that we and you know and love, for we feel it may serve to recount this little tale of what happened when one of our staff was perusing digital watches in a nameless emporium in Tottenham Court Road.

- Sales Person:** (*Closing in with a glint; Can I help you sir?*)
- ETI Dupe:** It is O.K. thanks I'm just looking at your men's watches — do you have any in stainless steel?
- Sales Person:** (*Rubs hands speculatively*) You can see all we have down there — those Seiko are very nice machines(?)
- ETI Dupe:** How much?
- Sales Person:** £90.50 — plus VAT of course. Worth every penny though. Rolls-Royce of watches these — fantastic.
- ETI Dupe:** Yes very nice — but why are they so much more expensive than those others?
- Sales Person:** Oh there's no comparison. These work on a totally different principle to ANY other digital watch, and this method is much more expensive to make. Quartz you know.
- ETI Dupe:** (*Displaying his full range of knowledge on the subject*) But they all use quartz crystals in the oscillators, and most use the same frequency even don't they?
- Sales Person:** (*Gives smug look and shakes head sagely*) No, no, no, no — you've been reading some of these Sunday supplements. Absolute rubbish those. Seiko don't even use an oscillator at all — none of these frequencies at all. Not a moving part in the entire watch.
- ETI Dupe:** (*Beginning to lose contact with reality*) But if it doesn't use an oscillator what does it count to keep time?
- Sales Person:** (*Totally confident*): Days sir. Very reliable these. Accurate to five secs a month. LCD display, backlight, the whole bit.
- ETI Dupe:** (*Mystified*) LCD? What's that stand for?
- Sales Person:** (*Efficiently and knowledgable*) Lit Continuously sir. No need to push a button to find the time out here.

At that point we'll draw an editorial veil over the proceedings. Believe us or not as you wish — but perhaps shops should show the discourse to their staff, and fire anyone who can find nought wrong. P.S. We're working on a project for a watch that counts days, rather than messy 32k oscillator signals. Ours times the intervals between ice ages by periods of the moon, and divides by 11,500,000,000,000.

Texas at home

A users club now exists for those fortunate to own TI machines. Called the '59 Club' it resides at 27 Montem Lane, Slough, Berks under the watchful eye of one Tim London. A

program library is in there somewhere too, and a newsletter is envisaged. So if you're into Texas keystrokes you know where to go now.

THIS MONTH'S SPECIAL OFFER "Motorola Audio Amplifier 1watt I.C."

1 watt plus into 8-16 Ω, 9-16V, 10-400 MV sensitivity. Short circuit proof, no heatsink required. **Only 90p** with Data and circuits.

Sentinel Smoke and Gas Detector. This beautifully made unit uses quality components on fibreglass board, encased in heavy duty, domed diecast box, 3 1/2" diam. x 1 1/2" high. LED indicator, TGS105 plug in sensor, 24v. or 12v by altering 3 resistors, will drive relay or lamp. Ideal for caravans, boats, kitchens, etc., etc. £6.45 with circuit and data.

Miniature **Vemitron™ FM4 10.7MHz** ceramic filters 50p each, 3 for £1

Crystal earpieces with lead 40p each, 3 for £1

Magnetic earpieces with lead and plug 25p each 5 for £1

Ultrasonic transducers transmitter and receiver, 14mm diam 40 kcs. £4.25 per pair

4 aluminium boxes 128 x 44 x 38mm, ideal for signal injectors, etc. £1.00

100 miniature reed switches, ideal for burglar alarms, model railways, etc. £3.30

6.6 pole 12 volt reed relays on board £2.45

High quality **computer panels** smothered in top-grade components.

5lbs. £4.75

10lbs. £8.95

New **U.H.F. transistor TV tuners**. Rotary type with slow motion drive, aerial socket and leads £2.50

Aluminium **TV coax plus** -10 for £1

Miniature edgewise panel mounting level meters 200µa F.S.D. 90p

300 mixed resistors 1/2 & 1/4 watt £1.50

300 modern mixed caps most types £3.30

100 mixed **electrolytics** £2.20

300 mixed printed circuit components £1.50

300 mixed printed circuit resistors £1.00

100 high-wattage resistors, V.W., etc. £2.20

20 assorted **VDRs** and thermistors £1.20

25 assorted **presets**, skeleton/ etc. £1.20

25 assorted **pots and presets** £1.50

470 µF 25v radial, modern type 10 for £1

150 mixed 1- and 2-watt resistors £1.50

100k varicap pots, can be banked side by side, very compact 10 for £1

Mains Neons, long leads 15 for £1

100 mixed modern miniature ceramic and plate caps £1.20

Don't let your environment dehydrate you. BUY OUR "HONEYWELL HUMIDITY CONTROLLER". Membrane actuated, adjustable by 1/4" shaft. Ideal for greenhouses, offices, centrally heated homes, etc. 3.75A contacts at 250V. Build Humidifiers or dehydration alarms with this novel gadget at a fraction of original cost. £1 each, 3 for £2.50.

Semiconductor Bargains

New Super Bargain Diode Pack. Includes zener, power, bridge, varicap, silicon, germanium, marked, unmarked, etc., etc. Excellent value. 300 for £2.95.

New Improved Transistor Packs: 100 New and marked transistors including BC 148, BC 154, BF 274, BC 212L, BF 200 and lots of others. **only £4.95.**

200 transistors as above and including 2N3055, AC128, BD131, BFY50, **only £9.95.**

ITT 25kV ctv eht triplers for Decca Bradford; chassis brand new £2.50, 5 for £1.00

BD131 3 for £1.00

SN76115N (equivalent MC 1310) 50p

TBA 120A 50p

10 assorted convergence pots £1.00

12 Quil, low profile 14 pin i.c. sockets. £1.00

BF 200 6 — £1

BC 212L 10 — £1

BC 154 12 — £1

BF 274 12 — £1

BC 148 12 — £1

BC 148 12 — £1

Varicap diodes 20 for £1

(B.B. types)

Deluxe Fibre Glass Printed Circuit Etching Kits

Includes 150 sq. ins. copper clad f/g board, 1lb. ferric chloride, 1 dalo etch resist pen, abrasive cleaner, 2 mini drill bits, etch tray and instructions. **Only £5.30**

150 sq. ins. fibre glass board £2.00

Dalo pen 90p

1lb. ferric chloride to mil spec £1.25

5lbs. ferric chloride to mil spec. £5.00

Instruction sheet 20p

30p P&P ON ALL ABOVE ITEMS. SEND CHEQUE OR POSTAL ORDER WITH ORDER TO SENTINEL SUPPLY DEPT.,

ETI, 149A BROOKMILL ROAD

DEPTFORD, LONDON, SE8

Callers by appointment only

See The Show, Join The Club

A couple of quick items now. First the Personal Computer World Show will be held at the West Centre Hotel between September 21 and 23. The last day will be devoted to home systems but the whole three days should be worthwhile. Next the North London polytechnic Department of Electronic and Communications Engineering are to form a computer club. The inaugural meeting will be on Wednesday the 5th of October. I hope to be there in room 47 of the old building (their refertence not mine) in the Holloway road just opposite Holloway Road tube for the event. With three PETs and four SWTPC systems available for playing with the club will hopefully prove a fruitful activity for all concerned.

An update on the MK14 review of last month. I have received the new monitor PROM for this machine and as well as making the entry of data far easier, the RPOM contains an offset calculation routine as well as the software to drive the cassette interface for the MK14. A single step mode of operation is also possible with a small amount of additional hardware.

An update to the TRS-80 review as well. Phil Cornes, one of the panel who reviewed the machine has discovered a few memory saving tricks that can be used with the computer.

1. Whenever the last character of a PRINT statement are the final inverted commas of a printed message, those inverted commas may be omitted so that, for example —

10 PR.; "GALLONS USED"

could be abbreviated to —

10 PR.; "GALLONS USED

2. The abbreviation IN for the INPUT statement can be abbreviated still further to I so that —

45 I.X.Y.Z

becomes an acceptable INPUT statement.

3. This abbreviation is the most interesting of the three, and deals with the setting and resetting of flags within programs.

For example, suppose the following appears in one of your programs.

20 F=0

200 IF A=B THEN F=1

This could staggeringly be reduced to the following single statement:

200 F=A=B

In this example the second = is being used as a comparison operator and not as an arithmetic operator. Put into English, this statement would therefore read —

Let the value of F depend on the result of comparing the equality of A and B.

If A does equal B so that the result is a logical "TRUE" then set F to 1 or if A does not equal B (logical "FLASE") set F to 0.

The same type of statement can be made to work with any of the comparison operators, ><, <,>, =, <=, > =; so that —

200 F=C>B

would set F to 1 if C were greater than B otherwise it would set F to 0.

ETI

INTRODUCING TWO WORLD FAMOUS MICROPROCESSOR BASED GAMES UNITS

ETI PROJECT

'TOLINKA' CHESS REPORTER —FULL KIT OF PARTS

The original unit used in conjunction with the World Chess Championship at Manila, August '78, by both Chess Champion Vicktor Korchnio and BBC TV news.

Records every game step, auto en passant, queening and castling. Entire games may be recorded on most domestic cassette recorders. Based on 8060 Mk II Scamp. Full kit including all components — No extras required — **£109.50***




192 GAMES


'ATARI' VIDEO COMPUTER —READY BUILT CARTRIDGE SYSTEM

Designed and built by Atari (part of Warner Bros) in the USA this unit is the most advanced games centre available.

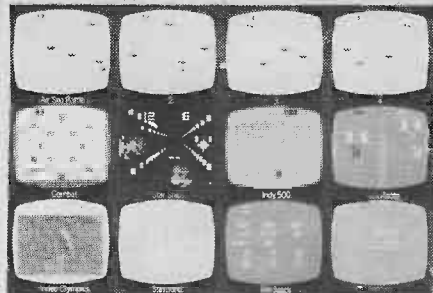Just look at a few of the many games available in full glorious multi-colour and rich sounds.



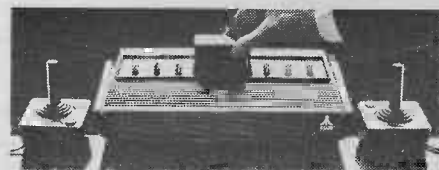The Video Computer (based on Signetics 2550) comes complete with the 27 Game Combat Cartridge, multifunction joysticks mains adaptor and aerial switching unit. Fully guaranteed for 12 months **£169.95***
Total of 9 Cartridges available — 192 games plus many more on the way, priced from **£14.95***



Full colour brochure available on request.

*Prices include VAT, packing & delivery charges and money back guarantee. Send cheque & PO to:

VIDEOTIME PRODUCTS 56 Queens Road, Basingstoke, Hants RG21 1REE
Tel: (0256) 56417. Telex 858747

audiophile.....

This month Ron Harris lends an ear (and an eye) to a new turntable aid that you can see through immediately; what could be the ultimate in DIY pre-amps and takes note of news about an amplifier in a class of its own.

FIRST — the brickbats. My prize for most inappropriate act of the month goes to Discount Audio in Tottenham Court Road for having the atheistic gall to use an SME Series III as a display stand for a £5 transistor radio. May your fuses continually blow.

It was also amusing to note a Pioneer SA9500 offered for sale nearby, in the window of a large establishment of some repute. Nothing wrong with that you might say — except that is upside down. No doubt a new-fangled output stage is in use here — the electrons are propelled across the junction by gravity — only someone somewhere put the chips in the wrong way round.

Enough To Make You Blush!

For some time now Crimson Elektrik have enjoyed a good reputation based upon the excellence of their power amp modules. And quite right too. The amps are well designed and if assembled carefully offer very good sound reproduction.


The appearance of a pre-amp from the same stable thus aroused the editorial interest and a sample procured. The photo shows the board sat sitting alongside its PSU, and as is evident the PCB is built to a very high standard. The specs are faultless and well detailed, and also too long to give here. Versions are available for both moving coil and moving magnet cartridge types.

To say they come with instructions is probably misleading. Application notes in the best sense of the word are provided, and good detail on usage (and abuse) are given to enable the customer to adapt the modules to his own requirements.

All that's left to tell you is how they sounded — and that I'm afraid I cannot do properly until next month, simply because, as always, the modules arrived very late in the month and there was simply no time to conduct the tests demanded by a product of this pedigree. Initial impressions, however, are very very favourable. Sorry folks but I'm saying no more till next time. Same time, same page — November!

Raise Your Glasses

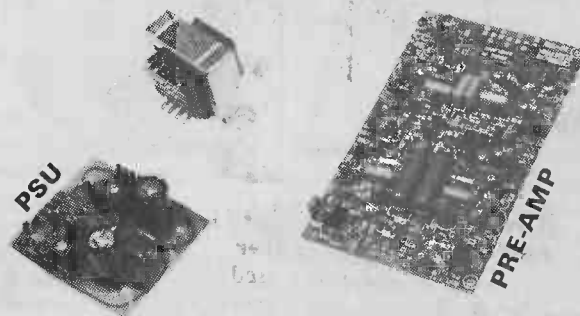One of the latest 'tuning' aids to appear on the hi-fi market are various types of turntable mat, which claim to improve the sound quality by offering more nearly ideal conditions for information retrieval from the LP. One of these that has risen to my eye from a small British firm, GA Audio, is composed of glass:



The collection of items which make up one Crimson Elektrik pre-amp. The large board on the right is the actual stereo pre-amp, the smaller one is the PSU stabiliser. To construct a separately powered pre-amp you need all three, but normally the pre-amp would be added to a Crimson power amp to produce an integrated unit.

With the success of the Planar 3 vaguely in mind, experiments with this refugee from a window frame were to prove interesting. It didn't take much to interest some other folks with inclination in this direction, and so a variety of turntables were available at various times to carry the mat.

Glass does have quite a few advantages for this sort of work if you think about it. It is extremely rigid, of good even mass distribution and of course easily kept clean. The felt mats which appear around so many spindles these days gather dust easier than booze attracts ETI staff and are infernally difficult to clean (as are ETI staff!).

By changing turntable mats around the overall sound from a system can be markedly altered — more so in my experience than with these 'super-cables' much vaunted of late as a cheap upgrade.

Turning Tables

The first machine we tried the 'Sound disc' glass mat on was a Technics SL 120 — a unit not much in favour with the musical mites of this world. However if the machine is properly sited on a wall mounted shelf, then its only real disadvantage is overcome that of being more sensitive to outside vibration than is perhaps needed. Used like this the SL 120 turns in a good all round performance and one that is not improved by use of a felt mat instead of the thick rubber platter provided. ►

However, the Soundisc *did* offer an improvement. The image was clearly improved and better defined. Best without the thin felt circle supplied by GA Audio, who would save themselves some money — and improve the product — by losing that completely and improving the instruction sheet instead. Spelling bass with an 'e' is just not *musical* lads, you can do better than that.

On a variety of other turntables, including the dreaded Linn, we found the Soundisc to offer variable results. On the Linn it seemed to make things worse, while it improved a Transcriptor Reference out of all recognition, to the extent that with the Soundisc mounted atop its little black blobs, the Reference came out sounding better than any other deck we tried (including you-know-what!)

A Painful Gain

Overall then the Soundisc is a good investment, unless you own a Linn or a Rega 3 where no gains can be expected. By supporting the LP properly the glass does appear to bring more information forth from the grooves, and to bring it forth more precisely. At its price of £10.30 I feel it's worth a try if you're unhappy with your present record playing system for reasons of clarity — but make sure it isn't the cartridge at fault first eh? Address: GA Audio, 82 Bromsgrove Road, Redditch, Worcs. B97 4RN.

H-bomb

From the States comes news of the first class H amplifier (Did I hear groans of "Oh no" from that weary music lover in the back row?) Like class G of Hitachi parentry H operates on the PSU.

This time, however, what is described as 'variable proportional analogue logic circuitry' (??) is employed to sense the line voltage needed by looking at the output power required at that time. A second power supply is also present, and is used to help beef up transients. If I were Hitachi I'd be looking pretty close at this little lot. Soundcraftsmen are guilty of class H, and the model number is MA 5002.


Is it now eyes down for I?

The Write Way To Do It

To all you nice people out there who have written in with questions for the Audiophile service — thank you and I hope I've answered you! Replies have been taking up to four weeks because there were so many of you. I've cleared the backlog now and replies should normally be return of post unless I get kidnapped, shot by bandits attacked by Felicity Kendal etc. (If the latter occurs allow 10 yrs for reply).


The service is still operating (just) so for newcomers: it is intended to be an enquiry service for matters relating to hi-fi. Please include full details of the system you're running and be as specific as possible. Address your envelopes to 'Audiophile,' ETI, 25-27 Oxford Street, London W1R 1RF.

ETI



TRAMPUS
ELECTRONICS LTD.

ELECTRONIC COMPONENT CENTRE
58-60 GROVE ROAD, WINDSOR, BERKS
SL4 1HS (TRADE AND EXPORT WELCOME)
HOTLINE FOR TELEPHONE CREDIT CARD ORDERS —
WINDSOR 54525



SEMICONDUCTOR DISTRIBUTORS ETI READERS OFFER: OVER £10 DISCOUNT 5% OFF. (THIS MONTH)
QUANTITY DISCOUNT FOR 100 OF ONE TYPE 10% OFF 1 UP PRICE

Cheque or cash orders over £5 Post Free. Other orders add 20p Post & Packing. Credit Card orders £5 min. by post or phone. + Post & Packing 20p. UK add 8% to prices marked. Add 12 1/2% VAT to all other prices. Free price list send S.A.E. All devices to makers specifications. Please quote ETI ad as prices may change. E.&O.E. 1978. Callers welcome Tues to Sat (Lunch 1-2).

MICRO POWER SUP- PORT	DISCO TRIAC 10A 400v	TRANSISTORS	7400N SERIES TTL
6"x4" Oil Board £2.25*	BR100 Diac 25p*	Look at our Pak T. Ten Plastic Power £1	ALL FULL SPEC BRANDED
PP3 or PP9 Clips. Pair 15p*	C1060 4A 400v SCR 55p*	Or Pak C: 4 x 2N3055 £1*	4000 15p* 4066 58p*
Oil Plugs. All 19p	TAG 1/400 lamp 55p*, 1/600 65p*	AC127 17p* 8FY50 16p*	4001 15p* 4067 £4*
Oil Sockets. All 10p	Switches Mini SPST 55p*	AC176 10p* 8FY51 16p*	4002 17p* 4069 22p*
Disc Strobe Tube £5*	Mini OPOT 69p*. Centre off 89p*	AC187 20p* 8FX29 28p*	4006 17p* 4070 32p*
DEVELOPMENT PAR- CELLS. All £5 each	Slide Switch 25p*	AF162 40p* MJ2955 £1*	4007 18p* 4071 21p*
SET 1: 250x50 volt Ceramic Capacitors 5% 10 each. From 22p to 0.1uf £5	Push-On 35p	AF239 42p* MJ340 44p*	4008 92p* 4072 21p*
SET 2: Tantals 1uf to 200uf 20v to 35 volt. Total 50 capacitors £5	FULL SPEC PAKS ALL £1	BC107 8p* MJ2955 £1*	4009 58p* 4073 21p*
SET 3: Electrolytic 25 volt 10 each (80) 1/2/5/10/47/100/220/1000 £5	Pak A: 12 x Red LEDs £1*	BC108 8p* MJ3055 80p*	4010 58p* 4075 23p*
SET 4: 1/2 watt Resistors 5% C.F. 10 each 10 ohm to 10 meg ohm. Total 500. Bulk packed in 1 bag £5	Pak B: 6 x 741C 8 pin £1*	BC109 9p* MPU131 35p*	4011 15p* 4076 £1.29*
SET 5: Zeners 400mw 5 each. 20 values 3 volt to 33 volt (Total 100) £5	Pak C: 4x2 M3055. T0 3 £1*	BC109C 15p* ORP12 35p*	4012 18p* 4077 40p*
SET 6: -100 Presets 10 off. SET 7: Heatsinks. 10 off. Each T018. T05. TV4 (T099) and small T0 3 £5*	Pak D: 12 x BC109 £1*	BC147 12p* TIP41A 60p*	4013 55p* 4078 21p*
PASSIVE GEAR	Pak E: 13 x BC182 £1	BC148 12p* TIP42A 65p*	4015 93p* 4081 22p*
Resistors 1/2 watt 5% CF 2p	Pak F: 13 x 2N3704 £1*	BC149 12p* TIP3055 60p*	4016 52p* 4082 21p*
Presets Type PR Vert 10p	Pak G: 7 x 8FY1 £1*	BC157 15p* TIP3055 50p*	4017 99p* 4089 £1.50*
45 Pots Log & Lin 25p	Pak H: 7 x 2N3819 ofet £1	BC158 15p* TI543 35p	4018 99p* 4093 85p*
CAPACITORS	New Pak I: 10 x Metal Trim. Knob 1/2" dia (synthesiser etc.) £1*	BC159 15p* 2N2646 39p*	4020 11p* 4507 55p*
Ceramic 50v 5% Hi Stab 22p to 0.1uf & 22/47 5p	Pak J: 6 x 2N3053 £1*	BC167 10p* 2N2905 22p*	4021 11p* 4508 £3*
Tantalum Caps 12p	Pak K: 50xIN4148 £1	BC168 11p* 2N3267 10p	4022 90p* 4510 £1.35*
ELECTROLYTICS 25 volt 1/10/47/100uf. All 10p	Pak L: 50 x 33uf 10 volt electrolytic £1	BC169 12p* 2N3053 16p*	4023 20p* 4511 £1.68*
(50 volt 20p) 220 or 470p 30p	Pak M: 4 x Pairs Plastic Power 2amp 60 volt. NPN/PNP B0131/2 Type £1	BC178 18p* 2N3702 9p	4024 76p* 4512 98p*
1000uf 25 volt 35p	Pak N: 50 x OA81/91 £1	BC182 10p* 2N3704 9p	4025 19p* 4514 £2.65*
KNOBBS. 1" dia & trim 15p	Pak P: 20 x Plastic 109 £1	BC183 10p* 2N3706 9p	4027 55p* 4516 £1.28*
HEAT SINKS. T05 & 18 9p*	Pak Q: 50 x 220uf 6.3v Volt Electrolytic £1	BC184 10p* 2N3819 18p	4028 90p* 4518 £1.05*
TV4 25p*. T03 small 25p*	Pak R: 14 x BC107 £1	BC212 12p* 2N3904 15p	4029 11p* 4520 £1.10*
	Pak S: 14 x BC108 £1	BC213 12p* 2N3906 15p	4030 58p* 4521 £2.68*
	Pak T: Top selling 10 x NPN Plastic Power 60 volt 2 amp B081 Type £1	BC214 12p* 2N3906 15p	4032 11p* 4522 £2*
		BC214 12p* 2N3906 15p	4034 £2* 4528 99p*
		BC214 12p* 2N3906 15p	4035 £1.20* 4534 £7.88*
		BC214 12p* 2N3906 15p	4038 £1.08* 4536 £3.60*
		BC214 12p* 2N3906 15p	4040 £1.05* 4541 £1.50*
		BC214 12p* 2N3906 15p	4041 86p* 4543 £1.75*
		BC214 12p* 2N3906 15p	4042 81p* 4553 £4.40*
		BC214 12p* 2N3906 15p	4043 96p* 4556 78p*
		BC214 12p* 2N3906 15p	4044 95p* 4558 £1.17*
		BC214 12p* 2N3906 15p	4046 £1.30* 4566 £1.59*
		BC214 12p* 2N3906 15p	4047 99p* 4569 £3.59*
		BC214 12p* 2N3906 15p	4049 52p* 4583 £1.10*
		BC214 12p* 2N3906 15p	4060 £1.15* 4585 £2.05*
		BC214 12p* 2N3906 15p	4063 £1.10*

TOP TROUBLE!

- 555 B Pin Timer 27p*
- 741C Full spec OIL 8. Branded Op Amp 19p*

NEW LINEARS Data 10p

- TL170 Hall effect 69p*
- TL071 Lo noise 741 75p*
- TL081 FET 741 69p*
- TL083 FET 87 41.49*
- TL080 FET 748/308 £1.15*

IC SUPERMARKET

- 301 Op Amp 30p*
- 555 Timer (NE555) 27p*
- 556 Dual 555 70p*
- 710 Comparator 40p*
- 723 Regulator 45p*
- 741C 8 Pin OIL DPA 19p*
- 741C T099 or OIL 14 39p*
- 748C Op Amp 35p*
- 3900 Quad Op Amp 55p*
- 7805 1 Amp 5 volt 95p*
- 7805 T03(309K) £1*
- 7808 or 7812 £1.25*
- 7815 15 volt plastic 69p*
- 7900 Negative Series £2.50*
- 8038 Sig Generator £3.55*
- 76013 & 76023 £1.35
- CA130 & CA3140 94p
- LM380 1 watt Amp 85p
- LM3801 Dual Preamp £1.55
- LM387 Dual Preamp £1
- LM3900 Quad OPA 55p*
- MC1310 Decoder £1
- MC1460, 1461 & 1469 93p
- MCMD5 14433, A/D £5*
- NE536 FET OPA £4*
- NE555 Timer 27p*
- NE556 Dual 555 70p*
- NE410 7w AF £1
- TB144 Radio 65p

DIL SOCKETS

Low Profile	8 pin	12p*	28 Pin	£1
	24 Pin	50p	40 Pin	£1.50
	14 or 16 Pin	15p		

AUDIO AND TEST EQUIPMENT CENTRE

MICROCOMPUTERS
LEVEL I AND II
TRS80 IN STOCK

ALL PRICES
INCLUDE VAT

Only regular stocks listed — other makes and models available.

Telephone your order with Access and Barclaycards



4D10A



DM235



TE20D

LONDON'S TEST GEAR CENTRE
OPEN 6 DAYS A WEEK 9 am-6 pm


SCOPES — IN STOCK

3" 5MHz single beam	92.50
4B10 5MHz single beam (4)	107.00
MS15 15MHz Batt/mains, portable	260.00
MS215. Dual trace version of above	290.00
4S6 Scope x 6MHz single beam	149.00
4D10A. Scope x 10MHz Dual beam	229.00
4D25. Scope x 25MHz Dual Beam	338.00
PROBES x 1 x 10 12.95 x 10 9.95 x 1 7.95. For 4S6/4D10A/4D25.	

EXCLUSIVE
New 5MHz mains
portable scope
now in stock
£92.50

LED AND LCD DIGITAL MULTIMETERS

DM235 Sinclair portable 3½ digit LED	52.99
PDM35 Sinclair Pocket 3½ digit LED (30kV Probes 15.95. Mains adaptors 3.75. OM235 carrycase 8.95)	79.95
LM3A 3 Digit Miniature with large LED displays	79.50
LM3.5A 3½ Digit Recharge Batts and charger 17 ranges	92.50
LM40A 4 Digit	136.00
LM300 3-digit Miniature battery operated 17 ranges	79.50
LM350 3½-digit with LCD displays 1µA/mV resolution	93.50

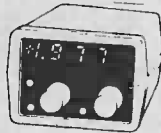

LM3.5A

MULTI-METERS — GENERAL PURPOSE & ELECTRONIC

Multi-Range Instruments featuring AC/DC volts, DC current, Resistance Ranges all with mirror scales except T1/IT1-2/T12/TM3A (TM3 AC volts only), some with AC current etc.	
TM11 incredible 120 Range Electronic Multi-meter	130.00
TM3B AC Micro voltmeter 3MHz > 4 Megohm	117.50
TM6B Broadband voltmeter 300kHz-400MHz	175.00
360TR 100k/volt 23 Range (plus transistor checker), Large scale	35.50
PROE 20k/volt 26 Range, Large scale	32.00
7081 50k/volt 36 Range Multi-meter	23.50
TMK500 30k/volt 22 Range Multi-meter (plus Continuity Buzzer)	21.00
680R 20k/volt 52 Range Pocket Multi-meter	34.50
7200 20k/volt 22 Range Double Multi-meter	17.95
Micro80 20k/volt 26 Range Pocket Multi-meter	17.90
IT1-2 20k/volt 16 Range Popular Multi-meter	11.95
LT22 20k/volt 19 Range Pocket Multi-meter with carry case	14.50
T12 5k/volt 13 Range Pocket Multi-meter	8.95
LT101 1k/volt 12 Range Pocket Multi-meter	7.50
EM2000 FET IC VOM 20 Ranges 10 Meg input	55.00
K200 FET VOM 38 Ranges	77.00
GT101, 20K/Volt 23 Ranges/Transistor Checker/Continuity Checker AVO 8s and a large range of replacement tests leads in stock	17.95

GENERAL EQUIPMENT

SWR50 SWR/Power Meter	19.50
LP30 30MHz Low Pass Filter	4.95
CX3A 150watt 3-way AE Switch	7.50
DC25kV 100 Meg HV Probe	11.95
8 Value CAP Subs Box	2.95
FX2000 Xtal Marker	3.90
LC1 Univ Logic Checker	11.95
CT1 Continuity Checker	26.00
MOD63 Signal Injector	21.00
TT169 In Circuit TR Checker	7.50
LB1 Transistor/Diode Checker	49.95
DRS10 35 Value Resis. Box	21.50
3101 Clamp Meter 0/1 K ohm. 0/150/300/	
600 AC Volts 0/300 Amp	32.95
C3042 SWR & FS Meter	9.95
MS319 2x100 Watt Audio Watt Meter	17.50
500V Megohmmeter 500 Megohms	48.00
1000V Megohmmeter 1000 Megohms	55.00
2 ½ Amp Variable Transformer	19.95
5 Amp Variable Transformer	33.00
10 Amp Variable Transformer	46.00
Decade Resis. Boxes:	
1-11, 110 ohm in steps of 1 ohm	29.70
10-111, 110 ohm in steps of 10 ohms	29.70
1-1,111, 110 ohm in steps of 1 ohm	38.00

GENERATORS

TG152 Series RC Oscillators	
Sine/Square output. 3Hz-300KHz	
TG152D	68.95
TG152 Dm (with meter)	89.95
TG200 Series RC Oscillators	
Sine/Square output. 1Hz-1MHz	
TG200D	93.85
TG200 Dm (with meter)	112.50
TG200 Dmp (Meter & Fine control)	117.50
TG66A Digital Sine Wave Decade control	249.50
TE22D (audio) 4 bands. Sine 20-200KHz.	65.00
Square 20-150KHz	65.00
TE20D (RF) 6 bands. 120KHz-500KHz	57.00

LOGIC PROBES AND MONITORS

LT2000 Economy Probe	11.95
LM1 Monitor	31.00
LP1 Probe 10MHz	33.48
LP2 1.5MHz	19.44

PIEZO HORN TWEETERS

Up to 100 watts each. No x-over reqd. Only .495 each (P/P 20p)

MICROPHONES, SPEAKERS AND COMPONENTS LARGE RANGE IN STOCK



TM11



TMK500



FM7 7 Digit 60MHz Rech. Batt. Freq. counter 140.00
SCS 512MHz Prescaler for above 72.50
MAX100 100 MHz 8 digit batt operated counter 83.75



TM3

CALL IN AND SEE FOR YOURSELF

AUDIO ELECTRONICS

301 EDGWARE RD., LONDON W2 1BN
01-724-3564. OPEN 9-6, MON-SAT.

ALSO AT 248 TOTTENHAM COURT ROAD, W. 1.

FREE CATALOGUE

SEND STAMPED (12" x 6" U.K.)
ADDRESSED ENVELOPE (MIN 9" x 6")
FOR YOUR COPY NOW

electronics tomorrow.....

by John Miller-Kirkpatrick

SOME months ago I mentioned a form of multi-voltage logic which was being developed by an American company. Recently I was discussing microprocessors with somebody, and they "invented" multi-voltage logic on the spot, after I told them that it had been done before they went on to discuss the ideas they had and with a few ideas of my own we came up with a logic system for the 1990s.

One problem with multi-voltage logic is that it is alien to the TRUE or FALSE logic used with binary or boolean logic. It seems that a logic system expressed in ten different voltage levels would be represented by 10 levels of possibility ranging from FALSE at zero volts to TRUE at 10 voltage units passing through REASONABLY TRUE at say 7 voltage units and SNOWFLAKE-IN-HELL at perhaps 1 voltage unit. Problems arise when you try to carry out logical operations such as ANDING 7 units with 1 unit — is the result $(7 + 1)/2$, $7/1$, $1/7$ or what "?" arithmetic is simple, it is even in decimal, for example 7 ADD 1 is undoubtedly 8 and 1 minus (Complement and ADD) 7 is 3 isn't it?

If you want to play with multi-value logic try using some CMOS devices run off about a 10v supply, CMOS switches from 0v to the supply voltage (near enough) and thus a CMOS output on this supply will switch from 0v to 10v. If the outputs in question are outputs from a 74C42 1 of 10 decoder then the outputs can be connected to a series of 9 resistors (all say 1K) arranged as a potential divider so that a common point will have a voltage of between 0v and 9v in 1v increments when the 74C42 inputs are driven from a BCD input. You now have a boolean to decan (?) logic converter, there are several methods of going the other way. One of the simplest methods is probably to use a set of transistors which will switch on at 10 different voltages (0-9) and then encode this with binary logic gates to give a 1 of ten and this BCD result.

Of course, you could simply use a variable power supply or two coupled to voltmeters, but somehow this seems to be cheating. Anyway, when you have your generator and readout device you can start to work out some of the rules involved in ten level logic — your ideas are probably just as valid as anyone else's. Perhaps you would like to send in any circuits or ideas to us at ETI so that we can publish them and start a whole new revolution in electronics.

Battery Logic

The logic generators described above could be run from a 9V battery and as they are simply CMOS, resistors and meters the current consumption would be very low. If you simply use some 9V batteries, switched potentiometers and meters as in the second example above you would not require any binary logic gates at all. Consider what is happening in this case (taking into account that I just passed "O" level physics and failed chemistry). The voltage in the battery is generated because of one of several types of chemical reaction, some alterations to this voltage may then be caused by logical or arithmetic operations and the result is used to activate a mechanical lever on an analogue voltmeter.

Would it be possible to use chemical reactions as logic elements and thus cut out some or all of the electrical interface. My knowledge of chemistry becomes obvious when I try to recollect the number of ways a chemical can be classified, one way is acid and alkali which I seem to remember are opposites. Surely a mixture of a percentage acidity could be mixed with another of a different acidity under certain conditions to create some form of logical combination which would be accurately repeatable? In which case the resultant could be used in another reaction to give a voltage output and/or a mechanical reaction?

If you consider the reactions of two complex chemicals such as hydrocarbons, nucleic acids, DNA and other things that I know little about, then the complexity of the logic operations which could be handled seems very varied. Having mentioned DNA perhaps I should point out that I see such chemical reactions taking place and being measured on a very small scale, nearly molecular rather than with 100ml beakers.

The microprocessor of the future may require feeding with sugar rather than any form of electricity, temperature and humidity may become more important factors than they are at present and it could get very upset if you spill hot tea on it. The output devices would of course be such things as a chemical print head working on pre-sensitised paper or tape (or screen), the input devices would measure chemical reactions on treated plates which would react to external chemicals such as the human skin. Increasing the memory capacity could be as simple as buying 1lb (500g) of fillet steak or even digging up a few carrots from the garden.

Although this may seem like mid-summer madness it could be a feasible alternative at some future date, after all, if you can operate on things like sugar, fillet steak and carrots (not necessarily together) then why not a microprocessor. Now there is a project for the NEB to invest £50million in!

Data Catalogues

When I first became interested in electronics as a hobby one of my main reference books was Henry's catalogue which was full of useful and seemingly useless items. The main attraction of the catalogue was the fact that there were many small but understandable circuit diagrams showing various applications of some of the more complex components. I based my very first digital clock circuit on the circuit by Dave Hunt in one of their catalogues and learnt a lot about digital electronics from what was effectively a sales catalogue.

Recently several manufacturers have donated their latest data books/catalogues to the JMK library (writing Electronics Tomorrow has hidden advantages). These data books are available (at a price) to anyone who cares to contact the manufacturers or their agents and together form a very comprehensive library of LSI components in and around micros, TV games, calculators and telecommunications. I can recommend all of the following books which are the ones I use now and are the latest in a series which I have used for several years now. I realise that several manufacturers other than those mentioned have similar books but these seem to cover a wide range and anyway I get these for free!

GIM produce a very comprehensive range of MPU, memory, clock, calculator, TV series, communications and industrial chips. The 1978 catalogue contains data on all of the TV games and interface circuits from the simple bat and ball to the complete home entertainment system. To take an example try looking up the data on the AY-3-1013 UART, the data, descriptions and applications for this IC goes on for about 15 pages and just when you think you have finished and just about exhausted UARTs you turn the page to find that GI also make a 1014, 1015, 1016, etc, with multitudinous options and alternatives on the basic design. The GI 1978 Data Catalogue costs £3.00 from General Instrument Microelectronics Ltd, 1-4 Warwick Street, London W1R 5WB. Tel. 01-439 1891.

Arming Intel

After a lot of arm twisting Intel were finally persuaded to part with their 1977 Data Catalogue which has a price of 2.50 dollars printed on it. This includes data on RAMs (including 2114), PROMs (including 2716), CCD memory, four MPU chips and associated components, Microcomputer systems and development systems. This book is a must for MPU addicts as Intel uses the "Microbus" approach on MPU add-on ICs which makes them usable on most MPU chips not just those made by Intel. After speaking to a young lady at Intel I am now informed that the 1978 catalogue is now available at £4.00 and that they can handle a few hundred orders easily but if everybody wants one . . . Intel are at: Intel Corporation UK Ltd, Broadfield House, 4 between Towns Road, Cowley, Oxford OX4 3NB. Tel (0865) 771431.

Naturally National

National Semiconductors would probably claim that their 1977 data books are so far ahead that their contents will remain current during 1978. Natsemi have a range of data books to cover their vast range of products including specialist books for linear, transducers and data acquisition. My library includes the 1976 Linear and 1976 TTL books and the 1977 issues of MOS/LSI (clocks, counters, watches, calcs, CB, COPS, displays, etc); Memory (you name it) and CMOS. The Natsemi CMOS book includes a 4000 series, the 74C TTL compatible series, some applications of these and also data and applications on many unique devices in the CMOS/LSI category. These latter include telephone diallers, TV clock/channel units, DVMs, A/D converters, display and keyboard controllers and 7 seg to BCD converters amongst many other clever and low-cost circuits which have the additional advantages of CMOS.

ETI

tech tips


Protection For Power Amplifiers

A. Hiley

In many amplifiers, the only protection against overload is a single fuse. Experience has shown that output transistors can blow faster than fuses. The simple circuit shown below will protect the amplifier in the event of a fault or gross overload.

Normally, the current through R1 biases both the transistors fully on. The P.D. across the LED is less than 2V, and it will not light up. In the event of a fault or overload, the current consumption of the amplifier will increase. The forward bias on the transistors will decrease, and they will tend to turn off. This will cause the potential across R to decrease, which will increase the bias on the transistors, turning them on again. The overall effect is that current limiting takes place. Under these conditions, the LED will light up, indicating a fault condition. If the fault or overload persists, the main fuse in the amplifier will probably blow. The actual protection circuitry needs no resetting.

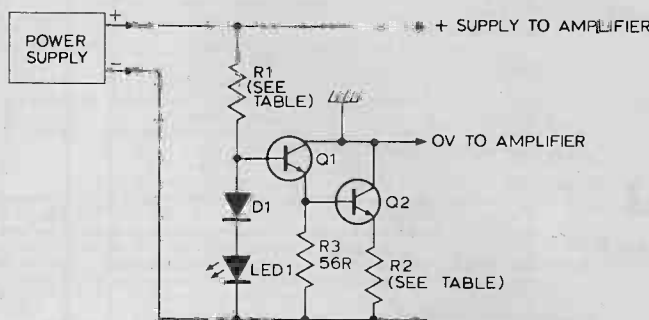Under fault conditions, the dissipation in Q2 will be very high, and so it must be bolted onto the chassis or the heatsink.



SUPPLY VOLTAGE	R1
10V to 22V	1k, 1/2 W
22V to 40V	1.8k, 1W
40V to 70V	2.7k, 2W

AMPLIFIER POWER (RMS Watts)	R2
15W, 8R or 4W + 4W, 8R or 4W, 4R	0.5R
60W, 8R or 15W + 15W, 8R or 15W, 4R	0.2R
30W + 30W, 8R or 30W, 4R	0.15R

NOTE


Q1 is BD131 (up to 45V supply) or BD139 (up to 90V supply)
 Q2 is 2N3055
 D1 is 1N914
 LED1 is a RED LED

Motorcycle Burglar Alarm


N. Hone

Currently available motorcycle alarms are either very expensive or ineffective. This circuit provides protection against theft, or tampering with the machine.

The alarm, a cross coupled latch is activated by a trembler switch (whose construction is shown), which will sound the alarm for 5 seconds before resetting. As the device is very sensitive, there is a 10 second delay (set by R2, C2) which gives enough time for the trembler switch to stop oscillating, and the keys to be removed. D1 and C3 prevent the supply to the circuit dropping when horn draws a high current and pulls the battery voltage down.

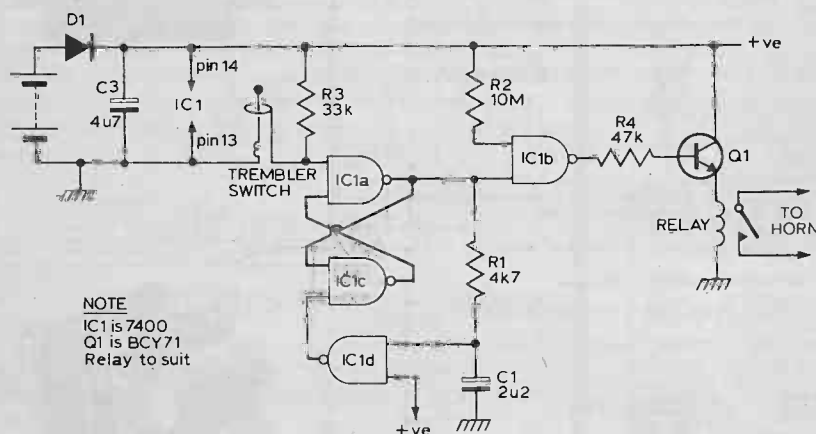

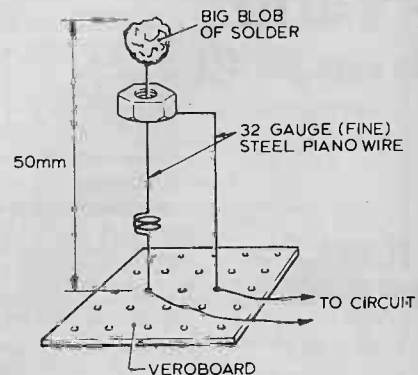NOTE
 IC1 is 7400
 Q1 is BCY71
 Relay to suit



Tech-Tips is an ideas forum and is not aimed at the beginner. We regret we cannot answer queries on these items.

ETI is prepared to consider circuits or ideas submitted by readers for this page. All items used will be paid for. Drawings should be as clear as possible and the text should preferably be typed. Circuits must not be subject to copyright. Items for consideration should be sent to ETI TECH-TIPS, Electronics Today International, 25-27 Oxford St., London W1R 1RF.

special

Audio Millivoltmeter


J. P. Macaulay

The circuit shown is of a very simple but effective and accurate millivoltmeter. The non inverting input is biased at half supply by the voltage divider R1/R2, decoupled by C2. The input impedance is defined by R3, whilst C1 isolates unwanted DC.

Due to normal op-amp action the inverting input follows any voltage present at the non inverting input. Because of this the current flowing through the meter, and the resistor selected by S1 is V_{RMS}/R . C3 prevents any DC flowing and hence makes offset nulling unnecessary.

With the component values shown the circuit has a flat response from 8Hz-50kHz (-3db) on the 10mV range. The upper limit remains the same on the less sensitive ranges but the lower frequency limit goes under 1Hz.

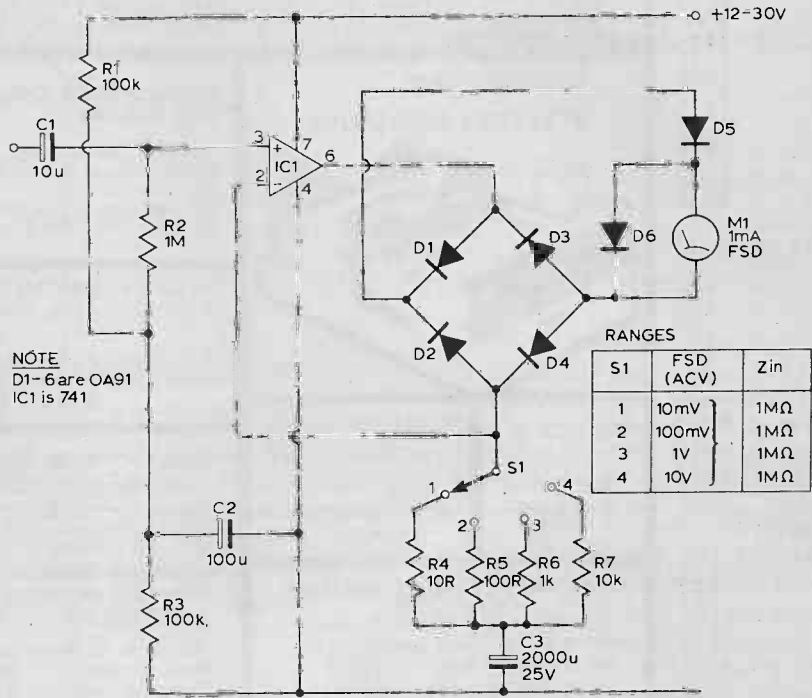D5 and D6 provide protection for the meter under reverse bias and overload conditions respectively. The circuit will work from supply rails between 12 and 30V, and in the quiescent state consumes only 2mA.




BCD Tone Generator

P. Bailey

When one of the binary codes in the table is set up on the data inputs, a corresponding preset connected to IC1 and 2 will be grounded, and the unijunction will start to oscillate. The frequency of oscillation depending on which output of the ICs is grounded.

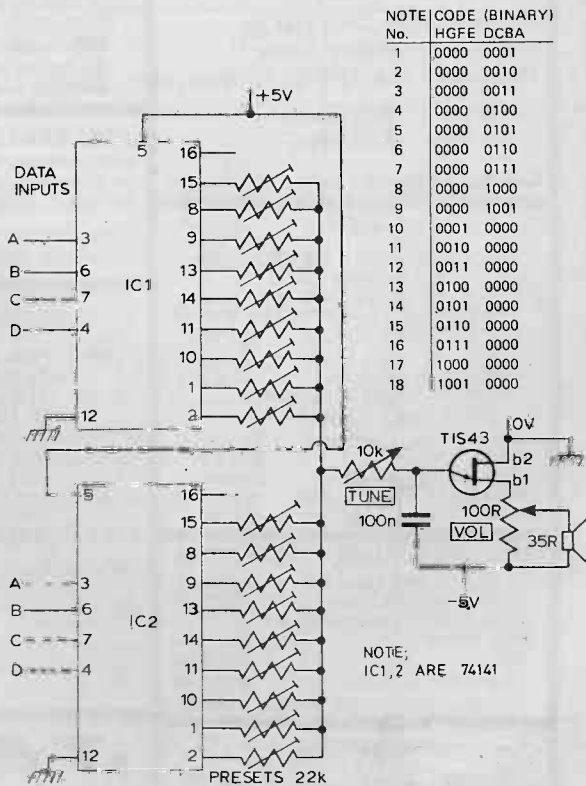If the 18 presets are tuned to form a chromatic scale and the inputs interfaced to your MPU data bus — hey presto you have a simple MPU controlled organ!



Temperature Control

S. H. Alsop


This circuit provides full phase proportion control of a heater, infrared lamp etc, uses no expensive transformers for its own power, and is extremely sensitive.

The LM3911 sensor is connected to the sensor via a 3 core cable, and enclosed in a rubber sleeve to enable it to be used as a probe. The output of the LM3911 varies by 10mV/°C and the minute change is amplified by the 741. Any increase in temperature will increase the output of the 741 which will lower the base current through Q1 and so reducing the constant charge current to C2. This variation of charge current with temperature will alter the time taken for the UJT to fire, changing the phase angle of the power to the load.

Peak Level Indicator

T. Norris

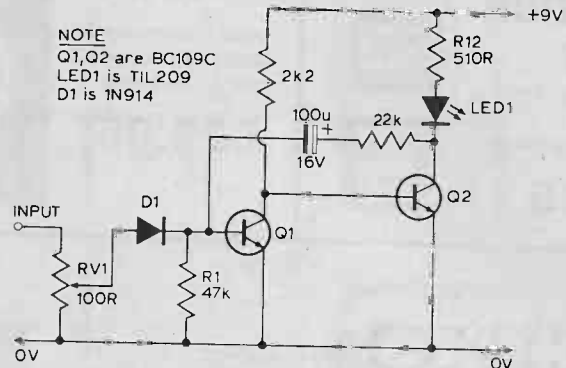
The diagram shows a simple monostable multivibrator with a LED which is normally lit, but will be briefly extinguished if the input exceeds a pre-set (by RV1) level. A possible application is to monitor the output voltage across a loudspeaker, when the LED will flicker with large signals.



NOTE
Q1, Q2 are BC109C
LED1 is TIL209
D1 is 1N914

The 5k lin pot is set to the temperature required and is linear over its entire range. The upper and lower

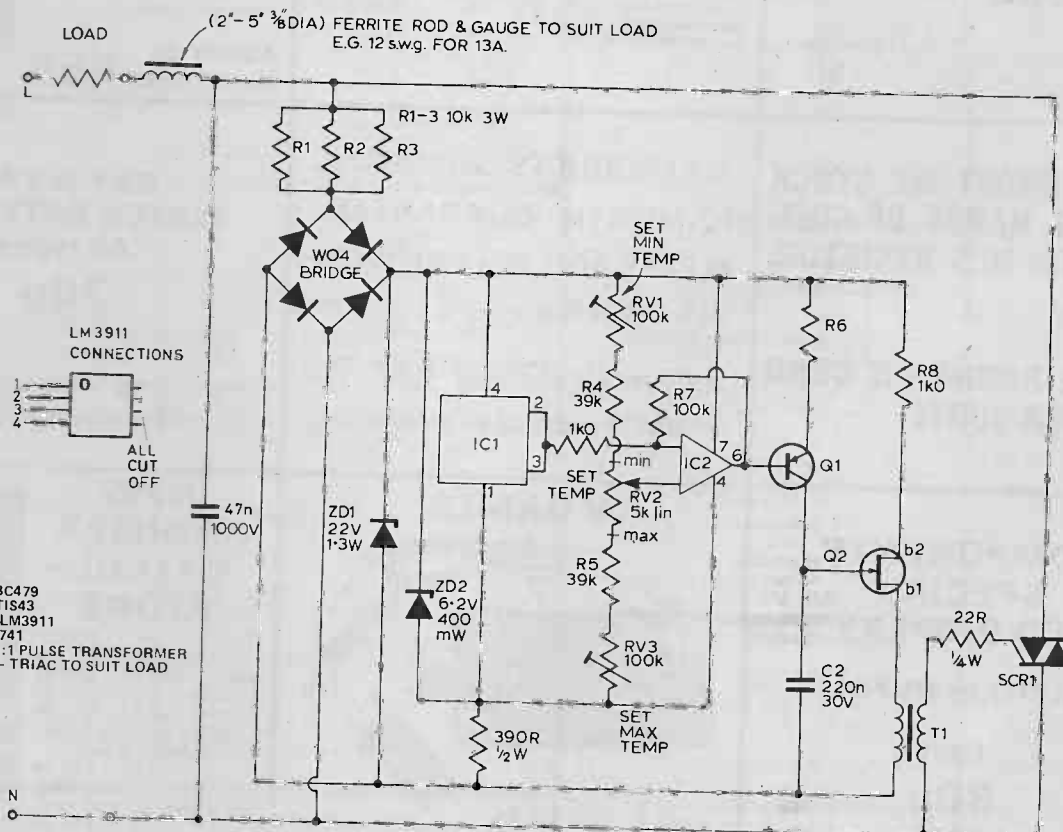limits of this control can be changed by adjusting the 100k presets.




NOTE:
Q1 IS BC479
Q2 IS T1S43
IC1 IS LM3911
IC2 IS 741
T1 IS 1:1 PULSE TRANSFORMER
SCR1 - TRIAC TO SUIT LOAD

Ni-Cad Charger Mod.

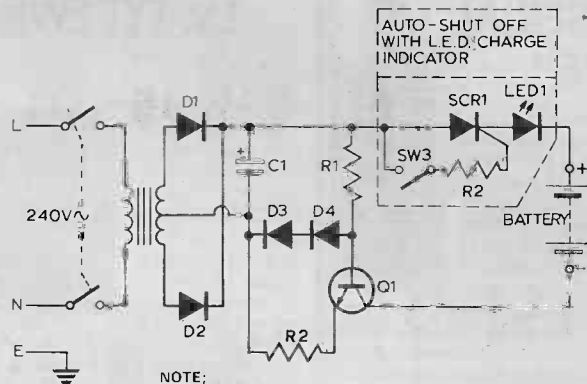B. V. Barton

This modification was made to the ETI 519 Ni-cad charger to protect the cells in case a power cut occurred while the cells were charging. Normally the cells on charge would rapidly discharge through the charging circuitry, causing possible damage.

The modification involved the addition of a low voltage thyristor in series with the battery. If power fails, the battery cannot discharge. When power is reapplied, the battery will not continue to charge until SW3 is closed momentarily.




NOTE:
LED1 IS TIL209
SCR1 ANY LOW VOLTAGE THYRISTOR
R2 SELECTED TO GIVE ONLY ONE
CHARGE RATE OF 45mA INSTEAD OF
SIX POSITION RANGE SWITCH GIVEN
IN ORIGINAL DESIGN

4 Channel Synthesizer

T. Huffinley

This circuit will synthesize two rear channels for 'quadraphonic' sound when fed with a stereo signal. The rear output for the Left channel, is a combination of the left channel input

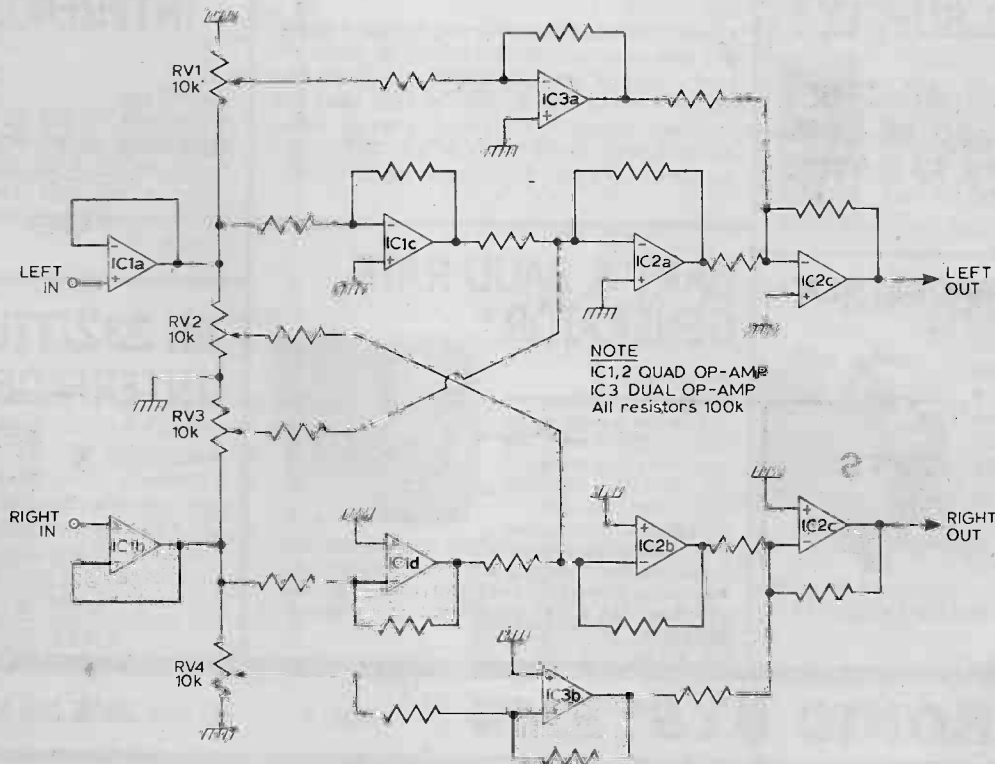180° out of phase, added to a proportion of the right hand channel (also out of phase). The right hand rear output is obtained in a similar way.




NOTE
IC1,2 QUAD OP-AMP
IC3 DUAL OP-AMP
All resistors 100k

Temperature to Frequency Convertor

P. Reynolds

This circuit uses the fact that when fed from a constant current source, the forward voltage of a silicon diode varies with temperature, in a reasonably linear way.


Diode D1, and resistor R2 form a potential divider, fed from the constant current source. As the temperature rises the forward voltage of D1 falls tending to turn Q1 off. The output voltage from Q1 will thus rise, and this is used as the control voltage for the CMOS VCO. With the values shown, the device gave an increase of just under 3HzC^{-1} (between 0°C and 60°C) giving a frequency of 470Hz at 0°C .

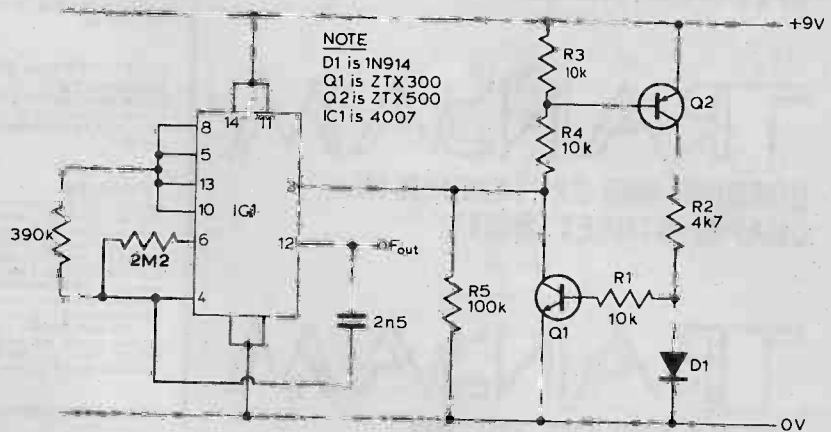

Lighting Effects

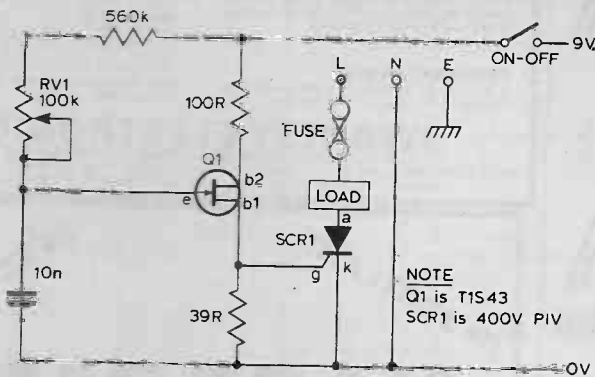D. Stewart


This circuit can be used to produce some interesting lighting effects. A unijunction relaxation oscillator is used to trigger the thyristor. The frequency of the oscillator is controlled by RV1. The load (a light bulb) will not be triggered at the same frequency as the unijunction oscillator, and some interesting effects can result. Care should be taken with this circuit as it is not isolated from the mains.




Logic Noise Detector

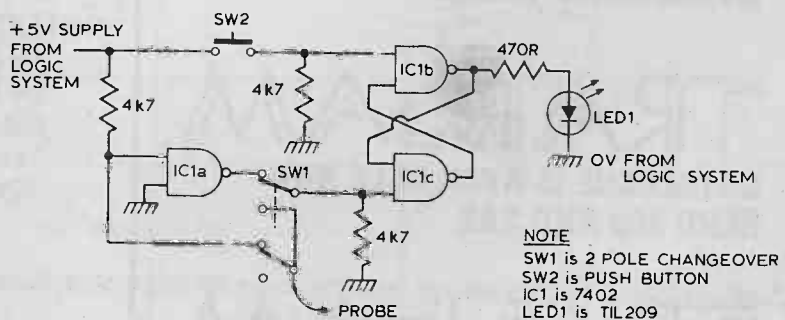G. Robinson

Ever since the advent of binary logic, spurious noise spikes and pulses have been the curse of the designers of even elementary systems. This circuit will help detect 'noisy' logic levels. With SW1 in position 1, any logic zero spikes occurring on a steady logic '1' will set the R-S latch and the LED will be illuminated. With SW1 in position 2, an extra inverter is brought in, and the circuit will be triggered by any logic '1' spikes.



WATFORD ELECTRONICS

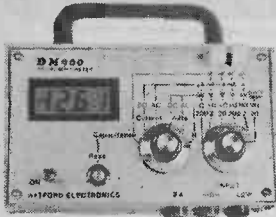

Introducing DM900 - The DIGITAL MULTIMETER with "Hidden Capacity" - It measures Capacitance too!

(as published in E.T.I. August 1978)
 Away with analogue meters for with some of these you may often as not use a crystal ball to make circuit measurements instead gaze into our crystal - not a ball but the 3 1/2 0.5" LIQUID CRYSTAL DISPLAY - on our amazingly accurate DMM incorporating:

- 5 AC & DC Voltage ranges; 6 resistance ranges
- 5 AC & DC Current ranges; 4 Capacitance ranges
- The prototype accuracy is better than 1%

This is a unique design using the latest MOS ICs and due to the minimal current drain, is powered by only one PP3 battery. There is also a battery check facility.
 The DM900 is an attractive hand-held, light weight device, built into a high impact case with carrying handle and has been ingeniously designed to simplify assembly.
 Never before have all these features been offered to the electronics enthusiast in a single unit.

Special introductory offer **£54.50*** (p&p insured add 80p)
 Calibration service charge for working Units **£5.75**. Readybuilt Units available by special order at **£78.50*** (p&p add 80p)
 (Optional extras, Probes **£1.50***; Carrying Case **£1.50***)
 (Demonstration on at our Shop)

JACK PLUGS		SOCKETS		
Screened chrome	Plastic body	open metal	moulded with break	in line couplers
2.5mm 12p	8p	8p	11p	12p
3.5mm 15p	10p	8p	13p	18p
MONO 23p	15p	13p	20p	18p
STEREO 31p	18p	15p	24p	22p

DIN	PLUGS	SOCKETS	In Line
2 PIN Loudspeaker	11p	7p	18p
3, 4, 5 Audio	13p	8p	20p

CO-AXIAL (TV)	PLUGS	SOCKETS	In Line
	14p	14p	14p

PHONO	PLUGS	SOCKETS	In Line
assorted colours	9p	5p single	15p
Metal screened	12p	8p double	—
		10p 3-way	—

BANANA	PLUGS	SOCKETS	In Line
4mm	11p	12p	—
2mm	10p	10p	—
1mm	7p	7p	—

WANDER	PLUGS	SOCKETS	In Line
3 mm DC Type	8p	8p	—
AC 2-pin American	15p	20p	—
	15p	15p	—

VOLTAGE REGULATORS	TRANSFORMERS*	ALUM. BOXES*	PANEL METERS*
TO3 Can Type p	6-0.6V 100mA 90p	WITH LID	FSD
1A +ve 5V, 12V, 15V, 18V 145	9-0.9V 75mA 95p	3x2x1 45	60x45x3.5mm
MVR5 or 12 180	12-0.12V 100mA 98p	2 1/2x5x1 1/2 65	0-50uA
1A -ve 5V, 12V 220	0-12-0.12V 150mA 140p	4x4x1 1/2 68	0-10mA
Plastic (TO92)	0-6-0.6V 280mA 160p	4x2 1/2x2 1/2 64	0-50mA
+ve 0.1A 5V, 6V, 8V, 12V, 15V 30	0-4.5-0.4.5V 0.5A 260p+	5x4x2 82	0-100mA
+ve 1A (TO220)	12-0.12V 0.5A 280p+	6x4x2 88	0-500mA
5V, 12V, 15V, 18V, 24V 85	0-12-0.12 0.5A 280p+	7x5x2 1/2 114	0-2A
-ve 0.5A 5V, 6V, 8V, 12V, 15V 95	15-0.15V 0.5A 260p+	8x6x3 148	0-25V
-ve 1A 5V, 12V 125	12-0.12V 1A 275p+	10x7x3 172	0-500mA
-ve 0.1A (TO92)	0-12-0.12V 1A 295p+	10x4x3 142	0-1A
5V, 12V, 15V 60	30-24-20-15-12-0.1A 1.2K Sec. 3.2Q 42p	12x5x3 165	0-300V AC
LM309K 135	Multi tappings 360p+	12x8x3 210	0-50V AC
LM320-12 165	30-24-20-15-12-0.1A 1.2K. Sec. 8Q 38p		0-300V AC
LM320-15 165	2A multi tap 445p+		"S"
LM323K 525	(Please add 48p p&p charge to all prices marked +, above our normal postal charge.)		"VU"
LM304H 240			475p each
LM317H 100			
LM317K 350			
LM325N 240			
LM326N 240			
LM723 45			

KNOBES*	HEAT SINKS*	COMPLEX SOUND GENERATOR
K1 Black Pointer type 9p	T092 8p	ETI Oct. 1978
K1a White Pointer type 11p	T075 8p	Parts now available. Send SAE for List.
K2 Slim Silvered Aluminium 12p	T018 8p	
K3 Satin Black Ribbed 22mm diam. 12p	T0220	
K4 Black Serrated Metal top with line indicator 35mm diam. 22p	T03 22p	
K4a As K4 but 25mm diam. 20p	T066 22p	
K5 Black Fluted, metal top & skirt, calibrated 0.9, 37mm diam. 28p		
K6 As K5 but with pointer on skirt 28p		
K7 Black Knurled, tapered, metal top & skirt. Calibrated 0-9 30mm 26p		
K7a As above but pointer on skirt 26p		
K8 Black or Silvered for Slider Pot 10p		
K12 Aluminium plastic with fine indicator, 22mm diam. 16p		
K19 Solid Aluminium Amplifier Knob Etchline indicator, skirted 22mm 30p		

74LS* cont.	86	43	157	76	259	160	245	270
26 48	90	60	158	96	261	450	247	190
27 28	91	104	160	128	266	52	248	190
28 48	92	89	161	98	273	244	249	190
30 22	93	89	162	138	275	250	251	134
32 27	95	116	163	118	279	66	253	142
33 39	96	116	164	114	283	192	257	110
38 39	107	54	165	75	290	128	258	146
40 28	109	55	166	226	293	128	384	86
42 98	112	55	170	288	295	185	386	86
47 98	113	50	173	105	298	168	390	230
48 120	114	50	174	106	324	240	393	230
49 49	122	70	175	110	325	290	395	218
51 24	126	70	181	398	326	294	396	215
54 28	127	180	183	286	327	286	398	276
55 30	128	60	190	140	347	148	399	230
63 150	132	60	191	140	348	186	399	230
73 46	136	95	192	130	352	228	445	150
74 41	137	85	193	130	353	228	447	144
75 48	138	85	194	166	365	65	490	180
76 40	139	85	195	136	366	65	668	182
78 80	145	100	196	100	367	65	669	182
83 115	147	170	197	140	368	66	670	248
85 118	156	96	242	232	377	212		
			243	232	378	184		
				232	379	215		

VOU Chip and MODULE for TV	KEYBOARDS*
Convert your TV into a VDU by using the new Thompson-CSF TV-CRT controller chip SF-F96364, 16 line by 64 characters text refreshment. Cursor management, Cursor management on screen, Line erasing. Compatible with any computing system.	Full Ascii Coded 56 Key
SF-F96364E £11.75*	
AY-3-1015 £5.60*	
AY-5-1013UART £4.50*	
71301 ROM £8.20*	
SFS80102 RAM £2.05*	
74LS163 RAM £1.18*	
LHF Modulator £2.50*	
Complete Module £136.50*	
(Send 30p stamps for full technical data)	
£45.50*	

... news digest.



feeling sporty?

Somewhere amid the teeming multitudes of watches that don't g tick in the night, this button ridden wristband from Casio appealed to us. Apart from the usual watch type functions the F100 is a 1/100S stopwatch with lap time facility. Depending on whether you go for the black case or the posh stainless one, it will cost you between £25 and £50.

rca has disc trouble

Oh for a standard that is a standard standard. Witness this latest piece of lunacy:


hang onto their own like grim death - if they take part in the talks at all - and thus create another battle which at best only one can win, and both will probably get clobbered in.

Sometime next year video discs will impact on our lives. Japanese firms are meeting to try and agree a standard format in an effort to avoid shades of four channel lunacy being seen again. So far so good. Unbelievably good in fact.

Informal talks are reported to have already begun in Japan and great interest being shown in combining both video and digital audio retrieval in one product. Good luck to those who would standardise and thus software nicely, and a plague of tolerance failures be upon those who would confound and confuse.

However just to be b...y awkward both RCA and Philips have their own totally incompatible systems all set to burst forth like over-ripe spots. It can be confidently expected that both will

stand before the bench

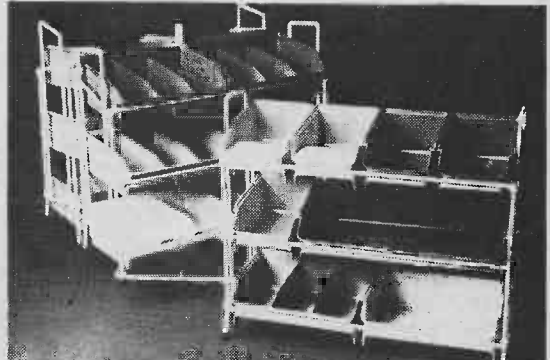

Although designed as a component handling system, it seems to us this little array would make a handy addition to the home constructors workbench. A wide array of bins are available and all


come in four colours to satisfy the houseproud or colour blind. Designated the 40-12-H it is produced by Link-Hampson Ltd of 5 Bone Lane, Newbury, Berkshire. Look ye thence for further details.

Exclusive OR and NOR gates

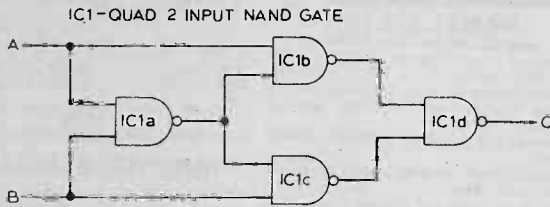D. S. Smith


When constructing logic circuits which need either an exclusive OR or exclusive NOR gate, and one is not available, the following arrangement

of NAND or NOR gates can produce the required results. The circuits can be constructed using standard TTL or CMOS gates.




TRUTH TABLE

A	B	C
0	0	0
0	1	1
1	0	1
1	1	0

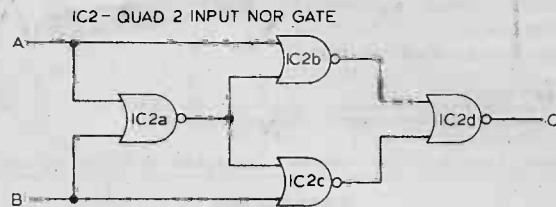


TRUTH TABLE

A	B	C
0	0	1
0	1	0
1	0	0
1	1	1

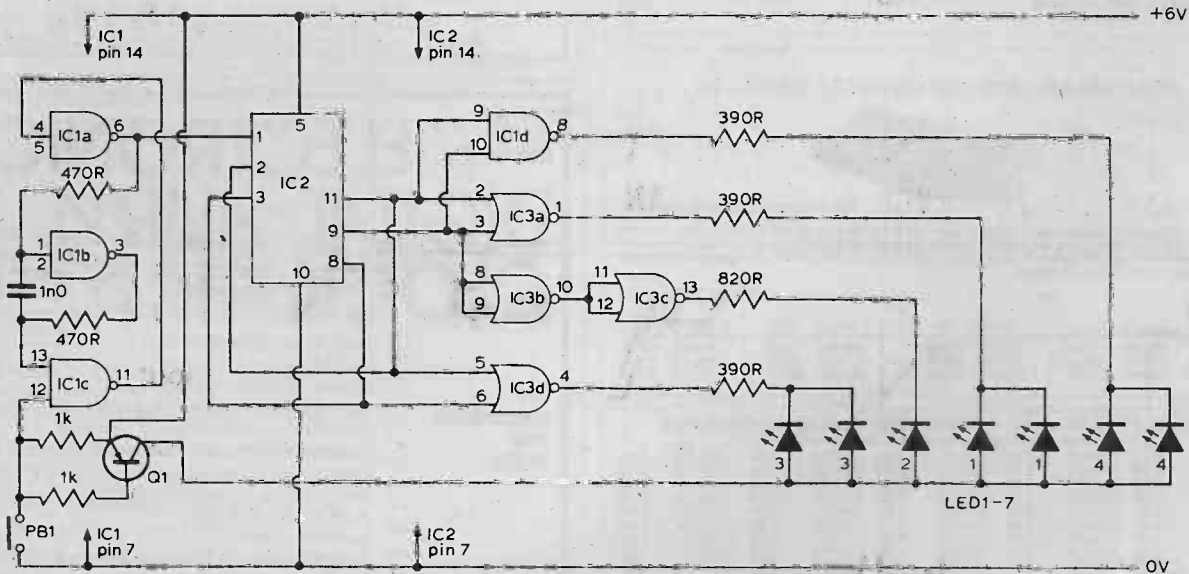

NOTE

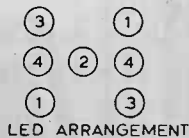LED1-7 are TIL209 or equivalent
 IC1 is 7400
 IC2 is 7493
 IC3 is 7402
 Q1 gen. purp. PNP $I_{cmax} > 50mA$
 PB1 is normally closed



Electronic Dice

G. Vance

This dice circuit is interesting, as the

six LEDs are arranged to produce a display the same as the dots on a dice. When PB1 is depressed, the display is blanked and the oscillator (IC7a, b, c) clocks IC2 at about 1MHz. IC2 counts

from zero and resets on seven. When PB1 is released, the display is enabled and a novel decoding system produce the correct output on the LEDs.

tech tips special


Test Unit for Sequential Logic

D. Rayner

Any one testing a sequential logic circuit requires input pulses free of contact bounce. This unit does this, providing two switched, jitter-free outputs and a 'slow' variable speed clock. The complements of these signals are also provided.

The components shown give the clock a frequency range of 1-200Hz. The clock's buffered output will drive up to two TTL inputs.

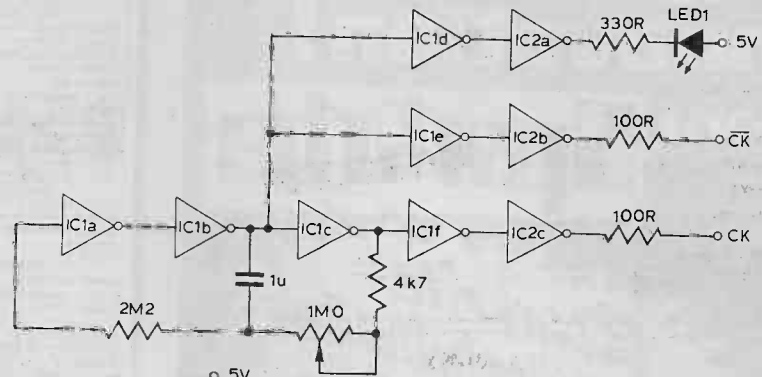The 100R resistors on all outputs provide some measure of accidental short circuit protection.



Speaker Power Indicator


J. Macauley

This circuit will indicate the peak level of an input signal applied to a speaker. It is primarily intended as a fail safe device when connected to an amplifier of higher power rating than the speaker.

The circuit is unique in that no separate DC power supply is required since the circuitry operates from the input voltage to the speaker.

R5 isolates the amplifier's output stage from possible fault conditions in the circuit. D1 to D4 full wave rectify the input signal and the resulting DC is used to supply the op amp.

The 741 is used as a comparator a reference voltage being obtained from across ZD3 and fed into the inverting input of the op-amp. The non inverting input samples the rectified input signal. When a peak is fed into the circuit the IC's output goes high and the led flashes. ZD1 prevents the LED turning on when the output of IC1 is low due to the output being unable to go less than 1.5V above earth under these circumstances. ZD2 defines the upper limit of the op amp's supply voltage in the presence of large transients whilst R2 is the current limit resistor. It should be obvious that the level at which the led lights is dependent upon the value of R3. The accompanying table shows the value required for this component for different input powers across an 8 ohm load. If different load values are to be used for the speaker the value of R3 can be determined from the equation,

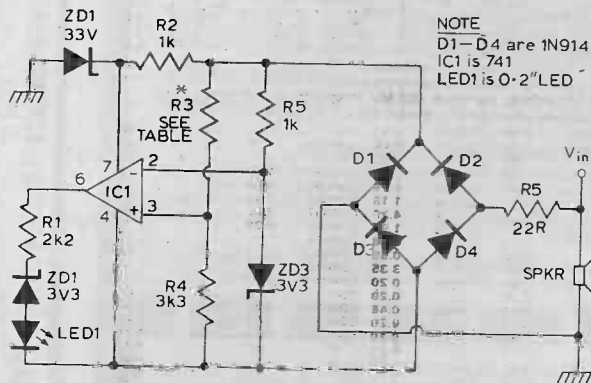


WATT/8Ω	5	10	15	20	25	30	35
R3kΩ	5·6k	9·1k	12k	15k	16k	18k	22k

$$R3 = 1.4 \sqrt{PR} - 3.3 \text{ k}\Omega$$

$$P = P_{out}$$

$$R = \text{load in } \Omega$$

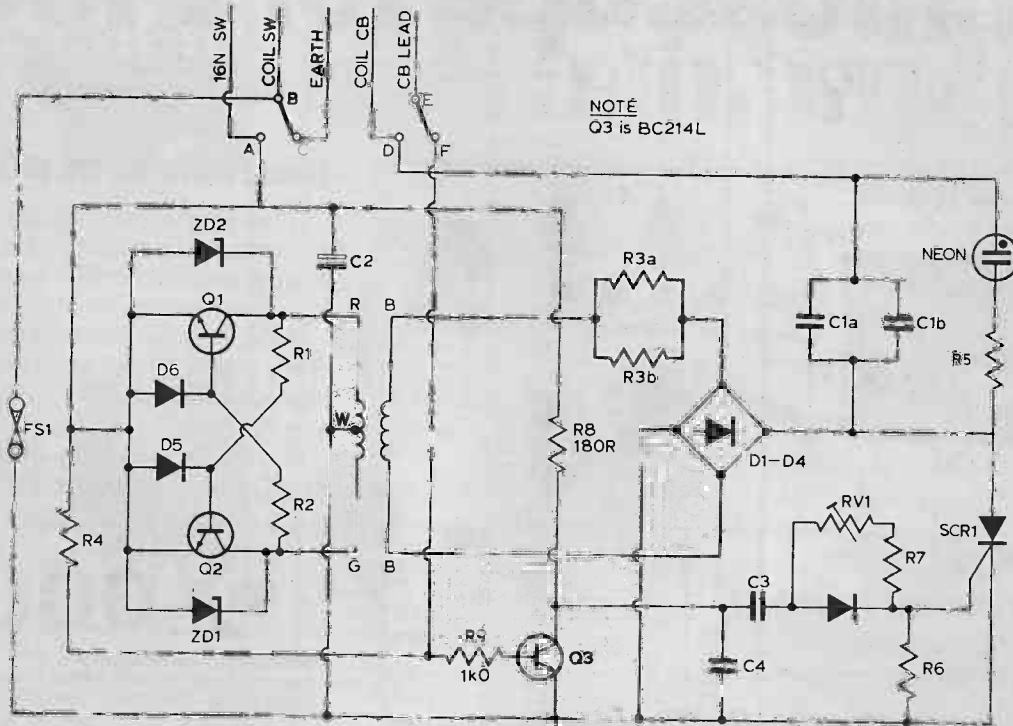

CDI for Positive Earth

R. Vivian

The CDI Mk II ignition published in the May issue has been designed for

negative earth cars. Attempting to install it in positive earth vehicles by reversing the supply connections will lead to problems caused by SCR1 triggering as C3 is discharged (ie as the contact points close, and not as they open).


This modification provides a solution by discharging (C3) through a transistor (Q3) which conducts when the points open. Any general purpose PNP transistor capable of sinking 200mA (eg BC212, BC214L) will do.

Brake Fluid Indicator

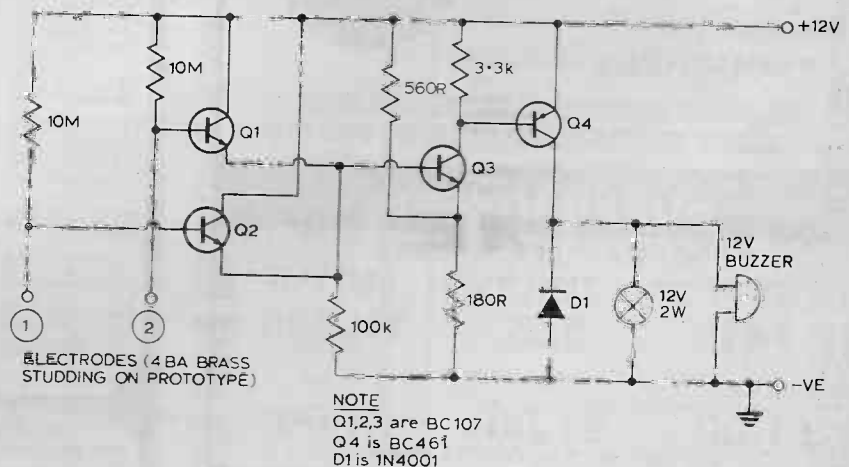D. Shorthouse

This circuit indicates by means of a warning light and a buzzer when the fluid in the tank of a braking system is getting low.

Normally both electrodes are immersed in the brake fluid, and the bases of Q1 and Q2 are at ground potential (the fluid makes a connection between the electrodes and the brake cylinder which is connected to the car chassis). If the fluid level should fall, and either of the electrodes becomes dry, Q1 or Q2 will turn on which will turn on Q3 and Q4 and the alarm energised.



COMPLEX SOUND GENERATOR

Not quite a synthesizer, but more than your average stylus organ — that's the ETI project team's musical offering this month

WHILE WE WOULD not claim that our Minisynth is the latest in polyphonic synthesizers (It'd never stand up in court) we want to emphasise that this is definitely not another in the never ending stream of Rolf Harris multivibrators.

Complex Chip, Easy Sound

The project is based on a new sound generator IC from Texas Instruments. This device has an on board VCO, low frequency oscillator, noise source, envelope generator and a number of mixing circuits.

The final instrument can be used to provide a number of sounds, some musical, some not. You can use it to entertain, or, in case of those of us whose talents lie in fields other than music, annoy friends and foe alike.

Construction

Construction of the project is relatively straight-forward. Carefully follow the component overlay, as usual, noting the orientation of all electrolytic and tantalum capacitors. It makes sense to use IC sockets for the three ICs.

Before starting construction of the electronic components it might be an idea to tin the keyboard area in order that a more reliable contact is made.

Tinning can be carried out by coating the 'keys' with blobs of solder, heating the whole area up (large soldering iron required — we hope you won't use this for the rest of the construction) and quickly wiping away excess solder with a wet cloth.

The probe can be fashioned from an old biro, which has had its innards replaced by a wire that is connected to the original pall point.

The choice case for the project is much up to personal taste. We put our instrument in a case we made ourselves from thin plywood, painted black.

Playing With

The only way to become familiar with the Minisynth is to sit down with the instrument and play with it. This is a painful experience for all concerned and while it won't make you blind could well make you deaf if


the volume is up too far. Some of the sounds produced at this stage are, to say the least, gruesome and for the sake of all concerned this learning period should take place in private. You can expose your talents when the mechanics of playing the machine have been mastered.


A good starting point for the controls is to set the DURATION, ATTACK and DECAY controls to minimum, the SLF OSCILLATOR's course control to the highest frequency range with the fine control set at minimum. Set the VCO and NOISE controls to their mid points and all the MIXER switches down (towards you) — this will select the output from the main VCO. The ENVELOPE/CONTINUOUS control should be down and the OSCILLATOR/KEYBOARD control away from you.

Switching the instrument on should produce a note, the frequency of which can be altered by the VCO control. At this stage the note will be unaffected by the keyboard.

By moving the OSCILLATOR/KEYBOARD control to the down position the Minisynth can be played via the keyboard, the VCO control as a tune facility.

With the ENVELOPE/CONTINUOUS control in its present position the note selected by the keyboard will be maintained until the probe is removed from the keyboard. Moving the switch to the up position will mean that the notes selected will be modified by the output of an envelope generator. The envelope generator is set up by the DURATION, ATTACK and DELAY controls. The control functions are self-explanatory, the only point to

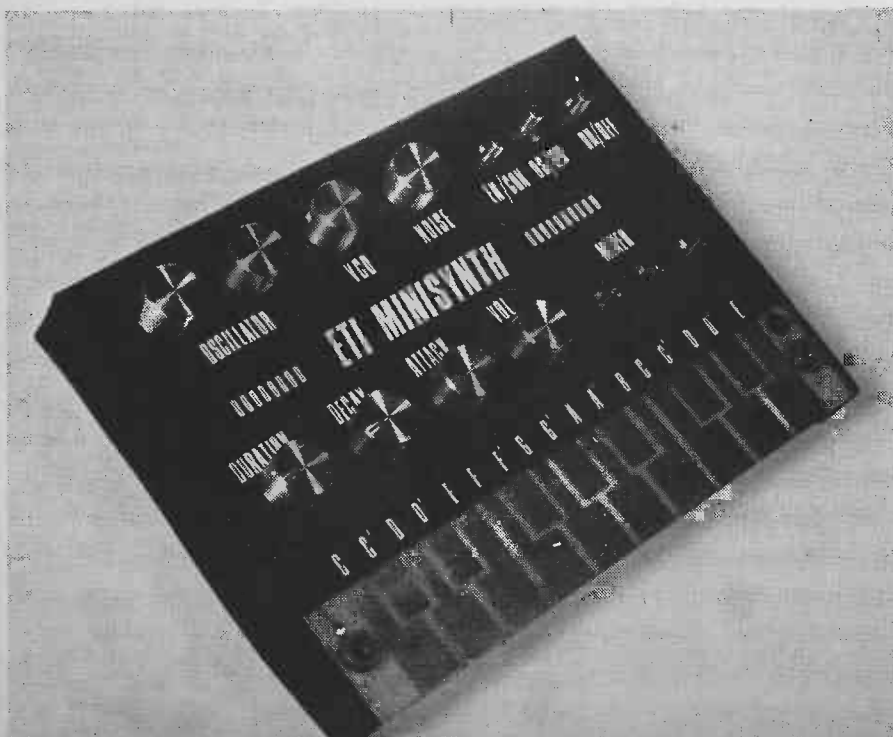

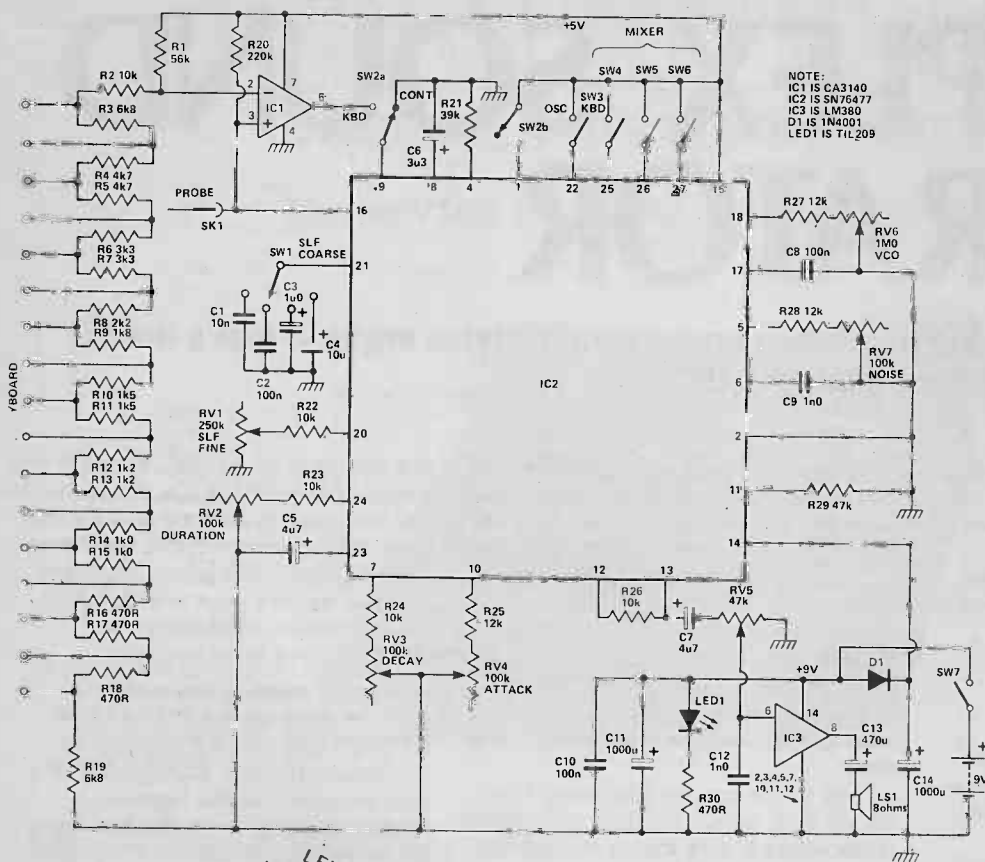

The SN76477 IC that forms the basis of the project is a bipolar/1¹/₂L device that provides VCO, low frequency oscillator, noise source a filter, an envelope generator plus various other mixing and control logic all in a 28 pin D package. The block diagram shows the inter-arrangement of the various blocks within the IC and the pins to which external control networks are connected. For full data on the device consult the data sheet published in February ETI.

Although the SN76477 does most of the work, we require two additional ICs, IC3 provides adequate audio output and IC1, which forms part of the keyboard circuit — the section we shall now look at in detail.


VCO and Keyboard

A voltage applied to pin 16 of IC2 will, if the external VCO select (pin22) is Low, determine the frequency of oscillation of the IC's on channel VCO. The Higher the external control voltage the lower the frequency produced. The range of the VCO is internally set at a ratio of 10:1, with the minimum frequency of operation is determined by C8 and by the series combination of RV7 and RV6(tune). The duty cycle of the oscillator is set at 50% by leaving pin 19 open.

The external control voltage is derived from the potential divider chain formed by resistors R1-R19, the particular value being tapped off by the stylus.

IC1 provides an indication that the stylus has touched the keyboard. The inverting input (pin 2) of IC1 is held at a voltage that is determined by the ratio of R1 to the sum of R2-R19. When

Fig. 1 (above) circuit diagram of the Complex Sound Generator. Fig. 2 (below) component overlay

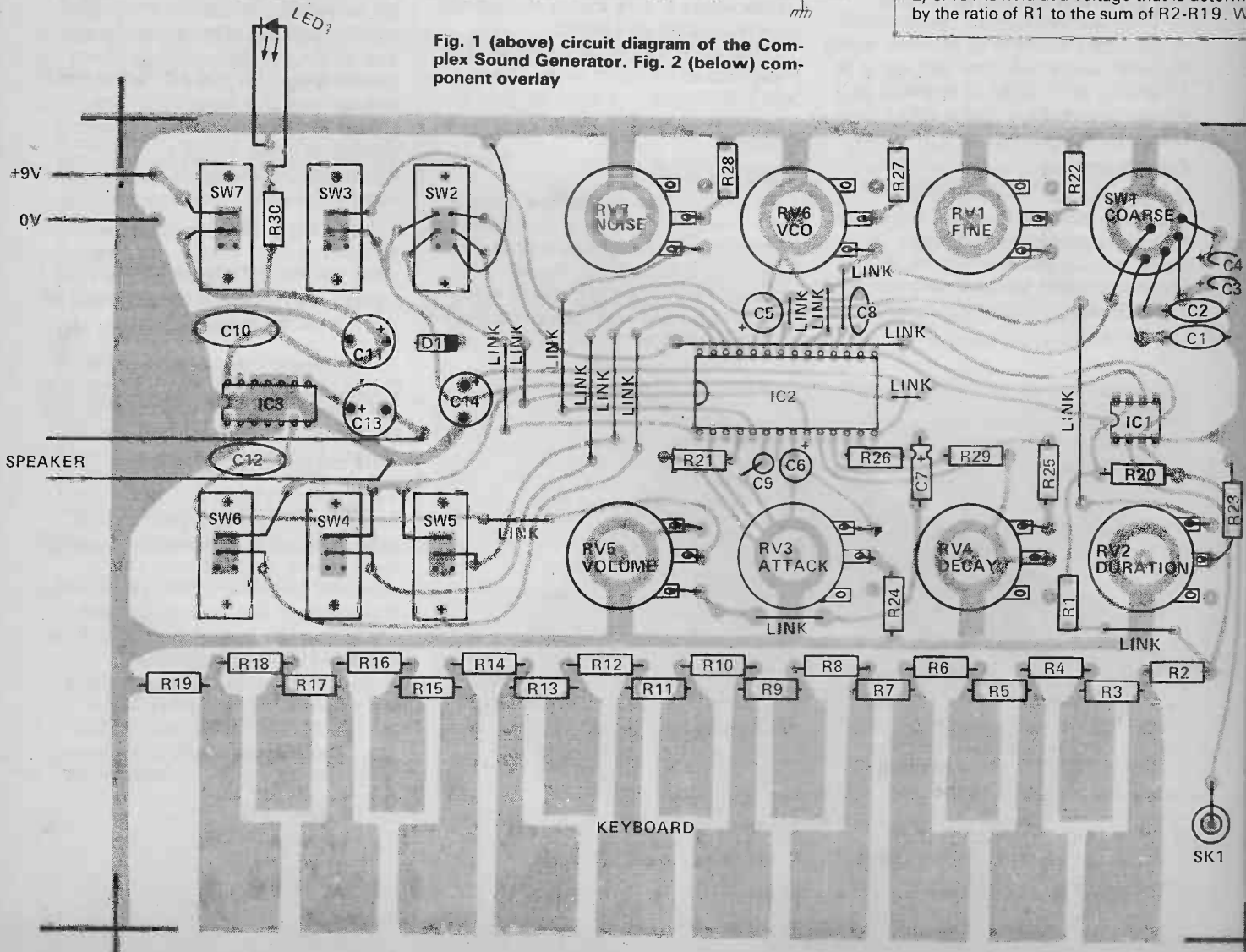

HOW IT WORKS

the stylus is not in contact with the keyboard R20 ensures that the non-inverting input (pin 3) is above this fixed voltage, the output of IC1 is thus high.

As the stylus touches the keyboard, the voltage at pin 3 will be pulled down to a level below that on pin 2 by the relatively low impedance voltage determined by the lower leg of the resistor chain. This will cause the output of IC1 to go low. The output of IC1 is taken to SW2a which selects either this signal or 0 V as the output to pin 9 of IC2.

Pin 9 is the system enable input. IC2 is inhibited when this pin is held high, taking it low enables the various sections of the IC. The transition of this pin from high to low (IC1's action as the keyboard is touched) also initiates the one shot logic (enabled by SW2b) that can provide sounds of short duration — this is described in detail below.

SLF Oscillator

The on chip VCO, as well as being controlled from the external voltage derived from the potential divider chain, can be modulated by an on chip Super Low Frequency oscillator. The VCO is controlled by this oscillator when the VCO select (pin 22) is high.

The SLF can be operated in the range 0.1-30 Hz, the particular frequency being set by the capacitors C1-C4 (selected by SW1) and by the combined resistance of R22 and RV1 (oscillator fine).

As well as providing a sawtooth output for control of the VCO, the SLF oscillator provides an output that is taken to the mixer section of IC2 described below.

Noise Generator and Filter

The on chip noise oscillator's input is taken, via R21, to ground. This sets up the conditions for correct operation of this section the output of which is fed to a noise filter. This modifies the noise generator's output by reducing the high frequency content of the signal. The specific 3dB point is set by C9 and by the value of R28 and RV7 (filter) in series.

Mixer

Outputs from the noise filter, VCO and SLF oscillator are fed to a mixer circuit. This combines the three signals in a manner determined by the logic levels on pins 25, 26 and 27 of the IC2 (mixer select). The particular output or combination of outputs corresponding to the eight possible states of these pins is shown in table 1. The output of the mixer is fed to the envelope generator and modulator.

It should be noted that as opposed to TTL ICs, unconnected inputs of the SN76477 assume a low state.

One Shot Logic

The one shot logic is used to provide sounds of a short duration. The circuit is triggered by a negative going edge on the system enable input, the duration of the "one shot" being determined by C5 and R23 plus RV2 (duration).

ADL

The attack/decay logic determines the envelope of the IC's output controlling as it does the envelope generator.

The attack/decay characteristics of the output are determined by C8 in conjunction with R25 and RV4 (attack) and R24 and RV3 (decay).

The ADL mode is selected by logic level signals on pins 1 and 28. In our circuit pin 28 is left unconnected while pin 1 is taken to SW2b. This selects the output of the one shot when held high and of the VCO when taken low.

Envelope Generator and Modulator

The output of the envelope generator is taken internally to an on chip amplifier the gain of which is set by the ratio of R26:R29. The output of the amplifier appears at pin 13 and is taken via C7 and the volume control RV7 to IC3 an LM380. This IC acts as a power output stage. C11 ensures that the LM380 is stable under all operating conditions, while C12 provides DC isolation between IC3's output and the loudspeaker LSI.

Output Amplifier

The 9 V input is used to power IC3 directly and is then taken via D1 (to drop 0.6 V) to pin 14 of IC2. This is the input to an internal voltage regulator that powers the IC and also provides a stable 5 V at pin 15 for use elsewhere in the circuit. C10, C11 and C14 provide supply decoupling while LED1, together with current limiting resistor R30, provide an indication that power is applied to the circuit.

Power Supply

The 9 V input is used to power IC3 directly and is then taken via D1 (to drop 0.6 V) to pin 14 of IC2. This is the input to an internal voltage regulator that powers the IC and also provides a stable 5 V at pin 15 for use elsewhere in the circuit. C10, C11 and C14 provide supply decoupling while LED1, together with current limiting resistor R30, provide an indication that power is applied to the circuit.

PARTS LIST

RESISTORS (all 1/4W 5%)

R1	56k
R2,22,23	
24,26	10k
R3,19	6k8
R4,5	4k7
R6,7	3k3
R8	2k2
R9	1k8
R10,11	1k5
R12,13	1k2
R14,15	1k0
R16,17,	
18,30	470R
R20	220k
R21	39k
R25,27,	
28	12k
R29	47k

POTENTIOMETERS

RV1	250k linear
RV2,3,	
4,7	100k linear
RV5	47k log
RV6	1M0 linear

CAPACITORS

C1	10n polyester
C2,8,10	100n polyester
C3	1u0 35 V tantalum
C4	10u 35 V tantalum
C5,7	4u7 10 V electrolytic
C6	3u3 35 V tantalum
C9,12	1n0 polystyrene
C11	1 000u 16 V electrolytic
C13,14	470 16 V electrolytic

SEMICONDUCTORS

IC1	CA3140
IC2	SN76477
IC3	LM380
D1	1N4001
LED1	TIL209

SWITCHES

SW1	single pole, four way rotary
SW2	DPDT
SW3-7	SPST

MISCELLANEOUS

PCB as pattern, case to suit, probe, 8 ohm loudspeaker, battery eliminator.

BUYLINES

All the components except IC2 should be widely available while IC2 will be stocked by Watford, Technomatic and other Texas suppliers. Watford are also to supply a complete kit for the project.

We do not have enough space to reproduce the foil pattern but it will be available on ETIPRINTS or can be obtained by sending an SAE to our offices. Please mark your envelope Complex Sound Foil Patterns.

note is that because the Minisynth does not have a sample and hold facility in the keyboard section, the note required must be maintained throughout the period of the envelope.

The mixer controls select the

outputs from the various noise sources and oscillators on the instrument. At present it is the output of the main VCO that we are hearing. By setting the ENVELOPE/CONTINUOUS control back to its former position and

moving the leftmost mixer control up the output from the SLF OSCILLATOR can be heard. This oscillator is controlled by the fine and course controls at the top right hand corner of the instrument.