

ELECTRONICS TODAY

electronics today international

AUGUST 1976

30p

SOUTH AFRICA 60c
CANADA \$1



HEADPHONE RADIO

**LOW
COST
VDU**

IT'S BARGAIN MONTH IN ETI
SEE CENTRE PAGES

5 FUNCTION: £18.95



NEW COMPONENT SERIES
SOUND LIGHT FLASH TRIGGER
HIGH POWER BEACON
UNIVERSAL TIMER
RTV CASSETTE REVIEW

NEWS . . . CONSTRUCTION . . . DEVELOPMENTS . . . AUDIO

INTRODUCING

3 Established Names to ETI Readers!

AMATEUR RADIO BULK BUYING GROUP


- Since our inception we have always aimed at giving the following 5 STAR service:
- ★ All components are brand new to manufacturers' full specifications.
 - ★ All components carry manufacturer's full guarantee.
 - ★ Orders normally despatched within 48 hours of receipt.
 - ★ Full refund offered on any item not in stock.
 - ★ All prices include V.A.T.

This service is difficult to match — join the many who now take it for granted.

The aims of the Amateur Radio Bulk Buying Group are simple. To help the construction side of the hobby by endeavouring to bring some of the more "difficult-to-get" components to you and to act as agents for some of the leading manufacturers in this country and abroad. All our regular items are brand new from current manufacturers' stock carrying full warranty. Semiconductors are generally from top British and American names such as Motorola, Mullard, National, Plessey and R.C.A., etc. In addition to selling **Jaybeam** VHF aerials, **Microwave Modules** converters, etc. and **Mini-Beam** H.F. aerials we are also the leading U.K. supplier of **Plessey SL600** series i.c.s., **KVG crystal filters** and a wide range of ignition suppression components for car radio use.

CATRONICS is the name of our own designed and produced equipment and specialised kits, Amateur Radio Bulk Buying Group is the name of our Amateur Components Division.

180 MHz DIGITAL FREQUENCY METER

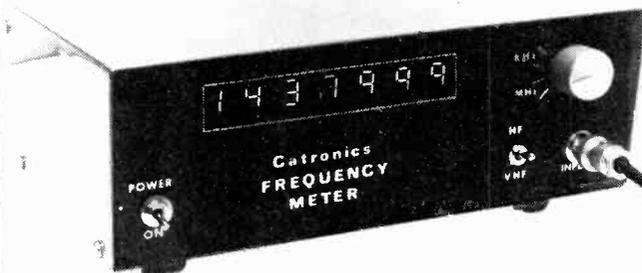

Enabling frequencies up to over 180 MHz to be read directly. It is now possible to measure frequencies on all bands from 160m. 2m. without any range switching, input level control adjustment or other operation. Additionally a low frequency position may be switched to, enabling audio frequencies and I.F.s to be read directly. This is a 7-digit model with 4-speed time base having gate times of 10S, 1S, 100mS, and 10mS with built-in automatic memory. Reading is displayed for 100mS plus gate time and then changes to display new reading from the integrated circuit memory. This gives a "non-blinking" continuous display even when using long gate times. The display is by long-life seven segment indicators giving a direct frequency reading in four ranges (2 for kHz and 2 for MHz) with automatically positioned decimal point.

The frequency accuracy is determined by a precision 10 MHz master oscillator having a stability of ± 2 ppm over the normal ambient temperature range.

Power supply is stabilised 240v. input unit, although operation from 12v. battery supply (-ve earth) can be arranged.

The instrument is housed in an attractive two-tone metal cabinet approx. 9in. x 3 1/2in. x 6 1/2in. Write for full specification.

Price only £130 plus £1.50 insured carriage. 25MHz only version also available — model DFM3 — £110.

CRYSTAL CALIBRATION

Catronics model M6 giving outputs at 1 MHz, 200 kHz, 100 kHz, 50 kHz and 25 kHz at the flick of a switch, with harmonics audible up to 2m band. 6 volt supply. Complete PCB module, accurately set to frequency and switch assembly — £8.90. Also available — kit of parts for regulator for operation on 9 to 20 volt supplies, £1.60.

Complete boxed unit with battery — £14.50 plus 50p p.p.

PRINTED CIRCUIT BOARD ETCH RESIST PEN


Make your own PCBs with a Decon Dalo etch resist pen — only 85p from us including full instructions for use

We also sell Ferrites, Mini-tron 7-segment indicators, plus a wide range of transistors and i.c.s. including Plessey SL6000 series.

See the above and other new products on our stand at the Radio Communication Exhibition, Alexandra Palace on July 30 — August 1st.

Send s a e for full price list or 30p plus large 1 1/2p S A E for your copy of our Data-Catalogue. All our prices include VAT at current rates. Please note our minimum U.K. post and packing charge, except where indicated is 15p. Export orders welcome — write for export price list. Please make cheques payable to Catronics Ltd. or VHF Communications, as appropriate.

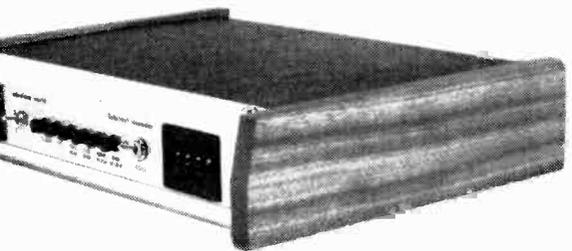Administration address (Callers by apptmt):
39 POUND STREET, Carshalton, Surrey.
Tel: 01-689 6701 (9 a.m. to 6 p.m., 1 p.m. Sat.)



TELETEXT DECODER KIT

CATRONICS Ltd. offer the world's first kit for the Home Constructor for decoding and displaying the CEEFAX and ORACLE television information display systems. The design of this decoder is being described in a series of articles being published by "Wireless World" (from November 1975 issue).

The decoder has all the usual features including full colour characters, Graphics, Newflash, Sub-Title and Timed Page facilities.

Our kit contains the printed circuit boards and all components necessary to build the complete decoder including power supply and video switching unit. Signal input required is a minimum of 1.0V detected video. The output is approx. 4V of R, G and B drive suitable for driving most types of Colour television sets, plus a luminance output for black and white sets. The power supply and video switching circuitry are normally installed within the television cabinet and the main decoding, control and memory circuitry are in a separate cabinet (approx. 10 1/2in. x 3in. x 7 3/4in.) positioned on top of the television. Lower case characters may be added by using an extra add-on printed circuit board unit.

Price of component kit — £104.10
Add On unit for lower case — £13.75
Cabinet and chassis — £13.50
Post & Packing — add £1.50

IGNITION SUPPRESSION COMPONENTS

We have the widest range of suppressors available as follows: Screened Plug Connectors (essential for VHF), straight or angled — £1.20, Plug in Distributor Suppressor — 55p, InF Capacitor, available with normal push fit lucar connector, large lucar or fully insulated with wire connectors 37p, 2uF normal or large lucar connector 52p, 2.5 uF Coax type £1.63, 3uF Capacitor for Lucas ACR alternator £1.50, 3A Chokes 71p, 7A Chokes £1.00, Solid Copper Standard Ignition Cable 7p per ft. Connectors 18p for 6.



VHF COMMUNICATIONS, the English language edition of the German publication UKW-BERICHT, is a quarterly amateur radio magazine especially catering for vhf/uhf/shf technology. It is published in spring, summer, autumn and winter.

The current subscription rate is £3.75 post free.

All special components required for the construction of the described equipment, such as printed circuit boards, coil formers, semiconductors and crystals, as well as complete kits, are available for despatch direct from Germany. Many of the printed circuit boards, in addition to a few selected kits, are stocked in the UK. A price list of kits and materials is available — send s a e for your copy.

All back issues are available, either post free from Germany (approx. 3 weeks) or can be despatched from UK stock (approx. 3 days) if UK postage is added.

	Sent from Germany	For delivery from UK add
Complete Volumes: 1970, 1971 (per year)	£2.75	30p per vol
1972, 1973, 1974	£3.20	30p per vol
1975	£3.65	30p
Individual back issues	90p	10p each
Plastic binder to hold 12 editions (three volumes)	£1.35	35p each
Vols 1970-72 with FREE BINDER	£9.00	70p
Vols 1972-74 with FREE BINDER	£9.45	70p
Vols 1970-75 with TWO BINDERS	£18.75	£1 00

Please address orders and enquiries to VHF COMMUNICATIONS at the address below.

All Mail orders and enquiries to: Dept 658, 20 THORNTON CRESCENT, Old Couladon, Surrey. Mail orders only to this address. NO CALLERS.

electronics today

international

AUGUST 1976

VOL 5, No. 8

Features

FIXED CAPACITORS	10
<i>Start of a new series on passive components</i>	
MEASUREMENTS	23
<i>Untangling some strands of mystery around this confusing subject</i>	
RTVC CASSETTE DECK REVIEWED	28
<i>A really low cost deck — how close to hi-fi is it?</i>	
ETI MICROFILE, PART SIX	50
<i>Take an MPU home today!</i>	
ELECTRONICS ITS EASY	58
<i>Digital display decoding techniques</i>	
TECH-TIPS	64
<i>Four pages of readers circuit ideas</i>	

Projects

UNIVERSAL TIMER	18
<i>Everything from eggs to snail races timed with one unit!</i>	
HIGH POWER BEACON	30
<i>Don't be caught out where you can't be seen</i>	
HEADPHONE RADIO	34
<i>AM Radio you don't need hands to operate!</i>	
SOUND/LIGHT FLASH TRIGGER	46
<i>Versatile flash trigger for unusual shots</i>	
LOW COST VDU — PART ONE	56
<i>Introduction to our superb low cost VDU project</i>	

Data Sheet

2513 CHARACTER GENERATOR	43
<i>A powerful IC system — used in our VDU</i>	
TAD 100 AM RADIO SUB-SYSTEM	44
<i>Complete AM radio system — with an offer combined!</i>	

News

NEWS DIGEST	6
ELECTRONICS TOMORROW	62

Information

SUBSCRIPTIONS	15
PULSAR OFFER	29
ETI SEPTEMBER PREVIEW	37
ETI SPECIALS	40
BOOK SERVICE	55
READER SERVICE INFORMATION	74

Special Offers

ETI BARGAIN MONTH VOUCHERS	38
NEW 5 FUNCTION WATCH OFFER	54

EDITORIAL AND ADVERTISEMENT OFFICES

36 Ebury Street
London SW1W 0LW
Telephone: 01-730 8282

HALVOR W. MOORSHEAD
Editor

ROBERT C. EVANS
Advertisement Manager

LES BELL, G4CFM
RON HARRIS B.Sc
Editorial Assistants

JEAN BELL
Production

INTERNATIONAL EDITIONS

COLLYN RIVERS
Editorial Director

AUSTRALIA
STEVE BRAIDWOOD
Assistant Editor

Modern Magazines (Holdings) Ltd
Ryrie House, 15 Boundary Street
Rusheuters Bay 2011
Sydney, Australia.

FRANCE
DENIS JACOB
Editor in chief
CHRISTIAN DARTEVILLE
Editor
Electroniques Pour Vous International,
17 Rue de Bucy
Paris, France

Electronics Today International is normally published on the first Friday of the month prior to the cover date.

PUBLISHED BY
Modmags Ltd
36 Ebury Street, London SW1W 0LW



DISTRIBUTED BY
Argus Distribution Ltd. (British Isles)
Gorden & Gotch Ltd. (Canada and South Africa)

PRINTED BY
QB Newspapers Limited, Colchester.

READERS' QUERIES. These can only be answered if they relate to recent articles published in the magazine. Rarely can we supply information in addition to that published. Written queries must be accompanied by a stamped addressed envelope, and telephone queries must be brief, not before 4pm and can only be answered subject to the availability of technical staff.

BACK NUMBERS. Back numbers of some issues are available for 40p each, plus 15p postage.

SUBSCRIPTIONS. Great Britain £5.00 per annum. Overseas £5.50 Canada \$10.

COPYRIGHT. All material is subject to world wide Copyright protection. All reasonable care is taken in the preparation of the magazine to ensure accuracy but ETI cannot be held responsible for it legally. Where errors do occur a correction will be published as soon as possible afterwards in the magazine.

RTVC

Now the VISCOUNT IV 30 x 30 Stereo Amp IN KIT FORM



£24.75
+£1.50 p&p

For the experienced constructor the Viscount IV amplifier comes complete with teak finished cabinet, front trim panel, knobs and all necessary metalwork. The specification for the NEW 30 x 30 is similar to the complete system offered below, but of course with the bigger output.

STEREO 21



COMPLETE ONLY
£23.00 + p&p £4.00

INCORPORATING A GARRARD DECK
Garrard 3 speed Deck automatic, manual facilities together with stereo cartridge and cueing device.

Stereo 21, easy to assemble audio system kit. No soldering required. The unit is finished in Simi Teak... and the acrylic top presents an unusually interesting variation on the modern deck plinth. Includes - 3 speed deck, automatic manual facilities together with stereo cartridge and cueing device.

Two speakers with cabinets.
Amplifier module. Ready built with control panel, speaker leads and full, easy to follow assembly instructions.
Specifications - For the technically minded. Input sensitivity 600mV. Aux. input sensitivity 120mV. Power output 2.7 watts per channel. Output impedance 8-15 ohms. Stereo headphone socket with automatic speaker cutout. Provision for auxiliary inputs - radio, tape, etc., and outputs for taping discs.
Overall Dimensions. Speakers approx 12" x 9" x 5". Complete deck and cover in closed position approx. 15 1/2" x 12" x 6".
Extras if required. Optional Diamond Stylus **£1.50**
Specially selected pair of stereo headphones with individual level controls and padded earpieces to give optimum performance **£5.25**

BSR DECKS WITH PLINTHS AT FANTASTIC REDUCTIONS



MP 60 Type (illustrated) **£14.40**
Less Cartridge p&p £2.00
C141 (not illustrated) **£10.80**
Auto. with Cue p&p £1.50
Fitted Stereo Cartridge
All plinths finished in matching Teak veneer.

EASY TO BUILD SPEAKER KITS

These superb simulated teak-finished speaker kits have been specially designed by RT-VC for the cost-conscious hi-fi enthusiast who wants top quality speakers but doesn't want to spend the earth. Built to EMI's exacting specification, these new RT-VC speaker kits (350 type kit) incorporate 13" x 8" woofer, 3" tweeter and matching crossover. Easily put together with just a few basic tools.
Specification (each speaker): Impedance 8 ohms. Power handling 15 watts RMS (30 watts peak). Response 20-20,000 Hz. Size 20" x 11" x 9 1/2" approx. Comparable built units (EMI LE3) sold elsewhere for over £45 pair.

£19.80 pair complete Complete with crossover Components and circuit diagram.
+ £5.20 p&p



EASYBUILD SPEAKER KIT THE NEW 'COMPACT'

A compact bookshelf speaker system giving a high electro acoustic efficiency for the low powered amplifier. The professional finish can be obtained with the minimum of tools, the infinite baffle type enclosures come ready mitred and professionally finished, and fix together with masking tape till glue dries. The cabinet measures 12" x 9" x 5" deep approx. finished in simulated teak, incorporating a quality 8" speaker, maximum power handling 7 watts, impedance 8 ohms nominal, magnet size 2 1/2" approx., with 1 1/2" parasitic tweeter.



£7.50
PAIR INCLUSIVE
+ p&p £1.70

EMI 350 KIT

£6.55 + £1.20 p & p.
Complete with crossover Components and circuit diagram

System consists of a 13" x 8" approx woofer with a 3" tweeter, crossover components and circuit diagram. Frequency response: 20 Hz to 20 KHz. Power handling 15 watts RMS into 8 ohms. (Peak 30 watts.)

VISCOUNT IV STEREO AMP

COMPLETE 20 x 20 SYSTEMS

SYSTEM 1b **£65.00**

The new 20 + 20 watt Stereo Amplifier incorporating the latest silicon transistor solid state circuitry, the RT-VC VISCOUNT IV gives you a powerful 20 watts RMS per channel into 8 ohms. Superb teak-finished cabinet, with anodised fascia to harmonise with any decor. Polished trim and knobs. The VISCOUNT IV has a comprehensive range of controls - volume, bass, treble, balance mono/stereo, mode selector, and scratch filter.

Front panel socket for stereo headphones. And a host of sockets at the rear - for left and right speakers, tape recorder, auxiliary, tuner, disc and microphone.

SPECIFICATION: 20 watts RMS per channel 40 watts peak. Suitable 8-15 ohms speakers. Total distortion at 10 watts better than 0.2%. Six switched inputs: 1. Magnetic P.U. - 3 millivolts at 47 K ohms (R.I.A.A.); 2. Crystal/ceramic P.U. - 50 millivolts at 50 K ohms (R.I.A.A.); 3, 4, 6. Tape Tuner/Aux. - 140 millivolts at 50 K ohms (flat frequency response); 5. Microphone - 3 millivolts at 50 K ohms (flat frequency response).

CONTROLS: Push button ON/OFF, stereo/mono, scratch filter, 6 position rotary selector. Individual rotary controls for treble, bass, balance and volume. Headphone socket, tape out socket. Aux. mains output. Frequency response: 25 Hz to 25 kHz at full rated output. Signal to noise ratio: better than -50 dB on all inputs. Tone control range: Bass ±15 dB at 50 Hz. Treble ±12 dB at 10 KHz. Power requirements: 250V A.C. mains at 60 watts.

Approx size: 15 1/2" x 3" x 10". MP60 type deck with magnetic cartridge, de luxe plinth and cover. Two Duo Type IIB matched speakers - Enclosure size 18 1/2" x 13 1/2" x 7 1/4" approx. in veneer teak. Drive unit 10" with 2 1/2" tweeter. 12 watts handling 24 watts peak.

SYSTEM 2 **£80.00**

Viscount IV amplifier (As System 1a)
MP60 type deck (As System 1a)

Two Duo Type IIB matched speakers - Enclosure size approx. 27" x 13" x 11 1/2". Finished in teak simulate. Drive units 13" x 8" bass driver, and two 3" (approx.) tweeters. 20 watts RMS, 8 ohms frequency range - 20 Hz to 18,000 Hz.

Complete System with these speakers **£80.00** + £7.60 p & p.

PRICES: SYSTEM 1a

Viscount IV amplifier **£24.75** + £1.90 p & p.
2 Duo Type IIB speakers **£27.00** + £6.50 p & p.
MP60 type deck with Mag. cartridge de luxe plinth and cover **£19.80** + £3.30 p & p.
Total if purchased separately: **£71.55**
Available complete for only: **£65.00** + £6.50 p & p.

PRICES: SYSTEM 2

Viscount IV amplifier **£24.75** + £1.90 p & p.
2 Duo Type IIB speakers **£41.40** + £7.50 p & p.
MP60 type deck with Mag. cartridge de luxe plinth and cover **£19.80** + £3.30 p & p.
Total if purchased separately: **£85.95**
Available complete for only: **£80.00** + £7.60 p & p.




Complete System with these speakers
£65.00
+ £6.50 p&p.

Scotland P & P Surcharge
System 1a £1.75 System 2 £3.50

Note: 30 x 30 kit available only as a separate item.

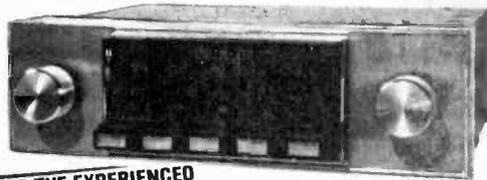PUSH BUTTON CAR RADIO KIT— THE TOURIST II



FOR THE EXPERIENCED CONSTRUCTOR WHO CAN SOLDER CORRECTLY ON A PRINTED CIRCUIT BOARD YOU CAN BUILD THIS KIT CORRECTLY

NOW YOU CAN BUILD YOUR OWN PUSH BUTTON CAR RADIO!

This construction kit comprises a fully built and aligned R.F.I.F. module; Printed circuit board, with ready mounted integrated circuit output stage and all other components. The push button tuning mechanism is fully built and tested ready to mate with the printed circuit board. (once it is assembled).
NOTE: No test equipment is required for alignment, but remember you must have the ability to solder on a printed circuit board.


TECHNICAL SPECIFICATION

(1) Output 4 watts RMS output. For 12 volt operation on negative or positive earth. (2) Integrated circuit output stage, pre-built three stage IF Module. Controls volume manual tuning and five push buttons for station selection, illuminated tuning scale covering full, medium and long wave bands. Size chassis 7" wide, 2" high and 4 1/2" deep approx. Speaker including baffle and fixing strip £1.80+45p. p&p. Car Aerial Recommended—fully retractable £7.40 +£1.05 p&p.

STEREO CASSETTE TAPE DECK KIT

Kit comprises of ready built cassette tape transport mechanism. Featuring pause control, solenoid assisted auto-stop, 3 digit tape counter, belt-driven balanced fly wheel, DC motor with electronic speed control, ready built and mounted record/replay PC board, and two VU meters, power supply, PC board, mains transformer. Input and output sockets and two level controls. Specification power source 240 AC 50Hz. Output more than 0.5v input mike -65dB 10KΩ. DIN -47dB 100KΩ. Track system 2 channel stereo record play-back. Tape speed 4.8CM/SEC. Frequency response 50-12000 Hz signal to noise ratio -42dB. Recording system AC Bias Erasing system AC erase. Bias frequency 57KHz. Size of mechanism 8" x 5" x 3 1/2" approx. unit easy to mount into your cabinet 3" required to clear base of mechanism approx.

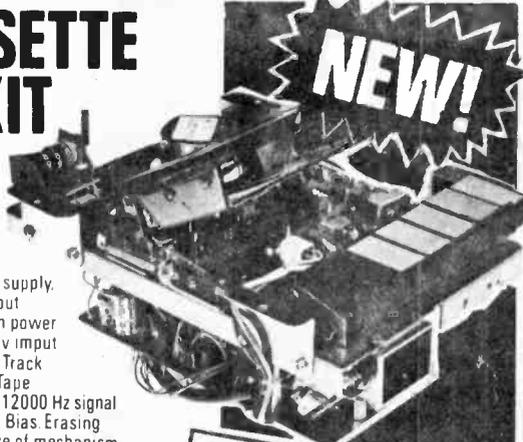* This is an advanced kit not suitable for those without electrical knowledge and those unable to solder.



£29.25
+ p&p £1.50
or send SAE for complete details.

NEW PRODUCT DISCO 35 MONO AMPLIFIER

An ideal general purpose 35 watt mono amplifier with full mixing facilities. Suitable for DISCO, PUBLIC ADDRESS & GUITAR/MUSICAL INSTRUMENTS. Unit housed in an attractively styled teak veneered cabinet. 4 Inputs: DISC 1 & DISC 2 (BOTH FOR CERAMIC CARTRIDGES), tape and microphone. CONTROLS: All level mixing controls are fitted with integral switches, push button type. DISC 1 & DISC 2: Volume combined treble filter. TAPE: Volume combined bass booster switch. MASTER: Volume control combined on/off. MIC: Volume combined bass booster switch. INDEPENDENT BASS AND TREBLE CONTROLS.

TECHNICAL SPECIFICATION

Power output: 35RMS into 4 ohms. Speaker: (Suitable for 4 to 15 ohms speakers). Sensitivities: DISC 1 & DISC 2: 30 mv (into 120k RIAA). Treble Filter Switch: 12 db@ 10 KHz. Tape: 100 mv (into 120k Flat). Bass Booster Switch+18 db@ 60 Hz. Mic: 2 mv (equalised for dynamic). Bass Booster Switch+20 db@ 60 Hz. Bass Control: ±15 db@ 60 Hz. Treble Control: ±12 db@ 10 KHz.

£25.00
+£1.40 p&p

8 TRACK HOME CARTRIDGE PLAYER



Yours for only


£12.60 +£1.70 p & p.

Elegant self selector push button player for use with your stereo system. Compatible with Viscount IV system, Unisound module and the Stereo 21. Technical specification Mains input, 240V. Output sensitivity 125mV.

SPECIAL OFFER

As above but complete with build yourself Unisound Amplifier Kit (see opposite panel) + 2 'Compact' easy to build speaker kits (see opposite page) **£24.50** + p & p £2.00

BUILD YOUR OWN STEREO AMPLIFIER

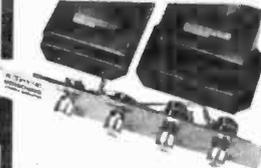


For the man who wants to design his own stereo - here's your chance to start, with Unisound - pre-amp, power amplifier and control panel. - Just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips which ensure very low distortion over the audio spectrum. 240V. AC only.

£8.00 £1.05 p & p.

Also available with the 'Compact' (see opposite page) easy build speaker kit £14.50 + £2 p & p

PORTABLE DISCO CONSOLE

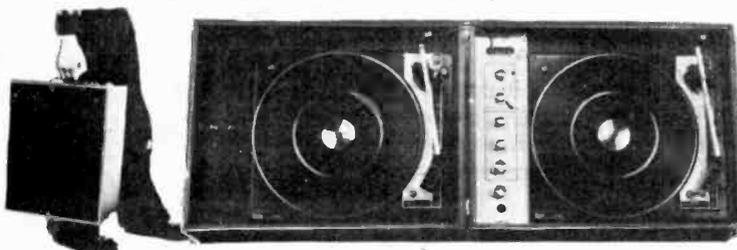

INCORPORATES: Pre-Amp with full mixing facilities, including switched input for mic with volume control, switched input for auxiliary with volume control, bass and treble controls, volume control and blend control for turntables. Two B.S.R. MP60 type single play professional series decks, fitted with crystal cartridges.

TECHNICAL SPECIFICATION:

Pre-amp - Output - 200mV. Auxiliary inputs - 200mV and 750mV into 1 meg. Mic input - 6mV into 100K. 240 volt operation. Turntables capacity - 7", 10" or 12" records. Rumble, wow and flutter Rumble Better than -35dB. Wow Better than 0.2%. Flutter Better than 0.06% (Gauumont kalee meter). Finish - Satin black mainplate with black turntable mat inlaid with brushed aluminium trim. Tonearm and controls in black and brushed aluminium.

Console size -

Unit Closed - 17 1/2" x 13 1/2" x 8 1/2" (app.)
Unit Open - 35 1/2" x 13 1/2" x 4 1/2" (app.)
This disco console is ideally matched for the Reliant IV and Disco 50 or any other quality amplifier.
The unit is finished in black PVC with contrasting simulated teak edging, diamond spun control knobs with matching control panel.

Yours for only

£51.00 +£6.50 p & p.

All prices include VAT at current rates

Mail orders to Acton. Terms C.W.O. All enquiries stamped addressed envelope. Goods not despatched outside U.K.

All items subject to availability. Prices correct at 1st June, 1976, and subject to change without notice.

Minimum order on ACCESS/BARCLAYCARD-£11.



DO NOT SEND CARD

Just write your order giving your credit card number


R T V C

21A HIGH STREET, ACTON, LONDON W3 6NG
323 EDGWARE ROAD, LONDON W2

Personal Shoppers EDGWARE RD: 9 a.m.-5.30p.m. Half day Thurs
ACTON: 9.30a.m.-5p.m. Closed all day Wed.

news digest

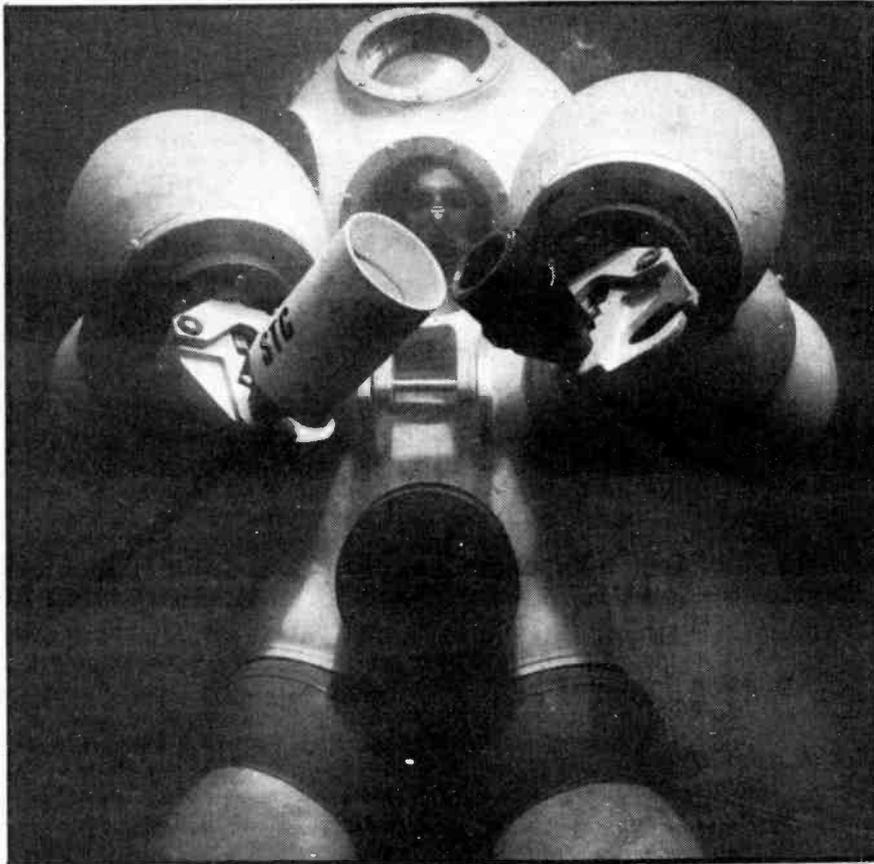THERE MUST BE AN EASIER WAY TO FIX A HI-FI



The picture shows the testing of a new STC underwater cable, which is unpluggable whilst live. It can operate at depths where the pressure is in excess of 700 p.s.i. Hence the 'Flash Gordon' repairman suit.

The suit is made by BHB Construction and is worn at the Admiralty Underwater Weapons Division. Finished in finest stainless steel, it is now available complete with matching hernia and free gold lamé truss!

Christian Dior — eat your heart out.

STC Christchurch Way, Greenwich, London SE10 0AG.

SCIENTIFIC PRICE REDUCTION

As a result of increased production and decreased costs, CBM have announced significant price reductions on their line of scientific calculators. These new prices were effective as of June 14th 1976:-

Model	Old Price	New Price
SR4190R	£59.95 inc. VAT	£49.95
SR4148R	£42.50 " "	£36.50
SR1800	£29.95 " "	£24.00
SR7919D	£16.95 " "	£14.50


WRAPPERS FOR CHIPS

Several companies are in the process of producing a calculator 'module', i.e. a complete PCB containing display chip and keying arrangements. These are for the low end of the market, where packages are the determining factor in price. Rockwell will introduce such a module in the US later this

month, and National are working on the devices for scientific and financial users.

RIDING HIGH

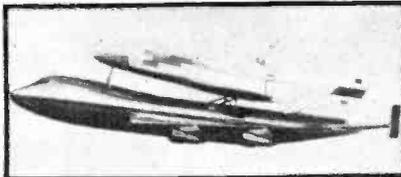The next step in America's space programme is the testing of NASA's space shuttle. Landing tests are to be carried out in mid 1977. Amazingly the machine will be launched 'piggy-back' from a Jumbo 747! Several



flights will be made to ensure stability before the shuttle is actually released. Trust Americans to build the world's largest airliner and then carry people outside it!

WHAT'S NEW IN THE BOOK WORLD

A couple of new books have come our way in the past month or so, published by Newnes-Butterworths. The *Electronics Engineer's Reference Book (4th ed., edited by L.W. Turner, £25)* is a massive tome, which somehow reminds us of an overgrown pocket diary — it seems to follow a similar format and presentation to the one you probably buy every year. It is very easy when trying to use this book to get side tracked into reading about subjects totally unrelated to your original interest as the format is (for a reference book) fairly readable. However, it always seems to be a characteristic of this type of book that, although it is undoubtedly full of concisely presented information, it never has just the particular piece of information you require. A particular criticism we can level at this book is the almost complete lack of information on digital circuit design, which is counterbalanced by chapters on valves (what are valves?, we hear a younger reader cry), Electronics in Weather Forecasting, Particle Accelerators, etc.. Never mind there's still a lot of good stuff in it.

BI-MOS OP AMP

RCA introduce a new operational amplifier combining different semiconductor technologies in the same device. Known as the CA3140, the operational amplifier uses a technique called BiMOS, combining a p-MOS input stage with a bipolar output stage

having a wide output voltage range.

Data sheets and applications brochures for the CA3140 are available from RCA Solid State — Europe at Sunbury-on-Thames, Middlesex TW16 7HW.

VITAL STATISTICS

The Statistician is a new release from CBM, a 'third generation' scientific calculator which takes a specialised application and 'pre-programmes' this to give greater user convenience than fully programmables, and greater power than earlier scientific.

The Statistician features many advanced specialist-user functions. It cuts down on operating time by reducing 'setting-up' to an absolute minimum and eliminating programming errors and the need to remember complex input routines. Chi-squared distribution, for example, only needs two inputs for computation, Gaussian only needs one.

Included in the price of £99.95 is a mains adaptor/charger which permits use of the Statistician during recharging. Also provided is a fully comprehensive instruction manual with many



worked examples, a protective carrying pouch, and is guaranteed for 12 months.


Pre-Programmed Functions

Linear regression, slope, intercept, residual sum of squares, coefficient of correlation, mean of x values, mean of y values, mean and standard deviations, one sample + two sample test statistics, Chi-squared statistic, Chi-squared distribution, hypergeometric distribution, binomial distribution, poisson distribution, F distribution, gaussian probability distribution, t distribution, permutations + combinations.

Basic Mathematical Functions

Eights memories each individually addressable, random numbers, parenthesis, all powers, all roots, square, square root, reciprocal, factorial, gamma function, pi, +/- sign

BOARD DECISION

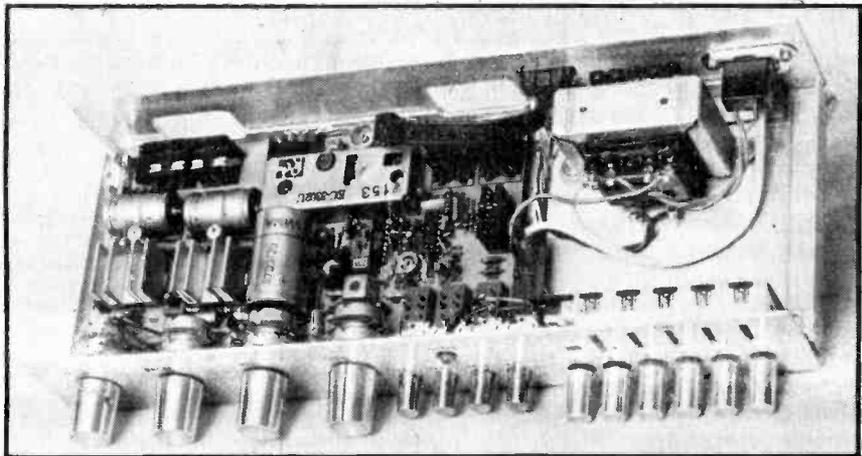

A fresh approach to audio kits has been shown by Jayen developments. Instead of selling complete parts and instructions, the idea is to provide the PCB's, overprinted, with circuit diagrams and 'shopping lists' of where to purchase components.


First in line is the FM7X7 stereo tuner amplifier with an excellent specification. The photo shows the board built into a prototype chassis. The inclusive price of the PCB's and instructions for this are £3.85 from Jayen Developments, 25 Westgate, Louth, Lincolnshire LN11 9YQ.

change, exponential entry, x/y exchange, significant number selection, Natural log, Napierian log, e^x , 10^x , sin, cos, tan, \sin^{-1} , \cos^{-1} , \tan^{-1} , degrees/radians conversions, 14 digit display, (10 digit mantissa, 2 digit exponent).

CBM Business Machines Ltd., Industrial Estate, Eaglescliffe, Stockton-on-Tees, Cleveland TS16 0PN.

JOY STICK TO PLAY WITH

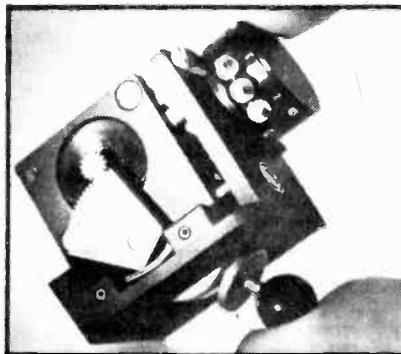The assembly consists of a self-centering control lever moving through a square pyramid envelope, meshing via gears with two-gang and single gang potentiometers. One potentiometer may be at maximum travel at 29° from centre, while the other moves



from maximum at one end, through zero at center to maximum. It is expected to be particularly suitable for application in electronic games equipment.

Beckman Instruments Limited, Queensway, Glenrothes, Fife, Scotland.

ETI/HENRY'S COMPETITION WINNER

Winner of the ETI/HENRY'S Sale-of-the-Century Competition in the March issue was H. Thompson of Hawkwell, Essex. Mr. Thompson wins £12.50 but also receives a 90% discount when spending this at Henry's making for a £125 prize. Runners up with £12.50 prizes were:

- G. Tanner, Fulbourn, Cambs.
- K. Perry, Beckenham, Kent.
- A. Kofinas, Sussex University.
- S. Brandon, Luton, Beds.
- D. Ward, Worthing, Sussex.
- G. Rowse, Bexhill, Sussex.

Additional runners-up who had included the 50p price coupon from the Henry's catalogue doubled their prize to were:

- R. R. Zick, Wolverhampton,
- P. Bolton, King's Lynn, Norfolk.
- H. F. Howard, Fishponds, Bristol.
- J. G. Brandon, Brentwood, Essex.

The answers were:

- | | |
|------------------|------------------|
| A 2n7 | F 22k |
| B 2n7 | G 10μ |
| C 15nF | H 100k |
| D 15nF | J 15k |
| E 22k | K 3k3 |

BRITISH CALCULATORS SAVED

A major threat to Britain's indigenous calculator industry has been removed by some government discussions in the EEC. At present 17.6% duty is charged on all imported displays, and both the companies (CBM and Sinclair) building in Britain rely on supplies outside the market. This is the charge levied on general electronic components rather than on calculator components (9.9%).

This naturally penalised our own industry against US and Japanese competitors. From July 1st all duty on displays will be lifted for a trial period of six months, and this is liable to become permanent.

If some such concession had not been made, the companies would almost certainly have moved production overseas.

DISPLAY OF INACCURACY

We've received the following letter from 'Metac International' concerning a comment in our 'Electronics It's Easy' article last month. We agree with the comments made in letter, and apologise for letting this slip by us!

The Editor,

Dear Sir,

I would like to comment on a statement regarding liquid crystal displays made in the July issue "Electronics It's Easy" article. The section I refer to is on the lifetime of LCD displays which the author claims is 10,000 hours and as short as 1000 hours. These figures I am sure, have been extracted from some very out of data literature and do much to harm the progress of LCD displays in industrial and consumer products.


The very early problems experienced with LCD displays was largely due to impurities in the Liquid Crystal material, also, poor sealing of the glass envelope. With improved techniques, manufacturers such as Thompson-CSF now claim a minimum of 50,000 hours and others claim 100,000 hours. The use of LCD displays is increasing in industry and for military applications. My own company is engaged in development work for LCD displays in cars on behalf of a major car manufacturer.

Our own experience as a supplier of liquid crystal display watches is that the display is as reliable as LED displays.

Yours faithfully,
Metac International.

8th June, 1976

LSI CMOS IC IN LCD DMM

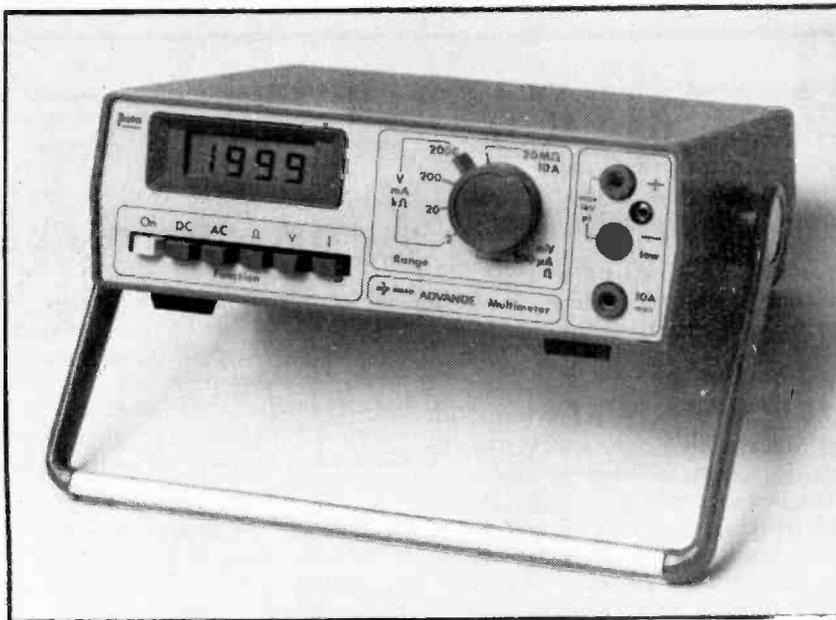

Paris, 10th June...Gould Advance today announced the Beta digital multimeter, a 0.2% accuracy instrument featuring 10A current ranges and optional temperature measurement. Heart of the instrument is a specially designed CMOS chip, produced by Motorola in association with Advance, which includes virtually all the analogue and digital circuitry including on-chip clock and display multiplexing. The resultant low parts count gives benefits in the form of higher reliability and lower cost - £99. The Beta uses a ¼" LCD display (also

made by Motorola) to ensure good readability in high ambient light. This also helps with power consumption: up to 600 hours on a set of batteries. Said Tony Grant, Beta Project Manager, at the launching Press Conference, "Beta has not been designed to replace the analogue multimeter, but one comparison may be of interest; when used for measurements on 5V TTL circuitry, the analogue multimeter will typically offer an impedance of 1.67kΩ per£ cost, whereas the Beta offers 222kΩ per £! Gould Advance Ltd., Roebuck Road, Hainault, Essex.

I²L DOORBELL

Matsushita Electrics have applied integrated injection logic to a new IC specifically intended for use in door-chimes. The IC produces four possible sounds, and naturally consumes little power.

The circuit consists basically of three oscillators, which can be combined and/or gated for differing times, giving the four sounds.

At the moment it is available only in Japan, but patent rights have been applied for in Britain, America, West Germany, France and Italy.

TI BUY UP MSI

Texas stepped up at an auction in the US recently to sell off Micro Systems International (deceased) hardware. They came away with approx £93,000 of equipment. The haul of loot included four crystal growers, three water polishers, a vapour deposition system (. . . . and a partridge in a pear tree?).

About 600 potential customers turned up at the auction, but there couldn't have been much left.

ERROR REPORT

EXPANDER/COMPRESSOR MAY 1976 ISSUE.

On the track layout C19/C20 is shown as connecting to pin 3 of IC9. The connection should be to pin 1 of that IC the correct detail is shown on the component detail.

OPTICAL COMMUNICATIONS CIRCUITS JUNE 1976 ISSUE.

Transmitter circuit:- R2 should be 6k8 and the 2N3702 has the emitter and collector transposed.

GOOD GOODS COME EASY AND FAST FROM SINTEL

TIME-KEEPING KITS CMOS and DISPLAYS

GUARANTEE. Telephoned orders received by 4.30 p.m. (Mon.-Fr.) guaranteed despatched the same day, **First Class Post.** The same applies to written orders. Telephone orders: Private customers (min. tel. order £5) quote Access Card No. Official orders, no minimum telephone order.



ACK

ATTRACTIVE 6-DIGIT ALARM CLOCK KIT

With optional CRYSTAL CONTROL for high accuracy and battery back-up (see below). Complete kit including attractive slim case with deep red panel for 6-digit alarm clock with beep alarm, snooze, automatic intensity control and high brightness display driving. Uses MK50253 IC and Jumbo 0.5" red LEDs. 12 or 24-hour format (easy to add a switch to switch between them). Optional "touch switch" for snooze (extra). Order as "ACK" **£26.80**

Complete kit as above, plus CRYSTAL CONTROL and BATTERY BACK-UP. If mains power is disconnected (through a power cut, accidental switching off or moving clock) the clock will keep perfect time. Accuracy to within a few seconds a month. The extra components, with two PP3 batteries, all fit in the same case. While on back-up, the displays are off to conserve battery life but the alarm remains fully operational. Order as "ACK + XTK + BBK" **£33.58**

SLIM GREEN CLOCK



Complete kit for this attractive 4-digit Mantlepiece Clock with bright 0.5" GREEN display. While constructing, select 12 or 24 hour format, flashing or fixed colon. Kit includes miniature transformer. Housed in a new all-white slim case with green perspex front panel. Easy to build. Order as "GCK" **£12.90**
Kit as above, but less case and perspex. Order as "GMK" **£11.14**

CRYSTAL CONTROL and BATTERY BACK-UP can be incorporated in this clock too. No need to reset your clock each time power is disconnected. For the complete kit including this feature, order as "GCK + XTK + GBBK" **£19.65**

Crystal Controlled 6-Digit CAR CLOCK Kit With Independent Journey Timer

Runs off 12V (car) battery — protected against low voltage drop-out — display comes on with ignition — internal battery back-up allows temporary disconnection. 6 digit timer times journeys up to 24 hours in hours, minutes and seconds — automatic intensity control (essential for car use) — uses 0.5" red LED digits. Same external appearance as our ACK but with 8 push-buttons for setting time, starting, stopping and resetting timer, selecting display to show "time" or "journey time" — all control buttons functional irrespective of display mode selected. Complete kit including case. Order as "CCK" **£39.50**

50 Hz CRYSTAL TIMEBASE KIT

Provides an extremely stable output of one pulse every 20 msec. Uses: Improving accuracy of digital clocks, to within a few seconds a month. If used with a battery back-up circuit also makes clocks power-out or switch-off proof. Replacing 50 Hz signal on battery-powered equipment. Providing film synchronisation. Monitoring or improving turntable speed. Complete kit (PCB dimensions: 64 x 49mm). Order as "XTK" **£6.28**

50Hz CRYSTAL TIMEBASE MODULE: as above, but built and tested and with output preset to within ±5ppm. Order as "671-50" **£9.80**

100 Hz CRYSTAL TIMEBASE MODULE. Use as a pulse generator for any system counting in units of 1/100th sec. High stability, low current consumption (3mA typical). Easily interfaced to TTL (requires 1 transistor — circuit given). 5 to 14V operation (typical). Built and tested and output preset to within ±5ppm. Order as "821-100" **£12.70**

STOPWATCH

Complete kit for stopwatch (as in Dec. ETI): choose 6 digit range from tens of hours to milliseconds. Uses 6 x MAN3M displays. All necessary parts, including case and Manganese batteries **£31.80**

STOPWATCH WITH ONE LATCH: As above, but kit also includes facility to repeatedly freeze the displays with count continuing **£43.23**



ADD VAT at 8%. 25p P&P on all orders. Access orders welcomed, by post or phone (see above).
Price List sent with orders or free on request.
Export orders very welcome. No VAT, but add 10% (Europe). 15% (Overseas) for Air Mail P&P. For rates on books, contact us first.

SINTEL 53 Aston Street, Oxford
Tel. 0865 49791

CMOS

from the leading manufacturers only

CD4000	0.18	CD4034	1.65	CD4068	0.20	CD4555	0.78
CD4001	0.18	CD4035	1.02	CD4069	0.20	CD4556	0.78
CD4002	0.18	CD4036	2.23	CD4070	0.48	MC14528	1.01
CD4006	1.02	CD4037	0.83	CD4071	0.20	MC14534	6.04
CD4007	0.18	CD4038	0.93	CD4072	0.20	MC14563	4.07
CD4008	0.83	CD4039	2.23	CD4073	0.20	MC14566	1.21
CD4009	0.48	CD4040	0.92	CD4075	0.20	MCM14552	8.05
CD4010	0.48	CD4041	0.73	CD4076	1.34		
CD4011	0.18	CD4042	0.73	CD4077	0.48	Clock Chips	
CD4012	0.18	CD4043	0.87	CD4078	0.20	AY51202	2.89
CD4013	0.48	CD4044	0.81	CD4081	0.20	AY51224	3.50
CD4014	0.87	CD4045	1.22	CD4082	0.20	MK50250	5.00
CD4015	0.87	CD4046	1.16	CD4085	0.62	MK50253	5.60
CD4016	0.48	CD4047	0.78	CD4086	0.62	MM5314	4.44
CD4017	0.87	CD4048	0.48	CD4089	1.34		
CD4018	0.87	CD4049	0.48	CD4093	0.69	Flat Cable	
CD4019	0.48	CD4050	0.48	CD4094	1.62	20-w 1M	1.00
CD4020	0.97	CD4051	0.81	CD4095	0.91	10m. for	8.00
CD4021	0.87	CD4052	0.81	CD4096	0.91		
CD4022	0.83	CD4053	0.81	CD4097	3.12	Other ICs	
CD4023	0.18	CD4054	1.01	CD4099	1.59	CA3130	0.88
CD4024	0.67	CD4055	1.14	CD4502	1.07	75491	0.96
CD4025	0.18	CD4056	1.14	CD4510	1.18	75492	1.22
CD4026	1.50	CD4057	21.56	CD4511	1.36	RCA 741	
CD4027	0.48	CD4059	4.77	CD4514	2.72	Mini-DIP	
CD4028	0.78	CD4060	0.97	CD4515	2.72	4 for	1.16
CD4029	0.99	CD4061	18.92	CD4516	1.18		
CD4030	0.48	CD4062	7.77	CD4518	1.08	Memory	
CD4031	1.92	CD4063	0.95	CD4520	1.08	P2102A-6	3.35
CD4032	0.92	CD4066	0.61	CD4527	1.37		
CD4033	1.21	CD4067	3.12	CD4532	1.25		

Motorola **CMOS DATABOOK** (Vol. 5 Series A) c. 500 pages **£2.77** (No VAT)
MEMORY IC from Intel: P2102A-6 (new version of 2102-2), 16-pin IC, TTL compatible, 1024 x 1 bit Static RAM (Data supplied with IC) **£3.35**
QUARTZ CRYSTALS: Min. Watch 32,768 kHz **£4.50**, 5.12 MHz **£3.60**



FND500

TIL321, TIL322

XAN652, XAN654

Part No.	Manufacturer	Colour	Type	Size	Price
FND500	Fairchild	Red	Common Cathode LED	0.5"	£1.02
TIL 321	Texas Instr.	Red	Common Anode LED	0.5"	£1.30
TIL322	Texas Instr.	Red	Common Cathode LED	0.5"	£1.20
XAN652	Xcitor	Green	Common Anode LED	0.6"	£1.75
XAN654	Xcitor	Green	Common Cathode LED	0.6"	£1.75
MAN3M	Monsanto	Red	Common Cathode LED	0.13"	48p
5LT01	Futaba	Green	Phosphor Diode	0.5"	£5.80

We have a min. transformer for the 5LT01, a 4-digit clock display with colon: 12.0-12/100mA, 1.5-0.1.5/50mA. Order as "5L-TRF" **£1.80**
Use the AY51202, 5LT01 and 5L-TRF for a very simple clock circuit.
Miniature transformer for clocks, etc., 6-0-6/300mA. Fits in ALL the Verocases below. Order as "LED-TRF" **£1.80**

Display PCBs (each fits neatly into Verocase 751410J). All are for multiplexed arrays, all are suitable for FND500, TIL321, TIL322.
D500-4 (for 4 digit clock) **90p**; D500-6 (for 6 digit clock) **£1.35**
D500-8 (for counter, up to 8 digits) **£1.35**

VEROCASES. Neat all-white ABS cases with PCB guides, etc., front and rear aluminium panels. We have pre-cut perspex panels for some cases, making them ideal for clocks or instruments. For 751410J, PX-R-J (Red) **30p**, PX-G-J (Green) **30p**, For 751411D, PX-R-D (Red) **40p**. The cases are as used in our ACK & GCK. Dimensions are in mm.

751410J (205x140x40)	£2.64	751237J (154x85x40)	£1.72
751411D (205x140x75)	£3.04	751238D (154x85x60)	£2.15

LOW COST IC SOCKETS

Soldercon Pins are the ideal low cost method of providing sockets for TTL, CMOS, Displays, ICs. Simply cut off the lengths you need, solder into board and snap off the connecting carrier. A single purchase of Soldercon Pins gives you any socket you may need, and at low prices: 8 pin for 4p, 14 pin for 7p, cheaper in quantity. 50p per strip of 100 pins. 1,000 for **£4.3,000 for £10.50**.

8-way BOSS Switch: 8 ultra-min. toggle switches in 16 pin DIL **£2.60**.

SINTEL

Official Orders Welcomed. Terms: 30 days for written or phoned orders from Companies, Govt. Depts., Nat. Inds., Univs., Polys., etc.
Fast delivery for R & D.

**NEW
SERIES**

FIXED CAPACITORS

This essentially practical down-to-earth series will study each family of electronic components — and provide all essential data that is otherwise so difficult to obtain.

MODERN FIXED CAPACITORS can be placed in three general classes according to the characteristics of their dielectric.

- (A) Low loss, high stability e.g. mica, low-K ceramic, polystyrene.
- (B) Medium loss, medium stability e.g. paper, plastic film, high-K ceramic.
- (C) Polarised capacitors e.g. electrolytic, tantalum.

MICA CAPACITORS

Mica capacitors have low RF losses right through to UHF and very good capacitance stability. They are suitable for use in RF circuits up to 500 MHz and are recommended for use in oscillators and filters where their stability characteristics are almost unrivalled. Mica capacitors of appropriate size can handle large RF currents and high voltages and are often used in transmitting applications.

Moulded Mica or "Postage Stamp" — the most common form is the "Postage stamp" style, so named because of its size and shape. Often cheaper than real postage stamps and taste better when licked! General purpose mica capacitors have good stability and can be obtained

with high voltage and high RF current ratings. They are constructed of layers of foil interleaved with mica (referred to as "stacked mica") or layers of metallized mica. Obtainable in values between 10 pF and 0.1 μ F. They may be marked 'M.S.' to indicate Stacked Mica.

Silvered Mica — usually labelled with an S.M. marking, not to be confused with Stacked Mica capacitors. These have very high stability and are recommended for use in oscillators, filters and other critical applications requiring highly stable capacitance. Tolerance is also very good, usually specified to $\pm 5\%$ but in practice often better. Generally obtainable in values from 4.7 pF to 3300 pF.

Metal-Clad Mica — a square or rectangular-shaped capacitor having a metal clamp holding the stack of interleaved plates of foil and mica. This form of construction has low lead inductance and can handle high RF currents. It is used for dc blocking and bypassing in RF circuits.

Button Mica — named after their shape. Very good RF bypasses. Made in standoff and feedthrough styles. They

have very low inductance connections and are used for RF bypass, filter, and tuned circuit applications up to UHF.

The feedthrough style provides a bypassed connection through a chassis while the standoff style provides a direct bypass or bypassed tie point. Obtainable in values between 5 pF and 10 000 pF.

Dipped Mica — this style is encapsulated by dipping in resinous material below atmospheric pressure. They have improved electrical characteristics and higher reliability than moulded types. Obtainable in values from 10 pF to 0.1 μ F.

CERAMIC CAPACITORS

There are two basic types of ceramic capacitors — low permittivity ("Low-K") and high permittivity ("High-K"). They have widely different characteristics.

Low-K ceramics have low loss and exhibit small, linear changes of capacitance with temperature. They are useful up to 1000 MHz and are made for both low voltage and high voltage applications.

High-K ceramics provide large capacitance values in small space. Their losses are dependent on applied ac and dc fields. They exhibit large, non-linear changes in capacitance against temperature. As a consequence they find application as decoupling and bypass capacitors (discussed later).

Low-K Ceramic Capacitors. Low-K ceramic capacitors are manufactured in a range of temperature characteristics. They are sometimes referred to as "temperature compensating" capacitors as they can be used to compensate for temperature changes in other circuit components. This property is particularly useful in RF oscillators and filters.

The temperature characteristic or coefficient, is quoted in parts per million per $^{\circ}$ C (ppm/ $^{\circ}$ C), either positive or negative e.g. a capacitor marked 100 pF/P100 will increase its capacitance by 100 ppm for each degree centigrade increase in temperature. For a temperature rise of 10 $^{\circ}$ C it will increase its capacitance by 0.1 pF. As a further example, a 1000 pF capacitor


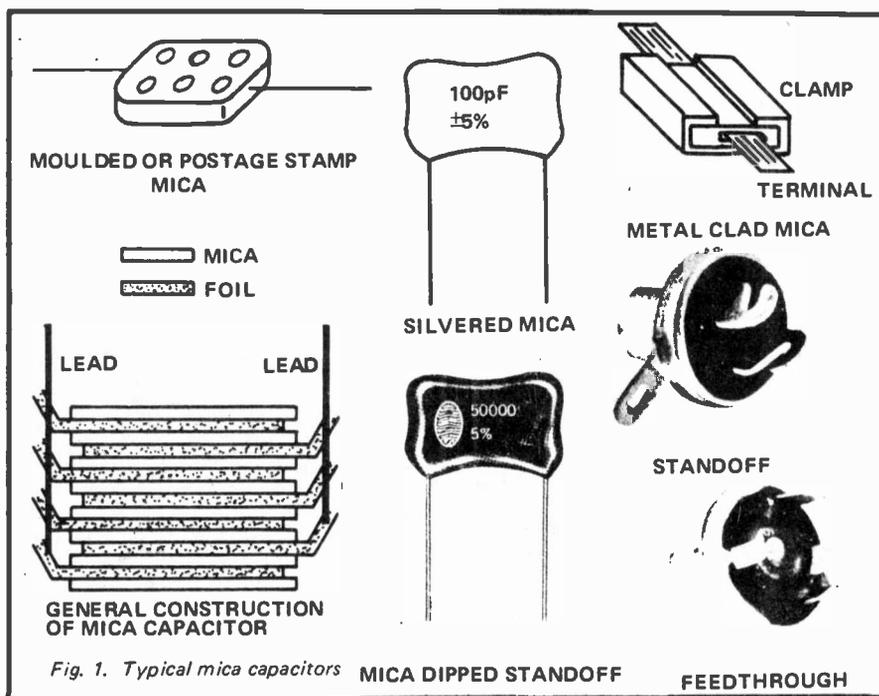


Fig. 1. Typical mica capacitors

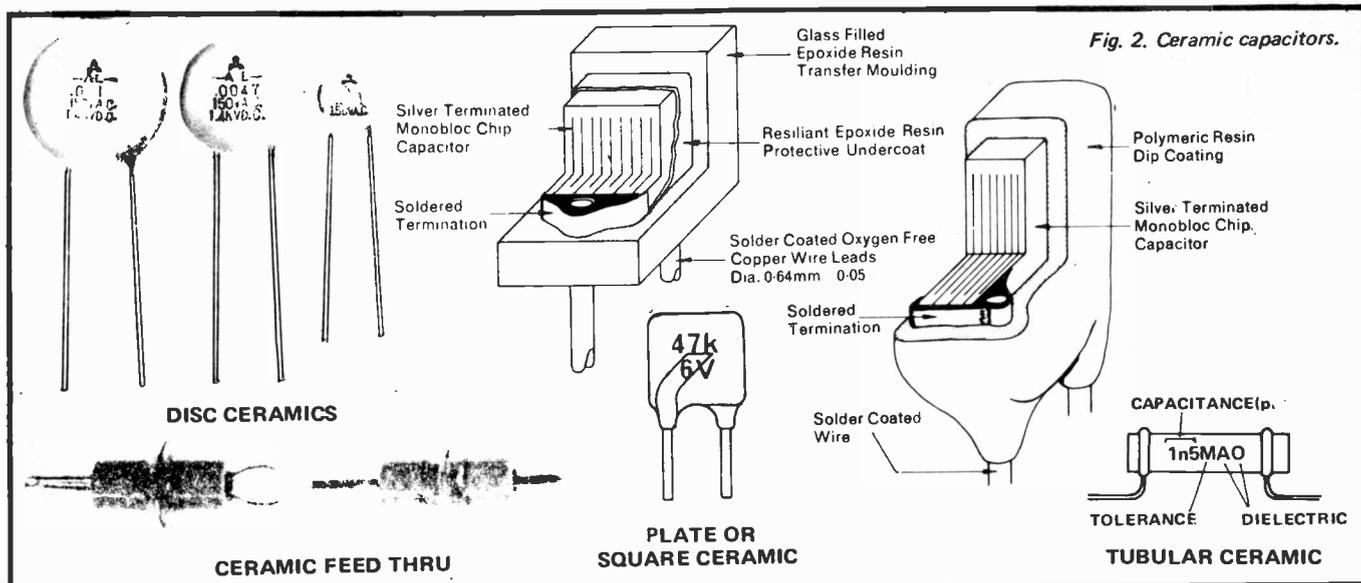

will decrease its capacitance by 1500 ppm for each degree centigrade rise in temperature. For a temperature rise of 10°C, its capacitance will drop by 15 pF.

Low-K capacitors are also produced having an extremely small temperature characteristic. These are known as NPO ceramics ("Negative-Positive Zero"). Their stability rivals that of silvered mica capacitors.

The graphs in Fig. 3 indicate the range of standard characteristics manufactured. The nominal value of ceramic capacitors is specified at 25°C. It should be noted that the change in capacitance is not strictly linear, having a small curvature, at low temperatures it becomes more negative. The tolerance on the temperature characteristic ranges from ± 30 ppm for NPO capacitors, to ± 1000 ppm for N5600. Below values of 10 pF stray capacitances begin to have a

marked effect on the temperature characteristic and the tolerances are widened as shown in Table 1.

The temperature coefficient of silvered mica capacitors is usually about +20 ppm/°C but may be as low as +5 ppm/°C which is somewhat better than NPO ceramics.

Low-K ceramic capacitors are made in disc, square and tubular forms. They are obtainable in a range of working voltages from 50 V to 15 kV. They are useful in RF circuits up to three or four hundred megahertz. Above this



frequency, leadless unencapsulated "chip" capacitors are used.

POLYSTYRENE CAPACITORS

Polystyrene capacitors are one type of plastic film capacitor. They are constructed usually by interleaving strips of foil and polystyrene film, the alternate strips of foil being staggered to provide connections. The assembly is then rolled up to form a tubular shaped capacitor. See Fig. 4. They exhibit low loss and good stability and are manufactured in a range of working

Characteristic	Capacitance range (pF)		
	0.4-2	2.2-3.9	4.7-10
NPO - N330	± 250 ppm	± 120 ppm	± 60 ppm
N470 - N750	± 250 ppm	± 120 ppm	± 120 ppm
N1500 - N5600	same as 10 pF and over		

TABLE 1

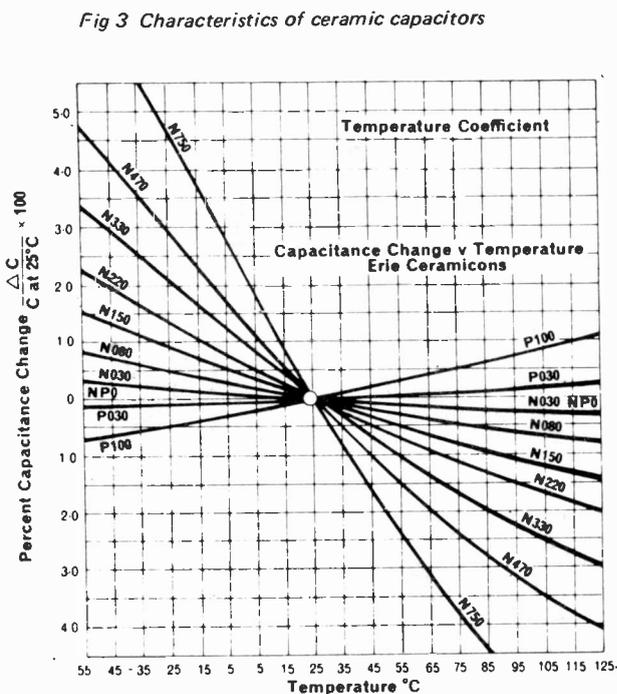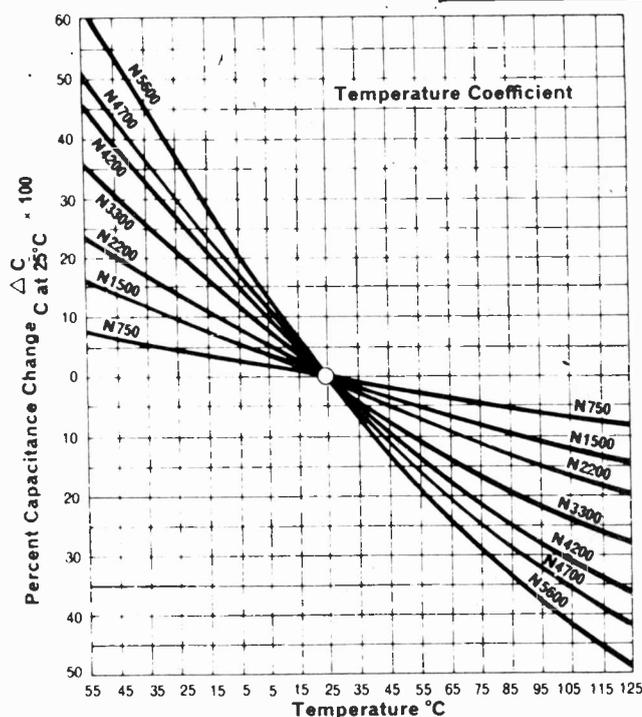

FIXED CAPACITORS

	Paper		Polyester		Polycarbonate		Polypropylene		Polystyrene	Ceramic		Mica	Electrolytic			
	metalized	film/foil	metalized	film/foil	metalized	film foil	metalized	film/foil		disc/tube	monolithic		aluminium foil	foil	tantalum solid & wet	
Insulation resistance (in megohms)	3×10^3	2×10^4	5×10^4	10^5	5×10^4	10^5	10^5	5×10^4	10^6	10^2	10^4	10^5	← variable →			
Tolerance	10%	5%	5%	5%	5%	2%	5%	2%	0.625%	10%	20%	0.5%	10%	10	5	
Temperature range (°C)	-30 to 100	30 to 100	-55 to 125	55 to 125	55 to 125	55 to 125	40 to 85	40 to 100	-40 to 70	-55 to 125	-55 to 125	-55 to 125	-20 to 80	-40 to 125	-40 to 150	
Size per CV*	small	large	small	small	small	small	small	small	large	small	small	small	very small	small		
Stability	fair	fair	fair	fair	fair	fair	fair	excellent	excellent	fair	fair	excellent	fair	very good	excellent	
Capacitance range (μF unless indicated)	0.01 to 100	0.001 to 100	0.001 to 10	100 pF to 0.01 μF	0.001 to 100	5 pF to 0.01 μF	0.001 to 100	100 pF to 0.47 μF	100 pF to 0.6 μF	5 pF to 1 μF	0.001 to 10	5 pF to 0.01 μF	typically 1-22 000	1-1000	3500 max	
Voltage (ac) (dc)	250-630	250-630	63-400	90-160	40-250	63-160	250-440	63-500	63-1000	63-250	63-10 000	63-450	63-630	6.3-500	6.3-300	1-50
Temperature coefficient PPM/°C	300	300	400	400 (non linear)	150	50 to 100	-170	120	150	non linear positive to 1000 neg	100	100	1500	1000 (non linear)	200-1000	
Appr.: resonance MHz	0.1	0.1	0.1	1	0.1	1	0.1	1	1	10	100	1.0	0.05	0.1	0.1	

Table 2. Capacitor Comparison Chart.

voltages from 100 volts to 630 volts. They exhibit a small negative temperature characteristic of about 150 ppm/°C and are sometimes used as temperature compensating capacitors. Their main application is in tuned circuits and as coupling capacitors up to about 100 MHz. The higher values (0.01 μF and above) are sometimes used in bypass and decoupling applications.

Polystyrene capacitors are affected by heat, greases and solvents. Care must be taken when using them to keep them away from heat sources (e.g. power resistors). Exercise care when soldering. Flux solvents and other chemical solvents will dissolve the capacitor, with disastrous effects.

PAPER CAPACITORS

Paper capacitors are medium loss, medium stability capacitors that were once widely used. They have been largely replaced by plastic film types for most purposes but are unsurpassed in high voltage dc and low frequency ac power applications.

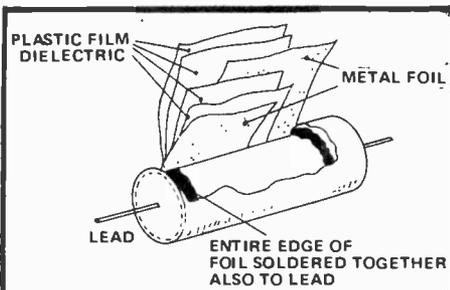


Fig 4 How polystyrene capacitors are made

There are two basic types of construction, the metal foil type and the metallized type. The metal foil type is constructed by winding together interleaved layers of foil and impregnated paper similar to plastic film capacitors, see Fig. 4. This type is best for high voltage and high current applications, a common form being the paper "block" capacitor. See Fig. 5. They are available in voltage ratings up to 4000 V and will withstand considerable charge-discharge currents. The metallized type has the impregnated paper dielectric coated with a thin layer of aluminium or zinc. This form of construction results in a capacitor of


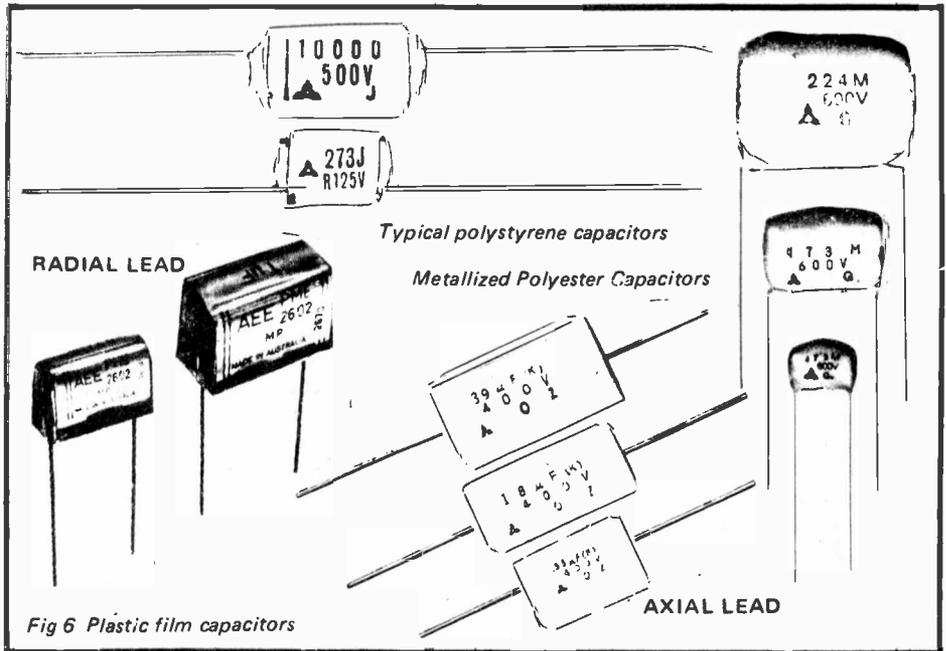


Fig 6 Plastic film capacitors

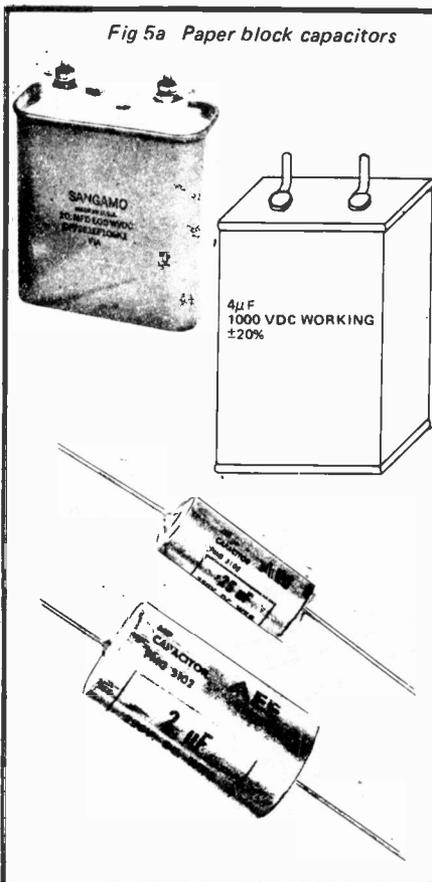

relatively smaller physical size.

The paper dielectric is impregnated with another dielectric substance to replace the water content inherent in paper and to prevent the absorption of moisture. A variety of natural oils or waxes, or synthetic chemicals, is used. Encapsulation of the capacitor assembly is usually by moulding in resin or encasing in hermetically sealed metal cans as is done with block capacitors.

PLASTIC FILM CAPACITORS

Plastic films are widely used in capacitor manufacture due to their high reliability and low cost. They have medium loss and medium stability characteristics except for polystyrene capacitors which have already been discussed. Many types of plastic film are used but these fall into three general groups:— polystyrene, polyester and polycarbonate.

The common form of construction uses strips of aluminium foil interleaved with the plastic film dielectric, alternate layers of foil being staggered to provide lead connections. The assembly is then rolled-up to form a tubular-shaped capacitor. Some types are wound flat to form a flat rectangular-shaped capacitor which enables it to be packed more densely on a printed circuit board. They

are referred to as 'flat film' capacitors.

Metallized film construction is also extensively used with plastic film capacitors, resulting in physically small dimensions. These capacitors have largely replaced paper capacitors in most low voltage applications owing to their superior electrical characteristics and considerably smaller size.

Plastic film capacitors are generally encapsulated in a tough, impervious plastic or resin or in a metal case.

The polyester films used are generally of the polyethylene type (Mylar, Melinex etc) or polypropylene, and for most purposes they have similar properties to polycarbonate films. The latter though, has less loss and exhibits less change in capacitance with temperature. Polyester capacitors are available in ratings up to 100 Vdc (or 250 V rms ac), Polycarbonate capacitors are usually only available in ratings up to 400 Vdc.

A comparison of the temperature, loss factor and insulation resistance of various capacitors is given in Figs. 7, 8, and 9.

A small defect, such as a hole, in the dielectric of a capacitor will allow an arc between the electrodes when a sufficiently high voltage is present. In foil capacitors, the arc usually destroys more of the surrounding dielectric, resulting in catastrophic failure — usually a short circuit.

This disadvantage does not occur in metallized capacitors. The heat generated by the arc rapidly vaporizes the electrode section, clearing the short. A very short pulse of current occurs and the voltage across the capacitor drops and then rises again in a few microseconds. Usually, no further damage results. The process is illustrated in Fig. 10.

HIGH-K CERAMIC CAPACITORS

High-K ceramic capacitors provide large values of capacitance in a very

small space. Owing to their method of manufacture they have appreciable loss and show large non-linear changes in capacitance with temperature. Primarily for these reasons they largely find application in bypassing and dc blocking. They change capacitance with applied dc and ac voltage, showing a decrease in capacitance with increasing dc voltage which ranges from 14% for the relatively low permittivity high-K ceramics to 80% for the higher permittivity ceramics. Ac voltage effects are the reverse of dc, giving an increase in capacitance with increasing voltage. This may be only 2% for the lower permittivity ceramic or up to 80% with the higher permittivity types.

High-K ceramic capacitors also change capacitance with frequency. The change is primarily dependent on the particular ceramic used, rather than high or low permittivity. They decrease in capacitance with increasing frequency. Most high-K capacitors only show a decrease of 5% between 1 kHz and 10 MHz, but others can drop 20% over the same range. These characteristics are usually of little consequence in most applications. However, care should be exercised in using them as bypass and decoupling capacitors around oscillator circuits. Plastic film capacitors or low-k disc ceramics are to be preferred.

In general, high-K ceramic capacitors have less internal inductance than plastic film or paper capacitors, as well as smaller size and are preferred in bypass applications. Disc or plate style ceramic capacitors are suitable for bypass applications from 10 MHz to 100 MHz. High-K ceramic capacitors are also made in button feedthrough and bypass styles for bypass applications to 1000 MHz. The tubular style is suitable in bypass applications to 50 MHz while the ceramic feedthrough is useful to 500 MHz. See Fig. 2 for illustrations. The large value (1000 pF — 0.47 μ F) 'chip' or 'block' style, which has very

low lead inductance, is very useful for bypassing in digital circuitry.

ELECTROLYTIC CAPACITORS TOLERANCES

Electrolytic capacitors consist basically of two aluminium foils interleaved with an absorbent paper and wound tightly into a cylinder. Contacts are provided by tabs of aluminium attached to the foils. The winding is impregnated with electrolyte and housed in a suitable container, usually an aluminium can, which is hermetically sealed (Fig. 11).

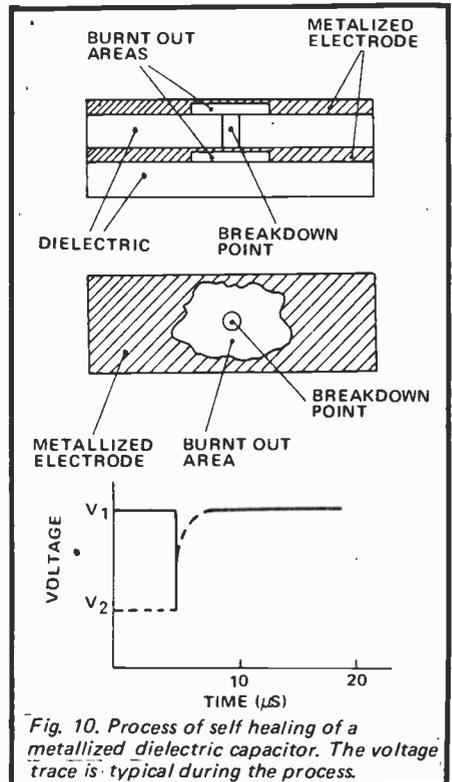


Fig. 10. Process of self healing of a metallized dielectric capacitor. The voltage trace is typical during the process.

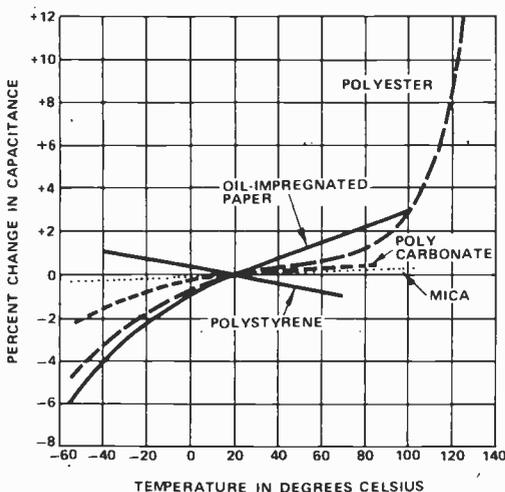


Fig. 7. Temperature versus change in capacitance.

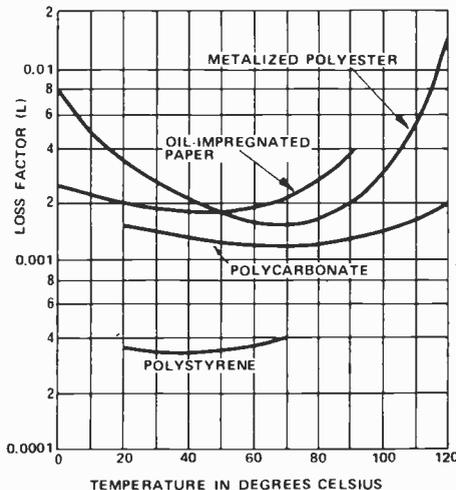


Fig. 8. Temperature versus loss factor.

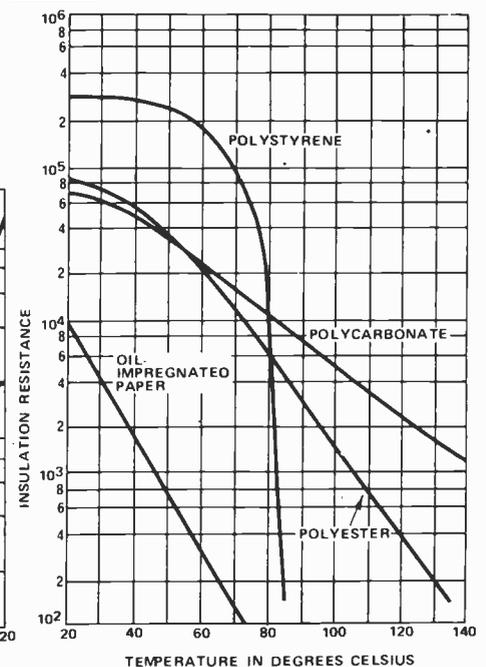


Fig. 9. Temperature versus insulation resistance.

FIXED CAPACITORS

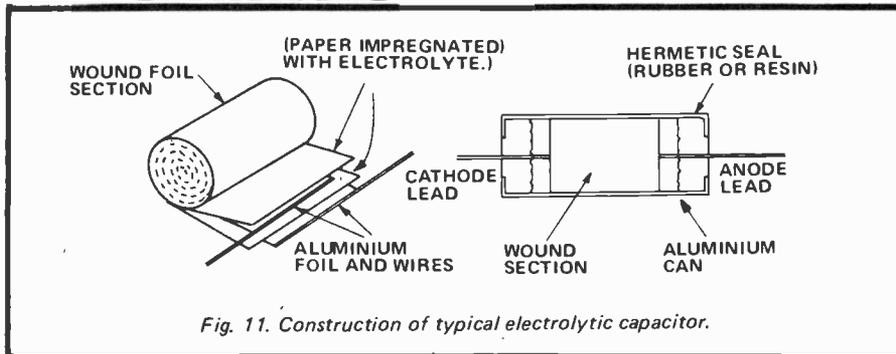


Fig. 11. Construction of typical electrolytic capacitor.

A dielectric layer of aluminium oxide is 'formed' electrolytically on the surface of one aluminium foil which acts as the positive plate, or anode, of the capacitor. The electrolyte serves as the second plate of the capacitor and also to repair any flaws in the oxide film when the electrolyte is polarised. The second foil, usually called the cathode foil, provides contact to the electrolyte. Since this film will have a thin oxide film, due to natural oxidation, it will also possess very high capacitance. The thinness of the oxide films, and their high breakdown potential, is responsible for the very high capacitance values per unit volume and high working voltages of electrolytic capacitors.

As a result of their construction, these capacitors are polarised and require the anode terminal to be at a positive potential to the cathode terminal. Most types will only withstand a reverse voltage of 1 V or 2 V for short periods and about 1.5 V peak-to-peak ac without a depolarising voltage.

There are two types of electrolytic capacitor, the plain foil type and the etched foil type. The plain foil construction is described above. The etched foil type is constructed similarly to the plain foil except that the

aluminium oxide on the anode and cathode foils has been chemically etched to increase its surface area and permittivity. It results in a capacitor which is physically smaller than a plain foil type of equivalent value but has the disadvantage of not being able to withstand high ac currents, compared with the plain foil type.

Etched foil electrolytics are best used in coupling, dc blocking and bypass applications. Plain foil types are better suited as reservoir capacitors in power supplies.

TOLERANCES

Electrolytic capacitors are usually manufactured to a tolerance of $-20 +100\%$ or $-50 +100\%$ (they really are!).

The capacitance value and leakage current both increase with temperature. The leakage current increases with applied dc voltage, this increase becoming more rapid at voltages in excess of the rated working value. This can lead to increased heat dissipation in the capacitor which will, in turn, increase the leakage current, leading ultimately to destruction.

Most electrolytics are rated to withstand a short voltage surge about 15–20% greater than the rated working voltage. e.g: a capacitor rated at 450 V may be marked 450 VWdc (volts, working, dc), 525 V surge.

Electrolytics can be used below their rated voltage. There may be a slight increase of capacitance with time. Leakage current is usually considerably reduced, resulting in an increased service life.

In manufacture, the internal negative connection may be taken directly to the case or to a tag on the insulated end disc. In this case the capacitor winding is inserted in the case without surrounding insulation so that, even though the negative tag is not directly connected to the case, it is not deliberately insulated from it and leakage current can flow between the case and negative terminal. These capacitors are usually covered in shrunk-on plastic sleeve to insulate the can.

Electrolytic capacitors are made in a

range of voltage ratings from 10 V to 600 V.

NON-POLARISED ELECTROLYTICS

These capacitors are constructed using several foils in one winding and connected 'back-to-back'. They are usually larger than polarised capacitors of equivalent value. Since double the foil area than is normally required is used they have increased leakage current. Ac voltage without a dc polarising voltage is permissible, the value depending on ripple current ratings and the frequency.

These capacitors are used as speaker coupling and crossover network capacitors. They are obtainable in values from 1 μF to 100 μF .

TANTALUM CAPACITORS

These capacitors use tantalum oxide as a dielectric. This has a much greater permittivity than aluminium oxide resulting in high value capacitance in relatively small space. Owing to their construction, they are also used as polarised capacitors.

There are three different types of tantalum capacitors, each having different construction. These are the tantalum foil type, the solid tantalum, and the wet-sintered tantalum. The tantalum foil type is similar in construction to electrolytic capacitors but the electrolyte and anode and cathode terminals use different materials.

Solid tantalum capacitors use solid manganese dioxide (which is a semiconductor) as the electrolyte, and a tantalum anode. The cathode connection is formed by coating the electrolyte with graphite and silver. These capacitors may be encapsulated in epoxy resin, polyester sleeve with epoxy seals, or a can with epoxy seals.

Tantalum capacitors are rated at much lower voltages than electrolytic capacitors. Their small size makes them very suitable for use in transistor circuits. Low leakage current and better capacitance stability than electrolytics are two features which make them suitable for timing applications.

Tantalum capacitors are generally available in values between 0.1 μF and 100 μF . Tolerance is usually $+50\%$ -20% . Solid tantalum capacitors are available in voltage ratings from 3 V to 100 V. Wet sintered tantalums are available up to 125 V rating and foil tantalums up to 450 V.

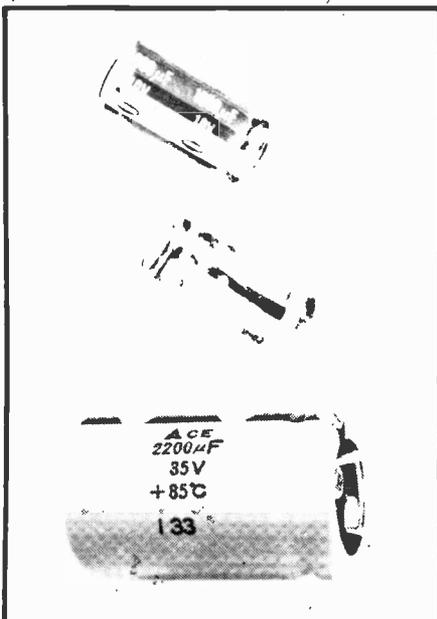


Fig. 12. Electrolytic capacitors.

Next month — all the various capacitor codes etc.

BUILD THE TREASURE TRACER MK III

METAL
LOCATOR



AS SEEN
ON BBC-1
& BBC-2
TV

- Genuine 5 silicon transistor circuit, does not need a transistor radio to operate.
- Incorporates unique varicap tuning for extra stability.
- Search head fitted with Faraday screen to eliminate capacitive effects.
- Loudspeaker or earphone operation. (both supplied).
- Britain's best selling metal locator kit. 4,000 already sold.
- Kit can be built in two hours using only soldering iron, screwdriver, pliers and side-cutters.
- Excellent sensitivity and stability.
- Kit absolutely complete including drilled, tinned, fibreglass p.c. board with components siting printed on.
- Complete after sales service.
- Weighs only 22oz; handle knocks down to 17" for transport.

Send stamped, self-addressed envelope for literature.

Complete kit with pre-built search coil **£12.50**
Plus 85p P & P
Plus £1.00 VAT (8%)

Built, tested and Guaranteed **£17.50**
Plus 85p P & P
Plus £1.40 VAT (8%)

MINIKITS ELECTRONICS,
6d Cleveland Road, South Woodford,
LONDON E18 2AN
(Mail order only)

Wilmslow Audio

*THE firm
for
speakers!*



Baker Group 25, 3, 8, or 15 ohm	£8.64
Baker Group 35, 3, 8 or 15 ohm	£10.25
Baker Deluxe, 8 or 15 ohm	£12.38
Baker Major, 3, 8 or 15 ohm	£10.69
Baker Regent, 8 or 15 ohm	£9.00
Baker Superb, 8 or 15 ohm	£16.31
Celestion MH 1000 horn, 8 or 15 ohm	£13.50
EMI 14" x 9" bass 14A/700 8 ohm	£11.92
EMI 8 x 5, 10 watt, d/c roll/s 8 ohm	£3.56
Elac 59RM 109 15 ohm, 59RM114 8 ohm	£3.38
Elac 6 1/2" d/c roll/s 8 ohm	£3.83
Elac 10" 10RM239 8 ohm	£3.83
Fane Pop 15 watt 12"	£5.25
Fane Pop 55, 12" 60 watt	£15.50
Fane Pop 60 watt, 15"	£17.95
Fane Pop 70 watt 15"	£18.75
Fane Pop 100 watt, 18"	£27.95
Fane Crescendo 12A or B, 8 or 15 ohm	£37.95
Fane Crescendo 15, 8 or 15 ohm	£49.95
Fane Crescendo 18, 8 or 15 ohm	£67.95
Fane 801T 8" d/c roll/s 8 ohm	£8.96
Goodmans 8P 8 or 15 ohm	£5.95
Goodmans 10P 8 or 15 ohm	£6.25
Goodmans 12P 8 or 15 ohm	£14.95
Goodmans 12P-D 8 or 15 ohms	£16.95
Goodmans 12P-G 8 or 15 ohms	£16.50
Goodmans Audiom 200 8 ohm	£13.46
Goodmans Axiom 100 8 ohm	£7.60
Goodmans Axiom 402 8 or 15 ohm	£19.80
Goodmans Twinaxiom 8" 8 or 15 ohm	£9.50
Goodmans Twinaxiom 10" 8 or 15 ohm	£9.76
Kef T27	£5.18
Kef T15	£6.25
Kef B110	£6.75
Kef B200	£7.85
Kef B139	£15.08
Kef DN8	£2.08
Kef DN12	£5.39
Kef DN13	£4.05
Richard Allan CG8T 8" d/c roll/s	£7.65
STC 400 1 G super tweeter	£5.90
Baker Major Module, each	£13.28
Goodmans Mezzo Twinkit, pair	£46.50
Goodmans DIN 20, 4 ohm, each	£13.28
Helme XLK30, pair	£21.95
Helme XLK35, pair	£26.75
Helme XLK40, pair	£38.50
Helme XLK50, pair	£55.50
Kefit 1, pair	£44.10
Kefit III, each	£39.38
Peerless 20-50, pair	£39.50
Peerless 20-60, pair	£53.00
Richard Allan Twinkit, each	£13.46
Richard Allan Triple 8, each	£20.25
Richard Allan Triple, each	£25.16
Richard Allan Super Triple, each	£29.25
Wharfedale Linton 2 kit, pair	£20.81
Wharfedale Glendale 3 XP kit, pair	£47.50
Wharfedale Dovedale 3 kit, pair	£59.40
Wharfedale Super 10RS/DD	£13.50
Castle Super 8 RS/DD	£9.28
Jordan Watts Module 4, 8 or 15 ohm	£15.36
Tannoy 10" Monitor HPD	£78.00
Tannoy 12" Monitor HPD	£86.00
Tannoy 15" Monitor HPD	£99.95

Prices correct at 11.6.76

ALL PRICES INCLUDE VAT

Cabinets, wadding, Vynair, crossovers etc

Send stamp for free booklet "Choosing a Speaker"

FREE with all orders over £10 - "HiFi Loudspeaker Enclosures" Book

All units are guaranteed new and perfect

Prompt despatch

Carriage: Speakers 55p each, 12" and up 85p each, tweeters and crossovers 33p each, kits £1 each (£2 pair).

WILMSLOW AUDIO
Dept. ET1

Swan Works, Bank Square, Wilmslow,
Cheshire SK9 1HF. Tel. Wilmslow 29599
(Discount HiFi, PA and Radio at 10 Swan
Street, Wilmslow)

ARE YOU BEING LEFT BEHIND?



31,269

Audited average
Jan-June 1975



41,803

Average Jan-June
1976 Subject
to audit

Our sales have gone up by 34% in the past year or so, but still some people are having trouble getting hold of ETI. If you're not sure of getting your's easily, why not take out a subscription? Twelve issues dropped through your door every month by the friendly neighbourhood postman.

To ensure a regular flow of our amazing articles, pulsating projects and nubile news just fill in the coupon below. We will do the rest!

—Cut—

ETI Subs, Electronics Today,
36 Ebury Street, London SW1W
0LW.

I enclose £5.00 (£5.50 overseas
subscriptions except Canada: \$10) for
the next twelve issues of ETI.

Please start with
the issue.


Please tick if this is a renewal

Name


Address

The easy way to a PCB...


...the Seno 33 system!

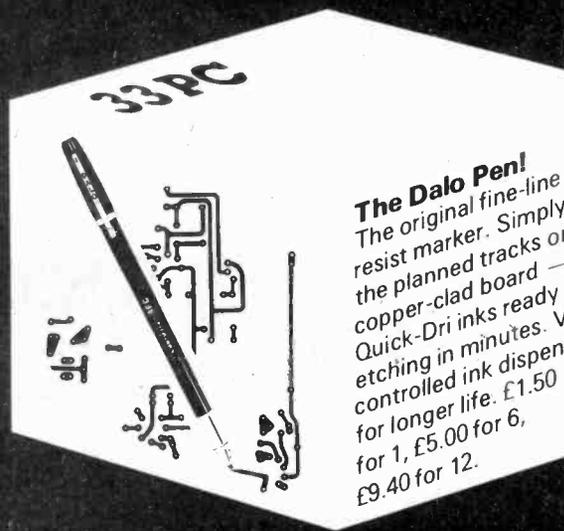

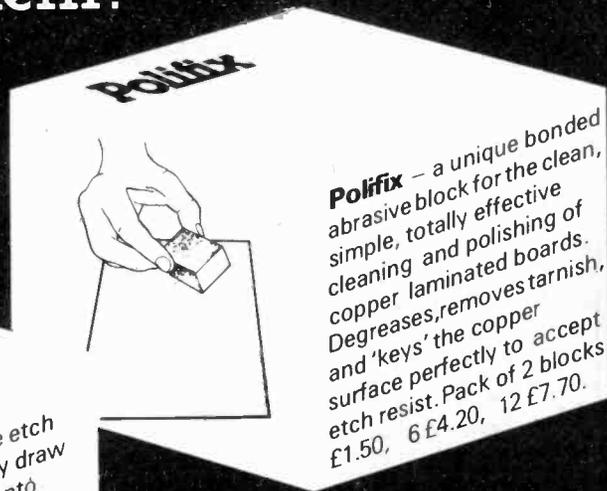
The Dalo Pen
The original fine-line etch resist marker. Simply draw the planned tracks onto copper-clad board — new Quick-Dri inks ready for etching in minutes. Valve controlled ink dispensing for longer life. £1.50 for 1, £5.00 for 6, £9.40 for 12.



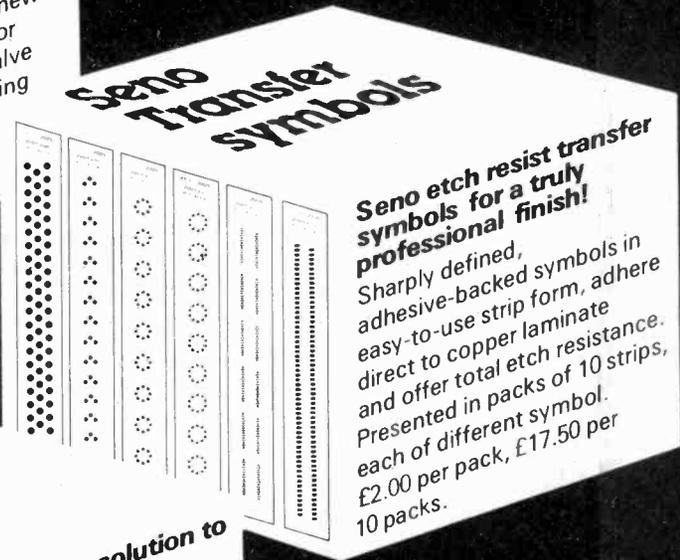Polifix — a unique bonded abrasive block for the clean, simple, totally effective cleaning and polishing of copper laminated boards. Degreases, removes tarnish, and 'keys' the copper surface perfectly to accept etch resist. Pack of 2 blocks £1.50, 6 £4.20, 12 £7.70.



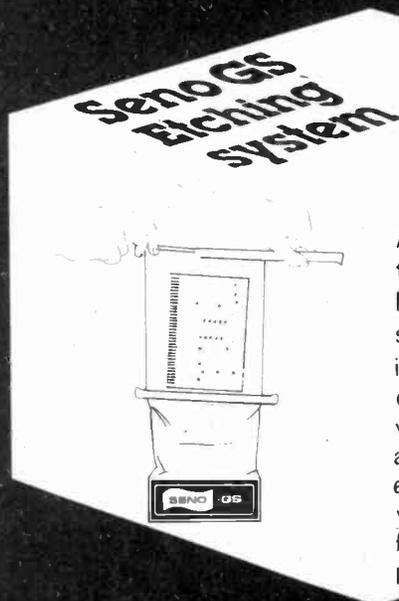Seno etch resist transfer symbols for a truly professional finish!
Sharply defined, adhesive-backed symbols in easy-to-use strip form, adhere direct to copper laminate and offer total etch resistance. Presented in packs of 10 strips, each of different symbol. £2.00 per pack, £17.50 per 10 packs.



A revolutionary solution to the problems of etching PCBs! Unique sealed system minimises the risk, inconvenience, storage and disposal problems associated with the use of acid etchants — a complete kit designed to etch up to eight boards rapidly, visibly, effectively and SAFELY! £4.00 for a complete kit, £3.45 per kit in packs of 6.

Seno 33 — The Laboratory in a box


From your usual component supplier or direct from:

DECON LABORATORIES LTD.
Ellen Street, Portslade,
Brighton BN4 1EQ
Telephone: (0273) 414371
Telex: IDACON BRIGHTON 87443

All prices post & VAT inclusive. Data sheets free of charge.

GET HUNG UP!

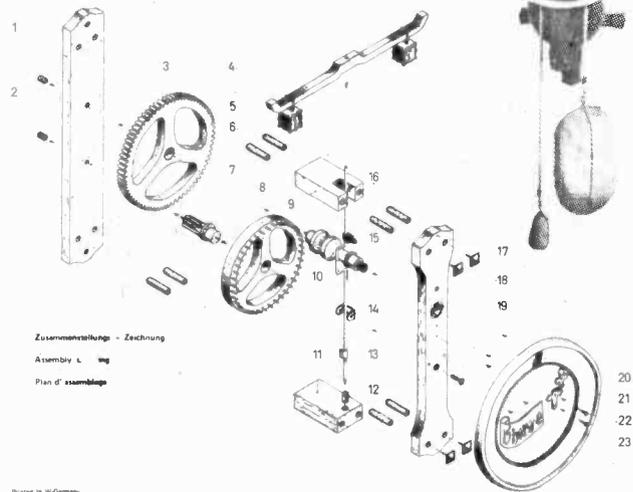Our new range of clock kits is based on designs hundreds of years old. These clock kits use wood, stone and iron to reproduce authentic "olde worlde" wall clocks in full detail. The kits contain all you need including glue, screws, etc., and very comprehensive instructions. This range complements our fully electronic clock kits.



PRICES (All inclusive)

	KIT	BUILT
Gothic Clock Kit—Diam. 6½"	£23.95	£36.50
Rotating Dial Kit—Diam. 6"	£19.95	£32.50
Wrought-Iron Kit—Diam. 5½"	£46.35	£69.50
Wooden Wheel Kit—Diam. 6½"	£31.50	£45.25
Knight Clock Kit—Diam. 7½"	£39.50	£62.45
Oak Foliot Kit—Diam. 14" (As illustrated)	£89.50	£125.00

For coloured Brochure please send 15p stamps.
Completed clocks can be seen at our offices

★ Use special offer coupon on Page 000 to save 15%

BYWOOD ELECTRONICS
68 Ebbens Road
Hemel Hempstead
Herts HP3 9QRC
Tel. 0442 62757

BYWOOD

PRICE LIST

CLOCK CHIPS

ALL PRICES EXCLUDE VAT AT 8%

NATIONAL

MM5309 7 seg + BCD with reset	1-9
MM5311 7 seg + BCD	5.69
MM5312 7 seg + BCD. 4 digit only	5.69
MM5313 7 seg + BCD	4.88
MM5314 7 segment	5.69
MM5315 7 seg + BCD with reset	4.88
MM5316 Non-mpx alarm clock	5.69
MM5318 7 seg + BCD (external digit select)	10.17
MM5371 Alarm clock 50Hz	3.36
MM5377 Car clock, crystal controlled. LCD	8.14
MM5378 Car clock, crystal controlled. LED	7.21
MM5379 Car clock, crystal controlled. Gas discharge	6.73

MOSTEK

MK50250 Alarm clock (12Hr+60Hz/24Hr+50Hz)	5.60
MK50253 Alarm clock (12Hr+50Hz/24Hr+50Hz)	5.60
MK50204 Stopwatch/Calculator	11.19
MK50395 UP/DOWN Counter—6 Decade	14.50
MK50396 UP/DOWN Counter—HHMMSS	14.50
MK50397 UP/DOWN Counter—MMSS 99	14.50

CALTEX

CT7001 Alarm/calender. 7 segment	7.30
CT7002 Alarm/calender BCD	7.30
CT7003 Alarm/calender 7 seg. Gas discharge	7.30
CT7004 Alarm/calender 7 seg	7.30

GENERAL INSTRUMENTS

AX5-1202 4 digit 7 seg.	4.76
AY5-1230 on-off — alarm, 7 seg	5.25

MHI CLOCK KITS

MHI-5309	1-9	MHI-50396	19.50
MHI-5311	7.35	MHI-50397	19.50
MHI-5314	7.35	MHI-7001	10.00
MHI-5318	6.60		
MHI-5378	7.35	MHI CASE Please include 25p post + packing)	2.95
MHI-50250	15.10		
MHI-50253	8.35	SOCKETS	
MHI-50204	8.35	18 pin	0.60
MHI-50395	14.00	24, 28 or 40 pin	1.00
	19.50	Soldercon strip sockets	0.30

DISPLAYS

LITRONIX

DL707, 704, 701	1.48
DL727, 728, 721	3.75
DL747, 746, 750	2.45

LITRONIX CLASS 11 PRODUCTS

DL707E, 704E	0.70
DL727E, 728E	1.80
DL747E, 750E	1.50

CASES (WITH PERSPEX SCREEN)

VERO 1 8" x 5½" x 3"	} £2.95+25p P&P
VERO 2 6" x 3¼" x 2¼"	

1-9 FUTABA PHOSPHOR DIODES

5LTO1 4 digit MPXD	5.80
5LTO2 4 digit static	5.80
5LTO3 5 digit MPXD	5.80

CLOCK MODULES — ALARM

MA1001F or MA1002F 12 hr. 50Hz	£7.97
MA1001H or MA1002H 24 hr. 50Hz	£7.97
SUITABLE TRANSFORMER	£0.90
MTX1001	

MHI DISPLAY KITS

MHI-707/4 (digit) 0.3"	1-9	MHI-727/6 0.5"	12.00
MHI-707/6 0.3"	6.60	MHI-747/4 0.6"	9.80
MHI-727/4 0.5"	9.50	MHI-747/6 0.6"	14.70
	8.50		

PAYMENT TERMS

Cash with order. Access, Barclaycard (simply quote your number and sign). Credit facilities to accredited account holders. Pro-forma invoices can be issued.


Please send 20p for post and packing.

ALL PRICES EXCLUDE VAT AT 8%
(EXCEPT MECHANICAL CLOCKS AS ABOVE)

BYWOOD

BYWOOD ELECTRONICS
68 Ebbens Road
Hemel Hempstead
Herts HP3 9QRC
Tel. 0442 62757

UNIVERSAL TIMER

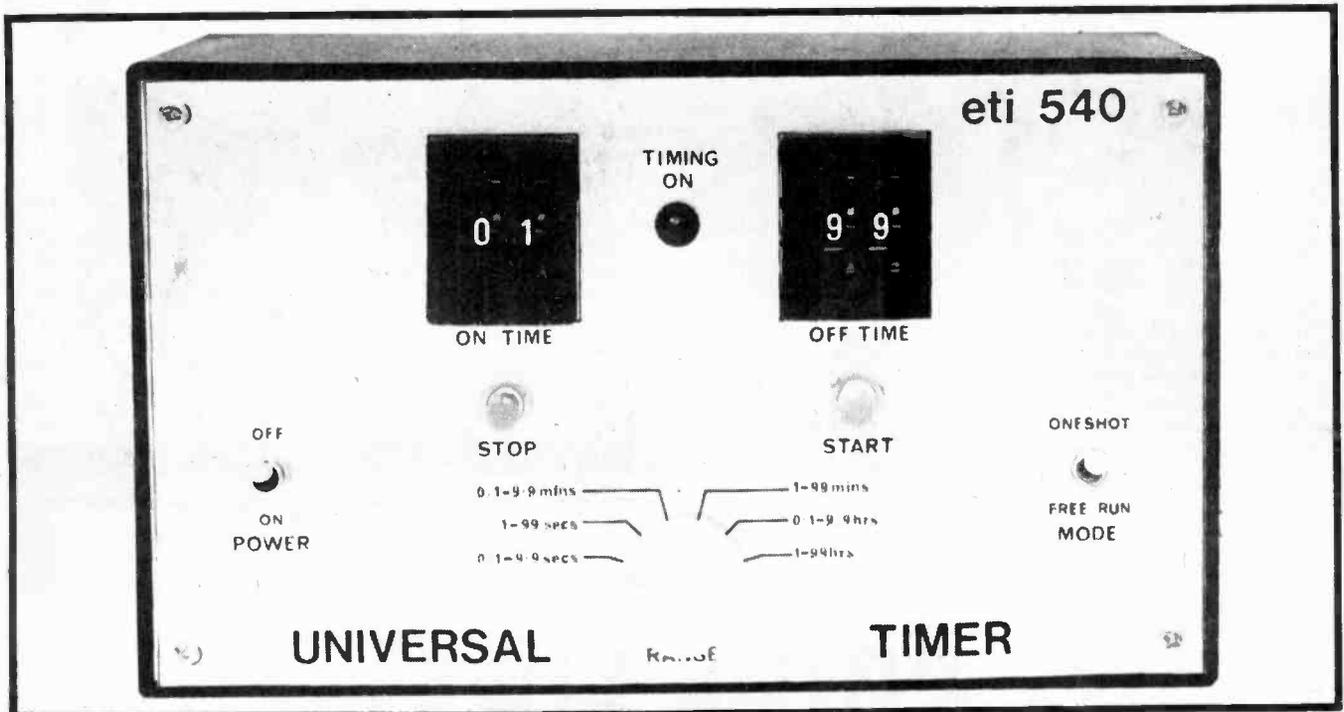

One tenth of a second to 99 hours. Both on and off times programmable. Manual or automatic operation, resettable at any time.

ETI 540

THE TIMING OF EVENTS and processes is becoming an ever-increasing necessity particularly in applications involving automation.

Unfortunately most timers are either specifically made for a particular application — and difficult to adapt to others — or have restricted timing range, accuracy and facilities.

The ETI Universal Timer described in this project is free of most such constraints. It is extremely flexible, accurate and versatile. Its timing range is from 0.1 seconds to 99 hours. Both 'on' and 'off' times can be programmed (for example 12 hours on and 47 hours off). It can be manually started, stopped, or reset at any time, can be set for automatic cycling or for single cycle operation. It may be triggered by an external source (light, sound or pressure transducer, etc). Finally, as the unit is digital —

the 50 Hz mains is used as the reference — timing accuracy is very high indeed, and a manual reset facility enables the timer to be synchronized with local time if so desired.

Clearly not all users will need all the facilities provided — so if the unit is required for a specific permanent use it is a simple matter just to leave out those ICs not required — several variations are described at the end of this project.

CONSTRUCTION

We strongly recommend that this unit be assembled using the printed circuit board shown.

Begin by fitting the links to the board as shown on the component overlay. Note that there are two points labelled 'a' and two points labelled 'b'. Link 'a' to 'a' and 'b' to 'b' using insulated hook-up wire

routed on the copper side of the board.

Mount the resistors to the board followed by the diodes, transistors, capacitors and finally the ICs. Take particular care to ensure that all the polarized components are orientated correctly — especially the integrated circuits.

Wires should now be attached to the board for later connection to the front panel switches. We used rainbow cable for the connections to the thumb-wheel switches as this makes the wiring easier and also helps to keep the wiring tidy. Mount the printed-circuit board into the case and mount the power outlet socket. Assemble the switches to the front panel and then interconnect the printed-circuit board, front panel and power socket in accordance with the interconnection diagram.

Finally after wiring the 240 Vac

power circuitry insulate all 240 V terminals with tape to ensure that there is no risk of personal contact when fault finding is required at any later date.

CUSTOMIZING

The unit need not necessarily be built in its complete form and many different modifications are possible to lessen the cost of the unit when it is to be used for one particular application only. The modifications required for a number of specific applications are described.

Specific fixed time — delete selector switches SW3 to SW6, and replace by wiring links from the appropriate outputs of IC4 and IC5 to the inputs of IC6/1 and IC6/2 respectively. The range switch may also be omitted by installing a link between the appropriate output of IC1 to IC3 and pin 13 of IC4.

Single shot operation — connect both inputs of IC6/2 to ground and omit switches SW5 and SW6.

Timing 99 hours or less — omit IC3 and connect inputs of IC7/3

and IC7/4 to ground.

Timing 99 seconds or less — omit IC2, IC3 and IC7.

External triggering — simplest way is a relay contact in parallel with start or stop button.

The main consideration when making any changes is that the logic is CMOS and any unused inputs must be connected to ground or to +12 volts to prevent damage to the IC (which may overheat with unconnected inputs).

SPECIFICATION ETI 540

MODES

- Freerun
- On/off (note 1)
- One shot
- Manual override (note 2)

TIMING RANGE

0.1 seconds to 99 hours (note 3)

ACCURACY

Mains synchronized


OUTPUT

240 volts ac relay switched


Note 1. Both on and off times are variable independently.

- Note 2. Unit may be stopped or started at any time. If the appropriate button is pressed whilst in the same mode the timing is recommenced.

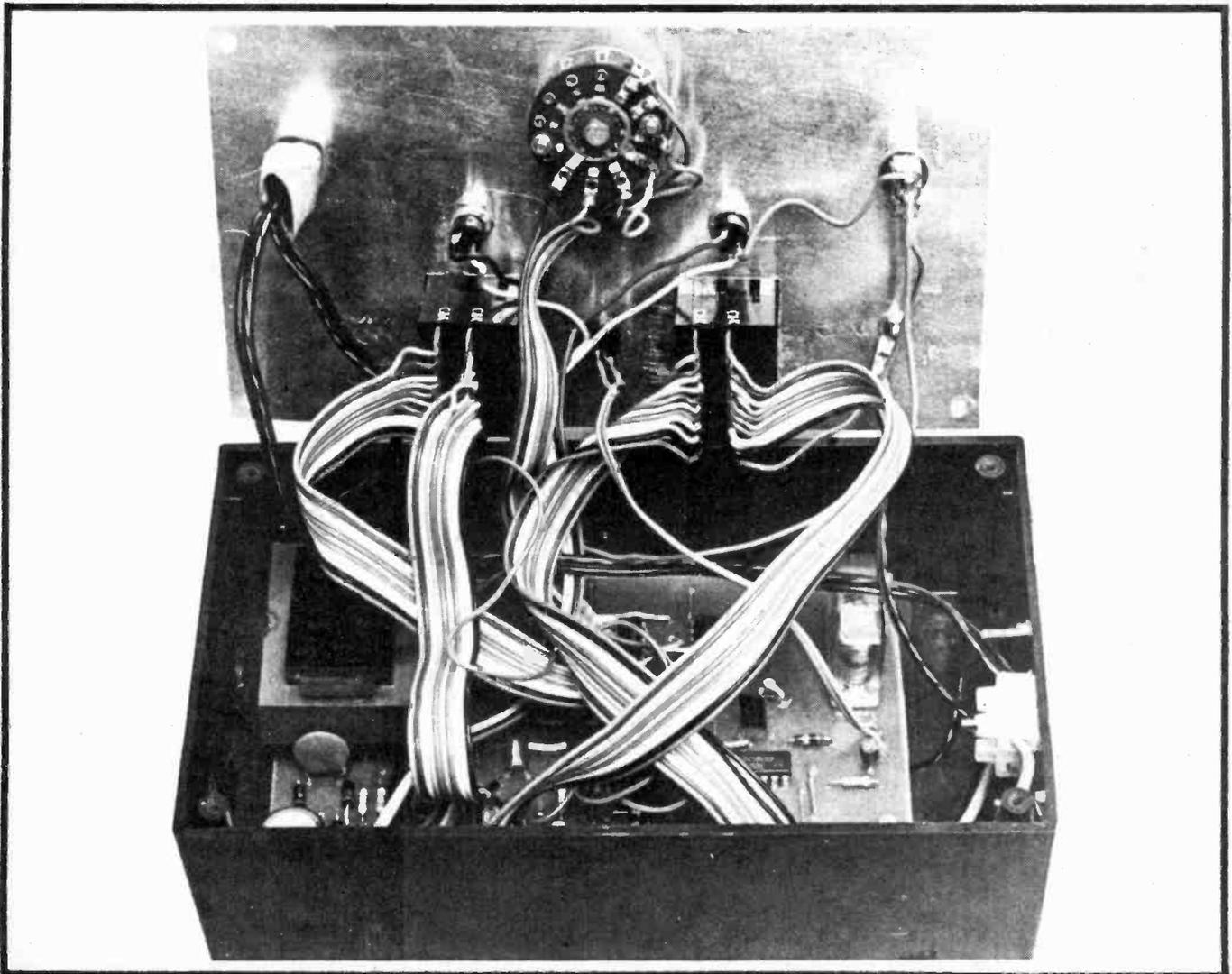Note 3. Timing is adjustable by a common coarse control which gives ranges having a full scale of 9.9 seconds, 9.9 minutes, 99 minutes, 9.9 hours and 99 hours. Each range is adjustable from 1 to 99 that is one second on and 99 seconds off is possible whereas one second on and two minutes off is not (different coarse range is required).



UNIVERSAL TIMER

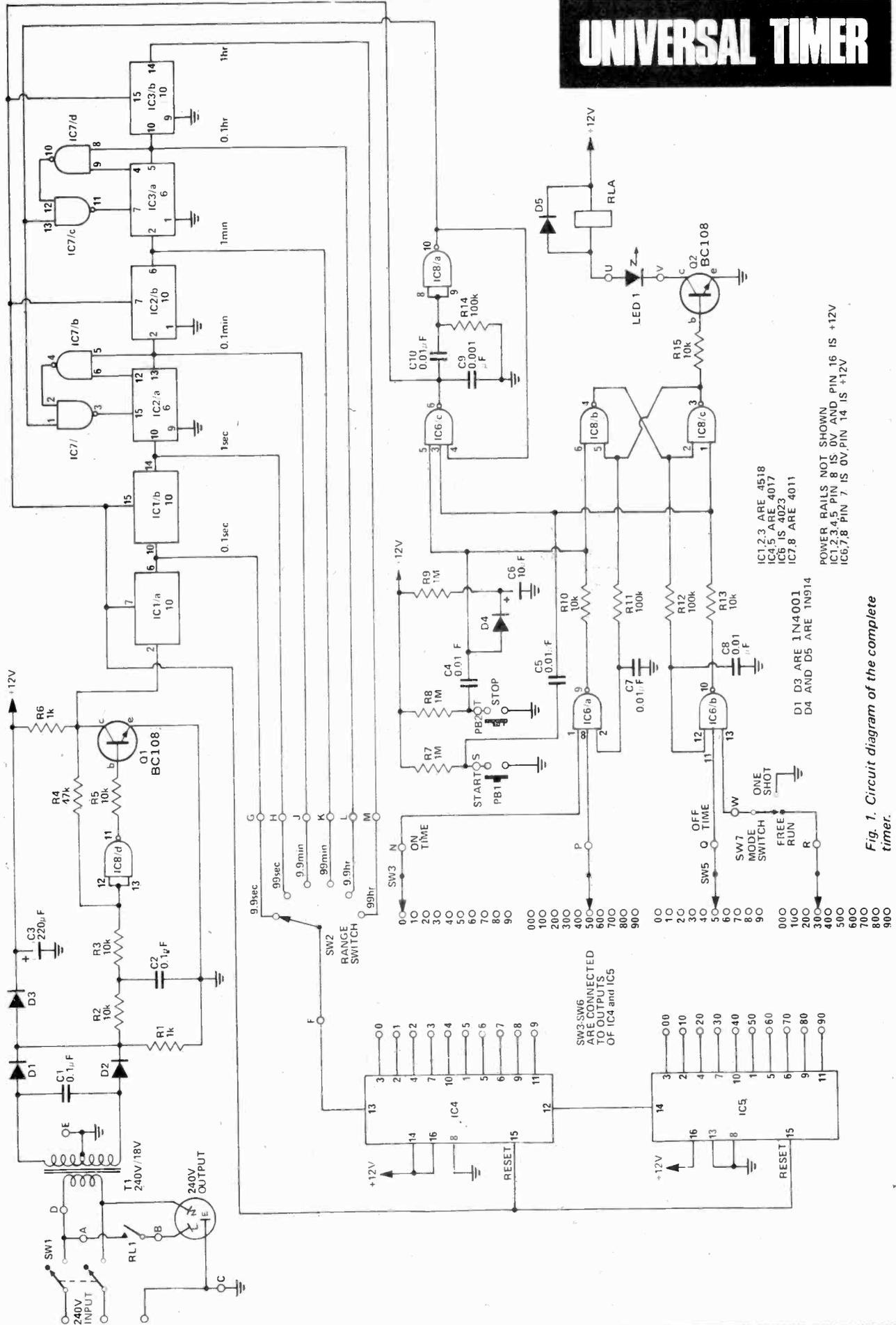

IC1,2,3 ARE 4518
 IC4,5 ARE 4017
 IC6 IS 4023
 IC7,8 ARE 4011

POWER RAILS NOT SHOWN
 IC1,2,3,4,5, PIN 8 IS 0V AND PIN 16 IS +12V
 IC6,7,8 PIN 7 IS 0V, PIN 14 IS +12V

Fig. 1. Circuit diagram of the complete timer.

HOW IT WORKS — ETI 540

The 240 Vac is reduced to 12 Vdc by transformer T1 and diodes D1 to D3. Diode D3 isolates the smoothing capacitor C3 from the rectifiers and therefore 100 Hz ripple appears across R1. This waveform is used for the basic timing reference for the timer. To operate the counting ICs reliably a very fast rise-time waveform is required at the clock input. This is obtained by feeding the 100 Hz to a Schmitt formed by IC8/1 and Q1. Capacitor C2 is included to prevent the control tones superimposed on the mains for the control of hot-water services from upsetting the timing accuracy.

The 100 Hz from the Schmitt trigger is divided by 10 by IC1/1 to give a 10 Hz or 0.1 second output — the first required. Note that due to the low frequencies involved from now on the outputs will be referred to as time periods not as frequencies. A second divide by ten stage is used to give a one second output. A division by six is then performed by IC2/1 with IC7/1 and IC7/2 being used to decode the six count and reset the counter. This gives the one minute (or sixty second) period required. Further divisions of 10.6 and 10 are used to provide the six outputs required to select periods from 0.1 seconds to one hour.

One of these six outputs is selected by the range switch SW2 and is fed to a 4017 IC — the first of a pair of decade counters which have ten decoded outputs. The ten outputs of each IC go high in turn for one clock period each. As the two 4017 ICs are in series, a total division of 100 is obtainable. We have labelled the outputs of IC4 and IC5 as 0 to 9 and 00 to 90 respectively. IC4 is triggered by the clock enable as negative edge triggering is required. The second IC is clocked normally by the carry output from IC4.

We pause at this point to go straight to the control output which is via a relay RL1, this in turn being controlled by the flip-flop made up of IC8/2 and IC8/3. This flip-flop can be controlled either manually by PB1 (manual on) and PB2 (manual off) or automatically by IC6/1 and IC6/2. To toggle the flip-flop automatically the output of either IC6/1 or IC6/2 must be low and for the output to be low the three inputs must all be


high. This occurs only when the number selected by SW3 and SW4 (for IC6/1) and SW5 and SW6 (for IC6/2) is held by the counters IC4 and IC5 and the third input from the flip-flop is used to ensure that the off-time of the relay is controlled only by the off-time selector switches. A small time delay is incorporated in the signal back from the flip-flop to avoid the ambiguity that could arise with equal times.

If the output of either IC6/1 or IC6/2 goes low the monostable formed by IC6/3 and IC6/4 is triggered and its resultant output is used to reset all the counters to zero. This reset also occurs if either of the manual push buttons is pressed. The push buttons are coupled into the logic by capacitors so that only the initial part of the press actuates the logic and there is therefore no dependency on the length of time for which the button is pressed.

The sequence of events is as follows assuming that initially the switches are set for 25 seconds on and 14 seconds off.

On first switch-on C6 ensures that the flip-flop is toggled into the off state and also that the counters are all reset to zero. The control inputs from the flip-flop to IC6/1 and IC6/2 are low and high respectively. Therefore until the flip-flop changes state only IC6/2 can have the three high inputs necessary to provide a low at the output. Meanwhile the counters IC4 and IC5 are counting up at the rate of one count per second. After 14 seconds all three inputs to IC6/2 are high and the output goes low toggling the flip-flop. The monostable is then triggered and all counters are reset to zero. This removes the three high inputs to IC6/2 and the output goes high again. The pulse output of IC6/2 is very narrow and is about a microsecond long. As the flip-flop has now changed state the relay has been closed and IC6/1 has been enabled (control input to pin 2 now high). After 25 seconds all the inputs to IC6/1 are high and the same procedure as before resets the counters and changes the state of the flip-flop.

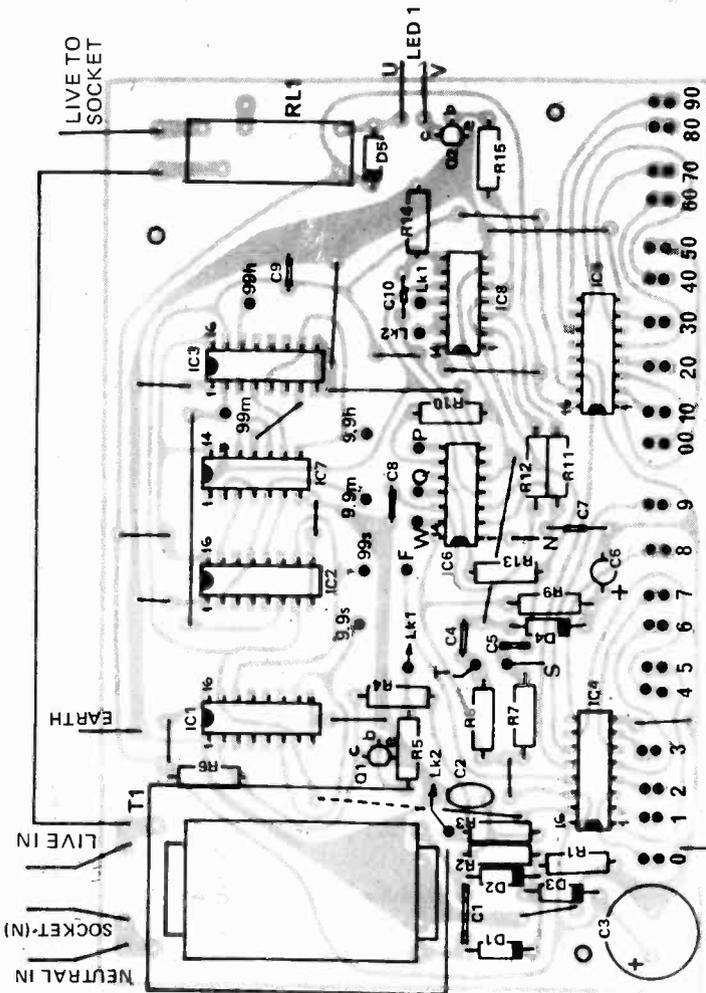In the one-shot mode of operation one input of the off timer is grounded and, the off time procedure is effectively disabled. The only way that the timer can now start is for the manual start button to be pressed.



PARTS LIST — ETI 540

Resistors	1 k	5%	Transistors	BC108 or similar
R1	10 k	"	Q1, Q2	
R2,3	47 k	"	Integrated Circuits	
R4	10 k	"	IC1-IC3	4518
R5	1 k	"	IC4,5	4017
R6	1 M	"	IC6	4023
R7-R9	10 k	"	IC7,8	4011
R10	100 k	"	Transformer	240 V/18 V CT RL18/5 VA
R11,12	100 k	"	pc Board	ETI 540
R13	100 k	"	Relay, single pole	280 Ω coil 240 V 5A contact
R14	10 k	"	Switches	
R15	10 k	"	SW1	double pole toggle switch
Capacitors	0.1 μF	50 V disc ceramic	SW2	single pole 6 position rotary
C1	0.1 μF	polyester	SW3-6	single pole 10 position *
C2	220 μF	16 V electro	SW7	single pole toggle
C3	0.01 μF	polyester	PB1,2	single pole "make" push buttons
C4,5	0.01 μF	polyester		
C6	10 μF	16 V electro		
C7,8	0.001 μF	"		
C9	0.01 μF	"		
C10	0.01 μF	"		
Diodes	1N4001 or similar			
D1-D3	IN914 or similar			
D4,5	TIL209 or similar			
LED1				

Measurements

Misunderstandings, misuse, mistakes, mirth and misrepresentation
by Dr. Peter Sydenham



The company balance sheet — what the numbers reveal is interesting but what they hide is vital. (Courtesy John Staunton)

MEASUREMENTS are useful as tools of control of the routine, or as a basis for gaining new knowledge.

Once a particular kind of measurement has been established as necessary, two things can happen. It either remains as is, being adequate for the daily need, or alternatively, constant effort is made to improve it in order to gain the benefits that might accrue from a better determination.

WHAT IS A MEASUREMENT?

To some people measuring implies attaching sophisticated black boxes to a system in order to obtain data about it. Others see the opposite — the use of simple tools such as a ruler to put data to an object. Both are right in a narrow sense. A first basic rule is that *measurement is the comparison of an unknown magnitude of a quantity with an agreed standard declared as the unit, the measure coming forth as the difference expressed in numerical form.*

The most basic number is a binary kind having just two states. The crudest measurement we can thus make is one that provides a yes or no, smaller or larger, up or down, go or no-go, true or false types of answer. Enormous effort can be expended to obtain (or try to obtain) such an answer in many cases. Indeed, it is this kind of measurement that is often the hardest to make. Politicians would give the earth to be able accurately to predict the outcome of an election, social-scientists would be enthralled at the prospects of certainty of success of implemented crime-control measures, geographers seek to know which factors affect what.

As the understanding of a subject is improved — by the use of simple tests giving yes-no type answers — it becomes possible to deploy more and more advanced techniques of hardware and software. The difference between the standard and the unknown (called the measurand) becomes expressible in continuous rather than two-state number terms. For example, the

Measurements

battery in the car will not turn the starter motor because its voltage is *too low* (the two-state situation has been extended by a superlative). Measurement using a voltmeter enables us to say that the battery output is only 6.6 V instead of 12.0 V (the designer's standard requirement now expressed in numbers on a continuous scale).

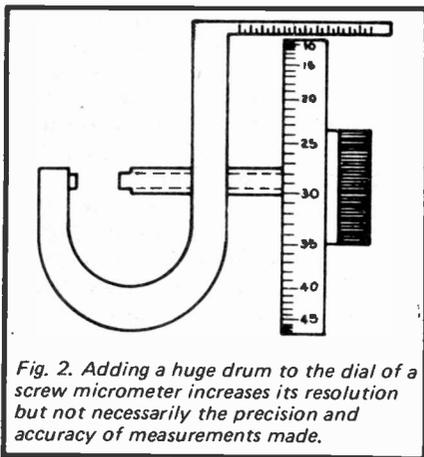


Fig. 2. Adding a huge drum to the dial of a screw micrometer increases its resolution but not necessarily the precision and accuracy of measurements made.

BASIC MEASUREMENT TERMS

Even though we have not yet talked in terms of sophisticated measurements or measuring equipment, the above explanation begins to reveal the need for some definitions of certain facets arising in the intercomparison

process. (We need more standards to define standards!)

The misuse and abuse of basic terminology is rife. A first group of terms relates to the description of results provided by the process.

Resolution — at the finest scale available from a particular process of comparison — is the ability to resolve between successive increments in the chosen scale. A person using a mercury-thermometer might be able to resolve, say, 0.1°C intervals, subdividing these intervals into two divisions by eye gives a resolution of 0.05°C. By adding an optical magnifying system (or mechanical gain in, say, a micrometer — as depicted in Fig. 2) which has an inscribed scale at its focal plane, it is possible to raise the resolution 10 times or higher.


The unexperienced, unenlightened measurer will often quote this fact as a measure of how good a device is for measuring with but having resolution may not mean much in reality. It is very much the first basic requirement of comparison, but if it lacks accuracy the answers can be quite wrong. For example, if the optical magnifier on the thermometer has a badly ruled scale or optical distortion each increment will not be equal. Furthermore, the thermometer is supposed to measure temperature but, in fact, pressure of the air or liquid around it will also cause the mercury to rise or fall a little.

Precision — Two men argue as to

which is the better rifle-shooter. It is to be settled by a contest on the range. The standard of excellence is to place the shots into the bulls-eye of the target but the game places the contestants sufficiently far back from the target that this is not easy to achieve. If it were, and each man placed all shots in the bulls-eye, the only assessment made would be that both were equally good. This situation lacks resolution to discriminate between them; the range is increased to increase the resolution. Thus emerges an important second rule of measurement — *there must be adequate resolution to a measuring process or little will be learned from the measurement.*

Each fires his group of shots and the two sets are intercompared. The first thing to be seen is that one group lies in a smaller total enclosed area on the target — as shown in Fig. 3a — but (in our chosen case) none is in the bulls-eye. The other shooter, on the other hand, has shots which are contained in a much larger circle, with one actually in the bulls-eye, as shown in Fig. 3b. The argument begins as to who is the better shot. The better shooter is probably the first, not the second, for his precision, that is, his ability to keep on the same spot, is much better than the other person. *Precision then, as the third rule, is the measure of scatter of values obtained in a test.*

In this case the first shooter would

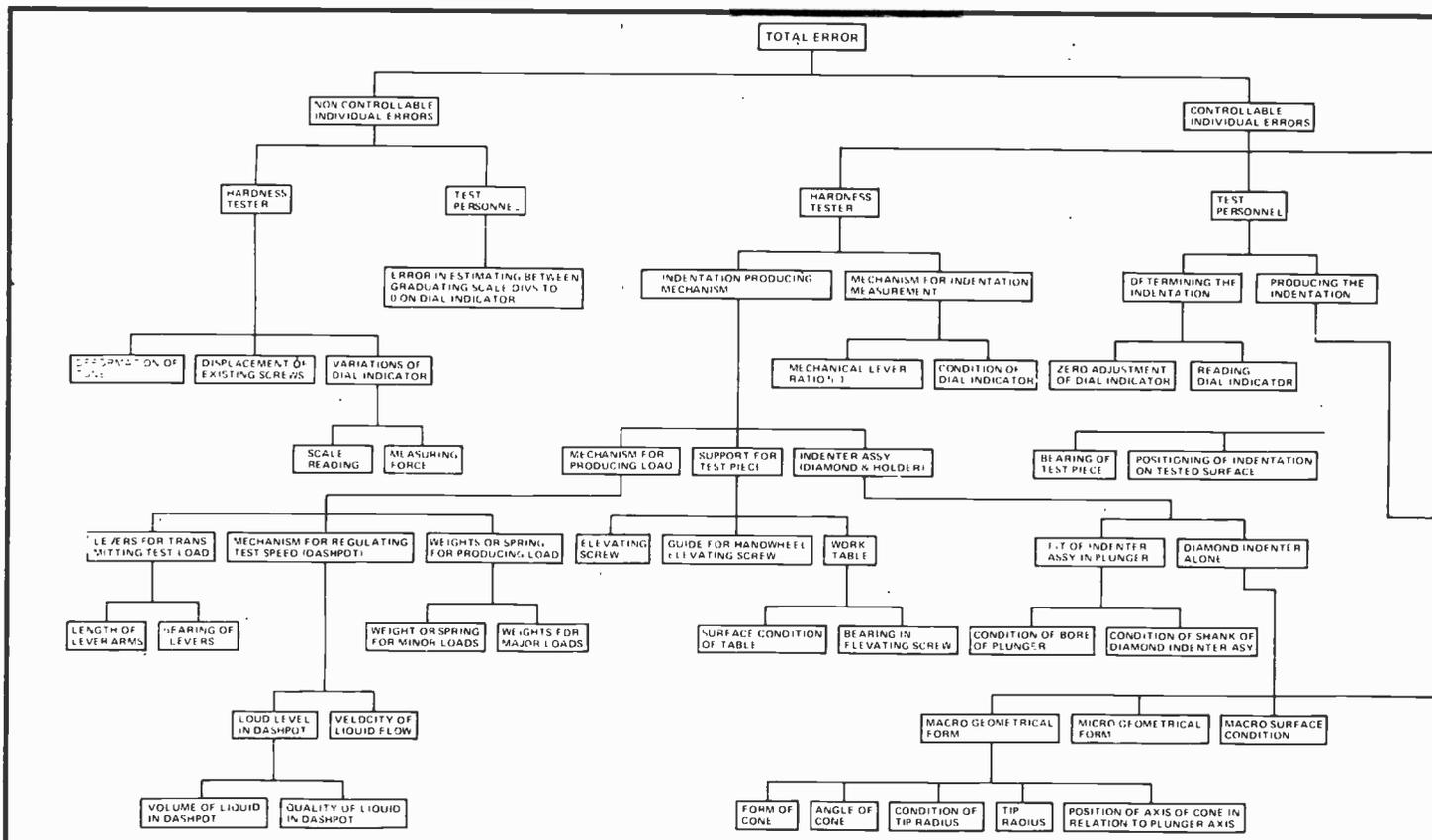

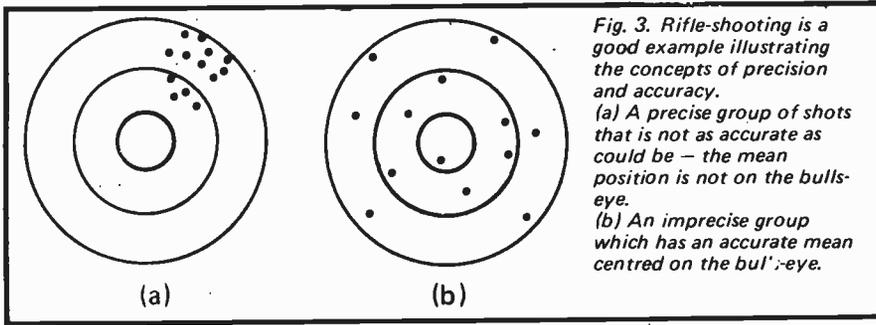


Fig. 3. Rifle-shooting is a good example illustrating the concepts of precision and accuracy.
 (a) A precise group of shots that is not as accurate as could be - the mean position is not on the bulls-eye.
 (b) An imprecise group which has an accurate mean centred on the bulls-eye.

be able to make a correction to his sight or allow for cross wind in order to move his group over to put more on the bulls-eye than the other person. The less precise shooter could not improve his accuracy. This leads us to what is accuracy in measurement.

Accuracy - In the shooting exercise the aim of each shooter was to reduce the distance between his individual shots and the bulls-eye - which is defined as the standard in this determination. The measurement that gives the closest value to the agreed standard is the most accurate. But in the example above the less precise shooter is, in fact, the most accurate if they decide that the averaged central position of the group is the criteria chosen.

In electrical terms a voltmeter may provide precise values but be very inaccurate due to a bent pointer or an altered value series ballast resistor.

Thus a fourth rule can be seen: *Precision and accuracy are quite*

different descriptive terms. These are too often confused. Excellent precision does not imply equally fine accuracy and vice versa. It is always necessary to provide adequate resolution in order to determine the desired fineness of precision and to state the accuracy precisely enough.

TYPES OF ERRORS

The numerical value between the standard value and the measurand is termed the measurement error. Error magnitudes may affect the degree of precision and the accuracy obtained. They arise from many different sources, ranging from clearly identifiable processes, to never-identified mechanisms. Ideally, the measurer desires to eliminate all errors but the fact of life is that the closer we investigate a process in order to improve its resolution, precision and accuracy, the more errors loom up. Numerous sources of error can be identified with: even the simplest of processes. Several years ago a study was made of the make-up of total error of a simple measurement (in principle at least) involving the pressing of a hardened point into a surface to measure its relative hardness by the degree of penetration - the Rockwell-C hardness test in this case. Something close to 40 sources of error were identified (as shown in Fig. 4).

There are three main classes of error into which similar errors can be typified. Each has to be eliminated, reduced or lived with in different ways. A fifth rule of measurement is that *errors limit the usefulness of a measurement* and need to be reduced to tolerable levels.

Systematic errors - these are the derivations of values that always occur in the same way, and for which a

corrective value can be applied to get the right value once the magnitude of the error is known. The rifle shooter resets his sights, the bent pointer is straightened. Or, the voltage reading can be corrected by adding the difference due to a bent pointer, or multiplied by a constant to make up for a wrong value series ballast resistor. It is, however, not necessary to know what causes the systematic error, only what its rules of occurrence are so that it can be allowed for.

Random errors - In strong contrast are errors that appear as the name implies, with random amplitude and sign. It is by definition impossible to predict what the random error will be on an individual value basis - the best that can be done is to place a level of probability of such and such a value arising at a certain time. In other words, seen as a group rather than a single occurrence of errors, it is possible to be reasonably certain about the value of such parameters as the *mean value* of the group and the *spread* of the group, but never the facts about the individual until it has occurred.

Random values follow statistical laws for collections of events. The most common occurrence of random error is with the so-called Gaussian distribution (also called top-hat or normal distribution). This form of error has a symmetrical profile for the plot of probability of occurrence of a value versus value changing as shown in Fig. 7. The peakiness of the curve is a measure of the spread of values and from the mathematical laws of this type of error it is possible to define a term that expresses the peakiness - the standard deviation (or s.d. or δ). In practical terms a s.d. of 1 means the limits $\pm 1\delta$ contain 68 per cent of values, $\pm 2\delta$ limits contain 95 per cent and $\pm 3\delta$ limits contain 99.7 per cent. If the chance of a value occurring is 50 per cent within a given limit and 50 per cent outside this limit then the probable error - has a value of 0.67 δ .

It is conventional practice to quote the random error of a process in terms of the standard deviation as this conveys the tightness of the random error in the measurement situation.

A trap that exists, however, is that not all random processes are Gaussian in distribution. Nuclear radiation particle occurrence, for instance, has a lop-sided distribution (Poisson) and another quite different set of mathematical formulae describes the chance of occurrence of values. In the majority of cases Gaussian statistics apply - white noise for example in electronic circuits.

Personal errors - To be correct these

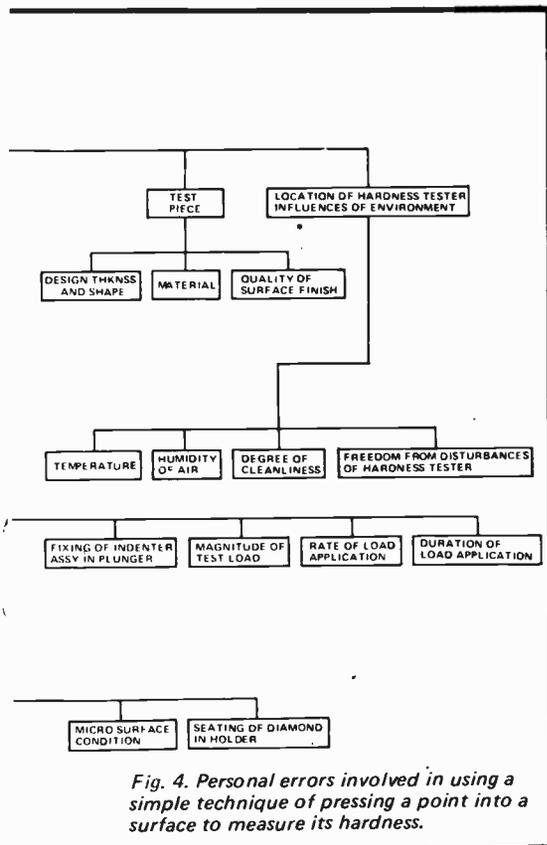


Fig. 4. Personal errors involved in using a simple technique of pressing a point into a surface to measure its hardness.

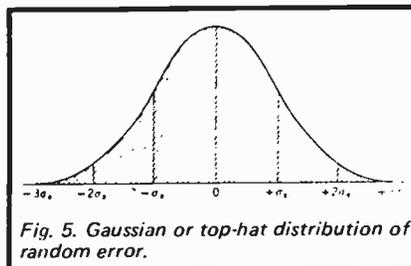


Fig. 5. Gaussian or top-hat distribution of random error.

Measurements

reduce to random or systematic causes of error, but by treating them as a specific group the deleterious effects of human observation are emphasised. There are numerous sources of personal error. The individual making the measurement may view a scale line at a different angle to another person thus introducing parallax error, the way of driving an adjustment screw dial may be different to another — moving from the opposite direction to the mark or at a different speed could introduce slightly differing values from one observer from another. In surveying practice it is quite normal for the theodolite or level operator to repeat the observation from the opposite direction. This reduces systematic errors of calibration by differential cancellation, thus reducing the personal error.

TRACEABILITY

We saw above how a standard must be created as the sole legitimate value of the unit, and how a measurement was made by comparing the unknown against this.

If the standard varies, then so does the measurement value. In the case of physical standards such as length, mass and time it is possible to provide some defined physical apparatus that acts as the standard. In some disciplines this is not so easy. Biological experiments use a control group — a group of test subjects that do not undergo the test given to the test group — as the temporary standard. In economic studies even the concept of a control group is hard to create, for we cannot ask half the country's population to stay the same economically and isolated at the same time as the other half have their financial situation altered. We would probably learn more about economic procedures if we could!

Whatever the standard it must be adequately constant for a long enough duration and be usable. For physical standards the demand for use is so great that it is necessary to have a sole fundamental standard controlling many working standards in each country, these controlling, in turn, the field standards used by individual laboratories. These control the value of the unit actually used in practice. Thus we can have as many as five or six steps between the fundamental standard and the working instrument. Each stage loses some accuracy so international standards must be maintained in the highest state

possible by a national laboratory devoted to this task — the National Measurement Laboratory in Australia, the National Physical Laboratory in Britain, the National Bureau of Standards in the USA, etc.

Clearly if this tree of standards were not strictly controlled any individual unpoliced link could upset the sequence. The process of traceability is used to ensure that a measurement (at least with high-performance instrumentation) is traceable right through to the fundamental standard with the loss in accuracy being designed at each level. This concept is vital to the maintenance of standards in practical use.

MIRTH

Looking back in time, man's measurement endeavours include some highly amusing methods of producing standards. One early standard of length for the inch was 'three barleycorns, round and dry'. Another standard of length was prescribed by taking the first 16 men as they came out of church, making them stand with their left feet end to end — this gave a standard 'rod'. Not quite as bad as it may seem for at least a vaguely reproducible average was obtained. But the last man out defined the foot! In 1800, in Germany, there were 112 different size standards used to define just one common unit of length.

A peculiarity still with us today, concerns the gallon — the US gallon being smaller than the British Imperial gallon. In fact the US gallon is the earlier British gallon — the Pilgrim Fathers used the then-smaller Imperial gallon when they emigrated to the Americas in the 15th century. The Americans retained the original standard (more or less) but the British one was subsequently re-defined.

A 14th century treatise related an English penny — called Sterling — as the same weight as 32 grains of wheat. Thus in a very round-about way 20 pence make an ounce, 12 ounces a pound, eight pounds make a gallon of wine and eight gallons make a bushel of London.

Today some of our basic standards are still based on physical apparatus that is subject to damage or change. The standard (prototype as it is called) kilogram is still a piece of metal held in Paris. Most standards, however, can now be reproduced from a stated description of an apparatus which can be used to replicate the standard to within extraordinarily fine limits. Length for instance is defined as so many wavelengths of radiation from a Krypton discharge lamp.

Some extraordinary anomalies in measurement occur in every-day life —

the most frequent being of a kind that imply an accuracy that does not exist.

A recent advertisement for a certain make of car — one that would be expected to be more careful over advertisements, says: "The car responds as quick as adrenalin". This is

- A recipe in a recent issue of an Australian magazine dutifully translated 'take 5 oz of flour' as 'take 141.75 grams' and half a pint of milk as '.354 litres'.
- Motoring magazines frequently quote standing quarter mile (or 400 metre) acceleration runs to three decimal places of one second. Yet one overseas magazine to my certain knowledge measures the required distance simply by a member of the staff pacing it out!
- A 'hundred thousand ton' ship was recently described in a daily paper as displacing '101,606.44 kilograms' — leaving aside that this contained an error of several orders of magnitude — the conversion implied that the original displacement was known almost exactly.
- After hearing that an aircraft was 'one minute late' I'm still trying to determine at precisely which point in its journey that an aircraft officially 'arrives'.
- Until very recently the altitude record for aircraft (and balloons) was recorded to two decimal places of a metre. Yet the actual height recorder was an aneroid instrument with an accuracy at best of plus or minus 0.1 per cent — thus the actual recorded height would not have been known to within 50 to 100 metres!
- A British millionaire was recently described as being worth \$1.612 million dollars!

an entirely meaningless expression. It states nothing of substance. The same advertisement states that the car is "20 per cent safer than the safest car on the road". How do we measure safety in quantitative number terms? It is also said to have "precise rack and pinion steering" — let's hope so! And later: "Every one of its over 5000 parts is the result of adaption and re-adaption of . . . s" pioneering safety programme. It is very doubtful if every single one has been such — if so the designers need sacking for never getting there first-time in their design. Finally, "you need greater reserves of power to outdistance danger" — what a meaningless jumble of measurement statements! ●

SUMMERTIME SAIL-AWAY

SCORCHER
7490.25p each.

WITH OUR **SIZZLING PRICES!!**



PAK OFFERS

ALL U PAKS, UIC PAKS +ULIC PAKS. AS SEEN IN OUR PREVIOUS ADVERTS AVAILABLE AT 40p PER PAK.

ZENER PAKS

400mW PAK No. 1 containing 20 3v-10v 2 containing 20-11v-33v **£1.00 PER PAK***

RESISTOR PAKS

R1 50 1/2w 100 ohm-820 ohm
R2 50 1/2w 1K-8 2K
R3 50 1/2w 10K-82K
R4 50 1/2w 100K-1M

BUY ONE OF EACH SPECIAL PRICE:

£1.60 the 4*

R5 30 1/2w 100 ohm-820 ohm
R6 30 1/2w 1K-8 2K
R7 30 1/2w 10K-82K
R8 30 1/2w 100K-1M

BUY ONE OF EACH SPECIAL PRICE

£1.60 the 4*

CAPACITOR PAKS

E1 18 ELECTROLYTICS 47µF-10µF
E2 18 ELECTROLYTICS 10µF-100µF
E3 18 ELECTROLYTICS 100µF-680µF

BUY ONE OF EACH SPECIAL PRICE

£1.20 the 3*

MC1 24 CERAMIC CAPS 22pf-82pf
MC2 24 CERAMIC CAPS 100pf-390pf
MC3 24 CERAMIC CAPS 470pf-3300pf

MC4 21 CERAMIC CAPS 4700pf-0.047µF

BUY ONE OF EACH SPECIAL PRICE

£1.60 the 4*

OPTOELECTRONICS

L.E.D. DISPLAYS PHOTO TRANSISTORS
DL707 0.3" .70p OCP71 5 for £1.00
DL747 0.6" £1.50 L.E.D.'s
DL727 0.5" RED TIL209 0.125" or FLV117 0.2" 5 of EITHER 50p

DOUBLE DIGIT I.T.T. NIXIE TUBES 5870 ST. 1" FIGURES LOWEST PRICE 5 for £2.00

PHOTO CELLS ORP12/NSL4931 38p ea. 0.2" 5 of EITHER 75p

CLIPS FOR LED'S. 0.125" ONLY. AVAILABLE AT 10 for 20p

IC's

NE555 TIMER 38p
NE556 Dual Timer 80p
709P 8-PIN DIL 15p
741P 8-PIN DIL 18p
747 14-PIN DIL 36p
748P 8-PIN DIL 25p
*A711 Dual Comparator 25p
*7230T op. amp. T099 25p
*72770 op. amp T099 50p

IC SOCKETS

BPS8 09p
BPS14 10p
BPS16 11p

TRIACS

2A/400PIV 50p
6A/400PIV 55p
10A/400PIV 75p

DIACS

BR100 15p
D32 15p

THYRISTORS

T05 15p
1A/50PIV 25p
1A/400PIV 36p
1A/600PIV 36p

T06 5A/50PIV 25p
5A/400PIV 40p
5A/600PIV 50p

T048 16A/50PIV 30p
16A/400PIV 60p

BRIDGE RECTIFIERS 2A/50 volt 25p
2A/100 volt 30p
2A/200 volt 35p
2A/400 volt 40p
2A/1000 volt 50p

F.E.T.s 2N3819 12p
2N5458 (MPF104) 15p

DIY PRINTED CIRCUIT KIT Normal Price **£7.80**

SALE PRICE **£5.50**

TRANSISTORS

AC127 10p *BF199 12p
AC128 10p BF257 18p
AC141K 20p BF258 19p
AC142K 18p BF259 20p
OC71 09p 8FX29 18p
BC107 06p BFY84 15p
BC108 06p BFY50 15p
BC109 06p BFY51 15p
*BC113 08p BFY52 15p
*BC148 08p 2N696 10p
*BC149 08p 2N697 11p
*BC157 11p 2N698 11p
*BC158 10p 2N706 06p
*BC159 10p 2N708 08p
*BC169C 07p 2N1613 15p
2N1711 15p
2N2219A 15p
2N2369 12p
2N2369A 12p
2N2905A 13p
*2N2926g 09p
*2N2926y 08p
*2N2926008p
2N3053 15p
2N3055 36p
*2N3702 08p
*2N3703 08p
*2N3704 09p
*2N3705 08p
*2N3706 08p
*2N3903 08p
*2N3904 08p
*2N3905 09p
*2N3906 09p
*2N4058 08p
*2N4060 09p
BD116 50p
BF167 10p *2N5172 09p
BF173 10p *ZTX300 05p
*BF194 09p *ZTX500 08p
*BF195 09p *ZTX107 05p
*BF196 10p *ZTX108 05p
*BF197 10p *ZTX109 05p
BF198 12p

DIODES

OA10 15p IN4002 3p
OA47 5p IN4003 3 1/2p
OA81 5p IN4004 4p
OA91 5p IN4005 4 1/2p
OA200/ IN4006 5p
BAX13 5p IN4007 6p
OA202/ IN4008 08p
BAX16 5p 3 AMP IN5400 11p
IN914 4p IN5401 12p
IN4148 4p IN5402 13p
IS44 4p IN5403 14p
IS920 5p IN5404 15p
IS923 5p IN5405 16p
IS970 5p IN5406 17p
BA100 6p IN5407 18p
BA148 10p IN5408 20p
IN4001 2 1/2p

VAT CHAT

Please add 12 1/2% to prices marked *. Remainder add 8%.

UNIUNCTION TRANSISTORS

U146, TIS43 12p

VOLTAGE REGS

L129/A7805 85p
L130/A7812 85p
L131/A7815 85p

DYNAMIC CASSETTE MIKE

With 2.5mm and 3.5mm Jack Plugs

£1.50*

I.C. INSERTION EXTRACTOR TOOL

32p!

CONTAINS 6 Pieces copper laminate, box of etchant powder and measure, tweezers, marker pen, high quality pump drill, Stanley knife and blades, 6" metal rule.

FULL easy to follow instructions.

P&P
Postage & Packing add 25p.
Overseas add extra for airmail.

BI-PAK
P.O. BOX 6, WARE, HERTS.



RTVC

CASSETTE REVIEW

WE MUST ADMIT to some initial scepticism on first encountering this deck. The price puts it well down into those murky regions known as the 'junk jungle', an area notorious for huge discounts and spectacular failures.

However, RTVC are well known for the reliability of their goods, the best known perhaps being the car radio the 'Tourist'. The company thus has to contend with people's wary attitudes at these price levels, and are paying for being somewhat of an exception to a rule. It was thus with a great deal of interest we approached the cassette unit supplied to us.

Looking over the manufacturer's specification the unit would seem to be suited to the budget audio market, and we were given no reason to quibble with the spec during our dealings with the machine, except to say it is a little vague and if detailed closer could only benefit RTVC.

KITTED OUT

On arrival the kit consists of a main assembly, PSU board, mains transformer and assorted components, i.e. level meters, rotary level controls and knobs, input (DIN) and headphone socket, mains switch and knob. Wire and the few attendant resistors are also provided.

The instruction sheet included is comprehensive enough to show a suggested layout, and offer some sound advice on boxing up the player. (Ours went into the inevitable aluminium box from the equally inevitable H. L. Smiths!). RTVC's layouts are very sensible and should be followed by all but the genius class amongst you! Wiring diagrams are given, as are photographs of the inter connections. Sections cover 'Housing', 'Connections', 'Setting Up' and 'Trouble shooting'.



HOUSE CONNECTIONS

Wiring up the kit entails only connecting the main (pre-assembled) circuit board to the ancillaries. After mounting the transport and the PCB's, the wiring is undertaken, and the order used in the instruction sheet is best followed. Each connection is dealt with, and the steps are sufficiently clear to circumnavigate most problems. If the description of what you've got to do sounds reasonable to you, then probably you'd find building the kit simple enough. As kits go this is a pretty simple example to construct. The complications arise in the setting up.

COMPROMISING POSITIONS

As is to be expected, the alignment and bias adjustments, if left to the home constructor, have to be a compromise. While it is hard to approve of these procedures, it is harder to suggest any other way of carrying out the adjustments at a price compatible with the kit! RTVC have at least been ingenious in solving the equations. Let us hope people involved in construction are faithful to the execution of the instructions.

When setting up the deck to RTVC's instructions, choose yourself a brand of tape, align and bias for this brand, AND THEN STICK

MANUFACTURER'S SPECIFICATION

Frequency Response:	50-12k Hz
Output Level:	>0.5V
Input Levels:	-65dB 10k -47dB 100k (DIN)
Tape Speed:	4.8 cms ⁻¹ (1 7/8 ips)
Bias Frequency:	57kHz
Price:	£29.25

TO IT. This will ensure maximum performance. If you do have to change the tape, it would be best to re-align and re-bias the machine, although improvements may be marginal.

With reference to this procedure, we would take odds with RTVC over their recommendation to use a pre-recorded cassette for the purpose. These are notorious in their variation, and provide at best questionable high frequency accuracy. It would be better to use a tape recorded by a friend from disc or FM radio (MCPS licensed we hope!).

SHOOTING TROUBLES

A nice touch is the inclusion of a small listing of possible faults and their causes. Most fault conditions will arise from constructional errors, and careful checking of all work is a must before contacting any kit company with a complaint. Better still get someone else to give the wiring the once-over for you.

We encountered no real problems with building our sample, although the metalwork required is a little 'fiddly' and will soak up a fair bit of patience and time to get it right.

SAMPLED DELIGHTS


As we said earlier building up the unit posed us no problems, and it took us about 2 hours to wire up the unit, and several times longer to carry out the metalwork!! We followed RTVC's setting up, using a BASF C60 cassette as an example of a 'typical' tape.

There is one error in that instruction sheet - Fig. 7. - the 'fast fwd' and 'stop' switches have become transposed on the diagram. Not a major mistake, but a little confusing nonetheless. The setting up procedure was indeed a compromise - no doubt better results could be obtained using

a calibrated test tape and lab equipment, however time prevented us from attempting this ourselves.

Using RTVC's methods, the results obtained were certainly fair value for money. A very audible hiss was naturally present, as was a certain amount of 'wow'. Not a machine to record piano concertos! The alignment position proved highly critical and the screw is best secured once the 'best' spot is found.

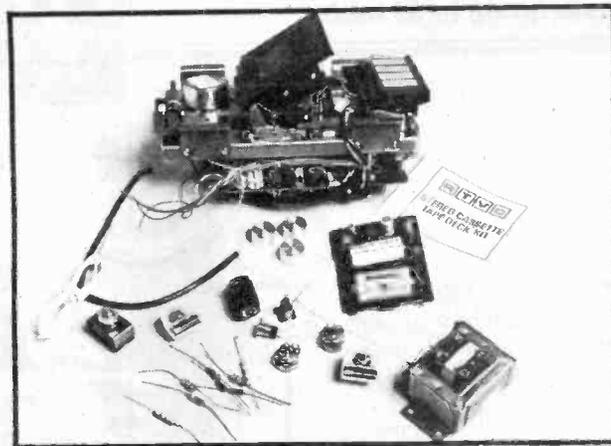Overall not a bad attempt at low cost cassette audio, and would probably make a starting point for someone who can wave a soldering iron in the correct direction. ●



PULSAR; £13.95

THE LONG-RUNNING OFFER ON A DIGITAL ALARM CLOCK HAS BEEN ONE OF OUR MOST SUCCESSFUL EVER! OUR PRICE INCLUDES VAT AND POST & PACKING



Fullsize = 5in across and 3 1/2 in deep.

Pulsar shows the time 0.7in high on bright Planar Gas Discharge displays (there is a brightness control on the back). The dot on the left of the display shows AM/PM, and the flashing (1Hz) colon shows that the alarm and clock are working.

A bleeper alarm sounds until the clock is tipped forwards. Then the "snooze" facility can give you 5 minutes sleep before the alarm sounds again, and then another 5 minutes, etc, until you switch the alarm off. The clock also features a mains-failure indicator.

We have a large number of units in stock for this offer but please allow 28 days for delivery.

PULSAR OFFER
ETI MAGAZINE
36 Ebury Street,
London SW1W 0LW

I enclose cheque/P.O. for £13.95 (payable to ETI) for a Pulsar Alarm Clock. Please write your name and address on the back of your cheque to speed processing of your order.

NAME

ADDRESS

.....

.....

.....

Those not wishing to cut their magazine may order on their own notepaper.

High Power Beacon

Truly portable battery-operated unit generates immensely bright flashes about fifty times a minute for up to 20 hours.

Project 240

A COMPLETELY PORTABLE emergency flash unit has many applications — particularly as a rescue aid when boating or hiking in isolated areas.

For such purposes it is essential that the unit be self-contained, compact and light in weight. It must above all produce a brilliant powerful flash that will attract attention over long distances, yet be capable of operating for at least eight hours from a couple of torch batteries.

The two requirements of high power and battery economy preclude the use of incandescent globes. However a xenon flash tube is capable of producing about fifty 0.6 joule flashes per minute for 20 hours or so if energised — via suitable circuitry — from a pair of alkaline "D" cells.

CONSTRUCTION

This may take any number of suitable forms. One approach is shown in the drawings and photos in this feature. No doubt readers will be able to construct individual housings to suit their own requirements.

Our unit was based on a metal-cased torch powered by two "D" cells. We discarded the torch globe and reflector but retained the switch mechanism. Regardless of the form of housing, construction should be based on the printed circuit board shown. All components should be mounted on the board as shown in the overlay drawing taking care that the diode, SCR, power transistor and pulse



transformer are the correct way round.

The trigger lead of the pulse transformer is connected to a spiral of copper wire wound around the body of the flash tube to ensure reliable triggering. The inverter transformer is mounted to the board with a 4 BA or similar screw. This also secures the special bracket that contacts the positive terminal of the battery. This bracket is made from a piece of 18 gauge aluminium as shown in the side view diagram. The brass strip in the torch housing which normally makes contact with the reflector is soldered to the large pad provided for this purpose. This connection, as well as forming the negative battery connection, also holds the board down into the torch body.

We discarded the torch glass and the threaded flange which retains the glass, trimmed back the torch housing a little with tin snips, and then soldered the lid of a jam jar to the torch housing. The jar lid had previously had a hole cut through it to allow the electronics to protrude through into the jar. The jar should be kept over the unit whenever it is being operated as some parts of the circuit are at 400 volts or so and a nasty shock could be received.

The capacitor used for CI is not rated at 300 V but has been found to be entirely suitable for such intermittent pulse operation. A capacitor rated at the full voltage would not only be much bigger and much more expensive, but would not add anything in the way of reliability.

PARTS LIST – ETI 240

Resistors

R1,2*	—	220	½W	5%
R3,4	—	2M2	"	"
R5	—	10k	"	"

Capacitors

C1	—	10 μF	250 V
			polyester
C2	—	0.1 μF	200 V

Transistor

Q1 — TIP 3055

Diode

D1 1N4008

SCR1 C106D

Transformer

T1 See Table 1
T2 See Table 1

LP1, LP2, Neon Lamps NE2 (75 v)
LP3 Flash Tube (see Table 1)

PC Board ETI 240

Torch, Battery etc.

* For 6v operation change R1 to 470 ohm.

HOW IT WORKS – ETI 240

The flash tube requires about 300 to 350 volts to supply the flash energy, and about 4000 volts to trigger it into conduction. The 300 volts is generated from a three-volt battery supply via a blocking oscillator. The oscillator works as follows.

On switch-on the transistor Q1 is biased on by R1 and R2 and a small voltage is generated across the primary of transformer T1. Due to the action of the transformer a voltage is induced in the feedback winding of the transformer which turns on Q1 hard. The current in the primary therefore increases sharply until the transformer core-material saturates. At this time normal transformer action stops, the feedback voltage disappears and the transistor turns off. The polarity of the voltage on the primary reverses and the energy stored in the core must be dissipated. In effect the energy is dumped into capacitor C1 via the diode D1 causing C1 to charge to the 300 volts or so required. If the capacitor was not present the voltage on the collector of the transistor would be high (60 volts or more) and the secondary voltage would be well over 1000 volts. Therefore it is essential that the oscillator never be run

without the load connected. It is also essential that the polarity of the windings be correct as marked on the circuit diagram (PS for primary start etc).

When the energy in the core has been dumped into C1 the transistor turns on again and the cycle is repeated. The repetition rate depends on the voltage across C1 but is typically within the range 8 to 15 kHz.

When the voltage across C1 reaches 300 to 350 volts the voltage across the scr is about 150 volts and at this point the two neon lamps conduct thus triggering the 'SCR. The SCR now discharges C2 via the primary of the pulse transformer thus generating a pulse of about 4000 volts amplitude on the secondary. The pulse is applied to the trigger electrode of the xenon tube causing it to strike. The flash tube then discharges capacitor C1 in about 10 microseconds giving a very intense and high-speed flash of light. The peak current in the flash tube is about 350 amps.

The SCR turns off automatically due to ringing of the pulse transformer and the low amount of current available through R3.

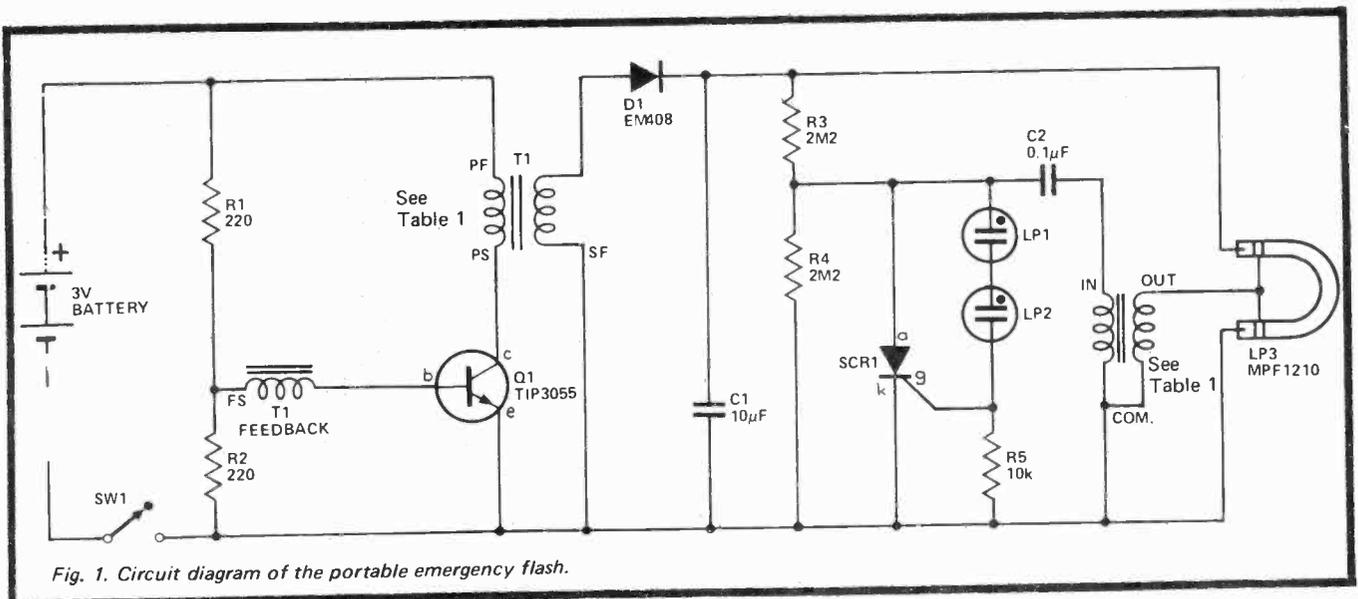
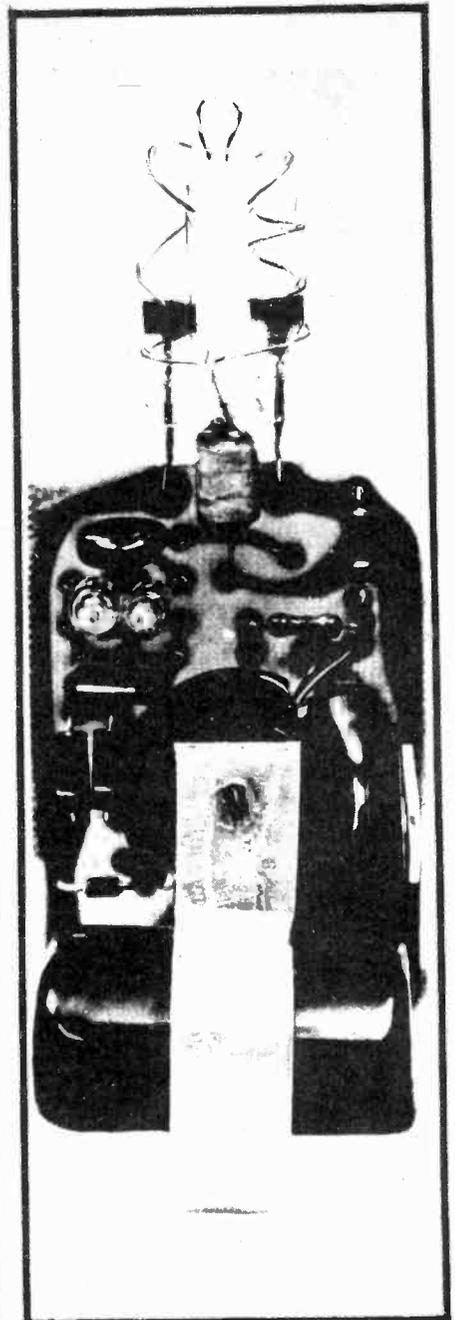


Fig. 1. Circuit diagram of the portable emergency flash.

TABLE 1

Winding details transformer T1.

CORE	FX2240 (2 halves) plus single section bobbin to suit see below
SECONDARY (wound first)	4 turns 0.5 mm wire (or two 0.315 mm in parallel)
PRIMARY	4 turns 0.5 mm wire (or two 0.315 mm in parallel)
FEEDBACK	4 turns 0.315 mm wire

Mark the start of all windings clearly as polarity is important. Add a layer of Sellotape over the secondary for insulation. Note that for six volt operation primary should be wound with eight turns of 0.315 mm.

With Philips 126048 or MPF1210 the TR-4KN trigger transformer should be used, but with the Tandy 272 1145 the secondary of T1 should be reduced to 110 turns and the matching trigger transformer 272 1146 used.

High Power Beacon

Fig. 3. Side view of the flash unit showing how board is secured into the torch body. Note particularly the bracket which connects to the battery positive terminal.

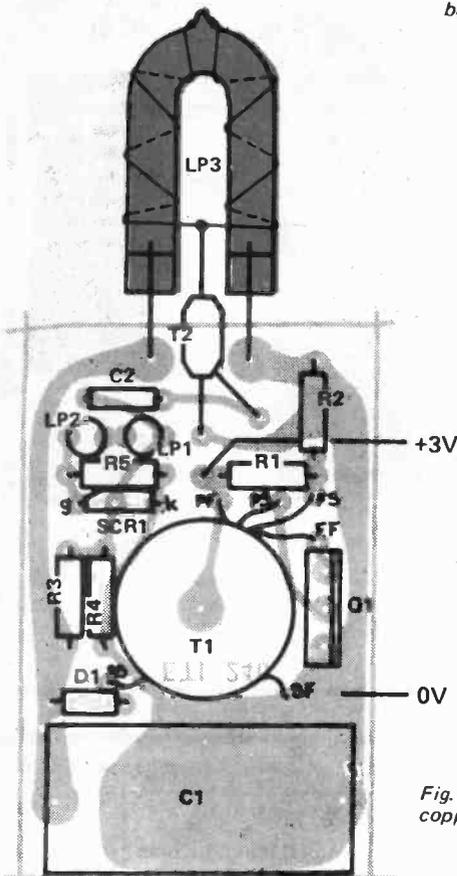
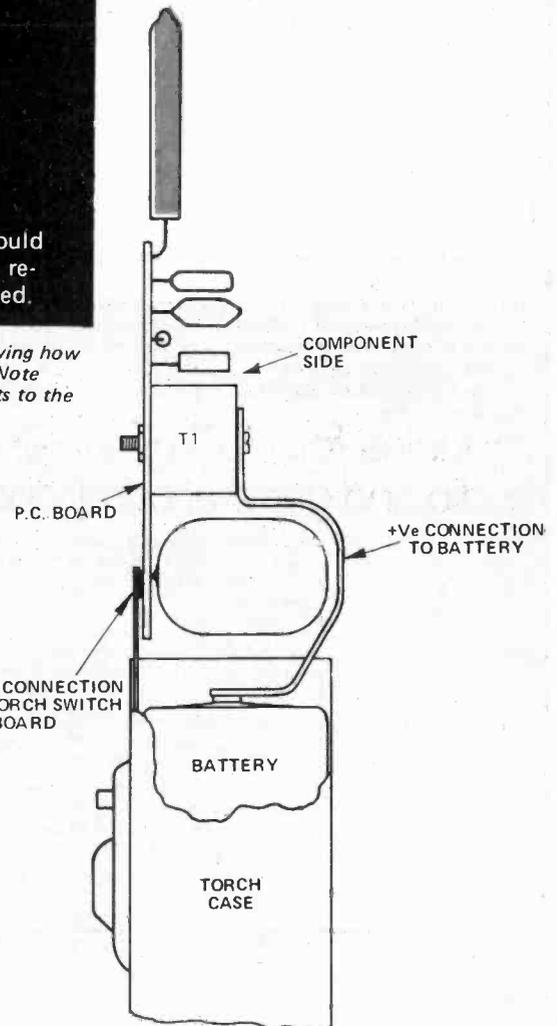


Fig. 2. Component overlay. Note copper wire spiral around flash tube.

SPECIFICATION ETI 240

INPUT	
Voltage	3 volts (nominal)
Current	400 to 450 mA at 3 volts
Power	1.25 watts
OUTPUT POWER	
FLASH RATE	0.6 joules/flash
EXPECTED BATTERY LIFE (2 D size cells)	1.2 seconds per flash typical
EXPECTED BATTERY LIFE (2 D size cells)	
Alkaline	20 hours
Normal	8 hours
Nickel cadmium	10 hours


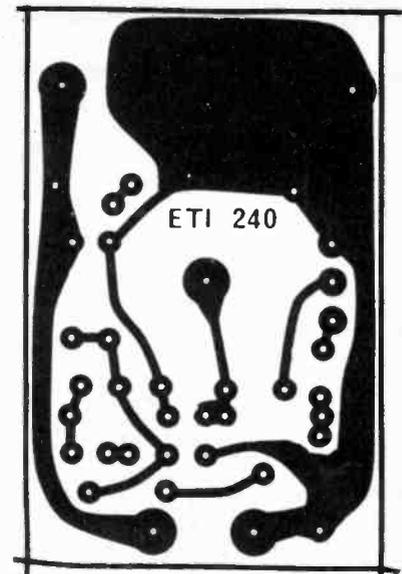


Fig. 4. Printed-circuit layout for the flash. Full size 73 x 47 mm.

ambit international

WIRELESS SPECIALISTS

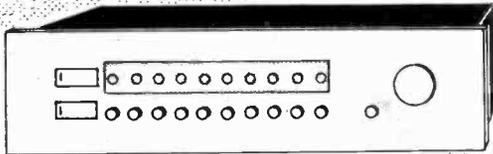

fm tuner number two

The New FM Tuner from Ambit.

1.2uV for 30dB SN, adjustable output voltage, ultrasonic suppression better than 70dB. 6 presets, geared manual drive. Double IC stabilizers. Supplied with prealigned Larshot RF/IF and decoder module. Complete with black woodgrain cabinet, and solid aluminium front panel. Kit £55.50 (£62.43 inc. VAT)
Built and tested £79.75 (£89.71 inc. VAT)
(Carriage £3.00 extra)

modules for rf,if,mpx: (12v) audio and general components

- | | | |
|-------------|-------|---|
| NEW | 7020 | Dual ceramic filters, 2 stage preamp into the improved CA3089E (HA1137W), with mute, AFC to suit ANY varactor tunerhead, meter output and edge terminations.
kit £5.25 built £6.55 |
| NEW | 92310 | The MC1310 mpx decoder, with twin audio preamps, and BLR3107 ultrasonic block filter.
kit £5.35 built £6.65 |
| NEW | 71197 | A new varicap tuner for MW/LW, with ceramic filter, 80dB AGC, low noise and distortion.
kit with ferrite rod £9.65 built £11.35 |
| NEW | 5800 | The state of the art in FM tunerheads. 6 double varicap tuned circuits, 2 MOSFET AGC controllable RF stages, double tuned IF output stage.
kit £11.35 built £14.00 |
| TDA2020 kit | | A stereo power amp, with the TDA2020 15W RMS 0.1% THD IC from SGS.
£7.85. (Special extruded heatsinks 75p each). |

LINEAR ICs	(* at 8%)	DISCRETE DEVICES
CA3089E 1.94	LS8038 3.10*	ZTX107/8/9n 0.14
CA3090AQ 3.75	NE560 2.50	ZTX212/3/4p 0.16
MC1310 2.20	NE561 2.50	ZTX551/451pn 0.18
SN76660 0.75	NE562 2.50	BF256 0.34
TBA120AS 1.00	NE565 2.50	40673/MEM616 0.50
TBA651 1.81	NE566 2.55*	40822/MEM615 0.38
uA720 1.40	7805UC 1.55*	BD535n(60v - 50w) 0.52
LM380 1.00	TDA1412 0.95*	BD536p(60v - 50w) 0.53
LM381 1.81	78M20UC 1.20*	BD609n(80v - 90w) 0.70
TBA810 1.09	uA723 0.80*	BD610p(80v - 90w) 1.20
TCA940 1.80	NE550 0.80*	n = NPN type
TDA2020 2.99	NE567 2.50*	p = PN P type

VARACTORS	FOIL TRIMMERS	POTS
MVAM2 1.05	3 - 12pF 0.18	100k+100k LIN 0.60
MV104/BB104 0.45	4 - 30pF 0.23	100k+100k with... 0.65
BA102 0.30	6 - 45pF 0.26	20 turn 100k... 0.35
BA121 0.30	(7.5 diameter types)	diode law

TOKO COILS, FILTERS, TUNERS FOR AM/FM AND MPX.

Full details of standard types in lists:

10mm IFTs for 455-470kHz	27p	Linear Phase filter for 10.7MHz	2.25
10mm IFTs for 10.7MHz	30p	MFH41/71T mechanicals for 455	1.65
Ceramic filters for 10.7MHz	50p	SFD470 new Murata ceramic block	0.75
Ceramic filters for 6.0MHz	80p	BLR3107 19/38kHz notch (stereo)	1.60
Ceramic 455kHz type CFX104	1.50	Variable chokes 11, 23 & 36mH	.30
CFT455B/C, CFT470C ceramic	60p	EC3302 low cost varicap FM tuner	5.50
CFU050D 470kHz ceramic	65p	EF5600 5 stage varicap FM head	12.50

Send an SAE for a free price list and stock list. There is a new Larshot Signalmaster FM tuner and more details on our range of wireless products. PP 22p per order, VAT is generally at 12½% - and the min. CWO charge is £1. Min. invoice £7.50, Catalogue 40p. (* 8% VAT).

37 HIGH STREET,
BRENTWOOD, ESSEX.
CMI4 4RH tel 216029

DESIGNED BY TEXAS



30,000
ALREADY
SOLD

Texan Amplifier
as featured by
PRACTICAL WIRELESS
SOLE U.K. DISTRIBUTORS - HENRY'S

Build it yourself for only

£32 KIT PRICE INC. VAT + £1.00 p&p
Built and tested £42.00 inc. VAT + £1.00 p&p

Build the Texan stereo amplifier, then you can be doubly proud! For a start, you'll own a superb home entertainment unit. And have had all the pleasure of doing it yourself, with the Henry's kit.

Look at the Texan specification

Incorporating fully integrated stereo preamp and power amp, with 6 IC's, 10 transistors, 6 rectifiers and zener diodes. Plus stabilised, protected circuitry, glass fib pcb. Gardeners low-field low-line mains transformer, all facilities and controls. Slim design, chassis 14½" x 6" x 2" overall, 20 watts per channel RMS, less than 0.1% distortion at 1 kHz.

★ Can be built Stage by stage
Ask for leaflets 5.
★ Everything necessary supplied.
Full after sales service and guarantees.

TEXAN FM TUNER KIT **£23.50**
inc. VAT + 50p p&p

Built and tested £28.50 inc. VAT + 50p p&p

Build the matching Texan stereo tuner! Features advanced varicap tuning. Phase lock loop decoder. Professionally designed circuit. Everything you need is in the kit. From the glass fibre pcb to the cabinet itself. Excellent spec. 2.5 uV aerial sensitivity. 500 mV output (adjustable). Tuning range 87-102 MHz. Mains powered.

THE NATURAL FOLLOW-ON

DIGITAL 24 HOUR CLOCK

WITH BUILT-IN ALARM!



NORMALLY £24.00 WITH CASE

EXCLUSIVE HENRY'S PRICE **£6** LOTS OF 3 £16.50 INC. V.A.T. and P&P

All you have to do is make a casing and you've got a £24.00 Digital Unit!

Also from Henry's **MISTRAL DIGITAL CLOCK KIT £11.50** inc. VAT, 30p p&p

VIDEO SPORT



An up-to-the-minute game. Plugs into your own TV aerial socket. Switch on. And you're away! Choose your game - football, tennis or hole-in-the-wall. Absolutely safe. For you. Your children. And your TV. Mains powered. List Price £42.50

HENRY'S PRICE **£25.00**
inc. VAT + 50p p&p

★ OVER 10,000 ALREADY SOLD
★ IDEAL GIFT

● SILENT RUNNING ● LARGE ILLUMINATED NUMERALS ● A.C. MAINS ● SIZE 6½" x 2½" x 2½"

HENRY'S LATEST ELECTRONIC CATALOGUE

50p - 20p carr/pack.

TRANSISTOR & VALVE DISCOUNT PRICE LIST
over 2000 types
SEND FOR YOUR FREE COPY

Henry's RADIO

All mail to: Henry's Radio
303 Edgware Rd. London W2

LONDON W2: 404/6 Edgware Road. Tel: 01-402 8381

LONDON W1: 231 Tottenham Ct Rd. ^{Upper floor} Tel: 01-636 6681

*NOTTINGHAM: 94/96 Upper Parliament St. Tel: (0602) 40403

*READING, BERKS: 130/131 Friar Street. Tel: (0734) 583230

*CROYDON: 110 North End. Tel: 01-681 3310

*NEW STORES

Please Note: Mail Order Customers HENRY'S WILL CREDIT ANY VAT OVERPAYMENTS

HEADPHONE RADIO

ed project



WHILST IT MIGHT BE argued by some of our readers (and our competitors!) that this project is merely a cheap trick to boost sales by giving us an attractive (well isn't it?) cover, we think that the 251 headphones radio stands on its own merits as a good but simple project. It was designed simply because it seemed like a fun project which readers would enjoy building, and it was also a good trick to boost sales by giving us an attractive cover. (You bought it, didn't you?)

With summer upon us already people have taken up such worthwhile pursuits as sunbathing, walking in the park, or slaving over a hot soldering iron conjuring up projects like this one. It is only natural, in this solid state age, to grasp for one's personal pocket radio as one exits into the summer sunshine, in order to do whatever it is one intends to do, to music. The trouble is, a lot of people believe that transistor radios are unnatural devices, especially when efficiently radiating a watt or so into the air around their earhole.

SPOT THE . . .

This project then, is dedicated to those electronic ecologists who regard noise as pollution and who, in order that their fellow men (and women!) shall not suffer are willing to walk about looking completely loony with this contraption on their heads. On, then to the project itself.

In the interests of keeping the cost down, and the designer sane, it was decided not to include facilities for FM stereo reception in the 251. Consequently, the circuit is (ridiculously?) simple, using our old friend the ZN414, and we were going to use another well-known chip, the MFC4000B for audio output except that it's gone the way of all silicon, and so we used what the man in the shop gave us instead, an MC1306P. This is quite a nice little device which will deliver

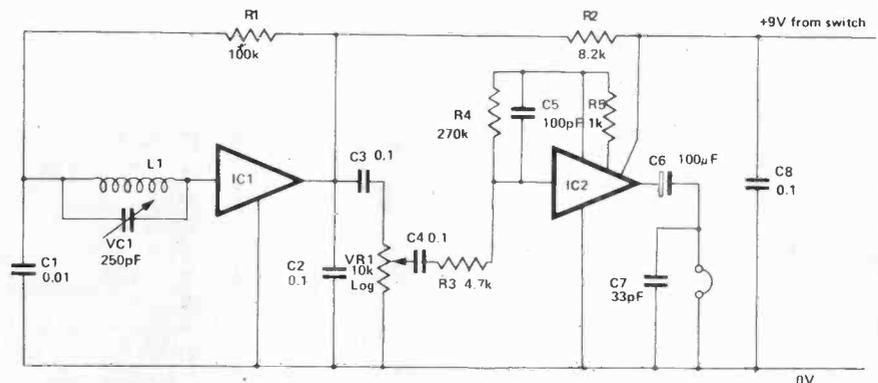


Fig. 1. Circuit diagram.

$\frac{1}{2}$ a watt for around 3mV input. Great, we said, and off we went, with a hey-ho, the ZN414 and the MC1306P, to buy a pair of headphones. We got ours from the local branch of a large photographic/hi-fi chain, called D'x'ns, and very cheap they were too. The assistant couldn't understand why we didn't want to buy the model XYZ1001 $\frac{3}{4}$ s with volume and tone controls plus built-in cocktail cabin-

et and binoculars, but we explained that we were mad electronics enthusiasts with journalistic aspirations, so he stopped the sales talk and humoured us.

Virtually any pair of 'orrible headphones will do, and obviously the size will vary enormously so that we have only given a generalized PCB layout as the PCB may have to be smaller or larger to suit your phones.

CONSTRUCTION

Construction is straightforward, with virtually all components mounting on the board except for the loudspeakers, on-off switch, and the 9V battery which we mounted together in the other earpiece. This meant that we had to replace the cable in the headband, with a three-core type, to carry +9V, speaker connection and earth/common. The speakers were wired in series since we didn't know how the MC1306P would like a 4 ohm load and didn't want to find out the hard way! Of course, if you want to try it...

The ZN414 is a 3-terminal TRF radio which suffers from one major bugbear: instability. If R2 is too low it will take off like a bat out of hell, whistling as it goes. If you do have a problem with instability, try increasing R2, and this may cure it. On the other hand, if you have a particularly docile 414, it could need just that little extra bit of oomph that a 6.8k for R2 might give it.

Apart from that, the only piece of advice is don't wear the things in public or you'll have a lot of explaining to do! Incidentally, these things are great for doing that old trick of getting people to put them on and then...

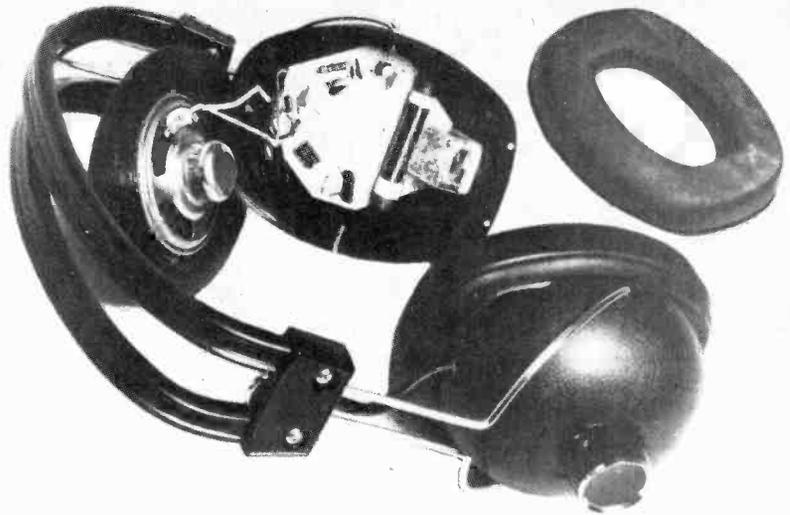


Fig. 2. Printed circuit board (full size),

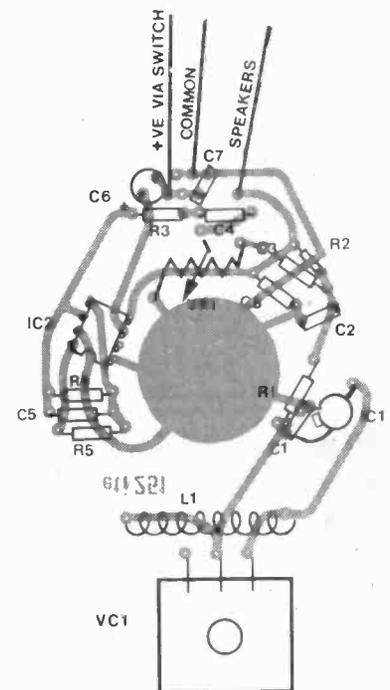
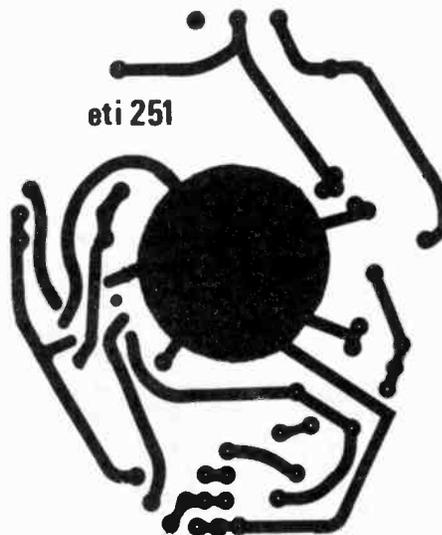


Fig. 3. Component overlay.

PARTS LIST - ETI 251

R1	100k
R2	8.2k
R3	4.7k
R4	270k
R5	1k
VR1	10k log

C1	0.01pF
C2	0.1pF
C3	0.1pF
C4	0.1pF
C5	100pF
C6	100µF
C7	33pF
C8	0.1pF

IC1	ZN414
IC2	MC1306P

L1 80 turns close-wound
32swg enamelled wire on
42 x 9mm ferrite rod
VC1 250pF (Home Radio
type TP4 is suitable)
PCB ETI 251 Knobs, switch,
9V battery (PP3), etc..

*Now there's a better way
to keep your copies*

We reckon ETI is worth keeping; and our surveys indicate that a staggering 97% of readers keep their copies for at least three months. Now we can offer you a binder which holds 12 issues whose quality befits the magazine: excellent. Send £2.00 (which includes VAT and postage) to:
ETI BINDERS, 36 EBURY STREET, LONDON SW1W 0LW.

MAINS TRANSFORMERS PRI. 240v sec. 27/0/27v at 800 m/a. £2.35. P.P. 50p. PRI. 110/240v sec. 50v at 10 amps. £10.00. P.P. £1.50. PRI. 110/240v sec. 50v at 10 a.ps. £10.00. P.P. £1.50. PRI. 110/240v sec. 20/21/22v at 8 amp. £6.00. P.P. £1.50. PRI. 110/240v sec. 23/24/25v at 10 amp. £7.00. P.P. £1.50. PRI. 110/240v sec. 24/40v at 1½ amp. £1.90. P.P. 60p. PRI. 240v sec. 20/40/60v at 2 amp. £3.00. P.P. 70p. PRI. 240v sec. 20v at 2½ amp. £2.00. P.P. 65p. PRI. 240v sec. 18v at 1.5 amp and 12v at 1 amp. £2.25. P.P. 50p. PRI. 240v sec. 18v at 1 amp. £1.10. P.P. 35p.	CIRCUIT BOARD P.C.B. 1/16 1 oz. COPPER	S-DECS AND T-DECS S-DEC £1.90 T-DEC £3.60 U-DEC A £4.20 U-DEC B £6.90 } P.P. 25p
12 volt MINI UNISELECTOR 11 way, 4 bank. (3 non-bridging 1 homing). £2.50. P.P. 35p	FORMICA Dim. 8-4 x 7-7 in 3 pcs. 80p. Dim. 9-4 x 8-1 in 3 pcs. 90p. Dim. 10-1 x 7-9 in 3 pcs. £1.00. Dim. 13-1 x 9-4 in 3 pcs. £1.20. Dim. 17-0 x 9-0 in 2 pcs. £1.20. } P.P. 35p	FIBRE GLASS BARGAIN PACK 200 sq in single & double sided pieces. £1.25. P.P. 25p.
24 volt MINI UNISELECTOR 11 way, 6 bank (5 non-bridging, 1 bridging). £2.00. P.P. 35p.	BARGAIN PACK 10 pcs. 10-1 x 7-9 in Plus free ½lb etching Xtals. £3.10. P.P. 45p.	HIGH CAPACITY ELECTROLYTICS 250mfd/63 volt. 20p. P.P. 8p 100mfd/100 volt. 70p. P.P. 25p 2200mfd/100 volt. 90p. P.P. 25p 4700mfd/25 volt. 65p. P.P. 20p 6800mfd/16 volt. 50p. P.P. 15p 10,000mfd/25 volt. 75p. P.P. 20p 47,000mfd/40 volt. £2.00. P.P. 50p 100,000mfd/10 volt. £1.50. P.P. 50p 160,000mfd/10 volt. £2.00. P.P. 50p
SIEMENS MINIATURE RELAYS 6v 4c/o with base. 65p ea. 24v 2c/o with base. 50p ea.	FIBRE GLASS P.C.B. Dim. 6 x 6 in. 50p each. Dim. 12 x 6 in. 75p each. } P.P. 15p Dim. 12 x 12 in. £1.30 each. Equals less than 1p sq. in.	3 GANG TUNING CAPACITOR 8 5pf to 320pf. 80p. P.P. 20p
MAINS RELAY 240v 3 c/o 10 amp contacts. £1 with base.	DOUBLE SIDED P.C.B. FIBRE GLASS 6 x 6 in. 40p. 12 x 6 in. 65p. } P.P. 15p 12 x 12 in. £1.20.	MINIATURE METERS 500 micro-amp (level-stereo beacon, etc.), scaled half black/half red. Size 1 x 1 in. 65p. P.P. 15p
MINIATURE RELAYS (1½ x 1½ x ½) 24v, 4 c/o. 40p.	ETCH RESIST PENS 55p. P.P. 5p.	A.M. F.M. TUNING METER 125-0-125µA, edgewise 1½ x ½ £1.10.
OVERLOAD CUT-OUTS Panel mounting 800 M/A 1.8 amp. 10 amp. 55p ea.	FERRIC CHLORIDE ETCHING XTALS 1 lb makes 1 litre pack. 70p. P.P. 35p 5 lb makes 5 litre pack. £2.65. P.P. 65p.	SIGNAL STRENGTH METER 260µA (illum) Edgewise 1½ x ½. £1.10.
SCR-THYRISTOR 1 amp 400 P.I.V. 35p. 5 amp 400p P.I.V. 35p.	PRINTED CIRCUIT KIT The no frills all value kit. Containing 4 pcs 8 x 7 Formica laminate, 1 pce 6 x 6 Fibre glass laminate, 1 lb Etching Crystals, 50 c.c. Resist ink, with instructions £2.40. P.P. 65p.	OUTPUT METER CLEAR PLASTIC 500µA 1½ x 1½ square £1.30.
EDGE CONNECTOR 54 way -1 vero size etc. Can easily be cut to any length. 55p. P.P. 10p Side Guides to suit the above 15p ea	BLUE P.C.B. INK Etch resist, use with any pen. Much cheaper than ready loaded pens 50 c.c. 55p. P.P. 10p	10 NELMES WAY, HORNCHURCH ESSEX RM11 2QZ HORNCHURCH 45167 MAIL ORDER ONLY. PERSONAL CALLERS BY APPOINTMENT

New to the UK from PRONTO

Battery operated LCD read out
CALENDAR CLOCK KIT - crystal accuracy -
 Bold Digits - runs on two Penlight Cells.

Now is the time for the hobbyist to move into Advanced Technology with Pronto!
PRONTO MODEL 301 - The first completely portable liquid crystal display, digital, CALENDAR CLOCK KIT offered in the United Kingdom.

- * Battery operation - two small alkaline cells give a minimum life of 12 months.
- * Superb accuracy through crystal control - of 3 minutes a year
- * Wide angle display with ½" digits
- * Push Buttons give choice of 3 display modes - hours minutes on 12 hour display with flashing colon, or seconds, or date.
- * PRONTO 301 comes complete with easy to follow

instructions AT £29.50 including V.A.T. You save Pounds off the recommended retail price of a comparable made up clock.

TERMS: Cash with order - make cheque and/or postal order payable to PRONTO ELECTRONIC SYSTEMS LIMITED. (P & P - U.K. £0.45 Overseas £1.50)



PRONTO Fluorescent Display Alarm Clock KIT

- Wake up to the electronic age with the new PRONTO 304 Alarm Clock
- * Large Bright Green Display
 - * Alarm with 10 minute 'snooze' feature
 - * AM/PM indication and simple setting
 - * Automatic brightness control on digits governed by room lighting

- * Ingenious gravity alarm - time setting mode switch
- * Full assembly instructions

AT £15.50 including V.A.T.
 With all PRONTO products - enquiries from the Trade, as well as the Hobbyist, are welcome, and you can also buy individual components!

PRONTO CONSTRUCTOR'S CLUB
 When you buy your first Pronto kit you're automatically a Member of the PRONTO CONSTRUCTOR'S CLUB. It will not only keep you in the picture on new ideas and kits... but gives you **FREE a £2 Voucher** against the purchase of your next kit!
 Isn't it time you joined the Club?



Please send me -

- PRONTO 301 KIT/S AT £29.50 EACH (Plus P & P)
 PRONTO 304 KIT/S AT £15.50 EACH (Plus P & P)

My cheque/P.O. for _____ is enclosed

NAME _____

ADDRESS _____

Pronto Electronic Systems Ltd.
 645/647 High Rd., Seven Kings,
 Essex IG3 8RA. 01-599 3041



electronics today

international

SEPTEMBER ISSUE ON SALE AUGUST 6th 30p


100W DISCO UNIT

100W — yes, one hundred watts per channel disco unit with all the facilities you'd expect from an ETI design — voice-operated fader and excellent monitor facilities. Constructional details in the September issue of ETI.

CMOS-TO-MAINS


George Hanslip delves into the interface between the high power world of mains and the low power world of CMOS. The use of CMOS for power control via TRIACs is thoroughly discussed, and practical circuits given.

TWO METRE POWER AMP

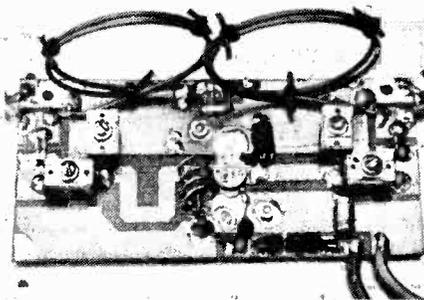

Based on the Motorola 2N6084 VHF power transistor, this project for the up-to-date radio amateur gives over 40 watts output at 145MHz. Solid state switching gives simple construction, low cost and a thumping mobile signal. See it at the RSGB exhibition, Alexandra Palace 30th-31st July and 1st August.

ETI 560 VDU

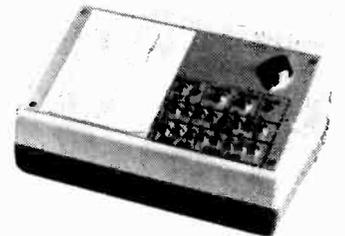

Full constructional details will be given next month for this low-cost video display unit. Primarily intended for microcomputer input/output, it can also be used for paging systems or to display scores for electronic games. Use your imagination; the ETI 560 makes it possible!

PCB KIT OFFER

NORMAL PRICE: £9.00

ETI OFFER PRICE:
£5.95



The kit, put together by Decon, comprises a Seno GS System PCB kit, a Dalo pen, 10 strips of dry transfer PCB markers and two Seno Polifix polishing blocks. Today's advertised price is £9.00 but using the coupon in next month's issue will enable you to get this for £5.95.

electronics — its easy Volume 2 NOW ON SALE


Our series Electronics — It's Easy has proved very popular — so much so that we have reprinted it into two volumes, the first of which was published some months ago.

Volume 2 takes the reader right up to Part 28 and the two parts form a thorough course which introduces the reader to electronics.

Cost is £1.20 plus 15p postage. If Volume 1 is ordered with Volume 2 send only £2.40 (post free). Send to

Electronics — It's Easy
(Volume 2)

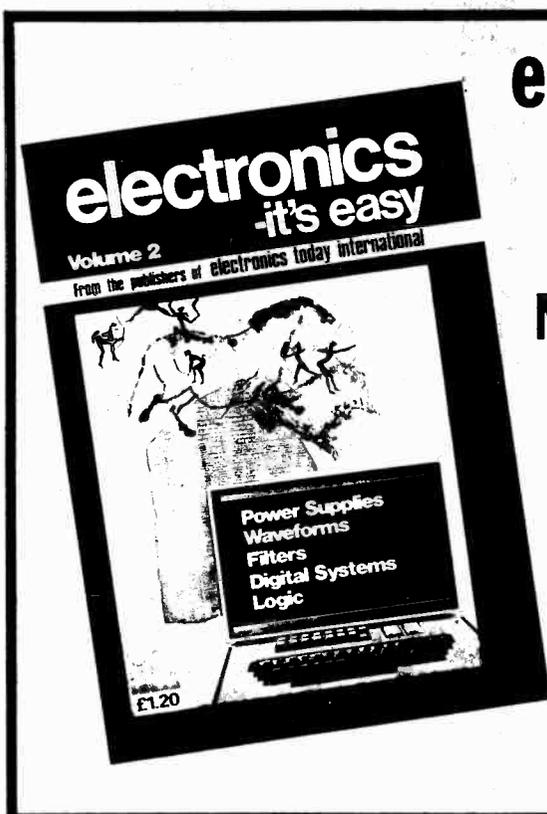ETI Magazine,
36 Ebury Street,
London SW1W 0LW



YOUR ETI BARGAIN VOUCHERS

Now it's a funny thing, but many people believe that nothing happens in the summer in the electronics field. Well ETI sales in the past haven't fallen in the summer though many of our advertisers say its a quiet period.

Well, we thought we would pep things up a bit and arrange a good lot of offers, covering a large range of goodies. Use the coupons below before August 31st and you qualify, as an ETI reader, to the savings given. We've specially arranged the coupons so that you don't cut into anything vital.

BI-PAK

PO BOX 6 WARE HERTS

SPECIAL REDUCTIONS ON AUDIO MODULES

OFFER PRICE including VAT & P&P	NORMAL PRICE including VAT & P&P	OFFER PRICE including VAT & P&P	NORMAL PRICE including VAT & P&P
AL250 £15.89	£17.43	PS12 £ 1.55	£ 1.41
AL60 £ 4.19	£ 4.64	S450 £22.64	£20.39
AL20 £ 2.87	£ 3.18	Stereo 30 £17.92	£16.04
AL30 £ 3.18	£ 3.52	MPA30 £ 3.18	£ 2.87
PA100 £13.87	£15.40	MK60 Kit £31.60	£28.49
PA12 £ 6.78	£ 7.51	Teak 60 £10.75	£ 9.91
SPM80 £ 3.24	£ 3.58		

This offer expires August 31st, 1976

15% off "old clocks"

This coupon entitles you to a 15% discount off the recommended price of the ancient clock kit range introduced by Bywood on page 17. Coupon must accompany order.

This offer expires August 31st, 1976

BYWOOD

BYWOOD ELECTRONICS
68 Ebbens Road
Hemel Hempstead
Herts HP3 9QR
Tel. 0442 62757

ILP ELECTRONICS

1/3 off HY30

15 Watts into 8Ω

SPECIFICATIONS
OUTPUT POWER 15W R.M.S. into 8Ω; DISTORTION 0.1% at 15W
INPUT SENSITIVITY 500mV FREQUENCY RESPONSE 10Hz-16kHz -3dB
SUPPLY VOLTAGE ±18V

£3.59 INC. V.A.T.

Postage and packing free.

SEE ADVERTISEMENT ON PAGE 49

This offer expires August 31st, 1976

B H COMPONENT FACTORS LTD.

LEIGHTON ELECTRONICS CENTRE, 59 NORTH ST.
LEIGHTON BUZZARD, BEDS. LU7 7EG. Tel. (05253) 2316.

FREE CATALOGUE

FOUR PLASTIC PACK

741's £1

INCLUDE VOUCHER WITH ORDER

This offer expires August 31st, 1976

Sparkrite

£2 off Mk2 Ignition kit

- £9.80

OR

£4.15 off Mk2 kit

plus c/o switch

- £11.95

PRICES INCLUSIVE

SEE ADVERT PAGE 41

This offer expires August 31st, 1976

ambit INTERNATIONAL



INTERNATIONAL MkII
STEREO TUNER

AS ADVERTISED PAGE 33

SPECIAL PRICE **£59.95**

PLUS £3 p&p

This offer expires August 31st, 1976

CROFTON ELECTRONICS

CCTV camera kit

£90
Inc. VAT, P&P

COMPLETE CCTV CAMERA KIT including lens and Vidicon Tube (Available as "Ready Built" camera at £100 inclusive).
Never have we been able to offer such a packaged deal at this price.
Delivery: We shall make every endeavour to despatch within four weeks from receipt of order with remittance, but should demand exceed expectations delivery period could be extended. All orders will be acknowledged stating delivery.
Full technical back up service available to all purchasers.
U.H.F. Modulator available as optional extra in order to use domestic T.V. as monitor. (Price £7.87 inclusive of P&P and V.A.T.).
CROFTON ELECTRONICS LIMITED, 35 Grosvenor Road, Twickenham, Middlesex. Telephone 01-891 1923.

SEE ADVERTISEMENT ON PAGE 71

This offer expires August 31st, 1976

Marshall's

ETI
SPECIAL

AD161	.50	LM380-1A	.90	OA91	.03
BA102	.15	LM381AN	1.60	OC42	.25
BC107	.095	LM709	.29	TIP29A	.39
BC108	.095	MPT107	.35	TIP30A	.49
BC109	.11	LM723	.45	TIP31A	.53
BC182	.085	LM748	.35	TIP32A	.60
BC183	.085	LM3900	.53	TIP41A	.68
BC184	.09	MC1310P	1.95	TIP42A	.60
BC212	.09	MJ481	.00	TIP2955	.74
BC213	.09	MJ491	1.35	TIP3055	.45
BC214	.10	MJE340	.43	SN76013N	1.30
BC237	.11	MJE370	.55	SN76023N	1.30
BC238	.10	MJE371	.65	Trac_3A	
BC239	.11	MJE520	.50	400V	.75
BD529	.35	MJE521	.60	Bidge 1A	
BD530	.35	MJE2955	1.00	400V	.25
BFY50	.20	MJE3055	.66	C106D	.55
BFY51	.20	MPT102	.25	2N3055	.45
BT106	.80	MPSA05	.16	Voltage regs	
BY126	.11	MPSA55	.16	TO220	
BY127	.14	NE555	.36	5 volt	1.30
LM741-B	.28	OA47	.08	12 volt	1.30
LM380-B	.75	OA90	.03		

FREE NEW CATALOGUE

with orders over £5

Available now.
158 pages of
data, equivalents,
circuits, Japanese
transistors, prices.

This offer expires August 31st, 1976

 FROM BI-PRE-PAK

10% OFF STIRLING SOUND RANGE

FOR DETAILS OF PRODUCTS
SEE AD ON PAGE 75

This offer expires August 31st, 1976

HENRY'S
RADIO

£1 off for every £5 spent
on the following

1/8th inch calculator displays

Fairchild FND-10, single digit,
£1.00.

HP 7414 4 digit, 12 pin d.i.l. pin
out, 99p.

Bowmar 8 1/2 digit, with pc connec-
tor, and red bezel, £1.85.

Texas 3 digit, 12 pin d.i.l. pin out,
85p.

Texas 4+5 digit, 2x14 pin d.i.l.,
£1.85 pair.

30 pin termination board (all types
except FND-10), 20p.

Texas calculator keyboards. 19 gold
plated 'snap' type key contacts on
gold plated pcb, 75p.

Prices include VAT

This offer expires August 31st, 1976

METAC WATCH OFFER

THIS EDITION ONLY

18% DISCOUNT ALL MODELS

LED Model TLE5	£19.95
LCD Model TLC4 gold	£34.88
rhodium	£32.71

NO MORE TO PAY

FILL IN COUPON ON PAGE 69 AND INCLUDE THIS
VOUCHER WITH REMITTANCE.

This offer expires August 31st, 1976

CAMBRIDGE

LEARNING ENTERPRISES

15% OFF ALL ORDERS ON PRESENTATION OF THIS VOUCHER

SEE ADVERTISEMENT PAGE 68

This offer expires August 31st, 1976

FREE MINI-LED

Send us a 9in. x 4in. s.a.e., asking for a FREE
catalogue, and we will also send you a 0.1in.
red Mini-LED FREE.

SPECIAL OFFERS

Add VAT at 8% ● P&P free

£2 off the price of any clock kit

AY-5-1224; £2.99. 5LT01; £4.50

µA741 from RCA in 8-pin DIL 15p ea.

SINTEL

53a Aston Street, Oxford
Tel. 0865 49791

This offer expires August 31st, 1976

res

MAPLIN ELECTRONIC
SUPPLIES

P.O. Box 3 Rayleigh Essex SS6 8LR

DIGITAL CLOCK OFFER COMPLETE WITH CASE

SIMPLE CLOCK KIT **£10.80**

ALARM CLOCK KIT **£12.29**

RADIO/ALARM KIT **£12.78**


ALL PRICES INCLUSIVE

This offer expires August 31st, 1976

SPECIALS

FROM ETI

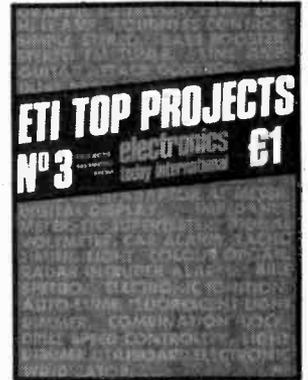To: ETI Specials, ETI Magazine, 36 Ebury Street, London SW1W 0LW.
POSTAGE AND PACKING is 15p for the first, 10p for subsequent (overseas 20p and 15p).



Projects Book Two – contains 26 popular projects from the pages of ETI, first published July 1975 75p + 15p p&p.

Electronics – It's Easy the first thirteen parts of our popular introductory series £1.20 + 15p p&p.

4600 Synthesiser – complete reprint of our superb, synthesiser design produced by Maplin £1.50 + 15p p&p.

Project Book Three – contains 27 popular projects from the pages of ETI, first published March 1976 £1.00 + 15p p&p.

WANT TO WORK FOR ETI?

We have two editorial staff vacancies at ETI. No, no one has left us: these are both new positions and we reckon that ETI readers are likely to fill these. These jobs are not being advertised elsewhere, at least at this stage. Both positions are full-time and permanent.

We are one of the fastest growing magazines in Britain in any field and to maintain our growth rate and to improve our magazine further we are looking for people to fill the positions described below. Oh, by the way, we genuinely have no objections to female applicants (some ETI staff members actually like girls).

1. Technician

We want someone who likes — and is very good at — building projects. The person would be working largely in our workshop, building and checking prototypes of projects.

A high standard of layout and craftsmanship is necessary and the job may be of interest to someone currently working as a prototype wireman in industry. Some mechanical skill in metalwork and even woodwork would be very useful. Ability to design p.c.b. layout is also highly desirable.

Some electronics knowledge is necessary but we are not looking to this person so much to initiate projects but to bring to fruition the ideas and projects of the editorial team. The successful applicant will be working without supervision for most of the time. Salary is negotiable.

2. Specials Editor

This position carries a variety of responsibilities but the prime one will be production of projects books and other specials. The other responsibilities? Well we don't want to say too much as our competitors read ETI avidly and it's a bit early to make some plans public.

The job will involve working methodically alone for long periods. Essential qualifications are (a) interest in electronics as a hobby, (b) high level of intelligence and common sense, (c) ability to work to a laid-down plan and to a schedule. Some knowledge of book or magazine production would be an advantage but is not an essential qualification for the right applicant. Salary is negotiable.

Working for ETI: The successful applicants will be working with a small but very enthusiastic team. The total staff of ETI, when these positions are filled, will be 11. ETI is published by Modmags Ltd which is independent of all other British groups but has strong international ties.

Applications must be made in writing with all relevant details and must reach us by Monday, 19th July. They should be sent to:

Halvor Moorshead
Editor
Electronics Today International
36 Ebury Street
London SW1W 0LW

**BULK PURCHASE — EXCLUSIVE TO HENRY'S
ALLOWS US TO SELL AT SUCH FANTASTIC PRICES!**

QUALITY ITEMS
Compare performance and
specification with units
costing 3 times as much!



**DIGITAL
24 HOUR
CLOCK**

WITH
BUILT-IN
ALARM

- SILENT RUNNING
- LARGE ILLUMINATED NUMERALS
- AC MAINS ● SIZE 6 3/8 x 2 3/8 x 2 3/4

NORMALLY
£24 WITH CASE



MECHANISM ONLY



Assemble
it in an evening!
MECHANISM AND CASE
Inc. assembly
instructions



Modern styling
COMPLETE UNIT

£6.00

£7.99

£8.99

THREE FOR £16.50

THREE FOR £22

THREE FOR £25


POST & VAT INCLUSIVE

Send cheque, P.O./M.O. for the correct
amount which includes VAT and
P & P or pay by Access/Barclaycard.
Send name, card number (if
applicable) and address to:

HENRY'S RADIO
303 EDGWARE ROAD,
LONDON W2
TRADE & EXPORT ENQUIRIES
contact MIKE BAKER 01-723 1008

**HENRY'S
Radio**
LONDON 404/6 Edgware Road, London W2
231 Tottenham Court Road, London W1
NOTTINGHAM 94-96 Upper Parliament Street
READING 130-131 Friar Street, Reading Berks.
HARROW 190, 4 Station Road, Harrow, Middx.
CROYDON 110 North End, Croydon, Surrey

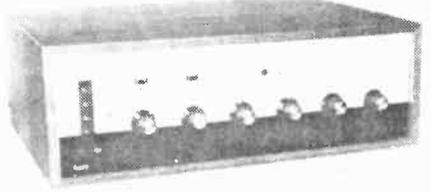HART ELECTRONICS
Audio Kit Specialists since 1961



STEREO BAILEY 30 WATT TUNER AMP.

This complete tuner amp unit is of the very highest quality and is the amalgam of our Compact FM Tuner, Bailey 30watt power amps and the Bailey Burrows Quilter pre amp. The wooden sleeve is available in either teak or sapele finish to blend with existing equipment or furnishings.

The combination of our excellently designed printed circuits and the high quality components used makes this unit unequalled on the kit market and approached in quality of performance and durability by few made up tuner amps. Full details are in our free lists.

STUART TAPE CIRCUITS. Our printed circuits and components offer the easy way to convert any suitable quality deck into a very high quality Stereo Tape unit. Input and output levels suit Bailey pre amp. Total cost varies but around £35 is all you need. We can offer tape heads as well if you want new ones. All in-ove kits have fibreglass PCB's. Prices exclude VAT but P&P is included.

FURTHER INFORMATION ON ALL KITS FREE if you send us a 9 in. x 4 in. S.A.E.

REPRINTS Post free, no VAT.

Bailey 30W 18p.

STUART TAPE RECORDER. All 3 articles under one cover 30p.

BAILEY/BURROWS/QUILTER Preamp circuits, layouts and assembly notes 15p.

All prices exclude VAT @ 12% per cent except for reprints which are exempt.

Penylan Mill, Oswestry, Shropshire

Personal callers are always welcome, but please note we are closed all day Saturday.

Sparkrite mk2

Capacitive discharge
electronic ignition kits



- * Smoother running
- * Instant all-weather starting
- * Continual peak performance
- * Longer coil/battery/plug life
- * Improved acceleration/top speeds
- * Up to 20% better fuel consumption

Sparkrite Mk. 2 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 15/30 mins.

Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). All kits fit vehicles with coil/distributor ignition up to 8 cylinders.

THE KIT COMPRISES EVERYTHING NEEDED

Ready drilled pressed steel case coated in matt black epoxy resin, ready drilled base and heat sink, top quality 5 year guaranteed transformer and components, cables, coil connectors, printed circuit board, nuts, bolts, silicon grease, full instructions to make the kit negative or positive earth, and 10 page installation instructions.

OPTIONAL EXTRAS

Electronic/conventional ignition switch.
Gives instant changeover from "Sparkrite" ignition to conventional ignition for performance comparisons, static timing etc., and will also switch the ignition off completely as a security device, includes switch connectors, mounting bracket and instructions. Cables excluded. Also available RPM limiting control for dashboard mounting (fitted in case on ready built unit).

CALLERS WELCOME. For Crypton tuning and fitting service — phone (0922) 33008.

PRICES INCLUDE VAT, POST AND PACKING.

Improve performance & economy NOW

POST TODAY!

Quick installation
No engine modification
required

Electronics Design Associates, Dept. ET18
82 Bath Street, Walsall, WS1 3DE. Phone: (0922) 33652

Name

Address

Mk. 2 DIY Ass. Kit @ £11.80	QUANTITY REQD.	I enclose cheque/PO's for £
Mk. 2 Ready Built Negative Earth @ £14.97		
Mk. 2 Ready Built Positive Earth @ £14.97		
Ignition Changeover switches @ £4.30		
R.P.M. Limit systems in above units @ £2.42		

Cheque No. _____

Send SAE if brochure only required.

Get a great deal from Marshall's

A Marshall (London) Ltd Dept: ETI
40/42 Cricklewood Broadway London NW2 3ET
Tel: 01-452 0161/2 Telex: 21492
& 85 West Regent St Glasgow G2 2QD
Tel: 041-332 4133
& 1 Straits Parade Fishponds Bristol BS16 2LX
Tel: 0272-654201/2
& 27 Rue Danton Issy Les Moulineaux Paris 92

Call in and see us 9-5.30 Mon-Fri 9-5.00 Sat Trade and export enquiries welcome. Catalogue price 35p (30p to callers)

Top 500 Semiconductors from the largest range in the UK — All devices branded and fully specified

2N456	0.80	2N3390	0.45	2N5295	0.48	AF186	0.46	BC259	0.17	BF194	0.12	LM7812	1.60	SN76023N	1.60
2N456A	0.85	2N3391	0.28	2N5296	0.48	AF200	0.65	BC261	0.25	BF195	0.12	LM7815	1.60	SN76033N	2.92
2N457A	1.20	2N3391A	0.29	2N5298	0.50	AF239	0.65	BC262	0.22	BF196	0.13	LM7824	1.60	ST2	0.20
2N490	4.00	2N3392	0.15	2N5457	0.29	AF240	0.90	BC263	0.25	BF197	0.15	MC1303	1.50	TAA300	1.64
2N491	4.38	2N3393	0.15	2N5458	0.26	AF279	0.70	BC300	0.38	BF198	0.18	MC1310	2.50	TAA263	1.20
2N492	5.00	2N3394	0.15	2N5459	0.29	AF280	0.79	BC301	0.34	BF199	0.18	MC1330P	0.90	TAA350	1.96
2N493	5.20	2N3402	0.18	2N5492	0.58	AL102	1.00	BC303	0.54	BF200	0.40	MC1351P	0.80	TAA550	0.32
2N696	0.22	2N3403	0.19	2N5494	0.58	AL103	0.81	BC307	0.17	BF244	0.21	MC1352P	0.80	TAA611C	2.18
2N697	0.16	2N3414	0.20	2N5496	0.61	BC107	0.14	BC308A	0.15	BF245	0.45	MC1466	3.50	TAA621	2.03
2N698	0.82	2N3415	0.24	2N5777	0.45	BC108	0.14	BC309C	0.20	BF246	0.58	MC1469	2.75	TAA661B	1.32
2N699	0.59	2N3416	0.21	2N6027	0.45	BC109	0.15	BC317	0.12	BF254	0.19	ME0402	0.20	TBA811B	2.25
2N706	0.14	2N3417	0.29	3N128	0.73	BC113	0.15	BC318	0.12	BF255	0.19	ME0412	0.18	TBA810	0.98
2N706A	0.16	2N3440	0.59	3N139	1.42	BC115	0.17	BC337	0.20	BF257	0.20	ME0412	0.11	TBA820	0.80
2N708	0.17	2N3441	0.97	3N140	1.00	BC116	0.17	BC338	0.20	BF258	0.47	ME0412	0.11	TBA820	0.80
2N709	0.42	2N3442	1.40	3N141	0.81	BC116A	0.18	BC339	0.20	BF259	0.55	ME4104	0.11	TBA920	1.79
2N711	0.50	2N3638	0.15	3N200	2.49	BC117	0.21	BCY31	1.03	BF299	0.24	MJ481	1.20	TIP29A	0.49
2N718	0.23	2N3638A	0.15	40361	0.40	BC118	0.14	BCY32	1.18	BF299	0.24	MJ481	1.20	TIP30A	0.58
2N718A	0.28	2N3639	0.27	40362	0.45	BC119	0.29	BCY33	0.96	BFS21A	2.30	MJ480	1.05	TIP31A	0.62
2N720	0.57	2N3641	0.17	40363	0.88	BC121	0.35	BCY34	1.00	BFS2B	1.36	MJ481	1.05	TIP32A	0.74
2N914	0.22	2N3702	0.12	40389	0.46	BC125	0.16	BCY38	1.00	BFS2B	1.36	MJ481	1.05	TIP33A	1.01
2N916	0.28	2N3703	0.12	40394	0.56	BC126	0.23	BCY39	1.50	BFS2B	1.36	MJ481	1.05	TIP34A	1.51
2N918	0.32	2N3704	0.15	40395	0.85	BC132	0.30	BCY40	0.97	BFS2B	1.36	MJ481	1.05	TIP35A	2.90
2N929	0.25	2N3705	0.15	40406	0.44	BC135	0.13	BCY42	0.28	BFX29	0.35	MJE370	0.65	TIP36A	3.70
2N930	0.26	2N3706	0.15	40408	0.35	BC136	0.17	BCY58	0.32	BFX85	0.35	MJE520	0.60	TIP36A	3.70
2N1302	0.19	2N3707	0.18	40408	0.35	BC136	0.17	BCY59	0.32	BFX85	0.35	MJE520	0.60	TIP36A	3.70
2N1303	0.19	2N3708	0.14	40409	0.52	BC137	0.17	BCY70	0.17	BFX87	0.28	MJE5055	0.75	TIP42A	0.90
2N1304	0.26	2N3709	0.15	40410	0.52	BC140	0.68	BCY71	0.22	BFX89	0.90	MP8111	0.32	TIP29c	0.80
2N1305	0.24	2N3710	0.15	40411	2.00	BC141	0.68	BCY72	0.18	BFY50	0.30	MP8112	0.40	TIP30c	0.85
2N1306	0.31	2N3711	0.15	40594	0.74	BC142	0.23	BD115	0.75	BFY51	0.28	MP8113	0.47	TIP31c	1.00
2N1307	0.30	2N3712	1.20	40595	0.84	BC143	0.25	BD116	1.00	BFY52	0.30	MPF102	0.39	TIP32c	1.25
2N1308	0.47	2N3713	1.20	40601	0.67	BC147	0.10	BD121	1.00	BFY53	0.26	MPSA05	0.25	TIP33c	1.45
2N1309	0.47	2N3714	1.38	40602	0.61	BC148	0.09	BD123	0.82	BFY53	0.26	MPSA06	0.31	TIP34c	2.60
2N1671	1.54	2N3715	1.50	40603	0.58	BC149	0.11	BD124	1.20	BFY90	1.37	MPSA12	0.35	TIP41C	1.40
2N1671A	1.67	2N3716	1.80	40604	0.56	BC153	0.18	BD131	0.40	BRV39	0.48	MPSA55	0.25	TIP42c	1.60
2N1671B	1.85	2N3717	2.20	40636	1.10	BC154	0.18	BD132	0.50	BSX20	0.28	MPSA56	0.31	TIP2955	0.98
2N1711	0.27	2N3772	1.80	40669	1.00	BC157	0.16	BD135	0.21	BSX21	0.30	MPSU05	0.63	TIP3055	0.50
2N1907	0.60	2N3773	2.65	40673	0.73	BC158	0.16	BD136	0.22	BU105	2.50	MPSU06	0.58	TIS43	0.28
2N2102	0.60	2N3779	3.15	AC126	0.20	BC160	0.78	BD137	0.24	BU205	2.50	MPSU06	0.63	ZTX300	0.13
2N2147	0.78	2N3790	2.40	AC127	0.40	BC167B	0.15	BD138	0.26	CA3080A	1.08	MPSU06	0.80	ZTX301	0.13
2N2148	0.94	2N3791	2.35	AC128	0.35	BC168B	0.15	BD139	0.71	CA3080A	1.08	MPSU06	0.80	ZTX302	0.20
2N2160	0.90	2N3792	2.60	AC151V	0.49	BC168C	0.15	BD140	0.87	CA3028A	0.79	NE555	1.30	ZTX500	0.15
2N2218A	0.47	2N3794	0.10	AC152V	0.49	BC169B	0.15	BD530	0.80	CA3052	1.62	NE560	4.48	ZTX501	0.13
2N2219	0.42	2N3810	0.37	AC153	0.40	BC170	0.15	BD520	1.05	CA3046	0.70	NE561	4.48	ZTX502	0.18
2N2220	0.52	2N3820	0.28	AC153K	0.40	BC170	0.15	BD520	1.05	CA3048	2.11	NE565A	4.48	ZTX530	0.23
2N2221	0.45	2N3823	0.58	AC154	0.45	BC171	0.16	BF115	0.25	CA3048	2.11	NE565A	4.48	ZTX531	0.22
2N2221A	0.18	2N3904	0.19	AC176	0.21	BC172	0.12	BF117	0.19	CA3089E	1.96	OC29	1.48		
2N2221A	0.21	2N3906	0.19	AC176K	0.40	BC177	0.19	BF121	0.19	CA3090Q	4.23	OC35	1.16		
2N2222	0.20	2N4036	0.67	AC187K	0.35	BC178	0.18	BF123	0.35	LM301A	0.48	OC42	0.50		
2N2222A	0.25	2N4037	0.42	AC188K	0.40	BC179	0.21	BF125	0.35	LM308	1.17	OC45	0.32		
2N2368	0.17	2N4054	0.18	AD142	0.57	BC182	0.12	BF152	0.20	LM309K	0.88	OC71	0.17		
2N2368A	0.22	2N4059	0.15	AD143	0.68	BC182L	0.12	BF153	0.25	LM380	0.98	OC72	0.25		
2N2369	0.22	2N4060	0.15	AD149	0.74	BC183	0.12	BF154	0.16	LM381	2.07	OC81	0.25		
2N2646	0.55	2N4061	0.15	AD150	0.63	BC183L	0.12	BF159	0.27	LM702C	0.75	OC83	0.24		
2N2647	0.98	2N4062	0.15	AD161	0.69	BC184	0.13	BF160	0.23	LM741CAN	0.38	ORP12	0.60		
2N2904	0.40	2N4126	0.21	AD162	0.69	BC184	0.13	BF163	0.32	BD1	0.40	R53	1.80		
2N2905	0.47	2N4289	0.34	AF108	0.40	BC207	0.27	BF166	0.40	AD14L	0.38	SL1414A	2.35		
2N2905A	0.45	2N4919	0.95	AF109R	0.40	BC208	0.11	BF167	0.25	LM710	0.47	SL610C	2.35		
2N2906	0.33	2N4920	1.10	AF114	0.35	BC212	0.16	BF173	0.27	LM3900	0.61	SL611C	2.35		
2N2906A	0.42	2N4921	0.83	AF115	0.35	BC212L	0.16	BF177	0.29	LM723C	0.66	SL612C	2.35		
2N2907	0.22	2N4923	1.00	AF117	0.35	BC214L	0.18	BF178	0.29	LM741T099	0.40	SL620C	3.50		
2N2907A	0.24	2N5190	0.92	AF118	0.35	BC237	0.16	BF179	0.43	LM709CAN	0.48	SL621C	3.50		
2N2924	0.20	2N5191	0.96	AF124	0.30	BC239	0.15	BF181	0.36	BD1	0.40	SL623	5.75		
2N2926	0.20	2N5192	1.24	AF125	0.30	BC251	0.25	BF182	0.35	AD14L	0.38	SL640C	4.00		
2N3053	0.25	2N5195	1.46	AF126	0.28	BC253	0.25	BF183	0.55	LM747	1.05	SL641C	4.00		
2N3054	0.60	2N5245	0.29	AF127	0.28	BC257	0.15	BF184	0.30	LM748	0.44	SN76023ND	1.55		
2N3055	0.65	2N5294	0.48	AF139	0.65	BC258	0.16	BF185	0.30	BD1	0.40	SN76003N	2.92		
										LM7805	1.60	SN76013N	1.95		

NEW RANGE TOOLS — HIGH QUALITY MINIATURE ELECTRONIC PLIERS INSULATED HANDLES

- Round nose box joint 4" long £2.50
- Diagonal cutters box joint 4" long £2.80
- Flat nose box joint 4" long £2.40
- Snipe nose box joint 4" long £2.40
- Desoldering tool £4.50

P.C. MARKER PEN DALO 33PC
0.87. ZENER DIODES 400MW
0.11, 1W 0.17, 2.5W 0.35. IC
SOCKETS 8DIL 0.12, 14DIL 0.14,
16DIL 0.16. RESISTORS 1/4W
0.02 (100 per value 0.013), 1/2W
0.03 (100 per value 0.02). SCOR-
PIO CAR IGNITION KIT £12.95.
BOX £1.80 TRANSFORMERS
£3.75 IMF 440 VAC £1.50
BOARD 0.95 JUMBO
7-SEGMENT DISPLAYS £2.00.
DL 707 £1.75. MINITRON £1.50.
LEDs RED YELLOW GREEN 2in.
dia 0.24.

SEE MARSHALL'S FOR CMOS

CD4000	.18	CD4018	.88	CD4042	.70
CD4001	.18	CD4019	.52	CD4043	.83
CD4002	.18	CD4020	.98	CD4044	.77
CD4006	.99	CD4021	.88	CD4045	.30
CD4007	.18	CD4022	.85	CD4046	.20
CD4008	.82	CD4023	.18	CD4047	.95
CD4009	.52	CD4024	.72	CD4049	.45
CD4010	.52	CD4025	.19	CD4050	.45
CD4011	.18	CD4027	.43	CD4510	.25
CD4012	.18	CD4028	.83	CD4511	.94
CD4013	.45	CD4029	.06	CD4516	.25
CD4014	.89	CD4030	.52	CD4518	.87
CD4015	.89	CD4031	.98	CD4520	.87
CD4016	.45	CD4037	.88	CD4534	.07
CD4017	.88	CD4041	.70		

63 volt Mini ceramic capacitors
1pF—0.015mF 5p
Siemens 5% Polystyrene capacitors
10pF—1500pF 5p
1500pF—3300pF 5p
4300pF—101pF 20p

Veroboard


	Copper		Plain	
	0.1</			

ETI DATA SHEET

2513 CHARACTER GENERATOR

SIGNETICS

ASCII CHARACTER FONT

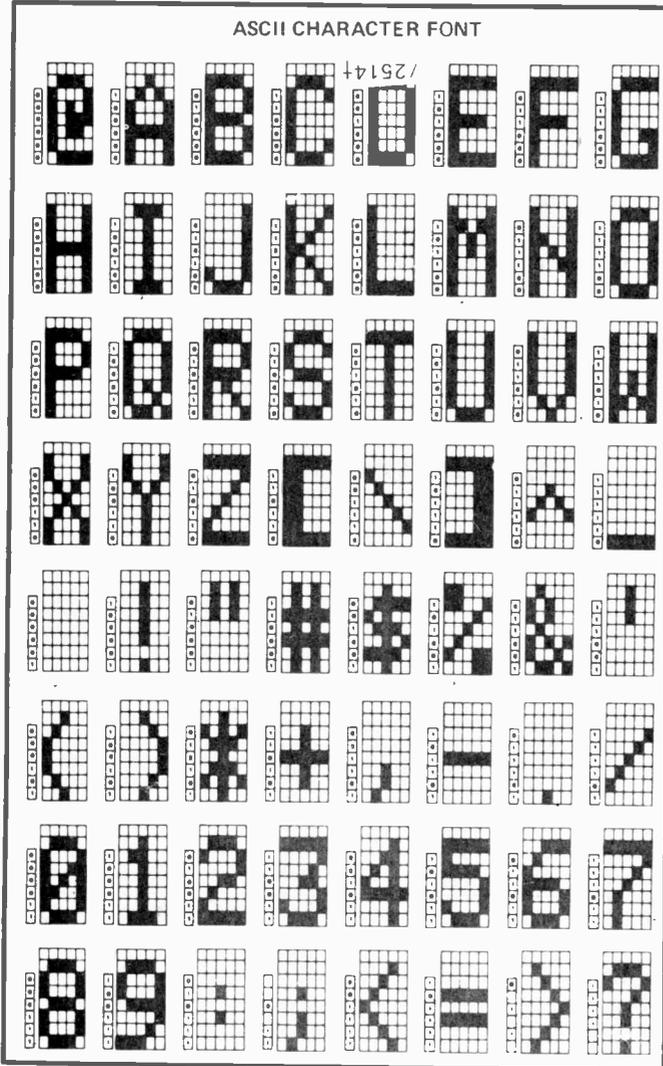

The Signetics 2513 is a high speed 2560-bit Static ROM available in 64x7x5, 64x8x5, and 512x5 versions. The product uses +5V, -5V and -12V power supplies, 5V TTL level input signals and Tri-State-Outputs for direct, low cost interfacing with TTL, DTL and MOS.

The use of Silicon Gate Low Threshold Process allows the design and production of higher functional density and operating speed.

All inputs of the 2513 can be driven directly by standard bipolar integrated circuits (TTL, DTL, etc). The data output buffers are capable of sinking a minimum of 1.6 mA, sufficient to drive one standard TTL load.

The 2513 is available from Catronics Ltd, 39 Pound Street, Carshalton, Surrey, at a price of £9.62 inc VAT plus 20p p&p.


MAXIMUM GUARANTEED RATINGS

CHARACTERISTICS	MAX
Input Load Current	500 nA
Output Leakage Current	1000 nA
V _{DD} Power Supply Current	18 mA
V _{GG} Power Supply Current	10 mA
Input Logic "0"	1.05 V
Input Logic "1"	5.3 V
Character Access Time	600 ns
Access Time (A ₄ - A ₉)	600 ns
Row Access Time (A ₁ - A ₃)	500 ns


NOTE

V_{DD} = -5V ±5%;
V_{CC} = 5V (8)
T_A = 25°C;
V_{GG} = -12V ±5%;

DTL/TTL INTERFACING

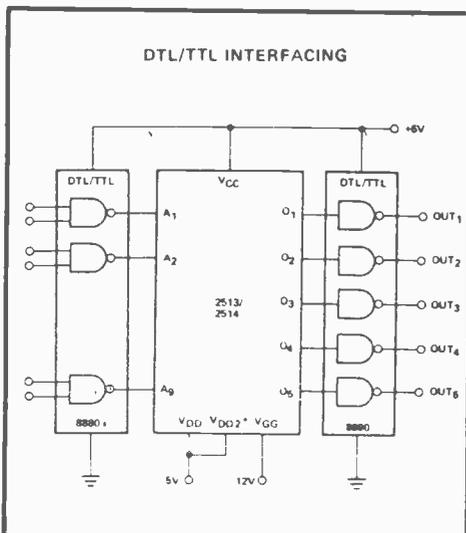

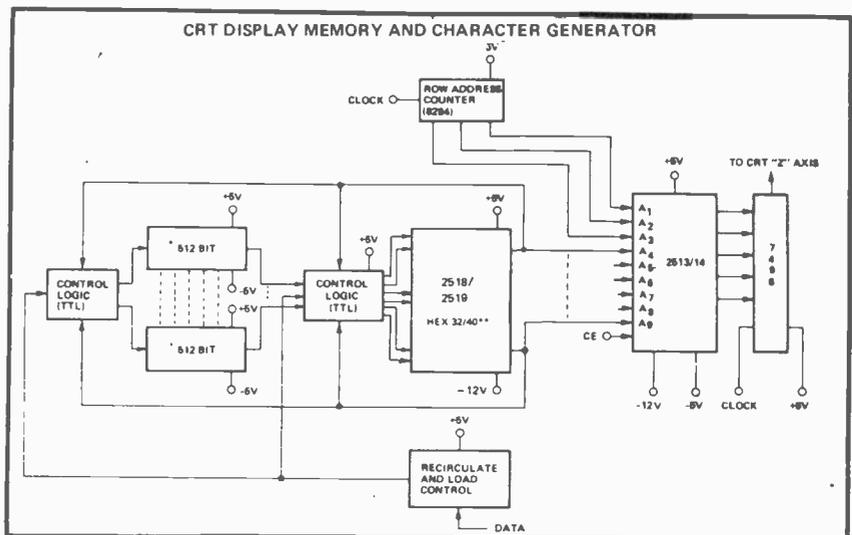CRT DISPLAY MEMORY AND CHARACTER GENERATOR



The TAD100 is a silicon integrated circuit primarily intended for a.m. receivers. The circuit incorporates the mixer, oscillator, i.f. amplifier, a.g.c. and audio pre-amplifier stages. The audio output transistors are not included so that different output power stages may be added to suit individual receiver requirements. The circuit incorporates a diode clamp to stabilise the oscillator voltage.

As a service to ETI readers, Marshalls Ltd of 42 Cricklewood Broadway, London NW2 3ET are offering the TAD 100 and the filters at a special price of £1.50 exclusive of V.A.T.

QUICK REFERENCE DATA

Supply voltage (nom.)	6.0	9.0	V
Receiver audio output power	0.7	1.5	W
Total receiver current drain (quiescent)	15	23	mA
Typical sensitivity (r.f. input voltage at pin 1 for 10mV a.f. at detector load)	6	4	µV
Typical a.g.c. range (change in r.f. input voltage for 10dB change in audio output)	59	62	dB
Typical signal-to-noise ratio (for signal level of 20µV at input)	25	24	dB
Distortion (over most of dynamic range)		< 2	%
Operating ambient temperature range	-10 to +55		°C

Refer to Fig 1.

COMPONENT VALUES

V _{CC}	6.0	9.0	9.0	V
P _{out}	0.7	1.0	1.5	W
R _L	4.0	8.0	5.0	Ω
R ₁₀	18	27	27	kΩ
R ₁₁	68	150	150	Ω
R ₁₂	390	680	390	Ω
R ₁₃	VA1040	VA1040	VA1034	
R ₁₆	3.9	15	15	kΩ
R ₁₇	4.7	10	10	kΩ
R ₁₈	27	100	120	Ω
C ₁₆	320	200	200	µF
	6.4	10	10	V
C ₂₂	640	200	400	µF
	6.4	10	10	V
C ₂₃	800	320	640	µF
	4.0	6.4	6.4	V
C ₂₄	125	32	32	µF
	4.0	4.0	4.0	V

RECEIVER SPECIFICATION

A.F. driver saturation voltage at I _C =30mA	Typ. 0.82	V
at I _C =1.0mA	—	V
R.F./I.F. sensitivity (R.F. input voltage at 1MHz 30% modulation 400Hz measured at pin 1 for 10mV a.f. at detector load)	4.0	µV
voltage at detector load for 100µV r.f. at mixer base (pin 1)	50	mV
A.G.C. range (change in r.f. input voltage for 10dB change in audio range)	62	dB
Signal-to-noise ratio for r.f. input voltage = 20µV at 1MHz	24	dB
Signal-to-noise ratio for r.f. input voltage = 1mV at 1MHz	40	dB
Percentage distortion (V _{AF} = 10mV, V _{in(RF)} modulated 30% at 400Hz)	4	%
Total receiver current drain (excepting the output pair TR1-TR2)	20	mA

NOTES

'1'
TR1-AC187, TR2-AC188. Tuning Gang Mullard type AC0049 (C₃, C₅) with 300pF padding capacitor (C₁₁) on oscillator section. C₁, C₇ are part of the i.f. filter. C₆, C₁₀ are trimmers on the tuning gang.

'2'
Oscillator coil specification
Tuned winding 100 3 × 46s.w.g. turns wavewound with
Coupling winding 10 turns bunched conductor wire on 0.2in former
Feedback winding 10 turns with ferrite core and frame Q₀ = 150

ABSOLUTE MAXIMUM RATINGS

Maximum voltage pin 6	12	V
Maximum voltage pin 2 or pin 9	9	V
Maximum current pin 6	30 peak 20 average	mA mA
P _{tot} -- Max total dissipation at T _{amb} = 55 °C	150	mW

Mullard Ltd, Mullard House, Torrington Place, London WC1E 7HD.

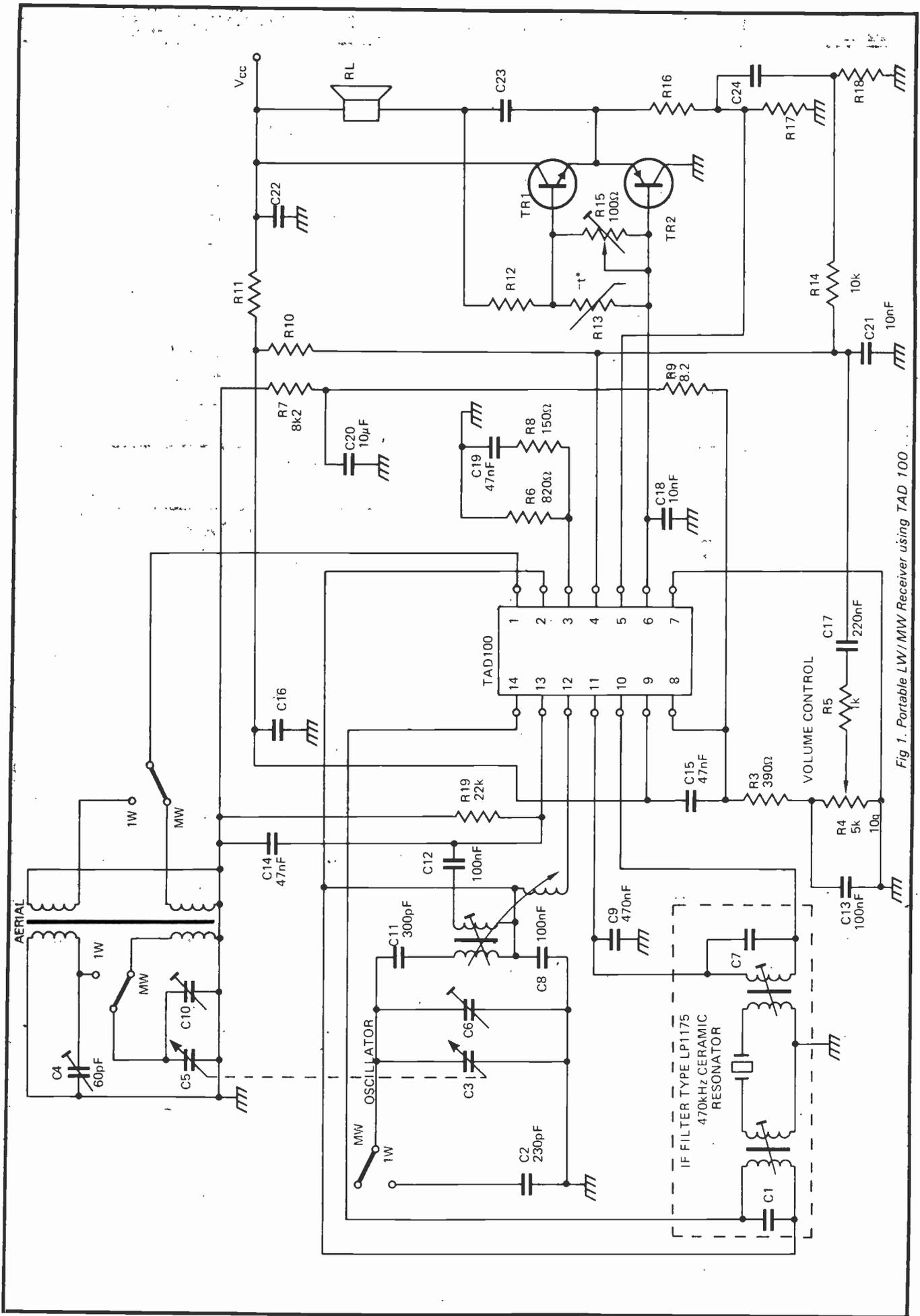


Fig 1. Portable LW/MW Receiver using TAD 100 . . .

SOUND LIGHT FLASH TRIGGER

514B

This flash trigger sets off any standard electronic flash unit a predetermined and adjustable time after a specific change in light or sound has occurred.

DURING the past few years we have received many requests to publish full constructional details of a light and sound operated photographic flash trigger that would be cheap to build, versatile in use and small enough to slip into the pocket or camera bag.

So here it is . . . it can be triggered by any sudden change in light or sound to photograph any related transient phenomena. It has innumerable applications in specialised photography, science and industry.

The device will set off any standard electronic flash unit a pre-determined time (adjustable between five milli-seconds and 200 milli-seconds) after a sudden change in ambient light or sound. The magnitude of the change required to trigger the unit is also adjustable.

The light triggering facility enables the trigger unit to be used as a slave flash.

CONSTRUCTION


Solder all components on to the printed circuit board — with the exception of the LDR and potentiometers RV1 and RV2. Ensure that capacitors C1 and C3 are correctly orientated — see overlay drawing.

Solder short lengths of tinned copper wire on to the potentiometer terminals — insert ends into the pc board and locate as shown.

Don't solder the leads through until the final position of the potentiometers relative to the rest of the assembly has been established.

When assembling the potentiometers on to the front panel space the potentiometers away from the panel by two washers on each potentiometer.

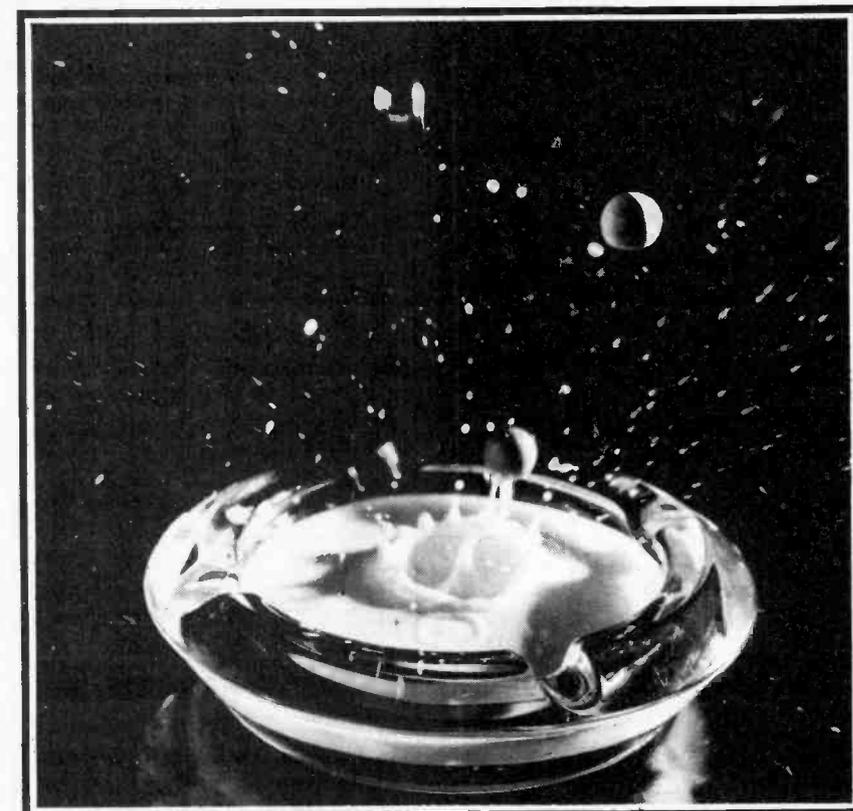Locate the LDR so that the light sensitive grid is lined up with the



hole in the front panel of the unit.

Finally mount the switch and microphone socket on to the front panel and wire them to the pc board and battery clip as shown in the component overlay.

A synchronisation extension flash lead must be purchased to suit the camera in use. Remove the unused connector from the end of the lead and solder the lead to the board as shown in the overlay.


OPERATION

To use the unit in the sound operated mode simply plug the microphone into the socket provided and connect the unit's flash lead to the camera.

Switch on SW1 and adjust RV1 so that the flash is not triggered by ambient noise, but will be triggered by the event to be recorded — ie gun firing, hands clapping, glass breaking, etc.

In most circumstances the stop action photography must be done in a dark room with the camera shutter open, or if only black and white film is used — using a red safelight.

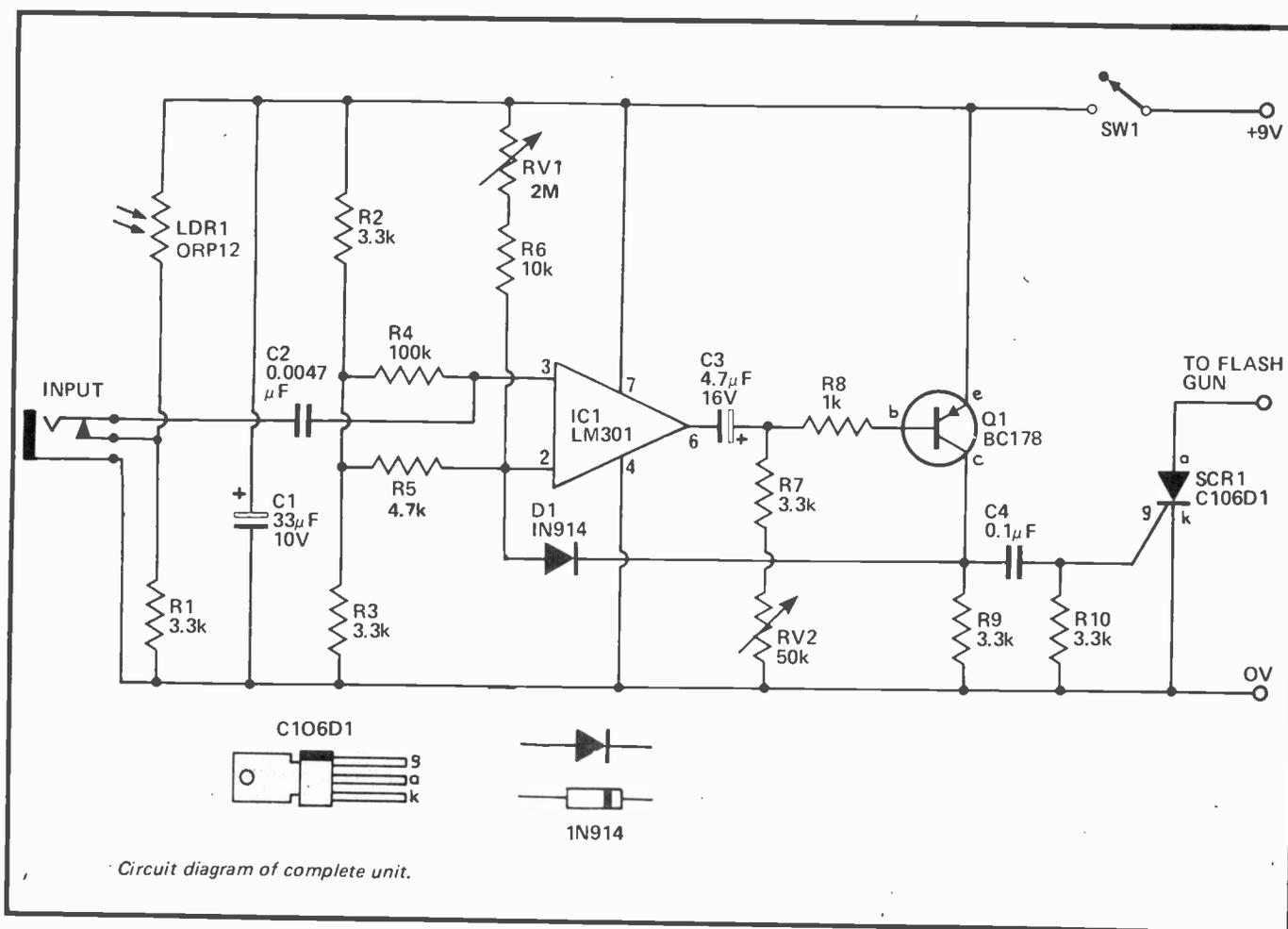Assume for example that you wanted to photograph a bottle at the instant it is broken by a stone from a catapult. The equipment, catapult and bottle are set up initially in the light and tested to confirm correct function and sequence.



PARTS LIST ETI 514B

Resistors

R1	—	3.3 k	5%	¼ W
R2	—	3.3 k	"	"
R3	—	3.3 k	"	"
R4	—	100 k	"	"
R5	—	4.7 k	"	"
R6	—	10 k	"	"
R7	—	3.3 k	"	"
R8	—	1 k	"	"
R9	—	3.3 k	"	"
R10	—	3.3 k	"	"

Potentiometers

RV1	—	2 M log rotary
RV2	—	50 k lin "

Capacitors

C1	—	33 µF 10 V electro
C2	—	0.0047 µF polyester
C3	—	4.7 µF 16 V electro
C4	—	0.1 µF polyester

Semiconductors

Q1	—	transistor BC178 or similar
D1	—	diode 1N914 or similar
IC1	—	integrated circuit LM301
SCR1	—	SCR C106 D1

Miscellaneous

LDR1	—	ORP12
PCB	—	ETI 514B
SW1	—	switch spst
3.5 mm phone jack		
plastic box, flash cord, microphone, battery and battery clip.		

HOW IT WORKS

Basically the microphone triggers the IC monostable circuit which subsequently triggers an SCR, and hence the flash, after a time delay. This delay is adjustable — by varying a monostable on-time — from 5 milliseconds to 200 milliseconds.

Integrated circuit IC1 is an LM301A. This is a dc differential amplifier with a high gain — typically 25 000. The output swing of the IC with a 9 volt dc supply is of the order of 6 volts, and this is obtained with an input swing of only 24 microvolts. This makes the IC ideally suited for use as a comparator and is the mode of operation utilised in our circuit.

Due to the very high gain and the relatively large output signals normally encountered, the IC is almost always either fully cut off or fully saturated. The linear region is very narrow and is not utilized in this circuit.

The two inputs of the IC (pins 2 and 3) would be at the same potential were it not for the bias current supplied through RV1. This raises the voltage at pin 2 of the IC by 10 mV or more above pin 3 depending on the setting of RV1. The IC will therefore normally be fully saturated and the output voltage will be low.

Transistor Q1 is normally held on by the current through RV2, and its collector is high.

When an audio signal from the microphone produces at pin 3 a level exceeding that set on pin 2 by RV1, the IC will rapidly change state and its output will go high.

The front edge of this transition turns off Q1 via C3. The collector of Q1 will fall, D1 becomes forward biased and pulls down pin 2 to about one volt — the IC output is maintained in its high state.

After a time — determined by the time constant of C3 and RV2 — Q1 turns on again allowing the IC to revert to its normal low output.

The output signal from Q1 is differentiated by C4 and R10. The positive pulse which occurs at the end of the delay period, triggers the SCR and fires the flash.

When the microphone is pulled out LDR1 and R1 are placed in circuit. When the light falling on the LDR suddenly increases, the resistance of the LDR falls and the voltage across R1 increases. This increase is passed via C2 to pin 3 of the IC triggering it if it is above that on pin 2.

SOUND LIGHT FLASH TRIGGER

A test film is then shot using an arbitrary setting of the delay in the now darkened room. This is done by opening the shutter, firing the catapult and then closing the shutter before turning on the lights. (Although shooting a bottle in the dark may seem difficult — with a little practice it is surprisingly easy. But do wear eye protection).

A run through the test film will show whether the chosen delay was correct. If too short, the bulb or bottle will be photographed before actually breaking up — if too late the action will have progressed further than needed or wanted.


Further pictures should then be taken, varying the time delay to bracket the actual delay that is now estimated as correct. With a little experience you'll be able to estimate the required delay accurately.

(Don't forget to get in a good supply of bottles).

As the flash duration is typically 1000-2000th sec, high speed action can be frozen as our lead picture shows.




light sensor in circuit — adjust the sensitivity so that the unit is triggered out by the master flash when it is operated. In this particular application the delay should be set to minimum for use as a slave flash.

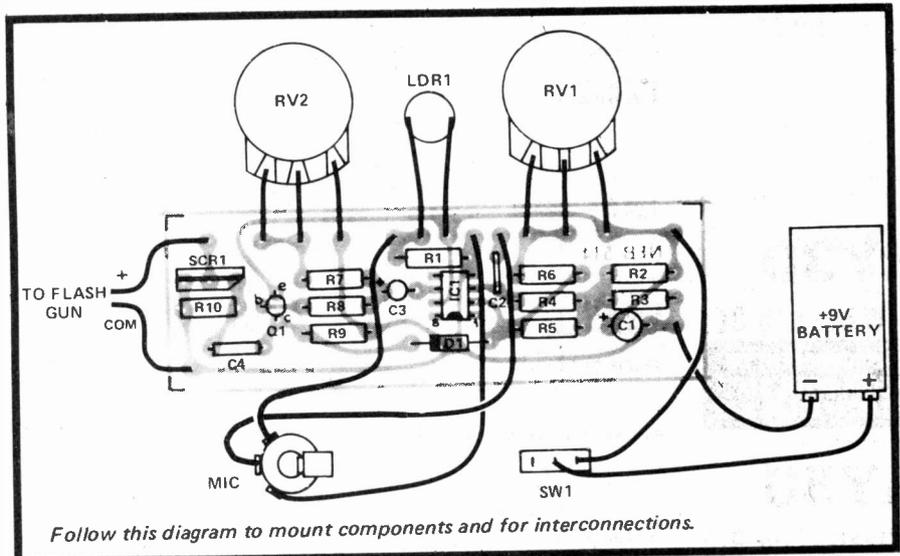Or some delay may be used to obtain a time sequence exposure. Note that the minimum delay is 5ms and hence the unit cannot be used as a slave flash for extremely fast action without a double exposure occurring. ●



SLAVE LABOUR

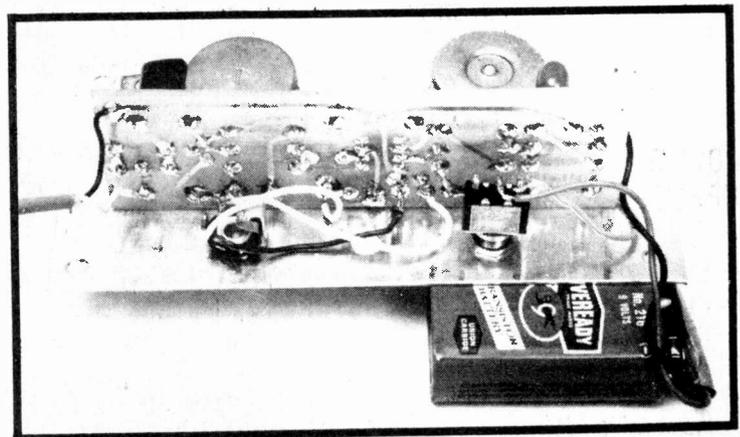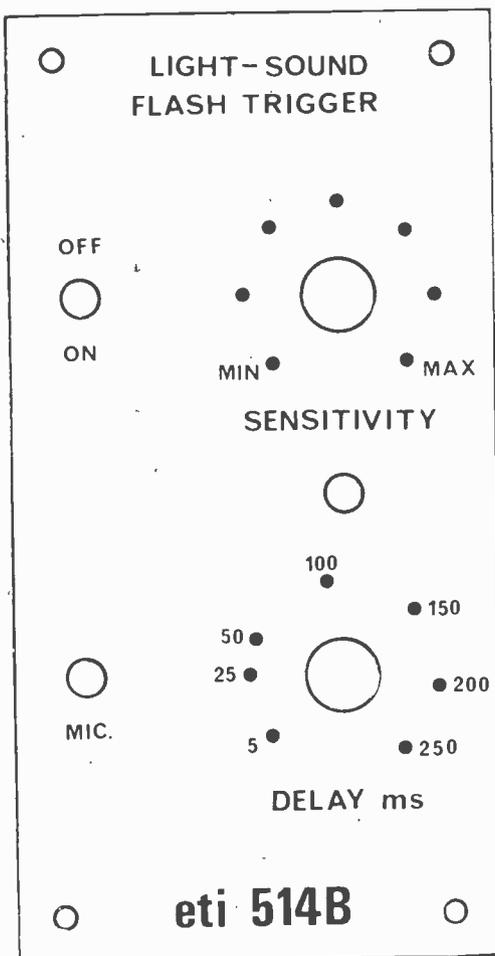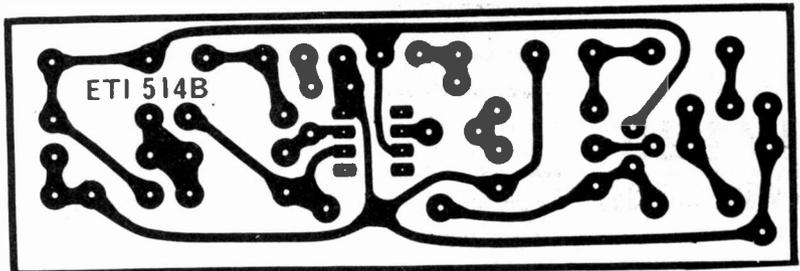To use the unit as a slave flash simply unplug the microphone. This automatically places the built-in



15 — 240 Watts!

HY5 Preamplifier

The HY5 is a mono hybrid amplifier ideally suited for all applications. All common input functions (mag Cartridge, tuner, etc) are catered for internally, the desired function is achieved either by a multi-way switch or direct connection to the appropriate pins. The internal volume and tone circuits merely require connecting to external potentiometers (not included). The HY5 is compatible with all I.L.P. power amplifiers and power supplies. To ease construction and mounting a P.C. connector is supplied with each pre amplifier.

FEATURES: Complete pre-amplifier in single pack — Multi function equalization — Low noise — Low distortion — High overload — Two simply combined for stereo

APPLICATIONS: Hi-Fi — Mixers — Disco — Guitar and Organ — Public address

SPECIFICATIONS:

INPUTS: Magnetic Pick-up 3mV Ceramic Pick-up 30mV Tuner 100mV Microphone 10mV Auxiliary 3 100mV input impedance 47k Ω at 1kHz


OUTPUTS: Tape 100mV Main output 500mV R.M.S

ACTIVE TONE CONTROLS: Treble +12dB at 10kHz Bass - at 100Hz

DISTORTION: 0.1% at 1kHz Signal Noise Ratio 68dB

OVERLOAD: 38dB on Magnetic Pick-up **SUPPLY VOLTAGE:** 16.50V

Price £4.75 + 59p VAT P&P free.

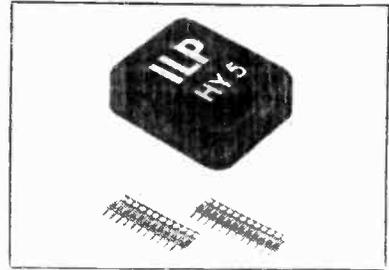

HY30

15 Watts into 8 Ω

**THIS COMPONENT ON
SPECIAL OFFER. SEE
DETAILS PAGE 38 & 39**

The HY30 is an exciting New kit from I.L.P. it features a virtually indestructible I.C. with short circuit and thermal protection. The kit consists of I.C., heatsink, P.C. board, 4 resistors, 6 capacitors mounting kit, together with easy to follow construction and operating instructions. This amplifier is ideally suited to the beginner in audio who wishes to use the most up-to-date technology available.

FEATURES: Complete Kit — Low Distortion — Short, Open and Thermal Protection — Easy to Build

APPLICATIONS: Updating audio equipment — Guitar practice amplifier — Test amplifier — audio oscillator

SPECIFICATIONS:

OUTPUT POWER: 15W R.M.S. into 8 Ω ! **DISTORTION:** 0.1% at 15W

INPUT SENSITIVITY: 500mV **FREQUENCY RESPONSE:** 10Hz-16kHz -3dB

SUPPLY VOLTAGE: 18V

Price £4.75 + 59p VAT P&P free.

**Available
June '76**

HY50

25 Watts into 8 Ω

The HY50 leads I.L.P.'s total integration approach to power amplifier design. The amplifier features an integral heatsink together with the simplicity of no external components. During the past three years the amplifier has been refined to the extent that it must be one of the most reliable and robust High Fidelity modules in the World.

FEATURES: Low Distortion — Integral Heatsink — Only five connections — 7 Amp output transistors — No external components

APPLICATIONS: Medium Power Hi-Fi systems — Low power disco — Guitar amplifier

SPECIFICATIONS: **INPUT SENSITIVITY:** 500mV

OUTPUT POWER: 25W RMS into 8 Ω ! **LOAD IMPEDANCE:** 4-16 Ω ! **DISTORTION:** 0.04% at 25W at 1kHz

SIGNAL NOISE RATIO: 75dB **FREQUENCY RESPONSE:** 10Hz-45kHz -3dB

SUPPLY VOLTAGE: 25V **SIZE:** 105x50x25mm

Price £6.20 + 77p VAT P&P free.



HY120

60 Watts into 8 Ω

The HY120 is the baby of I.L.P.'s new high power range designed to meet the most exacting requirements including load line and thermal protection this amplifier sets a new standard in modular design.

FEATURES: Very low distortion — Integral heatsink — Load line protection — Thermal protection — Five connections — No external components

APPLICATIONS: Hi-Fi — High quality disco — Public address — Monitor amplifier — Guitar and organ

SPECIFICATIONS:


INPUT SENSITIVITY: 500mV

OUTPUT POWER: 60W RMS into 8 Ω ! **LOAD IMPEDANCE:** 4-16 Ω ! **DISTORTION:** 0.04% at 60W at 1kHz

SIGNAL NOISE RATIO: 90dB **FREQUENCY RESPONSE:** 10Hz-45kHz -3dB **SUPPLY VOLTAGE:** 35V

SIZE: 114x50x85mm

Price £14.40 + £1.16 VAT P&P free.

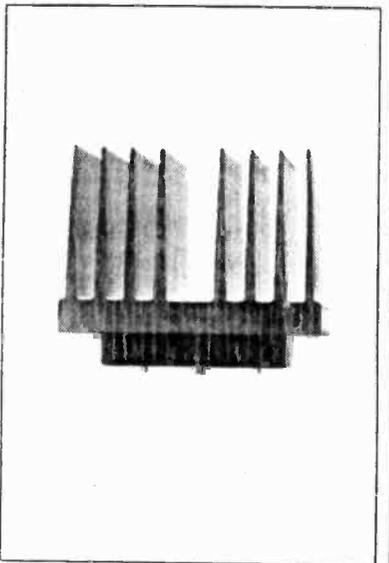

HY200

120 Watts into 8 Ω

The HY200 now improved to give an output of 120 Watts has been designed to stand the most rugged conditions such as disco or group while still retaining true Hi-Fi performance.

FEATURES: Thermal shutdown — Very low distortion — Load line protection — Integral heatsink — No external components

APPLICATIONS: Hi-Fi — Disco — Monitor — Power slave — Industrial — Public Address

SPECIFICATIONS:

INPUT SENSITIVITY: 500mV

OUTPUT POWER: 120W RMS into 8 Ω ! **LOAD IMPEDANCE:** 4-16 Ω ! **DISTORTION:** 0.05% at 100W at 1kHz

SIGNAL/NOISE RATIO: 96 dB **FREQUENCY RESPONSE:** 10Hz-45kHz -3dB **SUPPLY VOLTAGE:** 45V

SIZE: 114x100x85mm

Price £21.20 + £1.70 VAT P&P free.

HY400

240 Watts into 4 Ω

The HY400 is I.L.P.'s Big Daddy of the range producing 240W into 4 Ω ! It has been designed for high power disco or public address applications. If the amplifier is to be used at continuous high power levels a cooling fan is recommended. The amplifier includes all the qualities of the rest of the family to lead the market as a true high power hi-fidelity power module.

FEATURES: Thermal shutdown — Very low distortion — Load line protection — No external components

APPLICATIONS: Public address — Disco — Power slave — Industrial


SPECIFICATIONS:

OUTPUT POWER: 240W RMS into 4 Ω ! **LOAD IMPEDANCE:** 4-16 Ω ! **DISTORTION:** 0.1% at 240W at 1kHz

SIGNAL NOISE RATIO: 94dB **FREQUENCY RESPONSE:** 10Hz-45kHz -3dB **SUPPLY VOLTAGE:** 45V

INPUT SENSITIVITY: 500mV **SIZE:** 114x100x85mm

Price £29.25 + £2.34 VAT P&P free.

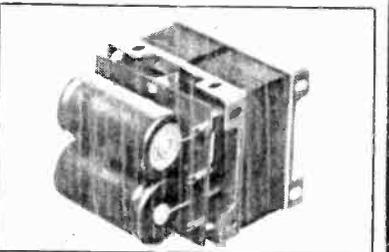

POWER SUPPLIES

PSU16 suitable for two HY30's £4.75 plus 59p VAT P. P. free
PSU50 suitable for two HY50's £6.20 plus 77p VAT P. P. free
PSU70 suitable for two HY120's £12.50 plus 1.00 VAT P. P. free
PSU90 suitable for one HY200 £11.50 plus 1.00 VAT P. P. free
PSU180 suitable for two HY200's or one HY400 £21.00 plus 1.68 VAT P. P. free

TWO YEARS' GUARANTEE ON ALL OF OUR PRODUCTS

I.L.P. Electronics Ltd
Crossland House
Nackington, Canterbury
Kent CT4 7AD
Tel (0227) 63218

Please Supply _____
Total Purchase Price _____
I Enclose Cheque Postal Orders Money Order
Please debit my Access account Barclaycard account
Account number _____
Name & Address _____
Signature _____

PART 6; MPUS 4 U

OVER THE PAST FEW MONTHS, a goodly proportion of our readers have been going through a general 'finding out' phase, and we've done our bit like a good informative electronics mag should do, to the extent of pushing microprocessors for what has seemed like no apparent reason. We've been through all the stuff about what a micro is, and what it does, and how it does it — all good stuff but a bit *theoretical*, wouldn't you say?


So what happens if you want to do something *practical* with microprocessors? At the moment, the answer is sadly, very little unless you have a fair amount of the crinkly green stuff (£800 for a teletype, etc, etc . . .). The amateur constructor is fascinated by this new device which could provide him with months of interest and enjoyment (that's what the hobby's about, right?) yet he can't quite get there because, no matter how cheap the chip is, there's a lot of expensive hardware got to go with it. Right?

WRONG

The main objection for the amateur is the cost of a teletype — but a teletype is not necessary for micro-processor system input/output. This is especially true of micro systems for amateurs. The micro-processor system can interface to just about anything from a single LED up. What places the teletype constraint is the monitor program, which is written with the professional user in mind, who of course, already has a spare teletype.

If we accept that a special purpose interface for low cost I/O, with a special purpose monitor program to drive it is possible (why not?), we can design a special low cost microcomputer system. Following a good systems engineering plan to go about this, we start by setting out the requirements the system must meet, i.e. what do we want it to do?

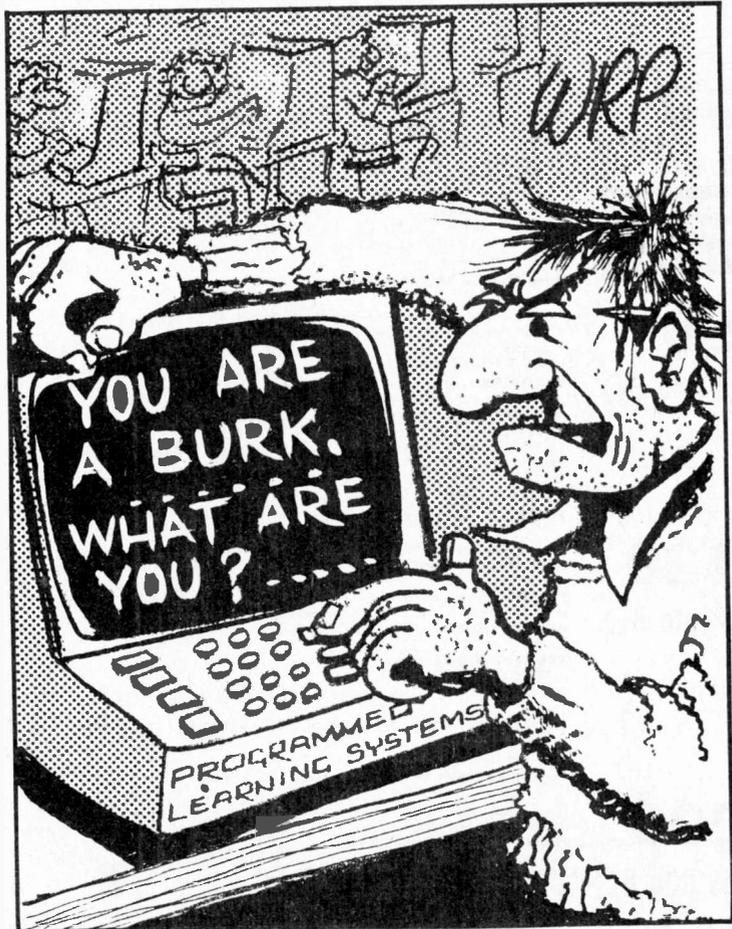If experience in the USA is anything to go by, a great many users want a MPU so they can take



up computer programming as a hobby. There is no doubt in the author's mind that programming will catch on, as people realise the potential for electronic games (moon landing, Mastermind etc), complex calculations or even just the challenge of getting a program to run. After the initial capital investment on your computer, it's cheap, useful and fun.

Beyond mathematical type programming, it is virtually impossible to predict just what people will want to do; they may want to interface to anything from a rat maze to an FM tuner. One obvious possibility, which has already been tagged for consideration at ETI, is to interface to a Teletext/Viewdata receiver. In short, a very general purpose interface is required.

PROGRAM 1/0

So far, we have postulated two types of I/O: a) through a terminal for programming and b) general purpose. Type a) will be required by everyone writing and developing programs. Let's look closer. The amateur does not have to share time on his computer terminal so he does not need hard copy, i.e. reams of paper to take away and analyse. He could write and amend his programs while sitting at the terminal with no threat of interruption.

The program in memory takes the form of pairs of hexadecimal digits, one pair to each byte of memory. Hence to load a program, the only characters required are the hex digits 0-9 and A-F, together with a key which will store each step

in memory. Also required is a key to specify the address in memory one is working at, and a key to commence program execution at a specified address. A desirable feature is a key which would let one examine the contents of a memory location for program review. That is really the bare essentials for input to the system, so let's look at output.

7-SEG DISPLAY

In *Microfile 4* (June 1976) while discussing the ROL instruction we postulated one method of driving a 7 segment display. If programmable calculators can communicate through displays of this kind, why not a basically similar MPU system? The 7 segment display can, in fact, be used to display all the Hex characters (admittedly, it's a mixture of upper and lower case) — try it yourself.

Readers who are familiar with minicomputers such as the ubiquitous DEC PDP8 will see a certain similarity to a regular front panel — except that this pseudo front panel works in a slightly different way, is to a slightly greater extent 'human engineered,' (binary brains, again!), and uses virtually no special hardware. The key to the system lies in a special ROM-stored control program which runs the whole system.

SYSTEM

OK — now we have a basic, low cost I/O system; what about the rest of the system? The keynote here, for the amateur, is *modularity*. Buy the bits you need, to start with, but that should not make expanding your system difficult, nor should you have to buy bits you don't need.

With this in mind, it seems that splitting the system into functional blocks, on sensible sized boards is a good idea, with all connections at one end so that the boards can easily be linked. The CPU board, for example, should carry the system clock, MPU and buffering to drive other boards, and a good size for this is 100 x 160 mm (Eurocard size) as a card frame can then be used to hold the boards, with connectors at the rear carrying the bus signals.

OPTIONS

The system described so far is basic, but can be used for simple program development. The main problem is the tedium involved in keying in a program each time you want to use

it. To get round this, some form of non-volatile storage is required, and perhaps the commonest form of this medium around today is cassette tape. A small board which will convert logic information to audio tones and vice versa could be coupled to an ordinary cassette recorder and programs or data stored for later use.

Another possible addition to the system is a low cost VDU such as the ETI 560 which is described elsewhere in this issue. This would permit the display of a full range of alpha numeric and special characters, thereby allowing prompts, full display of equations, etc.

PROGRAMME DEVELOPMENT

Writing programs for the simple display system can be done only in machine language, i.e. by entering the op codes of instructions directly into memory through the keyboard and then commencing execution at the first program location. Although this is slightly tedious, routines could be implemented in ROM to assist in program editing, by, for instance, re-packing memory. Another point is that output and input decoder routines could be available to the user's programs to permit input and output of data during runtime, for example.

Further developments could include the development of subroutines for multiple precision decimal addition, subtraction, etc, which could all be brought together in the form of a programmable calculator.

High-level languages are a possibility, with a VDU on the system, but the writing of assemblers and compilers is a time consuming task which most amateurs would not care to tackle, though no doubt someone will view it as a challenge to their programming ability and have a go. It's a bit like mountain climbing, really!

It will come as no surprise to many of our readers that we have been working on a system broadly similar to that described, here at ETI. We call it *System 68*, and have designed it expressly as a low cost, expandable system for the amateur. We have a number of applications programs (games etc.) under development so that there are no shortage of applications for the system, but obviously we'd like to know if you have any interesting ideas for using such a system, or any particular facility which we may have overlooked. Fortunately, the big advantage of designing with

micros is that major improvements can be incorporated into the system at a late stage at virtually zero cost. Anyway, let's hear your ideas. Remember, it's coming your way in ETI!



INTEL NEWS

Intel have just published the sixth edition of *Intel News*, a house magazine which is of interest to all engineers who are working with microcomputers or memory systems.

The publication contains a number of useful articles on such topics as refreshing dynamic RAMs in microcomputer systems, interfacing with keyboards and displays, the use of CCD memories and a novel method of producing neatly laid out programme listings. The centre pages give details of Intel's recently announced SBC-80/10 single board OEM computer and an 8-bit computer kit known as the SDK-80.

Intel Corporation (UK) Ltd., Broadfield House, 4 Between Towns Road, Cowley, Oxford OX4 3NB.

4K RAMs are dynamic devices, i.e. the information is stored as charge on capacitors which will leak away if not refreshed, so that the low order (row) address lines must be cycled periodically to prevent the stored information being lost. Intel have introduced three refresh controllers which contain all the necessary logic for this purpose. The 3222 is a refresh controller for 22-pin 4K RAMs such as the 2107A and B families. It contains a refresh timer, which is controlled by a simple RC network, and is complete with all control and I/O circuitry. Refresh can be automatic or under the control of a refresh request input line. There is also a second version of the device, the 8222, which is intended for use with the microprocessor-oriented 8107A or B 4K RAMs.

microfile

The 3232 refresh controller is intended for 16-pin multiplexed address RAMs, such as the 4K 2104, and can be used in a conventional or burst refresh mode. This device is fully compatible with 16K RAMs (when they become available).

The new SDK-80 Microcomputer Prototyping kit contains all the LSI chips, crystal, IC sockets, PCB, connectors, auxiliary components, etc., to build an 8-bit microcomputer around the new 8080A MPU, 8228 system controller and 8224 clock generator. The kit has 256 bytes of RAM, 2K bytes of PROM (including 1K of system monitor), a programmable serial communications I/O port and 24 other programmable I/O lines.

The system monitor enables the user to enter, run and check out a program, alter memory locations, examine registers etc.

Other devices announced by Intel include a special microcomputer programmable interface chip for driving keyboards and displays (the 4269) and a 256Kbit memory board designed to store video images of 512 elements by 512 lines (in-477). The 4269 will interface the 4040 MPU with a wide variety of input devices such as encoded and non-encoded keyboards and switches and will also drive alphanumeric, numeric or on/off displays, including seven-segment LEDs or Burroughs Self-scan and Panaplex displays.

Intel Corporation (UK) Ltd., Broadfield House, 4 Between Towns Road, Cowley, Oxford OX4 3NB.

ALTAIR IN UK

The Altair range of microcomputer kits and peripherals which are extremely successful in the USA, are now available in the UK from the exclusive distributor, *Compelec Electronics Ltd.* 310 Kilburn High Road, London NW6. The Altair 8800 system based on the Intel 8080 is available for £396. This includes documentation, assembly instructions, power supply, front panel components including switches and LEDs, all parts for the CPU board, card frame and box. A kit for the Motorola 6800 is also available at £290.

Comprehensive software, including a BASIC interpreter, an extended BASIC interpreter, and a BASIC disc-based operating system is available to users. The first convention of Altair users was held in Albuquerque

in March this year, and 700 people attended, many carrying their computers, to swap notes and take part in "software contests".

National Semiconductor are now in volume production of 4K RAMs in the series MM5270, 5271; MM5280, 5281 and MM5275. All utilise n-channel silicon-gate MOS, and employ single transistor cells to increase packing density and reduce cost-per-chip. Of particular interest is the MM5270, the industry's first 18-pin 4K RAM, which uses a unique concept that National call TRI-SHARE™. In this system a single lead serves three functions: (1) data read and write control, (2) logical selection of the RAM chip when operating in a system and (3) to enable an on-chip voltage regulator that is used with the output logic. Hence the TRI-SHARE™ feature, combined with TRI-STATE™ common input and output leads, eliminates four separate pins and allows almost twice the number of 4K devices on a PCB.

National Semiconductor UK Ltd., 19 Goldington Road, Bedford MK40 3LF.

NEW SEMICONDUCTOR LOGIC TECHNOLOGY

A new semiconductor technology — closed COS/MOS logic or C²L — is used in the latest microprocessor circuits from RCA Solid State. The first products using the C²L technique, which offers increased speed and packing density, are the CDP1802 single-chip 8-bit, 40-pin microprocessor and four of the associated family of memory and input/output circuits.

In conjunction with the self-aligned silicon-gate process used by RCA, C²L significantly increases device speed and packing density by a factor of 3. It differs from RCA's standard COS/MOS (complementary symmetry metal-oxide-semiconductor) technology in that it permits a common source structure, so that separate source connections are not needed for each transistor in the integrated circuit. In a C²L device, a gate electrode essentially forms a closed circle, providing the necessary gate terminations and eliminating the need for guard-bands. Even without guard-bands, C²L can still be used over the full COS/MOS voltage range.

RCA Solid State, Sunbury-on-Thames, Middlesex.

RCA MICRO KITS

The CDP 18S011 COSMAC Microtutor is a microcomputer based on the CDP 1800 series of microprocessors with 256 bytes of random-access

memory. Outputs are registered on a 2-digit hexadecimal display and a set of eight switches is provided for manual inputs. The Microtutor is intended primarily as a minimum-cost experimental/educational microprocessor system, and is accompanied by a manual written in simple language designed for people with only a basic electronics background.



Microcomputer concepts are demonstrated by sample programs which are simple to load and run on the Microtutor. All system signals can be directly observed, and an external option socket allows users to add their own circuits, typical examples being suggested in the manual. The Microtutor may also be used for prototyping COSMAC systems in applications which do not justify the use of more sophisticated programming aids.

The CDP 18S002 Stand-Alone Microkit is an enhanced version of the basic CDP 18S001 Microkit, and provides a vehicle for software support as well as a hardware prototyping environment. The additional features include expanded random-access memory capacity (4 kbyte); a modified terminal interface (providing tape reader control), a memory bank select card (for building the memory up to the full complement of 64 kbyte using 4 kbyte random-access memory cards) and expanded debugging hardware and 'firmware'.

RCA Solid State—Europe, Sunbury-on-Thames, Middlesex TW16 7HW.

'HANDS ON' MPU LEARNING MODULE

The new TI μ P Learning Module, designed to provide a simplified and effective method of gaining 'hands on' experience of microprocessor operations has recently been introduced by

Mogul Electronics Ltd. This hand held, 6½" x 5¼" x 1¼" module operates from rechargeable batteries and incorporates a 4-bit static parallel processor, is manually programmed, has VLED bus monitors, push button manual clock and contains a 40 pin socket for expansion. Also provided with this LCM 1001 module is a fully comprehensive, copiously illustrated instruction manual covering basic and advanced concepts of microprocessors.

Commencing with an introduction to Digital Machines, the manual moves through the areas of Microprocessor Operation, Data Handling, Loading and Read-out of Registers and concludes with illustrations and examples of Binary Multiplication, Division, BCD Adder and Test and Branch Operations with each stage being linked to a 'hands on' example utilising the Learning Module. The TI µP, together with the Instruction Manual and Battery Charger is available from Mogul Electronics Ltd. at £98, thereby providing a fast, low-cost method of understanding microprocessors.

Mogul Electronics Ltd. 123-124
The Stow, Harlow, Essex.

TAKING THE NAME IN VAIN!

Now available from the Engineering Division of The Exchange Telegraph

Company Ltd. (EXTEL), the DTC Micro-File combines a microcomputer, a dual flexible disc drive, and a basic 8k characters of random-access-memory (expandable to 56k) in a compact table top unit. The design concept of Micro-File is such that any RS-232 compatible data terminal can be transformed into a powerful stand-alone business system, file storage system or intelligent terminal.

Programming Micro-File is simplified by the availability of a BASIC compiler. The system incorporates a powerful text editor, allowing an operator to create, modify and erase data files or application programs. When combined with a high print quality terminal such as the DTC 300 (also available from EXTEL), Micro-File can be used as an extremely

versatile word processing system. An automatic letter writer program is already available with Micro-File.

An important software feature offered to Micro-File users is a BASIC assembler which enables users to write their own program in this widely used language. The BASIC assembler makes the machine ideal for carrying out a variety of business-oriented programs, and the cost of Micro-File is low enough to be justified for in-house use — an important asset for small business computer users.

Micro-File configurations start at £2800 (plus VAT) and a typical system using the BASIC assembler costs about £3700 (plus VAT).

The Exchange Telegraph Company Limited, Engineering Division, 73/75 Scrutton Street, London EC2A 4PB. ●




CONTINUOUS DISPLAY LCD WATCHES

UNIQUE ALTERNATING DISPLAY FEATURE

The watch continuously displays HRS. and MINS. with MONTH, DAY and SECONDS on demand. The owner selects the feature where the HRS. and MINS. or MONTH and DAY display alternatively for 2 second intervals until owner resets to normal display. During the alternating cycle seconds are still available on demand.

- **Finest American MOS technology
- **Quartz accuracy.
- **Multi-function:
Hrs., Mins., Month, Day, Seconds.
Alternating display Back-light.
Programmed 28, 30, 31 day months.
A.M./P.M. indication for ease of date setting
- **All important: UK factory manufacturing and servicing facilities.

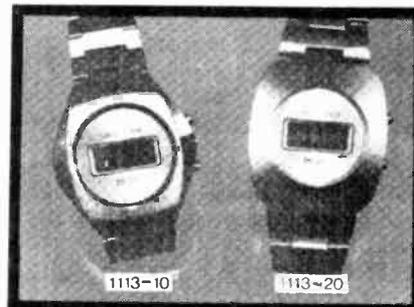Watch despatched with matching Gold plated bracelet, in presentation box with instruction booklet and guarantee. Model 1113-10 is also available in a stainless-steel bracelet.



£34.50
INCL. V.A.T. & P&P.

Leetronic

Watch Division, Lee Instrumentation Ltd.
Bedwas, Newport, Gwent NP1 8YZ
TEL. (0222) 885756-7-8. TELEX: 497084
Reg. No. 639437. VAT Reg. No. 133 8154 80

To: Leetronic, Lee Instrumentation Ltd., Newport, Gwent NP1 8YZ
Print — FREEPOST — no stamp required.

Please forward ___ (qty) model ___ at ___ each TOTAL: £ ___

I enclose cheque ___
 postal order ___
 money order ___

Name

Address

Signed

Barclaycard/Access no. _____

TECHNICAL BOOKS FROM ETI

CALCULATORS

- 99 WAYS TO KNOW AND USE YOUR ELECTRONIC CALCULATOR**
L. Frenzel £4.00
- SCIENTIFIC ANALYSIS ON YOUR POCKET CALCULATOR**
Smitt £8.25

COMPUTERS

- BEGINNERS' GUIDE TO COMPUTER LOGIC**
G. Stapleton £1.95
Grasp quickly computer codes, digital logic ops and switching circuits
- COMPUTER CIRCUITS AND HOW THEY WORK**
B. Wells £1.80
Become acquainted with the various parts of a computer and its technology
- COMPUTER TECHNICIANS HANDBOOK**
B. Ward £2.60
This giant volume compares to a 1 000 hour course on computer mechanics
- CONTROL ENGINEERING**
N. M. Morris £3.45
This is the 2nd edition of a highly successful book, keeping fully abreast of developments in control engineering
- DIGITAL ELECTRONIC CIRCUITS AND SYSTEMS**
N. M. Morris £2.60
The ideal book for the enthusiast confused by logic and digital techniques
- INTRODUCTION TO DIGITAL LOGIC**
A. Pottor £3.35
Up to date book using integrated circuits with emphasis on practical design methods

ELECTRONICS

- ACTIVE FILTER COOKBOOK**
D. Lancaster £9.75
Everything you need to know to build and use active filters
- ELECTRONIC ENGINEERS REFERENCE BOOK — 4th EDITION**
L. W. Turner £25.60
A completely new and up-to-date reference book for all engineers and students
- BASIC MATHS COURSE FOR ELECTRONICS**
H. Jacobowitz £1.75
Quick short cut way to learn the language of maths as applied to electronics
- BEGINNERS GUIDE TO ELECTRONICS**
T. L. Squires £2.55
Short cut for those wishing to obtain a quick acquaintance with modern electronics
- BEGINNERS GUIDE TO TRANSISTORS**
J. A. Reddihough £2.55
Covers the basic theory and practice of modern transistors
- DESIGNING WITH TTL INTEGRATED CIRCUITS**
Texas Instruments £5.70
Covers the entire family of TTL and practical applications of circuits in digital systems
- ELECTRONIC MEASUREMENTS SIMPLIFIED**
C. Hallmark £2.10
Covers just about every conceivable test or measurement you will need
- ELECTRONICS POCKET BOOK**
P. McGoldrick £4.15
- ELECTRONICS AND PHOTOGRAPHY**
R. Brown £2.20
Practical circuit projects devoted to photography
- ELECTRONICS SELF TAUGHT**
J. Ashe £2.20
Covers basic principles of electronics, includes a large number of simple circuits
- ESSENTIAL FORMULAE FOR ELECTRICAL AND ELECTRONIC ENGINEERS**
N. M. Morris £1.20
Handy reference book, includes a section on S1 units, resistor colour codes and preferred values
- HOW TO BUILD ELECTRONIC KITS**
V. Capel £2.10
Instructs the kit builder on how to check components, how to assemble and how to cure faults
- FIRE AND THEFT SECURITY SYSTEMS**
B. Wells £1.90
Selection and installation, home maintenance and business security devices
- HANDBOOK OF IC CIRCUIT PROJECTS**
J. Ashe £1.75
From hi-fi circuits to complete digital counters in a single package
- HOW TO READ ELECTRONIC CIRCUIT DIAGRAMS**
B. Brown £1.85
Everything you need to know from basic circuit components to integrated circuits
- HOW TO BUILD PROXIMITY DETECTORS AND METAL LOCATORS**
J. Shields £3.25
A practical do-it-yourself book

HOW TO USE IC CIRCUIT LOGIC ELEMENTS

- J. Streeter £3.25
Helps those unfamiliar with digital logic circuits
- INTEGRATED ELECTRONICS**
J. Millman £8.00
Using an IC approach the text leads the reader step by step from semiconductor physics to devices, models, circuits and systems
- INTEGRATED CIRCUIT POCKET BOOK**
R. C. Hibberd £3.90
Technology and fabrication of unipolar and bipolar IC's are discussed digital and linear IC's covered from a circuit point of view
- IC OP-AMP COOKBOOK**
W. Jung £8.25
Covers the basic theory of IC op amps in great detail, also includes 250 practical circuit applications
- INDEXED GUIDE TO MODERN ELECTRONIC CIRCUITS**
R. Goodman £2.25
Practical Schematics with concise theory and troubleshooting information
- INTRODUCING AMATEUR ELECTRONICS**
I. R. Sinclair £1.60
The book for the complete novice of any age
- INTRODUCING ELECTRONIC SYSTEMS**
I. R. Sinclair £1.75
Provides a basic insight into what makes electronics 'tick'
- INSTALLING AND SERVICING ELECTRONIC PROTECTIVE SYSTEMS**
H. Swearer £2.10
Covers installation and servicing of all electronic security systems
- LINEAR ELECTRONIC CIRCUITS AND SYSTEMS**
G. Bishop £2.55
Illustrates the use of the op amp in many different applications
- LINEAR INTEGRATED CIRCUIT APPLICATIONS**
G. Clayton £4.90
A practical approach is emphasised throughout, encouraging the reader to try out devices himself
- LINEAR IC PRINCIPLES EXPERIMENTS AND PROJECTS**
E. M. Neill £5.80
An introduction to one of electronics most exciting devices
- 110 OPERATIONAL AMPLIFIER PROJECTS FOR THE HOME CONSTRUCTOR**
R. M. Marston £2.85
Outlines the essential characteristics of op amps and presents useful projects
- 110 SEMICONDUCTOR PROJECTS FOR THE HOME CONSTRUCTOR**
R. M. Marston £2.85
Introduces the reader to FET's, SCR's and IC's with full construction details of many useful circuits
- 110 COSMOS DIGITAL IC PROJECTS FOR THE HOME CONSTRUCTOR**
R. M. Marston £3.10
- 110 INTEGRATED CIRCUIT PROJECTS FOR THE HOME CONSTRUCTOR**
R. M. Marston £2.85
All the projects have been devised, built and fully evaluated by the author
- 110 THYRISTOR PROJECTS USING SCR'S**
R. M. Marston £2.85
A companion to the author's previous books
- OPERATIONAL AMPLIFIERS DESIGN AND APPLICATIONS (Burr Brown)**
G. Tobey £5.00
Covers the entire field of operational amplifiers
- PIN POINT TRANSISTOR TROUBLES IN 12 MINUTES**
L. Garner £2.85
Complete information on circuit operations, troubleshooting charts and service procedures
- PRACTICAL TRIAC/SCR PROJECTS FOR THE EXPERIMENTER**
R. Fox £2.15
Thyristor theory and practical circuits with low cost SCR TRIACs and DIACs
- PRINCIPLES OF TRANSISTOR CIRCUITS**
S. Amos £4.40
Generally accepted as being a standard textbook on fundamental principles underlying the design of circuits and using transistors
- RAPID SERVICING OF TRANSISTOR EQUIPMENT**
G. King £2.85
A systematic guide to the servicing of transistor radio, television, tape and hi-fi equipment
- SEMICONDUCTOR CIRCUIT ELEMENTS**
T. D. Towers £6.00
Gives readers an account of all semiconductor devices commercially available, for each device it covers a general description, circuit diagram symbols and working principles
- SOLID STATE CIRCUIT GUIDE BOOK**
B. Ward £2.15
Step by step instructions to design circuits to your own specifications
- TRANSISTOR CIRCUIT DESIGN**
Texas £5.75
- TRANSISTOR POCKET BOOK**
H. Hibberd £3.65
Comprehensive guide to the characteristics and uses of various types
- TTL COOKBOOK**
D. Lancaster £5.90
Complete and detailed guide to TTL, how it works, how to use it and practical applications

UNDERSTANDING ELECTRONIC CIRCUITS

- R. Sinclair £4.00
Describes various circuits encountered today with a strong emphasis on fault finding and servicing procedures
- UNDERSTANDING ELECTRONIC COMPONENTS**
R. Sinclair £4.00
Explains about components and bridges the gap between elementary textbooks and unapproachable advanced treatments
- UNDERSTANDING CMOS INTEGRATED CIRCUITS**
R. Meien £3.50
Begins with basic digital IC's, covers semiconductor physics, CMOS fabrication technology and design
- UNDERSTANDING SOLID STATE CIRCUITS**
N. Crowhurst £1.90
Written to service the interests of anyone at sub-engineering level

SEMICONDUCTOR DATA

- INTERNATIONAL TRANSISTOR SELECTOR**
T. D. Towers £3.75
If it takes you longer than one minute to find out all about transistors, then you need a copy of this book
- POPULAR VALVE/TRANSISTOR SUBSTITUTION GUIDE** £2.15
Substitution data for both valves and transistors in one new volume
- RADIO VALVE AND SEMICONDUCTOR DATA**
A. M. Ball £2.50
Characteristics of 1,000 valves, cathode ray tubes, transistors, diodes, rectifiers and optical semi-conductors. This new edition (1975) is right up to date and over 450,000 copies have been sold
- TRANSISTOR EQUIVALENTS DATA BOOK** £3.00
- DIODE EQUIVALENT DATA BOOK** £2.65

TEST EQUIPMENT AND OSCILLOSCOPES


- BASIC ELECTRONIC TEST PROCEDURES**
I. M. Gottlieb £2.35
Shows how to get accurate measurement with VOMs meters and oscilloscopes
- ELECTRONIC TEST EQUIPMENT**
H. Kirchen £5.00
Explains the principles and requirements of particular types of test equipment including typical circuitry
- HOW TO TROUBLESHOOT AND REPAIR ELECTRONIC TEST EQUIPMENT**
M. Horowitz £2.15
Packed with practical data on repair of all types of instruments
- HOW TO TEST INSTRUMENTS IN ELECTRONIC SERVICING**
F. Schuneman £2.15
The all-in-one test instruments application handbook
- HOW TO USE VECTORSCOPES, OSCILLOSCOPES AND SWEEP SIGNAL GENERATORS**
S. Prentiss £1.95
A practical guide that tells how to use modern TV test instruments
- HOW TO USE YOUR VOM VTVM AND OSCILLOSCOPE**
M. Clifford £1.85
Tremendous value in helping to select instruments best suited to individual needs
- THE OSCILLOSCOPE**
G. Zwick £2.10
Starts from the first principles and takes the reader to an advanced level
- PRACTICAL TEST EQUIPMENT YOU CAN BUILD**
W. Green £2.15
For technicians, radio/TV service operators and serious experimenters
- RADIO, TV AND AUDIO TEST EQUIPMENT**
G. King £4.95
A practical guide to test instruments and applications, concerned largely with the oscilloscope
- TEST INSTRUMENTS FOR ELECTRONICS**
M. Clifford £1.65
Easy modifications to your VOM/VTVM and scope with the aid of this book
- WORKING WITH THE OSCILLOSCOPE**
A. Saunders £1.85
Includes workshop test projects with large size drawings
- SERVICING WITH THE OSCILLOSCOPE (January 1976)** £5.00
Includes a unique series of photographs showing oscilloscope traces to be found in normal and faulty equipment stereo radio colour TV Circuits servicing is dealt with

HOW TO ORDER

All prices are correct at the time of going to press but are subject to alteration without notice. All prices include postage. Please print your name and address clearly and list each title and price separately. Cheques and postal orders should be made payable to ETI Book Service. Books are sent on seven days' approval against a full cash remittance, plus postage. Book stock is not held at ETI's London offices and orders should be sent to: ETI BOOK SERVICE, 25 COURT CLOSE, BRAY, MAIDENHEAD, BERKS.

LOW COST VDU

ed project 560

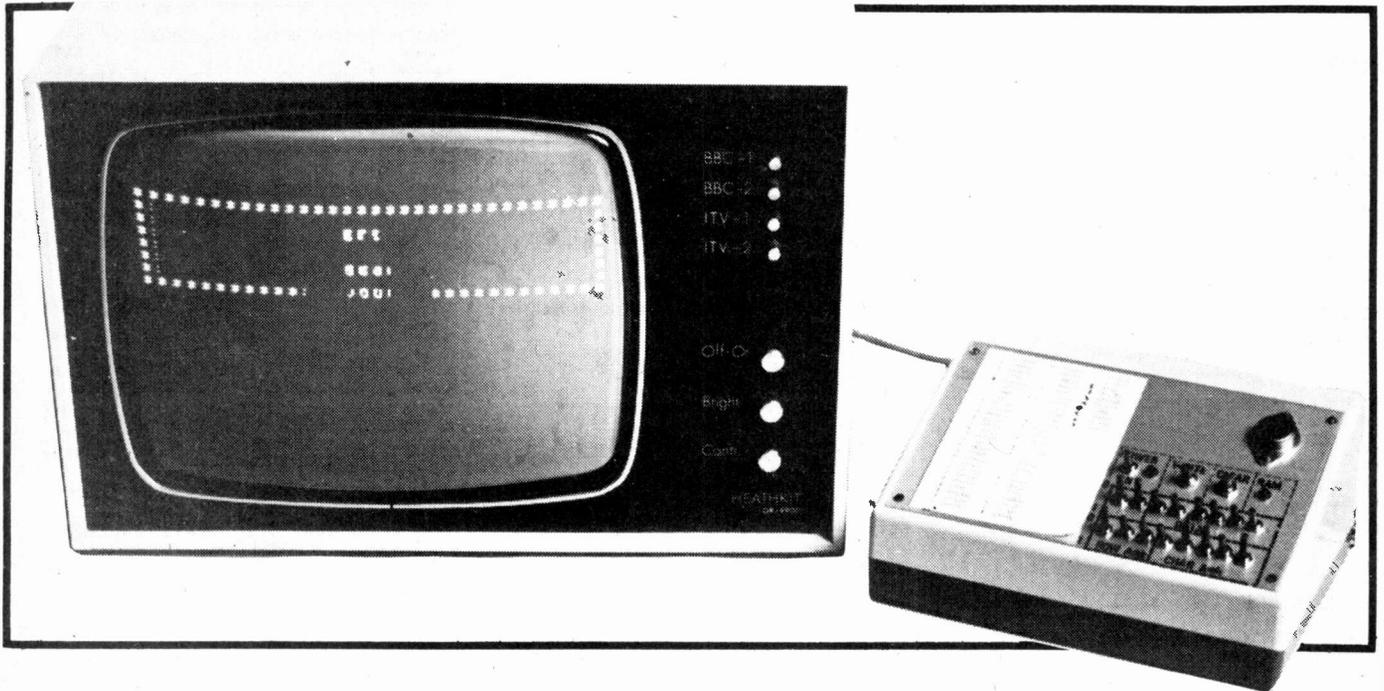

NO-FRILLS DESIGN IDEAL FOR MPU

Part 1: Introduction

A LOT OF YOU MAY now be used to seeing electronic character generation on a TV screen in TV games, Teletext and Viewdata, computer terminals, sports timings, etc. The 560 is a basic video character generation system which can be used for the above applications but is designed to be used as a VDU input/output peripheral for a micro-processor or for sub-titles or messages in a closed circuit TV system or studio. The basic system to be described next month will allow for several modifications and options but in its basic form will cost under £50 to build.

The VDU will display a total of 64 different characters in any of 256 positions set out as eight lines each containing 32 character spaces. It can be expanded to display either 8, 16 or 24 rows of 32 or 40 characters, and graphics and two-tone or flashing options can be added later.

Input to the system is via three sets of inputs — data, address and control, these can be generated from switches, MPU or from a keyboard controller.

DESIGN REQUIREMENTS


The character style usually used in this type of application is the 5x7 dot matrix where 35 dots are arranged as seven horizontal rows of five dots, and the pattern of illuminated dots defines a character. This information is supplied by a character generator ROM which outputs the status of the dots in each row on five outputs while a simple BCD 0-7 address defines which row is to be output (row 0 is always blank). On a TV screen the smallest characters can be obtained when one TV scan line is equivalent to one character row, if we allow for a space between each line of character on rows 1-7. With just over 300 scan lines on a TV

screen this gives us a maximum of 30 character lines and as the RAMs give us units of eight rows our maximum is therefore 24 character rows.

To get the verticals of our characters in ratio to the horizontals we must split up each TV line into just over 300 dots, again if we use a 7490 counter we need 320 dots (for 32 spaces) in just under one TV line. Each TV line is $64\mu\text{S}$, so that allowing for flyback time and a border at each side we have to generate 320 dots in approx $50\mu\text{S}$, ie at about 160nS intervals or 6.4MHz.

SYSTEM DESCRIPTION

Figure 1 shows the system block diagram in its simplest form. The sync signals for the TV are generated as field sync (FS) and line sync (LS) and a mixed sync which is passed to the video mixer stage. FS occurs off the screen to the top and thus we have to define a time after FS when we want the display to start. To do this a monostable is triggered by FS

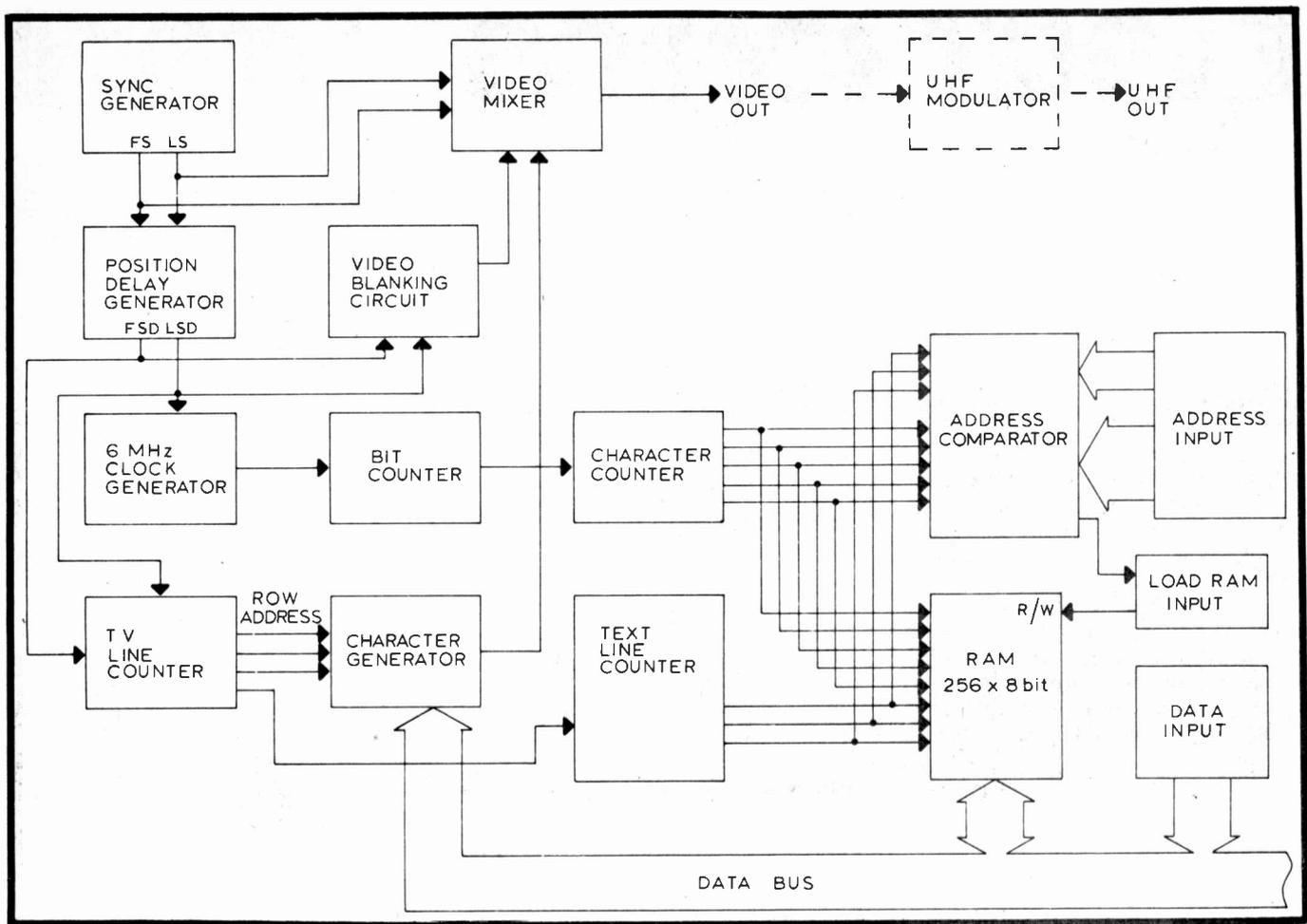

and its trailing edge is used to start the vertical display. This signal is called FSD and a similar signal LSD is derived from LS. These signals define our top and left-hand borders and are fed to the blanking circuit so that no video can be output during these periods. LSD is also used to synchronise the 6MHz clock so that the character dots all start at the same distance from the side of the screen, LS is used as a row counter input with 0-7 outputs to the character generator and a once per line output to the text line counter. The 6MHz signal is input to a bit counter and from there to the character generator and character counter. Data is input to the character generator from the RAM which is continuously addressed by the character and row counter outputs so that the data for each character is output as that character display position is addressed.

Data is input to the system by setting up the address of the required display position and comparing this address to the outputs from the character and row counters. When both addresses are the same an equal output is generated which may be used to transfer the data on the data bus into the RAM by enabling the WRITE input

of the RAM. The data is thus written into the RAM and will be displayed on the next cycle.

The output from the video mixer can be fed directly into the video input of any receiver or can be modulated to enable it to be fed in via a UHF aerial socket.

APPLICATIONS

On the basic system the input of data, address and controls is done with switches and push buttons which can be replaced with any TTL compatible inputs. The obvious application is to use the 560 as an I/O device connected to an MPU with the input being presented either from a PIA or by direct addressing with the data on the MPU data bus, the VDU RAM can be read by the MPU and thus a program can be written in the VDU and then executed by the MPU.

If the input is fed from a slow speed counter then this counter can be controlled by a cursor counter control connected to a full keyboard which would allow for much faster input to screenriter than from switches. A faster I/O method would be to use a cassette recorder to carry the input information; this data could be recorded on one track of a stereo machine with the bit clock

on the other track. The data could be loaded onto the cassette or read from it by a simple interface in the form of a complete 256 characters, rows of 32 characters preceded by a row address character or as a unique character address and data.

If used as a subtitle unit the sync signals would have to be derived from the rest of the CCTV system, here the unit could be used to put video sub-titles onto a video recording or could be used 'live' with input from a cassette recorder triggered by a manual signal.

If correct switching or TRI-STATE units are used for input then data for different parts of the screen can be derived from different units. For instance it would be possible to construct the unit so that the first characters in the first row were always loaded from a digital clock chip such as an MM5318.

CONSTRUCTION

Full constructional details of the basic unit will be given next month together with complete component list. The finished unit is self contained with its own power supply and an I/O socket at the rear for connection to MPU or other equipment.

Concluded next month.....

ELECTRONICS

-it's easy!

PART 30

Code converters and display systems.

IT IS both necessary and convenient to transfer data between sub units of a digital system, by means of some kind of code. We have seen in the previous section how counting stages are sometimes arranged to count in BCD (Binary Coded Decimal), and how this form of code must then be 'converted' into another form that is suitable for the particular kind of display device used. Thus codes and code converters are of great importance in digital instrumentation.

In this section we will not discuss codes like ASCII, Baudot, Excess 3 etc, which are computer and communication codes, but restrict ourselves to those codes and converters which are concerned with counting and display.

a much faster method is to use logic gates in a parallel arrangement. The parallel method works well for BCD to decimal and other cases but requires innumerable connections when set to convert decimal or BCD back to binary. It is little used in this reverse mode.

BINARY CODED DECIMAL TO DECIMAL AND OTHERS

Each BCD stage stores its decimal number as some form of binary code using four bits. The 1-2-4-8 weighting is the most usual form used but other codes such as the 'excess three' and the 'Aiken' variations, are also used. Thus, each of the digit values 0 to 9 (in decimal) is represented by four

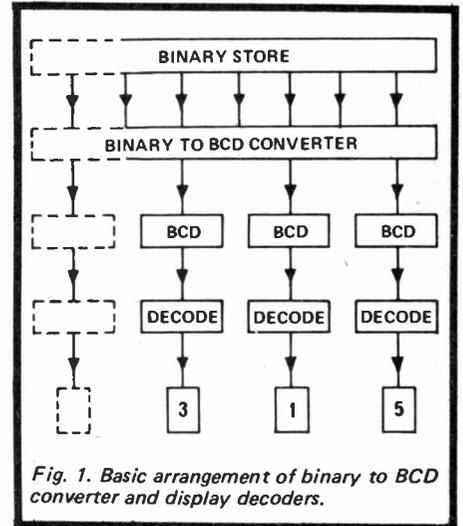


Fig. 1. Basic arrangement of binary to BCD converter and display decoders.

BINARY TO BCD CONVERSION AND VICE VERSA

To convert binary to BCD a common method is to set a binary counter — see Fig. 3 — to the desired number either by direct counting upward from zero, or by transferring the value across from another stage with a parallel converter. Clock pulses are then fed into both this binary counter, now set to count back down to zero, and to an up-counting BCD counter. A detector senses when the binary counter reaches the 0000 state upon which any further changes in the count state of both units are inhibited. The BCD equivalent of the binary number is now held in the BCD counter.

At this point the BCD number is cleared into a store or is available for any other system need, the binary counter is reloaded and the process repeated to convert the next number from binary to BCD.

The reverse, BCD to binary, is accomplished in the same manner except this time the roles are reversed as shown in Fig. 4. The BCD counter is set to the desired number, the clock, when enabled, clocks the BCD counter down to zero and at the same time the binary counter upward. When the BCD counter reaches zero state its outputs logically inhibit the clock input to both counters. The process is repeated for each new number after clearing and resetting the two counters to the correct starting conditions.

This serial method is fairly slow and

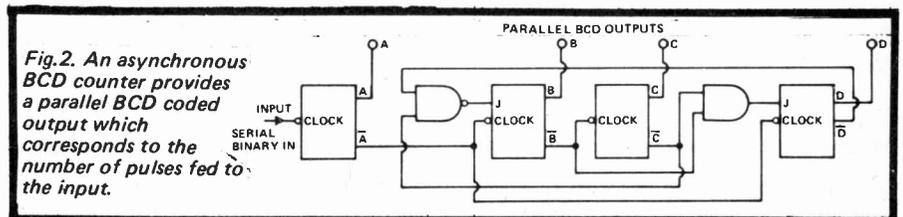


Fig. 2. An asynchronous BCD counter provides a parallel BCD coded output which corresponds to the number of pulses fed to the input.

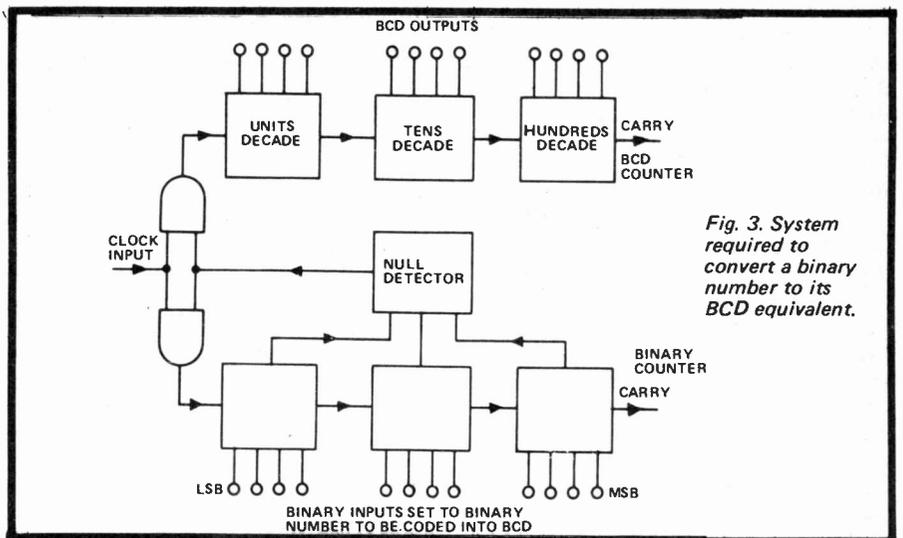


Fig. 3. System required to convert a binary number to its BCD equivalent.

lines, each having a '0' or a '1' state. This is demonstrated by studying the truth table for equivalent BCD and decimal states given in Fig. 5.

When the output must finally appear as decimal indication, it is necessary to energise the display or character printer segments appropriately. Displays, such as the neon tube or the columnar style — see previous part — require one output for each of the 0 — 9 numbers. From the truth-table of

Fig. 5 it can be seen that to energise, say, a decimal '4' output we must set up a logic gate that provides an output when the BCD state is 0100. For '8' we need a BCD state of 1000. It is not possible to totally economise by using only '1', as the logical indications for this leads to ambiguities between numbers. On the other hand there is no need to arrange for all code sequences and bit combinations as that introduces redundancies using up extra

unnecessary gates.

By careful design, and the use of inverters to invert '0' to '1's, it is possible to find a minimum number of AND gates and interconnections that will produce the 10 decimal states (0 to 9) as distinct outputs from the four-line (A B C D) outputs of the BCD stage. One such scheme is given in Fig. 6. Thus, by the use of logic gates alone we can provide a parallel code conversion from BCD to decimal.

Getting from BCD to a format suitable to drive a seven-segment display requires more gates, see Fig. 7, but the technique is basically the same. A decoder suited for the BCD to decimal requirement of a neon tube is quite unsuited to drive a seven-segment display. As both these and other conversions are in great demand they are available as simple ICs. Further, in some options the decoding logic is integrated onto the same chip as the BCD counter stage.

In practice the need to understand the internal operation of the decoder arrangement rarely arises, for the ICs are clearly marked with the connections to be made — it is just a case of making correct connections between the counter-stage chip, the decoder chip, and the display.

THE NEED FOR DISPLAY DRIVER STAGES

The power levels available from decoder stages are rarely adequate for direct drive of display units. A buffer stage which raises the power level is normally required. Again, these are generally incorporated into the decoder IC stage. Such integrated units are known as decoder/drivers. Different displays, even of the same format, require differing power needs so it is important to select decoder/driver stages suited to the display being used.

The buffer stage of a decoder/driver obtains current (or voltage gain) by the use of a transistor stage such as a Darlington pair or an emitter-follower circuit. A method recommended for driving seven-segment fluorescent displays is shown in Fig. 8 — these displays require high voltage drives.

Sometimes the need arises to drive displays from special-purpose one-off decoding circuits. In such cases a suitable driver stage is obtained by using standard IC inverter chips. (Discussed in Part 25).

THE ASSEMBLED BASIC COUNTER WITH DISPLAY

An illustration of the actual construction of a complete counting stage is to be found inside the digital clock shown in Fig. 9a. The display — neon tubes in this case — is arranged to

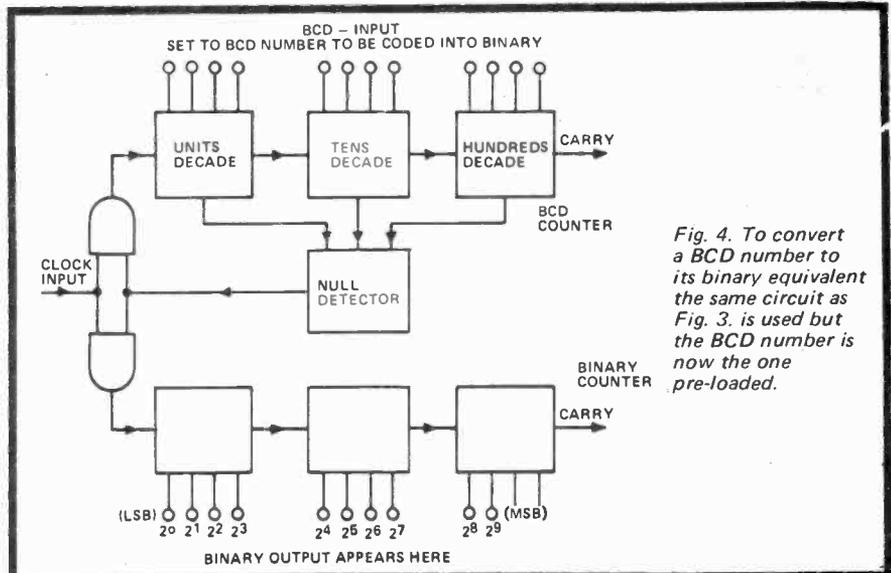


Fig. 4. To convert a BCD number to its binary equivalent the same circuit as Fig. 3. is used but the BCD number is now the one pre-loaded.

B.C.D. Inputs				Outputs										Decimal equivalent	
A	B	C	D	0	1	2	3	4	5	6	7	8	9		
0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0
1	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	1	0	0	0	0	0	0	0	0	0
1	1	0	0	0	0	0	1	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	1	0	0	0	0	0	0	0
1	0	1	0	0	0	0	0	0	1	0	0	0	0	0	0
0	1	1	0	0	0	0	0	0	0	0	1	0	0	0	0
1	1	1	0	0	0	0	0	0	0	0	0	0	1	0	0
0	0	0	1	0	0	0	0	0	0	0	0	0	0	1	0
1	0	0	1	0	0	0	0	0	0	0	0	0	0	0	1
0	1	0	1	0	0	0	0	0	0	0	0	0	0	0	0
1	1	0	1	0	0	0	0	0	0	0	0	0	0	0	0
0	0	1	1	0	0	0	0	0	0	0	0	0	0	0	0
1	0	1	1	0	0	0	0	0	0	0	0	0	0	0	0
0	1	1	1	0	0	0	0	0	0	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0	0	0	0	0	0

Fig. 5. Truth table relating four-line BCD with its decimal equivalents.


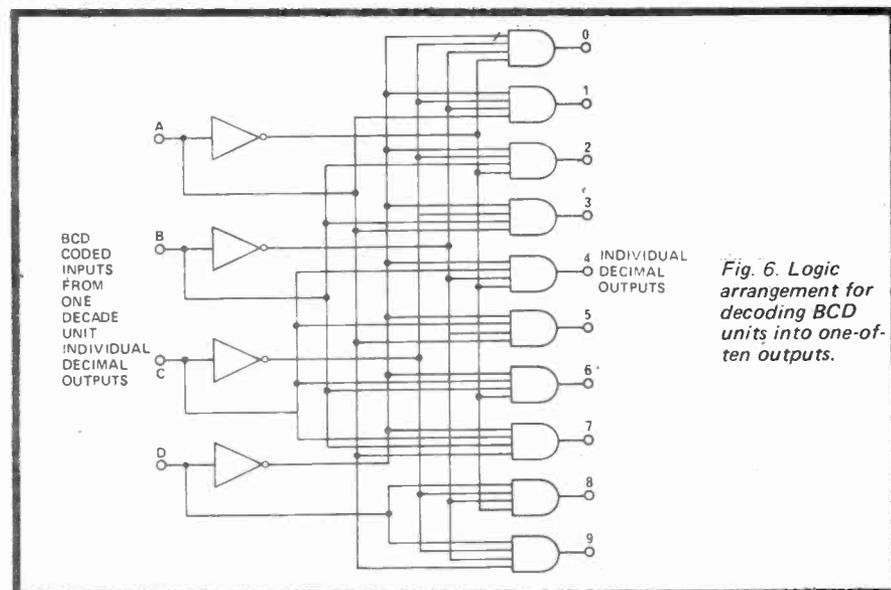
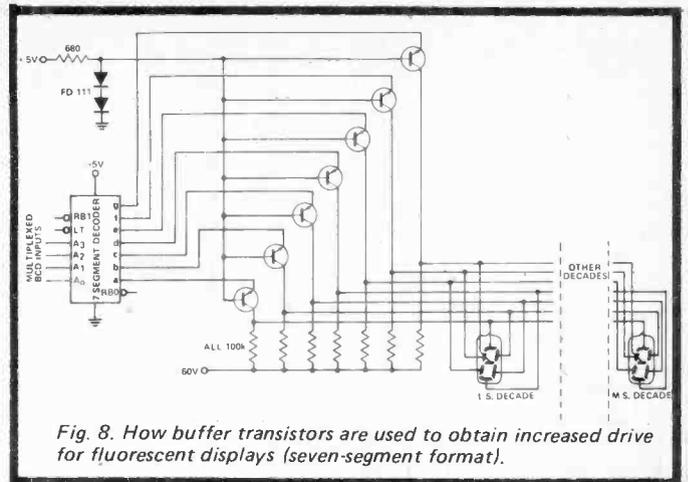


Fig. 6. Logic arrangement for decoding BCD units into one-of-ten outputs.

appear where required by using end-connected tubes which plug into the main printed-circuit board as shown in Fig. 9b. Immediately behind

each neon tube is the decoder/driver IC which, in turn, is driven by the counter IC located behind that again. On the circuit diagram these appear as

ELECTRONICS -it's easy!

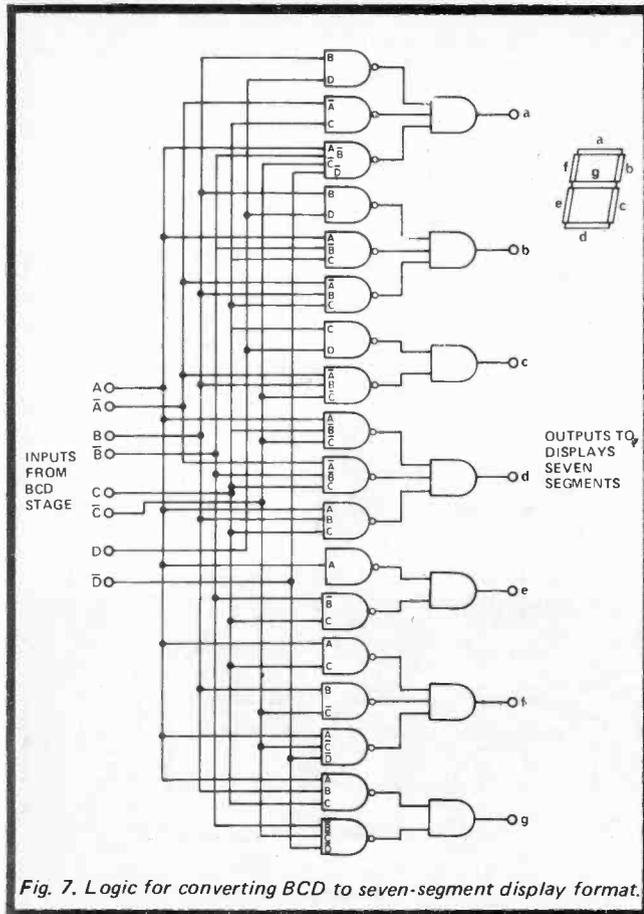

and decoder stages.

Internally a latch is a bi-stable designed specifically for the purpose of storing and transferring the value of a digital bit. Integrated circuit units provide four such latches in a dual-in-line package — see Fig. 11, thus allowing the four line data from a BCD counter to be sampled and stored by a single IC.

DECIMAL POINT

Facilities are usually provided in all displays to enable an input to energise a left-hand or right-hand point at each digit position. Obviously specific


shown in Fig. 9c and on the component overlay of the PC board as in Fig. 9d.

The Texas Instruments TIL 306 LSI is an example of an IC unit that incorporates the counter, decoder, driver, and display in one package. No doubt this will be the trend as it provides reduced assembly costs and smaller packaging. It should not be unrealistic to expect complete single-IC, multi-stage counter units to be in general use before long.


LATCHES




Direct coupling of the display to the counter stage results in a continuously changing display value. If the input is sufficiently dynamic it is awkward, if not impossible, to read values. Addition of a latch overcomes this by sampling and storing the count to be displayed for fixed intervals whilst the counter continues to cycle.

This is achieved using a memory stage between the counter and the decoder/driver stage as shown in Fig. 10. This system, the digital end of a digital voltmeter, displays a steady value for a short period by transferring the instantaneous value of the divider stage (the counter) into a buffer-store stage. The transfer or updating process is initiated by a common display timing line which is actuated at appropriate intervals. Such latches are invariably placed between the counter

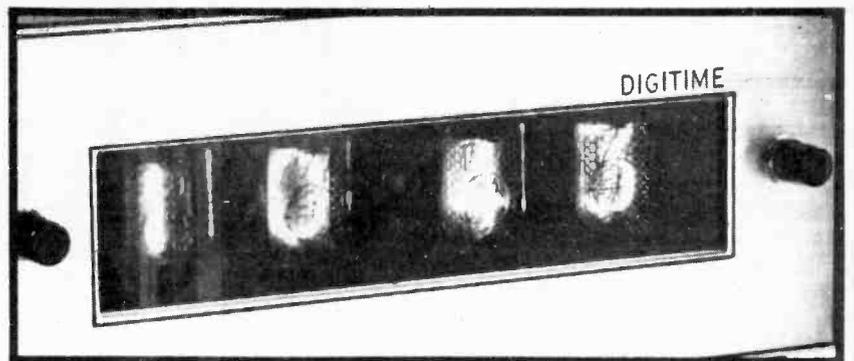

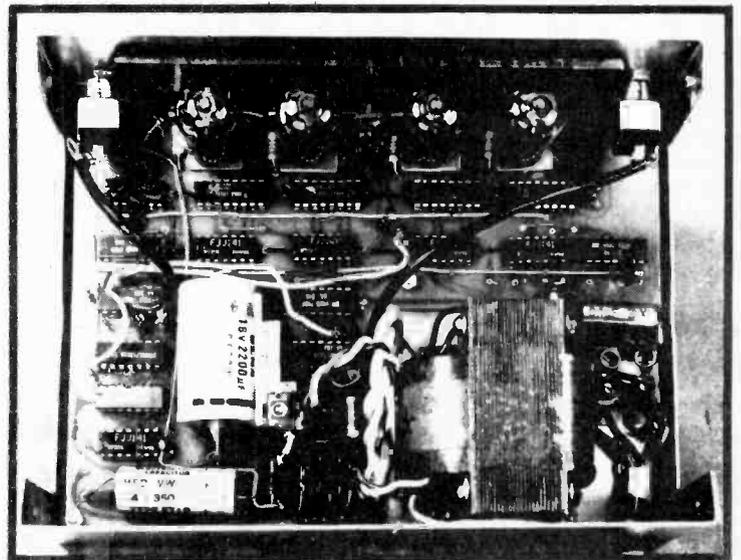(a) The frontal appearance of the Nixie display.



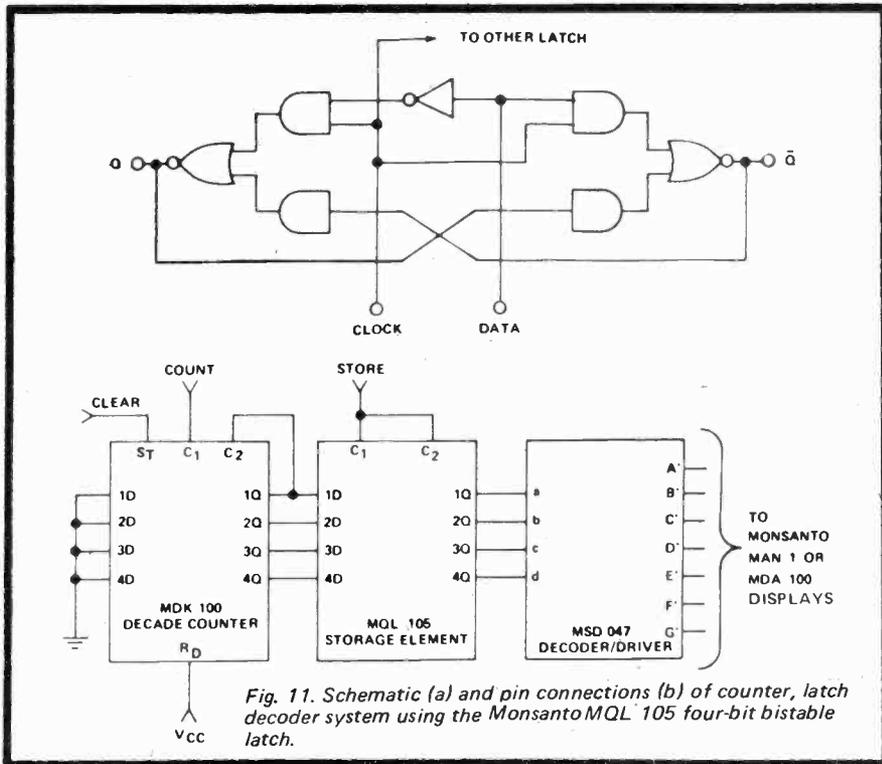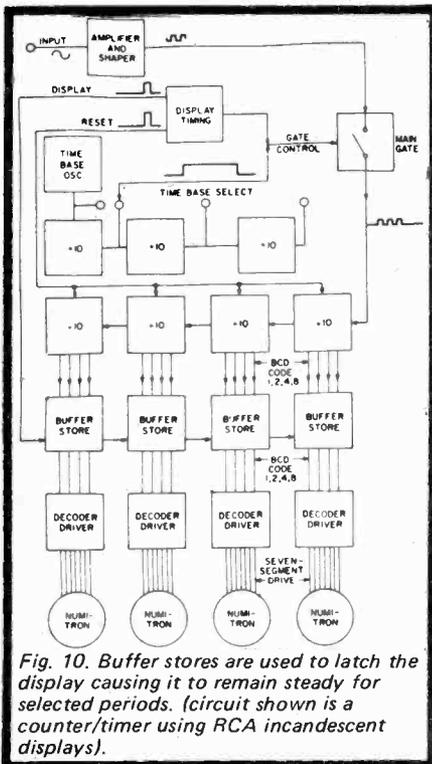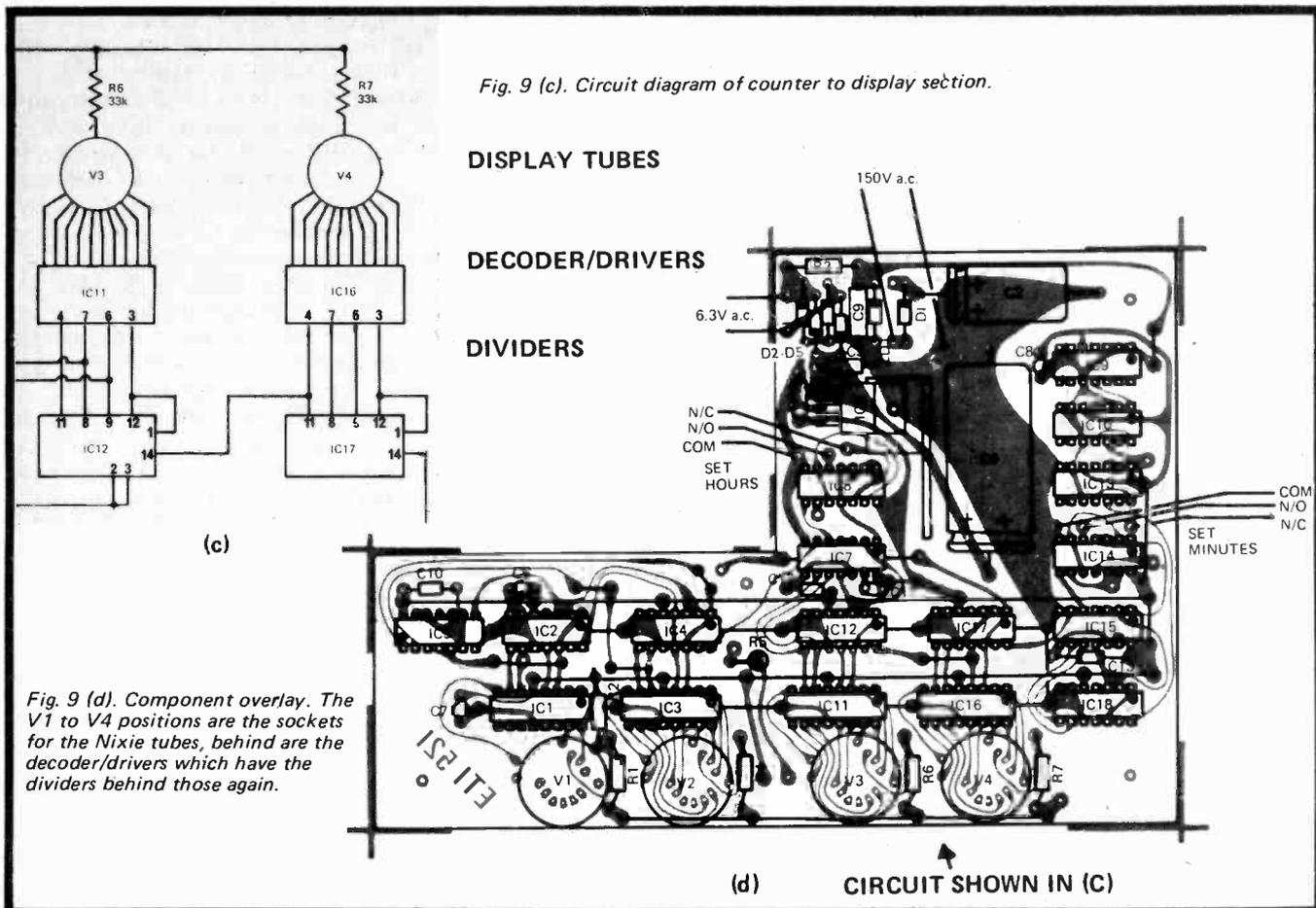

circuitry is required to energise just one of the total available in a multi-digit display in order to present the correct decimal number. The simplest arrangement is when the range switch of, say, a multi-range digital voltmeter decides the point to

use. In autoranging voltmeters (etc) and in many calculators, solid-state switching is used to select the correct point position.
Further Reading:
 "Solid State Alphanumeric Display Decoder/Driver Circuitry" — Hewlett

Packard application note 931 gives details of scanning methods used with 7 x 5 displays.
 "Mullard TTL Integrated Circuits — Applications" includes a chapter devoted to various kinds of code converter gating layouts.

ELECTRONICS TOMORROW

by John Miller-Kirkpatrick

WHAT A SCAMP!


National Semiconductors have been in the MPU market for some time with their PACE and IMP systems which are both designed for use in major computer sized machines. Now they have introduced SC/MP in the smaller MPU market, an 8 bit CPU in a single 40 pin package at a low price and with the usual NS technological back-up. SC/MP is intended for use in general-purpose applications where the cost per function is the most important factor as SC/MP is slower than the F8 and 6800 CPUs. For most applications the speed is not an important factor as the MPU is used to replace TTL type logic circuitry which would be too complex to build or require too much power for the required function. SC/MP includes a variety of useful functions that are not even provided by other MPU systems, like self-contained timing circuitry, 16 bit (65K) addressing capability, serial or parallel data transfer and common memory/peripheral instructions. These built-in features are combined with the low unit-cost make SC/MP the ideal answer to many applications which could not previously have been considered.

All input and output pins are TTL compatible and are also TRI-STATE which means that in addition to logic '0' and Logic '1' there is a third state of the outputs where the output will follow the status of any other TRI-STATE output connected in parallel with the first without damage to either output driver. This is similar to Wire ORing TTL outputs using the open collector gates except that in the latter a logic '1' on either (or any) parallel output will produce a logic '1' on the wire ORed line, with the TRI-STATE outputs the output is in a high impedance state until it is enabled thus one may choose logically which of the par-

alleled outputs is to be enabled and put data onto the common bus.

IN-OUT or IN-OUT

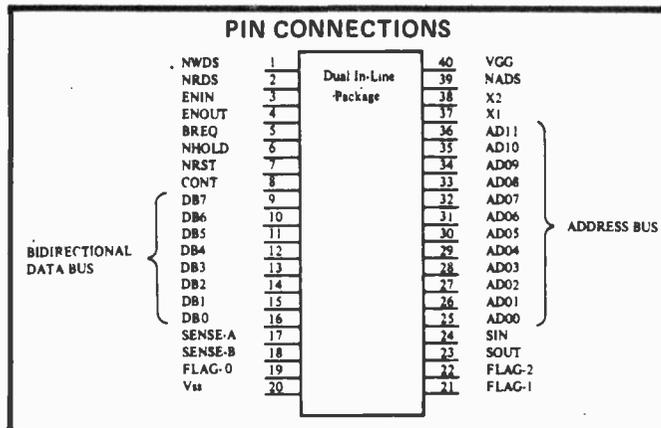The 40 pin pin-out of the SC/MP CPU chip is shown as fig 1. The functions of these pins working from pin 1 are as follows.



NWDS is an output to indicate to peripherals that CPU data is now valid, ie WRITE.

NRDS is an input which allows data from the data bus into the CPU, ie READ.

ENIN, ENOUT, BREQ are controls used in multiple CPU systems to denote which CPU chip has access to the address and data busses.

NHOLD this input causes the I/O address and data busses to lock in their present state until NHOLD input goes high, this can be used for slow I/O devices such as humans.

NRST reset input, when this is set low or on CPU power-on the internal registers are all initialised and the program pointer points at location Hex 0001.

CONT this input is similar to NHOLD except that the CPU is halted before fetching the next instruction whereas NHOLD stops it

halfway through an instruction. DB 0-7 Parallel I/O bus to/from ROMs, RAMS, I/O units, etc.

SENSE-A this is an external interrupt signal which can be sampled by the CPU or can be used to cause immediate transfer to an interrupt program, and is usually used by I/O devices to indicate that they wish to access the CPU.

SENSE-B this input is similar to SENSE-A except that it will not cause immediate transfer to another program as it has to be sampled by the CPU program. It could be used with SENSE-A to indicate a particular type of interrupt.

FLAG 0-2 These are output indicators to indicate to other units user designated states of the CPU or other peripherals. For instance they could be used as acknowledgment indicators in peripheral handshake routines to indicate to the peripheral that its interrupt request has been noticed by the CPU.

SIN, SOUT are serial I/O pins. An

instruction will cause a data bit at SIN to be transferred to an internal register or from the register to SOUT, this is used for example in teletype I/O or other VDU, CASSETTE, or KEYBD I/O routines.

ADA0-11 This is a 12 bit address bus which can directly access any location within a 4K 'page' it can be used in conjunction with the data bus to access any location within the 65K maximum for the CPU.

X1-X2 These are the timing pins which can have a 1MHz crystal on a 500pF capacitor connected across them, the crystal is only used where accuracy of instruction times is required, ie if an accurate DELAY is required.

NADS This is one of the most important pins on the whole device, its basic function is to denote to any I/O or memory unit that a valid address is available on

the address bus. If it is used to latch the data bus as well then the data bus has non-data information on it at NADS time.

This information is a four bit 'page' number to denote which of the 16 possible 4K pages is required (in a basic 4K system this address will always be 0000 and thus need not be latched). The other four bits of the data bus at NADS time shows the status of four flags R-FLAG shows whether input or output is to take place, I-FLAG shows whether data or instruction is being accessed, D-FLAG shows that a DELAY in in operation and H-FLAG can be used with the CONT input to enable a pro-

grammed halt.
Vss-VG Nominal 12 volt supply.

WE HAVE 'LIFT-OFF'

Perhaps your car is not quite capable of 'lift-off' but it may well have ignition problems, so why not solve the problems with SC/MP? Fig 2 shows a very complex and relatively expensive application for SC/MP which may find application in racing engines fitted to cars, boats, planes, etc. An analogue multiplexer samples various signals from transducers in significant parts of the engine and passes these to the CPU via an A/D converter. The selection of transducer input and output

selection is done via a latch connected to the data bus. The system may well be expensive as a straightforward electronic ignition system but remember that with all that information available to it the CPU would also be able to give outputs of RPM, MPG, general engine efficiency, etc., and still have enough time and core to control lights, heating, warning lamps, etc. In fact a car built around a SC/MP might be a very interesting proposition.

At a recent exhibition NS had a Scalextric racing car set run from a microprocessor which was not a SC/MP but could well have been according to NS engineers. The idea was for one car controlled by a human to race against another car controlled by the MPU, similarly one can imagine a very complex train layout being controlled by a SC/MP system—in its spare time of course after looking after the rest of the household heating and cooking and helping junior with his homework. Anybody got a nice N gauge layout they want to sell?

Price of the SC/MP CPU chip is only £12.50; an evaluation kit at £50 and a pseudo-TTY kit also at about £50. Available from NS distributors or Bywood starting July/August.

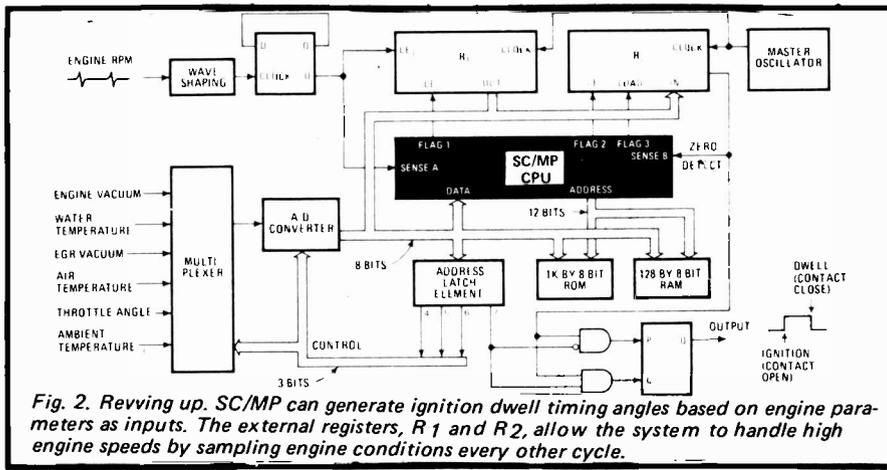


Fig. 2. Revving up. SC/MP can generate ignition dwell timing angles based on engine parameters as inputs. The external registers, R1 and R2, allow the system to handle high engine speeds by sampling engine conditions every other cycle.

LYNX ELECTRONICS (LONDON) LTD

Transistors	BC183 10p*	BF337 32p	CRS1-10 25p	2N697 12p
AC126 15p	BC183L 10p*	BFW60 17p*	CRS1-20 35p	2N706 10p
AC127 16p	BC184 11p*	BFX29 26p	CRS1-40 40p	2N929 14p
AC128 13p	BC184L 11p*	BFX30 30p	CRS1-60 65p	2N930 14p
AC128K 25p	BC207B 12p*	BFX84 23p	CRS3-05 34p	2N1131 15p
AC141 18p	BC212 11p*	BFX85 25p	CRS3-10 45p	2N1132 16p
AC141K 28p	BC212L 11p*	BFX88 20p	CRS3-20 50p	2N1304 20p
AC142 18p	BC213 12p*	BFY50 20p	CRS3-40 60p	2N1305 20p
AC142K 28p	BC213L 12p*	BFY51 18p*	CRS3-60 85p	2N1711 18p
AC176 16p	BC214 14p*	BFY52 19p	MJ480 80p	2N2102 44p
AC176K 25p	BC214L 14p*	BFY64 35p	MJ481 £1.05	2N2368 14p
AC187 18p	BC237 16p*	BFY90 65p	MJ490 90p	2N2484 16p
AC187K 25p	BC238 16p*	BR100 20p	MJ491 £1.15	2N2646 50p
AC188 18p	BC300 34p	BRV39 40p	MJE340 40p*	2N2905 18p
AC188K 25p	BC301 32p	BSX19 18p	MJE371 60p	2N2905A 22p
AD140 50p	BC323 80p	BSX20 18p	MJE520 45p	2N2926R 10p*
AD142 50p	BC327 18p*	BSX21 20p	MJE521 55p	2N29260 9p*
AD143 46p	BC328 16p*	BSY95A 12p	OAS 50p*	2N2926Y 9p*
AD149 45p	BC337 17p*	BT106 £1.00	OAS9 8p	2N2926G 10p*
AD161 35p	BC338 17p*	BT107 £1.60	OAB1 8p	2N3053 15p
AD162 35p	BCY70 12p	BT108 £1.60	OC41 15p	2N3054 40p
AL102 95p	BCY71 18p	BT109 £1.00	OC42 15p	2N3055 50p
AL103 93p	BCY72 12p	BT116 £1.00	OC44 12p	2N3440 56p
AF114 20p	BD115 55p	BU105 £1.80*	OC45 10p	2N3442 £1.20
AF115 20p	BD131 36p	BU105/02 £1.90*	OC71 10p	2N3570 80p
AF116 20p	BD132 40p	BU126 £1.60*	OC72 22p	2N3702 10p*
AF117 20p	BD135 36p	BY206 15p*	OC84 14p	2N3703 10p*
AF118 50p	BD136 39p	BY207 20p*	SC40A 73p	2N3704 10p*
AF139 33p	BD137 40p	BYX36-300 12p*	SC40B 81p	2N3705 10p*
AF239 37p	BD138 48p	BYX36-600 12p*	SC40D 98p	2N3706 10p*
BC107 14p	BD139 8p	BYX36-900 15p*	SC40F 65p	2N3707 10p*
BC107B 16p	BD181 88p	BYX36-1200 18p*	SC41A 65p	2N3714 £1.05
BC108 13p	BD182 92p	BYX36-1200 21p*	SC41B 70p	2N3715 £1.15
BC109 14p	BD183 97p	BYX38-300 20p	SC41D 85p	2N3716 £1.25
BC109C 16p	BD232 60p*	BYX38-600 20p	SC41F 85p	2N3717 £1.60
BC117 19p*	BD233 48p*	BYX38-900 20p	ST2 20p	2N3772 £1.60
BC125 18p*	BD237 55p*	BYX38-1200 20p	TIP29A 44p	2N3773 £2.10
BC126 20p*	BD238 60p*	BYX38-300 50p	TIP30A 52p	2N3819 28p*
BC141 28p	BD184 £1.20	BYX38-600 50p	TIP31A 54p	2N3904 16p*
BC142 23p	BDY20 80p	BYX38-900 50p	TIP32A 64p	2N3906 16p*
BC144 23p	BDY38 60p	BYX38-1200 60p	TIP34 £1.05	2N4124 14p*
BC147 9p*	BDY60 68p	BYX38-300 60p	TIP41A 68p	2N4290 12p*
BC147 9p*	BDY61 65p	BYX38-600 60p	TIP42A 72p	2N4348 £1.20
BC148 9p*	BDY62 55p	BYX38-900 60p	IN2069 14p*	2N4870 35p*
BC149 9p*	BF178 28p	BYX38-1200 65p	IN2070 16p*	2N4919 70p*
BC152 25p*	BF179 38p	BZX61 series zeners 20p	IN4001 4p*	2N4922 50p*
BC153 18p*	BF194 10p*	BZX83 or zeners 11p*	IN4002 5p*	2N4923 64p*
BC157 9p*	BF195 10p*	C106A 40p	IN4003 6p*	2N5060 20p*
BC158 9p*	BF196 12p*	C106B 45p	IN4004 7p*	2N5061 25p*
BC159 9p*	BF197 12p*	C106D 50p	IN4005 9p*	2N5062 27p*
BC160 32p	BF224J 18p*	C106E 50p	IN4007 10p*	2N5064 30p*
BC161 38p	BF244 17p*	C106F 35p	2N696 14p	2N5496 65p
BC168B 9p*	BF257 30p	CRS1-05 25p		
BC182 11p*	BF258 35p			

DIGITAL DISPLAYS & LED'S

DL704 99p	DL747 1.75	2 RED LED ONLY	13p
DL707 99p	DL750 1.75	GREEN CLEAR	15p

THYRISTORS

	8A (TO92)	1A (TO5)	3A (C106 type)	6A (TO220)	8A (TO220)	10A (TO220)
50	20	25	35	41	42	47
100	25	25	40	47	48	54
200	27	35	45	58	60	68
400	30	40	50	67	68	88
600		65	70	1.09	1.19	1.26

TRIACS (PLASTIC TO-220 PKG, ISOLATED TAB)

	4A	6-5A	8-5A	10A	15A
	(a)	(b)	(a)	(b)	(a)
100 V	0.60	0.60	0.70	0.78	0.83
200 V	0.84	0.84	0.75	0.87	0.87
400 V	0.77	0.78	0.80	0.83	0.97
600 V	0.96	0.96	0.87	1.01	1.13
				1.26	1.42
				1.50	2.11
				2.17	

N.B. Triacs without internal trigger diac are priced under column (a). Triacs with internal trigger diac are priced under column (b). When ordering please indicate clearly the type required.

74 TTL mixed prices

	1-24	25-99	100+	1-24	25-99	100+	1-24	25-99	100+
7400	14p	12p	10p	7445	85p	71p	57p	7492	57p
7401	14p	12p	10p	7447	81p	75p	65p	7493	45p
7402	14p	12p	10p	7448	75p	62p	50p	7495	67p
7403	15p	12p	10p	7447A	95p	83p	67p	74100	£1.08
7404	16p	13p	11p	7470	30p	25p	20p	74107	35p
7405	16p	13p	11p	7472	25p	21p	17p	74121	34p
7406	16p	13p	11p	7473	30p	25p	20p	74122	47p
7407	16p	13p	11p	7474	32p	26p	21p	74141	78p
7408	16p	13p	11p	7475	47p	39p	31p	74145	68p
7409	16p	13p	11p	7476	32p	26p	21p	74154	£1.82
7410	16p	13p	11p	7477	32p	26p	21p	74174	£1.00
7411	16p	13p	11p	7478	75p	62p	50p	74180	£1.06
7412	16p	13p	11p	7485	£1.30	£1.09	87p	74181	£1.06
7413	16p	13p	11p	7486	32p	26p	21p	74181	£3.20
7414	16p	13p	11p	7489	£2.92	£2.80	£2.10	74192	£1.35
7415	16p	13p	11p	7490	49p	40p	32p	74193	£1.35
7416	16p	13p	11p	7491	85p	55p	45p	74196	£1.64

LINEAR IC'S

301A 8 pin DIL	35p	3900 14 pin DIL	70p	565 14 pin DIL	£2.00*
307	55p	709 8/14 pin DIL	35p	566 8 pin DIL	£1.50*
309K	1.60	741 8 pin DIL	28p	567 8 pin DIL	£2.00*
380 14 pin DIL	90p	748 8 pin DIL	38p		
381 14 pin DIL	1.60*	555.8 pin DIL	45	CA3046 14 pin DIL	50p

Matching charge 20p per pair. P & P 20p—Overseas 80p. CA3045 85p

NATIONAL CLOCK CHIPS

MM5314 (Basic clock chip giving 6 digit display)	£3.75	MM 5316 (Sophisticated device including alarm, similar to CT 7001)	£5.25
--	-------	--	-------

HIGHAM MEAD, CHESHAM, BUCKS. Tel. (02405) 75151
VAT—Please add 8% except items marked * which are 25%


tech-tips

VIRTUAL EARTH PREAMP

This circuit caters properly for both magnetic and ceramic pickup cartridges and features an auxiliary input with a flat response.

A 741 op amp is used in the inverting mode as a virtual earth amplifier. In order to maintain a reasonable closed loop gain the feedback is tapped from the junction of R7 and R8.

Advantage is taken of the low impedance summing point to directly connect the various inputs reducing the complexity of the switching arrangements. Of particular interest is the equalisation for ceramic cartridges employed. It is based on the charge amplifier principle. R6 in parallel with C5 introduces a -3dB cut at 40Hz and C1 performs the same cut at 40Hz and C1 performs the same function at the magnetic P.U. input.

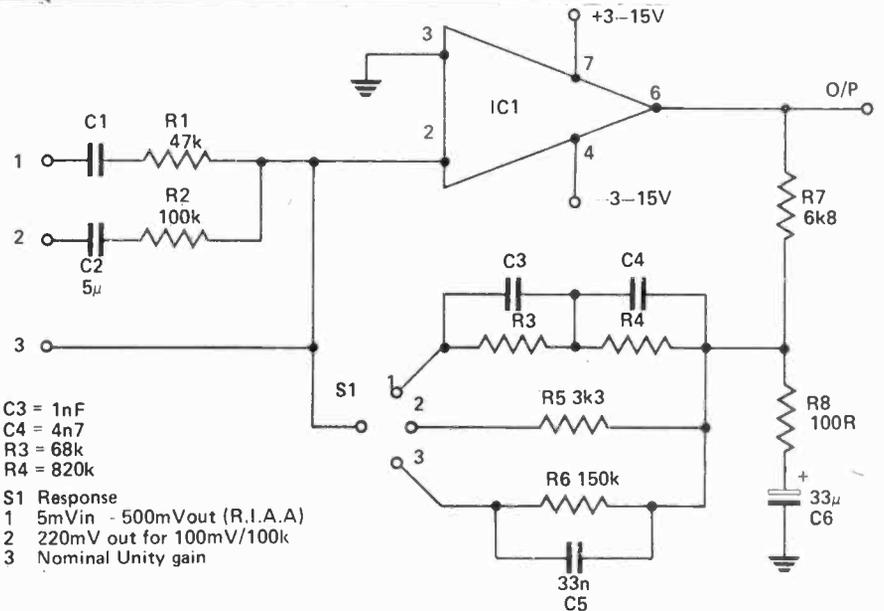

- C3 = 1nF
 C4 = 4n7
 R3 = 68k
 R4 = 820k
 S1 Response
 1 5mVin - 500mVout (R.I.A.A)
 2 220mV out for 100mV/100k
 3 Nominal Unity gain


C6 provides a further attenuation at this frequency providing, a steep cut rumble filter with a -6dB point at 40Hz.

NOVEL VOICE FADER

A cheap and effective alternative to cueing disco decks by PFL with headphones can be made by using LEDs to give a visual indication of the audio signal using this circuit.

R2 is used to ground the non-inverting input. The 1M pot and inverting input are used to ensure negligible output drain on the cartridge.

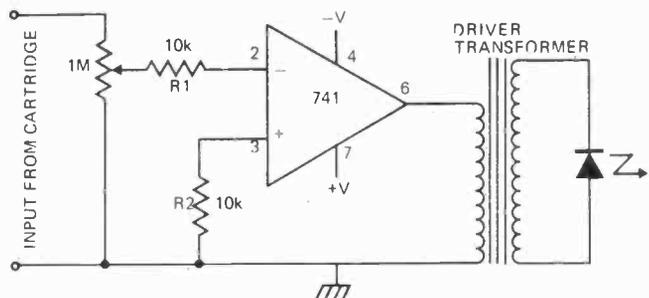The output of the 741 drives into the low impedance winding of an ordinary subminiature driver transformer. The secondary of this gives sufficient drive voltage to light the




LED.

As the current drain for the whole circuit is small it can be supplied either from the main dual-voltage supply lines of the existing equipment or

alternatively two PP3s. (Should last for several months).

The 1M pot is set to give no signal at the LED when the pick-up is on the lead-in track of the record.

SIMPLE ELECTRONIC LOCK

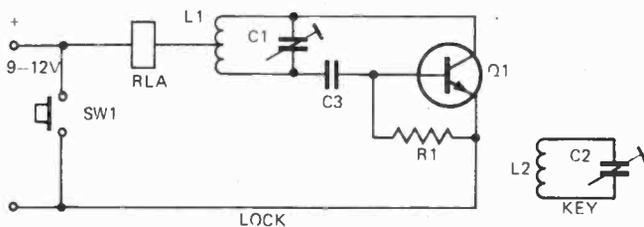

Operation is very simple, when the key is brought near the lock, providing L1-C1 have the same resonant frequency as L2-C2, the reed relay will open as the key absorbs energy from

the lock. After each operation of the lock, it should be reset by a short press on the reset button.

Setting up is best done with a resistor in place of the relay with a

voltmeter across it, making the operating range of the circuit more apparent.


- PARTS LIST**
 Q1 BC108
 C1/C2 250pF trimmers
 C3 1000pF ceramic
 L1/L2 80 turns 34swg on 3/8" diameter ferrite (L1 is tapped at 40 turns)
 R1 27k
 RLA Reed relay resistance around 5k
 SW1 Push-to-make switch
 P.S. Found that ETI's TIC-TAC radio could be used as key!

tech-tips

DUAL MODE AMP

This circuit was designed for use as the output of a relatively low accuracy (2%) Digital to Analog Converter (DAC). The DAC was required to have a bi-directional output, i.e. both positive and negative. It is quite expensive to provide this normally, so the simple invert/non invert amplifier was used.

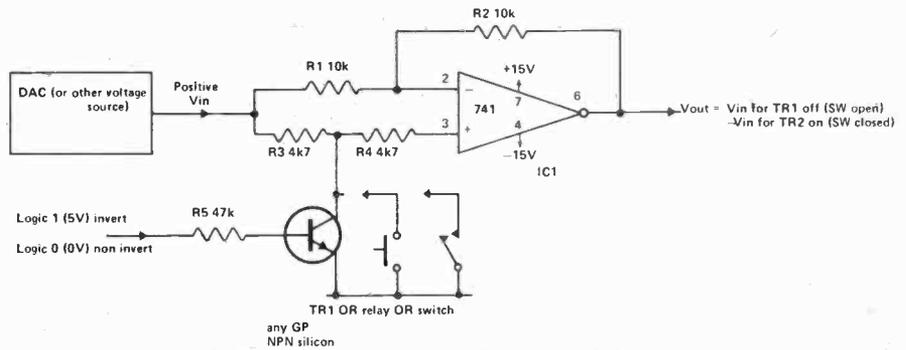With TR1 turned off the Operational Amplifier IC1 acts as a voltage follower because its inverting and non inverting inputs are at the same potential. In this sense the amplifier has unity gain and little offset. The only errors are caused by the amplifier offset (a few millivolts) which will appear at the output, and the voltage caused by the input currents flowing




through R1 and R3/4.

With TR1 turned on, the non-inverting input of the Op Amp is connected to 0V via R4, and the amplifier now behaves as a conventional unity gain inverting amplifier. The performance in this mode is not as good. The saturation voltage at TR2 collector

(typically 0.2V) will appear at the output subtracted from Vin. This limits the performance of the circuit to relatively low accuracy applications. It is possible to switch in a bias offset, but the complexity of this will usually be matched by having a bi-directional DAC.

FAST ACTING PSU PROTECTION

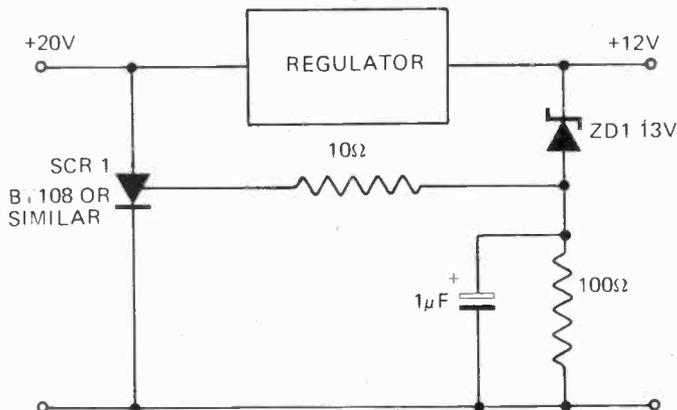

When using a regulated PSU to reduce a supply voltage there is always the

danger that component failure in the PSU might lead to a severe overvoltage

condition across the load. If the load is a circuit using ICs they can be permanently damaged under such conditions.


A fuse prevents excess current from flowing in a circuit but would generally be too slow to cope with over-voltage situations. The circuit shown is designed to protect the load under overvoltage conditions. Component values given are for a 20V supply with regulated output at 12V. The zener diode can be changed according to whatever voltage is to be the maximum.

If the voltage at the regulator output rises to 13V or above, the zener diode breaks down and triggers the thyristor which shorts out the supply line and blows the main fuse.

A TIMER WITH ZERO STANDBY CURRENT DRAIN

Most timer circuits draw current in both 'on' and 'off' states. For many applications this is no drawback, but for some purposes a timer is required which can remain in 'standby' indefinitely without drawing any supply current. The prototype is used with a toy siren similar to one in a previous "Tech-Tips" features, since young children delight in leaving such devices running indefinitely and a timed cut-out work wonders for parents' mental health! — but more practical uses would include delayed light switches for garages, communal areas in flats, etc, and 'sleep switches' to turn off radios used to lull one to sleep, where it could easily be built into the set.

In operation all transistors are 'off'

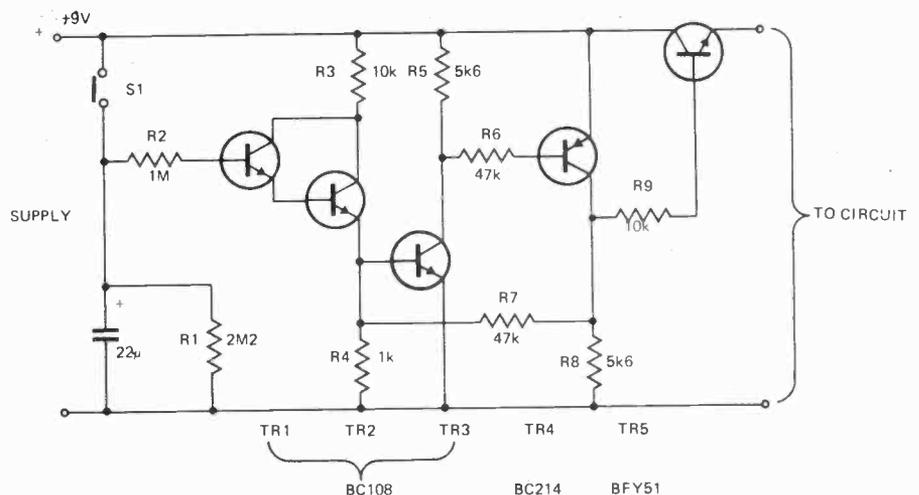

until push-switch S1 is operated momentarily, charging C1, after which

the darlington pair TR1 and TR2 start to conduct. A voltage then appears


across R4, and this used to operate the switch proper, TR3 and TR4. These two transistors are used in a positive feedback arrangement to give a sharp switching action as the voltage across C1 gradually falls below a threshold value. Some of the collector voltage from TR4 is fed back to TR3 base through R7 and helps hold it switched on; as TR3 starts to switch off so TR4 turns off and this holding current falls,

causing a sharp regenerative switching action to take place. TR5 is driven from TR4 collector and handles the supply current to the circuit being switched. R1 ensures C1 fully discharges since as long as any charge remains TR1 and TR2 continue to pass a small current (1mA).

The time depends on the value of C1 and R1, as shown around 2-3 minutes is obtained, but delays up to

½ hour or so should be easily obtainable with larger values of capacitor. Substituting a pot for R1 would provide some measure of control. C1 should for preference be a tantalum or low-leakage type. Almost any small silicon transistors should work, but germanium types are not recommended as their leakage currents might cause problems.


TWO TONE OSCILLATOR

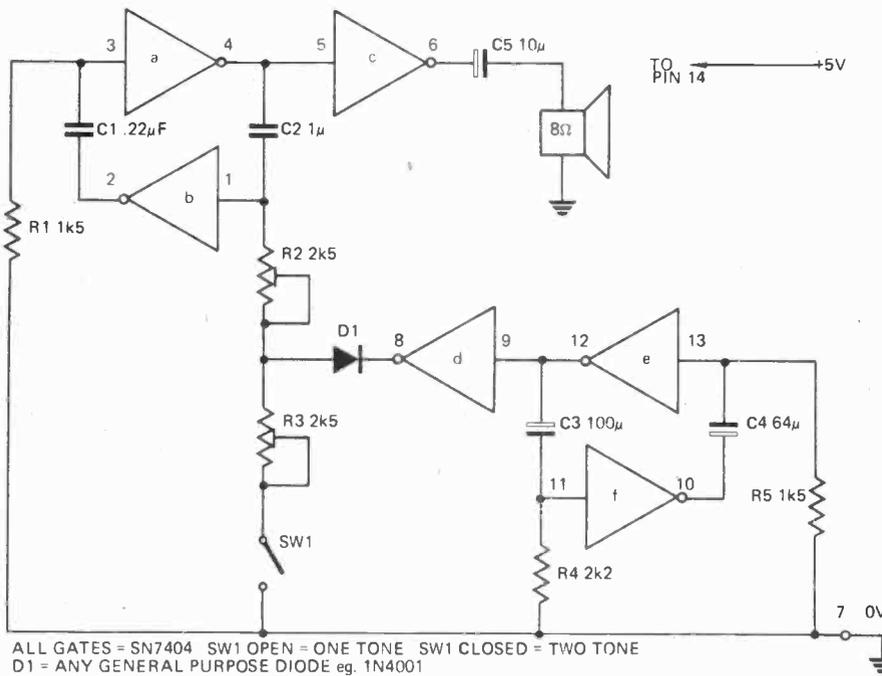

This simple circuit uses only 1 SN7404 IC and can either generate an altering two tone signal or a pulsed single tone, either of the two tones can be varied and the circuit will drive a loudspeaker or a crystal earpiece.

In the circuit gates 'A' and 'B' generate an AF signal, the frequency of which depends on the resistance of the two inputs to earth (Pins 1 and 3). Gates 'F' and 'E' switch at a lower frequency (typically .5Hz) and their o/p is fed to gate 'D'. Whenever pin 8 is at logic '0', D1 is forward biased and the effective resistance to earth from pin 1 is R2 plus the resistance of D1 and the inverter 'D'. Whenever pin 8 goes to logic '1', D1 is reverse biased and the effective resistance to earth from pin 1 changes to that of R2 + R3 therefore the AF output frequency changes, when the circuit is switching a high and low tone alternately, R2 sets the frequency of the high tone and R3 that of the low tone, when the circuit is giving a single frequency (i.e. SW1 open) then the o/p frequency is set by R2.

SEVEN SEGMENT TO DECIMAL CONVERTER

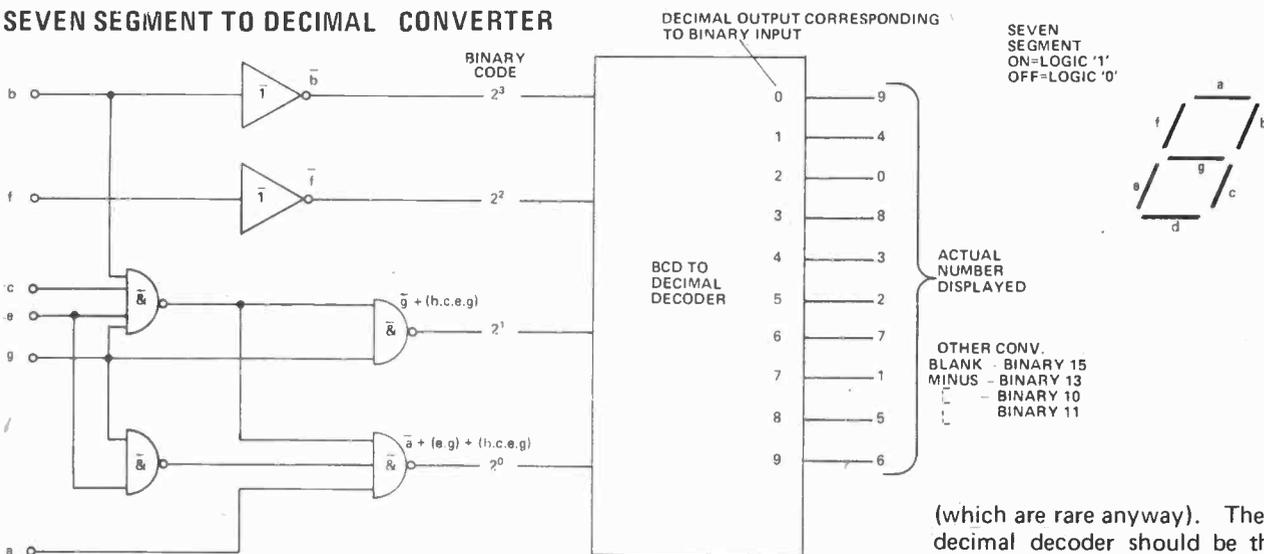

Note that the output from the gates is not 'straight' BCD so the outputs from the BCD to decimal decoder are

transposed. It will convert 6's and 9's with or without the top and bottom bars respectively but not 'hooked' 7's

(which are rare anyway). The BCD to decimal decoder should be the 'fully decoded' type with blanking for BCD inputs over 9 since a blank is encoded as binary 15, hence a 74141 instead of 7441. Some other conversions which result from this circuit are shown.

New Course in Digital Design


Understand the latest developments in calculators, computers, watches, telephones, television, automotive instrumentation

Each of the 6 volumes of this self-instruction course measures 11¼" x 8¼" and contains 60 pages packed with information, diagrams and questions designed to lead you step-by-step through number systems and Boolean algebra, to memories, counters and simple arithmetic circuits, and on to a complete understanding of the design and operation of calculators and computers.

After completing this course you will have broadened your career prospects and considerably increased your fundamental understanding of the changing technological world around you.

Design of Digital Systems
A Self-Instruction Course in 6 Volumes

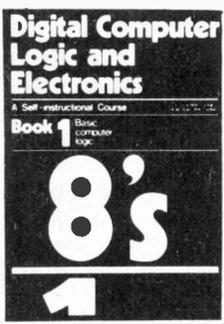- 1** Computer Arithmetic
- 2** Boolean Logic
- 3** Arithmetic Circuits
- 4** Memories & Counters
- 5** Calculator Design
- 6** Computer Architecture



Digital Computer Logic and Electronics
A Self-Instruction Course
Book 1 Basic Computer Logic

8's

£4.20 plus 80p p&p

Also available — a more elementary course assuming no prior knowledge except simple arithmetic.

In 4 volumes:

1. Basic Computer Logic
2. Logical Circuit Elements
3. Designing Circuits to Carry Out Logical Functions
4. Flip flops and Registers

Offer. Order this together with Design of Digital Systems for the bargain price of £9.70, plus 80p p&p.

Design of Digital Systems contains over twice as much information in each volume as the simpler course, Digital Computer Logic and Electronics. All the information in the simpler course is covered as part of the first volumes of Design of Digital Systems which, as you can see from its contents, also covers many more advanced topics.



£6.20

plus 80p packing and surface post anywhere in the world (VAT zero rated). Payments may be made in foreign currencies. Quantity discounts are available on request.

**Designer
Manager
Enthusiast
Scientist
Engineer
Student**

These courses were written so that you could teach yourself the theory and application of digital logic. Learning by self-instruction has the advantages of being quicker and more thorough than classroom learning. You work at your own speed and must respond by answering questions on each new piece of information before proceeding to the next.

Guarantee — no risk to you

If you are not entirely satisfied with Design of Digital Systems or Digital Computer Logic and Electronics, you may return them to us and your money will be refunded in full, no questions asked.

To: Cambridge Learning Enterprises, Dept. Dig., FREEPOST, St. Ives, Huntingdon, Cambs PE17 4BR

*Please send me set(s) of Design of Digital Systems at £7.00 each, p&p included

*or set(s) of Digital Computer Logic and Electronics at £5.00 each, p&p included

*or combined set(s) at £10.50 each, p&p included

Name.....

Address.....

.....

.....

*delete as applicable. ETI 8

No need to use a stamp—just print FREEPOST on the envelope.

For Toshiba say ERIE



For top quality, reliable transistors, FETs, diodes, LEDs (single and 7-segment), and ICs, choose Toshiba from ERIE. Here's a selection from the wide Toshiba range, with prices for quantities from 1 to 24 inclusive.

15% discount applies to all orders for quantities of 25 to 99. If you want 100 or more of any one item, special prices apply—send for price list direct from ERIE, or complete the reader service card.

Data sheets for devices ordered are supplied free on request, but if you want data sheets only, please send 10p for each set of device data, to cover costs.

P & P of 30p is applicable on all orders up to 100 devices (any mix of types).

VAT Please add 12½% for VAT to all prices, except those marked with an asterisk (*) which are rated at 8% VAT.

NEW SERIES! (TO-92)

Audio Amplifier Small Signal Transistor incorporating the Toshiba perfect crystal technology (P.C.T.) manufacturing process, giving excellent low noise characteristics.

	V _{CEO} (V)	I _C (mA)	P _C (mW)	h _{FE} max	Price Each
Audio Input BC451 NPN	50	100	300	800	11p
Audio Input BC452 NPN	30	100	300	800	11p
Low noise BC453 NPN	30	100	300	800	11p
Driver BC454 PNP	-50	-100	300	800	12p
Driver BC455 PNP	-30	-100	300	800	12p
Low noise BC456 PNP	-30	-100	300	800	12p
Low noise } 2SC1000 NPN	50	100	200	700	16p
Pre Amp. } 2SC1681 NPN	60	50	200	700	16p

Plastic Power (TO-126)

Audio Medium Power Amplifier Plastic Package also incorporating P.C.T.

	V _{CE} (V)	I _C (mA)	P _C (mW)	h _{FE} min	Price Each
Driver BD135 NPN	45	500	6.5W	250	33.5p
Driver BD136 PNP	-45	-500	6.5W	250	36.5p
Driver BD137 NPN	60	500	6.5W	250	36.5p
Driver BD138 PNP	-60	-500	6.5W	250	40p
Driver BD139 NPN	.80	500	6.5W	250	40p
Driver BD140 PNP	-80	-500	6.5W	250	44p

LED'S

ERIE's range of Toshiba Led's include:—

	V _R (V)	V _F (V)	I _R (mA)	I _F (mA)	P _D (mW)	I _v (mcd)	Price Each
Red Diffused Lens TLR102	4	2	.5	25	75	.1/5	21.5p
Red Clear Lens TLR103	4	2	.5	35	100	.5/3	21.5p
Red Diamond Lens TLR105	4	2	.5	35	100	.5/1.7	21.5p
Grn. Diffused Lens TLG102	4	2	.5	30	80	.05/1	35.5p
Grn. Clear Lens TLG103	4	2	.5	45	125	.3/3	35.5p
Grn. Diamond Lens TLG105	4	2	.5	45	125	.2/1.8	35.5p

NEW! (TO-3) Toshiba introduce the low priced S2530A/S2530 equivalent to the BUY69A/BUY69B.

	V _{CEO} (V)	I _C (A)	P _C (W)	h _{FE}	Price Each
*S2530 NPN	800	10	100	15	£3.22
*S2530A NPN	1000	10	100	15	£3.48

Also range of High Voltage/High Power Switching Transistor in the BU Series.

	V _{CEX} (V)	I _C (A)	P _C (W)	h _{FE} (min)	Price Each
BU 204	1500	2.5	10	2	£2.05
BU 205	1650	2.5	10	2	£2.05
BU 207	1550	5	12.5	2.25	£3.87
BU 208	1650	5	12.5	2.25	£3.45
BU 126	750	3	50	15	£2.37

Note: Ex stock Metal Power 2N3055 Audio Power Amplifier Transistor for immediate delivery price 86p. All TO-3 prices inc. H.W.

INTEGRATED CIRCUITS

Linear Power Amplifier TA 7205P	S1P 14F	PRICE £1.55
5.8W/13.2V/4 Ω		
TA 7093P 2W/24V/16 Ω	DIP 8F	PRICE £1.49
Four Channel Decoder TA 7117P	DIP 16P	PRICE £2.35

SEVEN SEGMENT

Common Cathode TLR 301 5.2 x 2.6mm character size, continuous current I_F/Segment 20mA, VR 3V, VF 2V, power dissipation 400mW. Total Luminous intensity 0.04/0.11 mcd PRICE £1.08

Common Cathode TLR 313 8.3 x 3.8mm character size, continuous current I_F/Segment 15mA, VR 3V, VF 2V power dissipation 350mW. Total luminous intensity 0.04/0.11 mcd PRICE £2.22

Common Anode TLR 315 same characteristics. PRICE £2.22

Common Cathode TLR 308 15 x 9mm character size, continuous current I_F/Segment 35mA, VR 3, VF 2V, power dissipation 750mW. Total luminous intensity 0.07/0.3 mcd PRICE £3.08

Common Anode TLR 306 same characteristics. PRICE £3.08

ERIE ELECTRONICS LIMITED

South Denes, Great Yarmouth, Norfolk.

Tel: 0493 56122 Telex: 97421

Components **TTT**

QUALITY WATCHES BY METAC

QUARTZ CRYSTAL

ELECTRONIC WATCH

The very latest in DIGITAL Time keeping The ultimate in accuracy

SEE OUR SPECIAL OFFER CENTRE PAGES



MODEL TLES

8 SEPARATE FUNCTIONS

SUPER COVER FULL 2 YEARS GUARANTEE CASH REFUND

1	12:00
2	12:30
3	:36
4	TU
5	TU 26

£21.95 + £1.80 VAT

18ct GOLD PLATED ADJUSTABLE BRACELET

6	MORNING A.M. INDICATOR
7	AFTERNOON P.M. INDICATOR
8	AUTOMATIC FADE OUT

SLIMLINE CASE

This new generation of advanced DIGITAL QUARTZ WATCHES has now been perfected to enable them to be made available to everyone. Science and space technology has produced integrated circuits containing thousands of transistors in a single package, there are no moving parts to oil or give mechanical trouble. You have our TWO YEAR GUARANTEE which enables you to wear your watch with CONFIDENCE.

LIQUID CRYSTAL CONTINUOUS DISPLAY WITH BACKLIGHT for night-time illumination

GREAT LCD VALUE

This impressive model incorporates the famous MICROMA MODULE thus ensuring reliability and long life. It really is good value (just look in the jewellery stores at similar models). Metac believes that finally the general public will find our continuous display watches preferable, they run for a year on a miniature battery and with the backlight facility the easy to read display is visible all the time. With METAC you can be assured of consistent after sales service for the life of this quality quartz watch.



MODEL TLC4

6 FUNCTIONS

SUPER COVER FULL 2 YEARS GUARANTEE CASH REFUND

1	12:0
2	12:30
3	:36
4	:16
5	2:36

BACK LIGHT

PM INDICATOR

£38.84

+ £3.11 VAT Gold plated Bracelet

SEE OUR SPECIAL OFFER CENTRE PAGES

£36.40

+ £2.91 VAT Stainless Steel Bracelet

SLIMLINE CASE

REMEMBER: with every WATCH you get METAC SUPER COVER

- ★ **DOUBLE GUARANTEE 2 FULL YEARS**
- ★ **REFUND** in full all money paid immediately upon request for a period of **7 DAYS** if not entirely satisfied with the product.
- ★ **REPLACE** or repair at our discretion any watch developing a fault for a period of **TWO YEARS** from date of purchase
- ★ **FREE** calibration check at end of 1st year; 2nd year and 3rd year, by fully trained technical staff
- ★ **FREE** advising service on all technical aspects of Electronic Timing to wearers of METAC watches

Mail order customers please add **58 pence** per order to cover postage and insurance

METAC INTERNATIONAL

CROSS LANE, BRAUNSTON, NORTHANTS

Tel. Rugby 890672

Please supply the following

Name

I enclose cheque

Address

postal order money order

I wish to pay by Barclaycard/Access and my number is

Signature

Don't forget the discount coupon

TELETYPE 35R0 ASC11 CODE HEAVY DUTY CONTINUOUS OPERATION

With 240 Volt Power Supply and Paper Feed. Circuits, Diagrams. Information supplied with all purchases.

A MUST AT £50 each

To all purchasers of the Teletype 35R0 a **REBUILDABLE Keyboard** can be purchased for **£10 only**
Attractive cast alloy front panel, vertical mount, size 16 1/2 x 15 x 5 1/2" containing **72 push buttons with manual or electrical reset (28V) with provision for labelling with your code; 65 illuminated symbols or functions (complete with 28V lamps) which again you can change; 15 bit front panel microswitch assembly to enable your coded cards to be read (sample supplied) and host of other electronic parts. Complete with circuit diagrams. LESS than 100 LEFT. £15 each.**

TRANSFORMERS — All 240V 50HZ inputs

Type A 17-0-17V 250 MA; 7.5-0-7.5V 250MA; 0-20V 5 Amps; 0-4V 5 Amps; 0-1-1.5V 5 Amps **£2 ea. P&P £1.25**
Type B 17-0-17V 250MA; 8-0-8V 250 MA; 0-12.5-13.5V 5 Amps; 0-1.5-2V 5 Amps; **£1.50 ea. P&P £1**
Type C 19-0-19V 250MA; 8-0-8V 250MA; 0-7.5V 5 Amps; 0-1.4V 5 Amps; **£1.25 ea. P&P £1.25**
Type D 34V 4 Amps; 19V 4 Amps; 17V 4 Amps; **£3 ea. P&P £1.25**
Type E 3V 1 Amp. **25p ea. P&P 50p**
Type F 17V 1 Amp. **85p ea. P&P 50p**
Type G 20-0-20V 200 MA; 0-6V 100MA. **75p ea. P&P 75p**. Atlantic series.
All Brand New. (APT surplus types A, B, C & D; Honeywell surplus type E; Recordacall surplus type F; Parmeko Atlantic series type G).

SEMICONDUCTORS — All at 8p ea*

P&P extra. Guaranteed all full spec. devices. Manufacturer's markings:
BC147 BC158. 2N3707. BC107 BF197; BC327. 2N4403. BC172B BC261B. BC251B; BC348B. BC171A/B.
2N3055 RCA **50p ea. P&P 8p**.
2N5879 with 2N5881 Motorola 150 Watt. Comp. pair **£2 pr. pair. P&P 15p**.
*Linear amp 709 **25p ea. P&P 8p**

VARIACS 240V input 0-270V output.
8 Amp **£18 ea.** 20 Amp **£30 ea.** Carr. extra.

BNC Plug to BNC Plug lead. Assembled ready to use **75p ea. P&P 20p**.
Ex-eq. BNC Socket **15p**. BNC Plug **20p**. **BNC Plug & Socket 30p pair.** P&P 15p.

*TELEPHONES

Post Office Style 746. Black or two-tone grey **£6.50 ea.**
Modern Style 706 Black or two-tone grey **£4.50 ea.**
Modern Standard Style in grey or black with a place to put your fingers like the 746, **£3 ea.** As above but discoloured grey only **£2 ea.** All telephones complete with standard dial and bells. P&P all styles 75p ea. Handsets, complete with 2 inserts and lead **£1.75 ea. P&P 65p**

NEW — UPGRADED CONTENTS — FOR LESS MONEY

*3lb Electronic Goodies **£1.60** post paid
*High Value Printed Board Pack — hundred of components, transistors, etc. — no flat to the board transistors **£1.65** post paid.

MUFFIN Fans. 115 Volt. Size 5 x 5 x 1 1/2". Superbly quiet and reliable. Ex-eq. but tested. **£1.50 ea. P&P 75p**

IBM CLOCKS — SLAVES. 11 1/2". **£3 ea. P&P £1**. 17 1/2" **£5 ea.**, Plus Carr. 23 1/2" **£7 ea.**, Plus Carr., ITR CLOCKS—SLAVES 7 1/2" **£5 ea. P&P 75p**.

*Meter PACKS — 3 different meters **£2, P&P £1**.

DON'T FORGET YOUR MANUALS. S.A.E. with requirements.

GRATICULES 12 x 14 cm high quality plastic **15p ea. P&P 10p**

*CAPACITOR PACK, 50 Brand New components, only **50p**. P&P 48p.

*TRIMMER PACK. All Brand New. 2 Twin 50/200pf ceramic, 2 Twin 10/60pf ceramic, 2 min. strips with 4 preset 5/20pf on each; 3 air spaced preset 30/100pf on ceramic base **25p the lot, P&P 15p**.

RESETTABLE COUNTERS, 4 digit by Stonebridge / Sodeco 1000ohm coil **£2 ea. P&P 35p**.

LATEST MINISTRY RELEASE

AVO SIGNAL GENERATOR CT378 AM Modulation. Freq. range 2 to 220 MHZ. 240V operation. Compact unit. Size approx. 15" wide x 10" high x 6" deep.

AVO VALVE TESTER CT160. "The Suitcase." Open and use.

SOLARTRON OSCILLOSCOPE TYPE CT316. DC-6MHZ. Size 8 1/2" x 11" x 20". With Circuit diagram.

DUE TO LARGE PURCHASES THESE 3 ITEMS ARE OFFERED AT THE VERY SPECIAL PRICE OF

£22.50 EACH

ALL TESTED AND WORKING

ONLY £10 EACH

Stabilised Power Supply. 240V 50HZ Input. Outputs —15V @ 10A; +15V @ 4A; —4.5V @ 12A; —21.5 @ 15A. Size 16 x 20 x 9". Auto overload trips on each voltage rail with pushbutton resets. MANY OTHER POWER SUPPLIES — Call and see.

*POT PACK. All Brand New Modern. Single and Ganged, our choice. **7 for 25p. P&P 48p**.

TUBES — All Brand New. Boxed. Electrostatic Deflection.
Type 408A 1 1/2" dia., 7 1/2" long. Blue Trace **£2.50 ea. P&P 75p**.
Type CV1526 (3EG1) 3" dia. **£4 ea. P&P £1**.

Type DB7/36 3" dia. (Replacement for Teletype S31) **£15 ea. P&P £1.50**.

Type 5BVP1 5" dia. PDA. X, Y Low Capacitance Side Pins. Green Trace **£5 ea. P&P £1.50**.

Type GEC 924F 3 1/2" dia. (Replacement for Teletype D33 & Solartron 1016 scopes) **£30 ea. P&P £1.50**.

Type GEC 924E 3 1/2" dia. (Replacement for Solartron 1015 scope) **£20 ea. P&P £1.50**.

Magnetic Deflection **12DP7 12" round. Blue with yellow afterglow. £1 ea.**

And for the VDU BUILDERS: M38-111GH Rectangular 30 x 20cm. Green Trace. Superb value **£12 ea.**

or Economy type CME1220 24 x 18cm. White Trace. **£9 ea.**

CRYSTALS. High quality B7G. etc. 2MHZ **£2.00 ea.**
1MHZ **£2.75 ea.**
100KHZ **£2.50 ea.**
50KHZ **£3 ea.**
20KHZ **£4.50 ea.**
P&P all 50p
*4.43MHZ CB Crystal at **25p ea. P&P 15p**.

*SPECIAL OFFER
Guaranteed full spec. devices. Manufacturers markings.
BC 204 & BC 207A **4p each. P&P extra**.

VERY SPECIAL PRICES

*1000F Feed thru Capacitors **10 for 30p. P&P 15p**.

*BEEHIVE TRIMMERS 3/30pf. BRAND NEW.
10 Off **40p**, P&P 15p; 100 off **£3.50**, P&P 75p; 500 off **£15**, P&P £1.25; 1,000 off **£25**, P&P £1.50.

HIVAC Miniature NEONS
App. 60V. Brand New. 10 off **20p**. P&P extra.

LARGE RANGE ELECTROSTATIC VOLTMETERS. from 0-300V 2" **£3**; to 250KV Max.
General guide 5KV 3 1/2" **£5**; thereafter **£1 per KV**. P&P 75p.

SERVOMEX MAINS VOLTAGE STABILISERS
AC2 — 9 amps. **£15 each**.
AC7 — 20 amps. **£35 each**.

MARCONI TF1101 Audio Oscillator. 20c/s to 200kc/s. Low distortion. 60db step attenuator. **£65 each**.

SOLARTRON VF252 AC Millivoltmeter. 1.5mv Full scale to 150V full scale in 10 ranges. Accuracy to within ±1%. 6" meter scale. Also calibrated in db's. Exceptional condition **£35 each**.

*POTENTIOMETERS — All **5p each**. P&P extra. Metal bodied AB Linear. PCB mount. Brand new. 10K single; 100K Ganged, 250K Ganged, 100K Ganged concentric shafts.

FIBREGLASS BOARD PACK. More board — less money. Larger pieces. Not less than 2.5 sq. ft. for **95p**, P&P 65p.
Double or single sided cut to any size. New Lower Price **1p per sq. in.** P&P extra.

RELAYS VP4 & similar style. P&P **15p ea.**
Siemens 5 8K 4 pole c/o **20p ea.**
ITT 52 ohm 5 pole c/o **60p ea.**
Inquiries for other values, prices, etc.

20HZ to 200KHZ

SINE AND SQUARE WAVE GENERATOR

In four ranges. Wien bridge oscillator thermistor stabilised. Separate independent sine and square wave amplitude controls, 3V max sine, 6V max square outputs. Completely assembled P.C. Board, ready to use. 9 to 12V supply required. **£8.85 each. P&P 35p**. Sine Wave only **£6.85 each. P&P 35p**.

WIDE RANGE WOBBLATOR

5MHZ to 150MHZ (useful harmonics up to 1.5GHZ) up to 15MHZ sweep width. Only 3 controls preset RF level sweep width and frequency. Ideal for 10.7 or TV IF alignment filters, receivers. Can be used with any general purpose scope. Full instructions supplied. Connect 6.3V AC and use within minutes of receiving. All this for only **£6.75**. P&P 35p (Not case, not calibrated).

Minimum Mail Order £2. Excess postage refunded

Unless stated — please add **£2.50 carriage to all units**

VALUE ADDED TAX not included in prices — Goods marked with * 12 1/2 % VAT, otherwise 8% Official Orders Welcomed. Gov./Educational Depts., Authorities, etc., otherwise Cash with Order

Open 9 a.m. to 5.30 p.m., Mon. to Sat.



CHILTMHEAD LTD



7/9 ARTHUR ROAD, READING, BERKS. (rear Tech. College, King's Road). Tel. Reading 582605

MINI-ADS

FOR DETAILS ON ADVERTISING IN
MINIADS, OR ELSEWHERE IN ETI,
CONTACT BOB EVANS, 01-730 8282

PRECISION POLYCARBONATE CAPACITORS

440V *All High Stability — Extremely Low Leakage

RANGE DIMENSIONS

VALUE (uF)	L (mm)	D (mm)	PRICE EACH	63V Range	1% ±	2% ±	5% ±
0.1uF	27	12.7	88p	0.47uF	£1.32	77p	51p
0.22uF	33	16	88p	1.0uF	£1.56	91p	60p
0.25uF	33	16	92p	2.2uF	£1.98	£1.32	75p
0.47uF	33	19	1.10	4.7uF	£2.82	£1.88	£1.23
0.5uF	33	19	1.16	6.8uF	£3.48	£2.32	£1.47
0.68uF	50.8	19	1.25	10uF	£4.98	£3.32	£2.01
1.0uF	50.8	19	£1.37	15uF	£7.14	£4.76	£2.88
2.0uF	50.8	25.4	£1.95	22uF	£9.66	£6.44	£3.90

*TANTALUM BEAD CAPACITORS — Values available: 0.1, 0.22, 0.47, 1.0, 2.2, 4.8, 6uF at 15V/25V or 35V; 10uF at 16V/20V or 25V; 22.0uF at 6V or 16V; 33.0uF at 6V or 10V; 47.0uF at 3V or 6V; 100.0uF at 3V. ALL at 12p each. 10p for £1.10, 50p for £5.00

TRANSISTOR & IC's

AC128	14p	*BC268A	10p	OC71	20p
AC176	16p	*BC547/558A	12p	*2N2926G	12p
AD149	40p	*BCY72	15p	*2N2926B	11p
AF238	40p	BD131/132	38p	*2N2929V	11p
BC107/8/9	38p	BF115/167	22p	2N3054	50p
*BC114	9p	BF173	24p	*2N3055	50p
*BC147/8/9	10p	BF178	28p	*2N3702	28p
*BC153	16p	BF184	22p	3704	11p
*BC157/8/9	12p	*BF194/195*	12p	TIP30A	52p
BC177	18p	*BF196/197*	13p	TIP31A	55p
*BC182/182L	11p	BF200	27p	TIP32A	64p
*BC183/183L	11p	*BF262/263*	60p	TIP35A	65p
*BC184/184L	12p	BFY50/51/52	20p	*MPL101	48p
*BC212/212L	12p	BFX84/86/88	20p	*NE555	81p
*BC213/213L	11p	BFX85	25p	*741C	32p
*BC214/214L	11p	BR101	41p	ZN414	£1.15
BC267	12p	GET872	25p	SN76013ND	£1.50
		OC44/OC45	20p		

POPULAR DIODES—1N914 6p, 8 for 45p, 18 for 90p; 1N916 8p, 6 for 45p, 14 for 90p; 1S44 5p, 11 for 50p, 28 for £1.00; 1N4148 5p, 6 for 27p, 12 for 48p; 1N4001 8p, 002 8p, 002 8p, 004 7p, 006 8p, 007 8p.
LOW PRICE ZENER DIODES—400mV, Tol. ±5% at 5mA. Values available: 3V, 3.3V, 3.6V, 4.7V, 5.1V, 5.6V, 6.2V, 6.8V, 7.5V, 8.2V, 9.1V, 10V, 11V, 12V, 13V, 13.5V, 15V, 16V, 18V, 20V, 22V, 24V, 27V, 30V. All at 7p each; 5 for 35p; 10 for 65p. SPECIAL OFFER: 100 Zeners for £8.00.

*RESISTORS—High stability, low noise carbon film 5%, 1/4W at 40°C, 1/4W at 70°C. E12 series only—from 2.2Ω to 2.2MΩ. ALL at 1p each, 8p for 10 of any one value, 70p for 100 of any one value. SPECIAL PACK, 10 of each value 2.2Ω to 2.2MΩ (730 resistors) £5.
SILICON PLASTIC RECTIFIERS—1.5 amp. brand new wire ended DO27, 100 P.I.V. 7p (4 for 28p), 400 P.I.V. 8p (4 for 30p).
BRIDGE RECTIFIERS—2½ amp, 200V 40p, 350V 45p, 600V 55p.
*SUBMINIATURE VERTICAL PRESETS—0.1W only. ALL at 5p each: 50Ω, 100Ω, 220Ω, 470Ω, 680Ω, 1kΩ, 2.2kΩ, 4.7kΩ, 6.8kΩ, 10kΩ, 15kΩ, 22kΩ, 47kΩ, 68kΩ, 100kΩ, 250kΩ, 680kΩ, 1MΩ, 2.5MΩ, 5MΩ.
PLEASE ADD 20p POST AND PACKING ON ALL ORDERS. ALL EXPORT ORDERS PLEASE ADD COST OF SEA/AIR MAIL.
PLEASE ADD 8p VAT to all items except those marked with *

Send S.A.E. for lists of additional ex-stock items. Wholesale price lists available to bona fide companies.

MARCO TRADING

(Dept. P3)
The Old School, Edstaston, Wem, Shropshire
Tel. Whixall (Shropshire) (STD 094872) 464/5
(Proprs. Minicost Trading Ltd.)

VALVES

Radio-TV Industrial Transmitting
2200 Types, 1930 to 1975 many obsolete. List 20p. S.A.E. for quotation. Postal export service. We wish to purchase all types of new and boxed valves. Wholesaler's Dealer's, etc., stocks purchased.

COX RADIO (SUSSEX) LTD., The Parade, East Wittering, Sussex, West Wittering 2923

FIBREGLASS P.C.B.s ex STOCK

Waa Waa Unit	ETI 455	Jun 76	240p
Touch Switch	ETI 539	May 76	75p
Temperature Generator	ETI 708		65p
Temperature Meter	ETI 130		50p
Audio Level Meter	ETI 438	Mar 76	100p
100w Guitar Amp	ETI 413	Top Pr1	140p
Digital Voltmeter (2pcb's)	ETI 117	Top Pr3	105p
Digital Display	ETI 533		110p
Int 25 Stereo Amp	ETI Int25		375p
50+50 Power Module	ETI 422	Jan 76	270p
Logic Tester	ETI 122		160p
Active Crossover 2 way	ETI 433A	Dec 75	90p
3 way	ETI 433B		90p
Bass Booster	ETI 018	Top Pr3	210p

PLUS most other E.T.I. Published projects.

Resistors HS Carbon Film 1/4 W 5% E12 Series 1p
Mixed Values. 50 45p 100 80p

Tantalum Bead Caps 2.2 uF & 47 uF only 7p
Electrolytics 10uF, 12v, 10, 25, 50, 330uF, 25v. 6p

This Months SNIPS!

CA 3046 Transistor Array 40p
TTL 7400 Series New Full Spec Devices 10 our mix 85p
Toggle Switches by Arrow DPST 240V 3a 17p
Slide Switches SPST 240V 3a 8p
Miniature Glass Reed Switches 10 for 50p

All prices include V.A.T. Please add 20p P & P
RFEQUIPMENT SPARES Ltd
3, Lucy Close, WIMBORNE, Dorset

GLASS FIBRE P.C.B.'s

Send 1:1 master and 7p per square inch tinned or 10p per square inch drilled and tinned PLUS 40p per board. Discount for quantity.

E.T.I. boards glass fibre drilled and tinned.

100W guitar amplifier E.T.I. 413 £1.40
Mixer pre amplifier E.T.I. 419 60p
Audiq 1 level meter E.T.I. 438 75p
G.P. Power Supply ETI 131 96p
Sweet Sixteen Amp ETI 457 £1.92

PROTO DESIGN

4 Highcliffe Way, Wickford, Essex
SS11 8LA

CMOS with discounts! (Any mix. disc. 10% 25+ 25% 100+)

4000/14000	0.15	4030/14507	0.45	4057/-	20.35
4001/14001	0.15	4031/-	1.80	4059/-	3.60
4002/14002	0.15	4032/14032	0.50	4060/-	0.90
4006/14006	0.95	4033/-	1.10	4061/-	16.40
4007/14007	0.15	4034/14034	1.55	4062/-	7.30
4008/14008	0.75	4035/14035	0.95	4063/-	0.90
4009/14009	0.45	4036/-	1.80	4066/14066	0.55
4010/14010	0.45	4037/-	0.75	4067/-	2.95
4011/14011	0.15	4038/14038	0.85	4068/14068	0.15
4012/14012	0.15	4039/-	2.95	4069/14069	0.15
4013/14013	0.45	4040/14040	0.95	4070/14070	0.45
4014/14014	0.80	4041/-	0.65	4071/14071	0.15
4015/14015	0.80	4042/14042	0.65	4072/14072	0.15
4016/14016	0.45	4043/14043	0.80	4073/14073	0.15
4017/14017	0.80	4044/14044	0.75	4075/14075	0.15
4018/-	0.80	4045/-	1.15	4076/14076	1.25
4019/14519	0.45	4046/14046	1.30	4077/14077	0.45
4020/14020	0.90	4047/-	0.70	4078/14078	0.15
4021/14021	0.80	4048/-	0.45	4081/14081	0.15
4022/14022	0.75	4049/14049	0.45	4082/14082	0.15
4023/14023	0.15	4050/14050	0.45	4085/-	0.55
4024/14024	0.60	4051/14051	0.75	4086/-	0.55
4025/14025	0.15	4052/14052	0.75	4089/-	0.85
4026/14026	0.45	4053/14053	1.75	4090/4093	0.65
4027/14027	0.45	4054/-	0.95	4094/-	1.50
4028/14028	0.70	4055/-	1.05	4095/-	0.85
4029/-	0.90	4056/-	1.05		

CA 3130 CMOS/MOS Operational Amplifier 75p

4096/-	0.85	14515/4515	2.55	14543/-	1.50
4097/-	2.95	14516/4516	1.10	14549/-	2.95
4098/14528	0.85	14517/-	5.40	14552/-	0.95
4099/-	1.50	14518/4518	1.00	14553/-	3.50
		14519/4019	0.45	14554/-	1.20
		14520/4520	1.00	14555/4555	0.70
		14521/-	2.00	14556/4556	0.70
4700/-	1.50	14522/-	1.75	14557/-	3.20
7083/-	4.25	14523/-	N/S	14558/-	0.90
		14524/-	1.50	14559/-	2.95
14501/-	0.15	14527/4527	1.20	14560/-	1.50
14502/4502	1.00	14528/4098	0.85	14561/-	0.45
14503/-	0.50	14529/-	1.30	14562/-	5.25
14505/-	3.30	14530/-	0.65	14566/-	1.35
14506/-	0.45	14531/-	1.25	14572/-	0.35
14507/4030	0.90	14532/4532	1.60	14586/40106	6.00
14508/4508	2.55	14534/-	6.00	14587/40106	3.05
14510/4510	1.10	14536/-	2.85	14582/40182	1.15
14511/4511	1.25	14537/-	15.25	14583/-	0.71
14512/-	1.05	14539/-	1.05	14585/-	1.45
14514/4514	2.55	14541/-	1.80		

Free on request: Data on AY-5-1224 and MK50253 clock chips. 4 and 8 digit alarm clock suggested circuit, quartz crystal timebase, and L.E.D. displays (if you can send an S.A.E., it makes things a little easier for us).

CLOCK CHIPS AY-5-1224 4 digit basic clock £3.50 MK 50253 4/6 digit alarm/snooze £5.50
ECONOMY RED LED DISPLAYS (Class II quality, but guaranteed by us, fully returnable if not satisfied).
DL-707E/DL-70E 6mm (0.3") 70p. DL-727E/DL-728E 12mm (0.5") Double Digit £1.80. DL-747E/DL-750E 16mm (0.6") £1.50.
Term: C.W.O. Add VAT to all prices at 8%. Post etc. U.K. 10p per order, export 75p (no VAT). All orders processed on day of receipt.

GREENBANK ELECTRONICS (Dept. T8E)
94 New Chester Road, New Ferry, Wirral, Merseyside L62
5AB, England. Tel: 051-645 3391

EIGHTEEN 7-SEGMENT DISPLAYS £1.
Postage 10p. In arrays of 9, Gas discharge type. With data and connecting to clock I.C. gen. Mr. Bobker, 29 Chadderton Drive, Unsworth, Bury, Lancs.

LOW-COST I.C. MOUNTING for any size DIL package. 100 Soldercon sockets 60p. 7 and 8 hole plastic supports 5p pair. Quantity rates. SAE details and sample. Trial pack 60p. (P & P. 10p/order). **P.K.G. ELECTRONICS**, Oak Lodge, Tansley, Derbyshire DE4 5FE.

DIGITAL CLOCKS MODULES KITS CALCULATORS NEW PRICES NEW MODELS

"DELTA" 12 hour from **£8.00**
4 RED 0.5" LEDs

	STD	ALARM
Module Kit	(excl. case) 8.00	10.50
Module Assembled	(excl. case) 8.50	11.00
Complete Clock Kit	Perspex Case 10.36	12.91
Ready built Clock	Teak or Perspex Case 14.00	16.50

ALARMS: Built-in alarm: Tilt operated snooze
AM/PM indicator: Power failure indicator

"ALPHA" 4 GREEN 0.5" DIGITS from **£9.00**
12/24 hour

	STD	ALARM
Module Kit	(excl. case) 9.00	12.00
Module Assembled	(excl. case) 9.00	13.00
Complete Clock Kit	Perspex Case 11.50	14.00
Ready-built Clock	Perspex case 14.50	17.00

Genuine Teak Veneer Case or Perspex Case Colours: Black, White, Red, Blue, Green, Orange. Available separately £3.78

Built Alpha Units: State 12 or 24 hour
2-YEAR GUARANTEE ON READY BUILT CLOCKS

NOVUS CALCULATORS
650 £5.40
850 £6.75

Send S.A.E. for complete range
Buy it with Access

CWO. PULSE ELECTRONICS LTD. (E.2), 202 SHEFFORD ROAD, CLIFTON, SHEFFORD, BEDS. Tel. Hitchin (0462) 814477

LED panel clip 1p	S	0.125	0.2	INFRA RED 550mW Aval lead 49p 6mW £1.55 OPTO Data free ORP 12 55p
	RED	15p	19p	
	G/Y	27p	33p	
	OR	27p	33p	

OPTO-ISOLATORS		SCR s	50V	100V	400V	Diac
TL111	1.5kV 150kHz	T05	1A	25p	27p	45p BR100
4350	2.5kV 5MHz	T066	3A	27p	35p	50p 21p
AVDEL BOND 2gm.		400V TRIACS 2A 60p 10A £1.50				

AC125/6/7/8	15p	2N3053	15p	VOLTAGE REGS
AD161/162	40p	2N3054	45p	5V 7805 Plastic
AF117	20p	2N3065	41p	12V 7812 1 Amp
AF124/5/6/7	34p	2N3702/3/4	12p	15V 7815 all
BC1107/8/9	8p	2N3903/4/5/6/16p		18V 7818 £1.50
BC109C	12p	2N2646	35p	723 DIP14 50p
BC147/8/9	10p	MFF102	40p	
BC157/8/9	11p	2N3819	25p	BRIDGE RECTS.
BC167/8/9	11p	2N3823	30p	2A 50V 30p
BC169C	12p	BA100	9p	2A 100V 38p
BC177/8/9	17p			2A 200V 41p
BC182/3/4L	11p	IN914	3p	2A 400V 46p
BC186/7	30p	IN4001	5p	
BC212/3/4L	12p	IN4002/3	6p	ZENERS 2.7-33V
BCY70/71/72	13p	IN4004/5	7p	BZ788 or sim 9p
BF194/5	12p	IN4006/7	8p	555 Timer 60p
BF196/7	12p	IN4148	4p	556 2x555 £1.10
BFY50/51	16p	BA100	9p	LM380 £1.00
BFX29	30p	OA47	6p	2N414 £1.10
BFX84	24p	OA70 OA79	5p	7400 16p
BSX19/20	16p	OA81 OA90	7p	
OC71	10p	OA91 OA95	6p	D.I.L. SOCKETS
2N706	10p	OA200	6p	8-pin 12p
2N1711	20p	OA202	7p	14-pin 13p
2N2219	20p			16-pin 14p
2N2904/5/6/7/10p		OP. AMPS		Wick + bushes
2N2904/5/6A 18p		709 all	25p	T03 T06 5p
2N2926(R) 7p		741 8-pin	29p	Dial Pen 70p
2N2926(G) 12p		748 D.I.L.	38p	

PRICES INCLUSIVE + 15p P&P (1st class)

ISLAND DEVICES, P.O. Box 11, Margate, Kent

P.C.B.s FOR E.T.I. PROJECTS

G.P. Power Supply	ETI 131	94p
Sweet Sixteen Amp	ETI 457	£1.94
Waa-Waa	ETI 455	£2.65
Touch Switch	ETI 539	58p
Marker Generator	ETI 706	50p
Audio Expander-Compressor	ETI 443	£3.00
Temperature Meter	ETI 130	50p
Calculator Stopwatch	ETI 534	42p
Audio Noise Generator	ETI 441	41p
Audio Millivoltmeter	ETI 128	£1.85
Audio Level Meter	ETI 438	75p
Active Crossover	ETI 433A	86p
Active Crossover	ETI 433B	86p
Logic Probe	ETI 120	35p
Logic Pulser	ETI 121	35p
Logic Tester	ETI 122	£1.85
Tone Burst Generator	ETI 124	83p
Graphic Equalizer	ETI 427	£1.96
International 25 Amplifier		£4.22
F.M. Tuner	ETI 751	£2.23
Line Amplifier	ETI 430	35p
Electronic Ignition	ETI 312	£1.86
Impedance Meter	ETI 116	88p
Digital Display	ETI 533a	42p
Digital Display	ETI 533b	35p
Digital Voltmeter	ETI 117a	35p
Digital Voltmeter	ETI 117b	35p

New projects and others in TOP PROJECTS BOOK 3 available at 1.25p per sq. cm. for single sided or 1.5p per sq. cm. for double sided (min. 35p). NOTE: All boards are fibre-glass and price inc. DRILLING AND TUNING.

Send s.a.s. for full list of boards and components available including cases, panels and hardware, etc.

Mail orders, please, to: **D.S.M. PRODUCTS**
Unit 14 Southern Road, Aylesbury, Bucks.

This Month MORE SPECIAL OFFERS, while stocks last, of BRAND NEW DEVICES

These are not economy fallouts

4 off FND 500 0.5" Com. Cath. 7-seg. LED Display £3.95
 4 off FND 357 0.375" Com. Cath. 7-seg. LED Display £3.15
 5 off FLV 117 0.2" Red LED with Chip 90p

Power Pack No. 1: Contains 2 off TIP2955, 2 off TIP3055 + Mfg. kits £2.10
 Power Pack No. 2: Contains 5 off 1N4002, 5 off 1N4003, 5 off 1N4004 50p
 Power Pack No. 3: Contains 2 off 1A/400V Bridges, 2 off 2A/600V Bridges £1.00

AUDIO PACK No. 1: Contains 8 Transistors + circuit for 10W 8 ohm Amplifier £1.75
 AUDIO PACK No. 2: Contains 8 Transistors + circuit for 20W 8 ohm Amplifier £2.25

Project Pack No. 1: Contains 2 off of each BC107/8/9, BFY50/51/52, 2N3055 (14 Devices total) £2.40
 Opto Pack No. 1: Contains 1 off each red, green, yellow, orange, 0.125" LED with Chips 80p

1,000. YES, ONE THOUSAND 10mfd/12V Axial Lead Capacitors (16mm x 7mm Dia.) £8.50

VAT INCL ALL ORDERS. 20p P&P

AUDIO-OPTICS, 19 MIDDEWAY CHINNOR, OXON. Tel. 0844 52683

MOTOROLA M6800

MICROPROCESSORS

DO YOU NEED ASSISTANCE?
 HARDWARE AND SOFTWARE EXPERTISE IS AVAILABLE

MEK kits & components supplied.
 Send SAE to:
FRASER-MANNING LTD.
 26 Hervey Street, Ipswich, Suffolk

PRINTED CIRCUITS and HARDWARE

Readily available supplies of Constructors' hardware, Aluminium sheet and sections, Printed circuit boards, top quality for individual designs.

Popular E.T.I. boards always in stock. Prompt service.

Send 15p for catalogue.

RAMAR CONSTRUCTOR SERVICES
 MASONS ROAD
 STRATFORD-ON-AVON
 WARWICKS. Tel. 4879

TURN YOUR SURPLUS capacitors, transistors, etc., into cash. Contact COLES-HARDING & CO., P.O. Box 5, Frome, Somerset. Immediate settlement.

FREE TV CIRCUIT DIAGRAMS

All main British TV sets (plus many foreign) comprehensively covered in our easy-to-follow TV Repair Manuals — 4 mono and 3 colour.

Just send model No., if colour (mfrs. chassis type helps) with £4 and receive the manual covering your set — plus your set's circuit diagram on request free. Set of 7 only £25.

British TV Circuit Diagram Manuals — the main mono (over 37 series) for £9.50 and virtually every colour for £16.

Full details of these and other publications from:
T.V. TECHNIC (ETI)
 76 Church Street, Larkhall, Lanarks, ML9 1HE
 Tel. (0698) 883334

SUPERB INSTRUMENT CASES by Bazelli, manufactured from heavy duty PVC faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range, competitive prices start at a low 75p. Over 400 Models, to choose from. Prompt despatch. Free literature (stamp would be appreciated). Bazelli, Department No. 27, St. Wilfreds, Foundry Lane, Halton, Lancaster, LA2 6LT.

Same Day Despatch Glass-Fibre PCBs

G.P. Power Supply	ETI 131	90p
Sweet Sixteen	ETI 457	180p
Waa Waa Unit	ETI 455	240p
Touch Switch	ETI 539	75p
Audio Level Meter	ETI 438	85p
Logic Tester	ETI 122	150p
INT. 25 Stereo Amp		375p

OTHER PROJECTS AVAILABLE Ex STOCK

ETI 022	115p	ETI 309	100p	ETI 441	50p
ETI 116	85p	ETI 312	170p	ETI 529A	225p
ETI 117A & B	90p	ETI 413	140p	ETI 529B	225p
ETI 120	60p	ETI 422	270p	ETI 533A&B	100p
ETI 121	60p	ETI 424	140p	ETI 534	50p
ETI 122	150p	ETI 433A	90p	ETI 751	225p
ETI 128	175p	ETI 433B	90p	ETI 951	30p

RESISTORS H.S. Carbon Film 1/4 w 5% E12 Series — 1p
 Mixed Values 50 45p 100 80p
 ELECTROLYTICS 10mF 12v 10 25 50 330mF 25v — 6p
 TANTALUM BEAD 2.2 & 47mf only — 7p

THIS MONTHS SNIPS

CA 3046	40p	uA 741	25p	7474	25p
NE 555	40p	7400	7p	7493	40p
Miniature Glass Reed Switches.				10 for	50p
Toggle Switches by Arrow.	DPST 240V.	3A			17p
Slide Switches.	SPST 240V	3A			8p

STOP PRESS FRONT PANEL for ETI 122 — 200p

All prices include V.A.T. Add 20p P & P. List 10p.

R.F. EQUIPMENT SPARES Ltd
 3 LACY CLOSE WIMBORNE DORSET

CMOS: Gates 4001, 4011 17p. Counters 4017 83p; 4040 86p. 8-pin DIL ICs 741 24p; 555 44p. TRIACS (Plastic) TAG250 400V/10A 67p (3+ 64p). DIAC 19p. Mini Mains TRANSFORMERS 100mA 6-0-6V 85p; 12-0-12V 95p. 2N6027 (PUT) 30p; 2N3055 36p; 1N4004 6p; 13x8C148 80p; 10x8C158 80p*. P&P 15p ADD 8% VAT (*25%). **T.K. ELECTRONICS, 106 Studley Grange Road, LONDON, W7 2LX.**

SHOP FROM HOME with our catalogue. Fully illustrated and covering over 3,000 components, audio and disco accessories, tools and test meters. Reviewed as one of the best catalogues available. Send 30p now for your copy (issue No 5). Access, Giro, Barclaycard, Government and educational orders accepted. (Giro No 331-7056).

B. H. COMPONENT FACTORS LTD.
 Leighton Electronics Centre
 59 North St., Leighton Buzzard, Beds
 Tel: 2316 (0286) Shop hours: 9-12.30, 1.30-5 p.m. Closed Wednesday

INDEX TO ADVERTISERS

Ambit International	Page 33	I.L.P.	Page 49
B.I.E.T.	Page 74	Kinnie Components	Page 36
Bi-Pak	Page 27	Lee Instrumentation Ltd	Page 53
Bi-Pre-Pak	I.B.C.	Lynx Electronics	Page 63
Bywood	Page 17	Maplin	O.B.C.
Cambridge Learning Enterprises	Page 68	Marco Trading	Mini-Ad
Catronics Ltd	I.F.C.	Marshall's	Page 42
Chiltmead Ltd	Page 70	Metac International	Page 69
Crofton Electronics	Page 71	Minikits	Page 15
D. B. M. Products	Mini-Ad	Pronto Electronics	Page 36
Decon Laboratories Ltd	Page 16	Pulse Electronics	Mini-Ad
E.D.A.	Page 41	Ramar Electronics	Mini-Ad
Erie Electronics	Page 69	R.F. Equipment Spares	Mini-Ad
Greenbank Electronics	Mini-Ad	R.T.V.C.	Page 4, 5
Hart Electronics	Page 41	Sintel	Page 9
Henry's Radio Ltd	Page 33, 41	Technomatic	Page 71
		Wimslow Audio	Page 15

ENGINEERS FREE

**YOURSELF FOR A
BETTER JOB WITH MORE PAY!**



This 44-page
FREE book
shows how!

Do you want promotion, a better job, higher pay? "New opportunities" shows you how to get them through a low-cost, Home Study Course. There are no books to buy and you can pay as you learn.

This easy to follow GUIDE TO SUCCESS should be read by every ambitious engineer. Send for this helpful 44-page free book NOW! No obligation, nobody will call on you. It could be the best thing you ever did.

CHOOSE A BRAND NEW FUTURE HERE

CUT OUT THIS COUPON

Tick or state subject of interest. Post to address below.

ELECTRICAL & ELECTRONICS

- Practical Radio & Electronics (with Kit)
- Electronic Engineering Certificate
- General Elect. Eng. Certificate
- C & G Elect Installations
- Elect. Install. & Work

- C & G Elect. Technicians

RADIO AND TELE-COMMUNICATIONS

- Colour TV Servicing
- C & G Telecoms. Technician's Cert.
- C & G Radio, TV & Electronics Mech. Certificate
- Radio & TV Engineering Course
- Radio, Servicing & Repairs
- Radio Amateur's Exam.

AUTO & AERO

- Motor Mechanics*
- C & G Motor V Mechanics
- General Auto Engineering
- A.M.I.M.I.
- Air Registration Board Certs.
- MAA/IMI Dip.

CONSTRUCTIONAL

- Heating Ventilating & Air Conditioning
- Architectural Draughtsmanship & Design
- L.I.O.B.
- Carpentry & Joinery
- Plumbing Technology
- General Building
- Painting & Decorating

MECHANICAL

- A.M.S.E. (Mech.)
- General Mech. Eng.
- Inst. Engineers & Technicians
- Maintenance Engineering
- Welding

MANAGEMENT & PRODUCTION

- Computer Programming
- Inst. of Cost & Management Accts.

DRAUGHTSMANSHIP & DESIGN

- General Draughtsmanship
- A.M.I.E.D.
- Electrical Draughtsmanship



G.C.E.
-58 'O' & 'A' Level Subjects
-over 10,000 Group Passes!

Aldermaston College

Dept. TET 17, Reading RG7 4PF

also at our London Advisory Office, 4 Fore Street Avenue, Moorgate, London EC2Y 5EJ. Tel. 01-628 2721.

NAME (Block Capitals)

ADDRESS

Postcode

Other subjects of interest

Age

Accredited by C.A.C.C.

Member of A.B.C.C.

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

electronics today

international

reader services

BACK ISSUES

These cost 40p each. Postage and packing costs 15p for the first, and 10p for each subsequent issue. Orders to ETI BACK ISSUES Dept please. We CANNOT supply the following issues:- All 1972: January, February and November 1973: January, March, September, October, November and December 1974: January, June, July, August, September, November and December 1975: January 1976.

SUBSCRIPTIONS

The annual subscription to ETI for UK readers is £5.00. The current rate for readers overseas is £5.50. Canadian subscription rate is \$10 per year. Send orders to ETI SUBS Dept. . . .

BINDERS

Binders, for up to 13 issues, are available for £2.50 including VAT and carriage. Send orders to ETI BINDERS DEPT . . .

EDITORIAL QUERIES

Written queries can only be answered when accompanied by an SAE, and the reply can take up to three weeks. These must relate to recent articles and not involve ETI staff in any research. Mark your letter ETI QUERY . . . Telephone queries can only be answered when technical staff are free, and never before 4 pm.

MINI-ADS & CLASSIFIEDS

This is a pre-payment service - rates on application to ADVERTISING

SPECIAL ISSUES

Presently we produce four specials - Top Project 2 and 3, Electronics Electronics it's Easy (Parts 1-13) and 4600 Synthesiser (published by Maplin). Prices are 75p, £1, £1.20 and £1.50 respectively. Post and packing 15p per copy. Orders to ETI SPECIALS Dept please.

BOOKS

ETI Book Service sells books to our readers by mail order. The prices advertised in the magazine include postage and packing. Send orders to ETI Book Service, 25 Court Close, Bray, Maidenhead, Berks.

NON-FUNCTIONING PROJECTS

We cannot solve the problems faced by individual readers building our projects unless they are concerning interpretation of our articles. When we know of any error we print a correction as soon as possible at the end of News Digest. Any useful addenda to a project will be similarly dealt with. We cannot advise readers on modifications to our projects.

PCBs

PCBs are available for our projects from companies advertising in the magazine, such as Ramar and Crofton, who do an excellent service.

T-SHIRTS

ETI T-shirts are available in Large, Medium, or Small sizes. They are yellow cotton with black printing and cost £1.50 each. Send orders to ETI T-SHIRTS Dept . . .

**ADDRESS FOR ETI DEPARTMENTS—
36 EBURY ST, LONDON SWW 0LW**

**PLEASE MARK REVERSE OF EACH CHEQUE
WITH NAME & ADDRESS AND ITEMS
REQUIRED.**

ALLOW 10 TO 14 DAYS FOR DELIVERY




Stirling Sound Products

FROM BI-PRE-PAK

UNIT 1 PRE-AMP/CONTROL STEREO MODEL

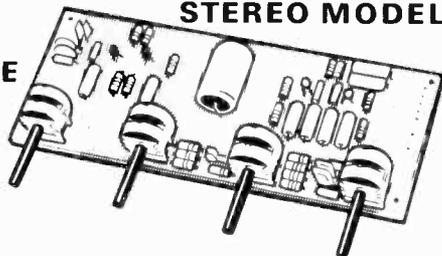SUPERB VALUE AT £7.80
with active tone control circuitry




UNIT 1 latest addition in the Stirling Sound range of realistically priced constructional modules is going to assure many many more constructors of obtaining quality where price has prevented it before

UNIT 1 offers full stereo facilities is guaranteed and easy to connect up

- Input sensitivity — 50 mV adjustable
- Output — 200 mV for 50 mV in
- Bass control — ± 15 dB at 30 KHz
- Treble control — ± 15 dB at 10 KHz
- Balance control, volume control, 1/4" spindles
- Operating voltage — 10 to 16V

MORE POWER — LESS V.A.T.

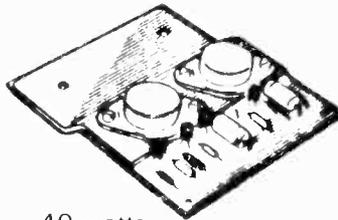

SS.140 Mk. 3 POWER AMP

Built for hard work
Now with built-in output capacitor

40 watts R.M.S into 4Ω

£3.95
+ 8% V.A.T.

Resulting from research and development, the Mk 3 version of this most popular power amp, now includes built-in output capacitor with improved stability under severe working conditions. Greatly used for P.A. disco and similar work. SS 140 offers fantastic value for the price

SUPER SPARK MK. 5 C.D.I. UNIT

Thousands are in use saving motorists time and money. Very easy to install. Incorporates switch for instant change to conventional ignition. Easy to set for pos. or neg. earth, anti-burglar immobilising switch, pre-set rev. limit control, neon light. The unit is on p.c.b. housed in strong enclosed metal box. With instructions and leads.

Size 7 7/8" x 4 1/2" x 2 1/4" (193 x 117 x 54MM) (P.P. — add 50p)

KIT **£7.95*** BUILT & TESTED **£10.50***

X-44 CROSS-HATCH GENERATOR

Operates at R.F. level

For colour and mono TV. Plugs into aerial socket of set. Operates without need for transmissions. 4 push-button operation. Runs on a self-contained penlite type batteries. Will fit easily into a large pocket. Strong plastic case.

BUILT **£27.50*** (less batts)

A USEFUL CATALOGUE — FREE

Send us a large S.A.E. with 10p stamp and we will send you the latest Bi-Pre Pack catalogue free by return. Packed with useful lines, it's a real money saver. **Semi-conductors, components, accessories, surprise bargains.**

MORE STIRLING SOUND MODULES

● TUNING

- SS.201 F.M. Front End with geared tuning and A.F.C. facility 88-108MHz **£5.00**
- SS.202 1 F. amp. A meter and/or A.F.C. can be connected (size 3" x 2") For use with SS 201 **£2.65**
- SS.203 Stereo decoder. For use with Stirling Sound modules, or with any other good mono F.M. tuning section. A LED beacon can be added (Price 18p) to indicate when a stereo signal is tuned in (3" x 2") **£3.85**

● POWER AMPS

- SS.103 Basic 3 watt r.m.s. I.C. power amp **£1.75**
- SS.103.3 Stereo version of above **£3.25**
- SS.105 5 watt amplifier to run from 12V (3 1/2" x 2" x 3/4") **£2.25**
- SS.110 Mk. 3 Similar to SS 105 but more powerful giving 10W into 4ohms, using 24 volts **£2.75**
- SS.120 Mk. 3 20 watt module when used with 34 volts into 4 **£3.25**
- SS.125 De-luxe 25 watt R.M.S. power amp having 0.04% distortion at all levels. Operates from 50V to give 25w.r.m.s. into 8 ohms **£5.00**

● CONTROL

- SS.100 Active tone control, stereo, ± 15dB cut and boost with suitable network **£1.60**
- SS.101 Pre-amp for ceramic p.u., radio & tape with passive tone control details **£1.60**
- SS.102 Stereo pre-amp with R.I.A.A. equalisation, mag. p.u., tape and radio in **£2.25**

● VOLTAGE STABILISER

- SS.300 **Power Supply Stabiliser.** Add this to your unbalanced supply to obtain a steady working voltage from 12 to 50V for your audio system, workbench, etc. Money saving and very reliable **£3.25***

10% OFF ALL s/s modules

TERMS OF BUSINESS:

VAT at 12 1/2% must be added to total value of order except for items marked * or (8%), when VAT IS TO BE ADDED AT 8%. No VAT on overseas orders. POST & PACKING add 30p for UK orders unless marked otherwise. Minimum mail order acceptable — £1. Overseas orders, add £1 for postage. Any difference will be credited or charged. PRICES subject to alteration without notice. AVAILABILITY All items available at time of going to press when every effort is made to ensure correctness of information.

Order your Stirling Sound products from

BI-PRE-PAK LTD




Co Reg No 820919

222 224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SSO 9DF.

TELEPHONE: SOUTHEND (0702) 46344


FACTORY — SHOEBOURNESS, ESSEX

All with easy to follow instructions

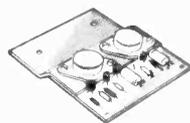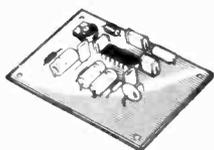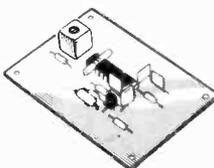

Stirling Sound

POWER PACKS

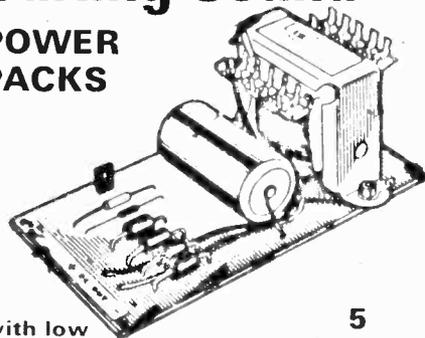

with low voltage take off point

5 models to choose from

Not only do these excellent power packs stand up unflinchingly to hard work, inclusion of a take-off point at around 13-15 V adds to their usefulness and once again price value is outstanding. Generously rated for reliability.

- SS 312 12V/1A **£3.75***
- SS 318 18V/1A **£4.15***
- SS 324 24V/1A **£4.60***
- SS 334 34V/2A **£5.20***
- SS 345 45V/4A **£6.25***

Please add 50p for P/p either model

TO STIRLING SOUND (BI-PRE-PAK) LTD, 222 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SSO 9DF

Please send

for which I enclose £

Inc V A T

NAME

ADDRESS


(ETI 8)

130 LOVE

Make it with MAPLIN!


ELECTRONIC COMPONENTS
WIDE RANGE • HIGH QUALITY • FAST SERVICE

The 4600 SYNTHESISER

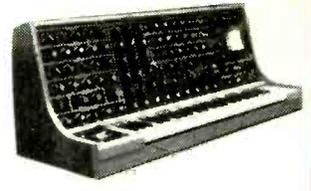

We stock all the parts for this brilliantly designed synthesiser, including all the PCB's, metalwork and a drilled and printed front panel, giving a superb professional finish. Opinions of authority agree the ETI International Synthesiser is technically superior to most of today's models. Complete construction details in our booklet now available price £1.50, or send SAE for specification.

ELECTRONIC ORGAN

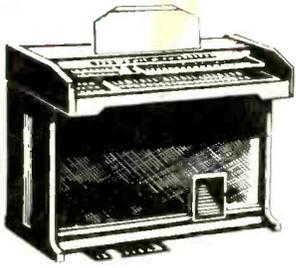


BUILD IT YOURSELF... IN STAGES

Get started with a 49 note instrument — features tremulant and reverberation. Ideal to learn on. Leaflet MES 51. Price 15p gives full details to build this complete instrument. Extend the range of MES 51 by adding another keyboard and several new tone colours. Leaflet MES 52. Price 15p also shows how to use 61 note keyboards.

Fully controllable attack and deCay controls (normally found only on the most expensive organs), up to seven footages on each keyboard, up to 70 controls including drawbars, and a 13 note pedalboard, make up the additions described in the step-by-step 22 page instruction leaflet MES 53. Price 35p.


GRAPHIC EQUALIZER

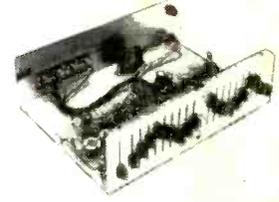

A really superior high quality stereo graphic equalizer featuring 9 octaves per channel. We stock all the parts (except woodwork) including the metalwork drilled and printed. 15p brings you a reprint of the article.

DIGITAL CLOCK KITS

ONLY **£8.60** INC. VAT E/P/P

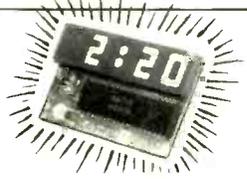

This is a fully constructed and tested electronic clock module as illustrated. Data sheet supplied. Simple to connect to alarm and your battery/mains radio. Smart case available. Data sheet available separately. Please send SAE.

- * Bright 4 Digit 0.5" Red Display
- * Flashing Colon (1Hz)
- * Switch for Display Seconds
- * Alarm Set Indicator
- * P.M. Indicator
- * Power Failure Indicator
- * Sleep Timer
- * Snooze Timer
- * Time can be set accurately to within one second
- * Leading Zero Blanking

SIMPLE CLOCK KIT — £9.38 ALARM CLOCK KIT — £10.99
ALARM CLOCK & RADIO CONTROLLER KIT — £11.51
SMART PLASTIC CASE with fully punched chassis — £2.49
Please send SAE for our Clock data sheet



100 W PER CHANNEL STEREO DISCO

- * Automatic voice operated fader
- * Belt drive turntables
- * Monitor facilities (Headphones and VU meter)
- * Sound operated light show — plus many other advantages

Send for our leaflet MES 41 giving full details for construction. Price 20p. Soon you'll be the Deejay everyone wants at their party!

Get our FABULOUS NEW 1977/78 CATALOGUE

PUBLICATION DATE OCT. 28, 1976 ON APPROVAL

All new • Completely re-written • Hundreds of new lines
Lots of exciting new projects to build — PRICE 50p
SEND NO MONEY NOW Overseas send R International reply coupons

JOIN OUR MAILING LIST NOW!

Published every two months our Newsletter gives full details of our latest guaranteed prices
Send 30p and we'll send you the next 6 issues as they are published

- * SAVE ££'s ON SPECIAL OFFERS!
- * DETAILS OF NEW PROJECTS AND NEW LINES

Please rush me a copy of your brand new 1977/78 catalogue the instant it is printed (Oct 28th 1976) Only if I am completely satisfied that it is worth every penny will I send 50p within 14 days of receipt. If I am not satisfied I may return the catalogue to you within 14 days without obligation. I understand that I need not purchase anything from your catalogue should I choose to keep it.

NAME _____
ADDRESS _____



MAPLIN ELECTRONIC SUPPLIES
All mail to: P.O. Box 3 Rayleigh Essex SS6 8LR
Shop 284 London Road Westcliff-on-Sea Essex
(Closed on Monday) Tel. Southend (0702) 44101

If you do not wish to cut magazine write your request for catalogue on separate sheet
1975 76 GREEN COVER CATALOGUE STILL AVAILABLE PRICE 40