

# electronics today

JANUARY 1979

INTERNATIONAL

50p

Take out the scratches with our



**eti**

CLICK  
ELIMINATOR

INPUT

CLICK

CLICK

LEVEL

# CLICK ELIMINATOR

**Digital Tacho**  
**Boris in Check**  
**Power Supplies**  
**Loudspeaker Principles**

**Inside:**  
**computing**  
**today no3**

... NEWS ... PROJECTS ... MICROPROCESSORS ... AUDIO ...

# TRANSCENDENT 2000 SINGLE BOARD SYNTHESIZER


LIVE PERFORMANCE SYNTHESIZER DESIGNED BY CONSULTANT TIM ORR (FORMERLY SYNTHESIZER DESIGNER FOR EMS LIMITED) AND FEATURED AS A CONSTRUCTIONAL ARTICLE IN ELECTRONICS TODAY INTERNATIONAL.

The TRANSCENDENT 2000 is a 3 octave instrument transposable 2 octaves up or down giving an effective 7 octave range. There is portamento, pitch bending, a VCO with shape and pitch modulation, a VCF with both low and high pass outputs and a separate dynamic sweep control, a noise generator and an ADSR envelope shaper. There is also a slow oscillator, a new pitch detector, ADSR repeat, sample and hold, and special circuitry with precision components to ensure tuning stability amongst its many features.

The kit includes fully finished metalwork, fully assembled solid teak cabinet, filter sweep pedal, professional quality components (all resistors either 2% metal oxide or 1/2% metal film!) and it really is complete — right down to the last nut and bolt and last piece of wire! There is even a 13A plug in the kit — you need buy absolutely no more parts before plugging in and making great music! Virtually all the components are on the one professional quality fibre glass PCB printed with component locations. All the controls mount directly on the main board, all connections to the board are made with connector plugs and construction is so simple it can be built easily in a few evenings by almost anyone capable of neat soldering! When finished you will possess a synthesizer comparable in performance and quality with ready built units selling for between £500 and £700!

**COMPLETE KIT  
ONLY  
£172.00 + VAT!**

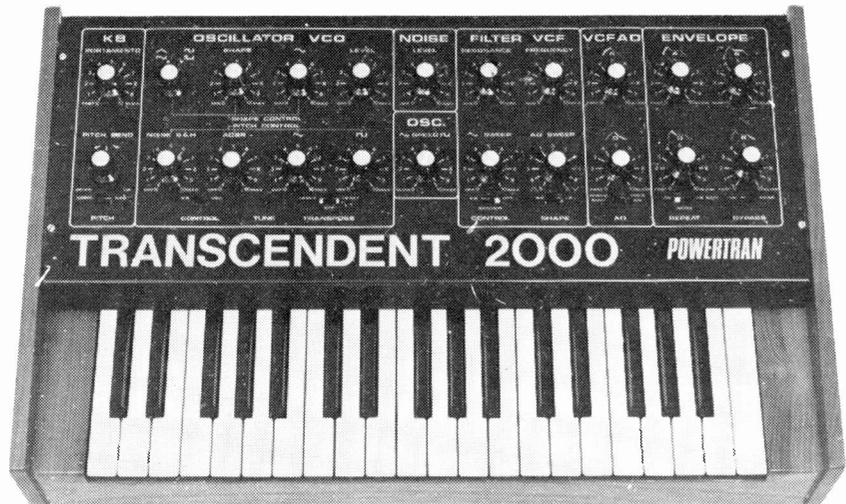Comprehensive handbook supplied with all complete kits! This fully describes construction and tells you how to set up your synthesizer with nothing more elaborate than a multi-meter and a pair of ears!



Cabinet size 24.6" x 15.7" x 4.8" (rear) 3.4" (front)

## LAST MONTH'S FRONT COVER FEATURE!



**COMPLETE KIT  
ONLY  
£49.50 + VAT!**

PSI 4002 STUDIO MODEL



cabinet size 17.2" x 17.2" x 6.7"

**COMPLETE KIT ONLY £196.90 + VAT**

The kits shown on this page are also available as separate packs (e.g. P.C.B. component sets, hardware sets etc) Prices are given in our FREE CATALOGUE

## 200+ 200 watt AMPLIFIER

As featured in *Electronics Today International*

**400W rms continuous — 800W peak!**

**0.03% THD at FULL power!**

**PLUS all the following features too!**

- ★ Each channel totally independent with its own stabilised power supply driven by custom designed TOROIDAL transformers!
- ★ Inherent reliability — monster heat sinks for cool running at the hottest venues — electronic open and short circuit protection!
- ★ Ultra low feedback (an incredible low 14dB overall!), super high slewing rate (20V/μs), 200W rms continuous to 4 ohm from EACH channel, input sensitivity 0.775V (0dB).
- ★ Professional quality components, sturdy 19" rack mounting chassis complete with sleeve and feet for free standing work too.
- ★ Easy to build — plenty of working space with ready access to all components, minimal wiring, extensive instruction suitable for both experience constructors and newcomers to electronics.
- ★ Value for money — quality and performance comparable with ready-built amplifiers costing over £600!

**PRICE STABILITY:** Order with confidence irrespective of any price changes. We will honour all prices in this advertisement until February 28th, 1979, if ETI January, 1979 issue is mentioned with your order. Errors and VAT rate changes excluded.

**EXPORT ORDERS:** No VAT. Postage charged at actual cost plus 50p handling and documentation.

**U.K. ORDERS:** Subject to 12% surcharge for VAT\* (i.e. add 1/6 to the price). No charge is made for carriage \*or at current rate if changed.

**SECURICOR DELIVERY:** For this optional service (U.K. mainland only) add £2.50 (VAT inclusive) per kit.

**SALES COUNTER:** If you prefer to collect your kit from the factory, call at Sales Counter (at rear of factory). Open 9 a.m.-4.30 p.m. Monday-Thursday

**OUR CATALOGUE IS FREE! WRITE OR PHONE NOW!**

## POWERTRAN ELECTRONICS

PORTWAY INDUSTRIAL ESTATE  
ANDOVER, HANTS SP10 3NM


ANDOVER  
(STD 0264) 64455

# electronics today


JANUARY 1979 VOL 8 NO 1 **INTERNATIONAL**



Time we did this p.84

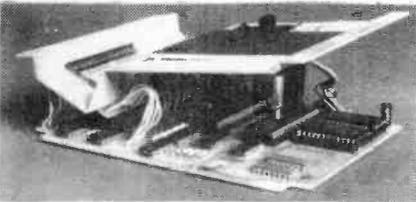

Check it out p.81

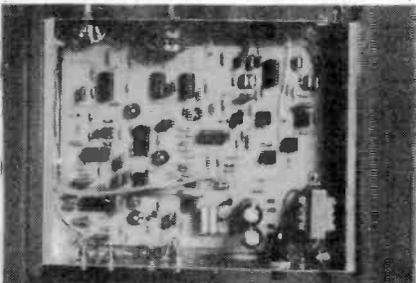

De-click de hi-fi p.73

## FEATURES

|                         |           |                                       |
|-------------------------|-----------|---------------------------------------|
| NEWS DIGEST             | <b>7</b>  | What goes on with whom and where!     |
| LOUDSPEAKER PRINCIPLES  | <b>14</b> | Cone-fident appraisal of all types!   |
| POWER SUPPLIES          | <b>27</b> | Tim Orr explains how — and why.       |
| ELECTRONICS IN MEDICINE | <b>40</b> | A history of the electron put to use. |
| DATA SHEET EXPLAINED    | <b>57</b> | This was your idea.                   |
| MICROFILE               | <b>67</b> | Big news for micro-men.               |
| BORIS IN CHECK          | <b>81</b> | A new chess machine tested.           |
| AUDIOPHILE              | <b>87</b> | A Shure winner?                       |
| TECHNICAL MEMORANDUM    | <b>91</b> | A revolutionary new concept!          |
| TECH TIPS               | <b>93</b> | Readers own ideas.                    |

## PROJECTS

|                  |           |                                     |
|------------------|-----------|-------------------------------------|
| DIGITAL TACHO    | <b>23</b> | Going around in the car accurately. |
| DIGITAL MODULE   | <b>35</b> | Useful four digit design.           |
| DIGITAL DIAL     | <b>49</b> | Medium wave high quality.           |
| LOG CONVERTOR    | <b>62</b> | Turn your keyboard to use.          |
| CLICK SUPPRESSOR | <b>73</b> | Record project!                     |

## INFORMATION

|                   |           |                              |
|-------------------|-----------|------------------------------|
| ETI BOOK SERVICE  | <b>47</b> | Fine print this.             |
| SPECIALS FROM ETI | <b>55</b> | All our publication on show. |
| PANEL TRANSFERS   | <b>59</b> | Finishing touch.             |
| HOBBY ELECTRONICS | <b>61</b> | Look out for it!             |
| BINDERS           | <b>69</b> | Keep 'em looking good.       |
| ETI PRINTS        | <b>71</b> | What other way is there?     |
| FEBRUARY PREVIEW  | <b>79</b> | News of next month's ETI.    |
| MARKETPLACE       | <b>84</b> | A new LADIES' watch!         |
| SUBSCRIPTIONS     | <b>92</b> | Make it easy on yourself.    |
| T-SHIRTS          | <b>98</b> | Good cover!                  |

### INTERNATIONAL EDITIONS

|           |   |
|-----------|---|
| AUSTRALIA | Collyn Rivers<br>Publisher<br>Les Bell<br>Acting Editor         |
| Holland   | Anton Kriegeman<br>Editor-in-Chief                              |
| CANADA    | Steve Braidwood<br>Editor<br>Graham Wideman<br>Assistant Editor |
| GERMANY   | Udo Wittig<br>Editor  |



ABC

EDITORIAL AND ADVERTISEMENT OFFICE  
25-27 Oxford Street, London W1R 1RF. Telephone 01-434 1781/2. Telex 8811896

|                            |                                |
|----------------------------|--------------------------------|
| Halvor W. Moorshead        | Editor                         |
| Ron Harris B. Sc           | Assistant Editor               |
| Gary Evans                 | Project Editor                 |
| Pete Howells               | Production Editor              |
| Paul Edwards               | Technical Illustrator          |
| Steve Ramsahadeo           | Project Development            |
| Margaret Hewitt            | Administration                 |
| Kim Hamlin, Brenda Goodwin | Reader Services                |
| Tim Salmon, Val Tregidgo   | Advertising Manager            |
| Mark Strathen              | Provincial Advertising Manager |
| David Sinfeld              | Advertising Assistant          |
| Joy Cheshire               |                                |

PUBLISHED BY Modmags Ltd., 25-27 Oxford Street, London W1R 1RF  
DISTRIBUTED BY Argus Distribution Ltd (British Isles)  
Gordon & Gotch Ltd (Overseas)  
PRINTED BY QB Limited, Colchester

Electronics Today International is normally published on the first Friday of the month prior to the cover date

COPYRIGHT: All material is subject to world wide Copyright protection. All reasonable care is taken in the preparation of the magazine to ensure accuracy but ETI cannot be held responsible for it legally. Where errors do occur a correction will be published as soon as possible afterwards.

# High quality audio modules for Stereo and Mono

## \$450

**STEREO FM TUNER**  
Fitted with phase lock-loop

**£22.30**

+ 40p p&p  
+ 12½% VAT



The 450 Tuner provides instant programme selection at the touch of a button ensuring accurate tuning of 4 pre-selected stations, any of which may be altered as often as you choose, simply by changing the settings of the pre-set controls. Features include FET input stage, Vari-Cap diode tuning, Switched AFC LED Stereo Indicator.

|                                   |                      |
|-----------------------------------|----------------------|
| FREQUENCY RANGE                   | 88 — 108 Mhz         |
| SENSITIVITY                       | 3.0µV                |
| BANDWIDTH                         | 250 kHz              |
| SPURIOUS REJECTION                | 50 dB                |
| SELECTIVITY ± 400 kHz             | 55 dB                |
| AUDIO OUTPUT (22.5 kHz deviation) | 100 mV               |
| STEREO SEPARATION                 | 30 dB                |
| SUPPLY REQUIREMENTS               | 20 to 30V (90mA max) |
| AERIAL IMPEDANCE                  | 75 ohms              |
| DIMENSIONS                        | 240mm x 110mm x 32mm |

## MPA30

**MAGNETIC CARTRIDGE PRE-AMPLIFIER**



**£2.95**

25p p&p  
+ 12½% VAT

Enjoy the quality of a magnetic cartridge with your existing ceramic equipment using the MPA 30 which is a high quality preamplifier/enabling magnetic cartridges to be used where facilities exist for the use of ceramic cartridges only

|                 |                                    |
|-----------------|------------------------------------|
| SENSITIVITY     | 3.5 mV for 100 mV output           |
| EQUALISATION    | Within ± 1 dB from 20 Hz to 20 kHz |
| INPUT IMPEDANCE | 50 K ohms                          |
| SUPPLY          | 18 to 30 V—re earth                |
| DIMENSIONS      | 110x50x25mm (inc DIN socket)       |

## Stereo 30

**COMPLETE AUDIO CHASSIS**

**£18.95**

+ 40p p&p  
+ 12½% VAT



7 + 7w R.M.S.

The Stereo 30 comprises a complete stereo pre-amplifier, power amplifiers and power supply. This, with only the addition of a transformer or overwind will produce a high quality audio unit suitable for use with a wide range of inputs i.e. high quality ceramic pick-up, stereo tuner, stereo tape deck, etc. Simple to install, capable of producing really first-class results, this unit is supplied with full instructions, black front panel knobs, main switch, fuse and fuse holder and universal mounting brackets.

|                                      |                              |
|--------------------------------------|------------------------------|
| OUTPUT POWER                         | 7 Watts RMS                  |
| LOAD IMPEDANCE                       | 8 ohms                       |
| TOTAL HARMONIC DISTORTION            | Less than 5% (Typically .3%) |
| FREQUENCY RESPONSE                   | 50 Hz to 20 kHz ± 3dBs       |
| tone control range                   | ± 12dBs at 100 Hz and 10kHz  |
| SENSITIVITY                          | 190 mV for full output       |
| INPUT IMPEDANCE                      | 1 M ohms                     |
| TRANSFORMER REQUIREMENTS             | 22 V.A.C. rated at 1A        |
| DIMENSIONS (Less controls and PARTS) | 200mm x 130mm x 33mm         |

## PA12

**STEREO PRE-AMPLIFIER**



**£7.10**

30p p&p  
+ 12½% VAT

The PA12 Stereo Pre-Amplifier chassis is designed and recommended for use with the AL 20/30 Audio Amplifier Modules, the PS12 power supply and the T538 Transformer. Features included on/off volume, Balance, Bass and Treble controls. Complete with tape output.

|                       |                       |
|-----------------------|-----------------------|
| FREQUENCY RESPONSE    | 20 Hz — 20 kHz (—3dB) |
| BASS CONTROL          | ± 12 dB at 60 Mz      |
| TREBLE CONTROL        | ± 14 dB at 10 kHz     |
| INPUT IMPEDANCE       | 1 Meg. ohm            |
| INPUT SENSITIVITY     | 300 mV                |
| CROSSTALK             | — 60 dB               |
| SIGNAL/NOISE RATIO    | — 65 dB               |
| OVERLOAD FACTOR       | ± 20 dB               |
| TAPE OUTOUT IMPEDANCE | 25 K ohms             |
| DIMENSIONS            | 152mm x 84mm x 35mm   |

## AL60

**AUDIO AMPLIFIER MODULE**  
25 Watts RMS

**£4.55** + 25p p&p

+ 12½% VAT



25w R.M.S.

This high quality audio amplifier module is for use in audio equipment and stereo amplifiers and provides output powers up to 25 RMS with distortion levels below 0.1%.

|                            |                               |
|----------------------------|-------------------------------|
| OUTPUT POWER               | 25 Watts RMS                  |
| SUPPLY                     | 30-50 V                       |
| LOAD IMPEDANCE             | 8-16 ohms                     |
| TOTAL HARMONIC DISTORTION  | Less than 1% (Typically .06%) |
| FREQUENCY RESPONSE         | 20 Hz to 30 kHz x 2 dBs       |
| SENSITIVITY                | 280 mV for full output        |
| MAX. HEAT SINK TEMPERATURE | 90 C                          |
| DIMENSIONS                 | 103mm x 64mm x 15mm           |

## PS12 POWER SUPPLY MODULE

Power supply for AL20A-30A, PA12, S450 etc. Transformer T538. INPUT A.C. VOLTAGE 15-20V. OUTPUT D.C. VOLTAGE 22-30V approx. (dependent upon input). OUTPUT CURRENT 800mA maximum. DIMENSIONS 60x43x26 mm.



**£1.30**

+ 12½% VAT P&P 25p

## AL80

**AUDIO AMPLIFIER MODULE**

**£7.15\*** + 25p p&p

+ 8% VAT



35w R.M.S.

The AL80 is similar in design to the AL60 above and is of the same high quality but provides output powers up to 35W with distortion levels below 0.1%.

|                            |                               |
|----------------------------|-------------------------------|
| OUTPUT POWER               | 35 Watts RMS                  |
| SUPPLY                     | 40—60 V                       |
| LOAD IMPEDANCE             | 8—16 ohms                     |
| TOTAL HARMONIC DISTORTION  | Less than 1% (Typically .06%) |
| FREQUENCY RESPONSE         | 20 Hz to 30 kHz x 2 dBs       |
| SENSITIVITY                | 280 mV for full output        |
| MAX. HEAT SINK TEMPERATURE | 90°C                          |
| DIMENSIONS                 | 103mm x 64mm x 15mm           |

## AL250

**POWER AMPLIFIER**

125w R.M.S.

**£17.25\*** + 40p p&p

+ 8% VAT



This unit, designated AL250, is a power amplifier providing an output of up to 125W RMS, into a 4 ohm load.

|  |                                      |
|--|--------------------------------------|
| OUTPUT POWER                           | 125 Watts RMS continuous             |
| OPERATING VOLTAGE                      | 50—80V                               |
| LOADS                                  | 4—16 ohms                            |
| FREQUENCY RESPONSE                     | 25 Hz — 20 kHz measured at 100 Watts |
| SENSITIVITY FOR 100 WATTS O/P AT 1 kHz | 450mV                                |
| INPUT IMPEDANCE                        | 33K ohms                             |
| TOTAL HARMONIC DISTORTION              | 50 Watts into 4 ohms 0.1%            |
| 50 WATTS into 8 ohms                   | 0.06%                                |

## AL30A

**AUDIO AMPLIFIER MODULES**

**£3.75**

+ 25p p&p

12½% VAT



10w R.M.S.

These low cost 5 and 10 watt modules offer the utmost in reliability and performance, whilst being compact in size

|                           |                       |
|---------------------------|-----------------------|
| MAXIMUM SUPPLY VOLTAGE    | 30V                   |
| POWER OUTPUT for 2% THD   | 10 Watts RMS          |
| TOTAL HARMONIC DISTORTION | Less than .25%        |
| LOAD IMPEDANCE            | 8 — 16 ohms           |
| INPUT IMPEDANCE           | 100 K ohms            |
| FREQUENCY RESPONSE        | 50 Hz kHz ± 3 dBs     |
| SENSITIVITY               | 75 mV for full output |
| DIMENSIONS                | 74mm x 63mm x 28mm    |

## SPM80

**STABILISED POWER SUPPLY**

**£4.25** + 25p p&p

+ 12½% VAT



Designed to power two AL60's at 15 Watts per channel simultaneously. Circuit Techniques include full short protection.

|                     |                     |
|---------------------|---------------------|
| INPUT A.C. VOLTAGE  | 33—40V              |
| OUTPUT D.C. VOLTAGE | 33 V nominal        |
| OUTPUT CURRENT      | 10 mA—1.5 amps      |
| OVERLOAD CURRENT    | 1.7 amps approx.    |
| DIMENSIONS          | 105mm x 63mm x 30mm |

## PA100

**STEREO PRE-AMPLIFIER**

**£15.80**

+ 40p p&p  
+ 12½% VAT



A top quality stereo pre-amplifier and tone control unit, the PA100 provides a comprehensive solution for the front end requirements of stereo amplifiers or audio units. The six push-button selector switch gives a choice of inputs together with two filters for high and low frequencies

|                           |                                    |
|---------------------------|------------------------------------|
| FREQUENCY RESPONSE        | 20Hz to 20 kHz x 1 dB              |
| TOTAL HARMONIC DISTORTION | Less than 1% (Typically .07%)      |
| SENSITIVITY 1. TAPE       | 100 mV / 100 K ohms) For an        |
| INPUTS 1. RADIO TUNER     | 100 mV / 100K ohms) output         |
| 3. MAGNETIC P.U.          | 3.5 mV / 50 K ohms) 250mV          |
| EQUALISATION              | Within ± 1 dB from 20 Hz to 20 kHz |
| BASS CONTROL RANGE        | ± 15 dBs at 75 Hz                  |
| TREBLE CONTROL RANGE      | + 10—20 dBs at 15 kHz              |
| SIGNAL/NOISE RATIO        | Better than 65 dBs (All inputs)    |
| INPUT OVERLOAD            | Better than 26 dBs (All inputs)    |
| SUPPLY                    | 20 to 40 V                         |
| DIMENSIONS                | 300x90x33mm (less controls)        |

## MA60 HI-FI AMPLIFIER KIT

Build your own reliable top quality amplifier and save yourself pounds. The MA60 kit comprises the following BI-kits modules. 2x AL60 amps, 1x PA100 pre-amp 1x SPMB0 stabilised power supply 1x BMTB0 transformer, thus giving 17 watts RMS per channel STEREO. All modules are covered by the usual BI-PAK satisfaction or money back guarantee. Further details of all the above modules are in this advert.  
**PRICE £32.00 + 12½% + 62p p&p**

## TC60 KIT

A beautiful designed genuine TEAK WOOD veneered cabinet to put the professional touches to your home built amplifier. Full set of parts incl. front and back panels, knobs, chassis, fuses, sockets, Noen, etc. Ideal for the MA60 Size 425mm x 290mm x 95mm  
**PRICE £19.95 + 12½% VAT + 86p p&p**

## TRANSFORMERS

|                                     |                                    |
|-------------------------------------|------------------------------------|
| T538 For use with S 450 AL30A MPA30 |                                    |
| Order No. 2036                      | Price £3.20 + 55p p&p + 12½% VAT   |
| T2050 For use with Stereo 30        | Price £3.25 + 55p p&p + 12½% VAT   |
| Order No. 2050                      |                                    |
| BMTB0 For use with AL60 SPM80       | Price £5.40 + 86p p&p + 12½% VAT   |
| Order No. 2034                      |                                    |
| BMT250 For use with AL250           | Price £6.35 + £1 10 p&p + 12½% VAT |
| Order No. 2035                      |                                    |

# BI-PAK

DEPT. ET16, P.O. Box 6, Ware, Herts

# High quality audio accessories

## AL120

**50W**  
R.M.S.

**AUDIO AMPLIFIER**  
(With integral heat sink and short-circuit protection)

**£11.95**  
+8% VAT P&P 25p



**OUTPUT POWER SUPPLY**  
LOAD IMPEDANCE  
TOTAL HARMONIC DISTORTION  
FREQUENCY RESPONSE  $\pm 1$ dB  
SENSITIVITY  
MAX HEAT SINK TEMP.  
DIMENSIONS

50 Watts R.M.S.  
70 Watts  
8-16 Ohms  
05% Max. (typically 02%)  
25Hz-20kHz  
500mV  
45 deg. C  
192x89x49mm

Introduced to fulfill the demand for a fully protected power amp. capable of driving high quality speaker systems at up to 50W, with distortion levels below 05%. Ideal for domestic use, discos, p.a. systems, electronic organs, etc. The generously rated components ensure continuous operation at high output levels.

## SPM120

STABILISED POWER SUPPLIES

SPM120/45  
SPM120/55  
SPM120/65

**£5.50**  
+12½% VAT P&P 25p

**NEW**



### A.C. INPUTS

SPM120/45  
SPM120/55  
SPM120/65

OUTPUT CURRENT  
RIPPLE

40-48V  
50-55V  
60-65V  
2.5A  
1A 100mV  
2A 150mV

SPM120 is a fixed voltage stabiliser available with an output voltage of either 45V, 55V or 65V. Designed primarily for use in audio applications, the stabiliser which provides output currents up to 2.5A, operates direct from a mains transformer requiring only the addition of 2 Electrolytic capacitors to complete the s/c protection.

## GE100 Mk. 2

10 Channel monographic equaliser

**£20**  
+12½% VAT P&P 35p

**NEW**



CONTROL RANGE  
DYNAMIC RANGE  
MAXIMUM OUTPUT  
FREQUENCY RESPONSE  
POWER SUPPLY  
VOLTAGE HANDLING INPUT  
T.H.D.

$\pm 12$ dB  
110dB  
+15dB  
30Hz-20kHz ( $\pm 1$ dB)  
15-0-15V  
3V R.M.S.  
005%

Only 155mmx65mmx50mm including the 10x10K lin slider potentiometers and knobs which are mounted on a board positioned above the circuitry. In the frequency range of 31Hz to 20kHz you can cut and boost  $\pm 12$ dB with the 10 sliders, each of which has its frequency marked on the circuit board. The GE100 has numerous uses including mixers, p.a. systems and discos. It will also greatly improve the sound reproduction of your existing audio equipment. Power supply for GE100, o/d SG30 £3.80.

## VPS30

Regulated variable stabilised power supply

**£7.60**  
+8% VAT P&P 35p



A.C. INPUT MAXIMUM  
VOLTAGE REGULATION  
REGULATED CURRENT  
Incorporating short circuit protection

25V  
2-30V  
0-2A

This NEW versatile Regulated Variable Stabilised Power Supply with short circuit protection and current limiting, is a must for all electronics enthusiasts. It incorporates adjustable voltage from 2V-30V, with a current limiting range of 0-2A. With this module there is no need to build a separate power supply for each of your projects, with the simple addition of a transformer (o/d 2033), 0-1mA (o/d 1310 or 1305), plus a suitable shunt, a voltmeter (o/d 1311 or 1306), a 470ohm pot (o/d 1896), a 4K7 pot (o/d 1899), it can be used again and again as a self-contained bench, power supply, eliminating the use of batteries and thus saving ££'s!

## PA200

STEREO PRE-AMPLIFIER

**£16.55**  
+12½% VAT P&P 40p



FREQUENCY RESPONSE  
TOTAL HARMONIC DISTORTION  
SENSITIVITY 1 TAPE  
INPUTS 2 RADIO TUNER  
3 MAGNETIC

20 Hz to 20 kHz x 1dB  
Less than 1% (typically .07%)  
100mV/100K ohms For an  
100mV/100K ohms output  
P U 3-5mV/50K

BASS CONTROL RANGE  
TREBLE CONTROL RANGE  
SIGNAL/NOISE RATIO  
INPUT OVERLOAD  
SUPPLY  
DIMENSIONS

Within  $\pm 1$ dB from 20Hz to 20kHz  
 $\pm 15$ dBs at 75kHz  
 $\pm 10-20$ dBs at 15kHz  
Better than 65dBs (all inputs)  
Better than 26dBs (all inputs)  
35 to 75V  
300x90x33mm (less controls)

The PA200 is basically our popular PA100. Modifications have been made to make it compatible with the higher output AL120 and AL250 amplifiers.

## HEADPHONES

A top quality headphone with cushioned earpads and headband. Separate balance/volume controls. Stereo or mono switch. Impedance 8ohms. Frequency 30-18,000Hz o/n 884 **£8.70** +12½% VAT P&P 70p. A brilliant compromise between price and performance. Superb stereo reproduction for the newcomer to Hi-Fi. Impedance 8ohms. Frequency 30-15,000Hz o/n 885 **£4.40** +12½% VAT P&P 50p.

## BIB

HI-FI ACCESSORIES

**Parallel Tracking GROOV KLEEN**  
The very latest in automatic record cleaning. Designed to suit all modern single play decks. Simple to fit, it is extremely efficient. Complete with two types of base and three height extensions o/n 8101 **£3.68** +8% VAT P&P 35p.

**Cassette Tape Editing Kit**  
Enables cassette tapes to be edited and joined easily, quickly and accurately. Kit comprises: Tape Splicer (3.2mm) 2 Precision Tape Cutters, Tape Piercer, 9 Self adhesive Labels, Reel of Splicing Tape, 3 Winders and removers and instructions, all in a handy wallet o/n 811 **£2.40** +8% VAT P&P 35p.

**GRDOV-STAT**  
The BIB Groov-Stat static reducer neutralises the static charge on records and other plastic surfaces o/n 8103 **£5.45** +8% VAT P&P 35p.

**Cassette Head Cleaner**  
Essential for cleaning of tape heads, capstans and rollers. Pack contains Tape Head Applicator and tape head polisher tools. Plus bottle of special formula cleaning fluid and full instructions o/n 832 **£0.56** +12½% VAT P&P 35p.

## ADAPTORS

**AC-DC** enables a large range of battery powered radios, recorders, calculators to be run off the mains (220-240V A.C.). Switchable for 6, 7.5 or 9 volts. Current rating 2,500mA. Polarity reversing switch. Universal plug incorporated. o/n 137 **£3.95** +12½% VAT P&P 35p.

**DC-DC** for use in all cars, boats, etc., with pos. or neg. earth for a regulated output of 6, 2.5 or 9 volts D.C. at 1A max. For radios, recorders, etc. o/n 138 **£2.80** +12½% VAT P&P 32p.

## CROSSOVER NETWORKS

**2-WAY** channels for high and low frequencies to correct speakers — high to tweeters, low to woofers. Complete with instructions. Frequency 3,000Hz o/d 1904 **£1.10** +12½% VAT P&P 35p.

**2-WAY** for Bohm speakers up to 30 watts. Frequency 3kHz o/n 1905 **£1.65** +12½% VAT P&P 35p.

**3-WAY** for Bohm speakers up to 3D watts. Frequency 800Hz and 4.5kHz o/n 1906 **£2.95** +12½% VAT P&P 35p.

## CASES

**TEAK 30** designed mainly for use with our stereo 30 Audio System but has proved very helpful to home constructors. Fitted with solid uncut front and back o/n 139 **£6.45** +12½% VAT P&P 70p.

**TEAK 60** for use with AL60/MK60 Audio Kit. Useful for the home constructor requiring an amplifier sleeve — has no front or back panel o/n 140 **£7.00** +12½% VAT P&P 85p.

## METERS

**Miniature Balance & Tuning Meter**  
Miniature moving-coil meter for stereo balance indicator, tuning indicator for FM or similar application. Pointer at centre indicates zero or null position. Robust construction. Sensitivity 100-0-100mA. Dimensions: 23x22x26mm. o/n 1318. **£1.95** +8% VAT P&P 35p.



**Balance and Tuning Meter**  
Clear view edgewise meter. Centre zero application. Sensitivity 100-0-100mA. Dimensions: 45x22x34mm. o/n 1319. **£2.00** +8% VAT P&P 35p.



**Miniature Level Meter**  
Moving coil, for accurate level indication for tape recorders, amplifiers, etc. Neat design, rugged construction — will withstand five times rated value. Sensitivity: FSD: 200uA, 0dB; 130uA. Dimensions: 23x22x26mm. o/n 1320. **£2.80** +8% VAT P&P 35p.



**VU Meter**  
Calibrated — 20 to +3 and 0-100%: making it suitable for use as a recording level meter or as a power output indicator. Sensitivity: 130uA. Dimensions: 40x40x29mm. o/n 1321. **£2.00** +8% VAT P&P 35p.



## MICROPHONES

### DYNAMIC CASSETTE

For equipment requiring a high quality microphone. Sturdy, solid moulded body in black with neat chrome surround. Pick-up pattern is omnidirectional. On/off switch. 1 metre of tough lead with floating 2.5 and 3.5mm plugs. Matching moulded strut. Impedance: 200ohms. Sensitivity: 90dB. Frequency: 90-10,000Hz. Size: 20mm dia. x 120mm. o/n 1326. **£1.50** +12½% VAT P&P 35p.

### DYNAMIC MICROPHONE

Superior quality portable cassette recorder mike with built-in remote control switch and lead fitted with 5-pin 240° DIN plug (remote switch) and 3-pin DIN plug (microphone). Provides a direct replacement for those supplied with recorders. With detachable stand. Omnidirectional. Impedance: 200ohms. Freq. response: 100 to 10,000Hz. Sensitivity: 79dB at 1,000Hz. o/n 1327. **£2.65** +12½% VAT P&P 35p.

### RE-317: DYNAMIC MICROPHONE

Highly sensitive, high-grade desk or hand mike suitable for use with many popular cassette decks. Incorporates on/off switch and 1 metre lead with moulded standard jack plug. Complete with desk stand. Omnidirectional. Impedance: 5,000ohms. Freq. response: 100 to 12,000Hz. Sensitivity: (-7dB at 1,000Hz) o/n 1336. **£4.10** +12½% VAT P&P 35p.

### OMNIDIRECTIONAL CARDIOID

Powered by a 1½ volt battery located within the aluminium body. Satin silver finish with front disk protection to the diaphragm housing. On/off switch. Also with 'Buxby' type windshield, 'U' bracket and stem and extremely supple cable. Consumption: 0.2mA from 1½V battery providing approx. 8-10,000 hours continuous life. Impedance: 600ohms. Sensitivity: 70dB. Frequency: 30-16,000Hz. Size: 23mm dia. x 267mm. o/n 1329. **£12.80** +12½% VAT P&P 35p.

### UNIDIRECTIONAL CARDIOID

Dual imp. 600 and 50,000ohms. Response 50 to 14,000Hz. Sensitivity: 54dB at 50K/ohms. Size: 1½" dia. x 6½" long. Weight approx. 190gm. o/n 1328. **£10.95** +12½% VAT P&P 35p.

## STANDS

### GOOSENECK CHROME FLEXIBLE HOLDERS

Length 320mm. o/n 1333. **£2.40** +12½% VAT P&P 30p.  
Length 515mm. o/n 1334. **£3.40** +12½% VAT P&P 30p.  
**FLOOR STAND**, Heavy chrome. Slow-away feet with rubber ends for maximum stability. Draws to a height of 5' maximum. o/n 1335. **£9.00** +12½% VAT P&P 85p.  
**BOOM ARM** for use with the above stand. Heavy chromed metal, it gives 30" reach from the stand. o/n 1337. **£8.00** +12½% VAT P&P 70p.

### WINDSHIELD COVERS

O/n 1531. Medium per pair **£1.20** +12½% VAT P&P 35p. o/n 1332. Large per pair **£1.80** +12½% VAT P&P 35p.

## AUDIO LEADS

- 107 FM Indoor Ribbon Aerial **£0.60\***
- 113 3.5mm Jack plug to 3.5mm jack plug. Length 1.5m **£0.75\***
- 114 5 pin DIN plug to 3.5mm Jack connected to pins 3 & 5. Length 1.5m **£0.85\***
- 115 5 pin DIN plug to 3.5mm Jack connected to pins 1 & 4. Length 1.5m **£0.85\***
- 116 Car aerial extension. Screened insulated lead. Fitted plug & socket **£1.10\***
- 117 AC mains connecting lead for cassette recorders & radios. 2 metres **£0.68\***
- 118 5 pin DIN phono plug to stereo headphone jack socket **£1.05\***
- 119 2 + 2 pin DIN plugs to stereo jack socket with attenuation network for stereo headphones. Length 0.2m **£0.90\***
- 120 Car stereo connector. Variable geometry plug to fit most car cassette, 8 track cartridge & combination units. Supplied with in-line fused power lead and instructions **£0.60\***
- 123 6.8m Coiled Guitar Lead Mono Jack Plug to Mono Jack Plug BLACK **£1.50\***
- 124 3 pin DIN plug to 3 pin DIN plug. Length 1.5m **£0.75\***
- 125 5 pin DIN plug to 5 pin DIN plug. Length 1.5m **£0.75\***
- 126 5 pin DIN plug to Tinned open end. Length 1.5m **£0.75\***
- 127 5 pin DIN plug to 4 Phono Plugs. All colour coded. Length 1.5m **£1.30\***
- 128 5 pin DIN plug to 5 pin DIN socket. Length 1.5m **£0.80\***
- 129 5 pin DIN plug to 5 pin DIN plug mirror image. Length 1.5m **£1.05\***
- 130 2 pin DIN plug to 2 pin DIN in-line socket. Length 5m **£0.68\***
- 131 5 pin DIN plug to 3 pin DIN plug. 1 & 4 and 3 & 5. Length 1.5m **£0.83\***
- 132 2 pin DIN plug to 2 pin DIN socket. Length 10m **£0.98\***
- 133 5 pin DIN plug to 2 phono plugs. Connected pins 3 & 5. Length 1.5m **£0.75\***
- 134 5 pin DIN plug to 2 phono sockets. Connected pins 3 & 5. Length 23cm. **£0.68\***
- 135 5 pin DIN socket to 2 phono plugs. Connected pins 3 & 5. Length 23cm. **£0.68\***
- 136 Coiled stereo headphone extension lead. Black. Length 6m **£1.75\***
- 178 A.C. mains lead for calculators, etc. **£0.45\***

# BI-PAK

DEPT. ET11, P.O. Box 6, Ware, Herts.

# AUDIO KITS OF DISTINCTION FROM **POWERTRAN**




cabinet size 18.3" x 12.7" x 3.1".

## DE LUXE EASY TO BUILD LINSLEY-HOOD 75W AMPLIFIER £99.30 + VAT

This easy to build version of our world-wide acclaimed 75W amplifier kit based upon circuit boards interconnected with gold plated contacts resulting in minimal wiring and construction delightfully straightforward. The design was published in Hi-Fi News and Record Review and features include rumble filter, variable scratch filter, versatile tone controls and tape monitoring whilst distortion is less than 0.01%
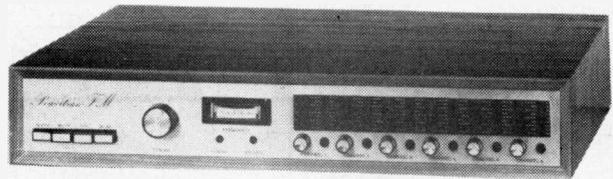
## WIRELESS WORLD FM TUNER £70.20 + VAT

A pre-aligned front-end module makes this Wireless World published design very simple to construct and adjust without special instruments. Features include an excellent a.m. rejection, push-button station selection as well as infinitely variable tuning and a phase locked loop stereo decoder incorporating active filters for "birdy" suppression.



cabinet size 18.3" x 12.7" x 3.1".




cabinet size 18.3" x 12.7" x 3.1".

## LINSLEY-HOOD CASSETTE DECK £79.60 + VAT

This design, published in Wireless World, although straightforward and relatively low cost provides a very high standard of performance. There are separate record and replay amplifiers and switchable equalisation together with a choice of bias levels are also provided. The mechanism is the Goldring-Lenco CRV with electronic speed control
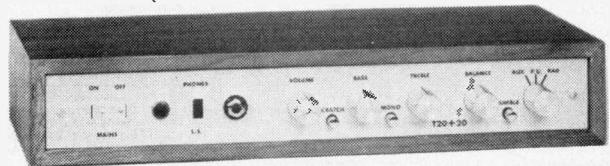
## T20 + 20 AMPLIFIER £33.10 + VAT

This kit, based upon a design published in Practical Wireless, uses a single printed circuit board and offers at very low cost, ease of construction and all the normal facilities found on quality amplifiers. A 30 watt version of this kit (T30 + 30) is also available for £38.40 + VAT.



cabinet size 15.5" x 6.7" x 2.8".




cabinet size 15.5" x 6.7" x 2.8".

## WWII TUNER £47.70 + VAT

This cost reduced model of our highly successful Wireless World FM Tuner kit was designed to complement the T20 + 20 and T30 + 30 amplifiers and the cabinet size, front panel format and electrical characteristics make this tuner compatible with either. Facilities included are pre-aligned front-end module, switchable afc, adjustable switchable muting, LED tuning indication and both continuous and push-button channel selection (adjustable by controls on the front panel).
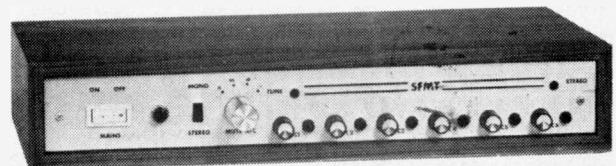
## POWERTRAN SFMT TUNER £35.90 + VAT

This is a simple low cost design which can be constructed easily without special alignment equipment but which still gives a first-class output suitable for feeding any of our very popular amplifiers or any other high quality audio equipment. A phase-locked-loop is used for stereo decoding and controls include switchable afc, switchable muting and push-button channel selection (adjustable by controls on the front panel). This unit matches well with the T20 + 20 and T30 + 30 amplifiers.



cabinet size 15.5" x 6.7" x 2.8".

**COMPLETE KITS:** Our complete kits really are complete. All of the projects shown on this page are supplied with fully finished metalwork, ready assembled high quality teak veneer cabinet, cables, nuts, bolts, etc., and full instructions — in fact everything!

All of the kits shown on this page are available as separate packs (except the Powertran SFMT Tuner) for those customers who wish to spread their purchase or perhaps make their own cabinets or metalwork. Prices are given in our FREE CATALOGUE.

**PRICE STABILITY:** Order with confidence! Irrespective of any price changes. We will honour all prices in this advertisement until February 28th, 1979. If ETI January, 1979 issue is mentioned with your order. Errors and VAT rate changes excluded.

**EXPORT ORDERS:** No VAT. Postage charged at actual cost plus 50p handling and documentation.

**U.K. ORDERS:** Subject to 12½% surcharge for VAT\* (i.e. add ½ to the price). No charge is made for carrier, \*or at current rate if changed.

**SECURICOR DELIVERY:** For this optional service (U.K. mainland only) add £2.50 (VAT inclusive) per kit.

**SALES COUNTER:** If you prefer to collect your kit from the factory. Call at Sales Counter (at rear of factory). Open 9 a.m. - 4.30 p.m. Monday-Thursday

OUR CATALOGUE IS FREE! WRITE OR PHONE NOW!

# POWERTRAN ELECTRONICS

PORTWAY INDUSTRIAL ESTATE  
ANDOVER HANTS SP10 3NM

ANDOVER  
(0264) 64455

# news digest.....


## FLEET OF FOOT?



For all us kiddies (anyone who isn't — please leave now) this is a good idea. Those nasty sneaky MPUs have invaded our nice little game of Battleships. Based on a TMS 1000 the unit contains enough

RAM to hold the board as seen by both players, and make appropriate noises at time of defeat or victory or whatever. Nice explosion sound effects etc too. And what's more it's British designed — which

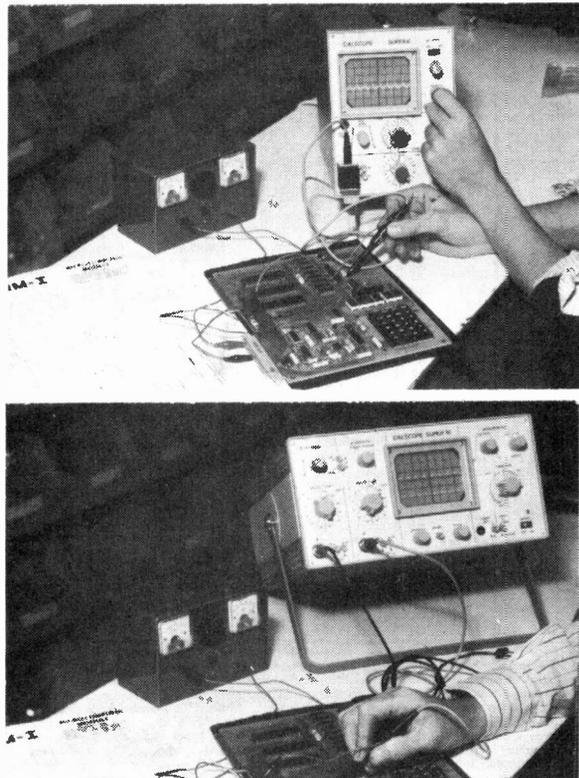is a distinct recommendation and selling well in America — which isn't. Price £29 or thereabouts. AID, 10 RATHBONE PLACE, LONDON W1P 2DN.



## NOT A TRACE OF GREED

Two new oscilloscopes for the home constructor, from the Scopex stable. Called the Calscope 6 and Calscope 10 they are probably indicative of the fact the home market is of growing importance to manufacturers. Specs. below.


**Calscope 6:** — single trace: sensitivity range 50mV to 50V per cm/in 12 ranges: Bandwidth 6MHz: time base range 1 and to 100 ms per cm. Time base triggering is claimed to be particularly good. Price £162.

**Calscope 10:** — dual trace: 10mV sensitivity: bandwidth 10MHz (displayable across full screen size): time base range 200ns to 100 ms: accuracy 3% all ranges. Price £219.

Both available from Maplin and Marshall both of whom you should know already.
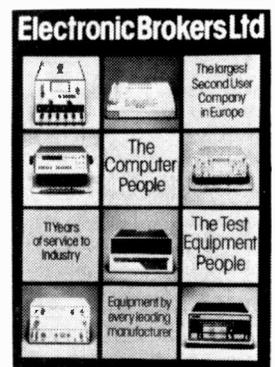
## PEDIGREE CATS

**Electronic Brokers** — superb range of second hand hardware that should interest most small firms and not a few individuals. Much new equipment is also included, and although the cost is high at £1 to private individuals companies can get it free!



Not fair this world is it? ELECTRONIC BROKERS, 4a PANCRAS ROAD, LONDON NW1 2GB.

**Ace Electronics** — good range of components. Poorly produced catalogue but it is free, and adequate, and contains some nice little kits amongst other things worth sending for. ACE MAILTRONIX, TOOTAL STREET, WAKEFIELD, W. YORKS.

## PUT THESE TO GOOD USE

Some new PUTs (at last), and in different packages too. The MEU21 and 2N6028 are intended for use in long internal timers and such and have low leakage (100nA max).

The MEU22 (and 2N6027) are general purpose types. All have specs of: 150nA peak point current (2N6028), low forward voltage (1V5 for 50mA  $I_{FWD}$ ) and high pulse output voltage (6V minimum) MICRO ELECTRONICS LTD, YORK HOUSE, EMPIRE WAY, WEMBLEY, MIDDX.

# ambit international <sup>®</sup>

Production of the new catalogue has been held up for a few weeks - since we have just been appointed as distributors for two of the most exciting ranges of radio-components products yet: The Micrometals range of iron dust torroids cores and formers, and the OKI range of VLSI for digital frequency displays for receivers. We apologize for any inconvenience, but these two ranges are really worth the wait, and include some products you will find hard to believe, like the MSM5523 IC, an IC with less than ten external components that gives AM frequency readout to 1kHz from LW to 39.999MHz, FM frequency readout in 100kHz steps - (all usual IF offsets programmable by diodes), a 24 hour format clock with 12 hour display, independent on and off timers, time signals on the hours, stopwatch facility and a sleep timer. This costs £14 with its timebase crystal, and makes all that has gone before an expensive and time wasting exercise. Rather like the way the Intersil ICM7216 has revolutionized the instrument counter market. (See the OSTs ad.) And those of you familiar with Amidon and IG dust torroids, favoured in many new RF designs, will be pleased to know Ambit will be stocking a broad range of the Micrometals types for applications from EMI filters to RF PA stages.

DKI frequency counter ICs: details in cat2  
MSM5523 for CA LEDs with RHPD such as FND507 £14 inc xtal  
MSM5525 for 3 1/2 digit LCD AM/FM with direct segment drive, no clock or timers £11 inc xtal  
Other types for fluorescent displays etc OA

Other new semiconductor additions:  
KB4437 pilot cancel mpw decoder 4.35  
KB4438 muting stereo preamp 2.22  
HA1370 supercedes TDA2020 2.99  
TDA1090 HiFi AM/FM 3.35  
TDA1220 low cost AM/FM 1.45

PRICES DOWN ON VMOS: as expected, this new technology in power transistor is getting cheaper. 120V comp pair /100W for £10.00  
Price reduction on CA3189E .....now £2.20  
New varicaps: to add to the biggest range.....  
KV1211 2.9v bias to tune MW, like the KV1210, but a double diode £1.75

New pilot tone filters from TOKO.....  
2068LR series, individual per channel with a 2673kHz version for pilot cancel decoder applications. Flat to 15kHz £0.90  
New crystal filter for amateur NB-FM.....  
TOYD 10M4B1 with over 90dB adjacent ch. rejection for 2m NB-FM, 10.7MHz £14

New ceramic IF filters for 455kHz.....  
CFM455H 6kHz/6dB, 15kHz max /60dB - ideal for MC3357 etc. £10.

A brief summary of some of our range of ICs:  
TDA1062/1.95; TDA1083/1.95; HA1197/£1.40  
CA3123E/£1.40; TB6651/£1.81; CA3089/1.94  
HA1137/£2.20; MC1310/£2.20; HA1196/£3.95  
KB4424/£2.75; KB4423/£2.53; SD6000/£3.75  
KB4412/£2.55; KB4413/£2.75; KB4417/£2.55  
MC1495L/£6.86\*; MC1496P/£1.25  
LM381N/£1.81; LM1303/£0.99; ULN2283B/£1.00; LM380N/£1; TB810AS/£1.09  
TCA940E/£1.80; TDA2002/£1.95;  
ICL2038C/£4.50\*; NE568/£2.50\*; NE567/£2.50\*; NE560B/£3.50; NE561B/£3.50;  
NE562B/£3.50\*; NE565A/£2.50\*

SEE THE OSTs ADVERT FOR CMOS/TTL REGULATORS, OPTO DISPLAYS, and other types of linear devices.

Some transistors for RF specifically:  
BF256LB/0.34; 40822/0.43\*; 40823/0.51\*  
40673/0.55\*; BF900/961/0.80\*; BF960A/60\*  
BF24/0.22; BF274/0.18; BF195/0.18;  
BF240/0.22; BF241/0.22; BF362/0.70;  
BF479/0.86; BF679S/0.70; BF790/0.90\*

Pin and other Varicap diodes:  
BA102/0.30; BA121/0.30; ITT210/0.30  
BB104B/0.40; MVAM2/£1.48; MVAM115/£1.05; MVAM125/1.05; KV1210/£2.75  
BA479/0.35; TDA1061/0.95; BA182/0.21  
METER MADE low cost panel meters:  
3 x 930 series with blanks and dry transfer sheet of scales and legends for £12.5

## At last, DIY HiFi which looks as if it isn't.


That's not to say it doesn't look like HiFi - just that it doesn't look like the usual sort of thing you have come to associate with DIY HiFi. The Mk3 outstrips and outperforms all British made HiFi tuners, and most imported ones too. Certainly at the price, there isn't one near it. But more than that, it looks superb. A small pic here would be an insult, so send an SAE for details on the kit that looks as if it isn't. It's something else.....

- \* Exceptionally high performance - exceptionally straightforward assembly
- \* Baseboard and plug-in construction. Future circuit developments will readily plug in, to keep the MkIII at the forefront of technical achievement
- \* Various options and module line-ups possible to enable an installment approach to the system

and now previewing the matching 60W/channel VMOS amplifier:

- \* Matching both the style and design concepts of the MkIII HiFi FM tuner
- \* Hitachi VMOS power fets - characterized especially for HiFi applications
- \* Power output readily multiplied by the addition of further MOSFETs
- \* VU meters on the preamp - not simply dancing according to vol level
- \* Backed with the usual Ambit expertise and technical capacity in audio
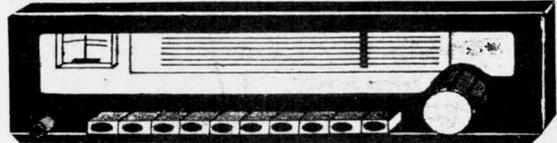
## The PW Dorchester-LW, MW, SW, & FM stereo tuner



In much the same way as we have swept away the 'old technology' in frequency/timer counters - with the OKI and Intersil single IC counters, we now offer a single IC 'All Band' radio tuner. Don't confuse this one chip radio with things like the ZN414 - for this is a genuine superhet receiver with a mechanical AM IF filter, and ceramic IF filters for FM. The AM section employs a balanced input mixer section, covering all broadcast bands - plus a BFO and MOSFET product detector for SSB/CW - though at this price, the tuner is not intended as a "communications receiver" - although we know of many lesser designs that make that claim. The AM sensitivity is nevertheless better than 5uV, and FM sensitivity is 1.2uV for 30dB S/N. As a multiband broadcast superhet receiver, it is a unique constructor project that fulfills the requests we very frequently get for a general coverage circuit that isn't over complicated. The set has CA3089E FM performance, with mute etc., and a PLL stereo decoder with full pilot tone filtering. The tuner board - with "on board" PCB mounted switching, all components etc : £33.00  
The case/cabinet with PSU, meter and mechanics etc £25.00  
An SAE for full details please. See the feature article in Practical Wireless (Dec/Jan)

TERMS etc: CWO please, VAT on Ambit items is generally 12%, except where marked (\*).  
Catalogue part 1:45p, part 2:50p all inclusive. Postage 25p per order, carriage on tuner kits £3.  
Phone Brentwood (0277) 216029/227050 9am-7pm. Callers welcome inc. Saturdays.

2 Gresham Road, Brentwood, Essex.

## OSTS

Since AMBIT introduced the "One Stop Technology Shop" to our service, we have been pleased to see just how many users of electronic components appreciate our guarantee to supply goods only from BS9000 approved sources. More than ever, professional and amateur electronics engineers cannot afford to waste time on anything less than perfect pedigree products.

## CD4000 CMOS

|      |      |      |      |      |      |
|------|------|------|------|------|------|
| 4000 | 17p  | 4059 | 563p | 4522 | 149p |
| 4001 | 17p  | 4060 | 115p | 4527 | 157p |
| 4002 | 17p  | 4063 | 109p | 4528 | 102p |
| 4006 | 109p | 4056 | 53p  | 4529 | 141p |
| 4007 | 18p  | 4057 | 40p  | 4530 | 90p  |
| 4008 | 80p  | 4068 | 25p  | 4531 | 141p |
| 4009 | 58p  | 4069 | 20p  | 4532 | 125p |
| 4010 | 58p  | 4070 | 20p  | 4534 | 614p |
| 4011 | 17p  | 4071 | 20p  | 4536 | 380p |
| 4012 | 17p  | 4072 | 20p  | 4538 | 150p |
| 4013 | 56p  | 4073 | 20p  | 4539 | 110p |
| 4016 | 52p  | 4075 | 20p  | 4541 | 141p |
| 4017 | 80p  | 4076 | 90p  | 4543 | 174p |
| 4018 | 80p  | 4077 | 20p  | 4549 | 399p |
| 4019 | 80p  | 4078 | 20p  | 4553 | 440p |
| 4020 | 93p  | 4081 | 20p  | 4554 | 153p |
| 4021 | 82p  | 4082 | 20p  | 4556 | 77p  |
| 4022 | 90p  | 4085 | 82p  | 4557 | 386p |
| 4023 | 17p  | 4086 | 82p  | 4558 | 117p |
| 4024 | 76p  | 4089 | 150p | 4559 | 388p |
| 4025 | 17p  | 4093 | 50p  | 4560 | 218p |
| 4026 | 180p | 4094 | 190p | 4561 | 65p  |
| 4027 | 55p  | 4096 | 105p | 4562 | 530p |
| 4028 | 72p  | 4097 | 372p | 4566 | 159p |
| 4029 | 100p | 4098 | 110p | 4568 | 281p |
| 4030 | 58p  | 4099 | 122p | 4569 | 303p |
| 4031 | 250p | 4160 | 90p  | 4572 | 25p  |
| 4032 | 100p | 4161 | 90p  | 4580 | 600p |
| 4033 | 145p | 4162 | 90p  | 4581 | 319p |
| 4034 | 200p | 4163 | 90p  | 4582 | 164p |
| 4035 | 120p | 4174 | 104p | 4583 | 84p  |
| 4036 | 250p | 4175 | 95p  | 4584 | 63p  |
| 4037 | 100p | 4194 | 95p  | 4585 | 100p |
| 4038 | 105p | 4501 | 23p  |      |      |
| 4039 | 250p | 4502 | 91p  |      |      |
| 4040 | 83p  | 4503 | 69p  |      |      |
| 4041 | 90p  | 4506 | 51p  |      |      |
| 4042 | 85p  | 4507 | 55p  |      |      |
| 4043 | 85p  | 4508 | 248p |      |      |
| 4044 | 80p  | 4510 | 99p  |      |      |
| 4045 | 150p | 4511 | 149p |      |      |
| 4046 | 130p | 4512 | 98p  |      |      |
| 4047 | 99p  | 4513 | 203p |      |      |
| 4048 | 60p  | 4514 | 260p |      |      |
| 4049 | 55p  | 4515 | 300p |      |      |
| 4050 | 55p  | 4516 | 125p |      |      |
| 4051 | 65p  | 4517 | 382p |      |      |
| 4052 | 65p  | 4518 | 103p |      |      |
| 4053 | 65p  | 4519 | 57p  |      |      |
| 4054 | 120p | 4520 | 108p |      |      |
| 4055 | 135p | 4521 | 236p |      |      |

## Micromarket

|             |      |      |        |
|-------------|------|------|--------|
| 8216        | 1.95 | 2114 | £10    |
| 8224        | 3.50 | 2708 | £10.55 |
| 6800P       | 6.50 |      |        |
| 6820P       | £6   |      |        |
| 6850P       | 2.75 |      |        |
| 6810P       | £4   |      |        |
| 6852        | 3.65 |      |        |
| 8080 series |      |      |        |
| 8080        | 6.30 |      |        |
| 8212        | 2.30 |      |        |

## Voltage Regs

NEW LOW PRICES  
7800 series UC TO220 package 1A all 95p  
7900 series UC TO220 package 1A all 91p  
78MUC series TO220 package 1/2A all 90p  
78LCP series TO92 100mA all 35p  
L200 up to 3A/adjustable V&A 195p  
78MGT2C 1/2amp adjustable volts 175p  
79MGT2C 1/2amp adjustable volts 175p  
723C precision controller 65p  
MAINS FILTERS FOR NOISE/RFI etc.  
1 amp in IEC connector £4.83  
5 amp in 'wire in' case £3.87  
NE550A 73p

## LINEARS non-consumer OPTO 7 seg displays


|         |      |         |         |                           |
|---------|------|---------|---------|---------------------------|
| CA3130E | 84p  | LM339N  | 66p     | 0.43" High Efficiency HP: |
| CA3130T | 90p  | LM348N  | 186p    | 5082: 7650 red CA         |
| CA3140E | 35p  | LM3900N | 60p     | 5082: 7653 red CC         |
| CA3140T | 72p  | 709HC   | 105 64p | 5082: 7650 yellow CA      |
| CA3160E | 90p  | 709PC   | 105 36p | 5082: 7663 yellow CC      |
| CA3160T | 99p  | 710HC   | 105 65p | 5082: 7670 green CA       |
|         |      | 710PC   | 105 59p | 5082: 7673 green CC       |
| Op amps |      | 723CN   | 65p     | 0.3" Standard HP          |
| LM301AH | 67p  | 741CH   | 105 66p | 5082: 7730 red CA         |
| LM301AN | 30p  | 741CN   | 84d 27p | 5082: 7740 red CC         |
| LM308H  | 121p | 747CN   | 70p     |                           |
| LM308N  | 97p  | 748CN   | 36p     |                           |
| LM318H  | 279p | NE531T  | 120p    | 0.5" Fairchild            |
| LM318N  | 224p | NE531N  | 105p    | FND500 red CC 150p        |
|         |      |         |         | FND507 red CA 150p        |

## TTL: Standard AND LP Schottky

| N'   | LSN' | N'    | LSN'  | N'  | LSN'  | N'    | LSN' | LSN   |       |     |               |                  |         |
|------|------|-------|-------|-----|-------|-------|------|-------|-------|-----|---------------|------------------|---------|
| 7400 | 13   | 20    | 7455  | 35  | 24    | 74126 | 57   | 44    | 74185 | 134 | 74377         | 124              |         |
| 7401 | 13   | 20    | 7460  | 17  |       | 74128 | 74   |       | 74188 | 275 | 74378         | 93               |         |
| 7402 | 14   | 20    | 7463  |     |       | 74132 | 73   | 78    | 74190 | 115 | 92            | 74379            | 130     |
| 7403 | 14   | 20    | 7470  | 28  |       | 74133 |      | 29    | 74191 |     |               | 74386            | 37      |
| 7404 | 14   | 24    | 7472  | 28  |       | 74136 |      | 40    | 74192 | 105 | 180           | 74390            | 140     |
| 7405 | 18   | 26    | 7473  | 32  |       | 74138 |      | 60    | 74193 | 105 | 180           | 74395            | 139     |
| 7406 | 38   |       | 7474  | 27  | 38    | 74139 |      | 60    | 74194 | 105 | 187           | 74396            | 133     |
| 7407 | 38   |       | 7475  | 38  | 40    | 74141 | 56   |       | 74195 | 95  | 137           | 74398            | 180     |
| 7408 | 17   | 24    | 7476  | 37  |       | 74142 | 265  |       | 74196 | 99  | 110           | 74399            | 150     |
| 7409 | 17   | 24    | 7478  |     |       | 74143 | 312  |       | 74197 | 85  | 110           | 74445            | 92      |
| 7410 | 15   | 24    | 7480  | 48  |       | 74144 | 312  |       | 74198 | 150 |               | 74447            | 90      |
| 7411 | 20   | 24    | 7481  | 86  |       | 74145 | 65   |       | 74199 | 160 |               | 74490            | 140     |
| 7412 | 17   | 24    | 7482  | 69  |       | 74147 | 175  |       | 74248 |     | 90            | 74668            | 110     |
| 7413 | 30   | 52    | 7483A |     |       | 74148 | 109  |       | 74249 |     | 93            | 74670            | 249     |
| 7414 | 51   | 130   | 7484  | 97  |       | 74150 | 99   |       | 74251 | 90  |               | MISCELLANY       |         |
| 7415 | 30   | 24    | 7485  | 104 | 99    | 74151 | 64   | 84    | 74253 | 105 |               | NE555            | 30p     |
| 7416 | 30   | 7486  | 64    | 40  | 74153 | 64    | 54   | 74257 | 108   |     | NE556         | 78p              |         |
| 7417 | 30   | 7489  | 205   |     | 74154 | 96    |      | 74258 | 420   |     | NE558         | 180p             |         |
| 7420 | 16   | 24    | 7490  | 33  | 90    | 74155 | 54   | 110   | 74259 | 420 |               | ICM7217          | 950p    |
| 7421 | 29   | 24    | 7491  | 76  | 110   | 74156 | 80   | 110   | 74260 | 153 |               | ICM7208          | 1495p   |
| 7422 | 24   | 24    | 7492  | 38  | 78    | 74157 | 67   | 55    | 74261 | 353 |               | ICL7106CP        | 140p    |
| 7423 | 27   | 24    | 7493  | 32  | 99    | 74158 | 67   | 60    | 74266 | 40  |               | LCD DVM IC       |         |
| 7425 | 27   | 24    | 7494  | 78  |       | 74159 | 210  |       | 74273 | 124 |               | LCD              | 955p    |
| 7426 | 36   | 27    | 7495A | 65  | 99    | 74160 | 82   | 130   | 74275 | 312 |               | LCD DVM KIT      |         |
| 7427 | 27   | 29    | 7496  | 58  | 120   | 74161 | 92   | 78    | 74279 | 52  |               | 2480p            |         |
| 7428 | 35   | 32    | 7497  | 195 |       | 74162 | 92   | 130   | 74283 | 120 |               | 3 1/2 digit LCD  |         |
| 7430 | 17   | 24    | 74100 | 119 |       | 74163 | 92   | 78    | 74290 | 90  |               | display          | 1150p   |
| 7432 | 25   | 24    | 74104 | 63  |       | 74164 | 104  |       | 74293 | 95  |               | ICL7107 LCD      |         |
| 7433 | 40   | 32    | 74105 | 62  |       | 74165 | 105  |       | 74295 | 120 |               | DVM kit          | 2065p   |
| 7437 | 40   | 24    | 74107 | 32  | 38    | 74166 |      |       | 74298 | 100 |               | ICM7218          | 8 digit |
| 7438 | 33   | 24    | 74109 | 63  | 38    | 74167 | 20   |       | 74324 | 157 |               | 10MHz DFM/       |         |
| 7440 | 17   | 24    | 74110 | 54  |       | 74168 |      |       | 74325 | 242 |               | timer            | £19.82  |
| 7441 | 74   | 24    | 74111 | 68  |       | 74169 |      | 200   | 74326 | 247 |               | (for LED C.Cath) |         |
| 7442 | 70   | 99    | 74112 | 88  |       | 74170 | 230  | 200   | 74327 | 237 |               | SCALAR ICs       |         |
| 7443 | 115  | 74113 |       |     | 74172 | 625   |      | 74332 | 100   |     | 8629 150MHz   |                  |         |
| 7444 | 112  | 74114 |       |     | 74173 | 170   |      | 74335 | 100   |     | divide by 100 |                  |         |
| 7445 | 94   | 74116 | 198   |     | 74174 | 87    | 120  | 74362 | 715   |     | 420p          |                  |         |
| 7446 | 94   | 74118 | 83    |     | 74175 | 87    | 110  | 74365 | 49    |     | 95H90DC       | 750p             |         |
| 7447 | 82   | 74119 | 119   |     | 74176 | 75    |      | 74366 | 49    |     | 11C90DC       | 440p             |         |
| 7448 | 56   | 99    | 74120 | 115 |       | 74177 | 78   |       | 74367 | 43  |               | new-divide       |         |
| 7449 | 97   | 99    | 74121 | 25  |       | 74180 | 85   |       | 74368 | 49  |               | by 100 or 10     |         |
| 7450 | 17   | 24    | 74122 | 46  |       | 74181 | 165  | 350   | 74373 | 77  |               | for 120/60MHz    |         |
| 7451 |      |       |       |     |       |       |      |       |       |     |               |                  |         |

# ..... news digest.....

## PROM-IN-AID TIME

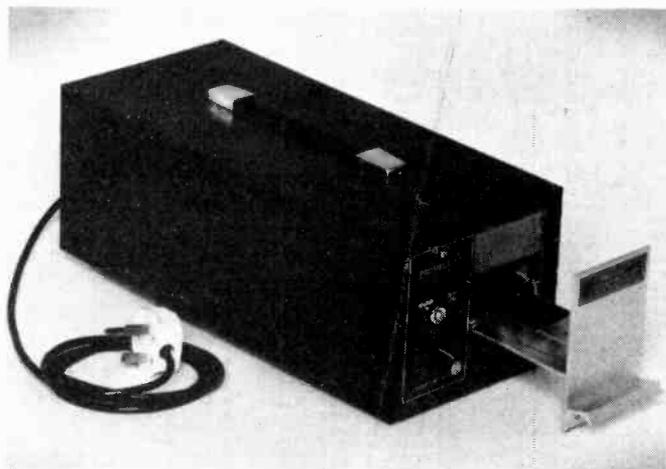

Micro-men take note. The Prombix 12 can wipe out twelve PROMs at once with variable erase time with safety interlock. Priced at £59.00 all inc. Should be of interest to

small firms and rich enthusiasts. GP INDUSTRIAL ELECTRONICS, SKARDON WORKS, SKARDON PLACE, NORTH HILL, PLYMOUTH PL4 8EZ.

## GETTING INTO PRINT



A low cost printer is announced by Kimberley Business Records giving a low cost printer is announced by Kimberley Business Records giving good quality output. This will allow the expansion of many home systems into the extensive field of word processing, and God help you then! A standard lever operated typewriter mechanism has been used, driven by 240V solenoids.

Designed for parallel data input with handshake control, ASCII coding is

accepted for the 88 characters available operating at a speed of 8 CAPS from a standard peripheral interface. It is supplied fully built and cased at £200 (including carriage and VAT). Alternatively as a print mechanism only, requiring all power other than 240V, case, and TTL logic to be added, the cost is £160.

KIMBERLEY BUSINESS RECORDS, 2, HARTINGTON ROAD, GOSPORT, HANTS. PO12 3AG.

# Catronics for

## SOLID STATE R.T.T.Y.

We can supply Printed Circuit Boards and components for the RTTY Video Display published by G3PLX in "Radio Communication".

This video display unit is designed to be an all-electronic replacement for a Teleprinter, and therefore does not suffer its disadvantages — bulk, unreliability and noise. The basic function is to take Murray Code — either from a Terminal Unit (on receive) or from a Keyboard — and produce a complete TV signal. This signal may be fed into a monitor or modulated and fed into the aerial of an ordinary domestic TV set. The resulting display is a page of 24 lines of up to 40 characters. It may also be used (with its keyboard) to send fully encoded Murray Code signals for transmit purposes.

Hundreds of these units have been built, with very little trouble, and the pleasures and fascination of RTTY operation are now being experienced by more and more amateurs. Listeners, too, find it very interesting to be able to read international news and other transmissions without the inconvenience of the mechanical teleprinter.

Kit price from £83.55 — send SAE for details.

Introducing the most comprehensive R.T.T.Y. TERMINAL UNIT you can, or indeed, need ever buy —

## THE CATRONICS CT100 R.T.T.Y. TERMINAL UNIT

### INPUTS for:

Audio FSK signal in  
Data in from V.D.U. (e.g. G3PLX)  
TTY Keyboard or Tape Reader

### OUTPUTS for:

V.D.U. or other TTL compatible equipment  
TTY Magnet — single or double current  
AFSK to drive Transmitter

Featuring a unique digitally controlled "Autoprint" circuit which is a superior replacement for the "Antispace" and "Autostart" facilities found on some other terminal units. The terminal will ignore most CW and phone signals but will respond to a correct RTTY signal. Tuning correctly into an RTTY signal is made simple with a single "correctly tuned" LED plus an additional "Mark frequency" indicator.

The FSK demodulator circuit utilises a special "state-of-the-art" system to give excellent performance and stability at low cost.

The teleprinter interface unit incorporates electronic "de-bounce" circuitry to eliminate spurious switching from the Keyboard.

### UNITS ARE AS FOLLOWS:

|  |        |
|--|--------|
| CT100. Receive only RTTY Terminal Unit housed in attractively styled metal cabinet approx 9 by 7 by 2 1/2 in., with integral mains power supply. | £71.00 |
| CT101. Receive Unit + Hi-stability AFSK oscillator for transmission purposes.  | £79.00 |
| CT102. Receive Unit + Teleprinter interface unit.  | £80.00 |
| CT103. Complete terminal unit for reception and transmission with facilities for connection to Teleprinter.                                      | £88.00 |

ADD £3 for Securicor delivery

## Catronics NEW KEYBOARD KIT

Catronics Ltd. are proud to announce the introduction of the world's first modular Keyboard Kit available to the home constructor!

The printed circuit board is designed to take a maximum of 70 keys but may be assembled with a smaller number of keys for a simpler keyboard.

The board is not dedicated to any specific coding, allowing it to be used for any project whether it requires ASCII, Baudot or any other code. This makes it suitable for many projects including

E.T.I. — System 68 MPU (54 keys)

Auto morse sender, etc.

The Keyswitches themselves are single pole push-to-make type and require no extra mechanical mounting arrangements

A legend sheet is provided with each kit enabling the constructor to label the keys to suit individual requirements.

Catronics price: Kit for 70 station Keyboard: £29.00

Please add 50p for post and packing

All prices INCLUDE VAT at current rates

Send SAE for FREE PRICE LIST or 45p and large (A4) 18 1/2p SAE for copy of our Data Catalogue.

**CATRONICS LTD.**  
**COMMUNICATIONS HOUSE**  
**20 WALLINGTON SQUARE**  
**WALLINGTON, SURREY SM6 8RG**

(DEPT.  
951)

Tel. 01-669 6700. Open Mon.-Fri. Also Sat. a.m.





**Introducing DM900 — The DIGITAL MULTIMETER with "Hidden Capacity" — It measures Capacitance too!**

(as published in E.T.I. August 1978)  
 Away with analogue meters for with some of these you may often as not use a crystal ball to make circuit measurements instead gaze into our crystal — not a ball but the 3 1/2 0.5" LIQUID CRYSTAL DISPLAY — on our amazingly accurate DMM incorporating

- 5 AC & DC Voltage ranges; 6 resistance ranges
- 5 AC & DC Current ranges; 4 Capacitance ranges
- The prototype accuracy is better than 1%

This is a unique design using the latest MOS ICs and due to the minimal current drain, is powered by only one PP3 battery. There is also a battery check facility.

The DM900 is an attractive hand-held, light weight device, built into a high impact case with carrying handle and has been ingeniously designed to simplify assembly.

Never before have all these features been offered to the electronics enthusiast in a single unit.

Complete Kit Only **£54.50\*** (p&p Insured add 80p)

Optional Extras Probes **£1.50\*** Carrying Case **£1.50\***

Calibration service charge for working Units only **£5.75.**

Ready-built and tested units only **£78.50\*** incl. Case & probes p&p 80p

Demonstration on at our Shop

| JACK PLUGS            | SOCKETS      |                  |                             | SWITCHES*        | SLIDE 250V         |
|-----------------------|--------------|------------------|-----------------------------|------------------|--------------------|
| Screened chrome       | Plastic body | open metal       | moulded with break contacts | in line couplers | 1A DPDT 14p        |
| 2.5mm 12p             | 8p           | 8p               | 11p                         | 11p              | 1A DPDT c/over 15p |
| 3.5mm 15p             | 10p          | 8p               | 12p                         | 12p              | 1/2A DPDT 13p      |
| MONO 23p              | 15p          | 13p              | 18p                         | 18p              | 4 pole 2 way 24p   |
| STEREO 31p            | 18p          | 15p              | 22p                         | 22p              | <b>PUSH BUTTON</b> |
|                       |              |                  |                             |                  | Spring loaded      |
|                       |              |                  |                             |                  | SPST on/off 60p    |
|                       |              |                  |                             |                  | SPDT c/over 85p    |
|                       |              |                  |                             |                  | <b>MINIATURE</b>   |
|                       |              |                  |                             |                  | Non Locking 70p    |
|                       |              |                  |                             |                  | Push to Make 15p   |
|                       |              |                  |                             |                  | Push Break 25p     |
| <b>DIN</b>            | <b>PLUGS</b> | <b>SOCKETS</b>   | <b>In Line</b>              |                  |                    |
| 2 PIN Loudspeaker 11p | 7p           | 7p               | 18p                         |                  |                    |
| 3, 4, 5 Audio 13p     | 8p           | 8p               | 20p                         |                  |                    |
| <b>CO-AXIAL (TV)</b>  | <b>14p</b>   | <b>14p</b>       | <b>14p</b>                  |                  |                    |
| <b>PHONO</b>          | <b>9p</b>    | <b>5p single</b> | <b>15p</b>                  |                  |                    |
| assorted colours 12p  | 8p double    |                  |                             |                  |                    |
| Metal screened 10p    | 3-way        |                  |                             |                  |                    |
| <b>BANANA</b> 4mm 11p | 12p          |                  |                             |                  |                    |
| 2mm 10p               | 10p          |                  |                             |                  |                    |
| 1mm 7p                | 7p           |                  |                             |                  |                    |
| <b>WANDER</b> 3mm 8p  | 8p           |                  |                             |                  |                    |
| DC Type 15p           | 20p          |                  |                             |                  |                    |
| AC 2-pin American 15p | 15p          |                  |                             |                  |                    |

**VOLTAGE\* REGULATORS**

T03 Can Type p

1A +ve 5V 12V 15V 18V 145

MVR5 or 12 150

1A -ve 5V 12V 220

Plastic (T092)

+ve 0.1A 5V 6V 8V 12V 15V 30

+ve 1A (T0220) 5V 12V 15V 18V 24V 85

-ve 0.5A 5V 6V 8V 12V 15V 86

-ve 1A 5V 12V 110

-ve 0.1A (T092) 5V 12V 15V 85

**TRANSFORMERS\*** (Mains Prim. 220-240V)

6-0-6V 100mA 9-0-9V 75mA 12-0-12V 100mA 95p

8VA: 6V-5A 6V-5A 9V-4A 9V-4A 12V-3A 12V-3A 15V-2.5A 15V-2.5A 195p

12V: 4.5V-1.3A 4.5V-1.3A 6V-1.2A 6V-1.2A 12V-5A 12V-5A 15V-4A 15V-4A 20V-3A 20V-3A 220p (20p p&p)

24VA: 6V-1.5A 6V-1.5A 9V-1.3A 9V-1.3A 12V-1A 12V-1A 15V-8A 15V-8A 20V-6A 20V-6A 290p (45p p&p)

50VA: 6V-4A 6V-4A 9V-2.5A 9V-2.5A 12V-2A 12V-2A 15V-1.5A 15V-1.5A 20V-1.2A 20V-1.2A 25V-1A 25V-1A 30V-8A 30V-8A 350p (50p p&p)

100VA: 12V-4A 12V-4A 15V-3A 15V-3A 20V-2.5A 20V-2.5A 30V-1.5A 30V-1.5A 40V-1.25A 40V-1.25A 50V-1A 50V-1A 650p (60p p&p)

**ALUM. BOXES\* WITH LID\***

3x2x1 45

2 1/2 x 5 1/4 x 1 1/2 60

4x4 1/2 68

4x2 3/4 x 1 1/2 60

4x5 1/4 x 1 1/2 78

4x2 1/2 x 2 64

5x4 2 82

6x4 2 88

7x5 2 114

8x6 3 148

10x7 3 172

10x4 1/2 x 3 142

12x5 3 165

12x8 3 210

**PANEL METERS\***

FSD 60x46x 35mm 0.50uA 0.100uA 0.500uA 0.1mA 0.5mA 0.10mA 0.50mA 0.100mA 0.500mA 0.1A 0.2A 0.25V 0.50V AC 0.300V AC 5VU 475p each

4 1/2 x 3 1/4 x 1 1/2 0.50uA 0.100uA 0.500uA 595p each

**EARPHONES**

Magnetic 2.5mm 18p

3.5mm 18p

Crystal 33p

**ULTRASONIC TRANS-DUCERS** £3.95\* per pair

**COMPUTER HARDWARE\***

2101 99

2102 100

2111 175

2114 650

2516 TBA

2532 TBA

2708 650

27L08 995

27L16 1650

3064 TBA

4027 190

4047 750

74S188 165

74S262 875

74S297 325

74S470 325

74S475 825

81LS95 70

81LS96 70

9900 £35

9980 TBA

1MS6011 TBA

280 TBA

**COMPUTER HARDWARE\***

2101 99

2102 100

2111 175

2114 650

2516 TBA

2532 TBA

2708 650

27L08 995

27L16 1650

3064 TBA

4027 190

4047 750

74S188 165

74S262 875

74S297 325

74S470 325

74S475 825

81LS95 70

81LS96 70

9900 £35

9980 TBA

1MS6011 TBA

280 TBA

**CMOS\***

4001 15

4001 17

4002 17

4006 105

4007 18

4008 87

4009 50

4010 50

4011 18

4012 18

4013 42

4014 86

4015 89

4016 45

4017 89

**CMOS\***

4001 15

4001 17

4002 17

4006 105

4007 18

4008 87

4009 50

4010 50

4011 18

4012 18

4013 42

4014 86

4015 89

4016 45

4017 89

**VDU Chip and MODULE for TV**

Convert your TV into a VDU by using the new Thompson CSF TV-CRT controller chip SF F96364 16 line by 64 characters text refreshment. Cursor management. Cursor management on screen. Line erasing. Compatible with any computing system.

SF F96364E £11.75\*

AV-3 1015 £5.60\*

AV-5 1013UART £4.50\*

71301 ROM £8.20\*

SF580102 RAM £2.05\*

74LS163 £1.18\*

SN75450 £1.20\*

SN75451 70p\*

SN75452 70p\*

SN75454 £2.25\*

UHF Modulator £2.50\*

Complete Module £136.50\*

(Send 30p stamps for full technical data)

# .....news digest.....



**POCKET ADVANTAGE**

A wallet type machine with hold-on memory. The new TI 50 has two memories, some scientific features, some statistical features and will turn itself off after 15 minutes if you aren't using it. Up to 15 levels of parenthesis are allowed. There is even a 'battery low' indicator.

Available now, it will cost under £30 and be in most shops that sell this sort of thing.

**SCREEN TEST**

The UK is now Hong Kongs largest market for TV games. We absorbed 26% of their export in the field, some 523,506 items if you please, in the first eight months of this year. Germany finished second

on 22% and the USA came third with 13%.

Somewhat of a surprise, and a shame, that we take more than the States of these items. I always thought we had more taste.

**SHORTS**

● Every Ready — now called Berec — have released four rechargeable consumer batteries, in the HP2, HP11, HP7 and PP3 varieties. Chargers are also available. An undoubted reaction to the phenomenal loss of dry cell power these days.

● Fairchild are making a big fuss about having their F16K Dynamic 16K RAMs available at last. Access times vary from 150 ns to 300 ns.

● Direct drive turntables yes. But direct drive MPUs? Also yes — now. The S2000 is a new release from AMI which can drive fluorescent displays directly, with HT drive and 7-segment decoding on chip. Also on board 64 x 4 RAM and 1K ROM. Intended for low lost applications.



● Ingersoll — the tick tock people — are into electronics. They have released three TV games, three clock radios, two Door Chimes, and a portable micro cassette player. Photo shows one of their new TV games. It must be Christmas.

|   |  |  |  |  |  |  |  |  |  |   |  |   |  |   |  |   |  |   |  |   |  |   |  |  |  |  |  |   |  |   |  |   |  |   |  |   |  |   |  |   |  |   |  |   |  |   |  |  |  |  |  |   |  |
|---|--|--|--|--|--|--|--|--|--|---|--|---|--|---|--|---|--|---|--|---|--|---|--|--|--|--|--|---|--|---|--|---|--|---|--|---|--|---|--|---|--|---|--|---|--|---|--|--|--|--|--|---|--|
| <b>TTLs by TEXAS</b><br>74186 700p<br>7400 13p<br>7401 13p<br>7402 14p<br>7403 14p<br>7404 17p<br>7450A 90p<br>7405 18p<br>7406 32p<br>7407 32p<br>7408 19p<br>7409 19p<br>7410 15p<br>7411 24p<br>7412 20p<br>7413 30p<br>7414 60p<br>7416 27p<br>7417 27p<br>7420 17p<br>7421 40p<br>7422 22p<br>7423 34p<br>7425 30p<br>7426 30p<br>7427 34p<br>7428 39p<br>7430 17p<br>7432 30p<br>7433 40p<br>7437 35p<br>7438 35p<br>7440 17p<br>7441 70p<br>7442A 60p<br>7443 112p<br>7445 100p<br>7446A 93p<br>7447A 60p<br>7448 80p<br>7450 17p<br>7451 17p<br>7453 17p<br>7454 17p<br>7456 17p<br>7457 17p<br>7459 17p<br>7470 30p<br>7472 30p<br>7473 34p<br>7474 30p<br>7475 36p<br>7476 35p<br>7480 50p<br>7481 100p<br>7482 84p<br>7483A 90p<br>7484 100p<br>7485 110p<br>7486 34p<br>7489 210p<br>7490A 33p<br>7491 80p<br>7492A 48p<br>7493A 33p<br>7494 84p<br>7495A 70p<br>7496 85p<br>7497 180p<br>74100 130p<br>74104 65p<br>74105 65p<br>74107 34p<br>74109 55p<br>74110 55p<br>74111 70p<br>74116 200p<br>74118 130p<br>74119 210p<br>74120 110p<br>74121 28p<br>74122 48p<br>74123 55p<br>74125 55p<br>74126 60p<br>74128 75p<br>74132 75p<br>74136 75p<br>74141 70p<br>74142 200p<br>74145 90p<br>74147 190p<br>74148 150p<br>74510 100p<br>74151A 70p<br>74153 70p<br>74154 100p<br>74155 90p<br>74156 90p<br>74157 70p<br>74159 190p<br>74160 100p<br>74161 100p<br>74162 100p<br>74163 100p<br>74164 120p<br>74165 130p<br>74166 140p<br>74167 200p<br>74170 240p<br>74172 720p<br>74173 120p<br>74174 93p<br>74175 85p<br>74176 90p<br>74177 90p<br>74178 160p<br>74180 93p<br>74181 200p<br>74182 90p<br>74184A 150p<br>74185 150p |  | <b>4000 SERIES</b><br>4000 15p<br>4001 17p<br>4002 17p<br>4006 95p<br>4007 18p<br>4008 80p<br>4009 80p<br>4010 80p<br>4011 17p<br>4012 18p<br>4013 50p<br>4014 84p<br>4015 84p<br>4016 45p<br>4017 80p<br>4018 80p<br>4019 45p<br>4020 100p<br>4021 100p<br>4022 100p<br>4023 22p<br>4024 50p<br>4025 20p<br>4026 130p<br>4027 50p<br>4028 84p<br>4029 100p<br>4030 55p<br>4031 200p<br>4033 180p<br>4034 200p<br>4035 110p<br>4040 100p<br>4041 80p<br>4042 80p<br>4043 90p<br>4044 90p<br>4046 110p<br>4047 100p<br>4048 55p<br>4049 32p<br>4050 48p<br>4051 80p<br>4052 80p<br>4053 80p<br>4054 150p<br>4055 125p<br>4056 135p<br>4059 600p<br>4060 115p<br>4063 120p<br>4066 55p<br>4067 450p<br>4068 22p<br>4069 20p<br>4071 30p<br>4072 22p<br>4073 22p<br>4075 22p<br>4076 107p<br>4081 22p<br>4082 22p<br>4093 80p<br>4094 175p<br>4098 107p<br>4111 11p<br>4502 120p<br>4503 70p<br>4507 55p<br>4510 99p<br>4511 150p<br>4514 250p<br>4516 110p<br>4518 100p<br>4520 90p<br>4528 100p<br>4543 180p<br>4553 450p<br>4560 250p<br>4583 90p<br>4584 90p<br>4001A 90p<br>4008A 200p<br>4009 90p<br>14411 11p<br>14412V 11p<br>14433 11p |  | <b>93 SERIES</b><br>9301 180p<br>9302 175p<br>9308 316p<br>9310 275p<br>9311 275p<br>9312 180p<br>9314 185p<br>9316 225p<br>9321 225p<br>9322 150p<br>9334 225p<br>9368 200p<br>9370 200p<br>9374 200p |  | <b>VERO BOARD</b><br>0 1 0 15<br>(2x3x3)<br>41p 33p<br>49p 45p<br>3x3x3 49p 45p<br>3x3x5 56p 60p<br>3x3x7 152p 121p<br>3x3x17 195p 163p<br>4x4x17 252p<br>Pkt of 35 pins<br>Spot face cutter 85p<br>Pin insertion tool 99p |  | <b>VERO WIRING PEN</b><br>Plus Spool 325p<br>Spare spool (wire) 80p<br>Combs 7p each |  | <b>TRANSISTORS</b><br>AC126 25p<br>AC127/8 20p<br>AC176 25p<br>AC287/8 25p<br>AF116/7 30p<br>AD149 70p<br>AD161/2 45p<br>BC107/8 11p<br>BC109 11p<br>BC117 20p<br>BC147/8 9p<br>BC149 70p<br>BC157/8 9p<br>BC159 11p<br>BC169C 12p<br>BC172 12p<br>BC177/8 17p<br>BC179 18p<br>BC182/3 10p<br>BC184 11p<br>BC187 30p<br>BC212/3 11p<br>BC214 12p<br>BC461 30p<br>BC477 8 30p<br>BC516/7 50p<br>BC547B 16p<br>BC548C 16p<br>BC549C 16p<br>BC557B 16p<br>BC558B 16p<br>BC559C 16p<br>BCY70 18p<br>BCY71 2 22p<br>BD135/6 54p<br>BD138 56p<br>BD140 56p<br>BD242 70p<br>BF506 200p<br>BF200 32p<br>BF244B 35p<br>BF258 82p<br>BF259 36p<br>BF329 30p<br>BF340 34p<br>BF384/5 30p<br>BF386/7 30p<br>BF388 30p |  | <b>BFW10 90p</b><br>BFY50 22p<br>BFY51 2 22p<br>BFY56 33p<br>BFY90 90p<br>BYE83 700p<br>BRV39 45p<br>BSX19/20 20p<br>BU104 225p<br>BU105 190p<br>BU108 250p<br>BU109 225p<br>BU205 200p<br>BU208 200p<br>BU406 145p<br>BU481 175p<br>MU491 200p<br>MU2501 225p<br>MU2955 100p<br>MU3001 225p<br>MU340 65p<br>MUJ2955 100p<br>MC182/3 11p<br>MC214 12p<br>MC461 30p<br>MC477 8 30p<br>MC516/7 50p<br>MC547B 16p<br>MC548C 16p<br>MC549C 16p<br>MC557B 16p<br>MC558B 16p<br>MC559C 16p<br>OC2B 130p<br>OC35 130p<br>R2008B 200p<br>R2010B 200p<br>TIP29A 40p<br>TIP29C 55p<br>TIP30A 48p<br>TIP30C 60p<br>TIP31A 58p<br>TIP31C 62p<br>TIP32A 68p<br>TIP32C 82p<br>TIP33A 82p<br>TIP33C 114p<br>TIP34A 110p<br>TIP34C 165p<br>TIP35A 225p<br>TIP35C 280p<br>TIP36A 270p<br>TIP36C 340p<br>TIP41A 65p<br>TIP41C 78p<br>TIP42A 70p<br>TIP42C 82p |  | <b>TIP2955 78p</b><br>TIP3055 70p<br>TIS43 34p<br>TIS93 30p<br>ZTX108 12p<br>ZTX300 13p<br>ZTX500 15p<br>ZTX502 18p<br>ZTX504 30p<br>2N457A 250p<br>2N696 35p<br>2N697 25p<br>2N698 45p<br>2N706A 20p<br>2N708A 20p<br>2N918 45p<br>2N930 18p<br>2N1131/2 20p<br>2N1613 20p<br>2N1711 25p<br>2N2102 60p<br>2N2160 120p<br>2N2219A 20p<br>2N2222A 20p<br>2N2369A 16p<br>2N2484 30p<br>2N2646 50p<br>2N2904/5 25p<br>2N2906A 24p<br>2N2907A 30p<br>2N3052 20p<br>2N3053 20p<br>2N3054 65p<br>2N3055 48p<br>2N3442 140p<br>2N3553 240p<br>2N3565 30p<br>2N3643/4 48p<br>2N3702 3 21p<br>2N3704/5 12p<br>2N3706/7 12p<br>2N3708/9 12p<br>2N3773 300p<br>2N3819 25p<br>2N3820 108p<br>2N3823 70p<br>2N3866 90p<br>2N3903/4 18p |  | <b>2N3905/6 20p</b><br>2N4036 65p<br>2N4058/9 6p<br>2N4060 12p<br>2N4061/2 18p<br>2N4123/4 22p<br>2N4125/6 22p<br>2N4289 20p<br>2N4401 3 21p<br>2N4427 27p<br>2N4871 60p<br>2N5087 27p<br>2N5089 27p<br>2N5172 27p<br>2N5179 90p<br>2N5191 83p<br>2N5194 90p<br>2N5245 40p<br>2N5296 55p<br>2N5401 50p<br>2N5457 8<br>2N5459 40p<br>2N5460 40p<br>2N5485 44p<br>2N6027 48p<br>2N6247 190p<br>2N6254 130p<br>2N6290 65p<br>2N6322 65p<br>2N6298 120p<br>2N6553 240p<br>2N6565 30p<br>3N201 110p<br>3N290 100p<br>3N290 250p<br>40360 40p<br>40361/2 45p<br>40364 120p<br>40408 70p<br>40409 65p<br>40410 65p<br>40411 300p<br>40594 97p<br>40595 108p<br>40673 75p<br>40841 90p<br>40871/2 90p |  | <b>DIODES</b><br>BY127 12p<br>OAA7 9p<br>OAB1 15p<br>OAB5 15p<br>OAO9 9p<br>OAA91 9p<br>OAA85 9p<br>OAO200 9p<br>OAO20 10p<br>IN914 4p<br>IN916 7p<br>IN4148 4p<br>IN4001/2 5p<br>IN4003/4 6p<br>IN4005 6p<br>IN4006/7 7p<br>IN4007/3 14p<br>IN5404/7 19p<br>IS920 9p |  | <b>ZENERS</b><br>2.7V-33V 9p<br>400mW 15p<br>1W 15p |  | <b>TRIACS</b><br>PLASTIC 80p<br>3A 500V 85p<br>6A 400V 70p<br>6A 500V 88p<br>8A 400V 75p<br>8A 500V 85p<br>12A 400V 105p<br>16A 400V 110p<br>16A 500V 130p<br>T2800W 130p |  | <b>HEAT SINKS</b><br>For TO220 Volt-age Regs and Transistors For TO5 |  | <b>THYRISTORS</b><br>1A 50V 40p<br>1A 400V 65p<br>1A 600V 70p<br>3A 400V 90p<br>8A 600V 140p<br>12A 400V 180p<br>16A 400V 180p<br>16A 600V 220p<br>BT106 110p<br>C106D 45p<br>MCR101 36p<br>2N3525 130p<br>2N4444 140p<br>2N5001 34p<br>2N5064 40p |  | <b>BRIDGE RECTIFIERS</b><br>1A 50V 21p<br>1A 100V 22p<br>1A 400V 35p<br>1A 600V 35p<br>2A 100V 35p<br>2A 400V 45p<br>3A 200V 60p<br>3A 600V 75p<br>4A 400V 100p<br>6A 500V 108p<br>6A 100V 100p<br>2 1/2 BR 70p<br>2 BR 75p<br>1 1/2 BR 75p |  | <b>MEMORIES</b><br>2102 100p<br>2102-2 120p<br>2102L-4 140p<br>2107B 500p<br>2111 1 225p<br>2112-2 225p<br>2114 10p<br>5101 510p<br>6810 350p |  | <b>UART</b><br>AY-3-1015P 500p<br>AY-5-1013P 400p<br>TMS6011NC 400p |  | <b>CHARACTER GENERATOR</b><br>3257ADC 995p<br>MCM6576 750p<br>RO-3-2513U C 600p<br>SN74S262AN 1360p |  | <b>SUBMINIATURE SWITCHES</b><br>Toggle SPST 51p<br>SPDT 53p<br>DPDT 55p<br>DPDT (centre off) 75p<br>Push to make (Red Green Yel Blue) 15p<br>Push to break (Black only) 25p |  | <b>CRYSTALS</b><br>100KHz 300p<br>1MHz 370p<br>3.2768MHz 350p<br>10.7MHz 350p<br>18MHz 300p<br>27.135MHz 300p |  | <b>EDGEBOARD CONNECTORS</b><br>0.156" Solder Tail<br>2 x 10 way 85p<br>2 x 15 way 100p<br>2 x 18 way 120p<br>2 x 22 way 135p<br>2 x 25 way 160p |  | <b>OTHER</b><br>3245 400p<br>4201 350p<br>4289 970p<br>4801 500p<br>6820 600p<br>6850 700p<br>8205 320p<br>8212 225p<br>8216 225p<br>8224 400p<br>8228 525p<br>8251 700p<br>8253 12p<br>8255 12p<br>8257 11p<br>8259 11p<br>MC14411 11p<br>MC14412V 11p |  | <b>ROM/PROMS</b><br>74S185 225p<br>74S287 400p<br>74S387 400p<br>93427 400p<br>93436 650p<br>93446 650p |  | <b>CPU'S</b><br>4040A 670p<br>6502 1200p<br>6800 900p<br>6801 TBA<br>8080A 550p |  | <b>EPROMS</b><br>1702A 600p<br>2708 900p<br>2716 125p<br>4702 900p |  | <b>LOW PROFILE DIL SOCKETS BY TEXAS</b><br>8 pin 11p<br>14 pin 12p<br>16 pin 13p<br>18 pin 25p<br>20 pin 28p<br>24 pin 28p<br>28 pin 42p<br>30 pin 51p |  | <b>WIRE WRAP SOCKETS</b><br>8 pin 30p<br>14 pin 40p<br>16 pin 55p<br>24 pin 80p<br>28 pin 100p<br>40 pin 120p |  |
|---|--|--|--|--|--|--|--|--|--|---|--|---|--|---|--|---|--|---|--|---|--|---|--|--|--|--|--|---|--|---|--|---|--|---|--|---|--|---|--|---|--|---|--|---|--|---|--|--|--|--|--|---|--|

**RESISTORS** High Stab Carbon Film 5% Tol E12 Series  
1.4W 10R-1M 1p 90p. 100 (one value)  
1.2 10R-10M 1 5p 120p. 100 (one value)

**MINIATURE PRESETS** Horiz / Vert  
100R-1M  
100R

**CARBON TRACK POTENTIOMETERS**  
1/4 LOG or LIN  
Single 5K-2M 26p  
Single with DP Switch 5K-2M 55p  
Dual 5K-2M 86p

**ANTEX SOLDERING IRONS**  
Model C 15W 360p  
CX 17W 360p  
X25 380p  
CCN 380p

Spare Bits C/CX/CCN 46p  
X25 50p

**VEROBOARDS**  
DIP Breadboard 4.5 x 6 15 270p  
(Suitable for 20 x 14 pin or 16 x 16 pin DIL ICs)  
Dip board 4.5 x 6 15 340p  
(With tracks for 31 way connector)  
Connector Plug 31 way 100p  
Connector Socket 31 way 110p  
VQ Board for ICs - no track cutting 105p

**VAT RATE:** All items at 8% except where marked \* where 12 1/2% applies.

Please add 25p p&p & VAT at appropriate rates.

Government, Colleges, etc. Orders accepted.

CALLERS WELCOME

Mon-Fri 9.30-5.30  
Saturday 10.30-4.30

**TECHNOMATIC LTD.**  
17 Burnley Road, London NW10  
(2 minutes Dollis Hill tube station) (ample street parking)  
Tel: 01-452 1500 Telex: 922800

# news digest.....

WHEN THE COMPUTING and Control department of Imperial College decided that they needed a logic hardware teaching lab, they were faced with several alternatives. One was to teach all the students in each year to solder and then let them loose on a handful of TTL and CMOS chips each. This would have meant a plethora of supply problems, technicians and even minor burns.

What they opted for instead was to use — you guessed it — a computer.

The setup works roughly like this: A computer terminal is situated in the centre of the 'lab' and is surrounded by 16 benches, each provided with an oscilloscope, a signal generator and other relevant test equipment and peripherals. Each bench also has a perspex case with several dozen sockets and LEDs in it. The student goes to the central console, tells the machine which bench he wishes to use and which logic elements he requires. He then goes to the bench and sticks labels on the perspex case. Each label is printed with the relevant logic symbol. By connecting patchcords between the sockets on the 'breadboard,' the student can build up a logic network. The LEDs indicate the state of the various outputs. Each of the boards also has various 'utilities' — several clocks, a random logic output and handswitches to provide inputs.


All of these functions are provided by the computer — the sockets all lead into it's bus and it is the computer which drives the LEDs. This means that not only is there no possibility of the students damaging ICs which would then have to be replaced, but also that any component can be 'synthesised' — the department has even designed an imaginary CPU for use with the system.

The computer also calculates propagation delays — the students learn the pitfalls of race hazards in digital systems. It is even possible to simulate faulty components — as a fault-finding exercise. Another system (experimental as yet) can pretend to be linear components as well. Clearly the teaching possibilities offered by such a system are tremendous — what price blobboards now?

— Phil Cohen



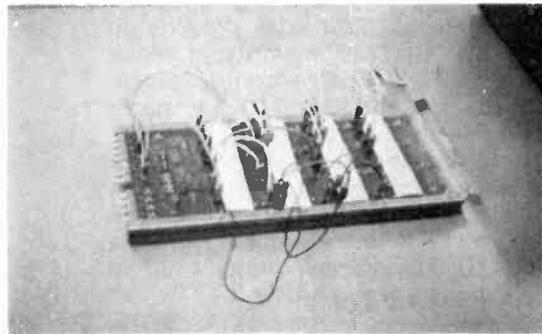Martin Cripps telling the machine what it's supposed to be!



What the students see. The wires disappear into the table — some conjuring trick!

Our thanks to Roy Francis and Martin Cripps of Imperial College for their time and trouble.

## Clearly-Precision within your grasp for only

# £79.<sup>00</sup> +P&P

**LCD Multimeter Kit — Measures Voltage (AC/DC), Current, Resistance, Temperature\*.**

This is a compact, portable, hand-held precision instrument, accurate to within  $\frac{1}{2}\% \pm 1$  digit and giving crystal-clear readout from  $\frac{1}{2}''$  'black-on-silver' digits. It has automatic polarity indication, automatic zero, battery state indication and a shockproof case in black ABS with brushed aluminium-finish fascia plates.

We supply full instructions for easy building on a single PCB (+display). No metalworking etc. required.

### TECHNICAL SPECIFICATION

- Accuracy:  $\frac{1}{2}\% \pm 1$  digit
- DC Volts: 200mV, 2V, 20V, 200V, 1000V
- AC Volts: 200mV, 2V, 20V, 200V, 500V
- Current AC/DC: 200 $\mu$ A, 2mA, 20mA, 200mA, 2A
- Resistance: 200 $\Omega$ , 2K $\Omega$ , 20K $\Omega$ , 2M $\Omega$
- \* Temperature: 0-100°C (with sensitive external sensor supplied)
- Connectors: 4mm sockets,  $\frac{3}{4}''$  spaced; 1 red + 1 black test probe provided.
- Internal battery: PP3 type (not supplied)
- Current consumption: < 10mA.
- Transflective display
- Critical components selected for  $\pm \frac{1}{2}\%$  accuracy.

PRICE INCLUDES VAT.



**REMINDER**  
The DORAM Electronic Hobbies Catalogue is now available.

## FREE

Order now.  
**Guarantee of Satisfaction.**  
Send the coupon immediately.  
Your Kit will be delivered within 25 days.  
If you are not completely satisfied you may return your purchase within 30 days for a full refund.  
Doram Electronics Ltd,  
PO Box TR8, Leeds LS12 2UF.  
An Electrocomponents Group Company  
**OFFER CLOSES 14th February 1979.**

To Doram Electronics Ltd PO Box TR8 LS12 2UF  
Please send .....60-632 Kit(s) at £79.95 ea. (£79.00+95p p&p)  
Please send a Hobbies Catalogue

I enclose cheque/PO for £  
I am paying via National Giro Centre Bootle Lincs to your Account Number 00/643/7257  
Please debit my ACCESS Card No.   
I expect delivery within 25 days  
Signature .....  
Name ..... (BLOCK LETTERS)  
Address .....

Doram Electronics Ltd Reg 1155856

ETI 12

---

---

# LOUDSPEAKER PRINCIPLES

ON PAPER most loudspeakers look to be terrible pieces of design. Distortion averaging 1%-2% — and what's worse varying with frequency. Efficiency only rarely exceeding 1% — so that the vast majority of those carefully nurtured, 0.002% THD amplifier watts pumped in down those non-inductive £10 a metre cables turn into nice, safe, un-musical heat!

The purpose of any loudspeaker is to convert an incoming complex electrical signal into compressions and rarefactions in the air—sound waves — which can be perceived as being as close to the original signal as possible. The different methods now being used to realise this end form the basis of this article.

## What Is Left Undone

You will find references throughout this article to frequency divider — crossover — networks. Unfortunately there is too much to be said on that subject to allow a full and proper treatment of it within this article, and we shall return to it in a companion article later.

Forgive us our evasion.

Loudspeakers of whatever variety interact crucially with the surroundings they are used in — the living room, studio or whatever. When judging performance it is vital to remember this, and even moving a speaker around in a room can significantly alter performance. Some manufacturers are becoming sensitive to this themselves — notably AR — and are producing designs specially tailored to a particular location, or allowing adjustment of output to suit varied positioning (AR 10π, AR9).

Such adjustments are generally carried out within the crossover network, and alter the electrical inputs to the units to compensate for specific emphasis placed on certain frequencies — usually the bass — by the loudspeakers position.

## And What Is Not

We have concentrated on the major fundamentally different systems in commercial use today, and tried to explain how they operate what their advantages are, and what are their drawbacks. Many minor variations have been left out simply through lack of space.

Forgive us our omissions.

The types covered are:

1. Moving coil — and methods of loading
2. Electrostatic
3. Isodynamic
4. Ribbon
5. Piezo-electric
6. Motional Feedback Control

**Every hi-fi must have not one but two. Loudspeakers are perhaps the weakest link in the precarious hi-fi chain. Many methods of improving the sound we hear have been tried. Few have succeeded well enough to reach production. Ron Harris explains the innermost secrets of those that made it!**

## MOVING COIL

This system dominates the field at present, and is certain to do so for the foreseeable future. The principle is an exact reverse of the microphone principle, and takes its being from the fact that a wire carrying a current  $I$  in a magnetic field of flux density  $B$  will experience a force,  $F$ , where


$$F = B.I.k \quad k = \text{a const.}$$

A coil of wire carrying the audio is sited within an intense magnetic field, and is attached to a 'cone' as shown in the diagram. The cone is held in position by the edge suspension and 'spider'.

When a signal passes through the coil the force produced tries to push it out of the field in one direction or another, and this movement is transferred to the air by the movement of the cone. The suspension system provides a 'return-to-rest' force. This movement is related more or less linearly to the input as long as the coil remains within a constant field.

If it moves out, then the relationship will change, introducing non-linearity or distortion. For this reason large and powerful magnets are employed, which have as great a depth of field as possible.

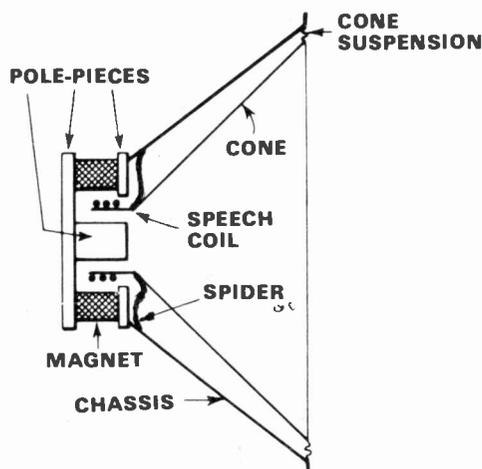Another solution is to use very long coils so that the number of turns of wire within the gap between the pole pieces remains relatively constant.




Basic schematic of moving coil loudspeaker. In practice the coil winding would be longer relative to the magnets, so that it did not move out of the field.

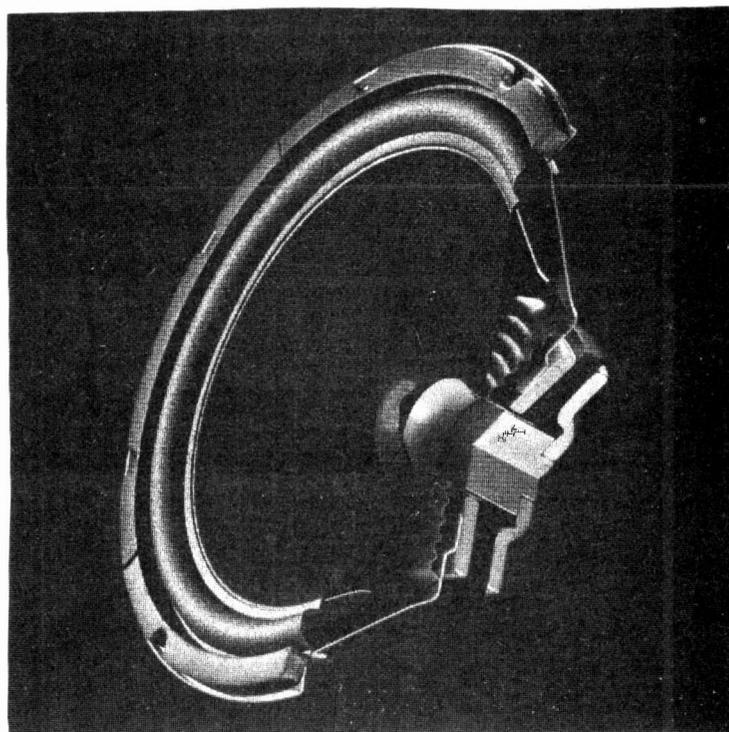
### Heated Exchange

Heat is generated in the coil and must be conducted away, usually by the magnet assemblies and chassis. AR speakers now incorporate a heat conducting fluid which is present in the gap and the coil is immersed in this. Heat conduction is thus improved and power handling raised. The fluid also acts as a damper to aid movement control.

The speaker chassis must be as rigid as possible, since the only reason the coil and cone move and it doesn't is that it weighs more! Any resonances present in the structure will act to transfer energy from the coil movement and hence distort the output.



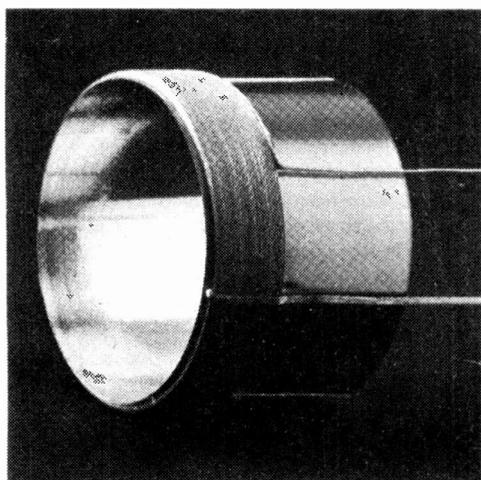Cutaway photo of a moving coil unit — in this case a Bose driver. If you look carefully you should be able to identify the voice coil, magnet assembly, spider and cone assembly.



Close-up of a voice coil. This is a machine wound unit belonging to a Bose driver. Note the winding is butted very close to the edge of the paper former, and the precise nature of the winding necessary for linearity.

### Cone-ventional?

The greatest drawback of this system is the cone itself. This is usually either doped paper or Bexetrene — an erstwhile packing material someone fell over once! It should act as a piston to the air, with the entire surface moving together to produce the required air movement.

However, since it is driven only at the centre, unless the material is possessed of infinite rigidity(!) flexing or

rippling will take place — once again deviating from the input signal. The larger the cone the worse the effect as the frequency rises, since the centre driven portion may well be oscillating with a period smaller than the time taken for the energy to be transmitted through the cone material to the outside edge.

Hence the centre of the cone leads the outside by a number of cycles, all of which appear as ripples in the cone. This is the reason for dividing up the incoming electrical signal, and for employing smaller coned drive units for higher, less energetic, frequencies.

To handle the high end of the audio spectrum, dome units have almost entirely replaced the coned variety, as they spread the sound more evenly, giving a better dispersion across the listening area. Also domes can be produced smaller, and a hemispherical dome, edge driven, will tend to act more as an integral surface than a centre driven cone.

### Getting A Hangover

Since the cone has mass, and therefore inertia (Dr. Who excepted) it cannot respond instantaneously to changes in direction called for by changes in polarity of the electrical signal. This inability to get back in time is called 'overhang' and is another problem facing designers. To minimise it driver mass has to be as small as possible, while rigidity has to be as high as possible.

This has led over the years to many experiments with metal cones, mylar cones, polyester et etc etc. Anywhere other than bass units most of these have proved successful. ▶

An integral part of a moving coil loudspeaker design is the method of housing the units, and thus putting an acoustic-loading upon the actual units. A brief discussion of the various methods is thus required at this point.

### Housing Shortages

There are basically six methods of providing a home for drive units and at the same time augmenting its performance. These are:

- (i) Finite Baffle
- (ii) Acoustic Suspension (sometimes called Infinite Baffle)
- (iii) Bass Reflex
- (iv) Auxiliary Bass Radiator
- (v) Transmission Line
- (vi) Horn Loading

All of these apply primarily to moving coil units with the exception of horn loading which can be used to enhance efficiency of several types. In order then:—

### Finite Baffle

Since the vibrating cone is emitting sound waves in both directions, unless prevented the two waves will interact causing cancellation and reduction in acoustic output. The effect is reduced by placing the speaker in the centre of a large solid board to make it difficult for a compression produced in front to cancel the rarefaction produced behind the speaker.

Obviously an infinitely large piece of wood prevents this entirely, but such things don't grow on (ANY) trees(!?) and so the finite baffle is an attempt to do the best that can be done.

Once the sound wavelength approaches the baffle size destructive interference takes place and response rolls off.

This method is responsible for those hardened enthusiasts mounting their bass units flush into walls and sides of houses!

Sinclair marketed a finite baffle speaker some years ago but this seems to have ceased to be.


### Acoustic Suspension

Here the rear radiation from the units is (hopefully) entirely suppressed by totally enclosing the unit in a box, and radiating through a hole in that box (sounds odd when phrased like that eh?).



**The AR9.** Coming from one of the 'founder' manufacturers it represents Acoustic Researches state of the art. The cabinet is treated around the baffle with absorption material to prevent diffraction and re-radiation effects that lesser enclosures suffer from. It also stands an endearing 53in high!

**Schematic of a Jordan Watts driver module.** Numbers refer to: 1. Metal cone contoured to hyperbolic law. 2. Phase correcting dome. 3. Resistive termination to dome centre. 4. Resistive termination to cone edge. 5. Acoustic damping. 6. Direct input signal cable. 7. Coil completely immersed in magnetic field. 8. High efficiency "Feroba" magnet. 9. Resistive termination at junction of cone, coil and suspension. 10. Connections to coil via suspension. 11. Silvered beryllium copper suspension cantilevers.

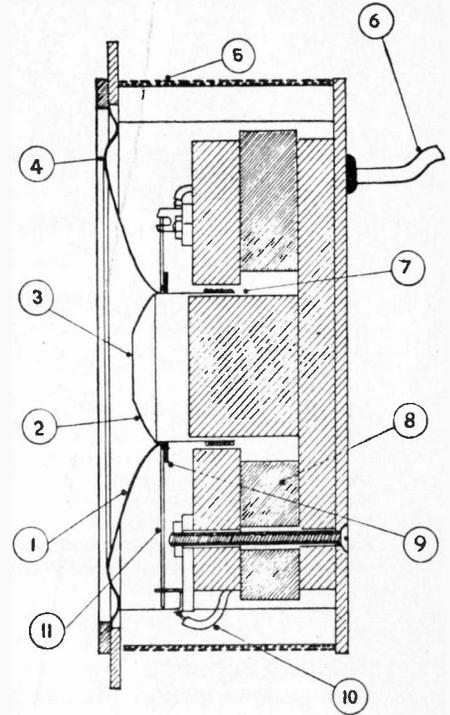

Damping of the cone movement occurs due to the compliance of the trapped air, and the suspension system now consists of both the actual cone suspension plus the air load.

In order to preserve bass response the enclosure should be fairly large and hence present a good air load allowing high levels of energy to be applied. Bass units designed for this type of loading have a high cone mass and high compliance. In addition they are generally of the long voice coil variety. The air load then applies most of the restoring force required by the design. Efficiency is reduced since the cone mass is increased and compliance (total) is low.


### Bass Reflex

The aim of this method is to raise efficiency at low frequencies and thus decrease the required enclosure size for a given bass output. This is accomplished by addition of a vent, or port, in the front panel of the enclosure. This allows a controlled movement of air between cabinet and room. The effect of careful design of vent dimensions and placement is to produce an effective addition to bass response below a certain frequency, such that the air moving out of the vent aids the air movement produced by the bass driver.

Above the operating frequency the vent has no effect on performance (they hope).
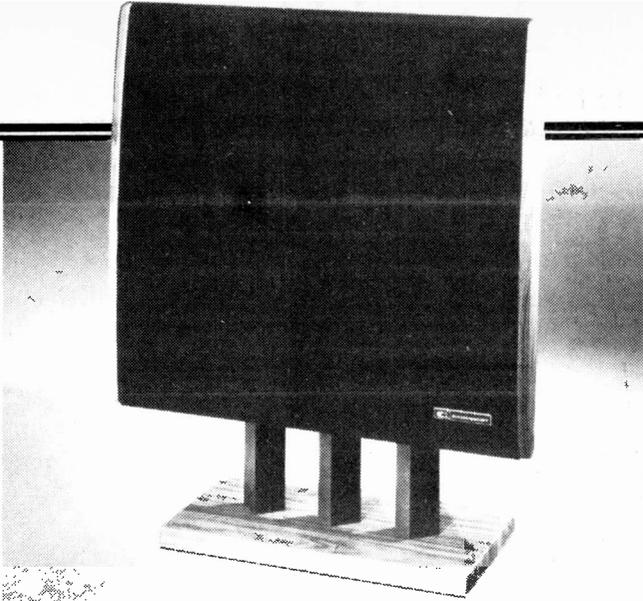
### Auxiliary Bass Radiator

Basically a variation on the above principle, but with the vent 'plugged' with a driverless unit or suspended mass. This is tuned to provide antiphase radiation in the required frequency band. Above this band the unit acts like part of the enclosure wall. Perfected and practised by Celestion, and perhaps epitomised by the Ditton 66 design.



**The DQ10.** This design makes use of what the makers term a 'phased array'. This means that the driver units are staggered so that their effective radiator 'points' are equi-distant from the listener which eliminates the time delay distortion (phase linear?) flat baffle designs are prone to. In addition each driver is mounted on its own optimum sized baffle to minimise diffraction problems.

## Transmission Lines

This is another method of 'losing' the rear radiation of a drive unit, or making it think it is working into an infinitely long column. This is achieved by having a maze of woodwork inside the enclosure which is filled with graduated damping material. In this way total column length can be far greater than enclosure dimensions.


If the far end of the column is open then help is afforded to the bass performance in much the same way as bass reflex cabinets.

The design is usually for almost total absorption of the rear wave — and this leads to a gradual and smooth fall off in bass response due to the almost constant velocity working conditions for the cone.

Conversely to both acoustic suspension and basis reflex loading methods, transmission line methods lower the bass resonance of the drive units and hence enhance LF performance.

IMF have championed this technique for long time passing now, and as exemplified in their products transmission line bass possesses a 'solid' quantity totally different to that from the other methods. It is more extended and more realistic. Used in a large enough room there is no better way to replay the lower registers.

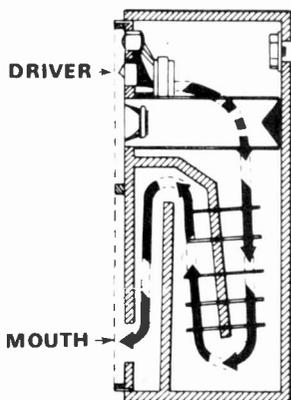Oh for a successful combination of transmission line bass and electrostatic HF!




The basic principle behind the transmission line speaker enclosure. The air from the rear of the cone gets 'lost' down the line.

**KEFs 105 linear phase design.** The upper two enclosures are rotatable to aid stereo imagery. Note the rounded edges to prevent re-radiation and the staggered drivers with respect to the listener.
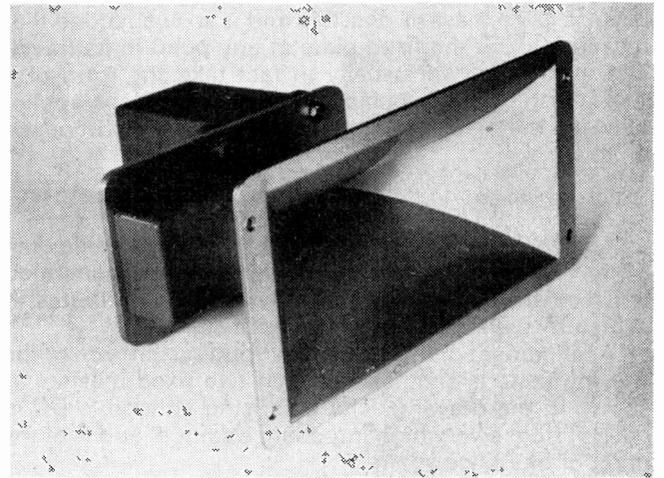
## Horn Loading

A method of designing to considerably reduce required driver excursion for a given acoustic output. The driving element is coupled to its air load by a gradually 'flaring' throat — usually exponential in cross section.


The horn converts the high pressure, low velocity sound energy present in the region of the driver into low pressure high velocity waves for propagation. The advantages of this type of loading are good damping of the driver, low distortion but a limited frequency response.



**The Decca London ribbon unit, loaded by a catenoidal horn.** The flare can be clearly seen in this photo leading down to the ribbon itself somewhere in that block at the back!

To design a single horn to cover the entire audio spectrum is a confused exercise, and one yielding impractical results for domestic use, since an exponential horn to reproduce 30 Hz has a mouth of 1.5m diameter and is some 4m long! Folding the horn back and forth within an enclosure can reduce dimensions, and the American firm Klipsch market units which employ the room walls as extensions of the horn to reach lower frequencies. Usually though, the system is used to load MF and HF units within a system.

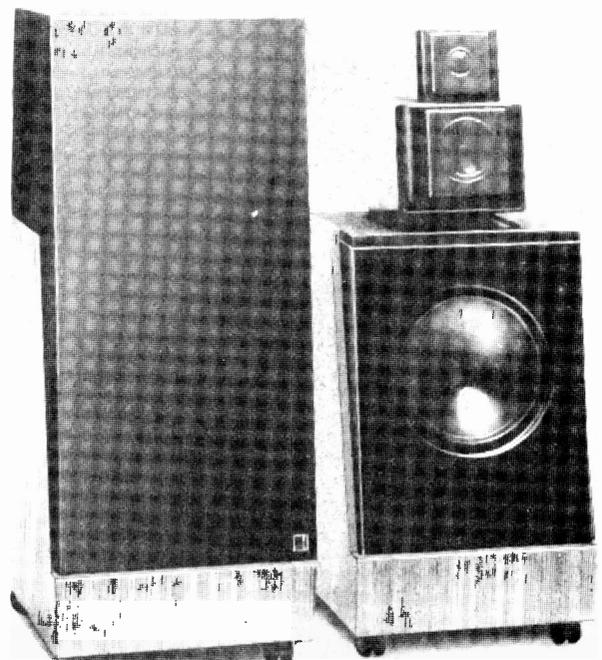Advantages of this principle are phenomenal efficiency  $\approx 10\%$  compared with 1% for bass reflex for bass reflex and 0.1% for transmission lines, and an attack unmatched by any other cone driver recipies. ▶



# ELECTROSTATIC


As we have seen the moving coil design suffers because the cone area is unevenly driven by the electrical music signal. The electrostatic principle, developed by both David Tombs and Peter Walker (of the Acoustical Manufacturing Company) is an attempt to produce a unit in which the entire surface of the unit is driven by the input signal.

At its most basic the design consists of two plates as shown in the diagram. The moveable plate is made to have as low a mass as possible and is so suspended that it cannot touch the fixed plate at any point in its travel. The fixed plate will usually in fact take the form of a metal 'mesh'. A high polarising voltage  $\approx 5\text{kV}$  is applied between the plates, and the audio signal superimposed on this.

An electrostatic force—such as that which holds dust on to LPs and LPs onto turntables—is thus generated between the plates and the moveable one vibrates in sympathy with variation in the input signal.

A refinement of this is the push-pull system where the moving plate is situated between two fixed meshes as shown in the drawing. The polarising voltage is DC in nature, from a very high impedance source, and is of the order of  $5\text{kV}$  once again.

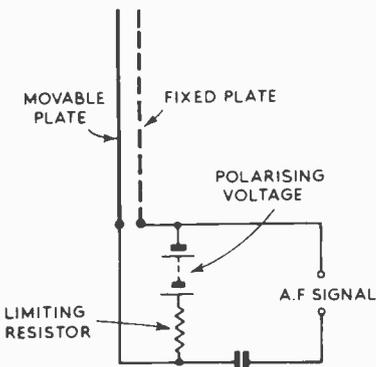The outer plates (meshes) are fed from a step-up transformer connected to load the incoming signal. This applies a high voltage electrical AC signal to these plates (the music signal) and causes the center plate to move in sympathy with this. Distortion is greatly reduced using this push-pull arrangement and can equal  $0.5\%$  in a good design.



**Scheme of operation for electrostatic loudspeakers. On the top we have the basic single ended design, and below that the commercially employed, much-improved push-pull scheme as employed by Quad and Koss amongst others.**

This system first appeared on the market many many years ago in the form of the Quad electrostatic system—which remains largely unsurpassed for lack of colouration and mid-range clarity.

The advantage of driving the plate evenly over its whole area show up as a linear frequency response—no rippling or 'break-up'—very low distortion and a good transient performance due to low driver mass.

However this system does have inherent drawbacks. Consider the Quad system as an example. It is noted for its mid-range clarity and its high frequency accuracy—but also for its lack of extreme bass and its beaming of top end signals—poor vertical dispersion.

The reason for this is its physical size. Since the push-pull radiator is by nature a dipole radiator—sound emitted both front and back, some cancellation at frequencies whose wavelength exceeds the plate dimension is inevitable.

The Quad is also very room sensitive for this same reason. Rear radiation can be dumped, but not without acoustically loading the plate—an undesirable excursion into non-linearity. At high frequencies there is low energy in the wave to absorb, and so this is easier to affect without adverse consequences on the drive plate.


KLH made a brave attempt to reach the theoretical size of plate for good bass response with their superb KLH9 full range units. These are almost exactly door sized—and you need **two** per channel! And they cost £2000 a pair. And they are probably unbeatable by any speaker on the market for sheer accuracy and delicacy. Their size endows them with a hefty bass punch too. Units to sell your soul for. (Anyone listening down there?)

## Loading Problems

Another less serious drawback is that transformer into which the electrical signal is fed: This presents an awkward load to the amplifier, and can produce some nasty effects from transistor amps.

Modern designs however—Lecson, Quad and the rest, can cope perfectly and experience no traumas when presented with the wickedly reactive termination characteristic of electrostatic speakers.

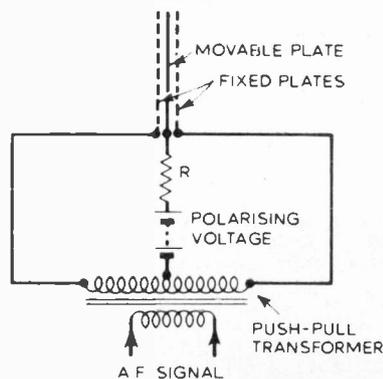Many attempts have been made to marry together electrostatic mid-high drivers with cone bass units. B&W DM70 was perhaps the first (and the best!) but not have been entirely successful. Perhaps its simply that the superior distortion and colouration properties of the electrostatics will always show up the bass units!



## ISODYNAMIC



With the release of the Stathearn 21000 speakers, and the new Wharfedale series incorporating Isodynamic tweeters, this approach is gaining ground. It certainly has a lot of promise, which we shall undoubtedly see exploited as time goes on.

The principle was pioneered by Wharfedale with their Isodynamic headphones some six years ago or so. It is really an attempt to gain the advantages of the electrostatic system, without the need for high voltages and attendant drawbacks.


A drive unit built to this principle consists of a thin sheet of mylar, or some such material, with a conductive track bonded onto it in a pattern which covers the surface in as symmetrical a manner as possible. This conductor acts as the voice coil of the speaker, and when an electrical signal is passed through it it responds to nearby magnets by moving the diaphragm in sympathy.

Once again colouration is low, and driver mass small—but also once again to obtain bass means large areas, and conductors capable of handling large currents. Stathearns units are above 500Hz operators only and are transformer coupled to the input. Wharfedale employ their invention in high frequency units only.

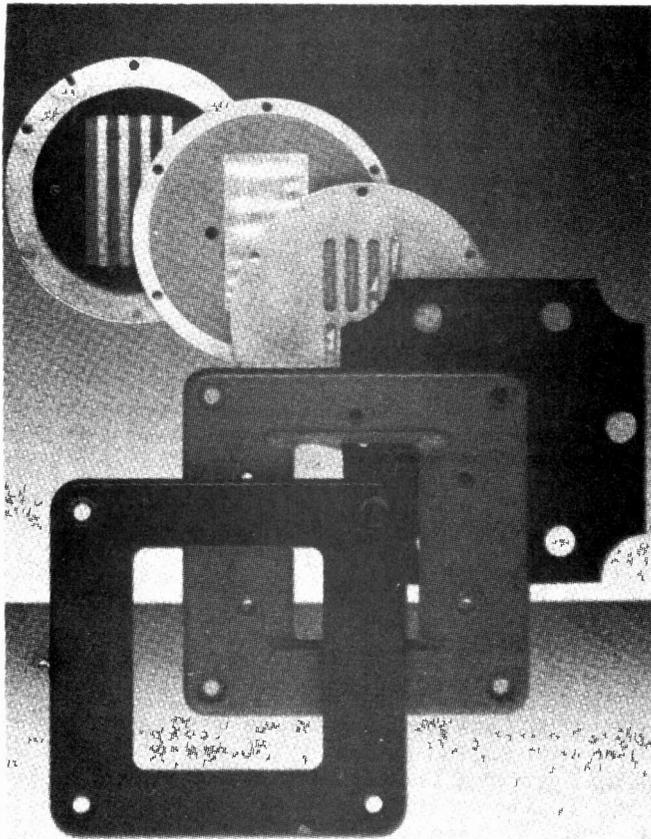
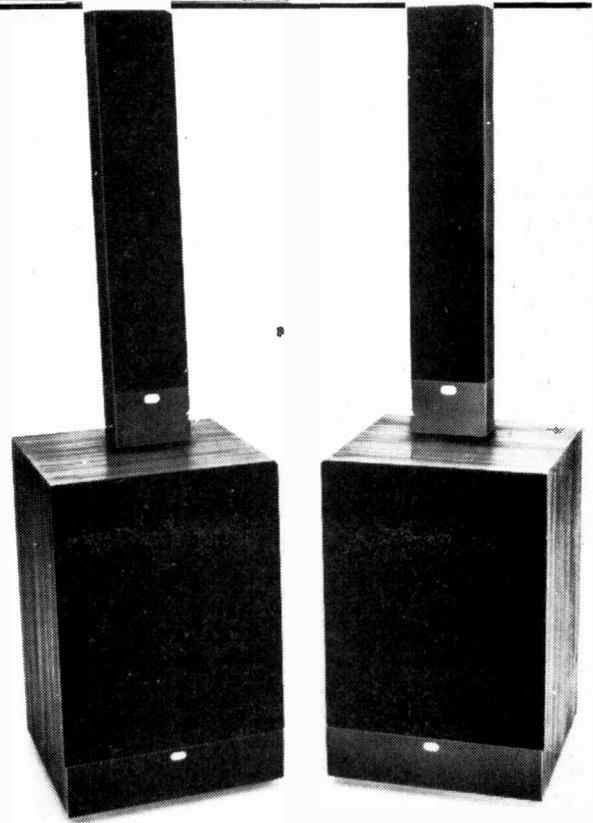
A pity—but one we might see rectified sometime in the future.



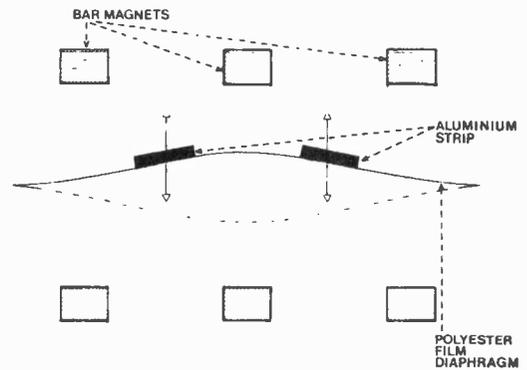Exploded view of the Wharfedale Isodynamic tweeter. The driver plane — second from the rear — uses a material 25 microns thick with an etched aluminium circuit.



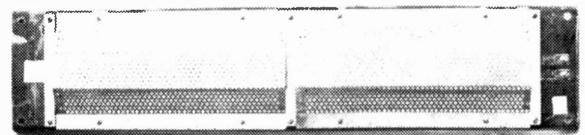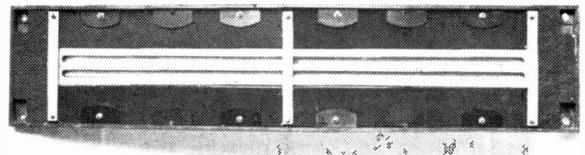The 21000 from all angles. At the top we have the full system. Below that the diagram shows the operating principle of the SLC1. The polyester diaphragm acts as the speaker cone. Below this caption two internal views of the unit. The radiating areas can be seen in the top diagram, and the lower rear view illustrates the damping material to control rear radiation.



## RIBBON


If we take the voice coil of moving coil speakers, and make this the active element, instead of the cone, we would do away with a lot of the causes of colouration in the process. Mass would be much smaller, break-up or rippling would be greatly reduced, if not eliminated and thus transient handling improved.

The ribbon loudspeaker does exactly this. A very thin metal 'ribbon' is suspended between the magnet pole faces and the signal passed through it. It will vibrate with the signal, and thus produce the sound output.

Acoustic output is low, and horn loading is usually employed to alleviate this problem.

Once again obtaining bass is a major problem, and moving coil units will take over from the ribbon as the frequency decreases.

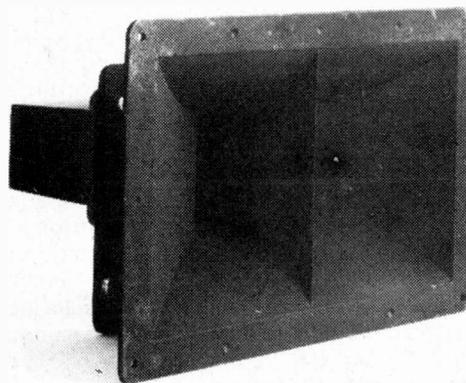Decca market an excellent example of this principle, which operates above 2.5kHz.



Decca's ribbon loudspeaker. This features a ribbon element one tenth the thickness of human hair, and is horn loaded to increase efficiency. An 'acoustic lens' can also be fitted to aid sound dispersion.

## PIEZO-ELECTRIC

In the July 1976 edition of ETI we reviewed the Motorola KN 6006A, the first piezo-electric unit to be released commercially. Since that time many commercial loudspeaker enclosures have employed piezo-electric tweeters for their total insensitivity to crossover networks, phenomenal transient response and clean subjective sound quality.

Piezo-electrics have been around in hi-fi for a long time now in the guise of crystal/ceramic cartridges. The principle of operation is based upon the fact that stress a piezo-electric crystal and a voltage proportional to the applied force is produced across its ends.

Conversely therefore if we apply a varying voltage across the ends of the crystal, mechanical deformation occurs, sympathetic to that voltage. No magnets are required, and no coil is used.

In the Motorola design two thin slices of ceramic material—lead zirconite-lead titanate in case it makes your life the fuller for knowing are epoxied onto a brass separator, and nickel electrodes deposited on to a facilitate connection. In order that the discs respond correctly to the input, they are polarised in opposite senses, so that on application of a common signal one disc expands and the other contracts—acting in the same direction therefore on the air load.

### Pros . . . . .


Since the impedance curve for the unit shows a steep rise in value with falling frequency, the unit does not need a crossover to reject low frequencies.

A perfect tweeter.

Since there is no voice coil or cone the driver mass is significantly lower than an equivalent conventional speaker.

Being composed of a ceramic material heat dissipation is less of a problem also, and the Motorola can stand 35V RMS for protracted periods with no signs of distress.

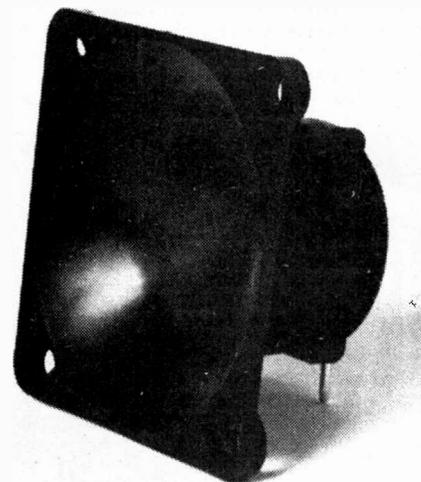Due to the nature of its impedance, it is difficult to compare efficiency with normal units, suffice it to say that 4V RMS produces 105dB at 18ins distance, and that this can be considered efficient!




Motorola's KN 6006 piezo-electric high frequency driver. The actual driver is the small section at the rear, and the horn is to increase acoustic efficiency.

### . . . . . And Cons.

Some amplifiers may not like the load any more than electrostatic units, but since these things are normally used with a good deal of attenuation and response shaping circuitry between them and the valued output stages this should not be too great a problem.

Subjectively these units have always sounded a little 'hard' to me, and never as smooth as a good dome unit like the Isophon or Celestion 2000 designs. Still personal taste and all that . . . . .

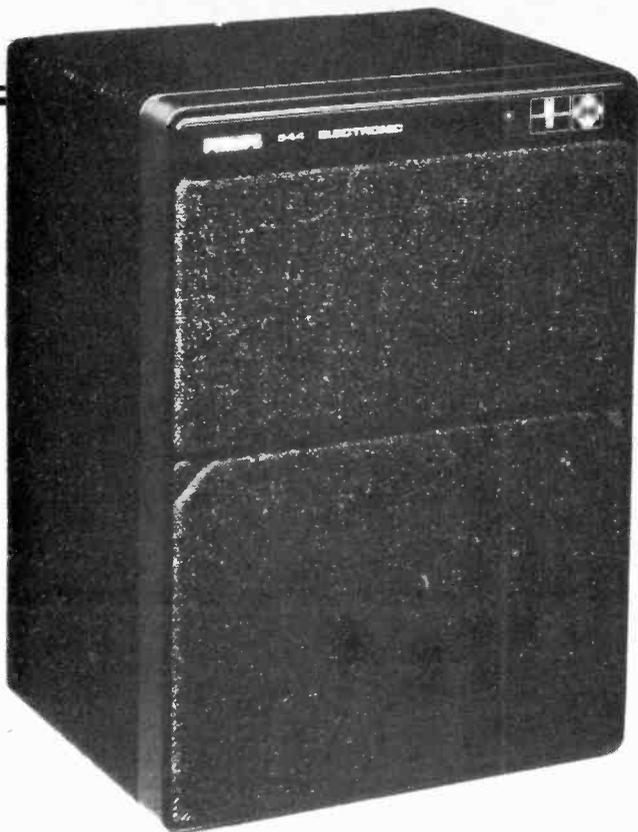Once again acoustic efficiency is low, and horn loading is employed.



### MOTIONAL FEEDBACK

Although this perhaps only a modification of earlier systems, the performance gains at LF are such that it warrants a closer look.

Motional feedback is a form of feedback control of the driver cone in moving coil systems. The power amplifier are mounted within the enclosure, a separate amp for each drive unit, and so signal feed is from a preamplifier. The system is marketed by Philips.

The main advantage of this extra complication lies at the bottom end of the range where the output for given enclosure volume is considerably enhanced. The complication lies in the sensor fitted onto the driver.


This is mounted on a small PCB and is a ceramic acceleration sensor. This generates a signal proportional to the actual driver output, and this is compared electronically to the incoming audio. Correction is applied to remove any errors present. Cross over is carried out at small signal level, and active filters with all their inherent superiority are applied.

There is a 'slave' output which allows the enclosures to be stacked up to increase power handling and effective output.

**ETI**

**Philips loudspeaker RH 544 Motional Feedback design. This unit incorporates a separate bass power amplifier, and a lower power amplifier for mid-high frequencies. Bass performance is exceptional for the tiny enclosure size, but other areas of output are undistinguished.**

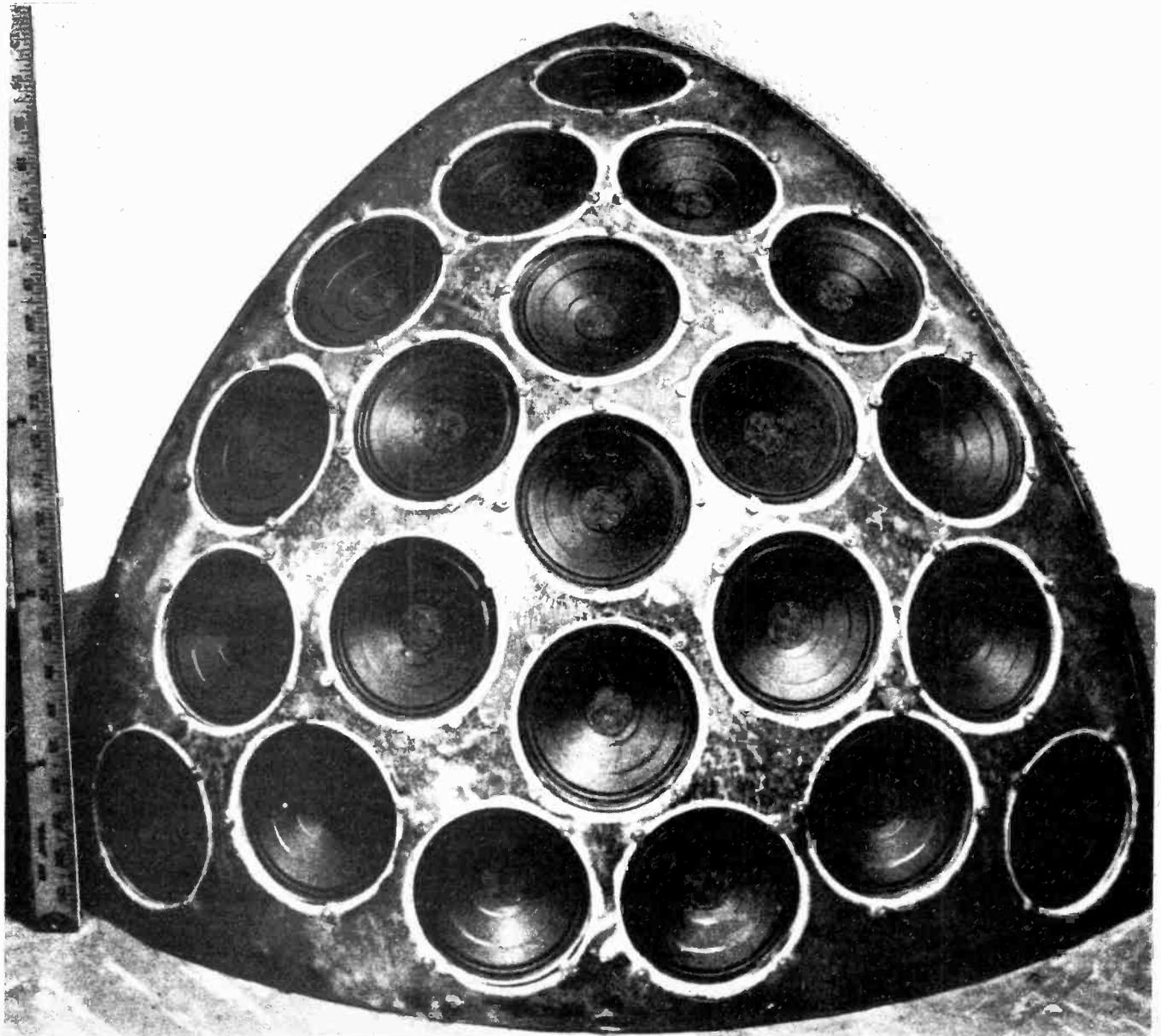**This is one-eighth of the perfect speaker! Many experts consider that elusive device to consist of a pulsating sphere operating in free field conditions. Bose built this approximation to test pulse waveform response. From here sprung the excellent Base 901 series III loudspeaker.**





# CAR TACHOMETER

**We've been contemplating a digital car tacho, but have been put off by resolution and response speed problems. However this Phase Locked Loop design overcomes these quite neatly — so here it is!**

WE HAD OFTEN considered the design of a digital tacho for automobile use, but had rejected several schemes as we were unable to get both good resolution and response time — the two seemed to provide a very good demonstration of Heisenberg's Uncertainty Principle.

Consequently, we were rather pleased when Mike Pratt of SM Electronics came to us with his phase-locked loop based design which got round the problem. Would we like to do it as a project, he asked? Obviously, we said yes, and here it is.

This tacho features a fast response time, coupled with 10 Hz resolution, through the use of a phase locked loop frequency multiplier. It can be set up, by means of a single link, to work on 4, 6 or 8 cylinder motors.

## Design Features

To measure the revolutions per minute of a motor is simply a matter of counting the number of ignition pulses over a given time. With a four-cylinder, four-stroke motor there is such a pulse twice per revolution. Therefore if we count these pulses for 30 seconds we will have revs/min with a one cycle resolution. Obviously this is much too long a sample period for practical use in a motor car and some compromise has to be made.

The usual solution is to use a 100 rev resolution and a sample time of 0.3 seconds (on 4 cylinders). We considered this inadequate which is why we have not published a design until now.



In this design an oscillator is used which is phase locked to the ignition pulses except at a higher frequency (x8 for 4 cylinder) allowing a short sample time (0.375sec) with a 10 rev resolution. By using a different multiplication factor compensation for different numbers of cylinders can be made. Unfortunately with the multiplication factors used (x8, x6, x4) the sample time for 6 cylinders is not exactly the same as that used for 4 and 8 cylinder motors. Altering the ratios to x12, x8 and x6 would enable a 0.25 sample time to be used for all ranges, but this is not possible with the divider IC utilised in this design.

## Construction

Assemble the PCB with the aid of the overlay ensuring the components are

orientated correctly. The tantalum capacitors normally have a + mark indicating the positive lead, or a dot on the side. When soldering the CMOS ICs (4, 6, 7) earth the tip of the soldering iron.

Note that there is one feedthrough or link between the two sides of the board near C10

## Calibration

Initially place a link between the point 'C' and the terminal corresponding to the number of cylinders. Now with the power supply connected feed a 50 Hz signal of between 12 and 30 V into the points input using the 0 V as common. Now adjust RV1 until the display reads 1500 RPM for 4 cylinders, 1000 for 6 or 750 for an eight cylinder car. ▶


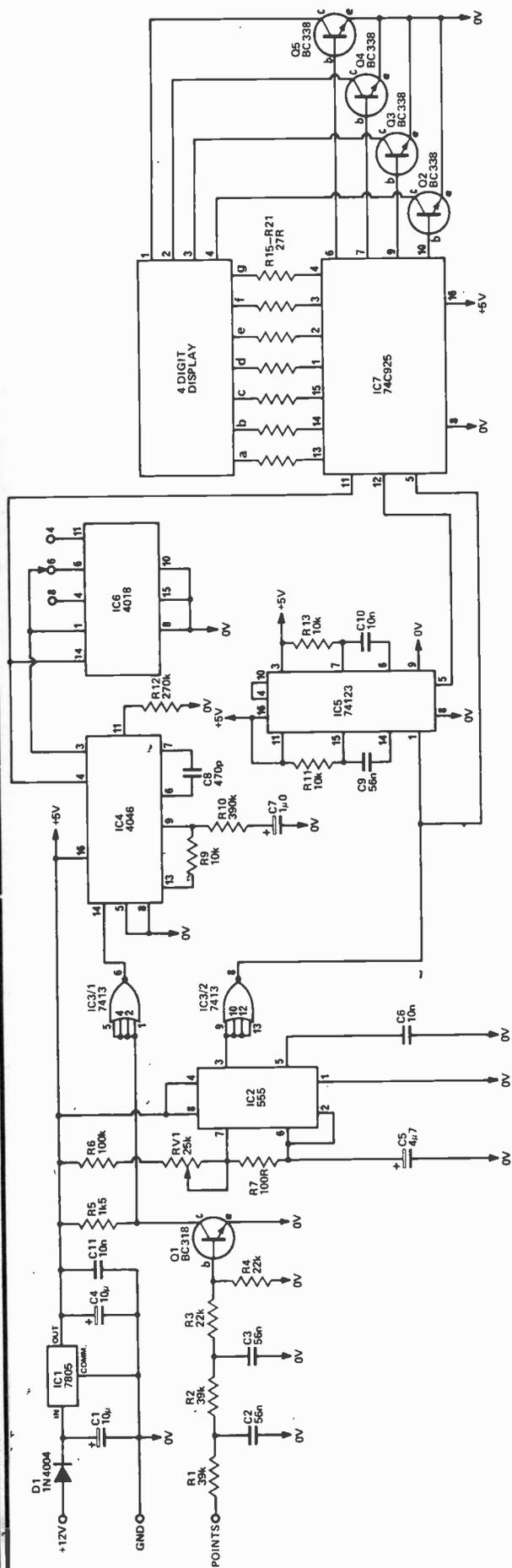


Fig. 2. Full circuit diagram for the digital car tacho unit.

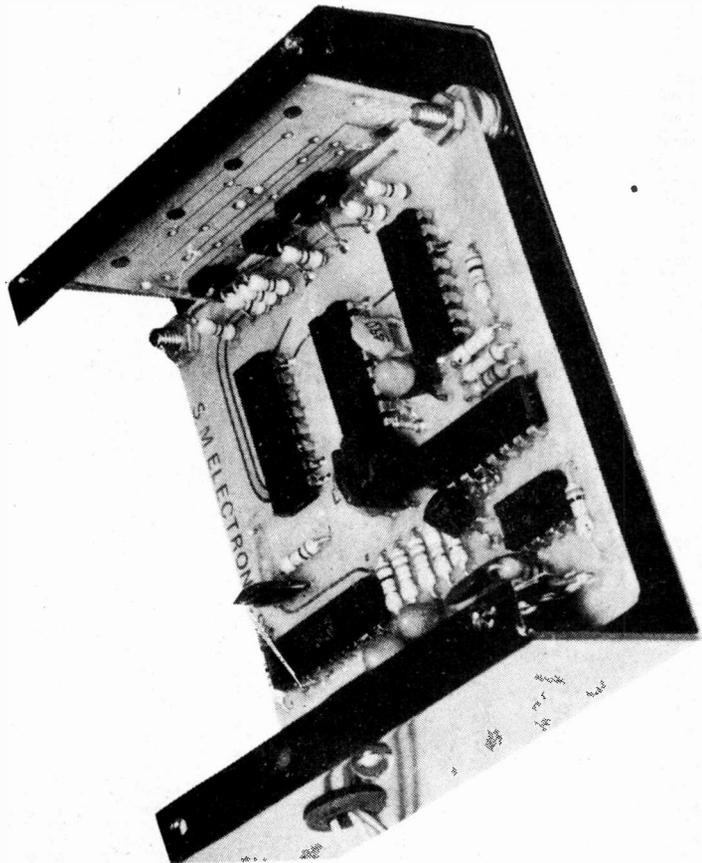

### HOW IT WORKS

The output from the points of the distributor is basically a 0 to 12V square wave with a 200 volt pulse on the rising edge. A filter network, R1-R4, C2, 3 is used to remove the high voltage pulse (and points bounce) and Q1 buffers it giving a +5 to 0V output on its collector. As the filter network removes the sharp edge of the input a schmitt trigger is needed on the output of Q1 to give fast edges. IC3/1 is used for this.

The output of IC3/1 is connected to the input of the phase-locked loop IC (4046). This IC has an internal voltage controlled oscillator and its output is divided by 4, 6 or 8 by IC6 and this lower frequency is fed back to the phase-locked loop IC. The IC then compares this frequency to that at its input and adjusts the internal oscillator until it is the same. The result is a frequency which is an exact multiple of the input.

The time base is generated by IC2 (555) which has a negative output pulse, about 300  $\mu$ s wide every 375 ms (or 333 ms for 6 cylinder). This is inverted by IC3/2 and is used as the strobe pulse for the 4 digit counter IC7. This pulse also triggers the first of the monostables in IC5 which gives a 200  $\mu$ s delay before triggering the second half of IC5; this gives a 40  $\mu$ s pulse to reset IC7 back to zero.

IC7 is a 4 digit counter with a latch (store) and seven segment decoders to drive the digits but the segment drivers are internal. As we need only a three digit counter, i.e. for good resolution, with the right hand permanently zero the least significant digit is connected to the second right digit, etc, with the most significant digit connected to the right hand digit. Provided one does not exceed 9990 RPM this digit will remain on 0 as intended!

The 555 timer, the TTL and the 74C925 needs a regulated +5V and IC1 provides this with D1 preventing damage due to reverse polarity inputs.

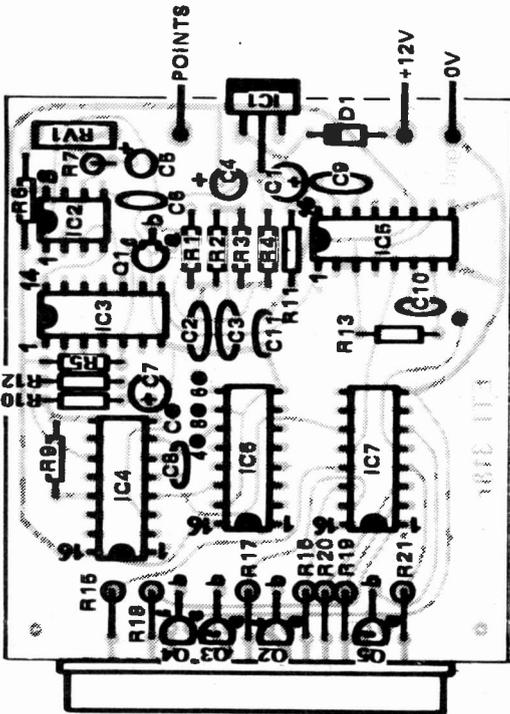


Fig. 1. The component overlay for the board. The board is double sided although only the lower surface is shown here. Note the link between the two surfaces of the board near C10.

## SPECIFICATION

**Range**  
 100 to 9990 RPM  
**Resolution**  
 10 RPM  
**Reading rate**  
 4 or 8 cylinders  
 6 cylinders  
**Power supply**  
 7 to 15V @ 400mA  
 Suitable ignition systems standard  
 CDI  
 transistor assisted  
 'it will not operate on  
 'pointless' systems

## PARTS LIST

|                |                        |
|----------------|------------------------|
| RESISTORS      | all 1/4 W, 5%          |
| R1,2           | 39k                    |
| R3,4           | 22k                    |
| R5             | 1k5                    |
| R6             | 100k                   |
| R7             | 100R                   |
| R8             | not used               |
| R9             | 10k                    |
| R10            | 390k                   |
| R11            | 10k                    |
| R12            | 270k                   |
| R13            | 10k                    |
| R14            | not used               |
| R15-R21        | 27R                    |
| POTENTIOMETER  |                        |
| RV1            | 25k trim               |
| CAPACITORS     |                        |
| C1             | 10u 25V tantalum       |
| C2,3           | 56n polyester          |
| C4             | 10u 25V tantalum       |
| C5             | 4u 7 25V tantalum      |
| C6             | 10n polyester          |
| C7             | 10u 25V tantalum       |
| C8             | 470p ceramic           |
| C9             | 56n polyester          |
| C10            | 10n polyester          |
| C11            | 10n ceramic            |
| SEMICONDUCTORS |                        |
| IC1            | 7805 regulator         |
| IC2            | 555 timer              |
| IC3            | 7413 dual schmitt      |
| IC4            | 4046 PLL               |
| IC5            | 74123 dual mono        |
| IC6            | 4018 divide by n       |
| IC7            | 74C925 4 digit counter |
| Q1             | BC318                  |
| O2-Q5          | BC338                  |
| D1             | 1N4004                 |
| Display        | NSB5881                |
| MISCELLANEOUS  |                        |
| PCB            | Case to suit           |

## BUYLINES

The components employed here are all readily available from any of the major mail order companies advertising in this issue. Note that the counter is a CMOS chip, and not a standard bi-polar TTC chip. The standard component will not operate on this mode.

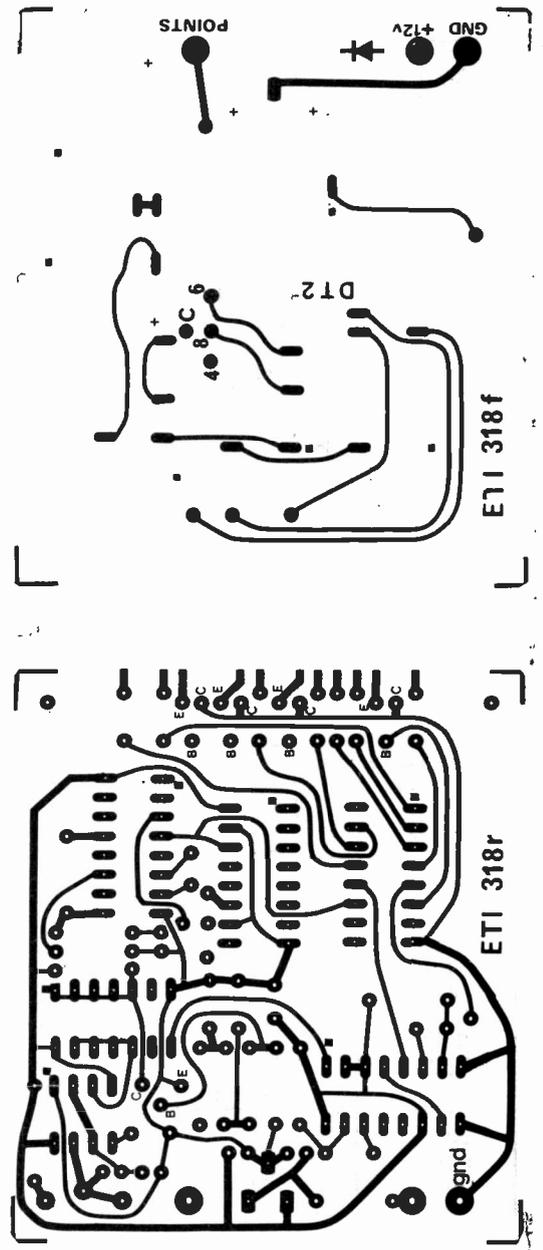


Fig. 3. PCB foil patterns shown full-size.

# ALARM-CHRONO WITH DUAL TIME



**ONLY £34.95**  
+ 60p P&P

This incredible watch is probably the most advanced of its kind. It offers the following functions:—

**THE TIME** gives hour, minute, sec, day, am or pm.

**THE CALENDAR** gives hour, minute, day or date by your selection.

**DUAL TIME** Time of any city of the world at your choice.

**ALARM** sounds every day at set time until reset or cancelled.

**CHRONO-TIMER** up to 12 hrs, 59 min, 59.9 secs and **LAP TIMES** as well.

(Available in Stainless Steel or Gold Look)

## KRAMER & CO.

9 October Place, Holders Hill Road  
London NW4 1EJ, Telex: 888941  
attn. Kramer k7. Tel: 01-203 2473

Mail order only. Callers by appointment

## ETCH RESIST TRANSFER KIT SIZE 1:1

Complete kit 13 sheets 6in x 4½in. **£2.50** with all symbols for direct application to P.C. board. Individual sheets 25p each. (1) Mixed Symbols (2) Lines 0.05 (3) Pads (4) Fish Plates and Connectors (5) 4 Lead and 3 Lead and Pads (6) DILS (7) BENDS 90° and 130° (8) 8-10-12 T.O.S. Cans (9) Edge Connectors 0.1 (11) Lines 0.02 (12) Bends 0.02 (13) Quad in Line.

## FRONT AND REAR PANEL TRANSFER SIGNS

All standard symbols and wording. Over 250 symbols, signs and words. Also available in reverse for perspex, etc. Choice of colours, red, blue, black, or white. Size of sheet 12in x 9in. Price **£1**.

## GRAPHIC TRANSFERS WITH SPACER ACCESSORIES

Available also in reverse lettering, colours red, blue, black or white. Each sheet 12in. x 9in contains capitals, lower case and numerals ½in kit or ¼in kit. **£1** complete. State size.

**All orders dispatched promptly.**

**All post paid**

Ex U.K. add 50p for air mail

Shop and Trade enquiries welcome  
Special Transfers made to order

**E. R. NICHOLLS**  
**P.C.B. TRANSFERS**  
Dept. HE/2

46 LOWFIELD ROAD  
STOCKPORT, CHES.061-480 2179

# TAMTRONIK LTD (DEPT ETI)

217 TOLL END ROAD, TIPTON  
WEST MIDLANDS, TEL: 021-557 9144

## ONE STOP SHOPPING — P.C.B.s

Components, Hardware, Cases, Part Kits, Full Kits. A complete service to the ETI Constructor.  
All Prices incl. VAT, P&P 30p per order.

| Mag. Issue | PROJECT                  | Ref.                   | PCB  | Component Pack | Hardware Pack | Case (Screened) | Total |       |
|------------|--------------------------|------------------------|------|----------------|---------------|-----------------|-------|-------|
| TOP        | Graphic Equaliser        | 601                    | 1.60 | 14.23          | 4.30          | —               | 20.13 |       |
|            | Graphic Equaliser PSU    | 602                    | .55  | 1.29           | —             | —               | 1.84  |       |
|            | R.F. Attenuator          | 603                    | —    | .26            | 1.54          | 1.35            | 3.15  |       |
|            | Watchdog                 | 604                    | .85  | 4.69           | 7.68          | 5.53            | 18.75 |       |
| PROJECTS   | Sweep Oscillator         | 605                    | .85  | 1.49           | 3.95          | —               | 6.09  |       |
|            | Stereo Simulator         | 606                    | 2.60 | 21.07          | 8.16          | 4.28            | 36.11 |       |
|            | Freezer Alarm            | 607                    | .60  | 2.30           | .53           | 2.24            | 5.67  |       |
|            | General Purpose Pre-Amp  | 608                    | .55  | .92            | 3.95          | 1.65            | 6.97  |       |
| NO         | G.S.R. Monitor           | 609                    | .85  | 3.13           | —             | —               | 3.98  |       |
|            | Burglar Alarm            | 610                    | .70  | 4.70           | 7.10          | 3.95            | 16.45 |       |
|            | Headlight Reminder       | 611                    | —    | .55            | 1.65          | —               | 2.20  |       |
|            | Bench Amplifier          | 612                    | .70  | 3.40           | 2.93          | 3.95            | 11.00 |       |
| 6          | Audio Visual Metronome   | 616                    | —    | 1.31           | 1.62          | —               | 2.93  |       |
|            | Compander                | 617                    | 1.60 | 10.10          | 8.30          | 3.15            | 23.15 |       |
|            | 50 watt High Power Amp   | 618                    | 1.30 | 6.46           | —             | —               | 7.76  |       |
|            | 100 watt High Power Amp  | 619                    | 1.30 | 9.16           | —             | —               | 10.46 |       |
|            | High Power Amp PSU       | 620                    | 1.10 | 5.66           | 7.89          | —               | 14.65 |       |
|            | LED Dice                 | 624                    | .50  | 2.92           | .66           | 1.65            | 5.73  |       |
|            | Marker Generator         | 626                    | .80  | 3.68           | 1.49          | .90             | 6.87  |       |
|            | Skeet                    | 627                    | 1.60 | 11.12          | .97           | 4.53            | 18.22 |       |
|            | Flash Trigger            | 628                    | .65  | 3.48           | .84           | 1.65            | 6.62  |       |
|            | Disco Lightshow          | 629                    | 3.05 | 12.79          | 5.85          | —               | 21.69 |       |
|            | Pink Noise Generator     | 630                    | .60  | 1.00           | —             | 1.65            | 3.25  |       |
|            | Nov 76                   | 541 Train Controller   | T001 | .75            | 5.27          | 5.84            | 3.95  | 15.81 |
|            | Jan 77                   | 444 5-watt Stereo      | T002 | 2.00           | 14.03         | 6.84            | 3.45  | 26.32 |
|            | Feb 77                   | 448 Stereo Disco Mixer | T003 | 1.60           | 13.74         | .87             | —     | 16.21 |
|            | Dec 77                   | Clock B                | T004 | 2.10           | 11.31         | —               | —     | 13.41 |
|            | Jan 78                   | House Alarm A          | T005 | 2.00           | 10.93         | 3.05            | 9.50  | 29.37 |
| Feb 78     | House Alarm B            | T006                   | .85  | 3.04           | —             | —               | 3.89  |       |
| Mar 78     | Metal Locator Mk. II     | T007                   | .92  | 5.91           | 8.76          | 3.38            | 18.97 |       |
| Mar 78     | Frequencer Shifter PSU   | T008                   | .65  | 4.14           | —             | —               | 4.79  |       |
| Mar 78     | Frequencer Shifter       | T009                   | 1.50 | 16.99          | —             | 2.40            | 20.89 |       |
| Mar 78     | LCD Meter                | T010                   | 1.00 | 24.62          | —             | —               | 25.62 |       |
| Apr 78     | Light Dimmer             | T011                   | .55  | 3.40           | 3.12          | —               | 7.07  |       |
| Apr 78     | Gas Monitor              | T012                   | .80  | 10.11          | 1.10          | 1.35            | 13.36 |       |
| May 78     | Star Trek Radio          | T013                   | .84  | 6.19           | .93           | —               | 7.96  |       |
| Jun 78     | Stars & Dots             | T014                   | 1.83 | 5.33           | 11.49         | 5.00            | 23.65 |       |
| Jun 78     | Spectrum Analyser        | T015                   | 1.83 | 35.76          | 18.02         | —               | 55.61 |       |
| Jul 78     | Wein Oscillator          | T016                   | .89  | 6.36           | 4.80          | 2.40            | 14.45 |       |
| Jul 78     | UFO Detector             | T017                   | 1.45 | 10.80          | .80           | —               | 13.05 |       |
| Jul 78     | Torch Finder             | T018                   | .45  | 1.27           | —             | —               | 1.72  |       |
| Jul 78     | Temperature Meter        | T019                   | 1.00 | 24.41          | —             | —               | 25.41 |       |
| Aug 78     | Etwtet                   | T020                   | .90  | 2.87           | 1.16          | —               | 4.93  |       |
| Sep 78     | Cross Hatch Generator    | T021                   | 1.40 | 5.33           | 3.66          | 1.65            | 12.64 |       |
| Sep 78     | Stop Timer               | T022                   | 2.30 | 14.27          | 11.04         | 1.65            | 29.26 |       |
| Sep 78     | Wheel of Fortune         | T023                   | 1.35 | 4.34           | .43           | 2.24            | 8.36  |       |
| Oct 78     | Complex Sound Generator  | T024                   | 2.95 | 10.15          | 8.78          | —               | 21.88 |       |
| Oct 78     | R.F. Power Meter         | T025                   | 1.10 | 2.24           | 7.12          | 2.38            | 12.84 |       |
| Oct 78     | Power Bulge              | T026                   | .60  | .71            | .78           | .79             | 2.88  |       |
| Oct 78     | Telephone Bell Extension | T027                   | .95  | 3.48           | 3.02          | 2.15            | 9.60  |       |
| Jul 78     | Proximity Switch         | T028                   | 1.95 | 7.91           | 3.25          | —               | 13.11 |       |
| Jul 78     | Ultra Sonic Receiver     | T029                   | .60  | 3.38           | 4.95          | —               | 8.93  |       |
| Jul 78     | Ultra Sonic Transmitter  | T030                   | .45  | .82            | 3.20          | —               | 4.47  |       |
| Nov 78     | Cuts Cassette Interface  | T031                   | 2.80 | 26.12          | .87           | 3.95            | 33.74 |       |
| Nov 78     | Audio Oscillator         | T032                   | 2.25 | 10.13          | .38           | —               | 12.66 |       |
| Dec 78     | Car Alarm                | T033                   | 1.80 | 2.80           | .92           | —               | 5.52  |       |
| Dec 78     | Wire Temp Meter          | T034                   | 1.10 | 1.31           | 1.31          | .45             | 5.78  |       |
| Dec 78     | Curve Tracer             | T035                   | 1.00 | 3.04           | 2.60          | 2.67            | 9.31  |       |
| Dec 78     | Eprom Prog main board    | T036                   | 2.25 | 17.75          | .21           | —               | 20.21 |       |
| Dec 78     | Eprom Prog PSU           | T037                   | 1.30 | 3.79           | —             | —               | 5.09  |       |

## SYSTEM 68

Except where copyright restrictions exist PCBs are available for all projects from Sept., 1976, and include

|                                  |      |
|----------------------------------|------|
| 560 A, B, C (set 3)              | 4.60 |
| 710 2m Power Amp                 | .90  |
| Double Dice                      | 1.35 |
| 152 A, B TV Patter Gen. (set 2)  | 2.85 |
| Heart Rate Monitor               | 1.00 |
| Reaction Tester                  | 1.45 |
| Metal Locator 549                | .85  |
| Door Bell                        | .65  |
| Drill Controller                 | .60  |
| 630                              | .60  |
| Digital Frequencer Meter (set 4) | 2.90 |
| Digital Thermometer              | 1.20 |
| Bongos                           | .65  |
| Loudhailer                       | .60  |
| Continuity Tester                | .50  |
| Spirit Level                     | .85  |
| 3-channel Tone Control           | .70  |
| Clock A                          | 1.05 |
| Experimenters Power Supply       | .90  |
| 555 Timer Board                  | .60  |
| Hammer Throw (set 3)             | 4.80 |
| Porch Light                      | .70  |
| RMS Meter                        | .95  |
| Rain Alarm                       | 1.00 |

## THIS MONTH'S BARGAINS

|  |       |
|--|-------|
| 100 x ½W 1k carbon resistors   | 30p   |
| 10 x 1W 5% 7k5 resistors   | 12p   |
| 10 x 1W 5% 1k5 resistors   | 10p   |
| 10 x 1W 5% 150R resistors  | 12p   |
| 10 x 6W 5% 390R wirewound  | 50p   |
| 10 x 47µ 10V Ax. Electrolytic Capacitors   | 25p   |
| 1 x 10k 1in Rotary potentiometer   | 15p   |
| 1 plug-in mains PSU 3V/6V/9V/12V DC 300mA, suitable for calculators and TV Games | £2.99 |

Full Set **£12.00**

## HOBBY ELECTRONICS

PCBs and Kits available from TAMTRONIK

PCBs and Kits also available for everyday electronics, send SAE for details.

For a few kits it is not possible to supply ALL components. To avoid disappointment we recommend you send SAE requesting kit details. Please quote project and kit reference number when details of a specific kit is required. SAE automatically brings you our catalogue.

OVER 120 KITS NOW AVAILABLE

TRADE AND EDUCATIONAL ENQUIRIES WELCOME

VISIT OUR SHOP AT:—

**32 Market Place**  
**Great Bridge, TIPTON**  
**West Midlands**



Buy it with Access

By letter or telephone

# POWER SUPPLIES

One more from Tim Orr. This time he takes us through a series of different methods for powering up circuits. On the way he explains the theory behind each.

THE JOB OF producing stable regulated power rails has been much simplified by the introduction (about seven years ago), of three terminal fixed voltage regulators. These devices can make the power supply design problem relatively simple, but even so the designer must be fully aware of a lot of other important details that can cause poor results. Firstly, consider a simple unregulated power supply, fig. 1.


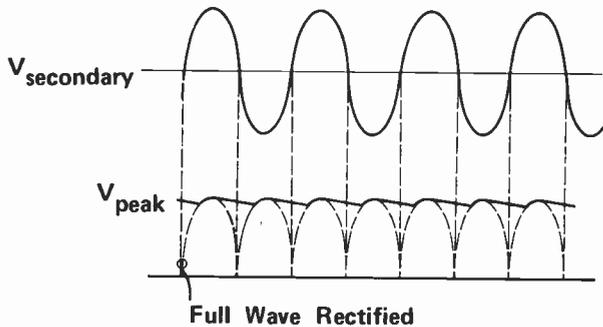


Figure 1. Below: an unregulated power supply. Above: The output (with a load resistor).

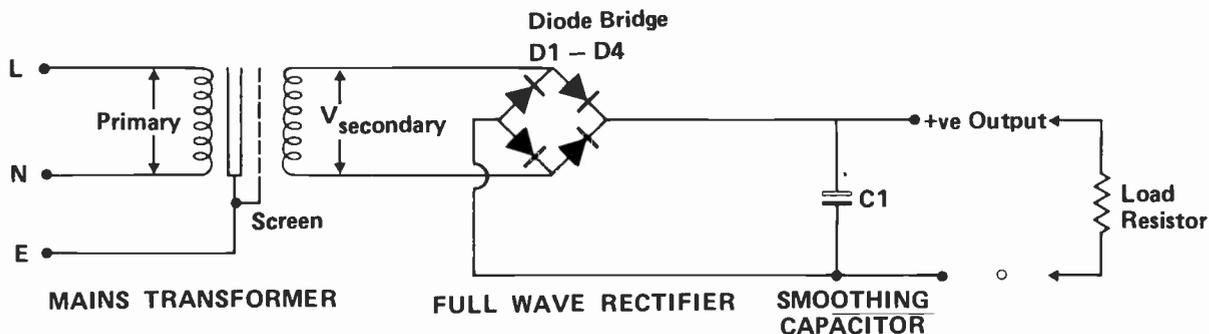

This piece of hardware has three sections, a step down, isolating transformer, a diode bridge and a smoothing capacitor. The transformer is driven from the mains, the voltage of which varies depending on where you live (it's 250V/RMS in Fulham). Some transformers have got a copper screen which isolates the primary winding from the secondary windings. For the purpose of safety, this should be connected to earth.

Also, for maximum safety, connect the 220/240/250 tapping to mains LIVE. Another type of mains transformer uses what is known as a split bobbin, the primary is wound on one bobbin, the secondary on another. Thus the two windings are inherently physically isolated, and so no safety screen is included. These two transformer types are generally constructed on what is known as an 'E' core; take one to bits and you will find that it is

The function of a mains isolating transformer is to physically separate the user end of a piece of equipment from the 'potentially' (!) lethal mains voltage. The transformer also provides a suitable voltage which can be rectified and smoothed and connected to a voltage regulator. This is the secondary voltage of a transformer and it is measured in VRMS at a particular loading.

That is, if the transformer is rated at 15V at 10VA, then the output voltage will be 15V when the load upon the transformer secondary is 10VA (10 watts).


If the load is removed the output voltage will rise. The percentage change from load to no load is known as the TRANSFORMER REGULATION and is typically of the order of 20%.

To convert the  $V_{RMS}$  voltage to a DC voltage it must be multiplied by 1.4142. Thus a 15VRMS (loaded) transformer secondary will generate 21V2 DC when full wave rectified and smoothed, which will rise to 25V45 DC when the load is removed (assuming 20% regulation see Fig. 1).

Thus care has to be taken when selecting a transformer such that the smoothing capacitor working voltage is not exceeded. Also, make certain that the polarity on this capacitor is correct, they can LITERALLY explode if wired up backwards!

constructed out of lots of 'E' shaped laminations. These 'E' laminations are butted into 'I' laminations, and clamped together. This butting together of the laminations can cause magnetic field problems. The wider the gap between the 'E' and 'I' laminations, the larger the magnetic field around the transformer.

The magnetic field generates a significant amount of induced hum in nearby electronics, this can be overcome by using a low leakage toroidal transformer which is constructed from circular laminations. The primary and secondary windings are wound through the centre of the toroid (see if you can imagine how). The toroidal transformer, by virtue of its 'continuous' laminations results in a low stray field and a low profile design, making it ideally suited for audio amplifier applications.

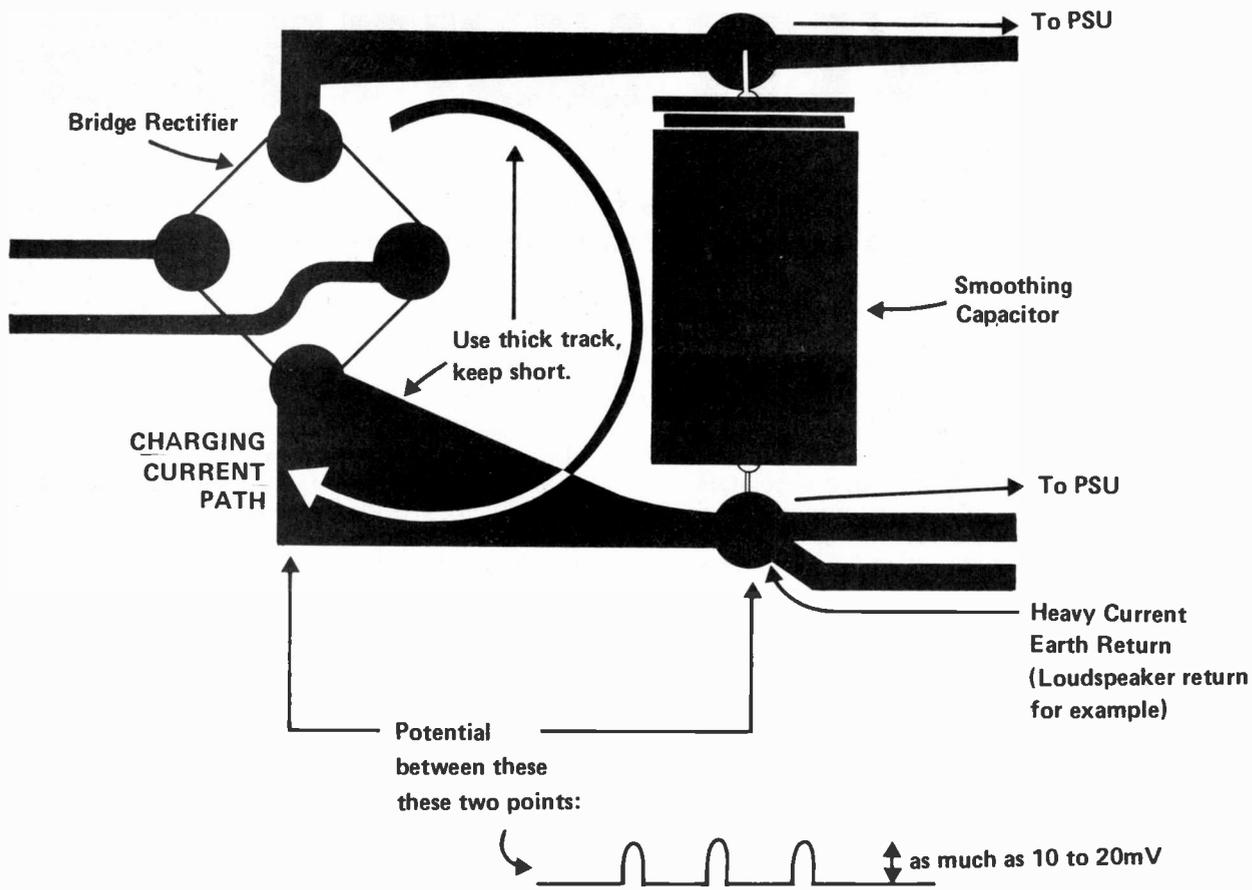


When a load is placed upon the power supply shown above, the output voltage appears as a DC voltage on top of which is a ripple voltage. This can be thought of as two separate periods, a charge period where the capacitor is charged up by the power supply and a discharge period where the load discharges the capacitor.

This charging and discharging generates a ripple voltage which has a period of 10 ms (100 Hz). A load current of 100 mA, and a 1000µF capacitor will result in a ripple voltage (Vpp) of about 7V.

As a rule of thumb I usually allow 1 to 1V5 maximum ripple if a voltage regulator is being used. This will generally result in an output ripple of less than 1 mV. If this ripple were to be obtained by just using a larger capacitor, then a 700,000µF-capacitor would be required!

Generally the discharge period is much longer than the charge period. This means that the transformer is only supplying power for short periods, in fact during the charge period. During these periods the smoothing capacitor is rapidly charged, and it is quite common for these current surges to exceed several amps. This can cause mains BUZZ problems when laying out printed circuit board designs for power supplies.

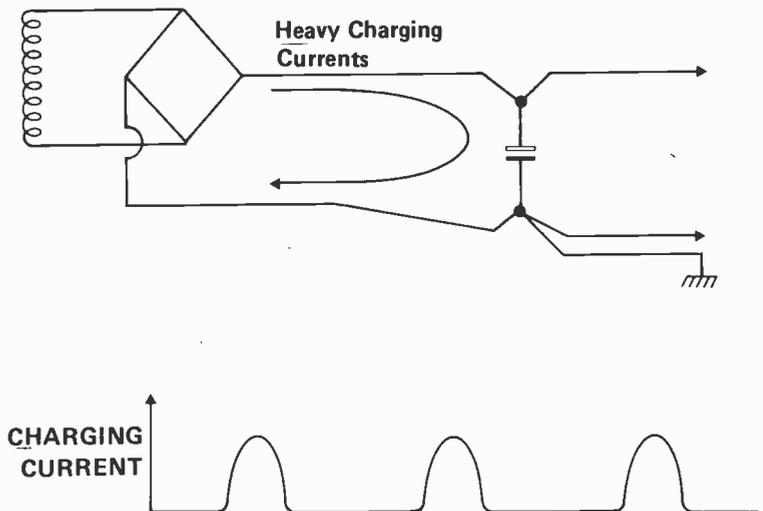The correct layout is shown below the circuit. If the current surge is 1 A and the track resistance is 20 milliohms then the voltage developed will be 20 mVpp.



## Voltage regulators

A voltage regulator takes a varying unregulated input voltage and produces a fixed regulated output voltage. There is a wide range of fixed voltage three terminal regulators to choose from, with a choice of maximum current handling, output voltage and positive or negative operation. The data sheets for these devices contain lots of seemingly complex pieces of information and so a glossary of terms is now included.

## Ripple Rejection

The ratio of the ripple voltage at the regulator input to that at the output, generally expressed in dB. Typically of the order of 60 dB (1000 to 1), that is 1 Vpp of ripple at the input ends up as 1 mVpp at the output.

## Temperature Coefficient

The output voltage change for a change in regulator temperature, expressed in mV/°C.

## Input Voltage range

The range of voltages over which the regulator will function normally. For example, a 12V regulator may work from 14V5 to 30V. At 14V5 the regulator will 'drop out' and lose its regulation. Regulators generally need 2 to 2V5 in excess of their output voltage. At 30V the regulator will go 'pop' (time to buy a new one).

## Output voltage

The voltage at the output terminal with respect to ground. Generally within  $\pm 5\%$  of stated value.

## Line Regulation

The ratio of the change in the output voltage caused by a change in the input voltage, typically of the order of 0.2%.

## Load Regulation

The output voltage change for a specific change in output load current.

## Short Circuit Current

The output current when the output is shorted to ground.

## Output Noise Voltage

The RMS noise voltage measured at the regulators output, not including any ripple.

## Power Dissipation

The maximum power that the regulator can safely generate on a particular heatsink.

As a rule of thumb the regulator case should not exceed about 80°C (which is hot to touch). However, always run the device at as low a temperature as possible. It is thermal ageing that eventually kills electronic devices and for higher temperatures the ageing process is disproportionately faster.


Some applications of voltage regulators are given below.

The table below relates the secondary voltage of a transformer to the peak voltage at rated load and the off load voltage, which will be considerably higher.

TABLE ONE

| V secondary at rated load | V peak at rated load | V peak off load transformer regulation 20% |
|---------------------------|----------------------|--|
| 5 VRMS                    | 7V07                 | 8V48                                       |
| 6 VRMS                    | 8V48                 | 10V18                                      |
| 9 VRMS                    | 12V72                | 15V26                                      |
| 10 VRMS                   | 14V14                | 16V97                                      |
| 12 VRMS                   | 16V97                | 20V36                                      |
| 15 VRMS                   | 21V21                | 25V45                                      |
| 20 VRMS                   | 28V28                | 33V93                                      |
| 25 VRMS                   | 35V35                | 42V42                                      |
| 30 VRMS                   | 42V43                | 50V92                                      |
| 35 VRMS                   | 49V50                | 59V40                                      |
| 40 VRMS                   | 56V57                | 67V88                                      |

T092 plastic

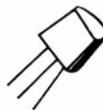

or

T05 metal



(100mA rating)

T05 metal



or

T0202 plastic power




(200mA rating)



T0202 TO220 (500mA)




T03 metal (2A)

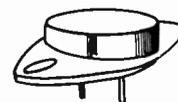


T03 metal (3A)

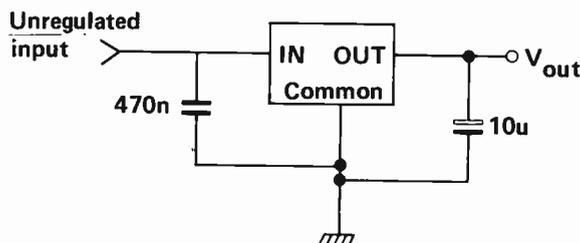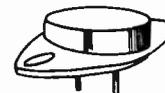

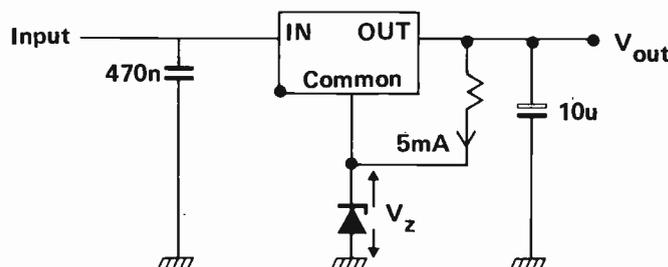
A) This circuit shows a conventional arrangement of a three terminal device. It is advisable to use a decoupling capacitor connected close to the input terminals. This prevents high frequency instability. If this capacitor is left out then regulation can sometimes be greatly reduced. The decoupling capacitor on the output helps reduce the impedance at high frequencies, where the regulator loses its performance. For best results use a tantalum capacitor.



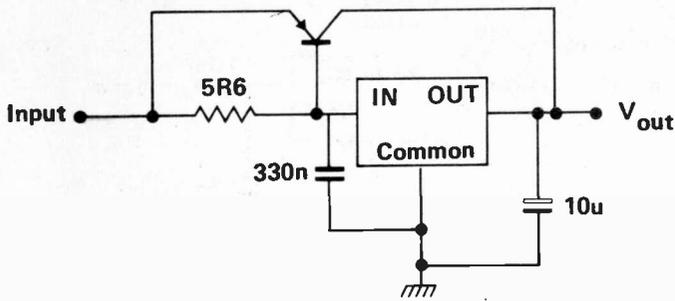B) The output voltage of a regulator can be increased by applying a voltage to the common terminal. This can be done by using a zener diode.



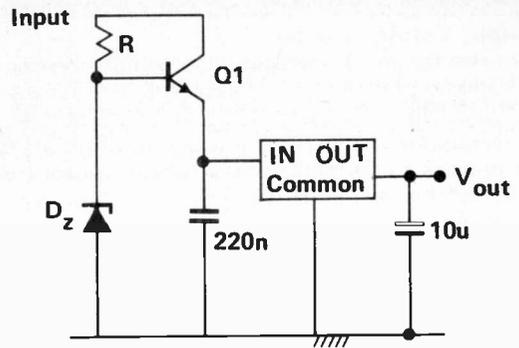C)  
The output current can be increased by using a bypass transistor. When the current flowing through the voltage regulator exceeds 100 mA (the voltage across the 5R6 being 560 mV), the bypass transistor begins to turn on. This transistor takes all currents in excess of 100 mA and yet the output still remains regulated. However a few extra components are needed to get current limiting in the transistor path.




D)  
A high voltage unregulated supply can cause problems when using regulators. It may at times exceed the maximum voltage rating of the regulator. A simple voltage regulator  $D_z$  and Q1 can be used to overcome this problem.  $D_z$  should be chosen so that it is about 6V greater than the regulator output voltage. This technique has the added advantage that the power dissipated in the regulator is less (the rest being dissipated in Q1), and the regulator is presented with a semiregulated voltage, so the output will have less ripple.
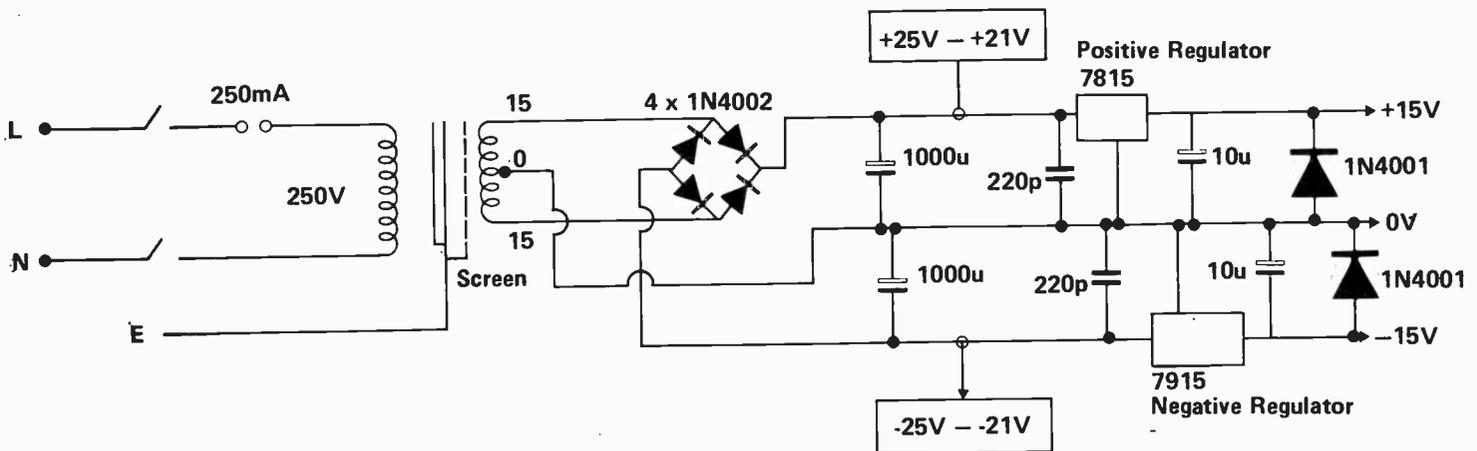
### Dual Power Supply


The circuit shows a complete regulated dual power supply. The unregulated rails are obtained from a split secondary transformer, a bridge rectifier and two smoothing capacitors. A positive and a negative regulator have been used to generate the + and - rails. These regulators should be mounted on heat sinks

and they should be insulated. The pin out of the negative regulator is different to that of the positive regulator. The two diodes at the output prevent latching up situations (on load) whereby one side starts up faster than the other and forcibly reverse biases it, preventing it from operating.


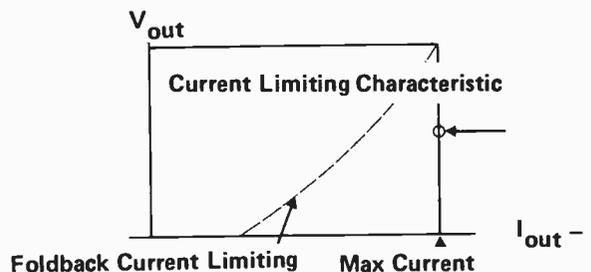
### Tracking Regulator


Instead of using a negative voltage regulator to obtain the negative rail, an op amp and a power transistor can be used. The resistor ratio, R1, R2 determines the negative rail voltage. The negative rail is not, however, current limited. The internal current limiting of the regulator is shown. When the load current exceeds the current limit, the output voltage drops to almost 0V. This makes the regulator short circuit protected. Another type of current protection is known as 'FOLD BACK' current limiting (shown dotted). This serves to reduce the short circuit current. These devices protect the power supply from abuse. Another type of protection device is the overvoltage clamp, which



protects the 'non-power supply electronics' from an increase in the power supply voltage. These are two terminal heavy current devices which are placed across the power supply. When the supply voltage exceeds a certain level a thyristor is triggered on and clamps the rail to ground. This is intended to pop a fuse and so disconnect the faulty power supply (which is better than replacing a £1,000 worth of IC's).

$$\text{-ve output} = -(\text{+ve output} \times R2/R1)$$

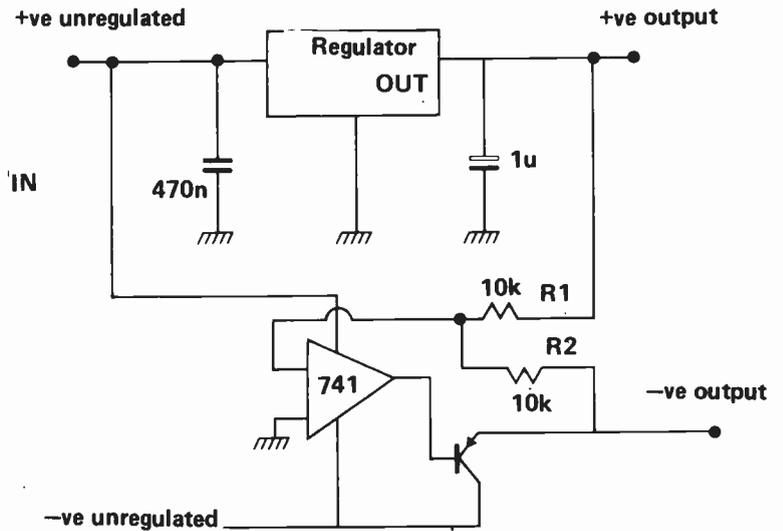
With foldback the short circuit power dissipated in the regulator is less than that with current limiting.


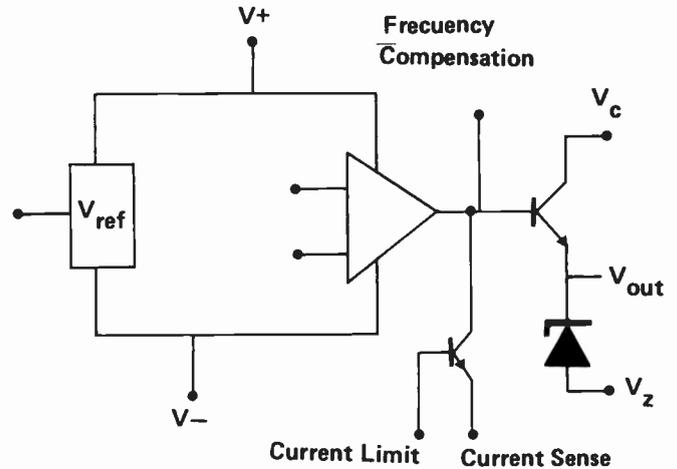
## 723 Voltage Regulator


The 723 is an industry 'standard' device. Many manufacturers produce it and the device itself is versatile. It comes in a 10 pin TO5 can or a 14 DIL pack. The device contains a precision voltage reference, with a temperature coefficient of 50ppm/°C, an error amplifier, an internal transistor capable of handling 100 mA and a current limiting mechanism. By using a few external resistors, a capacitor and maybe an external power transistor, a wide variety of regulator designs can be realised.

Left is shown the block diagram of the 723 regulator. As pinouts vary depending upon package, no pin numbers are shown.



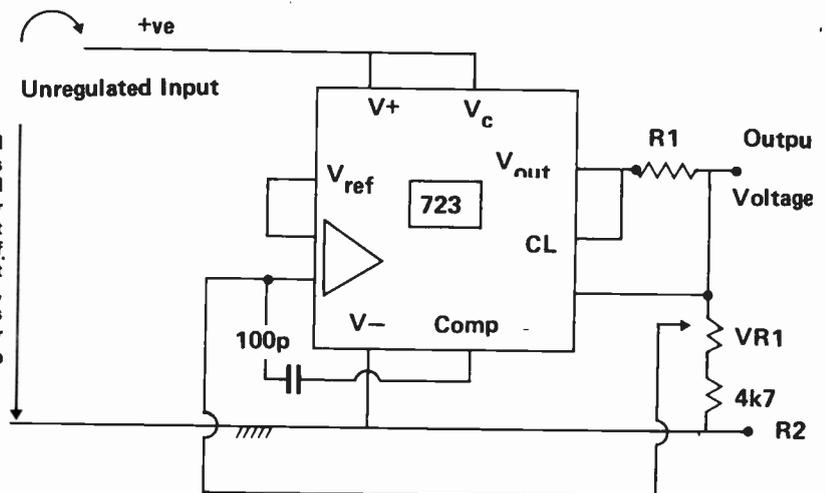
## Adjustable Positive Voltage Regulator

By using a variable feedback path (RV1), a variable regulated output voltage can be generated. The voltage reference is connected to the non-inverting input of the error amplifier and the output voltage (via RV1), to the inverting input. The error amplifier drives the output transistor and hence the output voltage is controlled by the feedback voltage from VR1. A 100pF capacitor is used to stabilise the device. R1 is used as a current limit control. When the current through R1 (the load current), exceeds 100 mA a voltage of 560 mV is set up across it. This is just about sufficient to turn on the current limiting transistor which in turn shorts out the regulating transistor, causing the output voltage to collapse towards 0V.


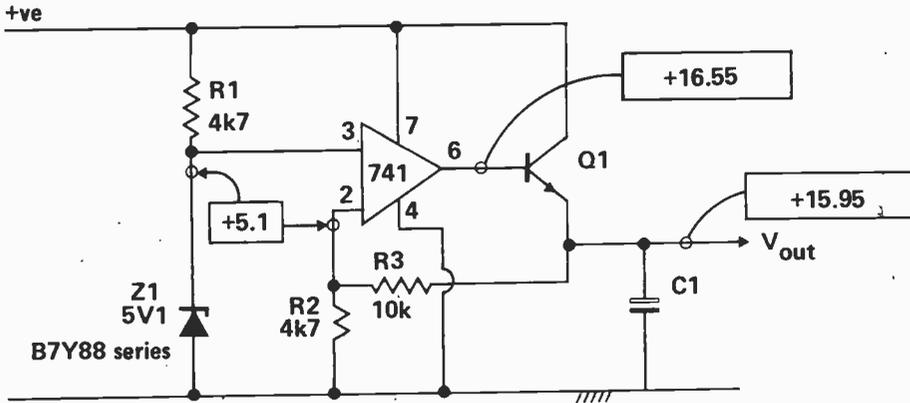
## Regulated Power Supply

Sometimes it is necessary to make a simple power supply using discrete components when a non-standard voltage is required.



Left: Circuit diagram of discrete component PSU. Voltage measurements are taken with high impedance voltmeter.

The circuit shown uses all the basic elements of a voltage regulator, that is, a reference voltage Z1, an error amplifier and a series control Transistor Q1. The zener diode, Z1 sets up a reference voltage of 5V1. This diode has a temperature coefficient of  $-1.2\text{mV}/^\circ\text{C}$  (a 5V6 zener is best at  $-0.2\text{mV}/^\circ\text{C}$ ). The resistor ratio of R3 and R2 sets the output voltage and the op amp provides the error correction (the regulation).


C1 is used to reduce the output impedance at high frequencies. The zener diode has a slope resistance of  $76\Omega$ , and so any fluctuations in the unregulated rail will be attenuated by the ratio of 76:7:0.016

R1 4700

Therefore a 1 Vpp ripple will end up as 16 mVpp, but will be multiplied by the gain of the R3, R2 network to nearly 50mV.
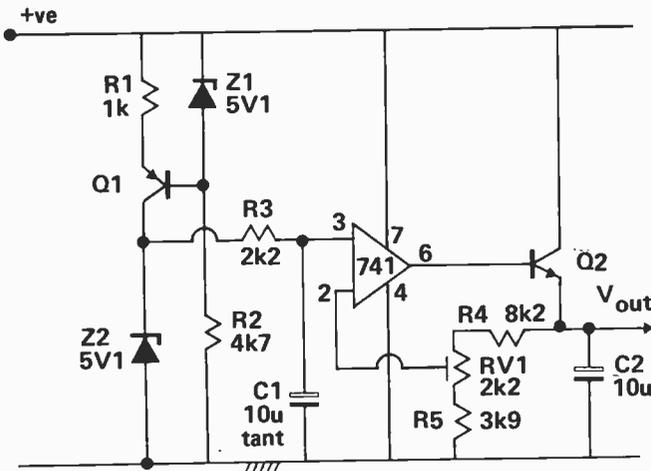
## Improved Regulated power supply

This power supply has various improvements over that shown. The reference zener Z2 is run at almost constant current by the R12, Q1 Z1 network. This makes Z2 much less sensitive to ripple and unregulated supply fluctuations. The filter R3 C1 (7 HZ low pass), further reduces any ripple voltage and noise from the zener diode. The preset VR1 allows the output voltage to be varied.



If a precision power supply is required then a precision voltage reference should be used. These can be obtained with temperature coefficients as low as  $10\text{ppm}/^\circ\text{C}$ . When using this level of stability, high stability resistors ( $\text{TC} = 10\text{ppm}/^\circ\text{C}$ ), and a low drift op amp should be used. Also, to reduce mains carried interference (mainly sharp clicks due to electric motors and thyristors turning on), a mains filter should be used. This is a passive inductor capacitor low pass filter network which attenuates high frequency spikes and clicks.

ETI

## MAINS OPERATED ELECTRONIC DIGITAL ALARM CLOCK

IMMEDIATE DELIVERY

£8.95

INCL. V.A.T. POST PAID

THREE FOR £26.00 POST FREE

ETI RECOMMEND THIS MODEL

BARCLAY ACCESS

Just phone in number

- Hanimex HC-1100
- Large Bright LED display
- White case with red display on black background
- Adjustable dim/bright control
- Silent operation, all electronic
- Space age technology L.S.I. circuitry
- Alarm and 9 minute snooze repeater
- P.M. indicator
- Hour and minute display
- Size 100mm x 130mm x 60mm high
- Fully guaranteed



**HENRY'S**  
RADIO

**HENRY'S RADIO**  
404 Edgware Rd. London W2  
PHONE (01)723 1008

# New Sinclair DM235 digital multimeter.

3½ digits...6 functions...fully portable...

Under £50!



The DM235 incorporates the most important features of a bench-top meter into a rugged yet lightweight instrument for true portability. High accuracy, resolution and input impedance mean superior performance to analogue meters – but at a price significantly lower than many. The DM235's design and specification makes it ideal for all but the most demanding applications.

#### Big, bright, unambiguous display

Full 3½ digit display, reading to  $\pm 1999$ . 8 mm LEDs, ultra wide angle of view.

#### Six functions, 26 ranges

DC Volts..... 1 mV to 1000V  
 AC Volts..... 1 mV to 750 V  
 DC Current..... 1  $\mu$  A to 1A  
 AC Current..... 1  $\mu$  A to 1A  
 Resistance..... 1  $\Omega$  to 20 M $\Omega$   
 Diode test..... 0.1  $\mu$  A to 1 mA  
 10 M $\Omega$  input impedance.

#### High accuracy

Basic accuracy of 0.5% (2 V DC range).  
 Other DC ranges and Resistance 1.0%.  
 AC ranges 1.5% 30 HZ – 10 kHz.

#### Easy to use, by anyone, anywhere

Automatic polarity operation, automatic decimal point placement, automatic out-of-range indication.

#### Lightweight but strong

High-impact moulded ABS case, size 10 in x 5.8 in x 1.6 in. Weight less than 1½ lb. Basic operation from disposable cells, for independence from AC supply. Line operation available via optional AC charger/adaptor.

#### A full range of optional accessories

DM235 meter complete with test leads and prods..... £49.80  
 AC adaptor/charger 240 V 50 HZ..... £3.50  
 Eveready carrying case with lead stowage compartment..... £8. 50  
 Rechargeable battery units..... £ 8.00  
 30 KV high voltage probe..... £15.00

(All prices subject to 8% VAT)

#### Find out more!

Sinclair Radionics are one of the world's largest producers of digital multimeters – the DM235 embodies over seven years' experience. It comes with a full 12 month guarantee. If you'd like to know more about the DM235, send the coupon below. We'll send all the facts (and a list of distributors) by return.

Sinclair Radionics Ltd, St Ives, Huntingdon, Cambs., PE17 4HJ.

**sinclair**

World leaders in fingertip electronics

To: Sinclair Radionics Ltd, St Ives, Huntingdon, Cambs., PE17 4HJ.

Please send me full illustrated details of the new Sinclair DM235.

Name \_\_\_\_\_

Position \_\_\_\_\_

Company \_\_\_\_\_

Address \_\_\_\_\_

ETI

# A MERRY CHRISTMAS & A HAPPY 'VIDEO TIME' NEW YEAR

## BARGAIN TV GAMES STAND ALONE KITS

Kits — full instructions, all PCB components. Mini kits — instructions, chip, skt, coil, PCB

|   | kits   | minikits |
|---|--------|----------|
| B&W Tank Battle (AY-3-8710)                   | £15.90 | £9.75    |
| B&W Stunt Rider (AY-3-8765)                   | £15.90 | £9.95    |
| B&W Road Race (AY-3-8603)                     | £14.90 | £8.50    |
| B&W 10 Game B/B (AY-3-8610)                   | £13.50 | £8.50    |
| <b>NEW</b> B&W Submarine/Spacewar (AY-3-8605) | TBA    | TBA      |
| B&W Wipeout/Breakout (AY-3-8606)              | £14.90 | £8.50    |

**LOW COST SOLUTION**

## MERCURY COMMANDER — Ready Built and Guaranteed

Made in Britain by Teleng — £37.95 with 10 games + accessories



CARTRIDGES — suitable for all Teleng Type Games VAT Inc.

Ready-made Road Race **£9.95**  
Stunt Rider with control **£13.95**  
Tank Battles with control **£21.50**  
Wipeout **£10.95**  
Breakout



**ATTRACTIVE PRICES**

## ATARI VIDEO COMPUTER

with big range of Cartridges 7 currently available plus NEW Breakout, Basic Math, Basketball



**£139.95** VAT Inc. with Combat Cartridge

Just look at these offers! plus we will match any better price offer

**£13.45** VAT Inc. most Cartridges

DETAILS ON REQUEST

## UNBELIEVABLE WATCH BARGAINS



VT01 5 FUNCTION LCD. Hour. Min. Sec. Month. Date. S/S strap. Backlight.

**ONLY £7.95**



VT07 12 FUNCTION CHRONOGRAPH Hour. Min. Sec. DATE. Month. 1/100th Sec. Time. 1 or 2 Event.

**ONLY £13.95**

VT03 SOLAR ALARM Hour. Min. Sec. Month. Date. Day. alarm-any time in 24 hour day.

**ONLY £22.95**



VT08 ALARM ONLY version of VT05

**ONLY £21.95**



VT05 CHRONOGRAPHY / ALARM Dual Time Zone Chrono lap time alarm

**ONLY £35.95**

VT09 STOPWATCH Version of VT01

**ONLY £8.95**



VT06 ALARM/STOPWATCH CLOCK & Snooze Alarm. Stop watch.

**ONLY £12.95**

★ Prices include VAT, packing & delivery charges and money back guarantee. Send cheque or P.O. to 56 Queens Road, Basingstoke, Hants RG21 1REA Tel: (0256) 56417. Telex: 858747.



## VIDEOTIME PRODUCTS

We welcome Barclay & Access Orders by telephone (Trade and Export enquiries welcome)



## TRANSFORMERS

Panel Meters, Bridge Rectifiers, Power Supply Units  
Multimeters - Semi Conductors - Timers - Safeloc

### Miniature & Sub Miniature

| Volts           | Milli-amps | Ref. No. | Price £ | P&P |
|-----------------|------------|----------|---------|-----|
| 3-0-3           | 1A 1A      | 238      | 1.95    | 55  |
| 0-6-0-6         | 100        | 212      | 2.60    | 55  |
| 9-0-9           | 330 330    | 13       | 1.85    | 40  |
| 0-9-0-9         | 500 500    | 235      | 1.95    | 40  |
| 0-8-9-0-8-9     | 1A 1A      | 207      | 2.35    | 55  |
| 0-15-0-15       | 1A 1A      | 208      | 3.50    | 55  |
| 0-20-0-20       | 200 200    | 236      | 1.95    | 40  |
| 0-20-0-20       | 300 300    | 214      | 2.35    | 70  |
| 20-12-0-12-20   | 700(DC)    | 221      | 3.10    | 70  |
| 0-15-20-0-15-20 | 1A 1A      | 206      | 4.20    | 85  |
| 0-15-27-0-15-27 | 500 500    | 203      | 3.65    | 70  |
| 0-15-27-0-15-27 | 1A 1A      | 204      | 4.75    | 95  |

### 12 AND/OR 24 VOLT

| Amps | Ref. No. | Price £ | P&P  |
|------|----------|---------|------|
| 0.5  | 111      | 1.95    | 55   |
| 1.0  | 213      | 2.30    | 70   |
| 2    | 71       | 2.90    | 70   |
| 4    | 18       | 3.75    | 70   |
| 8    | 108      | 6.25    | 1.00 |
| 10   | 72       | 6.95    | 1.00 |
| 12   | 116      | 7.85    | 1.00 |
| 16   | 17       | 9.25    | 1.10 |
| 20   | 115      | 12.75   | 1.30 |
| 30   | 187      | 16.60   | 1.30 |
| 60   | 226      | 22.90   | 1.60 |

### 30 VOLT (Pri. 220-240V)

| Amps | Ref. No. | Price £ | P&P  |
|------|----------|---------|------|
| 0.5  | 112      | 2.45    | 70   |
| 1.0  | 79       | 3.05    | 70   |
| 2.0  | 3        | 4.80    | 85   |
| 3.0  | 20       | 5.80    | 1.00 |
| 4.0  | 21       | 6.85    | 1.00 |
| 5.0  | 51       | 7.75    | 1.00 |
| 6.0  | 117      | 9.50    | 1.00 |
| 8.00 | 88       | 11.35   | 1.30 |
| 10.0 | 89       | 12.00   | 1.30 |

CATALOGUE 30p

### 50 VOLT (Pri. 220-240V)

| Amps | Ref. No. | Price £ | P&P  |
|------|----------|---------|------|
| 0.5  | 102      | 3.20    | 70   |
| 1.0  | 103      | 4.20    | 85   |
| 2.0  | 104      | 6.10    | 1.00 |
| 3.0  | 105      | 7.85    | 1.00 |
| 4.0  | 106      | 9.80    | 1.10 |
| 6.0  | 107      | 14.95   | 1.30 |
| 8.0  | 118      | 15.75   | 1.50 |
| 10.0 | 119      | 20.50   | 2.00 |

### 60 VOLT (Pri. 220-240V)

| Amps | Ref. No. | Price £ | P&P  |
|------|----------|---------|------|
| 0.5  | 124      | 3.40    | 70   |
| 1.0  | 126      | 4.65    | 85   |
| 2.0  | 127      | 6.50    | 1.00 |
| 3.0  | 125      | 9.15    | 1.10 |
| 4.0  | 123      | 11.25   | 1.30 |
| 5.0  | 40       | 11.80   | 1.30 |
| 6.0  | 120      | 14.75   | 1.40 |

### AUTO TRANSFORMERS

| VA (Watts) | Ref. No. | Price £ | P&P |
|------------|----------|---------|-----|
| 20         | 113      | 2.25    | 70  |
| 75         | 64       | 3.50    | 70  |
| 150        | 4        | 5.35    | 85  |

### MAINS ISOLATING (Centre Tapped & Screened)

| VA (Watts) | Ref. No. | Price £ | P&P  |
|------------|----------|---------|------|
| 60         | 149      | 5.75    | 85   |
| 100        | 150      | 6.40    | 1.00 |
| 200        | 151      | 10.00   | 1.10 |
| 250        | 152      | 11.95   | 1.30 |
| 350        | 153      | 14.45   | 1.40 |
| 1000       | 156      | 35.00   | 3.00 |

PROGRAM NAME

TO RUN IN

K DATE

MACHINE



**MICRODIGITAL LTD**

QUALITY DATA CASSETTE

## LOOK FOR THE LABEL!

The Micro-Digital "own-brand" C15 Cassette means high quality, specially made for your micro-computer.


- ★ Tape made against DIN reference tape 45513/16 C528V with anti-static carbon additive.
- ★ Five screw case fixing and transport mechanism using precision stainless steel roller axles.
- ★ Two special graphite impregnated slip shields guide tape edges to prevent pack scramble and dispel residual static.

10 quality C15 cassettes with library cases & special labels **£4.75** (inc. VAT & P + P)

**MICRODIGITAL LTD**  
25 Brunswick St., Liverpool L2 0BJ. Tel: 051-236 0707
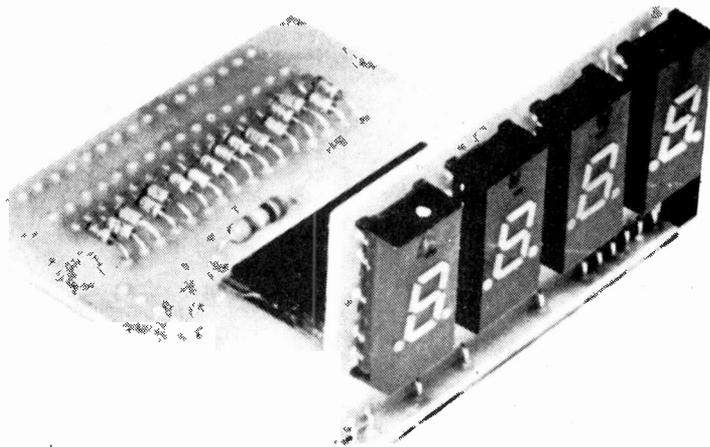
# DIGITAL MODULE

- \* 4 digit
- \* up/down counting
- \* drives LEDs directly
- \* latch
- \* presettable
- \* second register
- \* equal and zero outputs
- \* DC to 2MHz
- \* 5V operation



THE THREE DIGIT display we previously published has proved to be one of our most popular projects. We have used it in a number of projects and we know of several commercial companies using it in their own equipment.


Many people have asked us for a 4 digit version and we have been looking round at ICs available. We have chosen this Intersil device because we believe it offers the best versatility at the moment. Apart from being a 4-digit counter-decoder driver needing no external components except the displays, it also is an up-down counter and can be preset to any number. In addition, it has a separate register which also can be set to any number and comparators which give outputs when the counter is equal to the register and when it is zero — all in one IC!

## Mod Build

The unit is built on two small PCBs which are connected together with short links of tinned copper wire. Be careful to orientate the IC correctly as it is expensive!

The preset system is designed to use a 4 digit BCD thumbwheel switch

Fig 1. Full circuit diagram of the counter module. The How It Works section for this is given overleaf — but as this is really a "How To Use It" section it don't matter — does it?

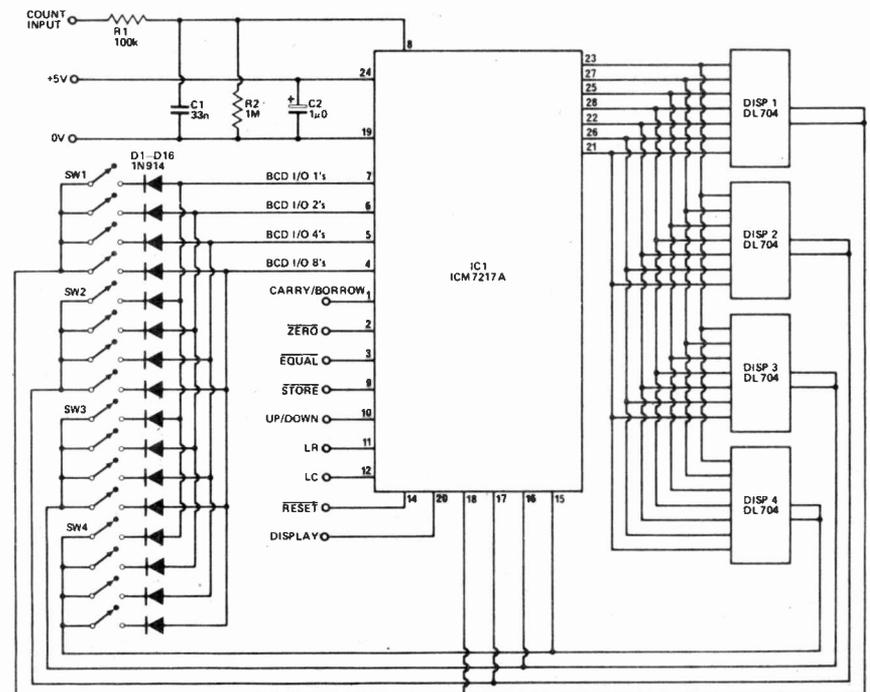

## SPECIFICATION

|                   |            |
|-------------------|------------|
| Number of digits  | 4          |
| Readout           | LED        |
| Maximum frequency | 2MHz       |
| Input impedance   | 100k       |
| Output drive      | 1 TTL load |
| Supply voltage    | 4.5 – 5.5V |
| Supply current    |            |
| low power mode    | 500µA      |
| all eights        | 100mA      |

(closed = '1') but individual switches can be used if required. Input is in BCD, therefore the switches will have the weighted values 8, 4, 2 and 1. If the preset is not needed then the diodes can be left out. If a preset is needed, but always to a fixed number, links can be inserted to replace the "on" switches and the other diodes left out.

ETI

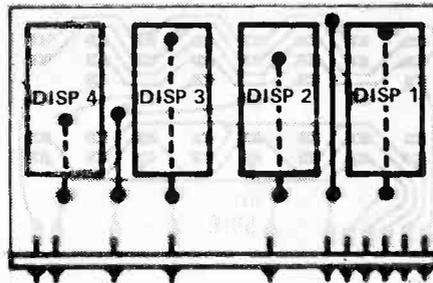


Fig. 2. The positioning of the displays and the links which must be installed before the displays.



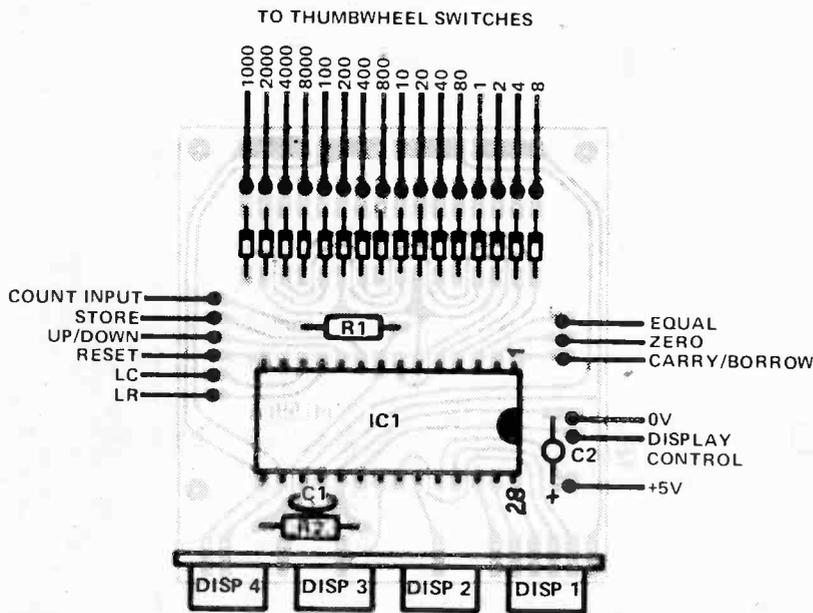
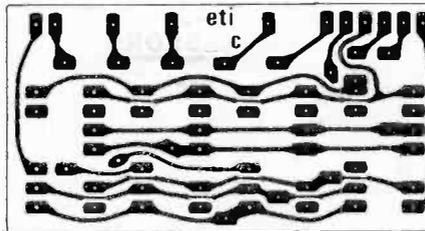


Fig. 3. The component overlay for the main board. The common connection from each of the thumbwheel switches goes to the track next to the other connections.

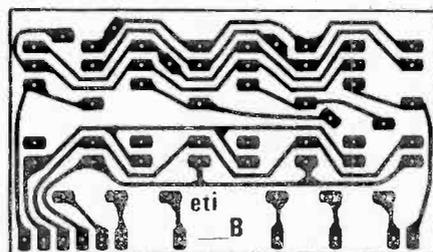

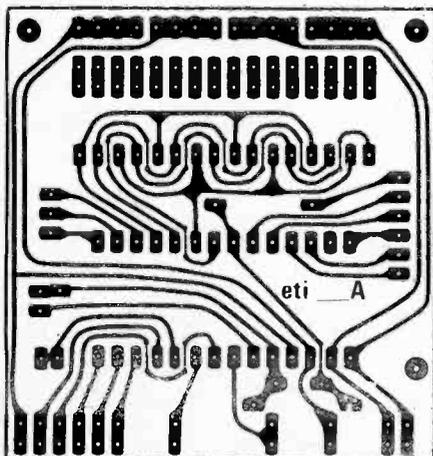Full patterns for the digital module project. Shown full size. Board C — above — is to fit high brightness displays such as employed in our digital dial project.



## HOW IT WORKS

### Count Input — Pin 8

The counter is incremented or decremented on the leading edge of this input. A schmitt trigger is provided with a 500 mV hysteresis on a 2 V trigger point. For high speed operation, or operation from a digital output, delete R2 and C1 and short out R1. Maximum frequency of operation is about 2 MHz.

### Up-Down — Pin 10

If this pin is left open or taken to +5 V the counter will be incremented by the count input. If it is taken to 0 V the counter will be decremented by the count input.

### Reset — Pin 14

If this pin is left open or taken to +5 V the counter is free to be incremented or decremented. If it is taken to 0 V the counters will be reset to zero and held there until reset is taken high again.

### Store — Pin 9

If this input is left open or taken to +5 V the latches are "closed" and the information which was in the counters at the time the store input went high will be remembered, decoded and displayed. The counters can be reset, incremented or decremented without affecting the display.

If it is taken to 0 V the counter contents will continuously be displayed for as long as this input is at 0 V. Any change in the counter contents will be shown on the display.

### Load Counter — Pin 12

This is a 3 level input. If it is left open the counter works normally. If it is taken to +5 V the counter is loaded with the BCD data which is set on the thumbwheel switches. If the latch is open, this number will also be displayed. If this input is taken to 0 V the BCD I/O pins become high impedance. If a 3 level input is to be controlled by other logic outputs they must be tristate devices.

### Load Register — Pin 11

This is also a 3 level input. If it is left open the counter works normally. If it is taken to +5 V the register is loaded with the BCD data. If taken to 0 V the circuit goes to a low power state with the multiplexing oscillator stopped, the display off and the BCD I/O pins in a high impedance state. The operation of the counter is unaffected except that there is no display.

## BUYLINES

Since this project is based entirely upon the one chip—ICM 7217A — this is all there is to cause problems! Since it appears in most peoples catalogues we cannot foresee any trouble here. Displays can be any type really — but for outdoor work use high brightness types.

# PROJECT: Digital Module

## Display Control - Pin 20

This is also a 3 level input. If it is left open, leading edge blanking occurs. If all digits are zero then all are blanked. If it is connected to +5 V the display is completely blanked irrespective of the value. If taken to 0 V all digits are ON irrespective of value.

## Scan - Pin 13

The internal multiplexing frequency is nominally 10 kHz giving a digit repetition rate of 2.5 kHz. With a 20 pF capacitor from this point to 0 V the frequency drops to 5 kHz and with 90 pF it is about 1 kHz.

## BCD I/O - Pin 4-7

This is a multiplexed data port, normally an output which can drive 1 TTL load. It becomes an input when either LC or LR is at +5 V. Pin 7 is the least significant bit.

## Digit Drives - Pins 15-18

These are used both to drive the LEDs and to provide data indicating which digit is being presented at the BCD I/O port. Pin 18 is the least significant digit.

## Zero - Pin 2

If the value of the counter is zero this output will be at 0 V.

## Equal - Pin 3

If the value of the counter is equal to the value of the register this output will be at 0 V.

## Carry/Borrow - Pin 1

When the counter goes from 9999 to 0000 or from 0000 to 9999 a 500 ns positive pulse occurs on this output. This is connected to the count input of a second unit when an eight digit display is needed.

# PARTS LIST

## RESISTORS (all 1/2W 5%)

R1 100k  
R2 1M

## CAPACITORS

C1 33n polyester  
C2 1u0 35V tantalum

## SEMICONDUCTORS

IC1 ICM 7217A  
D1-D16 1N914  
DISPLAYS DL704

# Greenbank

(Dept T1E) 92 New Chester Road,  
New Ferry  
Wirral, Merseyside. L62 5AG  
(Tel: 051-645 3391)

TERMS, VAT, C.W.O. Add VAT to all prices at 8% except where stated otherwise. Post etc.: UK 25p (+2p VAT = 27p) per order. Export: NO VAT but add 5p (Europe) and £2.50 elsewhere. (Polys, universities, govt. depts., etc can telephone their orders for immediate dispatch on account.)

## CMOS

These cut prices for Amateur Users and Export. Note: industrial users - quantity prices available.

| Mostly Motorola, RCA |        |        |        |
|----------------------|--------|--------|--------|
| 4000                 | 15p    | 4051   | 72p    |
| 4001                 | 17p    | 4052   | 72p    |
| 4002                 | 17p    | 4053   | 72p    |
| 4006                 | £1.05  | 4054   | £1.10  |
| 4007                 | 18p    | 4055   | £1.28  |
| 4008                 | 87p    | 4056   | £1.34  |
| 4009                 | 50p    | 4057   | £25.70 |
| 4010                 | 50p    | 4059   | £4.80  |
| 4011                 | 18p    | 4060   | £1.15  |
| 4012                 | 18p    | 4061   | £15.67 |
| 4013                 | 42p    | 4062T  | £10.00 |
| 4014                 | 86p    | 4063   | £1.09  |
| 4015                 | 89p    | 4064   | N/S    |
| 4016                 | 45p    | 4065   | N/S    |
| 4017                 | 89p    | 4066   | N/S    |
| 4018                 | 89p    | 4067   | £3.80  |
| 4019                 | 48p    | 4068   | 22p    |
| 4020                 | 99p    | 4069   | 20p    |
| 4021                 | 91p    | 4070   | 23p    |
| 4022                 | 86p    | 4071   | 21p    |
| 4023                 | 29p    | 4072   | 21p    |
| 4024                 | 66p    | 4073   | 21p    |
| 4025                 | 19p    | 4075   | 23p    |
| 4026                 | £1.80  | 4076   | 85p    |
| 4027                 | 45p    | 4077   | 23p    |
| 4028                 | 81p    | 4078   | 21p    |
| 4029                 | 89p    | 4081   | 20p    |
| 4030                 | 58p    | 4082   | 21p    |
| 4031                 | £2.05  | 4085   | 74p    |
| 4032                 | £1.00  | 4086   | 73p    |
| 4033                 | £1.45  | 4089   | £1.50  |
| 4034                 | £1.96  | 4093   | 63p    |
| 4035                 | £1.11  | 4094   | £1.90  |
| 4036                 | £2.45  | 4095   | £1.05  |
| 4037                 | £1.00  | 4096   | £1.05  |
| 4038                 | £1.08  | 4097   | £3.72  |
| 4039                 | £2.45  | 4098   | £1.10  |
| 4040                 | £1.05  | 4099   | £1.45  |
| 4041                 | 40p    | 4096T  | N/S    |
| 4042                 | 75p    | 4100   | £2.50  |
| 4043                 | 94p    | 4101   | £1.61  |
| 4044                 | 90p    | 4102   | £2.12  |
| 4045                 | £1.45  | 4103   | £2.12  |
| 4046                 | £1.28  | 4104   | £1.09  |
| 4047                 | 87p    | 4105   | £1.06  |
| 4048                 | 50p    | 4106   | 61p    |
| 4049                 | 48p    | 4107   | 68p    |
| 4050                 | 48p    | 4108   | £5.36  |
| 40189                | £1.02  | 41109  | £1.02  |
| 40181                | £3.39  | 40181  | £3.39  |
| 40182                | £1.40  | 40182  | £1.40  |
| 40192                | £1.40  | 40192  | £1.40  |
| 40193                | £1.40  | 40193  | £1.40  |
| 40194                | £1.18  | 40194  | £1.18  |
| 40257                | £1.48  | 40257  | £1.48  |
| 4160                 | £1.08  | 4160   | £1.08  |
| 4161                 | £1.08  | 4161   | £1.08  |
| 4162                 | £1.08  | 4162   | £1.08  |
| 4163                 | £1.08  | 4163   | £1.08  |
| 4174                 | £1.08  | 4174   | £1.08  |
| 4175                 | 99p    | 4175   | 99p    |
| 4176                 | 99p    | 4176   | 99p    |
| 4177                 | 99p    | 4177   | 99p    |
| 4194                 | £1.08  | 4194   | £1.08  |
| 4405                 | £6.59  | 4405   | £6.59  |
| 4409                 | £6.59  | 4409   | £6.59  |
| 4410                 | £5.73  | 4410   | £5.73  |
| 4411                 | £9.58  | 4411   | £9.58  |
| 4412VL               | £17.14 | 4412VL | £17.14 |
| 4412FL               | £12.92 | 4412FL | £12.92 |
| 4415V                | £7.50  | 4415V  | £7.50  |
| 4415F                | M/S    | 4415F  | M/S    |
| 4419                 | £2.68  | 4419   | £2.68  |
| 4422                 | £5.00  | 4422   | £5.00  |
| 4431                 | TBA    | 4431   | TBA    |
| 4432                 | £5.32  | 4432   | £5.32  |
| 4435                 | £2.93  | 4435   | £2.93  |
| 4436                 | £1.19  | 4436   | £1.19  |
| 4440L                | £11.58 | 4440L  | £11.58 |
| 4450                 | £2.67  | 4450   | £2.67  |
| 4451                 | £2.67  | 4451   | £2.67  |
| 4452                 | TBA    | 4452   | TBA    |
| 4461                 | £2.18  | 4461   | £2.18  |
| 4462                 | £2.42  | 4462   | £2.42  |
| 4490P                | £6.54  | 4490P  | £6.54  |
| 4490VP               | £4.92  | 4490VP | £4.92  |
| 4700                 | £1.75  | 4700   | £1.75  |
| 4500                 | £5.56  | 4500   | £5.56  |
| 4501                 | 17p    | 4501   | 17p    |
| 4502                 | 91p    | 4502   | 91p    |
| 4503                 | 88p    | 4503   | 88p    |
| 4504                 | £5.71  | 4504   | £5.71  |
| 4505                 | 51p    | 4505   | 51p    |
| 4506                 | 55p    | 4506   | 55p    |
| 4507                 | 51p    | 4507   | 51p    |
| 4508                 | £2.48  | 4508   | £2.48  |
| 4509                 | 99p    | 4509   | 99p    |
| 4511                 | £1.38  | 4511   | £1.38  |
| 4512                 | 81p    | 4512   | 81p    |
| 4514                 | £2.65  | 4514   | £2.65  |
| 4515                 | £2.99  | 4515   | £2.99  |
| 4517                 | £3.82  | 4517   | £3.82  |
| 4518                 | £1.02  | 4518   | £1.02  |
| 4519                 | 51p    | 4519   | 51p    |
| 4520                 | £1.08  | 4520   | £1.08  |
| 4521                 | £1.88  | 4521   | £1.88  |
| 4522                 | £1.08  | 4522   | £1.08  |
| 4524                 | N/S    | 4524   | N/S    |
| 4526                 | £1.08  | 4526   | £1.08  |
| 4527                 | £1.52  | 4527   | £1.52  |
| 4528                 | 99p    | 4528   | 99p    |
| 4529                 | £1.14  | 4529   | £1.14  |
| 4530                 | 85p    | 4530   | 85p    |
| 4531                 | £1.45  | 4531   | £1.45  |
| 4532                 | £1.27  | 4532   | £1.27  |
| 4534                 | £5.13  | 4534   | £5.13  |
| 4536                 | £3.69  | 4536   | £3.69  |
| 4537L                | £13.23 | 4537L  | £13.23 |
| 4538                 | £1.25  | 4538   | £1.25  |
| 4539                 | 91p    | 4539   | 91p    |
| 4541                 | £1.14  | 4541   | £1.14  |
| 4543                 | £1.59  | 4543   | £1.59  |
| 4549                 | £3.69  | 4549   | £3.69  |
| 4552                 | £10.55 | 4552   | £10.55 |
| 4553                 | £3.07  | 4553   | £3.07  |
| 4554                 | £1.19  | 4554   | £1.19  |
| 4556                 | 78p    | 4556   | 78p    |
| 4557                 | £3.86  | 4557   | £3.86  |
| 4558                 | £1.14  | 4558   | £1.14  |
| 4559                 | £3.69  | 4559   | £3.69  |
| 4561                 | 65p    | 4561   | 65p    |
| 4562                 | £5.33  | 4562   | £5.33  |
| 4566                 | £1.59  | 4566   | £1.59  |
| 4568                 | £2.38  | 4568   | £2.38  |
| 4569                 | £2.57  | 4569   | £2.57  |
| 4572                 | 25p    | 4572   | 25p    |
| 4580                 | £5.74  | 4580   | £5.74  |
| 4581                 | £2.62  | 4581   | £2.62  |
| 4582                 | 98p    | 4582   | 98p    |
| 4583                 | 76p    | 4583   | 76p    |
| 4584                 | 43p    | 4584   | 43p    |
| 4585                 | £1.01  | 4585   | £1.01  |
| 4599                 | £2.06  | 4599   | £2.06  |

## VIDEO

UM 1263 Sound Modulator £2.50 [+12 1/2% VAT]  
UM111E36 UHF Ch.36 Vision Modulator £2.50 [+12 1/2% VAT]  
UM1231 UHF Ch.36 Vision Modulator wide bandwidth (for computers etc.) £4.70 [+8% VAT]

## VEROBOARD

0.1" Pitch with copper strips  
2 1/2" x 1 1/2" (pack of 5) 59p  
2 1/2" x 3" 41p  
2 1/2" x 5" 49p  
2 1/2" x 7" £1.52  
3 1/2" x 3" 49p  
3 1/2" x 5" 56p  
3 1/2" x 7" £1.95  
4 1/2" x 7" £2.52  
0.1" Plainboard (no strips)  
3 1/2" x 2 1/2" 28p  
3 1/2" x 5" 45p  
3 1/2" x 7" 51p  
Terminal pins £1.50/500  
V-DIP board 98p  
DIP breadboard £2.42  
Spot face cutter 82p  
Pin insertion tool 99p

## QUARTZ

32.768 KHz (Watch) £3.23  
60 KHz £9.85  
100.0 KHz £3.23  
200.0 KHz £3.92  
204.8 KHz £3.92  
262.144 KHz £3.92  
307.2 KHz £3.92  
312.5 KHz £3.92  
455.0 KHz £4.95  
1.000 MHz £3.62  
1.008 MHz £3.92  
1.8432 MHz £3.62  
2.000 MHz £3.62  
2.09152 MHz £3.23  
2.4576 MHz £3.62  
2.56250 MHz £3.62  
3.000 MHz £3.62  
3.2768 MHz £3.23  
3.579545 MHz £1.95  
4.000 MHz £2.90  
4.032 MHz £3.23  
4.096 MHz £3.23  
4.194304 MHz £3.23  
4.433619 MHz £1.25  
4.608 MHz £3.23  
4.800 MHz £3.23  
4.915 MHz £3.23  
5.000 MHz £3.23  
5.120 MHz £3.23  
5.185 MHz £3.23  
6.000 MHz £3.23  
6.144 MHz £3.23  
6.400 MHz £3.23  
6.55360 MHz £3.23  
7.000 MHz £3.23  
7.168 MHz £3.23  
7.680 MHz £3.23  
7.86432 MHz £3.23  
8.000 MHz £3.23  
8.388608 MHz £3.23  
8.375 MHz £3.92  
9.800 MHz £3.23  
10.000 MHz £3.23  
10.700 MHz £3.23  
11.000 MHz £3.92  
12.000 MHz £3.92  
14.31818 MHz £3.23  
18.000 MHz £3.23  
18.432 MHz £3.23  
20.000 MHz £3.23  
20.134 MHz £3.23  
27.648 MHz £3.23  
38.5666 MHz £3.23  
48.000 MHz £3.23  
100.000 MHz £3.23  
116.000 MHz £3.23

## SOLDERLESS PINS

100/1000 50p/£3.50

## OIL SOCKETS

8/14/16 pin 10p/12p/13p  
18/20/22 pin 18p/20p/25p  
24/28/40 pin 30p/40p/50p

## TIMER ICs

NE555/556 29p/49p

## OP-AMPS

CA 3130E 84p  
CA 3140E 125p  
UA 741 (Texas) 22p  
6X741 (Texas) £1.00

## SPECIAL

MSB 3801 Multilayered 4x0.3" common cathode prime quality £2.95

## LED DISPLAYS

DL-704E/707E £5p  
DL-727E/728E £2.80  
DL-747E/750E £1.00  
FND 500/560 £1.20  
7.680 MHz £3.23  
7.86432 MHz £3.23  
8.000 MHz £3.23  
8.388608 MHz £3.23  
8.375 MHz £3.92  
9.800 MHz £3.23  
10.000 MHz £3.23  
10.700 MHz £3.23  
11.000 MHz £3.92  
12.000 MHz £3.92  
14.31818 MHz £3.23  
18.000 MHz £3.23  
18.432 MHz £3.23  
20.000 MHz £3.23  
20.134 MHz £3.23  
27.648 MHz £3.23  
38.5666 MHz £3.23  
48.000 MHz £3.23  
100.000 MHz £3.23  
116.000 MHz £3.23

## LIQUID CRYSTAL DISPLAY

4x0.5" Digital dot pin OIL £8.95

## CLOCK CHIPS

AY-51224A £2.60  
MK 50253 £5.50  
MK 50262/50366 16.50  
MC 14440 (ICD) £11.58

## SIX DECIMAL COUNTERS

MK 50395/6/7 £8.75  
MK 50398 £6.20

## SPECIAL: 280 DATA PACK

A set of the following 5 280 data manuals and all the related data we can find of interest to the 280 user

c80-page 280 CPU Technical Manual £3.45  
c200-page CMOS Databook (Motorola) £3.50  
CMOS Databook (National) £2.30  
MC 145008 ICU Handbook (Motorola) £2.25  
Understanding Microprocessors (Motorola) £2.75  
M6800 Microprocessor Applications Manual (Motorola) £9.95  
A Guide to SC/MP Programming (Kamtron) £3.50  
A Guide to Kitbug (Kamtron) 75p  
SC/MP Technical Description (National) £2.76  
SC/MP Microprocessor Applications Handbook (National) £3.45  
SC/MP Programming & Assembly Manual (National) £3.00  
AMI Reference Manual (National) £3.45  
16-page data for IMS 8154 ISP-BA/650 (National) 50p  
20-page data for SC/MP II (National) 50p  
CDP 1802 MPU User Manual (RCA) £4.50  
CDP 1802 Subroutines (RCA) £4.50  
COSMAC MPU Guide (RCA) 75p

## 74C

|       |       |        |       |        |       |        |        |
|-------|-------|--------|-------|--------|-------|--------|--------|
| 74C08 | 24p   | 74C09  | 85p   | 74C193 | £1.10 | 74C918 | £1.06  |
| 74C22 | 24p   | 74C53  | 85p   | 74C195 | £1.04 | 74C921 | £1.83  |
| 74C04 | 24p   | 74C85  | £1.04 | 74C200 | £6.78 | 74C922 | £3.66  |
| 74C08 | 24p   | 74C107 | £1.22 | 74C271 | £1.36 | 74C923 | £3.73  |
| 74C10 | 24p   | 74C150 | £4.12 | 74C901 | 54p   | 74C924 | TBA    |
| 74C14 | £1.41 | 74C154 | £3.67 | 74C902 | 54p   | 74C925 | £4.84  |
| 74C20 | 24p   | 74C157 | £2.20 | 74C903 | 54p   | 74C926 | £4.84  |
| 74C30 | 24p   | 74C160 | £1.10 | 74C904 | 54p   | 74C927 | £4.84  |
| 74C32 | 24p   | 74C161 | £1.10 | 74C905 | £7.26 | 74C928 | £4.84  |
| 74C42 | 92p   | 74C162 | £1.10 | 74C906 | 54p   | 74C929 | £11.93 |
| 74C48 | £1.38 | 74C163 | £1.10 | 74C907 | 54p   | 74C948 | TBA    |
| 74C73 | 54p   | 74C164 | £1.04 | 74C908 | 96p   | 80C95  | 54p    |
| 74C74 | 56p   | 74C165 | £1.04 | 74C909 | £1.63 | 80C96  | 61p    |
| 74C76 | 54p   | 74C173 | £1.10 | 74C910 | £6.78 | 80C97  | 54p    |
| 74C83 | £1.29 | 74C174 | £1.31 | 74C911 | TBA   | 82C19  | £4.13  |
| 74C85 | £1.29 | 74C175 | 90p   | 74C912 | £7.13 | 88C29  | £1.93  |
| 74C86 | 64p   | 74C192 | £1.10 | 74C914 | £1.41 | 88C30  | £      |

**SAME AS  
ETI OFFER**

**5 FUNCTION LCD**

Hours, mins, secs, month, date, auto calendar, back-light, quality metal bracelet.



**£7.65**

Guaranteed same day despatch Very slim, only 6mm thick.

**SPECIAL TO ETI READERS GENUINE SOLAR ALARM WATCH**

**Solar + alarm LCD watch**

New advance in High On quartz technology!




\* Hours, mins, secs displayed.  
\* Day, date, day of week.  
\* 24 hour penetrating alarm.  
\* Quality metal bracelet.  
\* Powered from solar panel.  
\* With battery back-up.  
\* Back-light + auto calendar.  
**£24.95**

**\* QUARTZ LCD ALARM \***

Snooze + backlight. Batteries last 1 year approx. Includes batteries and travel pouch. Excellent value

**£17.65**

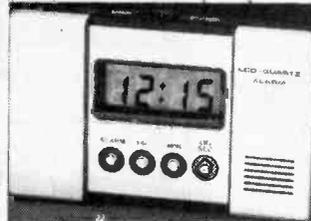

Guaranteed same day despatch

**THOUSANDS SOLD 11 FUNCTION SLIM CHRONO**

6 digit 11 functions  
\* Hours, mins, secs.  
\* Day, date, day of week.  
\* 1/100, 1/10, secs, 10 x secs, mins.  
\* Split and lap modes.  
\* Back light, auto calendar.  
\* Only 8 mm thick.  
This same watch is being sold for £22.00 in newspaper and magazine special offer ads.



**Metac Price £12.65**

Guaranteed same day despatch

**SEIKO SUPERIOR WATCHES**

World famous piercing alarm chronograph  
Please ring for delivery details



**ALARM CHRONO**  
List price £130  
**Metac Price £98**

**SEIKO SUPERIOR WATCHES**

Please ring for delivery details



**CHRONOGRAPH**  
List price £85  
**METAC PRICE £68**

**SEIKO**

SUPERIOR WATCHES 6 digit, 7 function watch with 4 alarms & volume control.  
Please ring for delivery details.



**MULTIPLE ALARM**  
List price £120  
**METAC PRICE £98**

**SEIKO**

SUPERIOR WATCHES Full spec. calculator + 6 function watch.  
Please ring for delivery details.



**CALCULATOR WATCH**  
List price £165  
**METAC PRICE £125**

**HANIMEX Electronic LED Alarm Clock**

Same as ETI offer  
Thousands sold



**Feature and Specification**  
\* Hour/minute display  
\* Large LED display with p.m. and alarm on indicator  
\* 24 Hours alarm with on-off control  
\* Display flashing for power loss indication  
\* Repeatable 9-minute snooze  
\* Display bright/dim modes control  
Size 5.15 x 3.93 x 2.36 (131mm x 100mm x 60mm)  
Weight: 1.43 lbs (0.65 kg).

Guaranteed same day despatch

**£8.65**

**GENUINE SOLAR**

5 function LCD

\* Solar panel with battery back-up.  
\* Back light + auto calendar.  
\* Hours, mins, secs, day, date.  
\* Quality metal bracelet.

**£10.95**

Guaranteed same day despatch



**LADIES LCD**

Only 25 x 20 mm and 6 mm thick. 5 function: hours, mins, secs, day, date, + back light and auto cal. Elegant metal bracelet in silver or gold. State preference.

**£10.95**

Guaranteed same day despatch



**ALARM LCD**

6 digit 7 functions + penetrating alarm.  
Hours Mins Secs Day Date Alpha Day Year.  
Back light + 200 year calendar.

**ONLY £21.95**



**THE METAC DIGITAL CLOCK \* COMPLETE KIT \***

- Pleasant green display - 12/24 Hour readout
- Silent Synchronous Accuracy - Fully electronic
- Pulsating colon - Push-button setting
- Building time 1 Hr - Attractive acrylic case
- Easy-to-follow instructions - Size 10.5 x 5.7 x 8 cm
- Ready drilled PCB to accept components

**PRICE £6.65**



**MICRO CASSETTE RECORDER**

Hand-held only 2 1/2 x 5 x 1 1/2 inch. Identical to well known models being sold at £35

**OUR PRICE £24**



**SINCLAIR SCIENTIFIC PROGRAMMABLE**  
+ free program library worth £4.00

**ONLY £11.65 FROM METAC**

All products carry full 12 months guarantee. Please add 30p p&p with all orders. All prices include VAT.

Shops open 9.30 to 6.00 daily.

Trade enquiries welcome. **Delivery: One week.** Except where same day delivery is stated.

**COMPONENTS**

2N3055 transistors 50p  
.2 inch LED's, red 12p  
green 15p  
yellow 15p  
orange 15p

DL 704 displays 80p  
DL 707 displays 80p  
Watch batteries 70p (state type)  
Mercury tilt switches 50p  
Crystal mic. inserts 50p

Also useful for sonic applications and sound transmitters (buzzers etc)


**GENUINE SOLAR CHRONOGRAPH**

**£16.95**

6 digit, 11 function.  
Hours Min Secs  
1/100 1/10 Secs Mins  
Split & lap modes,  
Auto cal + back light.  
Powered from solar panel with battery back-up.



**TV GAMES**

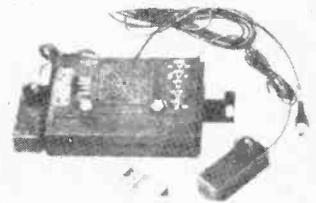

Black & white £8.95 Colour £12.95. 4 games, 2 ball speeds, 2 ball angles, 2 bat sizes.



**67 HIGH STREET  
DAVENTRY, NORTHANTS  
Tel. (032 72) 76545**

**METAC Electronics & Time Centre**

**327 EDGWARE ROAD  
LONDON W2  
Tel. (01) 723 4753**

Barclay & Access welcome  
Phone or Send Card Number  
with order




### SUPERIOR INDUCTION BALANCE METAL DETECTOR



- ★ Visual meter with audible indication.
- ★ Distinguishes between gold, silver, copper, bronze and non-ferrous metals and useless metal objects such as bottle tops, etc.
- ★ Range up to 10 inches on a single coin. Three feet for large objects.
- ★ Battery lasts 50 hours.
- ★ Telescopic 2-3 1/2 foot stem.
- ★ Volume & tuning controls.

**METAC PRICE £28.65**

### LCD CLOCK RADIO

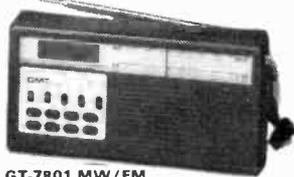

**GT-7801 MW/FM LCD CLOCK RADIO.** Radio with earphone and DC jack. IC controlled clock gives minimum 15,000 hrs. battery life from UM3x1. Features Wake to music or alarm, sleep timer, snooze, dual time zones, stop watch function, time lock-on/off, back light. 190 x 97 x 43mm.

**METAC PRICE £22.95**

### FLUORESCENT DISPLAY CLOCK RADIO



- ★ Mains operated
- ★ Soft glow green display
- ★ MW/FM radio
- ★ Alarm with 9 min. snooze feature
- ★ Programmable play-to-sleep setting

**METAC PRICE ONLY £19.95**

### DIGITAL LED CLOCK



- ★ Automatic brightness control
- ★ Weekend alarm cancel
- ★ 9 minute snooze alarm

**OUR PRICE £10.95**

### MILITARY STYLE RADIO

Medium wave. Long battery life. Good sound reproduction.



**SPECIAL OFFER**

**£2.45**

### CASIO SPORTS WATCH

Model F-100  
Black plastic case. (Epoxy based glass filled nylon.) Stop-watch. 11 functions.

**METAC DISCOUNT PRICE £23.95**

### CASIO CHRONOGRAPH 45CS-22B

**£49.95**

### CASIO WORLD TIME WATCH 29cs-11B

**£59.95**



### METAL DETECTOR

**8FO** Principal Audible indication Telescopic stem Ideal for beginners but also excellent for finding hidden pipes and wires



**ONLY £11.95**

### CBM ALARM WATCH

Superb 6 digit, 8 function alarm watch, with snooze repeater and conference warning bleep. (It beeps once 4 seconds before alarm sounds giving option to cancel). Hours - Mins - Secs. - Day - Date - Month - Back Light - Auto Call.



Top quality CBM finish

**METAC PRICE £29.95**

### CBM EXTRA LARGE DIGIT 5 FUNCTION LCD

- ★ Hours mins secs
- ★ Month date Auto calendar
- ★ Back-light
- ★ Real leather strap
- ★ Big digits in a slim 9mm thin case
- ★ Digits 50% larger than all other watches.



**METAC SPECIAL OFFER £9.95**

### CBM CALCULATORS

**METAC Discount price**  
72 Step programmable model PR100 **£36.85**  
Full scientific 3 memory model 4912 **£12.14**  
Full scientific 9 memory model 9190 **£24.95**



### RADIO CONTROLLED CAR

A fabulous new toy will give hours of fun. Forward and reversing controls. Outdoor range 150 ft. Indoor range 50 ft. A scale model of Bertoni's famous Lancia sports car. List price as sold in well-known mail order catalogues and top stores. £16.

**METAC SPECIAL CHRISTMAS PROMOTION OFFER**

**£11.95**



### AQ-1000 CALCULATING ALARM CLOCK PLUS 3-WAY STOPWATCH

- ★ Calculator with  $\frac{1}{2}$ ,  $\sqrt{\quad}$  & memory.
- ★ Continuous clock with
- ★ Hrs, mins, secs, day, month, day of week
- ★ Alarm
- ★ Stop-watch with 1/10 secs to 40 hrs + lap and split-time modes, 1st and 2nd.
- ★ Batteries last 1 year continuous operation
- ★ Dimensions 1 1/4" x 2 1/4" x 4 1/4" in.
- ★ Complete with leatherette wallet.

LIST PRICE £21.95

**METAC SPECIAL EXCLUSIVE PRICE**


**£19.95**

Cannot be found cheaper anywhere else


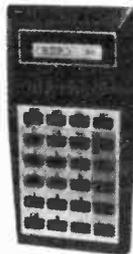
### GOOD QUALITY CALCULATOR MODEL 3000

x + - memory constant, per cent, 8 digits with red display.



**METAC SPECIAL OFFER £3.95**

### ALARM CHRONOGRAPH WITH DUAL TIME ZONE FACILITY

- Constant LCD display of hours and minutes, plus optional seconds or date display, plus day of the week and am/pm indication.
- Perpetual calendar, day, date, month and year.
- 24 hour alarm with on/off indication.
- 1/100 second chronograph measuring net, lap and first and second place times.
- Dual time zone facility. Night light.



### Telephone Special 24-hour phone service

Credit-card customers are welcome to buy by phone — simply phone 01-723 4753 with your credit-card number to place your order.

- Fully adjustable bracelet.

Please note Metac are probably the only people with this watch in stock. A very good alarm watch.

**METAC PRICE ONLY £29.95**

### PLEASE NOTE

All our products carry full money back 10-day reassurance.

Watches are despatched by **FIRST-CLASS POST**. They are fitted with new batteries, and include guarantee and instructions.

Battery fitting service is available at our shops for no extra charge. We stock most watch batteries and this service is available to all.

Metac have been selling electronic watches probably longer than anyone else in the UK. We take care of your watch not just this year but next year and the years after that.



**67 HIGH STREET DAVENTRY, NORTHANTS**  
Tel. (032 72) 76545

## METAC Electronics & Time Centre

**327 EDGWARE ROAD LONDON W2**  
Tel. (01) 723 4753

Barclay & Access welcome  
Phone or Send Card Number with order



# A HISTORY OF ELECTRONICS IN MEDICINE

THE USE OF ELECTRICITY FOR medical purposes dates back to the Ancient Greeks who used the electric eel to treat various maladies. In 1759 Wesley collected case histories of the use of electricity. The first recorded use of electricity for treatment in a hospital in London was in 1767.

Not quite 200 years ago, in 1786 to be precise, Professor Luigi Galvani — an anatomist at the University of Bologna, Italy — discovered by chance that the muscles of a dead frog contracted under the influence of an electrical quantity.

He wrongly assumed that animal electricity stored within the muscle caused this to happen. It was, in fact, the result of dissimilar metals forming a primary electric cell which energised the nerves of the muscle. Volta of the University of Paris proved it and subsequently gave the world the voltaic battery, in 1800.

The contribution of these two men provided, in the simple primary cell, a workable basis for using electricity in practical ways not previously possible with the electro-static form of electricity. Galvani's work on "animal fluid" was amongst the earliest electro-medical studies. The apparatus he used was crude by today's standards — see Fig. 1.



Fig. 1. Artist's idea of Galvani experimenting with frogs' legs in the 1780s. Note the friction electrostatic generator on the left and the Leyden jar on the right (Funk and Wagnells).

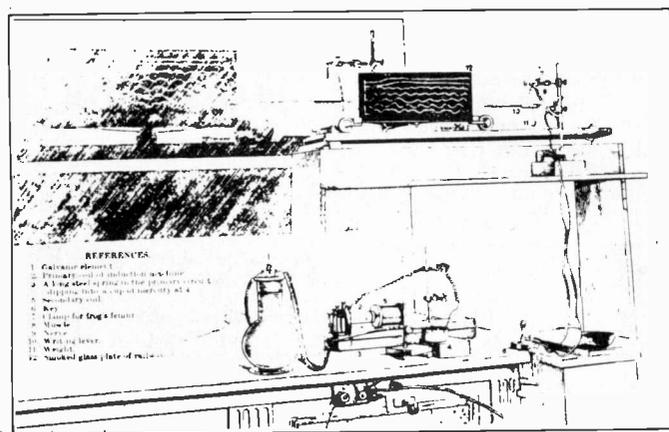



Fig. 2. Apparatus used by McKendrick to give lectures on life in motion to Royal Institution, London, audiences around 1890.

## Body Electric?


Research into physiological electric quantities gradually became more sophisticated as the 19th century passed. This development, however, had to wait for suitable experimental inventions such as the electromagnetic galvanometer which became available in its crudest form around 1830. A typical laboratory electro-medical instrumentation set-up of the 1890s is shown in Fig 2. A smoked glass plate moved steadily across the end of a mechanical pen secured to the end of a frog's leg muscle. The muscle was energised by high-voltage generated from a vibration induction coil which was energised by a chromate primary single cell of the Grenet kind. Smoked screen recorders are still in use today in some medical research measurements, blood flow parameters being one example.

The sphygmometograph (as a pulse measuring instrument was known in that time) was originated by Marey in 1860. A later design by Verdin is shown in Fig 3. Electronic method was little used in medicine in early times, as powerful electric signal amplification was not obtainable until the beginning of the 20th century —

**Electricity has long been used for medical purposes, here's the story of the past and a look into the future. By Peter Sydenham.**

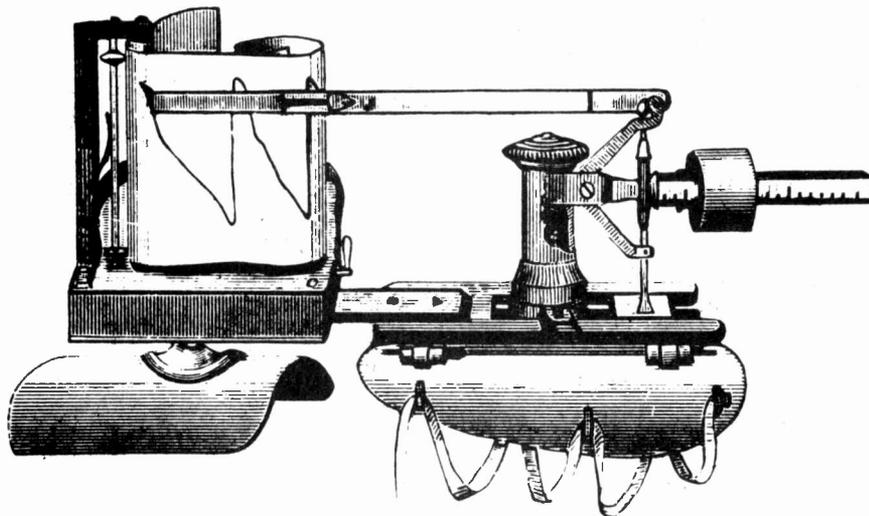

**Fig. 3. Verdin's apparatus of the 1890s for recording action of the pulse.**

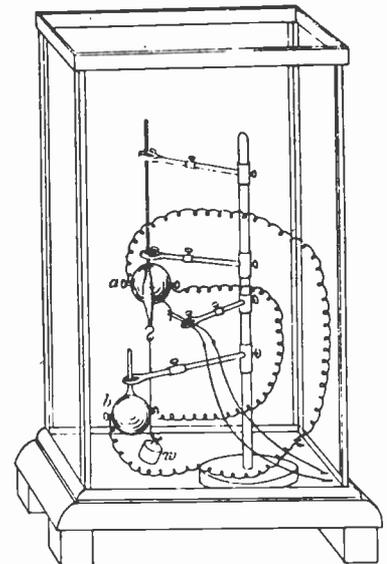

**Fig. 4. Schematic of McKendrick's 1891 method for measuring heat generation in muscle.**

when the thermionic valve was invented by Fleming (in 1904).

Figure 4 shows experimental equipment for measuring heat production of muscular contraction around 1880. Thermocouples, forming a thermopile, drive the crude galvanometer.

**Ion Therapy**

Another aspect of medicine where electricity is used is for therapeutic treatment. Since the very early 1800s output of the various kinds of electric current generator, namely the Faraday induction coil, the galvanic chemical battery, the sinewave rotating generator and the friction statical generator have been applied to appropriate parts of the body to provide a cure for all sorts of ailments.

X-ray equipment was born in 1895 when Roentgen discovered X-rays in a chance situation using photographic plates. There is probably no case in instrument history where application was more rapid. Edison, and others, had equipment in use in hospitals within months. Figure 5 shows contemporary American X-ray plant of 1899.

Measurement and recording of heart performance also began around 1900. Professor Einthoven of Holland devised a rapid response, high sensitivity detection instrument in 1903 — the string galvanometer. Soon after this was coupled to a photographic recording system, by the Cambridge Instrument Co., to produce an electrocardiograph. The first installation of this was made in 1909. By 1945 cardiographs were available in portable form. Figure 6 shows the interior of a 1930s. Both Brothers portable electro-cardiograph invented and made in Adelaide, South Australia — possibly one of the first portable units devised anywhere. It used a loud speaker drive unit (right) to mark a rotating smoked disk.

The record was viewed by the physician using an optical magnifier. Amplification to drive the stylus from skin electrode signals was obtained by thermionic tubes.


As with all disciplines, electronic method opened the door to new accomplishments. In medical electronics it happened from the 1920s onward. Equipment for researching physiology at Oxford University, in 1949 is shown in Fig 7. The unit, advanced for its time, incorporated amplifiers, a temperature control unit, stimulators to induce responses, a time base and a cathode ray tube display unit.

Electronic equipment used in medicine has come a long way during the past 50 years. This can be seen by comparing the apparatus pictured above, which covers the 1800s to 1930s period, with modern equipment such as that used in pathological testing and nuclear medicine.

**Future**

Against this background let me now suggest developments we can expect to experience over the next quarter century.

**Fig. 5. Complete X-ray apparatus in use in America around 1900. Note the lack of safety devices and precautions.**

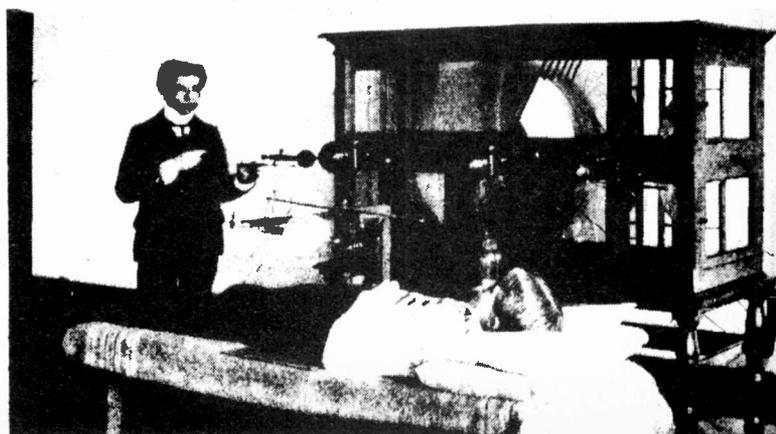

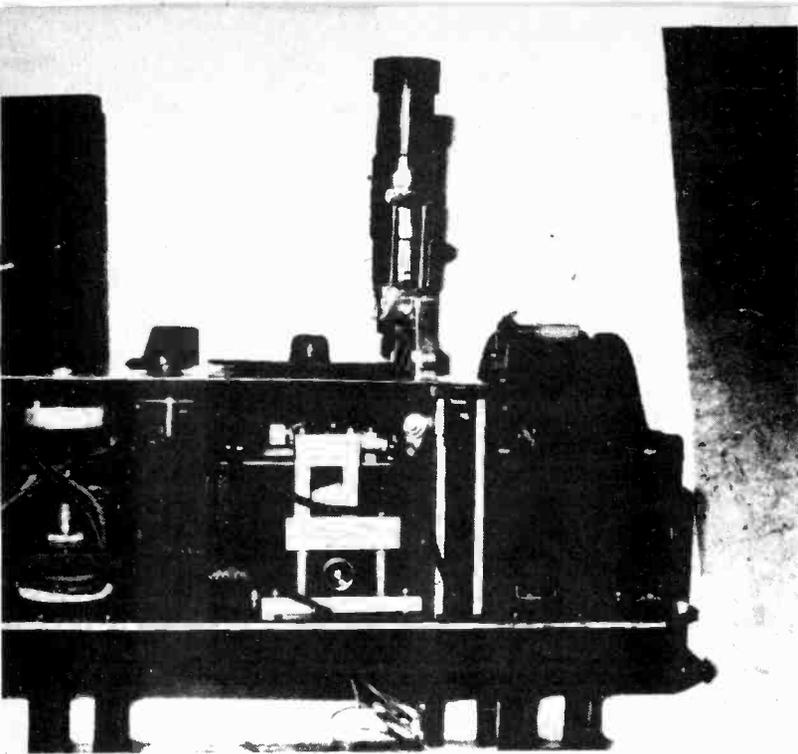


Fig. 6. Interior view of a Both portable electro-cardiograph machine made in Adelaide around 1930.

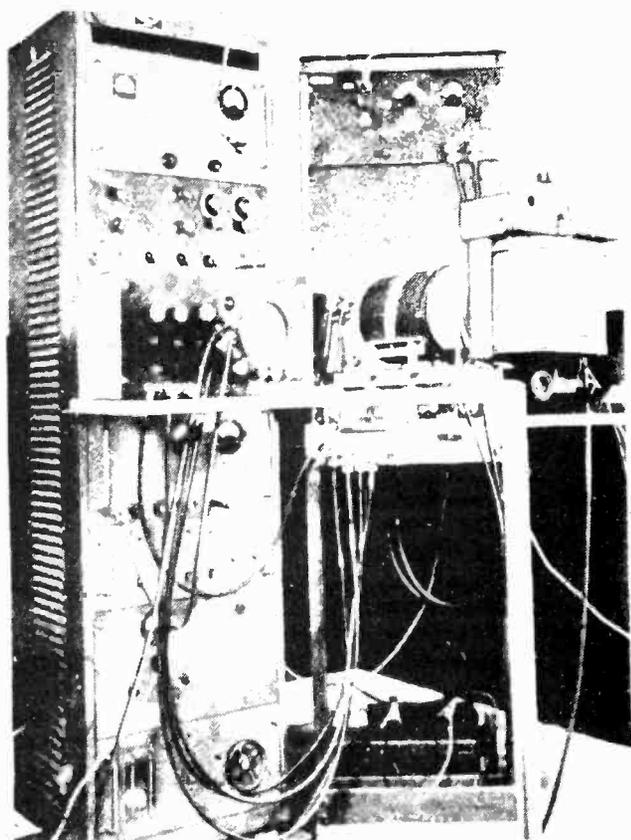


Fig. 7. E Electro-physiological research equipment used by Dickinson at Oxford University in 1949.

## Monitoring

The largest proportion of electro-medical equipment is concerned with measurement; for detection of abnormal states. At present comparatively few of the incredibly great range of medical measurements needed can be made in situ on the body and without disturbing its functions. Samples of tissue, blood, urine, etc. are removed for analysis in the pathological laboratory. This process, although performed faster today than ever before, can still take several hours before a diagnosis is available to the physician in order that he or she can decide corrective action. Analysers now exist that handle many measurements of a sample entirely automatically once the sample is loaded into the analyser. But the sample must first be extracted from the body and then be transported to the machine, processes which consume time and in some circumstances alter the sample from its original state.

It is realistic to expect the transport step to be eliminated in the future with most local clinics having their own units for analysis of samples. The next stage in progress will come about by the invention of units that measure parameters such as blood count, albumin, etc. by contact externally to a suitable vein or artery. Direct measurement like this would also provide more accurate measurement as the blood would be in its normal working state. Furthermore, it would then be possible rapidly to optimize drug dosage and to investigate changes in parameters as they happen. The concept of in-situ measurement will apply to numerous other tests.

In special cases some people have already been equipped with sensors of critical body parameters. The outputs are telemetered to a remote observer. Examples of this are in space-medicine, in fitness studies and in a few heart disease cases.

## Microbody

Considering the low-cost data processing power already available, and coupling this with inexpensive micro-miniature sensors we can expect to see developed in the future, it is possible that individuals will one day be able to obtain self-monitors that provide warning when body parameters exceed allowable limits.

Better measurements always leads to better control. As an example, respiratory tract problems, such as hay fever and asthma, are hard to combat effectively because of the lack of detailed data about each individual's characteristics in the various circumstances encountered. Not all people are allergic to the same pollens — we could benefit greatly if an easy way existed that determined the allergic pollens involved.

At present, a pollen count is usually taken by drawing the ambient air over a sticky surface for many minutes — hours sometimes. The surface is then observed with a microscope, the technician counting all pollen grains together to obtain the total pollen count. This process is now sometimes carried out using computer-controlled video TV camera systems, but the systems are still barely able to group the various kinds of pollen grain. (They are typically a micrometre in diameter or smaller — counts of a few grains per cubic metre can cause unwanted symptoms.)

A development that could help is a sensor that provides a virtually instant count of the individual kinds of pollen grain present — a real-time sampling analyser.

With such a device the sufferer could test for the hostile situation *before* symptoms arise and take remedial action in time. Technologically such an instrument appears feasible. It is, however, cost and physical size that holds up its development and its practical everyday use at present.

A likely parallel already existing is the Coulter counter that analyses the size and number of cells in a blood sample. Blood-cell counting of several years ago required the blood to be smeared on a microscope slide and the cells counted by eye under a microscope. Today the machine makes the measurements in a few seconds by counting particles as they pass a small orifice — but it is neither portable nor inexpensive. Figure 8 shows a Coulter counter installation as used in the larger pathological laboratories.

Development of personal monitors will almost certainly pass first through a telemetry method in which a central computer processes the data, perhaps with the help of the trained physician to begin with. A direct self-contained method will then be developed in which the specific data processing requirements that have emerged from experience, are integrated into the unit.

## Sensors

The human body is a vastly complicated chemical process plant. It has sensors feeding information to the brain for central processing. In turn, the brain sends signals to actuators — the muscles which cause the body to function and to do work. Nerves are the hardwired data channels for receiving and sending control information.

Slight deficiencies in the senses of sight and hearing have been aided using instruments — spectacles and hearing aids. The latter began as acoustic horns which provided sound pressure gain without active amplification. The advent of the telephone led to amplifierless hearing aids in the 1900's which used several mouthpieces coupled to the ear pieces (Fig 9). Then came electronic units which provided active signal gain from miniature thermionic tubes. Today we have integrated semi-conductor circuitry. We have still a way to go, however, before we are able to compensate for a failed action of the inner ear mechanism.

Vision, until very recently, was aided only by optical lens compensation. But this applies only where the eye is still largely operative as an optical-to-electrical transducer. Quite recently experiments have been reported in which a miniature video camera provides electronic signals that drive cells in the brain to provide illusion of sight. The method is still crude compared with the performance of natural process. Given time for research it seems reasonable to assume that quite compact and useful artificial eyes will soon be available for blind people. Bionic man is not so fantastic! Interestingly, once the bionic eye is developed it is an easy matter to provide greater than natural visual acuity and to offer sensitivity to other than the visible light band — infra-red for instance.

Providing electronic replacements for the sense of smell will most likely be a much later development. We know too little about the olfactory senses and have no really compact and cheap smell sensors at this time to expect great progress to occur in the near future.

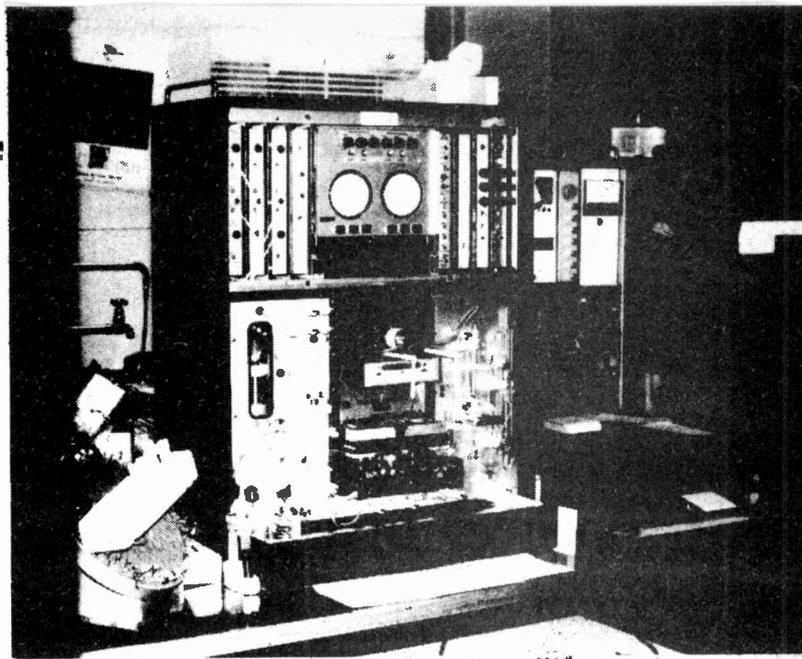


Fig. 8. Coulter counter unit of today that analyses blood sample particles providing a printout (IMUS, Adelaide).

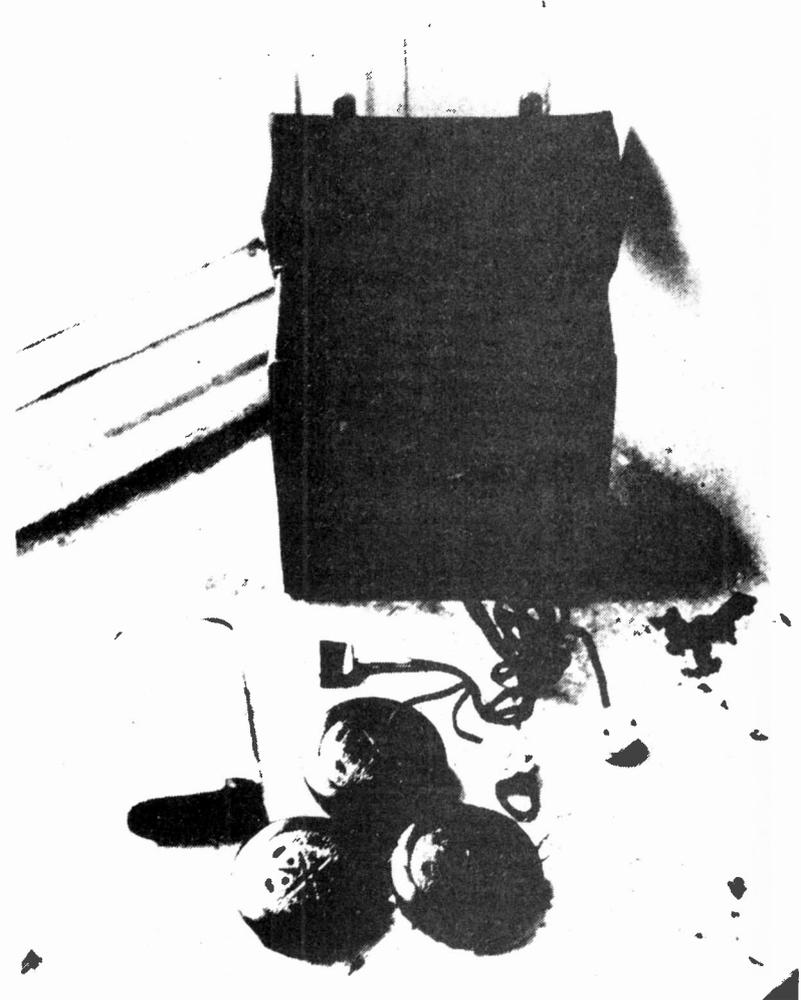


Fig. 9. 1900's hearing aid. The three receivers, which fit into the case, provide signal to the two earpieces. No active amplifier was involved. (Birdwood Mill Museum, S.A)

# FEATURE : Electronics in Medicine

Animals, such as dogs, possess a sense of smell vastly much more sensitive than humans. Ants track each other by a scent trail! Yet man has not yet produced small and inexpensive chemical analysers (small is a largely chemical process) that can meet the complex sensing requirements of smell detection.

## Scanners

X-ray and nucleonic diagnostic methods have the valuable feature that certain internal structures of the body can be seen. But all such methods lack the spatial resolution we obtain by visual examination with the unaided eye or through a microscope. A nuclear radiation source set-up within the body provides a rather diffuse output picture. Resolution is improved by increasing the number of individual elements at the sensing stage. The gamma camera, for example, provides two-dimensional pictures using over thirty scintillometers connected in such a way as to provide many more picture elements. The latest development senses the body area by scanning multiple sensors thereby collecting yet more data in a given time. Sophisticated processing is then used to provide video screen outputs which contain much more useful information than ever before. Similar techniques apply to X-ray, nucleonic and ultrasonic signal transmission. Now that vastly more powerful data processing capability exists the future development will be to incorporate many more sensors of the same kind and make more effective use of three-dimensional data. Other variables, such as, say, thermal emission will also be incorporated along with systematic experience gained into the processing, all this to providing data conversion for a more meaningful measurement process.

## Surgery

Electrical methods in surgery traditionally include endoscopes with which to see into inaccessible places and cauterizing probes for sealing blood flow, cutting and destroying cells where need be. The recent introduction of the laser as a cutting tool has most valuable properties. Selection of the appropriate wavelength decides which kind of body tissue will be cut. For example, it is possible to weld the retina of the eye through the pupil without need for surgery. The radiation is only absorbed by retinal material, the pupil and fluid of the eye ball being transparent to the wavelength used.

The selective property of narrow-band radiation will enable some highly precise surgical operations in the future. An operation might go as follows: a rigid framework holds the patient fixed with respect to an x-y-z translating pulsed laser operating head. Wired to the control unit of the translator are electrodes fixed to the body. These sense when low-power sensing pulses are energising the specific part of the body required to be operated upon. The unit scans until sensing signals (operated by a non-cutting wavelength source) verify the location of the beam. Once at such a point the laser is switched to full cutting power continuing to cut as the time-multiplexed sensing signals indicate position is satisfactory.

Looking back, electro-medical apparatus has only been with us for a mere 50 years. In the last 10 years of which we developed inexpensive and very powerful data processing methods. The next 25 years are likely to unfold undreamed of aids to medicine many of which we would regard as miraculous if we heard about them today.

ETI

STRUTT

ELECTRICAL AND MECHANICAL  
ENGINEERING LTD.

3C, Barley Market St.  
Tavistock, Devon PL19 05F.

TAVISTOCK 5439  
TELEX 45263

BUY BIG AND SAVE £££££££

|   |   |   |   |  |   |   |
|---|---|---|---|--|---|---|
| <p><b>Transistor 1+25+100+</b></p> <p>BC107 .09 .095 .088<br/>BC107A/B .10 .095 .075<br/>BC108 .09 .095 .090<br/>BC108A/B/C .10 .095 .075<br/>BC109 .09 .095 .088<br/>BC109C .10 .095 .075<br/>BC147A/B .12 .104 .088<br/>BC149 .12 .104 .088<br/>BC157A/B .13 .114 .106<br/>BC159 .09 .073 .057<br/>BC178 .14 .125 .106<br/>BC178A/B .16 .137 .115<br/>BC187 .24 .217 .182<br/>BC213/B .09 .06 .057<br/>BC237 .12 .104 .088<br/>BC238A/B .10 .081 .068<br/>BC238C .12 .104 .088<br/>BC239 .11 .081 .077<br/>BC239C .11 .081 .077<br/>BC239D .11 .081 .077<br/>BC239E .11 .081 .077<br/>BC239F .11 .081 .077<br/>BC239G .11 .081 .077<br/>BC239H .11 .081 .077<br/>BC239I .11 .081 .077<br/>BC239J .11 .081 .077<br/>BC239K .11 .081 .077<br/>BC239L .11 .081 .077<br/>BC239M .11 .081 .077<br/>BC239N .11 .081 .077<br/>BC239P .11 .081 .077<br/>BC239Q .11 .081 .077<br/>BC239R .11 .081 .077<br/>BC239S .11 .081 .077<br/>BC239T .11 .081 .077<br/>BC239U .11 .081 .077<br/>BC239V .11 .081 .077<br/>BC239W .11 .081 .077<br/>BC239X .11 .081 .077<br/>BC239Y .11 .081 .077<br/>BC239Z .11 .081 .077</p> | <p><b>Transistor 1+25+100+</b></p> <p>2N2006A .21 .19 .16<br/>2N2007 .18 .158 .134<br/>2N2008 .19 .171 .144<br/>2N2009 .21 .19 .16<br/>2N2010 .25 .222 .187<br/>2N2011 .30 .277 .222<br/>2N2012 .30 .277 .222<br/>2N2013 .30 .277 .222<br/>2N2014 .30 .277 .222<br/>2N2015 .30 .277 .222<br/>2N2016 .30 .277 .222<br/>2N2017 .30 .277 .222<br/>2N2018 .30 .277 .222<br/>2N2019 .30 .277 .222<br/>2N2020 .30 .277 .222<br/>2N2021 .30 .277 .222<br/>2N2022 .30 .277 .222<br/>2N2023 .30 .277 .222<br/>2N2024 .30 .277 .222<br/>2N2025 .30 .277 .222<br/>2N2026 .30 .277 .222<br/>2N2027 .30 .277 .222<br/>2N2028 .30 .277 .222<br/>2N2029 .30 .277 .222<br/>2N2030 .30 .277 .222<br/>2N2031 .30 .277 .222<br/>2N2032 .30 .277 .222<br/>2N2033 .30 .277 .222<br/>2N2034 .30 .277 .222<br/>2N2035 .30 .277 .222<br/>2N2036 .30 .277 .222<br/>2N2037 .30 .277 .222<br/>2N2038 .30 .277 .222<br/>2N2039 .30 .277 .222<br/>2N2040 .30 .277 .222<br/>2N2041 .30 .277 .222<br/>2N2042 .30 .277 .222<br/>2N2043 .30 .277 .222<br/>2N2044 .30 .277 .222<br/>2N2045 .30 .277 .222<br/>2N2046 .30 .277 .222<br/>2N2047 .30 .277 .222<br/>2N2048 .30 .277 .222<br/>2N2049 .30 .277 .222<br/>2N2050 .30 .277 .222<br/>2N2051 .30 .277 .222<br/>2N2052 .30 .277 .222<br/>2N2053 .30 .277 .222<br/>2N2054 .30 .277 .222<br/>2N2055 .30 .277 .222<br/>2N2056 .30 .277 .222<br/>2N2057 .30 .277 .222<br/>2N2058 .30 .277 .222<br/>2N2059 .30 .277 .222<br/>2N2060 .30 .277 .222<br/>2N2061 .30 .277 .222<br/>2N2062 .30 .277 .222<br/>2N2063 .30 .277 .222<br/>2N2064 .30 .277 .222<br/>2N2065 .30 .277 .222<br/>2N2066 .30 .277 .222<br/>2N2067 .30 .277 .222<br/>2N2068 .30 .277 .222<br/>2N2069 .30 .277 .222<br/>2N2070 .30 .277 .222<br/>2N2071 .30 .277 .222<br/>2N2072 .30 .277 .222<br/>2N2073 .30 .277 .222<br/>2N2074 .30 .277 .222<br/>2N2075 .30 .277 .222<br/>2N2076 .30 .277 .222<br/>2N2077 .30 .277 .222<br/>2N2078 .30 .277 .222<br/>2N2079 .30 .277 .222<br/>2N2080 .30 .277 .222<br/>2N2081 .30 .277 .222<br/>2N2082 .30 .277 .222<br/>2N2083 .30 .277 .222<br/>2N2084 .30 .277 .222<br/>2N2085 .30 .277 .222<br/>2N2086 .30 .277 .222<br/>2N2087 .30 .277 .222<br/>2N2088 .30 .277 .222<br/>2N2089 .30 .277 .222<br/>2N2090 .30 .277 .222<br/>2N2091 .30 .277 .222<br/>2N2092 .30 .277 .222<br/>2N2093 .30 .277 .222<br/>2N2094 .30 .277 .222<br/>2N2095 .30 .277 .222<br/>2N2096 .30 .277 .222<br/>2N2097 .30 .277 .222<br/>2N2098 .30 .277 .222<br/>2N2099 .30 .277 .222<br/>2N2100 .30 .277 .222</p> | <p><b>Transistor 1+25+100+</b></p> <p>2N2101 .30 .277 .222<br/>2N2102 .30 .277 .222<br/>2N2103 .30 .277 .222<br/>2N2104 .30 .277 .222<br/>2N2105 .30 .277 .222<br/>2N2106 .30 .277 .222<br/>2N2107 .30 .277 .222<br/>2N2108 .30 .277 .222<br/>2N2109 .30 .277 .222<br/>2N2110 .30 .277 .222<br/>2N2111 .30 .277 .222<br/>2N2112 .30 .277 .222<br/>2N2113 .30 .277 .222<br/>2N2114 .30 .277 .222<br/>2N2115 .30 .277 .222<br/>2N2116 .30 .277 .222<br/>2N2117 .30 .277 .222<br/>2N2118 .30 .277 .222<br/>2N2119 .30 .277 .222<br/>2N2120 .30 .277 .222<br/>2N2121 .30 .277 .222<br/>2N2122 .30 .277 .222<br/>2N2123 .30 .277 .222<br/>2N2124 .30 .277 .222<br/>2N2125 .30 .277 .222<br/>2N2126 .30 .277 .222<br/>2N2127 .30 .277 .222<br/>2N2128 .30 .277 .222<br/>2N2129 .30 .277 .222<br/>2N2130 .30 .277 .222<br/>2N2131 .30 .277 .222<br/>2N2132 .30 .277 .222<br/>2N2133 .30 .277 .222<br/>2N2134 .30 .277 .222<br/>2N2135 .30 .277 .222<br/>2N2136 .30 .277 .222<br/>2N2137 .30 .277 .222<br/>2N2138 .30 .277 .222<br/>2N2139 .30 .277 .222<br/>2N2140 .30 .277 .222<br/>2N2141 .30 .277 .222<br/>2N2142 .30 .277 .222<br/>2N2143 .30 .277 .222<br/>2N2144 .30 .277 .222<br/>2N2145 .30 .277 .222<br/>2N2146 .30 .277 .222<br/>2N2147 .30 .277 .222<br/>2N2148 .30 .277 .222<br/>2N2149 .30 .277 .222<br/>2N2150 .30 .277 .222<br/>2N2151 .30 .277 .222<br/>2N2152 .30 .277 .222<br/>2N2153 .30 .277 .222<br/>2N2154 .30 .277 .222<br/>2N2155 .30 .277 .222<br/>2N2156 .30 .277 .222<br/>2N2157 .30 .277 .222<br/>2N2158 .30 .277 .222<br/>2N2159 .30 .277 .222<br/>2N2160 .30 .277 .222<br/>2N2161 .30 .277 .222<br/>2N2162 .30 .277 .222<br/>2N2163 .30 .277 .222<br/>2N2164 .30 .277 .222<br/>2N2165 .30 .277 .222<br/>2N2166 .30 .277 .222<br/>2N2167 .30 .277 .222<br/>2N2168 .30 .277 .222<br/>2N2169 .30 .277 .222<br/>2N2170 .30 .277 .222<br/>2N2171 .30 .277 .222<br/>2N2172 .30 .277 .222<br/>2N2173 .30 .277 .222<br/>2N2174 .30 .277 .222<br/>2N2175 .30 .277 .222<br/>2N2176 .30 .277 .222<br/>2N2177 .30 .277 .222<br/>2N2178 .30 .277 .222<br/>2N2179 .30 .277 .222<br/>2N2180 .30 .277 .222<br/>2N2181 .30 .277 .222<br/>2N2182 .30 .277 .222<br/>2N2183 .30 .277 .222<br/>2N2184 .30 .277 .222<br/>2N2185 .30 .277 .222<br/>2N2186 .30 .277 .222<br/>2N2187 .30 .277 .222<br/>2N2188 .30 .277 .222<br/>2N2189 .30 .277 .222<br/>2N2190 .30 .277 .222<br/>2N2191 .30 .277 .222<br/>2N2192 .30 .277 .222<br/>2N2193 .30 .277 .222<br/>2N2194 .30 .277 .222<br/>2N2195 .30 .277 .222<br/>2N2196 .30 .277 .222<br/>2N2197 .30 .277 .222<br/>2N2198 .30 .277 .222<br/>2N2199 .30 .277 .222<br/>2N2200 .30 .277 .222</p> | <p><b>Transistor 1+25+100+</b></p> <p>2N2201 .30 .277 .222<br/>2N2202 .30 .277 .222<br/>2N2203 .30 .277 .222<br/>2N2204 .30 .277 .222<br/>2N2205 .30 .277 .222<br/>2N2206 .30 .277 .222<br/>2N2207 .30 .277 .222<br/>2N2208 .30 .277 .222<br/>2N2209 .30 .277 .222<br/>2N2210 .30 .277 .222<br/>2N2211 .30 .277 .222<br/>2N2212 .30 .277 .222<br/>2N2213 .30 .277 .222<br/>2N2214 .30 .277 .222<br/>2N2215 .30 .277 .222<br/>2N2216 .30 .277 .222<br/>2N2217 .30 .277 .222<br/>2N2218 .30 .277 .222<br/>2N2219 .30 .277 .222<br/>2N2220 .30 .277 .222<br/>2N2221 .30 .277 .222<br/>2N2222 .30 .277 .222<br/>2N2223 .30 .277 .222<br/>2N2224 .30 .277 .222<br/>2N2225 .30 .277 .222<br/>2N2226 .30 .277 .222<br/>2N2227 .30 .277 .222<br/>2N2228 .30 .277 .222<br/>2N2229 .30 .277 .222<br/>2N2230 .30 .277 .222<br/>2N2231 .30 .277 .222<br/>2N2232 .30 .277 .222<br/>2N2233 .30 .277 .222<br/>2N2234 .30 .277 .222<br/>2N2235 .30 .277 .222<br/>2N2236 .30 .277 .222<br/>2N2237 .30 .277 .222<br/>2N2238 .30 .277 .222<br/>2N2239 .30 .277 .222<br/>2N2240 .30 .277 .222<br/>2N2241 .30 .277 .222<br/>2N2242 .30 .277 .222<br/>2N2243 .30 .277 .222<br/>2N2244 .30 .277 .222<br/>2N2245 .30 .277 .222<br/>2N2246 .30 .277 .222<br/>2N2247 .30 .277 .222<br/>2N2248 .30 .277 .222<br/>2N2249 .30 .277 .222<br/>2N2250 .30 .277 .222<br/>2N2251 .30 .277 .222<br/>2N2252 .30 .277 .222<br/>2N2253 .30 .277 .222<br/>2N2254 .30 .277 .222<br/>2N2255 .30 .277 .222<br/>2N2256 .30 .277 .222<br/>2N2257 .30 .277 .222<br/>2N2258 .30 .277 .222<br/>2N2259 .30 .277 .222<br/>2N2260 .30 .277 .222<br/>2N2261 .30 .277 .222<br/>2N2262 .30 .277 .222<br/>2N2263 .30 .277 .222<br/>2N2264 .30 .277 .222<br/>2N2265 .30 .277 .222<br/>2N2266 .30 .277 .222<br/>2N2267 .30 .277 .222<br/>2N2268 .30 .277 .222<br/>2N2269 .30 .277 .222<br/>2N2270 .30 .277 .222<br/>2N2271 .30 .277 .222<br/>2N2272 .30 .277 .222<br/>2N2273 .30 .277 .222<br/>2N2274 .30 .277 .222<br/>2N2275 .30 .277 .222<br/>2N2276 .30 .277 .222<br/>2N2277 .30 .277 .222<br/>2N2278 .30 .277 .222<br/>2N2279 .30 .277 .222<br/>2N2280 .30 .277 .222<br/>2N2281 .30 .277 .222<br/>2N2282 .30 .277 .222<br/>2N2283 .30 .277 .222<br/>2N2284 .30 .277 .222<br/>2N2285 .30 .277 .222<br/>2N2286 .30 .277 .222<br/>2N2287 .30 .277 .222<br/>2N2288 .30 .277 .222<br/>2N2289 .30 .277 .222<br/>2N2290 .30 .277 .222<br/>2N2291 .30 .277 .222<br/>2N2292 .30 .277 .222<br/>2N2293 .30 .277 .222<br/>2N2294 .30 .277 .222<br/>2N2295 .30 .277 .222<br/>2N2296 .30 .277 .222<br/>2N2297 .30 .277 .222<br/>2N2298 .30 .277 .222<br/>2N2299 .30 .277 .222<br/>2N2300 .30 .277 .222</p> | <p><b>TTL</b></p> <p>7400 .03 .036 .034<br/>7401 .19 .171 .144<br/>7402 .45 .398 .336<br/>7403 .84 .736 .64<br/>7404 .120 .108 .912<br/>7405 .45 .398 .336<br/>7406 .118 .106 .896<br/>7407 .86 .778 .686<br/>7408 .86 .778 .686<br/>7409 .86 .778 .686<br/>7410 .86 .778 .686<br/>7411 .86 .778 .686<br/>7412 .86 .778 .686<br/>7413 .86 .778 .686<br/>7414 .86 .778 .686<br/>7415 .86 .778 .686<br/>7416 .86 .778 .686<br/>7417 .86 .778 .686<br/>7418 .86 .778 .686<br/>7419 .86 .778 .686<br/>7420 .86 .778 .686<br/>7421 .86 .778 .686<br/>7422 .86 .778 .686<br/>7423 .86 .778 .686<br/>7424 .86 .778 .686<br/>7425 .86 .778 .686<br/>7426 .86 .778 .686<br/>7427 .86 .778 .686<br/>7428 .86 .778 .686<br/>7429 .86 .778 .686<br/>7430 .86 .778 .686<br/>7431 .86 .778 .686<br/>7432 .86 .778 .686<br/>7433 .86 .778 .686<br/>7434 .86 .778 .686<br/>7435 .86 .778 .686<br/>7436 .86 .778 .686<br/>7437 .86 .778 .686<br/>7438 .86 .778 .686<br/>7439 .86 .778 .686<br/>7440 .86 .778 .686<br/>7441 .86 .778 .686<br/>7442 .86 .778 .686<br/>7443 .86 .778 .686<br/>7444 .86 .778 .686<br/>7445 .86 .778 .686<br/>7446 .86 .778 .686<br/>7447 .86 .778 .686<br/>7448 .86 .778 .686<br/>7449 .86 .778 .686<br/>7450 .86 .778 .686<br/>7451 .86 .778 .686<br/>7452 .86 .778 .686<br/>7453 .86 .778 .686<br/>7454 .86 .778 .686<br/>7455 .86 .778 .686<br/>7456 .86 .778 .686<br/>7457 .86 .778 .686<br/>7458 .86 .778 .686<br/>7459 .86 .778 .686<br/>7460 .86 .778 .686<br/>7461 .86 .778 .686<br/>7462 .86 .778 .686<br/>7463 .86 .778 .686<br/>7464 .86 .778 .686<br/>7465 .86 .778 .686<br/>7466 .86 .778 .686<br/>7467 .86 .778 .686<br/>7468 .86 .778 .686<br/>7469 .86 .778 .686<br/>7470 .86 .778 .686<br/>7471 .86 .778 .686<br/>7472 .86 .778 .686<br/>7473 .86 .778 .686<br/>7474 .86 .778 .686<br/>7475 .86 .778 .686<br/>7476 .86 .778 .686<br/>7477 .86 .778 .686<br/>7478 .86 .778 .686<br/>7479 .86 .778 .686<br/>7480 .86 .778 .686<br/>7481 .86 .778 .686<br/>7482 .86 .778 .686<br/>7483 .86 .778 .686<br/>7484 .86 .778 .686<br/>7485 .86 .778 .686<br/>7486 .86 .778 .686<br/>7487 .86 .778 .686<br/>7488 .86 .778 .686<br/>7489 .86 .778 .686<br/>7490 .86 .778 .686<br/>7491 .86 .778 .686<br/>7492 .86 .778 .686<br/>7493 .86 .778 .686<br/>7494 .86 .778 .686<br/>7495 .86 .778 .686<br/>7496 .86 .778 .686<br/>7497 .86 .778 .686<br/>7498 .86 .778 .686<br/>7499 .86 .778 .686<br/>7500 .86 .778 .686</p> | <p><b>1+25+100+</b></p> <p>7501 .20 .178 .15<br/>7502 .40 .355 .298<br/>7503 .23 .205 .173<br/>7504 .34 .307 .258<br/>7505 .35 .313 .264<br/>7506 .89 .803 .677<br/>7507 .44 .393 .331<br/>7508 .45 .398 .336<br/>7509 .45 .398 .336<br/>7510 .45 .398 .336<br/>7511 .45 .398 .336<br/>7512 .45 .398 .336<br/>7513 .45 .398 .336<br/>7514 .45 .398 .336<br/>7515 .45 .398 .336<br/>7516 .45 .398 .336<br/>7517 .45 .398 .336<br/>7518 .45 .398 .336<br/>7519 .45 .398 .336<br/>7520 .45 .398 .336<br/>7521 .45 .398 .336<br/>7522 .45 .398 .336<br/>7523 .45 .398 .336<br/>7524 .45 .398 .336<br/>7525 .45 .398 .336<br/>7526 .45 .398 .336<br/>7527 .45 .398 .336<br/>7528 .45 .398 .336<br/>7529 .45 .398 .336<br/>7530 .45 .398 .336<br/>7531 .45 .398 .336<br/>7532 .45 .398 .336<br/>7533 .45 .398 .336<br/>7534 .45 .398 .336<br/>7535 .45 .398 .336<br/>7536 .45 .398 .336<br/>7537 .45 .398 .336<br/>7538 .45 .398 .336<br/>7539 .45 .398 .336<br/>7540 .45 .398 .336<br/>7541 .45 .398 .336<br/>7542 .45 .398 .336<br/>7543 .45 .398 .336<br/>7544 .45 .398 .336<br/>7545 .45 .398 .336<br/>7546 .45 .398 .336<br/>7547 .45 .398 .336<br/>7548 .45 .398 .336<br/>7549 .45 .398 .336<br/>7550 .45 .398 .336<br/>7551 .45 .398 .336<br/>7552 .45 .398 .336<br/>7553 .45 .398 .336<br/>7554 .45 .398 .336<br/>7555 .45 .398 .336<br/>7556 .45 .398 .336<br/>7557 .45 .398 .336<br/>7558 .45 .398 .336<br/>7559 .45 .398 .336<br/>7560 .45 .398 .336<br/>7561 .45 .398 .336<br/>7562 .45 .398 .336<br/>7563 .45 .398 .336<br/>7564 .45 .398 .336<br/>7565 .45 .398 .336<br/>7566 .45 .398 .336<br/>7567 .45 .398 .336<br/>7568 .45 .398 .336<br/>7569 .45 .398 .336<br/>7570 .45 .398 .336<br/>7571 .45 .398 .336<br/>7572 .45 .398 .336<br/>7573 .45 .398 .336<br/>7574 .45 .398 .336<br/>7575 .45 .398 .336<br/>7576 .45 .398 .336<br/>7577 .45 .398 .336<br/>7578 .45 .398 .336<br/>7579 .45 .398 .336<br/>7580 .45 .398 .336<br/>7581 .45 .398 .336<br/>7582 .45 .398 .336<br/>7583 .45 .398 .336<br/>7584 .45 .398 .336<br/>7585 .45 .398 .336<br/>7586 .45 .398 .336<br/>7587 .45 .398 .336<br/>7588 .45 .398 .336<br/>7589 .45 .398 .336<br/>7590 .45 .398 .336<br/>7591 .45 .398 .336<br/>7592 .45 .398 .336<br/>7593 .45 .398 .336<br/>7594 .45 .398 .336<br/>7595 .45 .398 .336<br/>7596 .45 .398 .336<br/>7597 .45 .398 .336<br/>7598 .45 .398 .336<br/>7599 .45 .398 .336<br/>7600 .45 .398 .336</p> | <p><b>TTL</b></p> <p>7601 .16 .144 .122<br/>7602 .16 .144 .122<br/>7603 .16 .144 .122<br/>7604 .16 .144 .122<br/>7605 .16 .144 .122<br/>7606 .16 .144 .122<br/>7607 .16 .144 .122<br/>7608 .16 .144 .122<br/>7609 .16 .144 .122<br/>7610 .16 .144 .122<br/>7611 .16 .144 .122<br/>7612 .16 .144 .122<br/>7613 .16 .144 .122<br/>7614 .16 .144 .122<br/>7615 .16 .144 .122<br/>7616 .16 .144 .122<br/>7617 .16 .144 .122<br/>7618 .16 .144 .122<br/>7619 .16 .144 .122<br/>7620 .16 .144 .122<br/>7621 .16 .144 .122<br/>7622 .16 .144 .122<br/>7623 .16 .144 .122<br/>7624 .16 .144 .122<br/>7625 .16 .144 .122<br/>7626 .16 .144 .122<br/>7627 .16 .144 .122<br/>7628 .16 .144 .122<br/>7629 .16 .144 .122<br/>7630 .16 .144 .122<br/>7631 .16 .144 .122<br/>7632 .16 .144 .122<br/>7633 .16 .144 .122<br/>7634 .16 .144 .122<br/>7635 .16 .144 .122<br/>7636 .16 .144 .122<br/>7637 .16 .144 .122<br/>7638 .16 .144 .122<br/>7639 .16 .144 .122<br/>7640 .16 .144 .122<br/>7641 .16 .144 .122<br/>7642 .16 .144 .122<br/>7643 .16 .144 .122<br/>7644 .16 .144 .122<br/>7645 .16 .144 .122<br/>7646 .16 .144 .122<br/>7647 .16 .144 .122<br/>7648 .16 .144 .122<br/>7649 .16 .144 .122<br/>7650 .16 .144 .122<br/>7651 .16 .144 .122<br/>7652 .16 .144 .122<br/>7653 .16 .144 .122<br/>7654 .16 .144 .122<br/>7655 .16 .144 .122<br/>7656 .16 .144 .122<br/>7657 .16 .144 .122<br/>7658 .16 .144 .122<br/>7659 .16 .144 .122<br/>7660 .16 .144 .122<br/>7661 .16 .144 .122<br/>7662 .16 .144 .122<br/>7663 .16 .144 .122<br/>7664 .16 .144 .122<br/>7665 .16 .144 .122<br/>7666 .16 .144 .122<br/>7667 .16 .144 .122<br/>7668 .16 .144 .122<br/>7669 .16 .144 .122<br/>7670 .16 .144 .122<br/>76</p> |
|---|---|---|---|--|---|---|

# ELECTROVALUE Buying Guide

## Section 2

If you have already bought from Electrovalue, you will know just how large and varied our stocks are and how well your orders are looked after, whether you be beginner or a computer-minded expert. For those who have yet to know, we have been publishing a series of ads. month by month to give you up-to-date information and prices on the more important items we carry so that BY DETACHING AND SAVING THESE PAGES, YOU WILL HAVE A VALUABLE AND COMPREHENSIVE MONEY SAVING CATALOGUE. ALL MERCHANDISE IS BRAND NEW AND GUARANTEED. See below how easy it is to order — and how you save.

Be safe! Be satisfied! Buy it from Electrovalue

## Capacitors

Quantity prices available except for MDC.

| Product               | µF | Volts                        | Price |
|-----------------------|----|------------------------------|-------|
| <b>CERAMIC DISC ●</b> |    |                              |       |
| 500V: 1, 2, 5nF       | 3p | 4.7 16                       | 21p   |
| 50V: 0.02µF           | 3p | 4.7 40                       | 12p   |
|                       |    | 4.7 63                       | 12p   |
|                       |    | 4.7 100                      | 14p   |
|                       |    | 10 6.3                       | 21p   |
|                       |    | 10 25                        | 12p   |
|                       |    | 10 40                        | 12p   |
|                       |    | 10 63                        | 14p   |
|                       |    | 10 100                       | 15p   |
|                       |    | 22 10                        | 12p   |
|                       |    | 22 25                        | 12p   |
|                       |    | 22 40                        | 13p   |
|                       |    | 22 63                        | 15p   |
|                       |    | 22 100                       | 16p   |
|                       |    | 47 3                         | 12p   |
|                       |    | 47 10                        | 12p   |
|                       |    | 47 25                        | 14p   |
|                       |    | 47 40                        | 15p   |
|                       |    | 47 63                        | 16p   |
|                       |    | 47 100                       | 19p   |
|                       |    | 100 3                        | 12p   |
|                       |    | 100 10                       | 14p   |
|                       |    | 100 25                       | 15p   |
|                       |    | 100 40                       | 16p   |
|                       |    | 100 63                       | 22p   |
|                       |    | 100 100                      | 28p   |
|                       |    | 220 3                        | 13p   |
|                       |    | 220 6.3                      | 15p   |
|                       |    | 220 10                       | 15p   |
|                       |    | 220 16                       | 17p   |
|                       |    | 220 25                       | 20p   |
|                       |    | 220 40                       | 24p   |
|                       |    | 220 63                       | 30p   |
|                       |    | 220 100                      | 47p   |
|                       |    | 470 10                       | 19p   |
|                       |    | 470 16                       | 24p   |
|                       |    | 470 25                       | 22p   |
|                       |    | 470 40                       | 31p   |
|                       |    | 470 63                       | 45p   |
|                       |    | 470 100                      | 74p   |
|                       |    | 1000 3                       | 15p   |
|                       |    | 1000 6.3                     | 22p   |
|                       |    | 1000 10                      | 21p   |
|                       |    | 1000 16                      | 30p   |
|                       |    | 1000 25                      | 40p   |
|                       |    | 1000 40                      | 45p   |
|                       |    | 1000 63                      | 76p   |
|                       |    | 2200 3                       | 23p   |
|                       |    | 2200 10                      | 30p   |
|                       |    | 2200 16                      | 35p   |
|                       |    | 2200 25                      | 45p   |
|                       |    | 2200 40                      | 70p   |
|                       |    | 2200 63                      | 84p   |
|                       |    | 2200 100                     | 110p  |
|                       |    | 4700 16                      | 85p   |
|                       |    | 4700 25                      | 96p   |
|                       |    | 10000 3                      | 40p   |
|                       |    | 10000 10                     | 40p   |
|                       |    | 10000 16                     | 40p   |
|                       |    | 10000 25                     | 40p   |
|                       |    | 10000 40                     | 40p   |
|                       |    | 10000 63                     | 40p   |
|                       |    | 10000 100                    | 40p   |
|                       |    | 10000 160                    | 40p   |
|                       |    | 10000 250                    | 40p   |
|                       |    | 10000 400                    | 40p   |
|                       |    | 10000 630                    | 40p   |
|                       |    | 10000 1000                   | 40p   |
|                       |    | 10000 1500                   | 40p   |
|                       |    | 10000 2000                   | 40p   |
|                       |    | 10000 3000                   | 40p   |
|                       |    | 10000 4000                   | 40p   |
|                       |    | 10000 5000                   | 40p   |
|                       |    | 10000 6000                   | 40p   |
|                       |    | 10000 7000                   | 40p   |
|                       |    | 10000 8000                   | 40p   |
|                       |    | 10000 9000                   | 40p   |
|                       |    | 10000 10000                  | 40p   |
|                       |    | 10000 15000                  | 40p   |
|                       |    | 10000 20000                  | 40p   |
|                       |    | 10000 30000                  | 40p   |
|                       |    | 10000 40000                  | 40p   |
|                       |    | 10000 50000                  | 40p   |
|                       |    | 10000 60000                  | 40p   |
|                       |    | 10000 70000                  | 40p   |
|                       |    | 10000 80000                  | 40p   |
|                       |    | 10000 90000                  | 40p   |
|                       |    | 10000 100000                 | 40p   |
|                       |    | 10000 150000                 | 40p   |
|                       |    | 10000 200000                 | 40p   |
|                       |    | 10000 300000                 | 40p   |
|                       |    | 10000 400000                 | 40p   |
|                       |    | 10000 500000                 | 40p   |
|                       |    | 10000 600000                 | 40p   |
|                       |    | 10000 700000                 | 40p   |
|                       |    | 10000 800000                 | 40p   |
|                       |    | 10000 900000                 | 40p   |
|                       |    | 10000 1000000                | 40p   |
|                       |    | 10000 1500000                | 40p   |
|                       |    | 10000 2000000                | 40p   |
|                       |    | 10000 3000000                | 40p   |
|                       |    | 10000 4000000                | 40p   |
|                       |    | 10000 5000000                | 40p   |
|                       |    | 10000 6000000                | 40p   |
|                       |    | 10000 7000000                | 40p   |
|                       |    | 10000 8000000                | 40p   |
|                       |    | 10000 9000000                | 40p   |
|                       |    | 10000 10000000               | 40p   |
|                       |    | 10000 15000000               | 40p   |
|                       |    | 10000 20000000               | 40p   |
|                       |    | 10000 30000000               | 40p   |
|                       |    | 10000 40000000               | 40p   |
|                       |    | 10000 50000000               | 40p   |
|                       |    | 10000 60000000               | 40p   |
|                       |    | 10000 70000000               | 40p   |
|                       |    | 10000 80000000               | 40p   |
|                       |    | 10000 90000000               | 40p   |
|                       |    | 10000 100000000              | 40p   |
|                       |    | 10000 150000000              | 40p   |
|                       |    | 10000 200000000              | 40p   |
|                       |    | 10000 300000000              | 40p   |
|                       |    | 10000 400000000              | 40p   |
|                       |    | 10000 500000000              | 40p   |
|                       |    | 10000 600000000              | 40p   |
|                       |    | 10000 700000000              | 40p   |
|                       |    | 10000 800000000              | 40p   |
|                       |    | 10000 900000000              | 40p   |
|                       |    | 10000 1000000000             | 40p   |
|                       |    | 10000 1500000000             | 40p   |
|                       |    | 10000 2000000000             | 40p   |
|                       |    | 10000 3000000000             | 40p   |
|                       |    | 10000 4000000000             | 40p   |
|                       |    | 10000 5000000000             | 40p   |
|                       |    | 10000 6000000000             | 40p   |
|                       |    | 10000 7000000000             | 40p   |
|                       |    | 10000 8000000000             | 40p   |
|                       |    | 10000 9000000000             | 40p   |
|                       |    | 10000 10000000000            | 40p   |
|                       |    | 10000 15000000000            | 40p   |
|                       |    | 10000 20000000000            | 40p   |
|                       |    | 10000 30000000000            | 40p   |
|                       |    | 10000 40000000000            | 40p   |
|                       |    | 10000 50000000000            | 40p   |
|                       |    | 10000 60000000000            | 40p   |
|                       |    | 10000 70000000000            | 40p   |
|                       |    | 10000 80000000000            | 40p   |
|                       |    | 10000 90000000000            | 40p   |
|                       |    | 10000 100000000000           | 40p   |
|                       |    | 10000 150000000000           | 40p   |
|                       |    | 10000 200000000000           | 40p   |
|                       |    | 10000 300000000000           | 40p   |
|                       |    | 10000 400000000000           | 40p   |
|                       |    | 10000 500000000000           | 40p   |
|                       |    | 10000 600000000000           | 40p   |
|                       |    | 10000 700000000000           | 40p   |
|                       |    | 10000 800000000000           | 40p   |
|                       |    | 10000 900000000000           | 40p   |
|                       |    | 10000 1000000000000          | 40p   |
|                       |    | 10000 1500000000000          | 40p   |
|                       |    | 10000 2000000000000          | 40p   |
|                       |    | 10000 3000000000000          | 40p   |
|                       |    | 10000 4000000000000          | 40p   |
|                       |    | 10000 5000000000000          | 40p   |
|                       |    | 10000 6000000000000          | 40p   |
|                       |    | 10000 7000000000000          | 40p   |
|                       |    | 10000 8000000000000          | 40p   |
|                       |    | 10000 9000000000000          | 40p   |
|                       |    | 10000 10000000000000         | 40p   |
|                       |    | 10000 15000000000000         | 40p   |
|                       |    | 10000 20000000000000         | 40p   |
|                       |    | 10000 30000000000000         | 40p   |
|                       |    | 10000 40000000000000         | 40p   |
|                       |    | 10000 50000000000000         | 40p   |
|                       |    | 10000 60000000000000         | 40p   |
|                       |    | 10000 70000000000000         | 40p   |
|                       |    | 10000 80000000000000         | 40p   |
|                       |    | 10000 90000000000000         | 40p   |
|                       |    | 10000 100000000000000        | 40p   |
|                       |    | 10000 150000000000000        | 40p   |
|                       |    | 10000 200000000000000        | 40p   |
|                       |    | 10000 300000000000000        | 40p   |
|                       |    | 10000 400000000000000        | 40p   |
|                       |    | 10000 500000000000000        | 40p   |
|                       |    | 10000 600000000000000        | 40p   |
|                       |    | 10000 700000000000000        | 40p   |
|                       |    | 10000 800000000000000        | 40p   |
|                       |    | 10000 900000000000000        | 40p   |
|                       |    | 10000 1000000000000000       | 40p   |
|                       |    | 10000 1500000000000000       | 40p   |
|                       |    | 10000 2000000000000000       | 40p   |
|                       |    | 10000 3000000000000000       | 40p   |
|                       |    | 10000 4000000000000000       | 40p   |
|                       |    | 10000 5000000000000000       | 40p   |
|                       |    | 10000 6000000000000000       | 40p   |
|                       |    | 10000 7000000000000000       | 40p   |
|                       |    | 10000 8000000000000000       | 40p   |
|                       |    | 10000 9000000000000000       | 40p   |
|                       |    | 10000 10000000000000000      | 40p   |
|                       |    | 10000 15000000000000000      | 40p   |
|                       |    | 10000 20000000000000000      | 40p   |
|                       |    | 10000 30000000000000000      | 40p   |
|                       |    | 10000 40000000000000000      | 40p   |
|                       |    | 10000 50000000000000000      | 40p   |
|                       |    | 10000 60000000000000000      | 40p   |
|                       |    | 10000 70000000000000000      | 40p   |
|                       |    | 10000 80000000000000000      | 40p   |
|                       |    | 10000 90000000000000000      | 40p   |
|                       |    | 10000 100000000000000000     | 40p   |
|                       |    | 10000 150000000000000000     | 40p   |
|                       |    | 10000 200000000000000000     | 40p   |
|                       |    | 10000 300000000000000000     | 40p   |
|                       |    | 10000 400000000000000000     | 40p   |
|                       |    | 10000 500000000000000000     | 40p   |
|                       |    | 10000 600000000000000000     | 40p   |
|                       |    | 10000 700000000000000000     | 40p   |
|                       |    | 10000 800000000000000000     | 40p   |
|                       |    | 10000 900000000000000000     | 40p   |
|                       |    | 10000 1000000000000000000    | 40p   |
|                       |    | 10000 1500000000000000000    | 40p   |
|                       |    | 10000 2000000000000000000    | 40p   |
|                       |    | 10000 3000000000000000000    | 40p   |
|                       |    | 10000 4000000000000000000    | 40p   |
|                       |    | 10000 5000000000000000000    | 40p   |
|                       |    | 10000 6000000000000000000    | 40p   |
|                       |    | 10000 7000000000000000000    | 40p   |
|                       |    | 10000 8000000000000000000    | 40p   |
|                       |    | 10000 9000000000000000000    | 40p   |
|                       |    | 10000 10000000000000000000   | 40p   |
|                       |    | 10000 15000000000000000000   | 40p   |
|                       |    | 10000 20000000000000000000   | 40p   |
|                       |    | 10000 30000000000000000000   | 40p   |
|                       |    | 10000 40000000000000000000   | 40p   |
|                       |    | 10000 50000000000000000000   | 40p   |
|                       |    | 10000 60000000000000000000   | 40p   |
|                       |    | 10000 70000000000000000000   | 40p   |
|                       |    | 10000 80000000000000000000   | 40p   |
|                       |    | 10000 90000000000000000000   | 40p   |
|                       |    | 10000 100000000000000000000  | 40p   |
|                       |    | 10000 150000000000000000000  | 40p   |
|                       |    | 10000 200000000000000000000  | 40p   |
|                       |    | 10000 300000000000000000000  | 40p   |
|                       |    | 10000 400000000000000000000  | 40p   |
|                       |    | 10000 500000000000000000000  | 40p   |
|                       |    | 10000 600000000000000000000  | 40p   |
|                       |    | 10000 700000000000000000000  | 40p   |
|                       |    | 10000 800000000000000000000  | 40p   |
|                       |    | 10000 900000000000000000000  | 40p   |
|                       |    | 10000 1000000000000000000000 | 40p   |
|                       |    | 10000 1500000000000000000000 | 40p   |
|                       |    | 10000 2000000000000000000000 |       |



# Oscilloscope

AS RECOMMENDED BY  
ELECTRONICS TODAY  
INTERNATIONAL  
JULY 1978



SUPPLIED WITH FULL COMPREHENSIVE MANUALS FULLY GUARANTEED

## 3" OSCILLOSCOPE

£83.25  
Add VAT £6.66  
Carriage £1.50

FROM STOCK  
SOLE UK  
IMPORTERS

## 4" OSCILLOSCOPE

£99  
Add VAT £7.92  
Carriage £2.08

Appointed  
London Stockist

### SPECIFICATIONS (FOR BOTH MODELS)

#### ELECTRICAL DATA

##### VERTICAL AXIS (Y)

Deflection Sensitivity — 100mV/division  
Bandwidth (between 3 dB points) — DC—5MHz  
Input Attenuator — (calibrated) — 9 steps 0.1, 0.2, 0.5, 1, 2, 5, 10, 20 50V/div  
Input Impedance — 1 Meg/40 pf in shunt  
Input Voltage — Max — 600V P.P.

##### HORIZONTAL AXIS (X)

Deflection Sensitivity — 0-400mV/division  
Bandwidth (between 3dB points) — 1Hz-350KHz  
Gain Control — Continuous, when time base in EXT position  
Input Impedance — 1 Meg  
Input Voltage — Max — 600V P.P.

##### TIME BASE

Sweep Range (calibrated) — 100msec/div to 1µ sec/div in 5 steps  
FINE Control — Variable between steps — Includes timebase calibration position  
Blanking — Internal — on all ranges

##### SYNCHRONIZATION

Selection — Internal, external  
Synchronization Level — Continuous from positive to negative Input Voltage

##### POWER SUPPLY

— 115/220V AC— 10% at 50/60Hz — 3 inch DR 4 inch  
Power Dissipation 18 watt — Maximum high voltage — 1.5kV  
— Fitted with 8x10 division blue filter graticule

##### CRT DATA


PHYSICAL DATA  
Dimensions — 14cm (h) x 20.5cm (w) x 28cm (d)  
Weight — 4.3kg (approx)  
Stand — 2 position, flat and inclined  
Case — Steel, epoxy enamelled  
Front Panel — Aluminium, enamelled epoxy printing

Also from 248 Tottenham Court Road, London W1  
301 Edgware Road, London W2



**HENRY'S**  
RADIO

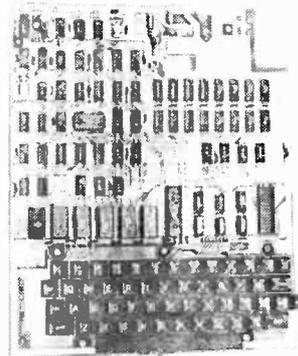All mail to:  
Henry's Radio  
404 Edgware Rd  
London W2  
Phone [01] 723 1008



## SUPERBOARD II COMPUTER

8K basic, 4K user Ram, built  
and tested

Only £263.84  
+ 8% VAT

- Uses the ultra powerful 6502 microprocessor
- 8K Microsoft BASIC-in-ROM
- Full feature BASIC runs faster than currently available personal computers and all 8080-based business computers.
- 4K RAM on board expandable to 8K
- Full 53-key keyboard with upper-lower case and user programmability
- Kansas City standard audio cassette interface for high reliability
- Full machine code monitor and I/O utilities in ROM
- Direct access video display has 1K of dedicated memory (besides 4K user memory), features upper case, lower case, graphics and gaming characters for an effective screen resolution of up to 256 by 256 points. Normal TVs with overscan display about 24 rows of 24 characters, without overscan up to 30 x 30 characters.

Available in mid-December

## WATFORD ELECTRONICS

33 Cardiff Road, Watford, Herts  
Tel. Watford 40588


Mail Order

Callers welcome
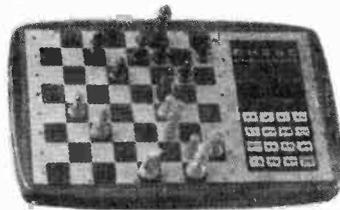
## CHESS CHALLENGER "10"

"It's You Against the Computer"

Are YOU good enough to challenge the CHALLENGER in any of the following 10 levels... and WIN??



| LEVEL                                    | AVERAGE RESPONSE TIME |                         |           |
|--|-----------------------|-------------------------|-----------|
| 1. Beginner                              | 5 Seconds             |                         |           |
| 2. Intermediate                          | 15 Seconds            |                         |           |
| 3. Experienced                           | 35 Seconds            |                         |           |
| 4. Advanced                              | 1.20 Minutes          |                         |           |
| 5. Superior                              | 2.20 Minutes          |                         |           |
| 6. Mate In Two (2 move Puzzlers)         | 60 Minutes            |                         |           |
| 7. Postal Chess (For Games by mail only) | 24 Hours              | 9. Excellent            | 6 Minutes |
| 8. Expert                                | 11 Minutes            | 10. Tournament Practice | 3 Minutes |

1. Ten Levels of play from beginner to expert including "Mate in two" and "Chess by mail"

2. Levels changeable during game. Change from level 1 to any level through 10 at any time on any move

3. Random Computer Responses vary every game

4. Selection of Legal Offense or Defense. Play from the bottom board or the top of the board. Choose either black or white

5. Does not permit illegal moves. Never makes an illegal move according to all the rules of chess

6. Position verification by computer memory recall

7. Plays opening defenses from chess books, i.e. Sicilian, French, Ruy Lopez, Queen Gambit declined

8. Analyzes as many as 3,024,000 board positions

9. Audio Feedback. Single tone each time you press a key. Double tone when computer responds

10. Problem Mode. Establish your own chess positions and watch the computer react

11. Override key to make multiple moves. Make two, three, or more moves before the computer responds

12. Add or subtract pieces during game. Put back the piece you lost by override or take away the computer's Queen for a more even game

13. Pawn Promotion to selected piece. Promote a pawn to a Queen automatically, or select a knight or another piece instead

14. En Passant

15. Castling

Numerous other features, including a solid walnut case, 13 x 8 x 1 1/2 inches high, with a deluxe simulated leather and brushed gold foil playing surface, large 1/2-inch LED display and hand carved solid wood, magnetized French Chess Pieces.

CHESS CHALLENGER "10" available from **KRAMER & Co., Dept. ET1**  
9 OCTOBER PLACE, HOLDERS HILL ROAD, LONDON NW4 1EJ  
TEL 01-203 2473 TELEX 888941 ATTN: KRAMER K7

EXPORT ORDERS WELCOME. Access and Barclay by arrangement.  
PRICE £199, INCL. VAT, P&P, CWO

Slightly used Master Chess Challengers available. SAE for details.  
Computer Draughts (checkers available, SAE for brochure).  
Mail Order only — Callers by appointment.

## Nascom UK Distributors

Barrow-in-Furness

Camera Centre

Tel: 0229-20473

Torquay

CC Electronics

Tel: 0803-22699

Egham & Manchester

Electrovalue

Tel: 07843-3603

Glenfield, Leicester

Eley Electronics

Tel: 0533-871522

London W2

Henry's Radio

Tel: 01-723 1008

Oldham, Lancs

Lock Distribution

Tel: 061-652 0431

Chesham, Bucks

Lynx Electronics

Tel: 02405-75151

Liverpool L2

Microdigital

Tel: 051-236 0707

New Barnet, Herts

Comp Components

Tel: 01-441 2922

Glasgow

Strathand

Tel: 041 552 6731

Bristol

Target Electronics

Tel: 0272 421196



Nascom Microcomputers

# ETI BOOK SERVICE

## BEGINNERS

Beginners Guide to **Electronics** Squires £2.65  
Beginners Guide to **Transistors** Reddihough £2.65  
**Electronic Measurement Simplified** C. Hallmark £2.20  
**Electronics Self Taught** Ashe £4.40  
Beginners Guide to **Integrated Circuits** Sinclair £3.15  
**Principles of Transistor Circuits** S. Amos £4.75  
Understanding **Electronic Circuits** Sinclair £4.10  
Understanding **Electronic Components** Sinclair £4.10  
Beginners Guide to **Radio** King £3.15  
Beginners Guide to **Audio** Sinclair £3.10  
Beginners Guide to **Audio** L. R. Sinclair £3.20

## COOKBOOKS

**TV Typewriters Cookbook** £7.75  
**CMOS Cookbook** £8.20  
**Active Filters** £11.30  
**IC Timer Cookbook** £7.50  
**IC Op-Amp Cookbook** £10.00  
**Video Cookbook** £7.00

## APPLICATIONS

Advanced Applications for **Pocket Calculators** J. Gilbert £4.20  
Build Your Own Working **Robot** D. Heiseman £3.55  
**Electronics and Photography** R. Brown £2.30  
**Fire and Theft Security Systems** B. Weis £2.00  
How To Build **Proximity Detectors and Metal Locators** J. Shields £3.90  
How To Build **Electronic Kits** Capel £2.10  
**Linear Integrated Circuit Applications** G. Clayton £5.40  
**Function Circuits Design & Applications** Burr Brown £15.95  
**110 Electronic Alarm Projects** R. M. Marston £3.45  
**110 Semiconductor Projects for the Home Constructor** R. M. Marston £3.25  
**110 Integrated Circuit Projects for the Home Constructor** R. M. Marston £3.25  
**110 Thyristor Projects Using SCRs** R. M. Marston £2.95  
**Handbook of IC Circuit Projects** Ashe £2.30  
**Practical Electronic Project Building** Ainslie and Colwell £2.45

## TV AND HI-FI

**Audio Handbook** G. King £6.50  
**Cassette Tape Recorders** J. Earl £2.25  
**Solid State Colour TV Circuits** G. R. Wilding £6.35  
**Hi-Fi Loudspeakers and Enclosures** Cohen £8.20  
How To Build **Speaker Enclosures** Badmateff £3.90  
**Master Hi-Fi Installation** King £2.80

## LOGIC

**Logic Design Projects Using Standard ICs** J. Wakerly £5.10  
**Practical Digital Design Using ICs** J. Greenfield £12.50  
**Designing With TTL Integrated Circuits** Texas Instruments £9.05  
How To Use **IC Circuit Logic Elements** J. Streater £3.65  
**110 COSMOS Digital IC Projects for the Home Constructor** R. M. Marston £3.20  
Understanding **CMOS Integrated Circuits** R. Melen £4.00  
**Digital Electronic Circuits and Systems** R. M. Morris £3.50  
**MOS Digital ICs** G. Flynn £5.10

## COMPUTING

**Microprocessors and Microcomputers** B. Sowick £18.00  
**Microprocessors** D. C. McGlynn £8.40  
**Introduction to Microprocessors** Aspinall £5.90  
**Modern Guide to Digital Logic (Processors, Memories and Interfaces)** £4.30  
**Beginners Guide to Microprocessors** £4.70  
**Beginners Basic** Gosling £3.35

## OP-AMPS

**Applications of Operational Amplifiers** Graeme (Burr Brown) £8.30  
**Designing With Operational Amplifiers** Burr Brown £16.65  
**Experiments With Operational Amplifiers** Clayton £3.40  
**110 Operational Amplifier Projects for the Home Constructor** R. M. Marston £2.95  
**Operational Amplifiers Design and Applications** G. Tobery (Burr Brown) £7.40  
**Op-Amp Circuit Design & Applications** J. Carr £4.00

## TEST INSTRUMENTS

**The Oscilloscope In Use** Sinclair £3.10  
**Test Instruments for Electronics** M. Clifford £2.40  
**Working With the Oscilloscope** A. Saunders £1.95  
**Servicing With the Oscilloscope** G. King £5.60  
**Radio Television and Audio Test Instruments** King £5.90

## SERVICING

**Electronic Fault Diagnosis** Sinclair £3.20  
**Rapid Servicing of Transistor Equipment** G. King £2.95  
**Tape Recorder Servicing Manual** Gardner Vol. 1: 1968-70 £8.50  
Vol. 2: 1971-74 £8.50  
**FM Radio Servicing Handbook** King £4.80  
**Basic Electronic Test Procedures** J. M. Gottlieb £2.45

## COMMUNICATIONS

**Communication Systems Intro To Signals & Noise** B. Carlson £7.50  
**Digital Signal Processing Theory & Applications** L. R. Rabiner £23.80  
**Electronic Communication Systems** G. Kennedy £8.50  
**Frequency Synthesis. Theory & Design** Mannassewitsch £21.70  
**Principles of Communication Systems** H. Taub £10

## THEORY

**Introduction to Digital Filtering** Bogner £10.20  
**Transistor Circuit Design** Texas Instruments £9.35  
**Essential Formulae for Electrical and Electronic Engineers** N. M. Morris £1.65  
**Modern Electronic Maths** Clifford £6.70  
**Semiconductor Circuit Elements** T. D. Towers £6.40  
**Foundations of Wireless Electronics** M. G. Scroggie £4.45  
**Colour Television Theory** Hudson £6.20

## REFERENCE

**Transistor Tabelle (Includes physical dimensions)** £4.10  
**Electronic Engineers Reference Book (Ed. 4)** L. W. Turner £27.70  
**Solid State Circuit Guide Book** B. Ward £2.25  
**Electronic Components** M. A. Colwell £2.45  
**Electronic Diagrams** M. A. Colwell £2.45  
**Indexed Guide to Modern Electronic Circuits** Goodman £2.30  
**International Transistor Selector** T. D. Towers £6.00  
**International FET Selector** T. D. Towers £4.35  
**Popular Valve/Transistor Substitution Guide** £2.25  
**Radio Valve and Semiconductor Data** A. M. Bell £2.60  
**Master Transistor/Integrated Circuit Substitution Handbook** £5.60  
**World Radio TV Handbook 1978 (Station Directory)** £8.00  
**Radio, TV and Audio Technical Reference** Amos £24.85  
**TV Technicians Bench Manual (New Ed.)** Wilding £5.10


## MISCELLANEOUS

**Integrated Electronics** J. Milman £7.90  
**Microelectronics** Hallmark £3.90  
**Practical Solid State DC Supplies** T. D. Towers £6.20  
**Practical Triac/SCR Projects for the Experimenter** R. Fox £2.25  
**Printed Circuit Assembly** Hughes & Colwell £2.45

Fallen behind recent advances?  
Just starting out?  
Need a decent reference book?  
ETI Book Service provides an easy  
way of getting your hands  
on the right title.

How to order: Make cheques etc payable to ETI Book Service. Payment in sterling only please. Orders should be sent to: ETI Book Service, PO Box 79, Maidenhead, Berks. All prices include P&P.

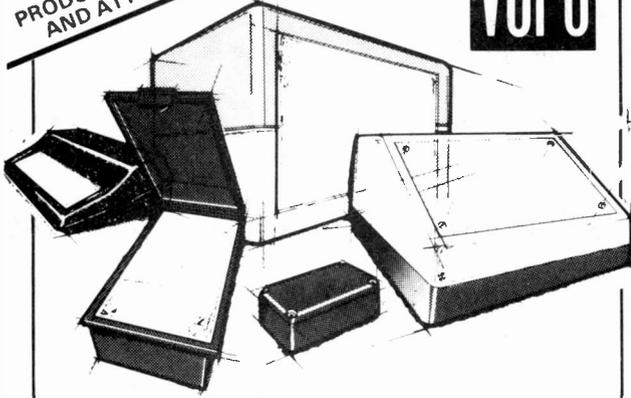OUR RANGE OF PRODUCTS ARE NOW INDIVIDUALLY AND ATTRACTIVELY PACKAGED



Our new 1978 catalogue lists a whole range of plastic boxes to house all your projects. And we've got circuit boards, accessories, module systems, and metal cases — everything you need to give your equipment the quality you demand. Send 25p to cover post and packing, and the catalogue's yours

**VERO ELECTRONICS LTD. RETAIL DEPT.**  
Industrial Estate, Chandlers Ford, Hants. SO5 3ZR  
Telephone Chandlers Ford (04215) 2956

# NEWNES RADIO AND ELECTRONICS ENGINEER'S POCKET BOOK

15th Edition

Prepared by the Editorial Staff of ETI

An invaluable compendium of facts, figures and formulae for all interested in electronics and project building.

- Completely revised and updated
- New material covers recent developments in radio and electronics
- New tables include TTL, CMOS and logic.

1978 192 pages 82 x 123 mm £2.55 \$5.25  
0 408 00314 6



Newnes-Butterworths  
Borough Green, Sevenoaks,  
Kent TN15 8PH

## AUDIO AND TEST EQUIPMENT CENTRE

MICROCOMPUTERS LEVEL I AND II TRS80 IN STOCK

ALL PRICES INCLUDE VAT

Only regular stocks listed — other makes and models available.  
Telephone your order with Access and Barclaycards or send cheque with order.



4D10A



DM235



TE200

LONDON'S TEST GEAR CENTRE  
OPEN 6 DAYS A WEEK 9 am-6 pm

### SCOPES — IN STOCK

|  |        |
|--|--------|
| 3" 5MHz single beam  | 89.90  |
| 4810. 5MHz single beam (4)                                   | 107.00 |
| MS15. 15MHz Batt./mains, portable                            | 286.00 |
| MS215. Dual trace version of above                           | 360.00 |
| Super 6/458 Scope x 5MHz single beam                         | 148.00 |
| Super 10/4D10A. Scope x 10MHz Dual trace                     | 229.00 |
| 4D25. Scope x 25MHz Dual trace                               | 338.00 |
| PROBES x 1 x 10 14.50, x 10 9.95 x 1 7.95 For 456/4D10A/4D25 |        |

**LOW COST**  
New 5MHz mains portable scope now in stock  
£89.90

### LED AND LCD DIGITAL MULTIMETERS

|  |        |
|--|--------|
| DM235 Sinclair portable 3 1/2 digit LED                        | 49.95  |
| PDM35 Sinclair Pocket 3 1/2 digit LED                          | 29.95  |
| DM350 New Sinclair 3 1/2 Digit                                 | 69.95  |
| DM450 New Sinclair 4 1/2 Digit                                 | 99.95  |
| (30kV Probes 18.25, Mains adaptors 3.75, DM235 carrycase 8.95) |        |
| LM3A 3 Digit Miniature with large LED displays                 | 98.00  |
| LM3.5A 3 1/2 Digit Recharge Batts and charger 17 ranges        | 106.00 |
| LM40A 4 Digit  | 210.00 |
| LM300 3-Digit Miniature battery operated 17 ranges             | 87.00  |
| LM360 3 1/2-Digit with LCD displays 1 µA/mV resolution         | 98.00  |



LM3.5A

### MULTI-METERS — GENERAL PURPOSE & ELECTRONIC

Multi-Range Instruments featuring AC/DC volts DC current Resistance Ranges all with mirror scales except T1/IT1-2/T12/TM3A (TM3 AC volts only) some with AC current etc

|   |        |
|---|--------|
| TM11 incredible 120 Range Electronic Multi-meter                | 136.00 |
| TM3B AC Micro voltmeter 3MHz >4 Megohm                          | 130.00 |
| TM85 Broadband voltmeter 300KHz-400MHz                          | 196.00 |
| 360TR 100k/volt 23 Range (plus transistor checker) Large scale  | 35.50  |
| PROE 20k/volt 125 Range Large scale                             | 32.00  |
| 7081 50k/volt 36 Range Multi-meter                              | 23.50  |
| Tmk500 30k/volt 22 Range Multi-meter (plus Continuity Buzzer)   | 21.00  |
| 680R 20k/volt 52 Range Pocket Multi-meter                       | 34.50  |
| 7200 20k/volt 22 Range Double Multi-meter                       | 17.95  |
| Micro80 20k/volt 26 Range Pocket Multi-meter                    | 17.95  |
| IT1-2 20k/volt 16 Range Popular Multi-meter                     | 11.95  |
| LT22 20k/volt 19 Range Pocket Multi-meter with carry case       | 14.50  |
| T12 5k/volt 13 Range Pocket Multi-meter                         | 8.95   |
| LT101 1k/volt 12 Range Pocket Multi-meter                       | 7.50   |
| EM2000 FET IC VOM 20 Ranges 10 Meg Input                        | 55.00  |
| K200 FET VOM 38 Ranges  | 77.00  |
| GT101, 20K/Volt 23 Ranges/Transistor Checker/Continuity Checker | 17.95  |

AVO B's and a large range of replacement test leads in stock

### GENERAL EQUIPMENT

|  |       |
|--|-------|
| TE7 Signal Tracer  | 8.95  |
| SWR50 SWR/Power Meter  | 19.50 |
| LP30 30MHz Low Pass Filter                                   | 4.95  |
| CX3A 150Watt 3-way AE Switch                                 | 7.50  |
| DC25MV 100 Meg HV Probe                                      | 11.95 |
| DR510 36 Value Resis. Box                                    | 3.95  |
| FX2000 Xtal Marker   | 11.95 |
| TR1000 Transistor checker in/out circuit                     | 11.95 |
| MOD43 Signal Injector  | 7.50  |
| TT100 In Circuit TR Checker                                  | 49.95 |
| LB1 Transistor/Diode Checker                                 | 21.50 |
| 3181 Clamp Meter 0/1 K ohm. 0/150/300/600 AC Volts 0/300 Amp | 32.95 |
| C3042 SWR & FS Meter   | 9.95  |
| MS319 2x100 Watt Audio Watt Meter                            | 17.50 |
| *500V Megohmmeter 500 Megohms                                | 48.00 |
| *1000V Megohmmeter 1000 Megohms                              | 55.00 |
| *2 1/2 Amp Variable Transformer                              | 19.95 |
| *5 Amp Variable Transformer                                  | 33.00 |
| *10 Amp Variable Transformer                                 | 46.00 |
| Decade Resis. Boxes:   |       |
| 1-11 110 ohm in steps of 1 ohm                               | 33.00 |
| 10-111, 110 ohm in steps of 10 ohms                          | 33.00 |
| 1-1-111, 110 ohm in steps of 1 ohm                           | 42.50 |
| Cap. Decade Box:   |       |
| 10pf — 111, 110pf in steps of 10pf                           | 33.00 |

### GENERATORS

|  |        |
|--|--------|
| TG152 Series RC Oscillators                          |        |
| Sine/Square output 3Hz-300KHz                        | 75.00  |
| TG152D   | 95.00  |
| TG152 Dm (with meter)                                |        |
| TG200 Series RC Oscillators                          |        |
| Sine/Square output 1Hz-1MHz                          | 100.00 |
| TG200D   | 121.00 |
| TG200 Dm (with meter)                                | 126.00 |
| TG200 Dmp (Meter & Fine control)                     | 126.00 |
| TG66A Digital Sine Wave Decade control 0.2Hz-1.22MHz | 267.00 |
| TE22D (audio) 4 bands Sine 20-200KHz                 | 65.00  |
| Square 20-150KHz                                     | 57.00  |
| TE20D (RF) 6 bands 120KHz-500MHz                     |        |


### LOGIC PROBES AND MONITORS

|                             |       |
|-----------------------------|-------|
| LT2000 Economy Probe. 10MHz | 11.95 |
| LM1 Monitor                 | 31.00 |
| LP1 Probe 10MHz             | 33.48 |
| LP2 15MHz                   | 19.44 |
| 16 Pin IC test clip         | 2.20  |

### PIEZO HORN TWEETERS

Up to 100 watts each. No x-over reqd. Only .4.95 each (P/P 20p) 10% Discount for 10 Plus

### MICROPHONES, SPEAKERS AND COMPONENTS LARGE RANGE IN STOCK

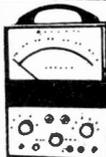


TM11



TMK500



FM7 7 Digit 60MHz Rock. Batt. Freq. counter 156.00  
SCS 512MHz Prescaler for above 81.00  
MAX100 100 MHz x 8 digit batt operated counter 83.75

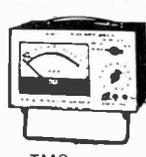

TM3

CALL IN AND SEE FOR YOURSELF

PRICES CORRECT AT NOV. 1st. E.&O.E

## AUDIO ELECTRONICS

301 EDGWARE RD., LONDON W2 1BN  
01-724-3564. OPEN 9-6, MON-SAT.

ALSO AT 248 TOTTENHAM COURT ROAD, W. 1.

**FREE CATALOGUE**

SEND STAMPED (12 x 1 1/2) ADDRESS ENVELOPE (MIN 9" x 6" x 1) FOR YOUR COPY NOW

# DIGITAL DIAL

**Most AM radio dials are pretty hopeless — especially portables and car radios. This application of our counter module can be a decided improvement.**

WITH MODERN RADIOS which are designed to be operated anywhere in the world, the local station call signs are no longer marked on the dial. Instead the dial is marked with frequencies making it more universal. Unfortunately the scaling on many receivers leaves a little to be desired, with many car radios lucky to have 3 or 4 markings. The use of pushbutton selection helps but when a cassette is fitted or you are out of your local area there is still the problem of knowing to what station you are tuned.

This project gives a direct readout of the station being received allowing for easy identification and selection. The display is remote from the receiver allowing it to be mounted on the dashboard for easy viewing.

## Design Features

This project is the first to employ our four digit module presented elsewhere in this issue. We will be using the module again over the next few months so don't lose track of it!

If this device is to be used outdoors i.e. in the car, it is recommended that high brightness displays, such as the Hewlett Packard HDSP 4133, be used. As these have a different pin-out a new display board is presented in this article.

The theory of operation is that we actually measure the frequency of the local oscillator in the radio and subtract the IF frequency. While we could have subtracted this using digital logic we chose to do it by resetting the display not to zero but to 9545 (10 000-455). The first 455 pulses in the timing period are then used getting to zero and in effect, only pulses after this are counted and displayed. This number can be loaded into the counter by



## SPECIFICATION

|                 |                                  |
|-----------------|----------------------------------|
| Frequency range | 500-1700 kHz                     |
| Accuracy        | ± 5 kHz                          |
| Sensor          | pickup coil or direct connection |
| Power supply    | 7-20VDC @ 80mA or 240VAC         |
| Display         | 4 digit LED                      |

selecting the appropriate diodes and using the "load counter" input instead of the reset line. The only difference is that as the data is entered into the counter serially the pulse used must be longer than 4 times the internal oscillator period. Also as the LC input is a three state input it cannot be driven by conventional two-state.

## Out of Tune

We initially tried capacitive coupling onto the tuning capacitor of our portable radio (oscillator section!) but the loading detuned the set too much. We then tried a pickup coil and found enough signal with it in the correct place not to require any electrical connection to the set. With

# PROJECT: Digital Dial



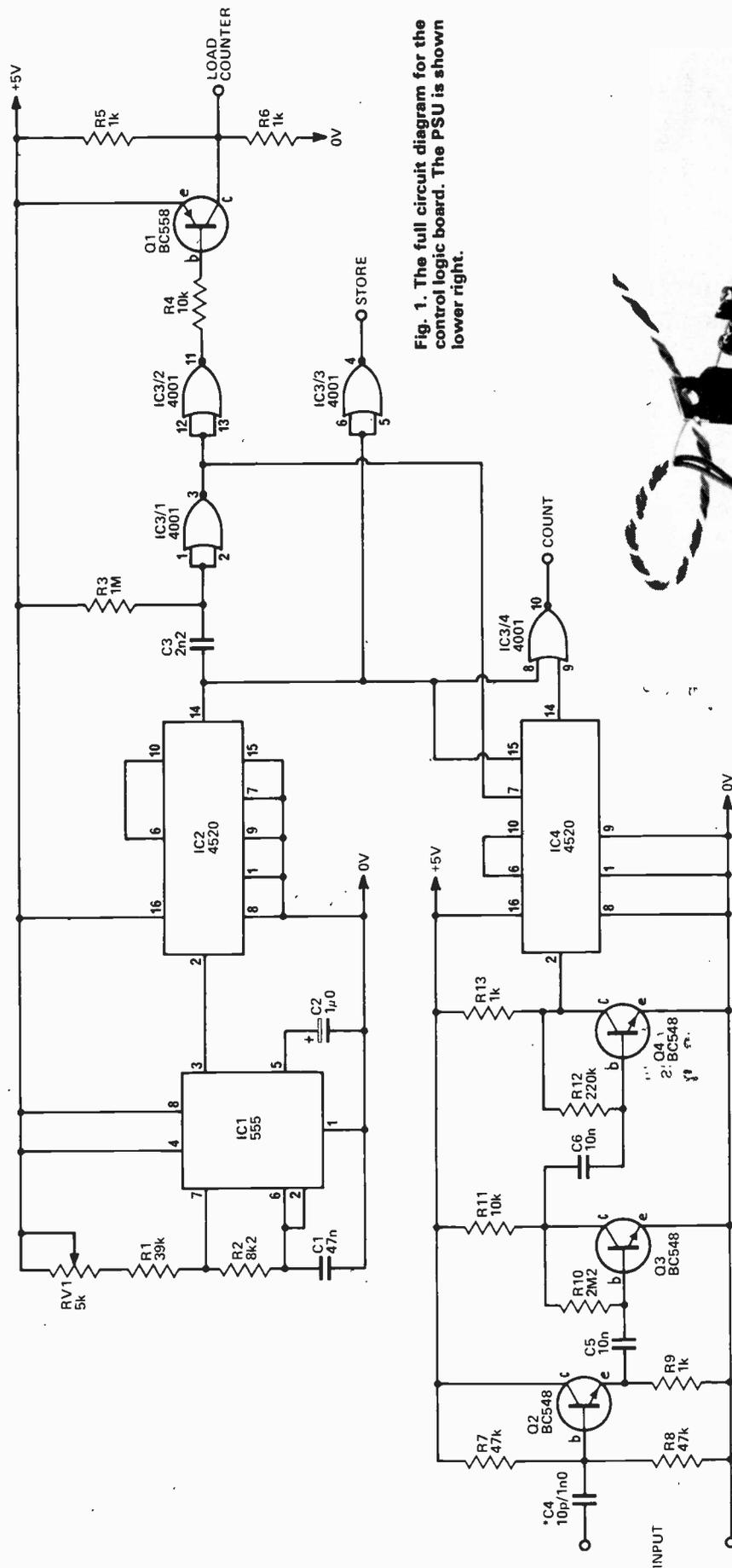


Fig. 1. The full circuit diagram for the control logic board. The PSU is shown lower right.

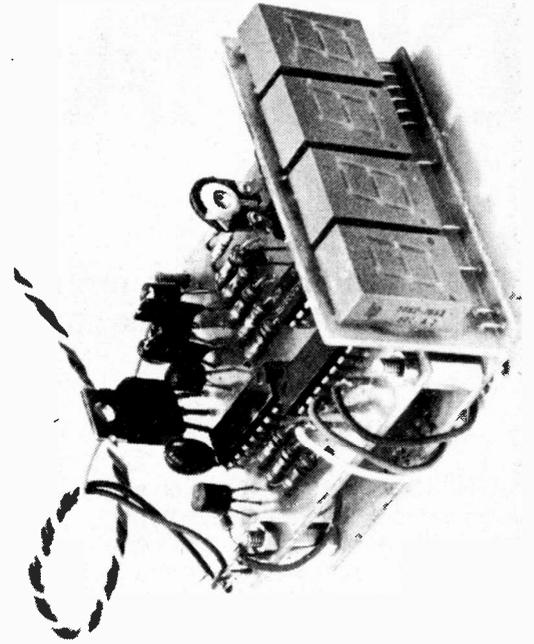

The photo to the right shows the module with the HP 5082-7663 displays. Suitable displays and their light outputs are given below.

| Type      | Colour | Size    | Light output         |
|-----------|--------|---------|----------------------|
| HDSP 4133 | yellow | 10.9 mm | 2100 $\mu$ Cd @ 20mA |
| HDSP 3733 | red    | 10.9 mm | 1800 $\mu$ Cd @ 20mA |
| 5082-7663 | yellow | 10.9 mm | 1500 $\mu$ Cd @ 20mA |
| 5082-7653 | red    | 10.9 mm | 1720 $\mu$ Cd @ 20mA |
| DL704     | red    | 7.6 mm  | 320 $\mu$ Cd @ 25mA  |

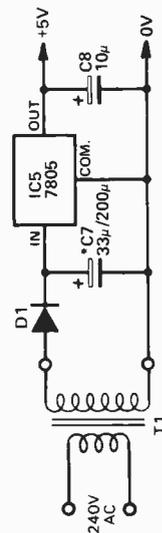

## HOW IT WORKS

A signal from the local oscillator in the tuner is picked up either by a pickup coil or by direct connection to the set. It is then amplified by Q2-Q4 to give a square wave on the collector of Q4. The gain of this amplifier is about 250 (48 dB). The frequency of this signal will vary from around 1 MHz to about 2 MHz and this signal is then frequency divided by 256 (2<sup>8</sup>) in IC4. This is used to clock the display module.

To measure the frequency we have to count the number of these pulses for 256/1000 seconds (256 because we divided the input by 256 and 1000 as we want a 1 kHz resolution). We used a 555 oscillator for the time base and its output is also divided by 256 (by IC2). This improves the stability of the time base by averaging out any short term variations in the 555 frequency.

The output of IC2 is a symmetrical square wave and when the output goes low a 1.5 ms wide pulse is generated by R3, C3 and IC3/1. This is inverted by IC3/2 which turns Q1 on for the 1.5 ms period. Two resistors are used to bias the output of Q1 to 2.5V to ensure that the three level input will work.

This pulse "loads" 9545 into the counters (in the display module). Counting now starts from this number and after 455 pulses it is passing through zero. 256 ms after the load pulse ended the output of IC2 goes high. This resets IC4 back to zero, inhibits any further clocking via IC3/4 and opens the latches via the strobe line allowing the total in the counter to be displayed. 257.5 ms later when the output of IC2 goes low again, the store is closed, the counter is once again preset to 9545 with the process starting again.

the car radio however the coils are shielded so well that reliable operation was not possible. However it was found that we could tap onto one side of the oscillator coil without affecting the operation.

We use a NE555 as the time base with its output being divided by 128 to improve stability. However if an accuracy of  $\pm 5$  kHz is to be maintained its frequency has to be better than 1/4% and a polystyrene capacitor for C1 and 2% resistors for R1 and R2 are recommended.

### Construction

The display board should be built according to the overlay in Fig. 4 which shows which diodes are required. Note that R1, 2 and C1 are not used in the display module and a link is used in place of R1.

The control card can now be assembled and wired to the display module. The two boards are

mounted one above the other using 9.6 mm spacers. Check that these screws do not touch any tracks and insulate them if too close.

Depending on whether the unit is going to be used with a car radio or portable the values of C4 and C7 will vary. The pickup coil is made by winding about 80 turns of 0.25 mm enamelled wire onto a 25 mm long piece of 10 mm ferrite rod with the end terminated onto a twisted pair of plastic covered wires long enough to go between the radio and the position of the display. Do not use coaxial cable for this as the capacitance is too high.

The case chosen has been left to the individual with our own being from a discarded digital clock. If you use the 240 V powered version be careful with the high voltage wiring. For the 12 V version the power can come from the radio via a twisted lead (3 wires).

When connecting into a car radio, tune the set to a local station and try the pickup wire on the terminals of the tuning coils in turn until one is found which will give a reading without moving it off station.

Permanently connect to this point. With a portable radio try moving the pickup coil around the set, probably in line with the aerial coil, until the best results are obtained.

### Calibration

Place the pickup coil in position such that reliable operation is obtained and tune to a known station (preferably near the top end of the dial). Now adjust RV1 until the digital dial agrees with that station. Check then with other stations.

Alternatively feed a known signal of between 1 and 2 MHz from an oscillator into the input and adjust RV1 until it reads 455 less than that frequency.



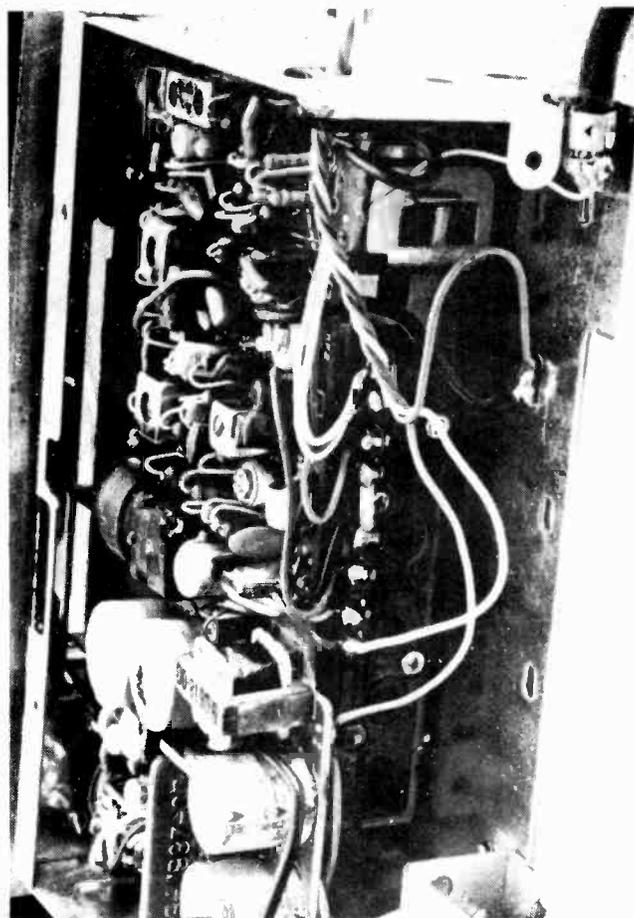


Photo showing where we tapped into the car radio.

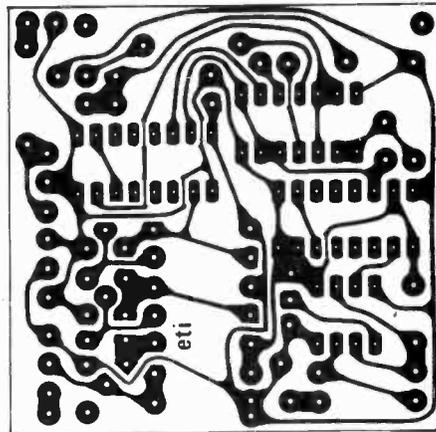

Right: full site foil patterns for the Digital control board. Refer to the module article for details of those PCBs. Not shown here i.e. the two display boards and the third for high brightness seven segment types.

# PROJECT: Digital Dial

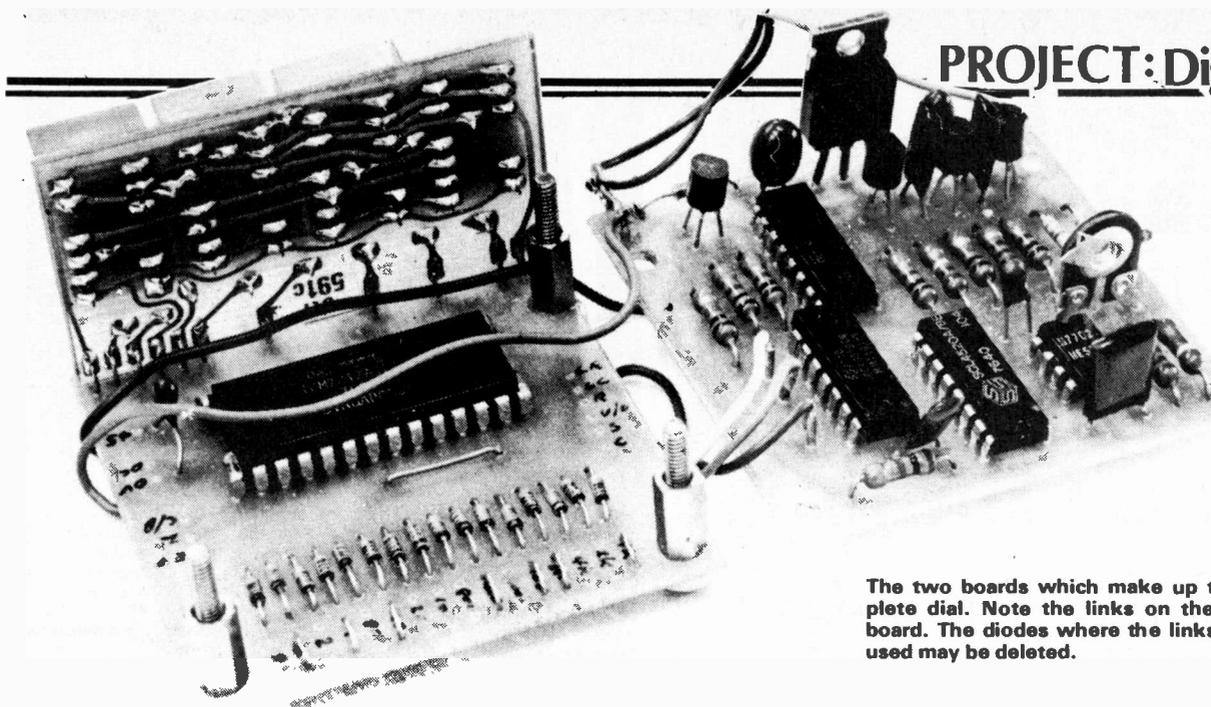

The two boards which make up the complete dial. Note the links on the display board. The diodes where the links are not used may be deleted.

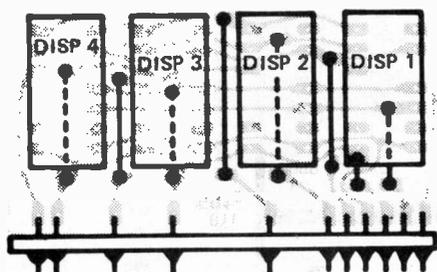


Fig 3(a) The overlay for the display board employing the high brightness displays. (b) Below that (left) the control board overlay.

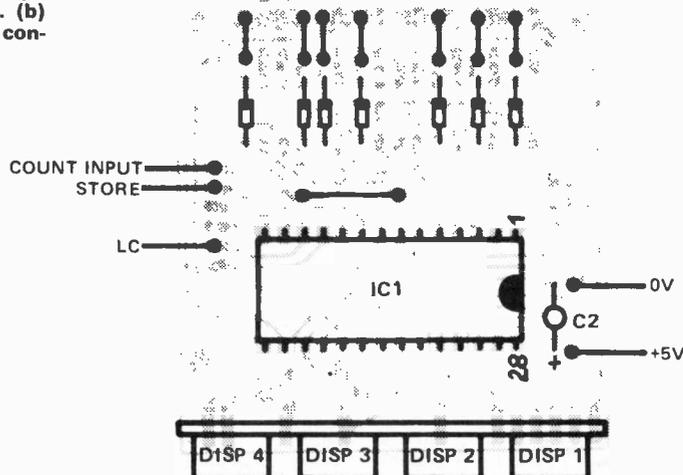
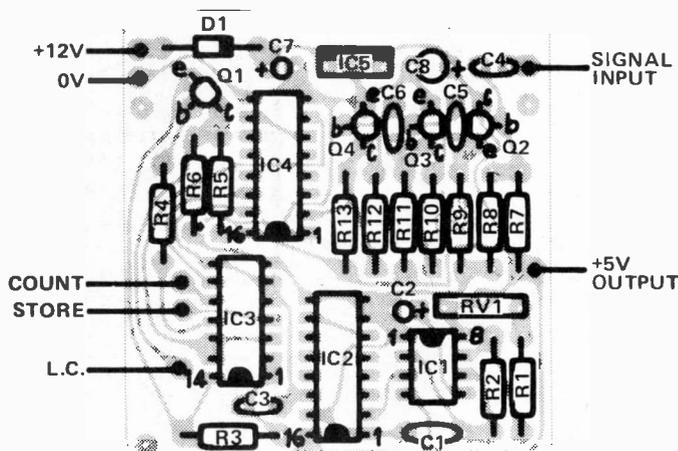


Fig. 4. The component overlay of the display module showing the diodes and links required.

## PARTS LIST

|               |                 |                |                      |
|---------------|-----------------|----------------|----------------------|
| RESISTORS     | all 1/2W, 5%    | *C7            | 33u tantalum         |
| R1            | 39k             | C8             | 10u 25V electrolytic |
| R2            | 8k2             | SEMICONDUCTORS |                      |
| R3            | 1M              | IC1            | 555                  |
| R4, 11        | 10k             | IC2            | 4520                 |
| R5, 6, 9, 13  | 1k              | IC3            | 4001                 |
| R7, 8         | 47k             | IC4            | 4520                 |
| R10           | 2M2             | IC5            | 7805                 |
| R12           | 220k            | Q1             | BC558                |
| POTENTIOMETER |                 | Q2-Q4          | BC548                |
| RV1           | 5k trimmer      | D1             | 1N4004               |
| CAPACITORS    |                 | MISCELLANEOUS  |                      |
| C1            | 47n polystyrene | *Transformer   | 240V-12V6, 150 mA    |
| C2            | 1u0 tantalum    |                |                      |
| C3            | 2n2 polyester   |                |                      |
| *C4           | 10p ceramic     |                |                      |
| C5, 6         | 10n polyester   |                |                      |

\*For 12 V operation delete transformer. For 240 V version C7 should be 220u 25 V. For use with pickup coil increase C4 to 1n0.

## BUYLINES

Any displays mentioned here are of course suitable and should be easily obtainable. The semiconductors are all available from Technomatic, or indeed from most other mail-order suppliers.

### Power Supply

The unit can be powered by an AC or DC voltage of between 7 and 20 volts. If an AC voltage is used the capacitor C7 should be increased to 220 u. A 240 V to 12V6, 150 mA transformer is recommended. **ETI**

# STEVENSON

## Electronic Components

### VEROBOARDS

| Size in.   | 0.1in. | 0.15in. | Veropins —   |
|------------|--------|---------|--------------|
| 2.5 x 1    | 14p    | 13p     | single sided |
| 2.5 x 3.75 | 42p    | 40p     | per 100      |
| 2.5 x 5    | 52p    | 50p     | 0.1in 35p    |
| 3.75 x 5   | 60p    | 60p     | 0.15in 40p   |
| 3.75 x 17  | 195p   | 180p    |              |

### TRANSFORMERS


PRIMARY 240 Volts

| Code | Secondary                          |      |
|------|------------------------------------|------|
| A1   | 6 - 0 - 6 at 0.5A                  | 155p |
| A4   | 9 - 0 - 9 at 0.4A                  | 155p |
| B1   | 6 - 0 - 6 at 1A                    | 205p |
| B4   | 12 - 0 12 at 0.5A                  | 205p |
| B8   | 15 - 0 15 at 0.4A                  | 205p |
| C4   | 9 - 0 - 9 at 1.2A                  | 305p |
| C8   | 12 - 0 12 at 1A                    | 305p |
| D12  | 0 - 12 - 15 - 20 - 24 - 30 at 1.5A | 395p |
| E12  | 0 - 20 - 25 - 33 - 40 - 50 at 2A   | 525p |
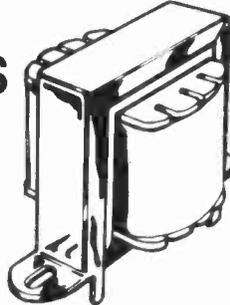
### MINIATURE TRANSFORMERS

240 Volt Primary

Secondary rated at 100mA.  
Available with secondaries  
of: 6 - 0 - 6, 9 - 0 - 9  
and 12 - 0 - 12. 92p each



### CRYSTALS

WIRE ENDED TYPE

| Freq. MHz |      |        |      |        |      |
|-----------|------|--------|------|--------|------|
| 0.100     | 380p | 4.000  | 250p | 12.000 | 250p |
| 0.300     | 380p | 5.000  | 250p | 18.000 | 300p |
| 1.000     | 320p | 6.000  | 250p | 20.000 | 300p |
| 2.000     | 320p | 8.000  | 250p | 32.000 | 300p |
| 3.276     | 250p | 10.000 | 250p | 48.000 | 300p |

### LOUDSPEAKERS

|           |         |      |
|-----------|---------|------|
| 56mm dia. | 8 ohms  | 70p  |
| 64mm dia. | 8 ohms  | 75p  |
| 64mm dia. | 64 ohms | 75p  |
| 70mm dia. | 8 ohms  | 100p |
| 70mm dia. | 80 ohms | 110p |



We now have an express telephone order service. We guarantee that all orders received before 5pm. are shipped first class on that day. Contact our Sales Office now! Telephone: 01-464 2951/5770.

ORDERS  
DESPATCHED  
BY RETURN  
POST

Quantity discounts on any mix TTL, CMOS, 74LS and Linear circuits: 25+ 10%. 100+ 15%. Prices VAT inc. Please add 30p for carriage. All prices valid to 30th April 1979. Official orders welcome.

BARCLAYCARD AND ACCESS WELCOME.



### TRANSISTORS

|        |     |        |     |        |      |
|--------|-----|--------|-----|--------|------|
| AC127  | 17p | BCY71  | 14p | ZTX109 | 14p  |
| AC128  | 16p | BCY72  | 14p | ZTX300 | 16p  |
| AC176  | 18p | BD131  | 35p | 2N697  | 12p  |
| AD161  | 38p | BD132  | 35p | 3N1302 | 38p  |
| AD162  | 38p | BD135  | 38p | 2N2905 | 22p  |
| BC107  | 8p  | BD139  | 35p | 2N2907 | 22p  |
| BC108  | 8p  | BD140  | 35p | 2N3053 | 18p  |
| BC109  | 8p  | BF244B | 36p | 2N3055 | 50p  |
| BC147  | 7p  | BFY50  | 15p | 2N3442 | 135p |
| BC148  | 7p  | BFY51  | 15p | 2N3702 | 8p   |
| BC149  | 8p  | BFY52  | 15p | 2N3704 | 8p   |
| BC158  | 9p  | MJ2955 | 98p | 2N3706 | 9p   |
| BC177  | 14p | MPSA06 | 20p | 2N3707 | 9p   |
| BC178  | 14p | MPSA56 | 20p | 2N3708 | 8p   |
| BC179  | 14p | TIP29C | 60p | 2N3819 | 22p  |
| BC182  | 10p | TIP30C | 70p | 2N3904 | 8p   |
| BC182L | 10p | TIP31C | 65p | 2N3905 | 8p   |
| BC184  | 10p | TIP32C | 80p | 2N3906 | 8p   |
| BC184L | 10p | ZTX107 | 14p | 2N4058 | 12p  |
| BC212  | 10p | ZTX108 | 14p | 2N5457 | 32p  |
| BC212L | 10p |        |     | 2N5458 | 30p  |
| BC214  | 10p |        |     | 2N5459 | 32p  |
| BC214  | 10p | 1N914  | 4p  | 2N5777 | 50p  |
| BC477  | 19p | 1N4001 | 4p  |        |      |
| BC478  | 19p | 1N4002 | 4p  |        |      |
| BC479  | 19p | 1N4004 | 5p  |        |      |
| BC548  | 10p | 1N4006 | 6p  |        |      |
| BCY70  | 14p |        |     |        |      |

### DIODES

|        |    |        |     |
|--------|----|--------|-----|
| 1N914  | 4p | 1N4148 | 3p  |
| 1N4001 | 4p | 1N5401 | 13p |
| 1N4002 | 4p | 1N5402 | 15p |
| 1N4004 | 5p | 1N5404 | 16p |
| 1N4006 | 6p | 1N5406 | 18p |

A SELECTION ONLY!  
DETAILS IN CATALOGUE.

|         |      |        |      |         |      |
|---------|------|--------|------|---------|------|
| 709     | 25p  | LM324  | 50p  | NE556   | 60p  |
| 741     | 22p  | LM339  | 50p  | NE565   | 120p |
| 747     | 50p  | LM380  | 75p  | NE567   | 170p |
| 748     | 30p  | LM382  | 120p | SN76003 | 200p |
| CA3046  | 55p  | LM1830 | 150p | SN76013 | 140p |
| CA3080  | 70p  | LM3900 | 50p  | SN76023 | 140p |
| CA3130  | 90p  | LM3909 | 60p  | SN76033 | 200p |
| CA3140  | 70p  | MC1496 | 60p  | TBA800  | 70p  |
| LM301AN | 28p  | MC1458 | 35p  | TDAl022 | 650p |
| LM318N  | 125p | NE555  | 25p  | ZN414   | 75p  |

### OPTO

| LEDs   | 0.125in. | 0.2in. |     |
|--------|----------|--------|-----|
| Red    | TIL209   | TIL220 | 9p  |
| Green  | TIL211   | TIL221 | 13p |
| Yellow | TIL213   | TIL223 | 13p |
| Clips  | 3p       | 3p     |     |

| DISPLAYS |           |      |  |
|----------|-----------|------|--|
| DL704    | 0.3 in CC | 130p |  |
| DL707    | 0.3 in CA | 130p |  |
| FND500   | 0.5 in CC | 100p |  |



### RESISTORS

Carbon film resistors.  
High stability, low noise 5%.

| E12 series. 4.7ohms to 10M. Any mix: |      |       |      |
|--------------------------------------|------|-------|------|
| each                                 | 100+ | 1000+ |      |
| 0.25W                                | 1p   | 0.9p  | 0.8p |
| 0.5W                                 | 1.5p | 1.2p  | 1p   |

Special development packs consisting of 10 of each value from 4.7 ohms to 1 Megohm (650 res.)  
0.5W £7.50. 0.25W £5.70

### CAPACITORS

HERE ARE JUST  
A FEW OF THE  
CAPACITORS STOCKED

| TANTALUM BEAD                                      |      |     |     |     |    | each |
|--|------|-----|-----|-----|----|------|
| 0.1, 0.15, 0.22, 0.33, 0.47, 0.68, 1 & 2.2uF @ 35V |      |     |     |     |    | 9p   |
| 4.7, 6.8, 10uF @ 25V                               |      |     |     |     |    | 13p  |
| 22 @ 16V, 47 @ 6V, 100 @ 3V                        |      |     |     |     |    | 16p  |
| MYLAR FILM   |      |     |     |     |    |      |
| 0.001, 0.01, 0.022, 0.033, 0.047                   |      |     |     |     |    | 3p   |
| 0.068, 0.1   |      |     |     |     |    | 4p   |
| RADIAL LEAD ELECTROLYTIC                           |      |     |     |     |    |      |
| 63V  | 0.47 | 1.0 | 2.2 | 4.7 | 10 | 5p   |
|  |      |     | 22  | 33  | 47 | 7p   |
|  | 100  |     |     |     |    | 13p  |
|  |      |     | 220 |     |    | 20p  |
| 25V  | 10   | 22  | 33  | 47  |    | 5p   |
|  | 100  |     |     |     |    | 8p   |
|  |      |     | 220 |     |    | 10p  |
|  |      |     |     | 470 |    | 15p  |
|  |      |     |     |     |    | 23p  |
| 10V  |      | 220 |     |     |    | 5p   |
|  |      |     |     | 470 |    | 9p   |
|  |      |     |     |     |    | 13p  |
|  |      |     |     |     |    | 23p  |

### 74LS

|      |     |       |      |
|------|-----|-------|------|
| LS00 | 16p | LS95  | 65p  |
| LS01 | 16p | LS123 | 56p  |
| LS02 | 16p | LS125 | 40p  |
| LS03 | 16p | LS126 | 40p  |
| LS04 | 16p | LS132 | 60p  |
| LS08 | 16p | LS136 | 36p  |
| LS10 | 16p | LS138 | 54p  |
| LS13 | 30p | LS139 | 50p  |
| LS14 | 70p | LS151 | 50p  |
| LS20 | 16p | LS153 | 50p  |
| LS30 | 16p | LS155 | 80p  |
| LS32 | 24p | LS156 | 80p  |
| LS37 | 26p | LS157 | 45p  |
| LS40 | 22p | LS164 | 90p  |
| LS42 | 53p | LS174 | 60p  |
| LS47 | 70p | LS175 | 60p  |
| LS48 | 48p | LS190 | 80p  |
| LS54 | 16p | LS192 | 70p  |
| LS57 | 29p | LS193 | 70p  |
| LS74 | 29p | LS196 | 80p  |
| LS75 | 44p | LS251 | 60p  |
| LS76 | 35p | LS257 | 55p  |
| LS78 | 35p | LS258 | 55p  |
| LS83 | 60p | LS266 | 40p  |
| LS85 | 70p | LS283 | 60p  |
| LS86 | 33p | LS290 | 55p  |
| LS90 | 45p | LS365 | 45p  |
| LS93 | 45p | LS366 | 45p  |
|      |     | LS367 | 45p  |
|      |     | LS368 | 45p  |
|      |     | LS386 | 35p  |
|      |     | LS670 | 180p |


### TTL

|      |      |       |      |
|------|------|-------|------|
| 7400 | 12p  | 7493  | 34p  |
| 7401 | 12p  | 7494  | 52p  |
| 7402 | 12p  | 7495  | 52p  |
| 7404 | 12p  | 7496  | 50p  |
| 7408 | 14p  | 74121 | 25p  |
| 7410 | 12p  | 74122 | 33p  |
| 7413 | 25p  | 74123 | 40p  |
| 7414 | 48p  | 74125 | 35p  |
| 7420 | 12p  | 74126 | 35p  |
| 7422 | 24p  | 74132 | 50p  |
| 7427 | 24p  | 74141 | 56p  |
| 7430 | 12p  | 74148 | 90p  |
| 7442 | 43p  | 74150 | 70p  |
| 7447 | 55p  | 74151 | 50p  |
| 7448 | 58p  | 74156 | 52p  |
| 7454 | 14p  | 74157 | 52p  |
| 7473 | 25p  | 74164 | 70p  |
| 7474 | 25p  | 74165 | 70p  |
| 7475 | 32p  | 74170 | 125p |
| 7476 | 28p  | 74174 | 68p  |
| 7485 | 70p  | 74177 | 58p  |
| 7489 | 145p | 74190 | 72p  |
| 7490 | 32p  | 74191 | 72p  |
| 7492 | 35p  | 74192 | 64p  |
|      |      | 74193 | 64p  |
|      |      | 74196 | 55p  |
|      |      | 74197 | 55p  |

### CMOS FULL DETAILS IN CATALOGUE

|      |     |      |      |
|------|-----|------|------|
| 4001 | 15p | 4029 | 60p  |
| 4002 | 15p | 4040 | 68p  |
| 4007 | 15p | 4046 | 100p |
| 4011 | 15p | 4049 | 28p  |
| 4013 | 35p | 4050 | 28p  |
| 4015 | 60p | 4066 | 40p  |
| 4016 | 35p | 4068 | 20p  |
| 4017 | 55p | 4069 | 16p  |
| 4018 | 65p | 4071 | 16p  |
| 4023 | 15p | 4075 | 16p  |
| 4024 | 45p | 4930 | 48p  |
| 4026 | 95p | 4511 | 70p  |
| 4027 | 35p | 4518 | 70p  |
| 4028 | 52p | 4520 | 65p  |

### SKTS

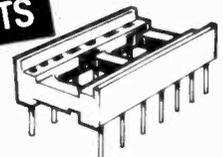

| Low profile by Texas |       |        |     |
|----------------------|-------|--------|-----|
| 8 pin                | 10p   | 24 pin | 24p |
| 14 pin               | 12p   | 28 pin | 28p |
| 16 pin               | 13p   | 40 pin | 40p |
| Soldercon pins:      | 100:  | 50p    |     |
|                      | 1000: | 370p   |     |

AT LAST! OUR  
NEW 40 PAGE  
CATALOGUE  
OF COMPON-  
ENTS IS  
AVAILABLE.  
SEND S.A.E.



Mail orders to: STEVENSON (Dept ET)

236 High St. Bromley, Kent, BR1 1PQ, England

## EMI SPEAKER BARGAIN

Stereo pair 350 kit. System consists of 13" x 8" approx. woofer with rolled surround, 2 1/2" approx. Audax tweeter, crossover components and circuit diagram. Frequency response 20 Hz to 20 KHz. Power handling 15 watts RMS. 20 watts max. 8 ohm impedance.

£14.95 Per stereo pair + £3.40 p&p.

★ As above but complete with all woodwork in kit form, finished in simulated teak veneer, with instructions. Size approx 20" x 11" x 9 1/2" **£28.00** Per stereo pair + £5.00 p&p

## EASY BUILD RECORD PLAYER KIT



for the D-I-Y man who requires a stereo unit at a budget price, comprising ready assembled stereo amp module, Garrard auto/manual deck with cueing device, pre-cut and finished cabinet work. Output 4 watts per channel, phones socket and record/replay socket including 2 SPHERICAL HI-FI speakers. **£19.95** p&p £4.05

## BARGAINS FOR PERSONAL SHOPPERS

### PORTABLE STEREO RADIO CASSETTE RECORDER UNREPEATABLE



MW, LW, SW and Stereo VHF. 6 watts output Battery/Mains operation.

**£69.95**

16v 18 VOLT MAINS TRANSFORMER. 2 1/2 amp.

**£2.50**

BSR Record auto deck on plinth with stereo cartridge ready wired.

**£11.95**

LED 5 function men's digital watch stainless steel finish

**£5.95**

LCD 5 function men's digital watch stainless steel finish

**£6.95**

LCD 8 Function CHRONOGRAPH men's digital watch, stainless steel finish.

**£13.95**

POCKET CALCULATOR. With LED display, memory and percentage key.

**£2.95**

### AM/FM DIGITAL CLOCK RADIO

Accurate 4 Digit Electronic Clock with 1/2" LED display. Buzzer and snooze timer.

**£11.95**

125 Watt Power Amp Module

**£13.95**

Mains power supply for above unit.

**£3.50**

MUSIC CENTRE CABINET with hinged smoke acrylic top, finished in natural teak veneers. Size 30 1/2" x 14 1/2" x 7 1/4" approx.

**£5.95**

MULLARD Built power supply

**£1.50**

DECCA DC 1000 Stereo Cassette P.C.B. complete with switch oscillator coils and tape-heads.

**£2.95**

DECCA 20w Stereo speaker kit comprising 2 8" approx. bass units + 2 3 1/2" approx. tweeter inc. crossovers

**£20.00**

VIDEOMASTER Super Score TV Game with pistol mains operation

**£14.95**

PORTABLE RADIO/CASSETTE RECORDER, AM/FM with clock.

**£41.95**

LW, MW, SW, VHF mains/battery operation.

**£8.95**

7" TAPE TRANSPORT Mechanism—a selection of models from

SANYO Nic/cad. battery, with mains charger equivalent in size and replaces 4 SP11 type batts. Size 3 1/2" x 1 1/4" x 2" approx.

**£7.50** p+p £1.50p

AM/FM STEREO TUNER AMPLIFIER CHASSIS COMPLETE

Ready built. Designed in a slim form for compact, modern installation.

Rotary Controls Vol/Dn/Off, Bass, Treble, Balance.

Push Buttons for Gram, Tape, VHF, MW, LW and 5 button rotary selection switch.

Power Output 5 watts per channel Sine at 2% THD into 15 Ohm 7 watts speech and music.

Tape Sensitivity Playback 400mV/30K OHM for max output Record 200mV/50K output available from 25KHz. (150mV/100K) deviation

FM signal Frequency Range (Audio) 50Hz to 17KHz within ± 1dB

Radio FM sensitivity for 30dB below limiting better than 10 uV

AM sensitivity for 20dB S/N MW 350 uV/Metre LW 1mV/Metre

Size approx length 16" x height 2 3/4" x depth 4 1/4"

240 Volts AC Complete with Circuit diagram. **£19.95** p&p £2.25


# Mullard

## AUDIO MODULES IN BARGAIN PACKS CURRENT CATALOGUE

PRICE £ **25** AT OVER PER PACK
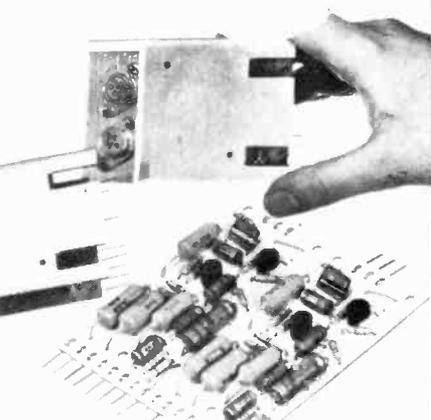
## SEE OUR PRICES

- PACK 1. 2 x LP1173 10w. RMS output power audio amp modules. + 1 LP1182/2 Stereo pre amp for ceramic and auxiliary input. **OUR PRICE** **£4.95** Illus. p+p £1.00
- PACK 2. 2 x LP1173 10w. RMS output power audio amp modules + 1 LP1184/2. Stereo pre amp for magnetic, ceramic and auxiliary inputs. **OUR PRICE** **£7.45** p+p £1.00
- PACK 3. 1 x LP1179/2 FM Tuning head with AM gang. 1 x LP1165/1 AM/FM IF module, 2 x LP1173/10w. RMS output power audio amp modules + 1 LP1182/2 Stereo pre amp for ceramic and auxiliary input. **OUR PRICE** **£9.95** p+p £1.00




## ACCESSORIES

Suitable power supply parts including mains transformer, rectifier, smoothing and output capacitors. **£1.00 p+p** **£1.95** p+p 50p **95p**

Recommended set of rotary stereo controls comprising BASS, TREBLE, VOLUME and BALANCE.

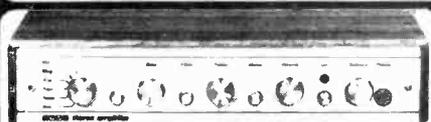**THIS MONTH'S OFFER**  
added to our bargain packs  
When you buy Pack 3 at £9.95, together with a mains transformer at £1.95 and a set of controls for 95p you receive **FREE** a Mullard LP1400 Decoder to match. **£12.85**  
Listed at £11.90



**20 x 20 WATT STEREO AMPLIFIER**  
Viscount IV unit in teak finished cabinet. Silver fascia with aluminium rotary controls/pushbuttons, red mains indicator and stereo jack socket. Functions switch for mic, magnetic and crystal pickup, tape tuner and auxiliary. Rear panel features two mains outlets DIN speaker and input sockets plus fuse 20x20 watts RMS 40x40 watts peak. For use with 8 to 15 ohm speakers. **£29.90** + £2.50 p&p

## SPECIAL OFFER FOR PERSONAL SHOPPERS ONLY

FREE. 4 dimensional stereo sound adaptor, when purchasing the 20x20 Viscount amplifier.

**30x30 WATT AMPLIFIER IN KIT FORM**  
For the experienced constructor complete in every detail, same facilities as Viscount IV, but with 30x30 output. 60x60 watts peak. For use with 4-15 ohms speakers. £23.00 without cabinet. £29.00 complete with cabinet. p&p £2.50 in each case.

**£23.00** + £2.50 (NDTE Cabinet not without cabinet. p&p available separately.) **£29.00** + £2.50 p&p complete with cabinet

## SPECIAL OFFER Complete with case 30x30 WATT AMPLIFIER IN KIT WITH SPEAKERS

2 Goodman compact 12" bass woofers with cropped size 14.000 Gauss magnet. 30 watt RMS handling + 3 1/4" approx. tweeters and crossovers. **£49.00** p&p £4.00

## BUILT AND READY TO PLAY 39.00

30x30 Viscount. Available fully built and tested. **£39.00** p&p £2.50

## BARGAIN PORTABLE DISCO CONSOLE



with built-in pre-amp  
Here's the big-value portable disco console from RTVC! It features a pair of BSR MP 60 type auto-return, single play professional series record decks. Plus all the controls and features you need to give fabulous disco performances. Simple connects into your existing slave or external amplifier.

**£64.00** p & p £6.50



**50 WATT MONO DISCO AMP**  
**£29.95** P&P £2.50  
Size approx. 13 1/2" x 5 1/2" x 6 1/2"  
50 watts rms. 100 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with integral push-pull switches. Independent bass and treble controls and master volume.

**SPECIAL OFFER.** The above 50 watt amp plus 4 Goodman Type 8P. 8" speakers. Package price £45.00 + £4.00 P&P.



**70 & 100 WATT MONO DISCO AM**  
Size approx. 14" x 4" x 10 1/2"  
Brushed aluminium fascia and rotary controls  
Five vertical slide controls master volume, tape level, mic level, deck level. PLUS INTER DECK FADER for perfect graduated change from record deck No. 1 to No. 2, or vice versa. Pre fade level control 70 watt peak (PFL) lets YOU hear next disc before fading 140 watt peak  
1 in. VU meter monitors output level. p & p £4.00  
Output 100 watts RMS 200 watts peak. 100 watt **£65**

## STEREO CASSETTE TAPE DECK ASSEMBLY

Consisting of ready built tape transport system/mechanism, mated to the electronics. Unit is ready built for installing into cabinet of own choice. Features include pause control, solenoid assisted auto-stop, 3 digit tape counter, belt driven balanced fly wheel by DC motor with electronic speed control. Twin VU meters. Specification Power Output more than 0.5w. mc. -85dB 10KHz. DIN -47dB 100KHz. Track 2 channel stereo record play-back. Tape speed 4.8cm/sec. Free response 50 1200 Hz signal to noise ratio 42dB Recording system AC bias Erasing system AC erase Bias Irreg. 57KHz. Compatible for both normal and chrome dioxide tapes. Size of mechanism only 4 1/2" x 6 1/2" x 11 1/4" approx. included a moulded top-plate as illustrated 13 1/2" x 9 1/2" approx with circuit diagram **£25.00** P&P £2.50

Opt. extras. Mains transformer to suite **£2.50** + £1 p & p.



323 EDGWARE ROAD, LONDON W2  
21E HIGH STREET, ACTON W3 6NG  
ALL PRICES INCLUDE VAT AT 12 1/2%  
All items subject to availability. Price correct at 1.11.78 and subject to change without notice

Personal Shoppers EDGWARE ROAD LONDON W2 Tel: 01-723 8432. 9.30am-5.30pm. Half day Thursday. ACTON: Mail Order only. No callers. GOODS NOT DESPATCHED OUTSIDE UK

# **computing today**

**No 3**

**January  
79**

THE NEW MAGAZINE  
FOR SMALL SYSTEMS  
WITH BIG IDEAS . . . . .



**Personal Computing~  
The Early Years**

**Softspot**

**Presented as a supplement to ETI.**

# Introducing the personal computer you've waited for. THE EXIDY SORCERER.

**SORCERER COMPUTER SYSTEM** Complete with Monitor

The Sorcerer Computer is a completely assembled and tested computer system. Standard configuration includes 63-key typewriter style keyboard and 16-key numeric pad, Z80 processor, dual cassette I/O with remote computer control at 300 and 1200 baud data rates, RS232 serial I/O for communications, parallel port for direct Centronics printer attachment, 4K ROM operating system, 8K ROM Microsoft BASIC in Rom Pac™ cartridge, composite video of 64 char/line 30 line/screen, 128 upper/lower case ASCII set and 128 user-defined graphic symbols, operation manual, BASIC programming manual and cassette/video cables, connection for S-100 bus expansion.

only **£950** Credit facilities available. + 8% VAT



**LOOK!**

- \*32K RAM on board
- \*RS232 interface
- \*8K BASIC ROM
- \*CUTS interface
- \*4K MONITOR
- \*KANSAS CITY interface
- \*S100 BUS
- \*User defined graphic symbols
- \*Z80 cpu

## KEY BOARD


756 GEORGE RISK

Brand new professional ASCII keyboards (USA)

Full technical details included. RRP £60.00

Only **£49.90** + 8% VAT.

Ready built, tested and guaranteed.

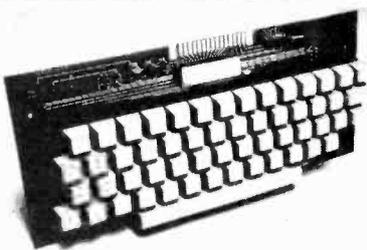


## COMPUTER JOYSTICK

Plugs into your Nascom P.I.O. No extras. Software and full documentation supplied. Plus free game cassette.

**£14.90** each **£28.90** per pair
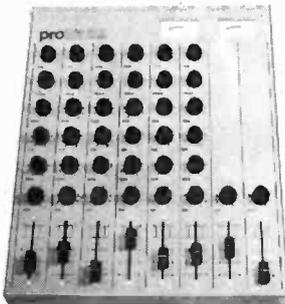
## COMP PRO Mixer

Professional audio mixer that you can build yourself and save over £100.



6 into 2 with full equalization and echo, cve and pan controls.

All you need for your own recording studio is a stereo tape or cassette recorder.

This superb mixer kit has slider faders, level meters and additional auxilliary inputs.

Only **£99.90** plus 8% VAT for complete kit Plus **FREE** power supply valued at £25.00


Ideal for  
**DISCOS STAGE MIXING HOME STUDIOS AND MANY OTHER APPLICATIONS**

## COMPUTER COMPONENTS

Send for our Spring 1979 catalogue. 0.60p Full of Computer Components, Peripherals and systems.
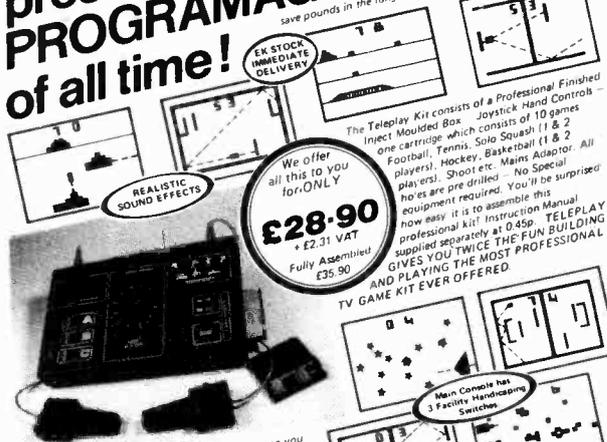
# Teleplay presents the PROGRAMAGAME of all time!

TELEPLAY have produced a new product of easy to assemble cartridge games, for you and all your family, that will not go out of date. Just ADD each new cartridge, as it becomes available, and your colour video centre will be up to date the Teleplay way. You will save pounds in the long run. Works OK on Black and White TV.



EX STOCK IMMEDIATE DELIVERY

We offer all this to you for **ONLY £28.90** + £2.31 VAT Fully Assembled £35.90

Every 3 months a NEW game will become available to you and those already under production include Submarines, Space War, Wipe Out and many more. The price of these will vary from £12 to £19 depending upon the complexity of the game.

Additional cartridges NOW available include:  
Stunt Cycle 4 games  
Tank Battle Cartridge  
Road Race 2 games

Cartridges and Hand Controls £14.90 - £14 VAT Fully assembled and £3.00  
Cartridge Controls already with basic kit £12.90 - £1.03 VAT  
NEW - WIPE OUT cartridge - 6 games £13.90 + £1.11 VAT

Cartridges come complete with printed case and easy to follow assembly instructions. All parts fully guaranteed.

Electrical knowledge is not a necessity to assemble this project just simple soldering

## INTERESTED IN HOME COMPUTING?

**FREE B BUG** valued at £23.00 plus 10 x C12 cassettes valued at £4.00 WITH EVERY NASCOM

Start now and don't get left behind **THE NASCOM 1** is here Ex-stock with full technical services

Plus the opportunity to join the fastest moving club of personal computer users enabling you to get the most out of your computer. You can OBTAIN and EXCHANGE programs and other software - many now available.

The Powerful Z80 Microprocessor  
Professional Keyboard  
1 Kbyte Monitor in EPROM  
2 Kbyte RAM (expandable)  
Audio Cassette interface  
Plugs into your domestic TV  
Easy construction from straightforward instructions  
- no drilling or special tools  
- Just neat soldering required.



Only **£197.50** + 8% VAT (includes p & p + insurance)  
Manuals separately 2.95  
Z80 programming Manual 6.90  
Z80 Technical Manual 2.95  
P10 Technical Manual 2.95  
(All prices add 8% VAT)

Monitor quality improved 2.50  
TV Modulator 2.50  
Power supply suitable for NASCOM 19.90

**NASCOM AD ONS** - Nascom improved monitor B Bug (2K) featuring - \*Four times tape speed \*Direct text entry without ASCII \*Extended keyboard facility \*Additional useful subroutines **£23.00**

Nascom Software library. Send SAE for lists and prices.

**BLANK C12 Racial Quality CASSETTES £4.00 for 10**

All prices include VAT except where shown. Orders over £5 post and packing free otherwise add 20p. Please make cheques and postal orders payable to COMP, or phone your order quoting BARCLAYCARD or ACCESS number.

**COMP COMPUTER COMPONENTS**

14 STATION ROAD · NEW BARNET · HERTFORDSHIRE · TEL: 01-441 2922 (Sales)  
CLOSE TO NEW BARNET BR STATION - MOORGATE LINE 01-449 6596  
OPEN - 10am to 7pm - Monday to Saturday



# Airamco Ltd.

## MICRO COMPUTER PRODUCTS

Distributors for JADE COMPUTER PRODUCTS  
All products brand new with full industrial specification

### STOP PRESS!

#### SD SALES Z-80 STARTER KIT

Single card development system — like a KIM or D2 but uses Z80, on board PROM PROG up to 2K RAM. 2 x 5100 sockets provided for on board — plus many new features.

KIT PRICE ..... £159.00  
ASSEMBLED + GUARANTEE ..... £249.95

| S100 COMPUTER CARDS KIT   | ASSEMBLED | BARE BOARD |
|---|-----------|------------|
| Mother Board ..... £71.00   | £82.50    | £26.25     |
| Desk Top Rack, 12 slot mother board + 15A @8V, 2A @ ± 16V ..... £199.00   |           |            |
| Jade 8080A CPU BOARD £75.00   | £122.50   | £22.50     |
| Jade 8K static RAM BOARD 450nS ..... £94.50                               | £112.50   | £19.95     |
| Jade 8K static RAM BOARD 350nS ..... £104.95                              | £119.96   | £19.95     |
| Jade 8K static RAM BOARD 250nS ..... £127.50                              | £142.50   | £19.95     |
| S.D. Sales "EXPANDORAM" Dynamic Memory 375nS access time 8K ..... £113.25 |           |            |
| Memory 375nS access time 16K ..... <b>£189.00</b>                         | £229.00   | £189.00    |
| Memory 375nS access time 32K ..... <b>£297.00</b>                         | £337.00   | £297.00    |
| Memory 375nS access time 64K ..... <b>£513.00</b>                         | £553.00   | £513.00    |
| VERSAFLOPPY DISK CONTROLLER (up to 4 drives 5 1/4" or 8") ..... £111.75   | £165.00   | ---        |
| SHUGART 8" Drive ..... ---  | £385.00   | ---        |
| PERTEC 5 1/4" Drive ..... ---   | £225.00   | ---        |

#### Components

|  |   |
|--|---|
| 2708 1024x8 EPROM £6.99                | AY-5-2736 ..... £9.50   |
| 2516 2048 x 8 EPROM ..... £29.90       | 21L02-1 450nS ..... £1.20   |
| (equivalent of above) T.I. ....        | 8 for ..... £7.92   |
| 1702 256x8 EPROM £4.85                 | 21L02 250nS ..... £1.40   |
| 2104 4096x1 DRAM £3.50                 | 8 for ..... £9.60   |
| 8 for ..... £26.00                     | 2112-1 256x4 (450) ..... £2.25  |
| 2107B-4 4096x1 DRAM ..... £3.50        | 4044 4Kx1 (450) ..... £7.45   |
| 8 for ..... £26.00                     | 4045 1Kx4 (450) ..... £8.25   |
| Note New Low Prices 16K Dynamic Memory | New Device MK4118 N4 (24 pin) 1k x 8 bit static RAM 250 NS. Similar pin out to 2708 EPROM. Price £16.50. Each data available. |
| 4115 8kM DRAM ..... £9.99              | 8212 ..... £2.49  |
| 4116 16kx1 DRAM ..... £14.99           | 8216 ..... £2.75  |
| 8 for ..... £89.95                     | 8224-4 ..... £7.46  |
| AY 51013 UART ..... £4.50              | 8226 ..... £2.95  |
| AY51014 UART(5V) ..... £6.50           | 3881 ..... £9.50  |
| AY53600 ENCODER ..... £9.99            | 3882 ..... £9.50  |
| 8080A CPU ..... £8.99                  | S100 Skts. ..... £3.30  |
| 2114 (450ns) ..... £6.75               | Textool 24 pin Zero force Skt. ..... £5.60  |
|  | 81LS95 ..... £1.25  |
|  | 81LS97 ..... £1.25  |

Secondhand ASR 33 Teletype with paper tape ..... £399.00  
Shugart Floppy Disc Drive Controllers, 8-inch and 5-inch

All Prices EXCLUDE VAT @ 8%.  
Trade discounts on Quantity  
Please add £1.00 P&P for S100 items then add VAT @ 8%.  
24-hr. Ansaphone order service with ACCESS or BARCLAYCARD.  
MAIL ORDER ONLY



For components please add 40p P&P, then add VAT @ 8%.

AIRAMCO LTD.  
30 WITCHES LINN  
ARDROSSAN  
AYRSHIRE  
KA22 8BR  
TEL 0294 65530  
TELEX 779808 RAMCO

Semiconductor prices are always changing and the trend is generally downwards. So ring for latest up-to-date details.

# computing today

## No.3 January 1979

|                        |    |                        |
|------------------------|----|------------------------|
| Letters                | 4  | U to us                |
| Small business machine | 6  | TRS-80 in action       |
| TRITON monitor         | 8  | Make more of TRITON    |
| The early years        | 18 | Youthful computing     |
| TRS-80 Level II        | 23 | One up on one          |
| BASIC explained        | 27 | Part 3 of our series   |
| Softspot               | 30 | Play the reversal game |

Editor: Gary Evans

Production: Pete Howells

Advertising: Mark Strathern, David Sinfield, Joy Cheshire



A number of errors that crept into last month's issue have been brought to our attention. Once again Phil Cornes was not credited in connection with the BASIC explained Series. Q1 in the EPROM Programmer should be shown as a 2N3638 and not PN3638 as in both Parts list and Circuit Diagram. The opto isolator is not a critical component and could be substituted by a more readily available device.

The missile program appearing in Softspot also contained a number of errors. Lines 90, 110 and 170 should be altered as follows

90 Y = (RND(16)-1)\* 64;Z = 1

110 VDU Z,32

170 VDU @(I+2),32

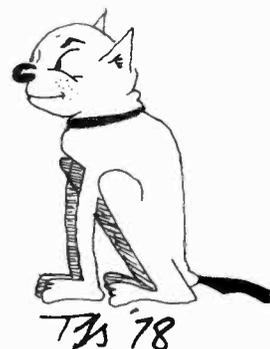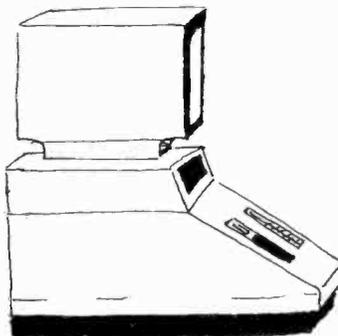

Man's best friends

# Letters

We would like to hear your views on computers and computing, we'll publish the best views in this, our new letters' page. This month, Mike Hughes — designer of the TRITON — answers a letter drawing attention to certain aspects of the computer design.

Dear Sir,

I am writing to request you to urgently consider the redesign of the Triton Computer, as it suffers from a serious design fault which will make it unreliable as it stands, and which will cause difficulties for expansion. As you may be now be aware I am referring to the data bus buffering. While the 8080a chip set has been buffered by a high drive (and unnecessary) 74LS245, the memory chips must also drive the data bus, and these have a single TTL drive capability. Bits 7 and 8 of the data bus are the most heavily loaded, with 5 LSTTL loads (= 1 TTL load), plus the UART, which presents 1 TTL load (at least this is what Texas say for the TMS 6011). Hence the memory chips are having to drive twice their rated load. Specifications being what they are this will usually be OK, especially when running so slowly. However usually is just not good enough in this situation, and several constructors are bound to get chips which are close to specification, and will be intermittent errors. The problem will become significantly worse when the bus expansion connector is used, as this will add an extra load, together with a lot of added cross-talk and bus noise.

As many of the people who may be considering the construction of this unit will not have the knowledge or equipment to detect this problem, I must, on their behalf, urge you modify this design as soon as possible.

A second, though less important, potential problem is in the -5V power supply, which is not a minor bias supply for 2708s (at least not according to Texas and Intel specifications). The specification is 30mA typical, 45mA max. Hence the power supply should be able to supply 180mA, which implies a series resistor of about 39-. This will dissipate a lot of power, and an IC regulator would be better.

Yours faithfully,

R. A. Cottis,

Corrosion and Protection Centre  
UMIST

I cannot disagree with anything in Mr Cottis' letter. I am, in particular, grateful to him for identifying the -5V rail problem which was an oversight on my part.

Unfortunately, the values given for R1 and ZD1 were a "hangover" from an early prototype which operated with a single EROM. These should have been changed to accommodate the higher current consumption of the completed system. Mr Cottis is quite correct in saying that R1 should be 39 ohm with a power rating of 1.5W. At the same time, ZD1 should be upgraded to have a power dissipation of 1W. The latter is necessary in the event of the system being operated with only one EROM in position.

Fortunately (or unfortunately as the case may be) this error will not show itself in cases which operate with 3 EROMS whose current consumption averages just below the "typical" value. Not many people will,

therefore, have experienced any problem. If they had the error would have been discovered earlier. Readers who have their system up and running with 3 EROMs in position need not react to the problem urgently — nevertheless, they should upgrade these components in due course prior to inserting a 4th EROM. Constructors just about to start are strongly advised to use the higher rated components from the word go.

The driving capabilities of the 2111 memories on the data bus is a much more difficult question to answer. Mr Cottis is quite correct in every thing he says by taking worst case input loads and output drive capabilities. The worst case conditions he mentions are, however, stated with a 0.4 or 0.45V maximum "O" level — allowing a 400mV low level noise margin.

Stretching the loading in the worst case condition will certainly encroach on the noise margin but as  $V_{OL}$  rises, as a result, so the input current will decrease. From figures available it would appear that in the worst case condition (including an extra LS load for an external bus driver), the noise margin could reduce to about 200 mV, and this would not be acceptable for stringent applications or in extremely high noise conditions.

As Mr Cottis implies, it is very unlikely that one will be so unlucky as to have all the worst case conditions stacked against him and this is what I was relying on to provide a reasonable noise margin for domestic/office noise environments. The "Bête Noire" is clearly the UART but I was reluctant to provide extra on board buffering for this for two reasons:-

1. It would have given rise to difficulties in layout — involving more board area.
2. This would have increased the board cost as well as possibly requiring extra components.

If one accepts that an extreme worst case conditions is unlikely there will be negligible problem at normal ambient temperatures. Even under a worse case situation at temperatures up to 60°C the system will still operate — but with impaired noise margin. It is in the latter situation that one might have problems with busbar noise etc.

I am indebted to Mr Cottis for drawing attention to this potential problem and in view of his comments, would suggest that readers planning expansions should keep their first umbilical cable from the main board to the peripheral mother board (soon to be published) as short as possible. They should also introduce a further bi-directional buffer on the data bus at the earliest position possible. This, incidentally, is already planned on the extension mother board.

To assure readers of the minimal chance of problems arising, we should point out that of the dozens of Tritons already built and working, there has not been one instance of bus noise problems. This includes one system which, already, has been externally expanded for a further 4k of RAM with no extra buffering.

M. J. Hughes

The exciting new  
**TRITON**  
 Personal Computer  
 exclusively from:

# TRANSAM



**Complete kit of parts available only £286 (+ VAT)**

**Basic in Rom:** a powerful 2k Tiny basic resident on board, makes Triton unique, easy to use and versatile.

**Graphics:** 64 Graphic characters as well as full alpha numerics.

**Single Board:** Holds up to 8k of memory, 4k RAM and 4k ROM, supplied with 3k ROM and 2k RAM.

**Memory Mapping:** 2 mode VDU, I/O or memory mapped for animated graphics.

**Cassette Interface:** crystal controlled Modem tape I/O with auto start/stop + "named" file search.

**UHF TV Interface:** On board uhf modulator, plugs into TV aerial socket.

**Comes Complete** with KEYBOARD, CASE, POWER SUPPLY, THRO-HOLE PLATED QUALITY P.C.B., FULL DOCUMENTATION POWERFUL 1k MONITOR & 2k TINY BASIC PLUS ALL COMPONENTS INCL. IC SOCKETS. NOTE TV SET & CASSETTE NOT INCLUDED.

**Expansion:** Fully buffered for up to 65k of memory on expansion busbar.

**Building a better computer wasn't easy – but we did it.**

# TRANSAM

All components can be bought separately and eleven packs can be purchased on an easy-to-buy scheme. See catalogue.

The P.C.B. alone is £50 + VAT plus £1 for packing and postage.

VAT rate is 8% on all kit components.

## TRANSAM

**TRANSAM COMPONENTS LTD.**  
 12 CHAPEL STREET  
 LONDON, NW1 TEL: 402 8137

NEXT TO EDGWARE ROAD TUBE STATION MET. LINE., TRITON COMPUTER IS THE TRADE MARK OF TRANSAM COMPONENTS LTD

I am interested in the Triton

Name \_\_\_\_\_

Address (please print) \_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

ET1 9

TO TRANSAM COMPONENTS LTD.  
 12 CHAPEL STREET, NW1

Please send me the following

1. A copy of your latest catalogue  
I enclose 30p + S.A.E. 9" x 7
2. A copy of the Triton Manual  
I enclose £5 + 70p P & P.
3. A complete kit of parts for  
Triton Computer. £286 + VAT  
+ £4 P & P
4. A Printed Circuit Board  
£50 + VAT & £1 P & P

TOTAL ENCLOSED £.....

Cheque, Money Order, etc.



BARCLAYCARD, ACCESS,  
 VISA & MASTER CHARGE  
 ARE WELCOME. SEND  
 YOUR CARD NUMBER WITH  
 ORDER



# TRS-80: A Small Business Application

TERRY JOHNSON owns, with a partner, an insurance brokerage firm with twelve branches spread across the country. The firm also has interests in various property. Having used a computer bureau to process various accounting information, the firm are at present installing a TRS-80 to provide all the bureau facilities plus additional services.

**How did you start in business?** About 20 years ago, after coming out of the RAF, where I was a night fighter pilot, I needed a job. I had no business background but managed to get a job with an insurance company. There I found out there were such things as insurance brokers and after a bit of a late night study, I set myself up as a broker. Things, like topsy, grew from there, at our peak in 1974 we had 18 branches, but have now cut back to 12 — We employ 10 managers and about 40 other staff.

**Your first involvement with computers was via a computer bureau?** That's right, about five years ago we decided that the volume of accounting work generated by the various branches was getting to a level where some form of automation was necessary. We approached a number of the recognised agencies to see if they could offer us the type of package we wanted, without exception the products they offered would have meant considerable changes to our systems — not at all what we wanted.

At this point we decided on a different approach, we found — through the yellow pages I think — a specialist computer firm which undertook to design programs to customers' requirements. The firm had a scientific background and had never tackled anything along the lines we were asking. They accepted the challenge and a short time later we had a FORTRAN program that did all we wanted — simply keeping track of money in and money out and of our commodity — insurance policies in our case — but it might just as easily have been nuts and bolts or oranges.

**Did you encounter any problems with the system?** No, everything went very smoothly, we prepared our own program cards on a second hand flexowriter we picked up for £1000 and 48 hours later we had our batch back. During that first year about the only thing that happened was that the system was improved to provide a profit/loss statement and balance sheet.

**When did the Tandy TRS-80 come onto the scene?** About the middle of the year but the first time I realised that an "in house" system might be within our reach was at the DIY computer show at the beginning of this year.

**Why even consider a new system when your existing one was working so well?** To save money. We calculated that a system costing around £2500/£3000 could save us money over a period of 5 years with, of course, all the benefits of in house computing.

**Back to the Tandy then?** — Yes, in April of this year I went to the States on holiday and after looking around at what was available off the shelf over there at that time I decided to buy a Tandy TRS-80. The machine I bought was a Level 1 16K machine.

**Any problems getting it through customs?** Not after it had been classified as a data recording machine by binary system — no I paid my 7% duty on hardware and 8% VAT and I was through. I'd saved myself a lot of money. The cost in pounds was about £520, compared to the £700 odd that Tandy UK wanted assuming there was such a machine in this country.

**What about servicing if the machine goes wrong?** Tandy have a 90 day warranty on their equipment, which is available to first and subsequent owners in any country where Tandy have outlets — I wasn't worried about servicing.

**Have you had any trouble with your machine?** Yes, soon after I began using it, the keyboard suffered from an excessive amount of contact bounce. I took it to my local Tandy dealer, and it was back within a week — repaired at no charge under the warranty.

**How did you get on with the machine in those early days?** I had no experience of programming but found the Tandy manual soon had me familiar with BASIC and frustrated at the limitations of the level 1 machine.

I sent my TRS-80 to Tandy together with £79 for it to be upgraded to a Level 2 unit.

**What was your next step?** Well now came the most frustrating time for me, Level 2 BASIC was just what I wanted, but without a printer, floppy and more

memory the system just could not cope with the work I wanted it to do. Tandy had plans for expansion but no hardware available. I started looking around at other machines. The PET would never be acceptable to any typist with its present keyboard but the APPLE looked promising. I bought an apple this July but returned it about a week later, the reasons were that my machine kept crashing and as the BASIC I was using, Applesoft II was on tape, a five minute restart each time became trying. Add to this the fact that I was promised a number of hardware items that just didn't turn up and the Apple was not working out.

**Back to Tandy?** Yes. August was a dull month but I'd been promised the first expansion interface to arrive in this country and that arrived in September. The expansion interface contains space for an additional 16K or 32K RAM, a dick-controller for up to four disks, dual cassette decks as well as a Centronics parallel port.

After a bit of persuasion Sintrom at Reading — having sold me their ex-demonstration printer — hooked the printer up to the TRS-80, as the lead supplied did not produce any results this was a great leap forward — hard copy.

Things were moving fast now, as soon after this I discovered that a Micropolis disc drive would plug directly into the Tandy interface. I now had a system that could do all that I demanded of it.

**Does this bring us up to date?** No, a couple of weeks ago I went to the States again and picked up a couple of Tandy disks, a screen printer, a back up CPU and some extra memory. About \$3000 worth, again a

considerable saving on buying over here.


**What about the software development?** Of course that's been going on all the time, I've had no real difficulties with the task. The bulk of the work is done now, it's just a matter of getting the time to sort out the rest of the system for our target start date of January 1st.

**Why should a small business man consider using one of these small computer systems?** Three main reasons I think. Staff time and skill levels can be cut if a sensible system is devised. Accounting information that is good enough for our auditors to accept can be produced. Thirdly a vast flow of statistical information can be generated that gives the business man a far better idea of the performance of his operation at any point in time. What most people do by feel now can be done far more accurately by the computer. These three things together all add up to cutting costs.

**Do you think small business men could cope with setting up a system such as yours without outside help?** Most small businessmen are of above average intelligence — they have to be to survive. They also, in general have the drive and energy to get things done. I hadn't any knowledge of computers at the start of this year and reckon that now I have put together a system that will save me time and money. If I can do it I'm sure many other people in my position could. With the various software packages coming on the market at low cost, the business man may only be involved in a very small amount of work to get a low cost system to do exactly what he wants of it.
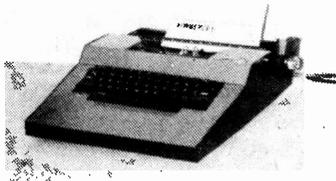
## Hard Copy

This printer puts word processing within the scope of your pocket



**TOP QUALITY TYPESCRIPT. SOLENOID DRIVEN FOR TTL CONTROL. ROM DECODED TO ACCEPT ASCII PARALLEL DATA INPUT. 8 CPS. 11" CARRIAGE (125 CHARS)**

Fully built with psu and case . . . **£182.86**

Also supplied as print mechanism only. Includes motor, solenoids and driver circuits. Add your own logic and case . . . **£144.65**

Add £3.50 p&p, then add VAT.

Other printers available; tally-roll dot matrix printer and low cost teleprinter. Send for details.

**KIMBERLEY BUSINESS RECORDS**  
2, Hartington Road, Gosport, Hants.

GOSPORT 86642

IN SCOTLAND

IN SCOTLAND

## NASCOM 1

Z80 Microcomputer kit

Undoubtedly the finest value for money kit available anywhere. Fully socketed.

INTERFACE FOR:

TV (UHF)  
TV Monitor  
Cassette  
Teletype  
32k Ram expansion board

May be seen working  
9 a.m. - 5 p.m. Mon.-Fri.

Callers welcome

**Price £197.50 + VAT (8%)**

Callers welcome



**STRATHAND**  
44 ST. ANDREW'S SQ.  
GLASGOW G1 5PL  
041-552 6731

Callers welcome



Tel. order welcome with Access and Barclaycard

# TRITON Software

## —MONITOR

Mike Hughes takes a detailed look at the Tritons monitor and describes some machine code programs that can be run on the computer

If you have built the TRITON computer you will want to get the best out of it and there are several modes in which it can be used. You can write and run programs in BASIC but you may wish to record and recall these to and from tape. To do this you need to know something about the MONITOR. You may wish to use the computer for control purposes for which you need to write machine language instructions. To do this it is essential to go through the Monitor — possibly making use of some of its in-built sub routines.

For those learning about computers it is a very good idea to get a grasp of MACHINE CODE. It is not difficult to learn and can make life much more exciting as you will be able to get the computer to respond much more quickly than it will through a BASIC Interpreter. Sometimes you can get several thousand times the speed for certain operations. To do this on the TRITON you must operate through the MONITOR.

TRITON's standard MONITOR is a program written in machine code which is held in ROM starting at address location 0000H. Its purpose is primarily to initialise the machine and to give it an elementary intelligence so that you can communicate with it. For this reason the machine must start off at the beginning of the monitor program every time it is switched on otherwise it becomes a worthless heap of rather expensive electronic components — unable to do anything. The first machine code instruction that the computer sees in the Monitor sets the STACK without which it would be impossible to do much in the way of decision making via nested sub-routines. It then proceeds to look at the next instruction which, in the case of TRITON, enables the interrupt operation if ever it is needed to be used. The following instruction is a JUMP which leads on to the first of the main routines called SCANMEM. This routine points to address 1600H and writes FFH into it. It then reads back the value from that address and checks that the FFH was actually stored. Furthermore it writes OOH into the same location and checks that too. This is a check that the memory is there and working which, at the same time leaves the memory location clear (i.e. containing OOH). The monitor routine then steps up one memory byte — to 1601H and does the same. This process is carried out on every successive location from 1600H upwards until the computer finds an error. The address of the location where the error occurred is most likely to be the top of the RAM work area but could be the address of a faulty IC. In either event this top address is written into a pair of RAM bytes used by BASIC 14.1 to tell BASIC how much work space is available. The two bytes of memory used for this are 1481H and 1482H. As a general rule

whenever two byte instructions or data are written into memory the 8080 microprocessor expects to see the least significant byte in the lower value of the two addresses. Thus if 2000H was the location where memory ended — as found by SCANMEM, location 1481H would contain OOH while 1482H would contain 20H.

After checking the memory the monitor initialises the computer which acknowledges this on the screen with its standard message:

```
TRITON READY  
FUNCTION? P G I O L W T
```

The Monitor then goes into a keyboard loop and the computer effectively waits for you to tell it what to do. This will depend on which key you depress. The letters it expects you to type are those shown in its acknowledgement and are abbreviations for seven different primary operations you can do with the monitor. These are:

- P = Inspect any memory location and, if necessary change, or insert a byte of data. When the data is entered the computer automatically steps to the next address showing what is currently there and waits to see if you wish to change it.
- G = Start running a program from any specified starting address location. The computer asks you, within this routine, what start location you want.
- I = Input from tape recorder. The computer asks you for the header code of the file and then searches for it. When it has been found the data is written into the computer's memory starting at location 1600H. When the flag marking the end of the record has been found the computer re-initialises with an abbreviated form of its initial "switch on" message.
- O = Output a program to the tape recorder. This, again asks you to give your recording a header code. The routine automatically outputs programs written in BASIC and stops when it gets to the end of file address (the address written into bytes 1600H and 1601H by BASIC). For user written machine code programs you have to manually enter the address immediately following your last instruction into these two bytes. Tapes are ALWAYS loaded and dumped with 1600H being the start location! When dumping has finished the computer re-initialises.
- L = List the machine code content of all locations starting from any specified address. The

computer asks for the first address then prints out the contents of this and the next 14. It then asks MORE? and expects you to type Y otherwise it re-initialises.

W = Typewriter mode. The computer behaves just as if it was a keyboard and VDU. Anything you type is displayed on the screen including graphics. Cursor control and special VDU functions — e.g. Clear Screen, Reset Cursor etc all operate but the computer responds to nothing except CONTROL C which makes it re-initialise.

T = Jump to BASIC L4.1. This command causes the computer to jump out of the control of the Monitor into the control of BASIC. CONTROL C will jump back out of BASIC into the initialisation condition of the Monitor.

Note that CONTROL C will, in nearly all cases, get you out of an operation and back to the initialisation condition. The only times when it fails to do this are when you are locked in a user written machine code program loop; are searching tape for a non-existent header or are outputting to the tape recorder. In these three cases you will have to use Interrupt 2 (which re-initialises without clearing memory) or RESET which goes through the SCANMEM routine and erases any data in memory.

When the computer asks for its initial instruction via one of the above letters you simply have to type the letter. No carriage return is needed. If you type the wrong letter the computer replies "INVALID" and waits for you to try again.

Here are some examples to try with the above functions:

#### LED PORT TEST ROUTINE

|      |      |          |    |   |
|------|------|----------|----|---|
| 1600 | CALL | INCH     | CD | Input data from keyboard to accumulator             |
| 1601 | —    | —        | 0B |   |
| 1602 | —    | —        | 00 |   |
| 1603 | CMA  | —        | 2F | Complement contents of accumulator.                 |
| 1604 | OUT  | PORT 03H | D3 | Output contents of accumulator to PORT 3 (LED port) |
| 1605 | —    | —        | 03 |   |
| 1606 | JMP  | 1600H    | C3 | Jump back to 1600H for next input from keyboard.    |
| 1607 | —    | —        | 00 |   |
| 1608 | —    | —        | 16 |   |

This program enables you to test out both the LED port and the keyboard by outputting the binary code from the keyboard to the LEDs. The program complements the accumulator to compensate for the fact that on TRITON the LEDs go on for level "0." In this program they will go on if a bit from the keyboard is "1." Because we are going through the monitor's INCH routine you will find that a shift inversion takes place. You get upper case alpha codes when unshifted and lower case alpha codes when shifted. This is designed in to make the keyboard more convenient to use. Numerical keys are not affected by the shift inversion. Again, because we are using INCH you can escape from this program loop with CONTROL C. You will notice that the most significant LED (bit 8) is permanently off; this is because bit 8 is used for the input strobe and this bit is masked off by the monitor as data is entered. Notice also that the data is latched on to the LEDs after the key has been released.

#### INTERRUPT DEMONSTRATION PROGRAM

|      |      |        |       |    |                                |
|------|------|--------|-------|----|--------------------------------|
| 1618 | LXI  | D      | 161FH | 11 | Load start of string saying    |
| 1619 | —    | —      | —     | 1F | IAM INTERRUPT 3                |
| 161A | —    | —      | —     | 16 |                                |
| 161B | CALL | PSTRNG | CD    |    | Print carriage return followed |
| 161C | —    | —      | 2B    |    | by string.                     |
| 161D | —    | —      | 00    |    |                                |
| 161E | RET  | —      | —     | C9 | Return to main program.        |
| 161F | DATA | I      | —     | 49 | String data starts here and    |
| 1620 | —    | SPACE  | —     | 20 | terminates with end of text    |
| 1621 | —    | A      | —     | 41 | marker 04.                     |
| 1622 | —    | M      | —     | 4D |                                |
| 1623 | —    | SPACE  | —     | 20 |                                |
| 1624 | —    | I      | —     | 49 |                                |
| 1625 | —    | N      | —     | 4E |                                |
| 1626 | —    | T      | —     | 54 |                                |
| 1627 | —    | E      | —     | 45 |                                |
| 1628 | —    | R      | —     | 52 |                                |
| 1629 | —    | R      | —     | 52 |                                |
| 162A | —    | U      | —     | 55 |                                |
| 162B | —    | P      | —     | 50 |                                |
| 162C | —    | T      | —     | 54 |                                |
| 162D | —    | SPACE  | —     | 20 |                                |
| 162E | —    | 3      | —     | 33 |                                |
| 162F | —    | EOT    | —     | 04 |                                |

An example of a user written interrupt routine using INT3 push button. Note that it starts at the re-vectored start address 1618:

Load this program then reinitialise and press INT3 button. Next press W and do a bit of screen typing and press INT3 from time to time. The interrupt should announce its presence. We hope that this simple example will show you that, contrary to popular belief, interrupts are quite easy to write programs for.

#### VIDEO TYPEWRITER PROGRAM

|      |      |        |       |    |   |
|------|------|--------|-------|----|---|
| 1600 | LXI  | D      | 1612H | 11 | Load start address of message string          |
| 1601 | —    | —      | —     | 12 | in DE register pair. This is                  |
| 1602 | —    | —      | —     | 16 | required by PSTRNG sub-routine.               |
| 1603 | CALL | PSTRNG | CD    |    | Call sub-routine which                        |
| 1604 | —    | —      | 2B    |    | prints string starting at address held in DE  |
| 1605 | —    | —      | 00    |    | register pair.                                |
| 1606 | CALL | PCRLF  | CD    |    | Call sub-routine which                        |
| 1607 | —    | —      | 33    |    | prints out carriage return and line feed.     |
| 1608 | —    | —      | 00    |    |   |
| 1609 | CALL | INCH   | CD    |    | Call sub-routine which                        |
| 160A | —    | —      | 0B    |    | inputs data from keyboard and                 |
| 160B | —    | —      | 00    |    | holds this in accumulator.                    |
| 160C | CALL | OUTCH  | CD    |    | Call sub-routine which prints                 |
| 160D | —    | —      | 13    |    | out ASCII character from data in accumulator. |
| 160E | —    | —      | 00    |    |   |
| 160F | JMP  | 1609H  | C3    |    | Jump back to address 1609H                    |
| 1610 | —    | —      | 09    |    | and wait for next character from              |
| 1611 | —    | —      | 16    |    | keyboard                                      |
| 1612 | DATA | 0      | 4F    |    | Start address of message string               |
| 1613 | —    | /      | 2F    |    |   |
| 1614 | —    | K      | 4B    |    |   |
| 1615 | —    | SPACE  | 20    |    |   |
| 1616 | —    | T      | 54    |    |   |
| 1617 | —    | Y      | 59    |    |   |
| 1618 | —    | P      | 50    |    |   |
| 1619 | —    | E      | 45    |    |   |
| 161A | —    | !      | 21    |    |   |
| 161B | —    | EOT    | 04    |    | End of text terminator code.                  |

When you run this program it acknowledges with the message O/K TYPE! and you can then use the TRITON as if it were in the W function operating mode (i.e. it becomes nothing more than a video typewriter). You can escape from the program by depressing CONTROL C (this applies to any program which repeatedly goes through the INCH routine).

#### ALPHABET TWELVE TIMES OVER USING I/O

|      |       |        |    |   |
|------|-------|--------|----|---|
| 1600 | RST1  |        | CF | Clear screen via special re-start instruction                                   |
| 1601 | MVI B | 0CH    | 06 | Set decimal value 12 (oCH) in B to specify                                      |
| 1602 | —     |        | 0C | number of alphabets required.   |
| 1603 | MVI A | 41H    | 3E | Set ASCII code for "A" in accumulator.  |
| 1604 | —     |        | 41 |   |
| 1605 | CALL  | OUTCH  | CD | Print contents of accumulator.  |
| 1606 | —     |        | 13 |   |
| 1607 | —     |        | 00 |   |
| 1608 | INR A |        | 3C | Increment ASCII code in accumulator by one.                                     |
| 1609 | CPI   | 5BH    | FE | Compare it with ASCII code which is   |
| 160A | —     |        | 5B | one greater than Z.   |
| 160B | JNZ   | 1605H  | C2 | If not greater than Z jump back to 1605H  |
| 160C | —     |        | 05 | and repeat until complete   |
| 160D | —     |        | 16 | alphabet is   |
| 160E | CALL  | PCRLF  | CD | printed. If alphabet is completed output carriage return and line feed.         |
| 160F | —     |        | 33 |   |
| 1610 | —     |        | 00 |   |
| 1611 | DCR B |        | 05 | Decrement value in B register by one.   |
| 1612 | JNZ   | 1603H  | C2 | If it is not zero we do not have 12 alphabets so jump back to 1603H and repeat. |
| 1613 | —     |        | 03 |   |
| 1614 | —     |        | 16 |   |
| 1615 | JMP   | REINIT | C3 | If it is zero re-initialise.  |
| 1616 | —     |        | B9 |   |
| 1617 | —     |        | 02 |   |

This program should be compared with the one following as they both do the same thing — print the alphabet twelve times and then re-initialise. This, first, program uses conventional I/O techniques whereas the second makes use of the powerful memory mapped option to the TRITON's VDU. We hope you will recognise the tremendous difference in speed of operation between the two methods. Note that in both programs we make use of the RST1 instruction at the beginning. This is one of 8 special re-start instructions which are fixed destination CALL instructions. Using RST1 will call the sub routine at location 0008H which, in the case of TRITON's MONITOR is then re- vectored with a jump to 0134H. The routine in question is the one which clears the VDU screen and resets the cursor. The advantage of using an RST instruction is that you do not have to specify the address of the sub routine hence saving two bytes in your program. You should only use RST instructions if the sub routine being called terminates in a RETURN command.

When you run the program try and judge the time it takes to display the 12 alphabets and then go on to the next example.

#### ALPHABET TWELVE TIMES OVER USING MEMORY MAPPING

|      |       |     |    |  |
|------|-------|-----|----|--|
| 1600 | RST1  |     | CF | Clear screen with special re-start instruction                     |
| 1601 | LXI H |     | 21 | Load HL register pair with address one less than start of VDU RAM. |
| 1602 | —     |     | FF |  |
| 1603 | —     |     | 0F |  |
| 1604 | MVI B | 0CH | 06 | Set number of alphabets required in register B.                    |

|                  |         |        |    |  |
|------------------|---------|--------|----|--|
| 1605             | —       |        | 0C |  |
| 1606             | MVI A   | 41H    | 3E | Set ASCII code for "A" in accumulator.   |
| 1607             | —       |        | 41 |  |
| 1608             | INX H   |        | 23 | Increment HL register pair by one.   |
| 1609             | MOV M,A |        | 77 | Copy contents of accumulator to memory.  |
| 160A             | INR A   |        | 3C | Increment contents of accumulator.   |
| 160B             | CPI     | 5BH    | FE | Compare contents of accumulator with code  |
| 160C             | —       |        | 5B | one greater than Z.  |
| 160D             | JNZ     | 1608H  | C2 | If it isn't greater than Z jump back to 1608H and repeat.                                      |
| 160E             | —       |        | 08 |  |
| 160F             | —       |        | 16 |  |
| 1610             | MOV A,L |        | 7D | If it is: copy contents of L to accumulator  |
| 1611             | ADI     | 26H    | C6 | Add 26H to this value.   |
| 1612             | —       |        | 26 |  |
| 1613             | CC      | 1629H  | DC | If addition causes a carry; call sub routine which increments H register by one                |
| 1614             | —       |        | 29 |  |
| 1615             | —       |        | 16 |  |
| 1616             | MOV L,A |        | 6F | Replace new low byte address in register L.  |
| 1617             | DCR B   |        | 05 | Decrement register B by one.   |
| 1618             | JNZ     | 1606H  | C2 | If it's not zero we do not have 12 alphabets so jump back to 1606H and repeat.                 |
| 1619             | —       |        | 06 |  |
| 161A             | —       |        | 16 |  |
| 161B             | MVI B   | 0CH    | 06 | Set decimal value 12 into B register.  |
| 161C             | —       |        | 0C |  |
| 161D             | MVI A   | 0AH    | 3E | Set accumulator to ASCII code for line   |
| 161E             | —       |        | 0A | feed.  |
| 161F             | CALL    | OUTCH  | CD | Output line feed to VDU to step cursor down. (to get it clear of last alphabet).               |
| 1620             | —       |        | 13 |  |
| 1621             | —       |        | 00 |  |
| 1622             | DCR B   |        | 05 | Decrement register B by one.   |
| 1623             | JNZ     | 161FH  | C2 | If it's not zero we have not stepped cursor to below the last line of alphabet so jump back to |
| 1624             | —       |        | 1F |  |
| 1625             | —       |        | 16 |  |
| 161FH and repeat |         |        |    |  |
| 1626             | JMP     | REINIT | C3 | If it is; re-initialise.   |
| 1627             | —       |        | B9 |  |
| 1628             | —       |        | 02 |  |
| 1629             | INR H   |        | 24 | Sub-routine to increment register H in event of a carry.                                       |
| 162A             | RET     |        | C9 |  |

Although this program is longer than the one just described you will see an element of similarity in the way the alphabet is formed (by incrementing the accumulator) and we keep track of the number of alphabets in the B register. Instead of using the I/O OUTCH routine we use the HL register pair to point to memory locations which are within the block of the VDU's RAM. This starts at 1000H and finishes at 13FFH. We then use the MOV M, A instruction which copies whatever is in the accumulator to the memory location being addressed by the HL register pair. By using the INX H instruction we can increment the latter to display the next character etc. Notice that carriage returns and line feeds are not needed in the main body of the program because we are using addressing to tell the computer exactly where to place each character. When one alphabet is finished we have to compute the address of the start of the next by adding the hex number 26 to the address currently in the HL register pair (this is done at instruction 1611H). Notice that after this operation we have to make allowances for a carry by calling an INR H sub routine.

When memory mapping the VDU you must remember that the clear screen/reset cursor operations does more than is immediately apparent to the eye. The addresses of different

positions on the VDU screen must correspond to specific places on the screen (1000H is the top left hand corner and 13FFH is the bottom right corner). If, as a result of previous activity, the VDU screen has been scrolling these absolute address values do not correspond to positions in an absolute manner you must carry out a cursor reset operation. This can be on its own or combined with the screen clear operation. A similar operation must be carried out if you use the VDU function when under the control of BASIC L4.1. Note that it takes the VDU 132mS to carry out a home cursor operation so if every you output the raw instruction in your own software you must introduce a time delay greater than this before outputting anything else to the VDU. The Clear Screen/Reset Cursor utility in the monitor has a delay of about 200mS built into it so you can call it without introducing any further delay.

Note that when this program runs the cursor stays stationary in its reset position (top left corner of screen). If we allowed it to stay there the re-initialisation message would overprint our alphabets so we have included some extra instructions (starting

at 161BH) which step the cursor down twelve positions immediately prior to re-initialisation.

To further demonstrate the flexibility of memory mapping you can alter the layout on the screen by altering the value added to the address to get the next line. Alter the data at location 1612H to 29 and re-run the program. The lines should have start points staggered by 3 character positions. Similarly you can alter the start location for the display as a whole by altering the data in locations 1602H and 1603H. Try making these 20 and 10 respectively and alter the data at 1612H to 25. When you run the program the rows should slant the other way.

When memory mapping the VDU you must always be careful to ensure that your memory pointer (HL register pair) cannot exceed the highest address of VDU (13FFH) otherwise you will start over-writing the input buffer and stack area of the monitor. If this happens all sorts of strange things will begin to take place and you will probably find you completely lose control through the keyboard. If this should happen you must resort to the RESET button and end up with a cleared memory!

## MEMORY MAP AND MONITOR UTILITIES

To help those who wish to get involved in machine code programming at an early stage here are the addresses of memory blocks and ports. It is assumed that you will be operating under the control of the standard Monitor program so we also list the addresses of its main Utilities.

### MEMORY START ADDRESSES

|                       |   |
|-----------------------|---|
| 0000H - 03FFH 1K EROM | (Holds standard MONITOR)  |
| 0400H - 07FFH 1K EROM | (Holds BASIC L4.1 "A")  |
| 0800H - 0BFFH 1K EROM | (Holds BASIC L4.1 "B")  |
| 0C00H - 0FFFH 1K EROM | (Spare location)  |
| 1000H - 13FFH 1K RAM  | (VDU memory — can only be written into by computer)   |
| 1400H - 14FFH ¼K RAM  | (Holds stack and tables for Monitor from 1400H to 147FH; 1480H upwards through this block will be used by BASIC L4.1 tables otherwise is free as M/C code work area)  |
| 1500H - 15FFH ¼K RAM  | (Completely reserved for BASIC L4.1 stack otherwise is free for the user)   |
| 1600H - 1FFFH 2½K RAM | (Work area for BASIC L4.1 or user programs. NOTE that locations 1600H and 1601H are made use of by tape I/O routines to store End of File address — hence user programs for saving/loading to and from tape should always start at 1602H) |

2000H - FFFFH 56K.

Available for "Off Board" extensions

### PORT DESIGNATIONS

|           |   |
|-----------|---|
| 00H       | Keyboard INPUT (NOTE special routine is necessary)  |
| 01H       | Tape I/O UART Status INPUT  |
| 02H       | Tape I/O UART Data Strobe (start transmission) OUTPUT   |
| 03H       | LEDs OUTPUT (NOTE LEDs are on for "O")  |
| 04H       | Tape I/O UART Receive Data Enable (receive data) INPUT  |
| 05H       | VDU OUTPUT (NOTE strobe — bit 8 — has to be specially formatted by software)                      |
| 06H       | Spare OUTPUT (NOTE only bits 7 and 8 are output)  |
| 07H       | Relay OUTPUT (NOTE bit 8 is used to drive tape control relay out bit 7 is output as a spare line) |
| 08H - FFH | Available for "Off Board" extensions  |


### MONITOR UTILITIES ETC

|            |   |
|------------|---|
| 0000H RST0 | Reset address. Enables Interrupt and checks and clears memory writing number of bytes available into locations 1481H (low order byte) and 1482 (high order byte). With full main board memory in place this should read 2000H. Then goes on to Initialise computer. |
|------------|---|

|       |        |  |  |
|-------|--------|--|--|
| 0008H | RST1   | Reacts to Interrupt 1 clearing VDU and resetting cursor.   | useful and can save a lot of redundant instructions elsewhere. NOTE you can only guarantee using these if you have MONITOR V4.1 on board!  |
| 000BH | INCH   | A CALL routine which inputs character from keyboard. Stays in keyboard loop until key is depressed.  |  |
| 0010H | RST2   | Reacts to Interrupt 2 clearing VDU and initialising computer without clearing memory. Used for normal reset operation.   | 0053H INIT Destination of Interrupt 2. Clears screen and initialises computer. Also resets stack so should only be used as destination of a JUMP instruction.  |
| 0013H | OUTCH  | A CALL routine which outputs character to VDU.   | 02B9H REINIT This should only be used as a JUMP destination. It resets the stack and re-initialises the computer WITHOUT clearing the screen. A useful instruction at the end of user programs to avoid having to use the HLT instruction. |
| 0018H | RST3   | Reacts to Interrupt 3 and re-vector to 1618H for user routine.   |  |
| 001BH | INDATA | A CALL routine which allows string of characters to be entered to any place in memory. Start location of string pointed to by DE register pair which must be pre-loaded before calling INDATA. Returns on Carriage Return.   | 0327H TPEON When called switches the tape control relay on (relay contacts could be used for other control purposes by the user). NOTE that routine returns with 80H in accumulator.   |
| 0020H | RST4   | Reacts to Interrupt 4 and re-vector to 1620H for user routine.   | 032CH TPEOFF When called switches the tape control relay off. Routine returns with 00H in accumulator.   |
| 0023H | PDATA  | A CALL routine which allows string of characters to be printed from any place in memory. DE register pair must be pre-loaded with start address before calling. Routine returns when it sees EOT terminator (04H) but DE steps to one address beyond terminator allowing immediate re-call for further string to be printed. | 03A1H ACKA Start address of string which prints INVALID. Use should be made of PSTRNG utility to insert Carriage Return and Line Feed.   |
| 0028H | RST5   | Reacts to Interrupt 5 and re-vector to 1628H for user routine.   | 03B5H ACKB Start address of string which prints START=. (Use via PSTRNG).  |
| 002BH | PSTRNG | A CALL routine identical to PDATA except that it outputs Carriage Return/Line Feed prior to printing string.   | 03C4H ACKC Start address of string which prints HEADER=. (Use via PSTRNG)  |
| 0030H | RST6   | Reacts to Interrupt 6 and re-vector to 1630H for user routine.   | 03CFH ACKD Start address of string which prints END. (Use via PSTRNG)  |
| 0033H | PCRLF  | A CALL routine which prints Carriage Return followed by Line Feed and then returns with the original contents of accumulator intact.   | 00AAH BASICIN Checks to see if a key has been depressed on keyboard. If it has it returns with the data otherwise returns immediately with the accumulator cleared and flags set accordingly. Useful for real time interactive programs.   |
| 0038H | RST7   | Reacts to Interrupt 7 and re-vector to 1638H for user routine.   | 010DH DLY When called introduces approximately 3mS time delay and returns with all registers (except flags) intact.  |
|       |        |  | 0116H FIVSEC When called introduces a delay of between 5 and 6 seconds. Returns with registers and flags intact.   |
|       |        |  | 0134H CLRSCN Clears screen and resets cursor. Approximately 200mS time delay is built into this routine. Returns with registers and flags intact.  |

The above are fixed location utilities whereas the following are within the main body of the MONITOR which are liable to be re-located if new generation monitors are written. They are, nonetheless, very

# This Is The Famous

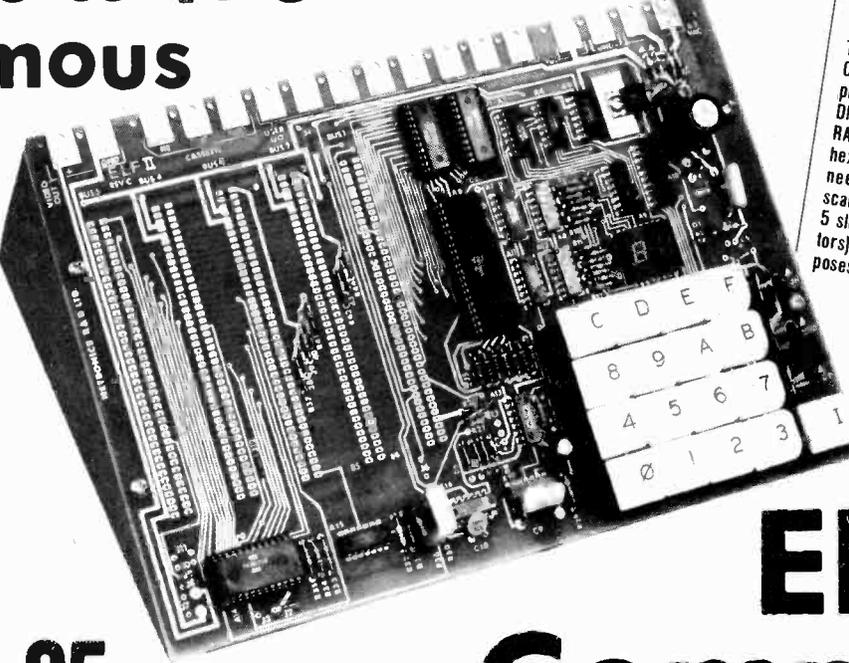

## SPECIFICATIONS

The £99.95 ELF II computer features an RCA COSMAC COS/MOS 1802 8-bit microprocessor addressable to 64k bytes with DMA, interrupt, 16 registers, ALU, 256 byte RAM expandable to 64K bytes, professional hex keyboard fully decoded so there's no need to waste memory with keyboard scanning circuits, built-in power regulator, 5 slot plug-in expansion bus (less connectors), stable crystal clock for timing purposes and a double-sided, plated-through pc board plus RCA 1861 video IC to display any segment of memory on a video monitor or TV screen along with all the logic and support circuitry you need to learn every one of the RCA 1802's capabilities.

# £99.95

PLUS 8% V.A.T.

# ELF 11 Computer

Stop reading about computers and get your hands on one! With ELF 11 and our new Short Course by Tom Pittman, you can master computers in no time at all! ELF II demonstrates all 91 commands an RCA 1802 can execute and the Short Course quickly teaches you how to use each of the 1802's capabilities.

ELF 11's video output lets you display an alphanumeric readout or graphics on any T.V. screen or video monitor and enjoy the latest T.V. games. But that's not all, once you've mastered computer fundamentals ELF 11 can give you POWER with add-ons that are among the most advanced found anywhere. American IEEE chapters plus hundreds of universities and major corporations have chosen the ELF 11 to introduce their students and personnel to microprocessor computing!

Learn The Skill That May Soon Be Far More Important Than Your College Degree!

The ability to use a computer may soon be more important to your earning power than college degree. Without a knowledge of computers you are always at the mercy of others when it comes to solving highly complex business, engineering, industrial and scientific problems. People who understand computers can command MONEY and to get in on the action, you must learn computers. Otherwise you will be left behind.

ELF 11 is the F.A.S.T Way to Learn Computer Fundamentals!

Regardless of how minimal your computer background is now, you can learn to programme a computer in almost no time at all. That's because Netronics has developed a special Short Course on Microprocessor And Computer Programming in non-technical language that leads you through every one of the RCA COSMAC 1802's capabilities so you'll understand everything ELF 11 can do and how to get ELF 11 to do it!

All 91 commands that an 1802 can execute are explained to you, step-by-step. The text, written for Netronics by Tom Pittman, is a tremendous advance over every other programming book in print. Keyed specifically to the ELF 11, it's loaded with "hands on" illustrations. When you're finished, ELF 11 and the 1802 will no longer hold any mysteries for you.

In fact, not only will you be able to use a personal computer creatively, you'll also be able to understand computing articles in the technical press.

If you work with large computers, ELF 11 and our Short Course will help you to understand what makes them tick.

A DYNAMITE PACKAGE FOR JUST £99.95 plus 8% VAT!

With ELF 11, you learn to use machine language — the fundamental language of all computers. Higher level languages such as FORTRAN and BASIC must be translated into machine language before a computer can understand them. With ELF 11 you build a solid foundation in computers so you really know what you're doing, no matter how complicated things get.

Video output also makes ELF 11 unique among computers selling for such a low price. Attached to your T.V. set, ELF 11 becomes a fabulous home entertainment centre. It's capable of providing endless hours of fun for both adults and children of all ages! ELF 11 can create graphics, alphanumeric displays and fantastic video games.

Only a low cost R.F. Modulator is required to connect ELF 11 to your T.V. (To order one see coupon below.)

H. L. Audio, 9b Garmen Road, London N17 0UR

SEND TODAY

### NOW AVAILABLE FOR ELF 11

- Tom Pittman's Short Course on Microprocessor & Computer Programming teaches you just about everything there is to know about ELF 11 or any RCA 1802 computer. Written in non-technical language, it's a learning breakthrough for engineers and laymen alike. £5.00 post paid.
  - Deluxe metal cabinet with plexiglas dust cover for ELF 11. £29.95 plus £1.50 p&p. R.F. modulator for use with T.V. set. £3.00 post paid.
  - GIANT BOARD kit with cassette I/O, RS 232-C/TTY I/O, 8-bit P I/O, decoders for 14 separate I/O instructions and a system monitor/editor. £39.95 plus £1.00 p&p.
  - KLUGE (prototype) BOARD accepts up to 36 IC's £17.00 plus 50p p&p.
  - 4k static RAM kit. Addressable to any 4k page to 64k. £89.95 plus £1.56 p&p.
  - Gold plated 86-pin connectors (one required for each plug-in board). £5.70 post paid.
  - Professional ASC11 Keyboard kit with 128 ASC11 upper/lower case set, 96 printable characters, onboard regulator, parity, logic selection and choice of 4 handshaking signals to mate with almost any computer. £64.95 post paid.
  - Deluxe metal cabinet for ASC11 Keyboard £19.95 plus £1.50 p&p.
  - ELF 11 Tiny BASIC on cassette tape. Commands include SAVE, LOAD, X, =, 0, 26 variables A-Z, LET, IF, THEN, INPUT, PRINT, GO TO, GO SUB, RETURN, END, REM, CLEAR, LIST, RUN, PLOT, PEEK, POKE. Comes fully documented and includes alphanumeric generator required to display alphanumeric characters directly on your T.V. screen without additional hardware. Also plays tick-tack-toe plus a drawing game that uses ELF 11's hex keyboard as a joystick. 4k memory required. £14.95 post paid.
  - Tom Pittman's Short course on Tiny BASIC for ELF 11. £5.00 post paid.
  - Expansion Power Supply (required when adding 4k RAM). £19.95.
  - ELF BUG TM Deluxe System Monitor on cassette tape. Allows displaying the contents of all registers on your T.V. at any point in your programme. Also displays 24 bytes of memory with full addresses, blinking cursor and auto scrolling. A must for the serious programmer! £14.95 post paid.
- COMING SOON: A-D, D-A converter, Light Pen, Controller Board, Colour Graphics & Music System and more!

\*Plus VAT at 8% on price and postage

CALL OR WRITE FOR WIRED PRICES

H. L. AUDIO LTD, DEPT E.T.1  
9b GARMAN ROAD  
LONDON N17 0UR  
(TEL 01-808 6127)  
Sole European Distributors for Netronics  
R&D Ltd U.S.A.

YES! I want to run programmes at home and have enclosed  £109.56 including postage and V.A.T. for RCA COSMAC ELF 11 kit  £5.94 including postage and V.A.T. for power supply (required),  £5.95 including postage and V.A.T. for RCA 1802 Users Manual,  £5.95 including postage and V.A.T. for Short Course On Microprocessor and Computer programming.

I want mine wired and tested with power supply. RCA 1802 Users Manual and Short Course included for just £164.10 including postage and V.A.T.  I am also enclosing payment (including postage and V.A.T.) for the items checked at the left.

Total enclosed


USE YOUR  ACCESS  BARCLAYCARD  
Interbank  
Account No

Signature \_\_\_\_\_ Exp date \_\_\_\_\_  
CREDIT CARD PHONE ORDERS ACCEPTED 01-808 6127  
PRINT  
Name \_\_\_\_\_  
Address \_\_\_\_\_

DEALER ENQUIRIES INVITED

# From Science of Cambridge: the new MK 14.

**only  
£39.95  
(+8% VAT)**

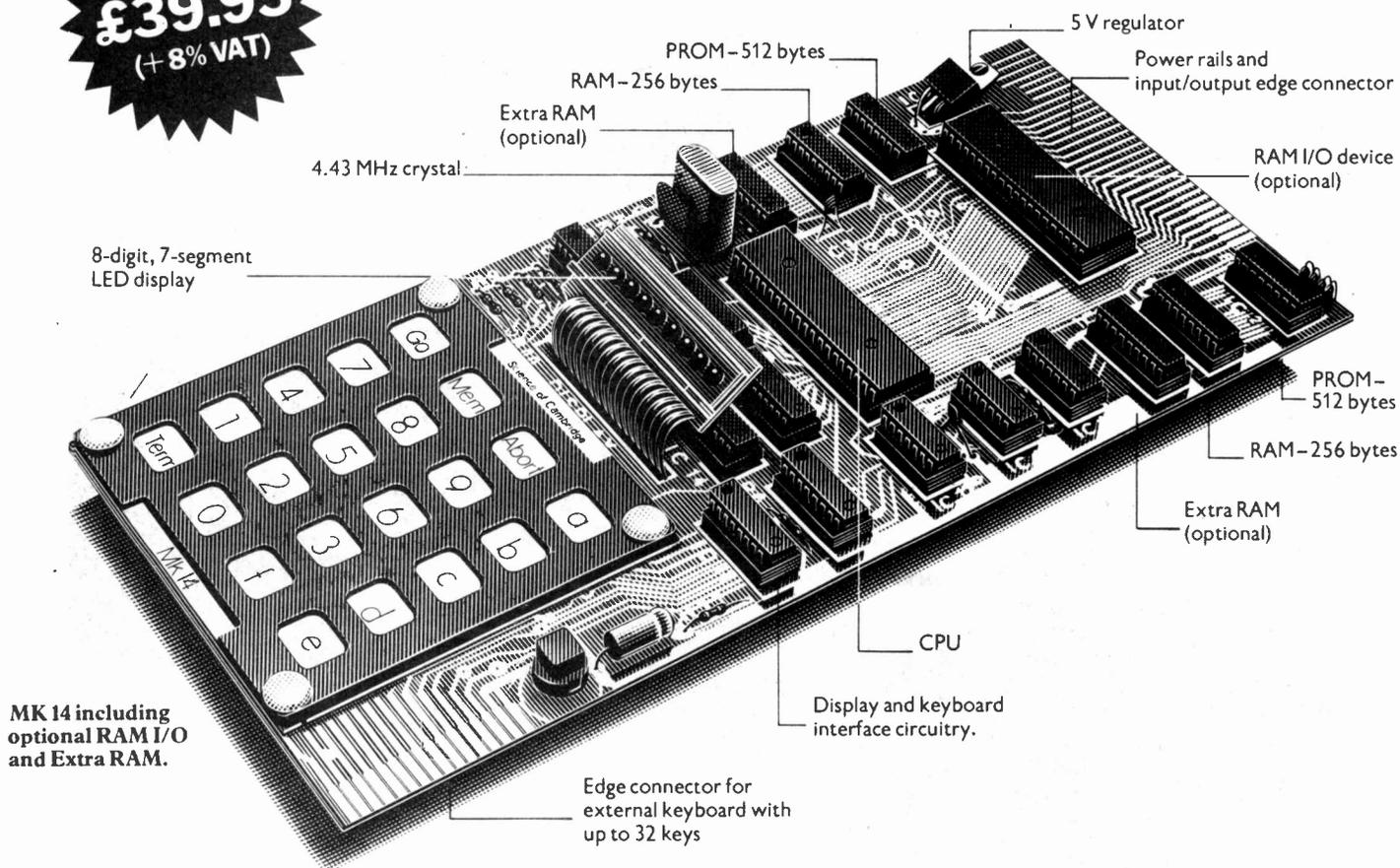

**MK 14 including optional RAM I/O and Extra RAM.**

## **MK 14 — a complete computer for £39.95 (+8% VAT)**

The MK 14 is a complete microcomputer with a keyboard, a display, 8 x 512-byte pre-programmed PROMs, and a 256-byte RAM programmable through the keyboard.

As such the MK 14 can handle dozens of user-written programs through the hexadecimal keyboard. (20 sample programs are provided in the Manual — which also contains comprehensive building instructions, and instructions on program-writing.)

Yet in kit form (which can be assembled by any fairly experienced kit-builder), the MK 14 costs only £39.95 (+£3.20 VAT, and p&p).

### **But that's only the start . . .**

The memory capacity of the basic kit is surprisingly powerful — but every computer owner, from a schoolboy to a multi-national corporation, soon feels the need for more memory.

With the MK14, it's yours!

Optional extras include an additional 256-byte RAM, and a 16-line external input/output device (allowed for on the PCB) which give a further 128 bytes of RAM.

## **And the next step?**

The next step is to add your own peripherals!

The first could be a low-cost module which provides an **interface with a standard cassette-recorder**. This means you can use ordinary tape-cassettes for the storage of data and programs.

To get the best from this configuration, you could uprate your system with a **revised monitor** — consisting of 2 replacement PROMs, pre-programmed with sub-routines for the interface, offset calculation and single step, and single-operation data entry.

The second peripheral could be your own **PROM programmer and blank PROMs** to set up your own pre-programmed dedicated applications. (Fusible-link device guarantees program safety.)

All are available now to owners of MK 14 — and remember Science of Cambridge keep you up to date *automatically* with advances in the MK 14 range. A TV interface device is already in the pipeline!

## **A valuable tool — and a training aid**

As a computer, it handles operations of all types — from complex games to digital alarm clock functioning, from basic maths to a pulse delay chain. Programs are in the Manual, together with instructions for creating your own genuinely valuable programs.


And, of course, it's a superb education and training aid — providing an ideal introduction to computer technology.

### **SPECIFICATIONS**

#### **MK 14**

- \* Hexadecimal keyboard
- \* 8-digit, 7-segment LED display
- \* 8 x 512 PROM, containing monitor program and interface instructions
- \* 256 bytes of RAM
- \* 4 MHz crystal
- \* 5 V regulator
- \* Single 8 V power supply
- \* Space available for extra 256-byte RAM and 16 port I/O
- Edge connector access to all data lines and I/O ports
- Optional Extras**
- \* Extra RAM — 256 bytes
- \* RAM I/O device
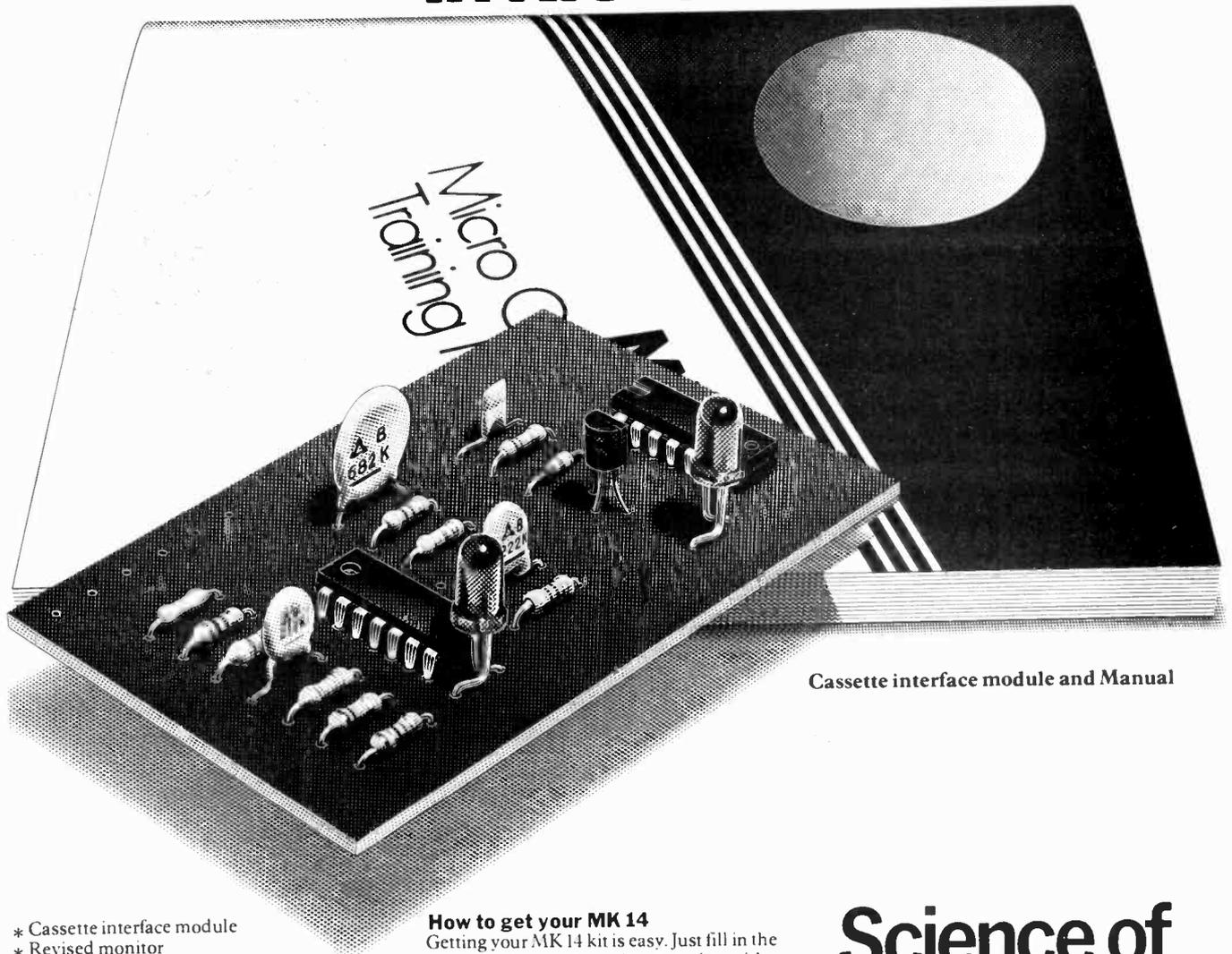
# Simplest, most advanced, most flexible microcomputer -in kit form.



Cassette interface module and Manual

- \* Cassette interface module
- \* Revised monitor
- \* PROM programmer
- \* Blank PROMS

#### Free Manual

Every MK 14 Microcomputer kit includes a Manual which deals with procedures from soldering techniques, through programming and use of RAM I/O to interfacing with complex external equipment. It contains operational instructions and examples for training applications, and numerous programs including math routines (square root, etc), digital alarm clock, single-step, music box, mastermind and moon landing games, self-replication, general purpose sequencing, etc.

#### Designed for fast, easy assembly

Each 31-piece kit includes everything you need to make a full-scale working microprocessor, from 15 chips, a 4-part keyboard, display interface components, to PCB, switch and fixings.

The MK 14 can be assembled by anyone with a fine-tip soldering iron and a few hours' spare time, using the illustrated step-by-step instructions provided.

#### How to get your MK 14

Getting your MK 14 kit is easy. Just fill in the coupon below, and post it to us today, with a cheque or PO made payable to Science of Cambridge. And, of course, it comes to you with a comprehensive guarantee. If for any reason, you're not completely satisfied with your MK 14, return it to us within 14 days for a full cash refund.

## Science of Cambridge

Science of Cambridge Ltd,  
6 Kings Parade, Cambridge, Cambs., CB2 1SN.  
Telephone: Cambridge (0223) 311488

To: Science of Cambridge Ltd, 6 Kings Parade, Cambridge, Cambs., CB2 1SN.

Please send me the following, plus details of other peripherals:

- MK 14 Standard Microcomputer Kit " £43.55 (inc 40p p&p.)
- Extra RAM " £3.88 (inc p&p.)
- RAM I/O device " £8.42 (inc p&p.)

I enclose cheque/money order/PO for £\_\_\_\_\_ (indicate total amount.)

Name \_\_\_\_\_

Address (please print) \_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_


ETI 1

Allow 21 days for delivery.

# ETI BOOK SERVICE
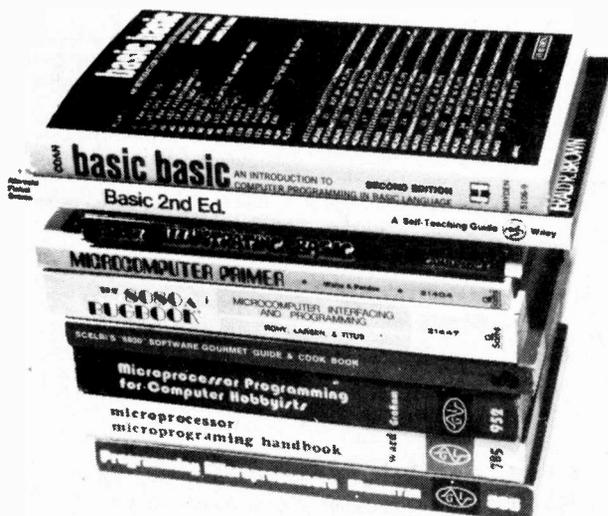
## computing

- BASIC: A Self Teaching Guide (2nd Edition)** £4.50  
by ALBRECHT, R. L.  
Teach yourself the programming language BASIC. You will learn how to use the computer as a tool in home or office and you will need no special maths or science background.
- Illustrating BASIC** £2.20  
by ALCOCK, D.  
This book presents a popular and widely available language called BASIC and explains how to write simple programs.
- Microprocessors** £10.65  
by ALTMAN, L.  
Gives a general overview of the technology design ideas and explains practical applications.
- Applying Microprocessors** £12.00  
by ALTMAN, L.  
Follow up volume which takes you into the second and third generation devices.
- Intro to Microprocessors** £6.00  
by ASPINALL, D.  
Explains the characteristics of the component.
- How to Buy and Use Minicomputers and Microcomputers** £7.50  
by BARDEN, W.  
Discusses these smaller computers and shows how they can be used in a variety of practical and recreational tasks in the home or business.
- How to Program Microcomputers** £6.75  
by BARDEN, W.  
This book explains assembly-language programming of microcomputers based on the Intel 8080, Motorola MC6800, and MOS Technology MCS6502 microprocessors.
- Introduction to Microcomputers and Microprocessors** £7.50  
by BARNA, A.  
Provides the basic knowledge required to understand microprocessor systems. Presents a fundamental discussion of many topics in both hardware and software.
- Microprocessors in Instruments and Control** £11.80  
by BIBBERO, R. J.  
Introduces the background elements, paying particular regard to the dynamics and computational instrumentation required to accomplish real-time data processing tasks.
- Basic BASIC** £7.50  
by COAN, J. S.  
An introduction to computer programming in BASIC language.
- Microprocessor Programming for Computer Hobbyists** £7.00  
by GRAHAM, N.
- The Computer Book** £6.20  
by HAVILAND, R. P.  
Building super calculators and minicomputer hardware with calculator chips.
- Microcomputers, Microprocessors, Hardware Software and Applications** £14.25  
by HILBURN, J. L.  
Complete and practical introduction to the design, programming, operation, uses, and maintenance of modern microprocessors, their integrated circuits and other components.
- Microprocessor Systems Design** £14.35  
by KLINGMAN, E.  
Outstanding for its information on real microprocessors, this text is both an introduction and a detailed information source treating over a dozen processors, including new third generation devices. No prior knowledge of microprocessors or microelectronics is required of the reader.
- BASIC Programming** £6.10  
by KEMENY, J. G.  
A basic text.
- Microprocessor and Small Digital Computer Systems for Engineers and Scientists** £19.00  
by KORN, G. A.  
This book covers the types, languages, design, software and applications of microprocessors.
- TV Typewriter Cookbook** £7.40  
by LANCASTER, D.  
An in-depth coverage of tv typewriters (tvts)—the only truly low-cost microcomputer and small-system display interface. Covers tvt terminology, principles of operation, tv configurations, memories, system design, cursor and update circuitry and techniques, hard copy, color graphics, and keyboards and encoders.
- Microprocessors — Technology, Architecture, and Applications** £8.00  
by MCGLYNN, D. R.  
This introduction to the "computer-on-a-chip" provides a clear explanation of this important new device. It describes the computer elements and electronic semiconductor technologies that characterize microprocessors.
- Programming Microprocessors** £5.50  
by MCMURRAN  
A practical programming guide that includes architecture, arithmetic/logic operations, fixed and floating-point computations, data exchange with peripheral devices/compilers and other programming aids.
- Microcomputer Based Design** £19.00  
by PEATMAN, J. B.  
This book is intended for undergraduate courses on microprocessors.
- Microprocessor and Microprocessor Systems** £20.50  
by RAO, G. U.  
A completely up-to-date report on the state of the art of microprocessors and microcomputers, written by one of the leading experts. It thoroughly analyzes currently available equipment, including associated large scale integration hardware and firmware.
- The 8080A Bugbook: Microcomputer Interfacing and Programming** £7.60  
by RONY, P. H.  
The principles, concepts and applications of an 8-bit microcomputer based on the 8080 microprocessor IC chip. The emphasis is on the computer as a controller.
- 6800 Software Gourmet Guide and Cookbook** £7.80  
by SCELBI
- 8080 Software Gourmet Guide and Cookbook** £7.80  
by SCELBI
- Understanding Microcomputers** £7.60  
Gives the fundamental concepts of virtually all microcomputers  
by SCELBI
- Microprocessors and Microcomputers** £18.00  
by SOUCEK, B.  
Here's a description of the application, programming, and interfacing techniques common to all microprocessors. It concentrates on detailed descriptions of representative microprocessor families and includes explanations of digital codes, logical systems, and microcomputer organization.
- Microcomputer Primer** £6.25  
by WAITE, M.  
Introduces the beginner to the basic principles of the microcomputers. Discusses the five main parts of a computer — central processing unit, memory, input/output interfaces, and programs. The important characteristics of several well-known microprocessors are given and a chapter is included on programming your own microcomputer.
- Microprocessor/Microprogramming Handbook** £6.00  
by WARD  
Authoritative practical guide to microprocessor construction, programming and applications.



**HOW TO ORDER:**  
Make cheques etc payable to ETI Book Service.  
Payment in sterling only please. Orders should be sent to: ETI Book Service, PO Box 79, Maidenhead, Berks.  
All prices include P & P.

# Softspot

Don Scales has written another game for the TRITON. We would like to expand Softspot over the next few months so please send us any software (machine code, BASIC etc.) which you feel would be of interest to others.

## REVERSAL (1K) DESCRIPTION

The REVERSAL GAME is a game of skill played with the computer. The computer will arrange the numbers 1 to 9 in a random sequence and your job is to arrange them into ascending order in the minimum number of moves.

For example

The machine might print the following sequence –  
8 3 7 9 1 4 2 6 5

You now have to get these arranged in ascending order. To do this, you are allowed to reverse the order of any number of digits starting at the left hand side. The machine will ask

### NUMBER TO REVERSE

If you enter 4 the result will be

9 7 3 8 1 4 2 6 5


If you now enter 9 you will get

5 6 2 4 1 8 3 7 9

You now have 9 in the correct place and can set about getting 8 7 6 etc. in their correct positions.

```

10 PRINT 'THE REVERSAL GAME'
20 FOR I=1 TO 9
30 LET A=RND(9)
40 IF I=1 GOTO 80
50 FOR J=1 TO I-1
60 IF @(J)=A GOTO 30
70 NEXT J
80 LET @(I)=A
90 NEXT I
95 LET B=0
200 PRINT #2, @(1), @(2), @(3), @(4), @(5), @(6), @(7), @(8), @(9)
210 INPUT 'NUMBER TO REVERSE' J
220 IF J<1 GOTO 240
230 IF J<10 GOTO 260
240 PRINT 'INVALID - TRY AGAIN'
250 GOTO 210
260 LET K=(J+1)/2
270 FOR I=1 TO K
280 LET A=@(I), @(I)=@(J+1-I), @(J+1-I)=A
290 NEXT I
295 LET B=B+1
300 FOR I=1 TO 9
310 IF @(I) # I GOTO 200
320 NEXT I
330 PRINT 'TOTAL', #3,B
340 GOTO 10
    
```

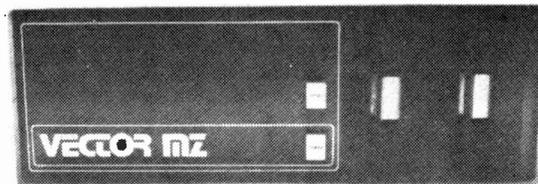

## THE TOTAL SOLUTION FROM ALMARC OF COURSE!

Now Almarc & Vector Graphic offer the complete solution to your computing needs for £2300.00\*. The Vector MZ needs only the addition of a V.D.U. and it's ready to go. Completely assembled and fully tested, the Vector MZ offers the following features as standard:—

- S-100 bus
- 4 MHz Z80A processor
- 158 instructions
- Two quad density Micropolis floppies — over 630k bytes on line
- Serial port
- Two parallel ports
- 32K static ram
- 12K prom/ram board with extended monitor
- Extended disc Basic

Simply connect your peripherals (Elbit V.D.U.s & Centronics printers are available from Almarc) and you're up and running and, because the MZ uses the S-100 bus, you can plug in a massive range of add-on units.

Ring or write for a demonstration to:—

### ALMARC DATA SYSTEMS LTD.

29 Chesterfield Drive  
Burton Joyce, Nottingham  
Tel: 0602 248565

\*Discount terms available

## MEMORY EXPANSION FOR NASCOM I

|                       |         |
|-----------------------|---------|
| 16K ready built ..... | £180.00 |
| 32K ready built ..... | £290.00 |
| 48K ready built ..... | £400.00 |

The above prices include all buffers and address decoding.

Due to limited quantity the above are available to callers only.

### KITS

|                                     |         |
|-------------------------------------|---------|
| Nascom 1 Microcomputer kit .....    | £197.50 |
| Jade Z80 CPU kit 2Mhz .....         | £95.00  |
| 13 slot S100 motherboard .....      | £48.50  |
| Jade 8K static memory 250ns .....   | £119.95 |
| KB756 Keyboard kit .....            | £45.00  |
| Mini disc drive (ready built) ..... | £200.00 |
| Kansas City interface .....         | £18.95  |

### I.C.s

|                               |         |                |         |
|-------------------------------|---------|----------------|---------|
| Z80 CPU .....                 | £13.00. | 8X 21L02 ..... | £7.90   |
| 4116 16K dynamic, 8 OFF ..... |         |                | £100.00 |
| 5270 4K dynamic, 8 Off .....  |         |                | £25.00  |
| 2107 4K dynamic 8 Off .....   |         |                | £25.00  |

Please add 40p postage then 8% VAT

**V & T ELECTRONICS**  
82 CHESTER ROAD, LONDON, N19

# Personal Computing — The Early Years

Tip toe through the early memories of the Personal Computing field

## In The Beginning

It all started back in 1974 when Intel introduced the 4004, the first true microprocessor. It developed almost by accident, as a result of Intel's efforts to produce a calculator of unprecedented flexibility. The shock waves of the hand-held calculator revolution were still being felt by every section of society and the back-room boys' eyes lit up with that "You ain't seen nothing yet" look as they drew up the chip-masks for their next product, the 8-bit 8008.

Assisted by the lessons learned from the cut-throat calculator business the microprocessor developed with frightening speed and predictability. Frightening not only because of the vast amount of high-technology and high finance poured into the field, but also because of the dramatic effect extrapolations of such technology can have on a broad spectrum of society. Predictable because everyone knew what was going to develop. The shrinking of calculators from giant cabinets to flip-top packs in the space of just a few years created an extraordinary blase attitude towards electronics. It was a spectacular demonstration of the omnipotence of the new technology of micro-electronics. It was proof that now nothing is impossible — just draw up the specifications, expend x thousand man-hours and y million dollars, and there you have it. So the microprocessor has been born at a time when nothing comes as a surprise any more. But maybe the real surprise is yet to come.

## The New "Hams"

Of all the sub-sets of electronics hobbyists the most clearly defined to date has been the radio amateur. Members of this particular sect follow a technological faith which started with the first wireless communication and has since flourished, gaining millions of followers in a relatively short time.

For many hams their hobby almost becomes a life-style within itself, always striving for that rare DX the eternal pursuit of that elusive one-to-one SWR. Is it possible that we are now witnessing the founding of a new faith, one whose god speaks in 1s and 0s rather than 5s and 9s?

By making a few comparisons between amateur radio and amateur computing certain patterns can be seen emerging which may be an indication of what course the future of personal computing might take.

## Power To The People

Like amateur radio, amateur computing is a high-technology which makes the latest developments in the science of electronics available to anyone at all who has the time and money to pursue them. The money factor is all important — the lower the cost of the hardware, the more people can afford to pursue the hobby. A reasonably useful microcomputer system might cost in the order of \$1,000. Hams might spend this sort of money on radio gear, for that matter a radio-controlled aircraft enthusiast, amateur photographer or stamp-collector could easily spend that much on his hobby. So thanks to the microprocessor the cost of your own personal computer is no longer a barrier to most people.

This new accessibility and the free interchange of ideas and information between hobbyists has the effect of distributing "computer power" over a broad spectrum of people. This leads to a breaking down of much of the mystique which has traditionally surrounded the world of computers; they are being de-mystified as the magic is systematically exposed as little more than sleight of hand. As large number of amateurs invade a hitherto sacred field which was once the sole province of a privileged few the elite will inevitably grow in number until it finally becomes plebian.

## "Homebrew" vs "Appliance"

As with amateur radio there are two factions within the computer cult, the "homebrewer" who builds his own equipment for the sake of the experience gained, and the "appliance operator" who buys a ready-built, going unit and gets what he wants from operating his instrument, writing programs and experimenting with the performance of the hardware as bought. His investment in the computer itself is more financial and less emotional than in the case of the homebrewer.

There is always some overlap between the two factions, but they can usually be classified by comparing the time spent building, testing and modifying the hardware to the time spent actually using it once it's working.

### The Sky's The Limit

Radio equipment has rather unique and interesting characteristics. It can never really be declared "finished". There is always more to add to the station, improvements to be made, better antennas, higher power, lower noise. Computers share this trait which makes them too the ideal subject for a hobby. Today's mass storage is tomorrow's scratch-pad. There is unlimited scope for improvement and expansion of the hardware.

If ever the computer itself should look like having its full complement of RAM, ROM, AND I/O parts, the hobbyist can turn his attention to the vast range of peripherals that are available to him. A radio transmitter can be hooked up to an antenna and a microphone and that's about it, but nothing can be so insular as to resist interfacing to a computer if the intrepid hobbyist uses a little imagination.

More importantly, once the computer is operative a literally infinite amount of software development waits to be done. Like radio operating, this phase of the hobby is particularly attractive because the operating cost is nothing more than the electricity bill.

### The Junk Box

Ever since the tradition of stripping a discarded radio chassis was established by the pioneers of amateur radio, the humble junk box has been the hallmark of the truly worthy hobbyist. In much the same way as one may judge someone's social standing by the way he dresses, how neatly his garden is kept, radio amateurs assess each other's status by the quality and quantity of a bits and pieces which lurk for years in the dark recesses of their junk box until their true worth is finally recognised and they are discarded. Because the microcomputer hobby is so new, junk box computer parts of good vintage are rarer, but there is always the stimulating challenge of pushing a seemingly irredeemable piece of obsolete equipment into service. Radio ham and computer hobbyist alike share the unique pride and joy of operating equipment which the professionals have officially declared worthless.

### Doing The Impossible

Besides the resurrection of dead equipment, hams are keen on performing another type of miracle. This involves proving by practical demonstration that something which should by rights not be possible does, in fact, work. With amateur radio this usually entails forging forth into extremes of technology (or bad practice, depending on how you look at it), generally revolving around a successful communication in spite of a red-hot "final", vast distances or an antenna made of wet string.

To the computer ham comparable feats entail successful execution of programs which are either

exceptionally short or unbelievably long or so cunningly convoluted that not even the person who wrote it knows how it works. Thanks to the new technology involved there is also a whole new set of miracles which rely on getting a phenomenal number of logic functions into an incredible small space.

Amateurs are in a rather unique position in that they are permitted to exceed manufacturers' ratings to see to what limits they can push a particular component or piece of equipment. This practice gave rise to many novel techniques in the field of radio and a similar thing is bound to happen in computing.



The software bugs seem to come out just before sunrise.

### Time Is Not Money

Amateurs make many other contributions to the science to which they are devoted as a result of the enormous amount of time they spend on their hobby. Because of the non-commercial nature of their pursuits, computer hobbyists can afford to undertake time-consuming projects which would not be economical as a professional enterprise.

Like the radio amateur who stays awake all night tuning across the bands looking for a rare contact, the computer ham often burns the midnight oil chasing an elusive bug in his software. Radio propagation never seems to be optimum at a civilized hour; similarly the software bugs only seem to come out just before sunrise.

With both amateur radio and amateur computing the real fun of the hobby lies in setting a goal and then achieving it no matter how long it takes or how inefficient the techniques used may be. The computer ham may devote hundreds of hours to developing a program that does nothing more than play a seemingly useless game. But, as with any technical hobby, a lot of valuable techniques are learned in the process.

### Spreading The Word

A natural development from any widely followed hobby is the formation of clubs where people with similar interests can meet and exchange ideas. Major amateur radio clubs like the Radio Society of Great Britain, the Amateur Radio Relay League and the Wireless Institute of Australia have been established for many years and cater for hundreds of thousands of enthusiasts.

Even though the do-it-yourself computer hobby is

# - The Early Years

so young there are already hundreds of computer hobby clubs. The biggest of these are found on the west coast of America which is where most of the world's microprocessor products originate. The Southern California Computing Society has about 5,000 members. At the moment there are nearly 200 smaller computer clubs in the USA and an estimated 20,000 people have their own personal computer.

Magazines devoted entirely to the computer hobbyist have been established with great success. The most widely read glossy is *byte* which now circulates over 60,000 copies.

The radio amateurs' "field day" has always provided a means of information exchange between individuals. As communication is the basis of ham radio, publicising such events poses no problems, but computer hams have only their specialist magazines for such promotion. A few conventions have been held by computer hobbyists where the main purpose has been to establish standards so that hobbyists can easily share the software they have developed. Manufacturers of personal computing hardware also take an interest in these gatherings because it is an excellent opportunity to find out what the hobbyist is interested in and therefore which products will sell.

## Speaking of Computers

Due to the unusually verbal nature of the hobby itself, radio amateurs have developed a unique vocabulary. The language which results has such a high jargon content and is spoken so fluently that it is quite unintelligible to the outsider. This serves to give the group its own identity and binds its members together.

Although amateur computing is still in its infancy its followers found that the computer industry had already provided them with a highly developed jargon, complete with an impressive range of off-the-shelf, buzzwords which have been nurtured to perfection by 20 years of professional verbal dazzling. This they have eagerly seized and followers now have a language of their own.

The most telling sign of both radio and computer hams is their often amusing ability to construct seemingly meaningful sentences using all the rules of English grammar except that the keywords are replaced with strings of number of initials. The radio amateur might say, "QRX, I've got to check my SWR", while the computer amateur could hit you with, "I've put a PIA on my 6800 for I/O."

To the uninitiated talking in code like this seems like an awfully anti-social way of passing secret messages between club members — it serves to keep the in-group "in" by providing a feeling of comradeship for members and it keeps out all but the most determined newcomers.

## Future Shock (Electric)

Although personal computing is already well established as a hobby, the real impact of its advent is yet to come.

It is a characteristic of any hobby that those who pursue it develop great expertise in the field. A keen 10 year old stamp collector may know as much about stamps as a professional stamp dealer. Having spent his youth building radio transmitters a ham of 20 might know as much about radio as a University-qualified electronic engineer.

We are now finding a new breed of hobbyist/expert, a hobbyist who has spent thousands of hours of leisure time building computers and programming them. He could well know more about computers than many professionals in the field. As the hobby grows there will be more and more people to whom computers are second nature, people who are fully conversant with a broad range of computer concepts and totally up-to-date with the state of the art.

Traditional training and qualifications are already being seriously challenged by these hobbyists who might enroll in a University computer science course already knowing more than they will be taught.

As this flood of expertise hits the workforce we are bound to see dramatic changes in the status of the computer professional. Will there be a sudden surplus of computer engineers and programmers, or will the wave of new technology bring with it expansion of the industry to absorb it?

The remarkable advances in solid state technology which led to the development of microprocessors have made their mark on the electronics industry, but it's the "expertise explosion" which will follow that will have the real impact on society.



There are rumours of an Opto-Pneumatic Power Cue being evaluated by leading players. Integral Laser Theodolite system determines range and angles while Microprocessor backpack computes and controls shot dynamics.

# MICRODIGITAL OF MERSEYSIDE

## SUPER SPECIAL PRE CHRISTMAS OFFERS!

**CHESS CHALLENGER** £120

(3 level) R.R.P. £140 ONLY  
Also in stock 10 level £200, BORIS £199

**TOSHIBA LC-836 MN Calculator**

30 memories - Alphanumeric LCD memories retained when calculator switched off, 12,000 hour battery life — 25% off R.R.P. **£49**

**COMPUTER BATTLESHIPS**

The Seek and Destroy Computer game with live action and sound. **£29.95**

**Optima 600 T.V. Game** £49.95  
ONLY

### WE ALSO SELL

Science of Cambridge  
MK 14  
Bearbags  
Nascom  
Rockwell AIM-65  
Apple II  
North Star Horizon  
CASU  
Panda

Chroma Chimes  
Monitel  
Chess/Draughts/  
Backgammon  
A superb selection of literature  
TI Programmer Calculator  
Multimeters (Digital),  
Soldering Equipment, Wire  
Wrap, etc. and much more

Demonstrators of most of these on display

Opening hours: 9-5.30 Monday  
to Saturday

Friendly, expert staff always on hand!

## MICRODIGITAL LTD.



25 BRUNSWICK STREET  
LIVERPOOL L2 0BJ

Tel: 051-236 0707

### This Month's Special Postal Offers:

Improve the video output of your Nascom I UM1111 E36 UHF Modulator with fitting instructions. **£4.00**

Give your Nascom I keyboard the bleep! Full kit with instructions. **£3.00**

10 quality C15 cassettes with library cases and special labels. **£4.75**

Science of Cambridge Socket Set 5 x 14 pin, 7 x 16 pin, 4 x 18 pin, 2 x 40 pin **£3.89**

Science of Cambridge power supply. **£5.75**

Universal microprocessor coding forms, pads, 100 sheets each. **£2.38**

*Above offers include V.A.T. and P. & P.*

Please send me the items ticked above. I enclose cheque/P.O. for ..... or

Access No. ....  
Barclaycard No. ....

Please send me free, complete brochure. I enclose S.A.E. (please tick)

Name.....  
Address.....

..... Tel. No.....  
Address to Microdigital Ltd., 25  
Brunswick Street, Liverpool L2 0BJ  
Telephone: 051-236 0707.

Please allow 14 days for delivery.

# ENTERPRISES

Room ETI/J  
313 Kingston Road, Ilford  
Essex IG1 1PJ, England

**From Adam Osborne Associates**  
**INTRODUCTION TO MICROCOMPUTERS**

|  |             |
|--|-------------|
| Volume 0: The Beginners Book                         | £5.95       |
| Volume 1: Basic Concepts                             | £5.95       |
| Volume 2: Some Real Microprocessors (without binder) | £18.95*     |
| Volume 3: Some Real Support Devices (without binder) | £11.95*     |
| Updating Subscriptions for Vol 2 and 3               | £18.95      |
| Updating subscriptions for Vol 2 and 3               | each £30.00 |
| 6800 Programming for Logic Design                    | £5.95       |
| 8080 Programming for Logic Design                    | £5.95       |
| Z80 Programming for Logic Design                     | £5.95       |
| 8080A/8085 Assembly Language Programming             | £6.95       |
| 6800 Assembler Language Programming                  | £6.95       |
| Some Common BASIC Programs                           | £5.95       |
| General Ledger (available from late summer 1978)     | £10.95      |
| Payroll with Costing Accounting                      | £10.95      |
| Accounts Payable & Accounts Receivable               | £10.95      |

**From Basic Software Library**  
(from Scientific Research Instruments)

|  |        |
|--|--------|
| Vol 1 Business and Personal Booking Programs   | £17.50 |
| Vol 2 Maths and Engineering Programs           | £17.50 |
| Vol 3 Advanced Business Programs               | £26.95 |
| Vol 4 General Purpose Programs                 | £7.95  |
| Vol 5 Experimenters Programs (General Purpose) | £7.95  |
| Vol 6 General Ledger Program                   | £32.50 |
| Vol 7 Professional Programs                    | £26.95 |

**From Kilobaud/73 Magazine Inc.**

|                          |       |
|--------------------------|-------|
| Hobby Computers Are Here | £3.95 |
| New Hobby Computers      | £3.95 |

|   |       |
|---|-------|
| TV Typewriter Cookbook by Don Lancaster | £7.50 |
| TTL Cookbook                            | £7.50 |
| CMOS Cookbook                           | £7.95 |
| IC Timer Cookbook                       | £7.50 |
| IC OP-AMP Cookbook                      | £9.50 |
| RTL Cookbook                            | £4.25 |
| Z80 Microprocessor Handbook             | £7.50 |

**Magazines: Back Issues**

|                         |       |
|-------------------------|-------|
| Personal Computing      | £1.75 |
| Interface Age           | £2.25 |
| Dr. Dobbs Journal       | £1.75 |
| Computer Music Journal  | £2.50 |
| Peoples Computers       | £1.75 |
| BYTE                    | £2.25 |
| Creative Computing      | £1.75 |
| Calculators & Computers | £1.75 |
| ROM                     | £1.75 |
| Kilobaud                | £2.25 |
| 73                      | £2.25 |
| Micro-6502 Journal      | £1.50 |

## HOW TO ORDER

Please note our prices include postage and packing, but not insurance, if wanted add 12p for every £10 of books ordered. Make cheques, POs etc. payable to —

**L.P. Enterprises.**  
CREDIT CARDS accepted  
BARCLAYCARD VISA / ACCESS  
DINERS CLUB / AMERICAN EXPRESS

Phone 01-553 1001 for Credit Card orders (24-hr service)

Send to address above  
Indicate Payment Method

All Orders must be Prepaid  
Total enclosed £ .....

..... My cheque, P.O., I.M.O. is enclosed in **Sterling on U.K. Bank**

..... Charge to Barclaycard / Visa / Access / Diners / American Express

Credit Card No. .... Expiry Date .....

Name .....

Address .....

POSTCODE .....

Signature .....

All publications are published in U.S.A. and shipped air-freight by **L.P. Enterprises.** In unusual cases, processing may exceed 30 days.  
\*At time of going to Press, price of binders unknown. Telephone enquiries welcome

**TRADE ENQUIRIES WELCOME**

## From BYTE Publications Inc.

Paperbytes

|   |       |
|---|-------|
| Tiny Assembler for 6800 Systems                   | £5.75 |
| Bar Code Loader for 6800, 8080, Z80 & 6502 Micros | £1.75 |
| Best of BYTE Volume 1                             | £8.95 |

## From Scelbi Computer Consulting Inc.

|   |        |
|---|--------|
| 6800 Software Gourmet Guide & Cookbook                | £7.95  |
| 8080 Software Gourmet Guide & Cookbook                | £7.95  |
| 8080 Programmers Pocket Guide                         | £2.25  |
| 8080 Hex Code Card                                    | £2.25  |
| 8080 Octal Code Card                                  | £2.25  |
| 8080 Guide and One 8080 Code Card                     | £4.20  |
| 8080 Guide and Both Code Cards                        | £6.00  |
| Understanding Microcomputers & Small Computer Systems | £7.95  |
| SCELBI 'BYTE' Primer                                  | £9.95  |
| 8080 Standard Monitor (In Book Format)                | £9.95  |
| 8080 Standard Assembler (In Book Format)              | £15.95 |
| 8080 Standard Editor (In Book Format)                 | £9.95  |
| 8080 Galaxy Game                                      | £7.95  |

## From Creative Computing Press:

|                                     |       |
|-------------------------------------|-------|
| Best of Creative Computing Volume 1 | £6.95 |
| Best of Creative Computing Volume 2 | £6.95 |
| Basic Computer Games                | £5.50 |
| The Colossal Computer Cartoon Book  | £3.95 |
| Computer-Rage (a Board Game)        | £6.95 |
| Artist and Computer                 | £3.95 |

|   |       |
|---|-------|
| Sybox Introduction to Personal & Business Computing     | £4.95 |
| Sybox Microprocessors from Chips to Systems by R. Zacs  | £7.95 |
| Sybox Microprocessors Interfacing Techniques by R. Zacs | £7.95 |
| Dilithium Home Computers Volume 1. Hardware             | £6.50 |
| Dilithium Home Computers Volume 2. Software             | £5.95 |
| Getting involved with your Own Computer                 | £4.75 |
| Best of MICRO   | £6.95 |

## From Dymax Inc.

|  |       |
|--|-------|
| Instant BASIC by Jerald R. Brown                           | £7.95 |
| Your Home Computer by James White                          | £7.95 |
| My Computer Like Me . . . When I Speak                     |       |
| BASIC by Bob Albrecht                                      | £2.75 |
| Games with a Pocket Calculator by Thiagarajan & Stilovitch | £1.75 |
| Games, Tricks and Puzzles for a Hand Calculator by W. Judd | £2.49 |

## From Peoples Computer Company

|  |        |
|--|--------|
| Reference Books of Personal & Home Computing | £4.95  |
| What to Do After You Hit Return              | £7.00  |
| Dr. Dobbs Journal Volume 1                   | £10.00 |

## Subscriptions start within 3 weeks

|   | UK Price | Overseas Price |
|---|----------|----------------|
| <b>MAGAZINES: Subscriptions</b>               |          |                |
| Personal Computing (Twelve Issues Yearly)     | £16.00   | £17.00         |
| Interface Age (Twelve Issues Yearly)          | £20.00   | £20.50         |
| Dr. Dobbs Journal (Ten Issues Yearly)         | £13.00   | £13.50         |
| Computer Music Journal (Four Issues Yearly)   | £8.50    | £9.00          |
| Peoples Computers (Six Issues Yearly)         | £8.00    | £8.50          |
| Kilobaud (Twelve Issues Yearly)               | £20.00   | £21.00         |
| Creative Computing (Twelve Issues Yearly)     | £16.00   | £16.50         |
| Calculators & Computers (Seven Issues Yearly) | £10.00   | £10.50         |
| 73 (Twelve Issues Yearly)                     | £20.00   | £21.00         |
| BYTE (Twelve Issues Yearly)                   | £21.00   | £21.00         |
| Micro-6502 Journal                            | £7.50    | £8.50          |
| Magazine Storage Box (Holds 12 minimum)       | £1.25    |                |

# TRS-80 Update

The August issue of ETI carried a review of the Tandy's TRS-80. The machine, made available for review, was equipped with the Tandy Level 1 floating point 'Tiny BASIC' ROM and 4K of dynamic RAM.

Since then Tandy have introduced a number of developments on the BASIC TRS-80 machine — The Level 1 system was made available with 16K of memory and the more powerful Tandy Level 2 BASIC was introduced into this country supported by both 4K and, top of the range, 16K of dynamic RAM. Any machine from the range can be upgraded in performance by returning it to Tandy for internal mods.

This update to the original review deals with the major differences between machines equipped with the Level 1 and Level 2 BASICs. For a general description of the TRS-80 machine, the comments of the original review are still valid.

## Key Improvement

The level 2 BASIC is a 12K version of the microsoft BASIC used by many machines in the TRS-80's price bracket. Before going on to describe the Level 2 BASIC, which is considerably more powerful than Level 1, in detail, it may be as well to mention two hardware orientated improvements implemented on this upgraded machine.

The TRS-80's keyboard is decoded by the resident software and in the Level 1 machine the decoding system used meant that one had to release one key before the computer would allow the entry of another. This led to such messages as "Plase tye in yor name" — Even those of us who are not touch typists could get up enough speed to defeat the Level 1 keyboard. Level 2 lets you hit the second key before you have released the first key. Even level 2 does not let you get away with too much, however, and if you hold down three or four keys at a time, some keys will then generate several characters as they are pressed.

The other major area of improvement on the hardware/software border is the speed at which programs are dumped to and loaded from the TRS-80's cassette recorder.

Level 1 used a data transfer rate of 250 baud — the level 2 rate is twice this at 500 baud. Because of this faster transfer rate it may be found that the volume setting on the recorder that was suitable for use with a Level 1 machine will have to be altered for satisfactory performance with Level 2, in general a lower volume control setting will be needed.

## Editing

One of the major differences between Level 1 and Level 2 is the provision of a powerful editing facility in the latter. We do not have enough space to go into a detailed description of the editor but a few examples of what can be accomplished should give an idea of its power.

One can list any line of a program individually, insert material anywhere in a line, delete material anywhere in a line, delete the remainder of a line beyond the cursor and insert new material in its place. Any desired number of characters to the right of the cursor may be deleted or a change may be made to a

specified number of characters. The editor provides a search facility, so that (for example) a line may be searched for the second occurrence of the letter G and move the cursor to that position or tell the computer to delete all characters to that point and leave the cursor there.

Other editing features allow you to quit the edit saving all changes, to quit deleting all changes or the cancel all changes made and restart.

All in all a very powerful editor.

Level two basic allows variables to be stored in different forms — single or double precision. A # (hash) after a calculation will cause the result to be output as a 16 place decimal (print 1/3 #), an ! (exclamation mark) will keep a variable at single precision (G!) and a % (percent) symbol will keep the number as an interger.

The system of representation can be selected for the type of work required — Tip, if you can work with whole numbers, store them as integers, your program will run twice as fast and occupy half the memory space as programs without these restrictions.

## Print Format

Level 2 BASIC allows some fairly sophisticated formatting of output. It can be used in many applications such as printing report headings, accounting reports etc. Using nine "Field Separators," one can specify digit positions, cause automatic rounding off, concatenate (join together) multiple strings or string variables, align columns — a comprehensive system that allows any output to be presented in an easily readable form.

## Strings

The Level 2 manual states that "Without string handling capabilities, a computer is just a superpowered calculator." What this makes the level 1 machine with its "String Things" — strings which one was not able to handle — is a question we leave open: Needless to say the Level 2 machine provides a wide range of string handling commands.

The DEFSTR statement allows any valid variable name to contain a string, adding a type declaration character (\$) has the same effect.

Each string can contain up to 255 characters and strings can be compared as well as concatenated.

Strings can be compared with the same symbols used for comparing numbers — The ASCII codes for the characters being the values compared.

Level 2 features ASC and CHR\$ commands. ASC gives the ASCII numerical code for a string character while CHR\$ performs the reverse operation.

The INKEY\$ function will allow an entry from the keyboard while a program is running — without the use of the return key, useful for "Real Time" games if nothing else. INKEY\$ will strobe the keyboard and return with a one character string — This being a null string if no key is pressed.

Manipulation of strings can be carried out with the following commands, LEFT\$, MID\$, RIGHT\$, LEN and string\$.

LEFT\$ (A\$, 3) will print the first three characters from the left of A\$ — Thus if A\$ were TANDY the command would select TAN — MID\$ will select characters from the middle of the string and RIGHT\$, not surprisingly, from the right. The formats are the same for LEFT\$.

STRING\$ provides a string of a specified character for a specified character for a specified length. For example STRING\$ (25, ?) would output 25 question marks.

### Trace

Level 2 BASIC provides a trace facility that is very useful for the debugging of programs. The command TRON followed by RUN will output to the screen the exact sequence in which the program lines are executed. To turn off the trace function the command TROFF is used.

### Functions

Level 2 adds considerably to the four in-built arithmetic features of level 1.

To MEM (size of used memory), INT (Convert variable to integer), ABS (absolute value of variable) and RND (Random number generator) are added 12 more.

These are the trig functions SIN, COS, TAN and ATAN — The maths functions EXP, LOG, SGN and SQR.

The command RANDOM at the beginning of a

program will ensure a different series of random numbers each time program is run. CDBL and CSNG concern themselves with the format in which a numerical variable is stored. CDBL provides a double-precision value of the expression following CDBL in brackets, even if the operands are single — precision or integers, CSNG does the opposite by providing a single precision value of the expression.

Many other functions may be created using the 16 Level 2 functions and Appendix E of the level two manual provides a guide to these.

### Error messages

Whereas level 1 BASIC provides three (WHAT? HOW: and SORRY) error messages, Level 2 has 23 two-letter codes providing a far more specific indication of the error. Level 1's feature of printing the error code at the exact point at which the error occurs is however lost — The message being printed on the following line.

Another facility present in Level 1 but lost in the more powerful version is that of abbreviated statements and commands.


Tandy, however, produce a conversion-tape which will allow software written for a Level 1 machine to be converted to run a Level 2 machine.

### Arrays

Arrays are permitted to Level 2, the number of dimensions being limited by the size of the available memory-string arrays are also allowed.

## TANGERINE

COMPUTER SYSTEMS LIMITED

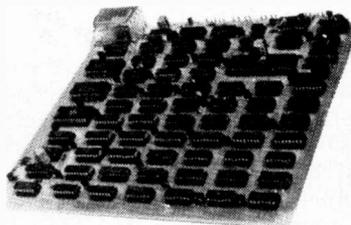

**DON'T FORGET  
SPECIAL OFFER**  
£10 discount  
Due to the  
large amount of  
interest shown  
Offer Extended  
to Mar. 12, '79

The new low cost VDU - Tangerine 1648  
(See page 16, ETI, Oct. '78 for feature details)

#### ORDERING INFORMATION

The normal **KIT price is £139.86**, which includes postage, packing and insurance and VAT @ 8%. HOWEVER, as an introductory gesture we are **discounting this price by £10**, for all orders received postmarked **BEFORE 12th December, 1978**.

If you require further information, send an A4 sized self-addressed envelope. If you wish to purchase a kit please send a cheque or money order made payable to

### TANGERINE COMPUTER SYSTEMS LIMITED

RIVERMILL LODGE, LONDON ROAD, ST. IVES,  
CAMBS. PE17 4BR  
Tel. St. Ives (0480) 65666

# NASCOM 1 HOBBY COMPUTER

A COMPLETE SYSTEM INCORPORATING  
THESE OUTSTANDING FEATURES:

Supplied in Kit Form for Self-Assembly.  
Full documentation supplied.  
Includes Printed Circuit Board.  
Full Keyboard included.  
Interfaces to Keyboard, Cassette Recorder & TV.  
2K x 8 RAM.  
1K x 8 Eprom Monitor Program.  
Powerful Z80 CPU, Mostek.  
16 line x 48 Character Display Interface to standard, unmodified TV set  
On board expansion to 2K x 8 Eprom.  
On board expansion facility for additional 16 Lines I/O.  
Total expansion to 256 Input Ports and 256 Output Ports.  
1K x 8 Nasburg Program in Eprom.  
Provides 8 Basic Operator Commands including single step.  
Expandable Software System via additional user Programs in Ram of Eprom.

Manuals  
Separately  
£3.50

Complete Kits  
NOW IN STOCK

**£197.50**  
+ VAT 8%

Sole Appointed  
for Bristol



## TARGET ELECTRONICS

16 Cherry Lane, Bristol BS1 3NG  
Telephone: 0272 421196

# TRS-80 Update

Level 2 BASIC provides the PEEK and POKE commands. Poke allows a specified value to be written into a specific RAM location PEEK allows the value stored at any RAM location to be retrieved.

POKE is particularly useful when producing graphics displays on the screen. Level 1's SET statements for handling screen graphics were rather slow — Level 2 provides 63 special graphics characters that can be speedily manipulated by the POKE command.

The display can also produce double width (same height) characters. By hitting shift key and right arrow the format is changed. Note however that anything on screen at the time only has every other letter enlarged. The clear key will return the display to the normal format.

## User Subroutines

Level 2 features the BASIC USR statement that permits the calling of user written subroutines.

## File Search

Level 2 allows the user to label files and to search for a the named file. CLOAD "TEST" will ignore all files on tape until the one called "TEST" is found. A useful feature is that as the machine searches for a file, the names of all those on the tape before the specific file is found will be displayed in the upper right hand corner of the display.

A file can be verified after being dumped by entering CLOAD? The machine will then load the program from tape and compare it with that stored in memory. A handy feature that allows one to ensure a program has been faithfully recorded.

## Manual

Unlike the level 1 manual, which makes an excellent job of teaching BASIC, the level 2 manual — As the forward says — Is not for the total beginner.

The manual does not go into the detail of the 233 page Level 1 manual. The Level 2 manual for example presents nine subroutines for array/matrix manipulation with very little explanation. 31 function codes are mentioned in one of appendices with little indication of how they are used in a program.

## Computer Conclusion

The Level 2 package certainly provides a significant improvement over the Level 1 version of this machine and, in our opinion takes the TRS-80 from the realms of the "Superpowered Calculator" — Tandy's words — into the area of real computing.

The number of add-ons available now — floppies, memory, printers etc means that the TRS-80 can form the heart of a flexible system suitable for a wide range of applications.

**See the article on a small business application of a TRS-80 system elsewhere in this issue.**

# A more interesting way to learn



## what is a microprocessor?

If you are considering buying a Micro-computer, Development System, or just want to learn more about this exciting technology, then this short introduction to Microprocessors is for you. Comprising of a 72-page book keyed to over two hours of cassette tapes the many aspects of Microprocessors are explained, including Binary and Hexadecimal counting, Internal structure, Operation, Programming Techniques, Devising a program, etc. Learn at your own pace with this valuable addition to your reference library.

To Technical Book Services  
P.O. Box 79  
Maidenhead, Berks SL6 2EG

### ORDER FORM

Please send me ..... copy/copies of What is a microprocessor?  
@ £10.75 each inclusive. I enclose remittance £.....

Name  
(Print Please)

Address

Registered office 21, Mincing Lane, London EC1 Registered No 12225

# THE MPU MAN

## KEY

- 1 Teletype unit.
- 2 Punched paper tape reader.
- 3 Floppy disc 'player' unit.
- 4 Home-made floppy disc experimental unit.
- 5 Incompatible systems interface patch-board.
- 6 Skeleton keyboard for manual entry.
- 7 Modulator for feeding display material to domestic magic lantern.
- 8 Domestic magic lantern showing results of simulated World cup final.
- 9 Another advanced game in progress.
- 10 Working microprocessor module.
- 11 Well ventilated reprogrammable read only memory.
- 12 Interesting teleprinter graphics — genuine system check — no kid!
- 13 Early home-made 8-bit processor.
- 14 Power supply with outboard cooling and attractive economy housing.
- 15 Another development module. Seems to have undergone pre-frontal lobotomy. . . . Last Night of the Proms?
- 16 Junked cassette player with sprinkling of cassette programmes. Alternative to papertape or manual entry.
- 17 Primitive one-shot switch input unit.
- 18 Aerosol spray for de-bugging.
- 19 Mighty de-bugged noughts and crosses programme listing being triumphantly brandished.
- 20 Attempt to fabricate home brew floppy disc.
- 21 Another teletype unit.
- 22 Personalised low density punched tape storage system.




# Beginning BASIC

Phil Cornes resumes his description of BASIC with a look at some of the conditional branching instructions featured in this language

## IF THEN

THIS IS THE first of BASIC's really powerful conditional branching statements (we look at the others below) that go into the make-up of BASIC and we will add an IF THEN statement to the previous program segments (last month) to see what it can do.

Consider the following—

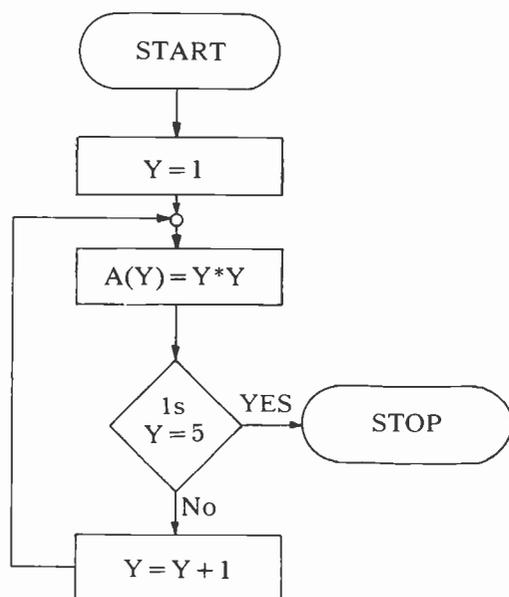

This is the same flow chart that we saw earlier except that now there is a two-way branch added which is made dependent upon the answer to the question 'IS Y = 5'.

Before we go on to look at the program derived from this flow chart, there is one other thing we need to consider. You will notice from the flowchart that IF Y is 5 when the decision box asks the question THEN we branch to a stop box. The statement in BASIC which causes the execution of a program to terminate is the END statement and you will find one of these in the program.

There is no statement in BASIC which corresponds to the start box on the flow chart (that is just presented for our information) and so the first box we consider contains  $Y = 1$ . The statement needed to

convey this to the computer is—

```
LET Y = 1
```

but remember that every statement in a program must have a line number, and so we have—

```
10 LET Y = 1
```

We now move on to the next box

$A(Y) = Y * Y$  and produce the statement—

```
20 LET A(Y) = Y * Y
```

The third box is the new one and we write—

```
30 IF Y = 5 THEN
```

THEN what? Well, we have to branch to the line number which contains the END statement, but we don't yet know which one this will be. So we can either sit and wait until we have written the END statement, or we can say always let the END statement exist on some high numbered line (say 9999) so if we ever need an END statement, we know what line it will appear on. We will do it this way so line 30 will read—

```
30 IF Y = 5 THEN 9999
```

and so if Y does equal 5, then we branch to the END statement that we will put in line 9999.

If the test (IS Y = 5) fails (answer is NO) then line 30 will be ignored and the computer will carry on executing the statements in the normal line number order.

The next box down contains  $Y = Y + 1$ , and so line 40 reads—

```
40 LET Y = Y + 1
```

From this we now branch back to the statement  $A(Y) = Y * Y$  which is on line 20 and we get—

```
50 GOTO 20
```

and lastly

```
9999 END
```

If we write this out in line number order, we get—

```

10 LET Y = 1
20 LET A(Y) = Y*Y
30 IF Y = 5 THEN 9999
40 Y = Y + 1
50 GOTO 20
9999 END

```

and this is our first complete program.

It does not matter that the line numbers do not follow on in multiples of 10, they don't have to, but what is more important is the fact that we do leave some numbers spare between our statements so that if we find we have missed out a line, or think of something else that we would like to add, then we have plenty of space to do so.

Consider the following—

```

5 REM INITIALIZE Y
10 LET Y = 1
15 REM PUT Y*Y IN A(Y)
20 LET A(Y) = Y*Y
25 REM TEST FOR Y = 5
30 IF Y = 5 THEN 9999
40 LET Y = Y + 1
50 GOTO 20
9999 END

```

REM (I thought REM was an android or something to do with sleep) in BASIC is short for REMark and tells the computer that whatever follows on this line is to be ignored because they are only notes for the programmer as a reminder of what is happening.

REMark statements in a program of this length are unnecessary, but we will soon be writing programs of sufficient length and complexity to justify their use as memory aids.

Returning now to our IF-THEN statement (IF Y=5 THEN 9999) the equals sign used here is not an arithmetic operator, but the first of the comparison operators. Any of the other comparison operators (<, >, <=, >=, <>) could also be used in an IF THEN statement, so that—

```

30 IF Y > 4 THEN 9999
130 IF Q < 19.2 THEN 55
902 IF A(17) >= 14.9 THEN LET P = P + 1

```

are all valid statements.

Notice here the twist in the tail of line 902. This is also a valid statement on most machines. This is easier to understand if we consider the IF-THEN statement as two separate statements. The first part (the IF part) asks a question (in line 902 — IS A(17) >= 14.9) to which the computer can answer either YES or NO. If the answer is NO then this statement is finished with and control passes on to the next higher numbered line. If the answer is YES then the computer passes on to the second statement on the line, the THEN part. THEN what? THEN LET P = P + 1 or THEN END or THEN 900 (this is really an abbreviation of THEN GOTO 900) or THEN any other statement. We can even put another IF THEN statement in.

Consider the following—

```
200 IF (A = 1)*(B = 1) THEN 900
```

The computer encountering this would first ask the question IS A = 1. If the answer is NO control passes to the next higher numbered line. If, on the other hand, A is equal to 1, we move on to the statement following the THEN and encounter another IF THEN statement which is treated in exactly the same way as the first. IS B = 1. If NO then carry on with the next line, if YES THEN GOTO 900. You will see that using this logic we will only pass control to line 900 if both A = 1 AND B = 1. At about this point your memory should be stirring to the fact that you have read something about logical operators earlier and indeed this is the place where they fit in. Depending on which machine you are considering, there are two ways of re-writing line 200 above to achieve the same result.

You could use—

```
200 IF A = 1 AND B = 1 THEN 900
```

which will normally be the format for machines with standard or extended BASIC, or—

```
200 IF (A = 1)*(B = 1) THEN 900
```

for the tiny BASIC machines

Notice the brackets in the second example. These tell the computer where one comparison ends and the other starts, otherwise the computer would attempt the following—

```
200 IF A = 1*B
```

(multiplication sign!) and then bomb out on the second equals sign.

The other common logical operator (OR) can also be used in a similar manner—

```
300 IF Q > 3*H OR S < 9 THEN R = R - 2
```

or

```
300 IF (Q > 3*H) + (S < 9) THEN R = R - 2
```

Notice the brackets again in the second example for similar reasons, and notice also the omission of the optional LET keyword before the R = R - 2. We will continue to omit the LET from now on.

Finally for this month, we will go on to consider one of the pre-defined functions of BASIC (somewhat out of turn, but we'll see why in a moment) the random number generator.

## RND(X)

We will start off by saying that the X within the brackets (the brackets are necessary and must be used whatever we replace X by) may be replaced by



# BASIC

any constant, variable name or expression with the proviso that when the computer evaluates the contents of the brackets they must not be negative or the computer will bomb out. When the computer has evaluated the brackets and checked that the answer is not negative, anything after the decimal point is chopped off (so that 0.238 would be truncated to 0, similarly 8.9 would become 8 and so on) if the result of this operation is zero, then the computer will generate a random decimal number (up to 6 digits) in the range zero to one, so that when—

20 R = RND(0)

is executed, R will take a random value between zero and one. If the result after truncating the contents of the brackets is not zero (it must by now be a positive integer) then the computer will generate a random integer between one and the number in the brackets inclusive, so that, for example—

50 R = RND(6.8)

Would assign a random integer to R with a value between 1 and 6 inclusive (6.8 would be truncated to 6). This is a very useful function for any statistical or games applications and has been included at this time so that we can set you some homework (you need the practice). You will find that you now know enough about BASIC to convert the three card shuffling routines presented in the first part into programs and we would suggest that if you are following this series seriously, you should attempt to do just this. Sample answers will be presented next month.

The answers to the questions posed last month are


- 1 The expression has a value of 21, and
- 2 the expression could be simplified to  $7 + 7 * 8 / 2 / ((12 + 8) * 2 / 20)$

You cannot remove the brackets round  $(12 + 8) * 2 / 20$  (if you made this mistake, think about why not).

Next month we go on to look at how we get the computer to print some answers, subroutines and some more conditional branching.

CTI

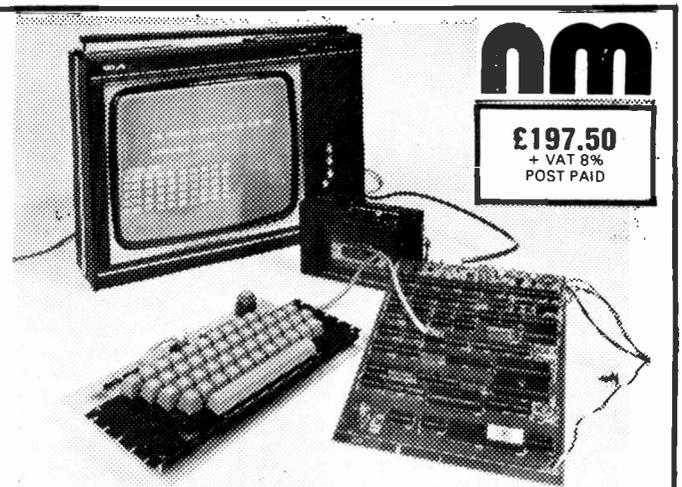PLEASE MENTION  
COMPUTING TODAY  
WHEN REPLYING  
TO ADVERTISEMENTS



## NASCOM I MICRO-COMPUTER for the HOBBYIST

As reviewed in E.T.I. Nov. '78:  
"Overall the Nascom is an excellent unit"

THE COMPLETE MICRO-COMPUTER  
AVAILABLE TO THE HOME CONSTRUCTOR

### FEATURES

- ★ Supplied in kit form for self-assembly
- ★ Full documentation supplied
- ★ Fully screened double-sided plated through hole printed circuit board
- ★ Full 48 key keyboard included
- ★ 2K x 8 Ram
- ★ 1K x 8 monitor program in Eprom
- ★ Powerful Mostek Z80 CPU
- ★ 16 x 48 character display interface to std un-modified T.V.
- ★ T.V. display memory mapped for high speed access
- ★ On board expansion to 2K x 8 Eprom
- ★ On board expansion for additional 16 I/O lines
- ★ Memory may be expanded to full 60K (plus 4K existing on board)

### SOFTWARE FEATURES

- ★ 1K x 8 monitor program providing
- ★ 8 operating commands, supporting Mem examine/modify, tabulate, copy, break, single step execute tape, load, tape dump.
- ★ Reflective monitor addressing for flexible monitor expansion through user programs
- ★ Monitor sub-routines include — delay ASCII coding, binary to hex conversion, clr screen, scroll up, string print, cursor shift and many others.

### EXPANSION

- ★ Expansion buffer board ..... £25.00
- MEMORY KITS (inclusive all hardware)**
- 3K ..... £85.00
- 16K ..... £140.00
- 32K ..... £200.00
- ★ I/O board with decoders and all hardware except ICS will accept up to 3 PIOs, 1 CTC and 1 UART ..... £35.00

**NEW "B-BUG"** extended monitor in 2K of EPROM. Fully software compatible with NASBUG, supporting additional features. — Full keyboard shift for all 128 characters, full cursor movement routines, Read and Write commands (fast tape load and dump), H and N commands (for inserting ASCII code directly into programme), Arith. command (for calculating relative jumps), Generate command (for automatic programme start), Intelligent copy (for non-destructive re-location of DATA), Random, block handling, ASCII to BCD and BCD to ASCII routines and many more. 2 EPROMS + full documentation — £21.86.

- ★ S.a.e. for full expansion details.

### OTHER HARDWARE

- ★ 3A power supply for up to 4K expansion ..... £19.90
- ★ 8A power supply for larger than 4K expansion ..... £60.00
- ★ Expansion card frame ..... £29.50
- ★ Programming manual ..... £4.00
- ★ Hardware & software manuals (supplied in kit) ..... £3.00

Export Trade, Government and Educational Enquiries Invited

Add VAT at 8% on all items except manuals



Demonstrations Continuous at our Store



Construction  
Manuals  
Separately  
£3.00

Complete Kits  
NOW IN STOCK

**£197.50**  
+ VAT 8%  
POST PAID

Sole Appointed  
London  
Stockists

**HENRY'S**  
RADIO

**HENRY'S RADIO**  
404 Edgware Rd. London W2  
England  
PHONE (01)723 1008

## AD INDEX

|                                  |       |
|----------------------------------|-------|
| AIRAMCO .....                    | 3     |
| ALMARC .....                     | 17    |
| COMP COMP COMP .....             | 2     |
| HAPPY MEMORIES .....             | 30    |
| HENRY'S .....                    | 29    |
| H. L. AUDIO .....                | 13    |
| KIMBERLEY BUSINESS RECORDS ..... | 7     |
| LOTUS SOUND .....                | 30&31 |
| L.P. ELECTRONICS .....           | 22    |
| MICRODIGITAL .....               | 21    |
| NEWBEAR .....                    | 32    |
| SCIENCE OF CAMBRIDGE .....       | 14&15 |
| STRATHAND .....                  | 7     |
| TANGERINE .....                  | 24    |
| TARGET .....                     | 24    |
| TECH. BOOK SERVICE .....         | 25    |
| TRANSAM .....                    | 5     |
| VERDURE .....                    | 30    |
| V + T ELECTRONICS .....          | 17    |



## TEE-SHIRTS

### HOW TO ORDER:

The new red ETI tee-shirts are available in large, medium or small size for only £2.00 inclusive of postage and packing.

Send cheques/POs to:  
**ETI Tee Shirts**  
 25-27 Oxford Street  
 London W1R 1RF

## MICRO-COMPUTER BARGAINS

We have a stock of untested micro-computer PCB's which are surplus to our requirement. Each board contains an Intel 4040 (CPU), 4201 (Clock), 4289 (Standard Memory Interface), 5MHz crystal, zero crossover detector cct, power on reset cct, skts for 6 x 1702A PROM and on board power supply containing transformer, rectifier, regulator, heatsink and reservoir capacitor.

These PCB's are sold with data on all chips and cct diagram, as untested units at the bargain price of

**£19.00 ea**

Also available:

|   |              |
|---|--------------|
| 1702A memory, used but erased .....               | <b>£6.00</b> |
| 1702A memory programmed to your requirement ..... | <b>£7.50</b> |
| 6265 gen purpose i/p-o/p device .....             | <b>£5.00</b> |

Cheque/Postal Order to:

### VERDURE LTD.

54/64 Morfa Road  
 Strand, Swansea

Mail Order Supplies Only

Tel: (0792) 41241/462684

## HAPPY MEMORIES



### ASCII KEYBOARDS £49

£1 p&p. Cursor Kit £2.50

All 128 ASCII characters, parallel output, 2 key rollover, Alpha lock, Auto-repeat, Two user-definable keys, positive and neg. strobe. All on 12½ x 6 inch PCB. Add-on five key cursor kit for up, down, left, right and home available. Send SAE for data sheet.

|   |   |
|---|---|
| Science of Cambridge Mk. 14             |   |
| Set of 18 Texas low-profile DIL sockets | <b>£2.80</b>  |
| 21L02 250 ns                            | <b>89p</b> , 16 up <b>86p</b> , 64 up <b>83p</b>    |
| 21L02 250 ns                            | <b>110p</b> , 16 up <b>107p</b> , 64 up <b>104p</b> |
| 2114 450 ns                             | <b>550p</b> , 4 up <b>525p</b>                      |
| 2114 300 ns                             | <b>625p</b> , 4 up <b>600p</b>                      |
| 4116 DRAM                               | <b>1150p</b> , 4 up <b>1100p</b>                    |
| 2708 450 ns                             | <b>725p</b> , 4 up <b>700p</b>                      |

|                                      |                            |
|--------------------------------------|----------------------------|
| Texas low-profile DIL sockets        |                            |
| Pins                                 | 8 14 16 18 20 22 24 28 40  |
| Pence                                | 10 11 12 17 18 20 22 28 38 |
| Antex 1mm bits for CX17 or CCN irons | <b>45p</b>                 |

Happy Memories, 5 Cranbury Terrace  
 Southampton, Hants SO2 0LH

All prices include VAT. Add 20p postage except where shown. COD available at cost.

## MEMORIES

|                               |               |
|-------------------------------|---------------|
| 2112 (256x4 Static RAM)       | <b>£1.03</b>  |
| 21L02 (450ns)                 | <b>99p</b>    |
| (1K x 1 Static RAM)           |               |
| 21L02 (250ns)                 | <b>£1.48</b>  |
| 2114 (1K x 4 Static RAM)      |               |
|                               | <b>£7.13</b>  |
| 4027 (300ns, equiv 2104)      |               |
|                               | <b>£1.87</b>  |
| (4K x 1, 16 pin, Dynamic RAM) |               |
| 5208 (equiv. 2107)            | <b>£2.77</b>  |
| (4K x 1, 22 pin, Dynamic RAM) |               |
| 4116                          | <b>£12.50</b> |
| (16K x 1, Dynamic RAM)        |               |
| 2708                          | <b>£6.50</b>  |
| (1K x 8 UVEPROM)              |               |
| 8080A (CPU)                   | <b>£6.60</b>  |
| 81LS95 (Buffer TriS)          | <b>.70p</b>   |
| 81LS96 (Buffer TriS)          | <b>.70p</b>   |

All chip prices VAT exclusive.

Please add 8% to order.

35p for p&p orders under £5

Please write for discounts over 100 pieces

## PET CORNER

Lotus now carry an exciting range of products for your CBM PET.

### Memory Expansion

- ★ Mounts inside PET
- ★ Runs from PET's own power supply
- ★ Takes 10 minutes to fit
- ★ Includes memory test program
- ★ 6 month warranty

**16k £276 + VAT**

**24k £377 + VAT**

**32k £394 + VAT**

### MUSIC BOX

Turns your PET into a programmable musical instrument. You can record and play up to 90 pages, 16 notes per page, change tempo, key, etc.

**£37.50 inc. VAT & P&P**

### T.I.S. WORKBOOKS

A set of 5 workbooks to give you a full understanding of all the ins and outs of your PET more fully than any previous manuals.

**£15.95 per set. inc. P&P**

**Dustcover £17.95 inc. VAT & P&P**

Lots of software and other goodies.

Send large SAE.



Tel: 01-981 3993  
 Telex: 261426  
 Attn. Lotus Sound

# The Age of Affordable Personal Computing Has Finally Arrived


Ohio Scientifics

## Superboard II

Full 8K basic and 4K user RAM  
Built and tested

# £284.95

inc. VAT & P&P

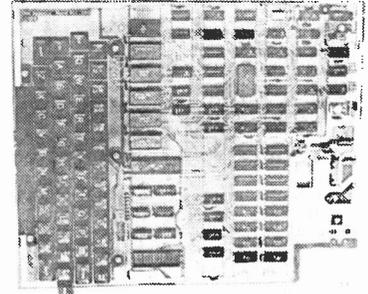

Ohio Scientific has made a major breakthrough in small computer technology which dramatically reduces the cost of personal computers. By use of custom LSI micro circuits, we have managed to put a complete ultra high performance computer and all necessary interfaces, including the keyboard and power supply, on a single printed circuit board. This new computer actually has more features and higher performance than some home or personal computers that are selling today for up to \$2000. It is more powerful than computer systems which cost over \$20,000 in the early 1970's.

This new machine can entertain your whole family with spectacular video games and cartoons, made possible by its ultra high resolution graphics and fast BASIC. It can help you with your personal finances and budget planning, made possible by its decimal arithmetic ability and cassette data storage capabilities. It can assist you in school or industry as an ultra powerful scientific calculator, made possible by its advanced scientific math functions and built-in "immediate" mode which allows complex problem

solving without programming! This computer can actually entertain your children while it educates them in topics ranging from naming the President of the United States to tutoring trigonometry all possible by its fast extended BASIC graphics and data storage ability.

The machine can be economically expanded to assist in your business, remotely control your home, communicate with other computers and perform many of the other tasks via the broadest lines of expansion accessories in the microcomputer industry.

This machine is super easy to use because it communicates naturally in BASIC, an English-like programming language. So you can easily instruct it or program it to do whatever you want, *but you don't have to*. You don't because it comes with a complete software library on cassette including programmes for each application stated above. Ohio Scientific also offers you hundreds of inexpensive programs on ready-to-run cassettes. Program it yourself or just enjoy it, the choice is yours.

### Standard Features

- Uses the ultra powerful 6502 microprocessor
- 8K Microsoft BASIC-in-ROM
- Full feature BASIC runs faster than currently available personal computers and all 8080-based business computers.
- 4K static RAM on board expandable to 8K
- Full 53-key keyboard with upper-lower case and user programmability
- Kansas City standard audio cassette interface for high reliability
- Full machine code monitor and I/O utilities in ROM
- Direct access video display has 1K of dedicated memory (besides 4K user memory), features upper case, lower case, graphics and gaming characters for an effective screen resolution of up to 256 by 256 points. Normal TV's with overscan display about 24 rows of 24 characters, without overscan up to 30 x 30 characters.

### Extras

- Available expander board features 24K static RAM (additional mini-floppy interface, port adapter for printer and modem and OSI 48 line expansion interface).
- Assembler/editor and extended machine code monitor available.

### Commands

CONT LIST NEW NULL RUN

### Statements

CLEAR DATA DEF DIM END FOR  
GOTO GOSUB IF...GOTO IF...THEN INPUT LET  
NEXT ON...GOTO ON...GOSUB POKE PRINT READ  
REM RESTORE RETURN STOP

### Expressions

#### Operators

-, +, \*, /, ↑, NOT, AND, OR, >, <, <>, >=, <=, =  
RANGE 10<sup>-32</sup> to 10<sup>+32</sup>

### Functions

ABS(X) ATN(X) COS(X) EXP(X) FRE(X) INT(X)  
LOG(X) PEEK(I) POS(I) RND(X) SGN(X) SIN(X)  
SPC(I) SQR(X) TAB(I) TAN(X) USR(I)

### String Functions

ASC(X\$) CHR\$(I) FRE(X\$) LEFT\$(X\$,I) LEN(X\$) MID\$(X\$,I,J)  
RIGHT\$(X\$,I) STR\$(X) VAL(X\$)

Plus variables, arrays and good editing facilities.

Fully built and tested. Requires only +5V at 3 amps and a videomonitor or TV and RF converter to be up and running.

At this price there is going to be an enormous demand for Superboard II and supplies are going to be extremely limited. Lotus Sound is expecting first deliveries from the States in mid-December and orders will be treated strictly in the order they arrive, so post off today if you want to avoid long delays.

# SOUND

4 MORGAN ST., LONDON E3 5AB

(Mail Order only)

To: LOTUS SOUND  
4 MORGAN ST., LONDON E3 5AB

Please send me ..... Ohio Scientific Superboard  
Computer(s)  
I enclose cheque/PO for £ .....

Name .....

Address .....



# NewBear Computing Store



## ★ SYM-1 ★

(Formally VIM-1)

The new 6502 micro from Synertek. Fully assembled and tested

Ex Stock @ **£199.00**

+ 8% V.A.T.  
Carriage £1.00

## ★ SALE ★

FOR CALLERS ONLY AT BONE LANE, NEWBURY. 1 ONLY V.D.U. £300 + 8% V.A.T. CASH ONLY.

A LARGE NUMBER OF FULLY POPULATED LOGIC BOARDS, EDGE CONNECTORS, P.C.B.s AND COMPONENTS ALL AT SILLY PRICES. PLUS SPECIAL OFFERS ON CERTAIN I.C.s.

CAN YOU BEAR TO MISS THIS OPPORTUNITY? SAT., 6th JAN. TO SAT., 13th JAN. INCLUSIVE.

## ★ NASCOM 1 ★

### Z80 BASED MICROCOMPUTER KIT

Ex Stock @ **£197.50**

+ 8% VAT  
£1.00. Carriage

|                 |        |        |
|-----------------|--------|--------|
| Z80 CPU 2.5 MHz | 2708   | £6.99  |
|                 | 2716   | £22.50 |
| Z80 P10 PS      | MIKBUG | £13.65 |
|                 | 4116   | £15.00 |
| Z80 CTC PC      |        |        |
|                 | £9.15  |        |
| Z80A CPU 4MHz   |        |        |
|                 | £20.00 |        |
| Z80A P10        | £11.05 |        |
| Z80A CTC        | £11.05 |        |
| MC 6800         | £8.75  |        |
| MC 6820         | £4.63  |        |
| MC 6850         | £6.74  |        |
| MC 6810         | £3.61  |        |
| MC 8602P        | £2.88  |        |
| MC14536P        | £3.69  |        |
| MC 3459         | £2.53  |        |
| SC/MP II        | £10.30 |        |
| 6502            | £14.93 |        |
| 8080A           | £8.00  |        |

### Interfacing I.C.'s

|           |        |
|-----------|--------|
| SFF 96364 | £16.20 |
| MC 1488P  | £1.40  |
| MC 1489P  | £1.40  |
| 75150P    | £1.30  |
| 75150N    | £1.20  |
| 75154     | £2.30  |
| 4N33      | £1.95  |
| AY-5-1013 | £4.50  |
| 6402      | £4.50  |
| 6571      | £6.70  |
| 2501      | £6.50  |

### Buffers

|        |       |
|--------|-------|
| 81LS95 | £1.30 |
| 81LS96 | £1.30 |
| 81LS97 | £1.30 |
| 81LS98 | £1.30 |
| 8T26   | £1.84 |
| 8T95   | £1.60 |
| 8T97   | £1.60 |
| 74367  | £1.30 |

### Memories

|         |        |
|---------|--------|
| 2102-1  | £1.25  |
| 2102L-1 | £1.35  |
| 2112    | £3.04  |
| 2513    | £6.50  |
| SWATBUG |        |
|         | £16.00 |
| 2114    | £8.25  |

## SEND FOR OUR NEW CATALOGUE

### COMPUTER DESIGNS

|                          |       |          |
|--------------------------|-------|----------|
| 77-68 6800 Microcomputer | £7.50 | P&PP .50 |
| WB-1 TTL Microcomputer   | £6.50 | .50      |

### FROM ADAM OSBOURNE ASSOCIATES

|  |        |      |
|--|--------|------|
| Introduction to Microcomputers                 |        |      |
| Volume 0 The Beginners Book                    | £5.95  | .50  |
| Volume 2: Basic Concepts                       | £5.95  | .50  |
| Volume 2 Some Real Products June 1977 Revision | £11.95 | 1.00 |
| 8080A/8085 Assembly Language Programming       | £6.95  | .50  |
| 6800 Assembly Language Programming             | £6.95  | .50  |
| Some Common Basic Programmes                   | £5.95  | .50  |
| 6800 Programming for Logic Design              | £5.95  | .50  |
| 8080 Programming for Logic Design              | £5.95  | .50  |
| Payroll with Cost Accounting in Basic          | £9.95  | 1.00 |

Instant Freeze-Dried Computer Programming in basic.  
By Jerald R. Brown £4.95 .75  
My Computer Likes Me When I Speak in Basic £1.65 .30

|                             |        |     |
|-----------------------------|--------|-----|
| Computer Programs that Work | £2.40  | .75 |
| Basic Software Library      |        |     |
| Volume 1:                   | £17.50 | .50 |
| Volume 2                    | £17.50 | .50 |
| Volume 3                    | £26.95 | .50 |
| Volume 4                    | £7.95  | .50 |
| Volume 5                    | £7.95  | .50 |
| Volume 6                    | T.B.A. | .50 |
| Volume 7                    | £26.95 | .50 |

### NEW BOOKS

|   |       |     |
|---|-------|-----|
| First Book of Kim                       | £7.00 | .50 |
| Z80 Microcomputer Handbook              | £7.25 | .50 |
| Using the 6800 Microprocessor           | £6.25 | .50 |
| Micro 6502 Journal                      | £1.70 | .50 |
| Learning Basic Fast                     | £6.30 | .50 |
| How to Program Microcomputers           | £6.30 | .75 |
| Getting involved with your Own Computer | £4.75 | .75 |
| 8080A Bugbook                           | £6.95 | .75 |

### SYBEX

|                                       |       |     |
|---------------------------------------|-------|-----|
| Microprocessors C201                  | £8.00 | .50 |
| Microprocessor Interfacing Techniques | £8.00 | .50 |

### BEAR BAGS

- 77-68 CPU PCB and Components £49.50
- 77-68 LED's and Switches £14.95
- 77-68 Power Supply £17.95
- 77-68 19" 5u Rack and Backplane £26.70 +
- 77-68 4K Ram PCB and Components £74.00
- 77-68 Mon 1 PCB and Components £50.00
- 4K Ram Exorciser PCB and Components £71.50
- 8K Ram Exorciser PCB and Components £160.00\*
- Petitevid VDU Kit £85.00
- Kansas City Cassette Interface £18.95
- UHF Modulator £4.50
- 77-68 VDU PCB and Components £69.50
- 77-68 Mon 2 PCB and Components Et. b. a.
- Prom Programmer PCB and Components £35.00
- PROMVERTER (Enables a 2708 to be used instead of MIKBUG) £8.50

50p Postage and Packing unless otherwise stated + £1.50 Postage and Packing.  
\*£1.00 Postage and Packing.


### 24-HOUR TURNROUND ON ORDERS

Please add 8% VAT to all prices. P&P 30p unless otherwise stated. Barclaycard and Access welcome. Overseas orders issued with Pro-Forma Invoice. Send for catalogue to NewBear Computing Store, Bone Lane, Newbury, Berks. Callers welcome Mon.-Sat., 9.00-5.30, but please phone us first on 0635 49223. New office — 2 Gatley Road, Cheadle, Cheshire. (Callers only). Telephone 061-491 0134.

### FLOPPY DISC DRIVES

- 5 1/4" SHUGART SA400 DISC DRIVE £255.00  
Carriage by Securicor 'C' Rate £4.50
- 8" DRI SINGLE SIDED DOUBLE DENSITY £325.00  
Carriage by Securicor 'C' Rate £5.00
- 8" DRI DOUBLE SIDED DOUBLE DENSITY £365.00  
Carriage by Securicor 'C' Rate £5.00

# SPECIALS

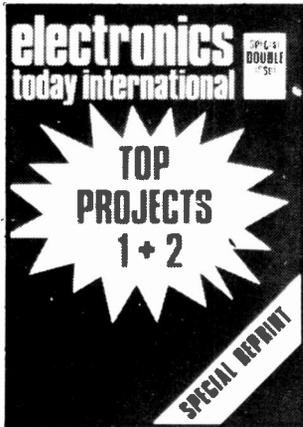

**£2.50 + 25p P&P**

ETI top projects 1 + 2 include:  
Master mixer, 100 W guitar amp., low power laser, printmeter, transistor tester, mixer preamp, logic probe.



**£1.00 + 25p P&P**

Ni-Cad charger, loudhailer, scope calibrator, electronic ignition, car theft alarm, turnindicator canceller, brake

light warning, LM380 circuits, temperature alarm, aerial matcher, UHF TV preamp, metal locator, four-input mixer, IC power supply, rumble filter, IC tester, ignition timing light, 50 W stereo amp. plus many more. . . .  
ETI Top Projects 3. This issue was so popular that it is now sold out!

ETI Top Projects 4 includes:  
Sweet sixteen stereo amp., waa-waa, audio level meter, expander/compressor, car theft alarm, headlight reminder, dual-tracking power supply, audio millivoltmeter, temperature meter, intruder alarm, touch switch, push-button dimmer, exposure meter, photo timer, electronic dice, high-power beacon, electronic one-armed bandit! . . .


ETI Top Projects 5. Twenty-two complete projects including:  
5 W stereo amp., stage mixer, disco mixer, touch organ, audio limiter, infra-red intruder alarm, model train controller, reaction tester, headphone radio, STD timer, double dice, gen.-purpose power supply, logic tester, power meter, digital voltmeter, universal timer, breakdown beacon, heart rate monitor, IB metal locator, temperature meter. . . .

ETI Top Projects 6, just published, includes:  
Graphic equaliser, 50-100 W amp. modules, active crossover, flash trigger, "star and dot" game, burglar alarm, pink noise generator, sweep oscillator, marker generator, audio-visual metronome, LED dice, skeet game, lie detector, disco light show. . . .



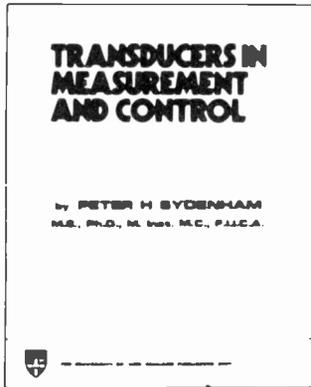**75p + 25p P&P**

Comprised entirely of new material, the edition covers such diverse subjects as Star Wars and hi-fi! The magazine contains projects for everyone — none of which have appeared in ETI or Hobby Electronics and a look at the future of MPUs, Audio, Calculators and Video. How can you not read it?



**£3.00 + 25p P&P**

This book is rather an unusual reprint from the pages of ETI. The series appeared a couple of years ago in the magazine, and was so highly thought of by the University of New England that they have re-published the series

splendidly for use as a standard textbook. Written by Peter Sydenham, M.E., Ph.D., M.Inst.M.C., F.I.I.C.A., this publication covers practically every type of transducer and deals with equipment and techniques not covered in any other book. Enquiries from educational authorities, universities and colleges for bulk supply of this publication are welcomed. These should be addressed to H. W. Moorshead Editor, Hobby Electronics.

## HOW TO ORDER

Postage and packing also refers to overseas. Send remittance in sterling only.

**Specials**  
Modmags Ltd  
25-27 Oxford Street  
London W1R 1RF

Please mark the back of your cheque or PO with your name and address.

Please supply me with the following Specials:

.....

.....

.....

.....

.....

Total cheque/PO enclosed = £ ..

Address:

M .....

.....

.....

.....

FROM THE PUBLISHERS OF  
ELECTRONICS TODAY INTERNATIONAL

## ETI CIRCUITS No 2

**£1.50**

Each volume contains over 150 circuits, mainly drawn from the best of our Tech-Tips. The circuits are indexed for rapid selection and an additional section is included which gives transistor specs. and plenty of other useful data.  
Sales of this publication have been phenomenal — hardly surprising when the circuits cost under 1p each! Each volume costs.

**£1.50 + 25p P&P**




ETI's successful beginners series came to an end some time ago now, and the whole series is available from us in reprint form. The three books between them contain all the information presented in the series (sometimes in more detail!) and together form an excellent starting point for anyone interested in learning the art of electronics. Each volume costs

**£1.20 + 25p P&P**

# The latest kit innovation!
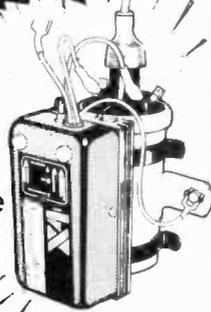
## from Sparkrite

*Sparkrite was featured by Shaw Taylor in "DRIVE IN"*



the quickest fitting  
**CLIP ON**  
capacitive discharge  
electronic ignition  
in KIT FORM

- Smoother running
- Instant all-weather starting
- Continual peak performance
- Longer coil/battery/plug life
- Improved acceleration/top speeds
- Optimum fuel consumption

Sparkrite X4 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 1/3 mins. Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). The circuit incorporates a voltage regulated output for greatly improved cold starting. The circuit includes built in static timing light, systems function light, and security changeover switch. All kits fit vehicles with coil/distributor ignition up to 8 cylinders.

### THE KIT COMPRISES EVERYTHING NEEDED

Die pressed epoxy coated case. Ready drilled, aluminium extruded base and heat sink, coil mounting clips, and accessories. Top quality 5 year guaranteed transformer and components, cables, connectors, P.C.B., nuts, bolts and silicon grease. Full instructions to assemble kit neg. or pos. earth and fully illustrated installation instructions.

NOTE - Vehicles with current impulse tachometers (Smiths code on dial RV1) will require a tachometer pulse slave unit. Price £3.35 inc. VAT, post & packing.

Electronics Design Associates, Dept. HE2  
82 Bath Street, Walsall, WS1 3DE. Phone: (9) 614791

Name

Address

Phone your order with Access or Barclaycard

including postage and packing UK only

QUANTITY REQ'D.

Send SAE if brochure only required.

I enclose cheque/PO's for

X4 KIT £16.65 inc. VAT

TACHS PULSE SLAVE UNIT  
£3.85 inc. VAT

£

Cheque No.

Access or Barclaycard No.

### SINCLAIR PRODUCTS\*

Microvision TV £172. PDM35 £27.25. Mains adaptor £3.24. Case £3.25. 30kv probe £18.95. DM235 £48.30. Rechargeable battery units £7.95. Adaptor/charger £3.70. Case £8.50. 30kv probe £18.95. Cambridge prog calculator £13.15. Prog library £3.45. Mains adaptor £3.20. Enterprise programmable calculator £20.95.

### S-DECS AND T-DECS\*

S-Dec £3.17. T-Dec £4.02. u-DeCA £4.40. u-DeCB £7.05. 16dill or 10T05 adaptors with sockets £2.14.

### CONTINENTAL SPECIALITIES PRODUCTS\*

EXP300 £6.21. EXP350 £3.40. EXP600 £6.80. EXP650 £3.89. EXP48 £2.48. PB6 £9.94. PB100 £12.74. LM1 £30.99. LP1 £33.48. LP2 £19.44.

### TV GAMES

Send sae for data. AY-3-8500 + economy kit £8.95. Tank battles. AY-3-8710 chip £6.90. economy kit £7.05. Stunt cycle. AY-3-8760 chip £6.90. economy kit £5.60. 10 game paddle 2 chip AY-3-8600 + economy kit £12.50. Racing car chip AY-3-8603 + economy kit £19.95. Modified shoot kit £4.96. Rifle kit £4.95. Colour generator kit £7.50.

### MAINS TRANSFORMERS

6.0-6V 100ma 74p. 1 1/2a £2.35. 6.3V 1 1/2a £1.89. 9.0-9V 75ma 74p. 1a £1.99. 2a £2.60. 12.0-12V 50ma 74p. 100ma 90p. 1a £2.49. 13V 1/2a 95p. 15.0-15V 1a £2.79. 30.0-30V 1a £3.59.

### JC12, JC20 AND JC40 AMPLIFIERS

A range of integrated circuit audio amplifiers supplied with free data and printed circuits. JC12 6 watts £1.60. JC20 10 watts £2.95. JC40 20 watts £3.95. Send sae for free data on our range of matching power and preamp kits.

### FERRANTI ZN414

IC radio chip £1.05. Extra parts and pcb for radio £3.85. Case £1. Send sae for free data.

### PRINTED CIRCUIT MATERIALS

PC etching kits economy £1.85. standard £3.99. 60 sq. in. pcb 55p. 1 lb. FeCl 1.05. Etch resist pens economy 45p. dalo 73p. Small drill bits 1/32 ins. or 1mm 20p each. Etching dish 68p. Laminate cutter 75p.

### BATTERY ELIMINATORS

3-way types with switched output and 4-way multi-jack 3/4v/6v 100ma £2.71. 6/7 1/2v/300ma £2.95. 100ma radio types with press-stud connectors 9v £3.35. 6v £3.35. 4 1/2v £3.35. 9+9v £4.50. 6+6v £4.50. 4 1/2+4 1/2v £4.50. Cassette recorder mains unit 1 1/2v/100ma with 5-pin din plug £3.35. Fully stabilised type 3/6/7 1/2v/9v 400ma £6.40. Car converters 12v dc input, output 9v 300ma £1.50. output 7 1/2v 300ma £1.50. Output 3/4 1/2v/6/7 1/2v/9/12v 800ma £2.50.

### BATTERY ELIMINATOR KITS

Send sae for data. 100ma radio types with press-stud connectors 4 1/2v £1.80. 6v £1.80. 9v £1.80. 4 1/2+4 1/2v £2.50. 6+6v £2.50. 9+9v £2.50. Cassette type 7 1/2v 100ma din plug £1.80. Heavy duty 13-way types 4 1/2v/6/7 1/2v/11/13/14/17/21/25/28/34/42v 1A £4.65. 2A £7.25. Transistor stabilised 8-way types for low hum 3/4 1/2v/6/7 1/2v/9/12/15/18v 100ma. £3.20. 1 Amp £5.40. Variable voltage stabilised models 2-18v 100ma £3.60. 2-30v 1A £6.95. 2-30v 2A £10.95. Car converter 12v dc input. Output 9/7 1/2v/6v 1A stabilised £1.95.

### BI-PAK AUDIO MODULES

Send sae for data. S450 £23.51. AL60 £4.86. PA100 £16.71. SPM80 £4.47. BMT80 £5.95. MK60 £38.74. Stereo 30 £20.12.

### COMPONENTS

1N4148 1.4p. 1N4002 3.6p. 741 8 dil 15p. NE555 8 dil 23p. BC182B. BC183B. BC184B. BC212B. BC213B. BC214C. BC547. BC548. BC549. BC550 4.5p. TIP31C. TIP32C 25p. TIP41C. TIP42C 37p. B0131. B0132 28p. Plastics equivers: BC107. BC109. BCY71. BCY72 4.8p. Fuses 20mm x 5mm Cartridge 5, 1, 2, 3. 5Amp quick-blow 1p. anti-surge 3.4p. Resistors 5% 1/4W £12. 10R to 10M 1p. 0.8p for 50+ of one value. Polyester capacitors 250V D15. 068. 1mf 1.5p. 01. 033. 33mf 2.7p. 022. 047mf 3.2p. 22. 47mf 4.8p. Polystyrene capacitors £12. 63v 10 to 10000pf 3p. Ceramic capacitors 50v £12. 22 to 1000pf 1.7p. E6 1n5 to 47n 2p. Electrolytic capacitors 50v 5, 1, 2mf 5p. 25v 5, 10mf 5p. 16v 22mf 5p. 100mf 6p. 470mf 11p. 1000mf 10p. Zeners 400mw E24 2v/7 to 33v 7p. Preset pots sub-miniature 0.1W horiz or vert 100 to 4M7 6.8p. Potentiometers 1/4W 4K7 to 2M2 log or lin single 26p. dual 76p.

## SWANLEY ELECTRONICS

Dept. ET1, 32 Goldsea Road, Swanley, Kent, BR8 8EZ

Mail order only. Please add 30p to the total cost of order for postage. Prices include VAT. Overseas customers deduct 7% on items marked \* and 11% on others. Official credit orders welcome.

## NO DISCO SYSTEM IS COMPLETE WITHOUT...



### CITRONIC MM 313 MIXER

Ideal for the DIY enthusiast building up a complete disco system. 4/6 ch. mono. inc. LED indicators, connections via phono sockets at rear. Bargain price, including PSU £80.46 inc VAT (P&P £1.50)

### PIEZO HORNS

FANTASTIC SPECIAL OFFER TO READERS OF THIS PUBLICATION

2 tweeters for your disco. PA system or Hi-Fi. Frequency range 5K-20K. No X or required. They can be used in any PA system up to 100W. Why pay more? OUR PRICE ONLY £4.99 each (P&P 35p each)



### BULGIN OCTAL PLUGS AND SOCKETS

There's always hundreds of Bulgin Octal multiway plugs and sockets in stock at Roger Squire's. Each pin rated 6A. Perfect for your Sound to Light System. P552 SOCKET £0.65 (P&P 35p) P551 PLUG £1.84 (P&P 35p) Carriage on 10 or more nominal £1.00. Also available 6-way multicore cable (6 Amps per core) ex stock. £0.65 per metre. Please phone for carriage quote.



### PROJECTORS SQUIRE MULTIFECT 150

including rotator and effects wheel. A truly versatile projector which uses a powerful 150W Tungsten bulb, all effects attachments simply slot in ready for use

A BARGAIN AT £40.50 (P&P £1.00)



### STARLITE 250

An exclusive new line to Roger Squire's Disco Centres. Superb high powered 250W quartz halogen bulb, fan cooled, accepts wide range of multifect attachments. Unique connection slot for orbit prism revolvers. Only

£70 (+P&P) attachments extra

### PLUS MANY DISCO ACCESSORIES

All Roger Squire's shops have a service department which carries large stocks of DISCO SPARES & ACCESSORIES. For example: Fane and H. H. Disco Speakers 12" and 15" BSR and Garrard decks at discount prices.



Plus sockets, Fuses, Plugs, etc etc.

## Roger Squire's DISCO GEAR

Send Mail Orders to: Roger Squire's Mail Orders, Barnet Trading Estate, Park Road, Barnet, Herts EN5 5SA. 01-441 3527 (Hotline) 01-441 1919 (Switchboard) Open: Mon-Fri, 9.5-3.0.

Personal callers: ROGER SQUIRE'S DISCO CENTRES

LONDON: 175 Junction Road, Tolwell Park N19 5QJ. 01-272 7474

BRISTOL: 125 Church Road, Redfield, Bristol BS5 3UR. 0272-550550

MANCHESTER: 251 Deansgate M3 4EN. 061-831 7676

GLASGOW: 1 Queen Margaret Road (off Queen Margaret Drive), Kelvinista, Glasgow G20 6DP. 041-946 3303

Open from 10-5 Tues-Sat 10-8 Weds. Closed Mondays

# DATA SHEETS EXPLAINED

The data sheets which we publish regularly are very popular, but from time to time we receive requests for a fairly simple explanation of the terms and abbreviations which one finds in semiconductor device data sheets, and so here it is!

THE INFORMATION contained in semiconductor device data sheets is often grossly misunderstood. Great care must be taken to ensure that the exact meaning of a term or abbreviation is clear. As an example, we can quote the following conversation which actually occurred between two people who should both have known better.

A representative of a semiconductor distributor was showing data on a new power device to a lecturer. The lecturer said that the device data was wrong, since the maximum collector current was quoted as 12A and the maximum collector-emitter voltage ( $V_{CEO}$ ) as 80V; this is a power level of  $12 \times 80 = 960W$ , but the maximum permissible dissipation quoted in the data sheet is only 90W. The representative could provide no answer!

The data was, of course, perfectly correct. The problem arose because neither of the people concerned had appreciated the exact meaning of  $V_{CEO}$  which signifies the collector-emitter voltage *with the base open circuited*. Under these conditions (with zero base current) the collector current will be very small and the power dissipation in the transistor will also be quite small. Thus there is a great deal of difference between  $V_{CE}$  (the collector-emitter voltage under any conditions) and  $V_{CEO}$  (the collector-emitter voltage with the base open circuited). If still more information is required, one must look into the SOAR (Safe Operating ARea) graph to ascertain the regions of the collector voltage/collector current curve where the device can be safely operated for limited or unlimited times.

This is a very simple example of the pitfalls one can encounter if one does not really understand the *exact* meanings of the terms and abbreviations used in data sheets. Such misunderstandings are very common, but not (we hope!) amongst the devices covered in our data sheets, since it is equally important that our readers understand the exact meanings of abbreviations used in data sheets on relatively simple devices such as ordinary diodes and transistors.

## Letter Symbols

Three of the most important symbols used in semi-conductor device data sheets are V, I and P for voltage, current and power respectively. Various subscripts are added to these three letters to indicate the electrode(s) to which the symbol is being applied and possibly certain circuit conditions. Some of the most commonly used subscripts are listed below.

|    |                          |
|----|--------------------------|
| A  | anode                    |
| AV | average                  |
| B  | base                     |
| BO | breakover                |
| BR | breakdown                |
| C  | collector                |
| D  | drain or delay           |
| E  | emitter                  |
| F  | forward                  |
| G  | gate                     |
| H  | holding                  |
| I  | input                    |
| J  | junction                 |
| K  | cathode                  |
| M  | peak value of a quantity |
| O  | open circuit or output   |

|   |   |
|---|---|
| R | reverse or repetitive                   |
| S | source, short circuit, series or shield |
| T | in the on state (that is, triggered)    |
| W | working                                 |
| X | specified circuit                       |
| Z | impedance                               |

## Order of subscripts

In most cases more than one subscript is needed; the subscripts are usually placed in a definite order governed by the following rules:

The first subscript indicates the electrode at which the current or voltage is measured.

The second subscript denotes the reference terminal or circuit mode. (This subscript is often omitted if it is felt no ambiguity will arise.)

The letter O may be used as a third subscript to show that the electrode not indicated by any previous subscript is open circuited. Similarly the letter S can be used as a third subscript to show the third electrode is shorted to the reference electrode of the second subscript, whilst the letter R as a third subscript indicates that a specified resistance is connected between the third electrode and the reference electrode.

The supply voltage to a collector is indicated as  $V_{CC}$ , the second suffix being a repetition of the first in the case of supply voltages. Similarly, one often meets the symbol  $V_{DD}$  for the positive supply to a CMOS (or COS/MOS) device, this being the supply to the drain. The negative supply to CMOS devices is normally represented by the symbol  $V_{SS}$ .

It should now be clear why  $V_{CEO}$  is the steady collector emitter voltage with the base open circuited. Similarly  $I_{CER}$  is the collector cut off current with a specified resistance between the base and emitter. It is current with the base and emitter joined, since either the base or emitter can be used as the reference electrode without any change when they are joined.

The parameters of individual devices vary from one device to another of the same type number. The typical value of a parameter such as transistor current gain is often quoted in data sheets by the abbreviation 'typ' after the quantity, but minimum and maximum values are also often quoted. In economical devices no maximum and minimum values may be quoted. In the case of breakdown voltages the minimum value applicable to any device of that type number is usually quoted so that the circuit designer knows that he can apply that value of voltage without danger of the device junction breaking down.

The above discussion gives the general principles of the way in which the symbols for various parameters are chosen. It is not complete, since we have not yet covered such items as current gain of a transistor or thermal characteristics of a device. However, these and other quantities will be covered in the following tables.

## Thermal characteristics

The symbols used for the following thermal quantities apply to all types of semiconductor device.

|           |   |
|-----------|---|
| $P_{tot}$ | total power dissipated within the device                  |
| $T_{amb}$ | ambient temperature                                       |
| $T_c$     | temperature of the case of the device                     |
| $T_j$     | temperature of the junction in the semiconductor material |
| $T_{mb}$  | temperature of the mounting base of the device (= $T_c$ ) |

|                         |   |
|-------------------------|---|
| $T_{\text{stg}}$        | storage temperature   |
| $\theta_h$              | thermal resistance of heat sink. (Units: °C/W)                              |
| $\theta_i$              | contact thermal resistance between the case of the device and the heat sink |
| $\theta_{j\text{-amb}}$ | junction to ambient thermal resistance                                      |
| $\theta_{j\text{-c}}$   | junction to case thermal resistance   |

## Symbols used mainly with diodes

|                  |  |
|------------------|--|
| $C_d$            | diode capacitance with reverse bias                                  |
| $C_f$            | diode capacitance with forward bias                                  |
| $C_j$            | capacitance of the junction itself                                   |
| $C_{\text{min}}$ | minimum capacitance (which occurs at the rated breakdown voltage)    |
| $C_o$            | diode capacitance at zero bias                                       |
| $f_{\text{co}}$  | cut off frequency of a varactor diode                                |
| $I_F$            | total dc forward current   |
| $i_F$            | instantaneous forward current  |
| $I_{F(AV)}$      | average forward current  |
| $I_{FM}$         | peak forward current   |
| $I_{FRM}$        | repetitive peak forward current                                      |
| $I_{FSM}$        | non-repetitive peak forward current occurring under surge conditions |
| $I_R$            | continuous reverse leakage current                                   |
| $i_R$            | instantaneous reverse leakage current                                |
| $I_{RRM}$        | repetitive peak reverse current                                      |
| $I_{RSM}$        | non-repetitive peak reverse current                                  |
| $I_Z$            | zener diode continuous operating current                             |
| $I_{ZM}$         | zener diode peak current   |
| $t_{\text{on}}$  | turn on time   |
| $t_{\text{off}}$ | turn off time  |
| $t_r$            | rise time  |
| $t_{rr}$         | reverse recovery time  |
| $t_s$            | storage time   |
| $V_F$            | steady forward voltage   |
| $v_F$            | instantaneous forward voltage  |
| $V_R$            | steady reverse voltage   |
| $v_R$            | instantaneous value of the reverse voltage                           |
| $V_{RM}$         | peak reverse voltage   |
| $V_{RRM}$        | repetitive peak reverse voltage                                      |
| $V_{RSM}$        | non-repetitive peak reverse voltage (on surges)                      |
| $V_Z$            | zener diode working voltage  |

## Symbols used mainly with transistors

|   |   |
|---|---|
| $C_{ob}$                                      | transistor output capacitance in the grounded base circuit  |
| $C_{oe}$                                      | transistor output capacitance in the grounded emitter circuit   |
| $f_T$   | transition frequency or gain-bandwidth product in common emitter circuit  |
| $h_{FE}$                                      | current gain in the grounded emitter circuit (or in the grounded base or grounded collector circuit).                               |
| $(h_{FB}, h_{FC})$                            |   |
| $h_{fe}$                                      | the increase in collector current divided by the small increase in the base current which produces it. (Small signal current gain.) |
| $I_B, I_C$<br>or $I_E$                        | the steady base, collector or emitter current.  |
| $I_{B(AV)}, I_{C(AV)}$<br>or $I_{E(AV)}$      | the average value of the base, collector or emitter current.  |
| $I_{CEX}, I_{CM}, I_{EM}$<br>or $I_{EM}$      | collector cut-off current in a specified circuit<br>peak value of collector, base or emitter current                                |
| $i_b, i_c$<br>or $i_e$                        | rms value of the alternating component of the current   |
| $I_{b(m)}, I_{c(m)}, I_{e(m)}$<br>or $I_{om}$ | peak value of the alternating component of the current  |
| $i_c, i_b$<br>or $i_e$                        | instantaneous value of the total current  |
| $i_c, i_b$<br>or $i_e$                        | instantaneous value of the alternating component of the current   |
| $I_{CBO}$                                     | collector cut off current with the emitter open circuited   |

|                           |   |
|---------------------------|---|
| $I_{CBS}$<br>or $I_{CES}$ | collector cut off current with emitter shorted to the base                                      |
| $I_{CEO}$                 | collector cut off current with the base open circuited  |
| $I_{CER}$                 | collector cut off current with a specified value of resistance between the base and the emitter |
| $I_{EBO}$                 | emitter cut off current with the collector open circuited                                       |
| $V_{BE(SAT)}$             | base-emitter saturation voltage   |
| $V_{(BR)}$                | breakdown voltage   |
| $V_{(BR)CBO}$             | collector to base breakdown voltage with emitter open circuited                                 |
| $V_{(BR)CEO}$             | collector to emitter breakdown voltage with base open circuited                                 |
| $V_{CB}$                  | collector-base voltage  |
| $V_{CBO}$                 | collector to base voltage with emitter open circuited   |
| $V_{CC}$                  | collector supply voltage  |
| $V_{CE}$                  | collector to emitter voltage  |
| $V_{CEO}$                 | collector to emitter voltage with base open circuited   |
| $V_{ce}$                  | collector to emitter rms voltage  |
| $V_{CE(SAT)}$             | collector to emitter saturation voltage   |
| $V_{EB}$                  | emitter-base voltage  |
| $V_{EBO}$                 | emitter-base voltage with collector open circuited  |
| $V_{eb}$                  | emitter-base rms voltage  |

## Symbols used mainly with FETS

|           |   |
|-----------|---|
| $I_D$     | steady value of the drain current                                       |
| $I_{DSS}$ | steady value of the drain current with the gate connected to the source |
| $I_m$     | peak drain current  |
| $I_G$     | steady gate current   |
| $I_S$     | steady source current   |
| $r_{DS}$  | drain to source (or channel) resistance                                 |
| $V_{DS}$  | steady drain to source voltage  |
| $V_{GS}$  | steady gate to source voltage   |

## Symbols used mainly with thyristors

|            |   |
|------------|---|
| $I_{FRM}$  | repetitive peak forward current.                          |
| $I_{FSM}$  | non-repetitive peak (surge) current                       |
| $I_{GD}$   | gate current which does not trigger the device            |
| $I_{GT}$   | gate trigger current                                      |
| $I_{GO}$   | gate turn off current                                     |
| $I_H$      | holding current required to maintain conduction           |
| $I_R$      | steady reverse leakage current                            |
| $I_{RG}$   | reverse gate current                                      |
| $I_{RRM}$  | repetitive peak reverse current                           |
| $I_{RSM}$  | non-repetitive peak reverse current (in surge conditions) |
| $I_T$      | steady anode-cathode 'ON' state current                   |
| $P_G$      | gate power  |
| $t_{gt}$   | gate controlled turn-on time                              |
| $t_{gt}$   | gate controlled turn-off time                             |
| $V_{(BO)}$ | breakover voltage   |
| $V_D$      | continuous off state voltage                              |
| $V_{FG}$   | forward gate voltage                                      |
| $V_{GT}$   | gate trigger voltage                                      |
| $V_R$      | steady reverse voltage                                    |

## Operational amplifier terms

**Bandwidth,  $\Delta f$ .** The frequency at which the gain falls by a factor of 0.7 relative to the gain at low frequencies.

**Common mode rejection ratio, CMMR.** The gain when a signal is applied to one of the inputs of the amplifier divided by the gain when the signal is applied to both the inverting and non-inverting inputs. It is usually expressed in dB.

**Frequency compensation.** An operational amplifier requires a capacitor to enable it to be used in circuits which are stable over a wide frequency range. Internally compensated operational amplifiers have this capacitor fabricated on the silicon chip, but an external capacitor must be used with other types of operational amplifier which do not contain an internal capacitor.

**Input bias current,  $I_{BIAS}$ .** The mean value of the currents at the two inputs of an operational amplifier.

**Input offset current,  $I_{OS}$ .** The difference in the two currents to the inputs of an operational amplifier. Normally much smaller than the input bias current.

**Input offset voltage,  $V_{OS}$ .** The voltage which must be applied between the two input terminals to obtain zero voltage at the output.

**Open loop voltage gain,  $A_{VOL}$ .** The amplifier gain with no feedback applied.

**Output resistance,  $R_O$ .** The small signal resistance seen at the output when the output voltage is near zero.

## Voltage regulator terms

**Dropout voltage,  $V_{DO}$ .** When the difference between the input and output voltages falls down below the dropout voltage, the device ceases to provide regulation.

**Foldback current limiting.** In regulators with foldback current limiting, the current will 'fold back' to a fairly small value when the output is shorted.

**Line regulation.** The change in the output voltage for a specified change in the input voltage.

**Load regulation.** The change in output voltage for a change in the load current at a constant chip temperature.

**Quiescent current,  $I_Q$ .** The current taken by the regulator device when it is not delivering any output current.

**Ripple rejection.** The ratio of the peak-to-peak ripple at the input of the regulator to that at the output. Normally expressed in dB.

## Monolithic timer terms

**Comparator input current.** The mean current flowing in the comparator input connection during a timing cycle.

**Timing capacitor,  $C_T$ .** This capacitor is normally connected between the comparator input and ground. The time taken for it to charge controls the delay time.

**Timing resistor,  $R_T$ .** This is the resistor through which the timing capacitor charges.

**Trigger current.** The current flowing in the trigger input connection, at the specified trigger voltage.

**Trigger voltage.** The voltage required at the trigger pin to initiate a timing cycle.

## Conclusions

Data sheets must be used intelligently and with much thought. Information on the conditions under which an entry in the data sheet is applicable is often stated in small print, but is of great importance. Data should always be thoroughly studied before a device is used for the first time, only then will you be able to fully understand the potential applications of the device.

Thus  $i_E$  is the instantaneous value of the total emitter current,  $i_{E(av)}$  the instantaneous value of the alternating component of the emitter current, and  $I_{E(AV)}$  the average (DC) value of the total emitter current. Other subscripts can be used in a similar way,  $I_F$  being the forward DC current with no signal,  $I_F$  the instantaneous forward current and  $I_{FM}$  the peak forward current.

ETI

# WE'RE OUT TO FINISH YOU OFF!

Rapitape #

eti PANEL TRANSFERS

MOD MAGS 1977 no 1

## GOOD AND PROPER!


... or at least your projects. If there is one thing which is impossible to do at home is lettering front panels to professional standards. At least until now. If you cast your eyes right a while you'll see our new panel transfers sheet, which has been carefully designed to allow you to do exactly that.

The transfers are easily rubbed down, and the two sheet set contains a mass of lettering and —uniquely—control scales for both rotary and slider pots.

Each sheet measures 180mm X 240mm and comes packed flat in a stiff cardboard envelope for protection. There should be enough for dozens of projects here - and the longer you wait the worse they'll look!

Send £1.75 (includes VAT and postage) for the two-sheet set to:

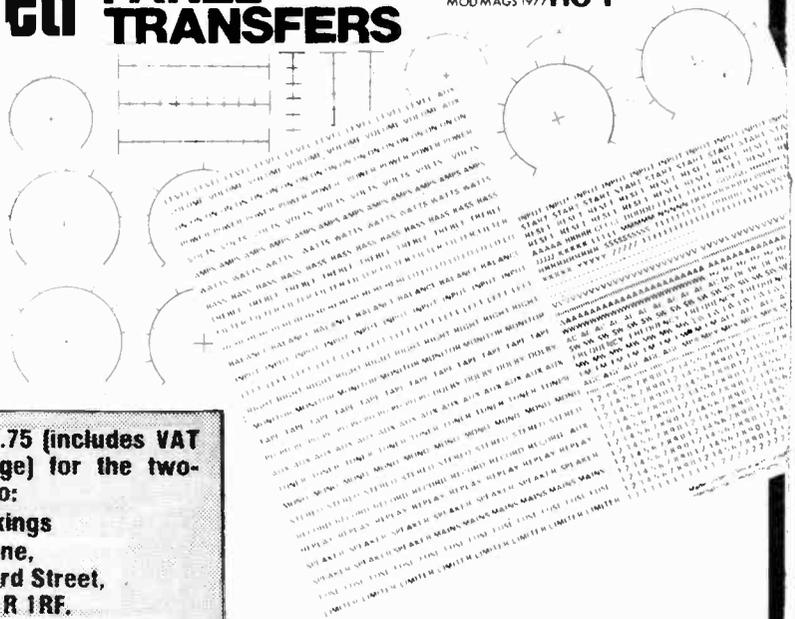Panel Markings  
ETI Magazine,  
25-27 Oxford Street,  
London W1R 1RF.



# Understanding Digital Electronics

## New teach-yourself courses



**Design of digital Systems** is written for the engineer seeking to learn more about digital electronics. Its six volumes — each A4 size — are packed with information, diagrams and questions designed to lead you step-by-step through number systems and Boolean algebra to memories, counters and simple arithmetic circuits, and finally to a complete understanding of the design and operation of calculators and computers.

### The contents of Design of Digital Systems include:

- Book 1** Octal, hexadecimal and binary number systems; conversion between number systems; representation of negative numbers; complementary systems; binary multiplication and division.
- Book 2** OR and AND functions; logic gates. NOT, exclusive OR, NAND, NOR and exclusive-NOR functions; multiple input gates; truth tables; De Morgans Laws; canonical forms; logic conventions; Karnaugh mapping; three-state and wired logic.
- Book 3** Half adders and full adders; subtractors; serial and parallel adders; processors and arithmetic logic units (ALUs); multiplication and division systems.
- Book 4** Flip flops; shift registers; asynchronous and synchronous counters; ring, Johnson and exclusive-OR feedback counters; random access memories (RAMs) and read only memories (ROMs).
- Book 5** Structure of calculators; keyboard encoding; decoding display data; register systems; control unit; program ROM; address decoding; instruction sets; instruction decoding; control program structure.
- Book 6** Central processing unit (CPU); memory organisation; character representation; program storage; address modes; input/output systems; program interrupts; interrupt priorities; programming; assemblers; computers; executive programs; operating systems and time sharing.



**Digital Computer Logic and Electronics** is designed for the beginner. No mathematical knowledge other than simple arithmetic is assumed, though the student should have an aptitude for logical thought. It consists of four volumes — each A4 size — and serves as an introduction to the subject of digital electronics. Everyone can learn from it — designer, executive, scientist, student, engineer.

Contents include: Binary, octal and decimal number systems; conversion between number systems; AND, OR, NOR and NAND gates and inverters; Boolean algebra and truth tables; De Morgans Laws; design of logic circuits using NOR gates; R-S and J-K flip flops; binary counters, shift registers and half adders.

**CAMBRIDGE LEARNING ENTERPRISES, UNIT 1, RIVERMILL SITE, FREEPOST, ST. IVES, HUNTINGDON, CAMBS. PE17 4BR, ENGLAND**  
**TELEPHONE: ST. IVES (0480) 67446**  
 PROPRIETORS: DRAYRIDGE LTD. REG. OFFICE: RIVERMILL LODGE, ST. IVES  
 REGD. IN ENGLAND No. 1328762

In the years ahead the products of digital electronics technology will play an important part in your life. Calculators and digital watches are already commonplace. Tomorrow a digital display could show your vehicle speed and petrol consumption; you could be calling people by entering their name into a telephone which would automatically look up their number and dial it for you.

These courses were written by experts in electronics and learning systems so that you could teach yourself the theory and application of digital logic. Learning by self-instruction has the advantages of being faster and more thorough than classroom learning. You work at your own pace and must respond by answering questions on each new piece of information before proceeding.

After completing these courses you will have broadened your career prospects and increased your fundamental understanding of the rapidly changing technological world around you.

**The six volumes of Design of Digital Systems cost only: £8.10**  
**And the four volumes of Digital Computer Logic and Electronics cost only: £4.60**  
**But if you buy both courses, the total cost is only: £12.00**

+ 90p. post & packing  
 + £1 post & packing

Price includes surface mail anywhere in the world — Airmail extra.

## Flow Charts & Algorithms

### HELP YOU PRESENT

safety procedures, government legislation, office procedures, teaching materials and computer programs by means of YES and NO answers to questions.

**THE ALGORITHM WRITER'S GUIDE** explains how to define the questions, put them in the best order and draw the flow chart, with numerous examples shown. All that students require is an aptitude for logical thought. Size: A5, 130 pages. This book is a MUST for those with things to say.

**£2.95** + 45p post & packing by surface mail anywhere in the world. Airmail extra.

### GUARANTEE

If you are not entirely satisfied your money will be refunded.

Cambridge Learning Enterprises, Unit 1 Rivermill Site, Freepost, St. Ives, Huntingdon, Cambs. PE17 4BR England.

Please send me the following books.

- ..... sets Digital Computer Logic & Electronics @ £5.50, p & p included
- ..... sets Design of Digital Systems @ £9.00, p. & p. included
- ..... Combined sets @ £13.00, p & p included
- ..... The Algorithm Writer's guide @ £3.40, p & p included

Name .....

Address .....

I enclose a cheque/PO payable to Cambridge Learning Enterprises for £ .....

Please charge my Access/Barclaycard/Visa/Eurocard/Mastercharge/Interbank account number .....


Signature .....

Telephone orders from credit card holders accepted on 0480-67446 (ansafone). Overseas customers should send a bank draft in sterling drawn on a London Bank.

# Hobby Electronics

Next  
Month


## 4-Channel Equaliser

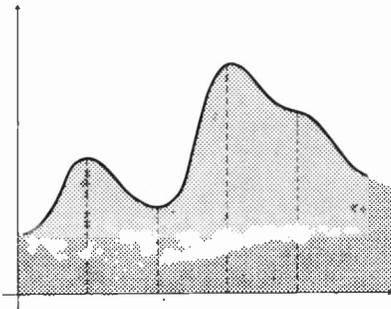

A fully-fledged graphic equaliser with four bands, allowing you to adjust the response of your Hi-Fi to suit the room it's in! Alternatively, this unit can be used as a really sophisticated tone control. This project was designed by a professional audio consultant especially for HE. We think it'll be a winner!




## Viewdata

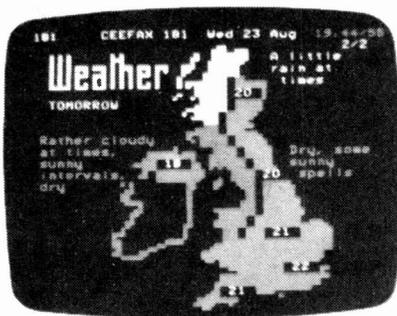

One of the most exciting developments in modern TV technology is the advent of data transmission and display. Viewdata is Britain's answer to advances which could mean shopping from the home, a computer terminal in every room or even the abolition of commuting!


## Slave Flash

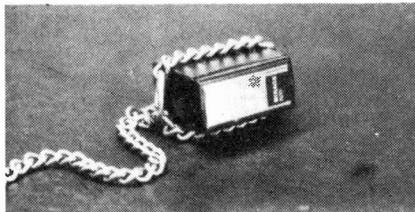

Using one flash gun is fairly straightforward — but how do you use two or more simultaneously?



## Touch Switch

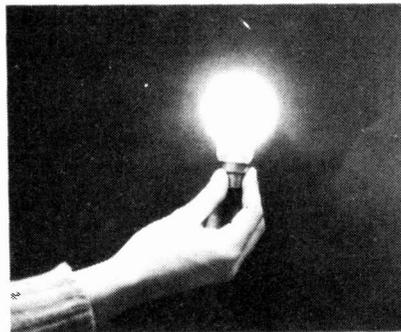

A switch with no moving parts! Just touch it and turn on the lights, motors or whatever turns you on. By the way, the above photo is not an illustration of the switch in action, but one of our staff having a bright idea.



## Holograms

Following on from the LASER article in this issue, we look into (!) holograms — what are they, how are they made and what use are they. This is a fascinating topic and one which is sure to make a big impact on all our lives in the future.

## Project Daedalus

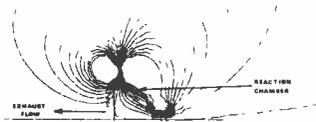


Fig. 9 Magnetic field created in the region of the vehicle

The British Interplanetary Society has just published a report which shows that interstellar flight by an un-manned vehicle is possible with modern technology. The report is nearly 200 pages of detailed drawings, calculations and specifications. We examine it clearly in detail.




## BASIC Programming

If you've ever wondered exactly what's involved in programming a computer, then this is for you. We look at BASIC — one of the most popular computer languages — and see what it's all about. This article will require no previous knowledge and will be much more than an introduction to the subject.



## Variwiper

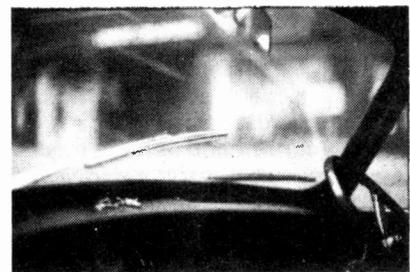

Ever been driving in one of those horrible drizzles which is too fine for the wipers to work properly? This circuit makes them repeat one sweep at pre-set time intervals — ideal for those conditions.


January issue will be on sale on December 8th

The items mentioned here are those planned for the next issue but circumstances may affect the actual content.
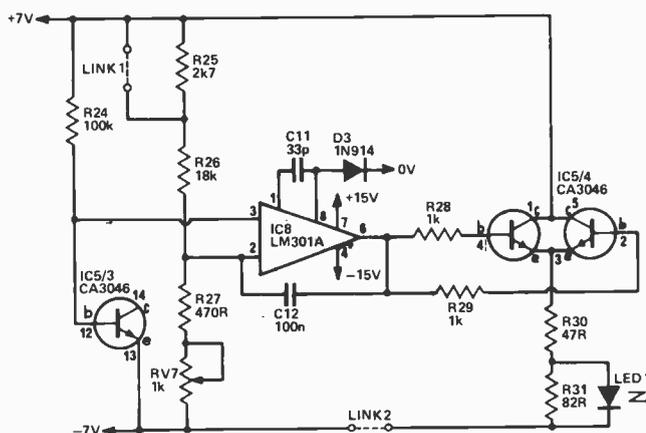
# TEMP STABILISED LOG CONVERTER

This design can be set up for either logarithmic or exponential operation and incorporates a neat heater circuit for temperature stability.

IN THE CONVENTIONAL musical scale, consecutive notes are not separated by the same frequency, but by the same ratio — the twelfth root of two. This is quite acceptable for most musical instrument manufacturers, except that in electronic music equipment it is easier to make oscillators which have an accurately linear frequency/control voltage characteristic. The keyboards of most music synthesizers give an output voltage of 1 V for each octave on the keyboard. This can easily be generated by a set of equal resistors between the contacts on each key and a voltage applied to each end (normally 5 V). However this means the oscillator is required to have an exponential frequency/control voltage response.



Below: the circuit diagram of the converter section. One channel only is shown here, the second — identical — uses the even components numbers. Above: the oven circuitry.


## Trouble

This is where the trouble usually starts. An exponential converter is normally used which relies for its operation on the relationship between current and voltage in a silicon diode or transistor. However, unless temperature stabilisation is used the oscillator will not stay in tune for very long. With this unit the transistor used is heated to around 55°C and stabilised at this temperature, eliminating the problem of thermal drift.


In the instrumentation field a lot of functions are displayed in dBs which are a logarithmic measurement. As this unit can be connected in either exp or log modes it is useful for this purpose also.

As the unit will normally be used with some other equipment, we have not described any mechanical housing.

| VALUES OF UNMARKED COMPONENTS |            |             |
|-------------------------------|------------|-------------|
|                               | LOG        | EXPONENTIAL |
| R3                            | 33k        | 390k        |
| R5                            | ∞          | 150k        |
| R13                           | ∞          | 100k        |
| R15                           | 22k        | 470k        |
| R17                           | 390k       | 33k         |
| RV3E                          | LINK       | 200k        |
| RV3L                          | 200k       | LINK        |
| LINKS REQUIRED                |            |             |
|                               | A-B<br>D-C | A-D<br>B-C  |

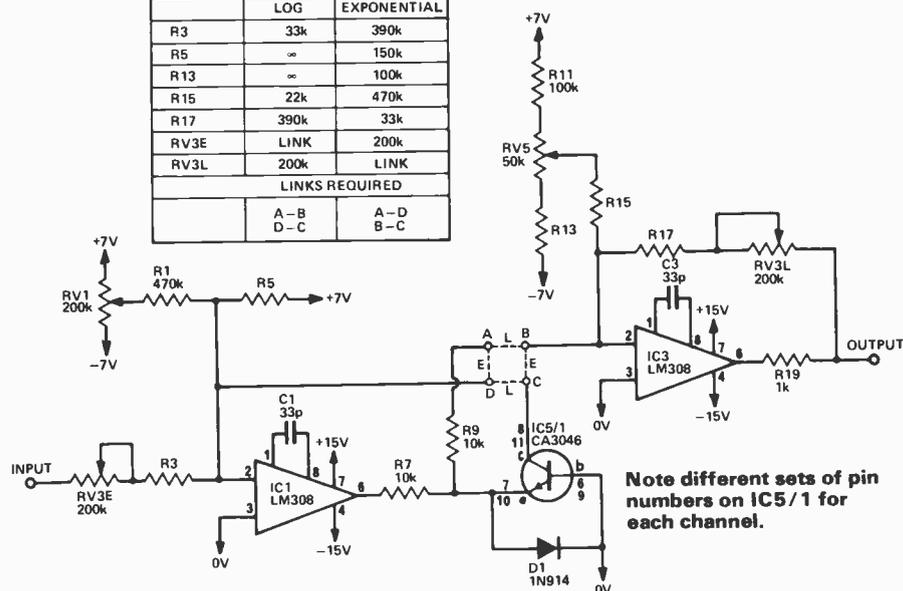

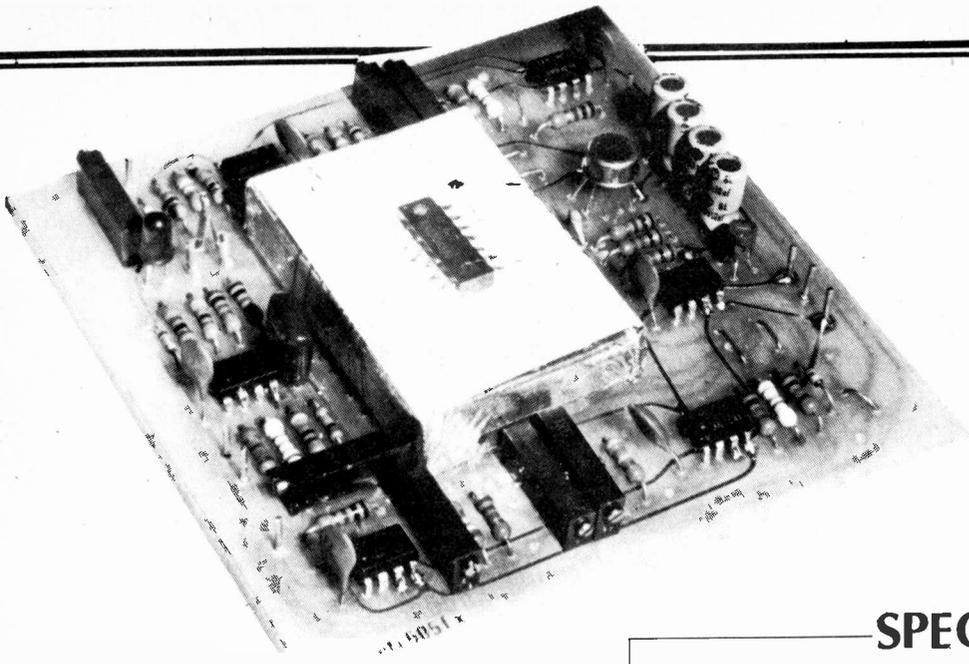Note different sets of pin numbers on IC5/1 for each channel.



The photo on the left shows the complete unit with the oven top removed to show IC5. Link 1 is made from a couple of valve socket pins in this prototype.

## SPECIFICATION

|  |  |
|--|--|
| <b>Transfer functions</b><br>exponential<br>log. | $V_{out} = 0.15625 \times 2V_{in}$<br>$V_{out} = \text{Ln}(V_{in}/0.15625)/\text{Ln}2$ |
| <b>Useful dynamic range</b>                      | 50dB or 8 octaves  |
| <b>Oven temperature</b>                          | approx. 55°C   |
| <b>Warm up time</b>                              | about 2 minutes  |
| <b>Power supply</b>                              | ± 10 to ± 15 volts   |

## HOW IT WORKS

This unit relies on the fact that the collector current of a transistor is exponentially related to the base voltage.

In the log mode the collector of the transistor is linked back to the input of IC1. In this way the collector current is proportional to the input voltage and therefore the voltage on its emitter is logarithmically related to the input voltage. This voltage is then amplified and level shifted by IC3 to give the desired output.

In the exponential mode the 10k resistor R9 is linked back to the input of IC1 and the voltage on the emitter of the transistor is proportional to the input voltage; the collector current is exponentially related to the input voltage. This current is converted to a voltage by IC3.

All this works well provided the transistor is at a constant temperature. Compensation can be made by using other junctions and thermistors, however even the self-heating effect of the transistors can affect linearity. The transistors we have used are part of a transistor array IC which has three individual NPN transistors and a differential pair. We heat the chip up by dissipating heat in the differential pair while measuring the base-emitter voltage of one of the individual transistors. IC8 is used to compare this voltage to one set by the divider R25, 26, 27 and RV7. The base-emitter voltage is normally about 0.67 V at 20°C and drops about 2.2 mV per degree above this temperature. IC8 then stabilises the chip temperature to about 35°C above the temperature at which it was initially calibrated. As it warms up the current in the transistors will fall and when hot the voltage drop across R31 will be low enough that the LED will extinguish. The transistor array is housed in a polystyrene housing to conserve heat.

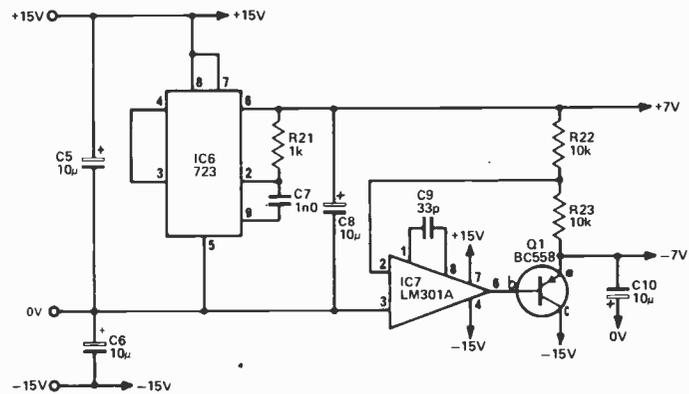


Fig. 1b. The power supply section which supplies the stable ± 7 V needed for the bias and adjustment controls.

The only difference between the assembly of this board and any other is the oven and the connections to the transistor array package. The oven is made out of two pieces of polystyrene about 55 x 35 x 12mm. The outside of the oven should be covered with aluminium foil to help reduce heat loss. The aluminium itself should be covered with a layer of adhesive tape where the leads can touch. A piece of thick paper should be used between the oven and the pcb to insulate the tracks.

## Half Baked

The centre of the oven should be hollowed slightly to hold the IC (bend the leads out straight as shown in the photo; a hot soldering iron is the easiest method. Do not remove more than necessary. Now solder a 40 mm length of thin copper wire (a single strand of multistrand cable is best) to each pin, then with the base of the oven in position, sit the IC in the oven and connect the leads to the appropriate holes. If a small amount

## PARTS LIST

RESISTORS all 2%, 5W  
 R1, 2 470k  
 R3-R6 see table 1  
 R7-R10, 22, 23 10k  
 R11, 12, 24 100k  
 R13-R18 see text  
 R19-R21, 28, 29 1k  
 R25 2k7  
 R26 18k  
 R27 470R  
 R30 47R  
 R31 82R

POTENTIOMETERS  
 RV1-RV4 200k multitrn trimmer  
 RV5, 6 50k multitrn trimmer  
 RV7 1k multitrn trimmer


CAPACITORS  
 C1-C4 33p ceramic  
 C5, 6 10u 25 V electrolytic  
 C7 1n0 polyester  
 C8 10u 25 V electrolytic  
 C9 33p ceramic  
 C10 10u 25 V electrolytic  
 C11 33p ceramic  
 C12 100n polyester

SEMICONDUCTORS  
 IC1-IC4 LM308  
 IC5 CA3046  
 IC6 723  
 IC7, 8 LM301A

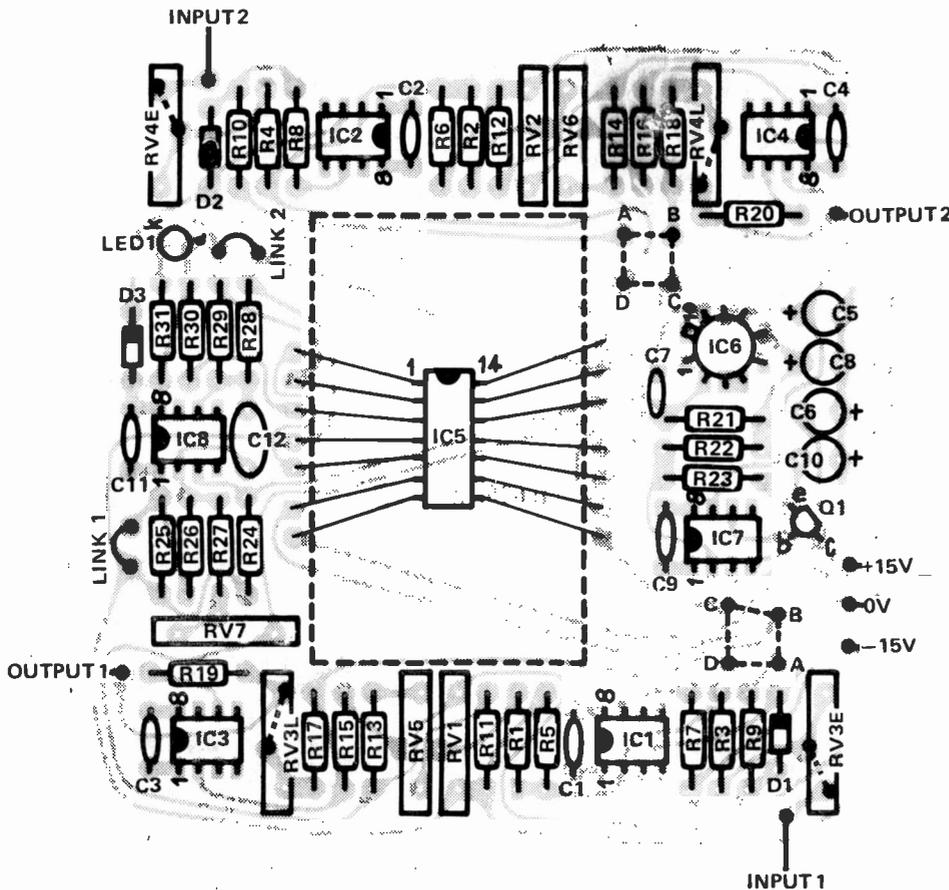Q1 BC558

D1-D3 1N914  
 LED T1L 209

MISCELLANEOUS  
 PCB  
 Polystyrene foam for oven



Component overlay for the complete log converter project.

## BUYLINES

The project depends upon the CA 3046 device — near equivalents will probably **not** function. The CA 3046 itself is readily available — we

found it in both the Marshalls and Stevenson catalogues when we looked for it! Initial reaction here had been that it would be difficult to obtain.

of epoxy cement is placed under the oven it will stay in position. Now fit the top of the oven and secure with a piece of adhesive tape until it has been checked out. It finally can be cemented with epoxy adhesive.

The potentiometer values chosen are a compromise between ease of adjustment and the ability to compensate different transistors. If the potentiometer does not have enough range then the series resistor will have to be varied. We have

specified 2% resistors throughout to obtain a better temperature coefficient than is possible with conventional 5% resistors. It will not help to select out of normal 5% types.

### Calibration

The equipment needed comprises an accurate digital voltmeter and a variable power supply with a fine voltage control. The + 7 V rail can be used for this with a multi-turn potentiometer.

## CALIBRATION TABLE

| A       | B       |
|---------|---------|
| -3.00 V | 19.5 mV |
| -2.00 V | 39 mV   |
| -1.00 V | 78 mV   |
| 0.00 V  | 156 mV  |
| +1.00 V | 312 mV  |
| +2.00 V | 625 mV  |
| +3.00 V | 1.25 V  |
| +4.00 V | 2.50 V  |
| +5.00 V | 5.00 V  |
| +6.00 V | 10.00 V |

This table shows the relationship between the input and output. In the exponential model A is the input with B the output while in the log mode B is the input and A the output.

## Oven Control

1. Before switching on, remove link 2 and fit link 1.
2. Switch on and monitor the voltage on the output of IC8 (pin 6).
3. Adjust RV7 until the voltage is about  $-5$  V. The potentiometer is sensitive in this area but the actual voltage is not critical.
4. Remove link 1 and fit link 2. The LED should now come on for about two minutes before slowly going out. This indicates that the oven is stable.

## Calibration of Log Mode

1. Set 0 V on the input.
2. Monitor the voltage on the junction of R7 and R9.
3. Adjust RV1 to give a negative voltage on this point. Now adjust RV1 slowly until the voltage just switches positive.
4. Set 0.15625 V in the input.
5. Adjust RV5 to give 0 V output.
6. Set 5.00 V on the input.
7. Adjust RV3 to give 5.00 V output.
8. Set 1.25 V on the input and check the output voltage. It should be 3.00 V. If it is higher go back to step 4 except adjust RV5 to give  $-0.010$  V and use RV1 to bring it back to zero. Continue with step 6, 7 and 8. If the output voltage at 1.25 V input is less than 3.00 V adjust RV5 to give  $+0.010$  V instead of  $-0.010$  V.



Continue until all three points are correct.

## Calibration of Exponential Mode

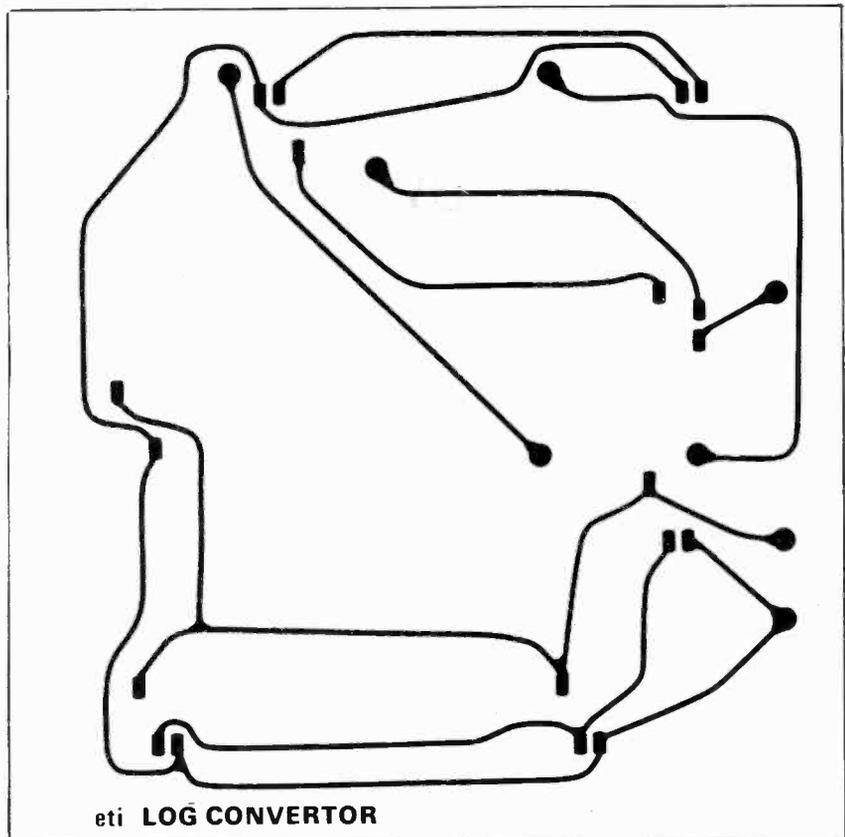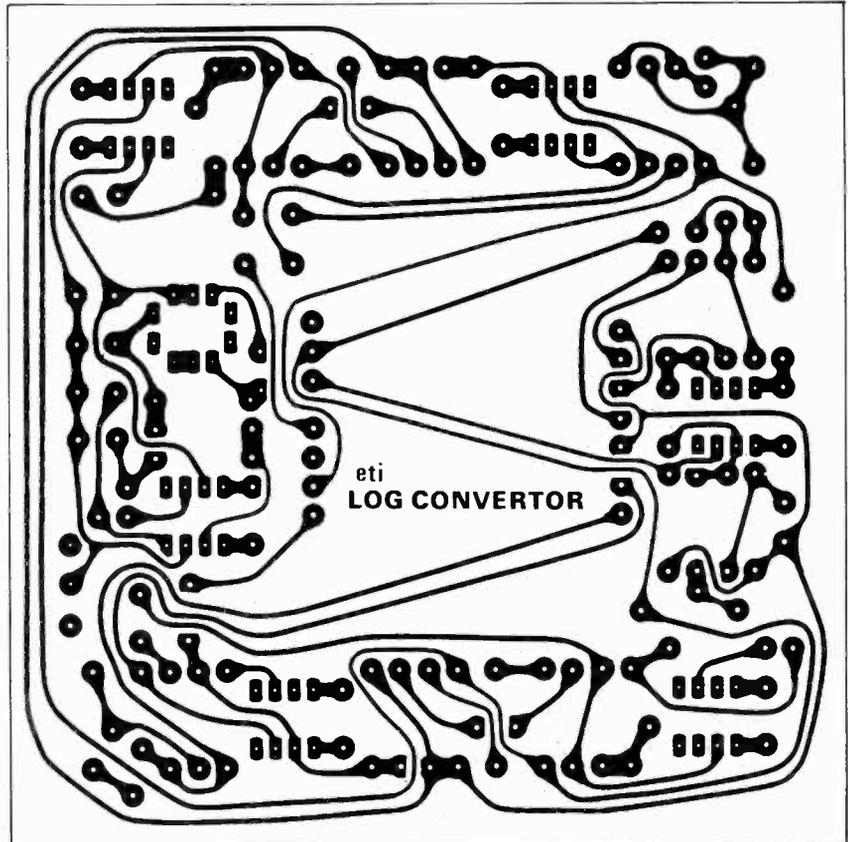1. Place a link between the junction of R7 and R9, and 0V.
2. Adjust RV5 to give 0.00 V output. Remove the link.
3. With 0.00 V input, adjust RV1 to give 0.15625 V output.
4. With 5.00 V input, adjust RV3E to give +5.00 volts output.
5. Check output voltage with 3.00 V input. It should be 1.25 V.
6. If high repeat steps 1-5 except output. If low, repeat steps 1-5 except adjust RV5 to give about 10mV output.


ETI

Both sides of the PCB shown full size. On the top is the underside and the pattern beneath that is for the topside of the board.



**BULK PURCHASE — EXCLUSIVE TO HENRY'S  
ALLOWS US TO SELL AT SUCH FANTASTIC PRICES!**

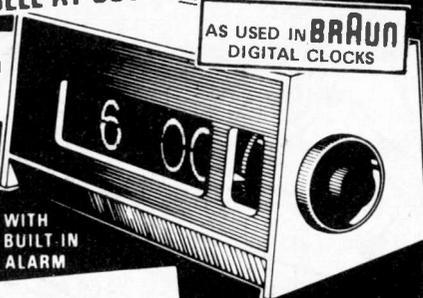**QUALITY ITEMS**  
Compare performance and specification with units costing 3 times as much!



AS USED IN **BRAUN**  
DIGITAL CLOCKS

**DIGITAL**  
24 HOUR  
**CLOCK**

WITH BUILT IN ALARM

- SILENT RUNNING
- LARGE ILLUMINATED NUMERALS
- AC MAINS ● SIZE 6 3/4 x 2 1/4 x 2 3/4



MECHANISM ONLY



Assemble it in an evening!  
MECHANISM & CASE  
Inc. assembly instructions



Modern Styling  
COMPLETE UNIT

**£5.00** **£6.99** **£7.99**

THREE FOR £13.50    THREE FOR £20    THREE FOR £23

POST & VAT INCLUSIVE

Send cheque, P.O./M.O. for the correct amount which includes VAT and P & P or pay by Access/Barclaycard. Send name/card number (if applicable) and address to:

**HENRY'S RADIO**  
404 EDGWARE ROAD,  
LONDON W2 1ED

EXPORT ENQUIRIES INVITED

AVAILABLE ONLY FROM

**HENRY'S**  
Radio


DELIVERY FROM STOCK

**DISCOUNT  
BOXES INSTRUMENT CASES AND COMPONENTS**




Aluminium box with lid and screws.

| L             | W | H |      |
|---------------|---|---|------|
| 3 x 2 x 1     |   |   | 44p  |
| 4 x 3 x 1 1/2 |   |   | 52p  |
| 4 x 3 x 2     |   |   | 60p  |
| 6 x 4 x 2     |   |   | 67p  |
| 6 x 4 x 3     |   |   | 78p  |
| 8 x 6 x 2     |   |   | 105p |
| 8 x 6 x 3     |   |   | 118p |

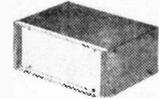

Professional black P.V.C. coated case with satin anodised front panel and trim.

| W              | D | H |      |
|----------------|---|---|------|
| 9 x 6 x 3      |   |   | 443p |
| 9 x 6 x 4 1/2  |   |   | 479p |
| 9 x 6 x 6      |   |   | 512p |
| 12 x 8 x 3     |   |   | 544p |
| 12 x 8 x 4 1/2 |   |   | 618p |
| 12 x 8 x 6     |   |   | 660p |

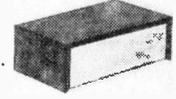

Black P.V.C. top with U-shaped aluminium chassis.

| L                 | W | H |      |
|-------------------|---|---|------|
| 6 x 4 1/2 x 2     |   |   | 134p |
| 6 x 4 x 3 1/2     |   |   | 145p |
| 8 x 5 1/2 x 2 1/2 |   |   | 165p |
| 10 x 6 1/2 x 3    |   |   | 215p |

|            |     |           |     |          |      |
|------------|-----|-----------|-----|----------|------|
| AD161/2 MP | 83p | BC347A    | 14p | BF274    | 24p  |
| OC36       | 60p | BD183     | 80p | BF394    | 30p  |
| BC108A     | 9p  | BD263A    | 42p | BF422    | 20p  |
| BC148      | 8p  | BF137     | 24p | LM741C   | 17p  |
| BC149C     | 9p  | BF194     | 10p | TBA120A  | 75p  |
| BC154      | 9p  | BF195     | 10p | SN76013N | 120p |
| BC171B     | 9p  | BF198     | 21p | SN76033N | 120p |
| BC172B     | 9p  | BF200     | 21p | SN76110N | 75p  |
| BC183A     | 10p | BF255     | 23p | SN76131N | 150p |
| BC30B      | 15p | BF256 FET | 33p | SN76660N | 75p  |

Ceramic Filters SEF 6. OMA 40p. 1V Colour Crystals 4.433619 MHz £1.50.

| AXIAL ELECTROLYTIC |     |          |     |
|--------------------|-----|----------|-----|
| 220/16v            | 11p | 22/50v   | 8p  |
| 330/10v            | 12p | 33/63v   | 9p  |
| 330/25v            | 10p | 47/16v   | 7p  |
| 10/25v             | 5p  | 330/63v  | 16p |
| 15/16v             | 6p  | 470/16v  | 15p |
| 22/10v             | 5p  | 470/40v  | 15p |
| 22/16v             | 6p  | 1000/25v | 18p |
| 22/25v             | 7p  | 2000/30v | 20p |
| 33/35v             | 8p  |          |     |
| 33/50v             | 9p  |          |     |
| 47/40v             | 10p |          |     |
| 100/10v            | 8p  |          |     |
| 100/63v            | 10p |          |     |

MIXED PACK OF 100 AXIAL AND P.C. ELECTROLYTICS 300p

DISCOUNT ON ALL ORDERS OVER £5 5% OVER £10 10% OVER £20 15% OVER £30 20%

All prices include post and packing


All orders under £1, please add 20p for handling charge

**HARRISON BROS., P.O. BOX 55, Westcliff-on-Sea, Essex**  
SS0 7LQ Phone: Southend 32338

**TOTAL AMPLIFICATION FROM CRIMSON ELEKTRIK**

**WE NOW OFFER THE WIDEST RANGE OF SOUND PRODUCTS**

**STEREO PRE-AMPLIFIERS**

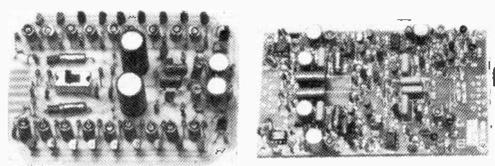

MC 1

CPR 1

**CPR 1—THE ADVANCED PRE-AMPLIFIER**

The best pre-amplifier in the U.K. The superiority of the CPR 1 is probably in the disc stage. The overload margin is a superb 40dB, this together with the high slewing rate ensures clean top, even with high output cartridges, tracking heavily modulated records. Common-mode distortion is eliminated by an unusual design. R.I.A.A. is accurate to 1dB; signal to noise ratio is 70dB relative to 3.5mV, distortion < 0.05% at 30dB overload 20kHz. Following this stage is the flat gain/balance stage to bring tape, tuner, etc. up to power amp signal levels. Signal to noise ratio 86dB, slew-rate 3V/μs; T.H.D. 20Hz — 20kHz < 0.08% at any level F.E.T. muting. No controls are fitted. There is no provision for tone controls. CPR 1 size is 138 x 80 x 20mm. Supply to be ±15 volts.

**MC 1 PRE-AMPLIFIER**

Suitable for nearly all moving-coil cartridges. Sensitivity 70/170μV switchable on the p.c.b. This module brings signals from the now popular low output moving-coil cartridges up to 3.5mV (typical signal required by most pre-amp disc inputs). Can be powered from a 9V battery or from our REG 1 regulator board.

**REG 1 — POWER SUPPLY**

The regulator module, REG 1 provides 15-0-15v to power the CPR 1 and MC 1. It can be used with any of our power amp supplies or our small transformer TR 6. The power amp kit will accommodate it.

**POWER AMPLIFIERS**



It would be pointless to list in so small a space the number of recording studios, educational and government establishments, etc., who have been using CRIMSON amps satisfactorily for quite some time. We have a reputation for the highest quality at the lowest prices. The power amp is available in five types, they all have the same specification: T.H.D. typically 0.1% any power, 1kHz 8 ohms; T.I.D. insignificant; slew rate limit 25V/μs; signal to noise ratio 110dB; frequency response 10Hz-35kHz. — 3dB; stability unconditional; protection drives any load safely, sensitivity 775mV (250mV or 100mV on request), size 120 x 80 x 25mm.

**POWER SUPPLIES**

We produce suitable power supplies which use our superb TOROIDAL transformers only 50mm high with a 120-240 primary and single bolt fixing (includes capacitors/bridge rectifier)

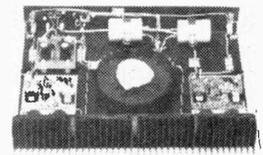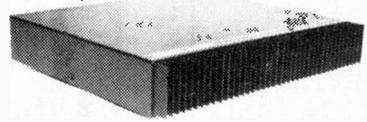**POWER AMPLIFIER KIT**

The kit includes all metalwork, heatsinks and hardware to house any two of our power amp modules plus a power supply. It is temporarily styled and its quality is consistent with that of our other products. Comprehensive instructions and full back-up service enables a novice to build it with confidence in a few hours



| POWER AMPLIFIER MODULES   |        |        |        |
|---|--------|--------|--------|
| CE 608 60W/8 ohms 35-0-35v  |        | £16.30 |        |
| CE 1004 100W/4 ohms 35-0-35v  |        | £19.22 |        |
| CE 1008 100W/8 ohms 45-0-45v  |        | £23.22 |        |
| CE 1704 170W/4 ohms 45-0-45v  |        | £28.12 |        |
| CE 1706 170W/8 ohms 60-0-60v  |        | £31.90 |        |
| TOROIDAL POWER SUPPLIES   |        |        |        |
| CPS1 for 2 x CE 608 or 1 x CE 1004  |        | £14.47 |        |
| CPS2 for 2 x CE 1004 or 2/4 x CE 608  |        | £16.82 |        |
| CPS3 for 2 x CE 1008 or 1 x CE 1704   |        | £17.66 |        |
| CPS4 for 1 x CE 1008  |        | £15.31 |        |
| CPS5 for 1 x CE 1708  |        | £22.68 |        |
| CPS6 for 2 x CE 1704 or 2 x CE 1708   |        | £23.98 |        |
| HEATSINKS   |        |        |        |
| Light duty, 50mm, 2 C/W   |        | £1.30  |        |
| Medium power, 100mm, 1.4 C/W  |        | £2.20  |        |
| Disc/group, 150mm, 1.1 C/W  |        | £2.85  |        |
| Fan, 80mm, state 120 or 240v  |        | £18.50 |        |
| Fan mounted on two drilled 100mm heatsinks, 2 x 4 C/W, 65 C max. with two 170W modules  |        | £29.18 |        |
| Thermal cut-out, 70 C   |        | £1.90  |        |
| POWER AMP KIT   |        | £32.40 |        |
| PRE-AMPS:   |        |        |        |
| These are available in two versions — one uses standard components, and the other (the S) uses MO resistors where necessary and tantalum capacitors |        |        |        |
| CPR1  | £29.49 | CPRIS  | £39.98 |
| MCI   | £18.50 | MCIS   | £28.49 |
| POWER SUPPLY:   |        |        |        |
| REG1  | £8.75  | TR6    | £1.75  |
| BRIDGE DRIVER, BDI  |        |        |        |
| Obtain up to 340W using 2 x 170W amps and this module, BDI  |        | £5.40  |        |

**CRIMSON ELEKTRIK**

1A STAMFORD STREET, LEICESTER LE1 6NL. Tel. (0533) 537722

All prices shown are UK only and include VAT and post COD 90p extra, £100 limit. Export is no problem, please write for specific quote. Send large SAE or 3 International Reply Coupons for detailed information

# microfile.....

**This month dynamic Gary (mines a pint) Evans goes random, ROMs the seas as a pirate and plays strange games with a T.V., but still finds time to visit North London.**

BEING CAUGHT PIRATING software could lead to all sorts of unpleasantness—boys in blue or more likely the boys in black (the legal eagles) looking for a large fee in some test case. At any rate copying, or rather being caught copying, software that someone, somewhere is willing to protect is something to avoid. It's for this reason that the guys at Transam — they who supply kits for the Triton — suffered a few nervous twitches when they heard that someone called Dobbs on the phone and he wanted to have a few words with them.

Now the BASIC that was used in the Triton has been around for some time. When development of the computer started we realised we could not undertake to write an 8080 interpreter from scratch and we looked around for something that was "in the public domain". The listing of an interpreter that appeared in Dr. Dobbs journal seemed to us to be just the thing we wanted — had we made a dreadful mistake.

Well gentle reader (I'm an Asimov fan) as it turned out we need not have worried at all. On picking up the phone, instead of some irate, distant American voice a softspoken northerner (north of England that is) greeted the ear.

This Dobbs had nothing to do with publishing a software journal working — as it turned out — for British Rail. He wanted to order a Triton.

Relief all round — is there a Mr. Byte in the house. What the manufacturers produce today, industry uses the next day and we, the amateurs, use the day after that and what the manufacturers are producing now are 16 bit MPUs. Intel, Motorola, Zilog Texas — everybody seems to have caught the 16 bit bug.

The first small system for the Home Office to use a 16 bit beast is almost certain to be the long awaited, and much talked about, Texas machine. Just what overnight "quantum jump" in performance these 16 bit based systems are going to provide, remains to be seen — but at least we should have something with a bit more to offer in terms of throughput and facilities than the current crop of 8 bitters. At what cost penalty will become evident over the next year or so.

Dynamic RAMs are very cheap, are they not? A couple of systems in use in this country feature such devices — the TRS-80, although here any cost savings do not seem to be passed on to the end user, and the NASCOM.

The more extensive use of dynamic RAM in small systems is probably a hang over from the days when it was all anybody could do to get a dynamic memory card up and running. There is no doubt that a dynamic card

can be a real pig to fault find. So many things have to happen at exactly the right time for the system to work at all. Unless some very sophisticated diagnostic equipment is available, it could prove almost impossible to decide what is wrong.

With the current crop of dynamic RAM controllers, however, hopefully there will be so little margin for error that we shall start to see nice cheap 4K and 16K memory expansion systems.

One example of a RAM controller that seems to do it all is the Intel 8202 — I have not yet managed to get a data sheet for this device but when I do I'll let you know just what it can do. In the meantime, if any of you have played around with dynamic devices, perhaps you'll let me know how you got on.

The North London Hobby Computer Club seems to be going from strength to strength. I was at their second meeting a while back and there was standing room only in the two rooms occupied by the club for demonstrating on the PET and the Triton. A continuing program of interesting talks and demonstrations is planned and if you live in North London, is recommended that you go along to the North London Poly in the Holloway Road and see what is going on for yourself.

Mine of Information Ltd is a company that is out to contest the high prices charged for many of the American microcomputer books brought over to this country. To quote from their literature "some worthwhile books are distributed by companies with exclusive European or British rights; there is a temptation to capitalize on the monopoly by increasing prices. In these circumstances Mol has to charge its customers more than is reasonable! Mol is taking action to contest the high prices. (When the choice of books is wider there will be no need to buy from such suppliers)."

A fresh attitude, as I can think of at least one outfit which must be making a mint from a number of exclusive titles sold at a high mark up. Some increase in cost from a straight \$70 £ conversion is acceptable — to quote Mol again — "It means extra hassle and expense to bring books to Britain" — but not as much expense and hassle as some would have us believe.

I wish Mol luck in their campaign and if you would like their lists send an SAE to

Mine of Information Ltd  
1 Francis Avenue  
St. Albans  
AL3 6BL

By the way members of the North London Computer Club get 10% off the prices in the list — yet another reason to pay a visit to the club. ▶

# NEWS: Microfile

The trend in America at the moment, or at least one of the trends, is for the home computer and the TV games to meet in a sort of common ground. One example of such a product is the Bally Arcade "box". The machine features a calculator style keyboard with slot for a Bally cartridge as well as sockets into which a number of accessories can be plugged, these include the two hand controllers supplied with the basic machine.

The machine features a number of built in games including the excellent gunfight which many of you may have seen in the arcades over here. This game produces good high resolution graphics in colour as well as a repertoire of musical sounds.

By plugging a ROM cartridge into the front panel socket additional games can be played on the machine and if a BASIC cartridge is used the Arcade is converted to a computer running the familiar TINY BASIC as per the TRITON.

Z80 based, the Arcade is supported by 8k of ROM to store the resident games and 4K of RAM which acts mainly as a screen memory.

The Bally Arcade is not the only product to appear in this area. Magnavox has the "Dyssey 2" machine from Intertec and it's rumoured, Atari are ready to launch something into this market.

ETI

## LINES FROM OUR VAST STOCKS—IMMEDIATE DELIVERY

All below manufacturers' prices — all new stocks. Quantity discounts — export enquiries invited. Postage & packing 35p per order.

**CALCULATOR CHIPS** General instrument GIMT4 on at-static foam 24 pin D.I.L. socket for use with Bowmar display £1.50 ea. Pack of 25 chips £25. 100 for £80. 500 for £350.

**BOWMAR 9 DIGIT CALCULATOR DISPLAY** with PC connector 0.2 digits. Common cathode with red bezel £1.25 ea. 10—£10.

**TEXAS 19** gold-plated snap key contact on gold-plated P.C. board. Size 70x80x2mm 75p ea. ORP12 light dependent resistance (Eq = RPY30). 2 for £1. 10—£4. 100—£35.

**FAIRCHILD FND100.15** 7 segment display C cathode 50p, 10 for £4.50, 100 for £40.

**TBA 120A** T.V. I.C. amplifier Siemens 75p, 10—£6. 100—£50, 1000—£350.

**BECKMAN 500** kcs Triggerable clocking oscillator for use with calculator chips 5v supply with circuit £1. 10 for £8. 100 for £65.

**BURROUGHS 9 DIGIT** Panapac calculator display 7 segment 0.25 digits. Neon type with red bezel socket and data. £2.25 ea. 10 for £20.

**ALMA PUSHBUTTON** high reliability reed switches. Push to make 18x27x18mm 40p ea. 10 for £3.50, 100 for £33.

**SMITHS INDUSTRIES** Audible warning devices 6-12 volts. 2 transistors 30x10mm encapsulated 50p ea. 10 for £4. 100 for £30.

**HONEYWELL PROXIMITY DETECTOR** integral amplifier 8v D.C. £2.50 ea. 10 for £20, 100 for £175.

**OSMOR CHANGE OVER REED RELAY** 12v coil 20mA & operating current 55x17x13mm 75p ea. 10 for £5, 100 for £45, 1000 for £400.

**MAINS TRANSFORMERS** (miniature) all with 240v primary.

|                                | ea    | 10  | per |
|--------------------------------|-------|-----|-----|
| 12 volt 100 m/amp              | ea    | 10  | 100 |
| 10x40x42 m/m                   | 85p   | 8   | £80 |
| 12-0-12v 100 m/amp 28x25x27mm  | £1.20 | £10 | £80 |
| Value output 40 1.61x15x42 m/m | 75p   | £6  | £50 |
|                                | 95p   | £8  | £65 |

20-0-20v 100 m/a

**SOLDER** (multicore type) Servisol

10 metres for £1.50 metres for £4. 100 m £7

**RADIATION DETECTOR** Quartz Fibre Dosimeters. Pen type with clip with lens and scale 0-50R. Originally over £5. **OUR PRICE 95p EACH.** 10 for £8. 100 for £80. 1,000 for £500.

**CLOCKING OSCILLATOR** (Pye-Dynamics), thick film 1MHz supply 5v 19x25x6mm 85p, 10 for £7. 100 for £60.

**TV TUNERS** by GEC UHF 38 mcs size 34x24x14 £2.50 ea. 10 for £20, 100 for £175.

**T.V. SOUND TUNER KIT.** Through your F.M. tuner. Kit of parts with instructions £5.50. Ready-built, tested, £7.00.

**JOYSTICK CONTROLS.** (Ideal for TV Games, model control), sturdy constructed compact giving full 360 movement and control. Each unit fitted 4-off 100K linear controls. Part £4.00.

**T4/RF LONG-MEDIUM & F/M TUNER** WITH MC1310 DECODER \* 5-BUTTON SELECTOR SWITCHES \* INPUT SELECTORS FOR GRAM AND TAPE \* Supplied complete with FRONT-END TUNER AND FERRITE AERIAL \* SIMPLE INTERCONNECTIONS \* Size 1913x6mm.

**THIS QUALITY AMPLIFIER £10.95 WITH CIRCUIT**

**POWER UNIT KIT FOR ABOVE MODELS 25/28 VOLTS £2.95**

**TAPE HEADS** 1/4 track. Record Marriot XRPS36 1.5. XES11 erase £1.25. XRPS 19 £3.50.

**MULLARD TUNER MODULES** with data. LP1171 combined AM/FM IF strip — £3.50 \* LP1179 FM front end with AM tuning gang, used with LP1171 — £3.50 \* LP1171 and 79 pair — £5.75 \* LP1157 complete AM strip — £2.05 \* 10 pairs for £50, 100 pairs for £400.

**SEVEN DIGIT MINIATURE COUNTER** by Durant 12-24 volts D.C. 3 Watts. Size 40x25HX 55L mm £1 each, 10 for £9, 100 for £80.

**2N3055A T30 POWER 80 VOLT VERSION.** 10 for £2.50, 100 for £22.00, 1,000 for £200.

**TRANSISTORS BY BULLARD, TEXAS, FAIRCHILD**

| Price ea per | 10    | 100   | 500   | 1,000 |
|--------------|-------|-------|-------|-------|
| AC128        | 0.230 | 0.200 | 0.180 | 0.150 |
| AD149        | 0.750 | 0.650 | 0.550 | 0.490 |
| AD161        | 0.380 | 0.330 | 0.290 | 0.250 |
| AD162        | 0.380 | 0.330 | 0.290 | 0.250 |
| BC107        | 0.100 | 0.085 | 0.075 | 0.065 |
| BC109        | 0.110 | 0.095 | 0.080 | 0.070 |
| BC109C       | 0.120 | 0.100 | 0.085 | 0.075 |
| BC114        | 0.080 | 0.065 | 0.050 | 0.040 |
| BC132        | 0.080 | 0.065 | 0.050 | 0.040 |
| BC153        | 0.085 | 0.070 | 0.055 | 0.045 |
| BC172        | 0.075 | 0.060 | 0.050 | 0.040 |
| BC173        | 0.075 | 0.060 | 0.050 | 0.040 |
| BC205        | 0.070 | 0.060 | 0.050 | 0.040 |
| BC208        | 0.075 | 0.060 | 0.050 | 0.040 |
| BC209        | 0.075 | 0.060 | 0.050 | 0.040 |
| BD181        | 0.600 | 0.500 | 0.440 | 0.400 |
| BD182        | 0.700 | 0.600 | 0.500 | 0.400 |
| BF181        | 0.240 | 0.16  | 0.140 | 0.125 |
| BF50         | 0.180 | 0.200 | 0.185 | 0.160 |
| BF51         | 0.180 | 0.160 | 0.140 | 0.125 |
| BF54         | 0.220 | 0.195 | 0.175 | 0.150 |
| BFY90        | 0.750 | 0.680 | 0.630 | 0.550 |
| BU205        | 1.00  | 0.900 | 0.800 | 0.750 |
| BU208        | 1.250 | 1.100 | 1.000 | 0.900 |
| BY127        | 0.110 | 0.090 | 0.075 | 0.065 |
| CA3085       | 0.440 | 0.385 | 0.350 | 0.300 |
| LM311H       | 0.700 | 0.600 | 0.550 | 0.500 |
| TBA258XB     | 0.680 | 0.600 | 0.550 | 0.500 |

**LOW PRICES EX-STOCK**

Buy it with Access



All mail to:  
Henry's Radio  
404 Edgware Rd  
London W12  
Phone (01) 723 1008




# TRAMPUS

## SEMICONDUCTOR DISTRIBUTORS

58-60 GROVE ROAD, WINDSOR BERKS SL4 1HS  
TELEPHONE WINDSOR (07535) 54525  
ORDERS WELCOME BY POST OR TELEPHONE  
TRADE, EDUCATIONAL & EXPORT SUPPLIED



## WINTER SALE

### THIS MONTH TO MAKE ROOM FOR NEW MICRO MEMORY PRODUCTS WE ARE REDUCING OVERSTOCK PRODUCT.

Post & Packing free on orders over £3. Other orders please add 25p P & P. Credit orders welcome by post or phone. Normally 24 hours turnaround on ex stock product. UK add 8% VAT to prices marked \* all other prices add 12 1/2% VAT. All priced each. Price list free send S.A.E. Data costs extra. Discounts: This month buy 10 PAKS get one free. Also 10% off 100 TTL or CMOS. All products to makers specification.



**DIP**. All grades 1. Big 1/2" displays  
FMS508 CA or CC only 80p  
0.2" displays 75p  
LEDs Big & Bright Red 3mm/1/2" dia 5p  
Red 5mm/0.2" dia 5p  
Semi Clip & Lock ring 2p  
TL209 Red & Blue Chip  
Green or Yellow with 3 or 5mm dia 15p  
Color LED no clip 15p  
MEMORIES: 10% off & up.  
2102 RAM 450ns 80p  
2102 RAM 250ns £1.20  
2102 RAM 250ns £1.35  
2114 Static 4K RAM  
Easy use. No clock. 5v 4x1k 10 Pts £8 each  
2708 Epm £5  
2716 Intel £20\* (see available)  
2532 5v Epm PMA  
MICRO BUSS STOPS  
6000 CPU 1MHz £5  
6000 CPU 2MHz £5  
6002 CPU/RAM 1MHz £12  
6046 PMA-BK BUS PROM  
+ Timer £25  
8620 & 8621 PIA £5  
6850 ACA 1MHz £5  
AT5 1014 UART £4  
AT5 1014 UART £5  
8350 VIO 1 Chip PMA  
INTERFACES: RS232C:3.  
MC1488 & 1489 80p  
MC6800 & 6809 £2  
8118S & 96 £1.40  
XTAL 1MHz £3

**DEVELOPMENT SETS**  
All loose packed in 1 bag.  
SET 1: 25x50 volt Ceramic Capacitors 5% 10 each 22p in 0.1uf £5  
SET 2: Testleads 1st in 200uf 20v to 35v Total 50 Capacitors £5  
SET 3: Electrolytic 25 volt Total 80. 10 each 10 ohms to 10 meg ohms. Total 500 £5  
SET 4: 1/2 watt Resistors 5%. C.F. 10 each 10 ohms to 10 meg ohms. Total 500 £5  
SET 5: 20x20mm Signal NPL. Similar to 100 £1  
SET 6: 30x22mm 0.5volt Electrolytic £1  
SET 7: 14x8x107 £1  
SET 8: 14x8x108 £1  
SET 9: 50x50 10v E1  
SET 10: 40x20 10v E1  
SET 11: 40x20 10v E1  
SET 12: 40x20 10v E1  
SET 342: 40x20 10v E1  
SET 343: 40x


### BAD NEWS FOR KNOB TWIDDLEDERS

A 300W Lightdimmer Kit with NO knob. Dimming and on/off functions are controlled by touch. Features include:

★ No mains rewiring  
★ Switches on to preset brightness

★ Can be switched and dimmed from many locations using TDE/K kit making 2-way switching easy

★★ PRICE £8.99  
TDE/K £1.50

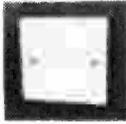

### TRIAC BARGAINS

|                     |      |
|---------------------|------|
| 400V Plastic Case   | 58p  |
| 3A                  | 80p  |
| 6.5A with trigger   | 74p  |
| 8A                  | 84p  |
| 12A                 | 105p |
| 16A                 | 165p |
| 20A                 | 190p |
| 25A                 | 50p  |
| SCR (C106D) 5A/400V | 21p  |
| Diac                |      |

### COMPONENTS

#### 0.2" L.E.D.S.

|                       |               |
|-----------------------|---------------|
| Red 12p               | £1/10         |
| Green 21p             | 25p           |
| DL727 5 digit         | £1.50         |
| LCD 5 4 digit         | £8.10         |
| LDR 5 dia             | 55p           |
| NE555                 | (4 for £1.00) |
| 741                   | (5 for £1.00) |
| LM3911 temperature IC | £1.00         |
| AY-5-1224             | £3.25         |
| AY-5-1230             | £4.85         |
| ZN1034E               | £1.80         |
| ICL7106 DVM IC        | £9.25         |
| 1N4001                | 6p            |
| IN4148                | 4p            |
| BC182L                | 10p           |
| 2N3819                | 20p           |

### MINI MAINS TRANSFORMERS

|                             |     |
|-----------------------------|-----|
| Standard 240V mains primary |     |
| 100mA secondary             |     |
| 6-0-6V                      | 85p |
| 9-0-9V                      | 90p |
| 12-0-12V                    | 95p |

### DIGITAL VOLTMETER THERMOMETER KIT

Based on the 7106 single IC 3½ digit DVM the kit contains a PCB, resistors, capacitors, presets, IC and 0.5" liquid crystal display. Components are also included to enable the basic DVM kit to be modified to a Digital Thermometer using a single transistor as the sensor.



ONLY £21.99

### 24 HR. CLOCK/APPLIANCE TIMER KIT

Switches any appliance of up to 1KW on and off at preset times once a day. KIT contains AY-5-1230 Clock/Appliance Timer IC, 0.5 LED display, mains supply, display drivers, switches, LEDs, triac, complete with PCBs and full instructions



White box (56x131x71mm)—drilled £2.50  
undrilled £2.50

Ready-built £21.25

PLEASE ADD 8% V.A.T. (\*12½%) TO ABOVE PRICES

QUANTITY DISCOUNTS ON REQUEST. ADD 25p POSTAGE & PACKING. MAIL ORDER ONLY

T.K. ELECTRONICS, 106 Studley Grange Road, London W7 2LX



# Wilmslow Audio

**THE firm for speakers!**

Send 15p stamp for the world's best catalogue of Speakers, Drive Units, Kits, Crossovers, etc., and discount price list

ATC ● AUDAX ● BAKER ● BOWERS & WILKINS  
● CASTLE ● CELESTION ● CHARTWELL ●  
COLES ● DALESFORD ● DECCA ● EMI ● EAGLE  
● ELAC ● FANE ● GAUSS ● GOODMAN ●  
HELME ● I.M.F. ● ISOPHON ● JR ● JORDAN  
WATTS ● KEF ● LEAK ● LOWTHER ●  
McKENZIE ● MONITOR AUDIO ● PEERLESS ●  
RADFORD ● RAM ● RICHARD ALLAN ● SEAS ●  
TANNOY ● VIDEOTONE ● WHARFEDAILE

## WILMSLOW AUDIO Dept. ETI

SWAN WORKS, BANK SQUARE, WILMSLOW  
CHESHIRE, SK9 1HF

Discount Hi-Fi, etc., at 5 Swan Street and  
10 Swan Street

TEL: WILMSLOW 0625 529599 FOR SPEAKERS  
MAIL ORDER AND EXPORT  
WILMSLOW 0625 526213 FOR HI-FI



### KEY:

- 1: The bit of chocolate you thought you'd leave for later.
- 2: Coffee stains (instant).
- 3: A useful-sized bit of stiff paper to stop the window from rattling.
- 4: Rough calculations for your new combined egg timer/laser cannon project.
- 5: ETI makes a fair soldering iron stand.
- 6: The dog insisted on carrying your copy to you along with your slippers.

## WHAT A BIND!

Half our orders for binders are repeats: we think that says a lot for their quality. At £3.00 all inc. you get a great deal of peace of mind too!

ETI Binders  
25-27 Oxford Street,  
London W1R 1RF.

# Codespeed

WHERE YOU CAN BE SURE OF  
A BARGAIN

## Full Spec. Devices

**CALCULATOR PACK M4.** Contains a production line reject calculator. Either fix them (not much wrong with some we checked) or strip them for spares (whichever part is defective the rest must be good value for money — case/keyboard/display/chip/PCB). We include all the info. we can find on repairing calculators. What a bargain at **£2.50**.

**PACK M1.** 2 Calculator keyboards. Each has 17 keys and two switches. Only **£1.00**.

**PACK M2.** 1 x 2102, a 1024 bit Static R.A.M. The most popular R.A.M. in professional and amateur electronics. With full data. **£1.25**

**PACK M3.** Build your own calculator! MM5725 calculator chip and data book. **£1.00**.

**PACK E2.** An 8 digit calculator style Liquid Crystal display. 0.33" high digits with right hand decimal points and overflow indicator. With data. **£2.95**.

**PACK E3.** Same as Pack E2 but with 0.5" high digits. **£4.25**.

**PACK E4.** A 1½ digit 0.3" high 7 segment gas discharge display. Requires 180V anode volts but can make an excellent replacement for LEDs in some of your mains operated projects. Fantastic value. With info. **90p**.

**PACK E5.** Same as Pack E4 but dual digit. **90p**.

**PACK E6.** Contains a brand new 6 digit Texas Instruments type DIS436 LED display. Multiplexed with built-in bubble magnifiers. **£1.00**.

**PACK E7.** A Genuine Burroughs Panaplex II. 180 volt, 12 digit, 7 segment gas discharge display. 0.3" digits. We include the special socket FREE. With data **£1.50**.

**PACK T2.** Back again by popular demand. A 0.2" 3½ digit Liquid Crystal wristwatch display with data. **£1.00**.

**PACK T4.** An 0.8" giant red LED clock display. Common cathode. 3½ digit with AM/PM indicator. An excellent display for your digital clock projects at **£4.95**.

**PACK P1.** An MM5330 Digital Voltmeter I.C. Now build your own digital multimeter or panel meter using this versatile chip. With data and circuit diagram. **£3.95**.

**PACK DM1.** 5 x 14 pin dual in line chips, each containing 23 quality matrixed signal diodes. With data. **50p**.

**PACK C1.** 10 x 12 pin Hybrid circuits each containing 16 resistors/capacitors. Useful values. Ideal for semiconductor circuits and PCB miniaturisation. With data. 10 Hybrid circuits for **50p**.

**SPECIAL OFFER PACK DM1/C1** — Buy a pack DM1 and a pack C1 for the special price of only **85p** for the pair.

## Untested Devices

**PACK E1.** (80% Guaranteed Good) 5 x MAN3. 7 segment 0.127" common cathode LED displays. Excellent value. **£1.00**.

**PACK DL1.** (Untested — so no guarantees.) Fantastic value for money. A jumbo pack of 30 mixed I.C.s. There could be anything in this pack. linear, digital — who knows. Guaranteed to sell out at only **£1.00**.

**PACK MU1.** (Untested — so no guarantees.) Another bargain. 2 x Upper half of a calculator case with built in keyboard. Most are ex-equipment, but believed to be O.K. A snip at only **60p** the pair.

Your satisfaction is guaranteed or return the complete pack for replacement or a refund.

**MAIL ORDER ONLY — NO CALLERS PLEASE**  
Postage and Packing please add 25p (Overseas Orders add 60p)

**CODESPEED, P.O. Box 23, 34 Seafield Road  
Copnor, Portsmouth, Hants. PO3 5BJ**

For a merry musical  
Christmas an electronic  
musical door chime which  
can play 24 different tunes!



A complete  
CHROMA-CHIME  
Kit for only £15.95

includes P & P + V.A.T

Plays  
Greensleeves  
God Save the Queen  
Rule Britannia  
Land of Hope and Glory  
Oh Come All Ye Faithful  
Oranges and Lemons  
Westminster Chimes  
Sailor's Hornpipe  
Beethoven's 'Fate Knocking'  
The Marseillaise  
Mozart  
Wedding March  
Cook House Door  
The Stars & Stripes  
Beethoven's Ode to Joy  
William Tell Overture  
Soldier's Chorus  
Twinkle Twinkle Little Star  
Great Gate of Kiev  
Maryland  
Deutschland uber Alles  
Bach  
Colonel Bogie  
The Loralie

The CHROMA-CHIME is exclusively designed by

**CHROMATRONICS**

River Way, Harlow, Essex.

To CHROMATRONICS River Way, Harlow, Essex, U.K.

£15.95

Please send  Chroma Chime Kits at £15.95 each including VAT and post and packing  
PLEASE USE BLOCK CAPITALS

Name \_\_\_\_\_  
Address \_\_\_\_\_

I enclose cheque PO value £ \_\_\_\_\_  
or debit my ACCESS BARCLAYCARD account No \_\_\_\_\_

Signature \_\_\_\_\_

ETI

Please allow 7-21 days for delivery.

\*These tunes play longer if the push button is kept pressed

|                    |            |             |            |            |             |                           |                          |  |                           |    |
|--------------------|------------|-------------|------------|------------|-------------|---------------------------|--------------------------|--|---------------------------|----|
| <b>TRANSISTORS</b> | BC328 15p  | BU208 160p  | 2N4062 20p | 7492 35p   | 74196 55p   | 4510 70p                  | <b>DIODES</b>            | 16p                                      | <b>ZENER DIODES 400mw</b> | 8p |
| AC126 18p          | BC338 15p  | OC25 76p    | 2N4123 23p | 7493 34p   | 74197 55p   | 4516 64p                  | BY127 16p                | 2.7V to 33V                              |                           |    |
| AC127 17p          | BC547 11p  | OC28 108p   |            | 7494 51p   | 74198 110p  | 4518 70p                  | 0A47 10p                 |  |                           |    |
| AC128 16p          | BC548 10p  | OC35 108p   |            | 7495 52p   | 74199 110p  | 4519 60p                  | 0A91 15p                 |  |                           |    |
| AC141 24p          | BC549 11p  | OC71 19p    | TTL        | 7496 50p   |             | 4520 65p                  | 0A200 6p                 | <b>VERO BOARDS 0.1" copper</b>           |                           |    |
| AC142 24p          | BC557 14p  | OC72 34p    | 7400 12p   | 7497 138p  |             | 4528 55p                  | 0A202 9p                 | 2.5" x 5"                                | 51p                       |    |
| AC151 42p          | BCY30 67p  | OC84 46p    | 7401 12p   | 74100 88p  |             | 4578 27p                  | IN4148 4p                | 3.75" x 5"                               | 60p                       |    |
| AC152 52p          | BCY34 74p  | IP29 40p    | 7402 12p   | 74104 50p  |             | 4583 82p                  | 1N916 5p                 |  |                           |    |
| AC153 53p          | BCY59 24p  | IP30 40p    | 7403 12p   | 74105 40p  | <b>CMOS</b> | 4585 105p                 | 1N4001 4p                |  |                           |    |
| AC176 18p          | BCY70 14p  | IP31 50p    | 7404 12p   | 74107 25p  | 4000 15p    |                           | 1N4002 4p                | <b>CERAMIC CAP 50V</b>                   | 2p                        |    |
| AC188 23p          | BCY71 14p  | IP32 55p    | 7405 13p   | 74109 30p  | 4001 15p    |                           | 1N4003 5p                | 22pF to 50,000pF                         |                           |    |
| AD149 65p          | BCY115 52p | IP33 75p    | 7406 24p   | 74110 46p  | 4002 15p    |                           | 1N4004 6p                |  |                           |    |
| AD161 35p          | BCY121 79p | IP34 98p    | 7407 24p   | 74116 160p | 4007 15p    | <b>VOLTAGE REGULATORS</b> | 1N4005 7p                | <b>POLYESTER CAP 250V</b>                | 5p                        |    |
| AD162 38p          | BCY123 79p | IP35A 253p  | 7408 14p   | 74118 82p  | 4008 64p    | 7805 60p                  | 1N4006 8p                | .01, .015, .022, .033, .047, .068, .1 uF | 5p                        |    |
| AF114 30p          | BCY124 97p | IP36A 389p  | 7409 14p   | 74120 125p | 4009 35p    | 7812 60p                  | 1N4007 9p                | .15, .22, .33 uF                         | 7p                        |    |
| AF118 30p          | BCY131 35p | IP41A 69p   | 7410 12p   | 74121 25p  | 4010 35p    | 7815 60p                  | 1N5400 13p               | .47, .68 uF                              | 13p                       |    |
| AF125 27p          | BCY132 35p | IP42A 69p   | 7411 19p   | 74122 33p  | 4011 15p    | 7818 60p                  | 1N5401 14p               | 1 uF                                     | 17p                       |    |
| AF126 27p          | BCY135 38p | IP2955 126p | 7412 17p   | 74123 40p  | 4012 15p    | 7824 60p                  | 1N5402 15p               | 2.2 uF                                   | 28p                       |    |
| AF127 27p          | BCY136 37p | IP3055 64p  | 7413 25p   | 74125 35p  | 4013 35p    | 7905 79p                  | 1N5403 20p               |  |                           |    |
| AF139 37p          | BCY137 38p | ZTX108 14p  | 7414 48p   | 74126 35p  | 4014 60p    | 7912 79p                  |                          |  |                           |    |
| AF186 54p          | BCY138 38p | ZTX109 14p  | 7416 24p   | 74132 50p  | 4015 60p    | 7915 79p                  | <b>BRIDGE RECTIFIERS</b> |  |                           |    |
| AF239 40p          | BCY140 35p | ZTX300 16p  | 7420 12p   | 74141 56p  | 4016 35p    | 7918 79p                  | 1A/50V 22p               | <b>ELECTROLYTIC CAP 25V</b>              | 7p                        |    |
| ASV53 81p          | BF115 25p  | 2N706 13p   | 7421 22p   | 74142 200p | 4017 55p    | 7924 79p                  | 1A/100V 24p              | 1 uF to 47 uF                            | 8p                        |    |
| ASV54 81p          | BF167 29p  | 2N1131 23p  | 7422 18p   | 74145 58p  | 4018 64p    |                           | 1A/200V 27p              | 68 uF, 100 uF                            | 8p                        |    |
| ASV55 69p          | BF173 27p  | 2N1132 23p  | 7427 24p   | 74147 110p | 4020 60p    |                           | 1A/400V 30p              | 150 uF                                   | 9p                        |    |
| BC107 8p           | BF178 34p  | 2N1302 38p  | 7428 28p   | 74148 90p  | 4021 60p    | <b>THYRISTORS</b>         | 2A/50V 34p               | 220 uF                                   | 12p                       |    |
| BC108 8p           | BF179 37p  | 2N1304 54p  | 7430 12p   | 74150 70p  | 4022 55p    | 1A/100V 28p               | 2A/100V 36p              | 330 uF                                   | 12p                       |    |
| BC109 8p           | BF180 37p  | 2N1305 25p  | 7432 23p   | 74151 50p  | 4023 15p    | 1A/200V 38p               | 2A/200V 38p              | 470 uF                                   | 15p                       |    |
| BC113 17p          | BF181 37p  | 2N1306 39p  | 7433 24p   | 74153 50p  | 4024 45p    | 1A/400V 40p               |                          |  |                           |    |
| BC117 20p          | BF182 37p  | 2N1308 40p  | 7437 22p   | 74154 85p  | 4025 15p    | 3A/100V 36p               | <b>OPTO/ DISPLAYS</b>    |  |                           |    |
| BC119 24p          | BF183 37p  | 2N1613 22p  | 7438 22p   | 74155 52p  | 4027 35p    | 3A/200V 38p               | 2N5777 50p               | 4.7 ohms to 1 Mohms                      | 1p                        |    |
| BC140 34p          | BF184 28p  | 2N1711 21p  | 7440 13p   | 74156 51p  | 4028 52p    | 3A/400V 51p               | OCF71 70p                |  |                           |    |
| BC142 27p          | BF185 30p  | 2N1893 44p  | 7441 51p   | 74157 51p  | 4029 60p    |                           | DRP12 70p                | <b>POTENTIOMETERS</b>                    | 25p                       |    |
| BC143 27p          | BF194 13p  | 2N2217 27p  | 7442 42p   | 74160 60p  | 4030 35p    | <b>LINEARS</b>            | DL704 115p               | 1 Kohm to 2 Mohms log/linear             | 58p                       |    |
| BC147 8p           | BF196 13p  | 2N2219 21p  | 7443 74p   | 74161 65p  | 4035 60p    | 710CN 40p                 | DL707 115p               | 5 Kohm to 1 Mohm log switch              |                           |    |
| BC149 8p           | BF197 13p  | 2N2369 16p  | 7444 74p   | 74162 65p  | 4041 57p    | 741-8 22p                 |                          | <b>PRESETS 0.1W horizontal</b>           | 5p.                       |    |
| BC157 8p           | BF198 16p  | 2N2483 26p  | 7445 64p   | 74163 65p  | 4042 54p    | 747C-4 50p                | <b>LEDs and 2'</b>       | 100 ohm to 1 Mohm                        |                           |    |
| BC158 9p           | BF200 36p  | 2N2484 22p  | 7446 55p   | 74164 70p  | 4043 54p    | 748C-8 30p                | Red 9p                   | <b>TRANSFORMERS 240V primary</b>         | 95p                       |    |
| BC159 9p           | BF224 16p  | 2N2905 22p  | 7447 55p   | 74165 70p  | 4044 50p    | CA301-1 80p               | Yellow 13p               | 6.0-6V 100mA                             | 360p                      |    |
| BC166 8p           | BF257 37p  | 2N2906 22p  | 7448 57p   | 74166 80p  | 4047 95p    | CA301-8 80p               | Green 14p                | 9.0-9V 100mA                             | 250p                      |    |
| BC170 9p           | BF258 40p  | 2N2907 22p  | 7450 14p   | 74167 180p | 4048 63p    | CA302-1 80p               | Clp 3p                   | 0.6Vx2 1Ax2                              | 290p                      |    |
| BC171 9p           | BF259 44p  | 2N2926 10p  | 7451 14p   | 74173 94p  | 4049 28p    | CA302-8A 85p              |                          | 9.0-9V 2A                                | 400p                      |    |
| BC172 9p           | BF299 30p  | 2N3053 18p  | 7452 13p   | 74174 70p  | 4050 28p    | CA303-5 140p              |                          | 0-12V 2A                                 | 370p                      |    |
| BC173 9p           | BF240 30p  | 2N3054 50p  | 7453 14p   | 74175 65p  | 4066 40p    | CA303-6 120p              |                          | 0-15Vx2 200mAx2                          | 240p                      |    |
| BC182 10p          | BF279 30p  | 2N3055 50p  | 7454 14p   | 74176 60p  | 4068 20p    | CA304-6 110p              | <b>DIL SOCKETS</b>       |  |                           |    |
| BC183 10p          | BF280 30p  | 2N3702 8p   | 7460 14p   | 74177 60p  | 4069 16p    | CA305-4 70p               | 8 pin 10p                |  |                           |    |
| BC184 10p          | BF292 25p  | 2N3703 8p   | 7470 24p   | 74178 80p  | 4070 16p    | CA308-0 40p               | 14 pin 12p               |  |                           |    |
| BC186 23p          | BF300 38p  | 2N3704 8p   | 7472 24p   | 74180 80p  | 4071 16p    | CA314-0E 70p              | 16 pin 13p               |  |                           |    |
| BC187 26p          | BF385 29p  | 2N3706 9p   | 7473 25p   | 74181 145p | 4072 16p    | LM301AN 28p               |                          |  |                           |    |
| BC207 10p          | BF386 31p  | 2N3707 9p   | 7474 25p   | 74182 60p  | 4073 16p    | LM308N 64p                |                          |  |                           |    |
| BC212 10p          | BF387 20p  | 2N3710 8p   | 7475 32p   | 74184 110p | 4077 25p    | LM380N 76p                |                          |  |                           |    |
| BC213 10p          | BFY50 15p  | 2N3711 8p   | 7476 28p   | 74190 72p  | 4078 16p    | LM381N 120p               |                          |  |                           |    |
| BC214 10p          | BFY51 15p  | 2N3772 177p | 7480 46p   | 74191 72p  | 4081 16p    | NE555 25p                 |                          |  |                           |    |
| BC237 14p          | BFY53 28p  | 2N3773 290p | 7485 69p   | 74192 65p  | 4082 16p    | NE556 60p                 |                          |  |                           |    |
| BC238 14p          | BSX19 25p  | 2N3866 54p  | 7486 24p   | 74193 64p  | 4086 59p    | T8A641 240p               |                          |  |                           |    |
| BC301 30p          | BSX20 21p  | 2N3904 8p   | 7490 32p   | 74194 60p  | 4501 19p    | T8A800 70p                |                          |  |                           |    |
| BC303 30p          | 8U205 140p | 2N4061 12p  | 7491 45p   | 74195 55p  | 4507 40p    | T8A810 100p               |                          |  |                           |    |

Add 25p for p&p. All items new and full spec.

**DELTA TECH & CO.**  
62 NAYLOR ROAD, LONDON, N20 0HN

# ETIPRINTS

ETIPRINTS are a fast new aid for producing high quality printed circuit boards. Each ETIPRINTS sheet contains a set of etch resistant rub down transfers of the printed circuit board designs for several of our projects. ETIPRINTS are made from our original artwork ensuring a neat and accurate board. We thought ETIPRINTS were such a good idea that we have patented the system (patent numbers 1445171 and 1445172).

## HOW IT WORKS



Lay down the ETIPRINT and rub over with a soft pencil until the pattern is transferred to the board. Peel off the backing sheet carefully making sure that the resist has transferred. If you've been a bit careless there's even a 'repair kit' on the sheet to correct any breaks!

## BUYLINES

### ORDER TODAY

Send a cheque or P.O. (payable to ETI Magazine) to —


ETI PRINT  
ETI MAGAZINE,  
25/27 OXFORD STREET, LONDON W1R 1RF.

**75p** inc p&p

## PARTS LIST

|     |                              |                        |
|-----|------------------------------|------------------------|
| 001 | 3 Channel Tone Control       | Oct 77                 |
|     | Spirit Level                 | Oct 77                 |
|     | Clock A                      | Nov 77                 |
|     | Digital Thermometer          | Oct 77                 |
|     | Skeet Game                   | Nov 77                 |
|     | Componder                    | Nov 77                 |
| 002 | House Alarm                  | Jan 78                 |
|     | Rev Monitor                  | Dec 77                 |
|     | Clock B                      | Dec 77                 |
| 003 | Race Track Game              | Jan 78                 |
|     | Hammer Throw                 | Jan 78                 |
|     | Freezer Alarm                | Dec 77                 |
| 004 | Metal Locator Mk II          | Feb 78                 |
|     | Ultrasonic Tx / Rx           | Feb 78                 |
|     | 5 Watt Stereo Amp (modified) | Jan 77                 |
|     | Metronome                    | Feb 78                 |
|     | Shutter Time                 | Feb 78                 |
| 005 | Op-Amp Supply                |                        |
|     | Frequency Shifter            | Mar 78                 |
|     | LCD Panelmeter               |                        |
|     | Light Dimmer (3 times)       |                        |
| 006 | CMOS Switched Preamp         |                        |
|     | From Experimenters P.S.U.    | "Electronics Tomorrow" |
|     | 555 Boards (twice)           |                        |
| 007 | Star Trek Radio              | May 78                 |
|     | CD Ignition                  | May 78                 |
|     | CCD Phaser                   | May 78                 |
|     | White Line Follower          | April 78               |
| 008 | Tank Battle                  |                        |
|     | Helping Hand                 | May 78                 |
| 009 | AM / FM Radio                |                        |
|     | Bridge Oscillator            | June 78                |
|     | CMOS Stars & Dots            |                        |
| 010 | Bench Amplifier              |                        |
|     | Freezer Alarm                | Project Book Six       |
|     | Marker Generator             |                        |
|     | LED Dice                     |                        |
|     | Watchdog (2 PCBs)            |                        |
|     | Stars & Dots PSU             |                        |
| 011 | Noise Generator              |                        |
|     | General Preamp               | Project Book Six       |
|     | Flash Trigger                |                        |
|     | Componder                    |                        |
|     | Active Crossover (2 PCBs)    |                        |
| 012 | Disco Lightshow              | Project Book Six       |
|     | Stereo Simulator             |                        |
|     | Digital Thermometer          |                        |
| 013 | Amplifier Module             | Project Book Six       |
|     | Amplifier PSU                |                        |
|     | Equaliser                    |                        |
|     | Equaliser PSU                |                        |
| 014 | Skeet Game                   | Project Book Six       |
|     | Sweep Oscillator             |                        |
|     | Burglar Alarm                |                        |
|     | GSR Monitor                  |                        |
| 015 | UFO Detector                 | July 78                |
|     | Torch Finder (twice)         | July 78                |
|     | Etiwet (twice)               | Aug 78                 |
| 016 | Stac Timer                   |                        |
|     | Xhatch Gen                   | Sept 78                |
|     | Wheel of Fortune             |                        |
| 017 | Complex Sound Gen            |                        |
|     | Tele Bell Extender           | Oct 78                 |
|     | Power Bulge                  |                        |
| 018 | RF Power Meter               | Oct 78                 |
|     | Proximity Switch             | Oct 78                 |
|     | Audio Oscillator (2)         | Nov 78                 |
| 019 | Car Alarm (2)                | Dec 78                 |
|     | Wine Temp (2)                | Dec 78                 |
|     | Curve Tracer                 | Dec 78                 |

## MORE SCOPE FOR YOUR MONEY

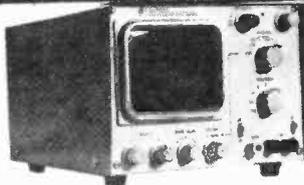

### SPECIFICATIONS

**ELECTRICAL DATA**  
**VERTICAL AXIS (Y)** Deflection Sensitivity — 100mV/division  
 Bandwidth (between 3dB points) — DC — 5MHz. Input Attenuator  
 — (calibrated) — 9 step 0.1, 0.2, 0.5, 1, 2, 5, 10, 20, 50/div  
 Input Impedance — 1 Meg/40 pF in shunt. Input Voltage — Max —  
 600V P.P.  
**HORIZONTAL AXIS (X)** Deflection Sensitivity — 0.400mV/div  
 division. Bandwidth (between 3dB points) — 1Hz-350KHz. Gain  
 Control — Continuous when time bases in EXT position. Input  
 Impedance — 1 Meg. Input Voltage — Max — 600V P.P.  
**TIME BASE** Sweep Range (calibrated) — 100msec/div to 1µ  
 sec/div in 5 steps. FINE Control — Variable between steps —  
 includes time-base calibration position. Blanking — Internal — on  
 all ranges.  
**SYNCHRONISATION** Selection — Internal, external. Synchronisation  
 Level — Continues from positive to negative.  
**POWER SUPPLY** Input voltage — 115/220V AC ± 10% at  
 50/60Hz. Power Dissipation — 18W.  
**CRT DATA** — 4in — flat face, single beam — Maximum high  
 voltage — 1.5kV — Fitted with 8x10 division blue filter graticule.  
**PHYSICAL DATA** Dimensions — 15cm(h) x 20cm(w) x 28cm(d).  
 Weight — 4.3kg (approx.). Stand — 2 position flat and inclined.  
 Case — Steel, epoxy enamelled. Front panel — Aluminium,  
 enamelled epoxy printing.

Cash with order

£99 (+ £7.92 V.A.T.)

Test leads available £2.00


Barclay and Access


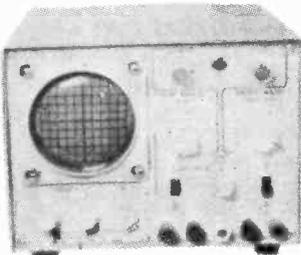
### 6 MHz OSCILLOSCOPE

Large 5" flat CRT. DC to 6MHz bandwidth. 10mV to  
 50V/cm in 12 calibrated steps. 0.5µs to 0.125cm/cm  
 sweep range in 6 calibrated steps plus 12.1Sec/cm  
 Magnifier x5. Fully automatic trigger. DC to 1.5MHz  
 horizontal bandwidth.

£120 (+ £9.60 VAT). SAE for further details.



3 inch medium-persistence tube response up to 5 MHz  
 (—3dB) — adjustable +ve. —ve or external sync.  
 External x-input. y-sensitivity down to 100mV/div.  
 Timebase: 100ms/div to 1µs/div in 5 steps. Dimensions:  
 15cm x 20cm x 28cm. Weight: 3.8kg (8½ lbs.).  
 3" spec as 4" shown above.

£83.25 cost. VAT £6.66. Carriage £1.50

### CALCULATOR SALE

**TEXAS**  
 PC100B £151.20. T157 £28.30. T151-3 £28.40.  
 T158 £64.80. T159 POA Software £24.  
 T1 Prog. £49.95. Little Prof. £10.80.  
**CASIO**  
 FX2500 £19.80. FX3100 P+2 LCD sci £24.30.  
 FX120 £21.95.  
 FX39 £15.60. FX140 £19.90. FX48 £19.95. ST24  
 £19.95.  
 CQ 81 £17.90. PQ7 £19.90.  
**HEWLETT PACKARD**  
 HP 31E @ £38.98. HP 33E £69.12. HP 25C £105.05.  
 HP 67 £299.16. HP97 £514.62. HP29C £118.90.  
**CBM**  
 PRO 100 £29.95/SRN190R £28.95.  
 COMMODORE Pet Computer 2001/8K £695.  
 P50 (8+2) 24 programmable steps £17.40.  
 Boris Microprocessor chess game £199.  
 Gammon Master II (computer backgammon) £149.95.  
 Ataria Microprocessor cassette TV game £149.  
 LCD Penwatch £29.55

## KRAMER & CO.

9 October Place, Holders Hill Road  
 London NW4 1EJ. Tel: 888941  
 attn. Kramer k7. Tel: 01-203 2473  
 Mail order only. Callers by appointment  
 We accept Govt./Co. purchase orders

## SEMICONDUCTOR OFFERS ALL FULL SPEC.

Common anode 0.3 7 seg displays Toshiba type TLR303 65p.  
 F.E.T.s similar to 2N3819 18p. Mosfet Sim to A0673 35p. 3N140  
 Mostets 50p. M203 Dual Matched Pairs. Mosfets Single Gate per  
 F.E.T. 40p. Intel 1024 bit MOS Rams 95p. Mullard BB113 Triple  
 Varicap Diode 35p. MC1310 Stereo Decoder I.C.s £1.20. C04051  
 CMOS 50p. 741 8-pin D.I.L. 23p. 500v 600mA Bridge Recs. (ex.  
 equip.) 25p. 1N4002 100v 1A Diodes 4p. 14005 800v 1A Diodes  
 7p. E.H.T. SIL Rec. 15kV 2.5mA, 15mm x 5mm 30p. 7812 12v  
 1A Plastic V. Regs 95p. Min. Nixes ITT 58705 13 x 6mm Fig Size  
 85. Nixes ITT 6N79A 13 x 8mm 65p. 0.2 or 0.125 Red LEDs  
 12p each. MAN3A 3mm LED Displays 50p. 7415 (wide  
 bandwidth) 35p. LM380 80p. LM381 90p. 2N4174 75p. TIL305  
 Alpha-numerical Displays, with data, £2.75. ORP61, Mullard,  
 new, boxed 30p. Special Offer: SGS TBA800 ICS, 10 for £5.00.

**MICROPHONES** EM506 Condenser Mikes. Uni-directional,  
 F.E.T. Amp. Dual impd., 50K/600ohms, 30-18KHz, on/off  
 switch. £11.00. Miniature Tie Pin Condenser mike 1K imp.,  
 omni-directional, uses hearing aid battery (supplied) £4.95.  
 Grundig Electret Inserts with built-in F.E.T. Preamp £1.50. Crystal  
 Mike Inserts 37mm 45p. Electret Condenser Mikes with 2.5 and 3.5  
 Jack Plug £2.95. Cassette Condenser Mikes with 2.5 and 3.5  
 Jack Plugs £2.95. Standard Cassette Mikes 200 ohm Imped with  
 2.5 and 3.5 Jack Plugs £1.20.

**MORSE KEYS** — Hi-speed Type, all metal, £2.25. Plastic Morse  
 Keys, 95p. Belling Lee L4305 Masthead Amplifiers and 240v AC  
 power unit Group "A" UHF. Only £7.50.

**CRYSTALS** 300KHz HC6U 40p. 0.1 Edge Connectors, 64 way  
 65p. 32 way 40p.

**RELAYS** Min. 220v AC Sealed Relay 2 pole C/O 45p. 240v AC  
 Sealed Relay 3 pole C/O 53p. Contacts 11-pin base 80p. 12 volt  
 4 pole N.O. Reed Relay 20p. Min. 24v DC Sealed 2-pole C/O  
 relays 3-amp contacts. New 55p. 12v DC 4pc.o. open type, new  
 50p each.

**MOTORS** 1.5 to 6v DC Model 20p. 115v AC min. 3 R.P.M. with  
 Gearbox 30p. 240v AC Synchron Motor 1.1 R.P.M. 65p. 240v AC  
 Synchron Motor 1/24th R.P.M. 65p. Crozet 115v AC 4 R.P.M.  
 Motors, new 95p. 12v DC 5-pole 35p.

**BOXES** Black A.B.S. Plastic with brass inserts and lid. 75 x 56 x  
 35mm 40p. 95 x 71 x 35mm 49p. 115 x 95 x 16mm 57p. 225 x  
 130 x 84mm £1.95

**TOOLS** Radio pliers, 5in, insulated handles £1.40. Diagonal side  
 cutters, 5in, insulated handles £1.40.

**MAINS TRANSFORMERS**, all 240v AC primary. Postage shown  
 in brackets per transformer.  
 6-0-6 100mA, 9-0-9 75mA, 12-0-12 50mA, 75p each (15p).  
 0-4-6-9 150mA, no mounting bracket, 65p (20p). 12-0-12  
 100mA, 95p (15p). 12v 500mA, 95p (22p). 12v 2 Amp, £2.25  
 (45p). 12v 4 Amp, £2.75 (54p). 15-0-15v 1 Amp, £2.10 (45p).  
 30-0-30v 1 Amp, £2.75 (54p). 0-12-15-20-24-30v tapped at 2  
 Amp, £4.50 (54p). 20-0-20v 2 Amp, £3.50 (54p). 25v 1.5 Amp,  
 £1.45 (45p). 18v 1.5 Amp rectified, £2.00 (45p). 35v, 2 Amp,  
 £2.5v 2 Amp toroid, £2.95 (54p). 20v 2.5 Amp, £2.20 (54p). 1.1  
 Xenon/triac pulse transformer, 30p.

**SWITCHES** — Min. Toggle, SPST 8 x 5 x 7mm 45p. DPDT 8 x 7 x  
 7mm 60p. DPDT Centre Off 12 x 11 x 9mm 75p. DPDT C/O  
 Sliders 20p. R.S. Single Pole C/O Push Buttons 45p. Roller Micro  
 Switches 15p. Min. Micro Switches 13 x 10 x 4mm 20p. Min.  
 Push to make or push to break Switches 16 x 6mm 15p.

**SOLDER SUCKER**, Plunger type, eye protection, replaceable  
 nozzle, high suction, £4.95. Reed switches 28mm norm. open, 6p  
 each.

**TAPE HEADS** — Cassette Stereo £3.00. BSR MN 1330 ½ Track  
 Dual Impedance Rec./Playback 50p. BSR SRP90 ¼ Track Stereo  
 Rec./Playback £1.95. TD10 Assemblies, two heads, ¼ Track  
 Rec./Playback Staggered Stereo with built-in erase per head  
 £1.20. Tape Head, Demag, 240v AC £1.95.

**BUZZERS** — GPO Type 6-12v 20p. Min. Solid State Buzzers  
 6-9-12 or 24v 15mA 75p. All Metal Buzzer, 30mm diam. 6-12  
 volts, high tone, 25p.

**U.H.F. TV** Transistorised Push Button Tuners (not Varicap), new  
 and boxed, £2.50.

**MURATA MA401L**, 40kHz Transducers, rec./send, £3.25 pair.

**METERS** — Grundig Batt. Level Meter 1mA 40 x 40mm £1.10.  
 Min. Level Meter 200µA 25 x 15mm 75p. Ferranti 600v AC Meter  
 £3.95.

**EDGE METER** — Large scale 0-100, new £2.75

**POT CORE UNIT**, Has 6-pot cores, including 1 FX2243 (45mm)  
 and 2 FX2242 (35mm), 3 20mm Panel Fuseholders, 3 T03 SIL  
 Power Transistors on heat sink, panel with various transistors and  
 diodes with a 5-amp plastic S.C.R. New £1.75 + 75p P&P.

**LA1230** adj. core 15mm dia. 14mH-18mH, HI Q, 10p each.

**8 TRACK** 12 volt motors new, £1.25  
**CASSETTE MOTORS** 6 volt new, £1.25

**SOLENOIDS** — 240v AC 45p. 12v DC H. Duty 75p. 240v 25lb  
 pull, 2 travel £3.95

**12-WAY MOTORISED CAM UNITS**, 50v AC low rev. motor  
 driving 12 C/O micro switches, supplied with a capacitor for 240v  
 AC use. Ex. equip. £1.95 + 35p P&P.

**13 Amp** rubber trailer extension sockets, 38p.

**8 WAY RIBBON-CABLE**, min solid core, 15p metre.

POSTAGE 30p UNLESS OTHERWISE SHOWN (EXCESS  
 POSTAGE REFUNDED WITH ORDER). OVERSEAS POST AT  
 COST. VAT INCLUDED IN ALL PRICES.

S.A.E. FOR LISTS

ORDER ADDRESS

**PROGRESSIVE RADIO**  
 31 CHEAPSIDE, LIVERPOOL 2

## CALCULATORS SCIENTIFIC

**SPECIAL OFFER**  
 TEXAS T159 together with PC100B  
 (Complete as manufacturer's specifications)  
 £285.00

TEXAS/HP Accessories available

- \*TEXAS T159 (New Card prog 960 prog steps of 100 mem) £156.50
- \*TEXAS T158 (New Key prog 480 steps or 60 mem) £80.00
- \*TEXAS PC100B (New updated Printing Unit for T158/T159) £140.00
- \*TEXAS T157 (Key Prog 8 mem. 150 Key Strokes / 50 Prog Steps) £28.20
- TEXAS T133 (New — same spec. as T130, but 3 mem) £13.95
- \*TEXAS T145 (New updated version of the Texas T140) £19.95
- \*TEXAS 42MBA (10 Dig Trin/Stat Prog 12 mem 32 key strokes) £42.95
- \*TEXAS TI PROGRAMMER (Hexadecimal Oct) £46.50
- \*TEXAS T151/iii (New 8 Dig + Exp 10 mem 32 Prog Steps. Stat/Sci) £26.30
- TEXAS T125 (new LCD Sci/Stat) £18.90
- TEXAS Little Professor (Child's Calculator / Game 5/9 year olds) £10.00

## "SLIM-LINE" Chronograph BARGAIN OFFER

You will not believe the luxury of this "Slim-Line" Chronograph until you have worn it... until you have enjoyed the compliments it generates.



The "Slim-Line" Chronograph gives continuous easy to read LCD display of hours, minutes, seconds, AM/PM. At the touch of button you have date — month date — day of week — reverting to normal display time at the release of the button.  
 Press again for immediate stop watch/stop time facility to 1/100 second. The "Slim-Line" even has a powerful back light for easy light use, the casing is chrome finished with matching linked bracelet.  
 We are so certain you will be delighted and satisfied with this "Slim-Line" Chronograph that in addition to the One Year Warranty we are offering a 14-day money back guarantee if you are not entirely satisfied.

ONLY £27.50 + £1.00 p/p ms. Send cheque/P.O. or order via Barclay/Access credit card today under our Special 14-day Trial Offer.

- \*TEXAS T158 with Applied Statistics £80.00
- \*TEXAS T159 with PC100B and Applied Statistics £305.00

### AUTUMN SALE

TEXAS T159 Calculator (complete as manufacturer's spec., master module, charger, etc.). PLUS statistics module and extra set of 40 Blank Prog Cards, with wallet, etc.  
 ONLY £180

- \*CBM 9190R (as 4190R but with 9 memories) £27.50
  - \*CBM Pro 100 (72 Step Prog) £29.50
  - \*HP 19C (Cont Mem Key Prog Printer) £118.50
  - \*HP 29C (as 19C but no Printer) £87.50
  - \*HP32E (8 mem Prog Sci/Stat) £64.00
  - \*HP32E (Advanced Sci with Statistics) £90.00
  - \*HP27 (10 Mem Sci/Fin/Stat) £73.50
  - \*HP31E (New Sci replaces HP21) £35.00
  - \*HP67 (Card Prog 224 Steps 26 Mem) £242.00
  - \*HP97 (Fully prog with Printer) £396.50
- All HP range avail. inc. new 'Exp' range.  
 CASIO FX360 (New 10 Dig + Exp 7 Mem 8) (St. Div Lin Regr. etc.) £45.00  
 CASIO AQ 1000 (LCD Cal 3-way Stop Watch / Alarm) £20.00  
 CASIO FX3100 (New version of FX3000-LCD Sci/Stat/Div Poles Rec. etc.) £22.50  
 CASIO FX8000 (as above + Stop Watch / Alarm) £27.73

### LOW PRICED COMPUTING THE COMMODORE PET COMPUTER

with 8K bytes RAM 2001-8  
 A complete personal computer that operates anywhere by simply plugging into Main supply. Allows communications directly from BASIC to IEEE — 488 standard devices —  
 Cassette, Video Display Unit and Keyboard built into PET  
 Fully guaranteed Warranty by CBM  
 complete only £643

### NOW IT'S YOU AGAINST COMPUTERS

- CHESS CHALLENGER "3" (3 levels of game — beginner to expert) £120.32
- CHESS CHALLENGER "10" (10 levels of game from beginner to master) £184.26
- BORRIS (the most advanced chess computer yet: BORRIS will even play against itself. Therefore ideal for learning from beginner to master. BORRIS will "PROMPT" you to better play) £184.26
- COMPUTER-CHECKERS- DRAUGHTS (4 levels of play) £83.28
- GAMMON MASTER (with doubling dice) £138.84

\*FREE — Mains / Charger included\*

GOODS FULLY GUARANTEED. PRICES EXCLUDE VAT (ADD 8%)  
 BUT INC. P&P CHEQUE WITH ORDER  
 Company / Hospital and Government orders accepted by phone  
 Barclaycard / Access accepted by phone

Tel. 01-455 9855

EXPORT ORDERS WELCOMED  
 Air Freight / Air Post Delivery  
 Quotations on request. Payments via Letter of Credit / Int.  
 Money Order / American Express, etc.

**MOUNTAINDENE**  
 22 Cowper St., London, EC2

# CLICK ELIMINATOR

**The Cat Sat On The Mat: or was there one of your favourite records on the mat? Never mind — ETI steps in to rescue your valuable vinyl from those evil clicks and pops.**

EVEN THE MOST fastidious of record collectors must have some records in his collection which during their career have picked up the odd scratch or two. Perhaps your record collection dates back to the time before you obtained that second mortgage, sold the wife or whatever, to get the latest in laser controlled fluid damped, tangential tracking phonograms, sorry record deck, and the previous system has left it's mark on these early platters.

## In The Click Of Time

However the scratches got there, they are bound to be obtrusive on any reasonably Hi-Fi set up and even if you do not qualify for the title Hi-Fi purist — someone who listens, not to the music, but to the defects, real or imagined, in the Hi-Fi chain — the clicks will detract from your enjoyment.

Enter ETI — we can help. The click suppressor described here will remove or greatly reduce the audible transient sounds — nice phrase — resulting from scratches on a record's surface.

## Design Decisions

When designing a click suppressor it is fairly obvious that we have to be able to tell the click from the cacophony as it were. Fortunately a click has several unique characteristics which set it apart from a music signal. For instance it will have very fast attack and delay times — even high frequency percussive sounds will delay slowly, although attack will be fast. A click will also be of a very short duration — again musical sounds are in general of a longer duration.

Once we have spotted our click, it is necessary to remove it. In our case we substitute a short period of silence

— subjectively unnoticeable — in place of the click.

As our click detection circuit requires a finite time in which to operate, we will also have to provide some sort of delay for the music signal within the system. Our circuit, and all the commercially available units, use a CCD delay line to provide this delay. It is the recent availability of this device that has made the click suppressor possible, or rather brought it within the financial reach of the constructor. ▶

**Next month we will be giving the full details for building and setting up the Click Eliminator**



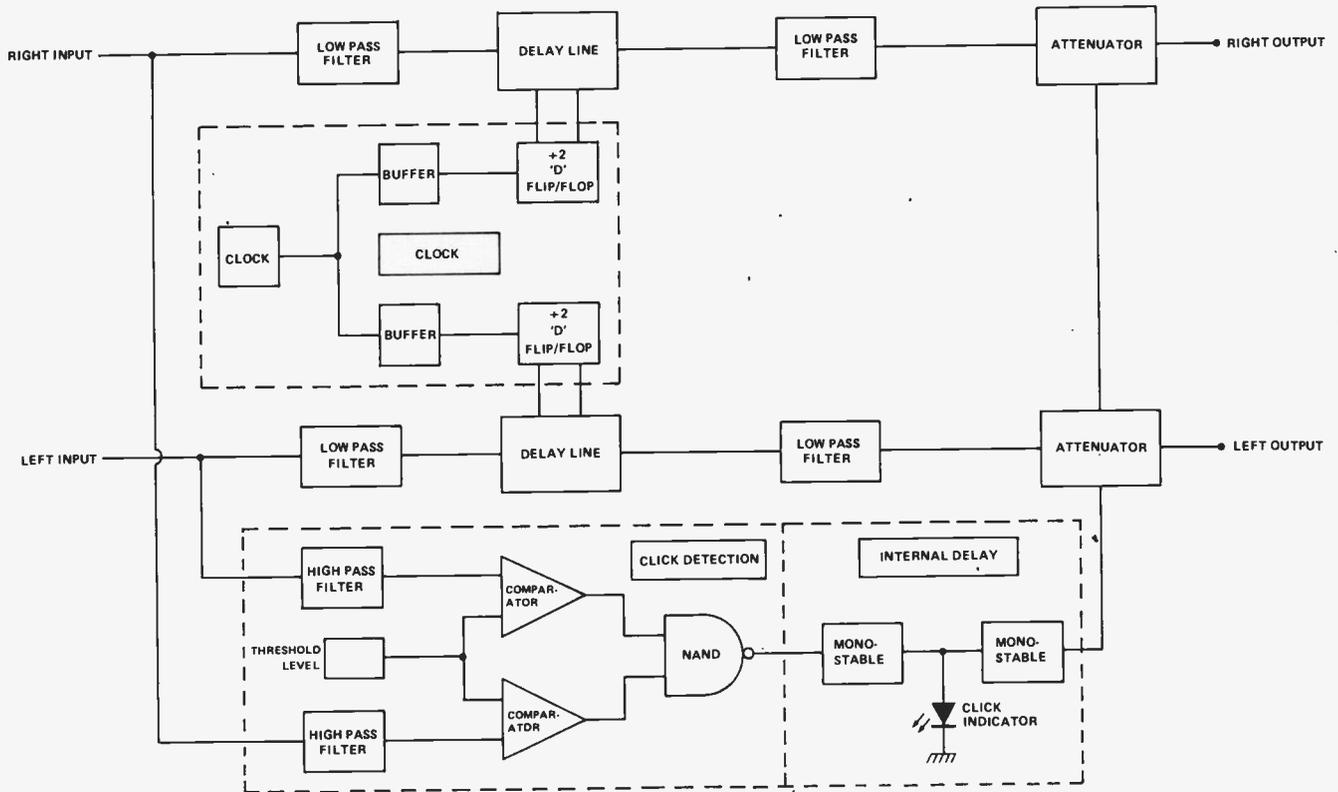


Fig. 1. Block diagram of the ETI click eliminator.

## HOW IT WORKS

Overall operation of the circuit can best be understood by reference to the block diagram shown in fig 1. The signal from each of the inputs is fed both to a delay line, with associated low pass filters, and to the "Click Detection" block. This provides a negative going signal at its output coincident with a click appearing on either input channel.

With the click identified, the next step is to remove it without affecting the subjective quality of the program material. The circuit operates by dramatically attenuating the signal passing through the unit for a brief period of time "Either Side" of the click.

If the attenuation is large enough and it's period accurately synchronised to the occurrence of the click, the effectiveness of the unit is dramatic. The loss of program material during this blanking period which might be thought to be as objectionable as the click itself, seems to produce little subjective disturbance.

It has been shown that periods of attenuation of this nature, up to 10ms, do not unduly disturb the signal, and the 2ms or so necessary to "straddle" a click goes entirely unnoticed.

It is necessary to incorporate a delay line within the circuit as a finite time is necessary for the click detection circuits to operate. The chain of events is shown in fig 2. The click is fed to the input of the delay line and at some time later will emerge from this device where it is passed to the attenuator. Meanwhile the click has been detected and activates two 555 timers acting as monostables. The first provides a click detection indicator for the front panel. As this returns to its stable state, it triggers the second 555. It is this IC that causes the 570 IC to suppress the signal.

By careful selection of the timing components associated with the 555's, the signal is blanked during the time when the click is emerging from the delay line.

A detailed description of the various circuit blocks now follows.


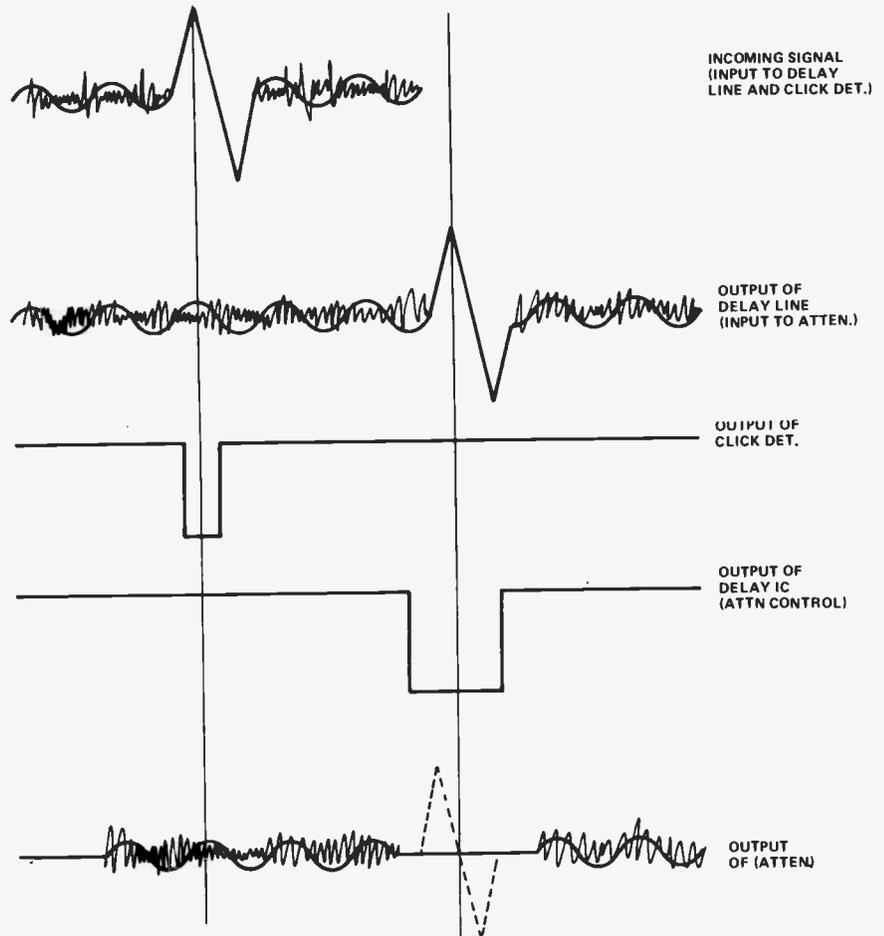
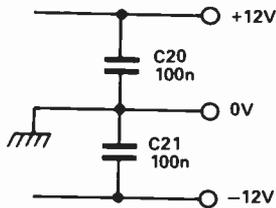


Fig. 2. Above are shown the waveforms that illustrate the action of the circuit when a click has been identified and is to be suppressed.

# PROJECT: Click Eliminator

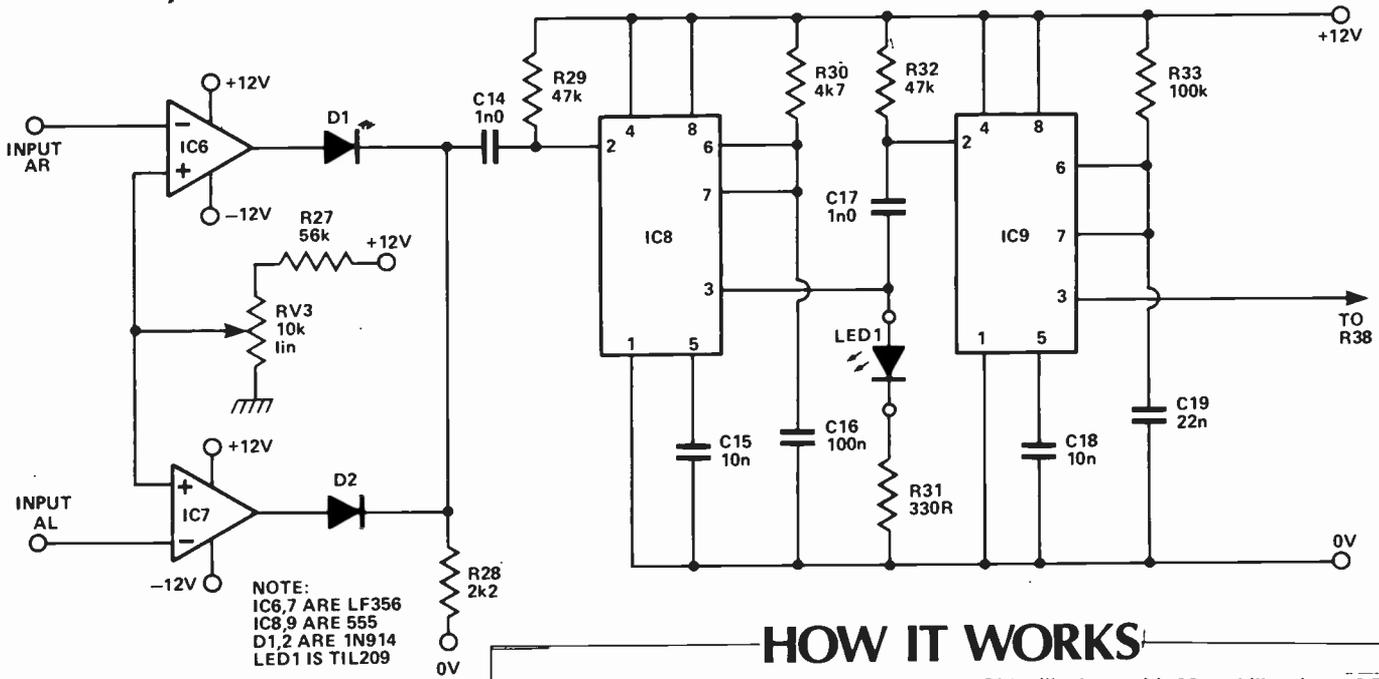

Second stage of the "click detection" circuitry.

## HOW IT WORKS

### CLICK DETECTOR AND ATTENUATOR CONTROL

Outputs from the low pass filters described above are passed to comparators IC6 and 7. The outputs of these IC's are usually high, but if the level at their inputs exceeds a level (set by RV3) they will go low. This control is set such that the comparator will operate only when a high amplitude click is passed to IC6 and IC7, the click being of greater amplitude than the program material.

Another unique characteristic of a click is that it will appear on both channels simultaneously. We therefore pass the outputs of the comparator IC's to the NAND gate formed by D1, D2, and R28. The junction of these components and C14 will be high unless both the comparator outputs are low.


A negative going signal applied to IC8 via

C14 will trigger this IC and illuminate LED 1 the click indicator LED. After X ms the IC's output will return to its stable state and in so doing will trigger IC9. This IC controls the attenuator and will suppress the program material during its astable state.
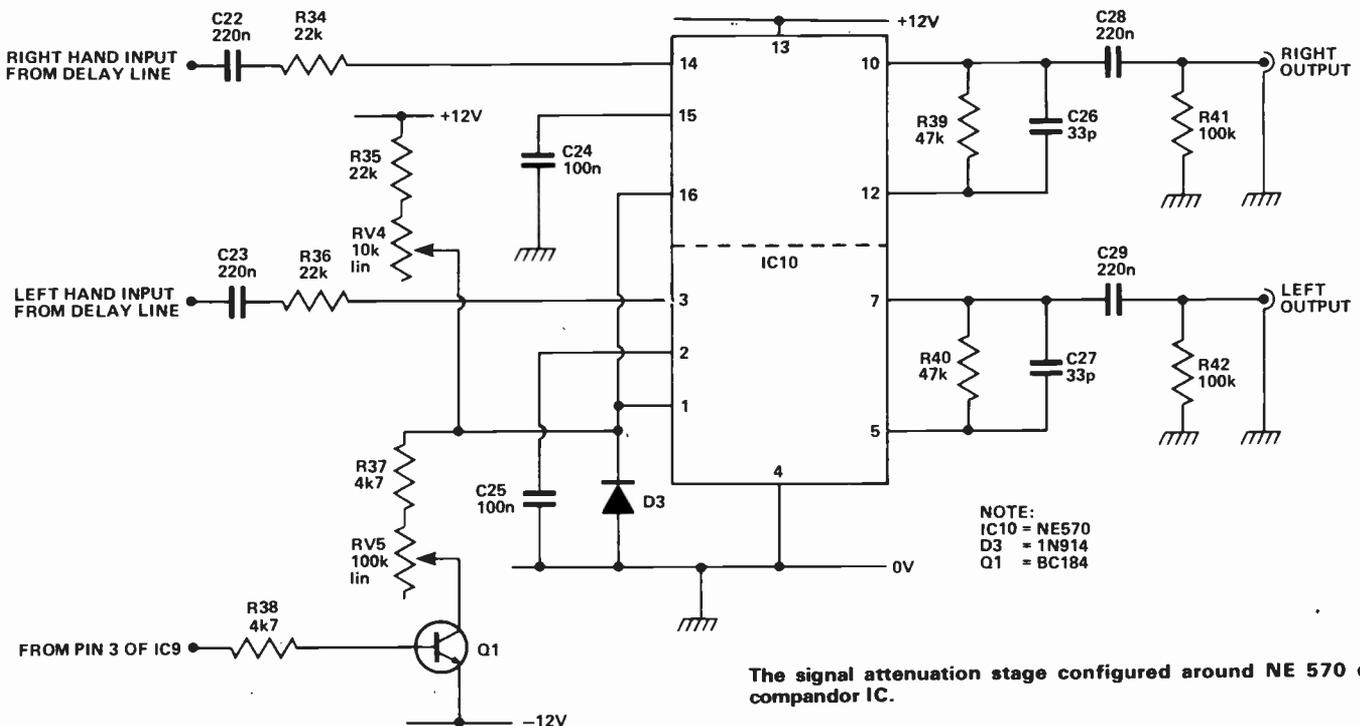
### ATTENUATOR STAGE


The attenuator is built around an NE570 dual compandor IC (see data sheet Oct 77 p.59). The inputs to the IC are at pins 14 and pin 3, the outputs — with suitable filters — are taken from pins 10 and 7. Gain control is achieved by robbing current from the NE570.

As the input to Q1 is taken high, the device will start to conduct and thus rob the NE570 of current, thus reducing the gain of the amplifier within the device. The control action is set up by RV4.



The signal attenuation stage configured around NE 570 dual compandor IC.

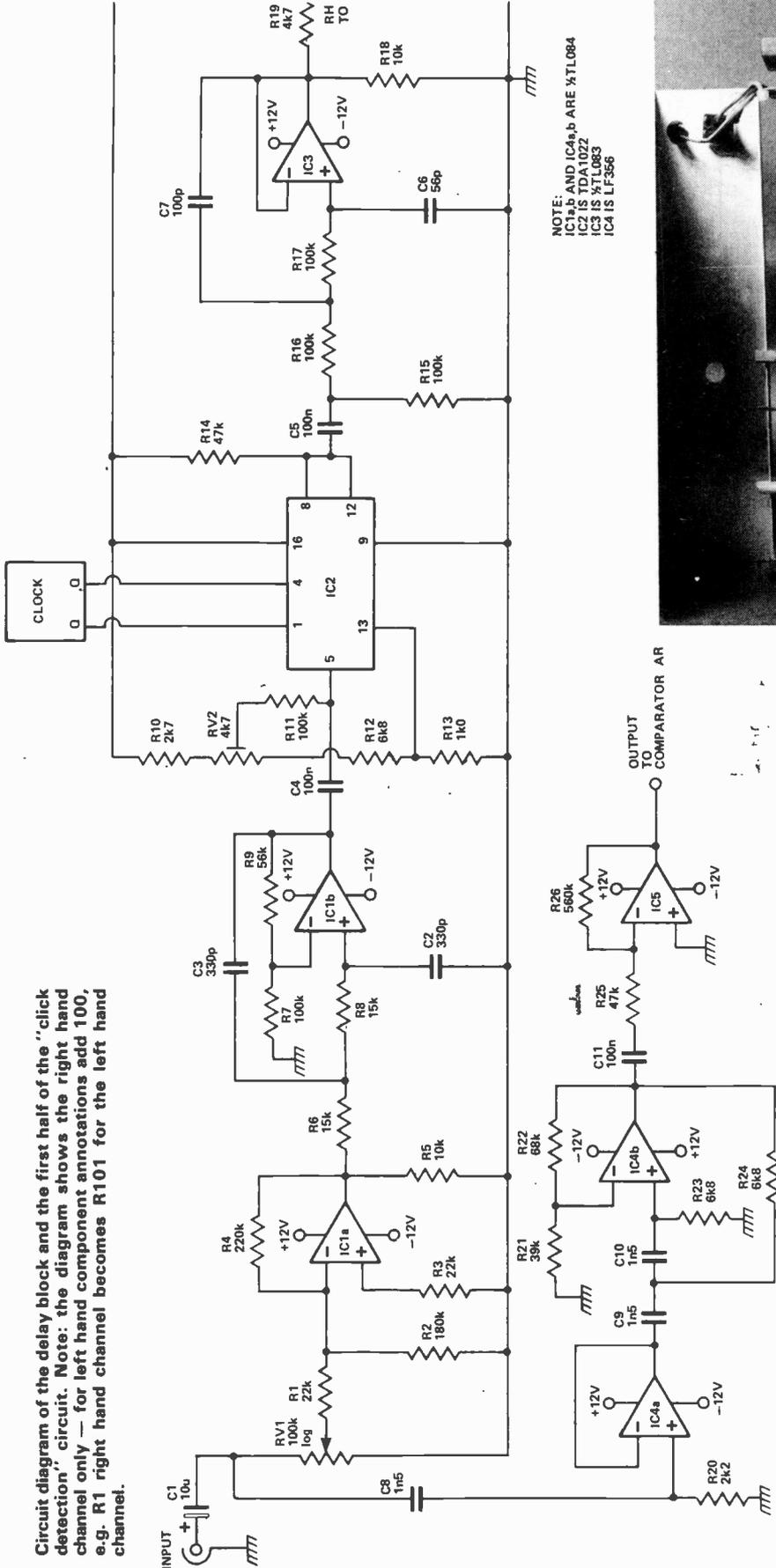Circuit diagram of the delay block and the first half of the "click detection" circuit. Note: the diagram shows the right hand channel only — for left hand component annotations add 100, e.g. R1 right hand channel becomes R101 for the left hand channel.



## HOW IT WORKS

**DELAY LINE AND FIRST STAGE OF CLICK DETECTOR**

The circuit block shown above forms one channel of the delay line and click detector circuitry (the other channel is identical). The input signal is first passed to IC1a, which is configured as an inverting amplifier. The output from this stage is fed to IC1b and associated components. This stage forms a second order Butterworth filter with an upper 3dB point of about 18kHz. The stage also has a small amount of gain in its pass band.


This configuration ideally meets the drive requirements of the delay line, which suffers from an insertion loss, made up for by the passband gain and must have the maximum frequency applied to it limited to, in this case, the audio spectrum of frequencies. The reason for the frequency limit is that the maximum frequency fed to a delay line must not be greater than half the frequency of the

clock signal superimposed on the output that might cause HF overload in subsequent stages.

The input of the delay line is pin 5, the filter section that forms the first stage of the click detector.

A click has a number of unique characteristics, one of which being that it is rich in HF energy — a result of its fast attack and delay time. The effect of passing the music signal through a low pass filter will be to highlight the high energy click amongst the generally low high frequency content of normal program material.

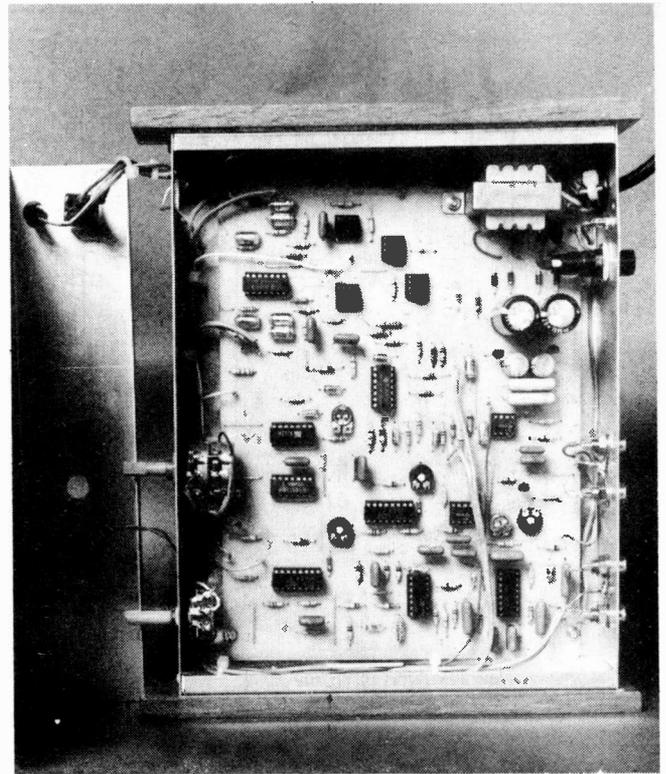The low pass filter is once again built around a second order Butterworth stage. The signal is passed to this stage after a simple HF filter and buffer (IC4a). The output from the filter is amplified by inverting amplifier IC5 and fed to the second half of the



by B. J. R.

# PARTS LIST

## RESISTORS

R1, 3, 34, 35, 36, 101, 103 22k  
 R2, 102 180k  
 R4, 104 220k  
 R5, 18, 105, 118 10k  
 R6, 8, 106, 108 15k  
 R7, 11, 15, 16, 17 39k  
 R22, 122 68k  
 R26, 126 560k  
 R30, 37 4k7  
 R31 330R

R12, 23, 24, 112, 123, 124 6k8  
 R13, 44, 113 1k0  
 R14, 19, 25, 29, 32, 39, 40, 43, 114, 119, 125 47k  
 R20, 28, 120 2k2  
 R21, 121 39k  
 R22, 122 68k  
 R26, 126 560k  
 R30, 37 4k7  
 R31 330R

## POTENTIOMETERS

RV1 +101 100k log gang  
 RV2, 102 4k7 min. preset  
 RV3 10k  
 RV4, 6 10k min. preset  
 RV5 100k min. preset

## CAPACITORS

C1, 101 10u 16V tantalum  
 C2, 3, 37, 102, 103 330p polystyrene  
 C4, 5, 11, 16, 20 21, 24, 25, 30, 104, 105, 111 100n polyester  
 C6, 106 56p polystyrene  
 C7, 107 100p polystyrene  
 C8, 9, 10, 108, 109, 110 1n5 polystyrene  
 C12, 13, 35, 36 47u 16V electrolytic  
 C14, 17 1n0 polystyrene  
 C15, 18 10n polyester  
 C19 22n polyester  
 C22, 23, 28, 29 220n polyester  
 C26, 27 33p polystyrene  
 C31, 32 1000u .25V electrolytic  
 C33, 34 470n polyester

## SEMICONDUCTORS

IC1, 4 TL084  
 IC2 TDA1022  
 IC3 TL083  
 IC5, 6, 7, 105 LF356  
 IC8, 9 555  
 IC10 NE570  
 IC11 4001  
 IC12 4013  
 IC13 78L12  
 IC14 79L12  
 Q1 BC108  
 D1, 2, 3 1N914  
 D4, 5, 6, 7 1N4001  
 LED1, 2 TTL209

## MISCELLANEOUS

PCB as pattern, case (Maplin B3), phono sockets, fuse (500mA) plus holder, switch (DPDT), knobs to suit, cable etc.

click detector described below.

### CLOCK AND POWER SUPPLY

Pls 1 and 4 of the delay line must be presented with 180° out of phase wave forms. The clock signal is generated by the CMOS oscillator based around IC11a and b, which after buffering is fed to the two D type flip-flops contained within IC12. The Q and Q' outputs of this device provide the required 180° out of phase drive signals.

The power supply is a straightforward design based on two three-terminal regulators.


clock signal used in controlling the device. If this precaution is not observed, the result is severe distortion.

The clock drive circuitry is described below.

The input of the delay line is pin 5, the resistor chain R10, R11, R12, R13 and RV2 is to hold pin 13 at 1V0 above ground, this ensures maximum dynamic range in the delay line, and to bias pin 5 for class A operation which minimises distortion.

The output from the delay line is taken, via C5, to another Butterworth filter, this stage being used to remove any high frequency

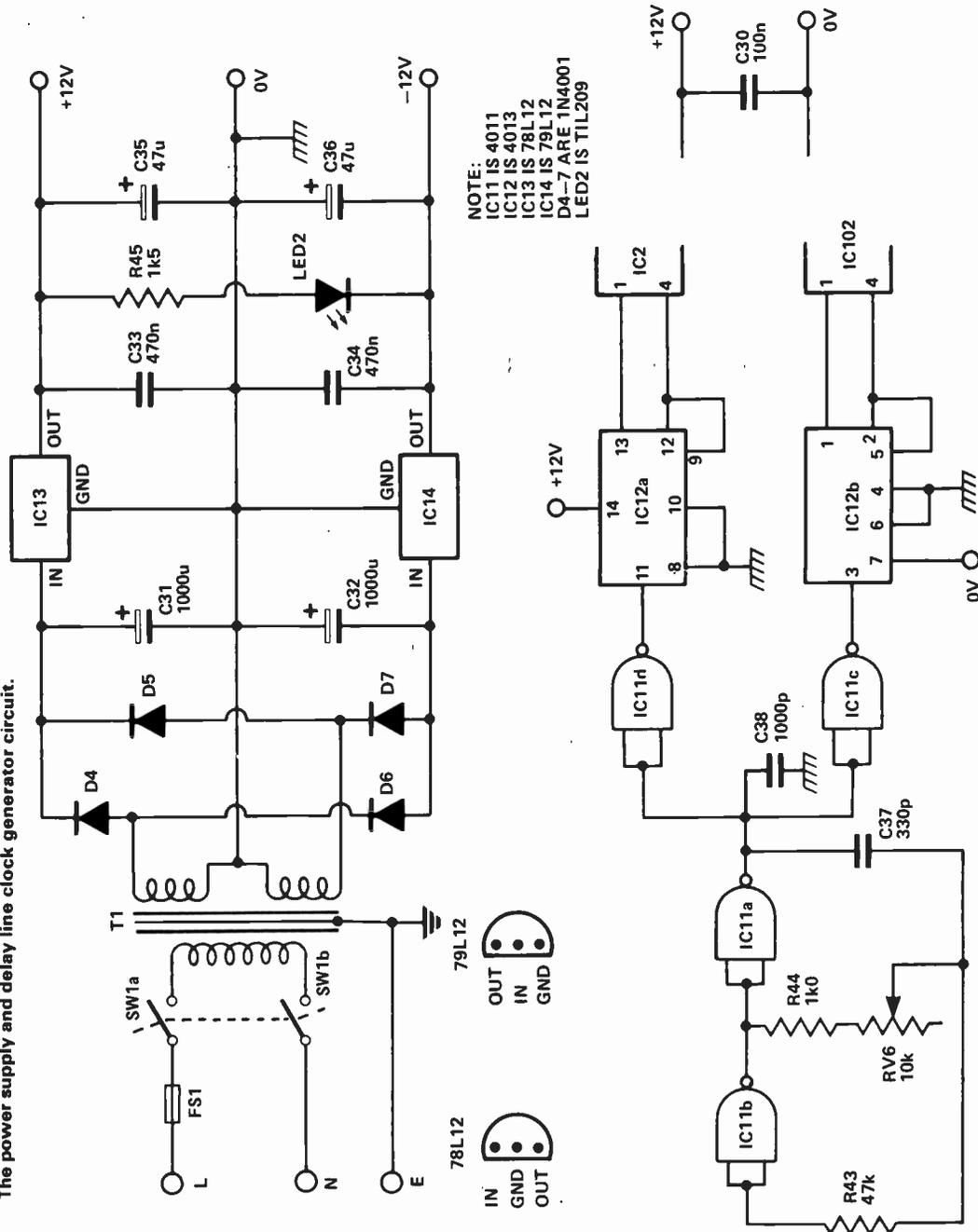The power supply and delay line clock generator circuit.



# BUILD-IT-YOURSELF NEW! TEST GEAR KIT

BASIC SERVICING  
INSTRUMENTS WITH  
EASY STAGE BY STAGE BUILDING  
INSTRUCTIONS - IDEAL FOR THE AMATEUR

## MULTI RANGE TEST METER

A general purpose meter covering all usual ranges of A.C. and D.C. volts current and resistance measurements

## AUDIO SIGNAL GENERATOR

New design covering 10Hz to 10KHz and variable output. Distortion less than 0.01%. Ideal for HI FI Testing.

## OSCILLOSCOPE

A basic 3" general purpose cathode ray oscilloscope for simple testing and servicing work. Sensitivity 0.3 volts/cm

## SEND NOW FOR FREE DETAILS

To LERNAKITS, P.O. Box 156, Jersey.

Name \_\_\_\_\_

Address \_\_\_\_\_

ETI 1/79

# HB COMPUTERS LTD.

Electronic Components Division  
22 Newland Street, Kettering  
Telephone: Kettering 0536 83922/520910

## BULK OFFERS

| TRANSISTORS  | PER 10 | PER 100 |
|--------------|--------|---------|
| BC107/8/9    | £0.85  | £7.50   |
| PBC107/8/9   | £0.65  | £5.50   |
| BC547/8/9    | £0.75  | £6.50   |
| BC557/8/9    | £0.75  | £6.50   |
| BC212/3/4    | £0.75  | £6.50   |
| BC194/5      | £0.80  | £7.00   |
| BF199        | £1.50  | £11.00  |
| BF200        | £2.50  | £22.00  |
| BFY50/1/2    | £1.65  | £15.00  |
| TIP31A/2A    | £3.20  | £30.00  |
| TIP41A/2A    | £4.80  | £43.00  |
| 2N3055 (TO3) | £4.20  | £38.50  |
| 2N3702/3/4   | £0.80  | £7.00   |

## DIODES

|                    |       |        |
|--------------------|-------|--------|
| 1N4001/2/3         | £0.48 | £3.90  |
| 1N4004/5           | £0.55 | £5.00  |
| 1N4007             | £0.70 | £6.00  |
| 1N4148             | £2.20 | £22.00 |
| Zener Diodes 400mW | £0.75 | £5.80  |

## LEDs

|                                      |       |        |
|--------------------------------------|-------|--------|
| 0.2 Red                              | £0.90 | £8.00  |
| 0.125 Red                            | £0.95 | £8.00  |
| 0.2 Red Flat Sides CQX10             | £1.60 | £15.00 |
| 0.2 Yellow/Green                     | £1.30 | £11.00 |
| 0.125 Yellow/Green                   | £1.30 | £11.00 |
| 0.2 Yellow/Green Flat Sides CQX11/12 | £2.20 | £20.00 |

## ORDERING DETAILS

**VAT:** Add high rate to items. Standard rate to others.  
**POST & PACKING:** 30p on all orders under £5.00. Otherwise free. Overseas please add freight costs and state surface or air. No VAT on overseas or BFPO orders. All orders sent first class post in heat sealed padded bags.  
**DELIVERY:** All orders processed on day of receipt. Goods offered subject to availability

## BARGAIN PACKS

| ICs            |       |        |
|----------------|-------|--------|
| LM324 (14 KIL) | £7.00 | £61.00 |
| LM555 (8 DIL)  | £2.80 | £23.00 |
| LM741 (8 DIL)  | £1.80 | £15.50 |

## TANT BEADS

|                     |       |        |
|---------------------|-------|--------|
| 0.1µf 0.22µf 0.47µf |       |        |
| 1µf 35v             | £0.75 | £6.30  |
| 2.2µf 35v           | £0.95 | £8.00  |
| 4.7µf 35v           | £1.20 | £11.00 |
| 10µf 35v            | £1.50 | £12.00 |
| 22µf 10v            | £1.50 | £12.00 |

## HARDWARE

|                           |       |        |
|---------------------------|-------|--------|
| B pin DIL Socket          | £1.00 | £8.00  |
| 14 pin DIL Socket         | £1.10 | £9.50  |
| 16pin DIL Socket          | £1.20 | £10.00 |
| Min side switches         | £1.50 | £12.00 |
| Min push to make switches | £1.50 | £12.00 |

**RESISTORS** 1/2 Watt Carbon Film (Min Type)  
Single. Values £1.25 per 100  
Mixed lots of 100 £10.00 per 1000.

## MICRO PROCESSORS

Wide range of micro parts stocked. Send for free list or visit our showrooms in Kettering and get hands on experience of the PET2001 and Apple II in stock now.

and our conditions of sale. Cash returned for out of stock items.

**PAYMENT:** Cash, cheque, postal order. Credit card orders accepted by letter or telephone.

**GUARANTEE:** All devices are brand new and full spec. No manufacturers' faults or rejects. Any faulty items returned in good condition will be replaced or refunded.

**ENQUIRIES:** Please enclose a suitable S.A.E.

# B. BAMBER ELECTRONICS

DEPT. ETI, 5 STATION ROAD, LITTLEPORT, CAMBS. CB6 1QE  
Tel. ELY (0353) 860185 (Tues. to Sat.)

CASH WITH ORDER. (MINIMUM ORDER £2.00)  
PLEASE ADD VAT AS SHOWN  
POST PAID (UK ONLY). SAE WITH ENQUIRIES  
CALLERS WELCOME BY APPOINTMENT ONLY

## ALL BELOW - ADD 8% VAT

**IC TEST CLIPS,** clip over IC while still soldered to pcb or in socket. Gold-plated pins, ideal for experimenters or service engineers. 28 pin DIL. £1.75; 40 pin DIL. £2.00. Or save by buying one of each for £3.50.

**MAINS TRANSFORMERS, TYPE 15/300 240V** input. 15V at 300mA output. £1.50 each

**MAINS TRANSFORMERS, TYPE 45/100, 240V** 220, 110, 20, 0V input. 45V at 100mA output. £1.50 each.

**SLOW-MOTION MOTORS,** 120V 50Hz 1RPM. Size approx. 2 dia. x 1 1/2 deep, with 1/2 spindle. 80p each, or 2 for £1.00.

**1 1/2 V DC MOTORS** (ideal for model makers, quite powerful). 50p each.

**SUB-MINIATURE ROTARY SWITCHES,** 4 x 5 way make contacts. Size approx. 1/4 dia. x 1 deep, 3/16 spindle. 50p each.

**30pf BEEHIVE TRIMMERS,** Brand new, 4 for 50p.

**Min. 5pf AIR SPACE TRIMMERS,** approx. 1/2 square. 3 for 50p.

**Min. 5pf COMPRESSION TRIMMERS,** 1/2 x 5/16. 4 for 50p.

**LARGE ELECTROLYTIC PACKS,** contain range of large electrolytic capacitors, low and high voltage types, over 40 pieces. £3.00 per pack (+ 12 1/2% VAT).

FULL RANGE OF BERNARDS' BABINI ELECTRONICS BOOK IN STOCK S.A.E. FOR LIST.

**DEUE TO A CHANGE OF SUPPLIER, OUR STOCK ALUMINIUM BOXES AND VINYL COVERED EQUIPMENT CASES WILL BE AS FOLLOWS:**

| Aluminium Boxes with Lids |       |  |
|---------------------------|-------|--|
| AL13 x 2 x 1              | 60p   |  |
| AL24 x 3 x 1 1/2          | 70p   |  |
| AL34 x 3 x 2              | 70p   |  |
| AL46 x 4 x 2              | 90p   |  |
| AL56 x 4 x 3              | £1.25 |  |
| AL68 x 6 x 2              | £1.50 |  |
| AL78 x 6 x 3              | £1.75 |  |

| Vinyl Equipment Cases<br>(Blue Vinyl covered steel tops with plain aluminium lower sections) |       |  |
|--|-------|--|
| BC05 x 2 1/2 x 2 1/2   | £1.00 |  |
| BC16 x 4 1/2 x 2   | £2.00 |  |
| BC26 x 4 x 3 1/2   | £2.25 |  |
| BC38 x 5 1/2 x 2 1/2   | £2.50 |  |
| BC410 x 6 1/2 x 3  | £3.00 |  |
| BC712" x 6 1/2" x 5"   | £3.25 |  |

## ALL BELOW - ADD 8% VAT

**MIXED COMPONENT PACKS,** containing resistors, capacitors, switches, pots, etc. All new, and hundreds of items. £2.00 per pack, while stocks last.

**IC AUDIO AMP PCB,** Output 2 watts into 3 ohm speaker. 12V DC supply, size approx. 5 1/2" x 1 1/2" x 1 1/2" high, with integral heatsink, complete with circuits. £2.00 each.

**NICAD CHARGER CONVERTER PCB,** (Low power inverter) Size approx. 4" x 1 1/4" x 1" high. 12V DC supply. 60V DC output, through pot on pcb, for charging Nicads, etc (ideal for charging portable batteries from mobile supply). Only needs one BFY50/51/52 or similar transistor, which can be mounted direct on the pcb pins on board, fitted with a ster-type heatsink (not supplied). £2.00 each.

**THE NEW EAGLE INTERNATIONAL CATALOGUE IS AVAILABLE ON REQUEST** containing Audio, Incar, and test equipment, etc.

**DECIMAL KEYBOARDS,** pressure sensitive type, when pressed contacts go from 0/C to approx. 25 ohms. Switches only, no encoders. Size approx. 3 x 3 with large square touch plates. 0-9 + Clear, A, B, Dual Watch, and spare. Few only. £2.00 while stocks last.

**TRANSISTORS**

BFY51 Transistors, 4 for 60p.  
BCY72 Transistors, 4 for 50p.  
BSX20 (VHF osc/mult.), 3 for 50p.  
BC107 (metal can) 4 for 50p.  
BC108 (metal can) 4 for 50p.  
PBC108 (plastic BC108), 5 for 50p.  
BF152 (LHF amp/mixed), 3 for 50p.  
2N3819 Fet, 3 for 60p.  
BC148 NPN SILICON, 4 for 50p.  
BC158 PNP SILICON, 4 for 50p.  
BAY31 Signal Diodes, 10 for 35p.  
741CG RCA OP Amps 4 for £1.00.  
SCRS400V at 3A, stud type, 2 for £1.00.  
TIP2955 Silicon PNP power transistor, 60V at 15A, 90 Watts. Flat pack type, 2 for £1.50.  
GERMANIUM DIODES, approx 30 for 30p.  
1N4148 (1N914) diodes 10 for 25p.

**VALVES**

QQV03/2DA (ex. equipment), £3.00.  
QQV03/10 (ex. equipment), 75p or 2 for £1.20.  
6B86 (ex. equipment), 2 for 50p.  
All the above valves are untested, except for heaters, and no guarantee of percentage of emission is given. Sorry - no returns.

**MULLARD BSA2 85V STABILISER VALVES** (brand new), 70p each or 2 for £1.20.

## ALL BELOW - ADD 8% VAT

**RED LEDs** (Min. type) 5 for 70p

**VIDICON SCAN COILS** (Transistor type, but no data), complete with vidicon base. £6.50 each. Brand new AEI CS108/R MICROWAVE DIODES, up to X-Band, max. noise figure 8.5dB at 9.375GHz. 80p each.

**DIE-CAST BOXES**  
SIZE APPROX.

|                                   |       |
|-----------------------------------|-------|
| 4.3 x 2.3 x 1.2 (111 x 60 x 30mm) | £1.25 |
| 4.8 x 2.3 x 1.5 (121 x 60 x 38mm) | £1.75 |
| 4.8 x 3.8 x 1 (121 x 95 x 25mm)   | £2.10 |
| 4.8 x 3.8 x 2 (121 x 95 x 51mm)   | £2.45 |
| 6.8 x 4.8 x 2 (171 x 121 x 51mm)  | £3.10 |
| 4.8 x 3.8 x 3 (121 x 95 x 76mm)   | £3.50 |
| 6.8 x 4.8 x 4 (171 x 121 x 101mm) | £4.47 |
| 8.8 x 5.8 x 2 (222 x 146 x 51mm)  | £4.25 |
| 10.6 x 6.8 x 2 (273 x 171 x 51mm) | £5.30 |

**SPIRALUX Tools** for Electronics enthusiast... SAE for list.

**4MHz XTAL PACKS** (10 assorted xtals between 4MHz and 5MHz). Our selection only £1.00 pack.

**SOLDER SUCKERS** (Plunger Type). Standard Model, £5.50.  
Skirted Model, £6.00.  
Spare Nozzles, 65p each.

**WELLER WP600** Mains operated temperature control, soldering iron. £15.00.

**SPARE TIPS** (for WP600). Two types available. TYPE C77 (W600) Standard. TYPE AA7 (W600). Finer tip. £1.60 each.

**WELLER TCP2** temperature controlled soldering iron, and PUZ20 power unit (replaces Weller TCP1). Iron + PSU £30.00. Spare tips C77 (standard), or K7 (finer tip) £1.50 each.

**Slider Switches,** 2 pole make and break (or can be used as 1 pole change-over by linking the two centre pins), 4 for 50p.

**PLASTIC PROJECT BOXES,** with screws on lids (in black ABS) with brass inserts.

Type NB1 approx 3 x 2 1/2 x 1 1/2 45p each.  
Type NB2 approx 3 1/2 x 2 1/2 x 1 1/2 55p each.  
Type NB3 approx 4 1/2 x 3 1/2 x 1 1/2 65p each.  
Type NB4 approx 8 1/2 x 5 1/2 x 3 1/2 £1.50 each.

**Slider Switches** 2 pole make and break (or can be used as 1 pole change-over by linking the two centre pins), 4 for 50p.

**OSMOR 10V REED RELAY COILS** (1k ohm coil) to fit 1/2 reeds (not supplied), 2 for 50p.

**HF CHOKES** wound on 1/4 x 1 long ferrites, 4 for 50p.

**VHF CHOKES** wound on 6-hole tubular ferrites, 5 for 40p.

## ALL BELOW - ADD 8% VAT

**DUAL TO18 HEATSINKS** 1 x 1/2 x 1/4 with screw-in clamps, 3 for 50p.

**GLASS BEAD FEEDTHROUGH INSULATORS,** solder-in type, overall dia. 5mm, pack of approx. 50 for 50p.

**LARGE GLASS BEAD FEEDTHROUGH INSULATORS,** as above but 8mm dia. pack of approx. 50 for 70p.

**20V RELAYS,** PCB mounting type, single pole change-over, 35p each.

**10.7MHz SSB XTAL FILTERS** (2.4kHz Bandwidth) Low imp. type, Carrier and unwanted sideband rejection min. -40dB (need 10 69835 & 10.70165 xtals for USB/LSB, NOT SUPPLIED). Size approx. 2 x 1 x 1. £10.00 each.

**LOW PASS FILTERS** (low imp. type), 2.9MHz, small metal encapsulation, size approx. 1 1/2 x 1/4 x 1/4 75p each.

## ALL BELOW - ADD 12 1/2% VAT

**CELESTION B x 5 ELLIPTICAL SPEAKERS** 20 ohm, 3 watts rated, £1.50 each + 12 1/2% VAT.

**VARICAP TUNERS** Mullard type. ELC1043/05. £5.00.

**BSR AUTOCHANGE RECORD PLAYER DECKS** with cue device. 33-45-78 rpm. for 7 10 12 records. Fitted with SC12M Stereo Ceramic cartridge and styl. Brand new, £14.00 + 12 1/2% VAT.

**GARRARD AUTOCHANGE RECORD PLAYER DECKS,** Model 6.300, with cue device. 33-45-78 rpm. for 7 10 12 records. Fitted with KS418 Stereo Ceramic cartridge and styl. Brand new, £16.00 + 12 1/2% VAT.

**TV LINE LINEARITY COILS.** Special offer 10 for £1.00.

**TV SCAN COILS, B/W,** to fit 110 degree tubes. £1.00.

**TV SCIN (pin type),** 4 for 50p.

**3-pin Din Plugs,** 4 for 50p.

**Din 3-pin metal sockets,** 15p each.

**Om Speaker Skts,** 2-pin, 4 for 30p.

**Dublier Electrolytics,** 50µF 450V, 2 for 50p.

**Dublier Electrolytics,** 100µF 275V, 2 for 50p.

**Plessey Electrolytics,** 470µF 63V, 3 for 50p.

**TCC Electrolytics,** 1000µF 30V, 3 for 50p.

**Dublier Electrolytics** 5000µF 35V, 50p each.

**Dublier Electrolytics,** 5000µF 50V, 60p each.

**ITT Electrolytics,** 6800µF 25V, high grade, screw terminals, with mounting clips. 50p each.

**Resistor PKs,** approx 300 pieces 1/2 to 2 watt types mixed values, our selection. £1.00 each.

**A RANGE OF CAPACITORS AVAILABLE AT BARGAIN PRICES. SAE FOR LIST.**

# electronics today

international

What to look for in the February issue: On sale Jan 5th

## TODAYS 100 WATT AMPLIFIER AT YESTERDAYS PRICES

ETI, Britain's most ingenious magazine has come up with a 100W mixer amplifier, with distortion below 0.1% at all signal levels, S/N ratio greater than 80dB, inputs for four sources, including one or two disc inputs as you wish. Somehow or other the design, by Richard Bekker, cost less than £50 to build

complete with metalwork.

A complete kit of parts will be made available and full constructional details will be given next month. The unit is finished to match the five channel light show presented in the December issue of ETI.

Crowds are expected to throng shops early next month — newsagents are preparing.

## BUILD YOUR OWN VCT AND FIND OUT WHAT VCT MEANS

The revolutionary device that will replace the op-amp.

We got fed up waiting for it to be released. We did something about it.

We show you how to construct your very own VCT next month!

Astound your friends!

Confuse your budgie!

Amuse your boss!

No home dare be without its VCT!

ETI brings home the bacon next month!

## VOICE SYNTHESIS CRISIS—

# MACHINES SPEAK OUT!

Panic in the streets! Women and children unsafe! Machines can speak! Prime Minister to go on steam radio tonight! From our undercover agent — Tim Orr — comes full details of the invention that could cause a bigger stir than the

double breasted jacket! Several methods are in use, and a new unit is soon to be available which promises to confound us all.

Speech synthesis is here to stay, and Special Agent Orr is right

there in the forefront reporting back for ETI readers exclusively next month. If you value your sanity you cannot afford to miss this! Thinking people everywhere will be talking about this — don't be left out at the dinner table!

## SLIDING INTO SYNCH?

OK you guys youse asked for this and now youse gonna get it, see? Youse bin ringing and hassle us boys down at ETI to do youse a slide synchroniser so long now dat the broad on de phone is going bananas see? So we gotta give it to youse see? Nuffin personal see? OK?

**NEXT MONTH: COMPUTING TODAY GOES TO 48 PAGES! CAN MANKIND SURVIVE? WILL YOU BYTE OFF MORE THAN WE CAN CHEW? FIND OUT IN COMPUTING TODAY NEXT MONTH!**

## SCILLY SCOPE

Make more use of your tele folks! Here is a unit to make the room pulsate with colour in time to your hi-fi! Hooks into music signals to give an oscilloscope type display on a television screen, in full glorious colour! What will they think of next? Pocket calculating machines?

Articles mentioned here are in an advanced state of preparation but circumstances may affect the final contents.

## Composer goes SCAMP

An amazing revelation came to the attention of the British electronics public today. ETI have plans for an MPU composer! Bach and Handel have been heard to revolve in their graves at 2000 RPM at this stunning news! This audacious machine employs a SC/MP processor and an amazingly low component count. All will be finally revealed in the next issue of ETI, and anyone remotely interested in music, synthesisers or electronics is urged not to miss it! A machine that thinks up and plays its own tunes has to be seen to be believed.

| 7400N AND 74LS00N SERIES TTL |      |     |       | Memory |      |      |      | Micro-PROCESSOR |      |         |     | ELECTROLYTICS |     |           |     |        |     |        |      |      |      |     |     |    |
|------------------------------|------|-----|-------|--------|------|------|------|-----------------|------|---------|-----|---------------|-----|-----------|-----|--------|-----|--------|------|------|------|-----|-----|----|
| 7400                         | .10  | .19 | 7400  | .34    | .60  | 2102 | 1.20 | 4012            | .14  | 4160    | .95 | 8C107         | .09 | BS125     | .25 | ZTX14  | .22 | 2N3709 | .08  | 1F   | 10   | 25  | 40V | 63 |
| 7401                         | .12  | .19 | 7491  | .65    |      | 4013 | .34  | 4161            | .95  | 8C107B  | .10 | 8C107H        | .10 | BY127     | .15 | ZTX31  | .20 | 2N3710 | .07  | 1    | .045 | 05  | 055 | 06 |
| 7402                         | .12  | .19 | 7492  | .36    |      | 4014 | .80  | 4162            | .95  | 8C108   | .09 | 8C108B        | .09 | BY206     | .32 | ZTX50  | .20 | 2N3711 | 2.20 | 2.2  | .045 | 05  | 055 | 06 |
| 7403                         | .12  | .19 | 7493  | .32    | .60  | 4015 | .66  | 4163            | .95  | 8C108L  | .10 | 8C108H        | .10 | BYX10     | .18 | ZTX52  | .18 | 2N3712 | 2.70 | 3.3  | .045 | 05  | 055 | 06 |
| 7404                         | .13  | .23 | 7494  | .80    |      | 4016 | .36  | 4164            | .95  | 8C109   | .09 | 8C109B        | .09 | BYX36-150 | .08 | ZTX54  | .20 | 2N3713 | 1.30 | 4.7  | .045 | 05  | 055 | 06 |
| 7405                         | .13  | .23 | 7495  | .52    | .80  | 4017 | .66  | 4174            | 1.10 | 8C110   | .11 | BZ261C3-      |     | ZTX56     | .25 | 2N3714 | .20 | 6.8    | .045 | 05   | 055  | 06  |     |    |
| 7406                         | .24  |     | 7496  | .50    |      | 4018 | .70  | 4175            | 1.10 | 8C109C  | .12 | E10V          | .16 | ZTX58     | .20 | 2N3715 | .13 | 10     | .05  | 06   | 07   | .09 |     |    |
| 7407                         | .24  |     | 7497  | 1.90   |      | 4019 | .42  | 4194            | 1.10 | 8C142   | .25 | BZ782-2v7-    |     | 2N3716    | .20 | 2N3716 | .12 | 22     | .10  | 12   | 16   | 22  |     |    |
| 7408                         | .14  | .20 | 74100 | .90    |      | 4020 | .75  | 4404            | .88  | 8C143   | .25 | 8C143         | .25 | 2N3717    | .12 | 2N3717 | .12 | 33     | .07  | 08   | 10   | 15  |     |    |
| 74508                        | .40  | .20 | 74104 | .42    |      | 4021 | .75  | 4412            | .25  | 8C147   | .25 | 8C147         | .25 | 2N3718    | .12 | 2N3718 | .12 | 47     | .08  | 10   | 12   | 19  |     |    |
| 7409                         | .14  | .22 | 74105 | .40    |      | 4022 | .68  | 4428            | .68  | 8C148   | .09 | 8C148         | .09 | 2N3719    | .12 | 2N3719 | .12 | 68     | .09  | 12   | 16   | 23  |     |    |
| 7410                         | .12  | .20 | 74107 | .25    | .38  | 4023 | .15  | 4445            | 1.30 | 8C149   | .09 | 8C149         | .09 | 2N3720    | .12 | 2N3720 | .12 | 100    | .10  | 13   | 18   | 26  |     |    |
| 7411                         | .19  | .22 | 74109 | .30    | .38  | 4024 | .60  | 4449            | .28  | 8C157   | .10 | 8C157         | .10 | 2N3721    | .12 | 2N3721 | .12 | 150    | .11  | 15   | 20   | 28  |     |    |
| 7412                         | .15  | .23 | 74110 | .38    |      | 4025 | .15  | 4501            | .17  | 8C158   | .11 | 8C158         | .11 | 2N3722    | .12 | 2N3722 | .12 | 220    | .12  | 16   | 22   | 32  |     |    |
| 7413                         | .25  | .35 | 74111 | .60    |      | 4026 | .90  | 4502            | .80  | 8C159   | .11 | 8C159         | .11 | 2N3723    | .12 | 2N3723 | .12 | 330    | .14  | 18   | 26   | 36  |     |    |
| 7414                         | .50  | .76 | 74112 | .38    |      | 4027 | .36  | 4503            | .62  | 8C171   | .11 | 8C171         | .11 | 2N3724    | .12 | 2N3724 | .12 | 470    | .16  | 20   | 29   | 40  |     |    |
| 7415                         | .24  | .24 | 74113 | .30    | .38  | 4028 | .58  | 4506            | .48  | 8C172B  | .11 | 8C172B        | .11 | 2N3725    | .12 | 2N3725 | .12 | 680    | .10  | 24   | 35   | 48  |     |    |
| 7417                         | .24  |     | 74115 | 1.25   | .38  | 4029 | .66  | 4507            | .48  | 8C172H  | .11 | 8C172H        | .11 | 2N3726    | .12 | 2N3726 | .12 | 1000   | .20  | 29   | 41   | 56  |     |    |
| 7420                         | .12  | .20 | 74118 | .82    |      | 4030 | .35  | 4508            | .21  | 8C178   | .15 | 8C178         | .15 | 2N3727    | .12 | 2N3727 | .12 | 29     | .41  | .56  |      |     |     |    |
| 7421                         | .22  | .22 | 74119 | 1.30   |      | 4031 | .95  | 4511            | .80  | 8C182/L | .11 | 8C182/L       | .11 | 2N3728    | .12 | 2N3728 | .12 | 3.3    | .30  | 48   | 65   | 95  |     |    |
| 7422                         | .18  | .23 | 74120 | .85    |      | 4032 | .95  | 4510            | .80  | 8C183/L | .11 | 8C183/L       | .11 | 2N3729    | .12 | 2N3729 | .12 | 4700   | .47  | 60   | 90   |     |     |    |
| 7423                         | .22  |     | 74121 | .25    |      | 4033 | 1.20 | 4512            | .70  | 8C184/L | .11 | 8C184/L       | .11 | 2N3730    | .12 | 2N3730 | .12 | 6.3v   | .20  | 63v  | 20   |     |     |    |
| 7425                         | .22  |     | 74122 | .42    |      | 4034 | 1.80 | 4513            | 1.60 | 8C208   | .12 | 8C208         | .12 | 2N3731    | .12 | 2N3731 | .12 | 800uf  |      | 8.3v | 20   |     |     |    |
| 7426                         | .24  | .26 | 74123 | .40    | .72  | 4035 | 1.10 | 4514            | 2.50 | 8C212/L | .12 | 8C212/L       | .12 | 2N3732    | .12 | 2N3732 | .12 | 4700uf |      | 6.3v | 20   |     |     |    |
| 7427                         | .24  | .28 | 74124 | 1.75   |      | 4036 | 2.80 | 4515            | 2.50 | 8C213/L | .11 | 8C213/L       | .11 | 2N3733    | .12 | 2N3733 | .12 | 6.3v   | .20  | 6.3v | 20   |     |     |    |
| 7428                         | .28  | .32 | 74125 | .35    | .46  | 4037 | .90  | 4517            | 3.80 | 8C214/L | .13 | 8C214/L       | .13 | 2N3734    | .12 | 2N3734 | .12 | 4700uf |      | 6.3v | 20   |     |     |    |
| 7430                         | .12  | .20 | 74126 | .35    | .46  | 4038 | .90  | 4518            | .70  | 8C237B  | .16 | 8C237B        | .16 | 2N3735    | .12 | 2N3735 | .12 | 6.3v   | .20  | 6.3v | 20   |     |     |    |
| 74530                        | .90  |     | 74128 | .65    |      | 4039 | 2.50 | 4519            | .42  | 8C238   | .15 | 8C238         | .15 | 2N3736    | .12 | 2N3736 | .12 | 4700uf |      | 6.3v | 20   |     |     |    |
| 7432                         | .23  | .24 | 74130 | .90    |      | 4040 | .70  | 4520            | .70  | 8C272   | .13 | 8C272         | .13 | 2N3737    | .12 | 2N3737 | .12 | 6.3v   | .20  | 6.3v | 20   |     |     |    |
| 7433                         | .23  |     | 74132 | .50    | .78  | 4041 | .75  | 4521            | 1.80 | 8C278   | .13 | 8C278         | .13 | 2N3738    | .12 | 2N3738 | .12 | 4700uf |      | 6.3v | 20   |     |     |    |
| 7437                         | .22  | .25 | 74134 | .36    |      | 4042 | .58  | 4522            | .85  | 8C282   | .11 | 8C282         | .11 | 2N3739    | .12 | 2N3739 | .12 | 6.3v   | .20  | 6.3v | 20   |     |     |    |
| 7438                         | .22  | .25 | 74135 | .65    |      | 4043 | .60  | 4523            | .85  | 8C287   | .11 | 8C287         | .11 | 2N3740    | .12 | 2N3740 | .12 | 4700uf |      | 6.3v | 20   |     |     |    |
| 7440                         | .13  | .25 | 74136 | .55    | .38  | 4044 | .90  | 4524            | 1.10 | 8C290   | .11 | 8C290         | .11 | 2N3741    | .12 | 2N3741 | .12 | 6.3v   | .20  | 6.3v | 20   |     |     |    |
| 7441                         | .90  |     | 74137 | .80    |      | 4045 | 1.20 | 4528            | .95  | 8C292   | .11 | 8C292         | .11 | 2N3742    | .12 | 2N3742 | .12 | 4700uf |      | 6.3v | 20   |     |     |    |
| 7442                         | .43  |     | 74138 | .60    |      | 4046 | .99  | 4529            | 1.10 | 8C297   | .15 | 8C297         | .15 | 2N3743    | .12 | 2N3743 | .12 | 6.3v   | .20  | 6.3v | 20   |     |     |    |
| 7443                         | .75  |     | 74139 | .60    |      | 4047 | .90  | 4530            | .90  | 8C311   | .15 | 8C311         | .15 | 2N3744    | .12 | 2N3744 | .12 | 4700uf |      | 6.3v | 20   |     |     |    |
| 7444                         | .74  |     | 74141 | .56    |      | 4048 | .45  | 4531            | .80  | 8C312   | .15 | 8C312         | .15 | 2N3745    | .12 | 2N3745 | .12 | 6.3v   | .20  | 6.3v | 20   |     |     |    |
| 7445                         | .55  |     | 74142 | 2.00   |      | 4049 | .36  | 4532            | 1.05 | 8C315   | .10 | 8C315         | .10 | 2N3746    | .12 | 2N3746 | .12 | 4700uf |      | 6.3v | 20   |     |     |    |
| 7446                         | .62  |     | 74143 | 2.50   |      | 4050 | .35  | 4534            | 4.50 | 8C317   | .10 | 8C317         | .10 | 2N3747    | .12 | 2N3747 | .12 | 6.3v   | .20  | 6.3v | 20   |     |     |    |
| 7447                         | .50  | .80 | 74144 | 2.50   |      | 4051 | .58  | 4536            | 3.00 | 8C321   | .13 | 8C321         | .13 | 2N3748    | .12 | 2N3748 | .12 | 4700uf |      | 6.3v | 20   |     |     |    |
| 7448                         | .50  | .95 | 74145 | .58    |      | 4052 | .58  | 4539            | .78  | 8C324   | .11 | 8C324         | .11 | 2N3749    | .12 | 2N3749 | .12 | 6.3v   | .20  | 6.3v | 20   |     |     |    |
| 7449                         | 1.00 |     | 74147 | 1.10   |      | 4053 | 1.00 | 4541            | 1.00 | 8C328   | .11 | 8C328         | .11 | 2N3750    | .12 | 2N3750 | .12 | 4700uf |      | 6.3v | 20   |     |     |    |
| 7450                         | .13  |     | 74148 | .90    |      | 4054 | 1.00 | 4543            | 1.28 | 8C333   | .80 | 8C333         | .80 | 2N3751    | .12 | 2N3751 | .12 | 6.3v   | .20  | 6.3v | 20   |     |     |    |
| 7451                         | .13  | .21 | 74150 | .70    |      | 4055 | .80  | 4549            | 3.25 | 8C335   | .40 | 8C335         | .40 | 2N3752    | .12 | 2N3752 | .12 | 4700uf |      | 6.3v | 20   |     |     |    |
| 7453                         | .13  |     | 74151 | .50    | .65  | 4056 | .20  | 4555            | .82  | 8C339   | .10 | 8C339         | .10 | 2N3753    | .12 | 2N3753 | .12 | 6.3v   | .20  | 6.3v | 20   |     |     |    |
| 7454                         | .13  | .18 | 74153 | .50    | .55  | 4057 | .16  | 4558            | 3.65 | 8C356   | .24 | 8C356         | .24 | 2N3754    | .12 | 2N3754 | .12 | 4700uf |      | 6.3v | 20   |     |     |    |
| 7455                         | .13  | .18 | 74154 | .85    | 1.20 | 4058 | .16  | 4559            | 1.55 | 8C358   | .23 | 8C358         | .23 | 2N3755    | .12 | 2N3755 | .12 | 6.3v   | .20  | 6.3v | 20   |     |     |    |
| 7456                         | .13  |     | 74155 | .52    | .96  | 4059 | .34  | 4562            | 4.45 | 8C360   | .20 | 8C360         | .20 | 2N3756    | .12 | 2N3756 | .12 | 4700uf |      | 6.3v | 20   |     |     |    |
| 7457                         | .13  |     | 74156 | .52    | .96  | 4060 | .14  | 4565            | .80  | 8C362   | .20 | 8C362         | .20 | 2N3757    | .12 | 2N3757 | .12 | 6.3v   | .20  | 6.3v | 20   |     |     |    |
| 7470                         | .28  |     | 74157 | .52    | .96  | 4061 | .16  | 4569            | 1.55 | 8C368   | .24 | 8C368         | .24 | 2N3758    | .12 | 2N3758 | .12 | 4700uf |      | 6.3v | 20   |     |     |    |
| 7472                         | .24  |     | 74157 | .53    | .55  | 4062 | .14  | 4593            | .38  | 8C371   | .18 | 8C371         | .18 | 2N3759    | .12 | 2N3759 | .12 | 6.3v   | .20  | 6.3v | 20   |     |     |    |
| 7473                         | .25  | .34 | 74158 | .58    | .60  | 4063 | .14  | 4594            | 1.50 | 8C375   | .18 | 8C375         | .18 | 2N3760    | .12 | 2N3760 | .12 | 4700uf |      | 6.3v | 20   |     |     |    |
| 7474                         | .25  | .35 | 74159 | 2.00   |      | 4064 | .16  | 4599            | 1.00 | 8C379   | .18 | 8C379         | .18 | 2N3761    | .12 | 2N3761 | .12 | 6.3v   | .20  | 6.3v | 20   |     |     |    |
| 74874                        | .90  |     | 74160 | .60    | 1.20 | 4065 | .64  | 4596            | .90  | 8C380   | .16 | 8C380         | .16 | 2N3762    | .12 | 2N3762 | .12 | 4700uf |      | 6.3v | 20   |     |     |    |
| 7475                         | .32  | .40 | 74161 | .65    | .75  | 4066 | .64  | 4599            | .90  | 8C382   | .16 | 8C382         | .16 | 2N3763    | .12 | 2N3763 | .12 | 6.3v   | .20  | 6.3v | 20   |     |     |    |
| 7476                         | .28  | .34 | 74162 | .65    | 1.20 | 4067 | .13  | 4599            | 1.00 | 8C383   | .16 | 8C383         | .16 | 2N3764    | .12 | 2N3764 | .12 | 4700uf |      | 6.3v | 20   |     |     |    |
| 7478                         | .38  |     | 74163 | .65    | .75  | 4068 | .64  | 4599            | .90  | 8C384   | .16 | 8C384         | .16 | 2N3765    | .12 | 2N3765 | .12 | 6.3v   | .20  | 6.3v | 20   |     |     |    |
| 7480                         | .45  |     | 74164 | .70    | 1.10 | 4069 | .34  | 4597            | 3.25 | 8C385   | .16 | 8C385         | .16 | 2N3766    | .12 | 2N3766 | .12 | 4700uf |      | 6.3v | 20   |     |     |    |
| 7481                         | .90  |     | 74165 | .70    | 1.10 | 4070 | .13  | 4599            | 1.00 | 8C386   | .16 | 8C386         | .16 | 2N3767    | .12 | 2N3767 | .12 | 6.3v   | .20  | 6.3v | 20   |     |     |    |
| 7482                         | .75  |     | 74166 | .80    |      | 4071 | .43  | 4565            | 1.15 | 8C387   | .16 | 8C387         | .16 | 2N3768    | .12 | 2N3768 | .12 | 4700uf |      | 6.3v | 20   |     |     |    |
| 7483                         | .60  | .75 | 74167 | 2.50   |      | 4072 | .14  | 4593            | .38  | 8C388   | .16 | 8C388         | .16 | 2N3769    | .12 | 2N3769 | .12 | 6.3v   | .20  | 6.3v | 20   |     |     |    |
| 7484                         | .90  |     | 74170 | 1.35   | 2.00 | 4073 | .13  | 4595            | .90  | 8C389   | .16 | 8C389         | .16 | 2N3770    | .12 | 2N3770 | .12 | 4700uf |      |      |      |     |     |    |

# BORIS IN CHECK

There are quite a few chess machines lying around the shops these days, and this one has a reputation for being one of the best. Armed with his "Best of Spassky Volume 2" Ron Harris went to check it out.

BORIS is a multi-level chess machine with the disconcerting ability to comment on its opponent's (your) moves. The level of its analysis is set by the user who determines how long BORIS may consider its reply. Thus a tyro may set the machine to minimum time to begin with, and steadily advance the machine as he improves.

## Present Arms

The presentation of the machine is excellent. The electronics consist of an F8 based system accessed by a 16 (multi-function) key array and interfaced to the outside world by a display consisting of eight alpha numeric devices. These are packed into a very smart wooden case which also holds the mains adaptor and chess pieces. A board is also provided, but is of a standard which suggests it is included out of duty rather than devotion. Alas, the chess pieces fall into this lamentable category also, but improvements are now being made by the importers, and the quality of replacements is much higher.


On the two units we were able to examine the mains adaptor terminates in a two pin American 'hi-fi' type of plug — which now fails BS of course. This is moulded into the adaptor body and makes life very awkward for the buyer. At first glance there is no way of getting mains into BORIS aside from wrapping wires around them. DANGEROUS. The importers *must* look into this very quickly. We are assured they are doing so — let us hope.

In the meanwhile I would advise purchasers to take a trip down to good ole Woolies and make off with one of their shaving adaptor plugs, into which BORIS's adaptor will neatly plug. 240V AC is a poor opening gambit in any game.
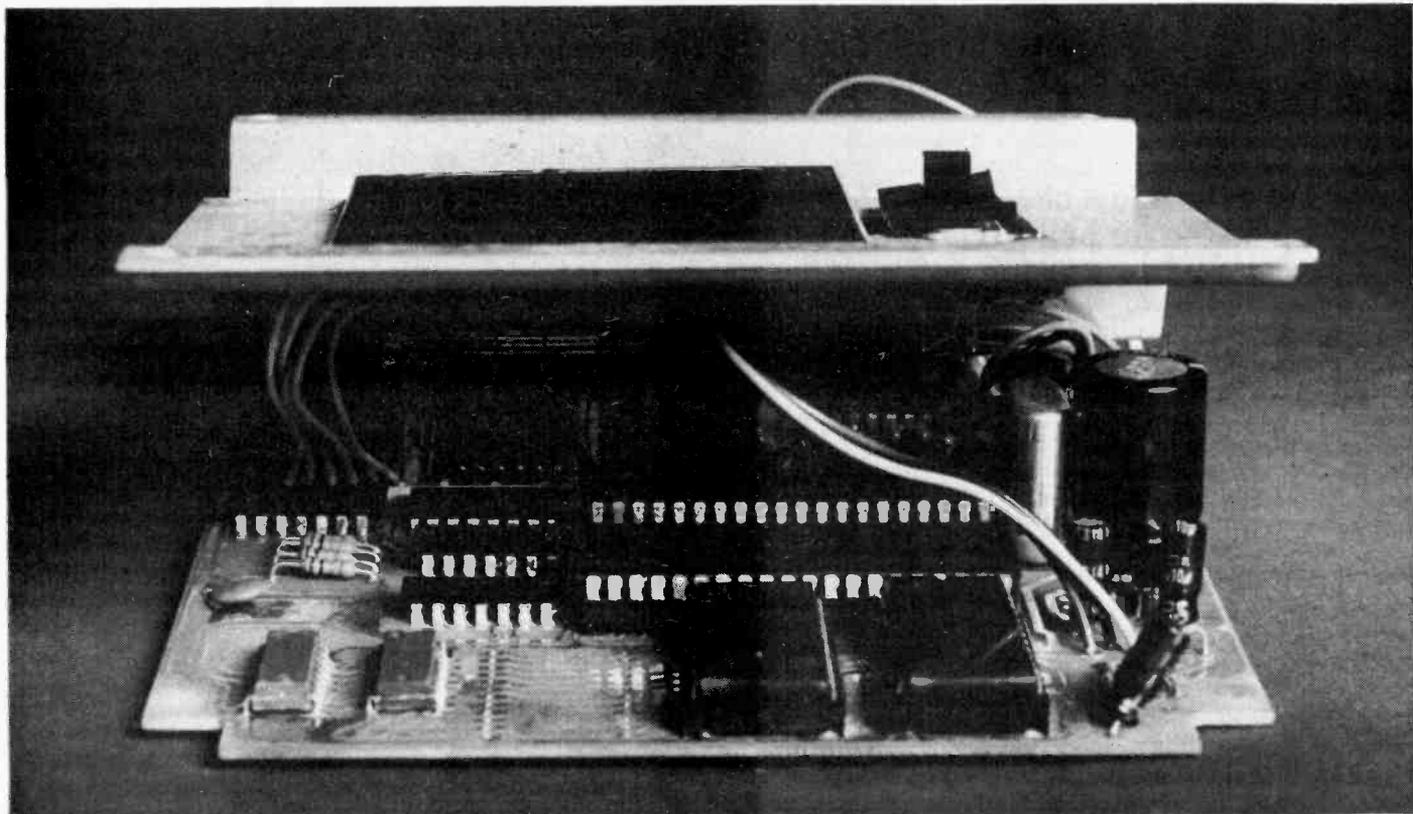
## Getting Rooked . . . and Pawned And . . .

Using this machine is both simple and interesting. The keyboard sets up your move on the display — which is also showing elapsed time — and the ENTRY key presents it to BORIS for reply. ▶





**BORIS exposed to the world!**

Once he's thinking about, the display flashes at 1 Hz, the timer counts down the time allotted to BORIS and the various moves he's cogitating appear on the display, settling finally at time 00 seconds. The display then counts down *your* time — but there's no penalty for not playing inside the time limits you've imposed on BORIS.

If for some reason (like cheating) you wish to alter the board at any time during a game, pressing RANK displays the contents of each row of the board using a very ingenious symbols set. The keyboard now creates or destroys pieces as required. Korchnoi could have done with *that* in his armoury. This makes correcting errors very easy.

Use of the RANK key while BORIS is having a think lets you watch the pieces moving around in his head(!?). Hypnotic.

### Alpha-numeric Big Mouth


Undoubtedly the first thing to impress about BORIS has nothing to do with his chess abilities. It's his big mouth. Exactly how many comments his PROMs contains is anyone's guess — the importers Optimisation aren't saying — but we counted 47 in two evenings of chess, and I don't think we got them all!

The comments appear in the eight displays and are clocked along right to left at about 2Hz. At any position on the board the program limits BORIS to a shortlist of appropriate comments, and a 'random' choice is made amongst them — or indeed not to comment at all. Saying nothing is the most likely choice of all, which means that the sayings do not always appear and so do not become boring with repetition.
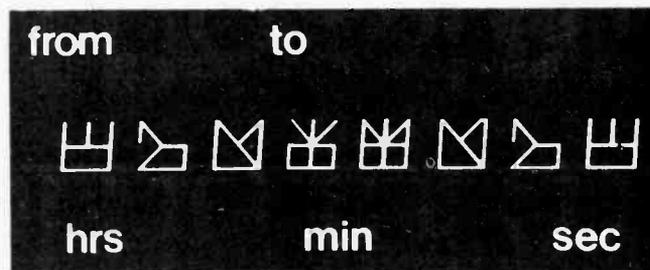
### Play It Again BORIS

Once in play BORIS is a fair match for most people. On its basic level the machine plays a good beginner's game, and will find most things you leave lying around the board. Responses differ sufficiently even at this level to make 'psyching out' difficult. The biggest drawback of BORIS's chess is his passion for exchanging pieces.

Being cowards we started at this level to see what he could do. The first comment we got was 'AWFUL' to our opening move. Frightening! From here we kept increasing the time BORIS had to think about his answers. At five minutes he was winning consistently, and at two it's a long, long struggle to get him to lie down and die!



The symbols BORIS uses to identify the chess pieces. Shown here is the back rank of the white men. The black appear upside down so you can tell which men are which. Pawns appear as triangles.

## FEATURE: Boris

Below: BORIS in play at the computer chess championship recently. He finished second to a private program.



We're only average chess players ourselves and so passed the infernal pawn-pusher onto a club standard player to get his comments.

On the longer response times, five minutes upwards, he considered BORIS a good opponent — and of course wouldn't admit how often he'd lost! Certainly everyone who had a game against him considered BORIS entertaining — the comments really do seem appropriate at times.

For example, in the middle of a game with BORIS hard pressed and the telephone ringing — I NEED LESS NOISE appears! Coincidence but fun all the same. One move away from being checkmated and he asks READY TO RESIGN? The classic must be after losing a queen to a knight fork — WHOOPS!

### Conclusions

All in all then BORIS can be confidently recommended to anyone interested in the game of chess. It can play a good game, and entertain while doing so. It is very difficult indeed *not* to think of the machine containing an (evil) little elf — a grand master type elf — plotting against your every manoeuvre, and unleashing sarcastic comments where possible. A definite winner. **ETI**

Our thanks to Kramer and Co for their assistance in the preparation of this article — they lent us a BORIS! (They also supply to the public!)

## GREENWELD

443 Millbrook Road Southampton  
SO1 0HX Tel: (0703) 772501

All prices quoted include VAT. Add 25p UK/BFPO Postage. Most orders despatched on day of receipt. SAE with enquiries please. MINIMUM ORDER VALUE £1. Official orders accepted from schools, etc. (Minimum invoice charge £5). Export/Wholesale enquiries welcome. Wholesale list now available for bona-fide traders. Surplus components always wanted.

### BUY A COMPLETE RANGE OF COMPONENTS AND THESE PACKS WILL HELP YOU

- \* **SAVE ON TIME**—No delays in waiting for parts to come or shops to open!
- \* **SAVE ON MONEY**—Bulk buying means lowest prices—just compare with others!
- \* **HAVE THE RIGHT PART**—No guesswork or substitution necessary!

ALL PACKS CONTAIN FULL SPEC. BRAND NEW, MARKED DEVICES—SENT BY RETURN OF POST. VAT INCLUSIVE PRICES.

**K001** 50V ceramic plate capacitors. 5%. 10 of each value 22pF to 1000pF. Total 210. **£3.35**

**K002** Extended range, 22pF to 0.1µF. 330 values **£4.90**

**K003** Polyester capacitors. 10 each of these values: 0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1, 0.15, 0.22, 0.33, 0.47µF. 110 altogether for **£4.75**

**K004** Mylar capacitors, min 100V type. 10 each all values from 1000pF to 10,000pF. Total 130 for **£3.75**

**K009**. Extended mylar pack. Contains all values from 1000pF to 0.47µF. Total 290 capacitors to **£11.25**

**K005** Polystyrene capacitors. 10 each value from 10pF to 10,000pF. E12 Series 5% 160V. Total 370 for **£12.30**

**K006** Tantalum bead capacitors. 10 each of the following: 0.1, 0.15, 0.22, 0.33, 0.47, 0.68, 1, 2.2, 3.3, 4.7, 6.8, all 35V; 10/25, 15/16 22/16 33/10 47/6 100/3. Total 170 tants for **£14.20**

**K007** Electrolytic capacitors 25V working, small physical size. 10 each of these popular values: 1, 2.2, 4.7, 10, 22, 47, 100µF. Total 70 for **£3.50**

**K008** Extended range, as above, also including 220, 470 and 1000µF. Total 100 for **£5.90**

**K021** Miniature carbon film 5% resistors, CR25 or similar. 10 of each value from 10R to 1M, E12 series. Total 610 resistors **£6.00**

**K022** Extended range, total 850 resistors from 1R to 10M **£8.30**

**K041** Zener diodes, 400mW 5% BZY88, etc. 10 of each value from 27V to 36V, E24 series. Total 280 for **£15.30**

**K042** As above but 5 of each value **£8.70**

### STEREO AMPLIFIER CHASSIS £5.50

Complete and ready built. Controls: Bass, treble, volume/on-off, balance. 8 transistor circuit gives 2 watts per channel output. Just needs transformer and speakers for low cost stereo amp. Suitable metal cabinet (W374) **£2.00** — or buy the amp, case and transformer for **£10.00** and get DIN speaker sockets and knobs free!!

### AMPLIFIER KIT £1.75

Mono gen. purpose amp with tone and vol./on-off controls. Utilizes sim. circuitry to above amp. Output 2W into 8 ohms. Input matched for crystal cartridge. 4 transistor circuit. Simple to build on PCB provided. Can be either battery or mains operated. (For mains powered version add **£2.20** for suitable transformer). Blue vinyl covered aluminium case to suit (W372) **£1.30**.

### BC182B OFFER

Special Offer for quantity users. 1k .035 + VAT, 5k .032 + VAT. Price negotiable on 10k + approx. 80k available.

### PC ETCHING KIT MK III

Now contains 200 sq. ins. copper clad board, 1lb. Ferric Chloride, DALO etch-resist pen, abrasive cleaner, two miniature drill bits, etching dish and instructions. **£4.25**.

### EDGE CONNECTORS

Special purchase of these 0.1" pitch double-sided gold-plated connectors enables us to offer them at less than one-third of their original list price!  
18 way **41p**; 21 way **47p**; 32 way **72p**; 40 way **90p**.

### THE NEW 1978-9 GREENWELD CATALOGUE

#### FEATURES INCLUDE:

- \* 50p Discount Vouchers
- \* Quantity prices for bulk buyers
- \* Bargain List Supplement
- \* Reply Paid Envelope
- \* Priority Order Form
- \* VAT inclusive prices

Price 30p + 15p Post.

### HEAT SINK OFFER

Copper T05 sink 17mm dia x 20mm. 10 for 40p; 100 for **£3**; 1,000 for **£25**.

### 74 SERIES PACK

Selection of boards containing many different 74 series ICs. 20 for **£1**; 50 for **£2.20**; 100 for **£4**.

### TMS4030 RAM

4096 bit dynamic RAM with 300ns access time; 470ns cycle time; single low capacitance high level clock i/p; Fully TTL compatible; Low power dissipation. Supplied with data **£2.75**.

### MISCELLANEOUS ICs

Supplied with data if requested. MC3302 quad comp. **120p**; 710 diff comp. (T099) **40p**; ZN1034E precision timer **£2.25**; LM711 Dual diff comp **65p**; LM1303 dual stereo pre-amp **75p**; MC1469R voltage reg **£1.50**; UPC1025H audio **£3.50**; 575C2 audio **£2.88**; TDA2640 audio **£2.92**; TBAB105 audio **70p**; SN75110 dual line driver **70p**; MC8500 CRCC gen POA.

### OSCILLOSCOPES

We have available from stock the following SCOPEX models: 4D10A — DC-10MHz; 10mV sensitivity; Stab. power supplies; Dual beam; 3% accuracy. Excellent value at **£214 inc. VAT** and carriage. 4S6 — DC-6MHz; 10mV sensitivity. Ideal portable scope. Solid state circuitry. All for **£150 inc. VAT** and carriage.

### RESISTOR PACK

Carbon film 5% mostly 1/4W, few 1/2W resistors. Brand new but have pre-formed leads, ideal for PC mntg. Wide range of mixed popular values at the unrepeatable price of **£2.50** per 1,000; **£11** per 5,000.

### DIN SOCKET OFFER

2 pin switched speaker socket, PC mntg. 5 pin 180° PC mntg. or chassis mntg. (clip fix). All the same price, any mix: 10 for **70p**; 25 for **£1.60**; 100 for **£5.50**.

### PUSH BUTTON SWITCH BANKS

Lots of diff. types illustrated in Bargain List No. 6 — send SAE for your copy.

### RELAYS

WB47 Low profile PC mntg 10 x 33 x 20mm 6V coil. SPCO 3A contacts **93p**.  
WB32 Sub. min type. 10 x 19 x 10mm 12V coil DPCO 2A contacts **£1.15**.  
W701 6V SPCO 1A contacts 20 x 30 x 25mm Only **56p**.  
WB17 11 pin plug in relay, rated 24V AC, but works well on 6V DC. Contacts 3 pole c/o rated 10A. **95p**.  
WB19 12V 1250R DPCO 1A contacts. Size 29 x 22 x 18mm min. plug-in type **72p**.  
WB39 50V ac (24V DC) coil. 11 pin plug-in type. 3 pole c/o 10A contacts. Only **85p**.  
WB46 Open construction mains relay. 3 sets 10A c/o contacts. **£1.20**.  
Send SAE for our relay list — 84 types listed and illustrated.


### LOW COST PLASTIC BOXES

Made in high impact ABS. The lids are retained by 4 screws into brass inserts. Interior of box has PCB guide slots (except V219).  
V210 80x62x40mm black **58p**  
V213 100x75x40mm black **72p**  
V216 120x100x45mm black **86p**  
V219 120x100x45mm white **86p**

### DIODE SCOOP!!!

We have been fortunate to obtain a large quantity of untested, mostly unmarked glass silicon diodes. Testing a sample batch revealed about 70% useable devices — signal diodes, high voltage rets and zeners may all be included. These are being offered at the incredibly low price of **£1.25** / 1,000 — or a bag of 2,500 for **£2.25**. Bag of 10,000 **£8**. Box of 25,000 **£17.50**. Box of 100,000 **£60**.

## ASSEMBLED LATCHED COUNTER MODULES

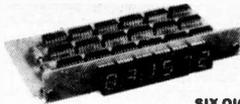

SIX DIGIT TTL COUNTER MODULE

Our range of Industrial Latched Counter Module Kits is now available ready-built. These counters use both CMOS and TTL ICs and will save you considerable design, purchasing, building and de-bugging time. Each module uses a set of red LED displays, and features a single in-line plug and socket. Instructions are provided. For full details please send for Catalogue.

|         | TTL      |        |          | CMOS   |          |        |          |        |
|---------|----------|--------|----------|--------|----------|--------|----------|--------|
|         | Part No. | Built  | Part No. | Kit    | Part No. | Built  | Part No. | Kit    |
| 2 digit | 401-404  | £13.22 | 328-412  | £18.52 | 885-988  | £13.82 | 948-478  | £18.42 |
| 4 digit | 715-884  | £23.98 | 657-412  | £17.98 | 512-568  | £22.63 | 885-478  | £18.11 |
| 6 digit | 293-484  | £33.78 | 721-412  | £25.88 | 393-568  | £32.31 | 191-478  | £25.85 |

## NEW PRICES AND SOME NEW CMOS ADDITIONS

If you need your CMOS by return - buy it from SINTEL

|        |      |        |      |        |      |         |      |         |      |
|--------|------|--------|------|--------|------|---------|------|---------|------|
| CD4000 | 0.15 | CD4027 | 0.44 | CD4051 | 0.82 | CD4086  | 0.84 | CD40182 | 1.40 |
| CD4001 | 0.17 | CD4028 | 0.77 | CD4052 | 0.82 | CD4089  | 1.39 | CD40192 | 1.40 |
| CD4002 | 0.17 | CD4029 | 1.03 | CD4053 | 0.82 | CD4093  | 0.80 | CD40193 | 1.40 |
| CD4006 | 1.04 | CD4030 | 0.50 | CD4054 | 1.04 | CD4094  | 1.89 | CD40194 | 1.19 |
| CD4007 | 1.18 | CD4031 | 2.00 | CD4055 | 1.18 | CD4095  | 0.84 | CD40257 | 1.48 |
| CD4008 | 0.87 | CD4032 | 0.89 | CD4056 | 1.18 | CD4096  | 0.94 | CD4502  | 0.81 |
| CD4009 | 0.80 | CD4033 | 1.28 | CD4058 | 4.28 | CD4097  | 3.35 | CD4510  | 1.01 |
| CD4010 | 0.50 | CD4034 | 1.71 | CD4060 | 1.00 | CD4098  | 0.88 | CD4511  | 1.25 |
| CD4011 | 0.18 | CD4035 | 1.06 | CD4063 | 0.98 | CD4099  | 1.65 | CD4514  | 2.47 |
| CD4012 | 0.20 | CD4036 | 2.88 | CD4066 | 0.55 | CD4100  | 2.50 | CD4515  | 2.82 |
| CD4013 | 0.43 | CD4037 | 0.85 | CD4067 | 3.35 | CD4101  | 1.61 | CD4516  | 1.01 |
| CD4014 | 0.83 | CD4038 | 0.98 | CD4068 | 0.20 | CD4102  | 2.13 | CD4518  | 0.97 |
| CD4015 | 0.83 | CD4039 | 2.78 | CD4069 | 0.20 | CD4103  | 2.13 | CD4520  | 1.04 |
| CD4016 | 0.48 | CD4040 | 0.97 | CD4070 | 0.46 | CD4104  | 1.10 | CD4527  | 1.43 |
| CD4017 | 0.79 | CD4041 | 0.75 | CD4071 | 0.20 | CD4105  | 1.06 | CD4532  | 1.21 |
| CD4018 | 0.83 | CD4042 | 0.69 | CD4072 | 0.20 | CD4106  | 0.82 | CD4555  | 0.78 |
| CD4019 | 0.50 | CD4043 | 0.88 | CD4073 | 0.20 | CD4107  | 0.89 | CD4556  | 0.78 |
| CD4020 | 1.11 | CD4044 | 0.84 | CD4075 | 0.20 | CD4108  | 5.38 | MC14528 | 0.83 |
| CD4021 | 0.80 | CD4045 | 1.28 | CD4076 | 1.17 | CD4109  | 1.03 | MC14553 | 4.43 |
| CD4022 | 0.82 | CD4046 | 1.20 | CD4077 | 0.39 | CD4160  | 1.19 | IM6508  | 8.05 |
| CD4023 | 0.18 | CD4047 | 0.89 | CD4078 | 0.20 | CD4161  | 1.19 |         |      |
| CD4024 | 0.70 | CD4048 | 0.50 | CD4081 | 0.20 | CD4162  | 1.19 |         |      |
| CD4025 | 0.20 | CD4049 | 0.50 | CD4082 | 0.20 | CD4163  | 1.19 |         |      |
| CD4026 | 1.55 | CD4050 | 0.43 | CD4085 | 0.84 | CD40181 | 3.40 |         |      |

For our full range of components send for Free Catalogue

Our offices are at Chapel Street, Oxford, but please do not use this as a postal address.

PRICES VALID UNTIL 31st MARCH, 1979

OFFICIAL ORDERS ARE WELCOME from Companies, Govt. Depts. Natn. Inds., Univs. Polys.

ORDERS: C.V.O. add VAT @ 8% + 35p p&p; TELEPHONE and CREDIT (invoice) ORDERS add VAT @ 8% + 60p p&p minimum charge (the balance will be charged at cost). Please see FAST SERVICE EXPORT ORDERS welcome, no VAT but add 10% (Europe), 15% (Overseas) for Air Mail p&p. For Export postage rates on heavy items - contact us first.

ORDERS TO: SINTEL, PO BOX 75A, OXFORD  
Tel: 0865 49791

FAST SERVICE: We guarantee that Telephone Orders for goods in stock, received by 4.15 p.m. (Mon.-Fri.) will be despatched on the same day by 1st Class Post (some heavy items by parcel post) and our stocking is good. Private customers should telephone and pay by giving their Access or Barclaycard number, with a minimum order value of £5. Official orders, no minimum.



**SINTEL**

## LISTEN TO THE SECRET WORLD OF PLANTS

As featured on Horizon, Nationwide, Radio and Worldwide Press

FIRST TIME IN THE U.K. IN KIT FORM, THE REVOLUTIONARY CONCEPT OF A BIOLOGICAL AMPLIFIER AND SOUND SYNTHESISER IN ONE UNIT, THE AMAZING

## Bio Activity Translator



- ★ Experience the unique musical form of plants
- ★ Hear the beautiful patterns of sound - created by their natural response
- ★ Compare house plants reactions to people - with the distinct tunes of those outside
- ★ Easy to operate, internal speaker and batteries

The naturally generated bio electrical potential across a plant leaf is picked up by 2 carbon foam electrodes. When amplified and filtered, a VCO, VCA and other exclusive synthesiser circuits are programmed by the control voltage from the plant to produce tracking sequences of notes. These follow in pitch, rhythm and volume the ever changing signal from the plant.

The Kit includes 6 I.C.s, 3 transistors, all high quality components, tinned and drilled fibreglass p.c.b., loudspeaker and comprehensive assembly instructions. Also included is a free case, ready punched, with wooden end cheeks and stick-on silk-screened front panel for a really professional finish. Runs on 2 4½-volt batteries (not supplied).


**SPECIAL INTRODUCTORY OFFER INCLUDES FREE CASE**  
KIT £19.90 ASSEMBLED AND TESTED £27.50 Price includes P & P and VAT

Allow 21 days for delivery. OFFER ENDS DECEMBER 31, 1978

JEREMY LORD SYNTHESISERS  
52 BECMEAD AVENUE, LONDON SW16 1VQ

# ETI

## Ladies LCD Watch

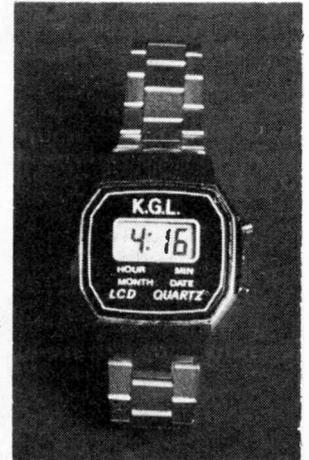

... and don't you ever say we don't listen to you again! Ever since we first did a gentlemen watch, we have been dealing with a constant never ending stream of requests for a ladies model. Well at long last we can claim to have done something about it!

It wasn't easy arranging this sort of price on a product this good - but ETIs done it again! The watch is small enough to look good on the prettiest wrist, and accurate enough to satisfy the most fastidious. Normal display shows time of course, with both date and seconds available on a push of a button. A backlight is also included.

Battery life should be greatly in excess of a year, and the bracelet is a smart stainless steel.

# £9.95

Inclusive of VAT and Postage

An example of this watch can be seen and examined in our reception at our Oxford Street offices.

LADIES LCD WATCH

To:  
**Ladies LCD Watch Offer**  
**ETI Magazine**  
**25-27 Oxford Street**  
**London W1R 1RF**

Please find enclosed my cheque/PO for **£9.95** (made payable to ETI Magazine) for a ladies LCD watch

Name .....

Address .....

Please allow 14 days for delivery.

# MARKET PLACE

## Digital Alarm



Size: 105mm wide 115mm deep x 55 mm high.

THIS IS THE THIRD digital alarm clock that we are offering (we regret the earlier versions are no longer available). We have sold thousands and thousands of these and our buying power enables us to offer a first rate branded product at a really excellent price.

The Hanimex HC-1100 is designed for mains operation only (240V/50Hz) with a 12 hour display, AM/PM and Alarm Set indicators incorporated in the large display. A switch on the top controls a Dim/Bright display function.

Setting up both the time and alarm is simplicity itself as buttons are provided for both fast and slow setting and there's no problem about knocking these accidentally as a 'locking' switch is provided under the clock. A 9-minute 'snooze' switch is located at the top.

### £8.95

Inclusive of VAT and Postage

An example of this clock can be seen and examined in our reception at our Oxford Street offices.

**DIGITAL ALARM**

To:  
Hanimex Alarm Offer  
ETI Magazine  
25-27 Oxford Street  
London W1R 1RF

Please find enclosed my cheque PO for £8.95 (payable to ETI Magazine) for a Hanimex Digital Alarm Clock.

Name .....

Address .....

.....

.....

Please allow 28 days for delivery

## LCD Watch



**New low price!**

The enormous numbers involved in ETI offers has enabled us to arrange a real bargain — a full spec LCD watch with adjustable metal bracelet for under half the going rate.

This watch gives continuous display of hours and minutes: press the button once and you'll get the date (American style). After a couple of seconds the display automatically reverts to time but if you press again you'll get a continuous seconds display.

Press another button and you get a back light, enabling you to see the display in the dark. Setting, or resetting is simplicity itself and a 'hold' facility allows you to set the watch spot on. The accuracy is magnificent, as with all the current range of digital watches and battery life is well in excess of a year.

### £8.95

(Inclusive of VAT and Postage)

An example of this watch can be seen and examined in our reception at our Oxford Street offices.

**LCD WATCH**

To:  
LCD Watch Offer  
ETI Magazine  
25-27 Oxford Street  
London W1R 1RF

Please find enclosed my cheque/PO for £8.95 (made payable to ETI Magazine) for my LCD Digital Watch.

Name .....

Address .....

.....

.....

Please allow 14 days for delivery



# audiophile.....

**What would you say if we told you about a cartridge which has a totally new stylus shape, a new improved magnet structure and revolutionary two part cantilever system — and a new radically different method of controlling operating conditions? It is all true, and its been around a few months too! Ron Harris took his time getting to the V15 Mk.4 — but found it worth the wait!**

IT HAS BEEN some time now since the launch of the V15 IV from Shure, and by now I hope all the fuss has died down. Never has a product been rumoured to appear for so long, and met with such polarised comment when it did. In the meanwhile since the release the cartridge has slowly gained ground, and now would appear to be highly regarded in all but the most partisan anti-moving-magnet circles.

## Changes By Design

There is a lot in this design to interest the engineer, so let's consider that aspect first. The criteria to be met were to produce a cartridge which performed as close to perfection as possible under ideal conditions, and which went some way to creating those conditions.

The ambition I applaud!

Naturally these days computer analysis of just about anything numerically expressible was undertaken — and quite right too! Everything down to body size and mass were considered, and then more models set up to attempt to blend the whole design successfully. (I don't think it would be an outrageous suggestion to make that the SME Series III was used as the optimum arm in all these cavortings.




The new features to come out of all this are a dynamic stabiliser — and it's *not* just a brush, a new cantilever assembly, a new stylus shape, and a static reduction system. In addition the effective mass of the dynamic system has been lowered significantly.

## Tipped For Shape

Shure have decided, somewhat bravely, to go it alone and produce a new stylus profile. The reason is they wanted lower distortion but without sacrifice of low wear and trackability in the process.

Any design for a stylus *must* include consideration of such factors as the actual groove itself, tip mass, manufacturing cost, record wear etc etc.

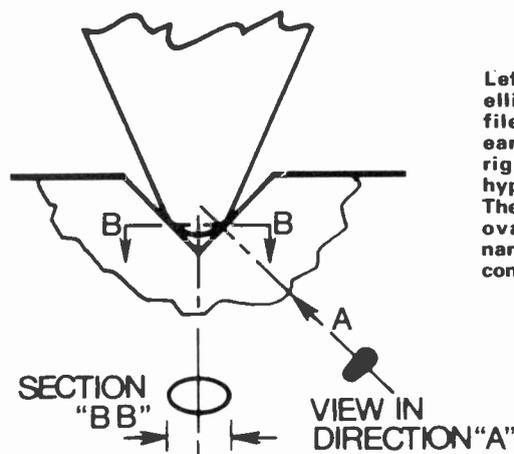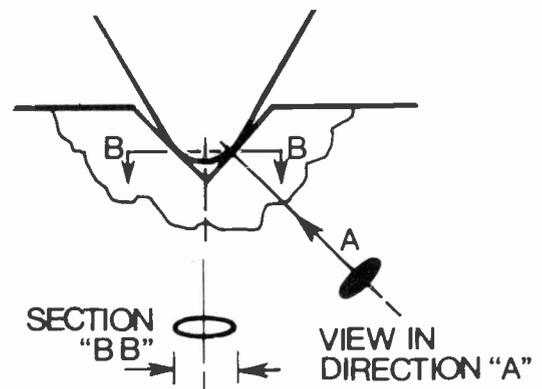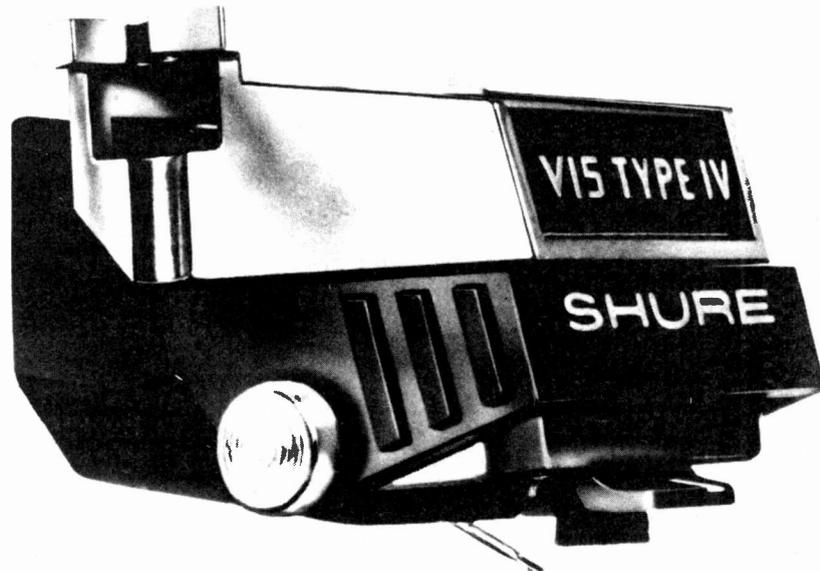As you can see from the diagram the end result of Shures endeavours is a long contact profile, basically a hyperbola from the front, termed a hyperelliptical design. Its actual contact radius is around 38 microns, while its tracing radius (parallel to groove tangent) is smaller than other types. The compromise does appear to offer advantage over other types, right enough.



Left: a conventional elliptical stylus profile, as used in the earlier V15/III, and right, the new hyperelliptical profile. The "footprint" (black oval) is longer and narrower than in the conventional profile.

## Magnetic Heart

The cantilever assembly is always the first section to come under scrutiny whenever a cartridge is to be improved, (just shows what improvements *could* be made if you ask me!) and it has not escaped this time.

After much playing with computers and trading off advantages against system requirements, Shure put themselves some prototypes together and carted them off for listening tests. Measurements, mathematical models and ears later a telescopic two element design emerged as the overall best solution, and was duly adopted.

Part of the reason for this is vibration control — presumably to suppress resonances excited by dynamic stresses — and this is assisted by an elastomer damping device. The earlier M24 featured something like this, but not so sophisticated apparently.

The magnet itself is of a new type, of lower mass but higher strength than its predecessors, allowing the cantilever unit mass as a whole to be lower. Taken together the improvements to the system are claimed to provide better high frequency tracking ability, and the shifting of the HF resonance to beyond 20 kHz.

## Brush Up On Damping

Now down to the obvious bit — which I had to do last just to keep you reading. Static on records can be blamed for most of the ills besetting disc reproduction as it now stands. It attracts dust — and holds it — leading to quicker wear of both disc and stylus and higher replay noise.

There are umpteen devices on the market for clearing static charge, most of which resemble gas lighters. But Shure make the valid point that unless you know what polarity the charge is you're trying to clear, you've a 50-50 chance of making it worse by pumping ions at it.


Another nasty well-known to LPs of all age groups is the warp. Warps come free with most records these days and provide such delights as variation in tracking angle, mis-tracking due to effective reduction of applied tracing force and overall disruption of the ideal conditions in which cartridges like to operate.

Damping applied at the arm pivots can help with this, but represent a compromise at best. It is better to have the control as close to the tip as possible. The dynamic stabiliser is designed to do exactly that. The carbon fibre brush is mounted to ride just ahead of the stylus, and is equipped with viscous damped pivots. These are designed to absorb the shock produced by a warp, be it gradual or sudden. The optimum distance between cartridge body and record is thus preserved.

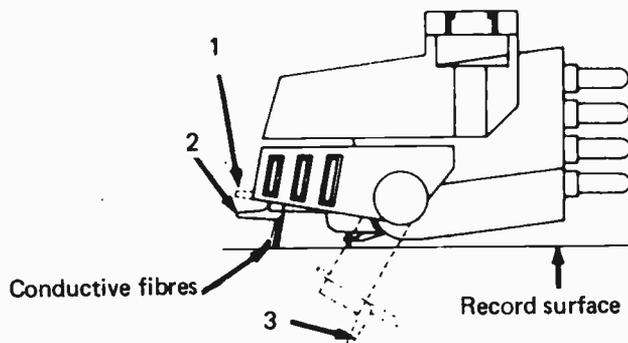
## Bristling With Pride

That brush is made up of about 10,000 carbon fibre bristles, ten of which would fit nicely into a record groove. Since it is carbon fibre it is conductive and can leak static charges to system earth since it is connected to one channel earth. Shure's research has indicated too that local static charges can increase tracking force by attracting the cartridge to the LP!


Sounds logical once someone tells you doesn't it? The brush does a good job shifting dust and muck out of the way too!



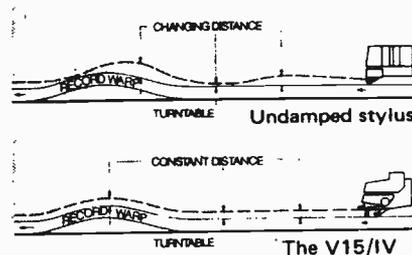The outrigger carbon-fibre brush may be set in any one of three positions: 1) in the "Up" position. 2) the dynamic stabiliser in its operating position 3) set down as a guard.



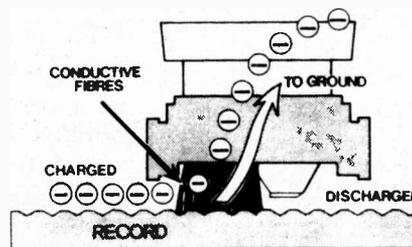
The V15 Type IV's brush with damped pivot is said to aid the tracking of warped discs by matching stylus movement more closely to the motion of the arm



The carbon-fibre brush is in continuous contact with one of the earth pins and leaks static charges to earth.
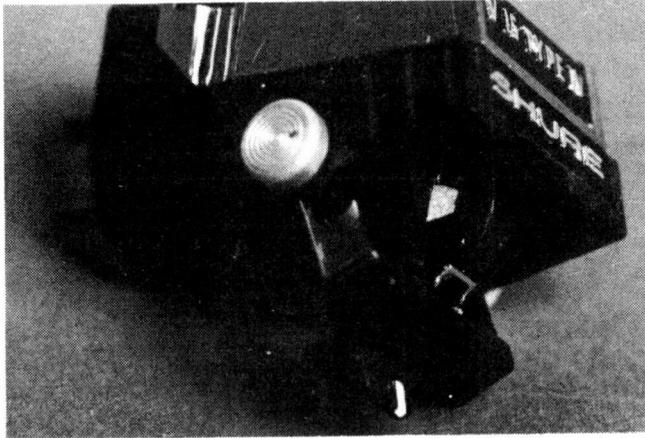
## Having A Fit

Setting up the V15 was very simple indeed. It's a shame to have to take it out of the box at all unfortunately, the packaging is superb indeed! Holding the body into the arm is done by screwing into a small metal block tapped for the bolts. Simpler than using fiddly nuts — if you'll pardon the expression — but probably more massive.



A close-up view of the stabiliser fitted to the V15 Mk-4, reposing in its guard position. The white line tells you where to line up the stylus when at play!

Because of the stabiliser, the stylus sees 0.5g less than is applied to the arm as a whole. This means that to get 1g tracking force, you set 1.5g. It can look confusing at first, and don't forget later and clip up the stabiliser, else the cantilever gets the lot!

### Tracing Class

After brief experiments, all our tests were conducted with 1g applied to the stylus, as the V15 tracked anything at this weight, regardless of how torturous we made our torture tracks. I failed to catch it out even once. Foiled again. One to Shure.

In contrast to the Mk3 the new model is sensibly specified for capacitive loading, and is apparently as insensitive to these things as it can be. Using a Sony TA-88 preamp enabled me to vary the loading while the cartridge was playing — a reviewer's delight! No adverse effects can be expected in normal use. Noise seems to be reduced too.

The stabiliser does offer real benefits as it definitely aids tracking and makes the system as a whole very tolerant of record 'flatness'. I tried the cartridge with and without pivot damping on the SME and would suggest it be used *with* damping — it somehow gains confidence that way!

### Sound Stuff?

This is the bit where I lose some 'musical' friends no doubt, because whatever anyone may have said amid the initial rash of reviews you will not find a cartridge better at information retrieval than the V15 IV. Its sound is incredibly detailed, and free from audible vices. It has a nice confidence about it altogether, and did not mis tracks — or mis-anything — even once.

The sound has an overall smoothness that is perhaps its most 'nameable' feature. The bass quality is good, although I have heard better. In the mid-range and treble the sound stands forward towards the listener presenting a good stable image with all the detail you could wish for, with no trace of hardness or brightness whatsoever.

### Conclusions

So there it is — interesting and worth the wait for its appearance. Whether you like the sound of the V15 or not only you can tell, but if you're considering spending around £70 on a cartridge you'd be ill-advised to miss listening to it.

### Main Trouble

One of the most oft repeated queries to Audiophile concerns the problem of mains borne clicks and pops appearing out of loudspeakers.

Unfortunately there is no immediate overall solution. The first thing to try is to move either the hi-fi or the appliance — usually a fridge — causing the clicks to another outlet.


If this doesn't work then there are several suppressors on the market, at varying prices, to deal with the trouble. The most expensive is the QED unit at about £10. It does work in most cases, but no more so than some others.

The cheapest such unit available is probably the RS mains suppressor. Your local component stockist should be able to order this for you, and fitting it is pretty simple. Its input comes from the mains, and its output feeds the hi-fi in question.

### Otherwise

If none of this works then pretty obviously your problem is not mains borne. For radiated problems there's not much you can do except move things around. This is pretty rare though.

### Change Of Load

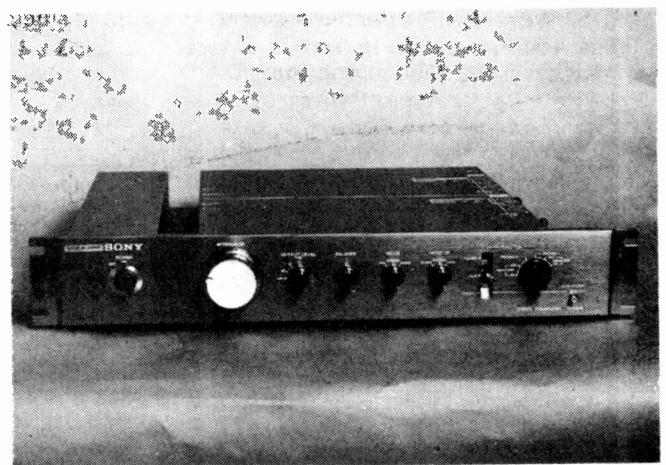

Above is the Sony TA88E preamp I mentioned a couple of months ago. Next month I'll be going through the circuits of this device in detail, as it represents a job done very very properly. At £699 so it should. The effect of all this engineering on the sound proved to be interesting too.

ETI



# A TECHNICAL MEMORANDUM

By Simian

DURING THE LAST FEW weeks some valuable research work has been incorporated into BSI and MIL standards, and this will greatly ease the specification of equipment. These standards help to combat a hitherto neglected environmental hazard; the users of equipment. A range of Standard Idiots (SIDs) has been defined, and these will be useful additions to any development laboratory.

## Using Standard Idiots

Standard Idiots are useful both for acceptance testing of incoming equipment, and for developing foolproof electronics. The latter is of particular value to manufacturers producing consumer goods. In general the technique of using SIDs is very simple: it consists merely of letting them come into contact with the equipment to be tested. Any flaws will be quickly shown up.

SIDs locate ergonomic faults very rapidly. It is instructive to watch them at work sometimes. If something is weak, they will break it; if no-one in their *right* minds would dry-off a poodle in a microwave oven, they will do just that.

Almost all old-style quality-control testing can be abolished. If SIDs are allowed to get at all products before they leave the factory, it will be found that only the perfect get through. This reduces the number of complaints received from users, but the cost of disposing of the rejects (in bulk) can be rather high.

## Types of Standard Idiot

Several specialist schools have been set up to train SIDs since these students are not well received at normal colleges. The coursework is intensive, and there are rigorous examinations to maintain standards. Over 600 people have received a Diploma in Idiocy (Dip. I) to date.

Many people have been found to have a natural aptitude for this work.

There are various grades of SID, ranging from the merely incompetent to those capable of sinking the Titanic, and there are many specialist fields:

(1) The 'non-technical' person (BS 91000-FOOL). This type normally panics when faced with more than two control knobs simultaneously. She (sometimes he) always mis-tunes radios, and would be hard put to it to recognise the difference between a watch and an oil refinery.

(2) Fiddler, or fidgeter (MIL-ID-99436/010). This

type is rapidly becoming an industry standard; the real world is full of them. If, for example, there is a switch controlling a lamp, the fiddler will flick it on and off for hours until either it breaks, or he spots something more exciting to play with. He will also use calculators to divide numbers by zero or to find  $\arcsin(-10)$ .

(3) The Ph.D (MIL-ID-12345/678) never reads instruction manuals. 'Of course, it's obvious that this piece of equipment works like so . . .' It is only when clouds of blue smoke issue from a new £2,000 oscilloscope that he scuttles back to his desk to read in the unused handbook that this model is for 110V, not 240V.

Ph.Ds are often quite intelligent.

(4) Dismantler. A member of this species is guaranteed to dismember any piece of equipment which he owns or uses. However, it is very rare for the article ever to be re-assembled. (They are usually foxed by the new child-proof pill boxes).

There are a few other specialist categories: for example, the 'jonah', whose mere presence in a room is enough to make clocks stop and television sets neurotic; or the Standard Irishman with fourteen fingers.

## Disadvantages

One major problem with SIDs is that of storage when they are not in use. Obviously they cannot be left to roam freely around the lab.! Normal work under these conditions is difficult. Even when they are stored in cupboards the voluble and plaintive cries of 'let me out' are disruptive.

There is another hazard which should not be overlooked: there have been a few unfortunate cases where standard idiots have been mistaken for engineers. Most of the companies where this has happened have now ceased trading.

## Conclusions

Standard idiots, in their present form, can be useful development tools, but there are associated hazards; on no account should they be left alone to amuse themselves. The new specifications are a major advance in a naturally chaotic field and standard idiots are adding a new dimension to destructive testing. This technological advance is helping to provide jobs for those people whose natural talents previously made them unemployable.

ETI

# SECOND GENERATION INDUCTION BALANCE METAL DETECTOR

DESIGNED SPECIALLY  
FOR THE HOME  
CONSTRUCTOR

EASY  
TO  
BUILD



EASY  
TO  
USE

- A second generation Induction Balance system with improved Variable-Tone detection.
- Designed by professionals for easy assembly by amateurs but with very good performance.
- The search coils are fully assembled and adjusted for you.
- Automatically rejects ground effect

Uses include:

- ★ Treasure hunting — it's amazing what you can find in the garden or on the beach.
- ★ Finding lost metallic items.
- ★ Locating waterpipes and cables under floorboards or in walls.
- ★ Checking old timber for nails before cutting, etc., etc., etc.

**KIT - COMPLETE WITH PRE-  
ASSEMBLED SEARCH COILS**

**£16.50**

Plus £1-00p&p Plus £1-32 VAT

**ASSEMBLED & TESTED**


**£22.50**

Plus £1-00p&p Plus £1-80 VAT

Send sae for free components stocklist

**Communication Measurement Ltd**  
15 MALLINSON OVAL, HARROGATE, YORKS.

## NON-SUBSCRIBERS START HERE

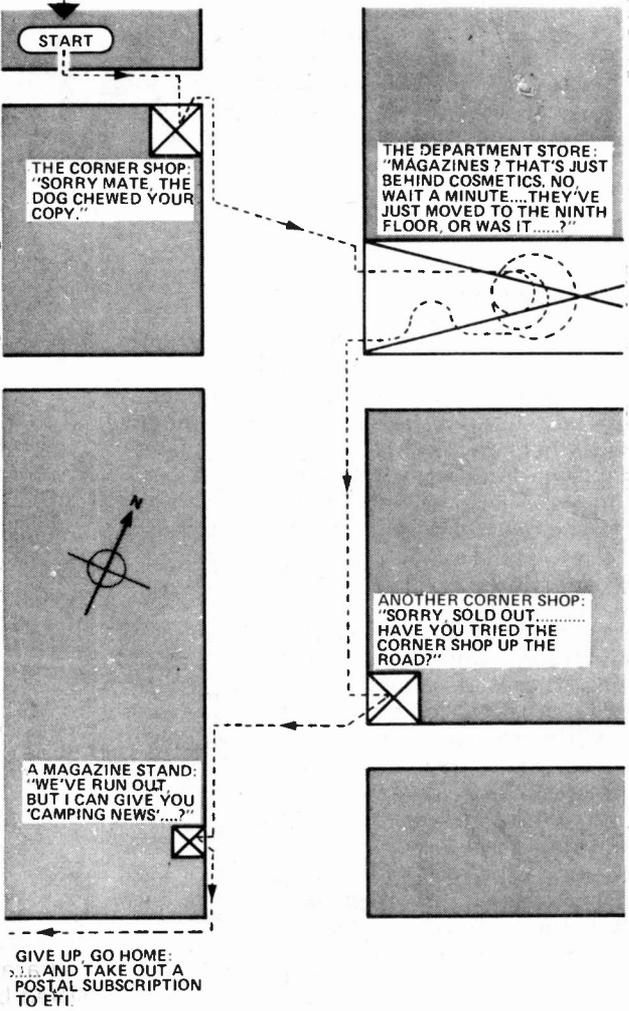


It can be a nuisance can't it, going from newsagent to newsagent? "Sorry squire, don't have it — next one should be out soon."

Although ETI is monthly, it's very rare to find it available after the first week. If it is available, the newsagent's going to be sure to cut his order for the next issue — but we're glad to say it doesn't happen very often.

Do yourself, your newsagent and us a favour. Place a regular order for ETI; your newsagent will almost certainly be delighted. If not, you can take out a postal subscription so there's nothing for you to remember — we'll do it for you.

For a subscription, send us £7.00 (£8.00 overseas) and tell us which issue you want to start with. Please make your payment (in sterling please for overseas readers) to ETI Subscriptions and keep it separate from any other services you want at the same time.

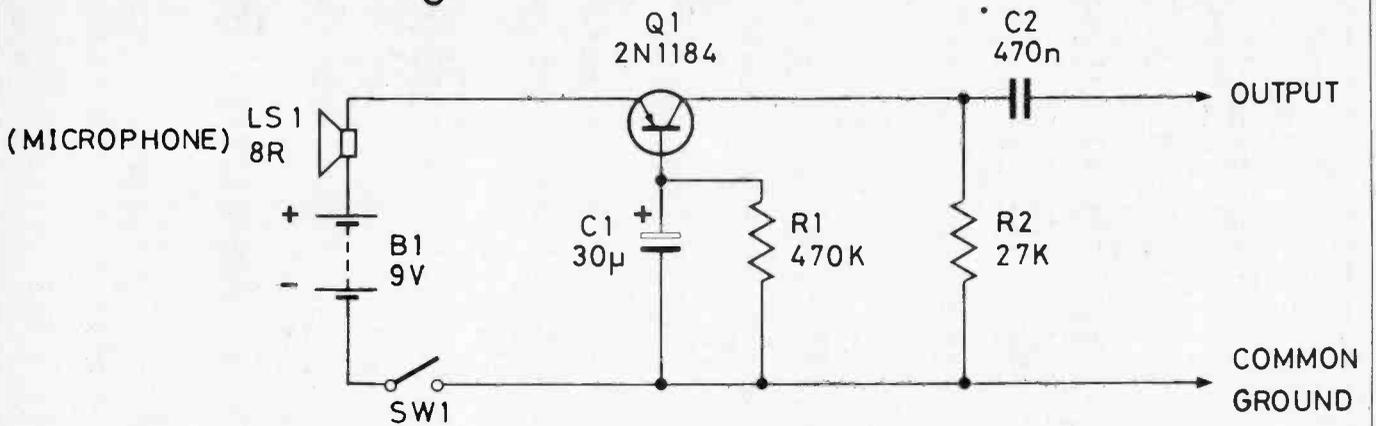**ETI Subscription Service**  
**Electronics Today International**  
25-27 Oxford Street, London W1R 1RF



### Microphone Speaker

J. Smith

What do you do if you need a microphone in a hurry — the shops are closed and your friends are on holiday? Or you are just a little short of money? The answer is to build the following circuit from your odds and ends box. This circuit uses a small speaker as a microphone, one transistor and only four other parts, draws only about 2 mA of current from a 9 volt battery so an on/off switch is not really necessary.

The transistor shown is 2N1184 and is a PNP germanium medium power type but is not critical — try the ones you have first before buying this new type. The components too are not critical and the prototype was found to work OK with 20% variation in values. The output is high impedance and is fed into the mic input of a tape recorder or pick-up input of an amplifier.

### Speed Alarm

D. Ian

It is all too easy, during a long journey on a motorway, to allow one's speed to gradually creep beyond that point which the boys in blue take an unwelcome interest; this alarm gives an audible nudge whenever you drift over a pre-set speed.


Pulses from the distributor points (due to the ignition coil up to 400V may be developed as the points open) are passed through a current limiting resistor, rectified and clipped at 4V7. Via Q1 and the diode pump a DC voltage, which is proportional to engine revs, is presented to RV1; the sharp transfer characteristic of a CMOS gate, assisted by feedback, is used to enable the oscillator formed by the remaining half of the 4011.

At the pre-set 'speed' (revs) a non-

ignorable tone emits from the speaker, and disappears as soon as the speed drops by three or four mph.

Calibration of Ca may be conducted with an accurate pulse generator remembering that, for a four stroke engine, frequency = revs per minute times the number of cylinders divided by 120; for a car with a specification of 17½ MPH per 1000 revs, in top gear,  $f = 133\text{Hz}$  at 70 MPH, 124Hz at 65 MPH (4000 RPM and 3714 RPM). The necessary frequency should be fed to Q1 and VR1 set so that the alarm is just off. Reliable switching occurs on the prototypes with a change of only 5Hz (150 RPM), ie less than 3 MPH for the above example.

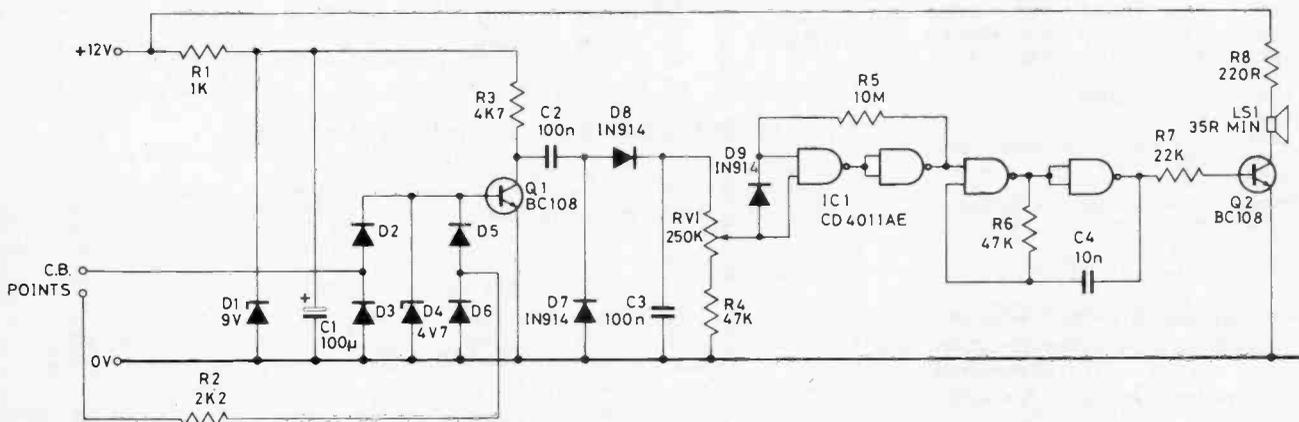Direct calibration 'on the road', while covering discrepancies due to tyre size, etc, will only be as good as the speedometer and obviously should be carried out by a passenger rather than the driver.



Tech-Tips is an ideas forum and is not aimed at the beginner. We regret we cannot answer queries on these items.

ETI is prepared to consider circuits or ideas submitted by readers for this page. All items used will be paid for. Drawings should be as clear as possible and the text should preferably be typed. Circuits must not be subject to copyright. Items for consideration should be sent to ETI TECH-TIPS, Electronics Today International, 25-27 Oxford St., London W1R 1RF.

|      |     |       |      |       |      |        |      |  |      |            |            |             |          |             |           |      |  |  |  |
|------|-----|-------|------|-------|------|--------|------|--|------|------------|------------|-------------|----------|-------------|-----------|------|--|--|--|
| 7400 | 10p | 7460  | 12p  | 74137 | 90p  | 74195  | 50p  | 4055   | 130p | CA 3140    | 60p        | LM 3909 N   | 65p      | TBA 480 Q   | 200p      |      |  |  |  |
| 7401 | 10p | 7470  | 25p  | 74138 | 100p | 74196  | 50p  | 4056   | 120p | LF 356     | 80p        | MC 1310 P   | 140p     | TBA 520 Q   | 200p      |      |  |  |  |
| 7402 | 10p | 7472  | 20p  | 74141 | 50p  | 74197  | 50p  | 4060   | 100p | LF 357     | 80p        | MC 1312 P   | 150p     | TBA 530 Q   | 200p      |      |  |  |  |
| 7403 | 10p | 7473  | 25p  | 74142 | 180p | 74198  | 100p | 4066   | 35p  | LM 211 H   | 250p       | MC 1314 P   | 190p     | TBA 540     | 200p      |      |  |  |  |
| 7404 | 12p | 7474  | 25p  | 74143 | 270p | 74199  | 100p | 4069   | 12p  | LM 300 TR5 | 170p       | MC 1315 P   | 230p     | TBA 550 Q   | 250p      |      |  |  |  |
| 7405 | 12p | 7475  | 25p  | 74144 | 270p | 74293  | 90p  | 4070   | 12p  | LM 301 AN  | 30p        | MK 50398    | 650p     | TBA 560 C   | 250p      |      |  |  |  |
| 7406 | 25p | 7476  | 25p  | 74145 | 55p  | 74L500 | 18p  | 4071   | 12p  | LM 304     | 200p       | MM 5314     | 380p     | TBA 641 A12 | 250p      |      |  |  |  |
| 7407 | 25p | 7480  | 40p  | 74147 | 100p | 745112 | 80p  | 4072   | 12p  | LM 307N    | 65p        | MM 5316     | 480p     | TBA 700     | 180p      |      |  |  |  |
| 7408 | 12p | 7481  | 85p  | 74148 | 90p  | CMOS   |      |  | 4081 | 12p        | LM 308 TO5 | 100p        | NE 529 K | 150p        | TBA 720 Q | 225p |  |  |  |
| 7409 | 12p | 7482  | 75p  | 74150 | 65p  | 4000   | 12p  | 4082   | 12p  | LM 308 DIL | 100p       | NE 555      | 25p      | TBA 750 Q   | 200p      |      |  |  |  |
| 7410 | 12p | 7483  | 75p  | 74151 | 45p  | 4001   | 12p  | 4093   | 70p  | LM 309 K   | 100p       | NE 556      | 90p      | TBA 800     | 80p       |      |  |  |  |
| 7411 | 15p | 7484  | 70p  | 74153 | 45p  | 4002   | 12p  | 4510   | 60p  | LM 310 TO5 | 150p       | NE 562 B    | 400p     | TBA 810     | 100p      |      |  |  |  |
| 7412 | 15p | 7485  | 60p  | 74154 | 70p  | 4006   | 80p  | 4511   | 70p  | LM 311 TO5 | 150p       | SAD 1024    | 1500p    | TBA 820     | 100p      |      |  |  |  |
| 7413 | 25p | 7486  | 25p  | 74155 | 45p  | 4007   | 14p  | 4516   | 65p  | LM 317 K   | 325p       | SL 917 B    | 650p     | TBA 920 Q   | 280p      |      |  |  |  |
| 7414 | 45p | 7489  | 130p | 74156 | 45p  | 4009   | 30p  | 4518   | 65p  | LM 324     | 70p        | SN 76003 N  | 150p     | TCA 270 Q   | 220p      |      |  |  |  |
| 7416 | 25p | 7490  | 25p  | 74157 | 45p  | 4011   | 12p  | 4520   | 65p  | LM 339     | 60p        | SN 76013 N  | 110p     | TCA 270 S   | 220p      |      |  |  |  |
| 7417 | 25p | 7491  | 40p  | 74160 | 55p  | 4012   | 12p  | 4528   | 80p  | LM 348 N   | 90p        | SN 76013 ND | 125p     | TCA 760     | 300p      |      |  |  |  |
| 7420 | 12p | 7492  | 35p  | 74161 | 55p  | 4013   | 30p  | 4583   | 70p  | LM 380     | 60p        | SN 76023 N  | 110p     | TCA 4500 A  | 450p      |      |  |  |  |
| 7421 | 20p | 7493  | 30p  | 74162 | 55p  | 4015   | 50p  | LINEAR   |      | LM 381 N   | 90p        | SN 76023 ND | 125p     | TDA 1008    | 350p      |      |  |  |  |
| 7422 | 15p | 7494  | 70p  | 74163 | 55p  | 4016   | 30p  | AY3 8500   | 450p | LM 382     | 90p        | SN 76033 N  | 150p     | TDA 1034    | 450p      |      |  |  |  |
| 7423 | 20p | 7495  | 45p  | 74164 | 60p  | 4017   | 50p  | CA 3039  | 70p  | LM 391     | 180p       | SN 7627 N   | 160p     | TDA 2002    | 300p      |      |  |  |  |
| 7425 | 20p | 7496  | 45p  | 74165 | 60p  | 4018   | 55p  | CA 3046  | 60p  | LM 555     | 25p        | SN 76228 N  | 180p     | TDA 2020    | 300p      |      |  |  |  |
| 7426 | 22p | 7497  | 120p | 74166 | 75p  | 4019   | 40p  | CA 3060  | 225p | LM 709 C   | 40p        | SN 76660 N  | 75p      | TL 084      | 120p      |      |  |  |  |
| 7427 | 22p | 74100 | 80p  | 74167 | 160p | 4020   | 50p  | CA 3065  | 200p | LM 710 TO5 | 60p        | TAA 300     | 100p     | XR 320      | 250p      |      |  |  |  |
| 7428 | 25p | 74104 | 40p  | 74170 | 100p | 4022   | 50p  | CA 3076  | 250p | LM 710 DIL | 65p        | TAA 350     | 190p     | XR 2206     | 450p      |      |  |  |  |
| 7430 | 12p | 74105 | 40p  | 74173 | 80p  | 4023   | 12p  | CA 3080  | 75p  | LM 723 TO5 | 40p        | TAA 550     | 35p      | XR 2207     | 450p      |      |  |  |  |
| 7432 | 20p | 74107 | 25p  | 74174 | 60p  | 4024   | 40p  | CA 3084  | 250p | LM 723 DIL | 40p        | TAA 570     | 220p     | XR 2208     | 600p      |      |  |  |  |
| 7433 | 28p | 74108 | 100p | 74175 | 60p  | 4025   | 12p  | CA 3085  | 85p  | LM 733     | 120p       | TAA 661 B   | 140p     | XR 2216     | 650p      |      |  |  |  |
| 7437 | 20p | 74166 | 75p  | 74176 | 50p  | 4026   | 80p  | CA 3086  | 60p  | LM 741     | 20p        | TAA 700     | 350p     | XR 2567     | 250p      |      |  |  |  |
| 7438 | 20p | 74109 | 25p  | 74177 | 50p  | 4027   | 30p  | CA 3088  | 190p | LM 748     | 40p        | TAA 790     | 350p     | XR 4136     | 150p      |      |  |  |  |
| 7440 | 12p | 74118 | 75p  | 74178 | 75p  | 4028   | 45p  | CA 3089  | 160p | LM 1303 N  | 100p       | TAD 100     | 150p     | XR 4202     | 150p      |      |  |  |  |
| 7441 | 45p | 74120 | 80p  | 74179 | 120p | 4029   | 50p  | CA 3090 AQ   | 360p | LM 1458    | 100p       | TAD 110     | 130p     | XR 4212     | 150p      |      |  |  |  |
| 7442 | 40p | 74121 | 25p  | 74180 | 90p  | 4030   | 30p  | CA 3123 E  | 130p | LM 3080    | 75p        | TBA 120 S   | 60p      | XR 4739     | 150p      |      |  |  |  |
| 7443 | 60p | 74122 | 35p  | 74181 | 130p | 4032   | 80p  | CA 3130  | 100p | LM 3900    | 55p        | TBA 120 T   | 85p      | ZN 414      | 100p      |      |  |  |  |
| 7444 | 60p | 74123 | 40p  | 74182 | 50p  | 4033   | 100p | IN 4148 Diodes by ITT/Texas, 100 for £1.50                         |      |            |            |             |          |             |           |      |  |  |  |
| 7445 | 65p | 74125 | 35p  | 74184 | 120p | 4040   | 60p  | Static Ram 2102 1024 x 1 bit 450 nano sec. £1.00 each              |      |            |            |             |          |             |           |      |  |  |  |
| 7446 | 50p | 74126 | 35p  | 74185 | 100p | 4043   | 60p  | 2112 256 x 4 bit 450 nano sec. £2.50                               |      |            |            |             |          |             |           |      |  |  |  |
| 7447 | 50p | 74128 | 60p  | 74188 | 320p | 4046   | 90p  | Murata Ultrasonic Transducers 40kHz, £2.00 each; £3.50 pair        |      |            |            |             |          |             |           |      |  |  |  |
| 7448 | 50p | 74130 | 120p | 74190 | 70p  | 4047   | 80p  | All prices include post and VAT                                    |      |            |            |             |          |             |           |      |  |  |  |
| 7450 | 12p | 74131 | 90p  | 74191 | 70p  | 4048   | 50p  | <b>T. POWELL</b>   |      |            |            |             |          |             |           |      |  |  |  |
| 7451 | 12p | 74132 | 45p  | 74192 | 60p  | 4049   | 25p  | 306 ST. PAULS ROAD, HIGHBURY CORNER, LONDON, N.1. TEL. 01-226 1489 |      |            |            |             |          |             |           |      |  |  |  |
| 7453 | 12p | 74135 | 90p  | 74193 | 60p  | 4050   | 25p  | Barclay / Access credit cards accepted                             |      |            |            |             |          |             |           |      |  |  |  |
| 7454 | 12p | 74136 | 80p  | 74194 | 55p  | 4054   | 100p | Shop closed from 21/12/78 to 2/1/79                                |      |            |            |             |          |             |           |      |  |  |  |

## FIRST GRADE DEVICES by MAJOR MANUFACTURERS

★ Special Xmas Offer. OF POPULAR ITEMS SELECTED FOR REGULAR REQUIREMENTS ★

|  |  |   |  |  |  |  |  |
|--|--|---|--|--|--|--|--|
| <b>TEXAS TTLs</b><br>7400 10p<br>7402 11p<br>7404 12p<br>7408 13p<br>7410 11p<br>7413 22p<br>7414 36p<br>7420 11p<br>7430 11p<br>7441 45p<br>7442 32p<br>7447 40p<br>7474 22p<br>7475 25p<br>7486 20p<br>7490 24p<br>7493 24p<br>7496 36p<br>74121 24p |  | <b>CMOS</b><br>4009 30p<br>4011 13p<br>4013 30p<br>4016 28p<br>4017 48p<br>4024 40p<br>4046 85p<br>4049 27p<br>4510 59p<br>4518 58p<br>4528 52p |  | <b>STAR OFFER</b><br>741 8 pin DIL 16p<br>555 8 pin DIL 20p<br>324 14 pin DIL 45p<br>3140 8 pin DIL 36p<br>3080 8 pin DIL 60p<br>1458 8 pin DIL 36p<br>LM380N 14 pin DIL 65p             |  | <b>VOLTAGE REGULATORS PLASTIC TO-220</b><br>1 Amp +ve 1 Amp -ve<br>5V 7805 55p 5V 7905 55p<br>12V 7812 55p 12V 7912 55p<br>15V 7815 55p 15V 7915 55p<br>100mA-T092 (+ve) 5V, 12V, 15V 25p<br>100mA-T092 (-ve) 5V, 15V 50p<br>78H05KC 5Amp/5Volts TO-3 550p |  |
| Full 74, 74LS, CMOS & Memories on offer list.  |  | <b>LOW PROFILE SOCKETS</b><br>8 Pin 9p 18 Pin 20p 24 Pin 27p<br>14 Pin 10p 20 Pin 22p 28 Pin 35p<br>16 Pin 11p 22 Pin 25p 40 Pin 43p            |  | <b>OPTO DEVICES</b><br>LEDs: 0.2" Red 14p, Green 16p, TIL209 10p.<br>DISPLAYS: FND 357 0.37" 100p Red C.C.<br>FND 500/507 0.5" 100p Red C.C./C.A.<br>TIL 321/322 0.5" 110p Red C.A./C.C. |  |  |  |

We stress the fact that we are totally quality conscious and do not offer sub-standard or rebranded products for sale.


Please send SAE for complete special offer lists  
 \*\*\*\*\*  
 QUALITY + LARGE SERVICE + STOCKS

Minimum order £10 exc. VAT.  
 DISCOUNTS { 10% on orders over £50  
 15% on orders over £100  
**OFFER CLOSES ON FEBRUARY 15, 1979**

Please add VAT to total  
 Please add Ins. P&P 54p

ABOVE OFFER VALID ONLY FOR CHQ./P.O./CASH WITH ORDER.

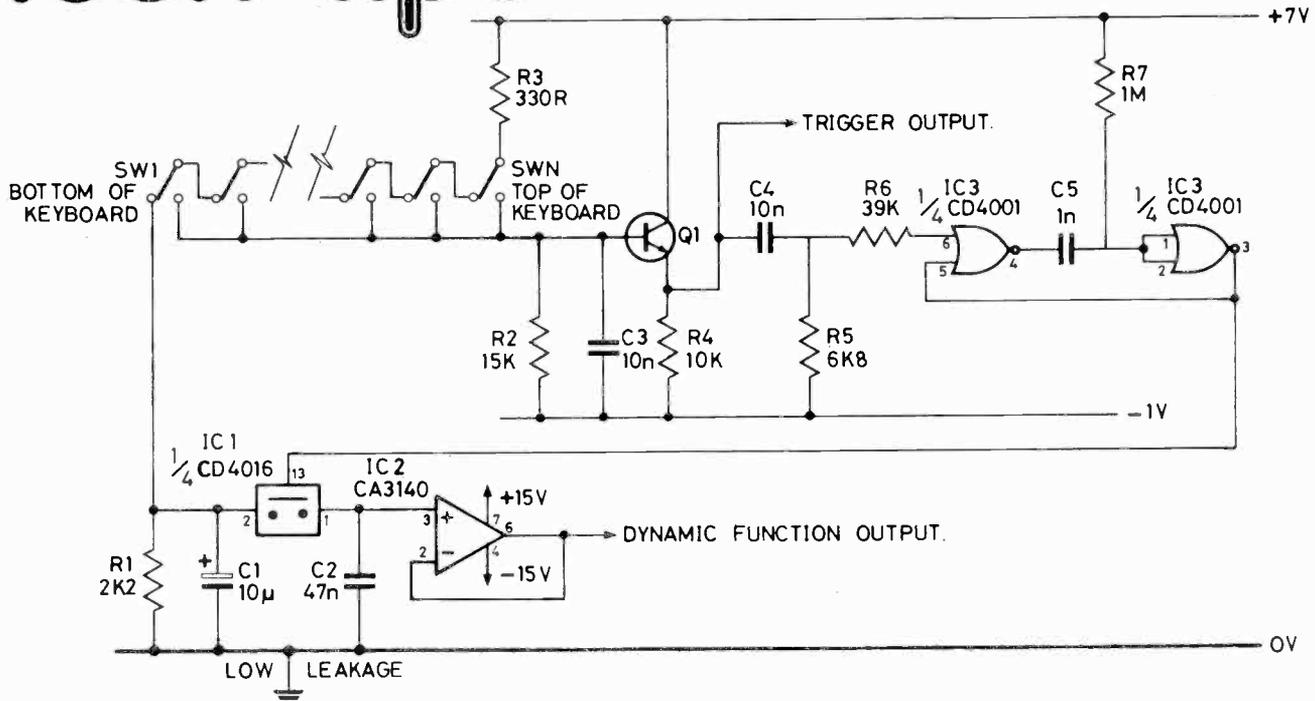**TECHNOMATIC LTD. (ETI)**  
 17 BURNLEY ROAD  
 LONDON, NW10




### Dynamic Sensitivity

W. Stride

A dynamic function (touch sensitivity) greatly increases the flexibility of expression available to the player of a music synthesizer. This circuit achieves the dynamic function by measuring the change over time of the keyboard switches, and hence the velocity of the key depressed.

The circuit is basically composed of three parts; firstly an RC time-constant network ( $R_1, C_1$ ) controlled by the keyboard switches, a buffer amplifier and monostable ( $Q_1, IC_3$ ) and a sample/hold circuit ( $IC_1, C_2, IC_2$ ).

Normally  $C_1$  is kept charged up to +7 volts through the 'chain' of closed keyboard switches. When a key is depressed, the 'chain' is broken and  $C_1$  discharges through  $R_1$ . As the key is further depressed, contact is made with the trigger busbar,  $TR_1$  is turned on, and the monostable triggered. The monostable gives out a 1 millisecond pulse, which causes the analog switch ( $IC_1$ ) to close allowing  $C_2$  to charge up to the voltage on  $C_1$  at that time. After this, the voltage is stored on  $C_2$ , the output being buffered by  $IC_2$ . Since the input impedance of IC is  $\sim 1.5 \times 10^{12}$  ohms the delay time of  $C_2$  is very long. An output is available from the emitter of  $TRQ_1$  to trigger envelope shapers etc. To make sure the response is the same all over the keyboard, the distance between the gold wires on all the contact assemblies should be made the same.

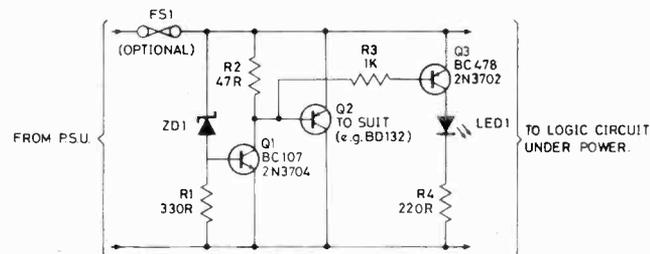

### Overvoltage Protection for Logic

E. Parr

With the introduction of integrated circuit voltage regulators it is very easy to make power supplies for logic circuits. Unfortunately it is only easy to blast a board of TTL by letting the voltage rise above 7V as could happen if the common line came off a regulator IC or the sense lines came off a commercial power supply.

The described circuit was designed by the author as a "last ditch" defence after a disconnected sense line allowed a commercial 5V supply to rise to 9V and blast 50 TTL chips. The circuit is simple to add onto any power supply, and it is the author's intention to build it "on board" with any future system containing more than about

10 TTL chips. Zener diode ZD1 senses the supply, and should the supply rise above 6V Q1 will turn on. In turn Q2 conducts clamping the rail.

Subsequent events depend on the source supply. It will either shut down, go into current limit or blow its supply fuse. None of these will damage the TTL chips.

The rating Q2 depends on the source supply, and whether it will be required to operate continuously in the event of failure. Its current rating obviously has to be in excess of the source supply. If the source supply is likely to sit down, LED1 should be added to indicate the circuit has operated.

The circuit will operate in approximately 500 nS space, so it will also protect the logic from transient spikes which a normal regulator would not block.

# SEIKO 20% OFF!

Analogue and digital from stock or to order.

## NEW FX003 MEMORY BANK



"STAR" of the 1979 Seiko range, available NOW from Tempus. Continuous display of hours, minutes, seconds, day, date, month. Displays past and future calendars from 1930 to 2009.

Flashing reminder for important dates in the coming 12 months.

R.R.P. £130

£104



NEW FB011  
R.R.P. £135

£104



FK009  
R.R.P. £55

£44



NEW FH003  
R.R.P. £165

£125

**BORIS** Communicating Chess Computer. One of the world's most advanced portable chess games. NO TV required.

£199

**CASIO FREE!** Spare batteries worth up to £1.95 with calculators below. (On request with order)

## NEW QL-10 CIGARETTE LIGHTER/CALCULATING ALARM CLOCK



Soft piezoelectric system gas lighter. 6-digit LCD clock,  $\pm 15$  seconds/month. Permanently prog. calendar (1901-2099). Two alarms plus countdown alarm/timer. Dual time zone. Calculator, with time/date calculations. K, %,  $\frac{1}{2}$  x  $2\frac{1}{4}$  x 4 inches. 3.6oz. 18 months battery Pouch

Prov. price £39.95

(RONSON electronic lighters, 10% off)

## AQ-1000 CALCULATING ALARM CLOCK PLUS 3-WAY STOPWATCH

Hours, minutes, seconds, am/pm. 24 hour Alarm with sign. Stopwatch: Net times, lap times, 1st & 2nd place times from 1/10 sec. to 10 hrs. with ST & LAP signs. Calculator: 4 key memory, %,  $\frac{1}{2}$  year batteries,  $\pm 20$  secs/month.  $\frac{1}{4}$  x  $2\frac{1}{2}$  x  $4\frac{1}{2}$  inches. RRP £26.95

Our Price £21.95



**CQ-81 CALCULATING ALARM CLOCK. Plus 2 Alarm/Timers.** 24 hour alarm and alarm/timers. 6 digit LCD clock. One year battery life.  $1\frac{1}{2}$  x  $2\frac{1}{4}$  x 5 inches. (RRP £22.95)

£17.95

**CQ-2. Special Offer.** Clock, calendar, 4 alarms, stopwatch. Time/Date calculator. (R.R.P. £39.95)

**The INCREDIBLE FX-8000.** 41 sc. funct., 1/100 sec. stopwatch, 2 x 5 alarm/timers. (£35.95)

**MINI CARD CALCULATORS**  $\frac{1}{2}$  x  $3\frac{1}{2}$  x  $2\frac{1}{2}$  ins.

**LC-78.** Full memory, %, K £16.95

**FX-48 Math. Card.** Full Scientific with S.D. £19.95

**ST-24 Card Time.** 24-hour stopwatch (or clock), 2 Alarm/Timers. Calculator as LC-78 £19.95

**ALL Casio scientifics.** Lowest prices

**ST-1.** Four way stopwatch £24.95

## CARTRIDGE T/V GAMES

**OPTIM** Coronet 600 £48.50

Cartridges from £9.95

**FAIRCHILD TIMEBAND** Grandstand £119.95

Cartridges from £12.50

**ATARI** Video Computer System £169.95

The very best available to date!

Cartridges from £14.95

**\* SPECIAL INTRODUCTORY OFFER**

TWO FREE extra cartridges worth £29.90 with Atari.

WATCH BATTERIES 65p each D.I.Y. KIT 35p

## THIS MONTH'S

### ★ STAR BUY

Just announced  
**CASIO 46CS-27B**  
ALARM/  
CHRONOGRAPH




CHRONO

Net, lap and 1st and 2nd place times from 1/100 second to 6 hours. Stainless steel case 7.8mm thick. Mineral glass face. Water resistant to 100 feet. 12 months+ battery life. Available soon.

6 digits. Hrs. mins. secs AM/PM and day, and day, date, month, year. Optional 12 or 24 hr. clock. 24 hrs. alarm. Optional hourly Chime

Prov. price £74.95

## NEW CASIO PQ-7

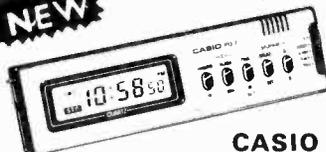

CASIO PQ-7

**TRAVEL ALARM CLOCK**

Battery-powered quartz alarm clock with repeat feature. Countdown alarm/timer. 1/10 second stopwatch. Constant LC Display. Nightlight. 1 year batteries.  $4\frac{1}{4}$  x  $1\frac{1}{4}$  x  $\frac{1}{2}$  inch. 1.6oz. For car, caravan or boat. (£24.95) £19.95.

**SOLAR powered watches** — so called. We won't sell them. Send us a S.A.E. and we will tell you why not.

**CBM Giant 4 digit.** 5 functions. Light.



9503 (£15.95)  
Chrome  
Bracelet

9502 (£14.95)  
Gilt  
Strap

£9.95  
1803 (right)  
ALARM



6 digits. 6 functions, plus backlight and alarm setting. 5-minute snooze facility (£28.95).

£22.95

## NEW THE INCREDIBLE FX-8000



**THE INCREDIBLE**  
**FX-8000**

43 Scientific funct., 1/100th sec. Stopwatch. Five Alarm/Timers, sequential (self-clearing) or repeat. 2 level parenthesis Memory. Deg Rad. Gra. Standard deviations. Fractions. Sexagesimal Rect. Polar convert. LCD 1300 hr. batteries.  $\frac{1}{4}$  x  $2\frac{1}{4}$  x  $5\frac{1}{2}$  x 2.7oz.

RRP £35.95

£29.95

## LADIES' LCD WATCHES

5 functions, backlight. Gold or Silver finish (please specify).

**Dress Watch.** Round, Milanese bracelet. L1 £14.95

**Cocktail Watches.** Integral bracelet. 3 styles £18.95



## CASIO LADIES' LCD WATCHES



7 + 2 functions  
**27CL-158**  
Round (Left)  
(£35.95)  
£29.95

**27CL-178**  
Stopwatch  
(£49.95)  
£39.95

Send 25p for our illustrated catalogue. Price include VAT and P&P. Send your cheque, PO or phone your credit card no to —

## CASIO QUALITY

All CASIO watches have a calendar display, night illumination, mineral glass and stainless steel cases, water resistant to 100 ft (except sports watches — 66).

## SPORTS WATCHES

**F-100**

Left, 9.45 mm  
(£29.95)

£24.95

**52QS-14B**  
Right 8 mm  
(£44.95)

£34.95



Up to 25 functions. Net, lap and first and second place times to 1/100th sec. F-100. Resin case, strap 52QS-14B. S/S encased version and bracelet.

**4 DIGIT WATCHES** (except World Time). Hours, minutes, ten seconds, seconds by flash, am/pm. Day, date, month. Stopwatch. Dual time (except 31QR-20B).



**31QR-20B** Left, 4 digit  
(£35.95)

£29.95

**51QR-19B.** 6 digit  
(£44.95)

£34.95

**6 DIGIT WATCHES** (except Sports and Alarm). Hours, minutes, seconds, day OR Hours, minutes, date, day, ten seconds, seconds by flash. Day, date, month, year. Selectable 12 hour (with am/pm) or 24 hour clock.

**54QS-16B**  
Left, 6 digit  
(£49.95)

£39.95

**54QS-15B**  
6 digit  
(£54.95)

£44.95



**CHRONOGRAPH.** 6 digits as above, with stopwatch measuring net, lap and 1st & 2nd place times from 1/100 sec to 6 hrs. Dual time facility.



**45CS-22B**  
Chronograph  
Left, 6 digit (£69.95)

£54.95

**29CS-11B**  
World Time (£84.95)

£69.95



**WORLD TIME WATCH.** The time in ten capitals plus one optional time. Instant summertime correction. Hrs, mins, 10 secs. secs by flash. Perpetual calendar, day, date, month. Running digital seconds display.

## ALARM WATCHES

**25CR-16B**  
Round (£74.95)

£54.95

**25CS-16B**  
Square (£84.95)

£69.95



Hours, mins, seconds (or hrs, mins, date) day, am/pm. Day, date, month, year. 24 hr. alarm, on/off indicator.

**ULTRA SLIM DRESS WATCHES** (Not 24 hour)

**53CS-18B**  
Left, 4 digit (£74.95)

£59.95

**49CS-25B**  
6 digit (£84.95)


£69.95



Not illustrated 53CS-19B, 4 digit barrel shaped £64.95. 49CS-24B, 6 digit (£79.95) £64.95. 53CS-17L, Gold plated, on strap (£84.95) £69.95.
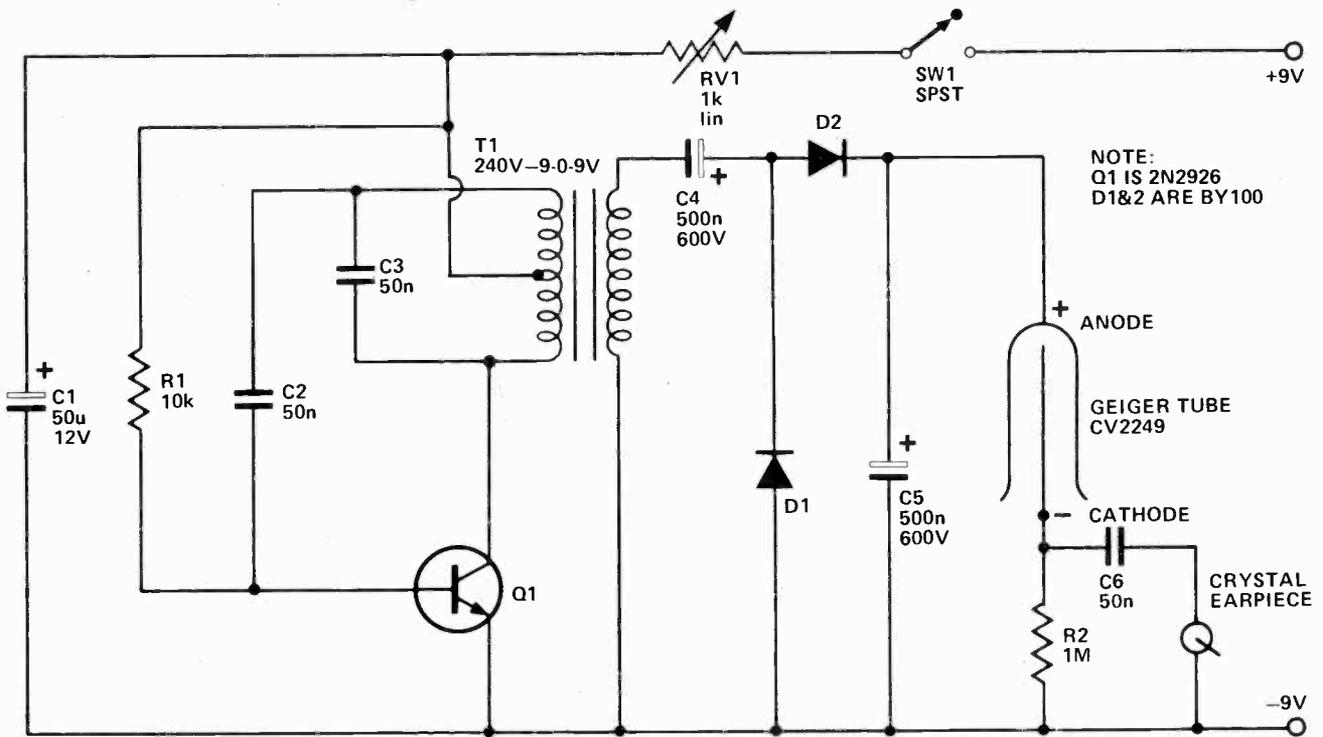
# TEMPUS

Dept. ETI, Talk of the Town  
19/21 Fitzroy Street  
Cambridge CB1 1EH. Tel. 0223 312866




NOTE:  
Q1 IS 2N2926  
D1&2 ARE BY100

### Geiger Counter

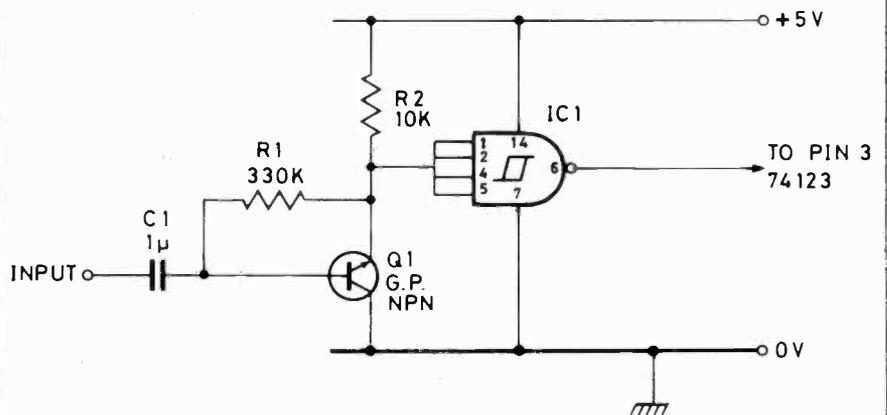A. Wheatley

Although the circuit is inexpensive and simple it is just as sensitive as many commercial devices. The important part is the geiger tube and this will probably cost about £1.90. It needs a high voltage supply which, in this case consists of Q1 and its associated components. The transformer is a low current 250V 9.0-9 and is connected in reverse. The secondary is connected into a Hartley oscillator, the base bias being provided by R1. RV1 is connected to control the voltage to the Geiger tube. A device to double the voltage is included because otherwise the voltage would still be insufficient to drive the tube. This comprises D1, D2, C4 and C5. This also rectifies it and smooths it. It is very important that C4 and especially C5 are of good quality and have low leakage. RV1 should be set so that each click heard is a nice clean one because over a certain voltage all that will be heard is a continuous buzz. The high voltage section is perfectly safe although if touched it will give a slight shock. This is unpleasant but quite harmless.



### Cuts Above

B. Houseley

The circuit here is an improved version of the original cuts encoder. If Q1 is preceded by a high impedance buffer, quite low signal levels can be accommodated successfully — and still trigger the 74123. A 74C02 or a 7402 was found to trigger only unreliably in this circuit.

**THIS MONTH'S SPECIAL OFFER**  
**"Motorola Audio Amplifier 1 watt I.C."**

1 watt plus into 8-16 Ω, 9-16V, 10-400 MV sensitivity. Short circuit proof, no heatsink required. **Only 90p** with Data and circuits.

**Sentinel Smoke and Gas Detector.** This beautifully made unit uses quality components on fibreglass board, encased in heavy duty, domed diecast box, 3½ diam. x 1½ high. LED indicator. **TGS105** plug in sensor, 24v, or 12v by altering 3 resistors, will drive relay or lamp. Ideal for caravans, boats, kitchens, etc., etc. £6.45 with circuit and data. Suitable relay for above £1, state voltage.

Miniature **Vemtron\* FM4 10.7MHz** ceramic filters. Data and circuits 20p.

50p each, 3 for £1  
**Crystal earpieces** with lead  
 40p each, 3 for £1

**Magnetic earpieces** with lead and plug  
 25p each 5 for £1

**Ultrasonic transducers** transmitter and receiver, 14mm diam 40 kcs.  
 £4.25 per pair

4 aluminium boxes 128 x 44 x 38mm, ideal for signal injectors, etc. £1.00

**100 miniature read switches**, ideal for burglar alarms, model railways, etc. £3.30

**6.6-pole 12 volt reed relays** on board £2.45

High quality **computer panels** smothered in top-grade components.  
 5lbs. £4.75  
 10lbs. £8.95

New **U.H.F. transistor TV tuners**. Rotary type with slow motion drive, aerial socket and leads. £2.50

Aluminium TV coax Plus 8 for £1

**Miniature edgewise panel mounting level meters 200u F.S.D.** 90p

300 mixed resistors ½ & ¼ watt £1.50

300 modern mixed caps most types £3.30

100 mixed **electrolytics** £2.20

300 mixed printed circuit components £1.50

300 mixed printed circuit resistors £1.00

100 high-wattage resistors, W.W., etc. £2.20

20 assorted **VDRs** and thermistors £1.20

25 assorted **presets**, skeleton, etc. £1.20

25 assorted **pots and presets** £1.50

150 mixed 1- and 2-watt resistors £1.50

**100k varicap pots**, can be banked side by side, very compact 10 for £1

100 mixed modern miniature ceramic and plate caps £1.20

**Don't let your environment dehydrate you... BUY OUR "HONEYWELL HUMIDITY CONTROLLER"**. Membrane actuated, adjustable by ¼ shaft. Ideal for greenhouses, offices, centrally heated homes, etc. 3.75A contacts at 250V. Build Humidifiers or dehydration alarms with this novel gadget at a fraction of original cost. £1 each, 3 for £2.50.

**Semiconductor Bargains**

**1000 Mixed Diodes**, mostly unmarked, similar to IN4148 etc, 70% okay £1.50

**New Improved Transistor Packs: 100** New and marked transistors including BC 148, BC 154, BF 274, BC 212L, BF 200 and lots of others, **only £4.95.**

**200 transistors** as above and including 2N3095, AC128, BD131, BFY50, **only £9.95.**

ITT 25kV c/vt triplers for Decca "Bradford" chassis brand new £2.50, 5 for £10

BD131 4 for £1.00  
 SN76115N (equivalent MC 1310) 50p  
 TBA 120A 50p

BF 200 6 - £1 BF 274 12 - £1  
 BC 212L 10 - £1 BC 148 12 - £1  
 BC 154 12 - £1

**Deluxe Fibre Glass Printed Circuit Etching Kits**

Includes 150 sq. ins. copper clad f/g board, 1lb ferric chloride, 1 dalo etch resist pen, abrasive cleaner, 2 mini drill bits, etch tray and instructions. **Only £5.30**  
 150 sq. ins. fibre glass board £2.00  
 Dalo pen 90p  
 1lb ferric chloride to mil spec. £1.25  
 5lbs ferric chloride to mil spec. £5.00  
 Instruction sheet 20p

30p P&P ON ALL ABOVE ITEMS. SEND CHEQUE OR POSTAL ORDER WITH ORDER TO SENTINEL SUPPLY DEPT., ETI, 149A BROOKMILL ROAD, DEPTFORD, LONDON, SE8

Callers by appointment only

**BUILT**  
 £247.50  
 + VAT

**NASCOM 1**  
 PERSONAL COMPUTER

**KIT**  
 £197.50  
 + VAT

**Texas I.C. Sockets Low Profile Packs of 10**

|        |      |        |      |
|--------|------|--------|------|
| 8 pin  | 1.10 | 22 pin | 1.90 |
| 14 pin | 1.20 | 24 pin | 2.20 |
| 16 pin | 1.40 | 28 pin | 2.80 |
| 18 pin | 1.70 | 40 pin | 3.30 |
| 20 pin | 1.80 |        |      |

|                   |      |
|-------------------|------|
| BC177             | 4p   |
| OC28/35/36        | 80p  |
| BD 133            | 60p  |
| BD 135/6/7/8      | 35p  |
| BO 139/40         | 36p  |
| BT106             | 1.00 |
| BU126             | 1.10 |
| BU 204/5          | 1.10 |
| TBA 800 Amp I.C.  | 70p  |
| P.C.B. Pushbutton | 35p  |
| Micro movement    | 35p  |

Minimum order £1

**1/12 Scale R/C Electric Car Kit**  
 Just add two channel R/C Porsche or Escort Body  
**£44.87**

**4 Digit Alarm Clock** chip and display G1 CK3000 I.C. + Plasma Display **£4.90**

**Microminiature Mercury Tilt Switch** **£1.00**

**12-digit Calculator Chip** Mostek 5012 4 Function Few only @ **£2.50 + 9p stamp**

**MERRY CHRISTMAS and HAPPY NEW YEAR**

**METAL DETECTORS**  
 BFO ALT3 £13.95  
 BFO 898 £9.95  
**NEW** IB 89N **£29.95\***

\* Features Speaker Meter, Telescopic Stem, Volume Control, Tuning Control, Induction Balance at BFO price. Complete with Battery and Ear Piece.

**BRISTLE DARTBOARD**  
 Only £9.95 + £1.00 P&P

**LOOK!!!**  
 8500 based T.V. Games **£3.50.** All work but have chip faults. Chess sets from **£7.30**

All prices include P&P + VAT unless shown otherwise  
**N.I.C. MODELS**  
 27 Sidney Road, London N22 4LT  
 Illustrated List of Chees Sets and Boards Send 15p  
 Please allow up to 21 days for delivery.

**COST EFFECTIVE FREQUENCY COUNTERS**



Frequency range 4Hz-32MHz  
 Sensitivity 10mV  
 Stability 1 in 10<sup>6</sup> (unovened)  
 Neon numerical indicators  
 Average or standard period facility  
 Two Tone Blue Case  
 Start/ Stop option

TYPE 401A **£138** plus VAT  
 Full range of 6 and 8 digit Counters with neon and 7 segment LED indicators, covering frequency range 4Hz-1.2GHz. Literature available. Manufacturers of Frequency Standards and Generators.



**R.C.S. ELECTRONICS**  
 6 Wolsey Road, Ashford, Middx.  
 Tel: Ashford 53661  
 (Postal Code TW15 2RB)

**BIDIRECTIONAL TEE-SHIRTS FROM ETI**



(ETI staff conference)

**HOW TO ORDER:**  
 The new red ETI tee-shirts are available in large, medium or small size for only **£2.00** inclusive of postage and packing.

Send cheques/POs to:

ETI Tee Shirts  
 25-27 Oxford Street  
 London W1R 1RF

No, she hasn't got it on backwards — the new ETI tee-shirt has ETI printed on it on **both** sides! Now you can say ETI in two directions at once!

# SERVICE TRADING CO

## WHY PAY MORE?!

**MULTI RANGE METERS Type MF15A.**  
A.C./D.C. volts 10 50 250 500 1000 Ma  
0.5 0.10 0.100 Sensitivity 2000V 24 ranges  
dimensions 133 x 93 x 46mm Price **£7.00** plus  
50p P&P (**£8.10** inc. VAT & P)



## TRIAC.

Raytheon tag symmetrical Triac Type Tag 250/500v 10 amp 500 piv  
Glass passivated plastic triac. Swiss precision product for long term  
reliability **£1.25** P&P 10p (**£1.46** inc. VAT & P) (inclusive of date and  
application sheet). Suitable Diac **22p.**

## 0 to 60 MINUTES CLOCKWORK TIMER.

Double pole 15 amp 230AC Contacts (no dial) **£1.50**, P&P 30p (**£1.94**  
inc. VAT & P) N.M.S.

## MERCURY SWITCH

Size 27m x 5mm. 10 for **£5.00**, P&P 30p. total  
VAT **£5.72**. Min quantity 10. N.M.S.



## 230 VOLT AC FAN ASSEMBLY

Powerful continuously rated AC motor complete  
with 5 blade 6 1/2 aluminium fan. New reduced  
price **£3.00** P&P 65p (**£3.94** inc. VAT & P)  
N.M.S.



## 21-WAY SELECTOR SWITCH with reset coil

The ingenious electro mechanical device can be  
switched up to 21 positions and can be reset from  
any position by energising the reset coil  
230/240v. A.C. operation. Unit is mounted on  
sliding chassis. Complete with cover. Price **£5.50**  
P&P 75p (**£6.75** inc. VAT & P) N.M.S.



## VORTEX BLOWER AND VACUUM UNIT

Dynamically balanced totally enclosed 9  
rotor with max. air delivery of 1.5 cubic  
metres per min. Max static pressure  
600mm W.G. Suction or blow from 2  
side-by-side 37mm I.D. circular apertures  
fitted to base of unit. Powerful continuously  
rated 115v a.c. motor mounted on alloy base  
with lining facilities. Dimensions Length  
22cm x width 25cm x height 25cm



These units are ex-equipment but have had minimum use. Fully tested  
prior to despatch. Price **£12** + **£1.50** P&P (**£14.58** inc. VAT & P)  
Suitable transformer for 230/240v a.c. **£6** + **£1** P&P (**£7.56** inc. VAT & P)

## CENTRIFUGAL BLOWER

**24V DC Blower Unit M.F.R. USA made 24V DC**  
8 amp blower that operates well on 12V. 4 amp  
DC producing 30 cu ft/min at normal air pressure  
Maximum housing dia 110mm, depth inc motor  
75mm, nozzle length 19mm, dia 22mm. Ideal for  
cooling mobile equipment, car, caravan etc.  
**£4.50** P&P 75p (**£5.67** inc)



Smith type FFB 1606 022 220/240V AC Aperture  
10x4 1/2cm overall size 16x14cm Price  
**£3.75** P&P 75p (**£4.88**) Other types  
available. S.A.E. for details.  
N.M.S.



## MINIATURE UNISELECTOR

12V 11 way 4 bank (3 non bridging 1 homing) **£2.50** P&P 35p (**£3.08**  
inc. VAT & P) N.M.S.


## MICRO SWITCHES

Sub min lever m switch type MML46 10 for **£2.50**  
Type 3 115M 906T 10 for **£2.50** post paid (**£2.70** inc. VAT  
& P).  
BF lever operated 20a c/o m. Unimax USA 10 for **£4.00**  
plus 50p P&P (min order 10) (**£4.86** inc. VAT & P).  
D.P.C. O lever m switch, mfg by Cherry Co. USA. Precious metal low  
resistance contacts. 10 for **£2.50**, P&P 30p. Total inc. VAT **£3.02** (min  
10). N.M.S.


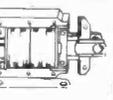
## NEW HEAVY DUTY SOLENOID

Mfg by Magnetic Devices 240V AC  
Operation approx 10lb. pull at 1/2 (intermittent  
rating). Price **£4.00** P&P 60p (**£4.96**  
inc. VAT)



**Pye Eythar 240V AC Solenoid** Approx 1lb pull. 1/2" travel. Intermittent  
rating. Price **£1.00** P&P 20p (**£1.30** inc. VAT & P)  
N.M.S.  
**Insulation Testers 500 Volts** price in brackets **£53.78** (Not £57.78)

## 240V AC SOLENOID OPERATED FLUID VALVE

Rated 1 p.s.i. will handle up to 7 p.s.i. Forged brass  
body. stainless steel core and spring 1/2 in b.s.p. inlet  
outlet. Precision made. British mfg.  
Price **£3.50** Post 50p (**£4.32** inc. VAT & P).  
N.M.S.



## PARVALUX 230/250V a.c. MOTOR

Type SD1B 240v AC reversible 30 rpm 50lbs inch  
Price **£15.00** P&P **£1.50** (**£17.82** inc. VAT) N.M.S.



## INSULATION TESTERS (NEW)

Test to I.E.E. spec. Rugged metal construction  
suitable for bench or field work. constant speed  
circuit. Size L 8 in. W 4 in. H 6 in. weight 6 1/2  
**500 VOLTS** 500 megohms  
**£49.00** Post 80p (**£57.78** inc. VAT & P)  
**1000 VOLTS** 1000 megohms  
**£55.00** Post 80p (**£60.26** inc. VAT & P)  
SAE for leaflet



## VARIABLE VOLTAGE TRANSFORMERS



**INPUT 230 v. A.C. 50/60**  
**OUTPUT VARIABLE 0/260v. A.C.**  
**BRAND NEW. All types.**  
**200W (1 Amp) fitted A/C**  
**volt meter** ..... **£14.50**  
**0.5 KVA (Max. 2 1/2 Amp)** ..... **£17.00**  
**1 KVA (Max. 5 Amp)** ..... **£22.50**  
**2 KVA (Max. 10 Amp)** ..... **£37.00**  
**3 KVA (Max. 15 Amp)** ..... **£45.50**  
**5 KVA (Max. 25 Amp)** ..... **£74.00**  
**10 KVA (Max. 50 Amp)** ..... **£168.00**  
**17 KVA (Max. 75 Amp)** ..... **£260.00**

Carriage extra

## LT TRANSFORMERS

0-10v-15v at 3 amp (ex new equip) **£2.50** P&P 50p (**£3.24** inc. VAT)  
13-0-13v at 1 amp **£2.50** P&P 50p (**£3.24** inc. VAT)  
25-0-25v at 2 1/2 amp **£4.50** P&P 75p (**£5.67** inc. VAT & P)  
0-4v/6v/24v/32v at 12 amp **£15.00** P&P **£1.50** (**£17.82** inc. VAT & P)  
0-6v/12v at 20 amp **£13.50** P&P **£1.50** (**£16.20** inc. VAT & P)  
0-12v at 20 amp. or 0-24v at 10 amp **£12.00** P&P **£1.50** (**£14.58** inc.  
VAT & P)  
0-6v/12v at 10 amp **£8.25** P&P **£1.25** (**£10.26** inc. VAT & P)  
0-6v/12v/17v/18v/20v at 20 amp **£16.50** P&P **£1.50** (**£19.44** inc.  
VAT & P)  
0-10v/17v/18v at 10 amp **£10.00** P&P **£1.40** (**£12.31** inc. VAT & P)  
Other types in stock. phone for enquiries or send sae for leaflet

## ROTARY VACUUM AIR COMPRESSOR & PUMP

Carbon vane oil free vacuum pump and compres-  
sor. Approx. 20 inch vacuum, 10 PSI at 79 CFM  
Powered by 110V a.c. 1.8 amp Parvalux motor  
fitted with additional shaft at rear. Suitable light  
loads. Inc. capacitor **£14.00** P&P **£1.50** (**£16.74**  
inc. VAT & P).  
Suitable transformer for 230/240v a.c. operation  
**£5.00** P&P **£1.00** (**£6.48** inc. VAT & P) N.M.S.



## BLOWER/VACUUM PUMP

3 phase A.C. motor. 220/250v or 380/440v. 1.425 rpm 1/2 hp cont.  
Direct coupled to William Allday Alcosa carbon vane blower/vacuum  
pump. 0.9 cfm 8 hg. Price **£22.00** P&P **£2.00** (**£25.92** inc. vat + p).  
N.M.S.

## STROBE! STROBE! STROBE!

**HY-LIGHT STROBE KIT Mk. IV**  
Latest type Xenon white light tube. Solid state timing and triggering  
circuit. 230/240 volt A.C. operation. Speed adjustable 1-20 f.p.s.  
Designed for large rooms, halls, etc. Light output greater than many  
(so called 4 Joule) strobes. Price **£19.00** post **£1** (**£21.60** inc. VAT  
& P). Specially designed case and reflector for Hy-Light **£8.80** Post  
**£1.00** (**£10.58** inc. VAT & P)

\*\*\*\*\*  
**ULTRA VIOLET BLACK LIGHT**  
**FLUORESCENT TUBES**  
4ft. 40 watt **£8.70** (callers only) 2ft. 20 watt **£6.20**. Post 75p  
(**£7.51** inc. VAT + P) (For use in stan bin fittings.) Mini 12in. 8  
watt **£2.80**. Post 35p (**£3.40** inc. VAT + P). 9in. 6 watt **£2.25**.  
Post 35p (**£2.81** inc. VAT + P). 6in. 4 watt **£2.25**. Post 35p  
(**£2.81** inc. VAT + P).  
Complete ballast unit. Either 6 9 or 12 tube 230v A.C. op.  
**£3.50**. Post 45p (**£4.27** inc. VAT + P). Also available for 12v D.C.  
op. **£3.50** plus P&P 45p (**£4.27** inc. VAT & P).  
400w UV lamp and ballast complete. **£31.50**. Post **£3** (**£37.26**  
inc. VAT + P). 400w UV lamp only **£11.25**. Post **£1** 20 (**£13.45**  
inc. VAT + P).

\*\*\*\*\*

## SQUAD LIGHT

A new conception in light  
control. Four channels each  
capable of handling 750 watts  
of spotlights or dozens of small lamps. Seven programs all speed  
controlled plus flash modulation, effectively giving 14 different displays  
noise free.  
Makes sound-to-light obsolete. Completely electrically and mechanically  
noise free.  
Price only **£60.00** plus 75p P&P (**£65.61** inc. VAT)  
S.A.E. (foolscap) for further details



## WIDE RANGE OF DISCO LIGHTING EQUIPMENT

S.A.E. (foolscap) for details

## XENON FLASH GUN TUBES

Range of Xenon tubes available from  
stock. S.A.E. for full details.



## RELAYS

Wide range of AC and DC relays available  
from stock. Phone or write in your en-  
quiries.

**230/240V A.C. Relays:** Arrow. 2c/o 15amp **£1.50** (**£1.84** inc. VAT & P).  
T.C.C. open type 3c/o 10 amp **£1.10** (**£1.40** inc. VAT & P) Omron or  
Keyswitch 1c/o 7 amp **£1.00** (**£1.30** inc. VAT & P)

**D.C. Relays:** Open type 9/12V 3c/o 7 amp **£1.00** (**£1.30** inc. VAT & P).  
Sealed 12V 2c/o 7 amp octal base. **£1.25** (**£1.56** inc. VAT & P) Sealed  
12V 3c/o 7 amp 11-pin. **£1.35** (**£1.67** inc. VAT & P) 24V. Sealed 3  
c/o 7 amp 11-pin **£1.35** (**£1.67** inc. VAT & P) (amps = contact rating).  
P&P on any Relay 20p.  
Other types available — phone for details. N.M.S.

Diamond H heavy duty A.C. relay 230/240v a.c. two c/o contacts 25  
amps res at 250V a.c. **£2.50** P&P 50p (**£3.24** inc. VAT & P&P) Special  
base 50p.


**VAT AT CURRENT RATE MUST BE ADDED TO ALL ORDERS FOR THE TOTAL VALUE OF GOODS INCLUDING POSTAGE UNLESS OTHERWISE STATED**

ACCOUNT CUSTOMERS MIN. ORDER £10.00

## GEARED MOTORS
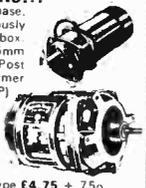
### 100 R.P.M. 115 lbs. ins.!!

115 lb. ins. 110 volt. 50Hz. 2.8 amp. single phase.  
split capacitor motor. Immense power. Continuously  
rated. Totally enclosed. Fan cooled. In-line gearbox.  
Length 250mm. Dia. 135mm. Spindle Dia. 15.5mm  
Length 115mm. ex-equipment tested **£12.00** Post  
**£1.50** (**£14.58** inc. VAT & P). Suitable transformer  
230/240 volt **£8.00** Post 75p (**£9.45** inc. VAT & P)  
R&T



## GEARED MOTORS

28 r.p.m. 20lb. inch 115v a.c. Reversible motor  
71 r.p.m. 10 lb. inch 115v a.c. Reversible motor  
Both types similar to above drawing. Price either type **£4.75** + 75p  
P&P (**£5.94** inc. VAT + P&P)  
Supplied with transformer for 240v a.c. operation **£7.25** + P&P **£1**  
(**£8.91** inc. VAT + P&P) N.M.S.

## FRACMO MOTOR

56rpm 50lbs inch 240vAC reversible. 0.7 amp.  
sharplength 35mm, dia 16mm, weight 6 kilos  
600 grams. Price **£15.00** P&P **£1.50** (**£17.82**).  
N.M.S.



## PARVALUX MOTOR TYPE S.D.2

12v D.C. shunt 1.30th ph motor. Continuously  
rated 4000 rpm. Price **£10.00**, P&P 75p (**£11.61**  
inc. VAT + P) N.M.S.

## CROUZET 230V A.C.

2 P.F.M. synchronous, brand new **£2.90**, P&P 30p (**£3.46** inc. VAT).  
N.M.S.

## CITENCO

FHP motor type C 7333 15 220/240V AC 19  
rpm reversible motor. torque 14.5 kg. Gear ratio  
14:1. Brand new incl. capacitor. our price  
**£14.25** + **£1.25** P&P (**£16.74** inc. VAT & P)  
N.M.S.



## REVERSIBLE MOTOR 230V A.C.

General Electric 230v A.C. 1.600 r.p.m. 0.25 amp. Complete with  
anti-vibration mounting bracket and capacitor. O/A size 110mm x  
90mm. Spindle 5/16 dia 20mm long. Ex-equipment test **£3.00**. Post  
50p (**£3.78** inc. VAT & P)

## RODENE UNISET TYPE 71 TIMER

0-60 sec. 230v a.c. operation. Incorporating a lapse time indicator and  
repeat facilities. A precision motorised timer ideal for process timing,  
photography, welding, mixing, etc. Price **£6 P** & P 60p (**£7.13** inc. VAT  
& P) N.M.S.



## METERS (New) — 90mm DIAMETER

A.C. Amp. Type 6272 0-1A. 0-5A. 0-20A. A.C. Volt.  
0-15V. 0-300V. D.C. Volt. Type 65C5 0-2A. 0-10A.  
0-20A. 0-100A. D.C. Volt. 0-15V. 0-30V. All types  
**£3.50** ea + P&P 50p (**£4.32** inc. VAT), except 0-100A.  
D.C. price **£5.00** + 50p P&P (**£5.94** inc. VAT)



## 'VENNER TYPE' ERD TIME SWITCH

200/250V AC 30 amp. 2 on/2 off every 24 hrs. at any  
manually pre-set time. 36-hour spring reserve and day  
omitting device. Built to highest Electricity Board  
specification. Price **£7.75** P&P 75p (**£9.18**). R & T




## SANGAMO WESTON TIME SWITCH

Type S251 200/250 V a.c. 2 on/2 off every 24 hours. 20 amps contacts with  
override switch diameter 4 x 3 price **£6.00** P&P 50p (**£7.02** inc. VAT & P).  
Also available with Solar dial. R & T
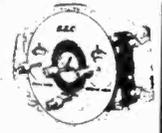
## A.C. MAINS TIMER UNIT

Based on an electric clock with 25 amp. single-  
pole switch, which can be preset for any period up  
to 12 hrs. ahead to switch on for any length of  
time. from 10 mins. to 6 hrs. then switch off. An  
additional 60 min. audible timer is also incorpo-  
rated. Ideal for Tape Recorders, Lights, Electric  
Blankets etc. Attractive satin copper finish. Size  
135 mm x 130 mm x 60 mm. Price **£2.25**. Post  
40p (Total inc. VAT & Post **£2.87**). N.M.S.



## POWER RHEOSTATS

New ceramic construction. vitreous enamel,  
embedded winding. heavy duty brush assembly,  
continuously rated.

**25 WATT** 10, 25, 100, 150, 250, 500 1k. 1.5k ohm **£2.40** Post  
20p (**£2.81** inc. VAT & P) **50 WATT** 100, 250 ohm **£2.90** Post 25p  
(**£3.40** inc. VAT & P) **100 WATT** 1/5 / 10 / 25 / 50 / 100 / 250  
500 / 1k / 1.5k / 2.5k / 5k ohm **£5.90** Post 35p (**£6.75** inc. VAT  
& P)  
**Black Silver Skirted Knob** calibrated in Nos. 1-9. 1 1/2 in. dia brass  
brush. Ideal for above Rhosats. 24p ea.

## 600 WATT DIMMER SWITCH

Easily fitted. Fully guaranteed by makers. Will control up to  
600w of lighting except fluorescent at mains voltage.  
Complete with simple instructions **£3.95** Post 25p (**£4.53**  
inc. VAT & P) 1000 watt model **£5.60** Post 25p (**£6.32** inc.  
VAT & P) 2000 watt model **£9.75** Post 40p (**£10.96** inc.  
VAT & P)



## YET ANOTHER OUTSTANDING OFFER

New IMFD 600V Dubilier wire ended capacitors. 10 for **£1.50** P&P 50p  
(**£2.16** inc. VAT + P&P) N.M.S.

N.M.S. — New Manufacturers Surplus  
R & T — Reconditioned and Tested

ALL MAIL ORDERS, ALSO CALLERS AT

57 BRIDGMAN ROAD, CHISWICK,  
LONDON, W4 5BB. Phone: 01-995 1560  
Closed Saturdays

# SERVICE TRADING CO.

SHOWROOMS NOW OPEN  
AMPLE PARKING

PERSONAL CALLERS ONLY

9 LITTLE NEWPORT STREET,  
LONDON, WC2H 7JJ  
Tel. 01-437 0576

### THE SINCLAIR PDM35 Digital Multimeter

Now a digital multimeter at an analogue price and look at the spec!

**D.C. VOLTS** 1mv-1000v(1% — 1 count) 10mΩ input.

**A.C. VOLTS** 1v-500v, 40Hz-5kHz (1% + 2 counts).

**D.C. CURRENT** 1 mA-200mA (1% count)

**RESISTANCE** 1Ω-20mΩ (1.5% + 1 count) **£29.80** C.W.O.

or £30.95 company or govt. purchase order. Adaptor £3.20. Padded case £3.20. 30kV probe £18.92.

New DM 350 3½ digit multimeter @ £71.28

New DM 450 @ £96. SAE for details.



### THE SINCLAIR MICROVISION

The amazing pocket T.V. that will pick up programs throughout the world, complete with rechargeable batteries. International model £172.50 inc. VAT. UK model £99 inc. VAT.

See (for detailed Brochure ex-stock)

Portable 3½ digit 6 function Multimeter. DC volts 1mV to 1000V AC volts 1mV to 750V AC & DC current 1µA to 1A Resistance 1Ω to 20MΩ Diode test 0.1vA to 1mA 10mΩ input, DC acc. 1.0% AC acc. 1.5% 30Hz-10KHz

### SINCLAIR DM235

£52.80 inc. VAT Cash with order Case £8.50. Adaptor £3.75 CWO



### SINCLAIR ENTERPRISE

79-step programmable calculator (Trigonometric functions, logs, etc.) has seven independent memories which can be used under program control, forward or backward stepping facility for examining the stored programme and conditional branching under program control. We have thrown in case, mains adaptor, alkaline battery and a three-volume software library containing 316 programs and an instruction manual.

## KRAMER & CO

We will match any lower advertised price on a cash with order basis if competitor has goods in stock. 9 October Place, Holders Hill Road, London NW14 1EJ. Telex 888941 Attn. Kramer K7. Tel. 01-203 2473. Mail order only. SAE for data sheets. Export enquiries welcome.

# BUILD THE TREASURE TRACER MK III METAL LOCATOR



AS SEEN ON BBC-1 & BBC-2 TV

- Genuine 5 silicon transistor circuit, does not need a transistor radio to operate.
- Incorporates unique varicap tuning for extra stability.
- Search head fitted with Faraday screen to eliminate capacitive effects.
- Loudspeaker or earphone operation (both supplied).
- Britain's best selling metal locator kit. 4,000 already sold.
- Kit can be built in two hours using only soldering iron, screwdriver, pliers and side-cutters.
- Excellent sensitivity and stability.
- Kit absolutely complete including drilled, tinned, fibreglass p.c. board with components sitting printed on.
- Complete after sales service.
- Weighs only 22oz.; handle knocks down to 17" for transport.

Send stamped, self-addressed envelope for literature.

Complete kit with pre-built search coil **£15.95** Plus £1.20 P&P Plus £1.37 VAT (8%)

Built, tested and guaranteed **£20.95** Plus £1.20 P&P Plus £1.77 VAT (8%)



Phone your order. 0203 611597 24 hrs.

**MINIKITS ELECTRONICS**, 6d Cleveland Road, South Woodford, LONDON E18 2AN (Mail order only)

### SANTA'S GOODIES

7409N 10p. £8-100, 7460N 10p. £8-100 74109N 15p. £12-100, 74155 35p. Min Order 10 of one type — 100+ POA p/p 20p

**PIHER SLIDER POTS** 47K Log Track 70 mm Overall 85mm, Singles 20p, £15-100, Doubles 50p, £40-100; Min Order 10, 100+ POA. p/p 20p.

### MAINS TRANSFORMER

250v Prim 0-10v-18v 2 amp £1.00 + 50p p/p. Octal Cable fitting plug, 20 way, 20p. Chassis mounting plug, 20 way, 20p. Cable mounting socket, 20 way 20p p/p 20p.

74S40 25p, 74S64 30p, MC1488L 75p, MC1489AL 75p + 20p p/p.

**TRIMPOTS** 50Ω T05 20p, 100Ω Cermet 20p, 100Ω Painton PCB 20p, 200Ω ditto 20p, 250Ω ditto 20p, 500Ω ditto 20p, 1K ditto 20p, 2K ditto 20p, 2K Helitrim 20p, 5K PCB 20p, 1M skeleton min. vert. 12p p/p 20p.

**CANNON D-TYPES** 15 way plugs 50p, 15 way sockets 50p, 25 way plug 60p, 25 way socket 60p, 37 way plug 80p, 50 way socket £1.20, 50 way w/wrap sockets £1.30, 25 way ribbon plugs 90p, covers with retainers 15 way 60p, 25 way 80p, 37 way £1, 25 way plastic (3M) 50p, all above limited stocks. P/P 20p.

### TTL 74 SERIES

|             |             |             |
|-------------|-------------|-------------|
| 7400 12p    | 7401 12p    | 7402 15p    |
| 7404 14p    | 7407 30p    | 7409 16p    |
| 7410 13p    | 7412 18p    | 7414 45p    |
| 7416 24p    | 7417 25p    | 7420 15p    |
| 7427 30p    | 7428 32p    | 7430 15p    |
| 7432 26p    | 7438 30p    | 7442 50p    |
| 7451 15p    | 7472 76p    | 7460 15p    |
| 7474 28p    | 7475 30p    | 7485 95p    |
| 7486 30p    | 7490 30p    | 7491 80p    |
| 7495 60p    | 7496 55p    | 7497 £1.50  |
| 74107 30p   | 74109 50p   | 74121 25p   |
| 74123 48p   | 74150 90p   | 74151 60p   |
| 74153 70p   | 74154 £1.10 | 74155 80p   |
| 74157 60p   | 74162 90p   | 74163 90p   |
| 74164 £1.00 | 74165 £1.10 | 74188 £2.50 |
| 74190 £1.00 | 74192 90p   | 74195 90p   |
| 74198 £1.30 | 74279 £1.20 | 74284 £3.60 |
| 74368 £1.35 | 75450 35p   | 76660 50p   |

P/P 20p

**SUPERSAVER 1** cassette recorder motor 9v Speed governed, brand new, fantastic value. 95p p/p 20p.

**SUPERSAVER 2** Hybrid Systems DAC 371-8 (8-bit) DIL packaged + data, ideal MPU users, brand new £2 (fraction of original cost) p/p 20p.

**SUPERSAVER 3** ICL P.S.U. 12v 1.8A (7.5v-15v) in maker's carton £10 p/p £2.

**MEMORIES** 2708 £6-85, 2102 (Signetics) £1, 1702A £2.95, 2513 (upper case) £5. p/p 20p

**SUBMIN. TOGGLES** (C & K, USA) spco extended toggle (1.25 inch) superb quality 75p. Standard submin. toggle dpco 80p. p/p 20p.

**9-WAY MALE/FEMALE** connector (Elco 8129) 0.1 inch pitch, PCB mounting ideal for bussing two PCBs together 35p/pair p/p 20p.

**LEDS** (red) TIL 209 8p, 0.2 10p, Vernitron Ceramic filters FM-4 10.7MHz 45p, BD 236 40p, 2N3055 (Ti) 40p, BC183L 10p, BC213L 10p, BF195 10p, 2521V (Dual 128 bit static shift register 65p), RS 12-0-12 50mA subminiature transformer £1.35, 5LT01 (green phosphor) £4, suitable clock IC £3.25, N825126N (PROM 256x4 bit) £1.30, TMS3128NC (static shift reg) £1.25, LM711CH T0-99 (voltage comparator) 25p, FPE 100 infra red emitter + data 15p, MM5314 £2.95, DIL SWTS 4 way 60p, TBAB10S + DATA 65p.

P/P 20p

All enquiries SAE please, Cat. SAE 8x6 or free with goods. P/P same for quantities except where greater than £1.

Merry Christmas to all customers and ETI

**L. B. ELECTRONICS** 43 WESTACOTT, HAYES, MIDDLESEX UB4 8AH, ENGLAND

|          |                 |                |                    |          |                      |        |    |
|----------|-----------------|----------------|--------------------|----------|----------------------|--------|----|
| 7400 TTL | 74151           | 58             | 74S22              | 38       | ZX500                | 18     |    |
| 7401     | 74154           | 1.00           | 74S37              | 38       | 2K353                | 20     |    |
| 7402     | 74156           | 50             | 74S51              | 28       | 2K354                | 57     |    |
| 7403     | 74157           | 54             | 74S64              | 28       | 2K355                | 57     |    |
| 7404     | 74160           | 1.04           | 74S74              | 38       | 2K3702               | 12     |    |
| 7409     | 74162           | 1.18           | 74S112             | 66       | 2K3704               | 12     |    |
| 7406     | 74163           | 80             | 74S124             | 3.25     | 2K3819               | 29     |    |
| 7409     | 74164           | 87             | <b>MICRO'S</b>     |          | <b>DRODES</b>        |        |    |
| 7410     | 74165           | 93             | 74S188             | 3.95     | 1M914                | 05     |    |
| 7411     | 74176           | 84             | 1702A              | 7.95     | 1M4148               | 05     |    |
| 7412     | 74180           | 86             | 2708               | 1.22     | 1M4151               | 04     |    |
| 7413     | 74190           | 1.04           | 2102-1             | 1.22     | 1M4001               | 06     |    |
| 7414     | 74192           | 98             | 2114               | 10.53    | 1M4002               | 06     |    |
| 7416     | 74193           | 98             | 8080A              | 7.02     | 1M4004               | 10     |    |
| 7417     | 74194           | 86             | 8251               | 7.06     | 1M4005               | 11     |    |
| 7420     | 74196           | 86             | <b>LINEAR</b>      |          | <b>ELECTROLYTICS</b> |        |    |
| 7426     | 74197           | 86             | LM380-14           | 80       | 1M4005               | 11     |    |
| 7427     | 74198           | 1.41           | LM3900             | 4P       | 1M4007               | 12     |    |
| 7430     | <b>74LS TTL</b> |                | LM741-8            | 21       | 1M4520               | 16     |    |
| 7432     | 74LS00          | 18             | NE555              | 29       | 1M4504               | 21     |    |
| 7433     | 74LS01          | 18             | NE565              | 7.14     | <b>UF/V</b>          |        |    |
| 7437     | 74LS02          | 18             | NE565              | 1.14     | 47/100               | 08     |    |
| 7438     | 74LS04          | 19             | NE566              | 1.43     | 1/30                 | 08     |    |
| 7440     | 74LS05          | 21             | NE567              | 1.62     | 2/253                | 08     |    |
| 7441     | 74LS09          | 21             | <b>REGULATORS</b>  |          | 3/3/83               | 08     |    |
| 7442     | 74LS09          | 21             | 7805               | 80       | 47/35                | 08     |    |
| 7443     | 74LS10          | 21             | 7812               | 80       | 47/63                | 08     |    |
| 7445     | 74LS11          | 21             | 7805               | 1.39     | 10/16                | 08     |    |
| 7446     | 74LS14          | 1.10           | 7812               | 1.39     | 10/35                | 08     |    |
| 7447     | 74LS20          | 18             | LM309              | 86       | 10/53                | 09     |    |
| 7448     | 74LS21          | 21             | LM723              | 38       | 22/16                | 08     |    |
| 7450     | 74LS32          | 24             | LM723              | 38       | 22/35                | 10     |    |
| 7451     | 74LS37          | 26             | <b>TRANSISTORS</b> |          | 22/63                | 12     |    |
| 7453     | 74LS38          | 29             | AC128              | 23       | 33/16                | 08     |    |
| 7454     | 74LS40          | 25             | AC176              | 10       | 33/35                | 11     |    |
| 7460     | 74LS42          | 54             | BC107              | 10       | 33/63                | 13     |    |
| 7410     | 74LS51          | 29             | BC108              | 10       | 47/16                | 09     |    |
| 7472     | 74LS74          | 32             | BC109              | 10       | 47/35                | 12     |    |
| 7473     | 74LS86          | 33             | BC177              | 18       | 47/35                | 15     |    |
| 7474     | 74LS90          | 86             | BC178              | 18       | 100/16               | 11     |    |
| 7475     | 74LS93          | 86             | BC179              | 18       | 100/35               | 13     |    |
| 7476     | 74LS107         | 34             | BC184              | 21       | 220/16               | 12     |    |
| 7483     | 74LS112         | 100            | BC187              | 32       | 220/25               | 17     |    |
| 7485     | 84              | 74LS123        | 85                 | BC477    | 24                   | 330/16 | 18 |
| 7486     | 25              | 74LS124        | 2.20               | BC478    | 24                   | 330/35 | 31 |
| 7489     | 1.95            | 74LS151        | 95                 | BC479    | 24                   | 470/16 | 18 |
| 7490     | 38              | 74LS153        | 64                 | BD131    | 54                   | 470/35 | 14 |
| 7491     | 62              | 74LS157        | 64                 | BD132    | 54                   | 470/16 | 18 |
| 7492     | 42              | 74LS164        | 1.14               | BFY50    | 23                   | 470/35 | 18 |
| 7493     | 29              | 74LS175        | 1.05               | BFY51    | 23                   | 100/16 | 30 |
| 7495     | 51              | 74LS193        | 1.33               | BFY52    | 23                   |        |    |
| 7496     | 67              | 74LS194        | 2.06               | BS195A   | 17                   |        |    |
| 74104    | 48              | <b>74S TTL</b> |                    | BC172    | 36                   |        |    |
| 74105    | 48              | 74S00          | 38                 | BC173    | 20                   |        |    |
| 74107    | 27              | 74S04          | 28                 | OC200    | 45                   |        |    |
| 74109    | 45              | 74S05          | 38                 | TIP 2955 | 85                   |        |    |
| 74121    | 25              | 74S08          | 38                 | TIP 3055 | 68                   |        |    |
| 74122    | 47              | 74S10          | 38                 | TIS 43   | 33                   |        |    |
| 74123    | 38              | 74S12          | 38                 | ZX300    | 17                   |        |    |
| 74141    | 71              | 74S11          | 38                 |          |                      |        |    |

All prices INCLUDE V.A.T. add 25p P&P. S.A.E. for full list

**IBEK SYSTEMS** 32 Dunsville Drive, Coventry CV2 2H5

### TRANSISTORS

|           |      |        |      |        |      |        |      |        |      |          |      |         |      |
|-----------|------|--------|------|--------|------|--------|------|--------|------|----------|------|---------|------|
| AC107     | 0.23 | BC117  | 0.15 | BC206  | 0.10 | BC559  | 0.11 | BF184  | 0.28 | BU205    | 1.30 | ZN1613  | 0.18 |
| AC125     | 0.17 | BC118  | 0.11 | BC208  | 0.11 | BC742  | 0.55 | BF185  | 0.20 | BU206    | 1.50 | ZN1671  | 1.10 |
| AC126     | 0.17 | BC119  | 0.25 | BC207  | 0.10 | BC750  | 0.20 | BF194  | 0.06 | BU208-02 | 1.75 | ZN1678  | 2.20 |
| AC127     | 0.16 | BC120  | 0.15 | BC209  | 0.09 | BC771  | 0.13 | BF194A | 0.07 | BU406    | 3.90 | ZN1711  | 2.20 |
| AC127K    | 0.23 | BC121  | 0.16 | BC210  | 0.16 | BC772  | 0.13 | BF195  | 0.06 | BU198A   | 6.75 | ZN1712  | 2.20 |
| AC128     | 0.14 | BC126  | 0.15 | BC213L | 0.10 | BD115  | 0.30 | BF195G | 0.07 | BU198B   | 2.00 | ZN1905  | 0.25 |
| AC128K    | 0.25 | BC136  | 0.15 | BC214L | 0.10 | BD116  | 0.30 | BF196  | 0.07 | BU198C   | 7.00 | ZN1906  | 0.25 |
| AC128/176 | 0.42 | BC137  | 0.15 | BC237  | 0.15 | BD123  | 0.60 | BF196  | 0.06 | BUY70A   | 5.00 | ZN2060  | 1.00 |
| AC142     | 0.18 | BC138  | 0.30 | BC237A | 0.16 | BD128  | 1.02 | BF197  | 0.06 | BUY71    | 4.50 | ZN2188  | 2.20 |
| AC153     | 0.55 | BC140  | 0.27 | BC237C | 0.21 | BD131  | 0.35 | BF198  | 0.06 | MP56517  | 0.48 | ZN2189  | 0.22 |
| AC158     | 0.50 | BC141  | 0.29 | BC238  | 0.15 | BD132  | 0.40 | BF224  | 0.19 | MP56523  | 0.27 | ZN2222  | 0.18 |
| AC176     | 0.16 | BC142  | 0.20 | BC238B | 0.10 | BD135  | 0.30 | BF255  | 0.18 | MP56528  | 0.18 | ZN2224  | 0.20 |
| AC187     | 0.50 | BC147  | 0.06 | BC238C | 0.18 | BD136  | 0.30 | BF255A | 0.18 | MP56533  | 0.72 | ZN2270  | 0.39 |
| AC187K    | 0.55 | BC147B | 0.07 | BC251A | 0.15 | BD137  | 0.30 | BF255B | 0.18 | NK1214   | 0.25 | ZN2368  | 0.10 |
| AC188K    | 0.55 | BC148  | 0.06 | BC251B | 0.17 | BD138  | 0.30 | BF257  | 0.16 | NK1224   | 0.25 | ZN2484  | 0.18 |
| AC192     | 1.02 | BC148A | 0.07 | BC252A | 0.15 | BD139  | 0.30 | BF258  | 0.28 | OC22     | 1.40 | ZN2484A | 0.18 |
| AC192K    | 1.02 | BC148B | 0.07 | BC252B | 0.17 | BD140  | 0.30 | BF259  | 0.28 | OC23     | 1.40 | ZN2484B | 0.18 |
| AD142     | 0.87 | BC149  | 0.06 | BC252C | 0.20 | BD144  | 0.40 | BF324  | 0.20 | OC29     | 0.85 | ZN3053  | 0.15 |
| AD143     | 0.87 | BC157  | 0.06 | BC258  | 0.20 | BD148  | 0.50 | BF335  | 0.25 | OC36     | 1.00 | ZN3117  | 0.15 |
| AD149     | 0.65 | BC157A | 0.07 | BC261A | 0.10 | BD178  | 0.72 | BF338  | 0.45 | OC44     | 0.12 | ZN3440  | 0.15 |
| AD181     | 0.35 | BC158  | 0.07 | BC262  | 0.20 | BD181  | 1.32 | BF457  | 0.60 | OC45     | 0.12 | ZN3638  | 0.10 |
| AD181/162 | 0.70 | BC158A | 0.06 | BC267A | 0.21 | BD183  | 1.50 | BF457A | 0.60 | OC71     | 0.09 | ZN3638A | 0.16 |
| AD182     | 0.35 | BC159  | 0.06 | BC267B | 0.22 | BD232  | 0.60 | BF594  | 0.10 | OC74     | 0.18 | ZN3643  | 0.24 |
| AD282     | 0.36 | BC159A | 0.06 | BC267C | 0.22 | BD233  | 0.60 | BF594A | 0.10 | OC75     | 0.18 | ZN3692  | 0.24 |
| AD283     | 0.36 | BC159B | 0.07 | BC304  | 0.25 | BD234  | 0.60 | BF434  | 0.54 | OC82     | 0.48 | ZN3705  | 0.06 |
| AD286     | 0.36 | BC159C | 0.07 | BC307  | 0.15 | BD235  | 0.40 | BF428  | 0.20 | OC139    | 0.50 | ZN3706  | 0.06 |
| AD211     | 4.05 | BC161  | 0.25 | BC307A | 0.15 | BD236  | 0.40 | BF434  | 0.70 | OC203    | 2.50 | ZN3707  | 0.06 |
| AF106     | 0.45 | BC167  | 0.06 | BC307B | 0.15 | BD237  | 0.40 | BF434A | 0.20 | OC207    | 2.70 | ZN3711  | 0.06 |
| AF108     | 0.36 | BC168  | 0.06 | BC307C | 0.15 | BD238  | 0.40 | BF435  | 0.20 | OC1072   | 2.50 | ZN3718  | 0.20 |
| AF124     | 0.25 | BC169  | 0.06 | BC308A | 0.15 | BD434  | 0.40 | BF435A | 0.20 | OC128    | 2.50 | ZN3809  | 3.00 |
| AF125     | 0.25 | BC170  | 0.07 | BC317B | 0.15 | BD507  | 0.50 | BF418  | 0.50 | OC208B   | 2.10 | ZN3904  | 0.06 |
| AF126     | 0.25 | BC170C | 0.07 | BC322  | 0.10 | BD508  | 0.50 | BF419  | 0.50 | TP30     | 0.35 | ZN3905  | 0.06 |
| AF127     | 0.25 | BC171  | 0.06 | BC327  | 0.16 | BD518  | 0.50 | BF433  | 0.50 | TP31     | 0.35 | ZN3906  | 0.06 |
| AF139     | 0.32 | BC171A | 0.07 | BC328  | 0.16 | BD537  | 1.02 | BF434  | 0.50 | TP31A    | 0.45 | ZN4037  | 0.25 |
| AF171B    | 0.30 | BC171B | 0.07 | BC337  | 0.16 | BD567  | 1.40 | BF435  | 0.50 | TP32     | 0.45 | ZN4038  | 0.10 |
| AF179     | 0.30 | BC172  | 0.06 | BC337A | 0.16 | BD567A | 1.40 | BF435A | 0.50 | TP33     | 0.45 | ZN4039  | 0.10 |
| AF200     | 0.36 | BC172A | 0.07 | BC348A | 0.15 | BD610  | 0.50 | BF452  | 1.12 | TP42     | 0.60 | ZN4344  | 2.00 |
| AF201     | 0.39 | BC172B | 0.07 | BC350A | 0.17 | BD620  | 0.50 | BF481  | 4.00 | TP2955   | 0.65 | ZN4448  | 1.50 |
| AS773     | 0.36 | BC172C | 0.07 | BC441  | 0.20 | BF115  | 0.35 | BF439  | 0.35 | TS90     | 0.18 | ZN4914  | 3.50 |
| AS215     | 0.60 | BC173  | 0.06 | BC461  | 0.24 | BF121  | 0.20 | BS320  | 0.10 | ZN3448   | 0.30 | ZN5172  | 0.25 |
| AS216     | 0.60 | BC173A | 0.06 | BC462  | 0.24 | BF122  | 0.20 | BS321  | 0.33 | ZN404    | 0.45 | ZN5245  | 0.30 |
| AS217     | 0.60 | BC173B | 0.07 | BC463  | 0.24 | BF123  | 0.20 | BS322  | 0.33 | ZN404A   | 0.45 | ZN5246  | 0.30 |
| AS103     | 0.60 | BC174  | 0.07 | BC464  | 0.24 | BF124  | 0.20 | BS323  | 0.33 | ZN404B   | 0.45 | ZN5247  | 0.30 |
| AS171     | 0.60 | BC177A | 0.12 | BC471A | 0.11 | BF127  | 0.20 | BS324  | 0.33 | ZN404C   | 0.45 | ZN5248  | 0.30 |
| AU107     | 1.00 | BC177B | 0.12 | BC471B | 0.11 | BF127A | 0.21 | BS325  | 0.30 | ZN527    | 0.48 | ZN5476  | 0.60 |
| AU110     | 0.90 | BC178  | 0.12 | BC471C | 0.11 | BF127B | 0.21 | BS326  | 0.30 | ZN585    | 0.50 | ZN5670  | 0.65 |
| AU210     | 0.90 | BC179  | 0.12 | BC484A | 0.11 | BF154  | 0.15 | BS329  | 0.54 | ZN705    | 0.10 | ZN5926  | 0.55 |
| BC187     | 0.06 | BC179A | 0.09 | BC484B | 0.11 | BF154A | 0.15 | BS330  | 0.15 | ZN706    | 0.10 | ZN6123  | 0.65 |
| BC107A    | 0.07 | BC179B | 0.07 | BC484C | 0.11 | BF154B | 0.15 | BS331  | 0.15 | ZN706A   | 0.10 | ZN6124  | 0.65 |
| BC107B    | 0.07 | BC183A | 0.09 | BC494A | 0.11 | BF167  | 0.25 | BS354  | 0.39 | ZN708    | 0.12 | ZN6303  | 0.90 |
| BC108     | 0.06 | BC183B | 0.09 | BC494B | 0.11 | BF173  | 0.20 | BS356  | 0.36 | ZN1039   | 0.15 | ZN6304  | 0.90 |
| BC108A    | 0.07 | BC183C | 0.10 | BC550  | 0.11 | BF174  | 0.20 | BS360  | 0.36 | ZN1050   | 0.15 | ZN6305  | 0.90 |
| BC108B    | 0.07 | BC184  | 0.08 | BC557  | 0.11 | BF177  | 0.25 | BS364  | 0.30 | ZN1111   | 0.15 | ZN6323  | 1.00 |
| BC109     | 0.06 | BC184A | 0.09 | BC557A | 0.11 | BF178  | 0.25 | BS368  | 0.30 | ZN1102   | 0.15 | ZN6324  | 1.00 |
| BC109B    | 0.07 | BC184B | 0.11 | BC557B | 0.11 | BF179  | 0.25 | BS368A | 0.30 | ZN1103   | 0.15 | ZN6325  | 1.00 |
| BC109C    | 0.07 | BC184C | 0.11 | BC557C | 0.11 | BF180  | 0.25 | BS368B | 0.30 | ZN1104   | 0.15 | ZN6326  | 1.00 |
| BC109D    | 0.07 | BC184D | 0.11 | BC557D | 0.11 | BF181  | 0.25 | BS368C | 0.30 | ZN1105   | 0.15 | ZN6327  | 1.00 |
| BC113     | 0.12 | BC187  | 0.19 | BC558  | 0.11 | BF181  | 0.20 | BS368D | 0.30 | ZN1106   | 0.15 | ZN6328  | 1.00 |
| BC114     | 0.15 | BC204  | 0.08 | BC558A | 0.11 | BF182  | 0.20 | BS368E | 0.30 | ZN1107   | 0.15 | ZN6329  | 1.00 |
| BC116     | 0.13 | BC204A | 0.09 | BC558B | 0.11 | BF183  | 0.20 | BS368F | 0.30 | ZN1108   | 0.15 | ZN6330  | 1.00 |

### TTL

|      |     |      |     |       |      |       |      |       |      |       |      |
|------|-----|------|-----|-------|------|-------|------|-------|------|-------|------|
| 7400 | .12 | 7426 | .25 | 7470  | .28  | 74107 | .28  | 74148 | 1.20 | 74176 | .90  |
| 7401 | .12 | 7427 | .25 | 7472  | .22  | 74109 | .45  | 74150 | 1.00 | 74177 | .80  |
| 7402 | .12 | 7428 | .34 | 7473  | .28  | 74110 | .46  | 74151 | .80  | 74178 | 1.20 |
| 7403 | .12 | 7429 | .33 | 7474  | .20  | 74111 | .70  | 74152 | .80  | 74179 | 1.10 |
| 7404 | .13 | 7432 | .34 | 7475  | .28  | 74116 | 1.60 | 74154 | 1.06 | 74180 | .70  |
| 7405 | .13 | 7433 | .32 | 7476  | .13  | 74118 | .82  | 74155 | .63  | 74181 | 1.95 |
| 7406 | .20 | 7437 | .24 | 7483  | .75  | 74119 | 1.30 | 74156 | .63  | 74182 | .75  |
| 7407 | .20 | 7438 | .24 | 7484  | .90  | 74120 | .82  | 74157 | .63  | 74184 | 1.20 |
| 7408 | .14 | 7440 | .13 | 7485  | .90  | 74121 | .28  | 74158 | 1.70 | 74185 | 1.20 |
| 7409 | .14 | 7442 | .62 | 7486  | .28  | 74122 | .40  | 74160 | .80  | 74186 | 0.70 |
| 7410 | .13 | 7443 | .65 | 7487  | 2.00 | 74123 | .65  | 74161 | .20  | 74188 | 5.40 |
| 7411 | .18 | 7444 | .90 | 7490  | .35  | 74125 | .65  | 74163 | .80  | 74190 | 1.10 |
| 7412 | .21 | 7445 | .70 | 7491  | .65  | 74126 | .48  | 74164 | .90  | 74191 | 1.00 |
| 7413 | .25 | 7446 | .70 | 7492  | .48  | 74128 | .62  | 74165 | .90  | 74192 | 1.00 |
| 7414 | .64 | 7447 | .66 | 7493  | .38  | 74132 | .70  | 74166 | 1.00 | 74193 | 1.10 |
| 7415 | .27 | 7448 | .80 | 7494  | .80  | 74141 | .65  | 74167 | 2.70 | 74194 | .92  |
| 7416 | .27 | 7450 | .13 | 7495  | .65  | 74142 | 2.02 | 74170 | 1.70 | 74195 | .85  |
| 7420 | .13 | 7442 | .65 | 7496  | .62  | 74143 | 2.02 | 74172 | 4.00 | 74196 | .92  |
| 7421 | .28 | 7452 | .13 | 7497  | 2.40 | 74144 | 2.02 | 74173 | 1.20 | 74197 | .92  |
| 7423 | .25 | 7454 | .13 | 74100 | .85  | 74145 | .65  | 74174 | .90  | 74198 | 1.60 |
| 7425 | .22 | 7460 | .13 | 74105 | .40  | 74147 | 1.38 | 74175 | .70  | 74199 | 1.50 |

### CMOS

|      |     |      |     |       |      |      |      |      |      |      |      |
|------|-----|------|-----|-------|------|------|------|------|------|------|------|
| 4000 | .15 | 4014 | .85 | 4025  | .20  | 4043 | .85  | 4069 | .20  | 4508 | 2.30 |
| 4001 | .15 | 4015 | .80 | 4026  | 1.35 | 4044 | .85  | 4070 | .20  | 4510 | 1.10 |
| 4002 | .25 | 4016 | .45 | 4027  | .65  | 4049 | .28  | 4071 | .20  | 4511 | .70  |
| 3006 | .95 | 4017 | .65 | 4028  | .70  | 4050 | .45  | 4073 | .20  | 4512 | .95  |
| 4007 | .20 | 4018 | .90 | 4029  | .90  | 4051 | .68  | 4075 | .20  | 4516 | .70  |
| 4008 | .94 | 4019 | .45 | 4030  | .50  | 4052 | .68  | 4076 | 1.10 | 4518 | .65  |
| 4009 | .48 | 4020 | .80 | 4033  | 1.40 | 4053 | .88  | 4078 | .20  | 4520 | 1.10 |
| 4010 | .50 | 4021 | .85 | 4034  | 1.00 | 4054 | 1.00 | 4081 | .20  |      |      |
| 4011 | .15 | 4022 | .85 | 4034A | .90  | 4055 | 1.00 | 4082 | .20  |      |      |
| 4012 | .15 | 4023 | .20 | 4040  | .90  | 4066 | .35  | 4502 | .90  |      |      |
| 4013 | .35 | 4024 | .68 | 4042  | .75  | 4068 | .20  | 4507 | .62  |      |      |

### RESISTORS

|   |  |   |  |
|---|--|---|--|
| 1/4W Values available in E12 series from 10R to 1M. Price 0.83 each.  |  | 17W Values available in E6 series from 1R0 to 22K.  |  |
| 1/4W Values available in E12 series from 1R0 to 10M. Price 0.03 each. |  | Prices 1R0 to 4K7 0.39 each.<br>6R8 to 22K 0.41 each.   |  |
| 1W Values available in E12 series from 2R2 to 10M. Price 0.06 each.   |  | 1/4W Single turn cermet potentiometer. Values available: 100R, 200R, 500R, 1K0, 2K0, 5K0, 10K, 20K, 50K, 100K, 200K, 500K, 1M. Price 0.87 each. |  |
| 2W Values available in E12 series from 10R to 10M. Prices 0.11 each.  |  | 1/4W Multiturn cermet potentiometer. Values available: 20R, 50R, 100R, 200R, 500R, 1K0  |  |

# 15 — 240 Watts!

## HY5 Preamplifier

The HY5 is a mono hybrid amplifier ideally suited for all applications. All common input functions (mag Cartridge, tuner, etc.), are catered for internally, the desired function is achieved either by a multi-way switch or direct connection to the appropriate pins. The internal volume and tone circuits merely require connecting to external potentiometers (not included). The HY5 is compatible with all I.L.P. power amplifiers and power supplies. To ease construction and mounting a P.C. connector is supplied with each pre-amplifier.

**FEATURES:** Complete pre-amplifier in single pack — Multi-function equalization — Low noise — Low distortion — High overload — two simply combined for stereo.

**APPLICATIONS:** Hi-Fi — Mixers — Disco — Guitar and Organ — Public address

**SPECIFICATIONS:**

**INPUTS:** Magnetic Pick-up 3mV Ceramic Pick-up 30mV Tuner 100mV Microphone 10mV

Auxiliary 3-100mV input impedance 47k $\Omega$  at 1kHz

**OUTPUTS:** Tape 100mV Main output 500mV R.M.S.


**ACTIVE TONE CONTROLS:** Treble = 12dB at 10kHz Bass = at 100Hz

**DISTORTION:** 0.1% at 1kHz Signal/Noise Ratio 68dB

**OVERLOAD:** 38dB on Magnetic Pick-up. **SUPPLY VOLTAGE:** 16.50V

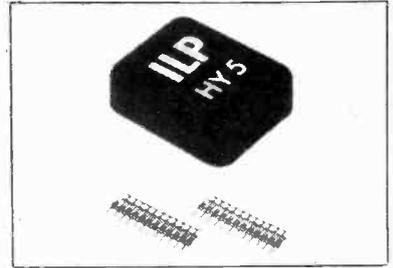**Price £6.27 + 78p VAT. P&P free.**

HY5 mounting board B1 48p + 6p VAT P&P free



## HY30 15 Watts into 8 $\Omega$

The HY30 is an exciting New kit from I.L.P. it features a virtually indestructible I.C. with short circuit and thermal protection. The kit consists of I.C., heatsink, P.C. board, 4 resistors, 6 capacitors, mounting kit, together with easy to follow construction and operating instructions. This amplifier is ideally suited to the beginner in audio who wishes to use the most up-to-date technology available.

**FEATURES:** Complete kit — Low Distortion — Short, Open and Thermal Protection — Easy to Build

**APPLICATIONS:** Updating audio equipment — Guitar practice amplifier — Test amplifier — Audio oscillator


**SPECIFICATIONS:**

**OUTPUT POWER:** 15W R.M.S. into 8 $\Omega$  **DISTORTION:** 0.1% at 15W

**INPUT SENSITIVITY:** 500mV **FREQUENCY RESPONSE:** 10Hz-16kHz — 3dB

**SUPPLY VOLTAGE:** 18V

**Price £6.27 + 78p VAT. P&P free.**

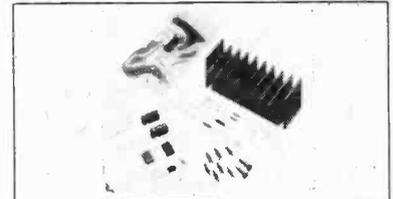

## HY50 25 Watts into 8 $\Omega$

The HY50 leads I.L.P.'s total integration approach to power amplifier design. The amplifier features an integral heatsink together with the simplicity of no external components. During the past three years the amplifier has been refined to the extent that it must be one of the most reliable and robust High Fidelity modules in the World.

**FEATURES:** Low Distortion — Integral Heatsink — Only five connections — 7 Amp output transistors — No external components

**APPLICATIONS:** Medium Power Hi-Fi systems — Low power disco — Guitar amplifier

**SPECIFICATIONS:** **INPUT SENSITIVITY:** 500mV

**OUTPUT POWER:** 25W RMS in 8 $\Omega$  **LOAD IMPEDANCE:** 4-16 $\Omega$  **DISTORTION:** 0.04% at 25W at

1kHz **SIGNAL/NOISE RATIO:** 75dB **FREQUENCY RESPONSE:** 10Hz-45kHz — 3dB

**SUPPLY VOLTAGE:** 25V **SIZE:** 105.50 x 25mm

**Price £8.18 + £1.02 VAT. P&P free.**



## HY120 60 Watts into 8 $\Omega$

The HY120 is the baby of I.L.P.'s new high power range, designed to meet the most exacting requirements including load line and thermal protection, this amplifier sets a new standard in modular design.

**FEATURES:** Very low distortion — Integral Heatsink — Load line protection — Thermal protection — Five connections — No external components

**APPLICATIONS:** Hi-Fi — High quality disco — Public address — Monitor amplifier — Guitar and organ

**SPECIFICATIONS:**

**INPUT SENSITIVITY:** 500mV

**OUTPUT POWER:** 60W RMS into 8 $\Omega$  **LOAD IMPEDANCE:** 4-16 $\Omega$  **DISTORTION:** 0.04% at 60W at


1kHz

**SIGNAL/NOISE RATIO:** 90dB **FREQUENCY RESPONSE:** 10Hz-45kHz — 3dB **SUPPLY VOLTAGE:**

35V

**Size:** 114 x 50 x 85mm

**Price £19.01 + £1.52 VAT. P&P free.**

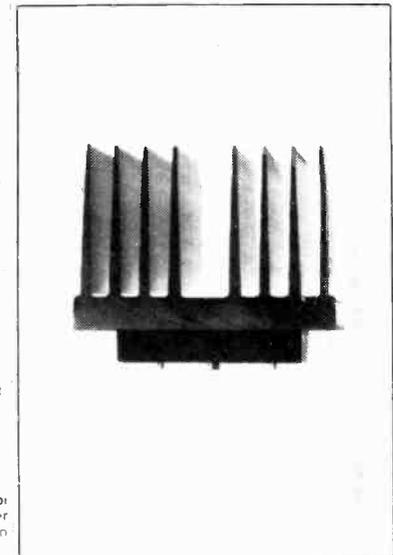

## HY200 120 Watts into 8 $\Omega$

The HY200, now improved to give an output of 120 Watts, has been designed to stand the most rugged conditions, such as disco or group white still retaining true Hi-Fi performance.

**FEATURES:** Thermal shutdown — Very low distortion — Load line protection — Integral Heatsink — No external components

**APPLICATIONS:** Hi-Fi — Disco — Monitor — Power Slave — Industrial — Public address

**SPECIFICATIONS:**

**INPUT SENSITIVITY:** 500mV

**OUTPUT POWER:** 120W RMS into 8 $\Omega$  **LOAD IMPEDANCE:** 4-16 $\Omega$  **DISTORTION:** 0.05% at 100W at

1kHz

**SIGNAL/NOISE RATIO:** 96dB **FREQUENCY RESPONSE:** 10Hz-45kHz — 3dB **SUPPLY VOLTAGE:**

45V

**SIZE:** 114 x 100 x 85mm

**Price £27.99 + £2.24 VAT. P&P free.**

## HY400 240 Watts into 4 $\Omega$

The HY400 is I.L.P.'s "Big Daddy" of the range producing 240W into 4 $\Omega$ ! It has been designed for high power disco or public address applications. If the amplifier is to be used at continuous high power levels a cooling fan is recommended. The amplifier includes all the qualities of the rest of the family to lead the market as a true high power hi-fidelity power module.

**FEATURES:** Thermal shutdown — Very low distortion — Load line protection — No external components

**APPLICATIONS:** Public address — Disco — Power slave — Industrial

**SPECIFICATIONS:**

**OUTPUT POWER:** 240W RMS into 4 $\Omega$  **LOAD IMPEDANCE:** 4-16 $\Omega$  **DISTORTION:** 0.1% at 240W at


1kHz

**SIGNAL/NOISE RATIO:** 94dB **FREQUENCY RESPONSE:** 10Hz-45kHz — 3dB **SUPPLY VOLTAGE:**

45V

**INPUT SENSITIVITY:** 500mV **SIZE:** 114 x 100 x 85mm

**Price £38.61 + £3.09 VAT. P&P free.**

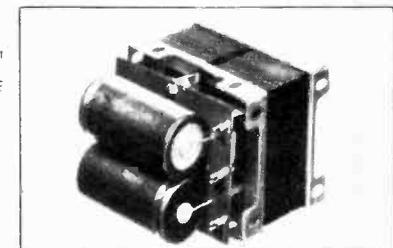

## POWER SUPPLIES

PSU36 suitable for two HY30's **£6.44 + 81p VAT**

PSU50 suitable for two HY50's **£8.18 + £1.02 VAT**

PSU70 suitable for two HY120's **£14.58 + £1.17 VAT**

PSU90 suitable for one HY200 **£15.19 + £1.21 VAT**

PSU180 suitable for two HY200's or one HY400 **£25.42 + £2.03 VAT**


TWO YEARS' GUARANTEE ON ALL OF OUR PRODUCTS

**I.L.P. Electronics Ltd.**  
**Crossland House**  
**Nackington, Canterbury**  
**Kent CT4 7AD**  
**Tel. (0227) 64723**

Please Supply \_\_\_\_\_  
Total Purchase Price \_\_\_\_\_  
I Enclose Cheque  Postal Orders  Money Order   
Please debit my Access account  Barclaycard account   
Account number \_\_\_\_\_  
Name & Address \_\_\_\_\_  
Signature \_\_\_\_\_

# All you want for Christmas

*Fast and Easy*

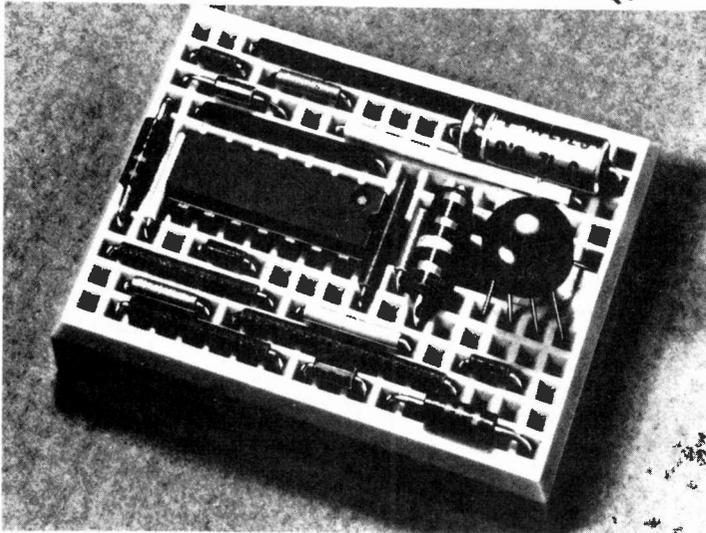

## Lektrokit Breadboards

FROM £3.25, inc p & p and VAT

Hole for hole, top value! Lektrokit breadboards are modular, so they can be linked together to form any size. With a pitch of 0.1", even the smallest breadboard—217L—can accept 8, 14, 16 or 18 pin DIL sockets. You just take a component, choose a hole, and push it in.

| Model No. | Contacts | Price, each |                          |
|-----------|----------|-------------|--------------------------|
| 217L      | 170      | £3.25       | <input type="checkbox"/> |
| 234L      | 340      | £5.75       | <input type="checkbox"/> |
| 248L      | 480      | £6.65       | <input type="checkbox"/> |
| 264R      | 512      | £6.65       | <input type="checkbox"/> |
| 264L      | 640      | £8.32       | <input type="checkbox"/> |

(All prices include packing, postage and VAT).

## Lektrokit Super Strip SS2


ONLY £11.05 inc p & p and VAT

Super Strip accepts all DIP's—as many as nine 14-pin at a time—and/or TO-5's and discrete components. With interconnections of any solid wire up to 20 AWG.

Super Strip has 840 contact points, combining a power/signal distribution system with a matrix of 640 contacts in groups of 5. Distribution system has eight bus-bars, each with 25 contact points.

Lektrokit's policy, as you know, is the right product, whatever the project, at the right price. And it's backed by a nationwide network of retailers.

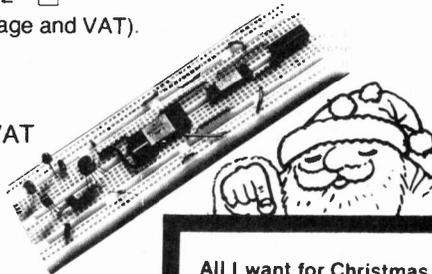But it could be that, whoever you get to complete your Christmas, doesn't know where the Lektrokit retailers are. So we've included an order coupon to help them—and you out!



## Leave this page open where it will do the most good!


You know, almost as well as we know, where to go to get the components a home projects constructor needs to pursue his hobby.

Either your nearest Lektrokit dealer. Or direct from Lektrokit by mail order.

Because Lektrokit offer the most comprehensive range of breadboarding and testing devices on earth.

Trouble is, the nice people who might give you Lektrokit for Christmas probably haven't the faintest idea what we—or even you—are on about.

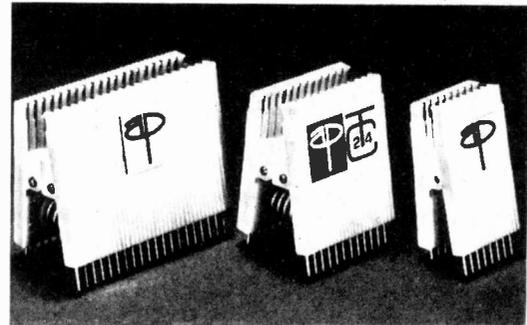So just tick the items you'd particularly like for Christmas. And then leave this page open in a strategic place!



## Lektrokit IC Test Clips

ONLY £3.08 inc p & p and VAT

Ten models to fit all DIP sizes.

Test clip grips IC's without slipping or shorting between pins—makes testing IC's on boards easier, aids removing and inserting DIP's without damage. Each IC pin can be brought up to a convenient contact post for hooking test leads or probe connections.

| Model | Price  |                          |
|-------|--------|--------------------------|
| TC-8  | £4.38  | <input type="checkbox"/> |
| TC-14 | £3.08  | <input type="checkbox"/> |
| TC-16 | £3.25  | <input type="checkbox"/> |
| TC-24 | £9.28  | <input type="checkbox"/> |
| TC-40 | £13.95 | <input type="checkbox"/> |

LEKTROKIT COMPLETES THE CIRCUIT—FOR CHRISTMAS!

All I want for Christmas is what I've marked above.

To Lektrokit Limited, London Road, Reading, Berks, RG6 1AZ.  
Telephone Reading (0734) 669116/7.

Please supply the above (tick items required)—IMMEDIATELY.

**CUT OUT THE COMPLETE ADVERTISEMENT AND SEND TO LEKTROKIT**

(All prices include packing, postage and VAT. All deliveries include name of nearest Lektrokit dealer—plus a FREE catalogue!)

I enclose P.O./cheque for £ .....

Name .....

Address .....

ETI 3

# LEKTROKIT

## COMPLETES THE CIRCUIT

# MINI-ADS & CLASSIFIED


## BARGAIN PACKS

**TTL**  
7400, 01, 02, 03, 04, 08, 10, 20, 30, 51 ANY MIX 10/£1.00, 100/£9.00.  
7433, 48, 104, 105, 109, 122, ANY MIX 10/£1.90, 100/£18.00  
7445, 46, 92, 95, 151, ANY MIX 4/£1.00  
7443, 83, 96, 156, 160, 162, 163,  
74165, 180, 193, 194, ANY MIX 3/£1.30, 10/£5.20.  
BC184, 2N711, 12/£1.00, OCP70 5/£1.00  
SIMILAR TO 2N2192 20/£1.00. **MAN 10 1.27"** 4/£3.00  
BAX13, IN4151 100/£1.50, TBA 120A 2/£1.00  
IN5400 10/£0.80, 74S10 20/£1.00  
PANAPLEX 9 DIGIT 7 SEG DISPLAY 2/£2.50  
THYRISTOR 3A 25V 3/£0.50  
"L/SP 2 1/2" DIA. 40 OHMS 2/£1.00  
**RESISTORS 10/£0.09, 100/£0.80, ANY MIX E12-10 OHMS TO 1 MEG**  
**CAPACITORS**  
CERAMIC 27P to 8,700P E12 Series 10/£0.30.  
POLYESTER 0.01 to 1 10/£0.50, ANY MIX 1 MF 10/£1.00  
ELECTROLYTIC 63V 1MF TO 10MF 10/£0.70. 16V 10MF TO 100MF 10/£0.70  
**TELEPHONE ORDERS:** COV. (0203) 611597 USING ACCESS CARD NO  
V.A.T. add 12 1/2% TO ITEMS MARKED \*. TO ALL OTHERS ADD 8%

**IBEK SYSTEMS**

32 DUNSVILLE DRIVE  
COVENTRY  
CV2 2HS
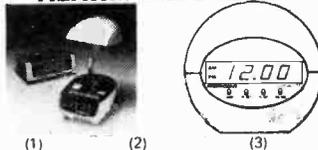
## BARGAINS FOR THE ELECTRONIC HANDYMAN BRANDED LED DIGITAL ALARM CLOCKS



Returned to Service Department within guarantee period.

- (1) With alarm repeat — S.R.S.P. of £17.00 offered at **£4.95 inc. VAT**
- (2) With luxury lamp and repeat alarm as featured in most major U.K. Mail Order catalogues. S.R.S.P. £31.00 — offered at **£8.95 inc. VAT**
- (3) With integral luxury light and repeat alarm also as featured in most major U.K. Mail Order catalogues. S.R.S.P. of £32.00 — offered at **£8.95 inc. VAT**

These will be sold as received from our customers with the existing fault(s) and without guarantee.

**PRESCOTT CLOCK AND WATCH COMPANY LIMITED**  
Prescott House, Humber Road, London NW2 6ER

## PRINTED CIRCUITS and HARDWARE

Comprehensive range Constructors' Hardware and accessories.

Selected range of popular components. Full range of HE printed circuit boards, normally ex-stock, same day despatch at competitive prices. P.C. Boards to individual designs. Resist-coated epoxy glass laminate for the d.i.y. man with full processing instructions (no unusual chemicals required).

Alfac range of etch resist transfers, and other drawing materials for p.c. boards.

Send 15p for catalogue.

**RAMAR CONSTRUCTOR SERVICES**  
MASON ROAD  
STRATFORD-ON-AVON  
WARWICKS. Tel. 4879

## MICROBITS NOW OPEN IN SURREY

Stockists of a wide range of Micro-Systems and Peripherals including the Exidy Sorcerer, Newbear 77-78, Panda, Nascom and Kim 1. Please telephone for details.

Also a wide range of Computer books and Bear Bags in stock.

34B London Road  
Blackwater  
Camberley  
SURREY  
Tel 0276 34044

## 1.2V NICADS

For UK orders add 50p for post and packing. All prices include VAT

### BUTTON CELLS

|        | Dia. | Hgt. | Price/Cell |
|--------|------|------|------------|
| 225mAh | 25.0 | 7.5  | 0.65       |
| 600mAh | 34.5 | 10.0 | £1.25      |

### VENTED CELLS

(for fast charge)


|           | Dia.            | Hgt.    | Price/Cell |
|-----------|-----------------|---------|------------|
| 0.45 Ah   | 17.5            | 28.0    | 0.95       |
| 0.5 Ah    | HP7 or          | Size AA | 1.10       |
| 1.2 Ah    | 22.5            | 49.0    | 1.40       |
| 1.8 Ah    | HP11 or         | Size C  | 1.95       |
| 4.0 Ah    | HP2 or          | Size D  | 2.75       |
| 6.0V Pack | 5x1.2 Ah nicads |         | 7.50       |

Tags available at extra 10p per cell for 0.5Ah, 1.2 Ah and 1.8 Ah nicads only.

Charger — Suitable for any of the above vented nicads — charges up to twelve similar cells in a series at a 50mA or 200mA rate. **£9.95**

Sizes approx. as shown.  
Mail order only

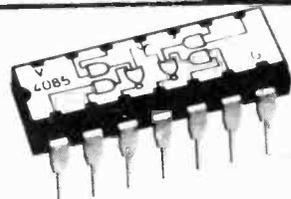**V&F SMALLCRAFT (POPLAR) LTD.**  
38 Stoneleigh Road, Clayhall, Ilford  
Essex  
01-550 6642



## LIVING LOGIC!

STICKIES are printed self-adhesive labels that stick to the top of ICs. They make dull, anonymous plastic blocks into diagrams that come ALIVE! See at-a-glance where to place your test probe or soldering iron — take the hassle out of ICs.

STICKIES are great for building and debugging prototypes, faultfinding, experimenting, teaching — even designing PCB layouts.

STICKIES come in packs for 7400- or 4000-series ICs. Each pack contains a sensible mix of more than 60 different IC types.

120-label pack — 80p, 480-label pack — £2.80, or 2-10 packs at £2.50 each, 11-plus £2.20 each.

Prices include VAT and first-class postage. Official orders welcome. Please state whether TTL or CMOS required.

For your STICKIES by return of post  
**CONCEPT ELECTRONICS, 8 Bayham Road**  
Sevenoaks, Kent TN13 3XA  
Phone: 0293 514110

## VIDEO MUSIC



Videograph II links to the aerial socket of your tv and provides a full colour GIANT oscilloscope display. A must for hi-fi, home entertainment, discos, organs etc.

New — signal invert control, integral square wave generator. Plus — full details for testing your audio system for transient distortion, crosstalk etc.

Complete **£19.95** Luxury cabinet and Kit only **£9.95** controls

INC POST PACKING VAT READY BUILT VIDEOGRAPH £59.95  
**WILLIAM STUART SYSTEMS LTD**  
Down House, Billingsley Road  
Herrington, Brentwood,  
Essex CM13 3SD  
Telephone: Brentwood (0277) 810244

## STRATHAND SECURITY ARMED?

If not you should be. We specialise in Alarm-equipment suitable for home, office or factory. All items brand new top quality fully guaranteed.

- 101 Magnet and reed switch. Flush fitting, 4 wire. Requires hole 12mm diameter by 34mm deep ..... 90p
- 102 Magnet and reed switch. Flush fitting screw terminals. Requires hole 15mm diameter by 14mm deep ..... £1.05
- 103 Magnet and reed switch. Surface fitting, 4 wire. Size 65mm by 13mm by 11mm ..... 90p
- 104 Magnet and reed switch. Heavy duty. Size 103mm by 20mm by 18mm. Two hole fixing ..... £3.00
- 105 Pressure pad — stair tread 22 1/2" x 6 1/2" ..... £1.35
- 106 Pressure pad — large 29 1/4" x 15" ..... £2.05
- 107 Window foil — self-adhesive — top quality. 70" roll by 1/4" wide. £3.17
- 108 Foil blocks — self-adhesive. (Joins foil to cable) ..... 19p
- 110 Keyswitches with mounting plate and cover ..... £3.70
- 111 Belt boxes heavy duty plastic coated metal ..... £8.05
- 112 Belt 6" heavy duty — very loud 12v D.C. .... £10.25
- 116 4 core cable 100mm — white ..... £10.75
- 123 Control panel to British Standard. Mains/battery, silent entry/exit. Anti-false alarm circuitry ..... £46.40

PLUS

Radar (microwave) units, automatic 999 dialling units with tape message, and many other items.

### STRATHAND SECURITY

44 St. Andrew's Square

Glasgow, G1

Tel: 041-552 6731/2

Callers Welcome

## ETI P.C.B.'s



Available for all ETI projects from day one of ETI, 'phone your order

SPECIAL OFFER — Single sided Pax PCB mat, four off. 4 1/4" x 6 1/2", 99p all up

**CROFTON ELECTRONICS LIMITED**

35 GROSVENOR ROAD, TWICKENHAM  
MIDDLESEX TW1 4AD · Tel: 01-891 1923

## THIS SECTION IS A PRE-PAYMENT SERVICE ONLY

**MINI-ADS: 31/4" x 21/8", 1-3 £38, 4-11 £36, 12 or more £34 per insertion. CLASSIFIED DISPLAY: 19p per word. Minimum 25 words. Boxed classifieds are £6.33 per col. centimetre. No P.O. Box Numbers can be accepted without full address.**

**Enquiries to: Advertising Department, 01-437 5982. 25-27 Oxford Street, London W1R 1RF**

**VMOS POWERFET VN67AF** (2A, 60V, 15W) 99p. Regulator 78L05 (TO-92) 29p. Fast LOC MOS, 4001B/07/11B/69 17p. 4013B 35p. 4016B 40p. 4017B 65p. 4020B 80p. Cheap Linear. 741 19p. CA3140E 40p. LF13741N (JFET 741) 35p. MC3401P (18V LM3900) 45p. 555 24p. 2N3819 14p. 10% discount over £5. P & P 20p. Mail Order only. More in informative lists. SAE to J. W. RIMMER, 367 GREEN LANES, LONDON N4 1DY.

### NASCOM 1

Complete with power supply, improved television modulator, updated monitor, full documentation and several useful programmes on cassette. Price £239. Tel. 029671 2097.

### COMMODORE PET HOME COMPUTER.

Six months old, as new. Plus books, manuals, games, tapes, and membership to users' club. £620. Write to A. Swenson, 'Lyndale,' Grange Road, Bowdon, Cheshire.

## MICROPROCESSORS 6800/Z80 CREED TELEPRINTERS

Consultancy, Stock  
Manufacture, Maintenance

**EPED**  
189 Hadlow Road  
Tonbridge, Kent

## DIGITAL TACHOMETER in kit form

Join the digital revolution  
Buy a Digitac rev. counter

#### Features:

Readable in direct sunlight  
Zero blanking  
Stable two digit reading  
Excellent resolution and linearity  
Suits all neg. earth ign. systems.  
Low cost. **£16.65** fully inclusive  
Please state system voltage, 2 or 4 stroke, number of cylinders and ign. coils.

## ELECTRONEQUIP

36, Merton Avenue,  
Portchester, Hants. PO16 9NE  
07018 73455

### MICROPROCESSORS AND COMPUTING

A book to give you a start

Contents. Binary Arithmetic, Principle of Operation, Programming, Glossary of Terms. 50 pages of explanation and diagrams. Price £2.30 plus 45p p&p (cheques, crossed P.O. only).

Educational Data and Technical Services  
59 Station Road, Cogenhoe, Northampton  
NN7 1LU

### NEW QUALITY STEREO AMP CHASSIS.

60W (RMS). Protected 3Qmin, 0.03% THD 12/30V Wkg 20 Trans, din socks controls; select, V/C, etc. Boxed data £9.95 (inc.) K. Lawrence, 1 Regent Road, Ilkley, W. Yorks.

### RAINBOW RIBBON CABLE at silly prices.

SAE for details. Trading Post, 4 Castle Street, Hastings, Sussex.

**HEWLETT-PACKARD HP-67.** As new, little used. Complete with: Case, recharger, battery, programme cards, blank cards, user's manual. £190. P. Burton, 10 Knowsley Close, Hoghton, Preston, 0254 852136.

## COLOUR MODULATOR

**Kit £6.95 FOR ALL TV GAMES!**  
Red, Green, Blue inputs (can be mixed)  
SUPER EXPLOSION FLASH EFFECT FOR  
- TANK BATTLE - FREE INTERFACE DE-  
MODULATOR  
inc. UHF  
Modulator  
TAILS  
**WILLIAM STUART SYSTEMS**  
Dower House, Billericay Road, Herongate, Brentwood, Essex  
CM13 3SO Tel. (0277) 810244  
Berclaycard/Access welcome

## MICROPROCESSORS AND MEMORIES

**STATIC RAMS**  
1K x 1 21L02 (250 nS) ..... £1.23  
256 x 4 2112 (450 nS) ..... £2.07  
1K x 4 2114 (450 nS) ..... £7.00

**MPU's**  
Z80 £15.00 8080A £7.60  
6800 £13.00

**8080 SUPPORT DEVICES**  
8212 .... £2.98 8228 .... £4.90  
8216 .... £2.10 8251 .... £5.75  
8224 .... £3.10 8255 .... £4.90

**6800 SUPPORT DEVICES**  
6810P .... £3.10 6821P .... £5.00  
6820P .... £5.00 6850P .... £6.70

**WIRE WRAP SOCKETS**  
16 pin ..... 45p 24 pin ..... 60p  
18 pin ..... 50p 40 pin ..... £1.12

(15p postage 9 packing)

## IMPS

Box 131, Reading RG6 2DR

**VALVE SOUND.** 16- and 30-watt Amplifiers by Parmeko. Excellent condition. Ex services. £18. — EPED 189 Hadlow Road, Tonbridge, Kent.

**FIFTEEN CMOS PROJECTS** — e.g. 70m.p.h. Alarm; Mini-'trombone'; Mystery Maze; Micro-power Indicator. Only £1 inc. brings FIFTEEN detailed circuits PLUS 14-pin socket and kits voucher, from DAVID IAN DESIGNS, 47 Hampton Court Parade, East Molesey, Surrey.

**CAR BATTERY MONITOR** all electronic with LED readout. PCB, IC and instructions only £2.75 inc. SAE for details. TRITECH ELECTRONICS, 190 RADING ROAD, LOUGHTON, ESSEX.

**TVH7 TELEVISION SOUND.** For high clarity HiFi listening and recording of Television programmes. Supplied built and tested on a single board measuring 105x52mm, for TV internal fitment, £9.80 inclusive, with wiring and comprehensive instructions. Eve Products, 7 Adel Heights, Leeds 16.

**20 INTO 2 E.T.I. MIXER SLIGHTLY CUSTOMISED.** Consisting of front panel and boards, sliders with pan, monitor, vol., gain, bass, treble, ETC. £220 ono, no pots. Must sell. Tel. (40) 64456.

### SPECIAL INTRODUCTORY OFFER £275

inc. VAT & P&P  
**OHIO SUPERBOARD II**  
computer on a board. BK basic in ROM, M/C code monitor in ROM. 4K user RAM plus 1K display RAM Upper/lower case plus gaming characters. Graphics. K.C. cassette interface. Modified for U.K. TV standard. Qwerty keyboard.

**BK VERSION £315 inc.**  
Extra available 24K RAM. Mini floppy interface. Output ports. Bus extensions. Ass/editor, etc.

**C.T.S.**  
1 HIGHER CALDERBROOK, LITTLEBOROUGH  
LANCS  
Tel. Littleborough (0708) 79332 any time

PLEASE  
MENTION  
ETI  
WHEN  
REPLYING  
TO  
ADVERTS

# SITUATIONS VACANT

## ASSISTANT FILM RECORDISTS & TRAINEES

Would you like to specialise in sound with BBC TV's Film Department?  
There are vacancies in West London

**ASSISTANT FILM RECORDISTS** work initially in sound transfer and dubbing areas operating sound recording and reproduction equipment for a wide range of programmes. There are prospects of progressing to mobile Film Recording work in due course. If you have professional experience in this field, the starting salary would be £3440 p.a. perhaps higher if exceptionally qualified, rising to £4140 p.a. An additional allowance is paid for shift work (not nights). Normal hearing is essential.

**EXCELLENT TRAINING** is given if you have ambitions to do this type of work but lack experience. You will need

'O' level standard of education, a basic knowledge of electronics and should be able to demonstrate a practical interest in sound and recording. Trainees will start at a salary of £3130 p.a. in Spring 1979 and should qualify for promotion to Assistant Film Recordists about a year later.

Conditions of Service are good and relocation expenses will be considered. Telephone or write immediately for an application form, enclosing addressed envelope and quoting reference number 78.G.2614/ET, to Appointments Department, BBC London W1A 1AA. Telephone 01-580 4468 Ext. 4619.



## AD INDEX

|                           |     |                          |                  |                         |             |
|---------------------------|-----|--------------------------|------------------|-------------------------|-------------|
| ALTEK .....               | 80  | GREENWELD .....          | 83               | POWERTRAN .....         | 2 & 6       |
| AMBIT .....               | 8   | HARRISON BROS .....      | 66               | PROGRESSIVE RADIO ..... | 72          |
| ASTRA-PAK .....           | 80  | H.B. COMPUTERS .....     | 78               | R.C.S. ....             | 106         |
| AUDIO ELECTRONICS .....   | 48  | HENRY'S .....            | 21, 32, 46 & 66  | ROGER SQUIRES .....     | 56          |
| BAMBER .....              | 78  | IBEK SYSTEMS .....       | 100              | R.T.V.C. ....           | 54          |
| BAYDIS .....              | 34  | I.L.P. ....              | 102              | SENTINEL SUPPLY .....   | 98          |
| BI-PAK .....              | 4&5 | JEREMY LORD              |                  | SERVICE TRADING .....   | 99          |
| B.N.R.S. ....             | 78  | SYNTHESISERS .....       | 84               | SINCLAIR .....          | 33          |
| CAMBRIDGE                 |     | KRAMER ...               | 26, 46, 72 & 100 | SINTEL .....            | 84          |
| LEARNING .....            | 60  | LB ELECTRONICS .....     | 100              | STEVENSON .....         | 53          |
| CATRONICS .....           | 9   | LEKTROKIT .....          | 103              | STRATHAND .....         | 86          |
| CHILTMead .....           | 90  | MAPLIN .....             | 108              | STRUTT .....            | 44          |
| CHROMASONICS .....        | 86  | MARSHALLS .....          | 22               | SWANLEY .....           | 56          |
| CHROMATRONICS .....       | 70  | METAC .....              | 38 & 39          | TAMTRONIK .....         | 26          |
| CRIMSON ELECTRIK .....    | 66  | MICRODIGITAL .....       | 34               | TECHNOMATIC .....       | 12 & 94     |
| CODESPEED .....           | 70  | MINIKITS .....           | 100              | TEMPUS .....            | 96          |
| COMMUNICATIONS MEAS ..... | 92  | MOUNTAINDENE .....       | 72               | T.K. ELECTRONICS .....  | 69          |
| COMP, COMP, COMP .....    | 107 | NASCOM .....             | 46               | TRAMPUS .....           | 68          |
| DELTA TECH .....          | 70  | NEWNES-BUTTERWORTH ..... | 48               | VERO .....              | 48          |
| DORAM .....               | 13  | NICHOLLS .....           | 26               | VIDEOTIME .....         | 34          |
| E.D.A. ....               | 56  | NIC MODELS .....         | 98               | WATFORD .....           | 10, 11 & 46 |
| ELECTROVALUE .....        | 45  | NORMAN INSKIP .....      | 101              | WILMSLOW .....          | 69          |
| GREENBANK .....           | 37  | POWELL .....             | 94               |                         |             |

# THE SORCERER HAS ARRIVED

Z80  
BASED  
32k RAM  
COMPUTER  
FOR LESS  
THAN  
£1,000

I WANTED  
TO SPEND LESS  
THAN £1,000 . . . . .  
MY SORCERER  
COST ME  
£950



## Introducing the personal computer you've waited for. The Exidy Sorcerer.

I didn't buy my personal computer until I found the one that had all the features I was looking for.

The Exidy Sorcerer does everything I wanted to do and a few things I never dreamed of.

It isn't magic. Exidy started with the best features of other computers, added some tricks of their own, and put it all together with more flexibility than ever before available. Presto! My reasons for waiting just disappeared.

### I wanted pre-packed programs.

Software on inexpensive cassette tapes for the Sorcerer is available from Exidy and many other software makers.

### I wanted user programmability

The Sorcerer's unique plug-in ROM PAC™ Cartridges contain programming languages such as Standard (Altair 8k\*) BASIC, Assembler and Editor (so I can develop system software), operating systems such as DOS (so I can also use FORTRAN and COBOL) and applications packages such as Word Processor.

\*Altair is a trademark of Perterc Computer Corp.

**I wanted Graphics**, and the Sorcerer is super. Its 256 character set — more than any other personal computer — includes 128 graphic symbols that I can define.

### I wanted high resolution video.

With 122,880 points in a 512 x 240 format, I get the most detailed illustrations.

### I wanted to display more information.

The Sorcerer displays 1920 characters in 30 lines of 64 characters — equal to a double-spaced typed page.

### I wanted a full, professional keyboard.

The Sorcerer's 79-key data processing keyboard provides designated graphics, the complete ASCII character set in upper and lower case, and a 16-key numeric pad.

**I wanted memory.** The 12k of ROM holds a Power-On Monitor and Standard BASIC; 32k of RAM is supplied on board.

**I wanted expandability.** Serial and parallel I/Os are built in, and the op-

tional 6-slot S-100 expansion unit lets my system grow.

### I wanted a computer that's easy enough for children to use.

I just connect my Sorcerer to a video display and a cassette tape recorder, and if I have any questions the easy-to-understand Operation and BASIC Programming manuals have the answers.

### I wanted to buy from an experienced Manufacturer.

In five years Exidy has become the third largest producer of microprocessor-based video arcade games.

### I wanted to spend less than £1,000.

(This is where COMP. does a little magic). My Sorcerer cost me £950!.

Now, what are you waiting for?

Call COMP. on 01-441 2922 or write to

**COMP** COMPUTER COMPONENTS

14 Station Road,  
New Barnet, Herts. EN5 1QW.

(Price shown ex. VAT)

DEALER ENQUIRIES INVITED, A LIMITED NUMBER OF DEALERSHIPS STILL AVAILABLE.

# MAPLIN

## launch their new Catalogue...

A massive new catalogue from Maplin that's even bigger and better than before. If you ever buy electronic components, this is the one catalogue you must not be without. Over 240 pages – some in full colour – it's a comprehensive guide to electronic components with hundreds of photographs and illustrations and page after page of invaluable data.

We stock just about every useful component you can think of. In fact some 5,000 different lines, many of them hard to get from anywhere else. Over 1000 new lines in our new catalogue. And with the service only Maplin provides, you won't regret sending for a copy of our fantastic catalogue. Orders paid before publication date will receive a set of 10 special offer coupons. Big Discounts on popular lines.

Several complete new projects for you to build with full construction details in the catalogue including:  
 A superb 40W per channel hi-fi stereo amplifier with lots of extra features found only on the most expensive ready-made equipment.  
 A hi-fi stereo tuner with FM, medium and long wave and UHF-TV sound Superb specification.  
 A complete home burglar alarm system including ultrasonic detectors.  
 A model railway train controller with inertia control for accelerating and braking.



# MAPLIN

## ELECTRONIC SUPPLIES

P.O. Box 3, Rayleigh, Essex SS6 8LR.  
 Telephone: Southend (0702) 715155.  
 Shop: 284 London Road, Westcliffe-on-Sea, Essex  
 (Closed on Monday).  
 Telephone: Southend (0702) 715157.

**Post this coupon now for your copy of our 1979-80 catalogue price 75p.**

Please send me a copy of your 280 page catalogue as soon as it is published (8th Jan. 1979). I enclose 75p but understand that if I am not completely satisfied I may return the catalogue to you within 14 days and have my 75p refunded immediately. If you live outside U.K. send £1 or ten International Coupons.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_