

electronics today

AUGUST 1979

INTERNATIONAL

50p

PLAY AWAY WITH ETI's
STRING THING

**AUDIO DISPLAY
CHEAP TRICK
MICROSENSE
BENCH AMP**



... NEWS PROJECTS MICROPROCESSORS AUDIO . . .

TRANSCENDENT 2000 SINGLE BOARD SYNTHESIZER


LIVE PERFORMANCE SYNTHESIZER DESIGNED BY CONSULTANT TIM ORR (FORMERLY SYNTHESIZER DESIGNER FOR EMS LIMITED) AND FEATURED AS A CONSTRUCTIONAL ARTICLE IN ELECTRONICS TODAY INTERNATIONAL

The TRANSCENDENT 2000 is a 3 octave instrument transposable 2 octaves up or down giving an effective 7 octave range. There is portamento, pitch bending, a VCO with shape and pitch modulation, a VCF with both low and high pass outputs and a separate dynamic sweep control, a noise generator and an ADSR envelope shaper. There is also a slow oscillator, a new pitch detector, ADSR repeat, sample and hold, and special circuitry with precision components to ensure tuning stability amongst its many features.

The kit includes fully finished metalwork, fully assembled solid teak cabinet, filter sweep pedal, professional quality components (all resistors either 2% metal oxide or 1/2% metal trim) and it really is complete — right down to the last nut and bolt and last piece of wire! There is even a 13A plug in the kit — you need buy absolutely no more parts before plugging in and making great music! Virtually all the components are on the one professional quality fibreglass PCB printed with component locations. All the controls mount directly on the main board, all connections to the board are made with connector plugs and construction is so simple it can be built easily in a few evenings by almost anyone capable of neat soldering! When finished you will possess a synthesizer comparable in performance and quality with ready built units selling for between £500 and £700!

**COMPLETE KIT
ONLY
£172.00 + VAT!**

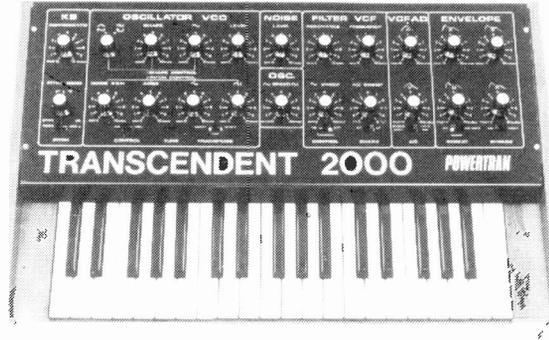Comprehensive handbook supplied with all complete kits! This fully describes construction and tells you how to set up your synthesizer with nothing more elaborate than a multi-meter and a pair of ears!



Cabinet size 24.6"x15.7"x4.8" (rear) 3.4" (front)

NEW!

THIS MONTH'S FRONT COVER FEATURE!


Another superb design by synthesizer expert Tim Orr!

TRANSCENDENT DPX

DIGITALLY CONTROLLED, TOUCH SENSITIVE, POLYPHONIC, MULTI-VOICE SYNTHESIZER

Like all of our kits the TRANSCENDENT DPX really is complete — fully finished metalwork, solid teak cabinet, professional quality components (all resistors 2% metal oxide), nuts, bolts, etc — even a 13A plug! Being digitally controlled the DPX may be operated by computer and the kit also includes a COMPUTER INTERFACE SOCKET!

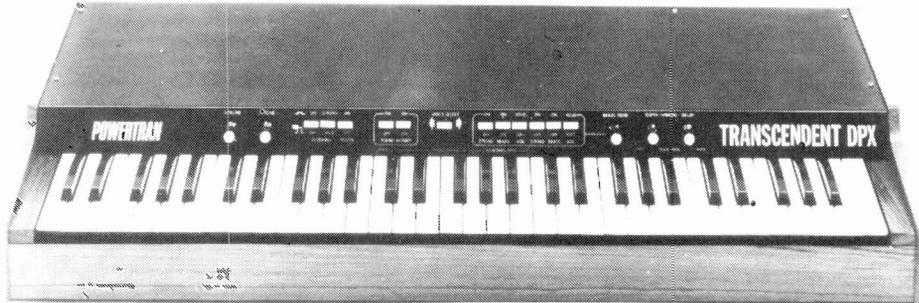**HARPSICORD
HONKY TONK
PIANO!
STRINGS!
BRASS!**




Panel size 19.0"x3.5". Depth 7.3"

**POWERFUL
DYNAMIC!
CHORUSING!
VIBRATO!
PHASING!**

COMPLETE KIT ONLY £365.00 + VAT!

CHROMATHEQUE 5000

**5 CHANNEL LIGHTING
EFFECTS SYSTEM**

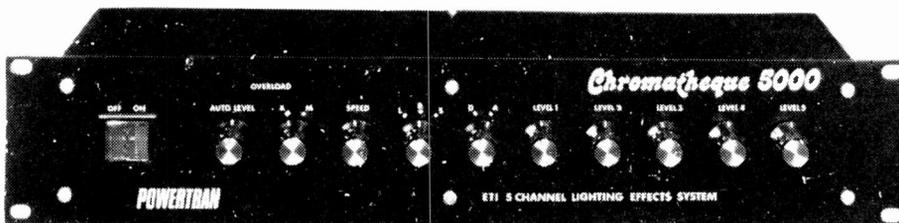

Cabinet size 36.3"x15.0"x5.0" (rear) 3.3" (front)

**COMPLETE KIT
ONLY
£49.50 + VAT!**

This versatile system featured as a constructional article in ELECTRONICS TODAY INTERNATIONAL has 5 frequency channels with individual level controls on each channel. Control of the lights is comprehensive to say the least. You can run the unit as a straightforward sound-to-light or have it strobe all the lights at a speed dependent upon music level or front panel control or use the internal digital circuitry which produces some superb random and sequencing effects. Each channel handles up to 500W and as the kit is a single board design wiring is minimal and construction very straightforward.

Kit includes fully finished metalwork, fibreglass PCB, controls, wire, etc — Complete right down to the last nut and bolt!

POWERTRAN

**ORDERING INFORMATION
AND MORE KITS ON PAGE 8**


All kits also available as separate packs (e.g. P.C.B., component sets, hardware sets, etc.) Prices in FREE CATALOGUE



Be an ensemble p.18



Amplify a beach p.67

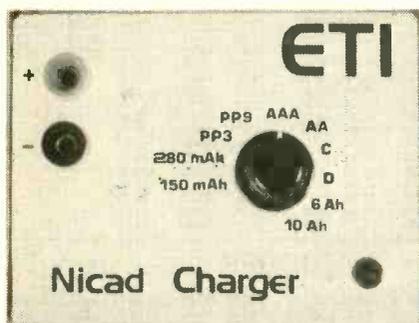

Make a charge p.29

electronics today

AUGUST 1979 VOL 8 NO 8 INTERNATIONAL

FEATURES

NEWS DIGEST	9	If it matters, it's in!
CHEAP TRICK	34	Make the pennies count
MICROSENSE	47	A new series for would-be MPUs!
MICROFILE	54	Home on the range
IMPEDANCE & PHASE	58	Well do <i>you</i> understand it?
ODD ODES	73	Getting physical!
READERS DESIGNS	79	Plain sailing
TECH TIPS	97	Readers circuit notions

PROJECTS

TRANSCENDENT DPX	18	Lots of strings to this
Ni-Cd CHARGER	29	Don't be flat broke
TELETEXT PART TWO	41	Final details
BENCH AMP	67	Vital workbench stuff!
AUDIO DISPLAY	87	Make a show of Blondie

INFORMATION

HOBBY ELECTRONICS	17	Next month's happenings
BINDERS	31	Keep it together
ETI BOOK SERVICE	33	Read this fine print
ETIPRINTS	40	The only way
TOP PROJECTS 7	45	Now out!
T-SHIRTS	53	Wear our colours
MARKETPLACE	62	Timely offers
SPECIALS	64	From us to you
ETI SEPTEMBER	71	A preview of the next ETI
COMPUTING TODAY	107	Just for micro-men

INTERNATIONAL EDITIONS

AUSTRALIA	Collyn Rivers Publisher Roger Harrison Acting Editor
HOLLAND	Anton Kriegsman Editor-in-Chief
CANADA	Graham Wideman Editor
GERMANY	Udo Wittig Editor



EDITORIAL AND ADVERTISEMENT OFFICE

25-27 Oxford Street, London W1R 1RF. Telephone 01-434 1781/2. Telex 8811896

Ron Harris, B.Sc.	Editor
Ian Graham B.Sc.	Editorial Assistant
Diego M. Rincon	Art Director
Pete Howells	Production
Paul Edwards, Tony Strakas	Technical Illustrators
Ray Marston	Project Editor
Keith Brindley, John Fitzgerald	Project Engineer
Steve Ramsahadeo	Project Development
Margaret Hewitt	Administration
Lorraine Stout	Editorial Secretary
Christopher Surgenor (Manager)	Advertising
Halvor Moorshead	Editorial Director

PUBLISHED BY
DISTRIBUTED BY

Modmags Ltd., 145 Charing Cross Road
Argus Distribution Ltd. (British Isles)
Gordon & Gotch Ltd. (Overseas)
QB Limited, Colchester

PRINTED BY

Electronics Today International is normally published on the first Friday of the month prior to the cover date

COPYRIGHT: All material is subject to world wide Copyright protection. All reasonable care is taken in the preparation of the magazine to ensure accuracy but ETI cannot be held responsible for it legally. Where errors do occur a correction will be published as soon as possible afterwards.

SEMICONDUCTORS - COMPONENTS

TRANSISTORS

AC107	£0.23	BC117	£0.23	BD179	£0.21	BFY50	£0.10	TP2955	£0.45	ZK29256	£0.10
AC113	£0.21	BC118	£0.10	BD180	£0.21	BFY51	£0.18	TP2955	£0.54	ZK29257	£0.09
AC115	£0.21	BC119	£0.27	BD181	£0.22	BFY52	£0.18	TP543	£0.24	ZK29258	£0.09
AC117	£0.32	BC120	£0.43	BD182	£0.27	BFY53	£0.18	TP590	£0.22	ZK29259	£0.09
AC117K	£0.36	BC125	£0.19	BD183	£1.03	BP19	£0.41	UT48	£0.20	ZK3010	£0.20
AC121	£0.21	BC126	£0.25	BD184	£1.19	BP29	£0.41	UT48	£0.20	ZK3011	£0.20
AC122	£0.16	BC132	£0.29	BD185	£0.73	BP19/20	£0.86	UT48	£0.11	ZK3053	£0.17
AC125	£0.19	BC134	£0.29	BD186	£0.73	BS225	£1.97	UT48	£0.11	ZK3054	£0.17
AC126	£0.10	BC135	£0.17	BD187	£0.81	BS226	£1.97	UT48	£0.11	ZK3055	£0.17
AC127	£0.19	BC136	£0.29	BD188	£0.81	BS227	£1.97	UT48	£0.11	ZK3056	£0.17
AC128	£0.15	BC137	£0.20	BD189	£0.84	BS228	£1.97	UT48	£0.11	ZK3057	£0.17
AC128K	£0.28	BC139	£0.35	BD190	£0.84	BS229	£1.97	UT48	£0.11	ZK3058	£0.17
AC132	£0.21	BC140	£0.32	BD191	£0.87	BS230	£1.97	UT48	£0.11	ZK3059	£0.17
AC137	£0.21	BC141	£0.30	BD192	£0.87	BS231	£1.97	UT48	£0.11	ZK3060	£0.17
AC138	£0.21	BC142	£0.30	BD193	£0.87	BS232	£1.97	UT48	£0.11	ZK3061	£0.17
AC141	£0.23	BC143	£0.24	BD194	£1.03	BS233	£1.97	UT48	£0.11	ZK3062	£0.17
AC141K	£0.32	BC145	£0.52	BD195	£1.07	BS234	£1.97	UT48	£0.11	ZK3063	£0.17
AC142	£0.21	BC147	£0.08	BD196	£1.07	BS235	£1.97	UT48	£0.11	ZK3064	£0.17
AC142K	£0.32	BC148	£0.08	BD197	£1.07	BS236	£1.97	UT48	£0.11	ZK3065	£0.17
AC151	£0.21	BC149	£0.08	BD198	£1.07	BS237	£1.97	UT48	£0.11	ZK3066	£0.17
AC153	£0.23	BC150	£0.23	BD199	£1.07	BS238	£1.97	UT48	£0.11	ZK3067	£0.17
AC154K	£0.32	BC151	£0.25	BD200	£1.07	BS239	£1.97	UT48	£0.11	ZK3068	£0.17
AC154	£0.21	BC152	£0.23	BD201	£1.07	BS240	£1.97	UT48	£0.11	ZK3069	£0.17
AC155	£0.21	BC153	£0.23	BD202	£1.07	BS241	£1.97	UT48	£0.11	ZK3070	£0.17
AC156	£0.21	BC154	£0.21	BD203	£1.07	BS242	£1.97	UT48	£0.11	ZK3071	£0.17
AC157	£0.21	BC157	£0.21	BD204	£1.07	BS243	£1.97	UT48	£0.11	ZK3072	£0.17
AC158	£0.21	BC158	£0.21	BD205	£1.07	BS244	£1.97	UT48	£0.11	ZK3073	£0.17
AC156	£0.21	BC159	£0.11	BD206	£1.07	BS245	£1.97	UT48	£0.11	ZK3074	£0.17
AC167	£0.21	BC160	£0.28	BD207	£1.07	BS246	£1.97	UT48	£0.11	ZK3075	£0.17
AC168	£0.27	BC161	£0.41	BD208	£1.07	BS247	£1.97	UT48	£0.11	ZK3076	£0.17
AC169	£0.21	BC167	£0.14	BD209	£1.07	BS248	£1.97	UT48	£0.11	ZK3077	£0.17
AC171	£0.27	BC168	£0.14	BD210	£1.07	BS249	£1.97	UT48	£0.11	ZK3078	£0.17
AC176	£0.27	BC169	£0.18	BD211	£1.07	BS250	£1.97	UT48	£0.11	ZK3079	£0.17
AC176K	£0.28	BC169C	£0.11	BD212	£1.07	BS251	£1.97	UT48	£0.11	ZK3080	£0.17
AC178	£0.27	BC170	£0.10	BD213	£0.50	BS252	£1.97	UT48	£0.11	ZK3081	£0.17
AC179	£0.27	BC171	£0.10	BD214	£0.50	BS253	£1.97	UT48	£0.11	ZK3082	£0.17
AC180	£0.30	BC172	£0.10	BD215	£0.50	BS254	£1.97	UT48	£0.11	ZK3083	£0.17
AC180K	£0.30	BC173	£0.10	BD216	£0.50	BS255	£1.97	UT48	£0.11	ZK3084	£0.17
AC181	£0.21	BC174	£0.10	BD217	£0.50	BS256	£1.97	UT48	£0.11	ZK3085	£0.17
AC181K	£0.30	BC175	£0.10	BD218	£0.50	BS257	£1.97	UT48	£0.11	ZK3086	£0.17
AC187	£0.19	BC177	£0.17	BD219	£0.50	BS258	£1.97	UT48	£0.11	ZK3087	£0.17
AC187K	£0.30	BC178	£0.17	BD220	£0.50	BS259	£1.97	UT48	£0.11	ZK3088	£0.17
AC188	£0.19	BC179	£0.17	BD221	£0.50	BS260	£1.97	UT48	£0.11	ZK3089	£0.17
AC188K	£0.30	BC180	£0.28	BD222	£0.51	BS261	£1.97	UT48	£0.11	ZK3090	£0.17
AC197	£0.30	BC181	£0.27	BD223	£0.51	BS262	£1.97	UT48	£0.11	ZK3091	£0.17
AC198	£0.37	BC182	£0.18	BD224	£0.51	BS263	£1.97	UT48	£0.11	ZK3092	£0.17
AC199	£0.37	BC182	£0.10	BD225	£0.51	BS264	£1.97	UT48	£0.11	ZK3093	£0.17
AC200	£0.37	BC183	£0.10	BD226	£0.51	BS265	£1.97	UT48	£0.11	ZK3094	£0.17
AC201	£0.37	BC184	£0.10	BD227	£0.51	BS266	£1.97	UT48	£0.11	ZK3095	£0.17
AC202	£0.37	BC184	£0.10	BD228	£0.51	BS267	£1.97	UT48	£0.11	ZK3096	£0.17
AC203	£0.37	BC184	£0.10	BD229	£0.51	BS268	£1.97	UT48	£0.11	ZK3097	£0.17
AC204	£0.37	BC184	£0.10	BD230	£0.51	BS269	£1.97	UT48	£0.11	ZK3098	£0.17
AC205	£0.37	BC184	£0.10	BD231	£0.51	BS270	£1.97	UT48	£0.11	ZK3099	£0.17
AC206	£0.37	BC184	£0.10	BD232	£0.51	BS271	£1.97	UT48	£0.11	ZK3100	£0.17
AC207	£0.37	BC184	£0.10	BD233	£0.51	BS272	£1.97	UT48	£0.11	ZK3101	£0.17
AC208	£0.37	BC184	£0.10	BD234	£0.51	BS273	£1.97	UT48	£0.11	ZK3102	£0.17
AC209	£0.37	BC184	£0.10	BD235	£0.51	BS274	£1.97	UT48	£0.11	ZK3103	£0.17
AC210	£0.37	BC184	£0.10	BD236	£0.51	BS275	£1.97	UT48	£0.11	ZK3104	£0.17
AC211	£0.37	BC184	£0.10	BD237	£0.51	BS276	£1.97	UT48	£0.11	ZK3105	£0.17
AC212	£0.37	BC184	£0.10	BD238	£0.51	BS277	£1.97	UT48	£0.11	ZK3106	£0.17
AC213	£0.37	BC184	£0.10	BD239	£0.51	BS278	£1.97	UT48	£0.11	ZK3107	£0.17
AC214	£0.37	BC184	£0.10	BD240	£0.51	BS279	£1.97	UT48	£0.11	ZK3108	£0.17
AC215	£0.37	BC184	£0.10	BD241	£0.51	BS280	£1.97	UT48	£0.11	ZK3109	£0.17
AC216	£0.37	BC184	£0.10	BD242	£0.51	BS281	£1.97	UT48	£0.11	ZK3110	£0.17
AC217	£0.37	BC184	£0.10	BD243	£0.51	BS282	£1.97	UT48	£0.11	ZK3111	£0.17
AC218	£0.37	BC184	£0.10	BD244	£0.51	BS283	£1.97	UT48	£0.11	ZK3112	£0.17
AC219	£0.37	BC184	£0.10	BD245	£0.51	BS284	£1.97	UT48	£0.11	ZK3113	£0.17
AC220	£0.37	BC184	£0.10	BD246	£0.51	BS285	£1.97	UT48	£0.11	ZK3114	£0.17
AC221	£0.37	BC184	£0.10	BD247	£0.51	BS286	£1.97	UT48	£0.11	ZK3115	£0.17
AC222	£0.37	BC184	£0.10	BD248	£0.51	BS287	£1.97	UT48	£0.11	ZK3116	£0.17
AC223	£0.37	BC184	£0.10	BD249	£0.51	BS288	£1.97	UT48	£0.11	ZK3117	£0.17
AC224	£0.37	BC184	£0.10	BD250	£0.51	BS289	£1.97	UT48	£0.11	ZK3118	£0.17
AC225	£0.37	BC184	£0.10	BD251	£0.51	BS290	£1.97	UT48	£0.11	ZK3119	£0.17
AC226	£0.37	BC184	£0.10	BD252	£0.51	BS291	£1.97	UT48	£0.11	ZK3120	£0.17
AC227	£0.37	BC184	£0.10	BD253	£0.51	BS292	£1.97	UT48	£0.11	ZK3121	£0.17
AC228	£0.37	BC184	£0.10	BD254	£0.51	BS293	£1.97	UT48	£0.11	ZK3122	£0.17
AC229	£0.37	BC184	£0.10	BD255	£0.51	BS294	£1.97	UT48	£0.11	ZK3123	£0.17
AC230	£0.37	BC184	£0.10	BD256	£0.51	BS295	£1.97	UT48	£0.11	ZK3124	£0.17
AC231	£0.37	BC184	£0.10	BD257	£0.51	BS296	£1.97	UT48	£0.11	ZK3125	£0.17
AC232	£0.37	BC184	£0.10	BD258	£0.51	BS297	£1.97	UT48	£0.11	ZK3126	£0.17
AC233	£0.37	BC184	£0.10	BD259	£0.51	BS298	£1.97	UT48	£0.11	ZK3127	£0.17
AC234	£0.37	BC184	£0.10	BD260	£0.51	BS299	£1.97	UT48	£0.11	ZK3128	£0.17
AC235	£0.37	BC184	£0.10	BD261	£0.51	BS300	£1.97	UT48	£0.11	ZK3129	£0.17
AC236	£0.37	BC184	£0.10	BD262	£0.51	BS301	£1.97	UT48	£0.11	ZK3130	£0.17
AC237	£0.37	BC184	£0.10	BD263	£0.51	BS302	£1.97	UT48	£0.11	ZK3131	£0.17
AC238	£0.37	BC184	£0.10	BD264	£0.51	BS303	£1.97	UT48	£0.11	ZK3132	£0.17
AC239	£0.37	BC184	£0.10	BD265	£0.51	BS304	£1.97	UT48	£0.11	ZK3133	£0.17
AC240	£0.37	BC184	£0.10	BD266	£0.51	BS305	£1.97	UT48	£0.11	ZK3134	£0.17
AC241	£0.37	BC184	£0.10	BD267	£0.51	BS306	£1.97	UT48	£0.11	ZK3135	£0.17
AC242	£0.37	BC184	£0.10	BD268	£0.51	BS307	£1.97	UT48	£0.11	ZK3136	£0.17
AC243	£0.37	BC184	£0.10	BD269	£0.51	BS308	£1.97	UT48	£0.11	ZK3137	£0.17
AC244	£0.37	BC184	£0.10	BD270	£0.51	BS309	£1.97	UT48	£0.11	ZK3138	£0.17
AC245	£0.37	BC184	£0.10	BD271	£0.51	BS310	£1.97	UT48	£0.11	ZK3139	£0.17
AC246	£0.37	BC184	£0.10	BD272	£0.51	BS311	£1.97	UT48	£0.11	ZK3140	£0.17
AC247	£0.37	BC184	£0.10	BD273	£0.51	BS312	£1.97	UT48	£0.11	ZK3141	£0.17
AC248	£0.37	BC184	£0.10	BD274	£0.51	BS313	£1.97	UT48	£0.11	ZK3142	£0.17
AC249	£0.37	BC184	£0.10	BD275	£0.51	BS314	£1.97	UT48	£0.11	ZK3143	£0.17
AC250	£0.37	BC184	£0.10	BD276	£0.51	BS315	£1.97	UT48	£0.11	ZK3144	£0.17
AC251	£0.37	BC184	£0.10	BD277	£0.51	BS316	£1.97	UT48	£0.11	ZK3145	£0.17
AC252	£0.37	BC184	£0.10	BD278	£0.51	BS317	£1.97	UT48	£0.11	ZK3146	£0.17
AC253	£0.37	BC184	£0.10								

BOOKS AND COMPONENTS

BOOKS BY BABANI

BP6	Engineers & Machinists Ref. Tables	40p†
BP14	2nd Book Transistor Equivs. & Subs	£1.10†
BP22	79 Electronic Novelty Circuits	75p†
BP24	52 Projects Using IC741 (or Equiv)	75p†
BP26	Radio Antenna Book Long Distance Reception & Transmission	85p†
BP27	Giant Chart of Radio Electronic Semiconductor & Logic Symbols	80p†
BP32	Build Metal & Treasure Locators	85p†
BP34	Practical Repair / Renovation C/TV	85p†
BP35	Handbook of IC Audio Pre-amplifier & Power Amplifier Construction	95p†
BP36	50 Ccts use Germ./Sil./Zener Diodes	75p†
BP37	50 Projects Using Relays/SCR/Triacs	£1.10†
BP39	50 Field Effect Trans Projects	£1.25†
BP40	Digital IC Equivs. & Pin Connection	£2.50†
BP41	Linear IC Equivs. & Pin Connection	£2.75†
BP42	50 Simple LED Circuits	75p†
BP43	How to make Walkie-Talkies	£1.25†
BP44	IC 555 Timer Projects	£1.45†
BP45	Projects on Opto-electronics	£1.35†
BP46	Radio Circuits Using IC's	£1.35†
BP47	Mobile Discotheque Handbook	£1.35†
BP48	Electronics Projects for Beginners	£1.35†
BP49	Popular Electronic Projects	£1.45†
BP50	IC LM3900 Projects	£1.35†
BP55	Radio Stations Guide	£1.45†
BP160	Coil Design & Construction Manual	85p†
BP202	Handbook of Integrated Circuits Equivalent & Substitutes	75p†
BP205	1st Book Hi-Fi Speaker Enclosures	75p†
BP213	Circuits for Model Railways	85p†
BP215	Shortwave Circuits & Gear for Experimenters & Radio Hams	85p†
BP216	Electronic Gadgets & Games	85p†
BP217	Solid State Power Supply Handbook	85p†
BP221	28 Tested Transistor Projects	95p†
BP222	Short-wave Receivers for Beginners	95p†
BP223	50 Projects using IC CA3130	95p†
BP224	50 CMOS IC Projects	95p†
BP225	A Practical Intro to Digital IC's	95p†
BP226	Build Advanced Short-wave Receivers	£1.20†
BP227	Beginners Guide to Building Electronic Projects	£1.25†

NEWNES BOOKS

216	Transistors 3rd Ed.	£1.00
217	Integrated Circuits	£1.00
218	Radio & Television	£1.25
219	Electronics	£1.15
220	Colour TV 2nd Ed.	£1.15
221	Hi-Fi	£1.15
222	20 Solid State Proj. for Car	£1.05
223	20 Solid State Proj. for Home	£1.05
224	110 Int. Circ. Proj. for Home	£2.95
225	110 Thyristor Projects	£2.50
226	Operational Amp. Proj. for Home	£2.50
227	110 Practical IC Proj. for Home	£2.75
228	Electricity	£1.15
229	Beginners Guide to Electronics	£2.25
230	Beginners Guide to Television	£2.25
231	Beginners Guide to Transistors	£2.25
232	Beginners Guide to Electric Wiring	£2.75
233	Beginners Guide to Radio	£2.25
234	Guide to Colour TV	£2.25
235	Electronic Diagrams	£1.80
236	Electronic Components	£1.80
237	Printed Circuit Assembly	£1.80
238	Transistor Pocket Book	£3.90
239	50 Photoelectric Circuits	£1.80
240	Semiconductor Handbook Part 1	£5.25
241	Semiconductor Handbook Part 2	£4.28
242	Electronics Pocket Book	£3.90
243	Radio Value & Semiconductor Data	£2.40
244	Beginners Guide to Integrated Circuits	£2.75
209	BI-PAK TTL Data Book	50p
	BI-PAK CMOS Data Book	50p

OPTOELECTRONICS

NEW INCREASED RANGE — ALL 1ST QUALITY LED'S (diffused)

O/no.	Type	Size	Colour	Price
1501	ARL209 (TIL209)	3mm (1.25)	RED	£0.10
1502	MIL3232 (TIL211)	3mm (1.25)	GREEN	£0.15
1503	MIL3331 (OP212A)	3mm (1.25)	YELLOW	£0.15
1504	ARL4850 (FLV117)	5mm (2)	RED	£0.10
1505	MIL5251 (TIL222)	5mm (2)	GREEN	£0.15
1506	MIL5351 (MV5353)	5mm (2)	YELLOW	£0.15
1509	FLV111	5mm (2)	CLEAR	£0.11
		(III, Red)		
SUPER 'Hi-Brite' Type				
1521	MIL32	3mm (1.25)	RED	£0.10
1522	MIL52	5mm (2)	RED	£0.10
1514	ORP12 Light dependent resistor			£0.55
1520	OC71 Photo transistor			£0.35
LED CLIPS				
1508/125	pack of 5	125 clips		£0.15
1508/2	pack of 2	2 clips		£0.18
DISPLAYS:				
DL703	7 segment D.P. left (1.30" height)		Common Anode	o/no. 1523 £0.70
RED Single Digit			Common Anode	o/no. 1510 £0.95
DL707	7 segment D.P. left (0.3" height)		Common Anode	o/no. 1524 £1.70
RED Single Digit			Common Anode	o/no. 1511 £1.70
DL527	7 segment D.P. left (1.50" height)		Common Anode	o/no. 1512 £1.70
RED Two-Digit Reflector			Common Anode	o/no. 1513 £1.70
DL727	7 segment D.P. right (1.50" height)		Common Anode	o/no. 1514 £1.70
RED Single Digit Light Pipe			Common Anode	o/no. 1515 £1.70

OPTO-ISOLATORS

Isolation Breakdown — Voltage 1500 — continuous fwd current 100mA

CIL74 Single Channel 6 pin DIP standard type — optically coupled pair with infra-red LED Emitter and NPN Silicon Photo Transistor
o/no. 1485 £0.50

CILQ74 Multi-Channel 8 pin DIP Two Isolated Channels
o/no. 1488 £1.00

CILQ74 Multi-Channel 16 pin DIP Four Isolated Channels
o/no. 1489 £2.20

MEL 11 (TILB1) NPN Light Detector
Silicon Photo Darlington Amplifier — VCB0.40V VCEO 30V VECO 10V Ic 100mA Ptot:300mW IL Min 0.5 Typ.2mA ID 100mA nA
£0.25

SWITCHES

Description	No.	Price
OPDT miniature slide	1973	£0.15
DPDT standard slide	1974	£0.16
Toggle switch SPST 1 1/2 amp 250V ac	1975	£0.37
Toggle switch DPDT 1 amp 250V ac	1976	£0.47
Rotary on-off mains switch	1977	£0.56
Push switch — Push to make	1978	£0.15
Push switch — Push to break	1979	£0.20

ROCKER SWITCH	Colour	No.	Price
A range of rocker switches SPST — moulded in high insulation material available in a choice of colours ideal for small apparatus	RED	1980	£0.33
	BLACK	1981	£0.33
	WHITE	1982	£0.33
	BLUE	1983	£0.33
	YELLOW	1984	£0.33
	LUMINOUS	1985	£0.33

Description	No.	Price
Miniature SPST toggle 2 amp 250V ac	1958	£0.78
Miniature SPST toggle 2 amp 250V ac	1959	£0.84
Miniature DPDT toggle 2 amp 250V ac	1960	£0.90
Miniature DPDT toggle centre off 2 amp 250V ac	1961	£1.06
Push-button SPST 2 amp 250V ac	1962	£1.01
Push-button SPST 2 amp 250V ac	1963	£1.06
Push-button DPDT 2 amp 250V ac	1964	£1.35

MIOGET WAFER SWITCHES

Single bank wafer type — suitable for switching at 250V ac 100mA or 150V dc in non-reactive loads make-before-break contacts. These switches have a spindle 0.25 in dia and 30 indexing.

Description	No.	Price
1 pole 12 way	1965	£0.54
2 pole 6 way	1966	£0.54
3 pole 4 way	1967	£0.54
4 pole 3 way	1968	£0.54

MICRO SWITCHES

Plastic button gives simple 1 pole change over action
Rating 10 amp 250V ac
£0.27

FUSE HOLDERS AND FUSES

Description	No.	Price
20mm x5mm chassis mounting	506	£0.18
1 1/4" x 1/4" chassis mounting	507	£0.13
1 1/4" car inline type	508	£0.18
Panel mounting 20mm	509	£0.22
Panel mounting 1 1/4"	510	£0.36

QUICK BLOW 20mm

Type	No.	Type	No.	Type	No.
150mA	611	6p	1A	615	5p
250mA	612	5p	1.5A	616	6p
550mA	613	5p	2A	617	5p
800mA	614	8p	2.5A	618	8p

ANTI-SURGE 20mm

Type	No.	Type	No.	Type	No.
100mA	622	1A	625	2.5A	628
250mA	623	2A	626	3.15A	629
500mA	624	1.6A	627	5A	630

QUICK-BLOW 1 1/4"

Type	No.	Type	No.	Type	No.
250mA	631	500mA	632	800mA	634

QUICK-BLOW 1 1/4"

Type	No.	Type	No.	Type	No.
1A	635	2.5A	638	4A	641
2A	637	3A	639	5A	642

NUTS AND BOLTS

BA BOLTS — packs of BA threaded cadmium plated screws slotted cheese head. Supplied in multiples of 50

Type	No.	Price	Type	No.	Price
1/16" OBA	839	£1.29	1/16" 4BA	846	£0.34
1/16" OBA	840	£0.81	1/16" 4BA	847	£0.27
1/16" 2BA	842	£0.70	1/16" 6BA	848	£0.43
1/16" 2BA	843	£0.48	1/16" 6BA	849	£0.22
1/16" 2BA	844	£0.56	1/16" 6BA	850	£0.27
1/16" 4BA	845	£0.47			

BA NUTS — packs of cadmium plated full nuts in multiples of 50

Type	No.	Price	Type	No.	Price
OBA	855	£0.77	4BA	857	£0.32
2BA	856	£0.51	6BA	858	£0.25

BA WASHERS — flat cadmium plated plain stamped washers supplied in multiples of 50

Type	No.	Price	Type	No.	Price
OBA	859	£0.15	4BA	861	£0.13
2BA	860	£0.13	6BA	862	£0.13

SOLDER TAGS — Hot tinned supplied in multiples of 50

Type	No.	Price	Type	No.	Price
OBA	851	£0.43	4BA	853	£0.23
2BA	852	£0.30	6BA	854	£0.23

AUDIO LEADS

No.	Type	Price
107	FM indoor Ribbon Aerial	87p
113	3.5mm Jack plug to 3.5mm Jack plug. Length 1.5m	84p
114	5 pin DIN plug to 3.5mm Jack connected to pins 3 & 5. Length 1.5m	96p
115	5 pin DIN plug to 3.5mm Jack connected to pins 1 & 4. Length 1.5m	96p
116	Car aerial extension Screened insulated lead. Fitted plug and socket	£1.41
117	AC mains connecting lead for cassette recorders and radios. 2 metres	77p
118	5 pin DIN phono plug to stereo headphone Jack socket	£1.18
119	2 + 2 pin DIN plugs to stereo Jack socket with attenuation network for stereo headphones. Length 0.2m	£1.01
120	Car stereo connector. Variable geometry plug to fit most car cassettes. 8 track cartridge and combination units. Supplied with inlined fuse power lead and instructions	67p
123	6.6m Coiled Guitar Lead Mono Jack plug to Mono Jack plug Black	£1.69
124	3 pin DIN plug to 3 pin DIN plug. Length 1.5m	84p
125	5 pin DIN plug to 5 pin DIN plug. Length 1.5m	84p
126	5 pin DIN plug to Tinned open end. Length 1.5m	84p
127	5 pin DIN plug to 4 Phono Plugs. All colour coded. Length 1.5m	£1.46
128	5 pin DIN plug to 5 pin DIN socket. Length 1.5m	90p
129	5 pin DIN plug to 5 pin DIN plug mirror image. Length 1.5m	£1.18
130	2 pin DIN plug to 2 pin DIN inline socket. Length 5m	77p
131	5 pin DIN plug to 3 pin DIN plug 1 & 4 and 3 & 5. Length 1.5m	93p
132	2 pin DIN plug to 2 pin DIN socket. Length 10m	£1.10
133	5 pin DIN plug to 2 Phono plugs. Connected pins 3 & 5. Length 1.5m	84p
134	5 pin DIN plug to 2 Phono sockets. Connected pins 3 & 5. Length 23cm	77p
135	5 pin DIN socket to 2 Phono plugs. Connected pins 3 & 5. Length 23cm	77p
136	Coiled stereo headphone extension lead. Black. Length 6m	£1.97
178	AC mains lead for calculators, etc	51p

CASES AND BOXES

INSTRUMENT CASES. In two sections, vinyl covered top and sides, aluminium bottom. front and back.

No.	Length	Width	Height	Price
155	8in	5 1/2in	2in	£1.80
156	11in	6in	3in	£2.74
157	6in	4 1/4in	1 1/4in	£1.68
158	9in	5 1/4in	2 1/4in	£2.28

ALUMINIUM BOXES. Made from bright ali... folded construction each box complete with half-inch deep lid and screws.

No.	Length	Width	Height	Price
159	5 1/4in	2 1/4in	1 1/4in	80p
160	4in	4in	1 1/2in	80p
161	4in	2 1/4in	1 1/2in	80p
162	5 1/4in	4in	1 1/2in	91p
163	4in	2 1/2in	2in	82p
164	3in	2in	1in	57p
165	7in	5in	2 1/2in	£1.34
166	8in	6in	3in	£1.71
167	6in	4in	2in	£1.11

TRANSFORMERS

MINIATURE MAINS Primary 240V

No.	Type	Price
2021	6V-0-6V 100mA	£1.01
2022	9V-0-9V 100mA	£1.01
2023	12V-0-12V 100mA	£1.26

MINIATURE MAINS Primary 240V
with two independent secondary windings

No.	Type	Price
2024	MT280-0-6V 0-6V RMS	£1.80
2025	MT150-0-12V 0-12V RMS	£1.80

1 AMP MAINS Primary 240V

No.	Type	Price	P & P
2026	0V-0-6V 1 amp	£2.70	P & P 45p

ACCESS
BARCLAYCARD
CASH
CHEQUE

■ FREEPOST ON ORDERS
■ VAT INCLUSIVE PRICES
■ ADD 30p P&P
■ 24 HR TELEPHONE ANSWERING SERVICE

GMT ELECTRONICS A

Freepost

Birmingham B19 1BR

TEL ORDERS WELCOME

DIGITAL INTEGRATED CIRCUITS

4000 Buffered CMOS - High Speed

5-15V 'B' Series, Up to 20MHz

7400 T.T.L.		7400 T.T.L.		7400 T.T.L.		7400 T.T.L.		7400 T.T.L.		7400 T.T.L.		7400 T.T.L.		7400 T.T.L.					
HEF4000	14	HEF4046	100	HEF4514	250	N7400N	9	N7444N	83	N74122N	39	N74192N	60	N74LS28N	32	N74LS138N	85	N74LS253N	105
HEF4001	14	HEF4047	87	HEF4515	298	N7401N	11	N7445N	65	N74123N	37	N74194N	80	N74LS30N	16	N74LS139N	85	N74LS257N	104
HEF4002	14	HEF4048	28	HEF4516	90	N7402N	11	N7446AN	62	N74125N	32	N74195N	79	N74LS32N	24	N74LS153N	76	N74LS258N	107
HEF4006	95	HEF4050	28	HEF4517	382	N7403N	11	N7447AN	51	N74126N	32	N74198N	120	N74LS33N	32	N74LS154N	122	N74LS260A	200
HEF4007	14	HEF4051	69	HEF4518	69	N7404N	12	N7448AN	44	N74128N	74	N74199N	139	N74LS37N	24	N74LS155N	80	N74LS261N	300
HEF4008	80	HEF4052	72	HEF4519	55	N7405N	12	N7449N	13	N74132N	46	N74221N	160	N74LS38N	24	N74LS156N	80	N74LS266A	40
HEF4011	14	HEF4053	72	HEF4520	65	N7406N	25	N7451N	13	N74133N	46	N74229N	116	N74LS40N	22	N74LS157N	54	N74LS273N	130
HEF4012	14	HEF4056	37	HEF4521	188	N7407N	27	N7453N	15	N74147N	125	N74298N	200	N74LS42N	53	N74LS158N	60	N74LS283N	116
HEF4013	32	HEF4067	380	HEF4528	99	N7408N	13	N7454N	13	N74148N	83	N74365N	150	N74LS51N	22	N74LS160N	120	N74LS289N	116
HEF4019	46	HEF4073	16	HEF4532	120	N7409N	13	N7460N	13	N74150N	65	N74366N	150	N74LS54N	16	N74LS161N	78	N74LS293N	100
HEF4015	60	HEF4068	14	HEF4534	510	N7410N	11	N7470N	26	N74151N	46	N74367N	120	N74LS55N	22	N74LS162N	78	N74LS298N	100
HEF4016	35	HEF4070	14	HEF4539	110	N7411N	18	N7472N	22	N74153N	55	N74368N	150	N74LS59N	29	N74LS163N	130	N74LS324N	170
HEF4017	55	HEF4071	14	HEF4543	155	N7412N	17	N7473N	23	N74154N	96			N74LS75N	40	N74LS164N	90	N74LS365N	105
HEF4018	65	HEF4072	16	HEF4555	78	N7413N	23	N7474N	23	N74155N	53			N74LS76N	33	N74LS165N	200	N74LS366N	105
HEF4020	88	HEF4075	16	HEF4557	385	N7414N	46	N7475N	28	N74156N	48			N74LS78N	33	N74LS166N	100	N74LS367N	105
HEF4021	85	HEF4076	85	HEF4565	97	N7417N	23	N7476N	26	N74157N	49			N74LS83AN	97	N74LS174N	100	N74LS368N	105
HEF4022	82	HEF4077	14	HEF4724	171	N7420N	11	N7483N	63	N74160N	74			N74LS85N	30	N74LS181N	320	N74LS374N	150
HEF4023	14	HEF4078	16	HEF4097	90	N7421N	26	N7485N	65	N74161N	74			N74LS87N	16	N74LS182N	91	N74LS375N	150
HEF4024	45	HEF4079	16	HEF4098	73	N7425N	27	N7486N	23	N74162N	74			N74LS89N	16	N74LS183N	91	N74LS376N	150
HEF4025	14	HEF4082	15	HEF4106	62	N7426N	22	N7489N	30	N74163N	74			N74LS91N	16	N74LS184N	91	N74LS377N	150
HEF4027	32	HEF4085	64	HEF4119	119	N7427N	22	N7491AN	60	N74164AN	65			N74LS93N	16	N74LS185N	128	N74LS378N	150
HEF4028	52	HEF4086	64	HEF4161	119	N7428N	30	N7492N	33	N74165AN	65			N74LS95N	22	N74LS186N	116	N74LS379N	150
HEF4029	60	HEF4093	50	HEF4162	119	N7430N	11	N7493N	31	N74166AN	93			N74LS97N	16	N74LS187N	120	N74LS380N	150
HEF4030	46	HEF4094	175	HEF4163	119	N7432N	21	N7494AN	74	N74170N	134			N74LS99N	38	N74LS188N	90	N74LS381N	150
HEF4031	200	HEF4104	166	HEF4174	119	N7433N	30	N7495AN	48	N74173N	111			N74LS101N	22	N74LS189N	90	N74LS382N	150
HEF4035	110	HEF4502	91	HEF4175	119	N7437N	21	N7496N	46	N74174AN	63			N74LS102N	22	N74LS190N	120	N74LS383N	150
HEF4040	68	HEF4505	571	HEF4192	140	N7438N	21	N74100N	88	N74175N	62			N74LS104N	74	N74LS191N	120	N74LS384N	150
HEF4041	75	HEF4508	51	HEF4193	140	N7439N	60	N74107N	25	N74180N	80			N74LS106N	24	N74LS192N	120	N74LS385N	150
HEF4042	54	HEF4510	70	HEF4194	119	N7440N	12	N74109N	42	N74181N	165			N74LS108N	16	N74LS193N	120	N74LS386N	150
HEF4043	79	HEF4511	114	HEF4195	117	N7442N	40	N74116N	146	N74182N	69			N74LS110N	22	N74LS194N	120	N74LS387N	150
HEF4044	84	HEF4512	98			N7443N	79	N74121N	23	N74192N	65			N74LS112N	24	N74LS195N	120	N74LS388N	150

LINEAR INTEGRATED CIRCUITS

CA3011	92	NE592K	162
CA3018	75	RC4136	130
CA3020	191	TBA1205	79
CA3028A	86	TCA580	346
CA3046	76	TCA720	450
CA3048	245	TCA740	450
CA3080E	70	TDA1008	326
CA3089E	253	TDA1022	648
CA3130E	90	TDA1028	338
CA3140E	32	TDA1029	338
CA3189E	266	TDA1034B	217
LM301AN	30	TDA2581	266
LM308N	95	TDA2640	292
LM318N	200	TLO81CP	75
LM319N	216	TLO84CN	140
LM324AN	70	UA709CT	46
LM339N	71	UA709CN	40
LM381N	110	UA710CN	41
LM381AN	180	UA711CN	65
LM382	120	UA711CT	42
		UA711CN	18
		UA747CN	50
		UA748CN	35
NC1458N	35		
NC1496N	97		
NE531	119	Voltage Regulators	
NE536T	216	LM309DA (K)	108
NE540	225	UA723CN	38
NE555N	25	UA7805CU	65
NE559A	60	UA7812CU	65
NE560N	351	UA7815CU	65
NE561N	427	UA7905CU	86
NE562N	461	UA7912CU	86
NE565N	120	UA7915CU	86
NE566N	155	UA7918CU	86
NE567N	170	UA78L06CS	32
NE570N	405	UA78L12CS	32
NE571N	459	UA78L15CS	32

OPTO ELECTRONICS

Light Emitting Diodes, Individual	Order Code
125" (3mm) Red	14 CQY54
Green	17 CQY95
Yellow	19 CQY97
Panel Mounting Clip to suit.	3 LEDs Clip
2" (5mm) Red	15 CQY24A
Green	17 CQY94
Yellow	19 CQY36
Panel Mounting Clip to suit.	5 LEDs Clip
Light Emitting Diodes - 7 Segment Display	Order Code
3" (7.6mm) C. Anode R.H. Decimal Pt. Red	160 XAN3061
C. Anode R.H. Decimal Pt. Green	199 XAN3051
C. Cathode R.H. Decimal Pt. Red, Low current drain	160 XAN3074
6" (15.2mm) C. Anode L.H. Decimal Pt. Red	230 XAN6620
C. Anode L.H. Decimal Pt. Green	230 XAN6520
C. Cathode L.H. Decimal Pt. Red	230 XAN6640
Phototransistors	Order Code
ORP12	90 ORP12
ORP61	90 ORP61
Photocoupler	Order Code
FCDB20	150 FCD820

SWITCHES

Miniature Toggle - Honeywell	Order Code
SPDT 2A/250V A.C., 5A/28V D.C.	58 SW 8A1011
SPDT C/Off	67 SW 8A1021
SPDT Double Bias To Centre	75 SW 8A1041
SPDT Single Bias To Centre	75 SW 8A1051
SPDT Bias	70 SW 8A1061
DPDT	86 SW 8A2011
DPDT C/Off	92 SW 8A2021
DPDT Double Bias To Centre	102 SW 8A2041
DPDT Single Bias To Centre	102 SW 8A2051
DPDT Bias	96 SW 8A2061
Miniature Push - C & K	Order Code
SP Push To Make, Momentary	54 SW 8531
SP Push To Break, Momentary	54 SW 8533
Slide - Switchcraft	Order Code
DPDT Standard Actuator	36 SW 46206
DPDT Slot Actuator, Voltage Change, Marked 110/240	43 SW 46206F

SEMICONDUCTORS

Diodes	Order Code
IN827	193
IN914	4
IN916	5
IN4001	4
IN4002	4
IN4003	6
IN4004	6
IN4005	7
IN4006	7
IN4148	8
IN5402	15
BAX13	5
BAV38	27
BB106(4)	12
BB110G	61
BY127	15
BY206	34
BYX10	19
DA47	10
OA90	7
OA91	7
OA200	9
DA202	9
Microwave	
BAW95D	1091
CL896C	252
CXY11	1280
Zener Diodes	Order Code
400mW CV7-C33	13W CV75-C75
BZY88/BZX79 + Voltage	8 BZX81 + Voltage
16	
Transistors	Order Code
2N929	37
2N1893	30
2N218A	28
2N2222	21
2N2369	19
2N2369A	20
2N2646	42
2N2704	49
2N2885	28
2N2904	24
2N2904A	24
2N2905	22
2N2906	19
2N2906	19
2N2907	22
2N2907A	25
2N2918	330
2N2926G	11
2N3053	17
2N3054	50
2N3055	50
2N3056	97
Full USB Test	88
2N3340	30
2N3442	141
2N3702	8
2N3703	8
2N3704	8
2N3705	9
2N3706	9
2N3707	9
2N3708	9
2N3709	11
2N3713	270
2N3819	20
2N3820	39
2N3866	97
2N3903	20
2N3904	8
2N3905	12
2N3906	12
2N3907	95
2N4347	227
2N4401	20
2N4403	20
2N4416	86
2N4427	206
2N4856	158
2N4858	134
2N4860	122
2N5294	43
2N5416	108
2N5457	35
2N5458	30
2N5459	32
2N6258	432
40673	80
AC188	22
AD159	38
AD162	38
BC107	10
BC107B	14
BC108	10
BC108B	14
BC108C	16
BC109	10
BC109B	17
BC109C	18
BC147	7
BC148	9
BC149	8
BC157	10
BC158	3
BC159	11
BC177	15
BC178	15
BC179	18
BC182	10
BC182L	11
BC183	10
BC183L	11

POWERTRAN

FOR ELECTRONIC KITS OF DISTINCTION

200 + 200 watt AMPLIFIER

As featured in *Electronics Today International*

400W rms continuous — 800W peak!

0.03% THD at FULL power!

PLUS all the following features too!

- * Each channel totally independent with its own stabilised power supply driven by custom designed TOROIDAL transformers!
- * Inherent reliability — monster heat sinks for cool running at the hottest venues — electronic open and short circuit protection!
- * Ultra low feedback (an incredible low 14dB overall!), super high slewing rate (20V/μs), 200W rms continuous to 4 ohm from EACH channel, input sensitivity 0.775V (0dB).
- * Professional quality components, sturdy 19" rack mounting chassis complete with sleeve and feet for free standing work too.
- * Easy to build — plenty of working space with ready access to all components, minimal wiring, extensive instruction suitable for both experience constructors and newcomers to electronics.
- * Value for money — quality and performance comparable with ready-built amplifiers costing over £600!

PSI 4002 STUDIO MODEL



cabinet size 17.2" x 17.2" x 6.7"

COMPLETE KIT ONLY £196.90 + VAT


MPA 200 100 WATT (rms into 8-) MIXER / AMPLIFIER

COMPLETE KIT ONLY £49.90 + VAT

Featured as a constructional article in ETI, the MPA 200 is an exceptionally low priced — but professionally finished — general purpose high power amplifier. It features adaptable input mixer which accepts a wider range of sources such as microphone, guitar, etc. There are wide range tone controls and a master volume control. Mechanically the MPA 200 is simplicity itself with minimal wiring needed making construction very straightforward.

The kit includes fully finished metalwork, fibreglass PCBs, controls, wire etc. — complete down to the last nut and bolt.

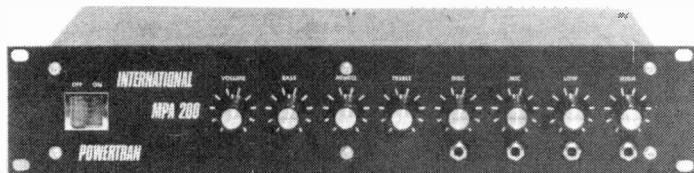MATCHES THE CHROMATHEQUE 5000 LIGHTING EFFECTS SYSTEM PERFECTLY!



DE LUXE EASY TO BUILD LINSLEY HOOD 75W STEREO AMPLIFIER £99.30 + VAT


This easy to build version of our world-wide acclaimed 75W amplifier kit based upon circuit boards interconnected with gold plated contacts resulting in minimal wiring and construction delightfully straightforward. The design was published in H-Fi News and Record Review and features include rumble filter, variable scratch filter, versatile tone controls and tape monitoring whilst distortion is less than 0.01%.

WIRELESS WORLD FM TUNER £70.20 + VAT

A pre-aligned front-end module makes this Wireless World published design very simple to construct and adjust without special instruments. Features include an excellent a.m. rejection push-button station selection as well as infinitely variable tuning and a phase locked loop stereo decoder, incorporating active filters for "birdy" suppression.

LINSLEY-HOOD CASSETTE DECK £79.60 + VAT

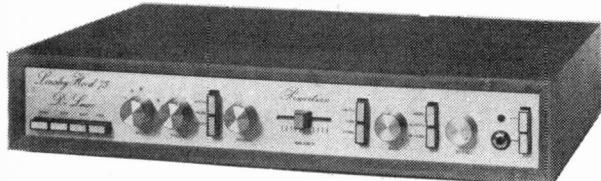This design, published in Wireless World, although straightforward and relatively low cost provides a very high standard of performance. There are separate record and replay amplifiers and switchable equalisation together with a choice of bias levels are also provided. The mechanism is the Goldring-Lenco CRV with electronic speed control.



T20+20 20W STEREO AMPLIFIER £33.10 + VAT

This kit, based upon a design published in Practical Wireless, uses a single printed circuit board and offers at very low cost, ease of construction and all the normal facilities found on quality amplifiers. A 30 watt version of this kit (T30+30) is also available for £38.40 + VAT.

MATCHING TUNERS — SEE OUR FREE CATALOGUE!

COMPLETE KITS: Our complete kits really are complete. All of the projects shown on this page are supplied with fully finished metalwork, ready assembled high quality teak veneer cabinet (last 4 kits on this page), or professional quality rack mounting cabinet (first 2 kits on this page), cables, nuts, bolts, etc., and full instructions — in fact everything!

All of the kits shown on this page are available as separate packs for those customers who wish to spread their purchase or perhaps make their own cabinets or metalwork. Prices are given in our FREE CATALOGUE.

PRICE STABILITY: Order with confidence. Irrespective of any price changes we will honour all prices in this advertisement until September 20th, 1979, if this month's advertisement is mentioned with your order. Errors and VAT rate changes excluded.

EXPORT ORDERS: No VAT. Postage charged at actual cost plus 50p handling and documentation.

U.K. ORDERS: Subject to 12½% surcharge for VAT (i.e. add ½ to the price). No charge is made for carriage, or at current rate if changed.

SECURICOR DELIVERY: For this optional service (U.K. mainland only) add £2.50 (VAT inclusive) per kit.

SALES COUNTER: If you prefer to collect kit from the factory, call at Sales Counter (at rear of factory). Open 9 a.m.-4.30 p.m. Monday-Thursday.




OUR CATALOGUE IS FREE! WRITE OR PHONE NOW!

POWERTRAN ELECTRONICS

PORTWAY INDUSTRIAL ESTATE
ANDOVER, HANTS SP10 3NM

ANDOVER
(STD 0264) 64455

.....news digest.....

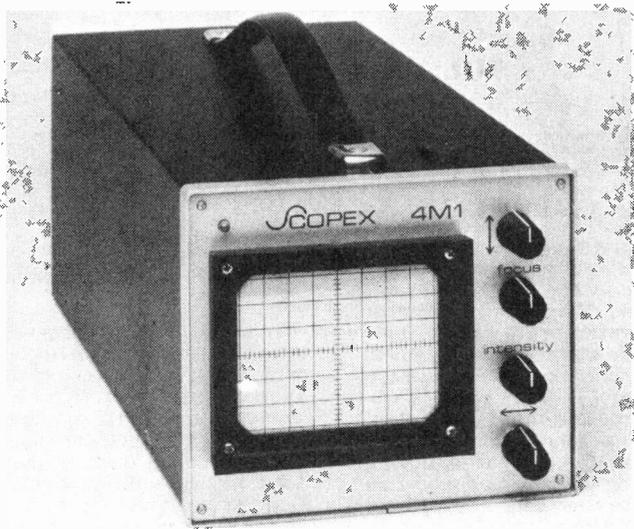

MONITORING SCOPEX

Scopex have announced the introduction of their first purpose-built monitor, the 4MI.

At £175 plus VAT, Scopex claim that the 4MI is probably less than a quarter of the price of its nearest competitor.


Introduced as a result of market demands, the 4MI has been designed to meet the diverse requirements of the OEM market for an XYZ display unit with a high degree of built-in versatility.

The matched vertical and

horizontal systems both have a sensitivity of 100mV/cm (internal preset permits adjustment of $\pm 10\%$) over a bandwidth of DC 1MHz (-3dB) with an accuracy of $\pm 3\%$ (of the preset sensitivity).

The vertical and horizontal shift controls use plug-in spindle potentiometers so that either front panel or internal preset operation may be selected.

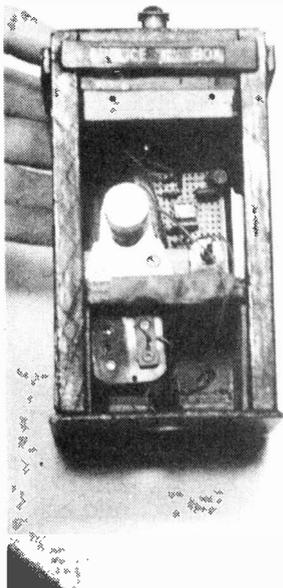For further details of the 4MI, contact Scopex Sales, Pixmore Avenue, Letchworth, Hertfordshire SG6 1JJ.



Be prepared to have your illusions shattered. ETI does it again. (Who said 'Publish and be damned'?) Yes, folks, it's true — Tom Baker is really a three inch tall midget. For the first time we show you the real TARDIS, packed with its electronic marvels (a genuine 555 Police Box flasher, time travellers for the use of).

JUST ARRIVED

Following on the heels of the film 'Battlestar Galactica' is 'Mattel Electronics' hand held 'Space Alert' game.


Your object is to intercept as many of the Cylon raiders as possible. The further away from your Battlestar you blast them, the more points you score. The game naturally features launch, impact, win and lose sound effects.

What's that? You don't know what a Cylon raider is. You are

sentenced to one evening at the nearest cinema showing Battlestar Galactica.

Also from Mattel and new to the UK is Auto Race. You have to successfully complete four laps of the circuit in the shortest possible time, steering round obstacles at four speeds from slow to just-a-blur. Full sound effects are featured.

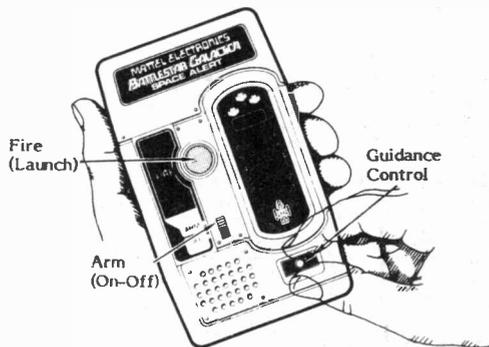The games are available at £15.90 each from N.I.C. Models, 27 Sidney Road, London N22 4LT, who will shortly be adding a soccer game to their range. It is expected to sell at £21.30.



POLYPHONIC KEYBOARD

We made a few errors in this article last month. To start with we credited the design to Tim Orr, when in fact Tony Keene of Arak should have received the accolades.

In addition to this we missed out the Buylines, which contained the details of the all-important designs kit from Arak Sound. Our apologies to them for our omission. For the missing details please consult the Arak ad on page 97 of this issue.

COURSE REGISTER

New from NCR, yes the cash register people, is their 'Basic Electronics Course With Experiments'. The 430 page paperback is a self-study course in both electronics theory and practical application.

The book is intended for use with an equipment kit including something called an op amp designer and, unfortunately, an oscilloscope. Unfortunately, because the sort of person likely to want to use this book is just the person who will not have a scope and probably doesn't know where to borrow one.

Although a scope is

necessary for some experiments, it is possible to cover most of the work without one. Arm yourself with the necessary components, a breadboard, a multimeter and if you can lay your hands on one, a function generator and you're away.

The book is a useful introduction to basic electronics with sections and written tests covering everything from simple atomic structure to transistor amplifiers. Don't cheat by looking up the answers.

The NCR Basic Electronics Course With Experiments costs £6.95.

news digest

PCB EYE POSTS


You can use Vero Electronics' miniature terminal assemblies to attach scope probes to PCBs, or use them as input/output stations.

The unique spring design allows the terminals to be inserted into plated through boards without damage to the hole plating. The terminals will remain in place when the board

is reversed for flow soldering.

Components can be fixed and replaced using the eye at the top of the terminal. The sintered glass bead has a recommended working temperature of 475°C and the terminals have a solder tinned finish.

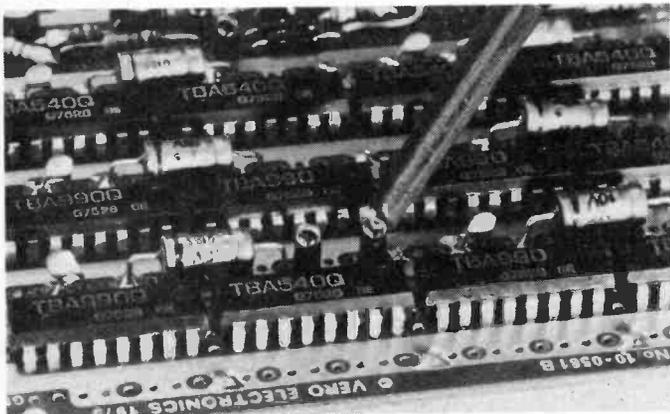For further details of the miniature terminal assemblies, contact Vero Electronics Ltd, Industrial Estate, Chandler's Ford, Eastleigh, Hampshire SO5 3ZR.



SILICON BOATS

No, not the messing-about-on-the-river type. These boats, new to the UK and Europe, could help semiconductor manufacturers boost their yields of the latest complex, high component density silicon chips.

Production of the latest generation of semiconductors demands critical handling during diffusion and oxidation processes. The new silicon boats, already in use in America, have several advantages over the conventional quartz boats. These include purity of the metal, four times that of quartz, and the lifetime of silicon, at least ten times that of quartz.

In addition, silicon boats will not devitrify, creating particles which can fuse into oxides causing yield losses. They can also be cleaned in HF solutions without degradation and minimum slot enlargement. As they have the same thermal coefficient of expansion as the slices they carry, warpage problems are eliminated. Rigidity is maintained up to 1400°C.


For further information contact Micro-Image Technology (Engineering) Ltd, Greenhill Industrial Estate, Riddings, Derby DE55 4DA.

WE'VE MOVED!

OXFORD ST

145 Charing Cross Road,
London WC2H 0EE.

Tel: 01-437 1002

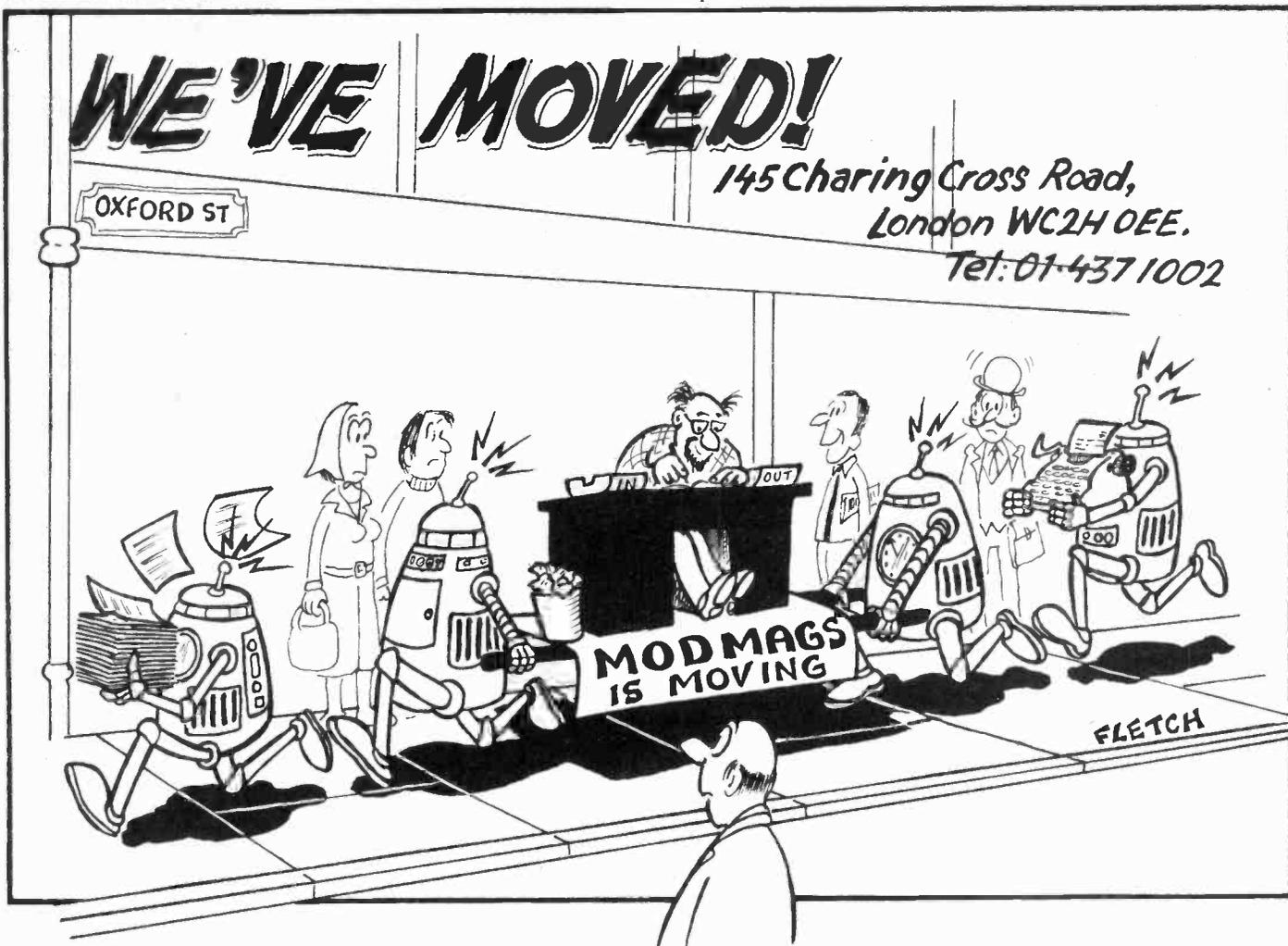

Measure Resistance to 0.01Ω ... At a Price that has no resistance at all


New **ELENCO PRECISION** Digital Multimeter M1200B
USA

ONLY £55 (+£3 p&p + VAT £4.64 = £62.64)

***FULLY GUARANTEED
FOR 2 YEARS**

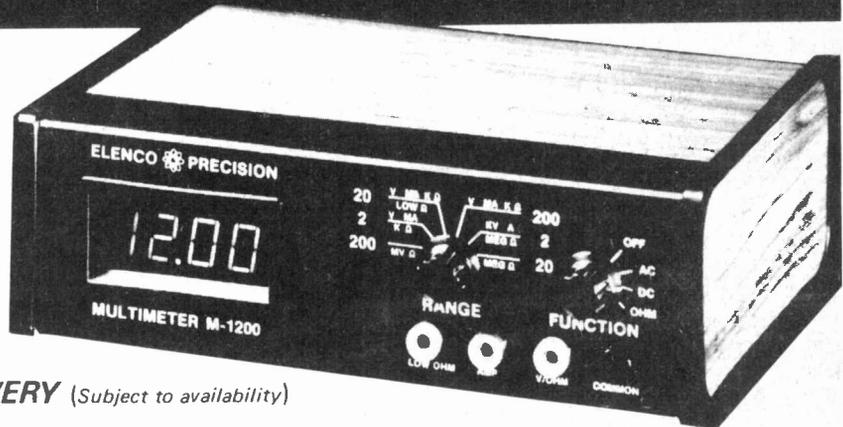***METAL CASE**

***EX STOCK DELIVERY** (Subject to availability)



THE ULTIMATE IN PERFORMANCE - MEASURES RESISTANCE TO 0.01 OHMS, VOLTAGE TO 100 MICROVOLTS, CURRENT TO 1 MICROAMPS AT LOWEST EVER PRICE!

FEATURES

- 3½ digits 0.56" high LED for easy reading
- 100μV, 1μA, 0.01Ω resolution
- High input impedance 10 Megohm
- High accuracy achieved with precision resistors, not unstable trimpots
- Input overload protected to 1000V (except 200mV scale to 600V)
- Auto zeroing, autopolarity
- Mains (with adaptors not supplied) or battery operation-built-in charging circuitry for NiCads
- Overrange indication
- Hi Low power ohms, Lo for resistors in circuit, Hi for diodes

SPECIFICATIONS:

DC Volts	Range 200mV, 2V, 20V, 200V, 1000V Accuracy 1% ± 1 digit, Resolution .1mV Overload protection 1,000 volts max
AC Volts	Range 200mV, 2V, 20V, 200V, 1000V (Response 45Hz to 5KHz) Accuracy 1.5% ± 2 digits, Resolution .1mV Overload protection 1000V max, 200mV scale 600V
DC Current	Range 2mA, 20mA, 200mA, 2amp. Accuracy 1% ± 1 digit, Resolution 1 Microamp Overload protection -- 2 amp fuse and diodes
AC Current	Range 2mA, 20mA, 200mA, 2 amp Accuracy 1.5% ± 2 digits, Resolution 1 Microamp Overload protection -- 2 amp fuse and diodes
Resistance	Range 20, 200, 2K, 200K, 2 Meg. 20 Meg. Accuracy 1% ± 1 digit, Resolution .01 ohms
Environmental	Temp coefficient 0° to 30° C ± .025%°C Operating Temp 0° to 50° C Storage - 20° to 60° C
General	Mains adaptor: 6 - 9 Volts @ 200mA (not supplied) 4C size batteries (not supplied) Size 8¼ x 5¼ x 2¼ Weight 2½ lbs.

At £55, M1200B is the best buy among DMM's currently available. Its 0.01 ohms resolution allows you to detect shorted windings in coils, transformers or motors. It is also useful in checking low contact resistance in switches, relays or connectors. Poor solder connections can also be spotted. The low power ohms function permits accurate measurements of in circuit resistance without forward biasing semiconductor junctions.

You have been waiting a long time for a digital multimeter with all these features at a price like this. Now its yours.

Also available from retail shops:

Audio Electronics, 301 Edgware Rd, London W2
Z & I Aero Services, 85 Tottenham Court Road
London W.1

***AGENTS WANTED**

ELENCO PRECISION Sole UK Distributor

ME

Maclin-Zand Electronics Ltd
38 Mount Pleasant, London WC1XOAP
Tel. 01-837 1165 or Hemel Hempstead
(0442) 832 966
Telex. 8953084

To: Maclin-Zand Electronics Ltd ET18
1st Floor, Unit 10, East Block
38 Mount Pleasant, London WC1X OAP

Please send me _____ DMM M1200B
@ £62.64 inc. p & p + VAT (overseas £60).

I enclose cheque/P.O./Bank Draft for £ _____

Name _____ (BLOCK

Address _____ LETTERS

PLEASE)

WATFORD ELECTRONICS

33/35 CARDIFF ROAD, WATFORD, HERTS, ENGLAND
MAIL ORDER, CALLERS WELCOME.
Tel. Watford 40588/9.

ALL DEVICES BRAND NEW, FULL SPEC. AND FULLY GUARANTEED. ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/P.O. OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS' OFFICIAL ORDERS ACCEPTED. TRADE AND EXPORT INQUIRY WELCOME. P&P ADD 30p* TO ALL ORDERS UNDER £10. OVERSEAS ORDERS POSTAGE AT COST. AIR/SURFACE.

VAT Export orders no VAT. Applicable to U.K. Customers only. Unless stated otherwise, all prices are exclusive of VAT. Please add 15% to all prices.

We stock thousands more items. It pays to visit us. We are situated behind Watford Football Ground, Nearest Underground/BR Station: Watford High Street. Open Monday to Saturday. Ample Free Car Parking space available.

POLYESTER CAPACITORS: Axial lead type. (Values are in μ F).
400V: 0.001, 0.0015, 0.0022, 0.0033, 0.0047, 0.0068, 0.01, 0.015, 0.02, 0.018 10p; 0.022, 0.033, 0.11, 0.22, 0.068 14p; 0.1, 17p; 0.15, 0.22, 24p; 0.33, 0.47 42p; 0.68 53p, 1.1F 17p.
160V: 0.039, 0.15, 0.22 11p; 0.33, 0.47 19p; 0.68, 1.0 22p; 1.5 29p; 2.2 32p; 4.7 48p.
DUBLIER: 1000V: 0.01, 0.015 20p; 0.022 22p; 0.047 26p; 0.1 36p; 0.2 44p.

POLYESTER RADIAL LEAD (Values in μ F): 250V.
0.01, 0.015, 0.022, 0.027 5p; 0.033, 0.047, 0.068, 0.1 7p; 0.15 11p; 0.22, 0.33 13p; 0.47 17p; 0.68 19p; 1.0 22p; 1.5 30p; 2.2 34p.

ELECTROLYTIC CAPACITORS: Axial lead type (Values are in μ F).
500V: 10, 40p; 47 68p; 250V: 100, 65p; 83V: 0.47, 1.0, 1.5, 2.2, 3.3, 4.7, 6.8, 8, 10, 15, 22, 25p; 47, 32, 11p; 63, 100, 27p; 50V: 50, 100, 220, 25p; 47, 32, 100, 50p; 22, 33, 8p; 100, 12p; 2200, 3300, 88p; 4700, 85p; 35V: 10, 33, 7p; 33, 47, 32p; 1000, 50p; 25V: 10, 22, 47, 8p; 80, 100, 160, 8p; 220, 250, 33p; 470, 640, 26p; 1000, 27p; 1500, 30p; 2200, 45p; 3300, 62p; 4700 74p; 10V: 10, 47, 68, 7p; 100, 125, 8p; 220, 330, 14p; 470, 18p; 1000, 1500, 20p; 2200, 34p; 10V: 100, 8p; 640, 12p; 1000, 14p.

TANTALUM LEAD CAPACITORS
35V: 0.1 μ F, 0.22, 0.33, 0.47, 0.68, 1.0, 2.2 μ F, 3.3, 4.7, 6.8, 25V: 1.0, 1.5, 2.2, 3.3, 4.7, 100, 220 40p.
10V: 15, 22, 25p; 47, 100, 220 40p.
10V: 15, 22, 30, 30p; 100, 35p.
6V: 47, 68, 100, 30p; 1V: 100, 20p.

MYLAR FILM CAPACITORS
100V: 0.001, 0.002, 0.005, 0.01 μ F 6p
0.015, 0.02, 0.04, 0.05, 0.056, 0.1 μ F 7p
0.1 μ F, 0.2, 0.22, 0.1 μ F, 50V: 0.47 μ F 12p
0.047 μ F 4p; 0.1 μ F 6p; 0.2 μ F 7p

CERAMIC CAPACITORS 50V
Range: 0.5pF to 10,000pF 3p
0.015 μ F, 0.022 μ F, 0.033 μ F 4p
0.047 μ F 4p; 0.1 μ F 6p; 0.2 μ F 7p

SILVER MICA (Values in pF): 3, 4.7, 6.8, 10, 12, 18, 22, 33, 47, 50, 68, 75, 82, 85, 100, 120, 150, 220, 330, 470, 500, 330, 330, 390, 470, 600, 800, 820, 1000, 1200, 1800, 2000, 20p each

POLYSTYRENE CAPACITORS
10pF to 1nF 8p; 1.5nF to 47nF 10p

MINIATURE TYPE TRIMMERS
2.5-50pF, 3-10pF, 10-40pF 22p
5-25pF, 5-45pF, 60pF, 88pF, 30p

COMPRESSION TRIMMERS
3-40pF, 10-80pF, 25-190pF 30p
100-500pF 46p; 1250pF 80p

GAS & SMOKE DETECTORS
TGS 812 & 813 415p; Socket 25p

JACKSONS VARIABLE CAPACITORS
Dielectric D 2 365pF with slow motion drive 140p
100/300pF 140p motion drive 325p
500pF 185p 00 208/176 285p
1/1 seal Drive 4511 DAF 115p motion drive 325p
Oval Drive 4183 31p motion drive 325p
6.1/36.1 660p; 25 50pF 175p
Drum 54mm 30p; 100 150pF 235p
0.1-365pF 245p L 3x310pF 495p
0.02 365pF 275p 00 3x250pF 485p

RF CHOKES
1 μ H 4.7, 10, 22, 33, 47, 100, 200, 470 75p, 1mH, 2.5, 5, 10 35p each
43mH 10 60p each

VERO BOARD (0.1 0.15 0.15 copper clad) (plain)
2 1/2 x 3 1/4" 45p 39p 24p
2 1/2 x 5" 55p 50p 31p
3 1/2 x 3 1/4" 55p 50p 31p
3 1/2 x 5" 62p 67p 43p
2 x 1 1/2" 169p 135p 92p
3 1/2 x 1 1/2" 218p 180p 120p
4 x 1 1/2" 283p 180p 120p
Pkt of 35 pins
Spot face cutter 22p
Pin insertion tool 120p

VERO WIRING PEN*
Plus Spool 32p
Spare spool (Wire) 80p; Combs 7p each

FERRIC CHLORIDE*
1lb bag Anhydrous 70p + 35p P&P

DALO ETCH RESIST PEN* + spare tip 7p

COPPER CLAD BOARDS
Fibre Single sided Double sided SRBP
Glass 8.5" x 8.5" 5" x 8.5" 8.5" x 12" 130p 175p 80p

EDGE CONNECTORS: .15" Spacing
2 x 10 way 85p; 2 x 15 way 99p; 2 x 18 way 120p; 2 x 22 way 135p; 2 x 25 way 160p.

DIL SOCKETS (TEXAS)
Low Wire Profile Wrap
8 pin 10p 25p 80 0.3W
14 pin 12p 35p 2 2 1/4" 68p
18 pin 13p 45p 2 5 1/2" 68p
20 pin 22p 55p 40Q 2.5" 68p
22 pin 25p 70p 64Q 2.5" 68p
24 pin 26p 73p 80 5" 175p
28 pin 39p 85p 7x4 5W 250p
40 pin 50p 109p 8 15W 480p

TRANSISTORS

AC107*	28	BC168C	12	BF177*	24	MPSA56	25	TIS44	45	2N2218A*	34
AC117*	35	BC169C	14	BF178*	20	MPSA57	24	TIS45	46	2N2219A*	22
AC125*	20	BC170	18	BF179*	20	MPSU02	58	TIS46	55	2N2220A*	28
AC126*	20	BC171	11	BF180*	11	MPSU05	60	TIS48	50	2N2222A*	20
AC127*	20	BC172	11	BF181*	36	MPSU06	50	TIS49	50	2N2230A*	46
AC128*	20	BC177*	18	BF182*	36	MPSU52	65	TIS50	47	2N2368*	21
AC141*	24	BC178*	17	BF183*	36	MPSU55	65	TIS54	47	2N2369A*	18
AC141A*	38	BC178*	18	BF184*	36	MPSU56	60	TIS90	20	2N2483*	28
AC142*	24	BC182	9	BF194	12	MPU131*	30	TC231	170	2N2484*	30
AC142K	38	BC183	9	BF195	12	OC23*	170	TC232	170	2N2485*	28
AC176*	24	BC194	9	BF196	12	OC25*	170	TC237	170	2N2486*	28
AC187*	24	BC182L	10	BF197	14	OC26*	170	TC238	170	2N2487*	28
AC188*	24	BC183L	10	BF198	18	OC28*	150	TC239	170	2N2488*	28
AC17*	40	BC184L	10	BF199	18	OC29*	150	TC240	170	2N2489*	28
AC18*	40	BC186*	30	BF200*	32	OC35*	130	TC241	170	2N2490*	28
AC19*	40	BC187*	28	BF224A	18	OC36*	130	TC242	170	2N2491*	28
AC20*	40	BC194	9	BF244B	30	OC41*	48	TC243	170	2N2492*	28
AC21*	40	BC212L	10	BF255*	60	OC42*	48	TC244	170	2N2493*	28
AC22*	40	BC223	10	BF256*	60	OC43*	65	TC245	170	2N2494*	28
AC27*	40	BC213L	11	BF257*	30	OC44*	31	TC246	170	2N2495*	28
AC28*	40	BC219	9	BF258*	30	OC45*	28	TC247	170	2N2496*	28
AC29*	38	BC214K	14	BF336	36	OC46*	28	TC248	170	2N2497*	28
AC34*	40	BC214L	10	BF394	27	OC70*	28	TC249	170	2N2498*	28
AD149	42	BC308	20	BF554	38	OC72*	48	TC250	170	2N2499*	28
AD162*	42	BC327	15	BF839	25	OC74*	45	TC251	170	2N2500*	28
AF106	50	BC328	15	BF840	25	OC75*	45	TC252	170	2N2501*	28
AF114*	50	BC338	12	BF841	28	OC76*	36	TC253	170	2N2502*	28
AF115*	50	BC441*	36	BF879	28	OC77*	78	TC254	170	2N2503*	28
AF116*	50	BC481*	36	BF880	28	OC78*	78	TC255	170	2N2504*	28
AF117*	50	BC482*	36	BF881	28	OC81D*	78	TC256	170	2N2505*	28
AF118*	55	BC547	12	BF898	108	OC82D*	80	TC257	170	2N2506*	28
AF121*	48	BC548	12	BF929	28	OC83*	48	TC258	170	2N2507*	28
AF124*	55	BC549C	13	BFX81*	46	OC84*	44	TC259	170	2N2508*	28
AF125*	55	BC557	15	BFX85*	28	OC122*	75	TC260	170	2N2509*	28
AF126*	50	BC558	20	BFX86*	28	OC123*	75	TC261	170	2N2510*	28
AF127*	35	BC559	20	BFX87*	28	OC139*	110	TC262	170	2N2511*	28
AF128*	35	BCY30*	57	BFX88*	28	OC140*	110	TC263	170	2N2512*	28
AF178*	75	BCY34*	85	BFX89*	28	OC141*	110	TC264	170	2N2513*	28
AF180*	70	BCY39*	80	BFY18*	50	OC170*	85	TC265	170	2N2514*	28
AF186*	50	BCY40*	78	BFY50*	20	OC171*	75	TC266	170	2N2515*	28
AF239*	48	BCY42*	48	BFY51*	20	OC200*	85	TC267	170	2N2516*	28
AF271	128	BCY43*	48	BFY52*	20	OC203*	85	TC268	170	2N2517*	28
AF292*	45	BCY58*	90	BFY53*	20	OC204*	85	TC269	170	2N2518*	28
AS27*	45	BCY59*	90	BFY54*	20	OC205*	85	TC270	170	2N2519*	28
AS28*	45	BCY70*	15	BFY55*	48	SJE055*	48	TC271	170	2N2520*	28
AS29*	65	BCY71*	20	BFY71*	20	TP29*	43	TC272	170	2N2521*	28
AS29*	65	BCY72*	20	BRV39*	28	TP29B	46	TC273	170	2N2522*	28
AS29*	65	BCY73*	20	BSX20*	18	TP29C	46	TC274	170	2N2523*	28
AS29*	65	BCY74*	20	BSX26*	78	TP30*	47	TC275	170	2N2524*	28
AS29*	65	BCY75*	20	BSX26*	78	TP30A	47	TC276	170	2N2525*	28
AS29*	65	BCY76*	20	BSX78*	55	TP30B	64	TC277	170	2N2526*	28
AS29*	65	BCY77*	20	BSY95A*	18	TP30C	64	TC278	170	2N2527*	28
AS29*	65	BCY78*	20	BU105*	140	TP31*	50	TC279	170	2N2528*	28
AS29*	65	BCY79*	20	BU205	190	TP31A*	50	TC280	170	2N2529*	28
AS29*	65	BCY80*	20	BU208	280	TP31B*	50	TC281	170	2N2530*	28
AS29*	65	BCY81*	20	BU308	280	TP31C*	50	TC282	170	2N2531*	28
AS29*	65	BCY82*	20	BU313*	43	TP31D*	50	TC283	170	2N2532*	28
AS29*	65	BCY83*	20	BU314*	43	TP31E*	50	TC284	170	2N2533*	28
AS29*	65	BCY84*	20	BU315*	43	TP31F*	50	TC285	170	2N2534*	28
AS29*	65	BCY85*	20	BU316*	43	TP31G*	50	TC286	170	2N2535*	28
AS29*	65	BCY86*	20	BU317*	43	TP31H*	50	TC287	170	2N2536*	28
AS29*	65	BCY87*	20	BU318*	43	TP31I*	50	TC288	170	2N2537*	28
AS29*	65	BCY88*	20	BU319*	43	TP31J*	50	TC289	170	2N2538*	28
AS29*	65	BCY89*	20	BU320*	43	TP31K*	50	TC290	170	2N2539*	28
AS29*	65	BCY90*	20	BU321*	43	TP31L*	50	TC291	170	2N2540*	28
AS29*	65	BCY91*	20	BU322*	43	TP31M*	50	TC292	170	2N2541*	28
AS29*	65	BCY92*	20	BU323*	43	TP31N*	50	TC293	170	2N2542*	28
AS29*	65	BCY93*	20	BU324*	43	TP31O*	50	TC294	170	2N2543*	28
AS29*	65	BCY94*	20	BU325*	43	TP31P*	50	TC295	170	2N2544*	28
AS29*	65	BCY95*	20	BU326*	43	TP31Q*	50	TC296	170	2N2545*	28
AS29*	65	BCY96*	20	BU327*	43	TP31R*	50	TC297	170	2N2546*	28
AS29*	65	BCY97*	20	BU328*	43	TP31S*	50	TC298	170	2N2547*	28
AS29*	65	BCY98*	20	BU329*	43	TP31T*	50	TC299	170	2N2548*	28
AS29*	65	BCY99*	20	BU330*	43	TP31U*	50	TC300	170	2N2549*	28
AS29*	65	BCY00*	20	BU331*	43	TP31V*	50	TC301	170	2N2550*	28
AS29*	65	BCY01*	20	BU332*	43	TP31W*	50	TC302	170	2N2551*	28
AS29*	65	BCY02*	2								

WATFORD ELECTRONICS

ILP MODULES 15-240 WATTS

We are now stockists for these world famous fully guaranteed (2 years guarantee on all modules) Pre amps, Amplifiers & Power Supplies.

- HY5** Preamplifier. Input, magnetic pickup 3mV, ceramic 30mV. Output: Mains 500mV RMS, Distortion 0.1% at 1KHz. **Price: £6.27**
- HY30** Amplifier Kit. 15 Watts into 8Ω, extremely easy to construct. Output 15W RMS, Distortion 0.1% at 15W Freq. 10Hz-16KHz. Supply ± 18V. **Price £6.27**
- HY50** Hi-Fi Amplifier Module. 25 Watts 8Ω. Input Sensitivity 500mV. Output 25W RMS. Distortion 0.04% at 25W. Freq. 10Hz-45KHz. Supply ± 25V. **Price: £8.18**
- HY120** Amplifier Module — 60 Watts 8Ω. Input sens. 500mV. Output 60W RMS. Distortion 0.04%. Freq. 10Hz-45KHz. Power Supply ± 35V. **Price: £18.98***
- HY200** Hi-Fi/Disco Amplifier Module — 120 Watts 8Ω. Input sens. 500mV 120W RMS. Freq. 10Hz-45KHz. Power Supply ± 45V. Size 114 x 100 x 85mm. **Price: £27.99***
- HY400** (Big Daddy) Amplifier Module — 240 Watts 4Ω. Ideal for High Power Disco or P.A. Output 240 Watts RMS 4Ω 114 x 100 x 85mm. Distortion 0.1%. **Price: £38.80***

JACK PLUGS		SOCKETS		SWITCHES*		SLIDE 250V:	
Screened chrome	Plastic body	open metal	moulded with break contacts	DPST	DPST	1A DPDT	1A DPDT c/over
2.5mm 13p	10p	8p	11p	DPST	DPST	1/2A DPDT	1/2A DPDT
3.5mm 15p	10p	8p	11p	DPST	DPST	4 pole 2-way	4 pole 2-way
MONO 25p	14p	13p	20p	4 pole on/off	4 pole on/off		
STEREO 32p	17p	15p	24p				

DIN		PLUGS		SOCKETS		IN LINE	
2 PIN Loudspeaker	10p	10p	7p	20p			
3, 4, 5 Audio	15p	15p	10p	20p			

DM900		TRANSFORMERS*		ALUM. BOXES*		PANEL METERS*	
3 1/2 DIGIT LCD	Multi-meter with Capacitance Meter	6.0-6V: 9.0-9V: 12.0-12V 100mA	8p	3x2x1"	48	35p	477p each
Complete Kit	£54.50* only (p&p 80p)	12V: 3A: 15V: 25A: 15V: 25A	18p	2x4x5 1/2"	68	85p	

CRYSTALS*		VOLTAGE REGULATORS		COMPUTER HARDWARE	
100KHz	385	1A TO3 +ve	220p	2102.2	170
455KHz	385	5V 7805	145p	21078	490
1MHz	323	12V 7812	145p	2111	195

ULTRASONIC TRANC-DUCERS		VDU Hardware	
LM300H	170p	74LS163	£1.02
LM305H	140p	74LS101	£8.20
LM309K	135p	AV-3-1013	£4.50

CMOS*		VDU Hardware	
4000	15	74LS163	£1.02
4001	15	74LS101	£8.20
4002	15	AV-3-1013	£4.50

ETI Projects:		VDU Hardware	
393	230	74LS163	£1.02
395	218	74LS101	£8.20
396	218	AV-3-1013	£4.50

..... news digest.....



HAM CRACKLING

If you're into amateur radio and constantly being blamed for every snap, crackle and pop of interference on neighbours' television sets, then the Radio Society of Great Britain have just done you a favour. They have published a 'Television Interference Manual', so that you can tackle the problem without blood pressure (yours or your neighbours) rising. Spurious-radiation and strong-signal interference are covered, as are problems in transmitter design which may cause interference. If you've spent a small fortune on your Hi-Fi and CW or SSB interference is making your life a misery, the chapter on audio breakthrough might interest your local radio ham. A useful data and reference section covers filter design.

The RSGB's Television Interference Manual by B. Priestley (80 pages) costs £1.35.

FALL-OUT BLEEPER

After the next world war, the High Street will probably be slightly more radioactive than it is now. Pocket radiation meters might be the 'in' fashion. With that in mind, no doubt, Andrex Radiation Products AS of Copenhagen have introduced a new version of their successful personal radiation monitor.

The new model is lighter and smaller than its predecessors, without any loss in performance.

The monitor remains on continuously, producing an intermittent reference beep to confirm operation and battery condition. The more radiation there is about, the faster the little box beeps. Sensitivity is from 1mR/h. Power is from a readily available 1.5 V battery lasting 3-6 months.

Weighing in at 80g, one of the lightest of these units on the market, it can be slipped into a pocket or clipped on to a belt. The monitor is aimed at personnel working in and around X-ray or isotope equipment or with on-site radiographic inspection gear.

The Andrex monitor will continue working even after exposure to extremely high and dangerous levels of radiation.

You can find out more about the Andrex pocket radiation monitor from its British suppliers, Andrex NDT Products (UK) Ltd, 12 Trafalgar Way, Bar Hill, Cambridge CB3 8SQ.

RC CHANGES

If you're thinking of building the radio control transmitter featured in our May issue, these component value changes will interest you.
R15,17 150k
C2,5,14 47n

.....news digest.....

BABANI DUO

Two new books from the Bernard Babani stable dropped through our letter box recently. The 'Beginners Guide to Digital Techniques' by G. T. Rubaroe covers everything from an introduction to the binary number system to applications such as digital computers and voltmeters.

As digital techniques spread into the hobby market, versatile and inexpensive digital

ICs are becoming available to the home constructor.

This compact paperback's 62 pages pack in chapters on number systems, codes, combinational and sequential logic, analogue to digital and digital to analogue conversion and finally applications.

Next from Bernard Babani we have the 'Second Book of CMOS IC Projects' by R. A. Penfold.

The publication of this second book of CMOS projects was prompted by the success of '50 CMOS IC Projects' by R. A. Penfold, published in 1977.

The second book provides a selection of useful, mostly simple, circuits, with the minimum of overlap between the two books.

In 122 pages, four chapters deal with CMOS basics, multivibrator projects, amplifier, trigger and gate projects and special devices.

The Beginners Guide to Digital Techniques is available for 95p and the Second Book of CMOS IC Projects for £1.50, both from Bernard Babani (publishing) Ltd.

SCOPE CUTS

Telequipment have announced price reductions for two of their oscilloscopes. (Don't they have inflation in Harpenden?)

The S61, a single beam 5 MHz general purpose instrument, is down to £156.

The D32, a battery/mains dual trace portable scope with a bandwidth of 10 MHz, is now selling at £406.

Both scopes are from Tektronix UK Ltd, Beaverton House, PO Box 69, Harpenden, Herts.


HOT SPOTS

These tiny, self-adhesive tabs from Carel Components could save your bacon (or your expensive ICs).

Only 1/8in square, the Levermore 'Temp-checker' temperature indicators change from silver to black within 1% of the rated temperature. Ratings range from 40°C to 260°C in 41 increments.

These hot spot indicators come, appropriately, in a book match pack. Six packs or more are supplied in an outer wallet.

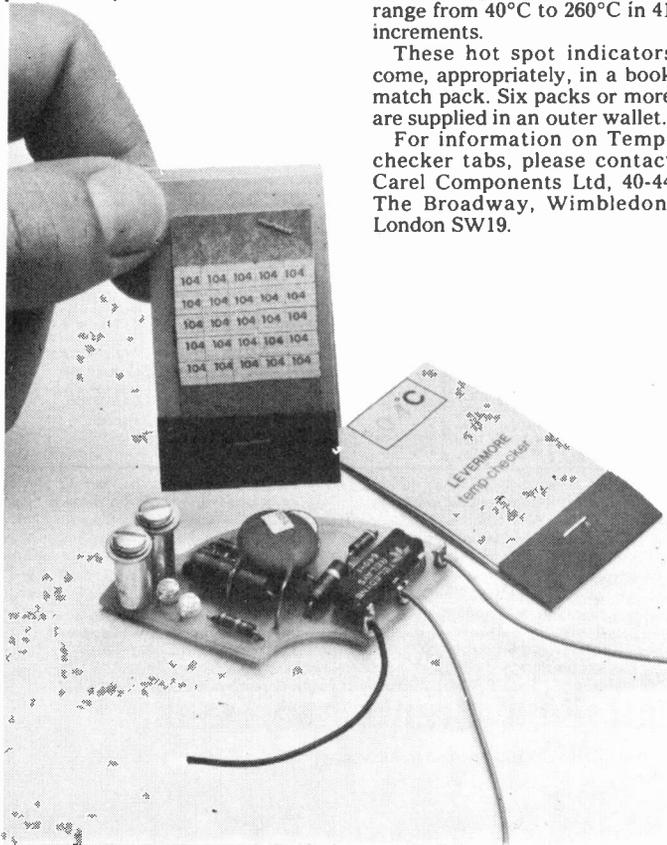For information on Temp-checker tabs, please contact Carel Components Ltd, 40-44 The Broadway, Wimbledon, London SW19.



VAT

INCREASE

As from June 18th the VAT rate is increased for all products to 15%.


Due to printing schedules most of the advertisements in this issue will carry prices based on the old rate of VAT.

Readers should take this into account when ordering from advertisers and it is advisable, if in doubt, to contact suppliers beforehand.

Tecknowledgedgey for sale

The Mark III FM Tuner

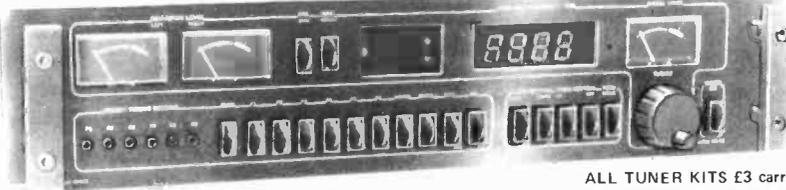DIY Hi-Fi will never seem the same again. Ambit's Mark III tuner system is electrically & visually superior to all others. Some options available, but the illustrated version with reference series modules: £149.00 + £18.62 VAT
With Hyperfi Series modules £185.00 + £23.12



Features of the system:

- * Precision construction & design of all parts
- * Time frequency display
- * State of the art performance with facilities for updates, using modular plug in systems.
- * Deviation level calibrator for recording
- * All usual tuner features

Digital Dorchester All Band Broadcast Tuner: LW/MW/SW/SW/SW/FM stereo

A multiband superhet tuner, constructed using a single IC for RF/IF processing - but with all features you would expect of designs of far greater complexity. The FM section uses a three section (air gang) tuned FET tunerhead, with ceramic IF filters and interstation mute; AM employs a double balanced mixer input stage, with mechanical IF filters - plus a BFO and MOSFET product detector for CW/SWB reception. Styled in a matching unit to the Mark III FM only tuner, employing the same degree of care in mechanical design to enable easy construction. MW/LW reception via a ferrite rod antenna.

Electronics only (PCB and all components thereon) £33.00 + £4.12 VAT
Complete with digital frequency readout/clock timer hardware £99.00 + £12.32 VAT
Complete with MA1023 clock/timer module with dial scale £66.00 + £8.25 VAT

Hardware packages are available separately if you wish to house your own designs in a professional case structure. Please deduct the cost of electronics from complete prices.

LW/MW/FM LCD Digital Frequency Display - July PW feature

Update your old radio, or build this into a new design. Or use it as a servicing aid - this low power unit with LCD display reads direct frequency in kHz/MHz, or with usual AM/FM IF offsets for received frequency. Low power LCD means no RF! - 15-20mA at 9v even with the divide by 100 prescaler. FM resolution is 100kHz, AM 1kHz. Sensitivities better than 10mV
Complete kit £19.50 + *£1.56 VAT. Built and tested version £24.00 + *£1.92 VAT
Various other DFM systems described in our catalogue part 2 - including a one chip solution to providing digital display of FRG7 kHz dial, combined with clock/timers etc.



PW SANDBANKS PI METAL LOCATOR

Maintaining our professional approach to home constructor kits, we offer the pulse induction 'Sandbanks'. Now with injection molded casing for greatly improved environmental sealing. £37.00 + *£2.96vat.

VHF MONITOR RX WITH PLESSEY IC 4/9

channel version of the PW design - but using standard 3rd OT crystals, and TOYO 8 pole crystal filter with matching transformers. Coil sets from our standard range to cover bands from 40 to 200MHz. Complete module kit £31.25 + *£3.90vat.

ETI - REMCON RADIO CONTROL

A tried and tested RC system with a full set of supporting hardware from a well known manufacturer. Please send for details - and watch our ads for further news of developments in RC products.

Radio and Audio Modules: The biggest range/ best specs:

EF5801/3/4 6 stage varicap tunerheads with LO feed and various levels of sophistication. New 5804 include pin AGC loop 'on board'. 5801: £17.45 + £2.18vat - 5803: £19.75 + £2.47vat - 5804: £24.95 + £3.18vat. Frequencies in 40-180MHz on approx.

EF5402 4 stage varicap with TDA1062, compound FET/Bipolar input stage, low noise, balanced mixer, pin agc, osc output. A worthy successor to the 5400. £10.75 + £1.34vat

The 5402 is available centred on a wide range of frequencies from 30MHz to 180MHz. Non standard units £14.75 + £1.84 - 3 weeks. 8319 4 stage varicap tunerhead from Larsholt using MOSFET

RF and mixer stages. New temperature compensated oscillator for wide ranges of ambient temperature £13.45 + £1.68vat

7252 Complete Larsholt FM tuner less stereo decoder. £26.50 + £3.31vat

7253 Stereo FM tuner set from Larsholt with FET head. (as 7252)

944378 Hyperfi stereo decoder. The very best. £19.95 + £2.19vat

911223 Pilot cancel stereo decoder, priced to make the MC1310 as obsolete as it now deserves to be. £12.50 + £1.56vat

Inotec 1-A fully DC tuned and switched LW/MW/FM stereo tuner to interface with synthesiser control etc. A first! Details OA.

COMPONENTS for Radio and Audio ICs, HMOS etc.

The list is too long to attempt here, but AMBIT specializes in all types of semiconductor for radio reception, including devices operating from DC to 5GHz. New low cost SBL1 diode ring mixers (equiv case MD108 etc) - first with HMOS fets, now with a PCB for DC amplifier, and offset sense and protection relay for speakers. See catalogue and updates for most info, please send an SAE for information on anything you cannot find in catalogues.

Radio ICs	cost + vat	Stereo ICs	cost + vat	AF power ICs	cost + vat
CA3089E	1.94 24	MC1310P	1.50 19	LM380N	1.00 12
CA3189E	2.45 30	uA758	2.20 27	TBA810AS	1.09 14
HA1137W	2.20 27	CA3090A	2.75 34	TDA2002	1.95 24
SN76660	0.75 9	HA1196	3.95 49	TBA820M	0.75 9
TDA1090	3.35 42	HA11223	4.35 54		
TDA1083	1.95 24	KB4437	4.35 54	LEDs: all colours and low prices	
TDA1220	1.40 17	KB2224	2.75 34		
SL6640	2.75 34			Preamp ICs/switches	2S/J48/25K134 HMOS
MC3357	3.12 39	TDA1028	3.50 44		9.90 + £0.80 vat (Pair)
HA1197W	1.40 17	TDA1029	3.50 44		Signal fets/transistors and TOKO COILS & FILTERS!
MC1496	1.25 16	TDA1074	4.14 52		
LM373/4	3.75 49	KB4438	2.22 28		

OSTS: Remember all OSTS stocks are obtained from BS9000 approved sources - your assurance that all devices are very best first quality commercial types. Some LPSN

TTL is presently in great demand, so please check by phone before ordering.

TTL: Standard AND LP Schottky

N'	LSN'	N'	LSN'	N'	LSN'	N'	LSN'	N'	LSN'	
7400	13	20	7455	35	24	74126	57	44	74185	134
7401	13	20	7460	17		74128	74		74188	275
7402	14	20	7463		124	74132	73	78	74190	115
7403	14	20	7470	28		74133	29	74191		
7404	14	24	7472	28		74136	40	74192	105	
7405	18	26	7473	32	38	74138	60	74193	105	
7406	38		7474	27	38	74139	60	74194	105	
7407	38		7475	38	40	74141	56	74195	95	
7408	17	24	7476	37	38	74142	265	74196	99	
7409	17	24	7478		38	74143	312	74197	85	
7410	15	24	7480	48		74144	312	74198	150	
7411	20	24	7481	86		74145	65	74199	160	
7412	17		7482	69		74147	175	74247	90	
7413	30		7483A		110	74148	109	74248	90	
7414	51		7484	97		74150	99	74249	93	
7415	30	24	7485	104	99	74151	64	74251	90	
7416	30		7486		90	74153	64	74253	105	
7417	30		7489	205	40	74154	96	74257	108	
7420	16	24	7490	33	90	74155	54	74258	153	
7421	29	24	7491	76	110	74156	80	74259	420	
7422	24	24	7492	38	78	74157	67	74260	153	
7423	27		7493	32	99	74158	60	74261	353	
7425	27		7494	78		74159	210	74266	40	
7426	36	27	7495A	65	99	74160	82	74273	124	
7427	27	29	7496	58	120	74161	92	74275	78	
7428	35	32	7497	186		74162	92	74279	312	
7430	17	24	74100	119		74163	92	74279	52	
7432	25	24	74104	63		74164	104	74283	120	
7433	40	32	74105	62		74165	105	74290	90	
7437	40	24	74107	32	38	74166		74293	95	
7438	33	24	74109	63	38	74167	20	74298	120	
7440	17	24	74110	54	54	74168		74324	157	
7441	74		74111	68		74169		74325	242	
7442	70	99	74112		38	74170	230	74326	247	
7443	115		74113		38	74172	675	74327	237	
7444	112		74114		38	74173	170	74327	237	
7445	94		74116	198		74174	87	74352	100	
7446	94		74118	83		74175	87	74353	100	
7447	82	89	74119	119		74176	75	74362	115	
7448	56	99	74120	115		74177	78	74366	49	
7449	18	99	74121	25		74180	85	74367	43	
7450	17		74122	46	57	74181	165	74368	49	
7451	17	24	74123	48	73	74182	160	74373	77	
7453	17		74124	13	137	74183		74374	77	
7454	17	24	74125	38	44	74184	135	74375	60	

CD4000 CMOS

4000	17p	4059	563p	4522	149p
4001	17p	4060	115p	4527	157p
4002	17p	4063	109p	4528	102p
4006	109p	4066	53p	4529	141p
4007	18p	4067	400p	4530	90p
4008	80p	4068	25p	4531	141p
4009	58p	4069	20p	4532	125p
4010	58p	4070	20p	4534	614p
4011	17p	4071	20p	4536	380p
4012	17p	4072	20p	4538	150p
4013	55p	4073	20p	4539	110p
4014	95p	4074	20p	4541	141p
4016	52p	4075	20p	4543	141p
4017	80p	4076	90p	4549	399p
4018	80p	4077	20p	4554	153p
4019	60p	4078	20p	4557	77p
4020	93p	4081	20p	4558	389p
4021	82p	4082	20p	4558	82p
4022	90p	4085	82p	4558	389p
4023	17p	4086	82p	4558	389p
4024	76p	4089	150p	4559	388p
4025	17p	4093	50p	4560	218p
4026	180p	4094	190p	4561	65p
4027	55p	4096	106p	4562	530p
4028	72p	4097	372p	4566	159p
4029	100p	4098	110p	4568	281p
4030	58p	4099	122p	4569	303p
4031	250p	4160	90p	4572	25p
4032	100p	4161	90p	4581	600p
4033	145p	4162	90p	4581	319p
4034	200p	4163	90p	4582	164p
4035	120p	4174	104p	4583	84p
4036	250p	4175	95p	4584	63p
4037	100p	4194	95p	4585	100p
4038	105p	4501	23p		
4039	250p	4502	91p		
4040	83p	4503	69p		
4041	90p	4504	51p		
4042	85p	4507	55p		
4043	85p	4508	248p		
4044	80p	4510	99p		
4045	150p	4511	149p		
4046	130p	4512	98p		
4047	99p	4513	206p		
4048	60p	4514	260p		
4049	65p	4515	300p		
4051	65p	4516	125p		
4052	65p	4518	103p		
4053	65p	4519	57p		
4054	120p	4520	109p		
4055	135p	4521	236p		

IMPORTANT: ALL OSTS PRICES EXCLUDE VAT - CURRENTLY 8% - BUT MAY BE CHANGED BY THE TIME YOU READ THIS. PLEASE REMEMBER TO ADD VAT, AND 25p POSTAGE !!

VOLTAGE / PSU REGULATORS

7800 series 95p
7900 series £1
78M series 90p
(TD220 pack)
78LCP series 35p
78MG2C 175p
79MG2C 175p
723C 65p
NE550A 73p
95L 195p

MAINS FILTERS

100 Amp IEC 4.83
157 6Amp IEC 5.83
242 5A wirew 3.87
247 All BS approved

Requests for the next issue of the catalogue now being 'booked' for despatch immediately
43 it is ready (about 49 November). Please send 50p to reserve a copy. (Part 3)

Micromarket

6800 series	£216	1.95	2114	170
6800P	6.50	£224	3.50	2708
LR20P	FG	£228	4.78	
6850P	2.75	8251	6.25	MEK6800 £220
6810P	E4	8255	5.40	TK80 £306
6852	3.65			AM1 Signetics
8080 series		2102	£1.70	TI Internat.
8080	6.30	2112	£3.40	Harris etc. OA
8212	2.30	4027	£5.78	

MISC. LSI/Scalars/DVMs

NE555	30p	NE556	78p	NE558	180p
LM3909	72p	95F901C	320MHz	7.80p	
ICM7216BPI	8 decade	10MHz	OFM/timer with direct LEO drive and all counter features	£19.82	
ICM7217AIB1	4 decade	programmable	cntr	£9.50	
ICM7207	clock pulse generator	IC		£4.95	
ICM7208	7 decade counter/display	IC		£4.95	
ICM7106CP	LCD DVM IC (3 1/2 digit)			£9.55	
ICM7107CP	LED DVM IC			£24.80	
ICM7107CP	LED DVM IC			£9.55	
ICM7107CP	LED DVM IC			£20.65	
SP8629	divided by 100	200MHz	scalar	£4.20	
MSL2318	divide by 100	to 175MHz	mm		
	divide by 10	to 45MHz	mm	£4.20	

PLEASE REMEMBER TO ADD 8% VAT TO ITEMS LISTED UNDER OSTs

Hobby Electronics

Next
Month

SATELLITE POWER


Have you ever considered what a wasteful object the Sun is. All that energy going to waste when we're so short of it here on earth. This feature investigates the research that's currently being carried out into using orbital power stations to provide for our future needs.

TOOLS



Back to basics. If you are still considering starting out into electronics for your hobby then do not miss this feature on tools, what to look for and what to avoid.

COMPETITION

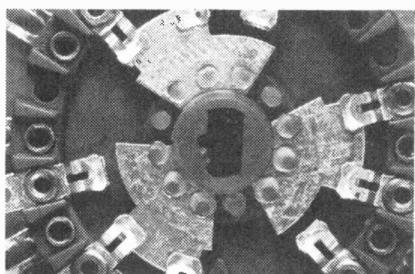

It's about time we had a competition, so keep an eye open for this one it's a real humdinger.

INJECTOR/TRACER


Another in our series of do-it-yourself test equipment. Anyone who has had to repair audio/radio equipment will testify to its usefulness. A very simple project taking only an hour or so to build but saving many hours of frustrating fault-finding.

HOME SECURITY UNIT




Well, we couldn't call this project a mere burglar alarm. It boasts a 'panic button', fire alarm option and as a further bonus it will drive either a mechanical bell or the electronic siren we're incorporating into the design.

VARIABLE RESISTORS

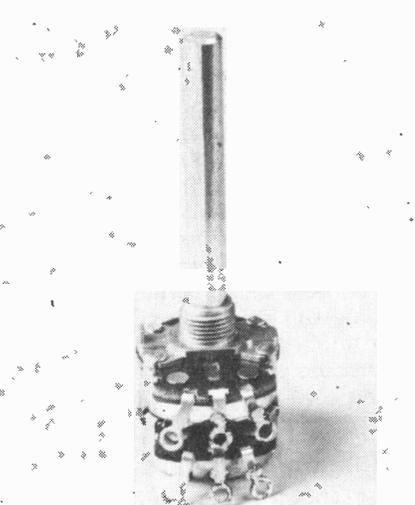

Concluding our short series on resistors. We take a look at all types of variable resistors, LDRs, VDRs, Thermistors and of course Potentiometers.

CONSTANT VOLUME AMPLIFIER

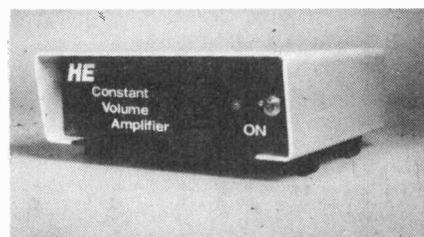

This natty little unit is primarily intended for tape-recorder, and audio enthusiasts in general. It will accept a wide range of inputs and will preserve the 'dynamic range' of your recordings.

LED TACHOMETER

We're quite proud of this project. It has a range of 0-10 000 RPM shown by the progressive illumination of 30 LEDs. (It won't cost as much as you think.) The circuitry is very advanced but not at the expense of cost or complexity, indeed it will still cost less than most commercial units.

CLEVER DICK

Next month we're trying out a little experiment. Judging from the response to our Technical Query service it seems like a good idea to have some sort of agony column. Our resident technical expert will attempt to answer any questions or problems that may arise from your hobby. Obviously it doesn't have to be specifically about articles in HE, (it would be nice though, we're not that clever). We won't be entering into any personal correspondence, we can't afford the stamps. So mark your letters 'Clever Dick's Problem Page', and we'll see what we can do. (We know it's a silly name, perhaps you can suggest a better one).

The August issue will be on sale July 13th

The items mentioned here are those planned but circumstances may affect the actual contents

ETI STRING THING

TRANSCENDENT DPX

This, the latest design from the Tim Orr stable, is a versatile digital polyphonic multi-voice keyboard instrument. Designed to have a minimum of wiring, it does not suffer from the signal breakthrough caused by the wiring jungles which some other instruments demand.

The machine features a touch sensitive (dynamic) keyboard action, and the keyboard can be 'split'. It is also polyphonic (chording) and has several voices. Included in the design is a CCD choraliser to give the machine a "several at once" facility.



The machine was designed to be a versatile keyboard instrument with a choice of several voices and characteristic waveform envelopes with a split keyboard and a dynamic option. Most string machines, organs or electric pianos usually involve a large amount of cables which can cause significant signal breakthrough and lots of wiring problems. With this in mind the machine was designed to have a bare minimum of wires, and even so, most of the resultant wiring is accomplished with manufactured 14 way ribbon cable connectors.

Layout

Ease of access is also very important and so the physical layout was given special attention. Merely by removing the lid and the base all the electronics become accessible. A multiplexed system was used, as this kept the wiring to a bare minimum and also enabled a relatively sophisticated dynamic and attack/sustain network to be employed. The note and envelope generation is contained on two

printed circuit boards using a conventional top octave generator and divider network. The envelope generators are programmable so that they will produce either a characteristic string/brass or a piano contour. Five audio outputs, one per octave are produced from these boards which are then routed to the tone control and voicing section. The filtered sound is then processed by the ensemble section which turns the relatively dull electronic signals into interesting 'natural sounding' signals by a process of complex phasing.


Multiplexed Keyboard

Multiplexing is a method of conveying several signals down one transmission line. The signals are time division multiplexed, that is each channel of information is sequentially transmitted down the line. The sequence is repeated rapidly so that, at the receiving end, the signal can be unscrambled (demultiplexed), and reconstituted so as to resemble the originally transmitted set of signals.

BUYLINES

Powertran Electronics are supplying a complete kit of parts for this project at £365+15% VAT. Delivery by Securicor is £2.50 extra. Everything is included in the kit, down to the last nut and bolt. They even give you a plug.

The keyboard has 61 notes and so a six bit binary code, which has a possible 64 decoded states, is used to address the multiplexer. In this way it is possible to interrogate each key on the keyboard, (this is done every millisecond) and to determine whether the key is released, pressed or in the process of being depressed. This generates a lot of information which tells us which keys are being pressed and by doing some timing, how hard they have been pressed. This information can then be used to control the volume of each note in proportion to the key velocity. The harder you play the note the louder it sounds. The advantage of using a multiplexing system is that all the information passes down one wire, so the wiring is relatively simple being one wire plus an address bus rather than 61 wires. It also enables the one piece of electronics to do all the dynamic computation for all the notes. Also, as only one dynamic circuit is involved, the note to note difference in dynamic performance should be greatly reduced and it is practical to use a relatively complex dynamic law.

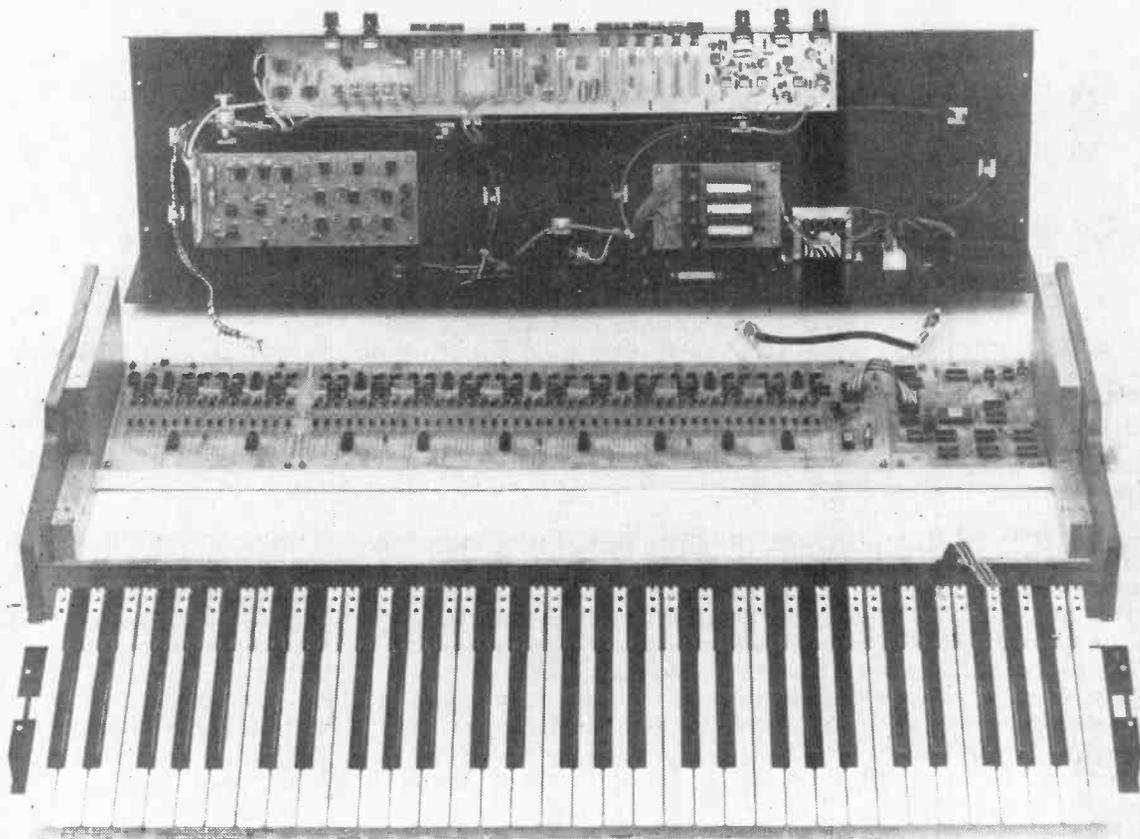

Playing Computers

As the key-pressed information is in a binary code it should be possible to interface the machine to a microprocessor system, such that a musical sequence can be memorised on say the lower two octaves and then replayed whilst you plan an accompaniment on the top three octaves.

The multiplexed signal, once it has passed through whatever processes have been selected, is then demultiplexed on the master note generating board. If, say, you press middle C on the keyboard, a voltage appears at the demultiplexer output that controls the middle C note, thus causing the note to be generated.


Keyboard Multiplexer

The job of the keyboard multiplexer is to look at every note on the keyboard once every millisecond and to convey this information to the dynamic and demultiplexing system. When a key is released it is connected to -5V, when it is pressed it is connected to +5V and when it is in the process of being depressed, (neither up or down), it is connected to 0V. Thus by examining the information from each key it is possible to determine what is happening on the keyboard; which notes are being played and those that


are not. Also, by timing the duration of the 0V period for each key, it is possible to determine the key velocity, (how hard the key was played), and to produce a signal whose volume is controlled by this. Loud notes have a timing of about 4 mS, whereas soft notes take 30 to 100 mS. The soft end of the range is very indeterminate and needs to be compressed.

Circuit Operation

A 6 bit code, generated by the dynamic network is used to address the keyboard multiplexer. This 6 bit code has a possible 2^6 (64) decoded outputs which is, therefore, sufficient to fully address the 61 notes of the keyboard. The scan time for the keyboard is approximately 1mS and so the time taken interrogating each note will be one sixty fourth of this, approximately 16 μ S per note. The multiplexer is made up out of 8 x 8 way multiplexers, the address inputs of which are driven by the three least significant bits of the 6 bit code. The three most significant bits are used to drive a BCD to decimal decoder, the lowest 8 outputs of which are used to sequentially enable the multiplexers. Thus the 6 bit code sequentially interrogates each of the 61 notes and sends the keyboard information (MPI) down to the dynamic network. ▶

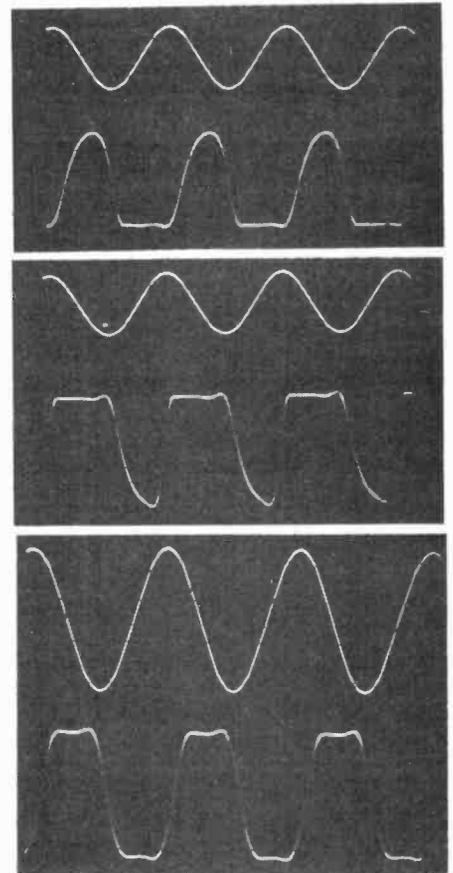

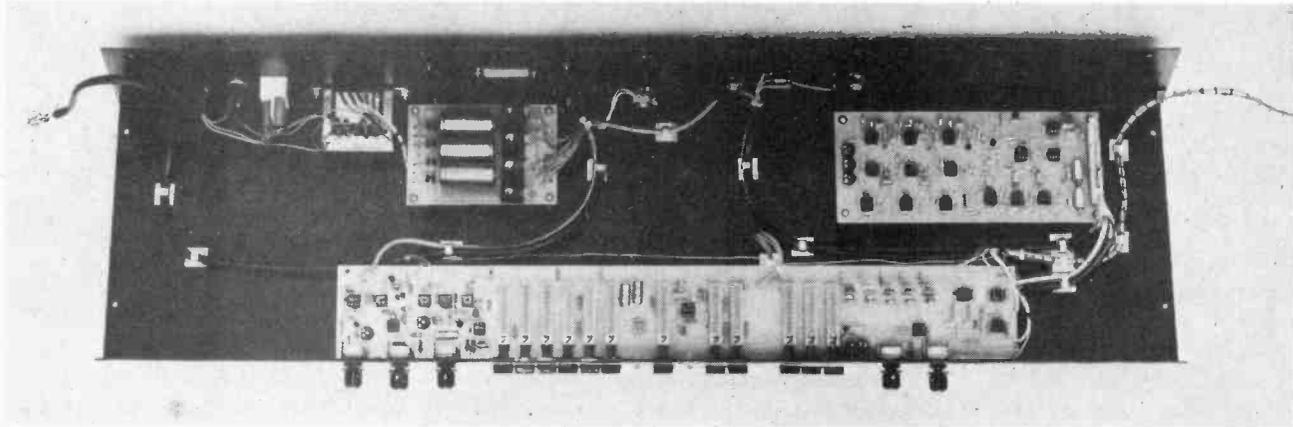Adjusting bias voltage on the delay lines (chorus board). In each case the top trace is the input signal. The lower trace indicates (a) bias too negative (b) bias too positive (c) correct bias, symmetrical clipping.



Power supply, voicing control panel and chorus board

Mechanical Construction

Assemble the two keyboard printed circuit boards with the exception of the key contacts.

Stick these two printed circuit boards onto the keyboard spacer and hold in position with some nuts and bolts whilst the glue dries. There should be a 0.1" gap separating the two boards. Next thread the bus bar lengths through the holes in the contact blocks. Make sure that these

bars are clean (give them a rub with a tissue), and try not to handle them as this will make them slightly greasy. Use gloves or tissues to hold them. Make certain that the gold plated wire of the contact block is in between the bus bars. Apply some glue to the bases of the contact blocks and position them onto the PCB, making sure that the bent ends of the wire pass through the holes provided. Line up the blocks and

then place a weight on them whilst the glue dries. Next solder in the board to board links, solder the bent ends of the contact blocks, solder together bus bar sections and wire them to +5 and -5V as shown in Fig. 4. Position the entire keyboard assembly onto the keyboard chassis such that it overhangs the punched holes by 0.2" (Fig. 5). Mark the fixing holes through the PCB with a pencil and drill them out with a


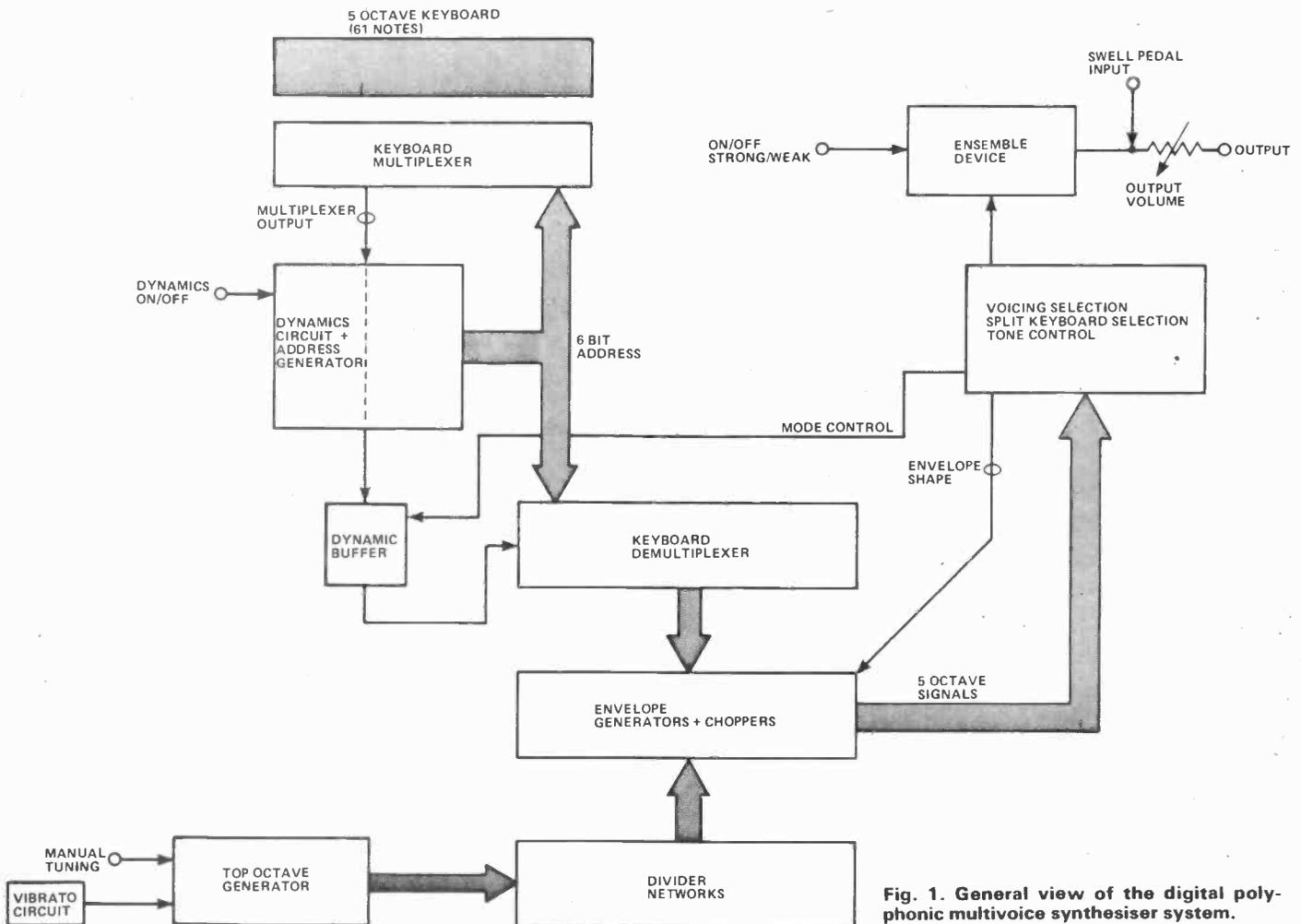


Fig. 1. General view of the digital polyphonic multivoice synthesiser system.

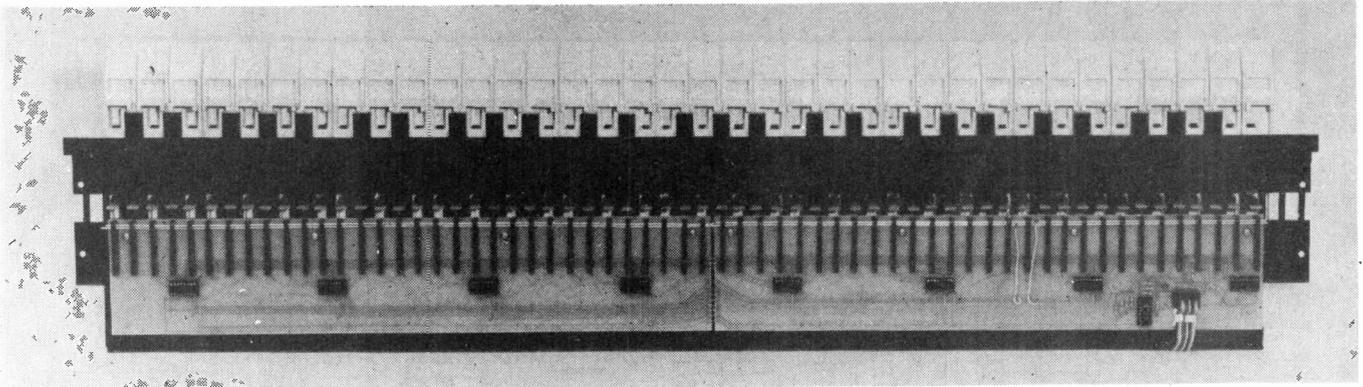

Keyboard with multiplex boards fitted. These carry the 61 contact assemblies through which the two bus bars pass. Connection to the dynamics board is made by DIL plug-on ribbon cable (bottom right).

suitable hole diameter for the self tapping screws. Screw the keyboard assembly into position and then check each contact wire and plunger. When the key is not pressed there should be about one twentieth of an inch gap between the wire and plunger. The wire can be bent with long nose pliers to obtain this spacing. Make sure that when each note is pressed the contact wire makes a firm contact with the +5V bus bar. If there are any dirty contact problems, then use a non residue cleaning spray to clean the contact blocks. I usually use Freon T TF112 (trichlorotrifluoroethane) which, although I can't pronounce it, seems to work OK.

Chorus—Ensemble Unit

Natural sounds tend to be more interesting than those generated electronically. This is mainly due to the fact that natural sounds have a great many changing parameters that make our 'forever analysing' ears sit up and take notice of them. Electronic sound structures can be given added interest by processing them with an ensemble unit (Fig. 6). This is a complex phasing unit that produces three layers of constantly moving comb frequency responses. The notches in the comb frequency response cancel out any harmonics that occur at that same frequency, but because the notches are continually moving this cancellation is not static. The overall effect of this on the sound structure is similar to the effect of several acoustic instruments trying to play the same piece of music, where a complex process of cancellation and addition is continually in operation. The ensemble unit simulates another parameter in the synthesis of the sound giving one more acoustic clue to its real identity.

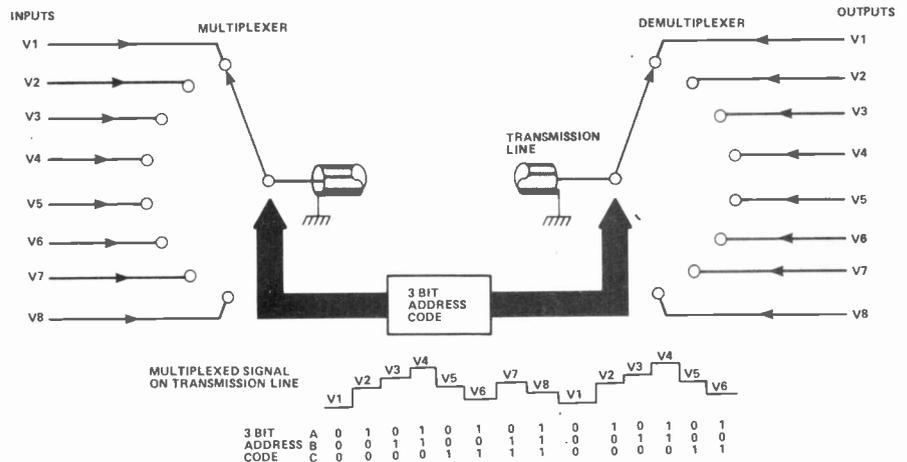


Fig. 2. The principle of the multiplexing/demultiplexing system.

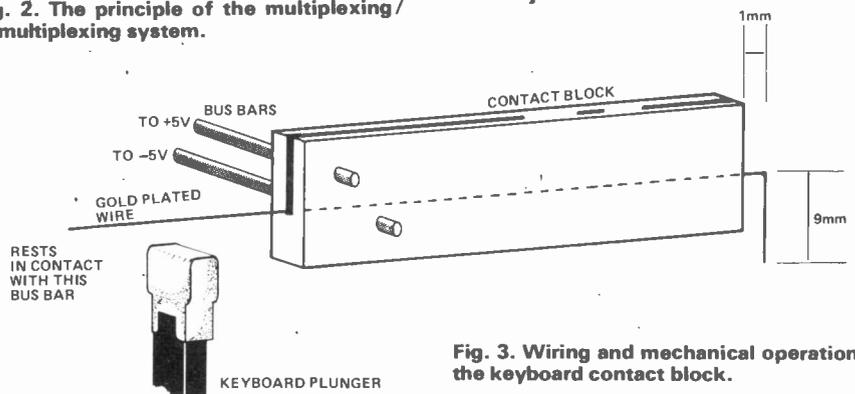


Fig. 3. Wiring and mechanical operation of the keyboard contact block.

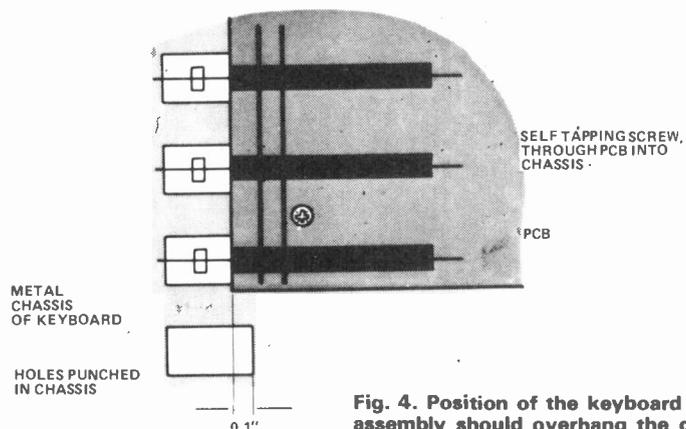


Fig. 4. Position of the keyboard PCB. The assembly should overhang the chassis by 0.1".

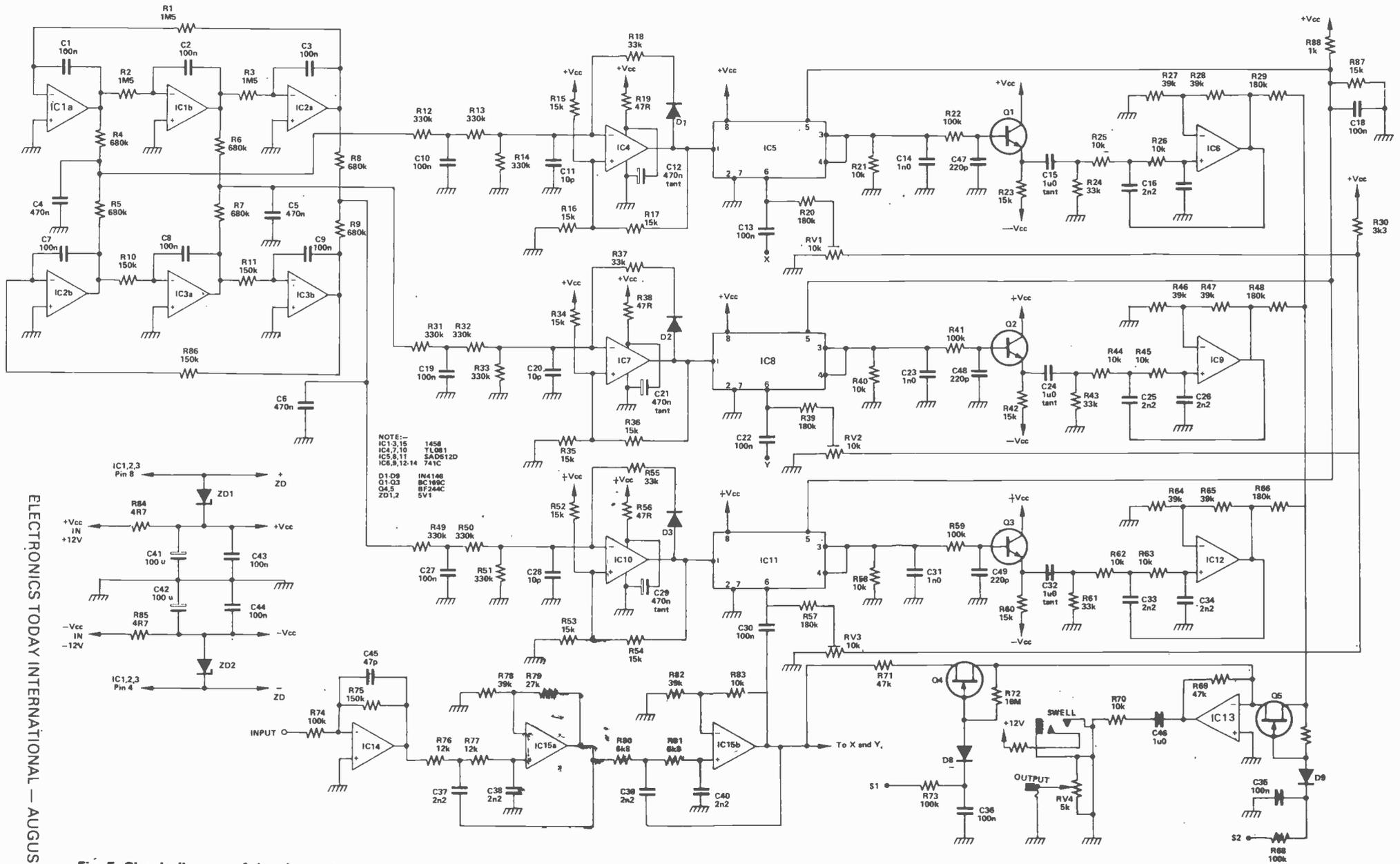


Fig. 5. Circuit diagram of the chorus / ensemble unit.

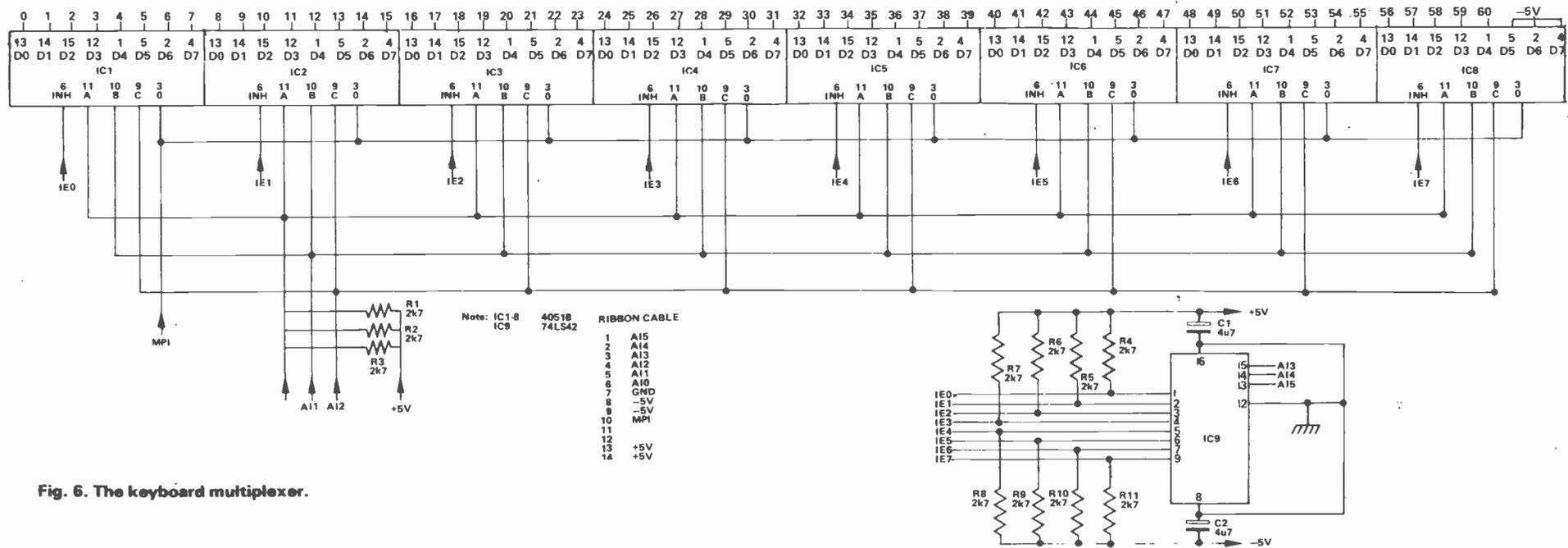


Fig. 6. The keyboard multiplexer.

HOW IT WORKS

The Op amps IC1, 2, 3 form a couple of three phase oscillators. Each oscillator is made up out of three integrators wired up in a loop. The overall DC loop phase is inverting, so it will never become latched up, but the circuit is inherently unstable and so will always oscillate. The output waveforms are trapezoidal in shape, each output being one third of a cycle behind its predecessor. One of the oscillators is set to run at 0.6 Hz, the other at 6 Hz. Pairs of outputs are mixed together and filtered by a simple RC lowpass filter. This removes most of the harmonics of the trapezoids producing reasonably pure sinusoids. The resulting waveform is a large 0.6 Hz sinewave with a smaller 6 Hz sinewave superimposed on top. This is then used to frequency modulate a fast running oscillator which in turn determines the position of the comb notches. The larger the modulation depth, the more pronounced is the ensemble effect. A milder effect is obtained by reducing the power supply voltage to the three phase oscillator (by introducing ZD1, 2 into the supply lines), which reduces the sinewave amplitudes.

The fast running oscillators, (IC4, 7, 10), are based around TL 081 op amps. These

have the same pinout as a 741 but are very fast having a slew rate of 13 V/uS. This enables them to be used as relaxation oscillators running in this case at frequencies of 100 to 200 kHz and generating pulse waveform with fast edges. The oscillator is a standard one op amp device that combines a Schmitt trigger and an integrator in the feedback route. The oscillation frequency is controlled by the modulation signal because this robs a varying amount of charging current from the 10 p timing capacitor.

Complex phasing is produced by passing the audio signal through the three delay lines, the output signals of which are mixed together. The time delay is controlled by the clock frequency which is calculated using the formula,

$$\text{Time delay} = \frac{512}{\text{Clock frequency}}$$

A clock frequency of 100 kHz will give a delay time of 5.12 mS, and 200 kHz gives 2.56 mS. The delay lines can be thought of as being analogue shift registers. On every clock pulse, the analogue signal is sampled and shifted along one position in

the register. After 512 clock periods, the original input signal appears at the output and so it can be correctly claimed that a time delay of 512 clock periods has been produced. The signal is not continuous, but is quantized into time intervals. This can result in a phenomena known as aliasing, which sounds rather like ring modulation, whereby the audio signal intermodulates with the clock (sampling) frequency. This generates a new set of signals (sidebands), some of which may fold back into the audio spectrum and cause annoyance. A lowpass filter (IC 15), is used to prevent these aliasing effects by band limiting the input signal to 7.5 kHz. The signals that appear at the delay line outputs (IC5, 8, 11, pins 3 and 4), are quantized in time and are restored to their former continuous shape by third order lowpass filters (Q1, IC6 for example). There is a preset control for each delay line that provides a DC bias level. This is adjusted so that the SAD 512D produces an unclipped signal at its output. The preset has enough range to enable clipping to occur on both positive and negative signal excursions but should be adjusted so that it is intermediate between these two extremes.

The continual modulation of the three time delays and the subsequent mixing of the signals produces a constantly moving frequency response that has several notches. This turns a relatively flat electronic sound into something that has a chorus or ensemble characteristic about it, which can be used to enhance the string, brass and even the piano output. The ensemble effect can be turned off and the original single only can be heard by use of electronic signal routing on the PCB.

This is achieved by using a couple of FET's, (Q4, 5) as voltage controlled switches, which obtain their command signals from the control panel. The output signal level can be controlled by both a manual volume control and by an optional swell pedal.

This device uses a lamp photo-cell variable optical slit to produce a foot operated variable resistor. As the foot pedal is rotated, more light falls onto the photocell via the slit and this reduces the cell's resistance. The life-time and smoothness of operation of this system is much better than that of a conventional pot with a rack and pinion linkage mechanism.


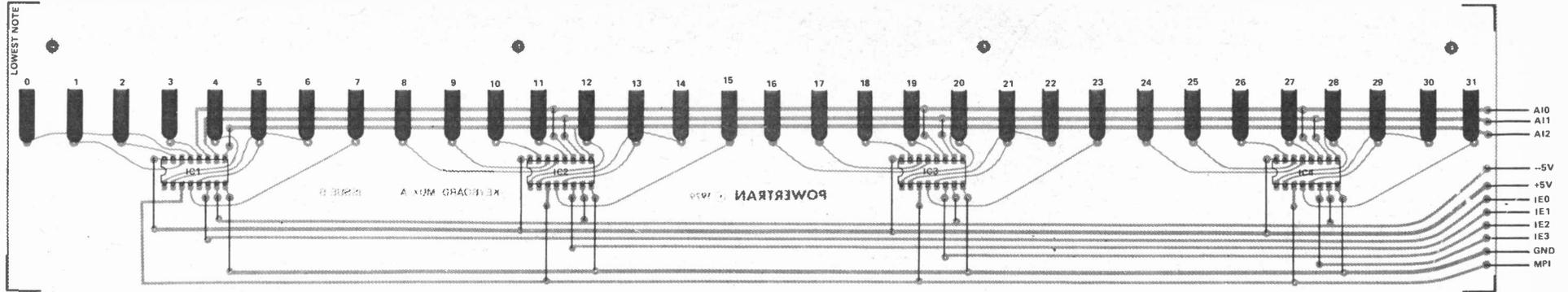


Fig. 7a (above) and 7b (below) show the component overlays for the two boards which go to make up the keyboard and multiplexer.

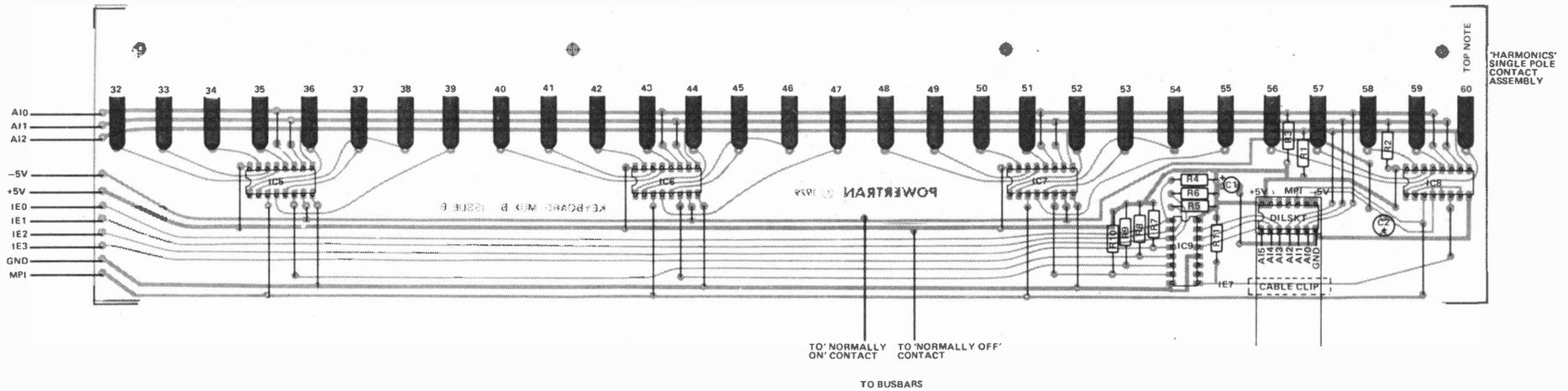

PARTS LIST

Keyboard Multiplexer

RESISTORS all 1/5W 5%

R1-11 2k7

CAPACITORS

C1, 2 4u7 16V tantalum

SEMICONDUCTORS

IC1-8 4051B

IC9 74LS42

MISCELLANEOUS

Keyboard multiplexer PCBs A and B, harmonics contact assemblies (single pole), 5 octave length of bus bar 1.4mm diam., 9 off 16 pin DIL sockets, one off 14 pin DIL socket, cable clamp (8 way ribbon), 14 way ribbon cable connector lead.

Ensemble Chorus Unit

RESISTORS all 1/5W 5%

R1,2,3 1M5

R4-9 680k

R10,11,75,86 150k

R12,13,14,31 32,33,49,50

51 330k

R15,16,17,23 34,35,36,42, 52,53,54,60, 87 15k

R18,24,37,43, 55,61 33k

R19,38,56 47R

R20,29,39,48, 57,66 180k

R21,25,26,40, 44,45,58,62, 63,83 10k

R22,41,59,68, 73,74 100k

R27,28,46,47, 64,65,78,82 39k

R30,70 3k3

R31,32,33,49, 50,51 330k

R67,72 10M

R69,71 47k

R76,77 12k

R79 27k

R80,81 6k8

R84,85 4R7

R88 1k

POTENTIOMETERS

RV1,2,3 10k

RV4 5k

CAPACITORS

C1,2,3,7,8,9, 10,13,18,19, 22,27,30,35, 36,43,44 100n

C4,5,6 470n

C11,20,28 10p

C12,21,29 470n 35V tantalum

C14,23,31 1n0

C15,24,32 1u0 35V tantalum

C16,17,25,26, 33,34,37,38 39,40 2n2

C41,42 100u 25V electrolytic

C45 47p polystyrene

C46 1u0

C47,48,49 220p ceramic

SEMICONDUCTORS

IC1,2,3,15 MC1458

IC4,7,10 TL081

IC5,8,11 SAD512D

IC6,9,12,13,14 741C

Q1-3 BC169C

Q4-5 BF244C



D1-9 1N4148

ZD1,2 5V1 400mW.

MISCELLANEOUS

Chorus board PCB, PC pins, 9 way connector, 15 off 8-pin DIL sockets.

Fig. 8 (above). Component overlay for the chorus/ensemble board.
 (Right) With the base plate removed, the multiplex boards can be seen under the keyboard.

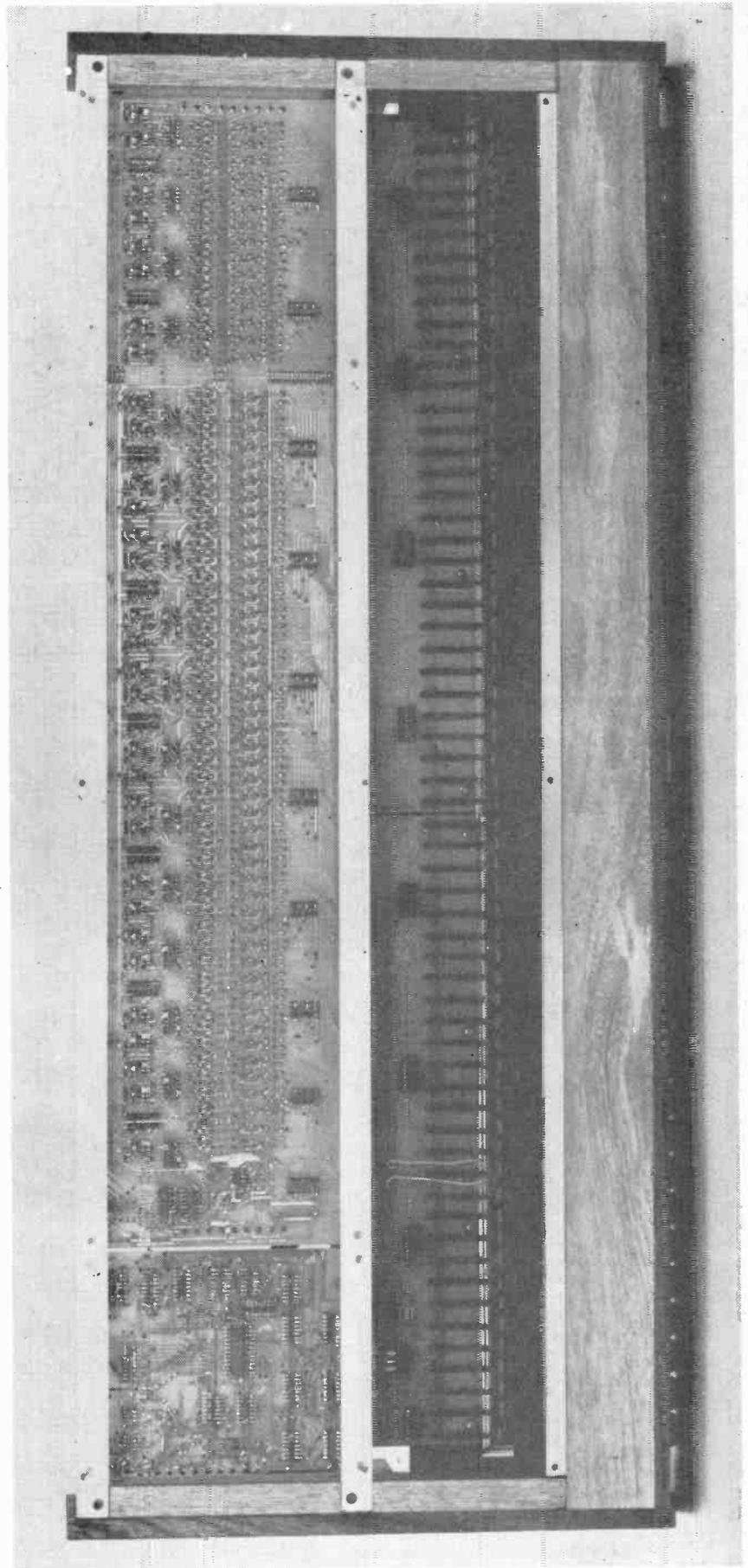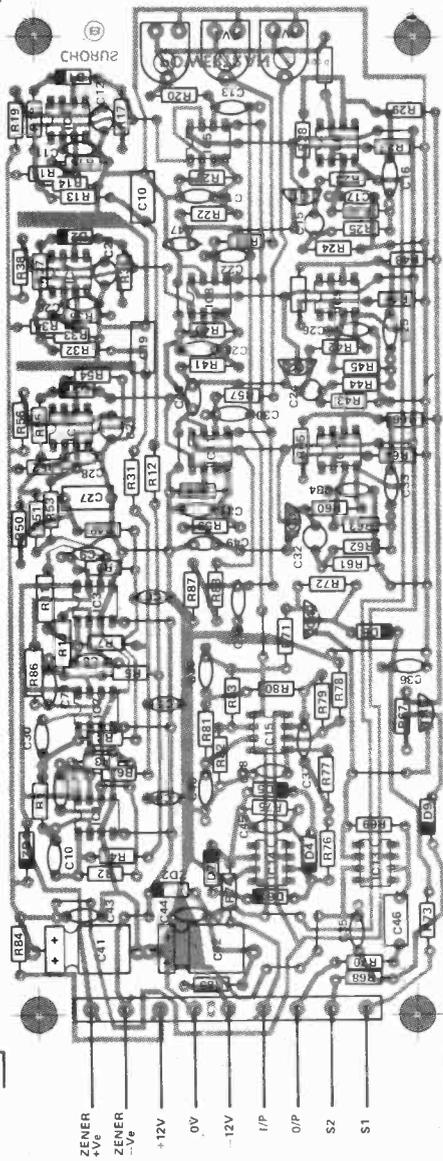



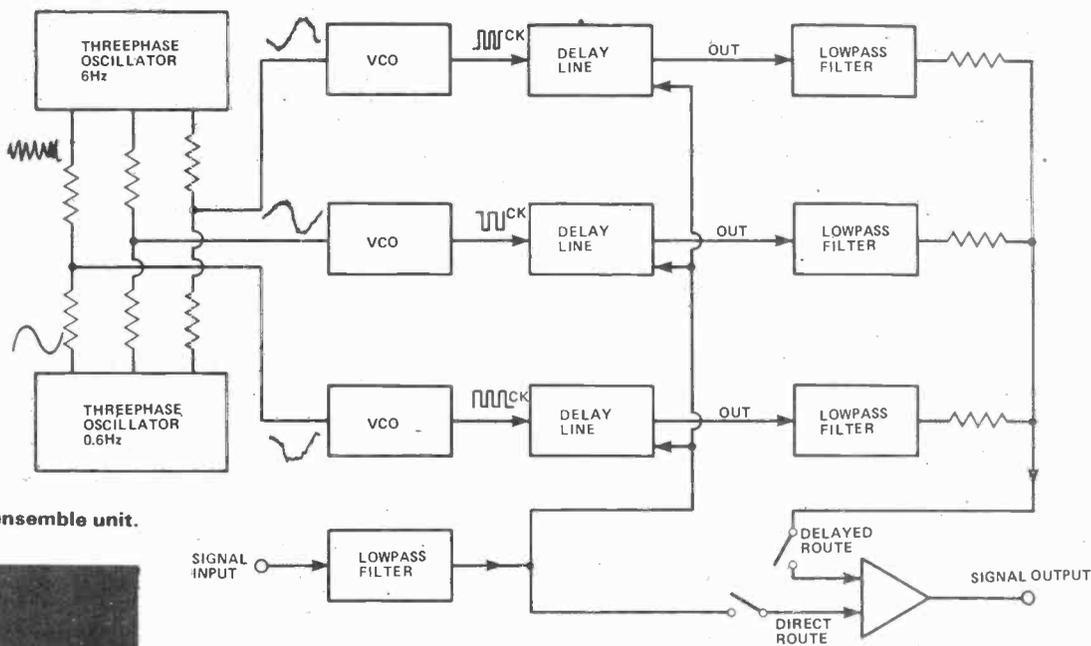



Fig. 5. Block diagram of the ensemble unit.

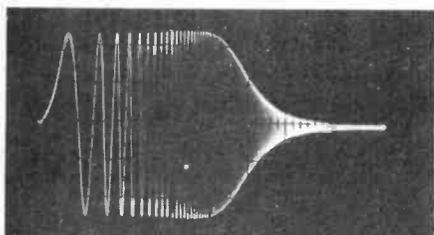

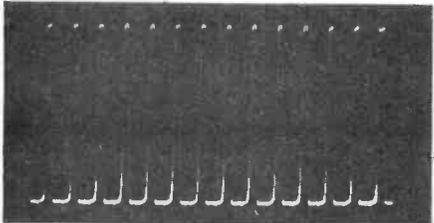
Frequency response of lowpass filters used in the chorus board.



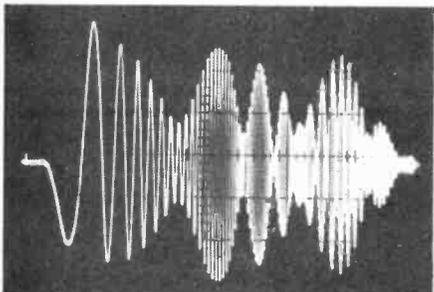Clock waveform of the high frequency oscillators used in the chorus board, sweep the delay frequency = 200 kHz.



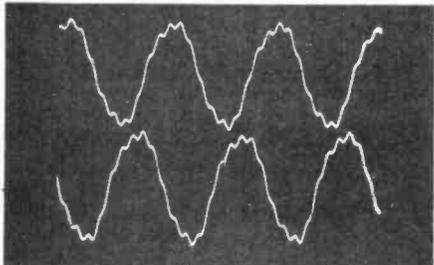Frequency response of the chorus unit. This pattern is constantly changing with the notches sweeping up and down.



Two of the three control voltages that sweep the delay lines in the chorus unit.



Cambridge Learning Enterprises

SELF-INSTRUCTION COURSES

UNDERSTANDING DIGITAL ELECTRONICS

In the years ahead the products of digital electronics technology will play an important part in your life. Calculators and digital watches are already commonplace. Tomorrow a digital display could show your vehicle speed and fuel consumption; you could be 'phoning people by entering their name into a telephone which would automatically look up their number and dial it for you.

These courses were written by experts in electronics and learning systems so that you could teach yourself the theory and application of digital logic. Learning by self-instruction has the advantages of being faster and more thorough than classroom learning. You work at your own pace and must respond by answering questions on each new piece of information before proceeding.

After completing these courses you will have broadened your career prospects and increased your fundamental understanding of the rapidly changing technological world around you.



Digital Computer Logic and Electronics is designed for the beginner. No mathematical knowledge other than simple arithmetic is assumed, though the student should have an aptitude for logical thought. It consists of four volumes - each A4 size - and serves as an introduction to the subject of digital electronics. Everyone can learn from it - designer, executive, scientist, student, engineer.

Contents include: Binary, octal and decimal number systems; conversion between number systems, AND, OR, NOR and NAND gates and inverters; Boolean algebra and truth tables; De Morgans Laws; design of logic circuits using NOR gates; R-S and J-K flip flops; binary counters, shift registers and half adders.

FLOW CHARTS & ALGORITHMS help you present: safety procedures, government legislation, office procedures, teaching materials and computer programs by means of YES and NO answers to questions.


The Algorithm Writer's Guide

explains how to: define the questions, put them in the best order and draw the flow chart, with numerous examples shown. All that students require is an aptitude for logical thought. Size: A5, 130 pages. This book is a MUST for those with things to say.

NEW from Cambridge Learning Enterprises O - LEVEL ENGLISH LANGUAGE

More and more jobs require a C-GRADE PASS, and over 250,000 people fail to get this every year. Will one of them be in your family? This new course, written by experts in a style that's serious yet fun to read, shows you how to mark your own work and compare it with the work of other people in their exam year. Set your own pace and assess your results immediately with no postal delays: watch your speed and standards improve. In Book 1 learn how you will be marked on COMPREHENSION, Book 2 covers SUMMARY, PUNCTUATION & SPELLING, and Book 3 coaches you in the principles of COMPOSITION. Size: 3 A4 volumes totalling 250 pages.

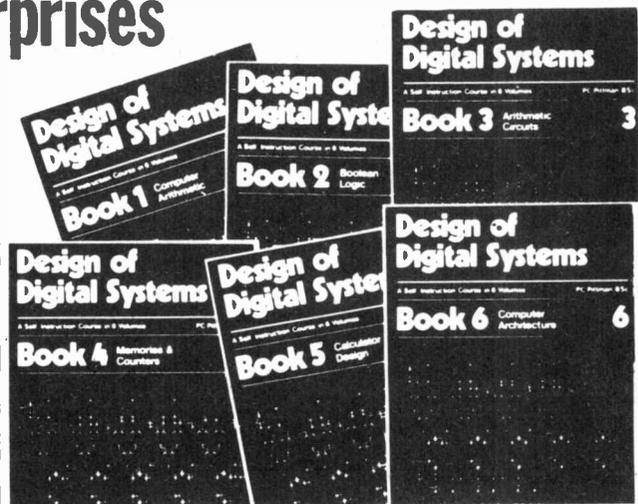**CAMBRIDGE LEARNING ENTERPRISES, UNIT 11
RIVERMILL SITE, FREEPOST, ST. IVES, HUNTINGDON,
CAMBS. PE17 4BR, ENGLAND
TELEPHONE: ST. IVES (0480) 67446.
PROPRIETORS: DAYRIDGE LTD. REG. OFFICE: RIVERMILL LODGE, ST. IVES
REGD. IN ENGLAND No. 1328762**



Design of Digital Systems is written for the engineer seeking to learn more about digital electronics. Its six volumes - each A4 size are packed with information, diagrams and questions designed to lead you step-by-step through number systems and Boolean algebra to memorys, counters and simple arithmetic circuits, and finally to a complete understanding of the design and operation of calculators and computers. Contents include:

Book 1 Octal, hexadecimal and binary number systems; conversion between number systems; representation of negative numbers; complementary systems; binary multiplication and division.

Book 2 OR and AND functions; logic gates; NOT, exclusive-OR, NAND, NOR and exclusive-NOR functions; multiple input gates; truth tables; De Morgans Laws; canonical forms; logic conventions; Karnaugh mapping; three-state and wired logic.

Book 3 Half adders and full adders; subtractors; serial and parallel adders; processors and arithmetic logic units (ALUs); multiplication and division systems.

Book 4 Flip flops; shift registers; asynchronous and synchronous counters; ring, Johnson and exclusive-OR feedback counters: random access memories (RAMs) and read only memories (ROMs).

Book 5 Structure of calculators; keyboard encoding; decoding display data; register systems; control unit; program ROM; address decoding; instruction sets; instruction decoding; control programme structure.

Book 6 Central processing unit (CPU); memory organization; character representation; program storage; address modes; input/output systems; program interrupts; interrupt priorities; programming; assemblers; computers; executive programs; operating systems and time sharing.

Four volumes Digital Computer Logic & Electronics at £6.50 inc p & p
Six volumes Design of Digital Systems at £10.50 inc p & p
Three volumes O-Level English Language at £6.50 inc p & p
The Algorithm Writer's Guide at £3.40 inc p & p
If your order exceeds £14 deduct £2 from your payment
Price includes surface mail anywhere in the world, airmail extra
GUARANTEE If you are not entirely satisfied your money will be refunded
Please allow 21 days for delivery

Cambridge Learning Enterprises, Unit 11 Rivermill Site, FREEPOST, St. Ives, Huntingdon, Cambs. PE17 4BR, England.

Please send me the following books:

..... sets Digital Computer Logic & Electronics at £6.50, p & p

..... sets Design of Digital Systems at £10.50, p & p included

..... O-Level English Language at £6.50 p & p included

..... The Algorithm Writer's guide at £3.40, p & p included

Name

Address

.....

I enclose a *cheque/ PO payable to Cambridge Learning Enterprises for £.....

Please charge my *Access/Barclaycard/Visa/Eurocard/Mastercharge/Interbank account number

Signature..... *delete as appropriate.

Telephone orders from credit card holders accepted on 0480-67446 (AnsaFone). Overseas customers should send a bank draft in sterling drawn on a London Bank, or quote credit card number.

EDITORIAL ENQUIRIES TO ETI

ETI editorial staff will answer readers questions about RECENT articles in any of our publications, either by telephone or through the post.

Telephone enquiries can only be answered on Monday afternoons, after 2.30 pm. This is to avoid confusion with our companion magazines, HE and CT. In addition this gives the editorial department the rest of the week to turn out the magazine! Accordingly this will be strictly adhered to, and we apologise for any trouble you may have in contacting us.

Postal problems are answered as soon as possible, but MUST contain an SAE if you want a reply outside the pages of ETI. Short letters which are phrased so as to lend themselves to YES/NO type answers will probably bring you a faster reply.

There are a lot more of you out there than there are of us in here, so please be patient with us if our service cannot always be return of post. Complaints about this service should be made, in writing, to the editor at the usual address which is (we've moved!):—

145 Charing Cross Road, London WC2H 0EE.

Semiconductor Guides



TVT '78 Vol. 1: A...Z
Transistor comparison table
Lists more than 25,000 equivalent types for approx. 5,000 transistors. 9th edition.
292 pages, 11 illustrations, 137 connection drawings. In handy wipe-clean format.
DIN A6, wipe-clean cover.
Order No. 30
ISBN 3-88109-010-X



IC-tin 1
Linear operational amplifiers.
Data and comparison table for integrated op amps and comparators. 2nd edition, DIN A6 compact format.
288 pages, types, functions, applicational examples, 152 connection drawings, 48 case drawings.
Order No. 11
ISBN 3-88109-008-8



THT '77
Data and comparison table for thyristors, tetrodes, trigger diodes, triacs, unijunction transistors (UJTs) and programmable UJTs (PUTs).
2nd edition, 430 pages listing 1,440 types and approx. 250,000 entries.
Order No. 20
ISBN 3-88109-009-6



TVT '78 Vol. 2: 2N...∞
Transistor comparison table.
Lists more than 35,000 equivalent types for approx. 7,000 transistors.
2N...—2SA...
2SB...—2SC...
2SD...—2SK...
3N...—∞
408 pages, 11 illustrations, 141 connection drawings. In handy wipe-clean format.
DIN A6, wipe-clean cover.
Order No. 31
ISBN 3-88109-011-8

new!

To: **Technical Book Services**
P.O. Box 79
Maidenhead, Berks SL6 2EG

ORDER FORM

Name
(Print Please)
Address

Registered office: 21 Mincing Lane, London, EC1 Registered No. 12225

TYPE
TVT78 A-Z
TVT782N
THT77
LIN 1
LIN 2

PRICE:
£4.00
£4.00
£4.00
£3.60
£3.80

ALSO AVAILABLE

DVT Diode Equivalent Book £2.30
DTE2 Diode Data Book £2.30
DIGI Digital I.C. Equivalent Book £5.50

I enclose £..... p..... for the books as marked X Prices Inc. P&P

Ni~Cd CHARGER

Not content with giving you the best value for money, we now come up with a good method of saving it!

IF YOU OWN OR use battery powered equipment then the price of batteries and the monotonous regularity with which replacements are necessary must surely cause manical depressions as well as burn holes in the proverbial pocket.

One answer is to buy Nicad cells — although you may have to arrange a second mortgage initially, because they are pretty expensive (about three times the cost of yer average cell). Their great advantage is that they are rechargeable and can have a working life of well over 500 recharges. Just think of all that money you could save!!!


Being Constant

Nicads need to be charged with a more or less constant current. This current is derived as a function of the capacity of a cell and the length of time being charged. To clarify this point we can take for an example a cell — size AA (equivalent to U11, HP11 etc). Capacities of cells vary from manufacturer to manufacturer but an AA sized nicad has an approximate capacity of 0.5Ah. Simply speaking, if 500 mA is drawn from the cell it will provide power for one hour. If 50 mA is drawn then the cell will provide power for 10 hours. Similarly, to recharge the cell to full capacity (assuming 100% efficiency) it would take 500mA for one hour or 250mA for two hours, etc.

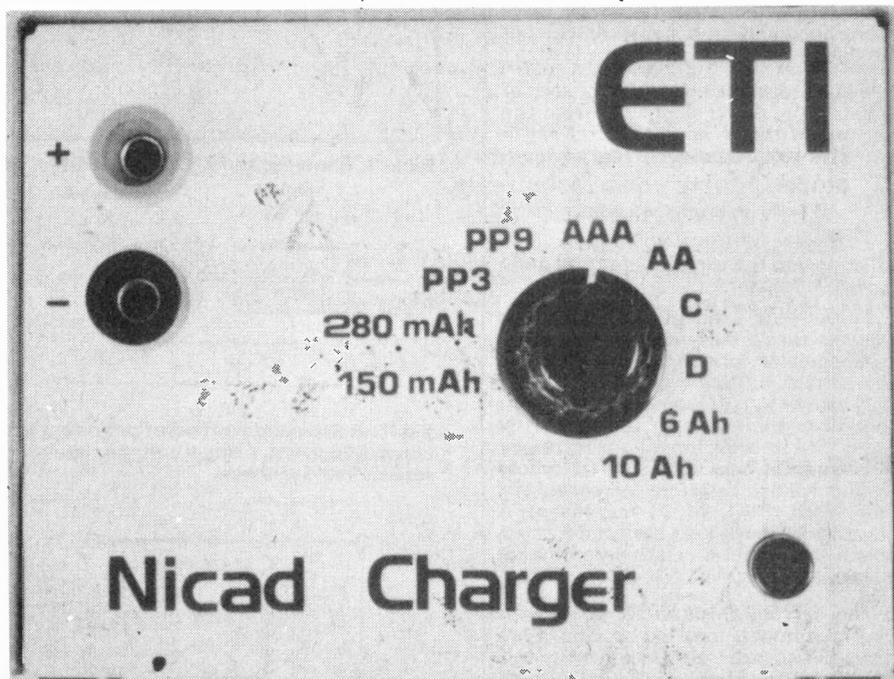Problems Problems

This is where the basic problem lies. Because of the make-up of the cell, if an overcharge is given eg 250mA for 3 hours, then permanent damage can be caused to it.

So, at any given charging current the cell must be disconnected at the time of full charge, or so it would appear. It is, however, a little known fact that at currents less than $\frac{C}{18}$ (where C is the capacity of the cell) then no permanent damage can occur, no matter how long the cells are connected to the charger. The ETI



nicad charger is designed with this criteria in mind. It will comfortably charge up to six cells in series (of the same type) at a rate of $\frac{C}{18}$ amps


The values given for R2-11 were theoretical, derived from Ohm's law. The charging current can be checked easily by connecting an ammeter across the Output (the current remains constant whatever the load)

and take readings with each resistor in circuit and change if necessary.

Building Up To It

Construction is simple — there are only 6 components in the main part of the circuit (not counting the current setting resistors R2 to R11).

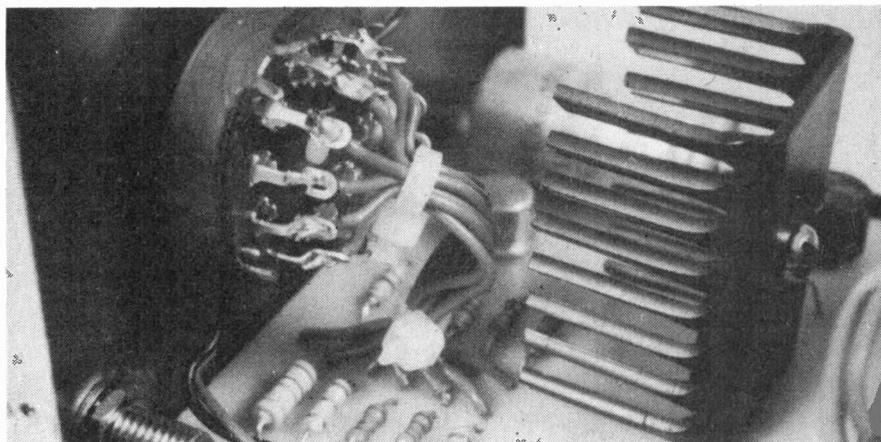Note the transistors Q2 needs a reasonable heatsink.



HOW IT WORKS

One of the most convenient methods of obtaining a constant current is to use a voltage regulator and a current limiting resistor, as in Fig. 1.

R1 determines the current. If a five volt regulator is in use then a constant 5V is held across it. From Ohm's law the current $I = \frac{V}{R}$. The common connection is essentially a negative feedback loop, acting to maintain a constant current through the resistor and into the load.

A slight disadvantage of this sort of circuit is the power dissipated from the resistor. With 5V across it and say a current of 500mA through it, the power P,

$$P = IV = \frac{1}{2} \text{ amp} \times 5 \text{ volts} = \frac{1}{2} \text{ watts.}$$

This means the use of a large and quite expensive resistor.

The circuit used in the ETI Nicad Charger uses a fairly standard type voltage regulator, formed by Q1 and Q2, but the current limiting resistor R2 (Fig. 2) only has the V_{BE} of Q1 across it — 0.6 volts for silicon transistors. If the V_{BE} of Q1 drops then its collector voltage increases, increasing the base voltage of Q2, whose emitter voltage therefore increases (and vice versa if V_{BE} of Q1 increases). A negative feedback loop has been formed, which maintains a relatively constant voltage across R2, of 0.6V.

The current through R2 is also the current through the load so Ohm's law gives the correct resistance for the required current, identical to that already discussed, but with the advantage that lower power resistors can be used (due to the lower voltage), even at high currents.

$$\text{eg. } P = IV = 500 \text{ mA} \times 0.6 \text{ volts} = 0.3 \text{ watts.}$$

It is simply now, a matter of choosing the required current and calculating the resistance.

TABLE I

Position	Resistor	Current	Type of cell & Capacity
1	R2	9mA	150 mA Hour Button cell
2	R3	17mA	280 mA Hour Button cell
3	R4	5.5mA	90 mA Hour PP3
4	R5	75mA	1.2 A Hour PP9
5	R6	11mA	0.18 A Hour AAA
6	R7	31mA	0.5 A Hour AA
7	R8	125mA	2 A Hour C
8	R9	250mA	4 A Hour D
9	R10	375mA	6 A Hour
10	R11	625mA	10 A Hour

Table 1. Showing switch SW1 positions related to cells under charge.

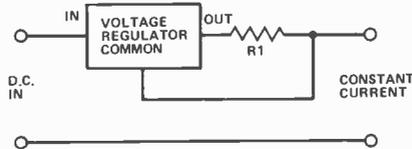


Fig. 1. A Standard method of providing a constant current, using a voltage regulator, resistor and feedback.

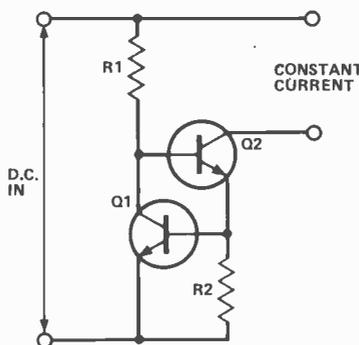


Fig 2. Improved constant current source.

PARTS LIST

RESISTORS
(all 1/4W, 5% except where shown)

R1	1K
R2	68R
R3	39R
R4	120R
R5	10R
R6	56R
R7	22R
R8	5R6
R9	2R7 1/2 watt
R10	1R8 1/2 watt
R11	1R0 1/2 watt

CAPACITORS

C1	1000u 25V
----	-----------

SEMICONDUCTORS


Q1	BFY 50
Q2	TIP 33A
BR1	1Amp 50V

MISCELLANEOUS

FS1+Holder	
TR1	12 V 1 Amp mains transformer
SW1	1-Pole 10-way Rotary Switch
Suitable connections to cells	
Case to suit.	

BUYLINES

There should be no problems in obtaining any of the components from any stockist.

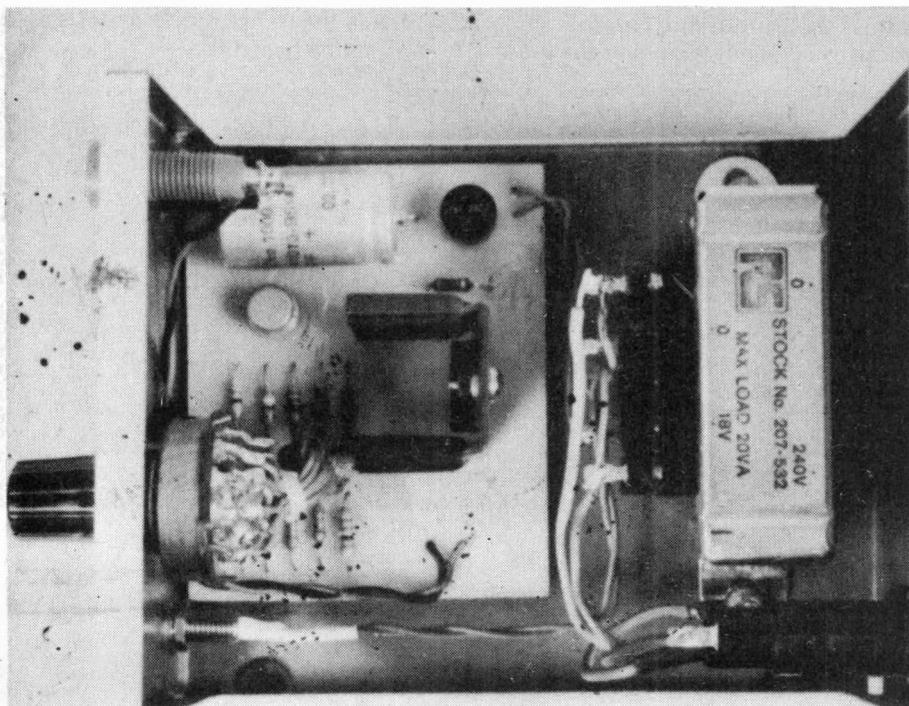

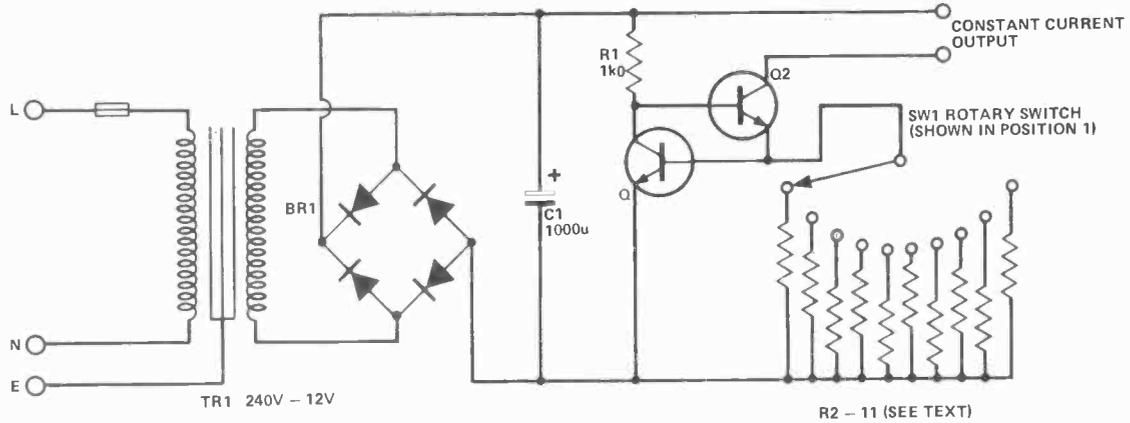



Fig 3. Circuit diagram for the ETI Charger. Resistor values are given in the text for the charger resistors.

per hour, therefore enabling them to be constantly trickle charged and kept at full capacity day and night. If the cells are partially discharged on connection they will take up to 16 hours to reach full capacity.

PP3 and PAP9 type nicads can also be charged but only one at a time, unlike the lower voltage types.

ETI

Fig. 4. Component overlay for the Ni-Cd Charger design.

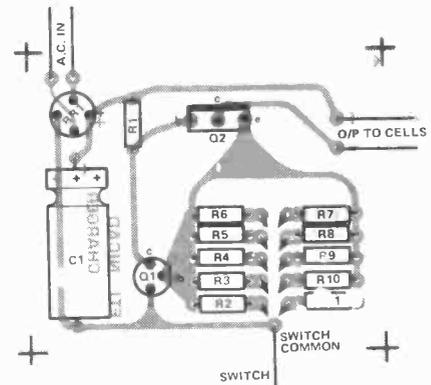

WHAT A BIND!

KEY:

- 1: The bit of chocolate you thought you'd leave for later.
- 2: Coffee stains (instant).
- 3: A useful-sized bit of stiff paper to stop the window from rattling.
- 4: Rough calculations for your new combined egg timer/laser cannon project.
- 5: ETI makes a fair soldering iron stand.
- 6: The dog insisted on carrying your copy to you along with your slippers.

Half our orders for binders are repeats: we think that says a lot for their quality. At £3.20 all inc. you get a great deal of peace of mind too!

ETI Binders
145 Charing Cross Road,
London WC2H 0EE

CALCULATORS

SCIENTIFIC

***SPECIAL OFFER**
TEXAS T159 together with PC100B
(Complete as manufacturer's specifications)
£285.00

- TEXAS / HP Accessories available
- *TEXAS T159 (New Card prog 960 prog steps of 100 mem) £156.50
 - *TEXAS T158 (New Key prog 480 steps or 60 mem) £80.00
 - *TEXAS PC100B (New updated Printing Unit for T158 / T159) £140.00
 - *TEXAS T157 (Key Prog 8 mem. 150 Keystrokes / 50 Prog Steps) £28.95
 - TEXAS T133 (New — same spec. as T130, but 3 mem) £13.95
 - *TEXAS T145 (New updated version of the Texas T140) £19.95
 - *TEXAS 42MBA (10 Dig Fin / Stat Prog 12 mem 32 keystrokes) £42.95
 - *TEXAS TI PROGRAMMER (Hexadecimal Oct) £46.50
 - *TEXAS T151/iii (New B Dig + Exp 10 mem 32 Prog Steps / Dig / Sci) £28.95
 - TEXAS T150 LCD (Sci / Stat. 2 Con Mem) £23.90
 - TEXAS T125 LCD (Sci / Stats) £18.50

"SLIM-LINE" Chronograph BARGAIN OFFER

You will not believe the luxury of this "slim-line" 12 function Chronograph until you have worn it... until you have enjoyed the compliments it generates.

The "Slim-line" Chronograph gives continuous easy to read LCD display of hours, minutes, seconds, AM/PM. At the touch of a button you have date — month — day of week — reverting to normal display time at the release of the button.

Press again for immediate stop watch / lap time facility to 1/100 second. The "Slim-line" now has a powerful back light for easy night use, the casing is chrome finished with matching linked bracelet.

We are so certain you will be delighted and satisfied with this "Slim-line" Chronograph that in addition to the One Year Warranty we are offering a 14-day money back guarantee if you are not entirely satisfied.



ONLY £16.50 + £1.00 p/p ins. Send cheque/P.O. or order via Barclay/Access credit card today under our Special 14-day Trial Offer.

- *TEXAS T153 with Applied Statistics £80.00
- *TEXAS T159 with PC100C and Applied Statistics £305.00

*SUMMER SALE

TEXAS T159 Calculator (complete as manufacturer's spec., master module, charger, etc.) PLUS statistics module and extra set of 40 Blank Prog Cards with wallet, etc.
ONLY £180

- *CBM 9190R (as 4190R but with 9 memories) £27.50
- *CBM Pro 100 (72 Step Prog) £29.50
- *HP 29C (as 19C but no Printer) £92.00
- *HP32E (8 Mem Pro Sci / Stat) £84.00
- *HP32E (Advanced Sci with Statistics) £60.00
- *HP27 (10 Mem Sci / Fin / Stat) £73.50
- *HP 1E (New Sci replaces HP21) £35.00
- *HP67A (C. Prog 224 Steps 26 Mem) £257.75
- *HP97A (Fully prog with Printer) £422.00
- CASIO AQ2000 (updated AQ1000 Cal. 3-Way Stopwatch / Alarm plus Date Calendar) £22.00
- CASIO FX3100 (LCD Sci. Std / DP / Rec.) £22.50
- CASIO FX8000 (as above + Stop Watch / Alarm) £27.73
- *CASIO FX202P (127 Step Sci Prog Con Mem) £34.50
- CASIO FX501P (Sci. LCD display Prog. 128 Steps. 11 Mem) £46.00
- CASIO FX501P (Sci. LCD display Prog 256 Steps. 22 Mem) £64.00
- CASIO Prog Adapter — permits Progs to be recorded on to standard cassette recorders for replay on to Casio FX501P / FX502P at later stage £23.00

THE COMMODORE PET COMPUTER

with 8K bytes RAM 2001-8
A complete personal computer that operates anywhere by simply plugging into Main supply. Allows communications directly from BASIC to IEEE — 488 standard devices —

Cassette. Video Display Unit and Keyboard built into PET
Fully guaranteed Warranty by CBM
complete only £850
PET 2001-16N £675

NOW IT'S YOU AGAINST 'COMPUTERS'

BORRIS is the most advanced chess computer yet. Borris is ideal for learning and improving your chess game from beginner to master. Borris can play against himself, has Alpha-Numeric prompting to help improve play and by simple switching you have facility to follow Borris's thinking while he analyses position before making a move. Walnut case, wooden chessmen, board mains adaptor, etc. £175.00
CHESS CHALLENGER '10' (10 Levels of beginner to master) £135.00
CHESS CHALLENGER '7' (7 levels of game) £88.00

*FREE — Mains / Charger included *

GOODS FULLY GUARANTEED. PRICES EXCLUDE VAT (ADD 15%) BUT INC. P&P CHEQUE WITH ORDER

Company / Hospital and Government orders accepted by phone
Barclaycard / Visa / Access accepted by phone

rel. 01-455 9823

EXPORT ORDERS WELCOMED

Air Freight / Air Post Delivery

Quotations on request. Payments via Letter or Credit / Int. Money Order / Credit Card, etc.

MOUNTAINDENE
22 Cowper St., London, EC2

Hello everybody — we're back!

SEIKO - 20% OFF!

LATEST MODELS — LOWER PRICES

- Japanese versions — similar to UK models listed.
- GG003 Chronograph (RRP £69.50) £55.50
 - GD007 Chronograph (£92.50) £74.00
 - FW007 Alarm / Chronograph (£115) £92.00
 - GC003 Programmable Alarm / Chrono (£135) £108.00
 - GH001 Solar Alarm / Chrono (£155) £124.00
 - FX003 Memory Bank (£130) £104.00

LCD PROGRAMMABLES

With non-volatile stores and memories and almost infinite programmability (using FA-1)


- CASIO FX-501P
128 steps
11 memories
5 levels ()
RRP £59.95
£49.95
- FX-502P
256 steps
22 memories
10 levels ()
RRP £79.95
£69.95



- FA-1 Adaptor
RRP £24.95
£19.95

51 scientific functions. Conditional jumps, etc. 1300 hours battery life. 3/4" x 2 3/4" x 5 1/2". Optional FA-1 permits programme / data storage on standard cassette tape recorder for re-entry later. Typical storage / re-entry time 9-16 seconds.

LATEST SCIENTIFICS

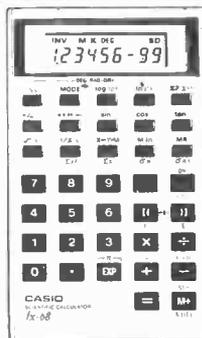

CASIO FX-68

LCD Display

Leatherette wallet

RRP £24.95

£19.95

37 scientific functions including trigs, logs, exponentiations, etc. Statistical — standard deviations. Polar to rectangular, R—P and sexagesimal to decimal conversions. Pi, cube root, 6 levels of parenthesis. Full memory. 500 hours battery. A very convenient 3/16" x 1 7/8" x 3 3/8".

- FX-80 Specification as above plus ENG key, 4000 hour battery life from two AA size batteries. 3/4" x 3" x 5 7/8" (£21.95) £16.95
- FX-48 (£18.95) £14.95. FX-58 (£29.95) £24.95.
FX-2500 (£24.95) £19.95. FX-3100 (£28.95) £23.95. FX-8000 (£35.95) £29.95.

CASIO CALCULATING ALARM CLOCKS
CQ-81 (£18.95) £14.95. CQ-82 (£24.95) £19.95. AQ-2000 (£20.95) £24.95. Melody 80 (£29.95) £25.95.

NEW CASIO CHRONOGRAPH

Puts most solar watches in the shade!

Casio 95QS-31B

Lithium battery

1 / 100 sec chrono

Dual time

RRP £29.95

Our price

£24.95



4-year Lithium battery outlasts most solar watches. Chronograph measures net, lap and 1st and 2nd place times from 1/100 second to 6 hours. Constant LC Display of hours, minutes, seconds, am/pm and day. (12 or 24 hour system). Automatic day, date, month and year calendar. Dual time facility (12 or 24 hour system). Stainless steel encased. Mineral glass face. Water resistant to a depth of 66 feet (2 at). Backlight, s/s bracelet with easily removable links.

EXCEPTIONAL VALUE

In our opinion this watch represents the finest value for money available today. At Christmas the 46CS-27B had a RRP of £89.95 and you would reasonably expect to pay at least that amount for a watch of this quality and specification.



Casio 46CS-27B

Alarm

Chimes

1 / 100 sec chrono

7.8mm thick

RRP £49.95

£39.95

Constant LC Display of hours, minutes, seconds, am/pm and day (12 or 24 hour system). Automatic day, date, month and year calendar. 24 hour alarm, optional hourly chime facility. Chronograph measures net, lap and 1st and 2nd place times from 1/100 second to 6 hours. Genuine stainless steel case (not "finish") only 7.8mm thick. Mineral glass face. Guaranteed water resistant to 100 feet (3 at). Backlight.

UNBEATABLE QUALITY AND VALUE FOR MONEY FROM JAPAN — WHY SETTLE FOR LESS?

Most CASIO products available from stock. Send 25p for illustrated brochures of this superb range of watches or calculators (both on request).

Prices include VAT, P&P. Send cheque/P.O. or phone your ACCESS or BARCLAYCARD number to:

TEMPUS

Dept. ETI, Beaumont Suite 164-167 East Road
Cambridge CB1 0DB Telephone: 0223 312866

ELECTRONICS TODAY INTERNATIONAL — AUGUST 1979

PLEASE SEE V.A.T. ADVERTISEMENT ON PAGE 15 BEFORE ORDERING GOODS FROM ADVERTISERS!

ETI BOOK SERVICE

How to order: Make cheques etc payable to ETI Book Service. Payment in sterling only please. Orders should be sent to: ETI Book Service, PO Box 79, Maidenhead, Berks. All prices include P&P.

BEGINNERS

Beginners Guide to **Electronics** Squires £2.65
Beginners Guide to **Transistors** Reddihough £2.65
Electronic Measurement Simplified C. Hallmark £2.20
Electronics Self Taught Ashe, £4.40
Beginners Guide to **Integrated Circuits** Sinclair £3.15
Principles of **Transistor Circuits** S. Amos £4.75
Understanding **Electronic Circuits** Sinclair £4.10
Understanding **Electronic Components** Sinclair £4.10
Beginners Guide to **Radio** King £3.15
Beginners Guide to **Audio** Sinclair £3.10

COOKBOOKS

TV Typewriters Cookbook £7.75
CMOS Cookbook £8.20
Active Filters £11.30
IC Timer Cookbook £7.50
IC Op-Amp Cookbook £10.00
Video Cookbook £7.00
TTL Cookbook £7.55
The Basic Cookbook £4.00 inc. p/p

APPLICATIONS

Advanced Applications for **Pocket Calculators** J. Gilbert £4.20
Build Your Own Working Robot D. Heisman £3.70
Electronics and Photography R. Brown £2.30
Fire and Theft Security Systems B. Weis £2.00
How To Build Proximity Detectors and Metal Locators J. Shields £3.90
How To Build Electronic Kits Capel £2.10
Linear Integrated Circuit Applications G. Clayton £5.40
Function Circuits Design & Applications Burr Brown £15.95
110 Electronic Alarm Projects R. M. Marston £3.45
110 Semiconductor Projects for the Home Constructor R. M. Marston £3.25
110 Integrated Circuit Projects for the Home Constructor R. M. Marston £3.25
110 Thyristor Projects Using SCRs R. M. Marston £2.95
Handbook of IC Circuit Projects Ashe £2.30
Practical Electronic Project Building Ainslie and Colwell £2.45

TV AND HI-FI

Audio Handbook G. King £6.50
Cassette Tape Recorders J. Earl £5.25
Solid State Colour TV Circuits G. R. Wilding £6.35
Hi-Fi Loudspeakers and Enclosures Cohen £8.20
How To Build Speaker Enclosures Badmateff £3.90
Master Hi-Fi Installation King £2.80

LOGIC

Logic Design Projects Using Standard ICs J. Wakerly £5.10
Practical Digital Design Using ICs J. Greenfield £12.50
Designing With TTL Integrated Circuits Texas Instruments £9.05
How To Use IC Circuit Logic Elements J. Streater £3.65
110 COSMOS Digital IC Projects for the Home Constructor R. M. Marston £3.20
Understanding CMOS Integrated Circuits R. Melen £4.00
Digital Electronic Circuits and Systems R. M. Morris £3.50
MOS Digital ICs G. Flynn £5.10

COMPUTING

Microprocessors and Microcomputers B. Soucek £18.80
Microprocessors D. C. McGlynn £8.40
Introduction to Microprocessors Aspinall £6.40
Beginners Guide to Microprocessors £4.70
Beginners Basic Gosling £3.35

OP-AMPS

Applications of Operational Amplifiers Graeme (Burr Brown) £8.30
110 Operational Amplifier Projects for the Home Constructor R. M. Marston £2.95
Experiments With Operational Amplifiers Clayton £3.40
Designing With Operational Amplifiers Burr Brown £16.65
Operational Amplifiers Design and Applications G. Tobery (Burr Brown) £7.40
Op-Amp Circuit Design & Applications J. Carr £4.00

TEST INSTRUMENTS

The Oscilloscope In Use Sinclair £3.10
Test Instruments for Electronics M. Clifford £2.40
Working With the Oscilloscope A. Saunders £1.95
Servicing With the Oscilloscope G. King £5.60
Radio Television and Audio Test Instruments King £5.90

SERVICING

Electronic Fault Diagnosis Sinclair £3.20
Rapid Servicing of Transistor Equipment G. King £2.95
Tape Recorder Servicing Manual Gardner Vol. 1: 1968-70 £8.50
Vol. 2: 1971-74 £8.50
FM Radio Servicing Handbook King £4.80

COMMUNICATIONS

Communication Systems Intro To Signals & Noise B. Carlson £7.50
Digital Signal Processing Theory & Applications L. R. Rabiner £23.80
Electronic Communication Systems G. Kennedy £8.50
Frequency Synthesis. Theory & Design Mannasewitsch £23.40
Principles of Communication Systems H. Taub £8.10

THEORY

Introduction to Digital Filtering Bogner £10.20
Transistor Circuit Design Texas Instruments £9.35
Essential Formulae for Electrical and Electronic Engineers N. M. Morris £1.65
Modern Electronic Maths Clifford £6.70
Semiconductor Circuit Elements T. D. Towers £6.40
Foundations of Wireless Electronics M. G. Scroggie £4.45
Colour Television Theory Hudson £6.20

REFERENCE

Transistor Tabelle (Includes physical dimensions) £4.10
Electronic Engineers Reference Book (Ed. 4) L. W. Turner £27.70
Solid State Circuit Guide Book B. Ward £2.25
Electronic Components M. A. Colwell £2.45
Electronic Diagrams M. A. Colwell £2.45
Indexed Guide to Modern Electronic Circuits Goodman £2.30
International Transistor Selector T. D. Towers £6.00
International FET Selector T. D. Towers £4.35
Popular Valve/Transistor Substitution Guide £2.25
Radio Valve and Semiconductor Data A. M. Bell £2.60
Master Transistor/Integrated Circuit Substitution Handbook £5.60
World Radio TV Handbook 1978 (Station Directory) £8.00
Radio, TV and Audio Technical Reference Amos £24.85
TV Technicians Bench Manual (New Ed.) Wilding £5.10

MISCELLANEOUS

Integrated Electronics J. Milman £7.90
Microelectronics Hallmark £3.90
Practical Solid State DC Supplies T. D. Towers £6.20
Practical Triac/SCR Projects for the Experimenter R. Fox £2.25
Printed Circuit Assembly Hughes & Colwell £2.45

Fallen behind recent advances?
Just starting out?
Need a decent reference book?
ETI Book Service provides an easy
way of getting your hands
on the right title.

A FEW CHEAP TRICKS!

Want a stable low voltage? Want to fire a thyristor without using unijunctions, or even make a thyristor? Whatever your semiconductor problem there is probably a cheap way round it.

When you look over all the circuits that are published in the time of one month, you might imagine you'd need several rooms just to hold all the semiconductors that are needed. It's not really so and the cunning experimenter can use several dodges to get by with a very limited stock indeed. There are several project designers, for example, who manage to test out their ideas using no more than two transistor types, a 2N2219 and a 2N2905. These are silicon switching transistors which look exactly alike and differ only in polarity — the 2219 is NPN and the 2905 is PNP. How's it done? Read on.

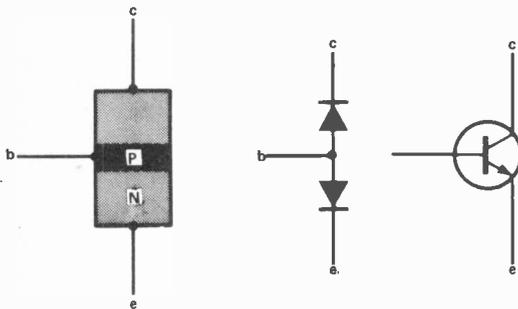


Fig. 1. Structure of a transistor. (a) The semiconductor sandwich, (b) connection of two diodes which gives the same readings when connected to resistance meters, (c) symbol (NPN illustrated).

Basically, a transistor is constructed like two back-to-back diodes (Fig. 1), the difference being that both diodes form part of one crystal. We can, therefore, use a transistor to substitute as a diode. Which bit do we use? The collector and base terminals form one diode, a high reverse voltage diode which will pass quite large currents. Transistors of the 2N2219 variety will dissipate 0.8W at the collector, so that their collector base diodes can be quite happily used in bridge rectifier circuits for up to 30 V supplies, keeping the emitter open circuit or shorted to the base.

A Bit Of Bias

The base-emitter diode, on the other hand, is much more of a small signal diode, more suited to low current, low

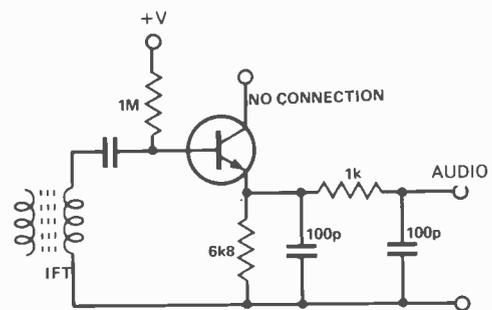


Fig. 2. Using the base/emitter junction of a transistor as a detector diode. The 1M resistor keeps the junction slightly conducting, so increasing the sensitivity.

voltage work. One minor drawback is that you can't approach the small forward voltage of a germanium diode, but there's no law to say you can't apply a bit of bias, as in Fig. 2. This makes the base emitter diode into a good, sensitive detector. While we're on the subject of detectors, why not be different and use an emitter follower detector, as in Fig. 3? It's a darn sight more linear than a straightforward diode, and has a low output impedance and high input impedance as well.

The circuit is a simple one. A capacitor is connected across the emitter resistor of an emitter follower. The size of the capacitor should be such that the time constant of emitter resistor x capacitor is small compared to the time of an audio wave but large compared to the time of the

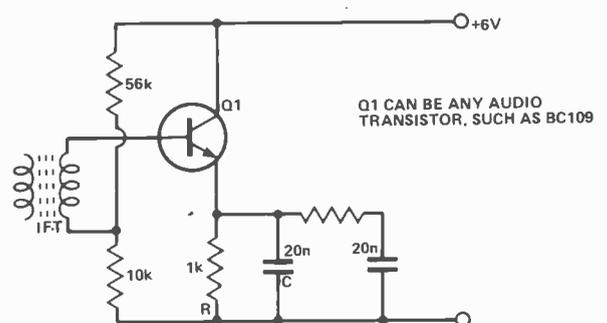


Fig. 3. The emitter-follower detector.

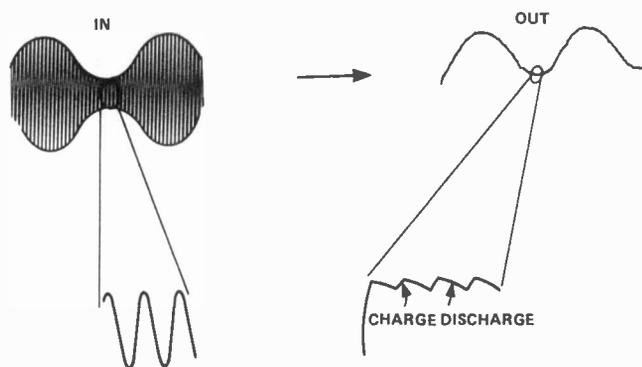


Fig. 4. Action of the emitter-follower detector. Capacitor C is charged by the current through Q1 during the positive part of a cycle, but can discharge only slowly through R. The voltage across C follows audio frequency changes, but not radio frequency changes.

RF wave. Time constants of 10 to 100 μ s are usually suitable for AM radio circuits, so that a typical circuit might use 1k emitter resistance and 20n (that's 0.02 μ) capacitance. The action is also straightforward (Fig. 4). The positive RF wave makes the transistor conduct, so that C1 charges up to the positive peak of the wave. Because the time constant is large compared to the time of one RF wave, though, the voltage at the emitter drops only slightly as the wave goes through the remainder of its cycle and the transistor cuts off until around the peak of the next RF wave. The AF modulation, however, makes the peaks of the RF signal occur at different voltages, tracing out the audio waveform, so that the audio signal appears at the emitter, with very little trace of RF so that nothing much in the way of filtering is needed. The emitter-follower detector also has lower distortion than the conventional diode detector.

Transistor Zener

We're not finished with diodes, though. The base-emitter diode of most planar silicon transistors (and that means most 'modern' silicon transistors manufactured in the last 15 years) will act as a zener diode. The circuit of Fig. 5 shows how this can be checked. The voltage across the base-emitter junction will stabilise at anything from 7 V to 18 V, depending on the construction of the transistor, when power is applied. You don't need to keep a drawer full of zener diodes, just make these 2N2219's work for their living.

This zener diode action, incidentally, can cause some odd effects in circuits where a negative pulse is applied

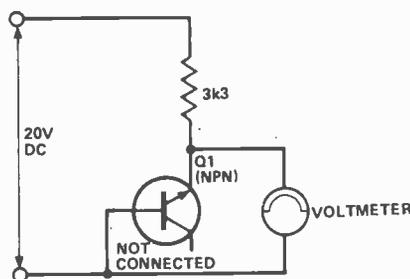


Fig. 5. Checking the zener voltages of a silicon transistor.

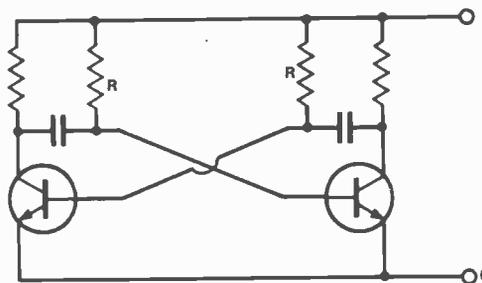


Fig. 6. Conventional multivibrator circuit.

to the base of a transistor. Multivibrator circuits, for example, operating on voltages greater than 7 V, suffer from this. Theory says that the time period of the MV is $1.4CR$ (Fig. 6), because the capacitor always charges up from $-V$ to about $0V$ whatever the value of V . The reason is that when one transistor conducts its collector voltage shoots down by about V volts, and the capacitor coupling to the next base makes that base move from about $0V$ to $-V$. Since the transistor switches on again at just above $0V$, the capacitor always charges to half way between $-V$ and $+V$, no matter what the value of V is. That theory doesn't apply if the base-emitter junction zeners, because the voltage at the base will be clipped by the zener action. We find therefore, that the frequency of the MV increases as we increase the voltage, whatever the books say about it!

Want a stable value of low voltage? Try the circuits of Fig. 7. The voltage between collector and emitter of a transistor is always low when the transistor is bottomed, with the base positive (NPN transistor) and a load resistor limiting the amount of current that can pass between collector and emitter. With the transistor the conventional way round, the voltage between collector and emitter can go as low as 0.2 V, but even lower voltages can be obtained if the transistor is inverted, with the emitter connected through the load resistor to the positive line and the collector to the negative rail. This, for example, can be very useful for clamping circuits if a small DC 'offset' is needed, but care should be taken to keep the currents low. Transistors are much more easily damaged when they are operated this way round.

Paint-scraping Saves

A few circuits specify phototransistors, which aren't always easy to obtain and sometimes (shop around!) costly. Now there isn't much you can do to make

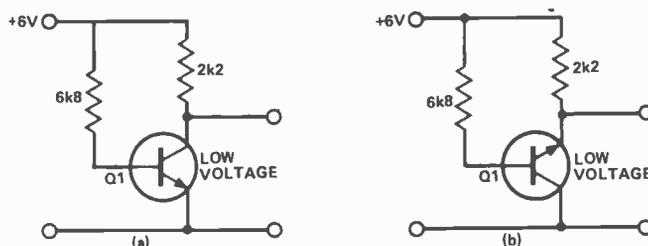


Fig. 7. Obtaining very low stabilised voltages (a) conventional method, (b) using an 'inverted' transistor for lower voltage output.

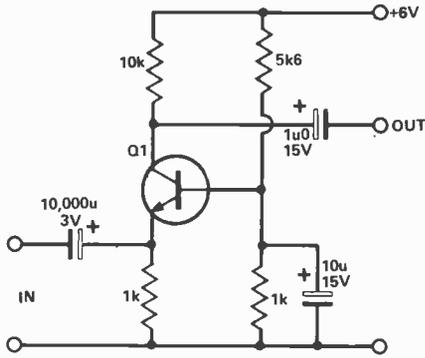


Fig. 8. Using a common-base amplifier. Note that the input capacitor must be of a very large value.

phototransistors out of modern silicon metal or plastic cased transistors, because light just doesn't pass through these materials. The old germanium transistors, like the OC72 series, were packaged in glass cases, however, and the cases then painted over. The reason for the paint is simple — any transistor junction will act as a light detector, so that a transistor in a glass case will be a phototransistor unless it is covered up! Scrape the paint off, and you have the phototransistor you need. Since old OC72's can often be got in lots at pennies, each, and the photo version, the OCP72, seems to fetch nearly a pound, it certainly saves money to do some paint scraping!

Ever want to drive a transistor amplifier from a really low-impedance source? There aren't many home-made ribbon microphones around, but a moving coil loudspeaker makes a useful microphone apart from its low resistance of 3R or so. Remedy here is to make use of the first type of transistor amplifying circuit that was ever used, the common-base circuit. In a common-base amplifier, the base is decoupled, with no signal input. The signal is fed into the emitter circuit, and taken in the usual way from the collector, using capacitors to keep the bias voltages correct. Advantages? There's voltage gain for a start, but the main advantage is that the input resistance is very low, offering a better match to the low resistance of the 'microphone'. Incidentally, a transistor operated this way round will amplify and oscillate at higher frequencies than is usually possible in the normal (common emitter) configuration.

Phase Splitting

This is an example of using a transistor to match impedances, like a transformer. The other impedance —

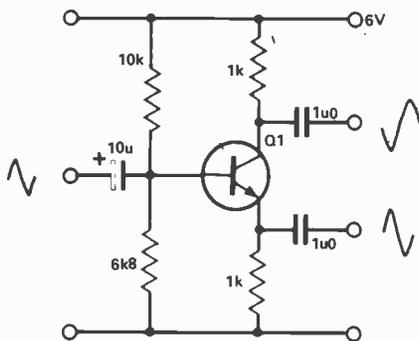


Fig. 9. The transistor phase-splitter.

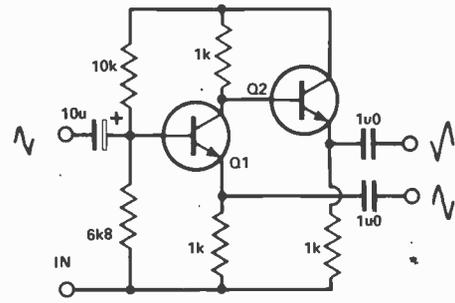


Fig. 10. Modified phase-splitter with equal output resistances.

transforming circuit is, of course, the well known emitter follower, with a high input impedance and low output impedance. If you need the phase splitter action of a transformer, but don't have a suitable transformer, don't get wound up, just try the circuit of Fig. 9. If you're driving signals into a low impedance of course, you may find that the difference between the impedance level at the collector and at the emitter causes bother (the impedance at the collector is equal to the collector load resistor, the impedance at the emitter is only a few ohms; roughly 25 ohms when the steady bias current is 1mA). In that case, another transistor added to the circuit equalises things a bit, as shown in Fig. 10.

You might think that the possibilities of the transistor were about exhausted; but we've only been using them, in ones so far. When we start using transistors in twos and threes, we can substitute a lot more devices.

Unijunctions

Unijunctions, for example. Who's got a set of unijunctions around? Useful little devices. In circuits like Fig. 11 they provide an oscillator which gives a pulse output ideal for firing thyristors. The wily experimenter doesn't worry if the unijunction drawer is empty, though. He connects up the circuit of Fig. 12, which does pretty well all that a single-package unijunction will do, with the additional advantage that the firing voltage can be variable.

The action is like this. Point B, where the base of Q1 is connected to the collector of Q2 is connected to a potential divider, resistors R1 and R2. For most applications, these resistors will be equal, using (typically) 47k to 10k values. The circuit will pass no current while the voltage at point A, the emitter of Q1, is less than the voltage at point B, because Q1 is cut off (PNP,

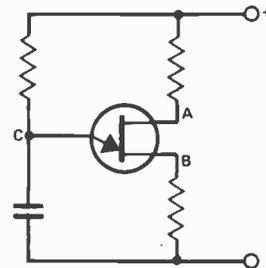


Fig. 11. A unijunction oscillator. A negative pulse is obtained at A, a positive pulse at B, and sawtooth at C.

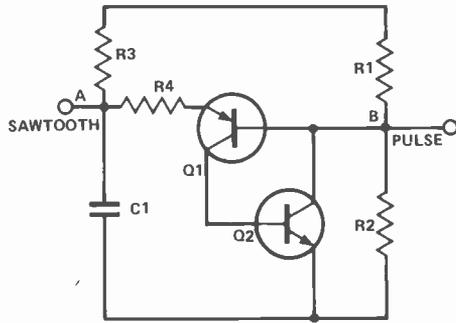


Fig. 12. A two-transistor equivalent of a unijunction.

remember), and it holds Q2 cut off as well. When point A reaches a voltage around 0.5 V higher than the voltage at point B, though, Q1 starts to conduct, and current starts to flow into the base of Q2, causing Q2 also to conduct. With Q2 conducting, the extra voltage drop across R1 causes the voltage at B to drop, dragging the voltage of point A with it. If the base current of Q1, is likely to be exceeded (as usually happens if there is a capacitor connected to point A), a small series resistor R4 (about 100R) is a good protective system. Note, by the way, that when a unijunction or this replacement is used in a timebase circuit, the value of the charging resistor, R3, must not be too low, otherwise the circuit can 'stick', not oscillating. A value of around 47k is usually regarded as a safe minimum, so that if the frequency is controlled by a variable, a 47k should be connected in series. The firing point of the unijunction substitute can be varied to some extent by making the voltage at point B variable, using a preset potentiometer, in place of R1, R2.

There is a limit, however, to the voltage range which can be used — if the voltage is too high, the circuit may not fire, if it's too low the circuit passes current continuously.

Another advantage, of course, of the circuit of Fig. 12 is that power transistors can be used. In this way, higher current pulses can be obtained than we can get from small unijunctions.

DIY Thyristor

You don't have to be stuck for lack of a thyristor, either. The circuit of Fig. 13 simulates the action of a thyristor, with the anode, cathode and gate connections as marked. With the 'gate' at cathode voltage, Q2 is shut off, so that its collector voltage is high. With the collector voltage of Q2 high, the base voltage of Q1 is also high. Since Q1 is a PNP type, having the base high means

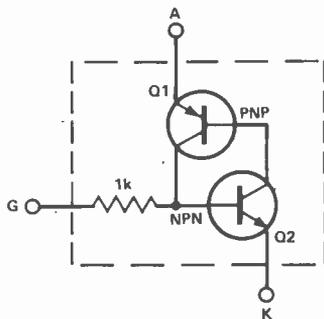


Fig. 13. Using two transistors in place of a thyristor.

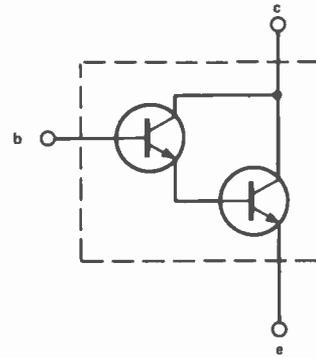


Fig. 14. The Darlington pair circuit — this behaves like one single transistor with a very high value of current gain.

keeping Q1 shut off. Now when the 'gate' lead is made more positive, so that Q2 starts to draw current, the current through the collector of Q2 is drawn through the base of Q1, ensuring that Q1 conducts. This in turn means that the base of Q2 is connected to the positive supply through the collector of Q1, keeping the pair of transistors switched on.

Don't expect to replace a large thyristor with this circuit, because the current between 'anode' and 'cathode' all passes through the base-emitter junctions. For medium-power transistors, such as the 2N2219 or BFY50 the absolute maximum base current is about 100 mA, and 50 mA is a safer limit. Power transistors such as the BD131, BD132 will stand up to 0.5 A through the base-emitter junction. The circuit will, incidentally, switch off if a negative pulse is applied to the 'gate' from a low impedance. In this respect, the circuit is similar to that of a small thyristor, most of which can also be switched off in the same way.

Changing Bias

Transistors in bunches can also be used to solve awkward problems. Suppose you want to substitute a transistor with another type which needs much more bias current. One way round, of course, is to adjust all the bias circuits. A much easier method is to make use of two transistors, with one emitter driving the base of the

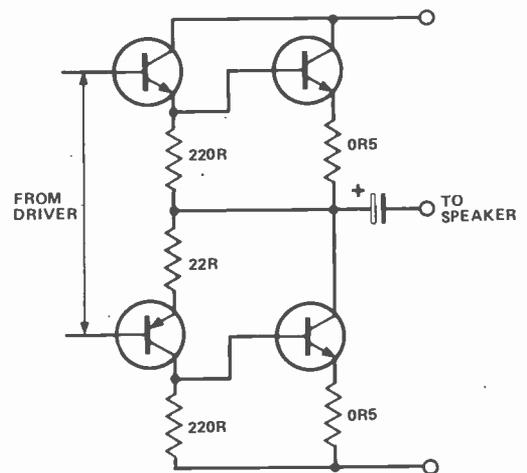


Fig. 15. A quasi-complementary output stage. The power transistors can both be NPN types.

next (Fig. 14). If the two share the same collector lead, this circuit is called the Darlington pair, but if the collector of the first transistor is returned directly to the power supply the circuit is simply an emitter follower feeding a common emitter amplifier. The difference between the two is that in the Darlington pair circuit, signal can feedback from the collector of Q2 through Q1 to the base of Q2, so reducing the voltage gain of the circuit considerably.

A two-transistor circuit can also be used to 'create' a PNP power transistor from an NPN one. The circuit uses a PNP medium power transistor (such as the 2N2905) coupled to the NPN power transistor, so that the combination behaves like a PNP power transistor. Like all two-transistor circuits, though, there is a penalty in the form of a change in DC levels. When two NPN's (or 2 PNP's) are coupled in a Darlington circuit, the voltage between the first base and the second emitter is more than 1V, when the circuit is correctly biased, instead of the 0.55 - 0.6 V we assume for a single transistor. For the PNP - NPN pair, the voltage is less than that for a single transistor - the base voltage of the power transistor will be 0.7 V or so above its emitter voltage, but the base voltage of the PNP transistor will be 0.6 V or so less, so that the DC input to the base of the PNP transistor is very close to the DC emitter voltage of the NPN one. The base-emitter voltages of these two will never be identical because the NPN power transistor will always be passing a much larger current than the PNP transistor.

Tapehead Drivers

We're still not finished with the two-transistor arrange-

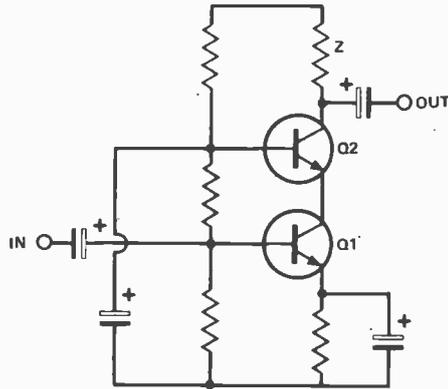


Fig. 16. A cascade stage. The load Z can be a tuned circuit or a high-value resistor providing the bias resistors are chosen to suit.

ments. Fig. 16 shows what is called a cascade circuit, with a common-emitter transistor Q1 driving a common-base stage Q2 directly coupled to it. This arrangement can also be treated as if it were one single transistor with the high gain of a common emitter transistor and the very high output resistance of a common-base transistor. It's an ideal arrangement for driving tuned circuits (because the high output resistance places very little load on the circuit) or tapeheads (because the high output resistance can ensure that the current signal into the tapehead is almost constant over a wide frequency range).

Circuits such as these described here make full use of transistors, exploiting more of their potential than the usual run of common emitter and emitter follower circuits. Make them work harder!

ETI

<p>MOTORS 1.5 to 12vdc Model Motors, 20p. Sub. Min. "Big Inch" Motors, 115vac 3rpm 30p. 12vdc 5 pole model motors 35p. 8 track 12vdc motors £1.25. Cassette motors vdc ac equip. 65p. Grandest general motor, 115vac 4rpm 95p. Smilba clock motor, synch. 240vac 1 rev. per hour. 65p.</p>	<p>SEMICONDUCTORS, All test spec. devices. 741 0 pin DIL 6 for £1.00. No 555 Timers 25p. TRANSISTORS IC's 50p. 7418 buffer board 25p. LM330 80p. Z844 radio IC's 75p. 2N3055 transistors 30p each. TL3095 Alpha numerical display £2.50. Miniature LDRS (same spec. as OPN12) 30p.</p>	<p>TOSHIBA LEADS, 0.2" green 13p. 0.2" green diffused 14p. 0.2" green flat top 14p. 0.2" Clear 17p.</p>	<p>MULTIMETERS big price reductions on pocket size meters. Model KRT100 1,000 ohms per volt, mirror scale, range selector switch, 1.000V AC/DC, 100Kcrac, 150ma DC current £4.85. Model KRT101 same spec. as the KRT100 but range selection is via prof insertion. £3.75. CONTINUITY TESTER. Tabular unit with probe and croc. fly lead. £1.35 with bat.</p>	<p>TRANSFORMERS, All 240vac primary (postage per transformer is shown in brackets after price. MINIATURE RANGE 6-0-6v 100ma, 9-0-9v 75ma, 12-0-12 50ma all 75p each (15p). 12-0-12 100ma 95p (15p). 0-6-0-6v 200ma £1.10 (20p). 0-4-0-4v 200ma these have no fixing bracket 85p (15p). 12v 500ma 95p (22p) 12v2A £2.25 (45p) 12v4A £2.75 (45p) 15-0-15v 1A £2.10 (45p). 30-0-30v 1A £2.75 (54p). 20-0-20v 2A £3.50 (54p). 0-12-12-20-24-30v 2 amp £4.50 (54p) 20v 2.5a £2.20 (54p).</p>	<p>ALUMINIUM PROJECT BOXES, 10 3.W.A. with fitted lid and screws. AD1 3Wx2.5x1.5 45p. AD2 4x2x1.5 55p. AD3 4x3x2.5 55p. AD4 6x4x2.5 65p. AD5 6x4x2.5 65p. AD6 8x4x2.5 65p. AD7 8x4x2.5 65p. AD8 8x4x2.5 65p.</p>
<p>BUZZERS, Miniature solid state buzzers, 33 x 17 x 15mm white plastic case, output at 3 volt 70db (approx low consumption only 15ma). 4 voltages available 6-9-12 or 24 vdc 75p each. LOUD 12v Buzzer, Cream plastic case, 50mm diam x 30mm high, 60p. 6PDC open type buzzer, adjustable, works 6-12vdc 25p. 8 tone tone tone, 12v B.C. Horn type, 125mm diameter, emits high pitched wailing note of varying frequency. £7.95.</p>	<p>TOOLS, SOLDER SUCKER, Plunger type, high suction, left hand nozzle, £4.75, spare nozzles 65p each. Good quality side cutters, insulated handles 5" £1.35. Good quality snub nose pliers, insulated handles, 5" £1.35. Antex Model C15 wall soldering iron 240vac £3.60. Antex Model C17 wall soldering iron, 240vac £3.60. Antex X25 25 watt soldering iron 240vac £3.60. Antex ST3 stands (suits all above models) £1.40. Antex heat shields 12p each. Servisol Solder Mop 45p each. Neon tester screwdrivers 8" long 40p. Miyama IC test clip, 16 pin £1.75.</p>	<p>10-PIECE PRECISION TOOL KIT, in plastic blinged case, consists of 5 spanners, 4x2/8mm, 5 nut drivers 2x5mm, 3 small screwdrivers, 2 Phillips drivers, 1 set, 3 Allen Keys £3.20.</p>	<p>TAPE HEADS, Mono cassette £1.80. Stereo Cassette £3.40. Standard 8 track stereo £1.75. 8SA 8001300 1/4 track 50p. 8SA 80090 1/4 track £1.95. TD10 dual head assembly 2 heads both 1/4 track R/P with built in erase £1.20.</p>	<p>TRICAC XENON PULSE TRANSFORMERS, 1 (GPO type) 30p. 1 (types 1 sub. min. pcb mounting 60p).</p>	<p>DIODES, M4001 10 for 30p. M4004 10 for 45p. M4007 10 for 50p. B1127 10 for 75p. IN514 (numbered) 100 for £2.25. 50 volt 1 amp Bridge Rect. 10p.</p>
<p>SPECIAL OFFER SEMICONDUCTORS, Plastic voltage regulators, 1 amp new reduced in price 7805, 7812, 7815, 7824 all at 75p each, 7805, 7812, 7815, 7824 all 80p each. 723 14-pin DIL rags 30p each.</p>	<p>MICROPHONES, ECM105, condenser, omni directional, 500 ohms, on/off switch £2.95. EM506 Condenser, cardioid, omni directional, 600ohms or 50k, heavy chromed copper case £12.95. Dynamic stick Mike, 5,000 ohms, on/off switch, fitted with standard jack £2.95. EM104 Sub. min. 10 pin microphones, condenser, 1,800 ohms imp., 50-15kHZ uses dual aid battery (supplied) £5.25. STANJAH cassette mixer 200 ohm imp., fitted with 2.5/3.5mm jacks, on/off switch, £1.25. DYNAMIC P.A. Microphone, suitable for mobile use, hand held with thumb switch, carry lead, 50k imp, £3.40. CRYSTAL INSERTS, 35x10mm 45p each.</p>	<p>SWITCHES, 50p. Min. Toggle, SPST, (8x5x7mm) 50p. DPDT (8x7x7) 60p. DPDT Centre off (12x11x9mm) 75p.</p>	<p>ROCKER SWITCHES, 2 amp SPST single pole fixing, various colours (red, black, yellow, green, white) 19p each. 250vac 6 amp white rocker, 21x15x13mm 17p each.</p>	<p>PROJECT BOXES, Sturdy ABS black plastic boxes with brass inserts and lid, 75x56x35mm 50p 95x7x35mm 60p 115x63x37mm 70p.</p>	<p>SPECIAL OFFER 5-piece jewellers screwdriver set, with individual handles, supplied in plastic wallet only 95p per set.</p>
<p>FETS Union carbide N channel similar to 2N3819 15p. 2N140 or 8F061 40p each. MC203 dual matched pair of single gate mosfets in one case 40p. 2N5063 plastic (1092) acts 100V 800MA 15p each. 81504 Opto Isolator, 4 lead infra red led to photocell 25p each.</p>	<p>SEND G.S. ETCHING KIT SYSTEM, Unique idea for etching P.C. boards, all done in a metal bag, supplied with everything needed for etching boards, will etch approximately 1600cm of copper board, £1.90.</p>	<p>PUSH SWITCHES 16x6mm, red top, push to make 14p each, push on break version (black top) 18p each.</p>	<p>RELAYS, Clear Eltel sub. min. relay 10x10mm 2 pole c/o, 1.250 coil new 75p. Miniature encapsulated reed relay, 0.1 matrix mounting, single make operated on 12vdc 50p. Conventional series, sealed plastic case type 24vdc, 3 pole c/o 5 amp contacts, new 85p. 230vac Sealed Relay, 3 pole 5 amp contacts, ex. equipment, 11-pin base, 60p each. Metal Cased reed relay 50x45x17mm, has 4 heavy duty make reed inserts, operates on 12vdc 35p each.</p>	<p>VERO HAND HELD BOX White ABS, 2.4"x3.7" tapered, with screws 65p each.</p>	<p>MURATA TRANSDUCERS, REC/SENDER, MA401 40KHZ £3.25 pair.</p>
<p>NEW STOCK ITEM - We are now stocking Exgo mini hand held drills, these are a precision British made tool, ideal for P.C. board drilling, model makers etc. They operate on 12VDC. Drill only: £6.95. Drill kit supplied in plastic blinged case, with drill and 21 accessories, drills, sanders, reamers, buffers etc, complete kit only £13.50.</p>	<p>STOP PRESS, New arrivals, 12 volt car stereo meters with polley only 55p each. 8 track stereo playback heads only 75p each. Car radio boards, complete chassis with 6 transistors FS chassis, etc., new but no info, 75p each. Car radio REF/IF and audio preamp boards, 2 transistors, LM302 IC, trimmers, IF etc., new but no info, 65p each.</p>	<p>SLIDE SWITCHES all DPDT 15x8x12mm 12p, 16x11x9mm 12p, 22x13x8mm 12p, 22x12x8 centre off 13p. Multipole slider, double action (12 tags) 25x5x11mm 24p.</p>	<p>POWER SUPPLIES, Switched type plugs into a 13 amp socket, has 3-4-5-6-7.5 and 0 volts D.C. out at either 100 or 400ma switchable £3.25. MC2448 stabilised power supply 3-6-7.5-9vdc at 400ma, has polarity reversing and on off switch and is fully regulated to give exact voltage from no load to maximum current £2.25.</p>	<p>VERO POTTING PLASTIC Boxes with lid and screws 70x50x20mm, white or black, 40p each.</p>	<p>TELEPHONE PKCK UP COM. Sucker type with lead and 3.5mm jack 55p.</p>

Terms. Cash with order (official orders welcomed from colleges etc) 30p postage please unless otherwise shown. VAT inclusive prices. S.A.E. for new illustrated lists.

PROGRESSIVE RADIO
31 CHEAPSIDE, LIVERPOOL L2 2JD

ETIPRINTS

ETIPRINTS are a fast new aid for producing high quality printed circuit boards. Each ETIPRINTS sheet contains a set of etch resistant rub down transfers of the printed circuit board designs for several of our projects.

ETIPRINTS are made from our original artwork ensuring a neat and accurate board. We thought ETIPRINTS were such a good idea that we have patented the system (patent numbers 1445171 and 1445172).


PARTS LIST

Shown below is the listing for the last year's ETIPRINTS.

Earlier sheets are available, ring Tim Salmon for details.

007	Star Trek Radio CD Ignition CCD Phaser White Line Follower	May 78 May 78 May 78 April 78	013	Amplifier Module Amplifier PSU Equaliser Equaliser PSU	Book Six	020	Digital Tacho Module Digital Dial	Jan 79 Jan 79 Jan 79
008	Tank Battle Helping Hand	May 78	014	Skeet Game Sweep Oscillator Burglar Alarm GSR Monitor	Project Book Six	021	Tape Slide Synch Tape Noise Limiter Light Tacho	Feb 79
009	AM / FM Radio Bridge Oscillator CMOS Stars & Dots	June 78	015	UFO Detector Torch Finder (twice) Etiwet (twice)	July 78 July 78 Aug 78	022	Logic Trigger Power Meter Headlight Delay (x2)	Mar 79
010	Bench Amplifier Freezer Alarm Marker Generator LED Dice Watchdog (2 PCBs) Stars & Dots PSU	Project Book Six	016	Stac Timer Xhatch Gen Wheel of Fortune	Sept 78	023	Click Eliminator Guitar Effects Unit (2 boards)	April 79
011	Noise Generator General Preamp Flash Trigger Compander Active Crossover (2 PCBs)	Project Book Six	017	Complex Sound Gen Tele Bell Extender Power Bulge	Oct 78	023A	Wind Speed Indicator	April 79
012	Disco Lightshow Stereo Simulator Digital Thermometer	Project Book Six	018	RF Power Meter Proximity Switch Audio Oscillator (2)	Oct 78 Oct 78 Nov 78	024A	Ambush (Boards 2 & 3) Car Immobiliser	April 79 May 79
			019	Car Alarm (2) Wine Temp (2) Curve Tracer	Dec 78 Dec 78 Dec 78	024B	Ambush (Board 1) Headphone Amplifier Double Die	May 79
						025	Metronome Mains Seeker Triton 8K Eprom Card	June 79
						026	Motor Speed Controller (2 Boards For Controller) Battery Indicator	July 79

HOW IT WORKS

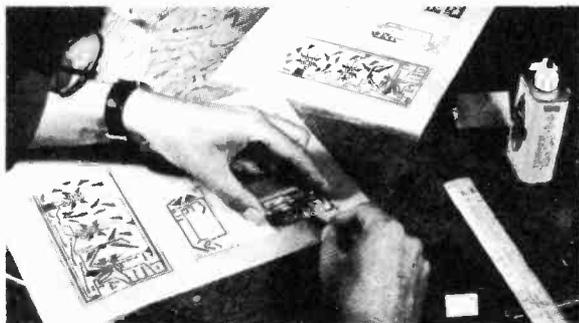

Lay down the ETIPRINT and rub over with a soft pencil until the pattern is transferred to the board. Peel off the backing sheet carefully making sure that the resist has transferred. If you've been a bit careless there's even a 'repair kit' on the sheet to correct any breaks!

BUY LINES

ORDER TODAY

Send a cheque or P.O. (payable to ETI Magazine) to:

ETI PRINT, ETI MAGAZINE
145 Charing Cross Road, London WC2H 0EE

80p

INC P & P

ELECTRONICS TODAY INTERNATIONAL — AUGUST 1979

TELETEXT SYSTEM

PART TWO: in this concluding part we give full constructional details for this superb design from GMT Electronics.

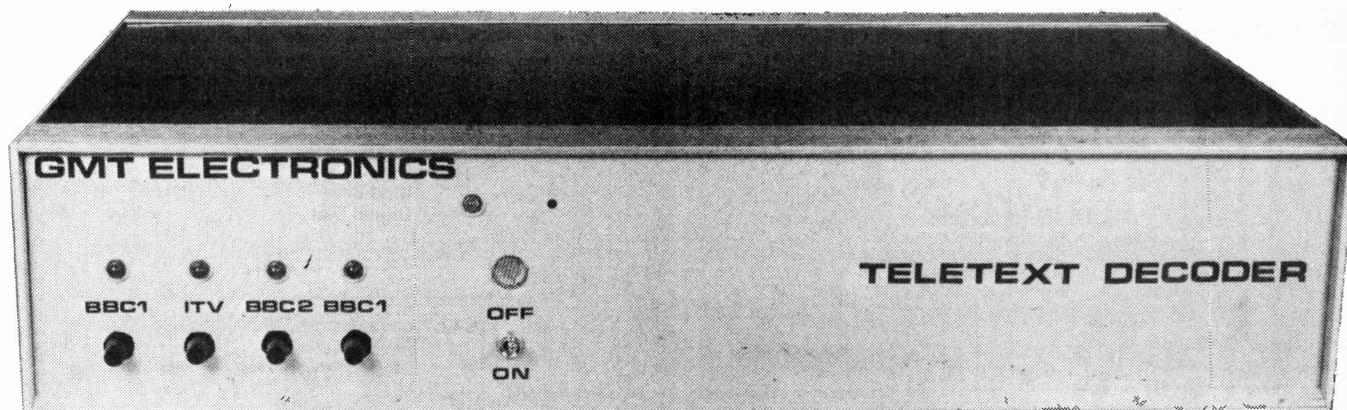


Fig. 1. Board two overlay.

Since we published the first part of their design last month, GMT have made some improvements to the kit for the Teletext decoder.

Three main changes are a combining of boards three and four into one. Effectively board four has ceased to exist! This simplifies construction still further and has our endorsement. We are republishing the combined circuits here to make things clear.


Construction

Putting together the unit should be very straightforward. The PCBs should be carefully assembled, following the overlays shown here. Check IC orientation especially closely as that chip set is very expensive to blow just because you didn't want to spend five more minutes doing that boring bit of re-checking.

When completed the boards should be interconnected following the wiring schedule given in this article. Check this carefully also.

Setting Up

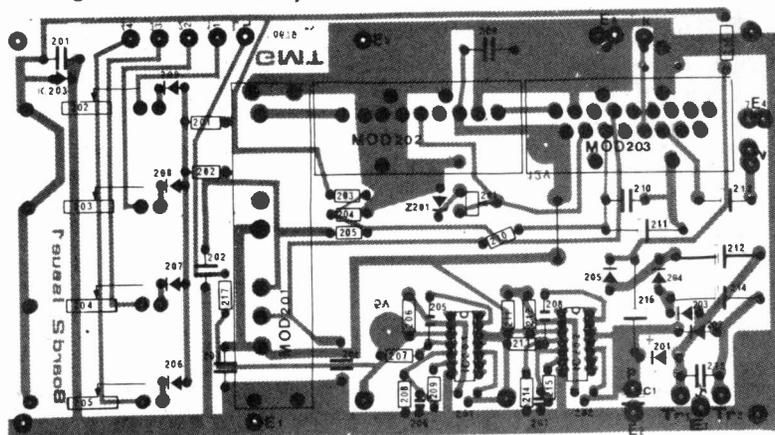Once the boards are assembled, follow the setting up procedure given in last month's article to complete the unit. It is worth remembering that to be sure of a good Teletext picture, you need a strong signal at the input. In areas of poor reception it is well worth investing in that better aerial you never got 'round to getting. . . .



Board Two

RESISTORS all 1/4W 5% unless specified

R201	150k
R202, 203, 204	47k
R205	1M5
R206, 211, 212	1R0 1/4 watt
R207, 213	4k7
R208	5k1
R209	2k2
R210	120R
R214	6k8
R215	2k7
R216	10k 1/2 watt
R217	1k0

POTENTIOMETERS

RV201	2k2 min. preset
horizontal	
RV202-205	100k VPN

CAPACITORS

C201-204, 209, 210, 215	100n polyester
C205, 208	470p ceramic

PARTS LIST

C206, 207	22u 16V tantalum
C211	220u 16V elec-
	trolytic
C212	100u 40V elec-
	trolytic
C213	1u0 63V electrolytic
C214	100u 25V elec-
	trolytic
C216	47u 63V electrolytic

SEMICONDUCTORS

IC201, 202	LM723CN
IC203	TAA550
Q201, 202	TLP31
D201-205	1N4001
D206-209	1N4148
ZD201	BZY88C3V6

MISCELLANEOUS

MOD201	U321
MOD202	BY01910
MOD203	BY00905
PCB	

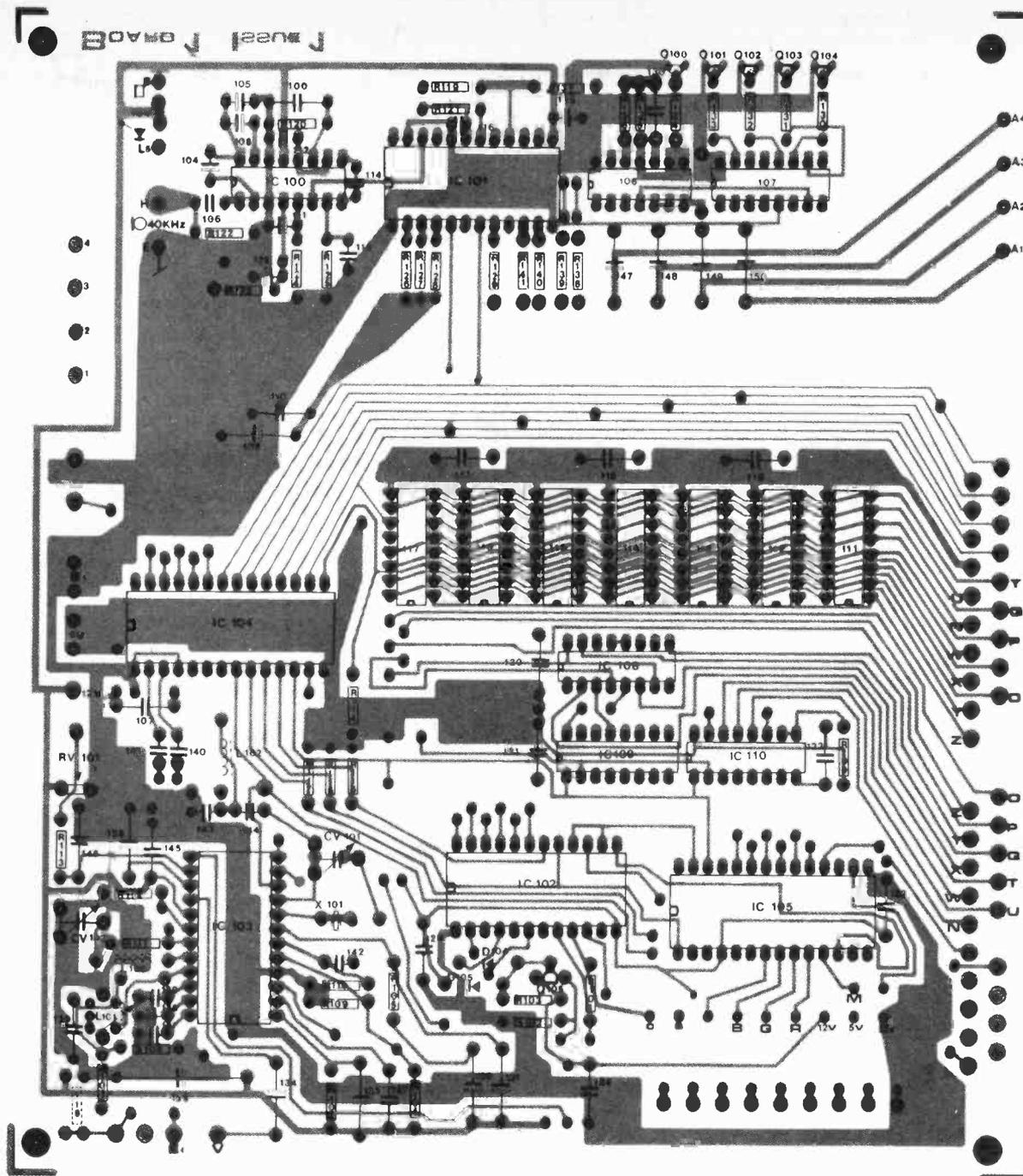


Fig. 2. Component overlay, board one.

PARTS LIST

Board One

RESISTORS (1/4W 5%)

R100, 102, 105, 118	1k
R101, 109, 122	6k8
R103, 126-129	10k
R104	47k
R106	100k
R107	680R
R108	1k5
R110	1k2
R113	33k
R119, 130-133	4k7
R120, 121	27k
R123	68k
R124	820k
R125	1M

CAPACITORS

C100-103, 117-130, 145	100n
------------------------	------

C104, 105, 109	6u8
C106	1n8
C107	470n
C108	4u7
C110	22n
C111	22u
C112, 144	10n
C113	560p
C114	390p
C115	
C116	27p
C131, 134, 136	1u0 63V
C132, 133	10u 25V
C135	100u
C137, 140, 141, 142	1n
C138	330p
C139	47p
C143	68p
C146	3n3
TC101, 102	5-65p trimmer

INDUCTORS

L100	33uH
L101	Clock coil
L102	10uH

SEMICONDUCTORS

IC100	TD81033
IC101-105	SAA5010-5050
IC106	HEF4001
IC107	HEF4017
IC108	74LS83
IC109-110	74LS161
IC111-117	2102
IC118	74LS11
IC100-Q103	BC548
Q104	BC148
D100-103	1N4148
D104, 105	BAW62

MISCELLANEOUS

X101	6MHz, PCB, IC sockets, mounting hardware
------	--

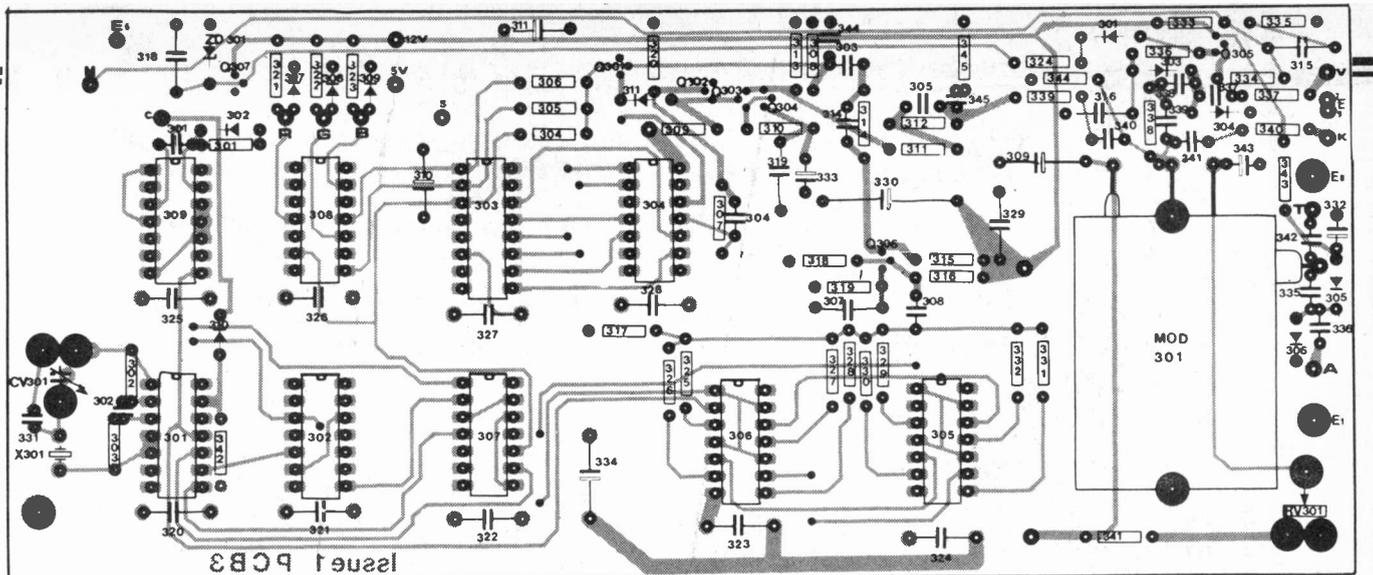


Fig. 3. Component overlay, board three.

BOARD INTERCONNECTION WIRING

FROM	LOCATION -BOARD	TO	LOCATION -BOARD	COLOUR	CABLE TYPE	COMMENTS
AE.SKT.	CHASSIS	E1	2	-	COAX	OUTER
AE.SKT.	CHASSIS	MOD 201	2	-	COAX	INNER
E2	2	-VE C1	CHASSIS	BLACK		
P	2	-VE C1	CHASSIS	RED		
E3	2	TR 1	CHASSIS	BLACK		INNER SEC TAGS
TR1	2	TR 1	CHASSIS			OUTER SEC TAGS
TR2	2	TR 1	CHASSIS			OUTER SEC TAGS
E4	2	E4	1	-	COAX	OUTER
V	2	V	1	-	COAX	INNER
E5	2	E5	1	BLACK		
E9	2	E9	3	-	COAX	OUTER
K	2	K	3	-	COAX	INNER
E7	2	E7	3	-	COAX	OUTER
V	2	V	3	-	COAX	INNER
E8	3	O/P SKT	CHASSIS	-	COAX	OUTER
T	3	O/P SKT	CHASSIS	-	COAX	INNER
E1	3	E1	1	-	COAX	OUTER
A	3	MOD 201	1	-	COAX	INNER
E8	1	E6	3	BLACK		
5V	2	5V	1	YELLOW		UNDER BOARD
12V	2	12V	1	PINK		UNDER BOARD
5V	1	5V	3	YELLOW		BY IC105
12V	1	12V	3	PINK		BY IC105
R	1	R	3	RED		BY IC105
G	1	G	3	GREEN		BY IC105
B	1	B	3	BLUE		BY IC105
S	1	S	3	GREY		BY IC105
C	1	C	3	BROWN		BY IC105
M	1	M	3	ORANGE		BY IC105
1	2	LED 1	CHASSIS			
2	1	LED 2	CHASSIS			
3	1	LED 3	CHASSIS			
4	1	LED 4	CHASSIS			
L	2	LED 1 to 4	CHASSIS			
O	1	O	1	WHITE		
P	1	P	1	WHITE		
Q	1	Q	1	WHITE		
T	1	T	1	WHITE		
U	1	U	1	WHITE		
N	1	N	1	WHITE		
W	1	W	1	WHITE		
X	1	X	1	WHITE		
Y	1	Y	1	WHITE		
Z	1	Z	1	WHITE		
B	1	*EARPIECE	CHASSIS			
L5	1	LED 5	CHASSIS			
H	1	TRANS-DUCER	CHASSIS			
E	1	TRANS-DUCER	CHASSIS	BLACK		TRANS-DUCER CASE
12V	1	*EARPIECE	CHASSIS			
12V	1	LED 5	CHASSIS	PINK		

PARTS LIST

Board Three

- RESISTORS all 1/4 W 5%
- R301, 344 5k6
- R302, 303 680R
- R304, 307, 320-324, 334 3k3
- R305 1k8
- R306, 314, 316, 343 10k
- R308 820R
- R309, 315, 336, 341 1k0
- R310 220R
- R311, 325 68R
- R312, 318 4k7
- R313, 317 56R
- R319 470R
- R326, 331, 332 10R
- R327, 330 180R
- R328, 335, 340 100R
- R329 150R
- R333 18k
- R337 6k8
- R338, 339 2k2
- R342 47k
- POTENTIOMETER
- RV301 470R min. preset horizontal
- CAPACITORS
- C301 2n2 ceramic
- C302, 304, 308, 314, 339 82p ceramic
- C303 56p ceramic
- C305, 341, 342 27p ceramic
- C307, 315, 316, 318-329 100n polyester
- C309, 310, 334 33u 16V electrolytic
- C311 10u 25V electrolytic
- C331 18p ceramic
- C332, 337, 338, 340, 343 6u8 25V tantalum
- C335, 336 1p8 ceramic
- Note C319-329 are decoupling components and are not shown on the circuit diagram.
- VARIABLE CAPACITOR
- CV301 22p



SEMICONDUCTORS

- IC301 74S04
- IC302 74S74
- IC303 74LS138
- IC304 7400
- IC305, 306, 308 7408
- IC307 7486
- IC309 7474
- Q301, 304 BC558
- Q302, 303, 305,

- 307 BC548
- Q306 BSX20
- D301-311 1N4148
- Z D 3 0 1 B Z Y 8 8 / BZX70C5V6

MISCELLANEOUS

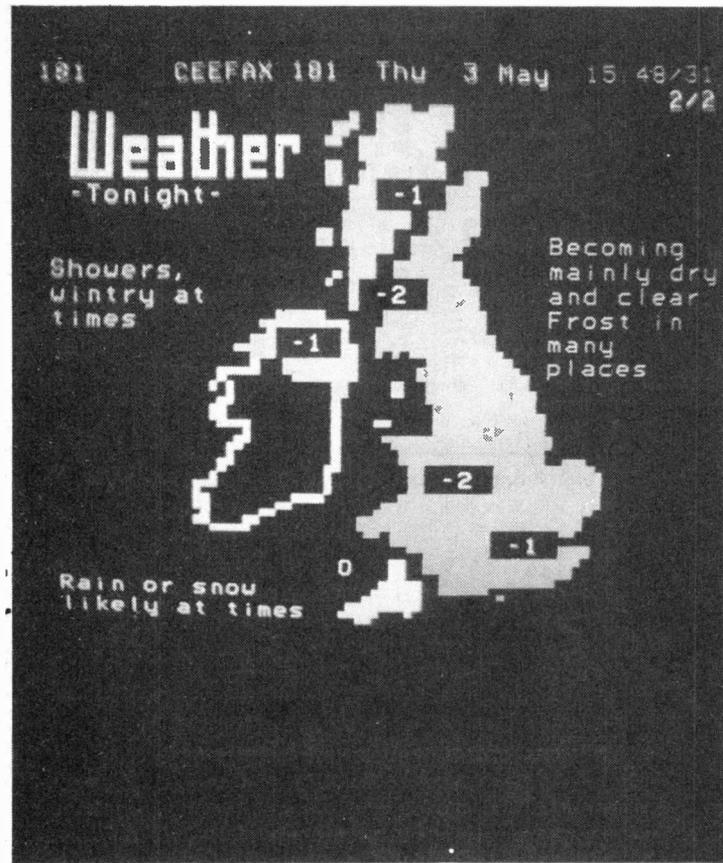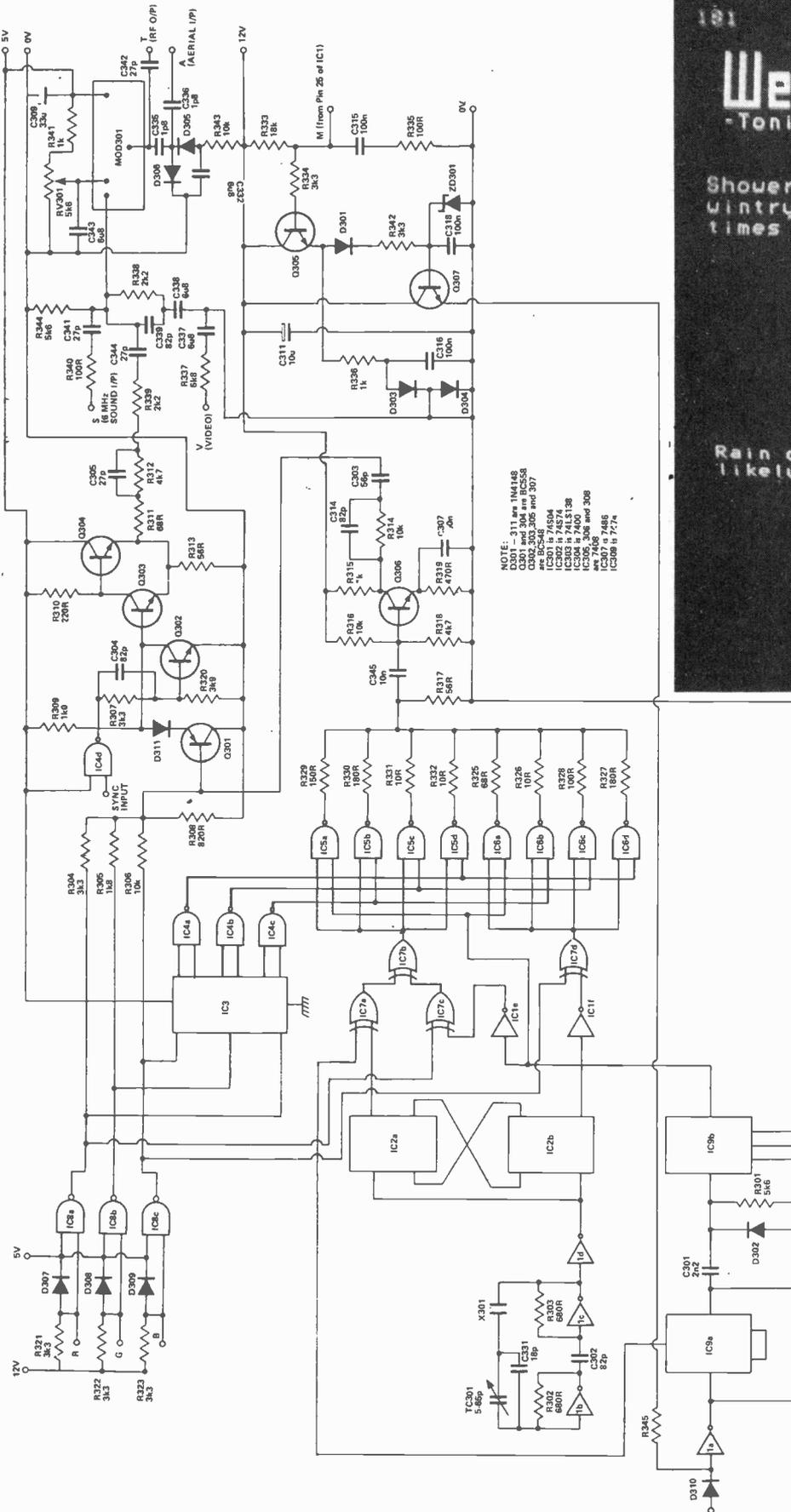- X301 17.73447 MHz
- MOD301 UM1231 Astec
- PCB



Above: Find out when it is supposed to rain. All you need is Teletext!

Fig. 4. (Left) The renumbered board three circuit.

BUYLINES

The designers of this project — GMT — have a complete kit of parts available. This includes all metalwork, PCBs and hardware. A manual is also included. Cost is £155 plus VAT (total £178 inc p&p).

As an alternative the teletext decoder board and control system is available separately at £125 for those who wish to wire into their own television.

PCBs and chip sets are available separately also — but are PoA.

See advert on page 6 for address.

Wide Range Oscillator..... Drunken Sailor
 House Alarm Digital Frequency Meter
 LCD Digital Multimeter..... Bench Supply
 LB Metal Locator..... Transcendent 2000
 CCD Phaser.... Poreh Light

ETI TOP PROJECTS

PROJECTS REPRINTED FROM

NO 7 electronics today £1.25

Light Dimmer..... Egg Timer
 Electronic Bongos.....
 ER11 Loudspeaker.....
 ETI Wet Plant Waterer.....
 Bass Enhancer..... 3 Bands

**ON
 SALE
 NOW!**

TRANSFORMERS

Panel Meters, Bridge Rectifiers, Power Supply Units
Multimeters - Semi Conductors - Timers - Safeloc

Minimum & Sub Miniature				50 VOLT (Pri: 220-240V) Sec: 0-19-25-33-40-50V			
Volts	Milli-amps	Ref. No.	Price £ P&P	Amps	Ref. No.	Price £ P&P	
3.0-3	200	238	2.25 .60	0.5	102	3.25	.80
0.5-0.6	1A 1A	212	2.65 .65	1.0	103	4.25	.95
9.0-9	100	13	1.95 .60	2.0	104	6.95	1.10
0.9-0.9	330 330	235	1.80 .60	3.0	105	8.25	1.10
0.8-9, 0.8-9	500 500	207	2.40 .65	4.0	106	10.50	1.20
0.8-9, 0.8-9	1A 1A	208	3.50 .65	6.0	107	14.75	1.40
0-15, 0-15	200 200	236	1.80 .60	8.0	118	19.85	1.60
0-20, 0-20	300 300	214	2.40 .80	10.0	119	23.75	2.10
20-12-0-12-20	700(DC)	221	3.15 .80	60 VOLT (Pri: 220-240) Sec: 0-24-30-40-48-60			
0-15-20, 0-15-20	1A 1A	206	4.25 .95	Amps	Ref. No.	Price £ P&P	
0-15-27, 0-15-27	500 500	203	3.70 .80	0.5	124	3.50	.80
0-15-27, 0-15-27	1A 1A	204	5.75 .95	1.0	126	5.25	.95
12 AND/OR 24 VOLT Pri: 220-240 Volts				2.0	127	7.20	1.10
	Amps	Price		3.0	125	10.75	1.20
12V	24V	Ref. No.	£ P&P	4.0	123	12.00	1.40
0.5	0.25	111	1.95 .65	5.0	40	13.80	1.50
1.0	0.5	213	2.40 .80	6.0	120	17.25	1.50
2	1	71	2.90 .80	AUTO TRANSFORMERS			
4	2	18	3.70 .80	Input/Output Tapped 0-115-210-240V			
6	3	70	5.25 .85	VA (Watts)	Ref. No.	Price £ P&P	
8	4	108	7.10 1.10	20	113	2.30	.80
10	5	72	7.90 1.10	75	64	3.75	.80
12	6	116	8.50 1.10	150	4	5.25	.95
16	8	17	10.50 1.20	Input/Output Tapped 0-115-210-220-240V			
20	10	115	13.50 1.40	300	53	8.85	1.10
30	15	187	18.50 1.40	500	67	10.50	1.40
60	30	226	33.00 1.70	1000	84	18.25	1.50
30 VOLT (Pri: 220-240V) Sec: 0-12-15-20-24-30V				Also 1500/2000/3000VA			
	Amps	Ref. No.	Price £ P&P	MAINS ISOLATING (Centre Tapped & Screened)			
0.5	112	2.50	.80	Pri: 120/240V			
1.0	79	3.25	.80	Sec: 120/240V			
2.0	3	5.25	.95	VA (Watts)	Ref. No.	Price £ P&P	
3.0	20	5.95	1.10	60	149	6.25	.95
4.0	21	6.25	1.10	100	150	7.25	1.20
5.0	51	9.25	1.10	200	151	10.75	1.20
6.0	117	10.75	1.10	250	152	12.95	1.40
8.0	88	14.00	1.40	350	153	15.95	1.50
10.0	89	16.25	1.40	1000	156	36.75	3.10

Please add VAT at 8%
Barclaycard and Access facilities available
Trade and Education Welcome


BAYDIS 7a William Street
Herne Bay, Kent
Herne Bay GA5486



TARGET ELECTRONICS

16 Cherry Lane, Bristol BS1 3NG
Telephone: 0272 421196

OFFICIAL ORDERS WELCOMED GVT/EDUCATIONAL DEPTS, ETC.

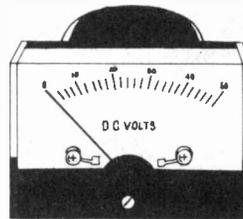

ME1 - ME22

Dims:- 50 x 45 x 33mm. Requires 38mm dia. cut-out

ref. cat. F.S.D.

ME29	MU50	0-50 UA	£3.80 each + VAT P&P 25p 10 Plus 10% discount
ME30	MU100	0-100 UA	
ME31	MU1	0-1 MA	
ME32	MUVU	"VU"	

Dims:- 60 x 47 x 33mm. Require 38mm dia. cut-out

ME1	T21	0-50 UA	£5.10 each + VAT P&P 25p 10 Plus 10% discount
ME2	T22	0-100 UA	
ME3	T23	0-500 UA	
ME4	T24	0-1 MA	
ME5	T25	0-5 MA	
ME6	T26	0-10 MA	
ME7	T27	0-50 MA	
ME8	T28	0-100 MA	
ME9	T29	0-500 MA	
ME10	T30	0-1 AMP	
ME10A	T31	0-2 AMP	
ME10B	T32	0-25 Volts	
ME11	T33	0-50v AC	
ME12	T34	0-300v AC	
ME13	T35	"S"	
ME14	T36	"VU"	
ME15	T40	50-0-50 UA	
ME16	T41	100-0-100 UA	
ME17	T42	500-0-500 UA	
ME17A	T43	0-30v DC	

APPOINTED DISTRIBUTORS

NASCOM 1 MICROPROCESSOR KITS

Z80 Microcomputer kit

Undoubtedly the finest value for money kit available anywhere. Fully socketed.

INTERFACE FOR:

- TV (UHF)
- TV Monitor
- Cassette
- Teletype
- 32k Ram expansion board

NOW AT THE NEW PRICE OF **£165**
+ VAT

Buffer Boards and Memory now available.

Callers welcome

Callers welcome



Tel. order welcome with Access and Barclaycard

BUILD YOUR OWN METAL DETECTOR TR/IB TR/VCO BFO...



Test equipment not required. Manuals for kits available at 25p each (refundable). UK prices post & VAT paid except where mentioned. Overseas: write for quote. Literature available: SAE Please.

Shadow TR/IB (illustrated). A true transmit receive/induction balance metal detector — uses the latest circuitry for maximum range and sensitivity. Speaker or phones. Pre-assembled search head with lightweight closed cell foam encapsulated coils for thermal insulation and water resistance. A very powerful machine!

Shadow TR/VCO. An advanced version of the above detector, use it as a sensitive TR/IB machine or switch to VCO mode when the depths achieved approach the maximum 'in air' range. Low power requirement: runs on standard 9 volt batteries. The most sophisticated detector available as a kit. Shadow TR/IB kit **£22.50** (£29.95 assembled). Shadow TR/VCO kit **£27.50** (£36.95 assembled).

Padded stereo headphones suitable for 'Shadow' detectors **£5.50**.

Designing your own detector? Then we can supply the (hard to obtain) hardware "shell" including fully adjustable shaft with handle, search head moulding with hinge assembly, special clips to mount your own control housing (any box is suitable), completely non-metallic: suitable for any type of detector (TR-PI-VLF-BFO etc.). Supplied undrilled as a kit with full instructions (as used on our Shadow range). Detector Shell kit **£8.50**.

Low cost BFO detector. 200mm (8") annular search head gives wide scan with easy pinpointing. Simple high efficiency circuit draws <3mA. Extra lightweight 300gms (10.5ozs) with battery. Very detailed construction manual: ideal as a first project. Absolutely everything supplied including pre-assembled search head, tuning coil and earpiece. ALT3 detector (kit) — **£13.95**. Padded high Z headphones for ALT3: **£4.90**.


Order by post or phone (24 hours) — for quickest delivery quote credit card number. Callers by appointment only please!

ALTEK

Dept. ETE, 1 Green Lane
Watton-on-Thames, Surrey
Phone (093 22) 44110

MICROSENSE

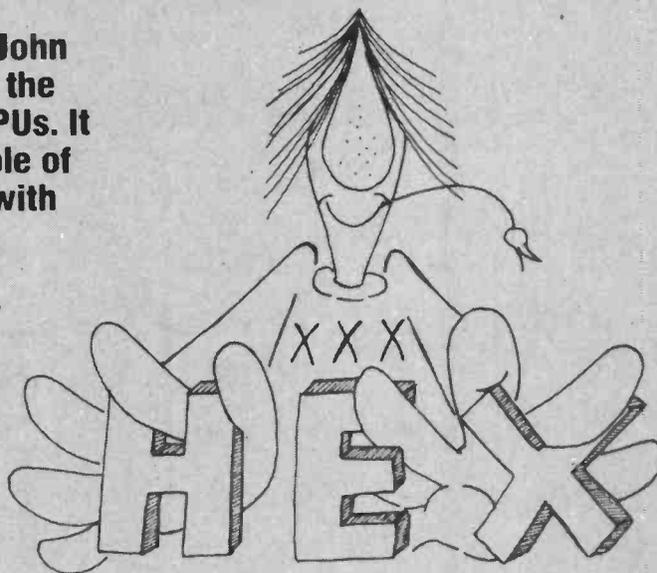PART ONE: a short series from John Miller Kirkpatrick designed to lead the reader gently into the realms of MPUs. It is designed to be of use to all people of all levels of knowledge. We begin with the hex system of counting . . .



Hexadecimal counting Systems

THE BINARY COUNTING system uses a set of 1s and 0s to indicate a particular number, in our example above 0101 0111 represents 87. Obviously it is faster to write 87 than it is to write 0101 0111 each time. It is not very easy to convert long binary numbers to decimal and vice versa, for example the binary number 1010 1010 1010 1010 represents the decimal number 43690 made up from:

1010	is	ten units of 1	=	10 or $2^4=8+2^1=2$	Total 10
1010 0000	is	ten tenths of 16	=	160 or $2^7=128+2^5=32$	Total 160
1010 0000 0000	is	ten units of 256	=	2560 = $29+2^{11}$	
1010 0000 0000 0000	is	ten units of 4096	=	4096 = $2^{13}+2^{15}$	thus the total
1010 1010 1010 1010	represents	the decimal 43690.			

Another way of showing this value is to write down one character for each set of four fingers. This is obvious for the values from 0-15 which can be expressed as a single character. The Binary decimal as new codes are —

0000=0 Written as 0.	0100=4 Written as 4.	1000= 8 Written as 8.	1100=12 Written as C.
0001=1 Written as 1.	0101=5 Written as 5.	1001= 9 Written as 9.	1101=13 Written as D.
0010=2 Written as 2.	0110=6 Written as 6.	1010=10 Written as A.	1110=14 Written as E.
0011=3 Written as 3.	0111=7 Written as 7.	1011=11 Written as B.	1111=15 Written as F.

Thus our large binary number can now be expressed as 1010 1010 1010 1010 or decimal 43960 or as AAAA in our new format. The new format is called Hexadecimal from HEX=six and DEC=10, which is a counting system based on units of 16 rather than units of 1 or 10.

The hexadecimal system can be easily converted from the binary system by simply breaking up the binary into groups of four binary digits (one hand full of four fingers) and converting each group into a single hex character. For example the binary 0010 0011 0101 0111 becomes hexadecimal 2357. Numbers in hex form are usually referred to by putting X '2357' to denote that this is Hex 2357 rather than decimal 2357. The binary 1010 1011 1100 1101 becomes 'ABCD' which does not require any differentiation from decimal.

A Cardboard Microprocessor

Microprocessor jargon includes bits, bytes, registers, RAM, ports, software and hardware. To help you understand all of this here is your own processor made out of paper. Cut out the PC/MP (Paper and Cardboard MicroProcessor) or copy it and glue it onto a piece of card. Cover the card with something like clear 'Fablon' so that you can write on it with a felt tipped pen and then clean it off again. You are now ready for your first terminology lesson (PCMP is figure 1).

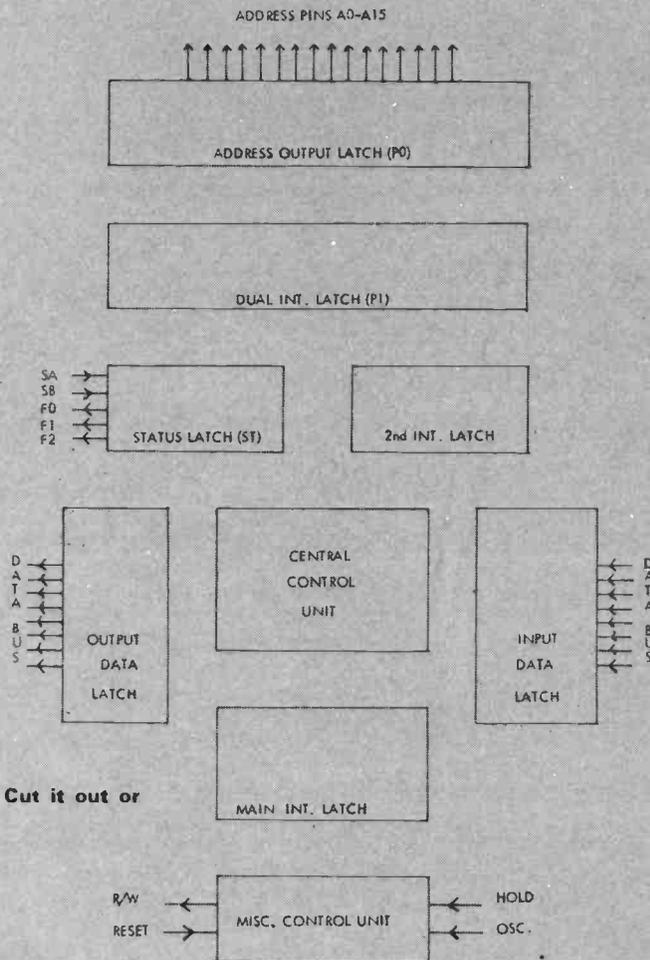


Figure 1. The PCMP processor. Cut it out or trace it carefully.

Bits and Bytes

A bit is a very small piece of information which can be in only one of two states, for example, assuming that there are not alternatives, put a 1 in box 1 over leaf if you are male a zero if you are female.

Thus one Bit can carry a value of 1 or 0 which a microprocessor can look at in two ways —

- a) As a numeric value of 1 or 0.
- b) As a True/False indicator where 1 is True and 0 is False.

Obviously the microprocessor is going to need to deal with numbers other than 1 or 0 and it does this by using a form of Binary arithmetic called Hexadecimal. In this way large numbers can be stored

For example write down your chest measurement in inches on a piece of paper, e.g. 39 inches. Now divide by two and put the remainder (1 or 0) in box 8, take the answer, and divide by two and put the remainder (1 or 0) in box 7, take the answer and divide by two and put the remainder (1 or 0) in box six, take the answer and divide by two and put the remainder (1 or 0) in box 5, take the answer and divide by two and put the remainder (1 or 0) in box 4, take the answer and divide by two and put the remainder (1 or 0) in box 3, take the answer it should be zero (unless you have a chest measurement larger than 63 inches!), write the answer (0 or 1) in box 2.

1	2	3	4	5	6	7	8

You should now have filled in all of the boxes and you have thus formed a Byte of data. A Byte is a unit of data which usually consists of 8 bits of data, the byte above defines your sex and chest size.

Note that Bit and Byte refer to the size of the data portion rather than its contents, thus the amount of storage area or memory attached to a microprocessor is counted in Bits and Bytes.

As these areas tend to be quite large they are counted in thousands of bytes or millions of bytes (Kilobytes and

Megabytes). With microprocessors you get an added bonus because 1K bytes of memory is not 1000 bytes as you would expect but 1024 bytes, an extra 24 for free! Similarly with 1M byte you get an extra 48,576 bytes free, this is simply because these are the nearest Hexadecimal equivalents to 1000 and 1,000,000 and the MPU prefers to count in Hex.

Data and Address Buses

A bus is a set of wires or other connectors which carries a set of data between one part of the circuit and another. Each wire can carry a positive voltage to indicate a logic 1 or no voltage to indicate a logic 0.

To carry the information in our sample byte from above we would need an 8 bit bus or 8 wires, one of the main buses on a microprocessor carries data from one part of the circuit to another, most microprocessors use an 8 bit data bus. The second main microprocessor bus is needed to inform the system where to send the data or where to get it from, an 8 bit bus can only define 256 addresses which is not much for a microprocessor. Two bytes are used to carry the data for an address thus giving a maximum of 65,536 address locations note that 65,536 is 64×1024 and is thus usually referred to as 64K.

A third microprocessor bus carries control signals the simplest of which is a signal to indicate whether we are Reading data or Writing data. This is referred to as a Read/Write control line or simply R/W (more mnemonics). Other controls on a microprocessor include:

RESET	restart program from address location 1.
HOLD	Suspend execution as long as this function is enabled.
OSC	Each oscillator pulse performs one machine cycle (NB several machine cycles make up one operation).
SENSE	Inputs to sense buttons or single bit data.
FLAGS	Single bit outputs used for driving lamps, buzzer, etc.

The PC/MP Microprocessor

The PC/MP consists of several areas of cardboard (defined as latches). These may be thought of as a form of 'pigeon hole' storage. Any information may be written into these boxes as required in the form of an 8 bit (or 16 bit) byte of data. The information can be copied into any other box (which overwrites any previous information in the second box). Some of the boxes allow communication of data in the box to outside the PC/MP.

As an example of an operation of the PC/MP assume that we instruct the PC/MP to READ our sample byte into its Main Internal Latch. It will do this by setting the R/W line to read data and inputting the data to the INPUT DATA LATCH, the data will then be copied to the MAIN INTERNAL LATCH. A second type of instruction can move data around inside the PC/MP, for example copy the data in the MAIN INTERNAL LATCH to the 2ND INTERNAL LATCH. Now enter the byte 0011 0000 into the MAIN INTERNAL LATCH via the INPUT DATA LATCH. You should now have your data byte in the 2ND LATCH and 0011 0000 in the MAIN LATCH.

The PC/MP can perform three operation types on these two data bytes

- a) LOGICAL operations (AND, OR, NOT, XOR)
- b) ARITHMETIC operations (ADD, COMPLEMENT, COMPLEMENT and ADD)
- c) SHIFT operations (SHIFT LEFT or RIGHT, ROTATE LEFT or RIGHT).


Firstly let's look at an AND operation, here if there is a 1 in one latch and a 1 in the same location in the second latch then there will be a 1 in that location in the result (the result ends up in the MAIN LATCH). Thus an AND operation means 1 AND 1 gives 1, otherwise 0.

AND together the MAIN LATCH and the 2ND LATCH and put the result in the MAIN LATCH, the result should be either 0000 0000, 0010 0000, 0001 0000 or 0011 0000. Of the two possible locations of a 1 the first represents a unit of 32 inches chest measurement and the second a unit of 16 inches chest measurement. Thus the four possible results tell us:

000 0000	Your chest measurement is either less than 16 inches or greater than 63 inches.
0010 0000	Your chest measurement is at least 32 inches and less than 48 inches.
0001 0000	Your chest measurement is between 16 inches and 32 inches.
0011 0000	Your chest measurement is at least 48 inches.

Let us assume that the PC/MP is to be used to define the shelf on which to find an overall in a clothing depot. The shelves are set out as

Top Shelf 7	Gents overalls sizes 48 inches to 63 inches
Shelf 6	Gents overalls sizes 32 inches to 47 inches
Shelf 5	Gents overalls sizes under 32 inches
Shelf 4	Overalls sizes under 32 inches
Shelf 4	Overalls either larger than 63 inches or under 16 inches.
Shelf 3	Ladies overalls sizes 48 inches to 63 inches
Shelf 2	Ladies overalls sizes 32 inches to 47 inches.
Shelf 1	Ladies overalls size under 32 inches.

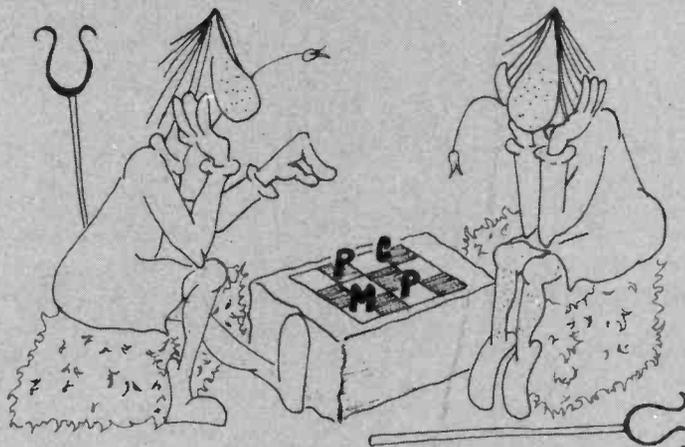

If your results from the AND was all 0's, read the following:- (otherwise go to next paragraph).

This is an example of the conditional jump instruction of the PC/MP. If you are still reading this paragraph then your chest size is, I am sure you will agree, somewhat unusual. In such cases it would seem to make very little difference whether you are male or female when ordering an overall! To help make up for this we will teach you what an OR instruction does, the others will have to wait until later. Copy the data in the MAIN LATCH into the right hand half of the DUAL LATCH and then input the byte 1000 0000 into the MAIN LATCH via the INPUT LATCH. You are now ready to OR. The OR instruction states that if there is a 1 in one latch or a 1 in the other latch then the result will have a 1 in the ensuing location.

THUS: 1 OR 1 gives 1 otherwise 0. If you OR the MAIN LATCH and the 2ND LATCH and put the result in the MAIN LATCH then the data in the MAIN LATCH should now have a 1 in the first position. After this little detour we need to make sure that you have the same data in the same latches as those people who bypassed this paragraph. Copy the MAIN LATCH into the 2ND LATCH and then copy the right hand half of the DUAL LATCH into the MAIN LATCH.

Here we are all together again in this paragraph, those of you who bypassed the instructions in the previous paragraph should read it but not actually *do* the operations.

Now lets learn about SHIFTS and ROTATES.

A SHIFT causes all of the bits in a byte to change their location by one position, the new empty location will be filled with a 0 and the location at the other end drops off the end and is thus lost. With the ROTATE the data is shifted but in this case the new empty location becomes filled with the data bit from the other end. As an example:

SHIFT LEFT 1011 11010 gives 0111 0100 and again gives 1110 1000

ROTATE LEFT 1011 1010 gives 0111 0101 and again gives 1110 1010

SHIFT RIGHT 2ND LATCH seven times to move the Male/Female bit from box 8 to box 1 and fill the rest with zeros

Now ROTATE RIGHT 2ND LATCH twice to put this bit at box 7.

Now OR the MAIN LATCH with 2ND LATCH put result in MAIN LATCH and you should have 0xxx 000 where x can be 0 or 1. SHIFT RIGHT four times the MAIN LATCH and this should be 000 0xxx.

To get the answer take the bit value in box 3 of the MAIN LATCH, multiply it by two and add it to the value in bit 2. Multiply this result by two and then add the value in box 1, the result should be a value in the range 1-7. The result calculation is an example of binary to decimal conversion and is the opposite of the calculation used to calculate your chest size in binary. Normally the MPU would output this RESULT via the OUTPUT DATA LATCH to an address where it would find a device which would display the result to the operator, an example would be a seven segment display plus decoder. All the foregoing is repeated in tabular form with a MALE chest size of 36 inches as follows:-

BYTE OF INFORMATION	1010	0111	SHOWS SEX AND CHEST SIZE
ENTER BYTE	1010	0111	TO INPUT DATA LATCH, COPY
TO MAIN INT LATCH	1010	0111	COPY
TO 2ND INT LATCH	1010	0111	STOP
ENTER	0011	0000	TO INPUT DATA LATCH, COPY
TO MAIN INT LATCH	0011	0000	STOP NOW
AND MAIN INT LATCH	0011	0111	WITH
2ND INT LATCH	1010	0111	RESULT OF AND NOW IN MAIN LATCH
0010 0000 STOP			

	CONDITIONAL JUMP INSTRUCTION		
DATA IN MAIN LATCH	0000	0000	COPY
TO RT. HALF OF DUAL LATCH	0000	0000	STOP
ENTER	1000	0000	TO INPUT DATA LATCH, COPY
TO MAIN INT LATCH	1000	0000	STOP NOW

F

OR MAIN INT LATCH	1000	0000	WITH
2ND INT LATCH	0000	0000	RESULT OF OR
NOW IN MAIN LATCH	1000	0000	COPY
TO 2ND INT LATCH	1000	0000	STOP COPY
RT. HALF DUAL LATCH	0000	0000	TO
MAIN LATCH	0000	0000	NOW
AND MAIN LATCH	0000	0000	WITH
2ND INT LATCH	1000	0000	RESULT
NOW IN MAIN LATCH	0000	0000	STOP

Instructions and Program Memory

The above example gives a generalised idea of what goes on inside a microprocessor assuming that it is given the correct instructions in the correct sequence. It must also input these instructions as well as inputting data, the instructions are input as a form of data which is recognised by the microprocessor in a very simple way. The microprocessor first looks on the input data bus for an instruction, this instruction will tell the microprocessor whether it must next get data or another instruction, thus there is a marker inherent in the instruction code which informs the microprocessor what to do next.

SHIFT RT. 2ND INT LATCH	1010	0111	7 TIMES
BECOMES	0000	0001	NOW
ROTATE RIGHT ONCE BECOMES	1000	0000	ROTATE RIGHT AGAIN
BECOMES	0100	0000	(ROTATED TWICE) STOP
DATA IN MAIN LATCH	0010	0000	STOP
DATA IN 2ND LATCH	0100	0000	STOP NEW
OR DATA IN MAIN LATCH	0010	0000	WITH
DATA IN 2ND LATCH	0100	0000	RESULT OF OR
NOW IN MAIN LATCH	0110	0000	STOP NOW
SHIFT RIGHT MAIN LATCH	0110	0000	4 TIMES
BECOMES	0000	0110	= $2^1 + 2^2 = 6$ Size of Male Overall required is on shelf No. 6.

We must define an area of memory addresses which hold the instructions, for this we will reserve the first 256 memory locations on address lines 0000 0000 0000 0000 to 0000 0000 1111 1111 (0-255 in decimal, 0000 00FF in Hex). The first instruction will be fetched from location 1, the next from 2, etc.

We must also define addresses at which we have a set of switches or a keyboard for input of the parameters and an address at which there is a display and decoder. We can use the upper half of the address to define that address. An upper byte code of 000 0000 will access the program, any address with an upper byte code of 0000 0001 will access the keyboard and an address with an upper byte code of 0000 0010 will access the display. Note that in the second two cases the value in the lower address byte does not matter.

We need to define a set of instructions for the PC/MP, such as:

0000 0 000	00	Activate the HALT feature and this suspend operation until the HALT input is pulsed.
0000 0001	01	Exchange the values in the MAIN LATCH and the 2ND LATCH
0000 0010	02	SHIFT LEFT MAIN LATCH
0000 0011	03	SHIFT RIGHT MAIN LATCH
0000 0100	04	ROTATE LEFT MAIN LATCH
0000 0101	05	ROTATE RIGHT MAIN LATCH
0000 0110	06	Exchange the values in the MAIN LATCH and the DUAL LATCH RIGHT
0000 0111	07	Exchange the values in the MAIN LATCH and the DUAL LATCH LEFT
0000 1000	08	Exchange the values in the ADDRESS OUTPUT LATCH with that in the DUAL INTERNAL LATCH, note this is a 16 bit exchange.
0000 1001	09	Exchange address OUTPUT LATCH and DUAL LATCH, copy MAIN LATCH to OUTPUT DATA LATCH and pulse R/W to indicate WRITE, re-exchange ADDRESS OUTPUT LATCH and DUAL LATCH (i.e. WRITE the data in MAIN LATCH to the address in DUAL LATCH).
0000 1010	0A	Exchange ADDRESS OUTPUT LATCH and DUAL LATCH, pulse R/W for a READ, copy the data in the INPUT DATA LATCH into MAIN LATCH, re-exchange ADDRESS LATCH and DUAL LATCH. (i.e. READ from the address in DUAL LATCH into MAIN LATCH).
0000 1011	0B	READ the data at the next address and copy it into MAIN LATCH
0000 1100	0C	AND MAIN LATCH and 2ND LATCH, put result in MAIN
0000 1101	0D	OR MAIN LATCH and 2ND LATCH, put result in MAIN.
0000 1110	0E	The data following this instruction indicates the number of instructions following it which can be ignored.
0000 1111	0F	As 0A but only if the value in MAIN is all zeros.
0001 000	10	As 0A but only if the value in MAIN is not all zeros.


ETI

Next month: Programming the PCMP and taking down some addresses!

DPS-1

Introducing the DPS-1 the full IEEE S100 bus computer system from Ithaca Intersystems — the S100 experts.

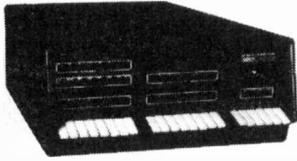FOR EDUCATION, INDUSTRY, RESEARCH and all professional uses, including hardware and software development, low cost OEM systems, teaching applications etc.



A MINI COMPUTER using MICRO technology at a ridiculous MICRO price!! The front panel with a backplane and power supply accepts S100 bus boards from many manufacturers.

Just look at these professional features!

- ★ FRONT PANEL (we won't ask you to debug our hardware, but we will give you the tools to debug yours!). Includes breakpoints, write or jump to any location, single or slow step (0.1 to 1000 IPS), stop on any data byte or address, scope trigger on breakpoint, repeat instruction (e.g. NOP's) and many other hardware diagnostic facilities.
- ★ 25 Amp power supplies (all rails separately fused)
- ★ 20 slot IEEE S100 motherboard
- ★ Full 16 data bit, 24 bit address lines as per IEEE (1979) S100 specification
- ★ Will run 16 bit micro S100 boards when available (e.g. Z8000 and 8086)
- ★ Suitable for 6800, 6502, 8080, 8085, Z80, Z80A etc.

The DPS-1 comes as a mainframe with front panel, motherboard and power supply. The system is truly modular allowing the user to build up the system he requires in his own time.

S100 boards from a number of manufacturers will plug into the DPS1 IEEE S100 bus.

Just add S100 Memory Boards — S100 cpu board — S100 disk controller boards — S100 I/O boards — S100 video and/or graphics boards — S100 EPROM boards — S100 disk boards etc.

All Ithaca Intersystems OEM products including K2 disk operating system and PASCAL/Z on 8" floppy drives will run in the DPS-1.

DPS-1 with S100 Z80 cpu board **£695**


DPS-1 less S100 Z80 cpu board **£645**

OEM S100 boards from the experts!

	bare board	Assembled and tested
8K Static RAM board	£18.75	£123.75
Z80 cpu board (2MHZ)	£26.25	£131.25
Z80 cpu board (4MHZ)	£26.25	£153.75
2708/2716 EPROM board	£18.75	£63.75
Prototype board	£18.75	—
Video display board (64x16, 128U/L Ascii)	£18.75	£108.75

New products from Ithaca audio!

High density graphics (1024 x 512 points)	T.B.A.	T.B.A.
Disk controller (up to 4 single or double sided drives)	£26.25	£131.25
I/O board (serial and parallel outputs)	T.B.A.	T.B.A.
S100 front panel (as used in DPS1)	—	£245.00

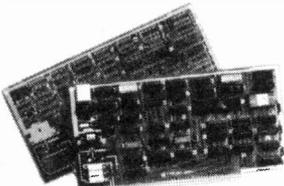

Over 15,000 boards delivered worldwide

InterSystems

Software for your S100 system

K2 operating system

8" disk based operating system — distributed on Shugat compatible 8" floppy disk ★ TED—52 command text editor with Macros. ★ PIP—File and directory handler. ★ ASMBLE—full Z80 2 pass assembler. ★ HDT—Hex debug tool. ★ QCI—Utility overlay/command decoder. ★ SYSGEN—System builder. ★ COPY—disk to disk file copier. ★ DUP—disk duplicator. **£56.25**


PASCAL/Z The new language for Micros **£131.25**

Runs under K2 operating system.

★ Compiler that produces direct assembler code — NO NEED for slow run time P-code interpreter. ★ Comes complete with Macro assembler. ★ Produces binary object modules — small and fast. ★ Modules are re-entrant and can be put into ROM. ★ IMBED, TRACE and ERROR debug facilities.

ASMBLE/Z Z80 Macro assembler **£37.50**

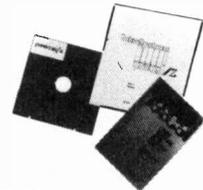
★ Full 2 pass Macro Assembler. ★ IF and ELSE — 255 nesting levels. ★ Produces symbol table. ★ Relative jumps.



UP-GRADE KITS


Trying to add computer memory is not much fun if you dont get everything you need.

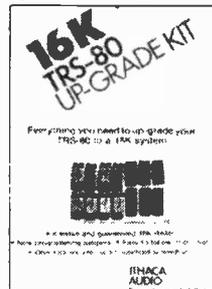with concise step by step directions and diagrams. And if a personality jumper is required, it's premade.



Receiving unprogrammed jumpers and having to program them yourself is not much better. Most important, that's the place where the problems are introduced.

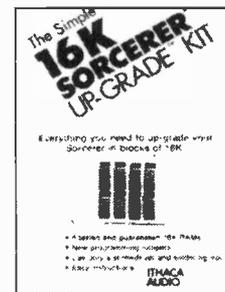So Ithaca Audio's better idea is the Simple Up-Grade. Each Simple Up-Grade is specially designed to make adding memory foolproof. We include all the parts you'll need; 8 prime, tested 16K RAMs, along



The TRS-80* memory expansion was our first Simple Up-Grade. Now there are two more — for owners of Apple II** and Exidy Sorcerer*** computers. Each kit is 100% guaranteed — if a part ever fails, we replace it FREE. Your Ithaca Audio dealer has them in stock, only £99. Now you can afford to add high quality, high density memory to your system for remarkably little — far less than you would expect to pay from Radio Shack, Apple, or Exidy directly. These Simple Up-Grades are Ithaca Audio's first step in adding more capability and reliability to your computer at lower cost. Other Up-Grades are on the way to your dealer now.

*TRS-80 is a registered trademark of Tandy Corp.

**Apple II is a registered trademark of Apple Computer, Inc.

***Sorcerer is a registered trademark of Exidy, Inc.



CONTACT THESE DEALERS

All prices quoted are exclusive of VAT.

NEWBEAR COMPUTING STORE — Telephone: Newbury (0635) 30505

AIRAMCO — Telephone: 0294 57755 Telex: 779808

SIRTON PRODUCTS — Telephone: 01-660 5617

COMPSHOP LTD — Telephone: 01-441 2922 Telex: 298755

ITHACA **InterSystems**
(formerly ITHACA AUDIO of New York)

UK & EUROPEAN DEALER ENQUIRIES INVITED — CONTACT EUROPEAN SALES HEADQUARTERS

58 Crouch Hall Road, London N8 8HG. UK. Telephone: 01-341 2447 Telex: 299568



Where would you be without an ETI T-shirt? This little lady (she's the one without the moustache) would find herself in an embarrassing predicament.

Why not follow the example set by our typical seven feet tall ETI reader (the one with the moustache) and cover your wives, girlfriends, grannies, pimples and indiscretions with an ETI T-shirt. We'd love to hear from our feminine fans too.

£2.12, including nasties like VAT, postage and packing, brings the scarlet sackcloth, the rubescent rag, the monogrammed marvel to your door. Orders to:

ETI Shirts,
145 Charing Cross Road,
London WC2H 0EE

Please specify size — S, M or L
and allow 14 days for delivery.

microfile.....

This month the ever present Henry Budgett drools over the finally announced Texas Instruments System. Between time he looks at a more down to earth training system called the Nano-computer.

WELL, IT is here at last, or rather TI is! Launched at the Consumer Electronics Show in Chicago on Sunday June 3rd the Texas Instruments home computer is with us. There are no real surprises unfortunately but the machine will probably provide a real challenge to both Apple and CompuColor. Based on the 990 series 16 bit microprocessor the system is built into a neat desktop console which measures 15" by 10" by 2½".


Configured with 16K of RAM, a sound generator which covers four full octaves, full 16 colour graphics and an extended BASIC. The machine will drive any black and white TV or monitor and any NTSC colour monitor with video input. Hopefully a PAL version will be available for Europe as at the moment it will cost about £400 for a suitable monitor. The machine uses an extension of the calculator Solid State Software system with up to five ROM chips in a module. A variety of these will be available for the UK launch in September including Pre-school learning, Video Chess, Home Budgeting and Video Games. Prices for the various packages will vary between £15 and £45. The main advantages of the Solid State system is the high speed of program loading and interchange.

Peripherals for the system will be announced in due course and should include a printer, disk drive, RS232 interface and a Speech Synthesiser. The synthesiser is based on the Speak and Spell chip set and has a vocabulary of 200 words, these can be called from user programs to give messages, instructions etc. The BASIC on the system is a 13 digit version with full floating point, ANSI compatible and has 24 basic statements, 14 commands and the colour graphics.

The cost of the machine is quoted at £645 but the change in VAT may mean a slight increase by the Autumn. For further details you should contact Roger Tilbury at Texas Instruments, Manton Lane, Bedford MK41 7PN. We will be reviewing the system as soon as we can lay our hands on one and I will keep you informed of any further developments through both ETI and CT.

New Training System

Newly arrived in our offices is a new training and educational system called the Nanocomputer. Definitely not to be confused with a popular TV show! Based on the Z80 the system is fully expandable from a single board with a hand held keypad right up to a full system and you can select the level at which you start. The unit is supplied in a case with a power supply and the keypad and a training manual. This takes you through the machine code programming of the Z80 and you can then go on to the experimental kits. For these one plugs onto the end of the board a prototyping kit which allows

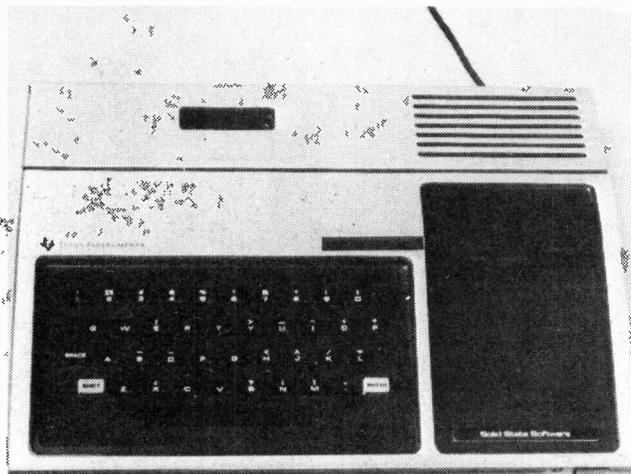

Above: At last! The Texas Instruments home computer system. Along time in the making


you to learn about interfacing to the system, amongst other things. The final stage is to upgrade the board to a full system in a card frame with a variety of peripherals such as a full ASCII keyboard, printer, VDU and disks.

A range of software is also available including various monitors, Editor Assemblers and an 8K BASIC. The unit is extremely well constructed on a double sided, plated through PCB and all interconnections are made with high quality header sockets thus eliminating the usual lash ups. A full review of the system will be appearing in the August issue of CT but for more information before then please contact Mr David Watson of the Midwich Computer Company at Hillsborough House, Churchgate Street, Old Harlow, Essex. The price of a basic system is £260, the full Experimental kit is around £430.

Club Forum

A varied bunch in this month's mailbag. Micro44 of Woking have formed an Exidy Sorcerer Users Group to be run by Andy Marshall. The group will be run as a division of the US group and will both take and contribute material to them. Membership fees are £5 a year to cover costs and a monthly newsletter will be produced. Contact Andy at Micro44, 44 Arthurs Bridge Road, Woking GU21 4NT or ring 04862-66084. Another club is being formed in the Nottingham area, primarily for Nascom users but anyone will be welcome. Meetings will be monthly, no dates are yet arranged and

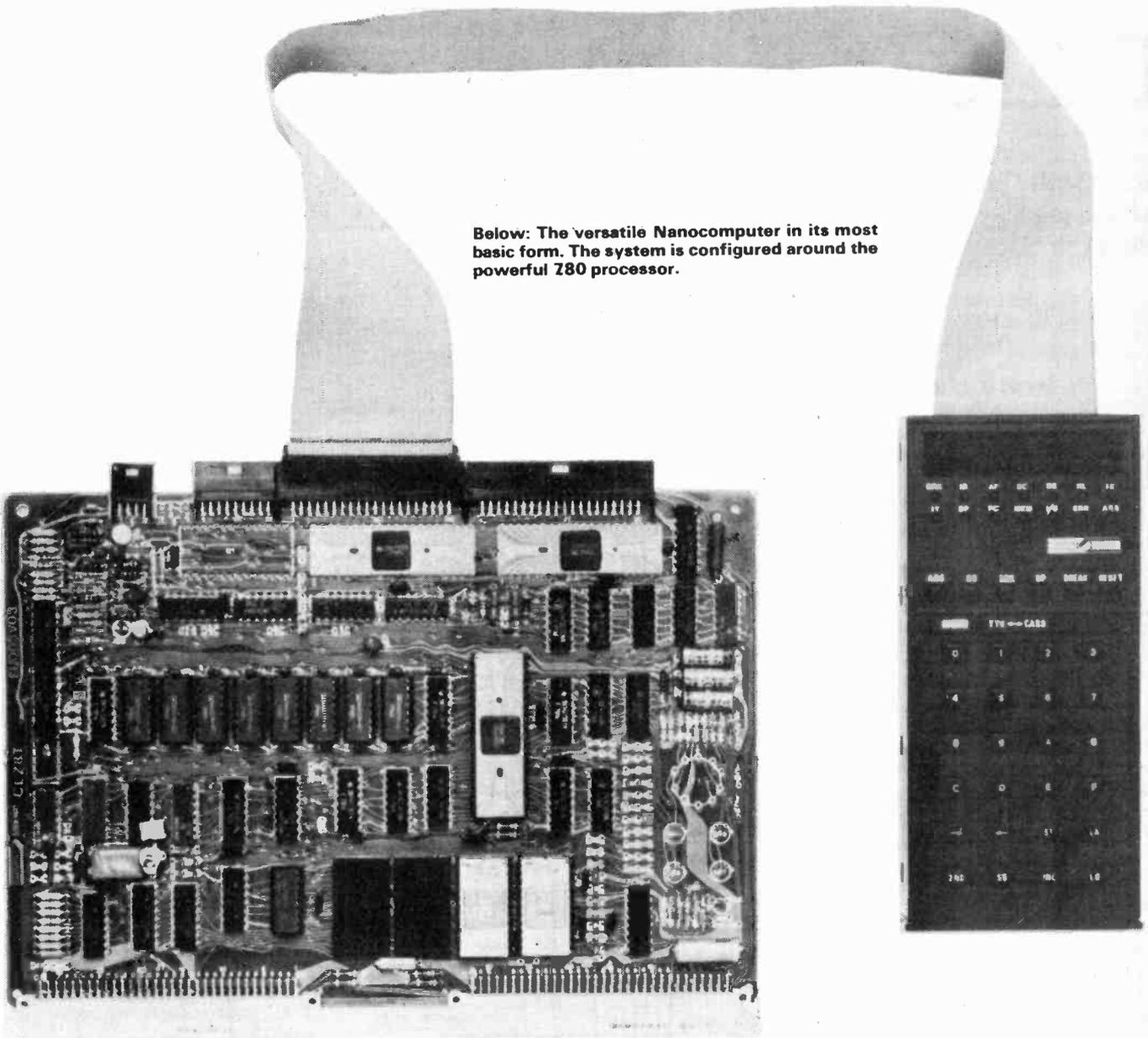Below: The versatile Nanocomputer in its most basic form. The system is configured around the powerful Z80 processor.



it is hoped to produce a newsletter and offer program exchange. For those interested please contact Mr K S Swainson at 9 Brayton Crescent, Highbury Vale Estate, Bulwell, Nottingham NG6 9DZ.

Ware Of The Soft Kind

A TRS 80 software exchange service is being planned by Chris Cain, if anyone is interested. He handles programs and tests them in any TRS 80 format and anyone interested should contact him at ENG Wing, RAF West Drayton, Middlesex. Please enclose an SAE. The final item is a request for our younger readers. If anyone who is into the SCMP micro and BASIC programming would like to help form a young persons computer club would they please get in touch with N. Sutcliffe Esq of 1 Suncliffe Road, Higher Reedley, Nr Burnley, Lancashire BB9 5EP and enclose an SAE.

ETI



**LOW COST
AUDIO SIGNAL
GENERATORS**

(Sine & Square Waves)
10Hz-100KHz
Very low distortion (-0015%)
£36 (or in kit form £31)
+ Tax 8%

Model 146/9

Low cost version, A0113 (02% dist), **£27.50 (Kit £23)**. Other instruments include: Millivoltmeter, Tachometer, Noise level meter, Distortion Analyser, F.M. Sig. Gen. Crystal Frequency Standard, KEF Speaker Units. Send S.A.E. for lists. VAT extra 15%. Post/Pkg. £1.50.

TELERADIO ELECTRONICS
325 Fore Street, Edmonton, N.9. 01-807 3719
Closed all day Thursday

MICRO CHIMES

FROM THE INVENTORS
OF MICROPROCESSOR
MUSICAL CHIMES

**VAT increases?
Our prices held!**

CHROMA- CHIME KIT

24 tune model!

Due to the fantastic
success of this product right
across the World we are able to offer it at

only **£9.95 + 75p p&p**

Comes complete with:

- * TMS1000 Micro
- * Superb cabinet
- * All R's & C's
- * Switches & pots
- * Fully prepared PCB
- * All semiconductors
- * Loudspeaker
- * Socket & Hardware
- * Fully detailed kit manual

TMS 1000N - MP0027A Micro-
computer chip available separately if
required. Full 24 tune spec device
supplied with data sheet and fully
guaranteed.

New low price only **£4.95** inc. p&p
(Only present 24 tune repertoire currently available.)

A COMPLETE KIT FOR THE NEW MICRO CHIME

This easy to
build kit includes:

- * TMS1000 Custom MPU Chip
- * Special purpose designed case
- * Fully drilled and legended PCB
- * All transistors, Resistors and Capacitors
- * Full set of mechanical parts
- * Smart fascia labels
- * IC Socket and Loudspeaker
- * Really Low Price!

only **£8.95 + 55p p&p**

ALL CHROMATRONICS PRODUCTS
SUPPLIED WITH MONEY BACK GUARANTEE
PLEASE ALLOW 7-21 DAYS FOR DELIVERY

Please send me:

TO: CHROMATRONICS, RIVER WAY, HARLOW, ESSEX, UK.

NAME _____



ADDRESS _____

I enclose cheque/PO value £ _____
or debit my ACCESS/BARCLAYCARD account no. _____

Signature _____

ETI.8.79

CHROMATRONICS

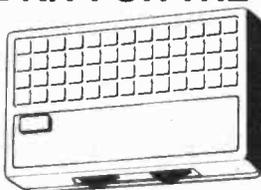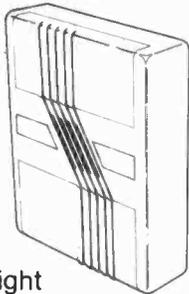

SINTEL

KITS OR ASSEMBLED LATCHED COUNTER MODULES

Our range of Industrial Latched Counter Module Kits is now available ready-built. These counters use both CMOS and TTL ICs and will save you considerable design, purchasing, building and de-bugging time. Each module uses a set of red LED displays, and features a single in-line plug and socket. Instructions are provided. For full details please send for Catalogue.

	TTL				CMOS			
	Part No.	Built	Part No.	Kit	Part No.	Built	Part No.	Kit
2 digit	401-484	£13.22	528-412	£10.52	905-560	£13.02	548-470	£18.42
4 digit	715-484	£23.38	657-412	£17.08	512-568	£22.63	808-470	£18.11
6 digit	293-484	£33.78	721-412	£25.06	383-568	£32.31	191-470	£25.85

NEW PRICES AND SOME NEW CMOS ADDITIONS

If you need your CMOS by return - buy it from SINTEL

CD4000	0.15	CD4027	0.44	CD4051	0.82	CD4086	0.84	CD40182	1.40
CD4001	0.17	CD4028	0.77	CD4052	0.82	CD4089	1.39	CD40192	1.40
CD4002	0.17	CD4029	1.03	CD4053	0.82	CD4093	0.80	CD40193	1.40
CD4006	1.04	CD4030	0.50	CD4054	1.04	CD4094	1.69	CD40194	1.18
CD4007	0.18	CD4031	2.00	CD4055	1.18	CD4095	0.94	CD40257	1.48
CD4008	0.87	CD4032	0.89	CD4056	1.18	CD4096	0.94	CD4502	0.81
CD4009	0.60	CD4033	1.25	CD4059	4.29	CD4097	3.35	CD4510	1.01
CD4010	0.50	CD4034	1.71	CD4060	1.00	CD4098	0.88	CD4511	1.25
CD4011	0.78	CD4035	1.06	CD4063	0.96	CD4099	1.85	CD4514	2.47
CD4012	0.20	CD4036	2.88	CD4066	0.65	CD4100	2.50	CD4515	2.82
CD4013	0.43	CD4037	0.85	CD4067	3.35	CD4101	1.81	CD4516	1.01
CD4014	0.83	CD4038	0.98	CD4068	0.20	CD4102	2.13	CD4518	0.97
CD4015	0.83	CD4039	2.78	CD4069	0.20	CD4103	2.13	CD4520	1.04
CD4016	0.48	CD4040	0.97	CD4070	0.46	CD4104	1.10	CD4527	1.43
CD4017	0.78	CD4041	0.78	CD4071	0.20	CD4105	1.06	CD4532	1.21
CD4018	0.83	CD4042	0.69	CD4072	0.20	CD4106	0.82	CD4556	0.78
CD4019	0.50	CD4043	0.88	CD4073	0.20	CD4107	0.89	CD4556	0.78
CD4020	1.11	CD4044	0.84	CD4075	0.20	CD4108	5.36	MC14528	0.93
CD4021	0.90	CD4045	1.26	CD4076	1.17	CD4109	1.03	MC14553	4.43
CD4022	0.82	CD4046	1.20	CD4077	0.39	CD4160	1.19	IM6508	8.05
CD4023	0.18	CD4047	0.89	CD4078	0.20	CD4161	1.19		
CD4024	0.70	CD4048	0.50	CD4078	0.50	CD40162	1.19		
CD4025	0.20	CD4049	0.50	CD4082	0.20	CD40163	1.19		
CD4026	1.55	CD4050	0.43	CD4085	0.84	CD40181	3.40		

Our offices are at Chapel Street, Oxford, but please do not use this as a postal address.
For full range of components send for Free Catalogue.

OFFICIAL ORDERS ARE WELCOME from Companies, Gov. Deps. Natn. Inds., Univs., Polys.
ORDERS: CW, Q, add VAT @ 35p p&p. TELEPHONE and CREDIT (Invoice) ORDERS add VAT @ 15% + 60p p&p
minimum charge (the balance will be charged at cost). Please see FAST SERVICE EXPORT ORDERS welcome, no VAT
but add 10% (Europe), 15% (Overseas) for Air Mail p&p. For Export rates on heavy items - contact us first.

ORDERS TO: SINTEL, PO BOX 75A, OXFORD
Tel: 0865 49791

FAST SERVICE: We guarantee that Telephone Orders for goods in stock, received by 4.15 p.m. (Mon.-Fri.) will be despatched on the same day by 1st Class Post (some heavy items by parcel post) and our stocking is good. Private customers should telephone and pay by giving their Access or Barclaycard number, with a minimum order value of £5. Official orders no minimum.

SINTEL

300w LIGHTING CONTROL KITS

TD300K Touch Dimmer.
Dimming and on/off functions are controlled by touch. Features include:
* No mains rewiring
* Switches on to preset brightness
* Can be switched and dimmed from many locations using TDE/K kit making 2-way switching easy.

★PRICE TD300K **£6.50**
TDE/K **£1.50**

TS300K TOUCHSWITCH & DIMMER combined. One touch-plate for on/off. Small knob controls brightness. **£5.50.**
TS300K TOUCHSWITCH. Two touchplates ON/OFF. **£4.30.**
TSA300K AUTOMATIC. One touchplate. Preset time delay off. **£4.30.**
LD300K LIGHTDIMMER. **£2.90.**

DIGITAL VOLTMETER THERMOMETER KIT

Based on the 7106 single IC 3½ digit DVM the kit contains a PCB, resistors, capacitors, pre-sets, IC and 0.5" liquid crystal display. Components are also included to enable the basic DVM kit to be modified to a Digital Thermometer using a single transistor as the sensor.
ONLY £20.75



TRIAC BARGAINS

T0220 Plastic Case 400v	
3A	49p
6.5A with trigger	80p
8A	62p
12A	70p
16A	90p
20A	165p
25A	190p
SCR (C106D) 5A/400V	38p
Diac	18p

COMPONENTS

0.2" L.E.D.S.	
Red 12p	(10 for £1.00)
Green or yellow	17p
DL 727 5" display	£1.50
	(2 for £2.80)
LCD 5" display 3½ digit	£8.10
LDR 5" dia.	50p
555 24p	(4 for 90p)
741 22p	(5 for 90p)
LM3911 Temperature IC	£1.00
AY-5-1224	£2.60
AY-5-1230	£4.50
ZN1034E	£1.80
ICL 7106 DVM IC	£7.50
IN4001	6p*
2N 4148	4p*
8C182L	10p*
2N3819	20p

MINI MAINS TRANSFORMERS

Standard 240V mains primary	
100mA secondary	
6.0-6V	80p
9.0-9V	85p
12.0-12V	90p

24 HR. CLOCK/APPLIANCE TIMER KIT

Switches any appliance of up to 1KW on and off at preset times once a day. KIT contains AY-5-1230 Clock/Appliance Timer IC, 0.5 LED display, mains supply, display drivers, switches, LEDs, triac complete with PCBs and full instructions.
White box (56x131x71mm)—drilled **£2.50**
undrilled **£2.20**
Ready-built **£22.50**



PLEASE ADD 15% V.A.T. TO ABOVE PRICES

QUANTITY DISCOUNTS ON REQUEST. ADD 25p POSTAGE & PACKING. MAIL ORDER ONLY

T.K. ELECTRONICS (ETI), 106 Studley Grange Road, London W7 2LX
CALLERS WELCOME BY APPOINTMENT. Tel. 01-579 9794

ELECTRONICS TODAY INTERNATIONAL - AUGUST 1979

PLEASE SEE V.A.T. ADVERTISEMENT ON PAGE 15 BEFORE ORDERING GOODS FROM ADVERTISERS!

Redundant Test Equipment?

Why not turn it into capital?

We Urgently Require
Oscilloscopes, spectrum analysers,
DVM's, signal generators, power
supplies. In fact we are interested
in buying all types of electronic test
equipment, give us a ring and we
will give you a price.

Call David Kennedy or
Kathy Goodman

Carston Electronics Limited

01-267 4257

Carston Electronics Limited
Shirley House, 27 Camden Road
London NW1 9NR. Telex 23920.



Wilmslow Audio

THE firm for speakers!

Send 15p stamp for the world's best catalogue of
Speakers, Drive Units, Kits, Crossovers, etc., and
discount price list.

● AUDAX ● BAKER ● BOWERS & WILKINS ●
CASTLE ● CELESTION ● CHARTWELL ● COLES ●
DALESFORD ● DECCA ● EMI ● EAGLE ● ELAC ●
FANE ● GAUSS ● GOODMANS ● I.M.F. ●
ISOPHON ● JR ● JORDAN WATTS ● KEF ● LEAK ●
LOWTHER ● MCKENZIE ● MONITOR AUDIO ●
PEERLESS ● RADFORD ● RAM ● RICHARD ALLAN ●
SEAS ● TANNOY ● VIDEOTONE ●
WHARFEDALE ● SHACKMAN ● AUDIOMASTER ●
TANGENT ● STAG ● YAMAHA

WILMSLOW AUDIO Dept. ETI

**SWAN WORKS, BANK SQUARE, WILMSLOW
CHESHIRE SK9 1HF**


Discount HiFi, etc., at:
5 Swan Street and 10 Swan Street

**TEL. WILMSLOW 529599 FOR SPEAKERS
WILMSLOW 526213 FOR HI-FI**

PROOPS BROTHERS LIMITED

Special purchase of Shinohara's SEW Panel Meters at
fantastic low prices

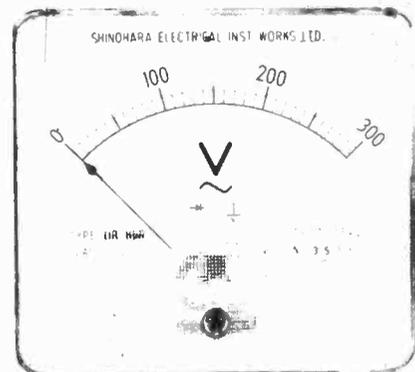MR RANGE — DC MOVING COIL TYPE
(Accuracy $\pm 2\%$)



DIMENSIONS:


110 x 120 x 47 mm	Ref 85P	£3.00
78 x 86 x 41 mm	Ref 65P	£2.50
60 x 60 x 40 mm	Ref 52P	£2.50
50 x 50 x 34 mm	Ref 45P	£1.50
42 x 42 x 32 mm	Ref 38P	£1.50

Prices inclusive of VAT. Add 25p per item for carriage and packing

References:	$\pm 50\mu\text{A}$	100mA — DC	10V — DC
	$\pm 100\mu\text{A}$	200mA — AC	15V — AC
	$\pm 500\mu\text{A}$	500mA — AC	15V — DC
	1mA	500mA — DC	50V — AC
	50mA	1A — AC	50V — DC
	200mA	1A — DC	150V — AC
	1mA'S	10A — DC	150V — DC
	5mA	30A — DC	300V — AC
	10mA	50A — AC	300V — DC
	50mA — AC	50A — DC	500V — AC
	50mA — DC	5V — DC	

Most values available in most sizes
Please state second preference when ordering

ED 107 EDUCATIONAL RANGE

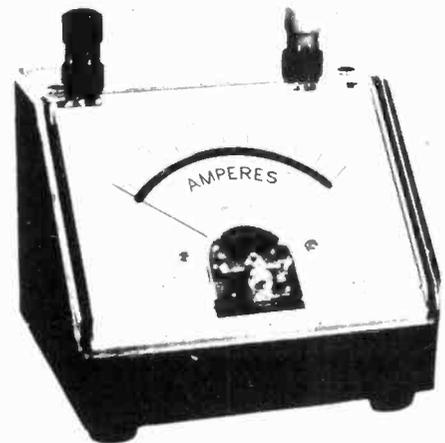

Dimensions: 78 (H) x 90 (D) x 100 (W) mm
£3.50 each including VAT. Add 50p per item carriage and packing

$\pm 1\text{mA}$	50 μA	5/50V DC	50V DC
10V	100 μA	20V DC	300V DC

Barclaycard & Access Accepted — Order by phone or post

Mail Orders to **PROOPS BROS. LIMITED, Dept ETI**
The Hyde Industrial Estate, Edgware Road, London NW9 6JS. Tel:
01-205 8006

Personal Shoppers: 52 Tottenham Court Road, London W1P 0BA, 9-6 Mon.-Sat.

IMPEDANCE AND PHASE

Life would be a lot easier if all components behaved like resistors. Inductors and capacitors make life difficult by separating voltage and current, so how do you find the voltage or current at any point in a circuit? Phase diagrams to the rescue.

In electronics, one often needs to know what the voltage of current at some part of a circuit will be, without actually building it to find out. When dealing with DC, this is usually pretty straightforward, using Ohm's law and a few rules of thumb, but AC signals in a circuit are a different matter, often reacting in totally different ways, predictable only by using impedance theory and phase diagrams. It is this type of theory, and the calculations used to find voltages, etc., in circuits, that concern this article.

AC Signals

First let's remind ourselves what an AC signal actually is. Plotting voltage against time for a typical signal would give us a graph like that in Fig. 1. This particular variety of round wave is known as a sine wave and in order to fully describe it, we must outline two quantities: its rms value and its frequency. The former is a measure of the amplitude, or height of the wave, and for reasons that need not be gone into here, is, in the case of a sine wave, 0.707 times the maximum value of the wave. For instance, if, as in Fig. 1, the wave has a maximum value

of 6 volts, the rms value of the signal is $0.707 \times 6 = 4.24$ volts. The other measure of the wave is the frequency. Take the interval between, say, A and B on Fig. 1. This interval, from one point to the next point where the voltage is acting in exactly the same way (in this case, from a point where it is zero and decreasing to the next point where it is both zero and decreasing) is called the period of the wave and is measured in seconds. During one period, the wave is said to have gone through one full cycle. The frequency of the wave, we can now say, is the number of cycles per second.

Impedance

Impedance can be described as the opposition to electrical current given by a circuit. Of course, we know about ordinary resistance, but there are other varieties. For instance, a capacitor may have a very high opposition to DC current, but a very low opposition to AC signals of a suitably high frequency. This obviously isn't ordinary resistance, because if it was, it would remain the same for AC and DC. In fact, the amount of opposition given to a signal by a capacitor is measured by the

Fig. 1. A voltage/time graph for a typical AC signal.


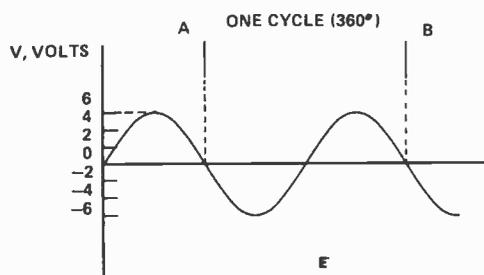


Fig. 2. Current and voltage plots for a capacitor, showing a phase difference between the two.

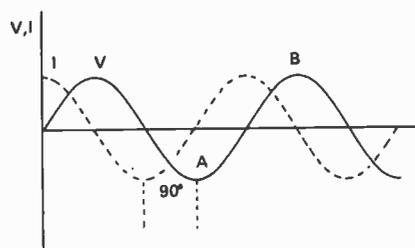

ratio of voltage across it to current through it. (V/I). This ratio is called the 'capacitive reactance' of the component, and it is given the symbol X_c . Like resistance, reactance is measured in ohms. Capacitive reactance may be calculated from the value of a capacitor by using the formula $X_c = 1 / 2\pi fC$, where π is the Greek letter Pi, and represents the number 3.14 . . . , f is the frequency of the signal being applied, and C is the value of the capacitor in Farads. Note that, as stated earlier, the opposition (reactance) of the capacitor becomes very small at high frequencies, but to DC (where the frequency is effectively zero) or to very low frequency signals, it becomes effectively infinite.

Inductors, too, have a variable reactance; in this case, the inductive reactance, X_L , which may be obtained from the value, L , in Henries of the inductor, from the formula $X_L = 2\pi fL$. Note that this reactance also varies with frequency, but here, it becomes greater at high frequencies, approaching zero only when f is very low, or when DC is encountered. Again, X_L is the ratio V/I in the inductor, and thus, given either the voltage or the current, it is possible to calculate the other in either a capacitor or an inductor, if we know the frequency at which the circuit is operating.

To conclude this section, we now give a rather more adequate definition of impedance than that which we began with. Impedance is the combined opposition to AC signals in a circuit given by the resistance and reactance of the circuit. If we represent it by Z , the resistance by R , and the reactance by X , then $Z = \sqrt{R^2 + X^2}$. We find that, in a combination circuit of several components, $Z = V/I$.

Phase Differences

In addition to information about voltages and currents in circuits, phase diagrams also give us information about phase differences in these circuits. What in the world is a phase difference? To answer that, we must return to the capacitor and inductor. Suppose that we are applying an AC voltage across a specimen of the former type of component. If we now look at the current flowing through it, we find that it is 'leading' the voltage by a quarter cycle. That is, although it goes up and down in the same way that the voltage does, the two quantities are not in time with each other. If the voltage has, say, gone up (as from point A to point B in Fig. 2), then the current did so 90° , or a quarter of a cycle earlier. (The figure 90° is used because a full cycle is taken as being divided into 360 degrees, as a circle is, and one quarter of a cycle is, therefore, represented by $\frac{1}{4} \times 360 = 90$. The reason for dividing a cycle into 360 degrees will

become apparent later.) If we superimpose a graph of current against time on top of one of voltage against time, we get something like Fig. 2.

In the inductor, a similar effect occurs, but here it is voltage which leads current by 90° , rather than vice versa. The 'phase difference', as it is called, is given both in the case of the capacitor and the inductor, the symbol ϕ — the Greek letter phi — and may also be measured in terms of radians, another unit of angle, rather than degrees.

To help remember that voltage leads current in the inductor, whereas current leads voltage in the capacitor, the mnemonic CIVIL is used. In a capacitor, (C) current (I) leads voltage (V), but voltage leads current, (I) in an inductor (L). Taken in order, the one-letter symbols for the components, voltages and currents spell CIVIL. (All right, I didn't think of it.)

Phase Diagrams

So far we have seen how voltage and current are related in terms of magnitude (size) and phase, in individual components. What happens, though, if we put two different components — a resistor and inductor, for example, in series or parallel? This is where the phase diagrams step in, folks. Let us suppose that these two components, each of known value, are connected in series, and that we know the current which is flowing through the combination, and this current's frequency. We wish to find the size and phase of the total voltage across the two components, and we might be misled into thinking that it would just be the sum of the two individual voltages across the individual components, but in fact, this will not be so. The current and voltage will be exactly 'in phase' in the resistor, but in the inductor, the voltage will be 90° out of phase; you can't just add voltages unless they are in phase with each other. Of course, we could find the magnitude of the total voltage by finding the total impedance of the circuit and multiplying this by the current, but we still wouldn't know the phase of this voltage with respect to the current, so a phase diagram is really our only option.

Which Reference

For our diagram, we shall want some quantity, either voltage or current, which will be the same for both components. Well, as we have just seen, the voltages across the individual components are definitely different, so that only leaves current. In fact, current serves as our 'reference quantity' in any series circuit, and voltage is used in parallel circuits. To represent the current, draw an arrow, pointing to the right. Now we

Fig. 3. A series circuit with a resistor and an inductor. Do you use voltage or current as the reference quantity?


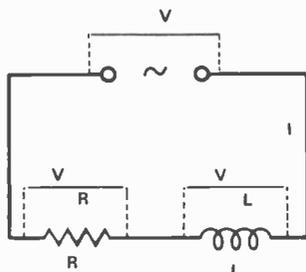


Fig. 4. The voltages across the resistor and inductor can be used to find the total voltage across the two components.

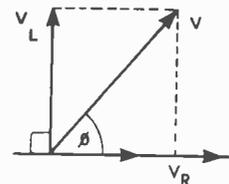

must draw in arrows to represent the voltages across individual components. The lengths of these arrows will be made, using a suitable scale, to represent the rms values of the voltages, and the phase of each voltage with respect to the current will be indicated by the angle, going anti-clockwise, which the voltage's arrow makes with that of the current, when both have their tails at the same place. Thus, the voltage across the resistor, which can be calculated by multiplying the current by the resistance, will be represented by an arrow actually on top of that showing the current, because the voltage and current here are in phase, so that the angle, ϕ , is zero. The voltage across the inductor can be calculated by finding the reactance of the component, and multiplying this by the current. This arrow will be placed at an angle of 90° to that representing the current (i.e. it will point straight up), because the voltage in an inductor leads the current by 90° . Were the component a capacitor, ϕ would be -90° , because the voltage here lags by a quarter cycle, which is equivalent to saying that it leads by -90° . The arrow would, then, point down, rather than up, as it does now.

If we imagine our two voltage arrows to be two sides of a parallelogram (in this case, a rectangle, because we know that one of the angles is 90°), and draw in the other two sides parallel to the ones we have, as in Fig. 4, we find that the diagonal of the rectangle, drawn in as an arrow starting at the same place as do all the others, has a length that, on whatever scale we have used to draw the lengths of our arrows, gives the total voltage across the two components. In addition to this (yes, you guessed it . . .), we find that the angle which this diagonal arrow makes with the horizontal gives the phase of the total voltage across the circuit, with respect to the current!

In fact, if we use Pythagoras' famous theorem about the squares of the lengths of the sides of a right angled triangle (whew!), to find the length of this diagonal, we find that, if we call the voltage across the resistor V_R , and that across the inductor V_L , then the total voltage, V , is given by the formula:—

$$V = \sqrt{V_R^2 + V_L^2}$$

Looking back to the section on impedance, we notice that this formula bears a remarkable resemblance to the one stated to give the combined impedance of a resistance and reactance; in fact, if we divide both sides of the

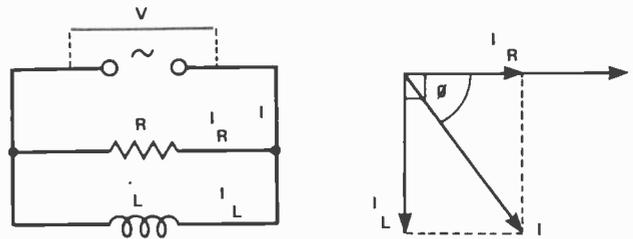


Fig. 5. (a) A resistor and an inductor in parallel. In this case voltage is used as the reference quantity. (b) The phase diagram for a parallel L-R circuit.

equation by the current, I , then V becomes Z , V_R becomes R and V_L becomes X_L (since Z , R and X_L are all defined to be equal to V/I) and the two equations become one and the same (Howzatt!!!).

The phase of the voltage can also be calculated, rather than measured directly from the diagram. The appropriate formula is:—


$$\phi = \tan^{-1} V_L / V_R.$$

What about parallel circuits? The procedure this time is pretty much the same as for series circuits, but now the 'reference' arrow, pointing to the right, represents the total voltage, not the current. The individual arrows represent the currents through the individual components, rather than the voltages, and the diagonal arrow gives the total current, and the angle by which the current leads the voltage. Note that if this angle is multiplied by -1 , it then gives the angle by which voltage leads the current.

LC Circuits

There are two more circuits, that should really be treated by themselves. These are the combination of capacitor and inductor in series or parallel, and they possess some rather interesting properties. If we draw a phase diagram for either of these two types of circuit, we find that the two arrows representing voltages or currents, as the case may be, in the individual components point in exactly opposite directions. To find the arrow that is the combination of these, we place the arrows end to end. That

Fig. 6. (a) A series L-C circuit, where current is the reference. (b) Phase diagram for the series L-C circuit. Inductor and capacitor voltages are 180° out of phase. (c) A parallel L-C circuit. (d) With voltage as reference, inductor and capacitor currents are 180° out of phase.

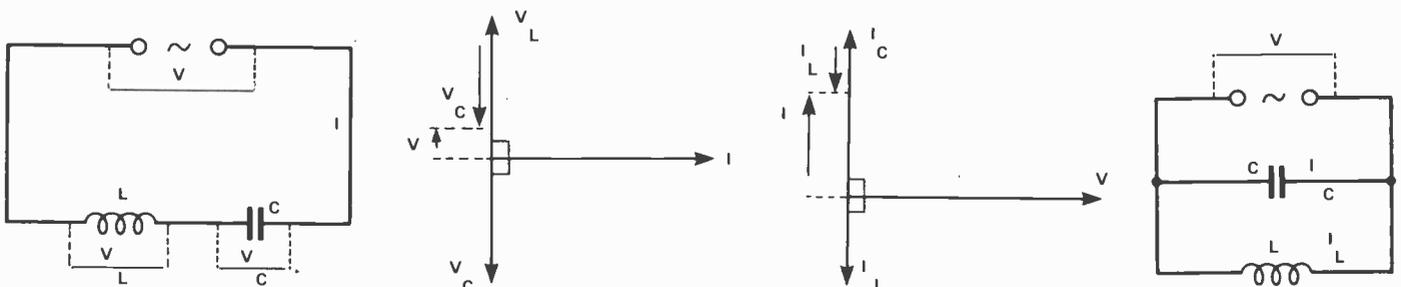

FEATURE: Impedance & Phase

is, we place the tail of one of them at the head of the other, keeping them pointing in the same directions. An arrow starting at the beginning of the first individual one, and ending where the second arrow does, gives the total voltage, or current. It can be seen from this that if $V_c = V_L$, then the two will exactly cancel out, and in a series circuit, there will be no voltage across the two components, and the circuit will be effectively shorted across. In a parallel circuit, there will be no current flowing, and the total impedance of the circuit will be effectively infinite. Under what circumstances, then we may ask, will the two voltage (or current) arrows be of equal length, and cancel? It turns out that this is so if $X_c = X_L$, and using the formulae for the reactances of the components, from the section on impedance, we find that $2\pi fL$ must equal $1/2\pi fC$. Here we notice that for any named combination of values for L and C, it should be possible to find some frequency — the so called **resonant frequency** — for which the circuits should react in the way described above. Manipulating the equations, we come up with the formula: —


$$f = 1 / 2\pi \sqrt{LC}$$

Thus, in a series circuit, signals at this, and only this, frequency, will be able to pass through the circuit unimpeded, whereas in a parallel circuit, any other frequency will be allowed to pass. These circuits are called, respectively, a notch filter and a tuned circuit. The latter is of great use in radio receivers, where it is often used to short all signals at frequencies other than those wanted to earth, thus effectively sorting out wanted signals to be amplified and listened to. The frequency required may be selected by adjusting one or other of the two components, and, in fact, the capacitor in the tuned circuit of a radio is usually a variable type, and forms the tuning control.

Two's Company . . .

Of course, you may want to find voltages or currents in circuits with more than two components, but this isn't as difficult as you might think. Just find the individual arrows of the separate components, and put them all end to end, as in Fig. 7. The final arrow, giving the total voltage or current, starts at the beginning of the first and ends where the last of the separate arrows does. **ETI**

Fig. 7. In circuits with more than two components, the voltage or current arrows for the individual components can be found, then the final arrow will give the total voltage or current. It's easy when you know how.

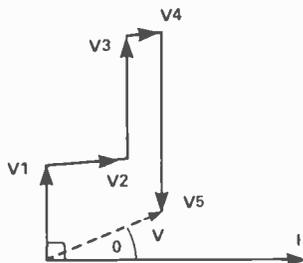

The latest kit innovation!

from Sparkrite

*Sparkrite -
was featured by Shaw Taylor
in "DRIVE IN"*

the quickest fitting
CLIP ON
capacitive discharge
electronic ignition
in KIT FORM



- Smoother running
- Instant all-weather starting
- Continual peak performance
- Longer coil/battery/plug life
- Improved acceleration/top speeds
- Optimum fuel consumption

Sparkrite X4 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 1/73 mins.

Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). The circuit incorporates a voltage regulated output for greatly improved cold starting. The circuit includes built in static timing light, systems function light, and security changeover switch. All kits fit vehicles with coil/distributor ignition up to 8 cylinders.

THE KIT COMPRISES EVERYTHING NEEDED

Die pressed epoxy coated case. Ready drilled, aluminium extruded base and heat sink, coil mounting clips, and accessories. Top quality 5 year guaranteed transformer and components, cables, connectors, P.C.B., nuts, bolts and silicon grease. Full instructions to assemble kit neg. or pos. earth and fully illustrated installation instructions.

NOTE — Vehicles with current impulse tachometers (Smiths code on dial RV1) will require a tachometer pulse slave unit. Price £3.85 inc. VAT, post & packing.

Electronics Design Associates, Dept. ETI 8
82 Bath Street, Walsall WS1 3DE. Phone (0922) 614791

Name _____

Address _____

Phone your order with Access or Barclaycard

Send SAE if brochure only required.

*Including postage and packing UK only

QUANTITY REQ'D.

X4 KIT £16.65 inc. VAT	.
TACHO PULSE SLAVE UNIT £3.85 inc. VAT	

I enclose cheque/PO's for

£ _____

Cheque No. _____

Access or Barclaycard No. _____

More
people in
Britain
buy




than
any
other
electronics
magazine.
Why?

Most magazines have their circulations independently audited according to very strict rules and ETI has just taken over as the largest selling magazine in the field in Britain. Starting as a small "also-ran", ETI has now overtaken mags originally selling four times the number of copies.

Find out why ETI is No. 1 for yourself. Could it be something to do that it's better than the competition?

CLOCK RADIO

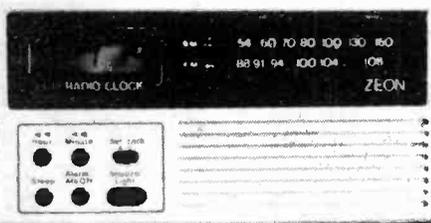

You probably won't believe us as we're selling the goods but we're going to tell you anyway! We have *rejected* eight clock radios for Marketplace, they were all cheap enough but the quality was so poor that we couldn't have lent our name to them. However, we are now able to offer a portable LCD Clock Radio to you which meets our standards.

The clock is a 12-hour one with AM/PM indicated and a back light. The radio is Medium Wave and FM with very nice quality for a small speaker — for FM there's a telescopic aerial. The alarm can be either a 'beep-beep' type or the radio, there's also a snooze facility.

The case is sensibly rugged and is printed on the back with a World Time Zones map, a bit of a cheek really, especially as the time is relative to Japan!

We won't even mention the RRP — but just check on comparable prices — you'll find ours a bargain.

An example of this Clock Radio can be seen and examined at our Charing Cross Road offices.

£17.95

(Inclusive of 15% VAT and Postage).

To:
CLOCK RADIO Offer,
ETI Magazine,
145 Charing Cross Road,
London WC2H 0EE.

Please find enclosed my cheque/PO for £17.95 (payable to ETI Magazine) for my Clock Radio.

Name

Address

Please allow 28 days for delivery.

ETI MA

DIGITAL ALARM



THIS IS THE THIRD digital alarm clock that we are offering (we regret the earlier versions are no longer available). We have sold thousands and thousands of these and our buying power enables us to offer a first rate branded product at a really excellent price.

The Hanimec HC-1100 is designed for mains operation only (240V/50Hz) with a 12 hour display, AM/PM and Alarm Set indicators incorporated in the large display. A switch on the top controls a Dim/Bright display function.

Setting up both the time and alarm is simplicity itself as buttons are provided for both fast and slow setting and there's no problem about knocking these accidentally as a 'locking' switch is provided under the clock. A 9-minute 'snooze' switch is located at the top.

A example of this clock can be seen and examined at our Charing Cross Road offices.

£10.60

(Inclusive of 15% VAT and Postage).

To:
Hanimec Alarm Offer
ETI Magazine
145 Charing Cross Road,
London WC2H 0EE

Please find enclosed my cheque/PO for £10.60 (payable to ETI Magazine) for a Hanimec Digital Alarm Clock.

Name

Address

Please allow 28 days for delivery.

MARKET PLACE

LCD CHRONO



We feel we've got to tell you carefully about this offer which we're introducing for the first time. Why? Because our price is so enormously lower than anywhere else you may suspect the quality.

The display is LCD and shows the seconds as well as the hours — and minutes — press a button and you'll get the date and the day of the week.

Press another button for a couple of seconds and you have a highly accurate stopwatch with hundredths of a second displayed and giving the time up to an hour. There is a lap time facility as well — and of course a back light.

Our Chrono comes complete with a high grade adjustable metal strap and is fully guaranteed.

£11.95

(Inclusive of 15% VAT and Postage).

To:
LCD Watch Offer
ETI Magazine
145 Charing Cross Road,
London WC2H 0EE

Please find enclosed my cheque/PO for £11.95 (payable to ETI Magazine) for my LCD Chronograph.

Name

Address

.....

.....

Please allow 28 days for delivery.

ALARM-CHRONO LCD



This new addition to our unbeatable selection of bargains is no ordinary LCD watch. It's a slim, multi-function, dual time chronograph alarm watch, no less.

This model will show hours, minutes, seconds, date, day of the week, stop watch, split time, alarm and alternate dual time zone — not all at once, of course. There is also a night light.

Hours, minutes, seconds and day of the week are displayed continuously, while the date will appear at the touch of a button. The day of the week is indicated by a flag. When used as a stopwatch, the maximum count is 0.1secs. short of thirteen hours.

£19.95

(Inclusive of 15% VAT and Postage).

To:
ALARM/CHRONO LCD WATCH Offer,
ETI Magazine,
145 Charing Cross Road,
London WC2H 0EE

Please find enclosed my cheque/PO for £19.95 (payable to ETI Magazine) for my Alarm/Chrono LCD watch.

Name


Address

.....

.....

Please allow up to 28 days for delivery.

SPECIALS

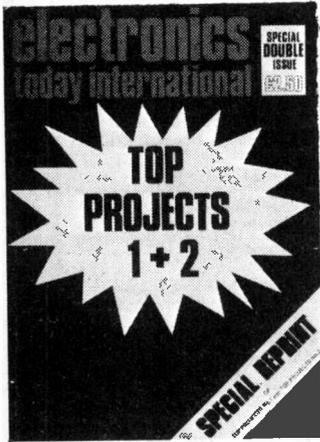

TOP PROJECTS

Book 1 + 2: £2.50 + 25p P&P.

Master mixer, 100W guitar amp, low power laser, printmeter, transistor tester, mixer preamp, logic probe, Ni-Cad charger, loudhailer, scope callibrator, electronic ignition, car theft alarm, turn indicator canceller, brake light warning, LM3800 circuits, temperature alarm, aerial matcher, UHF-TV preamp, metal locator, four input mixer, IC power supply, rumble filter, IC tester, ignition timing light, 50W stereo amp. and many more.

Book 3: SOLD OUT!

Book 4: £1.00 + 25p P&P.

Sweet sixteen stereo amp, waa-waa, audio level meter, expander/compressor, car theft alarm, headlamp reminder, dual-tracking power supply, audio millivoltmeter, temperature meter, intruder alarm, touch switch, push-button dimmer, exposure meter, photo timer, electronic dice, high-power beacon, electronic one-armed bandit...

Book 5: £1.00 + 25p P&P.

5W stereo amp, stage mixer, disco mixer, touch organ, audio limiter, infra-red intruder alarm, model train controller, reaction tester, headphone radio, STD timer, double dice, general purpose power supply, logic tester, power meter, digital voltmeter, universal timer, breakdown beacon, heart rate monitor, IB metal locator, temperature meter...

Book 6: £1.00 + 25p P&P.

Graphic equaliser, 50/100W amp. modules, active crossover, flash trigger, "Star and Dot" game, burglar alarm, pink noise generator, sweep oscillator, marker generator, audio-visual metronome, LED dice, skeet game, lie detector, disco light show...



ELECTRONICS TOMORROW

Comprised entirely of new material, the edition covers such diverse topics as Star Wars and Hi-Fi! The magazine contains projects for everyone — none of which have appeared in ETI — and a look at the future of MPUs, audio, calculators and video. How can you not read it?

75p + 25p P&P.



ELECTRONICS — IT'S EASY

Books 1, 2 & 3.

Our successful beginners series came to an end some time ago now, and the whole series is available from us in reprint form. The three books between them contain all the information presented in the series (sometimes in more detail!) and together form an excellent starting point for anyone interested in learning the art of electronics.

£1.20 + 25p P&P each.

FROM THE PUBLISHERS OF
ELECTRONICS TODAY INTERNATIONAL

ETI CIRCUITS No 2

£1.50

ETI CIRCUITS

Books 1 & 2.

Each volume contains over 150 circuits, mainly drawn from the best of our Tech-Tips. The circuits are indexed for rapid selection and an additional section is included which gives transistor specs, and plenty of other useful data. Sales of this publication have been phenomenal — hardly surprising when the circuits cost under 1p each!

£1.50 + 25p P&P each.

ORDER FROM

Specials Modmags Ltd, 145 Charing Cross Road, London WC2H 0EE

Postage and packing also refer^s to overseas. Send remittance in Sterling only.
Please mark the back of your cheque or PO with your name and address.

**TP7
NOW OUT!
SEE PAGE 45**

from ETI

SUMMER SPECIALS

Special just in full spec. 1702A (intel) £2.00 each p/p 20p. 2526 character generator 9x9 (dual rail) £3.50 p/p 20p. Mostek 4116 (200ns) 16k. Dynamic £8.50 p/p 20p. 74125 (tri-state buffers) 4 for £1.00. P&P 20p.

IS423 STUD MOUNTING RECTIFIERS 10A 400V. Silly price, 10 for £2 p&p 20p.

MC1303L Dual Stereo Preamp, plus data £1 p&p 20p.

7in NYLON CABLE TIES 100 for £1.50 p&p 20p. Cannon 25 way (d-type) male or female with cover plus 2 metres 25 way cable assembled £2.50 each plus p&p 20p.

ML723 (TO100). Monolithic adjustable voltage regulator. Plus or minus 2v-6v, 6v-8v, 8v-37v to 150mA plus data 55p p&p 20p.

PCB KEYBOARD 65mm x 82mm 18 key clickers less key tops, ideal hexadecimal, 35p each, p/p 20p. Hewlett Packard 4 digit displays 12 pin DIL 0.11" common cathode (LED red) £1.50 p/p 20p (few only).

CANNON D-TYPES. Only ones left: 15 way socket 50p, 37 way plug 80p, 50 way socket £1.20, 50 way wire wrap socket £1.30, 25 way ribbon plugs 90p. Cinch 25-way plastic cover 60p, Metal cover and retainer 80p. P/P 20p.

NEW SN76477 sound generator IC (train, plane, explosion, phaser gun etc.) with data, £2.80 + 20p P/P.

HONEYWELL 50 station push button keyboard (query) mounted on PCB 7-bit positive logic. Power requirement +5v 100ma. No other information. Good value. £12.00 each + £1.50 P&P.

SUPERSAVER 1 Price smash — 10K multivibrator electratrim panel mounting pots, 6 for £1, p&p 20p.

SUPERSAVER 2 Hybrid Systems DAC 371-8 (8-bit) DIL packaged + data, ideal MPU users, brand new £2 price smash! now £1.75 each (fraction of original cost) p/p 20p.

SUPERSAVER 3. LM 323K Voltage regulator, 5v at 3-amp, £3.50 each. P&P 20p.

MEMORIES 2708 £6.85, Character Generator MM5240 2560 bit, 64 x 8 x 5 plus data £2.95 (full spec.). P&P 20p. 2112 (200ns) £3.00. P&P 20p. 21L02 (250ns) £1.15. P&P 20p.

SUPERSAVER 4. RS338-383 miniature decade thumbwheel switch £1.35 p/p 20p.

9-WAY MALE/FEMALE connector (Elco 8129) 0.1 inch pitch, PCB mounting ideal for bussing two PCBs together 35p/pair p/p 20p.

LEDS (red) TIL 209 9p, 0.2 10p, Vernitron Ceramic filters FM-4 10.7MHz 45p, BD 236 40p, 2N3055 (TI) 40p, BC183L 10p, BC213L 10p, BF195 10p, 2521V (Dual 128 bit static shift register 65p), RS 12-0-12 50mA sub-miniature transformer £1.35, TM5312BNC (static shift reg) £1.25, LM711CH TO-99 (Voltage comparator) 25p, FPE 100 intra red emitter + data 15p, DIL SWTS 4-way 60p, TBA810S + DATA 65p. P/P 20p.


All enquiries, SAE please. P/P same for quantities except where greater than £1.

Rush orders as some stocks are limited.

Exciting news. Our new retail premises to open soon at 11 Hercies Road, Hillingdon, Middlesex (just off A40). Phone Uxbridge 55399. More details later.

L. B. ELECTRONICS
43 WESTACOTT, HAYES,
MIDDLESEX UB4 8AH, ENGLAND

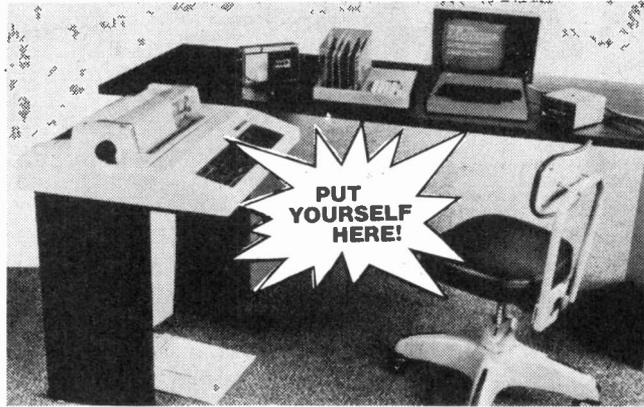HOBBYISTS! ENGINEERS! TECHNICIANS! STUDENTS!



Write and run machine language programs at home, display video graphics on your TV set and design microprocessor circuits — the very first night — even if you've never used a computer before!

ELF II featuring **RCA COSMAC** £79.95
microprocessor/mini-COMPUTER + VAT

THE FASTEST WAY TO LEARN COMPUTER FUNDAMENTALS! Owning an ELF II is probably the fastest, easiest, most foolproof way to gain a working knowledge of computers the world has ever known. First of all, you get your hands on *your own* computer, so you can spend all the time you want with it and use it for anything that turns you on.

Secondly, our *Short Course in Microprocessor And Computer Programming* makes it impossible for you to fail. We take you inside the RCA 1802 and teach you every instruction it can be given. Everything is explained in plain English. When you're finished, you'll know everything there is to know about using an ELF II. You'll be able to make ELF II do whatever you want it to do. You won't be limited to predeveloped software.

Third, once you understand ELF II inside and out, you'll be ready to use its highly sophisticated add-ons intelligently. And, as you expand your ELF II, you'll begin to appreciate just how advanced its technology really is.

In addition to I/O, monitor, memory, ASCII keyboard and BASIC, ELF II offers you exotic add-on features such as the ELF II Light Pen and the ELF II Colour Graphics and Music System.

It's no wonder ELF IIs are being used by schools and universities, factory training programmes, trade schools and R&D Labs.

ELF II and all ELF II add-ons are also available wired and tested. And, as if all that weren't enough, the help that's always available from our Service Department further guarantees your success!

PHONE ORDERS ACCEPTED
Call 01-739 1582

Now Available! Text Editor, Assembler, Disassembler and a new Video Display Board!

The **TEXT EDITOR** gives you word processing ability and the ability to edit assembly language programs while they are displayed on your video monitor. Lines and characters may be quickly inserted, deleted or changed. Add a printer and ELF II can type letters for you — error free — plus insert names and addresses from your mailing list!

ELF II's **ASSEMBLER** translates assembly language programs into hexadecimal machine code for ELF II use. The Assembler features mnemonic abbreviations rather than numerics so that the instructions on your programs are easier to read — this is a big help in catching errors.

ELF II's **DISASSEMBLER** takes machine code programs and produces assembly language source listings. This helps you understand the programs you are working with and improve them when required.

The new **ELF II VIDEO DISPLAY BOARD** lets you generate a sharp, professional 32 or 64 character by 16 line upper and lower case display on your TV screen or video monitor — dramatically improving your unexpanded £79.95 ELF II.



To: NEWTRONICS, HL AUDIO LTD
138 Kingsland Road, London E2 9BY
Please send me the items below

- RCA COSMAC ELF II kit @ £79.95 + VAT and handling (requires 8.3 to 8 volts AC power supply)
- Power Supply (required) £5 + VAT
- RCA 1802 User's Manual £4
- Tom Pittman's Short Course on Microprocessor & Computer Programming (teaches you just about everything there is to know about ELF II or any RCA 1802 computer. Written in non-technical language it's also available for ELF II)

- GIANT BOARD TM kit with cassette I/O, RS 232-C/TTY I/O, 8 bit P/I/O, decoders for 14 separate I/O instructions and a system monitor/editor £39.00 + VAT
- Kleag (Prototype) Board accepts up to 36 ICs £12.33 + VAT
- 4K Static RAM kit. Addressable to any 4K page to 8K £68.44 + VAT
- Gold plated 86-pin connectors (one required for each plug in board) £4 + VAT each
- Expansion Power Supply (required when adding 4K RAM) £19 + VAT
- Professional ASCII Keyboard kit with 128 ASCII upper/lower case set, 96 printable characters, onboard register, parity, logic selection and choice of 4 handshaking signals to mate with almost any computer £30.58 + VAT
- Deluxe metal cabinet for ASCII Keyboard £19.02 + VAT
- Video Display Board kit lets you generate a sharp professional 32 or 64 character by 16 line upper and lower case display on your TV screen or video monitor — dramatically improving your unexpanded £79.95 ELF II. Fits inside ASCII Keyboard cabinet £39.00 + VAT
- ELF II Tiny BASIC on cassette tape. Commands include SAVE, LOAD, ± x → [126 variables A-Z, LET,

- learning breakthrough for engineers and laymen alike. £4
- Deluxe Metal Cabinet with Plexiglas dust cover for ELF II £23.01 + VAT
- I am also enclosing payment (including postage and handling) for the items checked below.
- I want my ELF II wired and tested £98.95 + VAT
- Add £2 p/p for orders over £15

- IF/THEN, INPUT, PRINT, GO TO, GO SUB, RETURN, END, REW, CLEAR, LIST, RUN, PLAT, PEER. Comes fully documented and includes alphanumeric generator required to display alphanumeric characters directly on your TV screen without additional hardware. Also plays tic-tac-toe plus a drawing game that uses ELF II's hex keypad as a joystick. 4K memory required £13.98 + VAT
- Tom Pittman's Short Course on Tiny Basic for ELF II £4
- ELF-SUG TM Deluxe System Monitor on cassette tape. Always displaying the contents of all registers on your TV at any point in your program. Also displays 26 bytes of memory with full addresses, blinking cursor and auto scrolling. A must for the serious programmer! £13.98 + VAT
- Text Editor on cassette tape gives you the ability to insert, delete or edit lines and words from your video monitor. (Add printer and you can use ELF II to type error-free letters plus insert names and addresses from your mailing list) £16.95 + VAT
- Assembler on cassette tape translates assembly language programs into hexadecimal machine code for ELF II use. Mnemonic abbreviations for instructions (rather than numerics) make programs easier to read

Total enclosed £

Charge to: Access Barclaycard

Account No.

and help prevent errors £16.95 + VAT

- Disassembler on cassette tape takes machine code programs and produces assembly language source listings to help you understand and improve your programs on cassette tape £16.95 + VAT
- SAVE 10% Text Editor, Assembler and Disassembler purchased together only £45.76 + VAT
- Requires Video Display Board plus 4K memory
- ELF II Light Pen, assembled and tested £38.99 + VAT
- ELF II Colour Graphics & Music System Board kit £56.95 + VAT
- ELF II connects directly to the video input of your TV set without additional hardware. To connect ELF II to your various terminals instead, order RF Modulator £2.77 + VAT
- Cabling sets: A-D, D-A Converter, Controller Board and more!
- Print Name
- Address

DEALER ENQUIRIES INVITED

SERVICE TRADING CO

WHY PAY MORE?!

MULTI RANGE METERS Type MF16A
A.C./D.C. volts 10, 50, 250, 500, 1000. M.A. 0.5-0.10. 0-100. Sensitivity 2000V. 24 ranges. Dimensions 133 x 93 x 46mm. Price £7.04 plus 50p P&P (£8.10 inc. VAT & P).



TRIAC

Raytheon tag symmetrical Triac. Type Tag 250/500v. 10 amp 500 p.w. Glass passivated plastic triac. Swiss precision product for long term reliability £1.25 P&P 10p (£1.46 inc. VAT & P) (inclusive of date and application sheet). Suitable Disc 22p.

0 to 60 MINUTES CLOCKWORK TIMER.

Double pole 15 amp 230AC. Contacts (no dial). £1.50. P&P 30p (£1.94 inc. VAT & P). N.M.S.

MERCURY SWITCH

Size 27mm x 5mm. 10 for £5.00. P&P 30p. total including VAT £6.72. Min. quantity 10. N.M.S.



230 VOLT AC FAN ASSEMBLY

Powerfully continuously rated AC motor complete with 5 blade 6 1/2" or 4 blade 3" aluminium fan. New reduced price £3.000 P&P 65p. (£3.84 inc. VAT & P). N.M.S.



21-WAY SELECTOR SWITCH with reset coil

The ingenious electro mechanical device can be switched up to 21 positions and can be reset from any position by energising the reset coil 230/240v. A.C. operation. Unit is mounted on strong chassis. Complete with cover. Price £8.51 P&P 75p (£9.76 inc. VAT & P). N.M.S.



VORTEX BLOWER AND VACUUM UNIT

Dynamically balanced totally enclosed 9" rotor with max. air delivery of 1.5 cubic metres per min. Max. static pressure 600mm W.G. Suction or blow from 2 slide-by-side 37mm I.D. circular apertures fitted to base of unit. Powerful continuously rated 115v a.c. motor mounted on alloy base with fixing facilities. Dimensions: Length 22cm x width 25cm x height 25cm. These units are ex-equipment but have had minimum use. Fully tested prior to despatch. Price £12 + £1.50 P&P (£14.58 inc. VAT & P). Suitable transformer for 230/240v a.c. £6 + £1 P&P (£7.56 inc. VAT & P).




TORIN BLOWER

Smith type FFB 1606 022 220/240v A.C. Aperture 10x4 1/2cm overall size 16x14cm. Price £3.75 P&P 75p (incl. VAT £4.88). Other types available. S.A.E. for details. N.M.S.



24V DC BLOWER UNIT

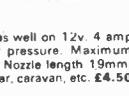USA made. 24v D.C. 8 amp blower that operates well on 12v. 4 amp O.C. producing 30 cu. ft. min. at normal air pressure. Maximum housing dia. 110mm. Depth inc. motor 75mm. Nozzle length 19mm. dia. 22mm. Ideal for cooling mobile equipment, car, caravan, etc. £4.50 P&P 75p (£5.67 inc. VAT & P). N.M.S.



MINIATURE UNISELECTOR

12V. 11 way 4 bank (3 non-bridging, 1 homing). £2.50 P&P 35p (£3.08 inc. VAT & P).



MICRO SWITCHES


Sub min lever m/switch type MML46. 10 for £2.50. Type 3 115M 906T 10 for £2.30 post paid (£2.70 inc. VAT & P).



BF lever operated 20a. c/o. mf. Unimax USA. 10 for £4.00 plus 50p P&P (min. order 10) (£4.88 inc. VAT & P). D.P. C/O lever m/switch, mfg. by Cherry Co. USA. Precious metal, low resistance contacts. 10 for £2.50. P&P 30p. Total inc. VAT £3.02 (min 10). N.M.S.

20LB PULL HEAVY DUTY SOLENOID

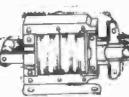Mfg. by Magnetic Devices. 240v A.C. Operation approx. 10lb. pull at 1/4 in. Rating Intermittent. Price £4.75 P&P 71p (£5.94 inc. VAT). N.M.S.



TYPE EYTHER

240v A.C. Solenoid. Approx. 1 lb pull, 1/4 in travel, intermittent rating. Price £1.00 P&P 20p (£1.30 inc. VAT & P). N.M.S.

WESTOOL TYPE MM8 MODEL 2

240V AC. Approx. 1 1/4 lb pull at 1/2 inch. Rating 1 Price £1.50 P&P 20p (£1.84 inc. VAT & P). N.M.S.


240 A.C. SOLENOID OPERATED FLUID VALVE

Rated 1 p.s.i. will handle up to 7 p.s.i. Forged brass body, stainless steel core and spring 1/2 in. b.s.p. inlet, outlet. Precision made. Brush mfg. PRICE £3.50 Post 50p (£4.32 inc. VAT & P). N.M.S.



INSULATION TESTERS (NEW)

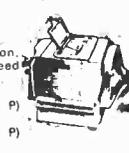Test to I.E.E. spec. Rugged metal construction, suitable for bench or field work, constant speed clutch. Size L 8 in., W. 4 in. H. 6 in., weight 6 lb. 500 VOLTS 500 megohms £49.00 Post 80p (£53.78 inc. VAT & P) 1000 VOLTS 1000 megohms £85.00 Post 80p (£90.26 inc. VAT & P) SAE for leaflet.



YET ANOTHER OUTSTANDING OFFER

New IMFD 600V Dubilier wire ended capacitors. 10 for £1.50 P&P 50p (£2.16 inc. VAT & P). (Min 10). N.M.S.

VARIABLE VOLTAGE TRANSFORMERS

INPUT 230 v. A.C. 50/60 OUTPUT VARIABLE 0/260v. A.C.

BRAND NEW. All types. 200W (1 Amp) fitted A/C volt meter £14.50
0.5 KVA (Max. 2 1/2 Amp) £17.00
1 KVA (Max. 5 Amp) £22.50
2 KVA (Max. 10 Amp) £37.00
3 KVA (Max. 15 Amp) £45.50
5 KVA (Max. 25 Amp) £74.00
10 KVA (Max. 50 Amp) £168.00
17 KVA (Max. 75 Amp) £260.00



Carriage extra

LT TRANSFORMERS

0.10V/15V at 3 amp. (ex new equip) £2.80 P&P 50p (£3.24 inc. VAT) 13.0-13V at 1 amp £2.50 P&P 50p (£3.24 inc. VAT) 25.0-25V at 2 1/2 amp £4.50 P&P 75p (£5.67 inc. VAT & P) 0.4v. 6V. 24V/32V at 12 amp £18.50 P&P £1.90 (£22.03 inc. VAT & P) 0.6V. 12V at 20 amp £14.70 P&P £1.50 (inc. VAT £17.50) 0.12v at 20 amp. or 0.24v at 10 amp £12.00 P&P £1.50 (£14.58 inc. VAT & P) 0.6V/12V at 10 amp. £8.25 P&P £1.25 (inc. VAT £10.26) 0.6V/12V/17V/18V/20V at 20 amp. £19.00 P&P £1.50 (£22.15 inc. VAT & P) 0.10V/17V/18V at 10 amp £10.50 P&P £1.50 (inc. VAT £12.96) Other types in stock. phone for enquiries or send sae for leaflet.

ROTARY VACUUM AIR COMPRESSOR & PUMP

Carbon vane oil-less. 100/115v a.c. 1/12 h.p. motor 50/60 cycle 2875/3450 rpm. 20" vacuum 1.25 c.f.m.. 10 p.s.i. (approx. figures). Mfr. by Gast Co. Fraction of maker's price £14.00 P&P £1.00 (Total: £16.20 inc. VAT). Suitable transformer £3.50 P&P 50p. (£17.38 inc. VAT). N.M.S.



BLOWER/VACUUM PUMP

3 phase A.C. motor 220/250v or 380/440v. 1,425 rpm 1/4 hp cont. Direct coupled to William Alliday Alcosa carbon vane blower/vacuum pump. 0.9 cfm 8 hg. Price £22.00 P&P £2.00 (£25.92 inc. vat + p) N.M.S.

STROBE! STROBE! STROBE!

HY-LIGHT STROBE KIT Mk. IV

Latest type Xenon white light tube. Solid state timing and triggering circuit. 230/240 volt A.C. operation. Speed adjustable 1-20 f.p.s. Designed for large rooms, halls, etc. Light output greater than many (so called 4 Joule) strobes. Price £19.00 post £1 (£21.80 inc. VAT & P). Specially designed case and reflector for Hy-Light £8.80 Post £1.00 (£10.58 inc. VAT & P).

ULTRA VIOLET BLACK LIGHT FLUORESCENT TUBES

6ft. 40 watt £8.70 (callers only). 2ft. 20 watt £8.20. Post 75p (£7.51 inc. VAT & P). (For use in stan. bin fittings). Mini 12in. 8 watt £2.80. Post 35p (£3.40 inc. VAT & P). 9in. 8 watt £2.25. Post 35p (£2.81 inc. VAT & P). 6in. 4 watt £2.25. Post 35p (£2.81 inc. VAT & P). Complete ballast unit. Either 6", 9" or 12" tube 230V. A.C. op. £3.50 plus P&P 45p (£4.27 inc. VAT & P). Also available for 12V D.C. op. £3.80 plus P&P 45p (£4.27 inc. VAT & P).

400w UV lamp and ballast complete £31.50. Post £3 (£34.26 inc. VAT & P) 400w UV lamp only £11.25 Post £1.20 (£13.45 inc. VAT & P).

SQUAD LIGHT

A new conception in light control. Four channels each capable of handling 750 watts of spotlights or dozens of small mains lamps. Seven programs all speed controlled plus flash modulation, effectively giving 14 different displays. Makes sound-to-light obsolete. Completely electrically and mechanically noise free. Price only £60.00 (£65.61 inc. vat + p) S.A.E. (foolscap) for further details. Post 75p



WIDE RANGE OF DISCO LIGHTING EQUIPMENT

S.A.E. (foolscap) for details



XENON FLASH GUN TUBES

Range of Xenon tubes available from stock. S.A.E. for full details.



RELAYS

Wide range of AC and DC relays available from stock. Phone or write in your enquiries.

230/240V A.C. Relays: Arrow. 2 c/o. 15 amp £1.50 (£1.84 inc. VAT & P). T.E.C. open type 3 c/o. 10 amp £1.10 (£1.40 inc. VAT & P). Omoron or Keyswitch 1 c/o. 7 amp £1.00 (£1.30 inc. VAT & P). D.C. Relays: Open type 9/12V 3 c/o 7 amp £1.00 (£1.30 inc. VAT & P). Sealed 12V 1 c/o 7 amp octal base. £1.00 (£1.30 inc. VAT & P). Sealed 12V 2 c/o 7 amp octal base. £1.25 (£1.56 inc. VAT & P). Sealed 12V 3 c/o 7 amp 11-pin. £1.35 (£1.67 inc. VAT & P). 24V. Sealed 3 c/o 7 amp 11-pin. £1.35 (£1.67 inc. VAT & P) (amps = contact rating). P&P on any Relay 20p. Other types available — phone for details. N.M.S.

Diamond H heavy duty A.C. relay 230/240V a.c.. two c/o contacts 25 amps res at 250V a.c. £2.50 P&P 50p (£3.24 inc. VAT & P&P). Special base 50p.

VAT AT CURRENT RATE MUST BE ADDED TO ALL ORDERS FOR THE TOTAL VALUE OF GOODS INCLUDING POSTAGE UNLESS OTHERWISE STATED

GEARED MOTORS

100 R.P.M. 115 lbs. ins.!!

115 lb. ins., 110 volt, 50Hz. 2.8 amp. single phase. split capacitor motor. Immense power. Continuously rated. Totally enclosed. Fan cooled. In-line gear box. Length 250mm. Dia. 135mm. Spindle Dia. 15.5mm. Spindle 11.5mm. ex-equipment tested £12.00 Post £1.50 (£14.58 inc. VAT & P). Suitable transformer 230/240 volt £8.00 Post 75p (£9.45 inc. VAT & P) R&T



GEARED MOTORS

28 r.p.m., 20lb. inch 115v a.c. Reversible motor. 71 r.p.m., 10 lb. inch. 115v a.c. Reversible motor. Both types similar to above drawing. Price either type £4.75 + 75p P&P (£5.84 inc. VAT & P&P) Supplied with transformer for 240v a.c. operation £7.25 + P&P £1. (£8.81 inc. VAT & P&P). N.M.S.

FRACMO MOTOR

58rpm 50lbs inch 240vAC reversible, 0.7 amp. sharp length 35mm. dia. 16mm. weight 6 kilos 600 grams. Price £15.00 P&P £1.50 (£17.82). N.M.S.



PARVALUX MOTOR TYPE S.D.2

12V DC shunt 1/30th ph motor. Continuously rated 4000 rpm. Price £10.00 P&P 75p (£11.61 inc. VAT & P). N.M.S.

PARVALUX 230/250V a.c. MOTOR

Type SD18 240V AC reversible 30 rpm 50lbs inch. Price £15.00 P&P £1.50 (£17.82 inc. VAT). N.M.S.



CITENCO

FHP motor type C 7333/15 220/240v A.C. 19 rpm reversible motor, torque 14.5 kg. Gear ratio 144:1. Brand new incl. capacitor, our price £14.25 + £1.25 P&P (£16.74 inc. VAT & P). N.M.S.



CRUZEY — 230/240V AC 2 rpm synchronous geared motor £2.90 P&P 30p (Total £3.46 inc. VAT). N.M.S.

HAYDON — 230/240V AC 1 rpm synchronous geared motor £2.90 P&P 30p (Total £3.46 inc. VAT). N.M.S.

REVERSIBLE MOTOR 230V A.C.

General Electric 230V A.C., 1,600 r.p.m., 0.25 amp. Complete with anti-vibration mounting bracket and capacitor. O/A size 110mm x 90mm. Spindle 5/16 dia. reversing. Ex-equipment tested £3.00. Post 50p (£3.78 inc. VAT & P).

12V DC GEARED MOTOR

Precision built miniature motor. 6/12V DC operation. Incredibly powerful for size. Approx speed at 6V 60 rpm 40 ma Approx speed at 9V 80 rpm 50 ma Approx speed at 12V 120 rpm 60 ma Size 27mm dia. 38mm length, weight 55 gram. Drive spindle 5 mm x 2 mm dia. Price: £2.50 post paid (£2.70 incl. VAT)

METERS (New) — 90mm DIAMETER

AC Amp., Type 62T2. 0-1A, 0-5A, 0-20A. AC Volt. 0-15V, 0-300V. DC Volt. Type 65C5. 0-2A, 0-10A, 0-20A, 0-50A. DC Volt. 0-15V, 0-30V. All types £3.50 ea. + P&P 50p (£4.32 incl. VAT). 0-50A D.C. 0-100A D.C. Price £5.00 + 50p P&P £5.94 incl. VAT)



'VENNER TYPE' ERD TIME SWITCH

200/250V AC 30 amp. 2 on / 2 off every 24 hrs. at any manually pre-set time. 36-hour spring reserve and day emitting device. Built to highest Electricity Board specification. Price £7.75 P&P 75p (£9.18). R & T.



SANGAMO WESTON TIME SWITCH

Type S251 200/250V AC 2 on / 2 off every 24 hours. 20 amps contacts with override switch, diameter 4" x 3". price £6.00 P&P 50p (£7.02 inc. VAT & P). Also available with Solar dial. R & T.

AEG TIMESWITCH

200/250V AC 1 on / 1 off every 24 hours. 80 amp contact (ideal storage heaters) Spring reserve £10.00 P&P 50p (Total: £11.34 inc. VAT). N.M.S.

AC MAINS TIMER UNIT

Based on an electric clock, with 25 amp, single-pole switch, which can be preset for any period up to 12 hrs. ahead to switch on for any length of time, from 10 mins. to 6 hrs. then switch off. An additional 60 min. audible timer is also incorporated. Ideal for Tape Recorders, Lights, Electric Blankets etc. Attractive satin copper finish. Size 135 mm x 130 mm x 60 mm. Price £2.25. Post 40p (Total inc. VAT & Post £2.87). N.M.S.



POWER RHEOSTATS

New ceramic construction, vitreous enamel embedded winding, heavy duty brush assembly, continuously rated.

25 WATT 10 25 100 150 250 500 1k 1.5k ohm £2.40 Post 20p (£2.81 inc. VAT & P) 50 WATT 250 ohm £2.90 Post 25p (£3.40 inc. VAT & P) 100 WATT 1 5 10 25 50 100 250 500 1k 1.5k 2.5k 5k ohm £5.90 Post 35p (£6.75 inc. VAT & P)

Black Silver Skirted Knob calibrated in Nos 1-9 1 1/2 in dia brass bush. Ideal for above Rheostats 24p ea.

SPECIAL OFFER

BERCO type L RHEOSTAT 85 ohm 300 watt 1.86 amp £7.50 P&P 50p (Total £8.64 inc. VAT) N.M.S.

FRACMO MOTOR

1400 rpm. HP 1/30 continuously rated 115V AC fitted with anti-vibration cradle mounting. Supplied complete with transformer for 230/240V AC op. £10.00 P&P £1.00 (Total: £11.88 inc. VAT). N.M.S.

N.M.S. — New Manufacturers' Surplus. R & T — Reconditioned and Tested

ACCOUNT CUSTOMERS

MIN. ORDER £10.00

ALL MAIL ORDERS, ALSO CALLERS AT:

57 BRIDGMAN ROAD, CHISWICK, LONDON, W4 5BB. Phone: 01-995 1560 Closed Saturdays

SHOWROOMS NOW OPEN AMPLÉ PARKING


SERVICE TRADING CO.

PERSONAL CALLERS ONLY

9 LITTLE NEWPORT STREET, LONDON, WC2H 7JJ Tel. 01-437 0576

A useful item of test gear designed with the audio constructor in mind.

BENCH AMPLIFIER

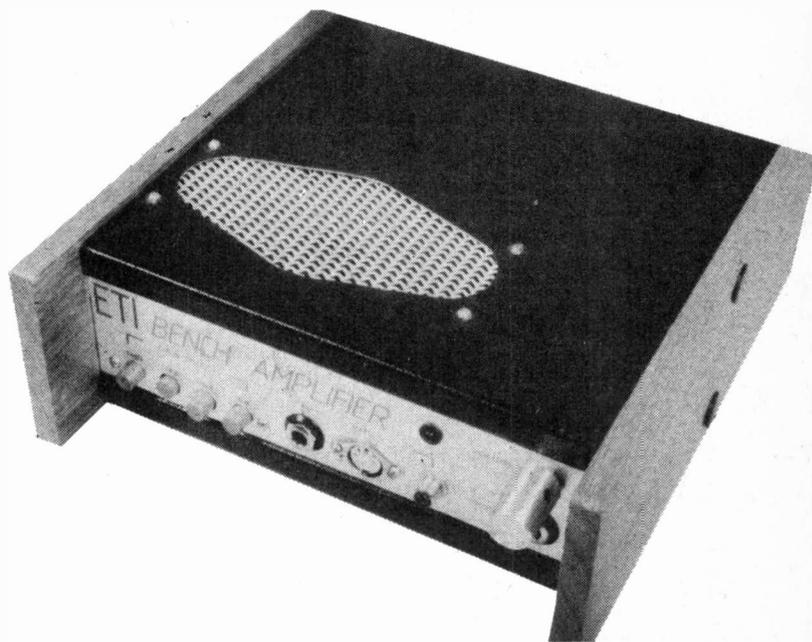

AN ESSENTIAL PIECE of equipment for any electronics workshop is an audio amplifier — useful for testing and checking other audio circuits. Ideally the amplifier should allow for a reasonably wide range of input signals and be adaptable for various outputs. The bench amplifier described here fulfills these criteria.

There are four inputs: (i) a high gain, flat response, intended for use with microphone or guitar, (ii) a phono (disc) input with RIAA equalisation, (iii) a medium gain, flat response for ceramic cartridge or tuner, (iv) an attenuated, flat response, for tape output.

Coupled with the master volume control the preamplifier section should cater for most audio signals.

A pre-amplifier output is obtainable (see case photograph) and

also an extension speaker outlet via necessary output sockets on the rear panel. Also provided is a low level power output suitable for headphones.

Construction

The prototype was constructed with various input connectors wired in parallel, 5 pin Din, ¼ inch Jack and Phono. This means that an input can be accepted from a signal lead with any of those three connector plugs. More can be added to personal preference, but it was felt that the chosen three would cover the majority of input functions.

The PCB is relatively uncluttered. Links 1 and 2 are provided to cut off the power supply to IC2 and IC3, the pre-amp and power amp stages. This may be useful in setting up and testing which can be done in three

stages — the power supply, the power amplifier and finally the pre-amplifier.

Note that IC2 and IC3 are inserted into the board in opposite directions.

SW2 consists of four two pole changeover switches soldered directly onto the PCB, thus alleviating wiring-up problems. Different sizes are obtainable so make sure that you obtain the correct ones.

Use screened cable for input and pre-amp output and also for the lead to the volume control, to minimise mains hum.

Our finished amplifier had all input sockets, the selector switch, volume control, power indicator and the headphone socket on the front panel, with the output sockets on the rear.

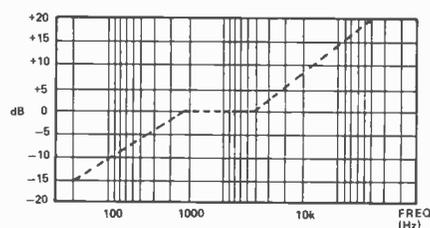


Fig. 1. Showing the variation of recorded signal with frequency.

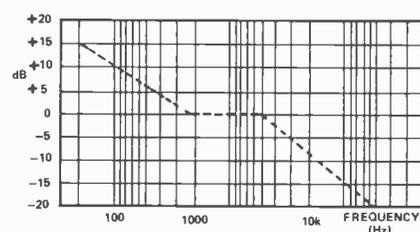


Fig. 2. Recorded playback signal attenuation with frequency.

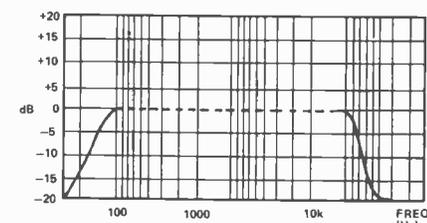


Fig. 3. Theoretical flat response output after pre-amp stage with associated equalization network.

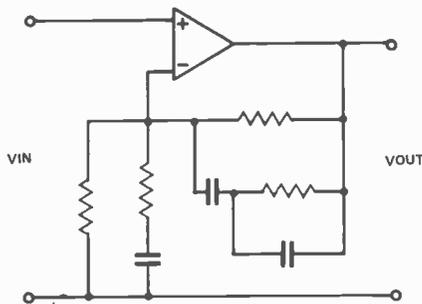
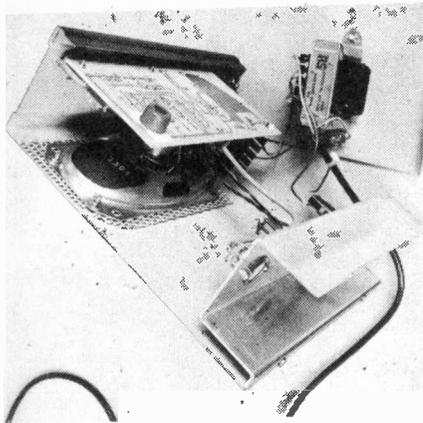


Fig. 4. An operational amplifier with equalization circuitry in its feedback loop.

HOW IT WORKS

The preamplifier section is formed around the LM 381 dual operational amplifier. One channel is used as a magnetic phono pre-amp with equalisation to RIAA characteristics. For the uninitiated amongst us, RIAA (Record Industry Association of America) equalisation is necessary in the playback stage of recordings made on record, to counteract the effect added to the signal in the recording stage. Figure 1 shows the kind of effect. It is a graph of recorded signal vs frequency.

On playback, it is now necessary to have an amplifying stage which has a diminishing response with higher frequency as in Fig. 2. The overall effect is to produce an output as shown in Fig. 3 where the signal amplitude does not vary (apart from the inaudible extremities) with frequency — a flat response. The underlying theory for such a complicated system is that of high frequency noise. When the recorded signal has its higher frequency sounds amplified its noise is not, whereas at the playback stage, all frequencies at the top end of the scale are diminished; noise included. The final output, therefore, has theoretically less noise i.e. the signal/noise ratio has been increased.

The usual way to reproduce the graph in Fig. 2 is to use an amplifier with frequency dependent components in its feedback loop so that it amplifies bass frequencies more than treble. (See Fig. 4).

The other half of the chip is used as a high gain amplifier with an essentially flat response. This input suits microphones or electric guitars.

The medium gain input from a ceramic cartridge or a tuner is fed straight through to the power amp, the line input being attenuated by R11, 12 before being taken to the power output stage.

Switch SW2 a, b provide necessary switching between the I/P and O/P of the preamplifier stage.

The power amplifier consists of a standard LM 380 IC power amp with the usual supply decoupling capacitor C14 and network R14, C16, to eliminate possible oscillations.

R15 drops the O/P power to a suitable level for headphones.



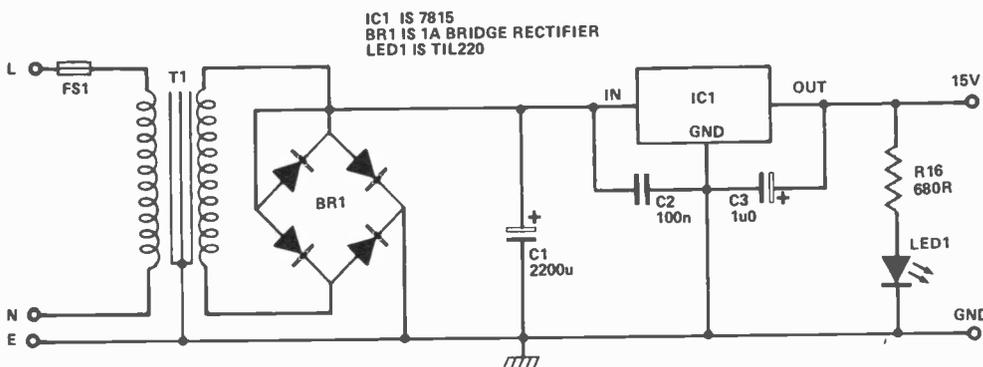


Fig. 5. Circuit diagram of the power supply.

Fig. 6. Main circuit diagram of the Bench Amplifier.

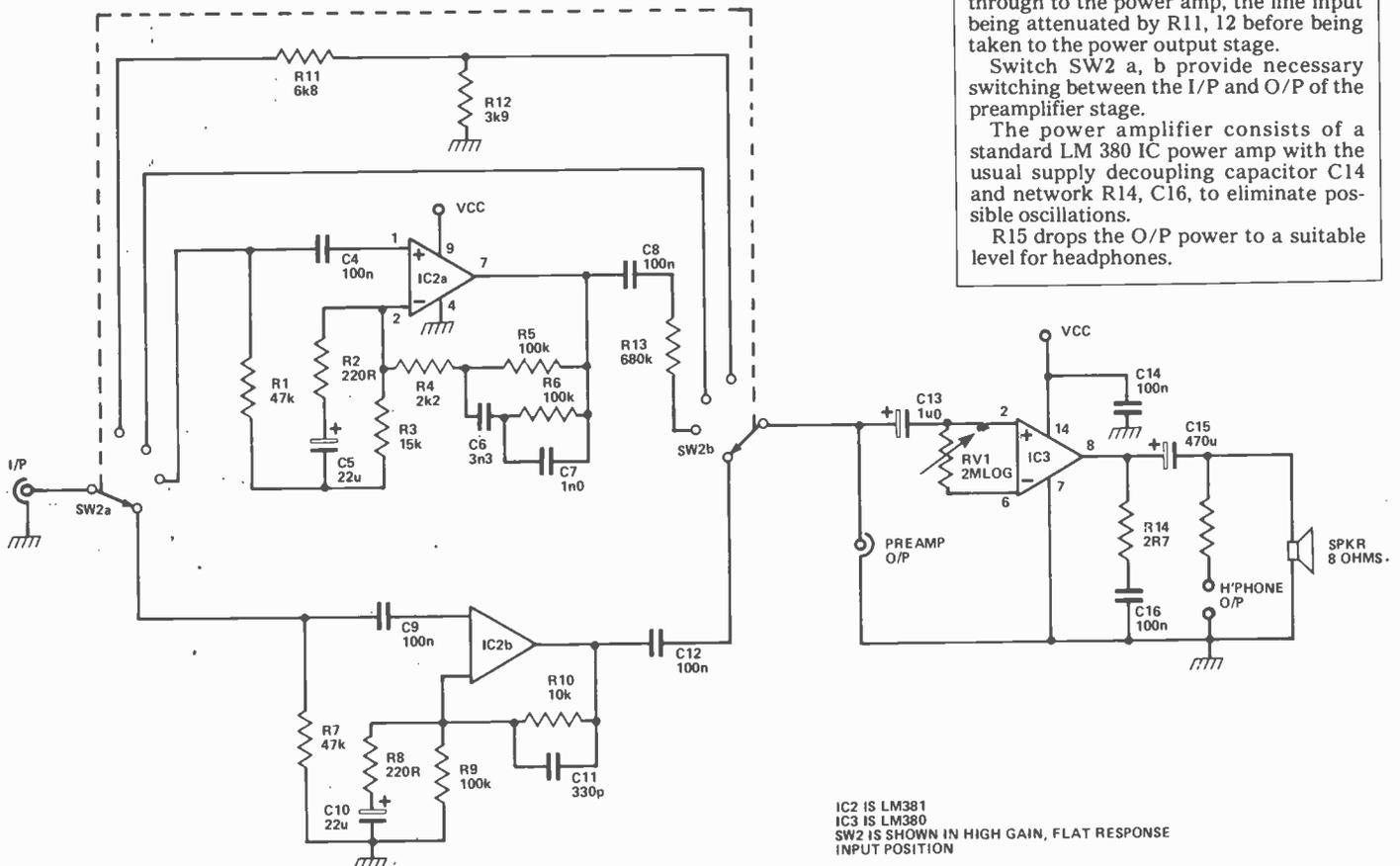

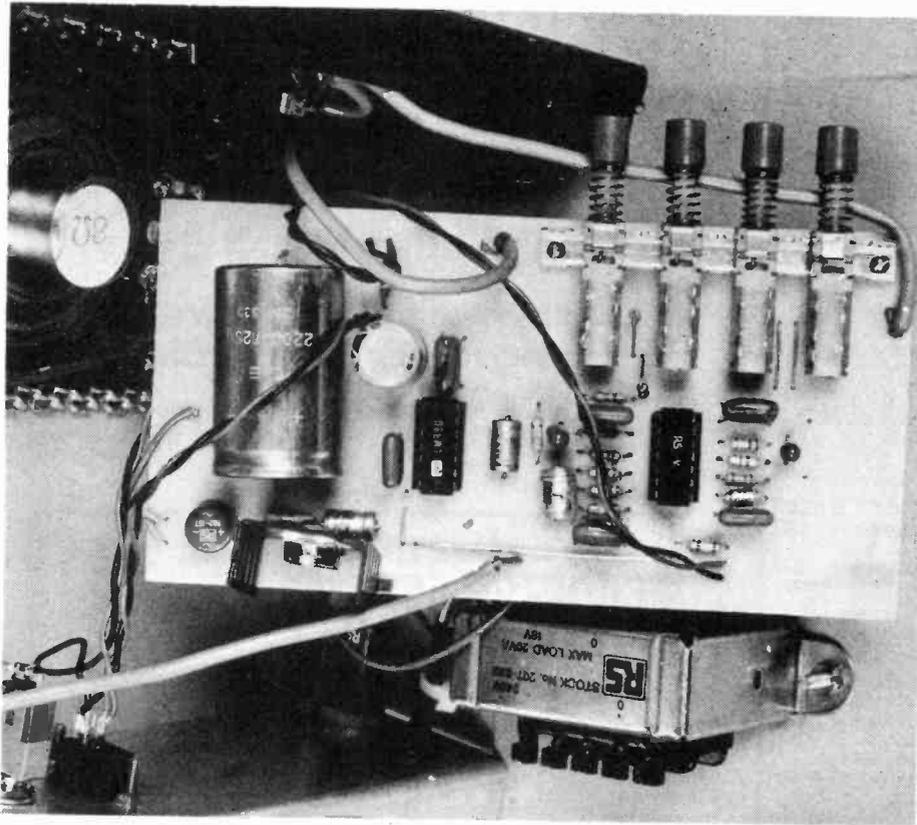IC2 IS LM381
IC3 IS LM380
SW2 IS SHOWN IN HIGH GAIN, FLAT RESPONSE INPUT POSITION



BUYLINES

There is nothing in the circuit which should present any difficulty in obtaining, except the correct size switches for SW2 a, b. We advise

that you take your circuit board with you when you buy the switch, and then you will be certain of getting the right ones.

PARTS LIST

RESISTORS ALL 1/4W 5%

R1, 7	47k
R2, 8	220R
R3,	15k
R4	2k2
R5, 6, 9	100k
R10	10k
R11	6k8
R12	3k9
R13	680k
R14	2R7
R15	100R
R16	680R

POTENTIOMETERS

RV1	2M Log
-----	--------

CAPACITORS

C2, 4, 8, 9,	
12, 14, 16	100n polyester
C3, 13	1u 16V electrolytic
C5, 10	22u 16V tantalum
C6	3n3 polyester
C7	1n polyester
C11	330p polystyrene
C15	470u 16V


SEMICONDUCTORS

IC1	7815
IC2	LM381
IC3	LM380
BR1	1A bridge rectifier
LED 1	TIL 220

MISCELLANEOUS


T1	18V 1A mains transformer
FS1 and holder	250 mA
I/P and O/P sockets	
8 ohm speaker	
SW2	4 off 2 pole changeover push switches and mounting bracket case to suit

Fig. 7. Component overlay.

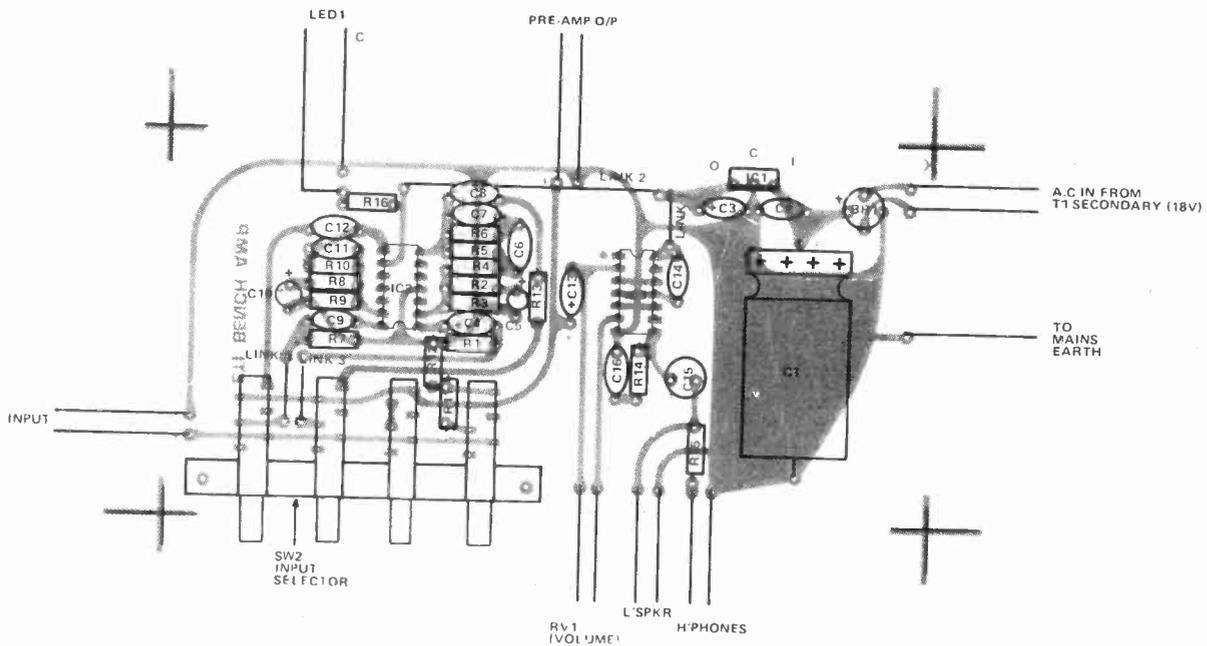

Two Bytes Are Better Than One

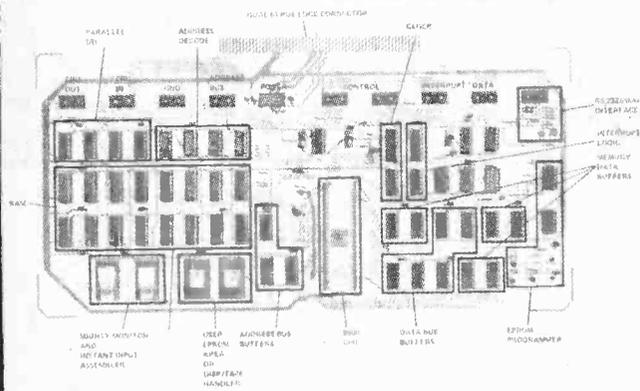TECHNICO SUPER STARTER SERIES 16-BIT MICRO-COMPUTER



SYSTEM CPU OR STAND ALONE MICROCOMPUTER

- 1.8" x 16" PC Board
- T19900 16-bit CPU
- 16 parallel individually addressable input bits
- 16 parallel individually addressable output bits
- DUAL 61^{nm} buss backplane edge connector and 10 16 pin socket connectors
- Operating Debug Monitor with 12 user commands (1K Byte)

STATIC MEMORY EXPANSION MODULE

- PC Module with DUAL 61^{nm} buss edge connector
- Memory Write Protect
- Can be expanded to 32K Bytes on board
- Assembled board includes sockets for 32K Bytes

INTELLIGENT FLOPPY DISK CONTROLLER

- Intelligent Controller which supports up to four SADD

T99SS-U £236
T99SS-A £347

- RS232 and 20 ma current loop I/O port
- 512 Bytes RAM (expandable to 2K Bytes)
- Fully socketed for additional 1.5K Bytes of RAM, and 3K Bytes of E-PROM
- 8 Vector Interrupts
- E-PROM Programmer for 2708 E-PROMS

T99ST-32KB-U £629
T99ST-32KB-A £840
T99ST-16KB-U £454
T99ST-16KB-A £586

- Unassembled board includes sockets for 16K Bytes
- Starting address is DIP Switch selectable
- CRU bit bank select for system memory expansion above 65K Bytes

T99FDC-A £645

- DUAL 61^{nm} buss edge connector

PICO BYTE PICO BYTE 65 Victory Close, Bristol Rd. Birmingham B5 7UT Tel. 021-440 5631

Another Crofton First Brand New Full Specification

10" Metal Cased Industrial Video Monitor

£118.80
Inc. to Personal Callers-Subject to availability.

Video Bandwidth 8MZ (3db down).
Ideal for Computer Terminal or General Video Monitor.
Complete With Own Power Supply.
Input Sensitivity IV Composite.

The unbeatable
CROFTON 6800 MICRO
is probably the best
value for money today

* Including Tiny Basic and on board Prom Programmer
— KIT* —
£220
+ VAT & P/P

POWER SUPPLY £20 EXTRA +VAT & P/P

CROFTON Electronics Limited
35 Grosvenor Road, Twickenham Middlesex • Tel: 01-891 1923

PETALECT

ELECTRONIC SERVICING LTD.

PET 2001/8 micro-computer

£550 + V.A.T.

WHY BUY A MICRO COMPUTER FROM US? BECAUSE:

- 1) Established Company trading since 1971.
- 2) Electronic servicing is our speciality.
- 3) We have in house programmers / systems analysts.
- 4) We have our own service engineers.
- 5) We will demonstrate the PET at your premises.
- 6) We can customise the PET to your requirements.
- 7) We can arrange finance.
- 8) We offer, after the three month warranty, an annual service contract from £69.50.
- 9) You benefit from our experience of having sold over 150 Micro Computers to industrial, educational and business, personal users.

VISIT OUR SHOWROOM AT: 34 Chertsey Road, Woking, Surrey

We supply the full range of C.B.M. PET Micro-computers. We also supply:

Dual Floppy Disks	£840
24K Memory Boards	£320
All types of Printers	from £450

All types of Printer Interfaces, Electronic balance Interfaces, Programs from C.B.M., Petsoft, Gemsoft. We also offer a full consultancy and programming service. We are developing a number of our own business packages for all applications. Books on Basic, Programming, Interfacing, etc. Full range of KIMs available. Tandy and ITT 2020 available. Maintenance, Hire Purchase facilities as well as ACCESS and BARCLAYCARD available.

Factory: Telephone WOKING 69032/68497/20727. Shop: Telephone: WOKING 23637.

electronics today

international

What to look for In the September Issue: On sale August 3rd



Made your contribution to Confuse-a-Car Week yet? Jog your jalopy's geriatric innards into thinking it's Christmas by giving it one of our car projects.

Now that the Great British Summer's here again, you'll need our heated rear window controller. Hit the button and the wonderful window warmer heats your hindsight for a respectable screen-clearing interval and then switches off again.

Or there's a warning lamp audible repeater. If you're in the habit of driving with your eyes closed (clunk click every trip) you won't see your oil or ignition warning lamps come on. With our repeater you'll hear them.

We're also planning an LED temperature gauge. Watch your radiator blow its top in full technical-our. . . . Next month in motoring ETI.

SATELLITE SPECIAL

The satellite age dawned in 1957 with Sputnik 1. Since then thousands of tons of hardware have been blasted into orbit around us.

The satellites we have now, a little more sophisticated than Sputnik, monitor our weather, let us look in on a foreign war or the American Open as it happens, take navigation out of the realms of sun and sextant and many more applications, including a few that are distinctly hush-hush.

Next month Ian Graham looks skywards and brings the eye-in-the-sky down to earth.

LM10? What In The Name Of ETI Is An LM10?

Until last month very few people had even heard of the LM10. In a few more months not having done so will be a bigger disgrace than supporting Chelsea. Ray Marston produces one of his special features to help you out of the second division next month, so don't miss it.

KEEP IT QUIET, DON'T HISS AND GET IT TAPED PROPERLY

No it's not Dolby. It is based on a brand new chip set from National. It has an amazing low component count. It turns in a very respectable 'sound' and is ideal for home usage. It is inexpensive and a very good reason to buy ETI next month.

DIODES/ZENERS			
QTY.			
1N914	100v	10mA	.05
1N4005	600v	1A	.08
1N4007	1000v	1A	.15
1N4148	75v	10mA	.05
1N4733	5.1v	1 W Zener	.25
1N4749	24v	1W	.25
1N753A	6.2v	500 mW Zener	.25
1N758A	10v	"	.25
1N759A	12v	"	.25
1N5243	13v	"	.25
1N5244B	14v	"	.25
1N5245B	15v	"	.25
1N5349	12v	3W	.25

SOCKETS/BRIDGES			
QTY.			
8-pin	pcb	.16 ww	.35
14-pin	pcb	.20 ww	.40
16-pin	pcb	.25 ww	.45
18-pin	pcb	.30 ww	.95
20-pin	pcb	.35 ww	1.05
22-pin	pcb	.40 ww	1.15
24-pin	pcb	.45 ww	1.25
28-pin	pcb	.50 ww	1.35
40-pin	pcb	.55 ww	1.45
Molex pins	.01 To-3 Sockets		.35
2 Amp Bridge	100-prv		.95
25 Amp Bridge	200-prv		1.50

TRANSISTORS, LEADS, etc.			
QTY.			
2N2222M	(2N2222 Plastic .10)		.15
2N2222A			.19
2N2907A	PNP		.19
2N3906	PNP (Plastic)		.19
2N3904	NPN (Plastic)		.19
2N3054	NPN		.55
2N3055	NPN 15A 60v		.60
T1P125	PNP Darlington		1.95
LED Green,	Red, Clear, Yellow		.19
D.L.747	7 seg 5/8" High com-anode		1.95
MAN72	7 seg com-anode (Red)		1.25
MAN3610	7 seg com-anode (Orange)		1.25
MAN82A	7 seg com-anode (Yellow)		1.25
MAN74	7 seg com-cathode (Red)		1.50
FND359	7 seg com-cathode (Red)		1.25

9000 SERIES			
QTY.		QTY.	
9301	.85	9322	.65
9309	.50	9601	.30
		9602	.45

C MOS							
QTY.		QTY.		QTY.		QTY.	
4000	.15	4017	.75	4034	2.45	4069/74C04	.45
4001	.20	4018	.75	4035	.75	4071	.25
4002	.25	4019	.35	4037	1.80	4081	.30
4004	3.95	4020	.85	4040	.75	4082	.30
4006	.95	4021	.75	4041	.69	4507	.95
4007	.25	4022	.75	4042	.65	4511	.95
4008	.75	4023	.25	4043	.50	4512	1.50
4009	.35	4024	.75	4044	.65	4515	2.95
4010	.35	4025	.25	4046	1.25	4519	.85
4011	.30	4026	1.95	4047	2.50	4522	1.10
4012	.25	4027	.35	4048	1.25	4526	.95
4013	.40	4028	.75	4049	.65	4528	1.10
4014	.75	4029	1.15	4050	.45	4529	.95
4015	.75	4030	.30	4052	.75	MC14409	14.50
4016	.35	4033	1.50	4053	.95	MC14419	4.85
				4066	.75	74C151	2.50

MICRO's, RAMS, CPU's, E-PROMS	
QTY.	
8T13	2.50
8T23	2.50
8T24	3.00
8T97	1.75
74S188	3.00
1488	1.25
1489	1.25
1702A	4.50
AM 9050	4.00
ICM 7207	6.95
ICM 7208	13.95
MPS 6520	10.00
MM 5314	4.00
MM 5316	4.50
MM 5387	3.50
MM 5369	2.95
TR 1602B	3.95
UPD 414	4.95
Z 80 A	22.50
Z 80	17.50
Z 80 P10	10.50
2102	1.45
2102L	1.75
2107B-4	4.95
2114	9.50
2513	6.25
2708	11.50
2716 D.S.	34.00
2716 (5v)	69.00
2758 (5v)	26.95
3242	10.50
4116	11.50
6800	13.95
6850	7.95
8080	7.50
8085	22.50
8212	2.75
8214	4.95
8216	3.50
8224	4.25
8228	6.00
8251	7.50
8253	18.50
8255	8.50
TMS 4044	9.95

- T T L -											
QTY.		QTY.		QTY.		QTY.		QTY.		QTY.	
7400	.20	7492	.45	74H20	.25	74LS76	.70				
7401	.20	7493	.35	74H21	.25	74LS86	.95				
7402	.20	7494	.75	74H22	.40	74LS90	.85				
7403	.20	7495	.60	74H30	.30	74LS93	.85				
7404	.20	7496	.80	74H40	.35	74LS96	2.00				
7405	.35	74100	1.15	74H50	.30	74LS107	.90				
7406	.25	74107	.35	74H51	.30	74LS109	1.50				
7407	.55	74121	.35	74H52	.20	74LS123	1.95				
7408	.20	74122	.55	74H53	.25	74LS138	2.00				
7409	.25	74123	.55	74H55	.25	74LS151	.95				
7410	.20	74125	.45	74H72	.35	74LS153	1.15				
7411	.25	74126	.45	74H74	.35	74LS157	1.15				
7412	.25	74132	.75	74H101	.95	74LS160	1.15				
7413	.45	74141	.90	74H103	.55	74LS164	2.90				
7414	.75	74150	.85	74H106	1.15	74LS193	2.00				
7416	.25	74151	.95	74L00	.30	74LS195	1.15				
7417	.40	74153	.95	74L02	.30	74LS244	2.90				
7420	.25	74154	1.15	74L03	.35	74LS259	1.50				
7426	.25	74156	.70	74L04	.40	74LS298	1.50				
7427	.25	74157	.65	74L10	.30	74LS367	1.95				
7430	.20	74161/9316	.75	74L20	.45	74LS368	1.25				
7432	.30	74163	.85	74L30	.55	74LS373	2.50				
7437	.20	74164	.75	74L47	1.95	74S00	.45				
7438	.30	74165	1.10	74L51	.65	74S02	.45				
7440	.20	74166	1.75	74L55	.85	74S03	.35				
7441	1.15	74175	.90	74L72	.65	74S04	.35				
7442	.55	74176	.95	74L73	.70	74S05	.45				
7443	.45	74177	1.10	74L74	.75	74S08	.45				
7444	.45	74180	.95	74L75	1.05	74S10	.45				
7445	.75	74181	2.25	74L85	2.00	74S11	.45				
7446	.70	74182	.75	74L93	.75	74S20	.35				
7447	.70	74190	1.25	74L123	1.95	74S22	.55				
7448	.50	74191	1.25	74LS00	.40	74S40	.30				
7450	.25	74192	.75	74LS01	.40	74S50	.30				
7451	.25	74193	.85	74LS02	.45	74S51	.35				
7453	.20	74194	.95	74LS03	.45	74S64	.15				
7454	.25	74195	.95	74LS04	.45	74S74	.70				
7460	.40	74196	.95	74LS05	.45	74S112	.60				
7470	.45	74197	.95	74LS08	.45	74S114	.85				
7472	.40	74198	1.45	74LS09	.45	74S133	.85				
7473	.25	74221	1.50	74LS10	.45	74S140	.75				
7474	.30	74298	1.50	74LS11	.45	74S151	.95				
7475	.35	74367	1.35	74LS20	.45	74S153	.95				
7476	.40	75491	.65	74LS21	.45	74S157	.98				
7480	.75	75492	.65	74LS22	.45	74S158	.80				
7481	.85	74H00	.20	74LS32	.50	74S194	1.50				
7482	.95	74H01	.30	74LS37	.45	74S196	2.00				
7483	.95	74H04	.30	74LS38	.65	74S257 (8123)	2.50				
7485	.75	74H05	.25	74LS40	.70	8131	2.75				
7486	.55	74H08	.35	74LS42	.95						
7489	1.05	74H10	.35	74LS51	.75						
7490	.55	74H11	.25	74LS74	.95						
7491	.70	74H15	.45	74LS75	1.20						

I ² L, LINEARS, REGULATORS, ETC.					
QTY.		QTY.		QTY.	
MCT2	.95	LM320K24	1.65	LM373	3.95
8038	3.95	LM320T5	1.65	LM377	3.95
LM201	.75	LM320T12	1.65	78L05	.75
LM301	.45	LM320T15	1.65	78L12	.75
LM308	.65	LM323K	5.95	78L15	.75
LM309H	.85	LM324	1.25	78M05	.75
LM309 (340K-5)	1.50	LM339	.75	LM380 (8-14 Pin)	1.19
LM310	.85	7805 (340T5)	1.15	LM709 (8-14 Pin)	.45
LM311 (8-14 Pin)	.75	LM340T12	.95	LM711	.45
LM318	1.50	LM340T15	.95	LM723	.40
LM320H6	.79	LM340T18	.95	LM725	2.50
LM320H15	.79	LM340T24	.95	LM739	1.50
LM320H24	.79	LM340K12	1.25	LM741 (8-14)	.45
7905 (LM320K5)	1.65	LM340K15	1.25	LM747	1.10
LM320K12	1.65	LM340K18	1.25	LM1307	1.75
LM320K15	1.65	LM340K24	1.25	LM1458	.65

LM3900	.95
LM75451	.65
NE555	.45
NE556	.85
NE565	1.15
NE566	1.25
NE567	.95
TA7205	6.95
76477	2.95
95H90	9.95

CABLE ADDRESS: ICUSD

Telex #697-827 ICUSD SDG

ODD ODES

A diode, the electronic one way street, is a versatile component. This tiny piece of crystal engineering can rectify AC signals, limit voltage, emit light or tune your radio. Ian Sinclair explains

IF YOU COMPARE a resistor to a crowded road and a capacitor to a multistory car park, then a diode is the nearest thing electronically to a one-way street. A diode has two terminals (the di-part of the name simply means two) and the current flows only when one of them, the anode, is more positive than the other, the cathode. This direction of current flow, anode to cathode, is called the forward direction and doesn't obey Ohm's Law. That means that we can't calculate how much current will flow simply by measuring the forward voltage and knowing a single figure of resistance of the diode, R . There are two features of the way in which a diode conducts which makes it quite different from a resistor. One is that current doesn't start to flow whenever the anode is positive to the cathode, only when the voltage is greater than about 0.5 V (for silicon diodes) or 0.15 V (for germanium diodes). The other feature is that, once the diode is conducting, its resistance drops as the current increase. The drop in resistance is so great that the voltage across a forward conducting diode is almost constant, around 0.55 V, even if the current changes considerably. For silicon diodes, a very useful rule of thumb is that the voltage changes by only 60 mV for a tenfold change of current. This means, for example, that if the voltage across a diode is 0.55 V when 1 mA is flowing, then increasing the diode current to 10 mA will raise the voltage by only 60 mV to 0.61 V. If the diode obeyed Ohm's Law, then a tenfold increase in current would cause a tenfold increase in voltage. In our example, a resistor which had a voltage of 0.55 V across it with 1 mA flowing (a 550R resistor) would have 5.5 V across it when 10 mA flowed. Diodes just don't behave that way.

Characteristics

If we can't use Ohm's Law then, what do we do? The answer is that we have to use characteristics, graphs which show how much current flows at each value of voltage. A full set of characteristics for a diode is quite an impressive sheaf of documents, but the two that are of most interest to us are the forward characteristic and the reverse characteristic. The forward characteristic shows how much current will flow at each value of forward voltage and at what voltage current can be expected to start flowing. The reverse characteristic shows how

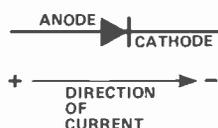


Fig. 1. Symbol for a diode. The arrowhead on the symbol shows the conventional direction of current (+ to -) through the diode.

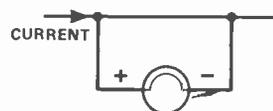


Fig. 2. Measuring the forward voltage for a conducting diode. This is always around 0V5 for a silicon diode. 0V2 for a germanium diode.

much reverse or leakage current will flow when the diode is reverse biased (cathode positive, anode negative) to various voltages. This reverse characteristic usually has a turnover (Fig. 3) and in the normal use of a diode we try to avoid applying a reverse voltage large enough to reach this turnover point. Why? Well, unless there's enough resistance in the circuit to make sure that the current which can flow in the reverse direction is very small, enough power will be dissipated to overheat the diode and destroy it. The power converted to heat (in milliwatts) is given by volts \times milliamps. If the diode can just safely pass 20 mA in the forward direction, when the forward volt is, say, 0V6 then the power it can handle

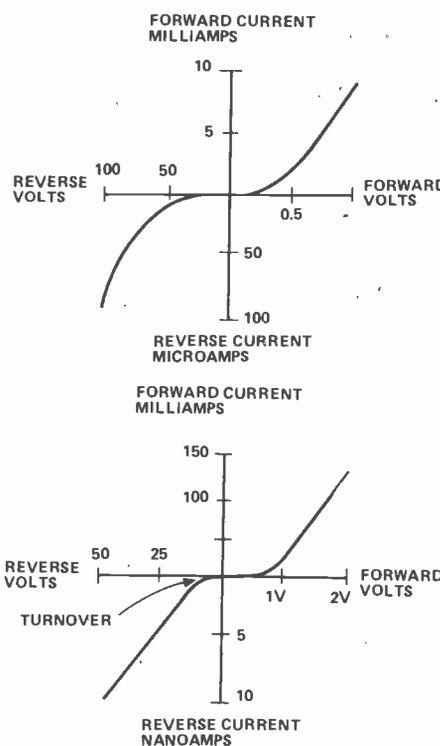


Fig. 3. Forward and reverse characteristics plotted on one graph. (a) Germanium diode, (b) Silicon diode. Notice that the scales for reverse voltage and current are not the same as the scales for forward voltage and current. This has to be done so as to get the two different characteristics on the same graph.

is $0.6 \times 20 = 12$ mW. In the reverse direction, if the turnover is at -20 V, then the power which has to be dissipated at 20 mA is $20 \times 20 = 400$ mW — and it won't like it!

Why Diodes Do It

That's what a diode does, but why does it do it? The answer to that question is not so easy, because it needs some understanding of how materials are formed from atoms and molecules. Let's try to get by with a simple explanation on the understanding that there's a lot more to it. First of all, the materials that are used for making diodes or transistors are solid crystals. Crystals of a given material always have the same angles between faces, and the reason is that they are formed by the atoms of the material always carrying themselves in the same pattern. This regular arrangement causes regular shape of crystals, and also makes it possible for a crystal to conduct electricity. For any material to conduct electricity, it must be well supplied with particles smaller than atoms which have an electric charge, positive or negative, and these particles must be able to move freely through the material.

The regular arrangement for atoms in crystals provides plenty of paths between the atoms for the easy movement of these charged particles, so that crystals only need a supply of particles to become conductors. The materials we call metals are crystals which can release about one charged particle from each atom, so they conduct electricity pretty well, though not equally well. Insulators, on the other hand, simply don't have many charged particles lying around and many of them aren't crystals either, making it doubly difficult for them to conduct. In between these two extremes are the curious materials called semiconductors, which form crystals but are not well supplied with the charged particles that are needed to make them into conductors.

These are two ways in which we can supply these particles. One way is to heat the materials. This causes a few atoms to shed one of their electrons (negatively charged particles), leaving behind a gap in the arrangement of particles in the crystal which we call a hole. The hole behaves like a positively charged particle and can slip from one atom to another. Raising the temperature of a semiconductor, therefore, makes it conduct, but the electrons will slip back into place again when the material cools so the change is not permanent.

Dope Charge

A permanent change can be caused by doping. Doping is adding a small amount of impurity to a semiconductor material. We don't use any old impurity, but materials whose atoms will fit nicely into the arrangement of atoms in the crystal. Some of these materials which fit perfectly into place have one electron more than is needed in the crystal. That electron is released from each impure atom, allowing the crystal to conduct electricity by movement of these electrons. A crystal doped in this way is called N-type. We can also dope with a material which has fewer electrons than its neighbours in the crystal, creating a hole and making the crystal conduct by hole movement. A crystal doped in this way is called P-type. When a semiconductor is made into a conductor by doping, the change is permanent because there are always electrons or holes which don't fit and can't just snap together again (recombine).

This business of doping is quite something, because

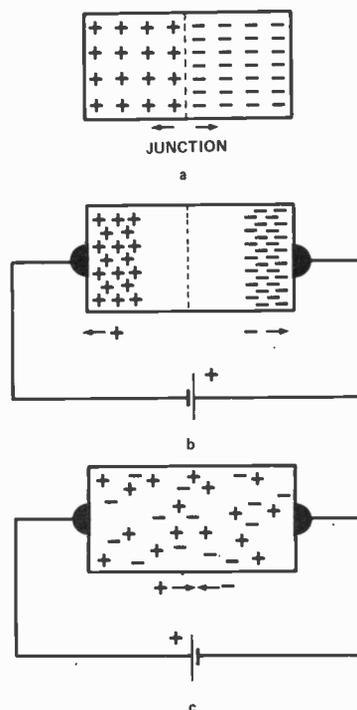


Fig. 4. When a junction is formed (a) the electrons and holes separate slightly at the junction. Reverse bias (b) makes the separation much greater so that the material can't conduct — there aren't any carriers. Forward bias (c) allows electrons and holes to cross the junction, making the material a conductor.

it allows us to do a bit of engineering on materials, creating crystals which can be fair conductors or good conductors, according to how much doping we use; or which are N-type or P-type according to what type of doping we use.

Attractive Likes

Now we've set the scene for learning why a diode works, and there's only one main point left. Charged particles, whatever their size, obey the laws of electrostatics. Of these laws, the important one for understanding the action of a diode is that two particles with the same sign of charge (two positives or two negatives) will repel each other, but particles with opposite signs (a positive and a negative) will attract each other. It's a simple enough law, but combined with what we now know about doping it's enough to explain what goes on inside a diode.

A diode is a single crystal with P-type doping at one end, or on one face, and N-type doping at the other end or face. Obviously, there's got to be a surface in the middle or thereabouts where these two types of doped material meet, and this surface is called the junction. The important thing about a junction is that it's somewhere inside a crystal with no break in the arrangement of the atoms. You can't make a junction by pressing a lump of P-type material up against a lump of N-type material — there's no chance that the rows of atoms would ever line up the way they do inside a crystal.

This arrangement is now a diode — a crystal with P-type material on one side of the junction and N-type material on the other. Remember what these terms mean — N-type material conducts because it has electrons free to move through the crystal. Because the crystal is in one piece, there's no reason why electrons or

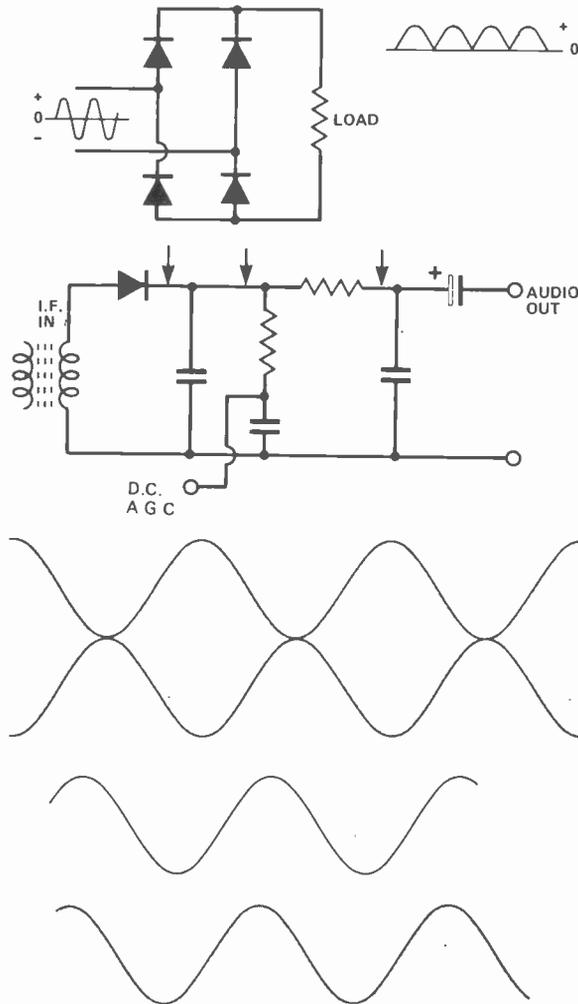


Fig. 5. Using diodes (a) for rectification (b) for radio signal detection. Both applications depend on the one-way flow of current through the diode.

holes should not move from one end of the crystal to the other, so the crystal can be made part of an electrical circuit.

Up The Junction

When the junction is formed, though, the free electrons of the N-type material at one side will be placed very close to the free holes in the P-type material on the other side and inevitably there's a bit of shuffling which ends up with some combination of electrons and holes. This leaves the junction without carriers and also causes the carriers to be pulled back a bit from the junction. The carriers are pulled back because the electrons removed from the N-type material leave a positive charge behind — originally there must be a positive charge for every electron — and the holes that are removed from the P-type material leave electrons (negatively charged) behind.

The affect of the remaining charges is to attract electrons and holes (carriers) away from the junction (Fig. 4a). The imbalance of charge also shows up as a voltage and this is what causes the OV5 of so we need before we can make a silicon junction conduct in the forward direction. The bit of crystal around the junction that has no free carriers is called the depletion layer and we'll look at it again when we discuss varicap diodes.

Minority Groups

The action of the diode in a circuit now becomes a bit easier to understand. When the diode is reverse biased, the polarity of the power supply (Fig. 4b) acts to attract carriers away from the junction, making the depletion layer wider. The electrons of the N-type material and holes of the P-type material simply don't cross the junction because they are pulled in the opposite direction. The only carriers that can cross are what are called minority carriers, holes which appear in the N-type material and electrons which appear in the P-type material. These minority carriers come from splitting bits off atoms in the crystal, using energy from the action of temperature or light. The higher the temperature of the diode the faster these minority carriers are formed. If we make the reverse voltage across the depletion layer high enough, the effect will be to accelerate these minority carriers to high speeds, so that they bang into atoms, knock more carriers off, and so cause the whole junction to become conducting. When that happens, the junction has 'broken down', the diode conducts and it can be damaged.

When the bias is in the forward direction (Fig. 4c) the carriers are attracted towards and across the junction. First of all, though, the voltage caused by the depletion process has to be overcome. Once the forward voltage has reached this amount, current starts to flow. Only a few of all the possible carriers cross the junction when the voltage is low, but raising the voltage even by a very small amount is enough to cause a great increase in the number of carriers crossing over the junction, so that the resistance of the junction becomes much less as the voltage and current are increased.

Shedding Light

This picture of what is happening inside a diode explains pretty well the action of signal or rectifier diodes which are used in the circuits such as those shown in Fig. 5. What about some of the other diodes that we use, like photodiodes, varicaps, LED's, and Zeners? Let's start with photodiodes. The main difference between a photodiode and an ordinary signal diode is that we deliberately put a photodiode into a transparent case so that light can reach the junction. Photodiodes are used in circuits where they are reverse-biased, with a fairly wide depletion layer. Now in darkness, the amount of current that can flow is only that caused by minority carriers — the few holes and electrons that are split off by the heat of the surroundings. Light, however, is a wave which, like all waves, carries energy. The energy of light falling on the depleted layer around the junction can cause lots more electrons and holes to be split off.

They're still minority carriers, but there's a lot more of them now, and so a layer current flows despite the

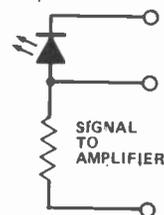


Fig. 6. Using a photo-diode as a light detector. The diode is reverse-biased, but will conduct slightly when light separates electrons from holes.

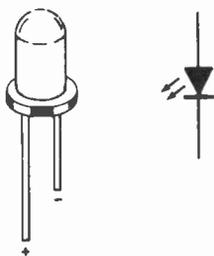


Fig. 7. The LED. When forward current flows, a glow of light is visible. Beware of reverse voltages — anything more than about 3V reverse will destroy the junction.

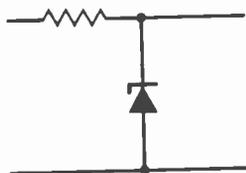


Fig. 8. The Zener diode used as a simple stabiliser. A load connected across the diode can draw current by reducing the current through the diode. Providing the diode current doesn't drop below about 2 mA, the voltage across the diode will remain constant.

reverse bias. Typically, the reverse current can change from around 0.1 μA in darkness to 100 μA in the light of a desk lamp. If the diode is forward biased, the change caused by light is hardly noticeable.

Togetherhness

The LED has an action which is just the reverse of that of the photodiode. Instead of light falling on the junction and causing electrons and holes to split off, as happens in the photodiode, the LED depends on electrons and holes coming together again and giving out light. You can imagine these two processes more clearly when you think of separating two strong magnets. The force which holds them together means that you have difficulty separating them — you have to do some work to separate them. You can get that work back again when the magnets attract each other back; you could even

make the magnetic force do something useful, like picking up a weight.

LED Light

LED's are made from semiconductors (such as Gallium phosphide) which are not heavily doped and don't conduct very well. Something like 2 V is needed across the junction of a typical LED to get current flowing and the movement of holes and electrons causes collisions which separate off more holes and electrons. On their way across the junction in opposite directions, holes and electrons collide — and release the energy it took to split them apart in the first place. The amount of energy is the same as that of a light wave and since the material is transparent a light wave is what we get. The colour of the light wave is decided by how much energy is released. Low energy gives red light, or the invisible infra-red. Higher energy gives yellow, green, blue light (in order of increasing energy), until we reach the invisible ultra-violet radiation. The amount of energy is fixed by the material that is used as a semiconductor, though, and we can't alter it noticeably by changing the voltage or current.

Avalanche

Zener diodes make use of the reverse breakdown which has already been described. Oddly enough, two effects cause this reverse breakdown, Zener effect and avalanche effect. The avalanche effect is the one we've described, in which minority carriers are accelerated so much by the reverse bias that they collide with atoms and split electrons and holes apart. This creates more carriers, which are in turn accelerated, splitting off yet more until the whole junction becomes conducting. The avalanche effect occurs mainly in lightly doped material, at reverse voltages of 6 V or more. The other effect, Zener effect (named after Clarence Zener who discovered it) takes place in heavily doped materials, mainly when the reverse voltage is less than 6 V. Because of the large number of electrons and holes which are present, the depletion layer is very thin and it's comparatively easy for a carrier to shoot straight across. Diodes which made use of either or both of these effects are called

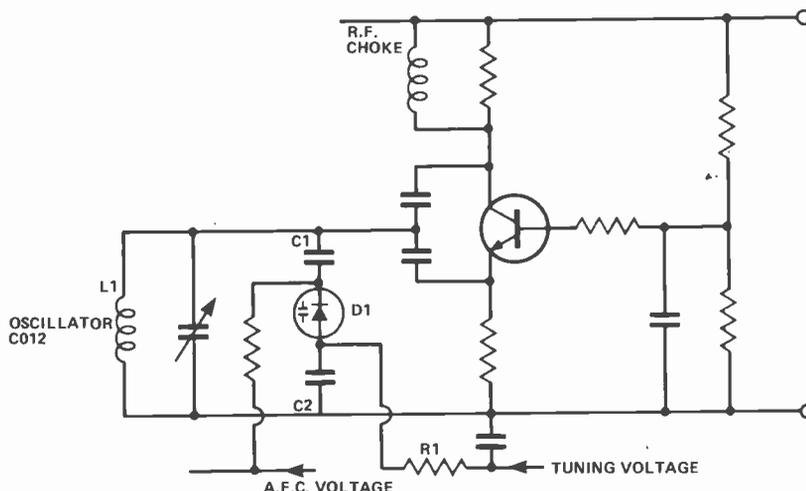


Fig. 9. The varicap diode, D1, is in series with C1 and C2, and is part of the tuning capacitance for L1. Since the diode capacitance is varied by the control voltage from R1, tuning can be carried out by altering this DC voltage.

Zener diodes, and we use them to stabilise voltage. The breakdown, particularly when it is caused by avalanche effect, takes place at a precise value of voltage, so that a Zener diode wired in the circuit of Fig. 8 will have an almost constant voltage across it, even if the current through it varies considerably.

Incidentally, avalanche effect has a positive temperature coefficient, which means that the voltage across the junction increases as the temperature is increased. Zener effect, by contrast, has a negative temperature coefficient, meaning that the voltage across the junction decreases as the temperature is increased. At voltages around 5V6, both effects take place, which means that the voltage is hardly affected by temperature. For this reason, 5V6 zener diodes are often specified rather than any other voltage.

Varicaps

Finally, among the diodes that are particularly useful, varicap diodes make use of the width of the depletion layer. The depletion layer, remember, is the part of the crystal around the junction which has had its carriers removed. The greater the reverse bias applied to the diode, the greater the attraction of carriers away from the junction and so the greater the width of the depletion layer.

Now a depletion layer is a chunk of insulating material which is sandwiched between two bits of conductor — the P and N materials. This is just the arrangement we know as a capacitor — an insulator between two con-

ductors — so that the reverse-biased diode has a capacitance. It's a variable capacitance, though, because the width of the insulator — the depletion layer — can be varied by changing the bias voltage. Like any other variable capacitor, the capacitance value is greatest when the insulating layer is very thin, and the capacitance value is least when the insulating layer is thick. Now the diode has a thick depletion layer when the reverse voltage is large, so that its capacitance is low; but when the reverse bias is small, the depletion layer is thin and the capacitance is large.

Varicap diodes solve an awkward problem — how to tune radio circuits without having any moving parts. A varicap diode in the oscillator circuit (Fig. 9) arranged in series with a fixed capacitor so that it is only part of the tuning capacitance, has no DC connection to the oscillating circuit and can have its capacitance varied by a voltage supplied from a potentiometer. The potentiometer doesn't have to be anywhere near the tuned circuits, so long as the connecting wires are well decoupled and the tuned circuits can be sealed inside a can, undisturbed by any movements.

That's dealt with the most common diodes, though there are dozens of types we haven't mentioned, ranging from the diodes which generate microwave signals to the breakdown diodes we use in thyristor firing circuits. Once you've grasped the basic principles, though, there aren't many surprises left, and you are better able to understand how to make efficient use of these indispensable components.

ETI


Codespeed Electronics

PO BOX 23, 34 SEAFIELD ROAD, COPNOR, PORTSMOUTH PO3 6BJ
ELECTRONIC MAIL ORDER SPECIALISTS

<p>SUPER 4 DIGIT L.C.D. A 4 digit, non-multiplexed Liquid Crystal display with 0.5" high digits (black digits on grey background). Supplied with data CR.95 Order catalogue number 298</p>	<p>DIGITAL CLOCKS A ready built and tested 12 hour alarm clock module with built-in LED display (0.5" digits). Only requires a mini audio transformer and three setting switches to make a fully functional clock. Supplied with full data. CR.50 each Order catalogue number 285</p>	<p>9 DIGIT GAS DISCHARGE DISPLAY A super bright 9 digit display with 0.25" high digits. Requires 100v dc mode volts but this is easily achieved in mains operated projects. Supplied with data sheet and edge connector socket. 75p ea. Order catalogue number 318.</p>	<p>SMITHING DIODES Ten 1N4151, high speed silicon switching diodes. Similar to 1N4148 with a PIV of 75V. Lots of uses for these! 10 diodes for 35p Order catalogue number 403.</p>		
<p>MMS314 CLOCK CHIP ROMANZA Offered at the unbelievable price of only £1.99 each. All brand new and fully guaranteed. Supplied with data sheet. Can be interfaced with either led or gas discharge displays. Order catalogue number 287</p>	<p>FACTORY REJECT CALCULATORS Production line reject LED calculator with lots of accessible goodies inside (calc. chip, display, keyboard etc). Ideal for breaking for spares (some could be repairable and we include a receipt of an article on repairing calculators). £2.50 each Order catalogue number 184.</p>	<p>POLARISING FILTER MATERIAL A highly tested 0.008" thick plastic polarising film made by Polaroid. Any size cut from 1 in. inch to a maximum size of 19" by 250 feet. — Only 2p per square inch (state dimensions required) Order catalogue number 781.</p>	<p>8 DIGIT L.C.D. These liquid crystal displays are dynamic scattering type LCD's and give white digits on a clear background. Digit height is 0.33" with right hand decimal points. Only £2.95 with data Order catalogue number 302.</p>		
<p>1 1/2 DIGIT G.D. DISPLAY A 1 1/2 digit gas discharge display with 0.25" high digits and right hand decimal points. Shows a bright orange display with good readability of 15 feet. A only of 50p each. With data. Order catalogue number 304.</p>	<p>25 GERMANIUM DIODES What a bargain! — of just 2p each. These 1N3470 diodes are miniature glass germanium diodes with a PIV of 35V of 600mA. All brand new. 25 diodes for only 50p Order catalogue number 401.</p>	<p>2102L-1 STATIC RAM's These 2102 static ram's are offered at an amazingly low low price. Features include single 5v supply, fully static protected, high speed, 16 and 64K compatible, and more besides. Supplied with data. Only 99p Order catalogue number 102.</p>			
<p>2 CALCULATOR KEYBOARDS for £1.00 Lots of uses for these neat multi-function keyboards. Each keyboard has 20 keys and size is approx. 3 1/2" x 2". Order catalogue number 101.</p>	<p>4 DIGIT L.E.D. DISPLAY A 4 digit non-multiplexed LED display with centre cable. Ideal for digital clock (and other) projects. Digits are 0.8" high and the display is common cathode. £3.95 each (with data) Order catalogue number 284.</p>	<p>PREAMPLIFIERS LBPA1. Stereo disc / tape LBPA2. 4 channel gen. purpose mixer. LBPA3. Stereo disco with mic. Preamp prices to be announced</p>			
<p>DIGITAL MULTIMETER CHIP Build a highly accurate digital voltmeter or panel meter with this MMS330 integrated circuit. Requires additional circuitry but can be built for half the cost of a ready built D.V.M. £3.95 each (with data) Order catalogue number 404.</p>				<p>COMPONENTS RES/CAPS SEMICONDUCTORS TRANSFORMERS Send for list</p>	
<p>A full refund guarantee on all items. Post and Packing please add 25p (Overseas orders add 60p) Lots more goodies in our catalogue. Send a medium sized SAE for your free copy.</p>				<p>POWER SUPPLIES LB25PS £8.70 LB100PS £10.40 LB250PS £18.00</p>	

LIGHTING & AMPLIFIER MODULES FROM L&B

JUST LOOK AT THESE PRICES!

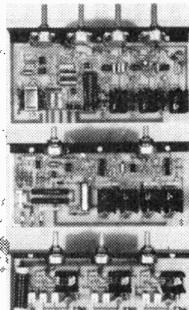

Superior high quality lighting control modules. No additional power supply, just ready to go!

— **LB31000SL** —
Sound-light, 3 channel x 1000W. Zero mains voltage switching, high sensitivity, high input impedance, excellent separation.
£15.70

— **LB41000LS** —
Light sequencer, 4 chan. x 1000W. Suedo-random, zero switching.
£12.70

Two-speed controls, excellent for stage lighting.

— **LB31000LD** —
Light dimmer, 3 chan. x 1000W. Stage lighting from full off to full on.
£11.20

Massive audio power at your fingertips! For use in many applications.

— **LB25** —
25W. RMS 4Ω
10Hz-50KHz
T.H.D. 0.1% 90dB S/N
£6.70



— **LB250** —
250W R.M.S. 4Ω
10Hz-20KHz
T.H.D. 0.3% 110dB S/N
£25.70



— **LB100** —
100W R.M.S. 4Ω
10Hz-25KHz
T.H.D. 0.4% 80dB S/N
£13.40

All above prices include VAT. Please add 50p p/packing. Quantity/trade discounts, up to 33% available! SAE for further info.:

L&B ELECTRONICS 45 WORTLEY ROAD, W. CROYDON
SURREY CR0 3EB. TEL: 01-689 4138

**QUARTZ LCD
5 Function**

Hours, mins., secs., month, date, auto calendar, back-light, quality metal bracelet.

£6.65

Guaranteed same day despatch.
Very slim, only 6mm thick.



M1

**SOLAR QUARTX LCD
5 Function**

Genuine solar panel with battery back-up. Hours, mins., secs. Day/date. Fully adjustable bracelet. Back-light. Only 7mm thick.

£8.65

Guaranteed same day despatch.



M2

**QUARTZ LCD
11 Function SLIM CHRONO**

6 digit, 11 functions. Hours, mins., secs., day, date, day of week. 1/100th, 1/10th, secs., 10X secs., mins. Split and lap modes. Back-light, auto calendar. Only 8mm thick. Stainless steel bracelet and back. Adjustable bracelet. Metac Price

£10.65 Thousands sold!

Guaranteed same day despatch



M3

**QUARTZ LCD
ALARM 7 Function**

Alarm Hours, mins., secs. Month, date, day. 6 digits. 3 flags plus continuous display of day and date or seconds. Back-light. Only 9mm thick **£12.65**

Guaranteed same day despatch



M4

**MULTI ALARM
6 Digits
10 Functions**

- ★ Hours, mins., secs.
- ★ Month, date, day
- ★ Basic alarm.
- ★ Memory date alarm.
- ★ Timer alarm with dual time and 10 country zone.
- ★ Back light.
- ★ 8mm thick.

£18.65



M5

**FRONT-BUTTON ALARM
Chrono Dual Time**

6 digits, 5 flags, 22 functions. Constant display of hours and mins. plus optional seconds or date display. AM/PM indication. Month, date. Continuous display of day. Stop-watch to 12 hours 59.9 secs. in 1/10 second steps. Split and lap timing modes. Dual time zones. Only 8mm thick. Back-light.

£22.65

Guaranteed same day despatch.



M6

**SOLAR QUARTZ LCD
Chronograph with Alarm
Dual Time Zone Facility**

6 digits, 5 flags, 22 functions. Solar panel with battery back-up. 6 basic functions stop-watch to 12 hours 59.9 secs. in 1/10 sec. steps. Split and lap timing modes. Dual time zones. Alarm. 9mm thick. Back-light. Fully adjustable bracelet.

£27.95

M7



**ALARM CHRONO
with 9 World
Time Zones**

- ★ 6 digits, 5 flags.
- ★ 6 basic functions.
- ★ 8 further time zones.
- ★ Count-down alarm.
- ★ Stop-watch to 12 hours 59.9 secs. in 1/10 sec. steps.
- ★ Split and lap timing modes.
- ★ Alarm.
- ★ 9mm thick.
- ★ Back-light.
- ★ Fully adjustable bracelet.

£29.65

M8



**SOLAR QUARTZ LCD
Chronograph**

Powered from solar panel with battery back-up. 6 digit, 11 functions. Hours, mins., secs., day date, day of week. 1/100th, 1/10th secs. 10X secs., mins. Split and lap modes. Back-light. Auto calendar. Only 8mm thick. Stainless steel bracelet and back. Adjustable bracelet. Metac Price **£12.65**

Guaranteed same day despatch.

M9



SEIKO Alarm Chrono

LCD, hours, mins., secs., day of week, month, day and date, 24 hour Alarm, 12 hour chronograph, 1/10th secs., and lap time. Back light, stainless steel, HARDEX glass. List Price £130.00 **METAC PRICE £105.00**

M10



**SEIKO MEMORY BANK
Calendar Watch M354**

Hours, mins., secs., month, day, date in 12 or 24 hour format all indicated continuously. Monthly calendar display, month, year and all dates for any selected month over 80-year period. Memory bank function. Any desired dates up to 11 can be stored in advance. 2-year battery life. Water resistant. **List Price £130 Metac Price £105**

M11




**SEIKO-STYLE
Dual Time-Alarm
Chronograph**

Mineral glass face Battery hatch for DIY battery replacement. Top quality finish with fully adjustable bracelet. **£35.00**

M12



**HANIMEX
Electronic
LED Alarm Clock**

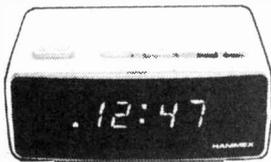

Features and Specification Hour/minute display Large LED display with p.m. and alarm on indicator. 24 Hours alarm with on/off control. Display flashing for power loss indication. Repeatable 9-minute snooze. Display bright/dim modes control. Size 5.15" x 3.93" x 2.36" (131mm x 11mm x 60mm). Weight: 1.43 lbs (0.65 kg).

£9.65 Thousands sold!
Mains operated.

Guaranteed same day despatch.

M13

**HANIMEX
Portable LCD
Clock Radio**

- ★ Back-light.
 - ★ Batteries supplied free.
 - ★ Quartz crystal controlled.
- £17.95**



M14

**QUARTZ LCD
Ladies 5 Function.**

Only 25 x 20mm and 6mm thick. 5 function. Hours, mins., secs., day, date and back light and auto calendar. Elegant metal bracelet in silver or gold. State preference. **£9.95**

Guaranteed same day despatch.

M15



**PRICE BREAKTHROUGH
ONLY
£18.95**



OUTSTANDING FEATURES

- **DUAL TIME.** Local time always visible and you can set and recall any other time zone (such as GMT). Also has a light for night viewing.
 - **CALENDAR FUNCTIONS** include the date and day in each time zone.
 - **CHRONOGRAPH/STOPWATCH** displays up to 12 hours, 59 minutes, 59.9 seconds.
 - **On command, stopwatch display freezes to show intermediate (split/lap) time while stopwatch continues to run.** Can also switch to and from timekeeping and stopwatch modes without affecting either's operation.
 - **ALARM** can be set to any time within a 24-hour period. At the designated time, a pleasant, but effective buzzer sounds to remind or awaken you!
- Guaranteed same day despatch.

M16

HOW TO ORDER

Payment can be made by sending cheque, postal order, Barclay, Access or American Express card numbers. Write your name, address and the order details clearly, enclose 30p for post and packing or the amount stated. We do not wait to clear your cheque before sending the goods so this will not delay delivery. All products carry 1 year guarantee and full money back 10 day reassurance. Battery fitting service is available at our shops. All prices include VAT.

Trade enquiries: Send for a complete list of trade prices — minimum order value £100. Telephone Orders: Credit card customers can telephone orders direct to Daventry or Edgware Rd., 24 hour phone service at both shops: 01-723 4753 03272-76545.



CALLERS WELCOME
Shops open 9.30 - 6.00.

Metac


**ELECTRONICS
& TIME CENTRES**

North & Midlands
67 High Street, DAVENTRY
Northamptonshire
Telephone: 03272 76545

South of England
327 Edgware Road
LONDON W.2
Telephone: (01) 723 4753

readers designs

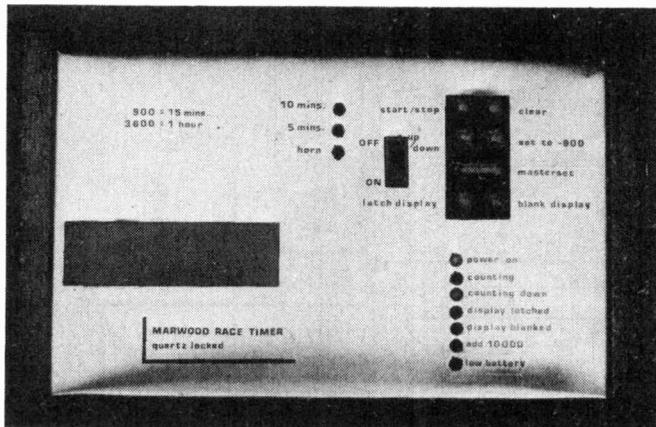SAILING CLUB RACING CLOCK Submitted by Mr K. P. Wood of Wakefield.



The business end of the completed race clock. The state of all clock facilities is repeated on the front panel.

ANY YACHT RACE, whether for the America's Cup, or for the most minor sailing club's weekend dinghy racing, should be started with a definite sequence of signals. At ten minutes before the start, a flag is raised and a sound signal is given. At five minutes, another flap is raised and a further sound signal given, and at the start both flags are lowered and a third sound signal given.

Accurate Handicap


As a few seconds error at the start can make a very substantial difference to a boat's finishing position, far out of proportion to the actual timing error, it is essential that an accurate clock be used to time the signals. In addition, if the racing is on a handicap basis, each boat's finishing time must be taken accurately, for processing to establish a corrected time which sets each boat's final position in the results.

Until recently, the time was taken in minutes and seconds on an ordinary clock or watch, and the corrected time obtained by looking up tables with reference to each class of boat's handicap number.

With the advent of the inexpensive electronic calculator, the tables were dispensed with, and the boat's elapsed time converted to seconds, divided by its handicap number and multiplied by 100 to obtain the corrected time.

One Pair of Hands

A race officer, working alone at the finish of the race, cannot watch both the finishing line and the clock to read the time whilst also giving a sound signal to let the boat's crew know that they have finished. I designed this clock, or more properly, seconds counter to simplify matters. Because it is crystal controlled, it is at least as accurate as any stopwatch which a helmsman may be using, and it counts in seconds to remove one operation from the corrected time calculations. The time can be latched by the race officer without watching the clock, and this can then be read later, up to the next boat finishing.

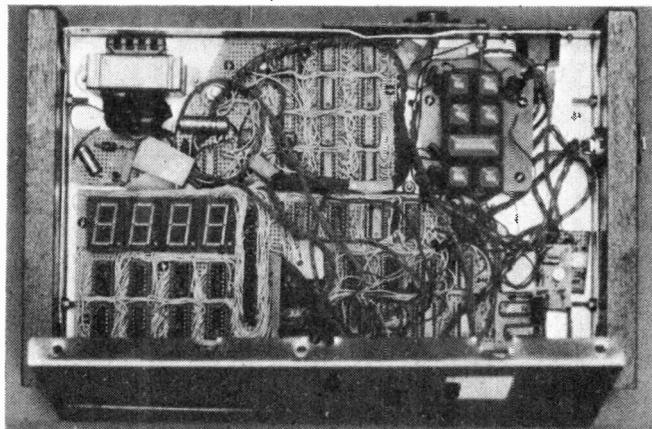

Top view of the completed unit. The crystal oscillator can be seen, bottom right, and the switch bank, top right.

A preset button sets the clock to count down from 900 seconds, and the race officer gives his signals as the count passes through 600, 300 and zero. When the countdown reaches zero, the clock changes over and starts to count up. There is also a clear switch to set the count to zero, and a display blanking switch to conserve battery charge if this is critical.

Repeated Facilities

The large four digit display gives a straightforward count of over two hours, which is usually enough for a race, and an LED indicator on the front of the clock shows if this has been exceeded. The state of all the clock facilities is repeated on the front of the clock. The battery is maintained with a mains charger, and the clock can be used on either battery or mains. The count is unaffected by the changeover.

The timer was used in the condition described for one full season with complete success, and then the automatic start signal facility was added. Logic was added to the clock on an additional board which carries out the signalling for the race officer at the correct intervals. The CMOS logic operates relays through transistor drivers and a four pin socket on the body of the clock. The relays control two lights and a horn which are visible and audible from anywhere on the sailing water and operate in the same sequence as the more traditional flags and guns. The state of the start signals is repeated on the clock face with LEDs. At this time the low battery indicator was added.

Because the clock was designed and built in two separate stages, there is probably some duplication in the logic, and if it were to be made up complete from a standing start the logic would probably be simpler, particularly in the zero sensing area. As I find NAND and NOR gates easier to get, there are a lot of inverters, but as these are all made up from spare gates, and there have to be a lot of spares because of the variety of gates, I do not think that the use of AND and OR gates would reduce the chip count significantly.

readers designs

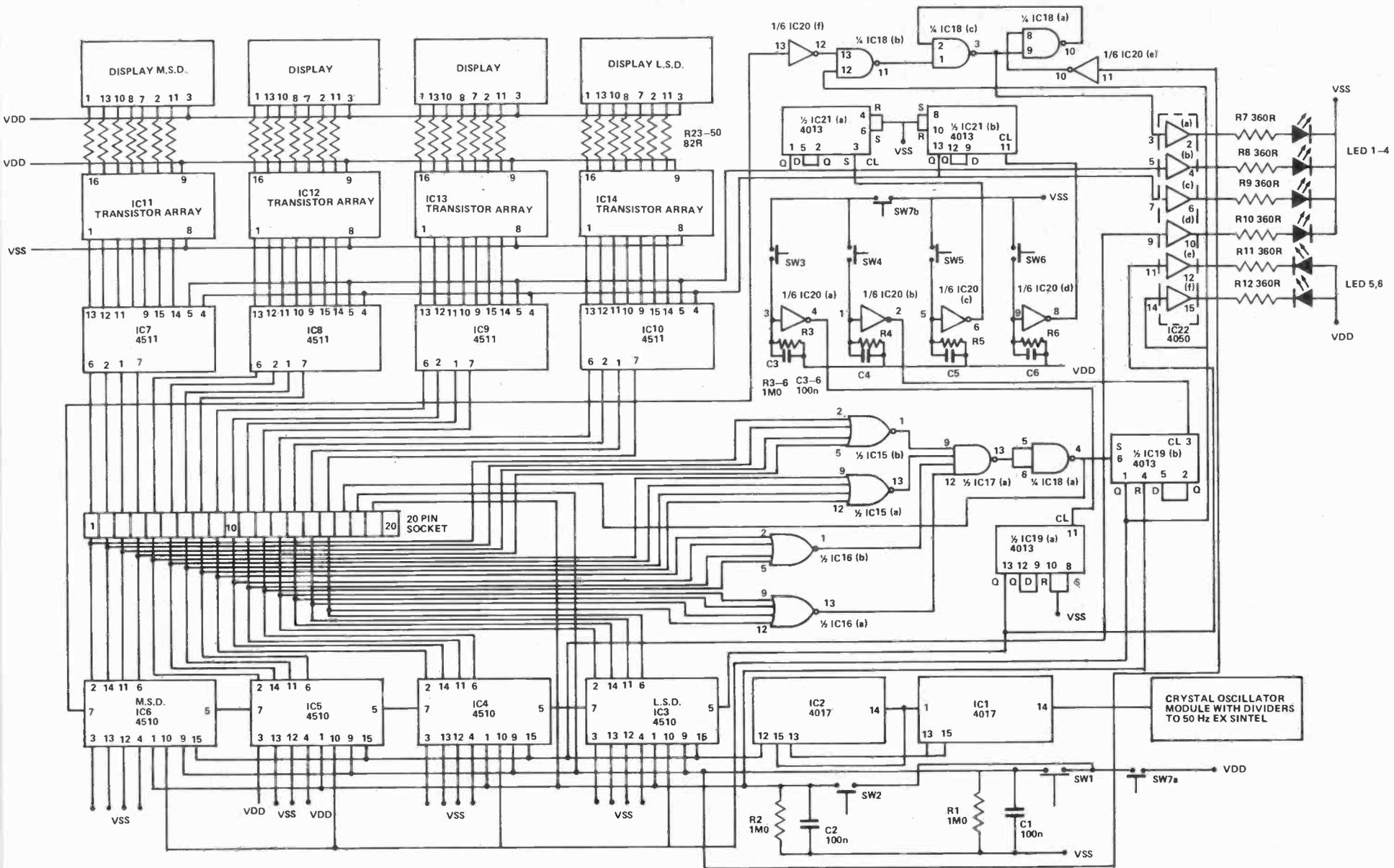


Fig 1. Circuit diagram of the main board. Part one of the How It Works refers to this.

HOW IT WORKS

PART 1 — the output from a 50 Hz crystal controlled oscillator-divider chain, made up from a Sintel kit, is further divided in IC1 and 2 to 1 Hz and the resulting pulse train is divided by IC3, 4, 5 and 6 to provide a four digit BCD count which is decoded to seven segment drive in IC7, 8, 9 and 10. The 4511 digit decoder-drivers would have adequate output to drive the digits direct, but the 1" displays are connected in common anode format so the transistor arrays invert and buffer the drivers to suit, whilst R23 to 50 limit the segment drive currents.

The 4510 counters are cleared to a zero count by a high level on pin 9 from SW1, and are preset to the BCD count set on pins 4, 12, 13 and 3 by a high level on pin 1 from SW2.

IC3, 4, 5 and 6 are wired for parallel clocking, and count synchronously when pin 5 of IC3 is held low by the Q output from the toggling flip-flop IC19a which is toggled by a high pin 11 from SW3 via the Schmitt trigger inverter IC20a. IC19a is wired to toggle on each pulse on the clock input pin, pin 11, by wiring the 'D' input and the Q output together. The R and S inputs of this IC are not used and are tied low to Vss.

The BCD preset inputs to IC3, 4, 5 and 6 are set by hard wiring the appropriate pins to either Vss or Vdd as required. With the wiring shown the counters are preset to 900. Operation of the preset-enable SW2 also pulls the rest pin of IC19b high, resetting the Q output low and setting the 4510 counters to count down. Thus the counters always count down from the preset count, IC19a can also be toggled by SW4 at any time independent of the state of the count.

The count shown on the displays can be latched at any time with SW5 which toggles IC21a, further operation of the same switch unlatching the display and showing the updated count. Similarly, SW6 toggles IC21b blanking the display and turning them back on as required.

SW3, 4, 5 and 6 all operate through Schmitt trigger inverters with C3, 4, 5 and 6 cutting out contact bounce and the switch outputs are tied high or low as required by R3, 6. SW1, 2 are not subject to contact bounce so are wired direct, with R1, 2 pull-up resistors, and C1, 2 slow down capacitors.

Because the count is sensitive to operation of SW1, 2, 3 and 4 some protection from inadvertent operation during a count is required and this is provided by SW7a, b. These are two separate switches mounted

under one large button so that both close when the button is pressed, enabling the switches SW1, 2, 3 and 4. In this way a deliberate action is required to operate any of these switches. SW5 and 6 are not count sensitive and do not require this protection.

The BCD count is tapped off the outputs of the 4510 counters to four, four input NOR gates IC15a, b and IC16a, b, so that when the four digit count is at 0000, the outputs from these NOR gates go high to the inputs of a four input NAND gate IC17a. The resulting low on the output of this gate is inverted in a spare NAND gate IC18a, and this output sets the Q output of IC19b high so that the counters change over and commence to count upwards.

LEDs 2-6 are driven from the outputs of the respective flip-flops, buffered in the non-inverting buffers in IC22, with current limiting resistors R8-12, to indicate the state of the various functions on the front of the clock.

The carry out from IC6, pin 7, drops low when the total count reaches 9999. This low is inverted to a high by the spare Schmitt trigger, IC20f and gated by the NAND gate IC18b, which is held open by a high output on pin 1 of IC19b so that IC18b is only open when the count is upwards. The output from IC18b toggles the RS flip-flop made up by cross-coupling the two NAND gates IC18c,d. The output of this RS flip-flop drives the LED marked 'add 10000,' giving an effective 4½ digit capacity and a total count without ambiguity of 20000. The RS flip-flop is cleared in the same operation as clearing the four counter ICs from SW1 via the spare Schmitt trigger inverter IC20e.

PART 2 — a 20-pin plug and socket connects the BCD data to a second board as shown in the drawing. The BCD data for the 10³, 10 and 1 digits is carried direct to NOR gates IC23 and 24a and b, so that at a zero count on these digits the NOR outputs all go high. The 10² digit BCD count goes to two separate sets of EX-OR gates IC25 and 26. Each bit of data goes to one input of an EX-OR gate and the other input of each gate is tied high or low to V_{cc} or V_{dd} in accordance with the digit required. The EX-OR gates compare each bit of the 10² digit from the counter with the levels set on the other inputs of the gates and when these are equal the output of the gate

goes low. The gate outputs in IC25 all go low at a count of 600, and those of IC26 at a count of 300, with the wiring to the inputs as shown.

These outputs are NOR'd in IC24b and IC27a respectively, and the output from IC24b is NAND'd with the outputs from IC23 and 24a in IC28a. Thus when the count reaches 600 the output from IC28a goes low, is inverted to a high in IC29b to clock flip-flop IC30b. Similarly, when the count reaches 300, IC28b goes low and clocks flip-flop IC 30a through inverter IC29a.

The Q output from IC30a is NAND'd in IC31a, inverted in IC33a and inverted and buffered in the transistor array IC34 to drive the coil for RLY 2. Similarly, the Q output from IC30b is processed in IC 31b, 28c to drive the coil of RLY 3.

The gating inputs of IC31a and b are held high during the down count by the Q output from the flip-flop IC32a which is set high by a pulse on pin 19 of the 20-pin plug from the preset to 900 switch SW2 and is reset low by a pulse from the zero sensing logic on the main board from pin 17 of the 20-pin plug. The outputs from IC29a, b, as well as driving the relay coils, are also NOR'd with the zero count signal from the main board in IC33b and used to trigger the 555 timer, IC34 which is wired as a monostable with a period of approximately two seconds. The output from the 555 is buffered and inverted in IC34 to drive RLY 1 for the horn drive. Operation of the 'clear' switch puts pin 4 of the 555 momentarily high and ensures that the timer is always enabled after the initial power-on of the clock. The input to the 555 from IC33b is inverted in IC31c and NAND'd with the Q output of IC32a so that the horn is disabled after the zero count and no further signals may take place. When the counter was first tested in practice, it was found that, at the zero count, the flip-flop IC32a was resetting and closing the gate before the 555 was triggered, so that the horn did not sound at the zero count. C14 was added to the reset input of IC32a to delay the reset pulse until the 555 had triggered.

It was also found that operation of the latching and blanking switches at any time during the count-down sequence was toggling the flip-flops in IC30 and 32, turning the lights on and off at indeterminate moments, presumably due to spikes on the supply lines and C9, 10 were wired across the supply to cure this effect.

A high on the clear line, or a high at the

zero count, both from the main board via pins 17 and 18 of the 20-pin plug, or NOR'd in IC27b and inverted in IC29c to reset the Q outputs of IC30a,b low disabling the relay drives. LEDs 7-9 are driven through current limiting resistors R13-15 from the relay drivers to repeat the state of the signals on the face of the clock. SW8 with D1 and R18 was added as an afterthought to allow the horn to be sounded at any time whatever the state of the count.

The 6-volt battery is maintained at full charge by the built-in mains charger. The charging voltage is set to 6V9 by adjustment of RV2.

The programmable unijunction transistor BRY39 (PUT) is used as a relaxation oscillator. As the battery voltage falls the voltage on the PUT gate falls whilst the voltage on the PUT anode is held relatively constant by ZD1, and the PUT starts to oscillate when the gate voltage falls some 0V6 below the anode voltage. As the battery voltage falls further, the PUT triggers at lower values of anode voltage and the rate of oscillation increases. With the values shown, RV3 is set so that the first odd flash takes place at about 5V2 on the battery, and at 4V8 the LED is flashing at 2/3 Hz. At this point there is about ten minutes of useful life left in the battery before the voltage goes to 4V5 and the crystal oscillator loses control. As the whole clock uses CMOS logic, it works perfectly satisfactorily from fully charged to 4V8 and no regulation was therefore thought necessary. The cathode gate of the PUT is not used and merely left open-circuit.

The switches are mounted on the board at a suitable height so that the buttons poke through a rectangular hole in the front panel.

The power supply regulator is mounted on a home made heat sink on the back of the case and runs very cool. The relays to drive the signals are mounted in a separate box with three 13 amp, three pin sockets on the front. The signal from the clock is taken to the relay coils from the four pin socket on the side of the case. The relay contacts are rated at 250 volts, 5A, AC and the signal lights are powered from the mains with a separate mains lead to the relay box.

The horn is an ordinary air-operated car horn, the compressor being driven from a 240/12 volt transformer and a 25 A diode bridge. Any bright lights may be used for the signals.

readers designs

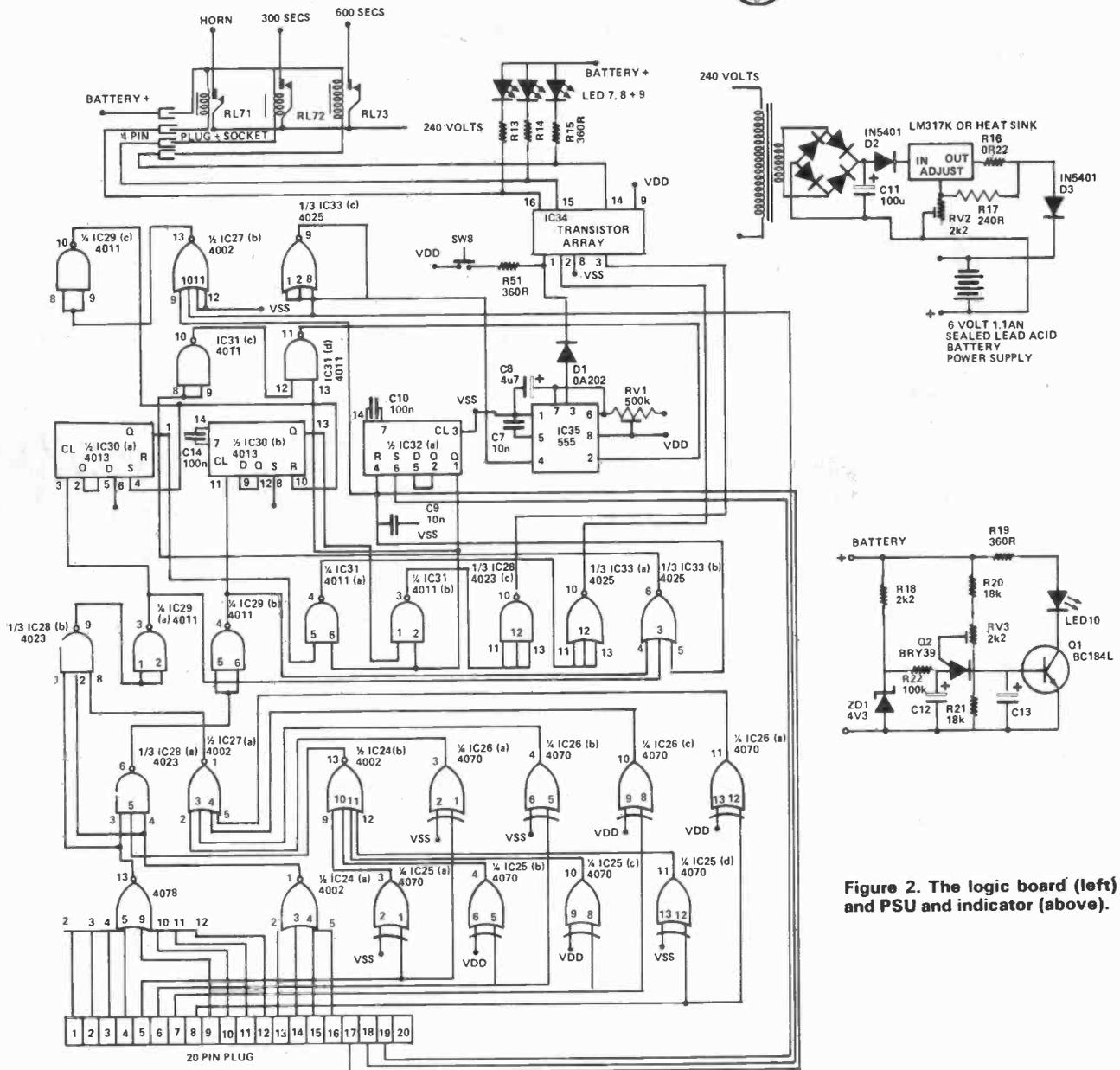


Figure 2. The logic board (left) and PSU and indicator (above).

RESISTORS 1/4W 10%

R1-6	1M
R7-15, 19, 51	369R
R16	0R22 2.5W W/W
R17	240R
R18	2k2
R20, 21	18k
R22	100k
R23-50	82R

POTENTIOMETERS

RV1	500k miniature cermet trimmer
RV2, 3	2k2 miniature cermet trimmer

CAPACITORS

C1-6, 10, 12-14	100n polyester
C7, 9	10n polyester

PARTS LIST

C8	4u7 electrolytic
C11	100u electrolytic
SEMICONDUCTOR	
IC1, 2	4017
IC3-6	4510
IC7-10	4511
IC11-14, 34	RS307-109 transistor array
IC 15, 16, 24, 27	4002
IC17	4012
IC18, 29, 31	4011
IC19, 21, 30, 32	4013
IC20	40106
IC22	4050
IC23	4078
IC25, 26	4070

IC28	4023
IC35	555
Q1	BC184L
Q2	BRY39
D1	OA202
D2, 3	1N5401
ZD1	BZY884V3
LED 1-10	0.2in. red
Diode Bridge	200V 2A
Regulator	LM317K
Displays	1in. common anode red

MISCELLANEOUS

SW1-8 SPST momentary n.o.
 12V, 20VA transformer, 3 off 6V 410ohm coil,
 250V 5A contact relays, 6V 1.1Ah sealed lead acid battery, stripboard, plugs, sockets, etc. case to suit.



20 x 20 WATT STEREO AMPLIFIER

Viscount IV unit in teak simulate cabinet. Silver finish rotary controls and pushbuttons with matching fascia. red mains indicator and stereo jack socket. Functions switch for mic, magnetic and crystal pickups, tape tuner and auxiliary. Rear panel features two mains outlets DIN speaker and input sockets plus fuse. 20x20 watts RMS. 40x40 watts peak. For use with 8 to 15 ohm speakers.

£29.90
£2.50 p&p

30x30 WATT AMPLIFIER IN KIT FORM

For the experienced constructor complete in every detail, same facilities as Viscount IV, but with 30x30 output 60x60 watts peak. For use with 4-15 ohms speakers.



£29.00 + p&p £2.50

SPECIAL OFFER


30 x 30 WATT AMPLIFIER KIT

with BSR P200 belt drive deck and Shure M75 cartridge.

£55.00
+ p&p £5.00

EMI SPEAKER BARGAIN

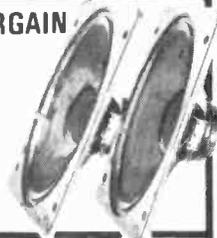Stereo pair 350 kit. System consists of 13" x 8" approx. woofer with rolled surround, 2 1/2" approx. Audax tweeter, crossover components and circuit diagram. Frequency response 20 Hz to 20 KHz. Power handling 15 watts RMS. 20 watts max. 8 ohm impedance.



£14.95

Per stereo pair + £3.40 p&p

BSR P200

Belt drive chassis turntable unit semi-automatic, cueing device.

£24.95
p&p £2.55

A O C QLM 30 Mk III Magnetic Cartridge to suit

£7.75



BSR Manual single play record deck with auto return and cueing lever. Fitted with stereo ceramic cartridge. 2 speeds with 45 r.p.m. spindle adaptor ideally suited for home or disco use.

OUR PRICE £10.95
p&p £2.55

GARRARD DECK MODEL CC 10A

Record changer with cueing device fitted with stereo ceramic cartridge ready to fit into your own plinth.

£7.95 p&p £2.00

Size 12" x 8 1/2"

SANYO Nic/cad battery, with mains charger, equivalent in size and replaces 4 SP11 type batts. Size 3 1/4" x 1 1/4" x 2" approx.

£7.50 p&p £1.50p

BARGAIN FOR PERSONAL SHOPPERS ONLY

Altone UA4 Stereo System

Features 8 watt total output. Full size BSR manual turntable with cueing and auto return. Socket for tape in and out and stereo headphones.

complete with speakers **£34.95**

Micro Cassette Recorder

Packet size—home or office use or when travelling.

£13.95

Battery operated fluorescent camping lamp.

Runs off 8 U2 batteries.

£4.50

Mullard

AUDIO MODULES IN BARGAIN PACKS

CURRENT CATALOGUE
PRICE & AT OVER **25** PER PACK

SEE OUR PRICES


1 PACK 1 2 x LP1173 10w RMS output power audio amp modules, + 1 LP1182/2 Stereo pre amp for ceramic and auxiliary input.
OUR PRICE £4.95
p&p £1.00

2 PACK 2 2 x LP1173 10w RMS output power audio amp modules + 1 LP1184/2 Stereo pre amp for magnetic, ceramic and auxiliary inputs.
OUR PRICE £7.45
p&p £1.00

illus.

£7.45
plus £1.50 p&p

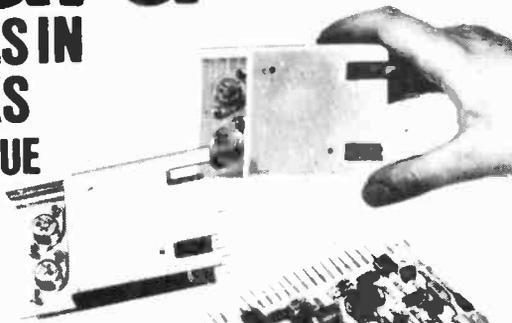ACCESSORIES ARE ONLY AVAILABLE TO THOSE CUSTOMERS WHEN BUYING OUR BARGAIN PACKS



ACCESSORIES

Suitable mains power supply parts, consisting of mains transformer, bridge rectifier, smoothing capacitor and set of rotary stereo controls for treble, bass, volume and balance.

Two Way Speaker Kit

Comprising of two 8" x 5" approx. 4 ohm bass and two 3 1/2" 15 ohm mid-range tweeter with two cross-over capacitors.

£2.90
plus £1.50 p&p


£3.95
per stereo pair plus £1.50 p&p

AVAILABLE ALSO TO PURCHASERS OF THE 10 + 10 AMPLIFIER KIT

10 + 10 AMPLIFIER KIT

An opportunity to buy a 10 watts per channel stereo amplifier kit which is suitable for use with a ceramic cartridge. The amplifier utilises proven Mullard modules and is available at a very competitive price. The amplifier kit comes complete with instructions and includes a Mullard LP1183 stereo preamplifier module, two LP1173 power amplifiers with integral heatsinks, a power supply, Zobel networks, front and back mounting panels, a finished fascia panel, all control potentiometers (bass, treble, volume and balance), switches, input, output and headphone sockets, wire, and an easily assembled wrap around cabinet to house the finished unit.

£11.95
p&p £2.05

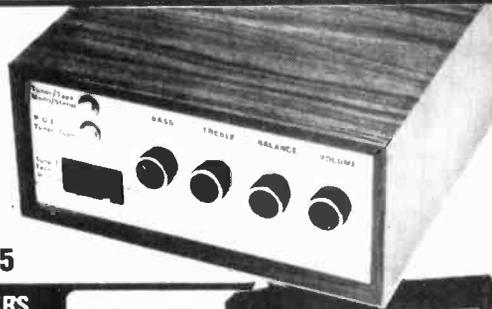

BARGAINS FOR PERSONAL SHOPPERS

LED 5 function men's digital watch stainless steel finish **£5.95**

LED 5 function men's digital watch stainless steel finish **£6.95**

LED 8 Function CHRONOGRAPH men's digital watch, stainless steel finish **£12.95**

POCKET CALCULATOR With LED display, memory and percentage key **£2.95**

AM/FM DIGITAL CLOCK RADIO Accurate 4 Digit Electronic Clock with 1/2" LED display, Buzz and snooze timer **£11.95**



125 Watt Power Amp Module **£13.95**

Mains power supply for above unit **£3.50**

MULLARD Built power supply **£1.50**

DECCA 20w Stereo speaker kit comprising 2 8" approx. bass units + 2 3/4" approx. tweeter inc. crossovers **£20.00**

VIDEOMASTER Super Score TV Game with pistol mains operation **£14.95**

PORTABLE RADIO/CASSETTE RECORDER, AM FM with clock LW MW SW VHF mains/battery operation **£41.95**

VIDEOMASTER COLOUR SHOT TV GAME Choice of three games—Football, Tennis and Squash. Ready to play—one or two players. MAINS OPERATED **OPPORTUNITY AT £9.95 ONLY**



**325 EDGWARE ROAD, LONDON W2
21E HIGH STREET, ACTON W3 6NG**

ACTON: Mail Order only. No callers. ALL PRICES INCLUDE VAT AT 12 1/2%


All items subject to availability. Price correct at 17/5/79 and subject to change without notice.

50 WATT MONO DISCO AMP

£29.95

Size approx. 13 1/4" x 5 1/4" x 6 1/4"

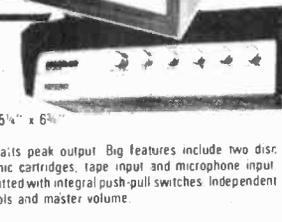50 watts rms 100 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with integral push-pull switches. Independent bass and treble controls and master volume.



70 & 100 WATT MONO DISCO AMP

Size approx. 14" x 4" x 10 1/4"

Brushed aluminium fascia and rotary controls

Five vertical slide controls, master volume, tape level, mic level, deck level. PLUS INTER DECK FADER for perfect graduated change from record deck No 1 to No 2, or vice versa. Pre fade level control (PFL) lets YOU hear next disc before fading it in. VU meter monitors output level.



70 watt **£57**

140 watt/peak p&p £4.00


100 watt **£65**

For personal shoppers only

DUO II SPEAKERS

Attractive teak finish, modern design, incorporating 2 speaker units—6" approx. woofer and 2 1/2" approx. tweeter. 45 to 1900 Hz. Impedance 8 ohms. Power 15 watts RMS. 20 watts max.

Per stereo pair **£17.00**

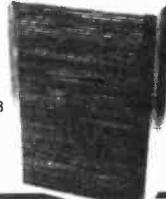

FOR PERSONAL SHOPPERS ONLY

STEREO RADIOGRAM CABINET

Finished in a natural teak veneer with opening top. Easily modified to accommodate stereo equipment of your choice.

Price **£10.95**

Size approximately 47" x 15 1/2" x 15"

Personal Shoppers EDGWARE ROAD LONDON W2 Tel: 01-723 8432. 9.30am-5.30pm. Closed all day Thursday. ACTON: Mail Order only. No callers. GOODS NOT DESPATCHED OUTSIDE UK

Now, complete your system!



Citronic MM313 Mixer

Ideal for the DIY enthusiast building up a complete disco system. 4/8 ch mono, inc. LED indicators, connections via phono sockets at rear. Bargain price, including PSU EB4 24.


The ultimate range of speakers

We carry a good selection of high quality chassis for the DIY speaker constructor. 12" or 15" Bass speakers and Dual Concentrics. Exponential horns from £13.77, or our fabulous Piezo Horns which handle a 5K-20K frequency range in any PA system up to 100W (No X over required) and cost only £6.18 each.




Projectors

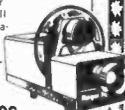Come and see our specially selected projectors from E42.12 (Squire Multi-lect 150) to E94.50 (Tutor 11E) plus the widest array of projector attachment and effects that you'll ever see on continuous demonstration.



Turntables

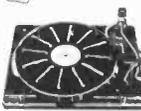Our unsurpassed Disco experience has enabled us to select the best turntables for your requirements. For example the new BSR P200 belt drive. ONLY £28.12.



Ropelights

Great effect at discos. 7 metres long. Multiway connectors. 4 channel. £43.20 (inc. pack of spare bulbs).

Bulgian Octal plugs and sockets

There's always hundreds of Bulgian Octal multiway plugs and sockets in stock at Roger Squire's. Each pin rated 6A. Perfect for your Sound to Light System. P552 SOCKET. £0.65. P551 PLUG. £1.94.



Multiway Cables
4 core (6A) 59p/metre
5 core (6A) 73p/metre
6 core (6A) 86p/metre

Many disco accessories

All Roger Squire's shops have a service department which carries large stocks of DISCO SPARES & ACCESSORIES.

ALL SHOPS OPEN TUE-SAT LATE NIGHT WED. (UP TO 8 PM)

PERSONAL CALLERS ONLY

Roger Squire's

Disco Centres

LONDON 176 Junction Road, N19. 50yds Turnel Park Tube Station. Tel: 01 272 7474
BRISTOL 125 Church Road, Redfield (Near St. George) 1 mile from end of M32
MANCHESTER 251 Deansgate 3, 15 mins from City Centre
GLASGOW 1 Queen Margaret Road (off Queen Margaret Drive) Kelvinside 20, just behind the BBC. Tel: 041 946 3303

OUR 1979 CATALOGUE

including the first edition of

STOP PRESS

- ★ Latest low prices
- ★ Fascinating new items
- ★ Special offers — a bargain on their own
- ★ Lowest prices ever for TTL
- ★ Free 45p worth of vouchers

RAM 2102A-2
1024 x 1 250ns
£1.19
16 for £16.96

C.P.U.
8080
£5.49

CATALOGUE
40p

JUST SEND S.A.E. FOR STOP PRESS

E. PROM
1702
£5.57

CHROMASONIC electronics

DEPT. ETI 8, 56 FORTIS GREEN ROAD
MUSWELL HILL, LONDON N10 3HN
TELEPHONE: 01-883 3705/2289

USE OUR "ORDER RING" LINES
VAT INCLUSIVE PRICES. P & P 25p

ZENER DIODES (400mW) 2.7V to 33V 8p	OPTO/DISPLAY 2N5777 50p OC71 70p OC712 70p OL704 100p OL707 100p 1.25" x 8.2" 125p 1.25" x 8.2" 125p	LINEARS 710CN 30p 741-8 22p 747C-14 45p 748C-8 40p CA3011 80p CA3018 80p CA3028A 85p CA3036 120p CA3046 65p CA3054 110p CA3080 70p CA3140E 60p LM301AN 28p LM308N 64p LM350N 70p LM381N 110p NE555 25p NE556 60p TBA641-811 200p	7443 40p 7444 60p 7445 64p 7446 50p 7447 50p 7448 50p 7450 10p 7451 12p 7453 12p 7454 10p 7460 14p 7470 20p 7472 20p 7473 20p 7474 22p 7475 25p 7476 25p 7480 35p 7485 60p 7486 20p 7490 25p 7491 30p 7492 30p 7493 25p 7494 50p 7495 40p 7496 40p 7497 120p 74100 70p 74105 40p 74107 22p 74109 30p 74110 46p 74118 75p 74121 25p 74122 30p 74123 40p 74125 35p 74126 35p 74132 45p 74141 45p 74142 180p 74145 50p 74150 65p 74151 45p 74153 45p 74154 65p 74155 45p 74156 40p 74157 40p 74160 55p 74161 50p 74162 55p 74163 50p 74164 60p	74165 55p 74166 75p 74173 80p 74174 60p 74175 55p 74176 50p 74177 50p 74180 80p 74181 110p 74182 45p 74190 65p 74191 70p 74192 55p 74193 60p 74194 55p 74195 50p 74196 50p 74197 50p 74198 100p 74199 90p	4048 50p 4049 25p 4050 25p 4066 35p 4069 12p 4070 8p 4071 12p 4072 12p 4073 16p 4081 14p 4082 14p 4086 60p 4510 60p 4511 60p 4516 65p 4518 65p 4520 65p 4528 80p	TRANSISTORS AC126 17p AC127 19p AC128 19p 128/176 17p MP 42p AC141 24p AC142 25p AC151 25p AC153 29p AC176 18p AC187 20p AC188 20p AC149 9p AC157 10p BC158 10p BC159 10p BC168 12p BC170 8p BC171 11p BC172 11p BC173 4p BC182 10p BC183 10p BC184 10p BC186 19p BC187 28p BC207 10p BC212 10p BC213 10p BC214 10p BC237 12p BC238 15p BC301 22p BC303 24p BC328 17p BC338 17p BC547 11p BC548 11p BC549 11p BC557 11p BCY30 55p BCY34 66p BCY70 14p BCY71 16p BCY15 44p BCY21 80p BCY23 90p BCY124 100p BCY131 35p BCY132 35p BCY135 35p BCY136 35p BCY137 40p BCY138 38p BCY139 38p BCY140 38p BCY115 18p BCY167 28p	8F173 20p 8F178 25p 8F179 24p 8F180 23p 8F181 18p 8F182 30p 8F183 23p 8F184 20p 8F185 23p 8F194 10p 8F196 10p 8F197 10p 8F198 18p 8F200 28p 8F224 18p 8F257 8p 8F258 8p 8F259 12p 8FR39 24p 8FR40 24p 8FR79 24p 8FR80 26p 8FX29 25p 8FX30 14p 8FX85 28p 8FX86 24p 8FX87 20p 8FY50 19p 8FY51 19p 8FY53 12p 8SX19 18p 8SX20 20p 8U205 130p 8U208 150p OC25 76p OC28 86p OC35 86p OC71 9p OC72 32p OC84 42p OC85 35p OC719 40p OC729 35p OC730 40p OC731 40p OC732 40p OC733 60p	TIP33C 90p TIP34A 65p TIP35A 230p TIP36A 290p TIP41A 70p TIP42A 70p TIP2955 65p TIP3055 55p ZTX108 12p ZTX109 12p ZTX300 15p ZTX500 15p 2N706 13p 2N1131 21p 2N1132 24p 2N1302 38p 2N1304 52p 2N1305 29p 2N1306 36p 2N1308 48p 2N1613 22p 2N1711 22p 2N1893 30p 2N217 30p 2N2219 21p 2N2369 15p 2N2484 22p 2N2905 22p 2N2906 15p 2N2907 20p 2N2926 10p 2N3054 50p 2N3055 50p 2N3072 11p 2N3703 11p 2N3704 11p 2N3706 11p 2N3707 11p 2N3710 11p 2N3711 11p 2N3772 150p 2N3773 280p 2N3866 80p 2N3904 15p 2N4061 12p
POLYESTER CAP (250V) .01, .015, .022, .033, .047, .068, 1 uF 1.5, 2.2, 33 uF 47, 68 uF 1 uF 2.2 uF	DIODES BY127 10p OA47 8p OA91 8p OA200 6p OA202 9p 1N4148 4p 1N916 5p 1N4001 4p 1N4002 4p 1N4003 5p 1N4004 6p 1N4005 7p 1N4006 8p 1N4007 9p 1N5400 13p 1N5401 14p 1N5402 15p 1N5404 20p	TTL 7400 10p 7401 10p 7402 10p 7403 10p 7404 12p 7405 12p 7406 20p 7407 24p 7408 12p 7409 12p 7410 12p 7411 15p 7412 15p 7413 25p 7414 45p 7416 24p 7417 24p 7420 12p 7421 12p 7422 15p 7423 15p 7424 15p 7425 15p 7426 15p 7427 15p 7428 25p 7430 12p 7432 16p 7433 28p 7437 16p 7438 17p 7440 10p 7441 46p 7442 40p	VOLTAGE REGULATORS 320H-05 40p 320H-24 40p 7805 60p 7812 60p 7815 60p 7818 60p 7824 60p 7905 80p 7912 80p 7915 80p 7918 80p 7924 80p	BRIDGE RECTIFIERS 1A/50V 22p 1A/100V 24p 1A/200V 27p 1A/400V 32p 2A/50V 34p 2A/100V 38p 2A/200V 44p 2A/400V 48p WD2M 25p WD6M 32p	OIL SOCKETS 8 pin 10p 14 pin 12p 16 pin 13p 18 pin 18p 22 pin 22p 24 pin 24p 28 pin 28p 40 pin 40p			


Add 25p for p&p

DELTA TECH & CO.
62 NAYLOR ROAD, LONDON, N20 0HN
All prices VAT inclusive

POWER-ONE

D.C. POWER SUPPLIES

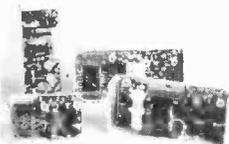Now, like Intel, Motorola and National you can buy Power-One open frame power supplies and enjoy quality and reliability at LOW LOW prices. Over 70 different models to choose from including floppy disc drive supplies as well as single, double, triple and quad output.



Single Output

5V at 2.7A w/OVP	£19.50
5V at 5.4A w/OVP	£41.60
12V at 6A	£67.60
15V at 5.4A	£67.60

Dual Output

±12 to 15V at 1.5A	£41.00
±18 to 24V at 0.4A	£32.50
±5V at 5.4A w/OVP	£78.00

Triple Output

5V, 9-15V, -5, -12, -15V at 1.8A to 10.8A	From £41.00 to £137.00
---	------------------------

Floppy Disc Drive Supplies

— with connectors and cables for Shugart drives if required.


CP-249 — drives one mini drive	£33.00
CP-323 — drives two mini drives	£80.00
CP-205 — drives one Shugart SA800 or equivalent 8" drive	£68.00
CP-206 — drives two SA800	£78.00

Discount available to bona-fide educational establishments. Quantity discounts start at five units. Trade enquiries welcome. Send large SAE for full catalogue and price list.



COMPUTERS LTD.,
133 Woodham Lane, New Haw, Weybridge, Surrey
KT15 3NJ. Telex. 8813487.

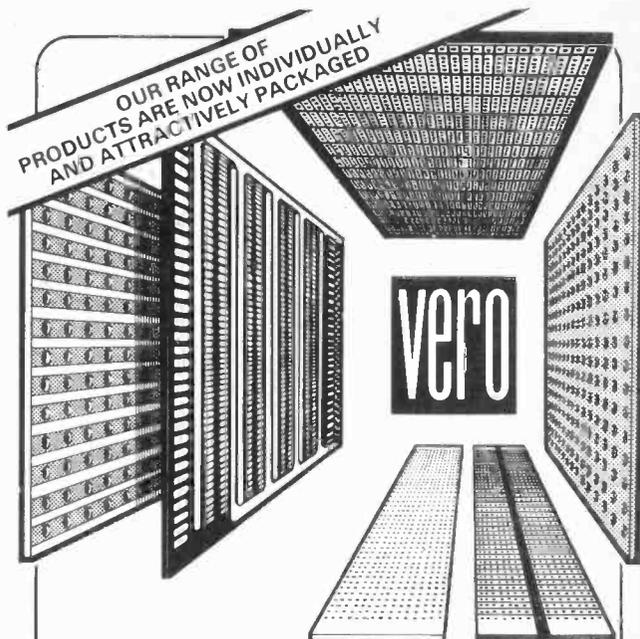OUR RANGE OF PRODUCTS ARE NOW INDIVIDUALLY AND ATTRACTIVELY PACKAGED



Our new catalogue lists circuit boards for all your projects, from good old Veroboard through to specialised boards for ICs. And we've got accessories, module systems, cases and boxes — everything you need to give your equipment the quality you demand. Send 25p to cover post and packing, and the catalogue's yours.

VERO ELECTRONICS LTD. RETAIL DEPT.
Industrial Estate, Chandlers Ford, Hants. SO5 3ZR
Telephone Chandlers Ford (04215) 2956

Extracts from our lists, which are now available, of Equipment, Components etc THAT MUST BE SOLD.

- TEK scope 545A with H plug-in £125 ea.
- TEK scope 545A with CA plug-in £175 ea.
- H.P. scope 175A 50MHZ Dual trace £175 ea.
- Single Trace £125 ea.
- SOLARTRON CD1014 6 MHz Twin Beam £90 ea.
- SOLARTRON CD1400 15 MHz Twin Beam £120 ea.
- Telegquipment D33R 6MHZ Twin Beam £80 ea.
- SOLARTRON CT316 6MHZ Single Beam £47.50 ea.
- Ex-Ministry CT52 Small. Single Beam £37.50 ea.
- WAYNE KERR Universal Bridge CT375 £75 ea.
- MARCONI Wave Analyser TF2330 £500 ea.
- MARCONI Audio Oscillator TF1101 20HZ-200KHZ £45 ea.
- ADVANCE Signal Generator J1A (CT433A) £35 ea.
- MARCONI Valve Voltmeter TF1041C £30 ea.
- NOISE GENERATOR CT410 — covers audio to VHF £8 ea.
- DIGITAL EQUIP. CORP. Disk Drives (Fixed) £160 ea.

Carriage all units £4 ea. V.A.T. at 15%.

- 10Way Multi Colour Ribbon Cable New 40p per metre P&P 50p
- STEPPING MOTORS 8/12 positions with additional where the ratio is calls. Drive can be used as a latch. Diagram supplied. Will actually work on 5 volts. 12/24 recommended. £1.50 ea. P&P 75p. Reduction for quantity.
- RAPID DISCHARGE capacitors 40V 4K. £5 ea. P&P £1.50.
- SEC UNF 4 button timer £2.50 ea. P&P 85p.
- DIGI-MINI Motor 110V AC 3rpm 50 cycle — very small. 50p ea. P&P 50p.
- CERTAUR 115V FANS. Brand New 4.5 x 4.5 x 1.5in. £4.50 ea. P&P 75p.
- EX Used Equipment — tested 60p ea. P&P 75p.
- POTTER & BRUMFIELD TIMER RELAY 115V AC Heavy duty 2 pole c/a with 2 second delay. Change R & C for different timing 50p ea. P&P 25p.
- CONTACTORS Heavy Duty 24V AC/DC 5 make. £1 ea. P&P 85p.
- SEC UNF 7W/6 button timer £4.50 ea. P&P £1.
- CAPACITORS 500pF & 1KV 20p ea. P&P 15p.
- SMITHS encapsulated transistorised AUDIBLE WARNING DEVICES 4V-12V can be driven from TTL 35p ea. P&P 25p.
- DIGITAL 24 HOUR CLOCK with built-in alarm as used in BRAUN Digital clocks. Silent running. Large illuminated numerals. AC mains. Size 6 1/2 x 2 1/2 x 2 1/2. ONLY £3.75 ea. P&P 50p.
- OSIA PHOTOMULTIPLIER in stainless steel container with window and built in resistor network £2 ea. P&P £1.
- SLIDER CONTROL 500K Log Single track complete with knob. Length 3 1/2in. 25p ea. P&P 25p.
- RANGE 250V 16A THERMOSTATS with Control knobs calibrated 50-200 degrees F. £2.50 ea. P&P £1.
- SOLID STATE UNF TUNERS 38 mcs. £1 ea. P&P 75p.
- GRUZZET/MBWTEK Arpen synchronous meters 115V. With detachable gearbox 30p ea. P&P 75p.
- BRAND NEX Blue wire wrap 30 metres for £1. P&P 25p. Six. SOLID RUBBER RINGS (1in. dia rubber) Keep the kids (or dogs) happy. 4 for £1 ea. P&P £1.25.

- TRANSFORMERS
- AUTO 240V Input 115V 1 Amp output £1.25 ea. P&P £1.25.
- 240V Input Sec 6V 1.66A Size 2 1/2 x 2 x 2 in. Good quality £1.50 ea P&P £1.
- 240V Input Sec 12V 0.92A Size 2 1/2 x 2 x 2 in. Good quality £1.50 ea. P&P £1.
- 240V Input Sec 12V 100MA Size 60 x 40 x 42 mm. 50p ea. P&P 75p.
- 240V Input Sec 12-0-12V 50 MA. Size 53 x 45 x 40mm £1 ea. P&P 75p.

SEMICONDUCTORS			
A1 2p ea.			
1N3043: 1844			
A1 5p ea.			
BC147: BC148B: BC157: BC158: BC184L: BC237: BF197: OA90: OA91: BA154: BA243: 1N4303: 11.3V Zener.			
A1 25p ea.			
TP931: TP41A: TP47: ZMS06: AF129: ZTX341.			
BY127-10p: BF181-20p: BQ235-40p: BQ241-40p: MJE340AT-40p: BQ222-50p: BQ233 & BQ234 Comp pair 25W — 80p per pair or 50p each.			
Regulator TL4625 0-20V in-5V out 100MA. T05 Cae. 50p ea.			
BF256C-20p.			
FHD10 7 segment display 0.15in. 40p ea.			
Integrated Circuits			
7453	5p	74H51	7p
7451	5p	74S38	10p
7401	5p	74S02	12p
7402	12p	74S00	12p
7476	20p	74154	70p
7495	35p	75325	£1
709	15p	SM15862	4p
74H74	12p	9-314	8p
74S10	5p	MC4028	60p
74S04	12p	7417	14p
		7441	40p

Motrola Dual in Line 6 pin Opto Coupler 50p ea.
AM9130 4K RAMS STATIC 5 Volt. Ceramic £4 ea.
AM9140 4K RAMS STATIC 5 Volt. Ceramic £4 ea.
Telephones. 706 style Black or Gray £8.50 ea. 746 style Black or Gray £7.50 ea.
Older style Black £2.50 ea. Postage £1 each.

Minimum order £3 value of goods. Postage & VAT @ 15% must be added to all orders.


CALLERS VERY WELCOME STRICTLY BETWEEN 9am-1pm and 2pm-5pm Monday to Saturday incl. BARCLAYCARD (VISA) and ACCESS taken. Official orders welcome.

CHILTMHEAD LTD

NORWOOD ROAD, READING TEL NO. READING 669656

(2nd left passed Reading Tech College in Kings Road then first right — Look on right for door with spoked wheel)

MORE SCOPE FOR YOUR MONEY

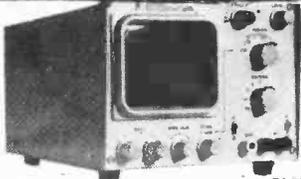

SPECIFICATIONS ELECTRICAL DATA

ELMAC 4" SCOPE
 VERTICAL AXIS (Y) Deflection Sensitivity — 100mV/division. Bandwidth (between 3 dB points) — DC — 5MHz. Input Attenuator — (calibrated) — 9 step 0.1, 0.2, 0.5, 1, 2, 5, 10, 20, 50/div. Input impedance — 1 Meg/40 pf in shunt input Voltage — Max — 600V P.P.
 HORIZONTAL AXIS (X). Deflection Sensitivity — 0.400mV/division. Bandwidth (between 3 dB points) — 1Hz-350KHz. Gain Control — Continuous when time bases in EXT position. Input Impedance — 1 Meg. Input Voltage — Max — 500V P.P.

TIME BASE Sweep Range (calibrated) — 100msec/div to 1 μ sec/div in 5 steps. FINE Control — Variable between steps — includes time-base calibration position. Blanking — Internal — on all ranges.
 SYNCHRONISATION. Selection — Internal external. Synchronisation Level — Continues from positive to negative.


POWER SUPPLY. Input voltage — 115/200V AC \pm 10% at 50/60Hz Power Dissipation — 18W.

CRT DATA — 4in. — flat face, single beam. — Maximum high voltage — 1.5kV. — Fitted with 8x10 division blue filter graticule.

PHYSICAL DATA Dimensions — 15cm(h)x20.5cm(w)x28cm(d) Weight — 4.3Kg(approx.) Stand — 2 position flat and inclined Case — Steel, epoxy enamelled. Front panel — Aluminium enamelled epoxy printing.
 (As recommended by ETI)

Cash with order Test leads available £2.00
 £109 (+ 08 72 VAT + Barclay and Access
 £2.08 Carriage)

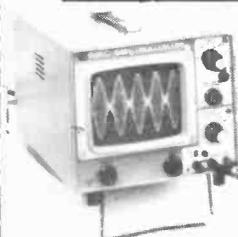10MHz Scope with 5 x Magnifier for £147.95.
 11.84 VAT + £2 carriage)



3106C

5" CRT

SAE for further details

As recommended by Practical Wireless

- 10mV to 50V/cm in 12 calibrated steps.
- 0.5 μ s to 0.1 Sec/cm sweep range in 6 calibrated steps plus 12 1 Vernier.
- Magnifier x5.
- Fully automatic trigger.
- DC to 2 MHz horizontal bandwidth.
- Rise time on 35ns
- Time base range from 0.5 μ s to 10ms/cm in 6 steps
- Flat 8x10cm display with graticule on blue filter. Smallest sub-division 2mm
- Fastest sweep 100ns/cm with magnifier.

Sensitivity: < 1 cm deflection 10 Hz to > 15MHz L.F. trigger extends below 5 Hz with 2 cm deflection. Trigger circuit locks to the mean value of the displayed waveform. It will lock to almost any waveshape including sine, square, triangle, pulse and TV video signals. When no signal is present to repetition rate is below 5Hz the trace free runs producing a bright base line. Company orders welcome by phone and Telex.

6MHz OSCILLOSCOPE 3106B

Similar in appearance to 10 MHz scope. SAE for details. Function Generator @ £150 + VAT, sae for details.

SINCLAIR PFM 200

FEATURES include:
 Resolution to 0.1Hz and sensitivity to 10mV. 8-digit LED displaying frequency range of 20Hz to 200MHz. Xtal time base accurate to 0.3ppm/°C at 10ppm/year and all this in a package weighing just 6oz. and 6.2" x 1.25". Adaptor £3.20. Padded case £3.20.

PDM35 £29.80
 UK microvision £90.24
 DM350 £96.76
 DM450 £68.08
 PFM200 £52.00
 DM235 £49.40

Boris Microprocessor chess game £178
 Boris Diplomat @ £95.00
 Chess Challenger 7 @ £95.00
 Chess Challenger 10 @ £154.00
 S.A.E. for details.

KRAMER & CO.

9 October Place, Holders Hill Road
 London NW4 1EJ. Telex: 888941
 attn. Kramer k7. Tel: 01-203 2473
 Mail order only. Callers by appointment

ETCH RESIST TRANSFER KIT SIZE 1:1

Complete kit 13 sheets 6in x 4 1/2in £2.50 with all symbols for direct application to P.C. board. Individual sheets 25p each. (1) Mixed Symbols (2) Lines 0.05 (3) Pads (4) Fish Plates and Connectors (5) 4 Lead and 3 Lead and Pads (6) DILS (7) BENDS 90° and 130° (8) 8-10-12 T.O.5. Cans (9) Edge Connectors 0.15 (10) Edge Connectors 0.1 (11) Lines 0.02 (12) Bends 0.02 (13) Quad in Line.

FRONT AND REAR PANEL TRANSFER SIGNS

All standard symbols and wording. Over 250 symbols, signs and words. Also available in reverse for perspex, etc. Choice of colours, red, blue, black, or white. Size of sheet 12in x 9in. Price £1.

GRAPHIC TRANSFERS WITH SPACER ACCESSORIES

Available also in reverse lettering, colours red, blue, black or white. Each sheet 12in. x 9in contains capitals, lower case and numerals 1/8in kit or 1/4in kit. £1 complete. State size.

All orders dispatched promptly.

All post paid

Shop and Trade enquiries welcome
 Special Transfers made to order

E. R. NICHOLLS
 P.C.B. TRANSFERS
 DEPT. ETI 8

46 LOWFIELD ROAD
 STOCKPORT, CHES. 061-480 2179

PLEASE
 MENTION
 ETI
 WHEN
 REPLYING
 TO
 ADVERTS

Car Audio

Manual MW/LW



Full medium and long wave tuning. Complete with speaker and mountings. Suitable for positive or negative chassis. Latest model.

£9.95 + £1.00 Post

Push-Button MW/LW



One LW, four MW buttons plus manual tuning. Complete with speaker and mountings. Latest model, negative chassis only.

£15.60 + £1.00 Post

Stereo FM/Cassette + MW



Standard cassettes and FM in stereo plus medium wave. Tone and balance controls. Fast forward facility on tape. Adjustable shafts. Suitable for 4 or 8 ohm speakers (not supplied). This model is discounted elsewhere at £50 up.

£39.95 + £1.00 Post

Stereo Speaker Set



Suitable for above stereo unit. Good quality in surface mounted casing. 5W nominal, 8W peak.

£3.95 (pair)

+ 70p Post

Telescopic Car Antenna

Multi-section standard type, suitable for angled mounting with locking key.

£1.60 + 30p Post

Metal Detectors

Treasure Tracer Mk III



The original Treasure Tracer. Sales exceed 7,000. 5-transistor circuit with Varicap tuning. Sensitive, stable BFO design. Built-in speaker and earphone. Fitted with Faraday shield. Kit supplied with pre-built search head.

Kit: £17.50 + £1.00 Post
 Built: £22.50 + £1.00 Post

★ Induction Balance Model



Built with sensitivity up to 10in on single coin; fitted with speaker and meter, PP3 battery; 7in dia. search head. Telescopic stem. Excellent pin-pointing, positive reaction to non-ferrous, negative reaction to iron. This model's normal price is £39.95!

£22.95 + £1.00 Post

All goods guaranteed one year. 10-day money-back offer. Goods ex-stock at time of going to press. Callers by appointment only please. Send s.a.e. for illustrated leaflet.

Minikits Electronics Ltd.

6D Cleveland Road
 S. Woodford
 London E18 2AN

AUDIO DISPLAY

Kinaesthetic kicks with scintillating new display which puts your music on show to the world. A superb ETI Project Team design.

SO MANY electronic projects rise phoenix-like from the smoke of the soldering iron and when shown to family and friends are greeted with looks of blank amazement and the inevitable question, 'I'm sure it's very clever, but what does it do?'

It is easy to understand how many projects can be confusing and uninteresting to a non-technical person. This attractive project is simple in operation and yet sophisticated in the effect it produces and will be enjoyed by anyone with an eye and an ear to spare.

Small Is Beautiful

The SCINTALITE LED audio display translates the dynamic flow of sound into a visual analogue. The circuit follows conventional lines with the input signal being amplified and filtered to extract the upper and lower frequencies. The outputs from the filters are then rectified and the peak

and mean DC levels detected and made available at the 'mood' switch. Operation of this control allows the relatively fast peaks of the music or the more slowly changing levels of the overall sound to control the display.

A novel feature of the display is the ability to produce a moving dot or bar of light. The upper frequencies are displayed using both techniques and the circuit switches between them as the input level rises and falls. The lower bass range is always displayed in bar form.


As can be seen in our photos the display is based on a pentagon and is about six inches in diameter. The upper frequencies drive five spiral arms of ten LEDs each and the bass frequencies are displayed on ten shorter straight radiating arms. There is also a circle of ten LEDs whose brilliance is controlled by the overall input signal.

Tripping The Light Fantastic

Scintalite can accept input signals from a wide variety of sources. Its sensitivity is variable from about five millivolts to five volts. Although designed primarily as an audio display, any input voltage within specified limits may be used to control the unit by replacing the input capacitor with a wire link. In this way, Scintalite could for example form the display device for a bio-feedback system. In such an application it should be noted that, except for very quickly changing signals, only the bass section will give a display and, as half-wave rectifiers are used, a negative going input signal is required owing to signal inversion in the first amplifier.

Construction and Use

The unit is assembled on one PCB with a separate power supply. The PCB holds all the signal conditioning

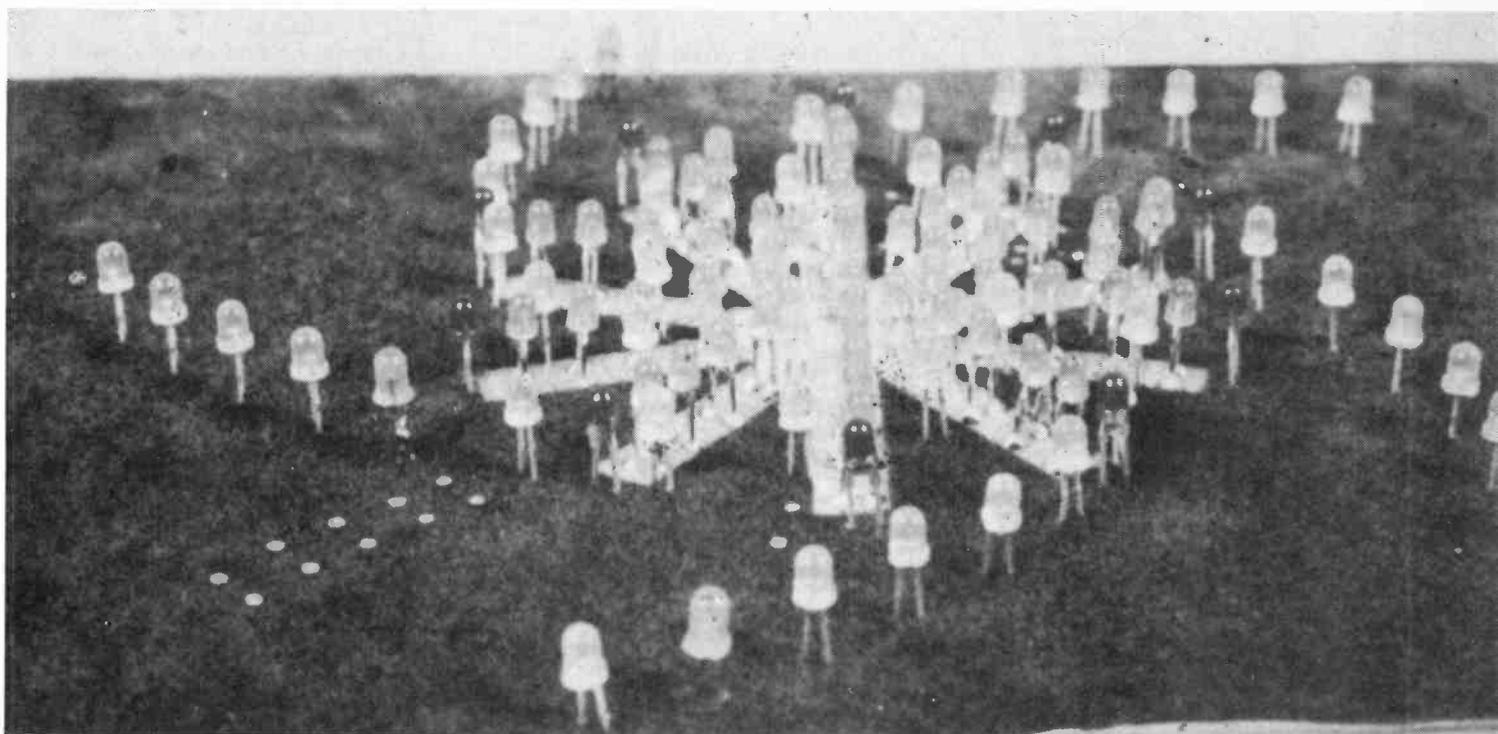

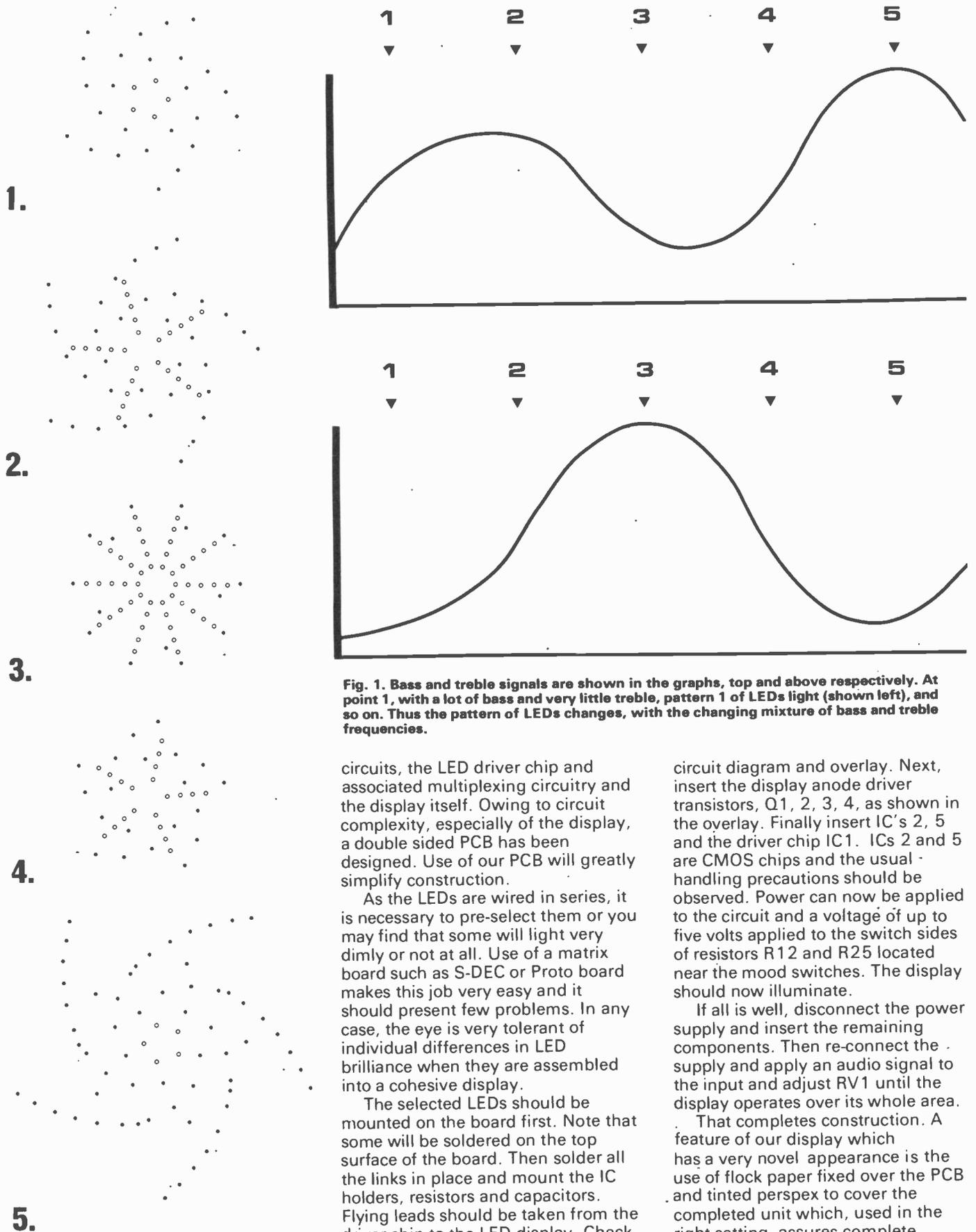


Fig. 1. Bass and treble signals are shown in the graphs, top and above respectively. At point 1, with a lot of bass and very little treble, pattern 1 of LEDs light (shown left), and so on. Thus the pattern of LEDs changes, with the changing mixture of bass and treble frequencies.

circuits, the LED driver chip and associated multiplexing circuitry and the display itself. Owing to circuit complexity, especially of the display, a double sided PCB has been designed. Use of our PCB will greatly simplify construction.

As the LEDs are wired in series, it is necessary to pre-select them or you may find that some will light very dimly or not at all. Use of a matrix board such as S-DEC or Proto board makes this job very easy and it should present few problems. In any case, the eye is very tolerant of individual differences in LED brilliance when they are assembled into a cohesive display.

The selected LEDs should be mounted on the board first. Note that some will be soldered on the top surface of the board. Then solder all the links in place and mount the IC holders, resistors and capacitors. Flying leads should be taken from the driver chip to the LED display. Check the connections carefully against the

circuit diagram and overlay. Next, insert the display anode driver transistors, Q1, 2, 3, 4, as shown in the overlay. Finally insert IC's 2, 5 and the driver chip IC1. ICs 2 and 5 are CMOS chips and the usual handling precautions should be observed. Power can now be applied to the circuit and a voltage of up to five volts applied to the switch sides of resistors R12 and R25 located near the mood switches. The display should now illuminate.

If all is well, disconnect the power supply and insert the remaining components. Then re-connect the supply and apply an audio signal to the input and adjust RV1 until the display operates over its whole area.

That completes construction. A feature of our display which has a very novel appearance is the use of flock paper fixed over the PCB and tinted perspex to cover the completed unit which, used in the right setting, assures complete kinaesthesia.

ETI

PARTS LIST

RESISTORS all 1/4W 5%

R1, 5, 15	1m
R2, 3, 16	47k
R4	1k
R6, 13, 19, 20	15k
R7	33k
R8p 10, 21, 23	100k
R9, 22	100r
R11, 24	220k
R12, 17, 18, 25	10k
R14	10m
R26	2k2
R27	680r
R28	1k

POTENTIOMETER

RV1 1M submin preset

CAPACITORS

C1	10n polyester
C2	10u electrolytic
C3, 4	3n3 polystyrene
C5, 6, 10, 11, 12	10u tantalum
C7	1u tantalum
C8	100n polyester
C9	47n polyester

SEMICONDUCTORS

IC1	LM3914
IC2	4016B
IC3	LM324
IC4	741
IC5	CA3140
IC6	8093B


Q1, 3	BC214L
Q2, 4,	BFX 88

D1, 2, 3, 4, 5, 6, 7 1N4148

LEDs 0.125"


MISCELLANEOUS

PCB	
SW1, 2	SPDT

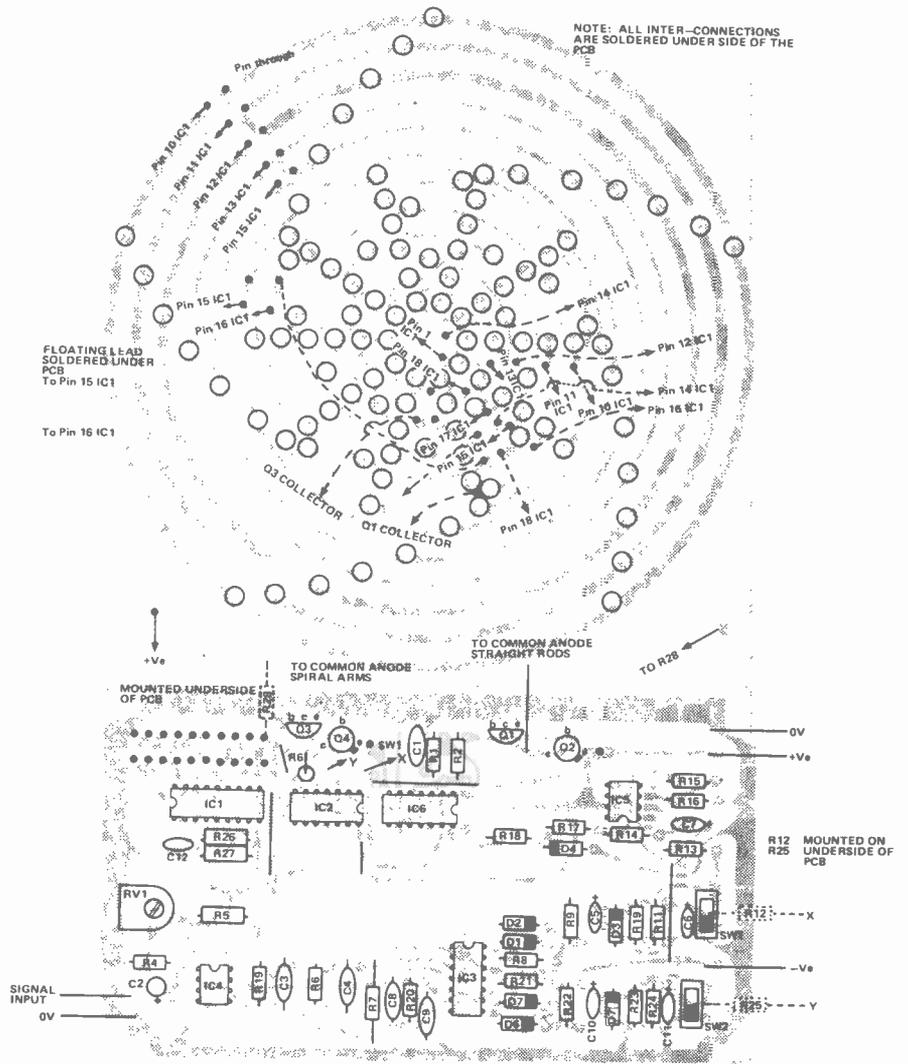


Above: Component overlay for the Scintellate Audio Display unit. Note that this PCB is in fact a double sided board, but for clarity we have only shown one side of the foil pattern.

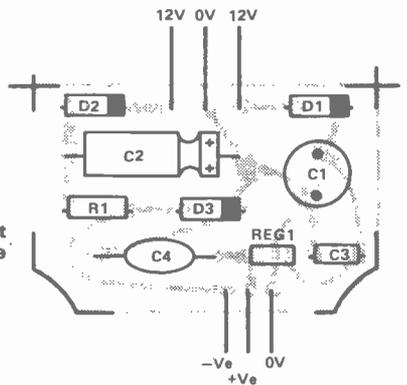
PSU is shown here. This can be any +12V supply rated at 250mA or over. Design of this is not critical, but ripple should be low.



BUYLINES

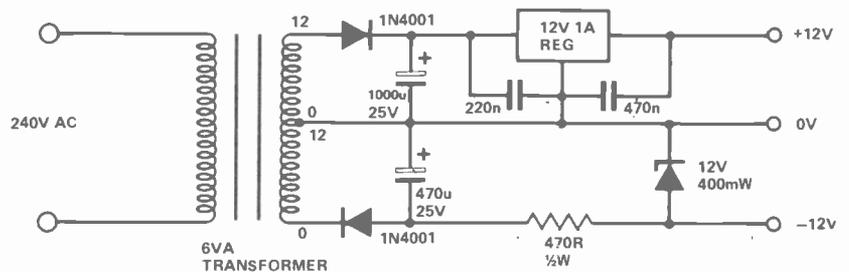The LM3914 bargraph display driver should be available from Marshall's Watford or Maplin. All the other components should be readily available from the usual suppliers.



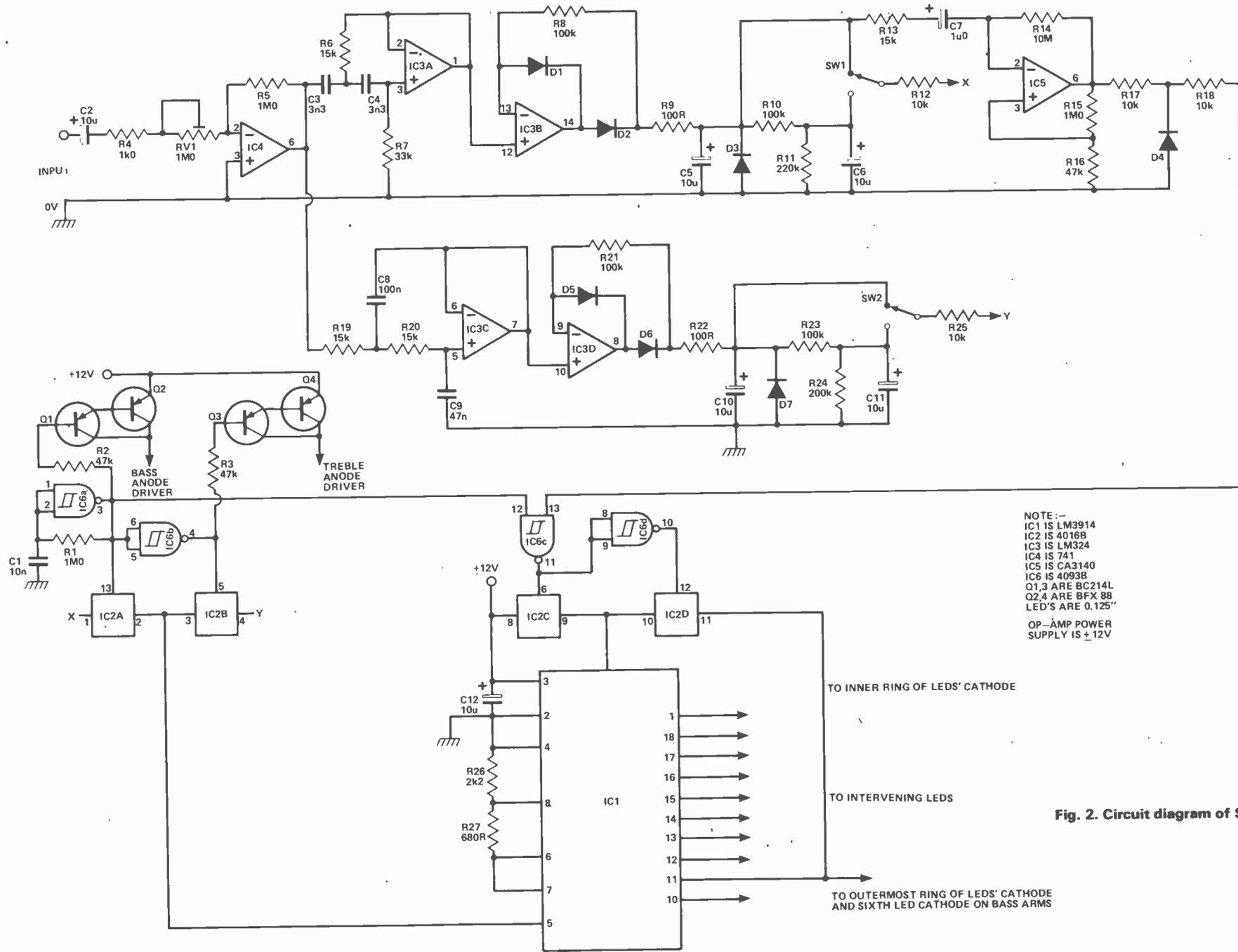

NOTE:--
 IC1 IS LM3914
 IC2 IS 4016B
 IC3 IS LM324
 IC4 IS 741
 IC5 IS CA3140
 IC6 IS 4093B
 Q1,3 ARE BC214L
 Q2,4 ARE BFX 88
 LED'S ARE 0.125"
 OP-AMP POWER SUPPLY IS +12V

Fig. 2. Circuit diagram of Scintalite.

HOW IT WORKS

The signal is input to IC4, a conventional inverting amplifier, via C2, R4 and RV1 which sets the gain of this stage. The output, about ten volts peak to peak, drives filters IC3a and IC3c. These are second-order with a Butterworth response.

IC3a is a highpass circuit and has a turnover point around 2.5 kHz. IC3c is lowpass with a turnover point around 250 Hz. The output from the filters drives identical half-wave rectifying peak detector circuits. Two signals are available from these stages; the peak signal from the top of C5 or C10 and a low pass filtered signal from C6 or C11. The signal required

is selected by operation of the mood switches SW1 and SW2.


To reduce component count and conserve power the LED displays are multiplex. IC2a and IC2b select the input signal for display driver IC1. IC6a is an oscillator running at a few kHz and around 50% duty cycle. Its output is inverted by IC6b. The antiphase signals from this network control the Darlington anode drivers Q1, 2, 3, 4 and analogue switches IC2a and IC2b. The remaining gates in these two chips are used to select dot or bar mode in the display driver chip.

The bass display select signal at pin 12 of IC6c forces a bar display. However, the treble display operates according to the

output level of IC5. This is a differentiating circuit whose output sign follows the slope of the treble peak detector output as the signal rises and falls. Some Schmitt action is provided by R15, 16.

IC1 is programmed by R26 and R27 for a full scale input of about five volts and a LED current of 20 mA. We used green LEDs for the bass display and yellow for the treble. It is important to use a regulated 12V positive supply as chip dissipation could otherwise be excessive.

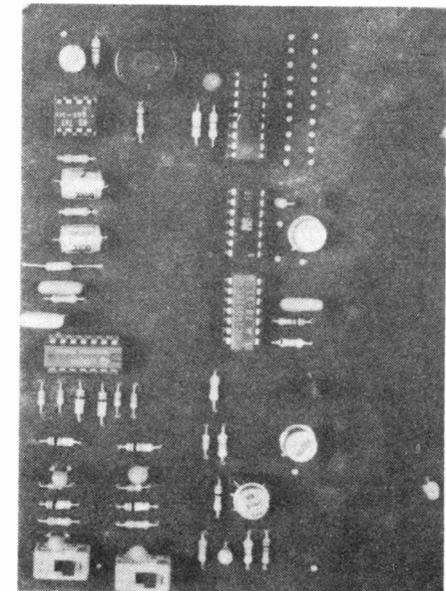The same problem could arise if red LEDs are used owing to their lower forward voltage drop. The negative supply is low-power and uncritical but should anyway be kept below 15V.



(Above) The business end of the Scintalite PCB.

(Below). Two stages in the construction of Scintalite. The spiral arms are fitted (right), and then the straight lines of LEDs (left).

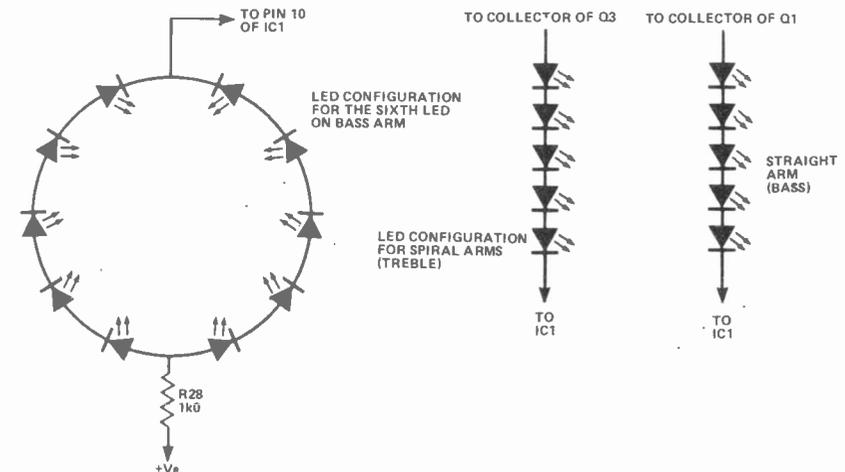
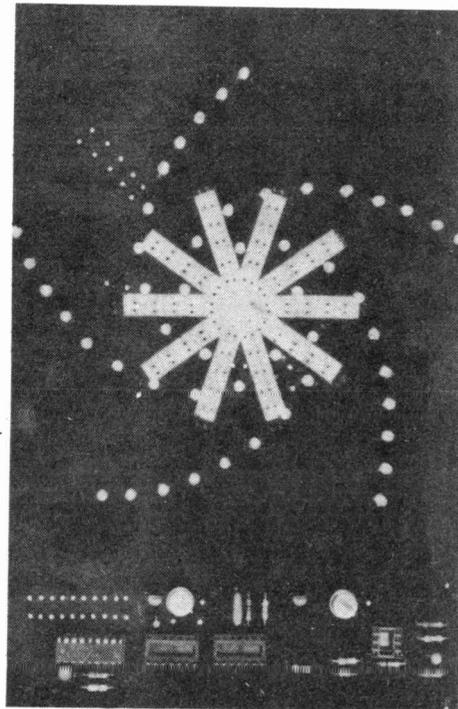
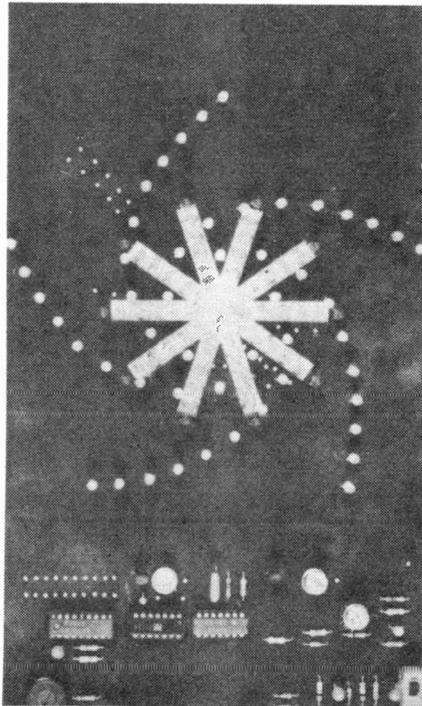


Fig. 3. LED configurations for the bass and treble lines.

Digital accuracy. Analogue price!

The new Fluke 8022A DMM now offers the best of both worlds at only

£89

CRISP LCD DISPLAY

Automatic polarity indication plus auto-zeroing "BT" Low battery indications when 20 hours remain.

6 RESISTANCE RANGES

200Ω to 20MΩ In-circuit test of semiconductor junctions available on 3 ranges.

8 CURRENT RANGES

From 2mA to 2A AC or DC. 10A Current SHUNT available.

10 VOLTAGE RANGES

200mV-1000V DC or 750V AC.

POCKET SIZE

Lightweight unit only 370gms

FULL OVERLOAD PROTECTION

Will withstand 6kV spikes.

RUGGED CASE

Meets tough mil-Specs - virtually indestructible.



It's true! The 8022A brings you digital precision and ruggedness—at analogue prices, from the world leader in digital multimeters.

Featuring the Fluke in-line pushbutton concept for easy single handed operation this pocket sized lightweight meter has a 0.25% DC accuracy, incorporates a custom designed CMOS chip for low power consumption and offers a full two year warranty.

For only £89.00 you can now hold the world of measurement in the palm of your hand.

FLUKE No.1 in DMM's

Fluke International Corporation, Colonial Way, Watford, Herts. WD2 4TT. Telephone: (0923) 40511. Telex: 934583

Also available from ITT Instruments Services, Harlow, Essex.

Northern Ireland and Eire contact Euro Electronic Instruments, 32 Brews Hill, Mavan, County Meith, Eire.

8022A Checklist

Whether you are buying your first multimeter or moving up to digital from analogue, check these features against your existing meter.

FULL 2 YEAR WARRANTY.

1 YEAR GUARANTEED ACCURACY FROM 18°C to 28°C.

DROP PROOF! Meets tough Mil-Spec tests for shock & vibration.

10 times better Accuracy than most analogue meters.

Single handed operation.

USER PROTECTION! Recessed input jacks and new Fluke designed safe test leads.

PROTECTED THREE WAYS against accidental over-voltage, over-current and transient to 6kV.

Easily accessible battery and current fuse.

200 hours continuous operation plus "BT" low battery volt indication.


Handy size. Fits easily into pocket, brief-case or toolbox.

Large, readily available range of accessories.

Worldwide parts and servicing facilities.

Price £89.00 complete with test probes.

? 8022A

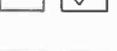

A no compromise Digital Multimeter at an analogue price.



Greenbank

Greenbank Electronics
(Dept TBE) 92 New Chester Road, New Ferry
Wirral, Merseyside L62 5AG
(Tel: 051-645 3391)

TERMS, VAT, C.W.O. Cheques etc payable to Greenbank Electronics. Add VAT to all prices at 8% except where stated otherwise. Post etc: UK 25p [+2p VAT = 27p] per order. Export: NO VAT but add 25p [Eire], 75p [Europe] and £2.50 elsewhere.
[Polys, universities, gov. depts., etc. can telephone their orders for immediate despatch on account.]

CMOS These cut prices for Amateur Users and Export. Note: industrial users - quantity prices available. Mostly Motorola, RCA

4000 15p	4042 75p	4089 E1.50	4419 E2.68	4531 E1.45
4001 17p	4043 94p	4093 63p	4422 E5.00	4532 E1.27
4002 17p	4044 94p	4094 E1.90	4431 TBA	4534 E5.13
4006 E1.05	4045 E1.45	4095 E1.05	4433 E11.32	4536 E3.69
4007 18p	4046 E1.28	4096 E1.05	4435 E7.93	4537 E13.23
4008 87p	4047 87p	4097 E3.72	4440 E11.58	4538 E1.25
4009 50p	4048 58p	4098 E1.10	4450 E2.67	4539 91p
4010 50p	4049 48p	4099 E1.45	4451 E2.67	4541 E1.14
4011 18p	4050 48p	40061 N/S	4452 TBA	4543 E1.59
4012 18p	4051 72p	40100 E2.50	4461 E2.18	4549 E3.69
4013 42p	4052 72p	40101 E1.61	4462 E2.42	4552 E10.55
4014 86p	4053 72p	40102 E2.12	4469P E8.54	4553 E3.87
4015 89p	4054 E1.10	40103 E2.12	4480P E3.48	4554 E1.19
4016 45p	4055 E1.28	40104 E1.05	4500 E6.95	4555 78p
4017 89p	4056 E1.34	40105 E1.06	4501 17p	4556 78p
4018 89p	4057 E25.70	40106 61p	4502 91p	4557 E3.86
4019 48p	4059 E4.80	40107 68p	4503 89p	4558 E1.14
4020 99p	4060 E1.15	40108 E3.36	4506 E5.71	4559 E3.89
4021 91p	4061 E15.67	40109 E1.02	4506 51p	4560 E1.84
4022 86p	4062 E10.00	40181 E3.38	4507 59p	4561 85p
4023 20p	4063 E1.09	40182 E1.40	4508 E2.48	4562 E5.33
4024 66p	4064 N/S	40192 E1.40	4509 E5.66	4566 E1.59
4025 19p	4065 N/S	40193 E1.40	4511 E1.38	4568 E2.38
4026 E1.80	4066 57p	40194 E1.18	4512 81p	4569 E2.57
4027 45p	4067 E3.80	40257 E1.48	4514 E2.65	4572 25p
4028 81p	4068 22p	4160 E1.08	4515 E2.99	4580 E5.74
4029 99p	4069 20p	4161 E1.08	4516 E1.08	4581 E2.62
4030 58p	4070 23p	4162 E1.08	4517 E3.82	4582 98p
4031 E2.05	4071 21p	4163 E1.08	4518 E1.02	4583 76p
4032 E1.00	4072 21p	4174 E1.08	4519 51p	4584 43p
4033 E1.45	4073 21p	4175 99p	4520 E1.08	4585 E1.01
4034 E1.96	4074 23p	4194 E1.08	4521 E1.08	4595 E1.20
4035 E1.11	4075 23p	4408 E6.39	4522 E1.08	4597 E2.32
4036 E2.45	4076 23p	4409 E6.59	4524 N/S	4598 E2.65
4037 E1.00	4077 21p	4410 E5.73	4526 E1.08	4599 E5.95
4038 E1.08	4081 20p	4411 E9.58	4527 E1.52	4700 E1.75
4039 E2.45	4082 21p	4412P E9.43	4528 99p	
4040 E1.05	4085 74p	4415P E7.50	4529 E1.14	
4041 80p	4086 73p	4415P N/S	4530 85p	

74C

74C00 24p	74C83 E1.29	74C164 E1.04	74C905 E7.26	*74C925 E4.84
74C02 24p	74C85 E1.29	74C165 E1.04	74C906 54p	74C927 E4.84
74C04 24p	74C86 64p	74C173 90p	74C907 54p	74C928 E4.84
74C08 24p	74C89 E4.38	74C174 E1.51	74C908 96p	74C929 E11.93
74C10 E1.41	74C90 85p	74C175 90p	74C909 E1.63	74C948 TBA
74C12 24p	74C93 85p	74C192 E1.10	74C910 E6.78	80C95 54p
74C14 24p	74C96 E1.04	74C193 E1.10	74C911 E1.10	80C96 61p
74C16 E1.41	74C107 E1.22	74C195 E1.04	74C912 E7.13	80C97 54p
74C20 24p	74C150 E4.12	74C200 E6.78	74C914 E1.41	80C98 61p
74C30 24p	74C151 E2.46	74C221 E1.36	74C915 E1.10	82C19 E4.13
74C32 24p	74C154 E3.67	74C373 E1.73	74C918 E1.06	88C29 E1.33
74C42 92p	74C157 E2.20	74C374 E1.73	74C921 E1.83	88C30 E1.93
74C48 E1.36	74C161 E1.10	74C391 E1.10	74C922 E3.56	
74C73 54p	74C162 E1.10	74C902 54p	74C923 73p	
74C74 56p	74C163 E1.10	74C903 54p	74C924 TBA	
74C76 54p		74C904 54p	74C925 E4.84	

VIDEO NEW SWITCH MODE PSUs

UM1111E36 UHF Ca.36 Vision Modulator £2.50 (+12% VAT)

UM1231 UHF Ca.36 Vision Modulator wide bandwidth (for computers etc) £4.70 (+8% VAT)

AC 52218 5v/10A remote sense £63.25

AC 82218 5v/5A +12v/1A -12v/1A £78.90

AC 92218 as 8221 but also -5v/0.1A £84.30

Typically 70% efficient. Dims. 4" x 8 1/2" x 2"

MICROPROCESSORS

COMPUTER BOARDS	8000	8000	8000
114 x 285 mm fibreglass with gold plated edge connector. Designed for a range of MPU's Z80, SC/MP etc.	5800 MPU £6.55	6800 MPU £9.95	6801 (28 x 8 RAM) £2.97
SC/MP Protoboard £5.95	6802 MPU £3.75	6803 (28 x 8 RAM) £3.75	6804 8221 PIA £3.98
Z80 CPU card £4.95	6805 A2A £3.06	6805 A2A £3.06	NC8880/89AP £2.64
YOU 'B' set £4.95	6502	6502 CPU £12.00	6502 PIA £9.22
YOU 'G' three £5.95	COSMAC	COSMAC 1802 £9.85	COSMAC 1804 £7.25
EPROM Programmer (2708s) £5.95	STATICS (Mostly 4500s)	2101-256 x 4 £2.25	2102-1K x 1 £1.20
8k PROM board (£2708) £5.95	2111-256 x 4 £1.75	2112-256 x 4 £2.25	2114-1K x 4 £3.50
2k RAM board (2102s) 1K-2K £5.95	2114-1K x 4 £3.50	4118-1K x 8 (2708 Compatible) £18.50	
8k RAM board (2114) 1K-2K £9.95	DYNAMICS	DK 4027 4K 250K £3.50	DK 4116 16K 250K £8.75
TAPE interface £4.95	DK 4816 2K x 8 £30.52	UV ERASABLES	S204 4K x 8 £7.50
PSU 5v +12v -12v board £4.95	2708 1K x 8 £7.50	2708 1K x 8 £7.50	2716 2K x 8 single 5v £32.28
PSU 5v -12v board £4.95	TMS 2716 £16.95	UV PROM ERASER	PROMOX 12 £63.63
Further details on request (Others is to be announced)	INTERFACE	81LS95/6/7/8 £1.25	75491 LED driver 50p
	75492 92p	75493 7912 £1.08	75494 7912 £1.08
	75495 7912 £1.08	75496 7912 £1.08	75497 7912 £1.08
	75498 7912 £1.08	75499 7912 £1.08	75500 7912 £1.08

74LS

74LS00 14p	74LS27 28p	74LS78 40p	74LS125 60p	74LS163 E1.18
74LS01 14p	74LS28 28p	74LS79 40p	74LS126 60p	74LS164 E1.14
74LS02 16p	74LS32 27p	74LS83 E1.15	74LS132 95p	74LS165 75p
74LS03 16p	74LS33 39p	74LS85 E1.18	74LS138 85p	74LS166 E2.25
74LS04 16p	74LS37 39p	74LS86 43p	74LS139 85p	74LS167 E2.88
74LS05 20p	74LS38 39p	74LS89 43p	74LS140 85p	74LS168 E2.88
74LS06 22p	74LS40 28p	74LS90 43p	74LS141 E1.70	74LS169 E2.88
74LS07 22p	74LS42 98p	74LS91 E1.04	74LS142 E1.73	74LS170 E2.88
74LS08 22p	74LS44 98p	74LS92 89p	74LS143 E1.16	74LS171 E1.05
74LS09 22p	74LS45 E1.20	74LS93 E1.16	74LS144 E1.16	74LS172 E1.05
74LS10 20p	74LS46 E1.20	74LS94 E1.16	74LS145 E1.06	74LS173 E1.05
74LS11 22p	74LS47 44p	74LS95 96p	74LS146 E1.06	74LS174 E1.06
74LS12 23p	74LS48 24p	74LS96 96p	74LS147 E1.06	74LS175 E1.06
74LS13 38p	74LS49 24p	74LS97 96p	74LS148 E1.70	74LS176 E1.06
74LS14 75p	74LS50 30p	74LS98 96p	74LS149 E1.70	74LS177 E1.06
74LS15 30p	74LS51 30p	74LS99 96p	74LS150 E1.70	74LS178 E1.06
74LS16 30p	74LS52 30p	74LS100 96p	74LS151 E1.70	74LS179 E1.06
74LS17 20p	74LS53 E1.50	74LS101 96p	74LS152 E1.70	74LS180 E1.40
74LS18 22p	74LS54 41p	74LS102 96p	74LS153 75p	74LS181 E1.40
74LS19 22p	74LS55 41p	74LS103 96p	74LS154 E1.70	74LS182 E1.40
74LS20 20p	74LS56 41p	74LS104 96p	74LS155 96p	74LS183 E1.40
74LS21 22p	74LS57 41p	74LS105 96p	74LS156 96p	74LS184 E1.40
74LS22 48p	74LS58 41p	74LS106 96p	74LS157 96p	74LS185 E1.40
74LS23 48p	74LS59 41p	74LS107 96p	74LS158 96p	74LS186 E1.40
74LS24 22p	74LS60 41p	74LS108 96p	74LS159 96p	74LS187 E1.40
74LS25 48p	74LS61 41p	74LS109 96p	74LS160 96p	74LS188 E1.40
74LS26 48p	74LS62 41p	74LS110 96p	74LS161 96p	74LS189 E1.40
		74LS111 96p	74LS162 96p	74LS190 E1.40
		74LS112 96p	74LS163 96p	74LS191 E1.40
		74LS113 50p	74LS164 96p	74LS192 E1.40
		74LS114 50p	74LS165 96p	74LS193 E1.40
		74LS115 50p	74LS166 96p	74LS194 E1.40
		74LS116 50p	74LS167 96p	74LS195 E1.40
		74LS117 70p	74LS168 96p	74LS196 E1.40
		74LS118 70p	74LS169 96p	74LS197 E1.40
		74LS119 70p	74LS170 96p	74LS198 E1.40
		74LS120 70p	74LS171 96p	74LS199 E1.40
		74LS121 E1.80	74LS172 96p	74LS200 E1.40
			74LS173 96p	74LS201 E1.40
			74LS174 96p	74LS202 E1.40
			74LS175 96p	74LS203 E1.40
			74LS176 96p	74LS204 E1.40
			74LS177 96p	74LS205 E1.40
			74LS178 96p	74LS206 E1.40
			74LS179 96p	74LS207 E1.40
			74LS180 96p	74LS208 E1.40
			74LS181 96p	74LS209 E1.40
			74LS182 96p	74LS210 E1.40
			74LS183 96p	74LS211 E1.40
			74LS184 96p	74LS212 E1.40
			74LS185 96p	74LS213 E1.40
			74LS186 96p	74LS214 E1.40
			74LS187 96p	74LS215 E1.40
			74LS188 96p	74LS216 E1.40
			74LS189 96p	74LS217 E1.40
			74LS190 96p	74LS218 E1.40
			74LS191 96p	74LS219 E1.40
			74LS192 96p	74LS220 E1.40
			74LS193 96p	74LS221 E1.40
			74LS194 96p	74LS222 E1.40
			74LS195 96p	74LS223 E1.40
			74LS196 96p	74LS224 E1.40
			74LS197 96	

TAMTRONIK LTD. (DEPT. ETI)

217 TOLL END ROAD, TIPTON
WEST MIDLANDS DY4 0HW

TEL. 021-557 9144

PRINTED CIRCUIT BOARDS and KITS FOR ETI PROJECTS

ADDITIONAL PRINTED CIRCUIT BOARDS

Pcbs are available for all projects from September 1976 (except where copyright restrictions exist).

Mag. Issue	Project	Kit. Ref.	P.C.B.	Kits	Kit. contents (see key)
Sep. 77	'Graphic Equaliser	601	2.50	23.75	BFGH
Sep. 77	'Graphic Equaliser P.S.U.	602	90	2.50	BFG
Aug. 77	'Sweep Oscillator	606	4.00	41.95	BFGHL
Sep. 77	'Stereo Simulator	607	1.05	6.95	BEGHL
Nov. 76	'General Purpose Preamp	609	1.00	4.85	BEG
Jul. 77	'GSR Monitor	612	1.10	19.75	BEGHL
Nov. 77	'Stereo Amplifier	615	1.15	13.20	BEGHL
Nov. 77	'Compressor	617	2.55	27.35	BEGHL
Mar. 77	'50 watt High Power Amp	618	2.10	9.75	BE
Mar. 77	'100 watt High Power Amp	619	2.10	12.80	BE
Mar. 77	'High Power Amp P.S.U.	620	1.65	8.70	BEJ
Oct. 77	'Digital Thermometer	621	1.70	21.85	BFGHL
Feb. 77	'LED Dice	624	90	7.10	BEGHL
Nov. 77	'Skeet	627	2.55	21.90	BEGHL
	'Flash Trigger	628	1.10	6.25	BEGJ
	'Disco Light Show	629	4.25	25.95	BFGJ
	'Pink Noise Generator	630	1.05	4.30	BEL
Nov. 76	541 Train Controller	T001	1.35	18.85	BEL
Jan. 77	444 5 watt Stereo (2 pcbs)	T002	3.10	26.95	BEGK
Feb. 77	448 Disco Mixer	T003	2.35	19.40	BEJ
Dec. 77	House Alarm A	T004	3.30	16.75	BE
Jan. 78	House Alarm B	T005	3.20	30.50	BEHM
Feb. 78	Metal Locator Mk. II	T006	1.50	5.50	BE
March 78	'Frequency Shift P.S.U.	T007	1.60	22.80	BEHL
	'Frequency Shifter	T008	1.10	5.95	BEL
	L.C.D. Meter	T009	2.50	24.95	BEG
Apr. 78	Light Dimmer	T010	1.60	27.95	BEH
May 78	Gas Monitor	T011	90	8.60	BEHL
May 78	Star Trek Radio	T012	1.40	15.95	BEH
June 78	Spectrum Analyser (2 pcbs)	T013	1.55	9.80	BFH
	Wein Oscillator	T015	1.45	76.95	CERM
	Torch Finder	T016	1.45	17.20	BEH
	Temperature Meter	T018	7.75	20.70	BEG
Aug. 78	Etiket Plant Waterer	T019	1.60	6.10	BEH
Sept. 78	Cross Hatch Generator	T020	1.30	14.95	BEGHL
	Stac Timer	T021	2.10	27.45	BEJL
	Wheel of Fortune	T022	1.55	9.80	BEHL
Oct. 78	Complex Sound Generator	T023	3.95	25.75	BEH
	R.F. Power Meter	T024	1.60	15.30	BEHL
	Power Bulge	T025	85	3.65	BEHL
	Telephone Bell Extender	T026	1.25	11.40	BEHL
Oct. 78	Proximity Switch	T027	2.30	15.35	BEGH
Feb. 78	Ultra Sonic Receiver	T028	1.00	10.75	BEH
Feb. 78	Ultra Sonic Transmitter	T029	90	5.65	BEH
Nov. 78	Cuts Cassette Interface	T030	2.70	14.95	BEH
	Audio Oscillator (2 pcbs)	T031	4.60	39.95	BEJ
	Car Alarm (2 pcbs)	T032	2.50	6.95	BEHL
Dec. 78	Wine Temperature Meter	T033	1.30	10.95	BEHL
	Curve Tracer	T034	1.20	23.35	BEH
	Eprom Programmer	T035	2.65	6.25	BE
	Car Tachometer	T036	1.70	12.20	BF
Jan. 78	Eprom Programmer P.S.U.	T037	2.50	21.55	BE
	Digital Module A & B (2 pcbs)	T038	1.40	8.90	BE
	Digital Dial (Excl. T039)	T039	3.60	26.75	BE
	Log Converter	T040	2.30	20.95	BEHL
Feb. 79	Tape Slide Synchroniser	T041	80	3.70	BEHL
	Tape Noise Limiter	T042	2.65	35.85	BEH
	Light Activated Tachometer	T043	75	6.75	BEHL
Mar. 79	Headlight Delay	T044	2.70	18.95	BEH
	Logic Trigger	T045	2.95	47.95	TBA
	Stage Dimmer Control Module	T046	6.30	26.30	BEH
	Stage Dimmer Module 10 amp	T047	6.30	27.55	BEH
	Stage Dimmer Module 20 amp	T048	3.45	72.45	BEH
	Audio Power Meter	T049	4.55	49.95	BEHL
Apr. 79	Click Eliminator	T050	3.40	27.40	BEH
	Wind speed Indicator	T051	1.20	11.69	BEGHL
	Guitar effect unit	T052	1.65	14.95	BEHM
May 79	Double Die	T053	2.75	23.30	BEH
	Headphone amp.	T054	2.75	7.95	BEH
	Car immoboliser	T055	90	5.45	BEGHL
June 79	Mains speaker	T056	2.10	15.95	BEGHL
	Accentuated beat metronome	T057			BEGHL

KITS WITH A PROFESSIONAL FINISH

CCD Phasor
Improved version of project from ETI May 1978 includes screen printed Facias & PCB. CCT DIAG.

Complete KN
Only £45.00 inc. VAT & P&P

SPECTRUM ANALYSER
June '78 Ref. T015
Includes: 2 x Pcb's with component screened layout. Components: switches, Electro Microphone, etc. Screen printed End Plate. Screen printed Case.
Price includes VAT & P&P £78.95

HOUSE ALARM
Jan. '78 Ref. T005/G
Control Console for complete house protection.
Kit includes Vero 'G' range brushed aluminium instrument case with black front panel screen printed.
Price includes VAT & P&P £36

KEY TO KIT CONTENTS

- A. Vero-board(s).
- B. Printed Circuit Board(s).
- C. With Screen printed component layout.
- D. Tag strip.
- E. All Resistors, potentiometers, capacitors, semi-conductors.
- F. As E but with exclusions. Please ask for details.
- G. DIL and/or transistor sockets and/or soldercon pins.
- H. Hardware includes switches, knobs, lamps and holders, fuses and holders, plugs and sockets, microphones, transformers, speakers, meters, relays, terminal blocks, battery connectors, etc. BUT excludes nuts, bolts, washers, connecting wire, batteries and special miscellaneous items.
- J. As H but with exclusions. Please ask for details.
- K. As H but including connecting wire.
- L. Suitable case(s).
- M. Suitable case with screen printed facia.
- N. Full kit to magazine specified standards.
- P. Kit with professional finish — incorporating all prime features including screen printed pcb and case where appropriate.

SYSTEM 68

631	3.35
Mainframe PSU	1.45
VDU A	4.50
VDU B	4.30
CPU	3.80
TTY	3.70
Cuts & 4K Ram	3.80

SPECIAL OFFERS

Plug-in mains PSU 3v-6v-9v-12v DC 300MA.
Suitable for calculators, TV Games, etc... £2.99.
100 x 1/2 W 1K Resistors 30p
4 x NE 555 £1.00

Tamtronik Ltd. reserves the right to change kit content without notice to incorporate current modifications or to make valid substitutions for temporary unavailable components.
The majority of kits advertised can be supplied from stock, however please allow 21 days delivery since demand on any kit is unpredictable.

Kits can be supplied excluding pcb and/or case. Send sae for details naming kit and kit reference and free catalogue.

Trade and Educational enquiries welcome

Minimum order £3 please
Prices include P&P
VAT please add only 5%

Telephone or Letter

PCBs and kits available from Tamtronik Ltd. for projects from HOBBY ELECTRONICS AND EVERYDAY ELECTRONICS. Send SAE for free catalogue. Please quote project and kit reference number when details of a specific kit are required, sae.



Clef Kits



Designer approved quality kits for Electronic Musical Instrument Construction.

JOANNA 72 & 88 PIANOS
Six and 7 1/4 Octave Electronic Pianos with unique Touch Sensitive Action, as used in the P.E. JOANNA, which electronically simulates piano key inertia — a feature not available in any other design.

P.E. STRING ENSEMBLE
The only kit available to the proven A. J. Boothman Design for this versatile String Machine.

Specialists in all sizes of square Front Keyboards

Send SAE to:

Clef Products (Dept E.T.I.)
16 Mayfield Road, Bramhall, Cheshire SK7 1JU.

NASCOM I KIT OR BUILT * SUPERBOARD II ON DEMO NOW * 2k BASIC FOR STANDARD NASCOM I

ELECTRONIC MASTERMIND

NEW



£15.85

Play 9 Mastermind games against the computer or set your own secret code 3, 4 or 5 digits.

Free Mini Mastermind with each order



All prices inclusive - P & P free

N.I.C. MODELS

27 Sidney Road, London N22 4LT
01-889-9736

CHESS CHAMPION

6-level Chess Computer
£95.30 with mains adaptor.

STAR CHESS TV GAME

in colour
A space-age chess game
£69.16 £63.36 with mains adaptor

CHROMA-CHIME
24-tune door chimes
Kit £10.50. Built £15.30.

TRS80-100 Programs on Tape
£49.50
S.a.e. with all enquiries.

Please allow up to 21 days for delivery

SINCLAIR PRODUCTS*

PFM200 £49.48, case £3.19, adaptor £3.19, connector kit £10.58. Microvision TV UK model £89.95, mains adaptor £6.73, PDM35 £28.95, mains adaptor £3.19, case £3.19, 30kV probe £18.90, DM350 £97.45, DM450 £95.95, DM235 £49.45. Accessories for all 3 models — rechargeable batteries £7.50, mains adaptor/charger £3.70, case £8.45, 30kV probe £18.90. Enterprise prog calculator with accessories £22.95. New 10MHz scope p.o.a.

CALSCOPE OSCILLOSCOPES*

Send size for details or see the Calscope advert in this magazine. Super 6: 6MHz single beam 60ns rise time £174. Super 10: 10MHz dual trace 35ns rise time £236.

COMPUTER GAMES*

Star Chess £58.45. Chess champion 6 £88.50 Chess challenger 7 £95. Chess challenger 10 £183.50. Voice challenger p.o.a. Checker challenger 2 £64. Checker challenger 4 £84. Atari video computer £138. Cartridges £13.48.

CONTINENTAL SPECIALITIES PRODUCTS*

EXP300 £21. EXP350 £3.40. EXP325 £1.73. EXP600 £8.80. EXP650 £3.89. EXP4B £2.48. PB6 £9.84. PB100 £12.74. LM1 £30.99. LP1 £33.48. LP2 £19.44. MAX100 £83.75.

TV GAMES

Tank battles kit £5.95. AY-3-8500 chip £4.95, kit £4. Stunt cycle AY-3-8760 chip £11.70, kit £4. 10 game paddle 2 AY-3-8610 chip £8.90, kit £8.60. Racing car chip AY-3-8603 £8.90. Modified shoot kit £4.99. Rifle kit £4.95. Colour generator kit £8.50. Joystick 220K £1.99.

MAINS TRANSFORMERS

6.0-6V 100ma 74p, 1 1/2 £2.35. 6.3V 1 1/2 £1.89. 9.0-9V 75ma 74p, 1a £1.89, 2a £2.60. 12.0-12V 50ma 74p, 100ma 90p, 1a £2.49. 13V 1/2 £8.95. 15.0-15V 1a £2.79. 30.0-30V 1a £3.59.

JC12 AND JC20 AMPLIFIERS

Integrated circuit audio amplifier chips supplied with free data and printed circuits. JC12 6 Watts £1.95. JC20 10 Watts £2.95. We also stock a range of matching preamp and power kits.

FERRANTI ZM414

IC radio chip £1.05. Extra parts and pcb for radio £3.85. Case £1.

S-DECS AND T-DECS*

S-Dec £3.80. T-Dec £4.02. U-Dec £4.40. U-o-ECB £8.73. 16 dii adaptor with socket £2.17.

PRINTED CIRCUIT MATERIALS

PC etching kits. Economy £2.18, standard £4.10. 40 sq ins pcb 60p. 1lb FeCl £1.13. Etch resist pens: Economy 45p, dial 79p. Small drill bits 1/32ins or 1mm 23p each. Etching dish 85p. Laminator cutter 75p.

BATTERY ELIMINATORS

3-way types with switched output and 4-way multi-jack: 3/4/5/6V 100ma £2.21. 6/7/8/9/300ma £2.95. 100ma radio types with press-stud connectors 9v £3.35, 6v £3.35, 4.5v, £3.35, 9+9v £4.50, 6+6v £4.50, 4 1/2+4 1/2v £4.50. Cassette recorder mains unit 7 1/2v 100ma with 5 pin din plug £3.35. Fully stabilised type 3/16/7 1/2/9v 400ma £5.30. Car converters 12v dc input, output 9v 300ma £1.50, output 7 1/2v 300ma £1.50. Output 3 1/4/5/6/7 1/2/9/12v 800ma £2.50.

BATTERY ELIMINATOR KITS

100ma radio types with press-stud connectors 4 1/2v £1.40, 6v £1.40, 9v £1.40, 4 1/2+4 1/2v £1.80, 6+6v £1.80, 9+9v £1.80. Cassette type 7 1/2v 100ma with din plug £1.40. Heavy duty 13-way types 4 1/2/6/7/8 1/2/11/13/14/17/21/25/28/34/42v 1A £4.95, 2A £7.25. Transistor stabilised 9-way types for low hum 3/4/5/6/7 1/2/9/12/15/18v 100ma £2.80, 1Amp £8.40. Variable voltage stabilised models 2-18v 100ma £2.80. 2-30v 1A £8.95. 2-30v 2A £10.95. Car converter 12v dc input. Output 9/7 1/2/6v 1A stabilised £1.35.

BI-PAK AUDIO MODULES

AL30 £3.95. PA12 £7.60. PS12 £1.39. T538 £2.95. S450 £23.51. AL60 £4.88. PA100 £16.95. SPM80 £4.47. BMT80 £5.95. Stereo 30 £20.12. MA60 £35.44.

COMPONENTS

1N4148 1.4p. 1N4002 2.9p. 741 8 dii 17p. 723 14 dii 29p. NE555 8 dii 23p. bc182b, b183b, bc184b, bc212b, bc213b, bc214c, bc547, bc548, bc549, 8p, tip31c, tip32c 34p, tip41c, tip42c 45p, bd131, bd132 31p. Plastic equiv bc107 4.8p. Fuses 20mm x 5mm cartridge .15, .25, .5, 1, 2, 3, 5Amp quickblow 1p, anti-surge 3.4p. Resistors 5% 1/4W £12 10R to 10M 1p, 0.8p for 50+ of one value Polyester capacitors 250v .015, .068, .1mf 1.5p, .01, .033, .33mf 2.7p, .022, .047mf 3.2p, .22, .47mf 4.8p. Polystyrene capacitors E12 63v 10 to 1000pf 3p, 1n2 to 10n4p. Ceramic capacitors 50v, 5, 1, 2mf 5p, 25v 5, 10 5p, 16v 22, 33, 47, 68mf 5p, 100mf 6p, 220mf 7.5p, 330, 470mf 9p, 1000mf 10p. Zeners 400mW E24 2v to 33v 7p. Preset pots subminiature 0.1W horiz or vert 100 to 4M7 8.8p. Potentiometers 1/4W 4K7 to 2M2 log or lin single 25p, dual 78p. 1/4" red LEDs 9.1p. IC sockets 8 dii 8.1p, 14 dii 9.5p, 16 dii 11.3p.

SWANLEY ELECTRONICS

DEPT. ET1, 32 GOLDSSEL ROAD, SWANLEY, KENT BR8 8EZ

Mail order only. Please add 30p to the total cost of order for postage. Prices include VAT. Lists 20p post free. Overseas customers deduct 7% on items marked * and 11% on others. Official credit orders welcome. If VAT rate is charged in budget please adjust prices.

THE ARAK VIII POLYPHONIC KEYBOARD CONTROLLER



The Arak VIII is so named because it can handle up to eight note polyphony, and that means that if you have a large enough synthesizer you can play eight notes at once, and each one can be set to sound totally different.

The Arak VIII is a controller in every sense of the word. For instance it has built in vibrato so you don't waste those precious V.C.O.s. You can instantly get back to that fat monophonic sound by flicking the unison switch. Just touch the keys with infinite sustain selected and the Arak VIII brings in a big power chord while you get on with playing another instrument. Memorising a chord is no problem using the memory bank facility. You can even sequence between two chords set in the memory banks and interact with them from the keyboard. We designed the Arak VIII to interface with just about anything, apart from the gate and control voltage outputs, which incidentally, can be scaled between zero and two volts per octave, there is an I/O so you can interface it to a computer. This allows a computer to take data from the Arak VIII or feed data in and control the synth.

The case is hand-built out of black anodised aluminium and is finished off with solid mahogany end cheeks. Legends are silk screened on the front and back so you know precisely what to twiddle and what to plug into.

Arak VIII kit £248.39
Arak VIII ready-built and tested £382.22

Prices include VAT

*Four more store / portamento circuits are needed to give the necessary number of control voltages.

ARAK SOUND
PRESTON HOUSE, HIGH STREET
CROWTHORNE, BERKS. TEL. CROWTHORNE 2550

24 TUNE DOOR CHIMES

DOOR TUNES £16.44 + VAT.

Waddington's Videomaster announce a doorbell that doesn't go Brrringgg, Ding-Dong or Bzzzzz. Instead it plays 24 different classical and popular tunes. It will play the tune you select for your mood, the season or the visitor you are expecting to call. Door tunes is not only great fun and a wonderful ice breaker, but is also very functionally and beautifully designed to enhance your home. There is something for Christmas, something for your continental visitors or your relations from the states, and even something for the Queen. Door tunes is easy to install and has separate controls for volume, tone and tempo.



T.V. GAMES

PROGRAMMABLE £29.50 + VAT.

COLOUR CARTRIDGE T.V. GAME.

The TV game can be compared to an audio cassette deck and is programmed to play a multitude of different games in COLOUR, using various plug-in cartridges. At long last a TV game is available which will keep pace with improving technology by allowing you to extend your library of games with the purchase of additional cartridges as new games are developed. Each cartridge contains up to ten different action games and the first cartridge containing ten sports games is included free with the console. Other cartridges are currently available to enable you to play such games as Grand Prix Motor Racing, Super Wipeout and Stunt Rider. Further cartridges are to be released later this year, including Tank Battle, Hunt the Sub and Target. The console comes complete with two removable joystick player controls to enable you to move in all four directions (up/down/left/right) and into these joystick controls are ball serve and target fire buttons. Other features include several difficulty option switches, automatic on screen digital scoring and colour coding on scores and balls. Lifelike sounds are transmitted through the TV's speaker, simulating the actual game being played.

Manufactured by Waddington's Videomaster and guaranteed for one year.



EXTRA CARTRIDGES

ROAD RACE — £8.87 + VAT.

Grand Prix motor racing with gear changes, crash noises

SUPER WIPEOUT — £9.17 + VAT.

10 different games of blasting obstacles off the screen.

STUNT RIDER — £12.16 + VAT.

Motorcycle speed trials, jumping obstacles, leaping various rows of up to 24 buses etc.

NON-PROGRAMMABLE TV GAMES

6 Game — COLOURSCORE II — £13.50 + VAT.

10 Game COLOUR SPORTSWORLD £22.50 + VAT.

CHESS COMPUTERS

STAR CHESS — £55.09 + VAT.

PLAY CHESS AGAINST YOUR PARTNER.

Using your own TV to display the board and pieces. Star Chess is a new absorbing game for two players, which will interest and excite all ages. The unit plugs into the aerial socket of your TV set and displays the board and pieces in full colour for black and white on your TV screen. Based on the moves of chess, it adds even more excitement and interest to the game. For those who have never played, Star Chess is a novel introduction to the classic game of chess. For the experienced chess player, there are whole new dimensions of unpredictability and chance added to the strategy of the game. Not only can pieces be taken in conventional chess type moves, but each piece can also exchange rocket fire with its opponents. The unit comes complete with a free 18V mains adaptor, full instructions and twelve months guarantee.



CHESS CHALLENGER 7 — £85.65 + VAT.

PLAY CHESS AGAINST THE COMPUTER.

The stylish, compact, portable console can be set to play at seven different levels of ability from beginner to expert including "Mate in two" and "Chess by mail". The computer will only make responses which obey international chess rules. Casting, on passant, and promoting a pawn are all included as part of the computer's programme. It is possible to enter any given problem from magazines or newspapers or alternatively establish your own board position and watch the computer react. The positions of all pieces can be verified by the computer memory recall button.



ELECTRONIC CHESS BOARD TUTOR £19.75 inc. VAT.

A special bulk purchase of these amazing chess teaching machines enables us to offer them at only £19.75 less than half recommended retail price. The electronic chess tutor is a simple battery operated machine that can actually teach anyone to play chess and improve their game right up to championship level. This machine is not only for total beginners but also for established players wanting to play better chess. Unit contains the electronic chessboard with 32 chess pieces, a 64 page explanatory booklet and a set of 32 progressive programme cards including 6 beginners cards, 16 check mate positions, 9 miniature games, 5 openings, 3 end games, 29 chess problems and 2 master games.

OTHER CHESS COMPUTERS IN OUR RANGE INCLUDE:

CHESS CHAMPION — 6 LEVELS £82.67 + VAT.

CHESS CHALLENGER — 10 LEVELS — £143.06 + VAT.

BORIS — MULTI-LEVEL TALKING DISPLAY £165.28 + VAT.


DRAUGHTS COMPUTERS

CHECKER CHALLENGER 2 LEVELS £43.98 + VAT.

4 LEVELS £80.09 + VAT.

PLAY DRAUGHTS/CHECKERS AGAINST THE COMPUTER

The draughts computer enables you to sharpen your skills, improve your game, and play whenever you want. The computer incorporates a sophisticated, reliable, decision making microprocessor as its brain. Its high level of thinking ability enables it to respond with its best counter moves like a skilled human opponent. You can select offence or defence and change playing difficulty levels at any time. Positions can be verified by computer memory recall. Machine does not permit illegal moves and can solve set problems. Computer comes complete with instructions, mains adaptor and twelve months guarantee.

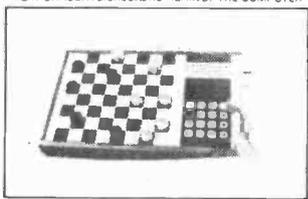

FOR FREE BROCHURES — SEND S.A.E

For FREE illustrated brochures and reviews on TV and chess games please send a stamped addressed envelope, and state which particular games you require information on.

Callers welcome at our shop in Welling — demonstrations daily — open from 9am-5.30pm Mon-Sat (9am-1pm Wed).

To order by telephone please quote your name, address and Access/Bardycard number.


Postage and Packing FREE.

AJD DIRECT SUPPLIES LIMITED, Dept. ET5, 102 Bellegrove Road, Welling, Kent DA16 3QD. Tel: 01-303 9145 (Day) 01-850 8652 (Evenings)

AUDIO AND TEST EQUIPMENT CENTRE

RETAIL
MAIL ORDER
EXPORT
ALL PRICES
INCLUDE VAT

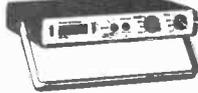Telephone your order with Access and Barclaycards or send cheque with order.



LONDON'S TEST GEAR CENTRE
OPEN 6 DAYS A WEEK 9 am-6 pm

SCOPES — (UK P/P £1.50 ea.)

3" 5MHz single beam	97.00
4" 5MHz Single beam	117.72
Super 6 Scope x 6MHz single beam	149.00
Super 10 Scope x 10MHz Dual trace	225.00
4D25. Scope x 25MHz Dual trace	339.00
PROBES x 1 x 10 14.50. x 10 9.95 x 1 7.95 For Super-6/10/4D25.	
SINCLAIR 10MHz Miniscope	Price to be announced

FREQUENCY COUNTERS

MAX 50 50MHz 6 digit pocket counter	57.50
MAX 100 100MHz 8 digit portable counter	83.75
MAX 550 550MHz 6 digit pocket counter	99.50
500 MHz Prescaler for max 50 or max 100	37.80
PFM200 Sinclair 200 mHz Pocket Counter 8 digit	49.95
OPTO7000 8 digit, 600 mHz Portable 1Hz RES with N/CADS and charger (was 168)	129.50

DIGITAL MULTIMETERS

DM235 Sinclair portable 3 1/2 digit LED	49.95
DM335 Sinclair Pocket 3 1/2 digit LED	29.95
DM350 New Sinclair 3 1/2 Digit } with 10 amp range	69.95
DM450 New Sinclair 4 1/2 Digit }	99.95
(30kV Probes 18.25. Mains adaptors 3.75. DM carrycase 8.95)	
M1200 Bench Portable 3 1/2 digit LED Resolution. 1 µA/0.1mv/0.01ohm	106.92
935 Data Precision 3 1/2 digit hand-held LCD 2 amp ac/dc	198.
198. Low cost 3 1/2 digit general purpose LCD	£49.95

MULTI-METERS — GENERAL PURPOSE & ELECTRONIC

Multi-Range Instruments featuring AC/DC volts, DC current, Resistance Ranges all with mirror scales except T1/IT1-T/2/T12/TM3A (TM3 AC volts only), some with AC current, etc.

TM11 incredible 120 Range Electronic Multi-meter	148.50
TM3B AC Micro voltmeter 3MHz > 4 Megohm	142.50
380TR 100k/volt	36.95
PROE 20k/volt	29.95
7081 50k/volt	21.95
Tmk500 30k/volt	21.95
680R 20k/volt	34.50
7200 20k/volt	17.95
Micro80 20k/volt	17.90
RE132m/171-2 20k/volt	11.95
LT22 20k/volt	14.50
T12 5k/volt	8.50
LT101 1k/volt	8.95
RE142m 20k/volt	13.50
RE152m 20k/volt	17.95
AT205 50k/volt 21 Range multi-meter	25.95
K200 FET VOM 38 Ranges	77.00
TR202 20k/volt 23 Ranges/Transistor Checker/Checker/Continuity Checker	£19.95

GENERAL EQUIPMENT

SE250 Signal Injector	4.95
TE7 Signal Tracer AF/RF	8.95
SWR50 SWR/Power Meter	19.50
LP30 30MHz Low Pass Filter	4.95
CX3A 150Watt 3-way AE Switch	7.50
DC25kV 100 Meg HV Probe	11.95
DRS10 36 Value Resis. Box	3.95
RP124 0/24v 0/1 Amp P/S Stabilised Single Meter	39.70
RP230N 0/30v 0/1 Amp. P/S Twin Meters	79.00
TR1000 Transistor checker in/out circuit	11.95
MOD63 Signal Injector	7.50
LB1 Transistor/Diode Checker	21.50
3101 Clamp Meter 0/1 K ohm 0/150/300/600 AC Volts 0/300 Amp	35.95
SWR9 SWR & FS Meter	9.95
SWR10 SWR Meter	12.50
MS319 2x100 Watt Audio Watt Meter	11.95
500V Megohmmeter 500 Megohms	48.00
2 1/2 Amp Variable Transformer	19.95

GENERATORS

TG152 Series 3Hz 300kHz 5 Ranges	61.00
TG152D	101.00
TG152Dm (with meter)	101.00
TG200 Series RC Oscillators Sine/Square output. 1Hz-1MHz 12 Ranges	125.00
TG200D	107.00
TG200Dm (with meter)	125.00
TG200Dmp (meter & line control)	137.00
TE22D (Audio) 4 bands. Sine 20-200KHz Square 20-150KHz	65.00
4001 Digital Pulse Generator 0.5Hz-5MHz 99.50	
2001 Function Generator-Sine/Square/Triangle/TTL Square 1Hz-100kHz	81.00

PROTO BOARD IN STOCK

KITS PR 6 £9.20, PR 100 £11.80.	
SEPARATES EXP300 £5.75, EXP600 £8.30, QT47B £1.30, EXP4B £2.30.	

LOGIC PROBES AND MONITORS

LT2000 Economy Probe. 10MHz	11.95
LM1 Monitor	31.00
LP1 Probe 10MHz	33.48
LP2 15MHz	19.44
16 Pin IC test clip	1.95


PIEZO HORN, TWEETERS

Up to 100 watts each. No xover reqd. Only	4.95 each
Flared Horns	6.50
Midrange Flared Horns	9.95
(P/P 20p per 1 or 2, 30p per 3 to 5)	

DRILLS AND DRILL KITS


9 to 12 volt Operated. 1/8" max.	
SMALL DRILL with collets	6.85
MEDIUM DRILL with 3 collets	9.90
SMALL DRILL with 20 drills etc.	16.95
SMALL DRILL with 6 P/C drills	12.95
MEDIUM DRILL with 20 drills etc.	16.95
MAINS Eliminators	9.95
VARIABLE Speed	13.95
12 volt 1/4" Heavy Duty Drill	12.50

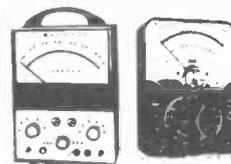MICROPHONES, SPEAKERS AND COMPONENTS LARGE RANGE IN STOCK



SPECIAL OFFER
GEC 20+20W Tower Amplifier
BW/LW/SW/STereo FM supplied
as two easy to connect units.
£24.95 p/p £1.00.

WE SELL
Kef, Seas, Audax, Fane,
Goodmans, Motorola,
Peerless
Speakers/Kits, etc.
Also Irons, Tools, etc.

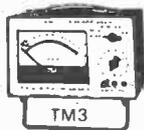

TM3

CALL IN AND SEE FOR YOURSELF

AUDIO ELECTRONICS

301 EDGWARE RD., LONDON W2 1BN
01-724-3564. OPEN 9-6, MON-SAT.

ALSO AT 248 TOTTENHAM COURT ROAD, W 1

FREE CATALOGUE

SEND STAMPED
(12" x 6" UK)
ADDRESSED ENVELOPE
(MIN 9" x 6")
FOR YOUR COPY NOW

GENTLEMEN the PET DISK has landed...



The U.K. designed and manufactured Novapac disk system for Commodore's PET*, first seen at Compec '78, is (after extensive industrial evaluation), now available to the domestic user. Its unique saddle configuration continues the integrated design concept of your PET, with no trailing wires or bulky desktop modules.

- Novapac may be used with any available RAM plane.
- Data transfer takes place at 15,000 char/sec — effectively 1000 times faster than cassette!
- Storage capacity is 125 K/bytes (unformatted) on 40 tracks per diskette side.
- Dual index sensors permit dual side recording for 250 K/bytes per diskette.
- Easy operation full width doors prevent media damage.
- System expandable to 1/2 M/byte on-line storage (4 drives).
- Dual head and 2D versions provide 2 M/bytes on-line.
- Industry Standard IBM 3740 recording format for industry-wide media compatibility only offered by NOVAPAC
- Dedicated Intel 8048 microprocessor and 177 1/2 FDC minimise PET software overhead.
- Local hardware and software support available.

The sophisticated Disk Operating System is disk resident, which allows for future DOS enhancements without hardware alterations. PDOS supports multiple file handling, dynamically allocating disk space to each as and when necessary. Any file may occupy from 1 to 600 sectors as required, at up to 16 non-contiguous locations on the disk, PDOS may be used alone, or within a BASIC program, and offers user-specified password security for any file. Multiple access-modes simplify BASIC program construction.

Novapac dual-disk system complete with PDOS and BASIC demonstration programs on disc **£950 + VAT**. Available from the manufacturer or selected dealers.

Terms: 50% with order, balance on delivery
Full cash with order is subject to 5% discount
VAT-FREE Export arranged (Must be shipped by us)

analog electronics

47A Ridgeway Avenue, Coventry
Tel: 0203 417761

Extension Trigger Device for Synthesizers

J. Trinder

The following device is intended to provide a trigger pulse for a synthesizer when using an external input source, e.g. a guitar.

The output from the guitar must first be amplified by a small power amplifier in order to bring the signal to a sufficient level to operate the device.

The AC input to the device is converted to DC by the bridge rectifier. When the DC level reaches a sufficient level the input of the AND gate is taken high. As the other input is already high its output becomes high.

When this happens the transistor is turned on, thus taking the output voltage to nearly zero. When the DC level at Pin 2 falls below the required level its output goes low thus turning

the transistor off.


The output from the device is approx 3V5 (off) and approx 0V (on). The LED is on when the unit is triggered.

The synthesizer intended for use with the circuit has an extension trigger input which requires less than -3V on, thus the common and output

connections of the external trigger device have to be reversed so that the external trigger input usually sees -3V5 (off) instead of +3V5.

The circuit can be easily modified to suit individual needs. An example of its use is to trigger a filter sweep when the input of, e.g. a guitar, reaches a certain level.

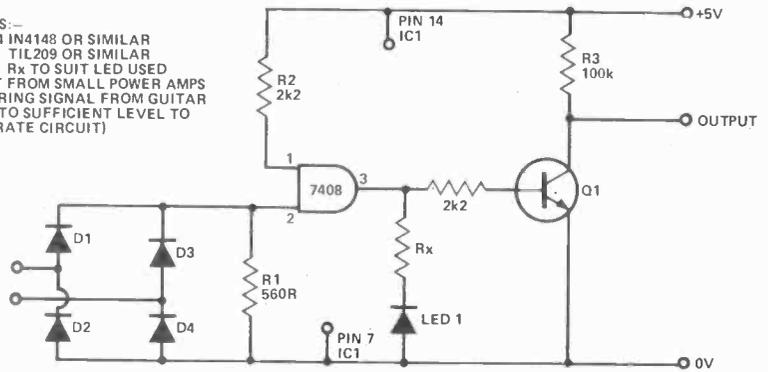NOTES:-
D1 - 4 1N4148 OR SIMILAR
LED 1 - TIL209 OR SIMILAR
Rx TO SUIT LED USED
INPUT FROM SMALL POWER AMPS
(TO BRING SIGNAL FROM GUITAR
ETC TO SUFFICIENT LEVEL TO
OPERATE CIRCUIT)



Solid State Tacho Circuit

P. Stephenson

The circuit is designed to give a non-critical display for those who like


(cheap) gadgets.

IC1a/b form an oscillator which drives decade counter IC2. During eight tenths of each cycle of this section, binary counter IC3 is counted up. On count "8", the counting stops and IC4 latches the out-

puts. On count "9" IC3 is reset.

The number now on IC4 output is decoded by IC 5/6 to light up one of 16 LEDs corresponding to rpm.

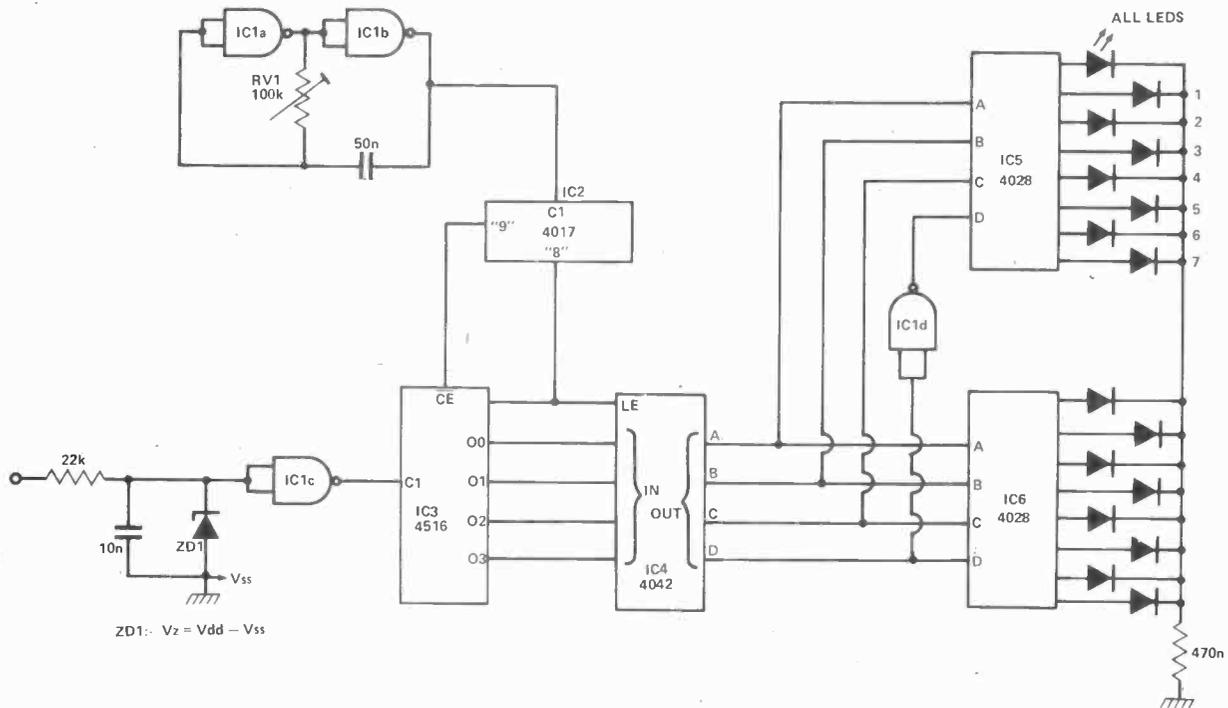Calibration is by adjusting RV1 whilst inputting a known frequency (e.g. mains frequency 50 Hz).




Tech-Tips is an ideas forum and is not aimed at the beginner. We regret we cannot answer queries on these items.

ETI is prepared to consider circuits or ideas submitted by readers for this page. All items used will be paid for. Drawings should be as clear as possible and the text should preferably be typed. Circuits must not be subject to copyright. Items for consideration should be sent to ETI TECH-TIPS, Electronics Today International, 145 Charing Cross Road, London WC2H 0EE.


HE

CITIZENS BAND

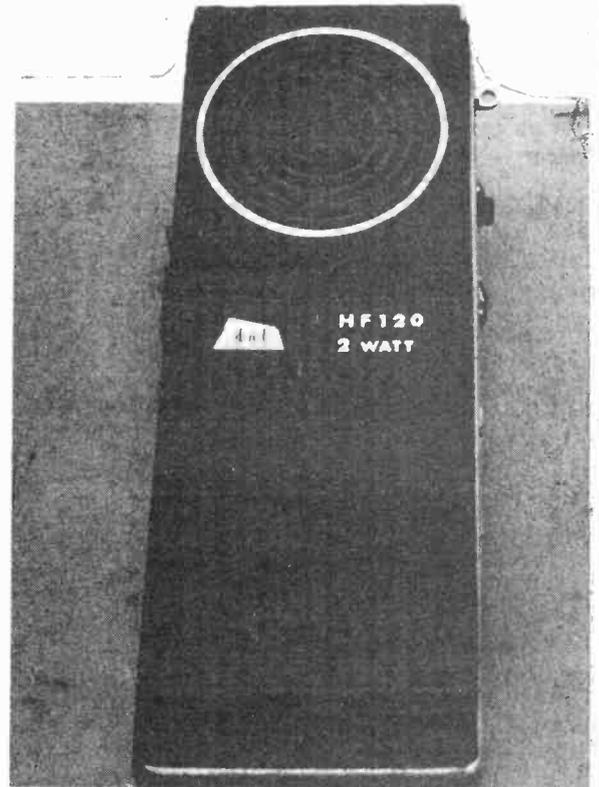The hottest news item in Britain, nay, the Universe. Hobby Electronics was the magazine that started the campaign and Hobby Electronics it is that brings you this 72-page bockbuster. All you ever wanted to know — and more. HE brings you the facts — now. Available in your newsagents NOW — price 60p or direct from us at 145 Charing Cross Road, London WC2H 0EE. Add 25p for P&P.




OUT NOW! 60p

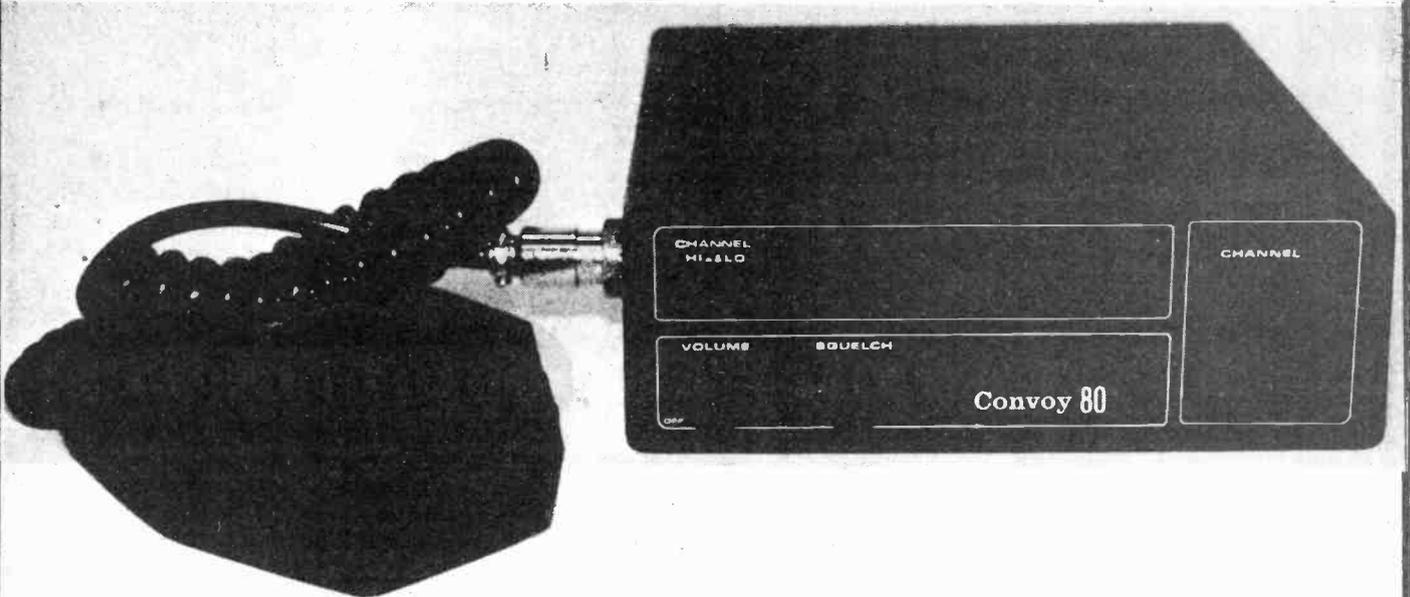

Mille-power Inverter

J. S. B. Dick

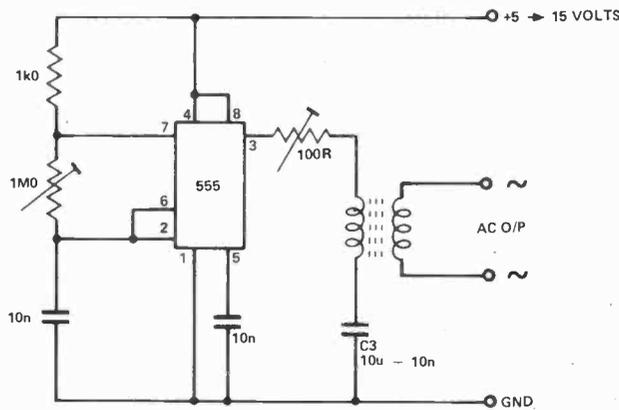

Many home-grown projects require a high voltage, low current source. The simplest and safest means of providing this is by an inverter. The circuit described here is versatile, efficient and easily capable of providing power for portable Geiger counters, dosimeter chargers, high resistance meters, etc.

The 555 timer IC is used in its multivibrator mode, the frequency being adjusted to optimise the transformer characteristics. When the output of the IC is high, current flows through the limiting resistor, the primary coil to charge C3. When the output goes low, the current is reversed. With a suitable choice of frequency and C3 a good symmetric output is obtained.

Precision AC to DC Converter

T. K. Tay

The circuit is a precision AC to DC converter (amplitude). The important feature is that the system operates happily with amplitude and frequency of V_{in} varying (e.g. speech signal).

IC1 in its inverting mode squares the incoming signal and leading-edge trigger mono 1 which produces a "sample pulse" to the switch. The sample pulse is in turn fed to mono 2 which triggers on the trailing-edge of the sample pulse and produces a pulse to clear or discharge C3.

IC2, the bipolar transistor and C3

form the rectifier and first hold circuit. C4 acts as the second hold circuit.



Thus after every $\frac{1}{2}$ cycle of V_{in} , the DC level of the first hold is being transferred to the second hold circuit by the sample pulse before the first

hold is clear again.

A level shifting network is used to shift the reference level to +6V.

With the components used in the circuit, the system works very well from 25 Hz to 20 kHz.

LEVEL SHIFTING NETWORK

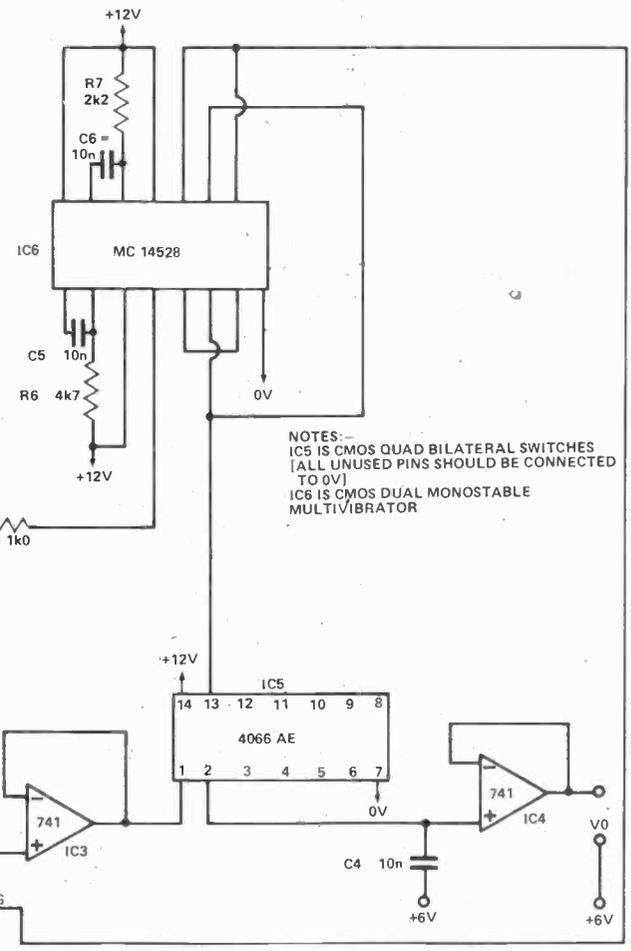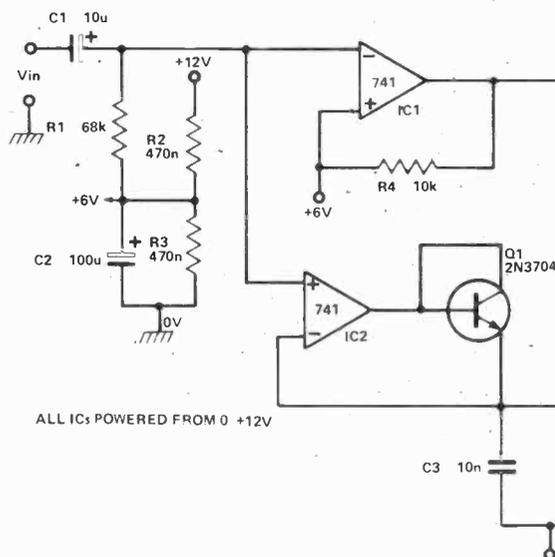


NOTES:-
IC5 IS CMOS QUAD BILATERAL SWITCHES
[ALL UNUSED PINS SHOULD BE CONNECTED TO 0V]
IC6 IS CMOS DUAL MONOSTABLE MULTIVIBRATOR


TOTAL AMPLIFICATION FROM CRIMSON ELEKTRIK

WE NOW OFFER THE WIDEST RANGE OF SOUND PRODUCTS

STEREO PRE-AMPLIFIER

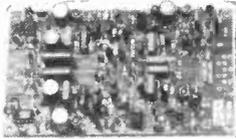

POWER AMPLIFIER

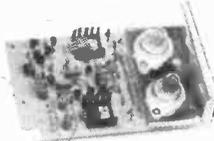


POWER SUPPLIES

We produce suitable power supplies which use our superb TOROIDAL transformers only 50mm high with a 1/20-240 primary and single bolt fixing (includes capacitors / bridge rectifier)

POWER AMPLIFIER KIT

PRE-AMPLIFIER KIT 1 THIS INCLUDES ALL METAL WORK, POTS, KNOBS, ETC. — TO MAKE A COMPLETE PRE-AMP WITH CPR 1 (S) MODULE AND THE MC1 (2) IS REQUIRED.

The kit includes all metalwork, heatsinks and hardware to house any two of our power amp modules plus a power supply. It is contemporarily styled and its quality is consistent with that of our other products. Comprehensive instructions and full back-up service enables a novice to build it with confidence in a few hours.

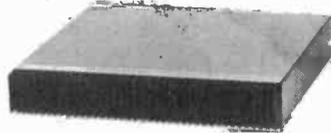

CPR 1—THE ADVANCED PRE-AMPLIFIER

The best pre-amplifier in the U.K. The superiority of the CPR 1 is probably in the disc stage. The overload margin is a superb 40dB, this together with the high slowing rate ensures clean top, even with high output cartridges tracking heavily modulated records. Common-mode distortion is eliminated by an unusual design. R.I.A.A. is accurate to 1dB; signal to noise ratio is 70dB relative to 3.5mV; distortion < .005% at 30dB overload 20kHz. Following this stage is the flat gain/balance stage to bring tape, tuner, etc., up to power amp. signal levels. Signal to noise ratio 86dB; slew-rate 3V/μs; T.H.D. 20Hz — 20kHz < .008% at any level. F.E.T. muting. No controls are fitted. There is no provision for tone controls. CPR 1 size is 138 x 80 x 20mm. Supply to be ± 15 volts.

MC 1 PRE-AMPLIFIER

Suitable for nearly all moving-coil cartridges. Sensitivity 70/170μV switchable on the p.c.b. This module brings signals from the now popular low output moving-coil cartridges up to 3.5mV (typical signal required by most pre-amp disc inputs). Can be powered from a 9V battery or from our REG 1 regulator board.

X02 : X03 — ACTIVE CROSSOVERS

X02 — two way, X03 — three way. Slope 24dB/octave. Crossover points set to order within 10%.

REG 1 — POWER SUPPLY

The regulator module, REG 1 provides 15-0-15v to power the CPR 1 and MC 1. It can be used with any of our power amp supplies or our small transformer TR 6. The power amp kit will accommodate it.

POWER AMPLIFIERS

It would be pointless to list in so small a space the number of recording studios, educational and government establishments, etc., who have been using CRIMSON amps satisfactorily for quite some time. We have a reputation for the highest quality at the lowest prices. The power amp is available in five types, they all have the same specification: T.H.D. typically .01% any power. 1kHz 8ohms; T.I.D. insignificant; slew rate limit 25V/μs; signal to noise ratio 110dB; frequency response 10Hz-35kHz; —3dB; stability unconditional; protection drives any load safely; sensitivity 775mV (250mV or 100mV on request); size 120 x 80 x 25mm.

POWER AMPLIFIER MODULES
 CE 608 60W/8 ohms 35-0-35v £18.33
 CE 1004 100W/4 ohms 35-0-35v £21.62
 CE 1008 100W/8 ohms 45-0-45v £24.38
 CE 1704 170W/4 ohms 45-0-45v £29.12
 CE 1708 170W/8 ohms 60-0-60v £31.90

TOROIDAL POWER SUPPLIES
 CPS1 for 2xCE 608 or 1xCE 1004 £15.55
 CPS2 for 2xCE 1004 or 2/4xCE 608 £17.86
 CPS3 for 2xCE 1008 or 1xCE 1704 £18.54
 CPS4 for 1xCE 1008 £16.08
 CPS5 1 for 1xCE 1708 £22.68
 CPS6mk 2xCE 1704 or 2xCE 1708 £23.98

HEATSINKS
 Light duty, 50mm, 2 C/W £1.35
 Medium power, 100mm, 1-4 C/W £2.20
 Disco / group, 150mm, 1-1 C/W £2.85
 Fan, 80mm, static 120 or 240v £18.50
 Fan mounted on two drilled 100mm heatsinks 2x4 C/W, 65 max. with two 170W modules £29.16

THERMAL CUT-OFF, 70°C £1.45

Distributors:
 Minic Teleprodukt
 Box 12035
 S-750 12
 Uppsala 12
 Sweden

CRIMSON ELEKTRIK
 1A STAMFORD STREET, LEICESTER LE1 6NL. Tel. (0633) 553508
 U.K. — please allow up to 21 days for delivery

Badger Sound Services Ltd., 46 Wood Street, Lytham St. Annes, Lancashire FY8 1QG.

All prices shown are UK only and include VAT and post. COD sup extra, £100 limit. Export is no problem, please write for specific quote. Send large SAE or 3 International Reply Coupons for detailed information.

INTRODUCING FROM OLYMPOS — ALARM CHRONOGRAPH



- ★ All Stainless Steel
- ★ Mineral Glass
- ★ Water Resistant
- ★ Fast Display

UM831
 Perpetual calendar, day, date, month, 24 hour alarm with on/off indication, 1/10 second chronograph measuring set, lap and first and second place times. Dual time zone facility, backlight. 12 months' guarantee

ONLY £29.95
 (Inc. VAT P&P)

SUPERBOARD II

(8K BASIC)

4k RAM — £259 8k RAM — £279

(modulator included)

FIBRE GLASS CASE £24.95

TRS 80 KEYBOARD

4K LEVEL II — £390* 16K — £490*

(modulator included)

POWER SUPPLY £9.90*

PHILIPS VIDEO COMPUTER

700 — £139* VIDEOPACS MOSTLY £10.95*

Complete range of games including a beginners computing course

SOFTY EPROM DEVELOPMENT-BURNER SYSTEM

(kit) — £79.50*

With direct O/P to TV and Cassette Interface

LCD ALARM CHRONOGRAPH

All usual features. Perpetual calendar, day, date, month and year. 24-hr. alarm with on/off indication. 1/10 second chronograph measuring set, lap and first and second place times. Dual time zone facility night light. 12-month guarantee



ONLY £21.95 (inc. VAT P&P) Same day despatch Same as ETI offer

LCD ALARM

24-hr. alarm Hours, mins, secs., date, month, back-light, auto calendar. Adjustable stainless steel bracelet. 12-month guarantee



VT10
 Same day despatch

ONLY £12.95
 (inc. VAT P&P)




Full details on request * Add 15% VAT unless included Cheques or P.O.s or telephone Card No. to

VIDEOTIME PRODUCTS, 56 QUEENS RD. BASINGSTOKE, HANTS RG12 1REA. Tel: (0256) 56417 TLX: 858747

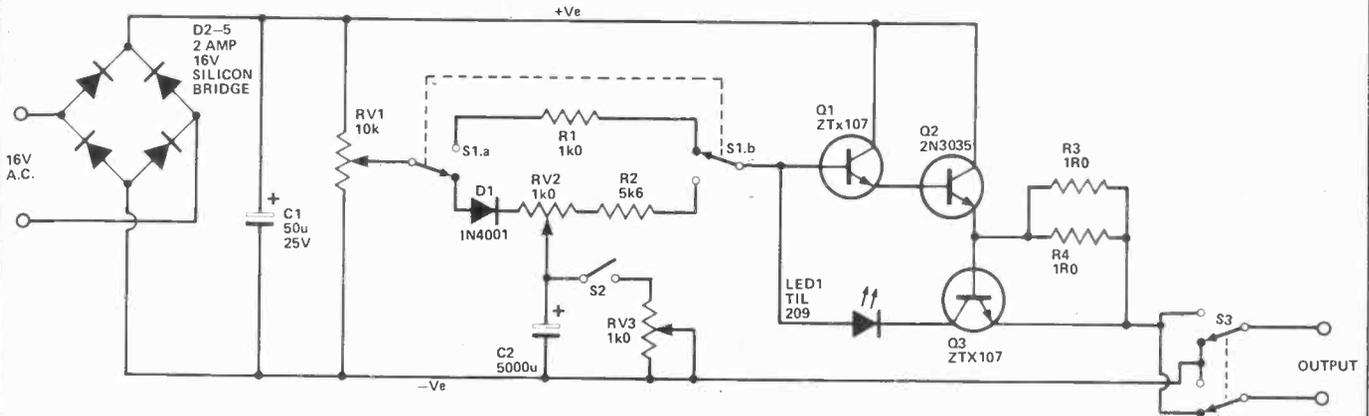FACTORY AGENTS WANTED MONEY BACK GUARANTEE. OFFERS SUBJECT TO AVAILABILITY TRADE ENQUIRIES WELCOME






Train Controller with Inertia and Brake

M. Bright

D2-5 full wave rectifies the AC and C1 smooths the output. RV1 acts as a regulator controlling train speed.

Switch S1 switches in the inertia simulator (comprising D1, RV1, R2 and C2). S2 switches in the brake, the action of which is altered by RV3. RV2 controls the amount of inertia, so that the train can take as long as ten seconds before even moving. Q1,2 act as a Darlington pair, supplying current to the output. Q3 monitors the

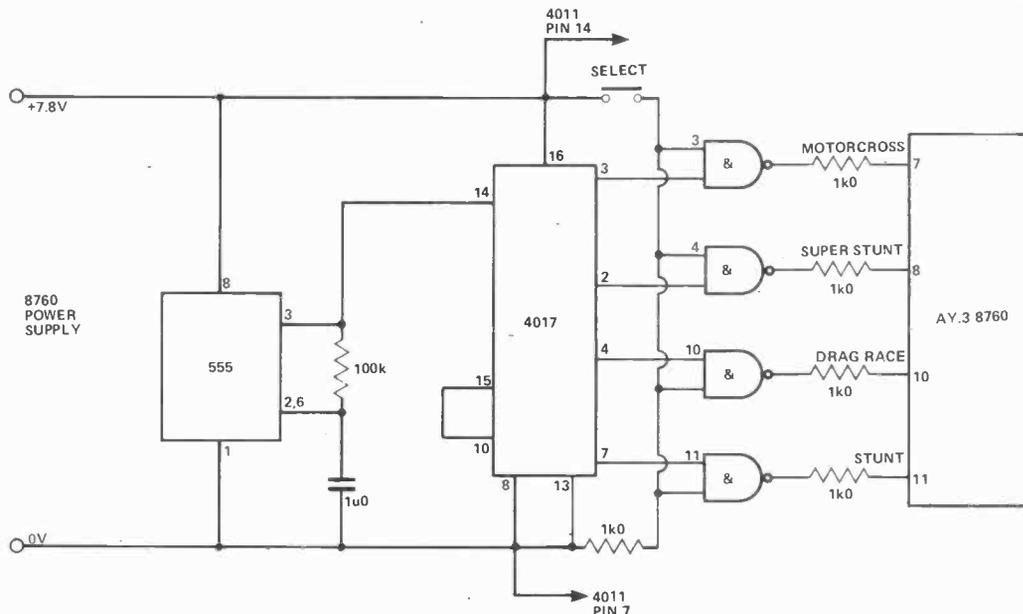output and provides short-circuit protection. When a short occurs, D2 lights up and the current into Q1 is reduced. Hence, the output is reduced. Two 1W resistors are used for R3,4 rather than a wirewound 1/2W resistor, which would cost more. S3 simply reverses the polarity and hence the train.



Auto Select for AY 3-8760 Stunt Cycle

S. D. Lang

Constructors of the Stunt Cycle TV game may wish to economise on switches and panel space by trying this circuit for game selection. Originally, game selection was by grounding the relevant game select pins. This requires four push switches; extravagant on switches

and panel space. In this circuit, three of those switches are made redundant in a novel game selection method. The only switch required is a push switch now entitled 'game select'. Upon depression of this switch, all four games are displayed upon the screen, one a time. When the playfield of the required game is displayed, the game select switch is released and play continues.

The circuit works from the power supply of the AY 3-8760. Circuit operation is straightforward, as follows: The 555 and associated com-


ponents form a pulse generator of period approx. 1 second. This pulse is applied to the input of the 4017 decade counter. Every pulse received advances the high output by one, so the high pin is 3,2,4,7 in that order. When pin 10 becomes high, the reset circuitry is operated. If the select switch is open, the output of all the NAND gates is high, so the game is played. When the select switch is closed, the selection circuitry may now operate, and the outputs of the NAND gates go low in turn, selecting the appropriate game.

POWERTRAN COMPUTERS
 (a division of POWERTRAN ELECTRONICS)
 PORTWAY INDUSTRIAL ESTATE
 ANDOVER HANTS SP10 3NM
 ANDOVER
 (0264) 64455

UK Carriage FREE

Value Added Tax not included in prices
PRICE STABILITY: Order with confidence. Irrespective of any price changes we will honour all prices in this advertisement until September 30th, 1979. If this month's advertisement is mentioned with your order. Errors and VAT rate changes excluded.
EXPORT ORDERS: No VAT. Postage charged at actual cost plus 50p handling and documentation.
U.K. ORDERS: Subsequent to 8% surcharge for VAT. No charge is made for carriage. Or current rate if changed.
SECURICOR DELIVERY: For this optional service (U.K. mainland only) add £2.50 (VAT inclusive) per kit.

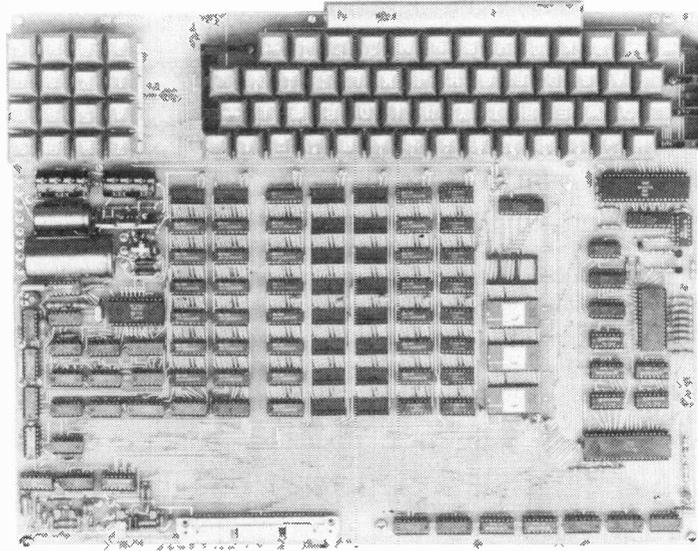SYSTEM EXPANSION COMING SHORTLY!
 e.g.
 8K RAM Board
 8K ROM Board
 From Programmer
 Printer Interface
 etc.
 etc.



PCB size 16.0" x 12.5"


Kit also available as separate packs: e.g. PCB, Keyboards, Cabinet, etc.

The kit for this outstandingly practical design by John Adams being published in a series of articles in Wireless World really is complete! Included in the PSI COMP 80 scientific computer kit is a professionally finished cabinet, fibre-glass double sided, plated-through-hole printed circuit board, 2K keyboards PCB mounted for ease of construction, IC sockets, high reliability metal oxide resistors, power supply using custom designed toroidal transformer, 2K Basic and 1K monitor in EPROMS and, of course, wire, nuts, bolts, etc.

PSI Comp 80, Z80 Based powerful scientific computer
 Design being published in Wireless World — NOW!

POWERTRAN

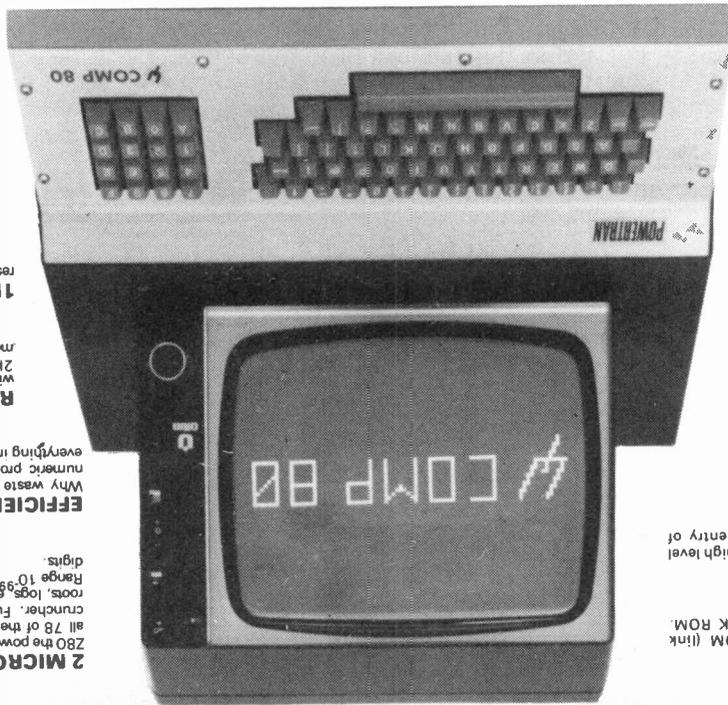
Cabinet size 19.0" X 15.7" X 3.3". Television by courtesy of Fumblewells Ltd., price £58.62



COMPLETE KIT

8K ON BOARD MEMORY!
 5K RAM, 3K ROM or 4K RAM, 4K ROM (link selectable). Kit supplied with 3K RAM, 3K ROM.
2 KEYBOARDS!
 56 key alphanumeric keyboard for entering high level of language plus 16 key Hex pad for easy entry of machine code.
GRAPHICS!
 64 character graphics option — includes transistor symbols! Only £18.20 extra!
MEMORY MAPPED
 high resolution VDU circuitry using discrete TTL for extra flexibility. Has its own 2K memory to give 32 lines for 64 characters.
KANSAS CITY
 Low error rate tape interface.

2 MICROPROCESSORS
 Z80 the powerful CPU with 158 instruction, including all 78 of the 8080, controls the MM57109 number cruncher. Functions include +, -, *, /, squares, roots, logs, exponentials, trig functions, inverses etc. Range 10⁻⁹⁹ to 9 x 19⁹⁹ to 8 figures plus 2 exponent digits.
EFFICIENT OPERATION
 Why waste valuable memory on sub routines for numeric processing? The number cruncher handles everything internally!
RESIDENT BASIC
 with extended mathematical capability. Only 2K memory used but more powerful than most 8K Basics!
1K MONITOR
 resident in EPROM.
SINGLE BOARD DESIGN
 Even keyboards and power supply circuitry on the superb quality double sided plated through-hole PCB.
ONLY £275.00 +VAT

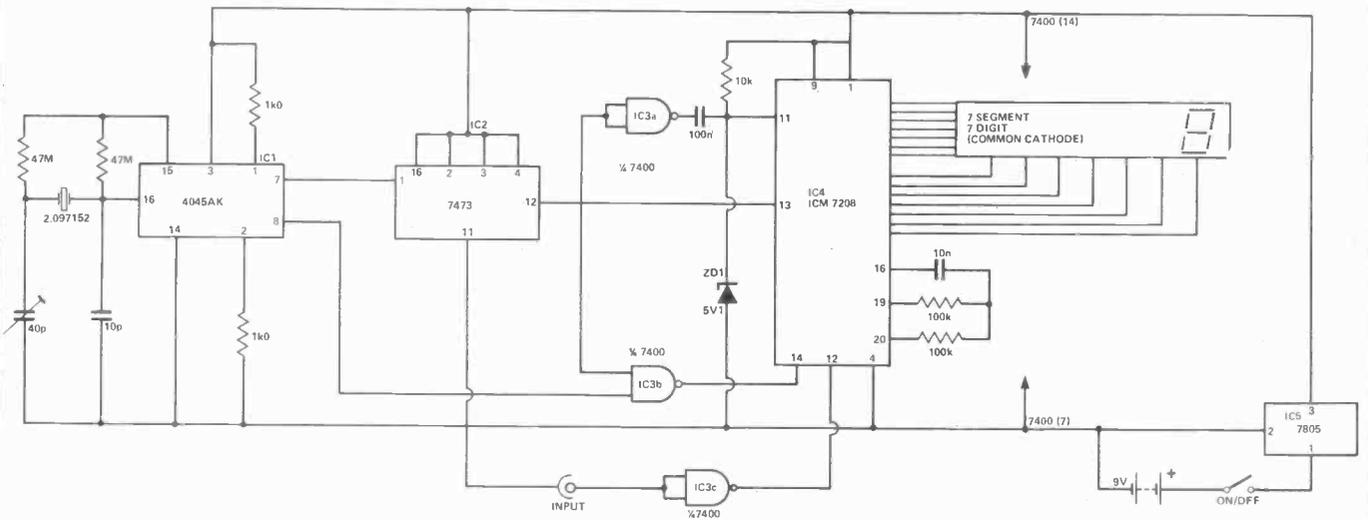


A Pocket Digital Frequency Meter

S. J. Barlow

The circuit uses only five ICs and 13 passive components. It is designed to fit into the casing of a pocket calculator and makes use of the calculator's seven segment display.

It has a single range measuring up to 10 MHz. The display is updated with new reading every two seconds. The preceding frequency count is held in the display during this period, thus avoiding a flashing display during the sampling interval.

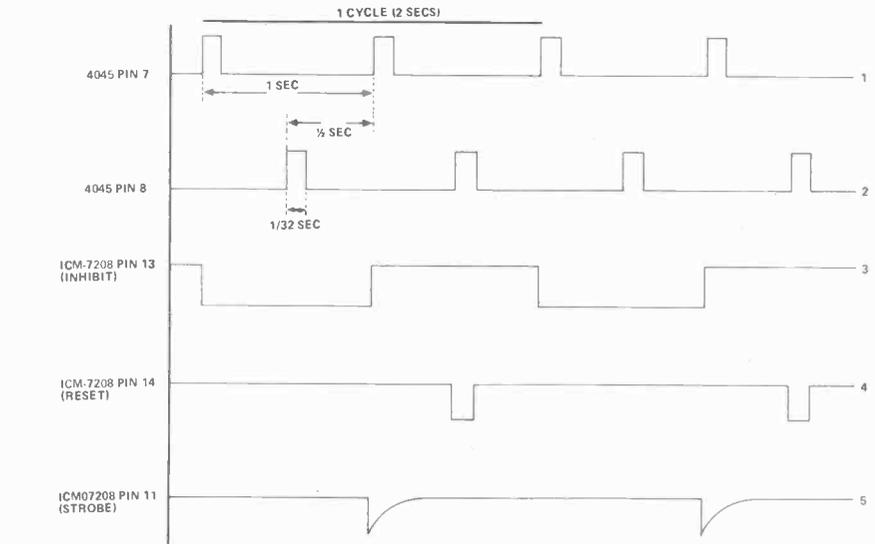The 7805 provides the 5V supply for the logic. The 4045 and the crystal form an oscillator and 21 stage binary counter producing 1/32 second pulses at 1 sec intervals as shown in waveforms 1 and 2. The 7473 flip-flop produces the one second gating




pulse (waveform 3). Waveforms 2 and 3 are NANDed into pin 14 of the ICM 7208s counter chip to produce the RESET signal. Waveform 3 is also inverted before driving a differentiator

with a 5V1 zener diode providing a clamp and discharge path. The differentiated waveform (5) gates the new frequency reading into the display.

Seat Belt Indicator for Vehicles

S. Winder

As a reminder to put the seat belt on, a small opaque panel with the inscription "SEAT BELT" can be fitted to the dashboard with a lamp behind, which lights up for ten seconds after the ignition has been turned on. The new VMOS power FET can be used in a very simple circuit to achieve this. The current between source and drain is dependent upon the gate/source voltage. When the ignition key is turned the +12 volt supply is initially dropped across R2, since the voltage

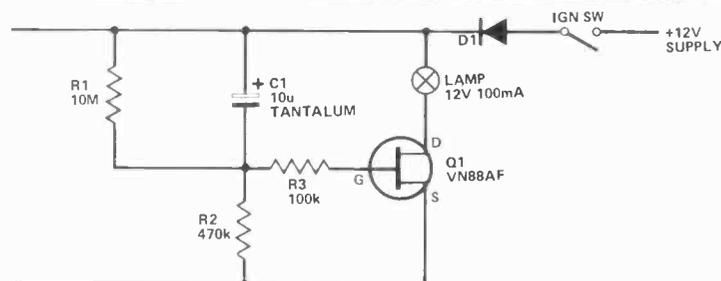

across a capacitor cannot change instantaneously (C1 is discharged by R1 when the supply is removed). As the capacitor charges up the gate potential of Q1 drops and the lamp extinguishes. The current drawn by

the circuit falls to about 50 uA after a minute. The gate resistor R3 is provided to protect the zener diode which is between gate and source of Q1, the input resistance of Q1 is too high to be affected by this resistance normally.



Largest range of quality components in the U.K. — over 8,000 types stocked

Marshall's

Head Office and Mail Order to Dept. ET1
A. Marshall (London) Ltd.
Kingsgate House, Kingsgate Place
London NW6 4TK. Tel: 01-624 8055
Telex 21492

Retail Sales: London: 40 Cricklewood Broadway, NW2 3ET. Tel: 01-452 0161/2. Also 325 Edgware Road, W2. Tel: 01-723 4242.
Glasgow: 85 West Regent Street, G2 2QD. Tel: 041-332 4133. And Bristol: 108A Stokes Croft, Bristol. Tel: 0272 426801/2

ZENER DIODES (full range in cat.)

400W	6Z85	1 WATT	2.5 WATT	8Z170	C110	C120
C2.4	.11	1M4728A 3.3	.23	C1V5	.67	C10
C2.7	.11	1M4729A 3.6	.23	C2V2	.67	C10
C3.0	.11	1M4730A 3.9	.23	C2V1	.67	C10
C3.3	.11	1M4731A 4.2	.23	C10	.67	C10
C3.6	.11	1M4732A 4.7	.23	C12	.67	C10
C3.9	.11	1M4733A 5.1	.23	C11	.67	C10
C4.3	.11	1M4734A 5.6	.23	C13	.67	C10
C4.7	.11	1M4735A 6.2	.23	C15	.67	C200
C5.1	.11	1M4736A 6.8	.23	C16	.67	
C5.6	.11	1M4754A 39	.25	5 WATT	8ZV40	20 WATT
C5.1	.11	1M4755A 43	.25	C10	.83	C10
C5.6	.11	1M4756A 47	.25	C11	.83	C11
C6.1	.11	1M4757A 51	.25	C12	.83	C11
C6.7	.11	1M4758A 54	.25	C14	.83	C11
C7.1	.11	1M4759A 62	.25	C14	.83	C15
C7.6	.11	1M4760A 68	.25	C15	.83	C16
C8.1	.11	1M4761A 75	.25	C16	.83	C18
C8.7	.11	1M4762A 82	.25	C17	.83	C20
C9.1	.11	1M4763A 91	.25	C18	.83	C22

NEW LOW PRICE "KIM" The Ready to use Microprocessor System

Not a kit but supplied fully tested, wired and guaranteed. Expandable Memory that grows with your system not just an evaluation kit. Starting with KIM 1 at £107.95 VAT inclusive. You get immediate capability which can be expanded to a complete system capable of addressing up to 65K BYTES of Memory. KIM IS EXPANDABLE. Expand as you learn up to 65K.

KIM 1 Basic board with above features assembled **£107.95**
KIM 3 BK static RAM card plus into motherboard **£40.35**
KIM 4 Motherboard (takes 6 KIM 3) + power supply **£76.55**

TTL (See Catalogue for full range)


74LS242N	E1.25	SN74242N	E0.77	SN74242N	E0.22	74LS00N	E0.26
74LS243N	E1.25	SN74243N	E0.77	SN74243N	E0.22	74LS01N	E0.26
74LS244N	E1.50	SN74244N	E0.77	SN74244N	E0.22	74LS02N	E0.26
74LS245N	E1.65	SN74245N	E0.77	SN74245N	E0.22	74LS03N	E0.26
74LS247N	E1.09	SN74247N	E1.00	SN74247N	E0.22	74LS04N	E0.29
74LS248N	E1.09	SN74248N	E1.00	SN74248N	E0.22	74LS05N	E0.29
74LS249N	E1.09	SN74249N	E1.00	SN74249N	E0.22	74LS08N	E0.26
74LS251N	E1.00	SN74251N	E0.95	SN74251N	E0.24	74LS09N	E0.26
74LS252N	E1.00	SN74252N	E0.95	SN74252N	E0.24	74LS10N	E0.26
74LS257B	E1.00	SN74257B	E1.00	SN74257B	E0.18	74LS11N	E0.26
74LS258N	E1.00	SN74258N	E0.95	SN74258N	E0.59	74LS12N	E0.26
74LS259N	E1.35	SN74259N	E1.30	SN74259N	E0.45	74LS13N	E0.26
74LS261N	E3.25	SN74261N	E2.50	SN74261N	E0.75	74LS14N	E0.75
74LS265N	E0.44	SN74265N	E1.25	SN74265N	E0.60	74LS20N	E0.26
74LS270N	E1.00	SN74270N	E0.95	SN74270N	E0.22	74LS20N	E0.26
74LS275N	E3.20	SN74275N	E1.00	SN74275N	E0.60	74LS21N	E0.26
74LS279N	E0.58	SN74279N	E0.86	SN74279N	E0.22	74LS22N	E0.26
74LS280N	E1.65	SN74280N	E1.70	SN74280N	E0.22	74LS26N	E0.32
74LS283N	E1.20	SN74283N	E0.85	SN74283N	E0.20	74LS27N	E0.32
74LS289N	E3.74	SN74289N	E3.06	SN74289N	E0.20	74LS28N	E0.26
74LS290N	E1.00	SN74290N	E0.95	SN74290N	E0.22	74LS29N	E0.26
74LS293N	E1.00	SN74293N	E1.00	SN74293N	E0.39	74LS32N	E0.27
74LS295N	E1.35	SN74295N	E1.34	SN74295N	E0.30	74LS33N	E0.27
74LS298N	E1.35	SN74298N	E1.34	SN74298N	E0.36	74LS33N	E0.29
74LS299N	E2.95	SN74299N	E1.48	SN74299N	E0.26	74LS37N	E0.32
74LS323N	E3.50	SN74323N	E1.17	SN74323N	E0.60	74LS38N	E0.32
74LS324N	E1.65	SN74324N	E1.17	SN74324N	E0.45	74LS40N	E0.26
74LS325N	E2.40	SN74325N	E0.17	SN74325N	E0.80	74LS42N	E0.00
74LS326N	E2.70	SN74326N	E0.17	SN74326N	E1.00	74LS47N	E1.09
74LS327N	E2.55	SN74327N	E0.15	SN74327N	E0.80	74LS48N	E1.09
74LS340N	E1.10	SN74340N	E0.22	SN74340N	E1.05	74LS49N	E1.00
74LS352N	E1.07	SN74352N	E0.39	SN74352N	E1.20	74LS51N	E0.26
74LS353N	E1.07	SN74353N	E0.39	SN74353N	E0.80	74LS54N	E0.26
74LS355N	E0.95	SN74355N	E0.22	SN74355N	E0.26	74LS55N	E0.26
74LS366N	E0.55	SN74366N	E0.22	SN74366N	E1.90	74LS63N	E1.26
74LS371N	E0.55	SN74371N	E0.22	SN74371N	E0.60	74LS73N	E0.42
74LS368N	E0.55	SN74368N	E0.20	SN74368N	E0.55	74LS74N	E0.42
74LS373N	E0.85	SN74373N	E0.20	SN74373N	E0.35	74LS75N	E0.50
74LS374N	E0.85	SN74374N	E0.36	SN74374N	E0.55	74LS76N	E0.42
74LS375N	E0.85	SN74375N	E0.20	SN74375N	E0.45	74LS78N	E0.42
74LS377N	E1.00	SN74377N	E0.25	SN74377N	E0.55	74LS83AN	E0.90
74LS378N	E1.00	SN74378N	E0.25	SN74378N	E0.55	74LS85N	E0.96
74LS379N	E1.25	SN74379N	E1.50	SN74379N	E0.55	74LS86N	E0.44
74LS386N	E0.44	SN74386N	E1.50	SN74386N	E0.55	74LS90N	E0.84
74LS390N	E0.90	SN74390N	E1.70	SN74390N	E0.55	74LS91N	E0.70
74LS393N	E0.90	SN74393N	E2.10	SN74393N	E0.55	74LS92N	E0.80
74LS395N	E1.50	SN74395N	E2.80	SN74395N	E0.55	74LS93N	E0.84
74LS398N	E1.90	SN74398N	E2.80	SN74398N	E0.55	74LS95AN	E0.80
74LS399N	E1.45	SN74399N	E0.90	SN74399N	E0.55	74LS96N	E1.35
74LS400N	E0.80	SN74400N	E0.90	SN74400N	E0.55	74LS107N	E0.42
74LS407N	E1.70	SN74407N	E0.90	SN74407N	E0.80	74LS109N	E0.42
SN74S00N	E0.90	SN74S00N	E1.10	SN74S00N	E3.10	74LS110N	E0.42
SN74S03N	E0.77	SN74S03N	E0.85	SN74S03N	E0.80	74LS113N	E0.42
SN74S04N	E0.94	SN74S04N	E1.25	SN74S04N	E2.62	74LS114N	E0.42
SN74S10N	E0.77	SN74S10N	E1.25	SN74S10N	E2.30	74LS122N	E0.62

TRANSISTORS (for full range see catalogue)

2K241D	1.40	2K2904A	.31	2K1313	5.00	40360	55	40458A	.70	8C231	.19	8D422C	.82	8F117	.27	8F246B	.82	8S161	.53	ME1100	.22
2K241E	1.00	2K2905A	.31	2K1314	8.00	40361	55	40459A	.80	8C232	.19	8D423A	.85	8F178	.27	8F247A	.80	8S176	.60	ME1120	.27
2K242	1.00	2K2906A	.31	2K1315	9.72	40362	55	40451A	1.60	8C237	.20	8D423C	.87	8F179	.33	8F248A	.80	8S177	.60	ME3002	.27
2K247	1.10	2K2906	.25	2K1316	91	40363	1.45	40537	6.60	8C328	.20	8D424A	.70	8F180	.37	8F249A	.26	8S110	1.10	ME4001	.16
2K248A	.30	2K2906A	.25	2K1317	1.50	40364	1.45	40538	1.50	8C337	.20	8D424C	.87	8F181	.37	8F252A	.26	8S124	.52	ME4002	.16
2K248B	.30	2K2907A	.25	2K1318	6.00	40372	1.15	40539A	5.00	8C338	.20	8D425A	.89	8F182	.37	8F257	.35	8S125	.85	ME4003	.16
2K249	2.40	2K2907A	.25	2K1319	33	40374	1.85	40541	1.18	8C350	.11	8D246A	.72	8F184	.41	8F258	.35	8S126	.55	ME4004	.16
2K251A	0.90	2K2920	3.30	2K1320	.99	40379	1.85	40542A/B	.29	8C347	.11	8D247A	.72	8F184	.41	8F259	.35	8S127	.55	ME4005	.11
2K251B	.70	2K2923	.17	2K1321	.99	40383	1.00	8C256A/B/C	1.18	8C382	.21	8D248C	.83	8F185	.37	8F262	.66	8S128	.44	ME4003	.11
2K251C	0.90	2K2924	.17	2K1322	4.05	40390	1.05	8C259A/B	1.19	8C382L	.21	8D249A	2.40	8F184	.41	8F263	.75	8S129	1.10	ME4004	.11
2K251D	.70	2K2925	.19	2K1323	4.5	40391	9.00	8C260	1.17	8C383	.19	8D249C	3.00	8F185	.41	8F264	.85	8S130	.33	ME6001	.16
2K256	1.70	2K2926	.17	2K1324	.39	40392	7.00	8C261A/B	2.5	8C383L	.19	8D250A	2.75	8F186	.41	8F265	.85	8S131	.33	ME6002	.16
2K257	1.55	2K2927A	.17	2K1325	1.35	40394	9.00	8C262A/B/C	2.6	8C384	.21	8D250C	3.00	8F187	.44	8F266	.85	8S131	.33	ME6003	.16
2K258	2.20	2K2928	.25	2K1326	.50	40395	1.45	8C263A/B/C	2.6	8C384L	.21	8D433	.44	8F188	.44	8F268	.35	8S132	.33	ME6004	.16
2K271	.30	2K3012	.37	2K1327	.65	40396	1.45	8C264	2.6	8C407	.27	8D434	.46	8F189	.44	8F269	1.85	8S133	.33	ME6005	.11
2K2712	.18	2K3013	.37	2K1328	.34	40406	7.00	8C265A/B	3.4	8C408	.27	8D435	.46	8F190	.44	8F270	.38	8S134	.36	ME8001	.22
2K2713	.25	2K3015	.47	2K1329	.43	40407	57	8C300	4.3	8C408L	.27	8D436	.46	8F191	.44	8F271	.85	8S135	.36	ME8002	.22
2K2714	.22	2K3019	.55	2K1330	.43	40408	82	8C301	4.3	8C409	.27	8D437	.46	8F192	.44	8F272	1.65	8S136	1.00	ME8003	.22
2K284B	1.10	2K3025	.75	2K1334	.82	40409	82	8C302	4.7	8C409L	.27	8D438	.46	8F193	.44	8F273	.85	8S137	1.42	ME9001	.22
2K285	2.20	2K3025	.75	2K1335	.54	40410	82	8C303	4.7	8C410	.27	8D439	.46	8F194	.44	8F274	.85	8S138	1.42	ME9002	.22
2K289	2.50	2K3054	.72	2K1336	.19	40411	3.10														

Simply ahead!

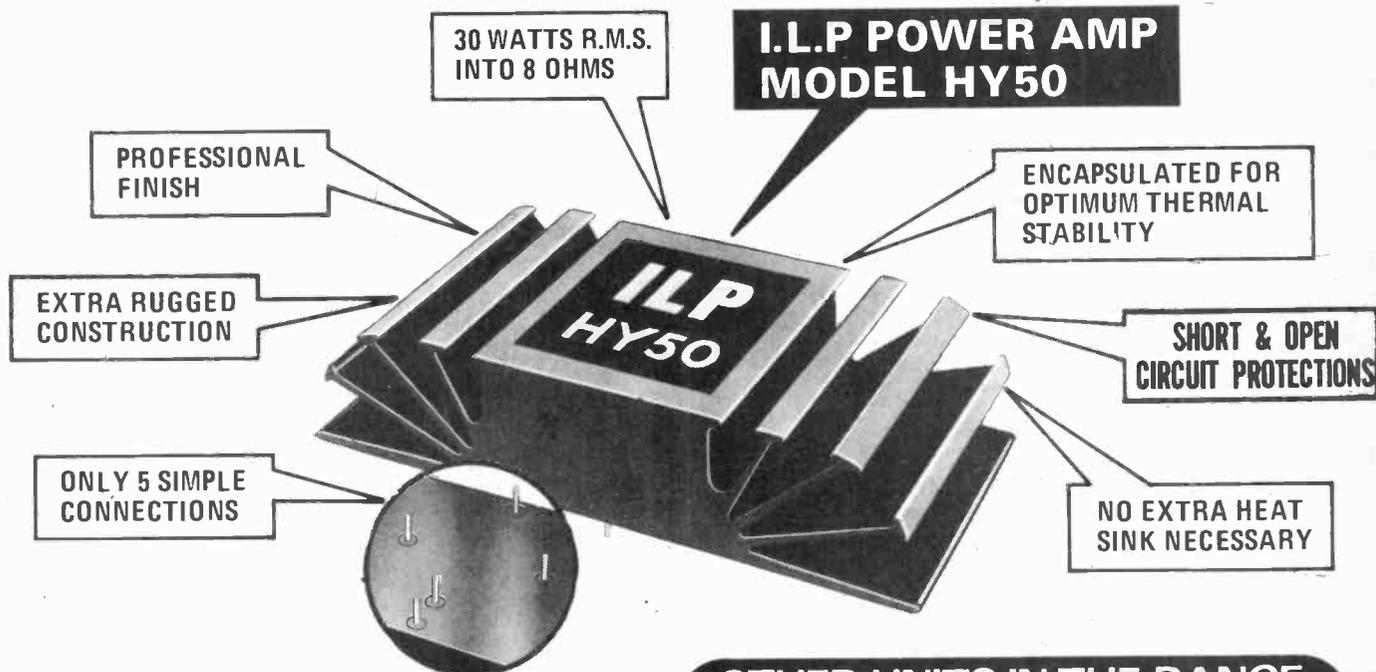HIGH PERFORMANCE MODULAR UNITS BACKED BY NO-QUIBBLE 5 YEAR GUARANTEE



Of all the purpose-built power amplifier modules by I.L.P., the HY50 is understandably the most popular with those wanting to build new or up-grade an existing hi-fi system, run a small high quality P.A. system, amplify a musical instrument (say for practice or small range use) or use it for lab work. Its useful 30 watts RMS output into 8 ohms, its rugged construction and freedom from heatsink worries make it the ideal all-purpose quality power amp — and it is unconditionally guaranteed for five years! Tens of thousands are in regular use throughout the world.

... and a spec that means just what it says!

Encapsulated power amp with integral full-rated heatsink.
Input — 500mV.
Output 30 watts RMS/ 8Ω.
Load Impedance — 4 to 16Ω.

S/N Ratio 75dB
Distortion — 0.02% from 100mW to 25 watts at 1KHz into 8Ω.
Supply Voltage ± 25V. Size 105 x 50 x 25mm.

Inc. VAT and postage in U.K.

£8.33

Nothing has been overlooked in the design and manufacture of I.L.P. Modular Units. Heavy duty heatsinks, encapsulated circuitry, no-compromise production standards and true professional finish ensure world leadership in their field for I.L.P. Now we have *up-graded* output ratings and *down-graded* prices to bring I.L.P. within easier reach of all who want the best with which to build with. Prices reduced by an average around 20%.


Guaranteed 7-day despatch on all products

FREE POST — No stamp required when sending your order or enquiry for information sheets.



FREEPOST 4, Graham Bell House, Roper Close, CANTERBURY
Kent CT2 7EP. Phone (0227) 54778. Telex: 965780

OTHER UNITS IN THE RANGE

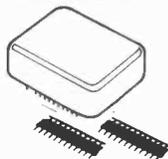


All prices inc. VAT at 15% and postage in the U.K.

HY5 PRE-AMPLIFIER

Compatible with all I.L.P. power amps and P.S.U.s. In a single pack, needs external pots and switches. Multi-function equalization. Mag./Ceramic/Tuner/Mic./Aux. inputs. High overload margin. Active tone controls; 500 mV out. Distortion at 1 KHz — 0.01%. Two HY5s connect easily for stereo.


£5.34

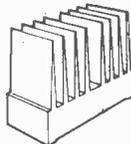

THE POWER AMPS

With heatsinks, full load line and thermal protection.
Distortion typically 0.05% at 1 KHz.

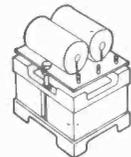HY120 60 Watts RMS/8Ω 114 x 50 x 85mm **£17.48**
HY200 120 Watts RMS/8Ω 114 x 50 x 85mm **£21.21**
HY400 240 Watts RMS/4Ω 114 x 100 x 85mm **£31.83**



THE POWER SUPPLY UNITS

(Split line outputs to suit I.L.P. power units and HY5).

PSU 50 for 1 or 2 x HY50 **£9.32**
PSU 70 for 1 or 2 x HY120 **£15.65**
PSU 90 for one HY200 **£15.65**
PSU180 for one HY400 or 2 x HY200 **£26.47**

★ **NOW-PRICES DOWN BY 20%**

Please supply

Total Purchase Price

I enclose Cheque Postal Orders Money Order

Please debit my Access/Barclaycard Account number.

Name and address

Signature

F.P. 48

NEW

PROMBOX 12 UV PROM ERASER



£63.89

includes P&P
Add £9.58 VAT @ 15%
Ex-stock

FEATURES:

- SIMPLE OPERATION
- ERASE TIME VARIABLE FROM 5 TO 50 MINUTES.
- SLIDING TRAY CAN ACCOMMODATE UP TO 12 UV EPROMS.
- SAFETY INTERLOCK PREVENTS ACCIDENTAL EXPOSURE.

Send cheques / official orders to:

GP INDUSTRIAL ELECTRONICS LTD.

SKARDON WORKS, SKARDON PLACE, NORTH HILL
PLYMOUTH PL4 8EZ. TEL. 0752 28627

Here's why you should buy an I.C.E. instead of just any multimeter

- * Best Value for money.
- * Used by professional engineers, D.I.Y. enthusiasts, hobbyists, service engineers.
- * World-wide proven reliability.
- * Low servicing costs.
- * 20K/volt sensitivity and high accuracy.
- * Large mirror scale meter.
- * Fully protected against overload.
- * Large range of inexpensive accessories.
- * 12 month warranty, backed by a full after sales service at E.B. Sole U.K. Distributors.


Prices from £16.60 —
£32.00 + VAT



I.C.E

ELECTROVALUE

Your leading direct suppliers for

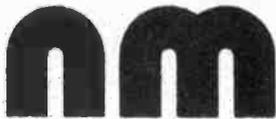

**NASCOM
MICROCOMPUTERS
AND FULL SUPPORTING
RANGE
OF ITEMS TO ENABLE YOU TO
WORK AT PROPER
PROFESSIONAL LEVELS**

- ★ At newest reduced prices.
- ★ Widest possible range stocked.
- ★ Information on request.
- ★ Enquiries from trade, industrial and educational users invited.

**Appointed distributors for the
fine products of:**

**SIEMENS, ISKRA, RADIOHM,
ORYX AND MANY OTHER
FAMOUS MANUFACTURERS**

It's a good deal better from

ELECTROVALUE LTD

Dept. ET8, 28 St. Judes Road, Englefield Green, Egham, Surrey TW20
0HB

Phone: Egham 3603. Telex 264475.
Northern Branch (Personal shoppers only), 680 Burnage Lane, Burnage,
Manchester M19 1NA. Phone (061) 432 4945.

● We pay postage in U.K. on orders list value £5 or over. If under, add 27p handling charge.

● We give discounts on C.W.O. orders, except items marked Net or N in our catalogues.

5% on orders, list value £10 or more.

10% on orders list value £25 or more.

Not on Access or Barclay orders

● We stabilise prices.

by keeping to our printed price lists which appear but three or four times a year.

● We guarantee all products brand new, clean and to maker's spec. No seconds, no surplus.

● WE WILL SEND YOU OUR 120-PAGE CATALOGUE No. 9 FREE ON REQUEST. Comprehensive, informative, very well produced. Write, phone, or call for your free copy, together with latest price list.

ELECTRONIC BROKERS LIMITED
49-53 Pancras Road, London NW1 2QB.
Tel: 01-837 7781. Telex: 298694.

Please send me full colour leaflet and prices on whole ICE range including accessories.

Name

Address

ET 8

ELECTRONICS TODAY INTERNATIONAL — AUGUST 1979


PLEASE SEE V.A.T. ADVERTISEMENT ON PAGE 15 BEFORE ORDERING GOODS FROM ADVERTISERS!

computing today

WHAT TO LOOK FOR IN THE
AUGUST ISSUE!
ON SALE JULY 27TH.

CT Systems Reviews

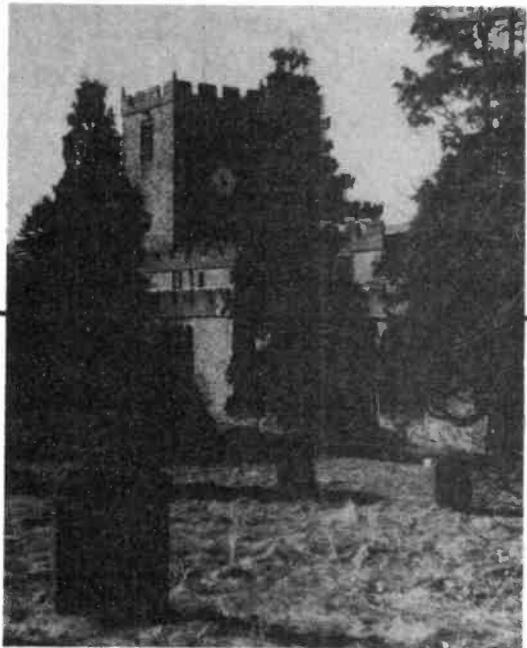We have two for you next month, the new Acorn 6502 based kit, a super MK14 (some would say) and an even newer educational and development kit called the Nanocomputer.



Ancient and Modern

One of the things that we love to hear from you about are your applications for microcomputers. In this tale from the past a PET is being used to collate old parish records. Not a bit ghoulish either!


The PET Bus

Computer busses often seem to be misunderstood, the PET's no exception. In this article we delve in and give you the facts.







Dateline 5000 AD

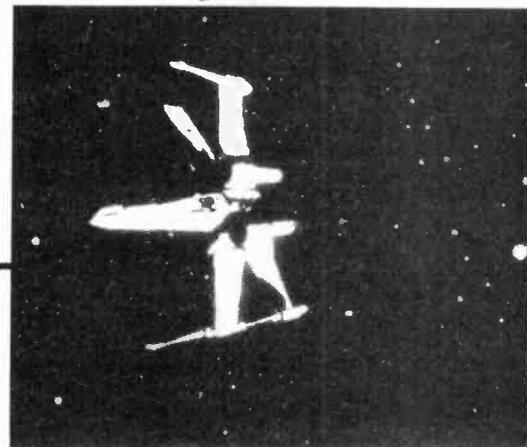
Your chance to colonise the galaxy from the comforts of the armchair. Despatch your fleets to investigate 'target' stars, determine the mineral value etc, and (of course) do battle with the baddies. Star Trek eat your heart out.




PCB FOIL PATTERNS

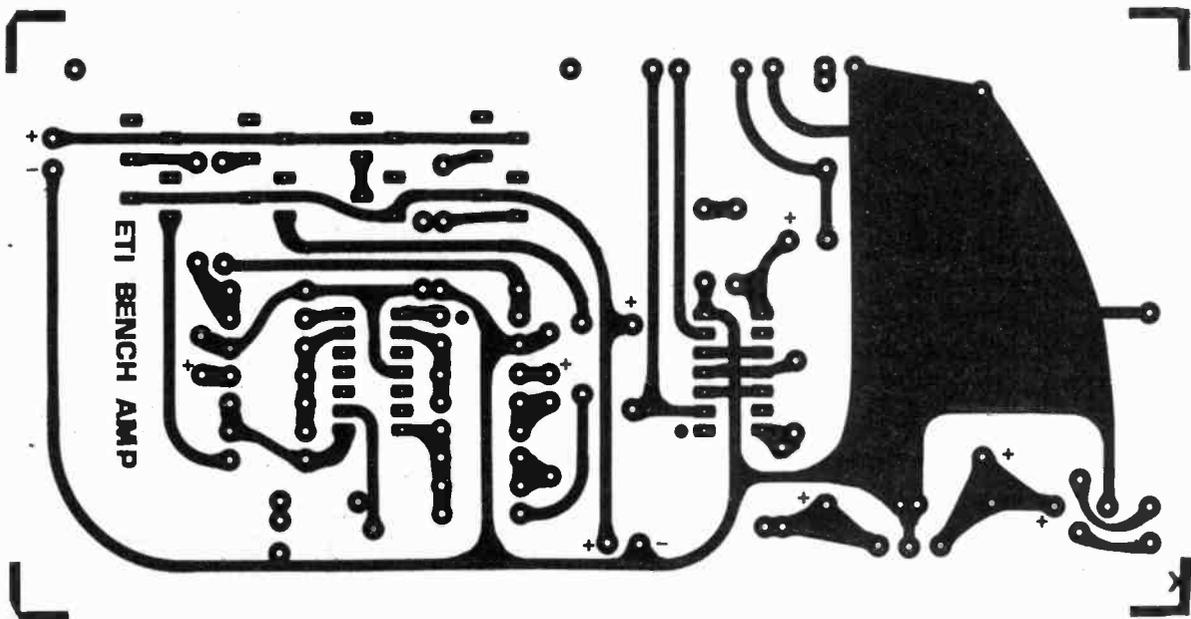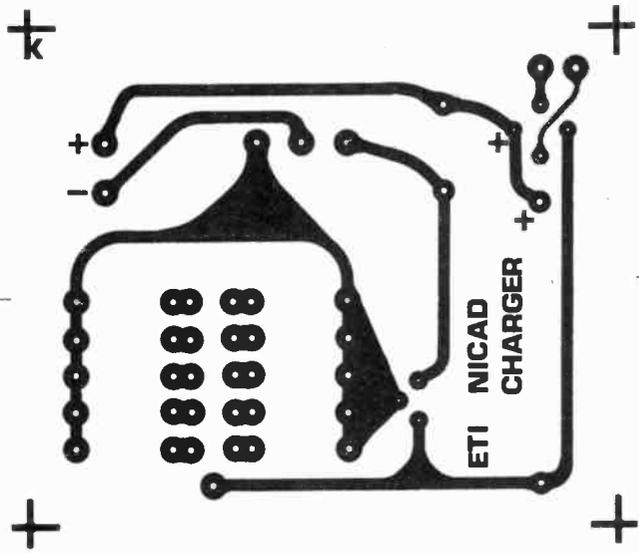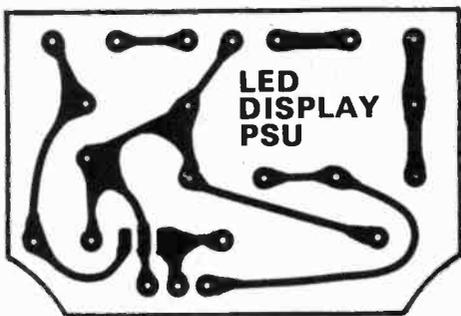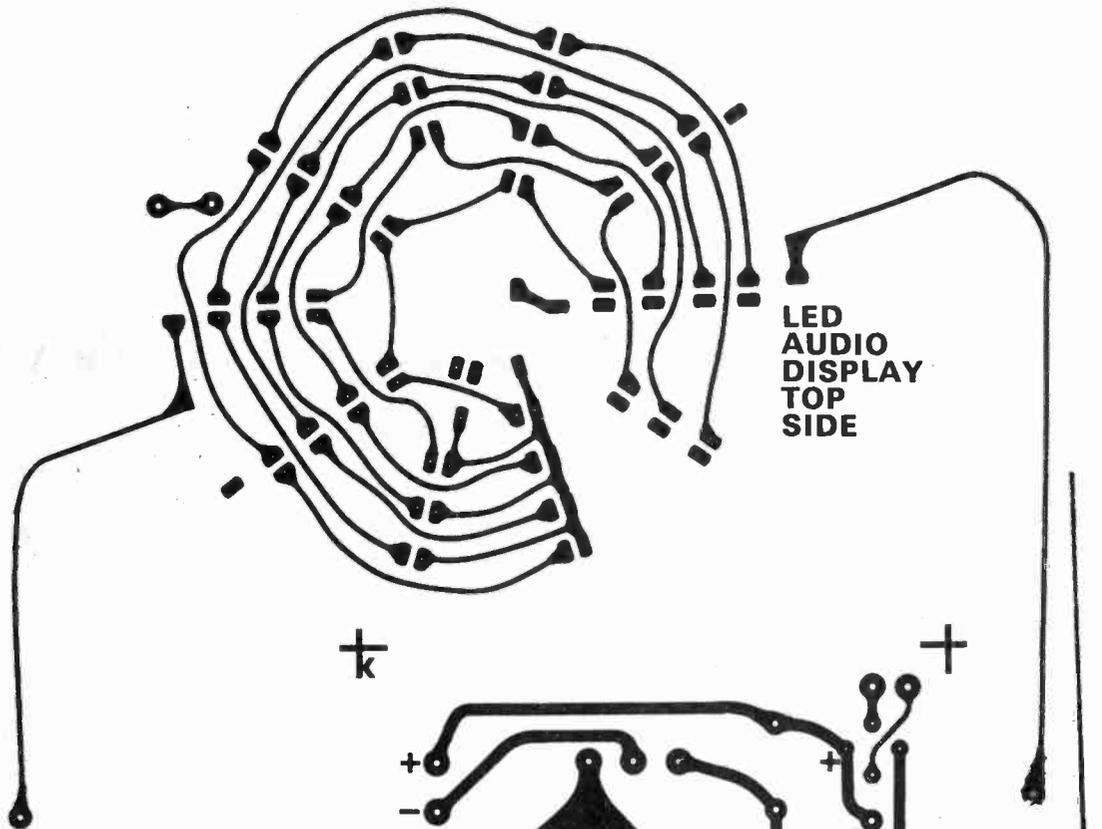This month's boards are a little strange in shape! Note the LED Display is double sided, and that both the Teletext and Transcendent are copyrighted and hence not here!



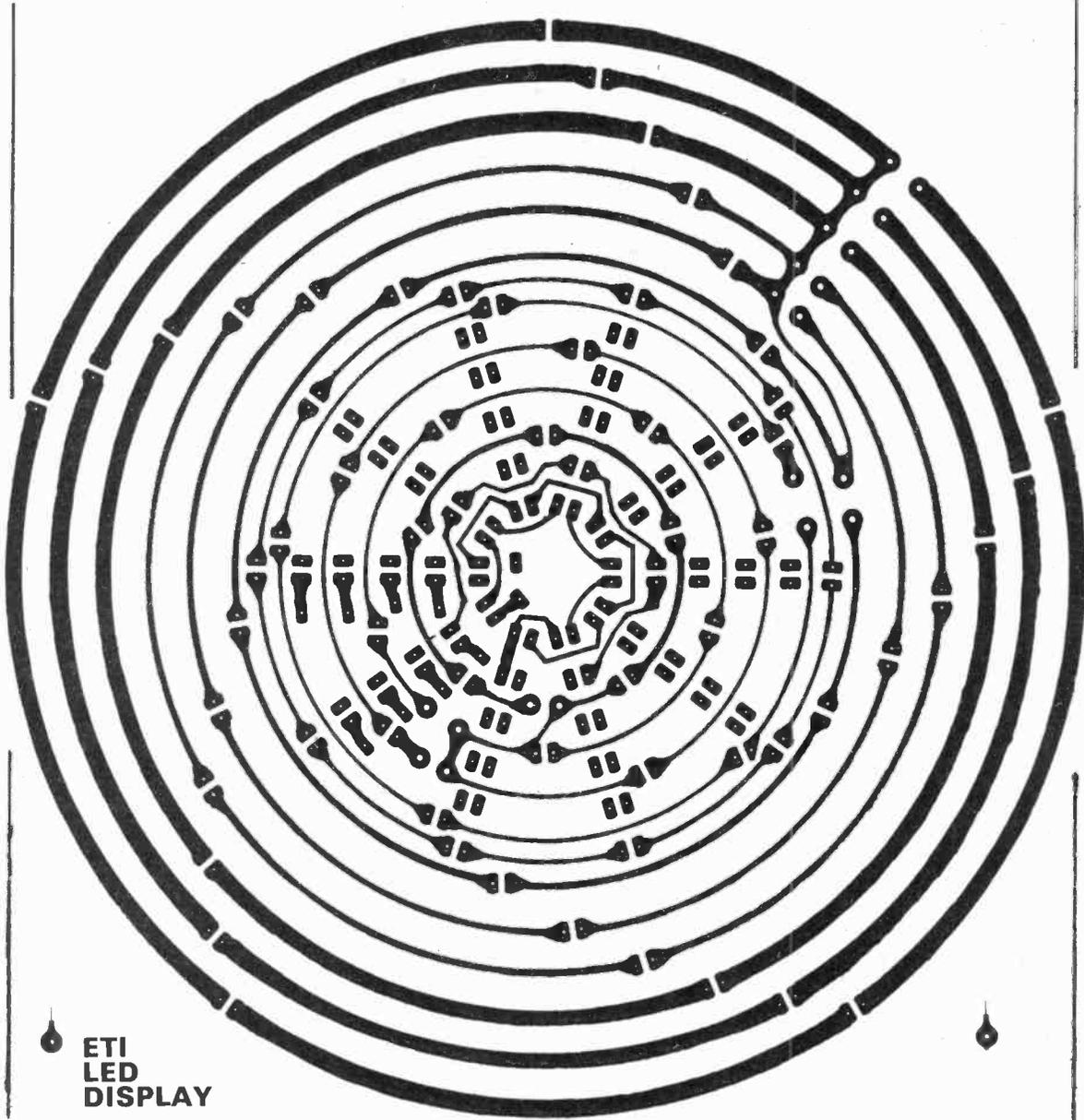

ETI
LED
DISPLAY

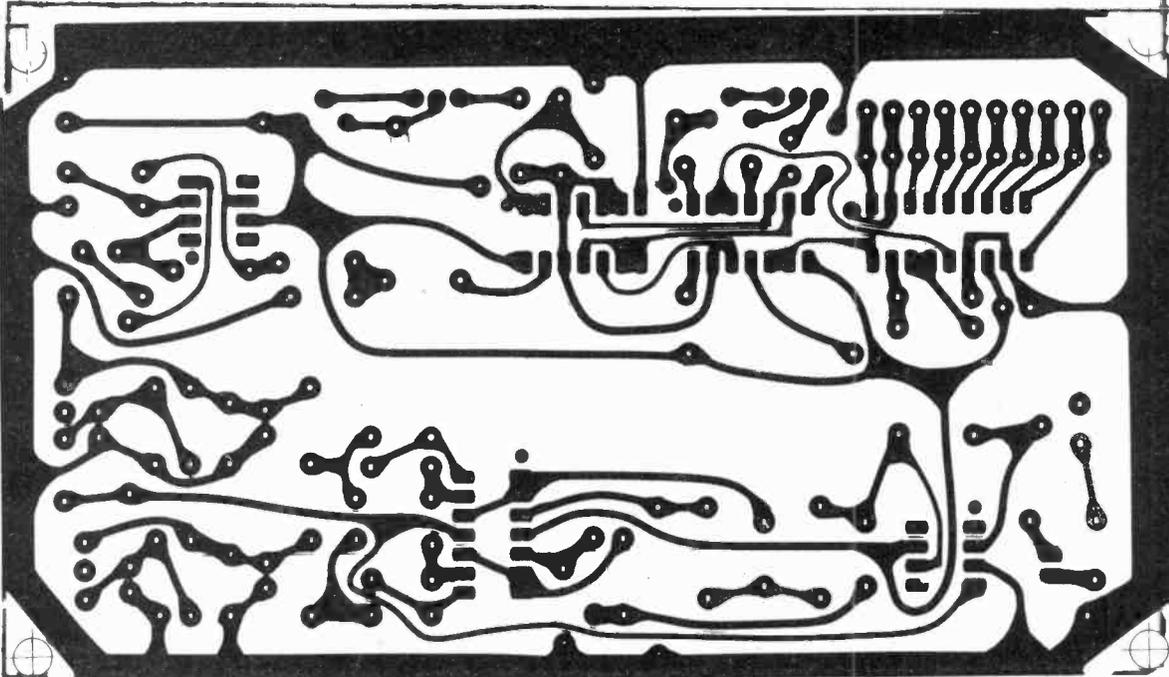

Pet Expansion



Computhink
Dual drive
minifloppy

Complete with 4K disk operating system in ROM, plugs into Expandapet memory. Adds 15 new commands to Pet's Basic to give full disk extended Basic. Loads 8K in 2.6 seconds. Automatic reorganisation of free space. Utility Disk

£833 + V.A.T.

Expandapet memory

Powered by Pet's own powersupply and mounted internally in 5-10 minutes without special tools.

16K..... **£261** + V.A.T.

24K..... **£320** + V.A.T.

32K..... **£374** + V.A.T.

All units are fully built and tested.

Apple II



Apple II was the original with full colour high resolution microcomputer Basic, and it is still the best. With a very wide range of expansion available, including disk drive, interface cards, voice recognition card, light pen and many others.

Apple II has been well tried and approved by the public (over 200,000 sold) because of its thoroughly professional design and high quality engineering. You cannot get better value for money. Please send us a large s.a.e. for further details.

With 16K user RAM only
(inc. PAL card)


£820 + V.A.T.

New 7khz 16 channel A to D board p.o.a.

Super Board II



**NEW
LOW
PRICE
!!!!**

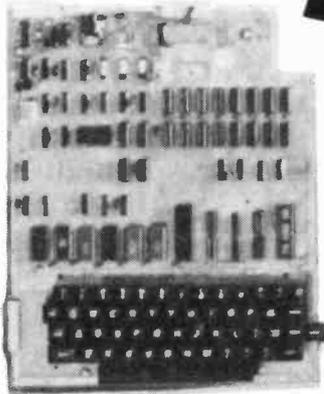

This 6502 based microcomputer comes with a full 8K Microsoft basic in ROM. Full keyboard. 4K static user RAM (on board expandable to 8K). Kansas City standard interface for use with an ordinary cassette recorder. Machine code monitor and I/O utilities in ROM. Direct Video access with 1K dedicated RAM (besides 4K user RAM) and full graphics set.

Fully built and tested only needs a 5V 3amp power supply and T.V. Monitor or R.F. modulator to be up and running.

NOW only **£229.00** + V.A.T.

Apple II & TRS80 Memory Expansion



Save Over £100

TRS 80 and Apple II memory expansion kits. Fully guaranteed and with full specification 4116 16K RAMs.

Kits come with full instructions and new jumper sets where necessary. Fitting takes 5-10 minutes, or bring along your Apple or TRS 80 and we will fit it for you for £5.


16K upgrade kit **£85** + V.A.T.

LOTUS SOUND

4 MORGAN STREET
LONDON E3 5AB

TELEPHONE: 01-981 3993
TELEX: 261426 ATN. LOTUS SOUND

MINI-ADS & CLASSIFIED

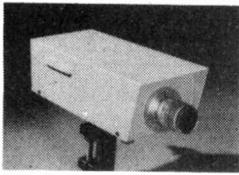

**CCTV
CAMERA**

£114.98 +P/P £3.45
Optional extra manual
£6

**BEST OFFER EVER
Camera Kit, Lens,
Vidicon & Modulator**

CROFTON

Tel: 01-891 1923 For full details

PRINTED CIRCUITS and HARDWARE

Comprehensive range Constructors Hardware and accessories

Selected range of popular components
Full range of HE printed circuit boards normally ex-stock, same day despatch at competitive prices
P.C. Boards to individual designs
Resist-coated epoxy glass laminate for the d.i.y. man with full processing instructions (no unusual chemicals required)

Alfac range of etch resist transfers, and other drawing materials for p.c. boards

Send 15p for catalogue.

**RAMAR CONSTRUCTOR
SERVICES
MASON'S ROAD
STRATFORD-ON-AVON
WARWICKS. Tel. 4879**

**VIDEO
MUSIC**



Videograph II links to the aerial socket of your tv and provides a full colour GIANT oscilloscope display. A must for hi-fi, home entertainment, discos, organs etc.

New — signal invert control, integral square wave generator. Plus — full details for testing your audio system for transient distortion, crosstalk etc.

Complete **£19.95** Luxury cabinet and Kit only **£9.95** controls. **£9.95**

READY BUILT UNIT £39.95 + £1.00 P&P

**WILLIAM
STUART
SYSTEMS Ltd**
ower House, Billerday Road
Herongate, Brentwood
Essex CM13 3SD
Telephone: Brentwood (0277) 810244


ELECTRONIC SERVICING.

Manufacturers/Distributors, we have facilities for field or bench service of a wide range of electronic equipment. If you require a service agent in the South West contact: Westbury Technical Services, 121 Barton Street, Gloucester. Telephone: 0452 76361.

TVH7 TELEVISION SOUND. For high clarity Hi-Fi listening and recording of television programmes. Supplied built and tested on a single board measuring 105x52mm, for TV internal fitment. £9.80 inclusive, with wiring and comprehensive instructions. EVE Products, 7 Adel Green, Leeds 16.

CIRCUIT DESIGN, Prototype construction, Analogue or Digital, Single Circuits or Complete Instruments/Systems. Write A. J. ATTWOOD, C.Eng., MIERE, Heathercote, Heatherton Park, Taunton, Somerset, TA4 1ET or Phone Bradford-on-Tone (082-346) 536.

ORGANISE YOUR COMPONENTS!

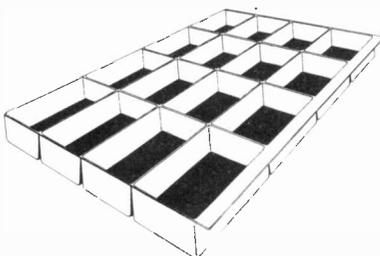


COMTRAYS

Store resistors, capacitors, IC's, screws, etc. Ideal for organising your project components — saves all that searching around while constructing. Plastic trays with 16 compartments, each compartment 3/4 x 2/4 x 1/2ins. deep.

£1.60 each, including p.p. and VAT
Four for **£5.90** (64 compartments)
Eight for **£10.90** (128 compartments)

Cheque or P.O. to:
HELISTAR SYSTEMS LTD.
150 WESTON ROAD
ASTON CLINTON
AYLESBURY, BUCKS HP22 5EP
Tel. Aylesbury 830364

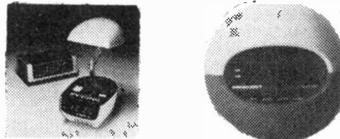BARGAINS FOR THE ELECTRONIC HANDYMAN BRANDED LED DIGITAL ALARM CLOCKS



(1) (2) (3)
Returned to Service Department within guarantee period.

- (1) With alarm repeat — S.R.S.P. of £17.00 offered at **£3.95** inc. VAT.
 - (2) With luxury lamp and repeat alarm as featured in most major U.K. Mail Order catalogues, S.R.S.P. £31.00—offered at **£7.95** inc. V.A.T.
 - (3) With integral luxury light and repeat alarm also as featured in most major U.K. Mail Order catalogues, S.R.S.P. of £32.00—offered at **£7.45** inc. V.A.T.
- These will be sold as received from our customers with the existing fault(s) and without guarantee.

Discounts available on large bulk purchases
**PRESCOTT CLOCK AND
WATCH COMPANY LIMITED**
Prescott House, Humber Road, London NW2 6ER

DIGITAL WATCH BATTERIES. Any make or size. Please quote type 60p + 10p P/P. 2 for £1.20, 4 for £2.40, 6 for £3.40. Discount for large quantity. — F. S. Butler, 511 Fulbridge Road, Peterborough PE1 6SB.

NASCOM USERS, program your 2708's in two minutes. Circuitry to plug into P10 ports. Send £2. — G. Benson, 2 Saxon Walk, Lichfield, Staffs.

TIRRO's new mail order price list of electronic components now available on receipt of SAE. TIRRO Electronics, Grenfell Place, Maidenhead, Berks.

INTRODUCTION TO MICROPROCESSORS AND COMPUTING. 50 pages of diagrams and explanation to get you started. Price £2.30 + 45p postage.
EDUCATIONAL DATA AND TECHNICAL SERVICES
59 Station Road, Cogenhoe, Northampton NN7 1LU

COMPONENTS TEST EQUIPMENT. CCT boards, anything electrical/electronic purchased for cash. "Q" Services Electronic (Cambridge) Ltd., 29 Lawford Crescent, Yateley (0252) 87148, Camberley, Surrey.

PRECISION SHEET METAL work chassis, panels, etc. Steel, stainless or aluminium, long/short runs, good deliveries. E.E.S. Limited, Clifford Road, Monks Road, Exeter 36489. Telex: 42401.

FOR COMPUTER OPERATORS. TI Programmer. Hexadecimal, octal, decimal calculator/converter for computer programmers. Performs arithmetic in any of three number bases. 15 sets of parentheses for complex problems. Independent memory and constant. Price £42.12 including VAT and P.&P. Or s.a.e. for details — R&E Marketing, Long Acre, The Ride, Ifold, Billingshurst, Sussex.

VMOS POWERFETS

(with free data and ideas sheet)
VN67AF (60v, 2A, 15W, TO202) **85p**
VN 10KM (60v, 1/2A, 1W, TO92+tab) **60p**
(plus 10p for 20% lower Ronmax. selection)
96 page VMOS Design Catalogue **45p**

BIFET OPAMPS

TL081CP (TL07/8 series 13v/μS) **29p**
TL074CN (Lo noise/distortion) **120p**
LF13741N (J FET 741) **27p**

BIMOS OPAMPS

CA3140E (MOS-TTL interface etc.) **38p**

QUAD NORTONS

LM3900N (cheap opamp substitute) **43p**
MC3401P (cheaper ditto) **35p**

OTHERS

709C (TO5. 12v/μS decompensated) **15p**
741C (famous!) **18p**
308 (I_gmax 7nA, I_{supply} 0.35mA) **25p**
LM78L05ACZ (5% accuracy, TO92) **29p**

FAST LOC MOS

4001B (t_p 25nS) **14p**
4007UB (t_p 20nS) **14p**
4011B (t_p 25nS) **14p**
4013N (t_{log} 25MHz) **28p**
4016B (BW 90MHz) **33p**
4017B (t_{log} 18MHz) **55p**
4020B (t_{log} 25MHz) **70p**
4069UB (t_p 20nS) **14p**

(all figures typical with 10-volt supply)
All offers subject to availability.
P&P 20p. Mail Order only

J. W. RIMMER
367 GREEN LANES,
LONDON N4 1DY

THIS SECTION IS A PRE-PAYMENT SERVICE ONLY

MINI-ADS: 31/4" x 21/8", 1-3 £38, 4-11 £36, 12 or more £34 per insertion. CLASSIFIED DISPLAY: 19p per word. Minimum 25 words. Boxed classifieds are £6.33 per col. centimetre. No P.O. Box Numbers can be accepted without full address.

Enquiries to: Advertising Department, 01-437 5982. 25-27 Oxford Street, London W1R 1RF

ETI PCB's

Buy it with Access.

Available for all ETI projects from day one of ETI, phone your order

SPECIAL OFFER—Single sided Pax PCB mat, four off, 4 3/4" x 6 1/2", 99p all up

ETI 681R

CROFTON ELECTRONICS LIMITED

35 GROSVENOR ROAD, TWICKENHAM
MIDDLESEX TW1 4AD · Tel: 01-891 1923

BRITISH MOTOROLA 6800 SYSTEMS

6800S: 16K Dynamic RAM, 1K Mikbug compatible monitor, room for 8K BASIC in ROM, VDU with u/I case and graphics, CUTS and HI Speed tape interfaces, Single pcb with power supply components. Price of kit from £275 with out kdb or £299.00 with keyboard.

Mini 6800 MK2. 1K user RAM, CUTS, VDU with u/I case and graphics with QUERTY keyboard from £152.50 NCU Board. This number cruncher using the MM57109 is supplied with our own Basic style program on tape (3K bytes) that will outperform any of the 8K Basics as a programmable calculator. Suitable for any 6800 system with Mikbug. Kit price £32.00 8K RAM (2114) and 5 or 10K PROM board. This pcb is bus compatible with the above systems and has all the buffering and decoding that you need. PCB only, £13.00

MICROCASE. A big beautiful grey ABS Moulding with heavy aluminium chassis big enough to house a big system. £29.00. ALL PRICES WITHOUT VAT AND POST. PLEASE SEND S.A.E. FOR LEAFLETS.

HEWART MICROELECTRICS
95 Blakelow Road, Macclesfield, Cheshire.

FOR NASCOM 1 IN SCOTLAND SEE STRATHAND

In stock now:

**Nascom 1
Buffer Boards
8, 16, 32K Ram Boards
Super Tiny Basic
Zeap on tape**

8K Basic on Tape

High speed cassette interface professional T.V. Monitor in kit form and other products arriving daily.

Please note it is not our policy to advertise Nascom products which are not currently available.

STRATHAND

**44 St. Andrew's Sq.
Glasgow G1 5PL
041-552 6731 or 2**

Access and Barclaycard sales welcome
Callers welcome 9-5 Monday to Friday

DESIGN AND CONSTRUCTION SERVICE. Prototype audio, digital, RF circuitry or equipment. For professional or amateur applications. Let us translate your ideas into hardware (or software). Contact: Westbury Technical Services, 121 Barton Street, Gloucester. Telephone 0452 76361.

LOST THE TIME?

MSF 60KHz TIME RECEIVER, data and audio outputs, built-in antenna, agc. £13.70.
SEQUENTIAL DISPLAY of year, month, date, day, hours, minutes, seconds for time receiver. £10.70 (no case or pcb, Veroboard okay). Right time always.
V.L.F. 7 10-150KHz Receiver, explore. £10.70.
MUSIC-CENTRE? NO RADIO 47 200KHz to Med. Wave Converter, coax and inductive outputs. £11.40.
Giro 21-923-4000. Ask overseas prices. Each easy-assembly kit includes all parts, printed circuit, case, postage, etc. Money-back assurance so SEND off NOW.

CAMBRIDGE KITS

45 (TV) Old School Lane, Milton, Cambridge

DISCO FOR SALE: High quality 100W custom built stereo system with a full lightshow at £950 ono. Will split up subject to reasonable offers. Phone Henry 01-437 1002 ext 12 daytime.

Complete repair instructions any requested TV £5 (with diagrams £5.50). Any requested service sheet £1 + s.a.e.
S.a.e. brings free newsletter, details of service sheets from 50p. Unique publications.

AUSETI

76 Church Street Larkhall, Lanarkshire

COLOUR MODULATOR

Kit £6.95 FOR ALL TV GRAPHICS!
Red, Green, Blue inputs (can be mixed).
SUPER EXPLOSION FLASH EFFECT FOR TANK BATTLE. FREE INTERFACE DETAILS.
WILLIAM STUART SYSTEMS
Dower House, Billericay Road, Herongate, Brentwood, Essex
CM13 3SD Tel: (0277) 810244
Barclaycard / Access welcome

TRITON COMPUTER for sale fully assembled and working full 4K RAM — Financial difficulty forces sale. Offers in region of £290, no reasonable offer refused. 62 Kirkstall Avenue, Leeds 5. Phone 782377.

SECURITY PRODUCTS

Designed for the Do-It-Yourself market. Easily installed. Full instructions supplied. As supplied to the trade.

Magnet and Reed Switch	Flush	85p
	Surface	85p
Pressure Mats	Large	£2.10
	Stair	£1.35
6" Heavy Duty Bells		£10.50
Sirens 12v 84dB @ 10'		£7.05
Bell Covers		£8.05
Window Foil Self-Adhesive		£3.20
Foil Blocks		20p
Door Loops, complete		£1.10
Key Switches, top grade		£4.00
Control Panels from		£29.50

Radar, Infra-Red, and many other items available. Price list supplied free
Please note that our prices now **INCLUDE VAT** at 12 1/2% + P&P

SECURITY CATALOGUE

Giving details of current professional alarm techniques — £1 (refundable on orders over £10)

Access and Barclaycard Sales welcome
We also sell Nascom 1

STRATHAND SECURITY

44 St. Andrew's Sq., Glasgow G1 5PL
041-552 6731 or 2



ROADRUNNER WIRE THREADING SYSTEM

Introkrit £9.88, Wiring Pencil with full Bobbin £2.44, Distribution Strips glue fix 20/pkt. 6" long £2.80 pkt., press fix 20/pkt. 2" long fit Vero/RS Bds. £2.92 pkt., Bobbins of "Q.S.E." wire 4 of 1 col./pkt. green, blue, copper, pink £2.12 pkt.

SPECIAL OFFER: Oryx 50 temp. cont. iron & stand £12.50 (rec. price £13.25). Microshear Cutters £3.15 pair, Conductive Paint £2.35, DIL Breadboards + & Gnd. Bus, 20 Ic Posns, Decouplers, C-Fingers £1.50 ea.

Prices include P&P. Please add 8% VAT.

T. J. Brine Associates
Blackdown Rural Inds.
Haste Hill
Haslemere, Surrey

INTENSIVE WEEKEND COURSES IN

BASIC

including hands-on mini computer operation.

This short intensive course is intended to instruct from minimal knowledge to an operational capability of computer programming in BASIC high level language. The course is fully residential from Friday evening to Sunday afternoon. Option of non-residential weekend, weekday evening and weekday courses available if required.

For further details of dates available, fees, etc.:

**Phone (041) 43139, or write to:
CLEVELAND BUSINESS SERVICES
Cleveland House, ROUTH
Beverley, North Humberside**

ADVERTISEMENT INDEX

AJD DIRECT SUPPLIES 95	GMT ELECTRONICS 6 & 7	POWELL 117
ALTEK 46	GP INDUSTRIAL ELECTRONICS	POWERTRAN ELECTRONICS
AMBIT 16 106 2 & 8
ANALOG ELECTRONICS 96	GREENBANK 93	POWERTRAN COMPUTERS 102
ARAK 95	HAL COMPUTERS 85	PROGRESSIVE RADIO 38
AUDIO ELECTRONICS 96	H.L. AUDIO 65	PROOPS BROS. 57
BAYDIS 46	ILP 105	ROGER SQUIRES 84
BI-PAK 4 & 5	INTEGRATED CIRCUITS 72	RTVC 83
CAMBRIDGE LEARNING 27	ITHACA SYSTEMS 52	SERVICE TRADING 66
CARSTON ELECTRONICS 57	KRAMER 86	SINTEL 56
CHILTMead 85	LB ELECTRONICS 65	SWANLEY 95
CHROMASONICS 84	L + B ELECTRONICS 77	TAMTRONIK 94
CHROMATRONICS 56	LOTUS SOUND 110	TARGET ELECTRONICS 46
CLEF PRODUCTS 94	MACLIN-ZAND 11	TECH BOOK SERVICE 28
CODESPEED 77	MAPLIN 116	TECHNOMATIC 14
COMP, COMP, COMP 114 & 115	MARSHALLS 104	TELERADIO 55
CRIMSON ELECKTRIK 100	METAC 78	TEMPUS 32
CROFTON 70	MINIKITS 86	TK ELECTRONICS 56
DELTA TECH & CO 84	MOUNTAINDENE 32	TRANSAM 39
E.D.A. 61	NICHOLLS 86	VERO 85
ELECTRONIC BROKERS 106	NIC MODELS 94	VIDEOTIME 100
ELECTROVALUE 106	PETALECT 70	WATFORD 12 & 13
FLUKE INTERNATIONAL 92&93	PICODYTE 70	WILMSLOW 57

7400 10p	7480 40p	74156 45p	4013 30p	LINEAR	LM348N 90p	SAS660 275p	TBA820 100p
7401 10p	7481 85p	74157 45p	4015 50p	AY38500 450p	LM380 75p	SAS670 250p	TBA920Q 280p
7402 10p	7482 75p	74160 55p	4016 30p	CA39039 70p	LM381N 150p	SL917B 650p	TCA270S 220p
7403 10p	7483 75p	74161 55p	4017 50p	CA3046 60p	LM382 120p	SN16889P 275p	TCA270Q 220p
7404 12p	7484 70p	74162 55p	4018 55p	CA3060 225p	LM391 180p	SN78003N 150p	TCA760 300p
7405 12p	7485 60p	74163 55p	4019 40p	CA3065 200p	LM555 25p	SN76013N 150p	TCA4500A 380p
7406 25p	7486 25p	74164 60p	4020 50p	CA3076 250p	LM565 130p	SN76013ND 130p	TDA1004 300p
7407 25p	7489 130p	74165 60p	4022 50p	CA3080 75p	LM709C 40p	SN76023N 150p	TDA1008 300p
7408 12p	7490 25p	74166 75p	4023 12p	CA3084 250p	LM710T05 60p	SN76023ND 150p	TDA1022 575p
7409 12p	7491 40p	74167 160p	4024 40p	CA3085 85p	LM710DIL 65p	SN76033N 180p	TDA1024 150p
7410 12p	7492 35p	74170 100p	4025 12p	CA3086 60p	LM723T05 40p	SN76131N 125p	TDA1034 250p
7411 15p	7493 30p	74173 80p	4026 80p	CA3088 190p	LM723DIL 40p	SN76227N 160p	TDA2002 300p
7412 15p	7494 70p	74174 60p	4027 30p	CA3089 160p	LM733 120p	SN76228N 180p	TDA2020 320p
7413 25p	7495 45p	74175 60p	4028 45p	CA3090AQ 360p	LM739 150p	SN76660N 75p	TL081 50p
7414 45p	7496 45p	74176 50p	4029 50p	CA3123E 130p	LM741 20p	TAA300 150p	TL082 100p
7416 25p	7497 120p	74177 50p	4030 30p	CA3130 100p	LM747 75p	TAA350 270p	TL083 130p
7417 25p	74100 80p	74178 75p	4032 80p	CA3140 60p	LM748 40p	TAA550 35p	TL084 130p
7420 12p	74104 40p	74179 120p	4033 100p	CA3161E 150p	LM1303N 100p	TAA570 250p	UAA170 220p
7421 20p	74105 40p	74180 90p	4040 60p	CA3162E 400p	LM1458 100p	TAA661B 150p	XR320 250p
7422 15p	74107 25p	74181 130p	4043 60p	CA3189E 270p	LM3080 75p	TAA700 350p	XR2003 150p
7423 20p	74108 100p	74182 50p	4046 90p	FX209 800p	LM3900 55p	TAA790 350p	XR2206 450p
7425 20p	74166 75p	74184 120p	4047 80p	LD130 460p	LM3909N 65p	TAD100 150p	XR2207 450p
7426 22p	74109 25p	74185 100p	4048 50p	LF356 80p	MC1310P 140p	TAD110 130p	XR2208 600p
7427 22p	74118 75p	74188 320p	4049 25p	LF357 80p	MC1312P 150p	TTD120A 60p	XR2216 675p
7428 25p	74120 80p	74190 70p	4050 25p	LM211H 250p	MC1314P 190p	TBA120S 70p	XR2264 450p
7430 12p	74121 25p	74191 70p	4054 100p	LM300T05 170p	MC1315P 230p	TBA120T 90p	XR2265 450p
7432 20p	74122 35p	74192 60p	4055 130p	LM301AN 30p	MK50398 650p	TBA480Q 200p	XR2567 250p
7433 28p	74123 40p	74193 60p	4056 120p	LM301T05 45p	MM5314 380p	TBA520Q 200p	XR4136 150p
7437 20p	74125 35p	74194 55p	4060 100p	LM304 200p	MM5316 480p	TBA530Q 200p	XR4151 350p
7438 20p	74126 35p	74195 50p	4066 35p	LM307N 65p	NE 529K 150p	TBA540 200p	XR4202 150p
7440 12p	74128 60p	74196 50p	4069 12p	LM308T05 100p	NE555 25p	TBA550Q 250p	XR4212 150p
7441 45p	74130 120p	74197 50p	4070 12p	LM308DIL 100p	NE556 90p	TBA560C 250p	XR4739 150p
7442 40p	74131 90p	74198 100p	4071 12p	LM309K 140p	NE562B 400p	TBA641A1250p	ZN414 100p
7443 60p	74132 45p	74199 100p	4072 12p	LM310T05 150p	NE566 150p	TBA700 180p	ZN1034E 200p
7444 60p	74135 90p	74293 90p	4081 12p	LM311T05 150p	NE567 170p	TBA720Q 225p	95H90 800p
7445 65p	74136 80p	74L500 18p	4082 12p	LM317K 325p	SAD1024 1500p	TBA750Q 200p	11C90 1400p
7446 50p	74137 90p	745112 80p	4093 70p	LM324 70p	SAS560 160p	TBA800 90p	
7447 50p	74138 100p		4510 60p	LM324 70p	SAS570 160p	TBA810 100p	
7448 50p	74141 50p		4511 70p	LM339 60p			
7450 12p	74142 180p		4516 65p				
7451 12p	74143 270p		4518 65p				
7453 12p	74144 270p	CMOS	4520 65p				
7454 12p	74145 55p	4000 12p	4528 80p				
7460 12p	74147 100p	4001 12p	4583 70p				
7470 25p	74148 90p	4002 12p					
7472 20p	74150 65p	4006 80p					
7473 25p	74151 45p	4007 14p					
7474 25p	74153 45p	4009 30p					
7475 25p	74154 70p	4011 12p					
7476 25p	74155 45p	4012 12p					

IN 4148 Diodes by ITT/Texas, 100 for £1.50
 Static Ram 2102 1024 x 1 bit 450 nano sec £1.00 each
 2112 256 x 4 bit 450 nano sec £2.50
 Murata Ultrasonic Transducers 40kHz £2.00 each £3.50 pair.
 All prices include post and VAT

T. POWELL
 306 ST. PAULS ROAD, Highbury Corner, London, N.1. TEL: 01-226 1489
 Barclay / Access credit cards accepted

INTERESTED IN HOME COMPUTING?

EX STOCK

FREE B BUG
valued at £23.00
plus 10 x C12 cassettes
valued at £4.00
plus Standard Modulator
valued at £2.25
WITH EVERY NASCOM

Start now and don't get left behind **THE NASCOM 1**
is here Ex-stock with full technical services

Plus the opportunity to join the fastest moving club of personal computer users enabling you to get the most out of your computer. You can OBTAIN and EXCHANGE programs and other software — many now available.

The Powerful Z80
Microprocessor
Professional Keyboard
1 Kbyte Monitor in EPROM
2 Kbyte RAM (expandable)
Audio Cassette interface
Plugs into your domestic TV
Easy construction from
straightforward instructions
— no drilling or special tools
— Just neat soldering
required.



SAVE
£60

Only ~~£197.50~~ + 8% VAT (includes p & p + insurance)

Manuals separately 2.95
Z80 programming Manual 6.90
Z80 Technical Manual 2.95
PIO Technical Manual 2.95
(All prices add 8% VAT)

NEW LOW PRICE
£165
Power supply suitable for
NASCOM 19.90

NASCOM AD ONS — Nascom improved monitor B Bug (2K)
featuring — *Four times tape speed *Direct text entry without
ASCII *Extended keyboard facility *Additional useful
subroutines **£23.00**

Nascom Vero Case £22.50
Nascom Joy Stick Kit £14.90
Nascom Music Box Kit £9.90
(write your own tunes and play
them on your Nascom.
Complete with full documentation).

GRAPHICS ADD ON BOARD £9.90
Complete kit to upgrade your NASCOM for graphics capability
includes full documentation and demonstration program.

NEW! AT LAST 8K BASIC £160
FOR NASCOM 1 Complete on S100 Board EX-STOCK
+ VAT

THE EXIDY SORCERER.

SORCERER COMPUTER SYSTEM

The Sorcerer Computer is a completely assembled and tested computer system. Standard configuration includes 63-key typewriter-style keyboard and 16-key numeric pad, Z80 processor, dual cassette I/O with remote computer control at 300 and 1200 baud data rates, RS232 serial I/O for communications, parallel port for direct Centronics printer attachment, 4K ROM operating system, 8K ROM Microsoft BASIC in Rom Pac™ cartridge, composite video of 64 char/line 30 line/ screen, 128 upper/lower case ASCII set and 128 user-defined graphic symbols, operation manual, BASIC programming manual and cassette/video cables, connection for S-100 bus expansion.

CPM NOW



SAVE
£100

LOOK!

*32K RAM on board
*RS232 interface *8K BASIC ROM
*CUTS interface *4K MONITOR
*KANSAS CITY interface *S100 BUS
*User defined graphic symbols *Z80 cpu

EX STOCK

16K £180 £725 * 32K £250 £790 * Credit facilities available. + VAT

MODULATORS UHF Channel 36

Standard 6 meg band width £2.25
High Quality 8 meg band width £4.90 EX-STOCK

**VAT AT COMP STILL 8%—WE
PAY THE EXTRA. PLEASE QUOTE
"ETI 200" ON ALL ORDERS**

PET COSTS LESS AT COMP and it's a pedigree

RRP £550

The No. 1 Personal Computer
in the U.K. **£499** SAVE
Affordable 8K + VAT £50
for the first time user and
the professional check out
the PET, the world's most
popular personal computer.



EX STOCK

Also 16K big professional keyboard £590 + VAT



NEW! THE ITT APPLE (2020)

ITT
MICRO COMPUTER

£827
+ VAT

EX-STOCK
4K

16K
£49
+ VAT

**LOW PRICE
MEMORY UPGRADE
PURCHASED AT TIME OF
ORDER**

* Audio cassette tape interface * Up to 48K RAM on board * BASIC in ROM (graphics commands include COLOUR = VLIN, HLIN, PLOT and SCRN)
* Built in Loudspeaker * Buckets of software already available * disk system (110 K byte per drive — includes controller) only £425 + VAT

EX-STOCK

THE TRS-80 (SPECIAL SCOOP) Low Priced, Ready to Go!



Use your own cassette

Level-II with 4K RAM
Improved graphics, print
formatting, and a faster cassette
transfer rate are features of
Level-II BASIC.

£350 + VAT

EX STOCK

PLUGS INTO
YOUR OWN TV

Level-II with 16K RAM
A combination of 16K RAM and
the powerful Level-II BASIC
produces a system capable of
handling most demands.

£399 + VAT

KEY BOARD ONLY

COMPLETE WITH
UHF MODULATOR

UK POWER SUPPLY INCLUDED

All prices include VAT except where shown. Orders over £5 post and packing free otherwise add 20p. Please make cheques and postal orders payable to COMP, or phone your order quoting BARCLAYCARD or ACCESS

OPEN — 10am to 7pm — Monday to Saturday
CREDIT FACILITIES ARRANGED



COMPUKIT UK101

LOW COST SUPERBOARD IN KIT FORM



The CompuKit UK101 has everything a one board 'superboard' should have.

- * Uses ultra powerful 6502 microprocessor
- * 50Hz Frame refresh for steady clear picture (U.S.A. products with 60Hz frame refresh always results in jittery displays)
- * 48 chars by 16 lines — 1K memory mapped video system providing high speed access to screen display enabling animated games and graphs
- * Extensive 256 character set which includes full upper and lower case alphanumerics, Greek symbols for mathematical constants and numerous graphic characters enabling you to form almost any shape you desire anywhere on the screen
- * 8K full Microsoft Basic in ROM compatible with PET APPLE SORCERER hence taking the headache out of programming by using simple English

FULL CONSTRUCTION DETAILS IN P.E. AUG 1979 EDITION

statements. Much faster than currently available personal computers

- * Professional 52 Key keyboard in 3 colours — software polled meaning that all debouncing and key decoding done in software
- * Video output and UHF Highgrade modulator (8MHz Bandwidth) which connects direct to the aerial socket of your TV Channel 36 UHF
- * Fully stabilised 5V power supply including transformer on board
- * Standard KANSAS city tape interface providing high reliability program storage — use on any standard domestic tape or cassette recorder
- * 4K user RAM expandable to 8K on board £49 extra
- * 40 line expansion interface socket on board for attachment of extender card containing 24K RAM and disk controller (Ohio Scientific compatible)
- * 6502 machine code accessible through powerful 2K machine code monitor on board
- * High quality thru plated P.C.B. with all I.C.'s mounted on sockets

Delivery date June 1979 at the 1979 MicroComputer Show. Customer orders in strict rotation only.

SEND ONLY £10.00 DEPOSIT TO RESERVE ONE


A tape of 10 programs on cassette — educational games, etc. will be supplied free of charge with each kit.

NO EXTRAS NEEDED JUST HIT 'RETURN' AND GO

Simple Soldering due to clear and concise instructions compiled by Dr. T. Berk, BSc PhD

Build, understand, and program your own computer for only a small outlay.

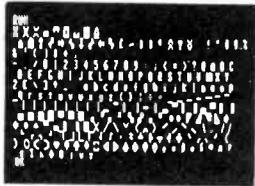ONLY £219 + VAT including RF Modulator & Power supply. Absolutely no extras.



The CompuKit UK101 Character Set

COMMANDS	NEW	NULL	RUN
CONT LIST			
STATEMENTS			
CLEAR DATA	DEF	DIM	END FOR
GOTO GOSUB	IF GOTO	IF THEN	INPUT LET
NEXT ON GOTO	ON GOSUB	POKE	PRINT READ
REM RESTORE	RETURN	STOP	

EXPRESSIONS
 OPERATORS
 + * / ^ NOT AND OR >> << > < = > < = RANGE 10³² to 10 + 32

VARIABLES
 A, B, C ... Z and two letter variables
 The above can all be subscripted when used in an array. String variables use above names plus \$ e.g. AS

FUNCTIONS	ATN(X)	COS(X)	EXP(X)	FRE(X)	INT(X)
ABS(X)	PEEK(I)	POS(I)	RND(X)	SGN(X)	SIN(X)
LOG(X)	SQR(X)	TAB(I)	TAN(X)	USR(I)	
SPC(I)					
STRING FUNCTIONS	FRE(X\$)	LEN(X\$)	MID\$(X\$, I, J)		
ASC(X\$)	CHR\$(I)	STR\$(X)	VAL(X\$)		
RIGHT\$(X\$, I)					

SPECIAL CHARACTERS

- ↵ Erases line being typed, then provides carriage return, line feed
- ⌫ Erases last character typed
- ␣ Carriage Return — must be at the end of each line
- ␣ Separates statements on a line
- ␣ CONTROL/C Execution or printing of a list is interrupted at the end of a line
- ␣ BREAK IN LINE 'XXXX' is printed, indicating line number of next statement to be executed or printed
- ␣ CONTROL/O No outputs occur until return made to command mode. If an Input statement is encountered, either another CONTROL/O is typed, or an error occurs
- ? Equivalent to PRINT

The Teleplay Colour Programagame

ENGLAND'S MOST POPULAR TV GAME KIT

now back in stock at reduced prices

AS REVIEWED IN HOBBY ELECTRONICS



TELEPLAY

have produced a new product of easy to assemble cartridge games, for you and all your family that will not go out of date. Just ADD each new cartridge, as it becomes available, and your colour video centre will be up to date the Teleplay way. You will save pounds in the long run. Works CK on Blackm and White TV. The Teleplay Kit consists of a Professional Finished Inject Mounted Box — Joystick Hand Controls — one cartridge which consists of 10 games — Football, Tennis, Solo Squash (1 & 2 players), Shoo, etc. Mains Adaptor. All holes are pre-drilled — No Special equipment required. You'll be surprised how easy it is to assemble this professional kit! Instruction Manual supplied separately at 0.45p. TELEPLAY GIVES YOU TWICE THE FUN BUILDING AND PLAYING THE MOST PROFESSIONAL TV GAME KIT EVER OFFERED.

Electrical knowledge is not a necessity to assemble this project — just simple soldering.

Every 3 months a NEW game will become available to you and those already under production include Submarines, Space War, Wipe Out and many more. The price of these will vary from £12 to £19 depending upon the complexity of the game. All Cartridges fully assembled.

STUNT CYCLE 4 games — Cartridges and Hand Controls — £12.90

WIPE OUT — 6 games — £11.90

TANK BATTLE — Cartridge and Hand Controls — £18.90

ROAD RACE — 2 games — Cartridge — Controls already with basic kit — £10.90

EUROPE'S LARGEST STOCKIST OF TV GAME COMPONENTS.

COMP IS AN APPOINTED DEALER FOR COMMODORE, EXIDY, APPLE, NASCOM, OHIO, GI, ATARI, TELEPLAY & ITHACA.

COMP COMPUTER COMPONENTS

14 STATION ROAD, NEW BARNET, HERTFORDSHIRE TEL: 01-441 2922 (Sales) 01-449 6596
 CLOSE TO NEW BARNET BR STATION — MOORGATE LINE TELEX: 298755
 OPEN — 10am to 7pm — Monday to Saturday CONTINUOUS DEMONSTRATIONS

(PART OF THE COMPSHOP LTD GROUP)

VISIT OUR NEW SHOP AT 1 WALLCOT BUILDINGS, LONDON ROAD, BATH, AVON.



Speakers from 1½ inch to 15 inch; megaphone, PA horns, crossovers etc. They're all in our catalogue. Send the coupon now!



A genuine 150W per channel stereo disco to build yourself. Full specification in our catalogue.




Our catalogue even includes some popular car accessories at marvellous prices.



Our catalogue describes a wide range of plugs and sockets, all at marvellous prices. See cat. pages 114 to 129 for details.



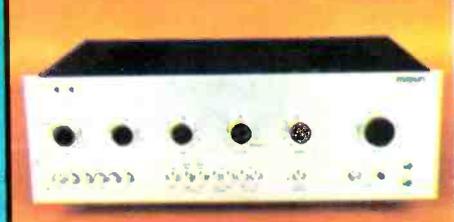61-note touch-sensitive piano to build yourself. Full specification in our catalogue.



A very high quality 40W per channel stereo amplifier with a superb specification and lots of extras. Full construction details in our catalogue.



A digitally controlled stereo synthesiser the 5600S with more facilities than almost anything up to £3,000. Build it yourself for less than £700. Full specification in our catalogue.



A hi-fi stereo tuner with medium and long wave, FM stereo and UHF TV sound! Full construction details in our catalogue.



These are just some of the metal cases we stock. There are dozens of plastic ones to choose from as well. See pages 52 to 57 of our catalogue.

MAPLIN

ELECTRONIC SUPPLIES LTD

All mail to:-
P.O. Box 3, Rayleigh, Essex SS6 8LR.
Telephone: Southend (0702) 554155.


Shop: 284 London Road,
Westcliff-on-Sea, Essex.
(Closed on Monday).
Telephone: Southend (0702) 554000



Multimeters, analogue and digital, frequency counter, oscilloscopes, and lots, lots more at excellent prices. See cat. pages 106 and 188 to 188 for details.



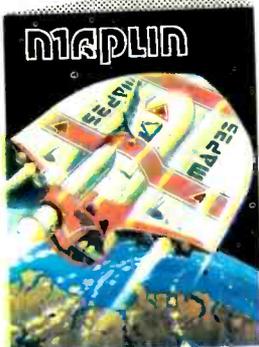A 10-channel stereo graphic equaliser with a quality specification at an unbeatable price when you build it yourself. Full specification in our catalogue.



A massive new catalogue from Maplin that's even bigger and better than before. If you ever buy electronic components, this is the one catalogue you must not be without. Over 280 pages - some in full colour - it's a comprehensive guide to electronic components with hundreds of photographs and illustrations and page after page of invaluable data.

Our bi-monthly newsletter contains guaranteed prices, special offers and all the latest news from Maplin.



A superb range of microphones and accessories at really low prices. Take a look in our catalogue - send the coupon now!

Post this coupon now for your copy of our 1979-80 catalogue price 75p.

Please send me a copy of your 280-page catalogue. I enclose 75p but understand that if I am not completely satisfied I may return the catalogue to you within 14 days and have my 75p refunded immediately. If you live outside U.K. send £1 or ten International Reply Coupons.

NAME NEAL CROOK
ADDRESS 19 GREENLANDS ROAD

ET1879