

# electronics today

OCTOBER 1979

INTERNATIONAL

50p

## **SUPER-FI AMPLIFIER PROJECT**

*Full details inside*

*Earth Satellites*


*Reaction Timer*


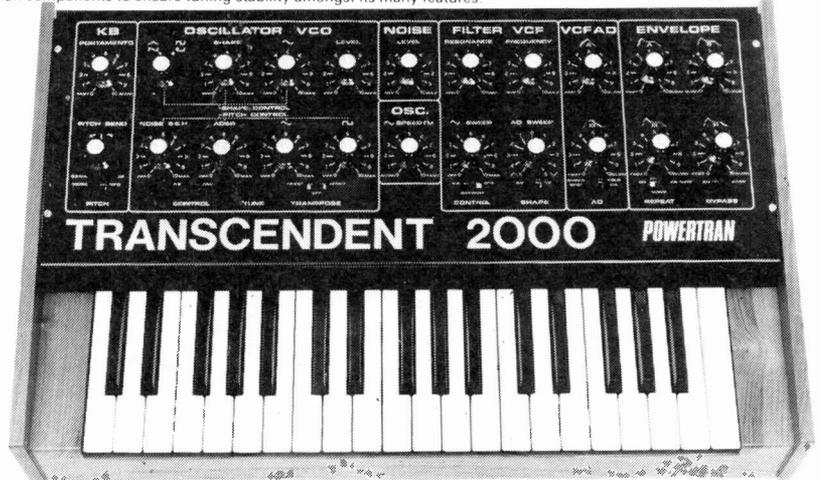
# TRANSCENDENT 2000 SINGLE BOARD SYNTHESIZER

LIVE PERFORMANCE SYNTHESIZER DESIGNED BY CONSULTANT TIM ORR (FORMERLY SYNTHESIZER DESIGNER FOR EMS LIMITED) AND FEATURED AS A CONSTRUCTIONAL ARTICLE IN ELECTRONICS TODAY INTERNATIONAL.

The TRANSCENDENT 2000 is a 3 octave instrument transposable 2 octaves up or down giving an affective 7 octave range. There is portamento, pitch bending, a VCO with shape and pitch modulation, a VCF with both low and high pass outputs and a separate dynamic sweep control, a noise generator and an ADSR envelope shaper. There is also a slow oscillator, a new pitch detector, ADSR repeat, sample and hold, and special circuitry with precision components to ensure tuning stability amongst its many features. The kit includes fully finished metalwork, fully assembled solid teak cabinet, filter sweep pedal, professional quality components (all resistors either 2% metal oxide or 1/2% metal trim) and it really is complete — right down to the last nut and bolt and last piece of wire! There is even a 13A plug in the kit — you need buy absolutely no more parts before plugging in and making great music! Virtually all the components are on the one professional quality fibreglass PCB printed with component locations. All the controls mount directly on the main board, all connections to the board are made with connector plugs and construction is so simple it can be built easily in a few evenings by almost anyone capable of neat soldering! When finished you will possess a synthesizer comparable in performance and quality with ready-built units selling for between £500 and £700!



Cabinet size 24.6" x 15.7" x 4.8" (rear) 3.4" (front)

**COMPLETE KIT  
ONLY  
£172.00 + VAT!**


Comprehensive handbook supplied with all complete kits! This fully describes construction and tells you how to set up your synthesizer with nothing more elaborate than a multi-meter and a pair of ears!

**BEING FEATURED IN THIS MAGAZINE!**  
Another superb design by synthesizer expert Tim Orr!

## **NEW!** TRANSCENDENT DPX

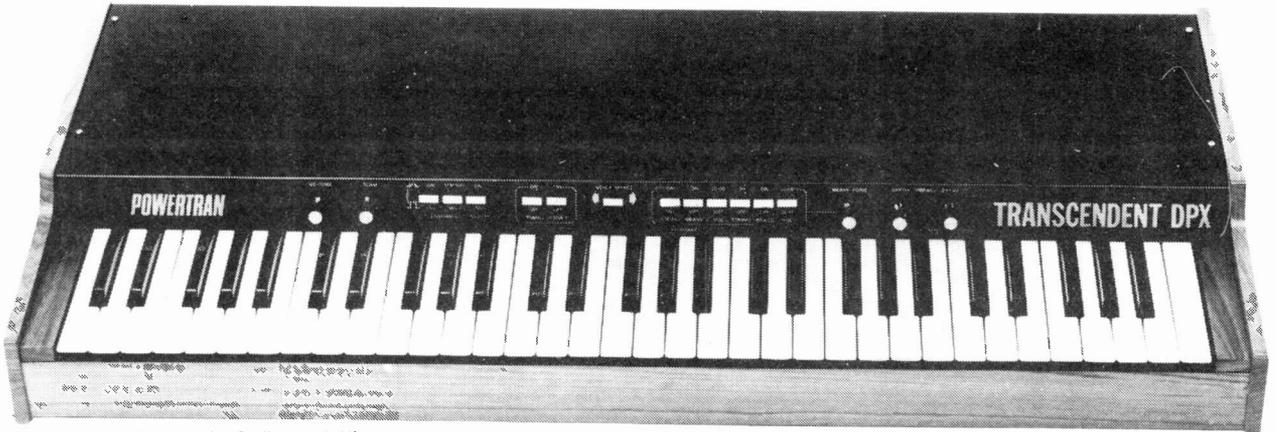**DIGITALLY CONTROLLED, TOUCH SENSITIVE, POLYPHONIC, MULTI-VOICE SYNTHESIZER**

The Transcendent DPX is a really versatile new 5 octave keyboard instrument. There are two audio outputs which can be used simultaneously. On the first there is a beautiful harpsichord or reed sound — fully polyphonic i.e. you can play chords with as many notes as you like. On the second output there is a wide range of different voices, still fully polyphonic. It can be a straightforward piano or a honky tonk piano or even a mixture of the two! Alternatively you can play strings over the whole range of the keyboard or brass over the whole range of the keyboard or should you prefer — strings on the top of the keyboard and brass at the lower end (the keyboard is electronically split after the first two octaves) or vice versa or even a combination of strings and brass sounds simultaneously. And on all voices you can switch in circuitry to make the keyboard touch sensitive! The harder you press down a key the louder it sounds — just like an acoustic piano. The digitally controlled multiplexed system makes practical touch sensitivity with the complex dynamics law necessary for a high degree of realism. There is a master volume and tone control, a separate control for the brass sounds and also a vibrato circuit with variable depth control together with a variable delay control so that the vibrato comes in only after waiting a short time after the note is struck for even more realistic string sounds.



Cabinet size 36.3" x 15.0" x 5.0" (rear) 3.3" (front)

**COMPLETE KIT ONLY £365.00 + VAT!**

To add interest to the sounds and make them more natural there is a chorus ensemble unit which is a complex phasing system using CCD (charge coupled device) analogue delay lines. The overall effect of this is similar to that of several acoustic instruments playing the same piece of music. The ensemble circuitry can be switched in with either strong or mild effects.

As the system is based on digital circuitry digital data can be easily taken to and from a computer (for storing and playing back accompaniments with or without pitch or key change, computer composing etc.) and an interface socket (25 way D type) is provided for this purpose.

Although the DPX is an advanced design using a very large amount of circuitry, much of it very sophisticated, the kit is mechanically extremely simple with excellent access to all the circuit boards which interconnect with multiway connectors, just four of which are removed to separate the keyboard circuitry and the panel circuitry from the main circuitry in the cabinet.

The kit includes fully finished metalwork, solid teak cabinet, professional quality components (all resistors 2% metal oxide), nuts, bolts, etc. even a 13A plug — you need buy absolutely no more parts before plugging in and making great music! When finished you will possess an instrument comparable in performance and quality with ready-built units selling for over £1,200!


# POWERTRAN

**ORDERING INFORMATION  
AND MORE KITS ON PAGE 8**


All kits also available as separate packs (e.g. PCB component sets, hardware sets, etc.)  
Prices in FREE CATALOGUE



Super amp project p.55

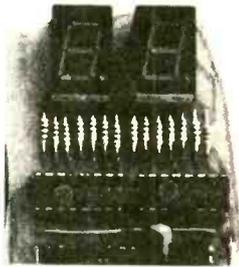

Take your time p.75

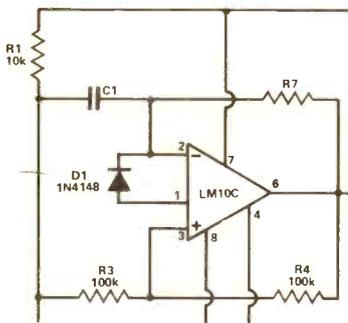

Well employed p.68

# electronics today

OCTOBER 1979 VOL 8 NO 10 INTERNATIONAL

## FEATURES

- NEWS DIGEST **7** Read it first here!
- EARTH SATELLITES **16** Round and round and round and . . .
- MICROSENSE **27** Further into the MPU maze
- RAVEN ON **42** Carpet tiles with feeling and flat tellys!
- MICROFILE **52** News for the small (system) men!
- LM 10 APPLICATIONS **68** Circuits galore for a new goodie.
- AUDIOPHILE **80** Competitions result and new speaker concept.
- DESIGNERS NOTEBOOK **85** Diode gates to new fields!
- TECH-TIPS **93** It's all your own work.

## PROJECTS

- CABLE TESTER **23** Build it once and stop worrying.
- TRANSCENDENT DPX **35** Control circuitry
- SPEECH COMPRESSOR **47** Avoid misunderstandings on the airways!
- AUDIO AMPLIFIER **55** The highest quality sound around.
- REACTION TIMER **75** Think you're quick huh?

## INFORMATION

- HOBBY ELECTRONICS **15** Don't miss out.
- MARKET PLACE **41** Timely offers.
- ETI PRINTS **45** The only way to do it!
- SPECIALS **51** All our own work . . .
- ETI NEXT MONTH **67** This you must see.
- BOOK SERVICE **79** Fine print indeed!
- COME AND JOIN US! **94** We need YOU at ETI.
- PCB FOIL PATTERNS **100** Get board with ETI.

### INTERNATIONAL EDITIONS

- AUSTRALIA Collyn Rivers  
Publisher  
Roger Harrison  
Acting Editor
- HOLLAND Anton Kriegsman  
Editor-in-Chief
- CANADA Graham Wideman  
Editor
- GERMANY Udo Wittig  
Editor



ABC

EDITORIAL AND ADVERTISEMENT OFFICE  
145 Charing Cross Road, London WC2H 8DEE. Telephone 01 437 1002/3/4/5

- Ron Harris, B.Sc. Editor
- Ian Graham B.Sc. Editorial Assistant
- Diego M. Rincon Art Director
- Dee Camilleri Production
- Paul Edwards, Tony Strakas Technical Illustrators
- Ray Marston Project Editor
- Keith Brindley, John Fitzgerald Project Engineer
- Steve Ramsahadeo Project Development
- Margaret Hewitt Administration
- Lorraine Stout Editorial Secretary
- Christopher Surgenor (Manager), Advertising
- Sandy Neville Ad. Production
- Steve Rowe Ad. Representative
- Halvor Moorshead Editorial Director

PUBLISHED BY  
DISTRIBUTED BY

Modmags Ltd., 145 Charing Cross Road  
Argus Distribution Ltd. (British Isles)  
Gordon & Gotch Ltd. (Overseas)  
QB Limited, Colchester

PRINTED BY

Electronics Today International is normally published on the first Friday of the month prior to the cover date

COPYRIGHT: All material is subject to world wide Copyright protection. All reasonable care is taken in the preparation of the magazine to ensure accuracy but ETI cannot be held responsible for it legally. Where errors do occur a correction will be published as soon as possible afterwards.

ALL PRICES IN PENCE EACH UNLESS OTHERWISE STATED

CAPACITORS				Electrolytic Axial Leads				Order Code			
-10% to +50% Tol				Cap 015 + $\mu$ F + V d.c.							
$\mu$ F	V d.c.	16	25	40	63						
1.0											
1.5											
2.2											
3.3											
4.7											
6.8											
10											
15											
22											
33											
47											
68											
100											
150											
220											
330											
470											
680											
1000											
1500											
2200											

Electrolytic Can Type				Order Code			
High Ripple, 1EC Grade 1, Low E.S.R.				Cap HR + $\mu$ F + Volts			
Supplied complete with Vertical Fixing Clip							
$\mu$ F	V d.c.	16	25	40	63		
2200	16V						
4700	16V						
10000	16V						
22000	16V						
2200	25V						
4700	25V						
10000	25V						
22000	25V						
1000	40V						
2200	40V						
4700	40V						
10000	40V						
2200	70V						
4700	70V						
10000	70V						
2200	100V						
4700	100V						
2200	100V						

Electrolytic Radial Leads				Order Code			
-10% to +50% Tol				Cap 034 + $\mu$ F + Volts			
$\mu$ F	V d.c.	10	16	25	35	40	50
47							
68							
10							
1.0							
1.5							
2.2							
3.3							
4.7							
6.8							
10							
15							
22							
33							
47							
68							
100							
150							
220							

Tantalum Bead				Order Code			
20% Tol				Cap PR + $\mu$ F + Volts			
$\mu$ F	V d.c.	3.15	6.3	10	16	25	35
0.1							
0.15							
0.22							
0.33							
0.47							
0.68							
1							
1.5							
2.2							
3.3							
4.7							
6.8							
10							
15							
22							
33							
47							
68							
100							

Trimmers				Order Code			
250V D.C. Wkg. Film Dielectric, Miniature				500V D.C. Wkg. C004 EA Tubular Type			
Value	Order Code	Value	Order Code	Value	Order Code	Value	Order Code
1.4 - 4.1pF	19	Cap 809 A	.8 - 3.9pF	46	Cap 802 3		
2 - 9pF	19	Cap 808 B	.8 - 6.8pF	48	Cap 802 6		
2 - 20pF	21	Cap 808 C	1 - 13pF	61	Cap 802 12		
5.5 - 59.5pF	29	Cap 808 D	1.7 - 19.7	62	Cap 802 18		

Minature Low Value				Order Code			
Polystyrene, Axial, 1% Tol., > 63V D.C. Wkg				Ceramic Plate, Radial, Low K, 1.5pF - 25pF Tol., 10-330pF - 2% Tol., 100V D.C. Wkg			
Ceramic Plate, Radial, High K, -20% to +80% Tol., 63V D.C. Wkg							
pF	424	632	630	629	pF	424	632
1					100	16	6
1.2					120	16	8
1.5					150	16	8
1.8					180	16	6
2.2					220	16	6
2.7					270	18	8
3.3					330	18	8
3.9					390	18	8
4.7					470	18	5
5.6					560	16	5
6.8					680	16	5
8.2					820	16	5
10					1000	16	5
12					1200	16	5
15					1500	18	6
18					1800	18	6
22					2200	18	6
27					2700	18	6
33					3300	18	6
39					3900	18	6
47					4700	23	7
56					5600	23	7
68					6800	23	7
82					8200	23	7

Polyester Radial Leads				Order Code			
Dipped Type, -20% Tol., > 250V D.C. Wkg. C280/352 Style				Moulded Type, -10% Tol., > 100V D.C. Wkg. 10.2mm Pitch Centres			
Moulded Type, -10% Tol., > 100V D.C. Wkg. 7.6mm Pitch Centres							
$\mu$ F	352	360	PHE290	$\mu$ F	352	360	PHE280
001							
0015							
0022							
0033							
0047							
0068							
01							
015							
022							
033							
047							
068							

### CASES

**Small Desk Console** - Boss Industrial Mouldings  
Slope Front Console, Recessed Top  
ABS Base, C/W Brass Bushes, In Orange  
1mm Aluminium Top Panel Finished Grey

Order Code	Case B1M1005 OR	Case B1M1006 OR
W161, D96, H39 (57)	186	
W215, D130, H47 (73)	268	

**Plastic Boxes** - Boss Industrial Mouldings  
Moulded Box and Close Fitting Flanged Lid  
ABS Box, C/W Brass Bushes, and Lid In Orange

Order Code	Case B1M2003 OR	Case B1M2005 OR	Case B1M2006 OR
L112 W62 D31	87		
L150 W80 D50	115		
L190 W110 D60	195		

### VERO ELECTRONICS PRODUCTS

2.5" x 5" 1" pitch Veroboard	59	VERO 21069J
3.75" x 5" 1" pitch Veroboard	66	VERO 21072D
2.5" x 1" 1" pitch Veroboard (5)	70/Pack	VERO 21076C
3.75" x 5" 1" pitch Plain Board	56	VERO 21078E
5.82" x 2.91" 1" pitch V-Q-DIP Board	111	VERO 21084E
Spot Face Cutter	89	VERO 21013A
Pin Insertion Tool for 040 type pin	122	VERO 21015F
DS Pins 040 (100)	38/Pack	VERO 21087G
SS Pins 040 (100)	38/Pack	VERO 21017B
6mm Board Standoff (100)	181/Pack	VERO 21321K
19mm Board Standoff (100)	215/Pack	VERO 21322G
19mm Board Standoff (100)	226/Pack	VERO 21323D
Verowire Kit (1 pen, 2-wire, 25-cmb)	375/Kit	VERO 21341D
Verowire Combs (100)	407/Pack	VERO 21339F
Verowire Wire (4)	228/Pack	VERO 21340G
Flip Top Box, Small, Black	192	VERO 21317D
Flip Top Box, Large, Black	250	VERO 21319J

### HARDWARE

**D.I.L. Sockets**

Order Code	DIL SKT 8	DIL SKT 14	DIL SKT 16	DIL SKT 24	DIL SKT 28	DIL SKT 40
8 Pin Low Profile Socket Tin	11					
14 Pin Low Profile Socket Tin		13				
16 Pin Low Profile Socket Tin			14			
24 Pin Low Profile Socket Gold				86		
28 Pin Low Profile Socket Gold					78	
40 Pin Low Profile Socket Gold						127

**Heatsinks**

Order Code	Sink 5F	Sink TV2	Sink TV3	Sink TV4	Sink TV5
Individual Type for 1 x T05 50°C/W	10				
Individual Type for 1 x T066 10.5°C/W	26				
Individual Type for 1 x T03 7.2°C/W	24				
Individual Type for 1 x T0126 17°C/W	23				
Individual Type for 1 x T0220 17°C/W	23				

**Instrument Case** - Boss Industrial Mouldings  
Covers Manufactured from 14SWG Aluminium  
Chassis Manufactured from 18SWG Mild Steel  
Covers Finished Orange  
Chassis Finished Matt Black

Order Code	Case B1M3000 OR
W250 D167.5 H 68.5 (Chassis 153mm Deep)	1480

**Plastic Boxes with Metal Lids** - Boss Industrial Mouldings  
Recessed Top Box  
ABS Base, C/W Brass Bushes, In Orange  
1mm Aluminium Top Panel Finished Grey

Order Code	Case B1M4003 OR	Case B1M4004 OR	Case B1M4005 OR
L85 W56 D29	97		
L111 W71 D42	130		
L161 W96 D53	182		

**Diecast Boxes** - Boss Industrial Mouldings  
Diecast Box and Flanged Lid  
Aluminium Box and Lid in Natural Finish

Order Code	Case B1M5003 NA	Case B1M5005 NA	Case B1M5006 NA
L113 W63 D31	104		
L152 W82 D50	181		
L192 W113 D61	280		

**Small Desk Consoles** - Boss Industrial Mouldings  
Slope Front Console, Recessed Top  
ABS Base, C/W Brass Bushes, In Orange  
1mm Aluminium Top Panel Finished Grey  
Ventilation Slots In Base

Order Code	Case B1M6005 OR	Case B1M6006 OR	Case B1M6007 OR
W105 D143 H32 (56)	206		
W170 D143 H32 (56)	271		
W170 D214 H32 (82)	375		

**All Metal Desk Consoles** - Boss Industrial Mouldings  
Slope Front Console, Recessed Top  
Top Piece All Aluminium Construction  
Ventilation Slots In Rear and Base  
Choice of 15°, or 30° Sloping Front  
Off White Top Panel, Blue Base

Order Code	Case B1M7151 A	Case B1M7156 A	Case B1M7158 A	Case B1M7301 A	Case B1M7303 A	Case B1M7306 A	Case B1M7308 A
W102 D140 H28 (51) 15° slope	1018						
W165 D211 H33 (76) 15° slope	1350						
W254 D287 H33 (76) 15° slope	1572						
W58 D287 H33 (76) 15° slope	1823						
W102 D140 H28 (76) 30° slope	1018						
W165 D183 H28 (102) 30° slope	1202						
W254 D259 H28 (102) 30° slope	1572						
W356 D259 H28 (102) 30° slope	1823						

**Eurocard Size Desk Console** - Boss Industrial Mouldings  
Slope Front Console  
ABS Case, C/W Brass Bushes, In Orange  
1mm Aluminium Top Panel, Finished Grey

Order Code	Case B1M8006 OR
W169 D127 H45 (70)	375

**P.C.B. Components**

Order Code	Pen 33PC
Dato Pen, Blue Ink, Slow Drying	92

**Fuseholders**

Order Code	Fuse/H20B	Fuse/H20C	Fuse/H20P	Fuse/H20T
Similar in Style to Fuse/H 20P Low Voltage Type Suits LES and M/F Bulbs.	8			
Panel Mounting, Screwdriver Slot	17			
Panel Mounting, Finger Release	77			
Panel Mounting, Finger Release	56			

**Fuses**

Order Code	Fuse 20	A/S Fuse 20
20mm x 5mm Glass.		
Quick Blow, Range 100mA - 5A	8	
Slow Blow, Range 250mA - 5A	22	

**Lampholders, Panel Mounting**

Order Code	Lamp LV	Lamp N
Similar in Style to Fuse/H 20P Low Voltage Type Suits LES and M/F Bulbs.	75	
Low Voltage, Red, Amber or Green	75	
Internal Neon 200/240V Red or Amber	95	

**Bulbs, Low Voltage, L.E.S.**

Order Code	Bulb LES
6V, 0.36W; 6.5V, 1W; 14V, 0.75W.	22

### RESISTORS

**Carbon Film, Fixed**

Order Code	Res RDx	Res RDx	Value
0.25W, E24 Values IRO-10M, 5% Tol.	1.5 ea.		90p/100 (Mult 10/Value)
0.5W, E12 Values IRO-4M7, 10% Tol.	2 ea.		1.25w/100 (Mult 10/Value)
		</	

- ACCESS
- BARCLAYCARD
- CASH
- CHEQUE

- FREEPOST ON ORDERS
- VAT INCLUSIVE PRICES \*
- ADD 30p P&P
- 24 HR TELEPHONE ANSWERING SERVICE

# GMT ELECTRONICS A

## Freepost Birmingham B19 1BR

TEL ORDERS WELCOME

\* DUE TO VAT INCREASE PLEASE ADD 5% TO ORDERS

### DIGITAL INTEGRATED CIRCUITS

4000 Buffered CMOS - High Speed

5-15V 'B' Series, Up to 20MHz

7400 T.T.L.

HEF4000	14	HEF4046	100
HEF4001	14	HEF4047	87
HEF4002	14	HEF4048	28
HEF4006	95	HEF4050	28
HEF4007	14	HEF4051	69
HEF4008	30	HEF4052	72
HEF4011	14	HEF4053	72
HEF4012	14	HEF4066	37
HEF4013	32	HEF4067	380
HEF4014	84	HEF4068	14
HEF4015	60	HEF4069	14
HEF4016	35	HEF4070	14
HEF4017	55	HEF4071	14
HEF4018	65	HEF4072	16
HEF4019	46	HEF4073	16
HEF4020	58	HEF4075	16
HEF4021	85	HEF4076	85
HEF4022	82	HEF4077	14
HEF4023	14	HEF4078	16
HEF4024	45	HEF4081	16
HEF4025	14	HEF4082	16
HEF4027	32	HEF4085	64
HEF4028	52	HEF4086	64
HEF4029	60	HEF4093	50
HEF4030	46	HEF4094	175
HEF4031	200	HEF4104	166
HEF4035	110	HEF4085	64
HEF4040	68	HEF4505	571
HEF4041	75	HEF4508	51
HEF4042	54	HEF4510	70
HEF4043	79	HEF4511	110
HEF4044	84	HEF4512	98

HEF4514	250	HEF4515	299
HEF4516	90	HEF4517	382
HEF4518	69	HEF4519	55
HEF4520	65	HEF4521	188
HEF4522	99	HEF4523	120
HEF4524	510	HEF4525	110
HEF4529	110	HEF4530	110
HEF4543	155	HEF4544	117
HEF4545	78	HEF4546	23
HEF4547	386	HEF4548	97
HEF4549	171	HEF4550	22
HEF4551	90	HEF4552	26
HEF4553	73	HEF4554	27
HEF4555	62	HEF4556	22
HEF4557	119	HEF4558	30
HEF4559	119	HEF4560	21
HEF4561	119	HEF4562	31
HEF4563	119	HEF4564	48
HEF4565	119	HEF4566	46
HEF4567	119	HEF4568	88
HEF4569	119	HEF4570	25
HEF4571	119	HEF4572	42
HEF4573	119	HEF4574	148
HEF4575	117	HEF4576	79

N7400N	9	N7400N	83
N7401N	11	N7401N	65
N7402N	11	N7402N	37
N7403N	11	N7403N	32
N7404N	12	N7404N	32
N7405N	12	N7405N	32
N7406N	25	N7406N	32
N7407N	27	N7407N	32
N7408N	13	N7408N	32
N7409N	13	N7409N	32
N7410N	11	N7410N	32
N7411N	18	N7411N	32
N7412N	17	N7412N	32
N7413N	26	N7413N	32
N7414N	23	N7414N	32
N7415N	23	N7415N	32
N7416N	22	N7416N	32
N7417N	22	N7417N	32
N7418N	22	N7418N	32
N7419N	22	N7419N	32
N7420N	11	N7420N	32
N7421N	26	N7421N	32
N7422N	27	N7422N	32
N7423N	22	N7423N	32
N7424N	30	N7424N	32
N7425N	30	N7425N	32
N7426N	22	N7426N	32
N7427N	22	N7427N	32
N7428N	30	N7428N	32
N7429N	21	N7429N	32
N7430N	21	N7430N	32
N7431N	30	N7431N	32
N7432N	30	N7432N	32
N7433N	30	N7433N	32
N7434N	21	N7434N	32
N7435N	21	N7435N	32
N7436N	21	N7436N	32
N7437N	21	N7437N	32
N7438N	21	N7438N	32
N7439N	60	N7439N	32
N7440N	12	N7440N	32
N7441N	40	N7441N	32
N7442N	40	N7442N	32
N7443N	79	N7443N	32

N74122N	39	N74122N	60
N74123N	37	N74123N	60
N74124N	32	N74124N	60
N74125N	32	N74125N	60
N74126N	32	N74126N	60
N74270N	32	N74270N	60

### LINEAR INTEGRATED CIRCUITS

CA3011	92	NE529K	162
CA3018	75	RC4136	130
CA3020	191	TBA120S	79
CA3028A	86	TC4580	346
CA3046	245	TC4740	450
CA3048	70	TDA1008	326
CA3080E	253	TDA1022	648
CA3130E	90	TDA1028	338
CA3140E	38	TDA1034B	217
CA3189E	266	TDA2581	286
LM301AN	30	TDA2640	292
LM308N	95	TL081CP	75
LM318N	200	TL084CN	140
LM319N	216	UA709CT	46
LM324N	70	UA709CN	40
LM339N	71	UA710CN	41
LM381N	110	UA711CN	65
LM381AN	180	UA711CT	42
LM382	120	UA741CN	18
		UA747CN	50
		UA748CN	35

### OPTO ELECTRONICS

Light Emitting Diodes, Individual		Order Code
125" (3mm)	Red	14 COY54
	Green	17 COY95
	Yellow	19 COY97
Panel Mounting Clip to suit.		3 LED3 Clip
2" (5mm)	Red	15 COY24A
	Green	17 COY94
	Yellow	19 COY96
Panel Mounting Clip to suit.		5 LED5 Clip
Light Emitting Diodes - 7 Segment Display		
3" (7.6mm) C. Anode R.H. Decimal Pt.	Red	160 XAN3061
	C. Anode R.H. Decimal Pt.	199 XAN3051
	C. Cathode R.H. Decimal Pt. Red, Low current drain	160 XAN3074
6" (15.2mm) C. Anode L.H. Decimal Pt. Red	Red	230 XAN6620
	C. Anode L.H. Decimal Pt. Green	230 XAN6520
	C. Cath	

# STEVENSON

## Electronic Components

### SOLDERING IRONS

ANTEX X25 (25W) or ANTEX CX (17W) 390p each  
Reel of solder (39.6M) 240p each

### LOUDSPEAKERS

56mm dia. 8ohms. 70p 64mm dia. 64ohms. 75p  
64mm dia. 8ohms. 75p 70mm dia. 8ohms. 100p  
Magnetic earpiece including 2.5 or 3.5mm plug. 15p each  
Crystal earpiece including 3.5mm plug. 30p each

### SWITCHES

Subminiature toggle. SPDT 70p. DPDT 80p  
Standard toggle. SPST 34p. DPDT 48p.



Slide switches (DPDT) miniature or standard 15p.  
Push to make switch. 15p. Push to break switch. 20p.

Wavechange switches: 1P12W, 2P6W, 3P4W, 4P3W. 43p

### CONTROL KNOBS


Ideal for use on mixers etc. Push on type with black base and marked position line. Cap available in red, blue, green, grey, yellow & black. 14p.



### MISCELLANEOUS

Connection cable available in single or stranded packs of eight colours.

	Single	Stranded
8 metre pack	18p	18p
40 metre pack	85p	80p

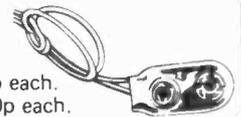

### BATTERY CLIPS

Battery clips for PP3 with lead. 6p each.  
Battery clips for PP9 with lead. 10p each.  
Miniature crocodile clips in red or black. 8p each.  
Red or black probe clips. 20p each.

### HEATSINKS

T018 push to fit heatsink	10p each.
T05 pushfit heatsink	9p each
T0220 twisted vane heatsink	20p each.
T03 twisted vane sink	22p each.




Murata Ultrasonic Transducers. 180p each. 350p pair.

### BOXES

Quality black ABS boxes by BIM. All dimensions in mm.  
100 x 50 x 25 90p each 150 x 80 x 50 140p each  
120 x 65 x 40 125p each 190 x 110 x 60 220p each

### REGULATORS

78L05 30p	7805 60p	7905 80p
78L12 30p	7812 60p	7912 80p
78L15 30p	7815 60p	7915 80p

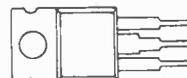

We now offer one of the widest ranges of components at the most competitive prices in the U.K. See catalogue for full details. We welcome callers at our shop in College Rd, Bromley, from Mon-Sat, 9am-6pm (8pm on Weds and Fridays). Special offers always available.

We also provide an express telephone order service. Orders received before 5pm are shipped same day. Contact our sales office now with your requirements.

TELEPHONE: 01-464 2951/5770.

Quantity discounts on any mix TTL, CMOS, 74LS and Linear circuits: 100+ 10%, 1000+ 15%. Prices VAT inclusive. Please add 30p for carriage. All prices valid to April 1980. Official orders welcome.



BARCLAYCARD & ACCESS WELCOME.

ORDERS  
DESPATCHED  
BY RETURN  
POST

Mail orders to: STEVENSON (Dept ET)

CMOS			
4001	13p	4025	13p
4002	13p	4026	90p
4007	13p	4027	28p
4009	30p	4028	45p
4011	13p	4029	50p
4012	13p	4040	55p
4013	28p	4041	55p
4015	50p	4042	55p
4016	28p	4043	50p
4017	47p	4046	90p
4018	55p	4049	25p
4050	25p	4060	80p
4066	30p	4068	13p
4069	13p	4070	13p
4071	13p	4072	13p
4081	13p	4081	13p
4093	36p	4510	60p
4511	60p	4511	60p
4518	65p	4520	60p
4528	60p		

FULL DETAILS IN CATALOGUE!

TTL			
7400	10p	7474	22p
7401	10p	7475	25p
7402	10p	7476	20p
7404	12p	7485	55p
7406	22p	7486	20p
7408	12p	7489	135p
7410	10p	7490	25p
7413	22p	7492	30p
7414	39p	7493	25p
7420	12p	7494	45p
7427	20p	7495	35p
7430	12p	7496	45p
7432	18p	74121	25p
7442	38p	74122	35p
7447	45p	74123	38p
7448	50p	74125	35p
7454	12p	74126	35p
		74127	35p
		74128	35p
		74129	35p
		74130	35p
		74131	35p
		74132	35p
		74133	35p
		74134	35p
		74135	35p
		74136	35p
		74137	35p
		74138	35p
		74139	35p
		74140	35p
		74141	55p
		74145	55p
		74148	90p
		74150	55p
		74151	40p
		74154	65p
		74157	40p
		74164	55p
		74165	55p
		74170	100p
		74174	55p
		74177	50p
		74190	50p
		74191	50p
		74192	50p
		74193	50p
		74196	50p
		74197	50p
		74199	90p

OPTO			
LED's	0.125in.	0.2in	each 100+
Red	TIL209	TIL220	9p 7.5p
Green	TIL211	TIL221	13p 12p
Yellow	TIL213	TIL223	13p 12p
Clips	3p	3p	
DISPLAYS			
DL704	0.3 in CC		130p 120p
DL707	0.3 in CC		130p 120p
FND500	0.5 in CA		100p 80p

SKTS					
8pin	8p	18pin	14p	24pin	18p
14pin	10p	20pin	16p	28pin	22p
16pin	11p	22pin	17p	40pin	32p
3 lead T018 or T05 socket. 10p each					
Soldercon pins: 100:50p 1000:370p					



PCBS			
Size in.	0.1in	0.15in	Vero
25 x 1	14p	14p	Cutter 80p
2.5 x 3.75	45p	45p	
2.5 x 5	54p	54p	Pin insertion tool 108p
3.75 x 5	64p	64p	
3.75 x 17	205p	185p	
Single sided pins per 100 40p 40p			
Top quality fibre glass copper board Single sided. Size 203 x 95mm 60p each			
'Dalo' pens. 75p each			
Five mixed sheets of Alfalac 145p per pack.			

RESISTORS			
Carbon film resistors. High stability, low noise 5%			
E12 series. 4.7 ohms to 10M. Any mix.			
0.25W	each	100+	1000+
0.5W	1p	0.9p	0.8p
	1.5p	1.2p	1p
Special development packs consisting of 10 of each value from 4.7 ohms to 1 Meg-ohm (650 res) £7.50. 0.25W £5.70.			
METAL FILM RESISTORS			
Very high stability, low noise rated at 1/4W 1%. Available from 51ohms to 330k in E24 series. Any mix:			
0.25W	each	100+	1000+
	4p	3.5p	3.2p

PLEASE WRITE FOR YOUR FREE COPY OF OUR 80 PAGE CATALOGUE OF COMPONENTS.

CONTAINS OVER 2500 STOCK ITEMS.

LINEAR			
LF356	80p	NE531	98p
LM301AN	26p	NE555	23p
LM308	60p	NE556	60p
LM318N	75p	NE567	100p
LM324	45p	RC4136	100p
LM339	45p	SN76477	230p
LM378	230p	TBA800	70p
LM379S	410p	TBA810S	100p
LM380	75p	TDA1022	620p
LM3900	50p	TL081	45p
LM3909	65p	TL084	125p
LM3911	100p	ZN414	80p
MC1458	32p	ZN425E	390p
MM57160	590p	ZN1034E	200p

TRANSISTORS			
AC127	17p	BCY72	14p
AC128	16p	BD131	35p
AC176	18p	BD132	35p
AD161	38p	BD139	35p
AD162	38p	BD140	35p
BC107	8p	BFY50	15p
BC108	8p	BFY51	15p
BC108C	10p	BFY52	15p
BC109	8p	MJ2955	98p
BC109C	10p	MPSA06	20p
BC147	7p	MPSA56	20p
BC148	7p	TIP29C	60p
BC177	14p	TIP30C	70p
BC178	14p	TIP31C	65p
BC179	14p	TIP32C	80p
BC182	10p	TIP2955	65p
BC182L	10p	TIP3055	55p
BC184	10p	ZTX107	14p
BC184L	10p	ZTX108	14p
BC212	10p	ZTX300	16p
BC212L	10p		
BC214	10p		
BC214L	10p		
BC477	19p	1N914	3p
BC478	19p	1N4001	4p
BC548	10p	1N4002	4p
BCY70	14p	1N4006	6p
BCY71	14p	1N5401	13p
		1N5402 ser	8p
		ITT Full spec. product.	
		1N4148	£1.40 100. £11 1000

DIODES			
2N2997	12p	2N3053	18p
2N3054	50p	2N3055	50p
2N3056	50p	2N3442	135p
2N3702	8p	2N3703	8p
2N3704	8p	2N3705	9p
2N3706	9p	2N3707	9p
2N3708	9p	2N3709	9p
2N3819	15p	2N3820	44p
2N3904	8p	2N3905	8p
2N3906	8p	2N4058	12p
2N5457	32p	2N5459	32p
2N5777	50p		

CAPACITORS			
TANTALUM BEAD			
0.1, 0.15, 0.22, 0.33, 0.47, 0.68, 1 & 2.2uF @ 35V			each 8p
4.7, 6.8, 10uF @ 25V			13p
22 @ 16V, 47 @ 6V, 100 @ 3V			16p
MYLAR FILM			
0.001, 0.01, 0.022, 0.033, 0.047, 0.068, 0.1			3p
			4p
POLYESTER			
Mullard C280 series			
0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1			5p
0.15, 0.22			7p
0.33, 0.47			10p
0.68			14p
1.0uF			17p
CERAMIC			
Plate type 50V. Available in E12 series from 22pF to 1000pF and E6 series from 1500pF to 0.047uF			
RADIAL LEAD ELECTROLYTIC			
63V 0.47 1.0 2.2 4.7 10			5p
	22	33	47
			7p
			13p
	220		20p
25V 10 22 33 47			5p
			8p
			10p
			15p
	220	470	23p

CONNECTORS			
JACK PLUGS AND SOCKETS			
	screened	unscreened	socket
2.5mm	9p	13p	7p
3.5mm	9p	14p	8p
Standard	16p	30p	15p
Stereo	23p	36p	18p
DIN PLUGS AND SOCKETS			
	plug	chassis socket	line socket
2pin	7p	7p	7p
3pin	11p	9p	14p
5pin 180°	11p	10p	14p
5pin 240°	13p	10p	16p
1mm PLUGS AND SOCKETS			
Suitable for low voltage circuits, Red & black. Plugs: 6p each Sockets: 7p each.			
4mm PLUGS AND SOCKETS			
Available in blue, black, green, brown, red, white and yellow. Plugs: 11p each Sockets: 12p each			
PHONO PLUGS AND SOCKETS			
Insulated plug in red or black 9p			
Screened plug 13p			
Single socket 7p Double socket 10p			



76 College Road, Bromley, Kent BR1 1DE.

# news digest.....

## MAIDEN STAR CHESS FINALS

Some time ago we received a colourful piece of fluorescent (or is it phosphorescent?) plastic in the post. An eerie green glow pervaded the office as we deciphered the strange hieroglyphs. They invited us to attend — wait for it — the Galactic, yes Galactic, finals of Star Chess, the TV game guaranteed to give a Grand Master a heart attack in 30 seconds flat.

When we arrived at the festival of cathode ray ballistics, we were instantly and eternally grateful to Colin Wild for designing the costumes which coffee and cream Star Maidens, Carolyn and Beverley, were in great danger of nearly wearing. It's truly amazing how a journalist's attention can wander from a six feet square telly screen so quickly.


Dr. Who's K-9 made a manly (dogly?) attempt at commenting on the final game, but I guess he's more familiar with multi-dimensional, hexagonal games with knobs on, because his speech circuits dried up after the first dozen moves (thank goodness). The final itself was relatively uneventful, neither player risking anything, his sights firmly set on the first prize of a trip to America (and back, of course). It was won by Peter Bond — one of our men at the Inland Revenue, God Bless him.

The fun began when the game finished, as we embarked on a tour of new games from Videomaster. On our way to the screens we noticed a novel chess set — the pieces were glasses of wine (red versus white) engraved with pawn, rook, etc. When you take a piece, you drain the glass. The two ladies who were deeply engrossed in the game seemed to be basing their strategy on how they could exchange the maximum number of pieces in the shortest possible time.

Meanwhile, we hogged the Videomaster Database—a new programmable TV game, including Black Jack, tank, horse racing, circus and boxing. However, we found the air-sea battle the most compelling. Other systems on show included sportsworld (ten games) and Colourscore 2 (six games). We'll tell you more about them just as soon as we can get hold of samples to play with (it keeps us off the streets).



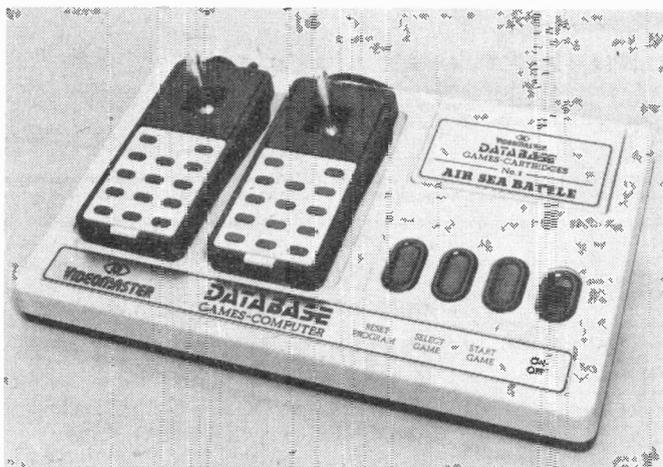The 1979 Star Chess Galactic Champion, Peter Bond, clutches his trophy, guarded by K-9 and Star Maidens, Carolyn and Beverley. The gent in the kilt is Cameron Macsween, managing director of Videomaster. The proceedings were overseen by Harry Golombeck, the Times chess correspondent.



## 'CHIPS AND BUGS'

The Economist has taken two tiny technologies with a big future and combined them in the latest of their excellent booklets.

Chips and Bugs, edited by Richard Casement, takes the microprocessor and biotechnology, two apparently unconnected fields, and brings you up to date with the latest developments. In fact they have three things in common. They both rely on studies of microscopic phenomena; they are controversial; and they rely less on building upon past developments than on fundamental discoveries at the frontiers of modern science.

The first half of the twenty page booklet deals with microcomputers — the technology, hardware, software, systems development and the superchips effect on our lives and jobs. The second half takes you from an explanation of the DNA building block to the intricacies of genetic engineering.

'Chips and Bugs' is £2.50 from The Economist Newspaper Ltd, 25 St James's Street, London SW1A 1HG. Hint: If you can get ten or more 'Chips and Bugs' fans together, The Economist will slash the price to £1.50 per copy for bulk orders.

## BOSSY LEDS

The BIM 33 and 34 from Boss, who have christened them BIMDICATORS, are front viewing, panel-mounting LED indicators.

Both devices use red, green or amber gallium phosphide LEDs, which have low current, low voltage characteristics, fast switching times and are fully IC compatible.

The BIM 33 has a nickel-plated brass body and is mounted in a 6mm hole, while the BIM 34 has a chromium-placed brass body and is mounted in an 8mm hole.

Further details from Boss Industrial Mouldings Ltd, Higgs Industrial Estate, 2 Herne Hill Road, London SE24 0AU.

## BLUE RESEARCH

Your choice of LED colours might include blue in the not so distant future. The new devices, being developed by Siemens, use silicon carbide and are predicted to have a forward voltage drop of 4 V at 50 mA.

# CHROMATHEQUE 5000

# POWERTRAN

## 5 CHANNEL LIGHTING EFFECTS SYSTEM

COMPLETE KIT

ONLY

**£49.50 + VAT!**



Panel size 19.0" x 3.5". Depth 7.3"

This versatile system featured as a constructional article in ELECTRONICS TODAY INTERNATIONAL has 5 frequency channels with individual level controls on each channel. Control of the lights is comprehensive to say the least. You can run the unit as a straightforward sound-to-light or have it strobe all the lights at a speed dependent upon music level or front panel control or use the internal digital circuitry which produces some superb random and sequencing effects. Each channel handles up to 500W and as the kit is a single board design wiring is minimal and construction very straightforward.

Kit includes fully finished metalwork, fibreglass PCB controls, wire, etc. — Complete right down to the last nut and bolt!


## MPA 200 100 WATT (rms into 8Ω) MIXER / AMPLIFIER

COMPLETE KIT

ONLY

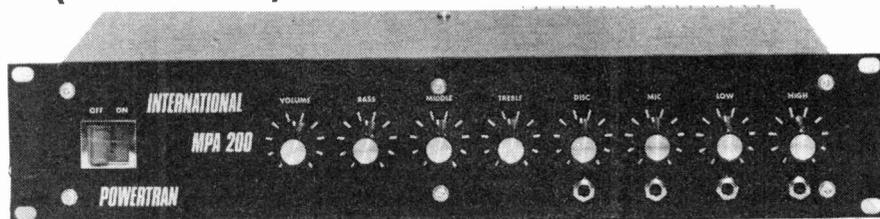
**£49.90 + VAT!**

**MATCHES THE  
CHROMATHEQUE 5000  
PERFECTLY!**



Panel size 19.0" x 3.5". Depth 7.3"

Featured as a constructional article in ETI, the MPA 200 is an exceptionally low priced — but professionally finished — general purpose high power amplifier. It features adaptable input mixer which accepts a wider range of sources such as microphone, guitar, etc. There are wide range tone controls and a master volume control. Mechanically the MPA 2000 is simplicity itself with minimal wiring needed making construction very straightforward. The kit includes fully finished metalwork, fibreglass PCBs, controls, wire, etc. — complete down to the last nut and bolt.

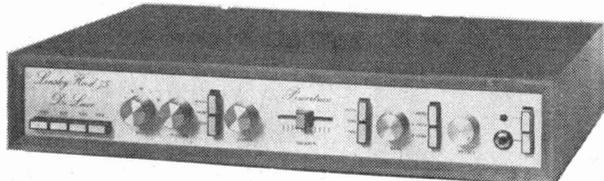


## DE LUXE EASY TO BUILD LINSLEY HOOD 75W STEREO AMPLIFIER £99.30 + VAT

This easy to build version of our world-wide acclaimed 75W amplifier kit based upon circuit boards interconnected with gold plated contacts resulting in minimal wiring and construction delightfully straightforward. The design was published in H-Fi News and Record Review and features include rumble filter, variable scratch filter, versatile tone controls and tape monitoring whilst distortion is less than 0.01%.


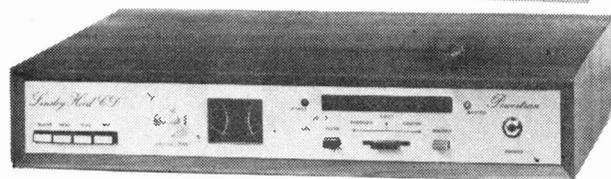
## WIRELESS WORLD FM TUNER £70.20 + VAT

A pre-aligned front-end module makes this Wireless World published design very simple to construct and adjust without special instruments. Features include an excellent a.m. rejection push-button station selection as well as infinitely variable tuning and a phase locked loop stereo decoder, incorporating active filters for "birdy" suppression.



## LINSLEY-HOOD CASSETTE DECK £79.60 + VAT

This design, published in Wireless World, although straightforward and relatively low cost provides a very high standard of performance. There are separate record and replay amplifiers and switchable equalisation together with a choice of bias levels are also provided. The mechanism is the Goldring-Lenco CRV with electronic speed control.

## T20+20 20W STEREO AMPLIFIER £33.10 + VAT

This kit, based upon a design published in Practical Wireless, uses a single printed circuit board and offers at very low cost, ease of construction and all the normal facilities found on quality amplifiers. A 30 watt version of this kit (T30+30) is also available for **£38.40 + VAT**.

**MATCHING TUNERS — SEE OUR FREE CATALOGUE!**

**COMPLETE KITS:** Our complete kits really are complete. All of the projects shown on this page are supplied with fully finished metalwork, ready assembled high quality teak veneer cabinet (last 4 kits on this page), or professional quality rack mounting cabinet (first 2 kits on this page), cables, nuts, bolts, etc., and full instructions — in fact everything!

All of the kits shown on this page are available as separate packs for those customers who wish to spread their purchase or perhaps make their own cabinets or metalwork. Prices are given in our FREE CATALOGUE.

**PRICE STABILITY:** Order with confidence. Irrespective of any price changes we will honour all prices in this advertisement until November 30th, 1979, if this month's advertisement is mentioned with your order. Errors and VAT rate changes excluded.

**EXPORT ORDERS:** No VAT. Postage charged at actual cost plus 50p handling and documentation.

**U.K. ORDERS:** Subject to 15% surcharge for VAT. No charge is made for carriage, or at current rate if changed.

**SECURICOR DELIVERY:** For this optional service (U.K. mainland only) add £2.50 (VAT inclusive) per kit.

**SALES COUNTER:** If you prefer to collect kit from the factory call at Sales Counter. Open 9 a.m. - 4.30 p.m. Monday-Thursday.



**OUR CATALOGUE IS FREE! WRITE OR PHONE NOW!**

# POWERTRAN ELECTRONICS

PORTWAY INDUSTRIAL ESTATE  
ANDOVER, HANTS SP10 3NM

ANDOVER  
(STD 0264) 64455




# news digest.....

## EXCLUSIVE — STAR WARS 2 LEAK

We've just received the first pictures of mechanical men from Star Wars 2, 'The Empire Strikes Back', to escape from their workshop (the pictures, not the mechanical men) somewhere in Hertfordshire. They arrived under plain cover (a brown envelope) by special messenger (GPO) from an anonymous reader.

R2-D2 peeps over the top of a work bench at the tall, dark handsome medical robot (microphone mouth), while an alien has a snooze in a plastic bag.

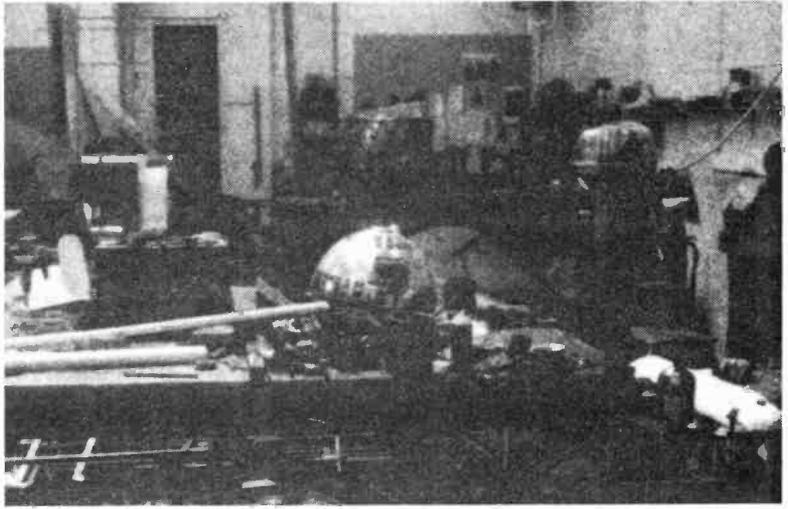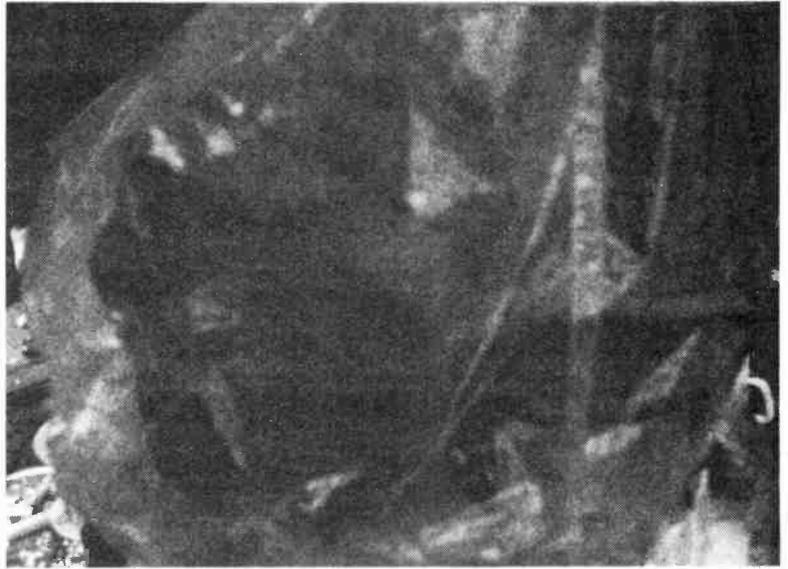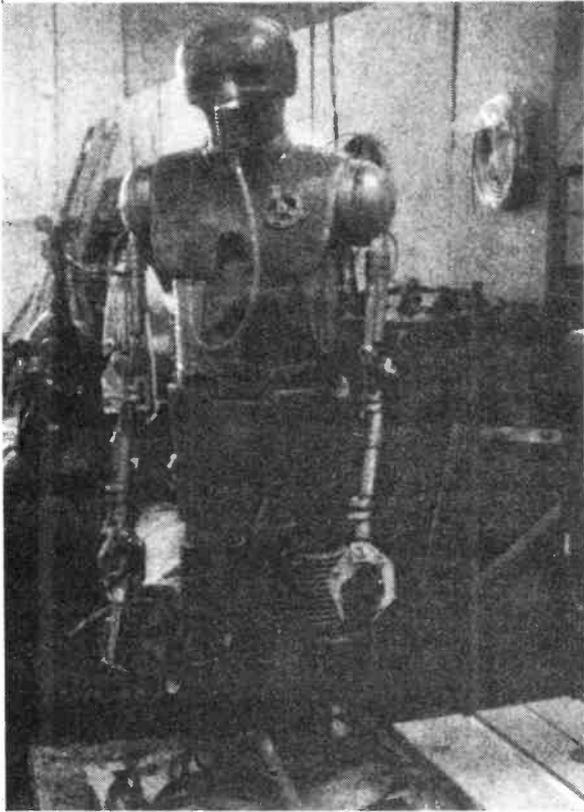Thank you Mr Anonymous, whoever you are. Can we have some more please? How about 'Alien' this time?



## ETISKI

As you can imagine we are invited to quite a few Press receptions, lunches, etc. to have a look at new products or meet people in the electronics industry.

This month our invitation-of-the-month award goes without a doubt to Sperry Univac, who are sponsoring the forthcoming first-ever World Water Ski Racing Championships. They decided to see how daft we really are by inviting us to have a bash at walking on water ourselves, while the British team was going through its paces in July. Thankyou Sperry, we would loved to have gone along, if only to see who else was mad enough to turn up and have a go.

The Championships will be held from September 9th to 16th at Whitstable in Kent,

Allhallows near the mouth of the Thames and the Welsh Harp Reservoir in London.

Sperry Univac will be providing a computerised results service throughout the event.



## PROGRAM REACTION

The NRC, the American nuclear watchdog, was happily watching its nuclear dogs when the telephone went.

The caller alleged that some nuclear plants were using a flawed design method, piping in the plants had been designed by invalid computer programs.

In March, the NRC closed five plants because it was unhappy about piping design. It is now studying the likelihood of damage due to earthquakes. If reactors remain closed indefinitely, the lights might start switching off in the areas served.

## TOP PROJECTS No 7

Have a look at the CCD Phaser circuit diagram on page 26. R31, 32 fix the voltage on IC5 pin 5 at 10V5. However, as they are labelled, pin 5 sits at a puny 1V5. To make IC5 feel better, make R31 10 k and R32 1k5.

# WATFORD ELECTRONICS

33/35 CARDIFF ROAD, WATFORD, HERTS, ENGLAND  
MAIL ORDER, CALLERS WELCOME.  
Tel. Watford 40588/9.

**ALL DEVICES BRAND NEW, FULL SPEC. AND FULLY GUARANTEED. ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/P.O.s OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS' OFFICIAL ORDERS ACCEPTED. TRADE AND EXPORT INQUIRY WELCOME. P&P ADD 30p TO ALL ORDERS UNDER £10. OVERSEAS ORDERS POSTAGE AT COST. AIR/SURFACE.**

**VAT** Export orders no VAT. Applicable to U.K. Customers only. Unless stated otherwise, all prices are exclusive of VAT. Please add 15% to all prices.

We stock thousands more items. It pays to visit us. We are situated behind Watford Football Ground. Nearest Underground/BR Station: Watford High Street. Open Monday to Saturday. Ample Free Car Parking space available.

**POLYESTER CAPACITORS:** Axial lead type. (Values are in  $\mu F$ )  
400V: 0.001, 0.0015, 0.0022, 0.0033, 0.0047, 0.0058, 0.01, 0.015, 9p; 0.018 10p; 0.022, 0.033, 11p; 0.047, 0.068 14p; 0.1 17p; 0.15, 0.22, 24p; 0.33, 0.47 42p; 0.68 53p, 1  $\mu F$  65p.  
160V: 0.039, 0.15, 0.22 11p; 0.33, 0.47 19p; 0.68, 1.0 22p; 1.5 29p; 2.2 32p; 4.7 48p.  
**DUBILIER:** 100V: 0.01, 0.015 20p; 0.022 22p; 0.047 26p; 0.1 38p; 0.47 48p.

**POLYESTER RADIAL LEAD** (Values in  $\mu F$ ) 250V: 0.068, 0.1 7p; 0.15 11p; 0.22, 0.33 13p; 0.47 17p; 0.68 19p; 1.0 22p; 1.5 30p; 2.2 34p.

**ELECTROLYTIC CAPACITORS:** Axial lead type (Values are in  $\mu F$ ) 500V: 10 40p; 47 68p; 250V: 100 65p; 63V: 0.47, 1.0, 1.5, 2.2, 3.3, 4.7, 6.8, 8, 10, 15, 22, 28p; 47, 32, 11p; 63, 100, 27p; 50V: 50, 100, 22p; 25p; 47p, 32p, 1000, 50p; 40V: 22, 33, 6p; 100, 12p; 2200, 30p; 85p; 470, 99p; 35V: 10, 33, 7p; 330, 47p, 32p; 1000, 50p; 25V: 10, 22, 47, 6p; 80, 100, 160, 8p; 220, 250, 13p; 470, 64p, 25p; 1000, 27p; 1500, 30p; 2200, 45p; 3300, 62p; 4700 74p; 16V: 10, 47, 68, 7p; 100, 125, 6p; 220, 33p; 14p; 47p, 16p; 1000, 150p, 20p; 2200, 34p; 10V: 1.0 6p; 640, 12p; 1000, 14p.

**TAG-END TYPE:** 450V: 100  $\mu F$  180p; 70V: 4700, 165p; 64V: 3300 130p; 2500 98p; 50V: 4700 150p; 3300 105p; 2200 99p; 40V: 15,000 399p; 4700 120p; 4000 92p; 3300 93p; 2500 85p; 10V: 4700 90p; 25V: 6400 105p; 4700 85p; 3300 80p; 2200 60p.

**TANTALUM BEAD CAPACITORS:** 35V: 0.1  $\mu F$  0.22, 0.33, 0.47, 0.68; 1.0, 2.2  $\mu F$  3.3, 4.7, 6.8, 25V: 1.5, 1.0, 70V: 1.5 18p; 100V: 1.5 13p each.  
14V: 15, 22, 25p; 47, 100, 220, 40p.  
10V: 15, 22, 33, 20p; 100, 35p.  
6V: 47, 68, 100, 30p; 3V: 100, 20p.

**MYLAR FILM CAPACITORS:** 100V: 0.001, 0.002, 0.005, 0.01  $\mu F$  6p; 0.015, 0.02, 0.04, 0.05, 0.056  $\mu F$  7p; 0.1  $\mu F$  9p, 0.2 11p, 50V: 0.47  $\mu F$  12p.

**CERAMIC CAPACITORS 50V**  
Range: 0.5pF to 10,000pF  
0.015  $\mu F$  0.022  $\mu F$  0.033  $\mu F$  4p  
0.047  $\mu F$  5p, 0.1  $\mu F$  6p, 0.2  $\mu F$  7p

**SILVER MICA** (Values in pF) 3.3, 4.7, 6.8, 10, 12, 15, 22, 33, 47, 50, 68, 75, 82, 85, 100, 120, 150, 220, 330, 470, 600, 800, 820, 250, 270, 300, 330, 360, 390, 470, 600, 800, 820, 16p each  
1000, 1200, 1800, 2000, 20p each

**POLYSTYRENE CAPACITORS:** 10pF to 1nF 8p; 1.5nF to 4.7nF 10p

**MINIATURE TYPE TRIMMERS**  
2.5-6pF, 3-10pF, 10-40pF 22p;  
5-25pF, 5-45pF, 60pF, 88pF, 30p

**COMPRESSION TRIMMERS**  
3.40pF, 10-80pF, 25-190pF 30p  
100 500pF 45p

**GAS & SMOKE DETECTORS**  
TGS 812 & B13 415p; Socket 25p

**JACKSONS VARIABLE CAPACITORS**  
Electronic 0.2-3.6pF with slow motion Drive 325p  
100 300pF 140p  
500pF 165p  
0.02 20B 176 285p  
1/2 Ball Drive with slow motion Drive 325p  
4511 DAF motor Drive 325p  
Dial Drive 4103 motor Drive 325p  
3 3p 650p 25 500p 175p  
Drum 54mm 31p 100 150pF 235p  
1-1.365uF 245p 3x310pF 495p  
RF 165pF 275p 0.03-2.5pF 430p

**RF CHOKES**  
1  $\mu H$ , 4.7, 10, 22, 33, 47, 100, 200, 470, 750, 1mH, 2.5, 5, 10, 35p each  
4.3mH, 100, 60p each

**VEROBOARD** 0.1 0.15 0.15 (copper clad) (plain)  
2 1/2 x 3 1/4" 46p 39p 24p  
2 1/2 x 5" 55p 50p 31p  
3 1/2 x 3 1/4" 55p 50p 31p  
3 1/2 x 5" 62p 67p 43p  
2 1/2 x 1 1/2" 169p 139p 92p  
3 1/2 x 1 1/2" 218p 180p 120p  
4 1/2 x 1 1/2" 280p 183p  
Pkt of 35 pins 22p  
Spot face cutter 99p  
Pin insertion tool 120p  
Dip BGARD (0166F) 268p  
VQ Board 90p  
Vero Group Board 1 60p  
S Board 1285p

**VERO WIRING PEN**  
Plus Spool 325p  
Spare spool (w/rel) 80p Combs 7p each

**FERRIC CHLORIDE**  
In bag & Myndrus 70p - 15p P&P

**DALO ETCH RESIST PEN** - sharp tip 75p

**COPPER CLAD BOARDS**  
Fibre Single Double SRBP  
Glass sided sided 8.5" x 8.5"  
6" x 6" 75p 90p 80p  
6" x 12" 130p 175p 80p

**SOLDERCON PINS**  
100 50p; 500 200p

**DIL SOCKETS (TEXAS) Low Wire prof. Wrap**  
8 pin 10p 25p  
14 pin 12p 35p  
16 pin 13p 45p  
18 pin 16p 52p  
20 pin 22p 65p  
22 pin 25p 70p  
24 pin 36p 78p  
28 pin 39p 85p  
36 pin 105p  
40 pin 50p 109p

**EDGE CONNECTORS:** Double type: 15  
+10 way 85p  
+13 way 99p  
+18 way 115p 120p  
+27 way 130p 135p  
+36 way 149p 160p  
+20 way 170p  
+26 way 194p  
+40 way 210p  
+43 way 232p

**DIODES**  
AA119 18  
AA215 15  
AA216 12  
BY126 12  
BY127 12  
CRO33 157  
CRO39 15  
OA47 12  
OA79 15  
OA81 15  
OA85 14  
OA90 7  
OA91 7  
OA95 8  
OA200 9  
IN914 4  
IN916 5  
IN4001/2 5  
IN4004/5 6  
IN4006/7 7  
IN4148 4  
IN5404 17  
IS44 20  
3A/100V 15  
3A/400V 20  
3A/600V 27  
3A/1000V 130

**BRIDGE RECTIFIERS**  
(plastic case) p  
1A/50V 20  
1A/100V 22  
1A/200V 25  
1A/400V 29  
1A/600V 34  
2A/50V 35  
2A/100V 44  
2A/200V 46  
2A/400V 53  
2A/600V 65  
4A/100V 72  
4A/200V 75  
4A/400V 79  
4A/600V 105  
6A/100V 73  
6A/200V 78  
6A/400V 85  
BY164 56  
VM18 DIL 40

**ZENERS**  
Range 2V to 39V 400mW  
8p each  
Range 3V3 to 33V 1.3W  
15p each

**NOISE Z5J 180**

**VARICAPS**  
MVAM115 140  
BA102 25  
BB104 40  
BB105 40  
BB106 40

**TRIACS**  
3A200V 49  
3A400V 50  
BA1100V 54  
8A400V 64  
8A800V 108  
12A100V 60  
12A400V 70  
12A800V 115  
16A100V 240  
16A400V 105  
16A800V 120  
25A500V 235  
25A800V 295  
T28000V 120

**DIAC**  
ST2 20

## TRANSISTORS

AC125	20	BC212L	10	BFX86	28	TIP34A	85	2N2221A	23
AC126	20	BC213	9	BFX87	28	TIP34C	110	2N2222A	20
AC127	20	BC214	11	BFY50	20	TIP35A	185	2N2303	45
AC128	20	BC214	9	BFY50	20	TIP35C	220	2N2368	21
AC141	38	BC214L	10	BFY51	20	TIP36A	220	2N2369A	15
AC142	24	BC307B	20	BFY52	20	TIP36C	255	2N2483	28
AC176	24	BC327	15	BFY64	40	TIP41A	63	2N2484	30
AC177	40	BC328	15	BFY71	20	TIP41B	73	2N2646	48
AC178	40	BC338	12	BRV39	20	TIP42A	64	2N2784	55
AC199	40	BC441	32	BS110	18	TIP42B	195	2N2904	22
AC200	40	BC461	36	BSX26	75	TIP47	199	2N2905A	22
AC211	40	BC477	25	BSY95A	18	TIP2955	65	2N2906	22
AC222	40	BC517	38	BU105	140	TIP3055	60	2N2907	22
AC278	40	BC547	12	BU205	190	TIS44	45	2N2907A	22
AC299	78	BC548	12	BU208	228	TIS45	45	2N2966	10
AC341	39	BC549C	13	ES567	65	TIS46	45	2N3011	24
AC44	39	BC556	15	MD8001	158	TIS90	20	2N3052	20
AD149	70	BC557	15	MJ4916	160	TIS91	24	2N3054	55
AD161	42	BC558	20	MJ2955	105	ZTX107	12	2N3055	48
AD162	42	BC559	20	MJ340	54	ZTX108	12	2N3108	32
AF114	50	BC70	15	MJ370	58	ZTX109	14	2N3442	140
AF115	50	BC71	15	MJ371	60	ZTX300	13	2N3663	26
AF116	50	BC72	20	MJE2955	99	ZTX301	16	2N3702	11
AF117	50	BD131	45	MJE3055	70	ZTX302	20	2N3703	11
AF118	55	BD132	45	MPF102	66	ZTX303	25	2N3704	11
AF139	35	BD133	43	MPF103	36	ZTX304	24	2N3705	11
AF178	70	BD135	38	MPF104	36	ZTX314	24	2N3706	11
AF186	50	BD136	40	MPF105	36	ZTX326	40	2N3707	11
AF239	42	BD137	40	MPF106	40	ZTX341	20	2N3708	11
AS221	60	BD138	50	MPSA05	25	ZTX500	15	2N3709	11
BC107	10	BD139	40	MPSA06	25	ZTX501	15	2N3710	16
BC107B	10	BD140	36	MPSA12	42	ZTX502	19	2N3711	16
BC108	10	BD144	198	MPSA55	25	ZTX503	15	2N3711	275
BC108B	10	BD145	198	MPSA56	25	ZTX504	25	2N3772	195
BC108C	12	BD205	110	MPSU06	56	ZTX531	25	2N3773	288
BC109	10	BD378	65	OC26	170	OC26	170	2N3819	22
BC109B	12	BD434	42	OC26	170	OC311	60	2N3820	45
BC109C	12	BD517	65	OC28	150	OC313	125	2N3823	95
BC117	20	BD695A	65	OC35	130	OC315	55	2N3866	90
BC119	28	BD696A	65	OC36	130	OC316	85	2N3903	20
BC140	35	BF115	34	OC41	48	OC42	48	2N3904	18
BC141	30	BF167	30	OC42	48	OC43	55	2N3907	62
BC143	30	BF180	35	OC43	55	OC44	55	2N3906	17
BC147	8	BF194	12	OC44	31	OC48	105	2N4037	52
BC147B	10	BF195	12	OC45	28	OC49	43	2N4058	17
BC148	8	BF196	12	OC70	28	OC71	28	2N4061	17
BC148B	10	BF197	14	OC71	28	OC72	45	2N4062	17
BC149	8	BF198	18	OC72	45	OC73	45	2N5172	25
BC149C	10	BF200	32	OC73	45	OC74	55	2N5179	60
BC153	27	BF224A	38	OC75	45	OC76	45	2N5191	70
BC154	27	BF244B	30	OC76	36	OC77	76	2N5305	40
BC157	10	BF256	60	OC77	76	OC81D	60	2N5457	32
BC158	10	BF258	60	OC82D	50	OC82D	50	2N5459	32
BC159	11	BF258B	50	OC83	48	OC84	44	2N5485	35
BC160	42	BF257	30	OC84	44	OC84	44	2N5777	45
BC167A	11	BF258	30	OC140	110	OC140	110	2N708	19
BC168C	12	BF259	30	OC141	110	OC141	110	2N708	19
BC169C	14	BF451	20	OC171	75	OC171	75	2N5930	18
BC170	18	BF501	35	OC210	45	OC210	45	2N5931	32
BC172	10	BF594	40	OC219	43	OC219	43	2N6122	22
BC177	18	BF595	38	TIP29C	56	TIP29C	56	2N1303	50
BC178	17	BF639	25	TIP30	64	TIP30B	64	2N1304	50
BC179	18	BF640	25	TIP30B	64	TIP30C	64	2N1305	28
BC182	9	BF641	28	TIP30C	64	TIP31A	62	2N1613	23
BC183	9	BF642	28	TIP31A	62	TIP31B	62	2N1614	150
BC184	10	BF643	28	TIP31C	62	TIP31C	62	2N1615	215
BC182L	10	BF644	28	TIP32A	58	TIP32A	58	2N1620	35
BC183L	10	BF645	28	TIP32B	58	TIP32B	58	2N2217	43
BC184L	10	BF646	28	TIP32C	58	TIP32C	58	2N2218A	34
BC187	28	BF648	26	TIP33C	105	TIP33C	105	2N2219A	26
BC187	28	BF648	26	TIP34	85	TIP34	85	2N2220A	22
BC187	28	BF648	26						


**TTL 74 (TEXAS)**  
7491 50  
7492 30  
7493 26  
7494 48  
7495 48  
7496 48  
7497 48  
7498 48  
7499 48  
7500 48  
7501 48  
7502 48  
7503 48  
7504 48  
7505 48  
7506 48  
7507 48  
7508 48  
7509 48  
7510

**WATFORD ELECTRONICS**

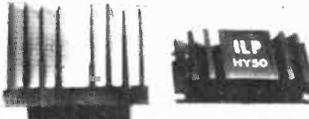**ILP MODULES 15-240 WATTS**

We are now stockists for these world famous fully guaranteed (2 years guarantee on all modules) Pre amps, Amplifiers & Power Supplies.

- HY5** Preamp. 500mV RMS **£4.75;** **HY120** Power Amp. 60W RMS/8Q **£15.40;**  
**HY30** Amplifier. 15W RMS/8Q **£4.95;** **HY200** Power Amp. 120W RMS/8Q **£18.50;**  
**HY50** Amplifier. 25W RMS/8Q **£7.25** **HY400** Power Amp. 240W RMS/4Q **£27.50.**




- POWER SUPPLIES**  
 PSU36 — Drives 2 x HY30s **£6.38**  
 PSU50 — Drives 2 x HY50s **£8.18**  
 PSU70 — Drives 2 x HY120s **£13.70**  
 PSU90 one HY200 **£13.70**  
 PSU180 2 x HY200 or one HY400 **£22.99**

**OHIO SUPERBOARD II Only £188.00**

Yes, we are now selling this popular single board microcomputer at the giveaway price of £188.00. Due to the recent devaluation of US Dollar against £ Sterling, we have been able to purchase a limited number of Superboards at lower price. Naturally, we wish to pass this price advantage on to our customers. Buy now to avoid disappointment should Mrs. Thatcher & Co. decide to devalue the Pound. Superboard II is supplied fully assembled and tested. Requires +5V at 3A and a Video Monitor or TV with RF Converter to be up and running (Data sheet supplied). We can also supply the RF Converter and Power Supply in Kit form or ready-built).  
 8K Microsoft BASIC in ROM 4K Static RAM — on BOARD expandable to 8K Full 53 Key Keyboard with Upper/Lower Case & User programmability and a lot more. See it for yourself. Continuous demonstration on at our retail shop.  
 Specially designed attractive fibreglass case also available **£25.00**

- SWITCHES**  
 TOGGLE 2A, 250V. **95p**  
 SPST **28p**  
 DPST **34p**  
 DPDT **38p**  
 4 pole on/off **54p**
- SUB-MIN TOGGLE**  
 SP changeover **59p**  
 SPST on/off **54p**  
 SPST biased **85p**  
 DPDT 6 tags **70p**  
 DPDT centre off **79p**  
 DPDT Biased **115p**
- SLIDE 250V:**  
 1A DPDT **14p**  
 1A DPDT c/over **15p**  
 1/2A DPDT **13p**  
 4 pole 2-way **24p**
- PUSH BUTTON**  
 Spring loaded SPST on/off **60p**  
 SPST c/over **65p**  
 DPDT 6 Tag **85p**
- MINIATURE**  
 Non Locking Push to Make **15p**  
 Push Break **25p**
- ROTARY:** Make your own multiway Switch. Adjustable Stop Shifting Assembly. Accommodate up to 6 Wafers **75p**  
 Mains Switch DPST to fit **34p**  
 Break Before Make Wafers. 1 pole/12 way **2p/6 way. 3p/4 way. 4p/3 way. 6p/2 way. 47p**  
 Spacer and Screen **5p**
- ROTARY: (Adjustable Stop)**  
 1 pole/2 to 12 way, 2p/2 to 6 way, 3 pole/2 to 4 way, 4 pole/2 to 3 way **41p**  
**ROTARY:** Mains 250V AC 4 Amp **45p**

# news digest .....

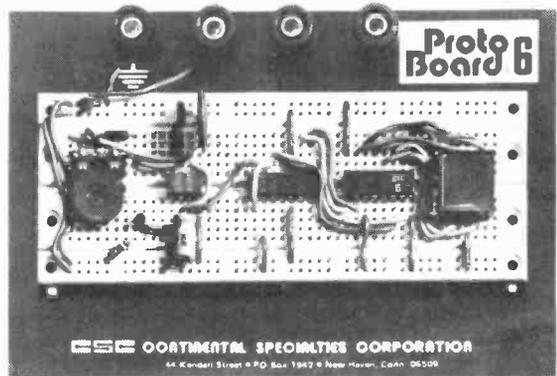

**CONTINENTAL BREAD**

Continental Specialties Corporation aim to get you from circuit diagrams to final designs in the cheapest and easiest way possible with their range of solderless breadboarding systems.


You can take your first plunge into breadboarding without wringing out your wallet, with the CSC Proto-board PB-6. For £9.20, you get a pre-assembled breadboard socket, two solderless bus strips, four 5-way binding posts all on a metal baseplate. Up to six 14-pin ICs can be accommodated on its 630 tie points.

Moving up the range, PB-100 gives you 760 solderless contact points. Other boards in the range also have built-in power supplies.

If you want to build an L-shaped circuit, you want CSC's Quick Test Sockets. Available in various sizes, they can be snapped together in any combination to produce a breadboard of any shape or size. It's as close to instant circuits as you'll get.

The Experimentor series of breadboards will snap together horizontally or vertically, if your circuit layouts are driving you up the wall. The range starts at £3.15 for Experimentor 350, offering 270 contacts. The Experimentor 650, at £3.60, and the 600 are the only breadboards on the market with full 4-terminal fan-out for microprocessors, clock chips, RAMs, ROMs and other large DIL packages. Also in the range, and particularly useful, is the Experimentor scratchboard — a pad of paper with a full-size layout of the hole and connection pattern of the breadboard. Your finished design can then be transferred to the Experimentor Matchboard, already drilled and etched to match the breadboard contact layout.

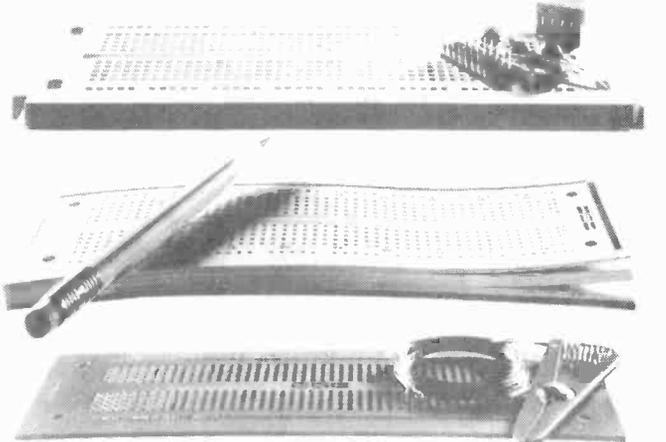CSC's new catalogue features their full range of breadboarding equipment and test instruments. Catalogues and further details of products are available from Continental Specialties Corporation, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ.



**CRYSTALS**

100KHz	385
455KHz	383
1MHz	323
1.6MHz	323
1.8MHz	323
1.0008M	395
1.8432MHz	362
2.4576MHz	362
3.2768M	323
4.032MHz	323
4.433619M	135
5.0MHz	355
6.5536M	208
7.680M	323
8.08333M	275
9.375M	323
10.0MHz	323
10.7MHz	323
12MHz	392
14.3181MHz	300
18MHz	323
18.432M	323
20.0MHz	323
27.648M	323
48.00MHz	323
100.00MHz	323

**TRANSFORMERS (Mains Prim. 220-240V)**

6.0-6V 9.0-9V. 12.0-12V 100mA	95p
8VA: 6V-5A 6V-5A 9V-4A 9V-4A 12V-3A	195p
12V-3A: 15V-25A 15V-25A	
12V: 4.5V-1.3A 4.5V-1.3A 6V-1.2A 6V-1.2A	
12V-5A 12V-5A 15V-4A 15V-4A 20V-3A	
20V-3A	220p (20p p&p)
24VA: 6V-1.5A 6V-1.5A 9V-1.3A 9V-1.3A	
12V-1A 12V-1A 15V-8A 15V-8A 20V-6A	
20V-6A	290p (45p p&p)
50VA: 6V-4A 6V-4A 9V-2.5A 9V-2.5A 12V-2A	
12V-2A 15V-1.5A 15V-1.5A 20V-1.2A 20V	
1.2A 25V-1A 25V-1A 30V: 8A 30V-8A	
100VA: 28V-0.28V-2A	650p (60p p&p)
100VA: 12V-4A 12V-4A 15V-3A 15V-3A	
20V-2.5A 20V-2.5A 30V-1.5A 30V-1.5A	
40V-1.25A 40V-1.25A 50V-1A 50V-1A 650p	
(60p p&p). (N.B. p&p charge to be added above our normal postal charge.)	

**ALUM. BOXES\* WITH LID**

3x2x1"	54
2 1/2 x 5 1/2 x 1 1/2"	72
4 1/2 x 1 1/2 x 1 1/2"	72
4 1/2 x 1 1/2 x 2 1/2"	72
4 1/2 x 1 1/2 x 3 1/2"	88
4 1/2 x 2 1/2 x 2 1/2"	72
4 1/2 x 2 1/2 x 3 1/2"	98
4 1/2 x 2 1/2 x 4 1/2"	98
4 1/2 x 2 1/2 x 5 1/2"	145
4 1/2 x 3 1/2 x 3 1/2"	185
4 1/2 x 3 1/2 x 4 1/2"	210
4 1/2 x 3 1/2 x 5 1/2"	175
4 1/2 x 5 1/2 x 3 1/2"	215
4 1/2 x 5 1/2 x 4 1/2"	265

**PANEL METERS\***

FSD 60x46x	
0-50mA	34
0-100mA	34
0-500mA	45
0-1mA	45
0-5mA	45
0-10mA	45
0-50mA	45
0-100mA	45
0-500mA	45
0-1A	45
0-2A	45
0-25V	45
0-50V	45
0-300V AC	45
"S"	45
"VU"	45
475p each	

**ETI Projects:**  
 Parts available for: Click Eliminator  
 Ambush; Guitar Effect Unit;  
 Audio Display;  
 DM900, Audio-ophile Amp.  
 60W Amplifier System.  
 Send SAE plus 5p for list.

**VOLTAGE REGULATORS**

1A TO3 +ve	-ve	
5V 7805 145p	7905 220p	
12V 7812 145p	7912 220p	
15V 7815 145p		
18V 7818 145p		
1A TO220 Plastic Casing		
5V 7805 80p	7905 90p	
12V 7812 80p	7912 90p	
15V 7815 80p	7915 90p	
18V 7818 85p	7918 90p	
24V 7824 85p	7924 90p	
100mA TO92 Plastic Casing		
5V 78L05 30p	79L05 65p	
6V 78L62 30p		
8V 78L82 30p		
12V 78L12 30p	79L12 65p	
15V 78L15 30p	79L15 65p	

**OPTO ELECTRONICS**

LEDs with Clips		
TIL209 Red	13	
TIL211 Grn	17	
TIL212 Yel	18	
TIL220 2" Red	14	
2 Green, Yellow or Amber	18	
Square LEDs: Red, Green, Yel	48	7 Segment Displays
TIL32 Infra Red	58	TIL312 3" CA 105
LS400	255	TIL313 3" CC 105
OCF71	120	TIL321 5" CA 115
ORP12	63	TIL322 5" CC 115
ORP61	85	DL704 3" CC 99
2N5777	45	DL707 3" CA 99
		DL747 6" CA 180
		FND357 Red 120
		3" Green CA 180
		6" Green CA 225
		95 LCD 3 1/2 Digit 875
		110 LCD 4 Digit 975

293	128	006	68	4045	145	4097	372	4515	459	4549	375
295	185	4007	14	4046	66	4098	99	3516	52	4553	398
298	168	4008	55	4047	87	4099	145	3517	382	4554	150
324	240	1009	30	4048	58	4160	78	3518	58	4555	46
325	290	4010	27	4049	25	4161	78	3519	55	4556	44
326	294	4011	18	4050	33	4162	78	3520	55	4557	365
327	286	4012	14	4051	45	4163	78	3521	228	4558	105
347	148	4013	35	4052	45	4174	82	3522	149	4559	375
348	186	4014	55	4053	45	4175	78	3526	65	4560	210
352	228	4015	63	4054	110	4194	90	3527	152	4561	65
353	228	4016	25	4055	99	4208	670	3528	55	4562	375
365	65	4017	60	4056	110	4209	670	3529	145	4566	155
366	65	4018	60	4057	1650	4410	670	3530	85	4569	280
367	65	4019	32	4059	480	4411	795	3531	135	4572	26
368	66	4020	70	4060	90	4412F	1250	3532	67	4580	595
373	180	40	52	4061	1200	4412V	1050	3534	575	4581	297
374	180	4022	50	4062	995	4415F	520	3536	365	4582	130
375	160	4023	14	4063	110	4415V	390	3538	142	4583	75
377	212	4024	40	4064	30	4419	280	3539	105	4594	63
378	184	4025	14	4067	280	4422	426	3541	135	4585	105
379	215	4026	100	4068	14	4433	780	3543	155		
384	86	4027	35	4069	14	4435	540				
390	230	4028	50	4070	14	4440	1275				
393	230	4029	54	4071	14	4450	260				
395	218	4030	50	4072	14	4455	220				
396	215	4031	150	4073	14	4457					
398	276	4032	80	4075	14	4490F	310				
399	230	4033	95	4076	57	4490	240				
445	150	4034	116	4077	14	4501	16				
447	144	4035	80	4078	14	4502	57				
449	180	4036	80	4081	14	4503	42				
668	182	4037	104	4082	14	4506	46				
669	182	4038	108	4085	52	4507	35				
670	248	4039	320	4086	52	4508	160				
		4040	51	4089	110	4510	55				
		4041	60	4093	35	4511	80				
		4042	50	4094	95	4512	70				
		4043	46	4095	48	4513	206				
		4044	46	4096	105	4514	140				

**UHF MODULATOR**  
 £2.50  
 UHF Modulator 8Meg Bandwidth special for Computer.  
 Thompson-CSF Ready Built and tested VDU Board **£69.00**

# Top value test equipment from TANDY

## LCD DIGITAL MULTIMETER.

Low-cost hand held digital multimeter with a full 3½ digit LCD display. 0.5% basic accuracy, auto polarity operation. 10 Mohm DC input impedance. Reading to ± 1999.




**Scales:**  
**DC volts:**  
 1mV to 1000V  
 (1% ± 1 digit accurate)  
**AC volts:**  
 1mV to 500V  
 (1% ± 2 digits accurate)  
**DC current:**  
 1µA to 200mA  
 (1% ± 1 digit accurate)  
**Resistance:**  
 10Ω to 20 MΩms  
 (1.5% ± 1 digit accurate)  
**Power source:**  
 9V battery or AC  
 with optional adaptor.  
**Size:**  
 155 x 75 x 30 mm.  
 22-198

**PRICE**  
**53.19**
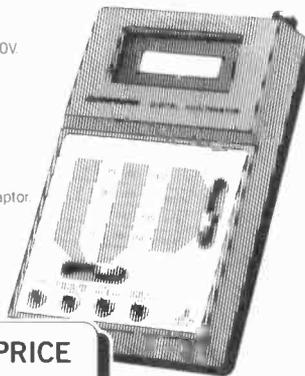
## LOW-COST LCD MULTIMETER COMPONENTS AND PARTS

A portable, compact sized multimeter with a full 3½ digit LCD display. Auto polarity operation, low battery indicator. 10 MΩ Input impedance.

**Scales:**  
**DC volts:**  
 2 20 200 1000V  
**AC volts:**  
 200 500V  
**DC current:**  
 2 20 200mA  
**Resistance:**  
 2 20 200  
 2000 KOHM  
**Power source:**  
 9V battery or AC adaptor.  
**Size:**  
 37 x 85 x 130 mm.  
 22-197




**PRICE**  
**39.93**

CAT No	DESCRIPTION	PRICE
276-032	LED	4 for 69p
276-033	LED	2 for 48p
276-034	LED	2 for 59p
276-142	Infra-Red Emitter Detector Pair	£1.37
277-1003	12V DC Automotive Digital Clock Module	£17.52
276-9110	6 pin edge connector for 277-1003	40p
276-1373	Power Transistor Mounting Hardware	50p
276-1363	TO-220 Heat Sink	60p
276-1364	TO-3 Heat Sink	81p
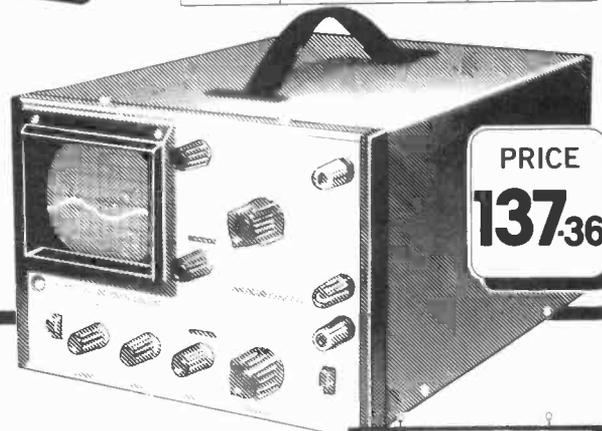
## AC/DC 8 MHz OSCILLOSCOPE

A new approved 8MHz version of last years' winner! The advance design features of this oscilloscope make it an absolute essential for industrial uses on production lines, in laboratories and schools. Ideal for radio and TV servicing, audio testing, etc.

**Specifications:**  
**Horizontal axis:** Deflection sensitivity better than 250mV/DIV. **Vertical axis:** Deflection sensitivity better than 10mV/DIV (1DIV = 6mm). Bandwidth 0.8MHz. **Input impedance:** 1MΩ parallel capacitance 35pF. **Time base:** Sweep range: 10Hz - 100kHz (4 ranges) Synchronization Internal. **Size:** 200 x 155 x 300mm. Supply 220-240 50Hz 22-9501.



**PRICE**  
**137.36**

You save because we design, manufacture, sell and service. Tandy have over 7,000 stores and dealerships worldwide. Over 2,500 products are made

specifically for or by Tandy at 16 factories around the world. The quality of our products has been achieved by over 60 years of continuous technological advancement.

KNOWN AS RADIO SHACK IN THE U.S.A. MAKERS OF THE WORLD'S BIGGEST SELLING MICROCOMPUTER TRS80

# TANDY

The largest electronics retailer in the world.

Offers subject to availability. Instant credit available in most cases.

OVER 170 STORES AND DEALERSHIPS NATIONWIDE.



## TANDY DEALER

Most items also available at Tandy Dealers. Look for this sign in your area.



Access. Barclaycard and Trustcard welcome

**Measure Resistance to 0.01Ω ...  
At a Price that has no resistance at all**

**New ELENCO PRECISION Digital Multimeter M1200B  
USA**

**ONLY £55** (£3 p&p + VAT £8.70 = £66.70)

**\*FULLY GUARANTEED  
FOR 2 YEARS**

**\*METAL CASE**

**\*EX STOCK DELIVERY**



**THE ULTIMATE IN PERFORMANCE –  
MEASURES RESISTANCE TO 0.01 OHMS,  
VOLTAGE TO 100 MICROVOLTS, CURRENT  
TO 1 MICROAMPS AT LOWEST EVER PRICE!**

**FEATURES**

- 3½ digits 0.56" high LED for easy reading
- 100μV, 1μA, 0.01Ω resolution
- High input impedance 10 Megohm
- High accuracy achieved with precision resistors, not unstable trim pots
- Input overload protected to 1000V (except 200mV scale to 600V)
- Auto zeroing, autopolarity
- Mains (with adaptors not supplied) or battery operation-built-in charging circuitry for NiCads
- Overrange indication
- Hi Low power ohms, Lo for resistors in circuit, Hi for diodes

**SPECIFICATIONS:**

DC Volts	Range 200mV, 2V, 20V, 200V, 1000V Accuracy 1% ± 1 digit, Resolution .1mV Overload protection 1,000 volts max
AC Volts	Range 200mV, 2V, 20V, 200V, 1000V Accuracy 1.5% ± 2 digits, Resolution .1mV Overload protection 1000V max, 200mV scale 600V
DC Current	Range 2mA, 20mA, 200mA, 2amp. Accuracy 1% ± 1 digit, Resolution 1 Microamp Overload protection – 2 amp fuse and diodes
AC Current	Range 2mA, 20mA, 200mA, 2 amp Accuracy 1.5% ± 2 digits, Resolution 1 Microamp Overload protection – 2 amp fuse and diodes
Resistance	Range 20, 200, 2K, 200K, 2 Meg, 20 Meg. Accuracy 1% ± 1 digit, Resolution .01 ohms
Environmental	Temp coefficient 0° to 30° C ± .025% °C Operating Temp 0° to 50° C Storage – 20° to 60° C
General	Mains adaptor: 6 - 9 Volts @ 200mA (not supplied) 4C size batteries (not supplied) Size 8 1/2 x 5 1/2 x 2 1/2      Weight 2 1/2 lbs.

To: Maclin-Zand Electronics Ltd  
1st Floor, Unit 10, East Block  
38 Mount Pleasant, London WC1X 0AP

Please send me ..... DMM M1200B  
@ **£66.70 inc. p&p + VAT (overseas £60)**  
I enclose cheque/PO/Bank Draft for £ .....

Name .....

Address .....

(BLOCK  
LETTERS  
PLEASE)

**ELENCO PRECISION** Sole UK Distributor

**ME** Maclin-Zand Electronics Ltd  
38 Mount Pleasant, London WC1X0AP

Tel. 01-837 1165  
Telex. 8953084 MACLING

© N Zand

# news digest.....



**IN-CAR COMPUTING**


There's a lot of it about. It's even happening in cars now — microprocessor control, I mean.

General Instrument Microelectronics have developed a clever little car brain based on its PIC 1655 single chip microcomputer. It's designed to replace speedometer, odometer and tripmeter (how far you've travelled since reset) functions. If you want to go mad and computerise everything in sight, there is sufficient on-chip memory to be allocated to other functions, such as water temperature, oil pressure, fuel, tachometer, etc.

Considering the wide variations in current car systems

requirements, it's not surprising that GI's system has been designed with a great deal of in-built flexibility. It can drive fluorescent discharge tubes, LED or LCD devices. Distances can be shown in kilometres or miles and pressure, temperature, fluid measures, etc can be displayed in metric or in good, old-fashioned pounds, bushels and inches.

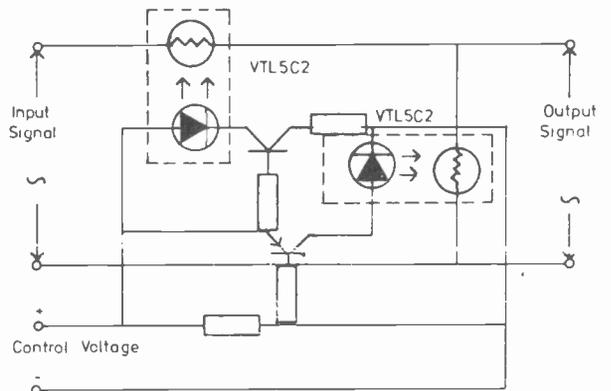GI claim that the system will save space and weight, and increase reliability and performance. Further details, specification, etc are available from General Instrument Microelectronics Ltd, Regency House, 1-4 Warwick Street, London W1R 5WB.



**NEVER SAY DIE**

Norbain claim that if you use their Vactrols properly (within their ratings) they have virtually unlimited life expectancy — the Vactrols, not Norbain.

Sounding like the baddie in a Sci-Fi saga, a Vactrol consists of an LED and a photoresistor in a common package. It provides high input-output isolation and low coupling capacitance (about 0.5 p).

One of the several types of audio attenuators possible is shown. The degree of attenuation is varied by adjust-

ment of the control voltage.

The distortion level for Norbain's VTL5 Vactrols is about 0.5% at IV rms, for a cell resistance of 3k, when using VTL5C4 or 7 types. It is reduced to less than 0.1% with a VTL5C2 and can be further reduced when using the VTL5C3 and 6 types under the same conditions.

Maximum attenuation with a single cell is 40 to 60 dB. Higher values can be achieved by cascading several stages.


For more information contact Norbain Electro-Optics Division, Norbain House, Arkwright Road, Reading, Berkshire RG20LT.



**Next  
Month**


# Hobby Electronics

## ELECTRONIC GAMES

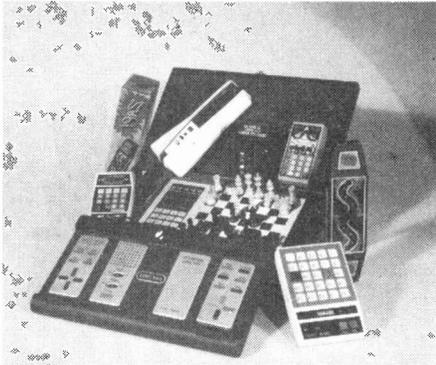

With one eye on Christmas we proudly present the HE review of electronic games. (We enjoy playing with them too). From the humblest hand-held to the most sophisticated video computer, the latest chess playing micros, they're all here next month.

## HOME COMPUTING

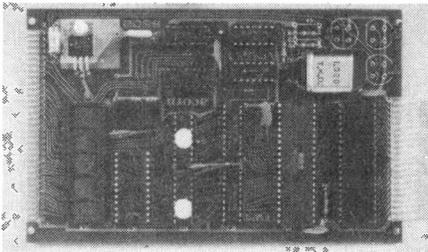


Sorry about the distinct lack of Computing this month, not to worry though, our resident computer expert Pete Howells takes a personal look at the current computer scene, what it's all about, what's happening now and what we can expect in the very near future.

## COMPETITION


We hope we will be able to bring you the results of our August picture competition in next month's HE.

## MICROWAVE COOKING

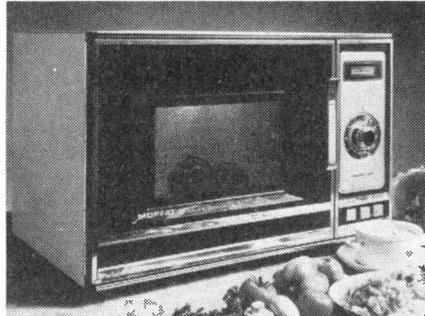

What's all the fuss about? Chances are it's because most people don't understand Microwave cookers, they've never gained the wide acceptance they deserve in this country. Next month one of the countries leading authorities on microwaves looks at what makes them tick, just how can a Chicken cook in 30 minutes, or a Hamburger in 5? Find out next month.

## AUDIO ANALOGUE FREQUENCY METER

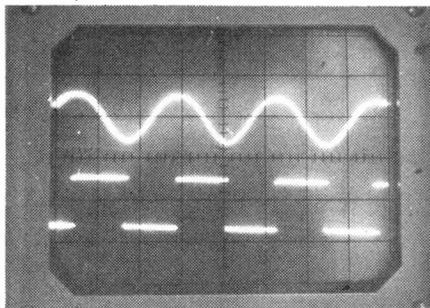

Some people seem to think that unless its got a digital its old-fashioned. We will prove them wrong with this beautifully designed piece of test equipment. The circuit is extremely simple to build yet will give a highly accurate readout of frequencies within the audio range.

If built and calibrated correctly this very useful piece of test equipment should prove to be invaluable for servicing, troubleshooting and experimental purposes. No need to guess anymore.

## HOBBYTUNE

We sat around for ages trying to think of a name for this musical project, nothing seemed to do it justice. See what you think about this stylus operated, miniature organ. We won't promise it'll turn you into a virtuoso overnight but we would be surprised if you're not playing tunes in just a couple of minutes. The HOBBYTUNE has many of the features found on instruments costing three or four times as much to buy, a great project for the kids, it must be better than buying them a drum for Christmas.

## MULTI OPTION SIREN



Yes folks, it's annoy the neighbours time again. Now you can plague them with a variety of different siren noises, yes before you ask, it will sound like an American police siren, but not only that, like a lot of other sirens too. Not recommended for people of a nervous disposition.

## HE TANTRUM



We think the wait will be worthwhile, the Tantrum is a really superb piece of design work. We've incorporated a facility for remote control, (coming up soon) so not only will you be able to enjoy your favourite music from the comfort of your armchair you'll be able to control it as well. Again apologies for its absence this month, they do say it makes the heart grow fonder.

**The October issue will be on sale September 14th**

The items mentioned here are those planned but circumstances may affect the actual contents

## Arresting Motion

As the name suggests, a satellite in a geostationary orbit appears to hold its position in the sky over the same spot on the Earth's surface. It is, of course, orbiting the Earth as any other satellite does, but at an altitude of nearly 36000 km, in a circular orbit, it keeps pace with the Earth's rotation and so appears to be stationary.

## Around The World In 90 Minutes


From TIROS-9 onwards satellites have also been launched into polar orbits, with a period of 1½ to 2 hours. The satellite orbits in the same plane, with the Earth rotating beneath it. The ground track of each orbit is some 28 degrees to the west of the previous one. Each spot on the Earth's surface is overflown twice a day, once at night and once during daylight hours. Two imaging systems are used. Visible light pictures are taken during daylight and infra-red at night.

## Clearly IR


Infra-red sensors on the spacecraft can monitor temperatures from sea level up to the highest cloud. High cloud is the coldest and tropical sea the warmest. Light grey or white patches on the familiar black and white weather pictures of the UK, now a regular feature of television weather forecasts, are the colder cloud areas. Darker areas are the warmer land and sea masses. Coastlines will show clearly if there is sufficient difference in temperature between land and sea. In general, infra-red pictures show more detail than those taken by visible light, as they successfully avoid the problems of reflected glare from cloud tops and ground shadows from thick cloud.
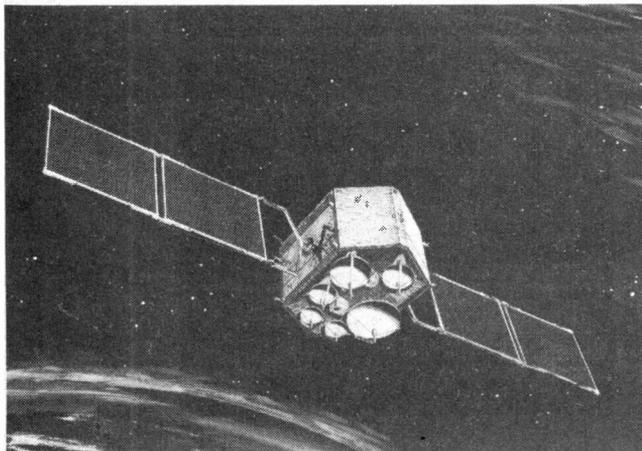
## Communications — The Early Days

It all started with Telstar in 1962. During each orbit of about five hours, Telstar and the succeeding Relay could only provide simultaneous visibility from both sides of the Atlantic for about 45 minutes. The Syncom series of satellites in 1963 explored the possibility of building a system from a small number of satellites in geostationary orbits. Syncom also showed that minor perturbations in a satellite's orbit, due to the non-uniformity of the gravitational sea in which it floats, could be rectified by the use of small correcting gas jets.



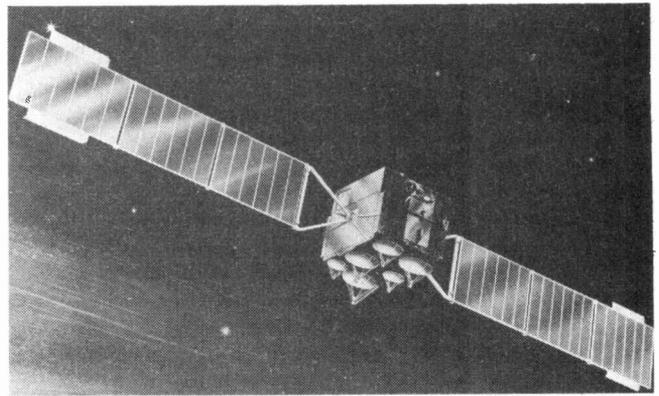OTS-2, the forerunner of the European Communications Satellite, is intended to provide pre-operational capacity until ECS begins operations in 1981/2.



The European Communications Satellite (ECS) will carry a large proportion of European telephone, telex and television traffic.

## Delay Fears

One fear, which never materialised, was that the increase in transmission time when bouncing telephone conversations off high altitude satellites would be unacceptable. The one way delay is a little over a quarter of a second. In 1964, Early Bird (later to become known as Intelsat 1) showed that the delay, inherent in the system, was not a serious problem.

Intelsat is an important name in the short history of communication satellites. In 1969, three Intelsat-3 satellites established the first global communications network. Even before the launch of Telstar, the Earth to satellite (uplink) and satellite to Earth (you guessed it — downlink) frequencies had been carefully selected. Below about 1 GHz ( $10^9$  Hz) galactic background noise is a significant factor. Below about 0.5 GHz it exceeds atmospheric noise. Above 10 GHz atmospheric noise rises steeply, moreso in heavy rain. The frequencies chosen then and adopted for the Intelsat programme were, therefore, between 1 and 10 GHz — 6 GHz for the uplink, 4 GHz for the downlink.


Britain is playing a particularly active role in satellite communications. British contractors contributed to the Intelsat 3, 4 and 4A programmes and British Aerospace is currently involved in the Intelsat 5 system, due to become operational in 1980.

## European Communications

In May 1978, the European Space Agency's Orbital Test Satellite (OTS) was launched. It will test transmission techniques and prove the performance and reliability of on-board equipment in space. This is the forerunner of its operational successor, the European Communications Satellite (ECS) — a regional satellite communications system. It will be capable of carrying a significant proportion of future European telephone, telex and television traffic. OTS-2 will also provide adequate pre-operational traffic capacity. Two ECS spacecraft should become operational in 1981/82. Two maritime versions of ECS, to be known, not surprisingly, as MARECS, are also scheduled for launching in 1981/82. MARECS is planned to provide direct telephone and telex links between ships and shore stations in the UK and elsewhere.
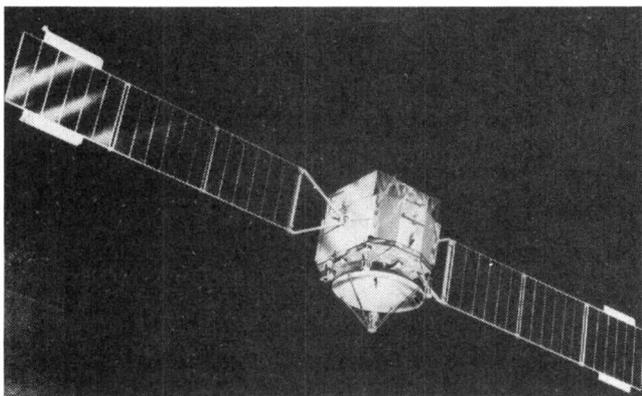
## Radio Piggy Back

In October 1978, the 1045th Cosmos satellite was placed in Earth orbit. It carried two smaller satellites called Radio 1 and 2, designed and built by radio hams.



**MARECS, a marine version of ECS, is intended to provide communications links between ships and shore stations.**

Radio 1 and 2 use frequencies in the two and ten metre amateur bands and are intended for use by both American and Soviet radio hams, complementing the service already provided by America's Orbiting Satellite Carrying Amateur Radio (OSCAR) satellites.

## Active Limits And Passive Freedom

There are two basic types of navigational system — active and passive. In an active system, the user has to interrogate the satellite(s) to determine his position. That necessarily limits the number of people who can use the system, because each satellite has a finite number of communications channels available at any time.

A passive system, however, relies on ground stations receiving continuously transmitted signals from the satellite(s) and then calculating position from them. It has the advantage that there is no limit to the number of users who can listen in to the satellite transmissions.

The capacity to fix position continuously is not available with the US Navy's Transit system, even with six satellites in operation. Transit is, therefore, not suitable for air traffic control, as an aircraft could travel a considerable distance between fixes. Also, as Transit uses a Doppler technique, the speed of an aircraft affects the measurement of the frequency shift.

Throughout the seventies, the system has been updated and improved. However, expansion of Transit has been dropped in favour of a new system, NavStar, which should be fully operational by about 1985 and will be suitable for use by aircraft.

## Home Sweet Home

A major part of Earth satellite applications is concerned with turning the cameras and sensors back towards mother Earth to find out more about this lump of rock that is our home. This field of self-interest can be split into two related and overlapping areas — Earth resources and research satellites.

On the 26th of April 1978, an Applications Explorer Mission satellite (AEM-1) was launched from Vandenberg to measure day and night temperature differences on the Earth's surface. This is the first of NASA's Explorer missions. The second, AEM-2, followed it into orbit on February 18th, 1979. The spacecraft were both of a modular design to keep costs down.

AEM-1, the Heat Capacity Mapping Mission (HCMM), will determine the feasibility of using data from thermal

infra-red sensors for:

- discrimination of rock types and possibly location of minerals
- monitoring surface soil moisture changes
- measuring plant canopy temperatures
- measuring urban heat islands
- measuring land and sea surface temperature changes
- predicting water run-off from snow field information

The results will also be correlated with Landsat data and ground observations.

## Military Embryo


The early development of the American satellite programme was *entirely* in military hands, for obvious reasons. The motivation then was a belief in the axiom of conventional warfare that says, 'he who holds the high ground, controls the battlefield.' The military objective was the high ground — Earth orbit.

## The Spy In The Sky

Satellites have been used for military reconnaissance since 1959, with the launch of the first of the Discoverer series, designed by Lockheed. In addition to the use of visible light photography to monitor ground operations, infra-red sensors can be used to detect, for example, heat from aircraft engines or local changes in sea temperature caused by submarines manoeuvring close to the surface or by surface craft manoeuvring at night.

It's difficult to estimate how many Soviet satellites are launched for military reconnaissance purposes, as most go by the 'family' name of Cosmos, whatever their application. However, information about their orbits and duration of flight can be used to deduce their possible applications.

In June 1971 a Titan 3D launch vehicle, capable of putting over 13 tonnes into a polar orbit, lifted a 'Big Bird' low altitude surveillance platform into a Sun-synchronous orbit. The Sun-synchronous orbit ensures that when the spacecraft overflies the target again and again, the Sun angle is always the same. That makes it much easier to compare photos of the same site and detect movements of troops, vehicles, missile launching sites, etc. ▶

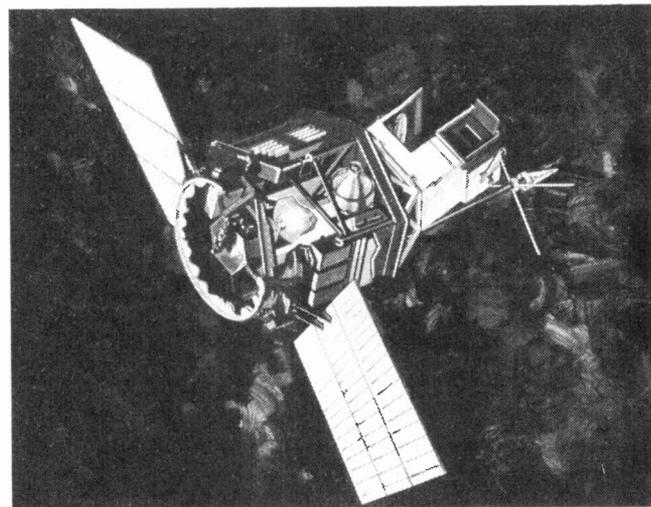

**An engineer's conception of AEM-1, a heat capacity mapping mission (HCMM) spacecraft and the first of the NASA's Applications Explorer Missions. The hexagonal shaped base module for this spacecraft, launched in April 1978, was built for the NASA/Goddard Space Flight Center by the Boeing Aerospace Company of Seattle, Washington.**

Soviet satellites are generally recovered intact and the film removed on the ground, but American satellites remain in orbit, while a number of film magazines in protective capsules are ejected. They re-enter the Earth's atmosphere and begin their descent to the surface on parachutes but, long before they get there, they are collected by specially equipped military aircraft.

In the early years of military satellites, once a spacecraft reached its position in Earth orbit, it was relatively safe. However, recent years have seen the development of hunter-killer spacecraft. Search and find craft have been used before to locate targets for photoreconnaissance. More sinister is the hunter-killer craft, which manoeuvres close to a target spacecraft and then explodes. Just how many of these are active and already in Earth orbit is a matter for conjecture. There have also been reports of spy satellite cameras being 'blinded' by intense flashes of laser light. As they say, 'all's fair in love, war and spying.'

## Outward To Deep Space

If the sensors can be pointed down towards Earth, they can equally be pointed out into space. The greatest contribution of the satellite to near-Earth research has been the capacity to make on-the-spot measurements of parameters which previously could only be estimated by indirect means.

Britain has been particularly active in this field with the Ariel series. The satellites were called UK 1, 2, etc. until they achieved successful operational orbit, when they were renamed Ariel 1, 2, etc. Ariel 1 and 2, launched in 1962 and 1964 respectively, had substantial American involvement, but Ariel 3, launched in 1967, was the first satellite to be entirely designed and built in Britain. It was a very successful system, which operated for two years — twice its designed lifetime. British Aerospace was the principle contractor.


The latest of the series, Ariel 6, was successfully launched in June this year.

## The X-Ray Sky

NASA has focused its attention on X-ray sources in the sky with its high energy astronomy programme. The first High Energy Astronomy Observatory (HEAO-1) made a general X-ray sky survey and identified approximately 1500 sources. Precise altitude control is essential for astronomical observations. HEAO-1's mission came to an end, therefore, when its supply of altitude control gas ran out in January this year. HEAO-2, launched in November 1978, can be pointed at selected X-ray sources. A third HEAO is scheduled for launch this year. The satellites are placed in low circular orbits, but their altitude allows them to detect radiation which would not reach the Earth's surface.
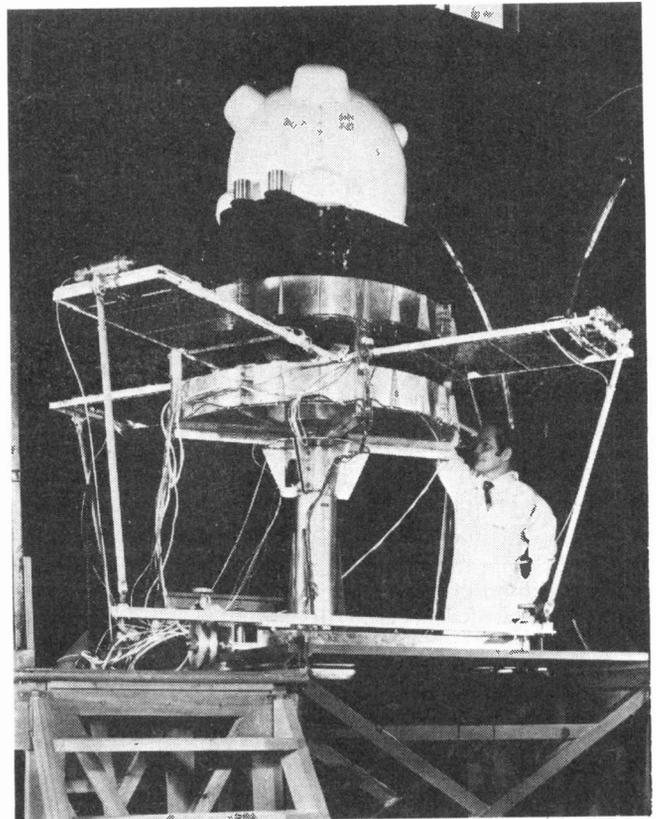
## The Future

The immediate future should bring improved communications and navigation by satellite as more powerful systems are launched to give global coverage. The, by now familiar, sight of a launch rocket slowly lifting off a pad, carrying its payload towards Earth orbit will inevitably become much rarer. The Space Shuttle will be the first of a generation of reusable spacecraft, which will gradually replace 'one-off' rockets.



**Ariel 6 will spend the next two years orbiting the Earth every 96 minutes, studying the ultra-heavy component of cosmic radiation and investigating X-ray sources.**

## Power From Orbit

When the oil wells finally dry up, we may supplement our energy requirement by building huge solar arrays in orbit and transmitting the collected power to Earth by microwave. The transmission of power by microwave has already been proven over short distances. You'll find more about power satellites in the August edition of Hobby Electronics.


Whatever the future *does* hold for satellites and their applications, it boils down to how much money governments are prepared to spend on space research. That begs the question — how do you value the returns from space? What price do you put on better weather forecasting, clearer and easier communications, improved air traffic control, etc? As if that wasn't a complex enough question, it doesn't stop there. Whether or not to embark on or continue an existing satellite programme is also inextricably tied up with national prestige, international relations, employment, high technology experience which can be translated to other fields of engineering and electronics . . . . shall I go on? In the long term, your crystal ball is as good as mine.

**ETI**


*I would like to express my thanks to the following for their assistance in preparing this article:*  
British Aerospace  
The Boeing Aerospace Company, Seattle
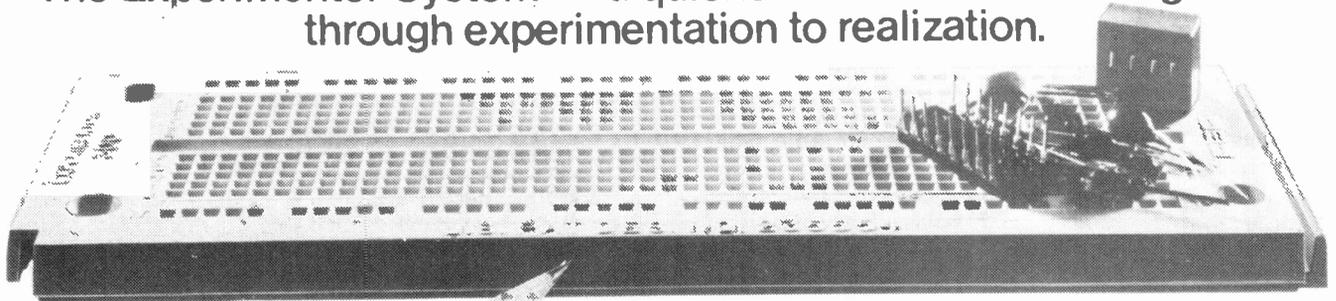
# You can't beat The System.


The Experimentor System™ — a quicker transition from imagination through experimentation to realization.



Experimentor solderless breadboard.

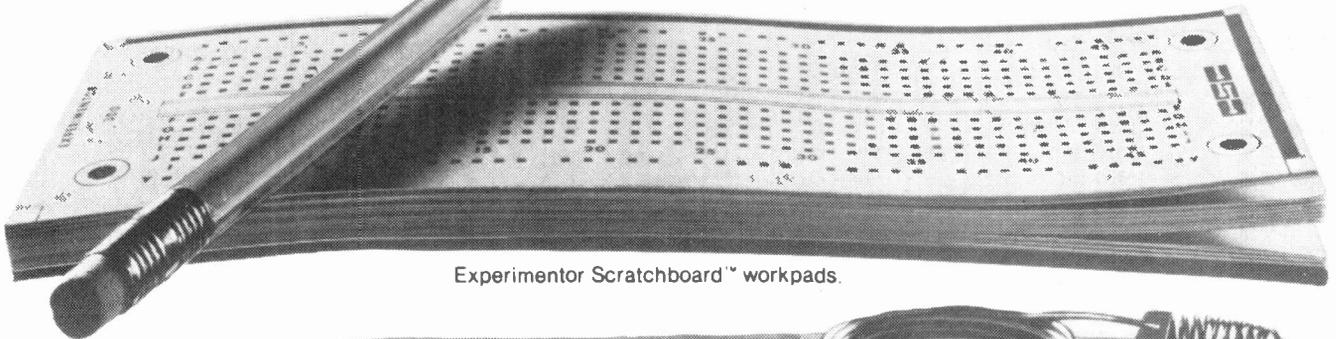

Experimentor Scratchboard™ workpads.

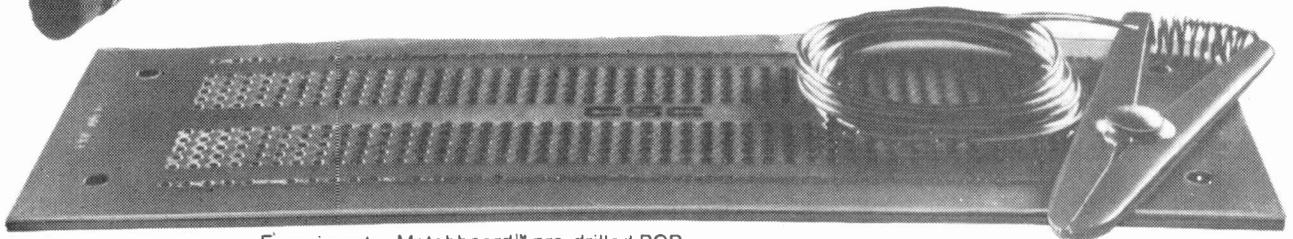

Experimentor Matchboard™ pre-drilled PCBs.

When you have a circuit idea that you want to make happen, we have a system to make it happen quicker and easier than ever before: The Experimentor System.

You already know how big a help our Experimentor solderless breadboards can be. Now we've taken our good idea two steps further.

We've added Experimentor Scratchboard workpads, with our breadboard hole-and-connection pattern printed in light blue ink. To let you sketch up a layout you already have working so you can reproduce it later.


With Experimentor Matchboard you can go from breadboard to the finished product nonstop! We've matched our breadboard pattern again, this time on a printed circuit board, finished and ready to build on. All for about £1.32.

There's even a letter-and-number index for each hole, so you can move from breadboard (where they're moulded) to Scratchboard™ (where they're printed) to Matchboard™ (where they're silkscreened onto the component side) and always know where you are.

When you want to save time and energy, you can't beat The Experimentor System.

1. EXP-300PC, which includes one item: A Matchboard pre-drilled PCB **£1.32**      2. EXP 302 which includes three items: Three 50-sheet Scratchboard workpads **£1.68**      3. EXP 303 which includes three items: Two Matchboards and an EXP 300 solderless breadboard **£8.60**      4. EXP 304 which includes four items: Two Matchboards, an EXP-300 breadboard and a Scratchboard workpad **£9.30**

CONTINENTAL SPECIALTIES CORPORATION

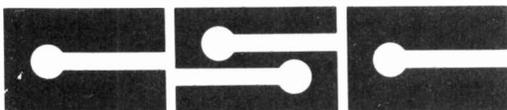

EUROPE, AFRICA, MIDEAST: CSC UK LTD.  
Dept. 9W  
Shire Hill Industrial Estate Units 1 and 2  
Saffron Walden, Essex CB 11 3AQ  
Telephone: SAFFRON WALDEN (0799) 21682  
TLX 817477

CONTINENTAL SPECIALTIES CORPORATION, DEPT. 9W

Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex

Name \_\_\_\_\_

Address \_\_\_\_\_

Inc P&P and 15% VAT

1. EXP 300PC <b>£2.38</b>	Qty. Reqd.	2. EXP 302 <b>£2.79</b>	Qty. Reqd.	FREE Catalogue tick box <input type="checkbox"/>
3. EXP 303 <b>£11.04</b>	Qty. Reqd.	4. EXP 304 <b>£11.85</b>	Qty. Reqd.	I enclose cheque PO for

£ \_\_\_\_\_

Phone your order with Access, Barclaycard or American Express

Card No. \_\_\_\_\_ Expiry date \_\_\_\_\_

# BI-PAK

**SEMICONDUCTORS SEND YOUR ORDERS TO  
DEPT ETI 9, PO BOX 6, WARE, HERTS.  
VISIT OUR SHOP AT: 3 BALDOCK ST, WARE, HERTS.**

## TRANSISTORS

AC126	£0.21	BC148	£0.08	BC549	£0.12	BU105	£1.84	ZTX109	£0.11
AC127	£0.21	BC149	£0.08	BC550	£0.16	BU105/02	£2.24	ZTX300	£0.13
AC128	£0.18	BC150	£0.12	BC556	£0.18	BU204	£1.81	ZTX500	£0.14
AC128K	£0.30	BC151	£0.12	BC567	£0.15	BU205	£1.81	2N1613	£0.23
AC132	£0.23	BC159	£0.12	BC558	£0.14	BU208/02	£2.58	2N1711	£0.23
AC134	£0.23	BC167	£0.14	BC559	£0.16	MJE2955	£1.04	2N1889	£0.51
AC137	£0.23	BC168	£0.14	BD115	£0.58	MJE3055	£0.69	2N1890	£0.51
AC141	£0.25	BC169	£0.10	BD116	£0.92	MJE3440	£0.80	2N1893	£0.35
AC141K	£0.38	BC169C	£0.12	BD121	£0.76	MPF102	£0.32	2N2147	£0.86
AC142	£0.24	BC170	£0.10	BD124	£0.81	MPF104	£0.40	2N2148	£0.81
AC176	£0.21	BC171	£0.10	BD131	£0.60	MPF105	£0.40	2N2160	£1.15
AC176K	£0.30	BC172	£0.10	BD132	£0.60	MPSA05	£0.23	2N2192	£0.44
AC178	£0.20	BC173	£0.10	BD133	£0.46	MPSA06	£0.23	2N2193	£0.44
AC179	£0.20	BC177	£0.18	BD135	£0.44	MPSA55	£0.23	2N2194	£0.44
AC180	£0.23	BC178	£0.18	BD136	£0.40	MPSA56	£0.23	2N2217	£0.25
AC180K	£0.32	BC180	£0.18	BD137	£0.40	OC22	£1.73	2N2218	£0.25
AC181	£0.23	BC181	£0.10	BD138	£0.41	OC23	£1.73	2N2218A	£0.23
AC181K	£0.32	BC181	£0.10	BD139	£0.41	OC24	£1.85	2N2219	£0.23
AC187	£0.21	BC182L	£0.10	BD140	£0.41	OC25	£1.15	2N2219A	£0.25
AC187K	£0.32	BC183	£0.10	BD155	£0.92	OC26	£1.15	2N2904	£0.23
AC188	£0.21	BC183L	£0.10	BD175	£0.89	OC28	£0.92	2N2904A	£0.24
AC188K	£0.32	BC184	£0.10	BD176	£0.89	OC29	£1.09	2N2905	£0.20
AD140	£0.80	BC179	£0.13	BD177	£0.78	OC35	£1.03	2N2905A	£0.23
AD142	£0.88	BC208	£0.13	BD178	£0.78	OC36	£1.03	2N2906	£0.18
AD143	£0.86	BC209	£0.14	BD179	£0.86	OC70	£0.27	2N2906A	£0.21
AD149	£0.86	BC212	£0.10	BD203	£0.92	OC71	£0.17	2N2907	£0.23
AD161	£0.40	BC212L	£0.10	BD204	£0.92	TC44	£0.33	2N2907A	£0.25
AD162	£0.40	BC213	£0.10	BDY20	£0.92	TC45	£0.40	2N2926G	£0.10
AD161	£0.40	BC213L	£0.10	BF457	£0.43	TIP29A	£0.46	2N2926Y	£0.09
AF124	£0.35	BC214	£0.10	BF458	£0.43	TIP29B	£0.46	2N2927	£0.09
AF125	£0.35	BC227	£0.18	BF459	£0.44	TIP29C	£0.51	2N2928R	£0.09
AF126	£0.35	BC238	£0.18	BF594	£0.35	TIP30A	£0.46	2N2928S	£0.09
AF127	£0.37	BC251	£0.17	BF839	£0.28	TIP30B	£0.46	2N3052	£0.18
AF139	£0.40	BC201	£0.13	BF840	£0.29	TIP30C	£0.50	2N3054	£0.46
AF186	£0.58	BC210	£0.17	BF841	£0.29	TIP31B	£0.46	2N3055	£0.46
AF239	£0.47	BC302	£0.33	BF880	£0.32	TIP31C	£0.50	2N3615	£1.21
AL102	£1.38	BC303	£0.32	BFX29	£0.25	TIP32A	£0.46	2N3616	£1.21
AL103	£1.38	BC304	£0.44	BFX30	£0.35	TIP32B	£0.46	2N3646	£0.10
AL104	£1.61	BC327	£0.18	BFX84	£0.25	TIP32C	£0.50	2N3702	£0.50
AU110	£1.81	BC328	£0.17	BFX85	£0.28	TIP41A	£0.50	2N3703	£0.09
AU113	£1.81	BC337	£0.17	BFX86	£0.28	TIP41B	£0.50	2N3704	£0.08
BC107A	£0.09	BC338	£0.17	BFX87	£0.28	TIP41C	£0.50	2N3705	£0.08
BC107B	£0.10	BC440	£0.35	BFX88	£0.25	TIP42A	£0.50	2N3706	£0.09
BC107C	£0.12	BC441	£0.35	BFX50	£0.18	TIP42B	£0.52	2N3707	£0.09
BC108A	£0.09	BC460	£0.44	BFY51	£0.18	TIP42C	£0.55	2N3708	£0.08
BC108B	£0.11	BC461	£0.44	BFY52	£0.18	TIP2955	£0.68	2N3709	£0.08
BC108C	£0.12	BC477	£0.23	BP20	£0.44	TS43	£0.26	2N3710	£0.08
BC109A	£0.09	BC478	£0.23	BP20	£0.44	TS90	£0.20	2N3711	£0.08
BC109B	£0.10	BC479	£0.23	BIP19	£0.44	UT46	£0.23	2N3819	£0.21
BC109C	£0.12	BC547	£0.12	20MP	£0.82	ZTX107	£0.11	2N3820	£0.40
BC147	£0.08	BC548	£0.12	BRV39	£0.61	ZTX108	£0.11		

## 74 SERIES TTL

Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
7400	£0.10	7427	£0.27	7432	£0.27	74105	£0.43	74163	£0.78
7401	£0.12	7428	£0.29	7473	£0.28	74107	£0.27	74164	£0.78
7402	£0.12	7430	£0.12	7474	£0.28	74110	£0.41	74165	£0.78
7403	£0.12	7432	£0.25	7475	£0.33	74111	£0.66	74166	£0.89
7404	£0.12	7433	£0.24	7476	£0.28	74118	£0.92	74174	£0.74
7405	£0.12	7437	£0.26	7480	£0.50	74119	£1.38	74175	£0.71
7406	£0.25	7438	£0.24	7481	£0.28	74121	£0.27	74176	£0.66
7407	£0.25	7440	£0.13	7482	£0.78	74122	£0.44	74177	£0.66
7408	£0.14	7441	£0.57	7483	£0.66	74123	£0.46	74180	£0.74
7409	£0.14	7442	£0.46	7484	£1.01	74136	£0.59	74181	£0.66
7410	£0.12	7443	£0.80	7485	£0.78	74141	£0.63	74182	£0.80
7411	£0.19	7444	£0.80	7486	£0.25	74145	£0.63	74184	£0.80
7412	£0.17	7445	£0.74	7487	£1.95	74150	£0.78	74190	£0.78
7413	£0.27	7446	£0.89	7490	£0.38	74151	£0.85	74191	£0.71
7414	£0.57	7447	£0.55	7491	£0.73	74153	£0.94	74192	£0.69
7416	£0.26	7448	£0.64	7492	£0.40	74154	£0.94	74193	£0.66
7417	£0.26	7450	£0.12	7493	£0.34	74155	£0.67	74194	£0.71
7420	£0.12	7451	£0.12	7494	£0.88	74156	£0.67	74195	£0.81
7421	£0.23	7453	£0.12	7495	£0.87	74157	£0.67	74196	£1.20
7422	£0.18	7454	£0.12	7497	£0.28	74160	£0.66	74197	£1.20
7423	£0.24	7460	£0.12	74100	£0.87	74161	£0.71	74198	£2.12
7425	£0.21	7470	£0.28	74104	£0.44	74162	£0.71	74199	£2.12

## CMOS ICs

Type	Price								
CD4000	£0.16	CD4015	£0.87	CD4026	£1.38	CD4043	£1.01	CD4071	£0.19
CD4001	£0.17	CD4016	£0.48	CD4027	£0.57	CD4044	£0.94	CD4072	£0.19
CD4002	£0.18	CD4017	£0.86	CD4028	£0.78	CD4045	£1.81	CD4073	£0.19
CD4006	£1.05	CD4018	£0.97	CD4029	£0.97	CD4046	£1.49	CD4074	£0.19
CD4007	£0.18	CD4019	£0.48	CD4030	£0.55	CD4047	£1.00	CD4075	£0.20
CD4008	£1.05	CD4020	£1.03	CD4031	£2.30	CD4048	£0.48	CD4076	£0.13
CD4009	£0.51	CD4021	£0.94	CD4032	£1.15	CD4050	£0.48	CD4511	£1.09
CD4010	£0.55	CD4022	£0.94	CD4033	£1.09	CD4054	£1.26	CD4516	£1.15
CD4011	£0.17	CD4023	£0.17	CD4040	£1.01	CD4055	£1.35	CD4518	£1.16
CD4012	£0.18	CD4024	£0.74	CD4041	£0.87	CD4056	£1.55	CD4520	£1.15
CD4013	£0.46	CD4025	£0.17	CD4042	£0.82	CD4069	£0.19	CD4014	£0.92

## LINEAR

Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
CA3011	£0.82	CA3130	£1.06	MC1350	£1.38	UA710C	£0.46	SN76115	£2.18
CA3014	£1.55	CA3140	£0.80	MC1352	£1.61	72710	£0.34	SN76600	£0.86
CA3018	£0.74	LM301	£0.33	MC1469	£3.59	UA710E	£0.36	SL414	£2.24
CA3020	£1.85	LM304	£1.84	MC1496	£1.83	72711	£0.36	TA8550	£0.40
CA3028	£0.82	LM308	£1.15	NE530	£3.05	UA723C	£0.52	TA8621A	£2.80
CA3035	£1.61	LM309	£1.72	NE550	£1.09	72723	£0.52	TA8621B	£2.87
CA3036	£1.15	LM320-5V	£1.72	NE555	£0.27	UA741C	£0.27	TA8661	£1.72
CA3042	£1.72	LM320-12V	£1.72	NE556	£0.69	72741	£0.27	TAD190	£1.49
CA3043	£2.12	LM320-15V	£1.72	NE565	£1.38	72742	£0.23	TA8540	£2.41
CA3046	£0.85	LM320-24V	£1.72	NE566	£1.38	UA747C	£0.69	TR810S	£0.86
CA3052	£1.84	LM380	£0.97	NE567	£1.95	72747	£0.69	TR810	£1.12
CA3054	£1.26	LM381	£1.86	UA702C	£0.52	UA748	£0.40	TR820	£0.80
CA3075	£1.72	LM3900	£0.66	72702	£0.52	72748	£0.40	TR8200	£2.87
CA3081	£1.72	MC1303L	£0.97	UA703	£0.28	748P	£0.40	TC4270S	£2.90
CA3089	£2.30	MC1304	£2.18	72709	£0.28	SN76013N	£2.01	TR800	£0.92
CA3090	£1.14	MC1310	£1.09	72709	£0.52	SN76023	£2.01		
CA3123	£2.18	MC1312	£2.18	72709	£0.28	SN76110	£1.72		

## THYRISTORS


Volts No	Price	Volts No	Price
50 THY1A/50	£0.29	50 THY7A/50	£0.55
100 THY1A/100	£0.32	100 THY7A/100	£0.58
200 THY1A/200	£0.36	200 THY7A/200	£0.65
400 THY1A/400	£0.43	400 THY7A/400	£0.71
600 THY1A/600	£0.48	600 THY7A/600	£0.80
800 THY1A/800	£0.66	800 THY7A/800	£1.05

## SILICON RECTIFIERS

200MA	£0.07	10 Amp	£0.21
IS920 50v	£0.07	IS10/50 50v	£0.21
IS921 100v	£0.08	IS10/100 100v	£0.24
IS922 150v	£0.09	IS10/200 200v	£0.26
IS923 200v	£0.10	IS10/400 400v	£0.40
IS924 300v	£0.11	IS10/600 600v	£0.46
1 Amp	£0.09	IS10/800 800v	£0.58
IN4001 50v	£0.05	IS10/1000 1000v	£0.69
IN4002 100v	£0.05	IS10/1200 1200v	
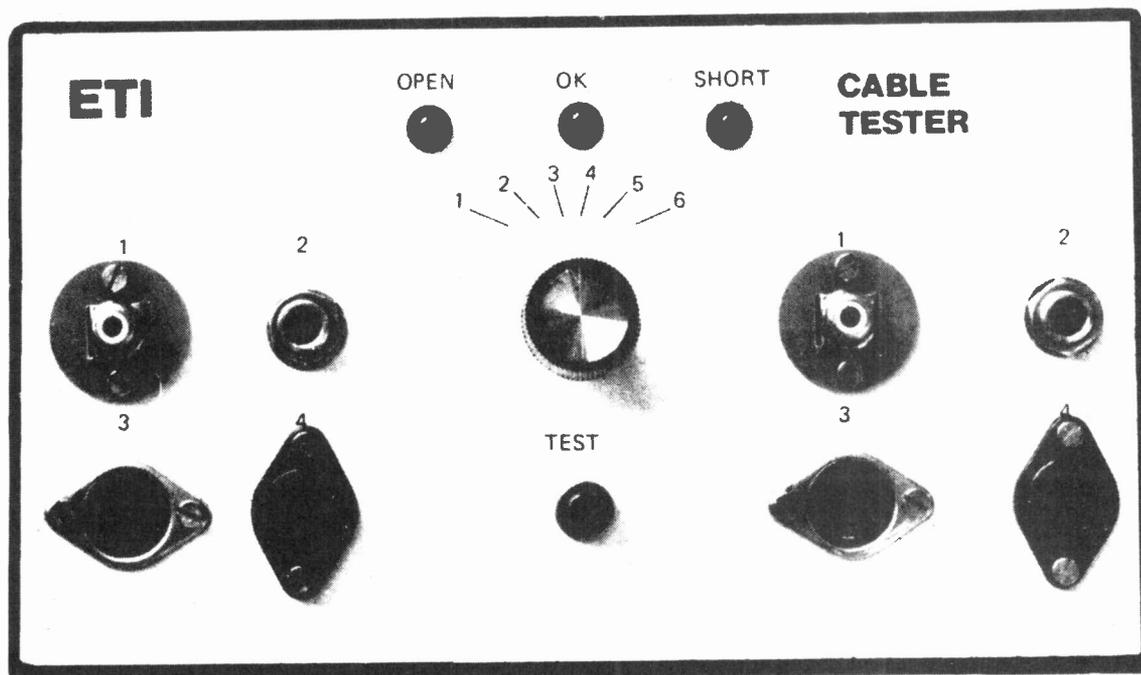
# CABLE TESTER

Quickly test your cables with this invaluable project



ALMOST ALL THE faults in an audio system are caused by cables. Have you ever tried to find which cable is broken among the many connections in a stage audio system, especially with anxious people looking over your shoulder?

The answer is to check each cable before the performance, a rather tedious business.

This Cable Tester checks each wire in turn for both open circuits and short circuits to earth. Each cable can then be thoroughly tested before use and hopefully faults can be found before they cause problems.

The circuit makes cunning use of a

7474 dual D flip flop to light one of three LED's after the test switch is pushed, indicating short, open or OK.

## Construction

The unit is mounted on a standard plastic box measuring 196 x 113 x 60 mm. If it is to be used on-stave, then use the strongest box you can find, such as diecast aluminium.

Wiring the switch is the only difficult part of the construction. Note that some of the switch contacts are linked together as shown in Table 1.

The transformer we used is a commonly available Ferguson PCB mounting type.

The sockets we have chosen for the prototype are the most common type, however there is no reason why others can't be substituted. The jack plugs, SK7, 8 and the phono sockets SK1, 2 must be insulated from the metal front panel, or the earth connections will be permanently connected together through the panel. Phono sockets are available with insulating mountings, while insulating washers can be made from plastic sheet for mounting the jack sockets. ▶



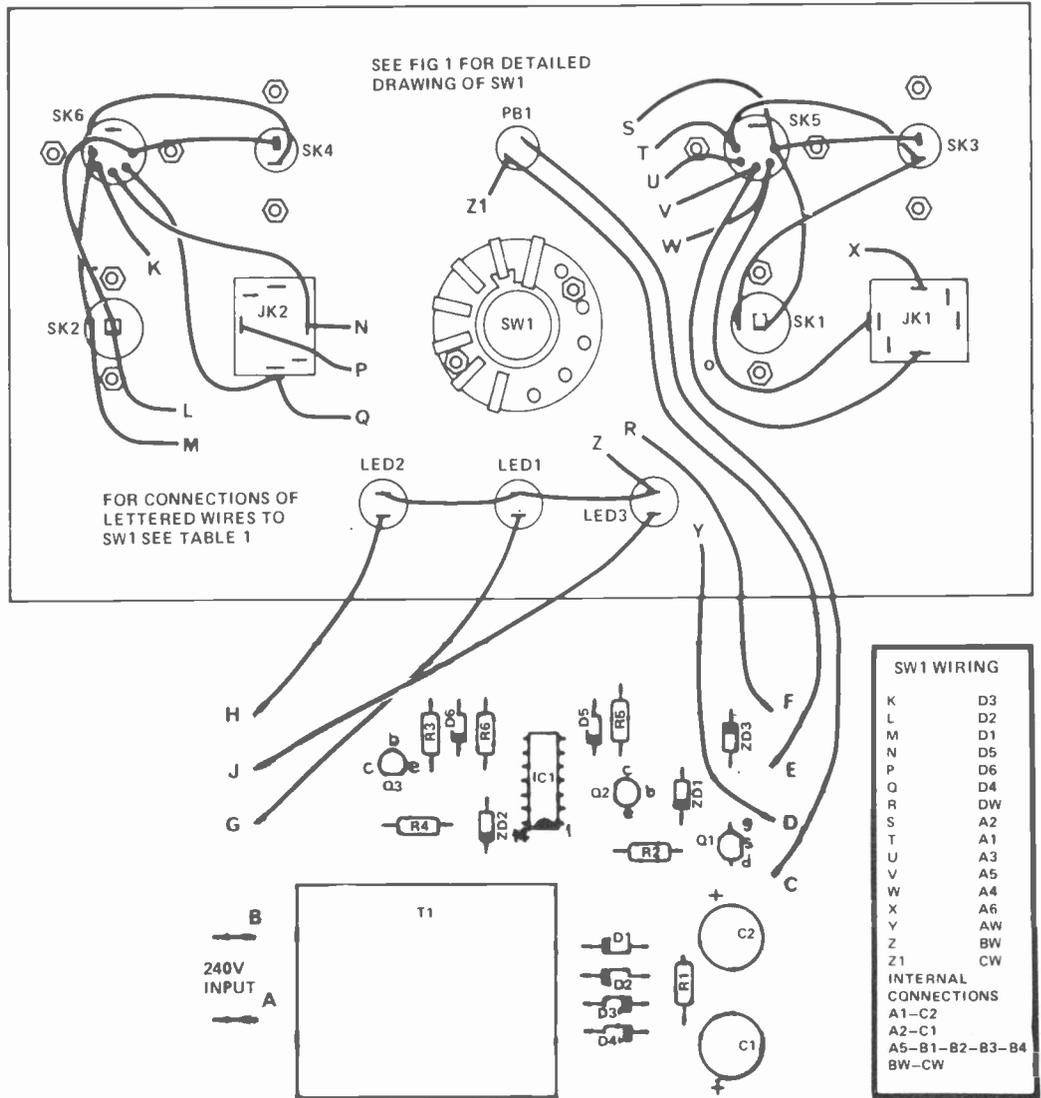


Fig. 2. Component overlay and front panel connections.

## PARTS LIST

RESISTORS	all 1/4W 5%	ZD1	6V8 400mW
R1	100R	ZD2	5V1 400mW
R2	220R	ZD3	3V3 400mW
R3	10k	LED1-3	TIL 209 or similar
R4	150R	SOCKETS	
R5, 6	47R	SK1, 2	phono skt
CAPACITORS		SK3, 4	2pin DIN
C1, 2	220 25V electrolytic	SK5, 6	5pin DIN
SEMICONDUCTORS		SK7, 8	stereo jack
IC1	7474	MISCELLANEOUS	
Q1	2N5484	SW1	4p 6way
Q2, 3	BC548	T1	6-0-6V 500mA
D1-4	1N4001	PB1	push to make
D5, 6	1N914		Box to suit, pcb, power lead, etc.

## BUYLINES

None of the electronic components in this project will be difficult to get hold of, and the mechanics depend on the application. For stage use a couple of Cannon sockets could be added and wired in accordingly. The switch SW1 should be break before make.

# VOICE CHESS CHALLENGER

"THE FIRST THINKING CHESS GAME THAT SPEAKS TO YOU"



LEVEL	Average Response Time
1. Beginner	5 Seconds
2. Intermediate	15 Seconds
3. Experienced	35 Seconds
4. Advanced	1:20 Minutes
5. Superior	2:20 Minutes
6. Tournament Practice	3 Minutes
7. Tournament Teacher	3 Minutes
8. Excellent	20 Seconds
9. Expert	6 Minutes
H. Infinite	11 Minutes

£229.95 inc. VAT cwo

It computes move until you stop, or search is exhausted. The Strongest Chess Program ever placed in a microprocessor. Approximately twice as fast as previous models, this is the FIRST Thinking Chess Game that speaks out and talks! It is so smart, it is available in English, German, French or Spanish by special order.

- Large repertoire or chess book openings.**
    - 40 book opening variations randomly selected.
    - Special feature allows you to select a book opening of your choice.
    - Approximately 1200 book opening moves. Book openings selectable whether computer plays black or white.
    - Computer teaches book openings by displaying next move to be entered.
    - All "Book" moves are instant response regardless of level of play.
  - The Chess Teacher**
    - On levels 2, 5, 7, 9, and H, the computer will display best suggested move for you to enter.
    - Plays against itself with white usually the winner.
    - Never makes an illegal move.
    - Teaches end game solutions.
    - Book openings teaches opening game.
    - Announces mate-in-two for you to solve.
    - Problem mode permits setting up of all chess book positions.
  - Your Friendly Speaking Opponent**
    - Tells you all of its moves.
    - Repeats all of your moves.
    - Can be used by the blind, as the game will audibly tell you every move and capture, and will repeat board position on demand.
    - Voice feature allows you to tape record game play.
    - It even suggests your moves.
  - An Advanced Computer**
    - 128,000 to 160,000 bits of Read Only Memory
    - Has over 8,000 bits of Random Access Memory.
    - At the conclusion of the game when it loses, the computer displays the number of moves played.
- Encompasses all of our other renowned features, including a solid hardwood case, 13 1/2 x 8 1/2 x 1 1/2 inches high, deluxe playing surface with raised keyboard, 1/2 inch LED Display and Staunton design magnetized Chess Pieces. 100% solid state.
- Orders now being accepted for delivery. We will match any lower price, if competitor has goods in stock. See for brochure and list of 42 book openings CC7 at £95.**
- KRAMER & CO., Dept. ETI 2**
- 9 OCTOBER PLACE, HOLDERS HILL ROAD, LONDON NW4 1EJ**  
Tel: 01-203 2473 Telex: 888941 ATTN: KRAMER K7  
Mail order only. Callers by appointment. Barclay & Access by arrangement

## SINCLAIR PRODUCTS

PFM200 £52.69, case £3.40, adaptor £3.40, connector kit £11.27, Microvision TV UK model £91.44, mains adaptor £6.88, PDM35 £29.76, mains adaptor £3.40, case £3.40, 30kV probe £20.13, DM350 £71.82, DM450 £102.17, DM235 £52.86. Accessories for all 3 models rechargeable batteries £7.99, mains adaptor / charger £3.94, case £9, 30kV probe £20.13. Enterprise prog calculator with accessories £23.37. New 10 MHz scope p o

## CALSCOPE OSCILLOSCOPES

Send see for details or see the Calscope advert in this magazine. Super 6 6MHz single beam 60ns rise time £185. Super 10 10MHz dual trace 35ns rise time £251.

## COMPUTER GAMES

Star Chess £82. Chess champion 6 £94. Chess challenger 7 £81. Chess challenger 10 £152.50. Voice challenger £239. Checker challenger 2 £46. Checker challenger 4 £88. Atari video computer £147, cartridges £14.32.

## CONTINENTAL SPECIALITIES

### PRODUCTS

EXP300 £6.61. EXP350 £3.62. EXP325 £1.84. EXP600 £7.24. EXP650 £4.14. EXP48 £2.64. PB6 £10.58. PB100 £13.57. LM1 £32.99. LP1 £35.65. LP2 £20.70. MAX100 £89.18.

### TV GAMES

Tank battles kit £6.34. AY-3-8500 chip £5.27, kit £4.26. stunt cycle AY-3-8760 chip £12.46, kit £4.26. 10 game paddle 2 AY-3-8610 chip £9.48, kit £7.03. racing car chip AY-3-8603 £9.48, modified shoot kit £5.28, rifle kit £5.27, colour generator kit £9.05, joystick 220K £1.80.

## MAINS TRANSFORMERS

6.0-6V 100ma 76p, 1 1/2a £2.50. 6 3V 1 1/2a £2.01. 9.0-9V 75ma 76p, 1a £2.12, 2a £2.77. 12.0-12V 50ma 76p, 100ma 92p, 1a £2.65. 13V 1 1/2a £1.01. 15.0-15V 1a £2.97. 30.0-30V 1a £3.82.

## JC12 AND JC20 AMPLIFIERS

Integrated circuit audio amplifier chips supplied with free data and printed circuits. JC12 6 Watts £2.08. JC20 10 Watts £3.14. We also stock a range of matching preamp and power kits

## FERRANTI ZN414

IC radio chip £1.12. Extra parts and pcb for radio £4.10. Case £1.06.

## PRINTED CIRCUIT MATERIALS

PC etching kits economy £2.32. Standard £4.36. 40 x 50 mm pcb 84p. 1 lb 84p. £1.20. Etch resist pens economy 48p, dial 84p. Drill bits 1/32 ins or 1mm £5.00 each. Etching dish 72p. Laminate cutter 80p.

## S-OECS AND T-DECS

S-Dec £4.05. T-Dec £4.28. u-DecA £4.69. u-DecB £7.16. 16,dil adaptor with socket £2.81.

## BATTERY ELIMINATORS

3-way types with switched output and 4 way multi-jack 3/4x1/2x1/4 100ma £2.89. 6/7x1/2x1/4 300ma £3.14. 100ma radio types with press-stud connectors 9v £3.57, 6v £3.57, 4 1/2v £3.57, 9+9v £4.78, 6+6v £4.79, 4 1/2+4 1/2v £4.79. Cassette recorder mains unit 7 1/2v 100ma with 5 pin d/n plug £3.57. Fully stabilized type 3/6x7 1/2v 400ma £5.64. Car converters 12v dc input output 9v 300ma £1.60, output 7 1/2v 300ma £1.60, output 3/4x1/2x1/4 12v 800ma £2.66.

## BATTERY ELIMINATOR KITS

100ma radio types with press-stud connectors 4 1/2v £1.49. 6v £1.49, 9v £1.49, 4 1/2+4 1/2v £1.92, 6+6v £1.92, 9+9v £1.92. Cassette type 7 1/2v 100ma with d/n plug £1.49. Heavy duty 13-way types 4 1/2x6/7/8x1/2/1/3/1/4/1/7/21/25/28/34/42v 1A £4.95, 2A £7.72. Transistor stabilized 8-way types for low hum 3 1/2x6/7/8x1/2/1/3/1/4/1/7 100ma £2.98, 1Amp £6.81. Variable voltage stabilized models 2 18v 100ma £2.98, 2-30v 1A £7.40, 2-30v 2A £11.66. Car converter 12v dc input Output 9/7 1/2v 6v 1A stabilized £1.44.

## BI-PAK AUDIO MODULES

AL30 £4.04. PA12 £7.77. PS12 £1.42. T538 £2.70. S450 £24.03. AL60 £4.97. PA100 £17.33. SPM80 £4.57. BMT80 £6.08. Stereo 30 £20.57. MA60 £36.23.

## COMPONENTS

1N4148 1.4p. 1N4002 3.1p. 741 9 dil 18p. 723 14 dil 31p. NE555 8 dil 25p. bc182b bc183b, bc184b bc212b bc213b bc214c bc547 bc548, bc549 5p. tp31c tp32c 38p. tp41c tp42c 48p. bd131 bd132 33p. Plastic equiv bc107 5p. Fuses 20mm x 5mm cartridge 15 25 5 1.2 3-6 200k 1p, anti-surge 3.0p. Resistors 5% 1/4W £12 10R to 10M 1p, 9.9p for 50p or one value. Polyester capacitors 250v 015 068 1mf 1.5p, 01 033 33mf 2.8p, 022 047mf 3.3p, 22 47mf 4.0p. Polystyrene capacitors E12 63v 10 to 10000p 3p, 1n2 to 10n 4p, ceramic capacitors 50V E6 22pf to 47n 2p. Electrolytic capacitors 50v 5, 1 2mf 5p, 25v 5 10 5p, 16v 22 33 47 68mf 5p, 100mf 8p, 220mf 7.5p, 330 470mf 9p, 100mf 10p, Zeners 400mW E24 2v7 to 33v 7p. Preset pots subminiature 0 1W horiz or vert 100 to 4M7 7.2p. Potentiometers 1/4W 4K7 to 2M2 log or 1in single 27p, dual 78p. 1/2 red LEDs 9.7p. IC sockets 8 dil 8.6p, 14 dil 10.1p, 16 dil 12p.

# SWANLEY ELECTRONICS

DEPT. ETI, 32 Goldslee Road, Swanley, Kent BR8 8EZ  
Mail order only. Please add 30p to the total cost of the order for postage. Prices include VAT. Lists 20p post free. Overseas customers deduct 13%. Official credit orders welcome.

# NEW! BUILD-IT-YOURSELF TEST GEAR KIT

BASIC SERVICING INSTRUMENTS WITH EASY STAGE BY STAGE BUILDING INSTRUCTIONS - IDEAL FOR THE AMATEUR

## MULTI RANGE TEST METER

A general purpose meter covering all usual ranges of A.C. and D.C. volts current and resistance measurements

## AUDIO SIGNAL GENERATOR

New design covering 10Hz to 10KHz and variable output. Distortion less than 0.01% Ideal for HI-FI Testing.

## OSCILLOSCOPE

A basic 3" general purpose cathode ray oscilloscope for simple testing and servicing work. Sensitivity 0.3 volts/cm

SEND NOW FOR FREE DETAILS

To LERNAKITS, P.O. Box 156, Jersey.

Name \_\_\_\_\_

Address \_\_\_\_\_

ETI 10 / 79

# Now, complete your system!



## Citronic MM313 Mixer

Ideal for the DIY enthusiast building up a complete disco system 4/6 ch mono inc. LED indicators, connections via phono jacks at rear. Bargain price, including PSU £89.70

## The ultimate range of speakers

We carry a good selection of high quality chassis for the DIY speaker constructor 12" or 15" Bass speakers and Dual Concentrics. Exponential horns from £13.90 or our fabulous Piezo Horns which handle a 5K-20K frequency range in any PA system up to 100W (No X over required) and cost only £6.32 each



## Projectors

Come and see our specially selected projectors from £50.60 (Squire Multi-fact 150) to £83.37 (Tutor IIE DDU) plus the widest array of projector attachment and effects that you'll ever see on continuous demonstration



## Ropelights


Great effect at discos 7 metres long. Multiway connectors 4 channel £46.00 (inc pack of spare bulbs)
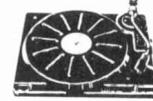
## Bulgin Octal plugs and sockets

There's always hundreds of Bulgin Octal multiway plugs and sockets in stock at Roger Squire's. Each priced 6A Perfect for your Sound to Light System. P552 SOCKET £0.69 P551 PLUG £1.72



Multiway Cables  
4 core (6A) 63p/metre  
5 core (6A) 78p/metre  
6 core (6A) 92p/metre



## Turntables

Our unsurpassed Disco experience has enabled us to select the best turntables for your requirements. For example the new BSR P200 belt drive ONLY £28.75

## Many disco accessories

All Roger Squire's shops have a service department which carries large stocks of DISCO SPARES & ACCESSORIES

Roger Squire's

Disco Centres

PERSONAL CALLERS ONLY

ALL SHOPS OPEN TUE SAT LATE NIGHT WED (UP TO 8 PM)


LONDON 176 Junction Road N19 5DVs Trafalgar Park Tube Station Tel: 01 272 7474

BRISTOL 125 Church Road, Redfield (W. of St. George) 1 mile from end of M32 Tel: 0272 560550

MANCHESTER 251 Deansgate 3 15 mins from City Centre Tel: 061 831 7676

GLASGOW 1 Queen Mary Road Inverleith 20, just behind the BBC. Tel: 041 946 3303

# MICROSENSE

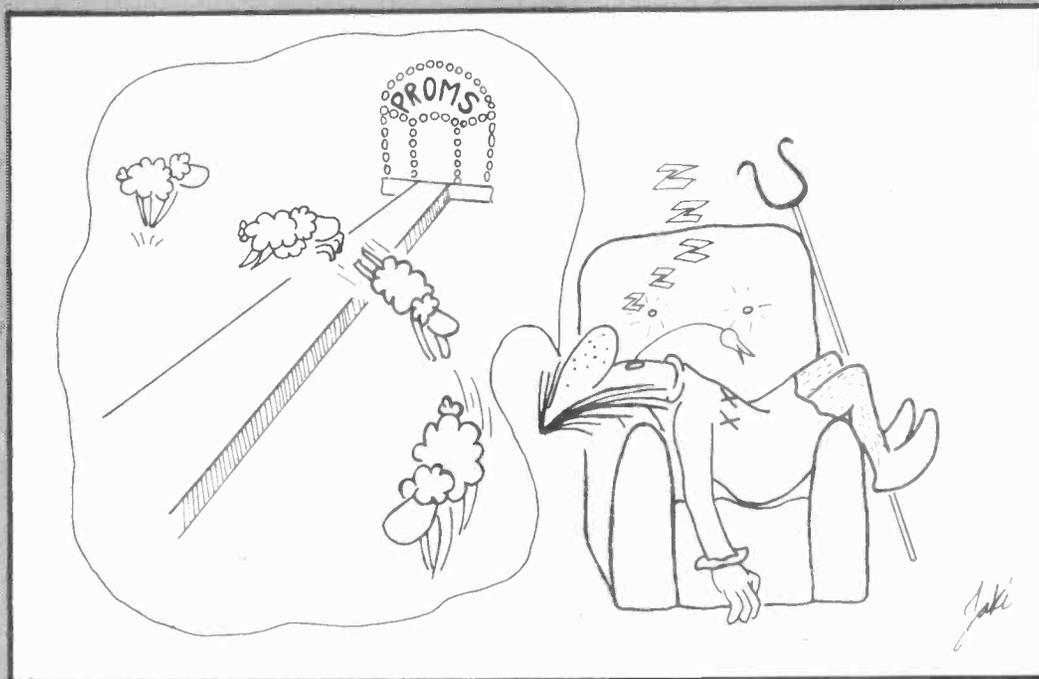

## RAMS and PROMS are MEMORIES

MICROPROCESSOR systems are made up from two distinct parts called Hardware and Software, the Software is the program which is run on the system, the Hardware is the physical components which go to make up such a system. We will assume that you are able to differentiate between resistors, capacitors and diodes which apart from the crystal and PCB (Printed Circuit Board) leaves only the mysterious ICs and sockets.

An IC looks like a lump of black plastic or similar material with numerous pins sticking out on each side, each IC should have a socket associated with it. For ease of testing and replacement the sockets are soldered into the PCB and the ICs plugged into the sockets. The important things to remember about inserting or removing ICs from the sockets are:

1. Make sure that no power is applied to the PCB.
2. Make sure it is the correct IC for that location.
3. Make sure it is the correct way round.
4. Ensure that all of the pins are correctly sitting in the socket.

Each IC is identified by a number printed on the top surface of the package, pin 1 of each IC is marked either with a dot, indentation or horseshoe groove near pin 1. If the IC is held with the pins downward and the dot or horseshoe away from you then pin 1 is always the furthest pin on the left.

SCRUMPI contains several ICs which may be broken down into the following categories.

**Main Control Chip.** This is the SC/MP microprocessor chip.

**Buffers and encoders, etc.** These ICs typically have a code such as 74LS xx or 81LS xx and are used to handle control of counting, device address decoding, latching or buffering the address bus and data bus.

**RAMS. Random Access Memories.** The theory of the insides of these ICs can be likened to a chessboard or a set of 'pigeon holes.' The data in the MM2112 RAM chips is organised as 256 locations each of four bits, if we use two M2112 chips in parallel it is possible to have an organisation of 256 locations each of 8 bits (or 1 byte). Each of the 256 locations can be accessed directly by the MPU chip and the data at that location copied onto the data bus or the ▶

data on the data bus copied into the selected location. The data in such a memory will remain there until the supply voltage is removed. When first powered-up each time, the contents of a RAM are random and variable.

RAMs can be used for storage of programs or data for the program to be operated upon, under some circumstances even a program can be considered to be data.

PROMs, ROMs, etc. There are a second type of memory device similar in concept to the RAM except that the program or data stored in the device remains even if the power supply is removed. They are thus suitable for holding the fixed programs and data and are a convenient method of shipping such data from one installation to another.

ROM stands for READ ONLY MEMORY and it is usually assumed that the data in a ROM is installed at the time of manufacture of the chip and as such can be referred to as Mask programmed ROMs. PROMs and EPROMs on the other hand are programmed after manufacture and are thus referred to as Programmable Read Only Memories. The E in EPROM shows that the data in the PROM can be erased by exposing the inside of the chip to intense UV radiation, this is usually accomplished through the transparent quartz window let into the top of these devices.

The type of Read Only Memory used in SCRUMPI is the MM5204Q EPROM, this can be replaced with either of the following pin compatible devices —

MM5214      Mask Programmed ROM  
                 Field Programmable ROM

The alternatives offer the advantages of large volume / low cost and / or simplification or power supply to 5V only (no — 12V supply is required).

Ports are the method that an MPU uses to communicate to the external world. A port is simply an integrated circuit whose function is to interface the MPU data bus in whole or only in part to devices which cannot interface directly to the MPU system. There are several reasons why external devices cannot be directly coupled to the MPU data bus.

Firstly the devices may not be TRI-STATE output devices which means that they could not be connected to the data bus otherwise their outputs would always be in the logic 1 or logic 0 state and not in the high impedance TRI-STATE mode required. Alternatively the external devices may operate too fast for the MPU, or too slowly, or require buffering so as not to unduly load the drive capabilities of the MPU data bus. The INS8154 is a single chip device containing the logic required to operate 16 of its pins as PORTs, the 16 pins can be operated as two 8 bit ports or as individual Input / Output lines. Each pin can operate in either Input mode or Output mode the choice being made by Software selection, each pin is also capable of latching the data on that pin at either input or output time. In addition to the two 8 bit ports the INS8154 also contains 128 bytes of RAM which is sufficient as a working storage RAM in most applications.



### The effects of Scrumpi

If you study the circuit diagram of SCRUMPI you will quickly see that all of the major signals to and from the SC/MP chip are available at one of the two edge connectors so that SCRUMPI is able to communicate with other electronic devices. It can thus be used as the heart of many electronic circuits and can be used in this form to help with the design and debugging of projects by the electronics engineer or by the amateur constructor.

The single-step circuitry shown as IC's 2, 3 and 4 allow the SC/MP to be run at a very slow speed (down to 1 step per hour if necessary), this slow single step speed is useful in checking the effect of each instruction as it is executed. The actuation of the STEP switch causes a single pulse output from IC 4. This pulse sets a Flip-Flop (a simple electronic switch) at IC3 and thus drives the NHOLD line to a positive voltage which instructs the SC/MP to execute an instruction. During this instruction the SC/MP outputs a pulse on the NADS (Address Strobe) output, this pulse

RESETs the Flip-Flop which in turn puts the NHOLD input low and thus stops the SC/MP from executing any further instructions. The next instruction will only be executed after the next actuation of the STEP switch.

A similar situation exists with the single-step switch in the FAST position excepts that here IC 4 will generate a pulse automatically at a rate which is dependent on the value of C1 (usually about 5 pulses per second). This mode can be used to step through a program faster than single-stepping but not at the maximum possible speed.

If CS 4 is put into the RUN position then the SC/MP will execute the program at the maximum speed. Between this mode and the FAST single-step mode is the HALT mode which can be used to stop execution of the program at predetermined points. Here the pulse for the Flip-Flop is generated whenever the SC/MP executes a HALT (X'00') instruction; this pulse RESETs the Flip-Flop and thus terminates execution until the next actuation of the STEP switch. The data bus is connected to a set of switches which can be used either in the DIRECT mode to enter a logic 1 or 0 onto the data bus at any time or in the ADDRESSED mode only when addressed by the SC/MP. This allows the switches to be used to program the memory in the single step mode or to enter data when required by a program.

Both the data bus and the address bus are connected via wire links to LED lamps. The LED lamps thus show the status of these buses at any stage of the program, the branching and data addressing of the program can thus be checked easily. Alternatively the LED lamps can be linked to other signal lines by redirecting the wire links, they can then be used to show the status of an output device.

A typical input-output device is shown as IC's 15 and 16, two 74C173 latches. These ICs can latch the status of a signal on the inputs so that the outputs carry a copy of that status at a given time even after the original status has disappeared. In the output from SCRUMPI 2 mode the latch can store the data on the data bus at the time that the latch was addressed by the SC/MP. Any data written to the latch will appear on the data bus at the same time as a strobe pulse is output at point 'P' or 'Q'. If the data bus is connected to the inputs of the latch and the pulse used as the clocking strobe to the latch then the data will appear at the outputs of the latch and stay there until the next write to the latch. As an example, some of the LED lamp drivers could be connected to the latch outputs to indicate a particular data output to the operator.

Using the latch for input is a similar operation except that the latch is used the other way round. The outputs are connected to the data bus and the address strobe ('P' or 'Q') is used as the OUTPUT ENABLE control to the latch. Any data in the latch will be read onto the data bus when 'P' or 'Q' is strobed, the data enters the latch via the inputs when the clocking input is pulsed with a logic 0.

The P and Q strobes mentioned above are output from the device decoding circuitry at IC's 17, 18, 19, 20 and 22. This circuitry decodes the addresses specified by the address bus and produces a set of strobes which enable or disable the devices connected to the data bus. Three enable strobes are output to the RAM memories at ICs 5-10, each pair of IC's being enable for Read or Write operation. One enable strobe can be used to enable the outputs from a MM5204 PROM if there is such a PROM at IC21. Output 'P' is enabled if an address in the range X'500' — X'5FF' is addressed, similarly 'Q' is enabled for the X'600' range, either of these strobes can be used to strobe either of the latches for input or output. Strobed output V is normally connected to the ADDRESSED mode of the data switches which means that any data on the switches will be input to the SC/MP when any address in the X'700' range is read.

Examples of microprocessor interfaces to other equipment can be seen in most of the associated hobby magazines and in the 'SC/MP Applications Guide' published by National Semiconductor.



## Teaching Your Scrumpi to talk to Outsiders

Some microprocessors are used solely for writing, checking and executing programs, this type is usually to be found in offices handling accounts or stock control. Other microprocessors control equipment and machinery with complex testing and control interface, usually this type of MPU system can be found in vending machines, production lines, complex timing systems, etc. The same microprocessor chip may be found in both types of application but the interfaces to the outside world will be different. In the first type the interfaces will be to printers, keyboard large VDU, floppy disks, etc to handle the collection, sorting and printing of, for example, account details. In the second type the interfaces will be to switches, motors, lamps and buzzers to handle the input of data from various sensors and control machinery accordingly.

## Thou Art a You Art

The Universal Asynchronous Receiver / Transmitter is better known as a UART (pronounced You Art) for obvious reasons. Its basic function is to translate the 8 bit data available on the data bus from parallel form to a serial form and vice-versa. The advantage of this idea is that data can thus be transmitted along a single pair of wires rather than the dozen or so wires which would be needed for parallel transmission. Many interfaces to other equipment such as printers, TTYs and telephone use serial transmission to save on wire costs or for convenience if the remote unit is any considerable distance from the MPU.

A transmission starts with the output of the UART at a logic 1 state which is referred to as a MARK condition. Data is written from the data bus into the UART by enabling the Data Strobe input, this immediately signals back to an internal Flip-Flop that the UART transmitter is BUSY and cannot receive any more parallel data at present, in normal practise this Flip-Flop is tested by the MPU software before any attempt to write to the UART; the program loops until the Flip-Flop is reset at the end of the data transmission.

Once the UART has some data to transmit it shifts to the SPACE condition by changing the UART output to a logic 0, this START signal is one bit time long. The time taken to transmit each bit is defined by the rate of the 16x clock input. The frequency input at this pin is divided by 16 to give the bit transmission rate or BAUD RATE.

After sending the START BIT the UART sends each of the data bits in sequence as a MARK or a SPACE condition for 1 bit time each. To ensure that the START BIT of the following byte of data will be recognised by a receiving UART the transmitter now outputs two STOP BITS which are denoted by a MARK condition for two bit times, thus the total number of bits transmitted is not 8 but 11 made up from the 8 bits of data plus a START and two STOP bits.

In the receive mode the UART looks at its input pin continuously and waits for it to go from MARK to SPACE condition to indicate a START bit. After doing various checks to ensure validity the UART will then read in the 8 data bits and verify the presence of at least one STOP bit. On receipt of the first STOP bit the Data Available Flip-Flop is set to indicate to the MPU that parallel data is available, the MPU can now read this data and release the receiver by Resetting the Data Available (RDAV) Flip-Flop.


The UART thus handles most of the data shifting, verification transmitting and receiving. The UART is even clever enough to handle both transmitting and receiving at the same time — this is referred to as FULL DUPLEX MODE, using a UART solely for either transmission or reception is known as SIMPLEX MODE.

## Serial Standards

There are a set of standards associated with serial data transmission and used by many manufacturers in peripheral equipment. The usual one is the 'Teletype' TTY interface working at 110 Baud over a 20 mA current loop. The 110 baud refers to the bit transmission rate of 110 bits per second, when a UART is used, this rate will transmit 80 data bits or 10 bytes per second. The 20 mA current loop refers to an interface system in which the presence or absence of a current loop defines whether a MARK or SPACE is being transmitted, a lot of TTY equipment still uses relays and switches as an interface where thus the circuit is either open or completed, the current loop is inherited from this type of equipment.

An external printer might require a 1200 Baud RS232 interface, again the 1200 baud refers to the bit transmission rate of approximately 100 bytes per second. The RS232 interface is based on voltage levels and is usually something simple such as MARK = +3v and SPACE = -3v with respect to a common ground wire.

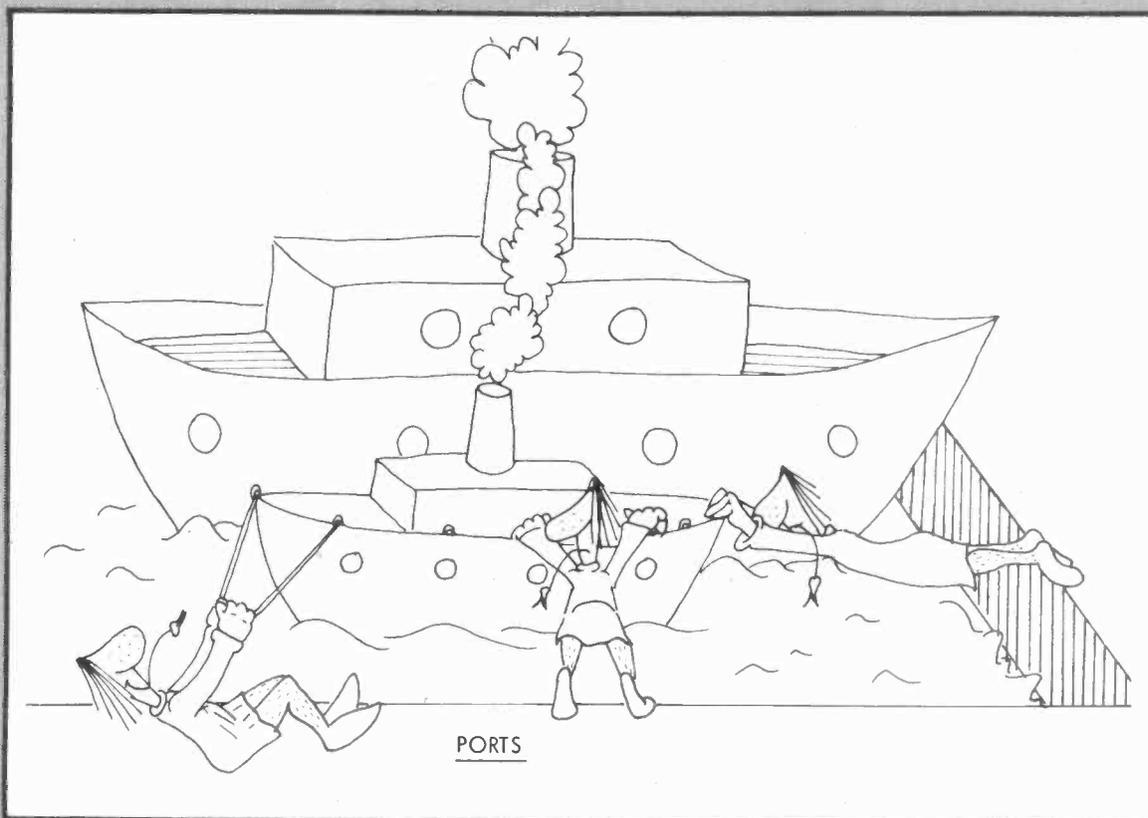**Interested in the mystic might of the microprocessor? Wrapped up in the crafty cabbalistic conjecturings of the software religion? Searching for a holy book to cover these black arts? Try Computing Today (surprise!) — The magazine for all**



### London, Liverpool and TTL

Just as London and Liverpool are ports allowing goods to enter and leave the country so an MPU port allows data to enter and leave the MPU. A port is usually assumed to be 8 bits wide, that is it will carry 8 parallel bits of data into out of the MPU and in the case of the usual 8 bit MPU the port interface directly to the data bus.

To the MPU the port looks like a single address location at which it can read or write data, the MPU addresses the port physically by decoding a unique address strobe from the address bus. Any time that this address is accessed the strobe will become active and thus inform the port that it is being accessed and should thus take appropriate action.

To the engineer and to external equipment the port looks like an 8 bit TTL latch. When used for output the data on the MPU data bus is latched into the port and thus appears latched at the port output pins, from here onwards these outputs can be assumed to have come from any similar TTL type of device. When used for input the port becomes an 8 bit latch presenting its inputs to the external circuitry, usually one of the inputs or an additional control pin acts as the clocking input. Data is presented to the port inputs and latched by strobing the clock input, the data at the inputs can now be released as the data is now held in the port. At the same time the MPU is informed (or finds out for itself) that there is new data in the port, it can thus 'read' the port address which will enable the port output to deposit their data onto the data bus and thus into the MPU chip. In applications of this type the MPU would then signal to the port that it had read the data and that the port could now input some more, this sequence of 'I've got some data for you' 'thank you, I've read it' is called 'Handshaking'.

The two theoretical ports described above are assumed to work in only one direction in each circuit. Some of the newer port chips are bi-directional which means that under software control they can either read data from external devices or write to external devices. The latest port chips allow individual bits to be specified as input or output by the software and can thus be changed halfway through a program. **ETI**

**frantic fanatical followers of small system computation, competition and construction. ETIs answer to sliced bread.**

**October issue now on sale — don't be behind the Jones in the queue, get yours today!**

Please add 25p for p&p.

# DELTA TECH & CO.

62 NAYLOR ROAD, LONDON, N20 0HN  
All prices VAT inclusive

<b>ZENER DIODES (400mW)</b> 2.7V to 33V 8p		1A/400V 34p		LM339 60p	7453	13p	74192 50p	4528 85p	8C328 19p	OC25 70p	
<b>VERO BOARDS (.1" Copper)</b> 2.5" x 5" 55p 3.75" x 5" 65p		2A/50V 40p		LM348 90p	7454	13p	75193 64p	TRANSISTORS	8C338 19p	OC28 86p	
<b>RESISTORS</b> (1/4 W E12) 10 ohm to 1 Mohm 1.5p (20 of 1 value: 20p)		2A/100V 42p		LM377 185p	7460	13p	74194 64p	AC126 20p	BC547 12p	OC35 86p	
<b>PRESETS (Horizontal)</b> 100 Ohms To 1 Mohm 5p		2A/200V 48p		LM380N 75p	7470	25p	74195 53p	AC127 20p	8C548 12p	OC71 9p	
<b>POTENTIOMETERS</b> (Carbon) 1 Kohm to 2 Mohm Log Or Linear 22p		2A/400V 55p		LM381N 140p	7472	21p	74196 53p	AC128 20p	8C549 13p	OC72 34p	
<b>CERAMIC CAP (50V)</b> 22pF To 50nF 3p		<b>VOLTAGE REGULATORS</b> 320H-05 45p 320H-24 45p 7805 70p 7812 70p 7815 70p 7818 70p 7824 70p 7905 90p 7912 90p 7915 90p 7918 90p 7924 90p		LM382N 140p	7473	20p	75197 50p	128/176	BC557 13p	OC84 30p	
<b>POLYESTER CAP (250V)</b> .01 .015 .022 .033 .047 .068 1 uF 5p 15 22 33 39uF 6p 47 .68 uF 12p 1 uF 15p 2.2 uF 20p		<b>OPTO DISPLAY</b> 2N5777 55p OCF71 75p ORP12 70p DL704 110p DL707 110p 125" & 2" LEDs Red 10p Green 14p Yellow 14p .125" clip 3p .2" clip 4p		LM1310N 150p	7474	22p	74198 107p	MP 40p	BCY30 55p	TIP29 35p	
<b>ELECTROLYTIC CAP (25V)</b> 1uF to 50uF/25V 6p 68/50, 100/25V 7p 150/40V 8p 220/25V 9p 500/35V 14p 1000/25V 22p		<b>LINEARS</b> 709 40p 710 33p 747-14 48p 748-8 44p CA301B 86p CA302BA 90p CA3046 70p CA3054 120p CA3080 75p CA3130 100p CA3140 45p LF351N 65p LF356N 85p LM301AN 32p LM308N 80p LM318 200p LM324 74p		LM3900N 55p	7475	26p	74199 107p	AC141 20p	BCY34 66p	TIP298 40p	
<b>DIL SOCKETS</b> 8pin 11p 14pin 13p 16pin 14p 18pin 18p 22pin 22p 24pin 24p 28pin 28p 40pin 40p		<b>DIODES</b> BY127 10p OA47 8p OA91 8p OA200 6p OA202 9p 1N914 4p 1N916 5p 1N4148 4p		LM3909N 70p	7476	40p	4000 14p	AC142 20p	8CY59 26p	TIP30 35p	
<b>BRIDGE RECTIFIERS</b> 75A/200V 25p 75A/600V 32p 1A/50V 22p 1A/100V 27p 1A/200V 32p		<b>CMOS</b> 4001 14p 4002 14p 4006 78p 4007 15p 4008 66p 4009 32p 4010 42p 4011 43p 4012 14p 4013 32p 4014 85p 4015 54p 4016 32p 4017 53p 4018 59p 4019 43p 4020 53p 4021 64p 4022 53p 4023 14p 4024 43p 4025 14p 4027 32p 4028 48p 4029 54p 4030 32p 4035 107p 4041 78p 4042 58p 4043 64p 4044 72p 4047 85p 4048 48p 4049 27p 4050 27p 4066 38p 4069 13p 4070 14p 4071 14p 4072 14p 4073 17p 4081 14p 4082 14p 4086 65p 4510 69p 4511 75p 4516 69p 4518 69p 4520 69p		MC1496P 85p	7480	40p	4528 85p	AC151 27p	8CY70 16p	TIP30B 40p	TIP31 40p
<b>STEREO CASSETTE TAPE DECK ASSEMBLY</b>		<b>TTL</b> 7400 11p 7401 11p 7402 11p 7403 11p 7404 13p 7405 13p 7406 26p 7407 26p 7408 13p 7409 13p 7410 13p 7411 16p 7412 16p 7413 27p 7414 48p 7415 25p 7417 25p 7420 13p 7421 21p 7422 16p 7427 22p 7428 26p 7430 13p 7432 20p 7433 30p 7434 19p 7438 19p 7440 12p 7441 49p 7442 43p 7443 60p 7444 64p 7445 60p 7446 53p 7447 53p 7448 53p 7450 13p 7451 13p		NE561 105p	7485	64p	4528 85p	AC153 32p	8CY71 18p	TIP32 40p	TIP33 64p
<b>STEREO CASSETTE TAPE DECK ASSEMBLY</b>		<b>CMOS</b> 4000 14p 4001 14p 4002 14p 4006 78p 4007 15p 4008 66p 4009 32p 4010 42p 4011 43p 4012 14p 4013 32p 4014 85p 4015 54p 4016 32p 4017 53p 4018 59p 4019 43p 4020 53p 4021 64p 4022 53p 4023 14p 4024 43p 4025 14p 4027 32p 4028 48p 4029 54p 4030 32p 4035 107p 4041 78p 4042 58p 4043 64p 4044 72p 4047 85p 4048 48p 4049 27p 4050 27p 4066 38p 4069 13p 4070 14p 4071 14p 4072 14p 4073 17p 4081 14p 4082 14p 4086 65p 4510 69p 4511 75p 4516 69p 4518 69p 4520 69p		NE565 25p	7486	26p	4528 85p	AC176 20p	8CY72 18p	TIP34 64p	TIP35 80p
<b>STEREO CASSETTE TAPE DECK ASSEMBLY</b>		<b>CMOS</b> 4000 14p 4001 14p 4002 14p 4006 78p 4007 15p 4008 66p 4009 32p 4010 42p 4011 43p 4012 14p 4013 32p 4014 85p 4015 54p 4016 32p 4017 53p 4018 59p 4019 43p 4020 53p 4021 64p 4022 53p 4023 14p 4024 43p 4025 14p 4027 32p 4028 48p 4029 54p 4030 32p 4035 107p 4041 78p 4042 58p 4043 64p 4044 72p 4047 85p 4048 48p 4049 27p 4050 27p 4066 38p 4069 13p 4070 14p 4071 14p 4072 14p 4073 17p 4081 14p 4082 14p 4086 65p 4510 69p 4511 75p 4516 69p 4518 69p 4520 69p		NE566 140p	7489	30p	4528 85p	AC187 21p	8CY73 18p	TIP36 220p	TIP37 80p
<b>STEREO CASSETTE TAPE DECK ASSEMBLY</b>		<b>CMOS</b> 4000 14p 4001 14p 4002 14p 4006 78p 4007 15p 4008 66p 4009 32p 4010 42p 4011 43p 4012 14p 4013 32p 4014 85p 4015 54p 4016 32p 4017 53p 4018 59p 4019 43p 4020 53p 4021 64p 4022 53p 4023 14p 4024 43p 4025 14p 4027 32p 4028 48p 4029 54p 4030 32p 4035 107p 4041 78p 4042 58p 4043 64p 4044 72p 4047 85p 4048 48p 4049 27p 4050 27p 4066 38p 4069 13p 4070 14p 4071 14p 4072 14p 4073 17p 4081 14p 4082 14p 4086 65p 4510 69p 4511 75p 4516 69p 4518 69p 4520 69p		TBA641A 200p	7493	25p	4528 85p	AC188 21p	8CY74 18p	TIP38 200p	TIP39 220p
<b>STEREO CASSETTE TAPE DECK ASSEMBLY</b>		<b>CMOS</b> 4000 14p 4001 14p 4002 14p 4006 78p 4007 15p 4008 66p 4009 32p 4010 42p 4011 43p 4012 14p 4013 32p 4014 85p 4015 54p 4016 32p 4017 53p 4018 59p 4019 43p 4020 53p 4021 64p 4022 53p 4023 14p 4024 43p 4025 14p 4027 32p 4028 48p 4029 54p 4030 32p 4035 107p 4041 78p 4042 58p 4043 64p 4044 72p 4047 85p 4048 48p 4049 27p 4050 27p 4066 38p 4069 13p 4070 14p 4071 14p 4072 14p 4073 17p 4081 14p 4082 14p 4086 65p 4510 69p 4511 75p 4516 69p 4518 69p 4520 69p		TBA641B 200p	7494	25p	4528 85p	AC189 21p	8CY75 18p	TIP40 200p	TIP41 220p
<b>STEREO CASSETTE TAPE DECK ASSEMBLY</b>		<b>CMOS</b> 4000 14p 4001 14p 4002 14p 4006 78p 4007 15p 4008 66p 4009 32p 4010 42p 4011 43p 4012 14p 4013 32p 4014 85p 4015 54p 4016 32p 4017 53p 4018 59p 4019 43p 4020 53p 4021 64p 4022 53p 4023 14p 4024 43p 4025 14p 4027 32p 4028 48p 4029 54p 4030 32p 4035 107p 4041 78p 4042 58p 4043 64p 4044 72p 4047 85p 4048 48p 4049 27p 4050 27p 4066 38p 4069 13p 4070 14p 4071 14p 4072 14p 4073 17p 4081 14p 4082 14p 4086 65p 4510 69p 4511 75p 4516 69p 4518 69p 4520 69p		TBA800 75p	7495	35p	4528 85p	AC190 21p	8CY76 18p	TIP42 200p	TIP43 220p
<b>STEREO CASSETTE TAPE DECK ASSEMBLY</b>		<b>CMOS</b> 4000 14p 4001 14p 4002 14p 4006 78p 4007 15p 4008 66p 4009 32p 4010 42p 4011 43p 4012 14p 4013 32p 4014 85p 4015 54p 4016 32p 4017 53p 4018 59p 4019 43p 4020 53p 4021 64p 4022 53p 4023 14p 4024 43p 4025 14p 4027 32p 4028 48p 4029 54p 4030 32p 4035 107p 4041 78p 4042 58p 4043 64p 4044 72p 4047 85p 4048 48p 4049 27p 4050 27p 4066 38p 4069 13p 4070 14p 4071 14p 4072 14p 4073 17p 4081 14p 4082 14p 4086 65p 4510 69p 4511 75p 4516 69p 4518 69p 4520 69p		TBA810 110p	7496	45p	4528 85p	AC191 21p	8CY77 18p	TIP44 200p	TIP45 220p
<b>STEREO CASSETTE TAPE DECK ASSEMBLY</b>		<b>CMOS</b> 4000 14p 4001 14p 4002 14p 4006 78p 4007 15p 4008 66p 4009 32p 4010 42p 4011 43p 4012 14p 4013 32p 4014 85p 4015 54p 4016 32p 4017 53p 4018 59p 4019 43p 4020 53p 4021 64p 4022 53p 4023 14p 4024 43p 4025 14p 4027 32p 4028 48p 4029 54p 4030 32p 4035 107p 4041 78p 4042 58p 4043 64p 4044 72p 4047 85p 4048 48p 4049 27p 4050 27p 4066 38p 4069 13p 4070 14p 4071 14p 4072 14p 4073 17p 4081 14p 4082 14p 4086 65p 4510 69p 4511 75p 4516 69p 4518 69p 4520 69p		ZN414 100p	7497	128p	4528 85p	AC192 21p	8CY78 18p	TIP46 200p	TIP47 220p
<b>STEREO CASSETTE TAPE DECK ASSEMBLY</b>		<b>CMOS</b> 4000 14p 4001 14p 4002 14p 4006 78p 4007 15p 4008 66p 4009 32p 4010 42p 4011 43p 4012 14p 4013 32p 4014 85p 4015 54p 4016 32p 4017 53p 4018 59p 4019 43p 4020 53p 4021 64p 4022 53p 4023 14p 4024 43p 4025 14p 4027 32p 4028 48p 4029 54p 4030 32p 4035 107p 4041 78p 4042 58p 4043 64p 4044 72p 4047 85p 4048 48p 4049 27p 4050 27p 4066 38p 4069 13p 4070 14p 4071 14p 4072 14p 4073 17p 4081 14p 4082 14p 4086 65p 4510 69p 4511 75p 4516 69p 4518 69p 4520 69p		ZN1034 200p	7499	128p	4528 85p	AC193 21p	8CY79 18p	TIP48 200p	TIP49 220p
<b>STEREO CASSETTE TAPE DECK ASSEMBLY</b>		<b>CMOS</b> 4000 14p 4001 14p 4002 14p 4006 78p 4007 15p 4008 66p 4009 32p 4010 42p 4011 43p 4012 14p 4013 32p 4014 85p 4015 54p 4016 32p 4017 53p 4018 59p 4019 43p 4020 53p 4021 64p 4022 53p 4023 14p 4024 43p 4025 14p 4027 32p 4028 48p 4029 54p 4030 32p 4035 107p 4041 78p 4042 58p 4043 64p 4044 72p 4047 85p 4048 48p 4049 27p 4050 27p 4066 38p 4069 13p 4070 14p 4071 14p 4072 14p 4073 17p 4081 14p 4082 14p 4086 65p 4510 69p 4511 75p 4516 69p 4518 69p 4520 69p		7400 11p	74100	80p	4528 85p	AC194 21p	8CY80 18p	TIP50 200p	TIP51 220p
<b>STEREO CASSETTE TAPE DECK ASSEMBLY</b>		<b>CMOS</b> 4000 14p 4001 14p 4002 14p 4006 78p 4007 15p 4008 66p 4009 32p 4010 42p 4011 43p 4012 14p 4013 32p 4014 85p 4015 54p 4016 32p 4017 53p 4018 59p 4019 43p 4020 53p 4021 64p 4022 53p 4023 14p 4024 43p 4025 14p 4027 32p 4028 48p 4029 54p 4030 32p 4035 107p 4041 78p 4042 58p 4043 64p 4044 72p 4047 85p 4048 48p 4049 27p 4050 27p 4066 38p 4069 13p 4070 14p 4071 14p 4072 14p 4073 17p 4081 14p 4082 14p 4086 65p 4510 69p 4511 75p 4516 69p 4518 69p 4520 69p		74105 43p	74107	80p	4528 85p	AC195 21p	8CY81 18p	TIP52 200p	TIP53 220p
<b>STEREO CASSETTE TAPE DECK ASSEMBLY</b>		<b>CMOS</b> 4000 14p 4001 14p 4002 14p 4006 78p 4007 15p 4008 66p 4009 32p 4010 42p 4011 43p 4012 14p 4013 32p 4014 85p 4015 54p 4016 32p 4017 53p 4018 59p 4019 43p 4020 53p 4021 64p 4022 53p 4023 14p 4024 43p 4025 14p 4027 32p 4028 48p 4029 54p 4030 32p 4035 107p 4041 78p 4042 58p 4043 64p 4044 72p 4047 85p 4048 48p 4049 27p 4050 27p 4066 38p 4069 13p 4070 14p 4071 14p 4072 14p 4073 17p 4081 14p 4082 14p 4086 65p 4510 69p 4511 75p 4516 69p 4518 69p 4520 69p		74107 20p	74109	80p	4528 85p	AC196 21p	8CY82 18p	TIP54 200p	TIP55 220p
<b>STEREO CASSETTE TAPE DECK ASSEMBLY</b>		<b>CMOS</b> 4000 14p 4001 14p 4002 14p 4006 78p 4007 15p 4008 66p 4009 32p 4010 42p 4011 43p 4012 14p 4013 32p 4014 85p 4015 54p 4016 32p 4017 53p 4018 59p 4019 43p 4020 53p 4021 64p 4022 53p 4023 14p 4024 43p 4025 14p 4027 32p 4028 48p 4029 54p 4030 32p 4035 107p 4041 78p 4042 58p 4043 64p 4044 72p 4047 85p 4048 48p 4049 27p 4050 27p 4066 38p 4069 13p 4070 14p 4071 14p 4072 14p 4073 17p 4081 14p 4082 14p 4086 65p 4510 69p 4511 75p 4516 69p 4518 69p 4520 69p		74109 20p	74111	80p	4528 85p	AC197 21p	8CY83 18p	TIP56 200p	TIP57 220p
<b>STEREO CASSETTE TAPE DECK ASSEMBLY</b>		<b>CMOS</b> 4000 14p 4001 14p 4002 14p 4006 78p 4007 15p 4008 66p 4009 32p 4010 42p 4011 43p 4012 14p 4013 32p 4014 85p 4015 54p 4016 32p 4017 53p 4018 59p 4019 43p 4020 53p 4021 64p 4022 53p 4023 14p 4024 43p 4025 14p 4027 32p 4028 48p 4029 54p 4030 32p 4035 107p 4041 78p 4042 58p 4043 64p 4044 72p 4047 85p 4048 48p 4049 27p 4050 27p 4066 38p 4069 13p 4070 14p 4071 14p 4072 14p 4073 17p 4081 14p 4082 14p 4086 65p 4510 69p 4511 75p 4516 69p 4518 69p 4520 69p		74111 42p	74118	80p	4528 85p	AC198 21p	8CY84 18p	TIP58 200p	TIP59 220p
<b>STEREO CASSETTE TAPE DECK ASSEMBLY</b>		<b>CMOS</b> 4000 14p 4001 14p 4002 14p 4006 78p 4007 15p 4008 66p 4009 32p 4010 42p 4011 43p 4012 14p 4013 32p 4014 85p 4015 54p 4016 32p 4017 53p 4018 59p 4019 43p 4020 53p 4021 64p 4022 53p 4023 14p 4024 43p 4025 14p 4027 32p 4028 48p 4029 54p 4030 32p 4035 107p 4041 78p 4042 58p 4043 64p 4044 72p 4047 85p 4048 4									


# TRANDAM

# COMPUTER PRODUCTS
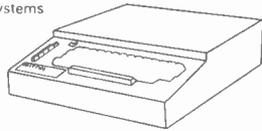
## TRITON

SINGLE BOARD PERSONAL COMPUTER

Three new exciting expandable systems designed for ease of construction and flexibility. Kits come complete with case, power supply, full keyboard, PCB. All components available separately, see catalogue. Full hardware and programming manual available. The system is easy to expand and is well supported.



- Single board
- Holds up to 8k memory
- UHF or Video output
- Cassette interface

- Three firmware options
- Basic in Eprom
- 64 graphics characters
- Plug in expandable boards


### Personal Computer

**£286 FROM + VAT**
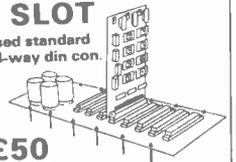
## EXPANSION MOTHERBOARD

TRITON. Expand your Triton simply and easily with our new 8-slot motherboard complete with its own P.S.U. takes 8 plug-in Euro cards. Plug-in 8k RAM card and Eprom cards now available. Kit complete with P.S.U. + 1 set connectors.


**8 SLOT**  
Used standard 64-way din con.



**£50 + VAT**
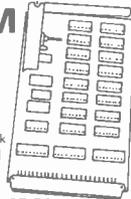
## 8K RAM CARD


Triton 8k static Ram card kit uses 2114L low power 4k static rams on board regulation Mem jump select  
PCB only **£15**. Rams **£5.50**.  
Kit less Rams **£31** (incl 5 skts + components).



COMPLETE KIT  
**£97 + VAT**
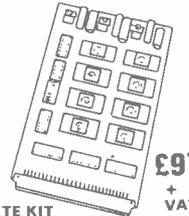
## 8K EPROM CARD

Triton 8k Eprom card kit designed to take up to 8 x 2708 Eproms (1k x 8) as Ram card PCB only **£15**  
Kit less Eproms **£31**  
Eproms (blank) **£9**  
Plus VAT



**£97 + VAT**

COMPLETE KIT

## BI DIRECTIONAL MATRIX PRINTER

**£595 + VAT**

The 8D80 is a low cost 80 column line printer with microprocessor control to provide excellent reliability and performance.

- 5 x 7 dot matrix
- 10 char per inch
- 6 lines / inch
- 400 char buffer
- Full ASCII char set
- 10 lines / sec paper advance
- 112 char / sec
- 84 lines per minute
- Self-test
- Fully cased



A UNIQUE PRINTER FAST AND RELIABLE


Switch selectable band rate from 110 to 9600 on a standard V24 and RS232C interface. Send SAE for further details. Ideal printer for Triton or any system requiring high-speed, reliable hard copy. We can supply consumables.

## VIDEO MONITOR

NEW

A brand new, fully cased (metal) high resolution 10" video monitor with PSB for only **£69 + VAT**. Ideal for Triton, or any home computer system. Carriage by Securicon can be arranged. Send SAE for details or see our new catalogue.

**ONLY £69! + VAT**

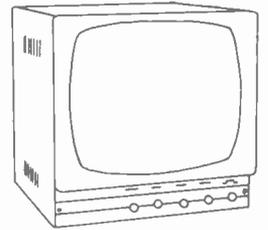

## PCB CONNECTORS

Extra connectors (odd contact) double sided PCB connectors.


1.1"	Price	1.56"	Price
22 44	<b>£3.20</b>	20	<b>£1.62</b>
25/50	<b>£3.60</b>	10 20	<b>£1.90</b>
28/56	<b>£3.90</b>	15 30	<b>£3.00</b>
30/60	<b>£4.15</b>	18 36	<b>£3.00</b>
35 70	<b>£4.60</b>	22 44	<b>£3.00</b>
36 72	<b>£4.75</b>	28 56	<b>£3.40</b>
40 80	<b>£5.00</b>	36 72	<b>£3.90</b>
43 86	<b>£5.50</b>	43 82	<b>£4.60</b>
50 100	<b>£5.80</b>	50 100	<b>£5.80</b>



+ VAT
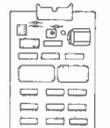
## VIDEO DISPLAY INTERFACE MODULE

Completely built and tested the SFXE x 68364 card uses the industry standard SFF46364 CRT control chip and allows ASCII parallel input of data to be output to video monitor 64 character by 16 line display, full cursor control single 5V supply. Full details available on request (send SAE) UHF modulator available **£2.50 extra + VAT**.



**£69 + VAT**

## COMPONENTS 74LSXX

SN74LS00N .18	SN74LS54N .21	SN74LS138N .75	SN74LS195AN .85	SN74LS325N 2.56
SN74LS01N .18	SN74LS55N .21	SN74LS139N .75	SN74LS196N 1.20	SN74LS326N 2.55
SN74LS02N .20	SN74LS563N 1.50	SN74LS145N 1.20	SN74LS197N 1.20	SN74LS327N 2.95
SN74LS03N .18	SN74LS573N .35	SN74LS148N 1.75	SN74LS221N 1.25	SN74LS352N 1.35
SN74LS04N .20	SN74LS574N .40	SN74LS151N .85	SN74LS240N 2.20	SN74LS353N 1.50
SN74LS05N .26	SN74LS575N .46	SN74LS153N .80	SN74LS241N 1.99	SN74LS365N .85
SN74LS08N .20	SN74LS676N .35	SN74LS154N 1.60	SN74LS242N 1.90	SN74LS365AN .85
SN74LS09N .22	SN74LS678N .35	SN74LS155N 1.25	SN74LS243N 1.95	SN74LS367 N .65
SN74LS10N .18	SN74LS683AN 1.15	SN74LS158N 1.25	SN74LS244N 2.10	SN74LS368AN .85
SN74LS11N .26	SN74LS685N 1.10	SN74LS157N .80	SN74LS245N 2.00	SN74LS373N 1.75
SN74LS12N .25	SN74LS686N .40	SN74LS158N .90	SN74LS247N 1.25	SN74LS374N 1.70
SN74LS13N .55	SN74LS690N .65	SN74LS160N 1.15	SN74LS248N 1.99	SN74LS375N .72
SN74LS14N .89	SN74LS691N .90	SN74LS161N 1.15	SN74LS249N 1.30	SN74LS377N 1.75
SN74LS15N .25	SN74LS692N .90	SN74LS162N 1.15	SN74LS251N 1.45	SN74LS379N 1.32
SN74LS20N .20	SN74LS693AN .85	SN74LS163N .90	SN74LS253N 1.25	SN74LS379N 1.40
SN74LS21N .26	SN74LS694N 1.20	SN74LS164N 1.50	SN74LS257N 1.40	SN74LS361N 3.65
SN74LS22N .26	SN74LS696N 1.75	SN74LS165N 1.70	SN74LS258N .95	SN74LS368N .57
SN74LS26N .29	SN74LS697N .30	SN74LS166N 1.75	SN74LS259N 1.45	SN74LS390N 1.90
SN74LS27N .35	SN74LS698N .39	SN74LS168N 1.95	SN74LS260N .95	SN74LS393N 1.50
SN74LS28N .35	SN74LS699N .30	SN74LS169N 1.95	SN74LS261N 3.50	SN74LS395N 1.80
SN74LS30N .25	SN74LS711N .44	SN74LS170N 2.50	SN74LS266N .30	SN74LS396N 1.70
SN74LS32N .27	SN74LS713N .44	SN74LS173N 2.20	SN74LS273N 1.65	SN74LS398N 1.75
SN74LS33N .39	SN74LS715N .79	SN74LS174N 1.15	SN74LS275N .79	SN74LS399N 1.60
SN74LS37N .30	SN74LS716N .90	SN74LS175N 1.05	SN74LS280N 1.75	SN74LS424N 4.50
SN74LS38N .29	SN74LS718N 1.90	SN74LS181N 2.75	SN74LS283N 1.80	SN74LS445N 1.25
SN74LS40N .25	SN74LS725N .65	SN74LS190N 1.75	SN74LS290N 1.80	SN74LS447N 1.25
SN74LS42N .79	SN74LS726N .65	SN74LS191N 1.75	SN74LS293N 1.80	SN74LS490N 1.95
SN74LS47N .95	SN74LS732N .75	SN74LS192N 1.45	SN74LS295AN 2.20	SN74LS668N .85
SN74LS48N .95	SN74LS733N .39	SN74LS193N 1.75	SN74LS298N 2.20	SN74LS669N .95
SN74LS49N 1.09	SN74LS734N .40	SN74LS194AN 1.99	SN74LS324N 1.80	SN74LS670N 2.70

## MEMORY AND SUPPORT CHIPS (PRICES EXCLUDE VAT)

SUPPORT	RAMS	EPROMS	ROMS	VOLTS REGS	CRYSTALS	MISCLE
8212 2.20	2101 2.32	1702 6.00	LM555N .75	7805 .90	100K 3.09	2513 7.50
8216 2.80	2102.4 1.20	5204 8.00	LM7808N .37	7812 .90	200K 3.70	MS6011 5.00
8224 2.20	2111 2.32	2708 9.00	LM7809N .36	7815 .90	1MHz 3.68	MC14411 12.00
8226 2.20	2112 2.46	2516 28.00	LM723CN .50	7824 .90	1068K 3.50	MC14412 2.90
8228 4.20	2114 4.06	2716 22.00	LM723CN .43	7805K 1.50	96364 10.95	
8238 4.20	6810 8.18	7428 3.70	LM733CN 1.30	7812K 1.50	1813K 3.00	
8245 11.00	8154 5.50	7428T 12.00	LM739CN 1.30	7815K 1.50	2MHz 1.50	CPUs
8246 11.00	2114 1.50	7428T 12.00	LM741CN 14 .33	7824K 1.50	2157K 3.05	8080 6.33
8251 5.00	74C920 11.00	7428T 12.00	LM741CN 8 .25	7905 1.10	3276K 2.70	6800 10.00
8253 11.00	74C921 11.00	74579 12.48	LM747CN 14 .79	7912 1.10	3MHz 3.05	780 8.00
8255 5.00	74C929 11.00	745474 12.48	LM747CN 1.19	7915 1.10	4MHz 2.10	280A 15.00
8257 11.00	74C929 11.00	745474 12.48	LM748CN 8 .45	7924 1.10	4.5MHz 1.60	8085 12.95
8259 12.58	4044 14.70	r/D 12.90	LM748CN 4 .46	7905K 1.80	5MHz 2.70	5502 8.00
8292 18.00	4045 9.15	2513 7.50	LM748CN 8 .48	7912K 1.80	6MHz 2.70	SCMP0 10.00
6820P 4.50	4060 7.00	96364 13.12	LM1458N 8 .48	7915K 1.56	7MHz 2.70	6802 13.45
6821P 4.50	4060 7.00	13412 12.90	LM14880 .95	7924K 1.80	7.168M 2.50	9900 30.00
6829P 4.50	4060 7.50	LINEARS	LM14890 .65	8MHz 2.70	8MHz 2.70	W/WRAP SKTS
AY 5 2376 11.90	2107 7.00	LM301AN .39	LM1489AD .09	10MHz 2.70	10MHz 2.70	8 DL .20
MC14411 12.00	4116 8.00	LM301AN B 20.00	LM1496N 14 .05	14 DL .15	18M 2.90	14 DL .35
MS7109 12.43	4118 20.00	(Mem Duj) .30	LM3302N .85	18 DL .17	48M 2.90	16 DL .42
MS7160 10.00	280P10 10.00	LM309N .99	LM3401N .65	18 DL .24	18 DL .24	18 DL .60
MS7161 10.00	280 CTC 10.00	LM309K .99	LM3403N 1.29	18 DL .24	20 DL .27	24 DL .52
MS8011 5.00	280A P10 14.00	LM311H 1.45	LM3909N .54	20 DL .20	30 DL .20	24 DL .74
81LS95 1.80	280A CTC 14.00	LM311H 1.29	LM3909P 1.49	24 DL .36	CD 4911 .15	28 DL .74
81LS96 1.80	280A CTC 14.00	LM311H 1.29	LM3909P 1.49	28 DL .36	CD 4916 .70	40 DL .95
81LS97 1.80		LM322K 6.00	LM392CP 1.29	38 DL .50		
81LS98 1.80		LM322AN .79	LM392CN 1.65			
		LM339N .54	LM392CN 1.66			

## TRITON DOCUMENTATION

Available separately as follows. Prices include P&P.

- Triton manual — detailed circuit description + constructional details + user documentation on level 4-1 monitor. Basic **£5.70**
- L4 1 Listing + listing of 1k monitor + 2k tiny basic **£4.20**
- L5 1 user documentation on level 5-1 firmware **£1.20**
- L5 1 Listing + listing of 1.5k monitor and 2.5k basic **£5.20**
- L6 1 User documentation on 7k basic interpreter **£1.70**

Motherboard, Bk Ram and 8k Eprom constructional details User Group Newsletter subscription, £4 per annum Triton software. Send SAE for list of programs available from Triton **£5.00**

## HOME COMPUTING CATALOGUE

If you're in town, visit our showroom in Chapel Street, next to Edgware Road tube station. We have Tritons on display plus a comprehensive range of components and accessories, specifically for personal computer users. Books, mags, tapes, data, cables, plus much more. Showroom open 6 days a week (half day Thurs from 1 30)



**NEW**  
A4 size catalogue filled with our latest products 40p + SAE ALL PRICES EXCLUDE VAT

# TRANDAM



ELECTRONICS TODAY INTERNATIONAL — OCTOBER 1979

# VAT ALL PRICES EXCLUDE VAT

TRANSAM COMPONENTS LTD.  
12 CHAPEL STREET  
LONDON, NW1 TEL. 402 8137

# Cambridge Learning Enterprises

## SELF-INSTRUCTION COURSES

### UNDERSTANDING DIGITAL ELECTRONICS

In the years ahead the products of digital electronics technology will play an important part in your life. Calculators and digital watches are already commonplace. Tomorrow a digital display could show your vehicle speed and fuel consumption; you could be 'phoning people by entering their name into a telephone which would automatically look up their number and dial it for you.

These courses were written by experts in electronics and learning systems so that you could teach yourself the theory and application of digital logic. Learning by self-instruction has the advantages of being faster and more thorough than classroom learning. You work at your own pace and must respond by answering questions on each new piece of information before proceeding.

After completing these courses you will have broadened your career prospects and increased your fundamental understanding of the rapidly changing technological world around you.



**Digital Computer Logic and Electronics** is designed for the beginner. No mathematical knowledge other than simple arithmetic is assumed, though the student should have an aptitude for logical thought. It consists of four volumes - each A4 size - and serves as an introduction to the subject of digital electronics. Everyone can learn from it - designer, executive, scientist, student, engineer.

Contents include: Binary, octal and decimal number systems; conversion between number systems, AND, OR, NOR and NAND gates and inverters; Boolean algebra and truth tables; De Morgans Laws; design of logic circuits using NOR gates; R-S and J-K flip flops; binary counters, shift registers and half adders.

**FLOW CHARTS & ALGORITHMS** help you present: safety procedures, government legislation, office procedures, teaching materials and computer programs by means of YES and NO answers to questions.

### The Algorithm Writer's Guide


explains how to: define the questions, put them in the best order and draw the flow chart, with numerous examples shown. All that students require is an aptitude for logical thought. Size: A5, 130 pages. This book is a **MUST** for those with things to say.

**NEW** from Cambridge Learning Enterprises
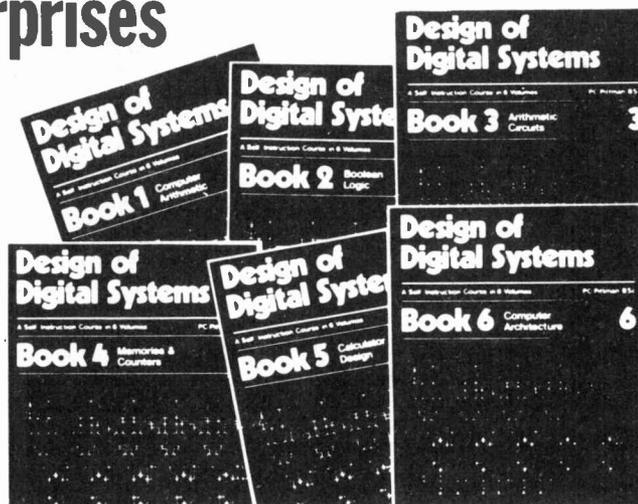
### O - LEVEL ENGLISH LANGUAGE

More and more jobs require a C-GRADE PASS, and over 250,000 people fail to get this every year. Will one of them be in your family? This new course, written by experts in a style that's serious yet fun to read, shows you how to mark your own work and compare it with the work of other people in their exam year. Set your own pace and assess your results immediately with no postal delays: watch your speed and standards improve. In Book 1 learn how you will be marked on **COMPREHENSION**, Book 2 covers **SUMMARY**, **PUNCTUATION & SPELLING**, and Book 3 coaches you in the principles of **COMPOSITION**. Size: 3 A4 volumes totalling 250 pages.

**CAMBRIDGE LEARNING ENTERPRISES, UNIT 13  
RIVERMILL SITE, FREEPOST, ST. IVES, HUNTINGDON,  
CAMBS. PE17 4BR, ENGLAND  
TELEPHONE: ST. IVES (0480) 67446.  
PROPRIETORS: DAYRIDGE LTD. REG. OFFICE: RIVERMILL LODGE, ST. IVES  
REGD. IN ENGLAND No. 1328762**



**Design of Digital Systems** is written for the engineer seeking to learn more about digital electronics. Its six volumes - each A4 size are packed with information, diagrams and questions designed to lead you step-by-step through number systems and Boolean algebra to memories, counters and simple arithmetic circuits, and finally to a complete understanding of the design and operation of calculators and computers. Contents include:

**Book 1** Octal, hexadecimal and binary number systems; conversion between number systems; representation of negative numbers; complementary systems; binary multiplication and division.

**Book 2** OR and AND functions; logic gates; NOT, exclusive-OR, NAND, NOR and exclusive-NOR functions; multiple input gates; truth tables; De Morgans Laws; canonical forms; logic conventions; Karnaugh mapping; three-state and wired logic.

**Book 3** Half adders and full adders; subtractors; serial and parallel adders; processors and arithmetic logic units (ALUs); multiplication and division systems.

**Book 4** Flip flops; shift registers; asynchronous and synchronous counters; ring, Johnson and exclusive-OR feedback counters; random access memories (RAMs) and read only memories (ROMs).

**Book 5** Structure of calculators; keyboard encoding; decoding display data; register systems; control unit; program ROM; address decoding; instruction sets; instruction decoding; control programme structure.

**Book 6** Central processing unit (CPU); memory organization; character representation; program storage; address modes; input/output systems; program interrupts; interrupt priorities; programming; assemblers; computers; executive programs; operating systems and time sharing.

Four volumes Digital Computer Logic & Electronics at £6.50 inc p & p  
Six volumes Design of Digital Systems at £10.50 inc p & p  
Three volumes O-Level English Language at £6.50 inc p & p  
The Algorithm Writer's Guide at £3.40 inc p & p  
If your order exceeds £14 deduct £2 from your payment  
Price includes surface mail anywhere in the world, airmail extra  
**GUARANTEE** If you are not entirely satisfied your money will be refunded  
Please allow 21 days for delivery

Cambridge Learning Enterprises, Unit 13 Rivermill Site, FREEPOST, St. Ives, Huntingdon, Cambs. PE17 4BR, England.


Please send me the following books:  
..... sets Digital Computer Logic & Electronics at £6.50, p & p  
..... sets Design of Digital Systems at £10.50, p & p included  
..... O-Level English Language at £6.50 p & p included  
..... The Algorithm Writer's guide at £3.40, p & p included

Name .....  
Address .....

I enclose a \*cheque/PO payable to Cambridge Learning Enterprises for £.....  
Please charge my \*Access/Barclaycard/Visa/Eurocard/Mastercharge/Interbank account number .....

Signature..... \*delete as appropriate.  
Telephone orders from credit card holders accepted on 0480-67446 (Ansafone). Overseas customers should send a bank draft in sterling drawn on a London Bank, or quote credit card number.

# STRING THING

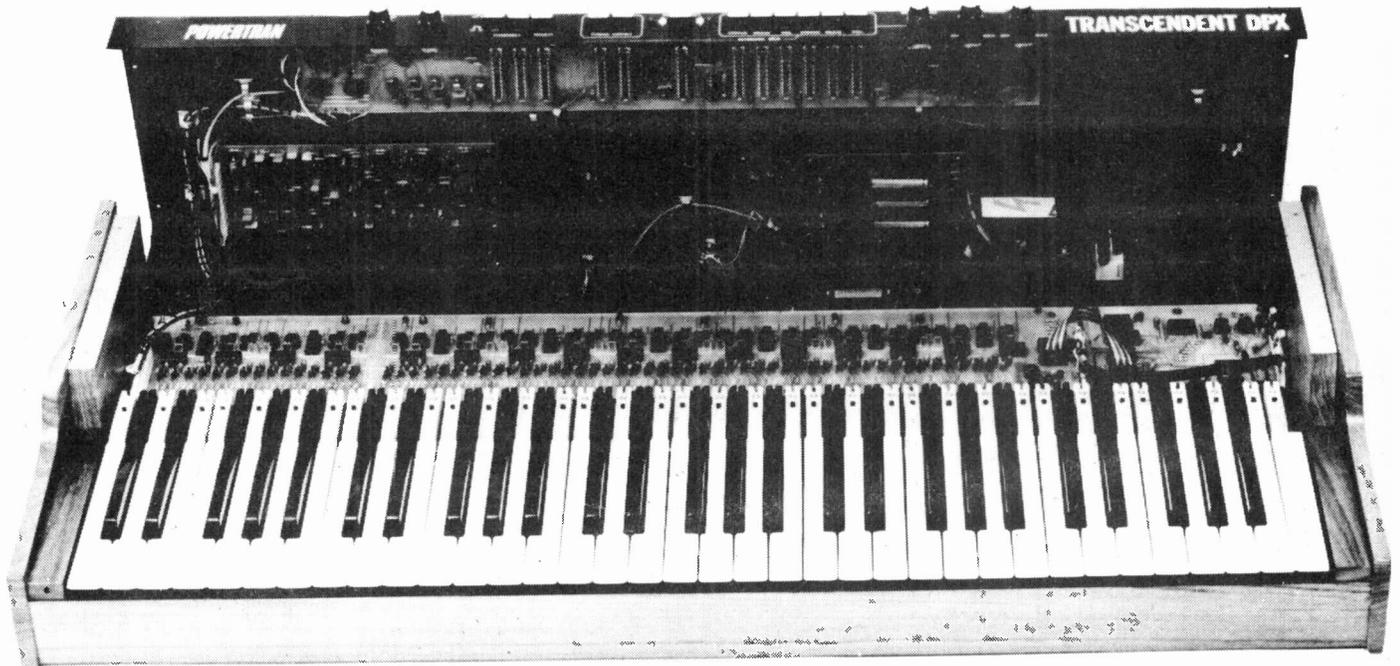

We continue this month with Part 3 of the String Thing Saga (Son of Part 2 from Tim Orr. For those of you who missed Part 2, String Thing, otherwise known as the Transcendent DPX, is a digital, polyphonic, multi-voice keyboard instrument. (We suspect it probably makes marvellous coffee too.)

Voicing is one of the stronger parameters that goes to characterise generated sound structures. The sounds in the DPX are built out of the same basic components, asymmetric squarewaves. The envelope contour is different for each type of instrument and vibrato can be added to emphasise the 'string' sound. However, all the voices, if they were left unfiltered would sound very much the same. But, by filtering the signals, it is possible to add a great deal of information to the sound structure. It must be remembered that natural instruments always sound very different from electronically produced ones, this being due to the incredibly complex structure of most instruments. If you have the opportunity to observe the low notes of a piano on an oscilloscope you will be amazed at the complexity of the signal.



**Part 3:** This month we bring you details of the String Thing's control circuitry and inter-board wiring.


## BUYLINES

Powertran Electronics are supplying a complete kit of parts for this project at £365+15% VAT. Delivery by Securicor is £2.50 extra. Everything is included in the kit, down to the last nut and bolt. They even give you a plug.


Powertran will also supply components, boards, etc separately. Please send an sae for details.

**Part 4:** Next month we conclude String Thing (no, we really mean it this time) with details of the power supply and dynamics boards, and the final constructional details to sort out your nuts and bolts.

Fig. 1. Circuit diagram of the voicing and control boards.

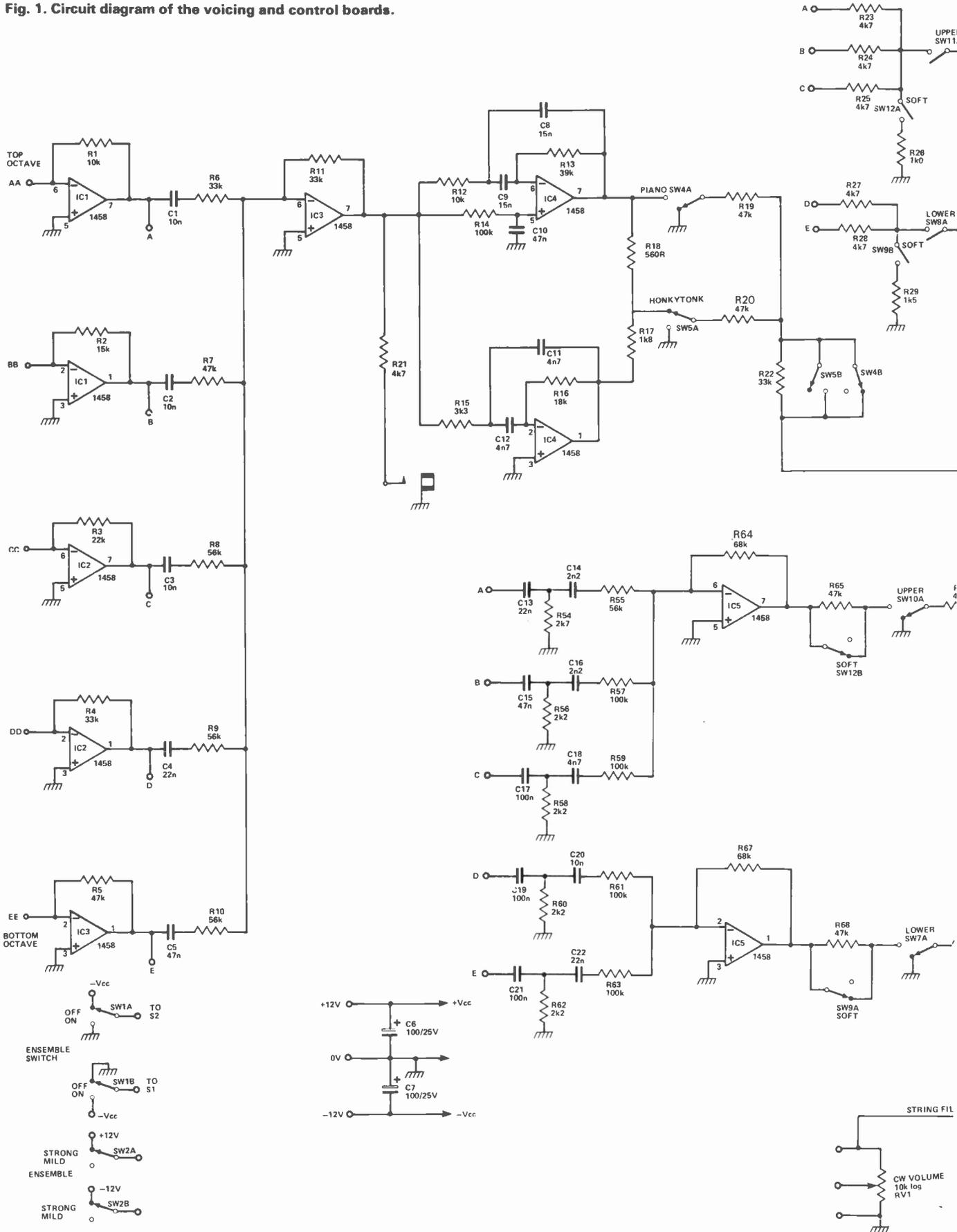

# PROJECT: String Thing

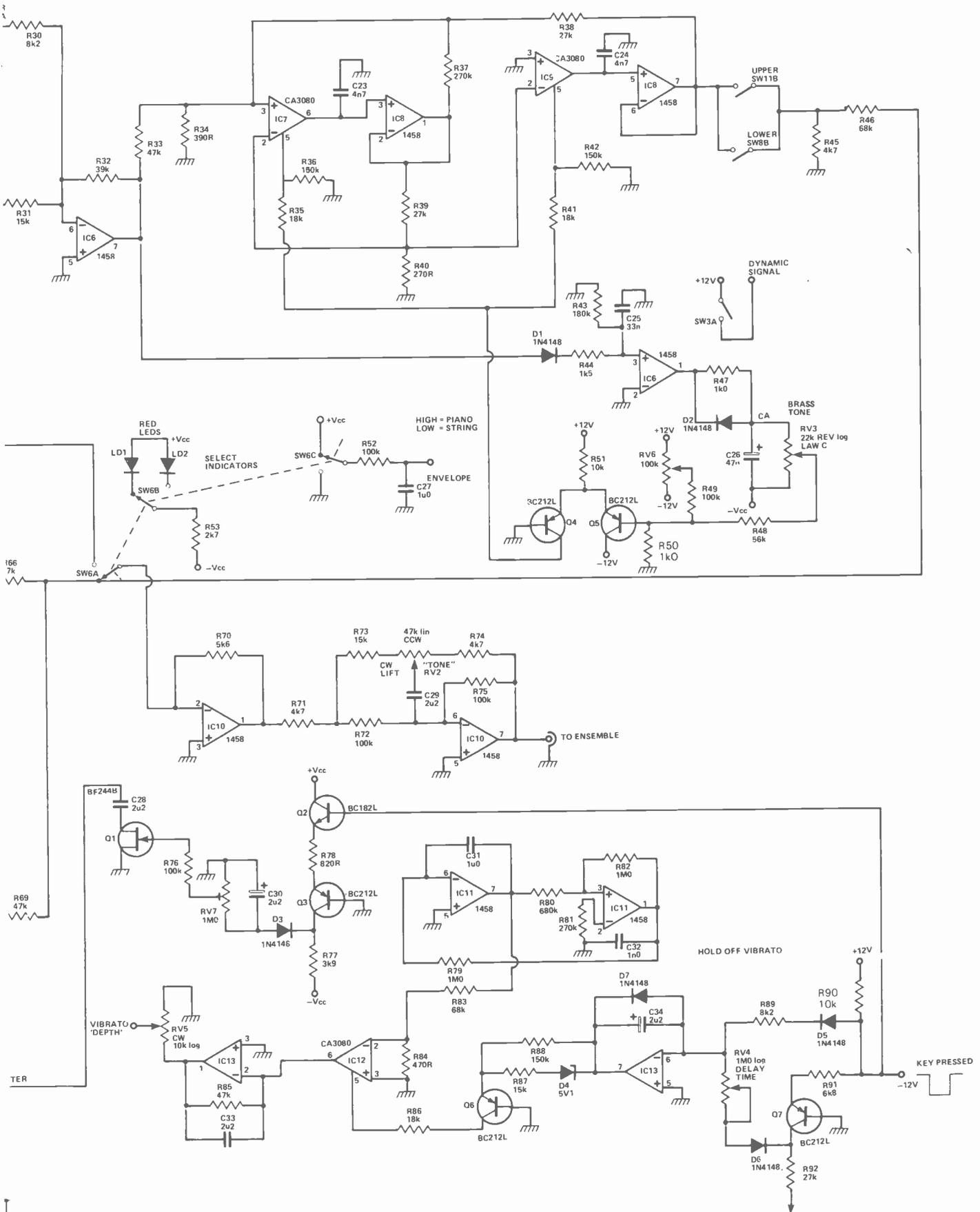

# HOW IT WORKS

Each octave of the keyboard is mixed together on the main note generating board. These five octave blocks of signals are fed into virtual earth amplifiers (IC1,2,3) which serve to correct the signal amplitudes. By careful circuit design and layout it is possible to reduce this breakthrough to 70 or 80 dB down on the individual note generating circuits, but the overall effect of 61 circuits, each contributing a slight amount, makes the overall background chorus much worse. Some organs are particularly bad with a performance of about 30 to 40 dB.

The signals from the input amplifiers are then split up and sent to various voicing circuits. The piano/honky-tonk section doesn't have a split keyboard option and so it is driven directly by the sum of all the octave signals. The piano voicing (IC4, pins 5,6,7) is a bandpass filter with a centre frequency of 500 Hz and a Q factor of 1. A slight low frequency lift has been added via R14,C13. This provides moderately pure sinusoids at the top end of the keyboard and much richer sounds at the low end. To obtain the honky-tonk sound, a second resonance is added (IC4, pins 1,2,3) at 5 kHz. This makes the sound much brighter.

The brass voice is a peaky low pass filter (IC6,7,8,9). The filter is swept up in

resonant frequency when a note is played, which greatly helps to characterise the brass sound. A tone control. (RV3) determines the depth of the sweep. Switches SW11a and SW8a select the upper and lower sections of the keyboard and switches SW12a and SW9b attenuate the signal level when the 'SOFT' mode is selected. The filter is tuned with a pair of CA3080's. As the current into their control input (pin 5) is increased, the resonant frequency of the filter is also increased. This current is generated by IC6, pins 1,2,3. When a note is played, the output of the op amp goes high, which is lowpass filtered by R47,C26. This voltage is used to sweep the brass filter via the common emitter pair Q4,Q5. PR2 is adjusted so that the filter sweep sounds correct.

The string voice (IC5) is composed of a set of high pass filters. The string sounds can be selected on upper and lower manuals (SW10a, SW7a), and there are also soft mode switches (SW12b, SW9a).

To reduce the effects of background and chorus/ensemble noise, a FET switch (Q1) is used to mute the output signal. When a note on the keyboard is pressed, the key-pressed signal goes low. This causes the collector of Q3 to fall to -12 V which turns off Q1. In this state the

output signal is not muted.

When the note is released, the collector of Q3 goes high. D3 is then reverse biased and the voltage on the gate of Q1 moves towards 0 V with a time constant of C30. PR1, which is selected to be slightly longer than the longest time constant of any note on the keyboard. As the gate voltage of Q1 approaches 0 V, Q1 turns on and mutes the output signal. RV1 is adjusted so that, with a key pressed, no attenuation is produced by Q1. The key-pressed signal is also used to start the hold-off vibrato circuit. IC11 is a Schmitt trigger/integrator oscillator which produces a low frequency triangle waveform (pin 7). This signal is fed into a CA3080 (IC12) which distorts the triangle by bending it into a sinewave shape. A buffer (IC13) is used to amplify and filter the 'sinewave' which is then used to modulate the master oscillator. The size of the sinewave is controlled by the current flowing into pin 5 of IC12. This current has a delay time constant which is determined by RV5. When a key is pressed, the collector of Q6 goes low and so C34 is charged up via RV5. The voltage on the end of C46 determines the current flowing into pin 5 of IC12. When the key is released, the collector of Q6 goes high and so C34 is discharged via R89,D5.

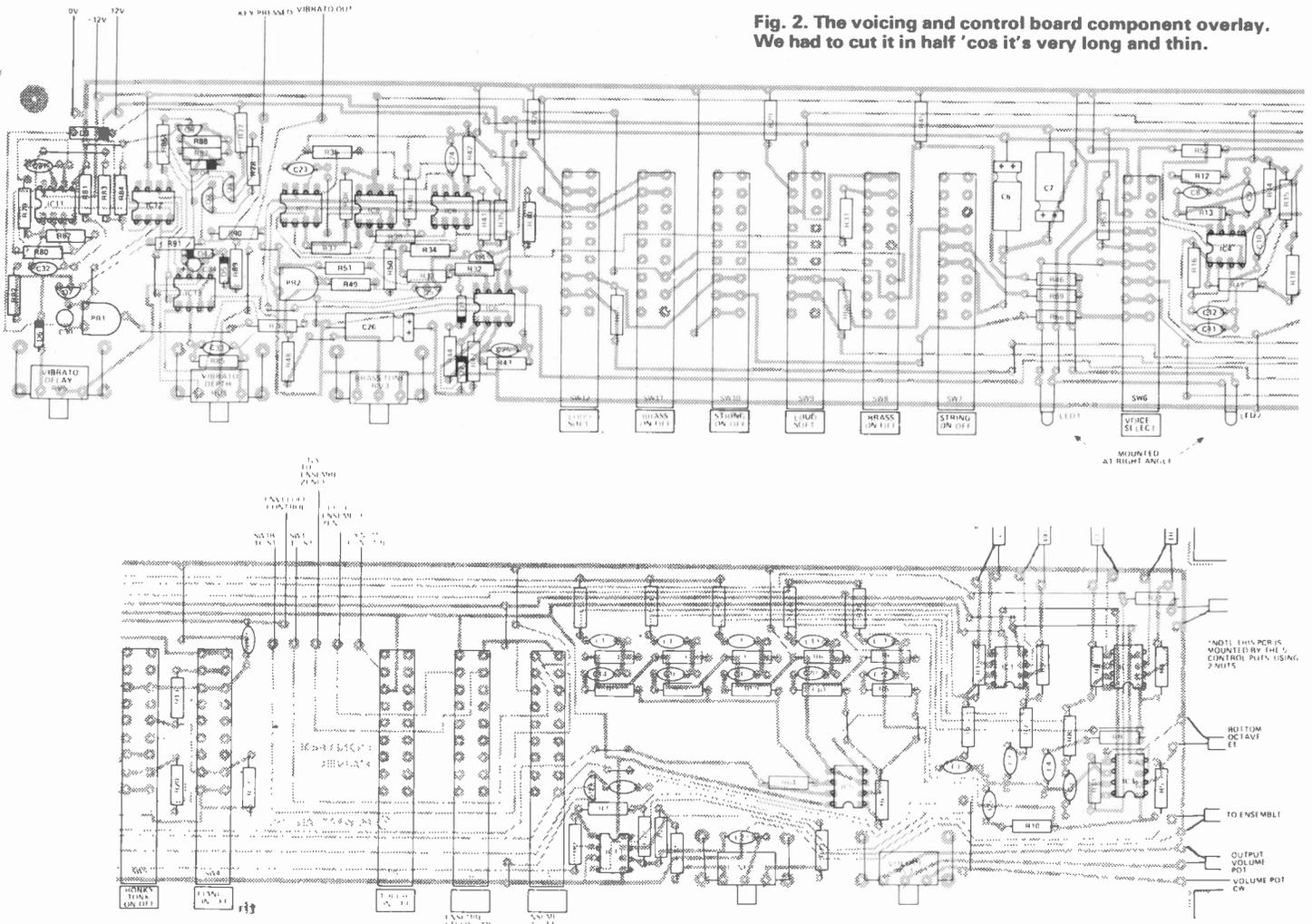


Fig. 2. The voicing and control board component overlay. We had to cut it in half 'cos it's very long and thin.

## PARTS LIST

RESISTORS all 1/4W 5%

R1, 12, 51, 90	10k
R2, 31, 73, 87	15k
R3	22k
R4, 6, 11, 22	33k
R5, 7, 19, 20, 33,	
65, 66, 68, 69, 85	47k
R8, 9, 10, 48, 55	56k
R13, 32	39k
R14, 49, 52, 57, 59,	
61, 63, 72, 75, 76	100k
R15	3k3
R16, 35, 41, 86	18k
R17	1k8
R18	560R
R21, 23, 24, 25, 27,	
28, 45, 71, 74	4k7
R26, 47, 50	1k0
R29, 44	1k5
R30, 70, 89	8k2
R34	390R
R36, 42, 88	150k
R37, 81	270k
R38, 39, 92	27k
R40	270R
R43	180k
R46, 64, 67, 83	68k
R53, 54	2k7
R56, 58, 60, 62	2k2
R77	3k9
R78	820R
R79, 82	1M0
R80	680k
R84	470R
R91	6k8

POTENTIOMETERS

RV1, 4	10k log
RV2	47k lin
RV3	22k log
RV5	1M0 log
PR1	1M0 preset horiz.
PR2	100k preset horiz.

CAPACITORS

C1, 2, 3, 20	10n polyester
C4, 13, 22	22n polyester
C5, 10, 15	47n polyester
C6, 7	100u 25V electrolytic
C8, 9	15n polyester
C11, 12, 18, 23, 24	4n7 polystyrene
C14, 16, 29	2n2 polystyrene
C17, 19, 21, 27, 31	100n polyester
C25	33n polyester
C26	47u 25V electrolytic
C28, 33	220n polyester
C30	22n 35V tantalum
C32	1n polystyrene
C34	2u 2 35V tantalum

SEMICONDUCTORS

IC1-6, 8, 10,	
11, 13	1458
IC7, 9, 12	C43080
Q1	BF244B
Q2	BC182L
Q3-7	BC212L
D1-3, 5, 6, 7	1N4148
D4	5V1 zener
LED1, 2	0.2 inch red

MISCELLANEOUS  
 PCB, PCB-mounting push-switches (12 off),  
 8-pin  
 DIL sockets (13 off)


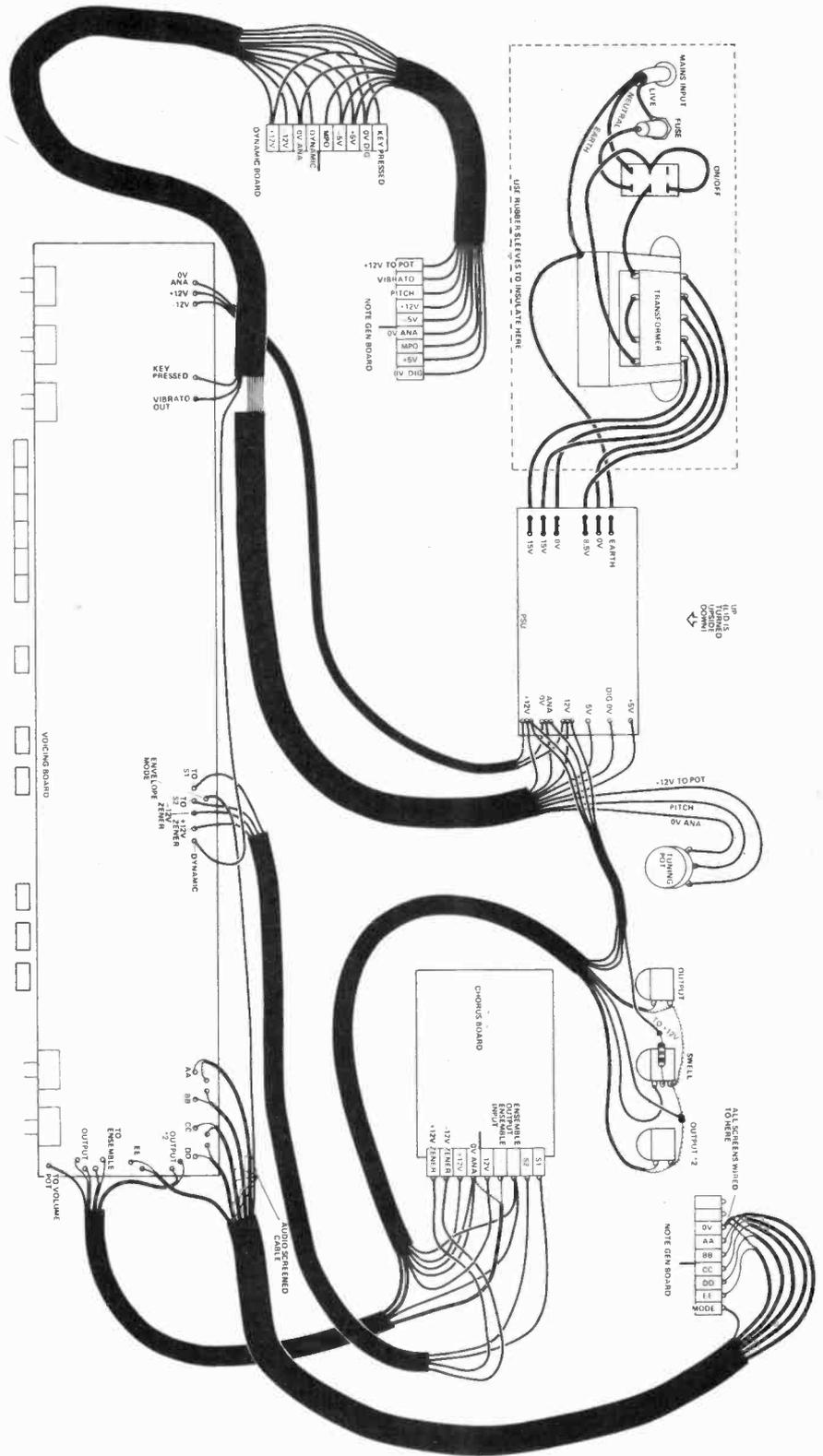


Fig. 3. When you've got your boards finished, this is how they go together.

# LIGHTING & AMPLIFIER MODULES FROM L&B

JUST LOOK AT THESE PRICES!

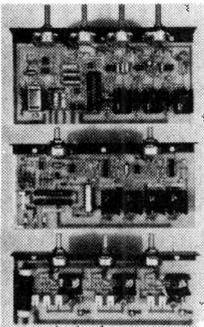

Superior high quality lighting control modules. No additional power supply, just ready to go!

### — LB31000SL —

Sound-light, 3 channel x 1000W. Zero mains voltage switching, high sensitivity, high input impedance, excellent separation. **£18.90**

### — LB41000LS —

Light sequencer, 4 chan. x 1000W. Suedo-random, zero switching. **£14.90**

Two-speed controls, excellent for stage lighting.

### — LB31000LD —

Light dimmer, 3 chan. x 1000W. Stage lighting from full off to full on. **£12.90**

### — LB250 —

250W R.M.S. 4Ω  
10Hz-20KHz  
T.H.D. 0.3% 110dB S/N **£29.50**

### — LB100 —

100w R.M.S. 4Ω  
10Hz-25KHz  
T.H.D. 0.4% 80dB S/N **£15.70**

Massive audio power at your fingertips! For use in many applications.

### — LB25 —

25W. RMS 4Ω  
10Hz—50KHz  
T.H.D. 0.1% 90dB S/N **£8.20**

### PREAMPLIFIERS

**LBPA1.** Stereo disc/ tape. **£14.50.**

**LBPA2.** 4 channel gen. purpose mixer. **£13.50**

**LBPA3.** Stereo disco with mic. **£22.00.**

### POWER SUPPLIES

**LB25PS** ..... **£10.00**  
**LB100PS** ..... **£12.20**  
**LB250PS** ..... **£21.20**

All above prices include VAT. Please add 50p p/packing. Quantity/trade discounts, up to 33% available! SAE for further info.:

**L&B ELECTRONICS** 45 WORTLEY ROAD, W. CROYDON SURREY CR0 3EB. TEL: 01-689 4138

# OUR 1979 CATALOGUE

including the first edition of

## STOP PRESS

(Send SAE for copy)

- ★ Latest low prices
- ★ Fascinating new items
- ★ Special offers — a bargain on their own
- ★ Lowest prices ever for TTL
- ★ Free 45p worth of vouchers



# CHROMASONIC electronics

DEPT. ET1 9, 56 FORTIS GREEN ROAD  
MUSWELL HILL, LONDON N10 3HN  
TELEPHONE: 01-883 3705/2289

USE OUR "ORDER RING" LINES

VAT INCLUSIVE PRICES. P&P 25p

7400 12p	7476 35p	74160 90p	4013 50p	CA3039 70p	LM348N 90p	SAS660 270p	TBA810 100p
7401 12p	7480 50p	74161 100p	4015 80p	CA3046 70p	LM380 80p	SAS670 250p	TBA820 80p
7402 12p	7481 85p	74162 100p	4016 45p	CA3060 225p	LM381N 150p	SL917B 650p	TBA920Q 290p
7403 12p	7482 75p	74163 100p	4017 80p	CA3065 200p	LM382 120p	SN76666N 100p	TCA2270S 250p
7404 12p	7483 80p	74164 115p	4018 80p	CA3076 250p	LM391 170p	SN76003N 170p	TCA270Q 250p
7405 18p	7484 100p	74165 120p	4019 50p	CA3076 250p	LM555 25p	SN76013N 150p	TCA760 300p
7406 30p	7485 75p	74166 140p	4020 100p	CA3080 75p	LM565 125p	SN76013ND 130p	TCA4500A 300p
7407 35p	7486 35p	74167 200p	4022 95p	CA3084 250p	LM709C 40p	SN76023N 150p	TDA1004 300p
7408 18p	7489 200p	74170 200p	4023 25p	CA3085 80p	LM710T05 65p	SN76023ND 130p	TDA1008 320p
7409 18p	7490 35p	74173 120p	4024 55p	CA3086 50p	LM710DIL 65p	SN76033N 180p	TDA1022 600p
7410 12p	7491 80p	74174 90p	4025 20p	CA3088 185p	LM723T05 40p	SN76131N 115p	TDA1024 125p
7411 20p	7492 40p	74175 90p	4026 150p	CA3089 225p	LM723DIL 40p	SN76227N 150p	TDA1034 250p
7412 18p	7493 35p	74176 85p	4027 50p	CA3090AQ 400p	LM733 120p	SN76228N 150p	TDA2002 320p
7413 30p	7494 85p	74177 80p	4028 85p	CA3123E 200p	LM739 150p	SN76666ON 80p	TDA2020 320p
7414 50p	7495 70p	74178 160p	4029 100p	CA3130 100p	LM741 20p	TAA300 250p	TL081 50p
7416 30p	7496 60p	74179 140p	4030 80p	CA3140 70p	LM747 70p	TAA350 250p	TL082 100p
7417 30p	7497 190p	74180 95p	4032 100p	CA3161E 150p	LM748 40p	TAA550 35p	TL083 110p
7420 16p	74100 130p	74181 180p	4033 150p	CA3162E 450p	LM748 40p	TAA570 250p	TL084 130p
7421 30p	74104 65p	74182 90p	4040 100p	CA3189E 250p	LM1303N 95p	TAA661B 150p	UAA170 200p
7422 18p	74105 65p	74184 140p	4043 95p	FX209 780p	LM1458 60p	TAA700 340p	XR320 250p
7423 30p	74107 35p	74185 140p	4046 120p	LD130 460p	LM3900 60p	TAA790 340p	XR2003 150p
7425 30p	74109 55p	74188 320p	4047 100p	LF356 90p	LM3909N 70p	TAD100 150p	XR2206 400p
7426 40p	74120 115p	74190 100p	4048 80p	LF357 90p	MC1310P 150p	TAD110 130p	XR2207 400p
7427 30p	74121 25p	74191 100p	4049 45p	LM211H 240p	MC1312P 160p	TAA120A 60p	XR2208 590p
7428 35p	74122 50p	74192 100p	4050 50p	LM300T05 170p	MC1315P 230p	TBA120S 70p	XR2216 675p
7430 18p	74123 50p	74193 100p	4054 130p	LM301AN 30p	MK50398 650p	TBA120T 90p	XR2264 440p
7432 25p	74125 45p	74194 100p	4055 130p	LM301T05 45p	MM5314 380p	TBA480Q 190p	XR2265 440p
7433 40p	74126 60p	74195 100p	4056 135p	LM304 190p	MM5316 470p	TBA520Q 190p	XR2567 250p
7437 30p	74128 75p	74196 100p	4060 115p	LM307N 60p	NE529K 150p	TBA530Q 190p	XR4136 150p
7438 35p	74130 130p	74197 80p	4066 60p	LM308T05 100p	NE555 25p	TBA540 220p	XR4151 350p
7440 15p	74131 100p	74198 150p	4068 22p	LM308DIL 100p	NE566 70p	TBA550Q 250p	XR4202 150p
7441 70p	74132 75p	74199 150p	4069 20p	LM309K 140p	NE562B 420p	TBA560C 240p	XR4212 150p
7442 70p	74135 100p	74293 125p	4070 30p	LM310T05 150p	NE566 160p	TBA641A12 250p	XR4739 150p
7443 115p	74136 80p	74LS00 15p	4071 20p	LM311T05 150p	NE567 170p	TBA700 200p	ZN414 95p
7444 115p	74137 100p	74LS11 285p	4072 20p	LM317K 350p	SAD1024 1400p	TBA720Q 240p	ZN1034E 200p
7445 100p	74141 70p		4075 25p	LM324 70p	SAS560 155p	TBA750Q 200p	95H90 800p
7446 95p	74142 200p		4077 40p	LM339 70p	SAS570 150p	TBA800 90p	11C90 1400p
7447 60p	74143 300p		4081 20p				
7448 60p	74144 300p		4082 20p				
7450 18p	74145 75p		4093 80p				
7451 18p	74147 180p		4501 20p				
7453 18p	74148 130p	<b>CMOS</b>	4507 55p				
7454 18p	74150 100p	4000 14p	4510 100p				
7460 18p	74151 70p	4001 14p	4511 150p				
7470 30p	74153 70p	4002 15p	4516 120p				
7472 30p	74154 100p	4006 90p	4518 100p				
7473 35p	74155 65p	4007 18p	4520 100p				
7474 30p	74156 85p	4009 40p	4528 100p				
7475 35p	74157 70p	4011 18p	4583 80p				
		4012 18p					

IN 4148, DIODES BY ITT/Texas, 100 for **£1.50**  
Static RAM 2102 1024 x 1 bit 450 nano sec **£1.00** each  
2112 256 x 4 bit 450 nano sec **£2.50**  
Murata Ultrasonic Transducers 40kHz **£1.80** each **£3.20** pair

Orders:  
Post and Packing 25p  
Add 15% V.A.T. to total order  
Minimum order: £1.00

## T. POWELL

306 ST. PAULS ROAD, Highbury Corner, London, N.1. TEL: 01-226 1489  
Barclay / Access credit cards accepted

# ETI MARKET PLACE



## 1 CLOCK RADIO

How about a round clock radio which can double as a very smart desk clock — as we can testify!

To time, rotate one end of the cylinder to display the frequency selected. Most of the functions are controlled by a push-button panel and the display is a large, clear LCD affair.

Made by Hanimex, the battery clock radio comes in white, white or white. It will lull you to sleep and then turn itself off an hour later and waken you to the sound of Radio 1, or music if you prefer.

£17.95

To CLOCK RADIO offer  
ETI Magazine, 145 Charing Cross Road  
London, WC2

Name .....

Address .....

## 2 DIGITAL ALARM

This mains-only Hanimex alarm has a large 12-hour display incorporating AM/PM and alarm set indicators. You can have a dim or bright display at the touch of a switch. Fast and slow setting buttons make time setting simplicity itself. You can forget about knocking these accidentally in the morning scramble to turn off the alarm, as a locking switch is fitted under the clock. A 9-minute snooze switch completes the list of all mod. clock cons.

£10.60

To: DIGITAL ALARM offer  
ETI Magazine, 145 Charing Cross Road  
London, WC2

Name .....

Address .....

## 3 LCD CHRONO

Our Chrono comes complete with a high grade adjustable metal strap and is fully guaranteed.

The LCD display shows seconds as well as hours and minutes. Press a button and you get the date and day of the week.

Press another button and you have an accurate stopwatch with hundredths of seconds displayed, giving the time up to an hour. There's a lap time facility, too — and of course a back light.

£11.95

To: LCD WATCH offer  
ETI Magazine, 145 Charing Cross Road  
London, WC2

Name .....

Address .....

## 4 LCD ALARM CHRONO

This is no ordinary watch. It's a slim, multi-function, dual time LCD alarm chronograph.

This model will show hours, minutes, seconds, date, day of the week, stopwatch, split time, alarm and alternate dual time zone — not all at once of course. There's a night light, too.

Hours, minutes, seconds and day of the week are displayed continuously, while the date will appear at the touch of a button. The alarm is beefy enough to wake you up in the morning and get you to work on time (or wake you up when it's time to go home).

£19.95

To: ALARM/CHRONO LCD WATCH offer  
ETI Magazine, 145 Charing Cross Road  
London, WC2

Name .....

Address .....

All prices include 15% VAT and postage

Examples of Marketplace offers can be seen at our Charing Cross Road offices.  
Please mark your envelope with the offer that you want.

q001  
q2a

# RAVEN ON...


**This month's little ramble takes us through foam backed carpets into flat tellys by Sinclair and the best LCD displays in the world — British!**

PREDICTIONS OF the effect microprocessors will have in the home are still being made. However, it looks as though 1979 will see the first really domestic products starting to appear. Home Computing is now well established among electronics hobbyists, but the effect of MPU's is not so obvious to people outside the electronics arena. As with the other new technologies the novelty attractions are the first areas to be exploited. Calculators and LED watches were the first to appear using an LSI it has taken a further three to four years of serious product design to incorporate devices into industry.
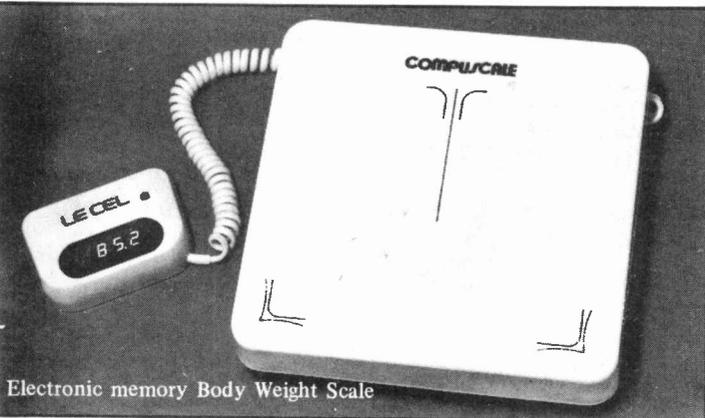
## Open Door

On the market in time for Christmas we shall see a whole new range of products that are only possible because of microprocessors. The now familiar twenty four tune door bells are being manufactured in Hong Kong along with new programmable TV Games that function like flight or vehicle simulators, coming complete with steering wheel. Hand held electronic pocket games, remote control cars and robots also the very sophisticated watches like the Seiko Memory Bank.

One further consumer product now available because of MPU's is the electronic bathroom scale.



This is of particular interest to me since I demonstrated a prototype to my Bank Manager back in 1975, when I had illusions of building a manufacturing complex the size of Plessey. The instrument was an adaption of a small capacitance meter my company was manufacturing and used a novel form of transducer.

It comprises of layers of foam backed carpet separated by layers of tin foil. The capacitance changed quite linearly when the mat was stood upon however I have no doubt that it may not have stood the test of time. The Bank Manager was very impressed but there was a noticeable lack of enthusiasm when it was suggested that he invest the bank's money in the project. With hind-sight he was a

very sensible chap since it is unlikely he would have won the support of his own boss in backing the project with the kind of money necessary to launch such an enterprise.

This major difficulty that companies experience in the UK is the main reason that new high volume consumer products are eventually manufactured in the Far East where large sums of development capital exists and also the huge export markets which soak up the bulk volume of these products.

Thousands of words have now appeared in print about minicomputers and the uses of MPU'S.

In fact you could quite easily form the impression that the only new developments taking place in electronics was associated with logic applications. This of course is nonsense and is a misconception that has arisen due to the fashionable use of words in science. One immediate consequence of these trends is that unless a scientist or development engineer can somehow design a microprocessor into his proposals then he has less chance of winning the support of financial backers.

## Material Gain

Electronics enthusiasts generally know about silicon (or the "silicon chip" as they say on telly) but you never hear Robin Day or Angela Ripoff talk about, Zinc Selenide or Germanium chips, Gallium Arsenide chips or silicon on sapphire chips.

Gallium Arsenide is an important semiconductor material. It is not particularly new since its been in use for making devices since the early sixties, Gunn Diodes, Light Emitting Diodes, Varactor Diodes and Field Effect Transistors.

FET's are probably the most exciting development coming from Gallium Arsenide since these transistors can operate at very high frequencies and are increasingly being used in satellite and space communications. Gallium Arsenide FET's (GaAs FET's) have been around for several years the first devices were made by Plessey ten years ago and it has taken all this time to establish the technology to a sufficient level for volume production. Many other companies around the world are also making GaAs fets now and you would currently have to pay in the region of £100 for a FET that will operate at about 18 GHz., (Imagine how it feels to blow one up). The likely effects of GaAs FET's in the next few years are to be seen in the communications field. Computer controlled cars with microwave eyes which can see in all weathers, C.B. Radio using satellites for communications, Digital watches or calculators with CB Radio why not?

## Switch Called For?

One area of computerisation I am aptricularly looking forward to is a computer controlled electronic switchboards. Telephone calls to companies out of office hours

quite frequently result in the callers being talked to by a phone answering machine. The recording is usually a flat monotone voice which immediately makes the caller feel uncomfortable and results in the phone being hung up. One answering machine story I know was a farmer who because he couldn't get a sensible reply from the recorder shouted a stream of abuse down the telephone and cancelled his contract for fuel oil, with the unsuspecting supplier. To tackle just such problems as abusive farmers there is now a computer controlled switchboard that can answer up to eight telephones lines at once. The computer has a voice recognition system and also a small vocabulary for replies.

A comparison method technique based on statistical analysis of spoken words is used. The machines vocabulary is assembled by taking 500 samples of one word spoken in different dialects from male and female speakers. Each word is sampled 12 times and each sample's overall amplitude is measured and its frequency spectrum plotted at 31 points between 300 and 3k3 hertz. This produces 384 numbers, or elements that describe the word.

The elements resulting from all 500 speakers saying the same word are combined to produce a set of 384 mean values and standard deviations, which are stored in the system as the reference for that word, the incoming unknown word is similarly sampled, analysed and compared element by element with reference words using an algorithm that finds the probability density function for the unknown word. When this probability density is above a certain threshold — which can vary from word to word or system to system — the system declares the word recognised

### Sinclair Flat Telly

More information is now available on the flat screened television mentioned in the September edition of ETI. The technology used is that of the conventional CRT and not liquid crystal that the Japanese are going for. The method described is a conventional cathode ray tube which is flat since the beam is projected at right angles to the screen instead of from the back as in a conventional TV.

### Glassy Eyed

Two sheets of glass form the front screen and a vacuum formed backing plate. The interior of the backing plate is coated with phosphor and is viewed through the front face from the same side as the electrons strike. The result is that the brightness is more than double that of a conventional CRT. Electrostatic deflection plates in the gun assembly provide horizontal and vertical scanning, and a third set between the phosphor screen and front-face bends the electron beam toward the screen. Without this additional focussing field, the angle of beam incidence would vary across the screen, spreading the beam spot into an ellipse. The focussing electrode is formed on the front face by a transparent tin-oxide coating.

The electron gun is set to one side of the screen with its axis parallel to the screen.

Folding the electron optics would normally distort the raster scan to produce a wedge shape with curved vertical edges, however, by using optical techniques corrections for distortion can be made.

### Screen Test

The screen height is reduced by half but the width is kept constant. This narrows the angle subtended by the electron beam onto the screen reducing distortion and deflection power. The picture height is restored by use of a Fresnel lens which is formed in a flat plastic face plate.

The assembly techniques used in producing the new CRT lend themselves to mass production and it is aimed by Sinclair's to set up a new factory for this purpose.

Coincidentally, news of a new imaging system with potential for use as a flat screen TV has been patented in Britain.

### New Visions

This system uses techniques not unlike those described in this column in September ETI and consists of liquid crystal technology. Two flat screens contain arrays of very thin parallel stripes placed at right angles to each other.

With an electroluminescent or other type of translucent panel behind the liquid crystal screens, light would only be visible at the intersections of the stripes, if these were switched accordingly.

By switching at a very high speed a scanning effect could be achieved as in a conventional TV.

Light could be modulated by altering the intensity of the light panel or by polarising the screens. Filters could also be incorporated for colour operation.

ETI

# SINTEL

## KITS OR ASSEMBLED LATCHED COUNTER MODULES

Our range of Industrial Latched Counter Module Kits is now available ready-built. These counters use both CMOS and TTL ICs and will save you considerable design, purchasing, building and de-bugging time. Each module uses a set of red LED displays, and features a single in-line plug and socket. Instructions are provided. For full details please send for Catalogue.

	TTL				CMOS			
	Part No.	Built	Part No.	Kit	Part No.	Built	Part No.	Kit
2 digit	401-484	£13.22	526-412	£10.32	595-568	£13.02	548-470	£10.42
4 digit	715-484	£23.38	657-412	£17.98	512-568	£22.63	669-470	£18.11
6 digit	293-484	£33.76	721-412	£25.06	393-568	£32.31	191-470	£25.85

### NEW PRICES AND SOME NEW CMOS ADDITIONS

*If you need your CMOS by return — buy it from SINTEL*

CD4000	0.15	CD4027	0.44	CD4051	0.82	CD4086	0.64	CD40182	1.40
CD4001	0.17	CD4028	0.77	CD4052	0.82	CD4089	1.39	CD40192	1.40
CD4002	0.17	CD4029	1.03	CD4053	0.82	CD4093	0.80	CD40193	1.40
CD4006	1.04	CD4030	0.50	CD4054	1.04	CD4094	1.69	CD40194	1.19
CD4007	0.18	CD4031	2.00	CD4055	1.18	CD4095	0.94	CD40257	1.48
CD4008	0.87	CD4032	0.89	CD4056	1.18	CD4096	0.94	CD4502	0.81
CD4009	0.50	CD4033	1.25	CD4059	4.29	CD4097	3.35	CD4510	1.01
CD4010	0.50	CD4034	1.71	CD4060	1.00	CD4098	0.98	CD4511	1.25
CD4011	0.18	CD4035	1.08	CD4063	0.98	CD4099	1.85	CD4514	2.47
CD4012	0.20	CD4036	2.88	CD4066	0.55	CD40100	2.50	CD4515	2.82
CD4013	0.43	CD4037	0.85	CD4067	3.35	CD40101	1.61	CD4516	1.01
CD4014	0.83	CD4038	0.98	CD4068	0.20	CD40102	2.13	CD4518	0.97
CD4015	0.83	CD4039	2.78	CD4069	0.20	CD40103	2.13	CD4520	1.04
CD4016	0.48	CD4040	0.97	CD4070	0.46	CD40104	1.10	CD4527	1.43
CD4017	0.79	CD4041	0.75	CD4071	0.20	CD40105	1.06	CD4532	1.21
CD4018	0.83	CD4042	0.89	CD4072	0.20	CD40106	0.62	CD4555	0.78
CD4019	0.50	CD4043	0.88	CD4073	0.20	CD40107	0.59	CD4556	0.78
CD4020	1.11	CD4044	0.84	CD4075	0.20	CD40108	5.36	MC14528	0.93
CD4021	0.90	CD4045	1.26	CD4076	1.17	CD40109	1.03	MC14553	4.43
CD4022	0.82	CD4046	1.20	CD4077	0.39	CD40160	1.19	IM6508	8.05
CD4023	0.18	CD4047	0.89	CD4078	0.20	CD40161	1.19		
CD4024	0.70	CD4048	0.50	CD4081	0.20	CD40162	1.19		
CD4025	0.20	CD4049	0.50	CD4082	0.20	CD40163	1.19		
CD4026	1.55	CD4050	0.43	CD4085	0.84	CD40181	3.40		

Our offices are at Chapel Street, Oxford, but please do not use this as a postal address. For full range of components send for Free Catalogue

OFFICIAL ORDERS ARE WELCOME from Companies, Govt Deps Natn Inds., Univs., Polys  
 ORDERS: C.W.O. add VAT @ 35p p&p TELEPHONE and CREDIT (Invoice) ORDERS add VAT @ 15% + 60p p&p  
 minimum charge (the balance will be charged at cost) Please see FAST SERVICE EXPORT ORDERS welcome, no VAT  
 but add 10% (Europe), 15% (Overseas) for Air Mail p&p For Export rates on heavy items — contact us first

ORDERS TO: SINTEL, PO BOX 75A, OXFORD  
 Tel: 0865 49791

FAST SERVICE: We guarantee that Telephone Orders for goods in stock, received by 4.15 p.m. (Mon-Fri.) will be despatched on the same day by 1st Class Post (some heavy items by parcel post) and our stocking is good. Private customers should telephone and pay by giving their Access or Barclaycard number, with a minimum order value of £5. Official orders, no minimum.



Largest range of quality components in the U.K. — over 8,000 types stocked

# Marshall's

Head Office and Mail Order to Dept. ET1  
A. Marshall (London) Ltd.  
Kingsgate House, Kingsgate Place  
London NW6 4TK. Tel: 01-624 8805  
Telex 21492

Retail Sales: London: 40 Cricklewood Broadway, NW2 3ET. Tel: 01-452 0161/2. Also 325 Edgware Road, W2. Tel: 01-723 4242.  
Glasgow: 85 West Regent Street, G2 2QD. Tel: 041-332 4133. And Bristol: 108A Stokes Croft, Bristol. Tel: 0272 426801/2

### ZENER DIODES (full range in cat.)

400mW	87863	1 WATT	2.5 WATT	BZX70	C10	92
C2.4	.11	1N4728A 3.3	23	CV75	.67	C120
C2.7	.11	1N4729A 3.6	23	CV82	.67	C140
C3.0	.11	1N4730A 3.9	23	CV91	.67	C150
C3.3	.11	1N4731A 4.3	23	C10	.67	C160
C3.6	.11	1N4732A 4.7	23	C11	.67	C170
C3.9	.11	1N4733A 5.1	23	C12	.67	C180
C4.3	.11	1N4734A 5.6	23	C13	.67	C190
C4.7	.11	1N4735A 6.2	23	C15	.67	C200
C5.1	.11	1N4736A 6.8	23	C16	.67	
C5.6	.11	1N4754A 3.9	25	5 WATT	BZV40	20 WATT
CV92	.11	1N4754A 4.3	25	C10	.83	C10
CV93	.11	1N4754A 4.7	25	C11	.83	C11
CV94	.11	1N4754A 5.1	25	C12	.83	C12
CV95	.11	1N4754A 5.6	25	C13	.83	C13
CV96	.11	1N4754A 6.2	25	C14	.83	C14
CV97	.11	1N4754A 6.8	25	C15	.83	C15
C10	.11	1N4760A 5.6	25	C15	.83	C16
C11	.11	1N4761A 7.5	25	C16	.83	C18
C12	.11	1N4762A 8.2	25	C17	.83	C20
C13	.11	1N4763A 9.1	25	C18	.83	C22

CD4000	£0.20	CD4028	£0.20	CD4049	£0.55	CD4076	£0.99	CD4516	£2.54
CD4001B	£0.20	CD4028B	£0.76	CD4050B	£0.55	CD4077	£0.70	CD4516B	£1.20
CD4002	£0.18	CD4028B	£0.20	CD4051B	£0.85	CD4078	£0.27	CD4518B	£1.20
CD4006	£1.25	CD4027B	£0.55	CD4052B	£0.85	CD4078B	£0.27	CD4519	£0.64
CD4007	£0.18	CD4028B	£0.60	CD4053B	£0.85	CD4082	£0.27	CD4520	£1.20
CD4008B	£0.58	CD4029B	£1.10	CD4054	£1.45	CD4085	£0.89	CD4522	£1.19
CD4009	£0.99	CD4030	£0.64	CD4055	£1.65	CD4086	£0.89	CD4526	£1.19
CD4010	£0.58	CD4031B	£2.25	CD4056	£1.65	CD4089B	£0.55	CD4527	£1.20
CD4011B	£0.20	CD4034B	£2.46	CD4059	£6.00	CD4093B	£0.65	CD4528	£1.26
CD4012	£0.20	CD4035B	£1.30	CD4060B	£1.15	CD4094	£2.30	CD4529	£1.41
CD4013B	£0.52	CD4037	£1.20	CD4063	£1.35	CD4095	£1.30	CD4543	£1.96
CD4014	£1.10	CD4040	£1.12	CD4066B	£0.75	CD4096	£1.30	CD4723	£1.60
CD4015	£0.75	CD4041B	£0.86	CD4067	£4.65	CD4097	£4.65	CD4724	£1.60
CD4016	£0.62	CD4042B	£0.86	CD4068B	£0.27	CD4099B	£1.60	CD4CoN	£0.24
CD4017B	£1.05	CD4043	£1.05	CD4069B	£0.20	CD4503	£0.58	CD402N	£0.24
CD4018	£1.05	CD4044	£1.00	CD4070B	£0.35	CD4507	£0.59	CD403A	£0.24
CD4019B	£0.52	CD4045	£1.75	CD4071B	£0.20	CD4510B	£1.20	CD409A	£0.24
CD4020B	£1.15	CD4046B	£1.50	CD4072	£0.27	CD4511	£1.75	CD401N	£0.24
CD4021	£1.05	CD4047B	£0.65	CD4073B	£0.20	CD4512	£0.99	CD41AN	£0.95
CD4022B	£1.00	CD4048	£0.58	CD4075B	£0.20	CD4514	£2.54	CD420N	£0.24

### PRESET POTENTIOMETERS-TRIMMERS

**PT10 SERIES (FULLY ENCLOSED)** 13p  
PT10h (2.5V) vertical mounting 0.15 watt at 40°C  
PT10V horizontal mounting 0.15 watt at 40°C  
Tel: 20% Please specify horizontal or vertical.

**PT15 SERIES (FULLY ENCLOSED)** 15p  
PT15 Nv vertical mounting 0.3 watt at 40°C  
PT15 Nv horizontal mounting 0.3 watt at 40°C  
Tel: 20% Please specify horizontal or vertical.

VALUES AVAILABLE: PT10 and PT15 100R 250R 500R 1k 2.5k 5k 10k 25k 50k 100k 200k 500k 1M 2.5M 5M 10M

### NEW LOW PRICE "KIM" The Ready to use Microprocessor System

Not a kit but supplied fully tested, wired and guaranteed. Expandable Memory that grows with your system. Not just an evaluation kit. Starting with KIM 1 at £107.95 VAT inclusive. You get immediate capability which can be expanded to a complete system capable of addressing up to 65K BYTES of Memory. KIM IS EXPANDABLE. Expand as you learn up to 65K.

KIM 1 Basic board with above features assembled £107.95  
KIM 3 Basic plastic RAM card plus in motherboard £140.35  
KIM 4 Motherboard (takes 8 x KIM 3) + power supply £75.55

### BOXES AND CASES ALUMINIUM BOXES

13 sizes in stock e.g. 4x4x1 1/2" 85p, 3x2x1 1/2" 60p, 6x4x2" £1.25. 12x8x3" £2.70.  
REXINE COVERED  
7 sizes available, e.g. 9x5x2 1/2" £2.40, 6x4 1/2 x 1 1/4" £1.75, 15x8x4" £5.00, 11x6x3" £2.90.



ABS PLASTIC 3x2x1 1/2" 55p, 3x2x2 1/2" 85p, 4 1/2 x 3 1/2 x 1 1/2" 85p, 8 1/2 x 4 1/2 x 3" £2.10.

PLUS WIDE SELECTION OF VERO & GAZELLI CASES

### 1979 CATALOGUE

40 page catalogue — new enlarged micro section — largest range of quality components from leading suppliers available in U.K. All VAT inclusive prices. Over 8,000 line items plus lots more. 45p post paid or 35p to callers at any of our four branches.

MAIL ORDER\*

Quick service on all orders — please add 40p for p&p to all orders. Telephone orders on credit cards £10.00 minimum.

### Get a great deal from Marshall's

#### 3 1/2 DIGIT LCD AND LED PANEL METER KITS

Low-cost, easy-to-assemble kits using the new Intersil 71067 A/D converters

Intersil's 7106 is the first single-chip CMOS A/D for driving LCD displays — including backplane — directly. The 7107 is the first single-chip CMOS A/D for driving Instrument-size LED displays directly without buffering. Each provides parallel seven segment outputs, ideal for DVMs, OPMs and anywhere modern digital displays are needed. Both have internal reference and clock, and both are CMOS so you get low noise (12 to 15µV) comparable with the finest bipolar devices, and low power (10mW max. @ 10V).

Kits provide all materials... including PCB board, for a functioning panel meter. Assembly time is only 1/2 hour.

ICL 7106/67 (LED) £26.99 SPECIAL OFFER £19.90  
ICL 7107/67 (LED) £21.99 SPECIAL OFFER £15.90  
CHIP ALONE ICL 7106/67 SPECIAL OFFER £8.90

### L200 — 5 TERMINAL ADJUSTABLE VOLTAGE AND CURRENT REGULATOR

The L 200 is a silicon monolithic integrated circuit for voltage and current programmable regulation

- ADJUSTABLE OUTPUT CURRENT UP TO 2A
- ADJUSTABLE OUTPUT VOLTAGE DOWN TO 2.85V

REDUCED PRICE NOW ONLY £1.95 each

### TTL (See Catalogue for full range)

74LS242N	£1.25	SN74200N	£0.77	SN74200N	£0.22	74LS00N	£0.26
74LS242N	£1.25	SN74200N	£0.77	SN74200N	£0.22	74LS01N	£0.26
74LS244N	£1.50	SN74200N	£0.77	SN74200N	£0.22	74LS02N	£0.26
74LS245N	£1.65	SN74200N	£0.77	SN74200N	£0.22	74LS03N	£0.26
74LS247N	£1.09	SN74112N	£1.70	SN7427N	£0.22	74LS04N	£0.29
74LS248N	£1.09	SN74112N	£1.70	SN7427N	£0.22	74LS05N	£0.29
74LS249N	£1.09	SN74112N	£1.70	SN7427N	£0.22	74LS06N	£0.26
74LS251N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS09N	£0.26
74LS252N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS10N	£0.26
74LS253N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS11N	£0.26
74LS254N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS12N	£0.26
74LS255N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS13N	£0.26
74LS256N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS14N	£0.26
74LS257N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS15N	£0.26
74LS258N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS16N	£0.26
74LS259N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS17N	£0.26
74LS260N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS18N	£0.26
74LS261N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS19N	£0.26
74LS262N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS20N	£0.26
74LS263N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS21N	£0.26
74LS264N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS22N	£0.26
74LS265N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS23N	£0.26
74LS266N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS24N	£0.26
74LS267N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS25N	£0.26
74LS268N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS26N	£0.26
74LS269N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS27N	£0.26
74LS270N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS28N	£0.26
74LS271N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS29N	£0.26
74LS272N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS30N	£0.26
74LS273N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS31N	£0.26
74LS274N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS32N	£0.26
74LS275N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS33N	£0.26
74LS276N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS34N	£0.26
74LS277N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS35N	£0.26
74LS278N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS36N	£0.26
74LS279N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS37N	£0.26
74LS280N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS38N	£0.26
74LS281N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS39N	£0.26
74LS282N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS40N	£0.26
74LS283N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS41N	£0.26
74LS284N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS42N	£0.26
74LS285N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS43N	£0.26
74LS286N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS44N	£0.26
74LS287N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS45N	£0.26
74LS288N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS46N	£0.26
74LS289N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS47N	£0.26
74LS290N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS48N	£0.26
74LS291N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS49N	£0.26
74LS292N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS50N	£0.26
74LS293N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS51N	£0.26
74LS294N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS52N	£0.26
74LS295N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS53N	£0.26
74LS296N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS54N	£0.26
74LS297N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS55N	£0.26
74LS298N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS56N	£0.26
74LS299N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS57N	£0.26
74LS300N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS58N	£0.26
74LS301N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS59N	£0.26
74LS302N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS60N	£0.26
74LS303N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS61N	£0.26
74LS304N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS62N	£0.26
74LS305N	£1.00	SN74188N	£2.70	SN7438N	£0.24	74LS63N	£0.26
74LS306N	£1.00	SN7					

# ETIPRINTS

ETIPRINTS are a fast new aid for producing high quality printed circuit boards. Each ETIPRINTS sheet contains a set of etch resistant rub down transfers of the printed circuit board designs for several of our projects.

ETIPRINTS are made from our original artwork ensuring a neat and accurate board. We thought ETIPRINTS were such a good idea that we have patented the system (patent numbers 1445171 and 1445172).

## PARTS LIST

Shown below is the listing for the last year's ETIPRINTS.

Earlier sheets are available, ring Tim Salmon for details.

<b>013</b>	Amplifier Module Amplifier PSU Equaliser Equaliser PSU	Book Six	<b>020</b>	Digital Tacho Module Digital Dial	Jan 79 Jan 79 Jan 79	<b>027</b>	CCD Phaser Rev. Monitor	Project Book Seven
<b>014</b>	Skeet Game Sweep Oscillator Burglar Alarm GSR Monitor	Project Book Six	<b>021</b>	Tape Slide Synch Tape Noise Limiter Light Tacho	Feb 79	<b>028</b>	Race Track, Spirit Level Egg Timer, Bongos Bench Supply, Oscillator	Project Book Seven
<b>015</b>	UFO Detector Torch Finder (twice) Etiwet (twice)	July 78 July 78 Aug 78	<b>022</b>	Logic Trigger Power Meter Headlight Delay (x2)	Mar 79	<b>029</b>	Bass Enhancer Digital Freq. Meter (4 boards)	Project Book Seven
<b>016</b>	Stac Timer Xhatch Gen Wheel of Fortune	Sept 78	<b>023</b>	Click Eliminator Guitar Effects Unit (2 boards)		<b>030</b>	ETIWET, Continuity Tester Metal Locator, Light Dimmer Ultrasonic Switch (2 boards)	Project Book Seven
<b>017</b>	Complex Sound Gen Tele Bell Extender Power Bulge	Oct 78	<b>023A</b>	Wind Speed Indicator	April 79	<b>031</b>	Tone Control House Alarm (2 boards) Torch Finder	Project Book Seven
<b>018</b>	RF Power Meter Proximity Switch Audio Oscillator (2)	Oct 78 Oct 78 Nov 78	<b>024A</b>	Ambush (Boards 2 & 3) Car Immobiliser	April 79 May 79	<b>032</b>	LED Audio Display (2 boards) (underside pattern)	Aug 79
<b>019</b>	Car Alarm (2) Wine Temp (2) Curve Tracer	Dec 78 Dec 78 Dec 78	<b>024B</b>	Ambush (Board 1) Headphone Amplifier Double Die	May 79	<b>033</b>	LED Audio Display (2 boards) (topside pattern) Bench Amp NICD Charger	Aug 79
			<b>025</b>	Metronome Mains Seeker Triton 8K Eprom Card	June 79			
			<b>026</b>	Motor Speed Controller (2 Boards For Controller) Battery Indicator	July 79			

## HOW IT WORKS



*Lay down the ETIPRINT and rub over with a soft pencil until the pattern is transferred to the board. Peel off the backing sheet carefully making sure that the resist has transferred. If you've been a bit careless there's even a 'repair kit' on the sheet to correct any breaks!*

## BUY LINES

### ORDER TODAY

Send a cheque or P. O. (payable to ETI Magazine) to:

ETI PRINT, ETI MAGAZINE  
145 Charing Cross Road, London WC2H 0EE


# 80p

INC P & P
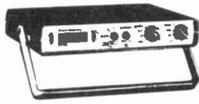
# AUDIO AND TEST EQUIPMENT CENTRE

RETAIL MAIL ORDER EXPORT  
ALL PRICES INCLUDE VAT

Telephone your order with Access and Barclaycards or send cheque with order.



LONDON'S TEST GEAR CENTRE  
OPEN 6 DAYS A WEEK 9 am-6 pm

## SCOPES — (UK P/P £1.50 ea.)

3" 5MHz single beam	102.00
4" 5MHz single beam	125.00
Super 6 6MHz single beam	£166.00
Super 10 10MHz dual trace	239.00
14D15 Scopes 15MHz dual trace	£325.00
4D25 Scope x 25MHz dual trace	£414.00
PROBES x 1 x 10 14.50, x 10 9.95 x 1 7.95 For Super-6/10/4D25	
SINCLAIR 1MHz Miniscope	Price to be announced

## DIGITAL MULTIMETERS

VDM235 Sinclair portable 3 1/2 digit LED	52.95
PDM35 Sinclair Pocket 3 1/2 digit LED	31.90
DM350 New Sinclair 3 1/2 Digit } with 10 amp range	74.45
DM450 New Sinclair 4 1/2 Digit }	106.45
(30kV Probes 19.00, Mains adaptors 4.00, DM carrycase 8.95)	
M1200 Bench Portable 3 1/2 digit LED Resolution 1µA/0.1mv/0.01ohm	67.50
D35 Data Precision 3 1/2 digit hand-held LCD 2 amp ac/dc	£113.85
188. Low cost 3 1/2 digit general purpose LCD	£52.95

## FREQUENCY COUNTERS

MAX 50 50MHz 6 digit pocket counter	61.00
MAX 100 100MHz 8 digit portable counter	88.75
MAX 550 550MHz 6 digit pocket counter	106.00
500 MHz Prescaler for max 50 or max 100	40.00
PFM200 Sinclair 200 mHz Pocket Counter 8 digit	53.00
OPTO7000 8 digit, 600 mHz Portable 1Hz RES with N/CADS	139.95

## MULTI-METERS — GENERAL PURPOSE & ELECTRONIC

Multi-Range Instruments featuring AC/DC volts, DC current, Resistance Ranges all with mirror scales except T1, T12, T12/TMK3A, TM3 AC volts only, some with AC current, etc

TM11 incredible 120 Range Electronic Multi-meter	158.00
TM38 AC Micro voltmaster 3MHz > 4 Megohm	151.75
360TR 100k/volt 23 Range (plus transistor checker) Large scale	38.95
PROE 20k/volt 26 Range Large Scale	29.95
7081 50k/volt 36 Range Multi-meter	22.95
TMK500 30k/volt 22 Range Multi-meter (plus Continuity Buzzer)	22.95
680R 20k/volt 52 Range Pocket Multi-meter	36.75
7200 20k/volt 22 Range Double Multi-meter	17.95
Micro80 20k/volt 26 Range Pocket Multi-meter	19.10
RE132m/171-2 20k/volt 16 Range Popular Multi-meter	11.95
LT22 20k/volt 19 Range Pocket Multi-meter	£14.50
LT101 1k/volt 12 Range Pocket Multi-meter	6.95
RE142m 20k/volt 17 Range Multi-meter	13.50
RE152m 20k/volt 19 Range Multi-meter plus transistor check	18.95
AT205 50k/volt 21 Range Multi-meter	26.95
K200 FET VOM 38 Ranges	77.00
TR202 20k/volt 23 Ranges/Transistor Checker/Checker/Continuity Checker	19.95

AVO 8s and a large range of replacement tests leads in stock

## GENERAL EQUIPMENT

SE250 Signal Injector	5.15
TE7 Signal Tracer AF/RF	9.95
SWR50 SWR/Power Meter	19.50
LP30 30MHz Low Pass Filter	4.95
CX3A 150 watt 3-way AE Switch	7.50
DC25kV 100 Meg HV Probe	11.95
DR10 36 Value Resis Box	3.95
RP124 D/24v 0/1 Amp P/S Stabilised	
Single Meter	42.00
RP230M 0/30v 0/1 Amp P/S Twin Meters	85.00
TR1000 Transistor checker in/out circuit	11.95
MDD83 Signal injector	8.65
L81 Transistor/Diode Checker	21.50
3101 Clamp Meter 0/1 K ohm 0/150/300/600 AC Volts 0/300 Amp	35.95
SWR9 SWR & FS Meter	10.50
SWR10 SWR Meter	12.50
MS319 2x100 Watt Audio Watt Meter	13.95
*500V Megohmmeter 500 Megohms	51.00
*2 1/2 Amp Variable Transformer	21.95

## GENERATORS

TG152 Series 3Hz 300kHz 5 Ranges	86.25
TG152Dm (with meter)	107.50
TG200 Series HC Oscillators Sine/Square output 1Hz-1MHz 12 Ranges	113.95
TG200Dm (with meter)	139.50
TG200Dmp (meter and fine control)	145.90
TE22D (Audio) 4 bands Sine 20-200KHz Square 20-150KHz	69.00
4001 Digital Pulse Generator 0.5Hz-5MHz	105.00
2001 Function Generator/Sine/Square/Triangle/TTL Square 1Hz-100kHz	86.00
605Z PAL UHF/UHF colour Bar Generator	250.00

## PROTO BOARD IN STOCK

KITS PR6 £9.20, PR 100 £11.80.  
SEPARATES EXP300 £5.75, EXP600 £6.30, QT7B £1.30, EXP4B £2.30.

## LOGIC PROBES AND MONITORS

LT2000 Economy Probe 10MHz	11.95
LM1 Monitor	33.00
LP1 Probe 10MHz	35.50
LP2 1 5MHz	20.50
16-pin IC test clip	1.95

## PIEZO HORN TWEETERS

Up to 100 watts each No x-over reqd. Only	4.95 ea
Flared Horns	6.50
Midrange Flared Horns	9.95
(P/P 20p per 1 or 2 30p per 3 to 5)	

## DRILLS AND DRILL KITS

9 and 12 volt Operated 1/4" max SMALL DRILL with collets	6.85
MEDIUM DRILL with 3 collets	9.90
SMALL DRILL with 20 drills, etc	16.95
SMALL DRILL with 6 P/C drills	12.95
MEDIUM DRILL with 20 drills, etc	16.95
MAINS Eliminators	9.95
VARIABLE Speed	13.95
12 volt 1/2" Heavy Duty Drill	12.50

## TV SOUND


High quality TV sound from your Hi-Fi Simply plug into aerial socket of your FM tuner. £6.50 (UK P&P 50p)  
As reviewed by 'Popular Hi-Fi', July '79

## SPECIAL OFFER

GEC 10+10 watt Tuner/Amplifier, MW/LW/SW/Stereo FH. Supplied as two easy to connect units. £24.95 P&P £1

## WE SELL


Kef. Seas, Audax, Fane, Goodmans, Motorola Peerless Speakers/Kits, etc Also Irons Tools, etc.

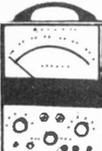

TM11



TMK500

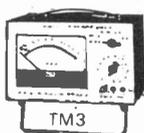

TM3

CALL IN AND SEE FOR YOURSELF

PRICES CORRECT AT 10.8.79

# AUDIO ELECTRONICS

301 EDGWARE RD., LONDON W2 1BN  
01-724-3564. OPEN 9-6, MON-SAT.


ALSO AT 248 TOTTENHAM COURT ROAD W 1

FREE CATALOGUE


SEND STAMPED (12" x 6")  
ADDRESSED ENVELOPE (MIN 9" x 6")  
FOR YOUR COPY NOW

# The latest kit innovation!

# from Sparkrite

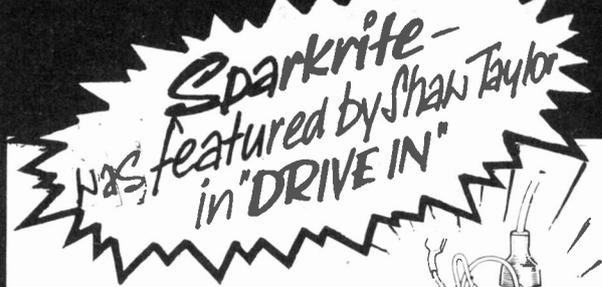

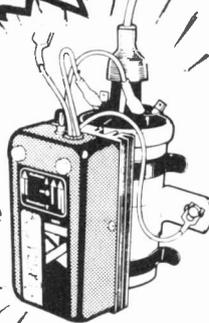the quickest fitting  
**CLIP ON**  
capacitive discharge  
electronic ignition  
in KIT FORM



- Smoother running
- Instant all-weather starting
- Continual peak performance
- Longer coil/battery/plug life
- Improved acceleration/top speeds
- Optimum fuel consumption

Sparkrite X4 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 1/3 mins. Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). The circuit incorporates a voltage regulated output for greatly improved cold starting. The circuit includes built in static timing light, systems function light, and security changeover switch. All kits fit vehicles with coil/distributor ignition up to 8 cylinders.

## THE KIT COMPRISES EVERYTHING NEEDED

Die pressed epoxy coated case. Ready drilled, aluminium extruded base and heat sink, coil mounting clips, and accessories. Top quality 5 year guaranteed transformer and components, cables, connectors, P.C.B., nuts, bolts and silicon grease. Full instructions to assemble kit neg. or pos. earth and fully illustrated installation instructions.

NOTE - Vehicles with current impulse tachometers (Smiths code on dial RV1) will require a tachometer pulse slave unit. Price £4.25 inc. VAT, post & packing.

Electronics Design Associates, Dept. ET10  
82 Bath Street, Walsall WS1 3DE. Phone: (9) 614791.

Name

Address

Phone your order with Access or Barclaycard

Including postage and packing UK only

QUANTITY REQ'D.

Send SAE if brochure only required.

X4 KIT £17.95 inc. VAT

TACHO PULSE SLAVE UNIT

£4.25 inc. VAT

I enclose cheque/PO's for

£

Cheque No.

Access or Barclaycard No.

# AUDIO COMPRESSOR

**Increase your talk power and improve legibility with this ETI Project team design that avoids the complication of RF clipping!**

THE HUMAN VOICE varies considerably in level, even when one is speaking in a normal conversational voice. The peaks are considerably higher than the lower levels, which can give rise to problems when the speech waveform is being modulated onto a carrier by a transmitter. For example, if the mic gain control is set so that the peaks are just giving 100% modulation, then soft sounds can barely be heard, whereas if the gain is turned up to give a higher level on vowel sounds, etc., then plosives (p-sounds) will give overmodulation and consequent splattering and poor speech quality.

A higher ratio of average power to peak voltage can be achieved by several methods, including

compression or clipping of the audio signal and compression or clipping of the radio frequency signal. Radio frequency compression or ALC (automatic level control) is often used in the final states of SSB transmitters.


Radio frequency clipping is the most effective method of increasing the average power; however it requires complex circuitry, since it is necessary to generate an SSB signal, clip, and then insert this signal into the transmitter IF chain.

Almost as effective as RF clipping is a combination of audio compression, clipping and filtering, which is relatively simple and can realise an improvement in signal to noise ratio of up to 5 dB on weak

signals.
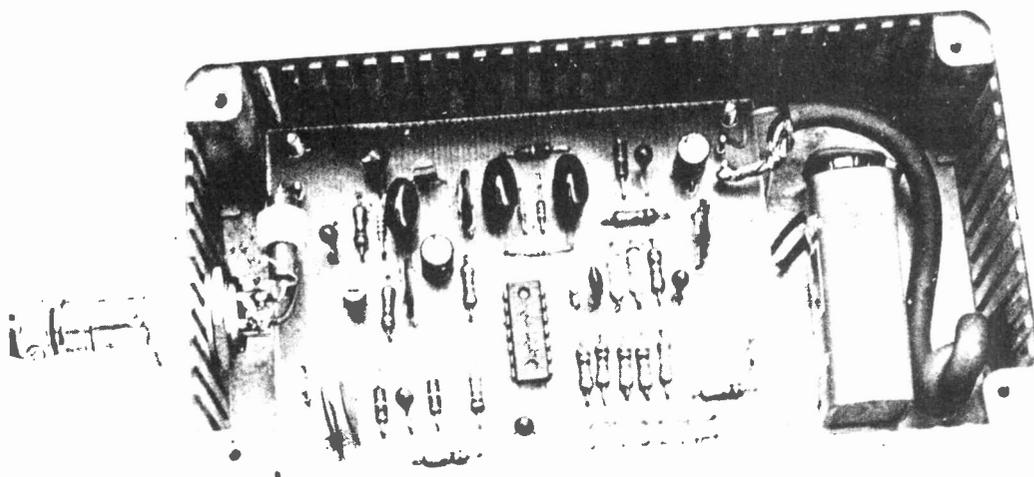
## Compression

When speaking into a microphone it is desirable to keep the voice level as constant as possible. This can be quite difficult as any change in the distance to the microphone will cause a drastic change in its output. To overcome this a variable gain amplifier can be used which senses the average speech level and adjusts its gain accordingly for a constant output voltage. The compressor operates with a fast attack (gain reduction) and a slow decay (gain increase), to quickly respond to the voice while remaining at this level to prevent amplification of background noise during speech pauses. ▶



**Inside view of the Processor.**  
The RF choke should be mounted as close as possible to the input socket.



## Filtering

When a waveform is clipped high order harmonics are produced which, if allowed to reach the transmitter, would cause splatter and interference to neighbouring stations. A filter must be used after the clipper to rapidly attenuate all frequencies above 3kHz, which are unnecessary for intelligibility. This is achieved by using an active filter with 12 dB/octave attenuation above 2k5 Hz.

## Clipping

The average power contained in a speech waveform is quite low compared to the peak voltage, and much less than the average power of a sine wave of the same amplitude. If the low energy high voltage peaks are cut off at a preset level the remaining signal can be increased without overdriving the transmitter. The average power is therefore increased. Clipping will slightly change the sound of the voice but will increase the intelligibility of a weak signal, as well as preventing the transmitter from being overdriven by limiting the maximum signal voltage.

## Construction

The speech processor is mounted in a diecast aluminium box to guard against feedback which can be caused by strong RF fields. Our box measured 150 mm x 80 mm x 50 mm deep. Either an internal 9V battery or the 12V transceiver supply can be used. The processor is designed to be used in the line from the microphone to the transmitter without any modification to either. A matching socket to the mic plug is used for the input and the output taken via a lead with a matching plug. The connections for the plug and socket vary between makes of transceivers and will have to be taken from the circuit diagram to the

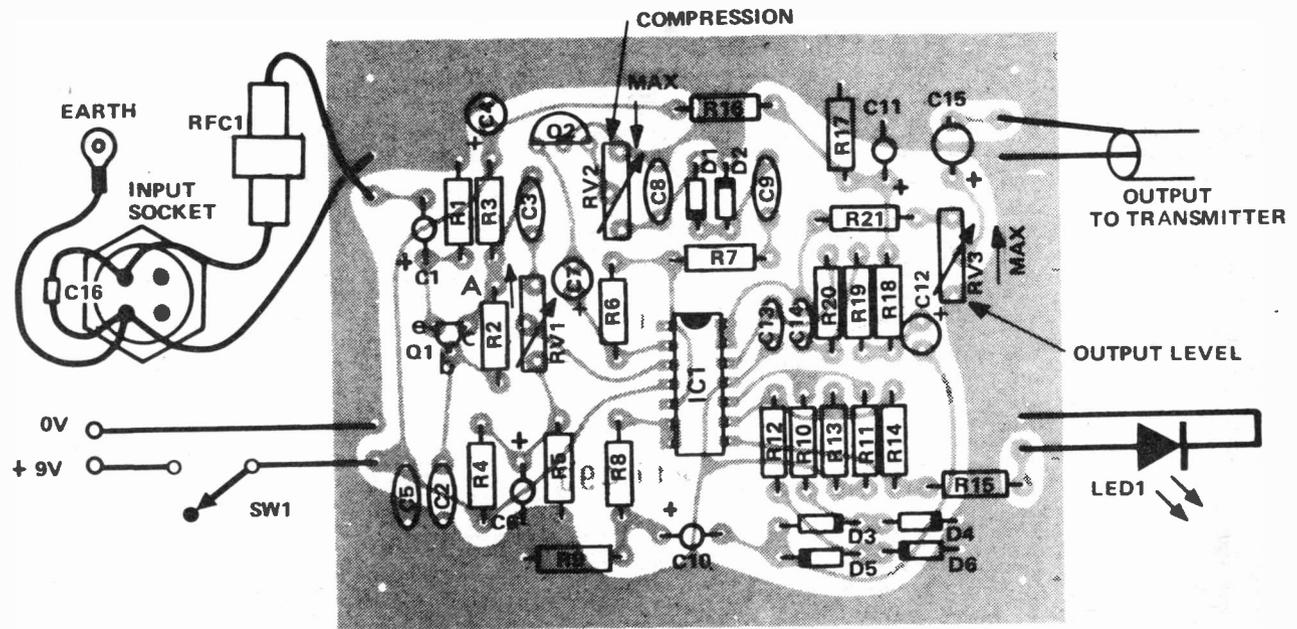


Fig. 2. Component overlay of the speech processor. Note the RF choke and capacitor mounted between the PCB and input socket.

transceiver. The clipping indicator (LED 2) and the power switch are mounted on the front panel.

## Setting Up

Turn the compressor control to maximum and speak into the microphone at the greatest distance you are likely to use (say 30 cm.). Increase the gain control until the clipping LED flashes. If this point cannot be reached decrease the compression control and try again. The setting of these two controls is best determined by on-air tests. The output level control should be set so the RF indicator on the transmitter reaches the same peak as with only the microphone plugged in.

For high output, high impedance microphones, such as crystal types, Q1 can be omitted, RV1 replaced with a 1M trimpot and the input fed to point A on the circuit.


The gain of Q1 is proportional to the value of R3. Increasing its value increases the gain. To guard against feedback the lowest value possible should be used.

## PARTS LIST

RESISTORS	all ¼W 5%	C2, 3, 8, 9	100n Polyester
R1, 9, 10, 12	10k	C4	33u 16V electrolytic
R2, 18	1M	C5	100n ceramic
R3, 8, 11, 13, 15, 21	1k	C7	10u 16V electrolytic
R4, 5, 16, 17	100k	C13	1n polyester
R6	68k	C14	3n3 polyester
R7	47k	C15	4u7 16V electrolytic
R14	270k	C16	1n ceramic
R19, 20	18k	SEMICONDUCTORS	
POTENTIOMETRES		Q1	BC549
RV1	47k lin trimmer	Q2	2N5485
RV2	1M lin trimmer	IC1	LM324N
RV3	100k lin trimmer	MISCELLANEOUS	
CAPACITORS		RFC1	1mH or higher
C1, 6, 10-12	1u 16V electrolytic	SW1	SPST min toggle
			MIC plug & skt, box to suit, battery & holder

# Simply ahead!
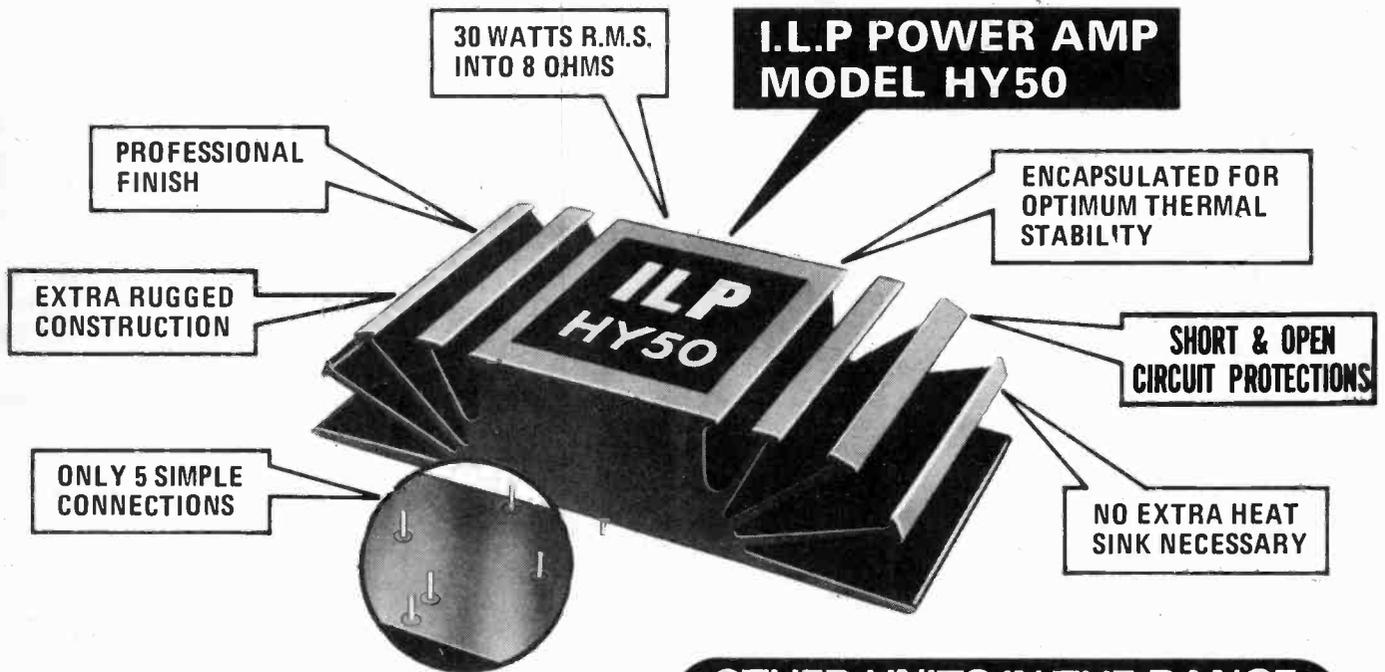
## HIGH PERFORMANCE MODULAR UNITS BACKED BY NO-QUIBBLE 5 YEAR GUARANTEE



Of all the purpose-built power amplifier modules by I.L.P., the HY50 is understandably the most popular with those wanting to build new or up-grade an existing hi-fi system, run a small high quality P.A. system, amplify a musical instrument (say for practice or small range use) or use it for lab work. Its useful 30 watts RMS output into 8 ohms, its rugged construction and freedom from heatsink worries make it the ideal all-purpose quality power amp — and it is unconditionally guaranteed for five years! Tens of thousands are in regular use throughout the world.

... and a spec that means just what it says!

Encapsulated power amp with integral full-rated heatsink.  
Input — 500mV.  
Output 30 watts RMS/8Ω.  
Load Impedance — 4 to 16Ω.

S/N Ratio 75dB  
Distortion — 0.02% from 100mW to 25 watts at 1KHz into 8Ω.  
Supply Voltage ± 25V. Size 105 x 50 x 25mm.

Inc. VAT and postage in U.K.

**£8.33**

Nothing has been overlooked in the design and manufacture of I.L.P. Modular Units. Heavy duty heatsinks, encapsulated circuitry, no-compromise production standards and true professional finish ensure world leadership in their field for I.L.P. Now we have **up-graded** output ratings and **down-graded** prices to bring I.L.P. within easier reach of all who want the best with which to build with. Prices reduced by an average around 20%.


**Guaranteed 7-day despatch on all products**

**FREE POST** — No stamp required when sending your order or enquiry for information sheets.

**ILP**  
**ELECTRONICS LTD.**

FREEPOST 4, Graham Bell House, Roper Close, CANTERBURY  
Kent CT2 7EP. Phone (0227) 54778. Telex: 965780

### OTHER UNITS IN THE RANGE

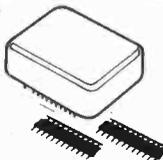


All prices inc. VAT at 15% and postage in the U.K.

#### HY5 PRE-AMPLIFIER

Compatible with all I.L.P. power amps and P.S.U.s. In a single pack, needs external pots and switches. Multi-function equalization. Mag./Ceramic/Tuner/Mic./Aux. inputs. High overload margin. Active tone controls; 500 mV out. Distortion at 1 KHz — 0.01%. Two HY5s connect easily for stereo.


**£5.34**

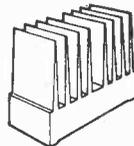

#### THE POWER AMPS

With heatsinks, full load line and thermal protection.  
Distortion typically 0.05% at 1 KHz.

HY120	60 Watts RMS/8 Ω	114 x 50 x 85mm	£17.48
HY200	120 Watts RMS/8 Ω	114 x 50 x 85mm	£21.21
HY400	240 Watts RMS/4 Ω	114 x 100 x 85mm	£31.83

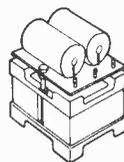

#### THE POWER SUPPLY UNITS

(Split line outputs to suit I.L.P. power units and HY5).

PSU 50	for 1 or 2 x HY50	£9.32
PSU 70	for 1 or 2 x HY120	£15.65
PSU 90	for one HY200	£15.65
PSU 180	for one HY400 or 2 x HY200	£26.47

### ★ NOW-PRICES DOWN BY 20%

Please supply .....

Total Purchase Price .....

I enclose Cheque  Postal Orders  Money Order

Please debit my Access/Barclaycard Account number.


Name and address .....

Signature .....

F.P.48

ELECTRONICS TODAY INTERNATIONAL — OCTOBER 1979

# SPECIALS

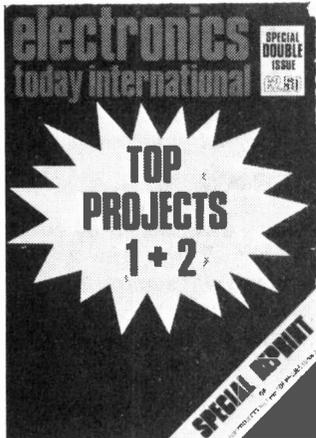

## TOP PROJECTS

Book 1 + 2: £2.50 + 25p P&P.

Master mixer, 100W guitar amp, low power laser, printmeter, transistor tester, mixer preamp, logic probe, Ni-Cad charger, loudhailer, 'scope callibrator, electronic ignition, car theft alarm, turn indicator canceller, brake light warning, LM3800 circuits, temperature alarm, aerial matcher, UHF-TV preamp, metal locator, four input mixer, IC power supply, rumble filter, IC tester, ignition timing light, 50W stereo amp. and many more.

Book 3: SOLD OUT!

Book 4: £1.00 + 25p P&P.

Sweet sixteen stereo amp, waa-waa, audio level meter, expander/compressor, car theft alarm, headlamp reminder, dual-tracking power supply, audio millivoltmeter, temperature meter, intruder alarm, touch switch, push-button dimmer, exposure meter, photo timer, electronic dice, high-power beacon, electronic one-armed bandit ...


Book 5: £1.00 + 25p P&P.

5W stereo amp, stage mixer, disco mixer, touch organ, audio limiter, infra-red intruder alarm, model train controller, reaction tester, headphone radio, STD timer, double dice, general purpose power supply, logic tester, power meter, digital voltmeter, universal timer, breakdown beacon, heart rate monitor, IB metal locator, temperature meter ...

Book 6: £1.00 + 25p P&P.

Graphic equaliser, 50/100W amp. modules, active crossover, flash trigger, "Star and Dot" game, burglar alarm, pink noise generator, sweep oscillator, marker generator, audio-visual metronome, LED dice, skeet game, lie detector, disco light show ...

Graphic Equaliser....Marker Generator  
Power Amplifier Modules....62 Sound  
CCTV Camera.....Headphone Adaptor  
LED Dice....Sound-Light Flash Trigger  
Expander-Compressor.....Skeet Game  
Rench Alarm  
**ETI TOP PROJECTS**  
**NO 6** electronics today £1  
Burglar Alarm...Digital Thermometer  
Stars & Dots Logic Game....Lightshow  
Active Crossover....Hear and Tell Unit  
Pink Noise Generator.....GSR Monitor  
Sweep Oscillator.....Stereo Simulator

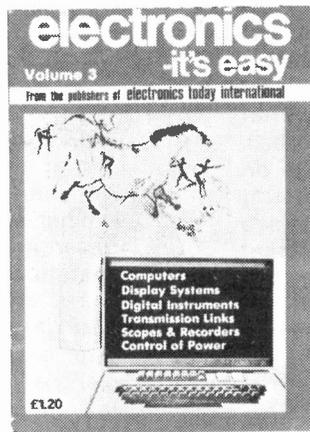

FROM THE PUBLISHERS OF  
ELECTRONICS TODAY INTERNATIONAL

## ETI CIRCUITS No 2

£1.50

## ELECTRONICS TOMORROW

Comprised entirely of new material, the edition covers such diverse topics as Star Wars and Hi-Fi! The magazine contains projects for everyone — none of which have appeared in ETI — and a look at the future of MPUs, audio, calculators and video. How can you not read it?

75p + 25p P&P.

## ELECTRONICS — IT'S EASY Books 1, 2 & 3.

Our successful beginners series came to an end some time ago now, and the whole series is available from us in reprint form. The three books between them contain all the information presented in the series (sometimes in more detail!) and together form an excellent starting point for anyone interested in learning the art of electronics.

£1.20 + 25p P&P each.

## ETI CIRCUITS Books 1 & 2.

Each volume contains over 150 circuits, mainly drawn from the best of our Tech-Tips. The circuits are indexed for rapid selection and an additional section is included which gives transistor specs, and plenty of other useful data. Sales of this publication have been phenomenal — hardly surprising when the circuits cost under 1p each!

£1.50 + 25p P&P each.

## ORDER FROM

Specials Modmags Ltd, 145 Charing Cross Road, London WC2

Postage and packing also refers to overseas. Send remittance in Sterling only.

Please mark the back of your cheque or PO with your name and address.



## TOP PROJECTS

Book 7: £1.25 + 25p P&P.

ER II loudspeaker, CCD phaser, 3-channel tone control, bass enhancer, continuity tester, bench supply, LCD digital multimeter, digital frequency meter, wide range oscillator, ETI wet, egg timer, house alarm, porch light, torch finder, light dimmer, IB metal locator, electronic bongos, puzzle of the drunken sailor, race track, ultrasonic switch, tic-tac radio, rev counter, Transcendent 2000, spirit level.

# from ETI

# microfile.....

**Henry Budgett, our busy micro-man, takes you on a tour of the latest shows and brings you up to date with the latest developments. Need a toolkit for your Pet?**

IT'S BEEN one of those months, if you know what I mean. You don't? Well the summer just seems to explode with things to do and places to go, so some of the items covered in this month's column are just a little late. Taking things chronologically, it helps. I shall start with the Microcomputer show. One short sentence can describe the overall situation. It was very hot and very busy!

Apparently the air conditioning had broken down on the Thursday but, despite repairs, it was still sweltering hot on the Friday morning. Nothing really spectacular was launched at the show but a large number of old friends were to be found. My first port of call was Technalogs, the Teletext/Prestel/BASIC system people, who were awaiting final PO approval. Well, as I mentioned briefly last month, they now have that approval and will commence delivery in September. They also had one of the rack mounting versions on display, complete with mini floppy. After breakfast at their stand, a quick pint, I moved round the hall to see Julian Allason at Petsoft. Trade there was so brisk that they had to send a truck back up to Brum twice for fresh stocks of software. Also there was Harry Saal, the man who brought you Cluster One, the distributed processing system.

## Lunch Break

Very thirsty work these shows, so after yet another pint in the company of a couple of my ex-colleagues who own a Research Machines, I carefully negotiated the rest of the hall. The Nanocomputer was there. A lot of people seemed to be very interested on the educational side.

The Nascom stand was overflowing as usual, they even sell T-shirts now. Apparently the '2' has gone into production at last, I wonder when we will see our review machine (gentle hint to Kerr).

The other main centre of interest was around the UK101. This is the redesigned Superboard II about which much rumour has been flying concerning legal action over software, PCB, etc. Nothing seems to have happened yet and the stand was certainly busy with interested people making up their minds to buy one.

The last laugh at the exhibition went to Online, the organisers. A friend of mine asked one of their staff where the nearest Tube was. "Thirty feet straight down" came the reply, nice one.


## Words On Words

Next in my crowded calendar comes the Word Processing Conference, held at Wembley. The Electronic Office seminar session that I attended was highly amusing. Presentations were given on the how's, why's and wherefore's of office systems by a number of companies, both British and American. However, the prize must go to the gentleman who floored the chair with some embarrassing comments on machine reliability after the Wang audio-visual extravaganza. After several seconds of embarrassed silence they decided to break for lunch. England 1, USA 0.

The companies on show all seemed to be vying for the most far out stand, the prettiest girls, etc. and overall I was left with the feeling that everyone had gone just a little over the top. Among the companies there were such giants as IBM and ICL as well as Wang and Wordplex among many others. It seems to me that the



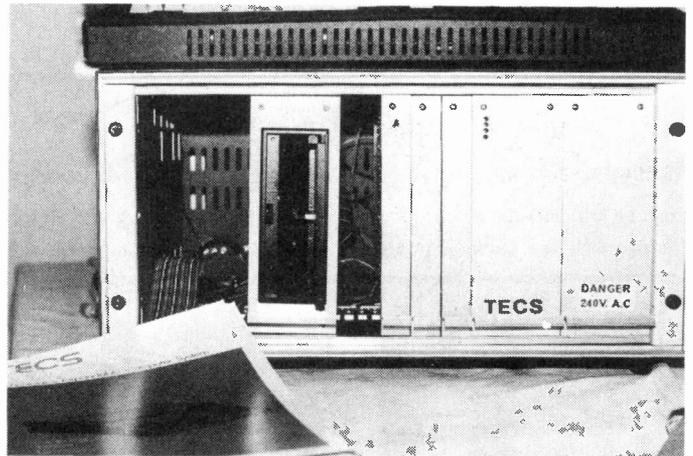Is it? No it's a UK101. Nearly the same though!



TECS's rack mounted Prestel system, disks coming soon.

WP field is really trying to exploit a market that is just not ready. Even the most sophisticated system will fall foul of a naive user and then the system gets the blame.

Once again thanks are due to Online, especially to the young lady who found me a set of conference notes after much hunting around.

### Northward Bound

Stage three of the month's travalogue takes place not a stone's throw from the Mersey. Liverpool, home of the music of the sixties and sit-coms, is also the home of Microdigital, who are not connected with either. They are, however, connected with microcomputers, and very seriously at that. They are one of the few UK computer shops to provide a full backup service in both hardware and software. Bruce Everiss, my host for the day, is justly proud of his achievements over the past year. They have expanded from shop to hire company and along the road have collected a software engineer, two hardware designers and the largest range of computer books in the country.

The software that they produce is mainly for local clients and is business orientated. The sample I tried, albeit only half developed, was very high quality indeed. The hardware team are currently working on a series of boards for the Nascom. The first, a relay board will be ready soon and the next one, an analogue input board is currently under design.

### Go West Young Man

Well, West was about the only direction left so I pointed my trusty vehicle in the direction of Newbury and went. The reason? To see the man who has probably done more to make the word software a household name than anyone, Julian Allason.

Despite the fact that Petsoft is now owned by ACT he has stayed on as a director and is actively engaged in finding software from any number of sources. His latest acquisition is the PET Programmers Toolkit, the goodie for PET that I mentioned earlier. Brought over from the States by Harry Saal and shown very briefly at the Microcomputer show it will so impressive that I went to see more.

It is really a piece of firmware, machine code program stored in a 2K PROM that plugs onto the PET expansion port. If you have a new ROM PET you only need the IC as it will plug inside your machine. Apart from plugging it

in no modifications are required and you have a vast increase in useability. If you have ever wished for built-in utility programs then this will provide them, it replaces about six cassette programs with single commands. I borrowed one of the only two samples to do a report for CT, but here are the available commands in a brief resumé.

AUTO: Automatic line numbering, any start, any step.  
 DELETE: Bulk line deletion, lines specified only.  
 RENUMBER: Any start, any step.  
 HELP: Displays just what caused that syntax error.  
 TRACE: Displays the last six program steps continuously, can be stopped and started at any time during run.  
 STEP: Single step version of TRACE.  
 APPEND: Compile programs from subroutine libraries on tape.  
 DUMP: Displays all variables and strings used in program.  
 FIND: Finds all occurrences of specified character string in the program.

The cost of this little gem is a mere £75 for the plug on version, £55 for the IC.

### Micro Coup


The latest coup for the firm is the acquisition of an American single board computer. Called the ACFA, it is based on the 6808, hopefully the 6809 soon, and has an impressive list of features. Complete with an 8K BASIC on cassette, it has 16K RAM, expandable to 48K RAM on-board, colour graphics using 4K of RAM, ASCII keyboard, Kansas City cassette and an RS232 interface. It will be supplied as a kit complete with PSU and case. The manuals supplied with the system are really a computer course on their own and have been prepared by Dr Veronis, a well-known American author.
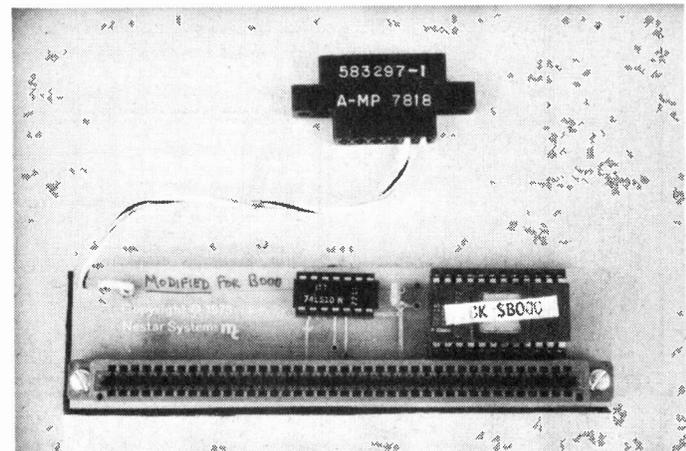
### The Final Word

The University of Salford have asked us to let you know about their forthcoming series of microprocessor courses. They are all one day courses and are being held in September. Preparing for the Microprocessors Age (Sept 24 £40), Fundamentals of Microprocessors (Sept 25 £60) and Microprocessor Systems (Sept 26 £60). A 10% discount is being allowed if more than one course is attended. For further details please contact Mrs Sumners, Room 110, University of Salford, Salford M5 4WT or ring 061-736 5842 extn 449. **ETI**



An open and shut case for the AIM 65. Get yours from Microdigital.



The PET programmer's Toolkit from Petsoft. The best thing to happen to a PET yet!

**QUARTZ LCD  
5 Function**

Hours, mins., secs., month, date, auto calendar, back-light, quality metal bracelet.

**£6.65**

Guaranteed same day despatch.  
Very slim, only 6mm thick.



M1

**SOLAR QUARTZ LCD  
5 Function**

Genuine solar panel with battery back-up. Hours, mins., secs. Day/date. Fully adjustable bracelet. Back-light. Only 7mm thick.

**£8.65**

Guaranteed same day despatch.



M2

**QUARTZ LCD  
11 Function** SLIM CHRONO

6 digit, 11 functions. Hours, mins., secs., day, date, day of week. 1/100th, 1/10th, secs., 10X secs., mins. Split and lap modes. Back-light, auto calendar. Only 8mm thick. Stainless steel bracelet and back. Adjustable bracelet. Metac Price

**£10.65** Thousands sold!

Guaranteed same day despatch



M3

**QUARTZ LCD  
ALARM 7 Function**

Alarm Hours, mins., secs. Month, date, day. 6 digits. 3 flags plus continuous display of day and date and seconds. Back-light.

**£12.65**

Guaranteed same day despatch



M4

**MULTI ALARM  
6 Digits  
10 Functions**

- \* Hours, mins., secs.
- \* Month, date, day
- \* Basic alarm.
- \* Memory date alarm.
- \* Timer alarm with dual time and 5 country zone.
- \* Back light.
- \* 8mm thick.


**£18.65**



M5

**FRONT-BUTTON ALARM  
Chrono Dual Time**

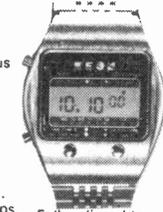6 digits, 5 flags, 22 functions. Constant display of hours and mins. plus optional seconds or date display. AM/PM indication. Month, date. Continuous display of day. Stop-watch to 12 hours 59.9 secs. in 1/10 second steps. Split and lap timing modes. Dual time zones. Only 8mm thick. Back-light.



Fully adjustable open bracelet.

**£22.65**

Guaranteed same day despatch.

M6

**SOLAR QUARTZ LCD  
Chronograph with Alarm  
Dual Time Zone Facility**

6 digits, 5 flags, 22 functions. Solar panel with battery back-up. 6 basic functions stop-watch to 12 hours 59.9 secs. in 1/10 sec. steps. Split and lap timing modes. Dual time zones. Alarm. 9mm thick. Back-light. Fully adjustable bracelet.

**£27.95**



M7

**ALARM CHRONO  
with 9 World  
Time Zones**

- \* 6 digits, 5 flags.
- \* 6 basic functions.
- \* 8 further time zones
- \* Count-down alarm.
- \* Stop-watch to 12 hours 59.9 secs. in 1/10 sec. steps.
- \* Split and lap timing modes.
- \* Alarm
- \* 9mm thick.
- \* Back-light.
- \* Fully adjustable bracelet.

**£29.65**



M8

**SOLAR QUARTZ LCD  
Chronograph**

Powered from solar panel with battery back-up. 6 digit, 11 functions. Hours, mins., secs., day date, day of week. 1/100th, 1/10th secs. 10X secs., mins. Split and lap modes. Back light. Auto calendar. Only 8mm thick. Stainless steel bracelet and back. Adjustable bracelet. Metac Price

**£12.65**

Guaranteed same day despatch.



M9

**SEIKO Alarm Chrono**

LCD, hours, mins., secs., day of week, month, day and date, 24 hour Alarm, 12 hour chronograph, 1/10th secs., and lap time. Back light, stainless steel, HARDLEX glass.

List Price £130.00

METAC PRICE

**£105.00**



M10

**SEIKO MEMORY BANK  
Calendar Watch M354**

Hours, mins., secs., month, day, date in 12 or 24 hour format all indicated continuously. Monthly calendar display, month, year and all dates for any selected month over 80-year period. Memory bank function. Any desired dates up to 11 can be stored in advance. 2-year battery life.

List Price £130

Metac Price **£79.50**

Water resistant. M11



M11

**Dual Time-Alarm  
Chronograph**

Mineral glass face Battery hatch for DIY battery replacement. Top quality finish with fully adjustable bracelet.


Spec same as M6

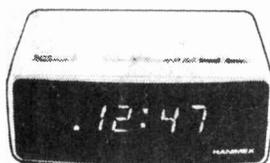**£35.00**



M12

**HANIMEX  
Electronic  
LED Alarm Clock**



Features and Specification Hour/minute display Large LED display with p.m. and alarm on indicator. 24 Hours alarm with on/off control. Display flashing for power loss indication. Repeatable 9-minute snooze. Display bright/dim modes control Size 5 15" x 3 93" x 2.36" (131mm x 11mm x 60mm) Weight 1.43 lbs (0.65 kg)

**£9.65** Thousands sold!  
Mains operated.

Guaranteed same day despatch.

M13

**HANIMEX  
Portable LCD  
Clock Radio**

- \* Back-light.
- \* Batteries supplied free.
- \* Quartz crystal controlled.

**£17.95**



M14

**QUARTZ LCD  
Ladies 5 Function.**

Only 25 x 20mm and 6mm thick. 5 function. Hours, mins., secs., day, date and back light and auto calendar. Elegant metal bracelet in silver or gold. State preference.

**£9.95**

Guaranteed same day despatch.



M15

**PRICE BREAKTHROUGH  
ONLY**

**£18.95**



**OUTSTANDING FEATURES**

- **DUAL TIME:** Local time always visible and you can set and recall any other time zone (such as GMT). Also has a light for night viewing.
- **CALENDAR FUNCTIONS** include the date and day in each time zone
- **CHRONOGRAPH/STOPWATCH** displays up to 12 hours, 59 minutes, 59.9 seconds.
- On command stopwatch display freezes to show **intermediate (split/lap) time** while stopwatch continues to run. Can also switch to and from timekeeping and stopwatch modes without affecting either's operation.
- **ALARM** can be set to any time within a 24-hour period. At the designated time, a pleasant, but effective buzzer sounds to remind or awaken you!

Guaranteed same day despatch. **M16**

**HOW TO ORDER**

Payment can be made by sending cheque, postal order, Barclay, Access or American Express card numbers. Write your name, address and the order details clearly, enclose 30p for post and packing or the amount stated. All products carry 1 year guarantee and full money back 10 day reassurance. Battery fitting service is available at our shops. Also Electronic Calibration Service. All prices include VAT.

**Metac Wholesale:**

**Trade enquiries:** Send for a complete list of trade prices and minimum order details  
Telephone Orders: Credit card customers can telephone orders direct to Daventry or Edgware Rd., 24 hour phone service at both shops: 01-723 4753 03272-76545.



**CALLERS WELCOME**  
Shops open 9.30 - 6.00.

**Metac**

**ELECTRONICS  
& TIME CENTRES**

**North & Midlands**  
67 High Street, DAVENTRY  
Northamptonshire  
Telephone: 03272 76545

**South of England**  
327 Edgware Road  
LONDON W.2  
Telephone: (01) 723 4753

# HIGH QUALITY AUDIO AMPLIFIER

If you're in the market for a true hi-fi amplifier, this is the place to start. A superb design which offers a reproduction quality equal to the very best around today.

IT HAS BEEN some time since we featured a complete stereo amplifier design in ETI — receivers and power amps yes, but not a full hi-fi set-up. When considering putting this right, we wanted to produce a design that could stand with the best commercial units of the day, and yet offer a considerable price saving over such designs in return for the effort of "doing it yourself."

We believe our Audiophile 4000 fulfills these aspirations nicely.

## Full Of Philosophy

A study of the specification will show that our amp has no need to fear comparison with any other unit. That 60W RMS power rating is deceptive too — built with our PSU the 4000 will outperform most


100W rated commercial designs in terms of transient delivery, bass quality and sheer 'dynamics'.

Listening tests played a large part in determining the final design, and particular stress was placed upon delivery of detail and elimination of TID.

Construction is modular, and we have housed the system in THREE cases. Pre-amp, power amps and pre-amp PSU. You can of course

ignore our suggestions and build the whole thing in one box using one PSU for everything. You can *also* expect degraded performance if you do! Separate power supplies for each channel of the power amp should not be considered optional — they are very important to the final specification.

The three case approach has several advantages — not least of which is hum reduction. Casing it ►

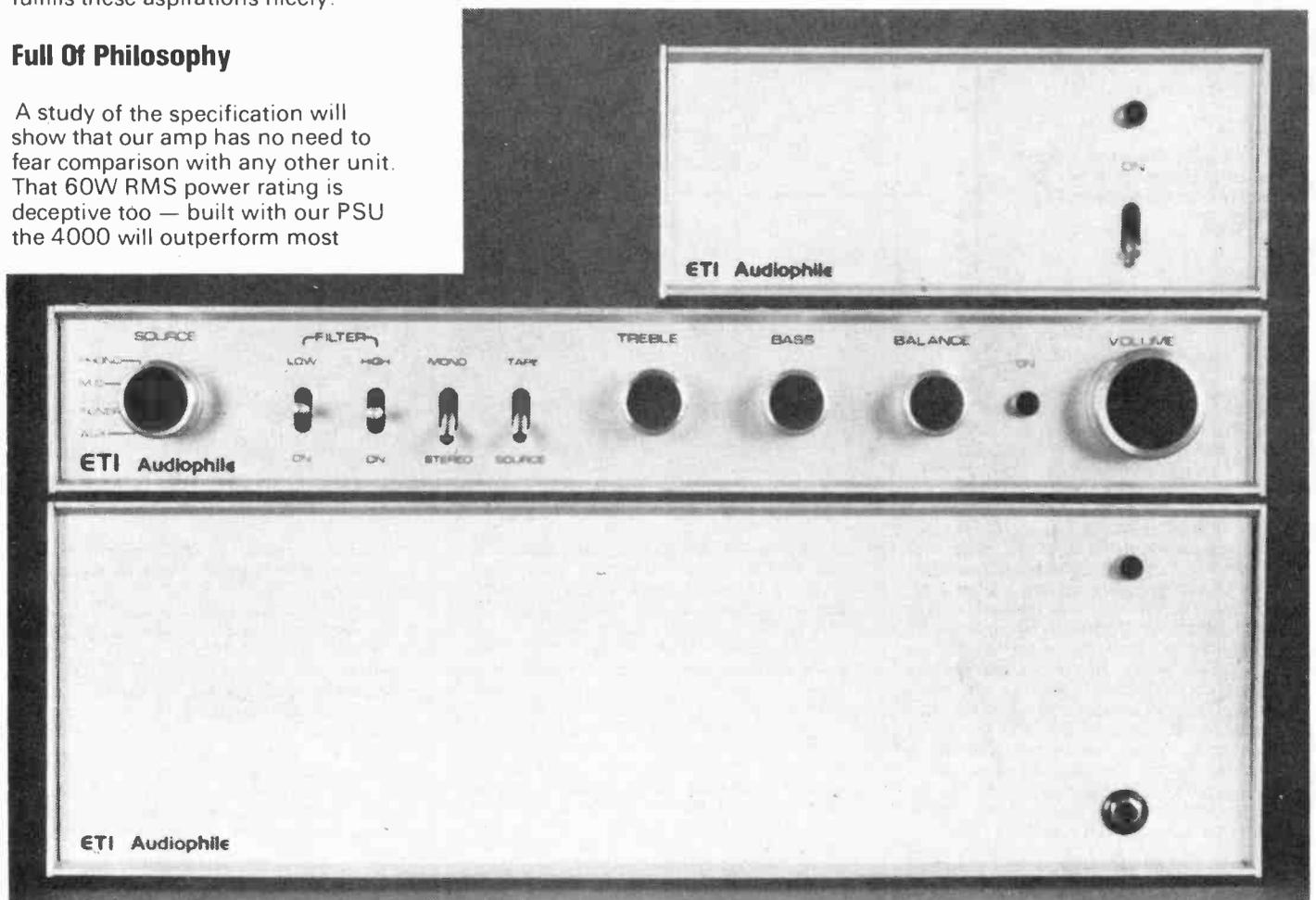

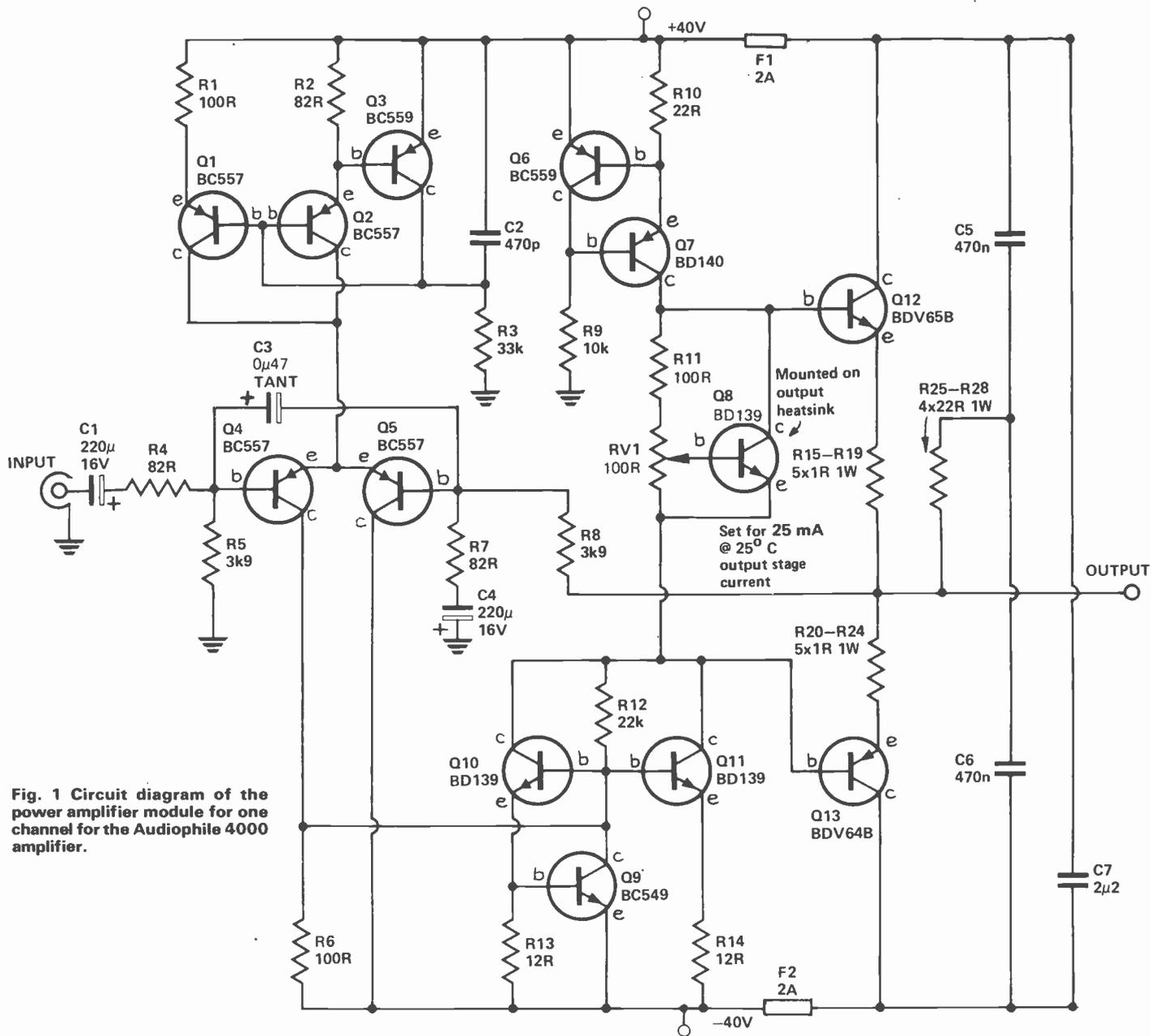


Fig. 1 Circuit diagram of the power amplifier module for one channel for the Audiophile 4000 amplifier.

## HOW IT WORKS

The input stage of the amplifier consists of an emitter coupled differential pair (Q4, Q5) with a constant current source (Q1, Q2 and Q3). The use of a constant current source reduces distortion, as well as the possibility of high frequency oscillation and prevents any ripple on the positive supply from unduly affecting the input stage. Unequal emitter resistors (R1, R2) allow the currents in Q4 and Q5 to be optimised. Input lag compensation is provided by C3, limiting the slew rate of the amplifier to reduce high frequency intermodulation. The gain of the differential pair, driving Q10 and Q11, is very low.

Almost all the gain of the amplifier

is obtained from the parallel pair Q10 and Q11. They are operated with series (R13, R14) and shunt (R12) feedback, and a constant current source (Q6, Q7). This results in a highly linear stage.


Q9 protects Q10 and Q11 from high peak currents or damage should a fault occur. When the current through R13 exceeds the safe limit, Q9 conducts and shorts out the drive to Q10 and Q11.

Bias from the output stage is set by RV1 and a shunt regulator (Q8). Q8 is mounted on the same heatsink as the output stages and stabilises the output bias current against heatsink temperature rise. Resistors R15-R24 in the emitters of the output Darlington, Q12 and Q13,

maintain operation in their safe region as well as reducing the chance of thermal run away.

Protection against ultrasonic oscillation is provided by C7 and the network consisting of R25-R28 and C5, C6.

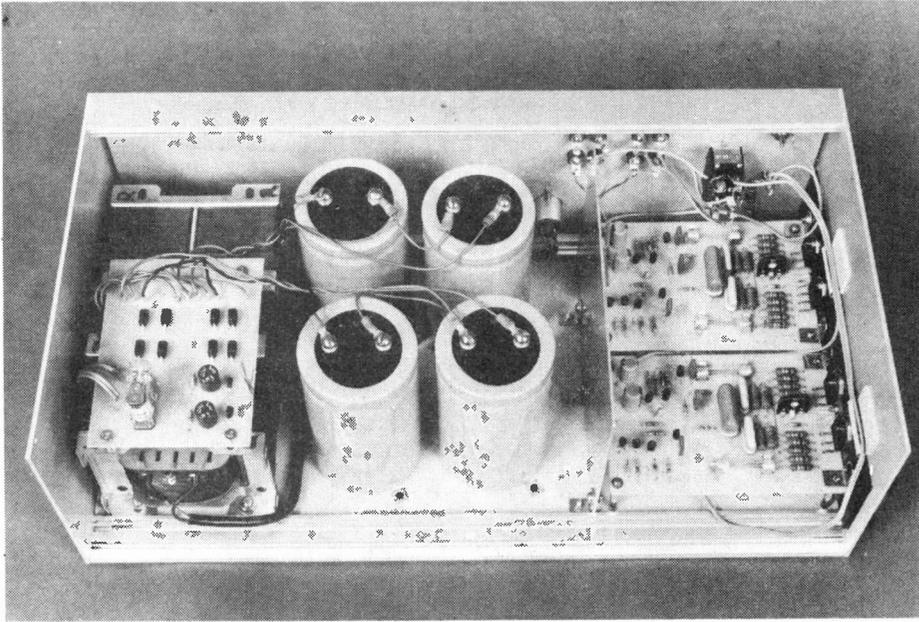Both DC and AC feedback is taken from the output, via R8, to the negative input of the differential pair, the amount of feedback being set by the ratio of R8 to R7. C4 increases the feedback, at very low frequencies. The feedback also automatically holds the DC output voltage at close to zero volts.



Inside the power amplifier case. The power supply for each channel sits on the right of the enclosure, and the rectifier board and de-thump board sits on top of the transformers. Note the screen between channels and the screening between modules and PSUs. Don't be tempted to use a single PSU for both amps — this will degrade transient performance to a considerable degree.

this way is a good 6dB better than the cheaper alternative is likely to be. Separate PSUs for the power and preamp also avoids LF instability caused by supply line droop when the output pair draw heavy currents.

## Preamp Pondered

The requirements for the control section of the system were set down after many hours of office discussion. In fact it would be fair to say that it evolved rather than was conceived.

There is still much discussion around the subject of tone controls and filters in amplifiers. A strong lobby exists to dispose of them completely, indeed in *systems* of the highest quality and in good listening conditions they have little to do with accurate sound replay.

However as most (nearly all) hi-fi falls far short of this level we have included them on our PCB. Also present are loudness, mute, low cut and high cut filters — the latter being of low phase shift variety at sensible turnover frequencies. These can be omitted from the final unit as you will. On our prototype, no loudness or mute facility was included, as you can see from the photos.

The MC input is in fact not RIAA equalised, to allow for connection of a head amplifier, one of which would almost certainly accompany the cartridge. We are working on a design for a mains powered unit ourselves and will present this at a later date, in a style to match the Audiophile.

The disc pre-amp section of an amplifier must be capable of handling very high input signals before clipping to preserve dynamic range — especially when used with head amps — and ours can take 400mV ptp before clipping. Dynamic range > 100dB).


## Powerful Discussion

This power amplifier offers a significant improvement in specifications and ease of construction over most kit amplifiers offered to date. It has been designed particularly with low transient intermodulation distortion in mind.

Although a difficult parameter to measure, transient intermodulation distortion is an inherent characteristic of many amplifier designs — especially those which incorporate large amounts of feedback to even out frequency response and reduce

## SPECIFICATION ~ POWER AMP

Power Output	60 watts into 8 ohms (±40V supply)
Frequency Response	10 Hz to 100 kHz ±0.5 dB
Input Sensitivity	500 mV rms for 60 W output
Hum and Noise	better than -110 dB on full output (dependent on power supply)
Feedback Ratio	35 dB
Distortion	at 1 kHz, 30 V p-p output into 8 ohms, Closed Loop . . . . . 0.04 % (open loop 1 %)
Stability:	The amplifier was found to be completely stable when operated into reactive loads consisting of R + C, L + C and pure L
Intermodulation (calculated values)	at 1kHz, 30 V p-p output into 8 ohms, 3rd order . . . . . less than 0.015 % 5th order . . . . . less than 0.0023 % (Intermodulation reduces with reduced power)

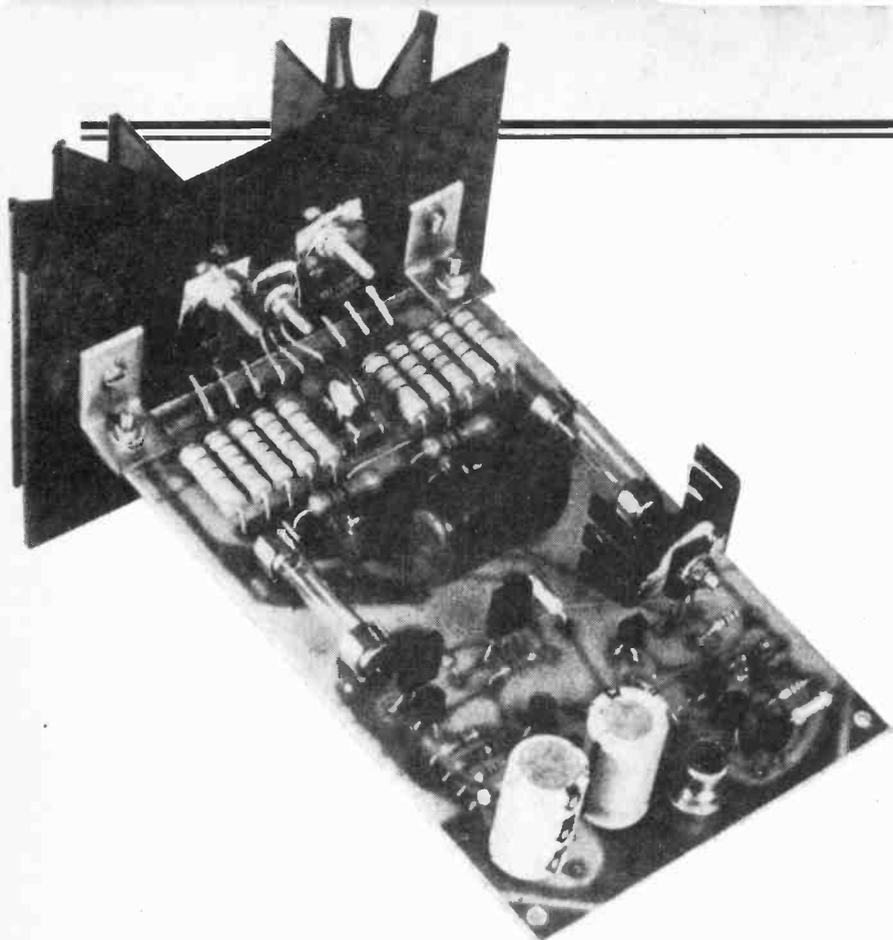

A completed module — fitted with phono socket input. This is optional, and if omitted wire direct to the foil side of the board. Below: — Fig. 2. Component overlay for the amplifier module.

## PARTS LIST

### POWER AMPLIFIER (each channel)

RESISTORS all 1/4W 5% unless marked

R1, 6, 11	100R
R2, 4, 7	82R
R3	33k
R5, 8	3k9
R9	10k
R10	22R
R12	22k
R13, 14	12R
R15-R24	1R 1W
R25-R28	22R 1W

### POTENTIOMETERS

RV1	100R trimmer
-----	--------------

### CAPACITORS


C1, 4	220u 16V	2x14
C2	470p ceramic	
C3	470n tantalum	
C5, 6	470n polyester	
C7	2u2 polyester	


### SEMICONDUCTORS

Q1, 2, 4, 5	BC557	15x4
Q3, 6	BC559	20x4
Q7	BD140	36
Q8, 10, 11	BD139	40x3
Q9	BC549	13
Q12	BDV65B or TIP142	100
Q13	BDV64B or TIP147	100
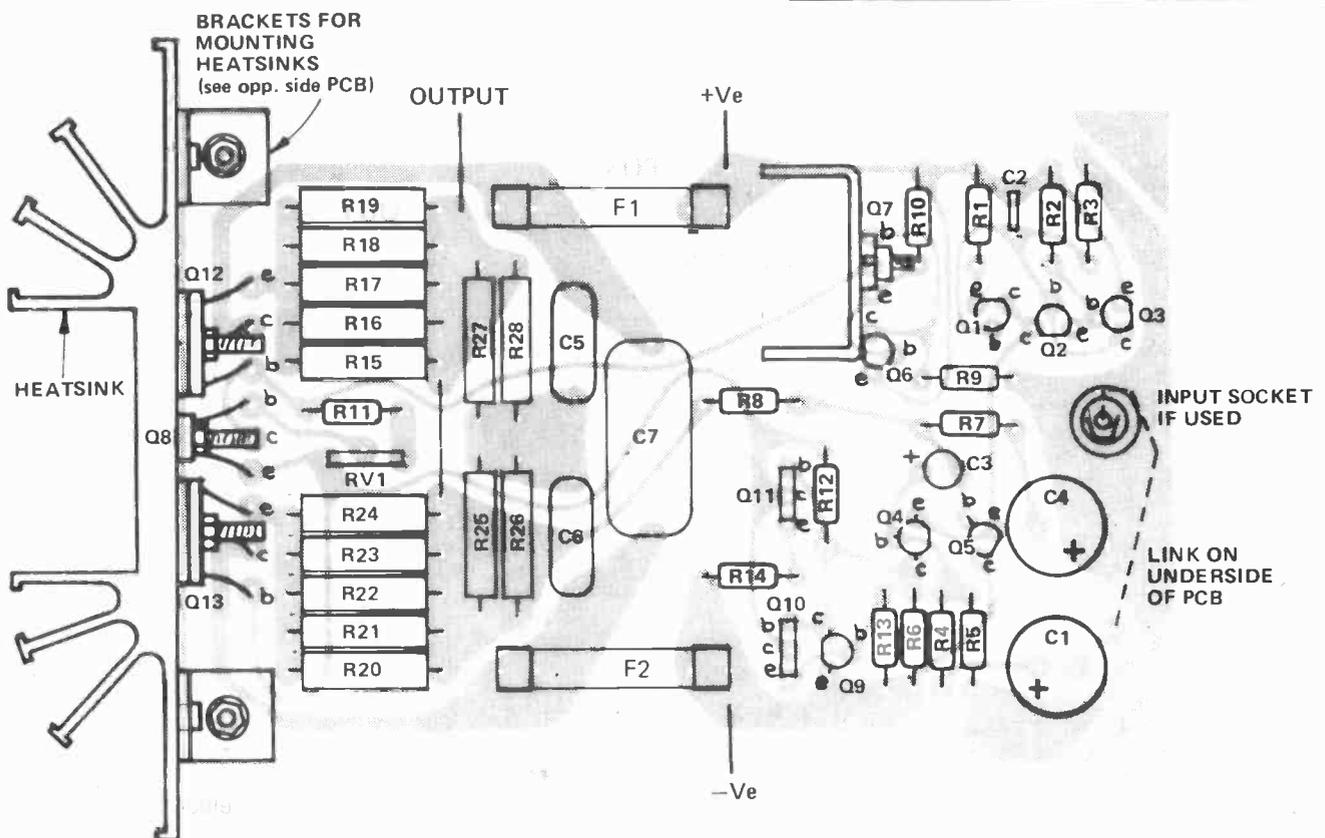
### MISCELLANEOUS

2A Fuse (2 off) with holders, insulating kits for Q8, 12, 13 heatsinks, brackets, spacers, PCB



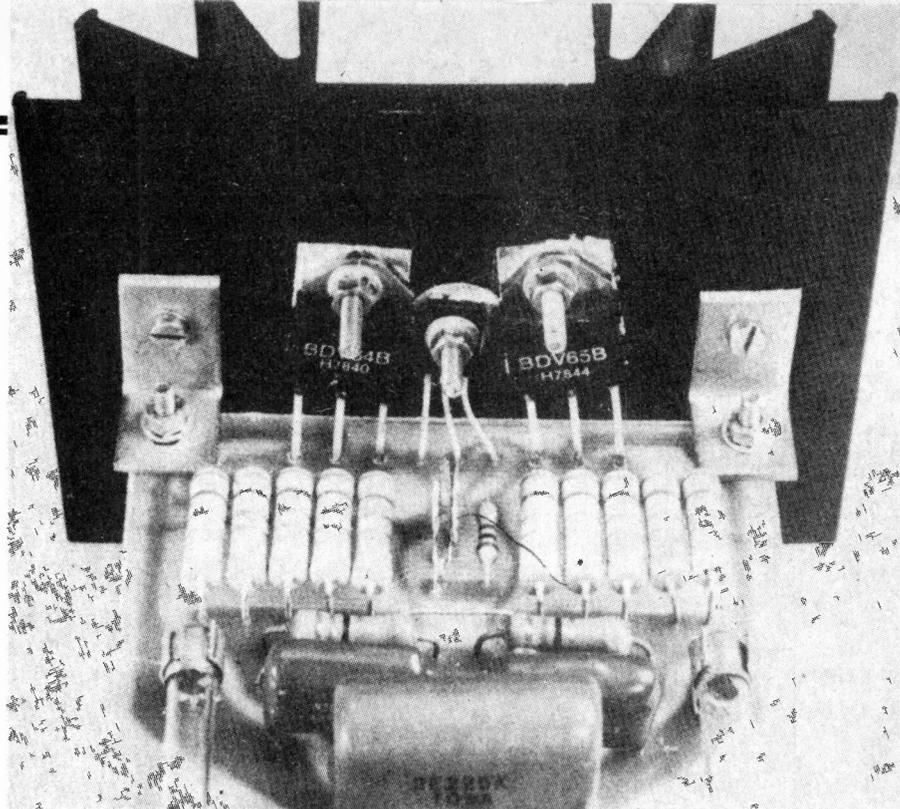

harmonic distortion. The heavy feedback 'school' of design produces an impressive list of specifications — but the difference *to the ear* between such an amplifier and one designed for low TID has to be heard to be believed.

The design of the power supply can mean the success or failure of an otherwise well-designed amplifier. The supply voltage should be well-regulated, varying less than 10% from no load to full load, and be able to supply high peak currents.

However, if a voltage regulator is employed it too must be capable of delivering the very high peak currents occasionally demanded. This necessitates an expensive regulator device and large, expensive filter capacitors.

The alternative is to use a fairly large transformer and large value filter capacitors on a capacitor-input bridge rectifier. This is what we chose.

## WHY LOW TID?

Looking at the circuit and a quick glance at the specifications, there's little in the circuit that looks outstandingly different from others. So what makes this amplifier special?

The difference in concept that makes this amplifier unique is the use of a very linear, high gain driver stage (Q10, Q11), with a constant current source (Q6, Q7), so that the gain of *this* stage is dependent upon the input impedance of the output transistors. However, *their* input impedance is dependent upon their gain, and therefore *the gain of the amplifier stage is dependent solely upon the characteristics of the output devices.*

Series and shunt feedback is used with Q10 and Q11 which results in a highly linear stage with a very low input impedance (about 28 ohms). The gain of the differential pair when

fed into this low impedance is close to unity, so almost all the gain of the amplifier is concentrated in Q10 and Q11.

Provided the phase shifts in the differential pair and the gain stage are negligible the feedback loop is unconditionally stable.

There are two other design features which result in low TID.

The total open loop (feedback disconnected) distortion is only 1% at 30 V p-p output. So, very little feedback is necessary to reduce this to an acceptable level.

Protection of the output transistors is done by fuses, rather than electronically, and very high transient currents can be fed to the speaker without being affected by the (inevitably) non-linear impedance of an electronic protection circuit.

## Powering Supplies

The circuit given here shows a power supply suitable for supplying a stereo amplifier using two of these modules. The filter capacitors C8 and C9 consist of two 15000  $\mu$ F, 60 volt electrolytic capacitors. This is the minimum value we would recommend.

The power supply output should be limited to a peak DC voltage of about 40 volts (for 60 W output). A C-core transformer will generally improve the hum and noise output figures apart from having a reduced field, thereby reducing possible hum pickup problems.

If the amplifier module is to be used with a 4-ohm speaker system the supply voltage must be limited to about 30 volts maximum, otherwise the output devices will attempt to deliver 100 watts followed by rapid self destruction!

Adventurous constructors may wish to try adding a second set of Darlington output devices, with their own emitter resistors as per the circuit, connected in parallel with the original pair. This combination may supply 100 watts or more into a four ohm speaker load. This technique is also recommended if you are contemplating driving highly reactive loads such as electrostatic loudspeakers.


## PULSE TESTING


*Operation into severely reactive loads was examined by looking at the ac component of the  $V_{be}$  of Q10 as a measure of the 'overshoot' of the loop and to see if transient overload occurred.*

$f = 1$  kHz. CRO is 0.2 mS/div. Output is 30 V into 8 ohms.

Upper trace 10 V/div. Output into 8 ohms.

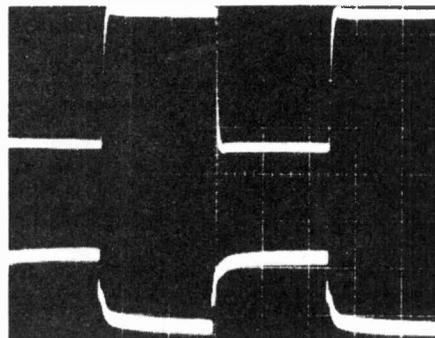Lower trace 10 mV/div.  $V_{be}$  of BD139 gain stage. No evidence of transient overload was visible.



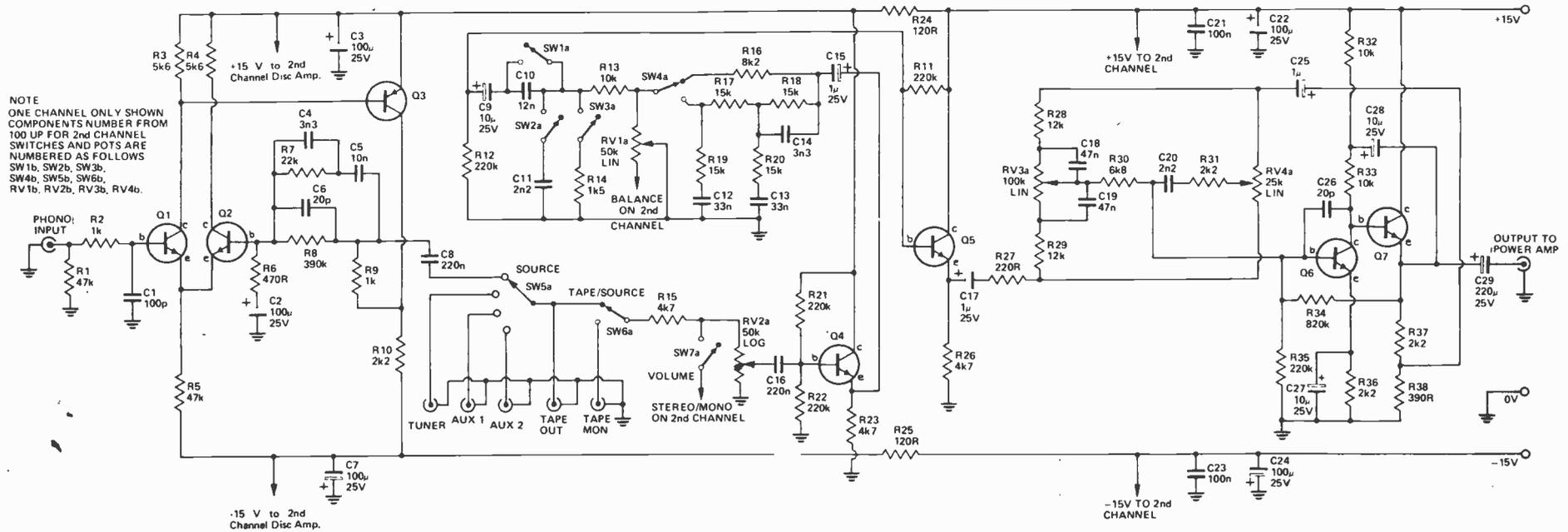

NOTE  
ONE CHANNEL ONLY SHOWN  
COMPONENTS NUMBER FROM  
100 UP FOR 2nd CHANNEL  
SWITCHES AND POTS ARE  
NUMBERED AS FOLLOWS  
SW1b, SW2b, SW3b,  
SW4b, SW5b, SW6b,  
RV1b, RV2b, RV3b, RV4b.

Fig 3. Circuit diagram of one channel of the preamp. Add 100 to all component numbers for second channel.

## HOW IT WORKS

The signal from a magnetic cartridge is fed to the base of Q1 via a low pass filter (R2 and C1) for attenuation of radio frequencies. Q1 and Q2 form a differential pair, each half operating at low collector current to minimise noise. The output of the differential pair is taken from the collector of Q1 and further amplified by Q3. Feedback is taken to the base of Q2, the negative input of the differential pair, through the RIAA equalisation network. Overall gain of the phono stage is set by the ratio of the feedback network impedance to the value of R6.

Subsonic bass roll-off of 6 dB/octave, to conform to the new IEC 65 specification, is achieved by a high pass filter consisting of C8 and RV2.

Output from the disc preamplifier is then fed via the Source Switch (SW5), Tape-Source switch (SW6), R15 and the volume control (RV2), to an emitter follower, Q4. This emitter follower presents a high impedance for the aux inputs and a constant impedance for driving the filters.

## SPECIFICATION ~ PREAMP

Distortion	.0015% at 1 kHz .0015% at 10 kHz (For all inputs, with 500 mV RMS output – distortion is mainly 2nd harmonic).	Output	.7 V p-p before clipping
Hum and Noise	.83 dB unweighted (With respect to 10 mV phono input).	Tape output	.150 mV RMS
Frequency Response	.Phono: Within 0.5 dB of RIAA from 20 Hz to 20 kHz (Follows new IEC curve).  Other inputs: 20 Hz to 20 kHz ± 0.5 dB  Subsonic rolloff: 6 dB/octave below 20 Hz	Sensitivity	.For 500 mV RMS output phono: 3 mV RMS other: 150 mV RMS (Phono overload level is 400 mV p-p).
		Tone controls	.Bass: ± 13 dB at 50 Hz Treble: ± 11 dB at 10 kHz
		Filters	.High: 6 dB/octave, -3 dB at 5 kHz Low: 6 dB/octave, -3 dB at 100 Hz
		Loudness	.8 dB boost at 15 kHz and 10 kHz.
		Mute switch	.20 dB attenuation

When switched in, the loudness network boosts the high and low frequencies with respect to the midrange. In actual fact, all frequencies are attenuated but the midrange is attenuated more. When the loudness is switched out, R16 approximates the impedance of the network.

Muting is achieved by switching R14 to earth. The ratio of R14 to R13 sets the attenuation to 20 dB. C11 shunts high frequencies to earth for high cut, while C10 reduces low frequency content when switched in, providing low cut.

A second emitter follower, Q5, presents a constant impedance source to the tone control stage.

A Baxandall tone stage is used here, a common circuit in many designs. Q6 is a gain stage with a bootstrapped collector load, via C28, to the output. Bootstrapping increases the gain by increasing the effective collection load impedance. Q7 is an emitter follower connected directly to the collector of Q6. This provides a very low output impedance. DC bias for Q6 is taken from the output.


Some of the output signal is fed back to the tone controls and split into high and low frequencies by RV3 and RV4. By adjusting the controls the percentage of the input to the negative feedback signal appearing at the base of Q6 can be varied, thereby varying the overall gain of the amplifier at either high or low frequencies. The gain of the tone stage is set by the ratio of R37 to R38. As R38 is reduced in value the negative feedback is reduced and therefore the overall gain is increased.

To preserve the very low output impedance of the pre-amplifier the balance control is placed ahead of, rather than after, the tone stage.


Power supply filtering and decoupling is provided by 1000u capacitors and resistors in each rail.
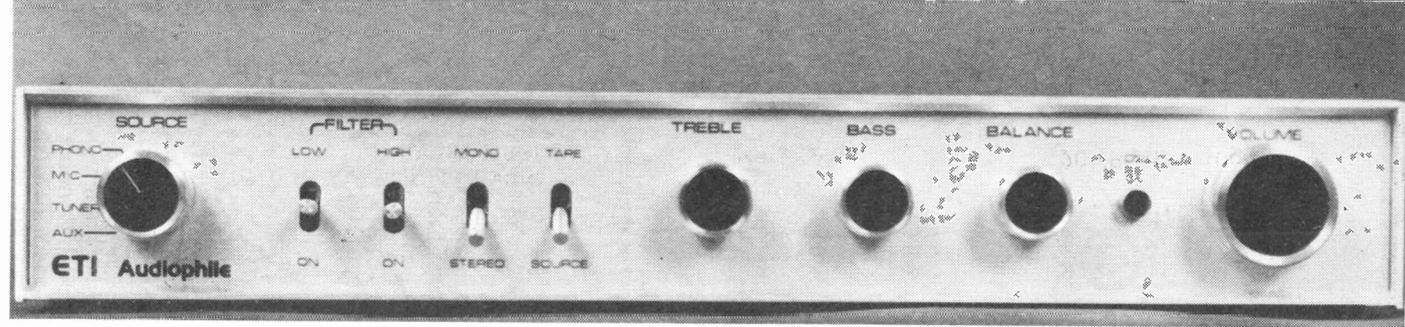
## Construction — Preamplifier

Assemble the PCB as per the overlay, checking carefully the polarity of all semiconductor and polarised components. Only attempt to wire the board to the chosen controls once you are satisfied that all is well. Check VERY thoroughly as mistakes now will cause quite a few headaches.



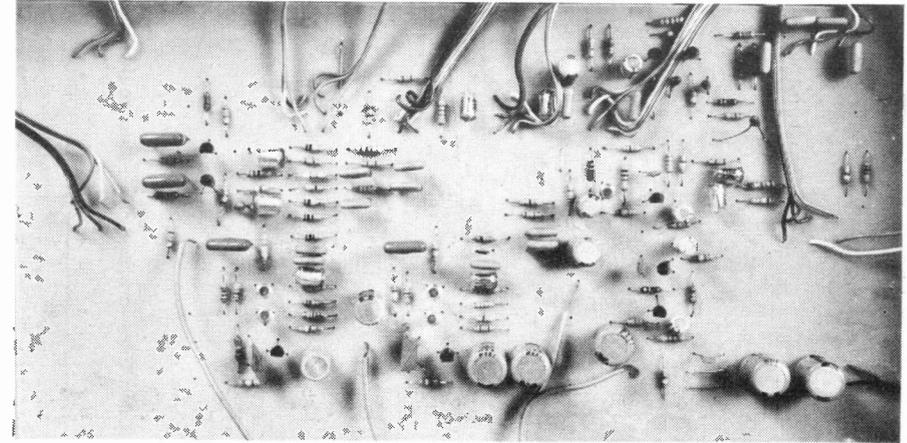Above: the finished preamplifier unit.  
Below: the PCB some way into construction.



Use only good quality screened audio cable for wiring between controls and board and keep the runs as short as you can. As there is no mains within the enclosure hum should not be a problem.

The PSU similarly is relatively simple to put together, but watch that mains wiring and make SURE the case is earthed. We used cannon connection for DC output. If you wish to fit mains outlets to power ancillary units, add them to this box, but watch the rating of the switch if it is to control everything.

When switching on don't forget the 'de-thump' circuit which will cause an agonising silence for several seconds after switch on!

## Construction — Power Amps

All components are mounted on a PCB — including the output devices. This method of construction is recommended. The module has been

designed so that it is mechanically simple to assemble, much simpler than our ETI 480 module.

Firstly, assemble and solder all the components on to the printed circuit board with the exception of Q12, Q13 (the output Darlington) and Q8. Carefully observe the polarity of all the electrolytic capacitors and orientation of the transistors.

The board is mounted hard against the heatsink using small right-angle brackets. Be careful to avoid shorting the ends of the one ohm emitter resistors, R15-19 and R20-24, to the brackets.

If the module is to be mounted in a chassis the bottom (copper) side of the board should be 25 mm above the bottom of the heatsink. This will allow the use of 25 mm spacers to support the 'input' end of the board (furthest from the heatsink).

Once the board is attached to the heatsink the output Darlington, Q12 and 13, and Q8 may be mounted. Insert them in the board and then press them back against the heatsink to form their leads to the right shape. Do not solder their leads yet.

Smear heat conducting compound on either side of the mica insulators (don't use too much though) and insert these between the devices and the heatsink.

Assemble the washers and mounting bolts for these, finally checking with an ohm-meter that there is not a short circuit between the metal tags (collectors) of the devices and the heatsink.

The input connection to the module is via a length of shielded cable soldered directly between C1 and the board common.

The power supply and speaker connection are soldered directly to ▶

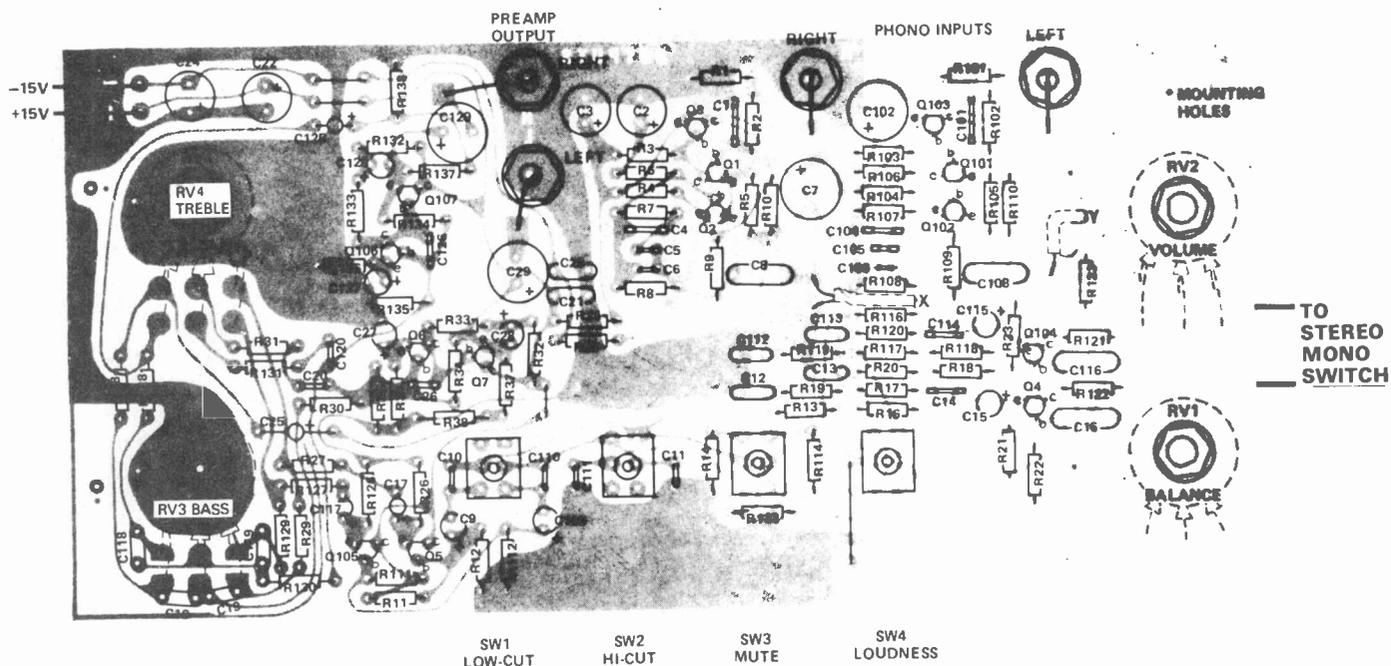


Fig 4. Component overlay for the pre-amp section of the 4000. Links X and Y are screened cable links to the 'phono' input of the selector.

## PARTS LIST

### Preamplifier

RESISTORS — all 1/4W 5%

R 1, 5	47k
R2, 9	1k
R3, 4	5k6
R6	470R
R7	22k
R8	390k
R10, 31, 36, 37	2k2
R11, 12, 21, 22, 35	220k
R13, 32, 33	10k
R14	1k5
R15, 23, 26	4k7
R16	8k2
R17-20	15k
R24, 25	120R
R27	220R
R28, 29	12k
R30	6k8
R34	820k
R38	390R

### POTENTIOMETERS

RV1	50k lin
RV2	50k dual log
RV3	100k dual lin
RV4	25k dual lin

### CAPACITORS

C1	100p ceramic
C2, 3, 7, 22, 24	100u 25V
C4, 14	3n3 polyester
C5, 10	10n polyester
C6, 26	22p ceramic
C8, 16	220n polyester
C9, 27, 28	10u 25V
C11, 20	2n2 polyester
C12, 13	33n polyester
C15, 17, 25	1u 25V tantalum
C18, 19	47n polyester
C21, 23	100n polyester
C29	220u 25V

### SEMICONDUCTORS

Q1, 2, 4-7	BC109, BC549
Q3	BC179, BC559
LED	TIL 220 or similar

### SWITCHES (see text)

SW1-4, 6	DPDT toggle
SW5	2 pole 4-way rotary (screened)
SW7	SPDT toggle

### MISCELLANEOUS

PCB, case, phono sockets, screened cable, spacers nuts and bolts etc.

Add 100 to component numbers for other channel

the appropriate copper lands on the underside of the board.


The 'earthy' side of the speaker must be returned directly to the zero volt connection of the power supply, as close to the filter capacitors as possible (preferably direct to the negative terminal). Do not connect this side of the speaker to the amplifier board.

### Setting Up


Once the amplifier has been assembled and carefully checked, the bias current for the output devices must be set. Remove the fuses, F1 and F2 and connect a 100 ohm resistor across each fuse holder. Remove any input signal. Connect the power supplies and measure the voltage drop across each of these resistors. Adjust the trim pot RV1 for a reading of 2V5 across each resistor. This corresponds to a bias current of 25 mA. The reading should be nearly the same across each resistor. Next check that there is no DC voltage across the output terminals.

If the reading across each of the resistors cannot be adjusted, or if there is a DC voltage across the output greater than one volt then there is a fault and the fuses should not be inserted.

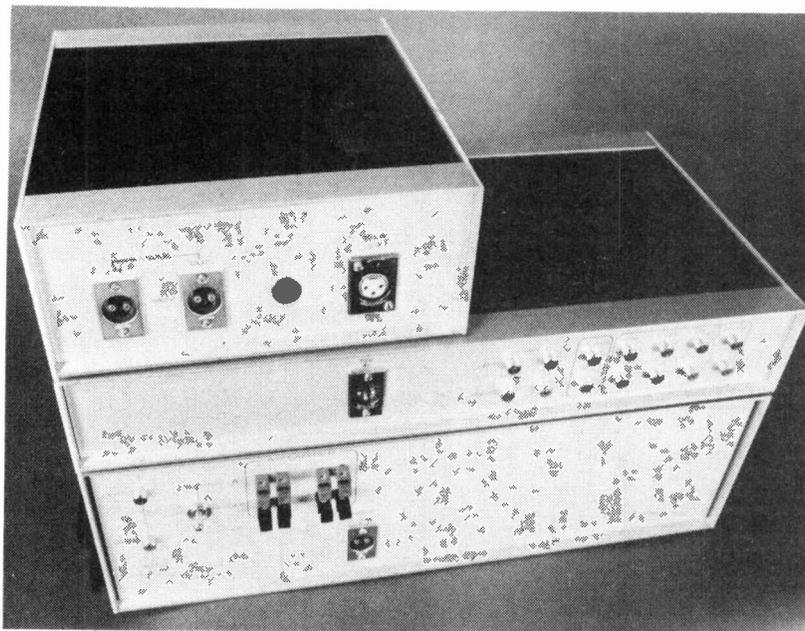If all is well, remove the two resistors and insert the fuses. Connect the speaker and away you go.



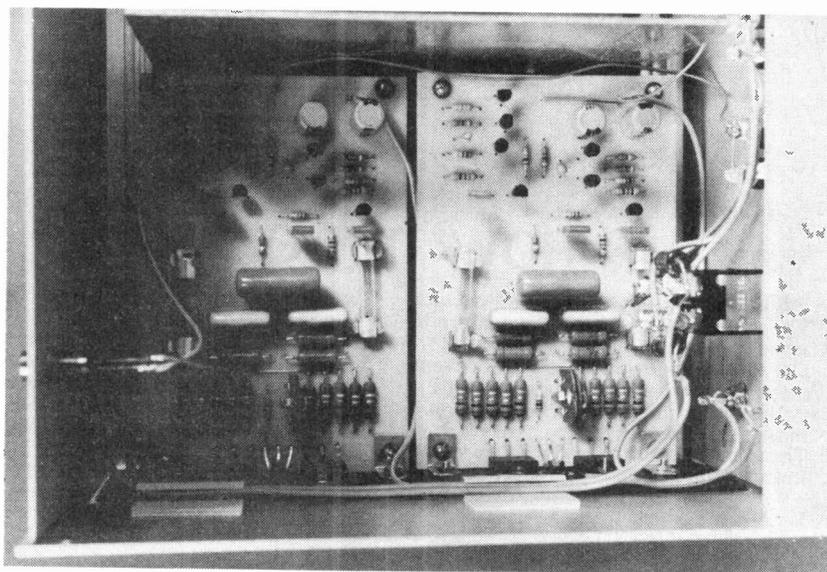Above: the rear end of the 4000 system. Note the use of Cannon connectors for power.



Right: fitting the power amps into the case. Here phono sockets have not been used, and stand-off pillars are employed to match up to the heatsinks cut into the side of the case.

## Power Supply

A completely separate PSU is used for each channel, as the performance is thus greatly improved at what amounts to a small cost increase.

Assemble both the PSUs first and test thoroughly *before* connection to the power amps. Make sure that within the common enclosure the actual amplifiers are well screened from the mains carrying circuits. See photos for guidance.

DO NOT use DIN loudspeaker plugs for the output. Screw down terminals are all we would recommend, fastened as tightly as your fingers will allow! The amplifier itself is stable into any load, and so special cable CAN be used, but quite frankly RS 20A is just as good subjectively and neither as expensive nor as awkward to drive. A better deal all around. ▶

## BUYLINES

The cases chosen for the Audiophile amplifier was obtained from West Hyde Development (see below for address) from their CLASSIC 2 range, order as CL2 CDL (preamp case), CL2 CGL (amplifier case), CL2 AES (preamp PSU case).

The following items are available from Watford Electronics:—  
TIP 142, TIP 147.

Hi-fi type switches, type TS14, TS15.

Preamp transformer 15-0-15 type 749. Amplifier module transformer 30-0-30 at 2A (also available from Electro-value, type GP602).

All other components used are readily available from major stockists that advertise in this issue.

West Hyde Development, Unit 9, Park St., Industrial Estate, Aylesbury, Bucks. HP20 1ET.



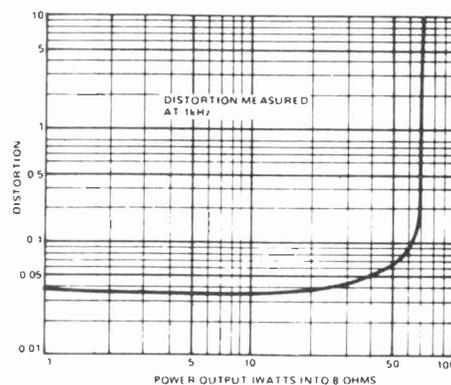


Fig 5. (Above) power output distortion for the Audiophile 4000 power amplifier.

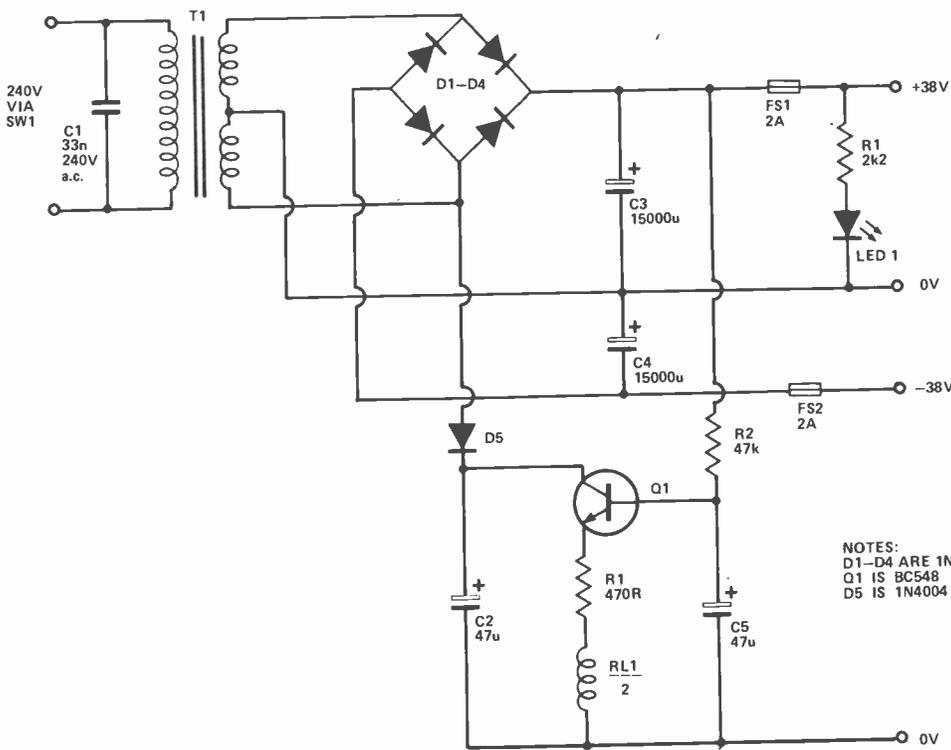

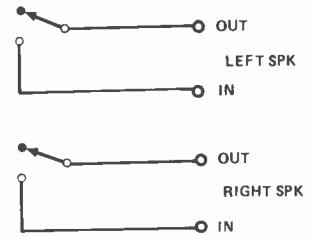Right: inside story of the pre-amp supply casing



NOTES:  
D1-D4 ARE 1N5408  
Q1 IS BC548  
D5 IS 1N4004

Fig 6 (above) circuit diagram for the power amplifier and de-thump sections of the Audiophile

## HOW IT WORKS


Both supplies are fairly standard circuits. The pre-amp PSU uses IC regulators to achieve good stabilisation. The capacitors C3, C4 on the output arc to prevent interference reaching the pre-amp rails.

The power amp PSU incorporates two massive smoothing capacitors C3, 4. These should not be reduced in value. Indeed if the case chosen — and budget —

will allow higher values will show advantages in sound output.




The transistor Q1 is part of an 'anti-thump' circuit which functions thus: as the power rails come up toward voltage, capacitor C5 charges via R2. Q1 conducts and pulls in RLA1 thereby connecting the loudspeakers.

Fig 7 (below) pre-amp power supply circuit.

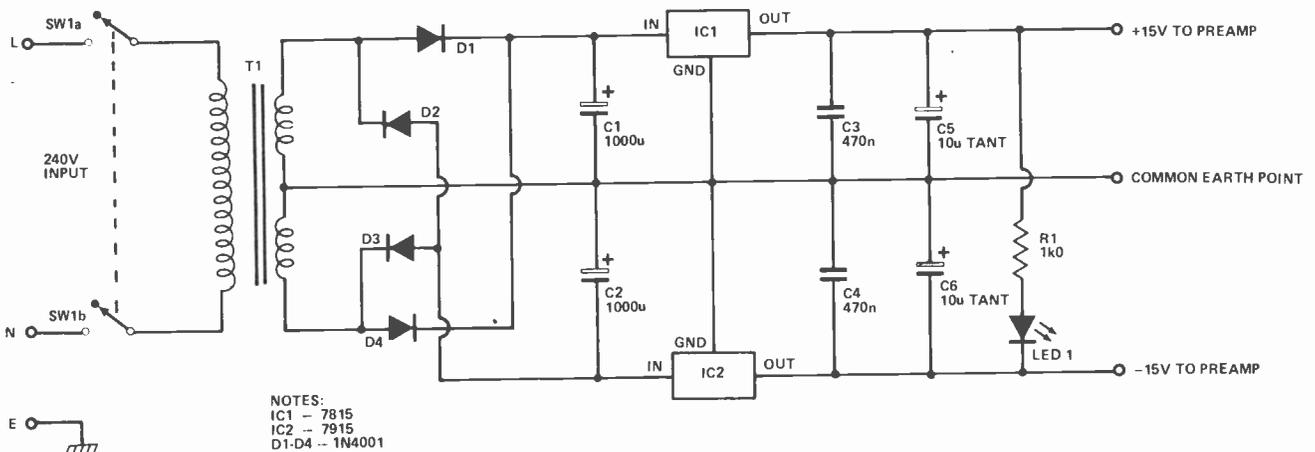


NOTES:  
IC1 - 7815  
IC2 - 7915  
D1-D4 - 1N4001

# PROJECT: Audio Amplifier

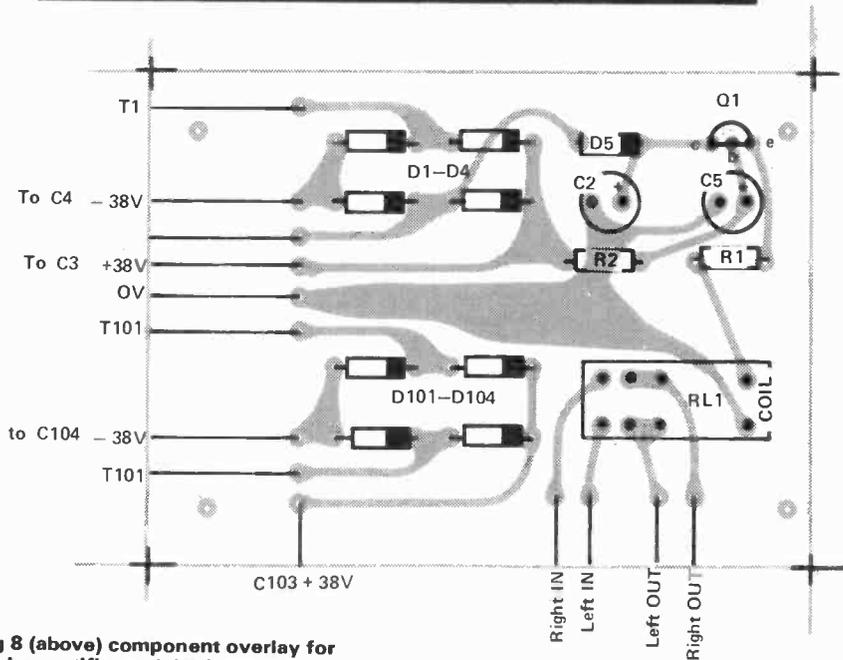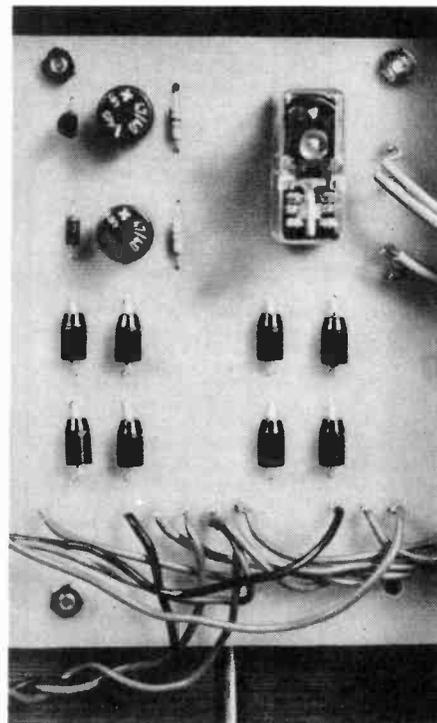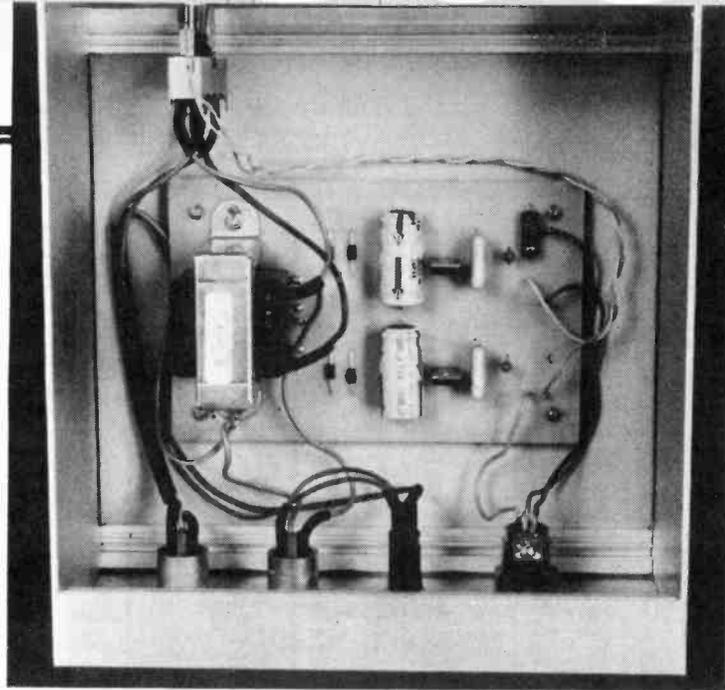

**Fig 8 (above) component overlay for bridge rectifier and de-thump circuitry. Above right: the finished article Fig 9 (below) component overlay for the pre-amp supply.**

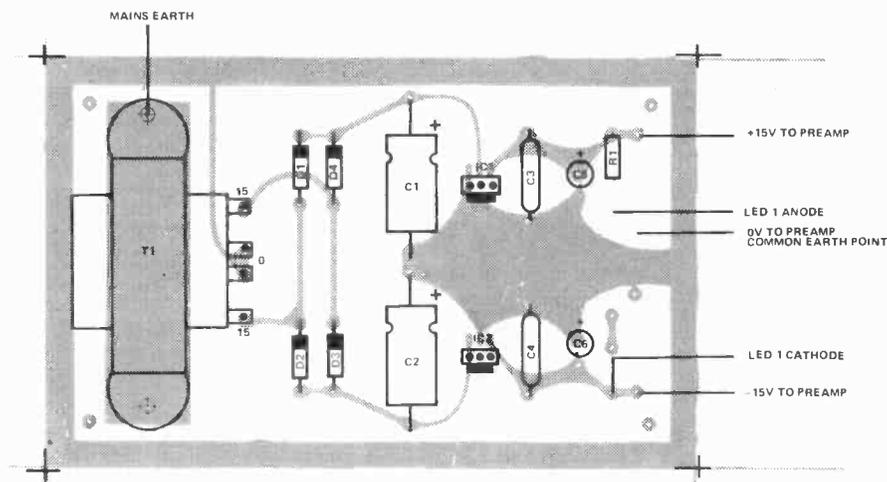

## PARTS LIST

### PRE-AMP SUPPLY

#### CAPACITORS

C1, 2	1000u 35V
C3, 4	470n polyester
C5, 6	10u 25V tantalum

#### SEMICONDUCTORS

D1-4	1N4001
IC1	7815
IC2	7915
LED	TIL220

#### MISCELLANEOUS

SW1	DPDT mains
FS1	500mA
TRI	20-0-20V secondary
PCB and hardware, case etc	
R1	1k 1/4W

### POWER AMP SUPPLY

#### CAPACITORS

C1	33n	240V AC
C2, 5	47u	63V
C3, 4	15000	63V

#### SEMICONDUCTORS

D1-4	1N5408
D5	1N4004
Q1	BC548
LED	TIL220

#### MISCELLANEOUS

R1 470R 1W, R2 47k 1/4W., T1 30-0-30 secondary, FS1 1/2 2A quick blow, RLA1 2 pole changeover 12V coil 2A contacts, R3 2K2 1W.



# electronics today

international

What to look for in the November issue: on sale October 5th

## TECH TIPS SPECIAL

Tech Tips has always been one of the most popular features of ETI. We're certainly not short of contributions. We thought it was about time we gave Tech Tips the deluxe treatment it deserves. Next month we have an 8-page Tech Tips Special — 8 pages of your ingenious suggestions for circuit designs.

## TV GAMES UNIT

Hooked on telly tennis or football? We've been carrying out some in-depth testing of (playing with) a TV games unit for you to build.

You can play pin-ball, break-out and solo target basketball. The target basketball game is particularly difficult as you not only have to stop the ball falling off the bottom of the screen, but also press a button to shoot it up towards the target at the same instant as it hits your bat.

Break-out proved to be the star of the system. You gradually knock bricks out of the wall until your ball breaks through and hits the rear wall. It bounces back at break-neck speed and — shock, horror — your bat has shrunk to half size. If you manage to clear the screen, another wall springs up.

The sneaky part is that when you reset the unit, the last score is also displayed on the screen along with your current score. So, of course you have to beat your last score — even if you have to play all night. It's addictive.



## GOT A LEAKY MICROWAVE OVEN?

You don't know, do you. If you use a microwave oven a lot, you'll naturally want to know how much radiation is leaking out to your kitchen. If you glow in the dark, you've got a good idea already.

To put your mind at rest, build our microwave oven leak detector. It couldn't be simpler.



## KEEP YOUR ROLLING STOCK UNDER CONTROL

We present the ultimate in train controllers. Need something to do on the long winter nights? Do your train set proud with the latest miracle from our design team's secret development lab. — somewhere in Charing Cross Road.

The central control unit gives you exceptionally fine speed control without the overheating problems you can expect from inferior designs. There's a built-in track cleaner to strip nasty oxides from the track and you can choose either conventional or push-button control.

OK, so now you've got the train trundling along on gleaming rails, but how do you tell it where to go? A capacitor discharge unit allows you to control up to 16 sets of points or relays.

If you prefer to put your feet up while bringing the 8.10 to a graceful halt, there's even a two-wire hand controller that lets you control four complete systems (tracks) and shows you which set of points is selected for switching.

Full details of this major model railway project will be in the November issue of ETI.




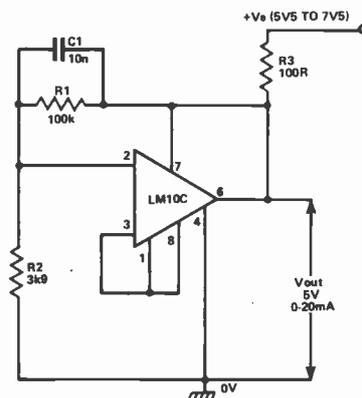
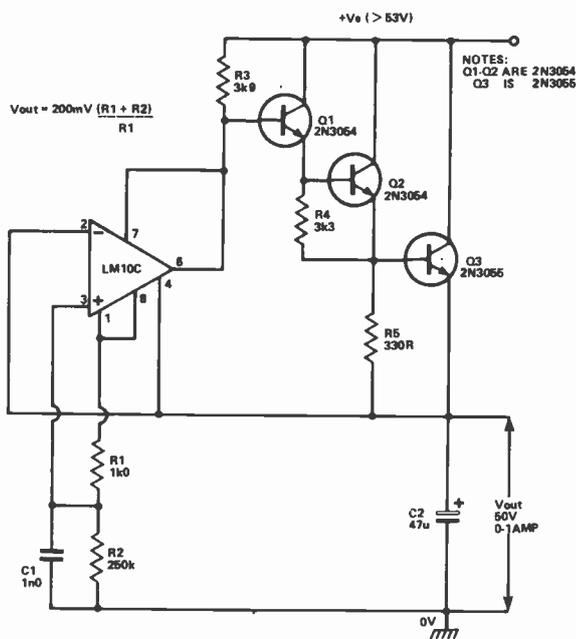
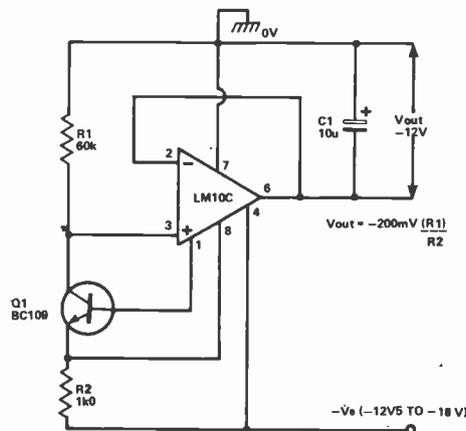


Figure 8: a simple example of the use of the LM10 as a 5 volt shunt regulator. Fig 9: how the IC can be made to act as a negative voltage regulator.

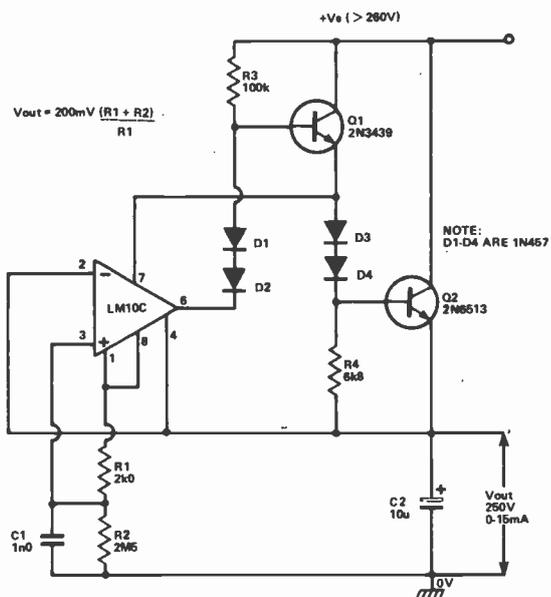Figures 6 and 7 show how the LM10 can be used in the 'floating' mode, to generate high output voltages. Note in both of these circuits that the IC is used in the 'shunt' mode, with load resistor R3, and that only a few volts are developed across the LM10 itself.



The LM10 can be used in a wide variety of voltage, current, and resistance-sensitive fault-indicator circuits with audible or visual outputs. Figures 10 to 23 show examples of circuits of this type.

In Figures 10 to 17 circuits, the op-amp is used as a simple voltage comparator, with its output feeding to either a LED indicator or an audible warning device via a suitable current-limiting resistor.

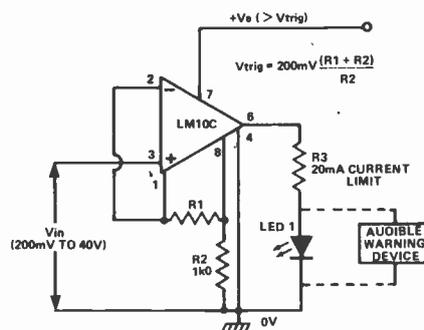


Fig 10: over-voltage indicator circuit, the test voltage is fed to the non-inverting terminal of the op-amp, and the trigger reference voltage is produced by the LM10's voltage reference and reference amplifier and is fed to the non-inverting terminal of the op-amp.

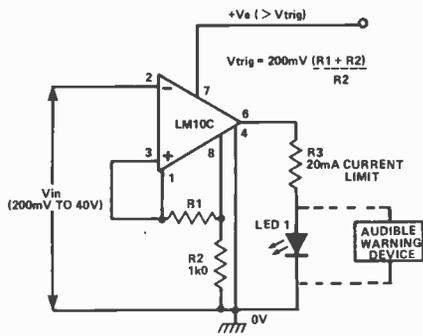


Fig 11: An alternative approach is used in the over-voltage circuit here. A 200 mV reference is fed to one input terminal of the op-amp and a potential-divided version of the test voltage is fed to the other.

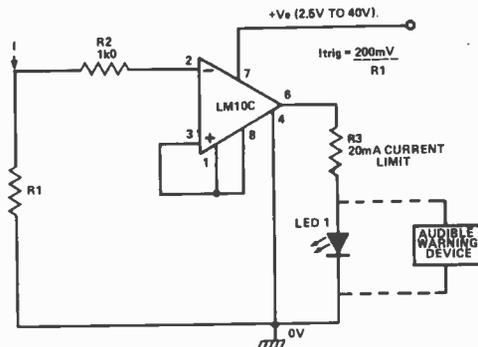


Fig 15 (above): precision under current indicator with LED or audible warning device output.

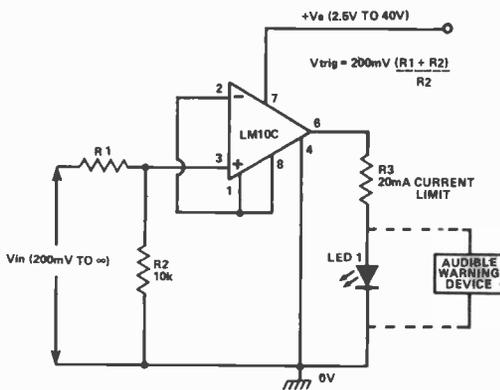


Fig 12: under-voltage circuit is similar, except that the op-amp input connections are transposed. A feature of both of these circuits is that the LM 10 supply voltage must be greater than the required trigger voltage.



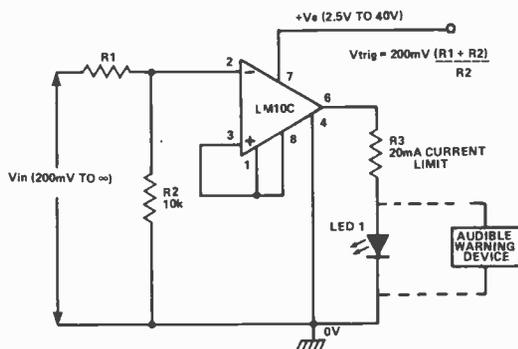
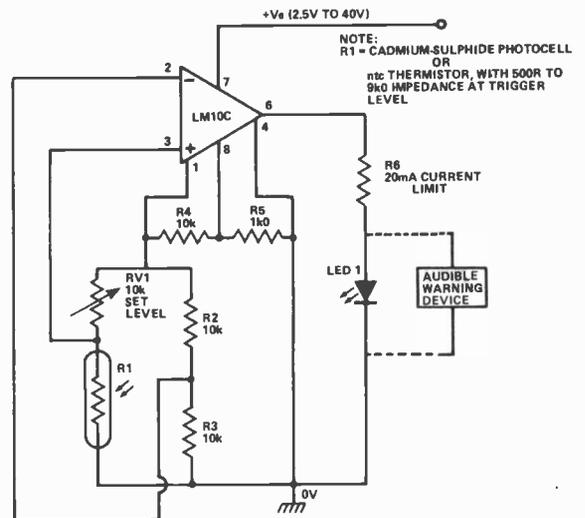


Fig 13 (above): precision under voltage indicator with LED or audible warning. Input sensitivity  $\approx 50k/v$ .  
Fig 14 (below): precision over voltage indicator with LED or audible warning.

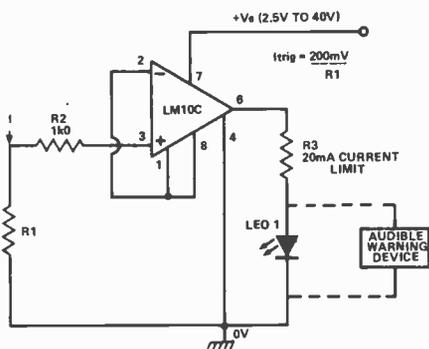

Figures 16 and 17 show precision circuits that can be triggered by any parameters, such as light or temperature levels, that can be sensed by a resistive element. In these circuits, the resistive element forms part of a Wheatstone bridge that is powered from the LM10's voltage reference amplifier, and the output of the bridge is used to activate the comparator-connected op-amp. In the examples shown, the bridge is powered from a 2V2 source.

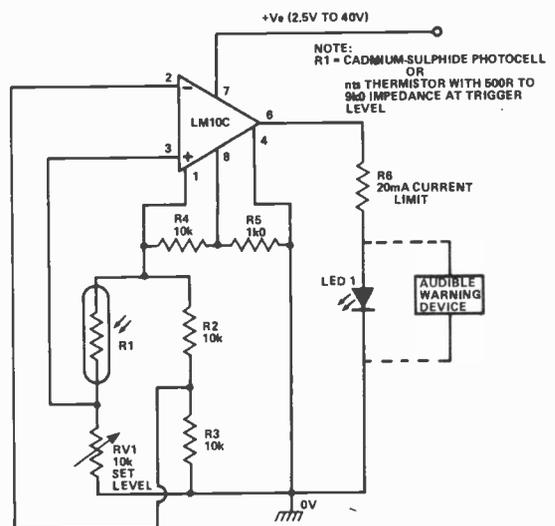

## Remote Amplifiers And 2-Wire Transmitters

One of the most interesting aspects of the LM10 is its suitability for use in remote-amplifier and 2-wire transmitter applications. The device has an output current drive capacity that is a couple of orders of magnitude greater than the device's quiescent current value, and has excellent supply-rejection characteristics. Consequently, the device can operate quite happily with its output terminal shorted to one or other of its supply terminals, in which case the supply leads can be used to carry both supply and output signal currents.

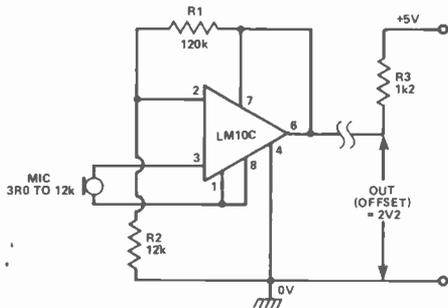


Fig 18 (above): remote 20dB voltage amplifier for use with inductive or magnetic input devices.

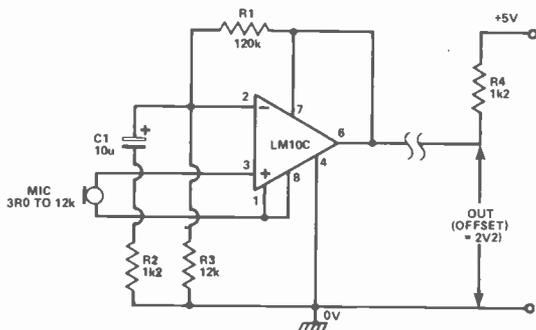


Fig 19(above): remote 40dB voltage amplifier.

Figures 18 to 21 show examples of remote linear amplifiers or 2-wire analogue transmitters. The Fig 18 and 19 circuits are suitable for use with low- to medium impedance input devices, such as moving coil or magnetic microphones, etc., and the Fig 20 circuit is suitable for use with high impedance devices such as crystal microphones or vibration sensors, etc. The Fig 21 circuit is suitable for use with resistive sensors.

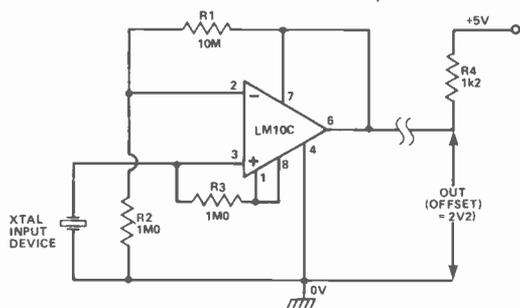


Fig 20 (above): 20dB voltage amp for use with high impedance input device.

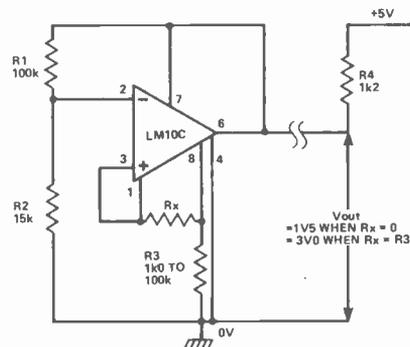


Fig 21 (above): a two-wire transmitter for use with a variable resistance sensor.

Figures 22 to 26 show the circuits of 2-level 2-wire 'fault-indicator' transmitters with either resistor, LED, or transistor outputs at their 'receiver' ends. Figures 25 to 30 show 2-wire 'fault indicator' transmitters with either flashing LED or monotone audio outputs.

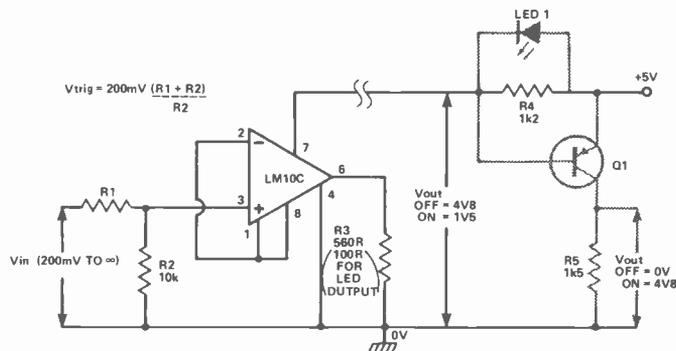


Fig 22 (above): two wire precision over-voltage transmitter with LED or resistor/transistor output.


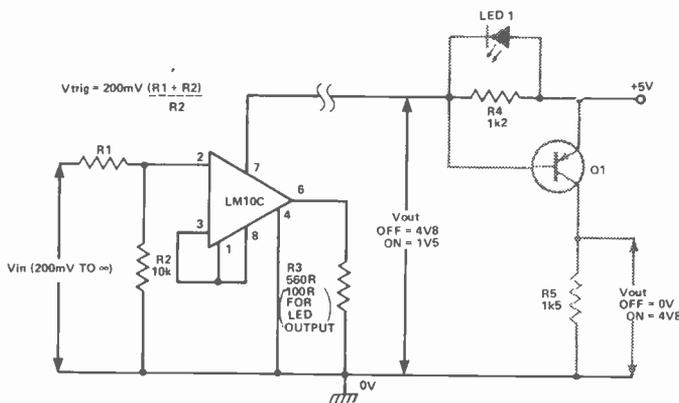


Fig 23 (above): under voltage version of Figure 22 circuit.  
Fig 24 (below): over current version of basic circuit.

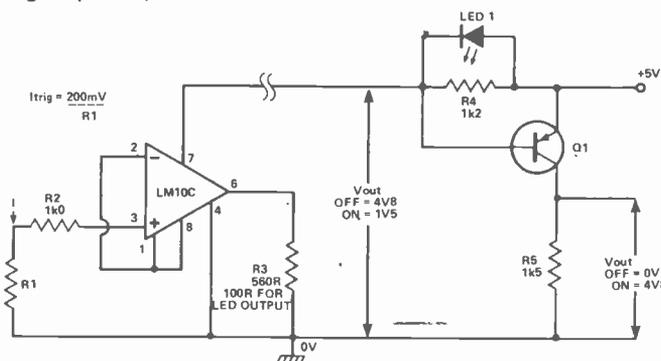

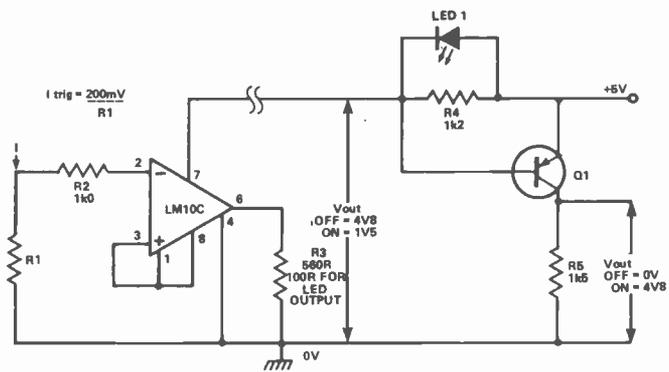


Fig 25 (above): two wire under current transmitter with LED, resistor or transistor output.

NOTE:  
R1 = CADMIUM-SULPHIDE PHOTOCELL OR  
THERMISTOR WITH 500R TO 9kΩ  
IMPEDANCE AT TRIGGER LEVEL

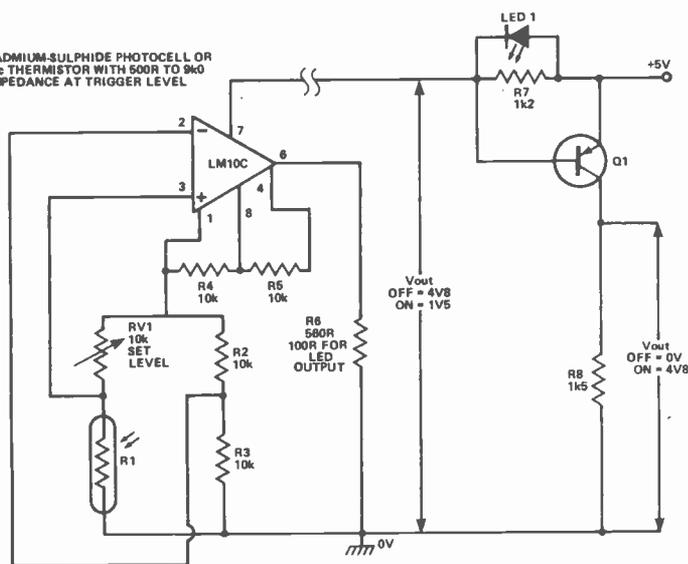


Fig 26 (above): two wire precision 'dark' or 'under-temp' transmitter with same basic outputs as previously. Transposing R1 and RV1 makes the circuit act as a 'light' or 'over-temp' alarm.

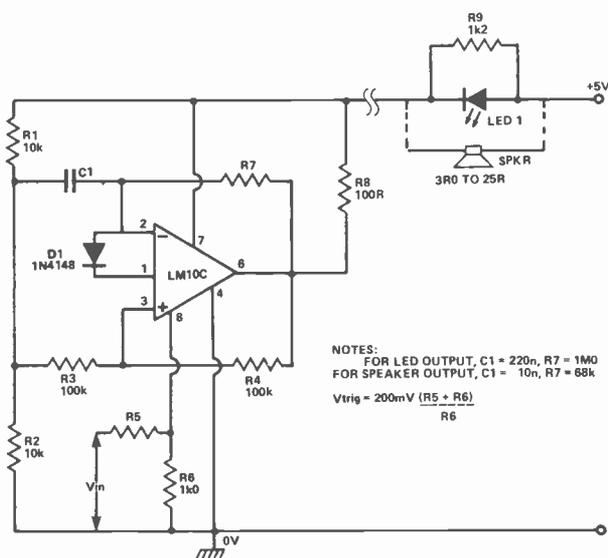


Fig 27 (above): two wire precision under-voltage transmitter with flashing LED or monotone audio output (400 HZ).

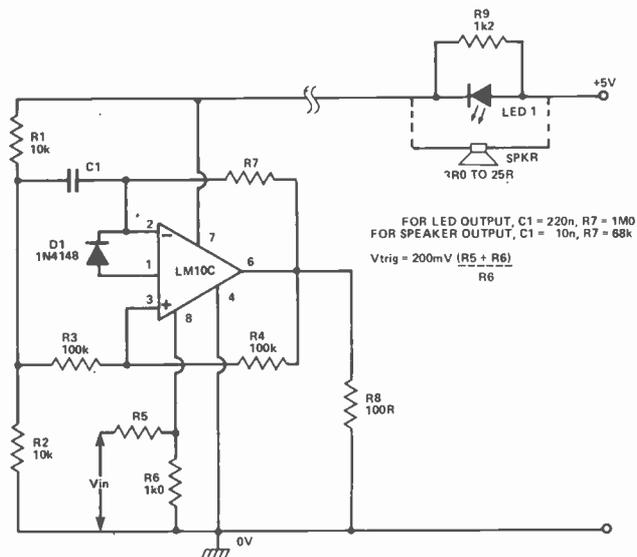


Fig 28 (above): over-voltage transmitter — output options on Fig 27.


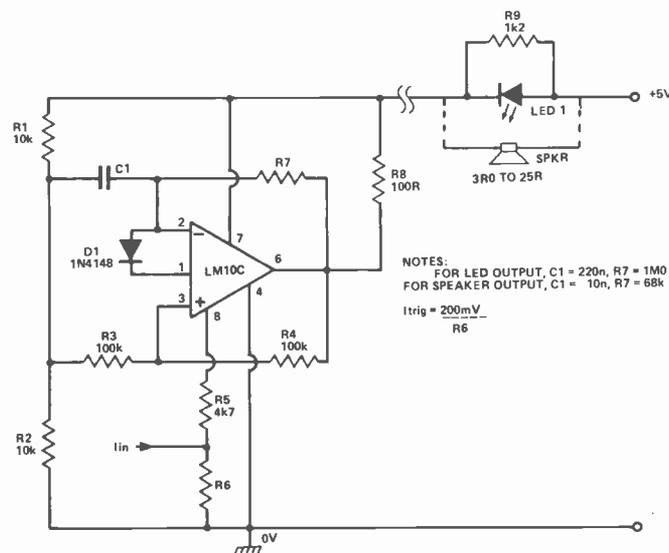


Fig 29 (above): under-current transmitter — output options as Fig 27.

Fig 30 (below): over-current transmitter — output options as Fig 27.

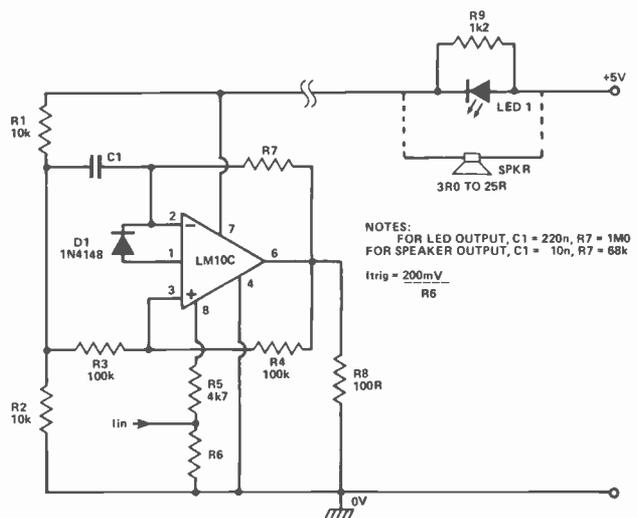

# FEATURE: The LM10 - Applications

## Meter Amplifier Circuits

To conclude this look at applications of the LM10, Figures 31 to 33 show a variety of ways of using the device as a moving-coil meter amplifier.

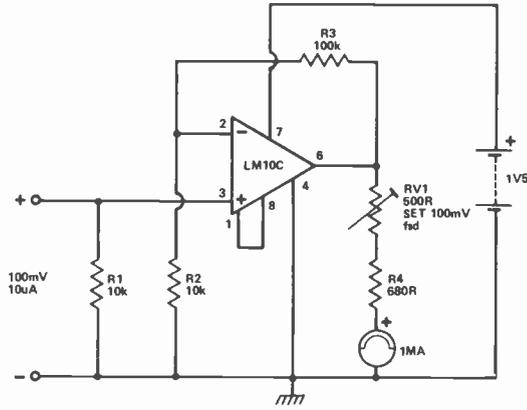


Fig 31: the op-amp is used as a simple non-inverting amplifier, and increases the meter sensitivity by a factor of about 100. This circuit has no 'set null' facility, and can give no indication of reverse-connected signals. The modified circuit of Fig 32 (below) does not suffer from this defect.


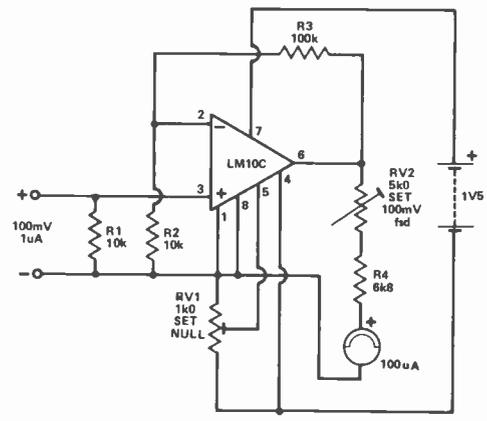


Fig 33 (below) how the basic Fig 32 circuit can be adapted for use as a four-range DC millivoltmeter. Note that these meter circuits are powered from a 1V5 cell! Not bad for an op-amp.

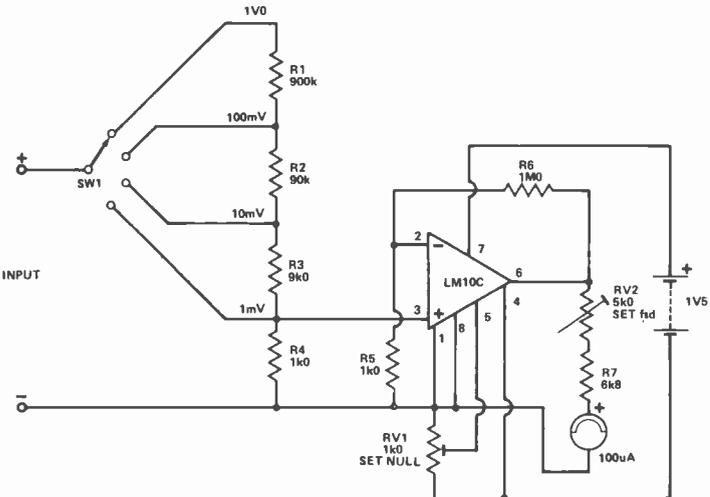

ETI

# ELECTROVALUE

Your leading direct suppliers for



**NASCOM**  
MICROCOMPUTERS  
AND FULL SUPPORTING  
RANGE OF ITEMS  
FOR WORKING TO PROPER  
PROFESSIONAL LEVELS

- ★ Widest possible range of ancillary Nascom items stocked
- ★ Information on request
- ★ Enquiries from trade, industrial and educational users invited

We are also Appointed Distributors for the fine products of:

**SIEMENS, ISKRA, RADIOHM, VERO AND MANY OTHER FAMOUS MANUFACTURERS**

It's a good deal better from



Dept. ET1 10 28 St. Jude's Road, Englefield Green, Egham, Surrey TW20 0HB  
Phone: Egham 3603. Telex 264475.  
Northern Branch (Personal shoppers only), 680 Burnage Lane, Burnage, Manchester M19 1NA. Phone (061) 432 4945.

● We pay postage  
in U.K. on orders list value £5 or over. If under, add 27p handling charge.

● We give discounts  
as follows on C.W.O. orders except items marked Net or N in our catalogues.

5% on orders list value £10 or more.

10% on orders list value £25 or more.

Not applicable to Access or Barclaycard orders

● We stabilise prices.  
by keeping to our printed price lists which appear but three or four times a year.

● We guarantee  
all products brand new, clean and to maker's spec. No seconds, no surplus.

● WE WILL SEND YOU OUR 120-PAGE CATALOGUE No. 9 FREE ON REQUEST.  
Comprehensive, informative, very well produced. Write, phone or call for your free copy, together with latest list (Available separately.)

## TRANSFORMERS

Panel Meters, Bridge Rectifiers, Power Supply Units  
Multimeters - Semi Conductors - Timers - Safeloc

Minimum & Sub Miniature				50 VOLT (Pri: 220-240V) Sec: 0-19-25-33-40-50V			
Volts	Milli-amps	Ref. No.	Price £ P&P	Amps	Ref. No.	Price £ P&P	
3-0-3	200	238	2.25 .60	0.5	102	3.25	.80
0.6, 0.6	1A 1A	212	2.65 .65	1.0	103	4.25	.95
9-0-9	100	13	1.95 .60	2.0	104	6.95	1.10
0.9, 0.9	330 330	235	1.80 .60	3.0	105	8.25	1.10
0.8-9, 0.8-9	500 500	207	2.40 .65	4.0	106	10.50	1.20
0.8-9, 0.8-9	1A 1A	208	3.50 .65	6.0	107	14.75	1.40
0-15, 0-15	200 200	236	1.80 .60	8.0	118	19.85	1.60
0-20, 0-20	300 300	214	2.40 .80	10.0	119	23.75	2.10
20-12-0-12-20	700(DC)	221	3.15 .80	60 VOLT (Pri: 220-240) Sec: 0-24-30-40-48-60			
0-15-20, 0-15-20	1A 1A	206	4.25 .95	Amps	Ref. No.	Price £ P&P	
0-15-27, 0-15-27	500 500	203	3.70 .80	0.5	124	3.50	.80
0-15-27, 0-15-27	1A 1A	204	5.75 .95	1.0	126	5.25	.95
12 AND/OR 24 VOLT Pri: 220-240 Volts				2.0	127	7.20	1.10
Amps				3.0	125	10.75	1.20
12V	24V	Ref.	Price £ P&P	4.0	123	12.00	1.40
0.5	0.25	111	1.95 .65	6.0	40	13.80	1.50
1.0	0.5	213	2.40 .80	6.0	120	17.25	1.50
2	1	71	2.90 .80	AUTO TRANSFORMERS Input/Output Tapped 0-115-210-240V			
4	2	18	3.70 .80	VA	Ref. No.	Price £ P&P	
6	3	70	5.25 .85	(Watts)	No.	Price £ P&P	
8	4	108	7.10 1.10	20	113	2.30	.80
10	5	72	7.90 1.10	75	64	3.75	.80
12	6	116	8.50 1.10	150	4	5.25	.95
16	8	17	10.50 1.20	Input/Output Tapped 0-115-210-220-240V			
20	10	115	13.50 1.40	300	53	8.85	1.10
30	15	187	16.50 1.40	500	67	10.50	1.40
60	30	226	33.00 1.70	1000	84	18.25	1.50
30 VOLT (Pri: 220-240V) Sec: 0-12-15-20-24-30V				Also 1,300/2,000/3,000VA MAINS ISOLATING (Centre Tapped & Screened) Pri: 120/240V Sec: 120/240V			
Amps	Ref. No.	Price £ P&P		VA	Ref. No.	Price £ P&P	
0.5	112	2.50 .80		(Watts)	No.	Price £ P&P	
1.0	79	3.25 .80		60	149	6.25	.95
2.0	3	5.25 .95		100	150	7.25	1.20
3.0	20	5.95 1.10		200	151	10.75	1.20
4.0	21	6.25 1.10		250	152	12.95	1.40
5.0	51	9.25 1.10		350	153	15.95	1.50
6.0	117	10.75 1.10		1000	156	36.75	3.10
8.0	88	14.00 1.40					
10.0	89	16.25 1.40					

Please add VAT at 15%  
Barclaycard and Access facilities  
available  
Trade and Education Welcome

**BAYDIS**  
7a William Street  
Herne Bay, Kent  
Herne Bay G45 8BE



# REACTION TIMER

## Check your reflexes with this ingenious project

WHILE WE HAVE published reaction timers before, the feature which makes this unit unique is that it gives a random time interval between tests. This prevents anticipation causing a shorter than actual reaction time. As the prototype was built on veroboard and used 9 TTL packages plus two of the nice (and expensive) HP displays (which have the decoder on board), we decided that at least one PCB was required.

On looking at the logic involved, we saw it could be simplified without any change in operation and with the use of CMOS the power supply is less critical than with TTL.


### Operation

If the unit has not been used for more than 30 seconds the display will be blank. Pressing the button and releasing it will initiate operation. When the display comes on again it will start counting from zero until the button is pressed. It should be held depressed while the time (in hundredths of seconds) is read. Releasing the button blanks the display for a random time before it comes on again, counting from zero for a second test. If the button is not pressed the display will blank after about 30 seconds to conserve power — no on/off switch is required.
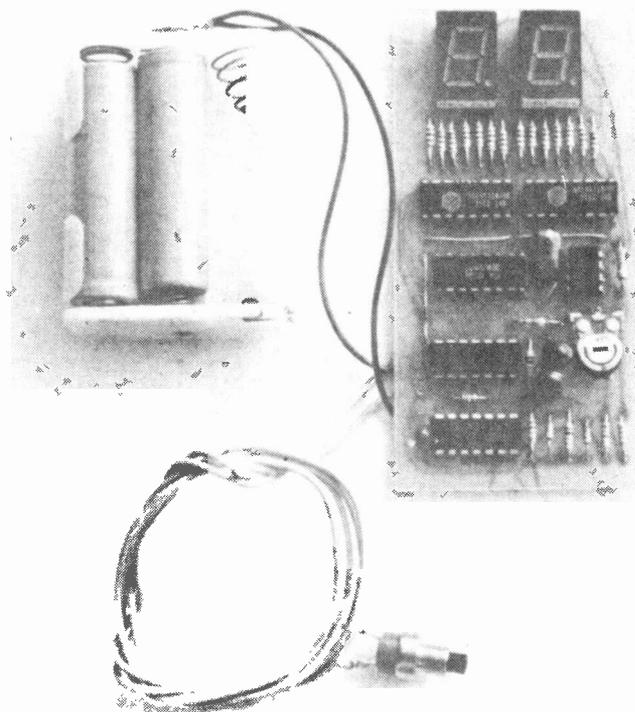
### Construction

We will describe only the electrical side of the project, leaving the housing details to individual tastes.

Assemble the PCB with the aid of the overlay in Fig. 1. Start assembly with the resistors, diodes and the four links. The 555 should now be fitted and soldered, followed by the other ICs. These are all CMOS and their pins should not be handled more than is necessary. As an added precaution, solder the power rails first (pins 7 and 14 on ICs 8 and 16) using an earthed soldering iron. The rest of the components can now be assembled. ▶



## SPECIFICATION

Reaction time  
Delay between tests  
Power requirements

0 to 0.99 seconds  
1/2 to 10 seconds (random)  
4 to 12 volts DC  
@ 50 mA (display on)  
@ 1.9 mA (display off)

## BUYLINES


Suitable displays for this project can be obtained from any of the large semiconductor suppliers advertising in this magazine. People like Technomatic, Marshalls, Maplin, etc. Most will stock all components needed.

Fig. 1. Circuit diagram.

IC5 IS 4001  
PIN 14 IS +6V  
PIN 7 IS 0V

D1-D4 ARE 1N914

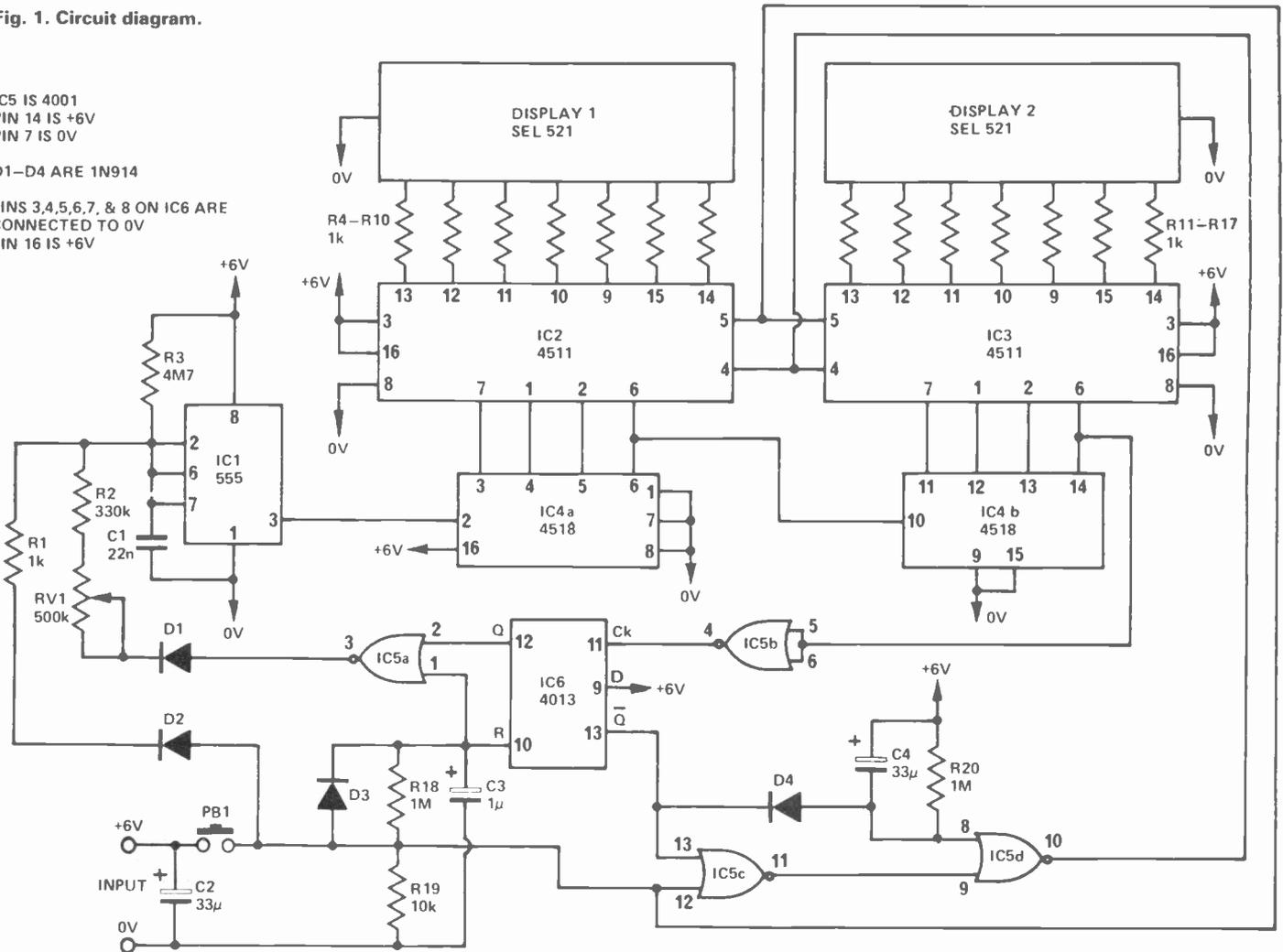PINS 3,4,5,6,7, & 8 ON IC6 ARE  
CONNECTED TO 0V  
PIN 16 IS +6V



## HOW IT WORKS

The unit is basically an oscillator, IC1, clocking two decade counters (i.e. ÷ 100), with their outputs being decoded by IC2 and IC3 and displayed on the LED displays. Control of the oscillator and displays is done by IC5 and IC6.

When the push-button is activated, IC6 is reset so that pin 13 is "0" and pin 12 is "1". Also, a "1" is applied to the latches in the decoders (IC2, 3) so that the number presented to the decoders at that instant is stored. It also applies a "1" to pin 12 of IC5c, forcing its output low. As there is a "0" on pin 13 of IC6, the diode D3 brings the voltage on pin 8 of IC5d low. Two "lows" on these gates (NOR) make the output go high. As the output of this gate controls blanking ("0" = dark), the display will be on.

The push-button also (yes, it does a lot) causes the 555 oscillator to run at about 50 kHz. The oscillator clocks the counter ICs — they are completely cycled 500 times per second.

When the button is released, the oscillator frequency drops to about 10 Hz. The display blanks as IC5c now has both zeros on its input, a "1" on its output and hence a "0" in the output of IC5d. The latches in the decoder ICs also

open, although counting cannot be seen as the display is blanked.

After about ½ sec the voltage on the reset input of IC13 (pin 10) falls below the threshold level, allowing it to be toggled by the clock input (pin 11). As when the push-button was released, the counters (IC4) could have started at any count, the time until the voltage on pin 14 of IC4 goes low is random. The delay on the reset line going low is to prevent IC6 from being toggled too soon.

When IC6 is toggled (after ½ sec to 10 sec), pin 13 goes high and pin 12 low. IC5a now has two lows on its input, giving a "1" on its output. This raises the oscillator frequency to 100 Hz. The "1" now on pin 13 of IC5c gives a "0" on pin 9 of IC5d and a "1" on pin 10. This brings the display back on. As IC6 can only be toggled on the overflow of IC4, the display comes on at the zero count.

The display continues counting up at 100 Hz until the button is pressed, freezing the display to indicate reaction time. The whole thing is then repeated.

If the button is not pressed for more than 30 sec the voltage on pin 8 of IC5d will go above the high threshold, forcing the output low and thus blanking the display.

## PARTS LIST

### RESISTORS all ¼W 5%

R1, 4-17	1k
R2	330k
R3	4M7
R18, 20	1M
R19	10k

### POTENTIOMETERS

RV1	500k trimmer
-----	--------------

### CAPACITORS

C1	22n polyester
C2, 4	33u 16V tantalum
C3	1u 16V tantalum

### SEMICONDUCTORS

IC1	555
IC2, 3	4511
IC4	4513
IC5	4001
IC6	4013
D1-3	1N914
DISP1, 2	SEL 521 or similar "jumbo" LED

### MISCELLANEOUS

PCB, box to suit, push to make pushbutton  
6V battery and holder



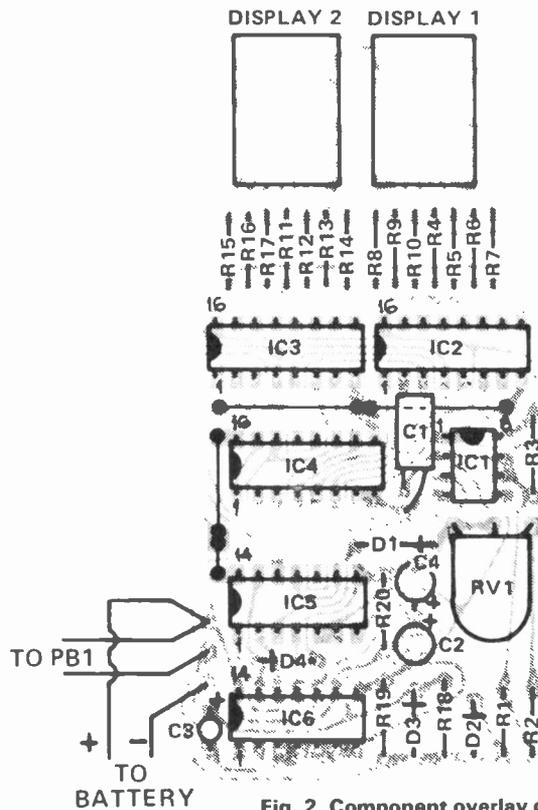
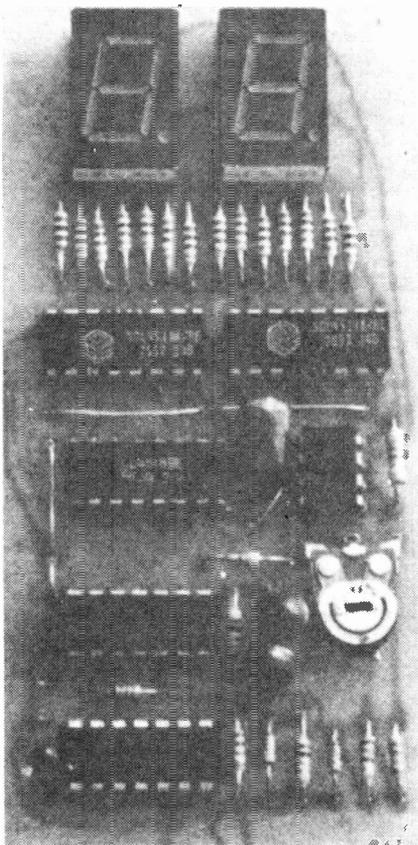


Fig. 2. Component overlay of the reaction timer.

## The professional scopes you've always needed.

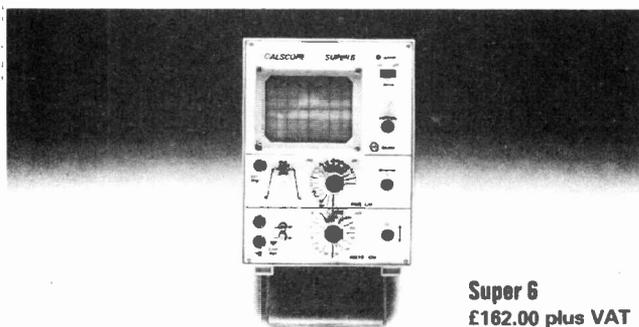

**Super 6**  
£162.00 plus VAT

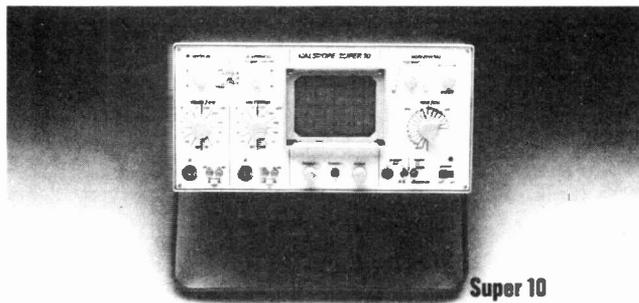

**Super 10**  
£219.00 plus VAT

When it comes to oscilloscopes, you'll have to go a long way to equal the reliability and performance of Calscope.

Calscope set new standards in their products, as you'll discover when you compare specification and price against the competition.

The Calscope Super 10, dual trace 10 MHz has probably the highest standard anywhere for a low cost general purpose oscilloscope. A 3% accuracy is obtained by the use of stabilised power supplies which cope with mains fluctuations.

The price £219 plus VAT.

The Super 6 is a portable 6MHz single beam model with easy-to-use controls and has a time base range of 1µs to 100ms/cm with 10mV sensitivity. Price £162 plus VAT.

Prices correct at time of going to Press

### CALSCOPE DISTRIBUTED BY

**Marshall's Electronic Components,**  
Kingsgate House,  
Kingsgate Place,  
London, N.W.6.

**Watford Electronics,**  
33-35 Cardiff Road,  
Watford, Herts.  
Tel: 0923 40588

**Audio Electronics,**  
301 Edgware Road, London W.2.  
Tel: 01-724 3564  
Access and Barclay card facilities  
(Personal Shoppers)

**Maplin Electronics Supplies Ltd.**  
P.O. Box 3  
Rayleigh, Essex.  
Tel: 0702 715 155  
Mail Order

# CALSCOPE

## Another Crofton First Brand New Full Specification

# 10" Metal Cased Industrial Video Monitor

**£115.00**  
Inc. to Personal Callers — Subject to availability.

Video Bandwidth 8MZ (3db down).  
Ideal for Computer Terminal or General Video Monitor.  
Complete With Own Power Supply.  
Input Sensitivity IV Composite.

The unbeatable  
**CROFTON 6800 MICRO**  
is probably the best  
value for money today

POWER SUPPLY £20 EXTRA +VAT & P/P

\* Including  
Tiny Basic and  
on board Prom  
Programmer

— KIT\* —  
**£220**

+ VAT & P/P

**CROFTON**  
**Electronics Limited**  
35 Grosvenor Road, Twickenham  
Middlesex • Tel: 01-891 1923

## CLEF KITS



Designer approved quality kits for  
**Electronic Musical Instrument  
Construction.**  
**JOANNA 72 & 88 PIANOS**  
Six and 7/4 Octave Electronic  
Pianos with unique Touch Sensitive  
Action, as used in the P.E.  
**JOANNA**, which electronically  
simulates piano key inertia — a  
feature not available in any other  
design.

## P.E. STRING ENSEMBLE

Component Kit **£164**  
Cabinet Kit **£52**

A fantastic sound at an economic price — hear it  
yourself on a demonstration cassette for £1.00.

Specialists in all sizes  
of square Front Keyboards

Send SAE to:

**CLEF PRODUCTS (Dept E.T.I.)**

16 Mayfield Road, Bramhall, Cheshire SK7 1JU.

**TEK** scope 545A with H plug-in **£125 ea.**  
**TEK** scope 545A with CA plug-in **£175 ea.**  
**H.P.** scope 175A 50MHZ Dual trace **£175 ea.**  
Single Trace **£125 ea.**  
**SOLARTRON CT316** 6MHZ Single Beam **£47.50 ea.**  
**Ex-Ministry CT52** Small. Single Beam **£37.50 ea.**  
**WAYNE KERR** Universal Bridge CT375 **£75 ea.**  
**MARCONI** Wave Analyser TF2330 **£500 ea.**  
**MARCONI** Audio Oscillator TF1101 20HZ-200KHZ **£45 ea.**  
**ADVANCE** Signal Generator J1A (CT433A) **£35 ea.**  
**MARCONI** Valve Voltmeter TF1041C **£30 ea.**  
**NOISE GENERATOR CT410** — covers audio to VHF **£8 ea.**  
**DIGITAL EQUIP. CORP.** Disk Drives (Fixed) **£160 ea.**  
**TEK** Transistor Curve Tracer **£225**  
**NAGARD** Pulse Generator 5002C **£50 ea.**  
**MARCONI** Carrier Deviation Meter TF791D **£75 ea.**  
**MARCONI** Wave Analyser type TF455E **£50 ea.**  
**SOLARTRON** DVM LM1420 with AC unit LM1477 **£40 ea.**  
**HONEYWELL** 1920 character Upper Case ASC11 VDU with edit and block mode transmission. Limited quantity. With data **£260 ea.**  
Carriage all units **£4 ea.** V.A.T. at 15%

10-Way Multi Colour Ribbon Cable **New 40p** per metre. P&P 50p.  
**STEPPING MOTORS** 6/12 position with additional where the rotor coils. Devise can be used as a tacho. Diagram supplied. Will actually work on 5 volts. 12/24 recommended **£1.50 ea.** P&P 75p  
Reduction for quantity  
**RAPID DISCHARGE** capacitors 8mld 4KV **£5 ea.** P&P £1 50  
**GEC UHF** 4-button tuner **£2.50 ea.** P&P 85p  
**BIG INCH** Motor: 110V AC 3rpm 50 cycle — very small **50p ea.** P&P 50p  
**CENTAUR** 115V FANS Brand New 4.5 x 4.5 x 1.5in **£4.50 ea.** P&P 75p  
**EX Used Equipment** — tested **60p ea.** P&P 75p  
**POTTER & BRUMFIELD** TIMER RELAY 115V AC Heavy duty 2 pole c/o with 2 second delay. Change R & C for different timing **50p ea.** P&P 25p  
**CONTACTORS** Heavy Duty 24V AC/DC 5 make. **£1 ea.** P&P 85p  
**GEC UHF/VHF** 6 button tuner. **£4.50 ea.** P&P £1  
**CAPACITORS** 500pf 6KV 20p ea. P&P 15p  
**SMITHS** encapsulated transistorised **AUDIBLE WARNING DEVICES** 4V-12V. Can be driven from TTL **35p ea.** P&P 25p  
**DIGITAL 24-HOUR** CLOCK with built-in alarm as used in BRAUN Digital clocks. Silent running. Large illuminated numerals. AC mains. Size 6 1/2 x 2 1/2 x 2 1/2. **ONLY £3.75 ea.** P&P 50p  
**931A PHOTOMULTIPLIER** in stainless steel container with window and built-in resistor network, **£2 ea.** P&P £1  
**SLIDER CONTROL** 500K Log Single track. complete with knob Length 3 1/2in **25p ea.** P&P 25p  
**RANCO** 250V 16A THERMOSTATS with Control knobs calibrated 50-200 degree F. **£2.50 ea.** P&P £1  
**SOLID STATE UHF TUNERS** 38 mcs **£1 ea.** P&P 75p  
**GROUZET / MURTEN** 4rpm synchronous motors 115V. With detachable gearbox. **30p ea.** P&P 75p  
**BRAND REX** Blue wire wrap 30 metres for £1. P&P 25p **SOLID RUBBER RINGS** (1 in dia rubber). Keep the kids (or dog) happy. 4 for **£1 ea.** P&P £1 25p  
**TRANSFORMERS**  
**AUTO** 240V Input 115V 1 Amp output **£1.25 ea.** P&P £1 25  
240V Input Sec 6V 1.66A Size 2 1/2 x 2 x 2in. Good quality **£1.50 ea.** P&P £1  
240V Input Sec 12V 0.92A. Size 2 1/2 x 2 x 2in. Good quality **£1 50 ea.** P&P £1  
240V Input Sec 12V 100MA. Size 60 x 40 x 42 mm **50p ea.** P&P 75p  
240V Input Sec 12V-12V 50 MA. Size 53 x 45 x 40mm **£1 ea.** P&P 75p  
115V Input. Secs 23V 15V 10V all at 1 1/2A Size 3 x 3 1/2 x 2 1/2 in **£1 ea.** P&P £1 or 2 for **£1.75.** P&P £1 50.

### SEMICONDUCTORS

**At 2p ea.**  
1N3063 1S44  
**At 5p ea.**  
BC147, BC148B, BC157, BC158, BC184L, BC237, BF197, OA9D, OA91, BA154, BA243, IN4303/11, 3V Zener.  
**At 25p ea.**  
TIP31, TIP41A, TIP47, 2N5296, AF139, ZTX341  
BY127-10p; BF181-20p; BD239-40p; BD241-40p; MJE3404T-40p; BD222-50p; BD233 & BD234 Comp pair 25W — **80p per pair** or **50p each.**  
Regulator TBA625 8-20V in-5V out 100MA. T05 Can. **50p ea.**  
BF256C-20p.  
FNO1D 7 segment display 0.15in **40p ea.**

### Integrated Circuits

7453	5p	74S38	10p
7451	5p	74S02	12p
7401	5p	74S00	12p
7402	12p	74154	70p
7476	20p	75325	£1
7495	35p	SN15862	4p
709	15p	9-314	8p
74H74	12p	MC4028	60p
74S04	12p	7417	14p
74H51	7p	7441	40p

**MOTOROLA** Dual in-line 6-pin Opto Coupler **30p ea.** Gold pin — faster version **50p ea.**  
AM9140 — 4K RAMS STATIC 5 volts. Ceramic. **£4 ea.**  
Telephones 706 style. Black or Grey. **£5.50 ea.** 746 style. Black or Grey **£7.50 ea.** Older style. Black. **£2.50 ea.** Postage £1 each.  
**HONEYWELL** Humidity Controllers, **50p ea.** P&P 40p  
**THYRISTOR** TIMER — solid state 15 secs adjustable (preset) in plastic relay case. Standard 7-pin base. Series delay. **50p ea.** P&P 85p  
**MINIATURE** PC MOUNT SLIDE SWITCH Single pole 3-way. **10p ea.**  
**DIGITAL** to ANALOGUE CONVERTER 8 bit — will fit standard TTL socket. With data. **£2.50 ea.** P&P 25p.  
**VARIACS** 2 Amp Standard 240 volts **£10 ea.** P&P £1 50  
**ELECTROSTATIC** VOLTMETERS 7.5KV **£6 ea.** P&P £1 Other ranges available — please enquire.

Minimum order £3 value of goods. P&P or Carriage and VAT at 15% on total must be added to all orders

**CALLERS VERY WELCOME STRICTLY BETWEEN 9am-1pm and 2-5 pm Monday to Saturday incl.**  
**BARCLAYCARD (VISA) and ACCESS taken. Official orders welcome.**

**CHILTMHEAD LTD**  
**NORWOOD ROAD, READING TEL NO. READING 669656**  
(2nd left passed Reading Tech College in Kings Road then first right — Look on right for door with spoked wheel)

# ETI BOOK SERVICE

How to order: Make cheques etc payable to ETI Book Service. Payment in sterling only please. Orders should be sent to: ETI Book Service, PO Box 79, Maidenhead, Berks. All prices include P&P.

## BEGINNERS

Beginners Guide to **Electronics** Squires £3.35  
Beginners Guide to **Transistors** Reddihough £3.35  
**Electronic Measurement Simplified** C. Hallmark £2.20  
**Electronics Self Taught** Ashe £4.40  
Beginners Guide to **Integrated Circuits** Sinclair £3.35  
**Principles of Transistor Circuits** S. Amos £5.50  
**Understanding Electronic Circuits** Sinclair £4.10  
**Understanding Electronic Components** Sinclair £4.10  
Beginners Guide to **Radio** King £3.35  
Beginners Guide to **Audio** Sinclair £3.35

## COOKBOOKS

**TV Typewriters Cookbook** £7.75  
**CMOS Cookbook** £8.20  
**Active Filters** £11.30  
**IC Timer Cookbook** £7.50  
**IC Op-Amp Cookbook** £10.00  
**Video Cookbook** £7.00  
**TTL Cookbook** £7.55  
**The Basic Cook** £4.00 inc. p/p  
**IC Converter Cookbook** £9.50

## APPLICATIONS

Advanced Applications for **Pocket Calculators** I. Gilbert £4.20  
**Fire and Theft Security Systems** B. Weis £2.00  
**How To Build Electronic Kits** Capel £2.10  
**Linear Integrated Circuit Applications** G. Clayton £5.40  
**Function Circuits Design & Applications** Burr Brown £15.95  
**110 Electronic Alarm Projects** R. M. Marston £3.95  
**110 Semiconductor Projects for the Home Constructor** R. M. Marston £3.95  
**110 Integrated Circuit Projects for the Home Constructor** R. M. Marston £3.95  
**110 Thyristor Projects Using SCRs** R. M. Marston £3.95  
**Handbook of IC Circuit Projects** Ashe £2.30  
**Practical Electronic Project Building** Ainslie and Colwell £2.60  
**110 Wave Form Generator Projects** R. M. Marston £3.95

## TV AND HI-FI

**Audio Handbook** G. King £7.50  
**Cassette Tape Recorders** J. Earl £5.25  
**Solid State Colour TV Circuits** G. R. Wilding £7.30  
**Hi-Fi Loudspeakers and Enclosures** Cohen £9.45  
**How To Build Speaker Enclosures** Badmateff £3.90  
**Master Hi-Fi Installation** King £3.45  
**Colour TV Servicing** King £8.40

## LOGIC

**Logic Design Projects Using Standard ICs** J. Wakerly £5.10  
**Practical Digital Design Using ICs** J. Greenfield £12.70  
**Designing With TTL Integrated Circuits** Texas Instruments £9.05  
**How To Use IC Circuit Logic Elements** J. Streater £3.65  
**110 COSMOS Digital IC Projects for the Home Constructor** R. M. Marston £3.95  
**Understanding CMOS Integrated Circuits** R. Melen £4.00  
**Digital Electronic Circuits and Systems** R. M. Morris £3.50  
**MOS Digital ICs** G. Flynn £5.10

## COMPUTING

**Microprocessors and Microcomputers** B. Soucek £19.00  
**Microprocessors** D. C. McGlynn £9.00  
**Introduction to Microprocessors** Aspinall £6.40  
**Beginners Guide to Microprocessors** £4.70  
**Beginners Basic** Gosling £3.35

## OP-AMPS

**Applications of Operational Amplifiers** Graeme (Burr Brown) £8.30  
**110 Operational Amplifier Projects for the Home Constructor** R. M. Marston £3.95  
**Experiments With Operational Amplifiers** Clayton £3.40  
**Designing With Operational Amplifiers** Burr Brown £16.65  
**Operational Amplifiers Design and Applications** G. Tobery (Burr Brown) £7.40  
**Op-Amp Circuit Design & Applications** J. Carr £4.00

## TEST INSTRUMENTS

**The Oscilloscope In Use** Sinclair £3.10  
**Test Instruments for Electronics** M. Clifford £2.40  
**Working with the Oscilloscope** A. Saunders £4.10  
**Servicing With the Oscilloscope** G. King £6.50  
**Radio Television and Audio Test Instruments** King £6.80

## SERVICING

**Electronic Fault Diagnosis** Sinclair £3.20  
**Rapid Servicing of Transistor Equipment** G. King £3.45  
**Tape Recorder Servicing Manual** Gardner Vol. 1: 1968-70 £9.10  
Vol. 2: 1971-74 £9.10  
**FM Radio Servicing Handbook** King £5.45

## COMMUNICATIONS

**Communication Systems Intro To Signals & Noise** B. Carlson £7.50  
**Digital Signal Processing Theory & Applications** L. R. Rabiner £23.80  
**Electronic Communication Systems** G. Kennedy £8.50  
**Frequency Synthesis. Theory & Design** Mannassewitsch £23.40  
**Principles of Communication Systems** H. Taub £8.10

## THEORY

**Introduction to Digital Filtering** Bogner £10.20  
**Transistor Circuit Design** Texas Instruments £9.35  
**Essential Formulae for Electrical and Electronic Engineers** N. M. Morris £1.65  
**Modern Electronic Maths** Clifford £6.70  
**Semiconductor Circuit Elements** T. D. Towers £7.40  
**Foundations of Wireless Electronics** M. G. Scroggie £5.00  
**Colour Television Theory** Hudson £6.20

## REFERENCE

**Transistor Tabelle (Includes physical dimensions)** £4.10  
**Electronic Engineers Reference Book (Ed. 4)** L. W. Turner £34.00  
**Solid State Circuit Guide Book** B. Ward £2.25  
**Electronic Components** M. A. Colwell £2.60  
**Electronic Diagrams** M. A. Colwell £2.60  
**Indexed Guide to Modern Electronic Circuits** Goodman £2.30  
**International Transistor Selector** T. D. Towers New update £8.70  
**International FET Selector** T. D. Towers £4.35  
**International Op-Amp Linear IC Selector** Towers £7.50  
**Popular Valve/Transistor Substitution Guide** £2.25  
**Radio Valve and Semiconductor Data** A. M. Bell £3.45  
**Master Transistor/Integrated Circuit Substitution Handbook** £6.20  
**World Radio TV Handbook 1978 (Station Directory)** £8.00  
**Radio, TV and Audio Technical Reference** Amos £24.85  
**TV Technicians Bench Manual (New Ed.)** Wilding £5.10

## MISCELLANEOUS

**Integrated Electronics** J. Milman £7.90  
**Microelectronics** Hallmark £3.90  
**Practical Solid State DC Supplies** T. D. Towers £6.20  
**Practical Triac/SCR Projects for the Experimenter** R. Fox £2.25  
**Printed Circuit Assembly** Hughes & Colwell £2.60

Fallen behind recent advances?  
 Just starting out?  
 Need a decent reference book?  
 **ETI Book Service** provides an easy  
 way of getting your hands  
 on the right title.


# audiophile.....

## Competition results, a new amplifier manufacturer and a totally new concept in loudspeaker design. Ron Harris considers . . .

MANY THANKS to all the readers who entered the Audiophile competition a while back.

Entries ranged from outright unprintable (but mostly hilarious) to outright obscure. All but displayed a wit of which Oscar Wilde would have been proud. In consequence I chose four runners-up all of whom will be receiving copies of Top Projects No 7 as some consolation.

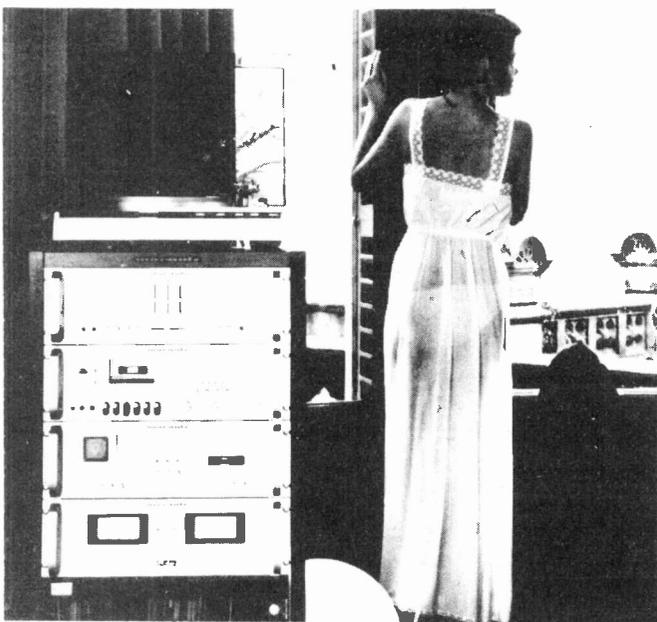The winning entries are given below, Mr Percival's triumphant ditty first:—



"Oh maid so beautiful and so fair,  
What vanity makes you look out there?  
The whistle was not from a handsome blade,  
But from your hi-fi, wrongly played!"

F. PERCIVAL  
SALE  
CHESHIRE

"I know it's wrong to doubt, but does my  
husband's fidelity match up to Marantz?"

S. IBBS  
WOLVERHAMPTON  
W. MIDLANDS

"It's transparently obvious that this unit has class — you don't  
need statistics to see there's no distortion."

P. HORSFALL  
SALE  
CHESHIRE

"Now, if I can just find a SPEAKER salesman . . ."

P. PARSONS  
BATH  
AVON

"Complete home entertainment for the discerning amateur."

S. GILLBARD  
DYLOE  
CORNWALL

Well done one and all

Now all I want is someone to offer ME a chance to enter a competition, with dinner at San Martinos with Felicity Kendal as the prize.

### Quantum Jump

Formation of new audio companies is always good to see. Quantum Electronics is a new name in the DIY amplifier market, being an off-shoot in both personnel and (developed) product from another VERY well known module manufacturer.

Quantum sell kits in the main, but will supply ready built units upon request. In kit form the amps arrive as tested PCBs network and output transistors. Couldn't be easier really. The pre-amp is of the 'Naim' species lacking tone controls and other frills.

Assembly of any of the range seems to consist of bolting in all the bits and wiring up inputs and outputs to the PCBs.



There are four amplifier variations and two pre-amps (moving coil and 'normal'). Prices range from £67.81 for the (mono) 45W P1 up to a mere £99 for the stereo 110W P4. RMS of course.

Tests will be under way soon, and Audiophile readers will hear the results very shortly I hope. Meanwhile if you're interested Quantum are existing at Stamford House, 1A Stamford Street, Leicester — from which the eagle-eyed will be able to infer which module company Quantum is sired by!

### Speaker Speaker

The following is from a letter I received from a reader named Mr H. Lipschutz. It outlines a brand new form of loudspeaker design he has pioneered (no pun — honest) and makes very interesting reading indeed.

Anyone — manufacturers for example — wishing to contact Mr Lipschutz can do so c/o Audiophile.

## Description

The low frequency output of a speaker does not depend on size of box but on size of cone area. This can be quadrupled for a given size of box by mounting drivers in the four usually unused side walls. The combined increase in efficiency due to this, and the direct coupling of low-cost power-ICs to each driver from a common electronic cross-over/12db per octave attenuator (to attenuate excess output at higher frequency), is traded off against loss due to operating woofer below resonance frequency, while medium/high frequency driver(s) are operated above resonance frequency. Thus neither is influenced by resonance effects. Cost of multiple drivers and ICs is saved on box and usual cross-over.

Result is: Small box, but output equal to unit several times its size.

There is no getting away from the fact that loudspeaker development, in terms of distortion, efficiency, and size, is well behind the rest of the hi-fi chain, even if the better speakers sound quite 'nice.' It is debatable which of the parameters needs improving most, but I decided that to reduce size without impairment of the other parameters would be a good start, especially as most buyers of hi-fi speakers would prefer the convenience of small size when given the choice, provided everything else was equal or even better than other speakers.

I therefore decided to develop such a speaker. As the problem of size is normally associated with the woofer and its box, my approach was concentrated upon that area.

To avoid cancellation of the pressure waves front and rear, bass drivers have to be enclosed in a box, the size of which is normally governed by

- a) the requirements of resonance of the system as a whole, and
- b) the cone area, which ideally should increase in line with the increase in wavelength towards the lower bass.

As below 125 Hz sound directivity is minimal, it did not matter which way the driver(s) faced; it was therefore possible to increase cone area at least fourfold without increase of box size merely by utilizing four sides of the box. The result — a considerable improvement in efficiency. The enclosure comes into its own mainly when used as a resonator, when it is intended to use resonance in order to boost output at a particular frequency, usually the lowest for which the system was designed.

This, however, required large size, which was therefore decided by the laws of physics. While it is convenient to use resonance of the systems for this particular purpose, it is not necessarily the only, or best way.

It has been stated in a number of textbooks and magazines that it is for all practical purposes impossible to force a great deal of electrical power into a speaker from an amplifier at frequencies below their main resonance, and that vastly greater distortion is produced below this resonant frequency, as well as speakers becoming very inefficient at generating sound output, so that normal designs suffer a great drop in output just where a peak is required, and distort badly as well.

This, however, is not the result of physical laws per se, but due to the limitations of the particular design. Clearly the normal bookshelf air suspension design with its 'enormous' 8-inch driver, and design resonance at approx. 75 Hz would attain maximum cone excursion at this very same frequency, caused and helped by resonance of the system. In order to move correspondingly further in and out, which it cannot do without hitting its end-stops, quite apart from the fact that in its work to compress and rarefy the enclosed air it now does not get any help from the effects of resonance.

If, however, it is designed to attain its maximum excursion at 32 Hz, regardless of whether it is helped to do so by resonance effects or not, then this is a different matter, although its movement at resonance, now being far too much, would have to be controlled. This can be done most conveniently by making the box so small that system resonance falls above the cross-over point, i.e. above, say, 125 Hz.

Accordingly a speaker with these features was built, with quadrupled cone area, utilizing four sides of the box, active cross-over before the amplifier, in order to avoid power loss in the usual passive cross-over; and the gain in acoustical efficiency traded off against the absence of the usual gain from resonance, with the cross-over frequency at 125 Hz, and a roll-off of 12 dB per octave towards the high end, in order to compensate for the increase in output due to the large cone area compared to the smaller wavelength towards 125 Hz.

The result was a speaker of similar efficiency to a transmission line speaker of 10 times its volume with the additional advantage of quadrupled voice-coils (connected in series/parallel) affording four times the heat dissipation capabilities of comparable normal designs, and therefore increased output reserve.

Furthermore, since the 'box' only consisted of not much more than a frame for the four drivers, it was extremely cheap and simple, and quite stiff as well.

Ideally each driver should be driven by its own amplifier.

In listening tests, compared to highly recommended professional monitor speakers, every listener so far has preferred the sound of the prototype, thus proving that the size reduction did not result in loss in any other parameter.

This principle has meanwhile been further developed, and patents are pending for new types of drivers, which permit an increased efficiency estimated to be more than tenfold over conventional systems, thus making possible the design of a speaker which combines small size, extended bass and very high efficiency — design parameters which until now have been considered to be mutually contradictory.

It is intended to follow this development with the construction of an advanced speaker, in which distortion and linearity is improved likewise by a factor of ten at least, thus bringing it more in line with the quality of the other links of the audio chain.

Provis. Patent applied. H. Lipschutz

ETI

## BORIS DIPLOMAT



**Travelling Chess Companion**  
£94.50 inc. VAT cw0

**BORIS DIPLOMAT** is the world's most portable personal chess companion. His compact size and battery operation make him perfect to slip into a briefcase.

The **BORIS DIPLOMAT** is the only full featured chess computer with complete Rank Display and Position Verification. He'll play at a level to teach a child, or let him loose, and he'll keep the attention of the Master.

**BORIS DIPLOMAT** is the perfect teacher and opponent. As a teacher, he'll guide you through your first game by suggesting the best moves. An exclusive Position Programmer allows you to set up problems, or remove pieces for handicapping.

**BORIS** is unlike any other game you've played. With his seemingly-human brain he can play for or against you. He knows all classic chess moves including castling and en passant, and features a built-in chess board.

Operates up to eight hours on 6AA alkaline batteries (not included). Operates on AC adaptor, included. Size: 8" x 7" x 1 1/2" (20.3cm x 17.78cm x 3.81cm).

DELUXE BORIS at £175.

### KRAMER & CO.

Dept. ET1, 9 October Place, Holders Hill Road, London NW4 1EJ. Tel. 01-203 2473. Telex: 888941. ATTN. KRAMER K7.

Mail order only. Send SAE for data sheet. Callers by appointment. Barclay & Access by arrangement.

## CALCULATORS

### CASIO SCIENTIFICS

FX80	£15.95
FX48	£13.95
FX58	£22.95
FX2500	£18.95
FX3100	£22.95
FX8000	£27.95

### LCD PROGRAMMABLES

FX501P 128 steps, 11 memories	£45.95
FX502P 256 steps, 22 memories	£62.95
FA1 ADAPTOR for prog. and data storage on cassette recorder	£19.95
TEXAS T158	£146.95
TEXAS T159	£58.95
PC100C Printer for above	£122.95

### CANON CALCULATORS

LC8M LCD Pocket	£13.95
L813 Small Desk	£25.00
P21 Print Out	£69.95
P21D Print and Display	£79.95
L1217 12-digit full feature desk	£74.95
P1014D Full feature desk print and display	£102.95

### DECIMO

BOSS Print out	£69.95
BIG BOSS Print and Display	£79.95
POCKET MEMO	£48.95

All prices inc. VAT AT 15% and postage and packing.

## CALCULATOR SALES AND SERVICE

ARROW WORKS, ARROW ROAD  
REDDITCH, WORCS. B98 8NN  
TEL. REDDITCH (0527) 43169

## Car Audio

### Manual MW/LW



Full medium and long wave tuning. Complete with speaker and mountings. Suitable for positive or negative chassis. Latest model.

**£10.25 + £1.00 Post**

### Push-Button MW/LW



One LW, four MW buttons plus manual tuning. Complete with speaker and mountings. Latest model, negative chassis only.

**£15.95 + £1.00 Post**

### Stereo FM/Cassette + MW



Standard cassettes and FM in stereo plus medium wave. Tone and balance controls. Fast forward facility on tape. Adjustable shafts. Suitable for 4 or 8 ohm speakers (not supplied). This model is discounted elsewhere at £50 up.

**£40.95 + £1.00 Post**

### Stereo Speaker Set



Suitable for above stereo unit. Good quality in surface mounted casing, 5W nominal, 8W peak.

**£4.00 (pair) + 70p Post**

### Telescopic Car Antenna

Multi-section standard type, suitable for angled mounting with locking key.

**£1.60 + 30p Post**

## Metal Detectors

### Treasure Tracer Mk III

The original Treasure Tracer. Sales exceed 7,000. 5-transistor circuit with Varicap tuning. Sensitive, stable BFO design. Built-in speaker and earphone. Fitted with Faraday shield. Kit supplied with pre-built search head.

Kit. **£18.60 + £1.00 Post**  
Built **£23.95 + £1.00 Post**

### ★ Induction Balance Model

Built with sensitivity up to 10in on single coin; fitted with speaker and meter; PP3 battery; 7in dia. search head. Telescopic stem. Excellent pin-pointing, positive reaction to non-ferrous, negative reaction to iron. This model's normal price is £39.95!

**£24.50 + £1.00 Post**

All goods guaranteed one year. 10-day money-back offer. Goods ex-stock at time of going to press. Callers by appointment only please. Send s.a.e. for illustrated leaflet.

**Minikits Electronics Ltd.**  
6E Cleveland Road  
S. Woodford  
London E18 2AN

## CALCULATORS

### SCIENTIFIC

\*SPECIAL OFFER  
TEXAS T159 together with PC100B  
(Complete as manufacturer's specifications)  
**£285.00**

TEXAS/HP Accessories available	
*TEXAS T159 (New Card prog 960 prog steps of 100 mem)	£156.50
*TEXAS T158 (New Key prog 480 steps or 60 mem)	£60.00
*TEXAS PC100B (New updated Printing Unit for T158/T159)	£140.00
*TEXAS T157 (Key Prog 8 mem. 150 Keystrokes/50 Prog Steps)	£25.00
TEXAS T133 (New — same spec. as T130, but 3 mem)	£13.95
*TEXAS T145 (New updated version of the Texas T140)	£19.95
*TEXAS 42MBA (10 Dig Fin/Stat Prog 12 mem 32 keystrokes)	£42.50
*TEXAS TI PROGRAMMER (Hexadecimal Oct)	£46.95
*TEXAS T151/iii (New 8 Dig + Exp 10 mem 32 Prog Steps, Stat/Sci)	£26.30
TEXAS T150 LCD (Sci/Stat. 2 Con Mem)	£23.00
TEXAS T125 LCD (Sci/Stats)	£18.50

### Make more of your Texas T158/59 Calculator MATH/UTILITIES MODULE

If you write your own programs this library is for you! Most programs in this library are designed to be used either on their own or as subroutines of your programs. Applications range from utility programs such as printer formatting and large-scale plotting to advanced mathematical routines.

Module includes:  
**Prompter, Alpha Messages, Printer Formatting, Superplotter, Sorting, Data Arrays, Data Packing, Prime Factors, Hyperbolic Functions, Gamma/Factorial, Random Numbers, Normal Distribution, Interpolation, Roots of a Function, Minimax, Romberg Integration, Differential Equations, Discrete Fourier Series, Calculator Status, Variable Arithmetic, Module Check.**

*TEXAS T158 with Maths/Utilities	£90.00
*TEXAS T159 with Maths/Utilities	£186.50
*TEXAS T158 with Applied Statistics	£80.00
*TEXAS T159 with PC100C & Applied Statistics	£305.00

### AUTUMN SALE

\*TEXAS T159 Calculator (complete as manufacturer's spec., master module, charger, etc.), PLUS statistics module and extra set of 40 Blank Prog Cards with wallet, etc.  
**ONLY £180**

*CBM 9190R (as 4190R but with 9 memories)	£27.50
*CBM Pro 100 (72 Step Prog)	£29.50
*HP33E (8 mem Pro Sci/Stat)	£49.00
*HP33E (Advanced Sci with Statistics)	£37.00
*HP31E (New Sci replaces HP21)	£25.00
*HP67A C Prog 224 Steps 26 Mem)	£190.00
*HP97A (Fully prog with Printer)	£389.00
CASIO AQ2000 (updated AQ1000 Cal. 3-Way Stopwatch/Alarm plus Date Calendar)	£22.00
CASIO FX3100 (LCD Sci Std/DP/Rec.)	£22.50
CASIO FX8000 (as above + Stop Watch/Alarm)	£27.73
*CASIO FX202P (127 Step Sci Progs Con Mem)	£44.50
CASIO FX501P (Sci. LCD Prog. 128 Steps, 11 Mem)	£46.00
CASIO FX501P (Sci. LCD Prog 256 Steps, 22 Mem)	£64.00
CASIO Prog Adapter — permits Progs to be recorded on to standard cassette recorders for reply on Casio FX501P/EX502P at latter stage	£20.00

**COMMODORE PET COMPUTER**  
with 8K bytes RAM 2001-8 **£550**  
PET 2001/4 **£499**  
Pet 2001/16N **£675.00**  
Fully guaranteed Warranty by CBM

### NOW IT'S YOU AGAINST 'COMPUTERS'

**BORRIS** the most advanced chess computer yet. Borris is ideal for the learning and improving your chess game from beginner to master. Borris can play against himself, has Alpha-Numeric prompting to help improve play and by simple switching you have facility to follow Borris's thinking while he analyses position before making a move. Walnut case, wooden chessmen, board mains adaptor, etc. **£135.00**  
**CHESS CHALLENGER '10'** (10 Levels of beginner to master) **£118.00**  
**CHESS CHALLENGER '7'** (7 levels of game) **£76.50**  
**'VOICE' CHESS CHALLENGER** **£200.00**

\*FREE — Mains/Charger Included \*  
**GOODS FULLY GUARANTEED. PRICES EXCLUDE VAT (ADD 15%) BUT INC. P&P CHEQUE WITH ORDER**

Company/Hospital and Government orders accepted by phone  
 Barclaycard/VISA/Access accepted by phone

**Tel. 01-455 9823**


EXPORT ORDERS WELCOMED  
 Air Freight/Air Post Delivery  
 Quotations on request. Payments via Letter or Credit/Int. Money Order/Credit Card, etc.

**MOUNTAINDENE**  
 22 Cowper St., London, EC2

# Tecknowledgemy for sale
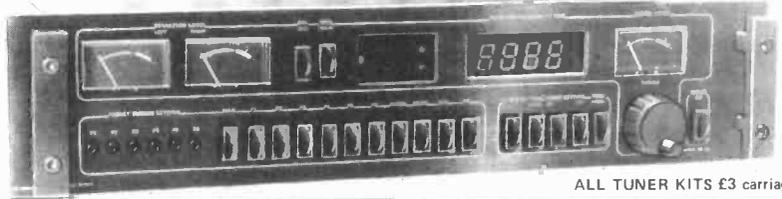
## The Mark III FM Tuner

DIY Hi-Fi will never seem the same again. Ambit's Mark III tuner system is electrically & visually superior to all others. Some options available, but the illustrated version with reference series modules: £149.00 + £18.62 VAT  
With Hyperfi Series modules £185.00 + £23.12



## Features of the system

- \* Precision construction & design of all parts
- \* Time/frequency display
- \* State of the art performance with facilities for updates, using modular plug in systems.
- \* Deviation level calibrator for recording
- \* All usual tuner features

## Digital Dorchester All Band Broadcast Tuner: LW/MW/SW/SW/FM stereo

A multiband superhet tuner, constructed using a single IC for RF/IF processing - but with all features you would expect of designs of far greater complexity. The FM section uses a three section (air gang) tuned FET tunerhead, with ceramic IF filters and interstation mute; AM employs a double balanced mixer input stage, with mechanical IF filters - plus a BFO and MOSFET product detector for CW/SSB reception. Styled in a matching unit to the Mark III FM only tuner, employing the same degree of care in mechanical design to enable easy construction. MW/LW reception via a ferrite rod antenna.  
Electronics only (PCB and all components thereon) £33.00 + £4.95 VAT  
Complete with digital frequency readout/clock-timer hardware £99.00 + £14.85 VAT  
Complete with MA1023 clock/timer module with dial scale £66.00 + £9.90 VAT  
Hardware packages are available separately if you wish to house your own designs in a professional case structure. Please deduct the cost of electronics from complete prices.

## LW/MW/FM LCD Digital Frequency Display - July PW feature

Update your old radio, or build this into a new design. Or use it as a servicing aid - this low power unit with LCD display reads direct frequency in kHz/MHz, or with usual AM/FM IF offsets for received frequency. Low power LCD means no RFI - 15-20mA at 9v even with the divide by 100 prescaler. FM resolution is 100kHz, AM 1kHz. Sensitivities better than 10mV  
Complete kit £19.50 + £2.93 VAT, built and tested module £27.00 + £4.05VAT  
Ambit stocks and distributes a wide range of frequency counter LSI for all types of DFM-part two of the catalogue contains details of the MS5523/4/5/6 range, and the versatile MSL2318 divide by ten or hundred prescaler IC. The DFM1 combined counter for AM, FM SW and direct/clock/stopwatch/timers - details available, but SAE please!



## PW SANDBANKS PI METAL LOCATOR

Maintaining our professional approach to home constructor kits, we offer the pulse induction 'Sandbanks'. Now with injection molded casing for greatly improved environmental sealing. £37.00+£5.55vat

## RADIO and AUDIO MODULES : Consistently the most advanced

- FOR FM**
- EF5801-3-4 series: 6 stage varicap tuning, all with oscillator output
    - 5801 Dual gate MOSFET RF stages, bipolar mixer £17.45 + 2.61VAT
    - 5803 Dual gate RF/mixer stages, amplified LO out £19.75 + 2.96VAT
    - 5804 'Hyperfi' series, with internal PIN diode agc, and ultra wide range tuning system £24.95 + 3.74VAT
  - EF5402 4 stage varicap tuner with TDA1062 and LO output. Uses FET/IC input. PIN agc £10.75 + 1.61VAT
- FOR 30-200MHz**
- The EF series are available on special order to cover bands (usually approx 20% of the centre frequency) in the range described. Details in our price list.
- FOR FM IFs at 10.7MHz**
- 7030 single 6 pole linear phase filter. JF with HA1137E10.95 + 1.64VAT
  - 7130 two 6 pole linear phase filter IF with CA3189E £16.25 + 2.44VAT
  - 7230 Hyperfi IF, switched bandwidth, AGC IF preamp, linear phase ceramic filters with diode switched narrow filter £24.95+3.74VAT
- DECODERS for MPX (STEREO)**
- Various types, guaranteed the world's biggest and best ranges
- LARS HOLT FM TUNERSSETS**
- 7252 MOSFET front end combined with CA3089 IF £26.50 + 3.97VAT
  - 7251 JFET front end, combined with IF and decoder £26.50 + 3.97VAT
- FM/AM tuning synthesiser, see details elsewhere in this advertisement

## COMPONENTS FOR RADIO/COMMUNICATIONS/AUDIO/TV etc.

- As usual, Ambit brings you the latest and best, a small selection of which is shown in this advertisement. The Ambit catalogues contain information on most of the devices mentioned here - and an order for the new part three will ensure you stay up with latest developments. Data photocopying service described in pricelist info.
- RADIO ICs for FM** vat SL1600 series Audio preamps vat
- CA3089E 1.94 29 SL1610 1.60 24 LM381N 1.81 27
  - CA3189E 2.45 37 SL1611 1.60 24 LM382N 1.85 25
  - HA1137W 2.20 33 SL1612 1.60 24 K84436 2.53 38
  - HA11225 2.20 33 SL1613 1.89 28 KB4438 2.22 33
  - SN76600N 0.75 11 SL1641 1.89 28 TDA1028 3.50 53
  - TDA1093 3.50 53 SL1621 2.17 33 TDA1029 3.50 53
  - TDA1090 3.35 50 SL1623 2.44 37 TDA1074 3.75 56
  - TDA1083 1.95 29 SL 624 3.28 49 Audio power
  - TDA1220 1.40 21 SL1625 2.17 33 TBAB200 0.75 11
  - IF AMPLIFIERS SL1626 2.44 37 TBAB10AS 1.09 16
  - KB4406 0.50 07 SL1630 1.62 24 LM380N 1.00 15
  - MC1350 1.20 18 SL1640 1.89 28 ULN2283 1.00 15
  - see comms ics also SL1641 1.89 28 TDA2002 1.95 29
  - COMMUNICATIONS SL6640 2.75 41 HA1370 2.89 54
  - KB4412 2.55 38 MC3357 3.12 47 TDA2020 2.99 45
  - KB4413 2.75 41 MC1496 1.25 19 FETs, MOSFETs, bipolar, and various others: see PL
  - SD6000 3.75 56 NE544 1.70 25
- 25x13/25x48 £10.00 + £1.50 pr. various high voltage drivers etc. from correctly matched Hitachi series transistors. (All 120v types)

## VHF MONITOR RX WITH PLESSEY IC 4/9

channel version of the PW design but using standard (fundx9) crystals, and TOYO 8 pole crystal filter with matching transformers. Coil sets from our standard range to cover bands from 40 to 200MHz. Complete module kit £31.25 + £3.90vat

## MICROMARKET OSTs overflow:

6800P	650p	8212	230p	1202	170p
6820P	600p	8216	195p	2112	340p
6850P	275p	8224	350p	2513	754p
8810	400p	8228	478p	4027	578p
8852	365p	8251	625p	2114	1000p
8860	630p	8255	540p	+15% VAT	

OSTs: Remember all OSTs stocks are obtained from BS9000 approved sources - your assurance that all devices are very best first quality commercial types. Some LPSN TTL is presently in great demand, so please check by phone before ordering.

## TTL Standard AND LP Schottky

N		LSN		N		LSN		N		LSN	
7400	13	20	7472	28	74142	265	74257	108	74257	108	74257
7401	13	20	7473	32	74143	312	74260	153	74260	153	74260
7402	14	20	7474	27	74144	312	74273	124	74273	124	74273
7403	14	20	7475	38	74145	65	74283	124	74283	124	74283
7404	14	24	7476	37	74147	175	74293	95	74293	95	74293
7405	18	26	7478	38	74148	109	74365	49	74365	49	74365
7406	38	48	7480	48	74150	99	74366	43	74366	43	74366
7409	17	24	7481	86	74151	64	74367	43	74367	43	74367
7410	15	24	7482	69	74153	64	74368	49	74368	49	74368
7411	20	24	7485	104	74154	96	74373	77	74373	77	74373
7412	17	24	7486	98	74155	54	74374	77	74374	77	74374
7413	30	24	7489	205	74156	80	74377	124	74377	124	74377
7414	51	7489	33	90	74157	67	74379	130	74379	130	74379
7415	24	7491	76	110	74158	60	74393	140	74393	140	74393
7416	30	7492	38	78	74159	210					
7417	30	7493	32	99	74160	82					
7420	16	24	7494	78	74161	78					
7421	29	24	7495	65	99	74162	96				
7422	27	24	7496	58	120	74163	92				
7425	27	24	7497	185	74164	104	130				
7426	27	24	7498	185	74165	105	130				
7427	27	24	7499	185	74166	105	130				
7428	35	32	74107	32	38	74169	200				
7430	17	24	74109	63	38	74170	230	200			
7432	25	24	74110	54	54	74172	230	200			
7433	25	24	74111	68	68	74173	625				
7434	40	24	74112	38	74174	87	120				
7438	32	24	74113	38	74175	67	110				
7440	17	24	74114	38	74176	75	110				
7441	74	24	74114	38	74177	78					
7442	70	99	74116	198	74181	165	350				
7443	115	74118	83	74183	210						
7444	112	74120	115	74184	135						
7445	94	74122	46	74186	134						
7446	94	74123	46	74188	275						
7447	82	89	74124	46	74190	92					
7448	56	99	74124	46	74192	105	180				
7449	99	74125	57	44	74193	105	180				
7451	17	24	74126	38	44	74194	105				
7453	17	24	74128	74	74196	99	110				
7454	17	24	74132	73	74197	110					
7455	35	24	74136	40	74198	150					
7460	17	24	74138	60	74199	160					
7463	74	124	74139	60	74247	90					
7470	28	74141	56	74253	105						

## CD4000


- Varicap tuning diodes for AM/FM/TV: 1-9 v AM tuning (Cr 15:1) from TOKO-KV1211 double matched 175p 26p vat KV1210 triple matched 245p 37p vat KV1215 triple snap-apart 245p 37p vat MVAM115 single 15p 105p 16p vat MVAM125 single 25p 105p 16p vat MVAM2 double 25v 148p 22p vat BB204/104 double FM 40p 6p vat BA102 single AFC etc 30p 4p vat BA121/ITT210 single AFC etc 30p 4p vat BB105B single UHF 40p 6p vat PIN DIODES, BANDSWITCH types BA479 PIN attenuator 35p 5v vat TDA1061P-form atten. 95p 14p vat BA182 Bandswitch 21p 3p vat All RF semiconductors stocked in depth. Please see for quantity pricing details.
- LINEARS**
- 4002 17 4522 149
  - 4001 17 4528 102
  - 4002 17 4529 141
  - 4006 109 4532 125
  - 4007 18 4538 150
  - 4008 80 4539 110
  - 4009 58 4543 174
  - 4010 58 4549 399
  - 4011 17 4554 153
  - 4012 17 4558 117
  - 4013 55 4560 218
  - 4014 95 4562 530
  - 4016 52 4566 159
  - 4017 80 4568 281
  - 4018 80 4569 303
  - 4019 60 4572 25
  - 4020 93 4584 63
  - 4021 82 4585 100
  - 4022 90
  - 4023 17
  - 4024 76 CA3130E 84
  - 4025 17 CA3130T 90
  - 4026 180 CA3140E 72
  - 4027 55 CA3140T 72
  - 4028 72 LM301A1 87
  - 4029 130 LM301AN 30
  - 4030 58 LM339N 66
  - 4035 120 LM348N 186
  - 4040 83 LM3900N 60
  - 4042 85 709HC 64
  - 4043 85 709PC 36
  - 4044 80 710HC 65
  - 4045 130 710PC 59
  - 4048 60 723CN 65
  - 4049 55 741CH 66
  - 4050 55 741CN 27
  - 4051 65 747CN 70
  - 4052 65 748CN 36
  - 4053 65 NE531N 105
  - 4055 135
  - 4059 568
  - 4060 115 HP5082 series.....
  - 4063 109 Red 7650 233p
  - 4066 53 7653 233p
  - 4068 25 Yell 7660 233p
  - 4069 20 7663 233p
  - 4070 20 Gm 7670 233p
  - 4071 20 7673 233p
  - 4072 20 Fairchild FND
  - 4073 20 500/507 150p
  - 4075 20
  - 4076 90

## MORE FROM THE GENERAL AMBIT CATALOGUES RANGES:

- MPU controllable digital frequency synthesiser PCB Preliminary:** Serial data controlled, with the standard swallow count system for maximum speed of operation. Multiple time constant filters, suitable for AM/FM and other communications/generator applications. Not for beginners. Full preliminary data package £1 + SAE. No phone enquiries answered on this system for the time being. Watch this space..... Projected cost of the controller PCB less than £30: comprises the two modulus counter, prog div., phase detector, multiple TC loop filter/integrators.
- TOP GRADE LEDs by AEG. PRICES ARE EXC. VAT (add 15%)**
- | SIZE      | Red | Green | Yellow | Orange                    | Quantity discounts for LEDs: |
|-----------|-----|-------|--------|---------------------------|------------------------------|
| 5mm 14p   | 16p | 15p   | 20p    | 10p per type - less 10%   |                              |
| 3mm 13p   | 15p | 18p   | 19p    | 10p per type - less 30%   |                              |
| 2x5x5 17p | 20p | 20p   | 24p    | 100 mix in 10s - less 25% |                              |
- FUTABA FLUORESCENT VACUUM DISPLAYS for CLOCKS etc**
- 5LT02 5 digit display (static drive) with AM/PM flags £9 + 1.35
  - 5LT03 DFM display for MS5525 LSI counter £3.45 + 1.42 vat
  - 6LT06 5 digit DFM display (GI AY58100) mpxed £9.75 + 1.42 vat
- TOKO COILS, FILTERS, CHOKES, etc for AM/FM/TV comms - TYPE Size: 5mm 7mm 10mm (please add VAT @15%)**
- AM IF 55p 33p 30p Various for ICs, transistor etc.
  - FM IF 55p 33p 33p Various for ICs, transistor etc.
  - SW coils 55p 33p 33p Two impedance series
  - OSC coils 55p 33p 33p For LW/MW/SW
  - TV vit's if 35p
- Various coils in the range 20kHz to 300MHz - see TOKO catalogue
- CERAMIC and MECHANICAL FILTERS (inc MURATA TYPES)**
- CFT455B/CF7455C 50p; CFX014 -180p; CFU4455C -85p
  - CFT470C -60p; CFU470C -65p
  - MURATA CFU455H and CFU455F ceramic block filters 1.95ea
  - MURATA CFM455 series ladder filters. D,E,F,G,H bandwidths available now (20, 16, 12, 8, 6, 4, 3.5 ea (metal encapsulated)
  - SFD455B, SFD470B, SFD472B 85p ea
  - CFM2 series mechanical elements types A,B,C,D (4-10kHz bandwidth) -65p ea. (33 used in RCME feature)
- MULTIPLEX/PILOT TONE FILTERS, FM IF FILTERS (see cat and)**
- CFSE10.7/SFE10.7 - stereo FM IF ceramic filters (5im FM4 etc) 50p
  - SFE10.7/SFE10.7M - mono bandwidth ceramic FM IF filters 50p
  - SFE10.7M/L - ultra linear phase stereo ceramic IF filters 70p
  - CDA10.7 - 10.7MHz ceramic discriminator (for CA3089 etc) 70p

Current news: A PCB for the Mullard DC tone and volume control system is now available £3 + 0.45 VAT. HMOS PA modules for 60-100W - kit £14 + £2.10VAT, heatsink £4.10+0.61. FM radio control system crystals £3.75 pair inc VAT (Sept on). MK50366N: static drive clock/timer IC £3.78 + 0.57 VAT. 12½kHz channel spacing 8 pole 10.7MHz XTAL filter by TOYO type H4402 £15.50 + £2.32VAT. A further updated pricelist is now available, and we would like to remind you that enquiries can only be answered if accompanied either by an official business letterhead, or an SAE. STOP PRESS: TOKO's new split-amp triple AM tuning diodes are in stock £2.45 + 37p VAT, (KV1215). \$ BL1 diode DBM 1.500MHz £4.25+0.64p.

Terms: CWO please. Account facilities for commercial customers OA. Postage 25p per order. Minimum credit invoice for account customers £10.00. Please follow instructions on VAT, which is usually shown as a separate amount. Overseas customers welcome - please allow for postage etc according to desired shipping method. Access facilities for credit purchases. Catalogues: Ambit. Part 1 45p. Part 2 50p 90p pair. TOKO Euro shortform 20p. Micrometals toroid cores 40p. All inc PP etc. Full data service described in pricelist supplements. Hours/phone: We are open from 9am - 7pm for phone calls. Callers from 10am to 7pm. Administrative enquiries 9am to 4.30pm please (not Saturdays). Saturday service 10am to 6pm.

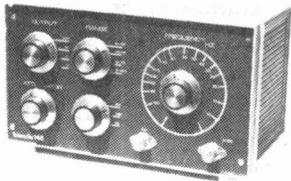

### LOW COST AUDIO SIGNAL GENERATORS

(Sine & Square Waves)  
10Hz-100KHz  
Very low distortion (-0015%)  
**£36 (or in kit form £31)**  
+ Tax 15%

Model 146

Low cost version, A0113 (02% dist), **£27.50 (Kit £23)**. Other instruments include: Millivoltmeter, Tachometer, Noise level meter, Distortion Analyser, F.M. Sig. Gen. Crystal Frequency Standard. KEF Speaker Units. Send S.A.E. for lists. VAT extra 15%. Post/Pkg. £1.50.

**TELERADIO ELECTRONICS**  
325 Fore Street, Edmonton, N.9. 01-807 3719  
Closed all day Thursday

### ETCH RESIST TRANSFER KIT SIZE 1:1

Complete kit 13 sheets 6in x 4 1/2in **£2.50** with all symbols for direct application to P.C. board. Individual sheets 25p each. (1) Mixed Symbols (2) Lines 0.05 (3) Pads (4) Fish Plates and Connectors (5) 4 Lead and 3 Lead and Pads (6) DILS (7) BENDS 90 and 130° (8) 8-10-12 T.O.5. Cans (9) Edge Connectors 0.15 (10) Edge Connectors 0.1 (11) Lines 0.02 (12) Bends 0.02 (13) Quad in Line.

### FRONT AND REAR PANEL TRANSFER SIGNS

All standard symbols and wording. Over 250 symbols, signs and words. Also available in reverse for perspex, etc.. Choice of colours, red, blue, black, or white. Size of sheet 12in x 9in. Price **£1**.

### GRAPHIC TRANSFERS WITH SPACER ACCESSORIES

Available also in reverse lettering, colours red, blue, black or white. Each sheet 12in. x 9in contains capitals, lower case and numerals 1/4in kit or 1/8in kit. **£1** complete. State size.


All orders dispatched promptly.  
All post paid

Shop and Trade enquiries welcome  
Special Transfers made to order

**E. R. NICHOLLS**  
**P.C.B. TRANSFERS**  
DEPT. ETI 10

**46 LOWFIELD ROAD**  
**STOCKPORT, CHES. 061-480 2179**

# Just a little bit more... NASCOM-2

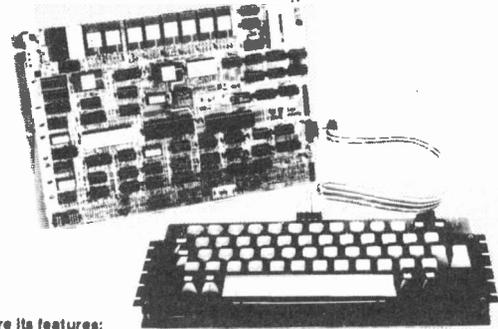

Compare its features:

- \*Z-80A 4MHZ. CPU: The most powerful 8-bit processor on the market.
- \*8K Basic: resident on board, MICROSOFT Basic, the industry standard, with extensions for on-screen editing, graphics, machine code interfacing. Optimised for speed (see benchmarks below).
- \*Full 57 Key Licon solid state keyboard: switch mechanisms are contactless, high reliability professional units for long trouble free life. Keyboard is mounted separately to avoid straining main P.C.B.
- \*Total of 20K on-board memory: 2K monitor (Nas-Sys 1), 1K Video RAM, 1K Work space RAM, 8K Microsoft Basic, 8K user RAM.
- \*Kansas City cassette interface: for reliable storage of programs and data at 300 or 1200 baud, with full checksum error detection.
- \*Nas-sys monitor: A powerful 2K machine code monitor provides an ideal environment for learning about and developing machine code programs. Nas-sys uses a blinking non destructive cursor, with 22 commands. ASCII terminals are fully supported via the serial interface; users can add their own I/O drivers via the system I/O vector table to support other devices.

Nas-sys commands are:

A—Hex arithmetic	N—return to normal
B—set breakpoint	O—Output to P.I.O.
C—Copy	Q—Query input port
E—Execute	R—Read tape
G—Generate	S—Single step
H—Operate as half duplex, terminal.	T—Tabulate memory
I—Intelligent copy	U—activate user I/O drivers
J—Execute at FFA	V—Verify tape
K—set keyboard options	W—Write tape
L—load from tape	X—set external device
M—Memory modify	Z—execute at FFD

\*On board P.I.O. — An uncommitted P.I.O. (MK 3881) giving 16 programmable I/O lines with handshake.

\*On board RS-232C Will interface directly into any standard teletype — allowing use of BASIC or Nas-sys from the teletype.

\*Full on-screen editing: a complete screen editor with cursor movement (UP, DOWN, LEFT, RIGHT), insert and delete, backspace etc.

Screen display of 16 lines x 48 characters: Stable, clear display to British television standards. Full 128 ASCII character set; option for further 128 graphics characters.

\*Fully buffered NASBUS compatible: Well defined bus structure with a range of expansion cards; including (shortly) a floppy disc system with CP/M — the industry standard operating system.

	Nett	Vat	Total
Nascom-2 .....	295.00	44.25	339.25
Power supply .....	24.50	3.68	28.18

#### PERSONAL COMPUTER WORLD BENCHMARK TESTS

	Nett	Vat	Total
Nascom-2 .....	295.00	44.25	339.25
Power supply .....	24.50	3.68	28.18
10 C15 cassettes .....	4.44	0.68	5.10
Z-80 Programming manual (Mostek) .....			4.50
Z-80 Microcomputer handbook .....			6.95
Practical microcomputer programming the Z-80 .....			20.00
Sargon-8K Z-80 Chess program (book) .....			9.50

BM 1	1.5	1.1	1.4	1.7
BM 2	3.2	5.4	6.5	9.9
BM 3	7.3	11.1	13.2	18.4
BM 4	7.2	11.6	13.9	20.4
BM 5	8.9	12.6	15.0	21.7
BM 6	18.6	19.3	22.3	32.5
BM 7	28.2	27.6	31.6	50.9
BM 8		5.2	6.2	12.3



# MICRODIGITAL

25 Brunswick Street, Liverpool L2 0BJ  
Tel: 051-236 0707 (Mail Order) 051-227 2535 (All other Depts)

ETI



### QUALITY REEL TO

### REEL & CASSETTE TAPE HEADS

SOME POPULAR UNIVERSAL CASSETTE TAPE HEADS

B12-01 MONO PLAYBACK .....	£1.89	E12-09 MONO/STEREO ERASE .....	£1.85
B12-02 MONO RECORD/PLAYBACK .....	£4.02	B22-02 TWIN HALF TRACK RECORD/PLBK .....	£5.97
B24-01 STEREO PLAYBACK .....	£3.30	C44RPS02 QUAD QUARTER TRACK REC/PLBK .....	£9.37
B24-02 STEREO RECORD/PLAYBACK .....	£6.86	C22ES02 TWIN HALF TRACK ERASE .....	£4.72
B24-RP STEREO GLASS FERRITE REC/PLBK .....	£11.80	MAGNETIC TAPE HEAD CATALOGUE 25 PENCE	
AUDIO AND HI-FI CATALOGUE 180 PAGE FULL COLOUR 15 PENCE			

**MONOLITH**  
THE MONOLITH ELECTRONICS CO. LTD.  
5/7 CHURCH ST., CREWKERNE, SOMERSET, ENGLAND. (0460) 74321

PLEASE ENCLOSE 30p P&P WITH ORDER

ALL PRICES INCLUDE VAT

# DESIGNER'S NOTEBOOK

Another look at the notebook of ETI's chief design engineer, project editor Ray Marston.

THERE ARE MANY occasions when the electronics design engineer needs one or two basic gates in a circuit and is faced with the possibility of having to wastefully commit an entire IC to this simple function. Alternatively, it may be the case that the inputs to a gate come from such widely separated points of a circuit that the use of an IC in a particular application will result in an excessively complicated PCB layout. In both of these instances, a simple diode gate may offer an ideal solution to the problem.

Figure 1 shows the practical circuit of a 3-input diode OR gate. The circuit is simple, reasonably fast, very cost-effective, and can readily be expanded to accept any number of inputs by merely adding one more diode to the circuit for each new input.

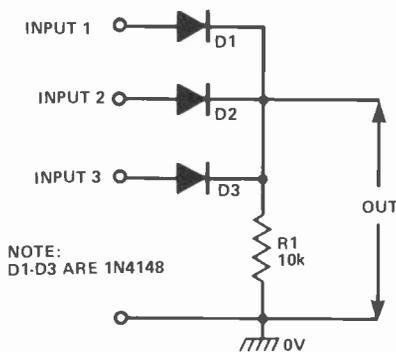


Fig. 1. The diode OR gate is simple but efficient. It can be expanded to accept any number of inputs by adding extra diodes.

The diode OR gate can be converted to a NOR type by either feeding its output through an NPN transistor inverting stage, as shown in Fig 2a, or by feeding its output through any type of IC inverting stage that happens to be 'spare' in the circuit that you are playing with, as shown in Fig 2b.

Figure 3 shows the connections for making a 3-input diode AND gate. The circuit can again be expanded to accept virtually any number of inputs by simply adding an appropriate number of diodes.

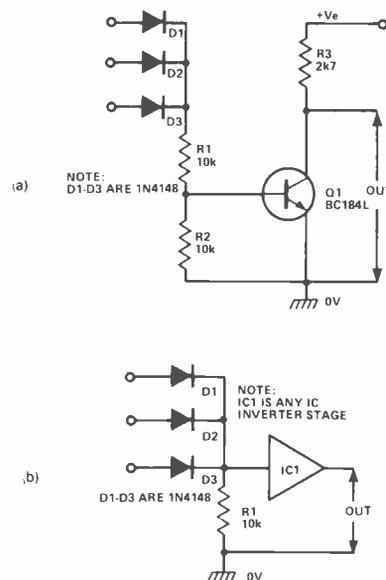


Fig. 2. The diode OR gate can be converted to a NOR type by feeding its output through a transistor (a) or IC (b) inverting stage.

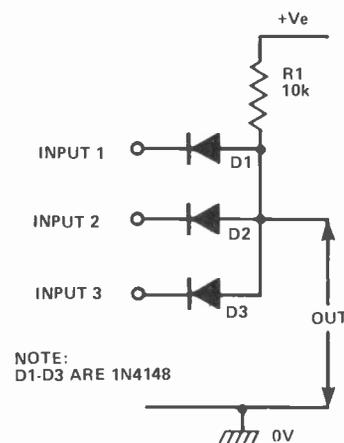


Fig. 3. The circuit of a 3-input AND gate. The number of inputs can be increased by adding extra diodes.

The AND gate can be converted to a NAND type by feeding its output through a PNP transistor or an IC inverting stage, as shown in Figures 4a and 4b respectively.

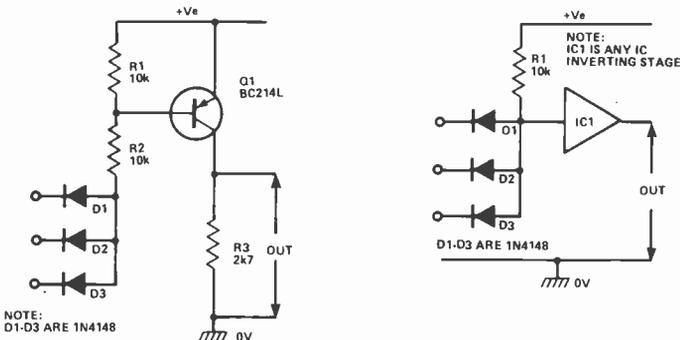


Fig. 4. The diode AND gate can be converted to a NAND type by feeding its output through a transistor (a) or IC (b) inverting stage.

### Linear Operation Of Diode Gates

Diode AND and OR gates can give very useful performances when one or more of their inputs are operated in the linear mode. Figures 5 and 6 show two useful ways of using the 2-input diode OR gate in linear applications.

In the case of the Figure 5 circuit, in which analogue voltages are applied to both of the input terminals, the output of the circuit is (ignoring a diode volt drop of about 600 mV) equal to the greater of the two input voltages.

Figure 6 shows what happens when a pulse signal is fed to one input of the OR gate and an analogue voltage is fed to the other. The output signal comprises a pulse with

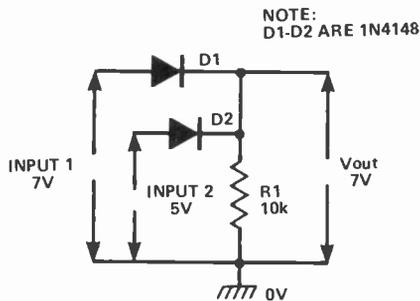


Fig. 5. When a diode OR gate is used in the linear mode,  $V_{out}$  equals the greater of the inputs.

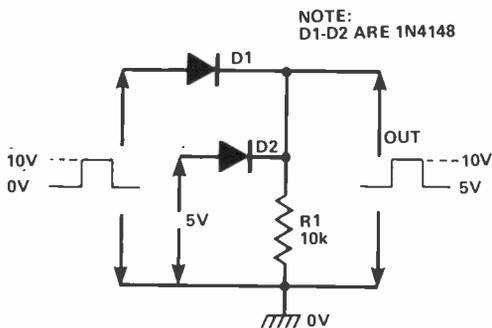


Fig. 6. The effect of feeding a pulse to one input and a DC voltage to the other input of a 2-input diode OR gate.

a peak amplitude equal to that of the input pulse, and with a 'zero' value equal to the analogue input voltage.

Figures 7 and 8 show similar circuits based on the 2-input diode AND gate. In the Fig 7 circuit, where analogue voltages are fed to both inputs, the output is (ignoring a diode volt drop 'gain' of about 600 mV) equal to the lesser of the two inputs.

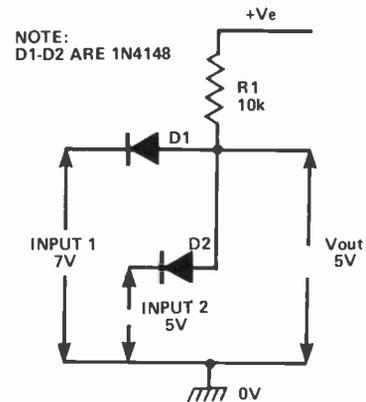


Fig. 7. When a diode AND gate is used in the linear mode,  $V_{out}$  equals the lesser of the inputs.

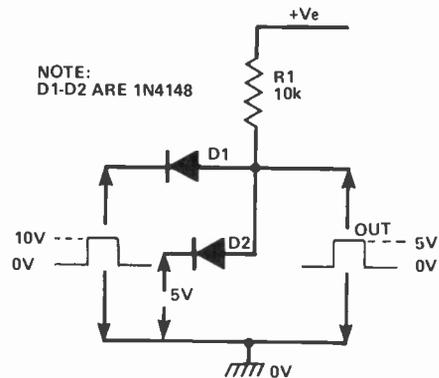



Fig. 8. The effect of feeding a pulse to one input and a DC voltage to the other input of a 2-input diode AND gate.

In the case of the Fig 8 circuit, where a pulse is fed to one input and an analogue voltage to the other, the output pulse has a peak amplitude equal to that of the analogue input voltage.


### Diode Volt Drops

We've mentioned above that the output of the 'analogue' diode gate may be 'within a diode volt drop' of the input signal. The magnitude of this 'volt drop' depends on the type of diode that is in use, on the magnitude of the diode forward current, and on the temperature of the diode junction. All silicon diodes have a negative temperature coefficient of about  $-2\text{mV}/^\circ\text{C}$ .


Figures 9 and 10 show typical volt-drop curves for the popular 1N4148 and 1N4001 silicon diodes at  $25^\circ\text{C}$ . The graph of Fig. 9 spans the current range 0.1 to 1 mA, and the graph of Fig. 10 spans the range 1 mA to 50 mA.

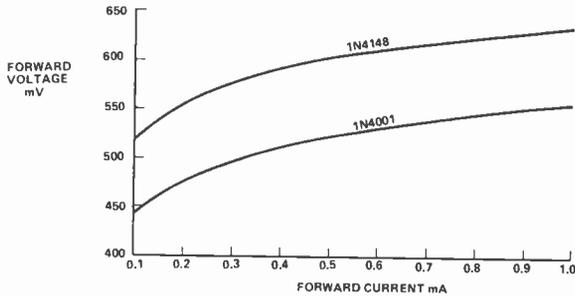

**Fig. 9.** Volt-drop curves for 1N4001 and 1N4148 diodes over the 0.1mA to 1mA current range.

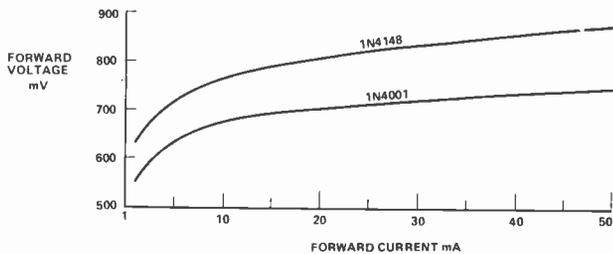

**Fig. 10.** Volt-drop curves for 1N4001 and 1N4148 diodes over the 1mA to 50mA current range.

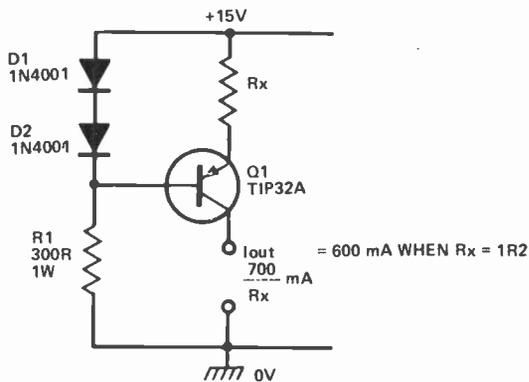

**Fig. 11.** A simple but useful constant-current generator.

Note that the 1N4148 volt drop typically ranges from 519 mV at 0.1 mA to 874 mV at 50 mA, compared to the 1N4001's range of 441 mV at 0.1 mA to 744 mV at 50 mA.

A point of particular note about the 1N4001 curve is that its volt drop of 714 mV at 25 mA increases by only a fraction over 4% (to 744 mV) when the current is doubled, to 50 mA. In other words, the diode has a voltage-to-current coefficient of about .04%/ % in this current range. The diode can thus be used as a reasonably stable voltage reference at these current levels, but has a negative temperature coefficient of about  $-0.3\%/^{\circ}\text{C}$ .

## A Constant Current Generator


Figure 11 shows how the above mentioned 'voltage reference' characteristics of the 1N4001 can be put to good use in a simple constant-current generator circuit that can be used for re-charging Ni-Cad cells or for linearly

charging large capacitors, etc. Here, two 1N4001's are wired in series and operated at a current level of roughly 50 mA. Consequently, the voltage across R<sub>x</sub> is equal to the volt drop of the two diodes minus the base-emitter volt of Q1 (about 700 mV), which gives an R<sub>x</sub> voltage of about 700 mV. The emitter (and hence collector) current of Q1 is thus approximately 700/R<sub>x</sub> mA.


To give an idea of the magnitudes of things, an R<sub>x</sub> value of 1R2 gives an output current of about 600 mA, 3R9 gives about 200 mA, and 6R8 gives about 100 mA. All in all, a simple but very useful circuit.

## Diode Protection Circuits

To wrap up this edition of 'Notebook', let's take a quick look at some diode 'protection' circuits. By 'protection' we mean circuits that are designed to insure devices against irreversible damage, and also circuits that are designed to prevent simple malfunctioning. Figures 12 to 15 show four circuits in this latter category.

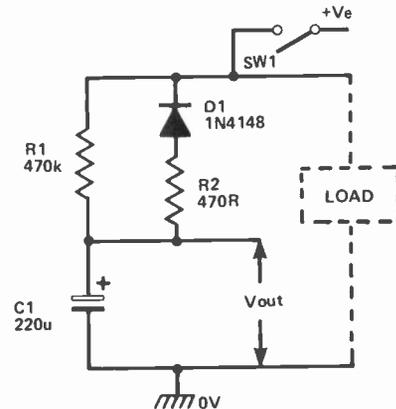

**Fig. 12.** An example of the use of a diode to rapidly discharge a timing capacitor when the power supply connection is broken.

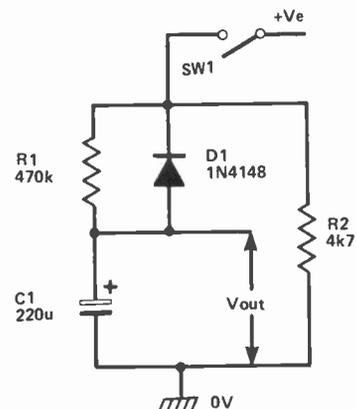

**Fig. 13.** A modification in the use of a capacitor discharge diode.

In the case of Fig 12, we have a basic time constant circuit in which a rising voltage with a time constant of about 100 seconds is developed across C1 each time

SW1 is closed. This voltage may be used to activate some additional circuitry. The problem is that once C1 has charged up, it has no means of rapidly discharging again (resetting) once SW1 is opened. If there is a load in parallel with the C-R network, as shown dotted in the diagram, C1 will of course discharge via R1 and the load, but then has a very long (greater than 100 seconds) time constant.

An easy way round this problem is to connect a discharge diode in parallel with R1, as shown in Figs 12 and 13. If there is a low-impedance load in parallel with the C-R network, a current-limiting resistor must be wired in series with the discharge diode, as shown in Fig 12. If there is no load in parallel with the C-R network, then an artificial load must be provided to complete the discharge path, as shown in Fig 13.

Figures 14 and 15 show two basic variations of the above circuits, in which the C and R networks are configured to give a falling output voltage across R1. Circuit operation should be self-evident.

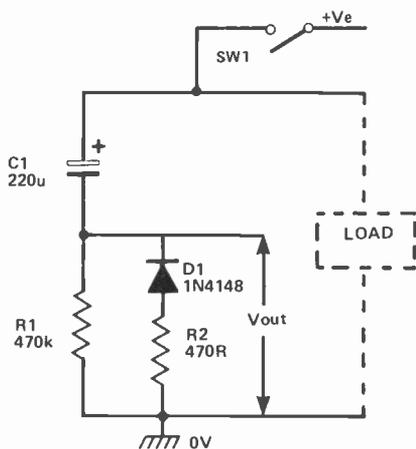


Fig. 14. A basic variant of the Fig. 12 circuit.

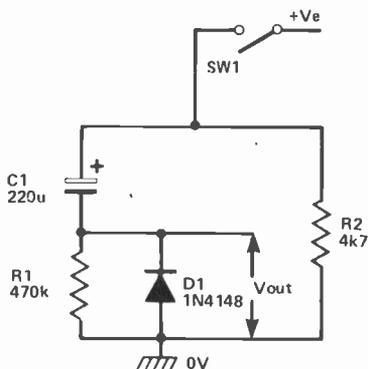


Fig. 15. A basic variant of the Fig. 13 circuit.

Finally, Figures 16 and 17 show ways of using diodes to protect two types of transistor circuit from destructive damage. Figure 16 shows how to protect a pulse-driven common-emitter amplifier that has a highly inductive collector load, such as a transformer or a relay coil. Very high back EMF's can be generated by inductive loads, and can easily be sufficient to destroy transistor junctions. In the diagram, D1 prevents the collector of Q1 from being driven above the positive supply rail value by these back EMF's and D2 prevents it from being driven below the zero-volts value.

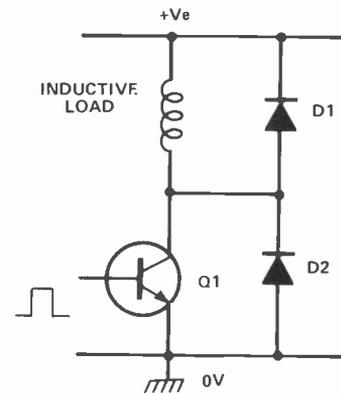


Fig. 16. An example of the use of diodes to protect a pulse-driven common emitter amplifier with an inductive collector load.

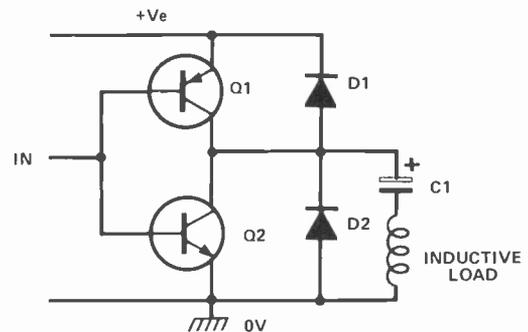


Fig. 17. An example of the use of diodes to protect the complementary emitter follower output stage of a power amplifier that is used to drive an inducting load.


Figure 17 shows how a similar type of protection can be given to the complementary emitter follower output stages of a power amplifier that is used to drive highly inductive loads. This circuit can give good protection to Hi-Fi amplifiers in which the speakers may be inadvertently plugged in at a moment when the amplifier is being hard driven. The protection diodes must have a current rating that is compatible with the inductive (speaker) load.

ETI

## 24 TUNE DOOR CHIMES
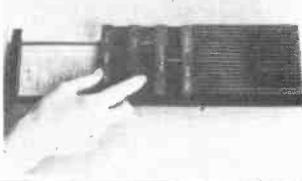
### DOOR TUNES £17.13 + VAT

Waddington's Videomaster announce a doorbell that doesn't go Brrringgg, Ding Dong or Bzzzzzz. Instead it plays 24 different classical and popular tunes. It will play the tune you select for your mood, the season or the visitor you are expecting to call. Door tunes is not only great fun and a wonderful ice breaker, but is also very functionally and beautifully designed to enhance your home. There is something for Christmas, something for your continental visitors or your relations from the states, and even something for the Queen. Door tunes is easy to install and has separate controls for volume, tone and tempo.



## T.V. GAMES

### PROGRAMMABLE £29.50 + VAT. COLOUR CARTRIDGE T.V. GAME.

The TV game can be compared to an audio cassette deck and is programmed to play a multitude of different games in COLOUR, using various plug-in cartridges. At long last a TV game is available which will keep pace with improving technology by allowing you to extend your library of games with the purchase of additional cartridges as new games are developed. Each cartridge contains up to ten different action games and the first cartridge containing ten sports games is included free with the console. Other cartridges are currently available to enable you to play such games as Grand Prix Motor Racing, Super Wipeout and Stunt Rider. Further cartridges are to be released later this year, including Tank Battle, Hunt the Sub and Target. The console comes complete with two removable joystick player controls to enable you to move in all four directions (up/down/right/left) and built into these joystick controls are ball serve and target fire buttons. Other features include several difficulty option switches, automatic on screen digital scoring and colour coding on scores and balls. Lifelike sounds are transmitted through the TV's speaker, simulating the actual game being played. Manufactured by Waddington's Videomaster and guaranteed for one year.



### EXTRA CARTRIDGES

#### ROAD RACE - £8.87 + VAT.

Grand Prix motor racing with gear changes, crash noises

#### SUPER WIPEOUT - £3.17 + VAT.

10 different games of blasting obstacles off the screen

#### STUNT RIDER - £12.16 + VAT.

Motorcycle speed trials, jumping obstacles, leaping various rows of up to 24 buses etc.

#### NON PROGRAMMABLE TV GAMES

6 Game - COLOURSCORE II - £13.50 + VAT.

10 Game COLOUR SPORTSWORLD £22.50 + VAT.

## CHESS COMPUTERS

### STAR CHESS - £56.09 + VAT.

#### PLAY CHESS AGAINST YOUR PARTNER.

Using your own TV to display the board and pieces. Star Chess is a new absorbing game for two players, which will interest and excite all ages. The unit plugs into the aerial socket of your TV set and displays the board and pieces in full colour for black and white on your TV screen. Based on the moves of chess. It adds even more excitement and interest to the game. For those who have never played, Star Chess is a novel introduction to the classic game of chess. For the experienced chess player, there are whole new dimensions of unpredictability and chance added to the strategy of the game. Not only can pieces be taken in conventional chess type moves, but each piece can also exchange rocket fire with its opponents. The unit comes complete with a free 18V mains adaptor, full instructions and twelve months guarantee.



### CHESS CHALLENGER 7- £86.65 + VAT. PLAY CHESS AGAINST THE COMPUTER.

The stylish, compact, portable console can be set to play at seven different levels of ability from beginner to expert including "Mate in two" and "Chess by mail". The computer will only make responses which obey international chess rules. Casting, on passant, and promoting a pawn are all included as part of the computer's programme. It is possible to enter any given problem from magazines or newspapers or alternatively establish your own board position and watch the computer react. The positions of all pieces can be verified by using the computer memory recall button.

Price includes unit with wood grained housing, and Staunton design chess pieces. Computer plays black or white and against itself and comes complete with a mains adaptor and 12 months guarantee.

#### OTHER CHESS COMPUTERS IN OUR RANGE INCLUDE:

**CHESS CHAMPION - 6 LEVELS £43.95 + VAT.**

**CHESS CHALLENGER - 10 LEVELS - £138.70 + VAT.**

**BORIS - MULTI-LEVEL TALKING DISPLAY £163.04 + VAT.**



### ELECTRONIC CHESS BOARD TUTOR £17.17 + VAT


A special bulk purchase of these amazing chess teaching machines enables us to offer them at only £19.75 less than half recommended retail price. The electronic chess tutor is a simple battery operated machine that can actually teach anyone to play chess and improve their game night up to championship level. This machine is not only for total beginners but also for established players wanting to play better chess. Unit contains the electronic chessboard with 32 chess pieces, a 64 page explanatory booklet and a set of 32 progressive programme cards including 6 beginners cards, 16 check mate positions, 9 miniature games, 5 openings, 3 end games, 28 chess problems and 2 master games.

## DRAUGHTS COMPUTERS

### CHECKER CHALLENGER 2 LEVELS £43.98 + VAT. 4 LEVELS £80.09 + VAT.

The draughts computer enables you to sharpen your skills, improve your game, and play whenever you want. The computer incorporates a sophisticated, reliable, decision-making microprocessor as its brain. Its high level of thinking ability enables it to respond with its best counter moves like a skilled human opponent. You can select offence or defence and change playing difficulty levels at any time. Positions can be verified by computer memory recall. Machine does not permit illegal moves and can solve set problems. Computer comes complete with instructions, mains adaptor and twelve months guarantee.
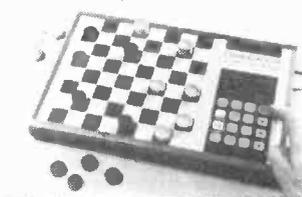
#### PLAY DRAUGHTS/CHECKERS AGAINST THE COMPUTER



## FOR FREE BROCHURES - SEND S.A.E

For FREE illustrated brochures and reviews on TV and chess games please send a stamped addressed envelope, and state which particular games you require information on

Callers welcome at our shop in Welling - demonstrations daily - open from 9am-5.30pm; Mon-Sat (9am-1pm) Wed

To order by telephone please quote your name, address and Access/Barclaycard number

Postage and Packing FREE

**AJD DIRECT SUPPLIES LIMITED, Dept. ET10, 102 Bellegrave Road, Welling, Kent DA16 3QD. Tel: 01-303 9145 (Day) 01-850 8652 (Evenings)**

# BI-PRE-PAK

## NICKEL-CADMIUM BATTERIES AT LESS THAN HALF-PRICE

BY A WORLD-FAMOUS  
MANUFACTURER  
IN 5 VALUABLE  
SIZES



BRAND NEW & GUARANTEED

Type	Capacity in mAh	Voltage	Charge Rate mA / 12 hrs	Size in mm dia. x Thickness	Our price inc. 15% VAT
NC20	200	1.24	20	24.8 x 7.4	45p
NC28	280	1.24	28	34.4 x 5.3	60p
NC50	500	1.24	50	34.3 x 9.5	80p
NC90	900	1.24	90	50.5 x 8.3	£1.20
NC175	1750	1.24	175	50.7 x 14.9	£1.75

- High capacity for very small size.
- Wide temperature operating range.
- Low internal resistance.
- Very simple charging circuit required.
- INDEFINITE SHELF LIFE.

### TO ORDER

Please send cash with order. Minimum order £3.00 plus 30p p/p in U.K. Orders over £10 oarr. paid U.K. All prices inc. V.A.T.

Ideal for portable & emergency equipment, instruments, etc.

(ETI) 222-224 West Road  
Westcliff-on-Sea, Essex  
SS0 9DF.

Telephone: 03708 5543

## BI-PRE-PAK LTD.

## AUTUMN SALE

### 24 HOUR CLOCK/ APPLIANCE TIMER KIT



Switches any appliance up to 1KW on and off at preset times once per day. Kit contains: AY-5-1230 IC, 0.5" LED display, tranc, PCBs and full instructions.  
CT1000K Basic Kit £12.00  
CT1000KB with white box (56x131x71mm) £14.00 Ready-built £19.00

### LIGHTING CONTROL KITS

Directly replace conventional light switch and control up to 300W of lighting. No mains rewiring. Insulated touchplates. Easy to follow instructions.  
TD300K TOUCHDIMMER Single touchplate with alternate action. Brief touch switches lamp on and off. longer touch dims or brightens lamp. Neon lamp helps find the switch in the dark. £6.00  
TDE/K Extension kit for TD300K for 2-way switching etc. £1.50  
TSD300K - TOUCHSWITCH & DIMMER. Single touchplate. small knob controls brightness. £4.50  
TS300K - ON/OFF TOUCHSWITCH. Two touchplates. £3.50  
TSA300K - AUTOMATIC Single touchplate. Time delay variable 2 secs. to 3 1/2 mins. £3.50  
LD300K - LIGHTDIMMER KIT £2.50

### OPTO

LEDs  
0.1" red 9p  
0.2" Red 9p  
0.2" Green 12p  
0.2" Yellow 12p

Square LED  
Red Size 5 x 2 5 x 9 mm high  
20p



DL277 0.5" 2 digit Display CA £1.00

DL34M 0.1" magnified 4 digit 7 segment display £8.50

Liquid Crystal Display 0.5" 3 1/2 digit £8.10

### BOXES

Moulded in high impact ABS. Supplied with lids and screws.  
Black or white  
PB2 95x71x35mm 65p  
PB2 115x95x37mm 70p

### ZENER DIODES RESISTORS

400mW 3.3V-30V 8p  
1.3W 7.5-30V 15p

1/4W 22ohm-10M 10p  
Pack of 10 (one value) 10p  
10 packs (mixed values) 80p

### TRIACS

400V Plastic Case (Texas)  
3A 49p 15A 165p  
8A 62p 20A 165p  
12A 70p 25A 190p  
6A with trigger 80p  
8A isolated tab 82p  
Diac 18p

### DIGITAL VOLTMETER/ THERMOMETER KIT



Based on the ICL 7106. This kit contains a PCB, resistors, presets, capacitors, diodes, IC and 0.5" liquid crystal display.

Components are also included to enable the basic DV kit to be modified to a Digital Thermometer using a single diode as the sensor. Requires a 3mA 9V Supply (PP3 battery) £17.50

### INTEGRATED CIRCUITS

555 Timer 21p  
741 Op. Amp 18p  
AY-5-1234 Clock £2.60  
AY-5-1232 Clock/Timer £3.80  
ICL7106 D.V.M £7.00  
ICM7217 Counter £7.90  
TDA1024 Zero Voltage Switch £1.20  
LM3911 Thermometer £1.00  
LM3914 Dot/bar Driver £2.60  
MM51760 (static) Timer £5.95  
5568B Touchdimmer £2.60  
59263 Touchswitch £4.85  
ZN1034E Timer £1.80  
All ICs supplied with data and circuit

ALL COMPONENTS ARE BRAND NEW AND TO MANUFACTURERS SPECIFICATION. ADD VAT AT CURRENT RATE TO ABOVE PRICES PLUS 25p P.P. MAIL ORDER - CALLERS WELCOME BY APPOINTMENT.

## TK Electronics

106 STUDLEY GRANGE ROAD  
LONDON W7 2LX. TEL: 01-579 9794

<p><b>MOTORS.</b> 1.5V Model motors 22p. Sub. min. Big pack 115vac 3 rpm motor 32p. 12vdc 5 pole motor 37p. Replacement 6 track 12vdc motor 50p. Gear motor 50p. 2 1/2 rpm. 75p. 115vac 4 rpm motor 95p. Cassette motor. 5-8vdc ex. equip. 70p.</p>	<p><b>RECORDING TAPE.</b> Low noise mylar, amplified unboxed. 7" 1200' £1.00. 7" 1800' £1.45. 10" 3000' £5.00. BLANK CASSETTES. C90 10 for £2.75. C90 10 for £3.85. TAPE HEAD DEMAGNETISER. 240vac carred probe £2.85. LOW COST 1/2" tape applicator £1.95.</p>	<p><b>AMPHENOL CONNECTORS (PL259) PLUGS</b> 47p. Sockets 42p. Elbows 90p. Reducers 13p. <b>DUMMY LOADS (PL259)</b> 52ohms 1 watt with indicator bulb 97p.</p>	<p><b>MULTIMETERS</b> big price reductions on pocket size meters. Model KRT100 1,000 ohms per volt, mirror scale, range selector switch, 1,000V AC/DC, 1000v, 150ma DC current £4.90. Model KRT101 same spec. as the KRT100 but range selection is via probe insertion. £4.10. <b>CONTINUITY TESTER.</b> Tubular unit with probe and croc. fly lead. £1.45 with batt.</p>	<p><b>TRANSFORMERS.</b> All 240vac primary (postage per transformer is shown in brackets after price). <b>MINIATURE RANGE</b> 6-0-6v 100ma, 9-0-9v 75ma, 12-0-12 50ma at 75p each (15p). 12-0-12 100ma 90p (15p). 0-6-0 200ma £1.20 (20p). 0-4-0 9v 200ma these have no fixing bracket 70p (15p). 12v 500ma 90p (22p) 12v2A £2.35 (45p) 12v4A £2.85 (45p) 15-0-15 1A £2.25 (45p). 30-0-30V 1A £2.85 (54p) 20-0-20v 2A £3.65 (54p). 0-12-12 20-24-30v 2 amp £4.75 (54p) 20v 2.5a £2.35 (54p).</p>	<p><b>ALUMINIUM PROJECT BOXES.</b> 18 S.W.S. with fitted lid and screws. AB1 30x25x10 52p. AB2 4x3x1.5in 52p. AB3 4x3x2in 65p. AB4 6x4x2in 74p. AB5 6x4x3in 92p. AB6 8x6x2in £1.05. AB7 8x6x3in £1.25.</p>
<p><b>BUZZERS.</b> Miniature solid state type. 33x17x15mm. 70db at 3 feet. 15ma drain. 4 types. 6-9-12 or 24v 80p. LOUD 12 volt buzzer 50x30mm 63p. GPO type adjustable buzzer 6-12 volts 27p. 12VDC SIREN. all metal rotary type. high pitched wail. £7.50.</p>	<p><b>TOOLS. SOLDER</b> sucker, good section. tinned nozzle. £4.99. Sine cutters 5" £1.45. Pliers 5" £1.45. <b>MEDM DRIVER</b> 8" LONG 43p. <b>MUYA</b> 16 pin IC test clip £1.85. 5 PIECE precision screwdriver sets. 10-division handles. £1.05. <b>JUMPER TEST LEAD SETS</b> 10 pairs of leads with insulated crocs each end 50p.</p>	<p><b>19-PIECE PRECISION TOOL KIT.</b> In plastic hinged case. Consists of 5 spanners. 4x2/6mm. 5 nut drivers. 30mm. 3 small screwdrivers. 2 Phillips drivers. 1 wvl. 3 Allen Keys. £3.35.</p>	<p><b>MICRO SWITCHES.</b> Standard button operated 28x25x6mm make or break new 15p each. roller operated version of the latter but ex equip. 15p. Light action micro switch. 3 amp make or break 35x20x7mm 12p each. Cherry plunger operated micro switch. 2 amp. open and 2 amp. closed. plunger 20mm long (40x30x10mm) 25p each.</p>	<p><b>TRIC XENON PULSE TRANSFORMERS.</b> H (GPO style) 32p. H plus 1 sub. min. pcb mounting 65p.</p>	<p><b>DIODES.</b> IN4001 10 for 35p. IN4004 10 for 45p. IN4007 10 for 50p. BY127 10 for 75p. HW14 (numbered) 100 for £2.50 IN4140 (numbered) 100 for £2.25. 50 volt 1 amp Bridge Rects. 18p.</p>
<p><b>SPECIAL OFFER SEMICONDUCTORS.</b> 2N50B2 SCR's 10p. 6X504 opto isolator 25p. CA3130 95p. TBA800 50p. C1060 (400V) SCR 20p. 741 22p. 723 35p. ME555 24p. IM3400 40p. AD161/2 70p pair. 2N3055 38p. IM4005 10 for 35p. 60230 20p. 80430 20p. 7415 35p. 2N414 75p. TIL305 alpha numeric display £2.50. MAA3A 3mm LED displays 45p. MAA. LDR's 30p. LEDS 0.2" CLEAR 15p. GREEN 12p. RED 10p.</p>	<p><b>MICROPHONES.</b> Min. 10 pin. Del. case dual aid battery (supplied) £4.95. Low cost condenser ECM105 0mm. 600ohms on/off switch standard jack plug £2.95. EM507 Condenser. uni. 600ohms. 30-18kHz. highly polished metal body. £7.95. DYNAMIC click microphone dual imp. 600ohms or 20k. 70-15kHz. attractive black metal body. £7.75. EM506 Condenser. carded. uni. 600ohms or 50k. heavy chromed copper case. £12.95. DYNAMIC P.A. Mike. mobile radio etc. 500 ohm switch 50p. imp. £3.75. CASSETTE replacement microphone with 2.5/3.5 plugs £1.35. INSERT crystal replacement 35x10mm 40p. GRUNDIG Electro inserts. with built in FET preamp 3-8vdc. £1.00.</p>	<p><b>SWITCHES.</b> Sub. Min. Toggle. SPST 8x5x7mm. 52p. OPOT (8x7x7) 62p. OPOT Centre off (12x11x9mm) 77p.</p>	<p><b>ROCKER SWITCHES.</b> 2 amp SPST single hole fixing. various colours (red, black, yellow, green, white) 19p each. 250vac 6 amp white rocker. 21x15x13mm 17p each.</p>	<p><b>PROJECT BOXES.</b> Sturdy ABS black plastic boxes with brass inserts and lid. 75x56x35mm 54p 95x7x35mm 65p 115x93x37mm 75p.</p>	<p><b>SPECIAL OFFER</b> 5-piece jewelers screwdriver set, with individual handles, supplied in plastic wallet only £1.05 per set.</p>
<p><b>NEW STOCK ITEM</b> - We are now stocking Expo mini hand held drills. These are a precision British made tool, ideal for P.C. board drilling, metal markers etc. They operate on 12VDC. Drill only £7.35. Drill kit supplied in plastic hinged case, with drill and 21 accessories, drills, sanders, reamers, buffers etc. complete kit only £14.25.</p>	<p><b>SEND G.S. ETCHING KIT SYSTEM.</b> Unique idea for etching P.C. boards. off done in a sealed bag, supplied with everything needed for etching P.C. boards. will etch approximately 1600cm<sup>2</sup> of copper board. £12.10.</p>	<p><b>PUSH SWITCHES</b> (16x6mm, red top, push to make 15p each, push on break version black vinyl 17p each).</p>	<p><b>RELAYS.</b> Clara Elliot sub. min. relay 10x10mm 2 pole c/w. 1.25V coil new 75p. Miniature encapsulated reed relay. 0.1 matrix mounting. single make operated on 12vdc 50p. Continental series, sealed plastic case type. 24vdc. 3 pole c/w 5 amp contacts. new 65p. 230vac Sealed Relay. 3 pole 5 amp contacts. ex. equipment. 11-pin base. 60p each. Minia Casmod reed relay 50x45x17mm, has 4 heavy duty make reed inserts. operates on 12vdc 35p each.</p>	<p><b>VERO HAND HELD BOX</b> White ABS. 2.4"x3.1" tapered. with screws 60p each.</p>	<p><b>MORSE KEYS.</b> Beginners practice key £1.05. All-metal type. fully adjustable £2.80.</p>
		<p><b>SLIDE SWITCHES</b> all OPOT 15x6x12mm 13p. 16x11x9mm 13p. 22x13x9mm 13p. 22x13x8 centre off 14p. Multiple slider double echoes (12 tags) 29x9x11mm 25p.</p>	<p><b>STOP PRESS.</b> New arrival. 12 volt car stereo meters with pulley only 60p each. 6 track stereo playback heads only 85p each. Car radio boards, complete chassis with 6 transistors (IF chokes, etc. new but no info. 80p each. Car radio RF/IF and audio preamp boards. 2 transistors. IN382 IC. trimmers. F's etc. new but no info. 60p each.</p>	<p><b>VERO POTTING PLASTIC</b> Boxes with lid and screws 70x50x25mm, white or black. 43p each.</p>	<p><b>MURATA TRANSUCERS.</b> REC/SENDER. IM40H 46kHz £3.50 pair.</p>
		<p><b>16 pin D.I.I. SWITCHES</b> only 42p each.</p>		<p><b>CLIFF CLICKTEST.</b> 13 amp mains connector. ideal for workshop, etc. provides rapid and safe mains connection. tough moulded case and lid with neon indicator and fuse. £5.15.</p>	<p><b>TELEPHONE PICK UP COIL</b> Sucker type with lead end 3.5mm jack 62p.</p>
		<p><b>RIBBON CABLE</b> 8-way single core miniature 22p per metre.</p>		<p><b>PUSH BUTTON TV TUNERS</b> (not varicap) transistorised U.H.F. new £2.25.</p>	<p><b>JUMPER TEST LEAD SETS</b> 10 Pairs of leads with various coloured croc clips each end (20 clips) 90p per set.</p>
		<p><b>SMALL F.M. MICROPHONE.</b> Tenable 88-95MHz. approximate range (outdoors) 30 metres. Runs off two HP7 batteries (not supplied). £4.55.</p>		<p><b>POWER SUPPLIES.</b> Switched type plugs into a 13 amp socket. has 3-5-6-7.5 and 9 volts D.C. cell at either 100 or 400ma switchable £3.45. HC24AR stabilised power supply 3-5-7.5-9vdc at 400ma, has polarity reversing and an off switch and is fully regulated to give exact voltage from no load to maximum current £5.50.</p>	

Terms. Cash with order (official orders welcomed from colleges etc) 30p postage please unless otherwise shown. VAT inclusive prices. S.A.E. for new illustrated lists.


## PROGRESSIVE RADIO

31 CHEAPSIDE, LIVERPOOL L2 2JD

# TOTAL AMPLIFICATION FROM CRIMSON ELEKTRIK

## WE NOW OFFER THE WIDEST RANGE OF SOUND PRODUCTS

### STEREO PRE-AMPLIFIER

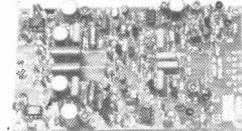

**CPR 1 — THE ADVANCED PRE-AMPLIFIER.** The best pre-amplifier in the U.K. The superiority of the CPR 1 is probably the disc stage. The overload margin is a superb 40dB, this together with the high slewing rate ensures clean top, even with high output cartridges tracking heavily modulated records. Common-mode distortion is eliminated by an unusual design. R.I.A.A. is accurate to 1dB; signal to noise ratio is 70dB relative to 3.5mV, distortion <.005% at 30dB overload 20kHz.

Following this stage is the flat gain/balance stage to bring tape, tuner, etc. up to power amp signal levels. Signal to noise ratio 86dB, slew-rate 3V/uS. T.H.D. 20Hz—20kHz <.008% at any level.

F.E.T. muting. No controls are fitted. There is no provision for tone controls. CPR 1 size is 138x80x20mm. Supply to be ± 15 volts.

**MC 1 — PRE-AMPLIFIER.** Suitable for nearly all moving-coil cartridges. Sensitivity 70/170uV switchable on the p.c.b. This module brings signals from the now popular low output moving-coil cartridges up to 3.5mV (typical signal required by most pre-amp disc inputs). Can be powered from a 9V battery or from our REG 1 regulator board.


**XO2:XO3 — ACTIVE CROSSOVERS.** XO2 — two way, XO3 — three way. Slope -24dB/octave. Crossover points set to order within 10%

**REG 1 — POWER SUPPLY.** The regulator module, REG 1 provides 15.0-15v to power the CPR 1 and MC 1. It can be used with any of our power amp supplies or our small transformer TR 6. The power amp kit will accommodate it.

**POWER AMPLIFIERS.** It would be pointless to list in so small a space the number of recording studios, educational and government establishments, etc., who have been using CRIMSON amps satisfactorily for quite some time. We have a reputation for the highest quality at the lowest prices. The power amp is available in five types, they all have the same specification. T.H.D. typically 0.1% any power 1kHz 8 ohms. T.I.D. insignificant, slew rate limit 25V/uS, signal to noise ratio 110dB, frequency response 10Hz-35kHz — 3dB stability unconditional, protection drives any load safely; sensitivity 775mV (250mV or 100mV on request), size 120x80x25mm

**POWER SUPPLIES.** We produce suitable power supplies which use our superb TOROIDAL transformers only 50mm high with a 120-240 primary and single bolt fixing (includes capacitors/bridge rectifier).

### POWER AMPLIFIER

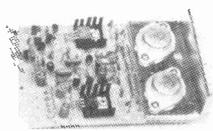


### POWER SUPPLIES

We produce suitable power supplies which use our superb TOROIDAL transformers only 50mm high with a 120-240 primary and single bolt fixing (includes capacitors/bridge rectifier)

**PRE-AMPLIFIER KIT** THIS INCLUDES ALL METAL WORK POIS KNOBS ETC - TO MAKE A COMPLETE PRE AMP WITH CPR 1(S) MODULE AND THE MC1(2) IS REQUIRED
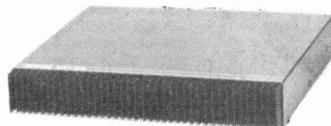
### POWER AMPLIFIER KIT

The kit includes all metalwork, heatsinks and hardware to house any two of our power amp modules plus a power supply. It is contemporary styled and its quality is consistent with that of our other products. Comprehensive instructions and full back-up service enables a novice to build it with confidence in a few hours.



**POWER AMPLIFIER MODULES**  
 CE 60B 60W/8 ohms 35-0-35v £19.52  
 CE 100A 100W/4 ohms 35-0-35v £23.02  
 CE 100B 100W/8 ohms 45-0-45v £25.96  
 CE 170A 170W/4 ohms 45-0-45v £31.00  
 CE 170B 170W/8 ohms 60-0-60v £33.97

**TOROIDAL POWER SUPPLIES**  
 CPS1 for 2xCE 60B or 1xCE 100A £16.56  
 CPS2 for 2xCE 100A or 2x4xCE 60B £18.80  
 CPS3 for 2xCE 100B or 1xCE 170A £19.75  
 CPS4 for 1xCE 100B £17.12  
 CPS5 for 1xCE 170B £24.15  
 CPS6mk 2xCE 170A or 2xCE 170B £25.53

**HEATSINKS**  
 Light duty, 50mm, 2 C/W £1.44  
 Medium power, 100mm, 1-4 C/W £2.35  
 Disco/group, 150mm, 1-1 C/W £3.04  
 Fan, 80mm, state 1-2U or 2-4Uv £19.70  
 Fan mounted on two drilled 100mm heatsinks 2x4 C/W, 65 max with two 170W modules £31.05

**THERMAL CUT-OFF, 70 C** £1.54

\*Distributors  
 Minic Teleproduktur  
 Box 12035  
 S-750 12  
 Uppsala 12  
 Sweden

Badger Sound Services Ltd., 46 Wood Street, Lytham St. Annes, Lancashire FY8 1QG

All prices shown are UK only and include VAT and post. COD 90p extra. £1.00 limit. Export is no problem, please write for specific quote. Send large SAE or 3 International Reply Coupons for detailed information



**POWER AMP KIT** £35.03

**PRE-AMPS**  
 These are available in two versions — one uses standard components, and the other (the S), uses MQ resistors where necessary and tantalum capacitors.

CPR1 £31.65  
 CPRIS £40.87  
 MC1 £21.28  
 MC1S £33.17  
 Pre-amp Kit £38.17

**ACTIVE CROSSOVERS**  
 XO2 £15.16  
 XO3 £23.58

**POWER SUPPLY**  
 REG1 £6.90 TR6 £1.97

**BRIDGE DRIVER, BD1**  
 Obtain up to 340W using 2x170W amps and this module £5.75

## CRIMSON ELEKTRIK

1A STAMFORD STREET, LEICESTER LE1 6NL. Tel. (0533) 553508  
 U.K. — please allow up to 21 days for delivery

# More second user bargains from Carston

Top Quality Test Equipment at the keenest prices

TEK 465 and 475A now ex-stock

TEXSCAN	Prices from £	
VS401 300 MHz sweeper		450
WAYNE KERR		
5121 10 Hz-120 KHz		25
022B 10 Hz-10 MHz		75
Spectrum Analysers		
HEWLETT PACKARD		
141T Display unit storage		845
8552A I.F. Plug-in		1600
8553L 1 kHz-110 kHz Plug-in		1650
8554L 500 kHz-1.250 MHz Plug-in		2100
T.V. Test Equipment		
MARCONI		
TF2909 Gray scale generator		250
Temperature & Humidity		
COMARK		
1604BLU Analogue thermometer		40
0 100 °C		
LEE-DICKENS		
HP5 Humidity probe		130
HUMIGUN Temp/humidity probe with meter		215
RAYTEK		
T1000 Infra red thermoprobe		200
Vibration		
DAWE		
1461 CV(M) Portable Vibration Analyser Kit		450
Voltmeters - Analogue		
AIRMEC		
264 Millivoltmeter 3 mV-1 V ranges		45
AVO		
8 Mk VAC/DC/OHMS		60
BOONTON		
93A 20 Hz-20 MHz True RMS		260
BRADLEY		
CT471 C AC/DC/Ω current multimeter and RF		165
DAWE		
614C Millivoltmeter 0.3 mV-300 V ranges		25
HEWLETT PACKARD		
427A AC/DC/Ω multimeter		275
3406A 10 kHz 1.2 GHz		395
KEITHLEY		
610B Electrometer recorder O P		330
LINSTEAD		
M2B DC/AC 10 Hz-500 kHz		25
MARCONI		
TF2603 AC voltmeter to 1.5 GHz		300
NORMA		
U-Function Dual channel peak/RMS meter		325
PHILIPS		
PM2454B AC voltmeter to 12 MHz		225
Voltmeters - Digital		
ADVANCE		
DMM3 1999 FSD AC/DC/Ω current		85
DANA		
5230 119999 FSD AC/DC		175
FLUKE		
8300A 119999 FSD DC only		150
HEWLETT PACKARD		
3474/2 9999 FSD AC DC/Ω		185
SOLARTRON		
A200 19999 FSD DC only		160
A205 19999 FSD AC/DC/Ω		300
*7045 19999 Auto AC/DC/OHMS		295
*7050 99999 Auto AC/DC/OHMS		395
Wave Analysers		
GENERAL RADIO		
1232A Tuned amplifier and null detector 20 Hz-20 KHz		75
HEWLETT PACKARD		
302A 20 Hz-50 kHz 75 db range		375
WAYNE KERR		
A321 20 Hz-20 KHz Sens 75 db		125

*8 Mk VAC/DC/OHMS		60
BOONTON		
93A 20 Hz-20 MHz True RMS		260
BRADLEY		
CT471 C AC/DC/Ω current multimeter and RF		165
DAWE		
614C Millivoltmeter 0.3 mV-300 V ranges		25
HEWLETT PACKARD		
427A AC/DC/Ω multimeter		275
3406A 10 kHz 1.2 GHz		395
KEITHLEY		
610B Electrometer recorder O P		330
LINSTEAD		
M2B DC/AC 10 Hz-500 kHz		25
MARCONI		
TF2603 AC voltmeter to 1.5 GHz		300
NORMA		
U-Function Dual channel peak/RMS meter		325
PHILIPS		
PM2454B AC voltmeter to 12 MHz		225
Voltmeters - Digital		
ADVANCE		
DMM3 1999 FSD AC/DC/Ω current		85
DANA		
5230 119999 FSD AC/DC		175
FLUKE		
8300A 119999 FSD DC only		150
HEWLETT PACKARD		
3474/2 9999 FSD AC DC/Ω		185
SOLARTRON		
A200 19999 FSD DC only		160
A205 19999 FSD AC/DC/Ω		300
*7045 19999 Auto AC/DC/OHMS		295
*7050 99999 Auto AC/DC/OHMS		395
Wave Analysers		
GENERAL RADIO		
1232A Tuned amplifier and null detector 20 Hz-20 KHz		75
HEWLETT PACKARD		
302A 20 Hz-50 kHz 75 db range		375
WAYNE KERR		
A321 20 Hz-20 KHz Sens 75 db		125

\*Equipment added this month

**Redundant Test Equipment**  
Why not turn your under-utilized test equipment into cash? Ring us and we'll make you an offer.  
VAT charged at Standard Rate

<b>Acoustic</b>	Prices from £	
BRUEL & KJAER		
2203 Precision sound level meter		400
2204 Precision sound level meter		475
1613 Octave filter set couples directly to 2203 & 2204		250
4216 Artificial Mouth		25
*2624 Charge Amplifier		65
CEL		
112 LEO meter digital readout		450
<b>Bridges etc.</b>		
DAWE		
210B Decade Capacitance box		20
0.1 μF-1 mF 0.1 μf step		
MUIRHEAD		
D30A Wheatstone bridge test set		75
SULLIVAN		
T1098 Decade resistance bridge		90
WAYNE KERR		
B601Z RF bridge to 5 MHz		275
SR268 Source for B601Z		
<b>Cable Test Equipment</b>		
MARCONI		
TF2091A/TF2092A White noise generator/receiver 300 channel system complete		350
*TF2333 Transmission Test Set		575
STC		
74226B Telephone cable test set		120
*74216A Noise Generator CCITT		240
*74261A Psophometer CCITT		475
<b>Circuit Magnification</b>		
MARCONI		
TF1245/46/47 'Q' Meter with Oscillators		525
<b>Counter Timers</b>		
HEWLETT PACKARD		
5263A Time interval plug-in		60
MARCONI		
TF2414A DC-40 MHz 7 digits		170
TF2422 Frequency divider to 300 MHz		30
RACAL		
9024 10 Hz-600 MHz 7 + 1 digits		325
9059 DC-560 MHz with battery pack		300
9835 DC-15 MHz 6 digits		145
9837 DC-80 MHz 6 digits		190
<b>Function Generators</b>		
HEWLETT PACKARD		
3300A 0.01 Hz-100 kHz sine square triangular		100
3301 Auxiliary plug in		
<b>Logic Analysers</b>		
HEWLETT PACKARD		
1601 L Logic state analyser 12 channel display		600
<b>Mains Monitors</b>		
AMPROBE		
LAV3X Mains voltage recorder		45
GEC		
FB31A Surge monitor records mains spikes + filter		85
RUSTRAK		
288 + CT Clamp-on AC recording ammeter		95
<b>Modulation Meters</b>		
AIRMEC		
*2101-300 MHz AM/FM		195
*4093-1500 MHz AM/FM		325
MARCONI		
*TF2300A 1-1000 MHz AM/FM		520

<b>Oscilloscopes</b>	Prices from £	
ADVANCE		
OS1000A DC-20 MHz dual trace		310
COSSOR		
110/111 DC-20 MHz dual trace		325
110/112 DC-1 MHz differential		275
HEWLETT PACKARD		
184A + 1801A + 1822A DC 50 MHz system, T.B. and amplifier included storage facility (storage de-rated please ask for details)		650
1707B20 DC-75 MHz dual trace D T B		700
1710B DC-200 MHz dual trace		1250
TEKTRONIX		
5103N/D15		
Storage system 800 div, ms DC-2 MHz		350
7A13 DC-100 MHz differential comparator		350
7B70 Dual time base with 7B71 delayed sweep (for 7000 series)		275
536 Mainframe 11 MHz X-Y		100
519 1 GHz Real Time Matching accessories included		850
535A/CA DC-15 MHz dual trace DTB		250
545B/CA DC-24 MHz dual trace DTB		350
585A/81 DC-80 MHz dual trace DTB		550
454 DC-150 MHz dual trace DTB		1350
<b>TELEQUIPMENT</b>		
D54 DC-10 MHz dual trace		240
D75 DC-50 MHz dual trace D T B (Portable)		550
D83 DC-50 MHz dual trace D T B (Bench)		575
D53/CD/G DC-15 MHz Dual Trace with differential amplifier		225
<b>Oscilloscope Probes - Current</b>		
TEKTRONIX		
P6021 AC current probe to 20 MHz		200
<b>Oscilloscope Probes - Voltage</b>		
HEWLETT PACKARD		
1121 A 500 MHz		90
TEKTRONIX		
P6046 Differential probe DC 100 MHz		215
<b>Oscilloscope Cameras</b>		
HEWLETT PACKARD		
195A Pack film polaroid		190
198A Pack film polaroid		120
TEKTRONIX		
C30AR Roll film polaroid		130
<b>Power Meters</b>		
HEWLETT PACKARD		
432A, 478A 10 MHz-10 GHz wideband with bolometer		350
<b>Power Supplies</b>		
HEWLETT PACKARD		
6265B DC stab variable 40 V, 3 A		195
ROBAND		
T101 50 V 1 A Variable		30
SOLARTRON		
As 751 50 V 1 A Variable		25
STARTRONIC		
117 20 V 0.5 A Variable		25
SYSTRON DONNER		
LNG 16-10 16 V, 10 A variable		75
<b>Pressure &amp; Displacement Transducers</b>		
ELECTRO MECHANISMS		
LVD1 DC linear variable ±0.50 inches		25

<b>Pulse Generators</b>	Prices from £	
E. H. RESEARCH		
G710 5 V/50 Ω 30 Hz-50 MHz RT 5 ns		100
132AL 50 V/50 Ω 5 Hz-3 MHz RT 12 ns		175
LYONS INSTRUMENTS		
PG2E 10 V/50 Ω 1 Hz-16 MHz RT 10 ns		130
PG23 10 V/50 Ω 1 Hz-10 MHz RT 5 ns		135
SYSTRON DONNER		
101 10 V/50 Ω 10 Hz-10 MHz RT 5 ns		95
<b>Recorders &amp; Signal Conditioning Equipment</b>		
BRUNO WOELKE		
ME102B Wow and flutter meter		75
ME102C Wow and flutter meter		90
<b>Recorders &amp; Signal Conditioning Equipment</b>		
BRUEL & KJAER		
2305B Stylus Recorder includes 50 db pot		650
HEWLETT PACKARD		
17502A Plug-in for 7100 series recorder temperature module		25
SE LABS		
3006DLT 12 channels UV 6 inch chart		450
A1000 Galvo 600 Hz 0.34 mA/cm		30
MICROMOVEMENTS		
M400 Galvo 300 Hz 50 μA/cm		25
M1000 Galvo 600 Hz 0.34 mA/cm		25
M1600 Galvo 1000 Hz 0.4 mA/cm		25
M8000 Galvo 5 kHz 15.5 mA/cm		25
SIEMENS		
KOMP III 2 pen potentiometric roll chart		425
<b>Signal Sources &amp; Generators</b>		
ADVANCE		
H1 15 Hz-50 KHz		40
DAWE		
410C 0.1 Hz-10 KHz		40
EH RESEARCH		
967 Attenuator 25W 0-40 db		
HEWLETT PACKARD		
200CD 5 Hz-600 kHz O/P 10 V RMS		75
8693, 100 3 7 8 3 GHz 5 mW sweeper plug in		525
* 608E 10-480 MHz AM		410
* 618C 3-8-7-6 GHz FM		1600
* 620B 7-11 GHz FM		1600
MARCONI		
TF791 FM Deviation Meter 4-1024 MHz		95
TF801D1 10-470 MHz AM PM		150
TF885 0-12 MHz Sine/Square		75
TF995A/2 1.5-220 MHz AM FM		350
TF995B/5 0.2-220 MHz AM FM		475
TF1060 0-1.2 GHz AM PM		150
TF2005A Two tone 20 Hz-20 KHz		200
ROHDE & SCHWARZ		
SWOB I 0.5-400 MHz 75 Ω		225
SWOB II 0.5-1200 MHz 50 Ω with delay line and accessories		1250



Contact David Kennedy  
**01-267 5311/2**  
Carston Electronics Limited,  
Shirley House, 27 Camden Road,  
London NW1 9NR Telex 23920

note our new telephone number

**LINES FROM OUR VAST STOCKS — IMMEDIATE DELIVERY**

**ALL BELOW MANUFACTURERS' PRICES — ALL NEW STOCKS.**

Postage & packing add 50p per order  
**CALCULATOR CHIPS** General instrument GIMT4 on anti-static foam 24 pin S I L socket for use with Bowmar display £1.50 ea Pack of 25 chips £25, 100 for £80, 500 for £350.  
**BOWMAR 9 DIGIT CALCULATOR DISPLAY** with PC connector 0 2 digits. Common cathode with bezel £1.25 ea 10 for £10.  
**ORP12** light dependent resistance (Eq = RPY30) 2 for £1, 10 for £4, 100 for £35.  
**TBA 120A** TV I C amplifier Siemens 55p, 10 for £5, 100 for £50, 1 000 for £350.  
**BECKMAN 500** kcs Triggerable clocking oscillator for use with calculator chips 5v supply with circuit £1, 10 for £8, 100 for £65.  
**BURROUGHS 9 DIGIT** Panaplex calculator display 7 segment 0 25" digits Neon type with red bezel socket and data £1.95 ea 10 for £17, 100 for £140.  
**HONEYWELL PROXIMITY DETECTOR** integral amplifier 8v 0 C £3.50 ea, 10 for £30, 100 for £275.  
**OSMOR CHANGE OVER REED RELAY** 12v coil 20m/a operating current 5x17x13mm 75p ea 10 for £5, 100 for £45.  
**MARRIOTT TAPE HEADS** Quarter track Type Each Per 100  
 XRPS18 Record Replay £3.00 £25.00 £200.00  
 XRPS36 Record Replay £4.00 £35.00 £250.00  
 XES11 Erase £1.25 £11.00 £100.00

**MULLARD AD161-AD162 Matched pairs**  
 1 pair 80p, 10 pairs £6, 100 pairs £50.  
 Cartons of 600 pairs £250 EX-STOCK  
**RADIATION DETECTORS** Quartz Fibre Dosimeters Pen type with clip with lens and scale 0-50R Originally over £5 **OUR PRICE 95p EACH**, 10 for £8, 100 for £60, 1 000 for £500.  
**CLOCKING OSCILLATOR** (Pye-Dynamics) thick film 1mHz supply 5v 19x25x8mm 85p, 10 for £7, 100 for £80, 500 for £250.  
**TV TUNERS** by Mullard UHF 38 mes size 3/4x2 3/4x1 1/2 £2.50 ea 10 for £20, 100 for £175, 500 for £750, 1 000 for £1,250.  
**NEW SILICON NPN TO92** BF216/BF220 (BC207 eq) Packs of 100 £3.50, packs of 1,000 £25.00, packs of 5,000 £100.00.  
**MULLARD TUNER MODULES** with data LP1171 combined AM/FM IF strip £3.50, LP1179 FM front end with AM tuning gang used with LP1171 £3.50, LP1171 and 79 pair £5.75, 10 pairs for £50, 100 pairs for £400.  
**CA3085 RCA POSITIVE VARIABLE REG.** 5volt 100m amp variable 1.8-24v 55p ea 10 for £5, 100 for £35, 1 000 for £300.  
**MULLARD LP1157** AM tuner modules with

circuit £2.50 ea 10 for £20, 100 for £175.  
**LUSTRAPHONE RIBBON MIKE** £1.50, pre amp on chassis 3x2x1in 10 for £12.50.  
**5 WATT GOULD-ADVANCE AMPLIFIER** (built) 500kc into 2K input 4-8 ohms with data £3 ea 11 5x6x3cm  
**AVO-B METER MOVEMENTS** for military version Precision 37.5 micro-amp (50µa with integral shunt) movement £10.50.  
**MINIATURE MAINS TX** 240 volt, primary 12v, 100m/amp Size 60x40x42mm 95p ea 10 for £8, 100 for £85, 500 for £250.  
**PHOTO CONDUCTIVE CELL** £1.25 High power Cds cell 600 mw for control circuits Resistance 800 ohm to 4K. Max volts 240 Size 1 1/2x1/2in 10 for £11, 100 for £100.  
**DYNAMIC MICROPHONE.** Low imp Foster insert. £1.45, 10 for £11, 100 for £100.  
**UHF TUNER BY GEC.** 38mc /s with slow motion tuning Size 5x3x2in, £3 ea 10 or £25, 100 for £220, 500 for £1,000.  
**TWO GANG MINIATURE VARICAP TUNER** 500pf with tuning knob size 3x1 1/2x1 1/2in £1.25 ea 10 for £10, 100 for £85.  
**SES-ATES U14652 AUDIO I.C. AMPLIFIER** 14 PIN D.I.L., 300 m watts 55p each. 10 for £4.50, 100 for £35.  
**GENERAL ELECTRIC** 2+2 watt I C stereo audio chips with circuit & data £1.95 each 10 for £17.00  
**R.C.A. CD4029AE** 16 pin D I L presettage up-down counter 85p each 25 for £15.00 100 for £50 1000 for £355 (in anti static tubes of 25)  
**U.H.F. TV TUNER** (preamp) with BF180 55p each Built on P C board 2 x 2in (sold without data) 10 for £4.50 100 for £35  
**MARCONI I C Oscillator Datil** (TO99 can) 30p each 10 for £2 100 for £15 1000 for £125  
**PLESSEY SL432A I C IF amplifier** (TO99 can) 55p each 10 for £4 100 for £29 500 for £120  
**V.H.F. MODULATORS** for tv games 55p each 2 transistor — on built P C sizes 2 x 2 x 1 1/4in 10 for £4 100 for £35 500 for £150  
**R F Filters** for above modulators 20p each Components and coils on built p circuit, size 2 x 2 x 1 1/4in, 10 for £3.50 100 for £30 500 for £125  
**HIGH VOLTAGE TV TRIPLER DIODES** BY I.T.T, stick type per 10 £1.50, per 100 £10, per 1000 £85.  
**TBA825 ATEs** variable voltage regulators 55p each 5 volts 100 m/amps (TO99) per 10 £4.50, per 100 £39, per 1000 £280.  
**MAINS LEADS** 2 core 2 metres lengths (grey) per 10 £2.50, per 100 £20, per 1000 £165.  
**MMS314 NATIONAL CLOCK CHIPS** £1.95 each, per 10 £17.  
**IN914 TYPE DIODES** tested, uncoated in boxes of 1 000 £10, 10 000 for £75, 100 000 for £500.



**HENRY'S**

All mail to:  
 404 Edgware Rd  
 London W2 England  
 Phone 01-723 1008



EXPORT ORDERS add ten per cent for carriage and pack

Payment in Sterling.

# SERVICING BY PROFESSIONALS

## THE COMPANY

Kode Services Limited, part of the British owned Kode International Group of Companies, is rapidly becoming a major U.K. service operation specialising on a whole range of equipment from basic terminals to microprocessor based systems.

Over 100 Field Service Engineers nationwide coupled with full depot and workshop facilities are available to support the following equipments:

Apple II Model 33, 40, 43 TT, Lear Siegler ADM1A, 2A, 3A, ADM42 and 31, Microstar V, Anadex D8000 Printer. We have the capability to service new products and are always evaluating new D.P. equipment.

Fullly comprehensive maintenance contracts or a full depot repair service can be offered.


## THE CAREER

Opportunities are available for experienced professionals and gifted amateurs who have a full understanding of TTL logic and digital techniques, and wish to move into a service orientated career applying their knowledge to the servicing of sophisticated electronic equipment.

For further details on maintenance or job prospects, please call or write to Mr. C. Marklew on 0249 813771.

**KODE SERVICES LTD.**  
 Station Road, Calne, Wiltshire

## Semiconductor Guides.

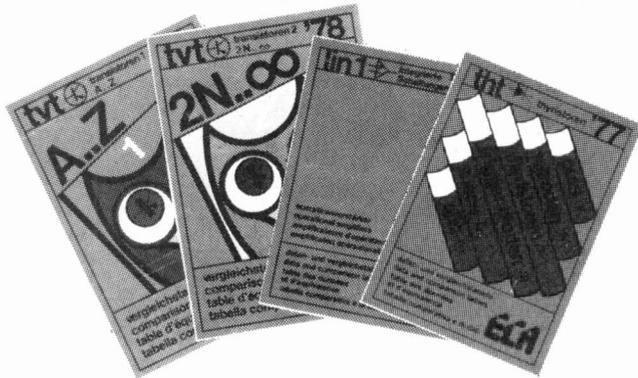

**THT '77**  
 Data and comparison table for thyristors, tetrodes, trigger diodes, triacs, unijunction transistors (UJTs) and programmable UJTs (PUTs)  
 250,000 entries  
 Order No. 20

**IC-jin 1**  
 Data and comparison table for integrated op amps and comparators. 2nd edition. DIN A6 compact format.  
 288 pages, types, functions, applicational examples, 152 connection drawings, 48 case drawings  
 Order No. 11.

**TVT '78 Vol. 1: A...Z**  
 Transistor comparison table  
 Lists more than 25,000 equivalent types for approx. 5,000 transistors  
 9th edition  
 292 pages, 11 illustrations, 137 connection drawings  
 In handy compact format  
 DIN A6, wipe-clean cover.  
 Order No. 30  
 ISBN 3-88109-010-X

**ALSO AVAILABLE**  
 Diode Equivalent Book £2.30  
 Diode Data Book £2.30  
 Digital I.C. Equivalent Book £5.50

**TVT '78 Vol. 2: 2N...∞**  
 Transistor comparison table  
 Lists more than 35,000 equivalent types for approx. 7,000 transistors  
 2N — 2SA  
 2SB — 2SC  
 2SD — 2SK  
 3N — ∞  
 408 pages, 11 illustrations, 141 connection drawings  
 In handy compact format  
 DIN A6, wipe-clean cover.  
 Order No. 31  
 ISBN 3-88109-011-8.

**TVT78 A-Z £4.00**  
**TVT78 2N £4.00**  
**THT77 £4.00**  
**LIN 1 £3.60**  
**LIN 2 £3.80**

## what is a microprocessor?





If you are considering buying a Microcomputer, Development System, or just want to learn more about this exciting technology, then this short introduction to Microprocessors is for you. Comprising of a 72-page book keyed to over two hours of cassette tapes the many aspects of Microprocessors are explained, including Binary and Hexadecimal counting, Internal structure, Operation, Programming Techniques, Devising a program, etc. Learn at your own pace with this valuable addition to your reference library. **£10.75.**

**Technical Book Services**  
**P.O. Box 79**  
**Maidenhead, Berks. SL6 2EG**
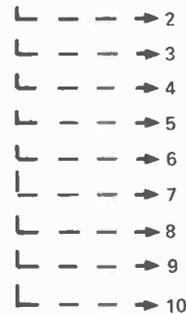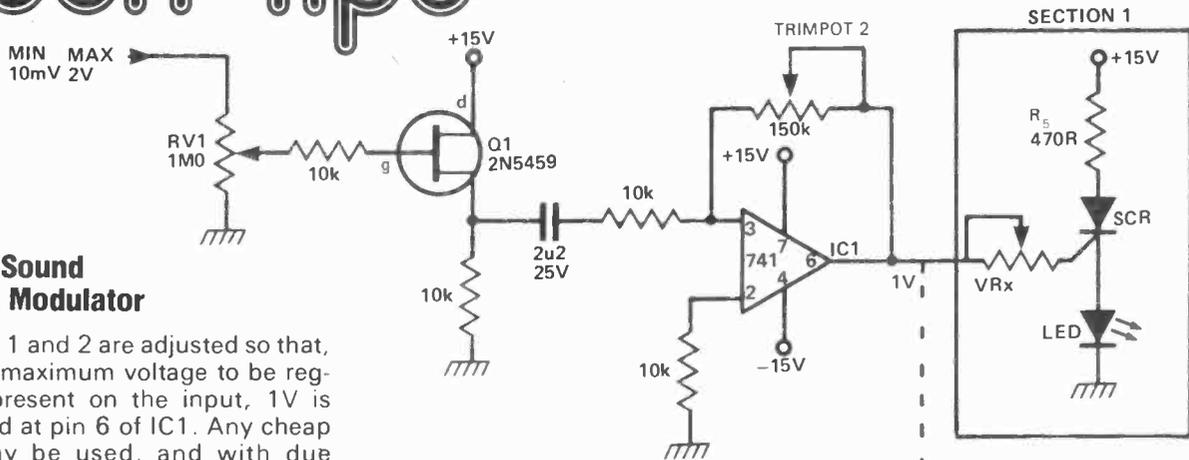
### Simple Sound to Light Modulator

Trimpots 1 and 2 are adjusted so that, with the maximum voltage to be registered present on the input, 1V is registered at pin 6 of IC1. Any cheap SCR may be used, and with due reference to the gate current of the SCR, VRx can be calculated:  $R(\text{ohms}) = V/I$ , where  $V = 1V$  and  $I = \text{gate current}$ . In setting up, VRx is adjusted in section 1 so that the LED lights up when 1V is present at pin 6 of IC1. This is repeated in sections 2-10 with VRx being adjusted with 0.9:0.8 . . . -0.1V at pin 6. Any number of sections can be added/subtracted with due adjustment to VRx. If the supply voltage is changed

(from 5-0-5 to 15-0-15) Rs must be changed to give approx 30 mA through the LED. The main advantage of this circuit is the very high input impedance given by the FET input and thus the original audio signal is hardly affected and has negligible current drawn from it (as is not the case with other VU circuits).



### CMOS Mixer

J. P. Macaulay


Although this circuit employs only one cheap CMOS IC and two transistors it is capable of high quality results. The IC, a 4011, contains four dual input NAND gates. Two of these are used with their inputs connected together to form inverters and biased into the linear mode by means of the feedback resistors, R2. Inputs are applied through the pots RV1/2 and are mixed by the gate to which they are coupled by C1, R1, R3 and C2. Although only two inputs are shown here, the circuit will mix up to four inputs by duplicating the input circuitry.

For clarity only one mixer gate is

shown in the schematic. The other gate, along with all the components to the left of C3 are duplicated on the other channel. The other two gates are used in a touch operated on-off switch.

The plates, which may consist of a small piece of Veroboard with alternate strips linked together and connected to the input of the gate and line respectively, control the output polarity of the gates.

When the circuit is turned on, by placing a finger on the touch plate, the output of this gate goes high switching Q2 hard on and supplying the circuit with current. To switch off the other touch plate is touched with the finger. The output then goes low removing the operating current from the circuit. The transistor Q2 gives the circuit a low output impedance and the gain with the input pot at maximum is four.

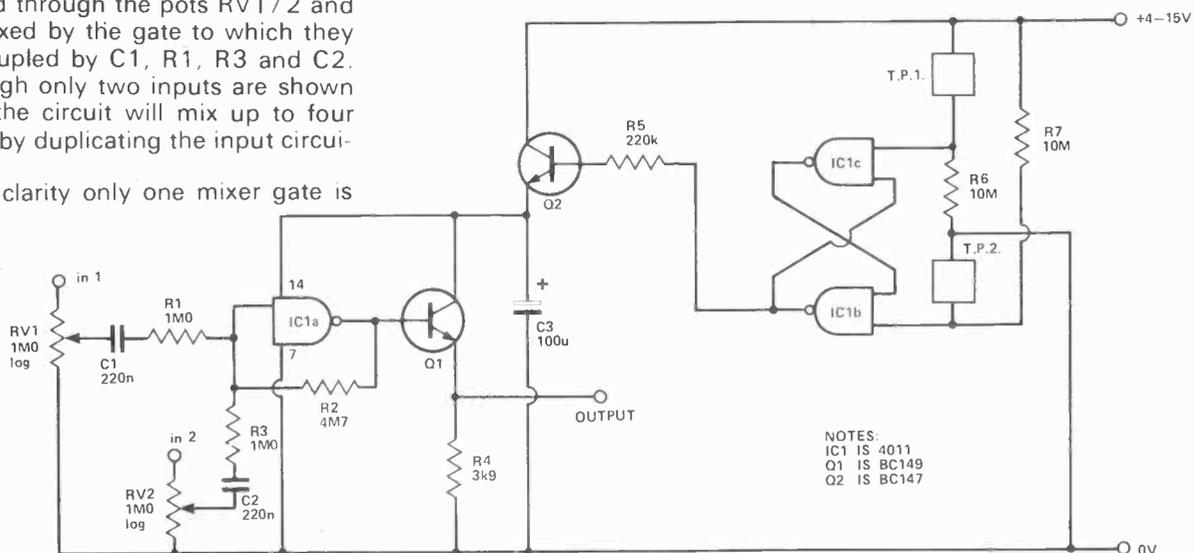


NOTES:  
IC1 IS 4011  
Q1 IS BC149  
Q2 IS BC147

Tech-Tips is an ideas forum and is not aimed at the beginner. We regret we cannot answer queries on these items.

ETI is prepared to consider circuits or ideas submitted by readers for this page. All items used will be paid for. Drawings should be as clear as possible and the text should preferably be typed. Circuits must not be subject to copyright. Items for consideration should be sent to ETI TECH-TIPS, Electronics Today International, 145 Charing Cross Road, London WC2H 0EE.

# HELP!

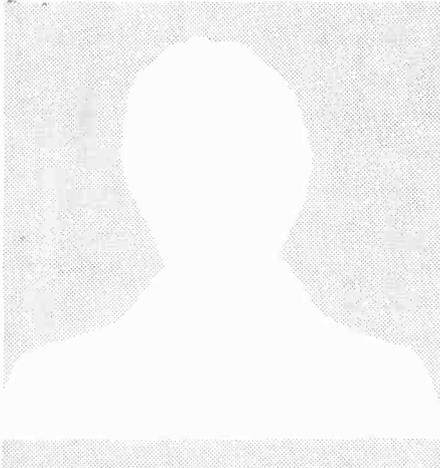

## EDITORIAL ASSISTANT

### SALARY CIRCA £4,000

We're looking for someone out there to come and be someone in here. Once more we are seeking to expand our editorial staff, and firmly believe that our past policy of recruiting enthusiastic readers is the best policy.

Applicants should be interested in electronics and able to express themselves — at least roughly — in English, although no journalistic experience is necessary. (Training will be given in technical journalism.)

An interest and a knowledge of radio frequency circuitry would be an advantage, in order to complement existing skills within our team.

Don't convince yourself that you haven't got the electronics expertise to apply for this job — you probably have! Write to the address below enclosing a C.V. — all applications treated in confidence.

Editorial Vacancy,  
Modmags Ltd,  
145 Charing Cross Road,  
London WC2.

## BUYING TIME? MAKE SURE IT'S CASIO

New Lithium batteries — outlast most solar watches

From Casio's New Collection comes one of the most sophisticated executive watches available today.

### THE 81CS-36B ALARM CHRONOGRAPH

LC Display of hours, minutes, seconds, day; and with day, date, month and year perpetual automatic calendar



**4-5 YEAR BATTERY.**  
1/100 th second chronograph to 7 hours. Net, lap and first and 2nd place times. User optional 12 or 24 hour display, 24 hour alarm. User optional, hourly chime. Backlight. Mineral glass, stainless steel case. Water resistant to 100ft. (3 at).

**£35.95**

### CASIO CHRONOGRAPHS

#### CASIO 95QS-31B

4-year battery. 1/100 sec. chrono to seven hours. Dual time, 12 to 24 hour. Stainless steel encased. Lightweight. Water resistant to 66 feet (2 at). RRP £27.95

**£23.95**



#### CASIO 95 CS-31B (De-luxe model)

5-year battery. 1/100 sec. chrono to six hours. Dual time. 12 to 24 hour. Solid stainless steel case. Water resistant to 100ft. (3 at). RRP £35.95

**£29.95**



New Lithium batteries put most SOLAR watches in the shade. Constant LCD display of hours, minutes, seconds, a.m./p.m. and day (12 or 24 hour). Dual time (12 or 24 hour). Automatic day, date, month and year calendar. Mineral glass face. Backlight. High quality s/s bracelets with easily removable links.

### HONGKONG WATCHES

Most low cost watches come from Hongkong and these are proving to be extremely unreliable, particularly those with multi-function modules, with failure rates of up to 60% or more. Repairs can take as long as three months and replacement parts are not always available.

Compare this with Casio, Citizen and Seiko, whose failure rate is typically under 1% and Casio's service time of 2-3 weeks and we ask you:

**ISN'T IT WORTH PAYING A LITTLE MORE FOR QUALITY AND RELIABILITY?**

Fully guaranteed for 12 months.

Prices include VAT, P&P, cheque/PO or phone your ACCESS or BARCLAYCARD number to:

# TEMPUS



#### CASIO F-8C 3-yr. battery

8-digit display of hours, minutes, seconds and DATE, with day and a.m./p.m. Auto. calendar, backlight, resin case and matching strap. Mineral glass, water resistant to 66ft. (2 at). RRP £12.95

Real quality and value for only  
**£10.95**

#### CASIO F-200 Sports Chrono

Hours, minutes, seconds, am/pm, and with day, date and month, auto calendar, 1/100 sec. chrono to 1 hour. Net lap and 1st and 2nd place times. Resin case and matching strap. Mineral glass. Water resistant to 66ft. (2 at.). Silver oxide battery. RRP £17.95

**£15.95**




### LATEST SCIENTIFICS

#### CASIO FX-68

LC Display. 37 scientific functions. Trigs, logs, exponentiations, etc. Standard deviations. Polar to Rectangular, R-P and sexagesimal to decimal conversions. Pi, cube root, six levels of brackets. Full memory. 500 hrs. battery. RRP £22.95.

**£19.95**

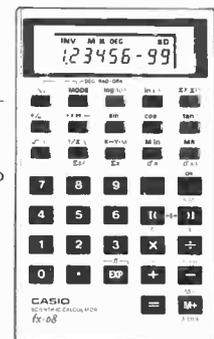

A very convenient 3/16 x 2 1/8 x 3 3/8" Wallet.

#### COLLEGE FX-80 POWERSAVER!

Specification as above plus ENG key. 4,000 hour battery life from two AA size batteries. 3/4 x 3 x 5 1/8". RRP £17.95.


**£15.95**

**PROGRAMMABLES.** FX-501P (£64.95), £54.95, FX-502P (£84.85), £74.95. FA-1 Adaptor (£24.95) £19.95.

**MELODY 80.** Now only £23.95 (£25.95).

Most CASIO products available from stock. Send 25p for illustrated brochures of this superb range of watches or calculators (both on request).

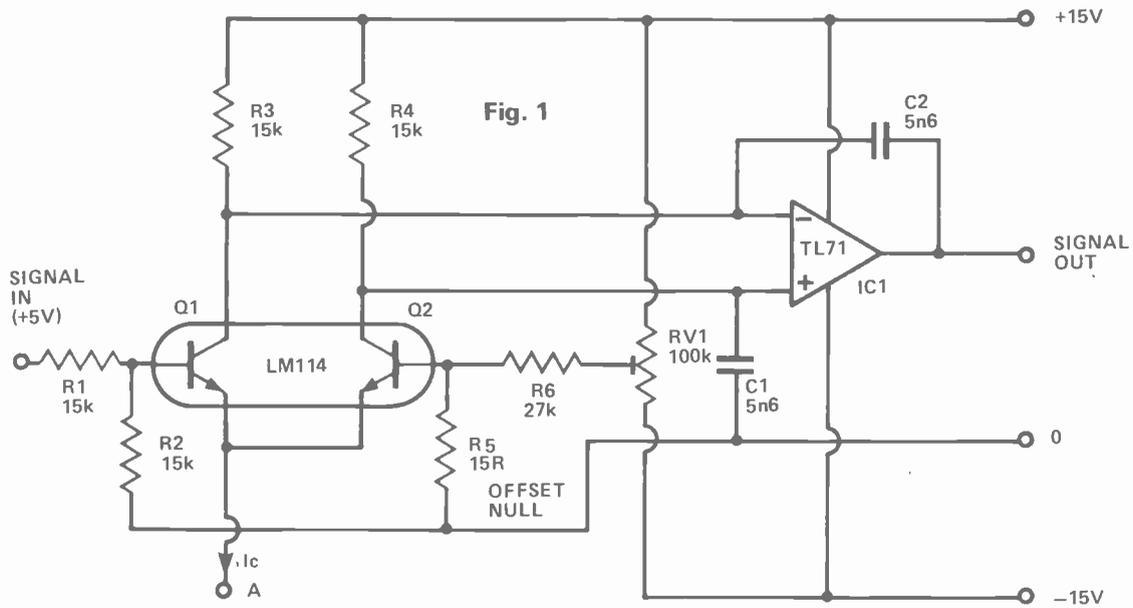Dept. ETI, Beaumont Centre, 164-167 East Rd., Cambridge CB1 1DB. Tel. 0223 312866



### Voltage Controlled Filter

T. W. Stride

The voltage controlled state variable filter has become almost standard in sound synthesizers, especially since the advent of the CA3080 transconductance amplifier. However, the

CA3080 is a reasonably noisy device and this can be annoying when large passbands and/or high Q values are being used in the filter. This circuit is for a low noise, high performance transconductance multiplier, which though not cheap, will offer a truly Hi-Fi performance.

R1 and R2 attenuate the input signal to keep distortion low, and Q1, Q2 with R3, R4 form the transconductance multiplier. The differential output current is integrated by means of IC1, C1 and C2, a differential integrator. RV1 is provided to cancel out the offset of Q1, Q2; it is best adjusted by sweeping the filter and adjusting for minimum DC output shift.

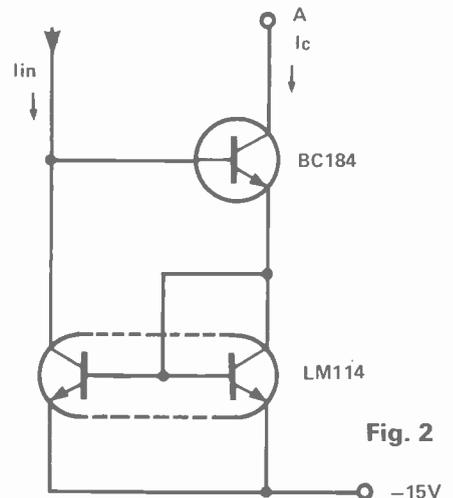


Fig. 2

As can be seen from Fig. 1, the gain of the integrator is controlled by a constant current IC. This current can be provided in two ways, either from a current mirror (Fig. 2) which then makes the circuit an almost exact replacement for the CA3080, or for original equipment designs, from a current source. If it is desired to use this circuit as a replacement for a CA3080 in, for example, the Transcendent 2000 synthesizer, the following modifications are necessary. The integrating capacitor on the output of the 3080 must be replaced with a 10 k resistor and the input attenuator on the above circuit is discarded. The control current that would flow into pin 5 of the 3080 is input to the current mirror and the output current is drawn from the transconductance multiplier (point A).

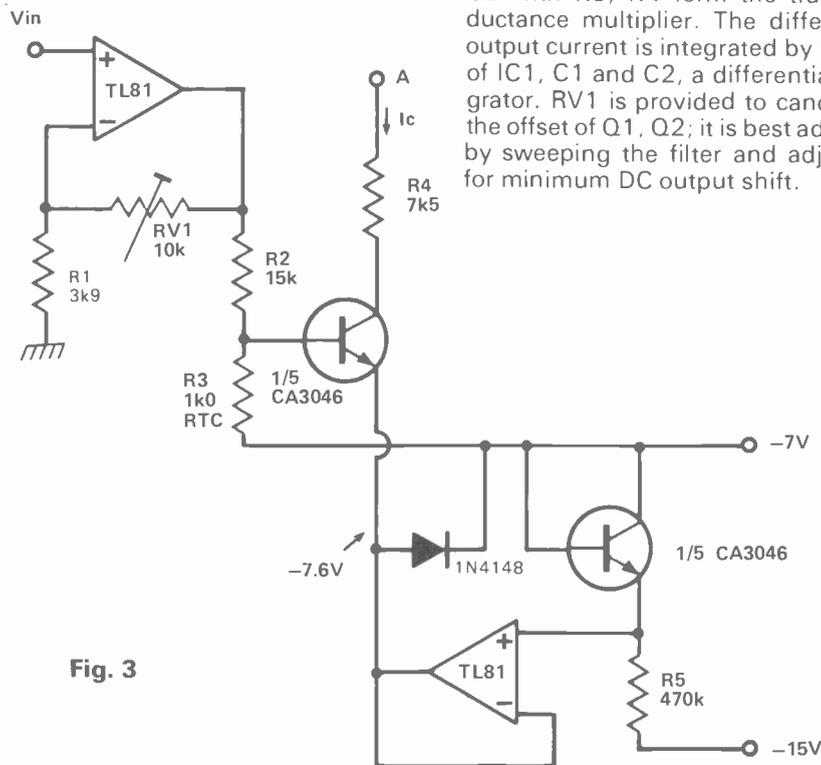


Fig. 3

# Codespeed Electronics

PO BOX 23, 34 SEAFIELD ROAD, COPNOR, PORTSMOUTH, PO3 5BJ  
ELECTRONIC MAIL ORDER SPECIALISTS  
New, Full Spec. Devices

- WRISTWATCH LCDs.** A high contrast 3 1/2 digit wristwatch LCD with centre colon. Supplied with polarizers and data. Only **£1.00**. Cat. No. 202
- MM5314 CLOCK CHIP.** A super value digital clock chip for only **£1.99**. With data Cat. No. 207
- 4 DIGIT LCD.** A high contrast, easy to solder display with four 0.5" high non-multiplexed digits. **£6.95** each with data. Cat. No. 206
- DIGITAL ALARM CLOCK MODULE.** Complete with giant 0.84" LED display. Add transformer and switches for complete clock. With data only **£6.50**. Cat. No. 205
- SLIDE SWITCHES.** A miniature slide switch with two pole change-over contacts. All brand new **15p** each. Cat. No. 702
- MOMENTARY SWITCHES.** Miniature spring loaded pushbutton switches with one normally open contact. Super value **15p** each. Cat. No. 703
- POLARIZING FILTER MATERIAL.** 0.006" thick plastic film. Any size cut — even 1 sq inch. Max width 1 1/2". Any length. Only **2p** per sq inch. Cat. No. 701
- PROGRAMMABLE UNIJUNCTIONS.** Four MEU21 PUTs (similar to 2N6027). Makes long delay timers, oscillators etc. With data and applications sheet. 4 for **50p**. Cat. No. 402
- MINI 6 DIGIT LED DISPLAY.** 6 digit 7 segment display from Texas. Common cathode multiplexed with 0.1" digits **£1.00**. Cat. No. 306
- DMM CHIP.** MM5330 dmm chip. Builds into high accuracy dvm or panel meter. Requires additional circuitry. Supplied with data and circuit. Only **£3.95**. Cat. No. 404
- GIANT LED DISPLAY.** Common cathode non-multiplexed super 4 digit LED clock display. Lots of other uses too. Only **£3.95** each. Cat. No. 204
- MINIATURE DIODES.** 25 mini 1N3470 germanium diodes (35v 600mA). Excellent value. 25 for **50p**. Cat. No. 401
- 20 KEY KEYBOARDS.** Calculator keyboards. Excellent key action. 20 keys per board. 2 keyboards for **£1.00**. Cat. No. 101
- 1 1/2 DIGIT DISPLAY.** Bright orange gas discharge display. 1 1/2 digits 0.25" high. With data only **50p**. Cat. No. 304
- MATRIXED SWITCHING DIODES.** 23 diodes on each 14 pin chip. Supplied with data sheet. 5 chips for **50p**. Cat. No. 504
- HIGH SPEED DIODES.** 1N4151 high speed switching diodes. Similar to 1N4148. 10 diodes for **35p**. Cat. No. 403
- 10 HYBRID CIRCUITS.** 8 resistors and 8 capacitors built into each hybrid circuit. Ideal values for semiconductor circuits. Excellent for minimizing PCB component space. 10 hybrids for **50p**. Cat. No. 801


### Untested Items

- LED DISPLAYS.** (Untested — no guarantee). 10 seven segment LED displays. 0.127" digits common cathode. 10 for **£1.00**. Cat. No. 311
- 30 MIXED ICs.** (Untested — no guarantee). Could include anything Linear or Digital. You test. Good value for **£1.00**. Cat. No. 503
- REJECT CALCULATORS.** Production line rejects. Yields lots of goodies when stripped down (not much wrong with some we tested). Only **£2.50** each. Cat. No. 104

A full refund guarantee on all items.

Post and packing please add 35p. (Overseas orders add 90p)  
Lots more goodies in our catalogue. Send a medium sized SAE for your free copy

## MORE SCOPE FOR YOUR MONEY

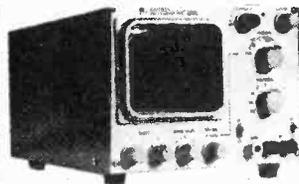


ELMAC 4" scope

### SPECIFICATIONS

**ELECTRICAL DATA VERTICAL AXIS (Y)** Deflection Sensitivity — 100mV/division. Bandwidth (between 3 dB points) — DC — 5MHz. Input Attenuator — (calibrated) — 9 step 0.1, 0.2, 0.5, 1, 2, 5, 10, 20, 50/div. Input impedance — 1 Meg/40 pf in shunt. Input Voltage — Max — 600V P.P. HORIZONTAL AXIS (X) Deflection Sensitivity — 0.400mV/division. Bandwidth (between 3 dB points) — 1Hz-350KHz. Gain Control — Continuous when time bases in EXT position. Input Impedance — 1 Meg. Input Voltage — Max — 500V P.P. TIME BASE. Sweep Range (calibrated) — 100msec/div to 1µsec/div in 5 steps. FINE Control — Variable between steps — includes time-base calibration position. Blanking — Internal — on all ranges.

**SYNCHRONISATION.** Selection — Internal external. Synchronisation Level — Continues from positive to negative. **POWER SUPPLY.** Input voltage — 115/200V AC ± 10% at 50/60Hz. Power Dissipation — 18W. **CRT DATA** — 4in. — flat face, single beam. — Maximum high voltage — 1.5kV. — Fitted with 8 x 10 division blue filter graticule. **PHYSICAL DATA** Dimensions — 15cm(h)x20.5cm(w)x28cm(d). Weight — 4.3Kg (approx). Stand — 2 position flat and inclined. Case — Steel, epoxy enamelled. Front panel — Aluminium enamelled epoxy printing.

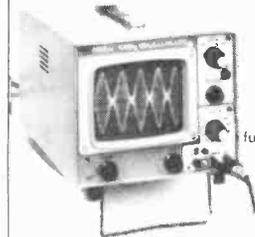Cash with order **Test leads available £2.00**  
**£109 (+ £16.35 VAT)** Barclaycard Access



3106C  
5" CRT

SAE for further details

### As recommended

### By Practical

### Wireless

### SPECIFICATION

Display: 8 X 10cm with 1cm graticule squares  
Tube: 130BE/P31  
EHT: 1.5kV  
**VERTICAL AMPLIFIER**  
Sensitivity: 10mV/cm to 50mV/cm in 12 steps  
Bandwidth: DC to 6MHz —3dB. DC to 10MHz —6dB  
Risetime: 55ns  
Input Impedance: 1MΩ and 30pF  
Input: 400V max  
**HORIZONTAL AMPLIFIER**  
Sensitivity: 720mV/cm to 50V/cm  
Bandwidth: DC to 1.5MHz —3dB  
X-Y Phase Shift: 5° d.c. to 50kHz  
**TIMEBASE**  
Range: 0.5µs/cm to 10ms/cm in 6 ranges  
Magnifier: X5 (100ms/cm fastest sweep speed)  
Calibration: 5%  
Vernier: 12:1 continuous  
Trigger Sensitivity: 1cm deflection 10Hz to 8MHz Automatic no manual controls  
Power Supplies: 100 to 135V and 200 to 265V  
48 440Hz 15W  
Dimensions: 182 x 200 x 405mm 4.5kg  
Accessories: Main test prods and leads, Handbook  
Price: £159.85 inc. 15% VAT and carriage

## KRAMER & CO.

9 October Place, Holders Hill Road  
London NW4 1EJ. Telex: 888941  
attn. Kramer k7. Tel: 01-203 2473  
Mail order only. Callers by appointment

Access: Barclaycard : Visa : Mastercharge

Ohio Scientifics

# SUPERBOARD III

Now only **£188** + VAT

Full 8K basic and 4K user RAM  
Power supply and R.F. Converter P.O.A.

Built and tested

( Delivery within 7 days)

### Features

- Uses the ultra powerful 6502 microprocessor
- 8K Microsoft BASIC-in-ROM
- Full feature BASIC runs faster than currently available personal computers and all 8080-based business computers.
- 4K static RAM on board expandable to 8K
- Full 53-key keyboard with upper-lower case and user programmability
- Kansas City standard audio cassette interface for high reliability
- Full machine code monitor and I/O utilities in ROM
- Direct access video display has 1K of dedicated memory (besides 4K user memory), features uppercase, lower case, graphics and gaming characters for an effective screen resolution of up to 256 by 256 points. Normal TV's with overscan display about 24 rows of 24 characters, without overscan up to 30 x 30 characters.

### Extras

- Available expander board features 24K static RAM (additional mini-floppy interface, port adapter for printer and modem and OSI 48 line expansion interface.
- Assembler/editor and extended machine code monitor available.

### Commands

Commands	LIST	NEW	NULL	RUN
Statements				
CLEAR	DATA	DEF	DIM	END FOR
GOTO	GOSUB	IF...GOTO	IF...THEN	INPUT LET
NEXT	ON...GOTO	ON...GOSUB	POKE	PRINT READ
REM	RESTORE	RETURN	STOP	

### Expressions

#### Operators

-, +, \*, /, ↑, NOT, AND, OR, >, <, <>, >=, <=, =  
RANGE 10<sup>-32</sup> to 10<sup>+32</sup>

### Functions

ABS(X)	ATN(X)	COS(X)	EXP(X)	FRE(X)	INT(X)
LOG(X)	PEEK(I)	POS(I)	RND(X)	SGN(X)	SIN(X)
SPC(I)	SQR(X)	TAB(I)	TAN(X)	USR(I)	

### String Functions

ASC(X\$)	CHR\$(I)	FRE(X\$)	LEFT\$(X\$,I)	LEN(X\$)	MID\$(X\$,I,J)
RIGHT\$(X\$,I)				STR\$(X)	VAL(X\$)

Plus variables, arrays and editing facilities.

Fully built and tested. Requires only +5V at 3 amps and a videomonitor or TV and RF converter to be up and running.

# LOTUS SOUND

4 MORGAN STREET  
LONDON E3 5AB

TELEPHONE: 01-981 3993  
TELEX: 261426 ATN.LOTUS SOUND

ELECTRONICS TODAY INTERNATIONAL — OCTOBER 1979

### 8K ON BOARD MEMORY!

5K RAM, 3K ROM or 4K RAM, 4K ROM (link selectable). Kit supplied with 3K RAM, 3K ROM. System expandable for up to 32K memory.

### 2 KEYBOARDS!

56 Key alphanumeric keyboard for entering high level language plus 16 key Hex pad for easy entry of machine code.

### GRAPHICS!

64 character graphics option — includes transistor symbols! Only £18.20 extra!

### MEMORY MAPPED

high resolution VDU circuitry using discrete TTL for extra flexibility. Has its own 2K memory to give 32 lines for 64 characters.

### KANSAS CITY

low error rate tape interface.

## COMPLETE KIT



Cabinet size 19.0" x 15.7" x 3.3" Television by courtesy of Rumblelows Ltd., price £58.62

### 2 MICROPROCESSORS

Z80 the powerful CPU with 158 instruction, including all 78 of the 8080, controls the MM57109 number cruncher. Functions include +, -, \*, /, squares, roots, logs, exponentials, trig functions, inverses etc. Range  $10^{-99}$  to  $9 \times 10^{99}$  to 8 figures plus 2 exponent digits.

### EFFICIENT OPERATION

Why waste valuable memory on sub routines for numeric processing? The number cruncher handles everything internally!

### RESIDENT BASIC

with extended mathematical capability. Only 2K memory used but more powerful than most 8K Basics!

### 1K MONITOR

resident in EPROM.

### SINGLE BOARD DESIGN

Even keyboards and power supply circuitry on the superb quality double sided plated through-hole PCB.

**ONLY  
£275.00  
+VAT**

# POWERTRAN


## PSI Comp 80. Z80 Based powerful scientific computer Design being published in Wireless World — NOW!

The kit for this outstandingly practical design by John Adams being published in a series of articles in Wireless World really is complete!

Included in the PSI COMP 80 scientific computer kit is a professionally finished cabinet, fibre-glass double sided, plated-through-hole printed circuit board, 2 keyboards PCB mounted for ease of construction, IC sockets, high reliability metal oxide resistors, power supply using custom designed toroidal transformer. 2K Basic and 1K monitor in EPROMS and, of course, wire, nuts, bolts, etc.
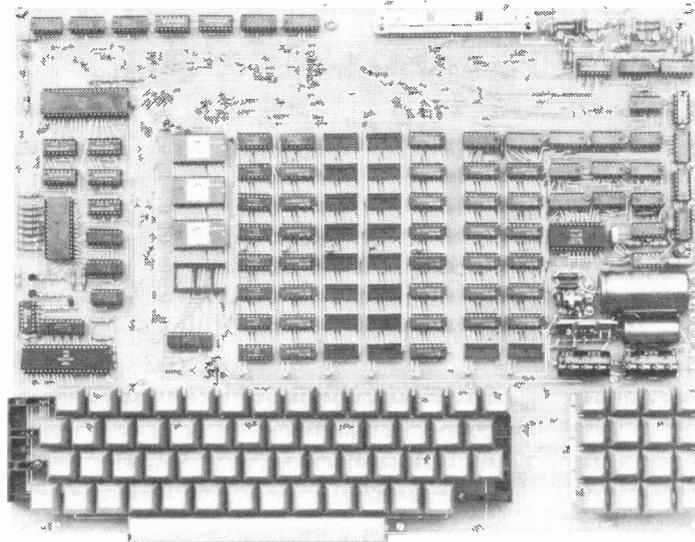
### SYSTEM EXPANSION COMING SHORTLY!

e.g.  
8K RAM Board  
8K ROM Board  
Prom Programmer  
Printer Interface  
etc.  
etc.



Kit also available as separate packs: e.g. PCB, Keyboards, Cabinet, etc.

PCB size 16.0" x 12.5"

### Value Added Tax not included in prices

**PRICE STABILITY:** Order with confidence. Irrespective of any price changes we will honour all prices in this advertisement until November 30th, 1979, if this month's advertisement is mentioned with your order. Errors and VAT rate changes excluded.

**EXPORT ORDERS:** No VAT. Postage charged at actual cost plus 50p handling and documentation.

**U.K. ORDERS:** Subsequent to 15% surcharge for VAT. No charge is made for carriage. \*Or current rate if changed.

**SECURICOR DELIVERY:** For this optional service (U.K. mainland only) add £2.50 (VAT inclusive) per kit.

### UK Carriage FREE

# POWERTRAN COMPUTERS

(a division of POWERTRAN ELECTRONICS)

PORTWAY INDUSTRIAL ESTATE

ANDOVER HANTS SP10 3NM

ANDOVER

(0264) 64455

ACCESSORIES ARE ONLY AVAILABLE TO THOSE CUSTOMERS WHEN BUYING OUR BARGAIN PACKS.

# Mullard

## AUDIO MODULES IN BARGAIN PACKS

### CURRENT CATALOGUE PRICE £ AT OVER 25 PER PACK

### SEE OUR PRICES

- 1 PACK 1 2 x LP1173 10w RMS output power audio amp modules, + 1 LP1182/2 Stereo pre amp for ceramic and auxiliary input. **OUR PRICE £5.00** p+p £1.00
- 2 PACK 2 2 x LP1173 10w RMS output power audio amp modules + 1 LP1184/2 Stereo pre amp for magnetic, ceramic and auxiliary inputs. **OUR PRICE £7.65** p+p £1.00


#### ACCESSORIES

Suitable mains power supply parts, consisting of mains transformer, bridge rectifier, smoothing capacitor and set of rotary stereo controls for treble, bass, volume and balance. **£3.00** plus £1.50 p&p
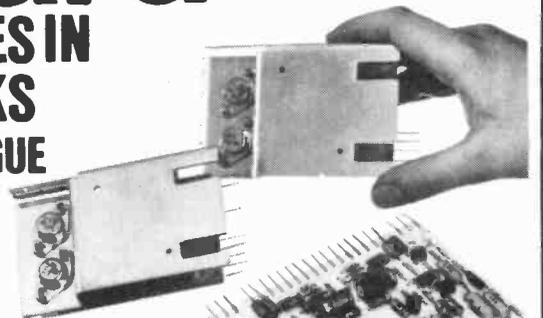
#### Two Way Speaker Kit

Comprising of two 8" x 5" approx. 4 ohm bass and two 3 1/2" 15 ohm mid-range tweeter with two cross-over capacitors. **£4.05** per stereo pair plus £1.55 p&p

AVAILABLE ALSO TO PURCHASERS OF THE 10 + 10 AMPLIFIER KIT



**20 x 20 WATT STEREO AMPLIFIER**  
Viscount IV unit in teak simulate cabinet Silver finish rotary controls and pushbuttons with matching fascia, red mains indicator and stereo jack socket. Functions switch for mic magnetic and crystal pickups, tape tuner and auxiliary. Rear panel features fuse holder, DIN speaker and input sockets. 20 x 20 watts RMS 40 x 40 watts peak for use with 8 to 15 ohm speakers. Size 14 1/2" x 3" x 10" approx. **NEW** feature—units now includes a built in four channel stereo sound facility. **£31.90** p&p £3.00

#### 30x30 WATT AMPLIFIER IN KIT FORM

For the experienced constructor complete in every detail, same facilities as Viscount IV, but with 30x30 output 60x60 watts peak. For use with 4 to 15 ohms speakers. **£31.50** p&p £3.00



#### SPECIAL OFFER

**30 x 30 WATT AMPLIFIER KIT** with BSR P200 belt drive deck and Shure M75 cartridge. **£57.00** + p&p £6.00

#### EMI SPEAKER BARGAIN

Stereo pair 350 kit. System consists of 13" x 8" approx. woofer with rolled surround, 2 1/2" approx. Audax tweeter, crossover components and circuit diagram. Frequency response 20 Hz to 20 KHz. Power handling 15 watts RMS. 20 watts max. 8 ohm impedance. **£15.25** Per stereo pair **£3.65** p&p



#### BSR P200


Belt drive chassis turntable unit semi-automatic, cueing device. **£25.50** p&p £2.60  
A D.C. QLM 30 Mk III Magnetic Cartridge to suit. **£7.95**



**BSR** Manual single play record deck with auto return and cueing lever. Fitted with stereo ceramic cartridge 2 speeds with 45 r.p.m. spindle adaptor ideally suited for home or disco use. **OUR PRICE £11.25** p&p £2.75

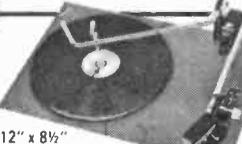
#### GARRARD DECK MODEL CC 10A

Record changer with cueing device fitted with stereo ceramic cartridge ready to fit into your own plinth. **£8.15** p&p £2.05 Size 12" x 8 1/2"


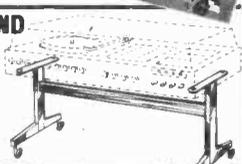
#### UNIT AUDIO STAND

Can be used with TV too! Finish in chrome with decorative wood spacer fitted with 4 Kenrick Mini Meteor castors. **£3.95** p&p £1.50 approx. **£11.50** p&p £1.50 approx. Size 24" x 12 1/2" x 11 1/2"



**BARGAIN FOR PERSONAL SHOPPERS ONLY**  
**Altone UA4 Stereo System**  
Features 8 watt total output. Full size BSR manual turntable with cueing and auto return. Socket for tape in and out and stereo headphones. **£35.75** complete with speakers.



**Micro Cassette Recorder**  
Pocket size—home or office use or when travelling. **£14.25**

**Battery operated fluorescent camping lamp.**  
Runs off 8 U2 batteries. **£4.80**

#### 10 + 10 AMPLIFIER KIT

An opportunity to buy a 10 watts per channel stereo amplifier kit which is suitable for use with a ceramic cartridge. The amplifier utilises proven Mullard modules and is available at a very competitive price. The amplifier kit comes complete with instructions and includes: a Mullard LP1183 stereo preamplifier module, two LP1173 power amplifiers with integral heatsinks, a power supply, Zobel networks, front and back mounting panels, a finished fascia panel, all control potentiometers (bass, treble, volume and balance), switches, input, output and headphone sockets, wire, and an easily assembled wrap around cabinet to house the finished unit. Size approximately 9 1/4" x 8 1/4" x 4". **£12.25** p&p £2.25



#### BARGAINS FOR PERSONAL SHOPPERS

- LCD Solar 5 function with backlite stainless steel finish case and strap **£7.40**
- LCD Solar Chrono 9 function with backlite stainless steel finish case and strap **£9.55**
- Chrono stop watch 9 function with back lite stainless steel finish case and strap. **£8.95**
- Solar Alarm LCD stainless steel case and strap. **£21.95**
- AM/FM DIGITAL CLOCK RADIO Accurate 4 Digit Electronic Clock with 1/2" LED display Buzzer and snooze timer **£12.20**

- 100 Watt Power Amp Module **£14.25**
- Mains power supply for above unit **£3.60**
- DECCA 20w Stereo speaker kit comprising 2 8" approx. bass units + 2 3 1/2" approx. tweeter inc crossovers **£20.45**
- 'VIDEOMASTER' Super Score TV Game with pistol mains operation **£15.95**
- PORTABLE RADIO/CASSETTE RECORDER, AM/FM with clock LW, MW, SW, VHF mains/battery operation **£42.90**
- ISP Radio Cassette recorder Mains/Battery AM/FM built in mic auto stop. **£24.50**



323 EDGWARE ROAD, LONDON W2  
21E HIGH STREET, ACTON W3 6NG

ACTON: Mail Order only. No callers  
ALL PRICES INCLUDE VAT AT 15%  
All items subject to availability. Price correct at 1.8.79 and subject to change without notice.

NOTE: Persons under 16 years not served without parent's authorisation.


#### 100 WATT MONO DISCO AMP

Size approx. 14" x 4" x 10 1/2"  
Brushed aluminium fascia and rotary controls. Five vertical slide controls, master volume, tape level, mic level, deck level. L PLUS INTER DECK FADER for perfect graduated change from record deck No. 1 to b No. 2, or vice versa. Pre fade level control (PFL) lets YOU hear next disc before fading it in. VU meter monitors output level. Output 100 watts RMS 200 watts peak. **£66.45** p&p £4.05


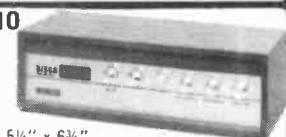
#### 50 WATT MONO DISCO AMP

**£30.60** p&p £2.70  
Size approx. 13 3/8" x 5 1/4" x 6 3/4"  
50 watts rms. 100 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with integral push-pull switches. Independent bass and treble controls and master volume.



#### FOR PERSONAL SHOPPERS ONLY

##### DUO II SPEAKERS

Attractive teak finish, modern design, incorporating 2 speaker units—8" approx. woofer and 2 1/2" approx. tweeter. 45 to 1800 Hz Impedance 8 ohms. Power 15 watts RMS. 18 1/2" x 13 1/2" x 7 1/2". Per stereo pair approx. **£16.50**



#### FOR PERSONAL SHOPPERS ONLY

##### STEREO RADIOGRAM CABINET

Finished in a natural teak veneer with opening top. Easily modified to accommodate stereo equipment of your choice. Price **£10.95**  
Size approximately 47" x 15 1/2" x 15"

Personal Shoppers EDGWARE ROAD LONDON W2 Tel: 01-723 8432. 9.30am-5.30pm. Closed all day Thursday ACTON: Mail Order only. No callers GOODS DESPATCHED TO MAINLAND AND N. IRELAND ONLY

DIODES/ZENERS			
QTY.			
1N914	100v	10mA	.05
1N4005	600v	1A	.08
1N4007	1000v	1A	.15
1N4148	75v	10mA	.05
1N4733	5.1v	1 W Zener	.25
1N4749	24v	1W	.25
1N753A	6.2v	500 mW Zener	.25
1N758A	10v	"	.25
1N759A	12v	"	.25
1N5243	13v	"	.25
1N5244B	14v	"	.25
1N5245B	15v	"	.25
1N5349	12v	3W	.25

SOCKETS/BRIDGES			
QTY.			
8-pin	pcb	.16 ww	.35
14-pin	pcb	.20 ww	.40
16-pin	pcb	.25 ww	.45
18-pin	pcb	.30 ww	.95
20-pin	pcb	.35 ww	1.05
22-pin	pcb	.40 ww	1.15
24-pin	pcb	.45 ww	1.25
28-pin	pcb	.50 ww	1.35
40-pin	pcb	.55 ww	1.45
Molex pins	.01 To-3 Sockets		.35
2 Amp Bridge	100-prv		.95
25 Amp Bridge	200-prv		1.50

TRANSISTORS, LEADS, etc.			
QTY.			
2N2222M	(2N2222 Plastic .10)		.15
2N2222A			.19
2N2907A	PNP		.19
2N3906	PNP (Plastic)		.19
2N3904	NPN (Plastic)		.19
2N3054	NPN		.55
2N3055	NPN 15A 60v		.60
T1P125	PNP Darlington		1.95
LED Green,	Red, Clear, Yellow		.19
D.L.747	7 seg 5/8" High com-anode		1.95
MAN72	7 seg com-anode (Red)		1.25
MAN3610	7 seg com-anode (Orange)		1.25
MAN82A	7 seg com-anode (Yellow)		1.25
MAN74	7 seg com-cathode (Red)		1.50
FND359	7 seg com-cathode (Red)		1.25

9000 SERIES			
QTY.		QTY.	
9301	.85	9322	.65
9309	.50	9601	.30
		9602	.45

MICRO's, RAMS, CPU's, E-PROMS	
QTY.	
8T13	2.50
8T23	2.50
8T24	3.00
8T97	1.75
74S188	3.00
1488	1.25
1489	1.25
1702A	4.50
AM 9050	4.00
ICM 7207	6.95
ICM 7208	13.95
MPS 6520	10.00
MM 5314	4.00
MM 5316	4.50
MM 5387	3.50
MM 5369	2.95
TR 1602B	3.95
UPD 414	4.95
Z 80 A	22.50
Z 80	17.50
Z 80 P10	10.50
2102	1.45
2102L	1.75
2107B-4	4.95
2114	9.50
2513	6.25
2708	11.50
2716 D.S.	34.00
2716 (5v)	69.00
2758 (5v)	26.95
3242	10.50
4116	11.50
6800	13.95
6850	7.95
8080	7.50
8085	22.50
8212	2.75
8214	4.95
8216	3.50
8224	4.25
8228	6.00
8251	7.50
8253	18.50
8255	8.50
TMS 4044	9.95

- T T L -				4.1-79	
QTY.		QTY.		QTY.	
7400	.20	7492	.45	74H20	.25
7401	.20	7493	.35	74H21	.25
7402	.20	7494	.75	74H22	.40
7403	.20	7495	.60	74H30	.30
7404	.20	7496	.80	74H40	.35
7405	.35	74100	1.15	74H50	.30
7406	.25	74107	.35	74H51	.30
7407	.55	74121	.35	74H52	.20
7408	.20	74122	.55	74H53	.25
7409	.25	74123	.55	74H55	.25
7410	.20	74125	.45	74H72	.35
7411	.25	74126	.45	74H74	.35
7412	.25	74132	.75	74H101	.95
7413	.45	74141	.90	74H103	.55
7414	.75	74150	.85	74H106	1.15
7416	.25	74151	.95	74L00	.30
7417	.40	74153	.95	74L02	.30
7420	.25	74154	1.15	74L03	.35
7426	.25	74156	.70	74L04	.40
7427	.25	74157	.65	74L10	.30
7430	.20	74161/9316	.75	74L20	.45
7432	.30	74163	.85	74L30	.55
7437	.20	74164	.75	74L47	1.95
7438	.30	74165	1.10	74L51	.65
7440	.20	74166	1.75	74L55	.85
7441	1.15	74175	.90	74L72	.65
7442	.55	74176	.95	74L73	.70
7443	.45	74177	1.10	74L74	.75
7444	.45	74180	.95	74L75	1.05
7445	.75	74181	2.25	74L85	2.00
7446	.70	74182	.75	74L93	.75
7447	.70	74190	1.25	74L123	1.95
7448	.50	74191	1.25	74L500	.40
7450	.25	74192	.75	74LS01	.40
7451	.25	74193	.85	74LS02	.45
7453	.20	74194	.95	74LS03	.45
7454	.25	74195	.95	74LS04	.45
7460	.40	74196	.95	74LS05	.45
7470	.45	74197	.95	74LS08	.45
7472	.40	74198	1.45	74LS09	.45
7473	.25	74221	1.50	74LS10	.45
7474	.30	74298	1.50	74LS11	.45
7475	.35	74367	1.35	74LS20	.45
7476	.40	75491	.65	74LS21	.45
7480	.75	75492	.65	74LS22	.45
7481	.85	74H00	.20	74LS32	.50
7482	.95	74H01	.30	74LS37	.45
7483	.95	74H04	.30	74LS38	.65
7485	.75	74H05	.25	74LS40	.70
7486	.55	74H08	.35	74LS42	.95
7489	1.05	74H10	.35	74LS51	.75
7490	.55	74H11	.25	74LS74	.95
7491	.70	74H15	.45	74LS75	1.20

C MOS					
QTY.		QTY.		QTY.	
4000	.15	4017	.75	4034	2.45
4001	.20	4018	.75	4035	.75
4002	.25	4019	.35	4037	1.80
4004	3.95	4020	.85	4040	.75
4006	.95	4021	.75	4041	.69
4007	.25	4022	.75	4042	.65
4008	.75	4023	.25	4043	.50
4009	.35	4024	.75	4044	.65
4010	.35	4025	.25	4046	1.25
4011	.30	4026	1.95	4047	2.50
4012	.25	4027	.35	4048	1.25
4013	.40	4028	.75	4049	.65
4014	.75	4029	1.15	4050	.45
4015	.75	4030	.30	4052	.75
4016	.35	4033	1.50	4053	.95
				4066	.75
					74C151 2.50

I <sup>2</sup> L, LINEARS, REGULATORS, ETC.			
QTY.		QTY.	
MCT2	.95	LM320K24	1.65
8038	3.95	LM320T5	1.65
LM201	.75	LM320T12	1.65
LM301	.45	LM320T15	1.65
LM308	.65	LM323K	5.95
LM309H	.85	LM324	1.25
LM309 (340K-5)	1.50	LM339	.75
LM310	.85	7805 (340T5)	1.15
LM311 (8-14 Pin)	.75	LM340T12	.95
LM318	1.50	LM340T15	.95
LM320H6	.79	LM340T18	.95
LM320H15	.79	LM340T24	.95
LM320H24	.79	LM340K12	1.25
7905 (LM320K5)	1.65	LM340K15	1.25
LM320K12	1.65	LM340K18	1.25
LM320K15	1.65	LM340K24	1.25

LM3900	.95
LM75451	.65
NE555	.45
NE556	.85
NE565	1.15
NE566	1.25
NE567	.95
TA7205	6.95
76477	2.95
95H90	9.95

CABLE ADDRESS: ICUSD

Telex #697-827 ICUSD SDG

HOURS: 9 A.M. - 6 P.M. MON. thru SUN.

## INTEGRATED CIRCUITS UNLIMITED

7889 Clairemont Mesa Blvd. • San Diego, California 92111 U.S.A.

NO MINIMUM

COMMERCIAL AND MANUFACTURING ACCOUNTS INVITED

ALL PRICES IN U.S. DOLLARS. PLEASE ADD POSTAGE TO COVER METHOD OF SHIPPING.  
ORDERS OVER \$100 (U.S.) WILL BE SHIPPED AIR NO CHARGE.

PAYMENT SUBMITTED WITH ORDER SHOULD BE IN U.S. DOLLARS.

ALL IC'S PRIME/GUARANTEED ALL ORDERS SHIPPED SAME DAY RECEIVED.




CREDIT CARDS ACCEPTED:


Phone (714) 278-4394 BarclayCard / Access / American Express / BankAmericard / Visa / MasterCharge

Total Order	Deduct
\$35-\$99	10%
\$100-\$300	15%
\$301-\$1000	20%


SPECIAL DISCOUNTS

# PCB FOIL PATTERNS

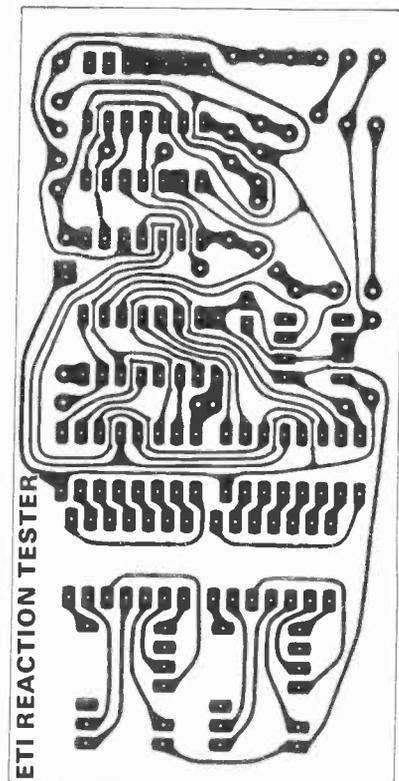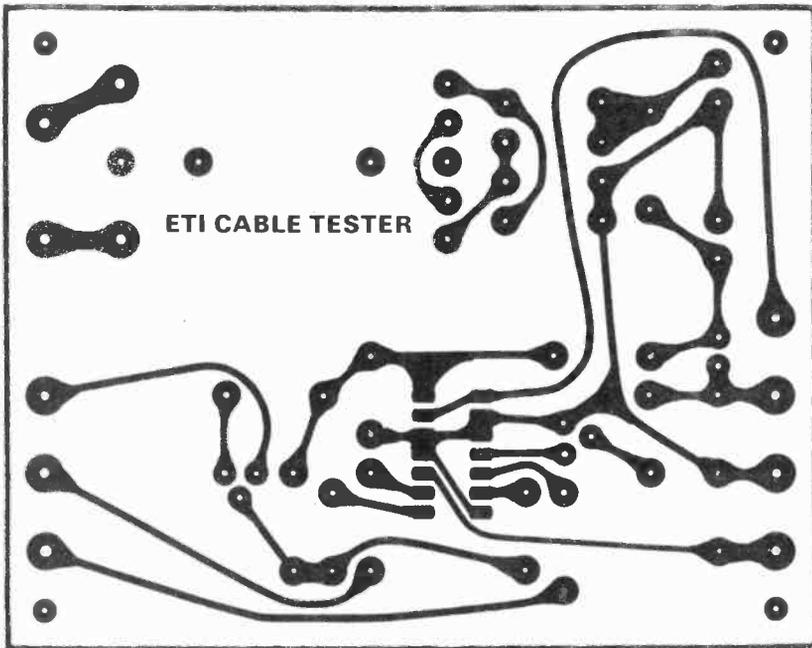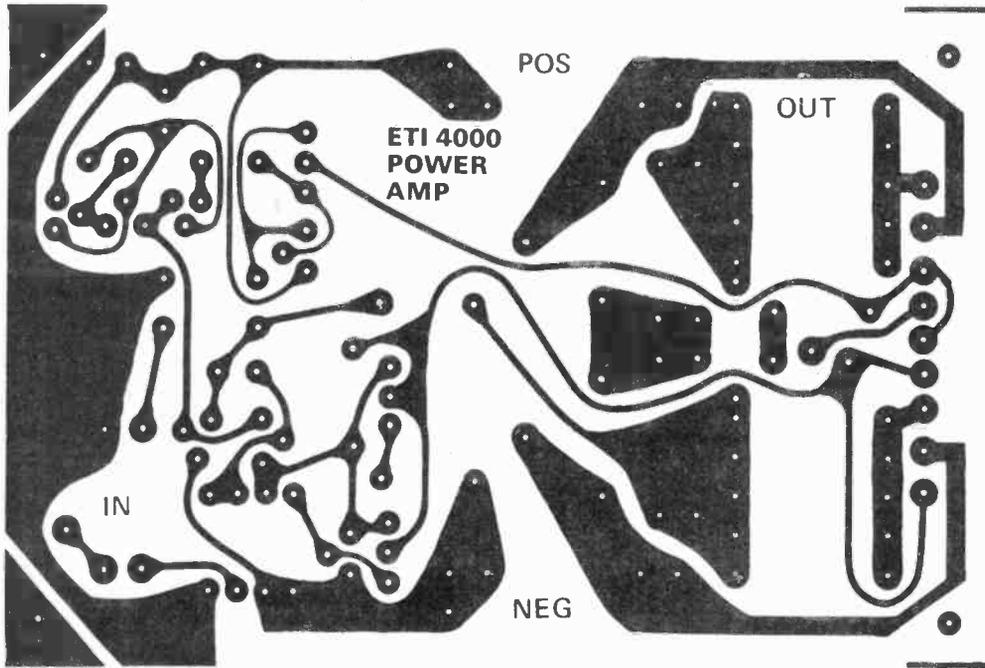


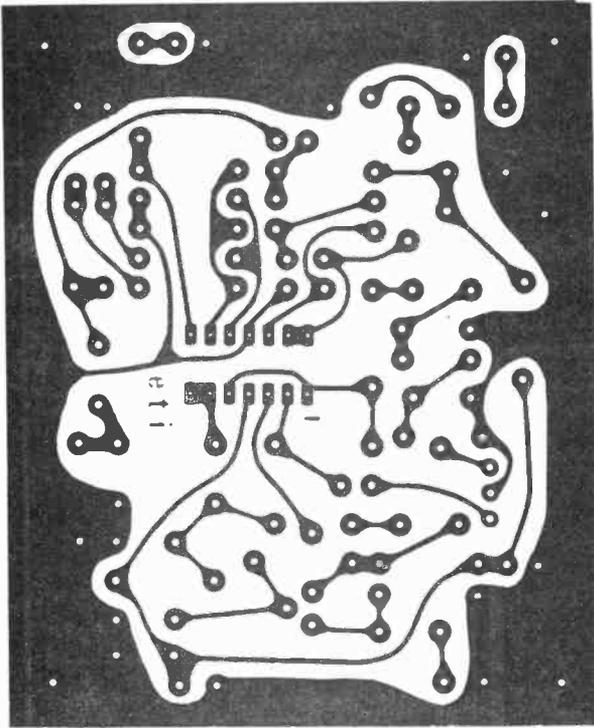

ETI SPEECH COMPRESSOR

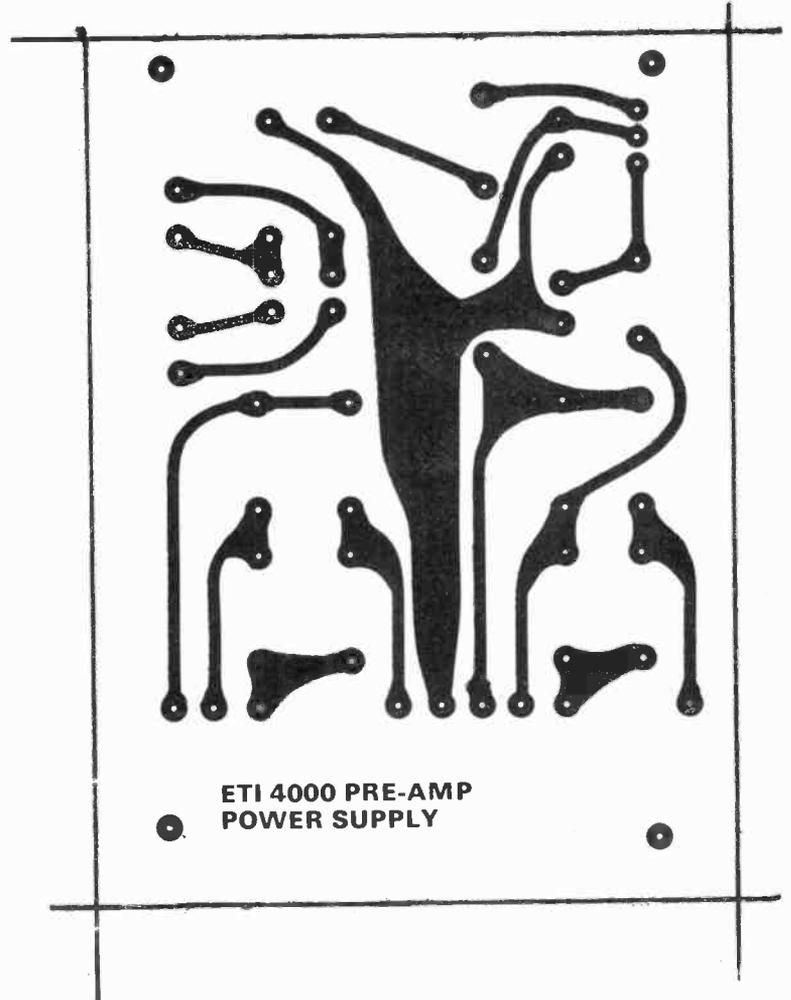

ETI 4000 PRE-AMP  
POWER SUPPLY

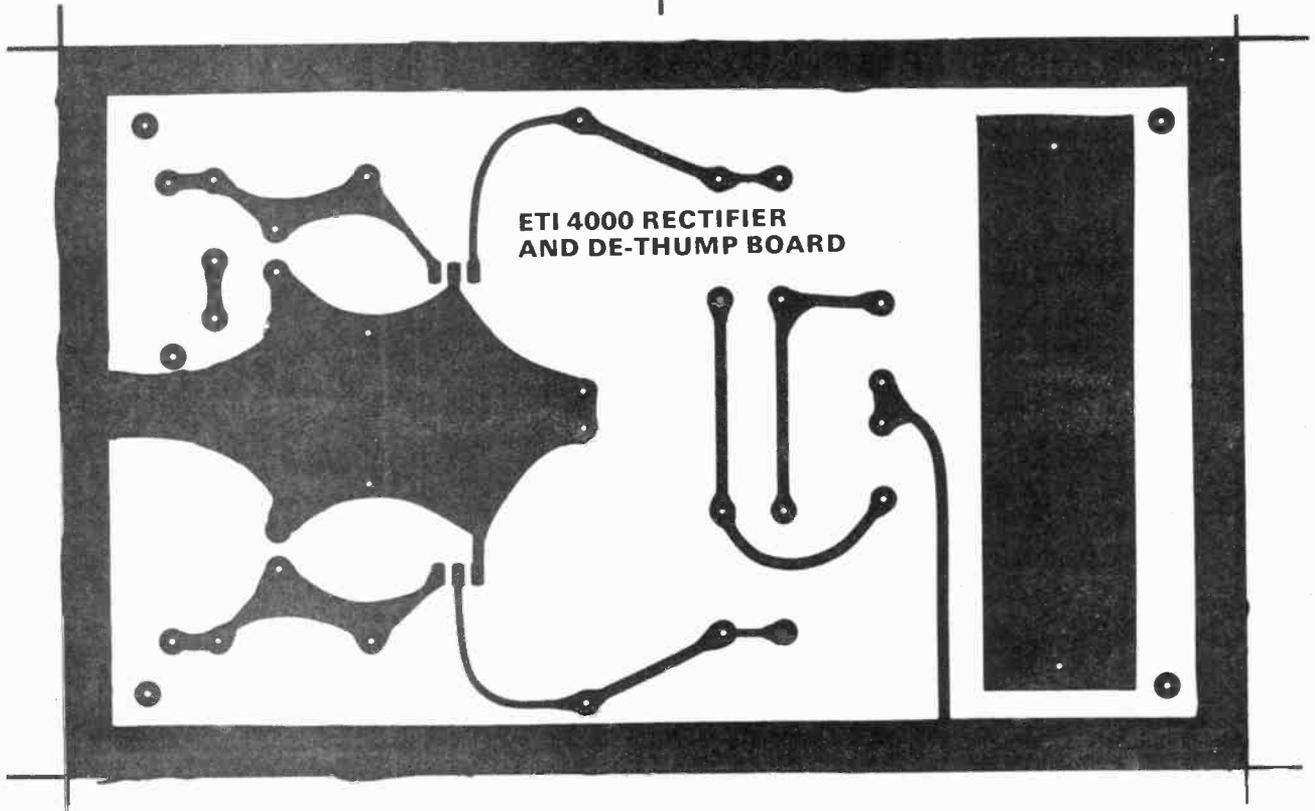

ETI 4000 RECTIFIER  
AND DE-THUMP BOARD

# THE ARAK VIII POLYPHONIC KEYBOARD CONTROLLER



The Arak VIII is so named because it can handle up to eight note polyphony, and that means that if you have a large enough synthesizer you can play eight notes at once, and each one can be set to sound totally different.

The Arak VIII is a controller in every sense of the word. For instance it has built in vibrato so you don't waste those precious V.C.O.s. You can instantly get back to that fat monophonic sound by flicking the unison switch. Just touch the keys with infinite sustain selected and the Arak VIII brings in a big power chord while you get on with playing another instrument. Memorising a chord is no problem using the memory bank facility. You can even sequence between two chords set in the memory banks and interact with them from the keyboard. We designed the Arak VIII to interface with just about anything, apart from the gate and control voltage outputs, which incidentally, can be scaled between zero and two volts per octave, there is an I/O so you can interface it to a computer. This allows a computer to take data from the Arak VIII or feed data in and control the synth.

The case is hand-built out of black anodised aluminium and is finished off with solid mahogany end cheeks. Legends are silk screened on the front and back so you know precisely what to twiddle and what to plug into.

Arak VIII kit ..... £248.39  
Arak VIII ready-built and tested ..... £382.22  
PCB set ..... £25.40

Prices include VAT

\*Four more store / portamento circuits are needed to give the necessary number of control voltages.

**ARAK SOUND**  
PRESTON HOUSE, HIGH STREET  
CROWTHORNE, BERKS.



# Wilmslow Audio

**THE firm for speakers!**

Send 15p stamp for the world's best catalogue of  
Speakers, Drive Units, Kits, Crossovers, etc., and  
discount price list.

● AUDAX ● BAKER ● BOWERS & WILKINS ●  
CASTLE ● CELESTION ● CHARTWELL ● COLES ●  
DALESFORD ● DECCA ● EMI ● EAGLE ● ELAC ●  
FANE ● GAUSS ● GOODMAN'S ● I.M.F. ●  
ISOPHON ● JR ● JORDAN WATTS ● KEF ● LEAK ●  
LOWTHER ● MCKENZIE ● MONITOR AUDIO ●  
PEERLESS ● RADFORD ● RAM ● RICHARD ALLAN ●  
SEAS ● TANNOY ● VIDEOTONE ●  
WHARFEDALE ● SHACKMAN ● AUDIOMASTER ●  
TANGENT ● STAG ● YAMAHA

**WILMSLOW AUDIO Dept. ETI**

SWAN WORKS, BANK SQUARE, WILMSLOW  
CHESHIRE SK9 1HF

Discount HiFi, etc., at:  
5 Swan Street

TEL. WILMSLOW 529599 FOR SPEAKERS  
WILMSLOW 526213 FOR HI-FI

# Romane Electronics

## INTRODUCTORY OFFER

### LOW POWER SCHOTTKY TTL EX-STOCK

We are holding substantial stocks of the Devices listed below. All orders, large and small, will be dealt with in strict rotation. Please add 15% V.A.T. to all orders plus 30p for P&P. Export orders no VAT but postage at cost air/surface. Prompt delivery on all orders.

Description	Price				
74LS00	13p	74LS78	40p	74LS175	92p
74LS01	14p	74LS83	90p	74LS190	88p
74LS02	13p	74LS85	75p	74LS191	88p
74LS03	14p	74LS86	31p	74LS192	100p
74LS04	15p	74LS90	42p	74LS193	100p
74LS05	25p	74LS93	51p	74LS195	110p
74LS08	16p	74LS95	75p	74LS196	80p
74LS09	20p	74LS107	36p	74LS197	100p
74LS10	16p	74LS109	36p	74LS221	120p
74LS11	21p	74LS112	38p	74LS244	200p
74LS12	23p	74LS113	38p	74LS245	250p
74LS13	34p	74LS114	38p	74LS247	92p
74LS14	70p	74LS123	60p	74LS248	92p
74LS15	22p	74LS125	40p	74LS249	90p
74LS20	15p	74LS126	40p	74LS251	85p
74LS21	22p	74LS132	70p	74LS273	200p
74LS22	22p	74LS136	32p	74LS279	85p
74LS26	24p	74LS138	70p	74LS283	70p
74LS27	25p	74LS139	70p	74LS290	68p
74LS28	30p	74LS151	55p	74LS293	88p
74LS30	19p	74LS153	55p	74LS298	90p
74LS32	24p	74LS155	80p	74LS352	98p
74LS37	22p	74LS156	94p	74LS353	98p
74LS38	25p	74LS157	55p	74LS365	95p
74LS40	21p	74LS158	55p	74LS366	95p
74LS47	80p	74LS160	110p	74LS367	95p
74LS48	92p	74LS161	74p	74LS368	95p
74LS49	95p	74LS162	118p	74LS374	150p
74LS73	29p	74LS163	70p	74LS386	30p
74LS74	32p	74LS164	95p	74LS670	170p
74LS75	38p	74LS173	90p		
74LS76	36p	74LS174	90p		

### LOW PROFILE DIL SOCKETS BY TEXAS

8 Pin	13p	18 Pin	25p	24 Pin	33p
14 Pin	14p	20 Pin	27p	28 Pin	43p
16 Pin	16p	22 Pin	28p	40 Pin	53p

A full range of breadboards, I.C. test clips, ribbon cable assemblies (mostly ex-stock). Send large s.a.e. for catalogue and price lists.

Cheques, P.O.s, Cash etc. should be made payable to:

## ROMANE ELECTRONICS

64 Newlyn Drive, Sale, Cheshire. M33 3LE  
Tel. 061-962 2606

# MINI-ADS & CLASSIFIED

## FOR NASCOM 1 IN SCOTLAND SEE STRATHAND

In stock now:  
Nascom 1  
Buffer Boards  
8, 16, 32K Ram Boards  
Super Tiny Basic  
Zeap on tape

### 8K Basic on Tape

High speed cassette interface professional T.V. Monitor in kit form and other products arriving daily.

Please note it is not our policy to advertise Nascom products which are not currently available.

### STRATHAND


44 St. Andrew's Sq.  
Glasgow G1 5PL  
041-552 6731 or 2

Access and Barclaycard sales welcome  
Callers welcome 9-5 Monday to Friday


## BARGAINS FOR THE ELECTRONIC HANDYMAN BRANDED LED DIGITAL ALARM CLOCKS



(1)

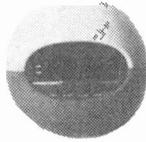

(2)

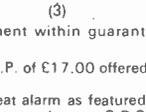

(3)

Returned to Service Department within guarantee period.

- (1) With alarm repeat — S.R.S.P. of £17.00 offered at **£3.95** inc. VAT
- (2) With luxury lamp and repeat alarm as featured in most major U.K. Mail Order catalogues, S.R.S.P. £31.00—offered at **£7.95** inc. V.A.T.
- (3) With integral luxury light and repeat alarm also as featured in most major U.K. Mail Order catalogues, S.R.S.P. of £32.00—offered at **£7.45** inc. V.A.T.

These will be sold as received from our customers with the existing fault(s) and without guarantee.

Discounts available on large bulk purchases

**PRESCOTT CLOCK AND  
WATCH COMPANY LIMITED**

Prescott House, Humber Road, London NW2 6ER

## TIME WRONG?

**MSF 60KHz TIME RECEIVER**, data and audio outputs, built-in antenna, 1000Km range **£13.70**  
**FRG77 NO RADIO 47** Get all the NEWS with a 200KHz to Medium Wave Converter **£11.40**  
**SIG. GEN.**, 10Hz-200KHz, logic and variable sine or square wave outputs, linear frequency scale **£10.80**  
**V.L.F.7 EXPLORE 10-150KHz**, Receiver only **£10.70**  
**INTERFERENCE?** Get rid of whistles, etc. with a Tunable Audio Notch Filter, 350-5000Hz **£8.90**

Each fun-to-build kit includes all parts, printed circuit, case, instructions, postage, etc.; money-back assurance; so SEND off NOW.

### CAMBRIDGE KITS

45 (TX) Old School Lane, Milton, Cambridge

**ASSEMBLED KEYBOARDS** to your requirements: 20 low-bounce key-switches on PCB, 5x4 format. Labelling to your specification or standard hexadecimal. Suitable for Mk. 14. £7.90. T. Davy, Electronics Today International, Box No. 101, Advertisement Dept., 145 Charing Cross Road, London WC2H 0EE.

**MEMORY ERASURE SERVICE.** 40p per Eprom plus £1 per order inclusive. Please ensure that EPROMS are adequately packaged when posting. Harris, Glanrafon, Llanfallteg, Whitland, Dyfed, Wales.


**A SUPERB QUALITY STEREO POWER AMPLIFIER OFFER!** Protected output of 60w (RMS-8Ω) Stereo via din socks. Case inc., controls vol., select etc., Power Smoothing, 12/35v wkg. 0.03% Thd, 22 trans., 1 amp drivers — 90.w plastic outputs. Tested — Boxed — data £10.50. Queries s.a.e. please. Klifco Electronics, 1 Regent Road, Ilkley, W. Yorks LS29 9EA.

**CM2506 DIGITAL CAPACITANCE METER** 1pF-2μF, 5 ranges on-board switch, 2½ digits, 0.6" leds; acc. 0.5%. Assembled module only £20.75 + VAT. Precision Measurements. P.O. Box 70, 8 St Stephens Ct., Canterbury, Kent (Callers by appointment).

**VHF/FM TRANSMITTER KIT.** New silicon chip design means low price (beats anyone else) and better performance. Very small — ideal bug, etc. . . . Fully tuneable 88-108 MHz. Instructions, etc., all included. **INTRODUCTORY OFFER** £1.95 + 30p P&P (unlicensable). M. Henry, Dept. ET1, 30 Westholme Gardens, Ruislip.

STOP PRESS: UK 101 Compatible!

## COLOUR YOUR NASCOM!

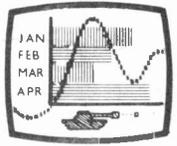

### DAZZLING COLOUR GRAPHICS FOR NASCOM 1

Genuine bit-addressable "pixel" system for straightforward programming of pictorial or mathematical functions.

8 Colour display plus 8 colour independent background facility. Full documentation with **FREE SOFTWARE**: powerful sub-routines for vector generation, demonstration program for animated effects. All runs in Nascom 1 without expansion. Complete with UHF Colour Modulator for operation with normal colour TV set. Superior design allows connection to most other micro-processor systems — send us diagrams etc of your b & w video circuitry for free advice. Don't be fooled by the price: this is a top quality product which will transform your computer.

NOW AVAILABLE FOR **£45** inclusive of VAT and postage.  
LIMITED PERIOD AT

**WILLIAM  
STUART  
SYSTEMS Ltd**

Dower House, Billericay Road  
Herongate, Brentwood  
Essex CM13 3SD  
Telephone: Brentwood (0277) 810244

**INTRODUCTION TO MICROPROCESSORS AND COMPUTING.** 50 pages of diagrams and explanation to get you started. Price £2.30 + 45p postage.  
**EDUCATIONAL DATA AND TECHNICAL SERVICES**  
59 Station Road, Cogenhoe, Northampton NN7 1LU

**HEWLETT PACKARD HP97**, advanced card programmer scientific calculator with thermal printer and application pack, £300. HP65 advanced card programmable scientific calculator with 3 application packs and spare charger, £100. Ring: Daytime 01-553 7094, evening 01-531 0716, ask for Mr. Yelland.

**PRECISION SHEET METAL** work chassis, panels, etc. Steel, stainless or aluminium, long/short runs, good deliveries. E.E.S. Limited, Clifford Road, off Monks Road, Exeter 36489. Telex: 42401.

## SUPERBOARD II AVAILABLE NOW AT £263.35

### LOOK!

**SPECIAL OFFER.** Limited quantity. **MARKSMAN** electronic game. Consists of a Pistol and an Owl target. Shoot the owl dead centre and it responds with flashing eyes and a chirping noise.

Sells in shops for £10-£14

Now Only **£5.90**

**SPACE ALERT** ONLY £15.90 EACH



FOOTBALL VERSION £21.50

### NEW PRICE

**CHESS CHAMPION** 6-Level Chess Computer. **New Low Price £63.95**, with adaptor.

**STAR CHESS** colour TV Game. A space age Chess game.

**£69.95** Our Price **£63.35**, with adaptor.

### SAVE £3

**ELECTRONIC MASTERMIND**

Play nine games against the computer, 3, 4

or 5 digits. **£15.85** Now **£12.85**.

**CHROMA-CHIME** 24-tune door chimes. **KIT £10.50. BUILT £15.30.**

### LOOK!!!

**5-pin DIN to 4 x 3.5mm JACK PLUGS.**

Leads can be used for Audio by replacing Jack Plugs with Phono plugs or use it with your computer by changing DIN plug to Phono plugs.


**ONLY £1.25.**

All prices inclusive - P & P free

**N.I.C. MODELS**

27 Sidney Road, London N22 4LT  
01-889-9736

Please allow up to 21 days for delivery

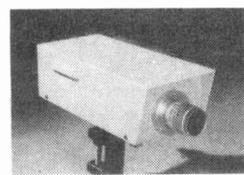

## CCTV CAMERA

**£114.99** + P/P £3.45  
Optional extra manual  
£6 Total £124.44

**BEST OFFER EVER**  
Camera Kit, Lens,  
Vidicon & Modulator

**CROFTON**

Tel: 01-891 1923 For full details

# Road Runner

## ROADRUNNER WIRE THREADING SYSTEM

Introkit £9.88, Wiring Pencil with full Bobbin £2.44, Distribution Strips glue fix 20/pkt. 6" long £2.80 pkt., press fix 20/pkt. 2" long fit Vero/RS Bds. £2.92 pkt., Bobbins of "Q.S.E." wire 4 of 1 col./pkt. green, blue, copper, pink £2.12 pkt.

**SPECIAL OFFER:** Oryx 50 temp. cont. iron & stand £12.50 (rec. price £13.25), Microshear Cutters £3.15 pair, Conductive Paint £2.35, DIL Breadboards + & Gnd. Bus, 20 Ic Posns, Decouplers, C-Fingers £1.50 ea.

Prices include P&P. Please add 15% VAT.

**T. J. Brine Associates**  
Blackdown Rural Inds.  
Haste Hill  
Haslemere, Surrey

## PRINTED CIRCUITS and HARDWARE

Comprehensive range Constructors Hardware and accessories

Selected range of popular components  
Full range of HE printed circuit boards normally ex-stock, same day despatch at competitive prices  
P.C. Boards to individual designs  
Resist-coated epoxy glass laminate for the d.i.y. man with full processing instructions (no unusual chemicals required)

Alfac range of etch resist transfers and other drawing materials for p.c. boards

Send 15p for catalogue.

**RAMAR CONSTRUCTOR  
SERVICES**  
Masons Road  
Stratford-on-Avon  
Warwicks. Tel. 4879

## INTENSIVE WEEKEND COURSES IN BASIC

including hands-on mini computer operation.

This short intensive course is intended to instruct from minimal knowledge to an operational capability of computer programming in BASIC high level language. The course is fully residential from Friday evening to Sunday afternoon. Option of non-residential weekend, weekday evening and weekday courses available if required.

For further details of dates available, fees, etc.:

Phone (0401) 43139, or write to  
Dept. ETI

**CLEVELAND BUSINESS SERVICES**  
Cleveland House, ROUTH  
Beverly, North Humberside

**LOW PROFILE DIL SOCKETS** 8pin-10p, 14pin-12p, 16pin-13p, 18pin-18p, 20pin-20p, 22pin-22p, 24pin-24p, 28pin-28p, 36pin-36p, 40pin-40p, OPTO/7 seg DISPLAYS led 2" 10p, .125" 10p, FND 500 .5" CC, 95p, DL707, 95p DL701, 95p fullsize 19 keypad HEX + CONTROL £12.00. 7447 80p. SOUND GENERATOR SN6477 £3.95 include 30p p&p. J. Towns, 12 Hilltop Cl., Baglan, Pt. Talbot, W. Glam.

**\*SCMP USERS!** 2708 programmer kit, all components; MK14 driving software (easily convertible to other systems); suitable power supply circuit, £9.99 incl. R. J. Hamilton, 32 Shandon Crescent, Balloch, Dunbartonshire, G83 8EX.

**CIRCUIT DESIGN,** Prototype construction, Analogue or Digital, Single Circuits or Complete Instruments/Systems. Write A. J. ATTWOOD, C.Eng., MIERE, Heathercote, Heatherton Park, Taunton, Somerset, TA4 1ET or Phone Bradford-on-Tone (082-346) 536.

**T159.** 6 months old, always used in plastic bag hence mint condition. Need quick sale — only £135 ono, ie £35 below discount price. Phone 03745 55900.

**DESPERATE** S/c furn/semi furn two single bedroomed flat wanted in London from 1st Oct. for two females on ETI staff. If you can help please write to Box No. SL1, ETI, 145, Charing Cross Road, London WC2H 0EE.

**FASCIA PANELS, DIALS, NAME-PLATES, ETC.** in metal or plastic, any quantity, including one-off. Fast delivery. Send 50p (redeemable against first order) plus sae for samples to: Dept. JY159, Lee-Stretton Artworks, 99 St. Leonard's Road, Windsor, Berkshire.

**E.T.I.** January 1975 to December 1978 inclusive. Sensible offer. Avo 8 Mark II recently serviced. £45. TE20D Signal Generator, hardly used, £30. Telephone Ely 2371, ext. 372.

## VIDEO MUSIC



Videograph II links to the aerial socket of your tv and provides a full colour GIANT oscilloscope display. A must for hi-fi, home entertainment, discos, organs etc.


**New** — signal invert control, integral square wave generator. **Plus** — full details for testing your audio system for transient distortion, crosstalk etc.

**Complete Kit only £26.95** **Luxury cabinet and controls. £12.95**

READY BUILT UNIT £49.95 + £1.00 P&P

**WILLIAM STUART SYSTEMS Ltd**  
Dower House, Billerica Road  
Herongate, Brentwood  
Essex, CM13 3SD  
Telephone: Brentwood (0277) 810244

## ORGANISE YOUR COMPONENTS!

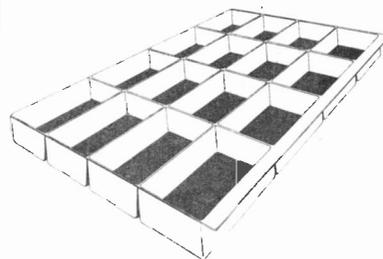

### COMTRAYS

Store resistors, capacitors, IC's, screws, etc. Ideal for organising your project components — saves all that searching around while constructing. Plastic trays with 16 compartments, each compartment 3/4 x 2/4 x 1 1/2 ins. deep.

£1.90 each, including p.p. and VAT  
Four for £6.95 (64 compartments)  
Eight for £12.60 (126 compartments)

Cheque or P.O. to:

**HELISTAR SYSTEMS LTD.**  
150 WESTON ROAD  
ASTON CLINTON  
AYLESBURY, BUCKS HP22 5EP  
Tel. Aylesbury 630364

## S50 BUS

32k dynamic RAM kit to fit into a single S50 Bus slot.

Give your SWTPC system a chance to handle some really big programs.

16k kit **£130.**

32k kit **£200** plus VAT and p&p.

S.A.E. for leaflet of these kits plus our range of 6800 computer kits starting at £130.

### HEWART MICROELECTRICS

95 Blakelow Road  
Macclesfield, Cheshire

## ETI P.C.B.'s

Buy it with Access  
BARCLAYCARD

Available for most ETI projects from day one of ETI, phone your order.

**SPECIAL OFFER** — Single sided Pax PCB mat, four off, 4 3/4" x 6 1/2", 99p all up

## CROFTON ELECTRONICS LIMITED

35 GROSVENOR ROAD, TWICKENHAM  
MIDDLESEX TW1 4AD · Tel: 01-891 1923

## THIS SECTION IS A PRE-PAYMENT SERVICE ONLY

**THERE will be a rate increase for Mini-Ads and Classifieds as from the November issue. Please call for new rates and any other enquiries to: Steve Rowe, Advertisement Dept. 01-437 1002/5 145 Charing Cross Road, London WC2H 0EE.**

### Electronic kits for the thrifty!

Build 50 Interesting Projects on a P.C. Chassis with surplus components from your "Spares-Box."

## EXPERIMENTER'S PRINTED CIRCUIT KIT

Contents: 4 small boards to suit the enclosed designs. Etching Powder, Resist Paint, Solvent, Degreaser and Etching Instructions; also 50 Circuit diagrams, Chassis Plans and Layouts for simple Crystal Sets, Transistor Radios, Transmitters, Amplifiers, Intercoms, Radio Control, Metal Detector, Photoelectric and Ultrasonic Alarms, "Perpetual Motions", Light-Beam Telephone Instruments, Testers, Gadgets, etc., you can build at negligible cost with "Surplus" or reclaimed parts and transistors you already have.

Price: £1.70. Postage and Packing 30p.

## PHOTOELECTRIC KIT

A kit of basic parts to build a simple I.R.-sensitive Photoelectric Switch. Contents: Phototransistor, Transistors, Diode Resistors, Connector, Latching Relay, Chassis Board, Case, Screws and full instructions.

Price: £4.50. Postage and Packing 50p.

## OPTICAL KIT

A kit of parts to build an I.R. folded-beam Projector and Receiver to suit the above kit. Contents: 2 Lenses, 2 Mirrors, 2 45-deg. blocks, Infra-Red Filter, Lampholder, Building Plans. Price: £3.70. Postage and Packing 30p. Both kits together make an Invisible-Beam Alarm.

### EXPERIMENTAL ELECTRONICS 335 Battersea Park Road, London SW11 4SL

Send SAE for full details of all kits and circuits

741 B pin di1 TO5 can 14p (13p 10+), MC 1458 35p, LM 3900 38p, IN4004/4005 3 1/2p, IN4007 4 1/2p, IN4148 2p, WO4 1.5A bridge 30p, BC107/8/9 BC147, 14B, 15B, 182 7p, 2N 3055 35p, OC71 15p. Resistors 1/2w 5%, E12 100 1p, 10 + 1 value 0.9 polyester caps 0.01-0.1µF 2p, 0.15, 0.22 3p, 0.33, 0.47 5p, 0.68 7p, 1.0 10p, 2.2 14p. Electrolytic 25v 2-64µF 4p, 100-160 6p, 220-500 8p, 1000 14p, 6800 55p.

## PROTON ELECTRONICS

1A, 2 & 4 STOPES ROAD  
RADCLIFFE, MANCHESTER M26 0TN

### VMOS POWERFETS

(with free data and ideas sheet)  
VN67AF (60v, 2A, 15W, TO202) ..... 85p  
VN10KM (60v, 1/2A, 1W, TO92 + tab) ..... 60p  
(plus 10p for 20% lower  $R_{on}$  max. selection)  
TO202 Heat Clip (4W diss. with VN67AF) ..... 12p  
TO92 Heat Clip (2W diss. with VN10KM) ..... 8p  
VMOS Design Catalog (96 page) ..... 45p

### INTEGRATED CIRCUITS

CA3080 (Programmable OTA) ..... 70p  
CA3140 (MOS opamp, drives TTL) ..... 38p  
LM308 (Precision opamp, 7nA max. bias) ..... 25p  
LM 733 (100 MHz diff. amp) ..... 50p  
LM741 (Famous, cheap opamp) ..... 18p  
LM78L05ACZ (5% accuracy, TO90, 5v reg.) ..... 29p  
LM3900 (Cheap, quad opamp substitute) ..... 43p  
MC3401 (Cheaper ditto!) ..... 30p  
TL081CP (FET opamp, 13v/µS SR) ..... 29p  
TL074CN (Quad TL081 + 10 noise) ..... 120p  
709C (TO5 opamp, 12v/µS decompensated) ..... 15p  
4001B (P25nS) ..... 14p  
4007UB (PnS) ..... 14p  
4011B (P25nS) ..... 14p  
4013B (P25MHz) ..... 28p  
4016B (BW 90MHz) ..... 33p  
4017B (P16MHz) ..... 55p  
4020B (P16MHz) ..... 55p  
4020B (P20MHz) ..... 70p  
4069UB (P20nS) ..... 14p  
LOC MOS figures are typical @  $V_{DD} = 10v$ .  
FET (near equiv. 2N3823, lo noise, RF) ..... 14p  
SCR (3A, 400v thyristor in TO66) case) ..... 40p

All offers subject to availability

P&P 20p Mail order only

## J. W. RIMMER

367 GREEN LANES, LONDON N4 1DY

## COLOUR MODULATOR

Kit **£9.95** FOR ALL TV GRAPHICS!

Red, Green, Blue inputs (can be mixed)  
Available now Nascom Colour Kit  
£45.00 inc. Graphics Software

### WILLIAM STUART SYSTEMS

Dover House, Billericay Road, Herongate, Brentwood, Essex  
CM13 3SD Tel (0277) 810244  
Barclaycard / Access welcome

## SECURITY PRODUCTS

Designed for the Do-It-Yourself market. Easily installed. Full instructions supplied. As supplied to the trade.

Magnet and Reed Switch ..... Flush £1.00  
Surface £1.00  
Pressure Mats ..... Large £2.50  
Stair £1.75  
6" Heavy Duty Bells ..... £11.50  
Sirens 12v 84dB @ 10' ..... £7.50  
Bell Covers ..... £8.50  
Window Foil Self-Adhesive ..... £3.20  
Foil Blocks ..... 20p  
Door Loops, complete ..... £1.00  
Key Switches, top grade ..... £4.50  
Control Panels from ..... £32.00  
Radar, Infra-Red, and many other items available. Price list supplied free

Please note that our prices now INCLUDE VAT at 15% + P&P


## SECURITY CATALOGUE

Giving details of current professional alarm techniques — £1 (refundable on orders over £10)

Access and Barclaycard Sales welcome  
We also sell Nascom 1
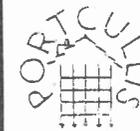
### STRATHAND SECURITY

44 St. Andrew's Sq., Glasgow G1 5PL  
041-552 6731 or 2



## SECURITY

ALL THE EQUIPMENT  
NECESSARY FOR THE DIY AND  
PROFESSIONAL BURGLAR  
ALARM INSTALLER. LARGE  
SAE FOR CATALOGUE

PORTCULLIS  
7 PARK HILL, TODDINGTON, BEDS.  
TEL TODDINGTON 2098

# ADVERTISEMENT INDEX

A J D Direct Supplies ..... 89  
Ambit ..... 83  
Arak ..... 102  
Audio Electronics ..... 46  
Baydis ..... 73  
Bi-Pak ..... 22  
Bi Pre-Pak ..... 89  
B K Electronics ..... 32  
B.N.R.S. .... 26  
Calculator Sales and Service ..... 82  
Cambridge Learning ..... 34  
Carston Electronics ..... 91  
Chiltmead ..... 78  
Chromasonics ..... 40  
Clef Products ..... 78  
Codespeed ..... 96  
Comp. Comp, Comp .. 106 & 107  
Crimson Elektrik ..... 90  
Crofton ..... 78  
C.S.C. .... 21  
Delta Tech ..... 32  
E.D.A. .... 46

Electrovalve ..... 73  
GMT Electronics ..... 4 & 5  
Greenbank ..... 66  
Henrys ..... 92  
ILP ..... 50  
Integrated Circuits ..... 99  
Kode Services ..... 92  
Kramer ..... 26, 82 & 96  
LB Electronics ..... 66  
L + B Electronics ..... 40  
Lotus Sound ..... 96  
Maclin-Zand ..... 13  
Maplin ..... 108  
Meprocst ..... 32  
Metac ..... 54  
Microdigital ..... 84  
Marshalls ..... 44  
Minikits ..... 82  
Monolith ..... 84  
Mountaineer ..... 82  
Nicholls ..... 84  
NIC Models ..... 103

Powell ..... 40  
Powertran Electronics ... 2 & 8  
Powertran Computers ..... 97  
Progressive Radio ..... 90  
Roger Squires ..... 26  
Romane Electronics ..... 102  
R.T.V.C. .... 98  
Scopex ..... 77  
Service Trading ..... 74  
Sintel ..... 43  
Stevensons ..... 6  
Swanley ..... 26  
Tandy ..... 12  
Tech. Book Service ..... 92  
Technomatic ..... 14  
Teleradio ..... 84  
Tempus ..... 94  
T K Electronics ..... 89  
Transam ..... 33  
Watsford ..... 10 & 11  
Wilmslow ..... 102

## TRS80 EXPANSION INTERFACE


Upgrade your system as your needs increase. Contains sockets for additional 16K or 32K RAM and a disk controller for up to 4-mini-disks. Software selectable dual cassettes can be used. Features a Centronics parallel port, real time clock, and a connector for an RS-232C interface or whatever. Requires Level-II Basic. 220/240V AC.

Complete with 32K RAM £299 + VAT



## ANADEX DP8000


ONLY £540 + VAT  
PET Connector — £49

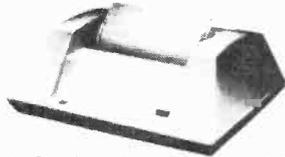

The DP 8000 prints the 96-character ASCII set in single or double width at 84 lines per minute. • The unit operates bi-directionally to print a 9 x 7 matrix on multiple copy, pin-feed plain paper. • This model accepts RS-232C or current loop serial data at baud rates switchable from 110 to 9600 and Parallel Bit data input at over 1000 characters per second.

• Standard storage capacity of 256 characters • Other features include Out of Paper Detector, Top of Form Programming and Skip Over Perforation Control.

## THE NEW ITT APPLE (2020)

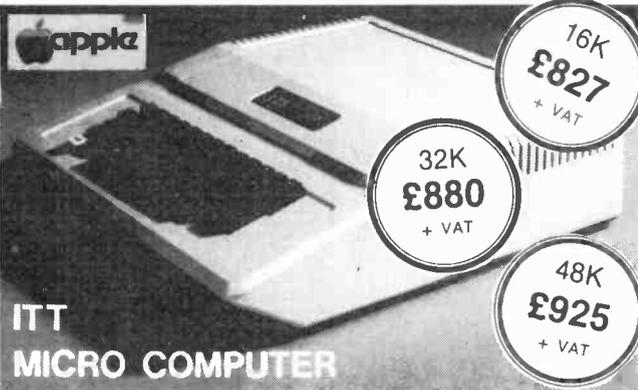

ITT  
MICRO COMPUTER

★ Full colour — UHF output ★ Audio cassette tape interface ★ Up to 48K RAM on board ★ BASIC in ROM (graphics commands include COLOUR = VLIN, HLIN, PLOT and SCRIN) ★ Built in loudspeaker ★ Buckets of software available ★ Disk System (110K byte per drive — includes controller) only £425 + VAT **EX-STOCK**

## THE TRS80 (Special Scoop) Low Priced, Ready to Go!



16K  
£399  
+ VAT

EXTENDED WARRANTY BY COMPUCARE

PLUGS INTO YOUR OWN TV  
Use your own cassette

LEVEL II BASIC WITH 16K USER RAM provides you with possibly the most powerful micro around. All our TRS80s are fully converted to English Television Standard and include a U.K. Power Supply, Cassette Leads, Sample Tape, Level I & Level II programming manuals, and special lead that enables you to connect direct into your own television.

Special features of Level II Basic enable you to: — Set or reset any point on the screen — Test for the presence of a point on the screen (these features enable easy animation) — Save or load data from cassette under program control — File handling capabilities on cassette using named files. — Graphics blocks as standard — design your own pictures and many many more features for only £399 + VAT

## PET COSTS LESS AT COMP and it's a pedigree

8K — Comes complete with integral cassette deck. Full manuals supplied. Powerful 8K Microsoft Basic in ROM. Masses of software available — £499 + VAT

16K — Same as above but with new improved keyboard and cassette supplied as extra. Machine code monitor on board so you can program in 6502 machine code — £590 + VAT

32K — for a little extra get 32K memory providing greater storage capacity for programs or data — £690 + VAT

External Cassette deck for 8K, 16K or 32K — £55 + VAT complete with cable and connector.



EXTENDED WARRANTY BY COMPUCARE

## HITACHI PROFESSIONAL MONITORS



9" — £129 + VAT  
12" — £199 + VAT

- Reliability Solid state circuitry using an IC and silicon transistors ensures high reliability.
- 500 lines horizontal resolution Horizontal resolution in excess of 500 lines is achieved at picture center.
- Stable picture Even played back pictures of VTR can be displayed without jittering.

- Looping video input Video input can be looped through with built-in termination switch.
- External sync operation (available as option for U and C types)
- Compact construction Two monitors are mountable side by side in a standard 19-inch rack.

## video 100

12" BLACK & WHITE  
LOW COST VIDEO  
MONITOR



- Ideal for home, personal and business computer systems
- 12" diagonal video monitor
- Composite video input
- Compatible with many computer systems
- Solid-state circuitry for a stable & sharp picture
- Video bandwidth - 12MHz + 3DB
- Input impedance - 75 Ohms
- Resolution - 650 lines Minimum In Central 80% of CRT, 550 Lines Minimum beyond central 80%.

Only £79 + VAT

## SORCERER SPEAKS YOUR LANGUAGE

For personal or business use. The best value for money around.

- ★ 512 by 256 point screen resolution ★ 16K or 32K

User RAM ★ Centronics Parallel Port ★ RS232C Serial Port ★ Composite IV peak to peak video output T.V. output supplied as extra. ★ 64 programmable graphics + 64 standard PET graphics ★ 79 key keyboard including 16 key numeric keypad. ★ Expansion bus for connection to S100 Expansion Box.

16K Sorcerer — £690.00 + VAT  
32K Sorcerer — £790.00 + VAT  
S100 Expansion Box — £210 + VAT

Word Processing Pac and Development Pac now available.  
Word Processing Pac — £70  
Development Pac — £70



EXTENDED WARRANTY BY COMPUCARE

## Break the language barrier £138



At a price equivalent to learning one language, LEXICON offers you, English, Spanish, French, German, Italian and Greek. The LK3000 comes to you with the person to person module which contains 6 languages, de-luxe carrying case and a charger adaptor using its own power source which will give you 4-5 hours continuous use, and can easily be re-charged from the mains supply, wherever you may be in the world. Every additional module carries a concise and understandable instruction book. Your deluxe carrying case has room for two additional modules.

ONLY £138 + VAT

## COMPUCARE

(Part of the Compshop Ltd. Group)

Compucare is a company that has been set up to provide servicing and maintenance for the popular makes of micro-computers i.e. Sorcerer, Pet, Apple, TRS80, Nascom, CompuKit.

Our charges are £7 per hour plus parts.

Because of the extensive range of spare parts stocked you can usually expect your micro to be repaired within 10 days for an average charge of £14 labour.

Emergency 24 hour repairs can be handled for a £10 surcharge where possible.

CompuKits and Nascoms unsuccessfully constructed will be charged a standard £25.

Maintenance contracts for these machines are available, see your local dealer for a Compucare Maintenance Application Form.

Please add VAT to all prices — Delivery at cost, will be advised at time of purchase. Please make cheques and postal orders payable to COMP, or phone your order quoting BARCLAYCARD, ACCESS, DINERS CLUB or AMERICAN EXPRESS number. **OPEN — 10am to 7pm — Monday to Saturday CREDIT FACILITIES ARRANGED**



JUST COMPARE OUR CASH AND CARRY PRICES!

SEND LARGE S.A.E. FOR OUR FREE '79 CATALOGUE

AS SEEN IN  
P.E. AUGUST, SEPTEMBER  
OCTOBER 1979

EUROPE'S FASTEST SELLING ONE BOARD COMPUTER —  
JUST CHECK THE SPEC'S.

# COMPUKIT UK101

SAMPLE TAPE  
WITH EXTENDED  
MACHINE CODE MONITOR  
AND DISSASSEMBLER  
INCLUDED FREE

## LOW COST SUPERBOARD IN KIT FORM

The CompuKIT UK101 has everything a one board 'superboard' should have.

- \* Uses ultra-powerful 6502 microprocessor
- \* 50Hz Frame refresh for steady clear picture (U.S.A. products with 60Hz frame refresh always results in jittery displays)
- \* 48 chars by 16 lines — 1K memory mapped video system providing high speed access to screen display enabling animated games and graphs
- \* Extensive 256 character set which includes full upper and lower case alphanumerics, Greek symbols for mathematical constants and numerous graphic characters enabling you to form almost any shape you desire anywhere on the screen
- \* Video output and UHF Highgrade modulator (8MHz Bandwidth) which connects direct to the aerial socket of your T.V. Channel 36 UHF
- \* Fully stabilised 5V power supply including transformer on board
- \* Standard KANSAS city tape interface providing high reliability program storage — use on any standard domestic tape or cassette recorder
- \* 4K user RAM expandable to 8K on board £49 extra
- \* 40 line expansion interface socket on board for attachment of extender card containing 24K RAM and disk controller (Ohio Scientific compatible)
- \* 6502 machine code accessible through powerful 2K machine code monitor on board
- \* High quality thru plated PCB with all I.C.'s mounted on sockets
- \* Professional 52 Key keyboard in 3 colours — software polled meaning that all debouncing and key decoding done in software



Simple Soldering due to clear and concise instructions compiled by Dr. A.A. Berk, BSc.PhD

NO EXTRAS NEEDED JUST HIT 'RETURN' AND GO.

Build, understand, and program your own computer for only a small outlay.

KIT ONLY **£219** + VAT including RF Modulator & Power supply.  
**Absolutely no extras.**

Available ready assembled and tested, ready to go for **£269** + VAT

**COMMANDS**  
CONT LIST NEW NULL RUN  
**STATEMENTS**  
CLEAR DATA DEF DIM END FOR  
GOTO GOSUB IF GOTO IF THEN INPUT LET  
NEXT ON GOTO ON GOSUB POKE PRINT READ  
REM RESTORE RETURN STOP  
**EXPRESSIONS**  
**OPERATORS**  
+ \* / † NOT AND OR >> << >=< RANGE 10<sup>32</sup> 10<sup>10</sup> +32  
**VARIABLES**  
A,B,C...Z and two letter variables  
The above can all be subscripted when used in an array. String variables use above names plus \$ e.g. AS

\*8K Microsoft Basic means conversion to and from Pet, Apple and Sorcerer easy. Many compatible programs already in print.  
**SPECIAL CHARACTERS**  
@ Erases line being typed, then provides carriage return, line feed.  
^ Erases last character typed.  
CR Carriage Return — must be at the end of each line.  
: Separates statements on a line.  
CONTROL/C Execution or printing of a list is interrupted at the end of a line.  
"BREAK IN LINE XXXX" is printed, indicating line number of next statement to be executed or printed.  
CONTROL/O No outputs occur until return made to command mode. If an input statement is encountered, either another CONTROL/O is typed, or an error occurs.  
? Equivalent to PRINT

**FUNCTIONS**  
ABS(X) ATN(X) COS(X) EXP(X)  
LOG(X) PEEK(I) POS(I) RND(X)  
SPC(I) SOR(X) TAB(I) TAN(X)  
FRE(X) INT(X)  
SGN(X) SIN(X)  
USR(I)  
**STRING FUNCTIONS**  
ASC(X\$) CHR\$(I) FRE(X\$) LEFT\$(X\$,I)  
RIGHT\$(X\$,I) STR\$(X)  
LEN(X\$) MID\$(X\$,I,J)  
VAL(X\$)

### EXTRAS AVAILABLE SOON

**COLOUR ADD-ON** enables you to choose your foreground and background colour anywhere on the screen. Flash any character on the screen at will. Full documentation and parts in kit form.

**AD-A-RAM EXTENDER CARD** provides up to 32K Dynamic RAM Expansion, 8 Eprom sockets for 2708's or 2716's. Parallel Port (centronics compatible) and an RS232C serial port.

## WIN YOURSELF AN ANADIX DP8000 LINE PRINTER

There's never enough good software around. That's why COMPUKIT LTD. are sponsoring a software contest. There are 2 categories:

- 1) **Business and Education**
- 2) **Fun and Games**

One lineprinter will be awarded to the winner of each category. Send or bring along to the address shown below the following:

- 1) The program on cassette in the format used by the COMPUKIT UK101
- 2) Any documentation that you have for the program (source listing not necessary)
- 3) This coupon signed by you accepting the rules and conditions of the competition.

**RULES:**

- 1) Entries, including documentation, must be printed by computer or typed double spaced, with your name on every page.
- 2) Send or bring your entries to the address shown below.
- 3) Entries must be received by midnight on 29/2/80, any received after this time are void.

Winners will be notified by post before 31/3/80.

4) You warrant by your signature that all programs and documentation material included is entirely your own creation, and that no rights to it have been given or sold to any other party, and you agree to allow COMPUKIT LTD. to use, publish, distribute, modify, and edit it as it sees fit.

- 5) All entries become the property of COMPUKIT LTD. No entries will be returned nor any questions answered regarding individual entries.
- 6) Judging will be by a selected panel chosen by, and including representatives of COMPUKIT LTD. Judges may assign programs to any of the categories as they see fit. Decision of the judges is final.
- 7) Employees of COMPUKIT LTD, its dealers, distributors, advertising agencies and media are not eligible to enter.

Name \_\_\_\_\_

Address \_\_\_\_\_

I agree to abide by the above mentioned rules.

Signature \_\_\_\_\_

**COMP** COMPUTER COMPONENTS

14 STATION ROAD, NEW BARNET, HERTFORDSHIRE TEL: 01-441 2922 (Sales)  
CLOSE TO NEW BARNET BR STATION — MOORGATE LINE 01-449 6596  
OPEN — 10am to 7pm — Monday to Saturday TELEX: 298755



All Products Ex-Stock Please check availability

(Part of the Compshop Ltd Group)

# MAPLIN



This superb organ – build the first working section for just over £100. Full specification in our catalogue.




Touch operated rhythm generator, the 'Drumsette'. Construction details 25p. (Leaflet MES49). Specification in our catalogue.



Multimeters, analogue and digital, frequency counter, oscilloscopes, and lots, lots more at excellent prices. See cat. pages 106 and 183 to 188 for details.



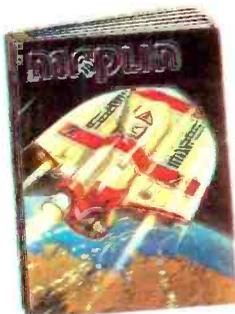61-note touch-sensitive piano to build yourself. Full specification in our catalogue.



A massive new catalogue from Maplin that's even bigger and better than before. If you ever buy electronic components, this is the one catalogue you must not be without. Over 280 pages – some in full colour – it's a comprehensive guide to electronic components with hundreds of photographs and illustrations and page after page of invaluable data.

Our bi-monthly newsletter contains guaranteed price, special offers and all the latest news from Maplin.



A range of highly attractive knobs is described in our catalogue. Our prices are very attractive too!



The 3800 synthesiser build it yourself at a fraction of the cost of one ready-made with this specification. Full details in our catalogue.



A pulse width train controller for smooth slow running plus inertia braking and acceleration. Full construction details in our catalogue.



Speakers from 1½ inch to 15 inch; megaphone, PA horns, crossovers etc. They're all in our catalogue. Send the coupon now!

Post this coupon now for your copy of our 1979-80 catalogue price 70p.

Please send me a copy of your 280 page catalogue. I enclose 70p (plus 37p p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the U.K. send £1.35 or ten International Reply Coupons. I enclose £1.07.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

ETI 10 79



A wide range of disco accessories at marvellous prices. Our catalogue has all the details.



A very high quality 40W per channel stereo amplifier with a superb specification and lots of extras. Full construction details in our catalogue.



A genuine 150W per channel stereo disco to build yourself. Full specification in our catalogue.

# MAPLIN

ELECTRONIC SUPPLIES LTD

All mail to:—  
 P.O. Box 3, Rayleigh, Essex SS6 8LR.  
 Telephone: Southend (0702) 554155.  
 Shop: 284 London Road, Westcliff-on-Sea, Essex.  
 (Closed on Monday).  
 Telephone: Southend (0702) 554000.